

Hobby

DECEMBER 1982

75p

Electronics

Project Electronics For Everyone

PROJECT SPECIAL

Ten Top Projects To Build For Christmas!



**Points Of View • Buylines
Famous Names • Radio Rules
Book Service**

**POPULAR
COMPUTING**
Components For
Computing
New Series!

You should see Ambit's new Autumn Catalogue...

IT SPEAKS FOR ITSELF

Another milestone in component supply...

If you've been wondering just what's been going on at Ambit lately, we are now taking the wraps off the most advanced and imaginative concept in component, tool, and information distribution since we launched WR&E last year.

We have included new items and information to plug a few gaps, and we are just starting to implement a new interactive computerised system of service and information that simply cannot be overlooked by anyone interested in the communications, electronics, video and computing business.

- ★ Price on the page
- ★ 24 Hour response -Guaranteed
- ★ Low prices
- ★ High quality
- ★ Export a speciality

No. 4, Autumn 1982

AMBIT INTERNATIONAL'S

WORLD of RADIO & ELECTRONICS

CONCISE PARTS CATALOGUE

128 PAGES

70 p

Some of the new items from this issue...

Weller/Cooper: Soldering Irons & Tools

You never regret buying the best!

- ★ TCP series
- ★ Tips & spares
- ★ Cutters/pliers
- ★ Toolkits

Motorola RF Power: Transformers for transmitting

- ★ 1W/30MHz to
- ★ 80W/150MHz
- ★ ..& beyond

Test equipment

A rapidly expanding range

- ★ Auto DMMs
- ★ 'Scopes
- ★ Bananas (?)
- ★ Sig gens

TOKO inductors

RM assemblies

Intelligent LCDs

Uni Crystal Filters

Coaxial relays

Micros & memories

Linears

Keyswitches

Panelware

Hardware

WR&E

LOWEST PRICE FULL SPEC ICADS 3 x 21 vouchers inside

128 Pages of the broadest component range in the business

24 HOURS A DAY, 7 DAYS A WEEK

AUTUMN '82 WR&E 70p

AT YOUR NEWSAGENT - OR DIRECT FROM

AMBIT INTERNATIONAL BRENTWOOD ESSEX CM14 4SG

Telephone (0277)230909, telex 995194 AMBITG, data RS232/300 baud (0277)230959*

- *Dial (0277)230959, hook in your low cost modem and terminal (most personal computers can be configured to access REWTEL, details are being published in R&EW over the next few months) and REWTEL will give you access to up to 5000 pages of background to the WR&E catalogue, equivalents, news, updates, hot off-the-press product news, information, jobs being advertised in the industry. It's computing at its most versatile and worthwhile: why be satisfied with a 64K MCU, when you can gain free access to the 70MByte+ of the REWTEL computer ??

Hobby Electronics

DECEMBER 1982
Vol 4 No 12

PROJECTS



- ★ HE MICROLOG 9
The analog computer strikes back.
- ★ STEREO NOISE GATE 20
Taking the hiss out of audio.
- ★ HE TV AMP 25
Clearer sound for the slightly deaf.
- ★ PHASE FOUR 37
A four stage audio phaser.
- ★ POP AMPS No. 1 52
A single op-amp microammeter.
- ★ SLIDE-TAPE SYNCHRONISER 56
Audio visuals with added bleep.
- ★ POP AMPS No 2 62
Voltage follow-and-hold for meters.
- ★ LOW COST ALARM 70
A security alarm that won't cost everything you've got.
- ★ HE LOFTY 74
Don't hide your loft lights — turn them off!
- ★ THE BIG EAR 80
An electronic eavsdropper for nature lovers.

FEATURES

- FAMOUS NAMES 33
J.M.E. Baudot.
- RADIO RULES 43
Single sideband.
- ★ COMPONENTS FOR COMPUTING 46
Part 1 gets into (and out of) I/O Ports.
- HC6010 DMM 65
Digital multimeter reviewed.

- Monitor 6
- What's On Next 18
- Points of View 31
- Buylines 34
- Clever Dick 51
- HE Book Service 46
- HE Backnumbers 74
- PCB Service 63
- PCB Printout 65
- Classified Advertisements 81

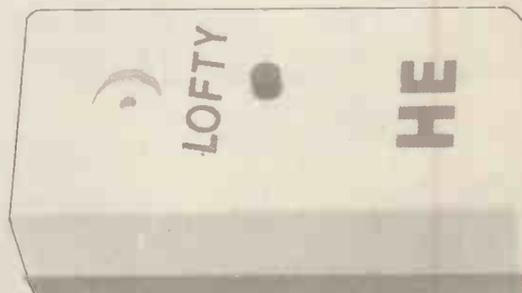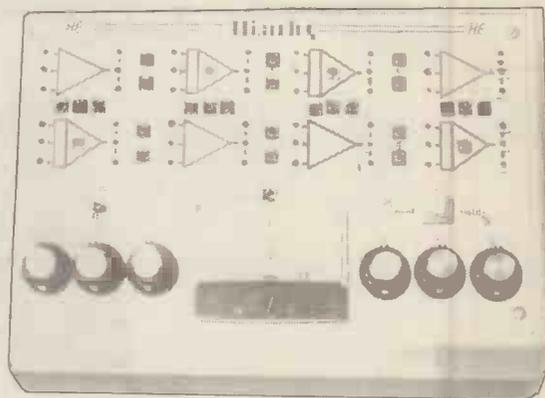Editor: Ron Keeley
 Editorial Assistant: Helen Armstrong
 Advertisement Manager: Gary Price
 Assistant Advert. Manager: Jolyn Nice
 Managing Editor: Ron Harris BSc
 Managing Director: T.J. Connell



Hobby Electronics is normally published on the second Friday of the month prior to the cover date.
 Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002. Telex No 8811896. Published by Argus Specialist Publications Ltd.
 Design and Organisation by MM Design and Print Ltd, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002.
 Distributed by S. M. Distribution Ltd, 16/18 Trinity Gardens, London SW9 8DX.
 Printed by QB Ltd, Colchester. Covers printed by Alabaster Passmore.

Notice: The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. All reasonable care is taken in the preparation of the magazine to ensure accuracy, but Argus Specialist Publications Ltd cannot be held responsible legally. ©Copyright 1982 Argus Specialist Publications Ltd. Member of Audit Bureau of Circulation.



Multicore makes soldering easy fast & reliable

Ersin Multicore

Ersin Multicore, solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required. Comes in handy dispensers and tool box reels in two different alloys 40/60 tin/lead for general purpose electrical soldering and 60/40 tin/lead ideal for small components and fine wire soldering.



Size PC115 60/40 tin/lead
£1.38 Handy pack 0.028mm dia



Size 3 40/60 tin/lead
£4.37 Per reel 1.6mm dia



Size 10 60/40 tin/lead
£4.37 Per reel 0.71mm dia



Size 19A 60/40 tin/lead
£1.15 Handy pack 1.22mm dia

Multicore Savbit

Multicore Savbit, solder increases the life of your soldering bit by 10 times, for better soldering efficiency and economy. Comes in two handy dispensers and tool box reels.



Size 5 Savbit
£1.15 Per pack 1.2mm dia



Size 12 Savbit
£4.37 Per reel 1.2mm dia



Size SV130 Savbit
£1.73 Per pack 0.048mm dia

Multicore Alu-Sol

Multicore Alu-Sol, solder contains 4 cores of flux, suitable for most metals especially aluminium. Comes in handy dispensers on tool box reels.

Size AL150 Alu-Sol
£2.07 Per pack 0.048mm dia



Size 4 Alu-Sol
£7.82 Per reel 1.6mm dia



Multicore Solder Wick

Multicore Solder Wick, absorbs solder instantly from tags and printed circuits with the use of a 40 to 50 watt soldering iron. Quick and easy to use, desolders in seconds.

Size AB10 Solder Wick
£1.43 Per pack



Multicore Tip Klean

Multicore Tip Klean, soldering iron tip wiping pad. Replaces wet sponges.



Size 2 Tip Klean
£0.92 Per pack

Bib Wire strippers and cutters

Wire strippers and cutters, with precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles.



Size 9 Wire Strippers
£2.69 Per pair

Bib Audio/Video Products Limited
(Solder Division), Kelsey House,
Wood Lane End, Hemel Hempstead,
Hertfordshire, HP2 4RQ.
Telephone: (0442) 61291
Telex: 826437

All prices inclusive of VAT. Available from most electrical and DIYs stores. If you have difficulty in obtaining any of these products send direct with 50p for postage and packing. For free colour brochure send S.A.E.

WATFORD ELECTRONICS

35c CARDIFF ROAD, WATFORD, HERTS, ENGLAND

MAIL ORDER CALLERS WELCOME, Tel. Watford 40588

ALL DEVICES IN AND NEW FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT ENQUIRY WELCOME. P&P Add 50p TO ALL CASH ORDERS. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. ACCESS ORDERS WELCOME.

VAT

All prices exclusive of VAT. Please add 15% VAT to the total cost incl. P&P. We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest underground/BR Station: Watford High Street. Open Monday to Saturday: 9am to 6pm

POLYESTER CAPACITORS: Axial Lead Type
 400V: 1nF, 1.5n, 2n2, 3n3, 4n7, 6n8 11p, 10n, 15n, 18n, 22n 12p; 33n, 47n, 68n 16p; 100n, 150n 20p; 220n 30p; 330n 42p; 470n 52p; 680n 60p; 1µF 68p; 2µ2 82p; 4µ7 85p.
 160V: 10nF, 12n, 100n 11p; 150n, 220n 17p; 330n, 470n 30p; 680n, 38p; 1µF 42p; 1.5µ 46p; 2µ2 48p.
 1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n 48p; 100n 50p; 150n 50p; 470n 99p.

POLYESTER RADIAL LEAD CAPACITORS: 250V:
 10nF, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p.
 330n, 470n 13p; 680n 19p; 1µF 23p; 1.5µ 40p; 2µ2 46p; 4µ7 60p.

ULTRASONIC TRANSDUCERS
 40kHz 325p/pr

ELECTROLYTIC CAPACITORS: (Values are in µF) 500V: 10 52p; 47 78p; 250V: 100 65p; 63V: 0.47, 1.0, 1.5, 2.2, 2.5, 3.3 8p; 6.8, 10, 10, 15, 22, 33 15p; 47 12p; 100, 15p; 100, 15p; 1000 70p; 50V: 47 7.8 22p; 100 10p; 220 24p; 470 32p; 2200 90p; 40V: 4.7, 1.5, 22p; 3300, 90p; 4700, 120p; 25V: 1.5, 6, 8, 10, 22, 33, 47 8p; 100 12p; 150 12p; 220, 15p; 330 22p; 470 25p; 680, 100p, 34p; 2200, 50p; 4700, 92p; 16V: 40, 47, 100 9p; 125, 12p; 220 13p; 470, 20p; 680 34p; 1000 27p; 1500, 31p; 2200 36p; 3300 74p; 4700 79p.

TANTALUM BEAD CAPACITORS
 35V: 0.1µF, 0.22, 0.33 15p; 0.47, 0.68, 1.0µF, 1.5 18p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10µF 28p; 16V: 2.2, 3.3 16p; 4.7, 6.8, 10 18p; 15, 36p; 22 30p; 33, 47 40p; 100 75p; 220 88p; 10V: 1.5, 22p; 3.3, 47 36p; 100 50p; 6V: 100 42p.

POTENTIOMETERS: Rotary, Carbon, Track, 0.25W Log & 0.5W Lin.
 500Ω, 1KΩ & 2KΩ (Linear only) Single Gang 30p
 5KΩ-2MΩ Single Gang D/P Switch 78p
 5KΩ-2MΩ Double Gang 88p

SLIDER POTENTIOMETERS
 0.25W log and linear values 60mm
 5KΩ-500KΩ single gang 70p
 10KΩ-500KΩ dual gang 110p
 Self Stick graduated Bezel 40p

MYLAR FILM CAPACITORS
 100V: 1nF, 2, 4, 4n7, 10 6p; 15nF, 22n, 30n, 40, 47 7p; 56, 100n, 200 9p; 470n/50V: 12p.

MINIATURE TYPE TRIMMERS
 2.8pF, 2-10pF, 2-25pF, 5-56pF 30p.

COMPRESSION TRIMMERS
 3-40pF; 10-80pF 20p; 20-250pF 28p; 100-580pF 38p; 400-1250pF 48p.

PRESET POTENTIOMETERS
 Vertical & Horizontal
 0.1W 50-M Ω Miniature 7p
 0.25W 100-M Ω 3-3 MΩ horiz. 10p
 0.25W 200-M Ω 4-7 MΩ vert. 10p

VOLTAGE REGULATORS
 1A TO3 +ve 7805 220p
 12V 7812 145p
 15V 7815 145p
 18V 7818 145p

100mA TO92 Plastic Casing
 5V 78L05 30p
 8V 78L08 30p
 9V 78L09 30p
 12V 78L12 30p
 15V 78L15 30p
 18V 78L18 30p

CA3085 95p LM317P 95p
 LM300H 170p LM323K 50p
 LM305H 140p LM337 175p
 LM309K 135p LM723 35p
 LM317K 350p TAA650 78p

DIL SOCKETS
 Low Wire Prof. wrap
 8 way 8p 25p
 14 pin 8p 35p
 16 pin 10p 42p
 18 pin 18p 52p
 20 pin 22p 60p
 22 pin 25p 70p
 24 pin 27p 70p
 28 pin 28p 80p
 40 pin 30p 99p

PROTO DEC
 Euroboard 650
 S Dec 520
 Bimbo I 500
 Veroblock 375

DENCO COILS
 DP VALVE TYPE
 Range 1 to 5 BL, RD, TL, Wh, 122p
 6-7 B-Y-R 110p
 1.5 Green 150p
 "T" type 1 to 5, Bl, Rd, Wh, Y, 150p
 BSA Valve Holder 142p

VERO BOARD
 0.1" Pitch clad plain
 21 x 31" 80p
 21 x 6" 91p
 31 x 3" 91p
 31 x 5" 105p 87p
 31 x 17" 360p 232p
 43 x 17" 470p
 Pkt of 100 pins 50p
 Spot face cutter 135p
 Pin insertion tool 178p

COPPER CLAD BOARDS
 Fiberglass
 6 x 6" 90p
 6 x 12" 150p
 6A/100V 40
 6A/400V 50
 6A/800V 65

S.R.B.P.
 9 x 8 95p
 Ferric Chloride
 1lb Anhyd. 195p

DIODES
 BY127 12
 BY127 12
 OA5 40
 OA47 12
 OA70 12
 OA79 15
 OA85 15
 OA90 8
 OA91 8
 OA95 8
 OA200 8
 OA202 8
 IN4001/2 5
 IN4003 6
 IN4004/5 6
 IN4006/7 7
 IN4148 4
 IN5401 15
 IN5404 16
 IN5408 17
 IS49 15
 IS521 9
 6A/100V 40
 6A/400V 50
 6A/800V 65

ZENERS
 Range 2V7 to 39V 400mW
 Range 3V3 to 33V 1.3W
 15p each

SCRs THYRISTORS
 5A/400V 40
 5A/600V 48
 8A/300V 60
 8A/600V 96
 12A/100V 78
 12A/400V 96
 12A/800V 188
 18A/100V 150
 18A/400V 150
 18A/800V 150
 25A/100V 240
 25A/400V 240
 25A/600V 240
 25A/800V 240

NOISE
 Diode 150p

BRIDGE RECTIFIERS
 1A/50V 18
 1A/100V 20
 1A/400V 25
 1A/600V 34
 2A/50V 36
 2A/200V 40
 2A/400V 45
 2A/600V 46
 6A/100V 83
 6A/400V 95
 6A/600V 125
 10A/200V 215
 10A/600V 298
 25A/200V 326
 25A/400V 326
 BY164 56
 VM18 50

TRIACS
 3A 100V 48
 3A 200V 54
 3A 400V 56
 8A 100V 60
 8A 400V 69
 8A 800V 115
 12A 100V 78
 12A 400V 82
 12A 800V 120
 16A 100V 115
 16A 400V 115
 16A 800V 120
 25A 800V 120
 25A 1000V 480
 25A 28000V 120

DIAC
 ST2 25

7400	11	74150	60	LS124	90	4050	25	AY-1-5051	160	MC1709G	90
7401	11	74151	60	LS125	24	4051	46	AY-3-8910	438	MC1710	79
7402	11	74153	40	LS126	35	4052	60	AY-5-1230	450	MC3302	90
7403	12	74154	50	LS132	85	4053	50	AY-6-1350	360	MC3340P	120
7404	13	74156	40	LS133	30	4054	86	CA3018	86	MC3360P	120
7405	15	74157	28	LS136	28	4055	86	CA3020	210	MC3401	66
7406	15	74158	30	LS138	29	4056	86	CA3025	250	MC3403	66
7407	20	74159	80	LS139	29	4057	1916	CA3035	250	MC68040	75
7408	20	74160	60	LS145	70	4059	435	CA3045	366	MK50398	636
7409	14	74161	48	LS147	100	4060	45	CA3046	70	ML24	276
7410	14	74162	40	LS148	70	4061	1195	CA3048	280	MM5303	636
7411	16	74164	40	LS151	40	4062	985	CA3059	225	MM5307	1275
7412	18	74165	40	LS153	40	4063	85	CA3075	340	MM5387	47
7413	18	74166	48	LS155	30	4066	24	CA3080E	70	NE59	225
7414	20	74168	48	LS157	27	4067	245	CA3081	190	NE531	140
7415	20	74169	150	LS158	30	4068	14	CA3085	95	NE543	225
7416	20	74170	125	LS160	32	4069	13	CA3089E	200	NE544	210
7417	20	74172	250	LS161	37	4070	13	CA3090A	375	NE555	160
7420	15	74173	54	LS162	37	4071	13	CA3123E	150	NE556	46
7421	20	174174	54	LS163	37	4072	13	CA3130	90	NE560	325
7422	20	74175	50	LS164	43	4073	13	CA3140	40	NE561	318
7425	18	74176	40	LS165	50	4075	13	CA3160	95	NE562	410
7426	18	74178	45	LS166	52	4076	50	CA3161	160	NE564	420
7427	18	74179	45	LS167	70	4077	13	CA3189	296	NE565	120
7428	25	74180	40	LS173	55	4078	16	HA1336V	240	NE566	156
7430	14	74181	50	LS174	50	4081	13	ICL106E	750	NE567	140
7432	22	74182	60	LS175	40	4082	13	ICL1710	975	NE570	410
7433	22	74184	90	LS180	90	4085	50	ICL8038CC	300	NE571	480
7437	25	74186	470	LS191	36	4088	125	ICM216A	1950	NE553	150
7438	22	74188	250	LS192	36	4093	20	ICM7224	785	RC4136	69
7439	15	74190	48	LS193	37	4094	70	ICM555	80	RC4136	69
7441	55	74191	46	LS194	33	4095	75	ICM556	150	SAB3209	425
7442	32	74193	45	LS195	33	4096	290	ICM557	250	SAB3210	325
7443	90	74194	45	LS196	45	4096	290	LAB0315	340	SAB3211	485
7444	55	74195	46	LS197	45	4097	190	LA4032	286	SAB4209	585
7445	55	74196	46	LS221	55	4098	75	LA4002	286	SN76013	360
7446	60	74196	46	LS240	55	4099	190	LC7120	300	SN76023	360
7447	35	74197	84	LS241	55	4160	75	LC7130	340	SN76477	420
7448	40	74199	84	LS244	55	4161	75	LC7137	385	SN76488	480
7450	18	74201	54	LS245	55	4162	99	LC7138	150	SN76489	480
7451	16	74221	54	LS257	30	4163	99	LF351	48	SL490	350
7453	16	74202	100	LS261	100	4175	105	LF353	50	SP6829	299

7454	18	74203	11	7456	10	4194	106	LF355	85	TA7120	150
7456	18	74204	11	7457	10	4195	106	LF356	95	TA7204	200
7457	18	74205	11	7458	10	4196	106	LF357	95	TA7205	200
7458	18	74206	11	7459	10	4197	106	LF358	95	TA7222	150
7459	18	74207	11	7460	10	4198	106	LF359	95	TA7223	150
7460	18	74208	11	7461	10	4199	106	LF360	95	TA7224	150
7461	18	74209	11	7462	10	4200	106	LF361	95	TA7225	150
7462	18	74210	11	7463	10	4201	106	LF362	95	TA7226	150
7463	18	74211	11	7464	10	4202	106	LF363	95	TA7227	150
7464	18	74212	11	7465	10	4203	106	LF364	95	TA7228	150
7465	18	74213	11	7466	10	4204	106	LF365	95	TA7229	150
7466	18	74214	11	7467	10	4205	106	LF366	95	TA7230	150
7467	18	74215	11	7468	10	4206	106	LF367	95	TA7231	150
7468	18	74216	11	7469	10	4207	106	LF368	95	TA7232	150
7469	18	74217	11	7470	10	4208	106	LF369	95	TA7233	150
7470	18	74218	11	7471	10	4209	106	LF370	95	TA7234	150
7471	18	74219	11	7472	10	4210	106	LF371	95	TA7235	150
7472	18	74220	11	7473	10	4211	106	LF372	95	TA7236	150
7473	18	74221	11	7474	10	4212	106	LF373	95	TA7237	150
7474	18	74222	11	7475	10	4213	106	LF374	95	TA7238	150
7475	18	74223	11	7476	10	4214	106	LF375	95	TA7239	150
7476	18	74224	11	7477	10	4215	106	LF376	95	TA7240	150
7477	18	74225	11	7478	10	4216	106	LF377	95	TA7241	150
7478	18	74226	11	7479	10	4217	106	LF378	95	TA7242	150
7479	18										

MONITOR

Directory Update

The response to our *Directory Of Electronic Component and Hardware Suppliers* has been tremendous, from both readers and the suppliers themselves. The reaction has been particularly strong from those suppliers who, for one reason or another, were either not included in our listings — or those whose address/telephone number got scrambled.

Naturally, they will all be listed (correctly) in our next Directory, here are some more companies operating on the supply side of our hobby . . .

**A.P.T. Radar Systems Limited,
Cybervox Language Laboratory
Division,**

Unit B, Sprint Industrial Estate, Chertsey Road, Byfleet, Surrey KT14 7LA. Tel. 09323 41331.

Specialists in the manufacture of tape recorders and related components together with headsets and spares.

Candis Electronics Ltd.

Highdown Works, Highdown Avenue, Worthing, West Sussex BN13 1PU. Tel. 0903 690750.

Specialists in temperature sensing components of all kinds.

Electronic Hobbies Ltd.,

17 Roxwell Road, Chelmsford, Essex CM1 2LY.

The correct telephone number is 0245 62149.

Garland Bros. Ltd.,

Chesham House, Deptford Broadway, London SE8 4QN. Tel. 01 692 4412.

"We are an established retail firm (20 years) dealing in electronic components, audio equipment, in-car entertainment, and we also do a very large range of CB equipment. A repair service for audio and CB is also available".

Garland Bros. carry all the lines mentioned in the charts, but do not operate a mail order service.

Roadrunner Electronic Products,

116 Blackdown Rural Industries, Haste Hill, Haslemere, Surrey GU27 3AY. Tel. 0428 53850.

"Developed and manufactured in Haslemere, our most well-known product is the Roadrunner prototype wiring system. This British product is already used extensively in industry and educational establishments, and is also ideal for the 'home engineer'.

Our hardware products range from packs of terminal pins to 19" subracks. We also handle computer and word-processing products, from typewriter ribbons through to microcomputer systems.

With a combination of the right product, a competitive pricing structure and excellent service, we make customer satisfaction our priority".

Roadrunner are moving to new, larger premises in Haslemere, with the intention of improving overall service to the professional and hobby markets. Orders using Access or Barclaycard are welcomed, either by phone or letter. There is no minimum order level, although a 50p handling charge is made on orders under £5. Carriage and pack-

ing charges are 5% of the total order before VAT is added.

TK Electronics,

11 Boston Road, London W7 3SJ.

The middle two numbers of TK's "easy to remember" telephone number were inadvertently transposed, rendering it 'not so easy'. The number should be, of course, 5-6-7-8-9-10.

The Vintage Wireless Company,

64 Broad Street, Staple Hill, Bristol BS16 5NL. Tel. 0272 565472.

"We are major stockists of obsolete electronic components, especially valves, and operate on a mail order business as well as personal calls to our premises. We try and offer a personal service, and also have a huge library of service data".

The range of services offered include: Sale of radio and television receivers, 1914 to 1954.

Sale of spare parts for the above.

Sale of radio, television and industrial valves.

Sale of service data, technical information, sales data, historical and other items of interest in vintage radio and TV. Restoration and overhaul (but not basic repairs of vintage equipment) of valve domestic and automobile radio of all types.

Sale of new and used books on the subject, plus second hand magazines, often dating back to the First World War!

Hire of radios and related props for theatrical purposes.

Sale of restored radios, with guarantee.

Sale of restored vintage car radios.

The full range of stock and vintage radio news can be found in The Antique Wireless Newsheet, published by the company from the above address — contact them directly for subscription rates.

Credit card sales are offered via Access and Barclaycard, and credit card orders are accepted by 'phone.

Flash Point Alarm

As if by magic, we have had replies to our request for suppliers of the difficult bits for this project.

First, the ICL7611 CMOS IC is readily available from Rapid Electronics, Hill Farm Industrial Estate, Boxted, Colchester, Essex CO4 5RD. The telephone number is 0206 36412.

The other tricky item was the thermocouple, without which the project had very little point; the exact thermocouple required is stocked in vast lengths by Candis Electronics Ltd., Highdown Works, Highdown Avenue, Worthing, West Sussex BN13 1PU. Tel. 0903 690750. Candis are specialists in the design and manufacture of temperature sensing equipment, and they carry a large stock of all kinds of thermal devices.

Add-Ons For The ZX Computers


Thurnall Electronics have produced a range of accessories for Sinclair's ZX 80 and 81 computers, with an adaptor system to fit the ZX Spectrum.

The range is based on a 16-line I/O port, and the modular system allows different add-ons to be used simultaneously via an inexpensive motherboard.

Thurnall recommend their system as "... an ideal way of learning about inputting and outputting information ..." from the computers. An analogue-to-digital converter and an RS232 interface are also promised. For details contact Thurnall Electronics, 95 Liverpool Rd., Cadishead, Manchester M30 5BG. A catalogue is available — but send an SAE with your enquiry.



MONITOR

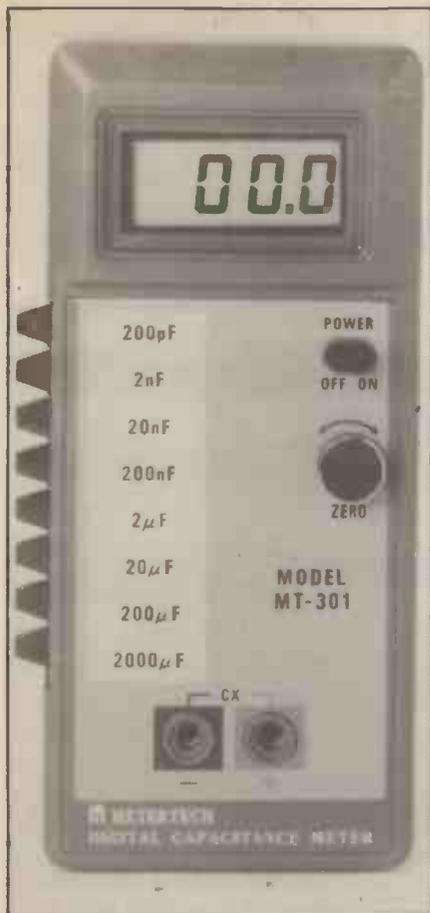

A Little Luxury

More advance builders, especially of radio equipment, may find Centemp Instrument's hand-held digital capacitance meter useful, provided they can spare £69. The little MT-301 is small and robust and designed to travel. It comes complete with battery, alligator test clips, spare fuse and instructions — all ready to go. A bold ½-inch, 3½ digit liquid crystal reads out from 0p1 to 200u across eight separate ranges; the controls are all push buttons for easy one-hand operation.

This is a slightly unusual piece of equipment, so anybody who feels the need of a digital capacitance meter could do worse than to start enquiring here. Incidentally, for the really rough rider, there's an optional "deluxe protective case" (fur-lined??) for an extra £6.00. Details from Centemp Instrument Co., 62 Curtis Rd., Hounslow, Middx. Tel. (01) 894 2723.

Hiding His Lights

Our apologies to Dr. D.L.H. Blomfield, who designed the *Three-Aspect Signal Lights Controller* project which appeared in our September '82 issue.

Dr. Blomfield has certainly earned our collective congratulations for his exceptional design, which has attracted high praise from several model rail enthusiasts.


We generally credit our designers — where would we be without them — but due to an oversight in this case, Dr. Blomfield's name was omitted from the article.

Full Protection, But No Racket

Radio buffs going mobile should take a look at a low-noise 24 to 12 volt switched-mode voltage converter gives an output of 13.6V (±0.2V) at 6A continuous current, has a low noise rating of 2 mV RMS below 1 MHz and 1 mV RMS above 1 MHz, and is fully protected and operable up to 50°C.

The 6A version is priced at £39.95 and is supplied with M4 bolts for bulkhead mounting if required. The unit is also available in a 10A version. For further information contact Davtrend Ltd., 89 Kimbolton Rd., Portsmouth, Hants PO3 6DA.

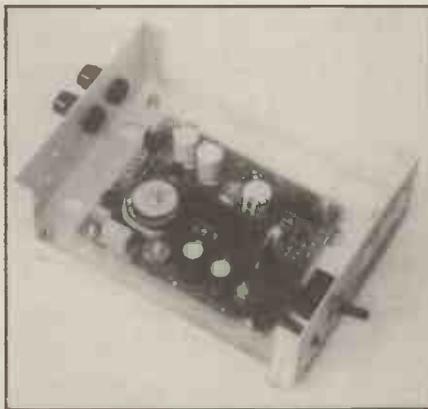And we'd better add that the unit is sold in a proper case, and not open to the air as our picture shows it!



Little Boxes

Things for putting other things in may not provide the total answer to how to run an orderly workshop, but they certainly do help, so SSI Fix Equipment have come up with a new system of component storage modules known as Portafix 6.

Each Portafix unit (sounds like something out of Asterix the Gaul, doesn't it?) has 12 bin-shaped drawers, each 2 x 4 x 3" deep. The overall size is 14 x 14 x 4", with a tray area on top, integral carrying handle and (an unusual feature) optional hooks, for carrying tools, at either end of the unit.

The whole thing seems to be designed for absolute minimum spillability and, for travelling, this principle can be taken even further — any two units can be hinged together face to face and securely locked shut — no more drawers sliding out every time the car tilts! Each little bin has a transparent dust-cover which opens upwards and the modules themselves can be stacked.

A very handy bit of storage equipment for any kind of craft which uses small components, from cake-decorating to woodworking to... well, electronics. At £7.40 for a single unit and £14.80 for a double (hinged) unit, this could knock a few of your Christmas present problems on the head!

At the moment Portafix 6 is only available from SSI Fix Equipment Ltd., Kingsclere Rd., Basingstoke, Hants RG21 2UJ, and prices don't include postage and packing, so you will have to enquire about that: telephone 0256 26511.

Rapid Electronics

MAIL ORDERS:
Unit 2, Hill Farm Industrial Estate,
Boxed, Colchester, Essex CO4 5RD.
TELEPHONE ORDERS:
Colchester (0206) 36412.



ACCESS AND BARCLAYCARD WELCOME

MICRO	2114-L2 75	Z80A CPU 290	81LS96 85
	2716 205	Z80A 10 260	81LS97 85
	2532 340	Z80A CTC 260	1488 55
BEST PRICES ANYWHERE!	4716 P20 70	Z80A BMA 1150	Epson Printers and D Connectors now available at low prices.
	6116-P3 150s 365	Z80A DART 500	
	440 480	81LS95 85	

CMOS	4016 20	4034 140	4054 78	4081 12	40193 65	4528 50
	4017 30	4036 249	4055 80	4082 12	4502 60	4529 150
	4018 45	4039 280	4059 430	4085 48	4503 32	4532 60
4000 10	4019 25	4040 4060	42 4086 50	4507 38	4534 400	
4001 10	4020 42	4041 40	4063 80	4089 125	4508 128	4538 110
4002 12	4021 40	4042 38	4066 22	4093 18	4510 45	4543 70
4006 50	4022 45	4043 40	4067 225	4094 68	4511 45	4549 360
4007 14	4023 16	4044 40	4068 14	4095 65	4512 50	4553 245
4008 36	4024 33	4046 50	4069 13	4097 290	4514 120	4555 35
4009 24	4025 16	4047 45	4070 13	4098 70	4515 120	4556 35
4010 24	4026 75	4048 38	4071 45	4099 70	4516 85	4559 390
4011 11	4027 20	4049 21	4072 13	4106 40	4518 40	4560 175
4012 15	4028 40	4050 21	4073 13	4109 110	4520 50	4584 40
4013 20	4029 45	4051 42	4075 13	4163 60	4521 130	4585 60
4014 45	4030 14	4052 48	4076 45	4173 100	4526 60	4724 140
4015 40	4031 125	4053 48	4077 14	4175 75	4527 50	

LS TTL	LS20 12	LS75 20	LS123 34	LS160 35	LS197 45	LS353 60
	LS21 12	LS76 17	LS124 24	LS161 35	LS221 60	LS366 28
	LS22 12	LS78 17	LS126 25	LS162 35	LS240 60	LS366 28
LS00 11	LS26 14	LS83 35	LS132 35	LS163 35	LS241 60	LS367 28
LS01 11	LS27 12	LS85 48	LS136 26	LS164 40	LS242 55	LS368 29
LS02 11	LS30 12	LS86 16	LS138 30	LS165 55	LS243 55	LS373 60
LS03 12	LS32 13	LS90 24	LS139 30	LS166 60	LS244 55	LS374 60
LS04 12	LS37 14	LS92 24	LS140 30	LS167 60	LS245 55	LS375 60
LS05 12	LS38 15	LS93 24	LS141 150	LS173 60	LS247 48	LS377 60
LS08 12	LS40 13	LS95 38	LS148 75	LS174 45	LS251 28	LS378 57
LS09 12	LS42 28	LS96 95	LS151 38	LS175 45	LS252 32	LS390 45
LS10 12	LS47 35	LS107 40	LS153 38	LS190 35	LS258 32	LS393 45
LS11 12	LS48 45	LS109 21	LS154 75	LS191 35	LS259 55	LS399 156
LS12 12	LS51 14	LS112 21	LS156 33	LS192 35	LS266 20	LS41 70
LS13 19	LS55 14	LS113 21	LS157 33	LS193 35	LS273 58	LS670 135
LS14 30	LS73 18	LS114 22	LS158 26	LS195 32	LS279 30	
LS15 12	LS74 17	LS122 35	LS158 29	LS196 45	LS283 38	

TTL	7413 17	7444 85	7483 30	74122 38	74161 46	74190 40
	7414 23	7446 58	7485 60	74123 38	74162 46	74191 40
	7416 19	7447 36	7486 19	74125 33	74163 46	74192 40
7400 11	7417 19	7448 43	7487 180	74126 33	74164 46	74193 40
7401 11	7420 14	7450 14	7490 19	74132 30	74165 46	74194 40
7402 11	7421 19	7451 14	7491 34	74141 54	74167 150	74195 40
7403 12	7422 19	7453 14	7492 24	74145 48	74170 115	74196 40
7404 12	7427 18	7454 14	7493 24	74147 75	74173 58	74197 40
7405 14	7428 25	7460 14	7494 33	74148 50	74174 53	74198 80
7406 19	7430 13	7472 22	7495 33	74150 48	74175 45	74199 80
7407 19	7432 20	7474 24	7496 38	74153 38	74176 35	74199 80
7408 13	7433 20	7474 19	7497 86	74154 47	74177 42	
7409 13	7437 23	7475 26	74100 78	74155 36	74179 75	
7410 13	7438 24	7476 25	74107 22	74156 36	74180 38	
7411 15	7440 14	7480 45	74109 24	74157 28	74181 100	
7412 17	7442 30	7482 65	74121 24	74160 55	74182 65	

LINEAR	LM339 45	LM3911 120	NE566 140	TL064 96
	LM348 60	LM3914 175	NE567 100	TL071 30
	LM348B 120	LM3915 195	NE570 370	TL072 30
555CMOS 80	ICL7106 700	LM377 170	LM3600 105	NE571 370
556CMOS 150	ICL7611 95	LM380 65	MC1496 68	RC4136 56
709 25	ICL7621 180	LM381 120	MC3340 135	RC4558 60
741 14	ICL7622 180	LM382 120	MF10CN 35	SL480 170
7400C 350	ICL8038 295	LM384 130	ML922 400	SL490 250
AY-31270 120	ICM722A 785	LM386 65	ML924 195	UA2240 120
AY-38910 370	ICM7551 85	LM393 100	ML926 140	SP829 250
AY-38912 625	LF355 45	LM709 25	ML927 140	TBA1205 70
CA3046 60	LF356 95	LM711 60	ML928 140	TBA800 96
CA3089 215	LM10 36	LM725 350	ML929 140	TBA810 96
CA3090A 375	LM301A 26	LM733 75	MM5387A 465	TBA820 70
CA3130E 85	LM311 70	LM741 14	NE529 225	TBA850 220
CA3140E 36	LM318 120	LM747 110	NE531 150	TDA1008 320
CA3161E 100	LM324 40	LM927 200	NE555 16	TDA1022 490
CA3189 290	LM3342 125	LM9900 45	NE556 45	TL061 40
CA3240E 110	LM3352 125	LM3909 70	NE565 110	TL062 60

TRANSISTORS	BC517 40	BF337 40	MPSU56 60	ZX108 8	2N3055 50
	BC547 7	BF440 23	TP129A 30	ZX109 12	2N3442 120
	BC548 10	BF480 23	TP129B 30	ZX100 14	2N3442 120
AC125 35	BC149 9	BC549 10	BF481 20	TP129C 37	ZX101 16
AC126 25	BC157 8	BC558 10	BFX29 25	TP130A 35	ZX102 15
AC127 25	BC158 10	BC570 18	BFY50 25	TP130B 50	ZX103 17
AC128 20	BC159 8	BCY71 18	BFY85 25	TP130C 37	ZX134 30
AC176 25	BC172 10	BFY86 18	BFY87 25	TP131 37	ZX135 30
AC181 22	BC168C 8	BD115 80	BFY88 25	TP131C 37	ZX501 18
AC188 22	BC169C 8	BD131 35	BFY98 25	TP132A 35	ZX502 15
AD142 120	BC170 8	BD132 35	BFY50 23	TP132C 37	ZX503 18
AD149 80	BC171 10	BD133 50	BFY51 20	TP133A 50	ZX504 25
AD161 40	BC172 8	BD135 50	BFY52 23	TP133C 75	2N687 20
AD162 40	BC177 18	BD136 30	BFY53 32	TP134A 60	2N698 40
AF124 60	BC178 18	BD137 30	BFY55 30	TP134B 60	2N706 20
AF126 50	BC179 18	BD138 30	BFY56 32	TP135A 105	2N708 20
AF139 40	BC182 10	BD139 35	BRX39 40	TP135C 125	2N918 35
AF186 70	BC182L 8	BD140 35	BSY20 20	TP136A 125	2N1132 22
AF239 75	BC183 10	BD204 110	BSX29 35	TP136C 135	2N1613 30
BC107 10	BC183L 10	BD206 110	BSY95A 25	TP141A 45	2N2218A 45
BC107B 12	BC184 10	BD222 85	BU205 160	TP142A 45	2N218A 25
BC108 9	BC184L 10	BF100 35	BUX86 200	TP120 90	2N2214 25
BC108B 12	BC212 10	BF122 35	BU208 170	TP121 90	2N2222A 25
BC108C 12	BC212L 10	BF184 25	BU295 99	TP122 90	2N2368 25
BC109 9	BC213 10	BF185 25	MJE340 50	TP141 98	2N2369 16
BC109C 12	BC213L 10	BF194 12	MJE520 65	TP142 98	2N2484 25
BC114 22	BC214 10	BF195 12	MJE521 95	TP147 110	2N2646 45
BC115 22	BC214L 10	BF196 12	MJE305 70	TPP95B 60	2N2904 20
BC117 22	BC237 9	BF197 12	MPF105 200	TP1305 55	2N2904A 20
BC119 35	BC238 14	BF198 10	MJF104 40	TP143 40	2N2905 22
BC137 40	BC308 15	BF199 18	MPSA05 22	TP144 45	2N2905A 22
BC139 40	BC327 14	BF200 30	MPSA06 25	TP150 30	2N2906 25
BC140 30	BC328 14	BF248 22	MPSA12 30	TP191 30	2N2906A 25
BC141 30	BC337 14	BF245 25	MPSA55 30	VN10KM 45	2N2907 25
BC142 25	BC338 14	BF256 45	MPSA56 30	VN46AF 75	2N2907A 25
BC143 25	BC347 9	BF257 35	MPSU05 55	VN65AF 9	2N2908 25
BC147 8	BC478 30	BF258 25	MPSU06 55	VN88AF 95	2N3053 23
BC148 8	BC479 30	BF259 35	MPSU55 60	ZX107 8	2N3055 50

SPECIAL OFFERS
TRC260 4A 400V 40
T1084 60
3mm red LED 5
7805 30
Offer ends 31/03/89

CAPACITORS
Polyester, radial leads, 250v, C280 type: 0.01, 0.015, 0.022, 0.033, 0.06, 0.047, 0.068, 0.1 - 7p; 0.15, 0.22, 0.3p; 0.33, 0.47 - 13p; 0.68 - 20p; 1u - 23p.
Electrolytic, radial or axial leads: 0.47/63V, 1/63V, 2.2/63V, 4.7/63V, 10/25V - 7p; 22/25V, 47/25V - 8p; 100/25V - 9p; 1000/25V - 14p; 470/25V - 22p; 1000/25V - 30p; 2200/25V - 50p.

POTENTIOMETERS
Rotary, Carbon track Log or Lin 1K - 2M2, Single 32p, Stereo 85p. Single switched 80p, Slide 60mm travel single Log or Lin 5K - 500K 63p each.
Preset submin, hor., 100 ohms - 1M 7p each.
Cermet precision multturn, 0.75W 1/4" 100 ohms to 100K - 88p each.

TOOLS
Small trimming tool 22
Small pocket screwdriver 16
Large pocket screwdriver 13
6 piece precision screwdriver set in plastic case 170
Low cost side cutters 160
High quality side cutters 650
Low cost pliers 160
High quality pliers 650
Wire strippers 120
Explo rellant drill 595
Espo Titan drill 1025
Drill stand 1200
Reduced shank drill bits for above 8.0mm, 60

REGULATORS	
78L05 30	79L05 65
78L12 30	79L12 65
78L15 30	79L15 65
7805 35	7905 40
7812 35	7912 40
7815 35	7915 40

SOLDERING IRONS
Antex CS 17W Soldering iron 460
2.3 and 4.7mm bits to suit 65
CS 17W element 450
Antex XS 25W 480
3.3 and 4.7mm bits to suit 65
Solder pump/dispenser tool 480
Spare nozzle for above 70
10 metres 22swg solder 100

OPTO	
3mm red 7	5mm red 7
3mm green 12	5mm green 12
3mm yellow 12	5mm yellow 12
Clips to suit 3p each	
Rectangular TL132 40	
Red 12	TL178 40
Green 17	TL1111 60
Yellow 17	ORP12 85
TL137 40	TL100 90
TLN877 45	Dual colour 60
Seven segment displays:	
Com cathode Com anode	
DL704 0.3" 95	DL707 0.3" 95
FND507	

HE Microlog

The return of the Analog Computer.

K. Manison

WITHOUT DOUBT we are living in a rapidly expanding digital world; *everything* is going digital. Clocks and watches, once precise mechanical instruments with analogue dials, now consist of tiny electronic circuits displaying the time in digits accurate to a tenth of a second. The acceptance of digital technology can be seen in the rapid increase in the availability of women's digital watches; it is no longer a symbol of male technology!

Digits are also appearing in other areas, long the exclusive domain of analogue indicators, but display methods are not the only field to fall to digital techniques. Our telephone conversations are digitised and transmitted as serial bit streams and who, today, hasn't heard of digital hi-fi? And with the recent release of video disc systems, digital video has finally arrived.

One of the reasons for the digital revolution, of course, is cost. With the rapid advances of digital integrated circuits — and that superstar the microprocessor — it has become much cheaper to produce a silicon circuit with an LED or LCD display, than to make a complicated mechanical indicator.


In many cases, the increased accuracy and resolution is definitely required and digital systems may be used to excellent effect. In other cases, however, the older analogue systems have many advantages, and that is true also of the analogue computer.

The Analogue Computer

Remarkable though it may seem, the analogue computer, which need not have a single TTL or CMOS logic chip in the whole of its circuit, manages to perform calculations that many digital machines would find difficult. Analogue computers have been around for decades in one form or another. In fact, many of us have used a slide rule without even being aware that it is an analogue computer.

Whereas a digital computer performs its calculations directly, using numbers, an analogue computer will use some physical parameter to represent the values it is to manipulate. The slide rule, for example, uses length; the length is considered to represent the log of a number so that adding two lengths together is *analogous* to adding logarithms which, of course, is a method of performing multiplication.

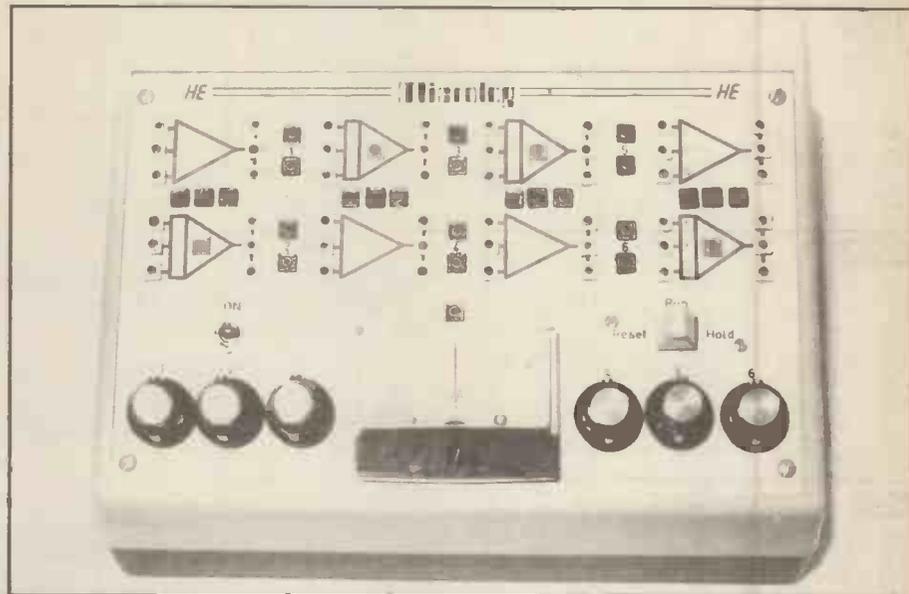Until the cheap digital calculator became available, the slide rule was dexterously manipulated by



generations of engineers and scientists, and it has in no way hindered the advance of technology! In fact, entering experimental results accurate to two decimal places into a calculator and getting out a result with eight places of decimals can be meaningless. If the data is limited to two place accuracy so is the result, and we have to round off the answer anyway. The slide rule, being accurate to two places, can in many cases produce answers that are just as valid as a calculator, and it is not much slower either! To further illustrate the difference between analogue and digital computation, let us look at a common problem. When changing a note for coins, the bank teller can count the money in one of two ways. The most obvious way is to empty a heap of 10ps on to the table and count the required number. For small sums this is adequate, accurate and, for the experienced teller, remarkably fast. However, if a large sum has to be changed, the digital computing method becomes too slow and also increases the chance of error. So, the teller will weigh the coins and, the weight of a single 10p piece being known, the scale can be graduated in pounds and pence. This is an analogue method in which weight is the analogue of value. In this case, the analogue method will be faster than physically counting each coin and, with an accurate scale, just as precise.

It is obvious that different applications are better suited to either digital or to analogue computation. For example, analogue computers have long been used for solving differential equations of the type frequently encountered in control theory and

servo systems. While these equations can be solved by digital means, it is a time consuming process and often expensive as well. However, an electronic analogue of the system can be constructed on an analogue computer, the stimulus then fed in and the output viewed in real time on an oscilloscope or chart recorder. Variables of the system can be changed independently and the process run again and again.

It is the speed of computation, and the graphical output, that give the analogue computer the edge on this type of problem. So now let's look into an analogue computer and see what it consists of and how it can be used. For those that are interested in experimenting with these machines, the Microlog is a simple and cheap analogue computer that can be used to try out some of these concepts.

Analogue Computing

An analogue computer performs the functions of summation (adding), multiplication, integration and differentiation. While a digital computer can perform all these functions, it can only do them one at a time. So, even though it works very fast it has to perform a series of calculations. Particularly where integration is concerned, many simple calculations have to be made to solve one integral, and, if the step size is kept small to increase accuracy or resolution, then more calculations are required and the time taken is increased.

Say, for example, the solution to the problem $X = Y + (V + U)/2$ is required. A digital computer would tackle the problem like this: first, V and U would

Project

be added together and stored as a variable; second, that variable would be divided by 2; last, it would be added to Y to give the required answer. A program, written in BASIC, to handle the problem may look like this:

```

10 INPUT U
20 INPUT V
30 LET X = (U + V) / 2
40 INPUT Y
50 LET X = X + Y
60 PRINT X
70 END
    
```

For a simple problem like this these steps take very little time, but if a large complicated formula were being calculated you can see that this sequential type of process may take a very long time indeed.

The analogue computer, however, uses separate modules to simultaneously perform each function required in the calculation, and the manner in which the modules are interconnected determines the formula being calculated. If two additions have to be performed then two summers will be used, one for each.

For the problem $X = Y + (V + U)/2$, an electronic analogue computer would have modules connected together as shown in Figure 1. The triangle symbols are summers and produce the algebraic sum of the input voltages. The circle symbol is a coefficient multiplier, used to divide the sum of $V + U$ by 2 (multiplication by 0.5). You can see that as soon as the input voltages corresponding to Y, V and U are presented to the modules, X will be instantly available. Notice that the analogue computer is effectively performing all of its calculations in parallel, not one after the other. It is also performing an 'on-line' calculation in that the output X will continually follow the inputs. A digital machine would have to prompt for updated values, or interrogate I/O ports for them. This is what gives the analogue computer a speed advantage, in many cases. To find out how an analogue computer works, let us examine each of the building blocks; then we will determine how to put them together!

Computing Units

An analogue computer uses voltage and time to represent numeric values. For example, a voltage rising from 0 volts to 3 volts over a period of a minute could be used to represent the filling of a 300 gallon tank in the same time. In this case, 1 volt represents 100 gallons, and its variation with time shows the changing level in the tank. So, a plot of voltage against time will show the physical movement of the system we are simulating with the analogue computer. The analogue computer, therefore, needs devices that will sum, integrate and multiply electronic voltages. If we think of these devices as circuit elements, then we can connect them together as a circuit to produce the function we require.

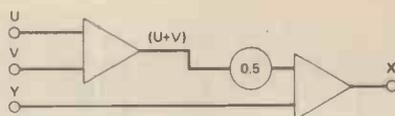


Figure 1. The analogue solution to the equation.

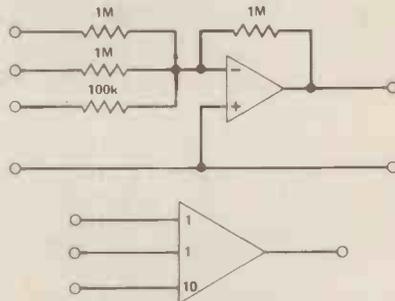


Figure 2(a). An analogue summing circuit (above); 2(b) the graphic symbol used for a summer (below).

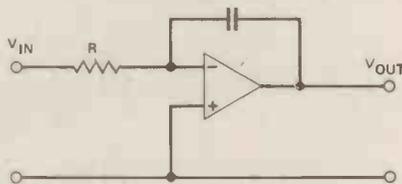


Figure 3. The circuit of an op-amp integrator.

Summers

If our computer is to use voltages to represent physical values then we need an electronic device to add two voltages together; it must produce a voltage which is the algebraic sum of two or more instantaneous voltages.

The simplest method is to use an op-amp; if we add several inputs through resistors, we get an output proportional to the sum of the input voltages. A typical circuit is shown in Figure 2a. The summer circuit module is usually shown by the symbol of Figure 2b. The gains, normally 1 and 10, are shown for each input.

Integrators

We stated at the beginning that analogue computers are used to produce solutions to differential equations, and this means that integration and differentiation are involved. Integration is essentially the sum of all the instantaneous values of a function. Normally it is performed between definite limits, say between the times $t = 0$ and $t = 100$. Some initial condition must also be specified if the integration is to be valid. For example, when integrating a voltage signal V , the starting condition may be $V = 2$ when $t = 0$. Therefore, the integrator must also have an "initial condition" input.

We can use an op-amp to integrate a voltage; consider the circuit shown in Figure 3. The output is given as:

$$V_o = -\frac{1}{RC} \int V_i dt$$

Of course, we can integrate multiple inputs in exactly the same way that we

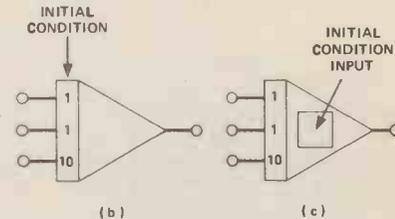
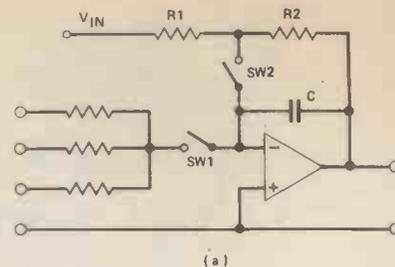


Figure 4. Above (a), the integrator circuit modified for initial condition input; (b) the usual graphic symbol; (c) the representation used on Microlog's panel.

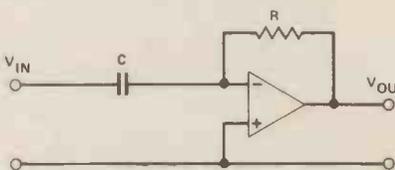


Figure 5. An op-amp differentiator.

summed several inputs, and it should also be clear that by changing the input resistors the integrator gains, expressed as $1/CR$, can be independently set for each input.

Now to set the initial conditions: we must be able to set the output (by setting the charge on the capacitor) to a desired value. In effect, the circuit must behave as a summer up to time $t = 0$, but operate as an integrator after that time. We achieve this by means of two switches, as shown in the circuit Figure 4a.

If switch SW2 is closed, you can see that you have a summer with only one input, $V_i \times R1/R2$. The capacitor will also have this voltage across it and will be charged to the desired initial condition.

If switch SW2 is opened and SW1 closed, we have an integrator with three inputs. When both switches are open, the circuit acts as a 'hold' circuit — the output will remain at whatever the voltage was when SW2 was opened. This is dependent, of course, on the capacitor remaining charged, but as the input impedance of the op-amp is very high, it can hold the voltage for an appreciable time.

In a large analogue computer, these switches are replaced by relays, which allows the machine to be switched from Reset to Compute repeatedly, and the response can be displayed on an oscilloscope. This mode of operation is called Rep-Op, short for Repetitive Operation.

Differentiators

We learn at school that integration is the opposite procedure to differentiation, so that the opposite



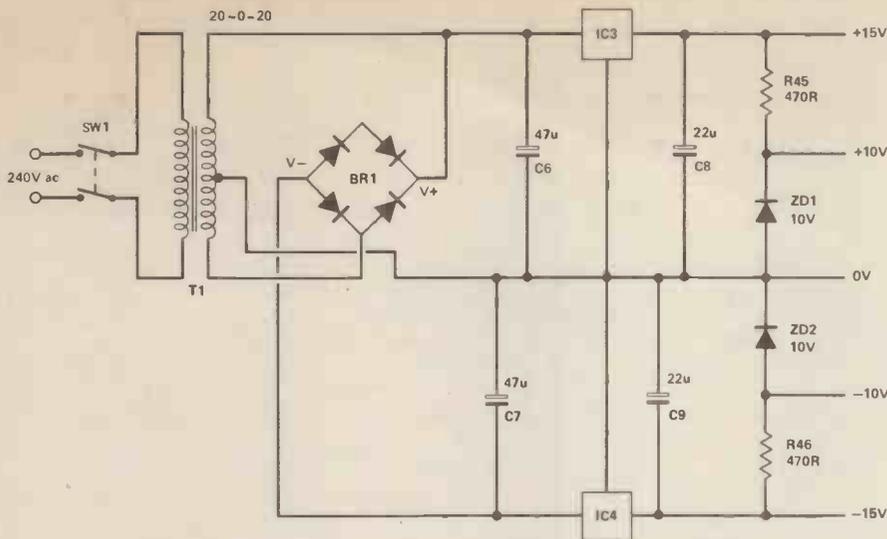



Figure 6. The complete Microlog circuit: (above) the power supply; (far left) the coefficient multipliers; (near left) the meter circuitry; (below left) the four summing circuits; (below right) the four integrators. Not all the components are mounted on the PCB; connection points are marked to aid wiring, which needs careful attention — see NOTE, below, and Figures 8 and 9.

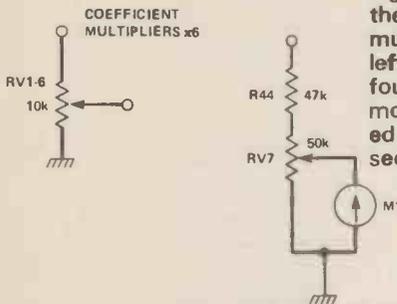

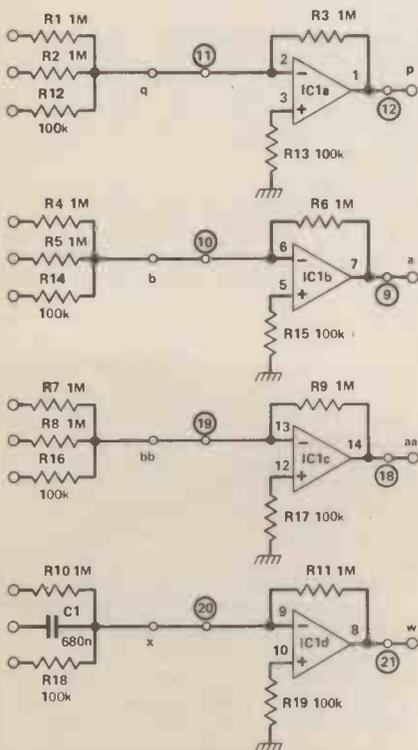NOTES:
IC1,2 ARE 348
IC3 IS 7815
IC4 IS 7915
M1 = 100µA CENTRE ZERO



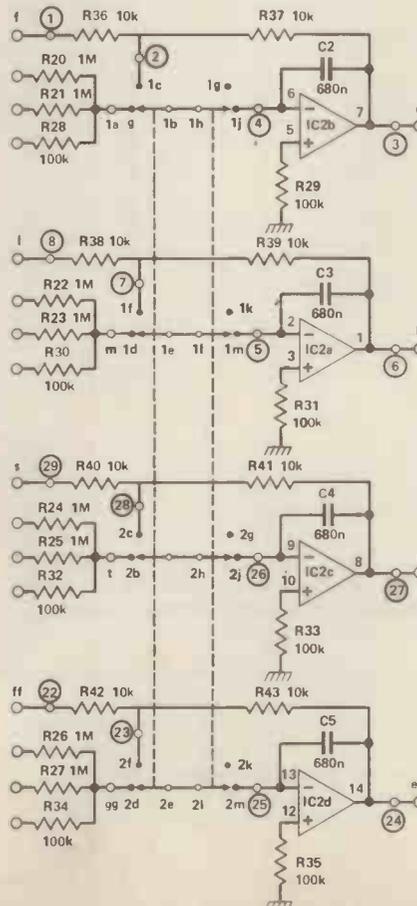NOTE:
CIRCLED NUMBERS = PCB CONNECTOR POINTS
LOWER CASE LETTERS = PATCH PANEL CONNECTOR POINTS
NUMBER AND LETTERS = LEVER SWITCH TERMINALS
LEVER SWITCH SHOWN IN "RUN"



configuration, in the op-amp circuit, will produce a differentiator. The circuit in Figure 5 produces the differential of the input voltage, and once again we can have several inputs with independent gains.

Coefficient Multipliers

So far we have shown our summers, integrators and differentiators with fixed gains of, eg., 1, 10, or 100. We could, of course, set them to any value required — 2.375 for example — but we lose flexibility if the gains are set to such 'strange' values, as they will only be useful for a calculation that needs that particular number! However, if we have a device that will divide a voltage by 11.2375 (ie. multiply by the coefficient, 0.2357) and then follow that by a summer with a gain of 10, we have achieved our required gain of 2.375. So we need a voltage, or potential, divider — which is nothing else but a potentiometer!

For analogue computers, the potentiometers have to be precise and stable. Also, there must be some means of setting them to the required value. The way this is achieved is to connect them across an accurate, known voltage and measure the output while adjusting the pot until the desired coefficient is reached. In large machines, this may be done automatically by small servo motors connected to the wiper mechanism. For small machines, such as the one described in this article, the pot has to be set manually. In the example above, the potentiometer could be connected across 10 volts and adjusted until the output at the wiper measured exactly 2.375 volts.

The HE Microlog

Microlog stands for Micrologue Computer (we can't have digital machines claiming sole rights to the term 'Micro'!). It has been designed as a conceptual trainer to give you a feel for analogue computing and, therefore, accuracy has been traded for low cost and simplicity.

Microlog's patch panel shown in Figure 7 and from it you can see that it has four integrators, four summers and six pots (coefficient multipliers). The Initialise-Integrate-Hold selection is performed by the keyswitch labelled Reset-Run-Hold; no rep-op mode is available as that would entail the use of relays, increasing the cost. The complete circuit is built on one PCB and fits in a type 104 Verobox, with 2 mm plugs used for the patch connectors. The most expensive item in the Microlog is the meter!

To keep everything simple, single chip voltage regulators are used for the 15 V power supplies and the reference supplies are simple zener diode regulators. Two 348 quad op-amps are used, one chip providing the four integrators and the other the four summers. One of the summers has a capacitor on one input to provide a differentiator function. The complete circuitry is shown in Figure 6.

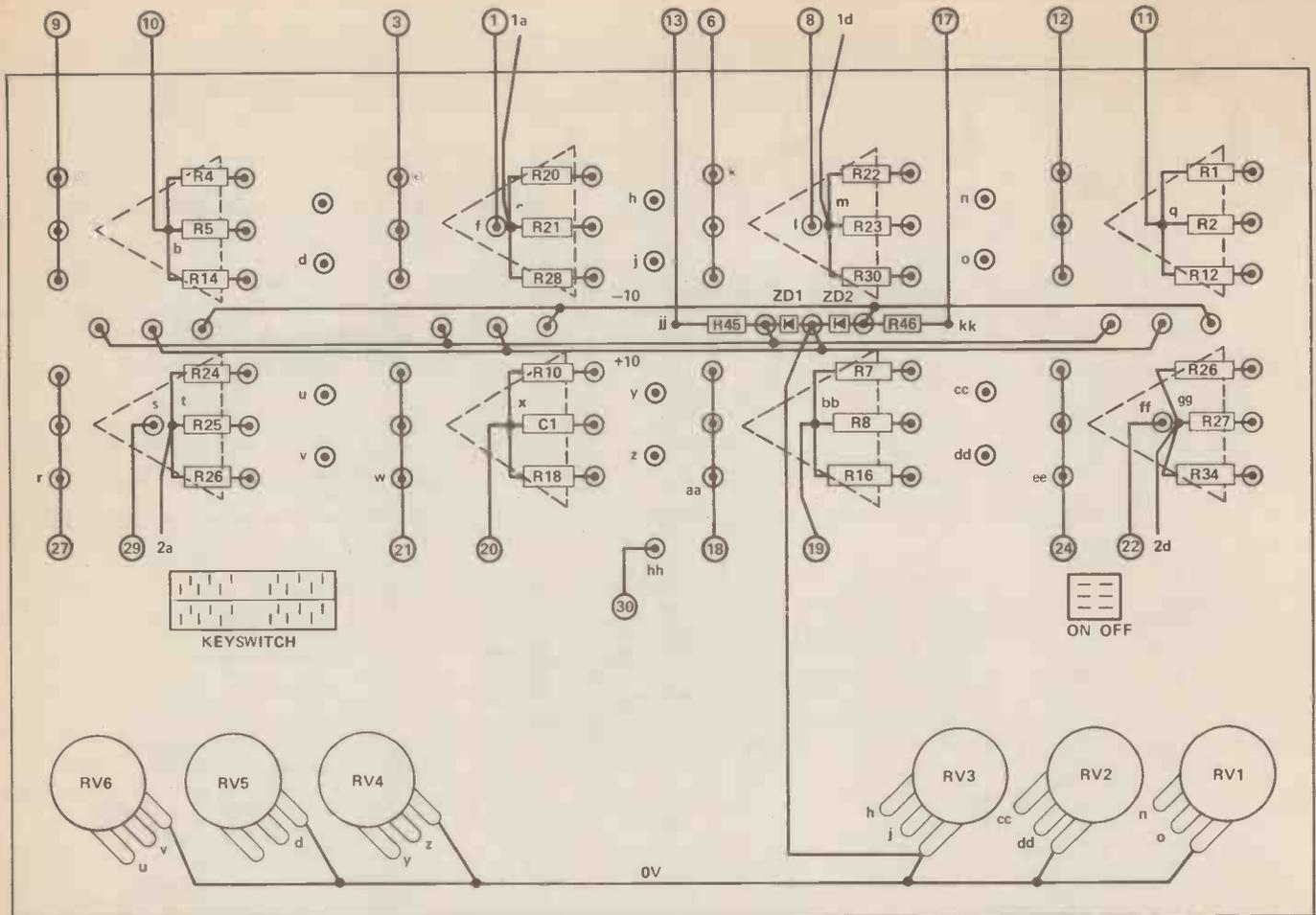


Figure 8. The front panel wiring diagram, showing the mounting positions of the components and the wiring points (eg, point 'f' goes to PCB point '1'; point 'g' goes to the leverswitch terminal '1a'). The switch terminal connections are shown in Figure 9.

The Patch Panel

Having designed the various computing elements that go to make up an analogue computer, we now require a method to interconnect them in order to solve problems. This is usually done by means of a patch panel. The inputs and outputs of each computing unit are brought out to sockets and jumper wires may then be used to connect the desired units to simulate a system or solve an equation.

Construction

The first thing is to drill the front panel of the Verobox for the 2mm sockets, pots, switches and the meter. Then, using Letraset or similar rub-down lettering, mark out the patch panel and spray with a clear polyurethane lacquer so that the markings will not rub off after a little use. The full-sized patch panel is reproduced on page xx for use as a template in this operation.

Next, mount all the sockets and pots. When tightening the nuts on the 2 mm sockets, take care not to overdo it or you may strip the thread. Using the wiring diagram, Figure 8, as a guide, connect up the pots to their respective sockets. Again, be very careful when soldering to the 2 mm sockets, as the plastic body melts very easily!

The next step is to mount the input resistors on the correct sockets for the summers and integrators (mounting

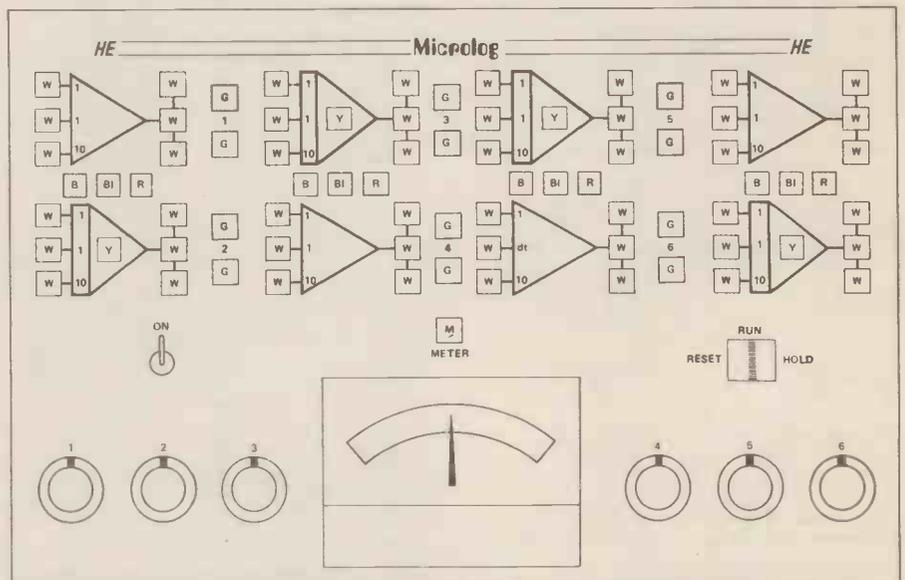


Figure 7. The front panel of Microlog.

□ 2mm SOCKETS
 B BLUE = -10V
 BI BLACK = 0V
 R RED = +10V
 G GREEN = POTENTIOMETERS
 Y YELLOW = INITIAL CONDITION INPUTS
 W WHITE = OP-AMP INPUTS AND OUTPUTS
 M = METER INPUT (BLUE)

them here, instead of on the PCB, reduces the amount of wiring from the patch panel to the PCB). Use the circuit diagram and the wiring diagram to determine the correct place for each resistor. Then mount the 10 volt Zener diodes, ensuring that you have put them in the right way round, and the 470R resistors.

The final front panel wiring is that from the keyswitch to the sockets. Take special care that this wiring is correct, as it is easy to get confused with the connections on the keyswitch. Use the circuit diagram and Figure 9 and double check it when you've finished. It is easier to change incorrect wires then, than at a later stage in the

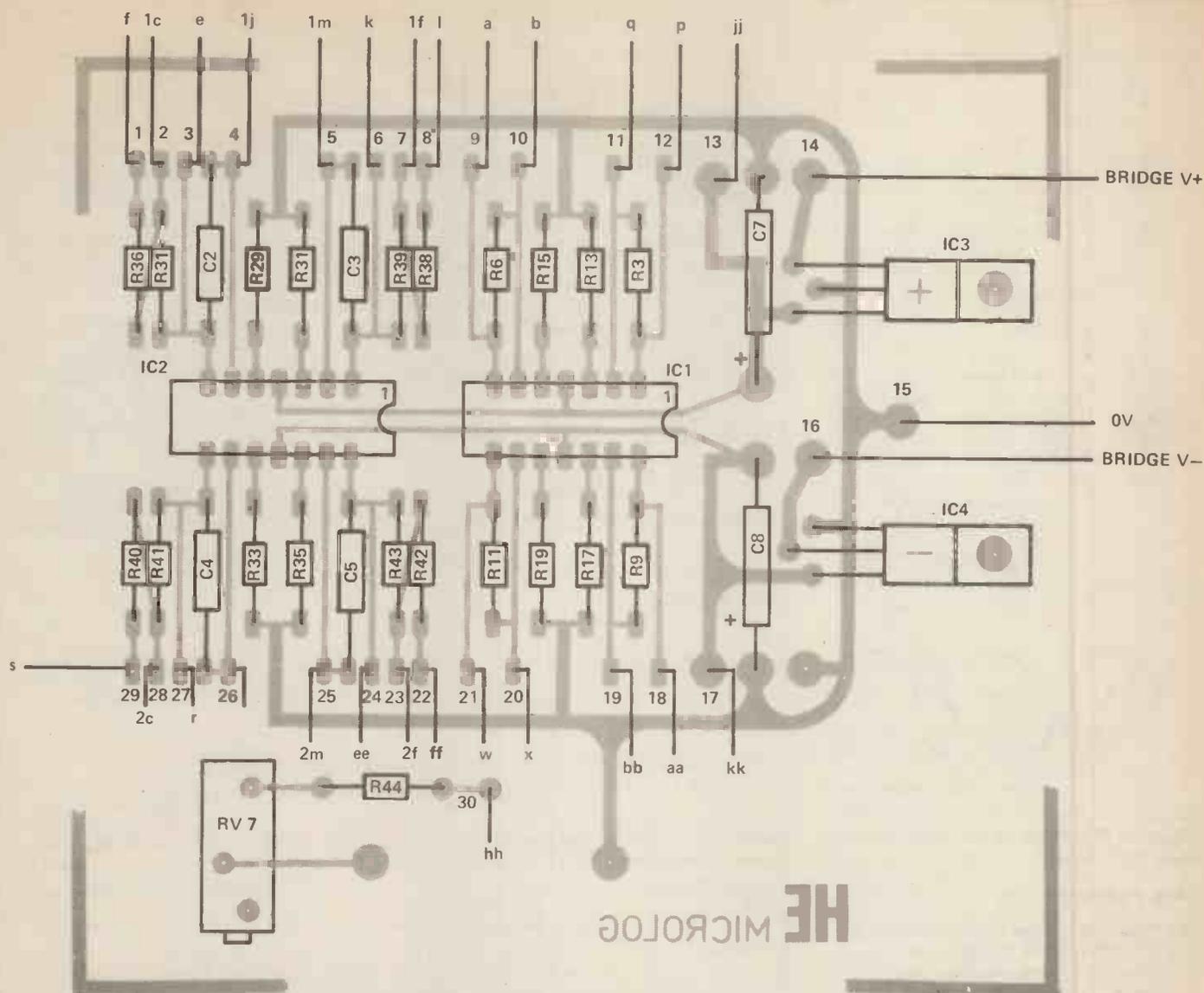


Figure 10. The PCB component overlay diagram; note the connection points.

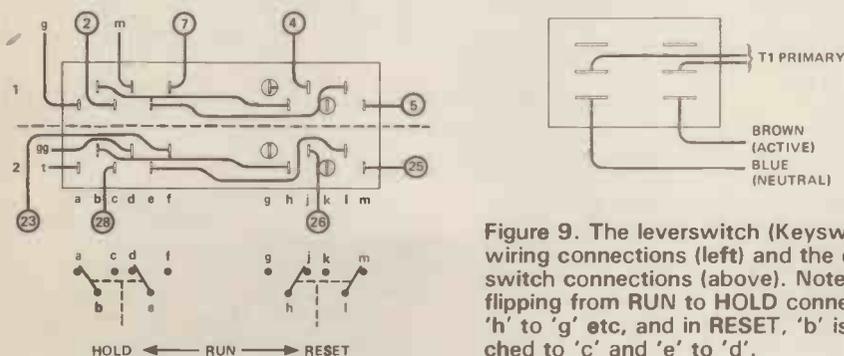


Figure 9. The lever switch (Keyswitch) wiring connections (left) and the on/off switch connections (above). Note that flipping from RUN to HOLD connects 'h' to 'g' etc, and in RESET, 'b' is switched to 'c' and 'e' to 'd'.

construction.

Before the panel can be put back on the Verobox, you will have to remove the central plastic strip that crosses the panel aperture. Don't worry — it doesn't weaken the box in any way. Some time before the testing stage, too, you will have to make up about 20 patch leads with 2 mm plugs on each end; it is best to make assorted lengths, say 3, 6 and 9 inches long.

Now you can start to mount the components on the PCB, using the Parts List and component layout Figure 10 to locate each part. First check the

tracks, to ensure there are no breaks or bridges, and then install the IC sockets and solder them in. Do not plug in the op-amps until the check-out procedure, later. Next, install the resistors on the board and once they are soldered, mount the capacitors. Ensure that the orientation of the electrolytic capacitors is correct; the layout diagram shows the way. Finally, install the two voltage regulator ICs; these are mounted with the metal face against the PCB and held in position with a small screw lockwasher and nut, and be sure the regulators are in the right

places. One is a positive voltage regulator and the other negative and if you accidentally swap them around, they won't last a second when you switch on! Bend the leads down into their respective holes and solder them in. Go over the board, then, checking for any solder bridges or dry joints, touching up where necessary.

Once the board is complete you can start wiring from the patch panel to the PCB connection points, using the wiring diagrams, Figures 8 and 9. This is where great care must be taken, as it is all too easy to get wires crossed. Give yourself enough length on the wires to be able to route them neatly, and to allow the panel or top of the box to be taken off without pulling the wires!

The wiring from the PCB to the keyswitch can be done next, again taking care that the correct connections are made. The PCB is then mounted to the panel, using the screw terminals of the panel meter, which also provides the electrical connections to the meter.

The last part of the construction is the power supply unit (PSU). This is extremely simple, consisting of the small transformer, a bridge rectifier

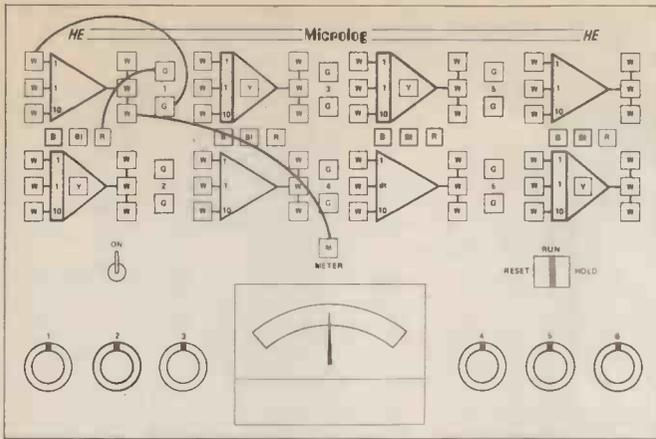


Figure 11. Patch diagram for testing the summing amps.

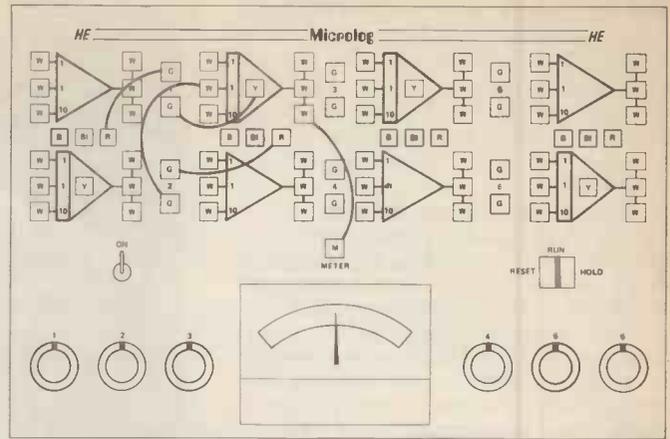


Figure 12. The patch for testing the integrators.

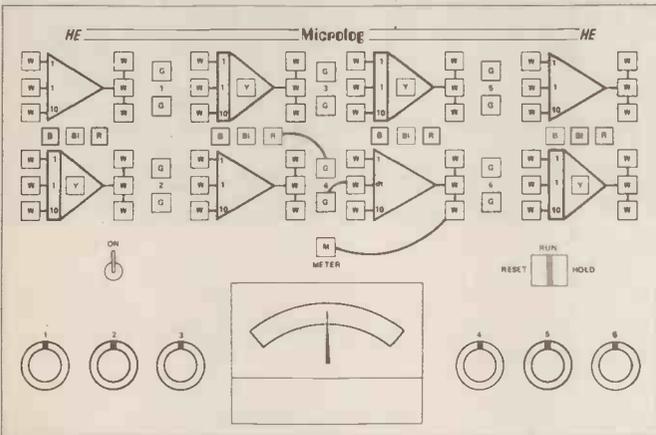


Figure 13. Testing the differentiator.

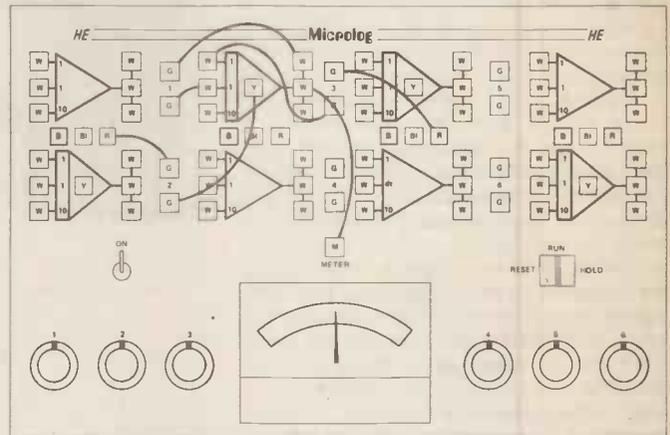


Figure 16. Patching the bathtub.

first seemed. First, then, we shall look at the filling problem with no outflow at all.

If we fill the bath from the tap the inflow will be a constant, 'K', determined by the setting of the tap and the water pressure. The quantity poured in, 'di', during time interval 'dt' is:

$$di = K \cdot dt$$

Now the rise in level 'dh' for quantity 'di' is:

$$dh = 1/A \cdot di$$

where 'A' is the area of the bath. Rearranging to make 'di' the subject we get:

$$di = A \cdot dh$$

Substituting this for 'di' and rearranging we get:

$$\frac{dh}{dt} = \frac{K}{A}$$

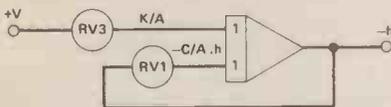


Figure 14. Developing the bathtub circuit.

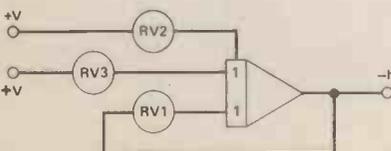


Figure 15. The bathtub completed.

So now we have a differential equation expressing the rise in level with time. The value 'K' represents the amount by which the tap is turned on and the main water supply pressure.

Now about the emptying part; the amount of water that will flow out in time interval 'dt' we shall call 'do'. Therefore, 'do' will be equal to the head 'h', multiplied by some constant 'C', where 'C' takes into account the size of the plug hole! Mathematically then:

$$do = C \cdot h \cdot dt$$

If the bath has a cross-sectional area of 'A' then the fall in head will be equal to:

$$dh = -\frac{1}{A} do$$

The sign is minus because the level is dropping. Rearranging we get:

$$do = -A \cdot dh$$

Substituting we get:

$$A \cdot dh = -C \cdot h \cdot dt$$

or:

$$\frac{dh}{dt} = -\frac{C}{A} h$$

This, too, is a differential equation showing the change of head with time, but this time it is due to the bath emptying. Therefore, the change in level at any instant in time will be the sum of the filling and emptying. So, finally, we can write:

$$\frac{dh}{dt} = \frac{K}{A} - \frac{C}{A} h$$

This is a differential equation of the type that Microlog can solve with ease; let's set up the circuit. First we will need an integrator, so that if we

put 'dh/dt' in we will get '-h' out (which is what we want). So, we have to put voltage signals corresponding to the right hand side of our equation into the integrator, and we will then get out a voltage that will be the analogue of the water level at any instant in time. The circuit, then, will look like Figure 14. Notice that each input does in fact represent a term on the right of our equation and that, as the inputs are summed, the terms are added, just as in the equation.

To complete the picture we have to set the initial conditions of the system; in this case the initial condition is the level of the bath water before we start the filling and emptying process. We can set it to zero (an empty bath) or at any level up to full. The complete circuit is shown in Figure 15 and the Microlog patch diagram is shown in Figure 16.

Now to run the program: first set Microlog to Reset and adjust RV2 to set the water level to full. That will be minus full scale deflection of the meter. Ensure that RV1 and 3 are turned fully off, anticlockwise, and switch to Run; the water level should remain constant. Now pull out the plug! You do that by turning up RV1; the value determines the size of the plug hole and thence the rate of outflow. Notice that the water level is dropping, as shown by the meter movement, and that the rate slows down as the bath empties. If we turn on the tap, RV3, you can fill the bath. Of course, the filling rate will have to

Project

be greater than the emptying rate or the level will slowly drop. It is interesting to start with an empty bath and start pouring water in. If the plug is open, the level will start to rise until the increased head causes the outflow to equal the inflow. At this point the level will remain constant. Turn down the inflow rate a little and after a while a new equilibrium level will be found. The time taken is the 'response time' of the system that we have just modeled on our analogue computer!

So instead of doing lengthy calculations, or getting wet running an experiment, Microlog has allowed you to set up an analogue of the system under test. You can try various settings for all the pots to see how the result changes.

Let's look at another application. You may remember that integrating SIN(X) gives -COS(X), and integrating COS(X) gives -SIN(X).

Again, this is a differential equation of the type easily set up on Microlog. Look at the circuit and patch diagram in Figures 17 and 20. If you patch this on Microlog, set the initial condition of integrator 1 to 10 volts and then switch to Run you will get out a sinewave or a 90 degree phase shifted sine wave (COS). Using pots RV1 and 2, you can slow down the frequency of oscillation (or by patching into the x10 inputs of the integrators you can speed it up). This makes quite a neat and simple very low frequency sinewave oscillator. Due to the tiny leakage of the capacitors and the small input currents of the op-amps the amplitude will decay eventually, but it will continue to oscillate for many minutes.

Loops and Bumps

Two areas in which analogue computers are often used are those of modeling dynamic systems and servo loops. These two problems require the solution of second order differential equations of the type:

$$A \frac{d^2x}{dt^2} + B \frac{dx}{dt} + Cx = 0$$

Let's take the front suspension of a car: what will happen if you hit a large pothole in the road and your shock absorbers are bad? Figure 19 is a simple representation of the type of system we are going to model, and the equation that describes the response of the system to a disturbance (a pothole) is:

$$M\ddot{X} + D\dot{X} + SX = 0$$

where $\ddot{X} = \frac{d^2x}{dt^2}$ and $\dot{X} = \frac{dx}{dt}$

$M\ddot{X}$ is the inertial force due to the mass of the car, $D\dot{X}$ is the viscous damping force produced by the shock absorber, and SX is the restoring force of your front spring. X , of course, is the displacement of the suspension system, and we want to see how quickly this will be restored to the original value.

To patch this on Microlog we first rearrange the equation so the \ddot{X} is the subject:

$$\ddot{X} = -\frac{DX}{M} - \frac{SX}{M}$$

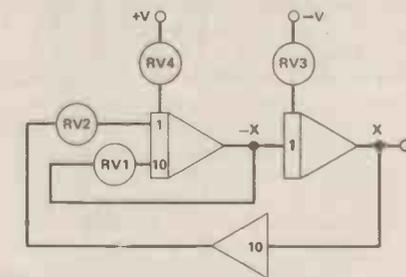
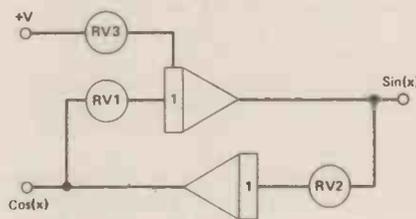
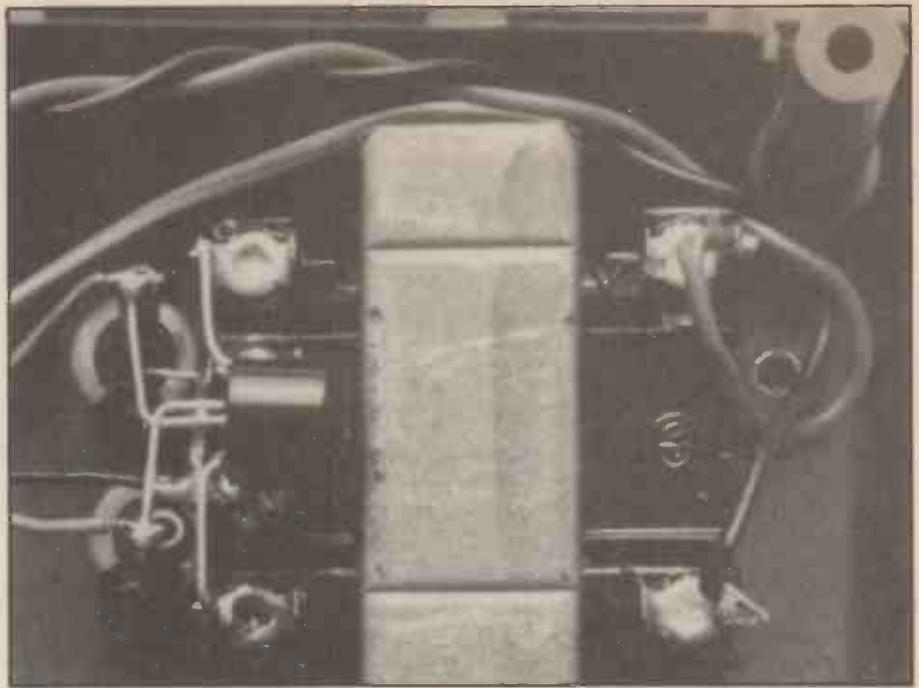





Figure 17 (top left). The Sin X/Cos X generator circuit.

Figure 18 (top right). A model suspension.

Figure 19 (middle left). Suspension circuitry.

Figure 22 (middle right). Model of a closed-loop servo system.

Figure 23 (right). Response curves of a closed-loop servo.

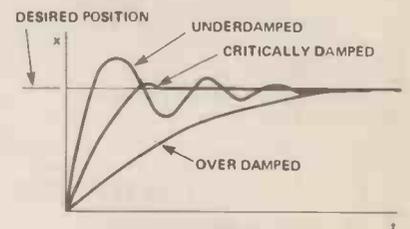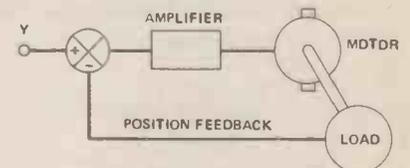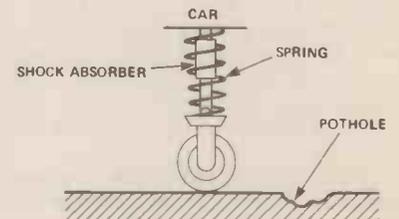

Integrating \ddot{X} gives \dot{X} , and integrating \dot{X} gives X . These can then be summed according to the formula to give \ddot{X} . The circuit and patch are shown in Figures 19 and 21. Pot RV1 is used to set the $D\dot{X}$ term and RV2 determines SX : Set them both to about mid range. But if we drive along a perfectly flat road the suspension will not move, so we have to simulate the bump. This is done by setting an initial condition into the integrators, to show that the suspension has been displaced.

Turn Microlog to Reset and set RV4

to about mid value and RV3 to give -50 on the meter - this is a medium sized pothole! Now switch to Run and watch the meter. It will return to zero (the original position) and then overshoot, then reverse direction but overshoot zero again, though not by so much this time. Eventually, it will settle down to a smooth ride again. Try playing around with RV1 and RV2; reducing RV2 reduces the effectiveness of the shock absorber and you will find the front end of your car bouncing up and down for the next few miles. Increase it, and it takes a

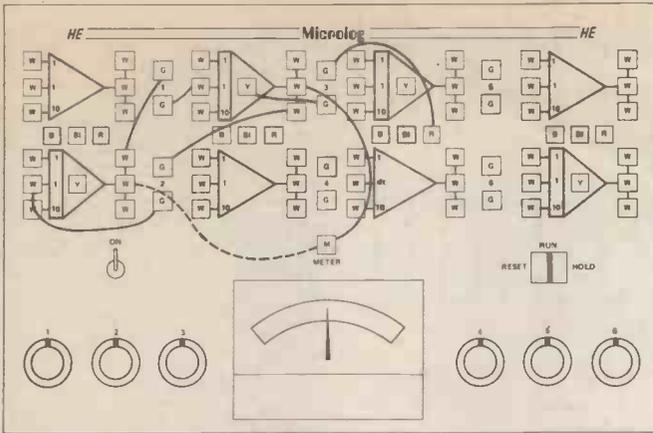


Figure 20. Sin X/Cos X patch.

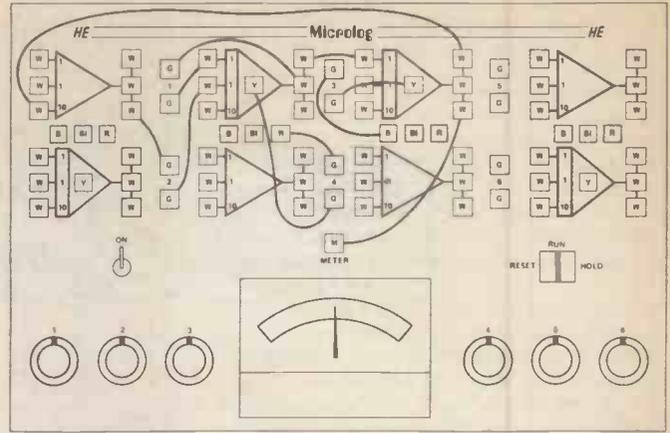


Figure 21. Pothole patch.

long time to return to the level condition again. If you increase RV1 you stiffen the spring. A high RV1 and RV2 setting simulates the rock hard suspension of a sports car, while a low setting for both (especially P1) gives you the ride of a big American Cadillac!

A closed loop servo system, of the type shown in Figure 22, also has a second order differential equation to describe its performance. In this case, instead of turning to the zero displacement position, the system must move to the position corresponding to the input signal Y.

Microlog can model this system too, and in fact it is very similar to the

car suspension problem. To change the patch to model the system shown in Figure 22, all you have to do is take the output of RV3 from the initial condition input of the integrator and plug it into the free summing input; this pot is now your position control. RV1 now sets the gain of the feedback loop and RV2 the inertia of the system. Switch Microlog from Reset to Run and then move RV3 to a new position; the meter output will follow but overshoot, and then come back. You can determine the best response by playing with the gain and inertia of the system, and if you have an oscilloscope you can plot the response and should be able to see the sort of

curves shown in Figure 23.

These are just a few of the possible systems and problems that can be solved with an analogue computer. Microlog is not designed to produce accurate numerical results; however, it can give a good idea of how a system will function, and give you a feel for analogue computing.

It can also be used to add signals, or the integrators can be set up to give you a very slow ramp. The differentiator input can be used to measure the slope of a ramp and it can also be used to detect drift in a circuit, so Microlog can be quite a useful lab instrument as well!

Go on. Build one!

HE

MODULES FOR SECURITY & MEASUREMENT

INTRUDER ALARM CONTROL UNIT CA 1250

As featured in PRACTICAL ELECTRONICS

only £19.95 + VAT

This exciting new module offers all the possible features likely to be required when building an intruder alarm system. Whether used with only 1 or 2 magnetic switches or in conjunction with several ultrasonic alarm modules or infra-red units, a really effective system can be constructed at a fraction of the cost of comparable ready-made units. Supplied with a fully explanatory Data Sheet that makes installation straight forward, the module is fully tested and guaranteed.

*available in kit form £16.95 + VAT

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charging facility
- Operates with magnetic switches, u/sonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage for external units
- 2 operating modes - full alarm/anti-tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for switching external loads
- Test loop facility

ULTRASONIC ALARM MODULE US 4012

Fully built & tested

only £10.95 + VAT

Adjustable range from 5ft. to 25ft.

A really effective fully built module containing both ultrasonic transmitter and receiver and circuitry for providing false alarm suppression. This module, together with a suitable 12V power supply and relay unit as shown, forms an effective though inexpensive intruder alarm. Supplied with comprehensive Data Sheet, it is easily mounted in a wide range of enclosures. A ready-drilled case and necessary hardware is available below.

DIGITAL VOLTMETER MODULE DVM 314

Fully built & tested

only £11.95 + VAT

- Positive & negative voltage with an FSD of 999mV which is easily extended
- Requires only single supply 7-12V
- High overall accuracy - 0.1% + 1 digit
- Large bright 0.43" LED displays
- Supplied with full applications data

With this fully built and calibrated module a wide range of accurate equipment such as multimeters, thermometers, battery indicators etc. can be constructed at a fraction of the cost of ready-made units. Full details are supplied for extending the voltage range, measuring current, resistance and temperature. Fully guaranteed, the unit has been supplied to electricity authorities, Government departments, etc.

Power Supply & Relay Units PS 4012 £4.25 + VAT

Hardware Kit HW 4012 £4.25 + VAT

Provides a stabilised 12V output and relay with 3A contacts. The unit is designed to operate one or two of the above ultrasonic units. Fully built and tested.

A suitable ready-drilled case with the various mounting pillars, mains switch socket and nuts and bolts. Designed to house the ultrasonic alarm module together with its power supply. Size: 153mm x 120mm x 45mm.

Siren Module SL 157 £2.95 + VAT

- * ACCESSORIES ***
- 3-position Key Switch for use with CA 1250 supplied with 2 keys £3.43
 - Magnetic switch (with magnet) £1.17
 - 5" Horn speaker for use with CA1250 and SL157 £4.95

Temperature Measurement Kit DT.10 £2.25 + VAT

Using the I.C. probe supplied, this kit provides a linear output of 10mV/°C over the temperature range from 10°C to +100°C. The unit is ideal for use in conjunction with the DVM module providing an accurate digital thermometer.

Power Supply PS.209 £4.95 + VAT

This fully built mains power supply provides two stabilised isolated outputs of 9V, 250mA each. The unit is ideally suited for operating the DVM at Temperature Measurement module.

Add VAT & 50p post and packing to all orders.
 Shop hours 9.00 - 5.30 p.m.
 (Wed. 9.00 - 1.00 p.m.)
 Units on demonstration - callers welcome, S.A.E. with all enquiries.

RISCOMP LIMITED
 Dept: ET1/12,
 21 Duke Street,
 Princes Risborough, Bucks.
 Princes Risborough (084 44) 6326

COMING SOON TO . . .

Hobby Electronics

THE HE DIGITESTER

A complete digital test system which will grow into a complete testing and breadboarding facility. The series commences with the description of our Chip Probe, a simple logic tester that can also stand alone as a handy test instrument.

SWITCHED MODE POWER SUPPLIES

A complete explanation with a useful easy-to-build project included! A must for CBer's and other users of mobile equipment.

CUMULATIVE INDEX, 1979-1982

Not only the best, but the whole of Hobby Electronics indexed for you in one issue (we're hoping it will cut down our mail!).

READER SURVEY, 1983

Yes, folks, once again it's the time of the year when WE ask YOU the questions. Come on, tell us what you think!

JFETS EXPLAINED

Often used in our projects, these devices are easily understood (which is why we use them).

Please reserve copies of the December issue of

**Hobby
Electronics**

for
Name

Address

.

.



**Hobby
Electronics**

**January issue on sale at
your newsagent
from 10th December .
Place your order now!**

Although these articles are being prepared for the next issue, circumstances may alter the final content.

Who but the people who made the micro possible
could help you understand it?

The Texas Instruments Electronic Library.

An in-depth series in understanding today's world of electronics.

The Understanding Electronics Series was specially developed and written to give you an in-depth knowledge of this world.

Each book is comprehensive, yet easy to understand. As informative for the electronics buff as for someone who's simply interested in what's going on today.

Together the library will give you the most complete range of titles available. Take advantage of our introductory offer and choose the book, or books you want from the titles below. You'll find whole new worlds of advanced technology unfolding before you.

Everything you've always wanted to know about:

1. Understanding Electronic Control of Energy Systems.

1st edition. Ref. LCB 6642. Covers motor, generator, power distribution, heating, air conditioning, internal combustion engine, solar and nuclear systems. *Softbound 272 pages. £3.95.*

2. Understanding Electronic Security Systems.

1st edition. Ref. LCB 720L A complete guide covering the basics of hard wired, photosensitive, infrared, ultrasonic and microwave systems and their use in different applications. *Softbound 128 pages. £3.95.*

3. Understanding Solid State Electronics.

3rd edition. Ref. LCC 336L The principles of solid state theory. It explains electrical movement, with intermediate tuition on the applications of solid state devices. *Softbound 282 pages. £3.95.*

4. Understanding Digital Electronics.

1st edition. Ref. LCB 331L Describes digital electronics in easy-to-follow stages. It covers the main families of digital integrated circuits and data processing systems. *Softbound 260 pages. £3.95.*

5. Understanding Microprocessors.

1st edition. Ref. LCB 4023. An in-depth look at the magic of the solid state chip. What they are, what they do. Applications of 8-bit and 16-bit microprocessors; and design from idea to hardware. *Softbound 288 pages. £3.95.*

6. Understanding Computer Science.

1st edition. Ref. LCB 547L This book tells you in everyday English how today's computer has been developed, what goes on inside it, and how you tell it what to do. *Softbound 278 pages. £3.95.*

7. Understanding Communications Systems.

1st edition. Ref. LCB 452L An overview of all types of electronic communications systems. *Softbound 282 pages. £3.95.*

8. Understanding Calculator Maths.

1st edition. Ref. LCB 332L Brings together the basic information - formulae, facts, and mathematical tools - you need to "unlock" the real power of the hand-held calculator. *Softbound 230 pages. £3.95.*

9. Understanding Optronics.

1st edition. Ref. LCB 5472. Optronics is the application of light and electronics to perform a wide range of useful tasks. From car headlights to missile guidance systems. *Softbound 270 pages. £3.95.*

10. Understanding Automotive Electronics.


1st edition. Ref. LCB 577L Learn how electronics is being applied to automobiles. How the basic mechanical, electrical and electronic functions and the new microprocessors and microcomputers are being applied in innovative ways for vehicle drive train control, motion control and instrumentation. *Softbound 288 pages. £3.95.*

How to order

Fill in the coupon below or if someone else has already used it, simply:

1. List reference numbers and quantities required.
2. Calculate total order value. Add £1.50 for postage and packing.
3. Send the list, plus your cheque payable to Texas Instruments Ltd, PO Box 50, Market Harborough, Leicestershire. Allow 30 days for delivery.

**TEXAS
INSTRUMENTS**

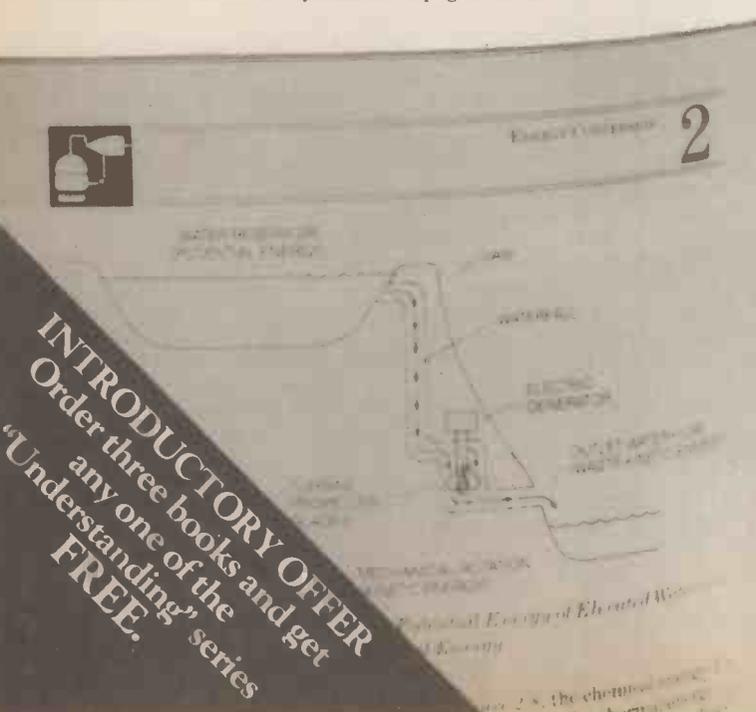

To: Texas Instruments Limited, PO Box 50, Market Harborough, Leics.
Please send me the following publications:

REFERENCE NO.	QTY.	REFERENCE NO.	QTY.
1.		7.	
2.		8.	
3.		9.	
4.		10.	
5.			
6.			

Free title choice: Understanding _____
I enclose a cheque for £ _____
Name _____
Company (if any) _____
Address _____

Registered office: Texas Instruments Ltd, Manton Lane, Bedford MK41 7PA.
Registered number: 574102 England.

Stereo Noise Gate

R.A. Penfold

Remove hiss and noise from your recordings!
Mono or stereo, our noise gate
deals with both.



Stereo Noise Gate

NOISE is present in every electronic circuit, and in audio circuits it results in the all too familiar background "hiss". Although modern electronics components have provided great improvements in noise performance in recent years, noise in audio circuits can still be very troublesome at times, and there can sometimes be a build-up of noise which results in a poor signal-to-noise ratio when using certain combinations of equipment. Re-recording material can also lead to a build-up of noise.

Two useful ways of combatting audio noise are to use either a noise gate or an expander. These two devices are very similar, but there is a very important distinction between them. A noise gate is rather like an automatic switch which normally allows the input signal to pass straight through, but cuts off the output when noise *only* is present at the input. Noise is most obtrusive during pauses in the main signal, and a noise gate can therefore give a large subjective improvement in performance.

An expander permits low level signals to pass normally but at medium and high signal levels, it gives a progressive boost to the processed signal. Thus the noise level remains the

same but the maximum volume level is increased; or, the noise level can be reduced with the maximum volume level remaining the same; or, a combination of the two, as desired. A simple volume expander was described in the January 1982 issue of *Hobby Electronics*.

Whether a noise gate or an expander is the best choice depends upon the particular circumstances in which the equipment will be used and, to some extent, on personal preferences. A disadvantage of an expander is that it alters the dynamic levels of the processed signal, whereas a noise gate simply cuts off the noise during breaks in the signal. A noise gate is therefore normally preferable for use where changes in dynamic level are undesirable. However, a gate is likely to be less satisfactory when the wanted signal may, at times, be almost lost in the noise, since it is then possible that the gate might cut off the signal. A noise gate is of most use when there is a fairly strong noise level, but the wanted signal is usually significantly above this level.

The unit described here is a stereo noise gate, although by using only one channel it can obviously be used in mono. Although expanders normally process each stereo channel separately

it is preferable for a stereo gate circuit to switch the two channels in unison, as it can be rather disturbing if one channel cuts out while the other is still present! This circuit therefore switches the two channels on and off simultaneously — see *How It Works* for an over-view of the system.

The Circuit

The full circuit diagram of the Stereo Noise Gate is shown in *Figure 1*. It is based on an LM13600N integrated circuit, which is a dual operational transconductance amplifier. An operational transconductance amplifier has features common with an ordinary operational amplifier, but there are also a number of important differences — a transconductance amplifier provides an output current (rather than an output voltage), governed by the differential input voltage, and it also has an additional input which enables the gain of the amplifier to be controlled over a wide range, from zero up to about 20 dB. Note that a gain of less than one is equivalent to attenuation!

In order to make a transconductance amplifier operate as a voltage amplifier, it is merely necessary to add a load resistor at the output; R20 is the load resistor for IC3a while R24 is the load for IC3b. The current flow into the

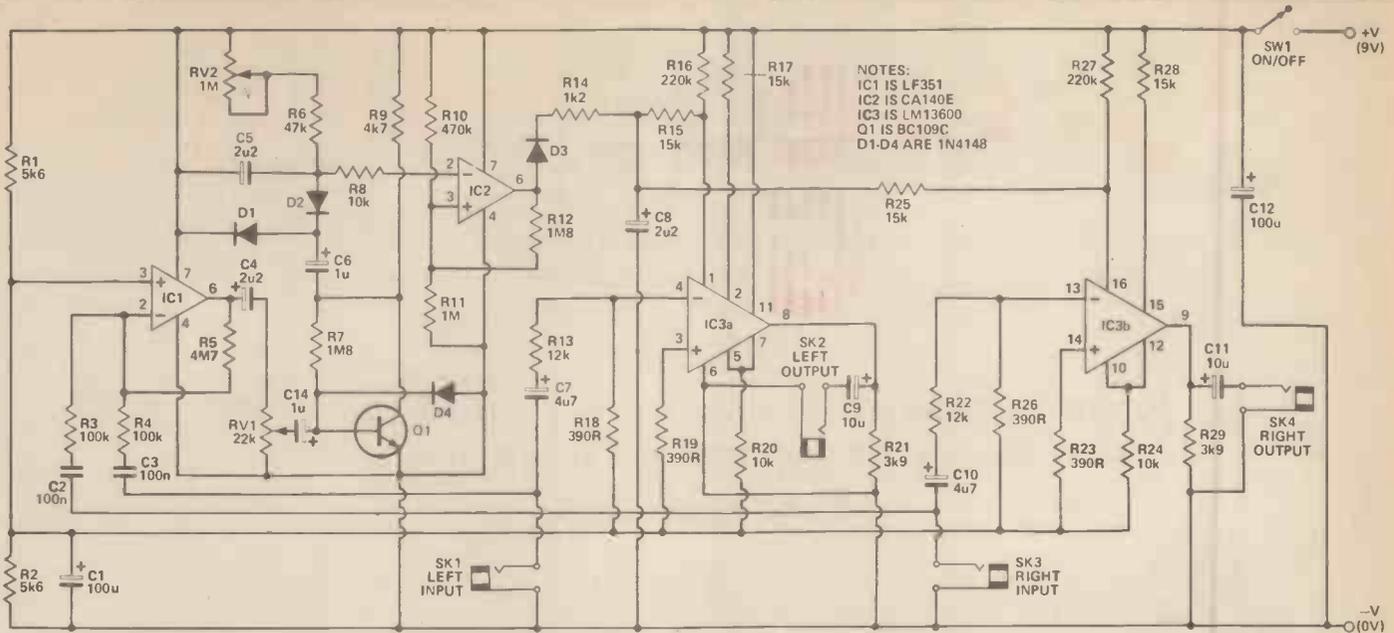


Figure 1. Circuit diagram of the Stereo Noise Gate. Note that both channels are included.

control input, rather than voltage, determines the gain of the amplifier. This is achieved by simply adding resistors (R15 and R25) in series with each control input so that the current flow is proportional to the applied voltage. Resistors R16 and R27 apply a small bias current to the control inputs; this gives the circuit about -20 dB of gain (ie, 20 dB attenuation) in the high attenuation mode, rather than completely cutting off the output signal, which usually gives more satisfactory results. The circuit can be made to operate as a true gate, if preferred, by simply omitting R16 and R27.

The LM13600N incorporates two Darlington Pair output stages which are used as emitter follower buffer stages, to give the VCAs a low output

Figure 2. Pin configuration for the LM13600 dual transconductance op-amp.

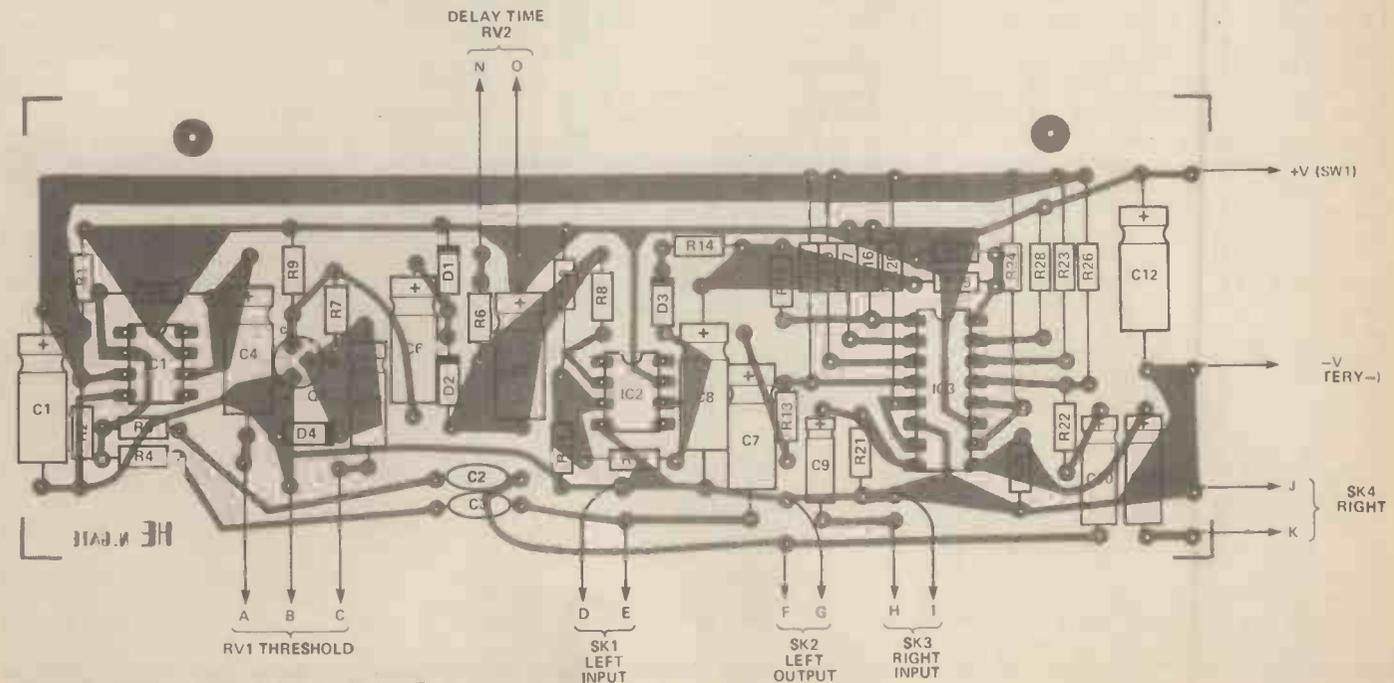
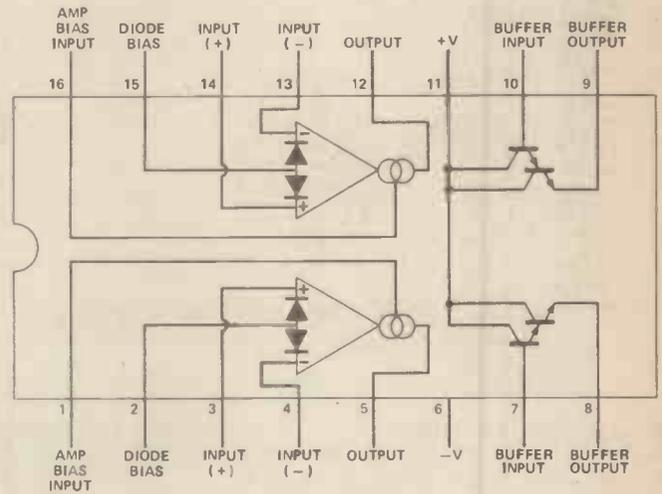


Figure 3. Overlay diagram for the Noise Gate.

Project

impedance. R21 and R29 are the discrete load resistors for these stages. The LM13600N has 'linearizing diodes', which enable a higher input signal level to be handled for a given distortion level, and these diodes are given the appropriate bias by R17 and R28.

In order to operate as a voltage controlled amplifier, a trans-conductance amplifier must be used open loop (ie, without any negative feedback). R1, R2, and C1 form a centre tap on the supply rails and the inputs of the two transconductance amplifiers IC3a, b, biased to this voltage by R18,19,23 and 26. R13 and R22 are used to reduce the voltage gain through each section of the unit to about unity (with a high control voltage), and also to boost the input impedance to a little over 12k.

The mixer stage is a conventional operational amplifier, IC1, and gives a voltage gain of about 47. Threshold control RV1 is a volume control type attenuator, and the output from this is coupled to a high gain common emitter amplifier based on Q1; the combined gain of Q1 and IC1 is needed in order to boost weak input signals to a high enough level to drive the subsequent circuitry.

The output of Q1 is coupled by C6 to a simple rectifier and smoothing circuit (D1, D2, C5 and R8) and RV2 controls the decay time of this circuit. Op-amp IC2 is used as a simple inverting trigger circuit, with positive feedback and hysteresis provided by R12;

'hysteresis' simply means that the input voltage at which the output triggers to the high state is lower than that at which it triggers back to the low state. This prevents instability when the input voltage is close to the switching threshold levels. D3 and R14 are used at the output of the trigger to very slightly slow the rise-time of the control

voltage, and to provide a slightly larger slowing of the fall-time. This prevents "clicks" from being introduced at the output as the gate changes state.

Construction

An aluminium and steel instrument case measuring about 152 x 114 x 44 mm is used to house this project — it is about


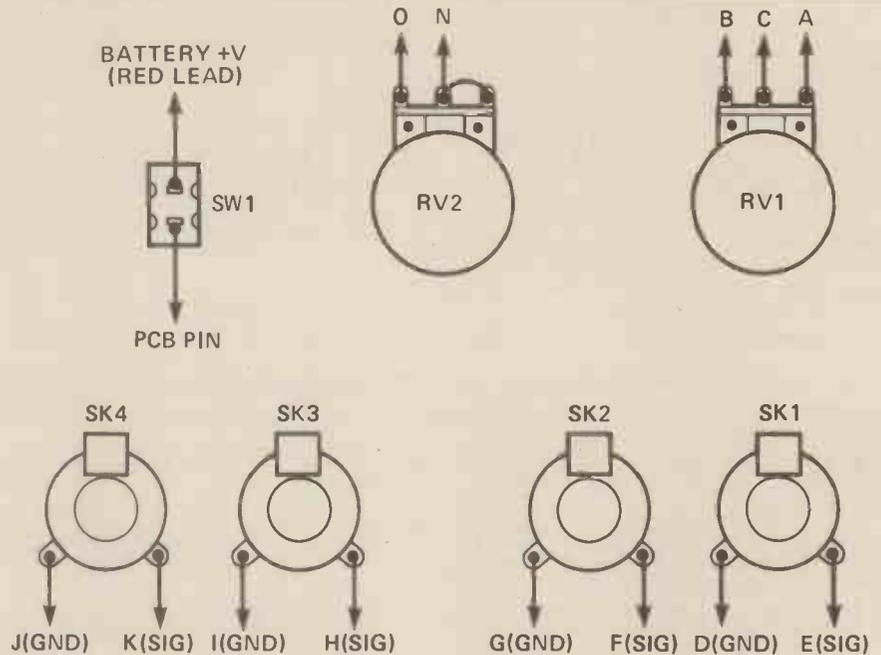


Figure 4. The internal wiring and connections inside the case of the Noise Gate.

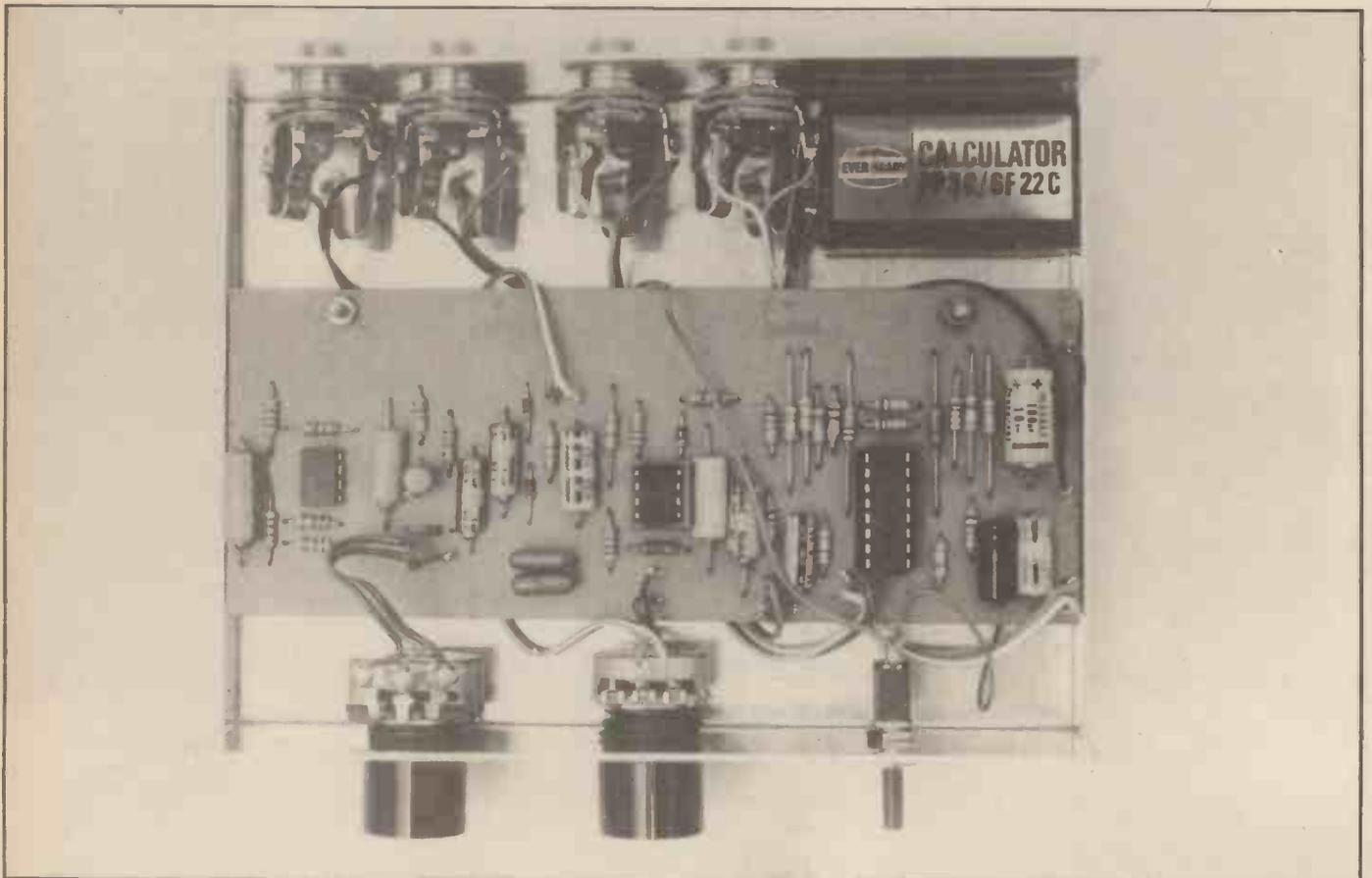

the smallest case that could be used to accommodate all the parts. The three controls are mounted on the front panel and four sockets are fitted on the rear panel of the case.

Apart from the battery, all the other components are mounted on the printed circuit board, and this is detailed in Figure 3. As IC2 is a MOS device, it should be fitted in an 8 pin DIL IC socket and the normal MOS handling precautions should be observed. Use Veropins where connections to off-board components will eventually be made.

The completed board is mounted on the base panel of the case using 6BA fixings, including 6.3 mm spacers to hold the connections on the underside of the board clear of the metal case. The unit is then completed by adding the point-to-point wiring, illustrated in Figure 4. Ordinary PVC covered multistrand connecting wire is used here; it is not necessary to use screened leads.

In Use

The unit is intended for use with a high level signal and can take inputs of 2 volts RMS or so without serious distortion occurring. The threshold voltage at which the gate switches to the unity gain (zero attenuation) state can be varied from about 1 mV RMS (with RV1 set fully clockwise) to about 70 mV RMS. The best setting is likely to be such that the noise signal alone is not quite sufficient to trigger the circuit to the zero attenuation state, but it is worthwhile experimenting a little to find

the setting which gives the best subjective results.

The circuit will respond very rapidly to an input signal (fast attack), but the decay — the delay between the cessation of the main signal and the gate switching to the high attenuation state — can be varied from less than a

tenth of a second to more than two seconds. A fast decay time will often give best results, but it might sometimes be found that the gate tends to switch back and forth between the two states fairly rapidly; a slightly longer decay time should eliminate this problem.

Parts List

RESISTORS

(All 1/4 watt 5% carbon)

R1,2	5k6
R3,4	100k
R5	4M7
R6	47k
R7,12	1M8
R8,20,24	10k
R9	4k7
R10	470k
R11	1M
R13,22	12k
R14	1k2
R15,17,25,28	15k
R16,27	220k
R18,19,23,26	390R
R21,29	3k9

POTENTIOMETERS

RV1	22k
		log carbon
RV2	1M
		linear carbon

CAPACITORS (All axial electrolytics unless noted)

C1,12	100u 10V
C2,3	100n
		C280 polyester

C4,5,8	2u2 63V
C6	1u 63V
C7,10	4u7 63V
C9,11	10u 25V

SEMICONDUCTORS

IC1	LF351
		JFET op-amp
IC2	3140E
		MOSFET op-amp
IC3	LM13600N
		dual transconductance amp
Q1	BC109C
		silicon NPN transistor
D1-4	1N4148
		silicon signal diode

MISCELLANEOUS

SK1-4	1/4" jack socket
		standard metal chassis type
SW1	SPST
		miniature toggle switch
Case	(see Buylines); PCB; 6BA	nuts and bolts; Veropins; IC
		sockets; knobs (2); PP3 battery,
		clip, wire, solder etc.

BUYLINES page 34


How It Works

THIS Noise Gate design is a stereo type which uses a separate VCA (voltage-controlled amplifier) to process each channel. With a low control voltage, each VCA gives a substantial amount of attenuation (about 20 dB — a 90% reduction in the signal voltage, in other words). A high control voltage gives unity gain (zero attenuation) through each VCA and the input signal is effectively allowed to pass straight through.

Automatic switching — to zero attenuation in the presence of a proper

input signal but high attenuation with only noise applied to the input — is achieved by first mixing the two input signals and then amplifying them. The amplified signal is then applied to a rectifier and smoothing circuit to produce a DC output level proportional to the strength of the combined input signals. this voltage is fed to a trigger circuit which has a high output voltage if the input voltage is above a certain threshold level, and a low voltage if it is not; this is the control voltage for the VCAs.

The circuit is adjusted so that with only background noise present at the input, the voltage fed to the trigger circuit is below the threshold voltage and the VCAs give a high attenuation level. With a high input signal, in addition to noise, the input voltage to the trigger circuit goes above the threshold level and the VCAs 'open' producing zero attenuation. Thus the required automatic attenuation of the noise-only input signal is obtained.

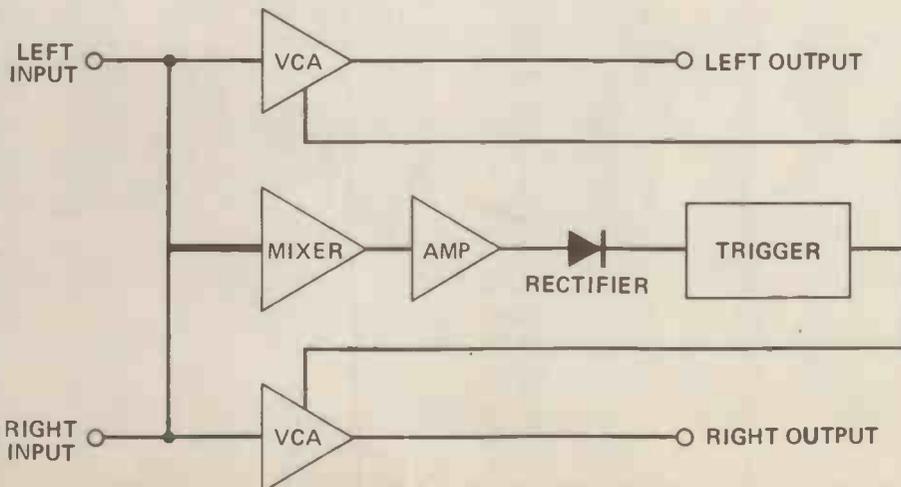

HE

CRICKLEWOOD ELECTRONICS LTD

40 Cricklewood Broadway, London NW2 3ET. tel 01 452 0161 tdx 914977

This is a small list from our vast stocks. Full price list free on request. You may order by phone quoting Access, Visa or American Express no., or by normal mail order. Callers welcome. All in stock items (95% ex stock) go by same day. Please add 15% VAT & 70p p&p. Govt Depts, schools, etc. orders welcome. Overseas orders no VAT but allow extra p&p. Qty discounts negotiable.

CRICKLEWOOD - STOCKING PARTS OTHER STORES CANNOT REACH!

SUPERIOR QUALITY CARBON FILM RESISTORS, HI STAB LOW NOISE	Rechargeable Batteries: Guaranteed minimum 500 charges	TRANSISTORS Probably the largest retail variety you don't see what you want please phone or write this is not a full list	2N5401 35p 2N5415 1.10 2N5418 1.54 2N5447 16p 2N5448 19p 2N5449 21p 2N5450 23p 2N5451 25p 2N5452 29p 2N5458 29p 2N5459 29p 2N5460 29p 2N5461 29p 2N5462 29p 2N5463 29p 2N5464 29p 2N5465 29p 2N5466 29p 2N5467 29p 2N5468 29p 2N5469 29p 2N5470 29p 2N5471 29p 2N5472 29p 2N5473 29p 2N5474 29p 2N5475 29p 2N5476 29p 2N5477 29p 2N5478 29p 2N5479 29p 2N5480 29p 2N5481 29p 2N5482 29p 2N5483 29p 2N5484 29p 2N5485 29p 2N5486 29p 2N5487 29p 2N5488 29p 2N5489 29p 2N5490 29p 2N5491 29p 2N5492 29p 2N5493 29p 2N5494 29p 2N5495 29p 2N5496 29p 2N5497 29p 2N5498 29p 2N5499 29p 2N5500 29p	1N4148 1.20 1N4149 1.20 1N4150 1.20 1N4151 1.20 1N4152 1.20 1N4153 1.20 1N4154 1.20 1N4155 1.20 1N4156 1.20 1N4157 1.20 1N4158 1.20 1N4159 1.20 1N4160 1.20 1N4161 1.20 1N4162 1.20 1N4163 1.20 1N4164 1.20 1N4165 1.20 1N4166 1.20 1N4167 1.20 1N4168 1.20 1N4169 1.20 1N4170 1.20 1N4171 1.20 1N4172 1.20 1N4173 1.20 1N4174 1.20 1N4175 1.20 1N4176 1.20 1N4177 1.20 1N4178 1.20 1N4179 1.20 1N4180 1.20 1N4181 1.20 1N4182 1.20 1N4183 1.20 1N4184 1.20 1N4185 1.20 1N4186 1.20 1N4187 1.20 1N4188 1.20 1N4189 1.20 1N4190 1.20 1N4191 1.20 1N4192 1.20 1N4193 1.20 1N4194 1.20 1N4195 1.20 1N4196 1.20 1N4197 1.20 1N4198 1.20 1N4199 1.20 1N4200 1.20
--	--	--	--	---

METAL OXIDE/FILM RESISTORS	Chargers	TYPE H: Adjustable to 8	2N6130 30p 2N6131 30p 2N6132 30p 2N6199 30p 2N6200 30p	TYPE H: Adjustable to 8 of any HP type available for 55p	2N6201 30p 2N6202 30p 2N6203 30p 2N6299 30p 2N6300 30p
-----------------------------------	----------	-------------------------	--	--	--

LOW OHMIC VALUE RESISTORS	TYPE A: HP7 Up to 4 in a time! £5.85	TYPE B: GRAPHIC PROCESSORS	2N6301 30p 2N6302 30p 2N6303 30p 2N6399 30p 2N6400 30p	TYPE A: HP7 Up to 4 in a time! £5.85	2N6401 30p 2N6402 30p 2N6403 30p 2N6499 30p 2N6500 30p
----------------------------------	--------------------------------------	----------------------------	--	--------------------------------------	--

WIREWOUND RESISTORS 5%	TYPE A: HP7 Up to 4 in a time! £5.85	TYPE B: GRAPHIC PROCESSORS	2N6501 30p 2N6502 30p 2N6503 30p 2N6599 30p 2N6600 30p	TYPE A: HP7 Up to 4 in a time! £5.85	2N6601 30p 2N6602 30p 2N6603 30p 2N6699 30p 2N6700 30p
-------------------------------	--------------------------------------	----------------------------	--	--------------------------------------	--

LOW RESISTANCE ROTARY POTS	TYPE A: HP7 Up to 4 in a time! £5.85	TYPE B: GRAPHIC PROCESSORS	2N6701 30p 2N6702 30p 2N6703 30p 2N6799 30p 2N6800 30p	TYPE A: HP7 Up to 4 in a time! £5.85	2N6801 30p 2N6802 30p 2N6803 30p 2N6899 30p 2N6900 30p
-----------------------------------	--------------------------------------	----------------------------	--	--------------------------------------	--

LOW RESISTANCE ROTARY POTS	TYPE A: HP7 Up to 4 in a time! £5.85	TYPE B: GRAPHIC PROCESSORS	2N6901 30p 2N6902 30p 2N6903 30p 2N6904 30p 2N6905 30p 2N6906 30p 2N6907 30p 2N6908 30p 2N6909 30p 2N6910 30p 2N6911 30p 2N6912 30p 2N6913 30p 2N6914 30p 2N6915 30p 2N6916 30p 2N6917 30p 2N6918 30p 2N6919 30p 2N6920 30p 2N6921 30p 2N6922 30p 2N6923 30p 2N6924 30p 2N6925 30p 2N6926 30p 2N6927 30p 2N6928 30p 2N6929 30p 2N6930 30p 2N6931 30p 2N6932 30p 2N6933 30p 2N6934 30p 2N6935 30p 2N6936 30p 2N6937 30p 2N6938 30p 2N6939 30p 2N6940 30p 2N6941 30p 2N6942 30p 2N6943 30p 2N6944 30p 2N6945 30p 2N6946 30p 2N6947 30p 2N6948 30p 2N6949 30p 2N6950 30p 2N6951 30p 2N6952 30p 2N6953 30p 2N6954 30p 2N6955 30p 2N6956 30p 2N6957 30p 2N6958 30p 2N6959 30p 2N6960 30p 2N6961 30p 2N6962 30p 2N6963 30p 2N6964 30p 2N6965 3
-----------------------------------	--------------------------------------	----------------------------	--

HE TV Amp

N.D.N. Belham



Specially designed to let Grandad hear the telly clearly without annoying the rest of the household, it will also double-up as a general-purpose bench amplifier.

ALTHOUGH we loved the old man and owed him a lot, Grandad was becoming a pest with his complaints that he couldn't hear the TV sound. For a while we did our best, though the volume was painful, but something obviously had to be done about it — if not for ourselves, then certainly for the sake of the neighbours! Fortunately our TV set is a modern one, with two headphone sockets built in, so when we bought him a pair of 'phones, we thought the problem had been solved — but it wasn't long before he refused to wear them because he didn't like the voices "inside his head" when they should have been coming from the screen. Anyway they became too


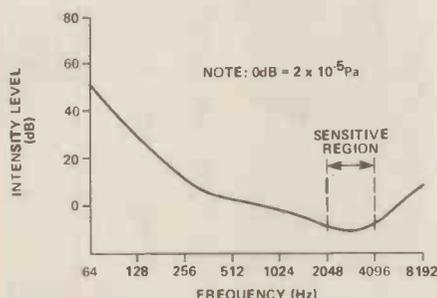


Figure 1. The response curve for the average person's sense of hearing (after Fletcher and Muson).

uncomfortable for him, after an hour or two. Another solution had to be found.

Grandad wasn't really deaf; he did not need a hearing aid, as he could carry on a normal conversation, but he did find it difficult to follow conversations on the telly. Strangely, it seemed to us, he preferred the sound from a small portable set to the one with full range hi-fi reproduction. Indeed, several factors seemed to be involved, some of a general nature and some peculiar to the elderly.

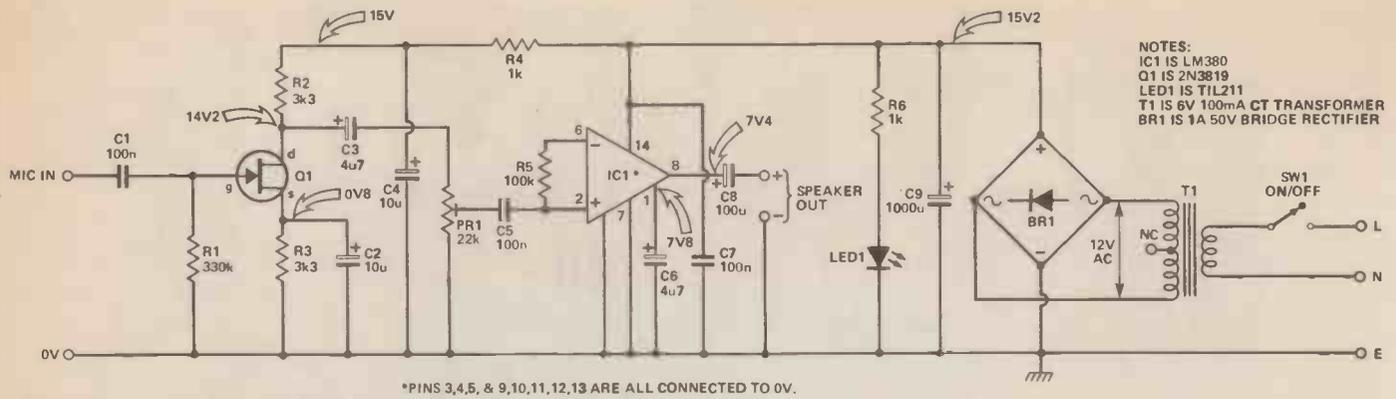The diagram of Figure 1 shows the average frequency vs intensity response for an average person's hearing. Clearly, the energy required for a sound to be just audible varies greatly



NOTES:
 IC1 IS LM380
 Q1 IS 2N3819
 LED1 IS TIL211
 T1 IS 6V 100mA CT TRANSFORMER
 BR1 IS 1A 50V BRIDGE RECTIFIER

Figure 2. The circuit; the input is high impedance and will accept any audio input of around 10 to 50 mV.

Parts List

RESISTORS

(All 1/4 watt 5% carbon)

R1	330k
R2,3	3k3
R4,6	1k
R5	100k

POTENTIOMETERS

PR1	22k miniature cermet preset
-----	--------------------------------

CAPACITORS

(All radial electrolytic unless stated)

C1,5,7	100n disc ceramic
C2,4	10u 16V
C3,6	4u7 35V
C8	100u 16V
C9	1000u 25V axial electrolytic

SEMICONDUCTORS

IC1	LM380 power amplifier
Q1	2N3819 FET transistor
BR1	50V 1A bridge rectifier
LED1	TIL211 0.2" green LED

MISCELLANEOUS

SW1	SPST mains toggle switch
T1	6-0-6 1.2VA Crystal microphone; centre-tapped transformer; speaker (see Buylines); Mains 'P' clip; mains lead and plug (2A fuse); case (see Buylines); 1/4" jack socket (plastic); LED bezel; PCB, wire, solder etc.

BUYLINES page 34

with frequency; very little sound energy is needed if it is at the right pitch, and the frequency range 2000 Hz to 4000 Hz is where the average ear is most sensitive.

Anyone who has worked in long range radio communication will know that restricting the audio bandwidth to between 500 Hz and 4000 Hz greatly improves the clarity of the transmission (especially in adverse atmospheric conditions), and this seems to indicate that, for speech, most of the essential information is contained in that frequency range.

Another factor, it seemed, was that the elderly find it difficult to concentrate on more than one sound at a time. They are easily put off by unwanted 'noise' — this is as much to do with the way in which sound is interpreted (psychoacoustics) as with


the sense of hearing. Hi-fi-quality sound, with its extended frequency range, produces too much 'noise' at the upper and lower limits of hearing which, for the elderly, masks the information in the mid-range frequencies. So, simply turning up the TV sound was not the solution because the unwanted frequencies are also boosted (this, also is why deaf aids are personally tailored to an individual's frequency response curve).

Grandad's Specifications

So, with these points in mind, we were able to write a specification for Grandad's TV amplifier:

- The output frequency must be tailored to peak at about 2000 Hz, with little response below 500 Hz or above 4000 Hz.
 - The output should be directional, so that it could be directed at Grandad, not at us!
 - The output level to be sufficient to allow it to be placed near the TV screen, to give it realistic 'TV sound'.
- The first step was to select a small loudspeaker, which automatically restricted the frequency response to the specified limits and also produced a degree of directivity. Unfortunately, the power available from a headphone socket is not sufficient to drive a loudspeaker, so an amplifier had to be designed and constructed. A single integrated amplifier, the LM380, proved adequate for the job, especially as it needs very few external components.

The price of batteries being what it is (expensive!), a simple mains power supply was built into the unit, together with an on/off switch and a LED power-on indicator. Since most TV sets do not have a headphone output, the circuit was adapted for general use by incorporating a microphone input. A crystal mic (use a short lead, because of its high impedance) is quite adequate, or a more expensive electret type can be used with a longer lead, if necessary. Dynamic microphones contain a coil which will respond to the varying magnetic field produced by the video scan, so they cannot be used here.

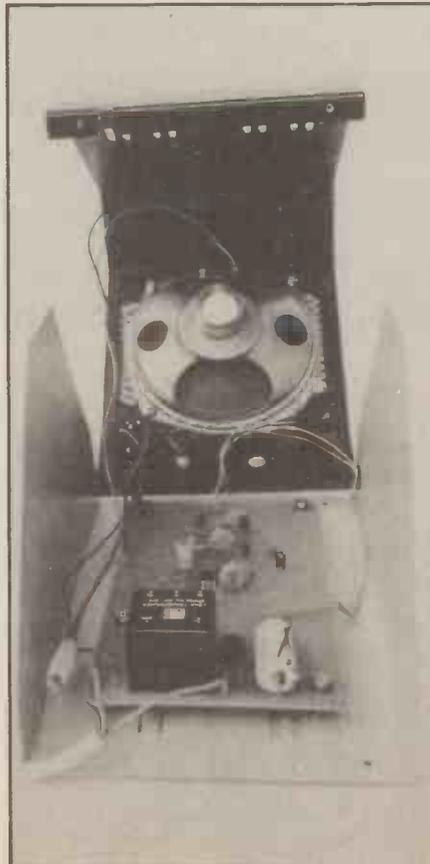

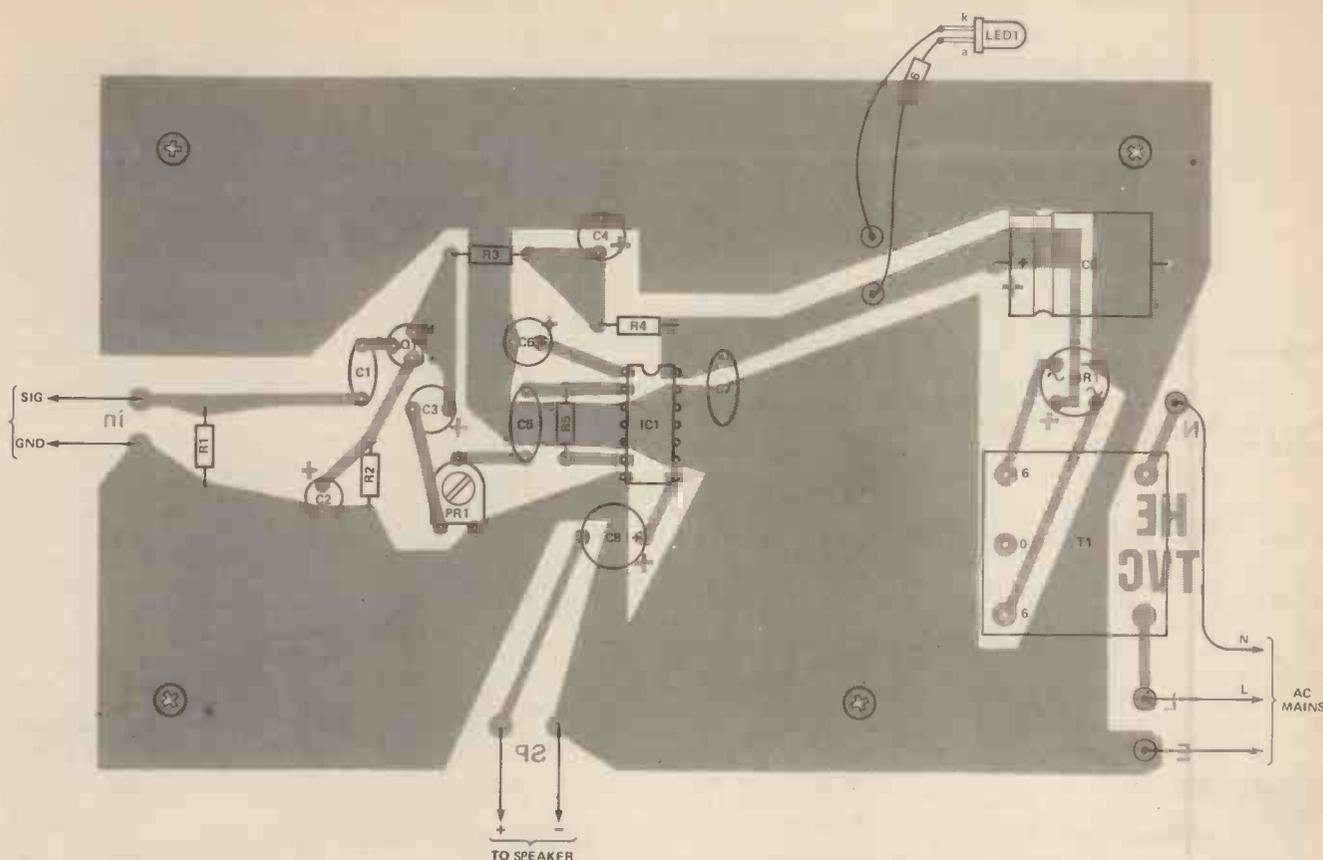


Figure 3. The PCB layout, viewed from the component side. Large areas of copper have been left to serve as a heatsink for the LM380 amplifier.

Granddad's Circuit

The microphone will give an output of a few tens of millivolts when placed fairly close to the loudspeaker with the volume control set for normal listening, and this is fed via coupling capacitor C1 to a FET amplifier, Q1. This provides the high impedance input required for the microphone and a voltage gain of between five and six.

A 4u7 capacitor, C3, couples the output of the FET stage to the preset volume control PR1, and C5 couples the signal to the inputs of IC1, the LM380 amplifier. This has an internally fixed gain of 34 dB (50Vout/Vin), but it is reduced to 20Vout/Vin by using a 'common mode' input, where part of the input voltage is coupled to the inverting input of the amplifier via the 100k resistor, R5.

Capacitor C6, connected to the bypass pin (pin 1) of IC1 de-couples the internal bias of the amp, preventing AC ripple on the output, while C7 performs the same function on the supply line.

The output is fed to the speaker via C8; together, C8 and the speaker voice coil impedance form a high pass filter, rolling off the response below 200 Hz when an 8R speaker is used. The speaker itself is the main factor in shaping the frequency response; by choosing a small 4" diameter unit and mounting it in an unsealed box, most of the lower frequencies are attenuated,

while the mechanical properties of the cone ensure that frequencies above about 4 kHz are also 'lost'.

Finally, the amp is powered from a simple DC supply derived from a 6V/100mA centre-tapped transformer and a diode bridge; the ripple voltage is filtered out by C9. LED 1 is included to provide 'power-on' indication, with R6 to limit the current through the LED.

Construction

In order to improve the stability of the amplifier (reducing the chance of it becoming an oscillator), it is mounted on a PCB which has a very large area of copper. The unused pins of the IC are soldered directly to these areas — do not use an IC socket in this project! This method also provides an effective heat sink.

The layout shown in Figure 3 is designed for a preset volume control to be mounted on the PCB; should a full-sized pot be required as a front panel volume control, leads must be taken from the PCB to the potentiometer solder tags. The choice of preset or variable volume control is left to the constructor — perhaps the solution depends on how many "knob-twiddlers" there are in the house!

Granddad's TV Amp can be built into any enclosure large enough to hold the components, including the speaker. Our prototype was cased in a rather

classy custom-built box from Newrad Instrument Cases Ltd (see Buylines for the ordering details); this also has a pre-drilled hole for a panel-mounted volume control.

Operation

The problem with any microphone-amplifying system is the risk of acoustic feedback, which will occur whenever the mic is picking up sound from the loudspeaker. Steps must be taken to prevent this from happening!

First, the best position for the TV Amp is on the floor, or on a low table in front of the TV set, so that the sound is coming from the same direction. Second, the mic should be placed as close to the TV speaker as possible, but without actually touching it. Then, the preset or volume control must be adjusted so that, at normal listening levels, there is no trace of whistling or "howl round" from the TV Amp.

In most cases, this arrangement will be quite satisfactory though for very deaf people, it may be necessary to place the Amp closer to the listener and to use a longer mic lead. If such is the case, a crystal microphone should not be used with a lead longer than about three feet.

CASIO MAGIC from TEMPUS

WORLD'S FIRST THERMOMETER WATCH

NEW


TS-1000
ONLY £24.95

- 100m water resist
- Full display
- 12/24 hour
- Thermometer
- Thermo alarm
- Daily alarm
- Time signal
- Pro. stopwatch
- World time
- Resin case



WORLD'S MOST VERSATILE WATCHES

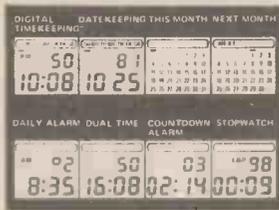10 alternative displays –
over 60 useful functions



AX-250
(left)
£21.50

AX-5
Resin
£19.95



WATER RESISTANT

Rugged, go anywhere sports watches. All have a full display of time and auto calendar. Alarm and selectable half-hourly time signal. Countdown alarm timer with repeat memory function, ideal for dinghy racing. Professional 1/100 second stopwatch. Time is always on display, regardless of display mode. Amazing 5/7 year lithium battery life. 12/24 hour display.

Except for the W-35, the stainless steel case watches have a protective black bezel. (2-450, W-450C).

50 metre water resistant



W-23
£14.95



W-24
£12.95

50m W/R



W-35
£19.95



W-300
£17.95

100m W/R



W-450
£22.95



W-450C
£19.95

Please also the J-30 under Jogging watches.

We also stock Citizen watches and Casio, Citizen and Seiko Divers watches.

IF YOU SEE A BETTER OFFER WE WILL BEAT IT

ANALOG/DIGITAL

Analog time plus 12/24 hour digital dual time, calendar, alarm, time signal, pro stopwatch.

AA-86 LCD hands. Also has C/D alarm timer £19.95

AQ-101 True analog hands, plus date memory £39.95

GAME WATCHES

Calendar, alarm, time signal, pro. stopwatch

NEW

GOLF WATCH
CC-9 £17.95

When playing real golf

Counts strokes at each hole. Totals strokes over 9 holes.

When playing Game Par for each of 9 holes.

Distance from hole indicator. Select golf club. Select direction out of bounds. Stroke counter. Memorises lowest score.



RESIN

GM-30
£19.95



GM-40
£19.95



GM-30 Destroyer/submarine sea battle game.

GM-40 Catch blocks from UFO and build pyramid.

GAME/CALCULATOR WATCHES

Calendar, alarm, time signal, pro. stopwatch.

Popular DIGITAL INVADER game



CA-86
Resin
£19.95



CA-851
£29.95

ULTRA SLIM CALCULATOR WATCH
CS-821 Specifications as CA-851, below centre, but without the game function. Only 6.6mm thick £24.95

MULTI-ALARM WATCHES

Daily alarm with pre-alarm; daily alarm with post-alarm; weekly alarm (or extra daily alarm); hourly time signal; Calendar; pro. stopwatch.



CA-951
£29.95



MM-400
£29.95

CA-951 Calculator. 2 melody alarms.

CA-95 Resin version of CA-951 £19.95

MM-400 6 melodies. Monthly alarm or extra daily alarm. Dual time. Time is always on display.

JOGGING WATCHES

Calendar, alarm, time signal, pro. stopwatch. Pacer signal for jogging and rhythmic sports.



J-30
£12.95



J-50
£15.95



J-100
£19.95

J-30 50 metre water resistant. Countdown alarm timer. Input data: Pacer signals. Output data: Elapsed time. 37.7 x 31.4 x 7.6mm thick.

J-50 Countdown alarm timer. Input data: Pacer signals, length of stride. Output data: Elapsed time, distance covered.

J-100 as J-50 but with calculator function instead of countdown alarm timer.

STANDARD WATCHES

Calendar, alarm, time signal, dual time, 1/10 second stopwatch.



F-85
Resin
£7.95



A-656
£9.95

VALUE FOR MONEY GIFTS

FREE ACCESSORIES WORTH 10%
of price on request with all
CASIOTONE KEYBOARDS
The world's fastest selling keyboards

GENERAL SPECIFICATIONS

All Casiotone keyboards (except VL-Tones) are polyphonic — up to 8 notes can be played simultaneously. They all have an integral amplifier and loudspeaker, plus output jacks for headphones and external amplification.

DIGITAL SYNTHESISER

CT-1000P



£325

A RUNAWAY SUCCESS ALREADY


10 preset voices and 1,000 switchable sounds, with a protected memory for your 10 favourites. 5-octave split keyboard; programmable arpeggio/real time sequencer; transposition. 4½ x 36 x 14½ inches. 22.5lbs.

BAR-CODE PROGRAMMABLE

The 345 (max) note steps and 201 (max) chord steps can be programmed by both Casio bar-coded music scores and/or manual entry via the keyboard.

The Auto Play function, One-Key-Play function and Melody Guide (lights above the keyboard show you the next note to play), can teach you to play your programmed selection. "One of the finest teaching aids so far developed." E&MM.

CT-701

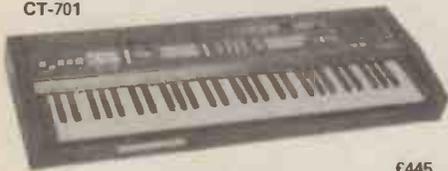

£445

5 octave, split keyboard, 20 preset sounds with variable vibrato and sustain. Fingered or auto chords with bass and arpeggio. 16 rhythm accompaniments with fill-in. Two sound effects. 5 x 37½ x 13½ inches. 27.6lbs.

MINI-PROGRAMMABLE

MT-70



£199

A portable mini keyboard version of the CT-701. 4 octave (not split) keyboard. 10 rhythm accompaniments. Without the two sound effects, it is otherwise very similar to the CT-701. Battery or mains powered, with optional mains adaptor. 2½ x 25 x 7½ inches. 6lbs.

PORTABLE 4 OCTAVE EASY-PLAY

MT-60



£149

25 voices with sustain and vibrato. 8 rhythm accompaniments with 'Intro/fill-in' function. Easy-play auto chords, bass and arpeggio. 2½ x 25 x 7½ inches. 5.5lbs. Battery or mains.

OTHER CASIOTONES

CT-403 £275, MT-40 £99, MT-31 £69, VL-5 £79.95, VL-1 £35.95, VL-10 £26.95.

Price includes VAT, P&P. Delivery normally by return, subject to availability. Send cheques, PO, or phone your ACCESS/VISA number to:

TEMPUS

Dept HE, 38 Burleigh Street,
Cambridge CB1 1DG
Telephone 0223 312866

**FREE 1982/3 CATALOGUE
AVAILABLE ON REQUEST**
Don't forget —
**IF YOU SEE A BETTER OFFER WE
WILL BEAT IT!**

ELECTRONIC GAMES



**CG-100
Space Shuttle
£12.95**



**CG-20
Money & Bomb
£12.95**

CG-10 and CG-20 are powered by solar cells and do not require batteries. Two very skilful games.

**BG-20 Boxing Game
£16.95**



A new version of the very successful BG-15. Now has a full screen with the calculator at the side. Clock and alarm functions.

CALCULATOR GAMES



**MG-880 £10.95
Digital Space Invaders**

MG-885


**MG-777
£14.95**

MG-777 3 games — A speed game, a game of skill and a game of chance. Built-in clock function. £14.95
MG-888 (not shown) compendium of 3 games £10.95

ALARM CLOCK COMPENDIUMS

BG-15 Boxing Game. Clock, alarm, calculator £14.95
FT-7 Fortune Teller, Matchmaker, Calendar £14.95
BQ-1100 Biotelor Alarm clock, calendar £16.95

MELODY ALARM CLOCK CALCULATORS

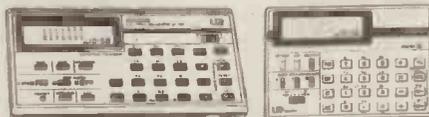

UC-365 £19.95

UC-360 £19.95

3 melodies, universal calendar, date memories, 2 date alarms, daily alarm, countdown alarm/stopwatch, time memory. UC-365 wallet size. UC-360 card size.

PORTABLE COMPUTERS

Details on request

BASIC FOR BEGINNERS

**CASIO
PB-100**
Learn As
You Go
£69.95



Now you can enter the exciting new world of computers with this easy to understand system.

FX-801P Casio's latest masterpiece. A high speed computer with integral micro-cassette data control and hard copy printer monitoring £349
FX-700P NEW scientific QWERTY computer £79.95
FX-702P The established favourite £79.95
SHARP PC-1500 BUSINESS COMPUTER £169.95

SCIENTIFIC CALCULATORS



Dims: 19 x 76.5 x 149mm
FX-78d, 23f, (f3) £9.95
FX-100 10d, 42f, SD, R/P, (f6) £14.95



Wallet size

FX-550 10d, 48f, SD, R/P, (f6) £15.95

FX-900 8d, 41f, SD, R/P, (f15), b £17.95

FX-950 10d, 49f, SD, R/P, (f15), £19.95

H, b SOLAR

FX-8100 8+2d, 46f, SD, R/P, (f5), H, b 1 year. Clock, calendar, 1/100 stopwatch, alarm, hourly chimes and 2 countdown alarms. Wallet size £19.95

PROGRAMMABLE SCIENTIFICS

Wallet size, with wallet. Non volatile memory
FX-3600P 10+2d, 50f, SD, R/P, (f18), Integrals, Regression, 2 program areas, 38 program steps, 7 memories £22.95
FX-602P Plus FREE Program Pack worth £9.95 £69.95
10+2d, 50f, SD, R/P, (f33), 10 program areas, up to 512 steps, up to 88 memories. Alpha/numeric.

SINCLAIR SPECTRUM SOFTWARE

Professional quality software from MICROL
USE AND LEARN Vol. 1 25 BASIC PROGRAMS on cassette tape plus SUPERB 100 PAGE BOOK £9.95
USE AND LEARN Vol. 2 30 MACHINE CODE ROUTINES. On tape plus 50 PAGE BOOK £9.95
THE DATABASE The best? 48K only £9.95
THE SPREADSHEET The best? 48K only £9.95

BE AN AGENT

**Sell our products to your friends
and family and earn yourself
10% commission**

TEMPUS, 38 Burleigh Street, CAMBRIDGE CB1 1DG

Please supply/send details of

Total £ enclosed, or debit my ACCESS/VISA card number

Name

Address

HE

YOUR GUIDE TO THE WORLD OF MICROPROCESSORS

MICRO-PROFESSOR

*A low cost tool for learning,
teaching & prototyping.*

Micro-Professor is a low-cost Z80 based microcomputer which provides you with an interesting and inexpensive way to understand the world of microprocessors.

Micro-Professor is a complete hardware and software system whose extensive teaching manual gives you detailed schematics and examples of programme code. A superb learning tool for students, hobbyists and microprocessor enthusiasts, as well as an excellent teaching aid for instructors of electrical engineering and computer science courses.

The **Micro-Professor** is much more than a teaching device. Use it for bread boarding and prototyping, designing your own custom hardware and software applications with Z80, 8080 and 8085 compatible code.

The standard 2K bytes of RAM is expandable to 4K, and the standard 2K bytes of ROM can be increased to 8K.

All this plus built-in speaker, a cassette interface, and sockets to accept optional CTC/PIO. Bus is extendable.

As well as being an exciting learning tool, the **Micro-Professor** is a great low-cost board for OEM's.



Micro-Professor
£79.95

EPB-MPF EPROM Programming Board
£84.95 + p&p


For all + 5V 1KP/2KB/4KB EPROMS Read/Copy/List/Verify Capability.

SSB-MPF Speech Synthesizer Board
£69.95 + p&p


A vocabulary of up to 400 words based on the TMS 5200 chip.

PRT-MPF Printer Board
£74.75 + p&p

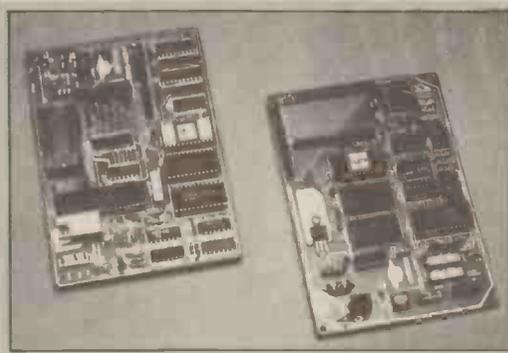Memory dump
BASIC program listing
Z80 disassembler



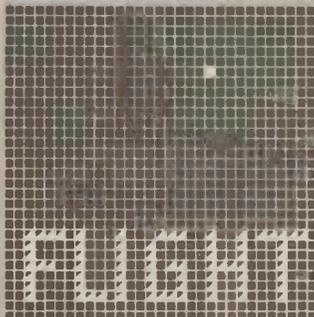Micro-Professor is a trade mark of Multitech Industrial Corporation.
Z80 is a trade mark of Zilog Inc.



Flight Electronics Ltd.

Complete the coupon today! Please allow 28 days for delivery.

HE

Please send me	Price	Qty	p&p	Name
Micro-Professor	£79.95		£2.95
SSB-MPF board	£69.95		£2.95	Address
EPB-MPF board	£84.95		£2.95
PRT-MPF board	£74.75		£2.95
		Total

I enclose cheque/P.O. for £.....



Mail order only • Trade enquiries welcome • Bulk order discounts • Prices include VAT

Flight House, Quayside Rd, Southampton, Hants SO2 4AD
Tel: (0703) 34003/27721. Telex: 477793



(by phone or post)

POINTS OF VIEW

Feel like sounding off?
Then write to the Editor stating your Point Of View!

New Devices for Old Effects

Dear Sir,
With regard to your Fuzz-Box project in the February '82 HE, please could you inform me where I can obtain the BC650 transistors, as I have been unable to find them listed in any catalogue.
Graham Walsh,
Pudsey.

When the Noiseless Fuzz-box was designed, the BC650 transistor had only recently come on to the constructors' market. Consequently it was difficult to obtain (one source was, and still is, Magenta) and we had to do a lot of leg-work to seek out suitable suppliers. Now, however, it has proved to be quite popular and should be available from the larger semiconductor stockists. Incidentally, it does no harm to ask about a component that doesn't appear in a given advertiser's list. Once the enquiries start flooding in, most companies will obtain stocks from the distributors.

Echoes On The Line

Dear Sir,
I tried to 'phone you for clarification of the HE Echo-Reverb (May '82, pages 33-37) but apparently you are no longer on the phone (why not pay the bill?). Two points: the circuit and layout differ for the diodes, and the circuit and Parts List differ on the value of R15. Are there any other discrepancies?

Do pay the phone bill — it's such a long wait by Post Office Non Communications system.
H. W. Fletcher,
Marlow Bottom,
Bucks.

The HE Gremlins chose our Echo-Reverb unit for their *pièce de résistance* — and they really did a job on it. The full list of errors are given in the reply to the following letter. Our apologies to all concerned; the Gremlins have been dealt with!

Our phone bill has been paid, but it won't help you — we cannot take enquiries and produce a magazine every month, and if we didn't produce the magazine, you'd have nothing to enquire about, would you?

Designer on the Dole

Dear Sir,
For an eight month old dole freak like myself, the HE Echo-Reverb met a very real need.

Some months ago I had scraped up the pennies and lashed out on two

TDA1022 ICs with a view to designing my own phaser/flanger/chorus/echo/reverb. Needless to say I found myself hopelessly out of my depth (even with the Mullard spec sheet to hand)! To cut a long story short, my courage has been rewarded by the appearance of your design (heaven-sent!).

Thanks! I now hope to proceed with: switchable clock timing capacitors for phase/flange/chorus/echo and possibly a sine-wave modulator for the VCO input of the 4046 clock. (I fear a saw-tooth oscillator would be prone to spikes and hence 'clicks' in the output.

Please keep up the cost pruning!
Thanks again.
D.P. Allen,
Wembley,
Middlesex.

The Echo-Reverb (HE May '82) has been one of our more popular projects. For a modest outlay and with careful setting-up, the unit will produce varying degrees of reverberation and echo. However, as with some other projects of this standard, a few errors crept into the printed article. So, to all readers who've had a few problems, here's the list — exhaustive, we hope!

p. 34 Figure 1. RV2 wiper comes from pin 9 of IC 1.

D2 is shown inverted (ie. cathode goes to OV).

p. 36 Figure 2. The end tags of RV2 are connected to +15 and OV supply rails. Transformer should be 9-0-9 V.

p. 37 Parts List RV1 should be 47K log. RV4 should be 22K log. The transformer should be 9-0-9 V. R15 should be 27K.

A Better Building Block

Dear Sir,
I enjoyed the series of articles Into Electronic Components. As a now regular reader of your magazine, however, I must say the most interesting and informative articles to date are the "Building Blocks" — I would appreciate more of the same. Detailed information on ICs, etc. is of great value, too.
A. Easom (G4OPI),
Scarborough,
N. Yorkshire.

We are pleased that you appreciate the Building Blocks series. A great deal of work goes into researching the

information and presenting it in a form that is easy to understand. However, details of applications for ICs and general constructional info can also be found in our How It Works sections, and Breadboard pages. And in this issue we start a special Building Blocks series on ICs used in microcomputers, called Components for Computing.

A Better Class of Meter

Dear Sir,
Having read copies of various electronic magazines, may I say that yours is very enjoyable and you can be sure that I will buy HE every month in future.

Is it possible to construct a voltmeter of range 0-16 VDC with a digital LED seven segment display, calibrated to read to a tenth of a volt?

If so I would be grateful if you could supply me with any relevant information including circuit diagrams, etc.

Paul Humphries,
Newcastle upon Tyne,
Co. Durham.

Thanks for the compliment, although we'll answer your questions (usually) even if you're rude about us! It's not only possible to build this voltmeter, but we have just done one in the August '82 issue, and with a better specification, at that.


A Little Ingenuity

Dear Sir,
In the Three-Aspect Signal Lights project (September '82) you suggest fitting microswitches to the points to obtain the required switching. Those modellers who have PECO points can use the PECO "accessory switch". This clips to the point motor (if fitted). I see no reason why this neat unit cannot be fitted to other makes of points, with a little ingenuity. I think this project has been one of your best yet. It would be ideal for large club layouts where there is more than one operator.
Yours in electronics.
M. Wilkins,
Ipswich,
Suffolk.

A double thanks to Mr. Wilkins; first for the comments and second for the information on accessory switches. We are always happy to pass on tips from readers who can provide extra info about any of our projects! Thanks too, to Dr. D.L.H. Bloomfield, who designed that model project, but who was not properly credited in the article.

ELECTRONIC IGNITION

Makes a good car better

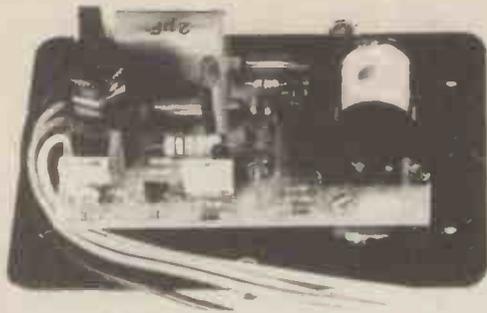

TOTAL ENERGY DISCHARGE electronic ignition gives all the well known advantages of the best capacitive discharge systems.

PEAK PERFORMANCE — higher output voltage under all conditions.

IMPROVED ECONOMY — no loss of ignition performance between services.

FIRES FOULED SPARK PLUGS no other system can better the capacitive discharge system's ability to fire fouled plugs.

ACCURATE TIMING — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

SMOOTH PERFORMANCE — immune to contact bounce and similar effects which can cause loss of power and roughness.

PLUS

SUPER POWER SPARK — 3½ times the energy of ordinary capacitive systems — 3½ times the power of Inductive systems.

OPTIMUM SPARK DURATION 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

BETTER STARTING — full spark power even with low battery.

CORRECT SPARK POLARITY unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

L.E.D. STATIC TIMING LIGHT for accurate setting of the engine's most important adjustment.

LOW RADIO INTERFERENCE fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

DESIGNED IN RELIABILITY an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

AS REVIEWED IN

ELECTRONICS TODAY INTERNATIONAL June '81 Issue
and EVERYDAY ELECTRONICS December '81 Issue

FITS ALL NEGATIVE EARTH VEHICLES,

6 or 12 volt, with or without ballast

OPERATES ALL VOLTAGE IMPULSE TACHOMETERS

Some older current impulse types (Smiths pre '74) require an adaptor — PRICE £2.95

STANDARD CAR KIT £15.90

Assembled and Tested £26.70

TWIN OUTPUT KIT £24.55

For MOTOR CYCLES and CARS with twin ignition systems

Assembled and Tested £36.45

PLUS
£1.00
U.K.
P. & P.
Prices
Include
VAT.

DIMENSIONS: Length 12.5 cm
Width 8.9 cm
Height 4.3 cm
Lead length 100.0 cm

TECHNICAL DETAILS

The basic function of a spark ignition system is often lost among claims for longer 'burn times' and other marketing fantasies. It is only necessary to consider that, even in a small engine, the burning fuel releases over 5000 times the energy of the spark, to realise that the spark is only a trigger for the combustion. Once the fuel is ignited the spark is insignificant and has no effect on the rate of combustion. The essential function of the spark is to start that combustion as quickly as possible and that requires a high power spark.

The traditional capacitive discharge system has this high power spark but, due to its very short spark duration and consequential low spark energy, is incompatible with the weak air/fuel mixtures used in modern cars. Because of this most manufacturers have abandoned capacitive discharge in favour of the cheaper inductive system with its low power but very long duration spark which guarantees that sooner or later the fuel will ignite. However, a spark lasting 2000µs at 2000 rev/min. spans 24 degrees and 'later' could mean the actual fuel ignition point is retarded by this amount.

The solution is a very high power, medium duration, spark generated by the TOTAL ENERGY DISCHARGE system. This gives ignition of the weakest mixtures with the minimum of timing delay and variation for a smooth efficient engine.

SUPER POWER DISCHARGE CIRCUIT A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems.

HIGH EFFICIENCY INVERTER A high power, regulated inverter provides a 370 volt energy source — powerful enough to store twice the energy of other designs and regulated to provide sufficient output even with a battery down to 4 volts.

PRECISION SPARK TIMING CIRCUIT This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

TYPICAL SPECIFICATION

	TOTAL ENERGY DISCHARGE	ORDINARY CAPACITIVE DISCHARGE
SPARK POWER (PEAK)	140 W	90 W
SPARK ENERGY (STORED ENERGY)	36 mJ	10 mJ
	135 mJ	65 mJ
SPARK DURATION	500 µs	160 µs
OUTPUT VOLTAGE (LOAD 50pF EQUIVALENT TO CLEAN PLUGS)	38 KV	26 KV
OUTPUT VOLTAGE (LOAD 50pF + 500 KΩ EQUIVALENT TO DIRTY PLUGS)	26 KV	17 KV
VOLTAGE RISE TIME TO 20 KV (Load 50pF)	25 µs	30 µs

TOTAL ENERGY DISCHARGE should not be confused with low power inductive systems or hybrid so called reactive systems.

ELECTRONIZE DESIGN

Dept..E, Magnus Road, Wilnecote

Tamworth, B77 5BY

Phone: (0827) 281000



Jean Baudot

Ian Sinclair

BAUDOT — the name might ring a few bells if you are into computing: drop the last two letters and you get baud, which is a unit for the speed of transfer of information. The old-fashioned teleprinter, for example, operates at a rate of 110 baud, but a modern cathode-ray terminal may work at 2400 baud or higher. Having established the connection, let's look at the story of J. M. E. Baudot.

Jean Baudot was born in 1845 at Magneaux in France, and you will search in vain for details of his early life, unless you are prepared to look through a fairly large library. You won't find his name mentioned, often; it's the usual problem — a brilliant engineer whose name has entered our language hardly gets a mention, even in his own country.

He seems to have had the conventional schooling of the French middle classes at the time, which was, incidentally, one of considerable social unrest, with minor revolutions breaking out all over Europe. His firm interest, from the time that he left school, was the growing technology of the electric telegraph, and it was to this that he turned his attention when the time came to earn his own living.

Dots and Dashes

In these early days, the universal code for telegraph use was Morse code, which relies on the use of two types of electric impulse, a long (dash) and a short (dot) — the form of the code is shown in Figure 1. Now there is nothing wrong with this as a code, and it is used, to a limited extent, to this day, but it was devised in 1832, long before electrical communications began to evolve into the systems that were beginning to be commonly used in the 1870s. Baudot, in particular, thought that the use of Morse code was very restricting. In 1874, he was working on the development of what we now call time-multiplex telegraphy, which allowed one telegraph line to carry several sets of messages between different sets of transmitters and receivers, with no interference between the signals. The system that he was working with was a completely mechanical one; each signal source was connected to a separate contact of a group arranged in a circle, over which a revolving contact, like the brush of a dynamo, revolved at high speed, connecting each contact in turn to the single telegraph line. The current return was through the earth, which is why we use the term "earth" to mean current return path to this day. At the receiving end, a similar arrangement was used to connect the signals from the telegraph line to the different receivers but obviously, the system could operate correctly only if the motors driving the rotating contacts were synchronised.

Another of the problems of using this

system with Morse code was that each dash was liable to be broken up, by the action of the rotating brush, into a series of dots, on different channels; unless the speed of the brush was varied, so that it spent more time on a contact transmitting a dash than on one transmitting a dot, it inevitably scrambled the message. Many other people, at the time, were trying to synchronise the movement of the rotating brushes to the varying dots and dashes of Morse code, but Baudot came up with a completely different answer.

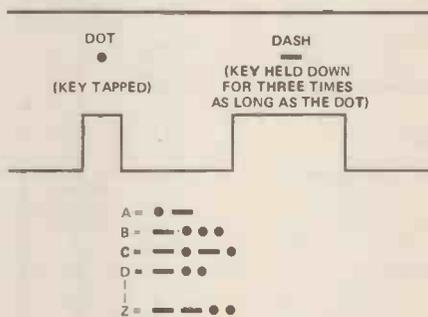


Figure 1. International Morse Code. The length of the pulse determines the meaning — dot or dash.

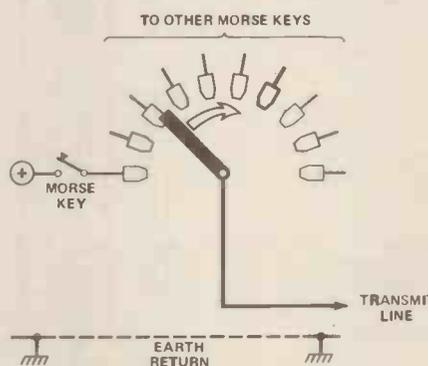


Figure 2. Early multiplex telegraphy.

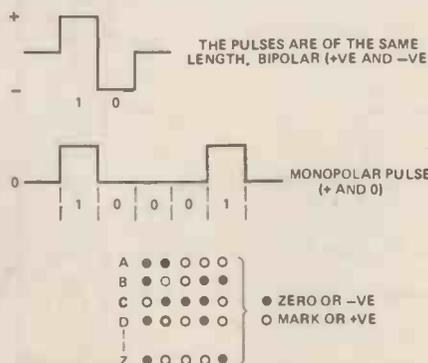


Figure 3. The modern 5-bit code. The bipolar version (top) is preferred because the difference between signal levels is easier to detect. This signal later became standardised as RS232.

A name to ring bells with.

Digital Codes

His approach was to use an entirely different code, one which used what we would now call digital signals — on and off — as distinct from the Morse code signals of 'long' and 'short'. The important point about Baudot's signals was that they were separated by *equal* time intervals. For example, if we take the two Morse signals, R (• — •) and S (• • •), the time between the first and last dots of each letter is not the same, because the middle dash of the R takes about three times as long as the middle dot of the S. Baudot devised a new 5-digit code, using pulses and spaces of equal length, so that the time needed to transmit a five-character message was always the same. This was the breakthrough that multiplex systems needed because the speed of the rotating contact (commutator) could now be synchronised to the pulse rate of the code.

Baudot patented his five-unit code in 1874. Five digits gave a choice of 32 characters, so that the early Baudot codes allowed the transmission of the letters of the alphabet (upper case) plus a few punctuation marks and operator signals (eg, BELL), but no digits. A later version of the code used seven digits and it is this version which has evolved into the ASCII seven-bit code that is used almost universally in computers.

The Baudot code was a major step forward in telegraphy because, as well as permitting more efficient multiplexing, it also permitted the faster development of the logical accompaniment to multiplexing — mechanical methods of sending and receiving telegraph signals.

The transmitter was primitive — if the operator released the key too soon, the wrong character would be sent — but it was a step forward from manual transmission. It was soon superseded by other methods.

Baudot's equally ingenious receiver used a method that was to remain current right up to the time when fully electronic printers were developed. It can still be seen, with some modern improvements, in some Telex terminals. It all looks like a mechanical nightmare — and anyone who has tried to get an old-style teleprinter going will agree that it is. Baudot's work vastly improved the rate at which data could be transmitted, and the principles which he established are in use to this day, although the methods have changed — for the better! Baudot code was not entirely logical and it was improved by Don Murray in 1903, so that the modern 5-bit code and its 7-bit successor are often known as Murray-codes rather than Baudot codes. The principles, nevertheless, are those of Baudot, and a good reason for immortalising his name in the term "baud rate".

ANNOUNCING THE NEW MAIL ORDER DIVISION OF THE GRENSON GROUP. VAST STOCKS AND COMPUTER CONTROLLED OPERATION HAVE ASSURED VERY COMPETITIVE PRICES. SEE FOR YOURSELF!

BENCH POWER SUPPLIES

As featured in Feb 82 'Practical Electronics'.

Unit (BPU1)	KIT	BUILT
	£35	£59
P x P	£3.35	£3.35
V.A.T.	£5.75	£9.35

Triple output unit (1 ± 15V and +5V) available shortly.

The Grenson Group have over twenty years experience designing power supplies. Contact us now and we will try to solve your problem.

LARGE ELECTROLYTICS.

Sprague/General Electric made — computer grade — ideal for power supplies — **ONLY £2.50 EACH!**

185,000 @ 15V, 300,000 @ 7V, 120,000 @ 15V, 100,000 @ 30V,
71,000 @ 40V, 60,000 @ 40V, 9,000 @ 50V

SMALL ALUMINIUM ELECTROLYTICS.

Axial Leads.				Radial Leads				
uF	V	Price	uF	V	Price	uF	V	Price
1000	6.3	15p	470	16	15p	470	16	15p
22	10	05p	4.7	25	05p	1000	25	25p
100	10	05p	330	25	15p	220	40	25p
22	16	05p	680	25	25p	470	40	25p

OLD TIMERS SECTION.

OC44	70p	OC45	37p	OC71	34p	OC70	36p	OC42	70p
OC35	90p	OC25	75p	OC16	200p	OC170	44p	OC22	150p
				(antiquel)					
2S024	200p	OC139	70p	OC140	75p	2S307	85p	2ST01	80p
OC84	25p	OC41	80p	2S301	80p	OC76	40p	OC73	40p
OC83	40p	OA5	10p	OA7	15p	OA10	15p	OA47	10p

MIXED BAGS.

CAPACITORS — 30 ASSORTED VALUES ONLY £1.00!

TRANSISTORS — 20 SMALL SIGNAL PLASTIC — ½ n.p.n. — ½ p.n.p. **ONLY £1.50.**

LISTS AVAILABLE ON REQUEST.

RESISTORS.

We have, amongst others, the following resistors in stock: —
Over 1 ½ million ¼ watt carbon film.
Over ½ million ½ watt metal oxide.
Over ¼ million wirewound.
Further stock listed in our free catalogue.

Typical Prices.

	1-9	10-99	100+
¼ watt carbon	2p	1½p	1p
½ watt metal oxide	6p	4p	3p
6 watt wirewound	25p	15p	12p

SERIES 74 I.C.'s

Comprehensive stocks, competitively priced.
Simple gates from only 10p.
See our free catalogue for details.

I.C. SOCKETS

14 way — 10p.
46 way — could be broken to make smaller strips — 25p.
16 way — gold pins — 20p.

TRANSISTORS.

AC107	30p	AC126	30p	AC188	27p	ACY17	66p	ACY19	65p
BC149	7p	BC159	12p	BC171	10p	BC173	10p	BC212	9p
BC212L	9p	BC213L	9p	BC237	12p	BC308	13p	BC327	18p
BC337	13p	BC558	14p	BF115	29p	BF194	13p	BF197	13p
BF198	13p	BF199	15p	BFR40	20p	BFX29	25p	BFY90	60p
2N706	15p	2N1131	20p	2N1132	20p	2N2222A	20p	2N2369A	15p
2N3702	10p	2N3705	10p	2N3711	10p	2N3904	15p	2N4061	10p
2N5172	15p	2N5179	30p						

VOLTAGE REGULATORS AND P.S.U. COMPONENTS

+ 5V	1A	TO220	.50p	-12V	1A	TO220	.50p
+ 5V	1.5A	TO3	1.50p	-12V	1.5A	TO3	2.00p
- 5V	1A	TO220	.50p	+15V	1A	TO220	.50p
- 5V	1.5	TO3	2.00p	+15V	0.5A	TO3	.90p
+ 6V	0.6A	TO220	.50p	-15V	1A	TO220	.50p
+12V	0.5A	TO220	.50p	-18V	1A	TO220	.50p
+12V	0.5A	TO3	.90p	-24V	1A	TO220	.80p
+12V	1.5A	TO3	1.50p				

2N3055 .35p, 2N4347 (120V) 1.50p, 2N6258 (250W) 1.80p, 400mW Zeners .05p
723 .30p

*** SPECIAL OFFER * SPECIAL OFFER * SPECIAL OFFER ***

For every order received in December 1982 of a value greater than £10.00, a free bag of assorted components worth at least £2.00 will be sent with the order. Please allow 21 days for delivery.

Dept. C1 High March, Daventry, Northants NN11 4HQ.
Tel: 03272 5523 Telex: 311245 GRENEL G.

Please add 50p per order postage and packing plus 15% VAT on total. No VAT on overseas orders, postage at cost. Cheques and postal orders made payable to Emos Limited. Send large SAE for comprehensive catalogue.

EMOS

BUY LINE

HE Microlog

Our prototype was built into a standard Verocase, code 65-2523E, however because of the amount of drilling and marking involved, we had a chat with Newrad Instrument Cases, who have designed a suitable case for the Microlog. It is available from them (their address is printed elsewhere in this column) for £7.90 including VAT, p&p, complete with screen printed front panel and all holes drilled and punched. The lever switch is a Post Office type 1000.

Tape/Slide Synchronizer

There should be no problem obtaining the parts for this project; just remember that the relay is a 12V, 2-pole subminiature (ie PCB mounting) type, and choose the jack sockets to fit your sound system.

Phase Four

If your local supplier does not stock the TL064, it is always available from Technomatic, who also stock the 2N5457 FETs; a TL084 can be substituted for the TL064, if you are willing to accept increased battery usage. Once again, the custom case for our prototype was made by Newrad Instruments (see elsewhere in this column for their address).

Intruder Alarm

All the components contained on the PCB should be easy to obtain. The remainder will vary in availability according to the sort of system you envisage. However as a guide, suitable sirens can be bought from Greenweld.

A source for most of the other switches, mats and foils etc is Maplin.

Stereo Noise Gate

Most of the components are readily available and you should be able to get the thing working within a few hours.

The low voltage electrolytic is sold by Greenweld, who also stock a range of suitable cases. Other sources for a case are Lightning and West Hyde.

Big Ear

A complete list of parts for this project is available from Bewbush Audio, 26 Hastings Road, Pound Hill, Crawley, Sussex. The cost of the kit is £15.00, including VAT, post and packaging.

TV Amp

Newrad Instrument Cases have produced a case for our prototype, as shown in the photograph; this is available for £5.00, plus postage. Newrad Instrument Cases are at Tiptoe Rd., Wootton, New Milton, Hants BH25 5SJ.

Phase Four

Paul Coster

A Four-stage audio phaser unit, based on last month's Breadboards design.

AN AUDIO PHASER is simply a circuit designed to produce a 'comb filter' (Figure 1). When the notches of the 'comb' are swept up and down the audio spectrum, the musical effect known as 'phasing' occurs. One of the first times this trick was used on a recording was in 1968; the song was "Pictures of Matchstick Men" by a group called Status Quo. Another was "Itchycoo Park", by the Small Faces.

As a slightly more interesting (and relevant) diversion, it is worth mentioning that 'phasing' is not the same as a similar musical effect called 'flanging'. Flanging depends on a reasonably long time delay — as much as, oh, a millisecond or so; mixing the delayed signal with an undelayed signal also results in a comb filter, but now the notch frequencies are spaced at musical intervals — thirds, fifths, flattened ninths and so on — and the effect so produced has a more "musical" quality, so it is said. Flanging was discovered by the American record producer, Phil Spector...but that's another story!

Shifting Circuits

The HE Phase Four, however, is a phaser. It is based on the circuit of Figure 2, a single stage phase shifter producing 90° of phase shift from input to output.



At zero frequency (DC), the input to the non-inverting pin of the op-amp is blocked by the capacitor, C1, so the circuit acts as an inverter with a gain of one; this, of course, is equivalent to a phase shift of 180°. At very high frequencies, though, the capacitor becomes a short circuit and so the op-amp becomes a non-inverting amplifier, still with a gain of one; the phase shift now is 0°.

But at some intermediate frequency, set by the time constant (RC) of the

high-pass filter network on the non-inverting input, the phase shift will be exactly 90°; the gain is still one! Essentially, the op-amp is buffering the phase-shift produced by the high-pass network of C1 and R3, maintaining a constant gain of one.

If two of these units are cascaded — the input signal passing through one, then the other — the total phase shift will be 180° at the frequency set by the RC time constant, and if the phase-shifted signal is then added to an un-

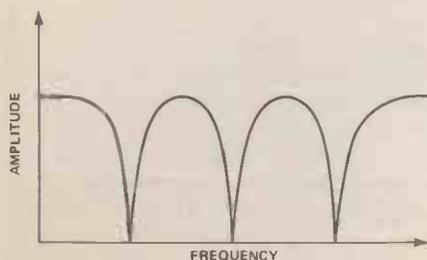


Figure 1. A comb filter forms a series of notches in the frequency response curve.

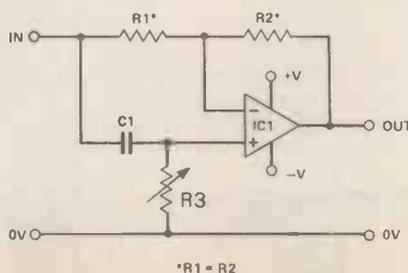


Figure 2. The basic phase shifting circuit.


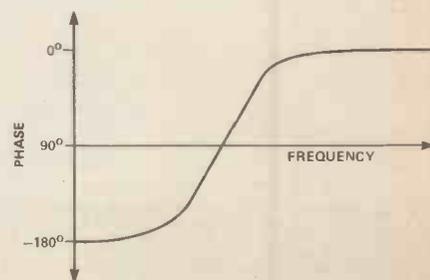


Figure 3. The frequency-phase response of the circuit in Figure 2. The crossover point is set by the values of R3 and C1.

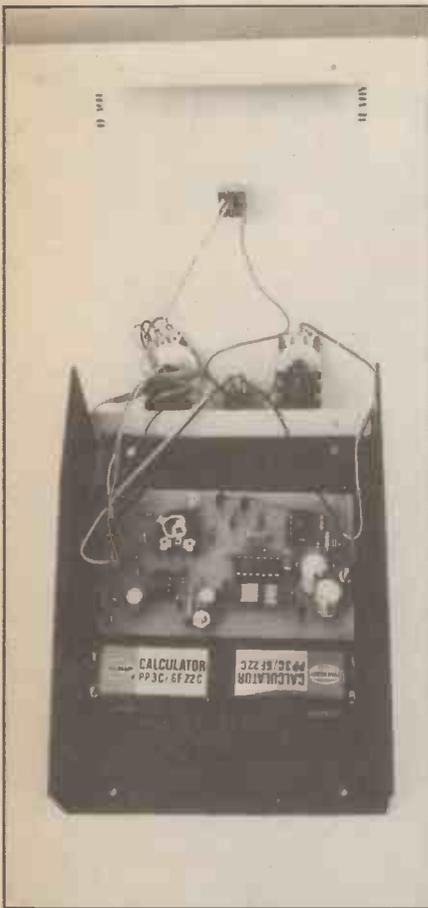

shifted signal, the result will be a notch in the response, at the specified frequency.

In fact, there are easier ways to produce a notch filter. The reason why this circuit is used so often for phasing units is because it is quite easy to change the position of the notch. At its simplest, this is done by varying R3, thus changing the time constant which determines the corner frequency (the two are really equivalent). In a manually operated phaser, this would be achieved by using a potentiometer in place of R3 and varying it, by means of a foot pedal or something similar, to produce a manual sweep (ie, movement of the notch, up and down the response band).

It is just as easy to produce an automatic sweep; Figure 4 also shows a FET transistor connected across R3; by varying the voltage to the gate of the

FET, its resistance can be changed from a few hundred ohms to around a few hundred megohms. All we need now is a way of producing a varying voltage to control the resistance of the FET, and a summing amplifier to combine the phase-shifted and unshifted outputs.

Phase Four

All these elements are brought together in the HE Phase Four circuit, shown in Figure 5. It uses four stages to produce a total phase difference of 360° between input and output, producing two notches in the response.

The input to the unit is buffered by a unity gain stage, IC1a; the IC used in this position was chosen for its low noise specification. The phase shifters use all sections of a quad op-amp package, IC2 (elected for low power consumption).

The values of C3,6,7,8 are chosen somewhat arbitrarily, but they will affect the total quality of the output. Capacitors C1,2,4 and 5 are to decouple the supply rails, eliminating high frequency spikes from the output.

The phase shifted signal is fed to a standard virtual earth mixer. The amount of shifted signal added to the output is set by the depth control, RV1, which determines depth of the notches. A switch is also included which allows the effect to be bypassed; PR1 is used to adjust the output so that the gain is

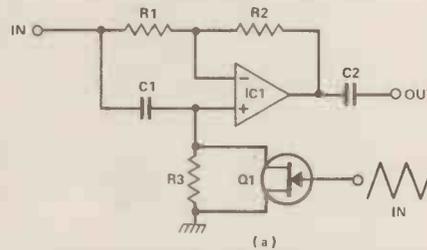


Figure 4. By putting an FET in parallel with R3, the effective resistance can be varied over a wide range.

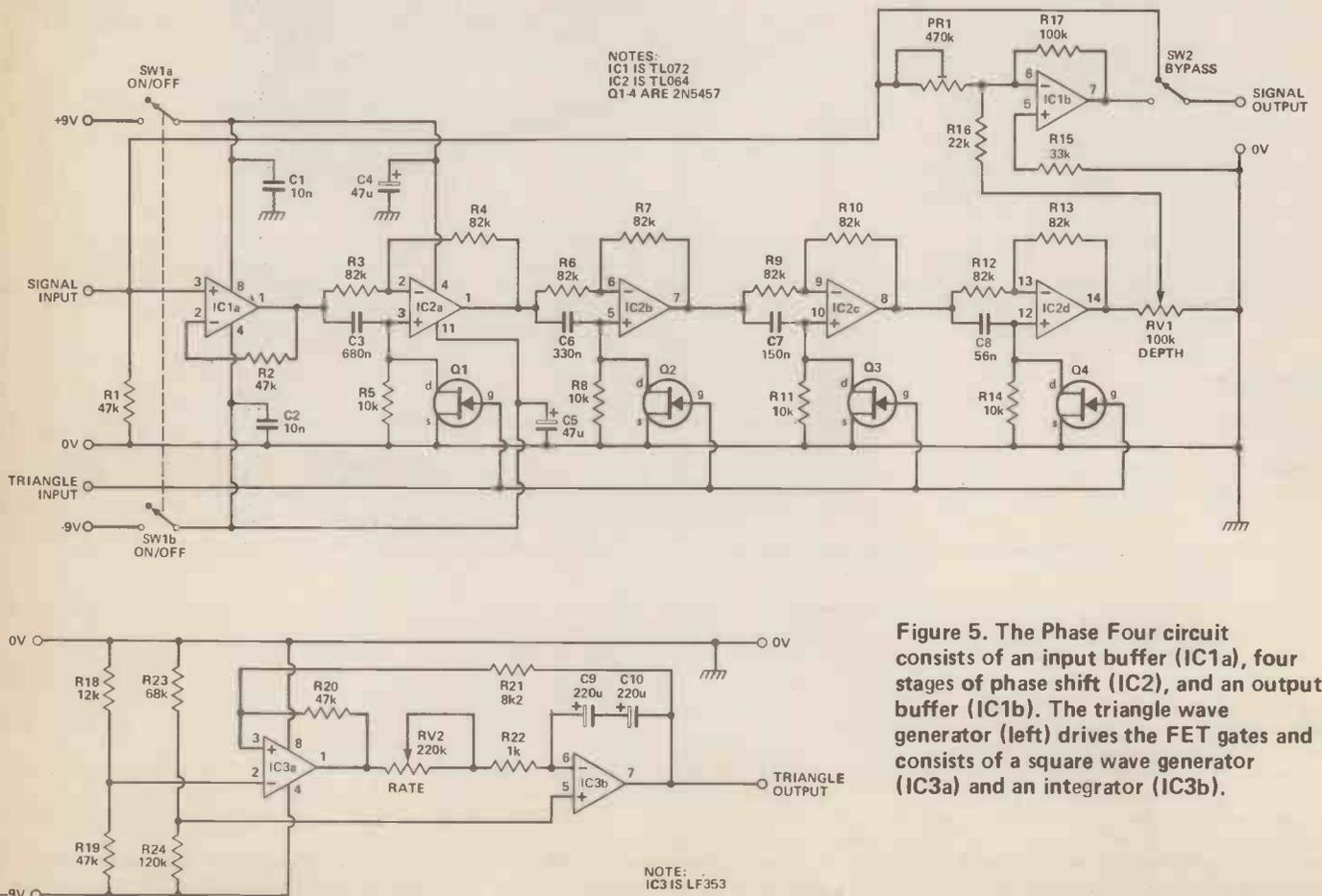


Figure 5. The Phase Four circuit consists of an input buffer (IC1a), four stages of phase shift (IC2), and an output buffer (IC1b). The triangle wave generator (left) drives the FET gates and consists of a square wave generator (IC3a) and an integrator (IC3b).

Parts List

RESISTORS

(All ¼ watt, 5% carbon)

R1,2,19,20	47k
R3,4,6,7,9,10,11,12	82k
R5,8,11,14	10k
R15	33k
R16	22k
R17	100k
R18	12k
R21	8k2
R22	1k
R23	68k
R24	120k

POTENTIOMETERS

PR1	470k
	horiz. carbon preset
RV1	100k
	log carbon
RV2	220k
	log carbon

CAPACITORS

(All metallised polycarbonate, unless noted)

C1,2	10n
	ceramic disc
C3	680n
C4,5	47u
	16V radio electro
C6	330n
C7	150n
C8	56n
C9,10	220u
	16V radio electro

SEMICONDUCTORS

IC1	TL072
	dual BIFET op-amp
IC2	TL064
	quad BIFET op-amp
IC3	LF353
	dual J-FET op-amp
Q1-4	2N5457
	N-Channel FET

MISCELLANEOUS

SW1	DPDT
	min. toggle
SW2	SPST
	footswitch
2 x ¼" jack sockets; 2 x PP3 battery clips; 2 x 8 pin, 1 x 14 pin DIL sockets; 2 x knobs; case (see Buylines); PCB; solder, wire etc.	

BUYLINES page 34


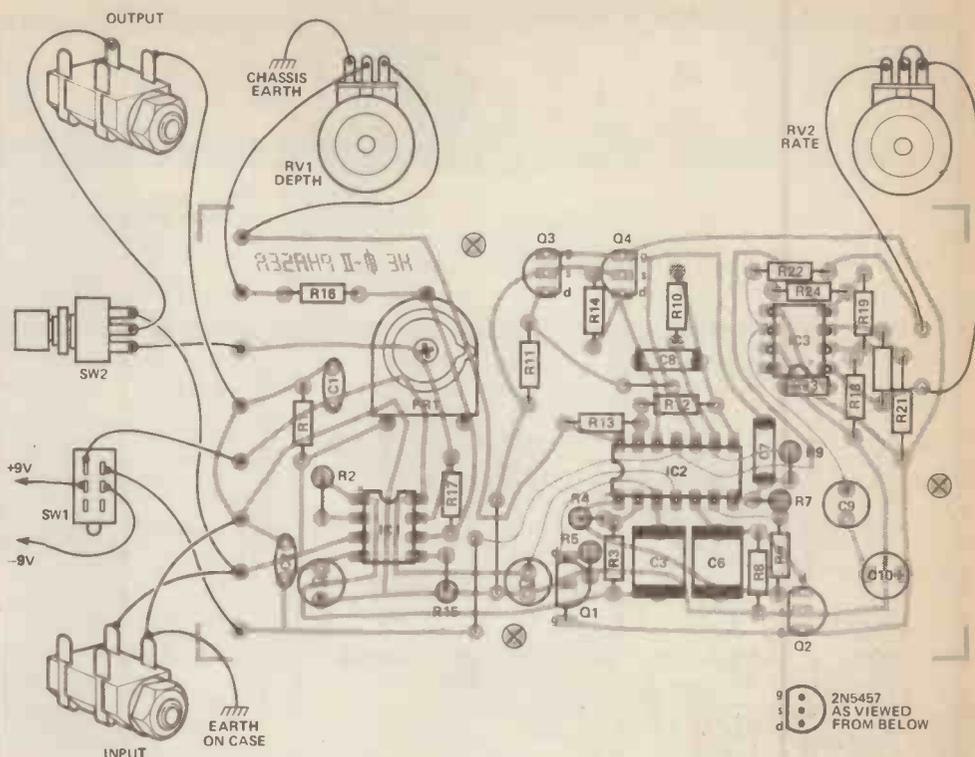


Figure 6. The PCB component overlay.

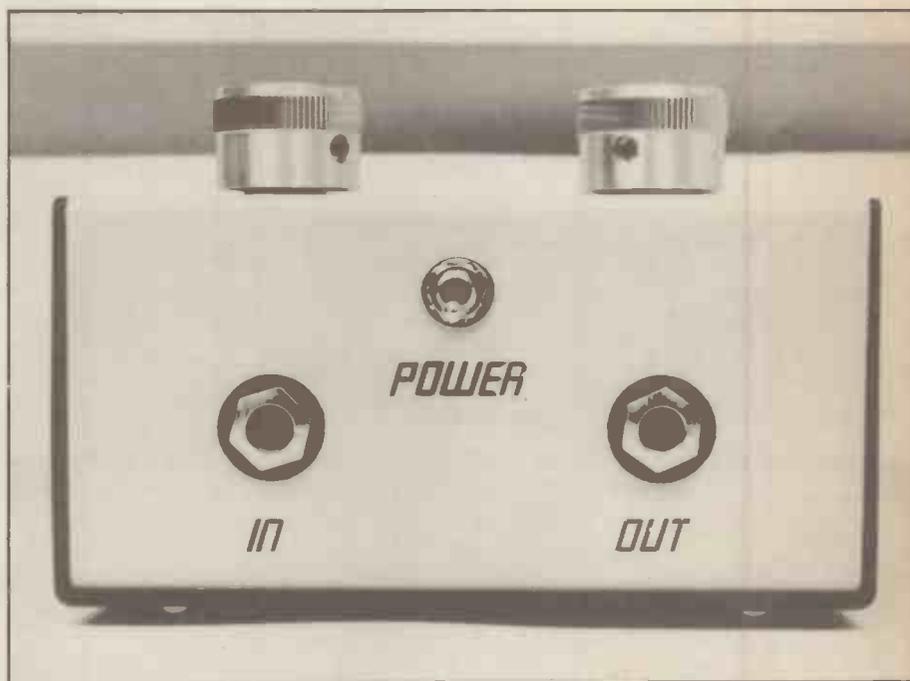

the same in either case.

The voltage sweep for the FETs is produced by ICs 3a,b, and LF353. The two op-amps are configured as a triangle-wave generator; in fact the sweep could be controlled by any slowly varying cyclic waveform, such as a sine wave or sawtooth, but the triangle shape works best in this application.

The circuit works in two stages: IC3a produces a square wave output and this is integrated by 3b to give the triangle shape. RV2 controls the frequency, ie the sweep rate, between the limits of about 0.1 and 10 Hz, with the values

chosen. The values of C9 and C10 are not critical, but they must be connected as shown, to form a simulated bi-polar capacitor.

Construction

Assembly of this project is not particularly difficult; simply follow the component overlay (Figure 6), taking care that the ICs and electrolytic capacitors are correctly positioned. One point to note is that RV2, a potentiometer with a logarithmic characteristic, must be connected the right way round; otherwise, the variation

in sweep speed will all come at one end of the rotation.

The ideal case for the Phase Four is the custom built job supplied by Newrad Instruments (see Buylines for details), though any case large enough to contain the PCB and batteries would do; it depends on how heavy-footed you are!

The only adjustment required is to set PR1 so that the gain through the phaser is the same as in the 'bypassed' condition. Simply set the depth control for minimum and adjust PR1, switching between effect and bypass, until the levels sound equal.

HE

BI-PAK AUDIO

THE PROFESSIONAL APPROACH

HIGH QUALITY MODULES FOR STEREO MONO AND OTHER AUDIO EQUIPMENT


BI-PAK Audio Modules are famous for their variety, quality of design and ruggedness. For over 10 years BI-PAK have been suppliers to manufacturers of high quality audio equipment throughout the world - to date, well over 100,000 modules have been sold - this is why discerning amateur enthusiasts and professionals alike insist on using BI-PAK modules in their equipment.

They know that every item is designed and tested to do the job for which it is intended before it leaves the factory. Whatever you are building there is a kit or module in the BI-PAK range to suit your every need.

AUDIO AMPLIFIERS

5-10 watts (RMS)
AL20 5 watt Audio Amp Module 22-30v supply **£3.57**
AL30A 7-10 watt Audio Amp. Module 22-32v supply

£4.16.

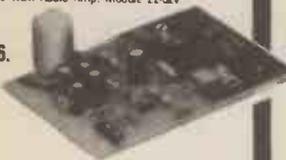

AUDIO AMPLIFIERS

15-25.35 watts (RMS)
AL60 15.25 watt Audio Amp Module 30-50v supply **£5.15.**
AL80 35 watt Audio Amp Module **£8.07**



AUDIO AMPLIFIER

Audio Amplifier, 50W R.M.S., with integral heat sink and short circuit protection
Introduced to fulfill the demand for a fully protected power amp., capable of driving high quality speaker systems at up to 50w with distortion levels below 0.5%. Ideal for domestic use Discos, P.A. systems, electronic organs, etc. The generously rated components ensure continuous operation at high output levels. AL120 50 watt Audio Amp Module 50-70v supply

£13.14.

AUDIO AMPLIFIER

125 watts (RMS), AL250
A power amplifier providing an output of up to 125w RMS, into a 4 ohm load. Four 115w transistors in the output stage makes it extremely rugged while damage from incorrect or short circuit loads is prevented by a four transistor protection circuit. For use in many applications such as disco units, sound reinforcement systems, background music players etc.
AL250 125 watt Audio Amp Module 50-80v supply

£19.60.



POWER SUPPLIES

PS12 24v Supply Suit: 2 x AL10 2 x AL20 2 x AL30 & PA12/SA53 **£1.65.** SPW80 33v Stabilised supply Suit: 2 x AL60 PA100 to 15 watts **£4.84.** SPM12045 45v Stabilised supply Suit: 2 x AL60 PA100 to 75 watts **£6.38.** SPM12055 55v Stabilised supply Suit: 2 x AL60 PA200 **£6.38.** SPM12065 65v Stabilised supply Suit: 2 x AL120 PA200 1 x AL250 **£6.38.** SG30 15-0-15 Stabilised power supply for 2 x GE100 MKII **£3.80.**



SPM120 is a fixed voltage stabiliser with an output voltage of either 45v, 55v, or 65v. Designed for use in audio applications, the stabiliser which provides output currents up to 2.5A operates direct from a mains transformer requiring only the addition of two electrolytic capacitors to complete the power supply.

STEREO PRE-AMPLIFIERS

PA12 Supply voltage 22-32v input sensitivity 300mV Suit: AL10/AL20/AL30 **£8.55.** PA100 Supply voltage 30-55v inputs. Tape Tuner Mag P.U. Suit: AL60/AL80 **£17.65.** PA200 Supply voltage 35-70v inputs. Tape Tuner Mag P.U. Suit: AL80/AL120/AL250 **£18.24.**



The PA200 is basically our popular PA100, modifications being made to make it compatible with the higher output amplifiers i.e. AL120 & AL250. The unit boasts six push button selectors giving a choice of 3 inputs, 2 filters, for both high and low frequencies and a stereo or mono button, all combining to give a top quality stereo pre-amplifier and tone control.

MINIATURE FM TRANSMITTER MODULE

Freq: 95-106 MHz Range: 1/2 mile Size: 45mm x 20mm Add 9v. batt. Not licensed in UK
Ideal for: 007-M19-FBI-CIA-KGB-etc. Price: **£5.50**

MAGNETIC CARTRIDGE PRE-AMPLIFIER

Enjoy the quality of a magnetic cartridge with your ceramic equipment using the MPA30 which is a quality pre-amp, enabling magnetic cartridges to be used where facilities exist for ceramic cartridges only. With a DIN input socket & full, easy to follow instructions
MPA30 Stereo Mag Cartridge, Pre-amp.
- input 35mV Output 100mV **£3.27.**



MONO PRE-AMPLIFIERS

MM100 suitable for disco mixer. MM100G suitable for guitar pre-amp mixer.
The MM100 and MM100G mono pre-amplifiers are compatible with the AL60, AL80, AL120 and AL250 power amplifiers and their associated power supplies.
MM100 Supply voltage 40-65v inputs. Tape Mag P.U.
Microphone Max output 500mV **£12.43.** MM100G Supply voltage 40-65v inputs. 2 Guitars, Microphones Max output 500mV



£12.43.

GE100 MKII

10 Channel Monographic Equaliser.

Only 156mm x 65mm x 50mm including the 10 x 10K 45mm slider potentiometers and knobs which are mounted on a board above the circuitry. In the range of 31Hz to 16KHz you can cut and boost $\pm 12dB$ with the 10 sliders, each with frequency marked on the circuit board. The GE100 uses include mixers, P.A. systems and discos. It will also improve the sound reproduction of your existing audio equipment. Power supply for GE100 old SG30. Together with Transformer no: 2043
GE100 MKII 10 Channel Monographic Equaliser with sliders & Knobs **£20.00.**



PUSH BUTTON STEREO FM TUNER

Fitted with Phase locked loop decoder
SA53 Provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, simply by changing the settings of the preset controls. Features include FET input stage, Varicap diode tuning.

£19.00.



Transformers are not included with power supplies. SPM120 Range also require reservoir and output capacitors

TRANSFORMERS

2034 1.7 amp 35v suit SPM80 **£4.90.** 2035 2 amp 55v **£6.85.** 2036 750mA 17v Suit PS12 **£2.85.** 2040 1.5 amp 0-45v-55v Suit SPM120/45 SPM120/55v **£6.45.** 2041 2 amp 0-55v-65v Suit SPM120/55 SPM120/65v **£8.40.** 2039 1 amp 0-20v Suit Stereo 30 **£3.50.** 2043 150mA 15-0-15v Suit SG30 **£1.80.**

ACCESSORIES

139 Teak Cabinet Suit Stereo 30 320 x 236 x 81mm **£7.00.** 140 Teak Cabinet Suit STA15 425 x 290 x 95mm **£3.50.** FP100 Front Panel for PA100 & PA200 **£1.80.** BP100 Back Panel for PA100 & PA200 **£1.80.** GE100FP Front Panel for one GE100MKII **£1.75.** TC60 Kit of Parts including Teak Cabinet chassis, sockets & knobs etc fits house STA15 Amplifier **£17.50.** PS250 Consists - 1 capacitor & 4 diodes for constructing unregulated power supply for AL250 to 125 watts **£2.90.**



BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of component you require, plus some very interesting ones you will soon be using and of course, the largest range of semiconductors for the Amateur and Professional you could hope to find
There are no wasted pages, of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, Bi-Pak's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a Bi-Pak Catalogue. Have one by you all the time - it pays to buy BI-PAK.

To receive your copy send **75p** plus 25p p&p

BI-KITS

STA5 5 watts per channel Stereo Amplifier Kit consisting of 2 x AL20 amplifiers 1 x PA12 pre-amplifier 1 x PS12 power supply 1 x 2036 transformer and necessary wiring diagram **£19.52.** STA10 10 watts per channel Stereo Amplifier Kit consisting of 2 x AL30 amplifiers 1 x PA12 pre-amplifier 1 x PS12 power supply 1 x 2036 transformer and necessary wiring diagrams **£20.83.**

STA15 15 watts per channel Stereo Amplifier Kit consisting of 2 x AL60 amplifiers 1 x PA100 pre-amplifier 1 x SPM80 power supply 1 x 2034 transformer 2 x coupling capacitors for 8 ohms 470 mfd 50v and necessary wiring diagrams. **£36.76.** STA25 25 watts per channel Stereo Amplifier Kit consisting of 2 x AL60 amplifiers 1 x PA100 pre-amplifier 1 x SPM120/45 power

supply 1 x 2040 transformer 2 x coupling capacitors for 8 ohms 470 mfd 45v 1 x reservoir capacitor 2200 mfd 100v and necessary wiring diagram **£45.76.** STA35 35 watts per channel Stereo Amplifier Kit consisting of 2 x AL80 amplifiers 1 x SPM120/55 power supply 1 x PA200 pre-amplifier 1 x 2035 transformer 2 x coupling capacitors 470 mfd at 50v for 8 ohms 1 x reservoir capacitor 2200 mfd 100v and necessary wiring diagram **£45.76.**

REGULATED VARIABLE STABILISED POWER SUPPLY

Variable from 2.30 volts and 0.2 Amps Kit includes -
1 - VPS30 Module, 1 - 25 volt 2 amp transformer, 1 - 0-50v 2" Panel Meter, 1 - 0-2 amp 2" Panel Meter, 1 - 470 ohm wirewound potentiometer, 1 - 4K7 ohm wirewound potentiometer. Wiring Diagram included VPS30 KIT **£20.**

SIREN ALARM MODULE

American Police type siren powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer break-down and other security purposes. BP124 5 watt 12v max - Siren Alarm Module **£3.85.**

BI-PAK

Send your orders to Dept HE12 BI-PAK PO BOX 6 WARE HERTS
SHOP AT 3 BALDOCK ST., WARE HERTS. **TELEPHONE 0456 511111**
TERMS, CASH WITH ORDER, SAME DAY DESPATCH, ACCESS
BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRD 388 7006
ADD 15% VAT AND 50% PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.
Remember you must add VAT at 15% to your order
Total. Postage add 50p per Total order.

BI-PAK BARGAINS



5T21 SCREWDRIVER SET
6 precision screwdrivers in hinged plastic case. Sizes: — 0.8, 1.4, 2.2, 4, 2.9 and 3.8mm **£1.75**

5T31 NUT DRIVER SET
5 precision nut drivers in hinged plastic case With turning rod. **£1.75**
Sizes: — 3, 3.5, 4, 4.5 and 5mm.

5T41 TOOL SET
5 precision instruments in hinged plastic case Crosspoint (Phillips) screwdrivers: — H 0 and H 1 Hex key wrenches: — 1.5, 2 and 2.5mm **£1.75**

5T51 WRENCH SET
5 precision wrenches in hinged plastic case. Sizes: — 4, 4.5, 5, 5.5 and 6mm. **£1.75**
BUY ALL FOUR SETS: 5T21-5T51 and get HEX KEY SET FREE
HEX KEY SET ON RING.
Sizes: 1.5, 2, 2.5, 3, 4, 5, 5.5 and 6mm.
Made of hardened steel.
HX/1. **£1.25**



"IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty*	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/4-watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm 2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm-2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.
*Quantities approximate, count by weight

25 pieces of Audio Plugs, Sockets and Connectors to include DIN 180°-240° Inline 3-6 Pin, Speakers, Phono, Jack Stereo and Mono etc Valued at well over £3 normal Order No. SX25.

Our Price **1.50** per pak. Guaranteed to save you money.

SX26	3 Pcs of 6 pin 240° DIN Pins and Chassis Sockets	50p
SX27A	60 Assorted Polystyrene Bead Capacitors Type 9500 Series PPD	£1.00
SX28A	50 Assorted Silver Mica Caps. 5.6pF-150pF	£1.00
SX29A	50 Assorted Silver Mica Caps. 180pF-470pF	£1.00
SX30A	50 High Voltage Disc Ceramics 750v min up to 8KV Assorted useful values	£1.00
SX31A	50 Wirewound 9 watt (avg) Resistors Assorted values 1ohm-12K	£1.00

"CAPABLE CAPACITOR PAKS"

Pak No.	Qty*	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 1pF-56pF	£1
SX19	100	Mixed Ceramics 68pF-0.5mF	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50-1000mF	£1
SX24	20	Tantalum Beads, mixed	£1

*Quantities approximate, count by weight.

BARGAINS

SX91	20 x Large 2" RED LED	£1
SX42	20 small .125 Red LED's	£1
SX43	10 Rectangular Green LED's 2	£1
SX46	30 Assorted Zener Diodes 250mW 2 watt mixed voltages, all coded. New.	£1
SX47	4 Black Instrument Knobs—winged with pointer 1/4" Standard screw. Fit size 29 x 20mm.	£1
SX49	20 Assorted Slider Knobs, Black/Chrome etc.	£1
SX80	12 Neons and Filament Lamps. Low voltage and mains — various types and colours — some panel mounting	£1

BRAND NEW LCD DISPLAY MULTITESTER.

RE 188m
LCD 10 MEGOHM INPUT IMPEDANCE
"3 1/2" digit *16 ranges plus hFE test facility for PNP and NPN transistors *Auto zero, auto polarity *Single-handed, pushbutton operation *Over range indication *12.5mm (1/2-inch) large LCD readout *Diode check *Fused circuit protection *Test leads, battery and instructions included.
Max indication 1999 or — 1999
Polarity indication Negative only.
Positive readings appear without + sign.
Input impedance 10 Megohms
Zero adjust Automatic
Sampling time 250 milliseconds
Temperature range — 5°C to 50°C
Power Supply 1 x PP3 or equivalent 9v battery

Consumption 20mW
Size 155 x 88 x 31mm

RANGES

DC Voltage 0-200mV
0-2-20-200-1000V. Acc: 0.8%
AC Voltage 0-200-1000V.
Acc. 1.2% DC Current 0-200uA.
0-2-20-200mA, 0-10 A. Acc: 1.2%
Resistance 0-2-20-200K ohms.
0-2 Megohms. Acc: 1%
BI-PAK VERY LOWEST POSS PRICE
£35.00 each



MINI VICE

This small cast iron quality made vice will clamp on to any bench or table having a max thickness of 1 1/2". The 2 1/2" jaws open to a max of 1 1/2". Approx size 80 x 120 x 66mm.
Bi-Pak's Mini Vice at a Mini Price only

£2.50

ORDER NO. SX82



The Third and Fourth Hand...

... you always need but have never got "until now". This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2" diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier. Our Price with magnifier as illustrated ORDER NO. T402 **£5.50**
Without magnifier ORDER NO. T400 **£4.75**



SX52 6 Black Heatsink will fit TO-3 and TO-220. Ready drilled. Hall price value. **£1**

SX53 1 Power finned Heatsink. This heatsink gives the greatest possible heat dissipation in the smallest space owing to its unique staggered fin design, pre drilled.

TO-3 Size 45mm square x 20mm high. 40p


TO-66 size. 35mm x 30mm x 12mm. 35p

SX54 1 Heat Efficiency Power Finned Heatsink 90mm x 80mm x 35mm High. Drilled to take up to 4 x TO-3 devices **£1.50** each



BI-PAK SOLDER-DESOLDER KIT

Kit comprises ORDER NO. SX80
1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl 3/16" (4.7mm) bit.
1 Quality Desoldering pump. High Suction with automatic ejection. Knurled, anti-corrosive casing and telon nozzle.
1.5 metres of De soldering braid on plastic dispenser.
2 yds (1.83m) Resin Cored Solder on Card.
1 Heat Shunt tool tweezer Type.
Total Retail Value over **£12.00**
OUR SPECIAL KIT PRICE **£8.95**

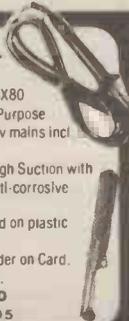

BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
1 Expo Mini Drill 10,000RPM 12v DC incl 3 collets & 1 x 1mm Twist bit.
1 Sheet PCB Transfers. 210mm x 150mm.
1 Etch Resist Pen.
1 1/2lb pack FERRIC CHLORIDE crystals.
3 sheets copper clad board.
2 sheets Fibreglass copper clad board.
Full instructions for making your own PCB boards.
Retail Value over **£15.00**
OUR BI-PAK SPECIAL KIT PRICE **£9.75**
ORDER NO. SX81



PROGRAMMABLE UNI-JUNCTION TRANSISTOR "PUT" case TO106 plastic MEU22 Similar to 2N8027/8028 PNP Silicon
Price: 1-9 10-49 50-99 100+ Normal Retail Price £0.35 each
Each: 20p 18p 15p 13p

SX33A	6 small (min) (SDST/SPDT Toggle Switches 240v 5amp	£1.00
SX35A	6 small (min) Rocker Switches 240v 5amp	£1.00
SX32A	12 Assorted Jack & Phono plugs, sockets and adaptors, 2.5m, 3.5mm and standard sizes	£1.00
SX71	50 BC108 "Fallouts" Manufacturers out of spec on volts or gain You test.	£1.00
SX72	A mixed bundle of Copper clad Board Fibre glass and paper. Single and double sided. A fantastic bargain	£1.00

5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module.

Specification
• Max Power Supply 30v • Power Output 5 watts RMS • Load Impedance 8-16 ohms • Frequency response 50Hz to 25KHz—3db • Sensitivity 70mv for full output • Input Impedance 50k ohms • Size 65 x 64 x 30mm • Total Harmonic distortion less than 5%
BI-PAK'S give away price

£2.25

You could not build one for this price.

MORE BARGAINS!

SX51	60 metres PVC covered Hook-up wire single and stranded. Mixed colours.	£1
SX58	25 Assorted TTL Gates 7400 Series 7401-7460	£1
SX59	10 Assorted flip Flops and MSI TTL	£1
SX60	20 Assorted Slider Potentiometers	£1
SX62	40 Assorted Pre-Settors/Vert etc.	£1
SX79	10 Reed Switches — glass type 3 Micro Switches — with lever	£1

TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical. Resistors of mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes. SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel. No rubbish all identifiable and valued in current catalogues at well over £25.00. Our Fight Against Inflation

— Beat the Budget
— Down with Depression

Price —
JUST £6.50.

BI-PAK

Send your orders to Dept HE12 BI-PAK PO BOX 6 WARE HERTS
SHOP AT 3 BALDOCK ST WARE HERTS
TERMS CASH WITH ORDER, SAME DAY DESPATCH ACCESS
BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRO 388 7006
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING



Use your credit card Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail
Remember you must add VAT at 15% to your order.
Total Postage add 75p per total order.

THE PROJECT KITS

I.C.S
TRANSISTORS
CAPACITORS

TOOLS
RESISTORS
HARDWARE

CASES
KITS
MAGENTA

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for H.E. Projects. We supply carefully selected sets of parts to enable you to construct H.E. projects. Kits include ALL the electronics and hardware needed. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of H.E. which includes the project — you will need to order the instruction reprint at an extra 45p each.

Reprints available separately 45p each + p. & p. 40p.

- ODOMETER Nov. 82 £14.98
DIANA V.C.O. Nov 82 £4.89
- FLASH POINT ALARM Oct 82 £19.98
CB SQUELCH UNIT Oct 82 £9.19
- 'JUNIOR' SLOT CAR CONTROLLER
Sept 82 £5.60 less case.
- ZX INTERFACE BOARD Sept 82 inc
edge con £11.33.
- AUDIO ANALYSER Aug 82 less case
£63.97.
- SWR METER Aug 82 £8.95.
T.V.I. FILTER July 82 £5.33
AUTO WAH June 82 £18.98 inc case or
£12.28 less case.
- AUTO GREENHOUSE SPRINKLER
June 82 £15.38 less pump and power
supply (12V 2A).
- TELEPHONE TIMER June 82 £33.42 less
power supply (suitable type below).
- POWER SUPPLY DESIGN 12V 500mA.
June 82 £9.98
- ECHO REVERB UNIT May 82. Less case
£33.98. Economy case WB3 £3.76 extra
- DIGITAL THERMOMETER May 82 ex-
cluding case + bezel £16.90
- AUDIO SIGNAL GENERATOR May 82
£20.98.
- CABLE TRACKER May 82 £9.98
DIGITAL CAPACITANCE METER Apr
82 £21.37
- SIGNAL TRACER Apr 82 £3.86
BIKE ALARM Apr 82 £11.74
DIGITAL DICE Mar 82 £7.29
BICYCLE SIREN Mar 82 £10.89
NOISELESS FUZZBOX Feb 82 £10.45
MASHHEAD AMPLIFIER Feb 82 £14.74
DRUM SYNTHESIZER Dec 81. Full kit
£21.37
- GUITAR HEADPHONE AMPLIFIER
Dec 81 £3.72
- IN CAR CASSETTE POWER SUPPLY
Dec 81 £4.77
- SCRATCH FILTER Nov 81 Mono £5.82
Stereo £8.98
- LED VU METER Nov 81 less case £4.87
SIMPLE STYLUS ORGAN Nov 81 less
case £4.98
- METRONOME Nov 81 £12.71
- TELEPHONE BELL REPEATER Oct 81
£13.67
- Med linking wire extra 14p metre
COMBINATION LOCK Oct 81 less
solenoid £18.65
- BABY ALARM Oct 81 £8.70. Fig 8 linking
wire 7p metre
- 'DIANA' METAL LOCATOR Sept 81
£34.50
- POWERPACK Sept 81 £10.25
REACTION TESTER GAME Sept 81
£12.81
- VARIABLE BENCH POWER SUPPLY
Aug 81 £26.98
- ULTRASOUND BURGLAR ALARM
July 81 £19.98
- ELECTRONIC DOOR BUZZER July 81
£5.98
- ELECTRONIC METRONOME July 81
£4.99
- CONTINUITY CHECKER June 81 £5.71
ENVELOPE GENERATOR June 81
£17.98
- AUDIO MIXER June 81 £5.33
PUBLIC ADDRESS AMPLIFIER March
81 £19.48. Extras - horn speakers £6.83
each. PA MIC £4.40
- FUZZBOX March 81 £10.98
- WINDSCREEN WIPER CONTROLLER
March 81 £8.20
- STEAM LOCO WHISTLE March 81
£12.98
- PHOTOGRAPHIC TIMER March 81
£3.50
- HEARTBEAT MONITOR Feb 81 £24.98
- TWO-TONE TRAIN HORN Feb 81 £5.60
less case
medium wave radio Feb 81 £8.20
- BENCH AMP Jan 81 £10.80
- NICAD CHARGER Jan 81 £8.20
- CHUFFER Jan 81, less case £7.53
- BATTERY CHARGE MONITOR Dec 82
£5.77
- MEMORY BANK — MINI SYNTH-
ESIZER Nov & Dec 80 £29.98
- TRANSISTOR TESTER Nov 81 £6.54 inc
test leads
- GUITAR PRE-AMP Nov 80 £6.65
case (diecast) extra £2.29
- INTRUDER ALARM Oct 80 £20.98
- TOUCH SWITCH Sept 80 £2.75 less case &
contacts
- guitar phaser Sept 80 £16.28
- SOUND OPERATED FLASH TRIGGER
July 80 no skt £5.33
- FOG HORN June 80 £6.64
- SPEED CONTROLLER FOR R/C April 80
£17.55 (less case)
- DIGITAL FREQUENCY METER April 80
£39.98
- DIGI-DICE Jan 80 £11.73
- GUITAR TUNER Nov 79 £12.82
- CAR ALARM Feb 79 £12.91

MORE PROJECT KITS — SIMILAR STYLE TO H.E.

INSTRUCTIONS INCLUDED (SEPARATELY 45p EACH)
PLEASE QUOTE REF. NO. WHEN ORDERING

- B1 PEST CONTROL 'Ultrasonic cat
scarer' £7.65
- B2 COMPONENT TESTER £8.88
- B4 GUITAR NOTE EXPANDER £17.98
- B5 CAMERA OR FLASH GUN
TRIGGER Infra red system £12.51
- B6 SIMPLE INFRA RED REMOTE
CONTROL £17.20
- B7 0-12V POWER SUPPLY £17.98
- B9 SOUND TO LIGHT — single channel
£8.42
- B10 THREE CHANNEL SOUND TO
LIGHT £21.44
- B11 IN SITU TRANSISTOR TESTER
£6.98
- B12 WEIRD SOUND EFFECTS
GENERATOR £5.98
- B13 AUDIBLE VISUAL METRONOME
£5.98
- B14 ELECTRONIC DICE £5.71
- B16 MINI EGG TIMER £4.34
- B18 LED JEWELLERY — Cross brooch
£2.77 Star brooch £9.91 Spiral brooch
£7.98

**MORE KITS AND
COMPONENTS
IN OUR LISTS**
FREE PRICE LIST
Price list included with
orders or send sae (9 x 4)
CONTAINS LOTS MORE
KITS, PCBs &
COMPONENTS

1982 ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all in-
cluded. Up-to-date price list enclosed. All products
are stock lines for fast delivery.
Sends 80p in stamps or add 80p to order.

MORE H.E. PLUS E.E. and E.T.I. PROJECT.
KITS IN THE PRICE LIST

MAGENTA gives you FAST DELIVERY OF QUALITY COMPONENTS & KITS.
All products are stock lines and are new & full specification. We give personal service &
quality products to all our customers—HAVE YOU TRIED US?

MAGENTA ELECTRONICS LTD

HS31, 135 HUNTER ST., BURTON-ON-TRENT, STAFFS.

DE14 2ST. 0283 65435. MON-FRI 9-5. MAIL ORDER ONLY
ADD 45p P&P TO ALL ORDERS PRICES INC VAT

ACCESS and BARCLAYCARD (VISA)
ORDERS ACCEPTED BY PHONE OR
POST.
SAE ALL ENQUIRIES.

Prices inc. VAT
OFFICIAL ORDERS WELCOME
OVERSEAS. Payment must be in sterling.
IRISH REPUBLIC and BFPPO: UK PRICES.
EUROPE: UK PRICES plus 10%.
ELSEWHERE: write for quote.

SOLDERING / TOOLS

- ANEX X5 SOLDERING IRON 25W £5.48
- SOLDERING IRON STAND £1.98
- SPARE BITS. Small standard, large,
65p each. For X5 + X25 99p
- SOLDER CARTON £1.84
- DESOLDER BRAID 69p
- HEAT SINK TWEEZERS 29p
- DESOLDER PUMP £6.48
- HOW TO SOLDER LEAFLET 12p
- LOW COST CUTTERS £1.69
- LOW COST LONG NOSE PLIERS £1.68
- WIRE STRIPPERS & CUTTERS £2.69

HELPING HANDS JIG £6.30

Heavy base. Six ball and socket
joints allow infinite variation of clips
through 360°. Has 2 1/2" diameter
(25 x) magnifier attached, used and
recommended by our staff.

VERO SPOT FACE CUTTER .. £1.49

PIN INSERTION TOOL £1.98

VEROPINS (pk of 100) 0.1" 52p

MULTIMETER TYPE 1 (11,000 opv) £5.48

MULTIMETER TYPE 2 (20,000 opv)
with transistor tester. Very good
..... £14.75

CROCODILE CLIP TEST LEAD SET.
10 leads with 20 clips 99p

- RESISTOR COLOUR CODE 21p
- CALCULATOR 49p
- CONNECTING WIRE PACK TYPE
ED. 11 colours 49p
- ILLUMINATED MAGNIFIERS
Small 2" dia. (5x mag.) £1.14
Large 3" dia. (4x mag.) £2.40
- CAST IRON VICE £2.98
- SCREWDRIVER SET £1.98
- POCKET TOOL SET £3.98
- DENTISTS INSPECTION MIRROR £2.85
- JEWELLERS EYEGLOSS £1.50
- PLASTIC TWEEZERS 69p
- PAIR OF PROBES WITH LEADS
(cc) 77p



MULTIMETER TYPE 2 - YN360 TR, £14.75

20,000 opv. Includes transistor tester.
AC + DC volts. DC current. 4 very
useful resistance ranges.
We've used it and we like it.

- | | |
|--------------------------------------|-----------------------------------|
| SPEAKERS. Miniature, 8 ohm 87p | MIN. BUZZERS. 6V. 50p. 9V. £1-10. |
| 64-75 ohm 89p | 12V. 65p. |
| CRYSTAL EARPIECE 65p | MAGNETIC EARPIECE 15p |
| MONO HEADPHONES £2-95 | STEREO HEADPHONES £4-35 |
| TELEPHONE PICK-UP COIL 72p | F.M. AERIAL 49p |
-
- | | | |
|--|-----------------------------------|-------------------|
| VEROBOARD 0.1" COPPER STRIPS 1
10 strips 24 holes £1.20 per 5 | PP3 CLIPS 10p | PANEL METERS |
| 24 strips 37 holes 78p | PP3 CLIPS 11p | 50uA; 100uA; 1mA. |
| 24 strips 50 holes 89p | | 1A, 25V. 100uA-0- |
| 36 strips 37 holes 89p | EUROBREADBOARD £6.20 | 100uA; 5A. AU |
| 36 strips 50 holes 99p | S DEC BREADBOARD £3.98 | £4.98 each. State |
| Terminal pins 0.1" 52p/100 | BIMBOARD 1 BREADBOARD £6.98 | value. |
| | VEROBLOC BREADBOARD £4.20 | |

BOOKS

- SEMICONDUCTOR DATA BOOK Newnes £5.90
- ELECTRONIC PROJECTS FOR HOME
SECURITY £3.35
- ELECT. PROJECTS IN PHOTOGRAPHY
..... £3.35
- 110 ELECT. ALARM PROJECTS
MODEL RAILWAY PROJECTS £1.95
- BASIC ELECTRONICS. Theory & practice
..... £7.98
- BEGINNERS GUIDE TO BUILDING ELECT.
PROJECTS £1.50

ADVENTURES WITH MICROELECTRONICS

Similar to 'Electronics' below.
Uses I.C.s. Includes dice, elec-
tronic organ, doorbell, reaction
timer, radio, etc. Based on Bim-
board 1 bread board.
Adventures with
Microelectronics. £2.55
Component pack £29.64 less
battery.

ADVENTURES WITH ELECTRONICS

by Tom
Duncan

An easy to follow book suitable for all ages. Ideal for beginners.
No soldering, uses an S-Dec breadboard. Gives clear instructions
with lots of pictures. 16 projects—including three radios, siren,
metronome, organ, intercom, timer, etc. Helps you learn about
electronic components and how circuits work. Component pack
includes an S-Dec breadboard and all the components for the
projects.
Adventures with Electronics £2.40. Component pack £18.98
less battery.

ADVENTURES WITH DIGITAL ELECTRONICS

New book by Tom Duncan in the popular 'Adventures' series. This book of
entertaining and instructive projects is designed for hobbyists, and students. It
provides a stepping stone to the microprocessor.
The first part deals with the properties of some basic ICs used in digital
electronics.
The second part gives details of how to build eight devices — shooting gallery, 2
way traffic lights, electronic adder, computer space invaders game etc.
For each project there is an explanation of 'how it works' and also suggestions for
'things to try'.
No soldering — all circuits built on 2 Bimboard 1 breadboards.
Adventures with Digital Electronics book £3.25. Component pack £42.50 ref
EHDC. All the components needed including 2 breadboards and hexadecimal
keyboard. Available less breadboards £29.98 ref EHDF. Both less battery.

RADIO RULES

Ian Sinclair

Single side band transmitters and receivers.

Single Sideband

If you think back to amplitude modulation again, you may remember that business of sidebands. When a carrier is amplitude modulated, the output signal contains the carrier frequency and both sets of sidebands (sum and difference), all requiring power at the PA stage to transmit. All the information of the audio signal is carried in one sideband, however (either one), and none by the carrier, so that this well-worn double-sideband scheme is very wasteful of transmitter power. The solution is to use only one sideband, eliminating the other sideband and most of the carrier. This system is called single-sideband-suppressed-carrier, usually abbreviated to SSB, though this could also refer to systems that eliminate one sideband but retain most of the carrier.

Starting with transmitters this time, how do we achieve these two aims of removing one sideband and most of the carrier? Once again, there are several methods, but the most popular one consists of using a balanced modulator to remove the carrier, and filtering to remove the unwanted sideband. A balanced modulator is a circuit to which both carrier and audio signal can be applied. If there is no audio signal, then there is no output from the circuit, but adding an audio signal spoils the balance of the circuit and the sidebands of the modulated carrier form the output. There is very little trace of the carrier frequency in the output.

A simple type of balanced modulator is illustrated in Figure 1. This is a bridge or ring modulator and its action depends on the use of the audio signal to bias a set of diodes into conduction. Imagine that there is no audio signal, so that the audio input to the diode bridge at A is at earth voltage as far as signals are concerned. The carrier signal is injected at a point where the voltage lies exactly between the bridge outputs, so that the carrier signals to the transformer primary ends are in phase. In this condition, there is no output.

Now imagine that an audio signal is applied and that the audio voltage has reached its positive peak. Diodes D1, D2 will conduct when the carrier voltage is zero, putting a bias voltage onto the output line, at X. Now the carrier signal is no longer balanced because, when the carrier has its negative peak at X and its positive peak at Y, the diodes D1, D4 will conduct carrier signal, and D2, D3 will not conduct. This will cause some out-of-phase carrier signal to reach the transformer. The situation reverses when the audio signal at A goes to its negative peak. Now diodes D4, D3 conduct when the carrier voltage is zero, but when the carrier wave is positive at Y, negative at X, then D1, D4 don't conduct but D1, D2, D3 do, producing a signal to the transformer again. These signals to the transformer are of sidebands only because no carrier can pass, by itself.

The circuit works well, but needs careful setting up. An alternative is to use a balanced-modulator IC — the Motorola MC1496G is an old favourite for this task. Even so, these methods can never totally remove all traces of carrier, but suppression of 30 to 50 db can be easily achieved.

The next part of single sideband modulation is the filtering system which removes one sideband. Unless you can test and adjust crystal filters, the filter units just have to be bought — these can be quartz crystal types or surface wave types. The filter characteristic can be arranged so that it contributes to the suppression of the carrier, as well as removing the unwanted sideband.

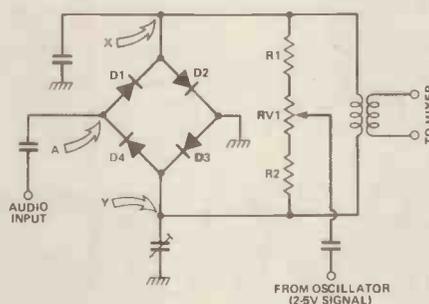


Figure 1. A bridge or Ring Modulator, which eliminates the carrier frequency from the output, is the first and most important stage in SSB transmission.

The combination of balanced modulator and filter is the complete single-sideband generator. The whole system can be designed around a low carrier frequency — 455 kHz is a favourite — or at high frequencies such as 9 MHz — the choice is fixed by the availability of commercially-built filters. You don't, of course, transmit at either of these frequencies. To reach the actual transmitting frequency, you would normally think of using multiplier stages, but this step is taboo with SSB transmitter circuits because multiplying up the carrier frequency means multiplying up the bandwidth of the sidebands. The alternative is 'frequency mixing', using another mixer stage to obtain a signal which is the sum of the modulated frequency and another crystal-controlled frequency.

Once the correct frequency has been reached (and several mixings may be needed, particularly if the original modulation was at 455 kHz and the final frequency is VHF), power amplification must use Class A or Class B circuits rather than Class C, to avoid distortion. This will make the efficiency of the output stage lower, but the effective power of the modulated signal, as com-

pared to a double-sideband signal with full carrier is so much greater that the loss is acceptable. As a guide, if we assume that the output stage is 66.7% efficient (meaning that 2/3 of the DC power fed to the output stage causes useful output), then the maximum allowed DC power of 150 W will cause an RF power of 100 W. This is all useful power however, so that the way in which we measure SSB power is in terms of what is called 'peak envelope power', which is four times the actual output power (100 W in this example). This is an approximation, but it implies that the SSB signal is equivalent in transmitted power to a conventional AM signal of four times its output power.

Problems, problems

Problems start when we want to receive a SSB signal. To start with, the demodulator must be a balanced type, operating like the modulator in reverse, and it has to be fed with a carrier signal of the correct frequency and phase. This is most easily arranged if transmitter and receiver share the same oscillator in the form of a transceiver, as the oscillator section of the transmitter can then provide a signal of exactly the correct frequency and phase to the demodulator. However, all of this makes a single-sideband rig a very complicated piece of goods, particularly if it is to be used at several frequencies, because there is a convention that the lower sideband is used at frequencies below 10 MHz while the upper sideband is used at frequencies above 10 MHz. Not many readers are likely to get involved in SSB as a do-it-yourself project! It's advantages, however, make impressive reading, and even more impressive listening. To start with, the bandwidth of the SSB signal is the same as that of the audio signal, no more. This means that a lot more SSB rigs can use a band than conventional AM rigs. There is also a gain in range, because all of the output power of the SSB transmitter is concentrated on the one sideband which the receiver uses. In addition, SSB is much less liable to atmospheric disturbance effects, such as fading and blasting, than conventional AM or even FM. The advantages of SSB can be increased by using speech-processing units which ensure that the modulation is always near the upper limit while you are speaking. SSB rigs of good quality are never cheap, but they represent just about the optimum in modern radio communications and a dream for every amateur licence holder to aspire to.



Due to space limitations in the November issue, this portion of Radio Rules was held over till December.

Next month we will back-track to examine AM Receivers.

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite

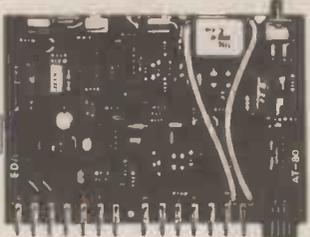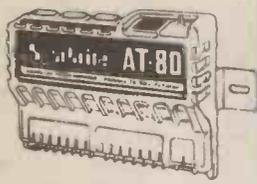BRANDLEADING ELECTRONICS
NOW AVAILABLE IN KIT FORM




AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen ● Fits all 12V neg earth vehicles
- Over 250 components to assemble

VOYAGER Car Drive Computer

- A most sophisticated accessory. ● Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd. ● Affords 12 functions centred on Fuel, Speed, Distance and Time. ● Visual and Audible alarms, warning of Excess Speed, Frost/Ice, Lights-left-on. ● Facility to operate LOG and TRIP functions independently or synchronously. ● Large 10mm high 400ft-L fluorescent display with auto intensity. ● Unique speed and fuel transducers giving a programmed accuracy of + or - 1%. ● Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours. ● Full Imperial and Metric calibrations. ● Over 300 components to assemble. A real challenge for the electronics enthusiast!

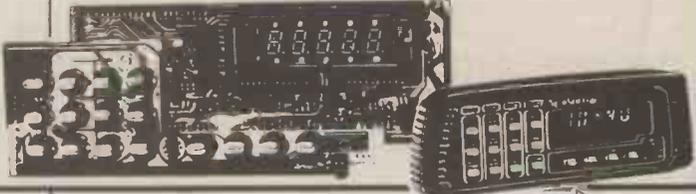


SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles


TX1002 Electronic Ignition

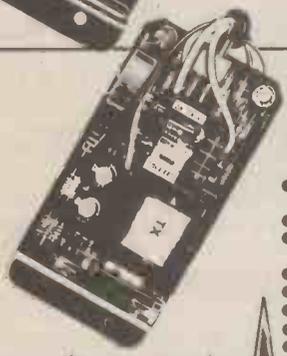- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge ● Three position changeover switch ● Distributor triggerhead adaptors included ● Die cast weatherproof case ● Clip-to-coil or remote mounting facility ● Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles ● Over 145 components to assemble.



SX2000 Electronic Ignition

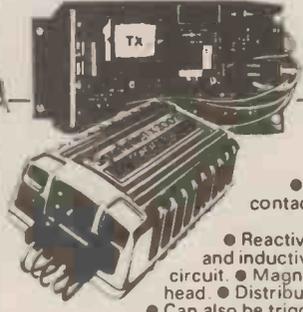- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles



TX2002 Electronic Ignition

- The ultimate system ● Switchable contactless. ● Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive. ● Extended coil energy storage circuit. ● Magnetic contactless distributor triggerhead. ● Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers.
- Die cast waterproof case with clip-to-coil fitting ● Fits majority of 4 and 6 cylinder 12v neg. earth vehicles.
- Over 150 components to assemble

All SPARKRITE products and designs are fully covered by one or more World Patents.

SPECIAL OFFER

"FREE" MAGIDICE KIT WITH ALL ORDERS OVER £45.00



MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

SPARKRITE

82 Bath Street, Walsall, West Midlands, WS1 3DE England.

tel: (0922) 614791 Allow 28 days for delivery

	SELF ASSEMBLY KIT
SX 1000	£12.95
SX 2000	£19.95
TX 1002	£22.95
TX 2002	£32.95
AT 80	£32.95
VOYAGER	£64.95
MAGIDICE	£9.95

PRICES INC. VAT. POSTAGE & PACKING

NAME _____ HE12
ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF _____

CHEQUE NO. _____

PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD
SEND ONLY SAE IF BROCHURE IS REQUIRED

BRANDLEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!

Hobby Electronics, December 1982

Amateur radio will become much clearer after 3rd Dec.

The radio market has become more complex. Things have become more confused.

Wires get crossed as new equipment floods onto the market.

At the end of the day, even the most avid enthusiast spends more time trying to find out about new equipment than on the airwaves using it.

As for the novice?

They stand little chance of picking anything up at all.

So we've decided to clear things up.

On December 3rd our new magazine Ham Radio Today begins.

Not a magazine you need a degree in electronics to decipher.

Or one that still calls your gear a wireless.

Rather a magazine that simply clarifies the vast range of electronic gadgetry available.

Lists new equipment, analyses its performance.

Thorough reviews, special features, news items and constructional projects.

In a clear and concise way that will give everyone a perfect 5 + 9.

Ham Radio Today.

Tomorrow... tune in and find out, 73.

**HAM
RADIO**

COMPONENTS FOR COMPUTING

This is the first of a series of articles in which the components of microcomputer systems will be discussed. We will investigate the many aspects of each type of component, including general functions and areas of application, internal circuit operation, external circuits and the range of products on the market.

WE WILL START by describing Input/Output (I/O) port components. This may not seem entirely logical, but it follows from our Micro-Trainer series of earlier this year. Consequently, in this issue alone, there will be specific references to the Micro-Trainer when the programming of I/O ports is considered.

What Is An I/O Port?

A port, whether input or output, is a device that interfaces between the 'raw' hardware of a computer's central processing unit (CPU) and the external machinery of a control system. In its simplest form, a port consists of a data latch or register connected to the three busses (address, data and control) of the CPU. The diagram of Figure 1 shows an eight bit output port and an eight bit input port connected to a simple microprocessor system. The ports have an eight bit capacity simply because the microprocessor has an eight bit data bus, and can therefore transfer data eight bits at a time!

The output port has eight inputs connected to the data bus and eight separate outputs for connection to external circuits, and a strobe. The outputs follow the logic states of the inputs for as long as the strobe input is high; however when the strobe is taken low, the data at the outputs is frozen or 'latched' indefinitely. An IC of this sort is called an 'Octal Transparent Latch', and a 74LS373 is a typical example using TTL Technology in the microprocessor system of Figure 1, the strobe is derived from the \overline{WR} signal of the control bus and the decoded address bus. Data will be latched into the port only when the MPU attempts to write to a specific address, as determined by the address-decode logic. This configuration is called 'Memory-Mapped I/O' because the port appears to the MPU as a single byte of memory, in this case a write-only memory location. Using simple 'store' instructions, the MPU is able to control the state of eight logical outputs, each of which can be interfaced to anything from a LED to a large industrial machine,

using no more than a few transistors and relays.

The input port, as shown in Figure 1, is also an octal latch but this time the outputs are wired to the data bus and the inputs are taken from the external circuit. For an input port, the latch must have (like the 74LS373) a control which can 'tri-state' the outputs to the data bus; this means that the outputs can go to a high impedance state, and thus have no effect upon the data bus when it is being used by other devices, such as RAM or ROM. The output control signal is decoded from the address bus and the \overline{RD} signal so as to 'map' the port to the desired memory location. The strobe to an input latch is not synchronised with the MPU as with the output port; it has to be provided by the external circuit to synchronise with incoming data. In certain applications (A/D conversion being the best example) the data presented to the MPU's input port may not be valid (true) at all times, which explains the reason for an external synchronising pulse.

However, the MPU is often required

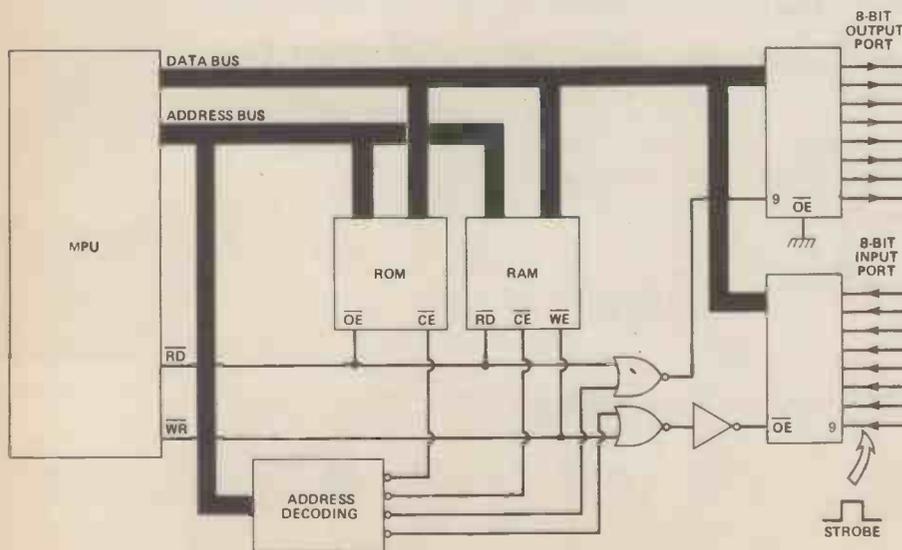


Figure 1. A simple microprocessor system with one output and one input port.

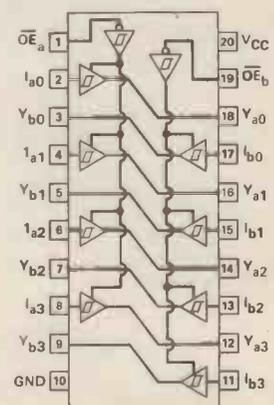


Figure 2. The logic diagram and pin outs of the 74LS244. The OE inputs latch the outputs to the high impedance (off) state.

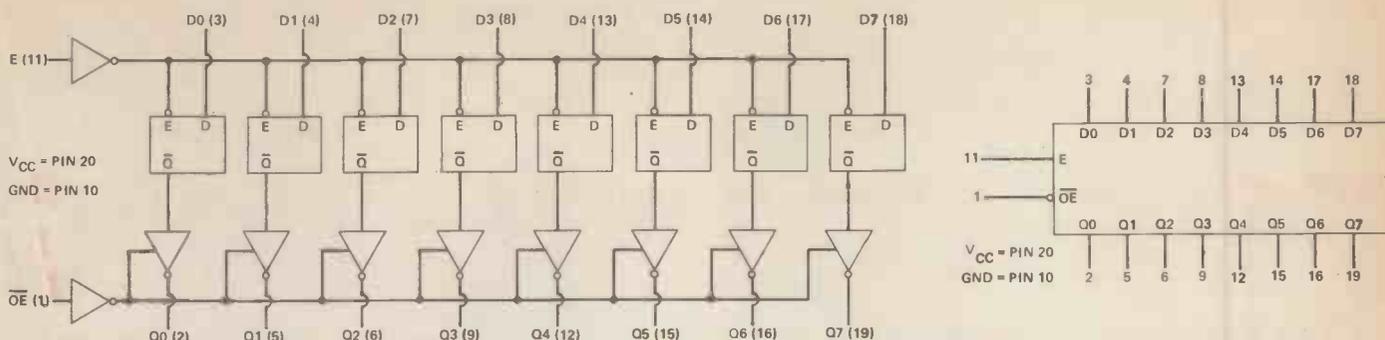


Figure 3. The logic diagram (above) and pin-outs (right) of the 74LS373. Data is latched by taking the E input low; a high on the OE input forces the outputs to the high impedance state.

only to sample the inputs periodically (if, for example, they connect to a set of logically independent switches) and in this case, latching of data is unnecessary; an "Octal Tri-State Buffer" (such as a 74LS244) will then be sufficient as an input port.

Memory mapped I/O is a system which can be readily applied to any microprocessor; yet there is a common alternative which is worth mentioning. "I/O Mapping" is a system which is unique for each type of microprocessor (some simply do not have the facility, eg. the 6800 and the 6502) because it requires specific sets of hardware and instructions. The 1802 has a three-bit address bus, separate from the normal address bus, which can be decoded to provide 'enables' for up to seven I/O devices; these addresses are generated only in response to special instructions (INP1 - INP7, OUT1 - OUT7).

Other processors (eg. the Z80 and many other Intel products) place I/O addresses (0-255) on the usual address bus and have a separate control line to indicate whether the instruction is to be executed on memory or on I/O.

I/O ports can easily be constructed from a few TTL chips, however the manufacturers of all microprocessor types offer more 'clever' devices designed for flexibility in applications, in a

single low cost package, with each device type intended for a particular microprocessor. Most of these contain several ports within a chip, and can be programmed to behave either as input or output devices; many have other interesting facilities, as we shall see.

The 8255

It is impossible, in these few pages, to describe every I/O device on the market so we shall concentrate on just one — the 8255. This device is intended to interface with the Intel 8080 and 8085 family of microprocessors; however, it can be used readily with the Z80 and, of course, the 1802, as in the Micro-Trainer. It is one of the most versatile PPIs (Programmable Peripheral Interface) available and has recently become very inexpensive.

Referring to the block diagram of Figure 4 and the pin diagram of Figure 5, you will see that the 8255 has three eight-bit ports within a 40 pin package. Port A (PA0-PA7) and Port B (PB0-PB7) can be separately programmed as either input or output, while Port C is logically divided into individually programmed upper (PC4-PC7) and lower (PC0-PC3) portions.

The 8255 possesses all the necessary signal inputs to interface directly to the CPU. Signals D0-D7 con-

nect directly onto the data bus, for bidirectional transfer of data between CPU and the ports and, likewise, the signals \overline{RD} and \overline{WR} connect directly to the corresponding signal lines of the CPU. The control signal \overline{CS} (Chip Select) is used to allow the CPU to use the 8255. For example, if \overline{CS} is provided with a logic low, decoded from the address bus (the Micro-Trainer uses an address in the range 2000H to 2003H) the device will be 'enabled'.

The signals A0 and A1, the two least significant bits (LSBs) of the address bus, will select one of the four internal registers, according to the address; three of these registers are, obviously, the ports A, B and C, while the fourth is a control register used for programming the device. These addresses (summaris-


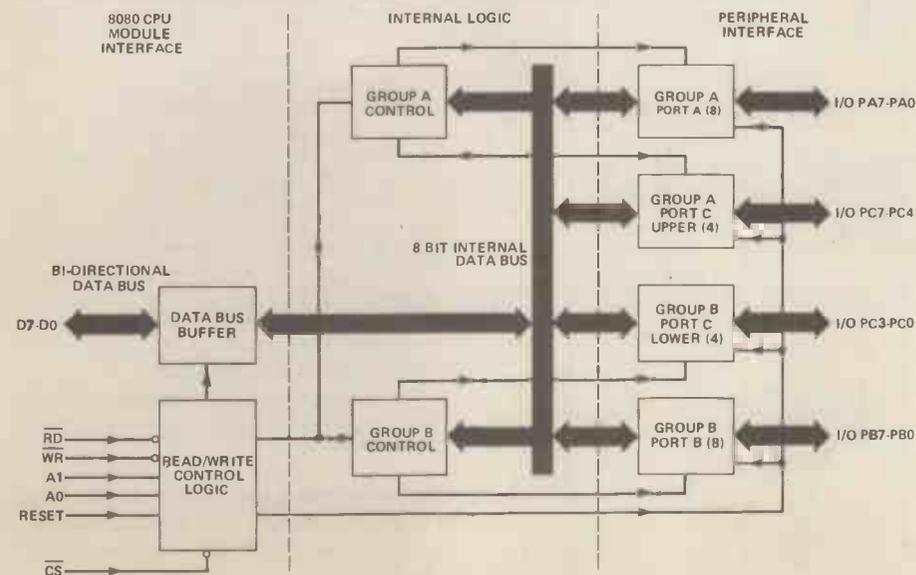


Figure 4. The logic diagram of the 8255 PPI; the ports are split into two groups for control purposes.

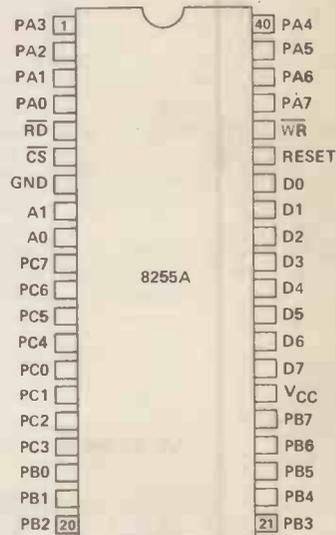

PIN NAMES

D7-D0	DATA BUS (BI-DIRECTIONAL)
RESET	RESET INPUT
\overline{CS}	CHIP SELECT
\overline{RD}	READ INPUT
\overline{WR}	WRITE INPUT
A0,A1	PORT ADDRESS
PA7-PA0	PORT A (BIT)
PB7-PB0	PORT B (BIT)
PC7-PC0	PORT C (BIT)
V _{CC}	+5 VOLTS
GND	0 VOLTS

Figure 5. The pin-outs of the 8255 (top) and their meaning (bottom).

A		B		GROUP A			GROUP B	
D4	D3	D1	D0	PORT A	PORT C (UPPER)	#	PORT B	PORT C (LOWER)
0	0	0	0	OUTPUT	OUTPUT	0	OUTPUT	OUTPUT
0	0	0	1	OUTPUT	OUTPUT	1	OUTPUT	INPUT
0	0	1	0	OUTPUT	OUTPUT	2	INPUT	OUTPUT
0	0	1	1	OUTPUT	OUTPUT	3	INPUT	INPUT
0	1	0	0	OUTPUT	INPUT	4	OUTPUT	OUTPUT
0	1	0	1	OUTPUT	INPUT	5	OUTPUT	INPUT
0	1	1	0	OUTPUT	INPUT	6	INPUT	OUTPUT
0	1	1	1	OUTPUT	INPUT	7	INPUT	INPUT
1	0	0	0	INPUT	OUTPUT	8	OUTPUT	OUTPUT
1	0	0	1	INPUT	OUTPUT	9	OUTPUT	INPUT
1	0	1	0	INPUT	OUTPUT	10	INPUT	OUTPUT
1	0	1	1	INPUT	OUTPUT	11	INPUT	INPUT
1	1	0	0	INPUT	INPUT	12	OUTPUT	OUTPUT
1	1	0	1	INPUT	INPUT	13	OUTPUT	INPUT
1	1	1	0	INPUT	INPUT	14	INPUT	OUTPUT
1	1	1	1	INPUT	INPUT	15	INPUT	INPUT

A1	A0	RD	WR	CS	INPUT OPERATION (READ)
0	0	0	1	0	PORT A = DATA BUS
0	1	0	1	0	PORT B = DATA BUS
1	0	0	1	0	PORT C = DATA BUS
					OUTPUT OPERATION (WRITE)
0	0	1	0	0	DATA BUS = PORT A
0	1	1	0	0	DATA BUS = PORT B
1	0	1	0	0	DATA BUS = PORT C
1	1	1	0	0	DATA BUS = CONTROL
					DISABLE FUNCTION
X	X	X	X	1	DATA BUS = 3-STATE
1	1	0	1	0	ILLEGAL CONDITION
X	X	1	1	0	DATA BUS = 3-STATE

X = DON'T CARE

Table 1 (right). The ports can be set up in any of 16 different ways.

Table 2 (above). Ports are addressed, as appropriate under program control. A WRITE instruction to a port set up for Input will be ignored.

ed in Table 3) are used in the Micro-Trainer to access the 8255.

In order to write data to a port, it is simply a matter of executing an 'STR' instruction to the appropriate address, eg:

```
LDI $20 PHI R3
LDI $01 PLO R3; R3 is pointer to Port B
LDI $0F STR (R3); data $0F appears on PBO-PB7
```

Data which has previously been written to an output port can also be read back from the same address — a feature which is not possible with the system of Figure 1.

We have not, so far, discussed how the ports are programmed — but there are no prizes for guessing that the control register is used for this. All the programming information is illustrated in Figures 7 and 8, but some explanation is also required.

The first step is to decide how the ports are to be configured (output or input) then, using the two diagrams, work out a control word on a bit by bit basis. You may be confused by the references to Modes 0, 1 and 2; just assume these bits are set to zeroes. Our description of the 8255's operation are all in Mode 0; the other modes configure certain bits of Port C as 'handshake' lines and as this facility is little used we will not discuss it here!

As an example, suppose we require PA0-PA7 as outputs, PC0-PC3 as outputs and PBO-7, PC4-PC7 all as inputs. Figure 7 tells us that the required data is 10001010 = 8AH so, simply by storing 8AH in the control register, our ports are set up as required. The contents of the control register may not be read back by the CPU. It is also well worth noting that each time a port is configured as an output, the contents are reset to zero.

During power-up, or reset of the MPU, it is normal to reset the 8255 also, using the hardware line RESET (pin 35). When this happens, all ports are configured as inputs in Mode 0, so that the machine's software must initialise the control register, as required, after reset. Figure 8, shows how Port C can be conveniently operated on bit by bit, when programmed as an output. Here, by storing the appropriate data in the control register, a single line of Port C may be set or reset. As an example, again, PC7 has been interfaced to a transistor (Figure 6).

This forms the cassette interface for the Micro-Trainer. It is controlled by a routine in ROM which recognises a LOAD or SAVE instruction, configures Port C (upper) as required, and then toggles bit 7 to transfer the data.

The other seven bits of Port C are all configured as outputs, buffered by a ULN2003 (IC7 in Figure 6), which provides open collector outputs suitable for driving LEDs, relays etc. Each output can sink up to 500mA.

Next month's installment will investigate the hidden depths of memory — RAMs, ROMs, and the multivariate degrees of PROMs.

A1	A0	MICROTRAINER ADDRESS	REGISTER ENABLE
0	0	2000H	PORT A
0	1	2001H	PORT B
1	0	2002H	PORT C
1	1	2003H	CONTROL

Table 3. The Micro-Trainer I/O addresses.

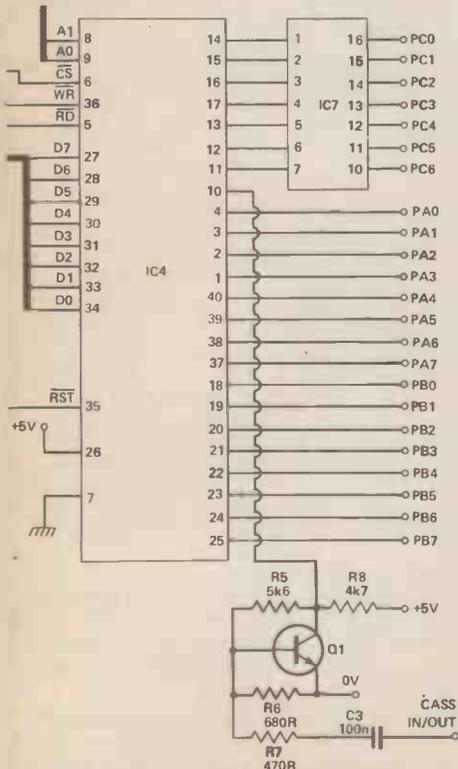


Figure 6. The I/O Port circuits of the Micro-Trainer; IC4 is an 8255.

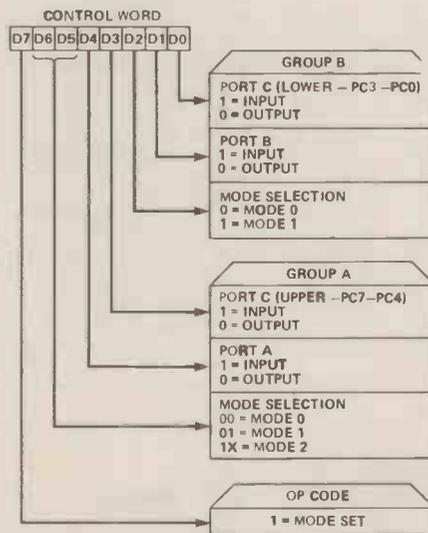


Figure 7. The mode control word can be constructed from this diagram.

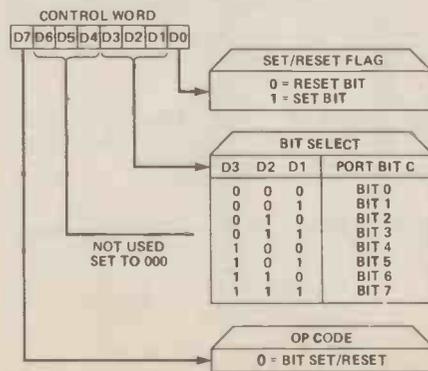


Figure 8. Deriving the control word to set or reset bits of Port C.

INTRODUCING TWO NEW HANDHELD DIGITAL MULTIMETERS

200µA — 10 AMP AC-DC

MODEL 6010

DC accuracy 0.5%

£29.95
plus VAT

1.999

MODEL 7030

DC accuracy 0.1%

£35.95
plus VAT

SPECIFICATION 6010 & 7030

BATTERY: Single av dry cell

BATTERY LIFE: 200 hours

DIMENSIONS: 170 x 89 x 38mm

WEIGHT: 400g inc battery

MODE SELECT: Push button

AC DC CURRENT: 200µA to 10A — 6 Ranges

AC VOLTAGE: 200mV to 750V — 5 Ranges

DC VOLTAGE: 200mV to 1000V — 5 Ranges

RESISTANCE: 200Ω to 20MΩ — 6 Ranges

INPUT IMPEDANCE: 10MΩ

DISPLAY: 3½ Digit 13mm LCD

O/LOAD PROTECTION: All ranges

OTHER FEATURES:

Auto polarity. Auto zero. Battery-low indicator.
Strong ABS plastic case with tilt stand.
Battery and test leads included.
Optional carrying case.



Please add 15% to your order for VAT. Postage & Packing is free of charge. Trade enquiries invited.

ARMON ELECTRONICS LTD.

Cottrell House, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH, England

Telephone: 01-902 4321 (3 lines)

TELEX No. 923985

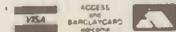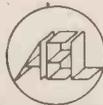

HOME LIGHTING KITS


These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

TD300K Remote Control Dimmer £14.30
MK6 Transmitter for above £ 4.20

TD300K Touchdimmer £ 7.00

TDE/K Extension kit for 2-way switching for TD300K £ 2.00

LD300K Rotary Controlled Dimmer £ 3.50

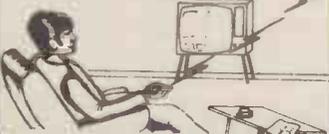

DISCO LIGHTING KITS

DL 1000K

This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. **£14.60**

DLZ1000K

A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. **Only £8.00**

Optional opto input DLA1
Allowing audio ("beat") — light response. **60p**

DL3000K

This 3 channel sound to light kit features zero voltage switching, automatic level control & built in mic. No connections to speaker or amp required. No knobs to adjust — simply connect to mains supply & lamps. (1Kw/Channel) **Only £11.95**

Add 55p postage & packing +15% VAT to total. Overseas Customers; Add £2.50 (Europe), £8.00 (elsewhere) for p&p. Send S.A.E. for further STOCK DETAILS. Goods by return subject to availability.

OPEN

9am to 5pm (Mon to Fri)
10am to 4pm (Sat)



CHRISTMAS PRESENTS GALORE

3-NOTE DOOR CHIME
Based on the SAB0600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions complete. AN IDEAL PROJECT FOR BEGINNERS. **£5.00**
Order as XK102.

LIGHT DIMMER KIT
Contains all components, including front panel and knob, to make a dimmer for lights up to 300W. **£3.50**

MW RADIO KIT
Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2 cms. Requires PP3 9V battery. IDEAL FOR BEGINNERS. **£5.00**

LCD 3½ DIGIT MULTIMETER
16 ranges including DC voltage (200 mw-1000 V) and AC voltage, DC current (200 mA-10 A) and resistance (0.2 M) + NPN & PNP transistor gain and diode check, input impedance 10M. Size 155x88x31 mm. Requires PP3 9v battery. Test leads included. **ONLY £29.00**

STOCKING FILLERS

- PACK (1) 650 Resistors 47 ohm to 10 Mohm - 10 per value £4.00
 - PACK (2) 40 x 16V Electrolytic Capacitors 10uF to 1000uF - 5 per value £3.25
 - PACK (3) 60 Polyester Capacitors 0.01 to 1 uF/250V - 5 per value £5.55
 - PACK (4) 45 Sub-miniature Presets 100 ohm to 1 Mohm - 5 per value £2.90
 - PACK (5) 30 Low Profile IC Sockets 8, 14 and 16 - pin - 10 off each £2.40
 - PACK (6) 25 Red LEDs (5mm dia.) £1.25
 - PACK (7) 20 BC182 NPN General Purpose Transistors £1.20
 - PACK (8) 20 BC212 PNP General Purpose Transistors £1.20
- All full spec. branded devices **BUY ANY 5 PACKS AND WE WILL SEND YOU 10 RED LEDs FREE**

DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3½ digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (—50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week

9999

Price £15.50

FREE

SHORT FORM CATALOGUE — send SAE (6" x 9"). We also stock Vero, Books, Resistors, Capacitors, Semi-Conductors etc.


FAST SERVICE · TOP QUALITY · LOW LOW PRICES

No circuit is complete without a call to —

TK

ELECTRONICS

11 Boston Road
London W7 3SJ

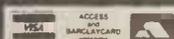

TEL: 01-567 8910 ORDERS
01-579 9794 ENQUIRIES
01-579 2842 TECHNICAL
AFTER 3PM

ALL PRICES
EXCLUDE VAT

When you
build it
yourself,
you know
what you're
getting.



With Heathkit, not only do you enjoy big savings, you're sure of the finest quality. Everything is provided, including detailed instructions. Even the solder you need is there. You'll end up with a superb piece of equipment. Hand crafted. One you'll be extra proud of. Because you built it yourself.

There are all sorts of kits to choose from. From a digital clock to a metal locator, a short wave listener's receiver, windspeed and direction indicator, digital readout electronic scale and plenty more.

There's even the HS-89-2 All-In-One computer kit. With 48K RAM, three serial ports, single density disc controller and green anti-glare screen. Now incredibly only £799 + VAT and carriage. A genuine bargain.

Send off for your catalogue now. The sooner you do, the sooner you'll see what you could get.

To: Heath Electronics (UK) Limited, Dept (HE12), Bristol Road, Gloucester GL2 6EE.



I'd like to get building. Please send me a copy of the Heathkit catalogue. I enclose 28p in stamps. HE12

Name _____
Address _____



HEATH **You build on our experience**
HEATHKIT

BRADLEY MARSHALL LTD

1983 CATALOGUE now available

SEE US AT
BREADBOARD
STANDS 1 & 2

PROBABLY THE LARGEST STOCK OF ICs &
TRANSISTORS IN THE SOUTH - TRY US
FIRST!

SPECIALIST ELECTRONIC COMPONENT DISTRIBUTORS
325 Edgware Road, London W2 1BN Telephone: 01-723 4242 Telex: 29544 BUSY B

SEND LARGE SAE & 75p TO ADDRESS BELOW

Crimson Elektrik PROFESSIONAL AMPLIFIER MODULES

PRICE LIST -
ELECTRONIC MODULES & ASSEMBLIES - APRIL 1981

CODE	DESCRIPTION	Less VAT		INC VAT		WT (Kg)
		£	£	£	£	
CE 608	Power Amplifier Module	18.26	2.74	21.00	0.18	
CE 1004	Power Amplifier Module	21.30	3.20	24.50	0.20	
CE 1008	Power Amplifier Module	23.90	3.60	27.50	0.21	
CE 1704	Power Amplifier Module	30.43	4.57	35.00	0.22	
CE 1708	Power Amplifier Module	30.43	4.57	35.00	0.22	
CE 3004	Power Amplifier Module	42.60	6.40	49.00	0.40	
BD 1	Bridge Driver Module	7.13	1.07	8.20	0.06	
TR 80	Toroidal Transformer 80VA	18.00	2.70	20.70	2.00	
TR 150	Toroidal Transformer 150VA	20.07	3.01	23.08	2.35	
TR 250	Toroidal Transformer 250VA	25.43	3.81	29.24	3.35	
TR 250Q	Toroidal Transformer (low noise)	33.20	4.98	38.18	2.80	
B 6	Bridge Rectifier (6 amp)	0.99	0.15	1.14	0.02	
B12	Bridge Rectifier (12 amp)	1.80	0.27	2.07	0.03	
C4700/40	Reservoir Capacitor and Clip	1.91	0.29	2.20	0.09	
C4700/63	REservoir Capacitor and Clip	2.40	0.36	2.76	0.11	
C4300/63	Reservoir Capacitor and Clip	2.60	0.39	2.99	0.11	
CPS 80	Power Supply	22.82	3.42	26.24	2.10	
CPS 80D	Dual Power Supply	27.63	4.14	31.77	2.25	
CPS 150	Power Supply	25.86	3.88	29.74	2.50	
CPS 150D	Dual Power Supply	31.65	4.75	36.40	2.60	
CPS 250	Power Supply	32.03	4.80	36.83	3.50	
CPS 250D	Dual Power Supply	39.43	5.91	45.34	3.65	
TS 70	Thermal Switch 70°C	1.92	0.29	2.21	0.02	
HS 50	50mm Heatsink	1.60	0.24	1.84	0.15	
HS 100	100mm Heatsink	2.60	0.39	2.99	0.30	
HS 150	150mm Heatsink	3.65	0.55	4.20	0.45	
FM 1	Fan Mounted on 2 x HS 100	32.13	4.82	36.95	1.20	
FM 2	Fan Mounted on 2 x HS 150	36.10	5.42	41.52	1.50	
CPR 1X	Pre-Amplifier Module	31.30	4.70	36.00	0.15	
MC 2	Moving Coil Pre-Pre-Amplifier Module	20.00	3.00	23.00	0.07	
REG 1	Regulated Power Supply	8.09	1.21	9.30	0.07	
TR 6	6VA Mains Transformer	2.87	0.43	3.30	0.21	
XO 2	2 Way Crossover Module	17.39	2.61	20.00	0.07	
XO 3	3 Way Crossover Module	26.09	3.91	30.00	0.07	
MU 1	Muting Circuit for XO 2 or XO 3	8.35	1.25	9.60	0.04	
CK 1010	Complete Pre-Amplifier Kit	78.26	11.74	90.00	2.50	
CK 1040	Complete 40 Watt Power Amplifier Kit	103.48	15.52	119.00	7.30	
CK 1100	Complete 100 Watt Power Amplifier Kit	129.56	19.44	149.00	7.30	
MC 2K	Add On Moving Coil Kit	21.74	3.26	25.00	0.12	
PSK	Pre-Amplifier Power Supply Kit	17.39	2.61	20.00	0.75	

SOLE DISTRIBUTION BRADLEY MARSHALL Ltd OF EDGWARE
325 EDGWARE RD. LONDON W21 BN
TEL: 01-723 4242

Clever Dick

A blast from the past

This seems to be a year for revivals — musicals in the West End, old pop songs from the 50s and 60s reappearing in the Charts, and now . . .

Dear Clever Dick, I have "Experimenter" and "S-Dec" boards and I am wondering if you could devise projects for these for future editions of HE. I find it very difficult to get anything suitable.

*P. Siddi,
Porthcawl,
Mid-Glam.*

. . . . "Short Circuits" have been brought back, in the shape of a new page called "Breadboards". Although these experimenter's circuits have been laid out and tested using Vero's Verobloc system, they can easily be adapted to any other breadboarding system.

*Dear CD, I have one short question; is there any errors in the shortwave Receivers veroboard diagram etc?
T Chapman
Fareham
Hants*

'Is there any errors' . . . it's enough to make you ask : is good grammar a thing of the past? Another question, which might be pertinent; which short wave receiver do you mean—we have published at least three?

However, passing over such minor considerations (it only took four times longer to sort things out), the receiver in question is probably that featured in September '81 issue. There were three errors discovered at the time; missing track cuts at F17 and G17, a missing link (not the . . . no it couldn't be) between F12 and G12 and no markings on D1—the cathode should go to F7.

*Dear CD, I am eleven years old, and have been alarmed to find a mistake on the "Intruder Confuser". Capacitor (C1) has been connected (not across) but in the same direction as the copper strips and there is no break between the two terminals. Also (according to the schematic diagram) the integrated circuit has been connected the wrong way round, there is also another problem. . . . I have, nowhere to store my Hobby Electronics magazine Yours Faithfully,
R Einstein
Ipswich
Suffolk*

(hint, hint). Life isn't all problems though, because I think your magazine's great

Correct on both points—though the issue was raised in a previous HE (June '82, I think). As for the mag, I also think it's great too (especially this page), but then I am a little biased!

Dear CD, I DO NOT WANT A BINDER!!! I would, however, like to pick your amazingly intelligent brain. Way back in January '79, HE published a Touch Switch project. I find it works fine if the OV level is connected to the mains earth, but if I try to run it off batteries (as you recommended, all those years ago) the operation becomes sporadic and unreliable.

So far as I can make out, the signal input level drops dramatically under certain conditions, depending on my posture (keep your remarks to yourself!).

Please could you suggest a circuit mod or, failing this, are there any ICs which I could use, preferably with several switches on one chip?

I am designing a piece of equipment for use by small children so that a single touch-control switch is important, as, of course is the electrical safety.

*Guy Incbald,
Burnage,
Manchester.*

The circuit is intended to be triggered by the 50 Hz hum voltage which we all carry around with us — effectively, the body acts as an antenna. Touching the contact transfers the voltage to the input of IC1, which amplifies it enormously. This is rectified by a diode and the resultant DC is used to switch another op-amp from low to high, thus turning on a LED, relay or whatever. Note, too, that this circuit does not latch up; it will turn off shortly after the finger is removed.

The unreliable operation is probably because the 50 Hz signal is being coupled to all parts of the circuit, (remember that a battery is a short circuit for AC, even at 50 Hz), so that the input op-amp is seeing similar 50 Hz voltages on both its inverting and non-inverting inputs. The easiest way to solve the problem is to physically isolate the touch plate from the circuitry; metal shielding may even be necessary. Alternatively, you could try increasing the sensitivity by increasing the gain of IC1; reduce R2 by stages until you find a value where the operation becomes reliable. However, you may find that the circuit becomes unstable if R2 is taken too low.

Dear Richard, I have had the HE watch dog intruder Alarm (Oct 80) working on a test basis for some months. But have found that it is triggered by an external source/s.

A 3 foot instant start fluorescent fitting and a portable TV that I know of, have, when switched off, bought on LED2 showing a short.

I don't know what electrical appliances my neighbours have but it has happened when I have only had a fridge working. Its only occasionally this happens, and after 2200 hrs, or the early hours of the morning.

The PB1 doesn't cancel LED2 and RV1 has to be re-adjusted to cancel it then adjusted back to its normal position, which may take five minutes or more of adjusting. The circuit board (its not a printed circuit, they were not available) is mounted in a metal box and the box is bonded to earth. The only alteration to the circuit is in the window, where the 22k resistor has been changed to 56k. resistor, to give a bigger window. But I find there is still only a small amount of movement of RV1, when adjusting, to equal door and window switches LED1 before LED2 comes on.

The value of my switch resistors are 470k. I have changed the ICs at different times but trouble always reappear's.

Have you had or heard of anyone having had this happen with the Intruder Alarm and how did you or they overcome it? My knowledge at the moment of electronics is limited so I'm hoping you can throw some light on to it for me.

*N. Kilbey
Ilford
Essex*

What can be deduced from this tale of woe? Gremlins in the alarm system . . . not likely . . . well, how about spikes in the mains . . . ah, that sounds more like it—mains borne interference.

What can be done about it? Well, first of all try putting the unit on a PCB—it's amazing the increased stability you'll get. There are also some other steps you can take. One is to wire a 100u capacitor across the supply rails; and try a 100n in parallel to cut out HF spikes. Another filter can be made by wiring a 10k resistor in series with the line from point X, followed by 4u7 capacitor down to earth (try different positions around the board). If you want to make RV1 more sensitive, change it to 1M and replace R2 with the original 22k value . . . and if all that fails, I hear Alsatians are also pretty effective!

POP-AMPS

Owen Bishop

Simple measuring circuits based on operational amplifiers.

No. 1: Microammeter

THIS circuit adapts any ordinary voltmeter to measure currents in the microamp range. You can also use it with a multimeter, switched to a voltage-measuring range. The lowest current range on a typical multimeter is 0 - 250 μ A, but with this circuit the range can be as small as 0 - 1 μ A. Of course, if you have an FET multimeter, you will probably not need this circuit, as it is likely to be built in to your meter already.

Measuring Currents

An ammeter is always connected in series with the circuit which is to be tested, and the current to be measured flows from the test circuit, through the meter and back to the test circuit. For this reason, the ammeter must have as low a resistance as possible, so that the flow of current in the test circuit is not reduced by the resistance of the meter. A typical microammeter has a coil resistance of around 750R, though some microammeters have coils of considerably higher resistance. However in this circuit, when it is used on its 100 μ A range, the resistance encountered by the current is only 100R, resulting in much greater accuracy. The improvement can be seen by taking a numerical example.

In Figure 1a, the current flowing through the 2k7 resistor is $0.2/2700 = 74\mu$ A. If we try to measure this using an ordinary microammeter (Figure 1b), with a coil resistance of 750R, the total resistance becomes 3450R and the current is reduced to 58 μ A. This is a 23% error!

Using the op-amp circuit (Figure 1c), the total resistance is much less affected. It becomes 2800R, reducing the current to 71 μ A, and the error is now only 4%.

Some reduction of current is inevitable, for we can not avoid using power to drive the measuring instrument. The advantage of using the op-amp microammeter then, is that it needs very little power and so has a relatively small effect on the current you are trying to measure.

The Circuit

We will assume that the circuit is being used on its 100 μ A range, when a current of 100 μ A flows through R5, the potential difference between its two ends is $[V = IR = 100 \times 10^{-6} \times$

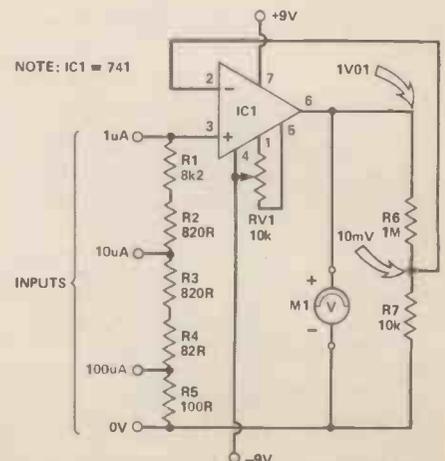
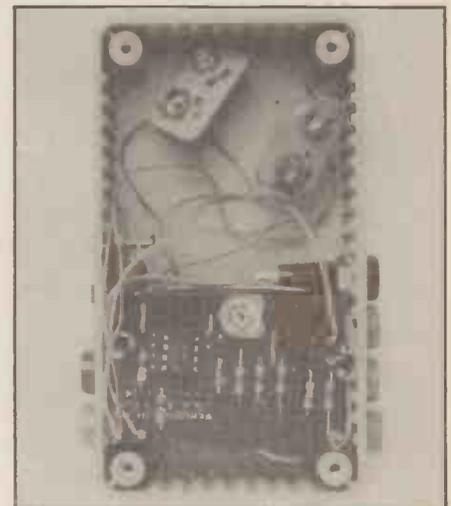
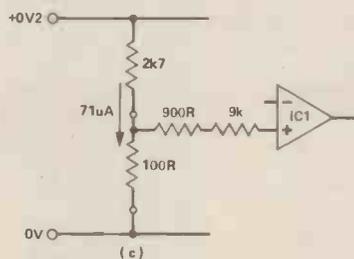
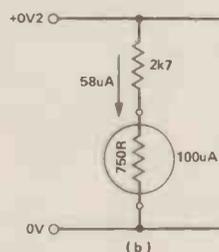
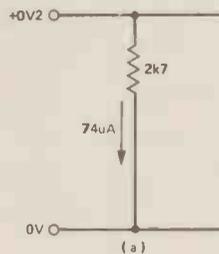
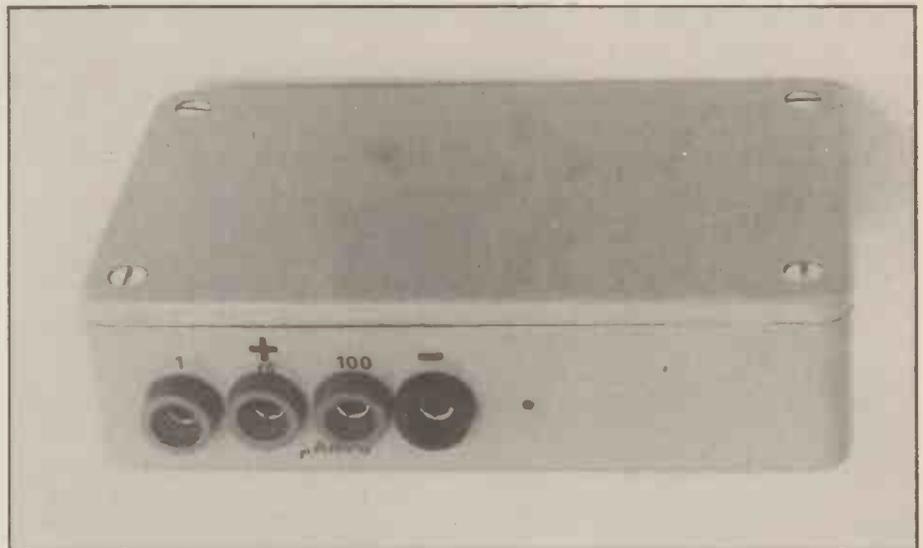


Figure 1. Measuring current (a) using a meter alone (b) results in a large error. The op-amp circuit (c) increases the accuracy of the measurement.

Figure 2. The Microammeter circuit.

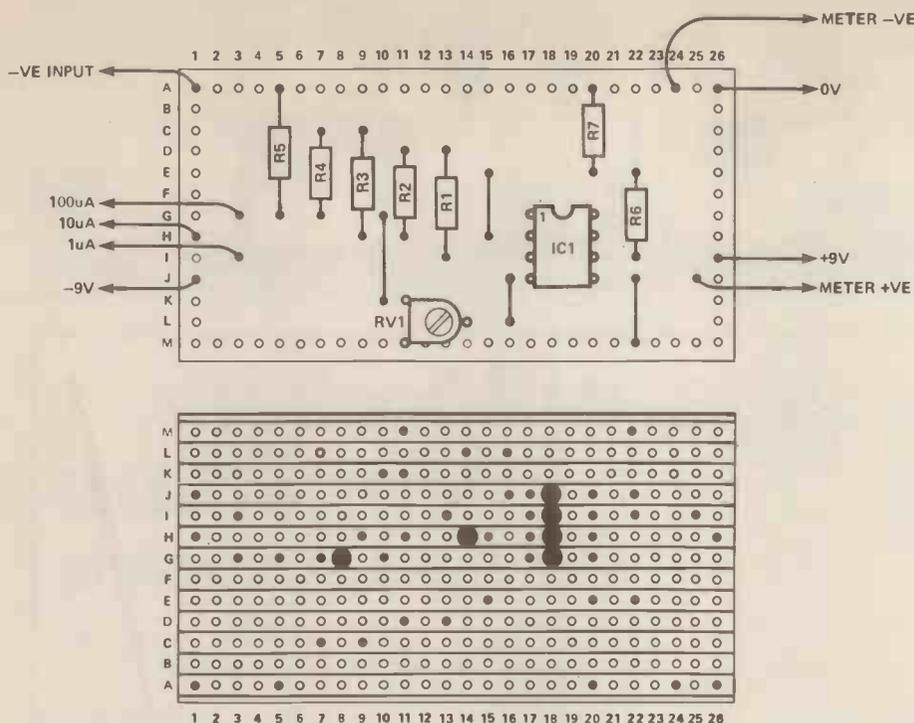


Figure 3. Veroboard component overlay and track-side view.

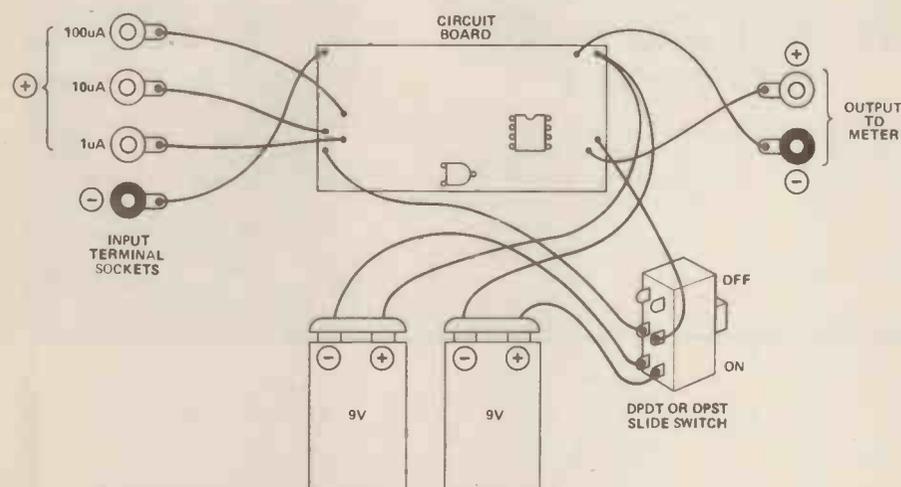


Figure 4. Wiring up the off-board components.

100 = 0.01 V [or 10 mV.] Thus, at full scale deflection (FSD), the non-inverting input (+ve) of the op-amp is at 10 mV compared with the 0 V line. We can ignore the effects of R1/R2 and R3/R4, since these are relatively small resistances compared with the input impedance of the op-amp (the input impedance of a 741 is typically 2M, so these resistors merely increase it to 2.0099M!). If the non-inverting input is at +10 mV, the amplifier adjusts its output to try to bring the inverting input (-ve) to the same potential. This is a special feature of op-amps, and one that is made use of in several other of the circuits we shall be describing.

If the inverting input is to be at +10 mV, the junction of R6 and R7 must be brought to +10 mV. Since R6 and R7 form a potential-divider network, the output voltage if the op-amp has to rise to +1.01 V to achieve this, and this is

the voltage which is measured by the voltmeter. When measuring a current of 100 uA, the voltage reading is 1.01 V; we can ignore the odd fraction of a volt and say that 1 V is equivalent to 100 uA. The currents equivalent to lower voltages are easy to calculate — 0V5 means 50 uA, 0V73 means 73 uA and so on, in proportion.

We work with a maximum potential difference of 10 mV on the other two ranges as well, so the reading obtained on the voltmeter is always between zero and 1 V. If the test circuit is connected to the 10 uA socket, the total resistance is 1k. With 10 uA flowing through this, the potential difference across R3/R4/R5 is 10 mV, as before. Now, a reading of 0V73 means a current of 7.3 uA. The 1 uA socket gives a total resistance of 10k, with a PD of 10 mV when 1uA flows. A reading of 0.73 V means a current of 0.73 uA.

Parts List

RESISTORS

(All 1/4 watt 1% carbon)

R1	8k2
R2,3	820R
R4	82R
R5	100R
R6	1M
R7	10k

POTENTIOMETERS

RV1	10k
		min. horiz. preset

SEMICONDUCTORS

IC1	741
		op-amp

MISCELLANEOUS

2.5 mm stripboard, 66 x 33 mm; 9 x 1 mm terminal pins; 2 x 4 mm red sockets, 2 x black; DPDT switch; 2 x PP3 battery clips; optional case; wire; solder etc.

BUYLINES page 34

Construction

Like all the circuits in this series, this one is built up on a single, small piece of stripboard (Figure 3). Whether you mount it in a case or not is a matter of preference. The circuit is powered by two PP3 batteries, giving the ±9 V supply required, though it is possible to operate on other balanced supplies, such as ±6 V or ±15 V.

Construction presents no problems but be sure to make the track cuts, and check the position of all components. Note that two pairs of resistors are wired in series (R1/R2 and R3/R4) to obtain the values 900R and 9kR, as nearly as possible.



Setting Up

To set up the circuit, connect the voltmeter as shown in Figure 4. This should, preferably, be a 1 V FSD panel meter or a multimeter switched to the 1 V DC range, but a 2 V or 3 V meter will do almost as well.

It does not matter if it is a cheap meter, with low coil resistance, since the op-amp is capable of supplying all the current required. If you can afford a meter for the purpose, there is no reason why you should not wire it to this circuit and mount it permanently in a case.


Now switch on the power; the meter will show a reading of some kind. Join the 1 uA input socket to the junction of R6 and R7, using a test-lead; this connects the two inputs of the op-amp together. The reading on the meter should be 0 V, but if not, adjust the offset null potentiometer (RV1) until the needle of the meter comes to rest at zero. The temporary lead may now be removed, and the circuit is ready for use. This is a simple circuit, with no provision for adjusting full-scale deflection or range; it is assumed that the use of 1% tolerance resistors will have ensured all the accuracy required.

GET BIG POWER

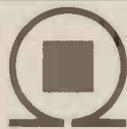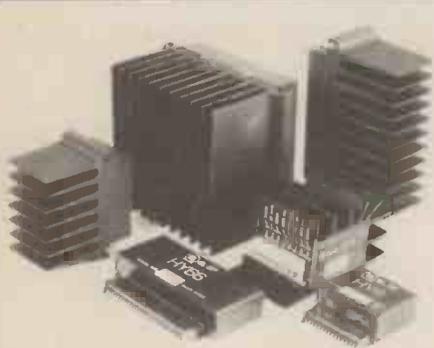

Modular Amplifiers the third generation

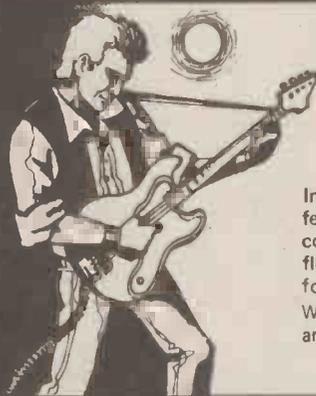Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
HY30	15	4-8	0.015%	<0.006%	± 18	76 x 68 x 40	240	£8.40
HY60	30	4-8	0.015%	<0.006%	± 25	76 x 68 x 40	240	£9.55
HY60/90	30 + 30	4-8	0.015%	<0.006%	± 25	120 x 78 x 40	420	£18.69
HY124	60	4	0.01%	<0.006%	± 26	120 x 78 x 40	410	£20.75
HY128	60	4	0.01%	<0.006%	± 35	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	± 35	120 x 78 x 50	520	£25.47
HY248	120	8	0.01%	<0.006%	± 50	120 x 78 x 50	520	£25.47
HY264	180	4	0.01%	<0.006%	± 45	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	± 60	120 x 78 x 100	1030	£38.41

Protection: Full load line, Slew Rate: 15V/ μ s. Rise time: 5 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz > 400.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
MOS 128	60	4-8	<0.005%	<0.006%	± 45	120 x 78 x 40	420	£30.41
MOS 248	120	4-8	<0.005%	<0.006%	± 55	120 x 78 x 80	850	£39.86
MOS 364	180	4	<0.005%	<0.006%	± 55	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice). Slew rate: 20V/ μ s. Rise time: 3 μ s. S/N ratio: 100db. Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms. Input impedance: 100K Ω . Damping factor: 100Hz > 400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

£9.14 (inc. VAT)

Robust construction.

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz, T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 90db, Load Impedance 3 Ω L

Input Sensitivity and Impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω .

Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre-amp	Mix/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre-amp	Mix/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre-amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre-amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp.

A separate PSU 30 is available purely for pre-amp modules if required for

£5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations.

Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05

(inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT	Model Number	For Use With	Price inc. VAT	Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93	PSU 52X	2 x HY124	£17.07	PSU 72X	2 x HY248	£22.54
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83	PSU 53X	2 x MOS128	£17.86	PSU 73X	1 x HY364	£22.54
PSU 42X	1 x HY128	£15.90	PSU 54X	1 x HY248	£17.86	PSU 74X	1 x HY368	£24.20
PSU 43X	1 x MOS128	£16.70	PSU 55X	1 x MOS248	£19.52	PSU 75X	2 x MOS248, 1 x MOS368	£24.20
PSU 51X	2 x HY128, 1 x HY244	£17.07	PSU 71X	2 x HY244	£21.75			

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

WITH A LOT OF HELP FROM



PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.



Hi Fi Separates

UC1 PRE AMP UNIT: Incorporates the HY78 to provide a "no frills", low distortion, (<0.01%), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

POWER AMPS: The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.

Power Slaves

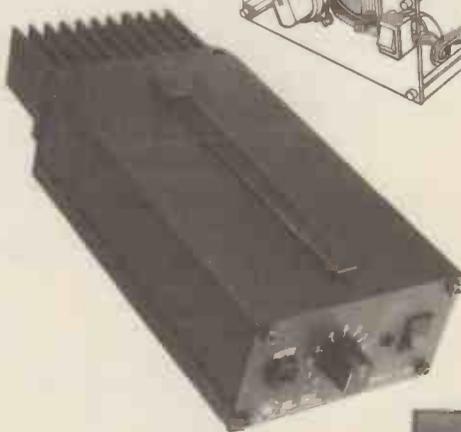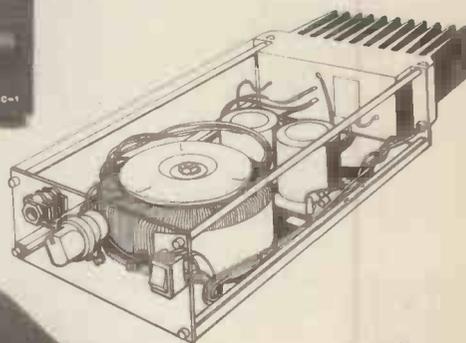Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.



TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd. if sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED

UNICASES

					Price inc. VAT
HiFi Separates					
UC1	Preamp				£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	HiFi	£54.95
UP2X	60W/4Ω	Bipolar	Mono	HiFi	£54.95
UP3X	60W/8Ω	Bipolar	Mono	HiFi	£54.95
UP4X	120W/4Ω	Bipolar	Mono	HiFi	£74.95
UP5X	120W/8Ω	Bipolar	Mono	HiFi	£74.95
UP6X	60W/4-8Ω	MOS	Mono	HiFi	£64.95
UP7X	120W/4-8Ω	MOS	Mono	HiFi	£84.95
Power Slaves					
US1X	60W/4Ω	Bipolar	Power	Slave	£59.95
US2X	120W/4Ω	Bipolar	Power	Slave	£79.95
US3X	60W/4-8Ω	MOS	Power	Slave	£69.95
US4X	120W/4-8Ω	MOS	Power	Slave	£89.95

Please note X in part number denotes mains voltage. Please Insert '0' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.) All units except UC1 incorporate our own toroidal transformers.

Post to: ILP Electronics Ltd, Freepost 6, Graham Bell House, Roper Close, Canterbury, CT2 7EP, Kent, England. Telephone: (0227) 54778. Technical: (0227) 64723. Telex: 965780.



Please send me the following _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

TAPE/SLIDE SYNCHRONIZER

R. A. Penfold



Keep your audio in sync with your visuals!

THERE ARE several different types of slide/tape synchroniser, but the function they all perform is to record short "bleeps" of tone, on a cassette or tape recorder, and then use these tones on playback to automatically operate the slide-change mechanism of the projector. In its most basic form, a unit of this type is simply used with a monophonic cassette or tape recorder as a programmable slide timer, or in conjunction with stereo tape equipment the "bleeps" can be recorded on one channel while the other carries background music and (or) a commentary.

More sophisticated units enable the tone to be mixed with the music or commentary during records. Then, during playback, circuits in the unit operate the projector only when the "bleeps" of tone are detected and ignore other signals on the tape, so that spurious operations of the projector are avoided. This system has the advantage of enabling the slide show to have a monophonic accompaniment using a monophonic recorder, or a stereo accompaniment using a stereo recorder, but is not very satisfactory in practice since the "bleeps" are clearly audible to the audience, and are something of a distraction.

This problem can be overcome using the arrangement described above *plus* an additional stage which operates during playback to filter the "bleep"

signals from the output. The HE Slide/Tape Synchroniser is of this type, but it is reasonably simple and inexpensive and does not require any test equipment to enable it to be set up correctly for use. It would not be true to say that there is no loss of quality introduced by adding in the "bleeps" to one channel and then filtering them out again, but the loss of quality is not likely to be noticed, even if your slide shows are not quite as riveting as they

might be!

The bursts of tone are at quite a high frequency (about 5kHz) and when these are filtered out, any signals at around this frequency in the music or commentary are also removed. This obviously gives a certain loss of audio quality but, as only a very narrow band of frequencies are seriously affected and the fundamental frequencies in music are usually below 5kHz (so that only harmonics are attenuated by the

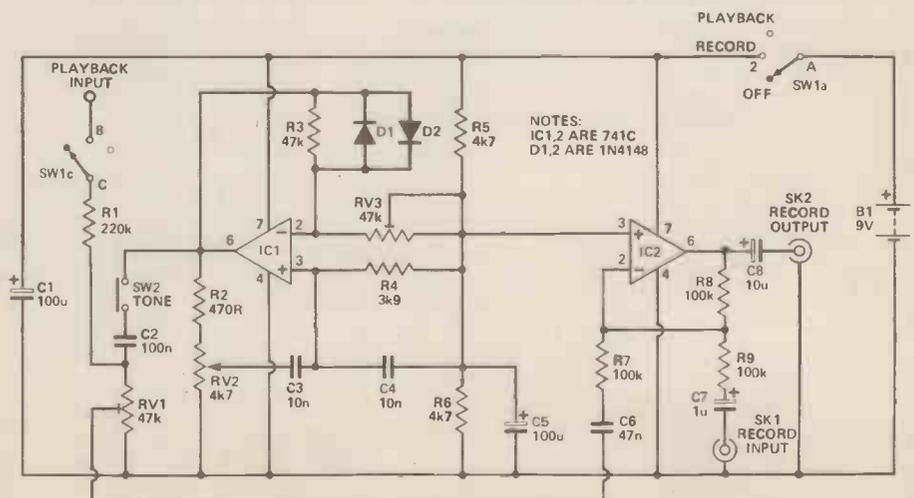



Figure 1. The Record section circuit.

How It Works

A MIXER and a tone generator are used to add bursts of high frequency tone to the input signal when a push button switch is briefly operated; the output is fed to the input of one channel of a tape recorder. Another circuit is used to process the signal when the tape is played back; the purpose of this circuit is to separate the bursts of tone and the main signal. The tone bursts are used to automatically operate the projector at the appropriate times, and this signal is filtered from the main signal using a bandpass filter tuned to the frequency of the tone signal. The output of the filter is fed to a driver circuit which pulses a relay when the tone bursts are detected; a pair of relay contacts are used to operate the slide change mechanism of the projector.

On playback the output from the tape recorder is also fed to a notch filter which gives very high attenuation at the frequency of tone bursts, and thus eliminates them, but enables other frequencies to pass unhindered. In practice, the notch filter will actually remove some of the wanted signal, while the bandpass filter permits some of the main signal to pass through to the relay driver. However, the loss of quality is not serious, and breakthrough to the relay driver should not cause spurious operation of the unit.

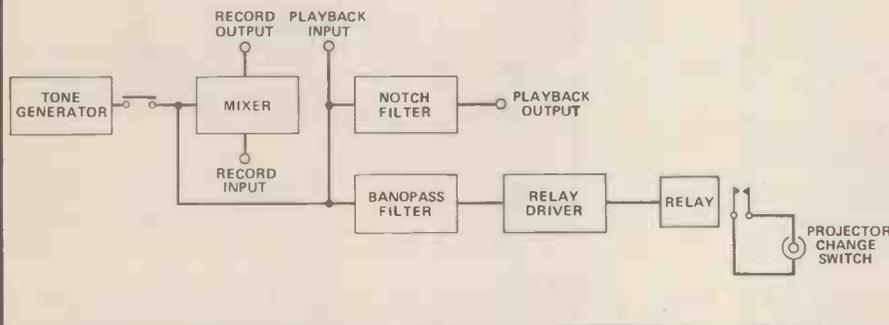The "bleeps" of tone are also fed to the bandpass filter and the Record Output so that the projector is operated when the push button is operated, so that the tone burst is added to the sound track as the projector is operated.



filtering) there is no drastic loss of quality. There is also, inevitably, a reduction in the signal-to-noise ratio, but this is marginal and is of no practical consequence.

The unit is powered from an ordinary 9 volt (PP6 size) battery, and it should be compatible with any normal cassette or reel-to-reel tape deck or recorder. It has unity voltage gain in both the recording and playback modes and should not introduce any problems of incompatibility between

the tape machine used and other items of equipment such as the amplifier used during playback.

The Circuit

If we consider the recording circuit first, (shown in Figure 1), IC1 is used as the tone generator. The oscillator configuration is a form of the Wien Bridge which is capable of giving a good quality sinewave output. The operating frequency is determined by

R2, RV2, C3, C4 and R4; adjusting RV2 permits the operating frequency to be varied from around 2kHz to 10kHz. In use, RV2 is adjusted to adjust the output frequency to give maximum attenuation from the notch filter in the playback circuit; this is nominally at 5kHz.

R3, D1 and D2 form a negative feedback network, RV3 can be set to give gentle oscillation with a reasonably pure output. D1 and D2 help to stabilise the feedback at the correct level and make the adjustment of RV3 a little less critical.

IC2 is used as a standard operational amplifier mixed circuit having unity voltage gain. RV1 controls the volume of the tone signal fed through to the output socket, so that it can be set at a suitable level relative to the main signal; however the tone signal is only coupled through to RV1 when SW2 is operated.

The circuit diagram of the playback section of the unit is shown in Figure 2. C17 couples the input signal (from the recorder) to a notch filter, which is basically a twin-T type using C18, 19, 20, R17, 18, 19, and RV5. RV5 enables the attenuation of the filter to be peaked at a very high level (about 80 dB or more).

A problem with a simple, twin-T filter is that it tends, also, to significantly attenuate signals at frequencies well away from the centre frequency, and in this application the audio quality would be adversely affected. Typically, a twin-T filter gives about 10 dB attenuation at half and double the operating frequency. In this circuit, the response of the filter is improved by the negative feedback loop around IC4. The circuit may look a little confusing, due to the use of two negative feedback loops, but the effect of this is to stabilise the gain of the circuit at unity. This can only be achieved at frequencies where the losses through the twin-T network are fairly low, however, and at the operating frequency of the filter its losses are far too high to be significantly reduced by the negative

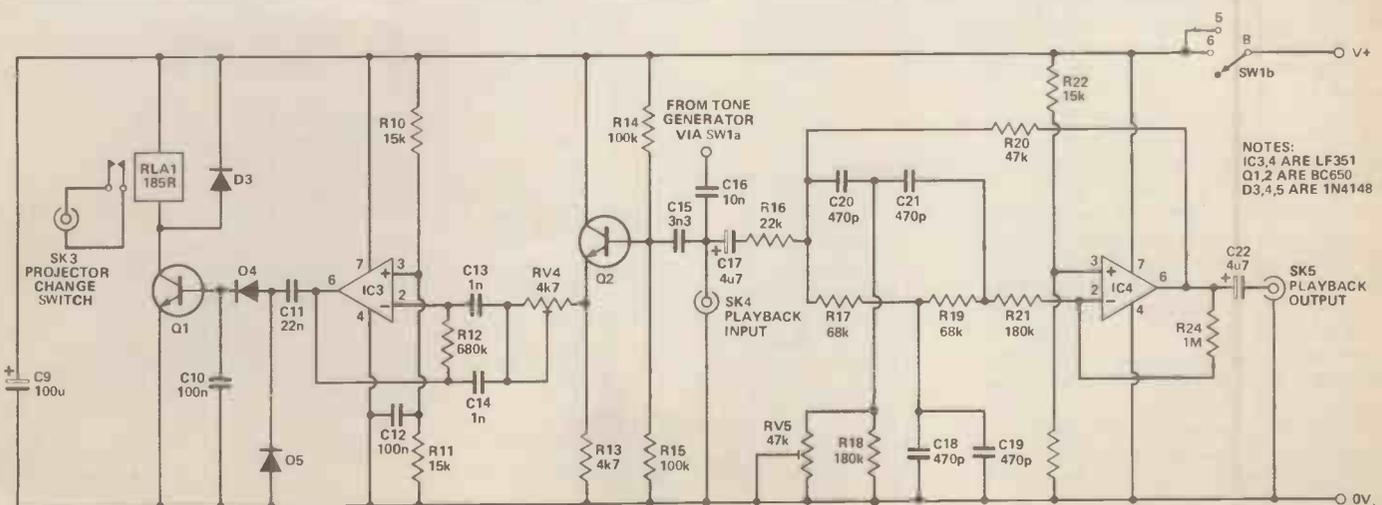


Figure 2. The Playback section; the tone filter circuit is on the right (IC4)

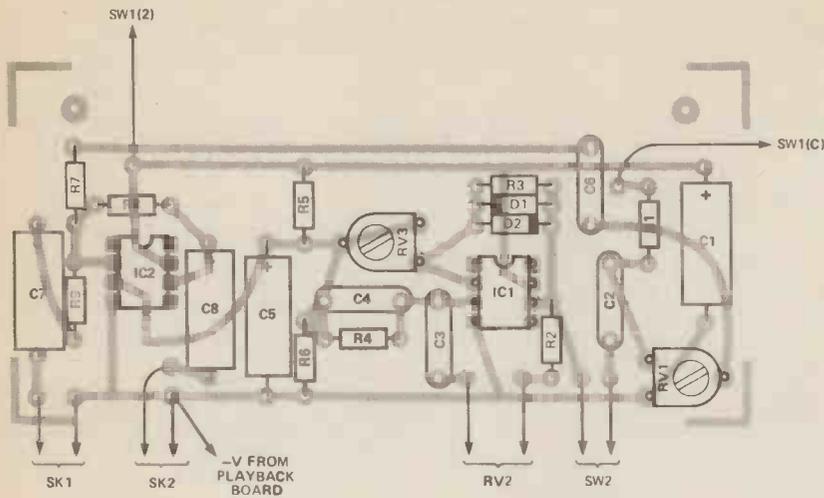


Figure 3. PCB overlay for the Record section circuit.

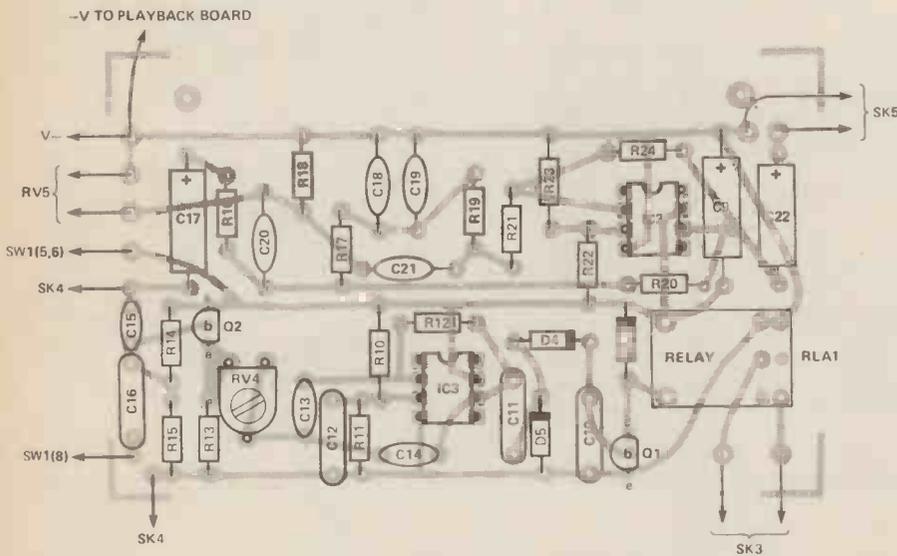
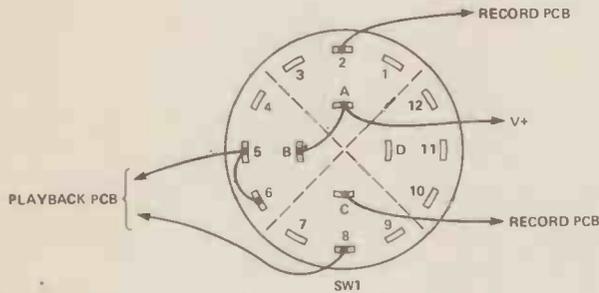


Figure 4. The PCB and component overlay of the Playback section.

feedback. Thus the response of the filter is improved, with reduced losses away from the operating frequency but with the deep attenuation notch being retained.

C15 couples the tape input signal to an emitter follower buffer stage which uses Q2, and this simply ensures that the next stage is fed from a suitably low source impedance. The next stage of the circuit is actually a standard operational amplifier bandpass filter using IC3, tuned by RV4 to peak the response of the circuit at the correct

frequency.

The output of IC3 is coupled to a smoothing and rectifier circuit which drives Q1 which, in turn, drives the relay coil. When the bursts of tone are present on the input signal, these produce a strong positive bias at the base of Q1, which is then switched on, activating the relay and the projector's slide change mechanism via a set of normally open relay contacts.

SW1 is the mode switch; this couples the output of the tone generator through to the playback

Parts List

RESISTORS

(All 1/4 W 5% Carbon)

R1	220k
R2	470R
R3,20	47k
R4	3k9
R5,6,13	4k7
R7,8,9,14,14	100k
R10,11,22,23	15k
R12	680k
R16	22k
R17,19	68k
R18,21	180k
R24	1M

POTENTIOMETERS

RV1,3	47k
	0.1W horizontal preset
RV2	4k7
	linear carbon
RV4	4k7
	0.1W horizontal preset
RV5	47k
	linear carbon

CAPACITORS

(All C280 polyester unless noted)

C1,5,9	100u 10V
	axial electrolytic
C2,10,12	100n
C3,4,16	10n
C6	47n
C8	10u
	25V axial electrolytic
C11	22n
C13,14	1n
	polycarbonate
C15	3n3
	ceramic
C17,22	4u7
	63V axial electrolytic
C18,19,20,21	470p
	polystyrene

SEMICONDUCTORS

IC1,2	741C
	op-amp
IC3,4	LF351
	bifet op-amp
Q1,2	BC650
D1,2,3,4,5	IN4148

MISCELLANEOUS

RLA1	12V 185n coil
	2 pole changeover contacts
SW1	3 way 4 pole rotary
SW2	Push to make non-locking type
B1	PP6, 9 volt
	Case, about 203 x 127 x 51 mm;
	battery clip (PP3 type); PCBs; three
	control knobs, wire, solder, etc.

BUYLINES page 34

circuit when the unit is in the record mode (it also provides on/off switching for both circuits). Note that power is applied to the playback circuit when the unit is in the recording mode, so that the relay activates the projector to synchronise the slide-change with the sound track.

Construction

An aluminium case measuring about 203 x 127 x 51 mm will comfortably accommodate all the components, including the battery. The four controls


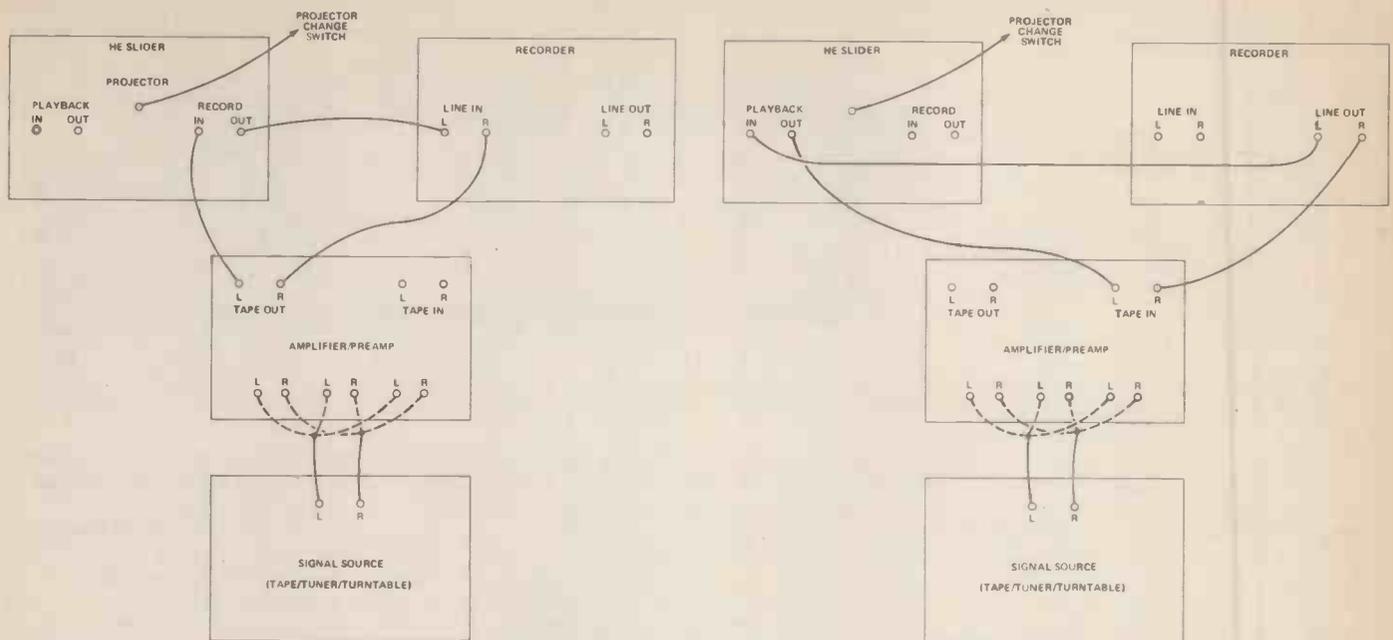


Figure 5. Connecting the unit for Record (left) or Playback (right).

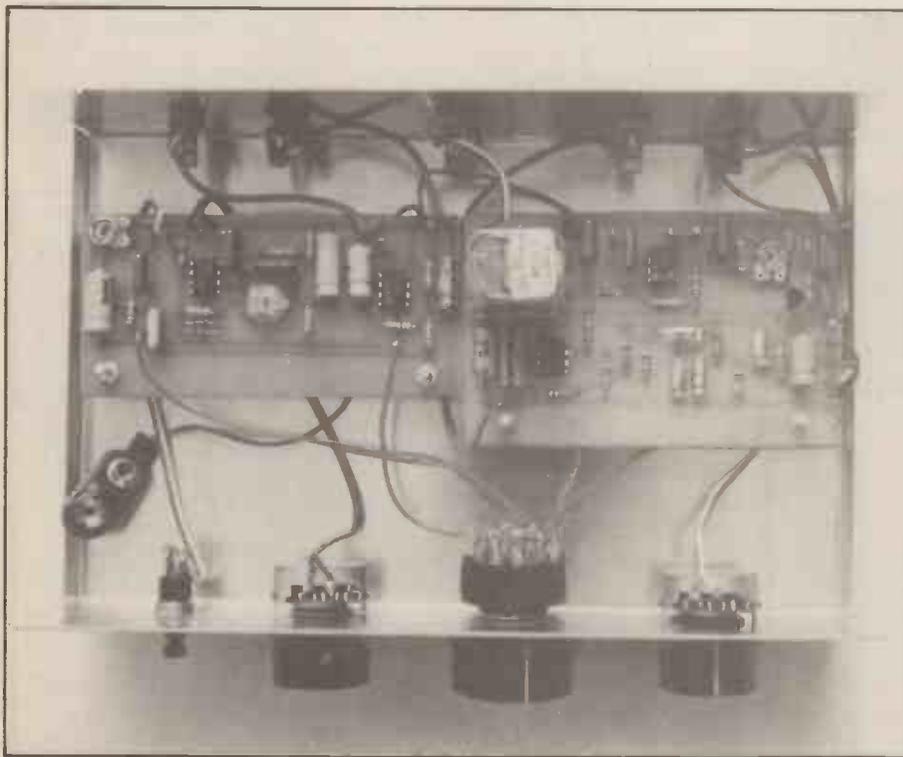

are mounted on the front panel, although SW2 can be mounted in a separate small (hand held) case and connected to the main unit via a lead several feet long, if this will be more convenient in use. The lead would need to be terminated in a two way plug and SW2 would be replaced (on the front panel of the case) by a matching two way socket. Note that this socket should be a type which is insulated from the case, such as a plastic jack type or a two way DIN socket. SK1 to SK5 are mounted along the rear panel

of the case; these are all 3.5 mm jacks on the prototype, but can be changed to any other type of socket, if this will be more convenient in use.

The other components are mounted on two printed circuit boards, one for the recording circuit and the other for playback. The component layouts and wiring are shown in Figures 3 and 4 respectively; use Veropins at points where off-board connections will be made. The specified relay will fit directly onto the printed circuit board, but other types will work provided they

have a coil resistance of about 185 ohms or more, will operate from about 6 volts, and have at least one set of normally open contacts rated at about 2 amps (AC) or more. However, if an alternative relay is used it will be necessary to alter the PCB to suit, or mount the relay off-board. Incidentally, the specified relay has two sets of changeover contacts, with four of its pins unused.

Setting Up

A quick initial check of the unit can be made by switching the unit to the recording mode and operating SW2. If the output of SK2 is monitored using an amplifier and loudspeaker (or even just a crystal earphone), a tone should be produced when SW2 is operated, provided that RV3 is set well into the anticlockwise position. RV1 should control the volume of the tone, with RV2 giving pitch control.

The next stage is to set RV5 at about half way and monitor the output from SK5. By adjusting RV2, it should be found that the tone is greatly attenuated at some setting that gives a fairly high pitch and, by repeatedly adjusting RV2 and RV5, it should be possible to eliminate the fundamental frequency of the tone. With the tone generator oscillating strongly there will be quite strong harmonics (multiples of the fundamental frequency) at the output although, due to the high frequency of the tone, probably only two harmonics will be audible. Setting RV3 further in a clockwise direction will produce more gentle oscillation but will alter the pitch of the tone slightly, and RV2 will need to be readjusted. A little experimentation with the settings of RV1 to RV3 should produce a reasonably pure tone, with the filter attenuating this to an insignificant level.

POP-AMPS

Owen Bishop

Simple measuring circuits based on operational amplifiers

No. 2: Voltage follow-and-hold circuit

ONCE in a while, and probably more often, it is necessary to measure a voltage which is changing rapidly — but trying to follow the needle of the voltmeter by eye and read it at *just* the right instant is tension-generating, to say the least! And, if your eye cannot follow the needle, it is likely that the needle cannot follow the rapidly changing input voltage, either, so whatever reading you have struggled to obtain will be doubly in error. This circuit, however, gives your eye *and* the needle a breathing-space in which to catch up with the changing voltage. Pressing the button, it takes a sample of the input voltage at any instant; the circuit then holds the meter needle while the needle of the meter comes to rest, and your eye has time to take the scale reading with all the accuracy you need.

The Circuit

The output of the circuit (Figure 1) follows the input voltage as long as the button is held pressed. When the button is released, the output remains constant at whatever value it had at the instant of release. When the button is pressed again, the output immediately becomes the same as the input voltage. The operation of the circuit is diagrammed in Figure 2.

The op-amp is connected as an inverting amplifier with unity gain and with the button pressed, output follows input except that it is inverted.

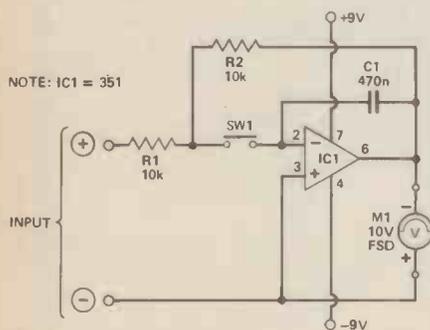
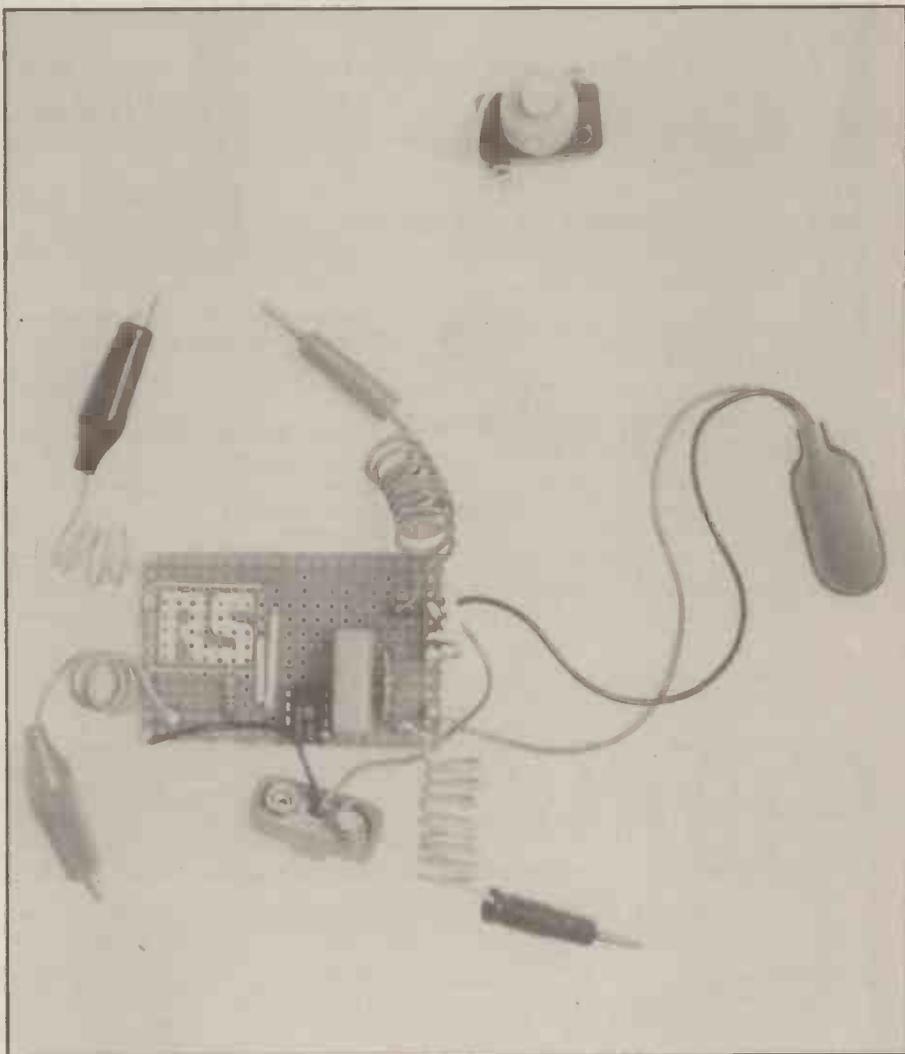


Figure 1. The Follow and Hold circuit.

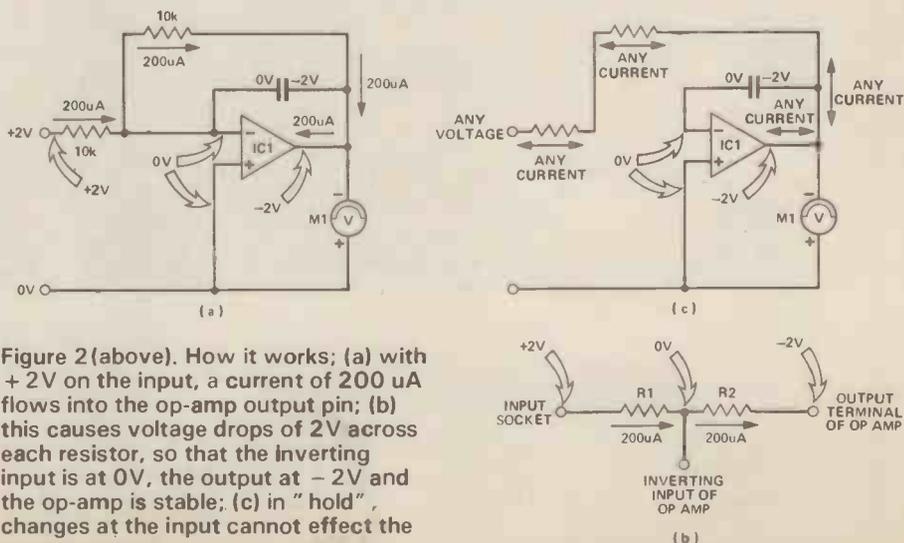


Figure 2 (above). How it works; (a) with +2V on the input, a current of 200 uA flows into the op-amp output pin; (b) this causes voltage drops of 2V across each resistor, so that the inverting input is at 0V, the output at -2V and the op-amp is stable; (c) in "hold", changes at the input cannot effect the op-amp output.

Now an op-amp is stable when there is no potential difference between its two input terminals. But since the non-inverting (+ve) input is wired to 0 V, the inverting input must also be at 0 V if the circuit is to be stable. So given an input of, say, +2 V, a current of 200 uA flows toward the inverting input, by way of the input resistor R1. The amplifier input has extremely high resistance, so almost no current enters it, but, instead, flows on through R2 and into pin 6 of the op-amp. Since R1 has the same value as R2, and the same current flows through each; the voltage difference across each resistor is the same (Figure 2b). Therefore, with a drop of 2 V across each resistor, the output potential is -2 V, the potential

at the inverting output is 0 V and the op-amp is stable. In this state, one side of capacitor C1 is at 0 V and the other is at -2 V; there is 2 V across it.

When the button is released, the circuit becomes as shown in Figure 2c. The input to the circuit may change, either increasing or decreasing in voltage, and a varying current may flow in either direction through R1, R2 and into or out of the output terminal of the op-amp — but the output of the op-amp is entirely unaffected by this! The potential at its inverting input is held at 0 V because of C1 and, since this is still the same as the potential at its non-inverting terminal, the amplifier is stable; it maintains an output potential of -2 V.

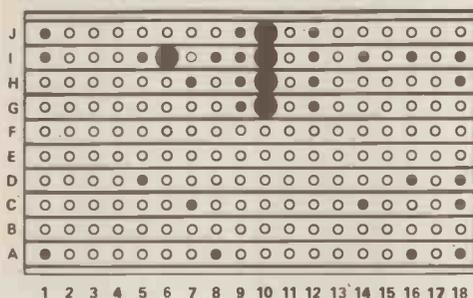
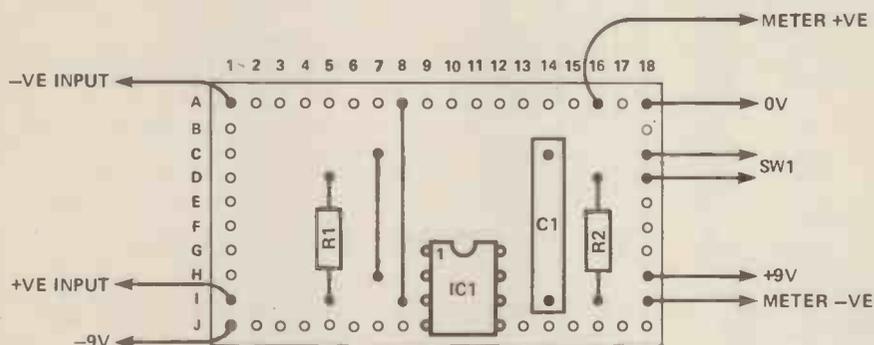


Figure 3. The Veroboard component overlay (top) and the track-side view (bottom), showing the positions where the strips are cut.

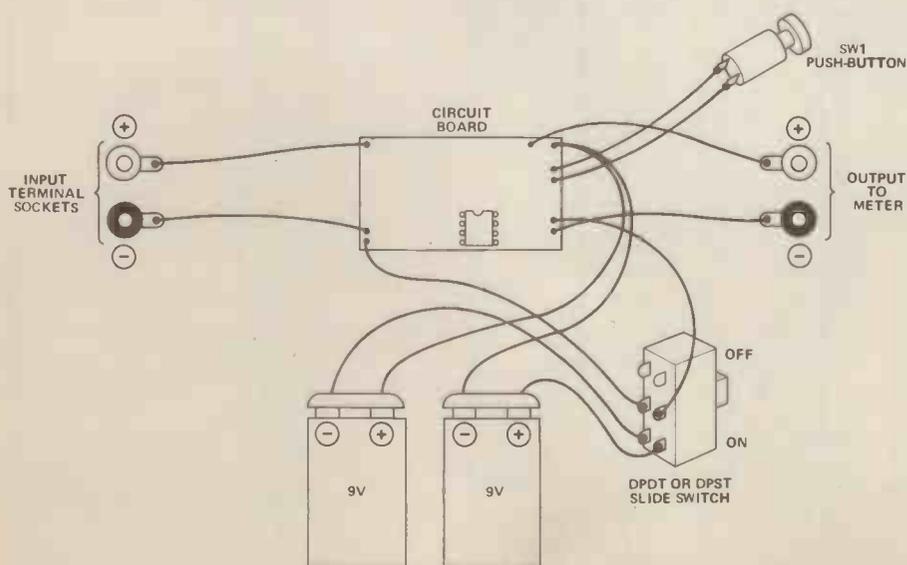


Figure 4. Wiring the external components to the Veroboard.

The capacitor retains its charge for a long time, since there is no way in which a large current can flow from one side of the capacitor to the other. The plates of C1 are effectively insulated from each other by the dielectric, which has a resistance of 20,000M or more, while leakage into the amplifier is very small too, since the input impedance is $10^{12}R$ — a million megohms! — and this high input impedance is the reason for choosing a JFET op-amp for the circuit. With such high resistances, a charge of 2 V on C1 takes 47 seconds to drop just a hundredth of a volt. This should give you (and the meter) plenty of time to cope!

The circuit described has unity gain, so meter readings are equal to input voltages, though increasing the value of R2, you can make the circuit amplify the voltages as well as hold them. The amplification is set by the ratio $R2/R1$; for example, if you replace R2 with 100k, the op-amp amplifies ten times.

The reason for choosing the 531 in preference to other JFET op-amps is that it has a very high slew rate (rate of change of output voltage) of 13V/us, which compared with the rate of 0V5/us for the 741, makes it a good device for sampling rapidly changing voltages.

Operating the multimeter on the 10 V range means that offset null adjustments (see *Pop Amps No. 1* in this issue) are less important and an offset potentiometer is not needed.

Construction

There are so few components that construction of the circuit takes only a few minutes. The component layout is shown in Figure 3. Whether you decide to mount it in a case is a matter of preference. If you have a 10 V meter to spare, you can mount this on the case; it does not need to have a high coil resistance, so a cheap one will do. Otherwise, plug your multimeter into the circuit, using the two sockets indicated. This circuit, like No. 1, can also be used with the LED Millivoltmeter featured in HE August 1982.

HE

Parts List

RESISTORS	
(All 1/4 Watt 1% carbon)	
R1,2	10k
CAPACITORS	
C1	470n polycarbonate
SEMICONDUCTORS	
IC1	7611 CMOS op-amp
MISCELLANEOUS	
2.5 mm stripboard, 48 x 25 mm; 6 x 1 mm terminal pins; 2 x 4 mm red sockets, 2 x black; push-to-make switch; DPDT switch; 2 x PP3 battery connectors; optional case; wire, solder etc.	
BUYLINES	page 34


HC6010 DMM

Paul Coster

An accurate and reliable DMM with some outstanding features.

WHEN I unpacked the HC6010 from its mustard coloured box, I could tell I was in for a few surprises. Described by the manufacturers as accurate and reliable, it is a digital multimeter with all the usual AC/DC current and voltage ranges and some extra ones not common to meters in this price range — for example, a basic DC accuracy of 0.5%. In use it was very robust — of the highest electronic standards of construction — and well thought out. In fact, my only real criticism was of an aesthetic nature rather than due to any great failing of the meter.

The 6010 multimeter is made by Hung Chang Products and distributed by Armon Products Ltd. The basic ranges are AC/DC current and voltage (extending up to 1000 V and 10 A DC, and 750 V and 10 A DC) and two resistance — low and high output voltages. The display is 3½ digit LCD with auto-zero, auto-polarity and 'lo-bat' indicators. Range and scale selection is made via a series of push-buttons along the left-hand side of the instrument. There are eight buttons in all, two for selecting AC/DC (or hi/lo resistance) and voltage/current/resistance and six for setting up the correct full scale deflection (FSD). For instance, to measure up to 20 mA AC you would press the top button (conveniently coded dark grey) for AC and the fifth button to read up to 19.99 mA. However, there's no need to worry if the value is over range, since the meter is protected against overloads by sparkgap (voltage), inrush current limiter (current) and a 2A fuse (current). Also protected are the battery eliminator input and resistance ranges and as if that isn't enough, the test lead sockets are recessed — not to make plugging and unplugging the leads as difficult as possible as I first thought, but to ensure there is no bare metal to give you any nasty shocks — as part of an overall philosophy of 'safety first'.

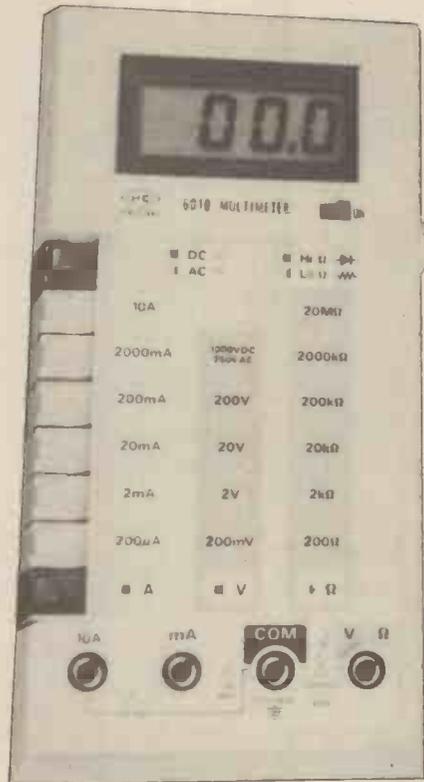

Clearly A Better Meter

The voltage ranges are chosen by pressing the lowest of the (dark grey) buttons. Both AC and DC voltage scales have the same ranges (apart from maximum values of 750 V AC and 1000 V DC) and so AC or DC can be switched by a single button. Accuracy is quoted at $\pm 0.5\%$ (reading + 1 digit) DC and $\pm 1\%$ (reading + 5 digits) AC, which despite being a strange way of expressing the tolerances, is pretty good for a meter of this price range.

Sinusoidal voltages are measured with an averaging response, but the meter is calibrated to read RMS (though this is not as good as direct reading RMS) and resolution for both AC and DC is a very good 100 μ V.

To measure current, you have to plug the red test lead into a different socket (slightly tedious with the safety measures mentioned earlier), and the two dark grey buttons operate in a similar manner as when reading voltage — upper for AC/DC, lower remains 'out'. In addition to this, if you want to take readings up to 10 A you must plug the red lead into a third socket. This was again a chore, but when you consider that most other meters need a shunt to measure such large currents, perhaps it's forgivable.

Accuracy on the current ranges is not as high as on the voltage, but since the worst case (2 A and 10 A AC) is still fairly good at $\pm 3\%$ (reading + 5 digits), I do not feel the 6010 is any poorer than the competition (I was particularly impressed by the clear manner in which *all* the technical specifications were presented). Resolution on both AC and DC current is adequate at 100 nA; but this meter, like others I have reviewed, would have benefitted from a lower limit of 10 nA, say — after all, isn't everyone interested in the current consumption of their LCD calculator!

Resistance measurements are made by pressing the lowest button and then selecting either the 'hi' or 'lo' ohms scale. These two scales are present, as with other meters, to allow in-circuit readings to be made. However, unlike some other similar instruments, the lo output is low enough (280mV) to facilitate testing around *most* semiconductors. Both outputs (hi and lo) have six ranges from 200 ohms up to 20 megohms, with resolution down to 100 milli-ohms on the 200R. Accuracy is very good on the four lower ranges (0.5% nominal) and creditable on the 2M and 20M settings (better than 2% nominal). The high range (up to 20M) is quite rare for a unit of this type and I was pleased to see it included.

Specs And The Rest

The HC6010 DMM comes complete with an instruction leaflet, which is very clear but (sadly) not that well laid out — whatever happened to those neat pocket-sized manuals that used to accompany most of the better meters! Even so, operation is easy to grasp and the leaflet is only necessary as a source of reference information. What I do commend Hung Chang for, is the inclusion of a circuit diagram and parts list — it is always a good sign if a manufacturer is proud enough of his design work to want to make it public. However, it's a pity this pride doesn't extend to the fascia panel, on the front of the case, which has the lettering printed on it. Not only does this have a tendency to peel off, but it gives the meter a gimmicky appearance. A bit of time spent here (and on improving the shape of the case and buttons) would pay in the long run — designers of the 'Mark II' take note.


So, for those of you who are after a robust and accurate digital multimeter, that is easy to use and out-performs most others at the price, I can recommend the 6010. However, if you're after something to show off to your friends, then keep looking... and one final surprise, a price tag of £34.44. For further information contact Armon Products Ltd, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH.

CAMBRIDGE LEARNING

SELF-INSTRUCTION COURSES

★ NEW! ★

COMPUTER
DIGITAL DESIGN

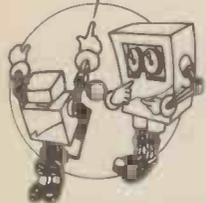

A self-instruction course from Cambridge Learning

DIGITAL COMPUTER DESIGN

£8.50

Our latest, up-to-date course on the design of digital computers, both from their individual logic elements and from integrated circuits.

Digital Computer Design is the best way for you to understand how simple computers are. You are first shown the way in which simple logic circuits operate and then, through a series of exercises, arrive at a design for a working machine.

GSC SUPERKIT £19.90

The original Cambridge Learning Superkit, a practical digital electronics kit for beginners, now re-written for the popular GSC EXP300 breadboard. The kit comes complete with an instruction manual, components, and breadboard to teach you all the basics of digital electronics.

DIGITAL COMPUTER LOGIC & ELECTRONICS £6.00

The theory course to support the practical Superkit, this 4-volume set covers basic computer logic; logical circuit elements; the design of circuits to carry out logical functions: flipflops and registers. No prior mathematical knowledge other than arithmetic is assumed.

GUARANTEE No risk to you. If you are not completely satisfied, your money will be refunded upon return of the item, in good condition within 28 days of receipt.

CAMBRIDGE LEARNING LIMITED, UNIT 10 RIVERMILL SITE, FREEPOST, ST IVES, CAMBS, PE17 4BR, ENGLAND. TELEPHONE: ST IVES (0480) 67446. VAT No 313026022

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice). Giro A/c No 2789159. Please allow 28 days for delivery in UK.

-SUPERKIT(S) @ £19.90
-DIGITAL COMPUTER DESIGN(S) @ £8.50
-DIGITAL COMPUTER LOGIC AND ELECTRONICS @ £6.00

I enclose a *cheque/PO payable to Cambridge Learning Ltd for £..... (*delete where applicable)

Please charge my:

*Access / American Express / Barclaycard / Diners Club Eurocard / Visa / Mastercharge / Trustcard

Expiry Date..... Credit Card No

Signature.....

Telephone orders from card holders accepted on 0480 67446 Overseas customers (including Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name.....

Address.....

Cambridge Learning Limited, Unit 91 Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs, PE17 4BR, England. (Registered in England No 1328762).

AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

TEST EQUIPMENT CENTRES¹ ALL MODELS ON DISPLAY² OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

TRIO 20 MHZ DUAL TRACE SCOPES

140mm Tube: DC to 20MHZ: 5mV sensitivity: CH2 Invert
CS1820 Delayed sweep: 0.2µsec to 0.5 sec
Sweep: Modes CH1, CH2, DUAL and ADD.
List Price £539.00 inc. VAT.
Our Price **£420.00** inc. VAT (UK c/p £4.00)

2 YEAR GUARANTEE



CS1566A NDR. AUTO. VIDEO: 0.5µsec Sweep:
Modes CH1, CH2, ALT. CHDP and ADD.
List Price £368.00 inc. VAT
Our Price **£299.00** inc. VAT (UK c/p £4.00)

Optional probes - see below.

100 KHZ TO 30 MHZ

140mm Tube: RF Generator, Int/ext. mod, variable 0/p to 100mV. AM Int 400 KHZ mod.
Special Price **£59.95** inc. VAT (UK c/p £2)
AG202A matching Audio Generator **£78** inc. VAT (UK c/p £2)



LOW COST DIGITAL MULTIMETERS

3 1/2 digit LCD Hand Held DMM's:
SW - Slide switch; PB - Push Button
RS - Rotary (Models * with carry case)
UK c/p 65p all models
*K025C 13 Range 0.2A DC 2 megohm (SW) £26.50
*K030C 26 Range 1A AC/DC 200 megohm (RS) £37.50
*K055C 28 Range 10A AC/DC 200 megohm (RS) £41.50
*601 26 Range 2A AC/DC 20 megohm (PB) £36.50
188m 16 Range 10A DC (no AC) 2 megohm Plus HFE (Transistor) Tester (RS) £43.50
189m 30 Range 10A AC/DC 20 megohm Plus HFE Tester (RS) £69.95

FREQUENCY COUNTERS

(All models battery operated) (UK C/P £1)
PFM 200A Pocket 8 digit LED 200 MHZ 10mV (THANDAR) £67.50
Max 50 50 MHZ 6 digit LED Pocket (GSC) £56.35
Max 550 6 digit LED Pocket (GSC) £97.75
8110A 8 digit LED 2 range 100 MHZ Bench (SABTRONICS) £77.00
8610A 8 digit LED 3 range 600 MHZ Bench (SABTRONICS) £94.00
Max 100 5HZ-100MHZ 8 digit Bench LED (GSC) £97.75
8610B 9 digit LED 3 range 600 MHZ Bench (SABTRONICS) £113.85
8000B 9 digit LED 3 range 1000 MHZ Bench (SABTRONICS) £178.00
TF040 8 digit LCO 40 MHZ (THANDAR) £126.50
TF200 8 digit LCO 2 range 200 MHZ (THANDAR) £166.75
Thandar prescalers for any counter up to 200 MHZ.
TP600 600 MHZ £43.13
TP1000 with P/S 1 GHZ £73.00
OPTIONS
TF series carry case £6.84
AC adaptors (TF Series) £5.69
8 series AC adaptors £5.69
All models probe kits £7.95



ANALOGUE MULTIMETERS GENERAL RANGE

Low cost reliable meters (All supplied with belts/leads) (UK C/P 55p)
BANANA 15 range pocket 20K/Volt plus cont. buzzer £20.64
ET102 14 range 2K/Volt Pocket £5.95
ST5 11 range pocket 4K/Volt £6.50
NH56R 22 range pocket 20K/Volt £10.95
YN360TR 19 range plus Hfe test 20K/Volt £2.95
KRT500 16 range 10 amp DC range double 50K/Volt £16.50
ST303TR 21 range plus Hfe Test 20K/Volt £16.95
AT1020 18 range Deluxe 2KV and Hfe Tester £17.50
TMK500 23 range plus 12A DC plus cont. buzzer 30K/Volt £23.95
168M 36 range large scale 10A AC/DC 50K/Volt £28.50
360TR 23 range large scale 10A AC/DC Hfe test 50 meg. ohm. 1KV AC/DC 100K/Volt £36.95

Choose from UK's largest range

GENERATORS

R.C. Pulse, RF Function, Audio (UK C/P £1)
All models 220/240V AC
AUDIO 4 band Sine /SQ output
TE220 Max distortion 1% 20HZ/200KHZ £59.95
LAG27 Max distortion 0.5-1% (LEADER) 10HZ-1MHZ £86.25
LAG120A 5 band 10HZ-1MHZ Sine/SQ 0.05-0.8% dist. £146.00
LAG125 As LAG120A but 0.02% dist. (LEADER) £273.00
AG203 10HZ-1MHZ 5 band 0.1% Sine/SQ (TRIO) £129.95



RF (All with Int/Ext mod. variable output)
TE20D 100KHZ-100MHZ 6 band (300MHZ harm) £49.95
LSG17 100KHZ-150MHZ (450MHZ-harm) £71.30
LEADER
FUNCTION (all sine/SQ/Triangle/TTL etc.)
5020A 1HZ-200KHZ (SABTRONICS) £90.00
TG100 1HZ-100KHZ (THANDAR) £90.85
TG102 0.2HZ-2MHZ (THANDAR) £166.75
PULSE
TG105 5HZ-5MHZ various outputs (THANDAR) £97.75
4001 Ultra-variable 0.5HZ-15MHZ (GSC) £113.85

OSCILLOSCOPE PROBE KITS


(UK C/P 50p per 1 to 3) 8NC plug X1 £7.95
X10 £3.45
X1-X10 £18.50
X100 £16.95

DIRECT READ HV PROBE

(UK C/P 65p) D/40 KV: 20K/Volt £18.40

OSCILLOSCOPES

(C/P Dual trace £4.00: SC110 £1.00: Single Trace £3.00)
HM307 Single trace 10MHZ 5mV: 0.5 micro sec. Plus built in component tester 6 x 7cm display (HAMEG) £158.70
Optional case £18.40
3030 Single trace 15MHZ, 5mV: 0.5 micro sec. Plus built in component tester. 95mm tube. Trig. to 20MHZ (CROTECH) £172.50
HM203/3 Dual 20MHZ: Trig to 30MHZ 5mV: 0.5 micro sec. 8 x 10cm display (HAMEG) £253.00
HM203/4, An above but 2mV + Algebraic add (HAMEG) £276.00
3131 Dual trace 15MHZ trig. to 35MHZ 5mV: 0.5 micro sec. 130mm tube plus component tester £276.00
HM204 New model with component tester Dual 20MHZ delayed sweep: trig to 40MHZ 5mV: 0.1 micro sec 8 x 10cm display (HAMEG) £419.75 (Optional case £21.85)

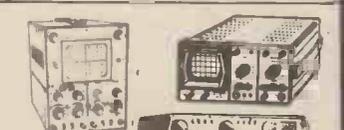

SC110A New model 10MHZ battery portable, 10mV: 0.1µsec 2" trace. All facilities (THANDAR) £171.00
(Options: Carry case £6.84 AC adaptor £5.69 Nicads £8.63)
SAFGAN - UK made dual trace Saigan all models 5mV sens. 0.5 micro sec 6.4 x 8cm display
DT410 Dual 10MHZ £205.85
DT415 Dual 15MHZ £217.35
DT420 Dual 20MHZ £228.85

AUDIO ELECTRONICS

301 EDGWARE ROAD, LONDON W2 1BN. TEL: 01-724 3564

ALSO AT HENRY'S RADII, 404/406 EDGWARE ROAD, LONDON W2

ALL PRICES INCLUDE VAT

Order by Post with CHEQUES/ACCESS VISA or Telephone your order. Allow up to 10 days for delivery (unless advised)

Sinclair ZX Spectrum

**16K or 48K RAM...
full-size moving-
key keyboard...
colour and sound...
high-resolution
graphics...**

**From only
£125!**

First, there was the world-beating Sinclair ZX80. The first personal computer for under £100.

Then, the ZX81. With up to 16K RAM available, and the ZX Printer. Giving more power and more flexibility. Together, they've sold over 500,000 so far, to make Sinclair world leaders in personal computing. And the ZX81 remains the ideal low-cost introduction to computing.

Now there's the ZX Spectrum! With up to 48K of RAM. A full-size moving-key keyboard. Vivid colour and sound. High-resolution graphics. And a low price that's unrivalled.

Professional power— personal computer price!

The ZX Spectrum incorporates all the proven features of the ZX81. But its new 16K BASIC ROM dramatically increases your computing power.

You have access to a range of 8 colours for foreground, background and border, together with a sound generator and high-resolution graphics.

You have the facility to support separate data files.

You have a choice of storage capacities (governed by the amount of RAM). 16K of RAM (which you can uprate later to 48K of RAM) or a massive 48K of RAM.

Yet the price of the Spectrum 16K is an amazing £125! Even the popular 48K version costs only £175!

You may decide to begin with the 16K version. If so, you can still return it later for an upgrade. The cost? Around £60.



Ready to use today, easy to expand tomorrow

Your ZX Spectrum comes with a mains adaptor and all the necessary leads to connect to most cassette recorders and TVs (colour or black and white).

Employing Sinclair BASIC (now used in over 500,000 computers worldwide) the ZX Spectrum comes complete with two manuals which together represent a detailed course in BASIC programming. Whether you're a beginner or a competent programmer, you'll find them both of immense help. Depending on your computer experience, you'll quickly be moving into the colourful world of ZX Spectrum professional-level computing.

There's no need to stop there. The ZX Printer—available now—is fully compatible with the ZX Spectrum. And later this year there will be Microdrives for massive amounts of extra on-line storage, plus an RS232 / network interface board.



Key features of the Sinclair ZX Spectrum

- Full colour—8 colours each for foreground, background and border, plus flashing and brightness-intensity control.
- Sound—BEEP command with variable pitch and duration.
- Massive RAM—16K or 48K.
- Full-size moving-key keyboard—all keys at normal typewriter pitch, with repeat facility on each key.
- High-resolution—256 dots horizontally x 192 vertically, each individually addressable for true high-resolution graphics.
- ASCII character set—with upper- and lower-case characters.
- Teletext-compatible—user software can generate 40 characters per line or other settings.
- High speed LOAD & SAVE—16K in 100 seconds via cassette, with VERIFY & MERGE for programs and separate data files.
- Sinclair 16K extended BASIC—incorporating unique 'one-touch' keyword entry, syntax check, and report codes.

Low Cost Alarm System

An easy-to-build security system that can be expanded to provide protection for any property.

Owen Bishop

THE COST of a professionally installed intruder detection system can be measured in hundreds of pounds so, with housebreaking on the increase, there is a lot to be said for a simple DIY system such as this. There are gains in the immediate savings on the considerable labour costs of installing the wiring, coupled with the fact that the commercially made 'box of electronic tricks' often seems to contain surprisingly little for the money. The electronic part of this system contains surprisingly little, too, but you will have to pay more than about £13 for all the components, including switches (but not including the case and battery). Perhaps this system does a little less than some of the more advanced of those commercially available, but it is straight forward in its action and there is virtually nothing to go wrong with it. Moreover it is not subject to false alarms caused by transients in the detector circuits, as are many of the simpler alarm systems. It has extremely low power consumption (only 0.75 mA) when quiescent, so it is ideally suited to battery power. A set of 'D' dry cells will last for many months of operation, 24 hours a day. A set of "AA" NiCad cells will last for 1 month on one charging. Thus, the system is independent of mains power failures or interruptions.

The noise generated by the solid state audible alarm is more than enough to wake the household or to rouse the attentions of neighbours. The alarm draws only 25mA, yet emits a piercing warbling tone with a power of 95 dB at 1m. Since its current requirements are low, it is feasible to wire two or more AWDs in parallel and site them in various parts of the house. But try using just one to begin with, for it is more than likely that you will find it does all that is needed.

The system has two kinds of detection circuit, the peripheral loop and the pressure mat system.

Peripheral Loop

This consists of normally closed switches mounted on all doors and windows, forming a loop which surrounds the area to be protected. The switches are in series so that, if any one switch is opened, the loop is broken and the alarm is sounded. It may be sufficient to protect ground-floor entry-points only, but upstairs windows should be protected too, if they are readily accessible from outside. Do not forget the less obvious points, such as coal-



shed doors, hatches and skylights.

It is best to use a magnetic switch specially made for the job. The switch consists of two parts (Figure 1). The reed switch itself is mounted on the frame of the door or window or may be concealed in a hole drilled in the frame. The other part contains a permanent magnet. This is mounted on or concealed in the door or window itself. When the door is shut, the magnet holds the reed switch closed. When the door is opened, even by only a centimetre or so, the switch opens and

the loop is broken.

The use of a normally-closed loop of this kind makes it difficult for an intruder to de-activate the system by cutting wires. A cut at any point on the loop sounds the alarm immediately. However, it is worth remembering that intruders do not always open doors or windows in the conventional way, in order to gain entry, especially if the door or window is securely locked or bolted. It may be easier for the intruder to quickly cut away the glass of a french door or picture

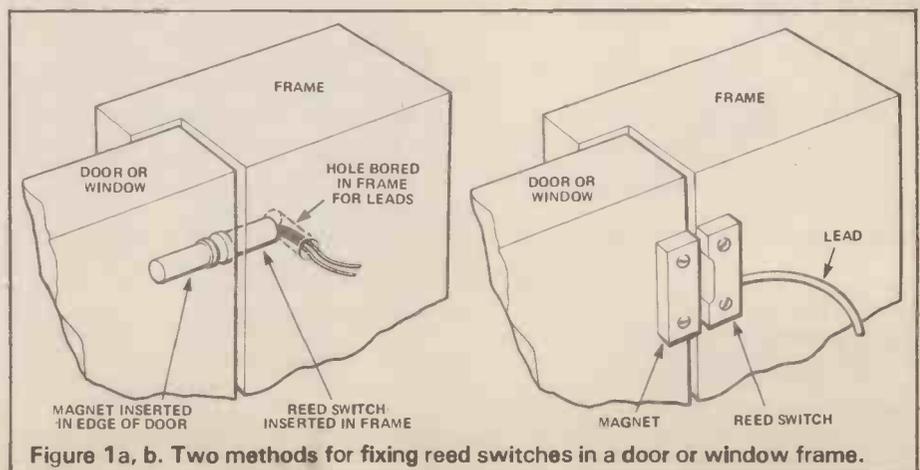


Figure 1a, b. Two methods for fixing reed switches in a door or window frame.

window, and enter through the hole. Another ploy is to cut an entry hole in the panel of a lightly-constructed door, or in the thin panelling which is often to be found alongside front-door units. Glass panes and thin panels may be protected by fixing strips of thin metal foil across them. Special window foil is sold for this purpose, together with terminal blocks for making connections to the end of the strip. These strips can be included as part of the peripheral loop.

Where the devices mentioned above are not suitable, it is usually easy to rig up a normally-closed microswitch which will be opened by an attempted break-in.

Pressure Mats

These are specially made mats which are placed beneath carpets or other floor coverings. They act as normally open switches, closing when stood on. If you have large pets loose in the house at night, or if any member of the family is a habitual sleep-walker, take care where you place them! Otherwise, they may be placed in strategic positions around the house, especially in areas such as the living room, where expensive equipment is likely to attract the intruder. The mats are wired in parallel, so that the circuit is completed when any one mat is stood on. This section of the system may also contain other normally-open switches. A valuable safety feature is to have a few push-buttons situated in the house where they can be used for sounding the alarm manually. This provides a quick and effective way of alerting the household in case of fire, for example. The wiring of this part of the system needs to be as carefully concealed as possible, for the system can easily be de-activated by cutting the wires, but since much of the wiring is beneath the carpets, this presents little difficulty. The wire used for the pressure mat system and the peripheral loop can be light-duty PVC covered wire (7/0.2 mm wire is cheap and perfectly satisfactory).

Circuit Details

The peripheral loop runs from the 12 V line, around the premises and back to the loop input terminal. If the loop is broken, the pull-down resistor, R2, causes the input voltage to IC1a to drop to 0V. The other input to IC1a is held high (at 12 V) by R1. If any one mat is stood on, the input voltage falls to 0 V (low). With two high inputs, the output of the NAND gate is low; this is the quiescent state. If the loop is broken, or if a mat is stood on, the output goes high.

A high output causes a current to flow through D1 and R3, charging C1. If the output remains high for long enough (about 0.5 seconds) the voltage rises above 6 V, which is effectively a high input to IC1b. The output then changes from high to low. If the output of IC1a is high for only a short time, as when a transient pulse appears on one of the inputs, C1 discharges through D2. Since there is no resistor in the return path, C1 discharges rather more rapidly than it charges, quickly eliminating the effect of the transient voltage. It would take an incredibly severe series of transients to break through this filter.

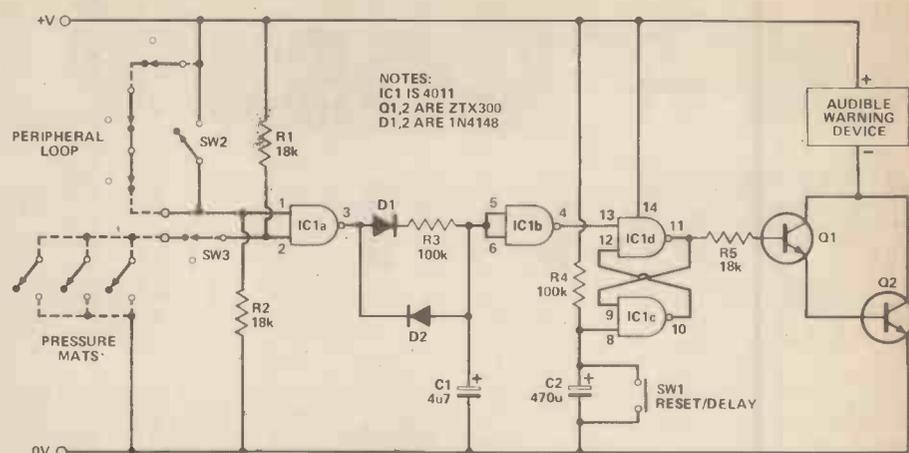


Figure 2. Circuit diagram of the alarm system.

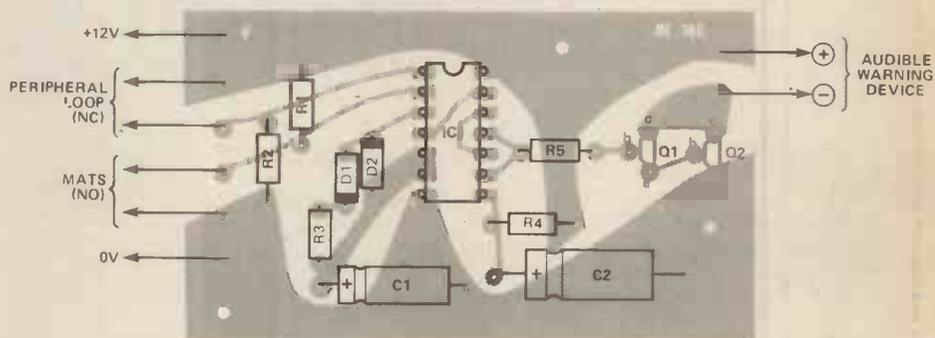


Figure 3. The component overlay.

Gates IC1c and d form a Set-Reset flip-flop. Its inputs are normally high and it is triggered to change state by a low pulse on one of the inputs. The Set input comes from IC1b. When this goes low, the flip-flop changes state, the output of IC1c changes from low to high and current flows to Q1, which is connected with Q2 as a Darlington pair to give sufficient current gain to operate the AWD.

The Reset input to the flip-flop comes from the junction of R4 and C2; it is held high by the pull-up action of R4, but when SW1 is pressed, the input falls immediately to low, thus resetting the flip-flop. While this input is low, a break in the loop or pressure on a mat can cause the input of the IC1c to go high and sound the alarm, but only for as long as the condition lasts, because the flip-flop does not change state permanently. The input to IC1c rises very slowly from 0 V as C2 charges through R4; it takes about 30 seconds to reach 6 V, providing the delay which allows the alarm to be set when the house is to be left unoccupied. After that, the flip-flop is ready to be triggered permanently by a low pulse from IC1b.

SW2 switches out the peripheral loop, by connecting the loop input directly to the 12 V line. This switch is not an essential part of the system, but it may be useful to de-activate the loop if, for example, a member of the household plans to return home late at night when the other members are in bed. This allows the mats to provide some kind of protection in the meantime. SW3 disconnects the mat system, and this too

is useful but not essential. During the evening, when all doors and windows are shut and the family is engrossed in the TV, the mat system is probably best kept inactivated. The peripheral loop gives adequate protection against intruders, many of whom prefer to break in when everyone is settled in one room with the sound from the TV to mask the noise of breaking glass or splintering timber.

Construction

There should be no problems in assembling the board and getting it to work straight away. As already mentioned, this circuit is ideally powered by a battery of 8 dry cells, or Ni-Cad cells. These may be contained in two 4-cell battery holders. Whether or not the circuit needs a case is a matter of opinion. It is preferable that the intruder should not be able to locate the circuit and cut off the power supply, so there is much to be said for hiding it away in a cupboard or drawer, eliminating the expense of a case.

The dead space below a table (Figure 5) is a good place to hide the circuit and batteries, though almost any other odd space will do; accessibility is not important, as you need renew the batteries so infrequently, provided that the switches can be reached easily. Concealed wiring should lead to the Reset/Delay button, hidden away in a convenient location fairly close to the door by which you normally enter the house. The AWD should be in some relatively inaccessible location, *not* beside the circuit itself. The wiring to it should be concealed as much as possible. The

Parts List

RESISTORS

(All 1/4 watt 5% carbon)
 R1, 2, 5 18k
 R3, 4 100k

CAPACITORS

(All electrolytic)
 C1 4u7 16V
 C2 470u 16V

SEMICONDUCTORS

Q1, 2 ZTX300
 silicon NPN transistor
 IC1 4011
 CMOS quad 2-input NAND
 D1, 2 1N4148
 signal diode

MISCELLANEOUS

SW1 Push-to-make
 push-button switch
 SW2, 3, 4 SPST
 standard toggle switches
 Siren (AWD), 12 V with optional
 multitone; battery holder (2); door
 and window switches; window foil
 and terminals; pressure mats; wire;
 solder etc.

BUYLINES page 34


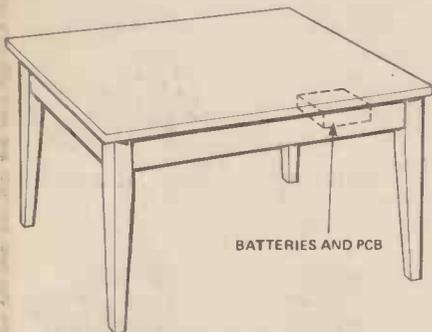



Figure 4. Top, the circuit board and power supply can be conveniently hidden underneath a table top — but make sure the switches are easily accessible (bottom) as well as being hidden.

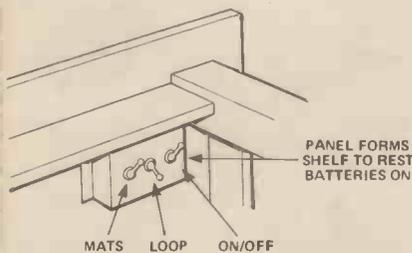

AWD could be mounted in the loft, where its sounds will readily be heard both inside and outside the house.

Maintenance

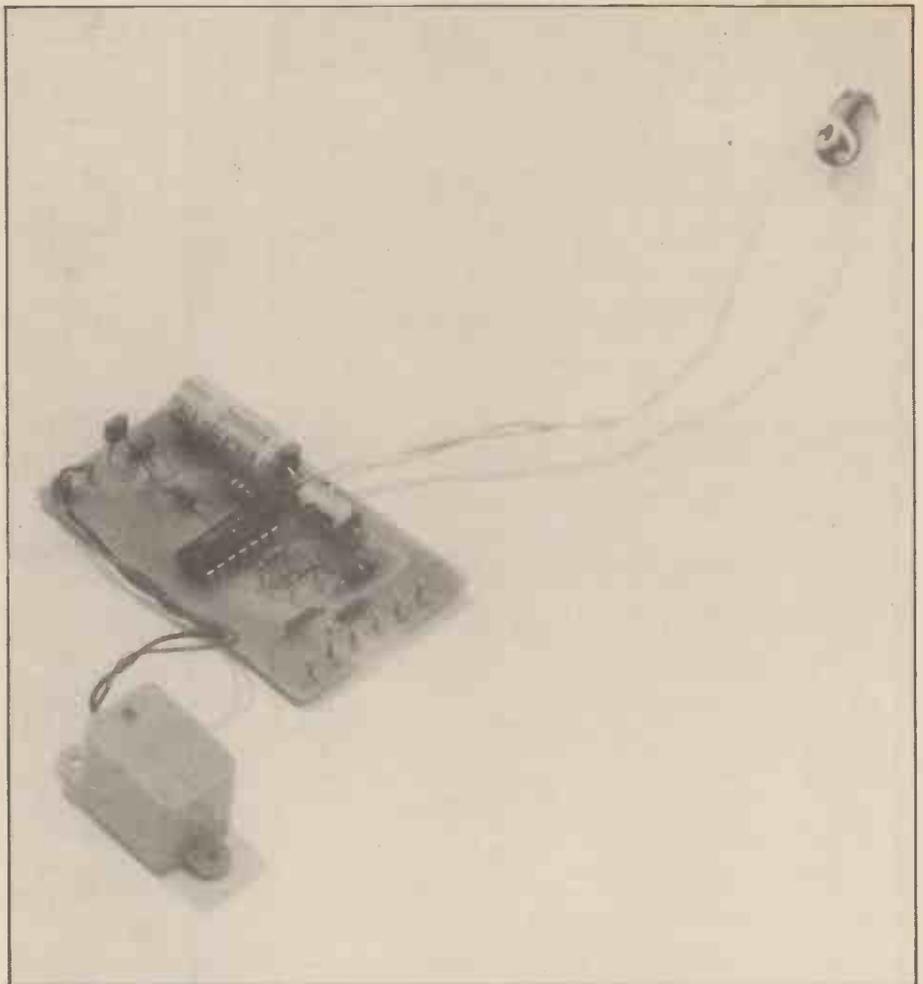A power-on lamp is not provided, since this would consume 25 times as much current as the quiescent circuit, so check the batteries regularly; remember that flat batteries will run the quiescent circuit well enough but may fail to provide enough power for the AWD. The check should include sounding the alarm; check each window and door switch every few months, and also each pressure-mat.




How It Works

THE TWO detecting systems, peripheral loop and pressure mats, provide inputs to the system which are normally high (12 V) but go low (0 V) when an intruder is detected. Since the wiring is many metres long and surrounds a houseful of electrical and electronic appliances, it frequently picks up transient electromagnetic signals. The switching on and off of equipment such as TV sets and refrigerators causes pulses to appear in the wires of detector systems, and these are often strong enough to trigger a flip-flop. The delay circuit filters out all these transients so that the alarm does not sound unless the detector circuit shows a low voltage for about half a second. It is not likely that an intruder could make an entry during so short a time, yet this is long enough for any transient to subside.

The action of the intruder triggers a flip-flop which sets off the alarm. This sounds continuously until the power supply is disconnected or the Reset/Delay button is pressed. Once the button is pressed, the flip-flop is inactive for a period of about 30 seconds. If the peripheral loop is broken during this period, the alarm sounds, but only for as long as the loop is broken. This delay is

essential if you are leaving the house empty, allowing the last person to remain in the house to press the Reset button and quickly leave by the front door. The alarm sounds very briefly as the door is opened and closed, but is silent after that. A few moments later the system becomes activated. On return to the house the alarm sounds but, if the first person in is prepared to act quickly and if the reset button is concealed not too far away from the door (on the inside, of course), it takes less than a second to silence the alarm. The delay operates similarly on the pressure-mat system, so there is no need to jump over the doormat on the way out.

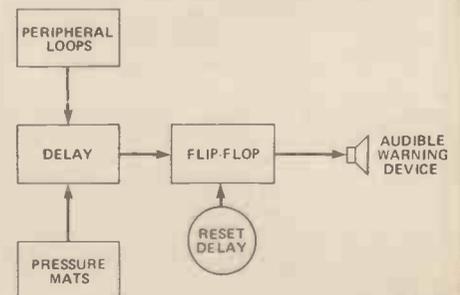

HE

Greenbank

Greenbank Electronics.
Dept E12H, 92 New Chester Road,
New Ferry, Wirral, Merseyside L62 5AG
(Tel: 051-645 3391)

READ THIS IF YOU VALUE YOUR JOB

I am writing to a worried man (or woman). I am writing to you. Are you scared of computers? Well not scared of the computers themselves, but scared of what they can do. Pretty well everywhere at work, on TV, these micro-things are being seen more and more all the time and you seem more and more to be getting left behind.

Do you have colleagues who are always spouting on and on about computers? Do you understand a word of what they're saying? Be honest, do you? Do they understand a word of what they're saying really, or are they just speaking words they've read out of a magazine or heard on T.V.?

What you need is a friend, an honest friend, who will try to help you. I will be your friend, I am your friend. My name is David Parkins, why not write to me or 'phone me? (my number is 051-645 3391).

I said I would be an honest friend so I'll begin now — I work for a firm which sells a computer in kit form, and I would like to sell you one. The name of the computer system is 'Interak 1'. I know you are going to buy a computer kit of some sort very soon, because you just can't let things go on as they are. 'Computing' is a club, and you're not a member yet. Worse still you may have bought a computer and found you still haven't a clue what goes on inside. Miracle chips they may be but it will be a miracle if you can understand what they do by just looking at them.

What I want to sell you is not just the pieces. I want to sell you 'the knowledge'. Then you'll know as much as I do, and you won't need me anymore. All I ask from you is that when you know what computing is really all about, that you treat others in the same way that you would like to be treated. Don't sneer at them because they don't know the difference between PASCAL and BASIC, they don't know what an RS232C interface is, or how a UART works, remember we all have to start somewhere.

Computers are bound to make our lives easier and happier (and richer) if they are used wisely, so it is vital that everyone be introduced to the 'Computer Club' as quickly as possible. Once everyone knows about computers we will be free to continue to make an honest living — at the moment there are all sorts of people who are uncropulously taking money from innocent people by taking advantage of their ignorance, and I for one just don't want to be a part of a business like that. Just read through a few advertisements, and think to yourself how can they all be the best?

When I said I am wanting to sell you 'the knowledge' please don't think I am offering a correspondence course. In my view that's not a suitable way to learn — a course has to proceed in simple logical steps — how an 'AND gate' works, and what is a 'flip-flop' and so on — microcomputers have left all that simple stuff behind long ago and you'll never catch up that way.

Learning computing is a bit like learning to swim, but you've got no time to waste. What I think you need is to be plunged in at the deep end — there's no time for splashing about in the paddling pool learning a bit at a time. But if you're going in at the deep end you'll need a friend to save you from drowning — that's what I'm here for.

Of course it's no swimming in a shallow end, but has to be replaced by the next model annually, before you can enter the water. Down at the shallow end this will cost you about £50 with a further £50 for the necessary RAM (memory). — at the deep end, where you'll find me, the cost is at least double.

I bet you're saying 'some friend this — he's already wanting me to spend twice as much as I thought'. Well it's true, I think you have got to, and here's why. The cheap systems are built down to a price — the 'chip count' (number of integrated circuits where all to be kept right down, preferably to four or five. There are two penalties to be paid. Firstly, no real expansion can be accommodated — the system will go so far then no further, secondly some special design 'tricks' have to be incorporated to make the chips do double duty and get the maximum performance out of the minimum resources. Don't get me wrong — some of the tricks are brilliant but the whole point in your buying a computer is so you can get an understanding yourself, not simply looking as a lump of silicon on (integrated circuit) where all the skill is buried. Once the design is 'encapsulated' in a master integrated circuit there's no way you'll ever find out what's inside unless the designer chooses to tell you, and he's hardly likely to tell you — he might want to use the same idea in the Mk II model next year.

Some people go into this with their 'eyes open' — but I think computing has come to a pretty poor state of affairs if you have to be prepared to throw away a hundred pounds or so on a system which cannot expand with you, but has to be replaced by the next model annually.

I would also say beware of committing the diametrically opposite mistake — a gimmick computer. This is one which is all things to all men. You name it, it's got it. This processor, that processor as an option. Level 1 expands to level 2 which has the optional what not interface which can easily be adapted for this or that.

Do you think the purchase of a computer is going to solve your problems?, of course not, learning is hard work. My computer (Interak 1) is ideal for your purposes I assume that you don't really know much about computers, you've probably got an interest in electronics, and with all the publicity that these micro chips are getting in magazines, TV, radio and newspapers you know that you've got to know all about them. Well I'll let you into a secret and give you some valuable information. There's too much going on for you to learn everything and new information is being created every day at such a rate that the longer you leave it to get started, the harder it will be to catch up.

Ask almost anyone what makes a good computer and they'll describe a monster. I'll show you the way to obtain sufficient knowledge to use computers for your pleasure, your work, and so that you can, if you want to, help others. It's all very well having a computer that has everything, but if you have too much hardware you'll be like the old woman who lived in the shoe — you won't know what to do.

I have a friend who has bought an Interak 1 System. (I say he's a friend but at the moment he thinks he's just a customer) and he's received a parcel, he's opened it and checked that he's got what we think we have sent him and I imagine he's ploughing his way through the manuals (yes one of the problems of being presented with a lot of information is having to read it all — carefully). He's got a lot of work ahead of him. Although he doesn't understand what it's all about, he'll learn from reading the manuals how to assemble the computer from its component parts, and then how to make it work.

I've put a lot of time and effort into this friendship, writing the words, and drawing what I think are helpful diagrams. I'm sure my friend will write to me with his problems and I'm also sure he will be delighted with his computer and any helpful remarks I may make.

I admit some of my answers to his problems may take the form of 'application notes', in fact most of them will, but that's just the way that I hope with helping lots of friends (when I get a letter with a problem or misunderstanding of something I've put in the manual, I write my answer in the form of an application note, then if I'm presented with the same problem again I can quickly give a well thought out answer in an application note with maybe just a covering letter.)

You've got a problem at the moment, you've either got a computer and not been able to learn all you need to know, or you haven't got one yet. Don't just go out and buy the first computer you see, or the biggest or the cheapest, buy the one that will help you to solve your problems. Remember that I'm here to help you, I've got a leaflet/data sheet set, that will probably tell you everything you need to know about my Interak 1 System. Write to me at Greenbank Electronics, using the above address and ask me to send you my Interak 1 leaflet. Now I warn you, there's quite a lot that I'll send you (about 36 sides of A4-size paper), it's type-written, with some hand drawn illustrations of the various kits. Of course it costs quite a bit to send through the post so an A4SAE would be appreciated but as you are my friend, if you don't enclose one I won't mind. By the way I'll probably enclose leaflets on some of the other things that my company sells but as I say to people I speak to, 'if I give you a leaflet you don't want please don't be offended'.

I'm being honest with you, I'm trying to make you into an Interak 1 user, because the more people who have this system, the more people I'll be able to exchange my programs with, and that's important.

You might not think that you are capable of building up a sophisticated computer system from component parts, but you need have no worries on that score. You do of course have to work carefully and patiently, but that's all you have to do. I haven't met anyone yet who was incapable of doing the job. Some people need a bit of help, some people need more help than others, but the way I look at it is that if you can't follow the instructions I have provided then it's my fault not yours. The same applies to testing the completed computer. If you make a board and you can't get it to work, I am here to help you — just pop the board into the post to me, and I'll plug it into my own system and will soon get it going for you.

Even if you don't buy the Interak 1 System then I do urge you to buy some sort of computer as soon as you can. If you have an children this is even more important. Children need computers almost as much as they need food and drink. There never was a more nutritious food for a young mind than a digital computer. Without a preconceived feeling that computers are somehow mystical, children are in a far better position to learn than we mere adults.

So far I have only let you think that the Interak 1 System will cost you money, but there are plenty of ways it will bring money in. Obviously if you have your own business you will know how much time and money a computer will save. And if you have brought yourself up to a standard where you can write your own programs and fix the system yourself (not that it will go wrong, you built it — remember) there won't be any hidden overheads to be paid. Other ways you can make money are writing programs that you can sell, or even writing a book. Don't think that you have to be particularly clever to do this. There may be thousands of people less fortunate than you who will be dying to hear of another's experiences. The last thing they will want will be some high faluting toms written by some lah-di-dah computer buff.








I look forward to hearing from you so I can tell you about my Interak 1 Computer. Write soon, David.



Post & Packing, 50p for KS kits, 75p for UK kits, £1.00 for cabinets. Send S.A.E. for catalogue of our extensive range of kits & cabinets. Trade, Educational & Export enquiries welcome.

7, Hughenden Road,
Hastings, Sussex,
TN34 3TG
Telephone: Hastings
(0424) 436004

ELECTRONIC KITS

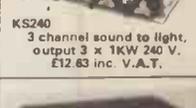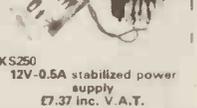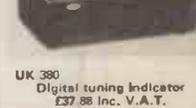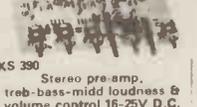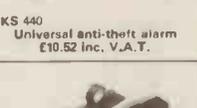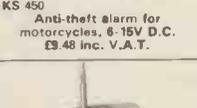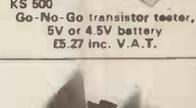 KS 100 Mini VHF Super-regenerative receiver 88-108 MHz 9V D.C. £9.27 inc. V.A.T.	 KS 130 2 Channel audio mixer, 20V D.C. Max £4.21 inc. V.A.T.	 KS160 Dark room timer, Timing range 1-99 secs. £11.58 inc. V.A.T.
 KS 200 Mini F.M. transmitter 88-108 MHz 9V D.C. (Not licenceable in U.K.) £7.37 inc. V.A.T.	 KS 238 3 channel microphone operated sound to light, 300W per channel, 240V A.C. £11.58 inc. V.A.T.	 KS240 3 channel sound to light, output 3 x 1KW 240 V. £12.63 inc. V.A.T.
 KS250 12V-0.5A stabilized power supply £7.37 inc. V.A.T.	 KS 300 Niccad battery charger, 10-20-46-150 mA, 15V D.C. max: 240V A.C. £8.42 inc. V.A.T.	 UK 380 Digital tuning indicator £37.88 inc. V.A.T.
 KS 390 Stereo pre-amp, treb-bass-mid loudness & volume control 18-25V D.C. £15.79 inc. V.A.T.	 UK 713 5 channel microphone mixer, A.C. 240V operated, £20.00 inc. V.A.T.	 KS 410 Car mounted digital clock, 12V D.C. £16.84 inc. V.A.T.
 KS 440 Universal anti-theft alarm £10.52 inc. V.A.T.	 KS 450 Anti-theft alarm for motorcycles, 6-15V D.C. £9.48 inc. V.A.T.	 KS 500 Go-No-Go transistor tester, 5V or 4.5V battery £5.27 inc. V.A.T.
 KS 420 Digital D.C. voltmeter, 999mV-999V, 0.5V D.C. £17.89 inc. V.A.T.	 UK 108 Miniature F.M. transmitter, Not licenceable in U.K. £3.46 inc. V.A.T.	 UK 113/U 10W integrated circuit amplifier £6.31 inc. V.A.T.
 UK 232 Antenna amplifier for AM/FM £5.27 inc. V.A.T.	 KS 260 3 channel chase light, 1KW per channel, 240V A.C. £10.52 inc. V.A.T.	 KS 300 Westminster chimes, (Big Ben) £9.48 inc. V.A.T.
 UK 562 Transistor and diode tester £14.73 inc. V.A.T.	 UK 716 Three-way stereo mixer £24.21 inc. V.A.T.	 UK 882 Centralized anti-theft alarm £33.67 inc. V.A.T.

PLASTIC CABINETS

MODEL	OUTSIDE DIMENSIONS				PRICE INC		
	WIDTH		HEIGHT				
	INCH	mm	INCH	mm			
OO/3001.00	7.54	191.4	1.81	46	6.89	175	£4.21
OO/3001.02	7.54	191.4	2.36	80		175	£4.21
OO/3001.04	7.54	191.4		74	6.89	175	£5.27

Lofty

A handy loft-light alarm to build

RETURNING from a weekend away, not so long ago when the weather was still warm, we happened to meet our neighbours from across the street. The evening was balmy, though the light was fading fast as we exchanged pleasantries about the weather and Botham's batting while we unloaded the car; then our neighbour dropped his bombshell. "By the way", he said innocently, "did you know you left a light on in your loft? We can see it from our upstairs window". In fact, we could see it from across the street, shining brightly through narrow chinks between some of the tiles.

That rapidly put an end to the conversation as, feeling foolish, I hurried into the house thinking, as I climbed the ladder, of the electricity bill we were about to receive (without thanks, oh lord); those lights (two 150 watt bulbs) had been burning continuously for at least three weeks!

From that incident, Lofty was born — a simple device that could be connected across the light switch and which would sound an alarm after a preset period, unless the light had been turned off. As finally constructed, Lofty actually has two alarms; a winking LED for visual warning and a two-tone beeper which, although not particularly loud, generates a penetrating tone that will be audible throughout a quiet house.

Another aim, when we designed Lofty, was to keep the size of the unit as small as possible, and to keep the cost low.

For these reasons, we used a novel transformerless power supply. As a result of this design, though, *all parts of the circuit are at mains potential with respect to earth and are therefore possibly lethal to touch. No metallic parts must be exposed when the unit is operational, and particular attention must be taken in the construction to ensure that the unit is effectively insulated.*


As an added precaution, it should be mounted in an inaccessible position, well out of the way of prying fingers! The method is perfectly safe provided these precautions are taken.

The Circuit

The transformerless power supply is based on C1; this has an impedance of 6k7 ohms at 50 Hz mains frequency. Therefore, the current through it at 240 VAC is 36 mA. Although it is acting as a 'dropping resistor' and is passing a fairly high current, C1 does not dissipate any power; that is, it does not get hot.

CAUTION

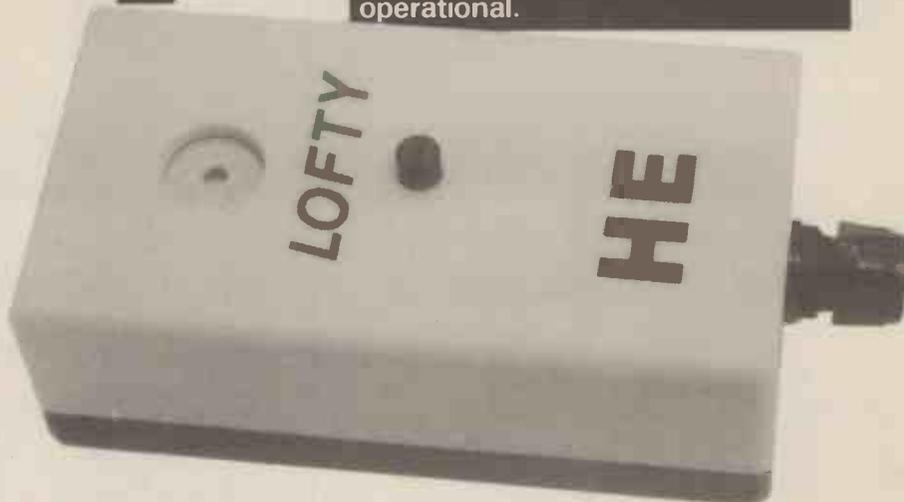The 'Lofty' uses a transformerless power supply and, as a result, all parts of the circuit are at mains potential and are possibly lethal to touch. No metallic parts must be accessible when the unit is operational.



The AC current through C1 is then rectified by the diode bridge, BR1, and charges C2 to a maximum of 15V, determined by ZD1; this is the power rail for most of the circuit. Resistor R1 drops the supply voltage further before it is fed to the internal shunt regulator in IC1, and C3 provides some additional filtering.

IC1 is a ZN1034 precision timer IC made by Ferranti. It contains an oscillator, a 12-bit counter and a regulator circuit. When power is applied to the chip, the counter is reset; 4095 oscillator cycles later, the output at pin 2 goes high.

The time period is determined by the oscillator frequency; the higher the frequency, the longer the time period. The frequency is set by just two components — R2 and C4. The values used here give a period of around 45 minutes, but this can easily be altered, as described later.

While IC1 is still counting, the two sections of IC2, a dual 555 timer, are prevented from operating by the low output from pin 2 of IC1 on their reset inputs, pins 4 and 10. Then, when IC1 times out, its pin 2 goes high and enables both sections of IC2. It is now possible for LED1 to light, since its anode is no longer at OV.

IC2b will oscillate at a frequency of a few kilohertz, but the tone will be modulated from the output from IC1a, which is generating an asymmetrical waveform at 1 or 2 Hz. As well as modulating the output from IC2b, this waveform also causes LED1 to flash on and off. The output from IC2b is fed to the piezo-electric sounder, X1, which generates the audio tone.

Construction

Start by assembling the timer and tone generator components on the PCB; points to watch here are that the ICs


and the tantalum capacitor (C4) are correctly oriented. At this stage, the time period can be changed by altering the values of R2 and C4. The delay, in seconds, is equal to $0.7 \times 4095 \times R2 \times C4$, with R in megohms and C in microfarads; R2 should not be reduced below 10k and C4 must be between 10n and 100u.

Before proceeding with the power supply section (BR1, ZD1 and C2), test the timer and audio beeper by connecting a temporary 12-15 volt supply to the unit. Naturally, you will have to wait 45 minutes (or whatever period you have set) to find out if all is well! If the unit does fail to work for some reason, first carry out the usual checks for solder bridges, dry joints and so on. The operation of IC2 can be checked by first removing IC1, then applying about 3V to the IC1 pin 2 connection. This will enable both sections of IC2 and it should immediately burst into life unless there is a fault present. Testing IC1 will be more difficult, although there is very little that can go wrong here. If you do need to check the IC, it would be best to change R2 and C4 to give a short time delay — 39k and 10n give a one second delay — otherwise fault-finding could take a very long time!

When the timer and audio generator are working, the power supply can be wired up. Before proceeding with this, however, check that the LED is bright enough to be seen. If not, reduce the value of R3, but not below 100R.

Power Supplied

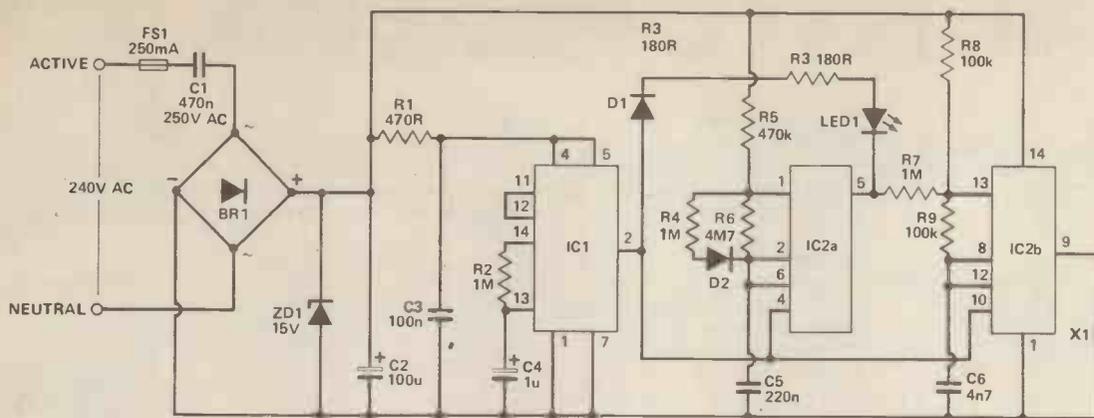The vital component in the transformerless power supply is C1; this must be rated for 240V/50Hz operation ie, at least 250 VAC, 600 VDC working. When it has been soldered in place, make sure C1 cannot vibrate by tying it down with two cable ties passed



NOTES:
 IC1 IS ZN1034
 IC2 IS 555
 D1,2 ARE 1N4148 OR SIMILAR
 ZD1 IS 15V 1W3 ZENER
 BR1 IS 1A 800V (W08)
 LED1 IS LARGE RED LED (PLASTIC)
 FOR PANEL MOUNTING
 X1 IS PB2720 PIEZO BUZZER

Figure 1. The complete Lofty circuit — note that the mains earth lead is not connected.

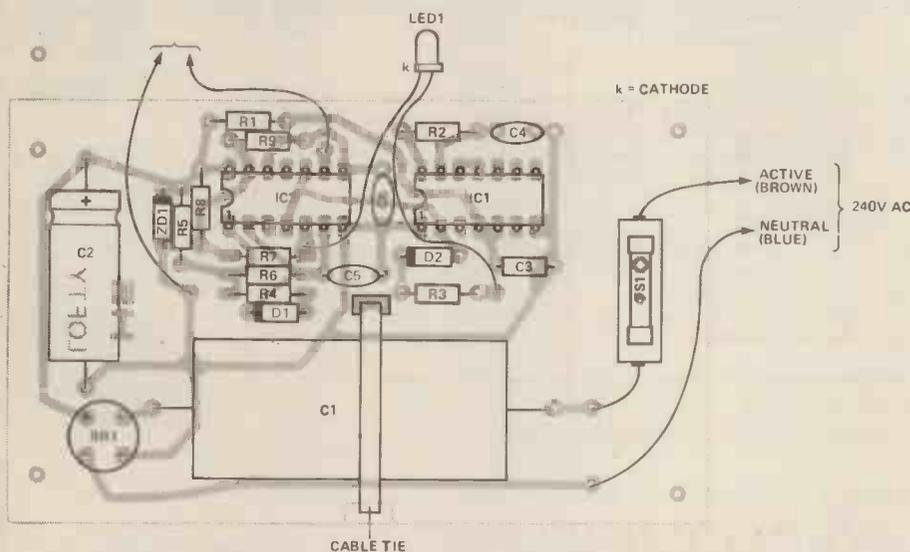


Figure 2. The PCB component overlay. Capacitor C1 takes up most of the board space!

through the holes in the PCB. Next, mount the diode bridge, C2 and the Zener diode, then the fuse, FS1. This is included to protect against the possible failure of C1; if it ever needs to be replaced, remember to *totally disconnect* the 'Lofty' before doing so!

Insulation

The last stage is to mount the piezo transducer and connect it to the appropriate points on the PCB. Use a stout piece of plastic film between X1 and the underside of the case to insulate the diaphragm of the transducer because, as explained earlier, this could be 'live' and thus potentially lethal to touch. Finally, mount the PCB in the case using M3 screws. It is now ready to be wired into the loft light circuit.

Wired Up

The unit should be placed near the loft opening, where it can easily be seen and the sound of the alarm will not be muffled. A length of ordinary two-core lighting flex is connected from the Lofty's mains input to the loft light, so that the unit is turned on with the lights. Forty five minutes later, the alarm will sound. If you are still working in the loft, reset the unit by briefly turning off the lights, initiating another timing period.



Parts List

RESISTORS

(All 1/4 watt 5% carbon)

R1	470R
R2,4,7	1M0
R3	180R
R6	4M7
R8,9	100k

CAPACITORS

(All polycarbonate unless noted)

C1	470n
	250 VAC/600 VDC minimum
C2	1000u
	25 V electrolytic
C3	100n
C4	1u
	35V tantalum
C5	220n
C6	4n7


SEMICONDUCTORS

IC1	ZN1034
	precision timer
IC2	555
BR1	W08
	800V, 1A bridge rectifier
ZD1	BZX61C15
	15V, 1.3W Zener diode
D2,3	1N4148
LED1	panel mounting LED
	with plastic (not metal) bezel

MISCELLANEOUS

FS1	250mA
	20 mm fuse
X1	PB2720
	piezo-electric buzzer
	Chassis-type fuse holder; small cable gland; plastic LED bezel; Verobox enclosure (see Buylines); PCB; IC sockets; stout plastic film, 1" x 1"; M3 bolts; cable ties; wire, solder etc.

BUYLINES page 34

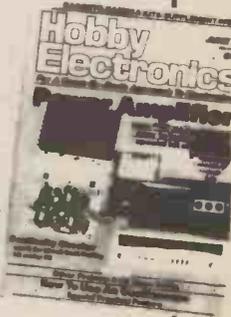

BACKNUMBERS

February 1980
Passion Meter, Win Indicator, Short Circuit Special, Kit Review Special, Into Electronics Construction Part 1.

May 1980
MiniClocks, 5080 Preamp, Model Railway Track Cleaner, 5080 Loudspeakers, Loudspeaker Crossover Design, Radio Controlled Model Survey.

June 1980
Microbe Radio Control System, Egg Timer, Two Watt Amplifier, Fog Horn, Short Circuits, LEDs and LED Displays.

July 1980
Sound-Operated Flash Trigger, 18+18 Car Stereo Booster, Hazard Flasher, Electronics in Photography, Electronic Espionage, Piezo Electricity.

August 1980
EquiTone Car Equaliser, Pass-The-Loop Game, Gaztec Gas Detector, OP-Amp Checker, In-Car Entertainment Survey, Introducing Microprocessors.

September 1980
MicroMixer, Reaction Tester, Guitar Phaser, Development Timer, Teletext Explained, Into Digital Electronics Part 1.

October 1980
Kitchen Timer, Tug 'o' War Game, Light Dimmer, Freezer Alarm, Intruder Alarm, Temperature-Controlled Soldering Iron.

January 1981
Car Rev-Counter, Bench Amplifier, Sound-Into-Light Converter, Chuffer, Electronic Games reviewed.

February 1981
Heartbeat Monitor, High-Impedance Voltmeter, Medium Wave Radio, Two-Tone Train Horn, Audio Signal Generator.

March 1981
Public Address Amplifier, Windscreen Wiper Controller, Bicycle Speedometer, Photographic Timer, Microcassettes.

April 1981
Pre-Amplifier Part 1, Super Siren, Guitar Tremolo, Russian Roulette Game, Doorbell Monitor, Anatomy of a Space Shuttle.

May 1981
Electronic Organ, Voice-Operated Switch, Infra-Red Controller, Pre-Amplifier Part 2, Audio Millivoltmeter.

June 1981
Power Amplifier Part 1, Continuity Checker, Envelope Generator, Early Radio, Gadgets, Games and Kits Supplement.

July 1981
Burglar Alarm, Doorbuzzer, Treble Booster, Electronic Aids for the Disabled, Power Amplifier Part 2.

August 1981
Electronic Ignition, Thermometer, Electronic Organ (final part), RPM Meter, Bench Power Supply, Radio Control Survey, Into Electronic Components Part 1.

All of the 1980 issues, except January and April, are still available together with the remaining issues from 1981.

All backnumbers cost £1.25 each. For those of you who only want copies of articles, we do offer a photocopying service. Each copy costs £1.25 and information as to its title and publication date should be given. Ordering backnumbers and photocopies could hardly be easier, just fill in the coupon, cut it out and send it to:

**Hobby Electronics,
145 Charing Cross Road,
London WC2H 0EE**

Please remember to mark your envelope with the service you require, **BACKNUMBERS** or **PHOTOCOPIES**, otherwise our mailroom won't like you.

HOBBY ELECTRONICS BACKNUMBER ORDER FORM

Please send me the following items:

NAME

ADDRESS

Back issues at £1.25 each

I enclose £.....

Cheques and Postal Orders should be made payable to ASP Ltd.

HOBBY ELECTRONICS PHOTOCOPY ORDER FORM

Please send me the following items:

NAME

ADDRESS

Photocopies of in the

..... issue at £1.25 each

I enclose £.....

Cheques and Postal Orders should be made payable to ASP Ltd.



19" RACK MOUNTING CABINET. £23.95
 Front Panel 480 x 150 mm Rear Case 425 x 250 x 140 mm **£19.50**



Or Free Standing
Brushed Ali Front
 with
'CROME HANDLES'

This is a professional rack mounting cabinet that will allow you to get your equipment off the bench. Rack mounting provides security for your equipment and easy access for maintenance. This Precision rack mounting cabinet has all of the features you would expect from a professional unit.

★ Top, bottom and rear cover removable for access ★ Plates have heavy duty grey paint finish ★ Front panel is heavy gauge - 3mm aluminium ★ Strong, screwed, construction throughout - screws included ★ Heavy gauge chassis mounting plate is pre-drilled and has four mounting positions to choose from ★ Front panel is of brushed aluminium finish enhanced with heavily floured handles ★

19" ENCLOSURES EURO SIZES

AT LOW COST	Rear Case h = u Size less 10mm
1u. z 44mm	2u - £17.50
Special Sizes Made To Suit REQUIREMENT	3u - £18.50
	4u - £22.75
	5u - £26.95
	6u - £35.25

28 SWITCH SLIDES TOGGLES PUSH ROCKERS RRP £3.50 Offer - £3.95

ADD V.A.T AT STD RATE & ORDERS UNDER £5.00. P & P 50p. ABOVE ITEM £2 P & P

'metal cabinets'

These are beautifully manufactured cabinets with an aluminium base and 18 gauge steel covers. They come fitted with rubber feet (to please the wife!), louzred for ventilation and finished in an attractive two tone finish. They make excellent cabinets for power supplies, remote control units and many more projects.

a - 102(d) x 66(h) x 83(w)mm	a £1.70
b - 160(d) x 61(h) x 103(w)mm	b £2.55
c - 160(d) x 76(h) x 134(w)mm	c £3.04
d - 184(d) x 70(h) x 160(w)mm	d £4.08

Ask for our **FREE Catalogue.**

TRADE PRICES ON CITY ORDERS

SOLDERING IRON 30 W ~~£1.75~~

RELAY-A-QUIP, Moat Lodge, Stock Chase, Maldon, Essex. phone, 0621-57242

VISA

11am 8pm MON-SAT

MARCO TRADING

Primary	Secondary	Current	1+	10+	100+
240V	4.5-0.4.5V	400m/a	50p	45p	35p
240V	6-0-6	100m/a	58p	52p	43p
240V	6-0-6	500m/a	55p	60p	48p

Manufacturers note: We can supply OFF THE SHELF 1000+ quantities of the above transformers.

These high quality British made European Adaptors are ideal for driving radio's, cassette recorders, TV games, calculators etc etc.

These adaptors fit the UK shaver socket.

			1+	10+	100+
E08	4.5V DC	200m/a	50p	45p	32p
EM3	6V DC	200m/a	£1.00	80p	55p
E09	6V DC	400m/a	£1.50	£1.25	85p

MULTIMETER SPECIAL

Russian type U4324 20,000 O.P.V.
 DC Voltage: 0.6, 1.2, 3, 12, 30, 60, 120, 600, 1200.
 AC Voltage: 3, 6, 15, 60, 150, 300, 600, 900.
 DC Intensity M/A: 0.06, 0.6, 6, 60, 600, 3000
 AC Intensity M/A: 0.3, 3, 30, 300, 3000.
 DC Resistance: 0.2, 5, 50, 500, 5000K.
 ge level dB: 10 to + 12.

Special Price £15.00 inc p/p and VAT

Send 25p Now for our latest Catalogue. Fantastic Value it includes capacitors, diodes, resistors, transistors, LEDs, boxes, cable, prepaid envelopes and much, much more.

Please add 35p postage and packing and 15% VAT to all orders.
 Send orders to:

MARCO TRADING (Dept HE12)
 The Maltings, High Street,
 Wem, Shropshire SY4 5EN
 Telephone: WEM (0939) 32763

Every order receives our latest special offer lists. Or send SAE.
 All orders despatched by return of mail.

ALCON SPECIAL OFFER

20Ω/V d.c.
 4kΩ/V a.c.

mini 20

The Mini 20 is an ideal instrument for the constructor.

This special offer is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £10 on the normal retail price.


The 28 ranges cover all likely requirements. Operation is straight-forward, just turn the selection switch to the required range position.

RANGES
 d.c. V: 100mV, 3V, 10V, 30V, 100V, 300V, 600V
 a.c. V: 15V, 50V, 150V, 500V, 1500V
 d.c. I: 50μA, 600μA, 6mA, 60mA, 600mA
 a.c. I: 30mA, 300mA, 3A
 Ohms: 2kΩ, 2MΩ
 (Accuracy: 2% d.c. & resistance, 3% a.c.)
 Dimensions: 105 x 130 x 40mm
 Movement protected by internal diode and fuse.

For details of this and the many other exciting instruments in the Alcon range, including multimeters, component measuring and electronic instruments please write or telephone:

ALCON Instruments Ltd.

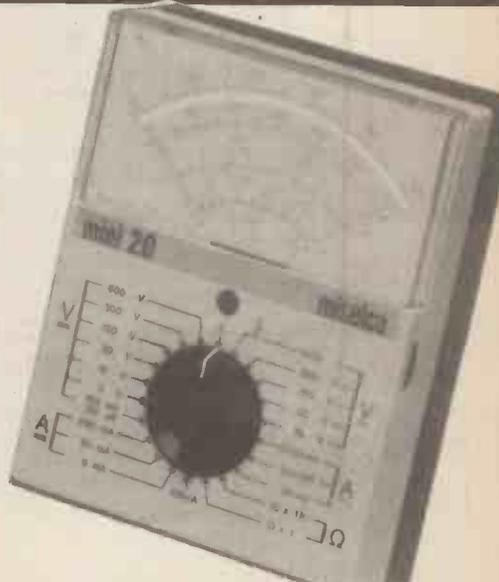19 MULBERRY WALK · LONDON SW3 6DX · TEL: 01-352 1897 · TELEX: 918867



Supplied complete with case, leads and instructions.

only £21.60
 INCLUSIVE OF POST PACKAGE - VAT
 Goods despatched by return of post

METERTECH MODEL 3T 3½ DIGIT LCD MULTIMETER



- ★ 12.5mm DISPLAY
- ★ 10MΩ INPUT IMPEDANCE
- ★ AUTOMATIC ZERO ADJUSTMENT
- ★ AUTOMATIC POLARITY SWITCHING
- ★ OVER RANGE INDICATION
- ★ FUSE CIRCUIT PROTECTION
- ★ BATTERY LOW INDICATION
- ★ HFE MEASUREMENT FACILITY
- ★ DIODE CONTINUITY CHECK
- ★ ACCESSORIES INCLUDED
- TEST LEADS, BATTERIES & INSTRUCTION MANUAL
- ★ SIZE 150 x 90 x 35mm
- ★ WEIGHT 300g
- ★ SAMPLING TIME 0.25 sec

PLEASE SEE AUGUST
EDITION HE FOR
REVIEW OF THIS
METER

DC VOLTAGE (5 ranges) 0.8% accuracy 100 μ V to 1000V
AC VOLTAGE (2 ranges) 1.2% accuracy 100mV to 1000V
DC CURRENT (5 ranges) 1.2% accuracy 100nA to 10A
RESISTANCE (4 ranges) 1% accuracy 1 Ω to 2M Ω

Price £49.95 includes VAT, postage & packing.
Optional accessories.

Deluxe protective case £6.90 including VAT p&p
10AC current shunt £8.90 including VAT p&p



62 CURTIS ROAD, WHITTON,
HOUNSLOW, MIDDLESEX TW4 5PT
TEL (01) 894 2723



Revolution in circuit
board maker kits from
leading manufacturer



CIRCUIT MAKER

The CM100 Circuit Maker provides everything necessary to produce positive photographic film masters from same-size published circuit layouts and to make either single or double-sided boards from these other positive film masters.

Features

- Economic and simple to use.
- No expensive equipment required e.g. darkroom, UV box, cameras etc.
- Photographic experience not needed.
- Simple etching process.
- Universal exposure and assembly frame custom-designed, professional quality.
- Ergonomically designed storage pack which includes free-standing shelf for chemicals.
- Step-by-step instruction manual, workbench and trouble-shooting charts provided.
- Special clearing process ensures excellent clear positive film masters.
- Photoresist available in non-aerosol form to eliminate 'spotting' when applied to the board.

Mercia Electronics, Coronet House, Upper Well St., Coventry CV1 4AF.

Send for full illustrated brochure
and price details, post to:

Name

Address

Signature



Coronet House,
Upper Well Street
Coventry CV1 4AF
Tel: (0203) 58541

B.N.O.S. ELECTRONICS

Don't miss the Christmas-rush. Don't waste your money on throw away Dry cell batteries. Buy EverReady **RECHARGABLE Nicad Batteries**, run your toys, radios, cassettes or even kitchen equipment. Each charge lasts as long as a dry cell, but you can re-charge them up a 1,000 times or more, so think of the money you can save at 1p a charge.

BUY NOW

and have a set charged ready for Christmas.
(Available in four standard sizes)

Ni-CAD 'AA'	Dry Cell Equivalent	Capacity	1-9	10-24	24-100
'AA'	HP7	0.5AH	0.90	0.85	0.82
'C'	HP11	2.2AH	2.40	2.30	2.20
SUB 'D'	HP2	1.5AH	2.30	2.15	2.00
'D'	HP2	4.0AH	3.40	3.20	3.05
PP3	PP3	0.11AH	3.90	3.65	3.40

Ni-Cad Battery Chargers

Type AC1 charges up to 4 x AA cells at a time £5.90

Type MC2 charges up to 4 x AA, C, D cells & also PP3's. £8.50

Postage FREE on mainland U.K. orders.

SEND NOW your cheque/Postal orders
All prices include VAT

B.N.O.S. ELECTRONICS, DEPT H.E.,

GREENARBOUR, DUTON HILL,
GT DUNMOW, ESSEX CM6 3PT
TEL: 0371 84767



Also ACCESS & VISA cards welcome

MIGHTY NINETY PACKS

SUPER VALUE PACKS ALL AT 90p each
BUY SIX PACKS AND GET A SEVENTH FREE

Please add 20p per pack postage

Please allow 7 days delivery.

- MN2. 200 ½ & ½-watt Resistors.
- MN3. 100 1 & 2-watt Resistors.
- MN4. 50 Wirewound Resistors.
- MN5. 100 metal oxide Resistors. 1%, 2% and 5%.
- MN6. 12 asstd potentiometers.
- MN7. 25 asstd skeleton preset Resistors.
- MN8. 50 asstd Electrolytic Capacitors.
- MN9. 100 asstd Ceramic Capacitors Pite. disc. tub and monolithic etc.
- MN10. 100 mixed capacitors. Polyester, Polystyrene, Metallised, Radial and Axial types.
- MN11. 20 asstd Silver Mica Capacitors.
- MN12. 8 Tantalum Bead Capacitors (useful values).
- MN13. 20 asstd Transistors. BC, 2N Series + Power etc.
- MN14. 40 IN4148 Diodes.
- MN16. 20 min. wire-ended Neons.
- MN17. 2 12-volt Relays. Ex nearly new equip. lampholders.
- MN19. 15 P.C.B. mounting M.E.S. lampholders.
- MN20. 1 240-110 to 12-volt 100ma Transformer.
- MN21. 1 240-110 to 24-volt 100ma Transformer.
- MN22. 8 2" Led's with clips, 4 red, 2 yellow, 2 green.
- MN23. 300 asstd screws, nuts, washers, self-tappers etc.
- MN25. 80 Assoc. rubber grommets.
- MN29. 75mts equipment, wire, asstd colours and sizes.
- MN30. 3 x 2mm length, 3 core, mains cable.
- MN32. 15 30pF Beehive trimmers.
- MN34. 25 min glass reed switch.
- MN35. 10 asstd switches, toggle, slide, micro etc.
- MN36. 10 sub-min SP, C/O slide switch.
- MN37. 10 asstd audio connectors. Din phone etc.
- MN40. 50 Polystyrene capacitors.
- MN45. 35 asstd diodes Zener, rect. signal, switching.
- MN46. 15 asstd Zener diodes.
- MN48. 200 items 4BA asstd length screws, nuts & washers.
- MN49. 200 items 6BA asstd length screws, nuts & washers.
- MN50. 3 pieces of veroboard useful sizes, min total 35 sq inch.
- MN51. 10 x 0.2" red LED.
- MN52. 10 x 0.125" red LED.
- MN53. 20 x 0.1 mfd 25v ceramic disc caps.
- MN54. 20 x 0.1 mfd 25v ceramic disc caps.
- MN55. 10 watt audio amp board with circuit.
- MN56. 10 14 pin low profile IC skt DIL.
- MN57. 10 16 pin low profile IC skt DIL.
- MN60. 10 asstd TTL IC's.
- MN63. 50 mixed polyester caps C280, Siemens etc.
- MN64. 5 Press to make min switches.
- MN68. 200 asstd veropins, turret tags, PCB pins etc.
- MN69. 4 min push to break switch.
- MN70. PCB with push SW with attractive chrome plastic knobs 1 x BD241, 1 x BC300, 2 x BC237, 1 x BC204, 4 x 1N4002, 2 x CMOS 4025, 200mm fuse holder + 22 resistors, capacitors, diodes etc.
- MN71. IZ414 RADIO IC.

See us at Breadboard, Stand 78
CHORDGATE LIMITED

RETAILER SHOPS AT
75 FARRINGDON ROAD, SWINDON, WILTS.
Tel. (0793) 33877
21 DEPTFORD BROADWAY, LONDON SE8

ELECTRONIC COMPONENTS

THE CHOICE IS YOURS — CALL AT OUR NEW SHOWROOM OR USE OUR VERY FAST MAIL ORDER SERVICE.

EITHER WAY WE'LL KEEP YOU HAPPY *****

Furthermore we promise if any part ordered by mail fails to please just return within 7 days for a full refund.

For a vast selection of electronic components & equipment of all kinds. Here is just a selection of our stocks. Many more items listed in our catalogue available now 70p post paid.

SPARE TIP		DENCO COILS		SPARE ELEMENT		DIL SKTS		DIODES	
55p	ST4 soldering iron stand with large sponge	IFT13	£1-15	1-70	1-70	8 pin	10p	1N4005	8p
55p	IFT18	£1-45	2-10	20 Pin	20p	14 Pin	11p	1N5408	29p
55p	3T & 5T Blue or Red	£1-34	1-80	22 Pin	24p	18 Pin	17p	1N4148	5p
Spare tip sizes available 1mm, 2.3mm, 3mm or 4.7mm (1mm not for X25)				24 Pin	27p	20 Pin	20p	100 for £2-50	
				28 Pin	35p	40 Pin	40p	0A47	10p
								400mW Zener	9p
								1.3V Zener	19p

RESISTORS		POTENTIOMETERS	
1W 5% C.F.	1R to 10M	2p each	100 for £1.00
1W 5% C.F.	10R to 1M	2p each	
1W 5% C.F.	10R to 820K	5p each	
1W 1% M.F.	10R to 680K	5p each	100 for £3.00
100 off prices one value only — no mixing		Preset .1W Horiz	
		.1W Vert	
		Std Single Pot	
		Single & Switch	
		Dual Gang	

CAPACITORS		ANEX SOLDERING IRONS	
Min Plate	1.8pF to 47pF	C	15 watt 4-30
Ceramics	56pF to 220pF	CCN	15 watt 4-45
	270pF to 1000pF	CX	17 watt 4-50
	1200pF to 4700pF	X25	25 watt 4-60
100 off any one type less 30%			
Electrolytics — polys — Tants — Full range in catalogue			

TRANSISTORS		INTEGRATED CIRCUITS	
AC128	0-24	CMOS	LS00
AF117	0-52	4001	0-14
BC107	0-10	4011	0-15
BC107C	0-12	4013	0-15
BC108	0-10	4017	0-15
BC109C	0-12	4022	0-28
BC109	0-10	4046	0-15
BC109C	0-13	4049	0-18
BC182L	0-10	4066	0-24
BC184L	0-10	4070	0-40
BC212L	0-10	4093	0-06
BC214L	0-10	40106	0-06
BD112	0-80	4511	0-28
BD115	0-68		
BD124	1-58		

V. REGULATORS (FIXED)		V. REGULATORS (VARIABLE)	
+ve	100mA	78L05	-78L12
-ve	100mA	79L05	-79L12
+ve	1 Amp	7805	-7812
-ve	1 Amp	7905	-7912

PRINTED CIRCUIT BOARDS		TRICs & SCR's	
1.6mm Single sided board	6 x 6	0-85	TIC226D
6 x 6	0-85	0-90	400V 8A triac
6 x 12	1-66	0-94	
12 x 12	3-05	0-89	

FOTO COATED RESIST BOARD		LED'S & SCR'S	
1.6mm Single sided	100 x 160mm Euro	1-70	3mm Red
203 x 114mm	1-83	2-10	3mm Green
203 x 228mm	3-60	2-16	3mm Yellow
467 x 305mm	9-10	4-10	3mm Clip

PANEL METERS		MIC INSERTS	
Until now panel meters have proved an expensive part of your project.		Xtal	45p
Now available this new quick fit type.		Condenser	60p
32mm Square Meter		Dynamic	75p

BARGAIN PACKS		MINI SPEAKERS	
12 Assd Panel Mtd Pots	£1-10	21"	64 ohm 70p
20 Assd Electrolytic Caps	£0-85	3"	8 ohm 75p
7 Assd Blob Boards	£1-10		
1 50pF Trimmer Cap	£0-20		
30 Assd Min Ceramic Caps	£0-70		
9 Assd 4000 Series CMOS	£1-10		
10 Assd 5 red/5 black croc clips	£0-80		
20 Plastic type BC109 trans	£0-75		
Push Buttons SPDT 15p each 10 for	£1-00		

LIGHTNING ELECTRONIC COMPONENTS
 Postage & Packing 50p per order (free over £10) Please add VAT at 15%.
 Telephone orders welcome by Access or Barclaycard
Showroom & Mail Order Distribution Centre at: —
18 Victoria Road, TAMWORTH, Staffs B79 7HR Tel. 0827-65767.

NEW GOODIES JUST ARRIVED!
 C12 K88A Darlington Power TO3 PNP 60V 12A 117V Hfe 750 @ 6A 75p
 C13 Nixie — Siemens ZM1336K, 14mm digit height, overall 25mm. Wire ended 50p
 C14 8Y212-750 power switching rect, 800V 4A, 4 for £1.50
 C15 GR05R 50V 5A switching rect. 4 for 50p
 C16 21PT5 50V 20A rect. 75p
 C17 KBL0A 4A 400V bridge 50p
 C18 BS1 1A 100V bridge 5 for £1

REGULATED PSU PANEL
 Exclusive Greenweld design, fully variable 0-28V @ 20mA-2A. Board contains all components except pots and transformer. Only £7.75. Suitable transformer and pots £6. Send SAE for fuller details.

SOLENOIDS AND RELAYS
 W821 Solenoid rated 48V at 25% duty cycle, but work well on 24V (700gm pull, 10mm travel) push or pull 27 x 18 x 15mm 55p
 W922 Mains 240V ac solenoid. 10% duty cycle, push or pull, 16mm travel. 50 x 20 x 16mm. Only £1.50
 W886 5V DC relay 500R SPCO 28 x 24 x 19 50p
 W733 11 pin plug in relay. 240V ac 3PCO 5A contacts £2.50. Base 36p
 W838 700R 24V 4PCO 'continental' relay 35 x 30 x 18. Only 84p. 10/£7.
 W847 37R 5 10V relay. SP 3A contact, PCB mntg 11 x 33 x 20 95p. 10/£7.50
 W893 Omron LY4 mains relay, 4PCO 5A contacts £2.50
 W896 24V ac coil, but works well on 6V DC. 2 10A c/o contacts. Ex-equip. only 60p

BRAND NEW VEROBLOC KIT!!!
 Just published by Babani, Mr R. A. Penfolds new book, "30 SOLDERLESS BREADBOARD PROJECT" — this book features 30 different projects for assembly on a Verobloc, and the kit contains all parts necessary to make:
 Audio Amplifiers
 Light & Dark Activated Switches & Alarms
 Timers
 Metronome
 Oscillators & Tone Generators
 Warbling Door Buzzer
 Two-tone Train Horn
 Touch Switch
 Reaction Game
 Sound Activated Switch
 Radio Receivers
 Fuzz Unit . . .
 4 lots more!

The introduction shows all the different components and explains how to use the breadboard. The Verobloc layout is shown for every project together with the circuit diagram and an explanation of how it works. Ideal for beginners in electronics, but also suitable for more advanced students.
 The complete kit is contained in an attractive plastic case, which can be divided up into 15 compartments in which your components may be stored.
 Complete Kit, including book, Verobloc & all parts £24.95
 Book only £2.25
 Kit without Verobloc £20.45.

5mm RED LED SCOOP
 Another company gone bust — to your advantage!!! We've bought all their 5mm red LED'S — GI type MV5754, and offer them as follows:
 25 £1.95; 100 £6.00; 250 £13.50; 1k £39.50; 5k £185.
 Add 30% for 2-part clip if required.
1,000 RESISTORS £2.50
 We've just purchased another 5 million preformed resistors, and can make a similar offer to that made two years ago, at the same price!!! K523 — 1,000 mixed 1/2 and 1/4W 5% carbon film resistors, preformed for PCB mntg. Enormous range of preferred values, 1,000 for £2.50; 5,000 £10; 20k £36.

FILAMENT DISPLAYS
 Z653 7 seg display 12.5mm high. Ideal for TTL operation, taking 5V 8mA per seg. Std 14 DIL package. Only £1 each, 4 for £3.00. Data supplied.

ELECTRO-DIAL

NOW DOWN IN PRICE!!

COMPUTER BATTLESHIPS
 Probably one of the most popular electronic games on the market. Unfortunately the design makes it impractical to test the PCB as a working model, although it may well function perfectly. Instead we have tested the sound chip, and sell the board for its component value only (PCB may be chipped or cracked). SN76477 sound IC; TMS1000 u-processor; batt clips, R's, C's etc. Size 160 x 140mm. Only £1.50. Instruction book and circuit 30p extra.

ALL PRICES INCLUDE VAT — JUST ADD 50p P&P
GREENWELD
 443F Millbrook Road, Southampton SO1 0HX

Big Ear



A high gain, directional microphone, ideal for nature studies.

THIS is one project where the mechanical work is greater than the electronic! The Big Ear consists of an omnidirectional microphone insert mounted in a length of common, garden variety 2½" PVC pipe, and a simple two-stage amplifier circuit. It was originally designed for recording or listening to the sounds of wildlife; however, the prototype has also proved useful as a stethoscope, and for listening in to distant conversations (be warned — the listener may not always like what he hears!)

The length of pipe serves two purposes; first, it acts as a resonant cavity with many resonant frequencies extending from a few hundred Hertz right up to the top of the audio band. Any pipe or tube has a fundamental resonant frequency which is a function of its length, and it is also resonant at overtones (harmonics) of the fundamental frequency. In general, the fundamental frequency, f , of a pipe which is closed at one end is approximately equal to $c/4l$, where l is the length of the pipe and c is the velocity of sound (330 metres per second, for most purposes). Thus the fundamental frequency of a pipe 0.25m long will be at 330 Hz; the overtones produced by a closed pipe occur only at odd harmonics, therefore resonant peaks will also occur at 990 Hz (3f), 1650 Hz (5f), 2310 Hz (7f) and so on. The effect of these resonances is to accentuate any sound at those frequencies, increasing the gain of the system at specific points in the audio spectrum. The length of the

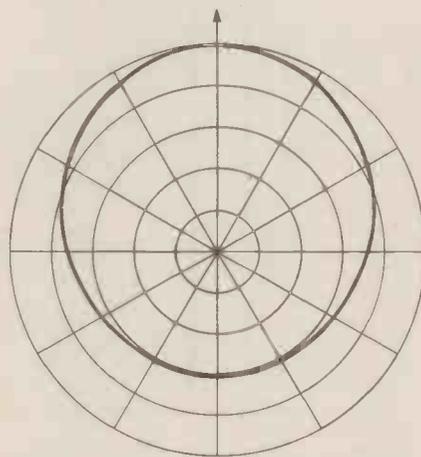


Figure 1. The directional response of the Big Ear.

pipe specified for this project has been arrived at after considerable experiment, and provides good results with minimum undesirable side-effects.

Second, the pipe provides a useful measure of directivity, due to diffraction effects. Diffraction is simply the change in direction of sound when it passes around an obstacle. The degree of bending depends on the ratio of the wavelength of the sound to the size of the obstacle and is greatest when the size of the object approaches the wavelength of the sound. In general, long wavelengths (bass frequencies) bend more easily because few everyday obstacles are more than about one metre long (the wavelength of a 100 Hz note, for example, is about 3.3m). The higher frequencies

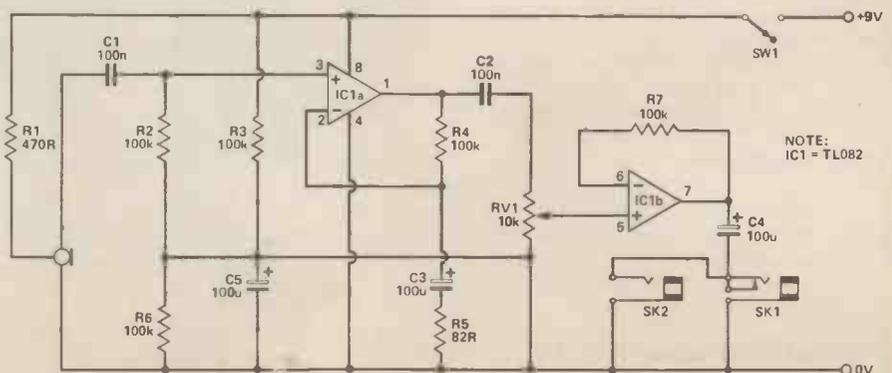


Figure 2. The internal circuitry of the Big Ear.

Parts List

RESISTORS

(All 1/4 watt 5% carbon)

R1 470R
 R2,3,4,6,7 100K
 R5 82R

POTENTIOMETERS

RV1 10K
 log carbon

CAPACITORS

C1,2 100n
 C352 * polyester
 C3,4,5 100u
 16V electrolytic
 *Replaces C280 Series

SEMICONDUCTORS

IC1 TL082
 dual op-amp

MISCELLANEOUS

SK1 3/4" stereo socket
 SK2 1/4" mono socket
 Small ABS case, approx. 80 x 60
 x 40 mm; omnidirectional electret
 microphone insert; 0.1" Veroboard,
 50 x 38 mm (20 holes x 15 strips);
 slide switch; PP3 battery clip; PVC
 pipe, 254 x 63 mm (10" x 2 1/2");
 wire, solder etc.

BUYLINES page 34


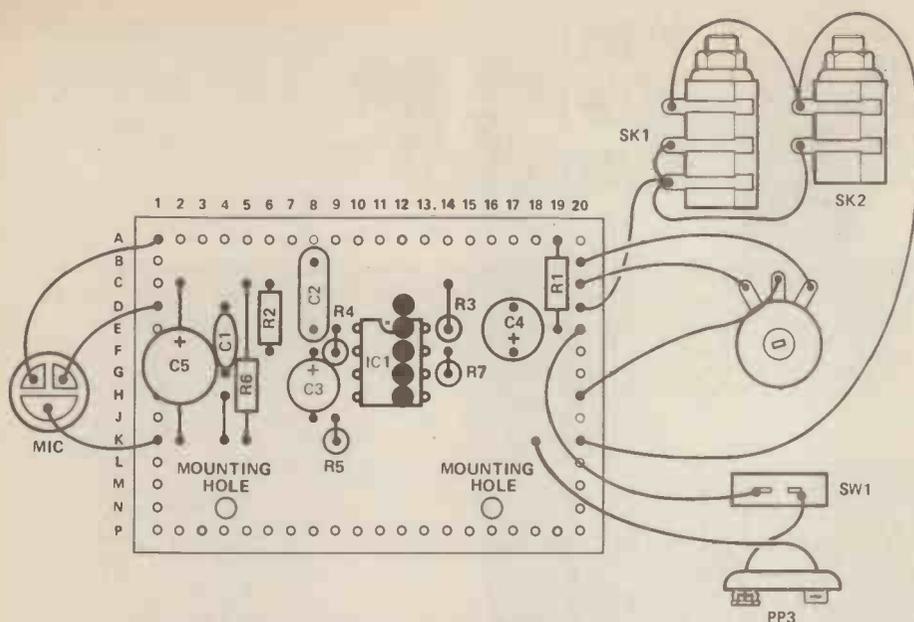


Figure 3. The project is simple enough to build on Veroboard. The diagram shows the component layout and the track cuts viewed from the top.

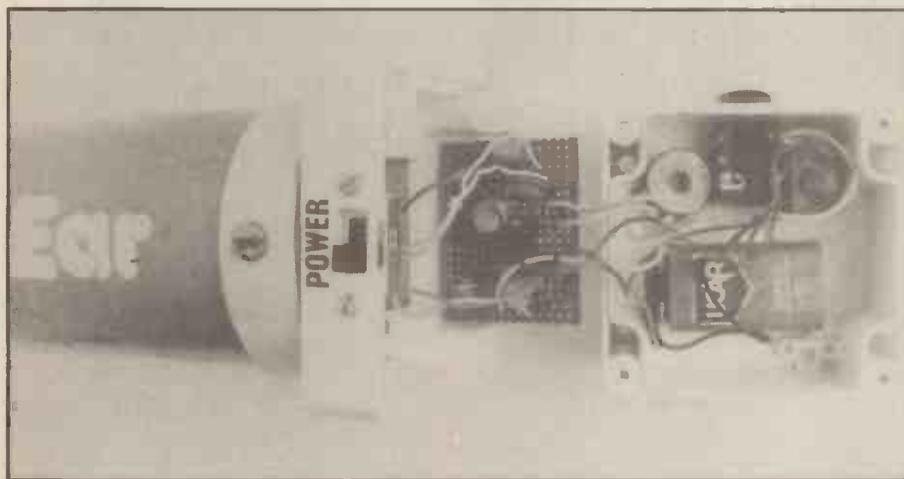

bend less easily and therefore are more directional, since they are reflected by common-sized obstacles rather than bending around them.

In the Big Ear, the pipe tends to 'hear' only those mid-range and high frequency sounds coming from directly in front, whereas sounds from the sides or rear will be rejected because they cannot bend around the edges of the opening. At low frequencies, however, the tube has no effect and so the response of the system reverts to that of the microphone insert, ie omnidirectional. To prevent these frequencies from being transmitted through to the output, the response of the amplifier is rolled off at the bass end. Overall, this combination of techniques gives a back-to-front ratio of 2:1 (see Figure 1).

The Big Ear is designed to be handheld, and for this purpose, a standard 2 1/2" pipe clip serves quite well as a handle in normal use; it will also do as a tripod mount, should that be required.

The amplifier section has two outputs: a headphone socket for monitoring purposes and a 1/4 jack

socket for connection to the line input of a tape recorder.

The Circuit.

The circuit (Figure 2) consists of two op-amps contained in a single TL082 IC package. The circuit can be split into two sections: a voltage amplifier and an output buffer.

Starting at the input (where else?), notice that the microphone has three connections to it. This is because it is an electret insert which contains a FET preamplifier to provide a low impedance drive from the high impedance microphone source. Thus, it must be connected to the supply rail via R1.

The input from the mic is fed to the non-inverting (-ve) input of IC1a. The value of the coupling capacitor, C1, is chosen to filter out the very low frequencies generated by handling the unit. Otherwise, these would create low rumbling sounds which would seriously interfere with the performance, especially at high gain settings! The voltage gain of this stage, set by the ratio of the values of R4 and R5, is x1000.

The Big Ear was intended to be

portable, and therefore a dual supply system, positive and negative rails, was not suitable because of the extra battery requirements. Instead, a half-supply voltage reference is created by the resistive divider network R3 and R6. The junction of the two resistors is bypassed to OV by C3 to remove any noise from the signal.

The full gain of the first stage is not always required (the results could be ear-splitting), so the output from IC1a is coupled to the buffer stage, IC1b, via a volume control, RV1; coupling capacitor C2 is chosen to roll-off the bass response. IC1b is set-up as a unity gain amplifier; its output is at a low impedance and is sufficient to drive an ordinary set of headphones or the input circuit of a tape recorder, via socket SK1. Blocking capacitor C4 is included to prevent the DC level at the output of IC1b from reaching the load.

Construction

As the circuit is so simple, it was decided to build it on Veroboard; the usual precautions concerning layout, track cuts and solder bridges apply! Pay particular attention to the correct orientation of the electrolytic capacitors and the IC.

When the board is assembled, attach flying leads about 9" long to each of the off-board connection points. Next comes the mechanical assembly.

Mark out and drill the mounting holes as shown in Figure 4. These are easily made — but the slot for the slide-switch will cause greater problems! Carefully drill 1/4" holes at each

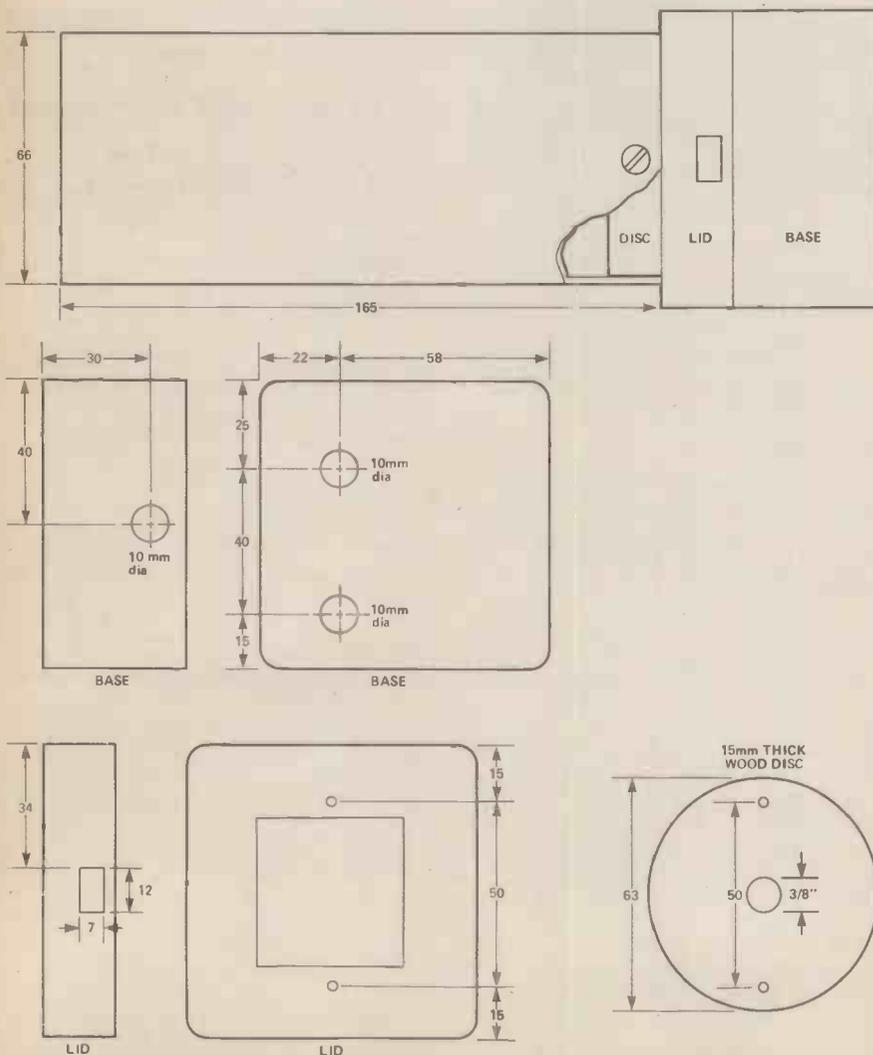
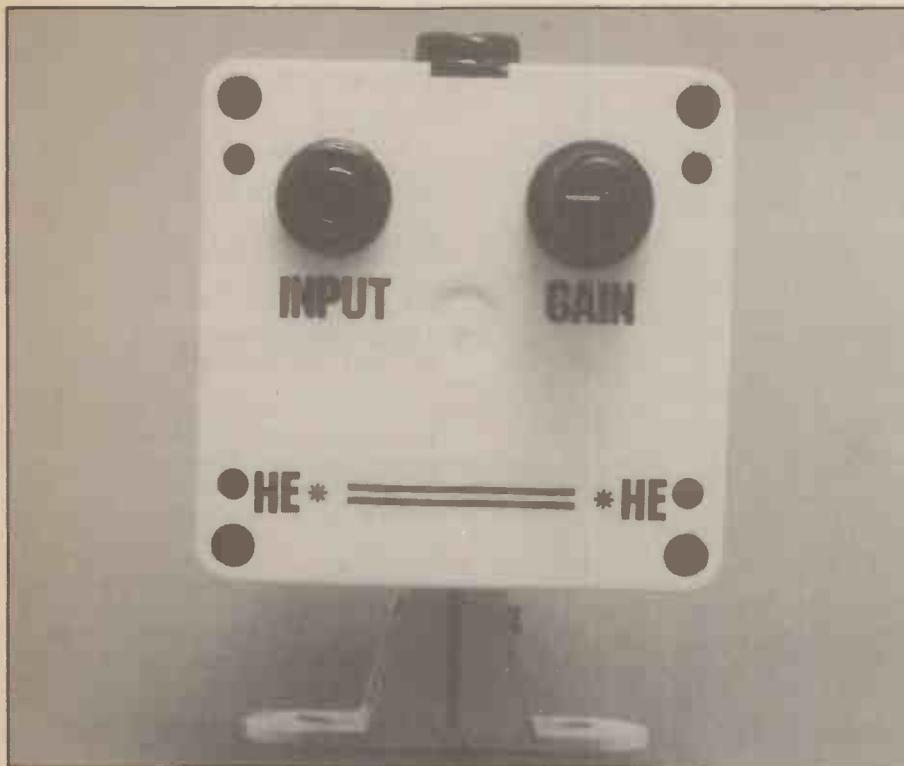


Figure 4. The mechanical details.

end of the slot, then file it to shape. A small flat file will be useful for finishing the task. Although the box cut-out for the microphone is shown as a square, this can be drilled out to 3/8" clearance, the size of the microphone insert.

Lastly, the wooden disc which holds the mic insert, and to which the length of 2 1/2" pipe attaches, must be cut out; the dimensions are shown in Figure 4. Preferably, the disc should be cut from a solid piece of wood; the pipe is held by screws into the sides of the disc, and chipboard has a tendency to fall apart if used in this fashion.

After the parts have been made, the Big Ear can be assembled. Mount the sockets, potentiometer and Veroboard; the mic insert should be a tight fit in the 3/8" hole through the centre of the wooden disc; glue it if you must, but the arrangement then becomes somewhat permanent! The disc itself is attached to the box by two small self-tapping screws, and the pipe can then be screwed onto the disc with three or four self-tappers. Finally, the flying leads should be connected as shown in Figure 3; the battery should be fixed to the base of the box with a piece of double-sided tape or Blu Tack, to prevent it rattling around inside.

At this point, the Big Ear is ready to use. Switch on and try it. There will be silence for a couple of seconds, then it should burst into life.

Why Not Experiment?

Although the final form of the Big Ear was arrived at after a considerable period of trial-and-error experiment, there are several other methods which could be used to improve the directional response.

The most effective would be to replace the omnidirectional mic insert with a directional type; however, these do not seem to be readily available and can probably only be had by dismantling a cheap directional electret mic of the type usually sold with cassette recorders.

The next most important factor determining the directivity is the aperture of the pipe; decreasing the diameter will increase the directional response to high frequencies, at the expense of less directivity at lower frequencies. Another trick is to form many small resonant cavities, rather than one large one, by filling the pipe with ordinary plastic drinking straws; the overall response can be 'tuned' by cutting the straws to different lengths. The directional response can also be improved by isolating the mic insert from the case and pipe, as some of the sound from the sides and rear will otherwise be conducted through the solid material to the microphone.

Finally, there are alternatives to the resonant tube system; one method worth trying is to use a parabolic or dish reflector; a simple plastic bowl would be adequate!



Bigger and Better for 1982
the colourful Wilmslow Audio brochure
- the definitive loudspeaker catalogue!

Everything for the speaker constructor - kits, drive units, components for HiFi and PA.

50 DIY HiFi speaker designs including the exciting new dB Total Concept speaker kits, the Kef Constructor range, Wharfedale Speakercraft, etc.

Flatpack cabinet kits for Kef, Wharfedale and many others.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our ★
two listening lounges
(Customer operated demonstration facilities)
- ★ Ample parking ★

Send £1.50 for catalogue
(cheque, M.O. or stamps - or phone with your credit card number)

- ★ Access - Visa - American Express accepted ★
- also HiFi Markets Budget Card.



☎
0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



TECHNICAL TRAINING IN ELECTRONICS, TELEVISION AND AUDIO

IN YOUR OWN HOME - AT YOUR PACE

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained man. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City & Guilds Certificates

**Radio Amateurs
Basic Electronic Engineering (Joint C&G/ICS)**

Certificate Courses

**TV and Audio Servicing
Radio & Amplifier Construction
Electronic Engineering* and Maintenance
Computer Engineering* and Programming
Microprocessor Engineering*
TV, Radio and Audio Engineering
Electrical Engineering,* Installation
and Contracting** *Quality for IET Associate Membership



Approved by CACC



Member of ABCC

POST OR PHONE TODAY FOR FREE BOOKLET

Please send me your FREE School of Electronics Prospectus.

Subject of Interest _____

Name _____

Address _____



Post to: Dept B262
ICS School of Electronics
160 Stewarts Road,
London SW8 4UJ



01-622 9911
(All Hours)

DIANETICS

THE MODERN SCIENCE
OF MENTAL HEALTH



A HANDBOOK OF
DIANETIC PROCEDURE
L. RON HUBBARD

**5 MILLION
BESTSELLER**

How to keep your self-respect...

Dianetics: the bright new science of the mind you can use. Understand how to think clearly and learn the techniques to really help people. **Dianetics** gives you the confidence of real solutions, not just interesting information.

“In Dianetics awareness is increased - without the use of drugs, hypnosis or any physical method- to the point at which the person can become aware of the source of his problems.”

Encyclopaedia of Alternative Medicine and Self-Help

£2.95 from leading bookshops or for further information from Dianetics, St. Mary's College, Rottingdean, Brighton BN2 7FS FREEPOST 36 pp.

DESOLDERING TOOL Make life easy with this superb anodised high suction desoldering tool. Essential for desoldering multi hypen lead e.g. transistors IC's. Especially handy for the experimenter and service engineer. Eliminating damage to PCB's and components. £4.45 + VAT Spare teflon nose 85p + VAT.

JAPANESE TRANSISTORS Equivalents available for most types. Please call, phone or write.

LOW COST VERSATILE MULTIMETER.

THE MIGHTY MINI MULTI-TESTER. Ideal for beginner and service engineer (fits into shirt pocket) DC and AC voltage ranges: 10V, 50V, 250V, 1000V. DC current range 100mA. Resistance: two ranges 0-1M OHMS (60 OHMS CENTRE SCALE). DECIBELS -10 to 22 DB mirror arc scale. Overload protection, complete with battery leads and instructions. £5.65 + VAT. ORDER FORM (ORDERS ON PLAIN PAPER ACCEPTED)

Name _____

Address _____

.....Desoldering tools at £4.45 = £ _____

.....Spare Teflon noses at 85p = £ _____

.....Mighty Mini Testers at £5.65 = £ _____

Postage, packing and insurance at 60p per one device, 25p for each additional device *E _____

Sub total _____

Add 15% VAT _____

I enclose cheque no/P.O. no _____

Alternatively please credit my VISA/ACCESS/AMERICAN EXPRESS No. _____

Signature _____

This offer applies to UK only. Please allow 7-10 days delivery. Overseas customers please do not add VAT but allow to cover postage. TRADE ENQUIRIES WELCOME.

CRICKLEWOOD ELECTRONICS LTD.

40 Cricklewood Broadway, London NW2 3ET. Tel: 01-452 0161

Electronic kits for the thrifty!

Build 50 Interesting Projects on a PC Chassis with surplus components from your 'Spare Box'.

EXPERIMENTERS'S PRINTED CIRCUIT KIT

Contents: 4 assorted boards to suit the enclosed designs. Etching Powder, Resist Paint, Solvent, Degreaser and Etching Instructions, also 50 Circuit diagrams, Chassis Plans and Layouts for simple Crystal Sets, Transistor Radios, Transmitters, Amplifiers, Intercoms, Radio Control, Metal Detector, Photoelectric and Ultrasonic Alarms, 'Perpetual Motion', Light Beam Telephone Instruments, Testers, Gadgets, etc. You can build at negligible cost with 'Surplus' or reclaimed parts and transistors you already have.

Price: £2.50. Postage and Packing 50p

PHOTOELECTRIC KIT

A kit of basic parts to build a simple Infra-Red Sensitive Photoelectric Switch. Contents: Phototransistor, Transistors, Diode, Resistors, Connector, Latching Relay, Chassis Board, Case, Screws and Instructions.

Price: £4.50. Postage and Packing 50p

OPTICAL KIT

A kit of parts to build an IR folden-beam Projector and Receiver to suit the above kit. Contents: 2 Lenses, 2 Mirrors, 2 45° blocks, Infra-Red Filter, Lampholder, Building Plans.

Price: £3.70. Postage and Packing 30p

Both kits together make an excellent Invisible-Beam Burglar Alarm

EXPERIMENTAL ELECTRONICS

335 Battersea Park Road, London SW11 4SL

Tel: 01-720 2683

Send SAE for full details of all kits and circuits

Send for my CATALOGUE ONLY 75p

(plus 25p post/packing)

My VAT and post/packing inclusive prices are *the* lowest. All below normal trade price — some at only one tenth of manufacturers quantity trade.

See my prices on the following:

CAPACITORS . . . ELECTROLYTIC; CAN, WIRE END, TANTALUM, MULTIPLE, COMPUTER GRADE, NON POLAR, PAPER BLOCK, CAN, POLY, MICA, CERAMIC. LOW AND HIGH VOLTAGE, RESISTORS. 1/8th WATT TO 100 WATT; 0.1% TO 10% CARBON, METAL AND WIRE WOUND + NETWORKS. FANS, BATTERIES, SOLENOIDS, TAPE SPOOLS, VARIABLE CAPACITORS AND RESISTORS, TRIMMERS, PRESETS, POTS . . . SINGLE, DUAL, SWITCHED, CARBON, CERMET AND WIREWOUND, SINGLE OR MULTITURN, ROTDRY AND SLIDE. DIODES, RECTIFIERS, BRIDGES, CHARGERS, STYLII, SOCKETS, PLUGS, RELAYS, TRANSISTORS, IC'S, CLIPS, CRYSTALS, ZENERS, TRIACS, THYRISTORS, BOXES, PANELS, DISPLAYS, LED'S, COUPLERS, ISOLATORS, NEONS, OPTO'S, LEADS, CONNECTORS, VALVES, BOOKS, MAGAZINES, TERMINALS, CHOKES, TRANSFORMERS, TIMERS, SWITCHES, COUNTERS, LAMPS, INDICATORS, BELLS, SIRENS, HOLDERS, POWER SUPPLIES, HARDWARE, MODULES, FUSES, CARRIERS, CIRCUIT BREAKERS, KNOBS, THERMISTORS, VDR'S, INSULATORS, CASSETTES, METERS, SOLDER, HANDLES, LOCKS, INDUCTORS, WIRE, UNITS, MOTORS, COILS, CORES, CARTRIDGES, SPEAKERS, EARPHONES, SUPPRESSORS, MIKES, HEATSINKS, TAPE, BOARDS and others.

Prices you would not believe before inflation!

BRIAN J. REED

TRADE COMPONENTS

ESTABLISHED 25 YEARS

161 St. Johns Hill, Battersea, London SW11 1TQ

Open 11 am till 7 pm Tues. to Sat. Telephone: 01-223 6016

LB ELECTRONICS

Brand New 4½" square mains fans, 115 volts AC £4.50 p/p 75p.

Brand new 3½" square mains fans, 220 volts AC £9.50 p/p 75p.

DC Power leads complete with power plug 3.5mm to fit your calculators, micros etc £1 for 10 p/p 25p.

REJECT RED FLASHING LED (some flash, some don't, some stay on permanently). Pack of 25 £1, 10 packs for £9 p/p free.

PCB Amplifier containing LM380 (or equivalent) 9 volt rail ½ watt output, brand new £1 each p/p 35p.

PCB TA 6½" x 9" Approx Alpha numeric touch keyboard, ASC11, with Data £7.95 p/p 65p.

EPROMS 1702A £5.00p. 2708 £2.50p. 2516 (450NS), 5 Volts used once, erased and guaranteed by us £1.95p. 10 for £17.00p. 2732 £5.00, 2532 £6.00p.

RAM 2114L £1.25p (450NS), 4116 (200NS) £1.00p, 2114 (200NS) £1.35p p/p 35p.

CPU 8080 £2.50p, 6502 £4.50p, Z80A (4 MHZ) £4.50p, Z8671 (Basic/Debug) £21.00p.

LB ELECTRONICS

11 Hercies Road

Hillingdon

Middlesex

Tel. 0895 55399



TYPE 161B

DUAL POWER SUPPLY KIT

INCORPORATES A POSITIVE & A NEGATIVE REGULATED SUPPLY

BOTH ARE ISOLATED & ADJUSTABLE 1.3V TO 16V D.C.

Interconnect to give 2.6V to 32V or

-1.3V/0/+1.3V to -16V/0/+16V

Output current 1A at 16V to 0.35A at 1.3V

Ripple is less than 1mV

£25.99

inc. P & P and VAT

Built & Tested

£37.95 inc. P&P and VAT



Comprehensive design details with calculations are included so that the kit is an exercise in power supply design. The kit, which uses quality components, is complete with instructions. Case punched and stove enamelled in attractive blue and grey with a printed front panel to give a professional finish. Excellent for the beginner, the experienced amateur and as a tutorial for schools and colleges.

SEND CHEQUE OR P.O.

ALLOW 21 DAYS FOR DELIVERY

BRANIME MARKETING LTD DEPT. E
BALTHANE IND. EST., BALLASALLA, ISLE OF MAN

Branime

TEACHING KIT
BUILD YOUR KNOWLEDGE

LITESOLD ARE OFFERING A COMPLETE SOLDERING KIT FOR ONLY

£13.95
inc. VAT & P.P.



Contains all you need to solder/de-solder any electronics project:

LITESOLD LC18H 240v high performance iron, made to professional standards in our own works, fitted with 3.2mm bit. 2 alternative bits, 1.6 and 2.4mm. Reel of 3 metres 18 swg flux-cored solder. Stainless steel tweezer. 3 soldering aids. Reel of 1.5 metres de-soldering braid. Packed in clear PVC presentation/storage wallet. Superb present — ideal for beginner or expert.

SPECIAL PRICE — £13.95 inc. VAT & P.P.

(normal resale value £17.49 inc.) IRON only — £5.66 inc. (normally £6.92). Spares, accessories and after-sales service available from us.




16-page colour catalogue — 60p. Send cheque/P.O. to LITESOLD or ring for Access/Barclaycard sales.



LITESOLD


LIGHT SOLDERING DEVELOPMENTS LTD.

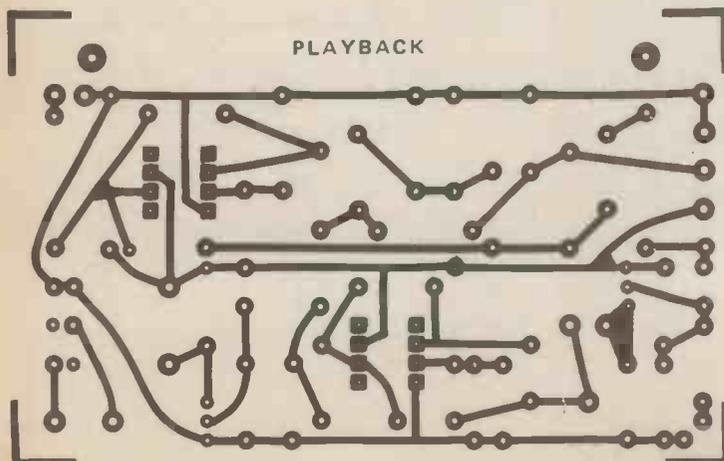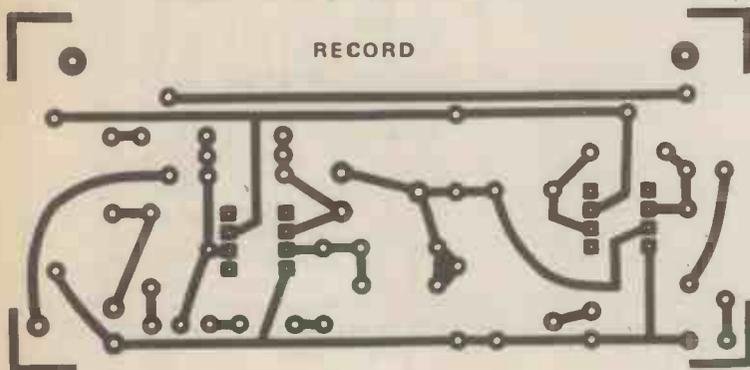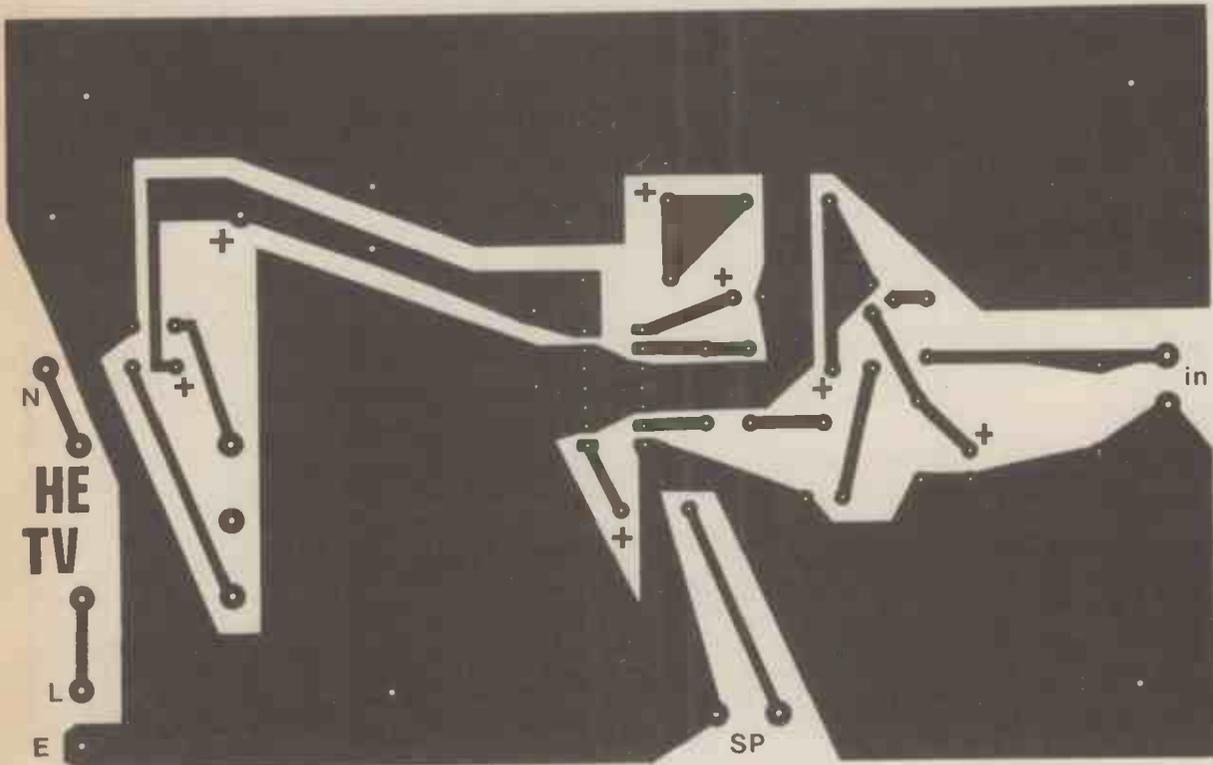Spencer Place, 97/99 Gloucester Road, Croydon CR0 2DN, Surrey. Tel: 01-689 0574.




Left: Both PCB patterns for the Tape/Slide Synchroniser; top, the Recording board; bottom, the Playback board.

PCBs

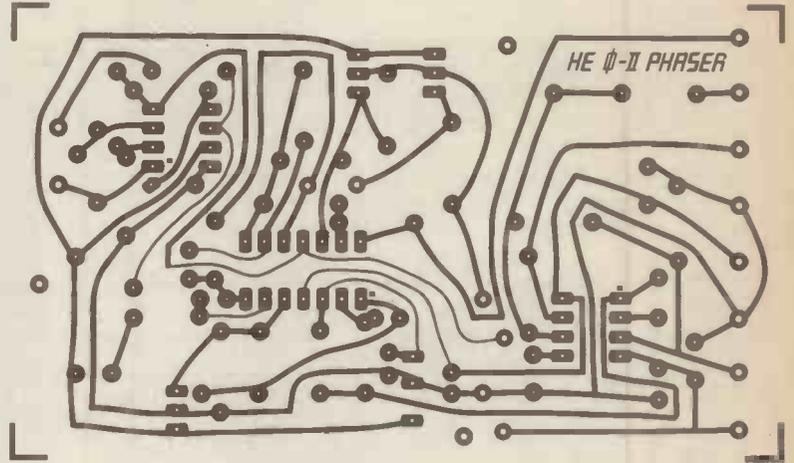


Right: The HE Phase Four PCB

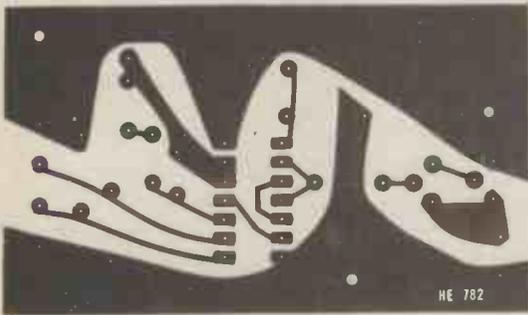

The Stereo Noise Gate PCB pattern (right). Note that there are only two mounting holes.

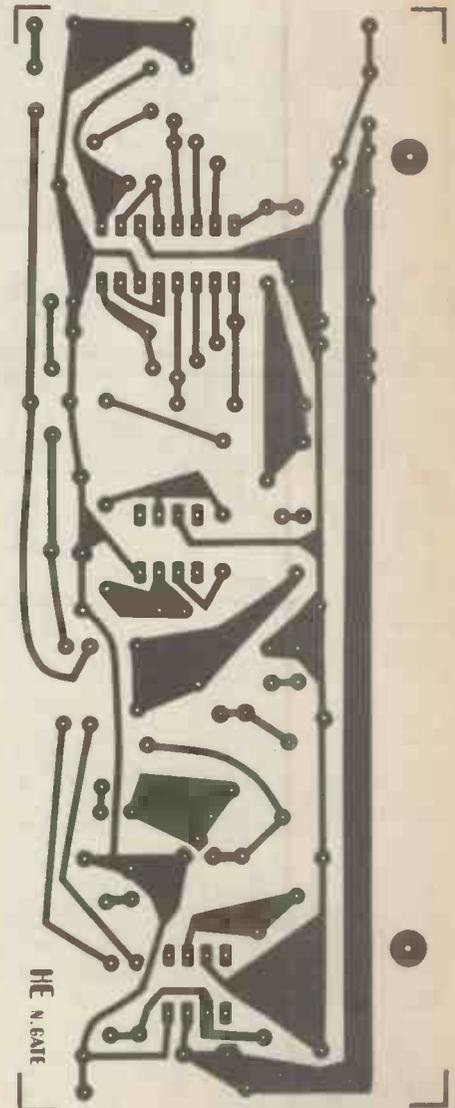Left: The PCB foil pattern for the Low Cost Alarm. The three large holes are for mounting bolts.



HE Microlog PCB

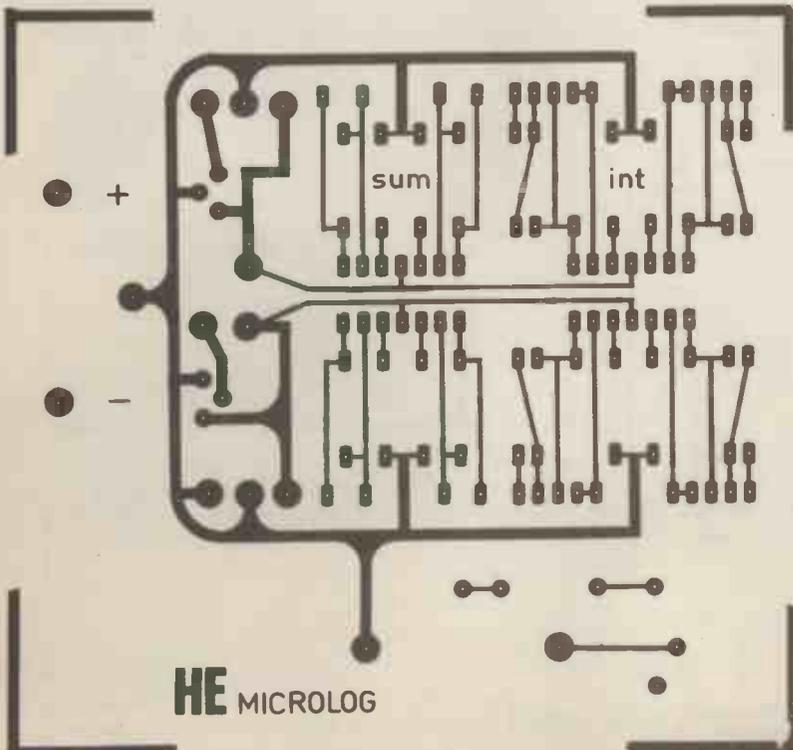


Photo Etch Services

8 Tufnell Gdns.,
Mackworth,
Derby DE3 4DY

MAKE YOUR OWN CIRCUIT BOARDS

**SAVE
£10**



**SPECIAL OFFER
£60 incl. p. & p.**

Offer for limited period only

- Reproduces direct from magazine circuits, etc.
 - Complete kit including film, exposing lamp, D/S fibreglass boards, printing/assembly frame, etc.
 - No darkroom or photographic experience needed
 - Full after sales service and consultancy
- Send loose stamp for free brochure

CNC 10 PCB HOLDER

Ideal for small scale production, testing, research, service engineers, education and the home constructor.
The CNC 10 has a board capacity of 8" x 8" and longer boards (maximum 8" wide) may be accommodated since they can project beyond the ends of the rails.
Adjustment of the board rails is extremely simple and they are locked in the desired position by one central locking clamp. A further clamp enables the PCB, when in position, to be rotated through 360 degrees and locked in the required position.
An optional foam pad is available which enables a number of components to be inserted prior to soldering. Pad size 8" x 8".



CNC 10: £16.10 INC. VAT

FOAM PAD & CLIP:

£5.64 INC. VAT

Please add £1.50 to cover postage.

Available direct from the manufacturer:

CARLTON NICHOL & CO. LTD.,
GOLDKEY INDUSTRIAL ESTATE,
KELVEDON, COLCHESTER, ESSEX

XMAS ELECTRONICS SALE

(Deduct 15% discount on orders of £15 and over)

MODERN DYNAMIC MOVING COIL MICROPHONES 200 ohms impedance. With switch fitted with lead and DIN plug. Used but in nice condition. Only £2 each p.p. 50p. MICROPHONE HEADPHONE EXTENSION LEADS Curly 4 core unscreened leads. High quality. Over 1 metre in length. 35p each p.p. 15p. 4 for £1.25 post free. AIRLITE HEADSETS with Boom Mike. Cost over £40 per pair. Our price £4.50 per pair p.p. £1. 2 pairs for £9 post free. Less boom mike £4 per pair p.p. £1. 2 pairs £9 post free. AMPLIVOX HEADSETS WITH BOOM MIKE £4.50 per pair postage £1. 2 pairs for £9 post free. Less boom mike £4 per pair, p.p. £1. 2 pairs for £8 post free. Impedance of above headphones 600 ohms. All headphones fitted with ex-Ministry plus. Standard new jack plugs available at 25p each. 2 for 40p. Headphone extension sockets only 25p each. 2 for 40p. GENUINE AFV TANK HEADSETS and MIKE £3.50, p.p. £1. 2 pairs for £7 post free. HAVE YOU SEEN THE GREEN CAT? 1000s of new components, radio, electronic, audio at unbelievably low prices. Send 50p and receive catalogue and FREE RECORD SPEED INDICATOR. Try a JUMBO PACK. Contains transistors, resistors, caps, pots, switches, radio and electronic items. Over £50 worth for £11. carriage £2.50. MINI JUMBO PACK (£20 worth) £5, p.p. £1.50. BRIDGE RECTIFIERS (Phillips) 400 PIV at 4 amps. Well made. Should be over £2 each. Our price 90p, p.p. 20p. SEMICONDUCTOR SALE ITT BC183 transistors. 10 for 30p or 4p each. ITT IN4002 diodes 3p each. 10 for 25p. OPTRON TYPE OP160 INFRA RED DIODES High output power. Matched to the OP500 and OP500SL series photo transistors. Our price 40p, 3 for £1. RIDICULOUS RESISTOR SALE. 1 watt carbon film resistors. 5% tolerance. High quality resistors made under exacting conditions by automatic machines. E12 range 10 to 10MΩ. In lots of 1000 (£5 per value). Only £8 per 1000. Lots of 5000 for £35. GENUINE EX GOVT COLLAPSIBLE AERIALS. A fully adjustable highly efficient whip aerial in 5 sections. Length open 1 1/2 metres. Closed 300mm. Copper plated sections. As used on Ex. Govt Manpacks. Brand new in makers boxes. £2.50 each, p.p. 75p. 2 for £5 post free. Please add 15% VAT to all orders including post packing and carriage.

MYERS ELECTRONICS

(HE), 12/14 Harper Street, Leeds LS2 7EA. Leeds 452045

New retail premises at above address (opposite Corals). Callers welcome 9 to 5 Mon. to Sat. (Lunch 12.15 to 3.15pm). Sunday open 10 to 3pm.

ELECTRONICS EMPORIUM

Easily reached from Leeds, Manchester, Yorks and Lancs

Open 8.30 to 5.30; Saturday 9 to 1

Vast range of bargains in stock includes Diodes, Heat Sinks, Thyristors, Bridge Rectifiers, Resistors, Capacitors, Terminals, Connectors, Relays, Switches, Wire and Cable, PCBs, Transformers, Measuring Instruments, Nibbler and other Hand Tools. Also ex-M.O.D. Surplus Test and other Equipment.

Some items by mail order — lists available.

A.C. TOWNLEY LIMITED

Harehill, Todmorden, Lancs OL14 5JY

MASTER ELECTRONICS NOW!
The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

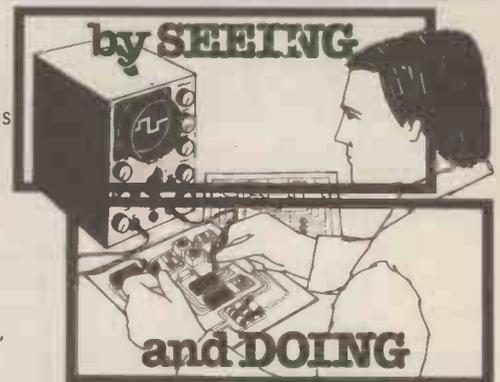

New Job? New Career? New Hobby? Get into Electronics Now!

FREE!
COLOUR BROCHURE

Please send your brochure without any obligation to

I am interested in:

HE/12/821

NAME _____

COURSE IN ELECTRONICS

as described above

ADDRESS _____

RADIO AMATEUR LICENCE

OTHER SUBJECTS _____

MICROPROCESSORS

LOGIC COURSE

POST NOW TO:

BLOCK CAPS PLEASE

British National Radio & Electronics School Reading, Berks. RG1 7BR



ADVERTISEMENT RATES

Semi-Display (min 2 cms)

1-3 insertions **£7.50** per cm

4-11 insertions **£7.00** per cm

12+ insertions **£6.50** per cm

Lineage 26p per word (min 15 words)

Box Nos. **£2.50**

Closing date **2nd Friday** of the month
preceding publication date.

All advertisements in this section must be prepaid. Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)

Send your requirements and cheque P.O. to:

HOBBY ELECTRONICS CLASSIFIED
ADVERTISING, 145, CHARING CROSS RD,
LONDON WC2H 0EE.



CLASSIFIED

THE PATH TO
SUCCESSFUL SALES!

01-437 1002

Ext 213

AERIAL AMPLIFIERS Improve weak television reception. Price £6.70. S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire BL0 9AGH.

ELECTRONICS component shop in MAIDSTONE, KENT! Thyronics Control Systems, 8 Sandling Road, Maidstone, Kent. Maidstone 675354.

BIG BARGAIN BOX

Our Big Bargain Box contains over a thousand components — resistors, capacitors, pots, switches, diodes, transistors, panels, bits and pieces, odds and ends. All useful stuff — would cost many times the price we are asking if bought separately. Approx. weight 4lbs.

ONLY £5.00 inc post — you're bound to come back for another!!

ESP 147F FOUNDRY LANE, SOUTHAMPTON, SO1 3LS

Lots of surplus bargains on our latest list — send an SAE for your copy now.

7LBS ASSORTED Components £5. 10lbs £6.50. 300, small components, transistors, diodes £2.20. Forty assorted 74 series ICs on Panel(s) £2.20. P.C.B.'s s/sided copper 11" x 8" 90p. 16" x 11" £1.70. Fibre glass 11" x 8" £1.50. 16" x 8" £2.90. Post paid. List 25p refundable. J.W.B. Radio, 2, Barnfield Crescent, Sale, Cheshire M33 1NL.

DIGITAL WATCH REPLACEMENT parts. Batteries, displays, backlights etc. Also reports, publications, charts. S.A.E. for full list. Profords, Copnersdrive, Holmergreen, Bucks HP15 6SGE.

REMOTE telephone bell kit, switches on your siren, buzzer bell, lamp etc when the phone rings. Battery operated micropower circuit draws negligible current from phone line. Complete kit including case and PCB only £9.95. Dept HE5, Unitech (Midlands), Freeport, Sutton Coldfield, West Midlands B74 2BR. (Not British Telecom Approved).

WANTED Automatic reset timer preferably 9v supply, timer to run for 30 secs and then re-set itself. Cash by return post. Tel. 550-8902

20 SIMPLE Electronic projects for your ZX81 by Stephen Adams, £6.95 including p&p. Come and browse or send SAE for list. Watford Technical Books, 105 St Albans Road, Watford, Herts. Tel. 0923 23324.

SPECTRUM VENTURE. Exciting new game for the Spectrum. (7 games in 1). In colour, with sound & fantastic screen effects. 16K & 48K version supplied on one cassette for £6. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

TRANSISTORS GP PNP silicon type MPS6518 5p each. SAE to SM Enterprises, 28 Preston Gardens, Enfield, London.

KIA RETURN AN.AD No 3: . . . Free — 3 Ferranti ZTX107 Transistors!! . . . Post + SAE. 8. Cunliffe Road, Ilkley.

BUY BULK — SAVE MONEY

All goods new full spec devices, sent by return. Post £1 any qty. No VAT. SAE List

1N4148 £10/k. 1N4003 £16/k. 1N4007 £22/k. BC107 £8/100. BC108 £8/100. 7805 £27/100. 7905 £27/100. 74LS93 £18/100. 74LS112 £12/100. 74LS132 £22/100. TBA120C 15/100. 2114 £10/100. 8085A £27/10. 14DIL skt £5/100. 16DILskt £5/100. 5mm Red LED £32/k. £5/100. BC182L £4/100. 2N3904 £4/100. 555 £13/100. LM380 £40/100.

PC ELECTRONICS

2 Thornhill, Romsey Road, Whitparish, Salisbury, Wilts
SP5 2SD
MAIL ORDER ONLY

SOLAR CELLS 3" dia. 900mA at 0.45V £7.59. Price lists 75p. Edencombe Ltd., 34 Nathans Road, Wembley, Middx. HA0 3RX

PSUs 5V 1A £10.99. 5V 3A £11.99. 5V 5A £25.99. Adj 1.2-30V 100mA £14.99. 1.5A £24.99. 5A £32.99. Edwards Electrics, Unit 3, Mill Lane, Bridgwater, Somerset.

WANTED Electronic components, boards, connectors, test equipment, good prices paid. "Q" Services, 29 Lawford Crescent, Yateley 871048 Camberley Surrey.

ELECTRONIC kits for sale: Electronic Organ £7, Dice £8.10. SAE for details. Bee Micro, 33 Bevendean Crescent, Brighton, E. Sussex.

H.E. ORGAN KITS £99.50 inc. p&p. 61 note keyboards £32.00. 13 note pedal boards £25.00 inc. p&p. A.T. Hawkins, 23, Blenheim Road, St. Albans, Herts. AL1 4NS.

500W Dual Channel Flasher Unit in a mains plug.

Use for parties, Xmas lights, discos, low budget pop groups.

Variable speeds, fused, no interference

£7.95 cheques/POs to

AMK

11 Queensway, Sunbury-on-Thames,
Middlesex TW16 6HA

MAIL ORDER ONLY

SMALL reed switches 10p. Magnets 16p. Small DC solenoids 35p. Postage 25p. Grimsby Electronic Components, Lambert Road, Grimsby, S. Humberside. Hundreds bargains at shop. SAE list.

SPECIAL OFFERS

All Capacitors & Diodes are packed in 10s. Price per pack of 10

<p>DIODES</p> <p>1N3470 £0.22</p> <p>1N4001 .25</p> <p>1N4148 .15</p> <p>1N4383 .30</p> <p>1N5401 1.00</p> <p>V.REGULATORS</p> <p>78L05 £0.25 ea</p> <p>7924 .25 ea</p> <p>LM723 DIL .30 ea</p> <p>12V 1W Zeners .05 ea</p> <p>POLYSTYRENE CAPACITORS</p> <p>1000pF 150V £0.40</p> <p>CERAMIC DISC CAPACITORS</p> <p>4.7pF 50V £0.25</p> <p>10pF 50V .25</p> <p>120pF 50V .25</p> <p>1000pF 50V .20</p>	<p>2200pF 50V .20</p> <p>3000pF 50V .20</p> <p>4700pF 50V .25</p> <p>10n 50V .15</p> <p>47n 25V .35</p> <p>100n 50V .50</p> <p>ELECTROLYTIC CAPACITORS</p> <p>AXIAL</p> <p>2.2uF 63V £0.35</p> <p>4.7uF 35V .29</p> <p>10uF 25V .40</p> <p>33uF 100V .50</p> <p>47uF 10V (PI) .45</p> <p>47uF 16V (PI) .45</p> <p>100uF 10V (PI) .50</p> <p>100uF 16V .60</p> <p>160uF 25V .65</p> <p>220uF 10V .50</p> <p>220uF 16V .75</p>	<p>220uF 25V .90</p> <p>220uF 40V 1.20</p> <p>220uF 70V 1.40</p> <p>470uF 10V 1.00</p> <p>470uF 16V .85</p> <p>ELECTROLYTIC CAPACITORS</p> <p>RADIAL</p> <p>4.7uF 50V PC £0.25</p> <p>4.7uF 100V PC .40</p> <p>10uF 25V PC .35</p> <p>10uF 250V PC .30</p> <p>22uF 100V PC .90</p> <p>33uF 25V PC .30</p> <p>33uF 160V PC .70</p> <p>100uF 40V PC .40</p> <p>220uF 10V PC .45</p> <p>330uF 6.3V .40</p> <p>330uF 10V .60</p> <p>330uF 25V .60</p> <p>470uF 10V PC .85</p> <p>470uF 16V PC .99</p> <p>2200uF 6.3V 1.00</p> <p style="font-size: x-small;">PC = Short Leads for PCB</p>
--	---	---

All devices brand new & guaranteed. Orders despatched by return of post. Cash/Cheque/Postal Orders with order. Please add 60p p&p. MAIL ORDER ONLY PLEASE

A.M. ELECTRONICS

TRADE/RETAIL SUPPLY OF ELECTRONIC COMPONENTS & EQUIPMENT
5 Wilson Street, Leicester LE2 0BB

ADVERTISERS INDEX

Aitken Bros	61	ICS	83
Alcon Inst Ltd	77	ILP	54, 55
Ambit.....	2	LB Elec.....	84
A. M. Elec.....	90	Lightning Elec.....	79
Amtron UK Ltd	73	Litesold	84
Armon Elec	49	Magenta	42
Audio Elec	66	Marco Trading.....	77
BK Elec	91	Mercia Elec Ltd	78
Bib	4	Myers Elec	88
Bi-Pak	40, 41	New Era Publications	83
BNOS Elec	78	Photo Etc Systems.....	88
BNRS.....	88	Pimac.....	64
Bradley Marshall	50	Rapid	8
Bramine Mktg	84	Relay A Quip	77
Cambridge Learning	66	Brian J Reed	84
Carlton Nichol.....	88	Riscomp Ltd.....	17
Centemp	78	Roadrunner	61
Chordgate	78	Silica Shop	92
Cricklewood Elec.....	24, 83	Sinclair Research	68, 69
Electronize Design	32	Sparkrite.....	44
Electrovalue.....	60	Technomatic	36
Experimental	83	Tempus.....	28, 29
Flight Elec.....	30	Texas Inst	19
Greenbank	73	TK Elec	49
Greenweld	79	Thumall (Elec) Eng	64
Grenson Elec	34	Townley AC.....	88
Heath.....	50	Watford Elec	5
Hemmings	64	Wilmslow Audio.....	83

CENTURION ALARMS

We manufacture, you save £££'s
Send s.a.e. or phone for our Free list of
professional D.I.Y. Burglar Alarm Equip-
ment and accessories.
Discount up to 20% off list prices,
e.g. Control Equipment from £15.98.
Decoy Bell Boxes from £5.95 inc.

TRADE ENQUIRIES WELCOME

☎ 0484-21000

or 0484 35527 (24 hr. ans.)

CENTURION ALARMS (HE)
1265 Wakefield Road, Huddersfield
HD5 9BE, W. Yorkshire

Access & Visa
Orders Welcomed

HAVEN Hardware. Spectrum fruit machine £4.95. UK101/Superboard products still available. ZX kits: repeat key £3.95. Inverse video £3.45. SAE for built prices/beeper/keyboard/software details. 4 Asby Road, Asby, Workington, Cumbria.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

STEREOPower 120 WATT AMPLIFIERS!! (60 + 60W protected). Case + controls. D.I.N. sockets. Fibreglass. Boxed + Data. £10.85. A. Law, 8 Cunliffe Road (Over Incatile), Ilkley LS29 9DZ.

THERMOCOUPLES for flash point alarm project available ex-stock £1.00 each inc p&p. From Candis Electronics, Highdown Works, Highdown Avenue, Worthing, Sussex BN13 1PU. Tel. 0903 690750.

BURGLAR ALARM EQUIPMENT. Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. Ltd. 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274-308920.



HOBBY ELECTRONICS CLASSIFIED ADVERTISEMENT — ORDER FORM

If you have something to sell now's your chance! Don't turn the page — turn to us!
Rates of charge: 26p per word per issue (minimum of 15 words). Box Nos. £2.50
and post to **HOBBY ELECTRONICS, CLASSIFIED DEPT., 145 CHARING CROSS ROAD, LONDON WC2**

					£3.90
					£5.20
					£6.50
					£7.80
					£9.10
					£10.40
					£11.70
					£13.00

Please place my advert in **HOBBY ELECTRONICS** for issues commencing as soon as possible.

I am enclosing my Cheque/Postal Order/International Money Order for: (delete as necessary) £ (Made payable to A.S.P. Ltd)



OR Debit my Access/Barclaycard
(Delete as necessary)



Please use **BLOCK CAPITALS** and include post codes.

Name (Mr/Mrs/Miss/Ms)

Address

.....

.....

Signature..... Date.....

Daytime Tel. No.

--	--	--	--	--	--	--	--	--	--

All classified advertisements must be paid for in advance.



MULLARD SPEAKER KITS

A PURPOSELY DESIGNED 40 WATT R.M.S. 8 OHM SPEAKER SYSTEM RECENTLY DEVELOPED BY MULLARD'S SPECIALIST TEAM IN BELGIUM. Kit comprises a Mullard 8" Woofer with foam surround and aluminium voice coil, Mullard 3" high power dome tweeter. B.K.E. built and tested crossover, based on Mullard circuit combining low loss components, glass fibre board and recessed size 240 x 216 x 445 mm. A superb sound at a relatively low cost. Complete with instructions. Price £14.90 + £1.50 p&p per kit.


New 5" 30 watt mini version of above now available. Recommended cabinet size 180 x 155 x 295mm

Price £13.90 + £1.00 p&p per kit.

STEREO CASSETTE TAPE DECK MODULE. Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2" x 11 1/4". Clearance required under top panel 2 1/2". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

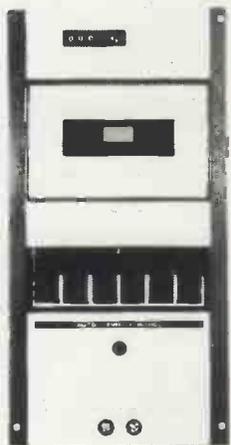Price £26.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.



6 piano type keys

NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8"). These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. **Specification and Price:**


15" 100 watt R.M.S. Impedance 8ohm 59 oz. magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. Price £32 each £3.00 Packing and Carriage each.

12" 100 watt R.M.S. Impedance 8 ohm, 50 oz magnet, 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. Price £23.70 each. £3.00 Packing and Carriage each.

8" 50 watt R.M.S. Impedance 8 ohms, 20 oz. 1 1/2" aluminium voice coil, Resonant Frequency 40Hz, Frequency Response to 6KHz. Sensitivity 92dB. Also available with black cone fitted with black metal protective grill. Price: White cone £8.90 each. Black cone/grill £9.50 each. P & P £1.25 each.

PIEZO ELECTRIC TWEETERS - MOTOROLA

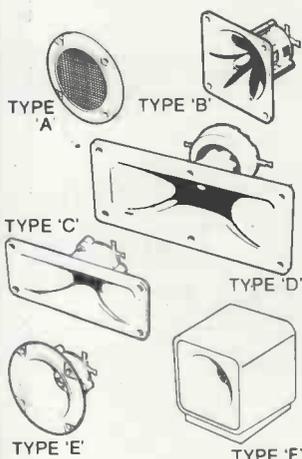Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £3.45 each.

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.35 each.

TYPE 'C' (KSN6016A) 2" - 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £5.45 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £6.90 each.

TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £4.35 each.

TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each.

U.K. post free for SAE for Piezo leaflets.



1000 MONO DISCO MIXER

A superb fully built and tested mixer/pre-amp with integral power supply. 4 Inputs 2 turntables (ceramic cartridge). Aux. for tape deck etc., plus Mic. with override switch, all with individual level controls. Two sets of active tone controls (bass and treble) for Mic. and main inputs. Master volume control. Monitor output with select switch and volume control.

Outputs Main 750 mV Monitor 500 mV into 8 ohms. Supply 220/240V AC50/60Hz Size 22 1/2" x 4 1/2" x 2 1/2" price £39.99 + £2.50 P&P

1K.WATT SLIDE DIMMER



- Controls loads up to 1KW
- Compact size
- 4 1/4" x 1 3/8" x 2 1/2" 16
- Easy snap in fixing through panel/cabinet cut out
- Insulated plastic case
- Full wave control using 8amp triac
- Conforms to BS800
- Suitable for both resistance and inductive loads

Innumerable applications in industry, the home, and discos/theatres etc.

Price: £11.70 each + 50p P&P (Any quantity)


BSR P256 TURNTABLE

P256 turntable chassis • S shaped tone arm • Belt driven • Aluminium platter • Precision calibrated counter balance • Anti-skate (bias device) • Damped cueing lever • 240 volt AC operation (Hz) • Cut-out template supplied • Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price: £28.50 + £2.50 P&P



POWER AMPLIFIER MODULES

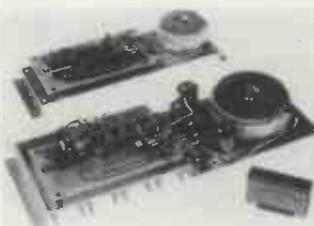

100 WATT R.M.S. AND 300 WATT R.M.S. MODULES

Power Amplifier Modules with Integral toroidal transformer power supply, and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. An LED Vu meter is available as an optional extra.

SPECIFICATION:
Max Output Power: 110 watts R.M.S. (OMP 100) 310 watts R.M.S. (OMP 300)
Loads: Open and short circuit proof 4-16 ohms.
Frequency Response: 20Hz - 25KHz ±3dB.
Sensitivity for Max. Output: 500mV at 10K (OMP 100) 1V at 10K (OMP 300)
T.H.D.: Less than 0.1%
Supply: 240V 50Hz
Sizes: OMP 100 360 x 115 x 72mm
OMP 300 450 x 153 x 66mm
Prices: OMP 100 £31.50 each + £2.00 P&P
OMP 300 £89.00 each + £3.00 P&P
Vu Meter £8.50 each + 50p P&P


Matching 3-way loudspeakers and crossover

Build a quality 60watt RMS system 8ohms
Build a quality 60 watt R.M.S. system.

- ★ 10" Woofer 35Hz-4.5KHz
- ★ 3" Tweeter 2.5KHz-19KHz
- ★ 5" Mid Range 600Hz-8KHz
- ★ 3-way crossover 6dB/oct 1.3 and 6KHz

Recommended Cab-size 26" x 13" x 13"
Fitted with attractive cast aluminium fixing escutcheons and mesh protective grills which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring loaded loudspeaker terminals and recessed mounting panel.
Price £22.00 per kit + £2.50 postage and packing. Available separately, prices on request.

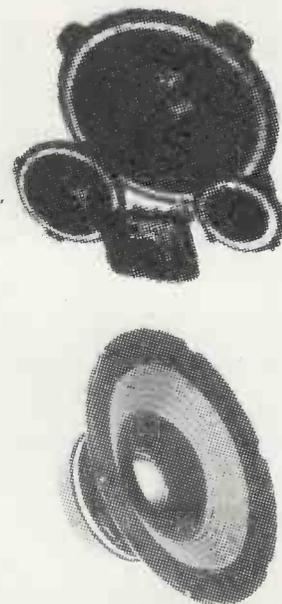12" 80 watt R.M.S. loudspeaker.
A superb general purpose twin cone loudspeaker. 50 oz magnet, 2 aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. Attractive blue cone with aluminium centre dome.
Price £17.99 each + £3.00 P&P.



BK ELECTRONICS

Prompt Deliveries
VAT inclusive prices
Audio Equipment
Test Equipment
by Thandar and Leader

KEYBOARDS



MEMBRANE KEYBOARDS manufactured from a tough polycarbonate film mounted on 1mm glass fibre printed circuit board assembly incorporating silver plated contacts.
16 way numeric keyboard manufactured from a tough polycarbonate keyboard providing 0-9 and A-F functions.
Size: 100mm x 100mm x 2mm Price: £5.99 + 35p p&p
Alpha Numeric Keyboard Full size 55 key non encoded keyboard with the commonly required functions in a Qwerty array. Matrix output via a 16 pin DIL socket.
Size: 350mm x 100mm x 2mm Price: £13.99 + 50p p&p

B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



100 FREE PROGRAMS

FROM SILICA SHOP — WITH EVERY PURCHASE OF AN

ATARI 400

800




ATARI PRICES REDUCED!

We at Silica Shop are pleased to announce some fantastic reductions in the prices of the Atari 400/800 personal computers. We believe that the Atari at its new price will become the U.K.'s most popular personal computer and have therefore set up the Silica Atari Users Club. This club already has a library of over 500 programs and with your purchase of a 400 or 800 computer we will give you the first 100 free of charge. There are also over 350 professionally written games and utility programs, some are listed below. Complete the reply coupon and we'll send you full details. Alternatively give us a ring on 01-301 1111 or 01-309 1111.

ATARI 400 with 16K	£199
ATARI 400 with 32K	£248
ATARI 800 with 16K	£449

400/800 SOFTWARE & PERIPHERALS

Don't buy a T.V. game! Buy an Atari 400 personal computer and a game cartridge and that's all you'll need. Later on you can buy the Basic Programming cartridge (£35) and try your hand at programming using the easy to learn BASIC language. Or if you are interested in business applications, you can buy the Atari 800 + Disk Drive + Printer together with a selection of business packages.

Silica Shop have put together a full catalogue and price list giving details of all the peripherals as well as the extensive range of software that is now available for the Atari 400/800. The Atari is now one of the best supported personal computers. Send NOW for Silica Shop's catalogue and price list as well as details on our users club.

THE FOLLOWING IS JUST A SMALL SELECTION FROM THE RANGE OF ITEMS AVAILABLE:

ACCESSORIES Cables Cassettes Diskettes Joysticks Le Stick - Joystick Misc Supplies Paddles	Mountain Shoot Rearguard Star Flite Sunday Golf	BUSINESS Calculator Database Managemt Decision Maker Graph-It Invoicing Librarian Mort & Loan Anal Nominal Ledger Payroll Personal Finl Mgmt Purchase Ledger Sales Ledger Statistics 1 Stock Control Teletink 1 Visicalc Weekly Planner Word Processor	DYNACOMP Alpha Fighter Chompelo Crystals Forest Fire Intruder Alert Monarch Moonprobe Moving Maze Nominoes Jigsaw Rings of The Emp Space Tilt Space Trap Stud Poker Triple Blockade	Maths-Tac-Toe Metric & Prob Solvg Mugwump Music Terms/Notarn Musical Computer My First Alphabet Number Blast Polycalc Presidents Of U.S. Quiz Master Starware Stereo 3D Graphics Three R Math Sys Video Math Flash Wordmaker	Scram States & Capitals Touch Typing	Castle Centurion Checker King Chinese Puzzle Codecracker Comedy Diskette Dice Poker Dog Daze Domination Downhill Eastern Front Galahad & Holy Grl Graphics/Sound Jax-O Jukebox Lookahead Memory Match Midas Touch Minotaur Outlaw/Mowitz Preschool Games Pro Bowling Pushover Rabbotz Reversi II Salmon Run 747 Landing Simul Seven Card Stud	Sleazy Adventure Solitaire Space Chase Space Trek Sultans Palace Tact Trek Tarry Wizards Gold Wizards Revenge	Jawbreaker Mission Asteroid Mouskattack Threshold Unvssrs/Golden Fl Wizard & Princess Terry Dog Daze Domination Downhill Eastern Front Galahad & Holy Grl Graphics/Sound Jax-O Jukebox Lookahead Memory Match Midas Touch Minotaur Outlaw/Mowitz Preschool Games Pro Bowling Pushover Rabbotz Reversi II Salmon Run 747 Landing Simul Seven Card Stud	PROGRAMMING AIDS from Atari Assembler Editor Dsembler (APX) Microsoft Basic Pascal (APX) Pilot (Consumer) Pilot (Educator) Programming Kit Disk Drive Epson Printers Program Recorder RS232 Interface Thermal Printer 16K Memory RAM 32K Memory RAM	PERIPHERALS Centronics Printers Epson Printers Program Recorder RS232 Interface Thermal Printer 16K Memory RAM 32K Memory RAM	ENTERTAINMENT from ATARI Asteroids Basketball Blackjack Centopede Chess Entertainment Kit Missile Command Pac Man Space Invaders Star Raiders Super Breakout Video Easel	PERSONAL INT from APX Adv Music System Banner Generator Blackjack Tutor Going To The Dogs Keyboard Organ Morse Code Tutor Personal Fitness Prg Player Piano Sketchpad	SANTA CRUZ Basics of Animation Bots Business Display Lists Graphics Machine Kids 1 & 2 Horizontal Scrolling Master Memory Map Mini Word Processor Page Flipping Player Missile Gr Player Piano Sounds Vertical Scrolling	SILICA CLUB Over 500 programs write for details
--	--	---	--	--	--	--	---	--	---	---	--	--	--	--

FOR FREE BROCHURES - TEL: 01-301 1111

For free brochure and reviews on our range of electronic products, please telephone 01-301 1111. To order by telephone, just quote your name, address, credit card number and order requirements and leave the rest to us. Post and packing is FREE OF CHARGE in the UK. Express 24 hour delivery available at an additional charge.

- SHOP DEMONSTRATION FACILITIES - we provide full facilities at our shop in Sidcup, Monday to Saturday, 9am to 5.30pm (closing Thursday 1pm, Friday 8pm)
- MAIL ORDER - we are a specialist mail order company and are able to supply goods direct to your door
- MONEY BACK UNDERTAKING - if you are totally unsatisfied with your purchase, you may return it to us within 15 days. On receipt of the goods in satisfactory condition we will give you a full refund and the rest to us.
- PART EXCHANGE SECOND HAND MACHINES - we offer a part exchange scheme to trade in many makes of TV, games for personal computers.
- COMPETITIVE PRICES - our prices, offers and service are very competitive. We are never knowingly undercut, and will normally match any lower price quoted by our competitors.
- HELPFUL ADVICE - available on the suitability of various computers.
- AFTER SALES SERVICE - available on all computers out of guarantee.
- VAT - all prices quoted above include VAT at 15%.
- CREDIT FACILITIES - we offer credit over 12, 24 or 36 months, please ask for details.

SILICA SHOP LIMITED
Dept HE 1082, 1-4 The Mews, Hatherley Road, Sidcup,
Kent DA14 4DX Telephone 01-301 1111 or 01-309 1111



FREE LITERATURE

I am interested in purchasing an Atari 400/800 computer and would like to receive copies of your brochure and test reports as well as your price list covering all of the available Hardware and Software.

Name

Address

Postcode

HE 12 82