

SEPTEMBER 1983

AN ARGUS SPECIALIST PUBLICATION

Hobby


Electronics

Project Electronics For Everyone


85p

IN THE PIPELINE

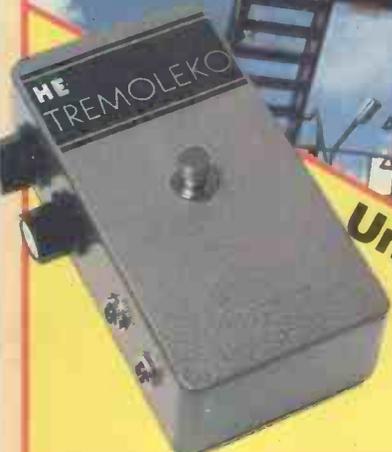Cable and
Satellite TV
Technology
Revealed




Unique "Tremoleko"
Sound Effect

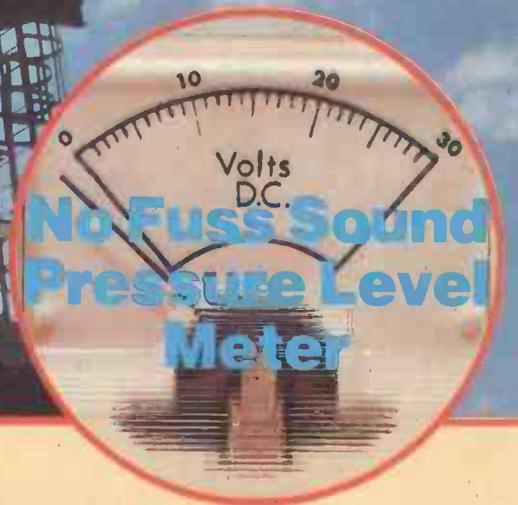

Variable Power Supply Project
Gripometer Project – Test Your Strength!

New cats for old !

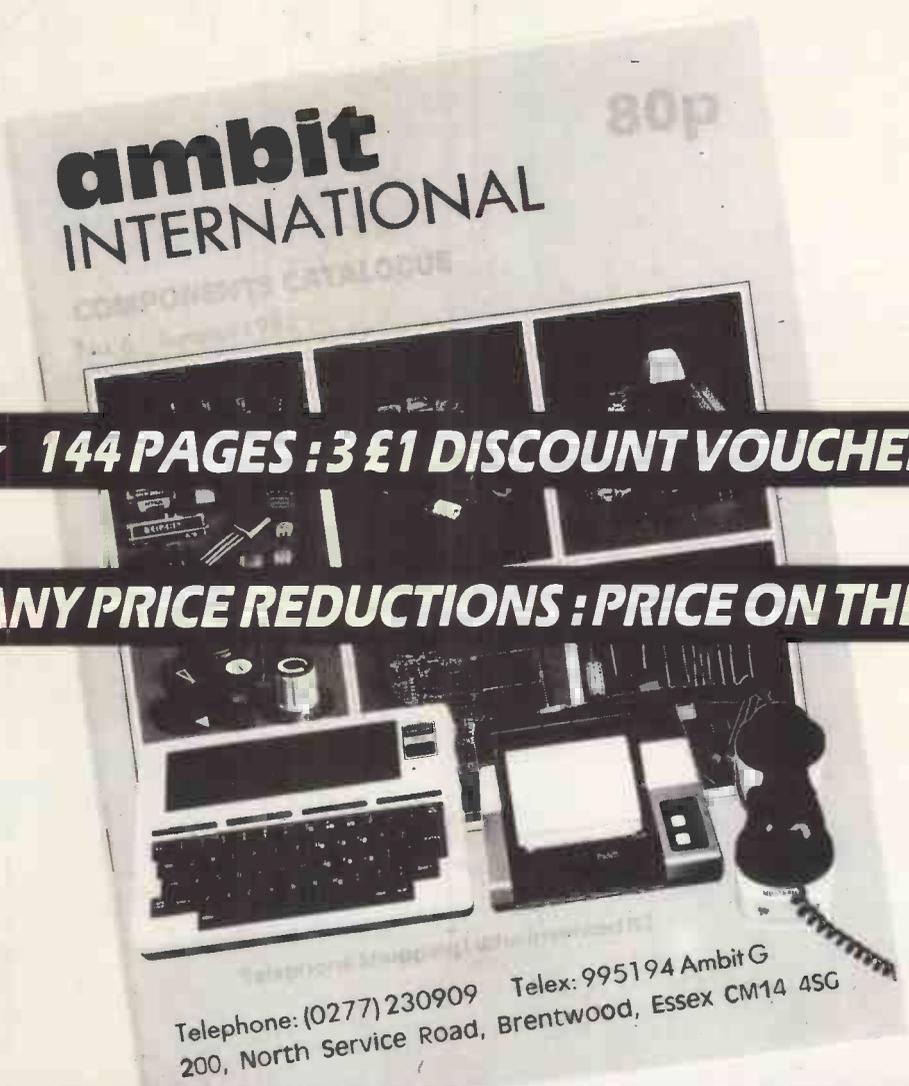SEND US THE COVER FROM ANOTHER COMPONENT SUPPLIERS CURRENT CATALOGUE, PLUS A 40p STAMP, AND WE'LL SEND YOU A FREE COPY OF THE LATEST (SUMMER) AMBIT CONCISE COMPONENT CATALOGUE. ALTERNATIVELY YOU CAN SIMPLY BUY A COPY FROM YOUR NEWSAGENT — OR SEND 80p TO THE ADDRESS BELOW.....



ambit
INTERNATIONAL
COMPONENTS CATALOGUE
80p

★ **144 PAGES : 3 £1 DISCOUNT VOUCHERS**

★ **MANY PRICE REDUCTIONS : PRICE ON THE PAGE**

Telephone: (0277) 230909 Telex: 995194 Ambit G
200, North Service Road, Brentwood, Essex CM14 4SG

★ **AVAILABLE AT NEWSAGENTS, OR DIRECT FROM**

ambit INTERNATIONAL

200 North Service Road
Brentwood
Essex
CM14 4SG

Telephone 0277-230909
Telex 995194 AMBIT G
Data 0277-232628 REWTEL »
300 BAUD DUPLEX

Hobby Electronics

SEPTEMBER 1983
VOL 5 No 9

PROJECTS

- ★ **SOUND PRESSURE LEVEL METER** 14
Is it a bird? Is it a plane? Is it Motorhead???
- ★ **TREMOLKO** 36
Tremolo/Echo-style effect for guitars.
- POWER SUPPLY UNIT** 54
Specially designed for use with projects.
- ★ **HE GRIPOMETER** 59
Test your strength, astonish your friends.

FEATURES


- ★ **MODEL RAIL COMPETITION** 22
Design a computer-controlled railway layout.
- ★ **CABLE AND SATELLITE TELEVISION** 25
A magnificent aerial display!
- ★ **CAREERS IN ELECTRONICS PART 5** 40
Getting into the (TV and Radio) studio.
- ★ **ALL ABOUT ELECTRONICS PART 3** 48
An introduction to resistance and capacitance.

REGULARS

- Monitor 6
- HE Backnumbers 10
- Forward Bias 11
- What's On Next 20
- Buylines 34
- HE Bookshelf 45
- 3readboard 58
- PCB Service 63
- PCB Printout 64

Clever Dick has been despatched overseas to do some important technical research into the effects of solar radiation on the body, not to mention modifications caused by treating the body in question with alcoholic spirits. He'll let you know the results when (if?) he gets back...

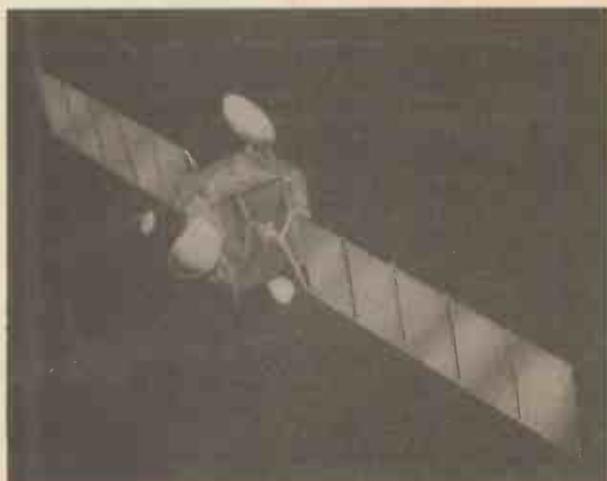Editor: Ron Keeley
 Assistant Editor: Helen Armstrong BA
 Technical Illustrator: Jerry Fowler
 Advertisement Manager: David Kitchener
 Assistant Advertisement Manager: Joanne James
 Managing Editor: Ron Harris BSc
 Managing Director: T.J. Connell



Cable And Satellite TV — page 25



Tremoloko - page 36



HE Gripometer — page 59

Hobby Electronics is normally published on the second Friday of the month prior to the cover date.
 Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002. Telex No 881 1896. Published by Argus Specialist Publications Ltd.
 Origination by Ebony Typesetting, Trion House, 13 Dean Street, Liskeard, Cornwall PL14 4AB.
 Distributed by S. M. Distribution Ltd, 16/18 Trinity Gardens, London SW9 8DX.
 Printed by QB Ltd, Colchester. Covers printed by Alabaster Passmore.

Notice: The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. All reasonable care is taken in the preparation of the magazine to ensure accuracy, but Argus Specialist Publications Ltd cannot be held responsible legally. ©Copyright 1983 Argus Specialist Publications Ltd. Member of Audit Bureau of Circulation.

The Rapid Electronics

MAIL ORDERS:
Unit 2, Hill Farm Industrial Estate,
Boxted, Colchester, Essex CO4 5RD.
TELEPHONE ORDERS:
Colchester (0206) 36412.

ACCESS AND BARCLAYCARD WELCOME

LINEAR		LM339		LM3911		NE566		TL064	
555CMOS 80	ICL7106 790	LM348 65	LM3914 175	LM358 50	LM3915 195	NE567 100	TL071 30	TL072 50	
555CMOS 150	ICL7611 95	LM377 170	LM13600 105	LM380 65	MC1496 68	NE570 370	TL074 95	TL074 95	
709 14	ICL7622 180	LM381 120	MC3340 135	LM382 120	MF10CN 350	RC4136 65	TL081 25	TL081 25	
748 35	ICL8038 295	LM384 130	ML922 400	LM386 65	ML924 195	RC4558 60	TL082 45	TL082 45	
9400CJ 350	ICL8211A 200	LM387 120	ML925 210	LM393 100	ML926 140	SN76477 300	ULN2003 90	ULN2003 90	
AY-3-1270 720	ICM7555 80	LM393 100	ML926 140	LM709 25	ML927 140	T8A800 75	ZN414 100	ZN414 100	
AY-3-8910 370	ICM7555 80	LM393 100	ML926 140	LM709 25	ML927 140	T8A810 96	ZN423 135	ZN423 135	
AY-3-8912 540	LF361 46	LM393 100	ML926 140	LM709 25	ML927 140	T8A820 96	ZN424 135	ZN424 135	
CA3048 60	LF363 85	LM393 100	ML926 140	LM709 25	ML927 140	T8A850 22	ZN425E 350	ZN425E 350	
CA3080 65	LF356 95	LM393 100	ML926 140	LM709 25	ML927 140	T8A810 96	ZN426 330	ZN426 330	
CA3089 190	LM301A 25	LM393 100	ML926 140	LM709 25	ML927 140	T8A810 96	ZN427E 650	ZN427E 650	
CA3090AO 376	LM301A 25	LM393 100	ML926 140	LM709 25	ML927 140	T8A810 96	ZN428E 480	ZN428E 480	
CA3130E 85	LM311 70	LM393 100	ML926 140	LM709 25	ML927 140	T8A810 96	ZN429E 285	ZN429E 285	
CA3140E 36	LM318 120	LM393 100	ML926 140	LM709 25	ML927 140	T8A810 96	ZN430E 200	ZN430E 200	
CA3161E 100	LM324 40	LM393 100	ML926 140	LM709 25	ML927 140	T8A810 96	ZN431E 350	ZN431E 350	
CA3189 290	LM334Z 100	LM393 100	ML926 140	LM709 25	ML927 140	T8A810 96	ZN432E 350	ZN432E 350	
CA3240E 110	LM335Z 125	LM393 100	ML926 140	LM709 25	ML927 140	T8A810 96	ZN433E 350	ZN433E 350	

TRANSISTORS		BC517		BC547		BC548		BC549	
AC125 35	BC149 9	BC517 40	BC547 7	BC548 7	BC549 10				
AC126 25	BC157 8	BC517 40	BC547 7	BC548 7	BC549 10				
AC127 25	BC158 10	BC517 40	BC547 7	BC548 7	BC549 10				
AC128 20	BC159 8	BC517 40	BC547 7	BC548 7	BC549 10				
AC178 25	BC160 45	BC517 40	BC547 7	BC548 7	BC549 10				
AC187 22	BC168C 10	BC517 40	BC547 7	BC548 7	BC549 10				
AC188 22	BC169C 10	BC517 40	BC547 7	BC548 7	BC549 10				
AD142 120	BC170 8	BC517 40	BC547 7	BC548 7	BC549 10				
AD149 80	BC171 10	BC517 40	BC547 7	BC548 7	BC549 10				
AD181 40	BC172 8	BC517 40	BC547 7	BC548 7	BC549 10				
AF162 40	BC173 8	BC517 40	BC547 7	BC548 7	BC549 10				
AF124 60	BC178 18	BC517 40	BC547 7	BC548 7	BC549 10				
AF126 50	BC179 18	BC517 40	BC547 7	BC548 7	BC549 10				
AF139 40	BC182 10	BC517 40	BC547 7	BC548 7	BC549 10				
AF186 70	BC182L 8	BC517 40	BC547 7	BC548 7	BC549 10				
BC101 10	BC183L 10	BC517 40	BC547 7	BC548 7	BC549 10				
BC1078 12	BC184L 7	BC517 40	BC547 7	BC548 7	BC549 10				
BC1088 12	BC212 10	BC517 40	BC547 7	BC548 7	BC549 10				
BC1096 12	BC218 10	BC517 40	BC547 7	BC548 7	BC549 10				
BC1099 12	BC219 10	BC517 40	BC547 7	BC548 7	BC549 10				
BC114 18	BC219L 10	BC517 40	BC547 7	BC548 7	BC549 10				
BC115 22	BC219L 10	BC517 40	BC547 7	BC548 7	BC549 10				
BC117 18	BC237 8	BC517 40	BC547 7	BC548 7	BC549 10				
BC119 35	BC238 12	BC517 40	BC547 7	BC548 7	BC549 10				
BC137 40	BC238 12	BC517 40	BC547 7	BC548 7	BC549 10				
BC139 40	BC237 8	BC517 40	BC547 7	BC548 7	BC549 10				
BC140 28	BC238 12	BC517 40	BC547 7	BC548 7	BC549 10				
BC141 30	BC237 8	BC517 40	BC547 7	BC548 7	BC549 10				
BC142 25	BC238 12	BC517 40	BC547 7	BC548 7	BC549 10				
BC143 25	BC237 8	BC517 40	BC547 7	BC548 7	BC549 10				
BC147 8	BC247 30	BC517 40	BC547 7	BC548 7	BC549 10				
BC148 8	BC249 30	BC517 40	BC547 7	BC548 7	BC549 10				

CABLES		20 metre pack single core connecting cable ten different colours. 65p	
Speaker cable	10p/m	Standard screened	18p/m
Twin screened	24p/m	2.5A 3 core mains	23p/m
10 way rainbow ribbon	65p/m	20 way rainbow ribbon	120p/m
20 way grey ribbon	38p/m	20 way grey ribbon	80p/m

HARDWARE		PP3 battery clips	
Red or black crocodile clips	6	Black point-on control knob	15
Pr Ultrasonic transducers	350	6V Electronic buzzer	65
12V Electronic buzzer	65	PB2720 Piezo transducer	75
64mm 8 ohm speaker	70	20mm panel fuseholder	25

CAPACITORS		Polyester, radial leads, 250V. C280	
type: 0.01, 0.015, 0.022, 0.033	8p	0.047, 0.068, 0.1, 7p; 0.15,	15
0.22, 9p; 0.33, 0.47, 1.3p; 0.68,	20p; 1u - 23p	Electrolytic, radial or axial leads:	
0.47/63V, 1/63V, 2.2/63V, 4.7/63V,	100/25V - 7p; 22/25V, 47/25V - 8p;	220/25V - 9p; 220/25V - 14p;	
470/25V - 20p; 1000/25V - 30p;	2200/25V - 50p	Tan and power supply electrolytics:	
2200/40V - 110p; 4700/40V - 160p;	2200/63V - 140p; 4700/63V - 230p	Polyester, miniature Siemens PCB:	
1n, 2n, 3n, 4n, 6n, 10n, 15n, 7p;	22n, 33n, 47n, 68n, 8p; 100n, 9p;	150n, 11p; 220n, 13p; 330n, 20p;	
470n, 26p; 680n, 29p; 1u 33p; 2u,	50p.	Tantalum bead:	
0.1, 0.22, 0.33, 0.47, 1.0 @ 35V -	12p, 2.2, 4.7, 10 @ 25V - 20p;	15/16V - 30p; 22/16V - 20p; 33/	
16V - 45p; 47/16V - 27p; 47/16V -	20p; 56/16V - 40p; 100/10V - 30p.	Car. disc. 22p-0.01u 50V, 3p each.	
Multilayer miniature ceramic plate:	1.8pF to 1000pF 6p each.	Polystyrene, 6% tol: 10p-100p, 6p;	
1500-4700, 8p; 6800 0.01u, 2u, 10p.	Trimmers, Multilayer 808 series: 2-10	pF, 2.2pF - 3.0p; 5.6-65pF, 3p	

REGULATORS		78L05 30	
78L12 30	79L12 65	78L15 30	79L15 65
78L15 30	79L15 65	78L20 30	79L20 65
78L20 30	79L20 65	78L25 30	79L25 65
78L25 30	79L25 65	78L30 30	79L30 65

POTENTIOMETERS		Rotary, Carbon track Log or Lin	
1K - 2M2 Single 32p. Stereo 85p.		Single switched 80p. Slide: 60mm	
travel single Log or Lin 5K - 500K		63p each.	
Pre-set submin. hor. 100 ohms - 1M		7p each.	
Cermet precision multiturn, 0.75W		% 100 ohms to 100K - 88p each.	

TRIACS		400V 8A 65	
400V 16A	95	400V 4A	25

DIODES		BY127 12	
0A11 7	1N4007 7	0A30 8	1N4006 7
0A31 7	1N4007 7	0A200 8	1N5401 12
0A202 8	1N5404 16	1N914 4	1N5406 17
1N4148 3	400mWzen 6		

JUMPER LEADS		Length 14pin 16pin 24pin 40pin	
5pin end of DIP header plug jumper	14 pin	15 pin	24 pin
5pin end of DIP header plug jumper	14 pin	15 pin	24 pin
5pin end of DIP header plug jumper	14 pin	15 pin	24 pin

BRIDGE RECTIFIERS		2A 200V 40	
2A 400V 45	80	1A 50V	20
1A 50V	20	VM18 DIL 0.9A	50
1A 400V	35	20V 50V	120

OPTO		3mm red 7	
3mm green 10 <td>5mm red 7</td> <td>3mm yellow 10 <td>5mm yellow 10</td> </td>	5mm red 7	3mm yellow 10 <td>5mm yellow 10</td>	5mm yellow 10
Clips to suit - 3p each		Rectangular - TIL32 40	
Green 12	TIL78 40	Red 17	TIL111 60
Yellow 17	ORP12 85	TIL38 40	TIL100 90
2N5777 25	Dual colour 60	Seven segment displays:	
Com cathode	Com anode	DL704 0.3" 95	DL707 0.3" 95
FN500 7	FN507 7	0.5" 100	0.5" 100
TIL310.3" 115	TIL3120.3" 115	TIL320.5" 115	TIL3120.5" 115
LCD: 3% digit 580p.	4 digit 1620p.		

COMPUTER CONNECTORS		ZX81 2 x 23 way edge connector	
wire wrap suitable for ZX81		add ons	
SPECTRUM 2 x 28 way edge connector wire-wrap suitable for SPECTRUM add-ons	150		

IDC CONNECTORS		PCB Plug	
Straight		Socket	
10 way	100	85	120
16 way	130	110	175
20 way	145	125	195
26 way	175	150	240
34 way	205	170	320
40 way	220	190	340
50 way	235	200	395
60 way	330	230	495

MIN. D CONNECTORS

Plugs solder lugs 9 way 15 way 25 way 37 way
50p 170p 340p 510p
Right angle 120p 180p 240p 350p
Sockets lugs 9p 130p 195p 290p
Right angle 160p 210p 290p 440p
Covers 100p 90p 100p 110p



SOLDERING IRONS

Antex CS 17W Soldering iron 495
2.3 and 4.7mm bits to suit 85
CS 17W/VS 25W element 210
Antex XS 25W 45
3.3 and 4.7mm bits to suit 85
Solder pump desoldering tool, 480
Spare nozzle for above 70
10 metres 22swg solder 100

CONNECTORS

DIN Plug Skt Jack Plug Skt
2 pin 9p 9p 2.5mm 10p 10p
3 pin 12p 10p 3.5mm 9p 9p
5 pin 13p 11p standard 16p 20p
Phono 10p 12p Stereo 24p 25p
1mm 12p 13p 4mm 18p 17p
UHF (CB) Connectors:
PL259 Plug 40p. Reducer 14p.
SO239 square chassis skt 38p.
SO239S round chassis skt 40p.
IEC 3 pin 250V/6A.
Plug chassis mounting 38p
Socket free hanging 60p
Socket with 2m lead 120p

electronize

AUTO-ELECTRONIC PRODUCTS

KITS OR READY BUILT

TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION



IS YOUR CAR AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
- ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains it from service to service.
- ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs, where the ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engines maximum (even with 8 cylinders).
- ★ Is the **PERFORMANCE SMOOTH**? The more powerful spark of Total Energy Discharge eliminates the "near misfires" whilst an electronic filter smooths out the effects of contact bounce etc.
- ★ Do the **PLUGS and POINTS** always need changing to bring the engine back to its best? Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.
- ★ **TOTAL ENERGY DISCHARGE** is a unique system and the most powerful on the market - 3 1/2 times the power of inductive systems - 3 1/2 times the energy and 3 times the duration of ordinary capacitive systems. These are the facts:
Performance at only 6 volts (max. supply 16 volts)
 SPARK POWER — 140W, SPARK ENERGY — 36mJ
 SPARK DURATION — 500µS, STORED ENERGY — 135mJ
 LOADED OUTPUT VOLTAGE
 50pF load — 38kV, 50pF + 500k — 26kV
 We challenge any manufacturer to publish better performance figures. Before you buy any other make, ask for the facts, it's probably only an inductive system. But if an inductive system is what you really want, we'll still give you a good deal.
- ★ All **ELECTRONIZE** electronic ignitions feature:
EASY FITTING, STANDARD/ELECTRONIC CHANGE OVER SWITCH, STATIC TIMING LIGHT and DESIGNED IN RELIABILITY (14 years experience and a 3 year guarantee).
- ★ **IN KIT FORM** it provides a top performance system at less than half the price of comparable ready built units. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2µF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

Most NEW CARS already have electronic ignition. Update YOUR CAR

PROTECT YOUR CAR WITH AN ELECTRONIZE ELECTRONIC ALARM



- ★ **2000 COMBINATIONS** provided by an electronic key - a miniature jack plug containing components which must match each individual alarm system. (Not limited to a few hundred keys or a four bit code).
- ★ **60 SECOND ALARM PERIOD** flashes headlights and sounds horn, then resets ready to operate again if needed.
- ★ **10 SECOND ENTRY DELAY** allows owner to dis-arm the system, by inserting the key plug into a dashboard mounted socket, before the alarm sounds. (No holes in external bodywork, fiddly code systems or hidden switches). Re-closing the door will not cancel the alarm, before or after it sounds, the key plug must be used.
- ★ **INSTANT ALARM OPERATION** triggered by accessories or bonnet/boot opening.
- ★ **30 SECOND DELAY** when system is armed allows owner to lock doors etc.
- ★ **DISABLES IGNITION SYSTEM** when alarm is armed.
- ★ **IN KIT FORM** it provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, CMOS IC's, random selection resistors to set the combination, in fact everything down to the last nut and washer plus easy to follow instructions.

FITS ALL 12 VOLT NEGATIVE EARTH VEHICLES. SUPPLIED COMPLETE WITH ALL NECESSARY LEADS AND CONNECTORS PLUS TWO KEY PLUGS

Don't Wait Until Its too Late ~
Fit one NOW!

fill in the coupon and send to:

ELECTRONIZE DESIGN Dept E Magnus Rd · Wilnecote · Tamworth · B77 5BY · tel 0827 281000

TOTAL ENERGY DISCHARGE (6 or 12 volt negative earth)

- Assembled ready to fit **£26.70** £19.95
 D.I.Y. parts kit **£15.90** £14.95

TWIN OUTPUT for cars and motor cycles with dual ignition

- Twin, Assembled ready to fit **£36.45** £29.95
 Twin, D.I.Y. parts kit **£24.55** £22.95

INDUCTIVE DISCHARGE (12 volt only)

- Assembled ready to fit **£15.95** £12.75

Prices include VAT.

P+P £1-00 (UK)

CAR ALARM

- Assembled ready to fit **£37.95**
 D.I.Y. parts kit **£24.95**

I enclose cheque/postal order OR debit my Access/Visa card

VISA ACCESS

Name _____

Address _____

Code _____

MONITOR

Well Done, Sir

Readers who can tear themselves away from their soldering irons long enough to read the Daily Rag or listen to the radio news will have heard that legendary all-round computer manufacturing and marketing genius Clive Sinclair (Yes, Sinclair, Clive, as in Sinclair, Spectrum and Sinclair, ZX81...) has been honoured with a knighthood in this year's Birthday Honours list. The

rumours say that this came as a complete surprise to Mr. Sinclair, but not to the rest of us. We always knew that the man who enabled the nation to pick up its micro with its daily papers and scared hell into the opposition deserved something special. Apart from a few million quid, that is. So, from Hobby Electronics editorial team, technical department and Beasties, well done, Sir...

One problem. Do we address him as Uncle Sir Clive, or Sir Uncle Clive?



The Future Is Here As Soon As You Can Afford It

Questions and answers time again: Grundig International, well-known perpetrators of video, hifi and TV, have initiated a Marplan survey to find out who does what with their television, how, where and when.

Marplan came up with a few interesting facts about the Youth of the Nation and their possessions, and preferences. For instance, 46 per cent of British homes have a second television (we presume they mean one in working order!) and the 'old' telly is often purloined by the younger generation. About 18 per cent of children have their own TV set (. . . that's nearly one in five. My mind begins to boggle. Where did Marplan do this survey??) and, having got it, they watch breakfast telly in their bedrooms!

Their survey also showed that whereas nearly every family in the land has its own radio but only 50% of children do, only 27% of families have a cassette player, but 27% of children do. Against that, 76% of families have a record player, but only 25% of children — this is the portable generation, by the look of it. The kids apparently, from this sample, have not yet moved into the VCR-owing class, but Grundig suspect that there may be specimens lurking out there, the first of a new species. It seems that videos have also eased the family relationships by making it easier to get the kids off to bed with the promise of recorded programmes the next day.

(I can confirm this from experience. My in-laws find it a great relief to leave us in the charge of a recording of *The Old Grey Whistle Test* while they go peacefully to bed — same principle, isn't it?)

Another little factoid which emerges, which we all knew in our hearts, is that people, especially children, like to record their favourite programmes and watch them over and over again (so that's why the In-laws won't release the videotapes till after they've retired to bed). Never mind information content *Top Of The Pops*, *Grange Hill*, *Fame* and *Kenny Everett* are among the favourites. A significant number of families (11 per cent) watch rented video tapes every day.

Your MONITOR person, being an old fogie who merely worships television but was actually raised by a portable radio, finds it encouraging that 92 per cent of children listen to the radio, and many of them like it because they can use their imaginations more than with TV, and they aren't tied to watching, but can get on with something else. Like writing MONITOR, for instance.

Grundig seem to have confirmed a few more things which we all thought we knew anyway, but which nobody had got round to telling us officially: we like video because we can record programmes we would otherwise miss and watch them later (have you any idea the suffering this sort of thing causes to someone who doesn't have a video? Like me?); and that 76 per cent of people who don't have videos would like to have one if only they could afford it (right again!). And that people with two televisions (chance'd be a fine thing. I can't even afford *one* at the moment . . .) and who don't have the second one purloined by their offspring (knowing my luck, if I had one, the cat would snatch it) prefer to have one upstairs in the bedroom (so that's what the In-laws get up to . . .) so they can watch it in bed. (Right yet again!) Slightly less expected is that some people watch breakfast television in bed. (How can they? How do they get their eyes open at that time of the day??)

Well, it's nice to know you're nearly normal.

Another factoid which tends to be confirmed by experience is that people want an integrated viewing/listening system, with all their hifi, video, television, radio, and whatever played through one system with 'speakers running anywhere they are desired.'

At this point, Grundig just are not adventurous enough. They conclude that people would like to be able to play everything back through their TV sets. Not round here, you don't! Is anyone out there going to spend £500 on a new compact disc player and then put it through the telly?? Surely the whole point of those things is that they don't sound as if they have been put through a telly . . . words fail me!

Let's think positive. When is Grundig,

or someone, going to come up with a decent, domestic-quality, domestic-priced multi-way switching amp? What about the household whose main problem is the inability to keep two cassette players, a record player, radio, television, video, home computer (come on. *Dream* a bit), closed circuit TV monitoring the food processor, several sets of headphones and an electric guitar running all at the same time? *This* is the future, believe me! These guys are just not thinking *big* enough.

Let's get off this provocative subject and onto something more mundane: Marplan have finally come up with some real observations on the effect of television in the bedroom.

For one, it's usually the man who has to leap out of bed to turn the telly off at the end of the evening's viewing. Either chivalry is not yet dead, or else it really is true that women are better at sleeping through a persistent din than men are. Having a television in the bedroom does interfere with other bedroom activities. 17 per cent said it was a problem trying to read and watch telly in bed at the same time. Others grumbled about the effect on knitting, Scrabble and pillow fights. Some even said that having a telly in the bedroom interfered with sex. Somebody ought to tell them to take the telly off the bed.

(Mind you, in a household where the main problem is getting the *cat* out of the bed, all this good advice isn't going to go very far, is it? These people don't know when they're well off, do they? Foam. Snarl.)

Apologies. This editorial bitterness is merely caused by the stress of having to be polite about the *Which Video* team so that we can use their TV occasionally. The things we go through . . . however, in order to deal with some of these problems, Grundig have produced a leaflet, *How To Choose And Use Your Television*. If you're interested in this, send a largeish SAE to "TV Leaflet Offer", Grundig Press Office, 50 Upper Brook Street, London W1Y 1PG. Unfortunately, it lacks a little bit of inspiration on the last range of points discussed above. How about a TV set with a book-prop on top? You have to think into the future, you know.



Cee Bee

At last, CB equipment for use on the 934 MHz UHF band is beginning to raise its head. A firm called BeeWare are producing a transverter, the LA83, which will convert a 27MHz transceiver to 934MHz by means of a PL Patch lead between the antenna output of the 27 MHz rig and the input of the transverter, and connection via an n-type connector to a 934MHz antenna.

For use as home base, the transverter needs a 5A PSU.

The 934MHz band, being UHF, is less prone to interference than 27 megs and (for the time being anyway!) as there are so few units able to access it, its twenty channels are far less crowded than the popular bands. How long will this last, we wonders? Perhaps the interest in UHF is another indication of a more "serious" approach towards hobby radio in general, along with the swing towards the more demanding rigours of Ham radio by people who began with an interest in CB.

The LA83 will retail for around £200.00, under the 'Grandstand' label. For further information, contact BeeWare, Adam Leisure Group Ltd., Ripon Road, Harrogate, North Yorkshire, HG1 2AU. Tel: (0423) 501151.

Splashproof Switch


Superswitch Electric Appliance have added a splashproof, outdoor model to the indoor remotely controlled light switches in their range. The three models now available, all switched by a small, infra-red transmitter, offer the convenience of remote switching for all domestic applications in and around the home.

The splashproof version is in an attractive, white, surface mounting case with a remotely actuated switch and a manual switching button. The Superswitch hand held infra-red transmitter which actuates the switch can be used as much as 50ft from it, and will operate through glass. Coming home at night, a driver can thus turn on the outside light without having to get out of the car or even open the window.

The new splashproof remote control

switch (catalogue number 2715) will switch 5A maximum tungsten lamps or resistive loads, with a maximum of 2A5 for fluorescent or inductive loads. It can be mounted with conduit entry above, below or at the side of the box, with no danger of seepage from rainwater. The infra-red transmitter, measuring only 1.5 x 5.25 x 1 in, is powered by a 9V alkaline battery. It has been proven in use with the indoor switches in the range, and shown to give no interference with remotely controlled TV or video recorders.

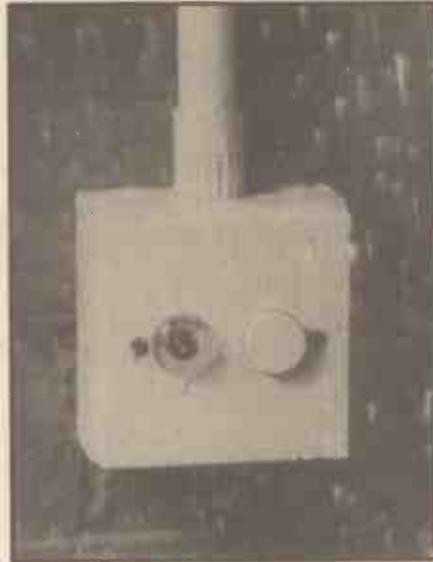Superswitch's latest product, which can be installed in one- or two-way switching circuits, has three modes of operation, set up by an internal switch during installation. The options are: switched on by infra-red beam, off manually; switched on as long as either



infra-red or manual switch is pressed, but goes off when released; switch on and subsequently off by either infra-red device or manual switch.

Superswitch say that they are in the business of providing convenience and security in the home. The model 2715 splashproof remotely controlled switch is the latest product with these objectives in mind. Further information from Superswitch Electric Appliances Limited, 7 Station Trading Estate, Camberley, Surrey, GU17 9AH. Tel: (0276) 34556.

Equipment Great And Small

New from Electronic & Computer Workshop is a particularly strong general purpose knife, precision engineered in vanadium stainless steel. With a blade measuring 3 1/4 in and a tough, moulded plastic amber coloured handle hinging down to encase completely and protect the blade when not in use, it fits safely and handily into pocker or tool box. The whole knife is of a very high quality, well engineered and


with no play on the rivets. The tensioned handle has finger and thumb grips and clips hold it open or firmly hinged shut. It is priced £2.50 plus 45p p&p and VAT.

The Crotech 3337 dual trace oscilloscope's specifications, overall size and rugged construction make it an effective instrument for the microcomputer and peripherals field service engineer. The front panel has related controls colour linked for ease of use.

A 30MHz bandwidth is specified for the vertical deflection system, but the smooth roll off designed into the amplifiers is said to extend its response to 40MHz. The rise/fall time of the fast transient or pulse can be readily displayed and analysed via a built-in signal delay line operative on both channels and a fast 11 ns7 rise time. The Post Deflection Accelerator (PDA) CRT operating at 10kV enables fast pulses at a relatively low repetition rate to be displayed. Deflection coefficients can range from 5mV to 20V/div. and are complimented by a variable control extending the range to 50V/div. This scope also features algebraic addition and subtraction (with Channel 2 inverted), valuable for the servicing and alignment of disk drives.

The 40ns to 1s/div. range on the horizontal deflection is covered by a 21 position calibrated timebase with x5 magnification. Vertical channel or external source selection and composite trigger for the investigation of non-frequency related signals, plus line frequency highlight the comprehensive triggering facilities of the 3337, which also gives selectable AC/DC trigger coupling. Further a single shot mode with a reset to capture intermittent or single transient signals is incorporated.

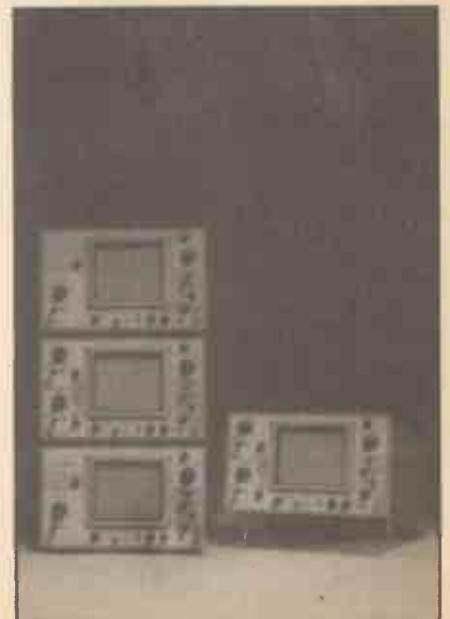Additionally the 3337 will trigger up to 50MHz in either the Auto or Trigger level mode, the level mode ensuring reliable triggering for complex waveforms and the auto mode giving a bright line in the absence of an input



MONITOR

signal (level selection is also operational here).

The 3337 is priced at £405 plus £12.00 p&p and VAT.



A microprocessor controlled EPROM programmer currently available from Electronic & Computer Workshop can be supplied in kit for £180 or built and tested for £270, plus £1.00 p&p and VAT.

The programmer, a stand alone unit complete with power supply, housing and test sockets, has facilities to test, verify copy and program the following EPROMs: 2716, TMS2516, 2732 and 2732A for 16 or 32K. Specified controls include a hexadecimal keyboard plus function keys incorporated into a 24 key pad with 12 address LEDs, four function LEDs (error, program, OK and size) and two hexadecimal displays.

Available functions make this microprocessor based programmer a comprehensive unit. Functions include blank test and error, verify test and error, reset, input or modify data in user RAM at a desired address, parallel load capability from a DMA controlled RAM field, OK indication for successfully executed functions, increment function storing the input data via the hexadecimal, and jumping to the next address in the user RAM.

Currently available is a 3½ digit LCD module, of first class professional quality with 12.7mm high characters, costing £7.50 (plus 45p p&p and VAT). The LCD has an attractive bezel which secures and protects the LCD and incorporates high reliability Zebra strips. These strips consist of alternating parallel layers of conductive and non-conductive silicone rubber. Thus mounted, shock and vibration protection for the LCD is ensured. The connectors further provide a gas tight seal of the contact surface to assure reliable operation in a hostile environment. The clear bezel ensures the LCD polariser is free from scratches. The assembly is available with a dual inline display, so that the viewing area is in the centre. Clever Dick says he's never seen a Zebra strip; can anyone advise him?

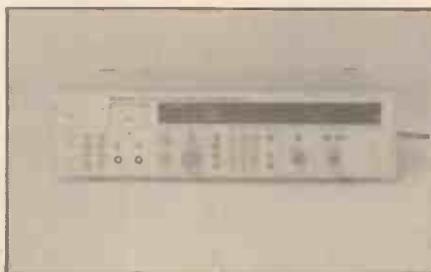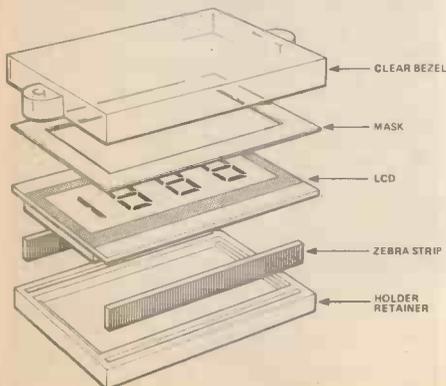For more information, contact Electronic and Computer Workshop Ltd., 171 Broomfield Rd., Chelmsford, Essex CM1 1RY. Tel: (0245) 62149.



All Round Exhibition

A new home computing, video and electronics show with families in mind is going ahead at the Birmingham National Exhibition Centre on the 4th, 5th and 6th November (going off with a bang!!). Atari, Sinclair and Ideal Toys are among the suppliers who are exhibiting at Brainwave '83 where, we gather, the emphasis will be not only upon household and entertainments electronics, but on making the subject interesting to people of all ages and interest levels, not just for the very technically minded. More information will be appearing in the press, and doubtless in HE too, as it comes out.

Japanese CB Parts

Guildford CB has contacted us to say that, as well as stocking a large number of CB rigs and accessories, as well as a growing range of amateur radio gear (73s to you!), they specialise in hard-to-find Japanese transistors and CB rig components — obviously important for rig doctors who can't find replacement parts. Guildford also supply VHF and UHF aerials and some replacement high wattage valves, and standard tools, plugs and sockets, batteries and PSUs. Trade enquiries are welcome as well as the public, and credit cards are acceptable. I notice from their notepaper that they also do 'video' as well, although they don't specify what, exactly.

All enquiries to Guildford CB, 34 Aldershot Rd., Guildford GU2 6AF. Tel: Guildford 577550, 571439 or 573868.

DMM And Sig-gen

Thandar Electronics a new LED 3½ digit multimeter to their range of DMMs. There is still a large demand for a bench/portable LED instrument where dark conditions apply, and LCD are not suitable. Designated the TM355, the meter has a basic accuracy of 0.25%; AC and DC voltage ranges from 100uV to 1000V (750 AC), current ranges from 100na to 10M and resistance measurement of 100mR to 20MR plus diode check, and is priced at £75.00 plus VAT.

Thandar have also introduced three new AM-FM memory programmable signal generators to their Leader range of instruments. Designated the LSG-215, LSG-216 and LSG-217 they have the following specification: display tuning, address location and output level is indicated in digital format; a 100 point memory programmable for any mix of FM and AM modulation, plus output level and frequency (memory is supported by battery after switch off); full PLL synthesizer system with high stability oscillator; a peak indication meter; frequency ranges covering 0.1MHz to 115MHz (-9 to 120dBu). Accessories are also available to enable the use of remote controller and a plug in ROM unit to retain a specific programme. For further information please contact: Thandar Electronics Ltd., London Rd., St. Ives, Huntingdon, Cambs PE17 4HJ. Tel: (0480) 64646.

Look Into This

Do you wish to examine stress cracks, rod or tube dimensions, breaks in electronic circuits, etc.? If so, then according to Hirsh Jacobson Merchandising Co., what you need is the Micro Mike pocket microscope.

Jesting aside, a little microscope like this, which gives 10x, 20x, 40x and 50x magnification, has a myriad of uses for anyone doing fine work or quality checking. The Micro Mike is USA-made and is guaranteed to function accurately indefinitely. It is a precision,

MONITOR

professional instrument. The standard model is £8.80 (VAT and postage extra), or £10.80 for a model with a built-in measurement scale to 0.1mm. The model in our photograph shows the microscope on the left, with an attachment, the Microlite (£6.00) which is designed to shine a light precisely onto the field of the Micro Mike in dark places.

It clips into the pocket like a pen, is housed in a light, tough aluminium case, specially designed to focus light into the opening and protect its four lenses from dirt and scratches. Altogether a very handy little beastie — someone can give me one for my birthday, if they like!

Enquiries to **Hirsh Jacobson Merchandising Co. Ltd.**, 91 Marylebone High St., London W1M 3DE. Tel: 01 935 4709. They do a nice brochure with some photographic samples of the microscope's uses.



Speech Synthesiser

For anyone with a micro and the confidence to know what they're doing with it, **General Instruments Microelectronics** has introduced a voice synthesis module, the VSM 2128-AL2.

The module contains a single chip, N-channel MOS/LSI circuit that is able, through stored allophones, to synthesise any phrase in English, through a stored allophone system. The module is interfaceable with digital systems using a standard 15-pin edge connector. Once selected, the module requires no support from user circuits, and enunciates all allophones and signals when complete.

The chip in use is General Instrument's SPO256-AL2 single chip speech synthesizer. The allophone technique of speech synthesis has a low bit rate. Each allophone has a six bit address, and assuming ten to twelve allophones a second in speech, synthesis requires less than 100 bits per second. It does not, unlike earlier

techniques, require the synthesizing and storing of entire words as units.

The cost is around £50. For more information, contact **General Instrument Microelectronics Ltd.**, Times House, Ruislip, Middx. HA4 8LE. Tel: Ruislip 33355 or 35700.



permanently wired in. Power consumption is half a watt, so that it can be safely left on without running down the battery. The case is ABS plastic and measures 5 x 4 1/4 x 2 1/2 in. The price is £00.00 and it will be available from high street stores as well as from Sidha.

Enquiries to **Sidha Technology Ltd.**, 15 Pit Hey Place, West Pimbo, Skelmersdale, Lancashire WN8 9PS. Tel: (0695) 22141.

Pocket Wear

People working on the move will be interested in **Semiconductor Supplies'** 130g digital multimeter, which is small enough to go easily into a pocket the DM 2350.

The meter has a 3 1/2 digit LCD display, 10mm high with unit symbol (auto/AC/BT/Lo) and a sampling time of 2s per sample. Features include low power ohms for in-circuit resistance (less than 0V4), three step protection by a bleep, a fuse and FET, AC/DC 10MR



Any Old Ion?

Y'all may have heard of the healthgiving virtues of the Negative Ion. What is a negative ion? Never you mind — it's enough to know that negative ions are found in bracing sea air and similar locations, and breathing them, deeply or otherwise, makes your heart beat faster, eyes brighter, head clearer, chest broader, etc. More to the point, stuffy enclosed places are deficient in negative ions, especially places filled with cigarette smoke, hydrocarbon fumes (plastics, petrol, etc.) and inactivity. Which is a fairly good description of the interior of a travelling car.

Ionisers for the home and office are now being followed up by ionisers for the car. The "Mountain Breeze" ioniser is made by **Sidha Technology**, a Lancashire company which 'specialises in environmental health and high technology'. The ioniser works by pouring out a stream of negative ions, clearing the air of dust, smoke and pollen, helping to relieve hay fever, stuffiness and car sickness and maintaining alertness and the ability to drive on safely with fewer brakes.

The unit can be plugged quickly into the cigarette lighter plug in the car, or



input impedance, high sensitivity with 200mV range and an adjustable bleep for continuity test work.

The DM 2350 costs £55 plus VAT, and comes with carrying case, leads, battery, spare fuse and manual. A shunt is supplied to extend the AC amps range to 20A.

Enquiries to **Semiconductor Supplies International Ltd.**, Dawson House, 128/130 Carshalton Rd., Sutton, Surrey SM1 4RS. Tel: 01 643 1126.

BACKNUMBERS



February 1980

Passion Meter, Win Indicator, Short Circuit Special, Kit Review Special, Into Electronics Construction Part 1.

May 1980

MiniClocks, 5080 Preamp, Model Railway Track Cleaner, 5080 Loudspeakers, Loudspeaker Crossover Design, Radio Controlled Model Survey.

June 1980

Microbe Radio Control System, Egg Timer, Two Watt Amplifier, Fog Horn, Short Circuits, LEDs and LED Displays.

July 1980

Sound-Operated Flash Trigger, 18 + 18 Car Stereo Booster, Hazard Flasher, Electronics in Photography, Electronic Espionage, Piezo Electricity.

August 1980

EquiTone Car Equaliser, Pass-The-Loop Game, Gaztec Gas Detector, OP-Amp Checker, In-Car Entertainment Survey, Introducing Microprocessors.

September 1980

MicroMixer, Reaction Tester, Guitar Phaser, Development Timer, Teletext Explained, Into Digital Electronics Part 1.

October 1980

Kitchen Timer, Tug 'o' War Game, Light Dimmer, Freezer Alarm, Intruder Alarm, Temperature-Controlled Soldering Iron.

January 1981

Car Rev-Counter, Bench Amplifier, Sound-Into-Light Converter, Chuffer, Electronic Games reviewed.

February 1981

Heartbeat Monitor, High-Impedance Voltmeter, Medium Wave Radio, Two-Tone Train Horn, Audio Signal Generator.

March 1981

Public Address Amplifier, Windscreen Wiper Controller, Bicycle Speedometer, Photographic Timer, Microcassettes.

April 1981

Pre-Amplifier Part 1, Super Siren, Guitar Tremolo, Russian Roulette Game, Doorbell Monitor, Anatomy of a Space Shuttle.

May 1981

Electronic Organ, Voice-Operated Switch, Infra-Red Controller, Pre-Amplifier Part 2, Audio Millivoltmeter.

June 1981

Power Amplifier Part 1, Continuity Checker, Envelope Generator, Early Radio, Gadgets, Games and Kits Supplement.

July 1981

Burglar Alarm, Doorbuzzer, Treble Booster, Electronic Aids for the Disabled, Power Amplifier Part 2.

August 1981

Electronic Ignition, Thermometer, Electronic Organ (final part), RPM Meter, Bench Power Supply, Radio Control Survey, Into Electronic Components Part 1.

All of the 1980 issues, except January and April, are still available together with the remaining issues from 1981.

All backnumbers cost £1.50 each. For those of you who only want copies of articles, we do offer a photocopying service. Each copy costs £1.50 and information as to its title and publication date should be given. Ordering backnumbers and photocopies could hardly be easier, just fill in the coupon, cut it out and send it to the appropriate address.

**HOBBY ELECTRONICS
BACKNUMBER ORDER FORM TO:**



513, London Road,
Thornton Heath,
Surrey, CR4 6AR
England.

Please send me the following items:

NAME

ADDRESS

.....

.....


.....

Back issues at £1.50 each

I enclose £.....

Cheques and Postal Orders should be made payable to ASP Ltd.

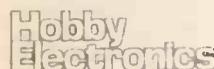**HOBBY ELECTRONICS
PHOTOCOPY ORDER FORM TO:**



145 Charing Cross Road,
London,
WC2H 0EE

Please send me the following items:

NAME

ADDRESS

.....


.....

Photocopies of in the

..... issue at £1.50 each

I enclose £.....

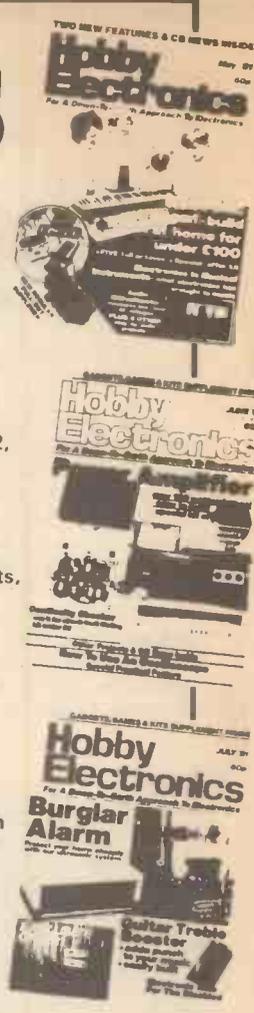Cheques and Postal Orders should be made payable to ASP Ltd.



FORWARD BIAS

Questions, answers and errata from readers and writers.

Telephone Timer

The Good News At Last

We have already apologised to readers for the regrettable failure of this project and announced our intention to correct the many design faults in it. The prototype *did* work and it was assumed that the circuit diagrams and PCB foil patterns supplied related to the working prototype, but it seems now that this was not the case. When we checked we found so many faults that the only recourse was to re-work the design and make new PCB foil patterns to ensure that it worked as described.

This task has been completed and all elements checked, double checked and checked yet again: not only does it work, but the circuit and PCB patterns exactly conform to the new prototype.

These new PCBs are now available and will be sent free of charge to any reader who sends us his old Telephone Timer PCBs together with an SAE adequate to cover the return postage (the boards are identical in size). This free replacement service is available only to readers who return their old boards to the HE editorial office (remember to remove at least the expensive components before you do!). First-time builders of the project must obtain their PCBs through our PCB service in the usual way.

We apologise again to readers both for the faults in the original project, which should have been spotted, and for the length of time it has taken us to correct matters: however we felt it was better to get it right the second time since we didn't the first.

We will be contacting all readers

who have written concerning the Telephone Timer project to ensure that they have the opportunity to successfully complete the project. Ample time will be allowed for other, less demonstrative readers to exchange their PCBs, but we regret that the free replacement offer cannot be maintained indefinitely: it closes without fail on 9th December 1983 and old boards received after that date will not be exchanged.

If any reader is either unable or unwilling to strip down the old boards, we will supply a new PCB component overlay and circuit to enable the necessary changes to be made, but we do not recommend this. Because of the complexity of the design and the faults, a large number of track cuts and bridges are required and such a highly modified PCB cannot be expected to operate reliably. We will, however, supply the modifications notes to any reader who insists and encloses an SAE with his demand.

HE DigiTester

Nearly The Good News

This project is a good example of a design that looked good on paper but completely failed to work in practice. The situation was compounded when the original author was transferred overseas, leaving us with a handful of notes and a cover project to complete!

Once more the project has had to be re-worked, practically from scratch, and although not yet finished work is proceeding rapidly so that we are confident that the Digital Test Unit, as we have re-named it, will be ready for publication shortly.

Hobby 'Scope

No Good News Here

We are currently pursuing every avenue in our efforts to complete this outstanding project. The Hobby 'Scope was offered to us, accepted and commenced in the June 1983 issue: it will be completed.

The Big Ear

Good News To Come

This project has proved unreliable, when made up by large numbers of readers, because of variations in component tolerances — particularly varying IC specifications (we'd like to design all our projects around MILSPEC components, which would guarantee reliable performance, but they do tend to be somewhat expensive...)

However, we have recently commissioned a modification to the circuit which should take care of the problem, so look out for it on this page, sooh.

Bat Light

Good News And Bad News

There were three errors in the published project: R12 was omitted from the component overlay; it should go between the two 'spare' pads that are between the supply voltage connections. The other two errors were in Figures 1a and 2 but since the PCB and overlay are otherwise correct, the project will work if it is constructed according to Figure 3, with R12 included.

All three corrections will be published in next month's Hobby Electronics.

COLLECTED BOOBS

Continuing excerpts from the Hobby Electronics Errata Box.

Short Circuit: Guitar Practice Amplifier (HE August '79)

On the Circuit Diagram, the +9V connection should be to pin 2 of IC1 and not pin 3 as shown.

Home Security System (HE August '79)

Figure 6: There is a track missing from the PCB for the siren. Link the junction of D1 and D2 to the adjacent pad where the 12V connection is made.

Figure 2: At the lower left corner of the Overlay, the wire marked Terminal Block 2 from R2 should be labelled Terminal Block 1. The OV connection to

Terminal Block 2 has not been shown — take it from any convenient point on the OV track.

Miniboard Projects (HE November '79)

This article suffered from incorrect page layouts. To correct these, swap over the Circuit Diagram. Figure 1 on page 21 and Figure 1 on page 27, and swap over the captions for Figure 1 on page 21 and Figure 1 on page 23.

All the circuits and Parts Lists will now make sense.

Figure 3, page 22: On the component overlay, the resistor labelled R6 is actually R4.

Guitar Tuner (HE November '79)

Figure 1: C1 should be 0.μF as in the Parts List, not 1μ0.



Figures 2 and 3: There should be a link from IC1 pins 8 and 9 to pin 7. C2 and R2 are transposed, but that won't affect operation.

Parts List: R3 should be increased to 100R to reduce current consumption.

R2D2 Radio (HE November '79)


Circuit Diagram: Q1 emitter should go to OV; R5 should connect to the junction of C2, R1 and C3.

GET BIG POWER

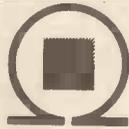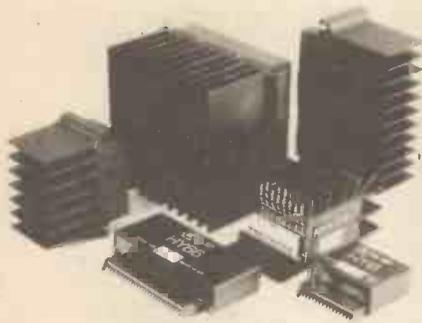

Modular Amplifiers the third generation

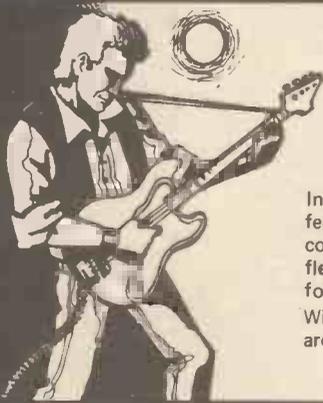Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
HY30	15	4-8	0.015%	<0.006%	± 18	76 x 68 x 40	240	£8.40
HY60	30	4-8	0.015%	<0.006%	± 25	76 x 68 x 40	240	£9.55
HY6060	30 + 30	4-8	0.015%	<0.006%	± 25	120 x 78 x 40	420	£18.69
HY124	60	4	0.01%	<0.006%	± 26	120 x 78 x 40	410	£20.75
HY128	60	8	0.01%	<0.006%	± 35	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	± 35	120 x 78 x 50	520	£25.47
HY248	120	8	0.01%	<0.006%	± 50	120 x 78 x 50	520	£25.47
HY364	180	4	0.01%	<0.006%	± 45	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	± 60	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15V/ μ s. Rise time: 5 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz >400.

PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre amp	As HY66 less tone controls	20mA	£14.20

Most pre amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards: For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83
PSU 42X	1 x HY128	£15.90
PSU 43X	1 x MOS128	£16.70
PSU 51X	2 x HY128, 1 x HY244	£17.07

Model Number	For Use With	Price inc. VAT
PSU 52X	2 x HY124	£17.07
PSU 53X	2 x MOS128	£17.86
PSU 54X	1 x HY248	£17.86
PSU 55X	1 x MOS248	£19.52
PSU 71X	2 x HY244	£21.75

Model Number	For Use With	Price inc. VAT
PSU 72X	2 x HY248	£22.54
PSU 73X	1 x HY364	£22.54
PSU 74X	1 x HY368	£24.20
PSU 75X	2 x MOS248, 1 x MOS368	£24.20

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
MOS128	60	4-8	<0.005%	<0.006%	± 45	120 x 78 x 40	420	£30.41
MOS248	120	4-8	<0.005%	<0.006%	± 55	120 x 78 x 80	850	£39.86
MOS364	180	4	<0.005%	<0.006%	± 55	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice). Slew rate: 20V/ μ s. Rise time: 3 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 100KHz. Input sensitivity: 500mV rms. Input impedance: 100K Ω . Damping factor: 100Hz >400.

'NEW to ILP' In Car Entertainments

C15
Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use. Robust construction. **£9.14 (inc. VAT)**

Mounts anywhere in car. Automatic switch on. Output power maximum 22w peak into 4 Ω . Frequency response (-3dB) 15Hz to 30KHz, T.H.D. 0.1% at 10w 1KHz S/N ratio (DIN AUDIO) 80dB, Load Impedance 3 Ω . Input Sensitivity and Impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω . Size 95 x 48 x 50mm. Weight 256 gms.

C1515
Stereo version of C15. **£17.19 (inc. VAT)**

Size 95 x 40 x 80. Weight 410 gms.

WITH A LOT OF HELP FROM ILP ELECTRONICS LTD

PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.



Hi Fi Separates

UC1 PRE AMP UNIT: Incorporates the HY78 to provide a "no frills", low distortion, (<0.01%), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

POWER AMPS: The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.

Power Slaves

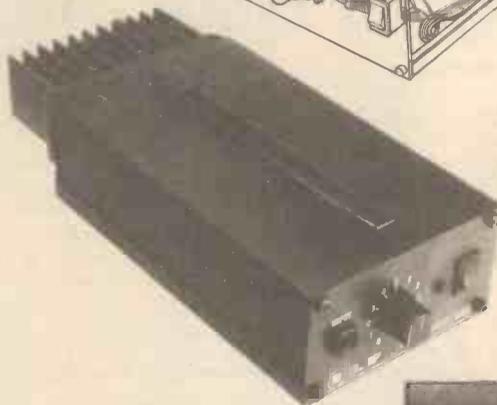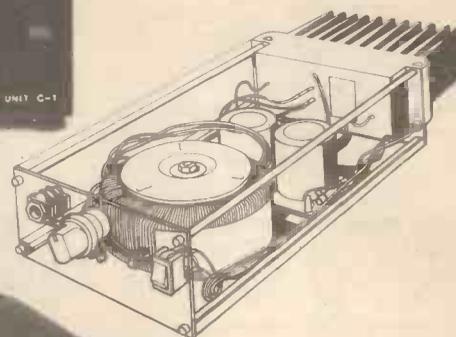Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.



TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd, if sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED

UNICASES

HiFi Separates					Price inc. VAT
UC1	Preamp				£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	HiFi	£54.95
UP2X	60W/4Ω	Bipolar	Mono	HiFi	£54.95
UP3X	60W/8Ω	Bipolar	Mono	HiFi	£54.95
UP4X	120W/4Ω	Bipolar	Mono	HiFi	£74.95
UP5X	120W/8Ω	Bipolar	Mono	HiFi	£74.95
UP6X	60W/4-8Ω	MOS	Mono	HiFi	£64.95
UP7X	120W/4-8Ω	MOS	Mono	HiFi	£84.95
Power Slaves					
US1X	60W/4Ω	Bipolar	Power	Slave	£59.95
US2X	120W/4Ω	Bipolar	Power	Slave	£79.95
US3X	60W/4-8Ω	MOS	Power	Slave	£69.95
US4X	120W/4-8Ω	MOS	Power	Slave	£89.95

Please note X in part number denotes mains voltage. Please insert 'O' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.). All units except UC1 incorporate our own toroidal transformers.



Post to: ILP Electronics Ltd., Freepost 4, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England. Telephone: (0227) 54778. Technical: (0227) 64723. Telex: 965780.

Please send me the following _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

Sound Pressure Level Meter

For those wishing to meet their sound, HE sounds out the meter — an easily calibrated Sound Pressure Level Meter, this is.


James E. Aman

The HE Sound Pressure Level Meter has been designed to provide a modestly priced and — most important — easily calibrated instrument for the measurement of sound levels in the range of 40 to 110 dB SPL. The range of sound pressure levels encountered in normal everyday living varies from about 50dB to around 100dB SPL (Figure 1), so the HE SPL meter is quite adequate for normal purposes, such as setting up a hifi system using a graphic equaliser and the SPL meter to check that the system is producing equal sound levels at all frequencies in the audio band. You can also use it for measuring the noise level from a neighbour's party before calling in the SAS!

On average the human ear can detect sound levels over a truly astounding range, from 0.0002 microbars up to 200 microbars, in fact (for comparison, the atmospheric pressure at sea level is 1,000,000 microbars). That is a range exactly of one million to one, and such large ratios are usually expressed as a logarithmic ratio with respect to an agreed reference level; in sound level measurement, the agreed reference level is 0.0002 microbars, corresponding to 0dB Sound Pressure Level (SPL). This level is also known as the Threshold Of Hearing and at the other end of the scale, around 120dB SPL, is the Threshold Of Pain, where a sound is so intense as to cause physical discomfort and possible injury. The level which is actually painful is very much an empirical level, different with different people, but 120dB SPL will cause degradation of hearing.

Traditionally the problem with SPL meters has been to devise a circuit which produces an accurate electrical analogue of the sound level, and then to calibrate a meter scale to accurately reflect changes in the sound pressure level. Normally the scale is logarithmic, since this is the only way to compress huge ratios into a meaningful scale (imagine a meter intended to read units from 0 to 1,000,000; that's an awfully long scale you've got there!)

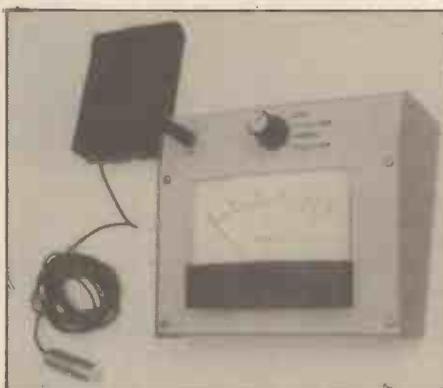The first problem is solved relatively easily by using a standard, known (but



inexpensive) microphone with a reliable linear response; that is, a given increase in the sound pressure level will produce a known increase in the microphone output.

The second problem is solved in a very radical manner, by using a digital integrated circuit to compress the linear scale of 1,000,000: 1 into a logarithmic scale ranging from 40 to 110dB SPL. The circuit, as you will see, consists of a switched range linear amplifier to boost the microphone signal; a precision rectifier to peak-detect the signal, and a logarithmic 30dB display driver coupled to a linear motor; the LM3915 LED bar-graph driver is used here as the linear answer to logarithmic metering! Now read on . . .

Sound Circuits

Sound is picked up by an electret condenser microphone, which produces a very strong output to give a good signal-to-noise ratio and freedom from hum and interference. This is fed to the non-inverting input of IC1 via a fixed attenuator consisting of R1 and R2, to reduce the signal to a manageable level.

IC1 is wired as a switched-gain non-inverting amplifier. The feedback around the IC is taken via SW1 so that three different gains are available; thus the sensitivity is selectable by plus or minus 20dB. The four positions switch from Off to Scale -20dB, Normal Scale and Scale +20dB.

The supply rails to IC1 are isolated from the main supply by two transistors, Q1 and Q2. The value of


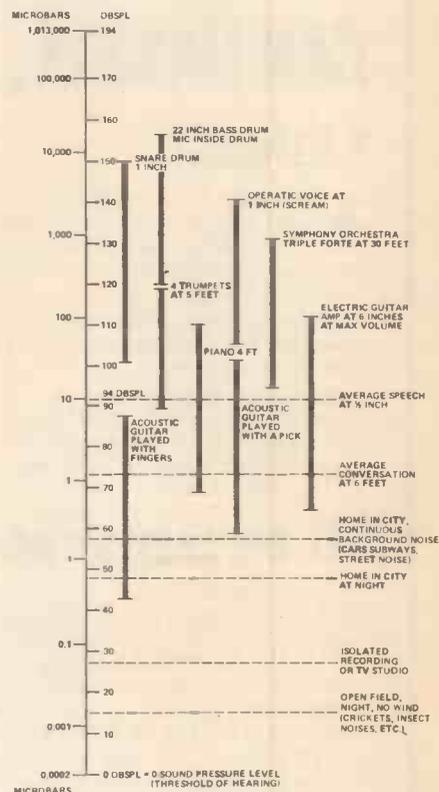


Figure 1. A sample of sound pressure levels encountered in everyday living (if you happen to live next door to a recording studio.).

the capacitors connected between base and earth are effectively multiplied by the beta (DC current gain) of the transistors, typically 100 for the types used, forming smoothing capacitors of around .02 farads. These keep the supply to IC1 rock steady, even when IC4 draws varying current, resulting in a very stable amplifier.

The output of IC1 is fed to IC2 for further amplification; it goes via PR1, which is used to set the overall system level.

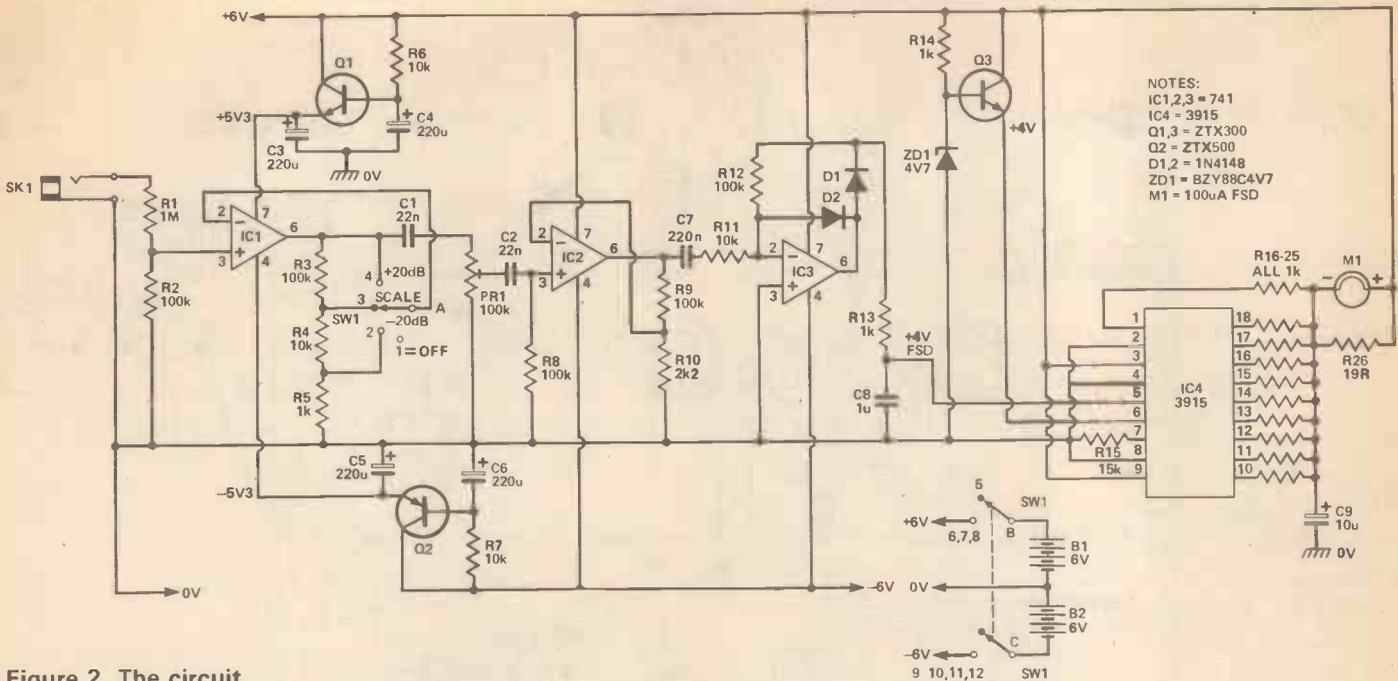IC3 is connected as a precision half-wave rectifier, where the threshold voltage (OV6) of the two diodes is effectively reduced by the equivalent of the open-loop gain of the op-amp. The precision rectifier is set-up as a peak detector; filter capacitor C8 is charged up on each positive peak, via R13, then discharges via R13 and R12.



NOTES:
 IC1,2,3 = 741
 IC4 = 3915
 Q1,3 = ZTX300
 Q2 = ZTX500
 D1,2 = 1N4148
 ZD1 = BZY88C4V7
 M1 = 100uA FSD

Figure 2. The circuit.

This arrangement gives the fast attack and slow decay times required for peak detection; to convert to average-reading, the values of R12 and R13 should be reversed, ie R12 should be 100k and R13, 1k.

The signal at the junction of R13 and C8 is a DC level, and this is fed to pin 5 of IC4, and LM3915.

This IC is normally used to drive an array of LEDs in either dot-mode, where only one LED is illuminated at one time, or in bar-mode, where the line of LEDs light up successively. It converts an analogue input voltage to directly drive up to ten LEDs, with the amplitude of the input determining the number of LEDs (in bar-mode) illuminated.

[Internally the LM3915 is very similar to the array of comparators driving the LEDs in this month's Gripometer project - See Figure 4, overleaf.]

Linear To Log

The LM3915 has logarithmic characteristics; each output is turned on by a successive 3dB increase in the input amplitude, which is exactly the required relationship for measuring sound pressure levels that vary linearly by a factor of over one million! Instead of tediously having to calibrate a logarithmic meter scale, this IC converts quickly and simply from linear scale to logarithmic.

Each output, which goes 'low' when it is 'on', normally drives an LED connected to V+, and for this reason the outputs are all open-collector, or 'uncommitted'; thus if each output is simply connected to V+ via individual resistors only, the total current that flows from the supply rail is the sum of the currents flowing into each output. In the circuit, the outputs are summed in resistors R16-25, while the total current is measured by M1.

Parts List

RESISTORS (All 1/4 watt 5% carbon)		SEMICONDUCTORS	
R1	1M	IC1, 2, 3	LF351
R2, 8, 9, 12	100k		JFET op-amp
R3	100R	IC4	3915
R4, 6, 7, 11	10k		log display driver
R5, 13, 14	1kR	Q1, 3	ZTX300
R10	2k2		NPN transistor
R15	15k	Q2	ZTX500
	(see text)		PNP transistor
R16-25	1k	D1, 2	1N4148 etc
R26	19R	ZD1	BCY88C4V7
	(see text)		
CAPACITORS		MISCELLANEOUS	
C1, 2	22n polyester	SW1	3-pole 4-way rotary (see Buylines)
C3, 4, 5, 6	220u 16V axial electro	SK1	3.5mm (1/4") mono
C7	220n polyester	M1	100uA panel meter
C8	1u polycarbonate		Altai EM-104 microphone; case; PCB; 2 x HP7 battery holders, PP9 clips; wire, solder, nus and bolts etc.
C9	10u 16V axial electro	BUYLINES	page 34

And since each output represents a 3dB increase at the input, the meter reading corresponds to the input level, on a logarithmic scale!

The outputs from IC4 are from pins 1 and 10-18; pin 9 is connected to V+ and sets the IC to bar-graph mode, so that as each output becomes active the current it draws is added to the others. Pin 7 is the 'reference output' normally used to set the size of the 'step' at which successive outputs turn on; it is not used for this purpose here, but the value of the resistor connected between pin 7 and 0V also sets the maximum current available to each output, so that R15 limits the total current to around six milliamps (corresponding to 90dB SP on the normal scale).

The reference voltage needed to set the step size for this application is 4V, provided by the emitter follower/Zener diode circuit consisting of Q3 and ZD1; the 0V base-emitter drop of Q3 is neatly offset by using a 4V7 Zener. The reference voltage is connected to the high end of the internal divider chain at pin 6, and the low end of the chain is connected to 0V, so that the maximum input voltage the IC can accept for full output is likewise, 4V. Pin 8, the 'reference adjust' input, is not used and is connected to 0V.

The specified meter is a 100 microamp type, which would not respond with pleasure to a maximum input sixty times higher, therefore it is shunted by R26 to increase the current range.

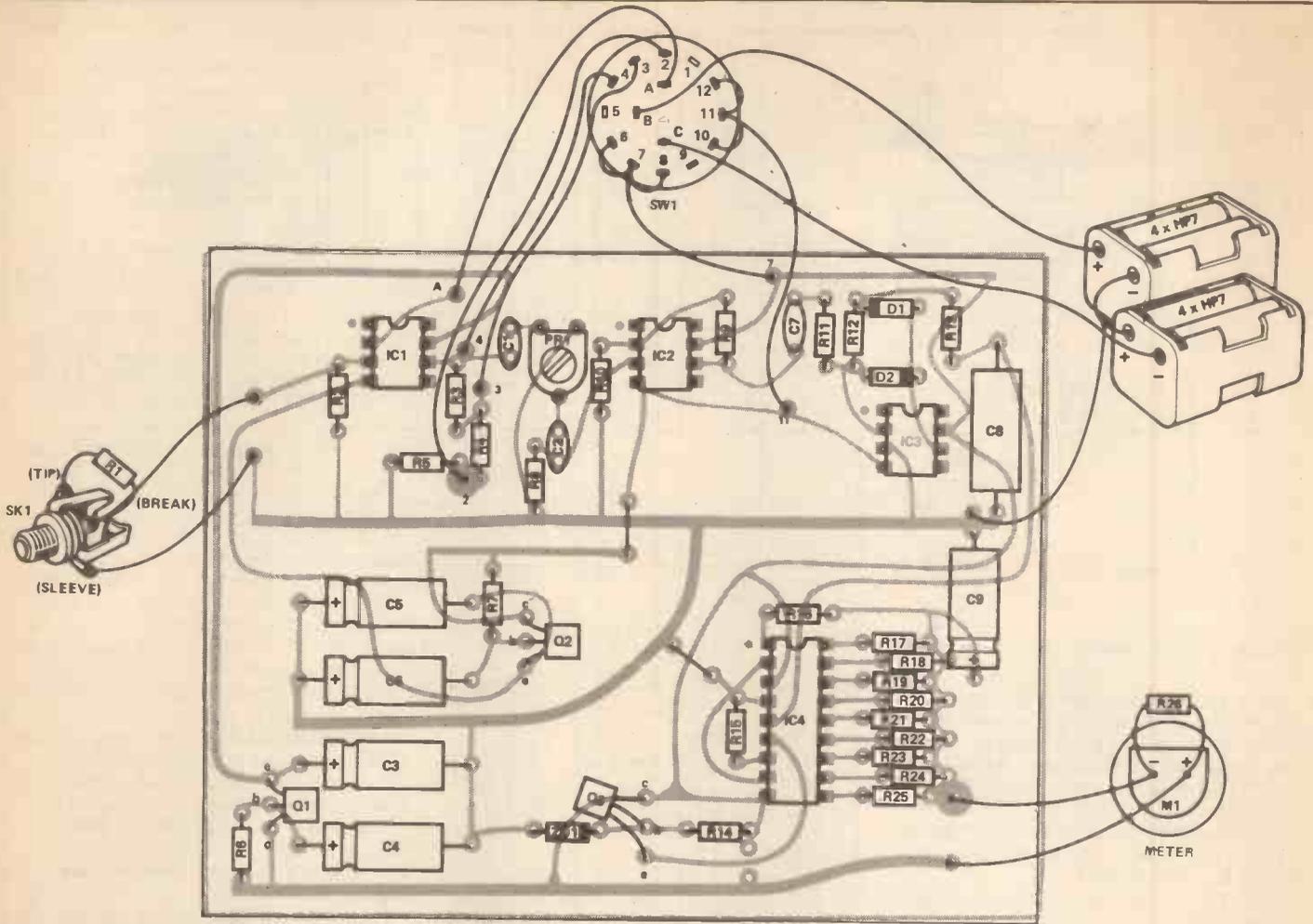


Figure 3. The PCB and components for the Sound Pressure Level Meter.

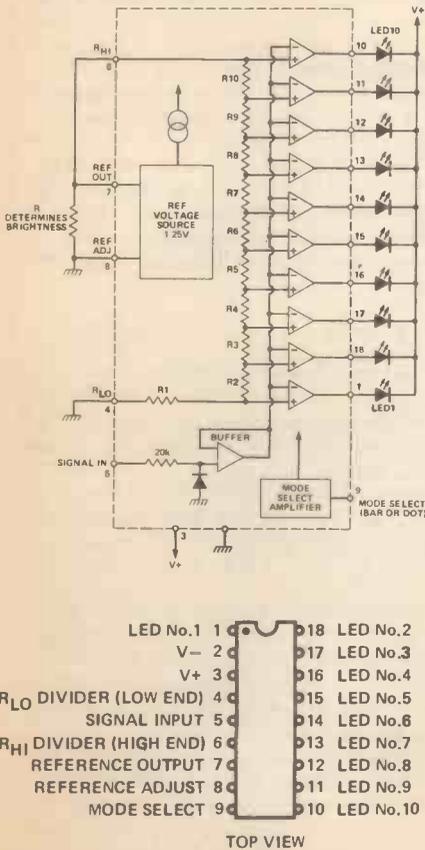


Figure 4. Inside the IC4, the LM3915 (see page 15 above).

Construction


Assembling this project should present no unusual problems. The PCB together with the component layout diagram (Figure 3) facilitate construction.

When wiring the microphone jack to the board, a twisted pair or screened lead should be used to minimise hum problems and R26 should be mounted directly on the jack socket. The one specified has an extra shorting contact which opens when a jack is inserted and this spare compact can be used to mount the R2-end of R1.


The meter shunt resistor R26 is made up from a 22 ohm resistor in parallel with 150 ohms, and these should be soldered across the meter terminals.

The range/power-on switch, SW1, should present few problems provided the specified type is used; it is a CK 3-pole, 4-way switch, readily available from most suppliers, and all the pins are numbered so they are simply connected to the numbered points shown in the overlay diagram.

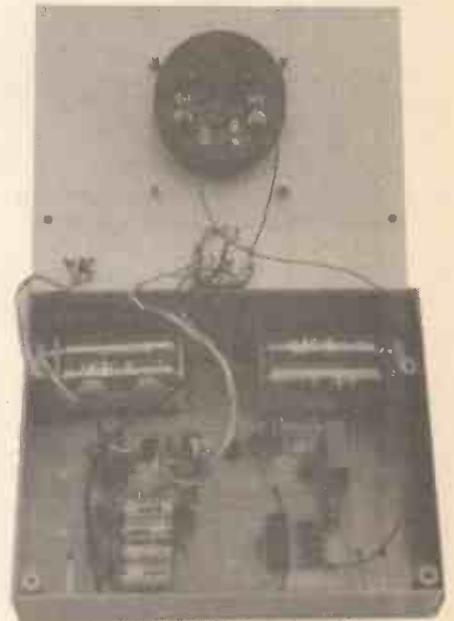Please note that the circuit is intended for use with an Altai EM-104 electret condenser microphone, which has a high level output and an exceptionally flat response for its type. They are readily available, but if another type is used then the calibration becomes a matter for the dedicated experimenter!



SW1 POSITION	IC1 PIN 6
SCALE -20dB	150mV p-p
NORMAL SCALE	15mV p-p
SCALE +20dB	1.5mV p-p

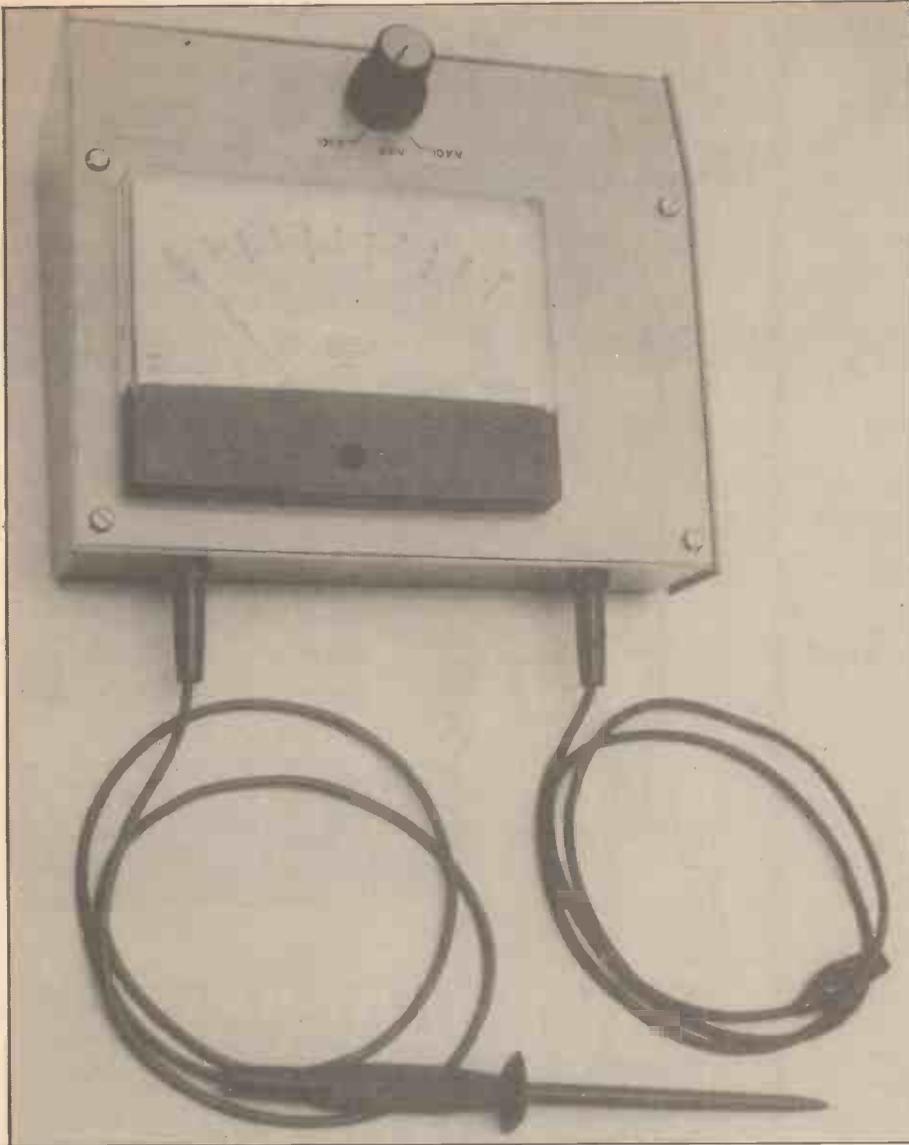

Calibration

With most sound pressure level circuits, accurate calibration requires an extensive range of test equipment and near-perfect acoustic conditions] but not this time! So long as the specified microphone is used, calibration of the HE SPL Meter is simplicity itself. For best results, an oscilloscope should be used, but an ordinary multimeter will do if less accuracy is acceptable.

First disconnect the microphone from the input jack and connect instead the output of an audio signal generator; the signal should be 15mV peak-to-peak at a frequency of $\approx 1\text{kHz}$. Now, with an oscilloscope if one is available, observe the output of IC1 at pin 6; it should follow the readings given in Table 1 as the range switch SW1 is rotated.

Leave the range switch on Normal Scale, move the 'scope probe to monitor the output of IC2 and adjust PR1 to bring this to 500mV p-p. Now you should be able to observe 2.5VDC at pin 5 of IC4 and a meter reading of 84, equivalent to 84dB SPL.

If the needle fails to come up to 84 — don't despair! It can be "tweaked in" by adjusting the value of either R15 or R25; reducing the value of R15 increases the current drive to the meter while increasing the resistor reduces the current; making R26 lower reduces the current but increasing it makes the meter read higher.

For those purists who doubt the effectiveness of the circuit, Table 2 gives the voltages on pin 5 of IC4 for meter readings at selected points (the meter current is also given to allow a different meter to be used, if necessary — the value of the shunt, R26, will need to be re-calculated though).

The simple circuit of Figure 5 can be connected between pin 5, IC4 and OV, first lifting R13, to check the calibration of the IC4 circuit against: the values given in Table 2, if desired.

Scopeless

If an oscilloscope is not available, the SPL meter can be calibrated with a multimeter set to the AC volts range. (*Pop Amp No. 9, the High Impedance Millivoltmeter, is ideal for this purpose*).

With the meter set to its most sensitive AC range (eg 3V FSD), connect it across the signal source as shown in Figure 6 and adjust the generator for a reading of 1VAC; then with the attenuator network shown, the required 15mV p-p can be applied to the input for a reading of 2.5VDC at IC4 pin 5, and a meter reading of 84dB SPL.

The meter scale face plate should be removed by its two screws and rescaled from 60 to 90dB across its 11 graduations, ie 60, 63, 66, 69, 72, 75, 78, 81, 84, 87, 90dB SPL.

Table 2

PIN 5 (V)	METER READING	CURRENT
4.0	90dB	6mA
2.8	87	5.4
2.0	84	4.8
1.4	81	4.2
1.0	78	3.6
0.7	75	3.0
0.5	72	2.4
0.36	69	1.8
0.25	66	1.2
0.17	63	0.6
0.	60	0.0

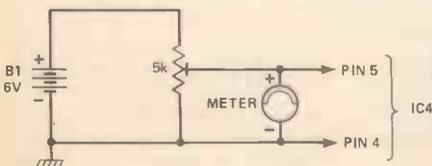


Figure 5. This circuit can be used to calibrate the IC4 circuit.

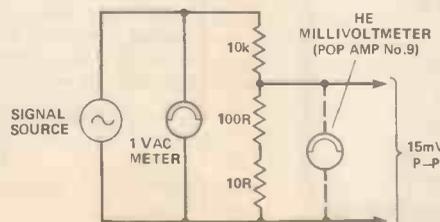


Figure 6. Using a millivoltmeter to calibrate the SPL meter.

ELECTRONI-KIT

FX-COMPUTER



Teach-Yourself Computer and Electronics Construction Kit

A complete introduction to the "How, Why and What" of Computers and Electronics in the most practical way ever devised

THE KIT IS BATTERY-OPERATED AND COMPLETELY SELF-CONTAINED. NO TELEVISION OR OTHER EQUIPMENT IS REQUIRED. VERY EXTENSIVE MANUALS ARE INCLUDED

Ministry of Science and Technology, Japan — Prize Winning Product

The **FX-COMPUTER** is the ideal introduction to the study and understanding of computers and electronics. The kit offers remarkable versatility because the components are interchangeable and circuits are constructed by simply plugging specified components into the board provided in accordance with the instruction manuals. You quickly understand the principles involved and new circuits can be easily devised, built and dismantled. No soldering or wiring is involved, no tools are required; the components themselves complete the circuits.

No previous knowledge is required — very extensive educational manuals have been provided by English experts in computers and electronics. Working through the manuals you will soon be able to write programmes and "run" them and understand how computers work.

The following are just a few of the programmes in the Computer Manual (there are too many to list here) and also a few of the projects in the Electronics Manual:

How to instruct the Computer and Store Information into Memories. Use of different Instructions and Programming Techniques. Adding, subtracting, multiplying, dividing, averaging, counting up, counting down, etc. etc. — in Decimal and Hexadecimal. Converting Hexadecimal to Decimal, storing Random Numbers. Games: Tennis, Catch-the-Rat, Gun Fight, Slot Machine, etc. Using the Computer as a Musical Organ, storing and playing-back tunes, etc. **OVER 100 PROGRAMMES SHOWN IN THE COMPUTER MANUAL PLUS EXPLANATIONS AND DEMONSTRATIONS OF ALL TECHNICAL TERMINOLOGY.**

Electronic Components and How they Work — batteries, conductors, resistors, capacitors, diodes, transistors, lamps, photo-electric devices (CdS cell is included in the kit), oscillators, burglar alarms, control systems, organ, lie detector, etc., etc. **OVER 65 PRACTICAL WORKING PROJECTS SHOWN IN THE ELECTRONICS MANUAL.**

All this is in ONE kit, costing about the same as the cheapest "Basic" ordinary Computer

The price is only £69.95 plus £3.00 P&P (overseas rates quoted on request)

TRADE & EDUCATIONAL ENQUIRIES WELCOMED

Send cheque/PO/Access/Barclaycard to **DEPT. HEFX. Electroni-Kit Ltd**

It's not JUST a computer!

**ELECTRONI-KIT LTD.
388 ST. JOHN STREET
LONDON, EC1V 4NN (01-278 0109)**

The MIGHTY MIDGETS SOLDERING IRON 18 WATT SUMMER

SPECIAL OFFER

£4 inc v.a.t & post

12 MONTH GUARANTEE

usual price £5.46 + 35p post

S & R BREWSTER LIMITED
86-88 UNION ST. PLYMOUTH PL1 3HG

PLEASE QUOTE YOUR NUMBER WHEN ORDERING

OFFER ENDS 30/9/83

0752 665011

RECHARGEABLE BATTERIES

AND CHARGERS

PRIVATE OR TRADE ENQUIRIES WELCOME
FULL RANGE AVAILABLE
SEND SAE FOR LISTS

£1.45 for booklet "Nickel Cadmium Power"

● TRADE PRICES FOR SCHOOLS & COLLEGES ●

SANDWELL PLANT LTD

2 Union Drive, Boldmere, Sutton Coldfield,
West Midlands 021-354 9764

After Hours: Lichfield 57977

Now open Saturday mornings

BECOME A RADIO AMATEUR

Train now for the Radio Amateur Licence examination. No previous knowledge needed, only a few hours per week of home study for 3 to 6 months. Post coupon now for details or tel. 0734 51515 (24 hr service)



British National Radio & Electronics School Reading, Berks. RG1 1BR



FREE brochure without obligation from:—
British National Radio & Electronics School
READING, BERKS. RG1 1BR

Name

Address

HE/9/846

BLOCK CAPS PLEASE

ADDITIONS TO OUR LIST

RADIO MOBILE CAR RADIO SPEAKERS

9" x 4" 4 ohm 5 watt — £1.70. 6" x 4" 3 ohm 4 watt — £1.35; 6" x 4" 4 ohm 4 watt — £1.15. 6" x 4" 16 ohm 5 watt — £1.15; 5" round 8 ohm 10 watt — £2.30. 6 1/2" round extra thin for door or back shelf. In fact these are only 1 1/2" thick 18 ohm 5 watt — £1.75. 5" round 18 ohm 5 watt chassis size 5 1/2" square (approx). — £1.15; 5" round 4 ohm 5 watt chassis size 5 1/2" square (approx). — £1.15; 5" round 4 ohm 6 watt with built in tweeter — £1.15. 9" x 3" 8 ohm £1.15.

IMPORTANT NOTE: The speaker prices above do not include postage but 10 or more speakers are post free — otherwise add £1.50 per order.

STABILISED POWER SUPPLY (Mains Input)

By LAMDA (USA) — Ideal for computer add-ons, d.c. output. Regulated for line volts and load current. Voltage regulation, 1% with input variations up to 20% — load regulation 1% from no load to full load — or full load to no load. Complete in heavy duty case — Models available: 5v - 6A £17.25, 5v - 9A £23. 12v - 1.5A £13.25, 15v - 1.2A £13.25, 24v - 2A £23.

PREPARED APPLIANCE LEADS

Buy these, they will save you time and money. Prices are for small quantities but if you are buying £100 lots or more — halve the prices. Twin circular, white, 1/2mm length 54" — 23p; 3 core circular, white 99" — 1.25mm — 57p; Twin circular black 77" — 5mm — 23p; 3 core circular, black 88" — 5mm — 35p; 84" — 5mm 46p; Twin circular black 114" — 1.25mm — 69p. Twin circular white 200" — 75 fitted 2 pin continental plug one end — 57p; 3 core circular white 54" — 75mm core sizes fitted continental two pin and earth plug one end and new type 3 flat pin appliance connector at other end — 75p.

MINIATURE TOGGLE SWITCHES

As used on TV cameras and other lightweight equipment. American made by the Arrow Company. Arrow ref. TCH3E Single pole changeover, centre off — 46p. Arrow ref. TSH3PCL Single pole changeover PCB mounting — 46p. Arrow ref. TCGM Double pole changeover, centre off — 69p.

REED RELAY KIT

High Inductance coil, moulded to take 4 reeds, operated by three volts DC or 12 ma. Could be used to close 4 circuits, or with the external magnets supplied, you could have two normally open, i.e. two changeovers. An exceptional bargain at 99p for the coil — 4 reeds and 2 magnets.

ROCKER SWITCHES

Standard size fit 11.5 x 28mm cut out. Single pole on/off — 23p; Single pole changeover 28p; Single pole changeover with centre off — 30p; Single pole on/off with neon — 46p, for double width cut out DpSt 36p, DpDT 46p.

NICAD BATTERY CHARGERS

This, although intended to charge button cells, bring leads from the contacts and then it will suit almost any Nicad battery, charge rate approximately 15mA but easy to vary.

MIXER MOTOR

If this had a case around it, it would be a complete mixer as it has a speed control switch giving three changes of main speed and it also has a gear box with two sockets for paddles. Three lower speeds are available from these sockets. £3.45 — post 60p.

LOW VOLTAGE SWITCH

Cover 1 1/2" diameter, the cover unscrews to enable the switch to be fixed and to keep the contacts covered, contacts look capable of up to 10 amps. 23p.

PILOT BULBS

Standard round 11mm 6.5v .3a by Philips. Box of 10 price 50p.

12 volt MOTOR BY SMITHS

Made for use in cars, etc. these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3" dia. They have a good length of 1/2" spindle — Price £3.45. Ditto, but double ended £4.25. Ditto, but permanent magnet £3.75.



EXTRA POWERFUL 12v MOTOR

Made to work battery lawnmower, this probably develops up to 1/2 hp., so it could be used to power a go-kart or to drive a compressor, etc. etc. £7.95 + £1.50 post. (This is easily reversible with our reversing switch — Price £1.15).

MAINS MOTORS

We have very large stocks of motors from 2 watts to 1/2 hp. Most at a price well below cost, let us know your requirements. Some new ones just arrived.

67 R.P.M. Motor: 1/10 hp. reversible mains operated split phase motor with gear box — shaft fitted with chain sprocket £11.50 plus £2 post.
100 R.P.M. Motor: 1/16 hp. Mains driven reversible motor with gear box, 1/2" shaft from gear box — Very powerful £16.50 plus £3 post.
BALANCED MOTOR: Disc or tape drive motor 1500rpm reversible — mains operated, 3" dia 2 1/2" long with good length 3/8" spindle £4.60 plus 80p post.

CROSSOVER NETWORKS

2-way: 4 or 8 ohm impedance — power input up to 25W, crossover frequency 2kHz with wiring dig. 87p each.
3-way: 4 or 8 ohm — power input up to 60W, crossovers at 700kHz and 3500kHz with wiring diagram. £1.15.

— BARGAIN OF THE YEAR —

The AMSTRAD Stereo Tuner.

This ready assembled unit is the ideal tuner for a music centre or an amplifier. It can also be quickly made into a personal stereo radio — easy to carry about and which will give you superb reception.

Other uses are as a "get you to sleep radio", you could even take it with you to use in the lounge when the rest of the family want to view programmes in which you are not interested. You can listen to some music instead.

Some of the features are: long wave band 115 — 270 KHz, medium wave band 525 — 1650 KHz, FM band 87 — 108MHz, mono, stereo & AFC switchable, tuning meter to give you spot on stereo tuning, optional LED wave band indicator, fully assembled and fully aligned. Full wiring up data showing you how to connect to amplifier or headphones and details of suitable FM aerial (note ferrite rod aerial is included for medium and long wave bands. All made up on very compact board.

Offered at a fraction of its cost: **only £6.00** + £1.50 post + insurance.

THIS MONTH'S SNIP

A PRESTEL UNIT, complete except for 6 plug-in IC's — so far as we know the unit would work once the missing IC's are fitted. Price: £19.75 + £2.00 Post. Contains all the items listed below.



VIEWDATA EQUIPMENT

ORACLE VB 100 PCB This is the heart of many viewdata systems, including the Prestel Unit which we are currently selling. This board uses 25 I.C.'s, 5 transistors, 2 crystals and very many other components. It has a TV aerial input and a TV UHF modifier (AZTEC UM 1233). We offer this board, new, unused and complete except for 6 of the 25 I.C.'s at £5.75. The plug in holders for the missing I.C.'s are on the board wired ready to receive them.

MINIKEY SERIES KL This is an American made membrane keyboard with silver contacts as used on Prestel to dial into the British Telecom phone system. It is really minimalist, only 60mm x 65mm x 5mm thick. It has 16 press buttons, giving standard 0-9 numbers and ABCD facilities. There are two other buttons engraved asterisks. This is an extremely well made board. £4.60.

TELEPHONE LINE TERMINATION UNIT As used with Prestel but undoubtedly suitable for other applications. Important components are phone line isolation transformer and 3 Clare Reed Relays. All mounted on a pcb with I.C. and other components P.C.B. size approximately 7" x 1 1/2" — £3.45.

VOLTAGE STABILISED POWER SUPPLY As used with Prestel this has a mains input transformer with a 13v - 0 - 13v 20 watt mains transformer. Rectifiers and semi-conductors all mounted on P.C.B. size approximately 4 1/2" x 2". The stabilised DC output from this is — 27v - 12v - 0 - +10 +12v +27v. Price £4.60.

INSTRUMENT CASE As used with the Prestel unit this comprises an aluminium chassis and a moulded front plastic cover secured to the chassis by self-tapping screws. Overall size approx 12" x 10" x 2 1/2" deep. On the front is fitted the minkeyboard as described above and although originally intended for Prestel, this case should have and other uses including telephone answering machine, etc. Price £5.75 + £1.50 post.

X-RAY EQUIPMENT

Beautifully made by the American GEC Company. We have a whole range of spares, all unused. **X-RAY TROLLEY** - This could be motorised, mains or battery driven with self retractable flex lead, so it could be used for carrying other main operated equipment which need to be manoeuvred easily in a relatively confined space. Switching and breaking is done from the handle and there is ample room and capacity for heavy transformers and smaller equipment. The overall size of this trolley is approx. 3' x 2' x 3'6". Price £69. **X-RAY HEAD** This comprises the x-ray tube in a radiation proof housing with plug in lead connectors. The tube enclosed in the housing is a hospital size tube and unused and new. Price £69. **EHT TRANSFORMER & RECTIFIER UNIT** We estimate that the output voltage of this is probably 30 or 40 KV. Completely enclosed in an oil filled container, size 12" x 14" x 15". There are four rectifier sections, each using 20 EHT rectifiers connected in series these plug in for ease of replacement. The unit is powered by a 600 cycle supply. Price £69. **600 CYCLE SUPPLY UNIT** Mains operated through a step down transformer, this contains all the electronic components to operate the equipment. Price £57.50.

MINI MONO AMP on p.c.b. size 4" x 2" (app.)

Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £11.95 each, or 10 for £100.



50 THINGS YOU CAN MAKE

Things you can make include: Multi range meter, Low ohms tester, A.C. amps meter, Alarm clock, Soldering iron minder, Two way telephone, Memory jogger, Live line tester, Continuity checker, etc. etc., and you will still have hundreds of parts for future projects. Our 10Kg parcel contains not less than 1,000 items - panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermistors, coils, condensers, resistors, neons, earphone/microphones, nicad charger, power unit, multi-turn pots and notes on the 50 projects.

YOURS FOR ONLY £11.50 plus £3.00 post.

MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument, jewelled bearings - 2000 o.p.v. mirrored scale. 11 instant range measures: DC volts 10, 50, 250, 1000. AC volts 10, 50, 250, 1000. DC amps 0 - 100 mA.



Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test prods and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 60p post and insurance.

FREE Amps range kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

J. BULL (Electrical) Ltd.

(Dept. HE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. Established 30 YEARS

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £12 add 60p service charge. Monthly account orders accepted from schools and public companies. Access & B/card orders accepted day or night. Haywards Heath (0444) 454563. Bulk orders: write for quote. Shop open 9.00 - 5.30, Mon to Fri, not Saturday.

EXTRACTOR FANS

Mains operated — ex-computer.

Woods extractor 5" — £5.75, Post £1.25 6" — £8.95, Post £1.25 5" Planair extractor £8.50, Post £1.25. 4" x 4" Muffin 115v, £4.50, Post 75p. 4" x 4" Muffin 230v, £5.75, Post 75p. 9" American made £11.50, post £2.00. 12 volt 6 1/2" extractor £6.90, post £1.50.



AUTO & ISOLATION TRANSFORMERS

2 KW ISOLATION TRANSFORMER 230v in 230v out with tapped primary and secondary, facilities any voltage changes that might be needed. This is a very heavy transformer, American made but not encased. The terminals are along the top on insulation board panels. Both primary and secondary are split so this could also be used as a 2KW isolation step down transformer. £57.50. Carriage at cost depending upon the distance. This is approx half the regular price.

2 KW AUTO TRANSFORMER Similar type of transformer to the above but has only the one winding. £28.50 + carriage £3.

1 KW ISOLATED AUTO TRANSFORMER It is not generally realised that many of the American made tools intended for 115v, if used on building sites and similar damp conditions must be isolated from the mains for safety reasons, as in many cases the insulation of this equipment is not good enough for 230v. We have American made isolated auto transformers, completely enclosed in sheet metal case with carrying handle with 230v lead and 110v American type plug. Price £46.00 + £4.50 post.

300 WATT AUTO TRANSFORMER completely enclosed, lead for the 230v input, American type plug for the 115v output £6.90 + £1.50 post.

100 WATT AUTO TRANSFORMER not enclosed terminals, output primary with tappings for voltage adjustments. Made to rigid specification for the GPO £4.60 + £1 post.

AMERICAN 2 PIN FLAT SOCKETS for use with these auto transformers — £2.30 each.

3M FACSIMILE EQUIPMENT — send or receive a document in 4 minutes. This equipment is used for sending letters and almost any data through the telephone system — "Mail by Phone". The machines we have are the 3M 600BB with autofeed complete with ansafonettes and connector box. We have three sets of the equipment, it is not old, in fact it was used only for about a year (1980-81), believed to be in good order and certainly in a very good condition — cost new over £10,000. We will accept £500 the lot — buyer to examine and take away on an "as seen" basis.

VENNER TIME SWITCH Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case but we can convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

IONISER KIT Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder — a complete mains operated kit, case included. £11.95 plus £2.00 post.

OTHER POPULAR PROJECTS

- R C Bridge Kit £9.95
- 3 Channel Sound to Light — with fully prepared metal case. £14.95
- Ditto — made up £25.00
- Big Ear, listen through walls £9.50
- Robot controller — receiver/transmitter £9.50
- Ignition kit — helps starting, saves petrol, improves performance £13.95
- Silent sentinel Ultra Sonic Transmitter and receiver £9.50
- Car Light "left on" alarm £3.50
- Secret switch — fools friends and enemies alike £1.95
- 3 - 30v Variable Power Supply £13.80
- 2 Short & Medium wave Crystal Radio £3.99
- 3v to 16v Mains Power Supply Kit £1.95
- Light Chaser — three modes £17.50
- Mullard Unilex HIFI stereo amplifier with speakers £16.75
- Radio stethoscope — fault finding aid £4.80
- Mug stop — emits piercing squawk £7.50
- Morse Trainer — complete with key £2.99
- Drill control kit £3.95
- Drill control kit — made up £6.95
- Interrupted beam kit £2.50
- Transmitter surveillance kit £2.30
- Radio Mike £6.90
- FM receiver kit — for surveillance or normal FM £3.50
- Seat Belt reminder £3.00
- Car Starter Charger Kit £14.00
- Soil heater for plants and seeds £16.50
- Insulation Tester — electronic megger £7.95
- Battery shaver or fluorescent from 12v £6.90
- Matchbox Radio — receives Medium Wave £2.95
- Mixer Pre-amp — disco special with case £16.00
- Aerial Rotator — mains operated £29.50
- Aerial direction indicator £5.50
- 40 watt amp — hifi 20hz — 20kHz £9.50
- Microvolt multiplier — measure very low currents with ordinary multimeter £3.95
- Pure Sine Wave Generator £5.75
- Linear Power output meter £11.50
- 115 Watt Amplifier 5Hz 25kHz £13.50
- Power supply for one or two 115 watt amps £17.50
- Stereo Bass Booster, most items £8.95

COMING SOON TO . . .

Hobby Electronics

THE HE BASIC CIRCUIT SELECTION

A collection of everyday useful circuits that form many of the basic elements of electronic design, presented in conjunction with Bernard Babani (Publishing) Ltd., and illustrated by many practical examples from the pages of Babani books.

AUDIO LEVEL METER

Log your audio levels with our compact meter. It uses an LED bargraph — or a series of individual LEDs, if you prefer — to register the volume level of an audio signal. The design is flexible, so that you can either build it into existing equipment or use it as a stand-alone accessory.

ULTRASONIC INTRUDER ALARM

Designed to register the Doppler shift of reflected ultrasonic sound waves, this unit will detect the slightest movement virtually anywhere in a room. When it does, the ear-splitting alarm is guaranteed to give even the most intrepid intruder a severe shock!

A ZENER DIODE PRIMER

An "A to Z" of Zener diodes: how to design circuits using them and how to ensure that they work as you expect them to!

HP-VOLT METER

DANGER . . . 10,000 Volts!!?

You can be sure, now, with our simple low cost High Voltage Meter. This simple extension to your test bench equipment is designed to put high voltage measurement within the experimenter's pocketbook, and measures voltages up to 10kV without significantly affecting the circuit under test.

Please reserve _____ copies of the October issue of

**Hobby
Electronics**

for
Name

Address

.....

.....



**Hobby
Electronics**

**October issue on sale
at your newsagent
from 9th September.
Place your order now!**

Although these articles are being prepared for the next issue, circumstances may alter the final content.

XK113 MW RADIO KIT

Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires PP3 9V battery. IDEAL FOR BEGINNERS. **£5.00**

HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

TOR300K Remote Control Dimmer **£14.30**


MK6 Transmitter for above **£4.20**

TD300K Touchdimmer **£7.00**

TS300K Touchswitch **£7.00**

TDEIK Extension kit for 2-way switching for TD300K **£2.50**

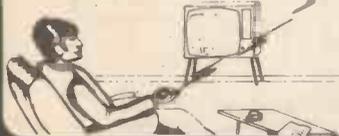LD300K Rotary Controlled Dimmer **£3.50**



DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week

7999

Price **£15.50**

THE JUPITER ACE MICROCOMPUTER

NOW available in stock

uses FORTH which executes about 10 times faster and requires less program memory than a comparable program using basic. Features 8K ROM, 3K RAM, built in speaker, 40 key keyboard and a 32 x 24 line-flicker free display on TV. Comes supplied complete with leads, mains adaptor, a comprehensive easy-to-follow manual on Forth programming + FREE cassette containing 5 sample programs.

ONLY £75.00 (+ £2.00 carriage + VAT)

DRAGON 32 **£143 + £7 carriage**

ORIC 1 **£143 + £2.50 carriage (48K RAM)**

JUPITER ACE SOFTWARE
 J3 SPACE INVADERS **£3.90**
 J4 SWAMP MONSTERS **£3.90**
 J5 DOT MAN **£3.90**
 J14 ASTRO & FLYTRAP **£4.35**

COMPONENT PACKS

PACK 1 650 Resistors 47 ohm to 10 Mohm - 10 per value **£4.00**
 PACK 2 240 x 16V Electrolytic Capacitors 10µF to 1000µF - 5 per value **£3.25**
 PACK 3 360 Polyester Capacitors 0.01 to 1µF/250V - 5 per value **£5.55**
 PACK 4 45 Sub-miniature Presets 100ohm to 1 Mohm - 5 per value **£2.90**
 PACK 5 30 Low Profile IC Sockets 8, 14 and 16 pin - 10 of each **£2.40**
 PACK 6 25 Red LEDs 15mm dia. **£1.25**

3-NOTE DOOR CHIME

Based on the SAB0600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS. Order as XK 102.

£5.00

LCD 3 1/2 DIGIT MULTIMETER

16 ranges including DC voltage (200 mv-1000 v) and AC voltage, DC current (200 mA 10 A) and resistance (0-2 M) + NPN & PNP transistor gain and diode check. Input impedance 10M. Size 155x88x31 mm. Requires PP3 9v battery. Test leads included **ONLY £29.00**

ELECTRONIC LOCK KIT XK101

This KIT contains a purpose designed lock IC, 10-way keyboard, PCBs and all components to construct a Digital Lock, requiring a 4-key sequence to open and providing over 5000 different combinations. The open sequence may be easily changed by means of a pre-wired plug. Size: 7 x 6 x 3 cms. Supply: 5V to 15V d.c. at 40mA. Output: 750mA max. Hundreds of uses for doors and garages, car anti-theft device, electronic equipment, etc. Will drive most relays direct. Full instructions supplied.

ONLY £10.50

Electric lock mechanisms for use with latch locks and above kit **£13.50**

DISCO LIGHTING KITS

DL 1000K

This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control.

£14.60

DL2100K

A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum.

Only £8.00

Optical opto input DLA1

Allowing audio ("beat") -light response. **60p**

DL3000K

This 3 channel sound to light kit features zero voltage switching, automatic level control & built in mic. No connections to speaker or amp required. No knobs to adjust - simply connect to mains supply & lamps. (1Kw/Channel) **Only £11.95**

Have you got our **FREE GREEN CATALOGUE** yet?

NO!! Send S.A.E. 6" x 9" TODAY!!

It's packed with details of all our KITS plus large range of SEMICONDUCTORS including CMOS, LS TTL, linear, microprocessors and memories; full range of LEDs, capacitors, resistors, hardware, relays, switches etc. We also stock VERO and Antex products as well as books from Texas Instruments, Babani and Elektor.

ALL AT VERY COMPETITIVE PRICES.

ORDERING IS EVEN EASIER - JUST RING THE NUMBER YOU CAN'T FORGET FOR PRICES YOU CAN'T RESIST.

5-6-7 8-9-10

and give us your Access or Barclaycard No. or write enclosing service evngs cheque or postal order. Official orders accepted from schools, etc. & weekends

Answering

service evngs

& weekends

ALL

PRICES

EXCLUDE VAT

HE

FAST SERVICE · TOP QUALITY · LOW LOW PRICES

No circuit is complete without a call to -

TK ELECTRONICS
 11 Boston Road
 London W7 3SJ


Add 65p postage & packing +15% VAT to total Overseas Customers;

Add £2.50 (Europe), £6.00 (elsewhere) for p&p Send S.A.E. for further STOCK DETAILS. Goods by return subject to availability.

OPEN

9am to 5pm (Mon to Fri)
 10am to 4pm (Sat)

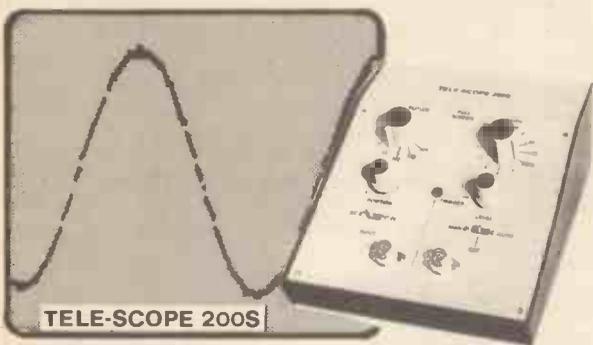TEL: 01-567 8910 ORDERS
 01-579 9794 ENQUIRIES
 01-579 2842 TECHNICAL AFTER 3PM



TELE-SCOPE 200S

Digitise at up to 10 MHz. Store, then display on a UHF TELEVISION. Single shot Capture up to 250 KHz. Storage Facility for less than £100.

The Tele-Scope is a new concept in data capture utilising the latest Digitising techniques. The Tele-Scope acts - controls - displays much like a conventional scope but does much much more.

A kit version is available for £89 and a Built unit for £109. A manual is included and specialist parts are available separately.

Prices exclude V.A.T. at 15% with postage and packing at £2.95 inc. The manual is available separately for £1.50 inc. which is refundable on subsequent purchase of a unit.

NAME & ADDRESS.....

 Cheques PO. made payable, I enclose Cash £ p

HAWK ELECTRONIC TEST EQUIPMENT

Bircholt Road, Parkwood Industrial Estate, Maidstone, Kent ME15 9XT. 0622 686811

Hobby Electronics, September 1983

FEEL HEALTHIER WITH ZEPHION

Bring fresh clean air into your home with the Zephion Air Ioniser.



Air free from smoke, dust and other pollutants of modern day living can bring to many the relief of breathing comfortably once again.

We are confident that you will be delighted with the Zephion Air Ioniser, but if you are not entirely satisfied a full money back guarantee is available if items are returned in good condition within 28 days.

BUILD IT YOURSELF!

clip the coupon

TO:- Dataplus Developments
 81, Cholmeley road
 Reading, Berks.
 RG1 3LY TEL:- 0734 67027

NAME:-

ADDRESS:-

PLEASE SEND:

ZEPHION KITS @ £24.15p
 (Kits include all parts)

ZEPHION AIR TONERS
 BUILT AND TESTED. @ £34.50p

Money immediately refunded if items returned in good condition.

Prices include VAT & postage; allow 14 days for delivery.

DATAPLUS HE

This is the Great

Hobby Electronics

Computer-Controlled Model Railway COMPETITION

Sponsored by Oric Products International Ltd., Beatties of London Limited and ASP Software (a division of Argus Specialist Publications Ltd.).

WHEN it was proposed that there should be a Grand Computer Controlled Model Railway Competition for the 1983 Breadboard exhibition, we rapidly became bogged down with seemingly endless complications. We spent most of the time during discussions simply explaining jargon: what, to a computer hardware man, is a "dead frog"? Something unpleasant by the roadside, was the popular answer! On the other hand our modelling consultant was somewhat bemused by the many acronyms that punctuate conversations between computer buffs: who, or what is a PIA? Bits of what? What is a multiplexer, and so on, and on, and on . . . !

In the end we were all quite bewildered — but this confusion ultimately gave us the clue to our Computer Controlled Model Rail Competition: no one, it seems, truly knows how best to marry a computer to a complex model rail layout or what it should do and, particularly, how it should be done.

We decided, finally, that the simplest and best approach would be to throw the thing wide open, with only a few essential restrictions. The only rule of the competition, then, is that the winning entry will be that which demonstrates the most ingenuity,

usefulness and practicality in adapting a modern home computer to control a model railway layout — the what, how and why we quite happily leave to our readers!

The essential limitation we felt obliged to impose is that the layout should measure no more than 6ft by 2ft — in other words, something that can be transported to the Breadboard exhibition in Hammersmith in late November this year.

We anticipate that most of the entries will be from constructors who have an existing computer interfaced layout, but the competition is open to all comers so anyone who wants to "have a go" will be welcome in the lists. For the benefit of those who fancy their chances at the Grand Prize, here are a few ideas that resulted from the meeting of the minds in Hobby's editorial offices (we won't mention the ideas that evolved later, down at the Royal George!).

● A fairly simple software application would be to write a program for storing and modifying timetables and operating schedules; an extension of this idea would be an interface to position sensing circuits so that an operator

would know not only when the next train was due to leave, but also when it was safe to start down the track.

● One of the most obvious ideas proposed was to program a mimic board which could show not only the track layout but the condition of signal lights and with 'train in section' indication: colour would be necessary for user-friendliness!

● Ways to adapt microprocessor technology to model train control: one option that might be easily constructed would be to computer-control sections of track rather than individual trains. However completely automatic running is not the goal of most railway modellers, so any system should allow lots of room for the operator to control the layout himself.

And that is about the limit of the ideas we came up with before brain fog set in. We'll leave it to the inventiveness and competitive spirit of our readers to stun the judges with brilliant projects we should have thought of . . . but didn't!





FIRST PRIZE

SECOND PRIZE

THIRD PRIZE

Hot off the production line, an Oric 48K colour computer, donated by Oric Products International Ltd.

Gift vouchers to the value of £50, redeemable on model rail products at any Beatties of London shop.

£25 worth of games and utility program tapes from ASP Software.

Entry forms, together with an entrance fee of £1.00 (cheque or money orders only, please) should be sent to:
The Exhibition Manager, BB83, ASP Exhibitions, 145 Charing Cross Road, London WC2H 0EE.
 Closing date is 31st October 1983. Judging will take place at Breadboard '83, Cunard Hotel, Hammersmith, London W6, on either Wednesday 23rd or Thursday 24th November 1983. Entrants will be informed of the day on which they will be required to present their layouts at the exhibition. Finalists will be asked to demonstrate their layouts at some time(s) during the open days of Breadboard '83 (25, 26, 27th November) and layouts will be available for collection between 1600 and 1800 hours on Sunday 27th November. The judges decision will be final and no correspondence will be entered into.

Entry Form

PLEASE USE BLOCK CAPS

NAME:

ADDRESS:


TEL NO: AGE ON 30TH NOV. 1983:

BRIEF DESCRIPTION OF LAYOUT AND FUNCTIONS:

SCALE: SIZE OF LAYOUT: (MAX 6FT X 2FT):

COMPUTER USED:

COMMERCIAL PERIPHERALS USED:

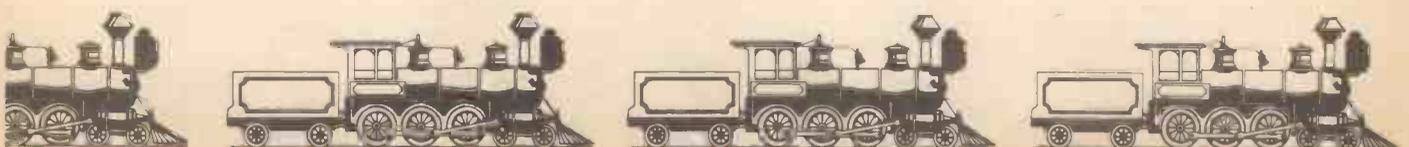

H.E. PROJECT KITS

I.C.s
TRANSISTORS
CAPACITORS

TOOLS
RESISTORS
HARDWARE

CASES
KITS
PCBs

MAGENTA

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Kits include ALL THE ELECTRONICS and HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.E. which includes the project — you will need to order the instruction reprint at an extra 45p each.

Reprints available separately 45p each + p. & p. 45p.

WHISTLE SWITCH Aug 83 less mic	£18.89	IN CAR CASSETTE POWER SUPPLY Dec 81	£4.77
STEREO SPREADER July 83	£5.79	SCRATCH FILTER Nov 81 Mono	£5.82
SOFT FUZZ July 83	£10.25	LED VU METER Nov 81 less case	£4.87
SINCLAIR SOUND BOARD Jun 83 less case	£18.23	SIMPLE STYLUS ORGAN Nov 81 less case	£4.96
TRAFFIC LIGHT TOY June 83 less stand	£6.23	METRONOME Nov 81	£12.71
BTL LIGHT (carbonyl indicator) June 83 less case	4.99	TELEPHONE BELL REPEATER Oct 81	£13.67
TTL LOGIC PROBE June 83	£7.98	Med linking wire extra	14p metre
AUTO TESTER May 83	£6.88	COMBINATION LOCK Oct 81 less solenoid	£18.65
STALL THIEF May 83 (inc relay)	£11.72	BABY ALARM Oct 82	£8.70
STEREO VOICE OVER UNIT April 83	£17.82	DIANA METAL LOCATOR Sept 81	Fig 8 linking wire
OPTIONAL MIC PRE AMP April 83 (no case)	£4.38	REACTION TESTER GAME Sept 81	£12.81
AUTO POWER DOWN April 83 no case	£6.05	VARIABLE BENCH POWER SUPPLY Aug 81	£28.96
LINEAR OHMMETER Mar 83	£13.55	ULTRABROAD BURGLAR ALARM July 81	£19.98
LOW RANGE OHMMETER Mar 83	£10.37	ELECTRONIC DOOR BUZZER July 81	£8.96
PHASE FOUR Dec 82	£18.71	ELECTRONIC METRONOME July 81	£19.48
STEREO NOISE GATE Dec 82	£13.82	CONTINUITY CHECKER June 81	£5.71
TAPE/SLIDE SYNCHRONIZER Dec 82	£21.73	ENVELOPE GENERATOR June 81	£17.96
BIG EAR Dec 82	£6.21	AUDIO MIXER June 81	£8.33
MICROAMMETER ADAPTOR Dec 82	£4.98	PUBLIC ADDRESS AMPLIFIER March 81	£12.04
OHMMETER Nov 82	£14.98	Extras — horn speakers £6.53 each	PA MIC £4.40
DIANA V.C.O. Nov 82	£4.89	FUZZBOX March 81	£10.96
CB SQUELCH UNIT Oct 82	£9.19	WINDSCREEN WIPER CONTROLLER March 81	£8.20
'JUNIOR' SLOTCAR CONTROLLER Sept 82	£5.50 (less case)	STEAM LOGO WHISTLE March 81	£12.96
ZX INTERFACE BOARD Sept 82 inc edge con	£11.33	PHOTOGRAPHIC TIMER March 81	£3.80
T.V.I. FILTER July 81	£7.39	HEATBEAT MONITOR Feb 81	£24.96
AUTO WAH June 82 £18.98 inc case or £12.28 less case	£5.33	TWO-TONE TRAIN HORN Feb 81	£5.60 less case
AUTO GREENHOUSE SPRINKLER June 82	£14.38	MEDIUM WAVE RADIO Feb 81	£8.20
less pump and power supply		BENCH AMP Jan 81	£10.80
TELEPHONE TIMER June 82	£33.42 less power supply	NICAD CHARGE Jan 81	£8.20
POWER SUPPLY DESIGN 12V 500MA June 82	£9.98	CHUFFER JAN 81, less case	£7.53
ECHO REVERSE UNIT May 82, Less case	£33.98	BATTERY CHARGE MONITOR Dec 82	£5.77
Economy case WB3	£7.76 extra	MEMORYBANK — MINISYNTHESIZER Nov & Dec 80	£29.96
DIGITAL THERMOMETER May 82 excluding case + bezel	£16.90	TRANSISTOR TESTER Nov 81	£6.84 inc test leads
AUDIO SIGNAL GENERATOR May 82	£12.98	GUITAR AMP Nov 80	£6.85
CABLE TRACER May 82	£9.98	INTRUDER ALARM Oct 80	£20.88
DIGITAL CAPACITANCE METER Apr 82	£21.37	TOUCH SWITCH Sept 80	£2.75 less case & contacts
SIGNAL TRACER Apr 82	£3.88	GUITAR PHASER Sept 80	£16.28
BLEND ALARM Apr 82	£11.74	SOUND OPERATED FLASH TRIGGER July 80 no act	£8.33
DIGITAL DICE May 82	£7.39	FOG HORROR June 80	£6.64
BICYCLE SIREN Mar 82	£10.89	SPEED CONTROLLER FOR R/C April 80	£17.55 (less case)
NOISELESS FUZZBOX Feb 82	£10.45	DIGITAL FREQUENCY METER April 80	£12.82
MASTHEAD AMPLIFIER Feb 82	£14.74	GUITAR TUNER Nov 79	£12.81
DRUM SYNTHESIZER Dec 81, Full kit	£21.37	CAR ALARM Feb 79	£12.81
GUITAR HEADPHONE AMPLIFIER Dec 81	£3.72		

BOOKS: ELECTRONICS & COMPUTING

205 First Book of Hi-Fi Loudspeaker Enclosures	£0.95	Semiconductor Data Book Newnes	£6.95
221 28 Tested Transistor Projects	£1.25	Basic Electronics Theory and Practice	£7.98
223 50 Projects Using IC CA3139	£1.25	Microprocessor for Hobbyist	£4.75
226 A Practical Introduction to Digital IC's	£1.25	Burglar Alarm Systems	£5.55
228 How to Build Advanced Short Wave Receivers	£1.95	Electronics: Build and Learn	£3.90
232 Essential Theory for the Electronic Hobbyist	£1.95	Electronic Projects in Music	£3.90
BP39 50 (FET) Field Effect Transistor Projects	£1.75	Electronic Projects in Photography	£3.90
BP40 Digital IC Equivalents and Pin Connections	£3.50	Electronic Projects in Home Security	£3.90
BP41 Linear IC Equivalents and Pin Connections	£3.50	Questions and Answers Electronics	£2.70
BP42 50 Simple L.E.D. Circuits	£1.50	Electronic Projects in the Car	£4.80
BP43 How to Make Walkie-Talkies	£1.95	20 Solid State Projects Car and Garage	£4.80
BP45 Projects in Opto-Electronics	£1.95	110 Electronic Alarm Projects	£5.95
BP47 Mobile Discotheque Handbook	£1.35	Computing is Easy	£2.75
BP48 Electronic Projects for Beginners	£1.95	ZX81 Users Handbook	£5.75
BP49 Popular Electronics Projects	£1.95	ZX81 Basic Book	£5.75
BP56 Electronic Security Devices	£1.95	Byteing Deeper into Your ZX81	£5.45
BP58 50 Circuits Using 7400 Series IC's	£1.75	The ZX Spectrum Explored	£6.45
BP59 Second Book of IC Projects	£1.75	24 50 CMOS IC Projects	£1.75
BP61 Beginners Guide to Digital Techniques	£0.95	BP24 52 Projects Using IC 741	£1.25
BP70 Transistor Radio Fault-Finding Chart	£0.50	BP44 IC555 Projects	£1.95
BP71 Electronic Household Projects	£1.75	BP50 IC LM3900 Projects	£1.35
BP75 Electronic Test Equipment Construction	£1.75	BP65 Single IC Projects	£1.50
BP78 Practical Computer Experiments	£1.75	BP69 Electronic Games	£1.75
BP79 Radio Control for Beginners	£1.75	BP72 A Microprocessor Primer	£1.75
BP80 Popular Electronic Circuits — Book 1	£1.95	BP73 Remote Control Projects	£1.95
BP81 Electronic Synthesiser Projects	£1.78	BP74 Electronic Music Projects	£1.75
BP82 Electronic Projects Using Solar Cells	£1.95	BP76 Power Supply Projects	£1.75
BP85 International Transistor Equivalents Guide	£2.95	BP83 VMO5 Projects	£1.95
BP87 Simple L.E.D. Circuits — Book 2	£1.75	BP84 Digital IC Projects	£1.95
BP92 Easy Electronics — Crystal Set Construction	£1.75	BP88 How to Use OP-Amps	£2.25
BP94 Electronic Projects for Cars and Boats	£1.95	BP90 Audio Projects	£1.95
BP98 Popular Electronic Circuits — Book 2	£2.25	BP93 Electronic Timer Projects	£1.95
BP101 How to Identify Unmarked IC's	£0.65	BP95 Model Railway Projects	£1.95
BP103 Multi-Circuit Board Projects	£1.50	BP97 IC Projects for Beginners	£1.95
BP108 International Diode Equivalents Guide	£2.25	BP99 Mini Matrix Board Projects	£1.95
BP109 The Art of Programming the 1K ZX81	£1.95	BP105 Aerial Projects	£1.95
BP114 The Art of Programming the 16K ZX81	£2.50	BP106 Modern OP-Amp Projects	£1.95
BP119 The Art of Programming the ZX Spectrum	£2.50	BP115 The Pre Computer Book	£1.95

282 Handbook of Integrated Circuits (IC's) Equiv. & Substitutes	£1.95	FUN WITH ELECTRONICS	£1.95
222 Solid State Short Wave Receivers for Beginners	£1.25	Enjoyable introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners — children and adults. Only basic tools needed.	£1.95
227 Beginners Guide to Building Electronics Projects	£1.95	64 full colour pages cover all aspects — soldering — fault finding — components identification and how they work.	£1.95
BP1 First Book of Transistor Equivalents and Substitutes	£1.50	Also full details of how to build 6 projects — burglar alarm, radio, games, etc. Requires soldering — 4 pages clearly show you how.	£1.75
BP14 Second Book of Transistor Equivalents and Substitutes	£1.75	COMPONENTS SUPPLIED	£1.75
BP27 Chart of Radio, Electronic, Semiconductor and Logic Symbols	£0.50	ALLOW ALL PROJECTS TO BE BUILT AND KEPT.	£1.95
BP32 How to Build Your Own Metal and Treasure Locations	£1.95	Supplied less batteries & case.	£1.95
BP36 50 Circuits Using Germanium, Silicon and Zener Diodes	£1.50	FUN WITH ELECTRONICS	£1.95
BP37 50 Projects Using Relays SCRs and TRIACS	£1.95	COMPONENT PACK £15.78	£1.95
BP51 Electronic Music and Creative Tape Recordings	£1.98	BOOK EXTRA £1.25	£1.95
BP53 Practical Electronics Calculations and Formulae	£2.95	Book available separately.	£1.95
BP57 How to Build Your Own Solid State Oscilloscope	£1.95		
BP60 Practical Construction Projects — Book 1	£1.45		
BP66 Beginners Guide to Microprocessors and Computing	£1.75		
BP67 Counter Drive and Neural Display Projects	£1.75		
BP88 An Introduction to BASIC Programming Techniques	£1.95		
BP107 30 Solderless Breadboard Projects — Book 1	£2.25		
BP110 How to Get Your Electronic Projects Working	£1.95		
BP117 Practical Electronic Building Blocks — Book 1	£2.25		
Elementary Electronics. Sladdin. Excellent theory and 35 constructional projects. Uses S-Dec. First steps to CSE level	£3.95		
Interfacing to microprocessors and microcomputers	£5.75		

ZX SPECTRUM AMPLIFIER

250mW output. Volume control. Internal speaker. Very simply connected using load/save lead. Puts real power even into the simplest "Beep" commands. Adds a real "zing" to musical programs and games. Requires PP3 battery — not supplied. Very low current drain. Supplied ready built complete with demo software and instructions.

ORDER AS: ZX SPECTRUM AMPLIFIER (SAHE) £6.98

ZX SPECTRUM SUPER AMPLIFIER

250mW output. Now add synthesizer quality to those "Beep" commands. Super circuit with adjustable ATTACK, SUSTAIN and DECAY envelope controls. Plus variable ECHO. Generates a wide range of special effects. Five graduated controls. Internal speaker. Very smart case. Requires batteries — not supplied. Very low current drain. Ready built complete with demo software and instructions.

ORDER AS: ZX SPECTRUM SUPER AMPLIFIER (SSAHE) £17.98

SOLDERING/TOOLS

ANTEX X5 SOLDERING IRON STAND	£5.48	MULTIMETER TYPE 2 (YN360TR)	£11.49
SOLDERING IRON STAND	£1.98	20K Ω p.v. with transistor tester.	£5.48
SPARE BITS. Small standard, large, For X5 + X25	65p each	DC current, 4 resistance ranges	99p
SOLDER. Handy size	99p	We've used it and we like it.	48p
SOLDER CARTON	£1.84		
DESOLDER BRAID	69p		
HEAT SINK TWEEZERS	29p		
DESOLDER PUMP	£6.48		
HOW TO SOLDER LEAFLET	12p		
LOW COST CUTTERS	£1.89		
LOW COST LONG NOSE PLIERS	£1.88		
WIRE STRIPPERS & CUTTERS	£2.69		
PRECISION PETITE 12V P.C.B. DRILL	£11.67		
DRILL STAND	£7.98		
GRINDING STONE	50p		
GRINDING WHEEL	50p		
SAW BLADE	85p		
BRASS WIRE BRUSH	50p		
BURR	50p		
VERO SPOT FACE CUTTER	£1.49		
pin insertion tool	£1.98		
VEROPINS (pk of 100) 0.1"	52p		
MULTIMETER TYPE 1 (1.00 opv)	£5.48		
CROCODILE CLIP TEST LEAD SET. 10 leads with 20 clips	99p		
RESISTOR COLOUR CODE CALCULATOR	21p		
CONNECTING WIRE PACK TYPE ED. 11 colours	48p		
ILLUMINATED MAGNIFIERS	£1.14		
Small 2" dia. (5 x mag)	£2.40		
Large 3" dia. (4 x mag)	£2.98		
CAST IRON VICE	£1.98		
SCREWDRIVER SET	£3.98		
POCKET TOOL SET	£2.85		
DENTIST INSPECTION MIRROR	£1.50		
JEWELLERS EYEGLASS	69p		
PLASTIC TWEEZERS	77p		
PAIR OF PROBES WITH LEADS (cc)	77p		
Q MAX PUNCHES	£2.98; £3.06; £3.17; £3.24		



Speakers min 8 ohm 87p; 64 ohm 89p;	80 ohm 88p	Brimboard breadboard	£6.98
Crystal earpiece	65p	Verobloc breadboard	£4.20
Magnetic earpiece	15p	PCB etching kit	£4.98
Stethoscope attachment	69p	ZX1 edge connector	£2.25
Mono headphones	£2.98	Ferrite rod 5 inch	59p
Stereo headphones	£4.35	PP3 clips	10p
Telephone pick up coil	72p	PP3 clips	11p
Min buzzer	6V 50p; 12V 85p	2 station intercom	£6.75
Euro breadboard	£6.40	IC sockets	8 pin 18p; 14 pin 17p; 16 pin 18p
S Dec breadboard	£6.98		

ADVENTURES WITH MICROELECTRONICS

Similar to 'Electronics' below. Uses I.C.s. Includes dice, electronic organ, doorbell, reaction timer, radio etc. Based on Bimboard 1 bread board. Adventures with Microelectronics £2.98 Component pack £29.64 less battery.

ADVENTURES WITH DIGITAL ELECTRONICS

Entertaining and instructive. Includes details of some digital ICs and 8 projects: shooting gallery, 2 way traffic lights, electronic adder, computer space invaders game etc. No soldering. Adventures with Digital Electronics book £3.25 Component pack including breadboards £42.50 less batteries.

ADVENTURES WITH ELECTRONICS by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects. Adventures with Electronics £2.85. Component pack £18.98 less battery.

30 SOLDERLESS BREADBOARD PROJECTS

Book 1 by R.A. Penfold Clear verobloc layouts and circuit diagrams. Includes fuzbox, radio, metronomes, timers, transistor checker, switches etc. Introduction gives basic information on components including resistors, capacitors, I.C.s, transistors, photocells etc. Ideal for beginners as well as those with some experience. Complete kit including verobloc, book and components (less batteries) £24.75 Less book £22.50, less verobloc £20.25. Book only £2.25.

MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST Price list included with orders or send sae (9 x 4) CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Send 80p in stamps or add 80p to order. FREE to Schools/Colleges requested on official letterhead.

MAGENTA gives you FAST DELIVERY OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers — HAVE YOU TRIED US?

MAGENTA ELECTRONICS LTD.

Magenta Electronics Ltd, HA39, 135 Hunter St., Burton on Trent, Staffs, DE14 2ST. MAIL ORDER ONLY. 0283 65435. Mon-Fri 9-5 Access/Barclaycard (visa) by phone or post. Add 45p P&P to all orders. Prices include VAT. SAE all enquiries. Official orders welcome. OVERSEAS. Payment must be in sterling. IRISH REPUBLIC and BFPO UK PRICES. EUROPE: UK Prices plus 10%. ELSEWHERE: write for quote.

CABLE AND SATELLITE TV

Helen Armstrong
Graham Brant

The arrival of television distributed by cable and by Direct Broadcast Satellite will give a wider viewing choice than ever before. We explain how the different systems will function and interact.

Thanks to British Telecom and BTI for permission to reproduce line drawings from their brochures.

IT IS APPROPRIATE that 1982, as Information Technology Year, saw the green light for both satellite and cable television, as well as the launching of Channel 4. The technological advances of the past decade have resulted all at once in a rapid expansion in the electronic media, which seems likely to change the face of broadcasting as we know it in a surprisingly short time. The technical and political aspects of these sudden changes present problems, not only new, but highly complex, considering the international nature of broadcasting. The debates go on. Only time will tell what form of programme networking will emerge, or how it will affect the TV system we have at the moment. Television has already invaded the territory of the cinema with video, and the uncertainties attending the arrival of rival video systems may be thrown into deeper confusion as television diversifies still further.



Courtesy of British Telecom

Cable Sources

Cable transmission began as long ago as 1929, with the distribution of radio programmes. The first television systems in this country started in 1948 with companies such as EMI, British Relay and Rediffusion being the early pioneers. From the start the cable systems in the UK have been localised, providing only BBC, IBA and some local community television programmes.

In the USA however, where cable TV is already a fact of life, the lack of a single national television network prompted the growth of cable in areas with little or no service, which was in the vast majority of areas away from the big city centres. VHF systems were generally used since VHF television sets were readily available.

Cable television systems have been set up in various new town developments around the country on an experimental

basis, starting in 1966 with Washington, Co. Durham, and extending later to Irvine in Scotland, Craigavon in N.Ireland, Brackla in Wales and Milton Keynes, Walderslade and Martlesham in England. The networks used dual cables, coax for the television signal and telephone cable for the audio. These were all set up and run by British Telecom. But all the schemes set up in the sixties and seventies ran into the Government's refusal to let them carry anything other than the two BBC and one ITV channels.

In November 1980 the Home Secretary licenced several pilot subscription TV schemes until December, 1983. Apart from British Telecom, companies involved were Rediffison, Visionhire, Philips Cablevision, Greenwich Cablevision and Radio Rentals — mostly big TV rental companies. The new schemes included general release feature films


and independent TV channels. However, what will happen when the initial period runs out is not known — except that it is now generally accepted that cable TV is here to stay and that it will include material completely independent of the BBC and IBA/Independent ITV companies. One result of this is bound to be an expansion of independent programme-making companies, with no involvement in transmission at all, simply making their own features to market to television companies. Cable networks are also allowed to supply feature films after one year's general release, as opposed to three years for the BBC and IBA — a purely economic arrangement.

Cable networks often use recording and transmission equipment which does not entirely match the 'broadcast standard' used by the big organisations, but this is hardly likely to cause a serious degradation of picture and sound quality — certainly less than that occurring with an ordinary domestic VCR, probably less than that caused by a slightly ill-adjusted telly — not a serious problem.

The System Today

With the present UHF television network the programme source, whether live or prerecorded, is generated at the studio or by an outside broadcast (OB) unit. Programme selection is carried out at a main broadcasting centre, or network switching centre, before the transmitter network is fed with the desired signal. The main UHF signal is then broadcast from about fifty or so high powered transmitters. Some, Crystal Palace for example, transmit at a power of 1MW from the aerial complex. Together these signals reach about 85% of the population of the UK through the extensive network of relay stations, either in operation or in the process of being built, which provide 'fill in' signals in areas of poor reception. Some of these are very localised indeed, particularly in mountainous areas where small valleys can be completely shielded from signals by surrounding hills.

The relay station building programme

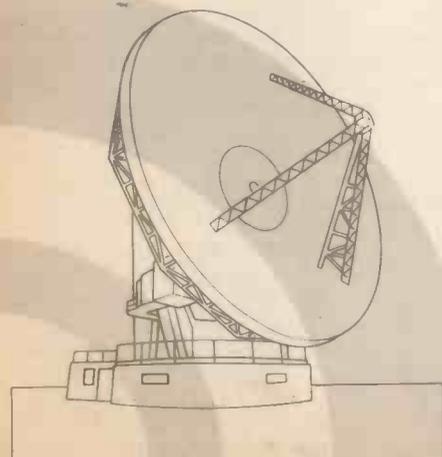

A 'spider man' services undergrounds cables.

Courtesy of British Telecom

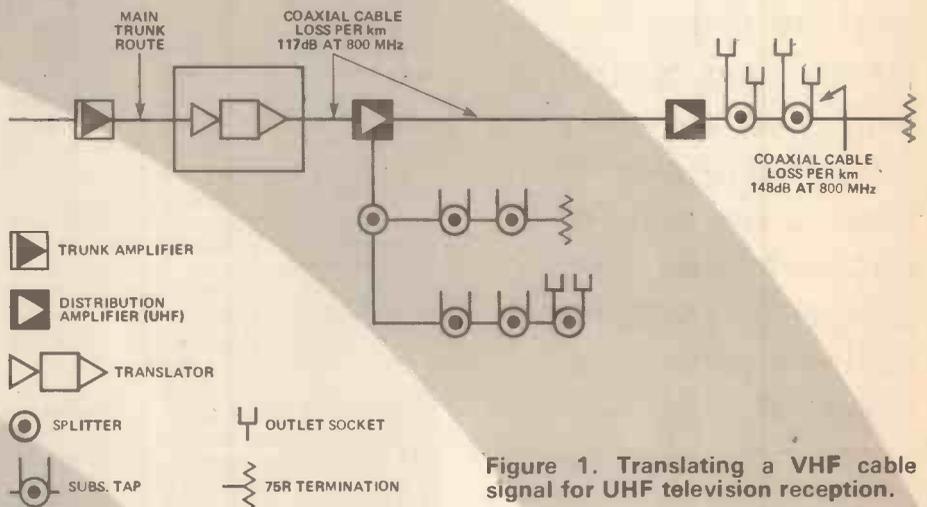


Figure 1. Translating a VHF cable signal for UHF television reception.

has now achieved an overall coverage of 99% of the population, which is perhaps one of the highest in the world from a terrestrial system — one of the advantages of being in a small country where networking efforts can be co-ordinated into a single system.

The initial costs were low, about £1 per potential viewer, but with small relay stations serving communities of down to 200 people the cost is more like £100 per head. With such an extensive network already in existence, it is perhaps not surprising that many people are sceptical of the future success of cable and satellite TV. Both the IBA and the BBC view cable with suspicion because of the potential loss of viewers and the higher costs generated by more programme competition. The BBC needs a large audience to justify the television licence fees, and the IBA likewise needs viewers to generate advertising revenue.

It is worth remembering that the large UHF stations are near population centres which could easily be cabled, whereas the relays tend to be located

in rural areas which are unlikely to be served by cable. Even plans to run TV cables along sewer networks will not succeed in carrying cables to many country areas!

Cable Works

There have been two approaches to cable distribution systems: Frequency Division Multiplex (FDM) and Space Division Multiplex (SDM) systems. With FDM, a number of television channels are sent down one cable, usually coaxial, whereas with SDM a separate cable is used for each channel, usually with balanced feeders rather than coaxial.

Anything up to seven channels can be provided, but many of the old experimental systems cannot even take Channel 4. About half of the existing channels are VHF, but most are UHF, and will therefore not need an adaptor for the average domestic television set. There are a few systems which use VHF for main trunk distribution and convert to UHF for local distribution. Although most of these systems only relay BBC

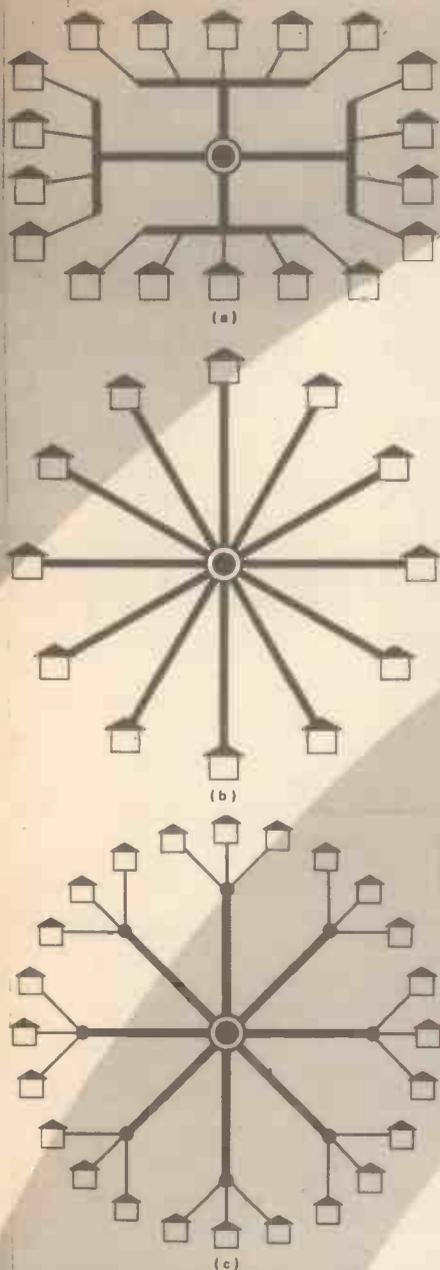


Figure 2. Alternative distribution networks: a) Tree and Branch b) Star and c) Multi-star.

and IBA programmes, there are a few which provide a pay-TV service, for example in such places as Milton Keynes and Greenwich, London. Most of these existing systems are technically worn out, and further developments have been slow to take place due to the good terrestrial broadcast system. On the Continent, operators have been allowed to broadcast foreign programmes as well as those produced locally, but development has still not taken place on the scale of that in the USA.

The USA cable systems were initially of six to twelve channel capacity using VHF frequencies, mainly relaying a number of channels from an off-air reception point. These later developed into thirty-channel systems, which included channels provided specifically by the specialist cable TV companies. There are now a few 'super' systems in

the cities such as New York and Los Angeles, and these provide up to 104 channels along two cables each of 52 channels capacity. Frequencies used are 54 to 400MHz, with the 5 to 35MHz spectrum available for viewer feedback, electronic voting, etc.

Star And Branch

While it might appear straightforward to connect every television consumer into a cable system, the architecture is not simple. There are two distinct systems in use in the UK, both using FDM: the 'Tree and Branch' system and the 'Star' system. The most common is the Tree and Branch, which is easiest to implement. With Tree and Branch all consumers are simply looped together with all services available to each consumer. The system is rather inflexible and has a number of drawbacks. The signal is continually split up on the outward transmission, requiring large numbers of distribution amplifiers which are very prone to producing distortion and unwanted by-products. In a similar fashion any unwanted signals on the network are continually added if they are feeding back to the source, ie the television company. This problem is usually apparent with random noise — and noise in the network can be a problem when added up. To overcome this a very high standard of network screening is required, because any extraneous interference has the potential of disturbing the whole system. If a two-way service such as electronic voting is desired, then a very complex digital protocol is required to sort out the mass of data which would arrive at the TV company at the same time.

The Star system has a more complex architecture, but is more versatile and can be readily expanded over a period of time after the main system has been constructed. The disadvantages are very much less than the Tree and Branch, especially with regard to distortion and interference problems at one point in the network, which would be very unlikely to be transmitted to any other part. The technology is very much newer though, and more technical research may be required, unlike the Tree and Branch system, which could be implemented tomorrow. This would provide a good chance to export British technology rather than import foreign products, such as happened in the rush for CB. The architecture is very similar to British Telecom's 'System X' telephone system, and it could well be that they are the best candidates to install any future network.


Forty Into One Won't Go

It is unlikely that any future service would be permitted to use VHF, as there are too many mobile radio, aeronautical and general communication services present in the UK, and any break in a large scale cable TV distribution system would provide a potentially major source of interference. It is likely

that frequencies would be restricted to those in the UHF TV band. This provides theoretically a maximum of forty channels per cable; there are however a number of factors which drastically reduce this figure. Local TV transmission channels must be avoided to prevent mutual interference. Local oscillator radiation must also be considered; when a TV receiver is tuned to one channel, then the local oscillator will usually be at the frequency very near that of another channel in the UHF band. This signal is often radiated from the receiver and can cause problems to a view in the network viewing the channel. Adjacent channels cannot be employed either, since the normal domestic receiver is not selective enough to differentiate between any two consecutive channels. Having taken these factors into account, it seems that it is only possible to utilise between seven and nine of the forty channels at any one time! For interference-free reception, optical fibre distribution would provide a solution, but the high cost of a decoder for each consumer is unlikely to prove attractive in the near future. Perhaps the best solution is provided by the Star system.

The main distribution trunks could then be optic fibres feeding flexibility points, while the individual cables feeding the consumer would use UHF. To overcome the shortfall in capacity of these local cables, programme selection could be carried out remotely at the flexibility points; in the ideal case the consumer would merely type in the programme of his choice. Unlike the Tree and Branch system, therefore, each consumer would not necessarily be in receipt of every channel.

Programmes are received, firstly, by an aerial array, and then processed into a form which can be routed along trunk cables, which may be up to 12km long. This requires the signal to be converted down to VHF to prevent disastrous attenuation in the cable — even then, amplification is needed every 420m. Subsequently, a translator link restores the signal back to UHF, with a VHF bypass for 405 line transmission, and radio. From there the signal goes through a series of cable splitters and subscriber taps to TV and radio outlets

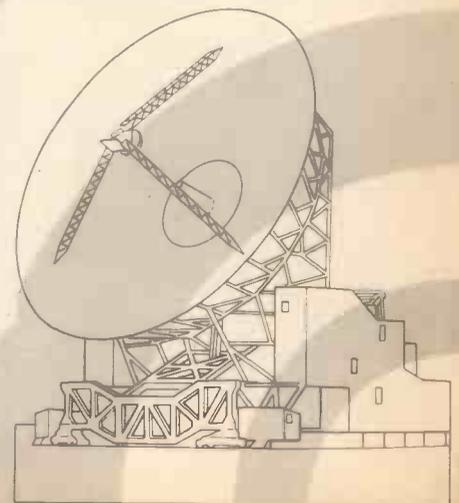

■ Cable And Satellite TV

in subscribers' homes. Another option which has only been tried experimentally so far is the use of optical fibres for cable transmissions. The economics of cable are such that the cost is approximately £12,000 per mile. It could cost £6M alone to cable Bromley in London! To cable the large UK cities and achieve a 50% population penetration could cost 2½ to 3½ billion pounds.

Bearing in mind the controversy over Channel 4, it is likely that some organisation will need much more convincing on potential returns before committing themselves to such an investment. The coming of cable-TV is unlikely to create more than a few hundred jobs in the long term, not the thousands predicted in the popular press. A scheme of thought against cable TV is that with the increasing ownership of VCRs, the younger generation are happy with what they have, and the older generation are perfectly content with existing media. This is, however, a rather pessimistic view.

Direct Broadcast Satellite

While cable television shows some signs of being a more conspicuous public issue, as well as a more established basic technology, 'satellite TV', referred to as DBS (Direct Broadcast Satellite) TV, to distinguish it from transmissions which make part of their journey from source to main transmitter via satellite links, is going to be with the general public first. It is, ironically, easier to put up a satellite to carry TV signals than it is to install ground cables to every television owning household in the UK.

DBS will also be different from cable TV in that it will be under the control of the public broadcasting concerns, the BBC and the IBA. They are under obligation to make the service available to everyone; therefore, the transmissions need to be capable of being received by all households. However, the responsibility for obtaining the dish aerials needed to receive DBS is of course in the hands of the viewer, not the broadcasting organisations!


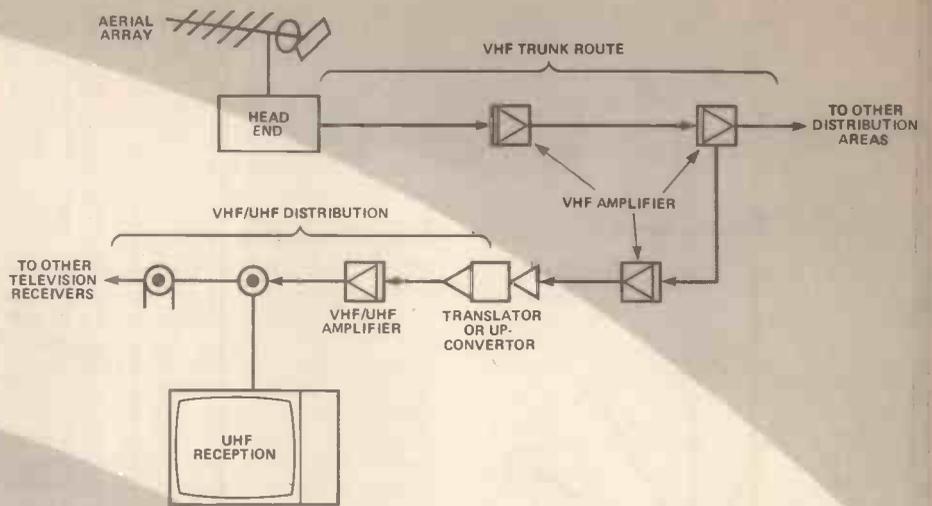
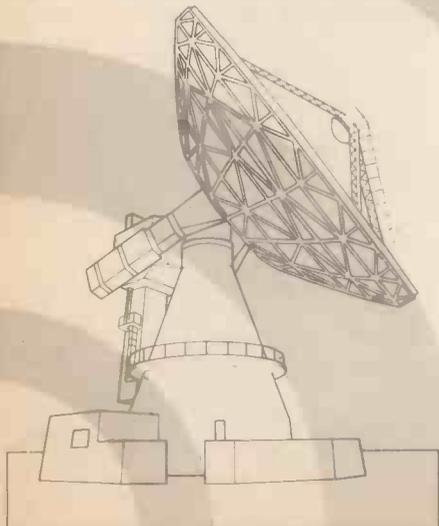


Figure 3. A typical hybrid VHF/UHF cable system.

Figure 4. Modes of distribution in the existing television network.

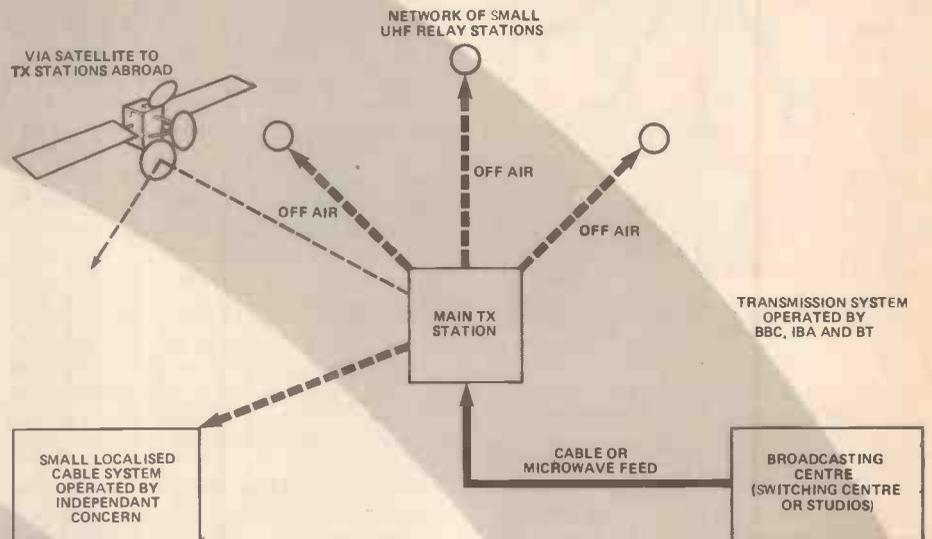

Government gave the go-ahead for DBS in the UK in 1982, with the BBC scheduled to start transmission in 1986. The international Telecommunications Union, of which Britain is a member, allocated five satellite channels to each member country in 1977. After thinking about opting out of DBS altogether, the BBC has chosen to participate and has been given two of the UK's five channels. The IBA has not yet been given one, but it is improbable that it won't; however, the remaining three channels remain unallocated as yet. One plan put forward is that one of their channels will be run on an extra license, and concentrate on 'quality' material from archives and foreign programmes — the best of everything, as it were; the other channel would then be a 'commercial' channel, funded by some form of subscription.

The UK's first DBS satellite, Unisat 1, a Eurostar class satellite 21 metres from 'wingtip' to 'wingtip', is being built by United Satellites Ltd., a company jointly owned by British Aerospace, British Telecom and GEC. British Aerospace is responsible for the design of the satellite itself, with GEC-Marconi doing the transponders, and the actual

operation of the transponders carried out by British Telecom. Unisat 1 will carry the BBC's two channels, so other satellites will eventually follow to carry channels used by other authorised broadcasters on the remaining three UK channels. In 1978, the European Space Agency (ESA) launched its Orbital Test Satellite (OTS), for experiments with television and telecommunications in general. The OTS is now being used already by one British company — Satellite Television PLC — for broadcasting, but only into Europe.

FM Transmissions

The transmission system employed is different from that used for terrestrial services, in order to achieve maximum efficiency from the power available in the satellite. The TV signal is modulated onto an FM carrier in a 27MHz wide channel. The use of FM, as opposed to AM, saves about 20dB of transmitting power for equal performance. Each adjacent channel uses different polarisation, which together with the signal capture effect of FM systems, allows a degree of channel overlap so that there are forty channels between

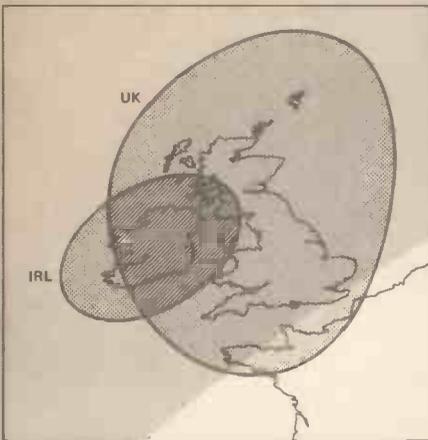


Figure 5. The Direct Broadcast Satellite's likely 'footprints' over the UK and Ireland.


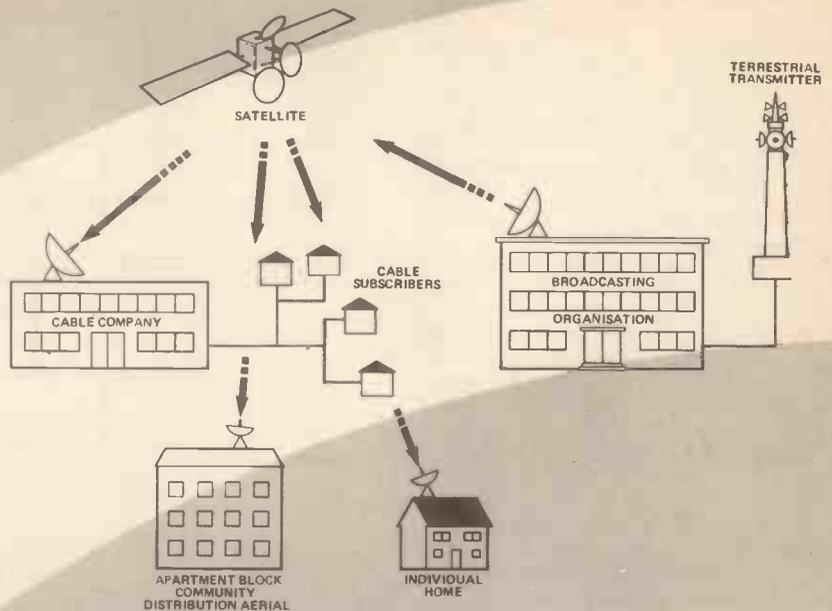


Figure 6. The integration of all modes of transmission.

British Aerospace Photograph

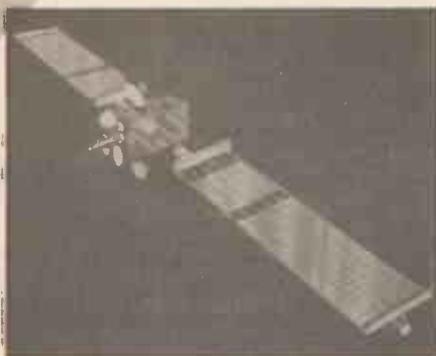

An artist's impression of the Unisat satellite.

11GHz7 and 12GHz5, with 19MHz2 channel spacing. With each channel being 27MHz wide, and the spacing between only 19MHz2, side-by-side channels are only assigned to countries in widely differing geographical positions. Also, circular polarisation is used — whenever the same channels are being used by countries which are not widely geographically divided (as must happen in some cases) opposite polarisations are used. Satellite locations above the equator, spaced at intervals of six degrees, were allocated to counties according to the suitability of their position in relation to their prospective satellite.

The UK's satellite position is 31°W, just off the eastern edge of Brazil, with Ireland, Iceland, Portugal and Spain in the same position (so that these related countries can receive each others' transmissions without complicated aerial adjustments). Our channel numbers are, 2, 6, 10, 14 and 18, with right-handed polarisation; several other countries in Europe share the same channels, but with left-hand polarisations.

The satellite must send its transmissions to fall over a narrow area, the UK being only a small land mass. The region 'covered' by the beam when it falls on the earth is shaped, because of the shape of the Earth and the angle of the beam, like an elongated egg, and is called the 'footprint' (a term normally used to describe the area covered by signals or noise affecting the

ground from above it). There will be a fringe area where reduced signals will be obtainable, but within our own footprint the signal strength will probably be around 140uV per metre, needing a dish aerial of about a metre in diameter to get a good signal.

Get The Picture?

Obtaining a good signal, however, will require a far more precise alignment than with a UHF aerial (and no twiddling it about on top of the TV set, either!) The beam will be narrow and quite low in the sky, and the accuracy of the alignment will have to be within about 0.1°, probably needing special measuring equipment to get an accurate fix — a professional job. This means that the expectation of being able to rotate the aerial easily to pick up European stations, which has been aroused in the popular press somewhat, will not be fulfilled unless some kind of precision mount with predetermined positions is provided (and this is, of course, without taking into account the different European Television standards, some of which are incompatible or only partially compatible with the British PAL system).


The low elevation of the satellite beam will also mean that places to the north, or in hilly areas, or simply behind massive buildings, may not be able to receive the signal. Fortunately, in many cases planners are already looking at communal receiver dishes and distribution systems to keep costs down, and this may be the answer.

So, there is more to DBS reception than merely putting a dish aerial on your roof. The dishes will have to be stabilised against the effects of temperature change, rain and hail, wind etc. and possibly fully enclosed. Other equipment will be needed to sort out the polarisation, to alter the frequency of the received signal for normal UHF TVs, and to convert it from FM to AM. The signal from the dish aerial may also be

amplified by a low noise amplifier before being converted to UHF frequencies. The UHF signal is then routed to the set top terminal where the decoding process takes place.

The aerial itself simply comprises a reflecting surface — the 'dish' — which focuses the signal to a central point, and a 'feedhorn', which actually picks up the microwaves; this is sited on a tripod or similar support, and can be adjusted for the best reception. The dish itself is made of aluminium (or aluminium over a fibreglass support), as though popular pictures show a round dish, by the time they become common a quadrilateral shape is more likely to abound, as this is easier to transport.

The 27MHz bandwidth for each DBS channel is wider than the 8MHz channel width used for UHF telly in the UK, which gives a lot of opportunity to improve on the present PAL-based system with the help of the extra signal space. In fact, the BBC has already presented a system known as E-PAL (Extended Pal) for just this purpose. However, IBA has come up with a completely new system, known as MAC (Multiplexed Analogue Component)

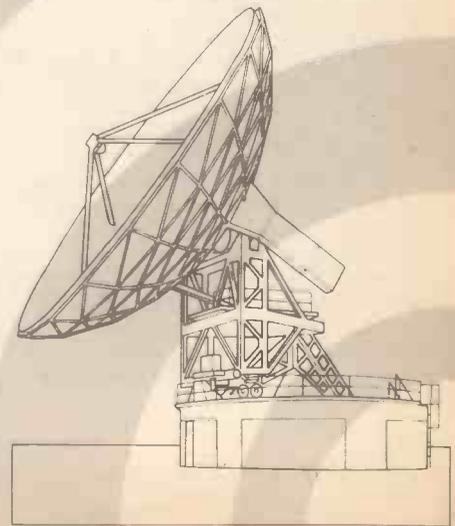

which has now been chosen by an Advisory Panel set up to examine alternative television systems for use with satellite broadcasts, and accepted by the Government. (The document to consult is *Direct Broadcasting By Satellite: Report of The Advisory Panel On Technical Transmission Standards*, HMSO Cmnd 8751, 1982, £5.20.)

A New Standard

MAC has been developed entirely to suit DBS's FM system, is technically more advanced than E-PAL, and is better suited to adapting for High Definition TV, which is still far off but definitely in sight in the future. It's a forward-looking system, much more than E-PAL, whose primary virtue (other than the fact that it is a good TV system) is that it is compatible with current TV receivers.

MAC has found favour with the commercial interests involved as well, including the cable TV companies since, as we said above, much DBS programming will make the final leg of its journey along the cables, being a cheaper option than each of us setting up a private dish aerial. Modifying E-PAL to meet all the cable companies' requirements looks like being uneconomic, so the Advisory Panel recommended MAC on this basis as well as that, having no sub-carrier, it would have been better suited to cable TV. They also decided, ironically, that it would be easier to adapt present receivers to MAC than to E-PAL, for comparable quality. MAC will also be easier to scramble to prevent unauthorised reception of DBS broadcasts — ie ones that haven't been paid for!

At the moment, the European Broadcast Union members are looking at the possibility of a single standard for the whole of Europe — a great boon if television is to have an international audience, and seen decidedly as a means of generating more revenue for the individual television companies. One effect of the increased diversification of television away from the licence-funded BBC with, effectively, only one (two since the arrival of Channel 4) commercial rival, is increased competitiveness between programme-makers and television transmitting bodies.

It is felt that MAC has a likelihood of being chosen as a common European standard, gradually superseding the variations on PAL and SECAM being used in Europe at present. It remains to be seen, of course, whether Europe will opt for MAC as a common standard at all! But EACEM, the European TV manufacturers' Association, has shown some interest in MAC. If television is to look into the future and not simply cling to existing technology, which is slowly but surely becoming outdated, then it makes sense to make bolder moves to help the new developments along.

You Pays Your Money . . .

The questions of exactly how

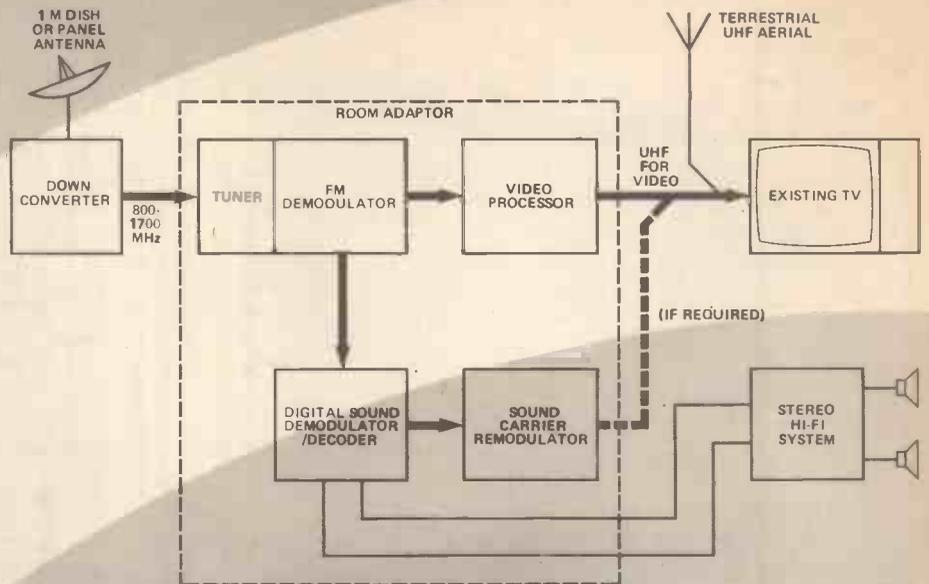


Figure 7. Stages in translating a DBS signal for a UHF receiver.

consumers will pay for their cable and DBS programming is far from being resolved. The government has decided against the 'pay-as-you-go' method for cable TV, and so it seems likely that this will be the case for DBS too, especially if DBS and cable are as intimately linked as it looks as though they might be. One projected method of getting a choice of channels to cable and DBS viewers' receivers is to have subscription channels, so that the viewer only receives the channels which he has paid to view. This also relieves the problem of a limited number of channels being available to any one receiver at one time.

Obviously some method of protection is required to prevent unauthorised viewing. There are two possible approaches to this problem, the negative, where the original signal is left intact, and the positive, where the signal is electronically encoded in some way.

An example of the first approach is the fitting of a filter in the consumer's feed which removes any channels which have not been paid for. There are two drawbacks to this: firstly there is an initially large capital expenditure in supplying filters, and secondly, the system is not very tamper-proof.

With this in mind, most systems have opted for some form of encryption. This can range simply from inverting the video to give a negative picture to nonconverting receivers, to the Rascal-Oak system, where each frame is randomly sent positive or negative modulated, with the sound sent as 'packets' of digital pulses inside the sync pulse. Of course, the more complex the encryption system, the higher the cost of the equipment needed by each consumer to decode the signal. If an operator accepts a protection ratio of about 90%, then an optimum system can probably be found.

Satellite and cable TV complement each other. And for a future National



British Aerospace Photograph

An array of solar cells, destined for a communications satellite, takes shape at British Aerospace.

Broadcasting System it is likely to be mandatory that all cable companies will distribute BBC and IBA programmes plus the DBS channels. This, together with single satellite receiving terminals for community TV distribution systems should prevent a sudden rash of unsightly dish aerials sprouting all over the countryside and will save the consumer money. But the individual in a rural area without cable will not miss out — a single dish aerial can be installed, for less than the price of a video recorder.

One thing looks certain: the terrestrial TV network is here to stay. Some areas, without cable, and also (especially in the north) facing more problems with clear DBS reception, will be largely reliant on the present system for many years to come. Nevertheless, the future would appear to be rosy, with plenty of exciting and innovative developments in the air — or should that be "in the pipeline"?

CALL IN AND SEE FOR YOURSELF


AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

TEST EQUIPMENT CENTRES ALL MODELS ON DISPLAY OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

DIGITAL MULTIMETERS (UK C/P Free)

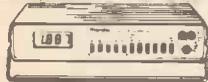

ALL MODELS 3 1/2 DIGIT UNLESS STATED



HAND HELD ■ With free carry case:
 KD25C=13 range 0.2A DC 2 meg ohm £24.95
 KD30S=16 range 10A DC 2 meg ohm £29.95
 KD30C=26 range 1A AC/DC 20 meg ohm £34.95
 KD55C=28 range 10A AC/DC 20 meg ohm £39.95
 6010+ 28 range 10A AC/DC 20 meg ohm £34.40
 7030+ As 6010 but 0.1% basic. £41.30
 KD615=16 range 10A DC 2 meg plus Hfe tester £39.95
 189M 30 range 10A AC/DC 20 meg plus Hfe tester £69.95
 HD30 16 range 0.2A AC/DC 2 meg ohm £41.95
 HD30/B As above plus cont. buzzer £44.50
 HD31 22 range 10A AC/DC 2 meg ohms plus cont. buzzer £58.95
 DM2350 = 21 range 10A AC/DC 20 meg ohm miniature hand held auto range £49.95
 Beckman T100 34 range 10A AC/DC 20 meg ohm £56.35

Beckman T110 As T100 plus Cont. test. etc. £67.85
 Sifam 22008 21 range 2A AC/DC 20 meg ohm £39.95
 +Optional carry case £2.95
BENCH MODELS
 TM353= 27 range LCD 2A AC/DC £86.25
 TM355= 29 range LED 10A AC/DC £86.25
 TM351= 29 range LCD 10A AC/DC £113.85
 +Optional carry case £6.84
 2001 28 range LCD 10A AC/DC plus 5 range Cap. Meter with case £108.00
 TM451 4 1/2 digit LCD every facility (0.02%) £171.00
 1503a 4 1/2 digit LCD every facility (0.05%) £171.00
 1503H a 0.03% basic version of above £189.00
 1504 true RMS version £201.25
 Sifam 2500 24 range LCD 2A AC/DC £99.95
 Metrix (ITT) professional 3 1/2 + 4 1/2 digit DMM's standard & true. RMS 4 models stocked £77.00 - £201.25

FREQUENCY COUNTERS



PFM200A MHz hand held pocket 8 digit LED £77.60
 8110A 8 digit LED bench 2 ranges 100 MHz £77.00
 8510B 9 digit LED bench 2 ranges 600 MHz £113.85
 8000B 9 digit LED 3 ranges 1 GHz £178.00
 TF040 = 8 digit LCD 40 MHz £126.50
 TF200 = 8 digit LCD 200 MHz £166.75
 ■ Optional carry case £6.84
 Prescalers - Extended range of most counters
 TP600 600 MHz £43.00
 TP1000 1 GHz £74.00

SIGNAL GENERATORS (220/240V AC)



FUNCTION : All sine/square/triangle/TTL etc TG100 1 Hz - 100 KHz £90.00
 TG102 0.2 Hz - 2 MHz £166.75
PULSE
 TG105 Various facilities 5 Hz - 5 MHz £97.75
 AUDIO : Multiband Sine/Square
 LAG27 10 Hz to 1 MHz £90.85
 AG202A 20 Hz to 200 KHz (List £94.50) £83.50
 RF
 SG402 100 KHz to 30 MHz (List £79.50) £69.50
 LSG17 100 KHz to 150 MHz £79.35

ELECTRONIC INSULATION TESTER

YF 501 500 V/0-100m with carry case £63.00

MULTIMETERS (UK C/P 65p)

HM102Z 20K/V 10A DC 22 range & cont. buzzer £13.50
 HM102Z 20 K/V 22 range & cont buzzer £14.95
 ETC5000/5001 21 ranges, 50K/V. Range doubler. 10A DC. £18.95
 TMK500 23 ranges 30K/V. 12A DC plus cont. buzzer. £24.75
 NH56R 20K/V. 22 range pocket £10.95
 ETU 102 14 range 2K/V pocket £6.50
 830A 26 range 30K/V. 10A AC/DC overload protection, etc. £23.95
 360TR 23 range 100K/V. Large scale 10A AC/DC plus Hfe £39.95
 AT1020 18 range 20K/V. Deluxe plus Hfe tester £18.95
 YN 360TR 19 range 20K/V plus Hfe tester £15.95
 Metrix Professional multimeters In stock 3 models from £74.75

VARIABLE POWER SUPPLIES (UK C/P £1.00)

PP241 0/12/24V. 0/1A £35.00
 PP243 3 amp version £59.95
 PS 1307S 8/15V 7 amp twin meter £24.95

DIGITAL THERMOMETER

TH301 LCD -50°C to +750° with thermocouple £68.43

AC CLAMPMETER

ST300 0/300A 0/600 VAC. 0/1 Kohm 9 ranges With carry case (UK C/P 65p) £28.50

LOGIC PROBES

LP10 10 MHz £28.50
 DLP50 50 MHz with carry case and accessories £52.33

OSCILLOSCOPES



Full specification any model on request. SAE by post.
HM Series HAMEG: 'SC' THANDAR: 'CS' TRIO: '3' CROTECH 'DT' Salfgan
SINGLE TRACE UK C/P £3.00
 3030 15 MHz 5mV. 95mm tube plus component tester C/P £3.00 £177.10
SC110A = Miniature 10 MHz battery portable Post free £171.00
 HM103 15 MHz 2mV. 6 x 7 display plus component tester C/P £3.00 £181.70
 ■ Optional carry case £6.84 AC adapter £6.69 Nicads £12.50

DUAL TRACE (UK C/P £4.00)

DT 520 Dual 20 MHz £241.50
 HM203/4 Dual 20 MHz plus component tester £303.60
 CS1562A Dual 10 MHz (List £321.00) £269.50
 3131 Dual 15 MHz + component tester £276.00
 CS1566A Dual 20 MHz All facilities (List £401.35) £349.50
 HM204 Dual 20 MHz plus component tester sweep delay. £419.75
 CS1820 Dual 20 MHz with extra facilities (List £508.30) £485.00
 OX710 Metrix dual 15 MHz + component tester £304.75

OPTIONAL PROBE KITS

X1 £7.95 X1- X10 £10.50 X10 £29.45 X100 £16.95

HIGH VOLTAGE METER

Direct reading 0/40 KV. 20K/Volt. (UK C/P 65p) £23.00

DIGITAL CAPACITANCE METER

0.1 pF to 2000 mfd LCD 8 ranges DM6013 £52.75 (Carry case £2.95)

TRANSISTOR TESTER

Direct reading PNP: NPN, etc. TC1 (UK C/P 65p) £21.95

AUDIO ELECTRONICS

Cubegate Limited

301 EDGWARE ROAD, LONDON W2 1BN. TEL: 01-724 3564
 ALSO AT HENRY'S RADIO.
 404/406 EDGWARE ROAD, LONDON, W2. TEL: 01-724 0323
 HENRY'S COMPONENT SHOP. TEL: 01-723 1008

FREE CATALOGUE SEND LARGE SAE (UK 20p)

ALL PRICES INCLUDE VAT

Order by Post with CHEQUE/ACCESS/ VISA or you can telephone your orders. All orders despatched within 8 days unless advised.

EASY ADD-ONS for ZX81-SPECTRUM-ACE

NEW



17 exciting electronic projects to build and run on your own micro.

- LIGHT PEN
- PICTURE DIGITISER
- KEY PAD
- MODEL CONTROLLER
- WEATHER STATION
- + OTHER EXCITING & INTERESTING PROJECTS

REALISE THE REAL WORLD POTENTIAL OF YOUR MICRO.

A newly released book written by well known author Owen Bishop and published by Bernard Babani gives fully descriptive details on how to build all 17 projects - all are fairly simple and inexpensive to construct - The most complex component (the DECODER) is supplied in kit form ready to assemble with all components and plated through PCB. - Components for the projects are readily available locally or found in your workshop drawers.

Once assembled and connected to your micro the decoder is able to run any or all of the projects simultaneously.

Simple Programmes are included to get you started but of course the more experienced programmer can have hours of fun writing complex programmes to take full advantage of these easy but exciting projects.

Please Send By Return (allow 28 days for delivery)

QTY	REF	DESCRIPTION	PRICE	TOTAL
	HB/2000	"EASY ADD-ONS" + DECODER KIT & BOOK	£24.00	
	HB/2001	"EASY ADD-ONS" BOOK ONLY	£3.00	
	HB/2002	DECODER KIT ONLY	£22.00	
	HB/2003	DECODER PCB ONLY	£8.00	
			TOTAL	

Price inclusive of VAT & carriage. Please allow 21 days for delivery. Cheques, PO's or signed Access orders welcomed.

Please Send Full Hobbyboard Mail Order Catalogue with full range of PCB materials & Hardware

Name
 Address

hobbyboard

a division of
 KELAN ENGINEERING LTD
 Hookstone Park
 Harrogate, N. Yorks

complete P.C.B. workshop

HE 9/83

POINTS OF VIEW

Feel like sounding off?
Then write to the Editor stating your Point of View!

Alternator Alternatives

Dear Editor,
In HE May '83, you replied to M. J. Maddison regarding the use of car alternators. Perhaps the following information may be of assistance in what is usually a very misunderstood subject.

Firstly, the different categories must be appreciated.

1. Six diode alternators: these require an external source of current to energise the motor, usually via a relay. (Examples: Lucas 11AC, Duceillier AC28, Simms (early model), CAV AC7 (early model), etc.)

2. Nine diode alternators: self-exciting, that is, they have some residual magnetism in the rotor. (Examples: Lucas 15AC, 16AC, 17AC, 20AC, etc., CAV AC7, AC203, BUTEC A10, Bosch, Ducellier, Motorola, Hitachi etc.)

3. Permanent magnet alternators, usually single phase and usually fitted to motor-cycles but there are exceptions.

4. Nine diode alternators with the voltage regulator fitted as in integral unit. These are a modification on category 2.

The current output of the alternators using a wound rotor is achieved by sensing the output voltage which in turn is used to control the current flowing through the rotor. Permanent magnet rotor alternators again sense the voltage, but utilise thyristors to control the output current.

In regard to using any alternator driven by a windmill, what must be looked at is the desired voltage (bearing in mind batteries will have to be used) and the speed at which the alternator produces a current of 0.5A (cutting-in speed).

Obviously by using a 12V regulator on a nominal 24V alternator suitable control can be achieved with a lowering of the cutting-in speed. However, if the alternator is chosen with this in mind, an alternator can be found which will begin to charge at 250 rpm.

In the main these units are those which are direct drive on a diesel engine, which are slow running anyway.

In this country the two units which are suitable are the 12V or 24V BUTEC H10 units as fitted to Gardener diesel etc. The 12V unit gives up to 100A at full stick with the 24V unit giving over 30A. The CAV AC203 from a bus (note: not a coach) is completely sealed and gives 80A at 28V and uses a voltage and a current

regulator. The snag is that these are expensive.

The choice of what he uses in Kimbali depends on what is available. It is probably that an oriental unit is a better choice out there.

Fancy electronic control systems are not required as the standard units are usually OK. The BUTEC regulator is completely repairable with a 6V7 Zener, a BC108 and a 2N3055 plus a few other bits.

If a small car gearbox is used driven backwards, ie the windmill blades driving the gearbox at the propshaft end and the alternator mounted where the clutch is normally four or five differing alternator speeds would be available. You could even drive the alternator backwards and be astounded that it worked exactly the same as forwards!

Finally, Bosch manufacture a special unit which fits on the axle box of a railway wagon to supply power for lighting, refrigeration etc. This works as soon as the train moves, no matter how slowly.

Yours faithfully,
H. D. Briggs,
Telford,
Shropshire.

PS. Regarding the "Stall Thief" (HE May '83), this can be achieved to a great extent by supplying the relay winding from the warning light terminal on the alternator. This terminal is the auxiliary output from the three diodes whose purpose is to supply the rotor energising current. The voltage goes from 0V when stationary to system voltage 12V or 24V at cut-in speed.

This means that any relay so connected will function at tickover or a slightly higher engine speed. With the relay fitted as in the Stall Thief on a mini, for example, the engine will be governed to a speed of about 550rpm, which means it takes about fifteen minutes to drive it off a pub car park.

Extra connections on the coil or distributor are a giveaway to the "tea leaf". The old Triumph 1300 got over this by using a thin but sturdy coax which looked like standard car-type cable.

Thanks for the suggestion. The Stall Thief author says, yes, this is a simple and ingenious adaptation which should present no problems.

Incidentally, the Police reckon that if you can stall your Tea Leaf for fifteen or twenty minutes, he will tend to feel that easier pickings can be had elsewhere. "If he's really determined to get in", they say "He will". The art is to confuse him into giving up!

Ignition Transformations

Dear Sirs,
I have just made the HE electronic ignition from HE April 1980 and have a small problem with it.

The spark is small and weak and therefore cold-starting is non-existent, but once running it seems to be ok. Instead of the large 47k resistor I have had to put a 56k one in, the storage capacitors although the correct value are a higher voltage, and thirdly there is a small possibility that the transformer may be a 12V one.

Please could you indicate which of the above three might cause the problem or anything else that might cause a very poor spark.

Yours faithfully,
Richard Stummer,
Dibden,
Hampshire.

You have three problems here. First, there is no 47k resistor in the circuit to change; the large resistor R9 is 47R, not "k", and the correct value (47 ohms) should be used.

The transformer is used as a step-up transformer, and the larger the ratio the larger the voltage induced in the primary. Since 9:240 equals 1:26 and 12:240 equals 1:20, a 12V transformer will not produce as much primary voltage.

The third problem you may not be aware of: the transformer is a 9-0-9V type, and a centre-tap must be connected to the V+ line, immediately below T1 on the circuit diagram. This connection was omitted from a published circuit.

As long as the voltage rating of the capacitors is higher than that specified, you're quite safe.

Ignition Transformation Part II

Dear Sir,
Some time ago I built the HE CD Electronic Ignition system from HE April '80. The design performs very well. I noticed that you recommend this unit for use with four or six cylinder negative ground cars, 12V. What if I wanted to use your design on my Honda CG125 motor cycle? Is this possible? It's 6V, single cylinder four stroke).

I thought that a change in the transformer voltage - say a 6-0-6 secondary, might compensate for the 6V ignition system - but do I need to change any other values? eg C3, C4 and/or R7 and 88? I would be very grateful if you could advise me.

Thanking you for your time and hoping to hear from you soon.
Yours faithfully,
C. S. Thompson,
Levenshulme,
Manchester.

There is no easy answer to this one — it effectively needs a redesign on the circuit, which we are not able to do. Have any other readers tried adapting this system for a motorbike?

Components Quest

Dear Sir/Madam,
I have written to you to ask for some information. The problem is that in your magazine the majority of addresses of electronic component suppliers are in the south and I would like to know the addresses of suppliers in the Birmingham area. This would be very convenient as I live in a small town near Birmingham.
Yours faithfully,
A. Patel,
Bilston,
West Midlands.

That's interesting — I hadn't noticed that there was a southern bias in our components directory. It's not intentional. We contacted every supplier whose address we actually had, and with a few exceptions who either did not want hobby custom or had moved away, we published details from all of them.

Your first and best recourse is the Yellow Pages phone directory, which you will find in your public library. Try phoning names under "Electronics Components Suppliers" and "Radio Equipment Suppliers" and anything similar. When you ring up, ask the person you speak to if he or she knows of any other suppliers locally. Do that a few times and you will be able to build up a file of suppliers in your area.

Your other solution, of course, is to go mail-order.

Look What The Cat Dragged In . . .

Dear Ed,
With reference to my Radio Controlled Gerbil project (HE April '83): I was perturbed to see some of your readers thought this was a 'joke'. As a professional electronics designer, such correspondence put into print could seriously damage my career. Indeed, the Arts Council have already rescinded their grant so work on follow-up projects such as the Robot Muskrat and Solar Powered Tortoise have been put in jeopardy (a small town in Suffolk, I believe.) I am currently trying to raise funds from the RSPCA, but if this dogged criticism continues my chance of sponsorship will be catastrophically affected.

Don't these people realise that without such advances in rodent technology the human race would

never have been able to put non-stick frying pans into space?? It's time they took their heads out of the sand, and stuck them in the nearest microwave.
Yours sincerely,
Dave Fountain,
2 Rat Terrace,
Clacton-on-Sea,
Essex.

PS. Whatever you do, don't print my address in the magazine.

You don't know when you're well off, mate! Never mind the outraged readers. Hibernia The Balrog wants to see you about your abuse of semicolons, and our technical department who has been scouring restaurants in vain for Artificial Gerbil Fur, wants a word with you, too. All he was offered was a load of 'fresh' stuff, and that was full of bullet holes, too. On the bright side, some minor modifications made in the office mean that you can apply to the British Confections Council for further sponsorship. Where did you say you lived?

Instant Assistants

Dear Sir,
I am writing with reference to a letter in HE April '83 from Paul Jenkin of Cornwall. In this letter he raised a couple of queries. 1: I have traced some references to an MOC3020 in an old RS catalogue which describes it as an opto-coupled triac. This is in the July to October 1981 edition of the catalogue. I take the liberty of quoting data from the catalogue:

Technical specification: diode: 1f max. 50mA at 25°C; Vr max. 3V; Vf max. 1.5V at 1f 10mA; triac: Vorm 400V; It (rms) max. 100 100mA; Vtm 3V at It 100mA; coupled characteristics: input current to trigger triac 5mA typ. 20mA Max. (main terminal voltage 3V, 150R load); isolation voltage (peak withstanding) 7500VAC for 5s; operating temperature range -40°C to +100°C. Pin 1 is the anode, pin 2 is the cathode and pin 5 is labelled 'substrate, do not connect'.

With regard to his query on data for the Ferguson 3400, has Mr. Jenkin checked his local reference library? They might have copies of Electrical and Electronic Trader magazine, who may have done one of their excellent service sheets on the 3400. I hope that some of this information may be of assistance.

To change the subject, I have noticed that magazines specialising in CB Radio are fast disappearing from the market, but there must still be a considerable interest in CB. As HE was one of the first UK mags to cover CB (if not the first?) how about resuming some coverage of CB?
Yours faithfully,
M.L. Peake,

Bilston,
West Midlands.

PS What is an HE binder?

Thank you very much, Mr. Peake. To show that CB is far from a lost cause, not only is our relation CB Radio Today still flourishing but we have also had a new arrival recently in Ham Radio Today. Ironically, one spinoff of CB radio has been an increase in the popularity of amateur radio. Can't be bad! On top of that, HE still runs articles (our popular Radio Rules series concluded last month) and projects on amateur and CB — see our CB Selective Caller project in HE January '83, for instance.

Dear Sir,
With reference to the letter published on page 17 of your April issue from Mr. Paul Jenkin, I am enclosing some information concerning the device about which he enquired and would be obliged if you would kindly pass it on to him in the stamped envelope also enclosed.
Yours faithfully,
J. G. Lewis,
Saintfield,
Co. Down.

Dear Sir,
In the April issue a reader enquired about a device marked MOC3020 . . . this is manufactured by Motorola and consists of an LED optically coupled to a silicon bilateral switch. They are for applications requiring isolated triggering of triacs.
Ray Harris.

There you are . . . ask and it shall be given unto you. Our thanks to Mr. Lewis and Mr. Harris. We will pass on the information to Mr. Jenkin as soon as we can extract his address from our April file.

HEBOT Hint

Dear Sir,
In HE November '82, you showed the HEBOT II compatible with the ZX81. I own a 16K ZX Spectrum. Will HEBOT work on this, will I need an interface, if so which one and will all the poles be the same in the programs? I am a new learner to computers and electronics so please can you reply advising me on these matters.
Yours gratefully,
A. J. Arnsby,
Cleestanton,
Shropshire.

No, the interface actually supplied with HEBOT II will not operate on a ZX Spectrum. The HEBOT decodes address lines A6 to A15, and if you look at the table of edge connector functions accompanying the ZX Sound Board project (see HE June '83), you will see that the Spectrum and ZX81 edge connectors, while very similar, are not compatible for addresses above A12. HEBOT's address will be different, but if you use the interface board published in HE September '82, you will have full use of your 16K memory because, when set up to operate from the Spectrum, this board addresses I/O space, rather than memory space.

Send for my **CATALOGUE ONLY 75p**

(plus 25p post/packing)

My all-inclusive prices quoted in the Catalogue are the lowest. All below normal trade price — some at only one tenth of manufacturers quantity trade.

See my prices on the following:

CAPACITORS . . . ELECTROLYTIC; CAN, WIRE END, TANTALUM, MULTIPLE, COMPUTER GRADE, NON POLAR, PAPER BLOCK, CAN, POLY, MICA, CERAMIC. LOW AND HIGH VOLTAGE, RESISTORS. 1/8th WATT TO 100 WATT; 0.1% TO 10% CARBON, METAL AND WIRE WOUND + NETWORKS. FANS, BATTERIES, SOLENOIDS, TAPE SPOOLS, VARIABLE CAPACITORS AND RESISTORS, TRIMMERS, PRESETS, POTS . . . SINGLE, DUAL, SWITCHED, CARBON, CERMET AND WIREWOUND, SINGLE OR MULTITURN, ROTARY AND SLIDE. DIODES, RECTIFIERS, BRIDGES, CHARGERS, STYLII, SOCKETS, PLUGS, RELAYS, TRANSISTORS, IC'S, CLIPS, CRYSTALS, ZENERS, TRIACS, THYRISTORS, BOXES, PANELS, DISPLAYS, LED'S, COUPLERS, ISOLATORS, NEONS, OPTO'S, LEADS, CONNECTORS, VALVES, BOOKS, MAGAZINES, TERMINALS, CHOKES, TRANSFORMERS, TIMERS, SWITCHES, COUNTERS, LAMPS, INDICATORS, BELLS, SIRENS, HOLDERS, POWER SUPPLIES, HARDWARE, MODULES, FUSES, CARRIERS, CIRCUIT BREAKERS, KNOBS, THERMISTORS, VDR'S, INSULATORS, CASSETTES, METERS, SOLDER HANDLES, LOCKS, INDUCTORS, WIRE, UNITS, MOTORS, COILS, CORES, CARTRIDGES, SPEAKERS, EARPHONES, SUPPRESSORS, MIKES, HEATSINKS, TAPE, BOARDS and others.

Prices you would not believe before inflation!

BRIAN J. REED


TRADE COMPONENTS

ESTABLISHED 26 YEARS

161 St. Johns Hill, Battersea, London SW11 1TQ

Open 11 am till 7 pm Tues. to Sat. Telephone: 01-223 6016

LITTLE SOLO

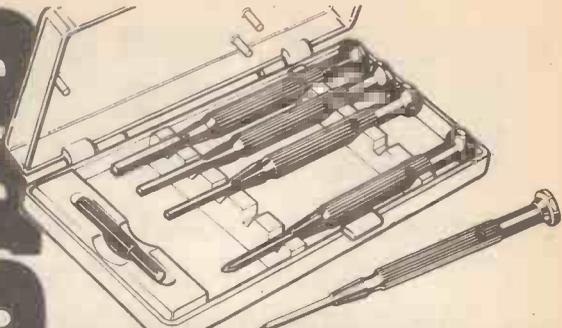

MINIATURE TOOL SETS AT MINIATURE PRICES

Ideal for work on optical and electronic equipment, instruments and models. Japanese made, top quality metric tools in hardened and tempered steel, with fitted plastic cases. Swivel-top, chromium-plated brass handles. Not to be confused with similar cheap non-Japanese sets.

SCREWDRIVER SET 113. 6 plain screwdrivers, blades 0.9, 1.2, 1.8, 2.3, 3.0 and 3.5mm. Price £2.70.

SOCKET SET 227. 5 socket spanners, 3.0, 3.5, 4.0, 4.5 and 5.0mm. Price £2.80.

CROSSPOINT/HEXAGON SET 305. 2 Japanese crosspoint screwdrivers, sizes 0 and 1. 3 Hex. key wrenches 1.5, 2.0 and 2.5mm. Price £2.70.

COMBINATION SET 228. 5 open spanners 4.0, 4.5, 5.0, 5.5 and 6.0mm. 5 socket spanners 3.0, 3.5, 4.0, 4.5 and 5.0mm. 2 crosspoint screwdrivers bit sizes 0 and 1. 3 screwdriver bits 1.5, 2.5 and 3.5mm. 3 Hex. keys 1.5, 2.0 and 2.5mm. 1 scriber. 1 swivel-top driver/holder. Price £4.83. All prices include postage and 15% VAT.

Ring for Access/Barclaycard Sales or send remittance to:



Light Soldering Developments Limited, 97-99 Gloucester Road, Croydon, Surrey CR0 2DN. Tel: 01-689 0574.

Grab a Banana

Pantec's revolutionary hand held multimeter introduces a new concept in low cost, high sensitivity meters. Banana's full range of functions make it a must for the electronics hobbyist.

- It's shock-proof
- It's totally protected up to 250v AC/DC
- It's got audible bleeper for continuity checks and battery test
- It's got permanently connected probes (no socket selection)
- You can operate it with one hand
- It's only **£25.99**

incl. VAT and UK P/P



SPECIFICATIONS

- Sensitivity: 20kΩ/V DC and 10kΩ/V AC
- DC Volts: 0.5-5-25-100-500V
- AC Volts: 50-250-1000V (max 750V)
- DC Current: 50μA-50mA-500mA-2.5A
- Resistance: Up to 2MΩ in 3 ranges
- Accuracy: 2% DC - 4% AC
- Dimensions: 173 x 86 x 29 mm
- Weight: 200g
- Supplied with soft carrying case and spare fuse

Write or phone for details

The Banana Multimeter

PANTEC

Carlo Gavazzi (UK) Ltd.,
162/164 Upper Richmond Road,
London SW15 2SL
Tel: 01-785 9022 Telex: 8952493

TREMOLEKO

A classic echo-effect unit is expensive to make, but the HE Tremoleko not only gives a fair echo effect, but is inexpensive and straightforward to build — ideal for the guitar player who wants to experiment with different effects.

R. A. Penfold

THE CONVENTIONAL WAY of electronically processing a signal to give an echo effect is to use a delay line of some kind, to give a delay of between 100ms and 1 second, and to feed the delayed signal back to the input of the line. The signal is therefore fed through many times, getting weaker each time it is fed back to the input and giving a good analogy of a natural echo and an excellent sound effect.

An obvious drawback of this system is the cost of a delay line which gives a sufficiently long delay time for this application. A bucket brigade type, having a few thousand delaying stages, is the lowest cost approach but even this method is not particularly cheap.


But there is an alternative system which is very simple and inexpensive indeed. Results obtained are not as good as those using more sophisticated techniques, which give a true echo effect, but it is a system well worth trying if a true echo is not feasible within your budget, or if you like experimenting with simple effects units.

The technique is simply to "chop" up the signal from a synthesiser or any other electrical or electronic instrument which has a suitable output signal. The main requirement is that the instrument should have a fast attack plus a relatively slow decay, like the envelope shown in Figure 1(a). Any monophonic synthesiser should be capable of giving a suitable output signal, and a guitar also gives an output of the correct type. When the signal is



"chopped" by effectively just switching it on and off at a rate of a few Hertz, this gives an envelope of the type shown in Figure 1(b).

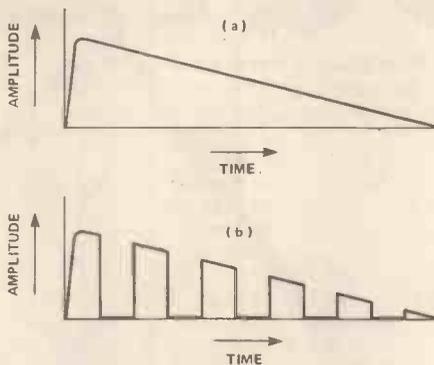This gives a signal which is similar to that obtained if a short burst of signal is applied to an echo effect unit, with an initial high signal level followed by a signal bursts of identical length but steadily decreasing amplitude, and quite interesting results can be obtained in practice, especially if the unit is used in conjunction with other effects such as



spring-line reverberations. However, it is important to realise that the effect obtained is not a genuine echo, and that a signal having a long decay is needed at the input to give an output which sounds like a short percussion signal. Results are not likely to be very convincing if the input signal does not have a suitable decay characteristic, or if the signal changes considerably as it dies away. A voice signal, for example, would probably not give good results when used with the unit (although you might find the effect interesting even though it might not be at all convincing as an echo effect).


The Circuit

A simple VCA based on a VMOS transistor is used as the basis of the unit, as can be seen from the circuit diagram of Figure 2.

A VMOS transistor has a very high drain-to-source resistance if the forward gate bias is zero (or very low), but this resistance drops to about 2 ohms if a forward gate bias of a few volts is applied to the device. In this circuit the VCA is formed by R6 and the drain-to-source resistance of Q1. There is very little voltage drop through R6 when Q1 is switched off,

Figure 1. How the input signal is 'chopped' by the Tremoleko.

Figure 2. The circuit.

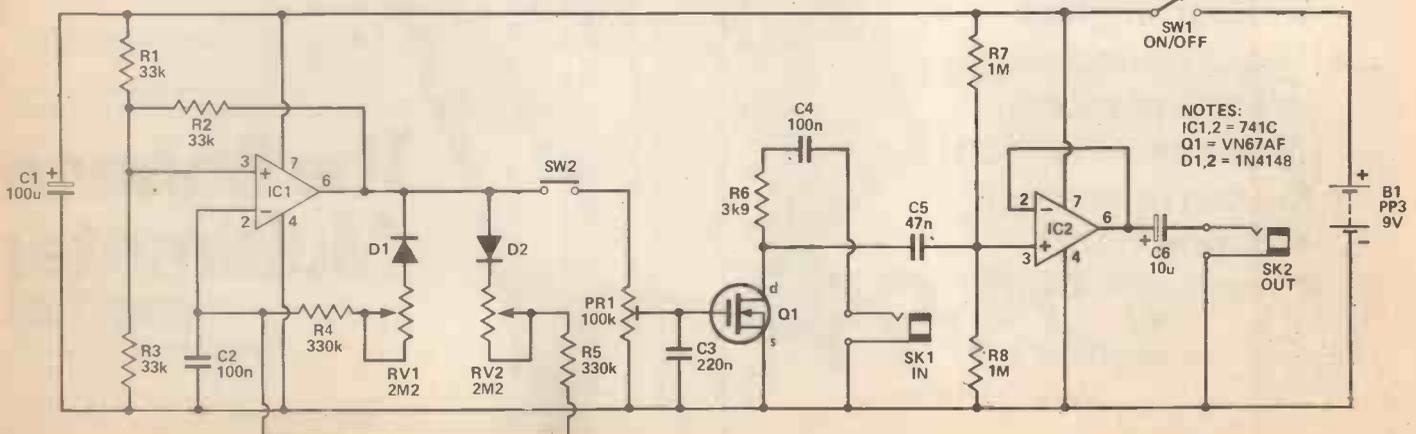

due to the high input impedance of the buffer amplifier formed by IC2 and its associated components, so the signal reaches the output virtually unattenuated, but when Q1 is switched on, most of the input voltage is dropped across R6 and a high level of attenuation (typically about 66dB) is produced.

Although this is a fairly crude form of VCA it is adequate for the present application, and does have an important advantage over most of the more complex alternatives in that there is no DC shift at the output as the circuit switches from the high attenuation state to the low attenuation one, and vice versa. This avoids the generation of "clicks" or "thuds" which would inevitably result if even a small DC voltage shift was produced by the circuit.

"Clicking" sounds could also be generated if the VCA was switched very rapidly between states so that the "chopped" signal had a very rapid rise and fall time. This would give a very unnatural effect, and much better results are obtained if the switching speed is slightly, but significantly slowed down. This is the purpose of C3.

IC1 is used in the pulse generator circuit, in what is basically a well known and frequently used configuration. However, it is slightly different to the standard circuit in that steering diodes D1 and D2 have been included in the timing circuit, and this gives separate timing resistances for the high and low output periods of the circuit. R4 and RV1 control the low output time while R5 and RV2 control the high output period. Apart from permitting the mark-space ratio of the control signal to be adjusted, these two controls also give a substantial degree of control over the operating frequency of the pulse generator. The frequency range is from about 2HZ with both RV1 and RV2 at minimum resistance to over 10HZ with both controls set at maximum.

SW1 enables the output of the pulse generator to be disconnected from the VCA; Q1 is then cut off, the input signal passes straight through to the output, and the effect is cut out. RV3 is needed to match the output voltage swing of the pulse generator to the input requirements of the VCA, and to an extent the effect obtained




How It Works

The input signal is passed through a voltage controlled attenuator (VCA) and then to the output signal socket by way of a buffer amplifier. The latter is simply needed to give the unit a low output impedance and to ensure that the output of the VCA is not excessively loaded. The VCA will provide an easy path for the input signal if the control voltage is low, but it will provide a very high level of attenuation and effectively block the input signal if the control voltage is a few volts or more.

A pulse generator is used to generate the control voltage, and as this has an output voltage which switches between virtually the negative supply voltage and almost up to the positive supply potential, the VCA is switched between its minimum and maximum attenuation levels. This gives the required "chopping" of the input signal to give the quasi-echo effect.

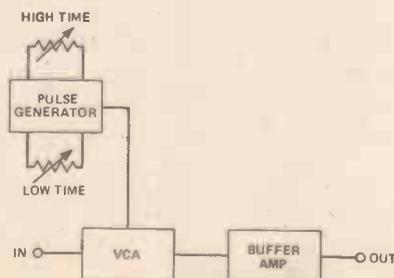Two controls enable the high and low output times of the pulse generator to be independently adjusted, and this gives a useful degree of control over the effect obtained. Apart from enabling the "chopping" frequency to be adjusted, it enables short bursts of signal to be allowed through the VCA, short gaps to be placed in the signal, or the on and off periods of the signal to be roughly equal.



Parts List

RESISTORS

(All 0W25 carbon)

R1, 2, 3	33k
R4, 5	330k
R6	3k9
R7, 8	1M

POTENTIOMETERS

RV1, 2	2M2
	1 in carbon
RV3	100k
	0W1 horizontal preset

CAPACITORS

C1	100u 10V
	axial elect
C2, 4	100n
	polyester
C3	220n
	polyester
C5	47n
	polyester
C6	10u 25V
	axial elect

SEMICONDUCTORS

IC1, 2	741C
	op-amps
Q1	VN66AF or VN67AF
	VMOS transistor
D1, 2	1N4148
	g.p. silicon diodes

MISCELLANEOUS

SK1	6.32mm jack
	with DPDT contacts
SK2	6.35mm jack
B1	9 volt PP3
SW1	heavy duty
	push button switch
	105x80x50mm diecast aluminium
	box; battery connector; two control
	knobs; printed circuit board; two 8-
	pin DIL IC sockets; Veropins; wire,
	etc.

BUYLINESpage 34

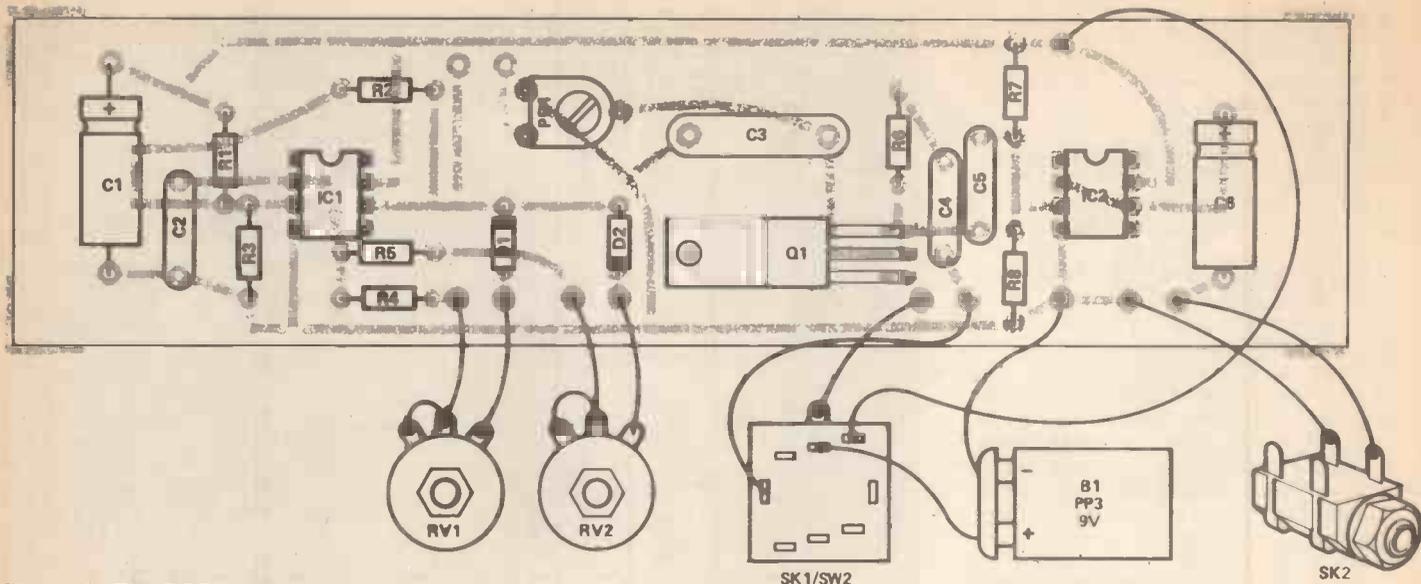


Figure 3. The PCB and components.

can be varied using RV3 since it sets the depth of the amplitude modulation.

The current consumption of the circuit is about 4mA, so a PP3 9V battery is an adequate power source.

Construction

Details of the printed circuit board are shown in Figure 3. Q1 is a MOS device, but both the VN66AF and VN67AF types have built-in 15 volt Zener protection diodes which render normal MOS handling precautions totally unnecessary. These devices are power types, but lower power VMOS devices (such as the VN10KM) should have a low enough "on" resistance to give good results in this circuit. Also the two devices specified are reasonably inexpensive and are readily available! Q1 is mounted horizontally so that it does not protrude too far above the board and prevent it from being installed in the case. This device dissipates an insignificant amount of power and obviously does not require a heatsink, but it is a good idea to bolt it to the printed circuit board so that it is firmly anchored in place.

In other respects construction of the board is quite straightforward, but the careful to fit the semiconductors the right way round. Also, it is helpful to fit Veropins at points where connections to off-board components will be made.

A diecast aluminium box having approximate outside dimensions of 150 x 180 x 50mm is reasonably inexpensive but makes a very tough and neat housing for the project. SW1 can be a heavy duty push button type fitted on the top panel of the case, and it can then be operated by foot (although an ordinary toggle or other type can be used if preferred). The two other controls and the two sockets are mounted on the front panel (one of the 150 by 150mm sides of the case), and SW2 is a set of

make contacts on input socket SK1. The unit will therefore switch on and off automatically when a jack plug is inserted into or removed from SK1. A socket having a single set of make contacts does not seem to be available so a type having DPDT contacts is used for SK1, but note that only two of the six switch tags of this component are connected into the circuit and that the other four are ignored. Of course, if preferred SW2 can be an ordinary switch and SK1 can be a standard unswitched socket.


When the printed circuit board has been connected to the rest of the unit using the usual multistrand hook up wire, the board can be fitted in place inside the case. It slots into a set of guide rails, fitting into the set nearest the rear of the unit with the component side of the board facing towards the front of the unit. There are several suitable spaces where the battery can be positioned.

In Use

The unit is simply coupled between the instrument and the amplifier using normal screened jack lead.

Signals of up to about 5 or 6 volts peak to peak can be processed without clipping and severe distortion being produced, and as the noise level of the unit is quite low there should be no difficulty in using it with a fairly low level signal such as that obtained from a low output guitar pick-up. Thus, in most cases there should be no problems when the unit is connected into a system, but it would be advisable to use some preamplification if the unit is fed from a very low level source such as a microphone.

A little experimentation with the two pulse length controls plus the controls of the synthesiser or other instrument should soon show what settings give the best effects. Similarly, a little experimentation with RV3 will enable it to be set for optimum results. In general, the further RV3 is advanced in a clockwise direction the deeper the amplitude modulation of the input signal, but if RV3 is advanced too far it will probably be found that Q1 becomes permanently switched on and little output signal at all will be obtained!

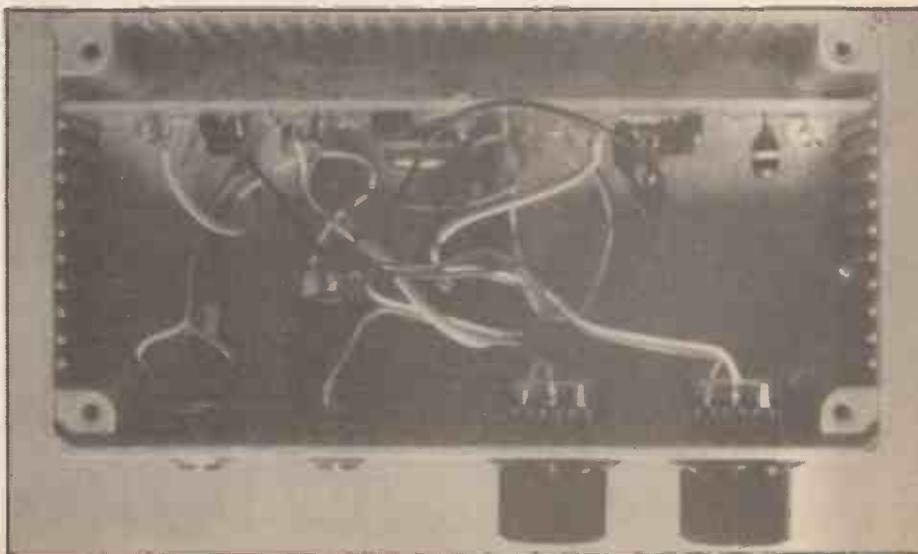

MASTER ELECTRONICS NOW! The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY
THIS IS THE AGE — OF ELECTRONICS!
the world's fastest growth industry...

There is a world wide demand for designers/engineers and for men to service and maintain all the electronic equipment on the market today — industrial — commercial and domestic. No unemployment in this walk of life!

Also — the most exciting of all hobbies — especially if you know the basic essentials of the subject. . . .

A few hours a week for less than a year — and the knowledge will be yours. . . .

We have had over 40 years of experience in training men and women successfully in this subject.

Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.



British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE!

COLOUR BROCHURE



POST NOW TO

Please send your brochure without any obligation to

NAME _____

ADDRESS _____

HE/9/841

BLOCK CAPS PLEASE

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS please state below

OR TELEPHONE US
0734 51515 OR
TELEX 22758
(24 HR SERVICE)



British National Radio & Electronics School Reading, Berks. RG1 1BR

Shelley Partridge

LAST MONTH we looked at starting a career as a Transmitter Engineer with the Independent Broadcasting Authority or the BBC. This month we will concentrate on opportunities for trainee Engineers and Technical Operators in television and radio stations.

Some of you may well be attracted by the idea of playing a creative part in TV or radio programme making through operating sound or camera equipment in a studio. Perhaps you have used video cameras at school or college, or built your own hi-fi equipment; perhaps you belong to a cine club, are a radio ham or work for a hospital radio station, and therefore you would like to make your career working with technical equipment in broadcasting. Because so many people want to work in broadcasting, competition for trainee posts is always fierce. However, you are someone who has a clear idea of the job you would like to do, have found out what qualifications you need to apply for training, and are determined to obtain these qualifications and you are already a dedicated amateur and the kind of person who can work in a team, and cope with some pressure and hassle, then your chances of getting started in a broadcasting career have never been so good as they are now and will be over the next few years.

Both radio and television broadcasting are expanding. The BBC now provides two and a half extra hours of television each day in its Breakfast TV show; Independent Television's new company TV-AM began transmitting in February this year; Channel 4 went on air in autumn '82. Channel 4's money has stimulated the setting up of many independent film and video production companies. Facilities companies providing television studio space, post-production services and technical expertise to these independents to make programmes for broadcasting and other purposes (training, sales, corporate communications), have been springing up, particularly in London, but also now in other regional centres. Cable and satellite television are only just around the corner, as you know only too well from this month's cover feature.

So let's consider which organisation may offer trainee opportunities, and what they will expect from you in the way of personal and academic qualifications, then look at recruitment and training patterns for each major broadcasting organisation, and conclude by offering some basic tips on how to get started.

Where The Work Is

The BBC employs some 28,000 people in radio and television, with a substantial concentration in various locations in central and west London, but also at regional centres throughout the country. The BBC is the only broadcasting organisation which recruits school and college leavers regularly as trainees into a limited number of job categories. For the

CAREERS IN ELECTRONICS

Hobby Electronics looks at the varied world of Studio Engineers in broadcasting.

'83



Picture courtesy BBC.

financial year 1983/84 the BBC are recruiting far more technical trainees than in recent years and anticipate that trainee recruitment will remain at a high level over the next several years.

Collectively the sixteen Independent Television Companies (including TV-AM), plus Independent Television News (owned by all the ITV companies except TV-AM which has its own news service), employ nearly the same

numbers in television broadcasting. These employees are, however, dispersed in much smaller units. Thames Television, for example, the largest ITV company, employs about 2,500 people in its Teddington and Euston studios. There are now forty Independent Local Radio stations on air, spread throughout the country, and another ten due to come on air in the next year or so. They vary in size from



Monitoring sound and vision signals before transmission.

Picture copyright Thames Television.



Picture courtesy BBC.

Tape editing in a BBC television sound gallery.

fewer than thirty employees to over one hundred. The Independent Broadcasting Authority is responsible for selecting and appointing ITV and ILR companies; supervises programme planning; controls the advertising and transmits the programmes for all the Companies.

Each ITV and ILR company recruits staff individually. Most of the ITV companies recruit trainees from time to time, the five largest — Thames, London Weekend, Yorkshire, Granada, Central Independent — taking the majority. Although one or two ITV companies (notably Thames and ITN) recruit technical trainees regularly and provide systematic training, in general trainees are recruited on an ad hoc basis when needed, and training is informal.

Basically both the BBC and ITV companies are looking for the same sort of young people to train as engineers and technical operators, in terms of qualifications and qualities, the numbers taken on by the ITV companies being just simply much smaller. This means that competition is always severe for the relatively few trainee posts which do arise in Independent Television, most recruitment being of people with relevant experience. However, in 1983 due to the current

expansion in broadcasting generally and difficulties in finding suitably experienced technical staff, a number of ITV companies are recruiting engineering and technical operations trainees.

Channel Four is a programme commissioning, not a programme making company. Its staff consists of experienced broadcasters and producers (who plan and coordinate programming), administrators and transmission engineers. The Channel is currently commissioning up to 50% of its programmes from independent film and video companies as well as from the other ITV companies. A few independents are large enough to have their own small studios and editing facilities; many use the studio and post-production services of the television facilities companies. Some of these companies are now beginning to recruit trainee operators and audio/video engineers since qualified and experienced people in these fields are in short supply.

Recruitment And Training

Broadcasting organisations demand a variety of pre-entry qualifications from

young people who apply for trainee positions. These employers are also at least as concerned to see how you have demonstrated keen interest through practical amateur activities. Applicants selected for training are more likely to have participated, for example, in a local cine or photographic club; college video or radio programme making, hospital or local radio; may have built hi-fi and electronic equipment, run a disco, recorded a pop group, or play a musical instrument. Appreciation is not enough; you need practical experience gained preferably on your own initiative rather than through school studies alone . . . in other words the sort of people who read *Hobby Electronics*!

Whatever the differences between broadcast radio and television and the video industry in terms of recruitment and training, the personal qualities you need to succeed in these organisations are similar. You should be able to work as a member of a team, long often irregular hours and remain calm and efficient under pressure. You need lots of common sense, a cheerful co-operative personality, and a bright, alert, inquiring mind. All these employers would like to encourage more suitably qualified women to apply for training; opportunities are very good. So make sure you choose to study the right subjects — particularly physics and maths.

The BBC

The BBC recruits Technical Assistants (trainee engineers) for network radio and television studios in London and the regional centres (Birmingham, Bristol, Manchester, Wales, Scotland, N. Ireland). 'Technical Assistants/Television and Radio studios' are trained to test, repair and maintain all equipment used to broadcast programmes, and control switching and routing; also to set up and align broadcasting equipment and in some areas operate it.

Training is completed in approximately three years, beginning with the twelve week 'A' course at the BBC Engineering Training Centre at Evesham. This course goes over basic principles studied in 'A' level Physics and introduces trainees to studio operations — studio layout, camera techniques, sound desk operation. Those who pass (any who fail have to leave the BBC) then proceed to induction and on the job training in television or radio for about eight months before returning to Evesham for the 'B' course. This is ten weeks in-depth study of basic principles and radio and television applications. Then follows another ten to twelve months 'on-the-job' experience before the final return to Evesham for the 'C' course — a detailed study of broadcasting engineering theory, how equipment works, fault finding, using manuals. On successful completion of the 'C' course the TA qualifies and becomes a Reserve Engineer.

To apply for a Technical Assistant's post you need 'O' Levels grades A/C or CSE '1' in maths, physics and English

Careers In Electronics

plus maths and physics studied to 'A' level or a TEC certificate/diploma in electronics/electrical engineering (with merit passes). You should have a keen interest in and knowledge of electronics possibly audio or video systems.

The BBC also recruits young people with Higher TEC or degree qualifications in Electronics, Electrical Engineering or Applied Physics for direct appointment as Engineers. The BBC's system of recruiting TAs aged 18 to 21 as potential engineer, as well as direct entry graduate engineers, provides suitably qualified young people with an unique choice and opportunity. For, if you have developed an interest in broadcasting engineering early, have studied the right subjects at school and then join the BBC as a TA you can do as well as the graduate engineer. Promotion after training is up to the individual.

Technical Operators

The BBC has recently created a new grade, Recording Operator, to deal with the increased work-load resulting from the great amount of pre-recording of BBC programmes on video-tape, and is currently offering a number of trainee opportunities in West London — at Television Centre, Lime Grove and New Enterprises Studios. Recording Operators prepare and operate video



Picture courtesy IBA.

film and tape equipment used for recording, editing, transmitting TV programmes and studio inserts. They are responsible for lining up programme material on magnetic tape or film and for ensuring equipment gives the highest standard or reproduction. You must be over 18, with 'O' Levels grade A/C or CSE '1' in maths, physics and English, plus science study — particularly physics — to 'A' Level or the equivalent TEC. You need good visual ability (an interest in film-making or art), and aural and technical ability (shown by such interests as sound recording, music, hospital/amateur radio or electronics. Training will be begun with the 'A' course at Evesham; then five months 'on-the-job' in video tape and five months in tele-cine, plus further courses at Evesham.

The BBC also recruits Camera Operators to work in television studios



Picture copyright Thames Television.

Directors and vision mixers in a Thames Television control room.

at Television Centre, Lime Grove and the Open University at Milton Keynes, Audio Assistants to work in radio and television studios in the Regions; and Technical Operators, Radio to work in Broadcasting House and External Services, Bush House. All Technical Operators start with the 'A' course at Evesham followed by on-the-job training and experience, and reach qualified operator status in three years.

Camera and Sound Operators work as junior members of a technical operations team in television studios or outside broadcast unit. They set up and operate cameras and associated equipment or sound reproduction equipment, sound booms and microphones, working closely with the production team. Radio Technical Operators route sound programme sources and completed programmes in the main control room, and operate sound reproduction equipment in radio stations. They are responsible for maintaining high technical quality of sound output.

For all Technical Operator grades you must be 18 plus with 'O' levels in maths, physics, English or TEC in electrical engineering. You need a good grasp of electricity and magnetism and appropriate practical interests.

The BBC has a small annual intake of Trainee Sound Managers; mainly graduates, for network radio — people with both technical and creative ability. They recruit periodically for the Local Radio Station Assistant's Registry and look for potential broadcasters from University/Polytechnic media studies type courses, with radio experience.

Independent Television

Only Thames Television among the ITV companies offers a formal Technical Training Scheme. About twelve trainees are recruited each Spring to begin nine months at the Teddington

Training Centre in October. The 1983 scheme is recruiting sound technicians, engineers and two film editors. Successful candidates are in age range 20 to 30, have completed a Higher TEC or degree course relevant to TV engineering (eg Ravensbourne College Higher TEC) or a film/television course or offer relevant professional experience.

ITN recruit six Trainee Broadcast Television Engineers each year to begin training in September and ask for Higher TEC in electrical/communications engineering with a broadcasting bias.

Facilities Companies

In the past the Facilities Companies have recruited only experienced staff, but are now also beginning to take on trainees. They look for technically minded young people with an interest in video systems and a background in electronics, usually over 18. You could be recruited as a trainee video tape operator or audio/video engineer or as an operator to do high quality transfer and cassette duplication work.

Getting Started

Broadcasting attracts many highly intelligent and well qualified people. Many of the trainee engineers and operators offer qualifications and relevant experience whether amateur or professional above the minimum required. Because so many talented young people like the idea of working in broadcasting, both the BBC, and ITV Companies can take their pick from many hundreds of able young people who apply each year.

The BBC has produced a comprehensive series of leaflets on training schemes, different jobs and careers with the Corporation which they



Picture courtesy BBC.

A BBC engineer setting up a video tape recorder.

will send on request. Be sure to specify the kind of work which interests you. These leaflets may also be available in your local careers office. The individual ITV companies provide information leaflets on jobs within their organisations which they will also send on request. In addition, The Independent Television Companies Association is preparing an information pack on behalf of all the ITV companies which will shortly be available; again, when writing be sure to specify the jobs which interest you.

For information on engineering and technical operator recruitment at the BBC write to:

The Engineering Recruitment Officer,
BBC Broadcasting House,
London W1A 1AA.

The IBA will supply up-to-date list of ITV and ILR companies; write to:

The Information Officer,
The Independent Broadcasting
Authority,
70 Brompton Road,
London SW3.

These addresses are also in the IBA handbook *Television & Radio 1983* published each year and obtainable from most bookshops. For The Independent Television Companies Association, write to:

The Training Adviser,
ITCA Ltd.,
Knighton House,
52-66 Mortimer Street,
London W1N 8AN.

Looking For The Opening

The BBC advertises vacancies in specialist publications such as the amateur electronics and radio press (according to type of work), in *The*

Listener, and sometimes *The Guardian* media page (Mondays). Details of trainee schemes aimed mainly at graduates are notified to University and Polytechnic careers services; those open to school and college leavers are notified to Local Authority Careers Offices in Central London and the South East, and in the Regional centres. Ask your careers officer for details (address and phone number in local telephone directory).

Trainee vacancies with the ITV companies must first be notified to the Trade Union (ACTT), 3 Soho Square, London W1. They are occasionally advertised in the national/specialist press, and are sometimes filled without advertising from the suitable speculative applications already held on file. So make sure you get your letter on file when you feel you have a realistic chance of being considered.

A small but interesting number of technical trainee vacancies with video production and facilities companies are notified to Inner London careers offices and to the Capital Radio Jobfinder service. You should also try making direct approaches to some of these companies. There are various reference books which will give you company details (eg *Contacts in Stage, Television, Screen & Radio; The Video Yearbook; The Creative Handbook*) held at the Westminster Central Reference Library and other good reference libraries.

If you are interesting in working in Independent Local Radio you should apply direct to the stations which interest you. You could also look into the courses offered by the National Broadcasting School, 14 Greek St., London W1, which provides training in radio production, engineering and journalism for ILR. Unfortunately, although these course are subsidised by the IBA, they are still expensive and Local Authority grants are not usually available.

Finally some tips for all would-be broadcasters:

- Achieve as high a standard of education as possible ensuring you are studying the appropriate subjects.
- Join a cine club or still photographic club at school, college or in your local area. If you are keen on sound, get involved with hospital or local radio, run a disco, record your local group.
- Find out as much as possible about the industry by reading books available on working in radio and television, by talking to people who work in the industry, by obtaining free audience tickets for a television studio show recording, by attending the Inner London Education Authority's Christmas Careers Lectures for sixth formers on television broadcasting if you live in the London commuting area (information from your careers officer).
- Watch films and television programmes analytically — which techniques make different programmes work?
- Look into the relevant further and higher education courses. If you decide to apply for a course, check the prospects well in advance to ensure you will be able to offer the right entry qualifications. Make your application as early as possible in the year before you wish to begin the course, and make early enquiries about your grant aid which may be available from your local education authority.



Picture courtesy IBA.

- Prepare yourself to go to interviews, sometimes at short notice; be ready to ask questions.
- Seek further advice and guidance from your local careers officer.

Don't consider a career in broadcasting simply because you think it will be exciting and glamorous. The glamour soon wears off. A camera operator with a heavy cold filming in filthy weather, who has to spend hours waiting for the weather to clear will hardly find the job glamorous.

Good luck with your search!

Shelley Partridge is a Careers Officer working for the Inner London Education Authority's Careers Service and specialises in the Broadcasting, Film and Video Industries.

EDUCATIONAL ELECTRONIC KITS

RADIO KIT



This AM radio is supplied with building instructions plus comprehensive electronic theory, exercises and test procedure. A complete learning package, requiring only a 9V battery.

The large fibreglass printed circuit board has been designed in 3 sections — a TRF radio, a bass treble control and an amplifier push-pull output circuit. Each section can be built and tested as a separate project.

This comprehensive radio circuit shows an application of tuned circuits, I.C.'s, field effect and bipolar transistors, common emitter and collector configurations, stabilizer circuits, feedback circuits, complementary output stages, etc.

The radio project kit should give entertainment and interest to the novice, yet provide valuable learning material for the electrical student. Particularly relevant to current T.E.C. electronic courses.

The price is only **£11.99 inc. VAT + £1.50 p&p.**

Educational and quantity enquiries welcome.

Send cheque or postal order to:-

HAZZLEWOOD ELECTRONICS
Sales Department,
149 Main Street,
Grenoside,
Sheffield, S30 3PN.
Tel: 0742 463585

Send an S.A.E. to receive a list of our current electronic project kits.

Elen Electronics — DISCO

Tired of boring 3 & 4 channel lighting controllers. Then try our new 8 CHANNEL PATTERNMAKER for spotlights or lighting screens.



16 different sequential patterns including Catherine Wheel, Screen Writer, Checker & Light Train.

Kit comprises PCB & all components including 2K PROM & Monitor LEDs. Only **£27.00 + VAT.**

Hardware kit including case, 12 way socket & matching plug, mains lead etc. Only **£9.50 + VAT.**

Please add 60p P&P to order.

ELEN ELECTRONICS
Unit 9, Telford OP. Centre,
Halesfield 14, Telford, Shropshire
Tel: 0952 585697

Further details on request

PARNDON ELECTRONICS LTD.

Dept. 22, 44 Paddock Mead, Harlow, Essex. CM18 7RR. Tel: 0279 32700

RESISTORS: ¼ Watt Carbon Film E24 range ± 5% tolerance
Bandoliered and colour coded. Full Range 1R0-10M.

£1.00 per hundred mixed (Min 10 per value) **£8.50** per thousand mixed (Min 50 per value)
Special stock pack 60 values. 10 of each **£5.50**

RECTIFIERS

1 Amp 3 Amp		
50V	3p	14p
100V	4p	14p
200V	5p	14p
400V	6p	19p
600V	8p	20p
1000V	9p	25p

3½ Digit LCD Display: 1 colon, 3 decimal points plus/minus sign and lo bat indicator.

Complete with low power 7106 A/D converter display driver.
Driver set **£8.95**
Display **£3.50** Driver **£6.50**

DIODES: IN4148 **£1.60** per hundred

DIL SOCKETS

8 pin - 10p. 14 pin - 11p. 16p pin - 12p. 18p pin - 19p. 20p pin - 21p
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

Full List Available — Send SAE
ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS
MIN ORDER — UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE
Same Day Despatch

HORIZON ELECTRONICS

(Midlands)
Dept. H/H Charlotte St. Rugby Tel: 78138
Prime quality. TERRIFIC PRICES. Mail order only

<p>REGULATORS (5/12/15V)</p> <p>100mA +ve 28p 1 amp +ve 33p 7.23 vr/ 28p</p> <p>ZENERS (3.3 to 30V)</p> <p>500mW 8p 1.3 watt 12p</p> <p>DIODES</p> <table border="0"> <tr> <td>IN 4001 3p</td> <td>OPTD TL112 83p</td> </tr> <tr> <td>4002 4p</td> <td>4N33 117p</td> </tr> <tr> <td>4004/8 5p</td> <td>MOC3020 185p</td> </tr> <tr> <td>IN 5401 12p</td> <td></td> </tr> <tr> <td>5402 13p</td> <td></td> </tr> <tr> <td>5406 14p</td> <td></td> </tr> </table> <p>BRIDGES</p> <table border="0"> <tr> <td>1 amp 50v 20p</td> <td>ABIAL 1.0 MFD 7p</td> </tr> <tr> <td>2 amp 100v 30p</td> <td>2.2 MFD 7p</td> </tr> <tr> <td>2 amp 200v 35p</td> <td></td> </tr> <tr> <td>2 amp 400v 38p</td> <td></td> </tr> <tr> <td>6 amp 100v 45p</td> <td></td> </tr> <tr> <td>6 amp 200v 47p</td> <td></td> </tr> <tr> <td>6 amp 400v 75p</td> <td></td> </tr> <tr> <td>10 amp 50v 170p</td> <td></td> </tr> <tr> <td>10 amp 100v 180p</td> <td></td> </tr> <tr> <td>10 amp 200v 195p</td> <td></td> </tr> </table> <p>TRANSISTORS (plastic)</p> <p>4 amp 400v 35p 8 amp 400v 60p</p>	IN 4001 3p	OPTD TL112 83p	4002 4p	4N33 117p	4004/8 5p	MOC3020 185p	IN 5401 12p		5402 13p		5406 14p		1 amp 50v 20p	ABIAL 1.0 MFD 7p	2 amp 100v 30p	2.2 MFD 7p	2 amp 200v 35p		2 amp 400v 38p		6 amp 100v 45p		6 amp 200v 47p		6 amp 400v 75p		10 amp 50v 170p		10 amp 100v 180p		10 amp 200v 195p		<p>TRIACS (plastic)</p> <p>4 amp 400v 50p 8 amp 400v 60p 25 amp 400v 168p</p> <p>TOGGLE SWITCHES</p> <p>Min SP ST 57p Min DP ST 70p S Min SP ST 48p S Min DP ST 62p</p> <p>TRANSISTORS</p> <table border="0"> <tr> <td>BC107B 9p</td> <td>BC137 8p</td> </tr> <tr> <td>BC108B 9p</td> <td>BC143 32p</td> </tr> <tr> <td>BC198B 10p</td> <td>BF178 25p</td> </tr> <tr> <td>BC140 25p</td> <td>BF178 30p</td> </tr> <tr> <td>BC142 22p</td> <td>BF257 30p</td> </tr> <tr> <td>BC150 35p</td> <td>BF258 30p</td> </tr> <tr> <td>BC177D 15p</td> <td>BF258 33p</td> </tr> <tr> <td>BCV71 15p</td> <td>BF885 27p</td> </tr> <tr> <td>BC182 7p</td> <td>BF885 28p</td> </tr> <tr> <td>BC212 7p</td> <td>BF887 28p</td> </tr> <tr> <td>BC237 8p</td> <td>BF888 25p</td> </tr> <tr> <td>BD300 62p</td> <td>BFY50 20p</td> </tr> <tr> <td>BC301 25p</td> <td>BFY51 22p</td> </tr> <tr> <td>BC302 30p</td> <td>TPR1B 35p</td> </tr> <tr> <td>BC303 30p</td> <td>TP32B 38p</td> </tr> <tr> <td>BC304 40p</td> <td>VN100M 50p</td> </tr> <tr> <td>BD135 33p</td> <td>VN66AF 85p</td> </tr> <tr> <td>BD136 35p</td> <td>VN68AF 95p</td> </tr> </table> <p>LINEAR IC's</p> <table border="0"> <tr> <td>747 50p</td> <td>RADIAL (63V) 7p</td> </tr> <tr> <td>748 53p</td> <td>1.0 MFD 7p</td> </tr> <tr> <td>ICM 7555 70p</td> <td>2.2 MFD 8p</td> </tr> <tr> <td>ICM 7558 130p</td> <td>4.7 MFD 10p</td> </tr> <tr> <td>LF 351 40p</td> <td>10 MFD 10p</td> </tr> <tr> <td>LF 353 70p</td> <td>22 MFD 12p</td> </tr> <tr> <td>LM 301A 24p</td> <td>47 MFD 13p</td> </tr> <tr> <td>LM 324 27p</td> <td>100 MFD 19p</td> </tr> <tr> <td>LM 380 60p</td> <td>220 MFD 44p</td> </tr> <tr> <td>LM 3909 88p</td> <td></td> </tr> <tr> <td>NE 587v 85p</td> <td></td> </tr> <tr> <td>TDK 2020 285p</td> <td></td> </tr> <tr> <td>TDK 2002 185p</td> <td></td> </tr> </table> <p>SOLDERING IRONS</p> <p>Antex C 15w 445p CMI 15w 465p R25 25w 470p 60p</p> <p>All bits</p> <p>LED's</p> <table border="0"> <tr> <td>2 Red 7p</td> </tr> <tr> <td>2 Green 8p</td> </tr> <tr> <td>2 Yellow 8p</td> </tr> </table> <p>D (Mini) connectors</p> <table border="0"> <tr> <td>15 way plug 86p</td> </tr> <tr> <td>Socket 128p</td> </tr> <tr> <td>Cover 98p</td> </tr> <tr> <td>25 way plug 122p</td> </tr> <tr> <td>Socket 180p</td> </tr> <tr> <td>Cover 99p</td> </tr> </table>	BC107B 9p	BC137 8p	BC108B 9p	BC143 32p	BC198B 10p	BF178 25p	BC140 25p	BF178 30p	BC142 22p	BF257 30p	BC150 35p	BF258 30p	BC177D 15p	BF258 33p	BCV71 15p	BF885 27p	BC182 7p	BF885 28p	BC212 7p	BF887 28p	BC237 8p	BF888 25p	BD300 62p	BFY50 20p	BC301 25p	BFY51 22p	BC302 30p	TPR1B 35p	BC303 30p	TP32B 38p	BC304 40p	VN100M 50p	BD135 33p	VN66AF 85p	BD136 35p	VN68AF 95p	747 50p	RADIAL (63V) 7p	748 53p	1.0 MFD 7p	ICM 7555 70p	2.2 MFD 8p	ICM 7558 130p	4.7 MFD 10p	LF 351 40p	10 MFD 10p	LF 353 70p	22 MFD 12p	LM 301A 24p	47 MFD 13p	LM 324 27p	100 MFD 19p	LM 380 60p	220 MFD 44p	LM 3909 88p		NE 587v 85p		TDK 2020 285p		TDK 2002 185p		2 Red 7p	2 Green 8p	2 Yellow 8p	15 way plug 86p	Socket 128p	Cover 98p	25 way plug 122p	Socket 180p	Cover 99p
IN 4001 3p	OPTD TL112 83p																																																																																																							
4002 4p	4N33 117p																																																																																																							
4004/8 5p	MOC3020 185p																																																																																																							
IN 5401 12p																																																																																																								
5402 13p																																																																																																								
5406 14p																																																																																																								
1 amp 50v 20p	ABIAL 1.0 MFD 7p																																																																																																							
2 amp 100v 30p	2.2 MFD 7p																																																																																																							
2 amp 200v 35p																																																																																																								
2 amp 400v 38p																																																																																																								
6 amp 100v 45p																																																																																																								
6 amp 200v 47p																																																																																																								
6 amp 400v 75p																																																																																																								
10 amp 50v 170p																																																																																																								
10 amp 100v 180p																																																																																																								
10 amp 200v 195p																																																																																																								
BC107B 9p	BC137 8p																																																																																																							
BC108B 9p	BC143 32p																																																																																																							
BC198B 10p	BF178 25p																																																																																																							
BC140 25p	BF178 30p																																																																																																							
BC142 22p	BF257 30p																																																																																																							
BC150 35p	BF258 30p																																																																																																							
BC177D 15p	BF258 33p																																																																																																							
BCV71 15p	BF885 27p																																																																																																							
BC182 7p	BF885 28p																																																																																																							
BC212 7p	BF887 28p																																																																																																							
BC237 8p	BF888 25p																																																																																																							
BD300 62p	BFY50 20p																																																																																																							
BC301 25p	BFY51 22p																																																																																																							
BC302 30p	TPR1B 35p																																																																																																							
BC303 30p	TP32B 38p																																																																																																							
BC304 40p	VN100M 50p																																																																																																							
BD135 33p	VN66AF 85p																																																																																																							
BD136 35p	VN68AF 95p																																																																																																							
747 50p	RADIAL (63V) 7p																																																																																																							
748 53p	1.0 MFD 7p																																																																																																							
ICM 7555 70p	2.2 MFD 8p																																																																																																							
ICM 7558 130p	4.7 MFD 10p																																																																																																							
LF 351 40p	10 MFD 10p																																																																																																							
LF 353 70p	22 MFD 12p																																																																																																							
LM 301A 24p	47 MFD 13p																																																																																																							
LM 324 27p	100 MFD 19p																																																																																																							
LM 380 60p	220 MFD 44p																																																																																																							
LM 3909 88p																																																																																																								
NE 587v 85p																																																																																																								
TDK 2020 285p																																																																																																								
TDK 2002 185p																																																																																																								
2 Red 7p																																																																																																								
2 Green 8p																																																																																																								
2 Yellow 8p																																																																																																								
15 way plug 86p																																																																																																								
Socket 128p																																																																																																								
Cover 98p																																																																																																								
25 way plug 122p																																																																																																								
Socket 180p																																																																																																								
Cover 99p																																																																																																								

ABOVE: Just a few examples. Send S.A.E./List
ADD: 65p p&p to all orders under £5.00
VAT: add 15% VAT to total order value

ALARMS

A
D
E

FREE BOOKLET

on

BURGLAR ALARMS

with

LOWEST U.K. DIY PUBLISHED PRICES

PHONE OR WRITE FOR YOUR COPY

051-523 8440

AD ELECTRONICS

217 WARBRECK MOOR
AINTREE, LIVERPOOL L9 0HU

It's easy
to complain
about
advertisements.


The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.
ASA Ltd., Brook House, Torrington Place, London WC1E 7HN

74 SERIES	74125 30p	74LS05 12p	74LS221 50p	4034 140p	ADCC808 990p	LM1014 150p	TL430C 70p	BSX19/20 20p	2N1613 30p	OA202 10p	Rectangular LEDs (R.G.V.)
7400 11p	74126 30p	74LS06 12p	74LS240 55p	4035 45p	AV1-5050 990p	LM1801 300p	UA2240 120p	BU104 225p	2N1711 25p	1N914 4p	LS5891 570p
7401 11p	74127 30p	74LS07 12p	74LS241 55p	4036 275p	AV3-1350 350p	LM1888 350p	UA2241 120p	BU108 250p	2N1712 25p	1N916 4p	LS5891 570p
7402 11p	74128 30p	74LS09 12p	74LS242 55p	4037 110p	AV3-8910 350p	LM2917 200p	ULN2003 75p	BU109 225p	2N2150 25p	1N4148 4p	TL131 60p
7403 12p	74129 30p	74LS10 12p	74LS243 55p	4038 290p	AV3-8912 500p	LM3002 75p	ULN2004 75p	BU126 150p	2N2219A 25p	1N4001/2 5p	TL1312/3 110p
7404 12p	74130 30p	74LS11 13p	74LS244 55p	4039 400p	CA3019 80p	LM3300 50p	ULN2802 200p	BU180A 120p	2N2269A 17p	1N4005 7p	TL1321/2 130p
7405 15p	74131 30p	74LS12 13p	74LS245 70p	4040 40p	CA3028 120p	LM3909 85p	UPC675 275p	BU205 175p	2N2484 25p	1N4006/7 6p	TL1330 140p
7406 15p	74132 30p	74LS13 15p	74LS246 70p	4041 40p	CA3048 120p	LM3911 125p	UPC592H 275p	BU206 175p	2N2646 40p	1N5401/2 12p	7750/60 200p
7407 18p	74133 30p	74LS14 25p	74LS247 70p	4042 40p	CA3048 120p	LM3915 200p	UPC1158H 275p	BU406 145p	2N2905A 25p	1N5403 14p	
7408 14p	74134 30p	74LS15 25p	74LS248 70p	4043 40p	CA3059 285p	LM3916 225p	UPC1185 85p	BUX80 400p	2N3052 25p	1N5404/7 12p	
7409 14p	74135 30p	74LS16 25p	74LS249 70p	4044 40p	CA3060 350p	LM3160 110p	XR2206 300p	BUY69C 200p	2N3053 25p	S920 5p	
7410 14p	74136 30p	74LS17 13p	74LS250 70p	4045 18p	CA3080 70p	LM13600 110p	XR210 400p	J310 50p	2N3054 55p		
7411 16p	74137 30p	74LS18 13p	74LS251 30p	4046 14p	CA3086 48p	M51513L 230p	XR221 575p	MJ8024 84p	2N3055 35p	31015F 200p	
7412 14p	74138 30p	74LS19 13p	74LS252 30p	4047 15p	CA3089 300p	M51516L 500p	XR221 575p	MJ2501 225p	2N3442 140p	DL704 140p	
7413 16p	74139 30p	74LS20 13p	74LS253 30p	4048 40p	CA3090Q375p	MB3712 250p	XR221 575p	MJ2955 90p	2N3442 140p	DL707 Red 140p	
7414 18p	74140 30p	74LS21 13p	74LS254 30p	4049 125p	CA3130C 90p	MB3730 400p	XR221 575p	MJ3001 225p	2N3442 140p	FN0367 120p	
7415 18p	74141 30p	74LS22 12p	74LS255 30p	4050 40p	CA3140C 40p	MC1310P 50p	XR221 575p	MJ4502 84p	2N3702/3 10p	FN0507 90p	
7416 14p	74142 30p	74LS23 13p	74LS256 30p	4051 90p	CA3140T 100p	MC1458 35p	XR221 575p	MJE340 50p	2N3706/7 10p	MAN3640 175p	
7417 14p	74143 30p	74LS24 13p	74LS257 30p	4052 90p	CA3161E 150p	MC1485L 350p	XR221 575p	MJE355 90p	2N3773 200p	MAN4640 200p	
7418 14p	74144 30p	74LS25 13p	74LS258 30p	4053 70p	CA3161E 150p	MC1496 70p	XR221 575p	MJE355 90p	2N3819 200p		
7419 14p	74145 30p	74LS26 13p	74LS259 30p	4054 70p	CA3162 450p	MC3340P 120p	XR221 575p	MJE355 90p	2N3823 300p		
7420 16p	74146 30p	74LS27 13p	74LS260 20p	4055 18p	CA3189C 300p	MC3403 65p	XR221 575p	MJE355 90p	2N3866 90p		
7421 18p	74147 30p	74LS28 13p	74LS261 130p	4056 290p	CA3240C 110p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7422 20p	74148 30p	74LS29 13p	74LS262 130p	4057 575p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7423 18p	74149 30p	74LS30 12p	74LS263 130p	4058 15p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7424 18p	74150 30p	74LS31 12p	74LS264 140p	4059 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7425 18p	74151 30p	74LS32 14p	74LS265 140p	4060 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7426 18p	74152 30p	74LS33 14p	74LS266 140p	4061 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7427 18p	74153 30p	74LS34 14p	74LS267 140p	4062 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7428 18p	74154 30p	74LS35 14p	74LS268 140p	4063 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7429 18p	74155 30p	74LS36 14p	74LS269 140p	4064 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7430 14p	74156 30p	74LS37 16p	74LS270 140p	4065 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7431 14p	74157 30p	74LS38 16p	74LS271 140p	4066 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7432 14p	74158 30p	74LS39 16p	74LS272 140p	4067 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7433 14p	74159 30p	74LS40 16p	74LS273 140p	4068 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7434 14p	74160 30p	74LS41 16p	74LS274 140p	4069 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7435 14p	74161 30p	74LS42 16p	74LS275 140p	4070 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7436 14p	74162 30p	74LS43 16p	74LS276 140p	4071 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7437 14p	74163 30p	74LS44 16p	74LS277 140p	4072 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7438 14p	74164 30p	74LS45 16p	74LS278 140p	4073 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7439 25p	74165 30p	74LS46 16p	74LS279 30p	4074 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7440 14p	74166 30p	74LS47 16p	74LS280 30p	4075 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7441 14p	74167 30p	74LS48 16p	74LS281 30p	4076 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7442 14p	74168 30p	74LS49 16p	74LS282 30p	4077 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7443 22p	74169 30p	74LS50 16p	74LS283 30p	4078 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7444 14p	74170 30p	74LS51 16p	74LS284 30p	4079 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7445 50p	74171 30p	74LS52 16p	74LS285 30p	4080 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7446 50p	74172 30p	74LS53 16p	74LS286 30p	4081 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7447 50p	74173 30p	74LS54 16p	74LS287 30p	4082 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7448 50p	74174 30p	74LS55 16p	74LS288 30p	4083 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7449 50p	74175 30p	74LS56 16p	74LS289 30p	4084 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7450 15p	74176 30p	74LS57 16p	74LS290 30p	4085 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7451 15p	74177 30p	74LS58 16p	74LS291 30p	4086 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7452 15p	74178 30p	74LS59 16p	74LS292 30p	4087 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7453 15p	74179 30p	74LS60 16p	74LS293 30p	4088 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7454 15p	74180 30p	74LS61 16p	74LS294 30p	4089 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7455 15p	74181 30p	74LS62 16p	74LS295 30p	4090 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7456 15p	74182 30p	74LS63 16p	74LS296 30p	4091 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7457 15p	74183 30p	74LS64 16p	74LS297 30p	4092 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7458 15p	74184 30p	74LS65 16p	74LS298 30p	4093 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7459 15p	74185 30p	74LS66 16p	74LS299 30p	4094 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7460 15p	74186 30p	74LS67 16p	74LS300 30p	4095 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7461 15p	74187 30p	74LS68 16p	74LS301 30p	4096 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7462 15p	74188 30p	74LS69 16p	74LS302 30p	4097 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7463 15p	74189 30p	74LS70 16p	74LS303 30p	4098 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7464 15p	74190 30p	74LS71 16p	74LS304 30p	4099 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7465 15p	74191 30p	74LS72 16p	74LS305 30p	4100 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7466 15p	74192 30p	74LS73 16p	74LS306 30p	4101 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7467 15p	74193 30p	74LS74 16p	74LS307 30p	4102 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7468 15p	74194 30p	74LS75 16p	74LS308 30p	4103 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7469 15p	74195 30p	74LS76 16p	74LS309 30p	4104 100p	CA3280C 200p	MC6039 37p	XR221 575p	MJE355 90p	2N3866 90p		
7470 15p</											

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.


Sparkrite

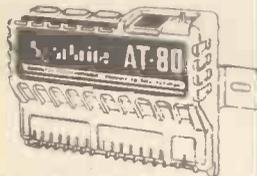BRANDEADING ELECTRONICS
NOW AVAILABLE IN KIT FORM



AT-80 Electronic Car Security System

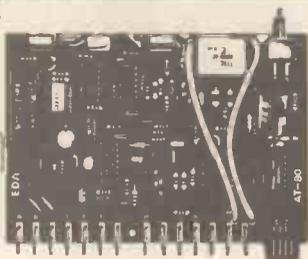- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen ● Fits all 12V neg earth vehicles
- Over 250 components to assemble



VOYAGER Car Drive Computer

- A most sophisticated accessory. ● Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd. ● Affords 12 functions centred on Fuel, Speed, Distance and Time. ● Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on. ● Facility to operate LOG and TRIP functions independently or synchronously
- Large 10mm high 400ft-L fluorescent display with auto intensity. ● Unique speed and fuel transducers giving a programmed accuracy of + or - 1%. ● Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours. ● Full Imperial and Metric calibrations. ● Over 300 components to assemble




SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles


TX1002 Electronic Ignition

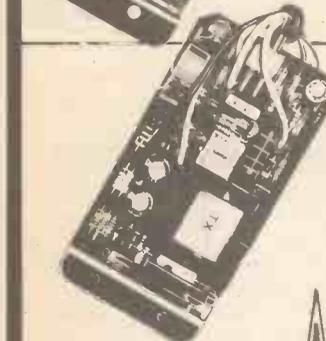- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge ● Three position changeover switch ● Distributor triggerhead adaptors included ● Die cast weatherproof case ● Clip-to-coil or remote mounting facility ● Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles ● Over 145 components to assemble.



SX2000 Electronic Ignition

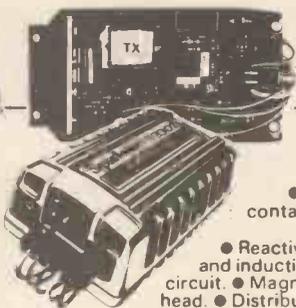- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles



TX2002 Electronic Ignition

- The ultimate system ● Switchable contactless. ● Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive. ● Extended coil energy storage circuit. ● Magnetic contactless distributor triggerhead. ● Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers.
- Die cast weatherproof case with clip-to-coil fitting ● Fits majority of 4 and 6 cylinder 12v neg. earth vehicles
- Over 150 components to assemble

All SPARKRITE products and designs are fully covered by one or more World Patents

SPECIAL OFFER

"FREE" MAGIDICE KIT WITH ALL ORDERS OVER £45.00



MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

SPARKRITE 82 Bath Street, Walsall, West Midlands, WS1 3DE England

tel (0922) 614791 Allow 28 days for delivery

	SELF ASSEMBLY KIT
SX 1000	£12.95
SX 2000	£19.95
TX 1002	£22.95
TX 2002	£32.95
AT 80	£32.95
VOYAGER	£64.95
MAGIDICE	£9.95

PRICES INC. VAT, POSTAGE & PACKING

NAME _____ HE 9

ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF _____

CHEQUE NO _____



BRANDEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!

ALL ABOUT ELECTRONICS

Our new Beginner's Series tells you all you'd like to know about electronics. From start to finish. All about components and circuits, all the theory you need to get started in the world of electronics.

Kevin Brindley

I PROMISED in the August issue of HE that I would discuss electronic components in this month's All About Electronics. And the first component family that we all need to know about in any study of electronics is the family of resistors. We've already talked about resistance of course; we know that a resistor is something which allows an electric current to flow through it. But the current is actually *controlled* by the value of the resistor. For instance, if the voltage across the resistor is maintained constant, increasing the value of the resistor would automatically reduce the current flowing through it. The three variables of current, voltage and resistance are totally described by Ohm's Law, which says simply that the ratio of the voltage across a body to the current through the body equals a constant which is the resistance of the body. Ohm's Law can be summarised by the formula

$$\frac{V}{I} = R$$

from which

$$V = IR \text{ and } \frac{V}{R} = I$$

can be derived. These three formulae mean that if we know any two of the three variables associated with a resistance, the third can be calculated.

We can express Ohm's Law and these three formulae graphically, as Figure 1 shows. The graph in Figure 1 shows three important points about the relationship between voltage across and current through a resistance:

- it is linear, ie a straight line
- it passes through the origin
- it occurs for negative values of both voltage and current.

A relationship which is defined for negative values of voltage and current is important because it means that Ohm's Law can be applied to resistors used with AC usage — where voltage and

current alternate between positive and negative values.

What Is A Resistor?

With our knowledge of the interdependence of each of these variables of current, voltage and resistance we can now go on to look at the make-up of a resistor. As you know, in electronics there are specific components which we call resistors. Size of each type is not necessarily related to value — in other words you could have a resistor of value 10MR (ie 10 megohms = 1×10^6 ohm) which is smaller than a 10R resistor. No — size is normally related to the power which a type of resistor can dissipate (ie, release as heat to the surrounding air — more of that later!).

One type of resistor which we met two months ago was simply a length of nichrome wire. Now, nichrome wire is made with a very even and constant diameter throughout its length. If you were to do a couple of experiments with two lengths of such wire — having different diameters — you would find that their resistance is proportional to length and inversely proportional to cross-sectional area. So: the longer the wire, the higher the resistance; the thicker the wire the lower the resistance (both fairly obvious, I think!). The actual resistance of the wire can be calculated by using the formula

$$R = \rho \frac{l}{a}$$

where l = length, a = cross-sectional area and ρ is the *resistivity* of the wire.

Any material has its own resistivity: for example, the resistivity of copper is 1.72×10^{-8} ohms per metre and the resistivity of aluminium is 2.82×10^{-8} ohms per metre, and the resistivity of nichrome is 1.10×10^{-8} ohms per metre.

So the resistance of a length of material can be calculated from knowledge of these three variables.

If we take the example of nichrome wire and calculate the resistance of a one metre length of wire, of cross-sectional area 0.1mm^2 , it will give us a good idea of the use of this resistance formula. Now, the resistivity of nichrome is 110×10^{-8} ohm metre, so the resistance is

$$\frac{1}{a} = \frac{110 \times 10^{-8} \times 1}{1 \times 10^{-7}} = 11R$$

From this result, it is fairly obvious that although a material such as nichrome wire exhibits the principles of resistance we couldn't use it to manufacture resistors to any great value — just think of the length of wire needed to make a 1M resistor.

To make high value resistors a material with a higher resistivity must be used. The most common material used is carbon. Carbon belongs to a group of substances we call semiconductors. For one reason or another (as we'll find out over the coming months) semiconductors are the most important elements in the electronics world. Other semiconductors often used are germanium and silicon.

Carbon's high resistivity (about 180×10^{-8} ohms per metre) means that high resistances can be manufactured with quite small body sizes. Two main types available are:

- 1) solid carbon resistor (Figure 2). Graphite (a form of carbon) is compressed into a thin rod and metal leads are connected to each end. The rod and connections are encased in an insulating body.
- 2) Carbon film resistor (Figure 3).

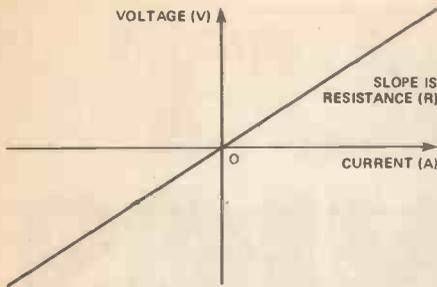


Figure 1. Showing the graphical relationship between voltage across a resistor and current through it.

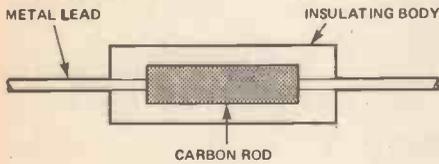


Figure 2. Make-up of a solid carbon resistor.

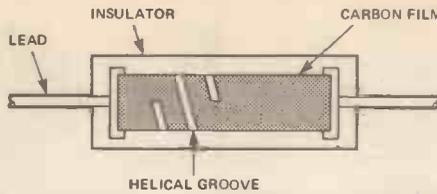


Figure 3. How a carbon film resistor is made-up.

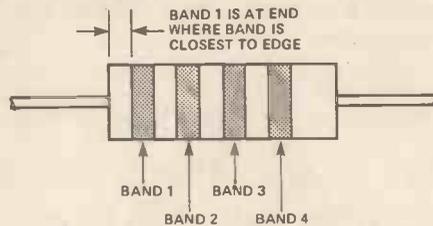


Figure 4. The resistor colour code and a table relating to each band and its colour to a resistor's value. The bulk of the colours (red to violet) are the colours of the spectrum.

Figure 5. Simplest resistor circuit it is possible to make — a single resistor connected to a 10V power source.

Graphite is deposited as a thin film on a ceramic insulating body. A groove is cut into the film until the required resistance is reached. Then metal caps are crimped to the ends to form connections and the whole resistor is coated with an insulator.

Resistors made from carbon are cheap and can be made to quite a high accuracy (say, within 5% of the required value). They are therefore used a lot in electronics. But they do, however, have some disadvantages:

- their resistance varies a great deal with changing temperature
- they are prone to resistance changes due to mechanical shock or just age.

So, for more exacting requirements we use other types

- metal film
- metal oxide film.

Construction is similar to carbon film resistors but a layer of metal or metal oxide is deposited on the insulating body. These make much more stable resistors and generally speaking better accuracy can be achieved (say, ± 1% of the required value).

NPV

Generally speaking a wide range of values of resistors is needed — anything from a fraction of an ohm to

several million ohms can be seen in any common piece of electronic equipment. It would obviously be impossible to manufacture every possible value: and anyway, resistors are rarely their exact quoted value — some are made with a tolerance of ± 20%, ie they could have a value within the range 20% under to 20% over the specified value. So to provide reasonable coverage of all possible values, resistors are made to standard ranges. A typical standard is the E12 range shown in Table 1.

Other standard ranges give different resistance. For example, common American resistances may have values such as 3K32 and 6K65. When we specify a particular resistor calculated for a circuit, then we have to use the nearest value to it from the standard range. The standard range value is known as the *nearest preferred value* (NPV). To differentiate values of

resistors (they all look the same, after all, don't they?) we code them with an internationally accepted code known as the *resistor colour code*. Resistors are coloured with thin loops or bands around their bodies. Coding and decoding what the different bands mean is quite straightforward and is shown in Figure 4.

Each of the first two bands stands for a digit. The third band stands for the 'multiplier' — quite simply the number of zeros behind the first two digits.

Thus a colour-coded resistor whose first three bands are red, violet, yellow would be of value 270000: red = 2, violet = 7, and yellow = four zeros, ie 27k. The fourth coloured band (if used at all) gives the resistor's tolerance.

Now we've looked at resistor values and codes it only remains to look at power ratings, and then we can go to look at circuits using resistors. Last month we discovered the heating effect of an electric current. Power is dissipated in the form of heat whenever a current flows through a resistor, and, if that heat is too great, the value of the resistor may change, or worse still, the resistor may be damaged — it may 'burn-out'. Manufacturers give resistors power rating, and the actual power which a resistor dissipates must always be less than its power rating.

Power dissipated by a resistor is calculated from the power formula we saw last month

$$P = IV \text{ (measured in watts)}$$

or because $V = IR$ and $I = V/R$.

$$P = I^2R = \frac{V^2}{R} \text{ watts}$$

So, knowing the voltage across a resistor, or the current through it, or both, the power dissipated by a resistor in a particular application can be calculated and a resistor can therefore be used of high enough rating.

Resistors In Circuits

We have looked at some simple circuits using resistors over the last two months. It's worth repeating them here, I think, before moving on to more complex circuits. The simplest circuit we could possibly build is shown in Figure 5.

E12 Resistance Values

10	100	1K	10K	100K	1M
12	120	1K2	12K	120K	1M2
15	150	1K5	15K	150K	1M5
18	180	1K8	18K	180K	1M8
22	220	2K2	22K	220K	2M2
27	270	2K7	27K	270K	2M7
33	330	3K3	33K	330K	3M3
39	390	3K9	39K	390K	3M9
47	470	4K7	47K	470K	4M7
56	560	5K6	56K	560K	5M6
68	680	6K8	68K	680K	6M8
82	820	8K2	82K	820K	8M2

Table 1. Resistor values in the E12 range. The first column lists the basic resistor values; all other resistors are simple decades of the basic resistors

The voltage across the resistor, V , is indicated by the arrow shown beside the resistor. The arrow head indicates the more positive side. Current is indicated by the arrow head within the circuit, which should always point in the direction of current flow, ie from positive to negative.

In the circuit of Figure 5, if $V = 10$ volts and $R_1 = 100R$ the current, I , must equal (from Ohm's Law)

$$\frac{V}{R} = \frac{10}{100} = 0A1$$

The resistor must therefore be capable of dissipating at least

$$\frac{V^2}{R} = \frac{100}{100} = 1 \text{ watt}$$

Figure 6 shows a more complex example of a circuit using two resistors. Such a circuit is often known as a voltage, or potential, divider because the voltage at the junction of the two resistors is always a strict ratio of the voltage across the whole circuit. We can think of the two resistors as forming a circuit which will provide an output voltage which is always a particular ratio of an input voltage.

The voltage at the resistor junction (classed as the output voltage, V_{out}) is given as the ratio of the output resistor (R_2), to the total resistance ($R_1 + R_2$), times the input voltage (V_{in}). As a formula

$$V_{out} = \frac{R_2}{R_1 + R_2} \times V_{in}$$

And, in the circuit of Figure 6

$$V_{out} = \frac{500}{1500} \times 12 = 4V$$

Certain types of resistors (potentiometers — called 'pots' for short) make use of this potential dividing capability to allow a continually variable output voltage to suit the application. The volume controls of a hi-fi system or TV are good examples of this. Such a pot is placed at the amplifier input of the equipment, and the output voltage is controlled by the ratio of the two resistors. Figure 7 shows the make-up of a simple pot. By varying the position of the 'wiper' (ie, the junction of the two resistors), the ratio between the two resistors is changed and so the output voltage changes. You should have gathered, from the example of a pot used to control volume from an amplifier, that pots (in fact all resistors too) can be used with AC voltages and signals as well as DC. Figure 8 shows the circuit symbols of a pot.

More Complex Circuits

Electronic circuits, of course, are usually far more complex than those of say, potential dividers and some methods must be established to help us understand them. Take for example the circuit in Figure 9. As the resistors are in series, the current, I , must flow through each of them. The voltage across each of these resistors depends

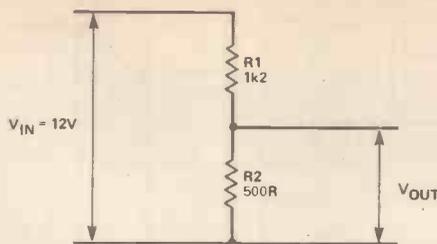


Figure 6. A voltage divider or potential divider is made with two resistors. The output voltage, V_{out} , is a ratio of the input voltage, V_{in} .


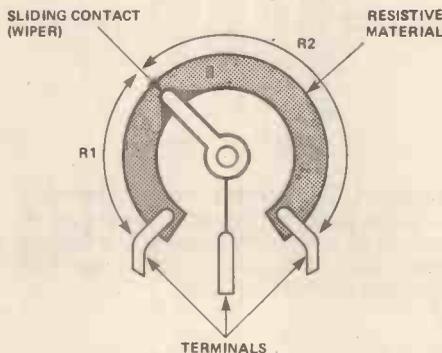


Figure 7. Make-up of a pot — a potentiometer. The wiper can rotate around the resistive material altering the ratio between R_1 and R_2 .

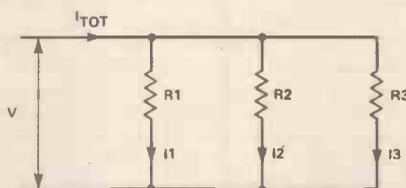

upon each resistor's value according to the formula.

$$V = IR$$

and the total voltage, V_{tot} equals the sum of the individual resistor voltages, ie

$$V_{tot} = V_1 + V_2 + V_3$$

However, when resistors are in parallel, as in Figure 10, the voltage across each resistor is equal, therefore the current through each is dependent on its resistance, according to the formula

$$I = \frac{V}{R}$$

and the total current, $I_{tot} = I_1 + I_2 + I_3$.

Equivalent Circuits

We can simplify complex circuits which may seem difficult to understand into equivalent circuits — circuits which theoretically perform the same job with a minimum of components. (I say 'theoretically' because these equivalent circuits might not work in a practical

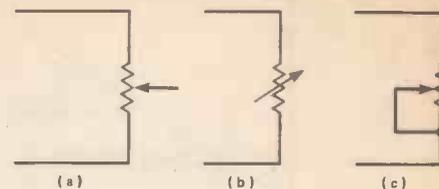


Figure 8. a) Symbol of a pot used as a potential divider. b) Symbols of a pot used as a variable resistor — either symbol is correct, but version c shows correctly how the pot is physically connected in a circuit.

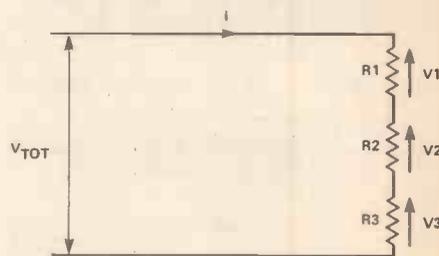


Figure 9. A more complex circuit, consisting of three resistors in series. The total voltage is made up of three voltages across each resistor. The current flows equally through each resistor.

Figure 10. Three parallel resistors. In this circuit the voltage across each resistor is the applied voltage, V , but the total current I_{tot} , is made up of the three separate currents through each resistor.

arrangement — they are often only used to aid our understanding of complex circuits.)

A simple example can be made of the circuit in Figure 9. The series resistors can be replaced by a single equivalent resistor. Its value can be found by using the formulae associated with Ohm's Law. We know the total voltage, V_{tot} , and we know the current, I . Therefore, the equivalent resistor.

$$R = \frac{V_{tot}}{I}$$

But, we also know that $V_{tot} = V_1 + V_2 + V_3$.

$$\text{So: } R = \frac{V_1 + V_2 + V_3}{I}$$

But, $V_1 = IR_1$, $V_2 = IR_2$, $V_3 = IR_3$, so

$$R = \frac{I(R_1 + R_2 + R_3)}{I}$$

therefore $R = R_1 + R_2 + R_3$

In other words, if resistors are in series (and this applies to any number of resistors), their equivalent resistance is found by simply adding their individual resistances. Likewise in the circuit of Figure 10 where three resistors are in

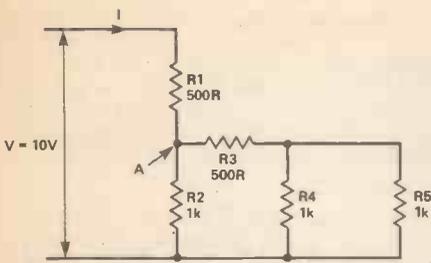


Figure 11. Quite a complex electronic circuit, but we can reduce it in complexity to an equivalent circuit.

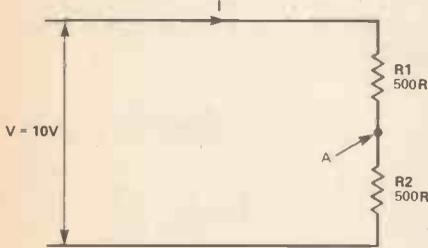


Figure 12. An equivalent circuit of that in Figure 11, used to calculate the voltage at point A.

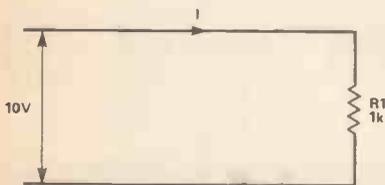


Figure 13. Another equivalent circuit of that in Figure 11, used to find the current, I, in the circuit.

parallel, we know that the equivalent resistance

$$R = \frac{V}{I_{tot}}$$

But, we know that $I = I_1 + I_2 + I_3$, and

$$I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}, I_3 = \frac{V}{R_3}$$

$$R = \frac{V}{\frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}}$$

$$= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

or, inverting both sides

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

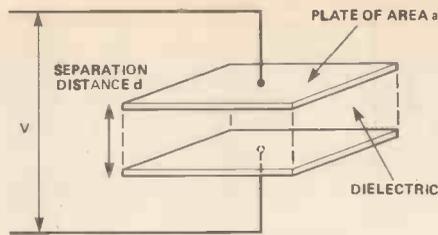


Figure 14. Basic form of a capacitor — two parallel conductive plates separated by a dielectric.

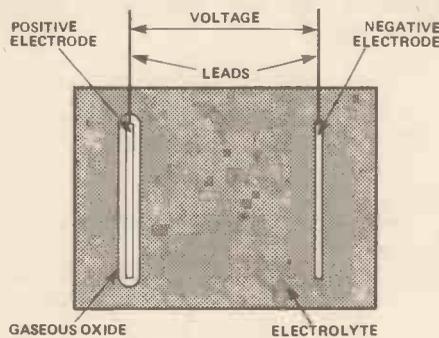


Figure 15. An electrolytic capacitor. The 'plates' are formed by the positive electrode and the surface of the electrolyte. The dielectric is the gaseous oxide layer around the positive electrode.



Figure 16. The circuit symbol for an electrolytic capacitor, showing that it is polarised and must be inserted the correct way round into a circuit. The solid bar indicates the negative lead.

In other words, for parallel resistors (any number) the reciprocal of the equivalent resistor is found by adding the reciprocals of the individual resistors.

Don't be put off by all of this: it's often easier to calculate the equivalent value of paralleled resistors than it would first appear. For instance, if two equal valued resistors are in parallel (say, two 10k resistors) the equivalent value is half of the value of a single resistor (ie, 5k). If three equal valued resistors are in parallel the equivalent value is one third the value of a single resistor (ie, 3k3, following the above example). With four equal resistors, the equivalent is one quarter, and so on.

The equivalent resistance of two unequal resistors (R_1 and R_2) in parallel can be calculated quite easily by the simple formula:

$$R = \frac{R_1 \times R_2}{R_1 + R_2}$$

However, if there are three or more unequal resistors in parallel then you'll have to use the reciprocal formula, but that doesn't happen often, thankfully.

Armed with all this knowledge, it is possible now to simplify some quite

complex circuits. An example might be something like that in Figure 11.

We might have to calculate the current I, and the voltage at point A in the circuit. It looks complicated but, in fact, isn't. Take it in the following stages:

- 1) Calculate the equivalent resistance resistors R4 and R5 — ie, two resistors of 1k in parallel = 500R
- 2) Calculate the equivalent resistance of R3 in series with that in stage 1 ie, two resistors of 500R in series = 1k
- 3) Calculate the equivalent resistance of R2 in parallel with that in stage 2 ie, two 1k resistors in parallel = 500R
- 4) The circuit has now been reduced to that in Figure 12. The voltage at point A must be 5V ie, it is at the mid-point of the potential divider formed by the two resistors
- 5) The total equivalent resistance is formed by two 500R resistors in series (= 1k) and so the final equivalent circuit is as shown in Figure 13.

From the formulae associated with Ohm's law, the current.

$$I = \frac{V}{R} = \frac{10}{1000} 10\text{mA}$$

QEDI Simple, isn't it?

The second component family we need to look at is that of capacitors. Any capacitor (Figure 14) consists essentially of two parallel plates of conducting material separated by an insulator (called a dielectric). When a capacitor is inserted in an electric circuit (such as that in Figure 14) so that the voltage appears across the capacitor plates, electrons gather on the negative side. Similarly electrons are repelled from the positive side so that a depletion of electrons occurs there. The circuit symbol for a capacitor is shown in Figure 15.

If the capacitor was instantly disconnected from circuit in this condition this gathering of electrons on one plate and depletion on the other will remain — the capacitor is said to hold its 'charge'.

The capacitance of a capacitor is a measure of its ability to hold this charge and is measured in Farads (abbreviated F). One Farad is a large unit in electronic terms and so capacitors of values in uF (microfarad ie, 10^{-6}F); nF (nanofarad ie, 10^{-9}F); pF (picofarad ie, 10^{-12}F) are often used.

In the same way that resistance of any material can be calculated from the formula

$$R = \rho \frac{l}{a}$$

so can capacitance of a capacitor be calculated from the formula:

$$C = \epsilon \frac{a}{d}$$

where a is the area of the capacitor plates and d is the distance between plates. The constant, ϵ , is the permittivity of the dielectric used in the capacitor (I suppose it could be called

'capacitance' but that's a bit of a mouthful!). Different insulators have different permittivities and in the same way that conductors are chosen for resistors because of their resistivity, so insulators are chosen for capacitors because of their permittivity.

Although the basic idea of a capacitor consisting of two plates separated by a dielectric remains true whatever dielectric is used, the actual shape and appearance is altered due to the physical characteristics of the dielectric. There are three common solid dielectrics: polyester, ceramic and mica. In addition, there is a capacitor whose dielectric is the thin layer of metal oxide which occurs due to electrolysis — this is known as an electrolytic capacitor. The four types are:

1) Ceramic

Ceramic is very brittle and cannot be easily shaped so capacitors are formed on the simple parallel plate basis already described. Ceramic has a high permittivity and so quite high capacitor values can be made with small body sizes.

2) Mica

Like ceramic, mica is very brittle and cannot be shaped, so again mica is only used in a parallel plate arrangement. Mica's permittivity is not so high as ceramic's, so for the same body size only lower capacitor values can be made. Mica's main advantage is the fact that it allows highly accurate capacitors ($\pm 1\%$) to be achieved.

3) Polyester

Polyester film is easily shaped and can be rolled between aluminium foil (the plates) to give large areas of plates therefore high capacitor values can be made with small body size.

4) Electrolytic

Electrolytic capacitors depend on the electrolysis of a liquid electrolyte to form a layer of gaseous oxide on one of two electrodes inserted into the electrolyte (Figure 16).

The two 'plates' consist of the positive electrode and the liquid electrolyte (not the negative electrode!) The distance between the plates is the thickness of the gaseous oxide. Electrolytic capacitors are *polarised* and so must be inserted into circuit the correct way round otherwise damage will occur. In practice they are marked with a symbol (+) or (-) to indicate polarity, or sometimes the positive end of the capacitor body is ridged. The circuit symbol of an electrolytic capacitor is shown in Figure 17.

It is impossible to manufacture accurate values of capacitors using electrolytic dielectrics but nevertheless they are extremely useful due to the fact that very high values (say, 10000F) can be made with relatively small body sizes.

All capacitors have a voltage rating and the potential difference applied to a capacitor's leads must never exceed the rated voltage (which is normally printed


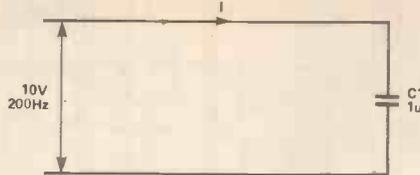


Figure 17. The simplest AC capacitor circuit. Calculation of the current flowing in the circuit is identical to a resistor circuit as long as we know the reactance of the capacitor] and that depends on the source voltage frequency.

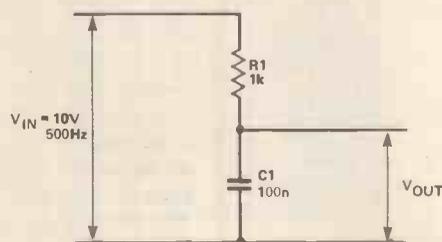

$$\text{The reactance of } C1 \text{ at } 500\text{Hz} = \frac{1}{2\pi \times 500 \times 100 \times 10^{-9}} = 3k2$$

$$\text{Therefore } V_{OUT} = \frac{3k2}{4k2} \times 10 = 7V6$$

Figure 18. A potential divider using a capacitor circuit. The output voltage depends not only on the value of the capacitor but also on the frequency of the input voltage!

on the capacitor's body). In a lot of cases the voltage rating will be high enough for the majority of applications but electrolytic capacitors for example have quite low ratings eg 10V and care should be taken to make sure the rating of any capacitor is not exceeded.

Now capacitive effects are very different in DC circuits from AC circuits. So different in fact that I am going to leave their DC effects until another month. For the rest of this instalment I will concentrate on capacitors in AC circuits.

I have already pointed out that resistors can be used in AC or DC circuits and all calculations are identical in either. The circuits used with resistors can be used with capacitors too, however the similarities between resistor circuits and capacitor circuits only occur when the power sources of the capacitor circuits are AC.

For example, the circuit of Figure 18 shows a capacitor of value 1uF connected to an AC source of 10V at 200Hz. Note that even though the power source is AC, I have assumed the circuit to be drawn in an instant in time — and at the particular instant in question the voltage at the top of the circuit is positive (hence the voltage arrow is pointing upwards and the current arrow heads points to the right). The voltage and current could equally have been the opposite way round if a different instant were chosen.

Now, how can we calculate the current in the circuit?

The answer comes from the fact that any capacitor has *reactance* (don't worry about what it is — just think of it for the time being as an AC resistance!) measured like resistance, in ohms, but given the symbol X. Now, a capacitor's reactance is given by the formula

$$X = \frac{1}{2\pi f}$$

From this formula, you will see that the reactance is inversely proportional to frequency of the source. So the capacitor's reactance will go down as the frequency goes up.

In other words, we need to know the frequency of the source to define exactly what the circuit does.

At 200Hz a capacitor of value 1uF will have a reactance

$$X = \frac{1}{2\pi f c} = \frac{1}{2\pi \times 200 \times 1 \times 10^{-6}} = 800R$$

So, the current I in the circuit of Figure 17.

$$I = \frac{V}{R}$$

or, more correctly speaking.

$$I = \frac{V}{X} = \frac{10}{800} = 12\text{mA}5$$

Likewise, any other of the circuits using resistors, that we have looked at this month can be used with capacitors (but AC only remember!)

Let's take a last look at the potential divider circuit but with a capacitor instead of one of the resistances, as in Figure 18.

The output voltage is defined exactly as before (but using reactance X, instead of resistance R2) in the formula. That is

$$V_{out} = \frac{X}{X+R_1} \times V_{in}$$

But, we know that reactance, X, changes with frequency, so the output voltage of the potential divider must also change as applied frequency changes! This concept is an important one — it forms the basis of many things, eg tone controls of an amplifier, and we will be studying it a great deal.

But that's enough for this month: we have seen a lot of new things — components, circuits, formulae etc. Next month we will look at another family of components — the most important as it happens. Like resistors, this family uses semiconductors as its main elements but with very different effects.

FOR HI-FI & ELECTRONICS ENTHUSIASTS
CONCEPT ELECTRONICS LTD
 51 Tollington Road, London N7 6PB

Mail order only

We are the specialist of electronic kits and rack mounting cabinets. A catalogue with complete range of products including pre-amp modules, power amp modules, pre and power amplifier modules, complete kits of amplifiers, equalizers, reverberation amplifiers (with cases), alarm clocks, appliance timers, CB amplifiers, test equipment, control modules, music generator, battery fluorescent light and high quality rack mounting cabinets etc. with illustrative pictures now available at the cost of 35p + 25p p&p.

Professional rack mounting cabinet



Panel Size W H (inch)	Rear Box		Price	
	WHD	AL	STEEL	
19 x 5	17 x 4.5 x 10	27.54	23.54	
19 x 4	17 x 3.5 x 10	25.24	21.24	
19 x 3.5	17 x 3 x 10	24.09	20.09	
19 x 3	17 x 2.5 x 10	24.09	—	
19 x 2.5	17 x 2 x 10	22.94	18.94	
19 x 6	17 x 5.5 x 12	28.69	24.69	
19 x 5	17 x 4.5 x 12	27.54	23.54	
19 x 4	17 x 3.5 x 12	25.24	21.24	
19 x 3.5	17 x 3 x 12	24.09	20.09	
17 x 3.5	15.5 x 3 x 9	21.79	17.79	
17 x 2.5	15.5 x 2 x 9	20.64	16.64	
17 x 4	15.5 x 3.5 x 12	25.24	21.24	
17 x 3	15.5 x 2.5 x 12	24.09	20.09	

Please add £2.50 p/p per item

★ Wholly made of black anodised aluminium sheets ★ Suitable for high quality amplifiers and many other purposes ★ Top, side and rear cover, removable for access
 ★ Separate front mounting plate ★ Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles ★ With ventilation slits and plastic feet.

The low cost steel version is also available. The size and features as well as the front panel is the same as the aluminium cabinets except the rear box is manufactured from steel painted in black.

CONTROL MODULES



- TY-7 Electronic touch switch
£2.90 Kit £4.50 Ass.
- TY-11 Light activated switch
£2.20 Kit £3.50 Ass.
- TY-18 Sound activated switch
(Clap switch) £4.50 Kit £5.95 Ass.
- TY-38 Sound activated switch
(voice-switch) £5.50 Kit £7.50 Ass.
- TY-41 Infra-red remote control
(Receiver and transmitter)
£17.20 Kit £21.95 Ass.

HI-FI AMPLIFIER MODULES



- TA-323A 30W + 30W stereo amplifier
£18.95 Kit £23.95 Ass.
- TA-820 60W + 60W stereo amplifier
£27.50 Kit £33.50 Ass.
- TA-920 70W + 70W stereo amplifier
£35.50 Kit £42.50 Ass.

MAIL ORDER PROTECTION SCHEME

If you order goods from Mail Order Advertisers in this magazine and pay by post in advance of delivery, this publication will consider you for compensation if the advertiser should become insolvent or bankrupt, provided:

1. You have not received the goods or had your money returned; and
2. You write to the publisher of this publication explaining the position not earlier than 28 days from the day you sent your order and not later than 2 months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the advertiser has been declared bankrupt or insolvent to a limit of £1,800 per annum for any one advertiser, so affected, and up to £5,400 p.a. in respect of all insolvent advertisers. Claims may be paid for higher amounts, or when the above procedures have not been complied with, at the discretion of this publication, but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of reader's difficulties.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine (not, for example, payments made in response to catalogues, etc. received as a result of answering such advertisements):

CLASSIFIED ADVERTISEMENTS ARE EXCLUDED.

Where on Earth can I obtain top quality Transistors, Ic's, Capacitors, Resistors, Cases, Cable, Fuses, Bulbs, Plugs, Sockets, Nuts, Bolts, Coils, Chokes, Test Instruments & Books, all at a price I can afford ?



But of Course !!!

We accept

Express Mail Order Service

Callers Most Welcome

Twyford

ELECTRONICS LIMITED

22 STATION ROAD, TWYFORD, near READING, BERKS.

Telephone 0734 340833

SEND S.A.E. A4 Size Plus 25p For Our Catalogue

Variable Power Supply

Chuck out your batteries and get plugged into the HE 3 - 30 volt Power Supply.

G. Macaulay

NO MATTER what your interest in electronics, there are two items of test gear that are essential. One is the common or garden multimeter and the other is a good power supply unit.

Most projects which appear in this publication need a power supply in the range of 3-30V, with a current consumption from a few hundred microamps to several hundred milliamps. Sometimes projects can be run from batteries — but since it costs nearly two thousand times more for battery power than for mains electricity, it obviously makes good sense to use the latter!

Looked at this way, a PSU can be seen as a good investment which will pay for itself in a short time. The design presented here is both simple to build and inexpensive, moreover it has a professional performance. The design is also tried and tested, since several hundred have already been supplied in kit form over the the last couple of years.

The desirable features of such a PSU are fairly easy to summarise.

Firstly, it must be capable of delivering about an amp of current; this will allow items such as power amps to be driven directly from the supply. It must also have a metered output so that the voltage can be set accurately, while low ripple is an important requirement, especially when powering audio and logic circuitry; this design has less than 10mV ripple voltage on the output.

Apart from these specifications, short circuit protection is essential — otherwise you will soon end up with a dead supply, and have to replace the output stage.

Considering the confined space in which many constructors work, it is almost inevitable that the output will be shorted out sooner or later! No power supply can be guaranteed to operate into a short indefinitely, but the present design will withstand limited duration short circuits without damage.

Last but by no means least the power supply must be portable. 'Murphy's Law' will dictate that the power supply will always be needed in the most inaccessible places!



The Current

The PSU has been designed specifically for experimenters and so meets all the requirements just outlined. Its output is fully variable from three to thirty volts and has automatic current limiting set at approximately 1.1 amps; the ripple voltage is typically 3mV peak-to-peak, 1mV RMS.

The circuit diagram is shown in Figure 1. For descriptive purposes it can be broken down into three parts: first, raw DC at about 30V is generated from the secondary (24V) winding of T1 by the bridge rectifier BR1 and is smoothed by the 2000u capacitor formed from C1, C2.

The next section, based on IC1, generates a very stable, ripple-free reference voltage. The IC is connected as a comparator with a gain of two; at


the switch-on, the Zener ZD1 presents a high impedance and therefore almost the full output voltage appears at pin 3 (the drop across R1 due to an input current of microamps is negligible). The output is also coupled to the inverting input, pin 2, via the voltage divider formed by R2 and R3, so that about half the input is applied to pin 2. Therefore no matter what the condition of the output when power is first applied, the non-inverting input is always more positive than the inverting input, so output *must* swing towards the positive rail.


But as it passes the Zener voltage, pin 3 stabilises at 15V, and the output remains rock steady on 30V. Once stabilised, the current drive to ZD1 is virtually constant and this results in very little ripple voltage on the reference output.

A proportion of the reference voltage is picked off by RV1 and drives the non-inverting input of IC2, another comparator but with a gain of one.

(Editorial Note: Although this circuit is tried, tested and has been proved to be generally reliable, it may not work as described with some 741 ICs. If any instability is encountered, reliable operation can be guaranteed by connecting a resistive divider of 10k and 4k7 between the 30V rail and 0V, and

Figure 1. The Circuit.

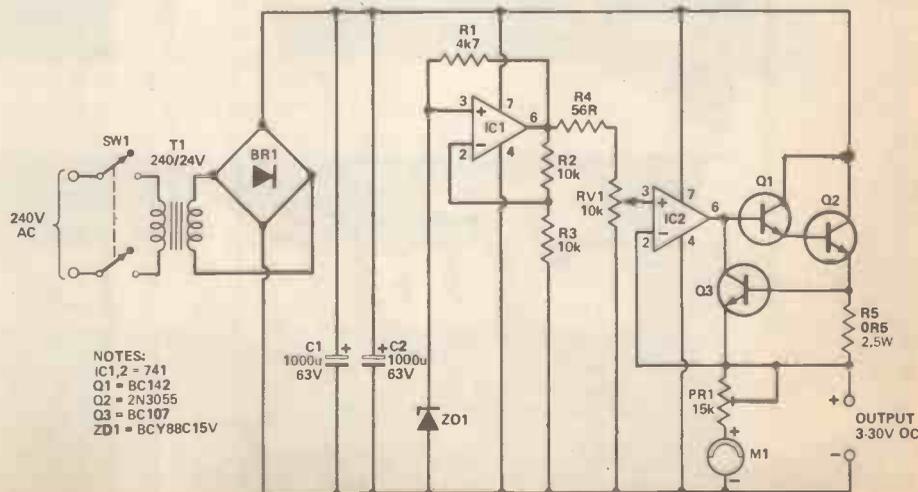

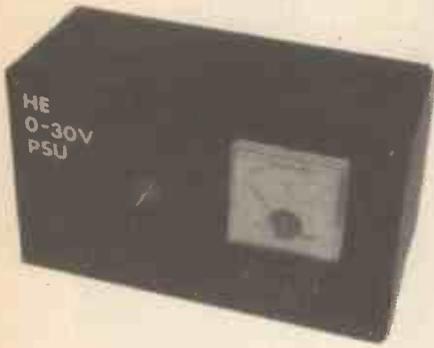

connecting a 1N4148 signal diode from the junction of the resistors to the cathode end of ZD1 (connect the cathodes together). Then, at power-on, the diode is forward biased, placing about 10V across ZD1 and ensuring a positive output from IC1. As soon as the voltage on the inverting input passes 10V, the new diode is reversed biased and the op-amp will maintain a constant current drive to ZD1. However this modification will only be required in exceptional cases - and it may be simpler just to use a 741 from a different batch.)

Parts List

RESISTORS

(all 1/4 watt 5% carbon, except as noted)

- R1 4k7
- R2, 3 10k
- R4 56R
- R5 0R5
2 1/2 watt wire-wound

POTENTIOMETERS

- RV1 10k
1in carbon
- PR1 15k
vert pre-set

CAPACITORS

- C1, 2 1000u 63V
axial electro

SEMICONDUCTORS

- IC1, 2 741
op-amp
- Q1 BC142
- Q2 2N3055
- Q3 BC107
- ZD1 BCY88C15V
- BR1 1A6/200V
PIV
bridge rectifier

MISCELLANEOUS

- SW1 DPDT
(part of RV1)
- T1 240/24V, 1 1/2A
- M1 2mA panel meter
PCB; case (see Buylines); control knob; 2 x sping-clip terminal; cable clamp; wire, solder, nuts and bolts etc.

BUYLINES page 34


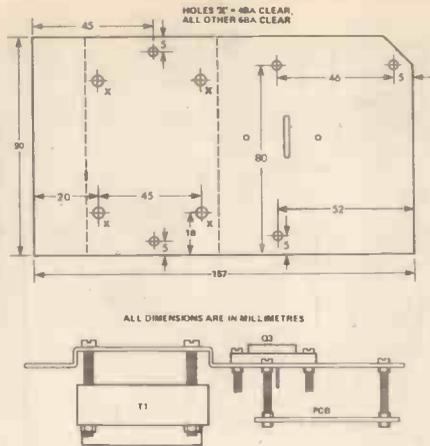


Figure 2. Assembly positions for the power supply's internal mountings: above, where and how to drill; below, the assembly seen from above.

Figure 3. The external mounting positions: above, the front; below, the back.

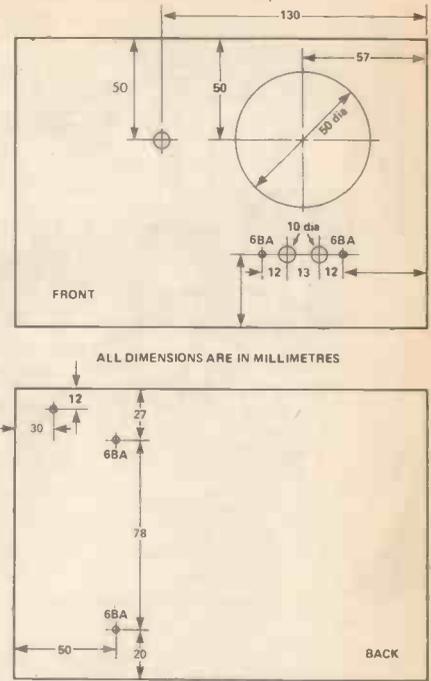

Pin 6 of IC2 drives the Darlington pair, Q1, 2. Because these are connected in the feedback loop around IC2, the output voltage at the emitter of Q2 will exactly equal the input voltage on pin 3, since the pin 6 voltage will be forced slightly higher to compensate for the base-emitter voltage of the two transistors, plus the voltage dropped across R5. At the same time, any fluctuation in output voltage caused by varying load currents will be reflected around the feedback loop, and will be similarly compensated for at the output of IC2.

The output voltage is monitored by M1 via scaling resistor PR1; current limiting and short circuit protection are provided by monitoring the voltage across R5, which is in series with the load. If excessive current is drawn from the supply, this voltage will go above the OV6 level required to turn on Q3, which then shunts current away from the base of Q1, thereby limiting the output current.

The circuit provides limited protection against operation into a short, and this should be avoided for prolonged periods because Q1 will eventually (and sooner than later) overheat and blow out. However at current of 1A or less, there is no danger of this occurring.

Construction

The work involved here falls neatly into two parts, mechanical and electronic; however it is far easier to do the mechanical part first. Start with the meter; examine the back of this and you will see two brass nuts. Undo these and remove the retaining shroud.


Next, following Figure 2, drill the front of the case. Attach the pot, SK1 and meter into position. Once this has been accomplished attention can be

turned to the heatsink. Figure 2 shows the position of all the mounting holes whilst Figure 3 shows the general arrangement of the completed assembly. Although it is possible to mark out all the hole positions it is easier, in practice, to use the PCB and transformer mounting holes as a template, as this also saves a considerable amount of time.

The transformer and Q2 can now be mounted. The mounting holes for the latter are already drilled in the heatsink; Q2 does not require an insulating kit in this application.

Lastly the mounting holes for the heatsink assembly should be drilled in the back of the box as shown in Figure 2, and this completes the mechanical assembly.

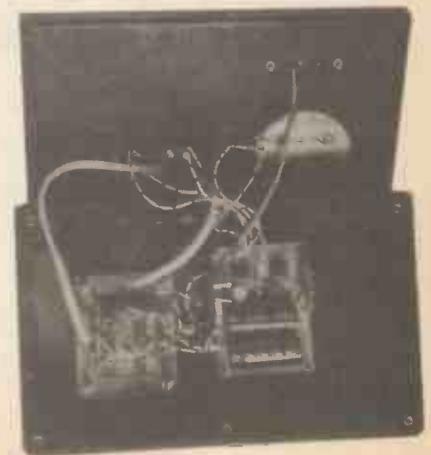Now the electronics can commence. The overlay and interwiring is shown in Figure 4. The PCB should be wired first, paying attention to the correct orientation of the electrolytics and semiconductors. Once the board has been completed it should be checked for solder blobs, dry joints etc before



Variable Power Supply

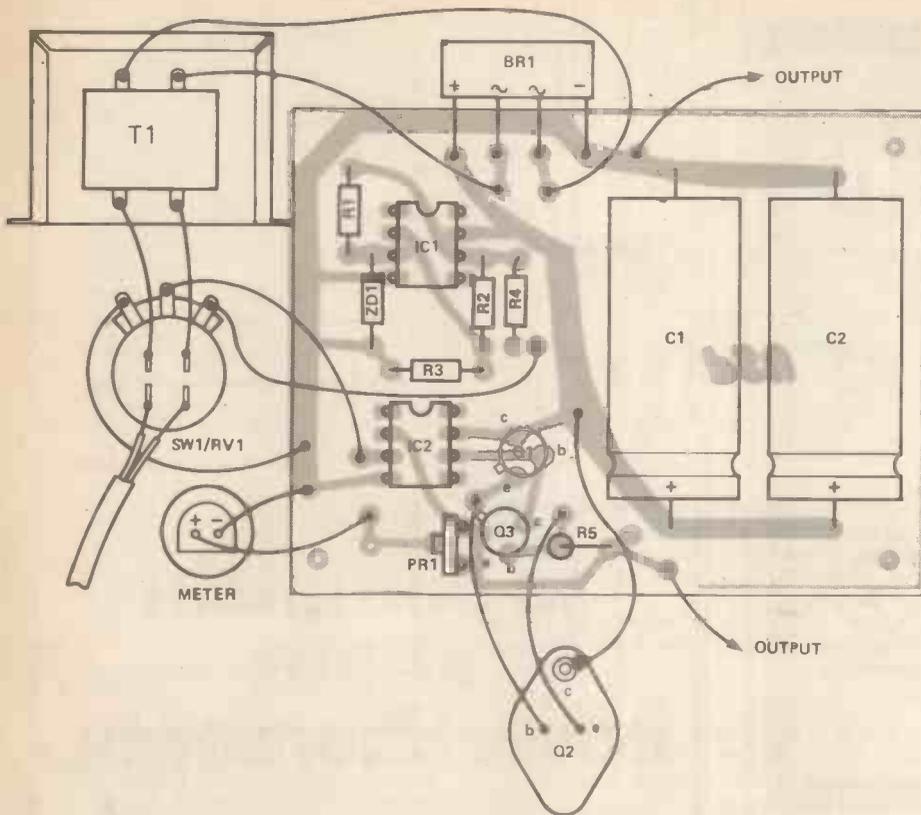


Figure 4. The components. The trick is to get the wire links short enough so that they don't make a 'rat's nest' and long enough so that they don't pull off if any components work loose in transit.

being mounted onto the heatsink.

As shown in the diagram the board is mounted by means of long 6BA screws, secured in position by nuts either side of the board. Ensure that the board is about 1½ in above the heatsink to facilitate connection to Q2. Before mounting the board, solder flying leads to it, leaving each about a foot long.

Once the PCB is mounted final assembly can commence. Connect the flying leads to their respective destinations, shortening them as required, then fit the completed assembly to the back of the case and the construction is completed.

Setting Up

Adjust PR1 to the half-way point and RV1 to minimum, then switch on. Now if you take RV1 to about the mid-point, there should be an indication on the built-in meter.

Connect a multimeter, set to read at least 30VDC, across the output and tweak RV1 until it reads 30V. Then with the lid removed — and being extremely careful not to come into contact with the mains wiring! — adjust PR1 until the PSU meter also reads 30V. This completes the set-up adjustments and rotating RV1 should now produce an output voltage between 3 and 30V for you to use as you please.

DURRANTS (ELECTRONIC COMPONENTS)

9 ST MARYS STREET, SHREWSBURY, SHROPSHIRE
TELEPHONE 61239

ALL PRICES INCLUDE V.A.T. add 40p P&P

Resistors ¼w 5% c/film all values 1p each (min 10); Resistors ½w 5% c/film all values 2p each (min 10); Capacitors (polyester) .001 MFD to .1 MFD 8p each; Capacitors (ceramic) 1pf to .047 MFD 6p each; Capacitor packs 100 polyester/ceramic £1.50, Resistor Packs 100 ¼w 5% c/film 60p; Resistor/Capacitor Packs 100 mixed 90p; Bush Stereo Cassette Panel (new with diagram) £1.00; T.C.E. Stereo Decoder Panel (new) £1.00, Copper Clad Board 8¼" x 5½" 75p; Copper Clad Board 4" x 5½" 39p; Slide Switch D.P.D.T. (min type) 12p each 10 for £1.00; Reed Switch N/o contacts 15p each 10 for £1.20; M.E.S. Lampholders (screw down type) batten 10p each; Relays 24v coil 2 pole c/over 30p each; Holder for above 10p each; Connecting Wire Assorted Colours 50 mtrs 60p; Micro switch 10a contacts, lever type 35p; Micro Switch Burgess (Min Type) 20p; Bridge Rectifier 30v350ma 25p each 5 for £1.00; Transistors BFR50 — BFY51 15p; ORP12 Light Dependant Resistor £1.20; Cassette Tape Counter Units 45p; Mains Filter 240v 15A £1.50; Terminal Blocks 12 way 25p; Stranded Connecting Wire: orange, brown or black 10 yds 20p; Heat Sink Compound 95p per tube; Soldering Irons 240v 25w £4.99; 100 mfd 63v Radial Capacitors 8p each 10 for 50p; 2.2 MFD 63v Axial Capacitors 5p each 10 for 40p; 100 Assorted Nuts and Bolts (B.A. & Metric) 25p

This is a sample of the many thousands of items in stock
Price lists 15p & 25p P&P

Modem Kit Only £39.95

- * CCITT standard
- * 300 baud full duplex
- * Direct connection:- greatly reduces data loss associated with acoustic couplers
- * Powered from phone lines therefore no power supply required
- * Opto coupled data in and data out for intrinsically safe operation

Build it yourself for £39.95 including VAT and postage (note — case not included).

Racom Ltd, Dept. A.
81 Cholmeley Road, Reading, Berks RG1 3LY
Tel: 0734 67027

PROBLEMS WITH THAT PROJECT?

We will — * BUILD
* TEST
* REPAIR

All your Electronics Kits and projects.

Prices from only £5.00

* Call us now for a quote. *

WEB Logic Systems Ltd
15 High Street, Harpenden, Herts.
05827-62119

'BARGAIN TIME'		VOLTAGE REGS. T0220 39p each	
UV PROMS 2716 £2.30 2732 £4.12		+7805 +7818 —7905 +7812 +7824 —7912 +7815 —7915	
DIODES In4148 2p each or £1.50/100 In4001/4002/4003 3p each Zener Diodes 400mW (BZY88C) 4p each or £3 per 100		LED'S — 5mm All with Clips Red 9p; Green 10p; Yellow 11p Special pack 10 of each £2.50	
I.C. SOCKETS Low profiles Turned pin Pins 8 6p — 14 9p 32p 16 9p 37p 18 12p 42p 20 14p — 22 16p — 24 15p 53p 28 19p — 40 26p 92p 64 — £2		RESISTORS — E24 Range Carbon Film, Bandoled 100 Assorted values 10 per value . . . 95p 1000 Assorted values 50 per value . . . £8	
HEATSINKS T0220/SOT32 Finger Heatsinks Vert. or Horiz. Mounting 18 deg c/w 20p each; 15 deg c/w 24p each To 6 push on 9p each 46 x 46mm Finger type drilled To3 7 deg c/w 28p each 55 x 55mm Finger typed drilled To3 4.5 deg c/w 31p each 65mm x 20mm x 50mm extruded sink 2.75 deg c/w 98p each			
TERMS: Strictly cash with order. All prices inclusive of VAT. HANDLING: Charge of 50p on orders under £5. Heatsink Listing and Data Sheets sent with all orders or on receipt of large sae with 26p of postage.			
CAMTEC CIRCUITS AND SYSTEMS LIMITED 5 York Road, Bognor Regis, West Sussex PO2 1QW Tel: (0243) 862911			

**HOBBY HERALD
HAS ALL THE
LATEST NEWS
FOR THE
ELECTRONICS
HOBBYIST**

When you need to update yourself with all that is available in the "Do-it-yourself" market, then you need the Hobby Herald.

Packed with product information essential to the electronics enthusiast, this new electronics catalogue lists over 60 exciting products ranging from All Purpose Cutters to Verobloc, the solderless breadboard. All products are available throughout the U.K. from over 200 stockists.

HOBBY HERALD

Alternatively ordering products through the Herald is simplicity itself, and you can pay by either cheque, Barclaycard or Access. So make sure you get your copy of Hobby Herald by ringing

(04215) 62829.



BICC-Vero Electronics Ltd.,
Industrial Estate,
Chandlers Ford, Hampshire,
SQ5 3ZR.

BICC

vero

SAVE £££'s ON HOME HEATING BILLS

UNIQUE DIGITAL THERMOSTAT
POSSIBLE FUEL
SAVINGS OF
UP TO 25%



Normally manufactured exclusively for the trade. Features: • Continuous readout of ambient temp via 3 digit 7 segment display • LED indicates when pump is in operation • 0.2°C Hysteresis • 240v 3A control contacts • Switched set temperature



High specification — Simple to calibrate — Connect in place of existing thermostat — Requires 240v 2VA supply — Kit includes all necessary components, Enclosure, diagrams and instructions.

Kit price only £29.95. Assembled Price £45.00
plus £1 p&p (prices include VAT)

Send cheque or PO to: **DICON ELECTRONICS LIMITED**
Bond Street, Bury, Lancs BL9 7DU Tel 061-797 5666

It's easy to complain about advertisements.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.

ASA Ltd., Brook House, Torrington Place, London WC1E 7HN.

FREE CAREER BOOKLET

Train for success, for a better job, better pay

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, Through ICS home study, used by over 8 million already! Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your FREE CAREER BOOKLET today
—no cost or obligation at all.

C & G BASIC
ELECTRONICS

ELECTRONIC
ENGINEERING

C & G RADIO
AMATEUR'S Exam

COMPUTER
PROGRAMMING

RADIO & AUDIO
ENGINEERING

TV & AUDIO
SERVICING

RUNNING YOUR
OWN BUSINESS

ELECTRICAL INSTALL-
ATIONS/CONTRACTING

AUTO
MECHANICS

C & G BASIC MECHAN-
ICAL ENGINEERING

Name _____

Address _____

P.Code _____

ICS
Division of National
Education Corporation

ICS
Dept L261
160 Stewarts Road,
London SW8 4UJ



01-622 9911
(all hours)



If you missed
out on Breadboard
'79, '80, '81 and '82
Now's the time to catch up with



Friday November 25th	10am - 6pm
Saturday November 26th	10am - 6pm
Sunday November 27th	10am - 4pm

Improved venue

We have transferred Breadboard to Cunard International Exhibition Centre, so that we can offer improved facilities to the visitor, including car parking and ease of access by rail, tube and car, all in a modern attractive setting. We have also arranged a reduced hotel/rail fare package to attract enthusiasts from all parts of the country.

Planned features include

1. Full range of lectures planned over 3 days to cover most aspects of electronics and computing.
2. Electronics/Computing Advice Centre — manned by experts.
3. Demonstration of electronic organs and synthesisers.
4. Holography presentation.
5. Practical Demonstration on "How to produce printed circuit boards".
6. Computer Corner — extensive display of computer hardware — "Try Before You Buy".
7. Amateur radio Action Centre.
8. Computer controlled model railway competition.
9. Pick of the Projects — Demonstration of the best from ELECTRONICS TODAY INTERNATIONAL, HOBBY ELECTRONICS and ELECTRONICS DIGEST over the past ten years.
10. Giant T.V. screen video games.
11. Robotic display.

Why not bring the family to the show and enjoy a weekend in London? We have arranged a complete hotel package for our visitors to the exhibition. All inclusive rail tickets also available. Send now for details of what we, the organisers, can offer you.

Write to: Breadboard '83
ASP Exhibitions
145 Charing Cross Road
London WC2H 0EE

GRIPOMETER

How strong are you? The answer's in your hands!

Ian Hickman

ARE YOU still feeling your way in the Wonderful World of Electronics? Or beginning to get the hang of it and looking for an interesting project to tackle? Either way, look no further! Here is a project which is not too complex, is educational and at the same time fun to build — and use. The components are all standard and inexpensive, so there's no problem there. Furthermore, just to keep your feet on the ground and remind you that electronics has to interface with the everyday world of people and things, the project involves just a wee bit of mechanics. (Did I hear you say UGH! — never fear, for those who can't face the construction work, a full kit of parts is being made available).

When I visited the annual fair as a lad, beside the big attractions like the steam roundabout with its mechanical organ, and the Dodgems there were smaller attractions as well — perhaps there still are. Among these were various "try-your-strength" stalls, like the punch bag and the one with a bell twenty feet up in the air which you could ring (if you were Superman) by wielding an enormous mallet. There was also one with a couple of handles you could squeeze, and a dial which measured the strength of your grip. This last one always fascinated me, though as a lad I couldn't even reach the handles and in any case preferred to save my pennies for the Helter-Skelter.

The fairground Test-Your-Grip machine was doubtless all done with good-old fashioned mechanics, but HE now presents an *all electronic* Gripometer. This is a gripometer with another difference too: with the aid of a secret "go faster" button, you can astound your friends with your superhuman strength!

Putting On The Squeeze

Figure 1 shows a block diagram of the Gripometer. The "linear displacement transducer" is quite simply a slider type potentiometer with 60mm travel, and it is operated by a level with a spring return. If you have grappled with the "O" level physics syllabus, you will recognize the three types of lever in Figure 2. The type-3 lever is the one which provides the least mechanical advantage for the "effort" — your hand — and is therefore just the one for our Gripometer! Your handgrip is opposed by a spring and the resultant


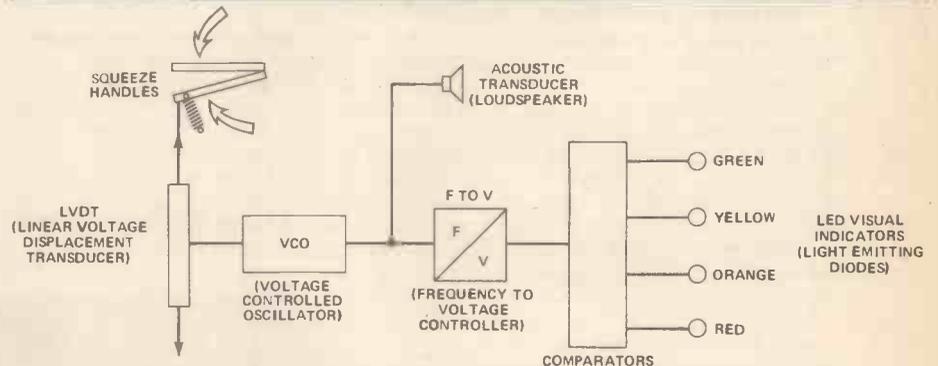
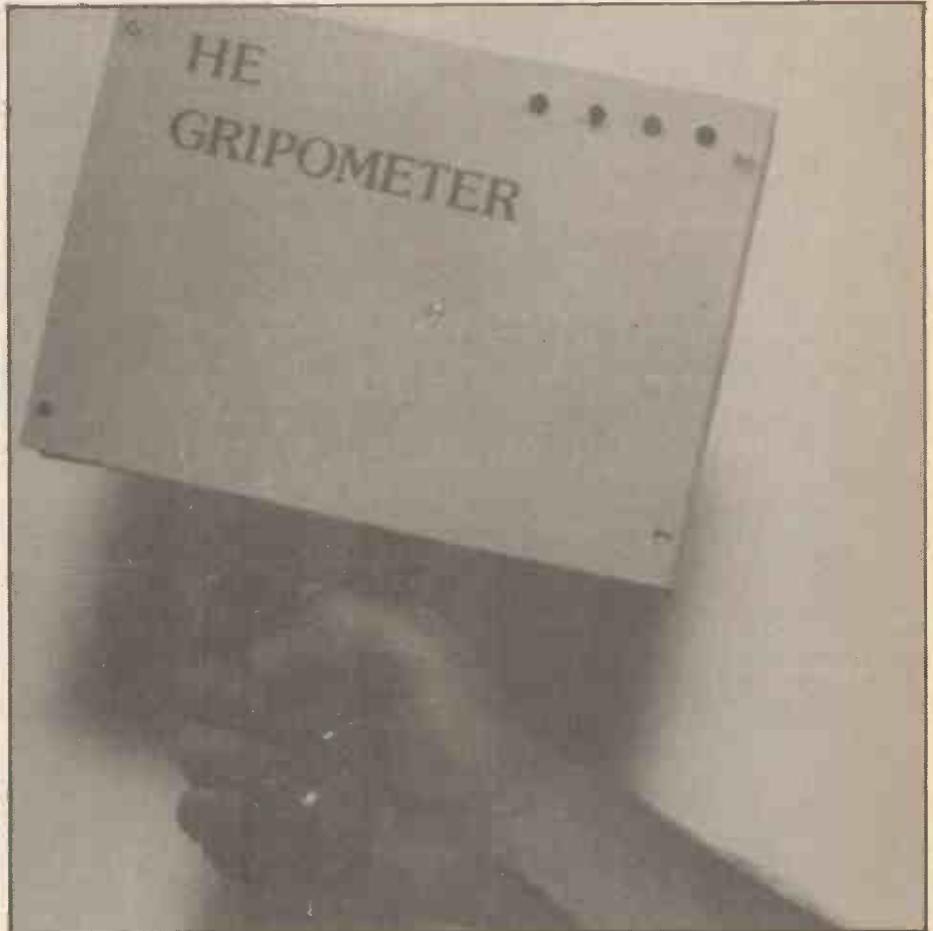


Figure 1. A block diagram of the HE Gripometer.

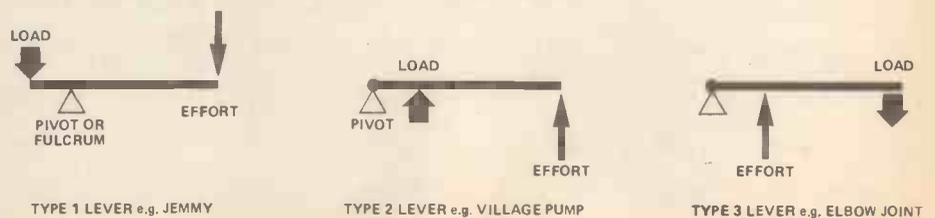

TYPE 1 LEVER e.g. JEMMY

TYPE 2 LEVER e.g. VILLAGE PUMP

TYPE 3 LEVER e.g. ELBOW JOINT

Figure 2. The three basic types of lever.

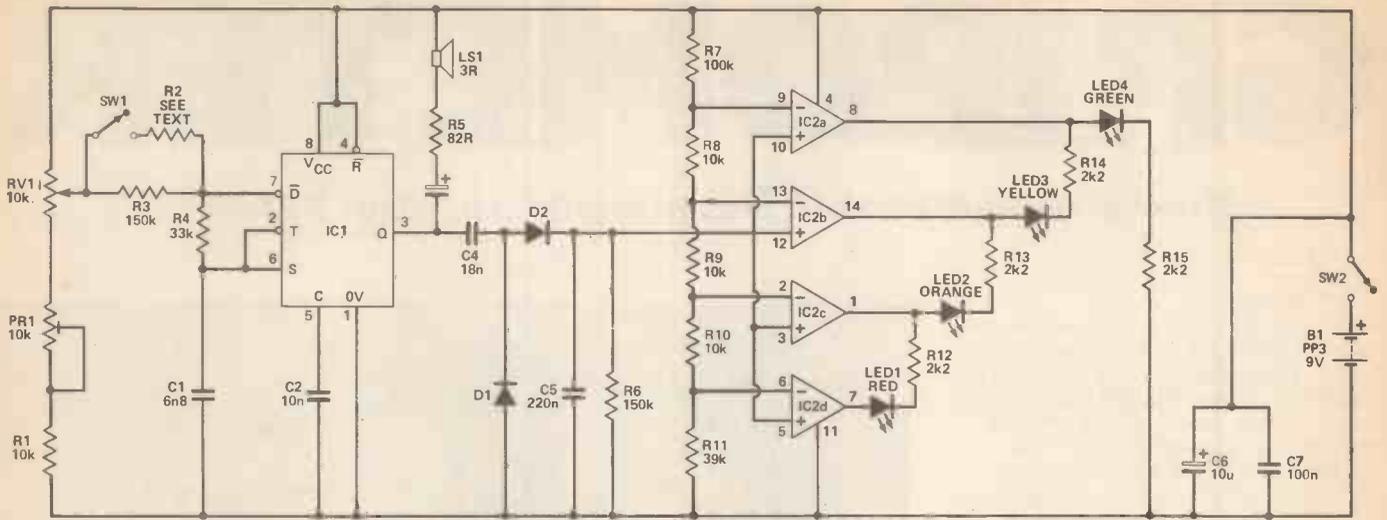


Figure 3. The Gripometer circuit.

movement of the lever works the linear potentiometer as in Figure 4.

This brings us to the circuit diagram of Figure 3, in which the linear potentiometer is RV1. The normal position of the wiper is near the bottom end of its travel, due to the action of the spring. In this position, the voltage at the wiper is less than $\frac{2}{3}$ of the battery voltage, with the result that (as explained elsewhere) the timer IC, IC1, will not oscillate. As the handgrip is squeezed, the wiper of RV1 moves upwards towards the positive supply rail, +9V. IC1 thus starts to oscillate as a low frequency, getting higher and higher as the wiper moves upwards. The output at pin 3 is drives the loudspeaker, giving a higher pitched sound the harder you squeeze the handles.

The pulse output waveform at pin 3 of IC1 is also applied to a simple frequency to voltage converter circuit, consisting of C4, D1 and D2, C5 and R8. On the negative going edge of a pulse at pin 3 of IC1, D1 conducts, leaving C4 discharged. On the following positive going edge, D2 turns on and the pulse voltage is shared between C4 and C5. As C5 is the larger, only a little of the voltage appears across it, but C4 is discharged again on the next negative going edge and adds a little charge to C5 on the next positive going edge again, and so on. The charge added to C5 on each positive edge builds up the voltage across C5 until a balance is reached with the discharge current through R8. The higher the frequency of the waveform at pin 3, the more charge per second is fed via D2 onto C5, and so the higher the voltage across it, although the relationship is not linear. This voltage is applied to the non-inverting (+ve) inputs of all four op-amps of IC2. The inverting (-ve) inputs of the op-amps are connected to voltages derived from the potential divider chain R9, 10, 11, 12 and 13. When IC1 is not oscillating, there is of course no voltage across C5, so the non-inverting input of each op-amp is at a lower voltage than its inverting input.

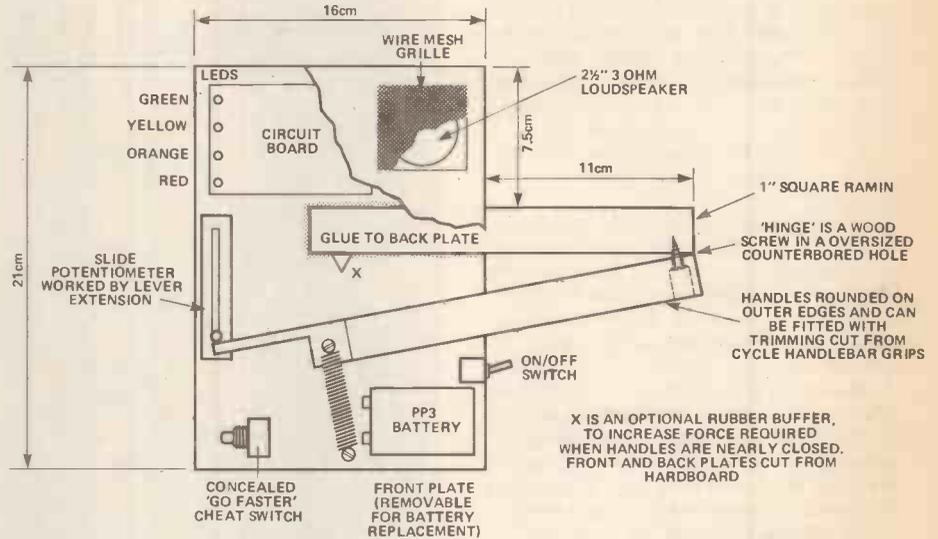



Figure 4. The mechanics of the Gripometer.

Consequently, the output of each and every op-amp is at 0V and none of the LEDs (light emitting diodes) LED1 - LED4 is lit.

As you squeeze the handles harder and the pitch of the sound rises, the voltage at the non-inverting input of op-amp IC2d will exceed that at the inverting input. Thus the output voltage of IC2d will rise to +9V, turning on LED1. As the pitch, and the voltage across C5, rises even higher, the output of IC2c will rise to +9V, extinguishing LED1 and lighting

up LED2. Then LED3 lights up and finally — if you are very strong — LED4 lights. Due to the deliberately arranged ripple on the voltage across C5, between one LED extinguishing and the next one lighting there is an intermediate state where both are alight. Thus although there are only four LEDs (red, orange, yellow and green) there are eight states: All Off, Red, Red+Orange, Orange, Orange+, Yellow, Yellow+Green and Green.

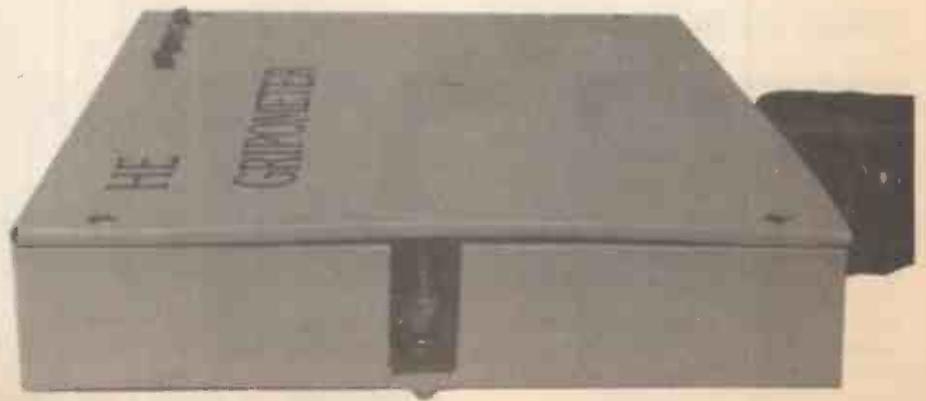Note that there is no feedback around the four op-amps — they are



Parts List

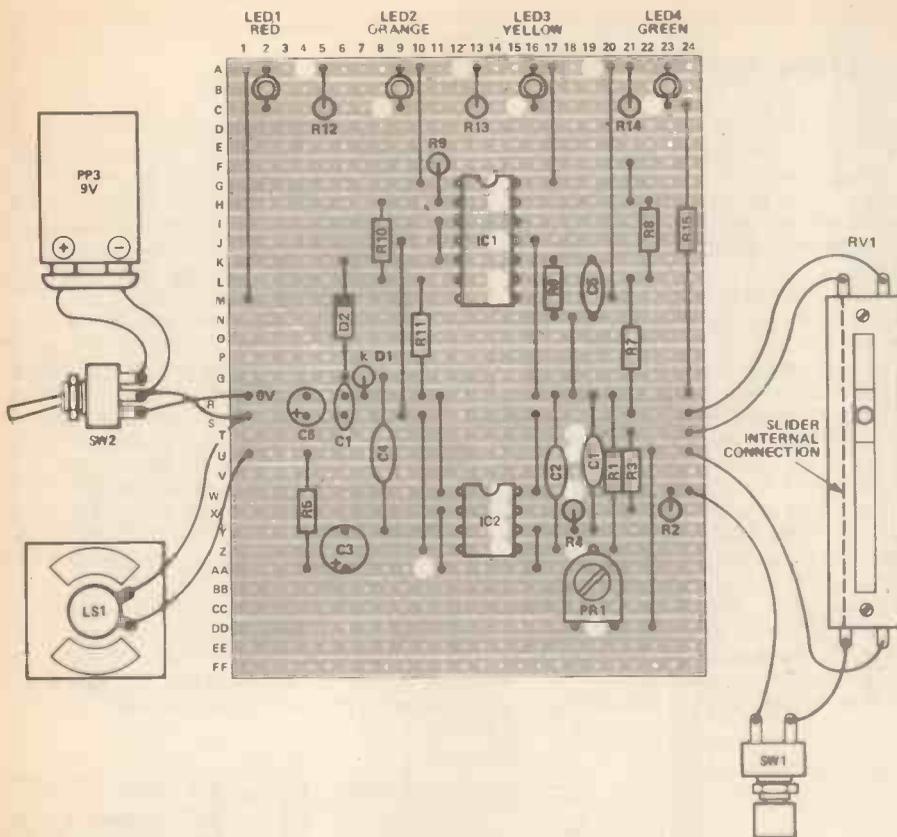


Figure 5. The Veroboard layout.

used "open loop", as simple comparators.

So that is basically how it works. The naughty bit is associated with SW1. The frequency of oscillation depends not only on the voltage at the slider of RV1, but also on the resistance between there and pin 7 of IC1. Closing SW1 connects R4 in parallel with R5, and results in a higher frequency of oscillation for any given setting of RV1. That is to say, the same frequency of oscillation will be achieved for a lower setting of RV1 which is equivalent to making your grip seem much more muscular than it really is!

Construction

No detailed dimensions are given as you will want to make your gripometer to suit your particular handgrip — you may even want to make the whole thing back to front if you are left handed! However, Figure 4 gives typical leading dimensions, and the construction method should be clear from this figure and the photograph. Note that for convenience a tension spring is used in place of the compression spring shown diagrammatically in Figure 1. You should be able to find a suitable spring at your local DIY or junk shop. By fitting it further from or close to the fulcrum (hinge point) you will make the handles harder or easier to squeeze respectively, and this provides a convenient method of adjusting the effort required. You

should aim to enable yourself to move the wiper of RV1 about $\frac{2}{3}$ of the way up. Then, when the whole unit is complete, if R4 is around 220 (you can experiment with different values here) you should be able to light the yellow LED, whereas with SW1 open the strongest man in the world won't be able to!

The electronics can be built up on a small piece of Veroboard as shown in Figure 5. This fits at the top of the unit so that the four LEDs are easily visible by the person trying his strength, as well as by bystanders. The loudspeaker (2.5in, 3R) fits next to the Veroboard, whilst the battery and on/off switch can be fitted at the bottom of the unit. The "cheat" switch SW1, which is of the "push for ON, push again for OFF" variety, was mounted so as to be readily accessible but not too obvious.

Setting Up

Before switching on for the first time, thoroughly check out the construction of the Veroboard circuitry and the wiring to other components — loudspeaker, RV1, SW1 and SW2. In particular, make sure that all the diodes, including the LEDs are connected the right way round. Next, disconnect RV1 from the spring lever and set it at the top of end (+9V) of its travel. Momentarily connect the 9V battery and you should hear a high pitched note from the loudspeaker. If you don't, disconnect the battery immediately and look for the fault.

RESISTORS

(All $\frac{1}{8}$ watt 5%)	
R1, 8, 9, 10	10k
R2	220k
	see text
R3, 6	150k
R4	33k
R5	82k
R7	100k
R11	39k
R12, 13, 14, 15	2k2

POTENTIOMETERS

RV1	10k
	65mm slide pot
PR1	10k
	horiz. preset

CAPACITORS

C1	6n8
	polyester
C2	10n
	polyester
C3	47u 16V
	radial electro
C4	18n
	polyester
C5	220n
	polyester min. layer
C6	10u 16V
	radial electro
C7	100n
	disc ceramic

SEMICONDUCTORS

IC1	555
IC2	LM324
	quad op-amp
D1, 2	1N4148
LED1	0.2" Red
LED2	0.2" Orange
LED3	0.2" Yellow
LED4	0.2" Green

MISCELLANEOUS

SW1	SPST
	push-on/push-off
SW2	SPDT
	toggle
LS1	2 $\frac{1}{2}$ " 3R
	Veroboard, 32 strips x 24 holes;
	Veropins; PP3 battery and clip;
	wire, solder, nuts and bolts, etc.

BUYLINES page 34

This could be a missing connection, but could just as easily be an unintentional extra one, where you have failed to cut completely one of the tracks of the Veroboard, say. It is worth examining each cut individually with a watchmaker's eyeglass, even more so if you have used a twist drill rather than a proper VERO track cutter.

When you have the sound responding to the movement of RV1, check that one or other of the LEDs lights. With RV1 reconnected to the spring lever, check that its rest position is near the PR1 end of its travel. Adjust PR1 so that there is no sound from the loudspeaker, but so that a low pitch is emitted as soon as the handles are squeezed. With a fresh PP3 battery and SW1 closed, you

Inside the 555

The figure below shows the internal architecture of the versatile 555 timer integrated circuit, a popular IC made by most manufacturers. It can be used in a number of ways, either as a monostable (a "one shot", which produces a single output pulse each time it is triggered) or as an astable (a free-running circuit which produces a repetitive pulse train). In this project we use it as an astable and do not need the facility for resetting the flip-flop, so we connect the RESET input, pin 4, to the positive supply at pin 8.


Whenever the voltage at pin 2 (TRIGGER) falls below $\frac{1}{3} V_{CC}$, the lower comparator sets the flip-flop, which turns off the DISCHARGE transistor at pin 7 and drives the output at pin 3 high. Whenever the voltage at pin 6 (THRESHOLD) rises above $\frac{2}{3} V_{CC}$, the upper comparator resets the flip-flop which turns on the discharge transistor and drives the output low. The absolute values of the

internal resistors RA, RB and RC which set the trigger and threshold voltages are not very accurate, but their ratios are precise. C2 is simply a decoupling capacitor. The operation of the stable connection shown is as follows.

The voltage at pins 2 and 6 will rise as C1 charges up through R1 and R2 in series, aiming at +Vcc. However, when it reaches $\frac{2}{3} V_{CC}$, the upper threshold is exceeded, the upper comparator will reset the flip-flop and the discharge transistor will turn on hard. This will effectively ground the junction of R1 and R2. The voltage at pins 2 and 6 will therefore start to fall as C1 discharges via R2, aiming at ground potential (zero volts). However, as soon as the voltage across C1 falls below $\frac{1}{3} V_{CC}$, the trigger voltage level, the comparator sets the flip-flop, turning the discharge transistor off again and the cycle repeats.

The voltage at pins 2 and 6 is

therefore a sawtooth waveform oscillating between $\frac{1}{3} V_{CC}$ and $\frac{2}{3} V_{CC}$ and back again, whilst the output at pin 4 sits alternatively "high" (nearly at Vcc) and "low" (near 0V ground). If R1 is increased, the frequency of oscillation will fall and vice versa, and similarly with R2. If instead of increasing R1, we return it to a voltage less than +Vcc, this will have the same effect. As we return it to a progressively lower voltage, less than $\frac{2}{3} V_{CC}$, the frequency will fall right down to zero, since the voltage across C1 can never operate the upper comparator, and the circuit stops oscillating altogether. Of course when the discharge transistor is ON, C1 is discharged via R2 regardless of R1, so the negative going half of the oscillation always takes the same length of time. Thus at low frequencies, the "square" wave driving the loudspeaker in Figure 3 becomes very asymmetrical.

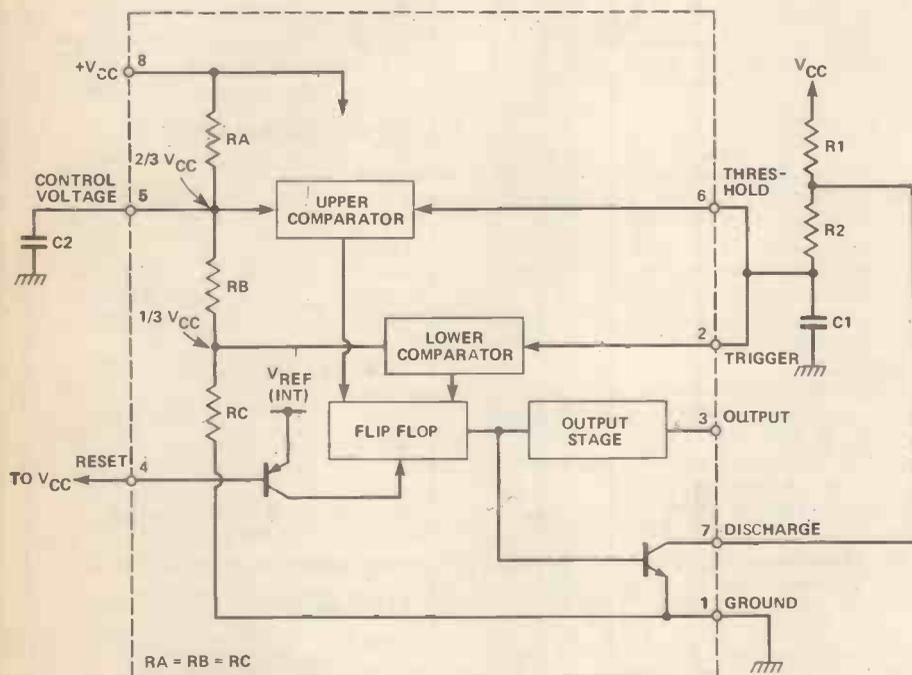

GROUND	1	8	+V _{CC}
TRIGGER	2	7	DISCHARGE
OUTPUT	3	6	THRESHOLD
RESET	4	5	CONTROL VOLTAGE

Figure 6. The diagram (left) and table (above) show the internal architecture of the 555 timer IC used in the Gripometer. This is described in detail in the box above.


should just be able to light LED4. If you can close the two handles completely, you should fit a stronger spring, but you should have sorted that out early in the constructional stage! With SW1 open it should not be possible to light LED4 even with the two handles completely closed. Note that a fresh battery should be used — as the battery voltage falls the audible output is largely unaffected, but it gets harder and harder to light the last two LEDs!

Having got it all working, you can fit the front panel and decorate it as you will. The Gripometer handles can be finished off using brightly coloured cycle handlebar grips, cut to fit round the outside edge of the handles. This not only provides a comfortable grip, it also adds a professional touch to the finish.


Naturally, when you hand it to your friends to try, SW1 will be open. Before demonstrating your own amazing strength, a little stagecraft — exaggerated adjustment to your grip and loud clearing of the throat — will provide the necessary cover for you to push SW1. And for your next trick . . . !



PCB FOIL PATTERNS

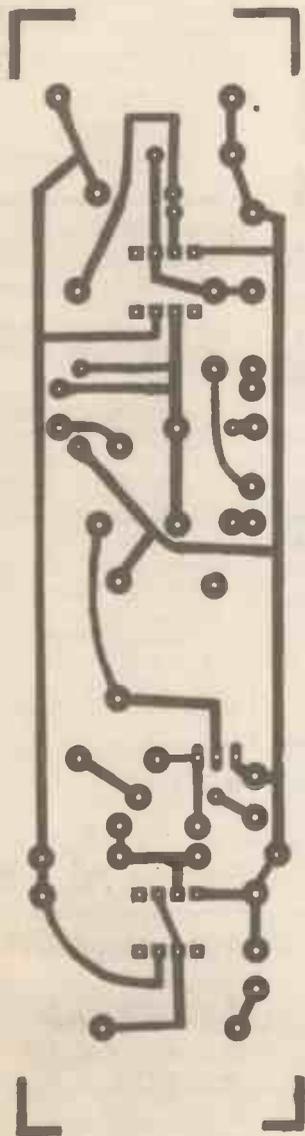

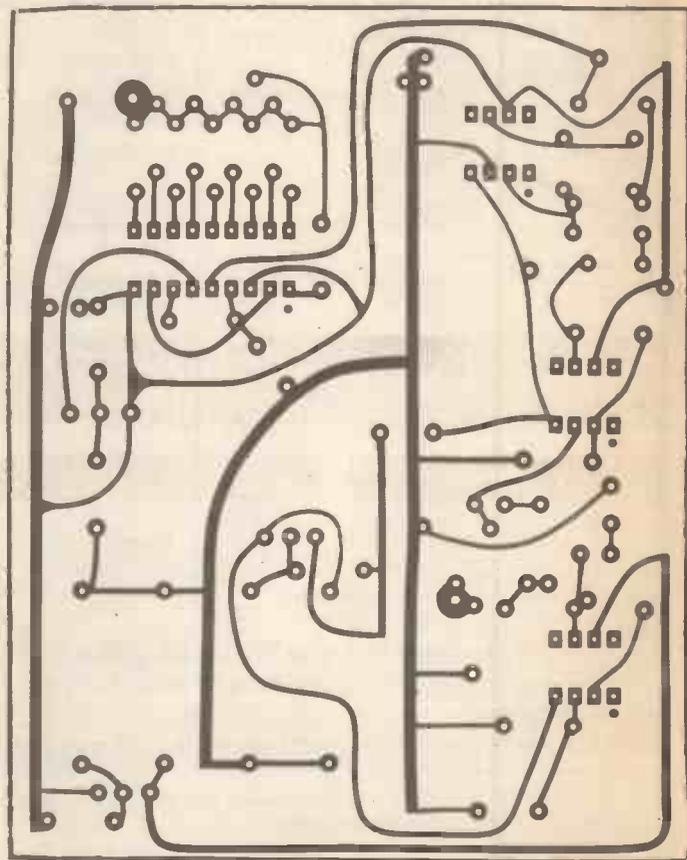Above: The PCB foil pattern for the Tremoleko project.



Above: The master pattern for the SPL Meter.

Lineage:

30p per word (minimum 15 words)
Semi-display £7.50 per single column centimetre
Ring for information on series bookings/discounts



01-437 1002
EXT 282

Send your requirements to:
Julie Bates,
ASP Ltd.,
145 Charing Cross Road,
London WC2H 0EF

All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)

BOOKS & PUBLICATIONS

PARAPHYSICS JOURNAL (Russian translations). Psychotronics, Kirlianography, heliphonic music tekinetics. Computer software. SAE 4 x 9"—Paralab, Downton Wilts.

SERVICES

JOHNSON INTRODUCES THE NEW

Tele-Recorder

Automatically record every telephone call



- Elegant, compact, unobtrusive
- Superior 2-way speech quality
- British Telecom approved
- Records up to 8 hours on a standard C120 tape

£95 (+ £2 p&p)

Johnson Electronics (Works), Star Warehouse, Camden Goods Depot, Chalk Farm Road, London NW1 0J-286 6119

ALARMS

BURLAR ALARM EQUIPMENT. Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. Ltd. 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274-308920.

COMPUTING

HAVEN HARDWARE

ZX81 £49.90. Inverse Video £4.50. Repeating Keymodule £5.95. ZX Spectrum software: Repulsor fruit machines and Solitair £4.95 each. Mancala and Patience £5.95 each. Jupiter Ace £89.90. Inverse Video £4.95.

Access taken, SAE for details.

HAVEN HARDWARE
4 Asby Road, Asby, Workington, Cumbria Tel: 094-686 627
Agency enquiries welcome

32% of our readers own a computer — reach them with

ASP Classified
01-437 1002

SOFTWARE APPLICATIONS

SPY CASSETTE. Spectrum/ZX81 lets you stop and copy any previously unstoppable tape. Simply press C for instant copy. If a Spectrum £3.95, ZX81 version £2.50. Bobker, 29 Chadlerton Drive, Bury, Lancs.

EQUIPMENT

AERIAL AMPLIFIERS improve weak television reception. Price £6.70. S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire BL0 9AGH.

FOR SALE

POWERAMPLIFIERS 200 watt £11.95! — case and controls, volume, balance and sockets. 4 x MJ3001 outputs, 100 & 100 watts!! (R.R.P. & Data = £38.40). KIA 8, Cunliffe Road, Ilkley.

Whatever you're selling, refer to
HOBBY CLASSIFIED

There are over 35,000 potential customers looking at this page, shouldn't you be reaching them?

For the best —
HOBBY CLASSIFIED

COMPONENTS

WAVEBANDS

Auto Electronics,
103 Coventry Street,
Kidderminster
Tel: (0562) 2179

Brand new components by return post or ring with Access/Barclaycard number for same day despatch.

All manufacturers guaranteed new stock. All at most competitive prices. Catalogue available only 50p. All prices inclusive of VAT.

HOBBY SHOP

DAVENTRY

EMOS HIGH MARCH
DAVENTRY NN11 4HQ
Tel: (03272) 5523

- ★ Open Mon-Sat 9am-4pm
- ★ Both retailers and wholesalers
- ★ Vast stocks of components
- ★ Large 'walk-round' electronics supermarket

IRELAND

IRELAND
Call A & A ELECTRONICS
for wide range of kits
17 Cuala Road
Bray
Co. Wicklow
Tel. 01-862422

TODMORDEN

PROFESSIONAL OR HOBBYIST?

Come and have a look at the EMPORIUM Bargains galore — catalogue available Electronic, Electrical and Mechanical Nuts & Bolts, Resistors, Capacitors, Meters, Semiconductors and much more.

A. C. TOWNLEY LTD
Harehill Mill
Harehill St (off Burnley Rd), Todmorden
Open 8.30-5.30 Sats till 1pm
(lunch 1-2pm)

Should you wish to promote your business in this section ring Julie on
01-437 1002
extn. 282

W YORKSHIRE



ACE MAILTRONIX LIMITED
3A Commercial Street
Batley, West Yorkshire
Tel. 0924 441129
Open: 9-5.30pm Weekdays
9.30-1pm Saturdays
Retailers and wholesalers

TRANSISTORS

SPECIAL OFFER of unmarked transistors (each type of transistor supplied in separate, marked bag). BC338, BC237B, BC239B, BC115, BC173B, BC182B, BC238B. Only 50p for 10 (excluding VAT). Add 25p p&p. Access/Barclaycard accepted. Van Gelder Ltd, P.O. Box 10, Southend-on-Sea, SS2 6Q6.

STEREOAMPS 120 watt (60 + 60)...Case — D.I.N sockets and controls...9-40 v/smoothing... protected outputs 3/15 ... tested & diagrams £10/inc ... KIA-8 Cunliffe Road, Ilkley.

PB2720 SOUNDERS 3 for £1. 5mm leds with clips, red or green, 10 for £1. Push to make switches 10 for £1 P.C.B. containing NE555 and 4011B 25p each 100 uf or 10uf caps 10 for £1. Post/packing 40p. Micro-Tech Industries, 1 Phoenix Street, Brighouse, W. Yorks HD6 1PD.

PLANS 'N DESIGN

CONVERT ANY TV into large screen oscilloscope. External unit plugs into aerial socket of TV. Circuit & plans £3 or SAE details. J. Bobker, 29 Chadder-ton Drive, Unsworth, Bury, Lancs.

AMAZING electronic plans, lasers, gas, ruby, light shows, high voltage teslas, van de graph, surveillance devices, ultrasonics, pyrotechnics, new solar generator, 150 more projects, catalogue S.A.E., Plan-centre, Bromyard Road Industrial Estate, Ledbury HR8

IN STOCK New telephone plugs and sockets also ZX81 plugs and spectrum plugs and wide range of burglar alarm equipment and all accessories for same plus large range of components. Shudehill Supply Co. Ltd., 53 Shudehill, Manchester 4. 061-834 1449.

KITS

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

DIGITAL WATCH replacement parts, batteries, displays, backlights, etc. Also reports publications charts. S.A.E. for full list: Profords Copners Drive, Holmer Green, Bucks HP15 6SGE.

HOBBY ELECTRONICS

CLASSIFIED ADVERTISEMENT — ORDER FORM

If you have something to sell now's your chance! Don't turn the page — turn to us!
Rates of charge: 30p per word per issue (minimum of 15 words).

and post to **HOBBY ELECTRONICS, CLASSIFIED DEPT., 145 CHARING CROSS ROAD, LONDON WC2**

Please place my advert in **HOBBY ELECTRONICS** for . . . issues commencing as soon as possible.

I am enclosing my Cheque/Postal Order/International Money Order for: (delete as necessary) £ (Made payable to A.S.P. Ltd)

Please use **BLOCK CAPITALS** and include post codes.



OR Debit my Access/Barclaycard
(Delete as necessary)



Classification

Name (Mr/Mrs/Miss/Ms)
(delete accordingly)

Address
.....

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

All classified advertisements must be paid for in advance.

Signature **Date**

Daytime Tel. No.



RECRUITING? SELLING A PRODUCT? OR A SERVICE?

**GET MAXIMUM BENEFIT FOR
YOUR MONEY**

**FIND OUT ABOUT OUR WHOLE
RANGE OF PUBLICATIONS IN:**

COMPUTING

VIDEO

RADIO

ELECTRONICS

Simply telephone

ASP CLASSIFIED

01-437 1002

(We take Access and Barclaycard)

HOBBY ELECTRONICS ADVERTISERS INDEX SEPTEMBER 1983


A.D. Electronics	44
Ambit International	IFC
Audio Electronics	31
Bicc Vero	57
B.K. Electronics	IBC
B.N.R.S.	18
J. Bull	19
Camtec	56
Concept Electronics	53
Dataplus Development	21
Dicom Electronics	57
Durrant Radio	56
Electroni-Kit	18
Electronize Design	5
Elen Electronics	44
Hawk Electronics	21
Hazzlewood Electronics	44
Hemmings Electronics	34
Horizon Elecontrics	44
ICS	57
ILP	12, 13
Kelan Engineering	31
Litesoldering Developments	35
Magenta Electronics	24
Pantec	35
Parndon Electronics	44
Racom	56
Rapid	4
Brian J. Reed	35
Sandwell Plant	18
Silica Shop	OBC
Sparkrite	47
S&R Brewster	18
Technomatic	46
T K Electronics	21
Twyford Electronics	53
W.E.B. Logic Systems Test Ltd	56



MULLARD SPEAKER KITS

Purposefully designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer (8" or 5") with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter. B.K.E. built and tested crossover based on Mullard circuit, combining low loss components, glass fibre board and recessed loudspeaker terminals. SUPERB SOUNDS AT LOW COST. Kits supplied in polystyrene packs complete with instructions. 8" 40W system — recommended cabinet size 240 x 216 x 445mm
Price £14.90 each + £2.00 P & P.
5" 30W system — recommended cabinet size 160 x 175 x 295mm
Price £13.90 each + £1.50 P & P.

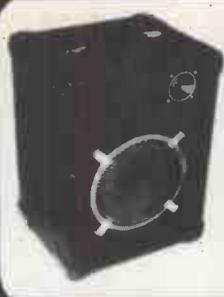Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self adhesive vinyl etc. 8" system cabinet kit £8.00 each + £2.50 P & P. 5" system cabinet kit £7.00 each + £2.00 P & P.




OMP 80 LOUDSPEAKER

The very best in quality and value. Ported tuned cabinet in hard-wearing black vinylite with protective corners and carry handle. Built and tested, employing 10in British driver and Piezo tweeter. Spec: 80 watts RMS; 8 ohms; 45Hz-20KHz; Size: 20in x 15in x 12in; Weight: 30 pounds.

Price: £49.00 each
£90 per pair
Carriage: £5 each £7 per pair

BK ELECTRONICS

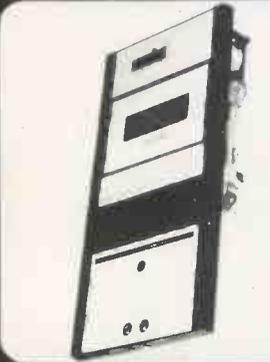Prompt Deliveries
VAT inclusive prices
Audio Equipment
Test Equipment
by
Thandar
and
Leader



STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.
Features: Three digit tape counter. Autostop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Inout Sensitivity: 100mV to 2V. Input Impedance: 68K. Output level: 400mV to both left and right hand channels. Output Impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V DC at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2" x 11 1/2". Clearance required under top panel 2 1/2". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.
Price £26.70 + £2.50 postage and packing.
Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50

PANTEC

HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 5 x 46 x 14mm (9 volt) Price: £7.99p
DIGITAL THERMOMETER -9.9°C to +99.9°C. LED display. Complete with sensor. 70 x 70 mm (9 volt) Price: £27.60p
3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled, professional performance. Range up to 3 miles 35 x 84 x 12 mm (12 volt) Price: £12.49p
SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22 mm 9/12 volt) Price: £16.49 Transmitter 80 x 50 x 15 mm (9/12 volt) Price £10.29 P&P All Kits +50p. S.A.E. for complete list.



3 watt FM Transmitter


LOUDSPEAKERS

THREE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8" See 'Photo'). Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons. Specification and Prices.
15" 100 watt R.M.S. Impedance 8 ohms 50 oz magnet 2" aluminium voice coil. Res. Freq. 20 Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. Price: £34.00 each + £3.00 P&P
12" 100 watt R.M.S. Impedance 8 ohms. 50 oz magnet 2" aluminium voice coil. Res. Freq. 25Hz. Freq. Resp. to 4 KHz. Sens. 95dB. Price: £24.50 each + £3.00 P&P
8" 50 watt R.M.S. Impedance 8 ohms. 20 oz magnet 1 1/2" aluminium voice coil. Res. Freq. 40Hz. Freq. Resp. to 6 KHz. Sens. 92dB. Black Cone. Price: £9.50 each. Also available with black protective grille. Price: £9.99 each. P&P £1.50.
12" 85 watt R.M.S. MCKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 98dB. Price: £22.00 + £3 carriage.
12" 85 watt R.M.S. MCKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz. Price £22 + £3 carriage.
15" 150 watt R.M.S. MCKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price: £47 + £4 carriage.




BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm ● Belt driven ● Aluminium platter ● Precision calibrated counter balance ● Anti-skate (bias device) ● Damped cueing lever ● 240 volt AC operation (Hz) ● Cut-out template supplied ● Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.
Price £31.35 each. £2.50 P&P

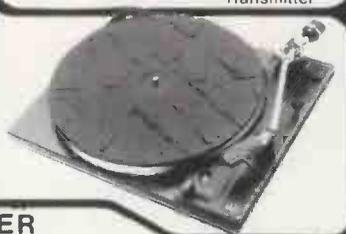

OMP POWER AMPLIFIER MODULE

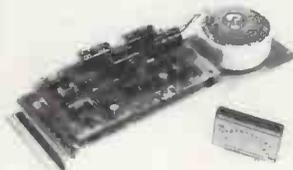


NEW OMP100 Mk.II POWER AMPLIFIER MODULE Power Amplifier Module complete with integral heat sink, toroidal transformer power supply and glass fibre p.c.b. assembly. Incorporates drive circuit to power a compatible LED Vu meter. New improved specification makes this amplifier ideal for P.A., Instrumental and Hi-Fi applications.
SPECIFICATION
Output Power:— 110 watts R.M.S.
Loads:— Open and short circuit proof 4/16 ohms.
Frequency Response:— 15Hz - 30KHz -3dB. T.H.D.:— 0.01%.
S.N.R. (Unweighted):— -118dB ±3.5dB
Sensitivity for Max Output:— 500mV @ 10K. Size:— 360 x 115 x 72 mm Price:— £31.99 + £2.00 P&P. Vu Meter Price:— £7.00 + 50p P&P.
OEM'S CONTACT BARRY PEARNE Tel. 0702 52752

New model.
Improved specification

PIEZO ELECTRIC TWEETERS - MOTOROLA

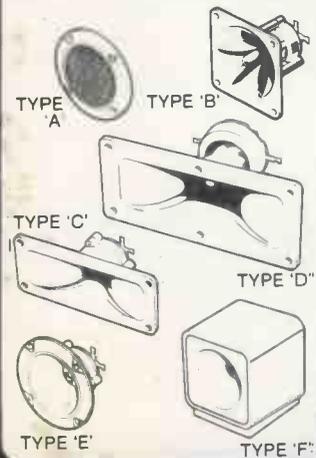
Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.29 each.
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each.
TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £5.99 each.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £7.99 each.
TYPE 'E' (KSN1038A) 2" x 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £4.99 each.
TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each
P&P 20p ea. (or SAE for Piezo leaflets).


HOME PROTECTION SYSTEM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. FULLY GUARANTEED.
Control Unit — Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch — off — test — armed. 30 second exit and entry delay.
Indoor alarm — Electronic swept freq. siren. 104dB output.
Outdoor Alarm — Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.
Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions

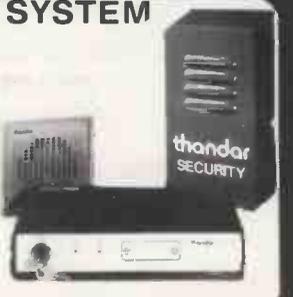

SAVE £128 Usual price £228.85
BKE's PRICE £99.p&p£4
SAE for colour brochure

SAFGAN DT-520 DUAL TRACE OSCILLOSCOPE. New British model. 12 month guarantee. 20 MHz Band Width. Specification: ★ CH1, CH2: 5mV/div-20V/div. ★ Time Base: 1 Sec/div-100ns/div. ★ XY Facility. Matched XY inputs. ★ Trigger: Level control ± slope selection. ★ Auto, normal, TV Triggering. ★ Z-Modulation. ★ CAL output 1V 1KHz. ★ Sweep output 0-9V. ★ Graticule blue ruled 10 x 8 cm. (5" C.R.T.) Very sharp trace. ★ Size: H235mm, W177mm, D360mm. ★ Weight: 6.5 Kgs. ★ Supply: 200-240 V. 40-60Hz. ★ Price: £241.50 — FREE Securocorder Delivery. Probes: X1 £8.05, X1/X10 Switched £10.93.

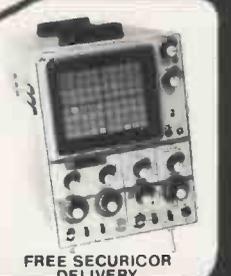

FREE SECURICOR DELIVERY

B.K.E. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR



★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★ All items packed where applicable in special energy absorbing PU foam. ★ Please phone 0702 527572 ★

100 FREE PROGRAMS

FROM SILICA SHOP — WITH EVERY PURCHASE OF AN

ATARI 400

800




ATARI PRICES REDUCED!

We at Silica Shop are pleased to announce some fantastic reductions in the prices of the Atari 400/800 personal computers. We believe that the Atari at its new price will become the U.K.'s most popular personal computer and have therefore set up the Silica Atari Users Club. This club already has a library of over 500 programs and with your purchase of a 400 or 800 computer we will give you the first 100 free of charge. There are also over 350 professionally written games and utility programs, some are listed below. Complete the reply coupon and we'll send you full details. Alternatively give us a ring on 01-301 1111 or 01-309 1111.

ATARI 400 with 16K **£149**

ATARI 400 with 48K **£198**

ATARI 800 with 48K **£299**

400/800 SOFTWARE & PERIPHERALS

Don't buy a T.V. game! Buy an Atari 400 personal computer and a game cartridge and that's all you'll need. Later on you can buy the Basic Programming cartridge (£35) and try your hand at programming using the easy to learn BASIC language. Or if you are interested in business applications, you can buy the Atari 800 + Disk Drive + Printer together with a selection of business packages.

Silica Shop have put together a full catalogue and price list giving details of all the peripherals as well as the extensive range of software that is now available for the Atari 400/800. The Atari is now one of the best supported personal computers. Send NOW for Silica Shop's catalogue and price list as well as details on our users club.


THE FOLLOWING IS JUST A SMALL SELECTION FROM THE RANGE OF ITEMS AVAILABLE:

ACCESSORIES Cables Cassettes Diskettes Joysticks Le Stick - Joystick Misc Supplies Paddles	Mountain Shoot Rearguard Star Flite Sunday Golf	AUTOMATED SIMULATIONS Crash Crumble Cmp Datesones of Ryn Dragons Eye Invasion Orion Rescue at Rigel Ricochet Star Warrior Temple of Apsah Upper Reaches Aps	BOOKS Basic Ref Manual Compute Atari DOS Compute Bk Atari Compute Magazine Die Re Atari DOS Utilities List DOS2 Manual Misc Atari Books Op System Listing Wiley Manual	CRISTALWARE Beneath The Pyram Galactic Quest House Of Usher Sands Of Mars Waterloo World War III	BUSINESS Calculator Database Management Decision Maker Graph-It Invoicing Librarian Mort & Loan Anal Nominal Ledger Payroll Personal Finl Mgmt Purchase Ledger Sales Ledger Statistics 1 Stock Control Telelink 1 Visicalc Weekly Planner Word Processor	DYNACOMP Alpha Fighter Chompelo Crystals Forest Fire Intruder Alert Monarch Moonprobe Moving Maze Nominoes Jigsaw Rings of The Emp Space Tilt Space Trap Stud Poker Triple Kickade	EDUCATION from APX Algebraic Atlas of Canada Cubbyholes Elementary Biology Frogmaster Hickory Dickory Inst Comptg Dem Lemonade Letterman Mapware	Maths-Tac-Toe Metric & Prob Solvg Mugyump Musical Computer My First Alphabet Number Blast Polycalc Presidents Of U.S. Quiz Master Starware Stereo 3D Graphics Three R Math Sys Video Math Flash Wordmaker	EDUCATION from ATARI Conv French Conv German Conv Italian Conv Spanish Energy Gear European C & Caps Hangman Invit To Prog 1/2/3 Kingdom Music Composer	Scram States & Capitals Touch Typing	EMUL SOFTWARE British Heritage Cribbage/Dominoes Darts European Scene Jig Hickory Dickory Humpty Dumpty Jumbo Jet Lander Snooker & Billiards Submarine Comdr Super Cubes & Tilt Tournament Pool	ENTERTAINMENT from APX Alien Egg Anthill Atlantk Avalanche Babel Blackjack Casino Block Buster Block 'Em Bumper Pool	Castle Centurion Checker King Chinese Puzzle Codecracker Comedy Diskette Dice Poker Dog Daze Dominion Downhill Eastern Front Galahad & Holy Grl Graphics/Sound Jax-O Jukebox Lookahead Memory Match Midas Touch Minotaur Outlaw/Howitzzer Preschool Games Pro Bowling Pushover Rabbitz Reversi II Salmon Run 747 Landing Simul Seven Card Stud	Sleazy Adventure Solitaire Space Chase Space Trek Sultans Palace Tact Trek Terry Wizards Gold Wizards Revenge	ENTERTAINMENT from ATARI Asteroids Basketball Blackjack Centipede Chess Entertainment Kit Missile Command Pac Man Space Invaders Star Raiders Super Breakout Video Easel	ON LINE SYSTEMS Crossfire Frogger	Jawbreaker Mission Asteroid Mouskattack Threshold Ulysses/Golden Fl Wizard & Princess	PERIPHERALS Centronics Printers Disk Drive Epson Printers Program Recorder RS232 Interface Thermal Printer 16K Memory RAM 32K Memory RAM	PERSONAL INT from APX Adv Music System Banner Generator Blackjack Tutor Going To The Dogs Keyboard Organ Morse Code Tutor Personal Fitness Prg Player Piano Sketchpad	PROGRAMMING AIDS from Atari Assembler Editor Dsembler (APX) Microsoft Basic Pascal (APX) Pilot (Consumer) Pilot (Educator) Programming Kit	SANTA CRUZ Basics of Animation Bobs Business Display Lists Graphics Machine Kids 1 & 2 Horizontal Scrolling Master Memory Map Mini Word Processor Page Flipping Player Missile Gr Player Piano Sounds Vertical Scrolling	SILICA CLUB Over 500 programs write for details
--	--	---	---	---	---	---	--	--	---	--	---	---	---	---	--	--	--	---	--	---	--	--

FOR FREE BROCHURES - TEL: 01-301 1111

- For free brochure and reviews on our range of electronic products please telephone 01-301 1111.
- To order by telephone just quote your name, address, credit card number, and order requirements and leave the rest to us. Post and packaging FREE OF CHARGE in the U.K. Express 24 hour delivery available at an additional charge.
- SHOP DEMONSTRATION FACILITIES - we provide full facilities at our shop in Sidcup, Monday to Saturday 10am to 5.30pm (closing Thursday 1pm - Friday 8pm).
- MAIL ORDER - we are a specialist mail order company and are able to supply goods direct to your door.
- MONEY BACK GUARANTEE - if you are not totally satisfied with your purchase, you may return it to us within 14 days. On receipt of the goods in satisfactory condition we will give you a full refund.
- PART EXCHANGE SECOND HAND MACHINES - we offer a part exchange scheme to trade in many makes of 16K games for personal computers.
- COMPETITIVE PRICES - our prices offers and service are very competitive. We are never knowingly undercut and will normally match any lower price quoted by our competitors.
- HELPFUL ADVICE - available on the suitability of various computers.
- AFTER SALES SERVICE - available on all computers out of guarantee.
- VAT - all prices quoted above include VAT at 10%.
- CREDIT FACILITIES - we offer credit over 12, 24 or 36 months please ask for details.

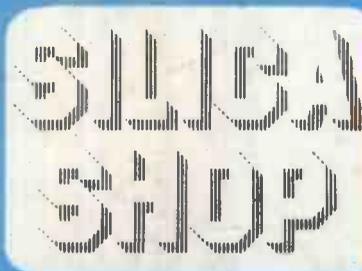SILICA SHOP LIMITED
Dept. HE 9 83, 1-4 The Mews, Hatherley Road, Sidcup,
Kent DA14 4DX Telephone 01-301 1111 or 01-309 1111



FREE LITERATURE

I am interested in purchasing an Atari 400/800 computer and would like to receive copies of your brochure and latest reports as well as your price list covering all of the available Hardware and Software.

Name

Address

Postcode

HE 09 83