

Hobby

Electronics

Project Electronics For Everyone

85p

AUDIO LEVEL METER PROJECT TO BUILD



ULTRASONIC INTRUDER ALARM


Sensitive Doppler
shift design
detects movement

**SPECIAL
EIGHT PAGE
CIRCUIT
SUPPLEMENT
—OVER 20
CIRCUITS**

HIGH VOLTAGE METER PROJECT
—measures up to 10,000 volts

New cats for old !

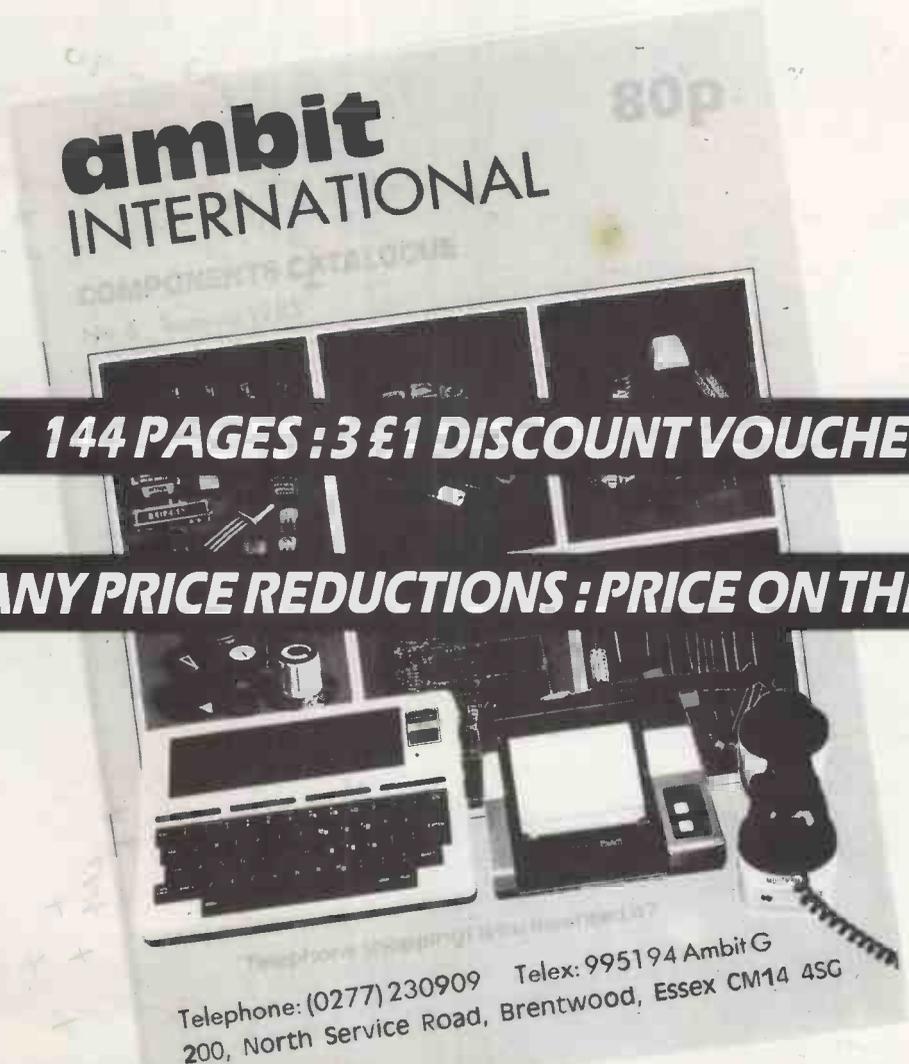SEND US THE COVER FROM ANOTHER COMPONENT SUPPLIERS CURRENT CATALOGUE, PLUS A 40p STAMP, AND WE'LL SEND YOU A FREE COPY OF THE LATEST (SUMMER) AMBIT CONCISE COMPONENT CATALOGUE. ALTERNATIVELY YOU CAN SIMPLY BUY A COPY FROM YOUR NEWSAGENT — OR SEND 80p TO THE ADDRESS BELOW.....



ambit
INTERNATIONAL
COMPONENTS CATALOGUE

80p

★ 144 PAGES : 3 £1 DISCOUNT VOUCHERS

★ MANY PRICE REDUCTIONS : PRICE ON THE PAGE

Telephone: (0277) 230909 Telex: 995194 Ambit G
200, North Service Road, Brentwood, Essex CM14 4SG

★ AVAILABLE AT NEWSAGENTS, OR DIRECT FROM

ambit INTERNATIONAL

200 North Service Road
Brentwood
Essex
CM14 4SG

Telephone 0277-230909
Telex 995194 AMBIT G
Data 0277-232628 REWTEL))
300 BAUD DUPLEX

Hobby Electronics

OCTOBER 1983
VOL 5 No 10

PROJECTS

- ★AUDIO LEVEL METER 11
An accurate, 10-LED bargraph level meter.
- HI-VOLTAGE METER 28
Protect your equipment, protect yourself.
- ★TRUMP CARD 58
Connects the Jupiter ACE to ZX add-ons.
- ★ULTRASONIC INTRUDER ALARM 63
Don't make a move...

FEATURES

- THE FX-COMPUTER 16
HE reviews a teach-yourself electronics kit.
- CAREERS IN ELECTRONICS PART 6 20
Customer Service engineering in computers.
- ALL ABOUT ELECTRONICS PART 4 48
Starting on semiconductors.
- ★MODEL RAIL COMPETITION 54
Design a computer-controlled railway layout.


SPECIAL

- ★GIANT CIRCUIT SUPPLEMENT 34
Eight pages of all-purpose circuits.


REGULARS

- Monitor 6
- What's On Next 18
- Breadboard 24
- Forward Bias 26
- Buylines 32
- HE Bookshelf 43
- Points Of View 44
- PCB Service 69
- PCB Printout 70
- Classified Advertisements 73

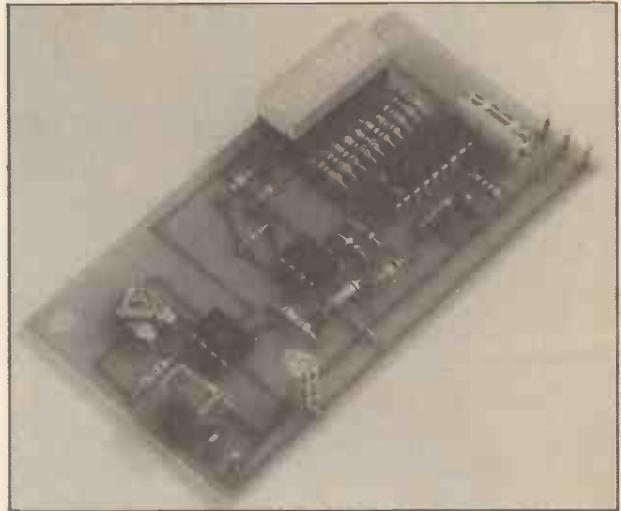Editor: Ron Keeley
 Assistant Editor: Helen Armstrong BA
 Technical Illustrator: Jerry Fowler
 Advertisement Manager: David Kitchener
 Assistant Advertisement Manager: Joanne James
 Managing Editor: Ron Harris BSc
 Chief Executive: T. J. Connell



Audio Level Meter - page 11

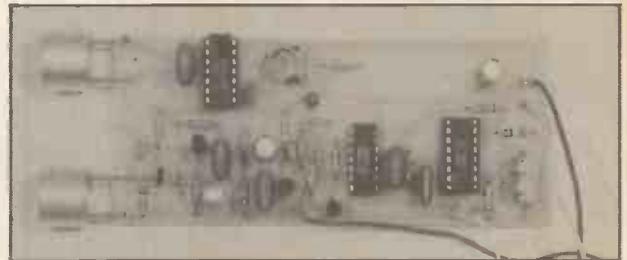

Ultrasonic Intruder Alarm — page 63



FX-Computer Review — page 16


Hobby Electronics is normally published on the second Friday of the month prior to the cover date.
 Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002. Telex No 8811896. Published by Argus Specialist Publications Ltd.
 Origination by Ebony Typesetting, Trion House, 13 Dean Street, Liskeard, Cornwall PL14 4AB.
 Distributed by S. M. Distribution Ltd, 16/18 Trinity Gardens, London SW9 8DX.
 Printed by QB Ltd, Colchester. Covers printed by Alabaster Passmore.

Notice: The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. All reasonable care is taken in the preparation of the magazine to ensure accuracy, but Argus Specialist Publications Ltd cannot be held responsible legally. ©Copyright 1983 Argus Specialist Publications Ltd. Member of Audit Bureau of Circulation.

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.


Sparkrite

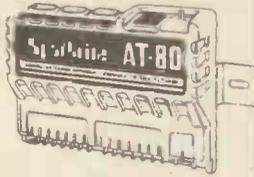BRANDLEADING ELECTRONICS
NOW AVAILABLE IN KIT FORM




AT-80 Electronic Car Security System

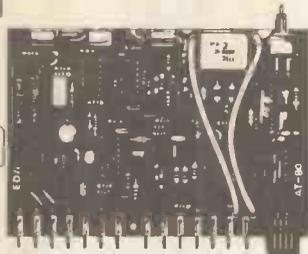- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble



VOYAGER Car Drive Computer

- A most sophisticated accessory
- Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd.
- Affords 12 functions centred on Fuel, Speed, Distance and Time
- Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on
- Facility to operate LOG and TRIP functions independently or synchronously
- Large 10mm high 400ft-L fluorescent display with auto intensity
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%
- Large LOG & TRIP memories 2,000 miles 180 gallons 100 hours
- Full Imperial and Metric calibrations
- Over 300 components to assemble
- A real challenge for the electronics enthusiast!

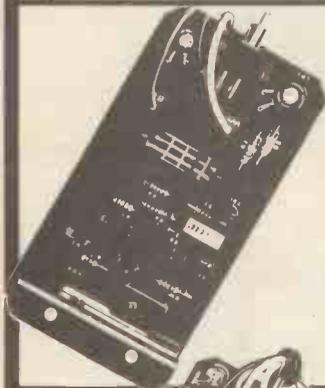


SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




TX1002 Electronic Ignition

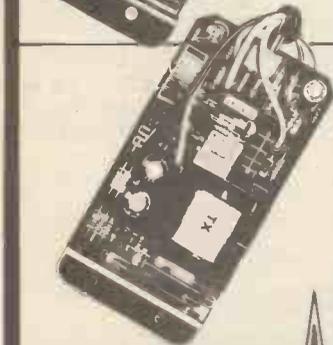- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge
- Three position changeover switch
- Distributor triggerhead adaptors included
- Die cast weatherproof case
- Clip-to-coil or remote mounting facility
- Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles
- Over 145 components to assemble.



SX2000 Electronic Ignition

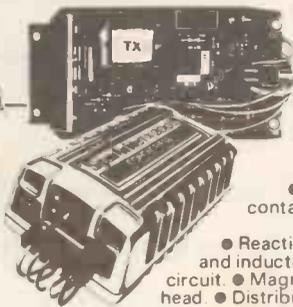- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles



TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit
- Reactive Discharge. Combined capacitive and inductive
- Extended coil energy storage circuit
- Magnetic contactless distributor triggerhead
- Distributor triggerhead adaptors included
- Can also be triggered by existing contact breakers
- Die cast waterproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg. earth vehicles
- Over 150 components to assemble

All SPARKRITE products and designs are fully covered by one or more World Patents.



SPECIAL OFFER
"FREE" MAGIDICE KIT WITH
ALL ORDERS OVER £45.00



MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in-5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

SPARKRITE 82 Bath Street, Walsall, West Midlands, WS1 3DE England.

Tel (0922) 614791 Allow 28 days for delivery

| | SELF ASSEMBLY KIT |
|----------|-------------------|
| SX 1000 | £12.95 |
| SX 2000 | £19.95 |
| TX 1002 | £22.95 |
| TX 2002 | £32.95 |
| AT 80 | £32.95 |
| VOYAGER | £64.95 |
| MAGIDICE | £9.95 |

PRICES INC VAT POSTAGE & PACKING

NAME _____ HE 10

ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF _____

CHEQUE NO _____



BRANDLEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!

| | | | | | | | | | | | |
|------------------|-----------|------------|-------------|-----------|---------------|--------------|--------------|--------------|-------------|-------------|---------------------------|
| 74 SERIES | 74125 30p | 74LS06 12p | 74LS221 50p | 4034 45p | ADC0808 990p | LM1014 150p | TL430C 70p | BSX19/20 20p | 2N1613 30p | OA202 10p | Rectangular LEDs (R.G.V.) |
| 7400 14p | 74126 30p | 74LS08 12p | 74LS240 60p | 4035 45p | AY1-5050 99p | LM1801 300p | UA2240 120p | BU104 225p | 2N1711 25p | N914 4p | |
| 7401 14p | 74127 30p | 74LS09 14p | 74LS241 55p | 4036 275p | AY1-270 825p | LM1886 65p | UA2170 110p | BU105 170p | 2N2102 70p | N915 7p | NS85881 570p |
| 7402 14p | 74128 30p | 74LS10 14p | 74LS242 55p | 4037 110p | AY3-1350 350p | LM1889 350p | ULN2003 75p | BU108 250p | 2N2107 25p | N1418 4p | TL1311 600p |
| 7403 14p | 74129 30p | 74LS11 14p | 74LS243 55p | 4038 290p | AY3-8910 500p | LM2917 200p | ULN2004 75p | BU109 225p | 2N219A 25p | N1418 4p | TL1312/3 110p |
| 7404 14p | 74130 30p | 74LS12 14p | 74LS244 80p | 4040 40p | AY3-8912 500p | LM3302 75p | ULN2008 290p | BU126 160p | 2N2222A 25p | N14003/4 5p | TL1321/2 130p |
| 7405 15p | 74131 30p | 74LS13 14p | 74LS245 80p | 4041 40p | CA3019 80p | LM3900 50p | ULN2802 200p | BU180A 120p | 2N2369A 17p | N14005 6p | TL1330 140p |
| 7406 15p | 74132 30p | 74LS14 25p | 74LS246 80p | 4042 40p | CA3028 120p | LM3903 85p | UPC575 275p | BU206 175p | 2N2484 25p | N14006/7 7p | TL750/60 200p |
| 7407 22p | 74133 30p | 74LS15 14p | 74LS247 80p | 4043 40p | CA3048 220p | LM3914 85p | UPC528H 275p | BU206 175p | 2N2648 40p | N14033 14p | DISPLAYS |
| 7408 14p | 74134 30p | 74LS16 14p | 74LS248 80p | 4044 40p | CA3048 220p | LM3914 85p | UPC156H 275p | BU206 175p | 2N2648 40p | N14033 14p | 31015F 200p |
| 7409 14p | 74135 30p | 74LS17 14p | 74LS249 80p | 4045 40p | CA3059 285p | LM3915 225p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | DL704 140p |
| 7410 14p | 74136 30p | 74LS18 14p | 74LS250 80p | 4046 40p | CA3060E 350p | LM3916 225p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | DL707 Red 140p |
| 7411 16p | 74137 30p | 74LS19 14p | 74LS251 80p | 4047 16p | CA3086 48p | LM3916 225p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | FND357 120p |
| 7412 14p | 74138 30p | 74LS20 14p | 74LS252 80p | 4048 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | FND507 90p |
| 7413 14p | 74139 30p | 74LS21 14p | 74LS253 80p | 4049 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | FND507 90p |
| 7414 20p | 74140 30p | 74LS22 14p | 74LS254 80p | 4050 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | MAN3640 175p |
| 7415 20p | 74141 30p | 74LS23 14p | 74LS255 80p | 4051 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | MAN4640 200p |
| 7416 20p | 74142 30p | 74LS24 14p | 74LS256 80p | 4052 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | DRIVERS |
| 7417 20p | 74143 30p | 74LS25 14p | 74LS257 80p | 4053 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 9368 250p |
| 7418 20p | 74144 30p | 74LS26 14p | 74LS258 80p | 4054 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 9370 300p |
| 7419 20p | 74145 30p | 74LS27 14p | 74LS259 80p | 4055 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | UDN6118 320p |
| 7420 18p | 74146 30p | 74LS28 14p | 74LS260 80p | 4056 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | UDN6118 320p |
| 7421 18p | 74147 30p | 74LS29 14p | 74LS261 80p | 4057 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | LOW PROFILE SOCKETS BY TI |
| 7422 20p | 74148 30p | 74LS30 14p | 74LS262 80p | 4058 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 8 pin 9p |
| 7423 18p | 74149 30p | 74LS31 14p | 74LS263 80p | 4059 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 14 pin 10p |
| 7424 18p | 74150 30p | 74LS32 14p | 74LS264 80p | 4060 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 16 pin 11p |
| 7425 20p | 74151 30p | 74LS33 14p | 74LS265 80p | 4061 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 18 pin 16p |
| 7426 18p | 74152 30p | 74LS34 14p | 74LS266 80p | 4062 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 20 pin 18p |
| 7427 20p | 74153 30p | 74LS35 14p | 74LS267 80p | 4063 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 22 pin 22p |
| 7428 18p | 74154 30p | 74LS36 14p | 74LS268 80p | 4064 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 24 pin 24p |
| 7429 14p | 74155 30p | 74LS37 14p | 74LS269 80p | 4065 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 28 pin 26p |
| 7430 14p | 74156 30p | 74LS38 14p | 74LS270 80p | 4066 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 40 pin 30p |
| 7431 22p | 74157 30p | 74LS39 14p | 74LS271 80p | 4067 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | WIRE WRAP SOCKETS BY TI |
| 7432 18p | 74158 30p | 74LS40 14p | 74LS272 80p | 4068 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 8 pin 25p |
| 7433 22p | 74159 30p | 74LS41 14p | 74LS273 80p | 4069 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 14 pin 30p |
| 7434 22p | 74160 30p | 74LS42 14p | 74LS274 80p | 4070 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 16 pin 35p |
| 7435 22p | 74161 30p | 74LS43 14p | 74LS275 80p | 4071 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 18 pin 50p |
| 7436 22p | 74162 30p | 74LS44 14p | 74LS276 80p | 4072 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 20 pin 60p |
| 7437 22p | 74163 30p | 74LS45 14p | 74LS277 80p | 4073 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 22 pin 65p |
| 7438 22p | 74164 30p | 74LS46 14p | 74LS278 80p | 4074 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 24 pin 70p |
| 7439 25p | 74165 30p | 74LS47 14p | 74LS279 80p | 4075 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 28 pin 90p |
| 7440 15p | 74166 30p | 74LS48 14p | 74LS280 80p | 4076 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 40 pin 100p |
| 7441 55p | 74167 30p | 74LS49 14p | 74LS281 80p | 4077 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | VERO BOARDS |
| 7442A 30p | 74168 30p | 74LS50 14p | 74LS282 80p | 4078 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 2.5" x 5" 9p |
| 7443 70p | 74169 30p | 74LS51 14p | 74LS283 80p | 4079 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 2.5" x 7.75" 85p |
| 7444 70p | 74170 30p | 74LS52 14p | 74LS284 80p | 4080 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 3.75" x 3.75" 95p |
| 7445 60p | 74171 30p | 74LS53 14p | 74LS285 80p | 4081 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | Vero Block 410p |
| 7446A 30p | 74172 30p | 74LS54 14p | 74LS286 80p | 4082 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 3.75" x 5" 90p |
| 7447A 30p | 74173 30p | 74LS55 14p | 74LS287 80p | 4083 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 3.75" x 17" 410p |
| 7448 45p | 74174 30p | 74LS56 14p | 74LS288 80p | 4084 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 4.75" x 7.9" 530p |
| 7449 15p | 74175 30p | 74LS57 14p | 74LS289 80p | 4085 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | 2.5" x 17" 110p |
| 7450 15p | 74176 30p | 74LS58 14p | 74LS290 80p | 4086 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | Spot Face Cutter 130p |
| 7451 15p | 74177 30p | 74LS59 14p | 74LS291 80p | 4087 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | SWITCHES |
| 7452 15p | 74178 30p | 74LS60 14p | 74LS292 80p | 4088 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | TDGGL SWITCHES |
| 7453 15p | 74179 30p | 74LS61 14p | 74LS293 80p | 4089 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | Subminiature |
| 7454 15p | 74180 30p | 74LS62 14p | 74LS294 80p | 4090 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | SPST 60p, SPDT 65p |
| 7455 15p | 74181 30p | 74LS63 14p | 74LS295 80p | 4091 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | Push to make |
| 7456 15p | 74182 30p | 74LS64 14p | 74LS296 80p | 4092 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | (R.G.B.) 5p |
| 7457 15p | 74183 30p | 74LS65 14p | 74LS297 80p | 4093 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | Slide Switch DPDT 10p |
| 7458 15p | 74184 30p | 74LS66 14p | 74LS298 80p | 4094 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | Square PCB Switch 65p |
| 7459 15p | 74185 30p | 74LS67 14p | 74LS299 80p | 4095 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | |
| 7460 15p | 74186 30p | 74LS68 14p | 74LS300 80p | 4096 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | |
| 7461 15p | 74187 30p | 74LS69 14p | 74LS301 80p | 4097 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | |
| 7462 15p | 74188 30p | 74LS70 14p | 74LS302 80p | 4098 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | |
| 7463 15p | 74189 30p | 74LS71 14p | 74LS303 80p | 4099 14p | CA3086 48p | M51513L 230p | UPC1185 65p | BU206 175p | 2N2648 40p | N14033 14p | |
| 7464 15p | 74190 30p | 74LS72 14p | 74LS304 80p | 4100 14p | CA3086 | | | | | | |

MONITOR

Flying Signals

Hawk Electronic Test Equipment of Maidstone have announced three pieces of equipment of interest, primarily, to small industrial users.

For the Apple micro, comes a 32 channel input/output card allowing external control and data feedback, with four 8 bit bi-directional I/O ports, four 16 bit interval timers, two serial to parallel, parallel to serial registers and handshake capability. The card costs £49.50 all-inclusive and comes with documentation and a sample program.


Another card allows the Apple to function as an IEEE 4888 Controller for tests, measurements and control. This card can run up to fourteen separate controllable devices, with a transmission path of up to 20m. The on-board software interfaces directly with Basic and Applesoft strings. The GPIB Interface Card costs £189.00 inc. VAT and p&p.

Hawk have utilised advances in analogue to digital flash converters to devise their Tele-Scope 200S digital scope, which uses an ordinary domestic TV set as a screen, via the UHF aerial input.

The Tele-Scope can digitise signals at the rate of one per 100ns and display them indefinitely, allowing for transient, single-shot capture up to 250kHz.

The Tele-Scope costs £89.00 for the kit, or £109.00 for a built and tested unit, with special parts available individually as necessary. The manual includes circuits and layouts, and is also available separately. Prices are exclusive of VAT and p&p.

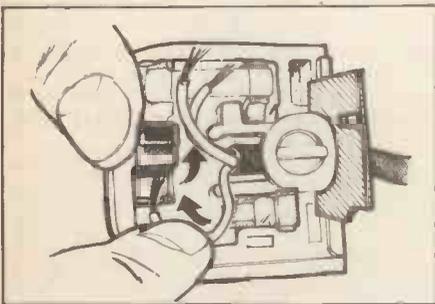Further information from Hawk Electronic Test Equipment, Parkwood Industrial Estate, Bircholt Road, Maidstone, Kent ME15 9XT Tel: (0622) 686811.



Electrician-Free Plug

At last, the perfect present for the electronics wizard who has everything. Particularly the boffins who raise their heads from their algebra only to be stymied by the necessity of putting an electric plug on their Fully Rotating Model Creation Of The Universe: the (almost) tool-free plug.

The TL-Handyplug, "A revolution in

plug design", to quote its makers, actually does only require one small screwdriver (or screwdriver substitute) to wire it up to a standard appliance cable, although a bit more wire trimming would be needed for a cable with a flat-cut end. The side of the plug (which looks, otherwise, no different from an ordinary plug) incorporates a small blade in a channel, which can be used to strip the inner cores of the flex, automatically to the required length.

The base of the plug releases by operating one screw through 90 degrees, and the bare ends of the wires are secured by locking clips. All very simple, and reported by our technical department to work very well.

Its other accomplishments are claimed to be speed of wiring, childproof features, impact resistance, flame resistance, and the availability of an accessory to help disabled people use it. The Handyplug is available from retailers at around £1.25, but for further information you can contact Toby Lec Marketing Ltd., Park Bridge Mill, Park Road, Blackburn, Lancs. Tel: (0254) 679911.

Heath Kits

The Heath Co. in the USA has appointed independent distributors in Europe for its well known Heathkits. The former Heath Electronics has changed its name to Zenith Data Systems Ltd., and will in future be concentrating on its own microcomputers and Heath Assembled Robots. In the UK, the distributors for Heathkits will be our old friends Maplin Electronics.

The old showroom in Tottenham Court Rd., London has been closed down. Any technical or other enquiries about kits obtained either from Tottenham Court Rd. or from their Gloucester address should be addressed to: Zenith Data Systems Ltd., Heathkit Division, 11B Bristol Road, Gloucester GL2 6EE, in writing only; any kits needing servicing should be sent to that address.

Kits obtained through Maplin, on the other hand, will be dealt with by Maplin themselves, at Maplin Electronic Supplies Ltd., P O Box 3, Rayleigh, Essex SS6 8LR. Tel: (0702) 554155. A free Heathkit catalogue is available now from Maplin.

New Hobby Shop

Twyford Electronics has been set up with the aim of supplying components and accessories to hobbyists at competitive prices — this is what we like to hear. They are situated about 100 yards from Twyford Station, about six miles out of Reading in Berkshire, and believe they are the only components suppliers for a considerable distance. They will be doing mail order as well as over the counter sales. We don't have a price list or catalogue for them as yet but

doubtless by the time you read this something will be available.

Phone, call or sent SAE to Twyford Electronic Ltd., 22 Station Road, Twyford, near Reading, Berks. Tel: (0734) 340333.

Exploring Jupiter

Jupiter Cantab have announced a 16K RAM pack and a 48K RAM pack, priced at £34.95 and £79.95 respectively, for the Jupiter ACE micro. As well as these, nine games tapes are now available, viz: Gobbledegook, Zombies and Potholes, and Othello for 19K memory; Greedy Gobbler, Blow Up The World, Missile Man, Spacefighter Pilot, Overtaker, Brands Hatch, Moo (!), Hangman, Fish ("swimming upstream to eat the floating detritus...") and Flutterer. The ninth tape is a Monitor tape (no relation) which enables the user to explore the inner workings of the computer and test programs.

Jupiter also have a new address, which is Jupiter Cantab Ltd., Cheshunt Building, Bateman Street, Cambridge CB2 1LZ. Tel: (0233) 313479. A glossy leaflet describing the ACE is also available.



Here Comes The Cavalry

You have obtained all the errata, tested all the components, checked all the dry joints, reversed all the electrolytics and changed the fuse. It still doesn't work. Do you despair? Do you give up electronics and take up flower arranging? No indeed! You contact WEB Logic Systems Ltd., who will build, test and/or repair any unstarted or partially and completed projects (I quote).

Logic Systems quoted around £10-£20 as an average cost for the complete assembly of most projects, and expect normally to turn a project around within five days of receipt.

Anyone interested, contact WEB Logic Systems Ltd., at Gainsborough House, 15 High Street, Harpenden, Herts. AL5 2RT. Tel: (05827) 62119.

Organ Kits

As more people turn to home music making as a hobby, and the interest in home computers and electronics continues to grow, home-built electronic organs can give you two hobbies in one — the enjoyment of putting together your own instrument from a set of easy-to-assemble kits, and playing your completed organ afterwards. As an added bonus, you also save money when comparing the cost of kits against that of a comparable commercial instrument.

The kits in question are produced in Germany by the Dr. Bahn company; they were the originators of the electronic organ kit over thirty years ago, and the range is now available in this country from **Swankit Instruments**.

The latest computer techniques are employed in the design of these organs, not only to make the building easy, but to give the best tones and effects. The range begins with a small single keyboard portable organ, as a starter project. Even people with no experience of electronics at all can get involved. The instructions are designed to be easy to follow, with clear diagrams. If you should have any problems, expert advice is just a telephone call away. At the other end of the range there are several large three keyboard machines, with enough features to keep the experienced amateur or professional player happy for years. The proprietor of Swankit Instruments is Graham Watkins, who is himself a keen amateur organist.

For information contact **Swankit Instruments, Chantry Park, Henfield, W. Sussex BN5 9JE. Tel: (0273) 494238.**

Shorts

House of Instruments have announced the first group in a brand new range of oscilloscopes from **Trio**. CS-1010, CS-1012, CS-1020 and CS-1022 are 10MHz single and dual trace and 20MHz single and dual trace respectively. All the new range have large six inch rectangular CRTs with illuminated inner-face graticule and high accelerator potential. All have extremely high input sensitivity of 1mV/cm which is continuously variable to 5V/cm. 1mV/cm is particularly valuable in conjunction with the 20 nsec/cm to 0.5 sec/cm sweep speed for

These full feature oscilloscopes measure a neat and compact 260(W) x 160(H) x 400(D) mm and weigh from 8.1 kg. They have all the performance and reliability you could expect from a high quality, professional oscilloscope. They are fully guaranteed for 00 years including free pick up, repair and return. Models with a tilt stand/carrying handle will be available. Please ask for free data sheets, prices or further information from **House Of Instruments, Clifton Chambers, 62**



High Street, Saffron Walden, Essex CB10 1EE. Tel: (0799) 24922.

The Electronic Organ Constructors Society is just that. They apparently have branch meetings in various parts of the country and publish a small magazine (A5, well printed, coloured card cover. The April issue has 40pp and I would guess it is published twice yearly). The emphasis in this issue is on traditional, theatre-style organs and *not* on rock music and synthesisers, just to put it in context, but the emphasis is genuinely on electronics nonetheless, with technical articles on a simple and advanced level, as well as area meeting reports and members' advertisements.

Contact the **Membership Secretary, Mr. W. Lewis, 8 St. John's Wood Rd., London NW8 8RE.**

Micro Peripherals have introduced the **Juki 6100**, a low cost 18CPS daisywheel printer designed for word processing use with personal and small business micros. The **Juki 6100** is a full featured daisywheel emulating **Diablo 630** protocol, fully compatible for use with **Wordstar**. Features include 18CPS bi-directional logic seeking; subscripts and superscripts; bold and shadow printing; character pitches 10, 12, 15 and proportional; graphics mode; 1/120 in min character spacing; 1/48 in line spacing; 2K buffer memory; 100 character **Triumph Adler** compatible 'drop in' daisywheel; 13 in platen with 11 in print line; linear motor for accurate positioning and low noise; **IBM 82** compatible single/multistroke ribbons.

A centronics compatible interface is provided as standard with an **RS232** serial and current loop interface as an option, and papers handling is either by friction feed or optional tractor feed. The price is £399.00 ex. VAT. Further details from: **Micro Peripherals Ltd., 69 The Street, Basing, Basingstoke, Hants. Tel: (0256) 3232.**

Elkan Electronics have just launched a new idea for **Dragon 32** users (not forgetting **Tandy TRS-80 Color Computer** users). This is the "**Dragon Supermarket**". There's now no need to search through endless magazines or contact numerous different suppliers — the "**Dragon Supermarket**" is a phone call or a **FREEPOST** (no stamp required) away.

In addition, the "**Dragon Supermarket**" is distributed free every month with "**Rainbow**" and "**Color Computer News**", two magazines from the USA which are devoted entirely to **Dragon 32** and **Tandy color computers**. Enquiries to **Elkan Electronics, 11 Bury New Rd., Prestwich, Manchester M25 8JZ. Tel: 061 798 7613.**

Ancom Ltd. write to say that they have just issued a four-page leaflet specifying their wide range of temperature and humidity measurement instrumentation. The ranges include digital thermometers, temperature indicators, controllers, annunciators, semi-intelligent devices and monitoring instruments, plus a psychrometer and a hydrometer. **Ancom** also do custom panels for non-standard requirements.

The leaflet we have at **Hobby** doesn't include prices, so specify, when writing, if you want a price list. Contact **Ancom Ltd., Devonshire St., Cheltenham GL50 3LT. Tel: (0242) 513861.**

Stotron's new main product catalogue has more than 160 pages and includes greatly enlarged ranges of **Alarms, Connectors, Displays, LED Lamps, Mains Filters, Indicators, Switches, Relays**, and many more products. A few of the suppliers that feature heavily are **Arcoelectric, Aries, Bulgin, C & K, Fabrillec, Hirose, ITW-Licon, Liton, National, Rafi, Roxburgh, Sifam, Star and Teka.**

All product lines are held in stock sometimes more extensively than the suppliers! Prices are aimed generally at the one-off and small quantity order market and there is no minimum order charge. For your copy of the catalogue contact **Stotron Ltd., 72 Blackheath Rd., Greenwich, London SE10 8DA Tel: 01 691 2031.**

The first batch of **ORIC's** specially commissioned software is now available from dealers. The five titles in the series are: **Oric Multigames (£7.95)**, a set of five family games comprising **Bandit, Projectiles, Colour Match, Quest and Reversi**; **Oric Flight (£7.95)**, simulation of aircraft landing; **Zodiac (£7.95)**, a sophisticated role playing adventure game; **Oric Chess (£9.99)**, five levels of difficulty with superb graphics; **Oric Base (£9.99** to include manual), a data management program which incorporates an easy to learn **Query** language. All cassettes are for the **48K** model.

The **Forth** tape is also expected to be available very shortly and will cost £17.95, which includes the price of the manual.

MONITOR

Oric Printer

Oric Products' first peripheral for the Oric I — the specially designed four-colour plain paper printer — is now available from retail outlets, priced £169.95. The printer, which features the Alps mechanism and an internal power supply, comes complete with a connecting lead, no other accessories are required. The Oric Colour Printer (MCP40) is plugged directly into the Oric expansion port and can be used with both 48K and 16K models.

Four colours — black, blue, red and green — are provided by rolling ball point pen dispensers. The printer features full alphanumeric capability and graphics specification, and sample programs are included in the comprehensive manual.

The Oric Colour Printer measures 10.75x6.37x2.50in high (lowering to 1.25in at the front) and is identical in colour to the micro — grey with blue stripes. The printer runs on 220/240 volts and, with a minor adjustment, can be used in the USA on 110 volts. Spare pens and paper rolls will be available through retailers.

The Oric MCP40 has a standard centronic interface and can be used with any microcomputer having a centronics interface.


Oric Products will be mounting a summer promotion until mid-September, offering a start-up pack of software valued at £40 with every 48K machine sold. The software package will contain four tapes — Home Finance, Teach Yourself BASIC, Oric Flight and Multi Games. Although the titles are subject to change the proportions of one home business, one educational and two games programs will remain unchanged. Oric I 48K retails for £169.95.

The 16K Oric I — due in retail outlets from early July onwards — will also be sold with a software pack (valued at £30) containing adaptations of the programs produced for the 48K. Once again there will be one home business program, one educational one and two games tapes. The 16K plus software package will retail at £129.95.

Digital DMM

Keithley Instruments' Model 128 hand held DMM claims to be one of the lowest priced digital 'beeper' DMMs around. It offers 0.5% accuracy, 3½ digit resolution (1mV, OR1), 10A capability, resistance to 20MR and five functions.

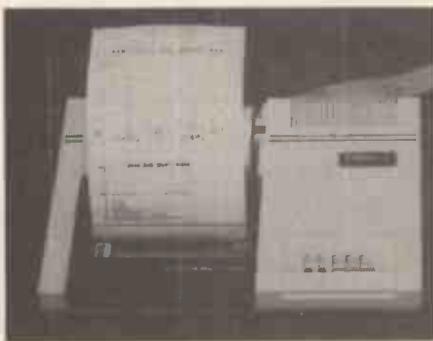The beeper indicates levels above the threshold when set to volts or amps, and below the threshold for ohms. The threshold is adjustable so that it can be set to the most useful point, from 10 to 300 digit, for the given situation. High input impedance (10MR) when the beeper is activated makes the 128 useful for sensing CMOS and other



logic levels. The beeper can be deactivated by a slider switch. The 128 has full overload protection, rotary switches and a colour coded faceplate. Battery life is 350 hours with alkaline batteries, and the price is £119 plus VAT and P&P.

Keithley have also recently introduced a range of four industrial standard digital thermometers, two models (865 for fahrenheit and 166 for centigrade) being thermistor thermometer and two, (the 868 and 869) with platinum resistance temperature detector sensors. These latter are the only four wire RTD hand-held thermometers on the market at present.

Further information from Keithley Instruments Ltd., 1 Bolton Rd., Reading, Berks RG2 0NL. Tel: (0734) 861287.

Control Modules For Micros

Centec Electronic Systems are designers and suppliers of hardware and software primarily for education and industry. One of their specialities is a range of control modules with BASIC or machine code, with which your micro can be programmed to switch lights, measure voltages, control motors etc. Centec have actually worked on devising hardware for a Schools Council "Microelectronics In Control" course which is now taught in many



schools, often as part of GCE 'O' level courses.

Their range includes a universal buffer module, A to D and D to A converters, DC motor and current buffer module, and a considerable list of other units both available now and under development. Compatible micros include the ZX81, Spectrum, Menta, 380Z, 480Z at present and others, including the BBC, to come.

Centec's 8-bit analogue to digital converter is designed to convert your computer system into an automatic data acquisition and analysis system, enabling you to automate the collection of any type of data for which the right transducer or sensor is available. It can monitor up to sixteen analogue channels and can be used by almost all BASIC and assembly language programs. The price is £42.95 one-off.

A range of mains switching units with one channel, two channels or four channels, features 5A per output socket (10A available optionally), LED monitors on socket outputs, 4mm sockets for connection to a computer, separate power supply and isolation from computer voltages. Units are priced £91.95, £29.95 and £49.95 respectively.

A separate power unit for the ZX81 features regulated DC output voltage, external voltage adjustments, short circuit protection, style to blend with the ZX81, among others. It is designed to power external hardware without overloading the micro, uses the micro's power supply and plugs straight in. The fixed 5 or 12V models are £6.95 each and the variable 5 to 12V model is £7.75. P&p is 45p per order.

Orders and enquiries to Centec Electronic Systems, 47 Spur Rd., Orpington, Kent BR6 0QR. Tel: Orpington 35353.

The Proto-Board[®]

Now circuit designing is as easy as pushing a lead into a hole . . .
 No soldering
 No de-soldering
 No heat-spoilt components
 No manual labour
 No wasted time



For quick signal tracing and circuit modification
 For quick circuit analysis and diagramming
 With or without built-in regulated power supplies
 Use with virtually all parts — most plug in directly, in seconds.
 Ideal for design, prototype and hobby

| NO | MODEL NO | NO OF SOLDERLESS TIE-POINTS | IC CAPACITY (14-pin DIP's) | UNIT PRICE | PRICE INC P&P 15% VAT | OTHER FEATURES |
|----|----------|-----------------------------|----------------------------|------------|-----------------------|----------------|
| 1 | PB6 | 630 | 6 | 11.00 | 13.80 | Kit |
| 2 | PB100 | 760 | 10 | 14.25 | 17.53 | Kit |
| 3 | PB101 | 940 | 10 | 19.65 | 24.32 | |
| 4 | PB102 | 1240 | 12 | 24.95 | 30.41 | |
| 5 | PB103 | 2250 | 24 | 40.95 | 48.81 | |
| 6 | PB104 | 3060 | 32 | 51.45 | 61.46 | |
| 7 | PB105 | 4560 | 48 | 74.50 | 87.97 | |
| 8 | PB203 | 2250 | 24 | 76.00 | 89.70 | 5V @1A |
| 9 | PB203A | 2250 | 24 | 105.00 | 124.20 | 5V ± 15V |
| 10 | PB203AK | 2250 | 24 | 85.00 | 100.05 | 5V ± 15V & Kit |

Tomorrow's tools for today's problems

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited, Dept. 14U
 Unit 1, Shire Hill Industrial Estate,
 Saffron Walden, Essex. CB11 3AQ.
 Telephone: Saffron Walden (0799) 21682
 Telex: 817477

G.S.C. (UK) Limited, Dept. 14U Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

1 Only Req 2 Only Req 3 Only Req 4 Only Req 5 Only Req 6 Only Req 7 Only Req 8 Only Req 9 Only Req 10 Only Req


Name _____ Address _____

I enclose Cheque/P.O. for £ _____ or debit my Barclaycard, Access.

American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION — The G.S.C. 24 hour 5 day a week service
 Telephone (0799) 21682 and give us your Barclaycard, Access.
 American Express number and your order will be in the post immediately

For FREE catalogue tick box

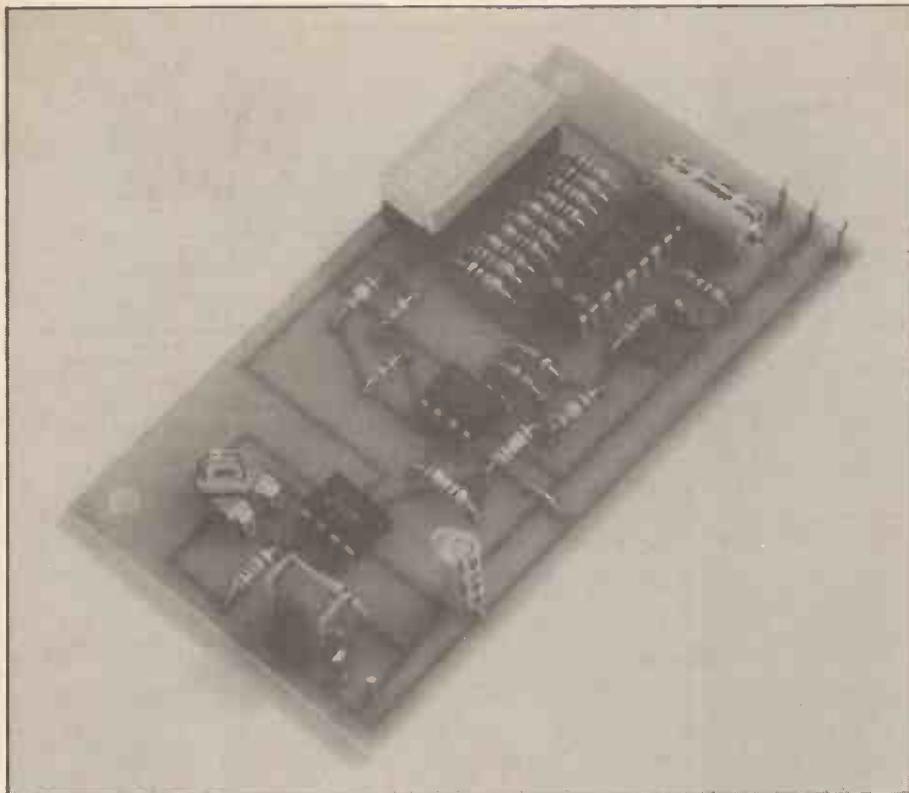

AUDIO LEVEL METER

R. A. Penfold

The golden secret of first-class sound reproduction is a reliable set of level meters. Our versatile log-driven peak-reading audio level meter can be built either with a 10-LED bargraph display, or ten separate LEDs, and cased either as part of another piece of equipment or separately, alone or as a pair . . . whatever you want.

ALTHOUGH not so long ago ordinary moving-coil meters were almost invariably used for audio level indication (the exceptions being the so called "magic eye" indicators), these days LED or liquid crystal displays seem to have largely taken over in this area. Superficially these look very similar to the old "magic eye" type indicators, but they are not just an expensive alternative to a high quality meter movement, and most types actually offer a higher level of performance than simple analogue VU meters. The latter are average reading, apart from some of those fitted to expensive items of equipment such as professional mixers. The drawback of the simple type is that many instruments, such as pianos, have a high peak-to-average signal level, so that the meter tends to under-read and severe distortion can result.

LED and liquid crystal level indicators are normally designed to be peak reading so that accurate and meaningful results are obtained regardless of the input waveform. Some give the option of average-reading so that someone who is familiar with the vagueness of this type of meter and prefers to use it can do so.

This audio level indicator is relatively simple and inexpensive, but nevertheless has a high level of performance. It uses a ten LED bargraph display, and the LED threshold levels are spaced at 3dB intervals. If, for example, the circuit is set up so that the highest LED switches on at +6dB, this would give LED threshold levels of -21, -18, -15, -12, -9, -6, -3, 0, +3, and +6dB. However, the unit can be set up to have any threshold levels within reason, but the spacing between the thresholds will always be 3dB and it is not adjustable. The circuit has the professional standard attack and decay times of 2.5ms and 1s respectively, and it gives very accurate and reliable results. The unit will fit into most situations without difficulty as it has a full drive sensitivity which is adjustable from about 20 to 900 millivolts RMS.

System Operation

There are few stages in this unit, as can be seen from the block diagram of Figure 1.

The amplifier at the input is merely used to boost the gain of the circuit if necessary. Its voltage gain is adjustable from about 50 times to unity, and this gives the unit its adjustable sensitivity.

Two precision rectifiers are fed with the output of the amplifier, and their outputs are mixed together. The two rectifier stages are not the same, and the important difference is that one does not invert the input signal whereas the other does. They both provide a positive output signal. In effect, one rectifier provides an output while the input signal is positive and the other provides an output while it

The VU meter

THE VU METER, now somewhat long in the tooth, was developed to fulfill the need for a device to indicate the relative volume levels of programme material — speech and music — so that overloading of circuits could be avoided. Being calibrated somewhat arbitrarily, its background and use can be somewhat mysterious. Here, then, the mystery is explained.

The history of the development of the VU meter — more properly called a Standard Volume Indicator — can be traced back to 1921 when American engineers set out to broadcast the ceremony of the burial of The Unknown Soldier by means of telephone lines and public address amplifiers. In order to minimize distortion, the level at which overloading of the various line amplifiers occurred was determined by experiment, and this level was taken to be the reference level. A "volume indicator" was then developed consisting simply of a 2dB step attenuator, calibrated in decibels with respect to the reference level; a triode valve detector and a milliammeter. The method used was to adjust the attenuator so that the signal peaks reached the mid-scale point of the meter once in ten seconds, on average. The volume level was then read directly from the attenuator scale. This instrument provided an indication of the volume levels but exerted no control over these levels.

The next stage of advancement came in 1942, when it had become apparent that the large number of similar instruments by then existing was causing

confusion. The American Standards Association published the results of a collaboration between engineers of the Columbia Broadcasting System, Bell Telephone Laboratories and the National Broadcasting Company, and in adopting the recommendations as a Standard, introduced the now universally accepted Standard Volume Indicator.

In the course of the work leading up to this Standard the effectiveness of both RMS and peak-reading meters was established as being virtually equal for systems extending over short distances. Group-delay effects (the term applied to the delay of different frequencies by differing amounts, which can be quite appreciable in long-haul links) however caused discrepancies in the peak-level meter readings, and therefore the RMS meter, happily of simpler design, was chosen for further development.


The final design consists of an RMS reading voltmeter, slightly underdamped to promote easier reading at peak level, calibrated in both Volume Units (hence the term VU) and in percentage of maximum permissible level. The scale has a buff-coloured background — said to reduce eye fatigue. In instruments designed for use with different systems, an attenuator is normally provided to suit the meter to the job in hand. More usually, the meter is permanently installed in one piece of equipment, and the OVU point will have been set at the level where overloading is just

beginning to occur.

Its most important characteristic is that it offers freedom from cumbersome and unnecessary absolute RMS voltage measurements. An operator, faced with a number of meters, treats each in an identical fashion, rather than having to know how the appropriate voltage levels at each measurement pick-off point.

Most people will meet the VU indicator while adjusting tape recording levels. In this case, the indicator should be treated according to the type of programme material. The meter deflection should be observed for about one minute for music, and for five to ten seconds for speech. Opinions are divided, at this juncture, whether to accept the occasional deflection of unusual amplitude as being the peak reading or not. The highest possible recording level is desirable to maintain a good signal-to-noise ratio and wide dynamic range, but the danger of overload distortion is always present. With today's noise-reduction systems and companders, S/N ratio is not the problem it was, and so it is probably better to operate at a lower level. On the other hand, most equipment manufacturers will be erring on the side of caution in their calibrations, and absolute maximum peak levels of +1 or +2VU will, in all probability, do no harm. In the end, individual equipment characteristics and personal preferences will dictate the exact method of use.

Steve Roberts

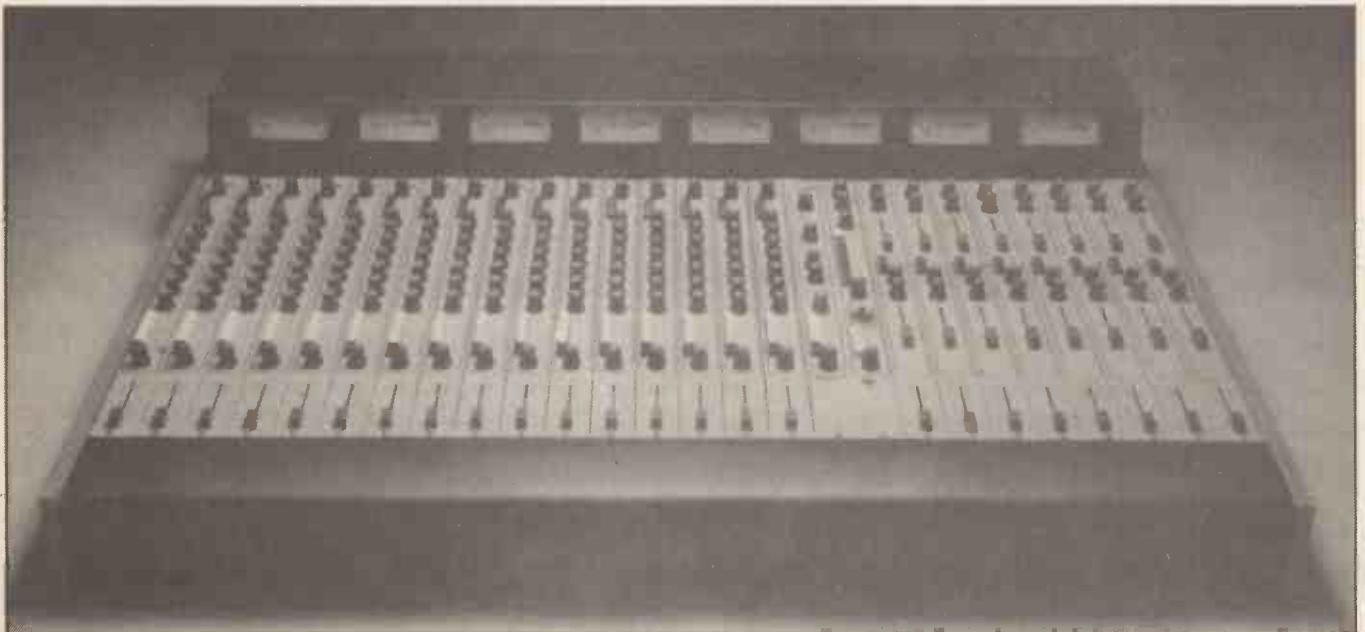

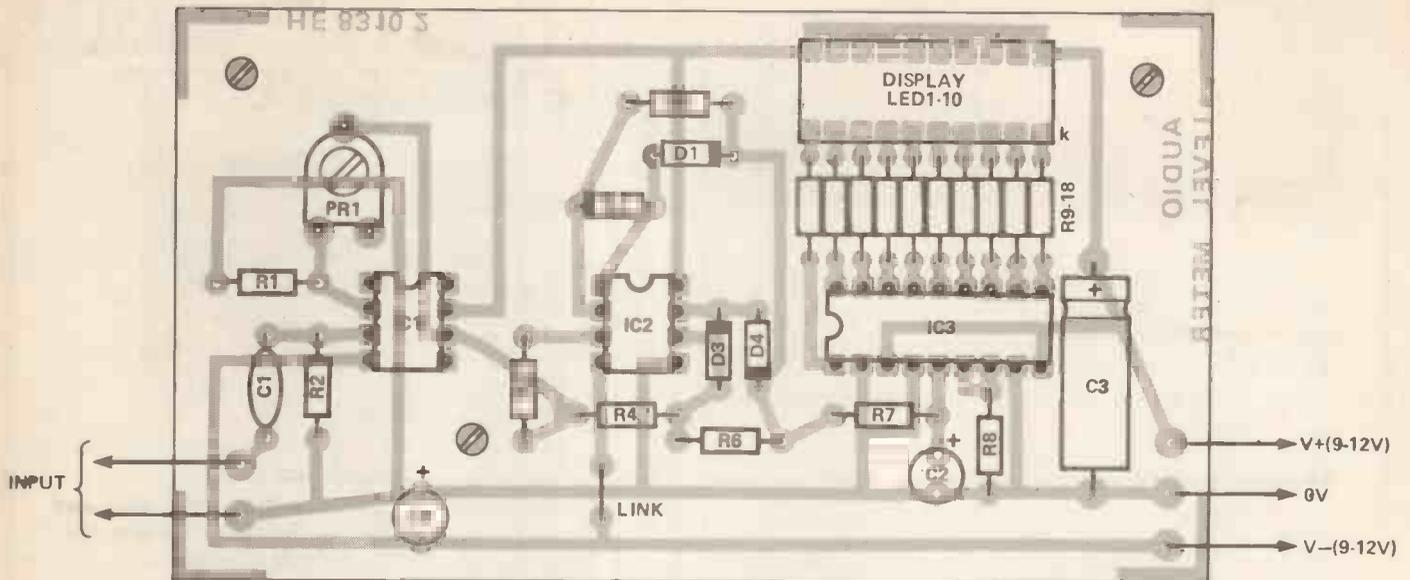


Figure 3. The components, with one wire link.

Parts List

RESISTORS

(All 1/4W 5% carbon)

| | |
|----------------|------|
| R1 | 10k |
| R2, 3, 4, 5, 6 | 100k |
| R7 | 220R |
| R8 | 1k5 |
| R9 to R18 | 1k |

POTENTIOMETERS

| | |
|-----|--------------------------------|
| PR1 | 470k 0.1W horizontal preset |
|-----|--------------------------------|

CAPACITORS

| | |
|----|---------------------------|
| C1 | 220n polycarbonate |
| C2 | 10u 16V tantalum bead |
| C3 | 100u 16V axial electro |
| C4 | 10u 25V radial electro |

SEMICONDUCTORS

| | |
|-------------|---------------------------------------|
| IC1 | 741C op-amp |
| IC2 | TL072CP dual BIFET op-amp |
| IC3 | LM3915N bargraph driver |
| D1, 2, 3, 4 | 1N4148 signal diode |
| D5 to 14 | 10 LED bargraph display any colour |

MISCELLANEOUS

Printed circuit board; 20 pin DIL holder for bargraph display; Veropins; screened cable, wire, solder, etc.

BUYLINESpage 32

display. An advantage of using individual LEDs is that LEDs of different colours can be used, and this can give a clearer and more attractive display, but it can be difficult to produce a really neat display. If you do use a proper bargraph display, make sure that it is connected the right way round. The normal method of identifying the polarity seems to be by having the device identification and other markings on the side of the device which has the anode pins. If the board is mounted horizontally (as shown in Figure 3) the display will read from left to right, like a conventional meter. Of course, it could be mounted vertically if it is felt that this would give a more easily interpreted display.

Mechanically construction must be varied to suit the way in which the unit will be used. It can be constructed as a self-contained unit powered from a couple of 9 volt batteries and housed in its own case, and a two pole on/off switch would then have to be included in the unit. Alternatively a mains power supply unit could be used as the power source. In some cases it might be possible to add the unit to an existing piece of equipment, or to build it into a piece of audio gear you are constructing.

If it is built as a separate unit the lead which connects it to the main item of equipment will have to be a screened type with the outer braiding connecting to the earths of the two pieces of equipment. This is not just a matter of preventing stray pick-up of hum and other noise from giving misleading readings from the unit, because without the use of a screened cable it is quite possible that noise could be fed into the main piece of equipment. It might also be necessary to use a screened lead if

the unit is housed in the main item of equipment.

Of course, the signal take-off point will depend on what type of equipment the meter is used with. It could, for instance be used to monitor the output of a preamplifier or mixer, but it is obviously not possible here to give detailed instructions on how the unit can be connected to numerous items of audio gear. This is something that the constructor must determine for his or her self, but in most cases the correct method of connection will probably be fairly obvious.

Adjustment

The finished unit only requires one adjustment, and this is to set PR1 for the correct sensitivity. In order to do this the main piece of equipment is fed with an audio signal that represents a level of 0dB (with controls on the main equipment being adjusted for the correct signal level as well, if necessary). PR1 is then adjusted just far enough in a clockwise direction to give a reading of 0dB from the display.

It is unlikely that the meter will prove to be over-sensitive even when set at minimum sensitivity, but if necessary a resistor of about 470k in value can be connected in series with the input to reduce the sensitivity to a satisfactory level.

If an average reading circuit is required it is merely necessary to raise the value of R7 to about 10k so that the attack time of the unit is lengthened and it responds less readily to transients. In the interest of obtaining an easily-read display it is advisable to retain the long decay time of the circuit.

MEON ELECTRONICS



MULTIPURPOSE STORAGE BINS

Set of 10 high quality storage bins which can be wall mounted or stacked in almost any configuration. Each bin measures approx. 109mm wide x 53mm high x 100mm deep and is of high impact co-polymer plastic construction. Supplied with 2 wall mounting bars. Ideal for storing components of hardware in workshops, garage, home etc.

* EXCELLENT VALUE at only £4.95 per set (p&p £1.50)

SPECIAL OFFER - RECHARGEABLE BATTERIES

Manufactured by Saft or Gould - Limited stocks available.

| | |
|--|------------|
| *HP7 (AA) pencils 0.5Ahr | £0.85p ea. |
| *HP7 (AA) pencils 0.5Ahr tagged | £0.90p ea. |
| *HP7 (AA) pencils 0.5Ahr vented, quick charge 150mA 3-5hrs | £1.00 ea. |
| *HP11 ('C' size) 1.2Ahr | £1.90 ea. |
| *HP11 ('C' size) 2.0Ahr | £2.25 ea. |
| *HP11 ('C' size) 2.0Ahr tagged | £2.30 ea. |
| *HP2 ('D' size) 1.2Ahr | £2.00 ea. |
| *HP2 ('D' size) 4.0Ahr | £3.25 ea. |
| *HP2 ('D' size) 4.0Ahr tagged | £3.30 ea. |
| *SUB 'C' 1.2Ahr | £1.45 ea. |

Please add 10% for post and packing.

All goods fully guaranteed. Despatch by return of post. Prices apply U.K. only. Trade enquiries welcome.

All orders to:
MEON ELECTRONICS
 P.O. Box 34, Luton, Beds LU1 1LS
 Tel: Luton 28606

LB ELECTRONICS

FRUSTRATED EXPORT ORDER BRAND NEW & BOXED. EPSON FX80 PRINTERS £350.00 + VAT (carriage £12 tnt)

SPECIAL OFFERS (while stocks last)
 Mullard .2" Red L.E.D.'s 0.06p, 7805 38p, 7805KC 5 Volt 1.5A 75p, 78H05 5V 3 AMP £3.50p, 5K 3/4" multiturn trim pots 14 for £2.50p

DISC DRIVE BONANZA

PERTEC FD650 DSDD £199 + VAT
 TEAC FD-55F 1/2 Height DSD 80 track/
 40 track selectable at our new low price £199 + VAT
 PAPT 3" Box Fan 220 volts 50hz require
 1uf capacitor £7.95 p/p £1.00
 As above but 12" 22mhz band width £88.70 + VAT
ASC11 coded qwerty Keyboard, manufactured by Alphanumeric (Woking UK). Model 60K brand new plus data..... £19.95p p&p £1.50

25 WAY 'D' Types, plugs £1.85, sockets £1.85 (solder tail) p&p 30p. Telephone for bulk prices.
8" Drive Cabinets complete with power supply (LINEAR) to take two 8" Drives, Brand New £99.95p + VAT (carriage cost)
Twin 5" Cabinets with power supply £30.00 + VAT (providing a disc drive is purchased from us, if drives purchased elsewhere £40.00 + VAT)
9" Green Phosphor Monitors Brand New and Cased Composite Video Input 18mhz band width £80 + VAT each (carriage cost)
Textool 24 dil Zif Skt (used) £3.95p p&p 30p
Brand New 13" Colour monitor fully cased. Full warranty 540 x 236 pixel. RGB TTL Input plus apple Input £220 + VAT (carriage at cost).
BNC Lead Bonanza coax lead with BNC plug at one end, 2 metres plus £1.00 p&p 30p and 10 metres plus £2.50 p&p 75p

LB ELECTRONICS

11 HERCIES ROAD, HILLINGDON,
 MIDDLESEX UB10 9 LS, ENGLAND
 TEL: UXBRIDGE 55399



ELECTRONI-KIT

FX-COMPUTER



Teach-Yourself Computer and Electronics Construction Kit

A complete introduction to the "How, Why and What" of Computers and Electronics in the most practical way ever devised

THE KIT IS BATTERY-OPERATED AND COMPLETELY SELF-CONTAINED. NO TELEVISION OR OTHER EQUIPMENT IS REQUIRED. VERY EXTENSIVE MANUALS ARE INCLUDED

Ministry of Science and Technology, Japan - Prize Winning Product

The **FX-COMPUTER** is the ideal introduction to the study and understanding of computers and electronics. The kit offers remarkable versatility because the components are interchangeable and circuits are constructed by simply plugging specified components into the board provided in accordance with the instruction manuals. You quickly understand the principles involved and new circuits can be easily devised, built and dismantled. No soldering or wiring is involved, no tools are required; the components themselves complete the circuits.

No previous knowledge is required - very extensive educational manuals have been provided by English experts in computers and electronics. Working through the manuals you will soon be able to write programmes and "run" them and understand how computers work.

The following are just a few of the programmes in the Computer Manual (there are too many to list here) and also a few of the projects in the Electronics Manual:

How to instruct the Computer and Store Information into Memories. Use of different Instructions and Programming Techniques. Adding, subtracting, multiplying, dividing, averaging, counting up, counting down, etc. etc. - in Decimal and Hexadecimal. Converting Hexadecimal to Decimal, storing Random Numbers. Games: Tennis, Catch-the-Rat, Gun Fight, Slot Machine, etc. Using the Computer as a Musical Organ, storing and playing-back tunes, etc. **OVER 100 PROGRAMMES SHOWN IN THE COMPUTER MANUAL PLUS EXPLANATIONS AND DEMONSTRATIONS OF ALL TECHNICAL TERMINOLOGY.**

Electronic Components and How they Work - batteries, conductors, resistors, capacitors, diodes, transistors, lamps, photo-electric devices (CdS cell is included in the kit), oscillators, burglar alarms, control systems, organ, lie detector, etc., etc. **OVER 65 PRACTICAL WORKING PROJECTS, SHOWN IN THE ELECTRONICS MANUAL.**

All this is in ONE kit, costing about the same as the cheapest "Basic" ordinary Computer

The price is only £69.95 plus £3.00 P&P (overseas rates quoted on request)

TRADE & EDUCATIONAL ENQUIRIES WELCOMED

Send cheque/PO/Access/Barclaycard to
DEPT. HEFX. Electroni-Kit Ltd
It's not JUST a computer!

ELECTRONI-KIT LTD.
388 ST. JOHN STREET
LONDON, EC1V 4NN (01-278 0109)

A Hobby Electronics hardware review

The FX-COMPUTER

The arrival of the Common, or Garden, microcomputer has made teach-yourself-computing one of the world's most popular pastimes. Now, using the same approach, we have teach-yourself-electronics — is it an advance? Read on . . .



Terry Westwood

The Japanese are said to value educational achievement more than any other nation, so it's hardly surprising when they come up with a self-training kit, for youngsters, in that apparently most essential of modern attainments, Knowing What To Do With A Microcomputer. The FX Computer is described as "A complete introduction to the How, Why and What of Computers and Electronics in the most practical way ever devised". It's certainly an attractive idea. The 'computer' is completely self-contained, not needing (and indeed prohibiting) any mains connection, while the actual components for experimentation are individually built in to plug-in plastic modules — an idea also used in industrial training kits, which removes the need for soldering and (more to the point) extensive desoldering, when experimenting with circuits.

The FX-Computer itself owes more in appearance to one of those fancy radio sets, covered in knobs, dials, loudspeakers and switches, than to a microcomputer. The casing is made of a reasonably tough plastic, but some of the joints give the impression of being rather flimsy. The 'peg-board' where the modules are plugged in to make up the circuit is so arranged that the modules plug in and stay put reasonably reliably — a matter of some importance, as the unit is designed to be used upright. The

young (or not-so-young) experienced in the use of Lego bricks will not be satisfied if the modules start dropping out onto the tabletop! But so far this does not seem to be a problem; how the modules stand up to extensive wear and tear remains to be seen. For storage, the area containing the modules is covered by a clear plastic lid which hinges into place.

Pure And Simple


The power for all the circuits is taken from six HP7-type batteries. This can prove expensive to run. It's a distinct advantage, though, for young children, to have something which has no connection to the mains. Circuits are built up, simply by pugging the component modules into the 'peg-board' in the right configuration. The modules are made of transparent, green-tinted plastic, with a component symbol etched in white on the top, so it's easy to see what components are being used. The actual component is also easily visible through the plastic. Connection is made via flexible metal strips on the sides of the modules, like ordinary battery-holder contacts.

The peg-board matrix provides the power connections, and also connects to other 'modules' within the overall unit, for instance an amplifier with a volume control and


loudspeaker, and a CdS cell which acts as a light-sensor for some of the experiments. Extra space is provided for future expansions such as a meter (and the FX's makers provide a number of kits which can be used to extend the FX's capabilities).

Two manuals are provided: one giving 65 electronics experiments, and the other with 100 computer programs. I can't recommend the manuals too highly. It's well known that a picture is worth a thousand words; this depends on the picture of course, but in this case the pictures are not only clear and illustrative, but pictures and text lead naturally on from one point to the next, making the whole thing supremely easy to follow, and I wish that a few other writers of self-instruction books would take a tip or two . . . For each project, the electronics manual gives clear instructions, circuit diagrams, outline identification and layout diagrams, with a simple and direct approach and with many ideas to aid the reader. This makes it much easier for the reader to associate these different aspects of project work. Being laid out step-by-step fashion, it will take a complete novice up to the point where he or she can build a series of simple circuits and understand basic electronics. Also provided are a pair of small cables for connection to external modules, provided with the kit.

● CAPACITOR

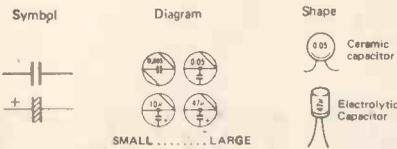

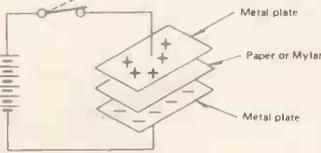A capacitor stores direct current (charges up) by way of two metal plates positioned face-to-face.



The amount of electricity stored (the electrostatic capacity) depends upon the size of the metal plates. Larger plates — more capacity (F).

$$1 \text{ F} = 1,000,000 \mu\text{F}$$

$$1 \mu\text{F} = 1,000,000 \text{ pF}$$

When a capacitor is fully charged the current stops flowing. Alternating currents however (e.g. voice signals, dial tones) continue to flow. Alternating current changes its flow direction and a capacitor repeats charging and discharging.

A simple description of capacitors and capacitance.

Dubious Connections

Despite the obvious merits of the system so far I have some complaints. The first and most annoying, considering that the FX-Computer is not a cheap bit of equipment, is that some of the modules did not have accurately-machined connectors, resulting in irritating open-circuits. Not a lot of use when you are trying to learn about electronics without learning to solder! Also, some of the circuit symbols on the modules could be confusing to a novice. For instance, some components can be used simply as links, but this is not very well indicated. Maybe the use of an alternative colour for those modules would help? The explanations of the circuits, so far as they go, are fine, but they do not go into enough detail to build up the kind of understanding which could lead to building more complex circuits — for this reason, the electronics is kept at a very basic level indeed. Also, there are simply not enough components. For instance, there is only one transistor — so you cannot even build a bistable. And you can't bias that transistor accurately, as there are not enough resistors and capacitors (although there is a good selection) to produce a full E20 standard set.

Taking that complaint to its 'logical' conclusion (!) is my most serious grumble: that is there is *no logic* or IC tutoring whatever, a factor which seriously undermines the FX-Computer's claim to be a complete introduction to computers and electronics. The most essential link is omitted altogether! With the great increase in the use of digital as opposed to analogue electronics, this kind of thing is to be regarded as basic, not an 'extra'.

So let's look at the actual computer module. This plugs in in exactly the same way as the components, but is a great deal larger. Using the same connections, it provides the facility to

learn about interface circuitry. The input is a hex key pad, which is also used as the tonic sol-fa for music programs. The outputs come in the form of a seven-LED strip, as single-figure seven segment display, and a loudspeaker, so that no television or monitor screen is needed.

The computing manual, as with the electronics manual, contains many good descriptions and clear diagrams. The flow charts describing the set exercises are easy to follow, and the manual takes you through an organized learning path, building up knowledge and confidence as you progress. Once again, we have a good idea, but with some serious drawbacks. The computer is designed to do teaching demonstrations, and that is all it can do. It can't be interfaced to any equipment not specifically designed to go with the FX-Computer system. The language used is a very low-level machine-code type, which does not bear a great deal of resemblance to the high-level languages normally used by microcomputer owners. And the manual, again, is excellent as far as it goes, but does not give enough detail for the bright enthusiast to progress further.


An Odd Couple

There is a case of trying to put a quart into a pint pot here: the FX does not have enough memory to provide a high-level language, yet tuition in a machine code gives the absolute novice no real introduction to practical computer programming, while those who are interested in code programming will find that the FX's level of electronics is laughable; even were each section of the FX's teaching scheme more extensive and ambitious, they would still be mismatched. I felt that there was

TESTING FX-MELODY AND CLOCK (where fitted)

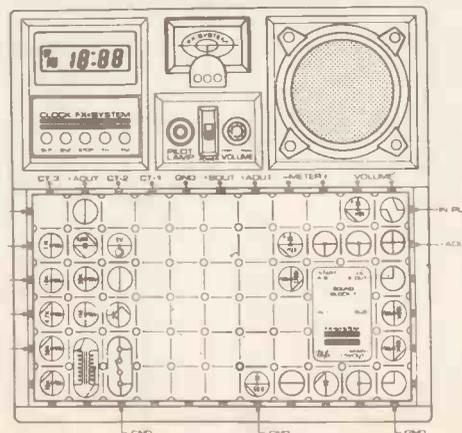- 1) Insert the batteries and press the Stop switch of the clock to test the clock unit.
- 2) Turn on the main switch to light the pilot lamp. A tune will play automatically; control the volume by turning Volume switch.
- 3) Press the key switch to light the Lamp.
- 4) If the above operations can be performed correctly the kit is functioning properly.

IF, AFTER THOROUGHLY CHECKING, THE KIT DOES NOT FUNCTION CORRECTLY, CONTACT YOUR DEALER OR DISTRIBUTOR.



Each project is accompanied by an assembly diagram showing the component modules.

a big jump in understanding between the electronics projects and the computing projects, and that the designers could have improved what linking there is between these two sections.


I feel that the FX-Computer is a good start in electronics for children

No.22 Use of TIY, AIY and AM to store data in memory

● PROGRAM

| address | command | machine |
|---------|---------|---------|
| 00 | TIY | A |
| 01 | (0) | 0 |
| 02 | KA | 0 |
| 03 | JUMP | F |
| 04 | (0) | 0 |
| 05 | (2) | 2 |
| 06 | AO | 1 |
| 07 | KA | 0 |
| 08 | JUMP | F |
| 09 | (0) | 0 |
| 0A | (E) | E |
| 0B | JUMP | F |
| 0C | (0) | 0 |
| 0D | (7) | 7 |
| 0E | AM | 4 |
| 0F | AIY | B |
| 10 | (1) | 1 |
| 11 | JUMP | F |
| 12 | (1) | 1 |
| 13 | (1) | 1 |
| 14 | JUMP | F |
| 15 | (0) | 0 |
| 16 | (2) | 2 |

FLOWCHART

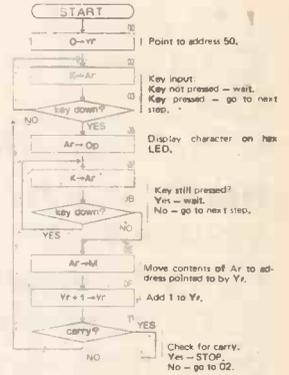

This program is another example of two KA commands being used in different ways. At the first KA, the program waits if a key has not been pressed; at the second it waits if a key has not been released. Program ends when data has been stored at all 16 addresses 50-5F.

Part of a programming instruction, showing a listing and flow diagram.

beginning at about 10 to 14 (or adults with no previous experience), but I would not want to pay the price (£69.95) for the system as it stands for my son or daughter. What with low-cost micros available, and an increasing variety of self-teaching booklets, not to mention computers in school, there are too many good alternatives for anyone with determination. Perhaps I feel a confidence that parents not acquainted with computers would not feel, but as for the children — they have plenty of confidence, and will probably meet with plenty of opportunities to learn something about computers!

Electronics is another matter — and it's worth noting that the same companies (just for the record, the Denshi Block Mfg. Co. Ltd., and the Gakken Co. Ltd.) and their UK distributor, Electroni-Kit Ltd., also deal in a whole range of electronics self-teaching modules, in the same style as the FX system, but without the programming part. These are known as EX (sic) kits, and come in a variety of prices and sizes, and Electroni-Kit do a brochure describing the contents. Electroni-Kit, of course, do their own range of small self-teaching kits as well. You can write to them at Electroni-Kit Ltd., 388 St. John Street, London EC1V 4NN.

Mind you, the FX-Computer has been awarded a design prize by the Japanese Ministry and Science and Technology, so somebody obviously thinks it's going to work. I continue to feel that it's a very good idea which just isn't capable of giving full value within its adopted format. But, who knows — it may start some interesting trends.

COMING SOON TO . . .

Hobby Electronics

PARA-Q THE HE STEREO PARAMETRIC EQUALIZER

The professional solution to many problems in audio equalisation!
Parametric equalisers are flexible and precise. They can be used in place of graphic equalisation systems in many situations, and for many other jobs where a graphic would not be equal to the task.

The HE Para-Q is a stereo parametric equaliser designed to semi-professional standards but that can be built at an amateur's price.

Up to 20dB of boost or cut is available at any centre frequency from 50Hz to 11kHz and the 'Q', which sets the bandwidth around the centre frequency, is variable up to a maximum of 25, allowing either a very narrow or a wide band of frequencies to be operated on.

It can be used for equalisation or hifi systems, home recording studios, for music synthesis or any other musical signal conditioning application.

PERSONAL CASSETTE BATTERY SAVER

A "home base" power supply unit to save your batteries when you're listening to your personal cassette unit at home or at work.

In addition, the PSU doubles as a Ni-Cad battery charger, so your spare batteries can be on charge at home while you're on your skates in the great outdoors!

MORE FOR THE MOTORIST

Two easy-to-build car accessory projects, to give your motor that extra touch of class.

IN CAR ENTERTAINMENT OFFER

A very special offer will be available to readers of Hobby Electronics, only, in our November issue.

If you've ever fancied a top class in-car stereo system but have always backed off at the price, you must see next month's issue for this sensational offer!

Please reserve mecopies of the November issue

Hobby
Electronics

for
Name

Address



Hobby
Electronics

November issue on sale at
your newsagent
from 14th October.
Place your order now!

Although these articles are being prepared for the next issue, circumstances may alter the final content.

MASTER ELECTRONICS NOW! The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY
THIS IS THE AGE — OF ELECTRONICS!
the world's fastest growth industry...

There is a world wide demand for designers/engineers and for men to service and maintain all the electronic equipment on the market today — industrial — commercial and domestic. No unemployment in this walk of life!

Also — the most exciting of all hobbies — especially if you know the basic essentials of the subject. . . .

A few hours a week for less than a year — and the knowledge will be yours. . . .

We have had over 40 years of experience in training men and women successfully in this subject.


Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.

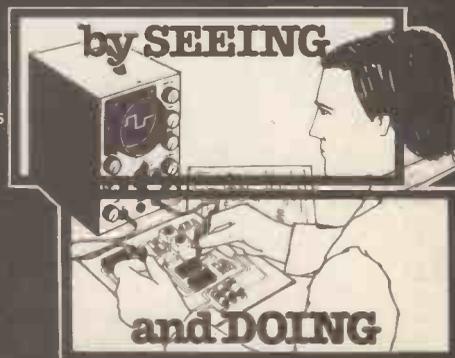

British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE!

COLOUR BROCHURE



POST NOW TO

Please send your brochure without any obligation to

NAME _____

ADDRESS _____

HE/10/841

BLOCK CAPS PLEASE

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS please state below

OR TELEPHONE US
0734 51515 OR
TELEX 22758
(24 HR SERVICE)



British National Radio & Electronics School Reading, Berks. RG1 1BR

CAREERS IN ELECTRONICS '83

Expertise in computer electronics does not only lead to the lab. It can lead to a career as a Customer Engineer, and further. This month we look at a special training course, and some other career routes in digital hardware

A Customer Service Engineer in any business needs a combination of technical and management skills which puts him not so much with a foot in each camp, as with both feet in both camps — unlikely as this may sound. This is doubly true of customer engineers in companies dealing in computer systems, where very expensive and specialised equipment is being sold, often in quantity, to non-specialist customers, many of whom (at the present) are dabbling in computer systems for the first time.

Customer Service Engineers are responsible for installing computer systems on the customer's site, and also maintaining equipment and solving any problems which arise, also on site. This calls for a fairly high level of technical skill, coupled with the ability to handle a possibly irate or anxious customer tactfully and maintain his confidence in engineer, company and system!


The Customer Engineer is very much his company's direct ambassador. (The vast majority of computer engineers are still men. This is due to lack of women applicants — as one college department said when asked why they had only taken in one woman engineer in a year: "We accepted all the applicant we had".)

He may also have the role of salesman for his company to established customers, consulting them on their future needs and advising them which equipment to install. Taking into account the competition from ever-hungry rivals, this can be a very responsible job indeed.

All-Rounders Needed

It's not surprising that computer systems companies have had some difficulty getting enough engineers of the calibre they want, even from among college leavers (or school leavers) with the right technical background. This is the reason why five major computer systems companies have banded together with a technical college of good repute, the Polytechnic of Central London (PCL) to devise a full-time, two-year course in computer technology which not only leads to a TEC (Technical Education Council) Higher Diploma, but is tailored specifically to the needs of the kind of company involved, and is more

Helen Armstrong

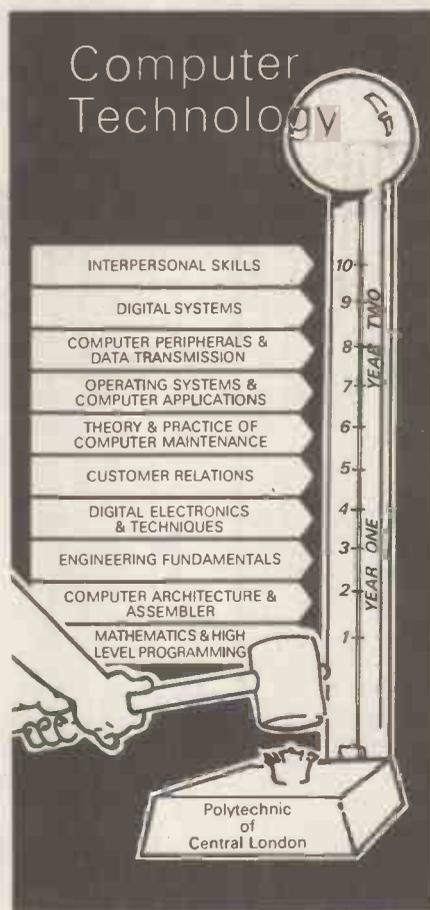

broadly-based than most technical courses.

The five companies involved are Data General, who specialise in broad, compatible product lines from micro-processors to multi-processor systems, plus peripherals; Data Logic, who deal in hardware, consultancy and customer service; the Digital Equipment Corporation, who invented the minicomputer, Harris Communication and Information Processing, who produce advanced equipment for information technology, and Hewlett Packard, a major computer and instrumentation manufacturer.

Hewlett Packard is one of the world's biggest electronics companies, and their Computer Systems side, which they developed comparatively recently, is their fastest-growing and principal

market area now, with 56% computer products.

World sales in 1982 well exceeded four billion dollars, (£169 million pounds in the UK) and there are 1300 Sales and Service employees in the UK, out of more than 67,000 employees worldwide. They are well known in their fields for measuring instruments, and medical electronics, but their computer products belong in the mainframe and minicomputer class, with desktop and realtime technical computers, business computers, and factory automation systems, word processing and a personal computer aimed at businessmen. Their pride and joy is the desktop-sized HP9000, which has the capacity of a 32 bit mainframe and is based on their custom NMOS III microprocessor.

Difficult Choice

While we're on the subject of careers in electronics, Hewlett Packard was formed in California in 1939 by Bill Hewlett and Dave Packard — in Packard Sr.'s garage — with a new form of audio oscillator designed by the partners. Great oaks from little acorns — but that's another story.

Mike Faithfull, an electronics engineer of long experience both outside and inside Hewlett Packard, spoke to Hobby Electronics both about the PCL course, and generally about entry into the many fields of electronics embraced by a large engineering concern.

As well as being an electronics man, Mike is also responsible for interviewing candidates for the PCL course on behalf of Hewlett Packard — one of a panel of assessors representing the five companies involved.

"The main problem in selecting people has been the combination of skills needed. Even the initial screening can be tricky, because PCL are used to selecting people by their academic achievements. That, and the fact that most applicants are very young. Youngsters change a lot in two years. You have to be able to spot a Customer Engineer in his unfledged state!"

There are, of course, minimum academic qualifications required. Candidates should have obtained (or expect to obtain) four GCE passes, including one at A level, in a mathematical or physical science subject, and

an O level in English. Equivalent qualifications from TEC, CGLI, OND or ONC are also considered. Once the applications have been screened, applicants are interviewed by the selection panel. Each successful applicant will be sponsored specifically by one of the sponsoring companies.

Students on the course, as well as their local authority grant, get a bursary of over £600 from their sponsor, as well as employment by the sponsoring firm during the long vacation at around £350 a month (which is tax free for anyone with normal student status), giving a real taste of practical working experience. It's also an opportunity for the trainee to work in different departments of the sponsoring company and see how the whole show runs.

Success Rate

Employment is not actually guaranteed at the end of the course, but Mike made it sound as if the trainees have to try quite hard in order to fail. "We have a better than 90% success rate" he says. "I'm astounded, when you look at the difficulty in selecting raw recruits." Nor do the sponsors have a cast of thousands to choose from: although they advertise in the press and approach local careers offices, they only just made their quota of students this year. This is less because the students they are looking for are rare creatures (although they are) than because conventional academic selection is geared more to qualifications and less to the right mix of technical aptitude and personality.

However, where a likely applicant doesn't have the required qualifications, Hewlett Packard is sometimes prepared to offer in-house training for two years, along with day release to take a TEC course, before the trainee goes out into the field. This is not commonplace in computer engineering, although it's not uncommon in other fields of electronics. As Mike explained, "Computers are just too big." Other types of equipment can be brought back and serviced in the company workshops, allowing an even workflow and time enough to allow day release. Computers need to be serviced on site — and immediately, or sooner — so that the service force needs to be constantly on call.

But Hewlett Packard's swift expansion on the computer side has led them to regard good customer engineers as an investment. Before the PCL course was devised, there was no standard training for customer engineers, and companies relied on attracting experienced engineers from their rivals — or poaching, as it is known in the trade! But this 'free exchange of talent' can no longer keep up with demand.

Casting an eye down the course's subject list is instructive: Mathematics and High Level Programming, Computer Architecture and Assembler, Engineering Fundamentals and Digital Electronics and Techniques are followed by Customer Relations; Theory and Practice of Computer Maintenance,



Students at the Polytechnic of Central London: computer engineering calls for the ability to unravel the mysteries of the computer both through its own language and through the hardware itself.

Operating Systems and Computer Applications, Computer Peripherals and Data Transmission, and Digital Systems are followed by Interpersonal Skills. Definitely, the candidates' ability, or potential ability, to present themselves positively, and communicate well is an important factor in selection. Mike Faithfull adds that interpersonal skills are highly rated by computer companies, but, in his opinion, not highly rated enough: he would place their importance at 30% to 70% with engineering skills.

Teamwork

Because the role of the customer engineer involves not only being able to install, maintain, repair, extend and trouble shoot computer systems, but also being able to do so under the nose of the customer, the course emphasises teamwork and the combination of individual and collective efforts from the start.

"There is not the emphasis on individual marks that you expect on a normal academic course" Mike explains. "Obviously individual study is essential, but within the college the work is structured as it would be in a business context. There is both group pressure, and group help. Everyone is on first name terms and has to work together on projects and presentations."

The sponsoring companies don't

remain aloof from the process; senior staff from the Managing Director downwards hold lectures and seminars for their students and pass on the benefit of their first-hand experience in the business — a style of motivating management commonplace in the USA and still uncommon in the UK. Hewlett Packard have found that, given the chance to contribute ideas, use their initiative and take responsibility, employees are more involved in their work, and happier (not to say more productive) for it.

Says Mike "We're looking for leaders rather than followers" — but he has no rigid way of defining the right applicant. Attention to detail — a businesslike style of dress, the ability to pay attention to and show an interest in the panel's questions, and express himself well in return, being firm without being aggressive and polite without being timid — are some of the bald character traits which a successful candidate might show, but Mike admits that it is 'gut reaction' which decides the final choice. This is the more important as successful students could well graduate from customer engineering to management or more specialised engineering, and the selection panel has this prospect in mind.

So much for the 'personality' aspects of customer engineering; what about the engineering? The academic qualifications are fairly basic, less than would be needed for, say, a university course

in engineering, and a comprehensive education in computer engineering is given at the Polytechnic. So what divides one candidate from another at selection stage? "They need a feel for practical things" says Mike. "We're looking for people who have a strong amateur interest in practical things: electronics, car mechanics, house wiring, amateur radio, — people who can make things work. Some people think we must be looking for people who have ZX81s and know a bit of BASIC — but this has very little relevance to hardware."

Mike has reason to appreciate practical ability with electronics. Starting from a hobby interest in electronics, Mike took the decision to work at something he enjoyed, and worked his way up from mechanical assembly ("I knew how to solder") via prototype wiring and R&D at British Aerospace (he worked on Concorde and is proud of the fact that his 'bits' are still part of the design) to Hewlett Packard while still under thirty. He reckons that five years' practical experience in industry — for the person who is attentive and watches out for opportunity — is as effective as five years' study but "The piece of paper is always worth having if possible."

No Time Like The Present

Mike believes that the present is a very good time for anyone wishing to work in computer engineering to get into the Customer Engineer side. The industry is expanding very fast, and a good supply of skilled people is needed to get the machinery up and running. In a few years, with servicing techniques more automated and standardised, the demand for skilled troubleshooters will have shrunk considerably, and the field will be carved up among technicians out on the road servicing and replacing modules, and a smaller backup force of highly skilled customer engineers for the real problems. Today's customer engineers are looking forward to a future where their versatility will open doors into management, Research and Development and higher-level computer engineering.

Hewlett Packard also take in graduates from the 'Milk Round', their representatives visiting nineteen universities in 1982 and, again, look for personal as well as academic qualifications. Once accepted, the graduate will be both sponsored out on training courses — IEE classes, for instance — and is encouraged to extend his or her own knowledge and put ideas forward in their field. There are also apprenticeships on the bench electronics side. They seek for, and take in, people from all kinds of sources — local advertising, YTS schemes, Job Centres, schools and colleges, and also employ a fair number of sandwich course students who are not destined for future employment with the company.

One important tribute to their motivational style of management is that engineers who have completed the training course successfully nearly always accept employment with the

company, although not compelled to do so, where some big corporations find themselves losing their trainees after the minimum time contracted, as they go in search of greener pastures or a more congenial atmosphere. And before we leave Hewlett Packard to look at a couple of other companies who employ Customer Engineers, some advice from Mike Faithfull for anyone who has ever applied for a course or a post — or several — and has been unlucky. "Keep trying" he says. "Don't take disappointment personally. If you keep applying, you will find the right place eventually. A lot of failures are simply bad luck; but it does pay to check that your approach has been right."

Other Companies

Another large company which sponsors students in a course which is specifically linked to industry needs is Ferranti Computer Systems. The course which they sponsor at the University College of South Wales at Bangor, along with GEC Marconi Electronics, aims to combine undergraduate study with industrial experience in an integrated four-year course, with a full ten weeks of industrial training during the long vacation — a rather different deal from doing a general arts or science degree!


Sponsored students receive a bursary while on the course, and a salary while working in industry. The course is divided into Engineering Science, Mathematics and Physics for Engineers, and Support Technology; the latter including Production, Commerce and Industry, Quality and Reliability and the appropriately named 'Human Component' course! The whole training, while very comprehensive, is far more specifically aimed at practical requirements than the purely academic, theoretical education offered by normal university courses. Application to this and similar courses is through UCCA in the usual way for a University.

Basic entry requirements for the course are A levels (Grade C or above) in Maths and Physics, plus O levels in English Language and two other subjects, or an ONC, OND, or TEC equivalent.

Ferranti also operate a Graduate Training Scheme of between one and two years for graduate engineers and programmers at their technical training centre in Bracknell — fields fall roughly into Engineering, Programming and Technical Documentation. Training is a combination of on-the-job, and coursework at the centre.

Computer giants IBM recruit both experienced Customer Engineers — often ex-BBC or British Telecom — and untrained applicants with A levels in Maths and Physics or equivalent qualifications. Training takes at least four years, and is a combination of on-the-job and classes; again, as the Customer Engineer is effectively a representative for the company, emphasis is placed on a businesslike approach and ability to communicate, as well as technical skills.

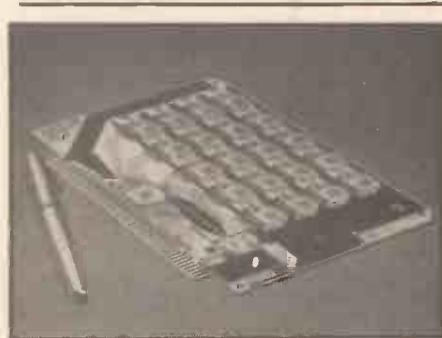Apart from Customer Engineering, IBM have an intake of Higher TEC students for jobs in product testing, test engineering and quality control; much of IBM's equipment is designed by them in-house, including microprocessors, so there are computer-related jobs in



Above: the memory board from the HP9000 desktop computer, compared in size to an ordinary fountain pen. Below: Generating graphics on the HP9000 itself.

production engineering and production management as well. Graduates are recruited on the 'Milk Round' for design and R&D careers, and at the other end of the scale there are jobs in testing and assembly on the manufacturing side — all under the umbrella of one large company.

Allied Business Systems have also switched from recruiting, primarily, experienced customer engineers with GCE or OND/HNC qualifications, to taking on trained but inexperienced engineers, often from TOPS courses. These trainees are given a ten week initial training course in the company's products, and another four weeks later. In other fields — R&D, workshop and production engineering, ABS recruit mostly experienced engineers, through electronics employment agencies. Such agencies are also a source of experienced customer engineers — good customer engineers are still sufficiently scarce for a company like ABS to feel that it is not worth their while advertising through the press; agency recruitment, while it is expensive, can get the right people for the job, quickly. And as always at the business end of industry, people are in demand who have specific skills and, even more important, the know-how in using their skills to get results.

The message is, that if you want to work with computer hardware, it pays to consider training with a specific bias in



One of Hewlett Packard's several R&D and manufacturing sites.

that direction. This can mean seeking either a sponsored course, or a trainee position in a computer systems company. Sources of information are the usual ones: schools and local authority careers offices, advertising in local, national and specialist press, TOPS for older students, and speculative applications to firms in the field. Discerning use of directories and the periodicals rack in your nearest central library is called for. Training for a

specific career is hard work and calls for dedication, but the rewards can be considerably more discernable than those beyond a purely academic university or polytechnic course.

Many thanks to Mike Faithfull and Hewlett Packard for talking to us about the Polytechnic of Central London's Computer Technology course; thanks also to ABS, Ferranti and IBM for supplying further information.

HE

Tomorrow's WORLD Self-Build Radio Controlled Car Kits

NOW AVAILABLE!


Complete Car Kit and Transmitter Kit

Clear build-up instructions included
only **£9.95 + 50p P&P**

Also

Porsche 935 Turbo Kit (2 speed)

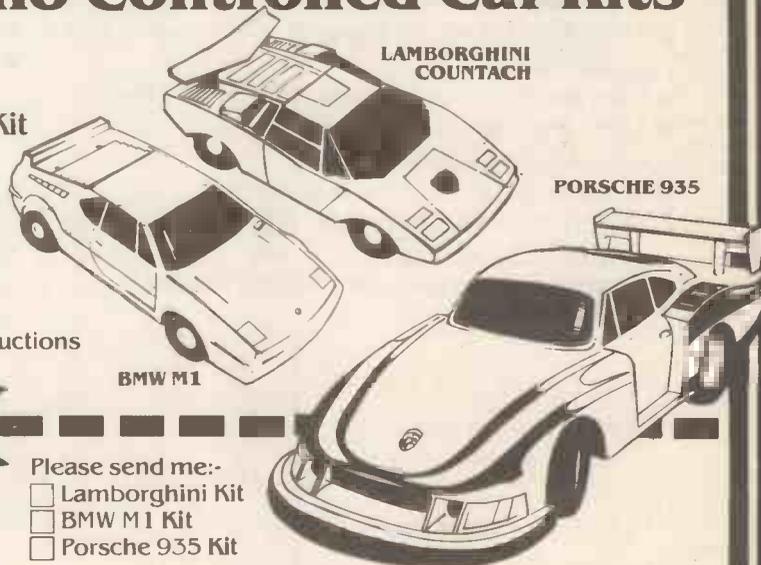Kit includes transmitter and full build-up instructions
only **£17.00 + 50p P&P**



Order now from:-
Tomorrow's World
Car Kit Dept.,
Hadleigh Road Ind. Estate,
Hadleigh Road,
Ipswich, Suffolk.
Tel: Ipswich (0473) 59175




Please send me:-
 Lamborghini Kit
 BMW M1 Kit
 Porsche 935 Kit

Name _____
Address _____

Please allow 14 days delivery in U.K.

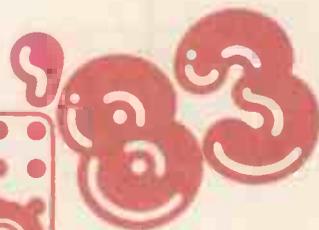If you missed
out on Breadboard
'79, '80, '81 and '82
Now's the time to catch up with



THE PREMIER SHOW FOR THE ELECTRONICS ENTHUSIAST!

Cunard International Exhibition Centre, Cunard Hotel,
Hammersmith, London W6

Improved Venue

We have transferred BREADBOARD to the Cunard Hotel, offering improved facilities to the visitor, including car parking and ease of access by rail, tube and car, all in a modern attractive setting. See below for our arranged reduced hotel/rail fare package to attract enthusiasts from all parts of the country.

Planned Features include

- Lectures: covering aspects of electronics and computing.
- Electronics/Computing Advice Centre.
- Demonstration: electronic organs/synthesisers.
- Holography presentation.
- Practical demonstration: 'How to produce printed circuit boards'.
- Computer Corner - 'Try before you buy'.
- Amateur Radio Action Centre.
- Computer controlled model railway competition.
- Pick of the projects - Demonstration of the best from ELECTRONICS TODAY INTERNATIONAL, HOBBY ELECTRONICS and ELECTRONICS DIGEST.
- Giant TV screen video games.
- Robotic display.

FRIDAY November 25th

10am - 6pm

SATURDAY November 26th

10am - 6pm

SUNDAY November 27th

10am - 4pm

Why not make your visit to Breadboard '83 the most enjoyable yet. At these *prices, why not bring a partner, do your Christmas shopping, have an evening on the town, see the lights, and have a weekend in London!

*see next page

HOLIDAY WEEKEND PACKAGE

- ★ Accommodation in a first class hotel with private bath, direct dial telephone, radio and colour television.
- ★ Return 2nd class rail travel from local British Rail station to London.
- ★ Ticket to Breadboard '83.
- ★ Breakfast at the hotel.
- ★ Prices quoted are inclusive of service and VAT.

Please note this offer closes on 1st November 1983.

| REGION | SINGLE | | TWIN | |
|---|---------|----------|---------|----------|
| | 1 Night | 2 Nights | 1 Night | 2 Nights |
| Beds, Berks, Bucks, Essex, Herts, Kent, Surrey and Gtr London | £29.25 | £54.25 | £47.75 | £84.75 |
| Cambs, Hants, Northants, Oxon, Suffolk, Sussex, Wilts | £32.50 | £57.50 | £57.25 | £94.25 |
| Avon, Derbyshire, Dorset, Glos, Gwent, Herefordshire & Worcs, I.O.W., Leics, Lincs, Norfolk, Notts, Somerset, Staffs, Warwickshire, West Midlands | £35.75 | £59.75 | £59.75 | £96.75 |
| Cheshire, Devon, Glams, Humber, Lancs, Gtr Manchester, Merseyside, Powys, Shropshire, West & South Yorks | £40.25 | £64.25 | £67.50 | £104.50 |
| Cornwall, Cumbria, Dyfed, Glwyd, Gwynedd, North Yorks | £44.25 | £69.25 | £75.00 | £112.00 |
| Borders, Cleveland, Durham, Dumfries & Galloway, Northumberland, Tyne & Wear | £48.50 | £73.50 | £83.25 | £120.25 |
| Central, Lothian, Strathclyde | £51.75 | £76.75 | £89.50 | £126.50 |
| Fife, Tayside | £55.00 | £80.00 | £95.00 | £132.00 |
| Grampian, Highland | £58.25 | £83.25 | £101.50 | £138.50 |

BOOKING FORM

Name:

Address:

..... tel:

Date of arrival: 25th Nov 26th Nov

Number of nights: 1 night 2 nights

Room(s) required: single twin

BR departure station:

Region:

Cheques should be made payable to
ASP Ltd. and sent to ASP Exhibitions,
145 Charing Cross Road, London WC2H 0EE

I enclose cheque value £
OR please debit my Access/B'card number:

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

Signature


FORWARD BIAS

Questions, answers and errata from readers and writers.

The Bat Light (HE June '83)

There were three errors in the Bat Light diagrams: R12 was omitted from the Component Overlay although it was quite clear in the photograph of the assembled Bat Light board; in Figure 1, R10 etc. should be connected direct to V+ and not via C2 and ZD2; in Figure 2, R1 etc. should be connected direct to V+, not via C2 and ZD2, while the positive rail should go to the op-amps.

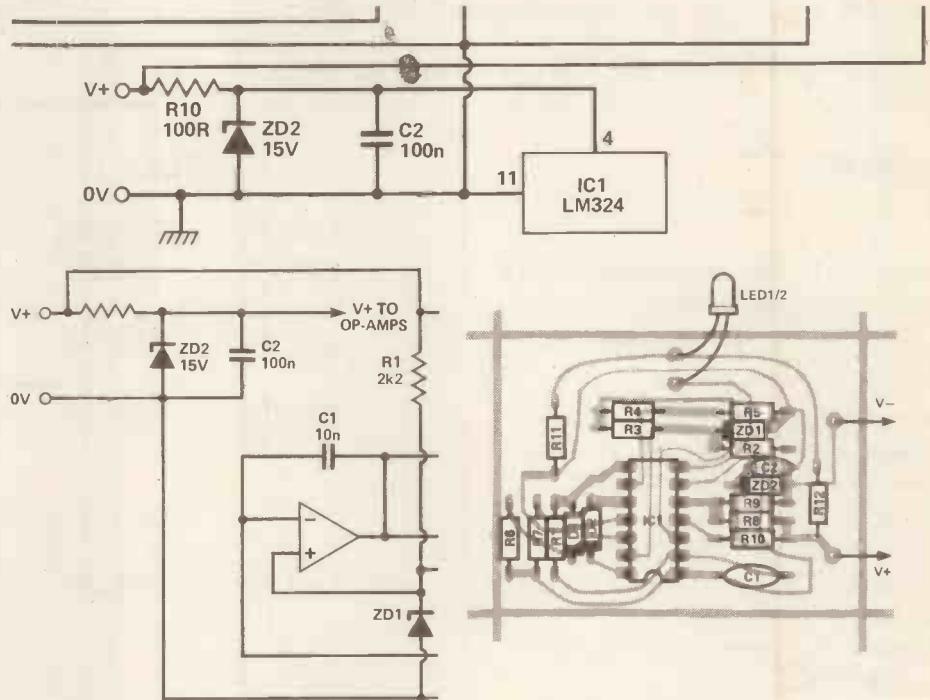However, if the project is constructed according to Figure 3, with R12 added as shown here, the project should work with no problems.



The diagrams show the correct details from Figure 1 (above) and Figure 2 (below left), and the whole of Figure 3, the component overlay, with R12 added.

Did You Notice Our Sneak Preview?

The sharp-eyed among you will have noticed that the **Sound Pressure Level Meter**, as featured on page 17 of the September issue, had two

probes which were not described in the project.

Were they for inserting into the listener's ears? Or for investigating the sub-plughole noise generated by draining bathwater? No. In fact, they belong to the Hi-Voltage Meter, as featured on page 28 of this issue. You weren't going mad. We were.

Tremoleko

Switch Two (SW2) was inadvertently omitted from the PCB overlay drawing of this project. It should connect between the two spare pads (because we left the switch out!) situated between R2 and PR1.

COLLECTED BOOBS

Continuing excerpts from the Hobby Electronics Errata Box.


Tantrum Amplifier (HE October '79)

Figure 1: SW2 is incorrectly drawn; the correction is shown here. The PCB is correct.

Parts List: The push button switches are obtainable from RS Components (via your local components stockist). You need four 2-pole changeover switches, four buttons, and a four-way mounting bracket C2, 102 can be PCB mounting electrolytic tapes.

The text running from p.11 over to p.14 has been scrambled — however, it is all there and the meaning will be clear to anyone reading it through.

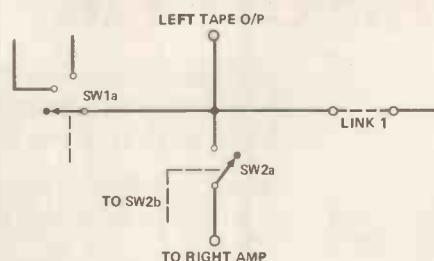Balance Control: Disconnect the ends from C13 and C113 and take them to the sliders of RV3a and RV3b respectively.



Multi Option Siren (HE October '79)

Circuit Diagram: Many people have wondered what happened to RV4. Look carefully at the photograph, and you'll see that lack of space meant that it had to go on the back of the box.

Figure 3: The wire coming from the junction of R12, R3 should be marked SK1 not SW1.

HEBOT I

(HE November '79)

The original HEBOT is now totally extinct, as the chassis and motor are no longer available.

Digi-Die (HE January '80)

Figure 5: The labels IC2 and IC3 on the Overlay should be swapped over. The link from IC2 pin 16 and IC3 pin 14 to the positive supply has gone missing — just wire in a link from these pins to the pad that goes to the battery positive (junction of R1 and R2).

Short Circuits: Noise Gate (HE January '80)

Circuit Diagram: Q1 is a P-channel FET as shown, and not N-channel as stated in the text.

HE

ADDITIONS TO OUR LIST

RADIO MOBILE CAR RADIO SPEAKERS

9" x 4" 4 ohm 5 watt — £1.70, 6" x 4" 3 ohm 4 watt — £1.35; 6" x 4" 4 ohm 4 watt — £1.15, 6" x 4" 16 ohm 5 watt — £1.15; 5" round 8 ohm 10 watt — £2.30, 6 1/2" round extra thin for door or back shelf. In fact these are only 1 1/2" thick 16 ohm 5 watt — £1.75; 5" round 16 ohm 5 watt chassis size 5 1/4" square (approx.) — £1.15; 5" round 4 ohm 5 watt chassis size 5 1/4" square (approx.) — £1.18; 5" round 4 ohm 6 watt with built in tweeter — £1.15. 9" x 3" 8 ohm £1.15.

IMPORTANT NOTE: The speaker prices above do not include postage but 10 or more speakers are post free — otherwise add £1.50 per order.

STABILISED POWER SUPPLY (Mains Input)

By LAMDA (USA) — Ideal for computer add-ons, d.c. output. Regulated for line volts and load current. Voltage regulation, 1% with input variations up to 20% — load regulation 1% from no load to full load — or full load to no load. Complete in heavy duty case — Models available: 5v - 6A £17.25, 5v - 9A £23, 12v - 1.5A £13.25, 15v - 1.2A £13.25, 24v - 2A £23.

PREPARED APPLIANCE LEADS

Buy these, they will save you time and money. Prices are for small quantities but if you are buying £100 lots or more — halve the prices. Twin circular, white .5mm length 54" — 23p; 3 core circular, white 99" — 1.25mm — 57p; Twin circular black 77" .5mm — 23p; 3 core circular, black 88" .5mm — 35p; 84" .5mm 46p; Twin circular black 114" 1.25mm — 69p. Twin circular white 200" 75 fitted 2 pin continental plug one end — 67p; 3 core circular white 54" .75mm core sizes fitted continental twin pin and earth plug one end and new type 3 flat pin appliance connector at other end — 75p.

MINIATURE TOGGLE SWITCHES

As used on TV cameras and other lightweight equipment. American made by the Arrow Company. Arrow ref. TCH3E Single pole changeover, centre off — 46p. Arrow ref. TSH3PL Single pole changeover PCB mounting — 46p. Arrow ref. TC6M Double pole high inductance, centre off — 69p.

REED RELAY KIT

High inductance coil, moulded to take 4 reeds, operated by three volts DC or 12 mA. Can be used to close 4 circuits, or with the external magnets supplied, you could have two normally open, i.e. two changeovers. An exceptional bargain at 99p for the coil — 4 reeds and 2 magnets.

ROCKER SWITCHES

Standard size fit 11.5 x 28mm cut out. Single pole on/off — 23p; Single pole changeover 28p; Single pole changeover with centre off — 30p; Single pole on/off with neon — 46p, for double width cut out DpSt 36p, DpDt 46p.

NICAD BATTERY CHARGERS

This, although intended to charge button cells, bring leads from the contacts and then it will suit almost any Nicad battery, charge rate approximately 15mA but easy to vary.

MIXER MOTOR

If this had a case around it, it would be a complete mixer as it has a speed control switch giving three changes of main speed and it also has a gear box with two sockets for paddles. Three lower speeds are available from these sockets. £3.45 — post 50p.

LOW VOLTAGE SWITCH

Approx 1 1/2" diameter, the cover unscrews to enable the switch to be fixed and to keep the contacts covered, contacts look capable of up to 10 amps. 23p.

PILOT BULBS

Standard round 11mm 6.5v .3a by Philips. Box of 10 price 50p.

12 volt MOTOR BY SMITHS

Made for use in cars, etc., these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3" dia. They have a good length of 1/4" spindle — Price £3.45. Ditto, but double ended £4.25. Ditto, but permanent magnet £3.75.



EXTRA POWERFUL 12v MOTOR

Made to work battery lawnmower, this probably develops up to 1/2 hp., so it could be used to power a go-kart or to drive a compressor, etc. etc. £7.95 + £1.50 post. [This is easily reversible with our reversing switch — Price £11.15].

MAINS MOTORS

We have very large stocks of motors from 2 watts to 1/2 hp. Most at a price well below cost, let us know your requirements. Some new ones just arrived. 67 R.P.M. Motor: 1/10 hp. reversible mains operated split phase motor with gear box — shaft fitted with chain sprocket £11.50 plus £2 post. 100 R.P.M. Motor: 1/6 hp. Mains driven reversible motor with gear box, 1/2" shaft from gear box — Very powerful £16.50 plus £3 post.

BALANCED MOTOR: Disc or tape drive motor 1500rpm reversible

— mains operated. 3" dia 2 1/2" long with good length 3/8" spindle £4.60 plus 80p post.

CROSSOVER NETWORKS

2-way: 4 or 8 ohm impedance — power input up to 25W, crossover frequency 2kHz with wiring diag. 87p each. 3-way: 4 or 8 ohm — power input up to 60W, crossovers at 700kHz and 3500kHz with wiring diagram. £1.15.

— BARGAIN OF THE YEAR —

The AMSTRAD Stereo Tuner.

This ready assembled unit is the ideal tuner for a music centre or an amplifier, it can also be quickly made into a personal stereo radio — easy to carry about and which will give you superb reception.

Other uses are as a "get you to sleep radio", you could even take it with you to use in the lounge when the rest of the family want to view programmes in which you are not interested. You can listen to some music instead.

Some of the features are: long wave band 115 — 270 KHz, medium wave band 525 — 1650KHz, FM band 87 — 108MHz, mono, stereo & AFC switchable, tuning meter to give you spot on stereo tuning, optional LED wave band indicator, fully assembled and fully aligned. Full wiring up data showing you how to connect to amplifier or headphones and details of suitable FM aerial (note ferrite rod aerial is included for medium and long wave bands. All made up on very compact board.

Offered at a fraction of its cost: **only £6.00** + £1.50 post + insurance.

THIS MONTH'S SNIP

A PRESTEL UNIT, complete

except for 6 plug-in IC's — so far as we know the unit would work once the missing IC's are fitted. Price: £19.75 + £2.00 Post.



Contains all the items listed below.

VIEWDATA EQUIPMENT

ORACLE VB 100 PCB This is the heart of many viewdata systems, including the Prestel Unit which we are currently selling. This board uses 25 I.C.'s, 5 transistors, 2 crystals and very many other components. It has a TV aerial input and a TV UHF modifier (AZTEC UM 1233). We offer this board, new, unused and complete except for 6 of the 25 I.C.'s at £5.75. The plug in holders for the missing I.C.'s are on the board wired ready to receive them.

MINIKEY SERIES KL This is an American made membrane keyboard with silver contacts as used on Prestel to dial into the British Telecom phone system. It is really miniature, only 60mm x 65mm x 5mm thick. It has 16 press buttons, giving standard 0-9 numbers and ABCD facilities. There are two other buttons engraved asterisks. This is an extremely well made board. £4.60.

TELEPHONE LINE TERMINATION UNIT As used with Prestel but undoubtedly suitable for other applications. Important components are phone line isolation transformer and 3 Clare Reed Relays. All mounted on a pcb with I.C. and other components P.C.B. size approximately 7" x 1 1/2" — £3.45.

VOLTAGE STABILISED POWER SUPPLY As used with Prestel this has a mains input transformer with a 13v 0-13v 20 watt mains transformer. Rectifiers and semi-conductors all mounted on P.C.B. size approximately 4 1/2" x 2". The stabilised DC output from this is -27v - 12v - 0 +12v +27v. Price £4.60.

INSTRUMENT CASE As used with the Prestel unit this comprises an all chassis and a moulded front plastic cover secured to the chassis by self-tapping screws. Overall size approx 12" x 10" x 2 1/2". On the front is fitted the minkeyboard as described above and although originally intended for Prestel, this case should have other uses including telephone answering machine, etc. Price £5.75 + £1.50 post.

X-RAY EQUIPMENT

Beautifully made by the American GEC Company. We have a whole range of spares, all unused. **X-RAY TROLLEY** — This could be motorised, mains or battery driven with self retractable flex lead, so it could be used for carrying other mains operated equipment which need to be manoeuvred easily in a relatively confined space. Switching and breaking is done from the handle and there is ample room and capacity for heavy transformers and smaller equipment. The overall size of this trolley is approx. 3' x 2' x 3 1/2'. Price £69. **X-RAY HEAD** This comprises the x-ray tube in a radiation proof housing with plug in lead connectors. The tube enclosed in the housing is a hospital size tube and unused and new. Price £69. **EHT TRANSFORMER & RECTIFIER UNIT** We estimate that the output voltage of this is probably 30 or 40 KV. Completely enclosed in an oil filled container, size 13" x 14" x 15". There are four rectifier sections, each using 20 EHT rectifiers connected in series these plug in for ease of replacement. The unit is powered by a 600 cycle supply. Price £69. **600 CYCLE SUPPLY UNIT** Mains operated through a step down transformer, this contains all the electronic components to operate the equipment. Price £57.50.

MINI MONO AMP on p.c.b., size 4" x 2" (app.)

Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.



50 THINGS YOU CAN MAKE

Things you can make include Multi range meter, Low ohms tester, A.c. amps meter, Alarm clock, Soldering Iron minder, Two way telephone, Memory jogger, Live line tester, Continuity checker, etc. etc., and you will still have hundreds of parts for future projects. Our 10kg parcel contains not less than 1,000 items — panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermostats, coils, condensers, resistors, neons, earphone/microphones, nicad charger, power unit, multi-turn pots and notes on the 50 projects.

YOURS FOR ONLY £11.50 plus £3.00 post.

MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument, Jewelled bearings - 2000 o.p.v. mirrored scale. 11 Instant range measures:



DC volts 10, 50, 250, 1000, AC volts 10, 50, 250, 1000, DC amps 0 — 100 mA.

Continuity and resistance 0 — 1 meg ohms in two ranges. Complete with test leads and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 60p post and insurance.

FREE Amps range kit to enable you to read DC current from 0 — 10 amps, directly on the 0 — 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

J. BULL (Electrical) Ltd.

(Dept. HE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. **Established 30 YEARS**

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £12 add 60p service charge. Monthly account orders accepted from schools and public companies. Access B/E card orders accepted day or night. Haywards Heath (0444) 454883. Bulk orders: write for quote. Shop open 9.00 — 5.30, mon to Fri, not Saturday.

EXTRACTOR FANS

Mains operated — ex-computer.

Woods extractor

5" — £3.75, Post £1.25

the retail price

5" Plannair extractor

£6.50, Post £1.25.

4" x 4" Muffin 115v.

£4.50, Post 75p.

4" x 4" Muffin 230v.

£5.75, Post 75p.

9" American made

£11.50, post £2.00.

12 volt 6 1/4" extractor

£6.90, post £1.50.



AUTO & ISOLATION TRANSFORMERS

2 KW ISOLATION TRANSFORMER 230v in 230v out with tapped primary and secondary, facilitates any voltage changes that might be needed. This is a very heavy transformer, American made but not encased. The terminals are along the top on insulation board panels. Both primary and secondary are split so this could also be used as a 2KW Isolation step down transformer. £57.50. Carriage at cost depending upon the distance. This is approx half the retail price.

2 KW AUTO TRANSFORMER Similar type of transformer to the above but has only the one winding. £28.50 + carriage £3.

1 KW ISOLATED AUTO TRANSFORMER It is not generally realised that many of the American made tools intended for 115v, if used on building sites and similar damp conditions must be isolated from the mains for safety reasons, as in many cases the insulation of this equipment is not good enough for 230v. We have American made isolated auto transformers, completely enclosed in sheet metal case with carrying handle with 230v lead and 110v American type plug. Price £46.00 + £4.50 post.

300 WATT AUTO TRANSFORMER completely encased, lead for the 230v input, American type plug for the 115v output £6.90 + £1.50 post.

100 WATT AUTO TRANSFORMER not enclosed terminals, output primary with tappings for voltage adjustments. Made to rigid specification for the GPO £4.60 + £1 post.

AMERICAN 2 PIN FLAT SOCKETS for use with these auto transformers — £2.30 each.

3M FACSIMILE EQUIPMENT

— send or receive a document in 4 minutes. This equipment is used for sending letters and almost any data through the telephone system — "Mail by Phone". The machines we have are the 3M 600BB with autofeed complete with ansafonettes and connector box. We have three sets of the equipment, it is not old, in fact it was used only for about a year (1980-81), believed to be in good order and certainly in a very good condition — cost new over £10,000. We will accept £500 the lot — buyer to examine and take away on an "as seen" basis.



VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case, but we can supply a plastic case — £1.75. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder — a complete mains operated kit, case included. **£11.95 plus £2.00 post.**

OTHER POPULAR PROJECTS

- R C Bridge Kit £9.95
- 3 Channel Sound to Light — with fully prepared metal case. £14.95
- Ditto — made up £25.00
- Big Ear, listen through walls £9.50
- Robot controller — receiver/transmitter £9.50
- Ignition kit — helps starting, saves petrol, improves performance £13.95
- Silent sentinel Ultra Sonic Transmitter and receiver £9.50
- Car Light 'left on' alarm £3.50
- Secret switch — fools friends and enemies alike £1.95
- 3 — 30v Variable Power Supply £13.80
- 2 Short & Medium wave Crystal Radio £3.99
- 3v to 16v Mains Power Supply Kit £1.95
- Light Chaser — three modes £17.50
- Mullard Unilux HiFi stereo amplifier with speakers £16.75
- Radio stethoscope — fault finding aid £4.80
- Mug stop — emits piercing squawk £7.50
- Morse Trainer — complete with key £2.99
- Drill control kit £3.95
- Drill control kit — made up £6.95
- Interrupted beam kit £2.50
- Transmitter surveillance kit £2.30
- Radio Mike £6.90
- FM receiver kit — for surveillance or normal FM £3.50
- Seat Belt reminder £3.00
- Car Starter Charger Kit £14.00
- Soil heater for plants and seeds £16.50
- Insulation Tester — electronic megger £7.95
- Battery shaver or fluorescent from 12v £6.90
- Matchbox Radio — receives Medium Wave £2.96
- Mixer Pre-amp — disco special with case £16.00
- Aerial Rotator — mains operated £29.50
- Aerial direction indicator £6.50
- 40 watt amp — hifi 20hz — 20kHz £9.50
- Microvolt multiplier — measure very low currents with ordinary multimeter £3.95
- Pure Sine Wave Generator £5.75
- Linear Power output meter £11.50
- 115 Watt Amplifier 5Hz 25kHz £13.50
- Power supply for one or two 115 watt amps £17.50
- Stereo Bass Booster, most items £8.95

Hi-Voltage Meter


Lightning from a clear sky? Check it out with the HE Hi-Volt Meter.

James E. Aman

DANGER 10,000 VOLTS!! But now this meter tames the kilovolts and brings high voltage measurement easily into the range of the experimenter's pocketbook. If you've been left "holding the probe", and getting nowhere because of the 1kV limit on your ordinary voltmeter, then this is the logical expansion to your compliment of bench test gear. And at around £15, one really can't afford not to build this project, if only to "save the bacon" of your digitally delicate devices.

High Voltage Circuit

The meter uses (now) readily available ultra-high value thick film resistors to make up the bulk of a resistor chain forming voltage divider. The measuring device is a MOSFET input op-amp which sports the facility of being able to sense voltages below the negative supply rail, making dual supplies unnecessary. Thus with the extremely high input resistance of 1000MR coupled to the FET op-amp we realize a circuit capable of monitoring up to 10 kilovolts without significantly affecting the circuit under test. When metering 10kV, an input impedance of 500 megohms draws 20uA which suggests that a resistor of a quarter watt is a bit "near the knuckle". Increasing the input impedance to 1000 meg ohms and using 0.4 watt resistors was more acceptable. Resistors 1-10 reduce the voltage across R11 to a manageable level, which is then sensed by IC1, and produced at its output to drive the current meter. IC1 is connected as a voltage follower, which presents the same voltage at the output as it sees across R11 (its input). It therefore is acting as an impedance transformer and supplies current to the 100uA

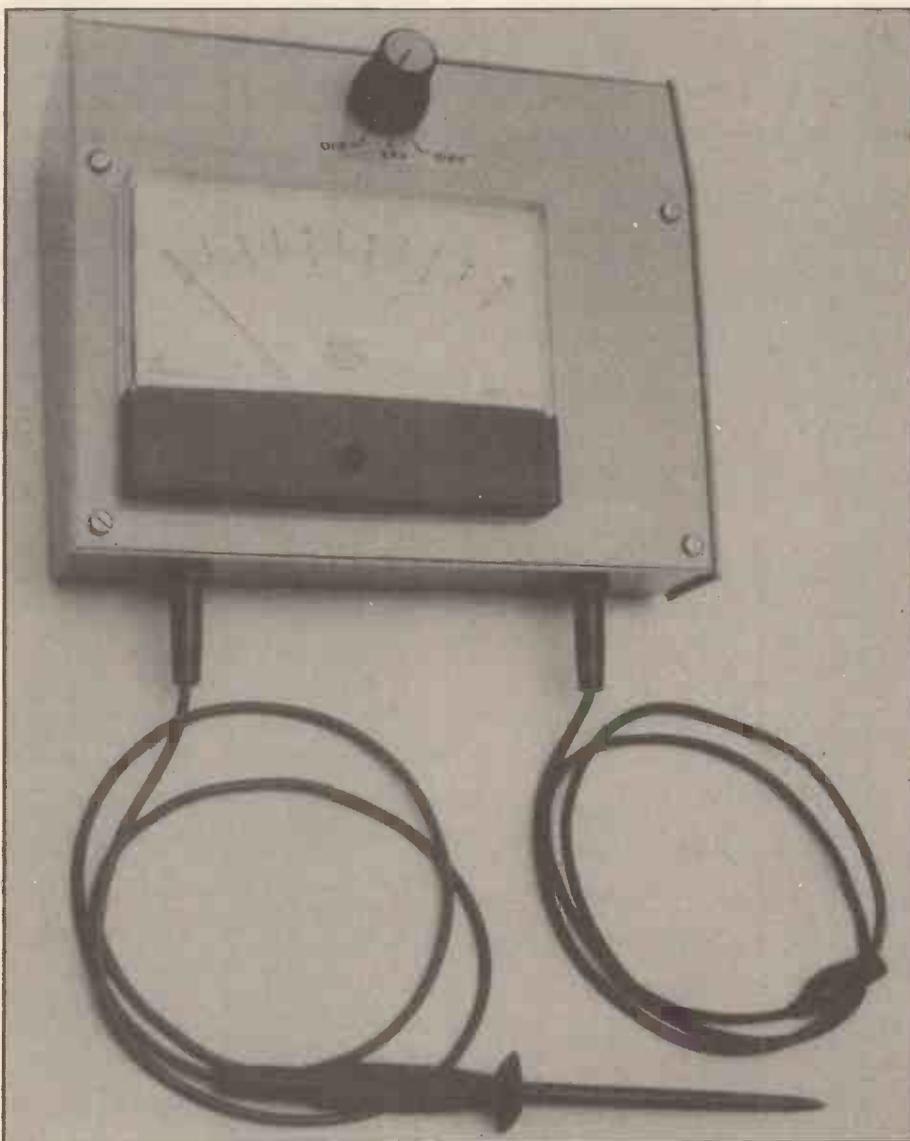

Parts List

RESISTORS

(All 1/4 watt 5% unless noted)

- R1-10 100M 0.4W
- R11 100k 1%
- R12 4k7
- R13 2k2

POTENTIOMETERS

- RV1 10k 1in
- PR1 10k horiz
preset

- PR2 5k horiz
preset

CAPACITORS

- C1 100n
disc ceramic
- C2 1000u 16V
radial electro

SEMICONDUCTORS

- IC1 CA3140
MOSFET op-amp
- ZD1, 2 BCY88C3V3

MISCELLANEOUS

- M1 panel meter
100uA
- SW1 2-pole 6-way
rotary
- PCB; case (see Buylines); HV probe
and leads (see text); PP3 battery and
clip; knob, wire, nuts and bolts etc.

BUYLINES page 32

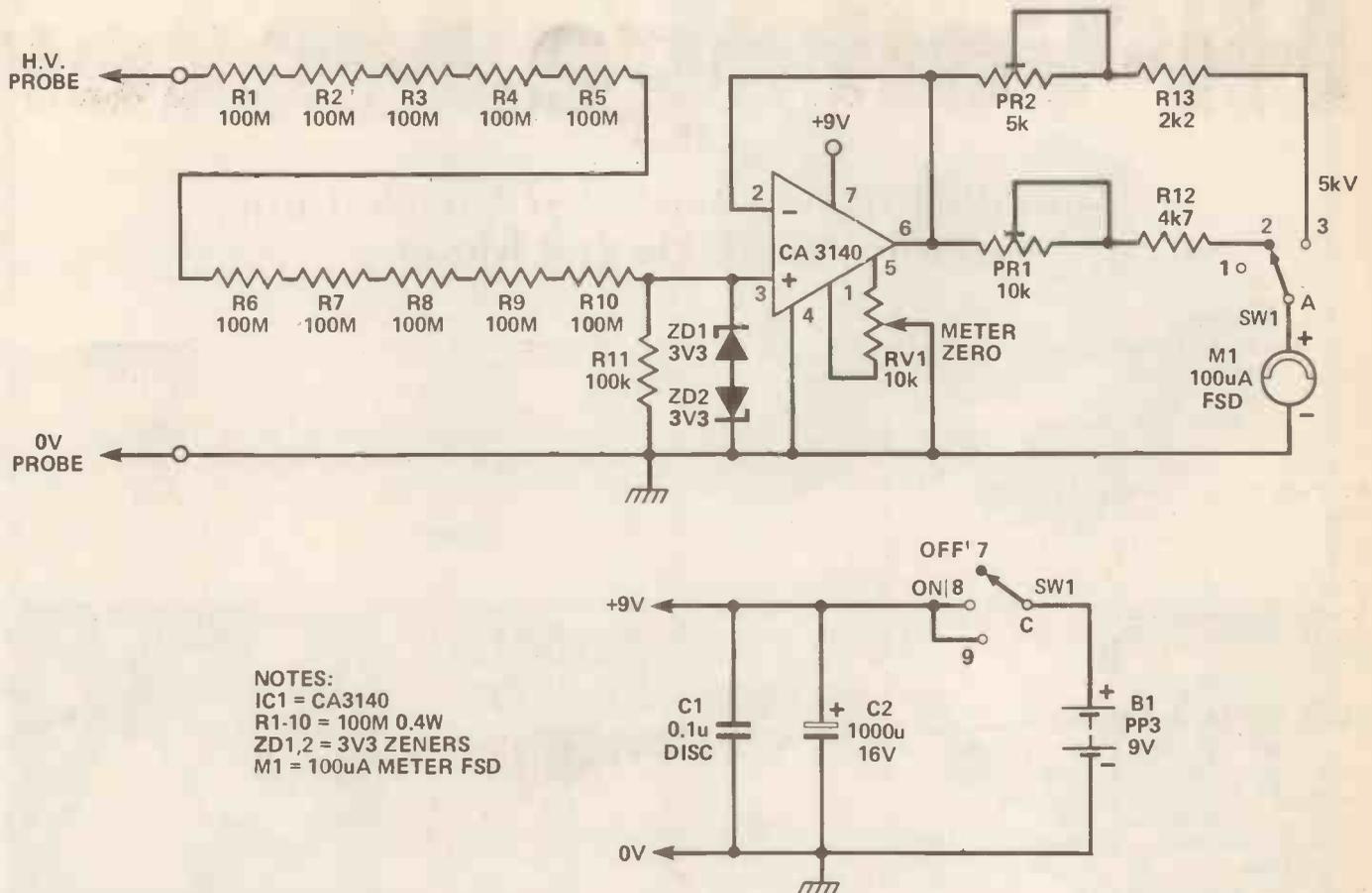


Figure 1. The circuit, in two parts.


meter. This is connected with a series resistor (adjustable for calibration) making it into a voltage meter, reading in kilovolts.

Calibration

The calibration procedure is sweet and simple. First zero the meter on the 5kV range, with the probes shorted together, via R16 on the front

panel. On the 10kV range simply connect 1V DC across R11 (negative to earth) and adjust PR1 to a full scale reading of 10kV. Then, on the 5kV range connect 0V5 DC across R11 and adjust PR2 for a full scale reading of 5kV. The meter face should be scaled 0-10kV in 1kV steps across the top of the meter and 0-5kV in 1kV steps across the bottom of these same gradations.

Figure 2. The simple component layout.

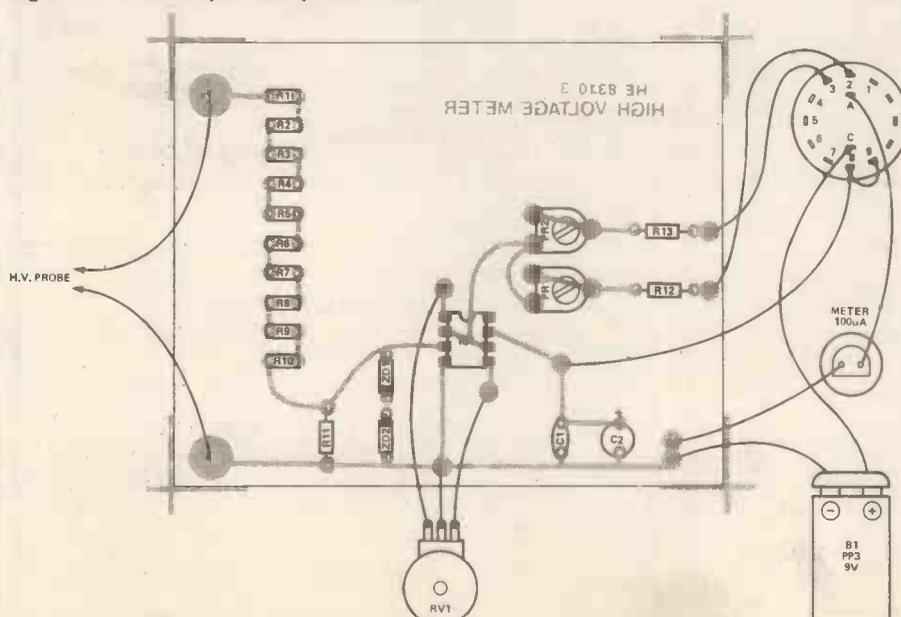


Construction

Construction of this project should pose no real problems. The high impedance resistor chain should be soldered and trimmed, leaving no sharp points on the leads. The meter-zero pot should be mounted on the front panel and the meter should be wired between the wiper (pin A) of SW1 and earth, as shown in the circuit diagram. Care should be used when installing IC1, as it is static sensitive.

Probe connections can be made through the case either by means of 4mm banana plugs and sockets or by (in the interest of safety) feeding the probe wires directly through matching holes in the case. In the latter case the leads should be knotted on the inside of the case, as a strain relief, and held in place with Superglue.


A HV probe with a rubber-booted crocodile clip may be used instead. The experimenter may prefer to test the HV source by first clipping the meter to the points under test and then switching on, but make sure power is *off* before approaching high voltage points! This method, used with sensible caution, can prove to be a safer and a less nerve racking procedure, since the probe isn't at hand during "power on" testing.

AMPLIFIERS

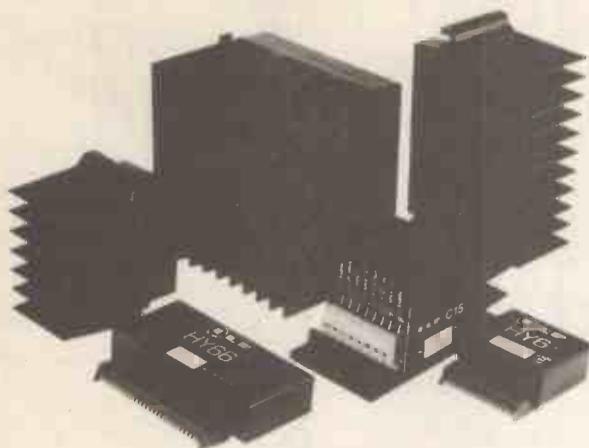

Over the last few years we have received feedback via the general public and industry that our products are from Taiwan, Singapore, Japan, etc... ILP are one of the few 'All British' electronics Companies manufacturing their own products in the United Kingdom. We have proved that we can compete in the world market during the past 12 years and currently export in excess of 60% of our production to over twenty different countries - including USA, Australia and Hong Kong. At the same time we are able to invest in research and development for the future, assuring security for the personnel, directly and indirectly, employed within the UK. We feel very proud of all this and hope you can reap some of our success.

I.L.Potts - Chairman

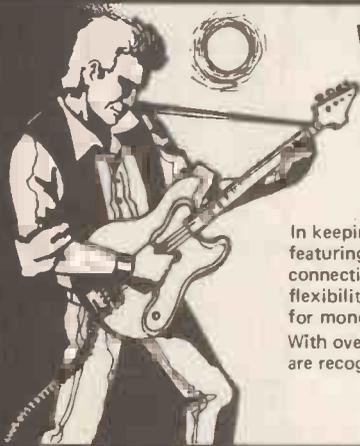

WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

| Module Number | Output Power Watts rms | Load Impedance Ω | DISTORTION | | Supply Voltage Typ | Size mm | WT gms | Price inc. VAT |
|---------------|------------------------|-------------------------|--------------------|-----------------------------|--------------------|----------------|--------|----------------|
| | | | T.H.D. Typ at 1KHz | I.M.D. Typ at 60Hz/7KHz 4:1 | | | | |
| HY30 | 15 | 4-8 | 0.015% | <0.006% | ± 18 | 76 x 68 x 40 | 240 | £8.40 |
| HY60 | 30 | 4-8 | 0.015% | <0.006% | ± 25 | 76 x 68 x 40 | 240 | £9.55 |
| HY6060 | 30 + 30 | 4-8 | 0.015% | <0.006% | ± 25 | 120 x 78 x 40 | 420 | £18.69 |
| HY124 | 60 | 4 | 0.01% | <0.006% | ± 26 | 120 x 78 x 40 | 410 | £20.75 |
| HY128 | 60 | 8 | 0.01% | <0.006% | ± 35 | 120 x 78 x 40 | 410 | £20.75 |
| HY244 | 120 | 4 | 0.01% | <0.006% | ± 35 | 120 x 78 x 50 | 520 | £25.47 |
| HY248 | 120 | 8 | 0.01% | <0.006% | ± 50 | 120 x 78 x 50 | 520 | £25.47 |
| HY364 | 180 | 4 | 0.01% | <0.006% | ± 45 | 120 x 78 x 100 | 1030 | £38.41 |
| HY368 | 180 | 8 | 0.01% | <0.006% | ± 60 | 120 x 78 x 100 | 1030 | £38.41 |

Protection: Full load line. Slew Rate: 15v/ μ s. Rise time: 5 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz > 400.

PRE-AMP SYSTEMS

| Module Number | Module | Functions | Current Required | Price inc. VAT |
|---------------|----------------|--|------------------|----------------|
| HY6 | Mono pre amp | Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble | 10mA | £7.60 |
| HY66 | Stereo pre amp | Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance | 20mA | £14.32 |
| HY73 | Guitar pre amp | Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix | 20mA | £15.36 |
| HY78 | Stereo pre amp | As HY66 less tone controls | 20mA | £14.20 |

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

| Model Number | For Use With | Price inc. VAT |
|--------------|------------------------------------|----------------|
| PSU 21X | 1 or 2 HY30 | £11.93 |
| PSU 41X | 1 or 2 HY60, 1 x HY6060, 1 x HY124 | £13.83 |
| PSU 42X | 1 x HY128 | £15.90 |
| PSU 43X | 1 x MOS128 | £16.70 |
| PSU 51X | 2 x HY128, 1 x HY244 | £17.07 |

| Model Number | For Use With | Price inc. VAT |
|--------------|--------------|----------------|
| PSU 52X | 2 x HY124 | £17.07 |
| PSU 53X | 2 x MOS128 | £17.86 |
| PSU 54X | 1 x HY248 | £17.86 |
| PSU 55X | 1 x MOS248 | £19.62 |
| PSU 71X | 2 x HY244 | £21.75 |

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

| Module Number | Output Power Watts rms | Load Impedance Ω | DISTORTION | | Supply Voltage Typ | Size mm | WT gms | Price inc. VAT |
|---------------|------------------------|-------------------------|--------------------|-----------------------------|--------------------|----------------|--------|----------------|
| | | | T.H.D. Typ at 1KHz | I.M.D. Typ at 60Hz/7KHz 4:1 | | | | |
| MOS128 | 60 | 4-8 | <0.005% | <0.006% | ± 45 | 120 x 78 x 40 | 420 | £30.41 |
| MOS248 | 120 | 4-8 | <0.005% | <0.006% | ± 55 | 120 x 78 x 80 | 850 | £38.86 |
| MOS364 | 180 | 4 | <0.005% | <0.006% | ± 55 | 120 x 78 x 100 | 1025 | £45.54 |

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20v/ μ s. Rise time: 3 μ s. S/N ratio: 100db

Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms

Input impedance: 100K Ω . Damping factor: 100Hz > 400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

£9.14 (inc. VAT)

Robust construction.

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz. T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 80dB. Load Impedance 3 Ω .

Input Sensitivity and impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω .

Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

| Model Number | For Use With | Price inc. VAT |
|--------------|------------------------|----------------|
| PSU 72X | 2 x HY248 | £22.54 |
| PSU 73X | 1 x HY364 | £22.54 |
| PSU 74X | 1 x HY368 | £24.20 |
| PSU 75X | 2 x MOS248, 1 x MOS368 | £24.20 |

TOROIDALS


The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

*Gold service available.
21 days manufacture for urgent deliveries.

*Orders despatched within 7 days of receipt for single or small quantity orders.

*5 year no quibble guarantee.

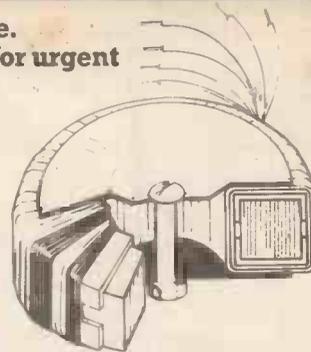

| TYPE | SERIES No | SECONDARY Volts | RMS Current | PRICE | TYPE | SERIES No | SECONDARY Volts | RMS Current | PRICE | TYPE | SERIES No | SECONDARY Volts | RMS Current | PRICE |
|---|---|---|--|---|---|---|---|--|--|---|--|--|---|---|
| 15 VA 62 x 34mm 0.35Kg Regulation 19% | 0x010 0x011 0x012 0x013 0x014 0x015 0x016 0x017 | 6+6 9+9 12+12 15+15 18+18 22+22 25+25 30+30 | 1.25 0.83 0.63 0.50 0.42 0.34 0.30 0.25 | £5.12 + p & p £0.78 + VAT £0.89 TOTAL £6.79 | 120 VA 90 x 40mm 1.2Kg Regulation 11% | 4x010 4x011 4x012 4x013 4x014 4x015 4x016 4x017 4x018 4x028 4x029 4x030 | 6+6 9+9 12+12 15+15 18+18 22+22 25+25 30+30 35+35 110 220 240 | 10.00 6.66 5.00 4.00 3.33 2.72 2.40 2.00 1.71 1.09 0.54 0.50 | £7.42 + p & p £1.72 + VAT £1.37 TOTAL £10.51 | 300 VA 110 x 50mm 2.6Kg Regulation 6% | 7x013 7x014 7x015 7x016 7x017 7x018 7x026 7x025 7x033 7x028 7x029 7x030 | 15+15 18+18 22+22 25+25 30+30 35+35 40+40 45+45 50+50 110 220 240 | 10.00 8.33 6.82 6.00 5.00 4.28 3.75 3.33 3.00 2.72 1.36 1.25 | £10.88 + p & p £2.05 + VAT £1.94 TOTAL £14.87 |
| (encased in ABS plastic) | | | | | 160 VA 110 x 40mm 1.8Kg Regulation 8% | 5x011 5x012 5x013 5x014 5x015 5x016 5x017 5x018 5x026 5x028 5x029 5x030 | 9+9 12+12 15+15 18+18 22+22 25+25 30+30 35+35 40+40 110 220 240 | 8.89 6.66 5.33 4.44 3.63 3.20 2.66 2.28 2.00 1.45 0.72 0.66 | £8.43 + p & p £1.72 + VAT £1.52 TOTAL £11.67 | 500 VA 140 x 60mm 4Kg Regulation 4% | 8x016 8x017 8x018 8x026 8x025 8x033 8x042 8x028 8x029 8x030 | 25+25 30+30 35+35 40+40 45+45 50+50 55+55 110 220 240 | 10.00 8.33 7.14 6.25 5.55 5.00 4.54 4.54 2.27 2.08 | £14.38 + p & p £2.40 + VAT £2.52 TOTAL £19.30 |
| 30 VA 70 x 30mm 0.45Kg Regulation 18% | 1x010 1x011 1x012 1x013 1x014 1x015 1x016 1x017 | 6+6 9+9 12+12 15+15 18+18 22+22 25+25 30+30 | 2.50 1.66 1.25 1.00 0.83 0.68 0.60 0.50 | £5.49 + p & p £1.10 + VAT £0.99 TOTAL £7.58 | 225 VA 110 x 45mm 2.2Kg Regulation 7% | 6x012 6x013 6x014 6x015 6x016 6x017 6x018 6x026 6x025 6x033 6x028 6x029 6x030 | 12+12 15+15 18+18 22+22 25+25 30+30 35+35 40+40 45+45 50+50 110 220 240 | 9.38 7.50 6.25 5.11 4.50 3.75 3.21 2.81 2.50 2.25 2.04 1.02 0.93 | £9.81 + p & p £2.05 + VAT £1.78 TOTAL £13.64 | 625 VA 140 x 75mm 5Kg Regulation 4% | 9x017 9x018 9x026 9x025 9x033 9x042 9x028 9x029 9x030 | 30+30 35+35 40+40 45+45 50+50 55+55 110 220 240 | 10.41 8.92 7.81 6.94 6.25 5.68 5.68 2.84 2.60 | £17.12 + p & p £2.55 + VAT £2.95 TOTAL £22.62 |
| 50 VA 80 x 35mm 0.9Kg Regulation 13% | 2x010 2x011 2x012 2x013 2x014 2x015 2x016 2x017 2x028 2x029 2x030 | 6+6 9+9 12+12 15+15 18+18 22+22 25+25 30+30 110 220 240 | 4.16 2.77 2.08 1.66 1.38 1.13 1.00 0.83 0.45 0.22 0.20 | £6.13 + p & p £1.35 + VAT £1.12 TOTAL £8.60 | 80 VA 90 x 30mm 1Kg Regulation 12% | 3x010 3x011 3x012 3x013 3x014 3x015 3x016 3x017 3x028 3x029 3x030 | 6+6 9+9 12+12 15+15 18+18 22+22 25+25 30+30 110 220 240 | 6.64 4.44 3.33 2.66 2.22 1.81 1.60 1.33 0.72 0.36 0.33 | £6.66 + p & p £1.72 + VAT £1.26 TOTAL £9.64 | ALSO AVAILABLE Sizes up to and including 5KVA are manufactured to order. | | | | |

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number

For 240V primary (UK) insert "2" in place of "X" in type number.

Also available at Electrovalue, Maplin

NEW PRODUCTS

HYBRID REGULATOR MODULES

The HR314 and HR614 regulated power supplies provide a constant 13.8 volt d.c. output at up to 3 Amp or 6 Amp respectively. The modules are encapsulated to an integral heatsink and are fully short circuit protected making them suitable for home or bench running of CB, car stereos or any 12 volt d.c. equipment required for many hobby or professional applications.

HR314 £10.23 inc. VAT

HR614 £18.51 inc. VAT

TECHNICAL SPECIFICATIONS

| MODULE | HR314 | HR614 |
|--|-------------------|--------------------|
| Output Voltage | +13.8v ±5% | +13.8v ±5% |
| Output Current | Up to 3A | Up to 6A |
| Current limit (nominal) | 3.5A approx | 7A approx |
| Maximum Input Voltage | +30v | +30v |
| Minimum Input Voltage | +16v | +16v |
| Maximum Input Voltage for nominal output current | +20v | +20v |
| Maximum output current at 30v input | 1.8A approx | 3.5A approx |
| Output ripple (100Hz) - See Note 1 | <10mV rms | <10mV rms |
| Size in mm. | 76 x 68 x 40 high | 120 x 78 x 40 high |

POWER SUPPLY UNITS: comprising toroidal transformer plus 90 x 50 x 55 mm high printed circuit board containing smoothing and rectification

PSU31X Suitable for running one HR314 at full rated current. £13.17 inc. VAT
PSU56X Suitable for running one HR614 at full rated current. £19.13 inc. VAT

For 110v operation insert 0 in place of X — brown primary leads.
220v (Europe) operation insert 1 in place of X — pink primary leads.
240v (UK) operation insert 2 in place of X — orange primary leads.

For mail order please make your crossed cheques or postal orders payable to ILP Electronics Ltd. Barclaycard/Access welcome. Trade orders standard terms.



Post to ILP Electronics Ltd, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England. Telephone (0227) 54778. Telex 955780

ILP ELECTRONICS LTD.
a division of
IPElectronics Ltd.

BUYLINES

Audio Level Meter

An all-purpose audio level meter that will find a home in many hifi systems and in semi-professional recording studios, where constant attention to the recording level is always required!

Most of the components are readily available, with only the TL072 and the 10-segment LED array likely to prove difficult. The TL072 is stocked by **Rapid Electronics**, for instance, as well as several other suppliers, but the LED array may have to be ordered — quote the Radio Spares part number 586-706 (for a red display) or 588-033 (if you'd prefer green), and your favourite supplier should be able to get it for you. Alternatively suitable types (again in red or green) are stocked by **Technomatic**.

Polycarbonate capacitors can be somewhat hard to come by, and are a little expensive for the average hobbyist: polyester types are an adequate substitute, and although the PCB is laid out for an axial capacitor, a C280 or equivalent polyester can be 'made to fit'.

Because of the many different potential applications of the Audio

Level Meter, a case has not been specified. However the cost, excluding case and PCB, should be in the region of £6.50.

Ultrasonic Alarm

The first thing to note is that a case or other enclosure has not been specified for this project. Although the author suggests standard metal or plastic boxes, a favourite trick is to disguise an alarm system such as this as an otherwise ordinary piece of household equipment — a bookshelf loudspeaker unit, for example. So, all things considered, we decided to leave the final choice to the individual.

The dimensions of the project can easily be judged from the PCB foil pattern reproduced on page 72, allowing virtually any shape of enclosure to be designed around it.

The components are almost all standard and can be obtained from one of the larger mail order companies, such as **Maplin Electronics**. Several of the transistors specified may not be available, but substitutes such as the BC184 or

BC209 for the BC239; or BC182, BC237 for the BC171, are quite acceptable. Similarly 1/3 watt resistors, which may be supplied in some instances, can be used instead of the specified 1/4 watt types.

The estimated cost of the Ultrasonic Alarm, excluding PCB and case, is around £10.00.

Hi-Volt Meter

Astute readers may have noticed the "special preview" of this project on page 17 of the last issue. Yes, that's right — we made a mix of the pix. However as you'll see by comparing the pictures in the September issue the two projects use virtually identical meters and are housed in a box that looks... well, they're very similar aren't they?

That being so, we again called upon **Greenweld Electronics**, who once more came to the rescue with an offer to supply all the components for just £21.95, including case, meter and high voltage probes. This price, as usual, excludes the cost of the PCB from our very own PCB service.

Trump Card

The Trump Card PCBs and 23-way-Ace edge connector are being supplied by **Innovonics**, 147 Upland Road, East Dulwich, London SE22 for £5.95 including VAT, p&p.

IT LIVES AGAIN!

From the past it came, growing daily, striking terror into the hearts of lesser publications, and spreading its influence across the country in its quest to infiltrate every town, every home, every mind.

Not a horror story, but a success story. And if electronics theory strikes terror into you, then you need the help of **Electronics — It's Easy**. Originally a long-running series in *Electronics Today International*, **Electronics — It's Easy** was printed as a set of three books. They sold out. It was reprinted as a single volume. It sold out. Now this phenomenally successful publication is available again, in its third reprint. **Electronics — It's Easy** is a comprehensive and simply-written guide which explains the theory (and the practice) of electronics step by step. Every aspect of the subject is covered, starting with the basic principles and working through to the how and why of today's technology.

You can obtain your copy of **Electronics — It's Easy** by mail order using the coupon below. Make cheques or postal orders payable to ASP Ltd; alternatively you may pay by Access or Barclaycard.

Send to: Sales Office (Specials),
513 London Road, Thornton Heath
Surrey CR4 6AR

Please send me copies of **Electronics — It's Easy**. I have enclosed £ (£4.95 each including p&p).


NAME


ADDRESS

Please debit my account

My Access/ Barclaycard No. is

Signature

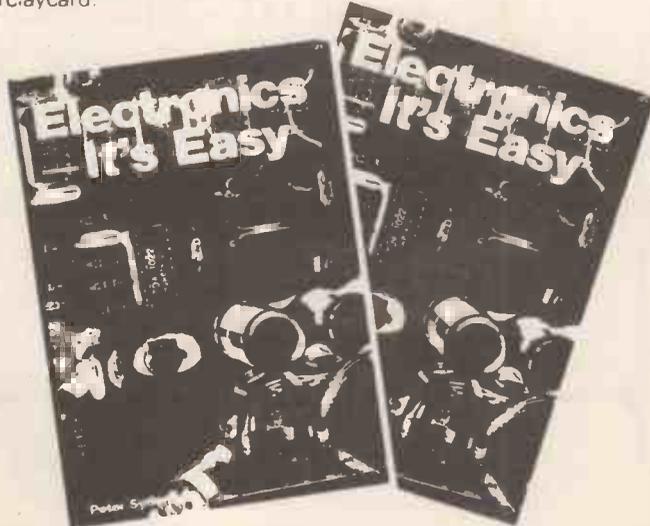

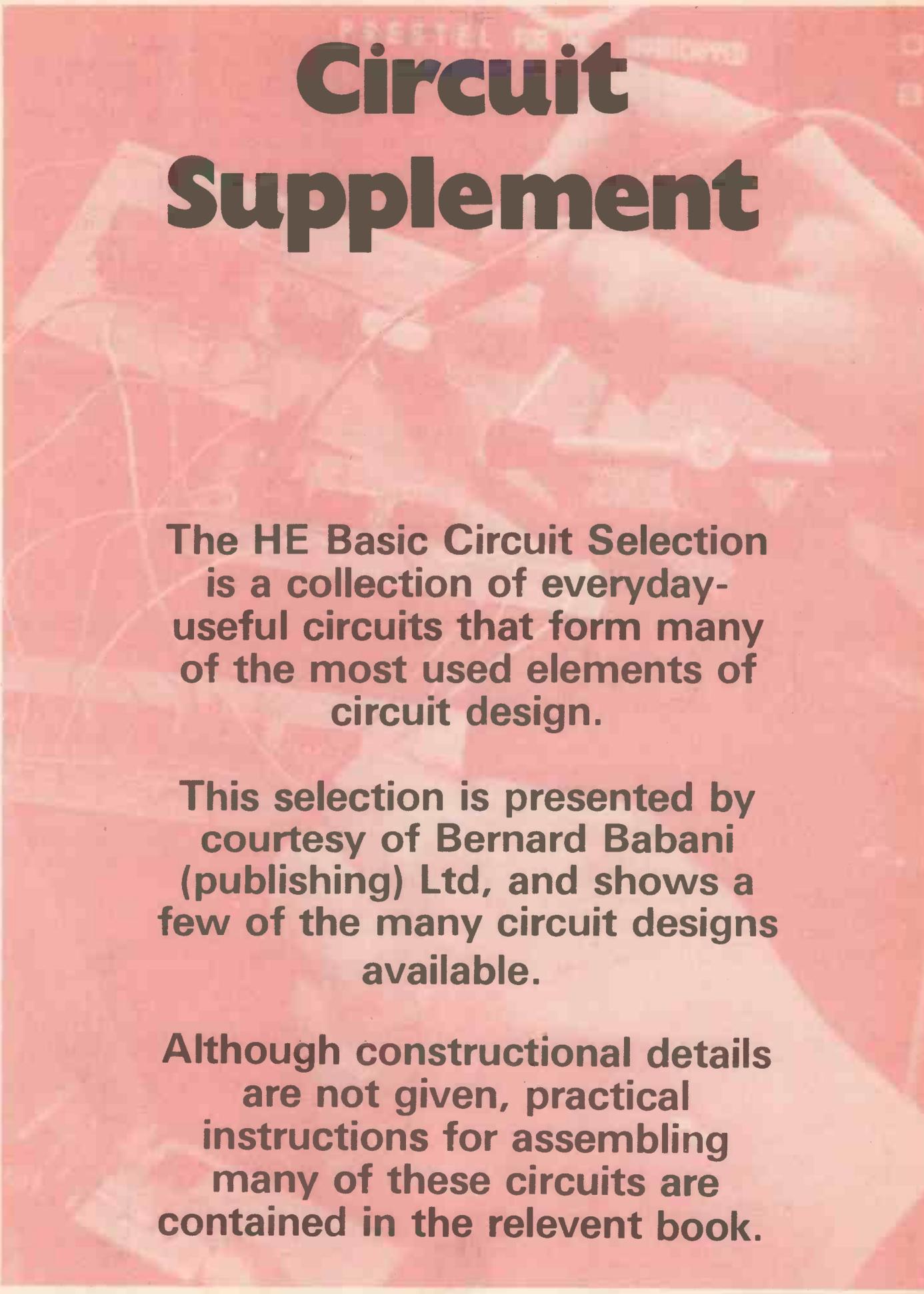

Circuit Supplement

The HE Basic Circuit Selection is a collection of everyday-useful circuits that form many of the most used elements of circuit design.

This selection is presented by courtesy of Bernard Babani (publishing) Ltd, and shows a few of the many circuit designs available.

Although constructional details are not given, practical instructions for assembling many of these circuits are contained in the relevant book.

555 Oscillators

The 555 timer integrated circuit has been featured in a great many projects for the electronics constructor, and this is not surprising when one considers the low cost and versatility of this device. It is well worthwhile being familiar with the capabilities of this device, and it will be considered in some detail in this section.

The standard 555 astable configuration shown will probably be familiar to most readers. It is really a form of relaxation oscillator with C2 first charging to two thirds of the supply voltage through R1 and R2, and then discharging through R2 to one third of the supply voltage. The operating frequency is therefore set by the values given to R1, R2 and C3, and is given by the formula:

$$\text{Frequency} = 1.44 / (R1 + 2R2) C2 \text{ Hz}$$

The reason for adding the value of R1 to double the value of R2 (rather than simply adding the two values together) is that R2 is both the charge and discharge paths of C2 and therefore has double the effect of R1. Rather than calculating the operating frequency with the resistance in ohms and the timing capacitance in farads it is better to use Megohms and microfarads. This avoids having very low figures for the capacitance and very large figures for the resistance.

Typical values for the timing components would be 4k7 for R1 and R2 plus 100nF for C2 giving an operating frequency of just over 1kHz.

There are, of course, certain limitations on the circuit values, and it is advisable to keep the combined resistance of R1 and R2 to no more than about 10MR. A resistance substantially higher than this could give rather unpredictable results or might result in the circuit failing to oscillate at all. This is due to the very low currents that would be present in the timing circuit, and consequent effects tiny input currents drawn by the 555 or leakage through C2 might have.

There is also a limit on the minimum value R1 should have, and this can be calculated by dividing the supply voltage by 0.2. This would, for example, give a figure of 45R with a 9V supply. In practice it is often necessary to use a value very much higher than this absolute minimum figure, and one reason for this is simply to keep the dissipation in the 555 down to a reasonable level. It should also be remembered that an internal transistor of the device places a virtual short circuit from pin 7 of the 555 to the negative supply rail during the discharge period of C2, and apart from any effects on the 555 itself, a low value component in the R1 position will give a

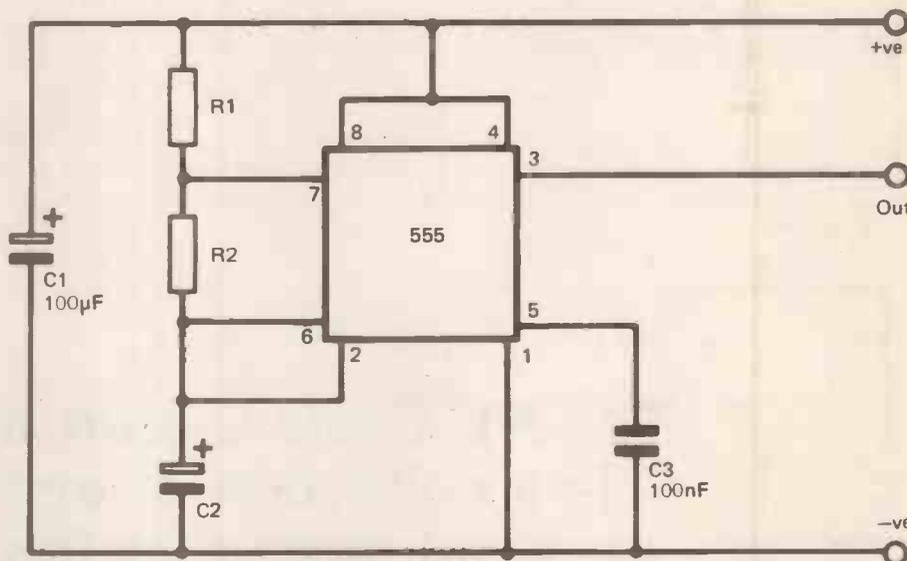


Figure 1. The trusty 555 geared up as an astable oscillator.

high dissipation in this resistor and a very high current consumption during the discharge period. A minimum resistance of about one kilohm is therefore more realistic.

Pin 3 is the output of the 555, and this terminal goes high while C2 is charging and low when it is discharging. This gives a rectangular waveform at the output of the device, but it is not a squarewave having a one-to-one-mark-space ratio. This is simply because C2 charges through both R1 and R2, but it discharges through R2 alone (plus the insignificant impedance of the discharge transistor within the 555).

The output of the 555 gives a peak to peak voltage almost equal to the supply voltage used, and it is at a low impedance. The device has a form of class B output stage, and it can source or sink up to 200mA. However, with high output currents the output is pulled well away from its normal (no load) level, and a combination of large output voltage and high current cannot be supplied directly by the device.

An output signal can be taken from across C2, but this is only permissible if a very low output current is taken since any loading here obviously has an effect on the charging and discharging of C2. The higher the values of R1 and R2, the less output current that is available. The waveform across C2 is roughly triangular, but C2 charges and discharges exponentially and so this is

obviously not a linear triangular waveform. Also, like the output at pin 3, the mark-space ratio of the signal is not one-to-one.

A slight shortcoming of the 555 is that once per output cycle the supply is "crowbarred" and a negative voltage spike is introduced onto the supply lines. C1 is included to decouple this noise.

C3 is also a decoupling capacitor, and this removes any stray pick-up at pin 5 of the 555.

Any electronic circuit will only operate between certain supply voltage limits, and this is something which must always be borne in mind. For the 555 device the minimum and maximum supply potentials are 5V and 15V. The 555 actually has a maximum permissible supply voltage of 16V, but with any figure of this type it is advisable to leave a small safety margin and 15V is therefore the maximum nominal supply voltage. The maximum operating frequency of the device is at least 500kHz, and there is no properly defined lower limit to the operating frequency. The lower limit is determined by the quality of the timing capacitor C2 which for very low frequencies must be a polarised type such as a tantalum or electrolytic type. Although in theory it is perfectly alright to use a capacitor of (say) 100uF with a total timing resistance of several megohms, in practice this is unlikely to work. The

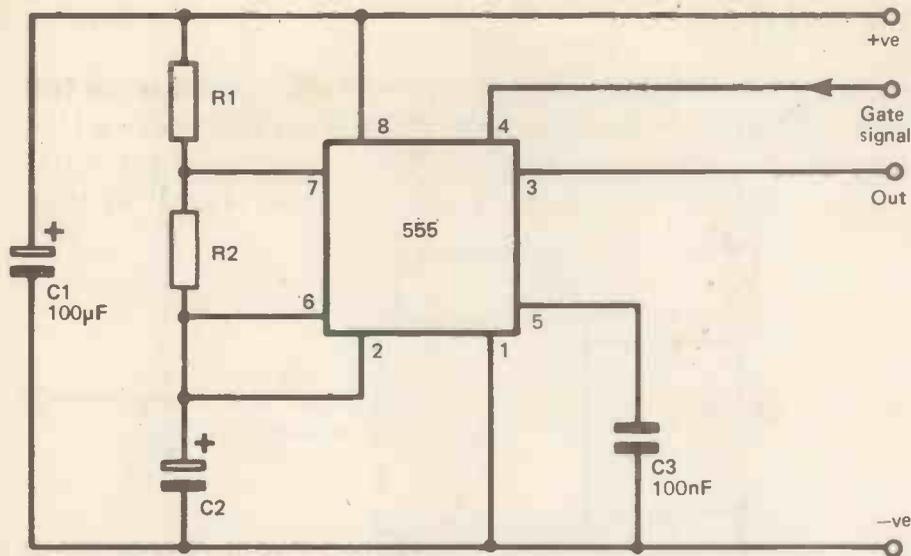


Figure 2. The gated astable can be used for producing tone-bursts or a gated clock signal.

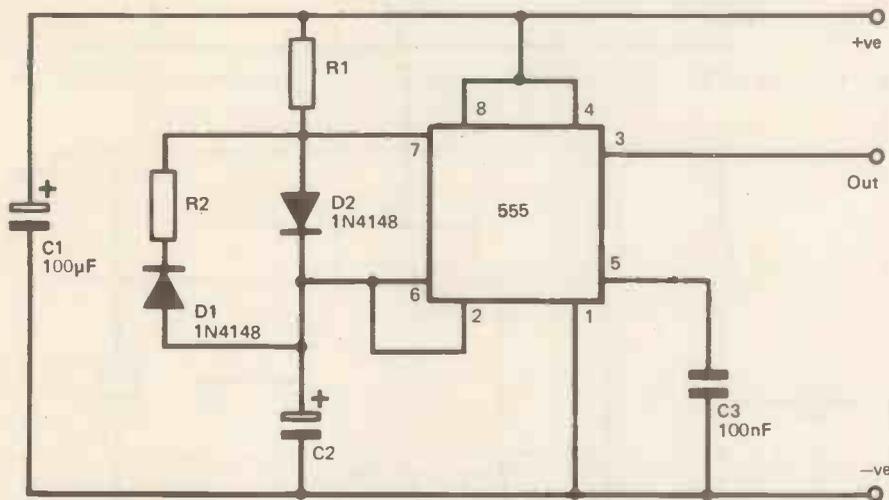


Figure 3. The mark-space ratio can be varied continuously if R1, R2 are replaced by variable resistors.

leakage resistance of the capacitor may well be only a few hundred kilohms, and this would limit the charge voltage to a level which would not permit correct operation of the circuit. Tantalum types are generally much better in this respect than electrolytic capacitors, and such a combination of timing component values might work well using a tantalum capacitor.

A point that is sometimes of importance, especially when the 555 is used in very low frequency applications, is that the first half of the initial cycle is longer than that obtained on subsequent cycles. This is simply due to C2 starting with zero charge on the first cycle, whereas it starts with a charge equal to one third of the supply voltage on subsequent cycles. This is not unique to the 555 by any means: in fact most simple C-R oscillators produce a longer initial cycle.

Gated Oscillator

The 555 can be used as a gated oscillator, as shown. This circuit is basically the same as the one shown

above but instead of pin 4 of the 555 being taken to the positive supply rail it is fed with the gating signal. Pin 4 must be taken below about 0V5 in order to switch off the oscillator, and the output goes to the low state when the circuit is gated off. The input current to pin 4 is only about 100µA. If pin 4 is left floating it is normal for the oscillator to operate, incidentally.

The current consumption of the 555 varies from about 3mA with a 5V supply to about 10mA with a 15V supply (it is about 7 to 8mA with a 9V supply).

Adjustable Duty Cycle

As mentioned earlier, it is possible to produce a 555 astable circuit that can give any desired mark-space ratio, and a circuit of this type is shown. This has steering diodes D1 and D2 which direct the charge current through R1 and the discharge current through R2. Thus a 1:1 mark space ratio can be obtained by simply making R1 and R2 the same value. If R1 is made larger in value than R2 the charge (high) time is made proportionately longer than the discharge

(low) time. Similarly, making R2 higher in value than R1 makes the discharge (low) time proportionately longer than the charge (high) time.

The formulas for calculating the operating frequency and high output time are slightly different since R2 is not in circuit while C2 is charging. Thus in the frequency calculation the timing resistance is simply R1 plus R2 rather than R1 plus double R2. Similarly, the timing resistance when calculating the high output time is simply R2 and not R1 plus R2. The two diodes have a marginal effect on the frequency, charge, and discharge times, but this will not normally be large enough to be of significance.

Frequency Modulation

As mentioned earlier, the operating frequency of a 555 astable can be modulated by a control voltage. This differs from the normal 555 astable configuration in that the decoupling capacitor at pin 5 of the device has to be removed and the control voltage is applied to this pin instead.

Pin 5 of the device connects to the internal potential divider circuit which sets the two thirds of the supply voltage threshold level at which the 555 triggers from the charge mode to the discharge one. By taking pin 5 above two thirds of the supply voltage the operating frequency is decreased since C2 has to charge to and discharge from a greater potential, and therefore takes longer to do so. Taking pin 5 below two thirds of the supply voltage reduces the voltage to which C2 has to charge and discharge so that both processes take less time and the operating frequency is increased. The output waveform at pin 3 remains unchanged, but there is a slight change in the waveshape and the amplitude of the signal across C2.

Pin 5 of the 555 does not connect directly to the internal potential divider of the device, and the threshold voltage at which the device triggers from the charge state to the discharge one is not equal to the voltage fed to pin 5. This limits the degree of control that can be obtained using a control voltage fed to pin 5, and the frequency is reduced by a little more than 50% if the control input is taken to the positive supply voltage. The output frequency is slightly more than doubled if the control terminal is taken to one third of the supply voltage, and it can be boosted a little further if it is taken slightly lower in voltage. However, if it is taken too low in voltage a malfunction occurs and the output frequency reduces considerably. It is therefore advisable to keep the control voltage between one third of the supply voltage and the full supply potential.

The control range is not very great but it is useful for applications such as modulated tone generators.

This circuit and description are taken from "Practical Electronic Building Blocks, Book 1", BP117, by R. A. Penfold, published by Bernard Babani (publishing) Ltd.

Basic 555 Monostable

The 555 timer IC can be used as a monostable multivibrator, and is often the most cost effective choice when a circuit of this type is required.

The basic 555 monostable configuration is shown in Figure 1.

Normally the input of the circuit is held at more than one third of the supply voltage, and under stand-by conditions the internal discharge transistor of the 555 hold C1 in uncharged state and the output at pin 3 is low. If the trigger input is taken below about one third of the supply potential the circuit is triggered, pin 3 of the 555 goes high, and the internal discharge transistor switches off so that C1 can charge by way of R1. This continues until the charge potential on C1 reaches two thirds of the supply voltage, and the circuit then reverts to its original state. At least, it returns to its original state provided the trigger input has been taken back above one third of the supply voltage.

The output pulse has a duration of $1.1CR$ seconds, and the minimum pulse length is about one microsecond, and the maximum pulse duration is limited only by the maximum practical timing capacitance (as for the astable mode).

Manual Triggering

An improved method of manual triggering is shown. Here R3 normally holds the trigger input at virtually the full positive supply voltage, but a brief negative pulse will be produced at the input when BP1 is operated due to C2 charging via R3. This gives the brief trigger pulse, and no matter how long PB1 is depressed, it is the time constant of R3 and C2 that sets the length of the trigger pulse. R2 rapidly discharges C2 when PB1 is released so that the circuit is almost instantly ready for another operation of PB1.

The trigger pulse applied to IC1 is only a few microseconds in duration, and the circuit will obviously work properly with output pulse lengths of around 10 μ s or more. For shorter pulse lengths of only about 1 μ s or so it would be necessary to decrease C2 in value, although triggering might become unreliable if this component is made much lower in value.

Reset Facility

In the monostable mode pin 4 of the 555 device is the reset terminal, and this should normally be in the high state. Taking this pin low during the output pulse can cause the pulse to be immediately brought to an end. The circuit shows how to add both manual and electronic reset facilities to a 555 monostable.

This circuit and description are taken from "Practical Electronic Building Blocks Book 1", BP117 by R. A. Penfold, published by Bernard Babani (publishing) Ltd.

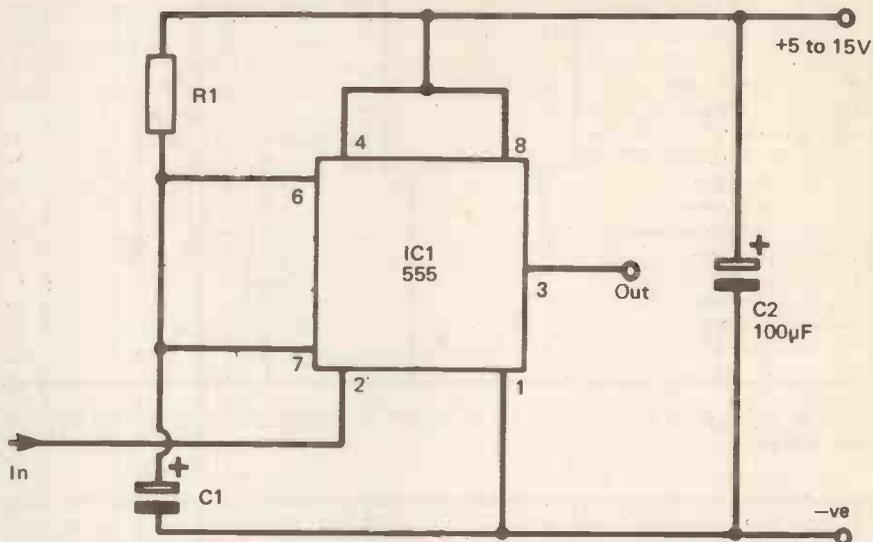


Figure 4. Basic 555 monostable. It is triggered by briefly taking pin 2 below $\frac{1}{3}$ V+.

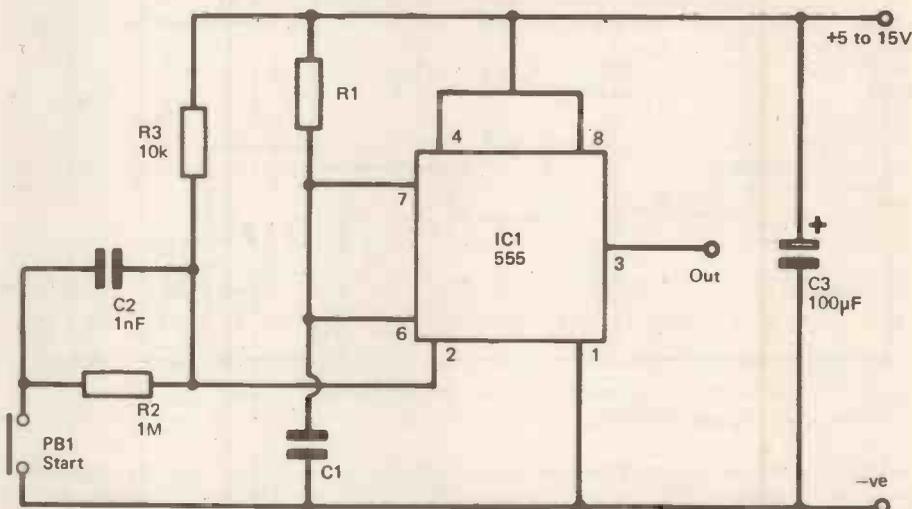


Figure 5. The length of the trigger pulse can be controlled by an RC network around the trigger switch.

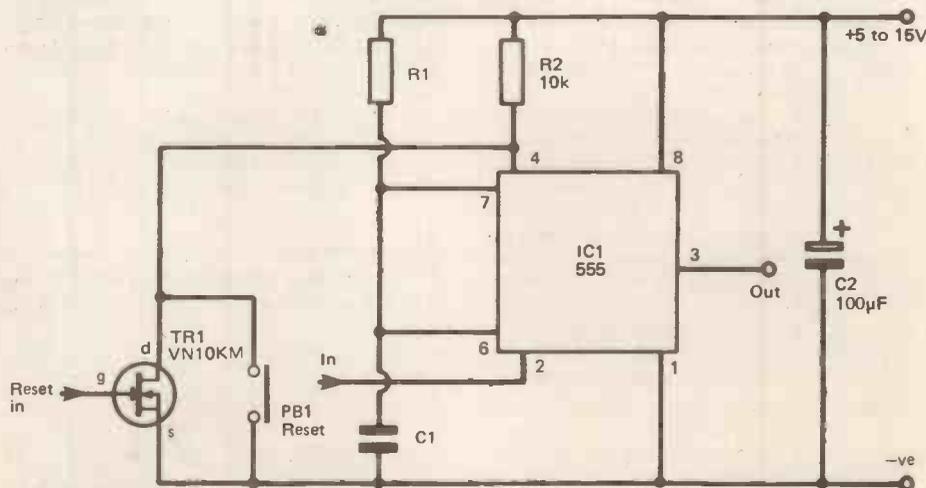


Figure 6. The monostable can be reset by taking pin 4 low, either manually with a switch or by taking the gate of TR1 a few volts positive.

Emitter Follower

Losses due to loading can be substantially reduced using a buffer amplifier.

Loading of one stage on another, or loading of a circuit of some kind on a transducer such as a microphone, can produce a large reduction in signal level.

An emitter follower has 100% negative feedback and therefore only unity voltage gain, but the full current gain of the transistor is realised so that only a small input current is needed to give a comparatively large output current, and the required high to low impedance conversion is thus obtained. It should perhaps be pointed out that an emitter follower stage does not actually give unity voltage gain, but in actual fact gives marginally less than unity gain (about 0.96 being the typical voltage gain obtained). This very small drop in signal level is not usually of any practical significance though.

The input impedance of the circuit is equal to the parallel impedances of R1, R2 and the input impedance of Tr1. These give an input impedance of roughly 100k using the specified values. The output impedance of the circuit is 2k2, but this does not take into account the effect of the source impedance of the input signal. This lowers the output impedance of the circuit to a figure which can be calculated by dividing the source impedance by the current gain of Tr1 (which is about 520 at the collector current used here). In fact the basic 2k2

output impedance of the amplifier is in parallel with the impedance obtained from the calculation detailed above, but in practice the output impedance of the circuit will normally be so low that this 2k2 is of no consequence.

Although the output impedance of the circuit is likely to be only about 100R or less in a practical situation, and normal loading of the output will not significantly reduce the output signal level of the unit, it is important to bear in mind that the maximum output current of the circuit is equal to the emitter current of Tr1, or about 2mA using the values specified. In other words, trying to provide an output signal of a few volts peak into a load impedance of only about a hundred ohms will not give satisfactory results since the output current capability of the circuit will be inadequate on signal peaks, and clipping will occur. The purpose of a circuit of this type is to match a source impedance of (say) about 10 or 20k to a comparatively low input impedance of (say) about 1 or 2k without producing the massive loss of signal level that would occur using direct connection of the two pieces of equipment.

The circuit is not intended to be a powerful amplifier and will not work as one.

The circuit will work reasonably well

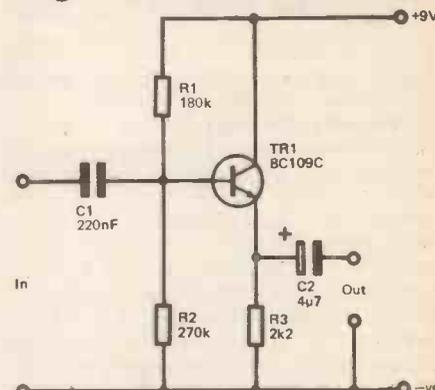


Figure 7. A simple emitter follower circuit is often used to reduce loading effects.

on any supply potential of between 3V and 18V. The current consumption from a 9V supply is about 2mA, and this changes roughly in proportion to alterations in the supply voltage.

Due to the large amount of negative feedback employed in the circuit the noise and distortion levels are both extremely low.

This circuit and description are taken from "Practical Electronic Building Blocks, Book 2", BP118, by R. A. Penfold, published by Bernard Babani (Publishing) Ltd

General Purpose Amplifier

This unit can feed any speaker having an impedance of 8 ohms or more and will produce a maximum output of about 1 watt into an 8 ohm load when used with a fresh battery

This simple design is intended for general purpose use, and it is an extremely useful piece of equipment to have around. It is surprising the number of occasions on which an amplifier of this type can be put to good use. The circuit diagram of the unit is shown.

The circuit is based on the popular LM380N IC which has the advantage over most other ICs of requiring very few discrete components to complete a practical amplifier. A practical amplifier can be constructed using this IC and just three discrete components. These are an output DC blocking capacitor (C5) an input DC blocking capacitor (C4), and a supply decoupling capacitor (C1).

There are two drawbacks to using just a basic circuit of this type in the present application, and these are the inadequate voltage gain and input impedance of the circuit. The LM380N has typical input impedance and voltage gain figures of 150k and 50 respectively. Ideally for this application these should be about ten times higher in each case, so that the amplifier could operate from high impedance low level loads, such as a crystal microphone.

Therefore, in order to boost the input

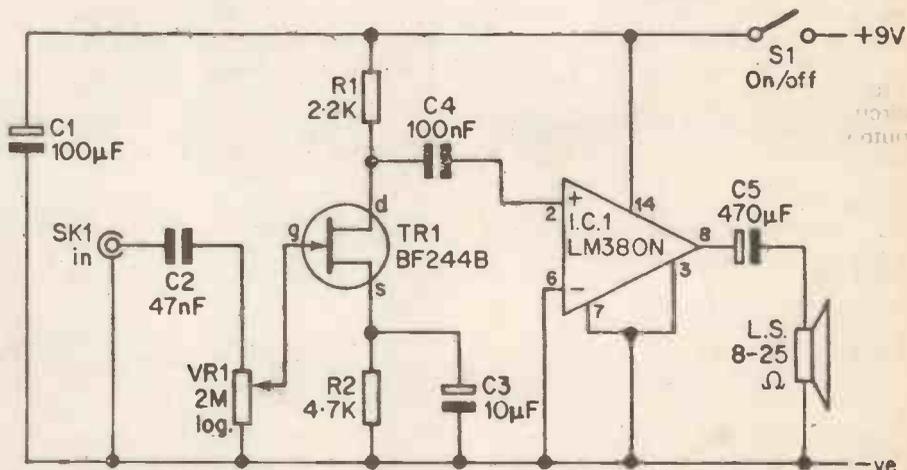


Figure 8. The LM380N has built-in thermal and short circuit protection, making it the ideal device for test and breadboard situations.

impedance and voltage gain of the basic circuit a FET common source preamplifier stage has been added. This utilizes Tr1. VR1 is the volume control, and this doubles as the gate bias resistor for Tr1. C2 provides DC blocking at the input. S1 is the on/off switch, and this can be gated with VR1 if

desired. C1 is the only supply decoupling capacitor that is required for the entire amplifier circuit.

This circuit and description are taken from "Popular Electronic Projects", BP49 by R. A. Penfold, published by Bernard Babani (publishing) Ltd.

Filters

Filters are required in many applications, and are often implemented by passive capacitor and inductive networks. Inductors are, however, bulky, expensive and somewhat difficult to obtain. The use of operational amplifiers with frequency selective feedback allows filters to be designed using only resistors and capacitors.

Low Pass Filters

Simple Low Pass Filter

The simplest possible low pass filter is shown. The capacitor C has infinite impedance at DC, and the low frequency gain is determined by R1 and R2 as described below. As the frequency rises the impedance of C decreases causing the gain to fall.

The roll off frequency is given by:

$$f = \frac{1}{2\pi CR2}$$

Classical Low Pass Filter

The classical operational amplifier low pass filter is shown. This has unity gain at low frequencies. To simplify calculations, R1 and R2 should be equal, and C1 should be twice the value of C2.

The cut off frequency is then given by:

$$f = \frac{\sqrt{2}}{4\pi RC}$$

If R1 = R2 = R, C2 = C and C1 = 2C.

With the relationships above the filter is said to be critically damped and the cut off is far sharper than the simple filter. If C1 is not twice C2 the cutoff frequency is given by:

$$f = \frac{1}{2\pi R\sqrt{C1.C2}}$$

if R1 = R2 = R.

Dependent on C1 and C2 the response can be made gentle or peaky as shown.

Similar low pass filters are the basis of audio scratch filters.

High Pass Filters

Simple High Pass Filters

The simplest high pass filter is shown. At high frequencies the gain will be determined by R1 and R2 (and the amplifier itself). At low frequencies C will have significant impedance reducing the gain. The cutoff frequency is given by:

$$f = \frac{1}{2\pi CR1}$$

Note that the high frequency gain will be reduced by the limited bandwidth of the amplifier itself.

Classical High Pass Filter

The circuit is identical to the low pass

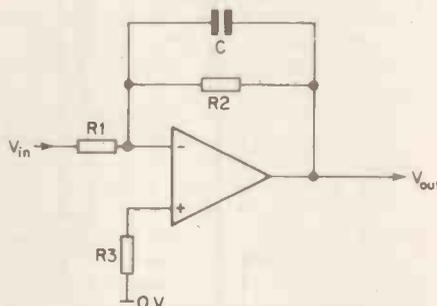


Figure 9. Simple op-amp low pass filter.

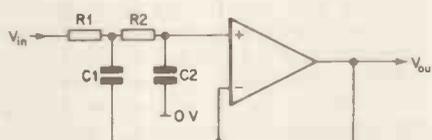


Figure 10. The classical filter gives a sharper cutoff.

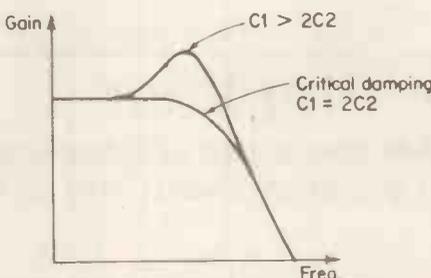


Figure 11. Response curves of the classical filter circuit.

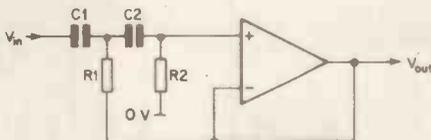


Figure 12. The classical high pass filter.

filter with the capacitors and resistors interchanged. Ideally the components should be chosen such that C1 and C2 are equal and R2 is twice the value of R1. The cutoff frequency is then given by:

$$f = \frac{\sqrt{2}}{4\pi RC}$$

where C1 = C2 = C, R1 = R and R2 = 2R. The general equation with C1 = C2 = C is:

$$f = \frac{1}{2\pi C\sqrt{(R1.R2)}}$$

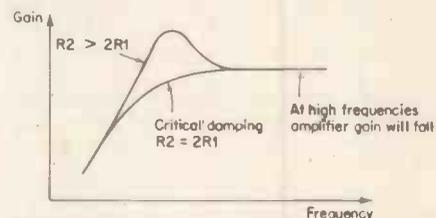


Figure 13. High pass filter response curves.

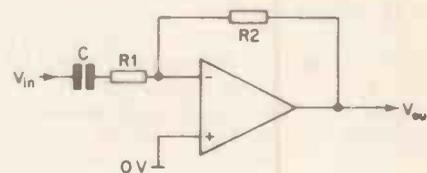


Figure 14. The simplest high pass filter circuit.

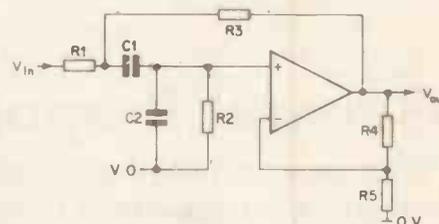


Figure 15. A single-amplifier band pass filter.

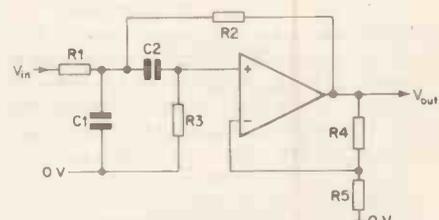


Figure 16. An alternative band pass circuit.

with the ratio of R1 to R2 determining the response at cutoff.

The high pass filter is widely used as a rumble filter in audio circuits.

Bandpass Filter

Introduction

A bandpass filter will, as its name implies, pass a specific band of frequencies and reject frequencies higher or lower than the specified band. A bandpass filter is specified simply by two parameters; the centre frequency and the ratio of the centre frequency to the -3dB bandwidth (denoted by Q). The higher the value of Q, the sharper the shape of the curve shown.

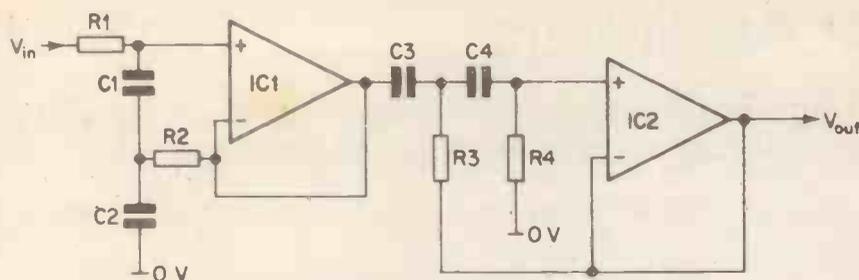


Figure 17. A two stage bandpass filter.

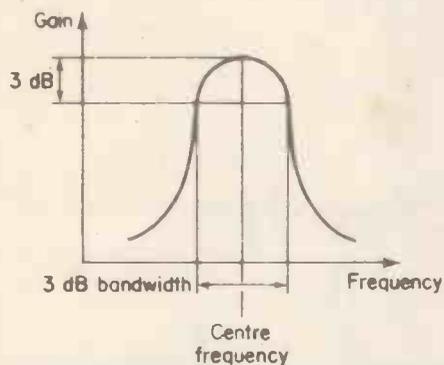


Figure 18. The response obtained by a bandpass filter.

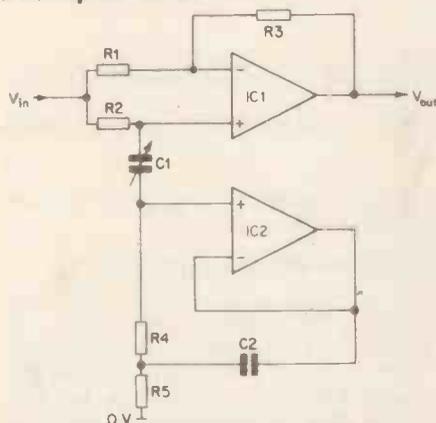


Figure 19. A turnable notch filter.

Single Amplifier Bandpass Filter

The circuit is widely used as a bandpass filter. To simplify calculation R1, R2, R3 should be equal (denoted by R) and C1 and C2 should be equal (denoted by C). The centre frequency, fo, is then given by:

$$f_o = \frac{\sqrt{2}}{2 \pi RC}$$

The Q of the circuit is determined by R4 and R5 with:

$$Q = \frac{R5\sqrt{2}}{4R5 - R4}$$

An alternative single amplifier circuit is shown. The components should be chosen such that R1 and R2 should be equal (denoted by R) and R3 should be chosen to be 2R. C1 and C2 should be made equal (denoted by C). The equations are somewhat simpler, with:

$$f_o = \frac{1}{2 \pi RC}$$

$$\text{and } Q = \frac{R5}{2R5 - R4}$$

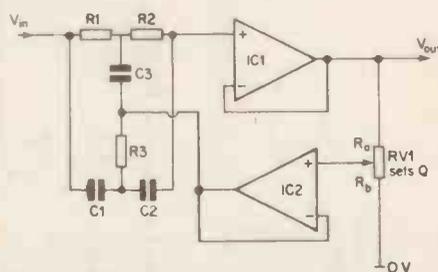


Figure 20. This notch filter has adjustable Q.

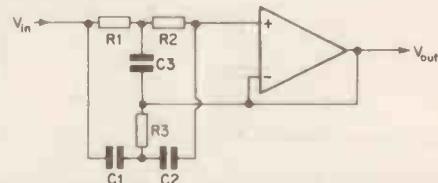


Figure 21. The high Q notch filter.

Two Stage Bandpass Filter

The circuit is easier to comprehend than those of the previous section, although it uses two amplifiers. IC1 is a low pass filter, and IC2 a high pass filter. The centre frequency is determined by:

$$f_o = \frac{1}{2 \pi RC}$$

if R1=R2=R3=R4=R and C1=C2=C3=C4=C.

The bandwidth is determined by the cutoff frequencies. If the above equalities do not hold, the upper and lower frequency cutoff can be determined separately.

Notch Filters

Introduction

A notch filter is the opposite of a bandpass filter in that it rejects a band of frequencies. Commonly the notch filter is used to reject 50Hz mains hum (60Hz outside Great Britain) in sensitive audio circuits and measuring instruments. The centre frequency and Q of a notch filter are defined in a similar manner to those of a bandpass filter.

Single Amplifier Notch Filter

The circuit gives a notch filter of very high Q. To simplify the design, the values should be chosen such that:

- R1 = R2 = R
- R3 = R/2
- C1 = C2 = C
- C3 = 2C

If the above conditions are met, the centre frequency is given by:

$$f_o = \frac{1}{2 \pi RC}$$

Two Amplifier Tunable Notch Filter

The circuit can be tuned by a single variable capacitor, C1. Normally C1 will be a few hundred picofarads and the C2 several microfarads. As usual, the design is simplified by the resistor equalities below:

- R = R2 = R3 = R
- R4 = R5 = R/2

The centre frequency is then given by:

$$f_o = \frac{1}{\pi R \sqrt{C1C2}}$$

Adjustable Q Notch Filter

The circuit allows the Q of a notch filter to be varied by a single potentiometer without varying the centre frequency. The potentiometer can be any reasonable value, the Q of the circuit being determined by the ratio Ra/Rb. As usual, some equalities must be observed:

- R1 = R2 = R
- R3 = R/2
- C1 = C2 = C
- C3 = 2C

The centre frequency is given by:

$$f_o = \frac{1}{2 \pi RC}$$

The adjustable Q notch filter is very useful in low level measuring instruments.

Practical Observations

The obvious is sometimes overlooked, but it should be noted that in all the above equations resistors must be in OHM and capacitors in FARADS giving results in Hz (cycles per second for older readers!)

Where equalities are given, precision resistors (at worst 1% tolerance) should be used and close tolerance capacitors. Multiples and division by two is often needed in the equations, and this is best achieved by one value of resistor and capacitor throughout, and using parallel or series combinations to produce the multiples required.

It will often be found that none of the preferred value resistors or capacitors give the required frequency. Series combinations of resistors should be used in preference to variable resistors. This is inelegant, but one of the sad facts of life in filter design. Alternatively precision wire wound or thin film resistors can be ordered to specific values. Although prohibitively expensive for home "one-offs" this approach is economically viable for production runs. The inherent inductance of wire wound resistors limits their use to low frequency circuits.

This circuit and description are taken from "How To Use Op-Amps", BP88, by E. A. Parr, published by Bernard Babani (publishing) Ltd.

Audio Operational Amplifiers

Some operational amplifiers are primarily designed for use in audio frequency amplifiers despite the fact that these devices were originally designed for use as DC amplifiers.

Operational amplifiers can be used in two basic modes of amplification; the inverting mode and the non-inverting one. This circuit is for an inverting amplifier (we will consider a non-inverting amplifier shortly).

R3 and R4 are used to bias the non-inverting input (and also the output) to approximately half the supply voltage. C2 filters out any hum or other noise which might otherwise be coupled to the non-inverting input of IC1 from the supply lines via the bias circuit. This also removes any stray feedback from the output of the amplifier to the non-inverting input and thus reduces the risk of instability.

R1 and R2 are a negative feedback circuit which determine the input impedance and voltage gain of the circuit. By giving these two components the appropriate values it is possible to set both these parameters with a high degree of accuracy, and this makes operational amplifier based circuits (or discrete circuits using similar techniques) ideal for use where it is essential to be able to set the gain and input impedance reliably and consistently.

The input impedance is equal to the value given to R1, and the voltage gain is equal to R2 divided by R1, or ten times using the specified values for these components. C1 and C3 are merely DC blocking capacitors.

Obviously R1 and R2 can be given values to set almost any desired input impedance and voltage gain. However, there are definite limitations on the voltage gain that can be obtained, and to a lesser extent on the input impedance than can be achieved in practice.

If we take the voltage gain first, it must be borne in mind that the gain-bandwidth product of the LF351 device is 4MHz. In other words, the maximum frequency the amplifier must handle multiplied by the voltage gain of the amplifier must be no more than 4MHz. For an amplifier that must cover the full audio band (which extends from about 20Hz to 20kHz) the maximum voltage gain that can be used is clearly 200 times (20kHz multiplied by 200 equals 4MHz). In most cases the LF351 will be able to provide sufficient voltage gain using a single stage of amplification, but two stages connected in series can be used where additional voltage gain is needed.

In theory there is no limit on the input impedance that can be achieved using a circuit of this type, but in practice there is the problem of obtaining resistors of

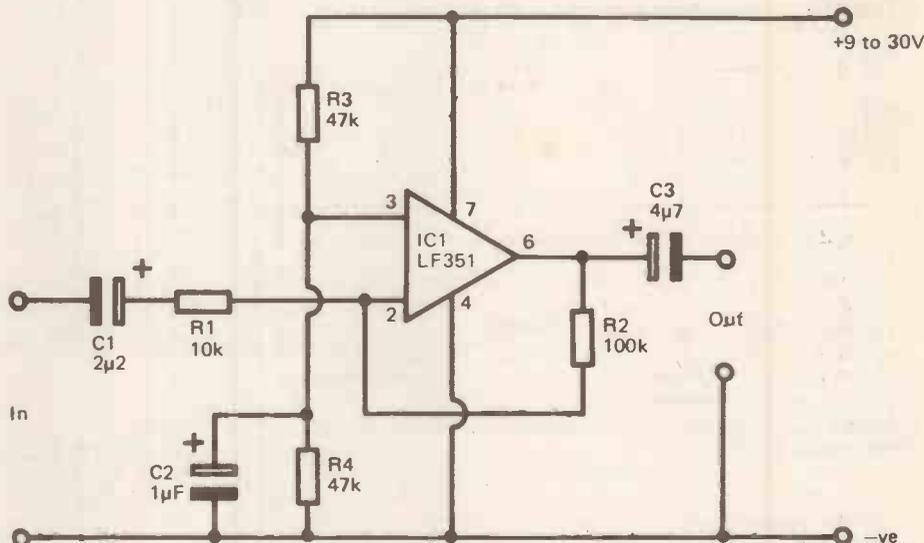


Figure 22. The circuit for an inverting amplifier using the LF351 op-amp, biased from a single supply rail.

sufficiently high value, especially in cases where a combination of high voltage gain and high input impedance of 10 Megohms and a voltage gain of 100 times would require R1 to have a value of 10M, and R2 to have a value of 1000M. This is clearly not a practical proposition, and in cases of this type it is better to use a low gain buffer stage to give the high input impedance, and a separate high gain stage to step-up the voltage gain to the desired figure.

Problems can arise with this type of due to the input capacitance of the operational amplifier effectively making the negative feedback, to a degree, frequency selective, so that unwanted peaks or dips in the frequency response are produced. This is only really likely to be a problem in circuits that are used to provide low voltage gain and a high input impedance, and the result is normally a roughly doubling in gain at a frequency of few tens of kilohertz with the response falling away at frequencies above the peak. Where low gain and high input and impedance are needed it is better to use a non-inverting amplifier since a low impedance feedback network can then be used, and the input capacitance of the operational amplifier becomes insignificant.

Bearing in mind the limitations mentioned above, the appropriate values for R1 and R2 are easily calculated. R1 is simply given the nearest preferred value to the the required input impedance, and then this figure is multiplied by the required voltage gain to give the value of R2 (and

again the nearest preferred value must be chosen).

Non-Inverting Amplifier

The circuit of an operational amplifier used in the non-inverting mode is shown. R3 and R4 bias the non-inverting input to about half the supply voltage with R5 being used to couple this bias voltage to IC1. C2 decodes any hum or other electrical noise on the supply lines so that it is not fed to the input of the amplifier. The value of R5 is equal to the required input impedance of the amplifier, and C2 provides DC blocking at the input (and should have its value chosen to suit the input impedance of the circuit).

R1 and R2 are the negative feedback network, and the voltage gain of the circuit can be calculated by first adding the values of R1 and R2, and then dividing this figure by the value of R1. The specified values given to R1 and R2 can be any two that have the correct ratio to give the desired voltage gain, but in practice it is not a good idea to have low values that will heavily load the output of the operational amplifier, or to have high values that would result in a far from flat frequency response due to the input capacitance of IC1. In practice it is therefore advisable to have the total value through R1 and R2 at something in the region of 25 to 100k.

In order to choose suitable values for R1 and R2 first decide on a value for R2, and any value of a few tens of kilohms should do. Then divide this by one less than the required voltage gain to find the correct value for R1. The nearest

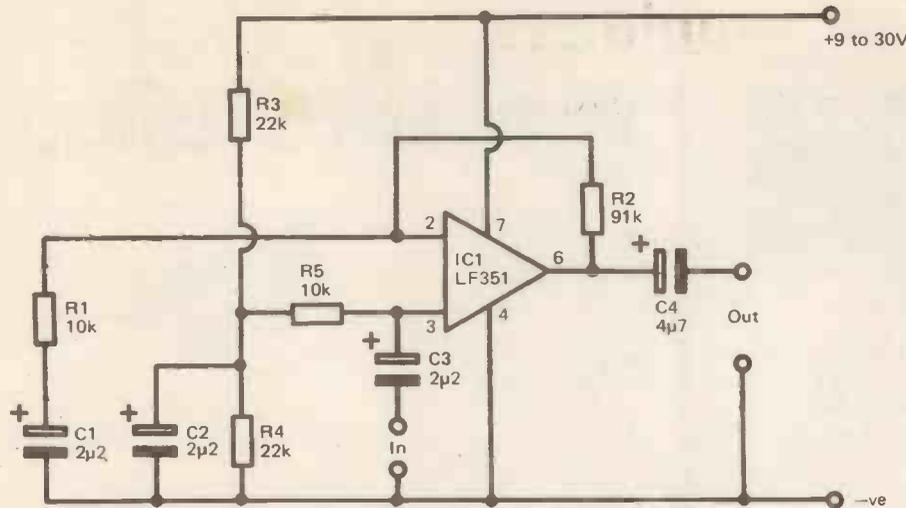


Figure 23. The LF351 in non-inverting mode.

preferred value to the calculated figure is the used. C1 is a DC blocking capacitor which gives the circuit 100% negative feedback and unity voltage gain at DC so that the circuit is biased properly. At audio frequencies it must not add significantly to the impedance provided by R1, and the correct value is calculated in the same way as the value of the input and output coupling capacitor values are obtained.

The distortion performance of the LF351 is extremely good with the distortion level being only about 0.02% provided the output is not heavily

loaded, the circuit is not driven into clipping and the amplifier is not used at very high gain levels. If used at fairly high voltage gains the distortion performance does reduce at high audio frequencies, although the distortion level is still likely to be less than 0.1%.

The noise performance of the LF351 is also extremely good with an output noise level of only about 500µV even if the amplifier is used at a high voltage gain of one hundred times.

One point that must be emphasized is that although in theory it is perfectly satisfactory to have a non-inverting

amplifier with an impedance of (say) 5M and a voltage gain of one or two hundred times, and the LF351 is quite capable of achieving these performance figures, in a practical situation it is highly unlikely that such a circuit could be made to operate satisfactorily. The problem is simply that there would inevitably be a certain amount of stray feedback from the output of the amplifier to the input, and as these two points are in-phase it is almost certain that instability would occur with the circuit breaking into oscillation. It is therefore better to use two stages of amplification with the first giving the high input impedance and the second providing the voltage gain.

This enables better separation to be obtained between the input and the output so that stray feedback can be reduced to an insignificant level. It is also a good idea to have the second stage of amplification of the inverting type so that the input and output of the amplifier as a whole are then out-of-phase, and any stray feedback will therefore be of the negative variety. This will not cause instability, but will simply result in a small reduction in the high frequency gain of the amplifier.

This circuit and description are taken from "Practical Electronic Building Blocks, Book 2", BP118 by R. A. Penfold, published by Bernard Babani (publishing) Ltd.

Supply Splitter

Many op-amp circuits require dual balanced power supplies of up to 12 volts each and, while a special power supply circuit can be built, a simple supply splitter is more convenient if a single-cell supply is already available.

A method of obtaining dual balanced supplies is to use a supply splitter that gives a low impedance centre-tap on a single supply, rather than generating two equal supplies and connecting them in series. A supply splitter such as the one shown in the circuit diagram is intended for use with an existing bench power supply, and is not an independent unit. This particular circuit will work well with supply voltages of between 15V and 30V, and each of the output rails has a potential equal to half the input voltage (thus 30V is needed at the input to give dual 15V outputs for example). The unit will readily handle currents of up to 100mA, and it should not be necessary to fit Tr3 and Tr4 with heatsinks.

The circuit is really just an unity gain amplifier having a high input impedance and a low output impedance class B output stage. A class B output stage is used as this gives the unit a low quiescent current consumption (only about 2mA). Tr1 and Tr3 are common emitter amplifiers, but as there is 100% negative feedback from Tr3's collector to Tr1's emitter these give only unit gain. Tr2 and Tr4 form a complementary

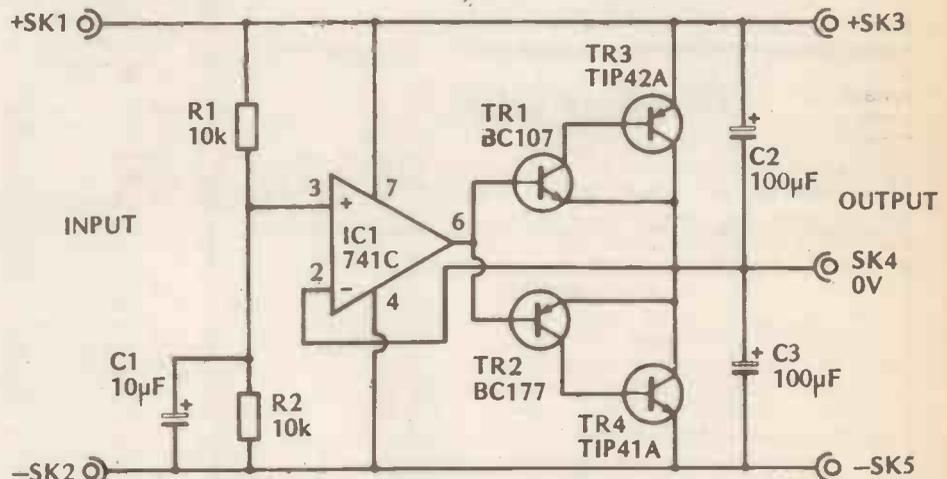


Figure 24. This supply splitter will prove its usefulness to the experimenter.

output pair for Tr1 and Tr3. There is 100% negative feedback from the output of the unit (Tr3 — Tr4 collectors) to the inverting input of IC1, and this gives unit voltage gain from the non-inverting input of IC1 to the output. R1 and R2 bias the non-inverting input of IC1 to half the supply potential, giving the same voltage at the output, but at

a very low impedance. The three capacitors are needed to maintain stability.

This circuit and description are taken from, "Popular Electronic Circuits Book 2", B98, by R. A. Penfold, published by Bernard Babani (publishing) Ltd.

G.P.E. SELF-FEED SOLDERING IRON Patented
A new concept in miniature soldering iron design



This new development in Soldering Irons combines light weight (80g.) with unique one-handed operation. Solder is housed in the transparent handle and applied directly to the joint by turning the serrated wheel (located in the handle) with the index finger, allowing a clean, bright joint to be made every time. To renew the solder, the spring clip at the end of the handle is released, the cap is removed and a refill is inserted.

ORDERING INFORMATION. (MAIL ORDER ONLY)

Soldering Iron 240v, 18w. Fitted with 2.3mm Dia. Bit. Complete with 4 metres of solder. **Price £14.95.**

Solder refills (Pack of 4) **Price £2.44.**

Spare Bits. (Long life) Tip. Dia. 2.3mm, 3mm or 4.7mm. **Price £1.36 each.**

All prices include VAT and P & P. S.A.E. for details.

Manufactured and supplied by:

GARDNER PRECISION ENGINEERING
North Road, Woking, Surrey GU21 5DS.
Tel. Woking 20722

Now open in Newcastle
FOR THE BEST
IN ELECTRONIC COMPONENTS
TEST EQUIPMENT
AND ACCESSORIES

**Marlborough
Electronic Components**

15, Waterloo Street Newcastle NE1 4DE
Tel: 618377

Open 9am-6pm Mon-Sat Easy Parking

STOCKISTS OF
TRANSISTORS RESISTORS
CAPACITORS I.C. DIODES
ELECTRONIC BOOKS Etc.



REPAIRS UNDERTAKEN

hi! performance hi! competitive hi!

**FULL HOUSE
OF MULTIMETERS**

Bench Models DL 705, 706, 720 and DF 760

TRIO


- 3½ and 4½ digit LED
- Rugged and Reliable
- 2 YEAR GUARANTEE
- Simple Operation - Auto Ranging
- Mains or Battery
- 7 Digit Frequency Counter
- Resolutions 1 and 0.1 mV
- DCV, ACV, DCA, ACA and Ohms
- Basic accuracy 0.8, 0.25, 0.1 and 0.05%
- Prices from just over £100 includes FREE Batteries, Hand Book and Test Leads



Hand Held Models HM101 and 102 Series, HC 601, 703, 6010 and 7030.

HC

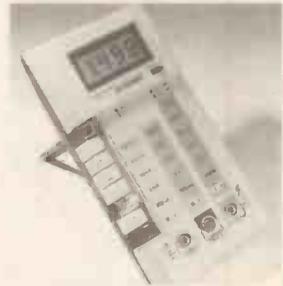- 3½ digit LCD and Analogue
- Colour coded front panel and edge switches
- High impact ABS with Tilt stand
- Safety features meets UL 1244
- Basic accuracy 0.6 and 0.2%
- Full Range of DCV, ACV, DCmA, ACmA and Ohms
- Audio Continuity Tone Plus 10A capability.
- Switched HI and LO ohms
- FREE Battery, Manual and Test Leads
- Analogue from approx £6 - Digital from approx £34



BBC GOERZ METRAWATT

MA1H, 2H, 3E and 5D. M2011, 2012, 2030, 2031 and 2032. Unigor 3N.

- Digital and Analog - Hand Held and Bench
- Huge LCDs - Many Safety Features
- Black, Rugged and Reliable
- 1 Year Guarantee
- 3½ and 4½ Digits
- Variable Viewing Angle - Hand free operation
- 20 Amp capability
- DCV, ACV, DCA, ACA, Ohms, Capacitance, Temp and Level in dBs
- Meet DIN 40050, 43780, 57410 or 57411 Requirements
- Prices from approx £27 includes FREE Batteries, manual and Test Leads



MIC

Hand Held Models 6000Z and 3300A

- 3½ digit LCD with easy single rotary control.
- 10 Amp., 1000V and 20M ohm capability.
- TRANSISTOR hFE measurement.
- Audible Continuity check and Diode Test.
- Optional accessories incl. Carry Case and Battery Eliminator.
- Fully Guaranteed for 12 months.
- Prices from approx £39 include Free Battery, Manual and Test Leads.



Prices do not include VAT or P + D.

House of Instruments
Clifton Chambers, 62 High Street
Saffron Walden, Essex CB10 1EE
Tel: (0799) 24922 Telex: 818750



hi! reliability hi! service hi! performance hi! competitive hi!

hi! reliability hi! service hi! performance hi! competitive hi!

hi! competitive hi!

House of Instruments Ltd.

POINTS OF VIEW

Feel like sounding off?
Then write to the Editor stating your Point of View!

Facing The Interface

I write to you in desperation. I have been an interested and happy reader of your brilliant mag since it first hit the newsgents' shelves - an 'Everyday Electronics' convert I be!

Since then I've built many projects, short circuits, etc. which have always eventually worked. Recently I purchased a ZX Spectrum, having read your "Spotlight on the Spectrum". I soon started on the I/O interface board (HE September '82). This time I cannot seem to get it to work! Hours have been spent with circuit diagram, manual and multimeter, but no result!

I beg of you - understanding that you are busy people - please take a look at the notes I have enclosed tabulating my results and in comparison with what you know to be happening inside the chips try to suggest reasons for my dilemma.

Testing Results:

Construction believed to be of good standard. Using PCB. Connection to Spectrum using ribbon cable rather than "piggy back" method. Using a 23 x 23 way connector. Polarising key position 3.

1) Components all correctly fitted in accordance with mag article, all solder joints sound. PCB tracks appear OK.

2) Computer functions correctly in normal mode.

3) Everything appears OK - things don't get warm!

4) The first PRINT IN 65503 gives correct 255, thereafter all input commands give result 56.

5) Outputs don't seem to change at all. Usually at OV4 (using 20kR/V meter).

6) Ribbon cable connections all seem OK and correct.

7) QUERY: the fact that pin 11B on the connector is not A15 on Spectrum but 10RQGE - is this supposed to be so?

*Thank you most sincerely,
A.D. Fraser,
Gosport,
Hants.*

It's difficult for us to tell, at the wrong end of a letter, whether the problem with a non-working project is because there is a fault in the design/printed circuit or whether there is a constructional error.

Some project errors do become apparent very quickly, while others turn up only after numerous queries from readers.

In the case of the relatively 'old' project such as this one, when no errors or mistakes have already been

brought to light, the most likely cause is a construction error.

In this case a clue is given by your query in para 7 of the testing results: pin 11B on the connector is not Spectrum address bit A15 - nor is it supposed to be the Spectrum 10RQGE line. It is, in fact, the ZX81's A15 line!

When using the I/O board with a Spectrum, this connection is non-operational since, as specified with Notes to the Circuit, the output of IC3c is NOT linked to IC3d.

It appears that you are confusing the alternative link-wires intended to adapt the boards for use EITHER with a Spectrum OR with a ZX81.

If you make sure that the links are wired in as per note "For IO Mapped Version (For Use With The Spectrum)", you should find that the project performs exactly as required.

Thank you by the way for an exemplary enquiry. If all our distressed enquirers made it quite so plain exactly what they had done with which project, we would have a much better chance of sorting their problems out for them. Also, going through your test procedures point by point often reveals oversights which help to sort out a problem straight away.

Note: you are nearly always closer than you think. Mr. Frazer had produced nine-tenths of his own solution and would only have needed a small flash of extra information to produce what we now hope is a final answer.

Personal Project

Dear Sir,

I'm a regular reader of your magazine, ever since I picked up your November '82 issue at the local newsagent. Your magazine is very interesting, especially your page.

I haven't built any of your projects so far because I haven't found any that suit my requirements. I'm particularly interested in the personal stereo cassette recorder and I'm looking forward to building one. I hope my idea will be considered. It will be different to play a machine you made by yourself.

*Yours sincerely,
Wing Lee.*

Certainly no shortage of ambition here! What can I say to this determined gent, who not only reads his Hobby even when he isn't building a project, but plans to build his own personal stereo? I positively quail to admit that we are not very likely to do

a personal stereo project, because the commercial companies have got it down to such a fine art that no magazine could possibly compete with them—not a hope! By the time all the parts which are too complicated to make at home have been provided (including the case) there would be little left to do but the assembly, and it would still be more expensive and less reliable than the ones you can buy in the shops. So it's not feasible as a magazine project. Sorry!

... And You Thought You Had Power Supply Problems

Dear Sirs,

Thank you for your January article. Supplied by overhead 220/380V lines in a rural area, power failures are commonplace here during frequent summer evening electrical storms. The failures last for plus/minus hours, but up to nine hours. Cooking is by gas stove from a cylinder. The refrigerator can cope. Dinner can be by candle light but it would be pleasant to have the use of the gramophone or TV for an hour or so. Using a clamp meter, the hifi averages less than the load of a 100W bulb, but can peak for brief intervals up to TV levels or higher momentarily in extreme cases. The TV has a high load switch on.

I use a car battery as a burglar alarm, fed by an SCR controlled variable charger. The battery is a standby for a vehicle, and is my basic power supply for electronics. It is coming to the end of its life after four years.

It seems that a 300W DC/AC inverter as suggested by you is the answer. However I am not sure if a sine wave is necessary. Fuses should not blow at peaks or switch on. Such a project would be welcome.

*On a related subject, so many circuits for AM radio, but what about a pure FM circuit from 12VDC supply, concentrating on purest sound with maximum simplicity, merely tuning and volume, assuming correct tone in the first place?
Yours faithfully,
E. Strang,
Krugersdorp,
South Africa.*

Fascinating to see how the other half of the world manages! Your project suggestions have been noted with thanks. On a general note, don't forget that if any reader has developed a circuit or is inspired to do so by someone else's suggestion, we

are always happy to have a look at them (the circuits, not the readers . . .) with possible publication in mind. Think of the glory! (It'll keep your mind off the money.)

Howling Error

Dear Sir,

Mr. Biggins' history brought back so many happy memories that it may seem a bit churlish to point out a mistake (*The Electronic Revolution*, HE '83):

The accumulator was used for the filament (cathode) not the anode (or "plate") which required a 100-volt dry battery the size of a brick.

The instability causing "howling" was due to feedback from the anode to the aerial circuit giving "reaction", and was a characteristic of the "superregenerative circuit", not the superheterodyne which came later.

Amateur radio construction before the war received its greatest setback when the highly efficient super heterodyne came into being in the early 30s, as they needed professional assistance to tune or "trim" the intermediate frequency transformer.

My first licence was a "provisional" dated October 1923.

Yours faithfully,
A.H. Jenkins,
Dringhouses,
York.

Thanks for these additions and corrections to "The Birth of Broadcasting" (HE February '83). Yes, the arrival of equipment with "non-user-servicable parts" does tend to discourage enthusiasts accustomed to being able to do everything themselves. But time usually brings a new crop of enthusiasts with some different approaches, or new ways of using the old ones, as we're seeing with amateur radio. We're told that general electronics is taking a knocking from home computing just at the moment, but I'd like to think that the new generation of computer wizards won't be content to sail on into the twenty-first century entirely ignorant of what goes on inside the micro, far from it. They'll probably all be reading "Hobby Chip Manufacture Today" or some such rag!

Recharging NiCads

Dear Sir,

I am interested in a NiCad charger working off my car battery.

The NiCad is seven amp hours' capacity, 12V nominal - so charging could be constant current OA2 to OA5 at 15V5.

What is the simple way of doing this? I did read in *Power Supply Projects* (see HE Bookshelf) about the DC step-up, ie IC1, TDA2030. This one is however OA1 to 9V. The car battery is, say, 14 to 11v.

Your advice will be greatly appreciated.

R. W. Kakébeeke,
Johannesburg,
South Africa.

Charging NiCad batteries from a car battery requires special circuitry — but don't worry. We're working on it for HE in the future.

Transmitter Needed

Dear Sir,

I have for some time now been reading your articles in *Hobby Electronics*. I am a student reading Vocational Education which includes *Electronics*. I read and carry out some simple projects.

Your article that really spurred me to write to you is that in HE October '82, 'Radio Rules'. Transmitters were the main theme. I was so excited and I thought by the time I am through, my dream of making my own transmitter would have materialised. But alas the whole text was just theories. I felt really disappointed I must say.

Please can you give me a transmitter circuit because I have not been able to lay hands on any. (I mean a functional circuit, a circuit with the component values inserted). I can make do with a low-powered transistor circuit or one using valves or both. Maximum power should be kept within the amateur range of 150W, because I hold an amateur licence.

Thank you.
Fleming Udofiah,
Abak,
Nigeria.

If you're going to build your own radio gear, you should look at a few possibilities. We and our radio-orientated relations here do not have a design which would obviously fulfil your needs without involving you in a lot of trouble and expense as well, and also we're not entirely clear what you are looking for — do you need a receiver as well, for instance, or do you already have one?

I suggest you contact the Radio Society of Great Britain, if there are no similar societies which can help you out in Nigeria, and tell them what you want. They will probably be able to advise you. The RSGB are now at Alma House, Cranbourne Rd., Potters Bar, Herts EN6 3JW.

The Tesla Controversy

Dear Sir,

I have just read your January issue (sea mail takes time to reach us here) and found the "Wireless Goes To War" article most interesting. However, surely there should be mention of Nikola Tesla, who transmitted signals by wireless before Marconi, and whose patents were upheld against Marconi?

On page 56 the caption to the lower right photograph says that the purpose of the "fan" is not known. I'm sure that the Science Museum must know that the "fan" is a wind

driven generator, used to power the wireless equipment. Battery power supplies with engine driven generators were not in use in 1914-1918!

Yours truly,
Martin Berner 9Y4TAM,
Trinidad,
The West Indies.

Tesla, it seems, was a genius whom the highest pinnacles of fame were doomed to elude. Consulting HE December '78 for its article "The Tesla Controversy", we find that Tesla seems to have discovered the Light Sword, for which credit subsequently went to Obi-wan Kenobi, and also invented the Tesla coil which, adds the article, is known as the Ruhmkorff coil.

More seriously, Tesla was the kind of genius whose greatest ideas were so far ahead of his time that they never achieved much in the way of commercial exploitation. This, of course, makes them difficult to fit neatly into any brief history of modern technology. But who knows where his theories will appear again in the future?

As for the now-famous fan, when you receive your March *Hobby Electronics* in May (by which time we shall be preparing the issue for August) you will find some pertinent comments from our resident balls of fuzz, and your mind will be at rest by the time you receive your October issue just in time for Christmas.

Don't Switch The Switch

Dear Sir,

I intend building the Touch Switch (HE October '81) and would like to install it in my car, running off 12 volts.

I would be very grateful if you could advise me of any modifications necessary and suggest a suitable relay to operate accessories such as fog lights, etc.

Yours faithfully,
G. Chamberlain,
Ebbw Vale,
Gwent.

There shouldn't be any problems with a 12V supply — just connect the switch directly. Check the current drawn by the lights you intend to use and make sure you have the right contacts. We're not auto-electric experts here, but suggest that around 10A would be suitable. The relay must be a 12V one, of course.

HE

Multicore makes solder

The Five Core Advantage

Only Multicore wire solders have a 5-core, or 4-core flux construction. The 5-cores identify non corrosive fluxes; the 4-core, water soluble fluxes.

If you were to slice through a section of Multicore cored solder you would see separate round cores of flux symmetrically arranged around its perimeter. Only a thin wall of solder separates the flux cores from the surface.

What are the advantages of the Multicore construction?

1. Because the flux is peripherally arranged it will react and flow faster.
2. Flux voids are eliminated with Multicore. That's why you can depend on continuity of the flux stream for complete wetting . . . every time.
3. Because wetting is faster, complete and uniform, you use less solder and transmit less heat to the joint area. With Multicore Solders, you get the highest purity metals, vigorous fluxing action and a wire solder that meets all applicable International standards.



Ersin Multicore

Contains 5 cores of non-corrosive flux.

Uses: For all electrical joints.
Handy Pack: **Size 19A** 60/40 tin/lead 1.22mm dia
£1.50 RRP

Tool Box Reel: **Size 3** 60/40 tin/lead 1.6mm dia
£4.37



Ersin Multicore

Contains 5 cores of non-corrosive flux.

Uses: Small transistors, components and fine wire.
Handy Pack: **Size PC115** 60/40 tin/lead 0.7mm dia
£1.61 RRP

Tool Box Reel: **Size 10** 60/40 tin/lead 0.7mm dia **£4.37**



Multicore Savbit

Increases the life of your soldering bit by 10 times.

Uses: For all electrical work.
Reduces copper erosion.
Handy Pack: **Size 5** 1.2mm dia **£1.38 RRP**

Tool Box Reel: **Size 12** 1.2mm dia **£4.37**



Digitise at up to 10 MHz. Store, then display on a UHF TELEVISION. Single shot Capture up to 250 KHz. Storage Facility for less than £100.

The Tele-Scope is a new concept in data capture utilising the latest Digitising techniques. The Tele-Scope acts — controls — displays much like a conventional scope but does much much more.

A kit version is available for £89 and a Built unit for £109. A manual is included and specialist parts are available separately.

Prices exclude V.A.T. at 15% with postage and packing at £2.95 inc. The manual is available separately for £1.50 inc. which is refundable on subsequent purchase of a unit.



NAME & ADDRESS

.....

Cheques PO. made payable, I enclose Cash £ p

HAWK ELECTRONIC TEST EQUIPMENT

Bircholt Road, Parkwood Industrial Estate, Maidstone, Kent ME15 9XT. 0622 686811

FEEL HEALTHIER WITH ZEPHION

Bring fresh clean air into your home with the Zephion Air Ioniser.



Air free from smoke, dust and other pollutants of modern day living can bring to many the relief of breathing comfortably once again.

We are confident that you will be delighted with the Zephion Air Ioniser, but if you are not entirely satisfied a full money back guarantee is available if items are returned in good condition within 28 days.

BUILD IT YOURSELF!

TO:- Dataplus Developments
81, Cholmeley road
Reading, Berks.
RG1 3LY TEL:- 0734 67027

NAME:-

ADDRESS:-

clip the coupon ✂

ZEPHION KITS • £24.15p
(Kits include all parts)

ZEPHION AIR TONERS
BUILT AND TESTED. • £34.50p

Money immediately refunded if items returned in good condition.


Prices include VAT & postage; allow 14 days for delivery. DATAPLUS

ing easy, fast and reliable

Multicore Solder Cream
Mixture of powdered 60/40 (tin/lead metal alloy and rosin flux).
Uses: Micro electronics and printed circuits.
Handy Tube: Size BCR 10
£1.73



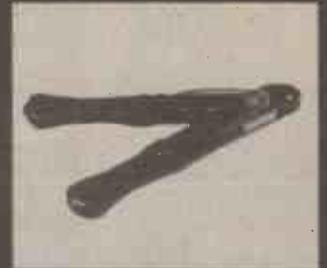Bib Wire Strippers and Cutters
With precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles.
Wire Strippers: Size 9
£2.88



Multicore Alu-Sol
Contains 4 cores of flux.
Uses: Suitable for aluminium and aluminium alloys. (non-electrical).
Handy Dispenser: Size HP27
1.6mm dia £0.99 RRP
Tool Box Reel: Size 4
1.6mm dia £7.82




Multicore Solder Wick
Absorbs solder instantly from tags and printed circuits with the use of a 40 to 50 watt soldering iron. Quick and easy to use, desolders in seconds.
Handy Pack: Size AB10
£1.43

Multicore All Purpose Handyman Solder Pak
Contains three types of solder for electrical, metal and aluminium repairs, all in handy easy to use dispensers.
Handy Pak: Size 8
£2.99



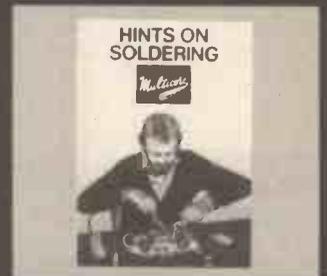All prices include VAT
Bib Audio/Video Products Limited,
(Solder Division),
Kelsey House, Wood Land End,
Hemel Hempstead, Hertfordshire. HP2 4RQ
Telephone: (0442) 61291 Telex: 823363



If you have difficulty in obtaining any of these products send direct adding 50p for postage and packing. For free colour brochure and Hints on soldering booklet send S.A.E.

XK113 MW RADIO KIT
Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires PP3 9V battery. IDEAL FOR BEGINNERS. £5.00

HOME LIGHTING KITS
These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

TDR300K Remote Control Dimmer £14.30
MK6 Transmitter for above £4.20

TO300K Touchdimmer £7.00

TS300K Touchswitch £7.00

TDE/K Extension kit for 2-way switching for TD300K £2.50

LD300K Rotary Controlled Dimmer £3.50

DVM/ULTRA SENSITIVE THERMOMETER KIT
This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital thermometer (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week
Price £15.50

NOW OPEN COMPUTER SHOWROOM

Hours: Mon-Fri 10am - 6pm
Sat 10am - 4pm

Jupiter ACE, DRAGON 32, BBC MODEL B, SPECTRUM, ORIC-1

We also stock peripherals and accessories - disc drives, printers, joy sticks etc. together with a wide range of books and the latest software for all the above computers including ZX81.
SEND S.A.E. FOR LIST TODAY!

3-NOTE DOOR CHIME
Based on the SAB0600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS. Order as XK 102.
£5.00

COMPONENT PACKS
PACK 1 650 Resistors 47 ohm to 10 Mohm - 10 per value £4.00
PACK 2 40 x 16V Electrolytic Capacitors 10µF to 1000µF - 5 per value £3.25
PACK 3 60 Polyester Capacitors 0.01 to 1µF/250V - 5 per value £8.55
PACK 4 45 Sub-miniature Presets: 100 ohm to 1 Mohm - 5 per value £2.90
PACK 5 30 Low Profile IC Sockets 8, 14 and 16 - pin - 10 of each £2.40
PACK 6 25 Red LEDs (5mm dia.) £1.25

LCD 3 1/2 DIGIT MULTIMETER
16 ranges including DC voltage (200 mv-1000 v) and AC voltage, DC current (200 mA-10 A) and resistance (0.2 M) + NPN & PNP transistor gain and diode check. Input impedance 10M. Size 155x88x31 mm. Requires PP3 9v battery. Test leads included **ONLY £29.00**

ELECTRONIC LOCK KIT XK101
This KIT contains a purpose designed lock IC, 10-way keyboard, PCBs and all components to construct a Digital Lock, requiring a 4-key sequence to open and providing over 5000 different combinations. The open sequence may be easily changed by means of a pre-wired plug. Size: 7 x 6 x 3 cms. Supply: 5V to 15V d.c. at 40uA. Output: 750mA max. Hundreds of uses for doors and garages, car anti-theft device, electronic equipment, etc. Will drive most relays direct. Full instructions supplied. **ONLY £10.50**
Electric lock mechanisms for use with latch locks and above kit **£13.50**

Have you got our **FREE GREEN CATALOGUE** yet?
NO! Send S.A.E. 6" x 9" TODAY!!
It's packed with details of all our KITS plus large range of SEMICONDUCTORS including CMOS, LS TTL, linear, microprocessors and memories; full range of LEDs, capacitors, resistors, hardware, relays, switches etc. We also stock VERO and Antex products as well as books from Texas Instruments, Babani and Elektor.
ALL AT VERY COMPETITIVE PRICES.
ORDERING IS EVEN EASIER - JUST RING THE NUMBER YOU CAN'T FORGET FOR PRICES YOU CAN'T RESIST.
5-6-7 8-9-10
and give us your Access or Barclaycard No., or write enclosing cheque or postal order. Official orders accepted from schools, etc.

DISCO LIGHTING KITS

DL 1000K
This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. **£14.60**

DLZ100K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. **Optional opto input DLA1 Allowing audio ("beat") -light response. £18.00**

DL3000K
This 3 channel sound to light kit features zero voltage switching, automatic level control & built in mic. No connections to speaker or amp required. No knobs to adjust - simply connect to mains supply & lamps. (1Kw/Channel) **Only £11.95**

FAST SERVICE · TOP QUALITY · LOW LOW PRICES
No circuit is complete without a call to
TK ELECTRONICS
11-13 Boston Road
London W7 3SJ

Add 65p postage & packing +15% VAT to total Overseas Customers;
Add £2.50 (Europe), £8.00 (elsewhere) for p&p
Send S.A.E. for further STOCK DETAILS.
Goods by return subject to availability.

OPEN 9am to 5pm (Mon to Fri)
10am to 4pm (Sat)

ALL PRICES EXCLUDE VAT

TEL: 01-567 8910 ORDERS
01-579 9794 ENQUIRIES
01-579 2842 TECHNICAL AFTER 3PM

ALL ABOUT ELECTRONICS

Our new **Beginner's Series** tells you all you'd like to know about electronics. From start to finish. All about components and circuits, all the theory you need to get started in the world of electronics.

Keith Brindley
3k3

TECHNICALLY SPEAKING, a semiconductor is an element which belongs to a particular group within the Periodic Table! Those readers who have studied Physics or Chemistry to any depth will know that the Periodic Table is simply a method of collating all known elements in tabular form. Figure 1 shows the Periodic Table and the elements in the shaded box: C (carbon); Si (silicon) and Ge (germanium) form the group we know as semiconductors. Although officially, carbon is a semiconductor, it is not used in the manufacture of electronic semiconductor components for technical reasons. All semiconductors are made with germanium, and particularly silicon.

Electronically speaking, the term *semiconductor* has been applied to the many electronic components which are constructed with the use of semiconductor materials. Electronic components belonging to the semiconductor family include: transistors, integrated circuits (ICs), diodes, thyristors, and triacs.

So that we can understand the operation of these semiconductor components, we must first look at the materials which are used in their construction — the elements of semiconductor materials themselves. Figure 2 represents a minute section of such an element — so minute that each circle in the figure is an atom of the element. Each atom is linked (bonded) to an adjacent atom by a covalent bond. A semiconductor atom has four electrons in its outside 'orbit' of electrons — and a covalent bond consists of one electron from one atom and one electron from the adjacent atom. So, a covalent bond is literally a shared pair of electrons.

Breaking The Bonds

An individual covalent bond is not a strong one and it is quite simple to

| | | | | | | | | | | | | | | | | | |
|--------------|----------|---------------------|----------|----------|----------|----------|----------|----------|----------|----------|----------|-----------|-----------|-----------|-----------|----------|----------|
| 1 H | | | | | | | | | | | | | | | | | 2 He |
| 3 Li | 4 Be | TRANSITION ELEMENTS | | | | | | | | | | 5 B | 6 C | 7 N | 8 O | 9 F | 10 Ne |
| 11 Na | 12 Mg | | | | | | | | | | | 13 Al | 14 Si | 15 P | 16 S | 17 Cl | 18 Ar |
| 19 K | 20 Ca | 21 Sc | 22 Ti | 23 V | 24 Cr | 25 Mn | 26 Fe | 27 Co | 28 Ni | 29 Cu | 30 Zn | 31 Ga | 32 Ge | 33 As | 34 Se | 35 Br | 36 Kr |
| 37 Rb | 38 Sr | 39 Y | 40 Zr | 41 Nb | 42 Mo | 43 Tc | 44 Ru | 45 Rh | 46 Pd | 47 Ag | 48 Cd | 49 In | 50 Sn | 51 Sb | 52 Te | 53 I | 54 Xe |
| 55 Cs | 56 Ba | 57* La | 72 Hf | 73 Ta | 74 W | 75 Re | 76 Os | 77 Ir | 78 Pt | 79 Au | 80 Hg | 81 Tl | 82 Pb | 83 Bi | 84 Po | 85 At | 86 Rn |
| 87 Fr | 88 Ra | 89† Ac | | | | | | | | | | | | | | | |
| * LANTHANONS | | 58 Ce | 59 Pr | 60 Nd | 61 Pm | 62 Sm | 63 Eu | 64 Gd | 65 Tb | 66 Dy | 67 Ho | 68 Er | 69 Tm | 70 Yb | 71 Lu | | |
| † ACTINONS | | 90 Th | 91 Pa | 92 U | 93 Np | 94 Pu | 95 Am | 96 Cm | 97 Bk | 98 Cf | 99 Ea | 100 Fm | 101 Md | 102 No | 103 Lr | | |

Figure 1. The Periodic Table of Elements. Those three elements in the shaded area, C (carbon), Si (silicon), Ge (germanium) form the group known as semiconductors.

remove an electron and use the electron as a charge carrier through the material, in the same way that electrons carry charge through any other conductor. The force required to break the bond and remove the electron is greater than the force needed with a good conductor say, copper, and so the semiconductor displays a certain amount of resistance to current flow. As we saw last month, of course, carbon (semiconductor) is actually used to make certain types of resistors.

But resistors are purely passive devices: if we apply a voltage across a resistor, a current will flow through it according to Ohm's Law and to the formula:

$$I = \frac{V}{R}$$

Remember?

It doesn't matter which way round the resistor or voltage is in the circuit, the effect will be the same. A resistor is passive and is acted upon by applied voltages and currents — the effect is dependent only on the size of the voltages and currents. The actual electronic components which have been given the name semiconductors (and remember this doesn't include carbon resistors!) are very much cleverer and more useful than this. Such semiconductor component are active: they can be used to act upon and control the applied voltages and currents.

We form these active components by combining slightly different types of semiconductor elements. These different semiconductor types are made by adding small quantities of impurities to change their electrical characteristics. Adding impurities to a semiconductor to change its electrical

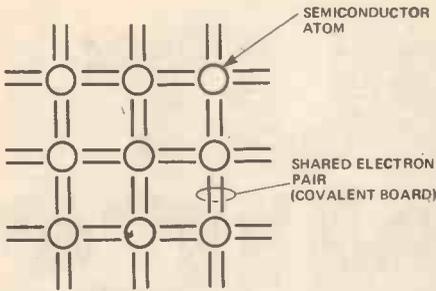


Figure 2. A minute section of semiconductor material showing atoms and covalent bonds.

characteristics is known as *doping*. Doping is done in two ways to make two separate types of semiconductor material:

- N-type — formed by adding atoms of elements with five electrons in their outside 'orbit'. Four of the electrons form covalent bonds with electrons from adjacent semiconductor atoms, leaving one electron unattached. These free electrons are used as charge carriers (Figure 3).
- P-type — formed by doping the semiconductor with atoms of elements with only three outer electrons as in Figure 4. These three electrons form covalent bonds with three adjacent atoms but what should be the fourth covalent bond has a missing electron — we call it a hole. Doped semiconductor holes can be thought of as charge carriers in exactly the same way that electrons can be thought of as charge carriers in type semiconductor materials. The holes are, of course, positively charged though (the missing negatively charged electron creates a positively charged hole, get it?).

The first active semiconductor device we shall look at is a diode. Diodes are the simplest of semiconductor devices: we call them two-terminal devices and they are formed by combining one layer each of n-type and p-type semiconductor as shown in Figure 5. At the junction between the two layers is a region known as the depletion region. The depletion region is an area where no charge carriers (either electrons or holes) exist because they are repelled by electrostatic charges.

Stop The Current

When a positive voltage is applied to the p-type layer (as in Figure 6) the effect of the electrostatic charges are lessened and the depletion region is narrowed until finally at a certain voltage (about 0V2 for germanium diodes, 0V7 for silicon diodes) it disappears and charge carriers can cross the junction and current flows. With a voltage applied the

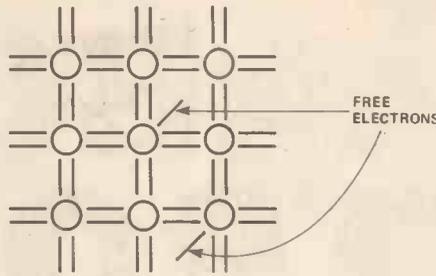


Figure 3. N-type semiconductor. Pure semiconductor material is doped with atoms which have five electrons in outer orbit. Four electrons pair with electrons of adjacent atoms leaving one free electron.

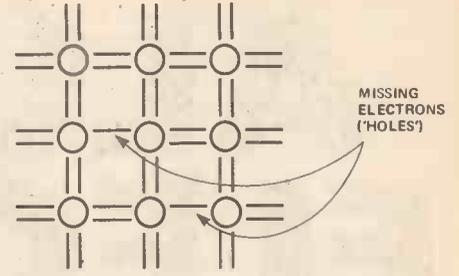


Figure 4. P-type semiconductor formed by doping pure semiconductor material with atoms having only three electrons in outer orbit. This leaves a hole for a missing electron.

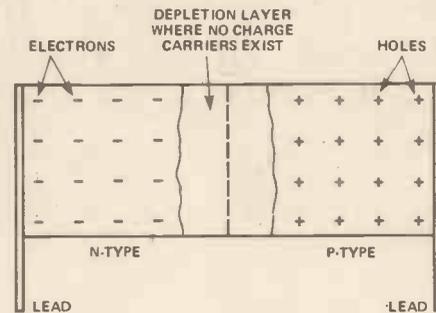


Figure 5. A diode, formed by a combination of P-type and N-type semiconductor material. No voltage is yet applied across the diode.

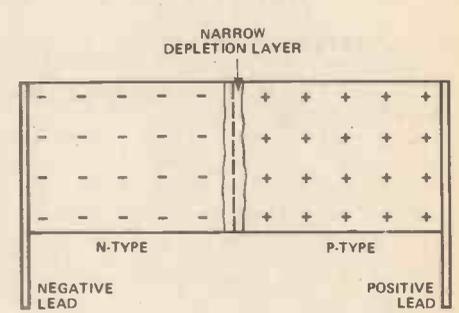


Figure 6. A diode with a positive potential applied to the P-type semiconductor layer. Above 0V7 (for a silicon diode) current flows.

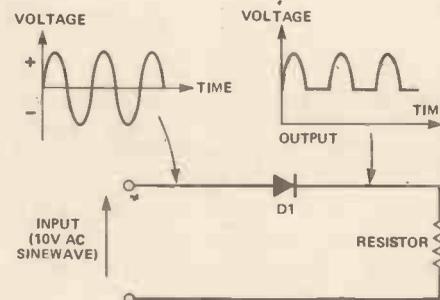


Figure 7. Application of an AC voltage to a diode gives a halfwave rectified output.

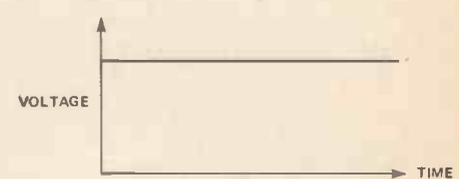


Figure 8. Output voltage of a cell is a very smooth DC.

other way round ie, negative to the p-type layer, holes are attracted towards the negative lead. A sort of electronic 'vacuum' is formed at the junction, the depletion region widens and no charge carriers cross the junction ie, no current can flow.

We have made a device which will allow current to flow in one direction but not in the other.

Now, how can we use such a device? A quick look at the circuit in Figure 7 shows one way. The AC input (alternating between positive and negative) after being applied to the diode has all of its negative half cycles removed. Incidentally, you should be able to see how the circuit symbol of a

diode in Figure 7 displays quite graphically how current passes in the direction of the arrow head but when voltage is reversed current cannot flow against the bar.

The output voltage of the circuit in Figure 7 is not AC because there are no negative cycles so it must be DC. Because only half a cycle of the total input waveform appears at the output we say the output is half-wave rectified DC. Admittedly its not a very smooth DC voltage. The voltage from a DC cell for example is perfectly smooth (Figure 8). But don't worry we'll see how we can improve the smoothness of the rectified DC waveform later.

By combining four diodes (Figure 9)

we form what is known as a bridge rectifier. This gives a full-wave rectified DC voltage output from an AC voltage input. Operation of the bridge rectifier can be explained with reference to Figure 10a and b.

Diodes In Pairs

Figure 10a shows how the circuit works when the AC voltage input is in a positive half cycle — point A is positive with respect to point B. Diodes D1 and D3 both conduct but diodes D2 and D4 do not. So current passes through diode D1 through the load resistor R1, and finally through diode D3. During the negative half cycle (Figure 10b) diodes D2 and D4 conduct, but diodes D1 and D3 do not. Now current passes through (from terminal B this time) diode D2, through the load resistor (in the same direction as in the positive half cycle) and finally through diode D4.

Any type of diode has a set of parameters (or limits) which define what the diode can be used for. For example, an application in which diodes are often used occurs in a meter when we wish to measure AC voltages and current. If you remember from the August issue of HE, the meters discussed were only used to measure DC voltages and currents. They simply would not work for AC! A meter can be used however, to measure AC voltages and currents if the AC voltage or current is rectified first (Figure 11). Now, the parameters of the diodes used in the bridge rectifier of Figure 11 must be great enough to ensure that any voltage or current measured will not damage the diodes. Say, for example that currents up to 1A and voltages up to 1000V ratings must be used. Other applications might call for higher ratings.

It's time now to consider how to improve the rectified DC voltages which diode rectifiers give and make them as smooth as possible. We do it with the addition of a single electronic component — and we have met the component already: the capacitor. Figure 12 shows a capacitor used to smooth the rectified DC output of a bridge rectifier. Use is made of the charge-holding capability of the capacitor to maintain the voltage at the peak of the full-wave rectified waveform during the trough till the next peak. When a capacitor is used in such a way it is called a smoothing (or more correctly speaking, a reservoir) capacitor, for obvious reasons.

Of course, simple addition of a capacitor to a rectifier circuit cannot completely remove all the peaks and troughs which occur, but they can be reduced to acceptable limits. There will always be, for example, a small variation in voltage — which is known as ripple — but as long as this is held within, say $\pm 100\text{mV}$, of the desired DC voltage then it is acceptable for most purposes. If we need a more accurate DC voltage then there are other component and complex circuits which can reduce ripple even further but we

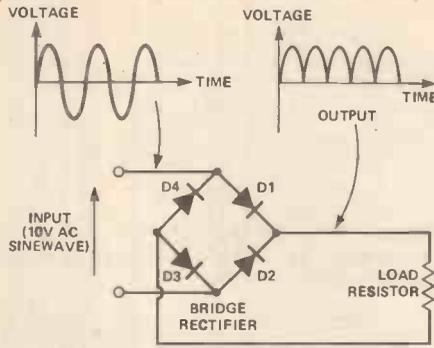


Figure 9. A bridge rectifier, consisting of four diodes, giving a full-wave rectified DC output from an AC sine wave input.

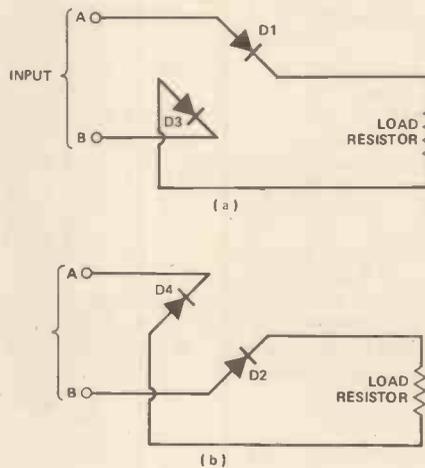


Figure 10: a) what occurs during the positive half cycle of input sine wave b) what occurs during the negative half cycle.

don't need to know about such methods yet. More about those another month.

Introducing Transistors

The diode is the simplest of active semiconductor devices — as we have already seen, it is a two-terminal device. The next type of semiconductor is a three-terminal one and its common name is a transistor. Within the family of transistors there are a number of different types. This month we shall look only at the variety known as bipolar transistors. In later months we shall look at other varieties such as field effect transistors (FETs) and also consider four-terminal semiconductors.

Bipolar transistors are made by combining three layers of doped semiconductor material so that two PN junctions (ie, combinations of p-type and n-type semiconductor) are very close together. There are two different ways this can be done of course:

- with the central layer of semiconductor being p-type and the

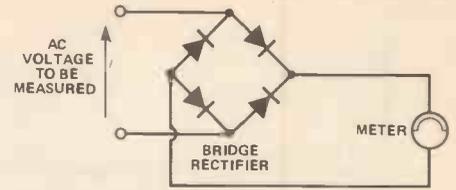


Figure 11. Measuring an AC voltage with a DC meter.

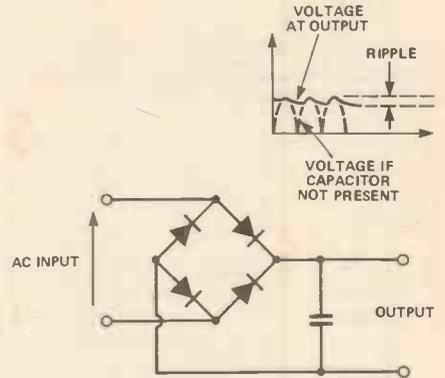


Figure 12. A reservoir capacitor used to smooth the full-wave rectified DC output of the bridge rectifier to an acceptable ripple.

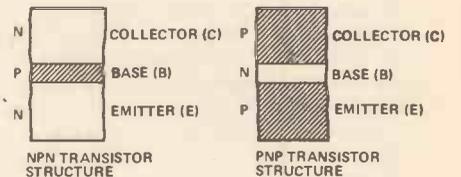


Figure 13. NPN and PNP transistor constructions.

outside layers n-type (forming what we know as an NPN transistor)

- with the central layer n-type and the outside p-type (forming a PNP transistor).

The central layer is always called the *base* and the outside layers are the *emitter* and the *collector*. Figure 13 shows both the NPN and PNP transistor constructions. Although the emitter and collector are made of the same type of material, there are usually constructional differences within the transistor which mean that their roles in a circuit cannot be reversed.

Circuit symbols for NPN and PNP transistors are shown in Figure 14. The arrowhead on the emitter of both types shows the general direction of current through the transistor when the emitter-base junction is forward biased (ie, the base is more positive than the emitter in an NPN transistor or the emitter is more positive than the base in a PNP transistor).

In the following discussion about transistor operation I am going to describe only the NPN transistor, but PNP operation is similar — only the

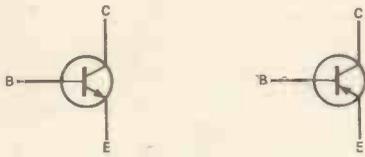


Figure 14. Circuit symbols for NPN and PNP transistors.

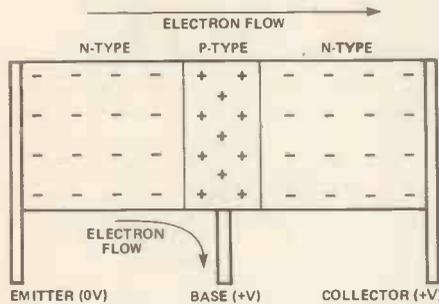


Figure 15. Basic format and applied potentials to an NPN transistor.

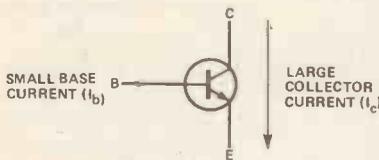


Figure 16. Summarised action of an NPN transistor.

Figure 20. Studying currents within a transistor circuit.

polarities of all applied voltages and currents should be reversed. I shall also assume use of silicon transistors, so a base-emitter voltage of 0.7V is used in all calculations. Figure 15 shows the basic format of an NPN transistor. The collector of the transistor is held at a positive potential to the emitter. The PN junction between base and emitter acts as a diode. So with no voltage applied to the base no current flows from base to emitter. However, if a positive voltage (greater than 0.7V) is applied to the base, the diode is forward biased and electrons flow from emitter to base (ie, current flows from base to emitter).

If the base is made thin, some of the electrons moving from emitter to base will carry on and move into the collector (because they are attracted to the positive potential of the collector). If the base is thin enough and the transistor construction is good a high percentage of the electrons entering the emitter (say 95%) will pass to the collector. Thus a larger current will flow from collector to emitter than that from base to emitter.

If we remove the positive voltage from the base the collector-to-emitter current (known as the collector current, I_c) stops. What we have made is a simple machine — in which a small current (created by the application of a

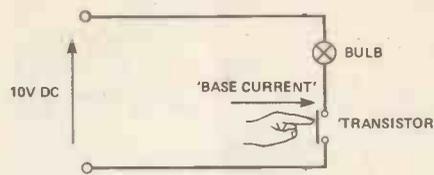


Figure 17. Likening the action of a transistor to that of a mechanical push-button switch.

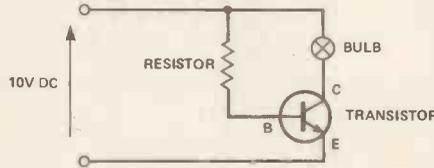


Figure 18. The circuit of Figure 17 — using a transistor.


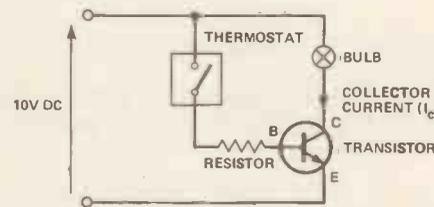


Figure 19. Automatically switching a transistor using a thermostat.

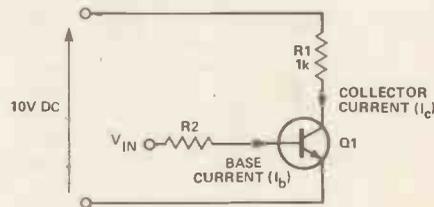

potential difference to the base) causes a large output current. This is summarised in Figure 16.

The ratio of the collector current, I_c , to the current from base to emitter (the base current, I_b) is:

$$\frac{I_c}{I_b} = \beta \text{ (the Greek letter, beta)}$$

and depends primarily on the type of transistor used. For example a common transistor, the BC109, has a β of about 200, ie for a base current of 0mA1 a collector current of about 20mA will occur.

Application of base current (I_b) effectively switches the transistor from being an insulator to a conductor. When the transistor has no voltage connected to its base the collector to emitter resistance is very high (about 20M). We say the transistor is 'off'. When a voltage is applied to the transistor base the resistance from collector to emitter is low (about 10R) and we say the transistor is on.

In a nutshell, that's all the transistor — any transistor — is really: a device, the resistance of which can be varied electronically (by the voltage to its base): a *transferrable resistor* — **TRANSISTOR** — get it?

Switching Circuits

When the resistance of a transistor is varied from high to low by the application of a voltage to its base, the transistor is acting as an electronic switch, and another way of looking at the operation of a transistor is shown in Figure 17. The 'transistor' is shown graphically as a push-button switch, and the 'base current' is shown as a finger about to operate the switch. As the finger (base current) operates the switch (transistor) the resistance of the switch goes from high (when it is open-circuit) to low (when it is closed-circuit) and the current passes through the bulb, lighting it.

Figure 18 shows the same circuit but replaces the switch and the finger with a transistor. Circuit operation, however, is identical: apply a base current and the bulb lights. The base current can, in fact, be supplied from the positive voltage supply to the bulb as in Figure 18. Note the resistor in series with the base, to limit the base current to a maximum level — too large base currents will cause high power dissipation which will irreparably damage the transistor.

Base current could be provided by say, a thermostat (which is simply a temperature controlled switch) as in Figure 19, so that when temperature falls below a certain minimum, the thermostat closes providing base current and automatically turning on the bulb. Of course, it might not be a bulb: it could be a heating pump, or a boiler etc.

It really doesn't matter what provides the base current to the transistor — it could be temperature (as in the thermostat example above), a magnetically operated reed-switch, another transistor, a computer, or whatever — the fact is that in this type of circuit the transistor is operating as an automatic electronic switch with only two states: on and off. When base current flows, the transistor is on; when no base current flows, the transistor is off.

Let's look further into this transistor switch circuit. Figure 20 shows a transistor with a 1k collector resistance, (ie, the resistor between the transistor collector and the positive supply rail, R_1). This could be a bulb as in Figure 18, or a relay which will turn almost anything on and off! Resistor R_2 is the transistor base resistor.

Calculating The Current

First we will consider the collector current. I said earlier on that the collector current, I_c , was a function of β and the base current, I_b :

$$I_c = \beta \times I_b$$

Well, I_c is also a function of the collector resistor, R_1 . Take for example the case when the transistor is on; its resistance is low (about 10R) and can be neglected compared with R_1 (1k). So the collector current is defined primarily by the collector resistor and the power supply

voltage by the formula (which, of course, we all know!):

$$I_c = \frac{V}{R}$$

$$= \frac{10}{1000} = 10\text{mA}$$

Now we can calculate the required base current to turn on the collector current — we know that the transistor $\beta = 100$ so for a collector current of 10mA, the base current needs to be:

$$I_b = \frac{I_c}{\beta} = \frac{10 \times 10^{-3}}{100} = 100\mu\text{A}$$

(Not a lot!) The base resistor, R2 can now be calculated as being:

$$R_2 = \frac{VR_2}{I_b}$$

where VR2 is the voltage across R2. This voltage depends on two things; the voltage at the base, and the voltage at the input V_{in} . The voltage at the base is easily worked out because it is the voltage at the emitter (0V) plus the base-emitter junction is a diode — remember?. Let's say the voltage V_{in} is to be 5V, then the voltage across R2:

$$VR_2 = 5 - 0V_7 = 4V3$$

Therefore

$$R_2 = \frac{4V3}{100 \times 10^{-6}} = 43000\Omega = 39k \text{ (NPV)}$$

So, with a base current of 100uA, 10mA of a collector current flows and, with no base current, no collector current flows. This is exactly what we wanted from our transistor switch.

In an electronic switch mode, transistors are either fully on (known as saturation) or fully off. But what happens in between these two limits? Let's look at the circuit of Figure 20 again but apply an input voltage of V_{in} of say 2V65. This sounds inconvenient but when we calculate the voltage across the base resistor, R2:

$$2V65 - 0V_7 = 1V95$$

and calculate the base current:

$$I_b = \frac{VR_2}{R_2} = \frac{1.95}{39 \times 10^3} = 50\mu\text{A}$$

then we see that the collector current:

$$I_c = \beta \times I_b = 5\text{mA}$$

ie, half the collector current of the previous calculation. In other words the transistor is half on. This illustrates another type of transistor operation — linear mode operation.

A transistor operating in its linear range can be likened to a control valve in a water system. If no base current flows the 'control valve' is closed and no collector current flows. But when the

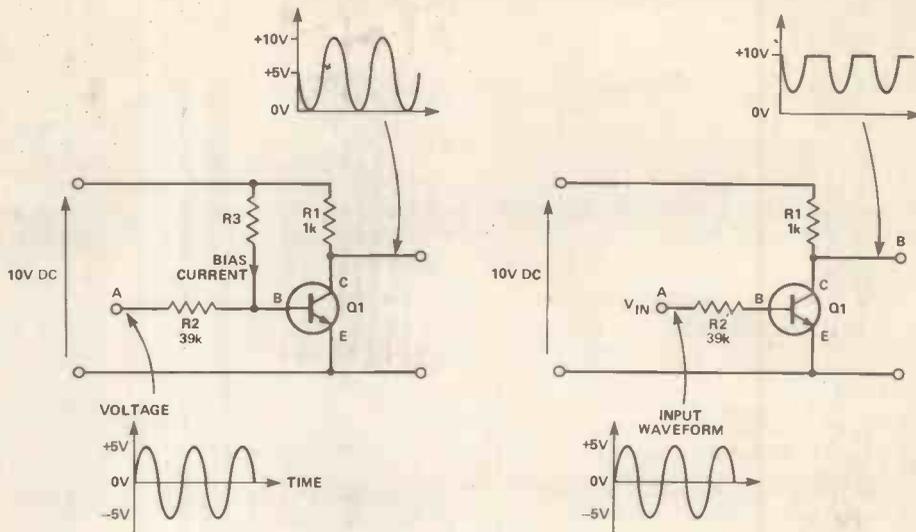


Figure 21. Attempting to use the circuit of Figure 20 to amplify a AC sinewave.

Figure 22. Turning the transistor half on, by applying a fixed bias current to the base, allows the transistor to be used with AC input.

'control valve' is half open, or a quarter open, or an eighth open; half the full collector current, a quarter, or an eighth the full collector current flows. We thus have linear mode transistor operation, the most important point of which is that the large collector current is controlled by a small base current. We have developed a very simple current amplifier generating a large current from a small current the gain of which is the transistor's β over the linear range, ie:

$$\text{amplifier gain} = \beta = \frac{I_c}{I_b}$$

The amplifier circuit of Figure 20 is effectively a DC circuit only — it will not operate with AC voltages and currents Figure 21 shows why not. The input to point A, ie, the input voltage, V_{in} to the transistor is a sinewave, varying from +5V to 0V to -5V. During the positive half cycles the transistor is operational in its linear range and its resistance varies from maximum (about 20M) to minimum (about 10R) as the sinewave varies. The lower the resistance of the transistor, the lower the voltage point β because the effective resistance of the transistor in series with the collector resistance R1 forms a voltage divider. So the output voltage (over the positive half cycle of the input sinewave) is the inverse of the input voltage!

I Say, AC, I See!

But what happens as the input voltage varies over the negative half cycle? Well, the transistor is off (and can't go any more off) so the output voltage stays at maximum. Thus the output voltage waveform is an inverse half-wave rectified version of the input voltage waveform. An AC current cannot therefore be amplified by this simple circuit. So, do we amplify an AC current?

If a fixed direct current (which

permanently turns the transistor half on) is applied to the base, at the same time as the sinewave output is applied then the collector current will vary up and down with the base current and all parts of the AC input waveform will be amplified. Figure 22 shows one way of supplying this fixed DC input. Because the collector resistor, R1, and the power supply voltage (10V) are the same as in Figure 20 we know that a collector current of 5mA means the transistor is half on. And with a β of 100 we know that the required current is 50mA to turn the transistor half on. Thus the voltage across the resistor, R3 is:

$$10 - 0V_7 = 9V3$$

So the required resistor value:

$$R_3 = \frac{VR_3}{I_b} = \frac{9V3}{50 \times 10^{-6}} = 186000$$

$$= 180K \text{ (NPV)}$$

The current to turn the transistor half on is known as the bias current, resistor R3 is the bias resistor, and the standing collector current is known as quiescent current.

We have now designed a very simple AC current amplifier from a transistor, with a gain β , which is also a voltage inverter.

That's about all for this month — we've covered a lot of ground and learnt some new ideas about electronic semiconductor components. In the next few months you'll see other semiconductor circuits and other semiconductor components, particularly those in the large family of integrated circuits (ICs), but the basis of semiconductors (ie, this month's topic) is applicable to them all.

Electronics

Third edition

W P Jolly

This exceptionally readable handbook explains simply and clearly the essentials of modern electronics. It looks first at the fundamental concepts — the electron, energy and waves — and the general principles of electronics. It then explains the nature and use of such materials as the valve, the junction diode, the transistor and electronic circuits. The most recent developments are also described. The new edition has been completely reset, and includes a glossary of technical terms.


0 340 32976 9 Illus. £2.95

Available through all good bookshops

Teach Yourself Books

Mill Road, Dunton Green, Sevenoaks, Kent TN13 2YD

WHITESOLD

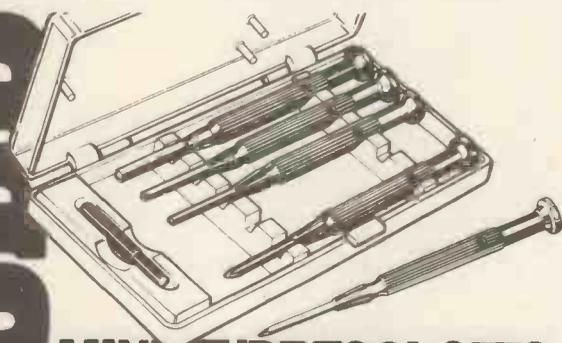

MINIATURE TOOL SETS AT MINIATURE PRICES

Ideal for work on optical and electronic equipment, instruments and models. Japanese made, top quality metric tools in hardened and tempered steel, with fitted plastic cases. Swivel-top, chromium-plated brass handles. Not to be confused with similar cheap non-Japanese sets.

SCREWDRIVER SET 113. 6 plain screwdrivers, blades 0.9, 1.2, 1.8, 2.3, 3.0 and 3.5mm. Price **£2.70.**

SOCKET SET 227. 5 socket spanners, 3.0, 3.5, 4.0, 4.5 and 5.0mm. Price **£2.80.**

CROSSPOINT/HEXAGON SET 305. 2 Japanese crosspoint screwdrivers, sizes 0 and 1. 3 Hex. key wrenches 1.5, 2.0 and 2.5mm. Price **£2.70.**

COMBINATION SET 228. 5 open spanners 4.0, 4.5, 5.0, 5.5 and 6.0mm. 5 socket spanners 3.0, 3.5, 4.0, 4.5 and 5.0mm. 2 crosspoint screwdrivers bit sizes 0 and 1. 3 screwdriver bits 1.5, 2.5 and 3.5mm. 3 Hex. keys 1.5, 2.0 and 2.5mm. 1 scriber. 1 swivel-top driver/holder. Price **£4.83.** All prices include postage and 15% VAT.

Ring for Access/Barclaycard Sales or send remittance to:

Light Soldering Developments Limited, 97-99 Gloucester Road, Croydon, Surrey CR0 2DN. Tel: 01-689 0574.



EASY ADD-ONS
for ZX81-
SPECTRUM-ACE

NEW



17 exciting electronic projects to build and run on your own micro.

- LIGHT PEN
- PICTURE DIGITISER
- KEY PAD
- MODEL CONTROLLER
- WEATHER STATION
- + OTHER EXCITING & INTERESTING PROJECTS

REALISE THE REAL WORLD POTENTIAL OF YOUR MICRO.

A newly released book written by well known author Owen Bishop and published by Bernard Babani gives fully descriptive details on how to build all 17 projects — all are fairly simple and inexpensive to construct — The most complex component (the DECODER) is supplied in kit form ready to assemble with all components and plated through PCB. — Components for the projects are readily available locally or found in your workshop drawers.

Once assembled and connected to your micro the decoder is able to run any or all of the projects simultaneously.

Simple Programmes are included to get you started but of course the more experienced programmer can have hours of fun writing complex programmes to take full advantage of these easy but exciting projects.

Please Send By Return (allow 28 days for delivery)


| QTY | REF | DESCRIPTION | PRICE | TOTAL |
|-----|---------|-------------------------------------|--------|-------|
| | HB/2000 | "EASY ADD-ONS" + DECODER KIT & BOOK | £24.00 | |
| | HB/2001 | "EASY ADD-ONS" BOOK ONLY | £3.00 | |
| | HB/2002 | DECODER KIT ONLY | £22.00 | |
| | HB/2003 | DECODER PCB ONLY | £8.00 | |
| | | TOTAL | | |

Price inclusive of VAT & carriage. Please allow 21 days for delivery. Cheques, PO's or signed Access orders welcomed.

Please Send Full Hobbyboard Mail Order Catalogue with full range of PCB materials & Hardware

Name

Address

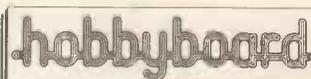

a division of
KELAN ENGINEERING Ltd
Hookstone Park
Harrogate, N. Yorks

complete P.C.B. workshop

HE/10/83

This is the Great

Hobby Electronics

Computer-Controlled Model Railway COMPETITION

Sponsored by Oric Products International Ltd., Beatties of London Limited and ASP Software (a division of Argus Specialist Publications Ltd.).

WHEN it was proposed that there should be a Grand Computer Controlled Model Railway Competition for the 1983 Breadboard exhibition, we rapidly became bogged down with seemingly endless complications. We spent most of the time during discussions simply explaining jargon: what, to a computer hardware man, is a "dead frog"? Something unpleasant by the roadside, was the popular answer! On the other hand our modelling consultant was somewhat bemused by the many acronyms that punctuate conversations between computer buffs: who, or what is a PIA? Bits of what? What is a multiplexer, and so on, and on, and on . . . !

In the end we were all quite bewildered — but this confusion ultimately gave us the clue to our Computer Controlled Model Rail Competition: no one, it seems, truly knows how best to marry a computer to a complex model rail layout or what it should do and, particularly, how it should be done.

We decided, finally, that the simplest and best approach would be to throw the thing wide open, with only a few essential restrictions. The only rule of the competition, then, is that the winning entry will be that which demonstrates the most ingenuity,

usefulness and practicality in adapting a modern home computer to control a model railway layout — the what, how and why we quite happily leave to our readers!

The essential limitation we felt obliged to impose is that the layout should measure no more than 6ft by 2ft — in other words, something that can be transported to the Breadboard exhibition in Hammersmith in late November this year.

We anticipate that most of the entries will be from constructors who have an existing computer interfaced layout, but the competition is open to all comers so anyone who wants to "have a go" will be welcome in the lists. For the benefit of those who fancy their chances at the Grand Prize, here are a few ideas that resulted from the meeting of the minds in Hobby's editorial offices (we won't mention the ideas that evolved later, down at the Royal Georget).

● A fairly simple software application would be to write a program for storing and modifying timetables and operating schedules; an extension of this idea would be an interface to position sensing circuits so that an operator

would know not only when the next train was due to leave, but also when it was safe to start down the track.

● One of the most obvious ideas proposed was to program a mimic board which could show not only the track layout but the condition of signal lights and with 'train in section' indication: colour would be necessary for user-friendliness!

● Ways to adapt microprocessor technology to model train control: one option that might be easily constructed would be to computer-control sections of track rather than individual trains. However completely automatic running is not the goal of most railway modellers, so any system should allow lots of room for the operator to control the layout himself.

And that is about the limit of the ideas we came up with before brain fog set in. We'll leave it to the inventiveness and competitive spirit of our readers to stun the judges with brilliant projects we should have thought of . . . but didn't!





FIRST PRIZE

Hot off the production line, an Oric 48K colour computer, donated by Oric Products International Ltd.



SECOND PRIZE

Gift vouchers to the value of £50, redeemable on model rail products at any Beatties of London shop.



THIRD PRIZE

£25 worth of games and utility program tapes from ASP Software.

Entry forms, together with an entrance fee of £1.00 (cheque or money orders only, please) should be sent to:
The Exhibition Manager, BB83, ASP Exhibitions, 145 Charing Cross Road, London WC2H 0EE.
 Closing date is 31st October 1983. Judging will take place at Breadboard '83, Cunard Hotel, Hammersmith, London W6, on either Wednesday 23rd or Thursday 24th November 1983. Entrants will be informed of the day on which they will be required to present their layouts at the exhibition. Finalists will be asked to demonstrate their layouts at some time(s) during the open days of Breadboard '83 (25, 26, 27th November) and layouts will be available for collection between 1600 and 1800 hours on Sunday 27th November. **The judges decision will be final and no correspondence will be entered into.**

Entry Form

PLEASE USE BLOCK CAPS

NAME:

ADDRESS:

TEL NO: AGE ON 30TH NOV. 1983:

BRIEF DESCRIPTION OF LAYOUT AND FUNCTIONS:

SCALE: SIZE OF LAYOUT: (MAX 6FT X 2FT):

COMPUTER USED:

COMMERCIAL PERIPHERALS USED:



electronize

AUTO-ELECTRONIC PRODUCTS

KITS OR READY BUILT

TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION

IS YOUR
CAR AS
GOOD
AS IT
COULD
BE ?



- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
- ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains it from service to service.
- ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs. where the ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engine's maximum (even with 8 cylinders).
- ★ Is the **PERFORMANCE SMOOTH**. The more powerful spark of Total Energy Discharge eliminates the "near misfires" whilst an electronic filter smooths out the effects of contact bounce etc.
- ★ Do the **PLUGS** and **POINTS** always need changing to bring the engine back to its best? Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.
- ★ **TOTAL ENERGY DISCHARGE** is a unique system and the most powerful on the market - 3 1/2 times the power of inductive systems - 3 1/2 times the energy and 3 times the duration of ordinary capacitive systems. These are the facts:
Performance at only 6 volts (max. supply 16 volts)
 SPARK POWER — 140W, SPARK ENERGY — 36mJ
 SPARK DURATION — 500µs, STORED ENERGY — 135mJ
 LOADED OUTPUT VOLTAGE
 50pF load — 38kV, 50pF + 500k — 26kV
 We challenge any manufacturer to publish better performance figures. Before you buy any other make, ask for the facts, its probably only an inductive system. But if an inductive system is what you really want, we'll still give you a good deal.
- ★ **All ELECTRONIZE** electronic ignitions feature:
EASY FITTING, STANDARD/ELECTRONIC CHANGEOVER SWITCH, STATIC TIMING LIGHT and DESIGNED IN RELIABILITY (14 years experience and a 3 year guarantee).
- ★ **IN KIT FORM** it provides a top performance system at less than half the price of comparable ready built units. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2µF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

Most NEW CARS already have electronic ignition. Update YOUR CAR

PROTECT YOUR CAR WITH AN ELECTRONIZE ELECTRONIC ALARM



- ★ 2000 **COMBINATIONS** provided by an electronic key - a miniature jack plug containing components which must match each individual alarm system. (Not limited to a few hundred keys or a four bit code).
- ★ **60 SECOND ALARM PERIOD** flashes headlights and sounds horn, then resets ready to operate again if needed.
- ★ **10 SECOND ENTRY DELAY** allows owner to dis-arm the system, by inserting the key plug into a dashboard mounted socket, before the alarm sounds. (No holes in external bodywork, fiddly code systems or hidden switches). Re-closing the door will not cancel the alarm, before or after it sounds, the key plug must be used.
- ★ **INSTANT ALARM OPERATION** triggered by accessories or bonnet/boot opening.
- ★ **30 SECOND DELAY** when system is armed allows owner to lock doors etc.
- ★ **DISABLES IGNITION SYSTEM** when alarm is armed.
- ★ **IN KIT FORM** it provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, CMOS IC's, random selection resistors to set the combination, in fact everything down to the last nut and washer plus easy to follow instructions.

**FITS ALL 12 VOLT NEGATIVE EARTH VEHICLES.
SUPPLIED COMPLETE WITH ALL NECESSARY LEADS
AND CONNECTORS PLUS TWO KEY PLUGS**

Don't Wait Until Its too Late ~
Fit one NOW!

fill in the coupon and send to:

ELECTRONIZE DESIGN Dept E · Magnus Rd · Wilnecote · Tamworth · B77 5BY · tel 0827 281000

TOTAL ENERGY DISCHARGE (6 or 12 volt negative earth)

- Assembled ready to fit £26.70 £19.95
 D.I.Y. parts kit £15.90 £14.95

TWIN OUTPUT for cars and motor cycles with dual ignition

- Twin, Assembled ready to fit £36.45 £29.95
 Twin, D.I.Y. parts kit £24.55 £22.95

INDUCTIVE DISCHARGE (12 volt only)

- Assembled ready to fit £15.95 £12.75

Prices Include VAT.

P+P £1-00 (UK)

CAR ALARM

- Assembled ready to fit £37.95
 D.I.Y. parts kit £24.95

I enclose cheque/postal order OR debit my Access/Visa card

VISA ACCESS DEBIT CARD

Name _____

Address _____

Code _____

TRUMP CARD

With the Trump Card, hardware designed for the Sinclair Spectrum or ZX81 can be used with the Jupiter ACE (with very few exceptions). Simple to make, it will add enormously to the ACE's versatility as a controller.

Colin Freestone

TRUMPCARD is a simple but very effective project for owners of the ever more popular Jupiter Ace computer. At present the Ace, even with the recent release of 16K and 48K RAM packs, still does not yet enjoy large scale hardware support, such as that available for the ZX81 or Sinclair Spectrum, that would allow the Ace user to extend the range of his computer activities.

The Ace, a versatile and useful computer, is becoming particularly popular for control applications. In time, a wide range of hardware accessories will no doubt become available for it (such as the RAM I/O board and the Joystick Controller in last month's issue of *Hobby Electronics*) but in the short term, users who might like to experiment with speech synthesizers and similar devices are bound to be somewhat frustrated.


The solution, though, is quite simple. The Ace and the ZX81 are very similar in many ways, and so it has proved simple enough to design an interface board that will allow most ZX81 add-ons to be used with the Ace.

Trumpcard is simply a small dual-sided PCB edge connector that can be wired to re-route the ZX81 signal lines to correspond with the corresponding Ace signals. The only limitation is since the Ace does not produce the control signals ROMCS and RAMCS (ROM and RAM Chip Select), Trumpcard cannot be guaranteed to operate reliably with an ZX add-on that makes use of these signals.

Construction

The connections between the two sets of edge connectors are made with short lengths of coloured wire — single stranded 'bell wire' is best. Coloured wire makes it easier to keep track of the links as they are made and also to fault-find, if this is later necessary. The colour scheme is optional, but that outlined in Table 1 is logical and consistent.

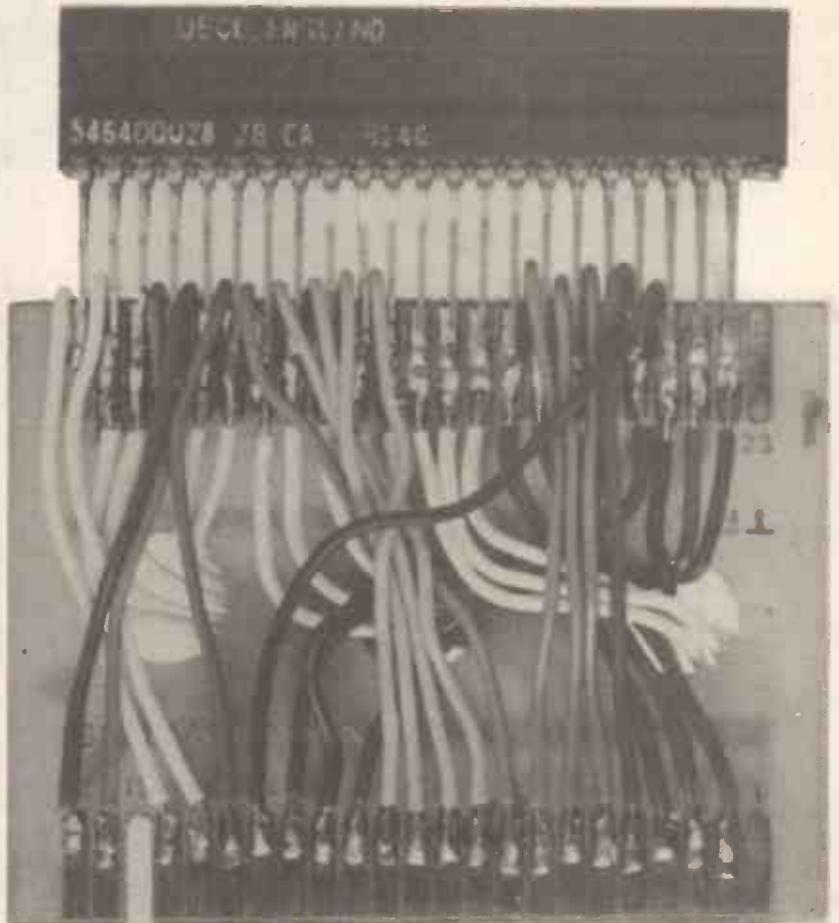The first step in assembling the Trumpcard is to modify the edge connector socket so that it can be wired onto the PCB. The socket is a



23+23 way (double sided) type with the keyway at one end and must have wire-wrap length pins.

Take a pair of long-nosed pliers and insert one jaw between the rows of pins; grasp one row firmly between the jaws and bend the pins outward by about 30° (you may need two bites at this, carrying out the operation from either end if the jaws are not long enough). Then bend the opposite row outwards by the same amount.

When this has been done, the next step is to bend the pins back inwards, but this time from the base so that the ends of all the pins all lie parallel and just far enough apart for the PCB to slip between the rows.

To achieve uniform bending in the second operation, hold the body of the connector against the edge of a table with the bottom row lying flat on the table surface; then push down, gently but firmly, bending the pins inward. Repeat for the other row and continue to bend both rows until the PCB just fits between the rows.

Now with the polarising key on the right and the ZX key-slot at your top left, align the socket with the Ace edge connectors on the PCB, making sure that they all line up accurately. Push the pins onto the tracks, but leave about 5mm of free copper for soldering on the link wires. If the pins have been bent correctly, they will all lie neatly against the copper pads,

TABLE 1A

| ACE PIN | TRUMPCARD NUMBER (ACE EDGE) | SIGNAL | 2K PIN NUMBER | TRUMPCARD NUMBER (ZX EDGE) | COLOUR | LENGTH (INCHES) | ROUTE |
|---------|-----------------------------|--------|---------------|----------------------------|--------|-----------------|--------|
| 1A | 23A | OV | 4B | 20B | WHITE | 2 1/4 | EDGE |
| 2A | 22A | OV | 5B | 19B | WHITE | 2 1/4 | EDGE |
| 3A | 21A | +9V | 2B | 22B | GREY | 2 1/4 | EDGE |
| 4A | 20A | +5V | 1B | 23B | GREY | 2 1/4 | EDGE |
| 5A | 19A | CLK | 6B | 18B | PINK | 2 1/4 | EDGE |
| 6A | 18A | A11 | 15B | 9B | ORANGE | 2 1/4 | EDGE |
| 7A | 17A | A12 | 14B | 10B | YELLOW | 2 1/4 | EDGE |
| 8A | 16A | A13 | 13B | 11B | YELLOW | 2 1/4 | EDGE |
| 9A | 15A | A14 | 12B | 12B | YELLOW | 2 1/4 | EDGE |
| 10A | 14A | A15 | 11B | 13B | YELLOW | 2 1/4 | EDGE |
| 11A | 13A | D4 | 10A | 10A | YELLOW | 1 1/4 | DIRECT |
| 12A | 12A | D3 | 9A | 9A | ORANGE | 1 1/2 | DIRECT |
| 13A | 11A | D5 | 8A | 8A | GREEN | 1 1/2 | DIRECT |
| 14A | 10A | A2 | 9B | 15B | BROWN | 2 | HOLE 2 |
| 15A | 9A | A10 | 16B | 8B | ORANGE | 2 1/4 | EDGE |
| 16A | 8A | A9 | 17B | 7B | ORANGE | 2 1/4 | EDGE |
| 17A | 7A | A8 | 18B | 6B | ORANGE | 2 1/4 | EDGE |
| 18A | 6A | A7 | 19B | 5A | RED | 2 1/4 | EDGE |
| 19A | 5A | A0 | 7B | 17B | BROWN | 2 1/4 | EDGE |
| 20A | 4A | D1 | 5A | 5A | BROWN | 2 1/4 | DIRECT |
| 21A | 3A | D6 | 7A | 7A | BLUE | 2 1/4 | DIRECT |
| 22A | 2A | WE | NC | NC | — | — | — |
| 23A | 1A | (SLOT) | — | — | — | — | — |

TABLE 1B

| ACE PIN | TRUMPCARD NUMBER (ACE EDGE) | SIGNAL | ZX PIN NUMBER | TRUMPCARD NUMBER (ZX EDGE) | COLOUR | LENGTH (INCHES) | ROUTE |
|---------|-----------------------------|--------|---------------|----------------------------|--------|-----------------|--------|
| 1B | 1B | NL | — | — | — | — | — |
| 2B | 2B | INT | 11A | 11A | PINK | 2 | HOLE 1 |
| 3B | 3B | NMI | 12A | 12A | PINK | 2 | HOLE 1 |
| 4B | 4B | HLT | 13A | 13A | PINK | 2 | HOLE 1 |
| 5B | 5B | MREQ | 14A | 14A | PINK | 2 | HOLE 1 |
| 6B | 6B | IORQ | 15A | 15A | PINK | 2 | HOLE 1 |
| 7B | 7B | RD | 16A | 16A | PINK | 2 | HOLE 1 |
| 8B | 8B | WR | 17A | 17A | PINK | 2 | HOLE 1 |
| 9B | 9B | BUSAK | 18A | 18A | PINK | 2 | HOLE 2 |
| 10B | 10B | WAIT | 19A | 19A | PINK | 2 | HOLE 2 |
| 11B | 11B | BUSRQ | 20A | 20A | PINK | 2 | HOLE 2 |
| 12B | 12B | RESET | 21A | 21A | PINK | 2 | HOLE 3 |
| 13B | 13B | M1 | 22A | 22A | PINK | 2 | HOLE 3 |
| 14B | 14B | RFSH | 23A | 23A | PINK | 2 | HOLE 3 |
| 15B | 15B | A6 | 20B | 4B | RED | 1 3/4 | DIRECT |
| 16B | 16B | A5 | 21B | 3B | RED | 1 3/4 | DIRECT |
| 17B | 17B | A4 | 10B | 2B | RED | 1 3/4 | DIRECT |
| 18B | 18B | A3 | 10B | 14B | BROWN | 2 | DIRECT |
| 19B | 19B | A1 | 8B | 16B | BROWN | 2 | DIRECT |
| 20B | 20B | D0 | 4A | 4A | BLACK | 2 3/4 | HOLE 3 |
| 21B | 21B | D2 | 6A | 6A | RED | 2 3/4 | HOLE 3 |
| 22B | 22B | D7 | 1A | 1A | PURPLE | 2 3/4 | HOLE 3 |
| 23B | 23B | (SLOT) | — | — | — | — | — |

Table 1. Wiring chart for the Trumpcard. Each TRUMPCARD NUMBER connects to the opposite EDGE via a length of coloured wire. The non-standard Trumpcard numbering is related to the conventional ACE and ZX81 numbering system, and the middle column shows the signal on each pin.

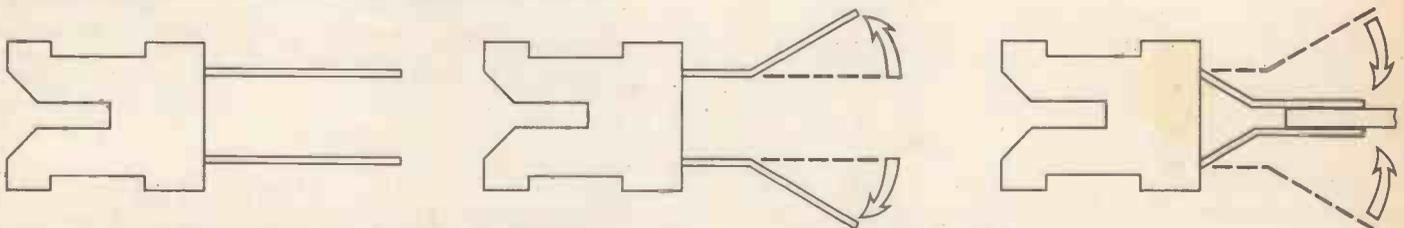


Figure 1. How to bend the pins on the edge-connector socket for soldering to the PCB.

ready for soldering.

Make sure the socket is running parallel with the edge of the PCB and quickly solder the outside pins to hold it in place. Then you can proceed to solder the remaining pins; for best

results use a good hot iron and touch the tip to both the pin and the track. Don't use too much solder, to avoid bridges between track pins, and don't overheat, as this can result in a dry joint.

At this stage the link wires should be prepared to the lengths recommended in Table 1. Pare off about 3mm insulation from each end and when all have been trimmed, the wiring can commence.

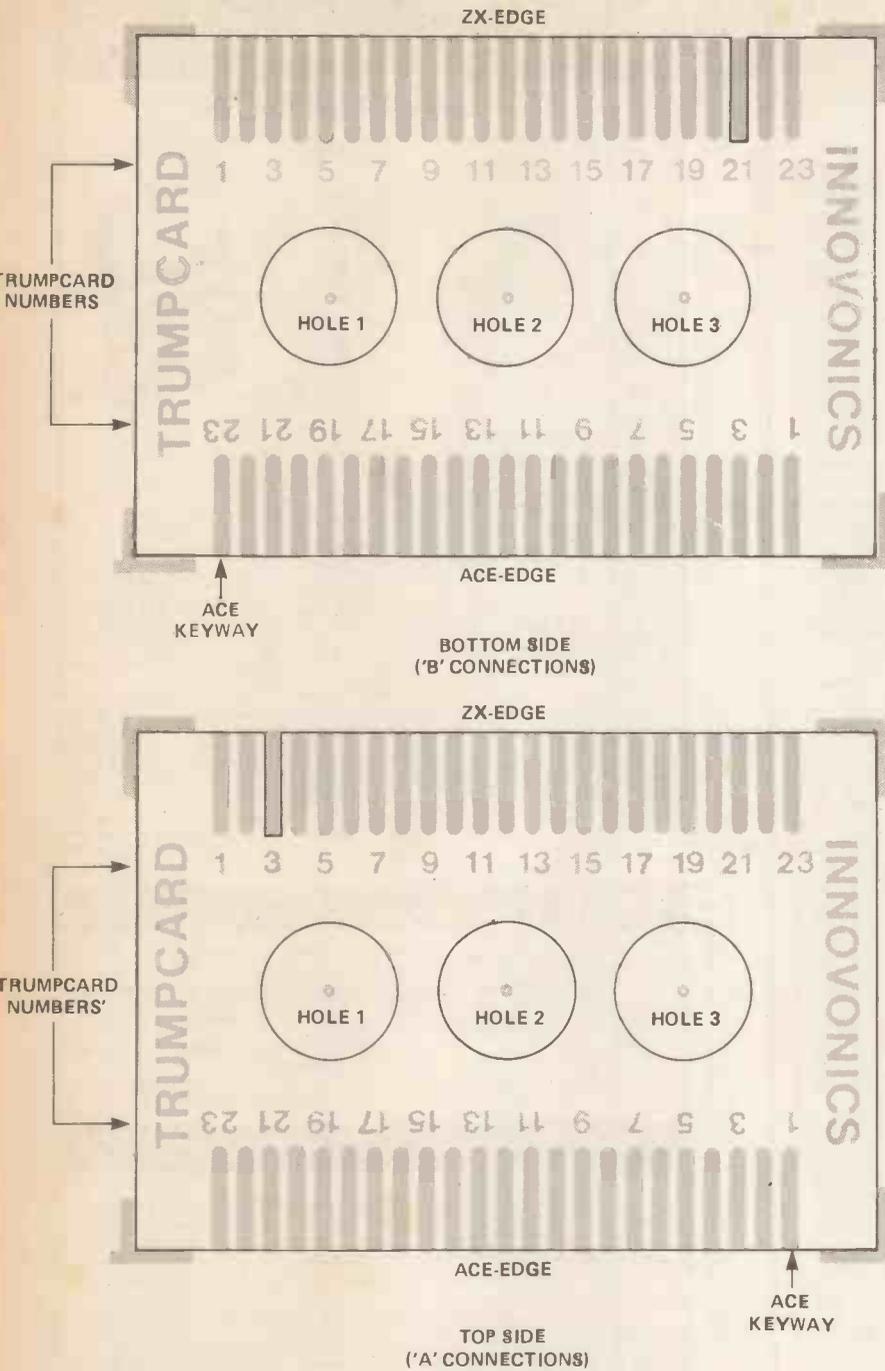


Figure 2. Wires are routed either via the HOLES in the PCB, DIRECT from edge to edge, or between the pins of the EDGE connector as seen in the photograph.

Start with the underside, at the Ace edge, and work from pin 2B across to the other end. The wires go by three different routes; either directly from edge to edge, via one of the three holes or, when you come to the other side, between the pins of the Ace edge connector ('Edge' route in Table 1). When attaching the wires to the ZX-edge be sure to leave at least 4mm of track free to accept the ZX add-on socket!

When the underside is complete, turn the PCB over and wire up the top side; this time most of the links go via the 'Edge' route, with a few direct connections and one link via Hole 2.

Testing

When the wiring is complete, test all the connections thoroughly, then plug onto the Ace and attach the ZX add-on of your choice (the RAM pack is best for testing purposes).

Power up, and you should get a normal screen; a white-out or loss of synchronisation (rolling screen) means that something is wrong, somewhere.

Assuming that all is well and that a RAM pack is attached, type

15384 @

This is the Ace's RAM TOP system variable, and with 16K RAM attached

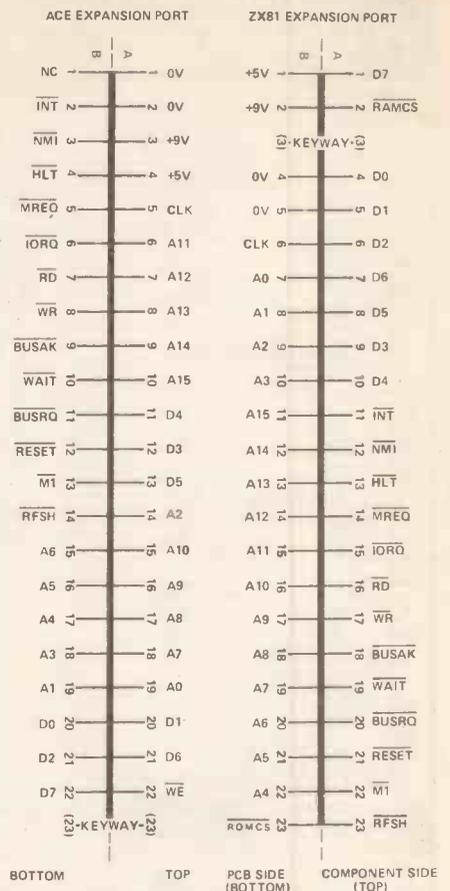


Figure 3. The ACE pins have been re-numbered according to the convention used for the ZX81.

it should return 32768. If the value returned is 16384 then the pack is not connecting properly and the seating of the pins should be checked.

If you do not have a RAM pack available, test the TRUMPCARD with some other add-on with which you are completely familiar, to assure yourself that it is working properly. Then, when you have successfully completed the project, you have added a formidable accessory to your Ace computer.

In the absence of any fixed convention for numbering the Ace pins in chart form, we have taken the liberty of re-arranging the author's system, for the sake of consistency, to conform with the well established standard for the Sinclair ZX81/Spectrum computers. Thus the 'Ace pin number' in Table 1, follows our convention (see also Figure 3), while the 'Trumpcard Number' is that etched onto the Trumpcard PCB (see Figure 2). Later issues of the PCB will follow the new numbering system.

Parts List

Trumpcard PCB; 23+23-way edge connector socket, keyway at position 23; 46 lengths coloured wire (see text), solder etc.

BUYLINES page 32

H.E. PROJECT KITS

I.C.s
TRANSISTORS
CAPACITORS

TOOLS
RESISTORS
HARDWARE

CASES
KITS
PCBs

MAGENTA

Make up your No. 1 SUPPLIER OF KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Kits include all the E.L.E.TRONICS AND HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.E. which includes the project — you will need to order the instruction reprint at an extra 50p. Reprints available separately 50p each + p. & p. 50p.

| | | | |
|--|-------------------|---|----------------------------|
| WHISTLE SWITCH Aug 83 less mic | £18.99 | IN CAR CASSETTE POWER SUPPLY Dec 81 | £4.77 |
| STEREO SPREADER July 83 | £5.75 | SCRATCH FILTER Nov 81 Mono | £5.82 |
| SOFT FUZZ July 83 | £10.25 | LED VU METER Nov 81 less case | £4.87 |
| SIMPLAIR SOUND BOARD Jun 83 less case | £18.95 | SIMPLE STYLUS ORGAN Nov 81 less case | £4.90 |
| TRAFFIC LIGHT TOY June 83 less stand | £8.23 | METRONOME Nov 81 | £12.71 |
| BAT LIGHT (car battery indicator) June 83 less case | £7.98 | TELEPHONE BELL REPEATER Oct 81 | £13.07 |
| TTL LOGIC PROBE June 83 | £8.86 | Mod linking wire extra | 14p metre |
| AUTO TESTER May 83 | £11.72 | COMBINATION LOCK Oct 81 less sciendol | £18.65 |
| STALL THIEF May 83 (inc relay) | £17.82 | BABY ALARM Oct 82 | £8.70 |
| STEREO VOICE OVER UNIT April 83 | £6.26 | 'DIANA' METAL LOCATOR Sept 81 | £24.50 |
| OPTIONAL MIC PRE AMP April 83 (no case) | £8.05 | REACTION TESTER GAME Sept 81 | £12.81 |
| AUTO POWER DOWN April 83 no case | £13.55 | VARIABLE BENCH POWER SUPPLY Aug 81 | £26.98 |
| LINEAR OHMMETER Mar 83 | £10.37 | ULTRASOUND BURGLAR ALARM July 81 | £19.98 |
| LOW RANGE OHMMETER Mar 83 | £18.71 | ELECTRONIC DOOR BUZZER July 81 | £5.90 |
| PHASE FOUR Dec 82 | £18.36 | ELECTRONIC METRONOME July 81 | £4.99 |
| STEREO NOISE GATE Dec 82 | £21.73 | CONTINUITY CHECKER June 81 | £5.71 |
| TAPE SLIDE SYNCHRONIZER Dec 82 | £8.21 | ENVELOPE GENERATOR June 81 | £5.33 |
| BIG EAR Dec 82 | £4.98 | AUDIO MIXER June 81 | £19.48 |
| MICROAMETER ADAPTOR Dec 82 | £14.90 | PUBLIC ADDRESS AMPLIFIER March 81 | £4.40 |
| OHMMETER Nov 82 | £4.86 | Extras — horn speakers | £8.83 each |
| DIANA V.C.O. Nov 82 | £9.19 | PA MIC | £10.90 |
| CS SQUELCH UNIT Oct 82 | £5.50 (less case) | FUZZBOX March 81 | £5.20 |
| 'JUNIOR' SLOTCAR CONTROLLER Sept 82 | £11.33 | WINDSCREEN WIPER CONTROLLER March 81 | £12.98 |
| ZX INTERFACE BOARD Sept 82 inc edge con | £5.33 | STEAM LOCO WHISTLE March 81 | £3.50 |
| T.V.I. FILTER July 82 | £14.38 | PHOTOGRAPHIC TIMER March 81 | £24.96 |
| AUTO WAH June 82 £18.95 inc case or £12.28 less case | £14.38 | HEATBEAT MONITOR Feb 81 | £5.60 less case |
| AUTO GREENHOUSE SPRINKLER June 82 | £9.98 | TWO-TONE TRAIN HORN Feb 81 | £8.20 |
| less pump and power supply | £33.98 | MEDIUM WAVE RADIO Feb 81 | £10.80 |
| TELEPHONE TIMER June 82 | £3.76 extra | BENCH AMP Jan 81 | £8.20 |
| POWER SUPPLY DESIGN 12V 500MA June 82 | £20.90 | NICAD CHARGER Jan 81 | £7.53 |
| ECHO REVERSE UNIT May 82. Less case | £18.90 | CHUFFER Jan 81, less case | £5.20 |
| Economy case WB3 | £12.98 | BATTERY CHARGER MONITOR Dec 82 | £29.96 |
| DIGITAL THERMOMETER May 82 excluding case + bezel | £20.96 | MEMORY BANK — MINI SYNTHESIZER Nov & Dec 80 | £29.96 |
| AUDIO SIGNAL GENERATOR May 82 | £8.98 | TRANSISTOR TESTER Nov 81 | £6.84 inc test leads |
| CABLE TRACKER May 82 | £21.37 | GIUITAR PRE-AMP Nov 80 | £8.65 |
| DIGITAL PARALLEL METER Apr 82 | £3.66 | INTRUDER ALARM Oct 80 | £20.98 |
| SIGNAL TRACER Apr 82 | £11.74 | TOUCH SWITCH Sept 80 | £2.76 less case & contacts |
| BIKE ALARM Apr 82 | £7.29 | GIUITAR PHASER Sept 80 | £16.28 |
| DIGITAL DICE Mar 82 | £10.45 | SOUND OPERATED FLASH TRIGGER July 80 no skt | £5.33 |
| KEYCYCLE SIREN Mar 82 | £14.74 | FOG HORN June 80 | £6.84 |
| NOISELESS FUZZBOX Feb 82 | £21.37 | FX CONTROL FOR F/R/C April 80 | £17.55 (less case) |
| MASTHEAD AMPLIFIER Feb 82 | £3.72 | TOUCH SWITCH Sept 80 | £12.82 |
| DRUM SYNTHESIZER Dec 81, Full kit | | GIUITAR TUNER Nov 79 | £12.91 |
| GIUITAR HEADPHONE AMPLIFIER Dec 81 | | CAR ALARM Feb 79 | £12.91 |

SOLDERING/TOOLS

| | |
|--|----------|
| ANTEX X5 SOLDERING IRON 25W | £5.48 |
| SOLDERING IRON STAND | £1.98 |
| SPARE BITS, Small standard, large, For X5 + X25 | 65p each |
| SOLDER, Handy size | 99p |
| SOLDER CARTON | £1.84 |
| DESOLDER PUMP | 69p |
| HEAT SINK TWEEZERS | 29p |
| DESOLDER PUMP | £6.48 |
| HOW TO SOLDER LEAFLET | 12p |
| LOW COST CUTTERS | £1.69 |
| LOW COST LONG NOSE PLIERS | £1.68 |
| WIRE STRIPPERS & CUTTERS | £2.69 |
| PRECISION PETITE | |
| 12V P.C.B. DRILL | £11.67 |
| DRILL STAND | £7.98 |
| GRINDING STONE | 50p |
| SAWING WHEEL | 50p |
| GRIND BLADE | 85p |
| BRASS WIRE BRUSH | 50p |
| BURR | 50p |
| VERO SPOT FACE CUTTER | £1.49 |
| pin inserter tool | £1.98 |
| VEROPINS (pk of 100) 0.1" | £1.29 |
| MULTIMETER TYPE 1 (1.00 opv) | £5.48 |
| CROCODILE CLIP TEST LEAD SET, 10 leads with 20 clips | 99p |
| RESISTOR COLOUR CODE CALCULATOR | 21p |
| CONNORING WIRE PACK TYPE ED, 11 colours | 48p |
| ILLUMINATED MAGNIFIERS | |
| Small 2" dia. (5 x mag) | £1.14 |
| Large 3" dia. (4 x mag) | £2.40 |
| CAST IRON VICE | £2.98 |
| SCREWDRIVER SET | £1.98 |
| POCKET TOOL SET | £3.98 |
| DENTIST INSPECTION MIRROR | £2.85 |
| JEWELLERS EYEGLASS | £1.50 |
| PAIR OF PROBES WITH LEADS (cc) | £1.99 |
| C MAX PUNCHES | 77p |
| 1/8" £2.98; 1/4" £3.06; 3/8" £3.17; 1/2" £3.24 | |



MULTIMETER TYPE 2, (YN360TR) 20k p.p.v. with transistor tester. £1.475 AC + DC volts DC current, 4 very useful resistance ranges. We've used it and we like it.



HELPING HANDS JIG £8.30 Heavy base. Six ball and socket joints allow infinite variation of clips through 360°. Has 2 1/2" diameter (2.5 magnifier attached), used and recommended by our staff.

| | |
|--|--|
| Speakers min 8 ohm 87p; 64 ohm 89p; 80 ohm 98p | Brimboard breadboard £8.30 |
| Crystal earpiece 65p | Verobloc breadboard £4.20 |
| Magnetic earpiece 15p | PCB etching kit £4.98 |
| Stethoscope attachment 69p | ZX81 edge Connector £2.25 |
| Mono headphones £2.98 | Ferrite rod 5 inch 59p |
| Stereo headphones £4.35 | PP3 clips 10p |
| Telephone pick up coil 69p | PP9 clips 11p |
| Min buzzer 6V 50p; 12V 65p | 2 station Intercom £6.75 |
| Euro breadboard £6.40 | IC sockets 8 pin 16p; 14 pin 17p; 16 pin 18p |
| S Dec breadboard £8.98 | |

BOOKS: ELECTRONICS & COMPUTING

| | | | |
|---|-------|--|-------|
| 205 First Book of Hi-Fi Loudspeaker Enclosures | £0.95 | Semiconductor Data Book Newnes | £6.95 |
| 221 28 Tested Transistor Projects | £1.25 | Basic Electronics Theory and Practice | £7.98 |
| 223 50 Projects Using IC CA3139 | £1.25 | Microprocessor for Hobbyist | £4.75 |
| 225 A Practical Introduction to Digital IC's | £1.25 | Burglar Alarm Systems | £5.95 |
| 226 How to Build Advanced Short Wave Receivers | £1.95 | Electronics, Build and Learn | £3.90 |
| 228 Essential Theory for the Electronic Hobbyist | £1.95 | Electronic Projects in Music | £3.90 |
| BP39 50 (FET) Field Effect Transistor Projects | £1.75 | Electronic Projects in Photography | £3.90 |
| BP40 Digital IC Equivalents and Pin Connections | £3.50 | Electronic Projects in Home Security | £3.90 |
| BP41 Linear IC Equivalents and Pin Connections | £1.50 | Questions and Answers Electronics | £2.70 |
| BP42 50 Simple L.E.D. Circuits | £1.50 | Electronic Projects in the Car | £3.90 |
| BP43 How to Make Walkie-Talkies | £1.95 | 20 Solid State Projects Car and Garage | £4.80 |
| BP45 Projects in Opto-Electronics | £1.95 | 110 Electronic Alarm Projects | £5.98 |
| BP47 Mobile Discotheque Handbook | £1.35 | Computing is Easy | £4.25 |
| BP48 Electronic Projects for Beginners | £1.95 | ZX81 Users Handbook | £5.75 |
| BP49 Popular Electronics Projects | £1.95 | ZX81 Basic Book | £5.75 |
| BP56 Electronic Security Devices | £1.95 | Fun with Electronics | £1.25 |
| BP58 50 Circuits Using 7400 Series IC's | £1.75 | 24 50 CMOS J.C. Projects | £1.35 |
| BP59 Second Book of CMOS IC Projects | £1.50 | BP24 52 Projects Using IC 741 | £1.25 |
| BP61 Beginners Guide To Digital Techniques | £1.95 | BP44 IC555 Projects | £1.95 |
| BP70 Transistor Radio Fault-Finding Chart | £0.50 | BP50 IC LM3900 Projects | £1.35 |
| BP71 Electronic Household Projects | £1.75 | BP65 Single IC Projects | £1.50 |
| BP75 Electronic Test Equipment Construction | £1.75 | BP69 Electronic Games | £1.75 |
| BP78 Practical Computer Experiments | £1.75 | BP72 A Microprocessor Primer | £1.75 |
| BP79 Radio Control for Beginners | £1.75 | BP73 Remote Control Projects | £1.95 |
| BP80 Popular Electronic Circuits — Book 1 | £1.95 | BP74 Electronic Music Projects | £1.75 |
| BP81 Electronic Synthesiser Projects | £1.75 | BP76 Power Supply Projects | £1.75 |
| BP82 Electronic Projects Using Solar Cells | £1.95 | BP83 V MOS Projects | £1.95 |
| BP85 International Transistor Equivalents Guide | £2.95 | BP84 Digital IC Projects | £1.95 |
| BP87 Simple L.E.D. Circuits — Book 2 | £1.35 | BP88 How to Use OP-Amps | £2.25 |
| BP89 Electronic Projects — Crystal Set Construction | £1.95 | BP90 Audio Projects | £1.95 |
| BP94 Electronic Projects for Cars and Boats | £1.95 | BP93 Electronic Timer Projects | £1.95 |
| BP98 Popular Electronic Circuits — Book 2 | £2.25 | BP95 Model Railway Projects | £1.95 |
| BP101 How to Identify Unmarked IC's | £0.85 | BP97 IC Projects for Beginners | £1.95 |
| BP103 Multi-Circuit Board Projects | £1.95 | BP98 Mini Matrix Board Projects | £1.95 |
| BP108 International Diode Equivalents Guide | £2.25 | BP105 Aerial Projects | £1.95 |
| BP109 The Art of Programming the 1K ZX81 | £1.95 | BP106 Modern OP-Amp Projects | £1.95 |
| BP114 The Art of Programming the 16K ZX81 | £2.50 | BP115 The Pre Computer Book | £1.95 |
| BP119 The Art of Programming the ZX Spectrum | £2.50 | | |

| | |
|---|-------|
| How to make and Design your own PCBs | £1.95 |
| 232 Handbook of Integrated Circuits (IC's) Equiv. & Substitutes | £1.95 |
| 232 Solid State Short Wave Receivers for Beginners | £1.95 |
| 227 Beginners Guide to Building Electronics Projects | £1.95 |
| BP1 First Book of Transistor Equivalents and Substitutes | £1.50 |
| BP14 Second Book of Transistor Equivalents and Substitutes | £1.75 |
| BP27 Chart of Radio, Electronic, Semiconductor and Logic Symbols | £0.90 |
| BP32 How to Build Your own Metal and Treasure Locations | £1.95 |
| BP36 50 Circuits Using Germanium, Silicon and Zener Diodes | £1.50 |
| BP37 50 Projects Using Relays, S.C.R.s and TRIACS | £1.95 |
| BP51 Electronic Music and Creative Tape Recordings | £1.95 |
| BP53 Practical Electronics Calculations and Formulae | £2.95 |
| BP67 How to Build Your Own Solid State Oscilloscope | £1.95 |
| BP60 Practical Construction of Pre-amps, Tone Controls, Filters & Attn | £1.45 |
| BP66 Beginners Guide to Microprocessors and Computing | £1.75 |
| BP67 Counter Drive and Nueral Display Projects | £1.95 |
| BP88 An Introduction to BASIC Programming Techniques | £2.25 |
| BP17 30 Solderless Breadboard Projects — Book 1 | £1.95 |
| BP110 How to Get Your Electronic Projects Working | £1.95 |
| BP117 Practical Electronic Building Blocks — Book 1 | £2.25 |
| Elementary Electronics, Sladina, Excellent theory and 35 constructional projects. Uses S-Dec. First steps to BE level | £3.95 |
| Interfacing to microprocessors and microcomputers | £5.75 |

| | |
|---|-------|
| FUN WITH ELECTRONICS | £1.95 |
| Enjoyable introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners — children and adults. Only basic tools needed. 64 full colour pages cover all aspects — soldering — fault finding — components (identification and how they work). | |
| Also full details of how to build 6 projects — burglar alarm, radio, games, etc. Requires soldering — 4 page clearly show you how. | |
| COMPONENTS SUPPLIED — ALLOW ALL PROJECTS TO BE BUILT AND KEPT. | |
| Includes less batteries & cases. | |
| FUN WITH ELECTRONICS COMPONENT PACK £15.75 BOOK EXTRA £1.25 | |
| Book available separately. | |

ZX SPECTRUM AMPLIFIER

250mW output. Volume control. Internal speaker. Very simply connected using load/save lead. Puts real power even into the simplest "Beep" commands. Adds a real "zing" to musical programs and games. Requires PP3 battery — not supplied. Very low current drain. Supplied ready built complete with demo software and instructions.

ORDER AS: ZX SPECTRUM AMPLIFIER (SAHE) £6.98

ZX SPECTRUM SUPER AMPLIFIER

250mW output. Now add synthesizer quality to those "Beep" commands. Super circuit with adjustable ATTACK, SUSTAIN and DECAY envelope controls. Plus variable ECHO. Generates a wide range of special effects. Five graduated controls. Internal speaker. Very smart case. Requires batteries — not supplied. Very low current drain. Ready built complete with demo software and instructions.

ORDER AS: ZX SPECTRUM SUPER AMPLIFIER (SSAHE) £17.98

ADVENTURES WITH MICROELECTRONICS

Similar to 'Electronics' below. Uses I.C.s. Includes dice, electronic organ, doorbell, reaction timer, radio etc. Based on Bimboard 1 bread board. Adventures with Microelectronics £2.98 Component pack £29.64 less battery.

ADVENTURES WITH DIGITAL ELECTRONICS

Entertaining and instructive. Includes details of some digital ICs and 8 projects: shooting gallery, 2 way traffic lights, electronic adder, computer space invaders game etc. No soldering. Adventures with Digital Electronics book £3.25 Component pack including breadboards £42.50 less batteries.

ADVENTURES WITH ELECTRONICS by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects. Adventures with Electronics £2.85. Component pack £18.96 less battery.

30 SOLDERLESS BREADBOARD PROJECTS

Book 1 by R.A. Penfold Clear verobloc layouts and circuit diagrams. Includes fuzz box, radio, metronomes, timers, transistor checker, switches etc. Introduction gives basic information on components including resistors, capacitors, I.C.s, transistors, photocells etc. Ideal for beginners as well as those with some experience. Complete kit including verobloc, book and components (less batteries) £24.75 Less book £22.50, less verobloc £20.25. Book only £2.25.

MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST Price list included with orders or send sae (9 x 4) CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Send 80p in stamps or add 80p to order. FREE to Schools/Colleges requested on official letterhead.

MAGENTA gives you FAST DELIVERY OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers — HAVE YOU TRIED US?

MAGENTA ELECTRONICS LTD.

Magenta Electronics Ltd, HA39, 135 Hunter St., Burton on Trent, Staffs, DE4 2ST. MAIL ORDER ONLY. 0283 65435, Mon-Fri 9-5 Access/Barclaycard (visa) by phone or post. Add 50p P&P to all orders Prices include VAT SAE all enquiries. Official orders welcome. OVERSEAS: Payment must be in sterling IRISH REPUBLIC and BFPO UK PRICES. EUROPE: UK Prices plus 10%. ELSEWHERE: write for quote.

CAMBRIDGE LEARNING

SELF-INSTRUCTION COURSES



GSC SUPERKIT £19.90

Learn the wonders of digital electronics!

This practical kit for beginners comes complete with an instruction manual, components, and

EXP300 breadboard to teach you all the basics of digital electronics. The course needs no soldering iron; the only extra you need to buy is a 4½V battery.

Using the same board you can construct literally millions of different circuits.

The course teaches boolean logic, gating, R-S and J-K flipflops, shift registers, ripple counters, and half-adders.

It is supported by our theory courses

DIGITAL COMPUTER LOGIC £7.00

which covers: basic computer logic; logical circuit elements; the design of circuits to carry out logical functions; flipflops and registers; and

DIGITAL COMPUTER DESIGN £9.50

Our latest, most up-to-date course on the design of digital computers, both from their individual logic elements and from integrated circuits. You are first shown the way in which simple logic circuits operate and then, through a series of exercises, arrive at a design for a working machine.

Other courses available include:

MICROPROCESSORS & MICROELECTRONICS @ £6.50
COMPUTER PROGRAMMING IN BASIC @ £11.50

GUARANTEE No risk to you. If you are not completely satisfied, your money will be refunded upon return of the item in good condition within 28 days of receipt.

CAMBRIDGE LEARNING LIMITED, UNIT 91 RIVERMILL SITE, FREEPOST, ST IVES, CAMBS, PE17 4BR, ENGLAND.
TELEPHONE: ST IVES (0480) 67446. VAT No 313026022

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice). Giro A/c No 2789159. Please allow 28 days for delivery in UK.



.....SUPERKIT(S) @ £19.90
.....DIGITAL COMPUTER DESIGN(S) @ £9.50
.....DIGITAL COMPUTER LOGIC @ £7.00

I enclose a *cheque/PO payable to Cambridge Learning Ltd for £..... (*delete where applicable)

Please charge my:

*Access / American Express / Barclaycard / Diners Club
Eurocard / Visa / Mastercharge / Trustcard

Expiry Date..... Credit Card No

Signature.....

Telephone orders from card holders accepted on 0480 67446
Overseas customers (including Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name.....

Address.....

Cambridge Learning Limited, Unit 91 Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs, PE17 4BR, England. (Registered in England No 1328762).



TYPE 161B DUAL POWER SUPPLY KIT

INCORPORATES A POSITIVE & A NEGATIVE REGULATED SUPPLY

BOTH ARE ISOLATED & ADJUSTABLE 1.3V TO 16V D.C.

Interconnect to give 2.6V to 32V or
-1.3V/0/+1.3V to -16V/0/+16V

Output current 1A at 16V to 0.35A at 1.3V

Ripple is less than 1mV

£25.99

inc. P & P and VAT

Built & Tested

£37.95 inc. P&P and VAT



Comprehensive design details with calculations are included so that the kit is an exercise in power supply design. The kit, which uses quality components, is complete with instructions. Case punched and stove enamelled in attractive blue and grey with a printed front panel to give a professional finish.

Excellent for the beginner, the experienced amateur and as a tutorial for schools and colleges.

SEND CHEQUE OR P.O.

ALLOW 21 DAYS FOR DELIVERY

BRANIME MARKETING LTD DEPT. HE/10
BALTHANE IND. EST., BALLASALLA, ISLE OF MAN

Send for my CATALOGUE ONLY 75p (plus 25p post/packing)

My all-inclusive prices quoted in the Catalogue are the lowest. All below normal trade price - some at only one tenth of manufacturers quantity trade.

See my prices on the following:

CAPACITORS . . . ELECTROLYTIC; CAN, WIRE END TANTALUM, MULTIPLE, COMPUTER GRADE, NON POLAR, PAPER BLOCK, CAN, POLY, MICA, CERAMIC. LOW AND HIGH VOLTAGE, RESISTORS. 1/8th WATT TO 100 WATT; 0.1% TO 10% CARBON, METAL AND WIRE WOUND + NETWORKS. FANS, BATTERIES, SOLENOIDS, TAPE SPOOLS, VARIABLE CAPACITORS AND RESISTORS, TRIMMERS, PRESETS, POTS . . . SINGLE, DUAL, SWITCHED, CARBON, CERMET AND WIREWOUND, SINGLE OR MULTITURN, ROTARY AND SLIDE. DIODES, RECTIFIERS, BRIDGES, CHARGERS, STYLII, SOCKETS, PLUGS, RELAYS, TRANSISTORS, IC'S, CLIPS, CRYSTALS, ZENERS, TRIACS, THYRISTORS, BOXES, PANELS, DISPLAYS, LED'S, COUPLERS, ISOLATORS, NEONS, OPTO'S, LEADS, CONNECTORS, VALVES, BOOKS, MAGAZINES, TERMINALS, CHOKES, TRANSFORMERS, TIMERS, SWITCHES, COUNTERS, LAMPS, INDICATORS, BELLS, SIRENS, HOLDERS, POWER SUPPLIES, HARDWARE, MODULES, FUSES, CARRIERS, CIRCUIT BREAKERS, KNOBS, THERMISTORS, VDR'S, INSULATORS, CASSETTES, METERS, SOLDER, HANDLES, LOCKS, INDUCTORS, WIRE, UNITS, MOTORS, COILS, CORES, CARTRIDGES, SPEAKERS, EARPHONES, SUPPRESSORS, MIKES, HEATSINKS, TAPE, BOARDS and others.

Prices you would not believe before inflation!

BRIAN J. REED
TRADE COMPONENTS
ESTABLISHED 26 YEARS

161 St. Johns Hill, Battersea, London SW11 1TQ

Open 11 am till 7 pm Tues. to Sat. Telephone: 01-223 5016

Ultrasonic Intruder Alarm

In the darkness, something stirred . . . the night was pierced by an unearthly wail. The HE Ultrasonic Intruder Alarm had done its work again.

R. A. Penfold

IDEALLY, every property would be protected by a comprehensive burglar alarm system but the cost, plus the difficulty of installation, makes it an impractical proposition in many cases. However, a fairly simple and self-contained system can be built at low cost, installed with minimal difficulty, and offer a worthwhile improvement in security. It is a unit of this type that is described in this article.

The system is of the ultrasonic Doppler-Shift type and when used, in even quite a large room, it will detect movement virtually anywhere in the room and sound the alarm. The alarm generated is a frequency modulated tone of quite high pitch and fairly high volume, which should alert the occupants of the building and (hopefully) scare away the intruder — who is unlikely to wait around to see if anyone responds to the alarm!

The circuit includes a switch-on delay which enables the user to activate the alarm and move away without triggering it. A delay to prevent the alarm from sounding until a few seconds after it has been triggered could also be included, so that the user has an opportunity to switch off the unit before the alarm sounds. However with this particular type of alarm, such a delay could make the unit less effective and more vulnerable, and with a small alarm for internal use having the alarm generator operate briefly each time it is switched off is not a major drawback. A switch-off delay has, therefore, been omitted from the unit.

System Operation

Figure 1 shows the various stages of the unit in block diagram form; there are two separate sections — the transmitter and the receiver.

The transmitter is by far the simpler; this is just an oscillator operating at a nominal frequency of 40kHz and feeding into a special transducer. A frequency of 40kHz is used because this is where the

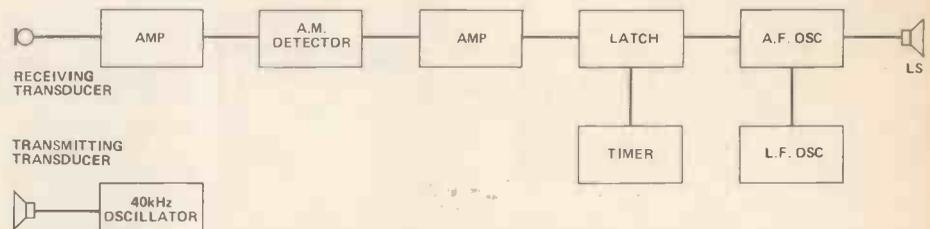
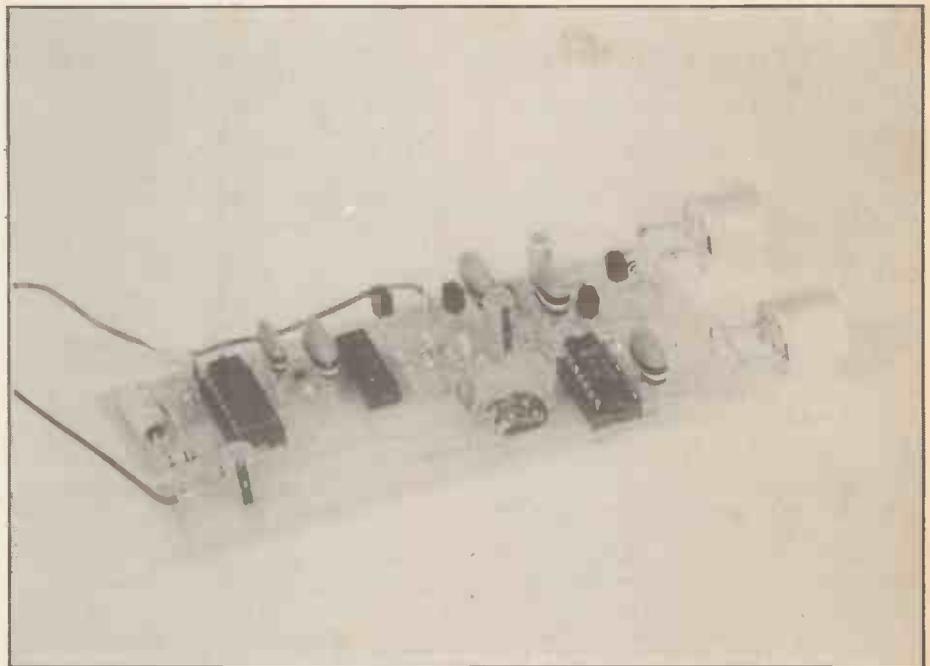


Figure 1. The block diagram, showing the transmitting and receiving stages.

transducer is most efficient and it is an ultrasonic frequency so that the sound waves produced by the transducer are too high in pitch to be heard by human ears. An intruder could not be alerted to the presence of the alarm by hearing the output of the transmitter.

A second ultrasonic transducer is used at the input of the receiver; this picks up sound waves from the transmitting transducer and converts them to small electrical signals. The

two transducers are mounted side-by-side and some of the pick-up is due simply to sound waves which travel *direct* from one transducer to the other. This accounts for only part of the received signal though, and a large part of it is received indirectly due to reflections from the walls, furnishings, or any other objects in the room (including people).

Signals received via the stationary objects will be at the transmitted frequency but, due to the well known

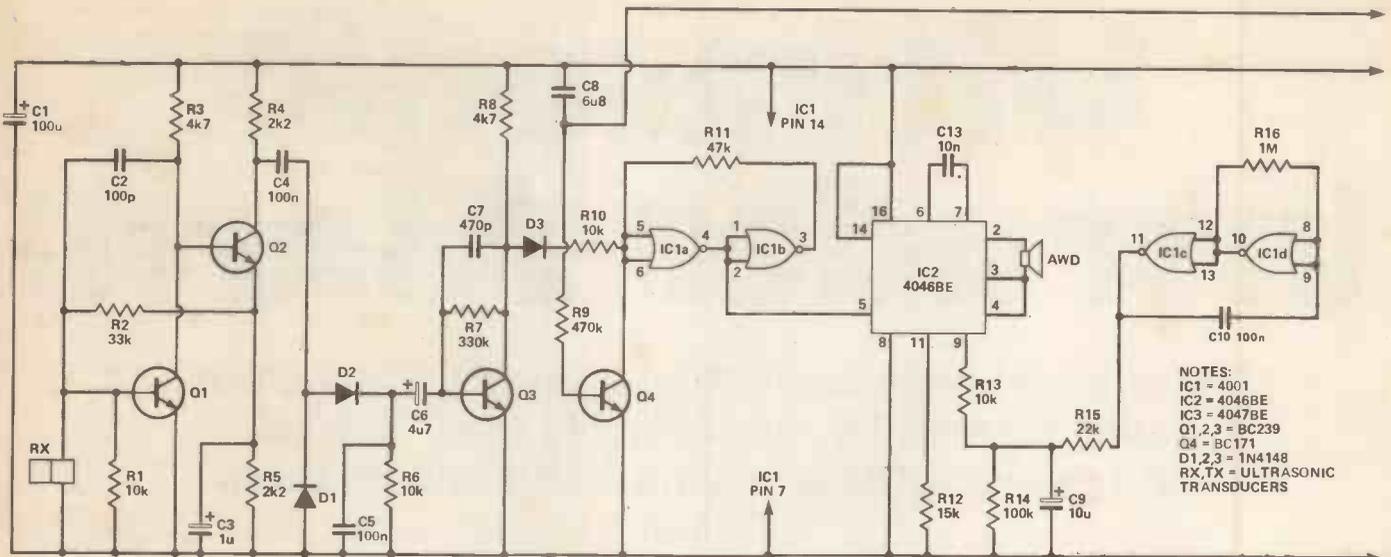


Figure 2. The circuit.

Doppler Shift effect, sounds received by way of any object which is moving towards the transducers will be raised in frequency, while any picked up via an object that is moving away from the transducers will be reduced in frequency. The frequency shift depends on the speed at which the object moves, but for someone walking around a room, it would be a low audio frequency of between a few tens of Hertz and a few hundred Hertz.

The frequency shifted signals mix with the non-shifted ones, but because of the varying phase of the two signals they first add together to give a strong signal and then tend to have a cancelling effect on each other, so that a much weaker signal is produced. Thus the strength of the received signal varies at the shift frequency, and an output at this

frequency can be obtained using an ordinary AM demodulator (ie, a rectifier and smoothing circuit). Of course, with no Doppler Shift there is no audio output from the detector, since the received signal will be of constant strength. The output from the receiving transducer is unlikely to be very large, and would typically be well under one millivolt RMS. A high gain amplifier must therefore be used ahead of the detector to give a usable signal level.

Further amplification is needed in order to bring the output of the detector to a sufficient strength to drive the next circuit, which is a latch (bistable) circuit. This permanently switches on an audio oscillator when an input signal, no matter how brief is received. This is an essential feature, as the alarm would otherwise only sound while someone was actually

moving around the room. A timer circuit disables the latch for a few seconds after switch-on so that the switch-on delay is produced. A low frequency oscillator is used to frequency-modulate the audio oscillator so that a more effective and penetrating alarm is produced.

The Circuit

The full circuit diagram of the Ultrasonic Intruder Alarm is shown in Figure 2; the transmitter is built around IC3. This is a CMOS 4047BE device which can be used in a variety of monostable and astable modes but in this circuit is employed as a straight-forward free running astable. RV1 is adjusted for the output frequency that give optimum efficiency from the circuit. The 4047BE has anti-phase outputs at pins 10 and 11, and by connecting the

Parts List

RESISTORS

(All 0.25W 5% carbon)

| | |
|---------------|------|
| R1, 6, 10, 13 | 10k |
| R2 | 33k |
| R3, 6 | 4k7 |
| R4, 5 | 2k2 |
| R7 | 330k |
| R9 | 470k |
| R11 | 47k |
| R12 | 15k |
| R14 | 100k |
| R15 | 22k |
| R16 | 1M |
| R17 | 8k2 |

POTENTIOMETER

| | |
|-----|------------------------|
| RV1 | 22k 0.1W hor preset |
|-----|------------------------|

CAPACITORS

| | |
|----|----------------------------|
| C1 | 100u 10V radial electro |
| C2 | 100p ceramic plate |

| | |
|---------------|---------------------------|
| C3 | 1u 50V radial electro |
| C4, 5, 10, 12 | 100n polyester |
| C6 | 4u7 50V radial electro |
| C7 | 470p ceramic plate |
| C8 | 6u8 tantalum |
| C9 | 10u 25V axial electro |
| C11 | 330p ceramic plate |
| C13 | 10n polyester |

SEMICONDUCTORS


| | |
|----------|---------------------------------------|
| Q1, 2, 3 | BC239 high gain NPN |
| Q4 | BC171 NPN |
| IC1 | 4001BE or 4001UBE quad 2-input NOR |

| | |
|----------|------------------------------|
| IC2 | 4046BE phase locked loop |
| IC3 | 4047BE astable/monostable |
| D1, 2, 3 | 1N4148 signal diodes |

MISCELLANEOUS

| | |
|---|--------------------------------------|
| SW1 | SPDT min, toggle or keyswitch |
| RX | Ultrasonic transducer type R40-16 |
| AWD | Ceramic resonator type PB2720 |
| TX | Ultrasonic transducer type T40-16 |
| B1 | 9 Volt battery preferably NiCad |
| Battery connector; printed circuit board; IC sockets; wire etc. | |

BUYLINES page 32

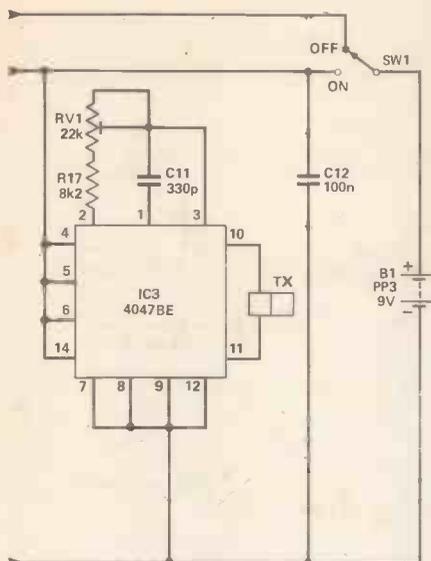

transmitting transducer across these (rather than from one output to earth) the voltage fed to the transducer is virtually doubled. This gives a useful boost to the performance of the equipment. The output impedance of the 4047BE is not very low, but the transducers are piezo types with an impedance of a few hundred ohms, typically, so a low drive impedance is not essential.

A two-stage, direct-coupled common emitter amplifier is used at the input of the receiver section. This is probably the most cost effective way of obtaining the required high gain at the signal frequency of 40kHz. As the receiving transducer is also a piezo type it can be direct coupled to the input of the amplifier. C2 rolls-off the response of the amplifier at radio frequencies which help to avoid problems with breakthrough of radio signals, as well as reducing the risk of instability.

The AM demodulator is a standard configuration, with D1 and D2 providing the rectification while R6 and C5 smooth the rectified signal. The audio output from the demodulator is coupled by C6 to the input of a single stage, high gain, common emitter amplifier based on Q.

R10, R11, and two CMOS NOR gates (connected here as inverters) form a simple latch circuit, and this has its input fed from the output of Q3 via D3. Under stand-by conditions R7 biases Q3 so that it has a low collector voltage, and the input of the latch is not taken high. However, if there is a suitable output from the detector, the collector of Q3 will swing positive and negative of its quiescent level, and on the first positive half cycle the latch will be triggered to the high state. D3 ensures that the latch cannot be taken back to the low state on negative excursions of Q3's collector.

At switch-on C8 will charge through R9 and the base-emitter junction of

Q4. This switches on Q4 which consequently holds the input of the latch in the low state. This provides the switch-on delay and also ensures the latch is initially set to the correct state. After about 15 seconds the charge current for C8 becomes too low to hold Q4 in the on state, and the circuit is then able to function normally. SW1 is the on/off switch, also used to discharge C8 when the unit is switched off so that a fresh switch-on delay is produced when it is turned on again.

The audio oscillator uses a 4046BE CMOS phase locked loop, but it is primarily the voltage controlled oscillator (VCO) section that is used here. One of the phase comparators is used as an inverter which gives anti-phase outputs to drive the loudspeaker, the latter being a ceramic resonator which is well matched to the high drive voltage and low current available from IC2.

IC2 is frequency-modulated by a low frequency oscillator formed using the remaining two gates of IC1. This provides a roughly squarewave output, but filtering by R15 and C9 converts this to an almost triangular waveform which sweeps the VCO smoothly up and down in frequency at a rate of a few Hertz. The VCO operates at frequencies of around 2 to 4kHz where the AWD (Audible Warning Device) has optimum efficiency and despite the low power at which it operates, provides a high volume.

A mains power supply unit capable of giving a well smoothed 9V output could be used to power the unit, but NiCad batteries represent a good alternative; six AA cells in a plastic battery holder are suitable. The unit could be powered from ordinary (non-rechargeable) batteries, but with

a quiescent current consumption of about 10 milliamps and the unit likely to be used for prolonged periods this would probably be an uneconomic way of doing things!


Construction

Details of the printed circuit board are shown in Figure 3. All three integrated circuits are CMOS types and the appropriate handling precautions should therefore be taken. It is advisable to fit IC2 and IC3 in DIL IC sockets, but as IC1 is a very inexpensive type it could reasonably be deemed not worthwhile to use a socket for this device.

The ultrasonic transducers can be mounted direct on the board, either vertically or horizontally if they are soldered onto pins. They have very narrow separation, and it might be possible to obtain improved performance by mounting them off-board and using greater separation. However, the prototype gives excellent results with the transducers mounted on-board, and it is probably not worthwhile experimenting with greater separation. The circuit should work properly using any normal 40kHz ultrasonic transducers and it is not essential to use the specified types (but obviously alternatives might give reduced performance).

C8 must have a low leakage level or the switch-on delay could be greatly extended, possibly not ending at all! A tantalum bead component is therefore preferable to an electrolytic type.

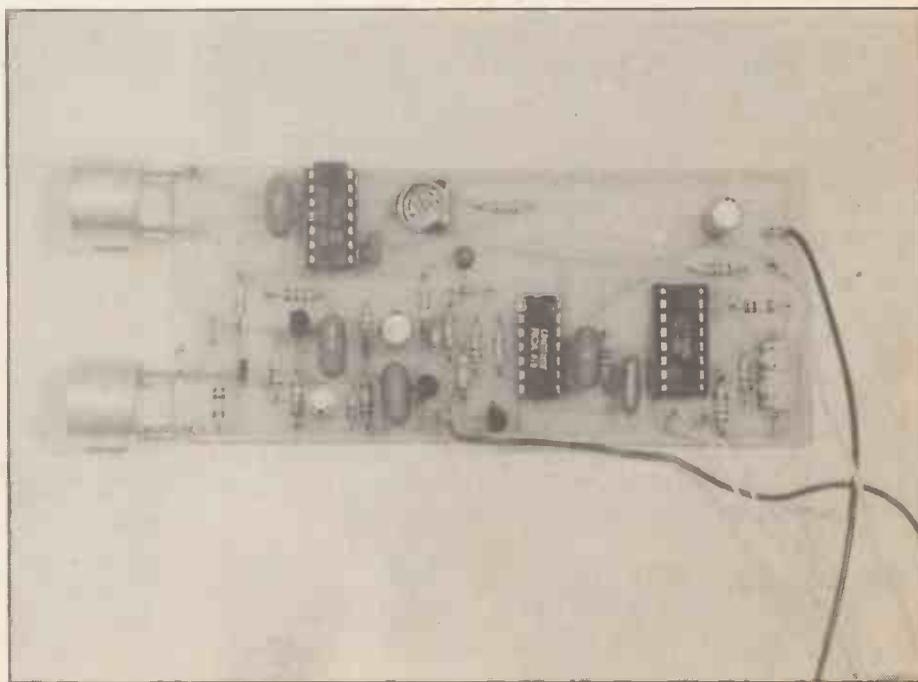Mechanical construction of the unit must be varied to suit your particular requirements. Alarms of this general type are often disguised as some ordinary household object such as a book or a small bookshelf



In the prototype, the transducers are mounted directly on the board.

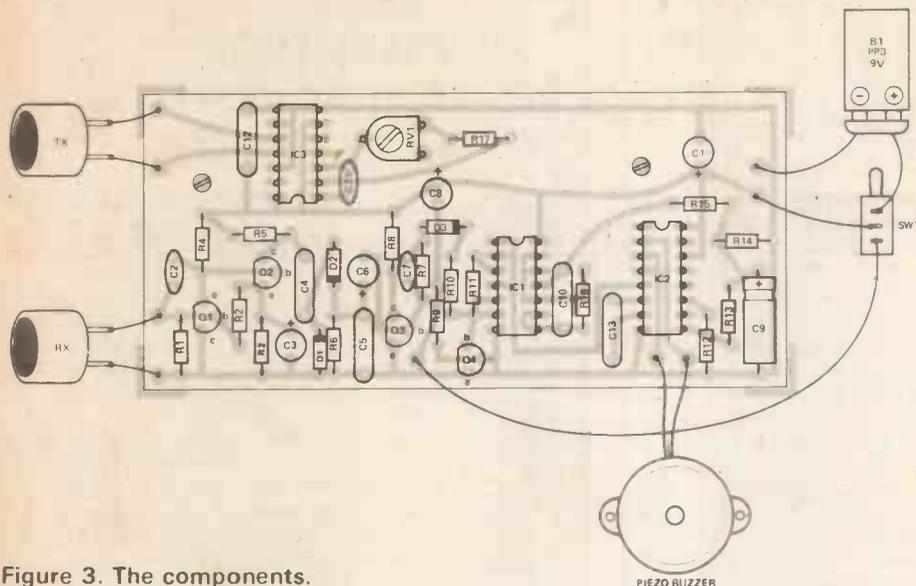


Figure 3. The components.

loudspeaker. However, the unit is almost certain to be triggered before any intruder realises what it is and can simply be built as a normal project fitted to a standard plastic or metal box. It should not be possible for an intruder to easily switch off the unit, so SW1 should be concealed in some way. The AWD is mounted on the exterior of the case, and the two ultrasonic transducers are fitted behind cutouts which enable the

sound waves to flow freely to and from the transducers.

Adjustment

There is only one adjustment to make before the unit is ready for use, and this is to set RV1 for optimum results. This can be done simply by trial and error, but there is a much quicker way if a multimeter is available. The multimeter is used to monitor the

voltage across C5, and RV1 is adjusted for the highest obtainable voltage reading. The two ultrasonic transducers should be aimed into a reasonably empty space while this adjustment is made. There may be two peaks at slightly different settings of RV1 and in this case the more pronounced of the two settings should be used.

If the switch-delay is considered to be too short it can be extended somewhat by increasing R9 to about 1 megohm, or using a higher value component for C8.

To a certain extent the performance of the unit will depend on where in the room it is located and where it is aimed. With a little experimentation a suitable position for the unit should soon be found. With this type of detector there are normally a few "dead" spots in the room where the unit is insensitive, but it should be possible to obtain good sensitivity over the majority of even quite large rooms. Remember that the unit responds to movement, not just to the presence of an object. Also bear in mind that false alarms can be produced by such things as curtains blowing in the wind, pets moving within the protected area and even turbulence in the air caused by a heater. Obviously the unit should be positioned where false alarms of this type are not likely to occur.

HE



VELLEMAN KIT

NEW
— K2585
Codelock
(£44.02 + VAT)

NEW
— KB12, KB12S, KB16, KB16S
Membrane keypads, with
or without symbols
(£7.34 + VAT)

K2588 —
Sound to light
(£18.26 + VAT)

NEW
— K2592
20 Watt
mono amplifier
(£9.06 + VAT)

NEW
— K2591
Programmable controller
module
(£49.52 + VAT)

NEW
— K2584
Precision
timer
(£53.50 + VAT)

Velleman electronic kits can be purchased directly from us at the address below and are also available from the following stockists:

Enquiries from Retail Shops always welcome.

Free illustrated catalogue and price list available on request.

VELLEMAN UK Ltd

P.O. Box 30, St Leonards-on-Sea,
East Sussex TN37 7NL, England.
Telephone: (0424) 753246

Annley Electro, Bedminster Down, Bristol
Baxol Tele Exports, Post Rathdrum, Co. Wicklow.
Bradley-Marshall Ltd., 325 Edgware Road, London
S&R Brewster Ltd., 86-88 Union Street, Plymouth
Camlab Electronics, 27 Faringdon Road, Swindon, Wilts.
Gaines Electronic Components, 3 West Street, Fareham, Hants.
L.R. Hanney, 77 Lower Bristol Road, Bath, Avon.
Hemmlings Electronics, 15 Brand Street, Hitchin, Herts.
R. Jones Electronics, 267 Rectory Road, Grays, Essex.
Lovering Bros., 76 King's Road, Reading, Berks.
Marshall Electronics, 86 West Regent Street, Glasgow
Twyford Electronics, 22 Station Road, Twyford, Berks.

HENRY'S AUDIO ELECTRONICS

COMPUTERS • COMMUNICATIONS • TEST EQUIPMENT • COMPONENTS

VISIT OR PHONE • OPEN 6 DAYS A WEEK • ALL PRICES INC VAT



THERMAL MATRIX & LINE PRINTER

SAVE £57

COMPLETE WITH FULL HANDBOOK, 3 ROLLS PAPER £113.00 + VAT (UK post etc £1.05) (List approx £187) 150 to 180 LPM • Full 96 CH ASC II • 40 CPL • 280 Data P/L • Auto-underline • 50 Graphic Symbols • Back Space Seal Test • VU/HDR TABS • 7 x 10 Matrix • 4.4" Wide Paper • Bidirectional • 220/240 V AC • Size Approx. 9.8 x 2.0 x 7.2"

INC. VAT £129.95

'CHERRY' ADD-ON KEYPAD

A compact 18 button keypad suitable for use with cherry keyboard to extend its functions. Supplied brand new with data A 4 x 4 non encoded single mode keyboard. £5.95 (inc. V.A.T) UK C/P Free



RECHARGEABLE BATTERIES

AA or HP7 size batteries 4 for £3.00 (UK C/P 30p)
Charger takes up to 4 any size 1x V rechargeables also, 1 x PP3 size (UK C/P 65p) £6.95

SPEAKERS, TWEETERS AND CROSSOVERS

- HIF20ESM 8 ohm 30/50 watt Bass/Mid range 8" £5.95
- HIF20ESM 4 ohm version 8" (UK C/P £1.00) £4.95
- HT25 2 1/2" 8 ohm 15 watt tweeter. Pair £3.50
- HIF87 BSM 4" 8 ohm 30/50 watt mid range £4.95
- PH30 3" 8 ohm 15 watt tweeter. Pair £3.50
- HT315F 5" x 3 1/4" 8 ohm 30 watt tweeter. Pair £5.50
- CN38 3 way 8 ohm 15 watt. Pair £2.00
- SM300 40 watt version. Pair £3.00 (UK C/P 65p per 1 to 3 items)

IN STOCK

Large range of semi-conductors, tools, components, accessories, cordless and electronic telephones, C.B. equipment, etc.

LOGIC PROBES

LP10 10 MHz £28.50
DLPS0 50 MHz with carry case and accessories £52.33



HIGH VOLTAGE METER

Direct reading 0/40 KV. 20K/volt. £23.00 (UK C/P 65p)



DIGITAL CAPACITANCE METER

0.1 pF to 2000 mfd LCD 8 ranges DM6013 £52.75



TRANSISTOR TESTER

Direct reading PNP-NPN, etc. TC1 (UK C/P 65p) £21.95



VARIABLE POWER SUPPLIES

(UK C/P £1.00)
PP241 0/12/24V. 0/1A £35.00
PP243 3 amp version £59.95
PS1307S 8/15V £24.95
7 amp 1w/meter



DIGITAL MULTIMETERS

- with case (rotary switches) £2.95
- Side button - case £2.95
- K025C 13 range 0.2A DC. 2 meg ohm £23.50
- K030S 16 range 10A DC. 2 meg ohm £26.95
- K030C 26 range 1A AC/DC 20 meg ohm £29.50
- Metrex 3000 30 range 10A AC/DC. 20 meg ohm £33.24
- 6010 28 range 10A AC/DC 20 meg ohm £34.40
- 7030 4-ASG010 high acc. D1% basic £41.30
- K0615 16 range 10A DC 2 meg plus Hfe tester £39.95
- SIFAM 2200B 21 range 2A AC/DC 20 meg Bench Models £39.95
- TM355 29 range LED 10A AC/DC 20 meg. Thandar £86.25
- TM356 26 range LCD 10A AC/DC 20 meg. Thandar £97.75
- TM351 29 range LCD 10A AC/DC 20 meg. Thandar £120.75
- SIFAM 2500 24 range LCD 2A AC/DC 20 meg. £99.95

MULTIMETERS (UK C/P 65p)

- HM102BZ 20K/V 10A DC 22 range & cont. buzzer £13.50
- ETC5000 21 ranges. 50K/V. Range doubler. 10A DC £18.95
- TMK500 23 ranges 30K/V. 12A DC plus cont. buzzer £23.95
- NM56R 20K/V. 22 range pocket £10.95
- ETU102 16 range 2K/V pocket £6.50
- 830A 26 range 30K/V. 10A AC/DC overload protection, etc. £23.95
- 360TR 23 range 100K/V. Large scale 10A AC/DC plus Hfe £39.95
- AT2100 31 range 100K/V deluxe 12A AC/DC £33.50
- AT102D 18 range 20K/V. Deluxe plus Hfe tester £18.95
- YN360TR 19 range 20K/V plus Hfe tester £15.95



SIGNAL GENERATORS (220/240V AC)

- FUNCTION: All sine/square/triangle/TTL, etc. TG100 1 Hz - 100 KHz £90.00
- TG102 0.2 Hz - 2 MHz £166.75
- PULSE TG105 Various facilities 5 Hz - 5 MHz £97.75
- AUDIO: Multiband Sine/Square LAG27 10 Hz to 1 MHz £90.85
- AG202A 20 Hz to 200 KHz (List £94.50) £83.50
- RF SG402 100 KHz to 30 MHz (List £79.50) £69.50
- LSG17 100 KHz to 150 MHz £79.35

OSCILLOSCOPES

- Full specification any model on request. SAE by post
- 'HM' Series HAMEG: 'SC' THANDAR: 'CS' TRIO: '3' CROTECH 'DT' Salign SINGLE TRACE UK C/P £3.00
- 3030 15 MHz 5mV 95mm tube plus component tester C/P £3.00 £177.10
- SC110A Miniature 10 MHz battery portable Post free £171.00
- HM103 15 MHz 2mV 6 x 7 display plus component tester C/P £3.00 £181.70
- Optional carry case £6.84 AC adaptor £6.69
- Nicados C12 50 DUAL TRACE (UK C/P £4.00) £241.50
- DT 520 Dual 20 MHz £241.50
- HM203/4 Dual 20 MHz plus component tester £303.60
- CS1562A Dual 10 MHz (List £321.00) £269.50
- 3131 Dual 15 MHz + component tester £276.00
- CS1566A Dual 20 MHz All facilities (List £401.35) £349.50
- HM204 Dual 20 MHz plus component tester sweep delay £419.75



FREQUENCY COUNTERS

- PFM200A 200 MHz hand held pocket 8 digit LED £77.60
- MET1008 digit LED bench 2 ranges 100 MHz £102.35
- MET6008 digit LED bench 3 ranges 600 MHz £132.25
- MET1000 8 digit LED 3 ranges 1 GHz £182.85
- TF040 8 digit LCD 40 MHz. Thandar £126.50
- TF200 3 digit LCD 200 MHz Thandar £166.75

SUPERKITS!

FOR BETTER MUSIC & EFFECTS

SETS INCL PCBs, ELECTRONIC PARTS, INSTRUCTIONS, BOXES, WIRE, SOLDER. BATTERIES NOT INCL, BUT MOST WILL RUN FROM 9V TO 15V DC SUPPLIES. FULLER DETAILS IN LIST

- CHORUS UNIT: A solo voice of instrument sounds like more
- COMPRESSOR: Limits & levels maximum signal strength
- ECHO UNIT: With double tracking
- FREQUENCY DOUBLER: Raises guitar frequency by 1 octave
- FREQUENCY CHANGER & WAVEFORM MODIFIER - Tunable unit
- FLANGER: Fascinating effects plus phasing
- FUZZ: Smooth distortion whilst keeping natural attack & decay
- GUITAR EFFECTS: Multiple variation of level & filter modulation
- GUITAR OVERDRIVE: Fuzz plus variable filter quality
- GUITAR SUSTAIN: Extends effective note duration
- JABBERVOX: Voice disguiser with reverb & tremolo
- MAD-ROJ: Variable sirens, incl police, galaxy, machine guns
- METRONOME: With audible & visual beat & down-beat marking
- MICROPHONE PRE-AMP: with bass & treble switching
- NOISE LIMITER: reduces tape & system hiss
- PHASER: with automatic & manual depth & rate controls
- REVERB: with variable delay & depth controls
- RYTHM GENERATOR: 15 switchable rhythms
- RING MODULATOR: with integral oscillator control
- ROBOVOX: versatile robot type voice modifier
- ROGER 2-GONG 2 gongs sounded at end of transmission
- SCRAMBLER: Codes & decodes transmissions authorised chans
- SPEECH PROCESSOR: for clearer transmission
- STORM EFFECTS: Automatic & manual, wind, rain, surf
- TREMLO: deep tremolo with depth & rate control
- VOCODAVOX: modular vocoda
- VODALEK: Robot type voice modulator
- VOICE-OP-SWITCH: with variable sensitivity & delay
- WAH-WAH: with auto-trigger, manual & oscillator control

- KIT162 £26.60
- KIT133 £12.38
- KIT168 £38.10
- KIT98 £9.34
- KIT172 £29.66
- KIT153 £18.73
- KIT91 £9.28
- KIT42 £13.54
- KIT56 £17.53
- KIT75 £9.36
- KIT150 £19.68
- KIT146 £8.23
- KIT143 £11.28
- KIT144 £7.06
- KIT145 £8.33
- KIT164 £17.56
- KIT122 £16.86
- KIT170 £32.40
- KIT179 £13.83
- KIT165 £18.16
- KIT126 £10.04
- KIT177 £18.09
- KIT110 £9.65
- KIT154 £13.66
- KIT136 £8.44
- KIT152 £59.09
- KIT155 £10.21
- KIT123 £13.80
- KIT140 £14.18

MANY OTHER GREAT KITS IN CATALOGUE such as Autowah, bass boost, call sing, comparator, frequency generator, Funky-wobulol, harmonia, hum-cut, mixers, sequencers, synthesiser interface, treble boost, tone control, vibrato, voice filter, voice operated fader, Wheeler-jeeby, wobble-wah. Plus digital synthesiser, junior synthesiser, envelope shaper, D-A converter, multiwaveform VCO, Keyboards, contacts, etc. Send S.A.E. for comprehensive catalogue (overseas send £1).

Add £1 P&P & 15% VAT to all orders. (Overseas post details stated in ct). Payment CWO, Chq, PO, Access, Barclay, or pre-arranged collection. Despatched usually 10-14 days. Details correct at press, E&OE.

PHONOSONICS MAIL ORDER
Dept HB50, 8 Finuence Drive, Oprington, Kent BR5 4ED
Tel: Oprington (STD 0689) 37821. Mon-Fri 10-5.
Callers by appointment

EVERYONE KNOWS

that TOOLMAIL offer the largest range of D.I.Y. tools available by post and that their 128 page colour catalogue contains over 2,000 quality tools.

But did YOU know that the range includes almost everything required by the Electronics Hobbyist: — Soldering Irons, Desolder Tools, Miniature Tools, PCB Holders, Drills, Pliers, Cutters, Tweezers, IC Extractors, Screwdrivers, Craft Knives, Hole Punches, Test Meters, Needle Files, Glue Guns, Nut Drivers, Wire Strippers, Component Formers, IC Inserters, De-solder Braid, and complete Electronics Tool Kits.

The catalogue normally cost £1 but is available FREE to Hobby Electronics readers. Send 50p postage for your personal copy.

SEE US AT '83

TOOLMAIL (1982) LTD
7 LONDON ROAD
SEVENOAKS
KENT TN13 1AH



TOOLMAIL

The world's best tool shop in your home

HENRY'S Cubegate Limited
404-406 Edgware Road, London, W2 1ED
Computer: 01-402 6822. Components: 01-723 1008
Test Equipment & Communications: 01-724 0323
AUDIO ELECTRONICS
301 Edgware Road, London, W2 1BN
01-724 3564 (All mail to this address)

JUST A SELECTION OF OUR STOCK. CALL IN AND SEE FOR YOURSELF.
FREE CATALOGUES - SEND LARGE S.A.E. (20p UK) ORDER BY POST OR PHONE.



PARNDON ELECTRONICS LTD.

Dept. 22, 44 Paddock Mead, Harlow, Essex. CM18 7RR. Tel: 0279 32700

RESISTORS: ¼ Watt Carbon Film E24 range ± 5% tolerance
Bandoliered and colour coded. Full Range 1R0-10M.

£1.00 per hundred mixed (Min 10 per value) **£8.50** per thousand mixed (Min 50 per value)
Special stock pack 60 values. 10 of each **£5.50**

RECTIFIERS

| | | |
|-------|-------|-----|
| 1 Amp | 3 Amp | |
| 50V | 3p | 14p |
| 100V | 4p | 14p |
| 200V | 5p | 14p |
| 400V | 6p | 19p |
| 600V | 8p | 20p |
| 1000V | 9p | 25p |

3½ Digit LCD Display: 1 colon, 3 decimal points
plus/minus sign and lo bat indicator.

Complete with low power 7106 A/D converter display driver.
Driver set **£8.95**

Display **£3.50** Driver **£6.50**

DIODES: IN4148 **£1.60** per hundred

DIL SOCKETS 8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

Full List Available — Send SAE

ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS

MIN ORDER — UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE

Same Day Despatch

'BARGAIN TIME'

UV PROMS
2716 £2.30
2732 £4.12

DIODES
In4148 2p each or £1.50/100
In4001/4002/4003 3p each
Zener Diodes 400mW (BZY88C)
4p each or £3 per 100

VOLTAGE REGS. T0220 39p each
+7805 +7818 -7905
+7812 +7824 -7912
+7815 -7915

LED'S — 5mm All with Clips
Red 9p; Green 10p; Yellow 11p
Special pack 10 of each **£2.50**

I.C. SOCKETS

| Pins | Low profiles | Turned pin |
|------|--------------|------------|
| 8 | 6p | — |
| 14 | 9p | 32p |
| 16 | 9p | 37p |
| 18 | 12p | 42p |
| 20 | 14p | — |
| 22 | 16p | — |
| 24 | 15p | 53p |
| 28 | 19p | — |
| 40 | 26p | 92p |
| 64 | — | £2 |

RESISTORS —

E24 Range Carbon
Film, Bandoliered
100 Assorted values
10 per value... 95p

1000 Assorted values
50 per value... £8

HEATSINKS

T0220/SOT32 Finger Heatsinks Vert. or
Horiz. Mounting 18 deg c/w 20p each;
15 deg c/w 24p each
To 6 push on 9p each
46 x 46mm Finger type drilled To 3 7 deg
c/w 28p each
55 x 55mm Finger typed drilled To 3
4.5 deg c/w 31p each
65mm x 20mm x 50mm extruded sink
2.75 deg c/w 98p each

TERMS: Strictly cash with order. All prices inclusive of VAT.
HANDLING: Charge of 50p on orders under £5. Heatsink Listing and Data Sheets
sent with all orders or on receipt of large sae with 26p of postage.

CAMTEC CIRCUITS AND SYSTEMS LIMITED

5 York Road, Bognor Regis, West Sussex PO2 1QW
Tel: (0243) 862911

FOR HI-FI & ELECTRONICS ENTHUSIASTS

CONCEPT ELECTRONICS LTD

51 Tollington Road, London N7 6PB

Mall order only

We are the specialist of electronic kits and rack mounting cabinets. A catalogue with complete range of products including pre-amp modules, power amp modules, pre and power amplifier modules, complete kits of amplifiers, equalizers, reverberation amplifiers (with cases), alarm clocks, appliance timers, CB amplifiers, test equipment, control modules, music generator, battery fluorescent light and high quality rack mounting cabinets etc. with illustrative pictures now available at the cost of 35p + 25p p&p.

Professional rack mounting cabinet



| Panel Size | Rear Box | Price |
|------------|-----------------|-------------|
| W H (Inch) | W H D | AL STEEL |
| 19 x 5 | 17 x 4.5 x 10 | 27.54 23.54 |
| 19 x 4 | 17 x 3.5 x 10 | 25.24 21.24 |
| 19 x 3.5 | 17 x 3 x 10 | 24.09 20.09 |
| 19 x 3 | 17 x 2.5 x 10 | 24.09 — |
| 19 x 2.5 | 17 x 2 x 10 | 22.94 18.94 |
| 19 x 6 | 17 x 5.5 x 12 | 28.69 24.69 |
| 19 x 5 | 17 x 4.5 x 12 | 27.54 23.54 |
| 19 x 4 | 17 x 3.5 x 12 | 25.24 21.24 |
| 19 x 3.5 | 17 x 3 x 12 | 24.09 20.09 |
| 17 x 3.5 | 15.5 x 3 x 9 | 21.79 17.79 |
| 17 x 2.5 | 15.5 x 2 x 9 | 20.64 16.64 |
| 17 x 4 | 15.5 x 3.5 x 12 | 25.24 21.24 |
| 17 x 3 | 15.5 x 2.5 x 12 | 24.09 20.09 |

Please add £2.50 p/p per item

★ Wholly made of black anodised aluminium sheets ★ Suitable for high quality amplifiers and many other purposes ★ Top, side and rear cover removable for access
★ Separate front mounting plate ★ Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles ★ With ventilation slits and plastic feet.

The low cost steel version is also available. The size and features as well as the front panel is the same as the aluminium cabinets except the rear box is manufactured from steel painted in black.

CONTROL MODULES



TY-7 Electronic touch switch
£2.90 Kit £4.50 Ass.
TY-11 Light activated switch
£2.20 Kit £3.50 Ass.
TY-18 Sound activated switch
(Clap switch) **£4.50 Kit £5.95 Ass.**
TY-38 Sound activated switch
(voice-switch) **£5.50 Kit £7.50 Ass.**
TY-41 Infra-red remote control
(Receiver and transmitter)
£17.20 Kit £21.95 Ass.

HI-FI AMPLIFIER MODULES



TA-323A 30W + 30W stereo amplifier
£18.95 Kit £23.95 Ass.
TA-820 60W + 60W stereo amplifier
£27.50 Kit £33.50 Ass.
TA-920 70W + 70W stereo amplifier
£35.50 Kit £42.50 Ass.

RECHARGEABLE BATTERIES AND CHARGERS

PRIVATE OR TRADE ENQUIRIES WELCOME
FULL RANGE AVAILABLE
SEND SAE FOR LISTS

£1.45 for booklet "Nickel Cadmium Power"

● TRADE PRICES FOR SCHOOLS & COLLEGES ●

SANDWELL PLANT LTD

656 Chester Road, Erdington,
Birmingham 021-373 9487
After Hours: Lichfield 57977

Now open Saturday mornings

BECOME A RADIO AMATEUR

Train now for the Radio Amateur Licence examination. No previous knowledge needed, only a few hours per week of home study for 3 to 6 months. Post coupon now for details or tel. 0734 51515 (24 hr service)



British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE brochure without obligation from:—
British National Radio & Electronics School
READING, BERKS. RG1 1BR

Name


Address

HE/10/846


BLOCK CAPS PLEASE

The MIGHTY MIDGEETS
SOLDERING IRONS AND ACCESSORIES
TYPE 1
£5.46 inc vat
postage 35p
12 month guarantee
18 WATT
From your Local Dealer or Direct from Manufacturers
S & R BREWSTER LIMITED
86-88 UNION ST. PLYMOUTH PL1 3HG
0752-665011 TRADE ENQUIRIES WELCOME

PCB FOIL PATTERNS

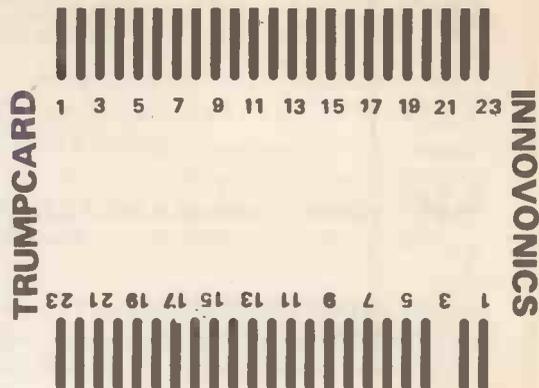


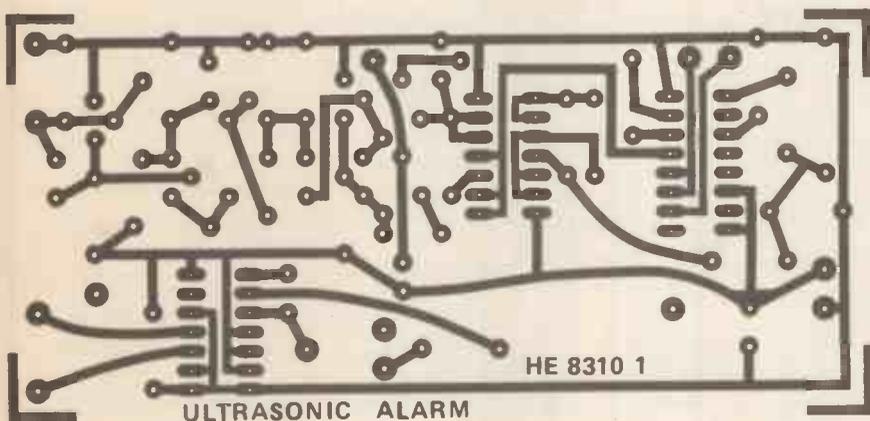
Above: The PCB foil pattern for the Trump Card is copyright by INNOVONICS, but is made available for home constructors by permission.



Left: The Ultrasonic Intruder Alarm PCB layout.

Below Left: The Hi-Volt Meter PCB layout.

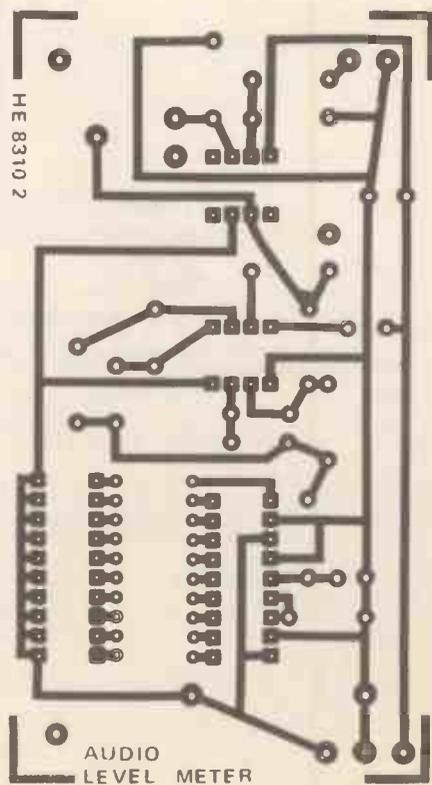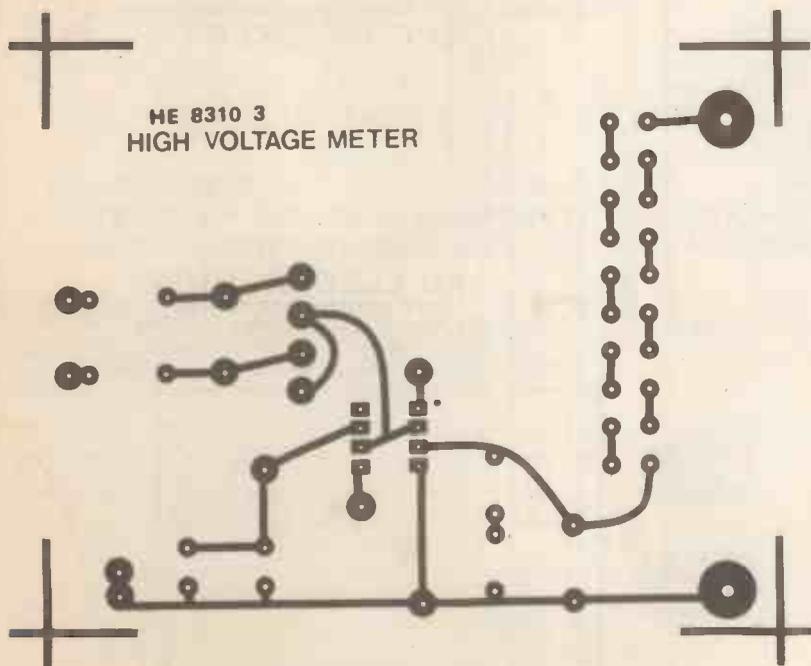Below: The Audio Level Meter PCB is laid out for a 10-LED module, but ten separate LEDs can be used instead.



DOUGLAS ELECTRONIC COMPONENTS
90 Wellington Street, Stockport, Cheshire. SK1 3AQ



BOOKS - CROSSOVERS - CABLE -
COMPONENTS - CONNECTORS - DECKS FUSES
- HEADPHONES - LEADS MICROPHONES -
MULTIMETERS - PROJECT BOXES -
SOLDERING IRONS SPEAKERS - STYLI &
CARTRIDGES TOOLS - VEROBOARD ETC.

Tel: 061-480 8971

SAVE £££'s ON HOME HEATING BILLS

UNIQUE DIGITAL THERMOSTAT
POSSIBLE FUEL
SAVINGS OF
UP TO 25%



Normally manufactured exclusively for the trade. Features: ●
Continuous readout of ambient temp via 3 digit 7 segment display
● LED indicates when pump is in operation ● 0.2°C Hysterisises
● 240v 3A control contacts ● Switched set temperature




High specification — Simple to calibrate —
Connect in place of existing thermostat —
Requires 240v 2VA supply — Kit includes all
necessary components, Enclosure, diagrams
and instructions.

Kit price only **£29.95**. Assembled Price **£45.00**
plus £1 p&p (prices Include VAT)

Send cheque or PO to: **DICON ELECTRONICS LIMITED**
Bond Street, Bury, Lancs BL9 7DU Tel 061-797-5666

POSITRONICS

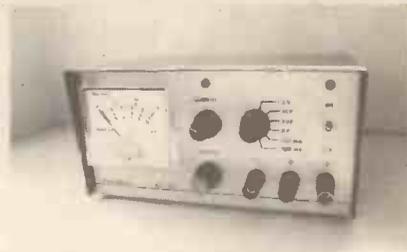TWO PROFESSIONAL POWER SUPPLY UNITS NOW IN



If you are looking for the basic tool of electronics then these features should impress:

1. 0-30 VOLT OUTPUT
2. 0-3 AMP OUTPUT

303
0-1.5 AMP OUTPUT

3. INTEGRAL MULTIMETER GIVING FULLY SIX RANGES
4. HIGHLY STABLE IN VOLTAGE AND CURRENT MODS
5. PRICE, YOU WON'T FIND SIMILAR PERFORMANCE FOR TWICE THE PRICE
6. IN KIT, STEP BY STEP INSTRUCTION

From kit or built and tested you will have a highly controllable power source of exacting design, engineering and quality.

| | | |
|------------------------------------|-------|-----|
| UNIT | 301.5 | 303 |
| Kit | £45 | £55 |
| (Built & Tested) | £60 | £70 |
| P&P £2.50. VAT not inc. | | |

Please allow 21 days delivery

POSITRONICS

Unit 4, New Enterprise III, Montgomery Street
Sparkbrook, Birmingham B11 1DS
Tel: 021-350 2267

PERMACON



Proved over many years in commercial use, now available to the hobbyist at competitive prices.

STANDARD CONNECTORS
TWO PITCHES .1 AND .15
FOUR CONTACT STYLES

Further details from:

COLNBROOK ELECTRONICS LTD
Crabbs Abbey, Stowbridge
Kings Lynn, West Norfolk
PE34 3PE

ALARMS



FREE BOOKLET
on
BURGLAR ALARMS
with
LOWEST U.K. DIY PUBLISHED PRICES

PHONE OR WRITE FOR YOUR COPY

051-523 8440


AD ELECTRONICS
217 WARBRECK MOOR
AINTREE, LIVERPOOL L9 0HU



MICRO-MIKE®

The Most Useful Inspection
Tool You'll Ever Own . . .
. . . And One Of The
Least Expensive

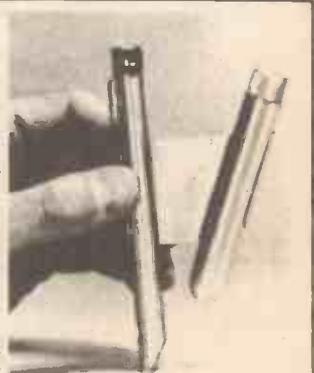The Powerful Pocket Microscope that's perfect for close inspection and measurement in all scientific work. Professional quality optics. Available in 10x to 50x magnifications. Scale reading 0.001 inch or 0.1mm. No moving parts. Easy to use. Always in focus. Rugged aluminium and glass construction. Virtually indestructible. Guaranteed for a lifetime of service.



Optional Micro-Lite attachment now available for full illumination in hard-to-see areas

| | |
|------------------------------------|--------|
| 10x, 20x, 40x, 50x Models | £10.35 |
| Measuring models with 0.1mm Scale | £12.65 |
| Micro-Lite Clip on accessory light | £8.60 |

Hirsh Jacobson Merchandising Co. Ltd.
51 Marylebone High St., London W1M 3DE
Tel. 01-935 4709

Prices include postage and VAT
State magnification required

Lineage:

30p per word (minimum 15 words)
Semi-display £7.50 per single column centimetre
Ring for information on series bookings/discounts



01-437 1002
EXT 282

Send your requirements to:
Julie Bates,
ASP Ltd.,
145 Charing Cross Road,
London WC2H 0EF

All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)

BOOKS & PUBLICATIONS

PARAPHYSICS JOURNAL
(Russian translations). Psychotronics, Kirlianography, heliphonic music telekinetics. Computer software. SAE 4 x 9":— Paralab, Downton Wilts.

SERVICES

JOHNSON INTRODUCES THE NEW

Tele-Recorder

Automatically record every telephone call

- Elegant, compact unobtrusive
- Superb 2-way speech quality
- British Telecom approved
- Records up to 8 hours on a standard C120 tape



£95 (+ £2 p&p)

Johnson Electronics (Works), Star Warehouse, Camden Goods Depot, Chalk Farm Road, London NW1 0T-286 8119

PLANS 'N DESIGN

AMAZING electronic plans, lasers, gas, ruby, light shows, high voltage teslas, van de graph, surveillance devices, ultrasonics, pyrotechnics, new solar generator, 150 more projects, catalogue S.A.E., Plant-centre, Bromyard Road Industrial Estate, Ledbury HR8

FOR SALE

POWERAMPLIFIERS 200 Watt £11.95! Case and controls. Volume balance and sockets. 4 x MJ3001 outputs 100 + 100 Watts!! (R.R.P. + data = £38.40). Kia, 8 Culliffe Road, Ilkley.

NEW "Maplin VIC20 Talkback Kit" LK00A. Built and tested. £33. A. Harvey, S8 St. Michaels Grove, Fareham, Hants.

COMPONENTS

BUMPER BOX OF BITS

WOW!! We've got so many components in stock, we can't possibly list them all! — So buy a box, in it you'll find resistors, capacitors, displays, switches, panels and transistors, diodes, IC's, etc., coils, pots... and so on. All modern parts — guaranteed at least 1000 items. Minimum weight 10lbs. ONLY £8.50 inc. 48 page catalogue 50p.

ELECTRONICS WORLD
1F Dewes Road, Sallsbury
Wilts SP2 7SN

ALARMS

BURLAR ALARM EQUIPMENT. Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. LTD. 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274-308920.

ULTRASONIC ALARM SELF-CONTAINED LOUDSPEAKER DESIGN

- ★ Easy installation
 - ★ Adjustable sensitivity control
 - ★ Automatic reset after time out
 - ★ Motion Detection using "Doppler Effect"
 - ★ Delay time features for exit and re-entry to premises
 - ★ External speaker or siren can be connected to the phono jack for remote monitoring
 - ★ Normally open relay contacts for auto switching of external devices during alarm mode
 - ★ Applicable for home security systems: Screw terminals available for the connection of normally closed (NC) type magnetic or trap switches
 - ★ AC/DC operation (requires mains adaptor)
- Fabulous value RRP £39.99.
Our Price £19.99 + £2.50 p.p. & insurance
(Note: we have a few units returned under guarantee which are unchecked and sold without guarantee @ £12.00 + p.p.)
Send cheque, postal order or phone with credit card details
Access — Barclaycard — Diners

LISTWOOD
6-10 Market Road,
London N7 9PP.
Telephone: 01-609 4526

COMPONENTS

WAVEBANDS

Auto Electronics,
103 Coventry Street,
Kildderminster
Tel: (0562) 2179

Brand new components by return post or ring with Access/Barclaycard number for same day despatch.

All manufacturers guaranteed new stock. All at most competitive prices. Catalogue available only 50p. All prices inclusive of VAT.

IN STOCK New telephone plugs and sockets also ZX81 plugs and spectrum plugs and wide range of burglar alarm equipment and all accessories for same plus large range of components. Shudehill Supply Co. Ltd., 53 Shudehill, Manchester 4. 061-834 1449.

HOBBY SHOP

DAVENTRY

EMOS HIGH MARCH
DAVENTRY NN11 4HQ
Tel: (03272) 5523

- ★ Open Mon-Sat 9am-4pm
- ★ Both retailers and wholesalers
- ★ Vast stocks of components
- ★ Large 'walk-round' electronics supermarket

IRELAND

IRELAND
Call A & A ELECTRONICS
for wide range of kits
17 Cuala Road
Bray
Co. Wicklow
Tel. 01-B62422

LANCASHIRE

ETESON ELECTRONICS
E.E.
15B Lower Green,
Pouton-le-Fylde,
Blackpool
Tel: (0253) 885107

Open 9:30am-12.30, 1.30-5.30.
Closed Wed & Sun
Electronic Component Specialists

EQUIPMENT

AERIAL AMPLIFIERS Improve weak television reception. Price £6.70. S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire BL0 9AGH.

JOIN OUR FREE mailing list for bargain electronics offers. Write to: Van Gelder Ltd, P.O. Box 10, Southend-on-Sea, Essex SS2 6QG or phone (0702) 548681.

KITS

FREE SOLDERING IRON STAND

With every soldering iron purchased, kit comes complete with quality British 17 watt iron, spring stand, inbuilt sponge, solder and instructions. Ideal for PCB work. Only £7.99 + 75p P&P. R.A.J., 63 Penn Road, Datchet, Berks SL3 9HT.

TODMORDEN

PROFESSIONAL OR HOBBYIST?

Come and have a look at the EMPORIUM Bargains galore — catalogue available Electronic, Electrical and Mechanical Nuts & Bolts, Resistors, Capacitors, Meters, Semiconductors and much more.

A. C. TOWNLEY LTD
Harehill Mill
Harehill St (off Burnley Rd), Todmorden
Open 8.30-5.30 Sats till 1 pm
(lunch 1-2pm)

TYNE & WEAR

NOW OPEN IN NEWCASTLE
FOR THE BEST IN ELECTRONIC
TEST EQUIPMENT AND
ACCESSORIES

Marlborough Electronic Components
15 Waterloo Street,
Newcastle NE1 4DE1
Tel: 618377

Open 9am-6pm Mon-Sat Easy Parking
Stockists of: Transistors, Resistors,
Capacitors, I.C. Diodes, Electronic Books
Etc. Repairs undertaken

W YORKSHIRE

ACE MAILTRONIX LIMITED
3A Commercial Street
Batley, West Yorkshire
Tel. 0924 441129

Open: 9-5.30pm Weekdays
9.30-1pm Saturdays
Retailers and wholesalers

KITS

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

DIGITAL WATCH replacement parts, batteries, displays, backlights, etc. Also reports publications charts. S.A.E. for full list: Profords Copners Drive, Holmer Green, Bucks HP15 6SGE.

HOBBY ELECTRONICS

CLASSIFIED ADVERTISEMENT — ORDER FORM

If you have something to sell now's your chance! Don't turn the page — turn to us!
Rates of charge: 30p per word per issue (minimum of 15 words).
 and post to **HOBBY ELECTRONICS, CLASSIFIED DEPT., 145 CHARING CROSS ROAD, LONDON WC2**

| | | | |
|--|--|--|--|
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |

Please place my advert in **HOBBY ELECTRONICS** for issues commencing as soon as possible.

I am enclosing my Cheque/Postal Order/International Money Order for: (delete as necessary) £ (Made payable to A.S.P. Ltd)

Please use **BLOCK CAPITALS** and include post codes.



OR Debit my Access/Barclaycard
(Delete as necessary)



Classification

Name (Mr/Mrs/Miss/Ms)
(delete accordingly)

Address

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

Signature **Date**

All classified advertisements must be paid for in advance.

Daytime Tel. No.



H.E. ADVERTISERS INDEX OCTOBER 1983

| | | | |
|-------------------------------|--------|--------------------------|--------|
| A.D. Electronics | 71 | House of Instruments | 33 |
| Ambit International | IFC | ICS | 72 |
| Audio Electronics | 67 | ILP | 30, 31 |
| Bib Audio | 46, 47 | Kelan Engineering | 53 |
| Bicc Vero | 57 | LB Electronics | 15 |
| B K Electronics | IBC | Litesold | 53 |
| B.N.R.S. | 19, 68 | Magenta Electronics | 61 |
| Branime Marketing | 62 | Marlborough Electronics | 33 |
| J. Bull | 27 | Meon Electronics | 15 |
| Cambridge Learning | 62 | Parnden Electronics | 68 |
| Camtec Circuits & Systems Ltd | 68 | Phonosonics | 67 |
| Colnbrook Electronics Ltd | 71 | Positronics | 71 |
| Dataplus Developments | 46 | Rapid Electronics | 10 |
| Dicom Electronics | 71 | Brian J. Reed | 62 |
| Douglas Electronic Components | 71 | Sandwell Plant | 68 |
| Electroni-Kit | 15 | Silica Shop | OBC |
| Electronize Design | 56 | Sparkrite | 4 |
| Europa Electronics | 57 | S&R Brewster | 68 |
| Gardner Precision Engineering | 33 | Technomatic | 5 |
| G.S.C. | 9 | T K Electronics | 47 |
| Hawk Electronics | 46 | Tomorrows World | 23 |
| Hirsh Jacobson | 71 | Velleman (UK) Ltd | 66 |
| Hodder & Stoughton | 53 | W.E.B. Logic Systems Ltd | 72 |
| Horizon Electronics | 72 | | |



MULLARD SPEAKER KITS


Purposefully designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer 18" or 5" with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter. B.K.E. built and tested crossover based on Mullard circuit, combining low loss components, glass fibre board and recessed loudspeaker terminals. **SUPERB SOUNDS AT LOW COST.** Kits supplied in polystyrene packs complete with instructions. 8" 40W system - recommended cabinet size 240 x 216 x 445mm Price £14.90 each + £2.00 P & P. 5" 30W system - recommended cabinet size 160 x 175 x 295mm Price £13.90 each + £1.60 P & P.

Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self adhesive vinyl etc. 8" system cabinet kit £23.00 each + £2.50 P & P. 5" system cabinet kit £7.00 each + £2.00 P & P.

STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Autostop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Input Sensitivity: 100mV to 2V. Input Impedance: 68K. Output level: 400mV to both left and right hand channels. Output Impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V DC at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2" x 11 1/2". Clearance required under top panel 2 1/2". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish. Price £26.70 + £2.60 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50

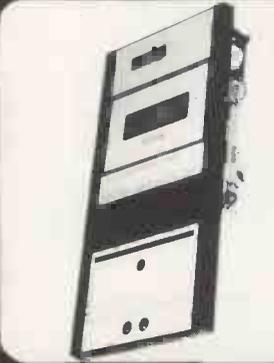

LOUDSPEAKERS POWER RANGE

THREE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8" See Photo). Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons. **Specification and Prices.**

15" 100 watt R.M.S. Impedance 8 ohms. 50 oz. magnet. 2" aluminium voice coil. Res. Freq. 20 Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. Price: £34.00 each + £3.00 P&P
12" 100 watt R.M.S. Impedance 8 ohms. 50 oz. magnet. 2" aluminium voice coil. Res. Freq. 25Hz. Freq. Resp. to 4 KHz. Sens. 95dB. Price: £24.50 each + £3.00 P&P
8" 50 watt R.M.S. Impedance 8 ohms. 20 oz. magnet. 1 1/2" aluminium voice coil. Res. Freq. 40Hz. Freq. Resp. to 6 KHz. Sens. 92dB. Black Cone. Price: £9.50 each. Also available with black protective grille Price: £9.99 each. P&P £1.50.

12" 85 watt R.M.S. McKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 98dB. Price: £23.00 + £3 carriage.
12" 85 watt R.M.S. McKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz., Price: £23 + £3 carriage.
15" 150 watt R.M.S. McKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price: £47 + £4 carriage.



PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**

TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.29 each.



TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £5.99 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £7.99 each.

TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £4.99 each.

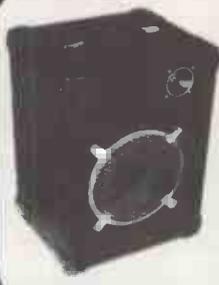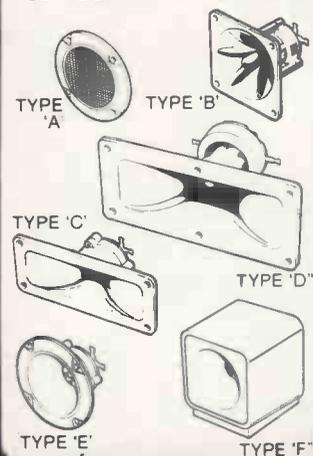TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each
P&P 20p ea. (or SAE for Piezo leaflets).



OMP 80 LOUDSPEAKER

The very best in quality and value.

Ported tuned cabinet in hard-wearing black vinyl with protective corners and carry handle. Built and tested, employing 10in British driver and Piezo tweeter. Spec: 80 watts RMS; 8 ohms; 45Hz-20KHz; Size: 20in x 15in x 12in; Weight: 30 pounds.

Price: £49.00 each

£90 per pair

Carriage: £5 each £7 per pair

BK ELECTRONICS

Prompt Deliveries
VAT inclusive
prices
Audio Equipment
Test Equipment
by
Thandar
and
Leader

PANTEC

HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £7.99p

DIGITAL THERMOMETER -9.9°C to +99.9°C. LED display. Complete with sensor. 70 x 70 mm (9 volt) Price: £27.60p

3-WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled. professional performance. Range up to 3 miles 35 x 84 x 12 mm (12 volt) Price: £12.49p

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27 MHz Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22 mm (9/12 volt) Price: £18.49 Transmitter 80 x 50 x 15 mm (9/12 volt) Price £10.29 P&P All Kits +50p. S.A.E. for complete list.



3 watt FM Transmitter

BSR P256 TURNTABLE

P256 turntable chassis • S shaped tone arm • Belt driven • Aluminium platter • Precision calibrated counter balance • Anti-skate (bias device) • Damped cueing lever • 240 volt AC operation (Hz) • Cut-out template supplied • Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price £31.35 each, £2.50 P&P



OMP POWER AMPLIFIER MODULE



New model.
Improved specification

OEM'S CONTACT BARRY PEARNE Tel. 0702 52752

NEW OMP100 Mk.II POWER AMPLIFIER MODULE Power Amplifier Module complete with integral heat sink toroidal transformer power supply and glass fibre p.c.b. assembly. Incorporates drive circuit to power a compatible LED Vu meter. New improved specification makes this amplifier ideal for P.A., Instrumental and Hi-Fi applications.

SPECIFICATION
Output Power:— 110 watts R.M.S.
Loads:— Open and short circuit proof 4/16 ohms.

Frequency Response:— 15Hz - 30KHz -3dB. T.H.D.:— 0.01%.

S.N.R. (Unweighted):— -11 dB ±3.5dB

Sensitivity for Max Output:— 500mV @ 10K. Size:— 360 x 115 x 72 mm Price:— £31.99 + £2.00 P&P. Vu Meter Price:— £7.00 + 50p P&P.

HOME PROTECTION SYSTEM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. **FULLY GUARANTEED.**

Control Unit - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed. 30 second exit and entry delay.

Indoor alarm - Electronic swept freq. siren. 104dB output.


Outdoor Alarm - Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £128 Usual price £228.85

BKE's PRICE £99.p&p£4

SAE for colour brochure

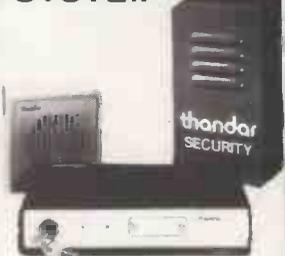


MIXERS DISCO

OMP PRO MIX MONO

OMP PROMIX MONO DISCO MIXER (As illustrated). 4 Inputs - 2 Mag. Disc. 1 Aux. plus Mic with override. Active bass and treble tone con'ts. Individual level controls plus master volume. Monitor output (head- phone) for all inputs. Output 1775mV Supply 240Vac. Size: 19" x 5 1/2" x 2 1/2". Price: £49.99 + £2.00 P&P

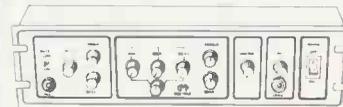ALSO STEREO DISCO MIXER with 7 band graphic, Vu display, All facilities. £99.99 + £2.00P&P



B.K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR



★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★ All items packed where applicable in special energy absorbing PU foam. ★ Please phone 0702 52752 ★

100 FREE PROGRAMS

FROM SILICA SHOP — WITH EVERY PURCHASE OF AN

ATARI 400

800




ATARI PRICES REDUCED!

We at Silica Shop are pleased to announce some fantastic reductions in the prices of the Atari 400/800 personal computers. We believe that the Atari at its new price will become the U.K.'s most popular personal computer and have therefore set up the Silica Atari Users Club. This club already has a library of over 500 programs and with your purchase of a 400 or 800 computer we will give you the first 100 free of charge. There are also over 350 professionally written games and utility programs, some are listed below. Complete the reply coupon and we'll send you full details. Alternatively give us a ring on 01-301 1111 or 01-309 1111.

ATARI 400 £129
with 16K

ATARI 400 £178
with 32K

ATARI 800 £279
with 16K

400/800 SOFTWARE & PERIPHERALS

Don't buy a T.V. game! Buy an Atari 400 personal computer and a game cartridge and that's all you'll need. Later on you can buy the Basic Programming cartridge (£35) and try your hand at programming using the easy to learn BASIC language. Or if you are interested in business applications, you can buy the Atari 800 + Disk Drive + Printer together with a selection of business packages.

Silica Shop have put together a full catalogue and price list giving details of all the peripherals as well as the extensive range of software that is now available for the Atari 400/800. The Atari is now one of the best supported personal computers. Send NOW for Silica Shop's catalogue and price list as well as details on our users club.

THE FOLLOWING IS JUST A SMALL SELECTION FROM THE RANGE OF ITEMS AVAILABLE:


| | | | | | | | | | |
|---|--|---|---|--|--|---|--|--|--|
| ACCESSORIES Cables Cassettes Diskettes Joysticks Le Stick - Joystick Misc Supplies Paddles | Mountain Shoot Rearguard Star Flite Sunday Golf AUTOMATED SIMULATIONS Crush Crumble Cmp Dates of Ryn Dragons Eye Invasion Orion Rescue at Rigel Ricochet Star Warrior Temple of Apsah The Count Upper Reaches Aps | BUSINESS Calculator Database Management Decision Maker Graph-It Invoicing Librarian Mort & Loan Anal Nominal Ledger Payroll Personal Finl Mgmt Purchase Ledger Sales Ledger Statistics 1 Stock Control Telexink 1 Visicalc Weekly Planner Word Processor | DYNACOMP Alpha Fighter Chompelo Crystals Forest Fire Intruder Alert Monarch Moonprobe Moving Maze Nominos Jigsaw Rings of the Emp Space Tilt Space Trap Stud Poker Triple Blockade | Maths-Tac-Toe Metric & Prob Solvg Mugwump Music Terms/Notatn Musical Computer My First Alphabet Number Blast Polycalc Presidents Of U.S. Quiz Master Starware Stereo 3D Graphics Three R Math Sys Video Math Flash Wordmaker | Scram States & Capitals Touch Typing EMI SOFTWARE British Heritage Cribbage/Dominos Darts European Scene Jig Hickory Dickory Humpty Dumpty Jumbo Jet Lander Snooker & Billiards Submarine Commdr Super Cubes & Tilt Tournament Pool | Castle Centurlon Checker King Chinese Puzzle Codecracker Comedy Diskette Dice Poker Dog Daze Domination Downhill Eastern Front Galahad & Holy Gr Graphics/Sound Jax-O Jukebox Lookahead Memory Match Midastouch Minotaur Outlaw/Howitzter Preschool Games Pro Bowling Pushover Rabbitz Reversi II Salmon Run 747 Landing Simul Seven Card Stud | Sleazy Adventure Solitaire Space Chase Space Trek Sultans Palace Tact Trek Terry Wizards Gold Wizards Revenge ENTERTAINMENT from ATARI Asteroids Basketball Blackjack Centipede Chess Entertainment Kit Missile Command Pac Man Space Invaders Star Raiders Super Breakout Video Easel ON LINE SYSTEMS Crossfire Frogger | Jawbreaker Mission Asteroid Mouskattack Threshold Ulysses/Golden FI Wizard & Princess PERIPHERALS Centronics Printers Disk Drive Epsom Printers Program Recorder RS232 Interface Thermal Printer 16K Memory RAM 32K Memory RAM PERSONAL INT from APX Adv Music System Banner Generator Blackjack Tutor Going To The Dogs Keyboard Organ Morse Code Tutor Personal Fitness Prg Player Piano Sketchpad | PROGRAMMING AIDS from Atari Assembler Editor Disassembler (APX) Microsoft Basic Pascal (APX) Pilot (Consumer) Pilot (Educator) Programming Kit SANTA CRUZ Basics of Animation 'Bots Business Display Lists Graphics Machine Kids 1 & 2 Horizontal Scrolling Master Memory Map Mini Word Processor Page Flipping Player Missile Gr Sounds Vertical Scrolling SILICA CLUB Over 500 programs write for details |
| ADVENTURE INT Scott Adams Adv No 1 Adventureint No 2 Pirate Adv No 3 Mission Imp No 4 Voodoo Cast No 5 The Count No 6 Strange Ody No 7 Mystery Fun No 8 Pyramid of D No 9 Ghost Town No 10 Sav Island 1 No 11 Sav Island 2 No 12 Golden Voy Angle Worms Deflections Galactic Empire Galactic Trader Lunar Lander | BOOKS Basic Ref Manual Compute Atari DOS Compute Bk Atari Compute Magazine De Re Atari DOS Utilities List DOS Manual Misc Atari Books Op System Listing Wiley Manual | CRYSTALWARE Beneath The Pyram Fantasyland 2041 Galactic Quest House Of Usher Sands Of Mars Waterloo World War III * | EDUCATION from APX Alpicalc Atlas of Canada Cubbyholes Elementary Biology Frogmaster Hickory Dickory Inst Compng Dem Lemonade Letterman Mapware | EDUCATION from ATARI Conv French Con+German Cr+Italian Conv Spanish Energy Czar European C & Caps Hangman Invit To Prog 1/2/3 Kingdom Music Composer | ENTERTAINMENT from APX Alien Egg Anthill Attank Avalanche Babel Blackjack Casino Block Buster Block 'Em Bumper Pool | ON LINE SYSTEMS Crossfire Frogger | | | |

FOR FREE BROCHURES - TEL: 01-301 1111

For free brochure and reviews on our range of electronic products, please telephone 01-301 1111. To order by telephone, just quote your name, address, credit card number, and order requirements and leave the rest to us. Post and packing is FREE OF CHARGE in the UK. Express 24 hour delivery available at an additional charge.

- **SHOP DEMONSTRATION FACILITIES** - we provide full facilities at our shop in Sidcup, Monday to Saturday, 9am to 5.30pm (closing Thursday 1pm - Friday 9am).
- **MAIL ORDERS** - we are a specialist mail order company and are able to supply goods direct to your door.
- **MONEY BACK UNDERTAKING** - if you are totally unsatisfied with your purchase, you may return to us within 15 days. On receipt of the goods in satisfactory condition we will give you a full refund.
- **PART EXCHANGE SECOND HAND MACHINES** - we offer a part exchange scheme to trade in many makes of TV games for personal computers.
- **COMPETITIVE PRICES** - our prices, offers and service are very competitive. We are never knowingly undersold and will normally match any lower price quoted by our competitors.
- **HELPFUL ADVICE** - available on the suitability of various computers.
- **AFTER SALES SERVICE** - available on all computers out of guarantee.
- **VAT** - all prices quoted above include VAT at 15%.
- **CREDIT FACILITIES** - we offer credit over 12, 24 or 36 months, please ask for details.

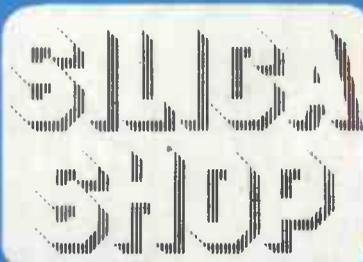SILICA SHOP LIMITED
Dept. HE1083 1-4 The Mews, Hatherley Road, Sidcup,
Kent DA14 4DX Telephone 01-301 1111 or 01-309 1111



FREE LITERATURE

I am interested in purchasing an Atari 400/800 computer and would like to receive copies of your brochure and test reports as well as your price list covering all of the available Hardware and Software.

Name:

Address:

.....

.....

Postcode:

Hobby Electronics HE1083