

Hobby


Electronics

Project Electronics For Everyone

85p

PARA-Q: The Professional Audio Processor

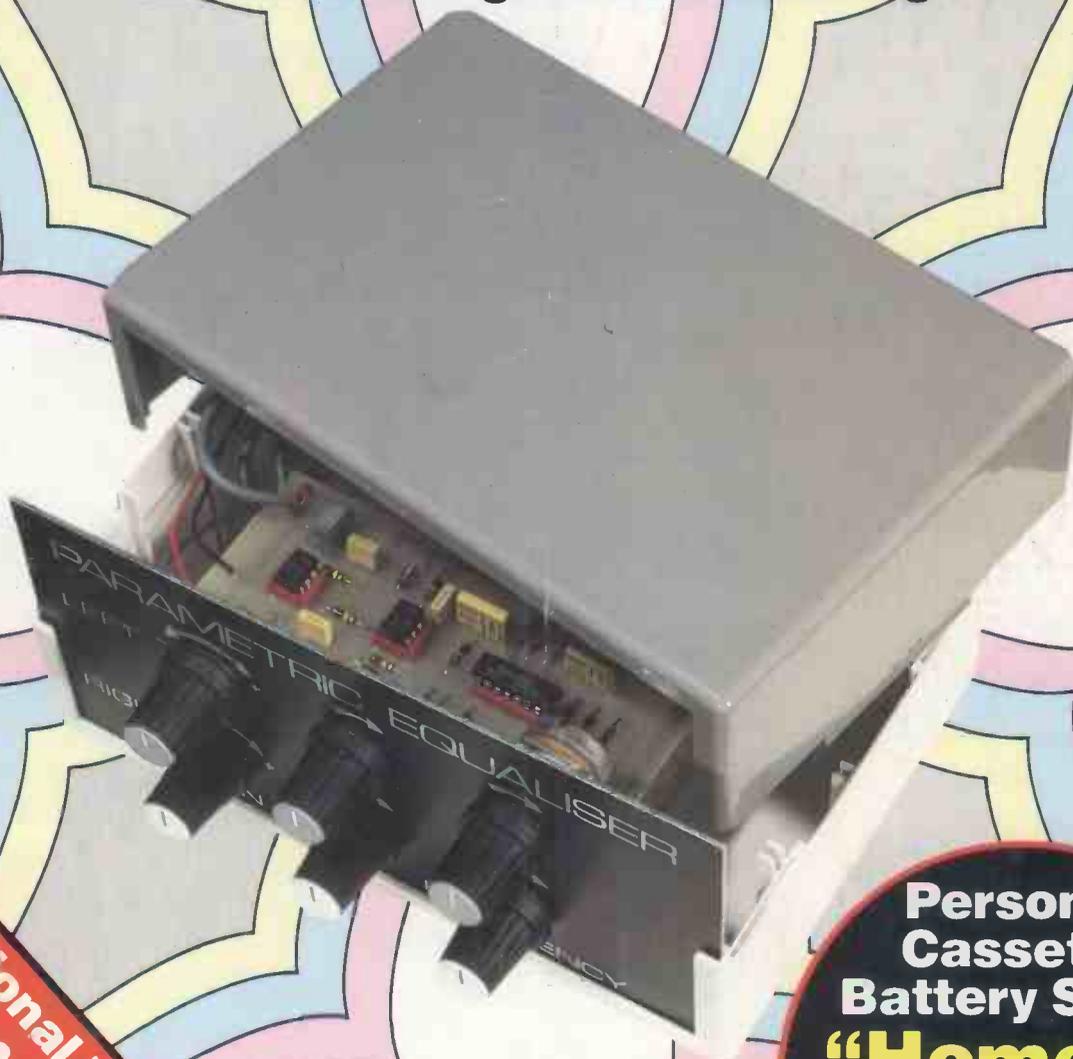Build this project for hifi systems, synthesis and all musical signal conditioning



Sensational In Car Entertainment Offer See Page 19 for the details!

Personal Cassette Battery Saver
"Home Base"
 Power Supply Unit To Build

MORE FOR THE MOTORIST
Two Easy-to-Build Accessory Projects

THE NEW MAPLIN CATALOGUE FOR 84!

NOW WITH PRICES ON THE PAGE


More data, more circuits, more pictures, in the brand new 480 page Maplin catalogue. Take a look at the completely revised Semiconductor section or the new Heathkit section with descriptions and pictures of dozens of kits and educational products from digital clocks to 16-bit business computers. The much expanded computer section itself, gives details of hundreds of pieces of software for Atari, BBC, Commodore 64, Dragon, Spectrum and VIC20. In addition to all this you'll find hundreds of fascinating new items spread through the rest of the catalogue.

As always, the Maplin catalogue is tremendous value for money and now has prices on the page!

Pick up a copy at any branch of W.H.Smith or in one of our shops for just £1.35 or send £1.65 including postage to our Rayleigh address. On sale from 1st Nov 1983.

PROJECTS FOR THE HOME CONSTRUCTOR

Choose from our huge range of value-for-money projects. Projects like our Modem, Mosfet Stereo Amplifier, Home Security System, Frequency Counter and Home Computer add-on kits. Full construction details in our Project Books and brief specifications in our new catalogue. Dozens of fascinating new projects coming soon including a Keyboard for the ZX Spectrum with electronics to make all shifts, single-key operations. Full details in Project Book 9 on sale 11th November 1983. Order As XA09K. Price 70p.

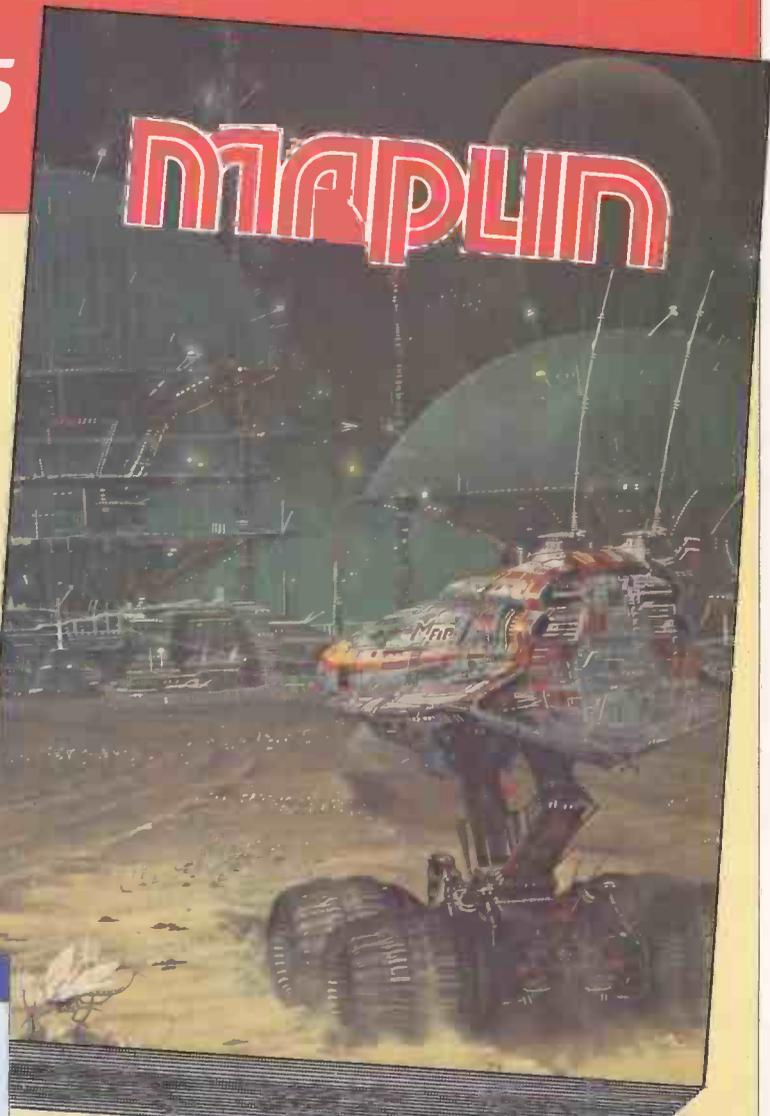

NEW MAPLIN STORE IN SOUTHAMPTON

Opening on 1st November 1983, our new south coast store is at 46-48 Bevois Valley Road, Southampton (Tel: 0703 25831). You will find our full range of components, projects and computers on sale. We are within easy reach of the city centre with good parking close by. Call in and see us soon.



Post this coupon now for your copy of the 1984 catalogue. Price £1.35 + 30p post and packing. If you live outside the U.K. send £2.20 or 11 International Reply Coupons. I enclose £1.65.

Name

Address

HE11/83

MAPLIN ELECTRONIC SUPPLIES LTD

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 ● Shops at: 159-161 King Street, Hammersmith, London W6. Tel: 01-748-0926 ● 8 Oxford Road, Manchester. Tel: 061-236-0281 ● Lynton Square, Perry Barr, Birmingham. Tel: 021-356-7292 ● 282-284 London Road, Westcliff-on-Sea Essex. Tel: 0702 554000 ● *46-48 Bevois Valley Road, Southampton. Tel: 0703 25831.

*Opens 1st November 1983.

All shops closed Mondays. All prices include VAT and carriage. Please add 50p handling charge to orders under £5 total value (except catalogue).

Hobby Electronics

NOVEMBER 1983
VOL 5 No 11

PROJECTS

- ★HE PARA-Q 13
Good quality parametric equaliser units for hifi.
- ★CAR INTERIOR LIGHT DELAY 26
A light shining in darkness . . .
- ★WINDSCREEN WIPER DELAY 36
Variable wipe modification for most cars.
- ★READER'S PROJECT: SIMPLE STEREO PREAMP.. 47
A little boost for subnormal stereos.
- ★DUAL PURPOSE POWER SUPPLY 54
A complete powerhouse for personal stereos.
- ★SHORT CIRCUITS 60
Reviving a fine old Hobby Electronics tradition.



Careers with Microcomputers — page 43

FEATURES

- ★ALL ABOUT ELECTRONICS PART 5 28
The ins and outs of digital circuits.
- ★CAREERS IN ELECTRONICS PART 7 48
Making a career with microcomputers.
- ★MODEL RAIL COMPETITION 44
Design a computer-controlled railway layout.

SPECIALS

- ★BREADBOARD 1983 58
What's on, where to go and how to get there.
- ★SPECIAL OFFER 43
An In-Car Cassette system at a special price.


REGULARS

- Monitor 6
- What's On Next 18
- Points Of View 20
- Buylines 34
- HE Bookshelf 39
- Forward Bias 41
- Readers' Service 53
- HE PCB Service 63
- HE PCB Printout 64
- Classified Advertisements 73

Editor: Ron Keeley
Assistant Editor: Helen Armstrong BA
Technical Illustrator: Jerry Fowler
Advertisement Manager: David Kitchener
Assistant Advertisement Manager: Joanne James
Managing Editor: Ron Harris BSc
Chief Executive: T. J. Connell



Para-Q — page 13

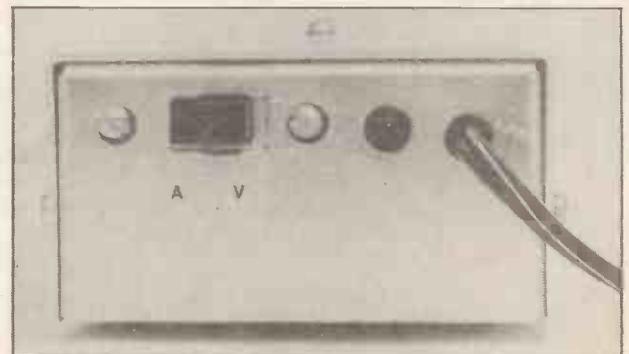

Dual PSU — page 54

Hobby Electronics is normally published on the second Friday of the month prior to the cover date.
Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002. Telex No 881 1896. Published by Argus Specialist Publications Ltd.
Origination by Ebony Typesetting, Trion House, 13 Dean Street, Liskeard, Cornwall PL14 4AB.
Distributed by S. M. Distribution Ltd, 16/18 Trinity Gardens, London SW9 8DX.
Printed by QB Ltd, Colchester. Covers printed by Alabaster Passmore.

Notice: The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. All reasonable care is taken in the preparation of the magazine to ensure accuracy, but Argus Specialist Publications Ltd cannot be held responsible legally. ©Copyright 1983 Argus Specialist Publications Ltd. Member of Audit Bureau of Circulation.

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite

SELF ASSEMBLY ELECTRONIC KITS

PRICES REDUCED
ON SUPER SAVE
D.I.Y. KITS



SX 1000 Electronic Ignition

- Inductive Discharge ● Extended dwell circuit stores greater energy in coil ● Three position changeover switch ● Patented clip-to-coil fitting ● Easy to assemble, easy to fit ● Contact breaker triggered - includes bounce suppression circuit.


SUPER SAVE

SX 2000 Electronic Ignition

- Reactive Discharge ● Combines inductive & capacitive energy storage ● Gives highest possible spark energy ● Patented clip-to-coil fitting ● Easy assembly sequence ● Contact breaker triggered - includes bounce suppression circuit.



SUPER SAVE

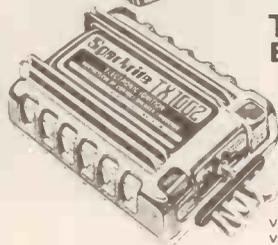


TX 1002 Electronic Ignition

- Inductive discharge ● Extended dwell circuit stores greater energy in coil ● Three position changeover switch ● Contactless or contact breaker triggered ● Clip-to-coil or remote mounting ● Rugged die-cast case ● Contactless adaptors included for majority of 4 & 6 cylinder vehicles ● Easy to build ● For details of vehicles fitted by contactless trigger, ring Technical Service Dept on (0922) 611338-9.

TX2002 Electronic Ignition

- Two separate systems in one unit! ● Reactive Discharge OR Inductive Discharge, with three position changeover switch ● Gives highest possible spark energy ● Clip-to-coil or remote mounting ● Rugged die-cast case ● Contactless or contact breaker triggered ● Contactless adaptors included for majority of 4 & 6 cylinder vehicles ● For details of vehicles fitted by contactless trigger, ring Technical Service Dept on (0922) 611338-9.

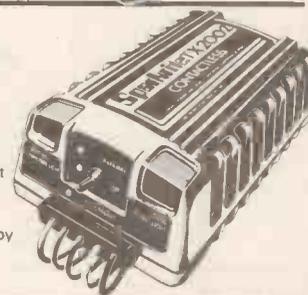

AT-40 Electronic Car Alarm


- Guards doors, boot, bonnet from unauthorised entry ● Armed/disarmed using concealed switch ● 30 second delay-to-arm: 7 second entry delay ● Can alternatively be wired to exterior key switch ● Flashes headlights & sounds horn intermittently for 60 seconds when activated ● Security loop protects accessories ● Low consumption C-MOS circuitry.



NEW

AT-80 Electronic Car Security System

- Guards doors, boot, bonnet from unauthorised entry ● Armed/disarmed from outside vehicle by magnetic key fob passed across sensor pad adhered to inside of windscreen ● Individually programmable code ● 30 second delay-to-arm ● Flashes headlights and sounds horn intermittently for 60 seconds when activated ● Security loop protects accessories ● Function lights to assist setting-up ● Low consumption C-MOS circuitry.

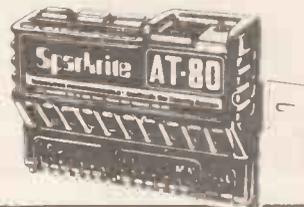

SUPER SAVE

ULTRASONIC Intruder Detector

- Supplementary to AT-40 & AT-80 ● Will work in conjunction with any door switch input or voltage sensing alarm ● Detects attempted break-in and movement within passenger compartment & triggers alarm ● Includes high efficiency ultrasonic transducers ● Crystal controlled for low drift ● Ingenious sensitivity control allows freedom from false alarms ● Low current consumption



NEW

VOYAGER Car Drive Computer

- 12 functions centred on Fuel, Speed, Distance and Time ● Single chip microprocessor ● Large high brightness fluorescent display with auto-dimming feature ● High accuracy distance & fuel transducers included ● Displays MPG, L/100km and miles/litre at the flick of a switch ● Visual & audible warnings of excess speed, ice, lights-left-on ● Independent LOG & TRIP functions ● Low consumption crystal controlled circuitry.



SPECIAL OFFER
"FREE" MAGIDICE KIT WITH
ALL ORDERS OVER £40.00



MAGIDICE Electronic Dice

- Triggered by waving hand over dice ● Completely random selection ● Bleeps & flashes during 4 sec tumble ● Throw displayed for 10 seconds then flashes to conserve battery ● Low consumption C-MOS circuitry.

SUPER SAVE

SPARKRITE (A Division of Stadium Ltd.) 82 Bath Street, Walsall, WS1 3DE England Tel: (0922) 614791

Allow 28 days for delivery

KIT	OLD PRICE	NEW PRICE
SX 1000	£12.95	£11.95
SX 2000	£19.95	£18.95
TX 1002	£22.95	£22.95
TX 2002	£32.95	£32.95
AT-40	—	£9.95
AT-80	£32.95	£24.95
ULTRASONIC	—	£17.95
VOYAGER	£64.95	£64.95
MAGIDICE	£9.95	£6.95

NEW!
NEW!

NAME _____ HE/11
ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF. _____

CHEQUE No. _____

PRICES INC. VAT, POSTAGE & PACKING

PHONE YOUR ORDER WITH



BRANDLEADING BRITISH ELECTRONICS
CUT OUT THE COUPON NOW!

74 SERIES

7400	0.25	74125	0.50	74LS05	0.20	74LA196	0.80	74LS887	4.50	74C157	1.50	4077	18p	CA3060E	350p	LM3916	225p	XR2206	400p	BUY69C	200p	2N3053	25p
7401	0.25	74126	0.50	74LS08	0.20	74LA197	0.80	74LS90	4.50	74C160	0.90	4078	16p	CA3080E	70p	LM13600	110p	XR2110	400p	JJ10	50p	2N3054	55p
7402	0.25	74127	0.50	74LS09	0.20	74LA221	1.90	74LS02	0.30	74C161	0.90	4081	14p	CA3088	48p	M51513L	575p	RC221	575p	MJ2024	E4	4N3055	35p
7403	0.25	74128	0.50	74LS10	0.20	74LS240	1.20	74S04	0.30	74C162	0.90	4082	15p	CA3089	200p	M51516L	500p	ZN414	80p	MJ2501	225p	2N3442	140p
7404	0.25	74129	0.50	74LS11	0.20	74LS241	1.20	74S05	0.60	74C163	0.90	4086	40p	CA3090A	375p	MB3712	250p	ZN419C	190p	MJ2955	90p	2N3553	240p
7405	0.30	74130	0.75	74LS12	0.20	74LS242	0.75	74S06	0.60	74C173	0.48	4089	25p	CA3130E	90p	MB3730	400p	ZN423E	130p	MJ3001	225p	2N3702/3	10p
7406	0.30	74131	0.75	74LS13	0.20	74LS243	0.75	74S10	0.40	74C174	1.00	4090	24p	CA3140E	100p	MC1310P	150p	ZN424E	130p	MJ3001	225p	2N3702/3	10p
7407	0.30	74132	0.75	74LS14	0.20	74LS244	0.75	74S11	0.40	74C175	1.00	4091	24p	CA3160E	100p	MC1459	36p	ZN425E	340p	MJ3001	225p	2N3707/1	10p
7408	0.30	74133	0.75	74LS15	0.20	74LS245	1.40	74S11	0.50	74C193	1.15	4096	70p	CA3160E	100p	MC1496	36p	ZN427E	580p	MJ3001	225p	2N3707/2	10p
7409	0.30	74134	0.75	74LS16	0.20	74LS246	0.70	74S12	0.50	74C194	1.20	4097	290p	CA3162E	150p	MC1496	36p	ZN428E	450p	MJ3001	225p	2N3707/3	10p
7410	0.30	74135	0.75	74LS17	0.20	74LS247	0.70	74S13	0.50	74C221	1.50	4099	100p	CA3189E	300p	MC3403	65p	ZN429E	210p	MJ3001	225p	2N3707/4	10p
7411	0.30	74136	0.75	74LS18	0.20	74LS248	0.70	74S14	0.50	74C222	1.40	4100	100p	CA3240E	110p	MF10CN	300p	ZN430E	780p	MJ3001	225p	2N3707/5	10p
7412	0.30	74137	0.75	74LS19	0.20	74LS249	0.70	74S15	0.50	74C241	1.80	4103	40p	CA3240E	110p	MC1459	36p	ZN435E	340p	MJ3001	225p	2N3707/6	10p
7413	0.30	74138	0.75	74LS20	0.20	74LS250	1.40	74S16	0.50	74C242	1.80	4104	40p	DA102	390p	MLN20	800p	ZN1034E	200p	MPSA20	50p	2N3707/7	10p
7414	0.30	74139	0.75	74LS21	0.20	74LS251	1.20	74S17	0.50	74C243	1.80	4105	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/8	10p
7415	0.30	74140	0.75	74LS22	0.20	74LS252	1.20	74S18	0.50	74C244	1.80	4106	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/9	10p
7416	0.30	74141	0.75	74LS23	0.20	74LS253	0.45	74S19	0.50	74C245	1.80	4107	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/10	10p
7417	0.30	74142	0.75	74LS24	0.20	74LS254	0.45	74S20	0.50	74C246	1.80	4108	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/11	10p
7418	0.30	74143	0.75	74LS25	0.20	74LS255	0.45	74S21	0.50	74C247	1.80	4109	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/12	10p
7419	0.30	74144	0.75	74LS26	0.20	74LS256	0.45	74S22	0.50	74C248	1.80	4110	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/13	10p
7420	0.30	74145	0.75	74LS27	0.20	74LS257	0.45	74S23	0.50	74C249	1.80	4111	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/14	10p
7421	0.30	74146	0.75	74LS28	0.20	74LS258	0.45	74S24	0.50	74C250	1.80	4112	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/15	10p
7422	0.30	74147	0.75	74LS29	0.20	74LS259	0.45	74S25	0.50	74C251	1.80	4113	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/16	10p
7423	0.30	74148	0.75	74LS30	0.20	74LS260	0.35	74S26	0.50	74C252	1.80	4114	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/17	10p
7424	0.30	74149	0.75	74LS31	0.20	74LS261	0.80	74S27	0.50	74C253	1.80	4115	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/18	10p
7425	0.30	74150	0.75	74LS32	0.20	74LS262	0.80	74S28	0.50	74C254	1.80	4116	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/19	10p
7426	0.30	74151	0.75	74LS33	0.20	74LS263	0.25	74S29	0.50	74C255	1.80	4117	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/20	10p
7427	0.30	74152	0.75	74LS34	0.20	74LS264	0.45	74S30	0.50	74C256	1.80	4118	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/21	10p
7428	0.30	74153	0.75	74LS35	0.20	74LS265	0.45	74S31	0.50	74C257	1.80	4119	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/22	10p
7429	0.30	74154	0.75	74LS36	0.20	74LS266	0.45	74S32	0.50	74C258	1.80	4120	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/23	10p
7430	0.30	74155	0.75	74LS37	0.20	74LS267	0.45	74S33	0.50	74C259	1.80	4121	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/24	10p
7431	0.30	74156	0.75	74LS38	0.20	74LS268	0.45	74S34	0.50	74C260	1.80	4122	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/25	10p
7432	0.30	74157	0.75	74LS39	0.20	74LS269	0.45	74S35	0.50	74C261	1.80	4123	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/26	10p
7433	0.30	74158	0.75	74LS40	0.20	74LS270	0.45	74S36	0.50	74C262	1.80	4124	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/27	10p
7434	0.30	74159	0.75	74LS41	0.20	74LS271	0.45	74S37	0.50	74C263	1.80	4125	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/28	10p
7435	0.30	74160	0.75	74LS42	0.20	74LS272	0.45	74S38	0.50	74C264	1.80	4126	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/29	10p
7436	0.30	74161	0.75	74LS43	0.20	74LS273	0.45	74S39	0.50	74C265	1.80	4127	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/30	10p
7437	0.30	74162	0.75	74LS44	0.20	74LS274	0.45	74S40	0.50	74C266	1.80	4128	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/31	10p
7438	0.30	74163	0.75	74LS45	0.20	74LS275	0.45	74S41	0.50	74C267	1.80	4129	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/32	10p
7439	0.30	74164	0.75	74LS46	0.20	74LS276	0.45	74S42	0.50	74C268	1.80	4130	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/33	10p
7440	0.30	74165	0.75	74LS47	0.20	74LS277	0.45	74S43	0.50	74C269	1.80	4131	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/34	10p
7441	0.30	74166	0.75	74LS48	0.20	74LS278	0.45	74S44	0.50	74C270	1.80	4132	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/35	10p
7442	0.30	74167	0.75	74LS49	0.20	74LS279	0.45	74S45	0.50	74C271	1.80	4133	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/36	10p
7443	0.30	74168	0.75	74LS50	0.20	74LS280	0.80	74S46	0.50	74C272	1.80	4134	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/37	10p
7444	0.30	74169	0.75	74LS51	0.20	74LS281	0.80	74S47	0.50	74C273	1.80	4135	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/38	10p
7445	0.30	74170	0.75	74LS52	0.20	74LS282	0.80	74S48	0.50	74C274	1.80	4136	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/39	10p
7446	0.30	74171	0.75	74LS53	0.20	74LS283	0.80	74S49	0.50	74C275	1.80	4137	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/40	10p
7447	0.30	74172	0.75	74LS54	0.20	74LS284	0.80	74S50	0.50	74C276	1.80	4138	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/41	10p
7448	0.30	74173	0.75	74LS55	0.20	74LS285	0.80	74S51	0.50	74C277	1.80	4139	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/42	10p
7449	0.30	74174	0.75	74LS56	0.20	74LS286	0.80	74S52	0.50	74C278	1.80	4140	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/43	10p
7450	0.30	74175	0.75	74LS57	0.20	74LS287	0.80	74S53	0.50	74C279	1.80	4141	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/44	10p
7451	0.30	74176	0.75	74LS58	0.20	74LS288	0.80	74S54	0.50	74C280	1.80	4142	40p	DA102	390p	MLN20	800p	ZN1040E	670p	MPSA20	50p	2N3707/45	10p
7452	0.30	74177	0.75	74LS59	0.20	74LS289																	

MONITOR

Show In Scotland

The first **Scottish Home Computer and Electronics Show**, sponsored by the Evening Times, will be held at the Anderson Centre, Glasgow from 11th to 13th November.

Opening times are: Friday 11th, 12 noon to 8 pm; Saturday 12th, 10am to 6pm; Sunday 13th, 10am to 5pm. The show is planned to cover home computers, hardware, software, add-ons, CB, amateur radio, hi-fi and video. The Anderson Centre is adjacent to the main bus depot and not too far from Central Station; car parking is said to be good.

Further information from **Trade Exhibitions Scotland, 53/55 Commissioner Street, Crieff, Perthshire PH7 4DA. Tel: (0764) 4204.**

CMOS Z80

A CMOS version of the popular Z80 microprocessor, fully hardware and software compatible with the NMOS part, is now available from **Altek Microcomponents**. The Sharp LH5080/5080L has all the features of the standard Z80, with a DC to 2MHz clock rate and the added bonus of low power consumption. Typical operating current is 10mA from a 5V power supply, and this can be cut to just 2uA with the LH5080L, which offers a power-down mode. The low power consumption offered by this design is of great importance in battery-powered equipment, such as portable instruments and remote telemetry stations.

Enquiries to **Altek Microcomponents Ltd., 22 Market Place, Wokingham, Berks. RG11 1AP. Tel: (0734) 791579.**

Companies In Bristol


HomeTech '83, a new computer and leisure technology exhibition, is being held at the **Bristol Exhibition Centre** on 11th, 12th and 13th November — the first major public exhibition of its kind to be held in the west of England.

The Friday is specifically for educationalists and small businessmen, while the other two days will be orientated to hobbyists, students and the rest of us.

Look for local advertising, or contact **Tomorrow's World Exhibitions, 9 Park Place, Clifton, Bristol BS8 1JP. Tel: (0272) 292156.**

PCB Protectors

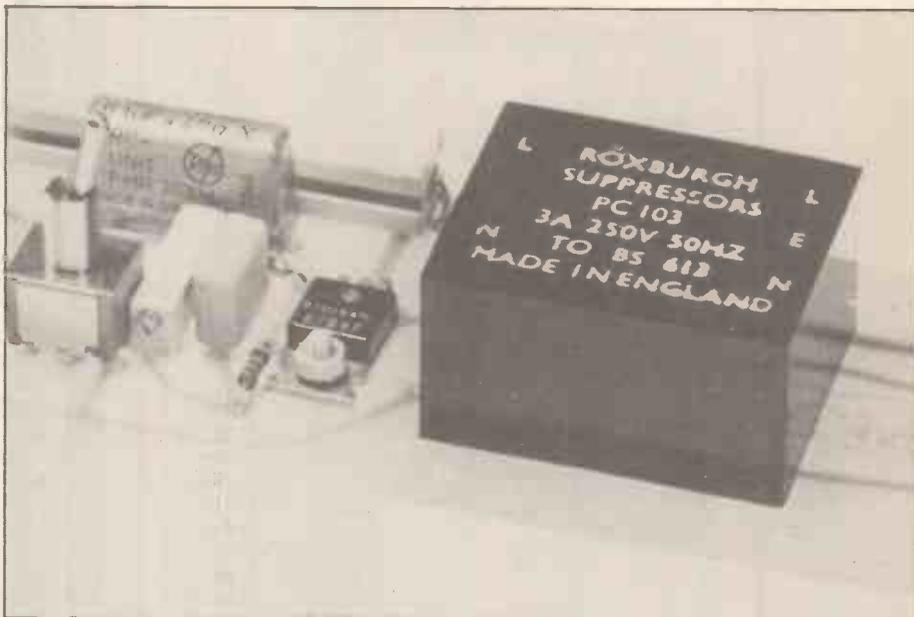The range of mains filters available from **Roxburgh Suppressors** now includes two filters designed for direct mounting onto a printed circuit board. Designated PC 103 and PC 105, they are rated at 3A and 5A respectively. The filters are



suitable for protecting a wide range of equipment from mains transients and interference. Rifa self healing capacitors ensure reliability and the units are fully encapsulated for complete environmental protection. The photograph shows the PC 103 mounted on a mains input board.

For further information please contact **Rick Keens at Roxburgh Suppressors. Tel: (0797) 223725.**

More Meters

The **Pantec Pan 2001**, a high quality professional multimeter is currently available from **Electronic & Computer Workshop**, priced at £99.00 plus £1.00 p&p and VAT. The meter, supplied with a shock proof plastic case, will measure capacitance and features a diode test facility plus a square wave generator from 15Hz to 15kHz in four ranges.

The unit will measure DC-AC voltages from 100uV to 1000V in five ranges; DC-AC current from 1uA to 10A in six ranges; resistances from 0R1 to 20R in six ranges and capacitance from 1pF to 20uF in five ranges. An optional temperature measuring facility gives a -50°C to +150°C measuring range.

Specifications include a 3½ digit 19mm LCD, automatic polarity, overload indication and battery test, a 10Hz frequency range, with protection on all ranges up to 250VAC/DC. Power consumption is low with battery life in excess of 200 hours continuous operation. Overall dimensions are 130 x 125 x 400mm.

The **Velleman Universal** four digit up/down counter with memory is a CMOS alternative to conventional TTL counters. In kit form, it is priced at £38.99 plus £1.00 p&p and VAT.

The counter incorporates four multiplexed displays, with a maximum display of 9999 and a maximum count frequency of 2MHz, together with the

benefit of low current consumption from a 5V supply.

Able to add or subtract (up or down), the counter has an 'Auto-Reset' facility, which halts the counter at zero producing a signal simultaneously with that of the counter passing through zero. BCD switches allow the counter and/or register to be loaded, and enables a number to be preset for continuous comparison with the content of the counter.

Further features allow the selection and display of any value, as a starting point for the counter, and the ability to hold a display value, whilst allowing the internal counter to run. Counter input is via an integrated Schmitt trigger and the display control has facilities for die out, normal operation, or the compression of conducting zeros.

The **Steinel Master Check 3** is a versatile voltage tester. Of handy pocket size, the Master Check 3 will test supply voltages, various AC and DC voltages, and battery operated appliances with applications ranging from testing batteries to three-phase AC motors. It operates in the 6 to 380VAC/DC range (with line voltages of either 110, 240, or 415V) and is surge voltage proof to 6kV. Input resistance is 2 to 5kR (PTC controlled) and frequency ranges from 0 to 100Hz, with an operating temperature range of -10°C to +50°C. Maximum peak current at 380V rms is 180mA, with continuous current after regulation approximately 10mA. The tester, which has a maximum operating period of 30s (DC), has been tested and approved to the German VDE 0425 standard.

The Master Check 3, designed for rigorous use, is £15.49 (plus £1.00 p&p and VAT). For further information please contact **Caroline Stewart, Electronic & Computer Workshop Ltd., 171 Broomfield Rd., Chelmsford, Essex CM1 1QJ. Tel: (0245) 62149.**

Fastware

JRS software for the ZX81 will be incorporating a new system which has been developed to enable programs to be loaded at the maximum speed possible within the limitations of the ZX81 itself, without needing any additional hardware. Data is loaded at between 300 and 500 bytes per second, or ten to fifteen times faster than the normal ZX81 rate, and almost any program can therefore effectively be loaded in under a minute.



This breakthrough has been achieved by drastic modification of the input/output signals, ie altering the waveform to take fullest advantage of ZX81 circuitry characteristics. At the same time, the maximum frequency has been limited to 4kHz, to guarantee reliable operation even when using poor quality tapes or low-cost cassette recorders (the system has been found to work perfectly within variations in normal tape speed from -10% to +12%).

JRS's sample program, using a full 16K of RAM with 'Fast Loading' system replaces the normal loading time over six minutes, with a 'Fast Loading' time of only 36 seconds, excluding the load routine, which takes 16 seconds.

For further information contact JRS Software Ltd., 19 Wayside Avenue, Worthing, West Sussex BN13 3JU. Tel: (0903) 65691.

Boxes And Tools

A new brochure from OK Industries describes the range of PacTec enclosures. The range of moulded enclosures offers off-the-shelf prototype kits and production units, moulded-through colour for long-lasting looks and inexpensive customising. Made of impact-resistant ABS the modular enclosures are constructed from standard parts and accessories to eliminating the cost of special tooling. A range of sizes covers small-to-medium enclosure requirements, and the 22 page catalogue details exact dimensions, accessories, colours and options.

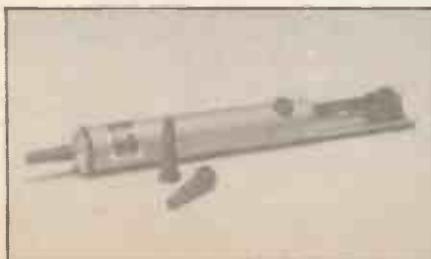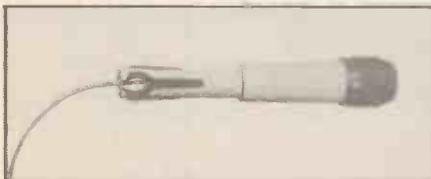

Suitable for field service, laboratory, light production or hobby use, OK's ST-400 is a micrometer-adjustable wire stripping tool which can accommodate both solid and stranded wire from 18 AWG through 30 AWG (1.0 to 0.25mm). The user simply turns the micrometer knob until the desired wire size is shown on the dial window, and this automatically adjusts the stripping blades for a precise and nick-free strip. Strip length is selected by using the moulded-in scale, and the tool can then be rotated once or twice to cut the insulation. Compatible with all common types of insulation, it has hardened steel blades for long life and is extremely compact and lightweight.

OK's 'desolder' pump has a tip made of a special bronze alloy composition designed for long life. Moreover, static discharges automatically through the hand of an earthed operator, making the DP-2 suitable for removing sensitive CMOS components. Suction is precisely regulated to prevent damage to delicate circuits.

For catalogue and prices contact OK Industries UK Ltd., Dutton Lane, Eastleigh, Hants SO5 4AA. Tel: 0703 610944.



Mini Robot

Colne Robotics have developed a two-wheeled mobile robot known as the Zeaker Micro-Turtle. Its movements can be controlled by any microcomputer, via a connecting umbilical ribbon cable. Software is provided which permits the movements to be memorised and reproduced — Zeaker has a learning capability. Sensors indicate when the robot touches an obstacle, and the computer instructs it to find an alternative path. Stimulation of the sensors produces one of two notes on a horn, according to the direction of Zeaker's movements.

An additional feature is the built-in, retractable pen beneath the unit, which can trace the path taken across a surface. The pen itself is controlled by the computer, and its position (lowered or retracted) is indicated by an LED on top of the robot. Two further LEDs can indicate the direction in which the unit is travelling.

The ZEAKER Micro-Turtle is aimed at the educational market in which schools wish to extend their computer teaching syllabus to cover control systems, through the use of microcomputers. Teachers are also interested in the fact that with appropriate software, ZEAKER is capable of drawing logo graphics. To keep in line with the rapid fall in microcomputer prices, the unit has deliberately been produced at a very low cost: £52.00 +VAT for the kit version and £69.50 +VAT for the assembled robot. The unit comes complete with interface, power supply, operation manual and software. It can be driven by any microcomputer which has an 8-bit bi-directional port, as well as by the ZX81 or Spectrum for which special interfaces are also available from Colne Robotics. Additional interfaces are planned for other popular microcomputers.

For further information contact Colne Robotics Co. Ltd., Beaufort Road, Off Richmond Road, East Twickenham, Middx. TW1 2PH. Tel: 01 892 8197.

But its not as cute as HEBOT!

Plug-In Power

A new range of low cost DC power supplies suitable for powering logic, microprocessor and linear circuitry is now available from Electronart Design.

All the units are housed within a



MONITOR

tough 13 amp plug style case, but there the similarity with calculator "AC Adaptors" and the various "Battery Eliminators" ends. These units are stabilised and well regulated with output by way of 4mm sockets, thermal fuse protection and LED output indicators. Models are available with single or twin outputs of 5, 12, 15 or 18VDC. Many extras such as crowbar overvoltage protection, power-on reset and power down signals for microprocessor and memory applications are available. The company can also supply 'specials' in any quantity.

The units should be of interest to hobbyists and educational users as well as industry. For further details and price list contact **Electronart Design, 78, Kimberley Ave., Ilford, Essex IG2 7AS. Tel. 01 590 7979.** They will send details as soon as these are available.



Chips From Ferranti

Ferranti Electronics has recently introduced the ZN411E which, with a minimum of external components, provides precise speed control for electric motors. Now generally available the circuit was originally designed for use in a professional power drill. The ZN411 will operate from the AC mains or a suitable DC supply and has an on-chip shunt regulator. The circuit has a power down reset facility and a 'soft start' capability whereby the speed builds up smoothly to the set speed.

The ZN414 tuned radio frequency (TRF) radio chip has been used in a wide range of consumer products.

In order to meet new applications requiring a higher output level, **Ferranti Electronics** has now introduced the ZN415E, which incorporates an output stage enabling the device to directly drive high-efficiency headphones. Like its predecessor, it operates off a single cell battery with low current consumption and is available in an eight pin DIL package. High quality AM medium and long wave reception is possible with only six external components including the ferrite aerial. Simple but effective AGC action is provided and no setting up or alignment is needed.

Full details are available from **Ferranti Electronics Ltd., Fields New**

Road, Chadderton, Oldham, Lancashire OL9 8NP. Tel: 061 624 0515.

Carry On Camel

Cambridge Microelectronics, popularly known as **Camel Products**, have a new batch of micro-related products now available. The PROMER-81 is a low cost Eprom programmer for use with the ZX81. The PROMER-81 will program 2516, 2536, 2716 and 2732 Eproms and comes with full user notes suited for novices as well as experienced users. The notes include the routines for blowing Eproms for programming.

All the standard programmer functions of CHECK, SPECIFY, READ, PROGRAM and VERIFY are provided, and the control program, which is supplied on tape, includes safety features such as a check on Vpp status before executing a task.

The PROMER-81 requires four PP/batteries to provide regulated programming voltage, and comes assembled and tested, with an extension connector at the rear. The price is £19.95 plus VAT. With the PROMER-81, pricing tables, toolkits, educational and scientific programs, assemblers, text editors etc. (to quote Camel) can be instantly and reliably called up from ROM readers like ROM-81 and DREAM-81, also by Camel (both of which have featured in these pages).

So far unfeatured by Monitor is the CRAMIC-81, a 16K memory module using special CMOS chips which need only a tiny amount of power to retain data when not in operation. The power is supplied by a ten-year-life Lithium battery in standby mode. When in use power comes from the ZX-81. The CRAMIC-81 behaves like an ordinary RAMPack, but can be powered down and removed from the micro without losing data.

It also has a rear connector so that another RAMPack can be used at the same time. While the two units occupy the same memory area, you can choose either memory via your program, without using links or switches, and actually run two separate programs with alternating screen displays.

The CRAMIC-81 comes in a moulded, low-lying ABS case with a cable connector. We don't have a price for it at present.

Last from Camel isn't a ZX-81 add-on, but a three-way PSU. This unit features maximum current ratings of +5V at 3A, +12V at 1A and -12V at .25A, with a normal maximum continuous power output rating of 25W at 40°C. The construction includes a toroidal mains transformer, high CXV, high surge rating electrolytic capacitors, and linear voltage regulators LM350T, 7812 and 7912 for short circuit protection on all outputs. The front panel includes double-pole mains rocker switch and

LED indicator, and the screw type connector block allows users freedom of choice in interface connectors.

We don't have a price for this one either, or a photograph, but as with all these products contact **Cambridge Microelectronics Ltd., One Milton Rd., Cambridge CV4 1UY** for details. Tel: (0223) 314814.

Switchable Switches


Dean Electronics have produced a compact PCB mounting switch module with an eight pin configuration, which allows designers to choose any of six different contact functions simply by selecting the appropriate pins when laying out the circuit.

The MED switch is designed for 0.1in grid PCB mounting, and is available in both momentary and push-key action.

The MED keycap system allows maximum versatility by providing buttons and bezels for the switch, which can accommodate one or two high brightness 'pinhead' or rectangular bar LEDs, or work without illumination, as desired. These allow for maximum mounting density in any configuration. The keycaps are available in ten standard colours.

The final aspect of the range is the Vario-Support, which provides a variable mounting frame which enables front panel mounting of the MEC range, removes the need for PCB mounting and consequent wear and tear on the PCB, and aids accurate alignment of the switch system to the front-panel cut-outs when assembling. Vario-Support is available in any cell combination from one times one to ten times ten matrix.

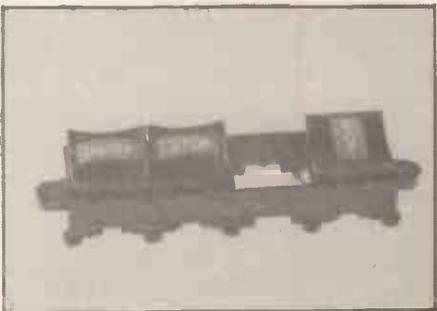For information contact **Dean Electronics Ltd., Glendale Park, Fernbank Rd., Ascot, Berks. Tel: (0344) 885661.**



Small Business Software

A demonstration tape of three programs for the 48K Spectrum, from **Hilderbay Ltd.**, is now available for £3.95. The three programs are business software: Payroll, Stock Control and Statutory Sick Pay.


The Stock Control program can keep records on over 1000 stock lines, handling either stock changes or closing stock, with information on current stock levels and value instantly available.

Stock lines can be located by name, inserted or deleted in under two seconds.

The Payroll program can deal with up to 50 employees at a time; tax and national insurance details are built into the program; where there are no changes, a single keystroke will compute an employee's situation, and another will print a payslip. Results from the Payroll program (but not the demo tape!) are guaranteed to be correct.

The Statutory Sick Pay program will carry out all the calculations associated with SSP, so that the user only has to enter essential information. Simple cases take about 40 seconds to enter, very complex cases up to 90 seconds.

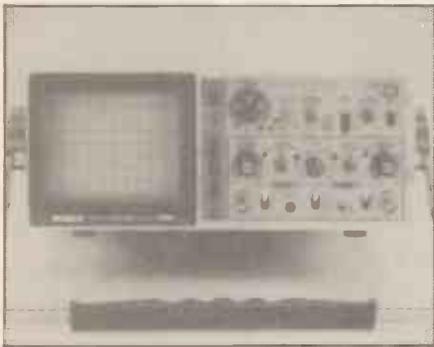For the demo tape or more information contact Hilderbay Ltd., 8/10 Parkway, Regent's Park, London NW1 7AA. Tel: 01 485 1059.




Slimline Oscilloscope

The new V-222 oscilloscope from Hitachi is a low-cost 20MHz dual-trace model incorporating a larger six rectangular CRT in an ultra-light, slim casing. The V-222 has a number of unique features to assist in the analysis of complex waveforms: an alternative sweep magnifier enables any section of the waveform to be expanded ten times and displayed simultaneously with the un-magnified signal; a DC offset control and offset measurement socket allows a digital voltmeter to be used to monitor voltages on the screen, whilst a low impedance signal output socket enables a frequency meter or a counter-timer to be connected.

Comprehensive triggering facilities include an active sync separator for video signals, and an alternate trigger made which enables two unsynchronised signals to be displayed simultaneously. The V-222 has a sensitivity of 1mV/cm and a maximum sweep speed of 20ns/cm. Fully variable gain and sweep rate controls have uncalibrated warning lights to avoid accidental measurement errors. Full XY mode and Z modulation facilities are provided, and the large CRT has an internal parallax-free graticule with variable illumination and 0,10,90 and 100% markers for rise time measurement.

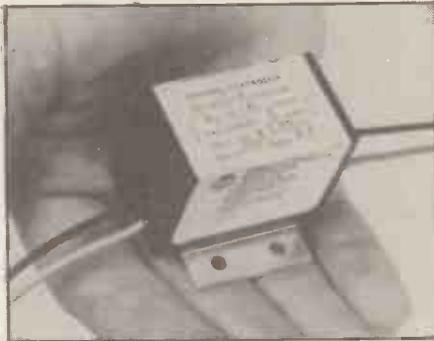The V-222 comes complete with two x1 and x10 switchable probes and carries a full two year warranty. Price in the UK is £340 plus VAT, a lower specification version is also available at £295 plus VAT. These new Hitachi oscilloscopes are available ex-stock from Reltech Instruments, Coach Mews, St. Ives, Huntingdon, Cambs PE17 4BN. Tel: (0480) 63570.



Battery Protection

A new device has been developed by S & W Battery Charging Systems to prevent premature battery failure and reduce the cost of battery maintenance. This unit simply be inserted between the charger and the battery.

No larger than a matchbox, the unit is designed to constantly monitor battery voltage without interrupting the system. Once the cells are full charged, the controller will pass only sufficient current to maintain the battery in a fully charged condition without overcharge. The controller may be adjusted externally to give a variety of voltages, making one unit suitable for a wide range of lead acid or nicad batteries. It is simple and quick to fit into existing charging systems, and reduces maintenance and energy costs.

Enquiries to: S & W Battery Charging Systems Ltd., Nailsea Trading Estate, Southfield Road, Nailsea, Bristol BS19 1JL. Tel: (0272) 855161.

Lynx Escapes

The new 96K version of Computers' popular Lynx microcomputer made its first public appearance at the Earls Court Computer Fair in London from June 16-19, and is available from retailers, priced £299 including VAT.

The expanded RAM of the 96K Lynx provides 37K5 directly accessible to Basic in high resolution full colour, with up to 24K more available to programs using machine code. At 20K, the ROM is 4K larger than that of the 48K Lynx; additional ROM features on the 96K Lynx include drivers for both parallel and serial printers, a range of pre-formatted sound effects, CIRCLE command and commands to use the

24K of machine code assessable RAM as a data store for programs running in Basic.

Owners of the 48K Lynx will be able to have their machines upgraded to full 96K specification through their Lynx dealers, who will arrange for the machines to be returned to Computers for upgrading. The price of the upgrade will be £89.95, including VAT.

Enquiries to: Computers, 33A Bridge Street, Cambridge CA3 4B. Tel: (0223) 315063.

Batting Back and Forth

Gould Activair UK, who have been developing zinc-air power-cell technology from a basis of NASA research on air electrodes, have now been awarded a NASA contract to provide zinc-air power packs for use on board the Space Shuttle.

Previously, NASA used long-life lithium batteries, but zinc-air batteries are now longer-lasting (in this case, 5 to 5.5 amp-hours as opposed to 3 amp-hours). This means fewer power packs, which in turn mean less weight for the Shuttle to carry.

The Shuttle power packs will be 15V each, measuring 138.4mm x 81.28 mm x 19.05mm, weighing 482g, and composed of sixty individual disc-shaped cells. They will be used to operate the in-cabin radio system which enabled the astronauts to talk to each other and to the ground.

Wonder if they listen to Radio One in between chats?



Short

The Vintage Wireless Co. have been tightening up their already tight act with new mail order procedures, the dropping of some 'time consuming' lines from their lists and — last but not least — they are moving to new premises, not far from the present ones. We don't yet have their new address, but anyone interested in old and industrial electronics and wireless equipment and VWC's regular price lists and newsletters should write as usual to 64 Broad St., Staple Hill, Bristol BS16 5NL. Tel: (0272) 565472.

MONITOR

Computer Fair

The Chiltern Computer Fair, the first of its kind in that region, will be held on 22 October at the Challney Community College, Stonygate Rd., Luton, Beds. There will be about a hundred companies covering all aspects of home, business and educational computers. The site is very near to junction 11 on the M1, so is easy to get to.

Enquiries from exhibitors and, presumably, others should go to Mr. John Pinney, on Luton (0582) 56400 or 508616.

Stand And Kit

Electroni Kit whose FX-Computer was reviewed in October's HE, write to tell us that they will be at the Leisure Electronics Trade Show, Heathrow Penta, from 13th to 15th February. Anyone who wants to inspect the FX-Computer, FX-Kits or Electroni-Kit's Chip Shop Kits, can do so.

Electroni-Kit are at 388 St. John Street, London EC1V 4NN. Tel: 01 278 0109.

Domestic Irons

Cooper Tools, who manufacture the professional-quality range of Weller soldering irons, have come up with the idea of marketing a set of soldering irons for home use, not restricted to conventional electronics soldering, but also for other hobby uses. The packs include operating instructions and hints on how to use the particular iron for best results.

The range comprises: A Mini Soldering Iron (WM12D) price £5.46 — a lightweight, pencil-thin, miniature soldering iron designed for hobby work (especially electronics) and household repairs, rating 12 watts; a Mini Soldering Iron Kit (WM12DK) price £7.79 — as above but including solder, tweezers and two soldering tips; a Fine Duty Soldering Iron (SI15D) priced £6.64 — ideal for the electrical repair shop or home hobbyist in audio equipment, rating 15 watts; a General Duty Soldering Iron (SI25D) price £6.46 — an all purpose iron that will deal with most household applications and yet is light and manageable enough for most intricate jobs, rating 25 watts; General Duty Soldering Iron Kit (SI25DK) price £8.32 — as above but including 1 spare soldering tip, a soldering aid tool and solder; a Medium Duty Soldering Iron (SI40D) price £7.18 — a workshop iron, recommended for jobs where a slightly higher temperature is required and where the iron is in continual use, rating 40 watts; a Heavy Duty Soldering Iron (SI75D) price £8.88 — as its name implies, this is an iron for the larger jobs such as heavy metal repairs, rating 75 watts; a Wood Burning Iron Set (WH1) price £9.50 — a specially designed tool



for wood and cork burning, leather branding and candle sculpting. It comes complete with all the necessary tips from fine to blocking and patterning, rating 25 watts; a Plastic Carving Knife (WH2) price £9.50 — a hot-knife for all types of plastics including acrylic, vinyl and expanded polystyrene, rating 25 watts; a Stained Glass Iron (WH3) price £12.75 — a simple to use iron for decorative glass work around the home, rating 75 watts.

All the prices are recommended retail prices, ex. VAT. For further information contact Cooper Tools Ltd., Sedling Rd., Wear, Washington, Tyne and Wear NE38 9BZ. Tel: 091 416 6062.

Counting Kits

Three new Velleman kits are available from the company.

The Precision Timer (K2584) has four programs which can vary from one second to ninety nine minutes and ninety nine seconds. The timer counts down to zero and activates the output, which can also be manually switched on or off. Running programs can be stopped, interrupted or continued. The unit has applications such as dark room timing, process control, light control etc. and comes with housing, transformer and sheet keyboard.

The Codelock (K2585) is a unit with two memory levels, each capable of storing twenty numbers of six digits each. The memory contains a CMOS RAM which is fed by a battery in case of power failure. All the numbers are retained even in the event of a month-long mains failure (would there still be anybody around to care after a month long mains failure?). The Codelock has

a sheet keyboard as a front panel and its applications including protection of machines, entry systems for flats and offices, and anti-burglar protection in general.

The Programmable Controller Module (K2591) is designed to control measurement of temperature, humidity acid and chlorine levels etc. It has a 24 hour clock, four programmable registers and a display for the input signal, which can be made up of an analogue voltage from 0 to 99mVDC. The module compares the input signal with the values programmed in the memory and switches on an output relay. Switching precision is 10mV to the input signal.

For full technical details and prices contact Velleman (UK) Ltd., PO Box 30, Leonards On Sea, East Sussex TN37 7NL. Tel: (0424) 753246.

Circuits To Build

Two new books of electronics circuits come from Elektor Books.

33 *Electronic Games* gives a selection of circuits which can be played once they've been built. The games don't need a TV screen, either, and are said not to be complex or to involve complicated software.


Following the same theme, 301 *Circuits* gives a selection of circuits from the very simple to more complex. It can be used as a source book for construction projects and general ideas.

The books cost £4.50 and £5.50 respectively, in paperback, and are both full illustrated with diagrams.

For more information, contact E P Publishing Ltd., East Ardsley, Wakefield, W. Yorks WF3 2JN. Tel: (0924) 823971.

New cats for old !

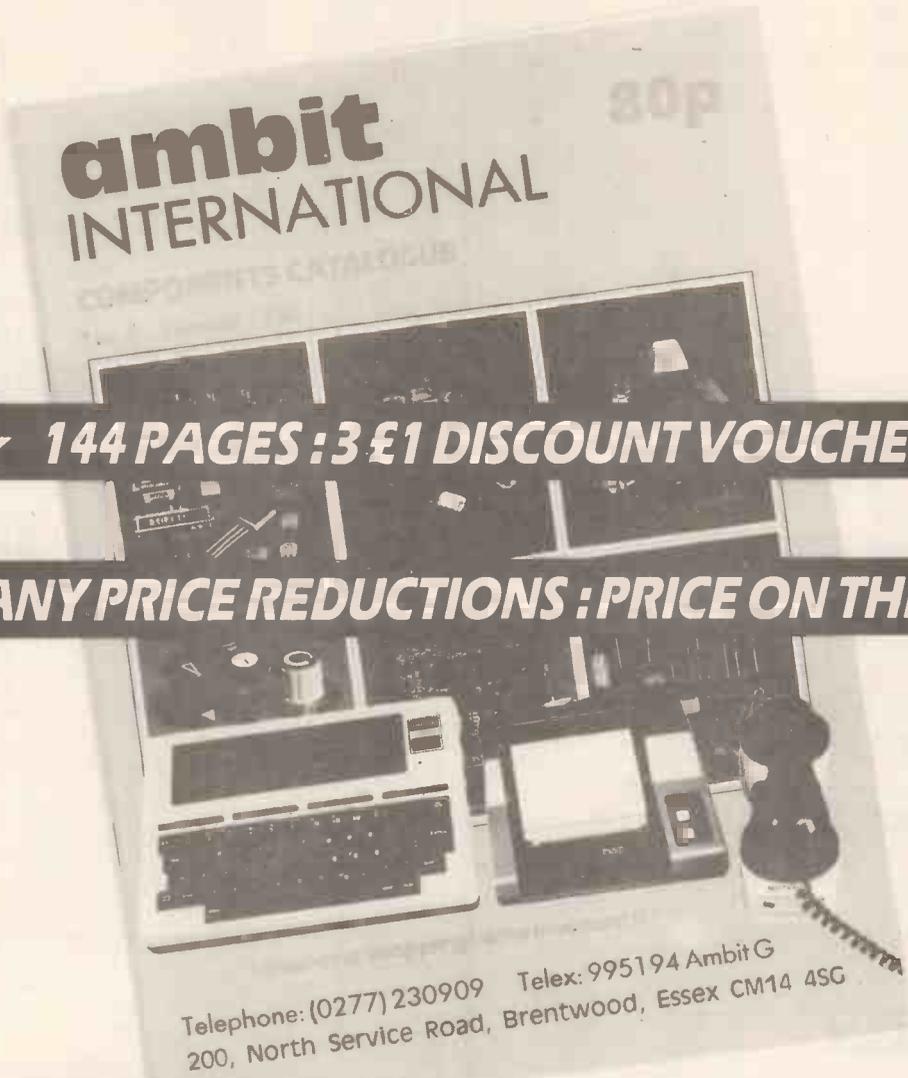SEND US THE COVER FROM ANOTHER COMPONENT SUPPLIERS CURRENT CATALOGUE, PLUS A 40p STAMP, AND WE'LL SEND YOU A FREE COPY OF THE LATEST (SUMMER) AMBIT CONCISE COMPONENT CATALOGUE. ALTERNATIVELY YOU CAN SEND 80p TO THE ADDRESS BELOW.....



ambit
INTERNATIONAL
COMPONENTS CATALOGUE

80p

Telephone: (0277) 230909 Telex: 995194 Ambit G
200, North Service Road, Brentwood, Essex CM14 4SG

★ **144 PAGES : 3 £1 DISCOUNT VOUCHERS**

★ **MANY PRICE REDUCTIONS : PRICE ON THE PAGE**

★ **DIRECT FROM**

ambit INTERNATIONAL

200 North Service Road
Brentwood
Essex
CM14 4SG

Telephone 0277-230909
Telex 995194 AMBIT G
Data 0277-232628 REWTEL »
300 BAUD DUPLEX

Para-Q

Charles Blakey



A stereo parametric amplifier that can be used with hi-fi systems, in semi-pro recording studios, for music synthesis or for any other audio signal processing application.

MOST READERS will be familiar with the graphic equaliser and its impressive array of slider potentiometers. Such a device consists of a number of frequency selective filters which allow the sound level to be boosted or cut at specific frequencies. The 'graphic' part originates from the fact that the knobs of the slider pots give a graphical display of the way its frequency response has been set up. It is intriguing to notice how such units have been set up by their users and one of the most interesting seen recently had a 'V' shape on each channel which attenuated those frequencies to which the ear responds best and so effectively reduced 'loudness': the unit was connected to a tape recorder providing background music!

While a graphic equaliser can be useful, especially if it has a large number of filters, it does have two main deficiencies. In the first place one of its objectives is to correct for


deviations from a flat audio response but nowadays even a modest hifi system will give good results, with the main deviations being caused by location of the sound system. That is, a comfortable living room will often result in absorption or boosting of certain frequencies in the sound emanating from the speakers. The usual effect is a frequency response curve displaying just two or three peaks or troughs, at least over the range 50Hz to 15kHz (the fall off outside this range is invariably due to the speakers). The first difficulty with a graphic equaliser which has relatively few bands is that the centre frequency of the filters will not correspond with one of the peaks or troughs you wish to correct. In these circumstances attempted correction may make matters worse.

The second difficulty is that the peaks and/or troughs are often very sharp, that is, the defect in the response only occurs over a fairly

narrow band of frequencies, whereas a graphic equaliser generally boosts, or cuts, a wide range of frequencies. The latter is due to the need to set the 'Q' (quality factor) of the filters so that the gain of adjacent channels overlap. Trying to eliminate a sharp peak with a wideband filter can easily result in two troughs in the frequency response — again worsening matters.

A parametric equaliser overcomes the above deficiencies since it has the capability for adjusting both the frequency and Q over a large range, as well as having the gain control. Furthermore in most situations the performance of a sophisticated graphic equaliser may be exceeded by two or three parametric equalisers per channel and even the stereo unit described in this article will yield very useful results.

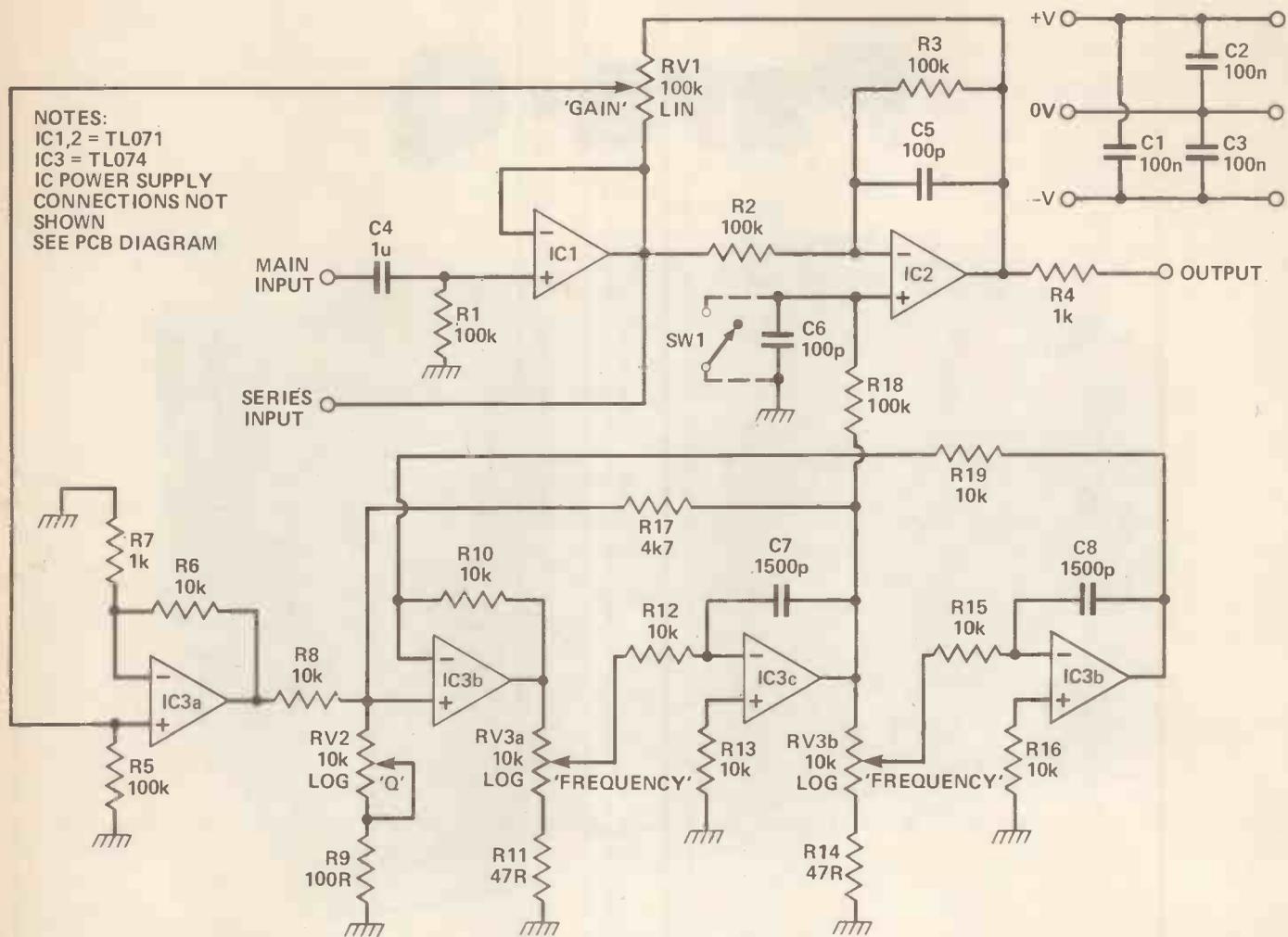The parametric equaliser described is a high performance unit suitable for use with even the most exotic hifi system. The prototype had a boost and



NOTES:
 IC1,2 = TL071
 IC3 = TL074
 IC POWER SUPPLY
 CONNECTIONS NOT
 SHOWN
 SEE PCB DIAGRAM

Figure 1. The circuit shown above is for one channel of the stereo pair. Switch SW1 is an optional bypass for the channel; several other modifications which alter the characteristics of the equaliser are described in the text.

cut range from zero to just over $\pm 20\text{dB}$; a Q variable from 1 to 25; and a frequency range of 50Hz to 11kHz. The Gain and Q measurements were made at 1kHz but uniformity of response is good over the full frequency range. The latter range is ideal for most audio applications since one rarely wishes to treat frequencies below 50Hz, and a 11kHz top level reduces the risk of damaging tweeters if the equaliser is set to a high boost at high frequencies (unless it is correcting for a trough in the response). The frequency range may, however, be easily altered as described later.

A high gain, high-Q parametric equaliser is particularly useful for 'correcting' recordings and the most common alterations are boosting frequencies deficient in the original and cutting out an unwanted frequency, eg a noise originating from one of the instruments.

Such equalisers are also ideal for electronic music applications. Firstly, for imitative synthesis it may be used as a so-called formant filter; that is, to boost a band, or bands, of frequencies which are characteristic of the

instrument being simulated. These equalisers are now often used as an effects unit since the tone changes they can introduce are quite dramatic, especially at high gain levels.

Circuit

The complete circuit diagram for one channel of the parametric equaliser is shown in Figure 1. The key feature of the equaliser is a band pass filter which is constructed around ICs 3a, 3b and 3c, arranged in what is known as a 'state variable' configuration. The band pass output is available at the output of IC3c and the centre frequency of the filter is governed by the integrating capacitors C7 and C8, plus the resistance provided by the ganged potentiometer RV3. With 1n5 capacitors the frequency range is 50Hz to 11kHz and this range may be altered by changing both C7 and C8. For example, if they are substituted by 1n the frequency range would be 75Hz to 16.5kHz, while 2n capacitors would give a range of 35Hz to 7.5kHz.

Reverting to the input stage, the main input is AC coupled to IC1,

which is simply a buffer stage primarily to provide a low impedance to the gain control, RV1; R1 sets the input impedance of the circuit. The signal then passes to the output via the unity gain amplifier IC2 and, if switch SW1 is closed so as to ground the non-inverting input of IC2, the filter section will not have any effect.

The input to the filter is via RV1, one end of which is connected to the original non-inverted signal at the output of IC1 while the other end of the potentiometer connects to the inverted signal at the output of IC2. The signal input to the band pass filter comes from the wiper of RV1 while RV3 determines which frequency components are passed by the filter and fed back into the non-inverting input of IC2. Thus if the wiper of RV1 is closer to the output of IC1 (the original signal) more of the selected frequency band of the original signal becomes added (boosted) onto the original signal at IC2. Likewise when RV1 wiper is close to the output of IC2 the effect will be to subtract (cut) the original signal in IC2. The effect is the same as a conventional graphics equaliser

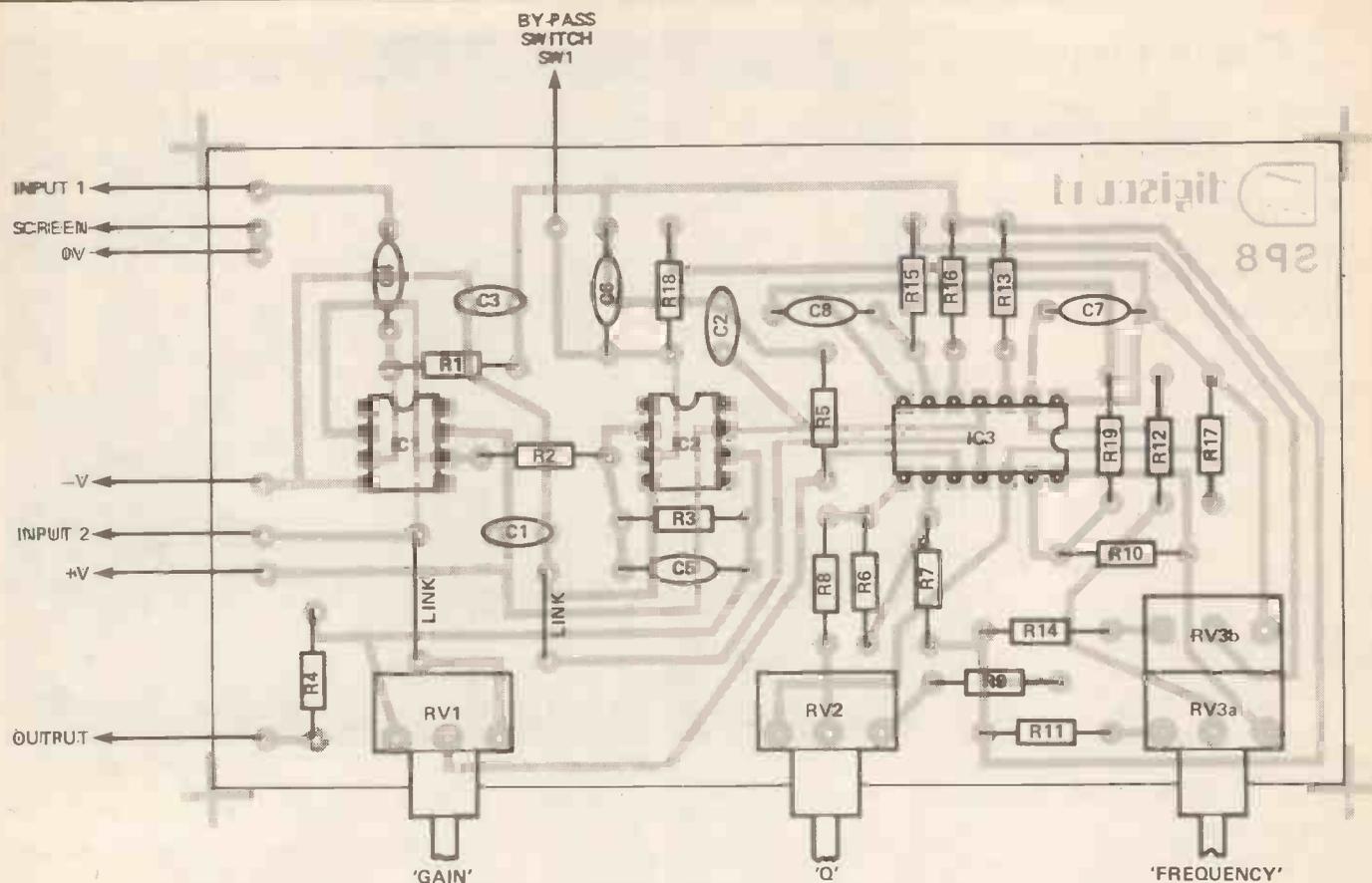


Figure 2. The printed circuit board accommodates the components for a single channel of equalisation. Two boards are required for the full stereo facility (see internal picture, next page) or any number can be connected in series using the series input (labelled input 2 in the diagram above).

but the ability to adjust the frequency over the full range is a major advantage. Typical outputs with boost and cut are shown in Figure 3.

The other feature that has to be incorporated into a parametric equaliser is a variable Q; the higher the Q the more peaked the response from the filter. Increasing Q is obtained by increasing the amount of feedback and one of the main reasons for choosing a state variable filter is to obtain a high Q without causing the filter to oscillate. In the absence of RV2/R the Q of the circuit would be determined by the ratio of R8 and R17 but altering these resistors would also alter the gain of the circuit unless the design is altered and dual potentiometers are incorporated to alter both resistor values. This problem is overcome by increasing the gain prior to R8 and then varying Q by attenuating the feedback signal using RV2.

Construction

All components, including the potentiometers, are mounted onto a printed circuit board and the component overlay is shown in Figure 2. The latter makes assembly about as simple as one can get for such a project, but there are several options available to the user which are discussed below.

Power Supplies. The parametric equaliser requires dual power supplies and these can be anything from $\pm 9V$ to $\pm 15V$. At $\pm 15V$ the power consumption is about 12mA per rail per unit, and so the project would be suitable for battery operation. In the latter event a power switch should be fitted to conserve battery power when not in use and one should also put a reservoir capacitor, say 47 μF , across the supply lines. For a single, or stereo unit, an alternative is to pick up dual supplies from some other equipment. Lastly, one could incorporate a mains derived supply into the case but if this option is used then carefully check the siting of the transformer before finalising the lay-out since filters may pick up and amplify the 'hum' being radiated from the transformer.

By-Pass Switch. A single pole, single throw switch may be connected from the points in Figure 2 marked 'by-pass switch, SW1' and 'OV'. When the switch is closed the non-inverting input of IC2 is grounded and the original signal will pass through the equaliser unaffected by the settings of any potentiometers. This facility may be useful when using the unit in a hifi chain, since the effect of the settings may then be rapidly checked by switching SW1. The by-pass arrangement is also useful when the parametric

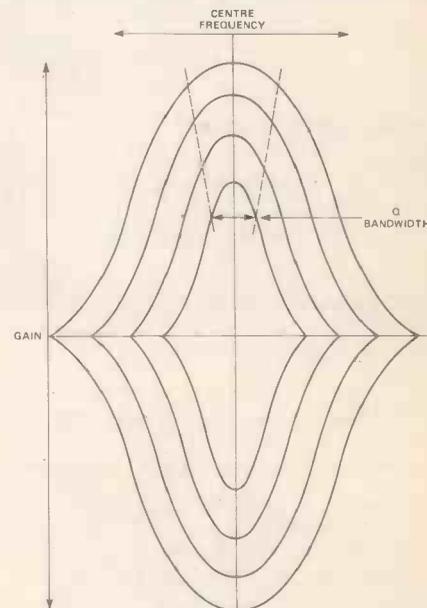


Figure 3. This graph shows a few of the infinite variety of response curves that the Para-Q can generate. There are three variables: the centre frequency can be positioned anywhere between 50Hz and 11kHz; the gain at that frequency can be varied by $\pm 20dB$; and the Q or bandwidth of frequencies effected can range from 1 to 25, giving boost or cut over a very narrow range or over a wide band of frequencies.

Parts List

Although a stereo parametric equaliser is illustrated, the reader may wish to use only one unit as an effects unit, or several for a hifi system. In view of this we show the basic set of components for a single unit and the choice of connectors and control knobs is left to the constructor.

RESISTORS

¼ watt, 5% carbon film

R1, 2, 3, 5, 18	100k
R4, 7	1k0
R6, 8, 10, 12, 13, 15, 16, 19	10k
R9	100R
R11, 14	47R
R17	4k7

POTENTIOMETERS

RV1	100k 1in carbon, PCB mount
RV2	10k log carbon, PCB mount
RV3	10k+10k dual log carbon, PCB mount

CAPACITORS

C1, 2, 3	100n min polyester
C4	1u0 MkH polyester
C5, 6	100p polystyrene
C7, 8	1n5 polycarbonate

SEMICONDUCTORS

IC1, 2	TL 071 JFET low noise op-amp
IC3	TL 074 JFET low noise quad op-amp


MISCELLANEOUS

8-pin DIL sockets (2); 14-pin DIL socket; PCB, wire, solder, etc.

BUYLINESpage 34

equaliser is used as an effects unit for music. One switch may be used for several equalisers housed within the same case or the user may use a switch for each unit so that the effect of single units may be rapidly checked.

Number of Equalisers and Connecting Up. If a single equaliser is used in each signal path then the channel input connects to the point on Figure 2 marked 'Main Input'; screened cable is preferred, with the screen going to the point marked 'screen' on the PCB overlay. The input socket(s) may be of any type to suit the user, for example, phono sockets, DIN socket, or jack sockets. The output is of low impedance and need not

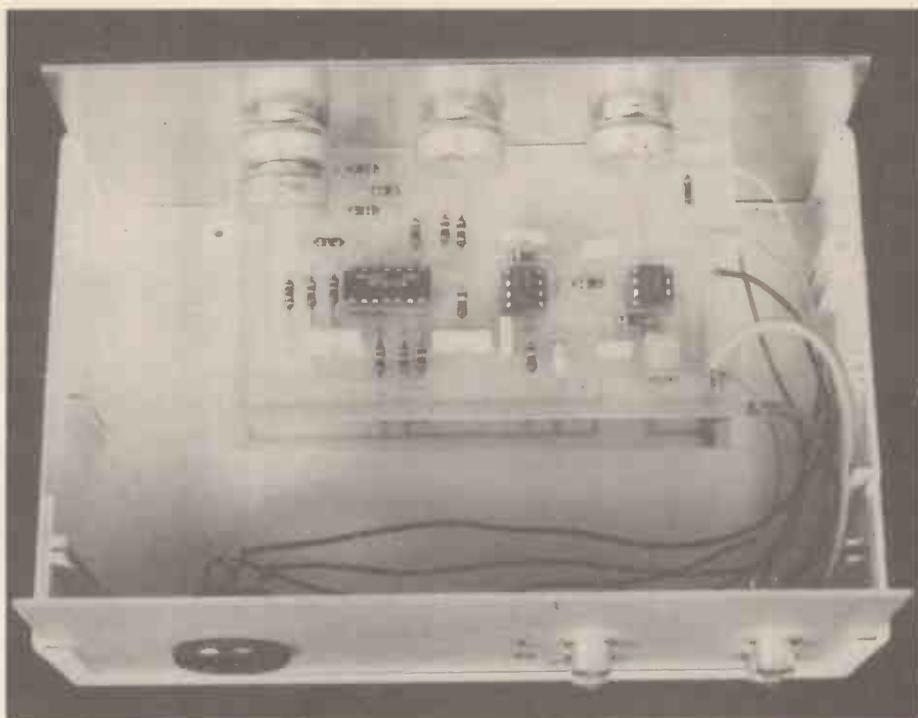

be screened within the housing of the equaliser, ie from the point marked 'output' on the overlay to the output socket.

As already mentioned, three parametric equalisers will usually be more effective in a hifi system than a ten, or more, channel graphic equaliser. If more than one unit is connected up per channel then they are connected in series. The signal to the first unit connects with 'Main Input', as described above, but the 'output' of unit 1 goes to the 'Series Input' of unit 2 ('output' of unit 2 to 'series input' of unit 3 and so on) and the 'output' from the last unit goes to the output socket of the particular channel. The second and following units do not require components IC1, C4 and R1 and if the latter have already been installed then the unit will not work until IC1 has been removed from these additional equalisers.

When several equalisers are employed then the most convenient method of housing them will be with the PCBs arranged vertically. The distance between PCBs should be 33mm or greater and, for information, the distance between potentiometer centres is 38mm.

In Use

With the gain control in the mid position, or the by-pass point connected to ground, the parametric equaliser has unity gain, that is, the level of the signal out is the same as the level of the signal in. The input signal should, therefore, be pre-amplified and with many audio amplifiers the monitor output is the appropriate point to use. Alternatively, when the equaliser is used for tape/cassette recording it may be installed in the signal line to the recorder.

Table 1

Power Supply	Max Signal Input
±9V	400mV
±12V	530mV
±15V	700mV


The signal level which can be used is partly governed by the power supply and partly by application. For hifi and many recording situations, the cut and boost control is only set to a level which will compensate for deficiencies in frequency response so as to ensure a nominally flat response. In these circumstances the unit will cope with signal levels likely to be encountered in such systems irrespective of the power supply used. If, however, the equaliser is used for special effects and gain is set at either extreme then the maximum signal levels shown in Table 1 are recommended in order to avoid clipping:

As regards setting of the controls, without having access to audio analysing equipment, you will have to start off by using an equaliser channel in much the same way as you use tone controls at present, that is, adjusting them by ear. Start with the Q control at, or near, minimum and then adjust gain gradually either way from the centre position and then slowly rotate the frequency control clockwise. You will be amazed by the results and will soon learn the best settings for your system. Note that when Q is increased the effect of the gain control is generally less marked since the band of frequencies being boosted or cut is much narrower and therefore not so noticeable to the ear unless it is centred on some constant frequency in the sound.

PREVIOUSLY ADVERTISED STILL AVAILABLE

Tape punch and reader	£22.50
Bench isolating transformer 250 watt	£7.75
BOAC in-flight stereo unit	£1.50
Drill assortment 4 each 25 sizes between .25mm & 2.5mm	£11.50
Flood lamp waterproof GEC	£9.90
Battery condition tester, less box	£1.75
Nicad chargers, mains	£0.75
Fluorescent inventor 13 watt from 12v	£3.50
Cassette mechanism with heads	£4.50
Ten digit stitch pad-pb phone etc.	£1.95
Uniselector 2 pole 25 way	£4.60
Water valve mains operated	£2.50
Counter 6 digit mains operated	£1.15
ditto 12v resettable	£3.45
Double glazing clear PVC sheet, 23 1/2" wide-per running ft.	£0.15
Locking mechanism with 2 keys	£1.15
Magnetic Clutch	£4.50
Mouth operated suck or blow switch	£2.30
Fire alarm break glass switch	£3.75
Solenoid with slug 8-12v battery op	£1.82
ditto 230v mains	£2.30
Timer Omron STP NH 110v AC Coil	£6.90
Key switch with 2 keys dp mains	£1.75
Air valve mains operated	£3.75
Latching relay mains operated	£3.50
Dry film lubricant aerosol can	£0.65
Coin op switch, cased with coin tray	£4.60
Auto transformer 1000 watts (plus postage for transformer)	£19.50 £3.00

3 CHANNEL SOUND TO LIGHT KIT

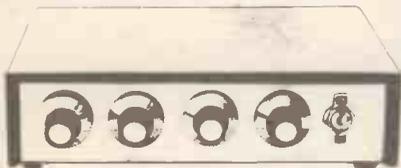

Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/2" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form or £25.00 assembled and tested.

12 volt MOTOR BY SMITHS

Made for use in cars, etc. these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3" dia. They have a good length of 1/2" spindle - Price £3.45. Ditto, but double ended £4.25. Ditto, but permanent magnet £3.75.



EXTRA POWERFUL 12v MOTOR

Made to work battery lawnmower, this probably develops up to 1/2 h.p., so it could be used to power a go-kart or to drive a compressor, etc. etc. £7.95 + £1.50 post. (This is easily reversible with our reversing switch - Price £1.15).

THERMOSTAT ASSORTMENT

10 different thermostats. 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses; appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 - 100°C. There is also a thermostatic pod which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 - however, you can have the parcel for £2.50.

CROSSOVER NETWORKS

2-way: 4 or 8 ohm impedance - power input up to 25W, crossover frequency 2kHz with wiring dig. 87p each.
3-way: 4 or 8 ohm - power input up to 60W, crossovers at 700kHz and 3500Hz with wiring diagram. £1.15.

- BARGAIN OF THE YEAR -

The AMSTRAD Stereo Tuner.

This ready assembled unit is the ideal tuner for a music centre or an amplifier, it can also be quickly made into a personal stereo radio - easy to carry about and which will give you superb reception.

Other uses are as a "get you to sleep radio", you could even take it with you to use in the lounge when the rest of the family want to view programmes in which you are not interested. You can listen to some music instead.

Some of the features are: long wave band 115 - 270 KHz, medium wave band 525 - 1650KHz, FM band 87 - 108MHz, mono, stereo & AFC switchable, tuning meter to give you spot on stereo tuning, optional LED wave band indicator, fully assembled and fully aligned. Full wiring up data showing you how to connect to amplifier or headphones and details of suitable FM aerial (note ferrite rod aerial is included for medium and long wave bands. All made up on very compact board.

Offered at a fraction of its cost: **only £6.00** + £1.50 post + insurance.

THIS MONTH'S SNIP

MULTI PURPOSE BINS

10 interlocking bins can be wall or bench mounted, each size approx 109x53x100mm, high impact plastic. Come complete with 2 wall mounting bars. Snip price £3.95 + £1.50 post.



REVERSIBLE MOTOR WITH CONTROL GEAR

Made by the famous Framco Company this is a very robust motor, size approximately 7 1/2" long, 3 1/4" dia. 3/8" shaft. Tremendously powerful motor, almost impossible to stop. Ideal for operating stage curtains, sliding doors, ventilators etc., even garage doors if adequately counter balanced. We offer the motor complete with control gear as follows:

1 Framco motor with gear box 1 push to start switch
1 manual reversing & on/off switch 2 limit stop switches
£19.50 plus postage £2.50 1 circuit diag. of connections

FREE OUR CURRENT BARGAIN LIST WILL BE ENCLOSED WITH ALL ORDERS.

ROTARY WAFFER SWITCHES

5 amp silver plated contacts. 1/2" shaft. 1" dia. wafer.

Single wafer types, 29p each, as follows:
1 pole 12 way 2 pole 6 way 3 pole 4 way
4 pole 3 way 6 pole 2 way 4 pole 3 way
Two wafer types, 59p each, as follows:
2 pole 12 way 4 pole 5 way 4 pole 6 way
6 pole 2 way 8 pole 3 way 12 pole 2 way
Three wafer types, 99p each:
9 pole 4 way 6 pole 5 way 6 pole 6 way
12 pole 3 way 18 pole 2 way

STOP PRESS! CASSETTE MECHANISM - Front loading with heads. Brand new: £6.95

A PRESTEL UNIT, brand new and complete except for 7 plug in ICs - so far as we know the unit would work once the missing ICs are fitted. Price: £19.75 + £2.00 post.



WATERPROOF HEATING

WIRE 60 ohms per yard, this is a heating element wound on a fibre glass coil and then covered with PVC. Dozens of uses - around water pipes, under grow boxes, in gloves and socks.

TIME SWITCH BARGAIN

Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs FOR ONLY £2.50.

ROPE LIGHT

4 sets of coloured lamps in translucent plastic tube arranged to give the appearance of a running or travelling light. With variable speed control box, ideal for disco or shop window display. Complete, made up, ready to plug into mains. £36.00 + £2 post.

50 THINGS YOU CAN MAKE

Things you can make include Multi range meter, Low ohms tester, A.C. amps meter, Alarm clock, Soldering iron minder, Two way telephone, Memory jogger, Live line tester, Continuity checker, etc. etc. and you will still have hundreds of parts for future projects. Our 10Kg parcel contains not less than 1,000 items - panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermostats, coils, condensers, resistors, neons, earphone/microphones, nicad charger, power unit, multi-turn pots and notes on the 50 projects.

YOURS FOR ONLY £11.50 plus £3.00 post.

MINI-MULTI TESTER Deluxe pocket size precision moving coil instrument, Jewelled bearings - 2000 o.p.v. mirrored scale.

11 instant range measures: DC volts 10, 50, 250, 1000. AC volts 10, 50, 250, 1000. DC amps 0 - 100 mA.



Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test leads and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 60p post and insurance.

FREE Amps range kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

J. BULL (Electrical) Ltd.

(Dept. HE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. Established 30 YEARS

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £12 add 60p service charge. Monthly account orders accepted from schools and public companies. Access & B/card orders accepted day or night. Haywards Heath (0444) 454563. Bulk orders: write for quote. Shop open 9.00 - 5.30, mon to Fri, not Saturday.

EXTRACTOR FANS

Mains operated - ex-computer.

Woods extractor
5" - £5.75, Post £1.25
6" - £6.95, Post £1.25
5" Planair extractor
£6.50, Post £1.25.
4" x 4" Muffin 115v.
£4.50, Post 75p.
4" x 4" Muffin 230v.
£5.75, Post 75p.
9" American made
£11.50, Post £2.00.
Tangential Blower 10x3
air outlet, dual speed
£4.60, Post £1.50.



TANGENTIAL BLOW HEATER

by British Solartron, as used in best blow heaters.

2Kw approx 9" wide £5.95,
3Kw either 9" or 12" wide
(your choice) £6.95 complete with 'cold' 'half' and 'full' heat switch, safety cut out and connection dig. Please add post £1.50 for 1 or £2.30 for two.



2.5 Kw KIT still available: £4.95 + £1.50 post.

SPIT MOTORS



These are powerful mains operated induction motors with gear box attached. The final shaft is a 1/2" rod with square hole, so you have alternative coupling methods - final speed is approx. 5 revs/min, price £5.50. Similar motors with final speeds of 80, 100, 160 & 200 r.p.m. same price.

COMPONENT BOARD Ref. WO998

This is a modern fibreglass board which contains a multitude of very useful parts, most important of which are: 35 assorted diodes and rectifiers including 4 3amp 400v types (made up in a bridge) 8 transistors type BC 107 and 2 type BFY 51 electrolytic condensers, SCR ref 2N 5062, 25 Out 100v DC and 100uf 25v DC and over 100 other parts including variable, fixed and wire wound resistors, electrolytic and other condensers. Two for £4.50.



VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case but we can supply a plastic case - £1.75. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder - a complete mains operated kit, case included.

£11.95 plus £2.00 post.

OTHER POPULAR PROJECTS

R C Bridge Kit	£9.95
3 Channel Sound to Light - with fully prepared metal case.	£14.95
Ditto - made up	£25.00
Big Ear, listen through walls	£9.50
Robot controller - receiver/transmitter	£9.50
Ignition kit - helps starting, saves petrol, improves performance	£13.95
Silent sentinel Ultra Sonic Transmitter and receiver	£9.50
Car Light 'left on' alarm	£3.50
Secret switch - fools friends and enemies alike	£1.95
3 - 30v Variable Power Supply	£13.80
2 Short & Medium wave Crystal Radio	£3.99
3v to 16v Mains Power Supply Kit	£1.95
Light Chaser - three modes	£17.50
Mullard Uniflex HiFi stereo amplifier with speakers	£16.75
Radio stethoscope - fault finding aid	£4.80
Mug stop - emits piercing squawk	£2.50
Morse Trainer - complete with key	£2.99
Drill control kit	£3.95
Drill control kit - made up	£6.95
Interrupted beam kit	£2.50
Transmitter surveillance kit	£2.30
Radio Mike	£6.90
FM receiver kit - for surveillance or normal FM	£3.50
Seat Belt reminder	£3.00
Car Starter Charger Kit	£14.00
Soil heater for plants and seeds	£16.50
Insulation Tester - electronic megger	£7.95
Battery shaver or fluorescent from 12v	£6.90
Matchbox Radio - receives Medium Wave	£2.95
Mixer Pre-amp - disco special with case	£16.00
Aerial Rotator - r.a.ins operated	£29.50
Aerial direction indicator	£5.50
40 watt amp - hi-fi 20hz - 20kHz	£9.50
Microvolt multiplier - measure very low currents with ordinary multimeter	£3.95
Pure Sine Wave Generator	£5.75
Line Power output meter	£11.50
115 Watt Amplifier 5Hz 25kHz	£13.50
Power supply for one or two 115 watt amps	£17.50
Stereo Bass Booster, most items	£8.95

COMING SOON TO . . .

Hobby Electronics

ALL-PURPOSE LIGHT METER

Not just a light meter. The range of this meter allows it to be used for measuring visible and UV light radiation from any light source including sunray lamps and other sources where light levels may be a matter of safety as well as efficiency.

DAMP METER

Whether you are deciding if the time is right to plaster, checking a prospective house purchase for leaks or rising damp, trying to locate a defect in your plumbing or — possibly — just deciding whether to go out for a walk, you won't be short of uses for the HE Damp Meter if you are the active sort. And you are, aren't you?

HE BASSMAN

Too many vocalists and not enough musicians? This synthesiser project will enable you to transform a spare voice into a very convincing approximation of a bass guitar.

CIRCUIT CONTINUITY TESTER

Another essential piece of bench test equipment, easy to build and easy to use.

CAREERS IN ELECTRONICS

HE's popular careers series looks at the training and career opportunities offered by the UK Armed Services.

Please reserve me copies of the December issue

**Hobby
Electronics**

for
Name

Address

.....

.....



**Hobby
Electronics**

**December issue on sale at
your newsagent
from 11th November.
Place your order now!**

Although these articles are being prepared for the next issue, circumstances may alter the final content.

Special Offer Special Offer Special Offer Special Offer

Fantastic In-Car Entertainment Offer for Hobby Electronics readers.

Your choice from two Hitachi Auto Reverse Stereo Cassette players* with LW/MW/FM stereo radio – at LESS THAN TRADE PRICE!

Hitachi CSK413D

Stereo radio/cassette combination with Dolby** Noise Reduction ...

- ★ Three band radio with six preset tuning buttons and LED stereo.
- ★ Phase Locked Loop circuitry with FM noise canceller.
- ★ High performance cassette deck with Dolby NR, metal tape equalisation.
- ★ Auto reverse, lock-on fast forward/rewind and LED tape run indicator.
- ★ Tone and stereo balance controls with fader control for four-speaker operation.
- ★ Automatic motorised aerial drive.
- ★ Built in power amplifier – 15 + 15 watts into two 4 ohm loudspeakers.
- ★ Radio frequency response 30Hz to 15kHz, tape response 50Hz to 15kHz.



Recommended Retail Price ... £176
Price to Hobby Electronics readers only ... £115.00, including VAT.

Hitachi CSK333

Auto Reverse Stereo Cassette player with three band radio ... unbeatable value at our very special price.

- ★ LW/MW/FM radio with six preset tuning buttons.
- ★ Exceptional sound quality from both radio and cassette player.
- ★ LED stereo tuning indicator and stereo/mono select button.
- ★ Tape track selector with in-built track direction indication.
- ★ Frequency response 50Hz to 14kHz, signal to noise ratio better than 50db, audio output 6 watts RMS per channel into 4 ohm speakers.



Recommended Retail Price ... £149
Special offer price ... £79.95, including VAT.

'Perfect' Slim-Line Loudspeakers

The perfect complement to either of the cassette/radio combinations on offer, these 5 1/2", 4 ohm full range speakers will handle a maximum of 20 watts.

Special price ... £9.50, including VAT.

*For 12v negative ground systems only.
 **Dolby is the trademark of Dolby Laboratories.

Please send me

- Hitachi CSK413D Stereo radio/cassette. £.....
- Hitachi CSK333 Stereo radio/cassette. £.....
- One pair of Perfect Loudspeakers. £.....
- Packaging & Postage £ 2.50
- I enclose my cheque/postal order/money order for (total) made payable to ASP Ltd. £.....
 (delete as necessary)

OR Debit my Access/Barclaycard (delete as necessary)



--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--



Name
 Address
 Signature

SEND TO:
 Hobby Electronics,
 ICE Offer,
 145 Charing Cross Road,
 London WC2H 0EE.

POINTS OF VIEW

Feel like sounding off?

Then write to the Editor stating your Point of View!

Power To The Housepersons!

Dear HE,

Good try for printing articles on the human side of electronics, but your writer John Biggin (*Power In The House*, HE June '83) presented an overoptimistic and one sided view of the impact of electricity in the home.

This is the other side.

1) Statistics show that women are spending as many hours as their mothers did on housework.

2) Phrases like 'working housewives' suggest that the tasks done in the home are not work. Homemaking is work - not to mention the job of bringing up children, which is done in the home and which can't be made automatic or mass produced.

3) Far from liberating women, the signs are that women are losing status in society because what is done in the home is under-valued. Don't forget, before the industrial revolution everyone worked at home and running that home was an important job.

I think it is a good thing that magazines like HE print articles about the impact of technology because people, men and women, could do with giving it a bit more thought. By the way, there are a number of women electronic hobbyists, including myself, who would prefer not to be referred to as 'The Ladies' - I have enough trouble with shop assistants talking to my husband about components I am buying!
Hilary Pegg,
Roundhay,
Leeds.

At last! One of our wimmin readers (apart from the One who filled in her Reader Survey in 1982) comes out of the woodwork. Your comments are much appreciated, and I don't think we can blame John Biggin for any bias in his article, as the idea that electrical gadgets don't actually save any time seems to be a fairly new one (and, I think, a mistaken one, but I'll come back to that).

Actually, the reference in the intro to 'The Ladies' was intended to draw to the attention of The Gents that this article was not directly relevant *only* to persons of the non-masculine gender (but I couldn't get that onto one line). Now some brief flurries of response:

1) Women may be spending as much time on housework as their mothers did, but I bet they don't spend as much time as their grannies (or their grannies' housekeepers) did.

After that, Parkinson's Law comes into operation. I have heard tell that some ladies (and probably gents as well) clean the grouting between their bathroom tiles with old toothbrushes, and iron their teatowels. Well, it's a free country.

2) Couldn't agree more about 'working housewife' - it reflects the attitude which accepts that a woman with a job must still have housework as her main occupation. The mass of men who also do a full-time job and cook and Hoover in the evenings don't get called 'working househusbands' do they?

3) Yes, but housework has always been undervalued because men have always tended to hold the reins of the Media and therefore (a normal human trait) have given their rôles the best press. Women, for instance, have tended to do the budgeting in every age and clime, but get precious little credit (no pun intended . . .) for it. However, the people who have denigrated the rôle of the housewife in these latter days have frequently been other women who have taken the selfrighteous attitude that people who don't have 'careers' are inferior. Women have more control over the media these days, and some of them glamorize their rôles at the expense of others.

There has always been talk about how technology has not made our lives any happier - as a medieval historian my only reply to this is (*language - Ed.*) The choice everyone has now about what to do with their time is an extraordinary gift which it is up to us to handle. True, it can make life very complicated, and it's more fun if you're wealthy and have an interesting job, but everyone has benefitted to some extent and nobody actually *has* to iron their teatowels, or wash their cars every Sunday. Let's enjoy it while we've got it!

OK, back to your workbenches, the lot of you, heads down and get soldering. And next time a shop assistant addresses your husband/dad/larger friend about your purchases, have them trained to say "I haven't a clue - ask the one who's doing the work."

But Can You Bend The Strings?

Dear Sir,

Many of us musicians have quite good pianos which were built say thirty or

so years ago, which can go on playing for a good many more years, they were built so well, but they do lack the tone and sound of a Steinway. I am sure other musicians will agree with me when I say that there is really nothing to compare with the feeling of playing the piano, as against that of an electronic one, especially as it applies to players who were taught from an early age to play piano. I have tried several electronic pianos, but there is not the same feeling in playing.

Discussing this with some musician friends, it was decided to carry out a small experiment, by placing a stereo mic in the bottom of one of our pianos, then running a lead to a hifi amplifier, which was connected to six hifi loudspeakers, 70 watt each channel, we were all agreeably impressed with the overall improvement, bearing in mind we had overcome our aversion to the feel or key response, which is inherent in electronic pianos.

All had the idea that it would be best to have the mic, amplifier and speaker incorporated in the piano, or else in a combo alongside, so that the player would immediately hear what was being played, the piano's normal acoustics being audible, but on the combo there would be controls to alter or adjust the electronic sound, or switch them off altogether.

We also agreed, that it would be best to put the whole project to some electronic wizards, who undoubtedly would be in a better position to advise the type of components to use, that would ensure the best results that could be achieved.

We would be very pleased to hear from you if you would consider taking up this challenging project, which I am sure would be of considerable interest to thousands of piano owners.

Yours truly,
R H Briggs,
Ringwood,
Hants.

We racked our brains for seconds to think of an answer to this one, and at last we found the elusive clue. About two decades ago (well, nearly) famous guitar person Dave Davies of The Kinks appeared on BBC TV playing a guitar which was adorned with the words: "THIS IS A PIANO". Naturally, at the time, we thought that he had overestimated our gullibility, but now we see that this was a time-encapsulated message planted to aid musicians who already

had pianos and would one day wish to bring them under the aegis of electricity.

To put it briefly, what you are looking for is a guitar amplifier. Consult your nearest electric guitar dealer, and when he has recovered from the idea that you want the amp for a piano, he will probably be able to advise you. The age of the Guitar Hero is over, and the age of the Piano Hero has dawned! You may even find you can play it with your teeth . . .

Airmail Abroad

Dear Sir,

I am interested in obtaining some of your projects for construction and back numbers of your magazine.

However, while you give the costs and postage, I feel sure that this does not cover postage to South Africa. May I suggest that you adopt the method used by the British Philatelic Bureau whereby they give postage rates to about three world zones. This would assist greatly in ensuring no delay of delivery to us. I have been receiving your magazine for a few years now, and am very pleased that you include a number of articles that start from the basics. This in fact is the main attraction of your magazine to me.

Yours faithfully,
R. B. Macgillivray,
Marshalltown,
South Africa.

I have consulted with our subscription department, and the reason that we don't quote in postal zones is quite simply that postal charges rise too frequently, and it is annoying and expensive for both us and our customers if they send enough money to cover an obsolete postal rate and we have to ask them for more — there are currency charges on each separate transaction, for example.

Our Backnumbers price of £1.50 a copy provides a basic postal charge for inland or surface mail to anywhere in the world. It also includes packing and handling charges. Airmail postage is very much more expensive.

However, extrapolating from our overseas air mail subscription rates, I would say that if you were to enclose an extra £1.00 per copy ordered and ask for air mail delivery, you would not be denied. This only makes sense for readers outside Europe, as the extra speed gained within the European postal area just ain't worth the extra cash.

More Rodents

Dear HE,
Please would you send me information on the Micromouse

Association? I am writing to you as you made some mention of a micromouse at the beginning of your Hebot II article in HE November '82.

I would be extremely grateful if you would oblige. I am designing one for my electronics project, at A level.

Yours sincerely,
Roy Freeman,
Welbeck College,
Workshop.

Unfortunately, we lost contact with the micromouse species in about 1939. The people most likely to know are the **Computer Users' Club**, c/o **Tony Latham, 72 Sidmouth Rd., Willing, Kent DA16 1DS.**

Missed The Program

Dear Sir,

I am writing in connection with the ZX81 HRG article which appeared in your July edition.

After a careful study of the entire magazine I cannot find the program 4 listing, referred to in the text. As I intend constructing the project I would be most grateful if you could supply me with the omitted program. Unfortunately I will be out of the country for the next couple of months, so I will miss the August issue, should it appear there.

Many thanks in anticipation.
Yours,
I. Jauncey,
Weston Favell,
Northampton.

The references to Program 4 were supposed to have been deleted from the text when we dropped the listing because of space limitations. Unfortunately we cannot supply the listing now (because of time limitations — I hope Einstein isn't listening) but if you want the listing (and it's only an example) you can send Cambridge Computing £4.50 at the address in the July issue and they will supply a cassette containing all four programs, which will save you the trouble of typing them in.

Miss the August issue? MISS THE AUGUST ISSUE??? Haven't you heard of the Hobby Electronics Backnumbers service?? What is the world coming to?

Prestel Kits

Dear Sirs,

With regard to the letter from C. V. Parker in HE June '83 enquiring about Teletext/Prestel kits. The following company supplies two teletext kits, the MK I at £170.20 inc. VAT and the MK II at £227.70 inc. VAT. P&P is extra: **Manor Supplies, 172 West End Lane, London NW6. Tel: 01 794 8751/7346. I hope this will be of some help.**

Yours,
R. J. Ford,
Croydon,
Surrey.

Theory And Practice

Dear Ed.,

Perhaps you could provide me with some information concerning your projects section.

Even though I have good theoretical knowledge by passing the ONC test the only practical work I have done has been on operating simple circuits on breadboards.

This is a common problem facing college leavers who are then refused employment due to unfamiliarity with PCB techniques and development.

A feature in HE August '82 called "Beginners Guide To Construction" was quite informative.

As I now wish to start constructing circuits, similar to those in HE but at a lower starting-off level, how should I go about it? Where can I find these practical circuits?

Having been a student until recently I do have a fairly small budget but what are the essential items that I should purchase to begin with? (eg PCBs, soldering iron, meters, testing equipment, crocodile clips, power supply etc., the list seems endless!)

Any advice that you would offer would be much appreciated.

Yours faithfully,
David O'Donnell,
S. Tottenham,
London.

This sort of problem faces school and college leavers at all levels, including graduates, and as you are showing good sense in trying to get round it by your own efforts. As you may have gathered from reading the Careers In Electronics series, employers look for practical ability as well as theoretical ability, and evidence of a personal interest in practical things can make the difference between getting a good job and not getting it.

Projects: get Hobby Electronics regularly. We run projects at all sorts of levels, most of them within the scope of a virtual beginner, and quite a few of our projects can be built from kits (or at least with a PCB Service circuit board) which takes some of the sweat out of the early stages of learning.

More projects: readers may have noticed our symbiotic relationship with **Bernard Babani (publishers) Ltd., of The Grampians, Shepherds Bush Rd., London W6 7NF**, who will send you a catalogue if you write and ask. This is because Babani publish a large number of small, inexpensive volumes of projects and on specific subjects, many of which are ideal for beginners, and require only a small investment. Some of these are on offer through our regular HE Bookshelf Service, for people who don't want to go to the trouble of getting in a catalogue.

Equipment: the most basic equipment will comprise a soldering iron, a small multimeter, a small pair of fine, long-nosed wiring pliers, a small, sharp pair of wire cutters, a small screwdriver (for casings, especially), and a sharp modeller's

Points Of View

knife for wire-stripping, track cutting etc.

Choose a soldering iron with a fairly fine tip, and which is compact enough to be wieldy in a small space. For a multimeter, choose one with 20 kilohms per volt and as many ranges as possible. A cheap, useful meter should cost about £20; the cost of irons varies. You will eventually find you need two irons, one about 15W and one of 30 to 50W. You can start as cheap as possible and up grade as you discover the limitations of your tools, but you get what you pay for. Our technical department mentions Tandy meters and Antex soldering irons as fair value for money.

You will discover what else you need as you go along. A soldering station is a luxury which could be classed as a necessity for the amount of irritation it can save!

Making PCBs is a specialisation which you will want to move on to, but steer clear of it till you have overcome the more basic tricks of construction.

We've said it before, we'll say it again: there is no foolproof way of ensuring that electronics constructions work properly first time, short of having a perfect design, perfect construction and using Military Spec. components. On top of the good grasp of theory needed by a pro., patience, careful method and intuition are essential. It's the ability to overcome the frustration of not knowing what's gone wrong (or failed to go right) and test, estimate and calculate your way to a solution that employers are looking for.

Synthesiser Request

Dear Sir,
Could you please tell me if you have ever published a Synthesiser project (not a minisynth)?

Thank you,
N. Simister,
Eccles,
Manchester.

Not yet; keep watching, it could happen.

Athletics Counter

Dear Sir,
Having read your magazine since February 1979 I would like to congratulate you on an all-round excellent magazine.

Now comes the request. I would be grateful if you could supply me with any information on track event counters. The system envisaged would start when the gun fires and finish when a runner crosses the line. Having seen commercial equivalents, perhaps it's time a hobbyist (ie cheap) version arrived. Below I give the characteristics of the device as proposed to me by a 100m sprinter.

1. Portable; 2. Battery operated; 3. Stop input, Start input, Reset control and 4-digit capability.

Yours,
David O'Sullivan,
Baldonnel,
Ireland.

An interesting idea, indeed one that crops up around the office from time to time. Unfortunately, it has never progressed beyond the "bright ideas" stage, so we can't help you with further information.

However we'll schedule it for development and see what happens, so keep in touch. Be warned, though: this is a "marathon" project, so don't expect results too "fast"!

Old Advertisers

Dear Sir,
Whatever happened to T. Powell? I saw his adverts in old issues of HE and his prices are very competitive.
Yours sincerely,
Ben Chaston,
Enfield,
Middlesex.

T. Powell appeared in the Directory of Electronic Components and Hardware Suppliers in HE J October '82 at the address of Advance Works, 44 Wallace Rd., London N1, Tel: 01 226 1489; hopefully, we'll have them in this year's survey when it appears in December.

However — a general warning — don't order straight away from suppliers advertising in issues more than two or three months old; people move, they mutate, prices go up, lines get dis-continued, anything can happen; write and/or phone them first and make sure they are where you think you are and have what you want.

Getting Into Radio

Dear Sir,
I am interested in radio electronics, and I have been experimenting with small, very low power transmitters with a range of about thirty feet, using circuits which our school electronics club has got.

I would now like to get into CB but I can not afford a shop bought rig, so I was wondering if you had got some circuits for CB radios and if so could you send me details.
Yours sincerely,
Simon Phillip,
Devizes,
Wilts.

Sorry, but radio transmission is very strictly controlled, so that those people who can or must use radio communications can do so without interference from 'pirate' transmitters.

All radio transmitters used in the UK must meet certain standards and with the exception of equipment used

by licensed radio amateurs, must be approved by the Department of Trade and Industry. All CB equipment included.

If you are serious about wanting to experiment with radio circuits your best bet is to sit for the Radio Amateurs' Examination. Contact the Radio Society of Great Britain, Alma House, Cranbourne Rd., Potters Bar, Herts EN6 3JW for more information.

In Short Supply

Dear Sir,
Please could you send me information on your Sound To Light Unit, HE January '81, because when I purchased the kit from Magenta, they did not enclose any technical information. And I found a few mistakes in your wiring diagram. And also could you let me know whether John Bull Electrical have closed down?
Yours faithfully,
Peter G. Rees,
Weyland,
Dyfed.

This depends on what information you want! We can tell you, for example, that there were two errors in the article: the Verobard track should be broken at co-ordinate B25, and that pins 6 and 7 of IC1 should be linked together.

As for J. Bull — they're still alive and well, as testified by any recent copy of HE, where they advertise their services regularly.

Seek The 'Speaker

Dear Sirs,
Please could you help me in obtaining a two and three way crossover unit for use in two loudspeaker systems. Each must be rated at about 100W. For the three-way crossover unit, the crossover frequencies must be between 1) 2500Hz and 3500Hz 2) 6500Hz and 7500Hz. For the two way unit, the crossover frequency must be between 5000Hz and 6000Hz.

If you could recommend any companies which produce such units I would be much obliged.
Yours faithfully,
R. J. Coleman,
Newark,
Notts.

Crossover units are designed for specific speaker systems, so it's unlikely you'll find one to exactly fit your requirements — but it's always worth a try. Wilmslow Audio make a variety of crossover units for their range of hifi speaker kits and may have one that will suit your design. Their address is 35/39 Church St., Wilmslow, Cheshire SK7 1AS.

H.E. PROJECT KITS

I.C.S.
TRANSISTORS
CAPACITORS

TOOLS
RESISTORS
HARDWARE

CASES
KITS
PCBs

MAGENTA

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Kits include ALL THE ELECTRONICS AND HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller-tinned) or Verobloc are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.E. which includes the project — you will need to order the instruction reprint at an extra 50p. Reprints available separately 50p each + p. & p. 50p.

WHISTLE SWITCH Aug 83 less mic	£18.89	IN CAR CASSETTE POWER SUPPLY Dec 81	£4.77
STEREO SPREADER Jul 83	£5.78	SCRATCH FILTER Nov 81 Mono	£5.82
SOFT FUZZ Jul 83	£10.25	LED VU METER Nov 81 less case	£4.87
SINCLAIR SOUND BOARD Jun 83 less case	£18.98	SIMPLE STYLE ORGAN Nov 81 less case	£4.98
TRAFFIC LIGHT TOY June 83 less stand	£8.23	METRONOME Nov 81	£12.71
BAT LIGHT (car battery indicator) June 83 less case	4.99	TELEPHONE BELL REPEATER Oct 81	£13.67
TTL LOGIC PROBE June 83	£7.98	Med linking wire extra	14p metre
AUTO TESTER May 83	£8.98	COMBINATION LOCK Oct 81 less solenoid	£18.95
STALL THIEF May 83 (inc relay)	£11.72	BBY ALARM Oct 82 E8.70	Fig 8 linking wire 7p metre
STEREO VOICE OVER UNIT April 83	£17.52	'DIANA' METAL LOCATOR Sept 81	£34.80
OPTIONAL MIC PRE AMP April 83 (no case)	£6.28	REACTION TESTER GAME Sept 81	£12.81
AUTO POWER DOWN April 83 (no case)	£13.55	VARIABLE BENCH POWER SUPPLY Aug 81	£28.98
LINEAR OHMMETER Mar 83	£10.37	ULTRASOUND BURGLAR ALARM July 81	£19.98
LOW RANGE OHMMETER Mar 83	£10.37	ELECTRONIC DOOR BUZZER July 81	£5.98
PHASE FOUR Dec 82	£15.38	ELECTRONIC METRONOME July 81	£4.99
STEREO NOISE GATE Dec 82	£21.73	CONTINUITY CHECKS June 81	£17.98
TAPE SLIDE SYNCHRONIZER Dec 82	£6.21	ENVELOPE GENERATOR June 81	£5.33
BIG EAR Dec 82	£4.98	AUDIO MIXER June 81	£19.48
MICROAMMETER ADAPTOR Dec 82	£14.98	PUBLIC ADDRESS AMPLIFIER March 81	£6.54 inc test leads
ODOMETER Nov 82	£4.98	Extras — horn speakers £6.83 each	PA MIC £24.40
DIANA V.C.O. Nov 82	£9.19	FUZZBOX March 81	£10.98
CB SQUELCH UNIT Oct 82	£5.60 (less case)	WINDSCREEN WIPER CONTROLLER March 81	£8.20
'JUNIOR' SLOT CAR CONTROLLER Sept 82	£11.33	STEAM LOCO WHISTLE March 81	£12.98
ZX INTERFACE BOARD Sept 82 inc edge con	£5.33	PHOTOGRAPHIC TIMER March 81	£3.80
T.V.I. FILTER July 82	£11.33	HATBATE MOTOR July 81	£24.98
AUTO WAH June 82 £18.98 inc case or £12.28 less case	£11.33	TWO-TONE TRAIN HORN Feb 81	£5.60 less case
AUTO GREENHOUSE SPRINKLER July 82	£14.38	MEDIUM WAVE RADIO Feb 81	£8.20
less pump and power supply		BENCH AMP Jan 81	£10.80
TELEPHONE TIMER June 82	£33.42 less power supply	NICAD CHARGER Jan 81	£8.20
POWER SUPPLY DESIGN 12V 800MA June 82	£9.98	CHUFFER Jan 81, less case	£27.53
ECHO REVERSE UNIT May 82, Less case	£33.98	BATTERY CHARGE MONITOR Dec 82	£3.77
Economy case WB3	£3.78 extra	MEMORY BANK — MINISYNTHESIZER Nov & Dec 80	£29.98
DIGITAL THERMOMETER May 82 excluding case + bezel	£18.98	TRANSISTOR TESTER Nov 81	£20.00
AUDIO SIGNAL GENERATOR May 82	£24.98	EXTRA PRINTING KIT Nov 80	£6.65
CABLE TRACER May 82	£9.98	INTRUDER ALARM Oct 80	£20.98
DIGITAL CAPACITANCE METER Apr 82	£21.37	TOUCH SWITCH Sept 80	£2.75 less case & contacts
SIGNAL TRACER Apr 82	£3.86	QUICQ PHASER Sept 80	£16.28
BIKE ALARM Apr 82	£11.74	SOUND OPERATED FLASH TRIGGER July 80 no akit	£5.33
DIGITAL DICE Mar 82	£7.29	FOG HORN Jun 80	£6.64
BICYCLE SIREN Mar 82	£10.89	SPEED CONTROLLER FOR R/C April 80	£17.55 (less case)
NOISELESS FUZZBOX Feb 82	£10.45	DIGITAL FREQUENCY METER April 80	£39.98
MASTHEAD AMPLIFIER Feb 82	£14.74	GUITAR TUNER May 79	£12.82
DRUM SYNTHESIZER Dec 81, Full kit	£21.37	CAR ALARM Feb 79	£12.91
QUITAR HEADPHONE AMPLIFIER Dec 81	£3.72		

BOOKS: ELECTRONICS & COMPUTING

205 First Book of Hi-Fi Loudspeaker Enclosures	£0.95	Semiconductor Data Book Nawnes	£8.95
221 28 Tested Transistor Projects	£1.25	Basic Electronics Theory and Practice	£7.98
223 50 Projects Using IC CA3139	£1.25	Microprocessor for Hobbyist	£4.75
225 A Practical Introduction to Digital ICs	£1.25	Burglar Alarm Systems	£5.55
226 How to Build Advanced Short Wave Receivers	£1.95	Electronics, Build and Learn	£3.90
228 Essential Theory for the Electronic Hobbyist	£1.95	Electronic Projects in Music	£3.90
BP39 50 (FET) Field Effect Transistor Projects	£3.50	CONTRAST Projects in Photography	£3.90
BP40 Digital IC Equivalents and Pin Connections	£3.50	Electronic Projects in Home Security	£3.90
BP41 Linear IC Equivalents and Pin Connections	£3.50	Questions and Answers Electronics	£2.70
BP42 50 Simple L.E.D. Circuits	£1.50	Electronic Projects in the Car	£3.90
BP43 How to Make Walkie-Talkies	£1.95	20 Solid State Projects Car and Garage	£4.80
BP45 Projects in Opto-Electronics	£1.95	110 Bells Alarm Projects	£4.25
BP47 Mobile Discotheque Handbook	£1.35	Computing is Easy	£5.75
BP48 Electronic Projects for Beginners	£1.95	ZX81 Users Handbook	£5.75
BP49 Popular Electronics Projects	£1.95	ZX81 Basic Book	£5.75
BP55 Electronic Security Devices	£1.95	Fun with Electronics	£1.25
BP58 50 Circuits Using 7400 Series ICs	£1.25	24 50 CMOS J.C. Projects	£1.25
BP59 Second Book of CMOS IC Projects	£1.50	BP24 52 Projects Using IC 741	£1.25
BP61 Beginners Guide to Digital Techniques	£0.95	BP44 IC555 Projects	£1.95
BP70 Transistor Radio Fault-Finding Chart	£0.50	BP50 IC LM3900 Projects	£1.35
BP71 Electronic Household Projects	£1.75	BP65 Single IC Projects	£1.50
BP75 Electronic Test Equipment Construction	£1.75	BP69 Electronic Projects	£1.75
BP78 Practical Computer Experiments	£1.75	BP72 A Microprocessor Primer	£1.75
BP79 Radio Control for Beginners	£1.75	BP73 Remote Control Projects	£1.95
BP80 Popular Electronic Circuits — Book 1	£1.95	BP74 Electronic Music Projects	£1.75
BP81 Electronic Synthesizer Projects	£1.75	BP76 Power Supply Projects	£1.95
BP82 Electronic Projects Using Solar Cells	£1.95	BP83 CMOS Projects	£1.95
BP85 International Transistor Equivalents Guide	£1.25	BP84 Digital IC Projects	£1.95
BP87 Simple L.E.D. Circuits — Book 2	£1.35	BP88 How to Use OP-Amps	£2.25
BP92 Easy Electronics — Crystal Set Construction	£1.75	BP90 Audio Projects	£1.95
BP94 Electronic Projects for Cars and Boats	£1.95	BP93 Electronic Timer Projects	£1.95
BP98 Popular Electronic Projects Working	£0.85	BP95 Model Railway Projects	£1.95
BP101 How to Identify Unmarked ICs	£0.85	BP97 IC Projects for Beginners	£1.95
BP103 Multi-Circuit Board Projects	£1.95	BP99 Mini Matrix Board Projects	£1.95
PI08 International Diode Equivalents Guide	£2.25	BP105 Aerial Projects	£1.95
BP109 The Art of Programming the 1K ZX81	£2.50	BP106 Modern OP-Amp Projects	£1.95
BP114 The Art of Programming the 16K ZX81	£2.50	BP115 The Pre-Computer Book	£1.95
BP119 The Art of Programming the ZX Spectrum	£2.50		

How to make and Design your own PCBs	£1.95
292 Handbook of Integrated Circuits (ICs) Equiv. & Substitutes	£1.95
222 Solid State Short Wave Receivers for Beginners	£1.25
227 Beginners Guide to Building Electronics Projects	£1.25
BP1 First Book of Transistor Equivalents and Substitutes	£1.50
BP14 Second Book of Transistor Equivalents and Substitutes	£1.75
BP27 Chart of Radio, Electronic, Semi-conductor and Logic Symbols	£0.50
BP32 How to Build Your Own Metal and Treasure Locators	£1.75
BP36 50 Circuits Using Germanium, Silicon and Zener Diodes	£1.50
BP37 50 Projects Using Relays SCR's and TRIACs	£1.95
BP51 Electronic Music and Creative Tape Recordings	£1.95
BP53 Practical Electronics Calculations and Formulae	£1.95
BP57 How to Build Your Own Solid State Oscilloscope	£1.95
BP60 Practical Construction of Pre-amps Tone Controls, Filters & Attn	£1.45
BP68 Beginners Guide to Microprocessors and Computing	£1.75
BP67 Counter Drive and Neural Display Projects	£1.75
BP66 An Introduction to BASIC Programming Techniques	£1.95
BP107 30 Solderless breadboard Projects — Book 1	£2.25
BP110 How to Build Electronic Projects Working	£1.95
BP117 Practical Electronic Building Blocks — Book 1	£2.25
Elementary Electronics. Sladdin. Excellent theory and 35 constructional projects. Uses S-Dec. First steps to CSE level interfacing to microprocessors and microcomputers	£3.95

FUN WITH ELECTRONICS	£1.95
Enjoyable introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners — children and adults. Only basic tools needed. 64 full colour pages cover all aspects — soldering — fault finding — components (identification and how they work).	
Also full details of how to build 6 projects — burglar alarm, radio, games, etc. Requires soldering — 4 pages clearly show you how.	
COMPONENTS SUPPLIED	
ALLOW ALL PROJECTS TO BE BUILT AND KEPT.	
Supplied less batteries & cases.	
FUN WITH ELECTRONICS COMPONENT PACK £15.78	
BOOK EXTRA £1.25	
Book available separately.	

ZX SPECTRUM AMPLIFIER

250mW output. Volume control. Internal speaker. Very simply connected using load/save lead. Puts real power even into the simplest "Beep" commands. Adds a real "zing" to musical programs and games. Requires PP3 battery — not supplied. Very low current drain. Supplied ready built complete with demo software and instructions.

ORDER AS: ZX SPECTRUM AMPLIFIER (SAHE) £6.98

ZX SPECTRUM SUPER AMPLIFIER

250mW output. Now add synthesizer quality to those "Beep" commands. Supercircuit with adjustable ATTACK, SUSTAIN and DECAY envelope controls. Plus variable ECHO. Generates a wide range of special effects. Five graduated controls. Internal speaker. Very smart case. Requires batteries — not supplied. Very low current drain. Ready built complete with demo software and instructions.

ORDER AS: ZX SPECTRUM SUPER AMPLIFIER (SSAHE) £17.98

SOLDERING/TOOLS

ANTEX X5 SOLDERING IRON 25W	£5.48
SOLDERING IRON STAND	£1.98
SPARE BITS. Small standard, large, For X5 + X25	65p each
SOLDER. Handy size	99p
SOLDER CARTON	£1.84
DESOLDER BRAID	89p
HEAT SINK TWEEZERS	29p
DESOLDER PUMP	£6.48
HOW TO SOLDER LEAFLET	12p
LOW COST CUTTERS	£1.89
LOW COST LONG NOSE PLIERS	£1.98
WIRE STRIPPERS & CUTTERS	£2.89
PRECISION PETITE	
1/2 P.C.B. DRILL	£11.67
DRILL STAND	£7.98
GRINDING STONE	50p
GRINDING WHEEL	50p
SAW BLADE	85p
BRASS WIRE BRUSH	50p
BURR	50p
VERO SPOT FACE CUTTER	£1.49
pin insertion tool	£5.71
VEROPINS (pk of 100) 0.1"	52p
MULTIMETER TYPE 1 (1.00 opv)	£5.48
CROCODILE CLIP TEST LEAD SET. 10 leads with 20 clips	99p
RESISTOR COLOUR CODE CALCULATOR	21p
CONNECTING WIRE PCKE TEST ED. 11 coloured	48p
ILLUMINATED MAGNIFIERS	
Small 2" dia (5x mag)	£1.14
Large 3" dia (4x mag)	£2.40
CAST IRON VICE	£2.98
SCREWDRIVER SET	£1.98
POCKET TOOL SET	£3.98
DENTIST INSPECTION MIRROR	£2.85
JEWELLERS EYEGLASS	£1.50
PLASTIC TWEEZERS	69p
PAIR OF PROBES WITH LEADS (cc)	77p
Q MAX PUNCHES	
1/4" £2.98; 1/2" £3.06; 3/4" £3.17; 1" £3.24	



MULTIMETER TYPE 2 (1V350TRI) 20K o.p.v. with transistor tester. £4.75 AC + DC volts DC current, 4 very useful resistance ranges. We've used it and we like it



HELPING HANDS JIG £6.30 Heavy base, 5/8" ball and socket joints allow infinite variation of clips through 360°. Has 2 1/2" diameter (2.5 magnifier attached), used and recommended by our staff.

Speakers min 8 ohm 87p; 64 ohm 89p; 80 ohm 98p	Brimboard breadboard	£6.98
Crystal earpiece	Verobloc breadboard	£4.20
Magnetic earpiece	PCB etching kit	£4.98
Stethoscope attachment	ZX81 edge connector	£2.25
Mono headphones	Ferrite rod 5 inch	59p
Stereo headphones	PP3 clips	11p
Telephone pick up coil	PP9 clips	11p
Min buzzer	2 station Intercom	£6.75
Euro breadboard	IC sockets	8 pin 16p; 14 pin 17p; 16 pin 18p
S Dec breadboard		£6.98

ADVENTURES WITH MICROELECTRONICS

Similar to 'Electronics' below. Uses I.C.s. Includes dice, electronic organ, doorbell, reaction timer, radio etc. Based on Bimboard 1 bread board. Adventures with Microelectronics £2.98

Component pack £29.64 less battery.

ADVENTURES WITH DIGITAL ELECTRONICS

Entertaining and instructive. Includes details of some digital ICs and 8 projects: shooting gallery, 2 way traffic lights, electronic adder, computer space invaders game etc. No soldering.

Adventures with Digital Electronics book £3.25

Component pack including breadboards £42.50 less batteries.

ADVENTURES WITH ELECTRONICS by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects.

Adventures with Electronics £2.85. Component pack £18.98 less battery.

30 SOLDERLESS BREADBOARD PROJECTS

Book 1 by R. A. Penfold

Clear verobloc layouts and circuit diagrams. Includes fuzx box, radio, metronomes, timers, transistor checker, switches etc. Introduction gives basic information on components including resistors, capacitors, I.C.s, transistors, photocells etc. Ideal for beginners as well as those with some experience.

Complete kit including verobloc, book and components (less batteries) £24.75

Less book £22.50, less verobloc £20.25. Book only £2.25.

MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST

Price list included with orders or send sae (9 x 4)

CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery.

Send 80p in stamps or add 80p to order. FREE to Schools/Colleges requested on official letterhead.

MAGENTA gives you FAST DELIVERY OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers — HAVE YOU TRIED US?

MAGENTA ELECTRONICS LTD.

Magenta Electronics Ltd, HA39, 135 Hunter St., Burton on Trent, Staffs. DE14 2ST. MAIL ORDER ONLY. 0283 85435. Mon-Fri 9-5. Access/Barclaycard (visa) by phone or post

Add 50p P&P to all orders. Prices include VAT. SAE all enquiries. Official orders welcome. OVERSEAS: Payment must be in sterling. IRISH REPUBLIC and BFPO UK PRICES. EUROPE: UK Prices plus 10%. ELSEWHERE: write for quote.

Digital & Micro ELECTRONICS

No 1 WINTER 1983

An Argus Specialist Publication

£2.25

**Photographic Colour-
Process Monitor: use your
Spectrum for accurate
darkroom control**

**State Scope kit
A low-cost high
performance Solid**

**Build a
low-cost joystick
for the Video Genie**

**The BBC Finds Its Voice!
Speech synthesis system
for the BBC Computer
reviewed**



NEW! OUT SOON

EASY ADD-ONS
for ZX81-
SPECTRUM-ACE

NEW



17 exciting electronic projects to build and run on your own micro.

- LIGHT PEN
- PICTURE DIGITISER
- KEY PAD
- MODEL CONTROLLER
- WEATHER STATION
- + OTHER EXCITING & INTERESTING PROJECTS

REALISE THE REAL WORLD POTENTIAL OF YOUR MICRO.

A newly released book written by well known author Owen Bishop and published by Bernard Babani gives fully descriptive details on how to build all 17 projects – all are fairly simple and inexpensive to construct – The most complex component (the DECODER) is supplied in kit form ready to assemble with all components and plated through PCB. – Components for the projects are readily available locally or found in your workshop drawers.

Once assembled and connected to your micro the decoder is able to run any or all of the projects simultaneously.

Simple Programmes are included to get you started but of course the more experienced programmer can have hours of fun writing complex programmes to take full advantage of these easy but exciting projects.

Please send by return.. Specify which computer

QTY	REF	DESCRIPTION	PRICE	TOTAL
	HB/2000	"EASY ADD-ONS" + DECODER KIT & BOOK	£24.00	
	HB/2001	"EASY ADD-ONS" BOOK ONLY	£3.00	
	HB/2002	DECODER KIT ONLY	£22.00	
	HB/2003	DECODER PCB ONLY	£8.00	
TOTAL				

Price inclusive of VAT & carriage. Please allow 21 days for delivery. Cheques, PO's or signed Access orders welcomed.

Please Send Full Hobbyboard Mail Order Catalogue with full range of PCB materials & Hardware

Name

Address

hobbyboard

a division of
KELAN ENGINEERING Ltd
Hookstone Park
Harrogate, N. Yorks

complete P.C.B. workshop

HE/11/83

SECURITY

Build your own system and SAVE POUNDS!

DIGITAL ULTRASONIC DETECTOR US 5063



- 3 levels of discrimination against false alarms
 - Crystal control for greater stability
 - Adjustable range up to 25ft.
 - Built-in delays
 - 12V operation
- This advanced new module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions. The module has a built-in exit delay and timed alarm period, together with a selectable entrance delay, plus many more outstanding features. This advanced new module is available at only £13.95 + V.A.T.

ULTRASONIC MODULE US 4012



- Adjustable range from 5-25ft.
- This popular low cost ultrasonic detector is already used in a wider range of applications from intruder detectors to automatic light switches and door opening equipment, featuring 2 LED indicators for ease of setting up, the unit represents outstanding value at £10.95 + V.A.T.

INFRA-RED SYSTEM IR 1470



Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft, operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications, the system is available at only £25.61 + V.A.T. Size 80 by 50 by 35mm.

POWER SUPPLY & RELAY UNIT PS 4012

Provides stabilised 12V output at 85mA and contains a relay with 3 amp contacts. The unit is designed to operate with up to 2 ultrasonic units or 1 infra-red unit IR 1470. Price £4.25 + V.A.T.

SIREN MODULE SL 157

Produces a loud penetrating sliding tone which, when coupled to a suitable horn speaker, produces S.P.L.'s of 110db's at 2 metres. Operating from 9-15V, the module contains an inhibit facility for use in 'break to activate' circuits. Price £2.95 + V.A.T.

5½" HORN SPEAKER HS 588

This weather-proof horn speaker provides extremely high sound pressure levels (110db's at 2 metres) when used with the CA 1250, PS 1865 or SL 157. Price £4.95 + V.A.T.

3-POS. KEY SWITCH 3901

Single pole, 3-pos. key switch intended for use with the CA 1250. Price £3.43 + V.A.T.

All modules are supplied with comprehensive instructions.

Units on demonstration.
Shop hours 9.00-5.30 p.m.
Wed. 9.00-1.00 p.m.
SAE with all enquiries.

ALARM CONTROL UNIT CA 1250



- The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system whether a highly sophisticated installation, or simply controlling a single magnetic switch on the front door.
- Built-in electronic siren drives 2 loud speakers
 - Provides exit and entrance delays together with fixed alarm time
 - Battery back-up with trickle charging facility
 - Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
 - Anti-tamper and panic facility
 - Stabilised output voltage
 - 2 operating modes – full alarm/anti-tamper and panic facility
 - Screw connections for ease of installation
 - Separate relay contacts for switching external loads
 - Test loop facility

Price £19.95 + V.A.T.

SIREN & POWER SUPPLY MODULE PSL 1865



A complete siren and power supply module which is capable of providing sound levels of 110db's at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 or US 4012 to form a complete alarm.

Price £9.95 + V.A.T.

HARDWARE KIT HW 1250



only £9.50 + V.A.T.

This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label. Size 200 by 180 by 70mm.

HARDWARE KIT HW 5063



only £9.95 + V.A.T.

This hardware kit provides the necessary enclosure for a complete self-contained alarm system which comprises the US 5063, PS 1865, loud speaker type 305 and key switch 3200. Attractively styled, the unit when completed, provides an effective warning system without installation problems.

ULTRASONIC MODULE ENCLOSURE



only £2.95 + V.A.T.

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063; for US 4012 order SC 4012.


Add 15% VAT to all prices.
Add 50p post & packing to all orders.

Order by telephone or post

using your credit card.

RISCOMP LIMITED

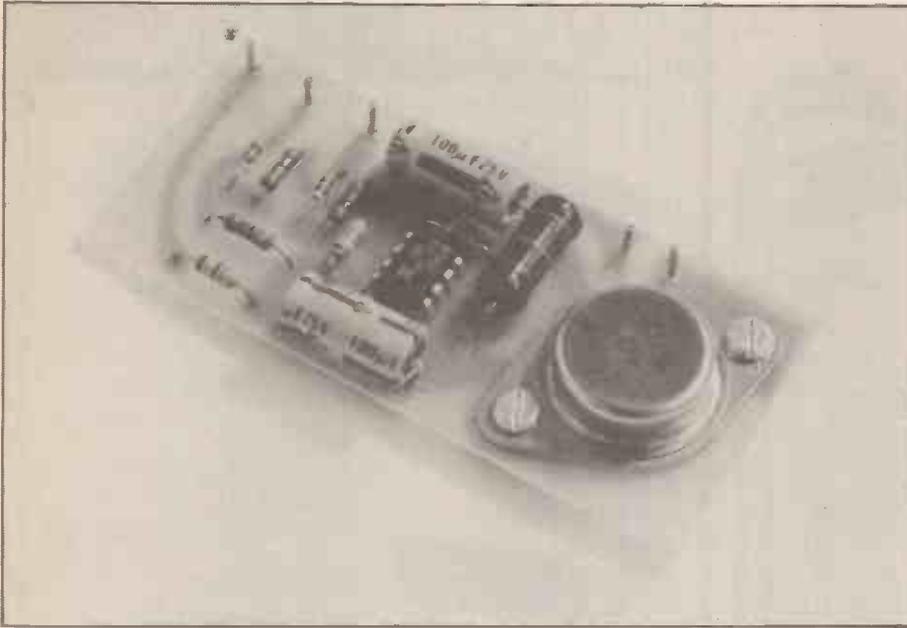Dept. HE6
21 Duke Street,
Princes Risborough,
Bucks. HP17 0AT
Princes Risborough (084 44) 6326



INTERIOR LIGHT DELAY

Tony Scragg

Lead, kindly light . . .

DO YOU want to improve the specification of your car to Cortina Crusader or even Jaguar XJ6 specification? With this circuit you can — at least in the interior light department. The circuit described here is suitable for all negative earth cars fitted with door switches to operate the interior light.

The function of the circuit is to keep the interior light on after the car door is closed, allowing time to find keys or the way out of the garage etc. The delay can be set to any value and with the component values given, this is about 30 seconds. Switching on the ignition over-rides the delay, allowing

the car to be driven away safely at night before the 30 seconds are over. Opening the doors with the ignition on causes the interior light to operate "normally", ie with no delay.

Installation of the circuit involves interrupting the connection between the light and the switches and making connections to battery, earth and ignition.

Circuit Description

The heart of the circuit is the 555 timer IC which is used as a comparator, in this application; its internal divider chain and good output

drive capability simplify the circuit considerably.

Basically there are two states of interest here. When the trigger and threshold inputs are less than $\frac{1}{3}V_{cc}$ the output is high, turning on the output stage, Q1. When inputs are greater than $\frac{2}{3}V_{cc}$ the output stage is turned off.

Referring to the circuit diagram, when the doors have been closed for some time (switch contacts open) C1 will be charged up to $\frac{2}{3}V_{cc} + 0V7$; this voltage is clamped by diode D3 and the internal divider chain, to protect the 555 inputs.

In this stage the light is off, but opening the door causes C1 to be discharged through R2 and D2 (R2 limits the current through D2). Hence the inputs go below $\frac{1}{3}V_{cc}$ and the light is turned on. Closing the door, D2 is reversed biased by R1, and C1 charges up through R4 — this defines the delay time. If the ignition is switched on during this time, C1 rapidly charges up through D1 and R3, hence the light goes off immediately. C2, ZD1 and R6 form a simple power supply filter and protection from high battery voltages.

Construction Details

Construction of the interior light delay unit is fairly straightforward, being simply a matter of soldering the components to the PCB as per Figure 2. Ensure that the IC, diodes and electrolytic capacitors are of the correct polarity and also note that the 2N3055 must be bolted down using metal bolts, as one of these forms the electrical connection to the transistor collector. It is also advisable to solder the nuts down to the PCB as this gives a more reliable joint and helps to stop the screws loosening!

Once the PCB is assembled, flying leads are attached to the five connections to the board and the board then mounted in any small plastic enclosure at hand (as the unit will be mounted out of sight behind the dashboard appearance is not of utmost importance). A piece of foam rubber is used to locate the board in the enclosure and the flying leads brought out to "chocolate block" connectors.

Installation

The first stage of the installation is to locate the interior light wiring, as the unit is most conveniently mounted near to this wiring. The wire of interest is that between the light and the door switches. In the case of roof mounted lights this wire runs up one of the windscreen or door pillars, so is quite easily traced where it emerges under the dash or carpet. Generally, both front doors and sometimes the rear doors have switches installed and it is important that all these have merged into one conductor to the light at the point that the connections are made, otherwise not all the doors will have delayed operation.

Once this wire has been located it

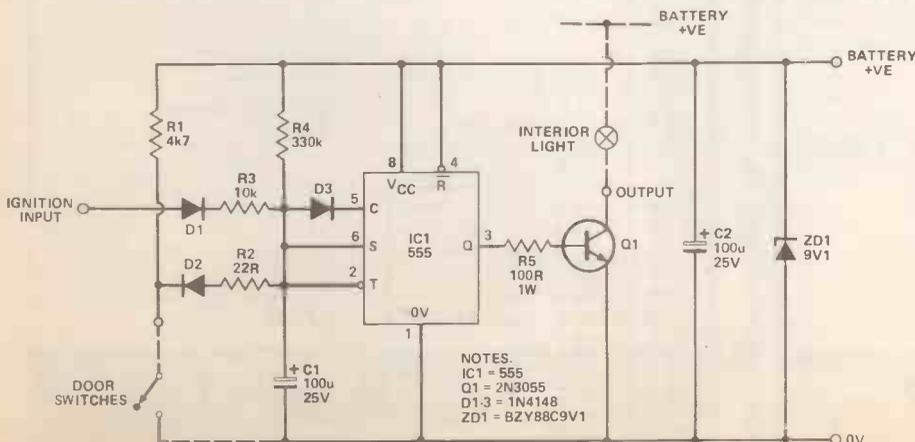


Figure 1. The circuit is based on a 555 used as a comparator.

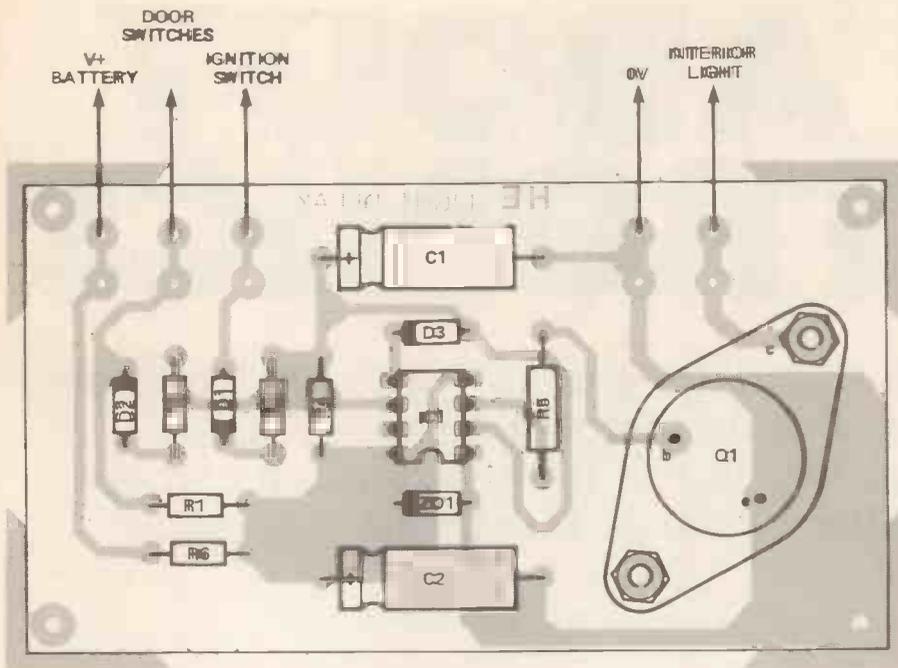


Figure 2. The PCB is compact, for easy installation.

is cut to generate two connections to the light delay unit — the door switches to the input and the light connection to the unit output. A permanent source of 12V is also

required — this can be taken from the interior light supply or the clock supply, for example. Any convenient earth connection can be used and the final connection is to the ignition

Parts List

RESISTORS
 (All 1/4 watt 5% carbon unless noted)

R1	4k7
R2	22R
R3	10k
R4	330k
R5	100R
R6	2.5W wirewound 47R

CAPACITORS

C1, 2	100u 25V axial electro
-------	-------	------------------------

SEMICONDUCTORS

IC1	555
Q1	2N3055
D1, 2, 3	1N916
ZD1	BZ788C9V1

MISCELLANEOUS
 PCB; optional case; wire, solder, nuts and bolts etc.

BUYLINES page 34

circuit, which can be taken from the back of the ignition switch.
 The unit requires no setting up and should be completely operational once connected.



MICROTANIC

COMPUTER SYSTEMS LTD.



IF YOU WANT FLEXIBILITY AND EXPANDABILITY THEN YOU WANT THE

MICROTAN 65

Start by building your own computer

FOR LESS THAN

£60



EXPANDABLE —

from 1K to 256K

FLEXIBLE 6502 system with the following options:

Parallel I/O Board	Disk Controller	Eprom Programmer Card	Sound Board	32K Ramboard
Serial I/O Board	Real Time Clock	Colour Graphics	32K Romboard	ASCII Keyboard

Building into a Disc-based system with a stylish System Rack to take whatever boards suit your needs.

FULL RANGE OF SOFTWARE AVAILABLE — All boards available in kit form or fully built

LANGUAGES AVAILABLE: MACHINE CODE · ASSEMBLY · BASIC · FORTH

DEALER ENQUIRIES WELCOME



SHOWROOM:
 16 Upland Road,
 Dulwich, London SE22

MAIL ORDER:
 235 Friern Road,
 Dulwich, London SE22



TELEPHONE: 01-693 1137

ALL ABOUT ELECTRONICS

Our new **Beginner's Series** tells you all you'd like to know about electronics. From start to finish. All about components and circuits, all the theory you need to get started in the world of electronics.

IN OUR FIRST LOOK at semiconductors, in last month's All About Electronics, we saw there were two basic ways of using transistors — in circuits where an electronic switch was required to turn on or off electrical equipment, and in circuits which required amplification of electrical current.

The first type of circuit — the transistor as a switch — is broadly classified as *digital*. In the electronic sense, this means that the circuits have fixed output states. We can further classify digital circuits as *binary digital*, ie, any circuit has only two logic states: *on* and *off*. These states are generally indicated by a voltage change at the output of the circuit, a typical voltage change being from 0V when the output is off, to 5V when on. Other circuits may have voltage level states of, say -5V, and +12V. The voltage levels are irrelevant; the important factor is the identification of two distinct logic states. In this way, the output state of one transistor stage can be used to apply the input state of the following transistor stage, so that complex and automatic electronic equipment can be built up. As a general rule, the numbers 0 and 1 are used to distinguish between the logic states — whatever the voltages used.

Simply Logical

We saw the simplest of these logic circuits last month if you remember. Figure 1 shows it — no more than the basic NPN transistor with a collector resistor and a base resistor. Let's take a look at its action to see what happens. With no voltage applied at point A (ie, logic 0) no base current flows so the transistor is off ie, no collector current flows and the transistor resistance is extremely high. A circuit equivalent to this condition is shown in Figure 2. The base resistor is effectively connected to the same voltage at both ends (0V) and so no current flows through it. The

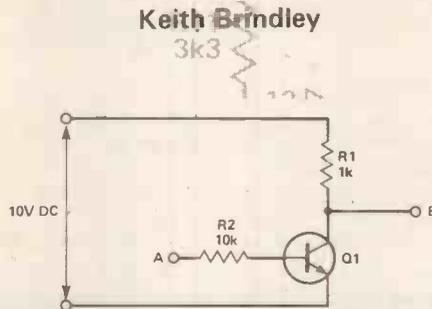


Figure 1. A single transistor used as an inverter logic gate.

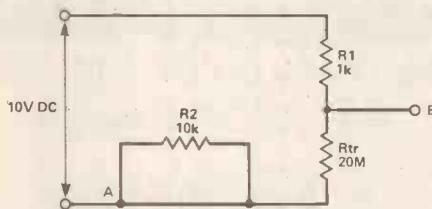


Figure 2. Equivalent diagram of a single transistor inverter with logic 0 at point A.

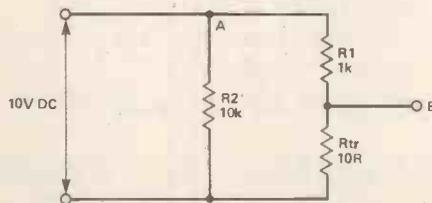


Figure 3. Equivalent diagram of a single transistor inverter, this time with logic 1 at point A.



Figure 4. Symbol of an inverter gate.

transistor resistance (R_{tr}) is shown as 20M (a typical value for a transistor in the off mode). Resistors R_{tr} and $R1$ form a voltage divider, the output voltage of which follows the formula:

$$V_B = \frac{R_{tr}}{R_{tr} + R1} \times V_A$$

$$= \frac{20M}{20M + 1k} \times 10$$

which is close enough to being 10V ie, logic 1, to make no difference. The output of our circuit is of the opposite logic state to the input.

If we now consider the transistor with a base current — the equivalent circuit is shown in Figure 3 — we know that the transistor resistance is low (shown as 10R by R_{tr} in Figure 3), hence the output voltage at point B is:

$$V_B = \frac{10}{1k + 10} \times 10$$

which is close to 0V (logic 0) as we'll ever get. So, in this mode the transistor output state is always the opposite of the input state. So whatever the input logic state, the output is the reverse. We call this simple digital circuit — you guessed it — an inverter.

Every Picture Tells A Story

To make it easy and convenient to design complex circuits using such transistor switches, symbols can be used instead of having to draw the whole transistor circuit. The symbol for an inverter is shown in Figure 4 and is fairly self-explanatory. The triangle represents the fact that the circuit acts

IN	OUT
1	0
0	1

Figure 5. Truth table of an inverter gate.

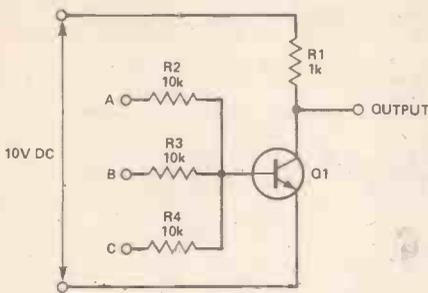


Figure 6. A single transistor, three-input NOR gate.

as what is called a buffer ie, connecting the input to the output of a preceding stage does not affect or dampen the preceding stage in any way. The dot on the output tells us that an inverting action has taken place and so the output state is the opposite to the input state in terms of logic level.

To aid our understanding of digital logic circuits, input and output states are often drawn up in a table — known as a truth table. The truth table for an inverter is shown in Figure 5.


Another transistor circuit used in digital logic is shown in Figure 6. Before I tell you what this circuit is called let's see if we can calculate how it works. Incidentally, circuits like the inverter and this one — and others which you will see over the coming months — are termed *gates*. The gate in Figure 6 looks similar to the inverter gate, doesn't it? But it has three inputs and three base resistors. If inputs A, B and C are at logic 0, then no base current flows, the transistor resistance is high, and so the output state is logic 1. However, if any one or more of the inputs is high (ie, at logic 1) then the output changes to a low (logic 0) state.

The operation of the gate can be summarised if we say that the only case in which the output state is high is when neither input A, nor input B, nor input C is high. Would you believe, this gate is known as a NOR gate. Its truth table is shown in Figure 7.

Figure 8 summarises a number of the symbols of the more common digital logic gates, all of which can be constructed using transistors. Their actual construction is unimportant, however, only the symbols need be learned. Binary digital logic is a fascinating topic in its own right really, and I'm not going to spend too much time talking about it now, but I will discuss it next month when All About Electronics will be dedicated to it.

A	B	C	OUTPUT
1	1	1	0
0	1	1	0
1	0	1	0
0	0	1	0
1	1	0	0
0	1	0	0
1	0	0	0
0	0	0	1

Figure 7. Truth table of a three-input NOR gate.

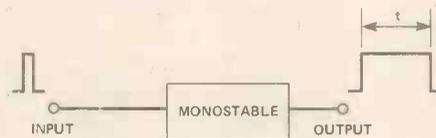

The next digital circuit we must study is known as the *bistable*. It is the first of a group of three circuits which is probably the most important group of digital circuits there is. Each of the three circuits can be formed by using two transistors and the bistable is shown in Figure 9.

Shutting The 'Stable Gate

A bistable is formed simply by connecting the output of one inverter gate to the input of a second. The output of the second is then connected back to the input of the first. In this way the overall output, at point B in Figure 9, is held at either state (high or low; logic 1 or logic 0) for an indefinite period. When the input state is changed so does the output: the output then remains stable in its new state indefinitely. The circuit is therefore stable in both logic states — hence the name 'bi-stable'! Bistables are given the nickname *flip-flop* which describes their operation in a more graphic (but no less accurate) way.

The next circuit in the group is the *monostable* — yes, you're right, it has only one stable state. Operation is best described by considering the block diagram in Figure 10. When an input pulse ie, a short variation of input

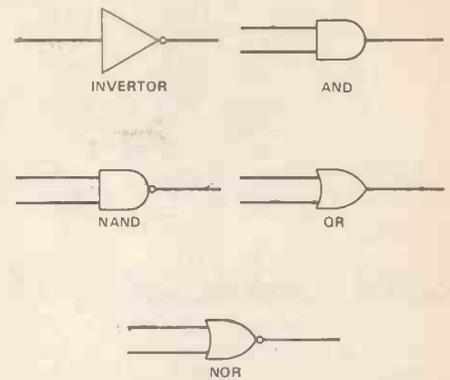


Figure 8. A selection of available logic gate.

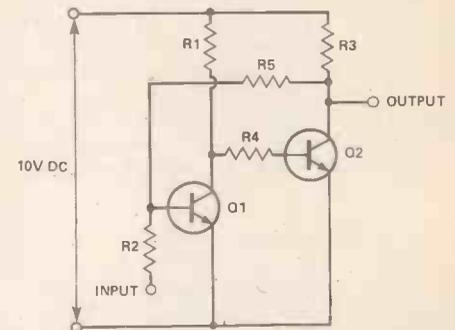


Figure 9. A two-transistor bistable formed by connecting the output of the first to the input of the second.

Figure 10. Block diagram of a monostable

voltage from logic 0 to logic 1 and back to logic 0 again occurs, the output varies as shown. The time, *t*, during which the output is high is fixed, so no matter what length the input pulse is, the output will be high for time *t*. Time, *t*, could be as short or as long as required. The circuit could form the basis of a controller for, say, an electric fire, where a single press of a push-button turns the fire on for a fixed time of twenty minutes, and then automatically turns it off again.

Again, as in the bistable, two transistors are used to build this circuit in Figure 11. Again the first transistor switches the second, which in turn switches the first. But this time a capacitor has been placed between transistors TR1 and TR2. So, how and why does this affect the operation of the original bistable to form this monostable?

To understand that, we have to take a closer look at capacitors. A couple of months ago we saw initially how capacitors worked, but to simplify things I did not discuss their operation in DC circuits. Well, now is the time to do so! Firstly, let's consider the capacitor in Figure 12a. The capacitor is connected to 0V at its lower end (hence the connection to the earth symbol). If we allow a constant current to flow into the top of the capacitor then obviously, the

voltage across the capacitor will increase at a constant rate. This is shown by the voltage on the graph in Figure 12b. Now, we should remember that the capacitor will hold a charge, so if the constant current is now removed the voltage across the capacitor will be held constant. This is shown by the level voltage on the graph in Figure 12b.

Resistors And Capacitors

This whole process of applying a constant current then removing it can be approximated quite simply by connecting a series resistor to the capacitor, then applying a DC voltage, as in Figure 13a. It is not possible with such a simple circuit to produce a truly constant current, as you will see, but the following explanation of circuit operation will show you that the overall effect is close enough. Take, for example, the instant the DC voltage is applied to the circuit. The voltage across the capacitor plus the voltage across the resistor must equal the applied voltage ie:

$$V_{cc} = V_{cap} + V_{res}$$

Now, at this instant the voltage across the capacitor must be zero, so all the applied voltage must appear across the resistor ie:

$$V_{cc} = V_{res}$$

So, the current in the circuit is, from Ohm's Law:

$$I = V/R$$

and, because the voltage is at maximum the current is also at maximum. This is shown by the fact that the voltage across the capacitor (Figure 13b) begins to increase over the first part of the graph at a high rate.

After a period of time the voltage has increased across the capacitor so the voltage across the resistor must have dropped. Let's say the capacitor voltage, V_{cap} is 5V, then obviously the resistor voltage V_{res} must also be 5V. Because the current in the circuit is defined from Ohm's Law and is directly related to the resistor voltage then, if the voltage falls, so must the current. Also, because the current falls, so does the rate at which the capacitor voltage increases. You can see this on the graph in Figure 13b because the slope of the graph decreases as the capacitor voltage increases.

Finally, the capacitor voltage increases so much that the resistor voltage decreases to zero, and so no more current flows. At this point the capacitor voltage levels out on the graph in Figure 13b and remains constant.

So overall we have produced an effect similar to that in Figure 12. The process of gradually increasing a capacitor voltage is known as charging a capacitor and the circuit consisting of a resistor and a capacitor is known as a *resistor-capacitor (RC) circuit*. The curve of the capacitor voltage which such a circuit

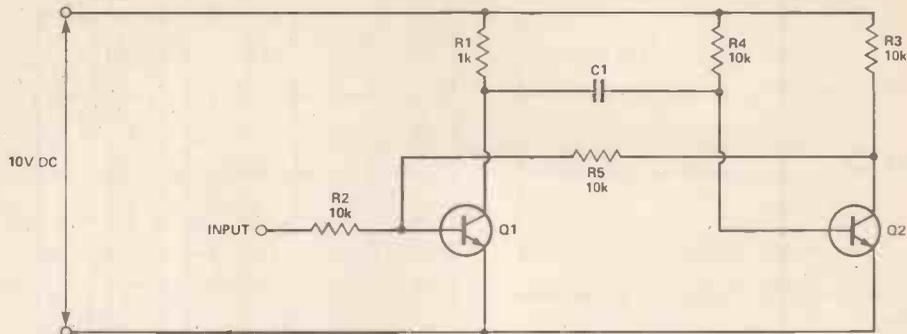


Figure 11. Monostable formed by two transistors connected by a capacitor.

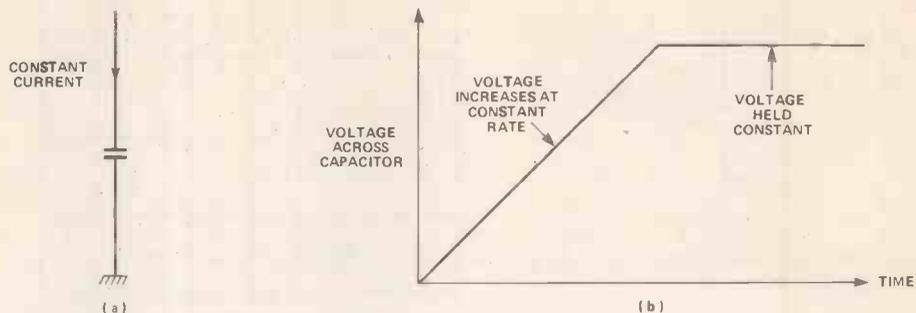


Figure 12. a) A constant current used to charge a capacitor b) Capacitor voltage when a constant current is applied then removed.

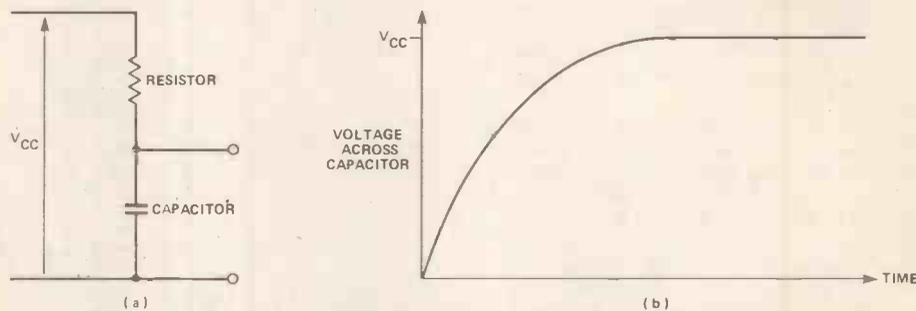


Figure 13. A practical approximation of Figure 12.

produces is known as an exponential curve and any combination of resistor/capacitor/applied voltage will produce an exponential curve of capacitor voltage — only the values of the graph areas would differ.

Likewise, we can take a charged capacitor and put a resistor in parallel with it to *discharge* the stored voltage. Of course, as current flows through the parallel resistor, the voltage across the capacitor falls, so less current will flow causing the voltage to fall at a slower rate. The curve produced and the circuit is shown in Figure 14. Again the curve is said to be exponential.

We've Got The Time

These two simple circuits are particularly useful because they both produce a time delay where their outputs occur a period of time after their inputs. And, the period of time is directly related to the charging (or discharging) current and the voltage across the capacitor: so increasing the value of either the resistor or the capacitor increases the time delay; and

decreasing the resistor or capacitor value decreases the time delay.

The product of the resistor and the capacitor value is known as the time constant, t , and has units of seconds ie:

$$t = C \times R \text{ (in seconds)}$$

So, if a capacitor has a value of, say, 1 μ F and a resistor has a value of 1M then the time constant:

$$t = 1 \times 10^{-6} \times 1 \times 10^6 = 1s$$

I have reproduced the graph of an exponential curve in Figure 15 and marked some important points on the curve relating to the time constant. These are:

- at a time equal to 0.69t the capacitor voltage is at a voltage of 0.5 of its final voltage.
- at a time t, the capacitor voltage is 0.63 of its final voltage.
- at time 3t, the capacitor voltage is 0.95 its final voltage.

Although I have shown these values on an exponential charging curve, they are the same for an exponential discharge curve, just upside-down.

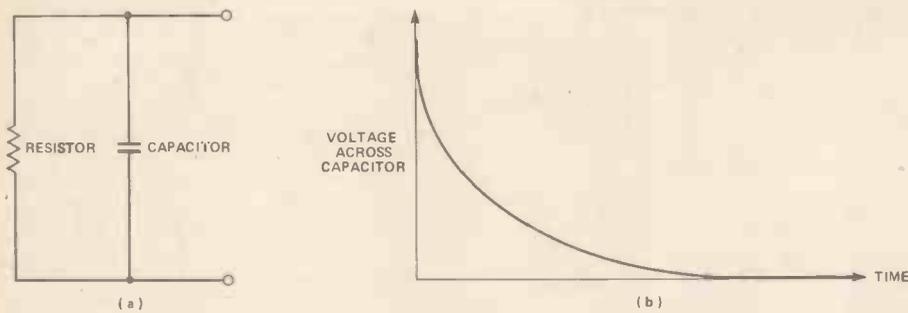


Figure 14. Discharging a charged capacitor through a parallel resistor.

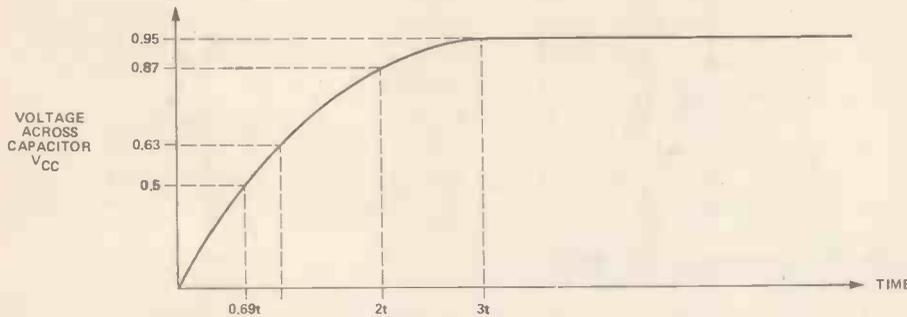


Figure 15. Important points on the exponential curve of a charging capacitor.

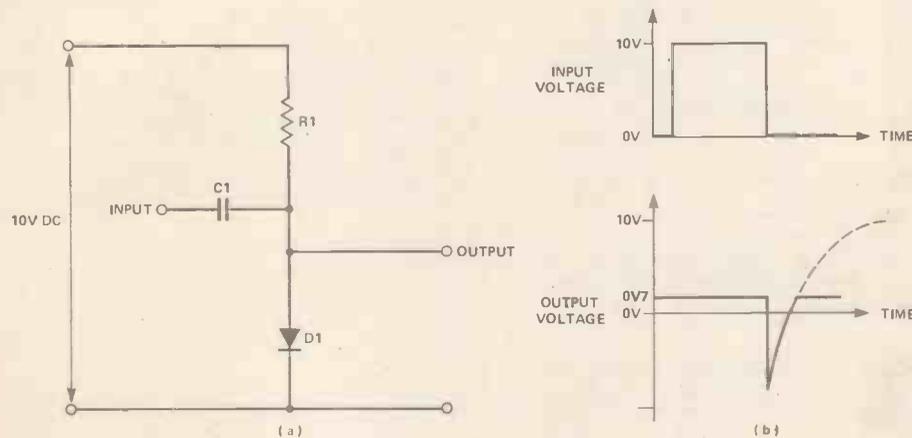


Figure 16a) Resistor/capacitor/diode (RCD) circuit b) Operating voltages of the RCD circuit.

Now, before we go back to the monostable we have to add a further component to the RC circuit — a diode. Figure 16a shows this RCD circuit and Figure 16b shows the input and resultant output waveforms. Normally the diode conducts, holding the output voltage at 0V7. When a positive going pulse is applied at the input the diode current is increased by the amount of the capacitor charging current, but the output voltage remains constant at 0V7. However, when the input voltage falls from a positive value to zero the output voltage also falls (because there is nowhere a large discharge current can flow) from 0V7 to -9V3. A discharge current now flows through R1 and the output voltage follows an exponential curve towards the supply voltage; however when the voltage reaches 0V7 the diode once again holds the voltage constant.

Monostable Circuit

At last we are now in a position to understand the operation of the monostable circuit of Figure 11. Capacitor C1, resistor R4, and the base-emitter diode junction of transistor TR2 form an RCD circuit identical to Figure 16a. Normally therefore, transistor TR1 is held on by the base current through R4. The output of transistor TR2 is low, which holds transistor TR1 initially off. The collector of transistor TR1 is therefore high (ie, 10 volts) so the initial voltage across capacitor C1 is 9V3 (ie, 10V - 0V7).

When an input pulse is applied, transistor TR1 turns on taking the collector low. The base of transistor TR2 goes low by the same amount (because of the action of the RCD circuit), turning transistor TR2 off. As transistor TR2 turns off, its collector goes high and the

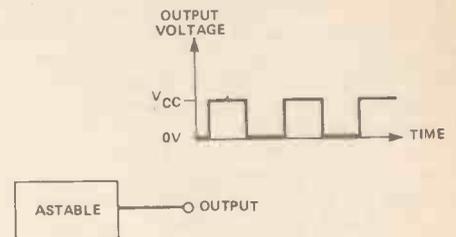


Figure 17. Block diagram of an astable.

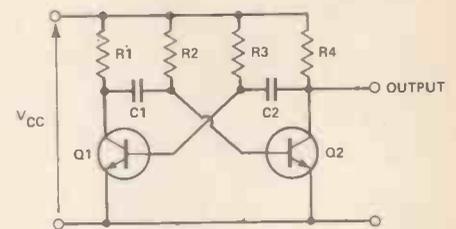


Figure 18. Astable formed by two transistors and two RCD circuits. The diodes of each RCD circuit are formed by the base-emitter junction of the transistors.

loop (via resistor R5) holds transistor TR1 on. Once this occurs the original input pulse can be removed and transistor TR1 stays on until transistor TR2 turns on again. This will happen when the capacitor, discharging through resistor R4 allows the base voltage to rise high enough to gain turn on transistor TR2. The circuit will then return to its initial state.

You should be able to see that the length of time the circuit remains in its unstable state (ie, with transistor TR2 off) is totally dependent on the values of resistor R4 and capacitor C1.

The final circuit in this group of three is the *astable*: it has no stable states and constantly oscillates ie, changes, between the two logic states 0 and 1. The block diagram of Figure 17 shows the basic action, and Figure 18 shows how the circuit can be made using two transistors and two RCD time delay circuits. Each transistor turns on the next after the time delay of its RCD circuit and the whole process repeats itself indefinitely. The frequency of oscillation depends upon the time constants of the two RCD time delays so by varying resistor or capacitor values we can make the circuit switch as fast or as slow as we wish.

Linear Circuits

The other main group of semiconductor circuits consists of transistors operating only in their linear range ie, all input and output voltages are somewhere in between the two extremes of logic 0 and logic 1, so we call them linear circuits.

Simplest of these circuits was the final circuit of last month's All About Electronics: the inverting AC current

amplifier — reproduced in Figure 19. If you remember (if not — why not?) the transistor amplifies an input current with a gain of β , up to a maximum collector current determined by the collector resistor R1.

As the emitter of the transistor is connected to the 0V supply rail (which is sometimes known as the common rail) the circuit is often called a *common emitter amplifier*.

Now, this circuit is very clever and useful but it does have one major drawback. Consider the case of a stereo high fidelity amplifier for example. Each channel of the amplifier is formed by such a circuit — obviously, I've oversimplified things somewhat here; no amplifier consists of a single stage but the effect is the same. Unless the transistor β of each channel is identical, one channel is always going to be louder than the other. And, even if two transistors with identical β could be found, it often happens that a transistor's β varies with time. Obviously this simple circuit is not acceptable as it stands. So what can we do to make it acceptable? Well, one simple way to add a resistor between the emitter and common rail, as in Figure 20. In this way the emitter current, I_e , which equals the base current plus the collector current, flows through the emitter resistor, setting up a voltage across the resistor i_e :

$$I_e = I_b + I_c$$

and,

$$V_{R4} = I_e \times R4$$

If we assume (because I_b can be neglected with respect to I_c) that $I_e = I_c$ and that $V_{R4} = V_{in}$ (actually there is 0.7V difference but that is close enough to show the principle!) then we can see that:

$$V_{out} = V_{cc} - I_c \times R1$$

and,

$$I_c = \frac{V_{in}}{R4}$$

So,

$$V_{out} = V_{cc} - V_{in} \frac{R1}{R4}$$

Now, before going any further, let's consider the voltage terms here. V_{out} and V_{in} are the output and input AC voltages concerned with the circuit. But V_{cc} is the DC power supply voltage. We don't want to have to worry about this DC voltage and so to eliminate it from the calculation we add a component at the input and output which will block (ie prevent) all DC terms, but pass all AC ones. You will remember from earlier on in this series such a component is a capacitor (Figure 21).

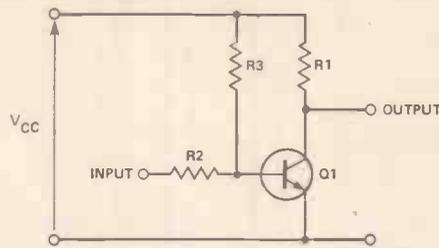


Figure 19. AC current amplifier formed by a single transistor.

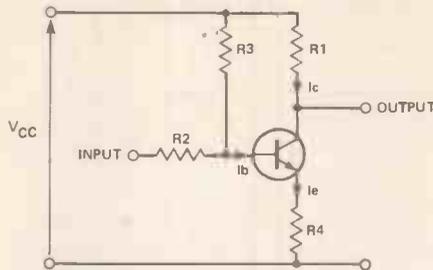


Figure 20. Common emitter amplifier with feedback.

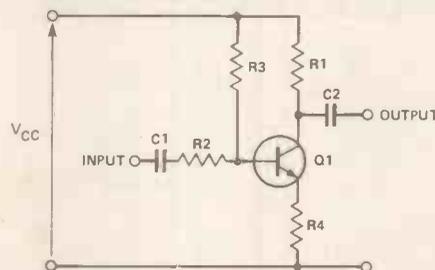


Figure 21. Common emitter amplifier with feedback and DC blocking capacitors.

Blocking the DC term, our relationship between input and output reduces to:

$$V_{out} = -V_{in} \frac{R1}{R4}$$

so the gain of the circuit,

$$\frac{V_{out}}{V_{in}} = - \frac{R1}{R4}$$

the minus sign indicates an inverting function. That is, the gain of the circuit now no longer depends on the transistor β , but on the simple ratio between two resistors. Thus, we can set the gain of the amplifier to whatever value we like (as long as the transistor operates within its linear range) simply by changing resistor value.

Feedback

Adding a resistor into the circuit so that the gain of the amplifier is related to the

resistor value is known as adding feedback. Remember the term because you'll see a lot of it over the coming months. Feedback is one of the most important concepts in linear electronics and different methods of applying it in the various circuits we look at and discuss, allow the circuits to function in varied ways — not just as straightforward amplifiers for high fidelity amplifiers etc.

Another single transistor linear circuit is shown in Figure 22. Instead of the emitter being common to a power supply rail, this time the collector is, so we call this circuit a common collector amplifier.

The voltage at the emitter of the transistor, V_e , is the voltage at the base, V_b , minus the base-emitter junction voltage i_e :

$$V_e = V_b - 0.7V$$

The DC blocking capacitors remove all DC voltage terms, leaving us with the simple relationship:

$$V_e = V_b$$

in other words:

$$V_{out} = V_{in}$$

In this circuit, the transistor is a non-inverting, unity gain amplifier. The emitter voltage is said to follow the base voltage and so the circuit is often called an emitter follower. The current gain is however, similar to the common emitter amplifier. Emitter current is equal to the base current plus the collector current:

$$I_e = I_b + I_c$$

But

$$I_c = \beta \times I_b$$

so,

$$I_e = I_b + \beta \times I_b \\ = I_b (\beta + 1)$$

so the current gain:

$$= \frac{I_e}{I_b} = \beta + 1$$

As β is normally large (ie 50), the current gain can be considered to be β .

The resistance of the circuit's input (ie input voltage over input current) is obviously β times the output resistance. Actually, when dealing with transistors we normally are considering AC input and output voltages so instead of talking about input and output resistances we use impedances (remember from the August issue of Hobby Electronics, impedance can be thought of as AC resistance).

For these reasons, emitter follower circuits are often used as buffers, where a large current is required when only a small current output is available from a preceding circuit. The high impedance input ensures that the preceding circuit is not affected, or dampened, in any way by the low impedance output of the emitter follower.

All This And Many More

There are many, many more transistor circuits, digital and linear, logic and amplifiers — far too many to discuss in any more detail than we've covered so far — and far too many to be able to discuss them all. But, being transistor based, their functions and operations are similar to the circuits we've already looked at. One or two more such circuits will crop up, no doubt, over the next few months, but even then we won't be considering them in any depth. We know as much about the basics of semiconductors as we need to know and any more circuits we look at will only be considered in terms of the job they perform rather than the way they perform it.

In this way we can look at very complex circuits and yet know how to use them without having to calculate how every part of the circuit works before being able to use it. From now on we will consider the action of circuits in block diagram form only, without going down to component level. We have already seen an example of this in the logic gate symbols of Figures 4 and 8. Although we know that transistors and other components form the actual circuits of say a NOR gate, we don't have to know what families of components are involved at all to understand circuit action: the block diagram (ie, circuit

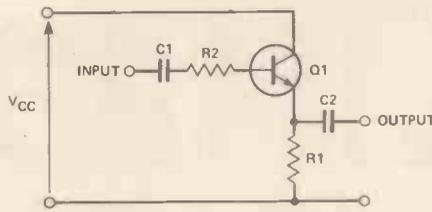


Figure 22. Common collector amplifier (emitter follower) formed by a single transistor.

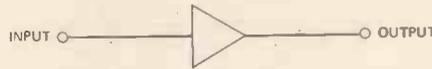


Figure 23. Symbol of a non-inverting amplifier.

symbol) is all we used. Another example is shown in Figure 23 of a non-inverting amplifier. The symbol is similar to the inverter of Figure 4 but of course without the inverting ring on the output. Both circuits are, in fact, buffers — hence the triangular shape which is used in both digital and linear circuits.

This method of using block diagrams to stand for a complex circuit is enhanced by the use in electronics of integrated circuits (ICs). ICs are simply a collection of individual components

formed in a circuit in a single body. Often, the circuit within the body is not complete and a few separate components — perhaps a couple of resistors or capacitors need to be connected to it to make it work. In this way the IC can be a general purpose but the addition of a few specific components can define the exact operation of the complete circuit.

Most ICs are constructed so that all connections to and from the circuit are made via legs on each side of the body, in two rows. For this reason the shape is classified as being dual-in-line (DIL). The individual legs of each row are 0.1 in (2.5mm) apart and the rows of the legs are 0.3in (7.5mm) apart. These dimensions are standard for most ICs with up to about twenty legs: above that the body size increases so that the rows of legs are 0.6in (15mm) apart.

With present miniaturisation techniques the circuits involved, (linear or digital), in some types of IC can be very complex. For example it is common to have an IC with a hundred or so transistors within its body. Some of the more recently introduced ICs have thousands, and in fact, some ICs have as many as 100,000 transistors in the one body.

Will it ever end?

HE

AN OSCILLOSCOPE & FUNCTION GENERATOR

IN ONE PRECISION INSTRUMENT

FOR JUST £295 plus VAT



Made in Britain

You can now buy a dual trace oscilloscope and function generator and have it delivered anywhere in the UK mainland for less than £300.

Or, if you have a Scopex dual trace scope, the function generator can be supplied separately for you to fit.

Only Scopex offers this total add-on compatibility.

SCOPEXTRA FG Combined oscilloscope and function generator £295 plus VAT.

FG4, FG14/25 Function generator for mounting on Scopex dual trace scopes £69 plus VAT.

FG1 stand-alone function generator in instrument case £79 plus VAT.

SCOPEX

the oscilloscope people

Scopex Instruments Limited, Pixmore House,
Pixmore Avenue, Letchworth, Herts SG6 1HZ
Telephone (04626) 72771

BUYLINES

Para-Q

A full kit of parts for the Para-Q parametric amplifier is available from Digisound Limited, 14/16 Queen Street, Blackpool, Lancs FY1 1PQ, priced at £8.50 for a single unit and £8.15 for additional units ordered at the same time.

The price includes postage, packaging and VAT, and the kit includes the PCB and all the components shown in the Parts List.

A case for the Para-Q has not been specified, since the system is expandable to as many boards as are needed for a particular application. For most situations a standard ABS plastic box would be suitable, but a metal box should be used if noise or hum is a problem, eg if a mains power supply is used and located close to the Para-Q unit.

Dual PSU

All the components for the unit are easily obtained and shouldn't pose any great problems. The case for the prototype, a plain aluminium box, was

from Greenweld Electronics, who can also supply most of the other components. The transformer, however, can be had from either **Ambit, Rapid or Watford Electronics.**

Interior Light Delay

A little persistence, possibly even some ingenuity, might be needed to obtain the low value resistors used in this project. The only other unfamiliar component is the 1N916 diode, a low capacitance version of the better known 1N914. It should be used for preference, and is stocked by **Maplin Electronics**, who can also supply the hard-to-find resistors. Note that although R5 is listed as 100 ohms, 2.5 watts wirewound, any type of 100R resistor rated at better than 2.5W will suit, though the higher wattage types may not fit neatly on the printed circuit board.


Windscreen Wiper Delay

Several unusual type numbers are in the parts list for this project, but most of them are stocked by major retailers.

The exception is D3, the MR751 diode; no direct equivalent for this device has been found however a similar type, the MR752 can be ordered from RS components through your local supplier. Alternatively type R250B, stocked by **Watford Electronics**, meets the required specification of 6A forward current and 100V maximum reverse voltage, and is a PCB mounting type. Other 6A diodes are available, but most are stud mounting and therefore not suitable for the PCB design.

All other components are also available from Watford.


Beasties

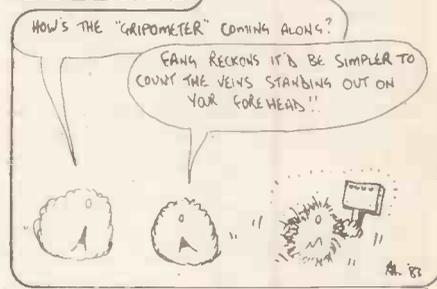

TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

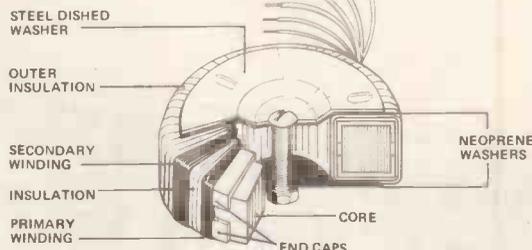Our large standard range is complemented by our **SPECIAL DESIGN** section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



15 VA 62 x 34mm 0.35Kg Regulation 19%	50 VA 80 x 35mm 0.9Kg Regulation 13%	120 VA 90 x 40mm 1.2Kg Regulation 11%	225 VA 110 x 45mm 2.2Kg Regulation 7%	500 VA 140 x 60mm 4Kg Regulation 4%																																																																																																																																																
<table border="1"> <thead> <tr> <th>SERIES</th> <th>SECONDARY No</th> <th>Volts</th> <th>RMS Current</th> </tr> </thead> <tbody> <tr><td>0x010</td><td>6+6</td><td>1.25</td><td></td></tr> <tr><td>0x011</td><td>9+9</td><td>0.83</td><td></td></tr> <tr><td>0x012</td><td>12+12</td><td>0.63</td><td></td></tr> <tr><td>0x013</td><td>15+15</td><td>0.50</td><td></td></tr> <tr><td>0x014</td><td>18+18</td><td>0.42</td><td></td></tr> <tr><td>0x015</td><td>22+22</td><td>0.34</td><td></td></tr> <tr><td>0x016</td><td>25+25</td><td>0.30</td><td></td></tr> <tr><td>0x017</td><td>30+30</td><td>0.25</td><td></td></tr> </tbody> </table> <p>(encased in ABS plastic)</p>	SERIES	SECONDARY No	Volts	RMS Current	0x010	6+6	1.25		0x011	9+9	0.83		0x012	12+12	0.63		0x013	15+15	0.50		0x014	18+18	0.42		0x015	22+22	0.34		0x016	25+25	0.30		0x017	30+30	0.25		<table border="1"> <thead> <tr> <th>30 VA 70 x 30mm 0.45Kg Regulation 18%</th> <th>80 VA 90 x 30mm 1Kg Regulation 12%</th> <th>160 VA 110 x 40mm 1.8Kg Regulation 8%</th> <th>300 VA 110 x 50mm 2.6Kg Regulation 6%</th> <th>625 VA 140 x 75mm 5Kg Regulation 4%</th> </tr> </thead> <tbody> <tr><td>1x010</td><td>6+6</td><td>2.50</td><td></td><td>9x017</td><td>30-30</td><td>10.41</td></tr> <tr><td>1x011</td><td>9+9</td><td>1.66</td><td></td><td>9x018</td><td>35+35</td><td>8.92</td></tr> <tr><td>1x012</td><td>12+12</td><td>1.25</td><td></td><td>9x026</td><td>40+40</td><td>7.81</td></tr> <tr><td>1x013</td><td>15+15</td><td>1.00</td><td></td><td>9x025</td><td>45+45</td><td>6.94</td></tr> <tr><td>1x014</td><td>18+18</td><td>0.83</td><td></td><td>9x033</td><td>50+50</td><td>6.25</td></tr> <tr><td>1x015</td><td>22+22</td><td>0.68</td><td></td><td>9x042</td><td>55+55</td><td>5.68</td></tr> <tr><td>1x016</td><td>25+25</td><td>0.60</td><td></td><td>9x028</td><td>110</td><td>5.68</td></tr> <tr><td>1x017</td><td>30+30</td><td>0.50</td><td></td><td>9x029</td><td>220</td><td>2.84</td></tr> <tr><td></td><td></td><td></td><td></td><td>9x030</td><td>240</td><td>2.60</td></tr> </tbody> </table>	30 VA 70 x 30mm 0.45Kg Regulation 18%	80 VA 90 x 30mm 1Kg Regulation 12%	160 VA 110 x 40mm 1.8Kg Regulation 8%	300 VA 110 x 50mm 2.6Kg Regulation 6%	625 VA 140 x 75mm 5Kg Regulation 4%	1x010	6+6	2.50		9x017	30-30	10.41	1x011	9+9	1.66		9x018	35+35	8.92	1x012	12+12	1.25		9x026	40+40	7.81	1x013	15+15	1.00		9x025	45+45	6.94	1x014	18+18	0.83		9x033	50+50	6.25	1x015	22+22	0.68		9x042	55+55	5.68	1x016	25+25	0.60		9x028	110	5.68	1x017	30+30	0.50		9x029	220	2.84					9x030	240	2.60	<table border="1"> <thead> <tr> <th>400 VA 110 x 45mm 2.2Kg Regulation 7%</th> <th>625 VA 140 x 75mm 5Kg Regulation 4%</th> </tr> </thead> <tbody> <tr><td>6x012</td><td>12+12</td><td>9.38</td></tr> <tr><td>6x013</td><td>15+15</td><td>7.50</td></tr> <tr><td>6x014</td><td>18+18</td><td>6.25</td></tr> <tr><td>6x015</td><td>22+22</td><td>5.11</td></tr> <tr><td>6x016</td><td>25+25</td><td>4.50</td></tr> <tr><td>6x017</td><td>30+30</td><td>3.75</td></tr> <tr><td>6x018</td><td>35+35</td><td>3.21</td></tr> <tr><td>6x026</td><td>40+40</td><td>2.81</td></tr> <tr><td>6x025</td><td>45+45</td><td>2.50</td></tr> <tr><td>6x033</td><td>50+50</td><td>2.25</td></tr> <tr><td>6x028</td><td>110</td><td>2.04</td></tr> <tr><td>6x029</td><td>220</td><td>1.02</td></tr> <tr><td>6x030</td><td>240</td><td>0.93</td></tr> </tbody> </table>	400 VA 110 x 45mm 2.2Kg Regulation 7%	625 VA 140 x 75mm 5Kg Regulation 4%	6x012	12+12	9.38	6x013	15+15	7.50	6x014	18+18	6.25	6x015	22+22	5.11	6x016	25+25	4.50	6x017	30+30	3.75	6x018	35+35	3.21	6x026	40+40	2.81	6x025	45+45	2.50	6x033	50+50	2.25	6x028	110	2.04	6x029	220	1.02	6x030	240	0.93	<p>Why a Toroid?</p> <ul style="list-style-type: none"> * Smaller size & weight to meet modern 'slimline' requirements. * Low electrically induced noise demanded by compact equipment. * High efficiency enabling conservative rating whilst maintaining size advantages. * Lower operating temperature. <p>Why ILP?</p> <ul style="list-style-type: none"> * Ex-stock delivery for small quantities. * Gold service available. 21 days manufacture for urgent deliveries. * 5 year no quibble guarantee. * Realistic delivery for volume orders. * No price penalty for call off orders.
SERIES	SECONDARY No	Volts	RMS Current																																																																																																																																																	
0x010	6+6	1.25																																																																																																																																																		
0x011	9+9	0.83																																																																																																																																																		
0x012	12+12	0.63																																																																																																																																																		
0x013	15+15	0.50																																																																																																																																																		
0x014	18+18	0.42																																																																																																																																																		
0x015	22+22	0.34																																																																																																																																																		
0x016	25+25	0.30																																																																																																																																																		
0x017	30+30	0.25																																																																																																																																																		
30 VA 70 x 30mm 0.45Kg Regulation 18%	80 VA 90 x 30mm 1Kg Regulation 12%	160 VA 110 x 40mm 1.8Kg Regulation 8%	300 VA 110 x 50mm 2.6Kg Regulation 6%	625 VA 140 x 75mm 5Kg Regulation 4%																																																																																																																																																
1x010	6+6	2.50		9x017	30-30	10.41																																																																																																																																														
1x011	9+9	1.66		9x018	35+35	8.92																																																																																																																																														
1x012	12+12	1.25		9x026	40+40	7.81																																																																																																																																														
1x013	15+15	1.00		9x025	45+45	6.94																																																																																																																																														
1x014	18+18	0.83		9x033	50+50	6.25																																																																																																																																														
1x015	22+22	0.68		9x042	55+55	5.68																																																																																																																																														
1x016	25+25	0.60		9x028	110	5.68																																																																																																																																														
1x017	30+30	0.50		9x029	220	2.84																																																																																																																																														
				9x030	240	2.60																																																																																																																																														
400 VA 110 x 45mm 2.2Kg Regulation 7%	625 VA 140 x 75mm 5Kg Regulation 4%																																																																																																																																																			
6x012	12+12	9.38																																																																																																																																																		
6x013	15+15	7.50																																																																																																																																																		
6x014	18+18	6.25																																																																																																																																																		
6x015	22+22	5.11																																																																																																																																																		
6x016	25+25	4.50																																																																																																																																																		
6x017	30+30	3.75																																																																																																																																																		
6x018	35+35	3.21																																																																																																																																																		
6x026	40+40	2.81																																																																																																																																																		
6x025	45+45	2.50																																																																																																																																																		
6x033	50+50	2.25																																																																																																																																																		
6x028	110	2.04																																																																																																																																																		
6x029	220	1.02																																																																																																																																																		
6x030	240	0.93																																																																																																																																																		


Prices including P&P and VAT

VA	Size	£	VA	Size	£
15	0	6.79	160	5	11.67
30	1	7.58	225	6	13.64
50	2	8.60	300	7	14.87
80	3	9.64	500	8	19.30
120	4	10.51	625	9	22.62

For 110V primary insert "0" in place of "X" in type number.
For 220V primary (Europe) insert "1" in place of "X" in type number.
For 240V primary (UK) insert "2" in place of "X" in type number.
IMPORTANT: Regulation - All voltages quoted are FULL LOAD.
Please add regulation figure to secondary voltage to obtain off load voltage.

Mail Order - Please make your crossed cheques or postal orders payable to ILP Electronics Ltd.

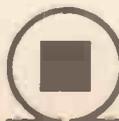Trade - We will open your credit account immediately upon receipt of your first order.



ILP ELECTRONICS LTD.

Post to: ILP Electronics Ltd., Dept. 5
Graham Bell House, Roper Close,
Canterbury, Kent. CT2 7EP
Tel: (0227) 54778 Telex: 965780

HENRY'S AUDIO ELECTRONICS

COMPUTERS • COMMUNICATIONS • TEST EQUIPMENT • COMPONENTS

VISIT OR PHONE • OPEN 6 DAYS A WEEK • ALL PRICES INC VAT



THERMAL MATRIX & LINE PRINTER

SAVE £57

COMPLETE WITH FULL HANDBOOK, 3 ROLLS PAPER
£129.95 inc. VAT
 £13.00 + VAT. (UK post etc £1.05) (List approx. £187)
 150 to 180 LPM • Full 96 CH ASC II • 40 CPL • 280 Dots P/L
 Auto-underline • 50 Graphic Symbols • Back Space • Sell
 Test • VU/HDR TABS • 7 x 10 Matrix • 4.4" Wide Paper
 Bidirectional • 220/240 V AC • Size Approx. 9.8 x 2.8 x 7.2"
 SUITABLE FOR: TANDY • BBS • ORIC • NASCOM • GEMINI •
 ACORN • NEW BRAIN • DRAGON • etc. etc.
 (Your enquiries invited)
 (Interface unit with leads £15 - state model).

'CHERRY' ADD-ON KEYPAD

A compact 16 button keypad suitable for use with cherry keyboard to extend its functions. Supplied brand new with data. A 4 x 4 non-encoded single mode keyboard.

£5.95 (Inc. V.A.T.)
 UK C/P Free



SANYO DM2112 HIGH RESOLUTION MONITOR

12" green display.
 Composite video:
 1280 characters:
 Over 15 MHz 8/W:
 240V AC 34 w:
 16 x 11 1/2" x 12 1/2"
 Alphanumeric and
 Graphic display: Usually **£89.95 - £99.95**
 Price **£69.95** (UK C/P & ins £2.05)



I.T.T. 2020 CABINET


Complete PROFES-
 SIONAL Case
 beautifully constructed
 with cut out for one
 'CHERRY' keyboard, plus
 ample room to house a COMPLETE SYSTEM and power
 supply. Complete with (strings) (Case top detachable). Unit is
 silver-grey in colour. Robust construction. Slipping front
 with side ventilation. Ideal for NASCOM, ACORN, TANGERINE
 or your own system. Size 18" x 15 1/2" x 4 1/2" (front slopes).

£27.50 (inc. VAT) (UK C/P £2.50)



LOGIC PROBES

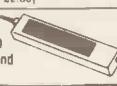LP10 10 MHz **£28.50**
 DLP50 50 MHz with carry case and
 accessories **£49.95**



HIGH VOLTAGE METER

Direct reading 0/40 KV.
 20K/Volt. **£23.00** (UK C/P 65p)



DIGITAL CAPACITANCE METER

0.1 pf to 2000 nfd LCD B ranges
DM6013 £52.75



TRANSISTOR TESTER

Direct reading PNP, NPN, etc.
TC1 £21.95
 (UK C/P 65p)



VARIABLE POWER SUPPLIES

(UK C/P £1.00)
 PP241 0/12/24V 0/1A **£35.00**
 PP243 3 amp version **£59.95**
 PS1307S 8/15V
 7 amp Irwin meter **£24.95**



FREQUENCY COUNTERS

PFM200A 200 MHz hand held pocket
 8 digit LED **£77.60**
 MET100 B digit LED bench 2 ranges 100 MHz **£102.35**
 MET600 B digit LED bench 3 ranges 600 MHz **£132.25**
 MET1000 8 digit LED 3 ranges 1 GHz **£182.85**
 TF040 8 digit LCO 40 MHz. Thandar **£126.50**
 TF200 3 digit LCO 200 MHz. Thandar **£166.75**

DIGITAL MULTIMETERS



■ with case (rotary switches)
 + Side button - case **£2.95**
 KD25C ■ 13 range 0.2A 0C.
 2 meg ohm **£23.50**
 KD30S ■ 16 range 10A 0C.
 2 meg ohm **£26.95**
 KD30C ■ 26 range 1A
 AC/OC 20 meg ohm **£29.50**
£33.50
 K055C ■ 28 range 10A AC/OC 20 meg ohm **£33.24**
 Metex 3000 ■ 30 range 10A AC/OC.
 20 meg ohm **£34.40**
 6010 ■ 28 range 10A AC/OC 20 meg ohm **£41.30**
 7030 4- AS6010 high acc. 0.1% basic
 KD615 ■ 16 range 10A 0C 2 meg plus
 Hfe tester **£39.95**
£29.95
 SIFAM 2200B 21 range 2A AC/OC 20 meg
 Bench Models
 TM355 29 range LEO 10A AC/OC 20 meg.
 Thandar **£86.25**
 TM356 26 range LCO 10A AC/OC 20 meg.
 Thandar (Replaces TM353) **£97.75**
 TM351 29 range LCO 10A AC/OC 20 meg.
 Thandar **£120.75**
 SIFAM 2500 24 range LCO 2A AC/OC 20 meg. **£79.95**
 ALSO IN STOCK Thurlby, Metrix and Beckman.
 Professional series Incl. True Rms. etc.

MULTIMETERS (UK C/P 65p)

C7081 50 K/Volt range doubler. 10A 0C.
 Total 36 ranges. Special Offer **£12.50**
 HM102BZ 20K/V 10A 0C 22
 range & cont. buzzer **£13.50**
 TMK500 23 ranges 30K/V.
 12A 0C plus cont. buzzer **£23.95**
 NM56R 20K/V. 22 range pocket
 B30A 26 range 30K/V. 10A AC/OC overload
 protection, etc. **£23.95**
 360TR 23 range 100K/V. Large scale 10A
 AC/OC plus Hfe **£39.95**
 AT2100 31 range 100K/V deluxe. 12A
 AC/OC **£33.50**
 AT1020 18 range 20K/V. Deluxe plus Hfe
 tester **£18.95**
 YN360TR 19 range 20K/V plus Hfe tester **£15.95**



SIGNAL GENERATORS (220/240V AC)


FUNCTION: All sine/square/triangle/TTL etc.
 TG100 1Hz-100 KHZ **£90.00**
 TG101 1Hz-200 KHZ **£113.85**
 TG102 0.2Hz-2 MHz **£166.75**
 PULSE
 TG105 Various facilities 5 Hz-5 MHz **£97.75**
 AUDIO: Multiband Sine/Square
 LA627 10 Hz to 1 MHz **£90.85**
 AG202A 20 Hz to 200 KHZ (list £94.50) **£83.50**
 RA6 120A 10Hz-1MHz Low Distortion **£159.85**
 RF
 SG402 100 KHZ to 30 MHz (list £79.50) **£69.50**
 LSG17 100 KHZ to 150 MHz **£79.35**

OSCILLOSCOPES

Full specification any model
 on request, SAE by post.
 'HM' Series NAMEG: 'SC'
 THANDAR: 'CS' TRIO:
 '3' CROTECH 'V' HITACHI
 SINGLE TRACE UK C/P £3.00
 3030 15 MHz 5mv. 95mm tube plus component
 tester C/P £3.00 **£177.10**
 SC110A Miniature 10 MHz battery portable
 Post free **£171.00**
 HM103 15 MHz 2mv 6 x 7 display plus
 component tester C/P £3.00 **£181.70**
 ■ Optional carry case £6.84 AC adaptor £6.69
 Nicads £12.50
 DUAL TRACE (UK C/P £4.00)
 HM203/4 Dual 20 MHz plus component
 tester **£303.60**
 CS1562A Dual 10 MHz (list £321.00) **£269.50**
 3131 Dual 15 MHz - component tester **£276.00**
 CS1566A Dual 20 MHz All facilities (list £401.35) **£349.50**
 HM204 Dual 20 MHz plus component tester
 sweep delay **£419.75**
 HM705 Dual 70 MHz sweep delay **£676.00**
 V212 Dual 20 MHz **£399.25**
 V222 Dual 20 MHz plus extra facilities **£391.00**
 V402 Dual 40 MHz portable **£586.50**
 V203F Dual Trace 20 MHz sweep delay **£408.25**
 V134 Dual Trace 10 MHz storage **£1092.50**



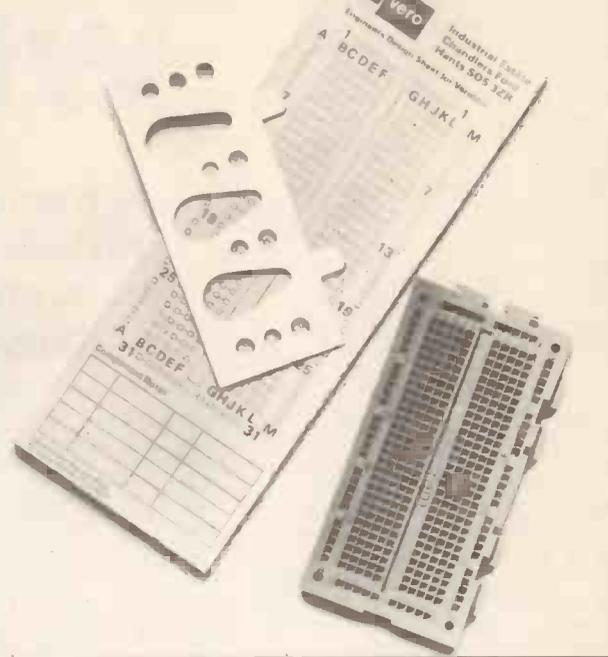Build and test your own circuit with the New Verobloc Kit



Try the new prototyping method of building and testing circuits with the British-made Verobloc kit. It consists of:

1. Verobloc.
2. A pad of design sheets for planning the circuits.
3. A component mounting panel for the larger components, i.e. switches, etc.

You can expand the circuit area by simply interlocking two or more Veroblocs and, of course, with normal usage, they can be used time and time again without damaging contacts or component leads. The glass nylon material is virtually unbreakable and able to withstand temperatures from -60°C to +120°C.

So take advantage of our special price of £5 per kit (including VAT) by completing the coupon below, or telephone (04215) 62829 (24 hours). This offer closes December 31st, 1983.

OUR NEW CATALOGUE CONTAINING OVER 150 NEW PRODUCTS IS AVAILABLE FROM MID OCTOBER.



BICC Vero Electronics Limited,
 Retail Dept., Industrial Estate,
 Chandlers Ford, Hampshire,
 SO5 3ZR.

I wish to purchase _____ Verobloc kit/s
 at £5 per kit inclusive of VAT for a total of £ _____
 I enclose my cheque/postal order or Debit my
 Access/Barclaycard No. (Delete where appropriate).

Name: _____
 Address: _____
 Postcode: _____

THIS UNIT is suitable for all negative earth single or dual speed wipers. It is designed to replace the slow speed with a delayed-action wipe of between zero and 30 seconds. The delay is controlled with a potentiometer either on the dash or steering column, and the unit is switched on using the existing wiper switch. The fast and single shot functions (if fitted) are not affected by this circuit.

Connection of the unit is quite simple, involving only the breaking of the original slow speed connection to the motor and making connections to each side of the break, to the park switch and a suitable ground. This is all shown in the circuit diagram

Wiped Out

In order to understand how the delay circuit works it will be helpful to describe the normal function of the wiper circuit. A dual speed circuit is described, as fitted to almost all modern cars. However single speed wipers are functionally the same; just ignore the fast speed circuitry. Single wipe facilities are provided by biased switch action to the slow speed setting.

Figure 1 shows the circuit diagram of the wipers. It can be seen that there are three electrical components: the motor itself; the park switch, which is enclosed inside the motor casing; and the control switch on the dashboard or stalk on the steering column.

The motor has three connections: common connected to ground, and two power connections, one for each speed. The park switch is also part of the motor assembly and its function is to ensure that the wiper blades stop (park) in the correct position. The contacts are changeover type; the centre contact is grounded at the correct park position, but otherwise is connected to the supply.

Overall control of the wipers is produced by the driver operated switch. Initially this is in the park position and the wipers are also parked and in this state the motor is shortcircuited to ground. When either operating speed is selected the motor is powered directly through the switch and operates continuously. When the switch is returned to the park position, power is supplied via the 'run' contact until the park position is reached; then the motor is again shorted out and the wipers stop. By shorting the motor, its back EMF causes dynamic braking of the wipers so there is less overshoot.

When delayed wipers are installed the slow continuous running connection is interrupted and replaced by a momentary action switch — in this case a transistor switch. A simple timing circuit generates a pulse to drive this switch, providing current until the park switch contacts change over and the 'run' contact then provides the current. A diode is

WINDSCREEN WIPER DELAY

Tony Scragg

A minimum modification accessory for motors, this unit suits all negative earth cars and provides wiper delay times of between zero and thirty seconds.



required in this supply path to stop the switching transistor initially shorting to ground through the park switch (D3, in the complete circuit diagram). Both the switching transistor and the diode must have high power ratings because the transistor must handle the motor starting surge current while the diode carries the motor current for most of the "wipe".

The original wiper connection is used to provide power for the delay circuit, as can be seen, from the circuit diagram.

Circuit Description

The circuit is based on the 555 timer IC, connected in the astable mode. The timing capacitor, C2, is charged through R1 and discharged through RV1, giving the variable rate. The output of the 555 drives Q1 and Q2

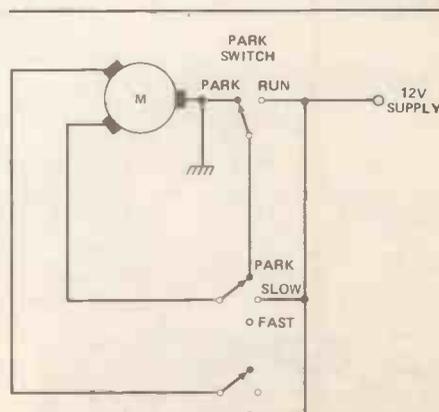


Figure 1. The wiper control circuit shown is conventional on most makes. The Delay unit is installed in the 'slow speed' circuit, but slow wipe is still possible by turning the delay to zero.

Parts List

RESISTORS

R1	10k
	1/4 watt
R2	100R
	1/2 watt
R3	330R
	1/2 watt
R4	20R
	2.5 watt wirewound

POTENTIOMETERS

RV1	1MR
	linear carbon

CAPACITORS

C1, 2	47u 16V
	tantalum
C3	100n
	ceramic

SEMICONDUCTORS

IC1	555
Q1	BFY51
Q2	MJ2955
ZD1	BZY88C9V1
D1	1N916
D2, 4	1N5401
D3	MR751

MISCELLANEOUS

PCB; optional case; wire, solder, nuts and bolts etc.

BUYLINES page 34

NOTES:
 IC1 = 555
 Q1 = BFY51
 Q2 = MJ2955
 ZD1 = BZY88C9V1
 D1 = 1N916
 D2,4 = 1N5401
 D3 = MR751

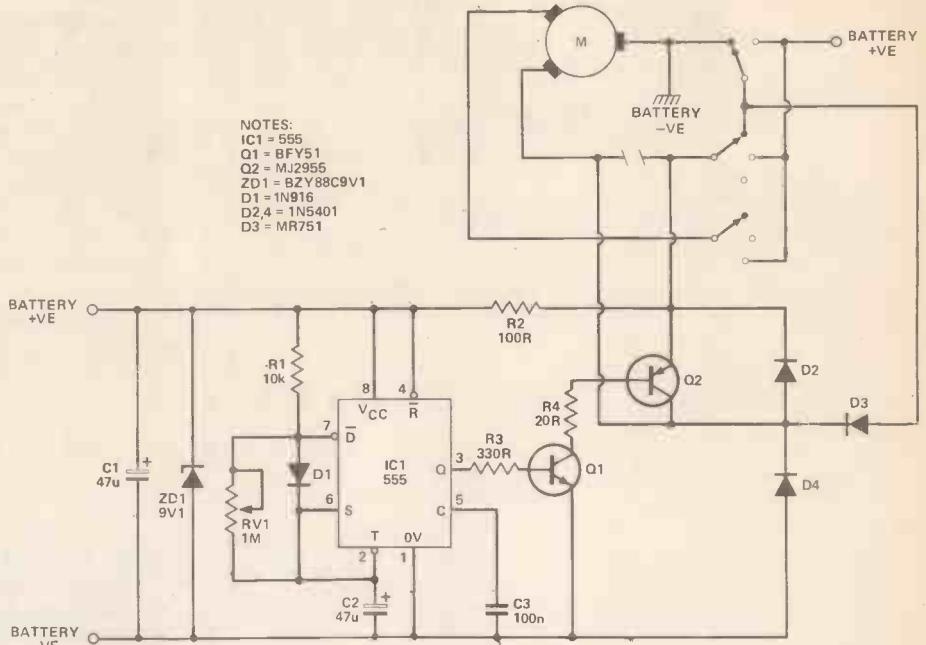


Figure 2. The circuit uses a 555 timer in the astable mode to provide the delay function. The unit is connected into the slow speed wiper circuit at the points indicated by the breaks.

which effectively perform the function of wiper on/off switch. The 555 output pulse is just long enough to move the wiper motor, causing the park switch to change over. The motor current then passes through D4 until the wipers are again in the park position. The armature is then shorted out by D3.

Diodes D2 and D4 provide clamping

to protect the output from the inductive motor load. R1, D1 and C1 provide a simple regulated power supply for the 555, giving protection against the noise on the car battery and possible high voltages — above the maximum for the 555 — under faulty charging conditions.

Construction and Installation

Construction is fairly straightforward as all components are mounted onto the PCB. The power transistor must be bolted down using metal nuts and bolts as this forms the electrical connection. Once assembled the board is enclosed in any small box — as the unit will be housed out of sight appearance is not too critical — with flying leads used to make connections with "chocolate block" type connectors. Three connections are required to the wiper circuit: the first step is to locate the wires concerned, either by consulting the workshop manual and comparing the circuit diagrams, or with a multimeter. If the latter approach is chosen set the multimeter to measure 12V and with the ignition on, operate the wipers. The slow speed connection will be at 12V as long as the wipers are operating; the park switch connection will have momentary 0V pulses in the level at the park position. Having located the correct wires, connections are made as per the circuit diagram; additional connection is required to a convenient grounding point. The potentiometer speed control connections are then made, having first found a convenient place to mount it within easy reach when driving!

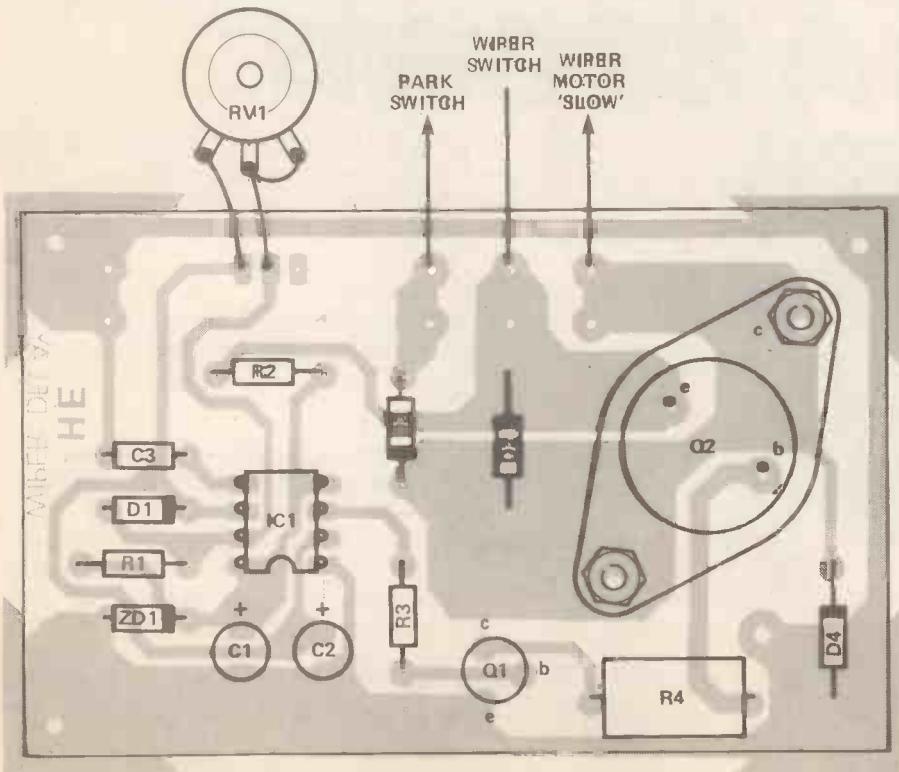


Figure 3. All components are mounted on the PCB except the control potentiometer, which can be mounted on the dashboard or steering column.

POSITRONICS

FOR PROFESSIONAL POWER SUPPLY UNITS



Positronics leads the field in providing an inexpensive range of professional specification power supply units, to industry and the enthusiast. Their features and performance being worthy of instruments twice their price, such as visual LED indication of mode, either constant current or constant voltage, ripple less than 1mv, voltage regulation better than 0.01%, load regulation better than 0.01% plus overload protected.

Also available in kit, they come complete with a step by step guide to problem free construction, placing them well within the pocket and competence of even the novice.

PSU 301

- * 0-30 volt output
- * 0-1 amp output continuous
- * Integral 6 range meter giving, 0-3v 0-100 mA 0-110v 0-300 mA 0-30v 0-1A
- * In Kit **£37.90**
- Built & Tested **£49.90**

PSU 301.5

- * 0-30 volt output
- * 0-1.5 amp output continuous
- * Integral 6 range meter giving, 0-3v 0-100 mA 0-10v 0-500 mA 0-30v 0-1.5 A
- * In Kit **£46.90**
- Built & Tested **£59.90**

From kit or built and tested you will have a highly controllable power source of exacting design, engineering and quality.

All prices inclusive of VAT. P&P £2.90. Please allow 21 days delivery.

POSITRONICS

Unit 4, New Enterprise III, Montgomery Street
Starbrook, Birmingham B11 1DS
Tel: 021-350 2267

PSU 303 (DVS)

- * 0-30 volt output
- * 0-3 amp output continuous
- * Integral 6 range meter giving, 0-3v 0-100 mA 0-10v 0-500 mA 0-30v 0-3A
- * Performance light weight toroidal transformer.
- * DVS Dual Voltage Switched Designed by Positronics this allows the unit to deliver twice the current of conventional variable power supply units.
- * In Kit **£58.90**
- Built & Tested **£74.80**

EVERYONE KNOWS

that TOOLMAIL offer the largest range of D.I.Y. tools available by post and that their 128 page colour catalogue contains over 2,000 quality tools.

But did YOU know that the range includes almost everything required by the Electronics Hobbyist: — Soldering Irons, Desolder Tools, Miniature Tools, PCB Holders, Drills, Pliers, Cutters, Tweezers, IC Extractors, Screwdrivers, Craft Knives, Hole Punches, Test Meters, Needle Files, Glue Guns, Nut Drivers, Wire Strippers, Component Formers, IC Inserters, De-solder Braid, and complete Electronics Tool Kits.

The catalogue normally cost £1 but is available FREE to Hobby Electronics readers. Send 50p postage for your personal copy.

SEE US AT '83

TOOLMAIL (1982) LTD
7 LONDON ROAD
SEVENOAKS
KENT TN13 1AH



TOOLMAIL

The world's best tool shop in your home

934's COMPANY 27's A CROWD.



LA83 27MHZ to 934MHZ TRANSVERTER KIT
Suggested Retail Price £399.95 including VAT (Kit comes complete with Bluebird 27MHZ Transceiver).

With the Grandstand LA83 934MHz Transverter Kit you can forget about irresponsible users and poor quality sound on the overcrowded 27MHz frequency.

Just connect the Bluebird 27MHz rig to the LA83 and a 934MHz antenna, switch to Channel 1 ...and you're on the new 934MHz Leisure Communication Band.

It's so easy! And you get a powerful 8 watts output with superb sound across the full range of channels.

For use either at home or in the car it's ideal not only for CB fans but for businessmen, amateur radio enthusiasts and many others. Send now for full details and the name of your nearest stockist.

GRANDSTAND

Design ahead of time.

Adam Imports Limited, A member of the Adam Leisure Group PLC
Ripon Way, Ripon Road, Harrogate, North Yorks., HG1 2AU. Telephone 0423 501151/6 Telex 57953 Adam G.



PRODUCTS BY

BEEWARE
LIMITED




MICRO-MIKE®

The Most Useful Inspection Tool You'll Ever Own . . .
 . . . And One Of The Least Expensive

The Powerful Pocket Microscope that's perfect for close inspection and measurement in all scientific work. Professional quality optics. Available in 10x to 50x magnifications. Scale reading 0.001 inch or 0.1mm. No moving parts. Easy to use. Always in focus. Rugged aluminium and glass construction. Virtually indestructible. Guaranteed for a lifetime of service.

Optional Micro-Lite attachment now available for full illumination in hard-to-see areas
 10x, 20x, 40x, 50x Models £10.35
 Measuring models with 0.1mm Scale £12.65
 Micro-Lite Clip on accessory light £8.60

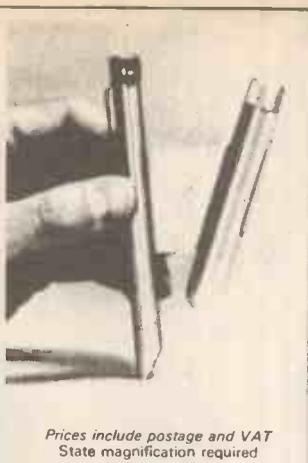Hirsh Jacobson Merchandising Co. Ltd.
 91 Marylebone High St., London W1M 3DE
 Tel. 01-935 4709



Prices include postage and VAT
 State magnification required

MEON ELECTRONICS

MULTIPURPOSE STORAGE BINS



Set of 10 high quality storage bins which can be wall mounted or stacked in almost any configuration. Each bin measures approx. 109mm wide x 53mm high x 100mm deep and is of high impact co-polymer plastic construction. Supplied with 2 wall mounting bars. Ideal for storing components or hardware in workshops, garage, home etc.

* EXCELLENT VALUE at only £4.95 per set (p&p £1.50)

SPECIAL OFFER - RECHARGEABLE BATTERIES

Manufactured by Saft or Gould - Limited stocks available.

*HP7 (AA) pencils 0.5Ahr	£0.85p ea.
*HP7 (AA) pencils 0.5Ahr tagged	£0.90p ea.
*HP7 (AA) pencils 0.5Ahr vented, quick charge 150mA	
3-5hrs	£1.00 ea.
*HP11 ('C' size) 1.2Ahr	£1.90 ea.
*HP11 ('C' size) 2.0Ahr	£2.25 ea.
*HP11 ('C' size) 2.0Ahr tagged	£2.30 ea.
*HP2 ('D' size) 1.2Ahr	£2.00 ea.
*HP2 ('D' size) 4.0Ahr	£3.25 ea.
*HP2 ('D' size) 4.0Ahr tagged	£3.30 ea.
*SUB 'C' 1.2Ahr	£1.45 ea.

Please add 10% for post and packing.

All goods fully guaranteed. Despatch by return of post.
 Prices apply U.K. only. Trade enquiries welcome.

All orders to:
MEON ELECTRONICS
 P.O. Box 34, Luton, Beds LU1 1LS
 Tel: Luton 28606

TWO GREAT HOBBIES ...IN ONE GREAT KIT!



The K5000 Metal Detector Kit combines the challenge of DIY electronics assembly with the reward and excitement of discovering Britain's buried past.

As a Metal Detector—the K5000 boasts the proven pedigree of C-Scope, Europe's leading detector manufacturer. As a Kit—simplified assembly techniques require little technical knowledge, and no complex electronic test equipment. All stages of assembly are covered in a finely-detailed 36 page manual.

Detector Features Analytical Discrimination & Ground Exclusion

Ask at your local Hobby/Electronics shop or use the coupon and send with your remittance to:
C-Scope International Ltd., PO Box 36, Ashford, Kent TN23 2LN

Please send me K5000 Kits @ £119.99(+£3.00 p+p) each.

Please debit my Barclaycard/Access £ _____
 I enclose Cheque/PO

Name _____

Address _____

BECOME A RADIO AMATEUR

Train now for the Radio Amateur Licence examination. No previous knowledge needed, only a few hours per week of home study for 3 to 6 months. Post coupon now for details or tel. 0734 51515 (24 hr service)



British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE brochure without obligation from:—
British National Radio & Electronics School
 READING, BERKS. RG1 1BR


Name _____

Address _____

HE/11/846

BLOCK CAPS PLEASE

UNIVERSAL NI-CAD BATTERY CHARGER

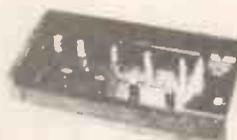

Only
£6.90
 Incl. of VAT

This unique charger will charge all of the standard consumer Ni-Cad batteries, i.e. AA, C, D, PP3. Batteries can be charged one at a time or any combination of 4 cylindrical cells, i.e. AA, C, D, plus one PP3. There is also a battery test facility to check if a battery needs charging.

RECHARGEABLE BATTERIES

HP2, 1.2v, 4.0AH	£3.95	HP7, 1.25v, 500mAH	£1.00
HP2, 1.2v, 1.2AH	£2.70	AAA, 1.2v, 180mAH	30p
HP11, 1.2V 1.2AH	£2.45	PP3, 8.4v 110mAH	£4.50

Please add £1 Postage and Packing
 All prices include VAT

CREDIT CARDS ACCEPTED

Call in or phone order through - Same day despatch

ENFIELD ELECTRONICS

208 Baker Street, Enfield
 Tel: 366 1873



FORWARD BIAS

Questions, answers and errata from readers and writers.

HE Auto-Tester

A number of errors have come to light in the circuit diagrams and in the PCB component overlay for this project, which was published in May, 1983.

On page 29 in Figure 1, the main circuit diagram, "R8" should read "R9" and "R9" should read "R8". R12, 2k7 was omitted from the circuit; it should have been shown connected between pin 12 and IC1d and the OV rail.

In Figure 3 on the same page, "LED4" should read "LED3", and in the text, the voltage referred to on the last line of the second paragraph

under the heading "Resistance" should be 1V2, not 1V3.

On the PCB overlay, Figure 6 on page 30, "LED2" should read "LED4" and "LED4" should read "LED2". The polarity of the LEDs were not indicated, but are shown below along with the corrected diagrams of Figure 1 and 3.

The printed circuit board is otherwise correct and there should be no further difficulty experienced by constructors of this versatile project for the motorist.

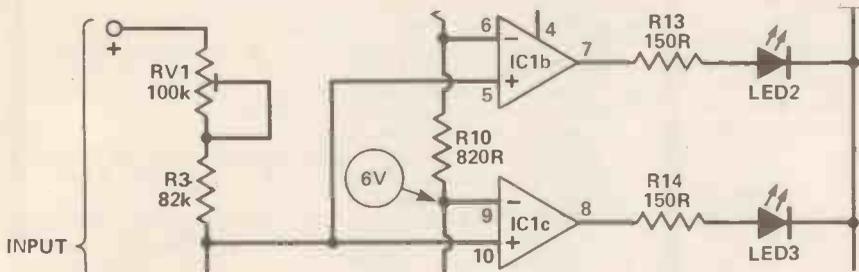


Figure 3


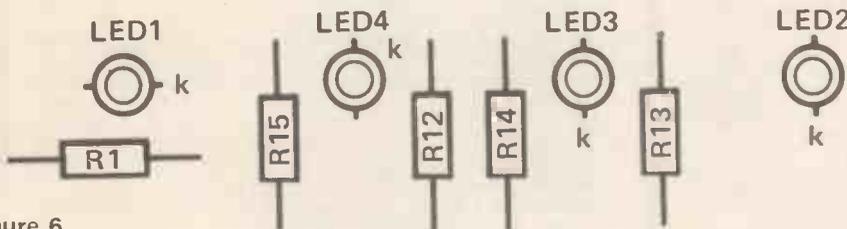


Figure 6

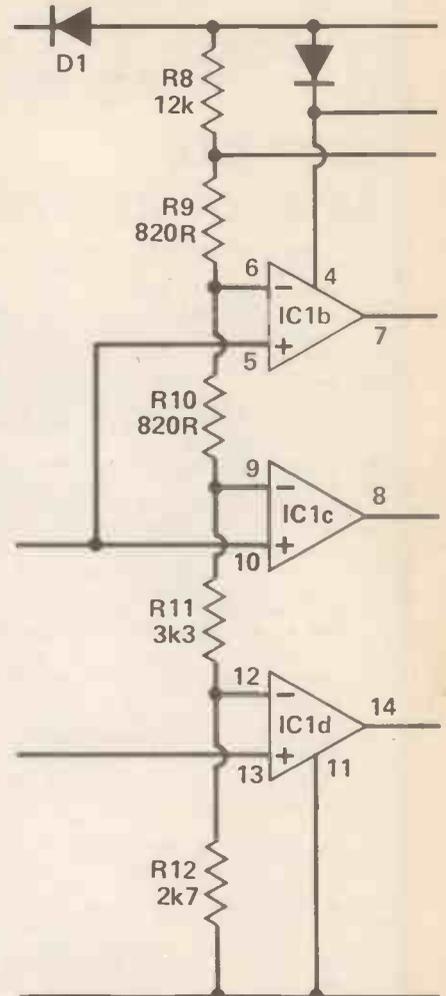

COLLECTED BOOBS

Continuing excerpts from the Hobby Electronics Errata Box

Infra Red Remote Control (HE February '80)


On page 32, the last paragraph of the second column of text should read: "(1) The EARTHS of the main input and output cables . . .", NOT the neutrals as this would be very dangerous.

Figure 2: R4 should be 1k0, not 1M0. The Parts List is correct.

5080 PSU Module (HE March '80)

Buylines (page 20) the transformer in our offer is now sold out. However, the Marshalls catalogue (1979/80) had a transformer type no. MT126FT which was suitable, using the 0-40 second-

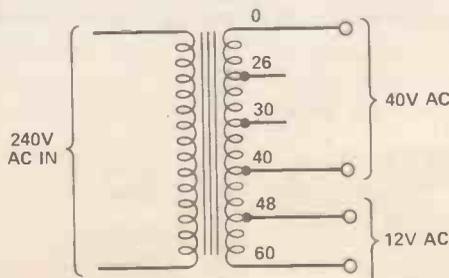aries for the high voltage supply and the 48-60 secondaries for the low voltage supply as shown here.



Another solution is to use two transformers: one 0-12V @ 100mA and one 20-0-20V @ 1A or 2A as required.

Electronic Ignition (HE April '80)

In Figure 1, on the secondary of T1, the OV tapping should be connected to the +V line immediately below.

In Parts List, the high voltage capacitors used have proved difficult to obtain in some places. Two replacements are suggested: the B32562 470n and B32562 1u0.

Rv1 should be 100k.

Speed Controller (HE April '80)

In the Parts List, 3BR should read 33R, C1, 8 should be 100n and not 100u, and C2 should also be 100n.

electronize

AUTO-ELECTRONIC PRODUCTS

KITS OR READY BUILT

TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION



IS
YOUR CAR

AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
 - ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains it from service to service.
 - ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs. where the ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engines maximum (even with 8 cylinders).
 - ★ Is the **PERFORMANCE SMOOTH**. The most powerful spark of Total Energy Discharge eliminates the "near misfires" whilst an electronic filter smoothes out the effects of contact bounce etc.
 - ★ Do the **PLUGS and POINTS** always need changing to bring the engine back to its best? Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.
 - ★ **TOTAL ENERGY DISCHARGE** is a unique system and the most powerful on the market - 3 1/2 times the power of inductive systems - 3 1/2 times the energy and 3 times the duration of ordinary capacitive systems. These are the facts:
Performance at only 6 volts (max. supply 16 volts)
 SPARK POWER — 140W, SPARK ENERGY — 36mJ
 SPARK DURATION — 500µS, STORED ENERGY — 135mJ
 LOADED OUTPUT VOLTAGE
 50pF load — 38kV, 50pF + 500k — 26kV
- We challenge any manufacturer to publish better performance figures. Before you buy any other make, ask for the facts, its probably only an inductive system. But if an inductive system is what you really want, we'll still give you a good deal.
- ★ All **ELECTRONIZE** electronic ignitions feature:
EASY FITTING, STANDARD/ELECTRONIC CHANGEOVER SWITCH, STATIC TIMING LIGHT and DESIGNED IN RELIABILITY (14 years experience and a 3 year guarantee).
 - ★ **IN KIT FORM** it provides a top performance system at less than half the price of comparable ready built units. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2uF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

Most **NEW CARS** already have electronic ignition. Update **YOUR CAR**

ELECTRONIZE ELECTRONIC CAR ALARM



HOW SAFE IS YOUR CAR ?

More and more cars are stolen each week and even a steering lock seems little help. But a car thief will avoid a car that will cause him trouble and attract attention. If your car has a good alarm system - well there are plenty of other cars to choose from.

LOOK AT THE PROTECTION AN ELECTRONIZE ALARM CAN GIVE :

- ★ **MINIATURE KEY PLUG** A miniature jack plug attaches to your key ring and is coded to your particular alarm.
- ★ **2025 INDIVIDUAL COMBINATIONS** The key plug contains two 1% tolerance resistors, both must be the correct value and together give 2025 different combinations.
- ★ **ATTRACTS MAXIMUM ATTENTION** This alarm system not only intermittently sounds the horn, but also flashes the headlight and prevents the engine being started.
- ★ **60 SECOND ALARM PERIOD** Once triggered the alarm will sound for 60 seconds, unless cancelled by the key plug, before resetting ready to be triggered again.
- ★ **30 SECOND EXIT DELAY** The system is armed by pressing a small button on a dashboard mounted control panel. This starts a 30 second delay period during which the owner can open and close doors without triggering the alarm.
- ★ **10 SECOND ENTRY DELAY** When a door is opened a 10 second delay operates to allow the owner to disarm the system with the coded key plug. Latching circuits are used and once triggered the alarm can only be cancelled by the key plug.
- ★ **L.E.D. FUNCTION INDICATOR** An LED is included in the dashboard unit and indicates the systems operating state. The LED lights continuously to show the system is armed and in the exit delay condition. A flashing LED indicates that the alarm has been triggered and is in the entry delay condition.
- ★ **ACCESSORY LOOP - BONNET/BOOT SWITCH - IGNITION TRIGGER** These operate three separate circuits and will trigger the alarm immediately, regardless of entry and exit delays.
- ★ **SAFETY INTERLOCK** The system cannot be armed by accident when the engine is running and the car is in motion.
- ★ **LOW SUPPLY CURRENT** CMOS IC's and low power operational amplifiers achieve a normal operating current of only 2.5 mA.
- ★ **IN KIT FORM** It provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, random selection resistors to set the code and full set of components etc. In fact everything down to the last washer plus easy to follow instructions.

fill in the coupon and send to:

Please send more information

ELECTRONIZE DESIGN Dept E · Magnus Rd · Wilnecote · Tamworth · B77 5BY · tel 0827 281000

TOTAL ENERGY DISCHARGE (6 or 12 volt negative earth)

- Assembled ready to fit £26.70 £19.95
 D.I.Y. parts kit £15.90 £14.95

TWIN OUTPUT for cars and motor-cycles with dual ignition

- Twin, Assembled ready to fit £36.45 £29.95
 Twin, D.I.Y. parts kit £24.55 £22.95

INDUCTIVE DISCHARGE (12 volt only)

- Assembled ready to fit £15.95 £12.75

Prices Include VAT £1-00 PP(UK) per Unit, D

CAR ALARM (12 volt negative earth)

- Assembled ready to fit (All wires and £37.95
 D.I.Y. parts kit connectors incl.) £24.95

I enclose cheque/postal order OR debit my Access/Visa card



VISA ACCESS

Name _____

Address _____

Code _____

GET BIG POWER

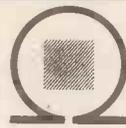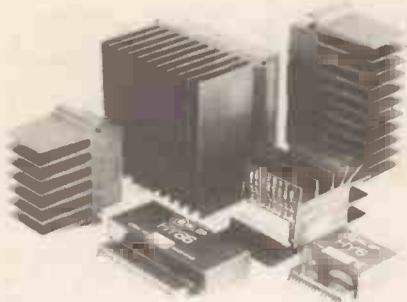

Modular Amplifiers the third generation

Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology, ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
HY30	15	4-6	0.015%	<0.006%	\pm 18	76 x 68 x 40	240	£8.40
HY60	30	4-8	0.015%	<0.006%	\pm 25	76 x 68 x 40	240	£9.55
HY6060	30 + 30	4-8	0.015%	<0.006%	\pm 25	120 x 78 x 40	420	£18.69
HY124	60	4	0.01%	<0.006%	\pm 26	120 x 78 x 40	410	£20.75
HY128	60	8	0.01%	<0.006%	\pm 35	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	\pm 35	120 x 78 x 50	520	£25.47
HY248	120	8	0.01%	<0.006%	\pm 50	120 x 78 x 50	520	£25.47
HY364	180	4	0.01%	<0.006%	\pm 45	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	\pm 60	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15v/ μ s. Rise time: 5 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz > 400.

PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83
PSU 42X	1 x HY128	£15.90
PSU 43X	1 x MOS128	£16.70
PSU 51X	2 x HY128, 1 x HY244	£17.07

Model Number	For Use With	Price inc. VAT
PSU 52X	2 x HY124	£17.07
PSU 53X	2 x MOS128	£17.86
PSU 54X	1 x HY248	£17.86
PSU 55X	1 x MOS248	£19.52
PSU 71X	2 x HY244	£21.75

Model Number	For Use With	Price inc. VAT
PSU 72X	2 x HY248	£22.54
PSU 73X	1 x HY364	£22.54
PSU 74X	1 x HY368	£24.70
PSU 75X	2 x MOS248, 1 x MOS368	£24.20

Please note: X in part no. indicates primary voltage. Please insert "O" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
MOS 128	60	4-8	<0.005%	<0.006%	\pm 45	120 x 78 x 40	420	£30.41
MOS 248	120	4-8	<0.005%	<0.006%	\pm 55	120 x 78 x 80	850	£39.86
MOS 364	180	4	<0.005%	<0.006%	\pm 55	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20v/ μ s. Rise time: 3 μ s. S/N ratio: 100db

Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz > 400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

Robust construction.

£9.14 (inc. VAT)

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz, T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 80dB, Load Impedance 3 Ω .

Input Sensitivity and impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω .

Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

ILP Electronics Ltd., DEPT 5 Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England.
Telephone: (0227) 54778 Technical (0227) 64723. Telex: 965780.

This is the Great

Hobby Electronics

Computer-Controlled Model Railway COMPETITION

Sponsored by Oric Products International Ltd., Beatties of London Limited and ASP Software (a division of Argus Specialist Publications Ltd.).

WHEN it was proposed that there should be a Grand Computer Controlled Model Railway Competition for the 1983 Breadboard exhibition, we rapidly became bogged down with seemingly endless complications. We spent most of the time during discussions simply explaining jargon: what, to a computer hardware man, is a "dead frog"? Something unpleasant by the roadside, was the popular answer! On the other hand our modelling consultant was somewhat bemused by the many acronyms that punctuate conversations between computer buffs: who, or what is a PIA? Bits of what? What is a multiplexer, and so on, and on, and on . . . !

In the end we were all quite bewildered — but this confusion ultimately gave us the clue to our Computer Controlled Model Rail Competition: no one, it seems, truly knows how best to marry a computer to a complex model rail layout or what it should do and, particularly, how it should be done.

We decided, finally, that the simplest and best approach would be to throw the thing wide open, with only a few essential restrictions. The only rule of the competition, then, is that the winning entry will be that which demonstrates the most ingenuity,

usefulness and practicality in adapting a modern home computer to control a model railway layout — the what, how and why we quite happily leave to our readers!

The essential limitation we felt obliged to impose is that the layout should measure no more than 6ft by 2ft — in other words, something that can be transported to the Breadboard exhibition in Hammersmith in late November this year.

We anticipate that most of the entries will be from constructors who have an existing computer interfaced layout, but the competition is open to all comers so anyone who wants to "have a go" will be welcome in the lists. For the benefit of those who fancy their chances at the Grand Prize, here are a few ideas that resulted from the meeting of the minds in Hobby's editorial offices (we won't mention the ideas that evolved later, down at the Royal George!).

- A fairly simple software application would be to write a program for storing and modifying timetables and operating schedules; an extension of this idea would be an interface to position sensing circuits so that an operator

would know not only when the next train was due to leave, but also when it was safe to start down the track.

- One of the most obvious ideas proposed was to program a mimic board which could show not only the track layout but the condition of signal lights and with 'train in section' indication: colour would be necessary for user-friendliness!

- Ways to adapt microprocessor technology to model train control: one option that might be easily constructed would be to computer-control sections of track rather than individual trains. However completely automatic running is not the goal of most railway modellers, so any system should allow lots of room for the operator to control the layout himself.

And that is about the limit of the ideas we came up with before brain fog set in. We'll leave it to the inventiveness and competitive spirit of our readers to stun the judges with brilliant projects we should have thought of . . . but didn't!





FIRST PRIZE

Hot off the production line, an Oric 48K colour computer, donated by Oric Products International Ltd.



SECOND PRIZE

Gift vouchers to the value of £50, redeemable on model rail products at any Beatties of London shop.



THIRD PRIZE

£25 worth of games and utility program tapes from ASP Software.

Entry forms, together with an entrance fee of £1.00 (cheque or money orders only, please) should be sent to: **The Exhibition Manager, BB83, ASP Exhibitions, 145 Charing Cross Road, London WC2H 0EE.**

Closing date is 31st October 1983. Judging will take place at Breadboard '83, Cunard Hotel, Hammersmith, London W6, on either Wednesday 23rd or Thursday 24th November 1983. Entrants will be informed of the day on which they will be required to present their layouts at the exhibition. Finalists will be asked to demonstrate their layouts at some time(s) during the open days of Breadboard '83 (25, 26, 27th November) and layouts will be available for collection between 1600 and 1800 hours on Sunday 27th November. **The judges decision will be final and no correspondence will be entered into.**

Entry Form

PLEASE USE BLOCK CAPS

NAME:

ADDRESS:


TEL NO: AGE ON 30TH NOV. 1983:

BRIEF DESCRIPTION OF LAYOUT AND FUNCTIONS:

SCALE: SIZE OF LAYOUT: (MAX 6FT X 2FT):

COMPUTER USED:

COMMERCIAL PERIPHERALS USED:

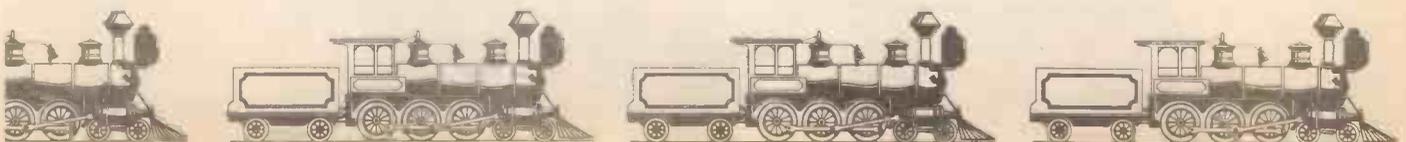

9" MONITOR in attractive case Non Standard Input. With Info £25 each. Carr £7 Matching ASCII coded Query Keyboard with Numeric Keypad and 27 Function Keys £25 each P&P £5 The Pair £40. Carr £7.

12" MONITOR. Cased Non Standard Input. With Info £20 each. Carr £7. With Matching ASCII coded Query Keyboard with Numeric Pad and 24 Function Keys £28 the Pair. Carr £7.

AZTEC 20" black & white monitor. Video in £30. TV style 20" Monitors £30

INSTRUMENT CASE standard 19" width x 16" depth x 10" high £5 each. Carr £7.

FLOPPY DISK DRIVE 8" by MEMOREX Connection details £75 each P&P £5

CRED 75 TELEPRINTER. Very good condition. £25 each. Carriage £7.

ELECTROLYTIC CAPACITOR 15,000 mfd 25V. 20p ea. 10 off £1.80.

SLOTTED OPTO SWITCH with data 50p. 10 off £4.

INFRA RED QUARTZ LAMP 230V 620 Watts Size 1 1/2 x 1/4" dia £1.50 ea. 10 off £10.

FERRANTI PHOTOCELL type MS15 — 50p ea. 10 off £4.

AMPLIFIER BOARD complete with heat sink & 2 output transistors type 2N5293. 12/24V Input. At least 5 Watt output. Circuit supplied £1.50.

VARIAC 2 amp. Ex-req. Good condition £12 ea. P&P £4.

LED type TIL209 Red with holder — 8p ea. 10 off 70p.

I.C. SOCKET 16 pin — 8p ea. 100 off £6.

GEARED MOTOR 117/234 Volt Input 50HZ. 4" dia x 5 1/2" deep. 1" shaft. New £3 each P&P £4.

MOTOR 12V DC Input. 3" dia x 4 1/2" deep. 1" shaft. New £3 each P&P £2.

DC MOTOR 6-12 Vols. Mechanical Constant Speed Control 1 1/2" dia. £1 each.

MOTOR 12V DC with pulley & semi-conductor speed control. £1 each.

SYNCHRONOUS MOTOR 2 Phase 9 volt AC. 375 RPM. Good torque (needs 30-40 mfd capacitor. Suitable for Robotics/Plotters etc. £1 each.

OTHER SYNCHRONOUS/STEPPING MOTORS AVAILABLE. PLEASE ENQUIRE

GEARED MOTOR 120V 50HZ. 4 Watt 1 rpm. 2" dia x 1 1/2" deep. £1.80 each.

CENTAUR FANS 41". 115V New. £4.80 each.

MUFFIN 116V 41". unused. £3 each P&P £2.

TRANSFORMERS — All brand new. All 240 volts input.

Sec 25.5V 2.5A. Size 3" x 2 1/2" x 2 1/2". £2.80 each.

Sec 115V1A (auto) £1.28 each. Sec 6V 1.06A £1.80

Sec 12V 100mA 80p each.

TRANSFORMER 120 Volt Input. Sec 10-0-10V 1A 75p each.

Sub Min TRANSFORMER 0-120-240V Input. Sec 12-0-12V 4VA 75p each 10 off £3.

TOROIDAL TRANSFORMER 0-115-230V Input. Sec 13.5-0-13.5V 8VA. £1.80 each 10 off £12.

TOROIDAL TRANSFORMER 0-120-240V Input. Sec 0-12V. 0-12V 10VA per winding. Encapsulated. £8 each. 10 off £38.

SOLARTRON SCOPE CD1405 DR
15MHZ £99
TELEQUIPMENT SCOPE S43 58
25MHZ £85
TELEQUIPMENT SCOPE S54-SB10MHZ
solid state £85

TELEPHONES. 706 style black. blue. green. grey. £8.50 each. 10 off £45.

Decoloured £4 each. 10 off £30.

746 style black or grey £7.80 each. P&P £2 each. 4-10 units £7. Over 10 by arrangements.

TOKIN NOISE FILTER VQ215FU. 260VAC 15A 50/60HZ. With fixing bracket. New £2 each.

VU METER. Scaled 0-5. size 1 1/2 x 7/8". 80p each 10 off £4.

I.T.T. LOUD SPEAKER. 3 1/2" dia. 50 ohm 0.2 Watt. New. 75p each. 10 off £3.80.

E.M.T. CABLE. Overall dia 5mm. 10p per metre. 100 metre drum £7.50 P&P £4.

Multi Colour RIBBON CABLE 10 way. 80p per metre. 10 metres £4. 14 way 75p per metre. 10 metres £3. 100 metres £40.

ILLUMINATED ROCKER SWITCH. 2 pole 260V 8 Amp. orange. 80p each. 10 off £4.

JOYSTICK SWITCH 4 directions. £3 each. P&P £2.

PCB KEYBOARD PAD. 19 push contacts. 0-9; A-F plus 3 optional. £1.80 each. 10 off £12.

KEYBOARD PAD. 12 Alms Reed Switches. push to make. 0-9; ; & Blank. size 3 x 2 1/2 x 2" high. £4 each. 10 off £16. P&P £3.

EPROM 2716 Single rail. £1.80 each. 2564 £3

SPECTRAL RELIANCE TEN TURN POT. 100 ohm ± 1%. Brand new. 75p each 10 off £3.

SLIDER POTENTIOMETER. Twin Gang. 200K or 2M. 25p each 10 off £3.

PANEL MOUNTING FUSE HOLDER for 1 1/2" fuse. 20p each. 10 off £1.80.

BELLING LEE CHASSIS MOUNTING FUSE HOLDER for 1 1/2" fuse. 15p each. 10 off £1.

I.E.C. MAINS LEAD. 2 metre length. heavy duty. 80p each. 10 off £5.

4 CORE CURLY WIRE extending to 2 metres. 20p each. 10 off £1.80.

MICROPHONE/EARPIECE INSERTS. Brand new. 75p each. 10 off £3.

TORIN SNAIL type BLOWER 230Volts 22 Watts. Overall size 5" x 1 1/2". £4 each P&P £2.

TURNABLE STYLE 240V AC MOTOR. Size 82 x 75 x 78mm. Shaft 43 x 4mm dia. £1.50 ea P&P £2.

TRANSFORMER Input 0-220-240V Sec 0-12. 0-24V 1 Amp. £2 each.

EXECUTIVE TELEPHONE-PUSH BUTTON. Functions include 10 number memory; repeat dialing; internal Microphone & Speaker and separate handset etc. Will connect direct to British Telecom System. BRAND NEW. ONLY £25 ea. P&P £4.

Minimum Order of Goods £3. Minimum P&P £1.80. VAT at 15% MUST be added to TOTAL OF GOODS & PACKAGING.

Many more components and test equipment available. S.A.E. or telephone for lists.

DOUGLAS ELECTRONIC COMPONENTS

90 Wellington Street, Stockport, Cheshire. SK1 3AQ



BOOKS - CROSSOVERS - CABLE - COMPONENTS - CONNECTORS - DECKS FUSES - HEADPHONES - LEADS MICROPHONES - MULTIMETERS - PROJECT BOXES - SOLDERING IRONS SPEAKERS - STYLIS & CARTRIDGES TOOLS - VEROBARD ETC.

Tel: 061-480 8971

PARNDON ELECTRONICS LTD.

Dept. 22, 44 Paddock Mead, Harlow, Essex. CM18 7RR. Tel: 0279 32700

RESISTORS: 1/4 Watt Carbon Film E24 range ± 5% tolerance

Bandolixed and colour coded. Full Range 1R0-10M. £1.00 per hundred mixed (Min 10 per value) £8.50 per thousand mixed (Min 50 per value) Special stock pack 60 values. 10 of each £5.50

RECTIFIERS

	1 Amp	3 Amp
50V	3p	14p
100V	4p	14p
200V	5p	14p
400V	6p	19p
600V	8p	20p
1000V	9p	25p

3 1/2 Digit LCD Display: 1 colon. 3 decimal points plus/minus sign and lo bat indicator.

Complete with low power 7106 A/D converter display driver. Driver set £8.95

Display £3.50 Driver £6.50

DIODES: IN4148 £1.60 per hundred

DIL SOCKETS

8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p. 22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

Full List Available — Send SAE

ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS MIN ORDER — UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE Same Day Despatch

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS. RG6 1PL

Tel: 0734 00941

Callers welcome 9 am-6.30 pm Monday to Saturday inclusive

XK113 MW RADIO KIT
Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires PP3 9V battery. IDEAL FOR BEGINNERS. £5.00

HOME LIGHTING KITS
These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

TDR300K Hamon Control Dimmer £14.30

MK6 Transmitter for above £4.20

TD300K Touchdimmer £7.00

TS300K Touchswitch £7.00

TDE/K Extension kit for 2-way switching for TD300K £2.50

LD300K Rotary Controlled Dimmer £3.50



DVM/ULTRA SENSITIVE THERMOMETER KIT
This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week

Price £15.50

NOW OPEN COMPUTER SHOWROOM

Hours: Mon-Fri 10am - 6pm
Sat 10am - 4pm.



We also stock peripherals and accessories - disc drives, printers, joy sticks etc. together with a wide range of books and the latest software for all the above computers including ZX81.

SEND S.A.E. FOR LIST TODAY!

COMPONENT PACKS

PACK 1 650 Resistors 47 ohm to 10 Mohm - 10 per value £4.00

PACK 2 40 x 15V Electrolytic Capacitors 10µF to 1000µF — 5 per value £3.25

PACK 3 60 Polyester Capacitors 0.01 to 1µF 250V — 5 per value £5.55

PACK 4 45 Sub-miniature Presets 100 ohm to 1 Mohm — 5 per value £2.90

PACK 5 30 Low Profile IC Sockets 8, 14 and 16 — pin — 10 of each £2.40

PACK 6 25 Red LEDs (5mm dia.) £1.25

3-NOTE DOOR CHIME

Based on the SAB0600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS. Order as XK 102.

£5.00

LCD 3 1/2 DIGIT MULTIMETER
16 ranges including DC voltage (200 mw-1000 v) and AC voltage. DC current (200 mA-10 A) and resistance (0-2 M) + NPN & PNP transistor gain and diode check. Input impedance 10M. Size 155x88x31 mm. Requires PP3 9v battery. Test leads included ONLY £29.00

ELECTRONIC LOCK KIT XK101
This KIT contains a purpose designed lock IC, 10-way keyboard, PCBs and all components to construct a Digital Lock, requiring a 4 key sequence to open and providing over 5000 different combinations. The open sequence may be easily changed by means of a pre-wired plug. Size: 7 x 6 x 3 cms. Supply: 5V to 15V d.c. at 40uA. Output: 750mA max. Hundreds of uses for doors and garages, car anti-theft device, electronic equipment, etc. Will drive most relays direct. Full instructions supplied. ONLY £10.50

Electric lock mechanisms for use with latch locks and above kit £13.50

DISCO LIGHTING KITS

DL1000K This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. £14.60

DL2100K A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. Only £8.00

Optional opto input DL41 Allowing audio ("beat") —light response. 60p

DL3000K This 3 channel sound to light kit features zero voltage switching, automatic level-control & built in mic. No connections to speaker or amp required. No knobs to adjust — simply connect to mains supply & lamps. (1Kw/Channel) ONLY £11.95

FAST SERVICE · TOP QUALITY · LOW LOW PRICES

No circuit is complete without a call to

HE ELECTRONICS

11-13 Boston Road London W7 3SJ

Add 65p postage & packing + 15% VAT to total Overseas Customers; Add £2.50 (Europe), £6.00 (elsewhere) for p&p Send S.A.E. for further STOCK DETAILS. Goods by return subject to availability.

OPEN 9am to 5pm (Mon to Fri) 10am to 4pm (Sat)

ALL PRICES EXCLUDE VAT

TEL: 01-567 8910 ORDERS
01-678 9794 ENQUIRIES
01-579 2842 TECHNICAL AFTER 3PM

READER'S PROJECT

Simple, untested circuits straight from Hobby readers.

STEREO PREAMPLIFIER

P. R. Pullin

THIS CIRCUIT was designed for a friend who recently up-graded his stereo cartridge from ceramic to a magnetic type — with disastrous results! He could get no more than a whisper from his amp.

What he needed was a simple stereo preamp to boost the 5mV output from his magnetic cartridge up to the 100mV input that the amplifier expected to see.

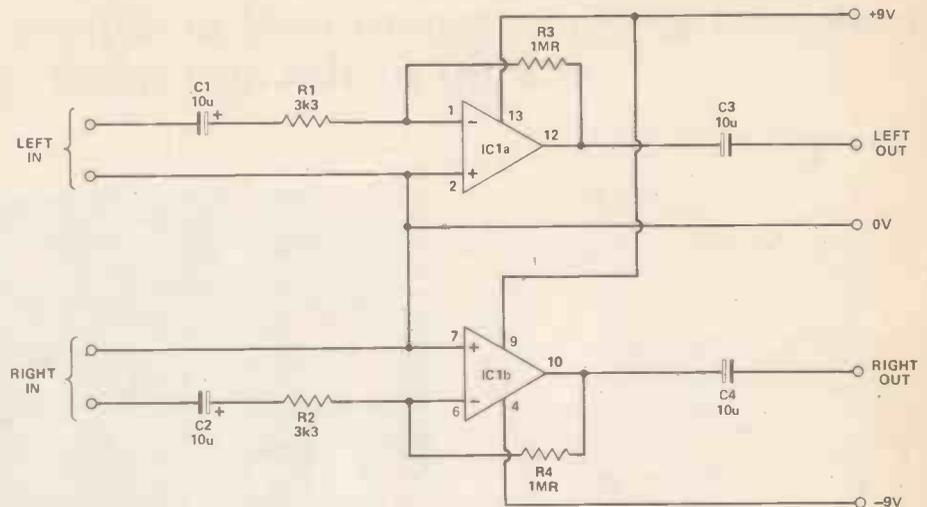


Figure 1. The circuit: a simple stereo preamp used for boosting a magnetic cartridge.

The Circuit

The ever-faithful 747 op-amp (a dual 741) proved well suited to the task. Each input is buffered with a 3k3 resistor, as the magnetic cartridge impedance is approximately 47k. The negative feedback provided by a 1M resistor gives each channel a gain of around 20.

Construction

Veroboard was chosen for this project because of its simplicity, and the layout was arranged so that there are no track breaks other than those between the IC pins. Axial electrolytic capacitors are used and fit quite snugly across the input. Screened cable must be used for all signal connections to reduce the noise to acceptable levels.

The original unit is in daily use, and performs quite satisfactorily. It is also suitable for other situations which require a low level signals to be boosted.

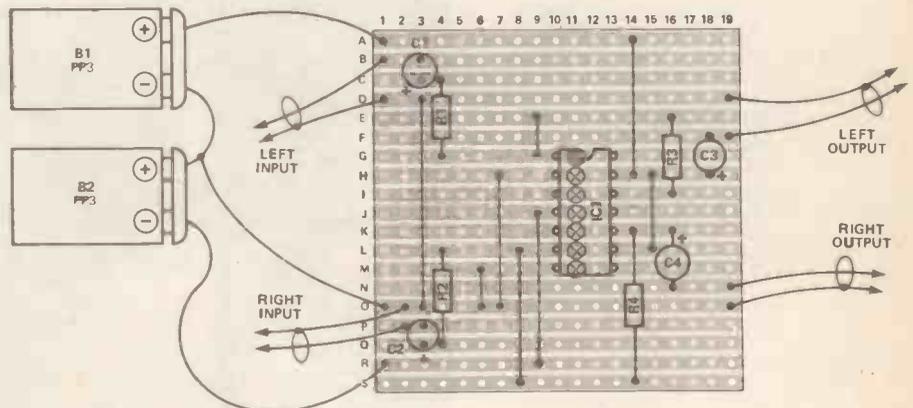


Figure 2. Careful use of screened cables for all inputs and outputs when constructing the Veroboard will keep undue noise out of the system.

Parts List

RESISTORS

(All 1/4 5% carbon)
 R1, 2 3k3
 R3, 4 1MR

CAPACITORS

(All axial electro)
 C1, 2, 3, 4 10u 35V

SEMICONDUCTORS

IC1 747
 dual 741 op-amps

MISCELLANEOUS

Veroboard, 2 x PP3 batteries;
 screened cable; wire, solder etc.

BUYLINES page 34

CAREERS IN '83 ELECTRONICS

Hooked by home computers, many enthusiasts want to make microcomputers their career. Here, an expert looks at the employment field and finds that the micro is only the tip of the computer iceberg

Angela Sharp

THE MICROCOMPUTER is perhaps the most obvious manifestation of the electronics revolution. It can be bought by anyone with £50 — or less — to spare; it appears in businesses large and small, and games and business applications can be programmed by anyone with logical ability and a knowledge of BASIC. It is therefore not surprising that many people express a desire to 'work with micros'.

Perhaps you've started to think about getting a job which combines your interest in electronics and in micros. What opportunities lie open to you, and what are the relevant courses?

For those of you who want courses which train you in basic electronic theory and practical assembly/repairing skills, there is

- CSE/O or A level electronics, preferably with those highly desirable additional subjects, maths and physics;
- City and Guilds 224, 225 or 232;
- TEC qualifications up to Level III
- A Youth Training Scheme, perhaps with a manufacturer or dealer handling computers or electronic office equipment;
- an ITEC (Information Technology Centre).

Flexibility

Youth Training schemes and ITECs are very new, and not much information is yet available about what happens to people when they leave and seek electronics work. However it seems likely that they will face the same problems as people with the other qualifications listed above:

- automation, which is affecting the more basic hardware jobs, especially in computer manufacture, but also in testing and repair. And some of the most successful computer manufacturers are the most highly-automated, with computerised assembly systems and cheap, easily-replaceable components and lots of diagnostic software to speed up and simplify fault identification;
- transferability from other areas of electronics, sometimes for the same reasons listed above.




Therefore, to get your own foot in the door, your keyword will have to be flexibility. You will have to be flexible in three ways:

- by considering electronics jobs other than those concerned with micro-computers. This is especially true if you are a 100% hardware person, happier repairing something behind the scenes than coping with a problem out front with a customer;
- by considering other jobs with micro computers. These are interesting to people whose prime interest is micros, and who have a broader range of talents and skills, notably in

dealing with people and in programming;

- by facing the fact that you may have a period of unemployment between the end of your course and finding the job of your choice. Employers now accept this — and they are interested in how you have used your enforced leisure. Therefore you should be making contingency plans for good use of your time, and hopefully offer further relevant training or experience leading to your real goal.

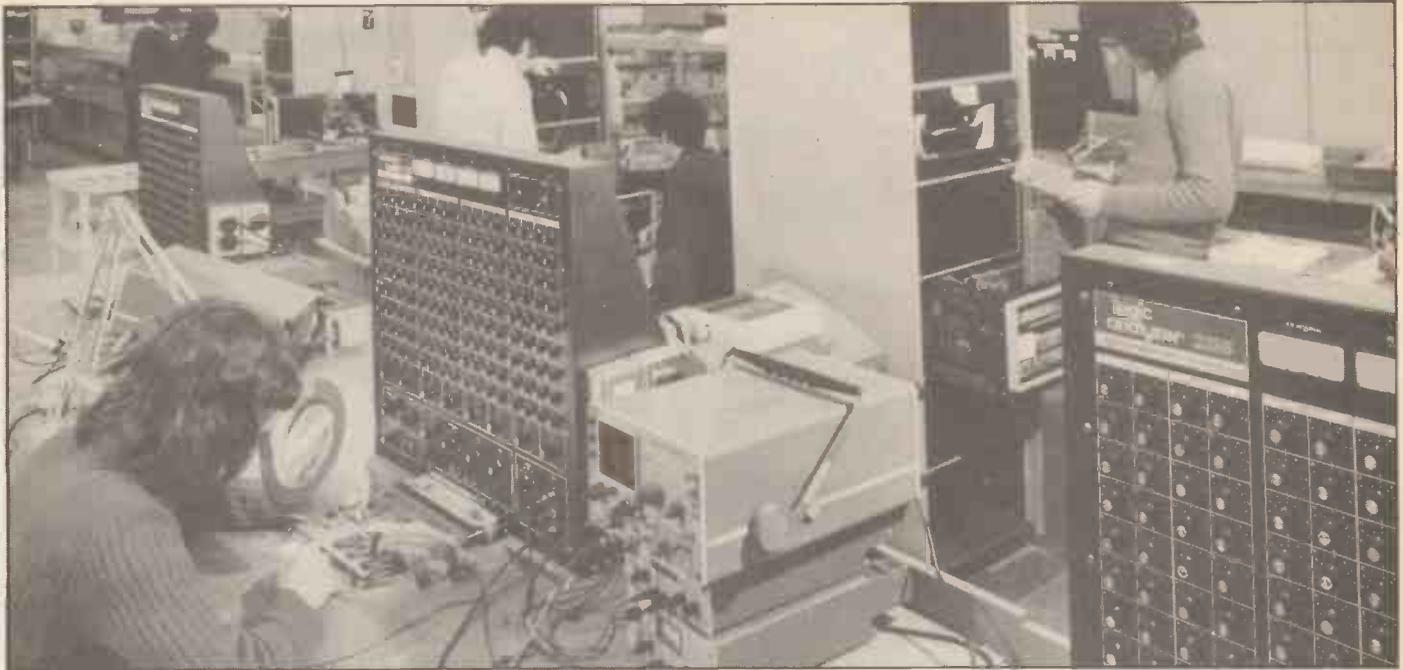Looking at jobs with micros, micro-computer manufacture is the smallest



For anyone with electronics qualifications or experience, the testing, installation and repair of computers is a field with varied opportunities.

area of employment. Many micros are manufactured abroad, or by highly automated methods. Assembly jobs in the routine sense are nowadays few and far between; there may be testing and quality control jobs, but, again, at the routine, mass-production level these have been automated, and the larger manufacturers are likely to require just a small number of more highly qualified people. Perhaps the brightest hopes in this area lie with the small, specialist manufacturer, producing one-off jobs to order — for example, computerised typesetting keyboards for use in the printing industry.

More Opportunities

Things get better: at the installation and repair stage because the number of microcomputer suppliers and dealers, who are the main employers of installation/repair people, far exceeds the number of manufacturers. The main problem here is that of competition from people who gained their training in other electronics areas. However, because of the "all-round" nature of many micro jobs, many employers are also seeking to establish a team with a good mix of backgrounds so don't give up hope!

Perhaps the best chance of a first job here lies with your high street computer shop — it is easy to spot, and is likely to sell the domestic micros and smaller business micros. The more up-market micro suppliers, selling larger, more expensive business micros and operating out of prestige office premises, are more likely to recruit installation/repair people at a higher level, or with relevant experience.

A micro dealer/supplier may sell its own product and associated software, but it is more likely to have franchises

for the sale and post-sales support of one or several other micros. (When you are being interviewed for a job, the dealers should be able to tell you immediately which products they handle, and the extent to which indepth or only basic hardware and/or software support is offered.)

If, as is likely, the dealer is a small company, employing for example less than twelve staff, this will have four basic effects on your working conditions:

- pay is likely to be lower than starting rates with larger micro dealers. It may not even be stated in advance, since the employer may prefer to look at different levels of people available before deciding;
- qualifications are likely to be flexible, ie the employer is open to consider anyone with the basic interest, knowledge and experience in electronics. This could be through any one of the courses listed above, or through related experience.
- varied work, including everything from packing and unpacking micros, delivering them and carrying them up the stairs, to loading software and checking it through. The employer is above all looking for someone willing to do the basic jobs, with the potential to pick up quickly, and largely through your own efforts, the hardware and software product knowledge.
- a probationary period. Since the employer has no way of knowing in advance whether you are quite as willing to carry heavy crates and make the tea as you claimed you were at the interview, and since (having asked only for a general and pretty basic electronics background) he/she has no way of telling whether you really can take it in and apply it, this probationary period is of crucial importance.

Smaller employers tend to take people on after a fairly cursory glance at the interview, and to fire them equally quickly after the first few weeks if they do not appear to 'have what it takes'. So don't be too depressed if this happens to you — regard it as a learning-experience which will help you to redefine your own aims.

- and finally, training: the smaller the company, the more your training will depend on your ability to pick things up from other people as you go along, and to find things out for yourself. Only the larger micro suppliers can afford off-the-job courses, or self-instruction packages.

Extra Strengths

The variety which is an essential part of micro-installation/repair jobs means that employers are looking for people with strengths in two areas besides electronics: social skills and software.

You need a pleasant manner and the ability to explain things, because you will have to keep a customer informed about what has gone wrong, what you are doing about it and the likely time he/she will have to wait before the computer is up and running. You may also find yourself training the customer in how to use the software packages that you have loaded.

Some employers can actually foresee ways in which you would be expected to do some programming. Others express a preference for programming knowledge (ideally in high level and assembler languages) so that you have a good general appreciation of the computer and how things can go wrong.

And one final essential for installation/repair work is a current driving licence. Ideally, you should have one before you start to look for jobs,

Careers In Electronics

because it will increase the range of possible employers. Otherwise, as soon as you are employed, get one as soon as you can. Without it, you will always be dependent on colleagues, and small companies cannot, quite literally, afford passengers!

Saleing Away

If you do not get into installation and repair, but if this is your ultimate ambition, then micro sales is the next best choice. Hardware knowledge is always useful when selling micros (especially when selling components to home built-it-yourself enthusiasts).

The graph, below, shows the approximate number of employers in the UK which in various ways sell micros. A software house lays the greatest emphasis on writing programs, but also supplies hardware; a hardware dealer lays greatest emphasis on fast sales of business micros to companies, accompanied by software packages, but offering less support than a consultancy.

However, the greatest growth area is the shops, where retail groups of all descriptions are getting in on the micro scene — starting with home micros but usually with plans to sell business micros eventually. Selling domestic micros while working as a sales assistant for a well-known chain of chemists or stationery shops may not sound very exciting — but it is always worth asking what their long-term plans are. These could include the opening up of quite separate computer sales centres, and they could be recruiting their basic sales staff with a view to transfer and training in this specialist area.

Sales support includes pre-sales support and post-sales support. Pre-sales support comprises everything that has to be done up to the time the sale takes place — from helping to organise advertising, answering enquiries coming in as a result of advertising, and arranging demonstrations. It is essentially an office job, holding the fort while sales staff are visiting customers. You need a very clear, confident telephone manner for everything from straightforward booking of appointments, to giving out detailed product information and even 'cold canvassing'



Microcomputer wares in a large electronics store which also deals in hi-fi and other home entertainment equipment.

Setting up and running demonstrations may be part of the job of selling microcomputers.

— telephoning companies out of the blue and interesting them in your products. Pre-sales support leads usually to sales work.

Post-sales support includes everything that has to be done to deliver the product and get the customer up and running. It really means the most basic tasks in the installation work already described and can lead to full installation/repair.

"Hands On"

The two final areas of work with micro computers are as a user and a programmer. Both would require a considerable switch of interest from someone starting from the electronics side.

The essential point about micro-user jobs is that the micro is just a sophisticated aide or tool in a job which already existed before. Scientists, office workers, professional people and technicians of all kinds from lawyers to architects all have micros and relevant software available for their specific needs.

Some users do, however, do their own programming — either extensively, or carrying out simple amendments. Nevertheless the first-entry job is nearly always as a user. Therefore you will need qualifications which relate to that user-job, plus a course of computer studies which has included some programming, typically in BASIC.

There are sometimes programming vacancies with software houses or micro suppliers which are appropriate for younger people who have again done a computer studies course including BASIC. However, micro




software houses tend to want good, highly productive programmers but they do not offer extensive training. Therefore you must either offer very good programming and business experience (almost impossible for a college leaver), or you must take a course of computer studies and be prepared to start with basic office work while at the same time teaching yourself about your employer's products.


A Higher Level

However, in the electronics world one simple fact predominates: the more highly-qualified you are, the greater will be the range of opportunities open to you. If you are qualified to degree, HND or TEC III level, you will be less limited to one area of the industry. You will regard yourself as an electronics engineer who happens to work with micros. You will be more likely to go into a design/development job, instead of being limited to the production, testing/quality control and repair jobs which are themselves being overtaken by automation.

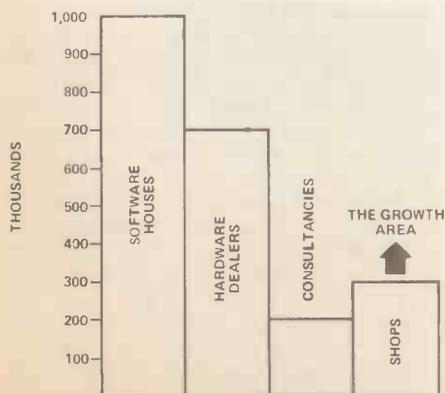Up to a point, there is no difference to employers in the acceptability of degrees or HNDs, especially in development, production, test and maintenance jobs. It is only at the most advanced levels of original research that employers demand good honours degrees and research PhDs.



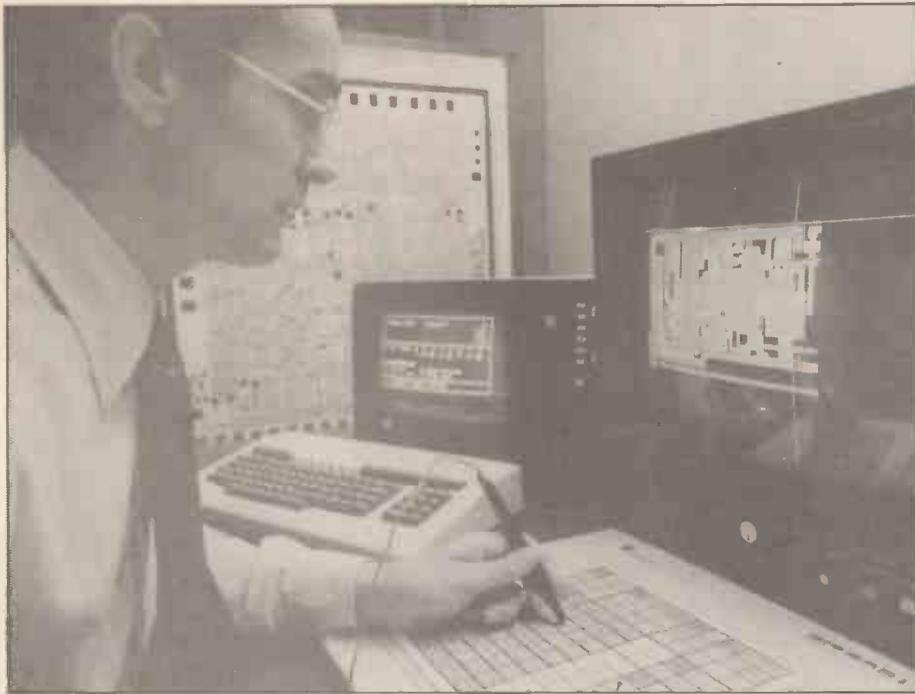Graph: Approximate numbers of micro suppliers in the UK in 1981.



Design and research: above, planning the layout of a microprocessor; below, laying out a large PCB mask.

Microprocessors and peripherals also have to be sold, and they are usually sold as components to computer manufacturers. These are known as OEMs (original equipment manufacturers), and they are only likely to be impressed by a salesperson with a sound knowledge of the product and the customer's needs. It is a quite different type of work from selling commercial micros to business users.

In considering the OEMs who buy the microprocessors and components we are finally drawing closer to the micro-computer with which we started — a desk-top piece of hardware made up of all the bits and pieces lovingly designed, developed and sold by others. A micro may be a stand-alone item or it may be part of a larger system, linked for example to a mainframe computer, or playing its part in a LAN (local area network) of several micros linked up for data processing, storage and transmission.

So once more, as at the micro-processor end of the market, it becomes apparent that 'working with micros' is a false distinction. It is being overtaken by the convergence of different aspects of electronic information technology into

'total systems' combining traditional data processing, word processing, telex, facsimile transfer, electronic mail and intelligent copiers.

A Program In Electronics

When it comes to programming, the electronics person is likely to find work relevant to his/her course in two areas:

- in micro-processor research and development, helping to produce firmware — chips with a built-in program which defines their function, for example as a storage device.
- in designing operating systems software, ie programs which control the overall running of a computer instead of the applications programs which do specific jobs.

Regarding applications programs you would make best use of your knowledge by writing programs which have a scientific, and ideally, an electronic application, rather than a commercial one such as a stock control or payroll program. There are plenty of other people wanting programming jobs in those areas! In any case, starting salaries in commercial programming are about £2,000 a year lower than those for technical specialists, including electronic engineers.

Micro computers have to be installed and maintained, and this offers the main employment field where graduates, HND people and holders of TEC III can compete on equal terms.

These jobs do not only require hardware knowledge and hardware repair skills. In fact diagnostic skills are more important, ie a good knowledge of electronics theory and of diagnostic

software. The diagnosis, and not the repair, is where the real skill lies.

Carrying The Responsibility

You may also require knowledge of applications programs. This is because many employers are small, young companies looking for one 'all-rounder' rather than several specialists. Despite your high qualifications, you should still be prepared to do everything: arranging delivery date, carrying the micro up the stairs and unpacking it, loading and checking the applications software, debugging where necessary and training the user. This will sometimes involve working 'after hours' to sort out a problem.

The final choice is whether to take a job at all, or a postgraduate course.

If you are thinking of a highly specialist postgraduate course, check first that it is not likely to prove a blind alley. Look at graduate vacancy lists, and ask a few pertinent questions of the course organisers. However, if your first degree is in pure science subject, then a postgraduate course in electronic engineering or computer studies could be extremely useful. There are also TOPS TEC conversion courses for science graduates based at Trent, Newcastle, Hatfield, Middlesex & Wales Polytechnics. The Middlesex course has the strongest computing bias, and they start in January 1984.

Courses which aim to broaden your horizons include new 'Information Technology Conversion Courses' funded by the Science and Engineering Research Council and open to people with a wide range of backgrounds. They aim to give students a broad and up-to-date understanding of the issues involved in the people/systems interface, and a grasp of hardware, software, storage and communications components of an IT system.

Finally if you want a longer and more research-based postgraduate training, which at the same time is geared to employers' needs, the SERC is also funding a new, 'total technology' approach to PhDs. These aim, in three years, to train engineers in all the stages of producing a product as discussed in this article, together with the management skills needed to weld the process together. This is perhaps particularly relevant to the smaller employers which cannot afford to carve each stage up into discrete departments. Several universities offer 'total technology' PhDs in electronic engineering, and you can get further details from the SERC, Total Technology Office, Polaris House, North Star Avenue, Swindon SN2 1ET.

Angela Sharp is the author of *Working with Computers* published by Batsford (1982), £5.95.

MASTER ELECTRONICS NOW! The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY
THIS IS THE AGE — OF ELECTRONICS!
the world's fastest growth industry...

There is a world wide demand for designers/engineers and for men to service and maintain all the electronic equipment on the market today — industrial — commercial and domestic. No unemployment in this walk of life!

Also — the most exciting of all hobbies — especially if you know the basic essentials of the subject. . . .

A few hours a week for less than a year — and the knowledge will be yours. . . .

We have had over 40 years of experience in training men and women successfully in this subject.


Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.

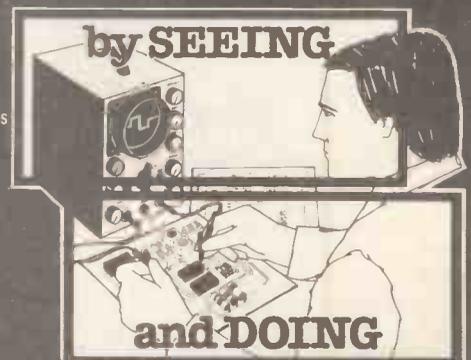

CACC
www

British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE!

COLOUR BROCHURE



POST NOW TO

Please send your brochure without any obligation to

NAME _____

ADDRESS _____

HE/11/841

BLOCK CAPS PLEASE

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS please state below


OR TELEPHONE US
0734 51515 OR
TELEX 22758
(24 HR SERVICE)

ACCREDITED BY
COUNCIL FOR THE ACCREDITATION
OF CORRESPONDENCE COLLEGES
CACC

British National Radio & Electronics School Reading, Berks. RG1 1BR

READERS' SERVICES

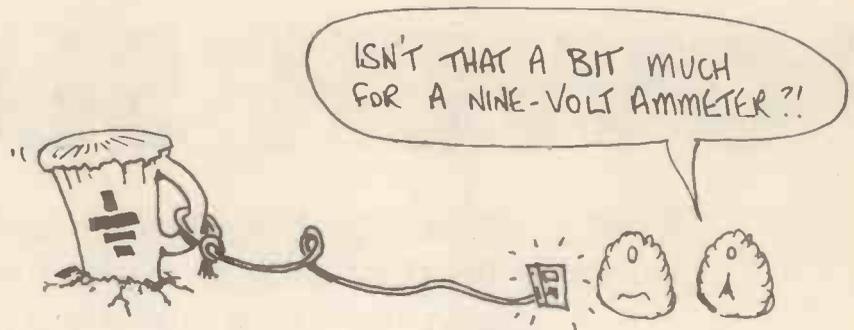Feeling stumped?
Looking for the
right connection?
It must be time to
reach for HOBBY
ELECTRONICS!
Here's how . . .



Letters

While we are always happy to receive correspondence from readers, it is simply not possible for the editorial staff to reply to every letter. Because of staff limitations and the fact that producing the monthly editions of HE must take precedence, *we cannot even guarantee to answer letters accompanied by an SAE.* Hopefully this situation will prove temporary and we can shortly resume a full service to readers.

In the meantime, to reduce the amount of mail to which we attempt a reply, certain guidelines have had to be imposed:

- Letters from readers who have been unable to successfully build a Hobby project will receive first claim on our attention. But we urge readers to first make sure they understand the problem, and to read all parts of the article thoroughly: it is wasting our time (which is better spent ensuring that current projects are error free) to reply (to pick a common case) that the supplier of certain components is given in Buylines, on page 34.

- Many enquiries are concerned with drafting errors in circuit diagrams or component overlays; corrections for most errors have been published in subsequent issues, so please check your back numbers before writing to us — the information may already be in your hands.

- Where there is a definite problem, we ask that readers first try to solve the problem themselves; again, reading the article carefully will often resolve what appears to be a contradiction between, say a Veroboard layout and the circuit diagram.

- If it is necessary to write, please try to supply useful information: it is impossible to give constructive advice to the reader who says "My project doesn't work. Can you help?". The short answer, and the only one possible, is *no!*

- We would like to hear from any reader who has had difficulty with a Hobby project and who has come up with a solution, but we cannot advise when a project has been modified and fails to work: if you decide to make

changes you will have to live with the consequences. Similarly, we are pleased to take readers suggestions for projects they would like to see in the magazine, or for modifications to improve a published project, but we cannot design circuits on request or re-design a project to suit the requirements of a single reader.

- We will try to answer any readers' questions on electronics in general, to suggest sources for components for old projects or to offer whatever advice we can when circumstances permit; however, we cannot advise on the purchase, use or modification of commercial equipment.

- We are unable to advise on the purchase of components in foreign countries; overseas readers are advised to read carefully the advertisements placed in HE by mail-order component suppliers and to write to them directly (this advice also applies to many UK readers wishing to obtain components for projects!).

- Unless specifically requested to the contrary, any letter to Hobby Electronics may be selected for publication in the magazine, including letters with an SAE if they are sufficiently interesting; in such a case a copy of the editorial comment will be returned to the reader prior to publication.

- Letters not accompanied by a stamped, self-addressed envelope may be selected for publication but will not receive a personal reply. We will attempt to reply to all enquiries backed by an SAE (if writing from outside the UK please include the correct number of International Reply Coupons, available from Post Offices) but we cannot guarantee a reply, nor can the publishers, Argus Specialist Publications, be held legally responsible for the accuracy of the information supplied.

Writing For HE

- Hobby Electronics' editor is continually looking for good projects, ideas for projects and designers to

develop an idea into working project.

However unless you are already a seasoned contributor, it is unlikely that your first effort will reach the standard required for publication in the magazine. So if you have an idea or a design and you personally think it would be suitable as a Hobby project, write and tell us about it — and please include a telephone number (night or day, we're open all hours here) where you can be contacted.

Similarly if you are a designer, perhaps with time to develop someone else's ideas, please write or phone the editor!

Any Old Rope?

We will also undertake to publish any suitable but undeveloped ideas as experimental "Reader's Projects". The article will generally fill one page when published and should include a circuit diagram and description, parts list, component overlay (the projects should generally be on Veroboard) and some brief suggestions as to how the device might be constructed by the adventurous reader! A working prototype will not be needed, and the flat rate for Reader's Projects will be £20.

Simple circuits are also needed for publication as "Short Circuits"; no constructional information is needed, and contributors of "Shorts" will be rewarded with £10 per idea.

The Back-Log

The above guidelines for writing to Hobby Electronics have had to be drawn up in response to the growing pile of yet un-answered letters from readers.

We apologise to all those still awaiting a reply; we are doing everything possible to clear the jam, but to enable us to do so in reasonable time we are retrospectively imposing the above restrictions on the type of enquiry with which we will deal. Therefore, any letter or question not relating to a Hobby Electronics project or a general electronics enquiry will be returned, with the SAE, to the reader.

DUAL PURPOSE POWER SUPPLY

William Leung

A nifty device to boost your batteries before you take them walkies, and to save your cells when listening quietly at home

FOR THOSE of you who are fed up having to purchase new batteries everytime the ones in your personal stereo cassette player run flat, here is a power supply which can provide a regulated 4.5 volts output for your player, and as an added bonus, it can also double as a recharger for Ni-Cad battery cells.

Although the circuit was designed to cater for the majority of cassette players which require three cells for operation, Table 1 give the necessary modifications for players which use two or four cells.

Power Circuit

From Figure 1, the mains voltage is stepped down by transformer T1 to around 6 volts at 250mA per secondary winding. Connecting both windings in parallel increases the current capability to 500mA RMS. This is then fed into the bridge rectifier BR1 which converts the AC into a pulsating DC voltage. Electrolytic capacitor C1 smoothes out the pulses to give a nominal voltage of 8.5 volts DC with a low ripple content.

With switch SW1 in the 'B' position, we have a conventional series regulator using a Zener diode. By the emitter follower action, the voltage at the emitter of Q1 will be approximately 0.6 volts less than that at its base. Therefore:

$$V_{out} = V_{ZDI} - V_{be}(Q1)$$

So that if $V_{ZDI} = 5.1$ volts, then the output voltage will be 4.5 volts ($5.1 - 0.6 = 4.5$) relative to the negative output terminal (ie the anode of ZD1). C2 removes any noise that is generated by the zener diode.

Q2 and either R4 and R5 provide constant current limiting at the output so that the circuit is protected from overload. The maximum current available is equal to:

$$0.65 \text{ volts/Rx Ohms}$$

Where RX is the selected current sense resistor.

The 0.65 volts mentioned is the approximate minimum base to emitter voltage of Q2. Current limiting occurs when the voltage across R4 or R5 due to load current exceeds this. Q2 then begins to conduct, pulling the base of Q1 down to a point where the corresponding lower output voltage can just maintain the maximum current (0.65 volts/Rx). At this point, ZD1 does not play any part in determining the output voltage. For example, suppose that the output was limited to 100mA and that there was a 1 Ohm resistive load, then from Ohm's Law the voltage developed across the load would be 1 volt and not 4.5 volts, due to the current limiting.

When the switch is in position 'A', the circuit operation is similar, except that the circuit is now working under current limiting continuously. This mode is used when recharging Ni-Cads.

ZD1	R2	T1	
3.6 volts	470 Ohms	6 volts	for 2 cell operation
6.8 volts	560 Ohms	9 volts	for 4 cell operation

Table 1. Provision is made for personal cassette players operating on two or four cells.



NOTES:
 T1 = 6-0-6V, 3VA
 Q1 = TIP42
 Q2 = BC109
 ZD1 = BZY89C5V1
 SW1/A = NI-CAD CHARGE
 SW1/B = 4V5 OUTPUT
 * = SEE TEXT


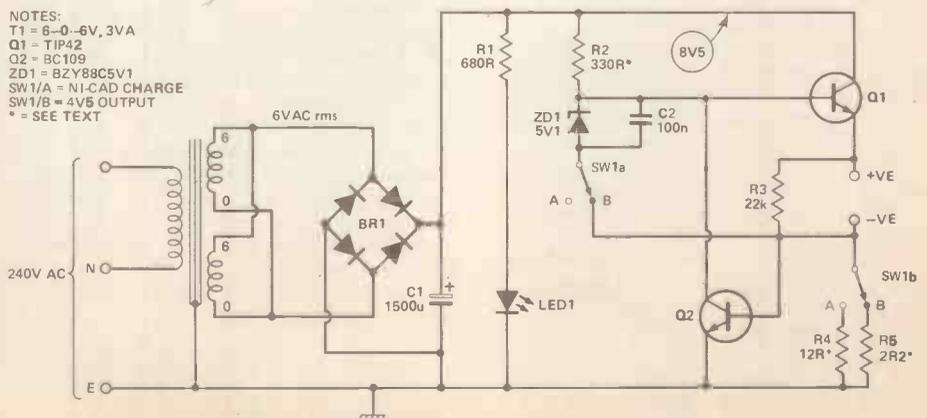


Figure 1. The values for current limiting resistors R4 and R5, must be calculated from the formula given in the text.

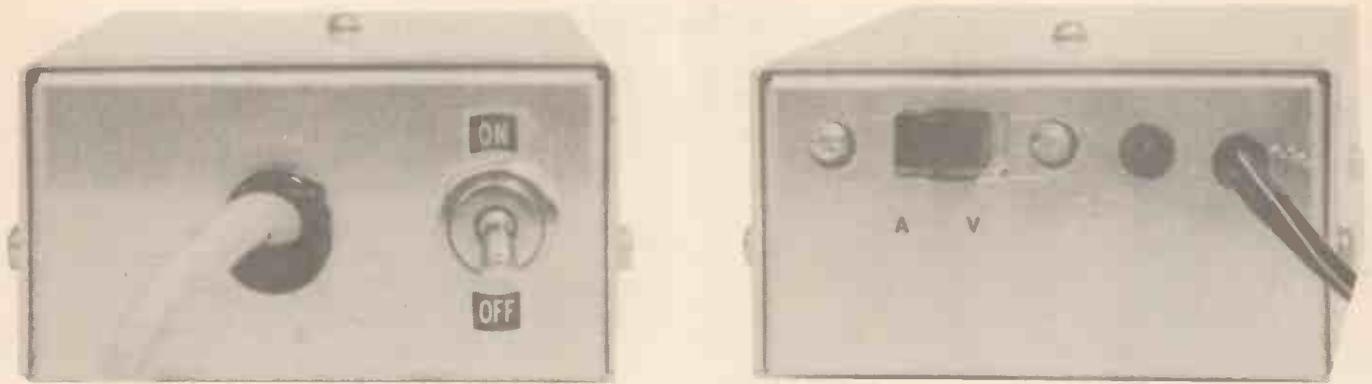

Finally, LED1 and its associated current limiting resistor R1 act as a simple 'Power On' indicator.

Current Sense

The value of R5 has been chosen so that the load can draw up to 250mA at the most, this being the maximum recommended DC current available from T1; it is more than enough to satisfy the needs of most stereo cassette players.

Since most players will require the use of AA sized Ni-Cad Cells, the value of R4 has been chosen to provide a 55mA charge rate for such cells over a period of 10 to 15 hours. The circuit can recharge up to three Ni-Cad Cells in series with the 6 volt transformer used. It should also be pointed out that Ni-Cads should never be recharged in parallel or, with this

unit, the switch is position 'B'. For other sized cells which require different charge rates, it is only a matter of calculating the new value of R4 from the formula $I_{LIMIT} = OV65/Rx$.

Construction

The Veroboard should be cut to size such that there are 20 holes in each of the 24 strips. Having done this, drill the four mounting holes and make the single break in the copper track as shown in Figure 2.

Then, in the usual fashion, solder in all the ten Veropins and the three wire links, followed up by the four resistors. Note that R1 is vertically mounted; the other resistors should be mounted a few millimetres off the board, since they will get rather warm in use. The capacitors should be

inserted next; in the case of C1, the one used in the prototype was just small enough to fit inside the specified case.

When it comes to inserting the semiconductors, stand them a few millimetres off the board and, in particular, make sure when soldering Q2 that its clip-on heatsink does not come into contact with either ZD1 or C2. As with any semi-conductor, try and keep the soldering time as short as possible.

Next the mounting holes should be drilled into the aluminium case used to house the complete project. SW1, LED1 and the grommet for the power lead to the cassette player are mounted on the front panel of the box, as can be seen from the photographs. Note that they are positioned on the upper half of the panel and this should be borne in mind when


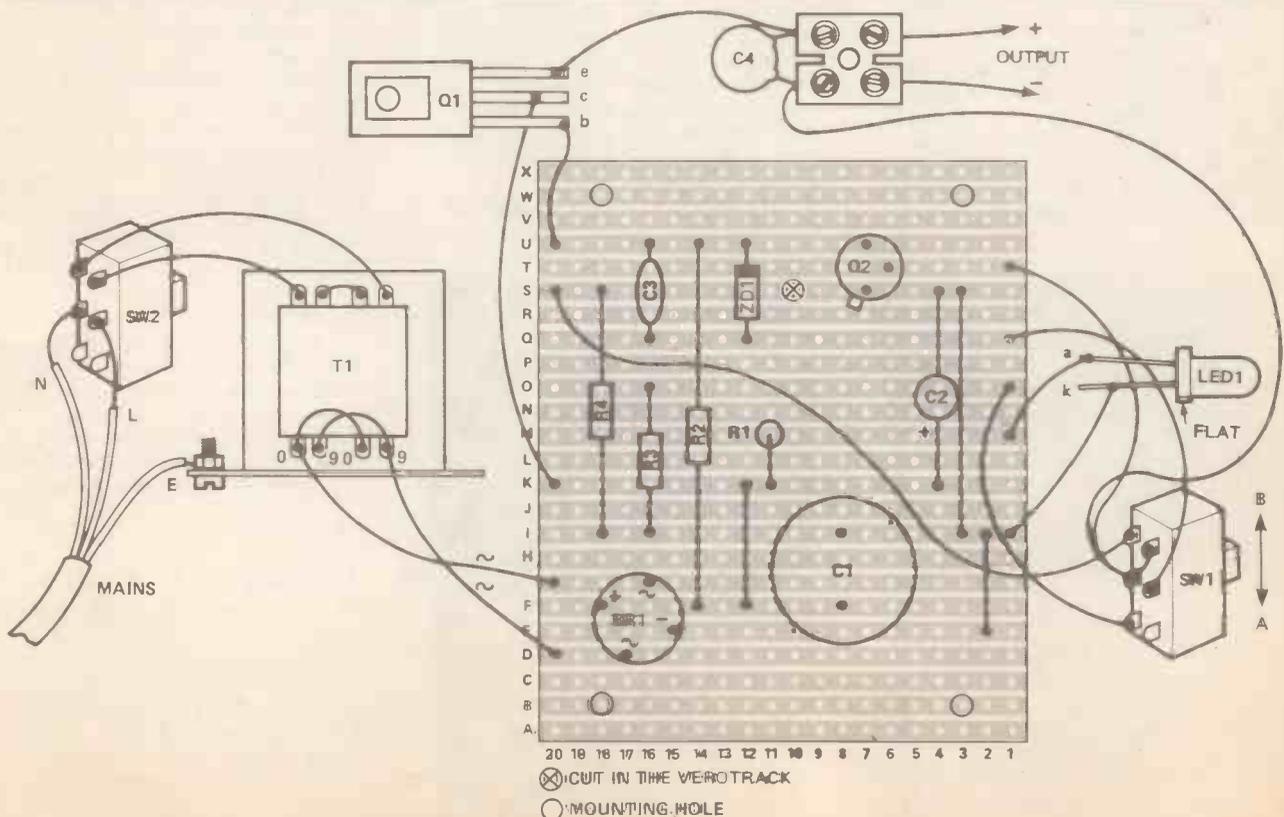


Figure 2. A small piece of Veroboard mounts most of the components, but there is a lot of off-board wiring.

Parts List

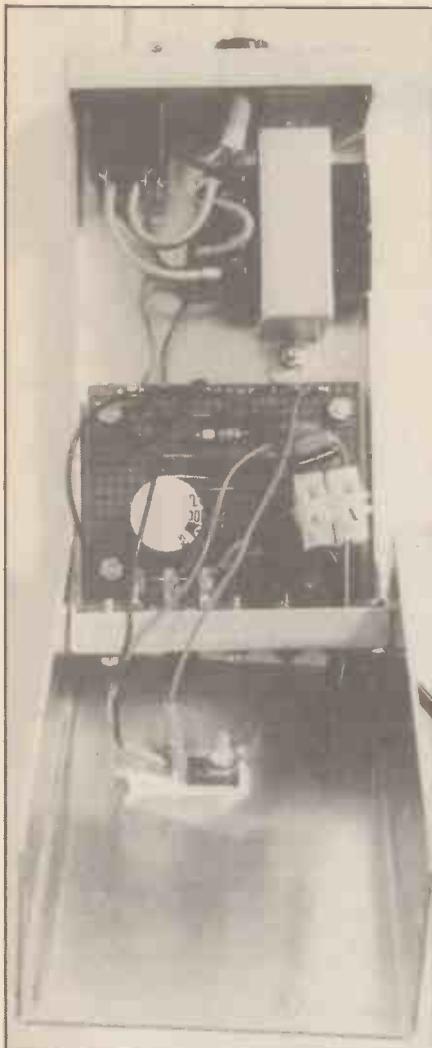

Careful construction is required when working with mains voltages, as usual. The output transistor, Q1, is mounted on the lid of the plain aluminium case, but isolated from it by a TO126 mounting kit; note the use of sleeves on the leads to this transistor.

RESISTORS

(1/2 watt 5% carbon film unless noted)

R1	1k
R2	220R
		3W wirewound
R3	12%
R4	2R2/3R3*
		3W wirewound

* see text

CAPACITORS

C1	1000u 25V
		radial electro
C2	10u 25V
		axial electro
C3, 4	100n
		polyester

SEMICONDUCTORS

Q1	BD139
		NPN transistor
Q2	BC142, BFY51 etc
		NPN transistor
ZD1	BZX61C5V1
		5V1 Zener diode
LED1	3mm red LED
BR1	WO05
		50V/1A bridge rect.

MISCELLANEOUS

T1	0-9V, 0-9V 6VA
		chassis transformer
SW1	DPDT
		slide or toggle
SW2	SPDT
		mains rated
Aluminium case, 133 x 70 x 38mm;		
TO5 clip-on heatsink; TO126		
mounting kit; mounting ring for		
LED1; mains cable grommet; plug		
to suit cassette player; Veroboard		
(see text); Ni-Cad battery holders;		
nuts and bolts, wire, solder etc.		

BUYLINES page 34

positioning the circuit board, since C1 may get in the way of SW1. On the rear panel are SW2 and the grommet for the mains cable.

From the photographs, it can be seen that Q1 is mounted on the case lid and this should be insulated from the case using the TO126 mounting kit.

Finally, it should be a straight-forward matter to wire up the project with the aid of the wiring diagram. Note that the Earth lead from the mains cable goes to the fixing bolt which holds T1 in place, and that the transistor leads of Q1 are insulated with either heatshrink sleeving or suitable insulation from some stripped wire.

The wires coming off Q1 emitter and the wiper of SW1A (the wiper with three wires coming off it) provide the output; these are soldered to the leads of C4 which are then screwed onto a two amp terminal block.

In the case of the author's prototype, the output power lead consisted of a reasonable length of 2 core cable which was connected to this terminal block and passed through a grommet on the front panel (the grommet was in fact a mounting clip for a 3mm LED!) and onto a 2.5mm plug, tip positive.

Testing

Before turning on the unit double check everything, paying particular attention to the wiring. If all seems well, turn on the power and LED1 should light up. If not, switch off immediately and check for errors.

To see that it is working properly put SW1 in position 'B' and measure the voltage at the output; this should be about 4.8 volts off load. To test the current limiting for both positions of SW1, simply connect a multimeter across the output set on a suitable current range and the meter readings should be about 55mA and 300mA (200mA if R4 has a value of 3R3) for SW1 in positions 'A' and 'B' respectively.

If all goes well at this stage, put SW1 in position 'B' and connect your personal stereo cassette player to the power supply and try a listening test. Hopefully, no problems should be experienced, however should there be any, recheck your construction.

Recharging Ni-Cads

When recharging Ni-Cads, SW1 *must* be in position 'A' and they must also be recharged in series, only. The value of R3 determines the charging current and this should be about 10% of the 'Amp-Hour' capacity of the cells (eg for AA Ni-Cads, 10% of 500mAh is 50mA), and from this, the appropriate value for R3 can be determined. At this current the charging period will be around 10-15 hours.



RECHARGEABLE BATTERIES

AND CHARGERS

PRIVATE OR TRADE ENQUIRIES WELCOME
FULL RANGE AVAILABLE
SEND SAE FOR LISTS


£1.45 for booklet "Nickel Cadmium Power"

- TRADE PRICES FOR SCHOOLS & COLLEGES •

SANDWELL PLANT LTD

656 Chester Road, Erdington,
Birmingham B23 5TE
021-373 9487 After Hours: Lichfield 57977
Now open Saturday mornings

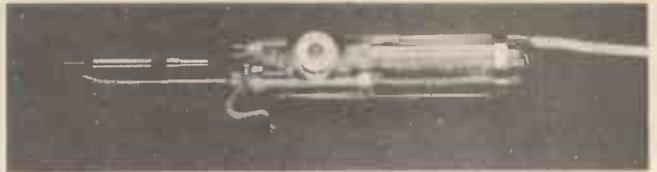New concept in miniature soldering iron design G.P.E. Self-Feed Soldering Iron Patented



- ★ Unique one-handed operation — solder is housed in the transparent handle and applied directly to the joint by turning the serrated wheel (located in the handle) with index finger.
- ★ Clean bright joint every time.
- ★ Light weight — (only 80g).
- ★ Easy to refill — just release spring clip at the end of handle. Remove cap and insert refill.

Available by Mail Order Only.
Send coupon to:-

Gardner Precision Engineering

North Road, Woking, Surrey GU21 5DS.
Tel: Woking 20722 or send SAE for details.

Name

Address

Soldering Iron 240V, 18w. Fitted with 2.3mm Dia. Bit.
complete with 4 metres solder
Solder refills (Pack of 4)
Spare Bits. Tip Dia. (Long Life) 2.3mm, 3m or
4.7mm

@ £14.95 □
@ £2.44 □
@ £1.21 □

All prices include VAT and P&P. S.A.E. for details.

ALARMS

FREE BOOKLET

on BURGLAR ALARMS

with
LOWEST U.K. DIY PUBLISHED PRICES
PHONE OR WRITE FOR YOUR COPY

051-523 8440

AD ELECTRONICS

217 WARBRECK MOOR
AINTREE, LIVERPOOL L9 0HU



Tomorrow's WORLD Self-Build Radio Controlled Car Kits

NOW AVAILABLE!

Complete Car Kit and Transmitter Kit

Clear build-up instructions included


only **£9.95** + 50p P&P

Also

Porsche 935 Turbo Kit (2 speed)

Kit includes transmitter and full build-up instructions

only **£17.00** + 50p P&P

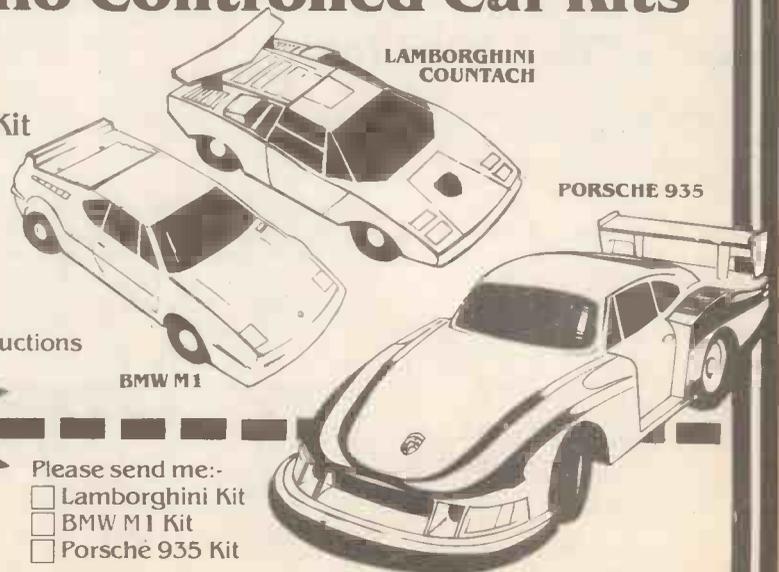

LAMBORGHINI
COUNTACH

PORSCHE 935

BMW M1



Order now from:-

Tomorrow's World
Car Kit Dept.,
Hadleigh Road Ind. Estate,
Hadleigh Road,
Ipswich, Suffolk.

Tel: Ipswich (0473) 59175

Please send me:-

- Lamborghini Kit
- BMW M1 Kit
- Porsche 935 Kit

Name _____

Address _____

Please allow 14 days delivery in U.K.


SHORT CIRCUITS

Circuit ideas from Hobby Electronics readers.

Hobby Electronics cannot undertake to answer queries on Short Circuits.

Radio Control Mixer

Over, Under, Sideways, and Around!

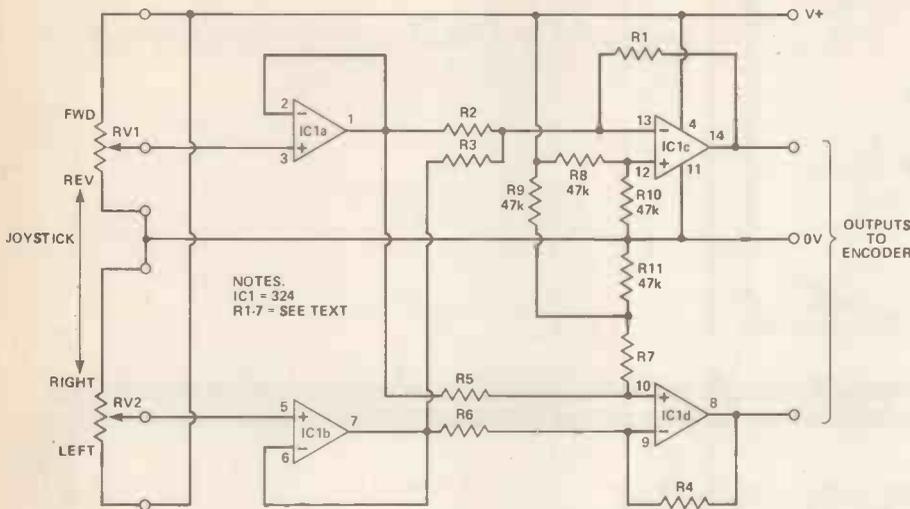

THIS mixer was designed to be fitted to a radio control transmitter to allow a tracked vehicle (eg a tank) to be controlled from a resistive joystick controller.

Potentiometer RV1 controls the Forward/Reverse speed, while RV2 controls the direction. The voltages from the two pots are buffered by IC1a and IC1b, and the outputs are fed to another pair of op-amps.

IC1c is connected as an inverting amplifier, while IC1d is connected as a differential amplifier. The buffered voltage from RV1 (Fwd/Rev) is fed to both IC1c and IC1d, and the voltage from RV2 is added to it at IC1c and subtracted from it at IC1d, thus producing the outputs necessary to steer a tracked vehicle.

The gain of ICs 1c, 1d are set by resistors R1 - R7. For most applications $R2/R1 = R5/R4$; $R3/R1 = R6/R7$, with $R3/R1$ less than $R2/R1$.

G. Foote,
Woodford Green, Essex.

Ringtone Monitor

Fed up with hanging on the telephone? Then here's a circuit that indicates when your call is answered . . .


THE CIRCUIT shown was developed to monitor a telephone ringing tone and give either an audible or visual indication when the telephone is

answered. It has proved very useful when calling companies with busy exchanges and has also shown its worth when I have had to contact

someone the moment they arrive at their home or office!

The signal from the telephone pickup coil is amplified by a 3130 op-amp and then fed to the trigger input of a 555 monostable. This signal also provides bias for a transistor connected across the timing capacitor thus preventing it from charging up. When the ringing tone stops, the mono is allowed to time out, switching on the audible warning device or LED.

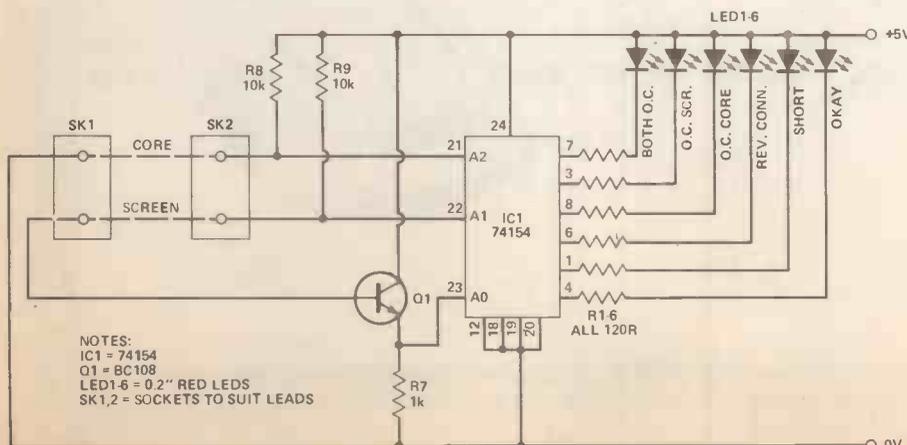
The gain of the op-amp should be set to give the best discrimination between the ringing tone and normal speech (the talking clock is a good reference) and the time constant of the 555 adjusted to hold the timer on for a period slightly longer than the pause between tone bursts.



P. Thompson
Glasgow

Headlight Warning Indicator

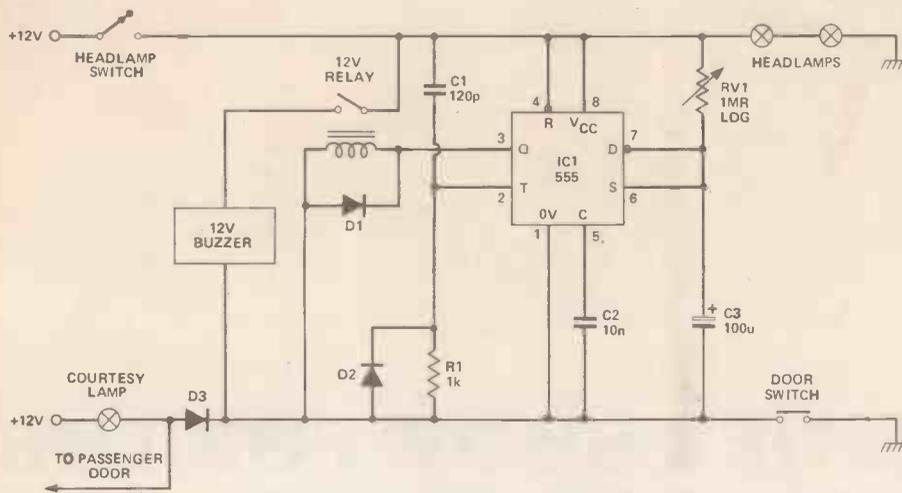A handy circuit to install in your car, that warns if the headlights have been left on when a door is opened.



THIS little circuit switches on a 12V buzzer when a car's lights are accidentally left on and the door opened, but then switches it off after a predetermined time (to avoid embarrassing incidents when the Highway Patrol opens your door as you are saying Goodnight to your girlfriend!).

The circuit consists of the widely used 555 timer connected in the monostable mode, triggered by the falling waveform generated by R1 and C1. The time duration of the buzzer is set by potentiometer RV1 and C3; up to 100 secs is available with the values given for these components.

The circuit shown is for a 12V negative earth system, but can easily be adapted for almost any car.

I. Jauncey
Northampton

Lead Tester

THE CIRCUIT shown may be used to check guitar or speaker leads for a number of different faults. Commercial units usually indicate three of four different faults. My design uses six LEDs to give direct indication of one of five faults, or that the lead is OK. The faults are: short circuit; open circuit core; open circuit

Keep Snap Crackle & Pop in the packet, where they belong!

screen; both open circuit; or reverse connection. The last is useful for checking speaker leads, where a reversed connection is a common fault and gives rise to the speakers being 'out of phase'. Double faults (for example a core open circuit and shorted to the screen) can occur, though rarely, but do not cause false

indication; in fact none of the LEDs will light in such cases.

The circuit uses a 74154 IC, which is a four-to-sixteen line decoder. For each of the 16 possible combinations of the four inputs, a single, unique output is produced. In the circuit only three inputs, A2, A1 and A0 are used, giving eight possible outputs, but only six of these are decoded to indicate one of five faults or 'OK', as shown in the truth table.

Without a lead plugged in — or if both screen and core are open circuit — inputs A2 and A1 are both held high by resistors R8 and R9 connected to the supply rail. Unconnected TTL inputs will float high, so A0 is 'pulled down' to logic 0 by resistor R7. This gives an input code of 110, which produces a low output from pin 7, lighting LED1 and indicating an open circuit condition.


With a good lead plugged into SK1 and SK2, A2 is connected to ground and therefore is at logic 0; A1 is connected to the base of Q1 and is also at logic 1; this voltage turns on Q1, so that almost the full supply voltage appears at its emitter, and A0 is also at logic 1. This combination of inputs (011) gives an output from pin 4 of the IC, turning on LED6, which is therefore marked "OK". In a similar manner all the possible fault conditions can be decoded and displayed.

A device such as this is very useful to anyone involved in electronic music or PA systems, where it is often necessary to check a large number of leads in a short time. It is certainly much faster than fiddling around with a test meter!

Brian Adams
Co. Antrim HI

A2	A1	A0	OUTPUT PIN	LED	CONDITION
0	0	0	1	5	Short
0	0	1	x	x	x
0	1	0	3	2	o/c screen
0	1	1	4	6	OK
1	0	0	x	x	x
1	0	1	6	4	reversed
1	1	0	7	1	both o/c
1	1	1	8	3	o/c core

x = not decoded

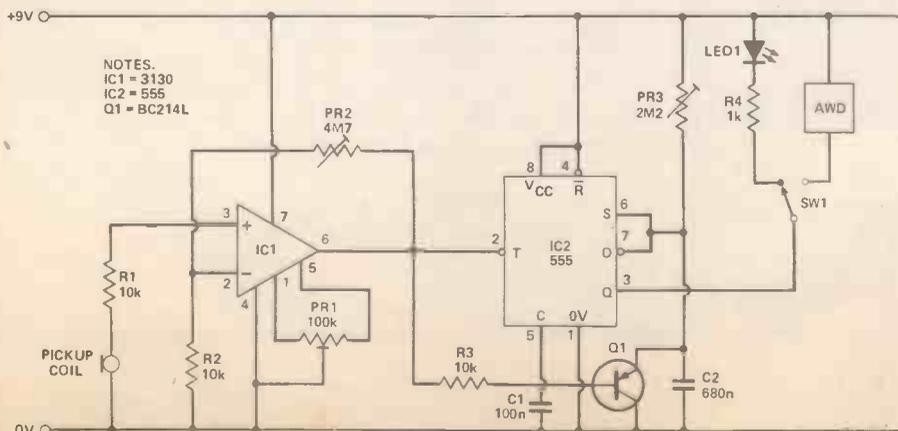

If you missed
out on Breadboard
'79, '80, '81 and '82
Now's the time to catch up with



THE PREMIER SHOW FOR THE ELECTRONICS ENTHUSIAST!

Cunard International Exhibition Centre, Cunard Hotel,
Hammersmith, London W6

Improved Venue

We have transferred BREADBOARD to the Cunard Hotel, offering improved facilities to the visitor, including car parking and ease of access by rail, tube and car, all in a modern attractive setting. See below for our arranged reduced hotel/rail fare package to attract enthusiasts from all parts of the country.

Planned Features include

- Lectures: covering aspects of electronics and computing.
- Electronics/Computing Advice Centre.
- Demonstration: electronic organs/synthesisers.
- Holography presentation.
- Practical demonstration: 'How to produce printed circuit boards'.
- Computer Corner - 'Try before you buy'.
- Amateur Radio Action Centre.
- Computer controlled model railway competition.
- Pick of the projects - Demonstration of the best from ELECTRONICS TODAY INTERNATIONAL, HOBBY ELECTRONICS and ELECTRONICS DIGEST.
- Giant TV screen video games.
- Robotic display.

FRIDAY November 25th

10am - 6pm

SATURDAY November 26th

10am - 6pm

SUNDAY November 27th

10am - 4pm

Why not make your visit to Breadboard '83 the most enjoyable yet. At these *prices, why not bring a partner, do your Christmas shopping, have an evening on the town, see the lights, and have a weekend in London!

*see next page

LITESOLD ARE OFFERING A COMPLETE SOLDERING KIT FOR ONLY



£14.55
inc. VAT & P.P.


Contains all you need to solder/de-solder any electronics project:

LITESOLD LC18H 240v high performance iron, made to professional standards in our own works, fitted with 3.2mm bit, 2 alternative bits, 1.6 and 2.4mm. Reel of 3 metres 18 swg flux-cored solder. Stainless steel tweezers. 3 soldering aids. Reel of 1.5 metres de-soldering braid. Packed in clear PVC presentation/storage wallet. Superb present — ideal for beginner or expert.

SK18H KIT SPECIAL PRICE £14.55 inc. VAT & P.P. (normal resale value £18.45 inc.) LC18H IRON only £6.00 (normally £7.39)

Spares, accessories and after-sales service available from us. 16-page colour catalogue — 60p. Send cheque/P.O. to LITESOLD or ring for Access/

Barclaycard sales.

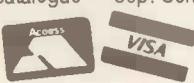

LITESOLD
LIGHT SOLDERING DEVELOPMENTS LTD.

Spencer Place, 97/99 Gloucester Road, Croydon CR0 2DN, Surrey. Tel: 01-689 0574.

FOR HI-FI & ELECTRONICS ENTHUSIASTS CONCEPT ELECTRONICS LTD 51 Tollington Road, London N7 6PB

Mail order only

We are the specialist of electronic kits and rack mounting cabinets. A catalogue with complete range of products including pre-amp modules, power amp modules, pre and power amplifier modules, complete kits of amplifiers, equalizers, reverberation amplifiers (with cases), alarm clocks, appliance timers, CB amplifiers, test equipment, control modules, music generator, battery fluorescent light and high quality rack mounting cabinets etc. with illustrative pictures now available at the cost of 35p + 25p p&p.

Professional rack mounting cabinet	Panel Size		Rear Box		Price	
	W	H (inch)	W	D	AL	STEEL
	19	x 5	17	x 4.5 x 10	27.54	23.54
	19	x 4	17	x 3.5 x 10	25.24	21.24
	19	x 3.5	17	x 3 x 10	24.09	20.09
	19	x 3	17	x 2.5 x 10	24.09	—
	19	x 2.5	17	x 2 x 10	22.94	18.94
	19	x 6	17	x 5.5 x 12	28.69	24.69
	19	x 5	17	x 4.5 x 12	27.54	23.54
	19	x 4	17	x 3.5 x 12	25.24	21.24
	19	x 3.5	17	x 3 x 12	24.09	20.09
	17	x 3.5	15.5	x 3 x 9	21.79	17.79
	17	x 2.5	15.5	x 2 x 9	20.64	16.64
	17	x 4	15.5	x 3.5 x 12	25.24	21.24
	17	x 3	15.5	x 2.5 x 12	24.09	20.09

Please add £2.50 p/p per item

★ Wholly made of black anodised aluminium sheets ★ Suitable for high quality amplifiers and many other purposes ★ Top, side and rear cover removable for access ★ Separate front mounting plate ★ Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles ★ With ventilation slits and plastic feet.

The low cost steel version is also available. The size and features as well as the front panel is the same as the aluminium cabinets except the rear box is manufactured from steel painted in black.

CONTROL MODULES

HI-FI AMPLIFIER MODULES




TY-7 Electronic touch switch
£2.90 Kit £4.50 Ass.
TY-11 Light activated switch
£2.20 Kit £3.50 Ass.
TY-18 Sound activated switch
(Clap switch) £4.50 Kit £5.95 Ass.
TY-38 Sound activated switch
(voice-switch) £5.50 Kit £7.50 Ass.
TY-41 Infra-red remote control
(Receiver and transmitter)
£17.20 Kit £21.95 Ass.

TA-323A 30W + 30W stereo amplifier
£18.95 Kit £23.95 Ass.
TA-820 60W + 60W stereo amplifier
£27.50 Kit £33.50 Ass.
TA-920 70W + 70W stereo amplifier
£35.50 Kit £42.50 Ass.

FEEL HEALTHIER WITH ZEPHION

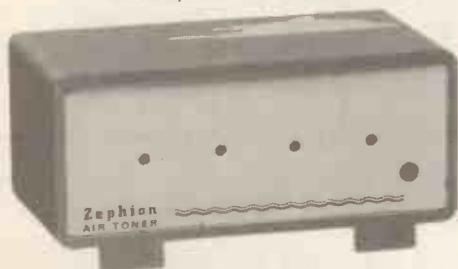Bring fresh clean air into your home with the Zephion Air Ioniser.



Air free from smoke, dust and other pollutants of modern day living can bring to many the relief of breathing comfortably once again.

We are confident that you will be delighted with the Zephion Air Ioniser, but if you are not entirely satisfied a full money back guarantee is available if items are returned in good condition within 28 days.

BUILD IT YOURSELF!

TO:- Dataplus Developments
81, Cholmeley road
Reading, Berks.
RG1 3LY TEL:- 0734 67027

NAME:- _____
ADDRESS:- _____

clip the coupon

PLEASE SEND:-

ZEPHION KITS @ £24.15p
(Kits include all parts)

ZEPHION AIR TONERS
BUILT AND TESTED. @ £34.50p

Money immediately refunded if items returned in good condition.

Prices include VAT & postage; allow 14 days for delivery. DATAPLUS.HE

Send for my CATALOGUE ONLY 75p (plus 25p post/packing)

My all-inclusive prices quoted in the Catalogue are the lowest. All below normal trade price — some at only one tenth of manufacturers quantity trade.

Millions of components: thousands of different lines

Watch/Calculator/Lighter etc, Mercury batteries
RW52(PX675) RW54 Made by Ray-O-VAC
RW56 (DH323,WH8) 31p each or
RW57, RW58 10 for £2.60, 100 for £21
IN4004 or IN4006 Diodes. 300 for £6.48p
TO5 or TO18 Heatsinks 7½p, 100 for £6.50, 1000 for £55
Clipover Heatsink for I/C or TO202 device 21 x 18mm
18p or 100 for £16.50 per 1000 for £155
Heatsink for T03 or Plastic Power 19p, 100/£17.50, 1000/£165
Modern Telephone Handset and lead in white, red, blue, grey, yellow, green or black £2
BU508A TV line output transistor, 1,500v, 15A, 125watt
£1.53p or 40 for £40 or 400 for £300

SEND PAYMENT PLUS 16p SAE OR LABEL ONLY



Prices you would not believe before inflation!

BRIAN J. REED
TRADE COMPONENTS
ESTABLISHED 26 YEARS

161 St. Johns Hill, Battersea, London SW11 1TQ
Open 11am till 7pm Tues. to Sat. Telephone: 01-223 5016

PCB FOIL PATTERNS

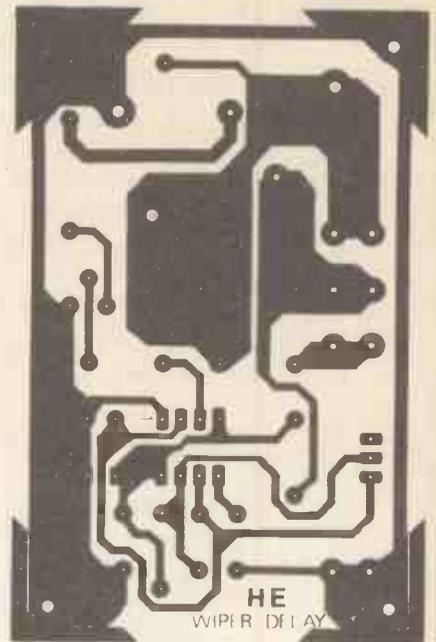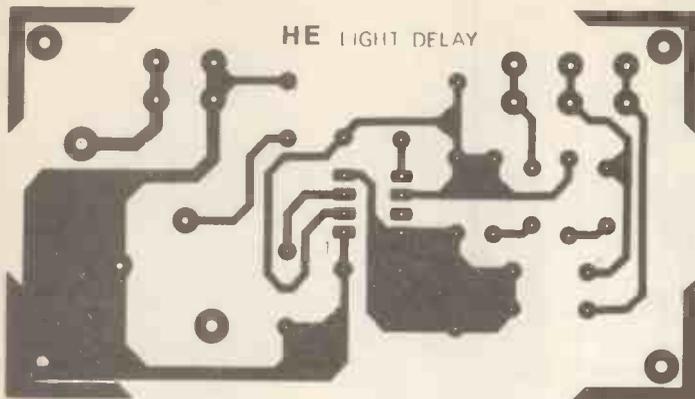Below: The PCB foil for the Interior Light Delay. If you want to etch away more of the copper, our technical department tells us that etching fluid is worth more after etching than before - because of its increased copper content. Another fascinating fact from Hobby Electronics ...



Above: Another project from the same designer: the HE windscreen wiper delay unit.

FREE CAREER BOOKLET

Train for success, for a better job, better pay

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, Through ICS home study, used by over 8 million already! Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your **FREE CAREER BOOKLET** today —no cost or obligation at all.

C & G BASIC ELECTRONICS <input type="checkbox"/>	ELECTRONIC ENGINEERING <input type="checkbox"/>
C & G RADIO AMATEUR'S Exam <input type="checkbox"/>	COMPUTER PROGRAMMING <input type="checkbox"/>
RADIO & AUDIO ENGINEERING <input type="checkbox"/>	TV & AUDIO SERVICING <input type="checkbox"/>
RUNNING YOUR OWN BUSINESS <input type="checkbox"/>	ELECTRICAL INSTALLATIONS/CONTRACTING <input type="checkbox"/>
AUTO MECHANICS <input type="checkbox"/>	C & G BASIC MECHANICAL ENGINEERING <input type="checkbox"/>

Name _____

Address _____

P.Code _____

ICS
Division of National Education Corporation

ICS
Dept N261
160 Stewarts Road,
London SW8 4UJ



01-622 9911
(all hours)



OPPORTUNITY for 4 freelance sales representatives to sell high quality electronic kit range and components to electronic retail shops. Commission only basis with good potential.

Apply in writing to:
Velleman (UK) Limited
PO Box 30
St. Leonards on Sea
East Sussex TN37 7NL

or by telephone:
0424 753246

WHY WRITE TO LONDON

When you can walk to the Midlands largest selection of DIY.

Plugs, sockets, connectors, cable, flex, leads, boxes, Aerials, styli, components, elements, semi-conductors, meters.

In fact the lot!

Spares and repairs for all electronic, electrical and audio.

H. G. Electronics Co.
1350 Stratford Road, Hall Green,
Birmingham B28 9EH
Telephone: 021-777 2369



Lineage:

30p per word (minimum 15 words)
Semi-display £7.50 per single column centimetre
Ring for information on series bookings/discounts



01-437 1002
EXT 282

Send your requirements to:
Julie Bates,
ASP Ltd.,
145 Charing Cross Road,
London WC2H 0EF

BOOKS & PUBLICATIONS

PARAPHYSICS JOURNAL
(Russian translations). Psychotronics, Kirlianography, heliphonic music telekinetics. Computer software. SAE 4 x 9":— Paralab, Downton Wilts.

FOR SALE

KIA RETURN AN ADNo 10. Delete and return... (a) Relays — 12/20/30V/PCB/50p ... (b) Autostab power supply — 12/24/35V/£4.00 ... (c) Slaveamp — 30 + 30/60/90W/£6.00 KIA-8 LS29 9DZ.

CLAIRTRONIC plug-top A.C. power unit. 240/12V at 400MA RMS. Output suitable for 12V regulators. Integral 3-pin plug moulding fitted with 2 metre jack lead. In-built thermal fuse. Price £3.20 p&p included. VAT 48p. Clairtronic Ltd, Churchfield Road, Chalfont St Peter, Bucks.

PLANS 'N DESIGN

AMAZING electronic plans, lasers, gas, ruby, light shows, high voltage teslas, van de graph, surveillance devices, ultrasonics, pyrotechnics, new solar generator, 150 more projects, catalogue S.A.E., Plant-centre, Bromyard Road Industrial Estate, Ledbury HR8

"ROBOT'S, DROIDS & FUTURISTIC THING'S"

Experimental Designs & ideas
£5.00

THOMSON ELECTRONICS
Droids Office
5 David Place, St Helier
Jersey, C.I.

COMPONENTS

BUMPER BOX OF BITS

WOW!! We've got so many components in stock, we can't possibly list them all! — So buy a box, in it you'll find resistors, capacitors, displays, switches, panels with transistors, diodes, IC's, etc., coils, pots ... and so on. All modern parts — guaranteed at least 1000 items. Minimum weight 10lbs. ONLY £8.50 inc. 48 page catalogue 50p.

ELECTRONICS WORLD
1F Dewes Road, Salisbury
Wilts SP2 7SN

ALARMS

BURGLAR ALARM EQUIPMENT. Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. Ltd., 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274-308920.

COMPUTING

HAVEN HARDWARE

ZX81 £49.90. Inverse Video £4.50. Repeating Keymodule £5.95. ZX Spectrum software: Repulsor fruit machines and Solitair £4.95 each. Mancala and Patience £5.95 each. Jupiter Ace £89.90. Inverse Video £4.95.

Access taken. SAE for details.
HAVEN HARDWARE
4 Asby Road, Asby, Workington,
Cumbria Tel: 094-686 627
Agency enquiries welcome

19K JUPITER ACE SOFTWARE: "CYGRMO" the ultimate graphic sci-fi adventure. "REVERSI" beats Jupiter's Othello. Each £6.95 from Richard Roberts, 52 Whalesmead Road, Bishopstoke Eastleigh, Hants SO5 6HL.

COMPONENTS

WAVEBANDS

Auto Electronics,
103 Coventry Street,
Kidderminster
Tel: (0562) 2179

Brand new components by return post or ring with Access/Barclaycard number for same day despatch.

All manufacturers guaranteed new stock. All at most competitive prices. Catalogue available only 50p. All prices inclusive of VAT.

IN STOCK New telephone plugs and sockets also ZX81 plugs and spectrum plugs and wide range of burglar alarm equipment and all accessories for same plus large range of components. Shudehill Supply Co. Ltd., 53 Shudehill, Manchester 4. 061-834 1449.

HOBBY SHOP

DAVENTRY

EMOS HIGH MARCH
DAVENTRY NN11 4HQ
Tel: (03272) 5523

- ★ Open Mon-Sat 9am-4pm
- ★ Both retailers and wholesalers
- ★ Vast stocks of components
- ★ Large 'walk-round' electronics supermarket

IRELAND

IRELAND
Call A & A ELECTRONICS
for wide range of kits
17 Cuala Road
Bray
Co. Wicklow
Tel. 01-862422

LANCASHIRE

ETESON ELECTRONICS



15B Lower Green,
Pouton-le-Fylde,
Blackpool
Tel: (0253) 885107

Open 9:30am-12.30, 1.30-5.30.
Closed Wed & Sun

Electronic Component Specialists

EQUIPMENT

AERIAL AMPLIFIERS Improve weak television reception. Price £6.70. S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire BLO 9AGH.

JOIN OUR FREE mailing list for bargain electronics offers. Write to: Van Gelder Ltd, P.O. Box 10, Southend-on-Sea, Essex SS2 6QG or phone (0702) 548681.

For all
your classified
needs
call: ASP
01-437 1002

TODMORDEN

PROFESSIONAL OR HOBBYIST?

Come and have a look at the EMPORIUM Bargains galore — catalogue available Electronic, Electrical and Mechanical Nuts & Bolts, Resistors, Capacitors, Meters, Semiconductors and much more.

A. C. TOWNLEY LTD
Harehill Mill
Harehill St (off Burnley Rd), Todmorden
Open 8.30-5.30 Sats till 1pm
(lunch 1-2pm)

TYNE & WEAR

NOW OPEN IN NEWCASTLE
FOR THE BEST IN ELECTRONIC
TEST EQUIPMENT AND
ACCESSORIES

Marlborough Electronic Components
15 Waterloo Street,
Newcastle NE1 4DE1
Tel: 618377

Open 9am-6pm Mon-Sat Easy Parking
Stockists of: Transistors, Resistors,
Capacitors, I.C. Diodes, Electronic Books
Etc. Repairs undertaken

W YORKSHIRE

ACE MAILTRONIX LIMITED
3A Commercial Street
Batley, West Yorkshire
Tel. 0924 441129

Open: 9-5.30pm Weekdays
9.30-1pm Saturdays
Retailers and wholesalers

KITS

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.


DIGITAL WATCH replacement parts, batteries, displays, backlights, etc. Also reports publications charts. S.A.E. for full list: Profords Copners Drive, Holmer Green, Bucks HP15 6SGE.



MULLARD SPEAKER KITS

Purposely designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer (8" or 5") with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter. B.K.E. built and tested crossover based on Mullard circuit, combining low loss components, glass fibre board and recessed loudspeaker terminals. **SUPERB SOUNDS AT LOW COST.** Kits supplied in polystyrene packs complete with instructions. 8" 40W system — recommended cabinet size 240 x 216 x 445mm. Price £14.90 each + £2.00 P & P. 5" 30W system — recommended cabinet size 160 x 175 x 295mm. Price £13.90 each + £1.50 P & P.

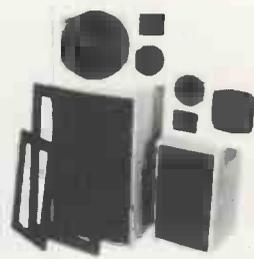Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self adhesive vinyl etc. 8" system cabinet kit £8.00 each + £2.50 P & P. 5" system cabinet kit £7.00 each + £2.00 P & P.



OMP 80 LOUDSPEAKER

The very best in quality and value.

Ported tuned cabinet in hard-wearing black vinyl with protective corners and carry handle. Built and tested, employing 10in British driver and Piezo tweeter. Spec: 80 watts RMS; 8 ohms; 45Hz-20KHz; Size: 20in x 15in x 12in; Weight: 30 pounds.

Price: £49.00 each
£90 per pair
Carriage: £5 each £7 per pair

BK ELECTRONICS

Prompt Deliveries
VAT inclusive
prices
Audio Equipment
Test Equipment
by
Thandar
and
Leader

STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Autostop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Input Sensitivity: 100mV to 2V. Input Impedance: 68K. Output level: 400mV to both left and right hand channels. Output Impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V DC at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2in x 11 1/2in. Clearance required under top panel 2 1/2in. Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish. Price £28.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £1.50.



LOUDSPEAKERS POWER RANGE

THREE QUALITY POWER LOUDSPEAKERS (15", 12" and 8" See Photo). Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons. Specification and Prices.

15" 100 watt R.M.S. Impedance 8 ohms. 50 oz. magnet. 2" aluminium voice coil. Res. Freq. 20 Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. Price: £34.00 each + £3.00 P&P
12" 100 watt R.M.S. Impedance 8 ohms. 50 oz. magnet. 2" aluminium voice coil. Res. Freq. 25Hz. Freq. Resp. to 4 KHz. Sens. 95dB. Price: £24.50 each + £3.00 P&P
8" 50 watt R.M.S. Impedance 8 ohms. 20 oz. magnet. 1 1/2" aluminium voice coil. Res. Freq. 40Hz. Freq. Resp. to 6 KHz. Sens. 92dB. Black Cone. Price: £9.50 each. Also available with black protective grille Price: £9.99 each. P&P £1.50.

12" 85 watt R.M.S. McKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz. Sens. 98dB. Price: £23.00 + £3 carriage.
12" 85 watt R.M.S. McKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz. Price £23 + £3 carriage.
15" 150 watt R.M.S. McKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price: £47 + £4 carriage.



PANTEC

HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £7.99p

DIGITAL THERMOMETER -9.9°C to +99.9°C. LED display. Complete with sensor. 70 x 70 mm (9 volt) Price: £27.60p

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled, professional performance. Range up to 3 miles 35 x 84 x 12 mm (12 volt) Price: £12.49p

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22 mm 9/12 volt) Price: £18.49 Transmitter 80 x 50 x 15 mm (9/12 volt) Price: £10.29 P&P All Kits +50p. S.A.E. for complete list.



3 watt FM Transmitter


BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm ● Belt driven ● Aluminium platter ● Precision calibrated counter balance ● Anti-skate (bias device) ● Damped cueing lever ● 240 volt AC operation (Hz) ● Cut-out template supplied ● Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price £31.35 each. £2.50 P&P



OMP POWER AMPLIFIER MODULE

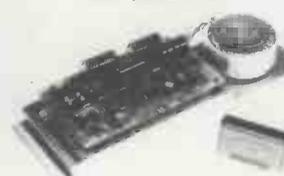

New model.
Improved specification

NEW OMP100 Mk.II POWER AMPLIFIER MODULE Power Amplifier Module complete with integral heat sink, toroidal transformer power supply and glass fibre p.c.b. assembly. Incorporates drive circuit to power a compatible LED Vu meter. New improved specification makes this amplifier ideal for P.A., instrumental and Hi-Fi applications.

SPECIFICATION
Output Power:— 110 watts R.M.S.
Loads:— Open and short circuit proof 4/16 ohms.
Frequency Response:— 15Hz - 30KHz -3dB.
T.H.D.:— 0.01%
S.N.R. (Unweighted):— -118dB ±3.5dB.
Sensitivity for Max Output:— 500mV @ 10K.
Size:— 360 x 115 x 72 mm Price:— £31.99 + £2.00 P&P. Vu Meter Price:— £7.00 + 50p P&P. R.M.S.

MOSFET VERSIONS AVAILABLE UP TO 300W R.M.S.

HOME PROTECTION SYSTEM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. FULLY GUARANTEED.

Control Unit — Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch — off — test — armed. 30 second exit and entry delay.

Indoor alarm — Electronic swept freq. siren. 104dB output.


Outdoor Alarm — Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £128 Usual price £228.85

BKE's PRICE £99.p&p£4

SAE for colour brochure

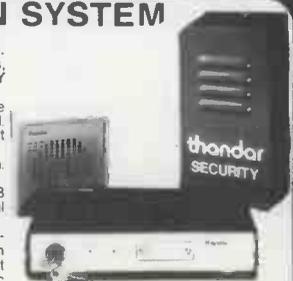

MIXERS

OMP PRO MIX MONO

OMP PROMIX MONO DISCO MIXER

(As illustrated), 4 Inputs - 2 Mag. Disc. 1 Aux. plus Mic. with override. Active bass and treble tone conts. Individual level controls plus master volume. Monitor output (head-phones) for all inputs. Output: 775mV Supply 240V ac. Size: 19" x 5 1/2" x 2 3/4". Price: £49.99 + £2.00 P&P

ALSO STEREO DISCO MIXER with 7 band graphic. Vu display. All facilities. £99.99 + £2.00 P&P

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.

TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.29 each.


TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £5.99 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £7.99 each.

TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £4.99 each.

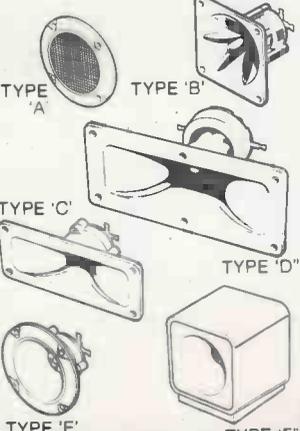TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each P&P 20p ea. (or SAE for Piezo leaflets).



B.K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR



★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★ All items packed where applicable in special energy absorbing PU foam. ★ Please phone 0702 527572 ★

100 FREE PROGRAMS

FROM SILICA SHOP — WITH EVERY PURCHASE OF AN

ATARI 400

800




ATARI PRICES REDUCED!

We at Silica Shop are pleased to announce some fantastic reductions in the prices of the Atari 400/800 personal computers. We believe that the Atari at its new price will become the U.K.'s most popular personal computer and have therefore set up the Silica Atari Users Club. This club already has a library of over 500 programs and with your purchase of a 400 or 800 computer we will give you the first 100 free of charge. There are also over 350 professionally written games and utility programs, some are listed below. Complete the reply coupon and we'll send you full details. Alternatively give us a ring on 01-301 1111 or 01-309 1111.

ATARI 400 £99
with 16K

ATARI 400 £158
with 48K

ATARI 800 £249
with 48K

400/800 SOFTWARE & PERIPHERALS

Don't buy a T.V. game! Buy an Atari 400 personal computer and a game cartridge and that's all you'll need. Later on you can buy the Basic Programming cartridge (£35) and try your hand at programming using the easy to learn BASIC language. Or if you are interested in business applications, you can buy the Atari 800 + Disk Drive + Printer together with a selection of business packages.

Silica Shop have put together a full catalogue and price list giving details of all the peripherals as well as the extensive range of software that is now available for the Atari 400/800. The Atari is now one of the best supported personal computers. Send NOW for Silica Shop's catalogue and price list as well as details on our users club.

THE FOLLOWING IS JUST A SMALL SELECTION FROM THE RANGE OF ITEMS AVAILABLE:


ACCESSORIES Cables Cassettes Diskettes Joysticks Misc. Supplies Paddles ADVENTURE INT Scott Adams Adv No 1 Adventure No 2 Pirate Adv No 3 Mission Imp No 4 Voodoo Cast No 5 The Count No 6 Strange Ody No 7 Myriety Fun No 8 Pyramid of D No 9 Ghost Town No 10 Sav Island 1 No 11 Sav Island 2 No 12 Golden Voy Angle Worms Deflections Galactic Empire Galactic Trader Lunar Lander	Mountain Shoot Resguard Star Flite Sunday Golf AUTOMATED SIMULATIONS Crush Crumble Cmp Datestones of Ryn Dragons Eye Invasion Orion Rescue at Rigel Ricochet Star Warrior Temple of Apsah Upper Reaches Adv BOOKS Basic Ref Manual Compute Atari DOS Compute Bk Atari Compute Magazine De Re Atari DOS Utilities List DOS2 Manual Misc Atari Books Op System Listing Wiley Manual	BUSINESS Calculator Database Management Decision Maker Graph-It Invoicing Librarian Mort & Loan Anal Nominal Ledger Payroll Personal Finl Mgmt Purchase Ledger Sales Ledger Statistics 1 Stock Control Telexlink 1 Wordical Weekly Planner Word Processor CRYSTALWARE Beneath The Pyram Fantasyland 2041 Galactic Quest House Of Usher Sands Of Mars Waterloo World War III	DYNACOMP Alpha Fighter Champelo Crystals Forest Fire Intruder Alert Monarch Moonprobe Moving Maze Nominoes Jigsaw Rings of The Emp Space Tilt Space Trap Stud Poker Triple Blockade EDUCATION from APX Algeaic Atlas of Canada Cubbyholes Elementary Biology Frogmaster Hickory Dickory Inst Comptg Dem Lemonade Letterman Mapware	Maths Tac-Tac Metric & Prob Solv Mugwump Music Terms/Notatn Musical Computer My First Alphabet Number Blast Polycalc Presidents Of U.S. Quiz Master Rings of The Emp Space Tilt Space Trap Stud Poker Triple Blockade EDUCATION from ATARI Conv French Conv German Conv Italian Conv Spanish Energy Czar European C & Caps Hangman Invt To Prog 1/2/3 Kingdom Music Composer	Sram States & Capitals Touch Typing EMI SOFTWARE British Heritage Cribbage/Dominos Darts European Scene Jig Hickory Dickory Humpty Dumpty Jumbo Jet Lanor Snooker & Billiards Submarine Commdr Super Cubes & Tilt Tournament Pool ENTERTAINMENT from APX Allen Egg Anthill Atank Avalanche Babel Blackjack Casino Block Buster Block 'Em Bumper Pool	Castle Centurion Checker King Chinese Puzzle Space Trek Sultans Palace Tact Trick Dice Poker Dog Day Domination Downhill Eastern Front Galahad & Holy Gr Graphics/Sound Jax-O Jukebox Lookahead Memory Match Medas Touch Minotaur Outlaw/Howitzzer Preschool Games Pro Bowling Pushover Rabbottz Reversi II Salmon Run Seven Card Stud ON LINE SYSTEMS Crossfire Frogger	Sleazy Adventure Solitaire Space Chase Space Trek Sultans Palace Tact Trick Terry Wizards Gold Wizards Revenge ENTERTAINMENT from ATARI Asteroids Basketball Blackjack Centipede Chess Entertainment Kit Missile Command Pac Man Space Invaders Star Raiders Super Breakout Video Easel PERIPHERALS Centronics Printers Disk Drive Epson Printers Program Recorder RS232 Interface Thermal Printer 16K Memory RAM 32K Memory RAM PERSONAL INT from APX Adv Music System Banner Generator Blackjack Tutor Going To The Dogs Keyboard Organ Morse Code Tutor Personal Fitness Prg Player Piano Sketchpad	PROGRAMMING AIDS from Atari Assembler Editor Dsembler (APX) Microsoft Basic Pascal (APX) Pilot (Consumer) Pilot (Educator) Programming Kit SANTA CRUZ Basics of Animation Bobs Business Display Lists Graphics Machine Kids 1 & 2 Horizontal Scrolling Master Memory Map Mini Word Processor Page Flipping Player Missile Gr Player Piano Sounds Vertical Scrolling
--	---	---	--	---	---	---	---	--

FOR FREE BROCHURES - TEL: 01-301 1111

For free brochure and reviews on our range of electronic products, please telephone 01-301 1111. To order by telephone, just quote your name, address, credit card number, and order requirements and leave the rest to us. Post and packing is FREE OF CHARGE in the UK. Express 24 hour delivery available at an additional charge.

- **SHOP DEMONSTRATION FACILITIES** - we provide full facilities at our shop in Sidcup, Monday to Saturday 9am to 5.30pm (closing Thursday 1pm, Friday 6pm)
- **MAIL ORDER** - we are a specialist mail order company and are able to supply goods direct to your door.
- **MONEY BACK UNDERTAKING** - if you are totally unsatisfied with your purchase you may return it to us within 15 days. On receipt of the goods in satisfactory condition we will give you a full refund.
- **PART EXCHANGE SECOND HAND MACHINES** - we offer a part exchange scheme to trade in many makes of TV games for personal computers.
- **COMPETITIVE PRICES** - our prices, offers and service are very competitive. We are never knowingly undercut and will normally match any lower price quoted by our competitors.
- **HELPFUL ADVICE** - available on the suitability of various computers.
- **AFTER SALES SERVICE** - available on all computers out of guarantee.
- **VAT** - all prices quoted above include VAT at 15%.
- **CREDIT FACILITIES** - we offer credit over 12, 24 or 36 months please ask for details.

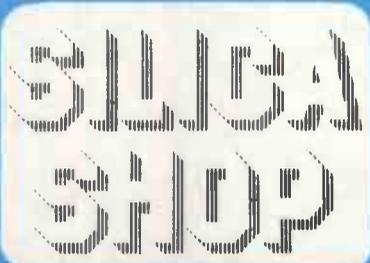SILICA SHOP LIMITED
 Dept HE1183 1-4 The Mews, Hatherley Road, Sidcup,
 Kent DA14 4DX Telephone 01-301 1111 or 01-309 1111



FREE LITERATURE

I am interested in purchasing an Atari 400/800 computer and would like to receive copies of your brochure and test reports as well as your price list covering all of the available Hardware and Software.

Name

Address

Postcode

Hobby Electronics HE1183