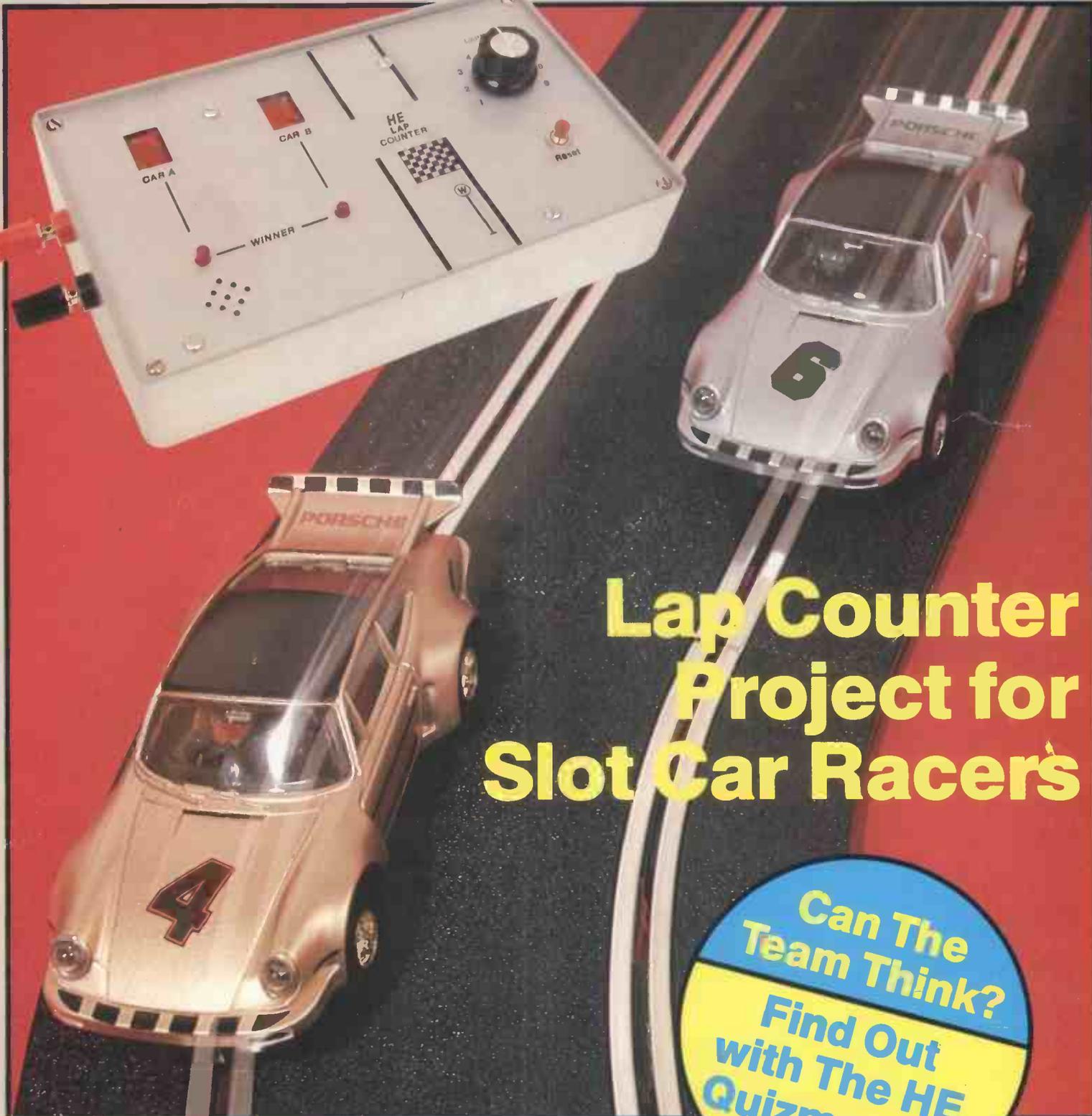


Hobby

# Electronics

Project Electronics For Everyone

90p



## Lap Counter Project for Slot Car Racers

Can The Team Think?  
Find Out with The HE Quizmaster!

Trans-Atlantic Power Reducer Project: 110/240V Converter For Heating Devices

Mainframe: Programmed Musicians Make It At Home

# ambit INTERNATIONAL

**ambit**  
INTERNATIONAL

**A topical selection from the current ambit parts and equipment catalogue — 148 pages plus 3 £1 discount vouchers! Send 80p for your copy now!**

★ mix quantity prices apply for callers to our sales counters



## NiCad battery bonanza time

0.5Ah

2.2Ah

4.0Ah\*

0.11Ah



AA



C



D



PP3

1-9      80p      £2.35      £3.05      £3.70

10-49    74p      £1.99      £2.65      £3.50

Stockcode 01-12004    01-12024    01-12044    01-84054

CH4/RX4

£7.49

01-02204



**CHARGERS**

CH4/50

£4.95

01-00409



**BATTERY ADAPTORS**

01-12001



A unique battery sleeve adaptor set that converts AA to C or D dimensions, and C to D. Ideal for emergencies.

1-9      10-24

96p    65p

**The ideal Christmas Gift!**

200 North Service Road, Brentwood, Essex CM14 4SG  
Tel: (0277) 230909

CALL AT OUR SALES COUNTERS AT  
SOLENT COMPONENT SUPPLIES,  
53 Burrfields Road, Portsmouth, Hants  
BROXLEA ELECTRONICS, Park Lane,  
Broxbourne, Herts.  
& at Brentwood, of course!

REMEMBER to add 15% VAT & 60p postage to all orders — THANKS!

# Hobby Electronics

JANUARY 1984  
VOL 6 No 1

## PROJECTS

- ★SLOT CAR LAP COUNTER ..... 20  
*It's getting around that really counts.*
- ★HE QUIZMASTER ..... 39  
*Hit that button.*
- ★TRANSATLANTIC POWER REDUCER ..... 59  
*Take the heat off and make the coffee.*

## FEATURES

- ★MAINFRAME ..... 27  
*Duo with a digital drummer.*
- ★CAREERS IN ELECTRONICS ..... 47  
*We start a three-part look at the Armed Forces with the Army.*
- ★ALL ABOUT ELECTRONICS PART 7 ..... 52  
*Op-amps.*

## SPECIAL


- ★1982 INDEX/1983 INDEX ..... 31/33  
*Two separate pull-out indexes, by special request.*

## REGULARS

- Monitor ..... 6
- Readers Services ..... 15
- Points Of View ..... 16
- What's On Next ..... 18
- Buylines ..... 26
- HE Bookshelf ..... 45
- Forward Bias ..... 58
- PCB Service ..... 63
- PCB Printout ..... 64

*Front cover: Scalextric slot racing cars and equipment available in boxed sets and individual pieces from Hamleys of Regent Street, London.*

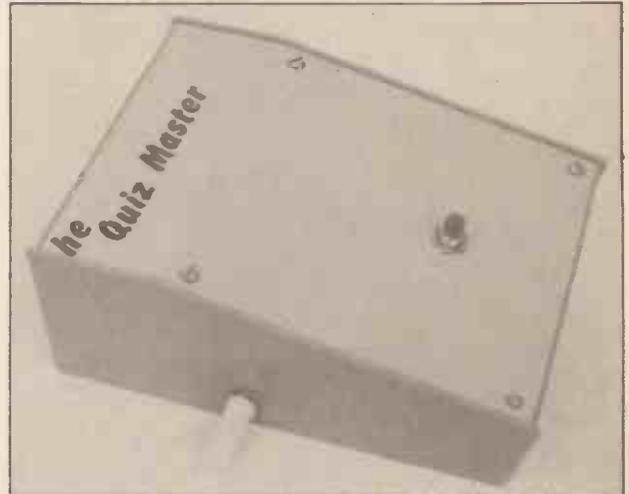**Editor:** Ron Keeley  
**Assistant Editor:** Helen Armstrong BA  
**Technical Illustrator:** Jerry Fowler  
**Advertisement Manager:** Joanne James  
**Managing Editor:** Ron Harris BSc  
**Chief Executive:** T. J. Connell



Quiz Master — page 39

# Index      Index 1982      1983

Binder Indexes — pages 31 and 33



Mainframe — page 27

Hobby Electronics is normally published on the second Friday of the month prior to the cover date.  
 Hobby Electronics, No. 1, Golden Square, London W1R 3AB, 01 437 0626. Telex No 8811869. Published by Argus Specialist Publications Ltd.  
 Origination by Ebony Typesetting, Trion House, 13 Dean Street, Liskeard, Cornwall PL14 4AB.  
 Distributed by S. M. Distribution Ltd, 16/18 Trinity Gardens, London SW9 8DX.

Printed by The Garden City Press, Letchworth, Herts SG6 1JS. Covers printed by Alabaster Passmore.


Notice: The contents of this publication including all designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Ltd. All rights conferred by the Law of Copyright and other intellectual property rights by virtue of international copyright conventions are specifically reserved to Argus Specialist Publication Limited and any reproduction requires the prior written consent of the Company. All reasonable care is taken in the preparation of the magazine to ensure accuracy, but Argus Specialist Publications Ltd cannot be held responsible legally. © Copyright 1984 Argus Specialist Publications Ltd. Member of Audit Bureau of Circulation.

## PREVIOUSLY ADVERTISED STILL AVAILABLE

Tape bench and reader	£22.50
Punch isolating transformer 250 watt	£7.75
BOAC in-flight stereo unit	£1.50
Drill assortment 4 each 25 sizes between .25mm & 2.5mm	£11.50
Battery condition tester, less box	£1.75
Nicad chargers, mains	£0.75
Flourescent inventor 13 watt from 12v	£3.50
Cassette mechanism with heads	£4.50
Ten digit slitch pad-pb phone etc.	£1.95
Uniselector 2 pote 25 way	£4.60
Water valve mains operated	£2.50
Counter 6 digit mains operated	£1.15
ditto 12v resettable	£3.45
Double glazing clear PVC sheet, 23 1/2" wide-per running ft.	£0.15
Locking mechanism with 2 keys	£1.15
Magnetic Clutch	£4.50
Mouth operated suck or blow switch	£2.30
Solenoid with slug 8 - 12v battery op.	£1.82
ditto 230v mains	£2.30
Timer Omron STP NH 110v AC Coil	£6.90
Key switch with 2 keys dp mains	£1.75
Air valve mains operated	£3.75
Latching relay mains operated	£3.50
Dry film lubricant aerosol can	£0.65
Coin op switch, cased with coin tray	£4.60



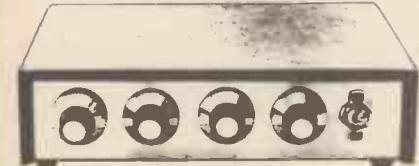**8 POWERFUL MODEL MOTORS (all different)**  
for robots, meccanos, drills, remote control planes, boats, etc. £2.95.



Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form or £25.00 assembled and tested.

### 12 volt MOTOR BY SMITHS

Made for use in cars, etc. these are series wound and they become more powerful as load increases. Size 3 3/4" long by 3 1/2" dia. They have a good length of 1/4" spindle — Price £3.45.  
Ditto, but double ended £4.25.  
Ditto, but permanent magnet £3.75.



### EXTRA POWERFUL 12v MOTOR

Probably develops up to 1/4 h.p. so it could be used to power a go-kart or to drive a compressor, etc. £7.95 + £1.50 post.

### THERMOSTAT ASSORTMENT

10 different thermostats. 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses; appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 — 100°C. There is also a thermostatic pod which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 — however, you can have the parcel for £2.50.

### MINI MONO AMP

on p.c.b., size 4" x 2" (app.) Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.



### — BARGAIN OF THE YEAR — The AMSTRAD Stereo Tuner.

This ready assembled unit is the ideal tuner for a music centre or an amplifier. It can also be quickly made into a personal stereo radio — easy to carry about and which will give you superb reception.

Other uses are as a "get you to sleep radio", you could even take it with you to use in the lounge when the rest of the family want to view programmes in which you are not interested. You can listen to some music instead.

Some of the features are: long wave band 115 — 270 KHz, medium wave band 525 — 1650KHz, FM band 87 — 108MHz, mono, stereo & AFC switchable, tuning meter to give you spot on stereo tuning, optional LED wave band indicator, fully assembled and fully aligned. Full wiring up data showing you how to connect to amplifier or headphones and details of suitable FM aerial (note ferrite rod aerial is included for medium and long wave bands. All made up on very compact board.

Offered at a fraction of its cost: **only £6.00**  
+ £1.50 post + insurance.

## THIS MONTH'S SNIP

**MAINS FILTER** — Don't let mains interference muck up your program or game — up to 13 amp load. Mains filter type FEC. SNIP PRICE ONLY £3.99.

### REVERSIBLE MOTOR WITH CONTROL GEAR

Made by the famous Framco Company this is a very robust motor, size approximately 7 1/2" long, 3 3/4" dia. 3/8" shaft. Tremendously powerful motor, almost impossible to stop. Ideal for operating stage curtains, sliding doors, ventilators etc., even garage doors if adequately counter-balanced. We offer the motor complete with control gear as follows:

1 Framco motor with gear box  
1 manual reversing & on/off switch  
1 push to start switch  
2 limit stop switches  
1 circuit diag. of connections

£19.50 plus postage £2.50

### FOR SOMEONE SPECIAL

Why not make your greeting card play a tune? It could play "Happy Birthday", "Merry Christmas", "Wedding March", etc. or "Home Sweet Home", etc. Wafer thin 3 part assemblies, for making cards musical. Mini microchip speaker and battery with switch that operates as the card is opened. Please state tune when ordering. Complete, ready to work £1.25.

### REEL TO REEL TAPE DECKS

Ex-Language Teaching School, Second, but we understand these are in good order; any not so would be exchanged. The deck is a standard BSR with normal record, replay facilities and an additional feature is tape rev counter. Nicely finished in teak type box. We have 30 only of these. Price £8.50 each + £3 carriage.

### TELEPHONE ITEMS

Plug and Wall socket — 4 pin or 5 pin	£3.45
Plugs only 4 pin or 5 pin	£1.15
Modern desk telephone	£7.50
Heavy black old type	£5.50
External bell unit	£6.50
Bell ringing power unit	£4.50
Pick up coil	£1.15

### STABILISED POWER SUPPLY (Mains Input)

By LAMDA (USA) — Ideal for computer additions, d.c. output. Regulated for line volts and load current. Voltage regulation .1% with input variations up to 20% — load regulation 1% from no load to full load — or full load to no load. Complete in heavy duty case — Models available: 5v - 6A £17.25. 5v - 9A £23. 12v - 1.5A £13.25. 15v - 1.2A £13.25. 24v - 2A £23.

**PRESTEL UNIT** — brand new and complete except for 7 plug in IC's — Price: £19.75 + £2.00 p&p.

Note: British Telecom may not connect this equipment as there is no manufacturer to guarantee it, however it is well worth buying for its immense breakdown value — sold originally at over £150.



### WATERPROOF HEATING

**WIRE** 100 ohms per yard, this is a heating element wound on a fibre glass coil and then covered with pvc. Dozens of uses — around water pipes, under grow boxes, in gloves and socks. Price: 23p per metre.

### TIME SWITCH BARGAIN

Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs **FOR ONLY £2.50.** 10 for £11.50!

### ROPE LIGHT

6 metres of translucent plastic tube full of coloured bulbs makes a wonderful display — suitable indoors or out. £25 + £2 post.

## 50 THINGS YOU CAN MAKE

Things you can make include Multi range meter, Low ohms tester, A.C. amps meter, Alarm clock, Soldering iron minder, Two way telephone, Memory jogger, Live line tester, Continuity checker, etc. etc., and you will have hundreds of parts for future projects. Our 10Kg parcel contains not less than 1,000 items — panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermostats, coils, condensers, resistors, mions, earphone/microphones, nicad charger, power unit, multi-turn pots and notes on the 50 projects.

**YOURS FOR ONLY £11.50 plus £3.00 post.**

### MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument, Jewelled bearings: 2000 o.p.v. mirrored scale. 11 instant range measures:

DC volts 10, 50, 250, 1000.

AC volts 10, 50, 250, 1000.

DC amps 0 — 100 mA.



Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test prods and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 60p post and insurance.

**FREE** Amps range: kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

## J. BULL (Electrical) Ltd.

(Dept. HE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. Established 30 YEARS

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £12 add 60p service charge. Monthly account orders accepted from schools and public companies. Access & B/card orders accepted day or night. Haywards Heath (0444) 454563. Bulk orders: phone for quote. Shop open 9.00 — 5.30, mon to Fri, not Saturday.

## EXTRACTOR FANS — MAINS OPERATED


Woods extractor.  
5" — £5.75, Post £1.25.  
6" — £6.95, Post £1.25.  
5" Planair extractor  
£6.50, Post £1.25.  
4" x 4" Muffin 115v.  
£4.50, Post 75p.  
4" x 4" Muffin 230v.  
£5.75, Post 75p.

All the above ex-computer, those below are unused.  
4" x 4" £8.50, Post 75p.  
9" American made  
£11.50, post £2.00.  
Tangential Blower 10x3  
air outlet, dual speed  
£4.60, Post £1.50.


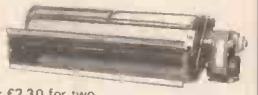
### TANGENTIAL BLOW HEATER

By British Solartron, as used in best blow heaters. 2Kw approx 9" wide £5.95, 3Kw either 9" or 12" wide (your choice) £6.95 complete with 'cold' half and 'full' heat switch, safety cut out and connection dig. Please add post £1.50 for 1 or £2.30 for two.



**2.5 Kw KIT** Still available: £4.95 + £1.50 post.

### DISCO PANEL

Make your party or disco more thrilling — add to your record player or amp, a multi-coloured, sound-enhanced lighting display. Made for Amstrad, their ref. No. RP10. Mains operated stereo or mono controlled — has 48 coloured lamps (plus 4 spares) and light level controls. Brand new and unused — offered at a never to be repeated price of £5.75 plus £2.00 post.

**BLEEP TONE** These work off 12v and have an unusual and pleasant bleep. 69p each.

**CONNECTING WIRE PACK** 48 lengths of connecting wire, each 1 metre long and differently colour coded, a must for those difficult interconnecting jobs. 85p the lot.

**RED LEDS** 10 for 69p. 100 for £5.75. 1000 for £52.

**IN LINE SIMMERSTAT** Ideal heat controller for soldering iron and many other hand-held appliances. £2.30. 10 for £17.25.



### VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case but we can supply a plastic case — £1.75. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off's per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

### IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder — a complete mains operated kit, case included. £11.95 plus £2.00 post.

## OTHER POPULAR PROJECTS

Short Wave Set — covers all the short wave bands using plug-in coils. Kit complete	£14.50
R C Bridge Kit	£9.95
3 Channel Sound to Light — with fully prepared metal case.	£14.95
Ditto — made up	£25.00
Big Ear, listen through walls	£9.50
Robot controller — receiver/transmitter	£9.50
Ignition kit — helps starting, saves petrol, improves performance	£13.95
Silent sentinel Ultra Sonic Transmitter and receiver	£9.50
Car Light 'left on' alarm	£3.50
Secret switch — fools friends and enemies alike	£1.95
3 — 30v Variable Power Supply	£13.80
2 Short & Medium wave Crystal Radio	£3.99
3v to 16v Mains Power Supply Kit	£1.95
Light Chaser — three modes	£17.50
Mullard Unilux HiFi stereo amplifier with speakers	£16.75
Radio stethoscope — fault finding aid	£4.80
Mug stop — emits piercing squawk	£2.50
Morse Trainer — complete with key	£2.99
Drill control kit	£3.95
Drill control kit — made up	£6.95
Interrupted beam kit	£2.50
Transmitter surveillance kit	£2.30
Radio Mike	£6.90
FM receiver kit — for surveillance or normal FM	£3.50
Seat Belt reminder	£3.00
Car Starter Charger Kit	£15.50
Soil heater for plants and seeds	£16.50
Insulation Tester — electronic megger	£7.95
Battery shaver or fluorescent from 12v	£6.90
Matchbox Radio — receives Medium Wave	£2.95
Mixer Pre-amp — disco special with case	£16.00
Aerial Rotator — mains operated	£29.50
Aerial direction indicator	£5.50
40 watt amp — hifi 20hz — 20kHz	£9.50
Microvolt multiplier — measure very low currents with ordinary multimeter	£3.95
Pure Sine Wave Generator	£5.75
Linear Power output meter	£11.50
115 Watt Amplifier 5Hz 25kHz	£13.50
Power supply for one or two 115 watt amps	£17.50
Stereo Bass Booster, most items	£8.95

electronize

# AUTO-ELECTRONIC PRODUCTS

KITS OR READY BUILT

## TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION



IS  
YOUR CAR

### AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
  - ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains it from service to service.
  - ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs. where the ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engines maximum (even with 8 cylinders).
  - ★ Is the **PERFORMANCE SMOOTH**. The more powerful spark of Total Energy Discharge eliminates the "near misfires" whilst an electronic filter smoothes out the effects of contact bounce etc.
  - ★ Do the **PLUGS and POINTS** always need changing to bring the engine back to its best? Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.
  - ★ **TOTAL ENERGY DISCHARGE** is a unique system and the most powerful on the market, 3 1/2 times the power of inductive systems - 3 1/2 times the energy and 3 times the duration of ordinary capacitive systems. These are the facts:  
Performance at only 6 volts (max. supply 16 volts)  
SPARK POWER — 140W, SPARK ENERGY — 36mJ  
SPARK DURATION — 500µs, STORED ENERGY — 135mJ  
LOADED OUTPUT VOLTAGE  
50pF load — 38kV, 50pF + 500k — 26kV
- We challenge any manufacturer to publish better performance figures. Before you buy any other make, ask for the facts, its probably only an inductive system. But if an inductive system is what you really want, we'll still give you a good deal.
- ★ **All ELECTRONIZE electronic ignitions feature:**  
EASY FITTING, STANDARD/ELECTRONIC CHANGEOVER SWITCH, STATIC TIMING LIGHT and DESIGNED IN RELIABILITY (14 years experience and a 3 year guarantee).
  - ★ **IN KIT FORM** it provides a top performance system at less than half the price of comparable ready built units. The kit includes: pre-drilled fibreglass-PCB, pre-wound and varnished ferrite transformer, high quality 2uF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

Most NEW CARS already have electronic ignition. Update YOUR CAR

## ELECTRONIZE ELECTRONIC CAR ALARM



### HOW SAFE IS YOUR CAR ?

More and more cars are stolen each week and even a steering lock seems little help. But a car thief will avoid a car that will cause him trouble and attract attention. If your car has a good alarm system - well there are plenty of other cars to choose from.

#### LOOK AT THE PROTECTION AN ELECTRONIZE ALARM CAN GIVE :

- ★ **MINIATURE KEY PLUG** A miniature jack plug attaches to your key ring and is coded to your particular alarm.
- ★ **2025 INDIVIDUAL COMBINATIONS** The key plug contains two 1% tolerance resistors, both must be the correct value and together give 2025 different combinations.
- ★ **ATTRACTS MAXIMUM ATTENTION** This alarm system not only intermittently sounds the horn, but also flashes the headlight and prevents the engine being started.
- ★ **60 SECOND ALARM PERIOD** Once triggered the alarm will sound for 60 seconds, unless cancelled by the key plug, before resetting ready to be triggered again.
- ★ **30 SECOND EXIT DELAY** The system is armed by pressing a small button on a dashboard mounted control panel. This starts a 30 second delay period during which the owner can open and close doors without triggering the alarm.
- ★ **10 SECOND ENTRY DELAY** When a door is opened a 10 second delay operates to allow the owner to disarm the system with the coded key plug. Latching circuits are used and once triggered the alarm can only be cancelled by the key plug.
- ★ **L.E.D. FUNCTION INDICATOR** An LED is included in the dashboard unit and indicates the systems operating state. The LED lights continuously to show the system is armed and in the exit delay condition. A flashing LED indicates that the alarm has been triggered and is in the entry delay condition.
- ★ **ACCESSORY LOOP - BONNET/BOOT SWITCH - IGNITION TRIGGER** These operate three separate circuits and will trigger the alarm immediately, regardless of entry and exit delays.
- ★ **SAFETY INTERLOCK** The system cannot be armed by accident when the engine is running and the car is in motion.
- ★ **LOW SUPPLY CURRENT** CMOS IC's and low power operational amplifiers achieve a normal operating current of only 2.5 mA.
- ★ **IN KIT FORM** It provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, random selection resistors to set the code and full set of components etc. In fact everything down to the last washer plus easy to follow instructions.

fill in the coupon and send to:

Please send more information

**ELECTRONIZE DESIGN** Dept E · Magnus Rd · Wilnecote · Tamworth · B77 5BY · tel 0827 281000

#### TOTAL ENERGY DISCHARGE (6 or 12 volt negative earth)

- Assembled ready to fit £26.70 £19.95
- D.I.Y. parts kit £15.90 £14.95

#### TWIN OUTPUT for cars and motor cycles with dual ignition

- Twin, Assembled ready to fit £36.45 £29.95
- Twin, D.I.Y. parts kit £24.55 £22.95

#### INDUCTIVE DISCHARGE (12 volt only)

- Assembled ready to fit £15.95 £12.75

Prices include VAT

£1-00 PP(UK) per Unit

#### CAR ALARM (12 volt negative earth)

- Assembled ready to fit (All wires and connectors incl.) ~~£27.95~~ £29.95
- D.I.Y. parts kit ~~£24.95~~ £19.95

I enclose cheque/postal order OR debit my Access/Visa card

VISA

Name \_\_\_\_\_

Address \_\_\_\_\_

Code \_\_\_\_\_

# MONITOR

## Easier To Digest

We have had a number of letters asking about back issues of *Electronics Digest*. You may have noticed that we rarely have room for a House Ad. for Digest, which is a pity because the back issues have some interesting stuff in them.

Our distribution department tells me that the following past Digests are still available:

Volume 1 no. 1 and 3; Volume 2 Nos 1, 2, 3, and 4; Volume 3 Nos 1, 2 and 3, and Volume 4 Nos 1 and 2.

To summarise briefly, Vol. 1 No.1 is a collection of circuits from *Electronics Today* (most of the project issues contain projects from ETI and HE); Vol 1 No. 3 "Data Book" is a components issue, with descriptions of different classes of components, types, pin connections, truth tables and general articles.

Vol. 2 No. 1 is a "Home Security" issue, with a collection of circuits for safeguarding home and car; Vol. 2 No. 2 is a project issue, primarily of ETI projects; Vol. 2 No. 3 is a bumper project issue with 150 projects; Vol. 2 No. 4 is a "Gateway To Electronics/Complete Constructor's Course", with twenty projects plus instructions on technique.


Vol. 3 No. 1 is a more advanced version of Vol. 2 No. 4, the "Designer's Notebook", with 120 circuits, design hints, techniques and construction notes; Vol. 3 No. 2 is a general projects issue; Vol. 3 No. 3 is a "Graded Course In Projects Building" based entirely around HE projects, with an introductory feature in components.

Vol. 4 No. 1 is an introduction to circuit design for the almost beginner, which starts by reprinting most of the popular HE series *Into Electronic Components*, and then follows with a section on techniques, followed by a directory of basic circuits: Vol. 4 No. 2 is a Data Book, this time on microprocessors and support devices, reprinting data on all the popular constructors' microprocessors. Vol. 4 No. 3, just out, is a collection of projects from ETI, under the headings *Home and Car, HiFi and Sound, and Lab Test*, and costs £1.95.

Because some issues have literally vanished from the face of the earth, we are *not* doing photocopies of the missing issues, but any of those listed above can be had for £2.25 a copy despatched to our usual backissues source, 513 London Road, Thornton Heath, Surrey CR4 6AR. Money orders and cheques should be made out to ASP Ltd.
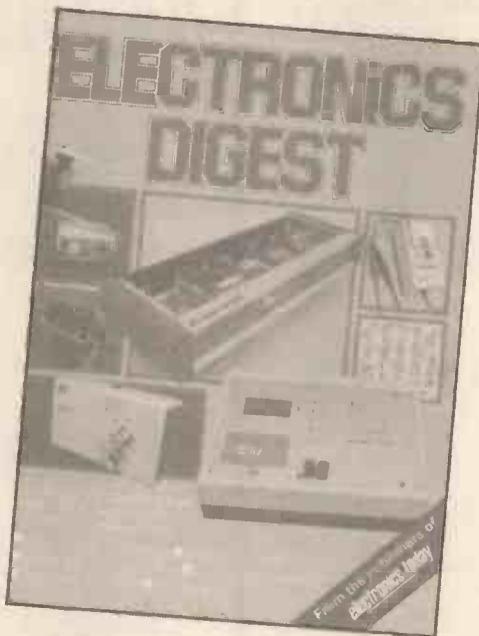
## A Cool Handle

Litesold have introduced a mains-voltage electronically temperature controlled soldering iron. The EC50 incorporates an electronic temperature control circuit mounted inside the handle, which operates in response to a



thermistor fitted inside the bit-mount. Power to the 50W heating element is controlled by a triac operated by a zero-voltage switching IC, to minimise spiking and RFI, and the iron is fully earthed so that it may safely be used on sensitive equipment and components.

A special feature of the design is that the low-voltage supply necessary for the control circuit is obtained by means (for which a patent is pending) which does not involve fitting a dropper resistor in or near the handle. This problem has previously prevented a mains iron of this type being made to run with a sufficiently cool handle.

The control circuit provides a proportional control band, so that power to the heating element is only fully on or

off outside a temperature band centred on the set value. Within this proportional band, power is supplied in regular phases of equal interval but of a length which varies according to the difference between 'actual' and 'set' temperatures. This feature, we are told, gives an extremely close control, with no swing or overshoot. An internal neon indicator glows through the translucent handle when the element is energised. Access is provided to the temperature control potentiometer, the settings may be varied from approximately 280 to 400°C. The standard setting is 370°C.


Prices and information from Light Soldering Developments Ltd., Spencer Place, 97-99 Gloucester Rd., Croydon CR0 2DN. Tel: 01 689 0574.

## Video Production Courses

JVC's Video Information Centre in London's Piccadilly is once again holding courses for those wishing to know more about video, video techniques and video production. The new lecturer at the Centre, Phil Compton, will be running two levels of course, basic and advanced, and, where requested, will also arrange special courses designed to suit particular needs. Courses are twice monthly, have already begun at the VIC and will begin shortly in Bristol.

The basic production course is a three day course designed for beginners with little or no experience of video production. Starting from the basics, the course builds over three days to form a complete education into the art of producing a coherent and effective programme or film.

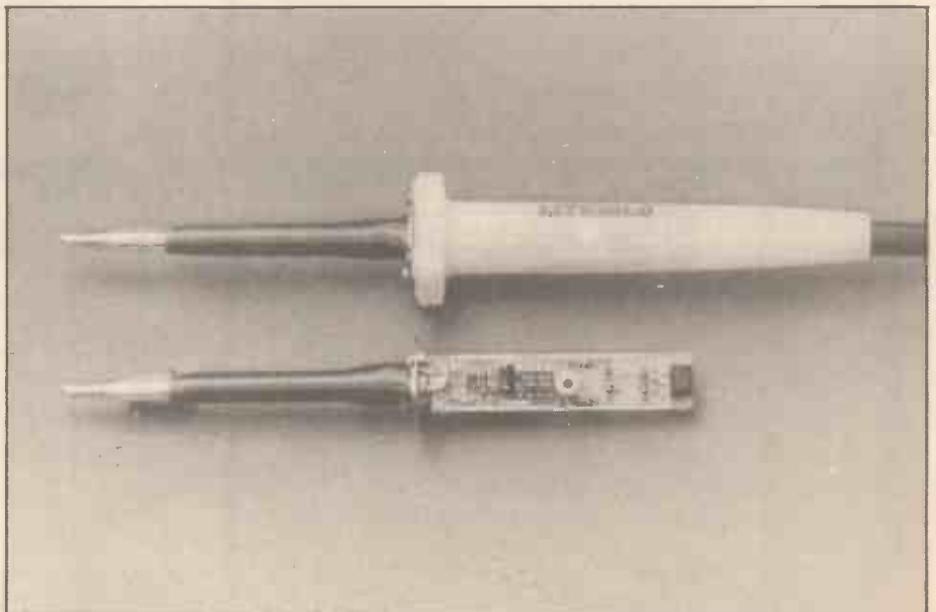The advanced course is a follow-on from the basic course, putting into practise much of what has been covered. However, the course broadens



# MONITOR

on the base and develops themes and ideas further, ensuring that the participants have comprehensive understanding of how to extract the most from their videos. Much of the emphasis of this two day course is on avoiding and correcting production problems.

For further information concerning availability and dates for these courses please contact Phil Compton or Mike Whyman at the JVC Video Information Centre, 82 Piccadilly, London W1. Tel: 01 491 3775.

## Modular Case System

Elinca Products have introduced a modular case system for electronic assemblies and instrument displays. Developed from the Elinca range of BEC cases first introduced in 1972, the new system is designed for use by manufacturers or for DIY.

The new BEC system comprises pre-formed body panels, facias and moulded end cheeks, which make up a wide variety of cases, ranging in size from 2x5x6in up to 2x5x13in. All case sections are pre-punched for instant assembly and are available in a choice of white or black, with natural aluminium or black fascia panels. Polished teak veneered end cheeks are also available.

The cases are manufactured in plastic coated metal which is anti-static with high insulation and screening properties, with end cheeks in textured high impact resistant polystyrene.

The BEC cases are available for DIY in hanging displays complete with screws and assembly instructions. Details of the new case system are available from Elinca Products Ltd., Lyon Works, Capel Street, Sheffield S6 2NL. Tel: 0742 339774.



## Electronic Memo Pad

A British-designed electronic memo pad which can carry out the functions of a calendar, diary, address book, note pad and expense account log has been launched into the UK by Domicrest Ltd. The unit measures 136x90x9mm and will therefore fit in the pocket or the handbag. Called the Biztek Pad, it will be priced £69.95.

Comprising a potential memory of 4000 characters, the Biztek Pad is battery operated and combines a 43 key push button keyboard with a large LCD with 16 alpha-numeric characters, 20 numeric and clock digits and 45 special symbols.

One of the Biztek Pad's prime uses is as memory aid. By keying in important appointments such as weddings,

birthdays and anniversaries, and adding a date and a time and utilising the alarm function the pad can be programmed to sound the alarm at the appointed time. The necessary reminder can then be recalled to appear on the screen. The unit will store such reminders for up to twenty years in the future.

As a diary the unit will store any day-to-day events that the user need to recall. Appointments for the day or the week can be recalled and reviewed in the order in which they were entered. Additional functions are a calculator, a stopwatch and a permanent calendar and time display. A memory save switch ensure that stored items are not inadvertently removed when the batteries are changed.

For further information contact Kestrel Communications Ltd., Regent House, Manor Place, Sutton, Surrey SM1 4BB. Tel: 01643 9131.

## Pics On The Printer

Softest of Romsey have produced an interface to connect the Spectrum or ZX81 with the Tandy GCP-115, and more recently a screen copy program which enables the contents of the Spectrum's screen to be copied onto the Tandy printer (in use with the same interface).

The Softest interface is a package designed to cope with the 'handshake' protocols between the micro and the printer, with a set of machine code device drivers to control the movement of the printer's four coloured pens. High level packages supplied allow listing of BASIC programs between line numbers and use of printer control codes.


The package is suitable for text, plans, drawings, program listings, PCB layouts, graphic presentations, charts and oversize lettering.

The Screen Copy program allows a Spectrum screen to be copied onto the Tandy printer. The screen is scanned horizontally by software and the printer information sent to the printer in synchronisation, enabling text and graphics to be copied. Colours are mapped to the four colours available to the printer, the mapping of the colour's under the user's control. The Softest program can be merged with the user's own programs, and the ability to overprint means that large block letters can be produced in one or two colours.

Softest will be supplying programs to allow users to examine graphics on the screen and send plot data at higher resolution to the Tandy printer. This combines the speed of screen viewing with the high resolution of the printer.

The interface costs £35, including connectors, leads, cassette software, instructions, postage and packing. The screen copy program costs £5.00 (on cassette).

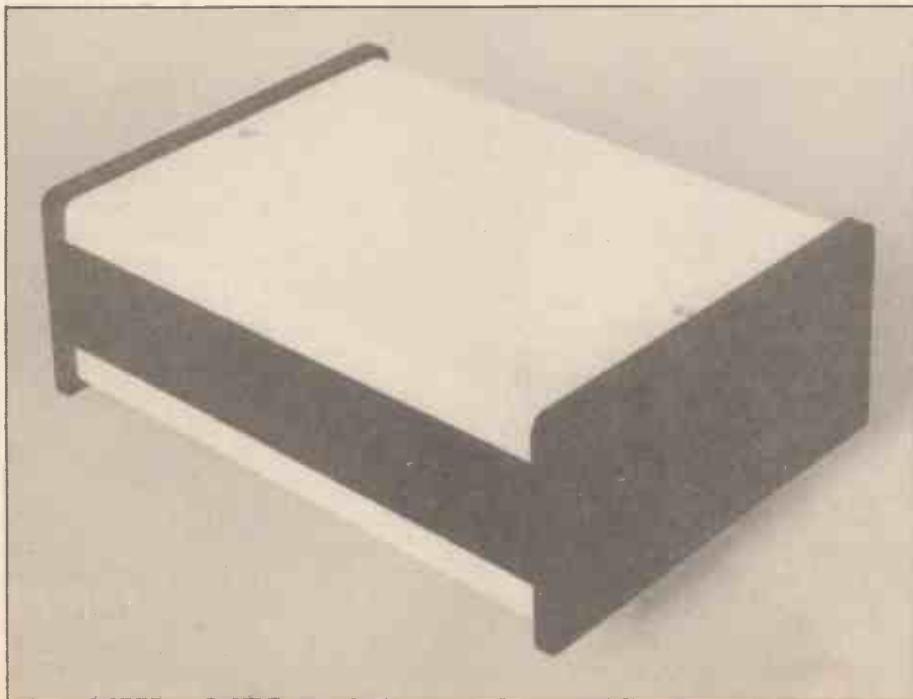Enquiries to Softest, 10 Richmond Lane, Romsey, Hants SO5 8LA.



# MONITOR

## Computer Chess

Eureka Electronics have a new, high-level chess computer to complement the rest of their range. The Novag Constellation is designed for enthusiasts playing at experienced club level. And it costs £149.95. That's all the information we have, but Eureka should be able to provide more details.

Advanced Computach is a chess computer with eight levels of play and an "incredibly strong program with an extensive opening book". Response time is from 5 seconds to fifteen minutes depending on level of play, and it costs £29.95. Computachess is a simple low-cost computer with a fast response time (a maximum of 45 seconds), and aimed at beginners and casual players. This one costs £24.95.

The Novag Micro II is a portable machine with eight levels, a varied opening book and take-back facility to re-play moves. This one provides a "strong challenge at all eight levels of play" and costs £49.95.


Further information from Eureka Electronics Ltd., 26 Castle St., Brighton, E. Sussex, BN1 2HD. Tel: (0273) 202016.

## Right, OK

New releases from OK Industries include a temperature controlled soldering station with tip mounted sensors and fast response and stability within 5% over 100 to 500°C. The mains powered unit comes with a 24V 48W low-leakage iron and is earthed for MOS and CMOS applications. The station iron has power and heater indications, proportional temperature control and a solder spool holder to take spools up to 7in (178mm) in diameter is also available.

The DE-720 is a flame-retardant ABS enclosure designed for data entry, keyboard or desk-top computer systems. 20in wide and 7in high to take 5¼ (U3) full, half or quarter rack frames, it is of modular construction so that all the panels can be easily removed for access and service.

A range of customizing services is

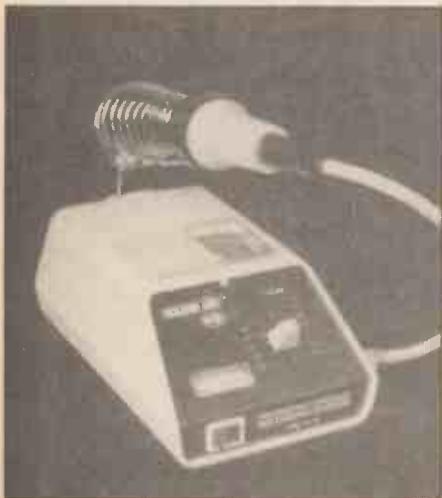

available, and features like bezels, control and connection openings or joysticks can be incorporated. There is even a choice of colours — the off the shelf colour is tasteful tan.

The SP-699 support unit is a mobile workstation with height adjustable between 555 and 780mm (with an additional 65mm if levelling feet or castors are used). Formica desktops and a mechanism to give ±18 degrees of tilt to the head are optional. Loads up to 50 kg can be carried.

Enquiries to OK Industries UK Ltd., Dutton Lane, Eastleigh, Hants SO5 4EE. Tel: (04246) 3993.



## Green On The Screen

Philips have introduced a low-cost video display TP 200 for personal computers. The mains-powered 12 in monochrome monitor has a composite video input compatible with most micro-computers including the Acorn/BBC Micro and Apple II. Crisp definition is achieved by the Philips green (P 31) anti-glare screen, which has 80 x 25 character resolution.

A useful design feature is an extendable stand fitting to the base of the display which enables the front of the unit to be raised tilting the screen to the correct angle for individual users.



Enquiries to Philips Digital Recording Department, c/o MEL, Manor Royal, Crawley. Tel: (0293) 28787.

## Going, Going, Gong

Siemens have developed an acoustic warning device for drivers which emits a signal as soon as reverse gear is engaged. The device is based on the SAB 0600 gong module, which emits a musical triad (a chord of three notes). The warning signal is triggered by the reversing-light switch.

Those who need to hire a car frequently are familiar with the problem of finding (or avoiding) reverse gear. Gear shift patterns differ from vehicle to vehicle, and the gear shift lever can be positioned in any of the corners of the gear shift pattern. It can be helpful if the action of selecting reverse gear is accompanied by an acoustic signal. A warning tone is always heard, irrespective of where the driver happens to be looking at the time. The SAB 0600 emits a triad from a very small and very compact loudspeaker. The three notes ensure that the signal cannot be obscured by any continuous tone.

The circuit requires very few external components. It comprises only ten items in addition to the gong module. The entire circuit is accommodated in a casing some 20x30x40mm.

For more information contact the Press Office, Siemens House, Windmill Rd., Sunbury-on-Thames. Tel: (09327) 85691.

# MONITOR



## Microprocessor DMM

Keithley's Model 175 is a microprocessor-based DMM offering six measuring functions and featuring many facilities that are normally found on high priced system DMMs. The measurement range is wide, giving 10uV resolution on DC to 1000V; AC measurements up to 100KHz using the TRMS convertor from 10uV to 750V; TRMS current from 10nA up to 10A; DC current from 10nA to 10A; Ohms from 10m up to 200M ten times more than conventional DMMs, dBs from -58dBm to -59.8dBm.

The internal processor enables the user to store a hundred readings in the built-in memory and monitor the maximum and minimum values at any time. There is no calibration pot in the 175; the calibration constants are held in the non-volatile memory, calibration can take place either from the front panel or over the IEEE bus. Security links are provided to defeat the digital calibration should this be required.

The 175 has a fast advantage with a 4½ digit LCD display. The display also carries a full set of annunciators to make it easy to use.

IEEE and battery options can be installed in the unit. The IEEE interface enables the user to program the range and take readings using simple bus commands. The battery pack gives field operation of up to six hours before recharge. Recharge takes place automatically when the instrument is switched on.

For further information please contact Keithley Instruments Limited, Boulton Rd., Reading, Berkshire. Tel: (0734) 861287.

## Sensible Authors

Microbooks, a newly established publishing company, has its first book coming out shortly. Entitled 'The Sensible 64' (128 pp, £5.95) and written by David Highmore, it is aimed at CBM 64 owners who have discovered this computer's many capabilities and want to expand their knowledge further.

David Highmore is currently writing a book using machine-code on the Dragon and this will be published in January 1984.

Microbooks are looking for new material for future books on all makes of home computer — any budding authors of either complete books or just individual programmes suitable for publication are invited to contact us at Microbooks, 443 Millbrook Rd., Southampton, SO1 0HX. Tel: (0703) 78020/1.

## Don't Move!

Riscomp have a number of additions to their range of security modules. Of particular interest is the US5063, an ultrasonic movement detection module which employs digital techniques for processing the received signal.

Such an approach has not only provided a superior performance analogue circuitry, but also allowed a choice of three levels of discrimination against false alarms. An exit delay and fixed alarm time have been incorporated together with a selectable entrance delay, whilst the transmitter section of the module being crystal controlled allows the use of several units, where large areas are to be covered, without inter-action problems. A 'hold' facility, together with a built-in LED indicator, is provided for setting up purposes.

Priced at £13.95 + VAT the module is supplied with a comprehensive Data Sheet. For further details please contact Riscomp Ltd., 21 Duke Street, Princes Risborough, Bucks HP17 0AT. Tel: (08444) 6326.

## A Rat's Nest

SF author Harry Harrison is one of several writers who have signed with a British publisher to create an entirely new form of fiction: using a home computer to take an active part in stories.

Harrison, best known for his 'Stainless Steel Rat' novels, is working with a computer programmer to create adventure game programs tied in with his own stories. Readers will be able to 'play' the scenes and determine the outcome.

The combined book and program package will be published early next year by a new company, Mosaic Publishing, which has been formed to produce books in combination with home computer software. The result will give a new meaning to the expression 'reader involvement': in future, authors may have to find out from their readers whether the hero got eaten or not... In addition to the Harry Harrison project, plans for 1984 include a package based on the 'Unorthodox Engineers' SF stories by Colin Kapp and a selection of children's, detective and educational non-fiction titles.

Sounds like a video game to me!

Enquiries to Mosaic Publishing Ltd., 187 Upper St., Islington, (land of the telephone call boxes and Hot black & Desiato), London, N1 1RQ. Tel: 01 359 7693.

## A Little Power

Edwards Electric, a small company specialising in low-voltage DC power supplies, mainly for education and industry, has produced a leaflet detailing their range of 2V to 65V supplies, providing a maximum power output of 4VA or 10VA. The units cost between £15.65 and £18.50 (plug provided), and the list is available if you send an SAE to Edwards Electric, P O Box 27, Unit 3, Mill Lane, Church St., Bridgewater, Somerset TA6 5AT. Tel: (0278) 421530.



# MONITOR



## Digital Thermometer

Candis Electronics have launched a new range of hand held digital thermometers. Their low cost model, the 1001, at £47.00 is designed for out of door and laboratory use. The casing is moulded ABS, the display is 3½ digit LCD, and all temperatures from -50°C to 1150°C can be measured, with automatic ambient and cold junction compensation. Candis also do a range of twenty standard probes, plus custom probes for special uses.

Leaflet and further information from Candis Electronics Ltd., Highdown Works, Highdown Avenue, Worthing, W. Sussex. Tel: (0903) 690750.

## Get Clamped

Electronic & Computer Workshop has available two forcep-type clamps in its range of high quality tools. These nickel-plated carbon steel clamps, designated PFC1 and 2, are 5in and 5½in long respectively and weigh about 30 gms. The jaws of these ratchet-operated clamps are cross-serrated, 15mm long x 4mm wide (type PFC1) or lateral-serrated, 25mm long x 3mm wide (type PFC2) and provide an extremely firm grip. Made entirely with a heat-conducting material, these clamps can be used as heat sinks, providing thermal shunting for delicate components during soldering. They are effective wire-clamps, and can be used to retrieve small articles from restricted areas, making a useful 'third hand'. Both types of clamp are £2.50 plus 45p p&p and VAT.

A 1000 watt dimmer kit is currently available priced from £4.33 to £13.80 for the suppressed version. These electronic dimmers incorporate a specially-designed circuit that frees them from hysteresis effect — in particular from switching systems. The dimmers are protected for use with drills and other inductive loads.

The unit has a 5 to 98 per cent regulation and is ideal for use with both resistive and inductive loads. The suppressed version is supplied with a toroidal choke.

A robust electrician's multimeter, the

Electro ISC, manufactured by Pantec, features a phase sequence and voltage indication. It also has overload protection which is given via both a fuse and neon discharger.

With a measured accuracy of two percent for DC and resistance and three percent for AC, this meter has a wide indicating range. It will measure DC voltages from 3 to 1000V, AC voltages from 15 to 1500V, DC and AC current from 3 to 30A and resistance from 0R5 to 1MR in two ranges. Overall dimensions are 130 x 125 x 40mm.

The Velleman four channel infra-red remote control priced at £38.58 plus £1.00 p&p and VAT, for the receiver and transmitter, is available in kit form.

The remote control which, with optional flip-flop ICs, provides a latched push-on/push-off function, may be used to operate several functions, including opening garage doors and for lighting control. Without the flip-flops the function is a straightforward on/off. Power switching relays may be connected directly to the output (50mA) if required. Maximum operating range is 20m.

The receiver pre-amplified is supplied in a screened box, which mounts onto a PCB with the remaining components, and a stabilised power supply operable from 12V to 14VAC supplies. A high degree of immunity to interference signals is provided with the use of coded signals.

The transmitter uses four power infra-red LEDs with reflectors, and comes complete with a compact styled case. Powered by a 9V battery normal operating life is approximately twelve months.

For further information please contact Caroline Stewart, Electronics & Computer Workshop Ltd., 171 Broomfield Rd., Chelmsford, Essex CM1 1RY. Tel: (0245) 62149.

## EPROM Eraser

Ground Control are offering an EPROM eraser for home computer owners (or other small-scale EPROM erasing operations). Their UVIPAC uses a low-profile transformer to attain the compact dimensions of 90 x 80 x 40mm

(cased). The unit can erase any three EPROMs or one CPU with an on-board EPROM in five to twenty minutes depending on type. The UVIPAC can be supplied with a built in fifteen-minute timer as an optional extra, and spare discharge tubes and conductive foam pads for loading the EPROMS can be supplied.

The standard UVIPAC costs £19.95 plus £1.95 p&p (UK only) and the timer version costs £24.95. Both prices include VAT. Overseas buyers please enquire, enclosing an IRC, for shipping costs. All enquiries to Ground Control, Alfreda Avenue, Hullbridge, Essex SS5 6LT. Tel: (0702) 230324.

## DIY Detector

C-Scope International, a leading manufacturer of metal detecting equipment, have produced a detector in kit form. The K5000 kit is designed for construction by the hobbyist with only a limited range of equipment and comes, say C-Scope, with a comprehensive construction and user's manual, so that even a beginner can be confident of success.

When complete, the K5000 is a six-control detector comparable to a £250 off-the-shelf model. We aren't told what the kit will cost, but you can enquire at your local hobby shop or direct to C-Scope International Ltd., Wotton Rd., Ashford, Kent TV23 2LN. Tel: (0233) 29181.



## A Day By The Sea

Taking a bold decision to put faces to some of the press releases, catalogues and trade circulars I wade through at *Monitor*, I ventured down to Brighton early in October to visit *Internecon*, one of the major trade hardware exhibitions and conferences.

My first response, after inveigling my way through the side entrance, was one of advanced sensory overload. The Metropole Hotel is a grand and plush building on the Brighton seafront, with a very large amount of exhibition space inside. Olympia it ain't, however, and most of the space is distributed in comparatively small parcels, with the effect of a monstrous technological termite nest.

However, having sorted that out, and discovered that, yes, the Press Office actually was under the stairs, although not the same stairs as originally indicated, I set out to circulate.

I retain the impression that the exhibition was around 40% industrial cables and connectors, and 40% custom mouldings machinery. The remainder, distributed seemingly at random, were dealing in small connectors and hand-tools of interest to home constructors.

What I wanted to find out was how these suppliers, who are normally geared up to dealing with industry, reacted to interest from amateurs, or if, indeed, they had a significant number of enquiries from amateurs. Particularly I had heard rumours that some firms set a high minimum-order value to forestall the classic handwritten-letter-and-postal-order request for one or two parts.

The picture that emerges is, as usual, somewhere between the extremes of wild enthusiasm and complete revulsion. While it is true that many firms set a minimum order value of, say, £50, this is less to discourage one-off orders than it is to encourage regular customers to order in packages which it's economic for the firm to handle (unlike HE, they can't tell their customers to 'send an SAE'), and often only applies to cash customers and not those with trade accounts or paying by credit card. Besides, these companies rarely deal in anything which the amateur could find a use for.

Believe me, industrial connectors are an art and science all to themselves.

Other companies, making mostly industrial goods but with some stuff useful to amateurs, have outlets through other distributors which

individuals can either access directly, or through local traders.

Some of them actually encourage amateur trade, and set up departments to deal with it.

**AB Engineering**, whose tools appear in *Monitor* from time to time, are one of such. They are, they tell me, going carefully but definitely into the amateur market. They will now take credit card orders, which are easier for all concerned. And they are going to be at Breadboard this year, so if you want to check out their range, this is the place to see them.

**Honeywell Control Systems** are in the rather different situation of not objecting to small orders, not pursuing small orders, and sometimes getting a rush of them unexpectedly — for instance, some time ago ETI published a light-pen project which generated a sudden demand for fibre optic links. *Monitor* has occasionally featured their touch-keypads. Honeywell have their own distributors, including RS, who you should be able to order from through your local electronics dealer.

**DAU**, who deal mostly in connectors, have a £50 minimum order limit, as it costs them too much otherwise, but automatically route any small orders to one of their distributors. **Swift-Sasco**, on the other hand, have a minimum cash-with-order value of only £5, and produce a catalogue. **Green Connectors** always refer enquiries to their distributors, and prefer not to have small order enquiries — this came as news to me, as we feature their projects from time to time. But news releases and product news is often handled by a PR company which spreads it more widely than the manufacturers realise.

(We get product news releases in this office which we would not dare to feature. Our readers would have a good laugh, and the manufacturers wouldn't thank us, either...)

**Bicc Vero Electronics** (close relations of Verospeed) who are best known for their project-boards and boxes, produce their own Hobbyist catalogues, with a department in charge of amateur orders, and there is no minimum order charge. They outlet a lot to the small constructor through local shops, and their stuff is used in schools and colleges.

**Litesold** on the other hand, are well known for their temperature-controlled soldering irons. I had always thought that they were mainly selling to home constructors, but not a bit of it. However,

they are one firm that is very definitely geared up to dealing with amateur orders, and occasionally do special offers for them (and they advertise regularly in HE, too).

Lest you be tempted to believe that it is only the amateur who is the victim of 'economies of scale', ie firms not catering for small buyers, I spoke later in the week to my sister, who buys components for a small electronics firm. She had also been to *Internecon*, searching for an economically priced flow-soldering machine (a device which solders a whole PCB in one go by washing a carefully-controlled ripple of solder over the underside of the board). Apparently, if you want to spend £5000 or £15000, you're well away, but if you only want to spend £2000 for a unit you can stand in the corner, the choice is pretty meagre. You think *you've* got problems!

The strategy to adopt if you want to obtain something from an unfamiliar source with no clear-cut ordering policy is to write to them with your enquiry and send an SAE — this is not to save the company money, as is popularly thought, but to save them the process of acquiring, typing out and stamping an envelope. The rule is this: for every part of the correspondence you can take out of *their* hands and see to yourself, your chances of getting a prompt and successful response increases. It's a by-product of Murphy's Law, and can be taken as fundamental without in any way derogating any company's order department. The other, related, rule, is to give as much useful information about your enquiry as possible. If this is beginning to sound like HE's Reader Services Page, it's because the same rules apply!

Oh yes — and when the time comes to send money, there's nothing wrong with the handwritten-letter-and-postal order, but print all part numbers etc., and cross your PO. For your own sake, it's safer if you use a cheque, and make a photostat or a carbon copy of your letter — if anything goes missing, it is then much easier to trace.

As a final thought, in case anyone is tempted to scorn their corner component shop, an acquaintance not entirely unconnected with a major aircraft concern with extensive dealing in both civil and military aviation are in the habit of nipping down to their local when they need a few bits for radio repairs and the like. It's the quickest way, they say, to get spares.

# MONITOR

## Speaking Spectrum

Currah Computer Components have produced a speech synthesis module for the Sinclair Spectrum.

Designed to be straightforward to use, the Microspeech gives a voice to all the keys on the Spectrum, requires no preprogramming, and can alter the intonation of sounds keyed in.

The technique used for building words is the now-established allophone system, which is flexible and allows an unlimited vocabulary — in English at least (I would be interested to know if anybody has succeeded in getting a speech synthesiser to produce reasonable results in any non-English language). It has a self diagnostic feature for syntax checking, microdrive capability and an audio output for use with hifi amp or tape recorder (immortalise your speeches).

The Microspeech costs £29.95 and comes with a demonstration and games cassette, and it will shortly be available for the ZX81, Oric, Dragon and BBC Micro.

Enquiries to Currah Computer Components Ltd., Graythorp Industrial Estate, Hartlepool, Cleveland.



## Interface The Facts

Sinclair Research have been busy: as well as their flat-screen television, newly come on the scene, they have launched the ZX Interface 2. The Interface provides the Spectrum with joystick and ROM cartridge facilities.

It's a solidly-built piece of equipment which plugs either directly into the Spectrum's rear expansion port, or the ZX Interface 1. There is a hinged porthole for cartridges, and two joystick ports for standard nine-way D plugs. The joystick ports are neatly covered with flush lids, which will, we anticipate, provide endless opportunity for losing them, as they are not hinged. We managed to lose three of ours within ten minutes of unpacking the unit, which is good going as there are only



two. In this respect, they have the same qualities as biro caps, only moreso. Still, this is only the preproduction model; perhaps they will think of something. Two lengths of strong elastic? Perhaps the easier option is just to let the covers go and give the unit a quick Hoover once a week.

all the ROM cartridges will work with a 16k Spectrum, even where the cassette version requires 48k — a real boon. Joysticks connected to the Interface will then work with ROM cart, cassette, or Microdrive programs. The Interface and cartridges are initially only available mail-order. We have been given the price £19.95 (inc. VAT but no mention of p&p) and suggest you contact Sinclair Research, Stanhope Rd., Camberley, Surrey GU15 3PS. Tel: (0276) 685311, for further information.

## Come In, Enterprise

The Elan Enterprise 64, announced as the first of a range of British home computers designed by Intelligent Software Ltd., boasts more built-in features than any other current machine in its class.

The Enterprise keyboard has sixty-nine full-travel contoured keys (like an electronic typewriter). Eight special 'user definable' keys allow you to write programs in which just one keystroke will carry out a number of commands.

The built-in joystick, on the right of the keyboard, is used for games and text manipulation, and two extra joystick sockets mean that games can be designed for three people.

The machine's memory — 64K RAM — lets you achieve the most from the outstanding colour graphics capability. It contains a unique memory controller and plug-in expansion system to allow

unrivalled RAM capacity. Providing more scope for helpful commands in the BASIC programming language, the Enterprise's large ROM (32K) also allows for a more powerful operating system.

The specially designed chips in the Enterprise are also noteworthy. The video chip (called 'Nick') gives the machine a tremendous flexibility in its screen display, and the sound chip ('Dave') handles the audio: four sound sources, each with full volume control on stereo output.

The built-in word processor handles word wrap, text centering, justification and paragraph moving, while its text handling makes it possible to choose a display with fifty-six lines on the screen — each with 84 columns.

In addition to the ability to generate stereo sound other outstanding features of new machine include a cassette loading meter, which helps you set the correct volume on the recorder, so that programs will load into the computer without difficulty.

Elan Computers are supported by Intelligent Software, who are putting together an extensive catalogue of software, written by them and by other software designers. Categories within the Elan Software range include video games, games of strategy, home applications, small business applications, educational programs and computer applications.

The Enterprise 64 and 128 models will reach the market early in 1984 and retail prices are from £200. Further enquiries to Elan Computers Ltd., 31-37 Hoxton Street, London N1 6JN. Leaflets are available.

The photograph shows a flexible connector linking the Enterprise to a 64K RAM expansion and a 3.5in microfloppy disk drive. New units can be plugged into the peripheral stack.



## Technology For Schools

**BBC School Radio** is breaking new ground with three series designed to prepare schoolchildren for the new technology, a computing series for junior schools, complete with software, and electronics series for junior schools and a microtechnology series for 'O' level and CSE students, complete with filmstrips and kits of parts. Working in collaboration with the Microelectronics Education Programme and the Department of Industry, School Radio hopes to make a major contribution to both teachers and pupils in their approach to the new technology.

The first series is *'Using Your Computer'*, a unit of five programmes in the *'Introducing Science'* slot for 9-12 year olds, which started on Tuesday, November 1 at 2.20 p.m. on Radio 4 VHF. This series will help teachers in primary and middle schools introduce children to the computers supplied to schools under the Dol 'computers in schools' scheme, the BBC Micro-computer, Model B, the Sinclair Spectrum and the Link 480Z. The series, which is designed for recording, offers a completely new dimension in educational broadcasting in which radio broadcasts are synchronised with computer software. The children cue the computer at the direction of the broadcast. In this way the computer is given a friendly voice which guides the children through the initial stages of the operation and application of the machine. Thus children learn to use a computer by using a computer. The software, consisting of four computer programs, costs £7.00.

*'Junior Electronic'* is a series for children in the same age range which starts the Spring term on Tuesday, February 28, at 2.20 p.m. on Radio 4 VHF. In the five programmes children are piloted through very simple practical work, learning to construct basic

electrical and electronic circuits on a specially designed circuit board. The circuit board is included in a special kit of parts, on sale from BBC Publications. The fifth broadcast is a Radiovision programme in which the children are shown the relevance of the real life applications of the circuits — why a street light lights up, how a burglar alarm works. The kit of parts, suitable for up to four children, costs £5.25 (there is a Dol subsidy of £1.50 on the first kit for each school). The Radiovision filmstrip costs £5.40.

Both *'Using Your Computer'* and *'Junior Electronics'* are designed so that they can be handled by teachers with little or no previous knowledge of the subjects. Each series is accompanied by very extensive teacher's notes.

Also in the Spring term is *'Microtechnology'*, ten programmes for 'O' level and 'O' grade CSE candidates starting at 10.45 a.m. on Friday, January 20. This series forms an introduction to basic microelectronics leading to ideas of control technology and is dependent on the medium of Radiovision (five of the programmes are Radiovision) associated with practical work. There is a kit of parts and a specially developed circuit board and power supply unit. (The kit is compatible with commercial prototype boards which schools may already possess). Computer software associated with the series will become available in the Spring. The Radiovision filmstrips cost £5.30 each. The kit of parts, suitable for use by up to three students, costs £18.50.

The series are produced by Arthur Vialls, and will be repeated in the autumn of 1984. For brochures detailing how to order suitable equipment for the series contact The BBC Press Office, 12 Cavendish Place, London W1.

## School PSU

Built for educational use, *PMF Design And Development's* twin channel power supply has been built to BBC School Radio specifications and passed by BBC Engineering, and is both physically and electrically robust, we are told. It is designed to fulfill normal power supply requirements for logic and analogue electronics courses.

The unit features twin 1A supplies separately switchable to 5, 9 or 12V. Supplies may be used independently, in common earth mode or to provide a split rail supply. Each supply has independent short circuit and thermal protection.

Regulation is better than 0.4% over full load range; ripple and noise is better than 12mV peak to peak at full load.

The price of the unit is £36.85 plus p&p and VAT. For quotation and specification contact *PMF Design and Developments Ltd.*, PO Box 5, Romford, Essex RM3 7LH.

## London Home Computer Show

Building upon the great success of the 1983 London Home Computer Show, the 1984 event is to be staged in the much larger New Hall of the Royal Horticultural Society, just around the corner from the Old Hall where the Show was held in 1983.

Staged just after Christmas, this will be the show for the micro hardware and software enthusiast wanting to try out and then buy the hardware or software of his choice. Its central location just behind Westminster's Victoria Street makes it ideal for visitors from London and the provinces, and is close to Victoria BR station.

Open from Friday January 6th to Sunday January 8th 1984 from 10 am to 6 pm each day except Sunday, when it closes at 4 pm, admission to the Show is £2.00 — under-sixteens £1.50.

Further enquiries to *ASE Ltd.*, Wolsey House, Wolsy Rd., Hemel Hempstead, Herts HP2455. Tel: (0442) 41221.

## Red, Amber, Green

*Vulcan Electronics*, a new company only doing mail order at the moment, have produced a car battery voltage monitor with a seven-LED display (two red ones, four green ones and an orange one). The monitor is built into a black box about 4 x 3 x 1½ in (97 x 73 x 37mm), and is connected up by means of two wires — very simple. It's suitable for positive or negative earth cars.


The unit costs £8.00 inc. p&p. Enquiries and orders to *Vulcan Electronics*, 32 Wigan Rd., Billinge, Wigan WN5 7XS.

# GET BIG POWER


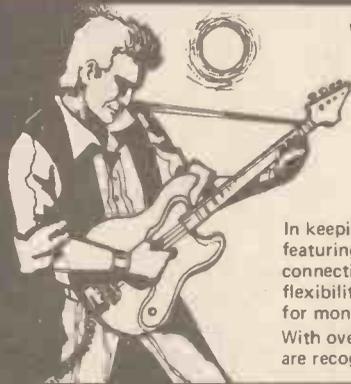
## Modular Amplifiers the third generation

Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



### WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



#### BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance $\Omega$	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
HY30	15	4-8	0.015%	<0.006%	$\pm 18$	76 x 68 x 40	240	£8.40
HY60	30	4-8	0.015%	<0.006%	$\pm 25$	76 x 68 x 40	240	£9.55
HY6060	30 + 30	4-8	0.015%	<0.006%	$\pm 25$	120 x 78 x 40	420	£18.69
HY124	60	4	0.01%	<0.006%	$\pm 26$	120 x 78 x 40	410	£20.75
HY128	60	4	0.01%	<0.006%	$\pm 35$	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	$\pm 35$	120 x 78 x 50	520	£25.47
HY248	120	4	0.01%	<0.006%	$\pm 50$	120 x 78 x 50	520	£25.47
HY364	180	4	0.01%	<0.006%	$\pm 45$	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	$\pm 60$	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15v/ $\mu$ s. Risetime: 5 $\mu$ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K  $\Omega$ . Damping factor: 100Hz >400.

#### PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU-30 is available purely for pre amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

#### Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

#### POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83
PSU 42X	1 x HY128	£15.90
PSU 43X	1 x MOS128	£16.70
PSU 51X	2 x HY128, 1 x HY244	£17.07

Model Number	For Use With	Price inc. VAT
PSU 52X	2 x HY124	£17.07
PSU 53X	2 x MOS128	£17.86
PSU 54X	1 x HY248	£17.86
PSU 55X	1 x MOS248	£19.52
PSU 71X	2 x HY244	£21.75

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

#### MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance $\Omega$	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
MOS 128	60	4-8	<0.005%	<0.006%	$\pm 45$	120 x 78 x 40	420	£30.41
MOS 248	120	4-8	<0.005%	<0.006%	$\pm 55$	120 x 78 x 80	850	£39.86
MOS 364	180	4	<0.005%	<0.006%	$\pm 55$	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20v/ $\mu$ s. Rise time: 3 $\mu$ s. S/N ratio: 100db

Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms. Input impedance: 100K  $\Omega$ . Damping factor: 100Hz >400.

#### 'NEW to ILP' In Car Entertainments

##### C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

Robust construction.

£9.14 (inc. VAT)

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 $\Omega$

Frequency response (-3dB) 15Hz to 30KHz. T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 80dB. Load Impedance 3 $\Omega$

Input Sensitivity and impedance (selectable) 700mV rms into 15K  $\Omega$  3V rms into 8 $\Omega$

Size 95 x 48 x 50mm. Weight 256 gms.

##### C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

Model Number	For Use With	Price inc. VAT
PSU 72X	2 x HY248	£22.56
PSU 73X	1 x HY364	£22.56
PSU 74X	1 x HY368	£24.20
PSU 75X	2 x MOS248, 1 x MOS368	£24.20

ILP Electronics Ltd., Dept 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England.  
Telephone: (0227) 547778 Technical (0227) 64723. Telex: 965780.

# Digital & Micro ELECTRONICS

No 1 WINTER 1983

An Argus Specialist Publication

£2.25


**Photographic Colour-Process Monitor: use your darkroom for accurate Spectrum**

**State Scope kit  
A low-cost high performance Solid**

**Build a low-cost joystick for the Video Genie**

**The BBC Finds Its Voice!  
Speech synthesis system for the BBC Computer reviewed**

**Spectrum Scanner  
X-Y Digitizer**

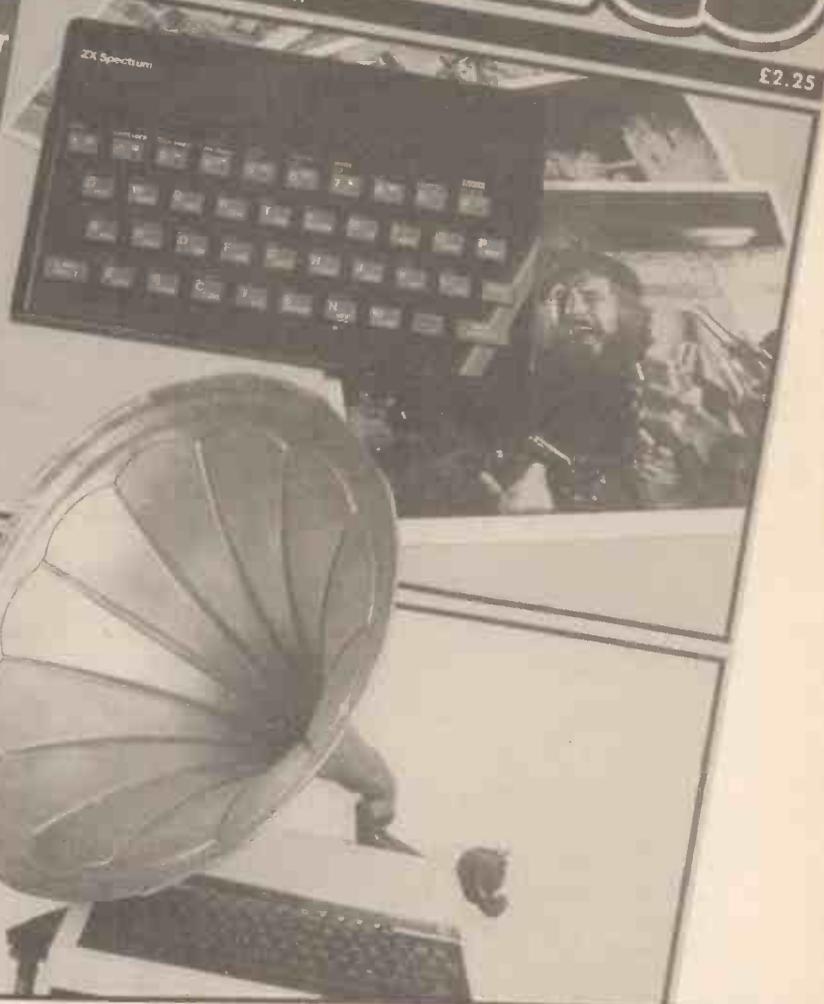

# NEW! OUT NOW

# POINTS OF VIEW

Feel like sounding off?  
Then write to the Editor stating your Point of View!

## Next Question . . .

*Dear Sir*  
*If you're short of material for HE might I suggest you reprint old projects (anything provided its nothing to do with !!\*\*\*!! computers, as every mag is crawling with them, micro this micro that. Thank goodness for Hobby, an analogue sanctuary. Although the beasts are creeping in).*

*And where's CD, is the Superhero of the Semiconductors recharging his ni-cads? Finally, why does everybody beg for lots of binders, one will do? I'll have to go now, my radio controlled gerbil has just eaten my best shoes.*  
*Yours constantly variable,*  
*P. Greenhouse,*  
*Kingstanding,*  
*Birmingham.*

This reader isn't happy with Excerpts From The Hobby Electronics Errata Box — he wants the original errors. Quick, nurse, the screens. However, for the mildly deranged, there is a source of HE reprints: it's called Electronics Digest, and can be found on your newsstands four times a year. Just to confuse the issue, the current ED has no Hobby reprints in it — but wait long enough and they'll soon come round again.

As for CD, at the last count he was nursing a badly sprained ankle somewhere in the Canary Islands. That was his story, anyway, but rumour has it that he was actually launching the first issue of *Digital And Micro Electronics*. Time alone will tell.

## No Joystick

*Dear Sir,*  
*I bought your August issue with the specific intention of making the joystick interface, but when I opened the issue I was faced with an incomprehensible component layout. Could you please send me separate component layouts for both side of the PCB, and the PCB foil patterns.*  
*Yours sincerely,*  
*G. Kelly,*  
*Limerick,*  
*Ireland.*

Sorry, but the PCB layout is copyright by Cambridge Computing, who designed the interface. If you write to them at 1 Benson St., Cambridge CB4 3QJ they may be willing to supply you with PCBs. Expect a delay in getting an answer, as demanded for the joystick interface has been vigorous.

## Now See Here

*Dear Sir,*  
*I have been a subscriber of yours for some time but I have a problem. Where can I get fibre optic cable from? I have looked through your magazine and can't find it anywhere. Perhaps you could help me.*  
*Yours hopefully,*  
*Richard Milburn,*  
*Burnham-On-Sea,*  
*Somerset.*

Our RS catalogue quotes part no. 367-909 for single core and 367-937 for double core optical cable, along with a bulkhead connector no. 456-403 and end-termination no. 456-396. You cannot of course order from RS directly but any reasonable components suppliers should be able to order for you. The Maplin catalogue also features optical cable under 'Fibre Optic Light Guide' on page 188. Maplin can be contacted at Maplin Electronic Supplies Ltd., PO Box 3, Rayleigh, Essex SS6 8LR. We would recommend that you find a local components supplier and get them to order for you, as an alternative to obtaining your own catalogue.

## A Poor Reception

*Dear Sir,*  
*I am writing for your help. Is it possible to use an aerial dish with my television, if so could you help me in finding one suitable as I've tried frantically in vain through all my electronics magazines and catalogues.*  
*And also would I need a special licence to use a dish as a television receiver.*  
*Thank you for any assistance.*  
*Yours faithfully,*  
*Martin Robertson,*  
*Glasgow.*  
*P.S. Keep up the good work! I enjoy your magazine very much.*

You don't say whether your question was sparked off by *Cable And Satellite Television* (HE September '83), but we'd like to think it was.

As public direct broadcast satellite TV has not yet begun in this country, there's no benefit in having a receiver dish unless you are a specialist hobbyist trying to catch continental programmes. It won't receive ordinary UHF transmissions. Likewise, the licensing terms have yet to be worked out. There is nothing to stop you from buying one (a few major

television/video stores in big cities can obtain them) but there is not a lot to use them on at present. All will become clear in the fullness of time as various new forms of transmission become established. Monitor will transmit whatever it hears as soon as it hears it, of course.

## Collector's Items

*Dear Sir,*  
*A subscriber to HE, some time ago I ordered all the backnumbers of HE from May '80 to January '82; I received all the backnumbers with the exception of February '81 and July '81. As a balance still stands in my credit side, I should like to ask you to send me photocopies of the two parts of the serial Into Electronics Construction, by Ian Sinclair, namely part 2 (March '80) and part 3 (April '80) to reach me by air.*

*How did I become interested in HE? By good luck! I entered the Mauritius Institute Public Library to cast a glance at Practical Philosophy Magazine, when I just came across some numbers of HE lying on the table. A student of Telecommunications Engineering, I plunged into the Electrical Components series and read about components not obeying Ohm's Law, that is, about diodes and transistors.*

*I could not believe that such a writer as Ian Sinclair existed in the world. I am temporarily handicapped, but I hope to order photocopies of the serial Into Electronics next year and some valuable missing parts. Clever Dick and Points Of View also make good reading. The way HE deals with electronics is praiseworthy. It takes the mystery out and puts it in its naked simplicity. HE is a great magazine. Please keep up the good work.*  
*Yours faithfully,*  
*I. Auleear,*  
*Fond De Sac,*  
*Mauritius.*

Ahem yes, as the backnumbers and photocopies are dealt with by different departments, if you order one and it is not available, the backnumbers dept. won't be able to supply a photocopy instead. When ordering backnumbers, always check on the ad. to see which ones we say are available. Save time and anguish.

We'll see about those photocopies although I can't promise anything about air mail.

You sound as if you may be interested in *Electronics Digest*, as featured in Monitor this month.

Ian Sinclair has oft been praised for his clear, down-to-earth approach to writing about electronics, through rarely in such extravagant terms! A writer who can make complicated things easy to follow has a worth far above rubies, perhaps even the equivalent of refined silicon (mind you, this has nothing whatsoever to do with what we pay him). Naked simplicity is perhaps going a bit too far. A fresh, new, unused resistor is nakedly simple. After that, things get interesting again (hence the need to consult such documents as *Practical Philosophy?* What next? *"Zen and the Art of Resoldering?"* *"Yoga and Relaxation for Fault-Finders?"* Why not?)

## Flatter Than Your Average Battery

Dear HE,  
A flat battery is not always a dead loss. Open the case with pliers (don't get acid all over yourself or your clothes), cut off the positive strip, then solder red and black wires onto the positive and the negative. Cover the connections over with insulating tape, and you end up with an almost free PP3 battery connector.



Yours faithfully,  
John Wardle,  
Doncaster,  
Yorkshire.

We always said it! HE readers do it with less . . .

## Missing Manual

Dear Sirs,  
I have just been given a Telequipment Serviscope D52 Dual Beam Oscilloscope, second hand of course, but there is no operator's manual. I want to write to Telequipment, but I can't find their address.

Keep up the good work.  
Andrew Pett,  
Norfolk,  
Dereham.

Can anybody help?

## Bowled Over

Dear Sirs,  
The Electronic Revolution article published in HE February '83 brought back many memories of the 1920 period when the wireless boom captured the imagination and crystal sets, then valve sets, were breathtakingly constructed on the kitchen table from diagrams published in the local paper. Yes, oscillation was a problem (when you got it to work) and yes, the headphones were placed in a basin as a loudspeaker until Dad was persuaded to buy a small Sterling speaker.

Since reading your articles and adverts enthusiasm boils again and I am truly amazed at the range and complexity of electronics today. I would like to construct a two transistor set using a small speaker. The kits advertised in your paper all seem to use headphones. I would be glad if you could help me on this.  
Yours faithfully,  
Charles Reid,  
Gateshead,  
Tyne & Wear.

We don't have any suitable projects, and can't advise on kits, but you could consult a small book published by Bernard Babani, *Electronics Simplified — Crystal Set Construction* (£1.75) or consult their catalogue to see if there is anything you prefer.

Unfortunately, adapting an amplifier designed for use with headphones to use with a loudspeaker is not a very simple job. I won't suggest getting a bigger basin!

BB's address is Bernard Babani (publishing) Ltd., The Grampians, Shepherd's Bush Road, London W6 7NF.

## Obscured Issue

Dear Editor,  
I have begun the 30V PSU project in HE September '83. However, upon making my PCB, it seems that there is an error involving the connection of the preset to the output.

The circuit diagram shows one side of the preset connected to IC2 pin 2, and emitter of Q3. The wiper arm then feeds the output. The other leg of the preset is then shown connected to the +ve side of the meter.

However, the PCB overlay does not correspond to this, as the wiper arm is shown to 'feed' the meter instead of the output.

I have been bying HE for a long time, but the clarity of the PCB overlay in the project is diabolical!

Could you please then clarify my query, and even perhaps enlarge or clarify the PCB overlay in the preset and transistor region.

Yours gratefully,  
M. S. Higgins,  
Hillsborough,  
Sheffield.

Unfortunately, the detail of the PCB

was obscured in the area of the preset by a line representing the wire joining the emitter of Q1 to the base of Q2. It thus appears that the preset is shorted out!

In fact the lower terminal of PR1 has simply been left open circuit, ie connected as a variable resistor. The wiper of PR1 does feed the meter, but electrically this is equivalent to the arrangement shown in Figure 1, and therefore is of no consequence.

## Alternative Technology

Dear Sir,  
As a regular reader of your magazine I notice what appears to be a growing interest in alternative energy. One reader writes enquiring about the purchase of Solar Heat Panels, another about a windmill generator using a car alternator. May I advise readers to write to 'Sun, Wind and Water', The Centre For Alternative Technology, "Machynlleth", Powys, South Wales. They are a conservation group who specialise in this field.  
Yours sincerely,  
K. Vitty,  
Huntingdon,  
N. Yorkshire.

## Lost And Found

A reader has written to ask if we know the present address of Doram Electronics Ltd., or whether they are still trading. Can anyone help?

In response to an enquiry last month, we have heard reports that T. Powell is still in business at 311 Edgware Road, London W2 (where else?). Tel: 01723 9246.

Reader A. Pickard of 14 Far Lash, Burbage, Hinckley, Leicestershire LE10 2PJ reports that he is interested in the use of the Science Of Cambridge (Sinclair) MK14 Micro for interfacing with the BBC and for robot control, and would like to hear from anyone working on similar projects.

A reader from Kingston On Thames wants to know if anyone knows of a firm making a 'bleeper finder' for locating lost carkeys and the like. We haven't had any success. Do you know?

For interested people, the Centre For Alternative Technology deals with all kinds of alternative technology and also welcomes visitors — their brochures can be found in tourist offices all over Wales, if you are passing through.

## Short Circuit Authors

Please will contributors G. Foote and B. Adams get in touch with us.

# COMING SOON TO . . .

# Hobby Electronics

## INFRA RED CAMERA CONTROL

Any camera which can be remotely released using an electric release facility should be able to operate with this infra red remote control. The control uses an AC, directional system with a range of about seven metres. The IR signal can be transmitted through glass as well as in the open, and multiple receiver units can be triggered by the same transmitter if required for more than one camera. A major photographic project.

## CB FIELD STRENGTH METER

This is a field strength meter with an extra feature. Usually, field strength readings have to be taken beside the transmitter, so that the operator can see the meter. Ideally, the readings would be taken further away, to give a true picture of the signal being transmitted. The HE meter includes a simple memory circuit, which holds the reading for a minute, enabling the operator to set it up well away from the transmitter.

## CAREERS IN ELECTRONICS

Our three part look at the Armed Forces continues with the Royal Navy.

## A BATTERY GUIDE

Britain's leading battery manufacturer, Ever Ready, explains the working and uses of a battery of batteries.

## GENERAL PURPOSE POWER SUPPLY

This is a versatile power supply suitable for use with Hobby Electronics projects past and future. It is also in effect the first part of a major audio preamp project to be featured in coming months (although an independent unit). It features two outputs, and a connection for a daughter board so that the PSU can be customised for special applications.

Please reserve me — copies of the February issue

**Hobby  
Electronics**

for  
Name .....

Address .....

.....

.....



**Hobby  
Electronics**

**February Issue on sale at  
your newsagent from 13th  
January. Place your  
order now!**

Although these articles are being prepared for the next issue, circumstances may alter the final content.

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

# Sparkrite

SELF ASSEMBLY ELECTRONIC KITS

PRICES REDUCED  
ON SUPER SAVE  
D.I.Y. KITS



## SX 1000 Electronic Ignition


- Inductive Discharge ● Extended dwell circuit stores greater energy in coil ● Three position changeover switch ● Patented clip-to-coil fitting ● Easy to assemble, easy to fit ● Contact breaker triggered - includes bounce suppression circuit.

**SUPER SAVE**

## SX 2000 Electronic Ignition

- Reactive Discharge ● Combines inductive & capacitive energy storage ● Gives highest possible spark energy ● Patented clip-to-coil fitting ● Easy assembly sequence ● Contact breaker triggered - includes bounce suppression circuit.

**SUPER SAVE**

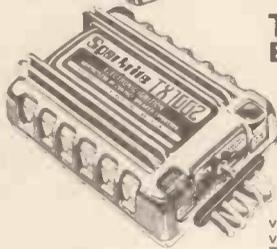


## TX 1002 Electronic Ignition

- Inductive discharge ● Extended dwell circuit stores greater energy in coil ● Three position changeover switch ● Contactless or contact breaker triggered ● Clip-to-coil or remote mounting ● Rugged die-cast case ● Contactless adaptors included for majority of 4 & 6 cylinder vehicles ● Easy to build ● For details of vehicles fitted by contactless trigger, ring Technical Service Dept on (0922) 611338-9.
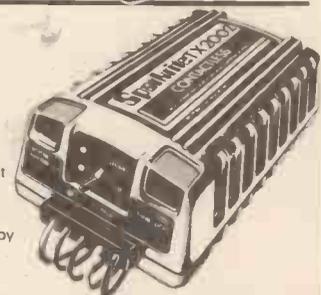
## TX2002 Electronic Ignition

- Two separate systems in one unit! ● Reactive Discharge OR Inductive Discharge, with three position changeover switch ● Gives highest possible spark energy ● Clip-to-coil or remote mounting ● Rugged die-cast case ● Contactless or contact breaker triggered ● Contactless adaptors included for majority of 4 & 6 cylinder vehicles ● For details of vehicles fitted by contactless trigger, ring Technical Service Dept on (0922) 611338-9.



## AT-40 Electronic Car Alarm


- Guards doors, boot, bonnet from unauthorised entry ● Armed/disarmed using concealed switch ● 30 second delay-to-arm: 7 second entry delay ● Can alternatively be wired to exterior key switch ● Flashes headlights & sounds horn intermittently for 60 seconds when activated ● Security loop protects accessories ● Low consumption C-MOS circuitry.



**NEW**
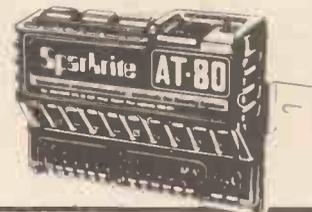
## AT-80 Electronic Car Security System

- Guards doors, boot, bonnet from unauthorised entry ● Armed/disarmed from outside vehicle by magnetic key fob passed across sensor pad adhered to inside of windscreen ● Individually programmable code ● 30 second delay-to-arm ● Flashes headlights and sounds horn intermittently for 60 seconds when activated ● Security loop protects accessories ● Function lights to assist setting-up ● Low consumption C-MOS circuitry.



**SUPER SAVE**

## ULTRASONIC Intruder Detector

- Supplementary to AT-40 & AT-80 ● Will work in conjunction with any door switch input or voltage sensing alarm ● Detects attempted break-in and movement within passenger compartment & triggers alarm ● Includes high efficiency ultrasonic transducers ● Crystal controlled for low drift ● Ingenious sensitivity control allows freedom from false alarms ● Low current consumption



**NEW**

## VOYAGER Car Drive Computer

- 12 functions centred on Fuel, Speed, Distance and Time ● Single chip microprocessor ● Large high brightness fluorescent display with auto-dimming feature ● High accuracy distance & fuel transducers included ● Displays MPG, L/100km and miles/litre at the flick of a switch ● Visual & audible warnings of excess speed, ice, lights-left-on ● Independent LOG & TRIP functions ● Low consumption crystal controlled circuitry.



**SPECIAL OFFER**  
"FREE" MAGIDICE KIT WITH  
ALL ORDERS OVER £40.00



## MAGIDICE Electronic Dice

- Triggered by waving hand over dice ● Completely random selection ● Bleeps & flashes during 4 sec tumble ● Throw displayed for 10 seconds then flashes to conserve battery ● Low consumption C-MOS circuitry.

**SUPER SAVE**

SPARKRITE (A Division of Stadium Ltd.), 82 Bath Street, Walsall, WS1 3DE England Tel: (0922) 614791

Allow 28 days for delivery

KIT	OLD PRICE	NEW PRICE
SX 1000	<del>£12.95</del>	£11.95
SX 2000	<del>£19.95</del>	£18.95
TX 1002	£22.95	£22.95
TX 2002	£32.95	£32.95
AT-40	—	£9.95
AT-80	<del>£32.95</del>	£24.95
ULTRASONIC	—	£17.95
VOYAGER	£64.95	£64.95
MAGIDICE	<del>£9.95</del>	£6.95

PRICES INC. VAT, POSTAGE & PACKING.

PHONE YOUR ORDER WITH



NAME \_\_\_\_\_ HE/1

ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ \_\_\_\_\_ KIT REF. \_\_\_\_\_

CHEQUE No. \_\_\_\_\_

**BRANDLEADING BRITISH ELECTRONICS**

**CUT OUT THE COUPON NOW!**

# SLOT CAR LAP COUNTER

The chequered flag drops and they're off and racing in the 1984 British Grand Prix . . . or is it the Le Mans 24 Hour? Count down to the finish line and flag the winner with this clever project.

Original circuit by Steven Devaney  
Development by Ram Chandru  
Text by Barry Foster

The original design of this project was for a lap counter and winning car detector for a fixed six-lap car race. This seems a little inflexible, so we decided to add a facility for selecting any number of laps between one and nine. This was easily achieved with the addition of just two low cost CMOS ICs and a double pole nine-way switch. Certain other refinements to guarantee reliability and to avoid ambiguity, were needed; and the odd gates remaining were used to add "bells and whistles", to make the working item just a bit more interesting!

The final design permits a race of between one and nine laps, with a lap counter for each car and positive detection of the winning car — a draw is not possible. The winning car is indicated by a flashing LED and a pulsed audio tone signals that the race is over. In addition a short audio tone sounds each time a car completes a lap.

An overflow of the design, in terms of circuit blocks, is given in the "How It Works" box.

## The Details

The full circuit of the Lap Counter is shown in Figure 1. The input sensors are magnetic reed relays, fixed to the tracks exactly on the Start/Finish line and triggered by small magnets glued underneath the racing cars. Each switch is by-passed by a capacitor, C10 and C11 respectively, to eliminate contact bounce and produce reliable low-going pulses each time a switch is closed. These pulses are fed to one or the other of a pair of input



Scaletric slot cars from Hamleys of Regent St.

gates, IC5a and b; these gates are enabled after Reset by a low from IC8d, pin 11. So as the pin 1 or 13 inputs go low, the gate outputs go high. ICs 1 and 2 count these pulses and produce outputs to drive the seven-segment LED display ICs, producing a continuous lap count for each car.

The high-going pulses from the input gates are also fed to IC5c. Between laps both inputs will be low so the output at pin 4 will be high; but when one car or the other completes a lap, either pin 5 or 6 will go momentarily high, taking the output low and triggering the one-second monostable flip flop formed by ICs 8a and 9a. Before triggering pins 8 and 9 of IC9a are both pulled low by pull-down resistor R23, so its output will be high; and with two high inputs the output of the NAND gate IC8a will be a low.

When pin 6 goes momentarily low,

pin 4 of IC8a will therefore go high. The voltage across a capacitor cannot change instantly, so this high is applied to pins 8 and 9, IC9a, forcing pin 10 low. This is fed back to the other input (pin 5) of IC8a, ensuring that its output stays high even after the lap pulse has ceased. Meanwhile the high on pins 8 and 9 falls off as C5 charges from IC5c; the time constant of C5 and R23 has been chosen so that the voltage takes about one second to drop below the high logic threshold, and when pins 8 and 9 drop below this level pin 10 switches high again.

At this time the output from IC8d, pin 11, is still low so the output from NAND gate IC8b will be held high. Thus both inputs to IC8c are high until the monostable is triggered at the completion of a lap, at which time pin 8, IC8c goes low for one second. The output of IC8c will therefore go high, and this is inverted by IC9b and

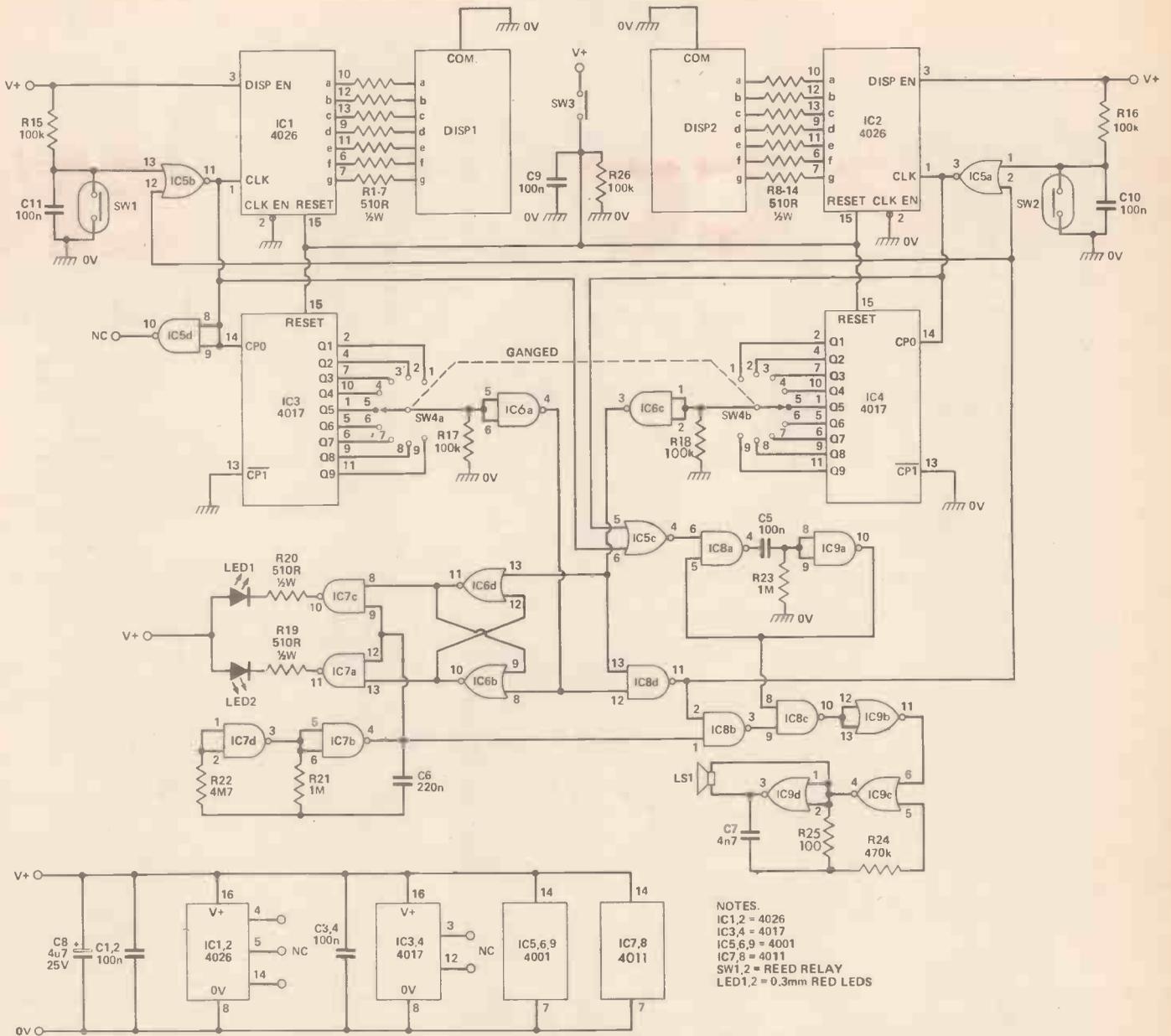


Figure 1. The circuit of the Lap Counter comprises two identical counting and display blocks, together with the win detection and indicator circuits, below.

Figure 2. The pin-outs of the 0.43" Common Cathode display IC.

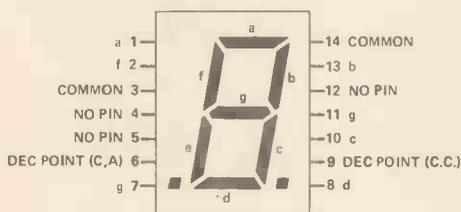


Table 1. Memory refresher — logic truth tables for AND, NAND, OR and NOR gates.

Table 1					
A	B	A.B	A.B	A+B	$\overline{A+B}$
0	0	0	1	0	1
0	1	0	1	1	0
1	0	0	1	1	0
1	1	1	0	1	0

triggers the 1kHz audio tone generator formed by ICs 9c and 9d, which sounds for around a second.

Backtracking a little, the high-going lap pulse from ICs 5a and 5b are also fed to a pair of 4017 decade counters, ICs 3 and 4. These devices have ten outputs which go high one after the other, taking ten clock pulses to cycle through a count from one to ten. However only nine outputs are used by this circuit with the output corresponding to the number of laps making up a race selected by SW4. The Q0 output goes high on the tenth clock pulse, so this is the one neglected by the circuit; also, lap selection for each car is performed by a dual ganged switch, which makes it impossible to cheat by selecting, say eight laps for one car and nine for the other!

After the preselected number of laps have been completed the inputs to either IC6a or IC6c will go high, depending on which car was fastest;

these inputs are normally pulled low by R17, 18, so the output of one or the other will switch from high to low.

Now IC8d has one low input, so its output will go high, and this is applied to the enabling pins of gates 5a and 5b which, being NOR gates, will be locked up with a low output until the circuit is reset.

The high from IC8d also gates a 1Hz squarewave from ICs 7b, d through IC8b; and then through IC8c (because pin 8 is high), thus sounding the 1kHz tone at 1Hz pulsed intervals to indicate the end of the race.

Meanwhile the output from either IC6a or 6c has tripped the latch formed by ICs 6b and 6d. Before this pins 8 and 13 are high, so the output from each gate will be low. However when one of the inputs from 6a or 6c goes low, the corresponding output will immediately switch high and, since the outputs are cross-coupled to the other gate's spare input, the second, losing gate, stays low.

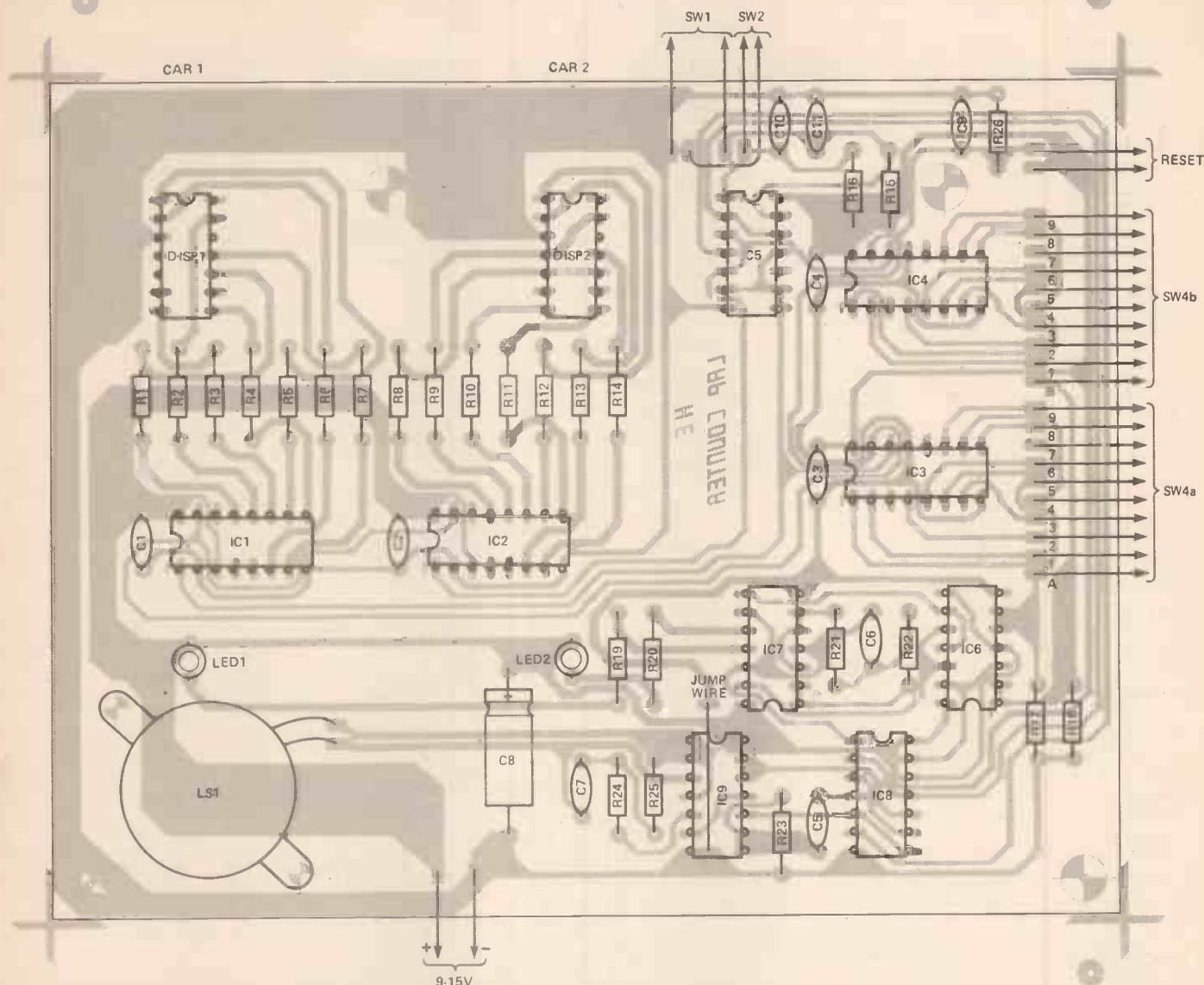


Figure 3. The PCB component overlay; most components are mounted on the board, including the piezo sounder. The power supply must be between 9V and 15V DC but does not have to be regulated.

## Parts List

### RESISTORS

(All 1/4 watt 5% unless noted)  
 R1-R14, 19, 20 ..... 510R 1/2W  
 R15-18 ..... 100k  
 R21, 23 ..... 1MR  
 R22 ..... 4M7  
 R24 ..... 470k  
 R25, 26 ..... 100k

### CAPACITORS

(Miniature layer unless noted)  
 C1-5, 9-11 ..... 100n  
 C6 ..... 220n  
 C7 ..... 4n7  
 C8 ..... 47u  
 25V axial electro

### SEMICONDUCTORS

IC1, 2 ..... 4026  
 decade counter/divider  
 IC3, 4 ..... 4017  
 decade counter

BUYLINES ..... page 26

IC5, 6, 9 ..... 4001  
 quad 2-in NOR  
 IC7, 8 ..... 4011  
 quad 2-in NAND  
 DISP 1, 2 ..... 0.43in  
 7-segment LED display  
 LED1, 2 ..... 0.2in  
 any colour

### MISCELLANEOUS

SPK1 ..... PB2720  
 piezo sounder  
 SW1, 2 ..... reed relay  
 SW3 ..... SPST  
 push-to-make momentary  
 SW4 ..... DP9-way  
 rotary  
 2 x 3.5mm jack sockets for sensors  
 connections; 2 x 4mm sockets for  
 power supply connections; case,  
 215 x 130 x 47/78mm, eg Maplin  
 M1006; small magnets; red filter  
 plastic; nuts, bolts, wire, solder etc.

Finally the high from the winning side of the latch gates the 1Hz squarewave through either IC7a or 7c to flash the LED and indicate which of the two cars has won.

The only other point to mention is the reset system, operated by SW3; when pressed, this applies a momentary high pulse to the reset inputs of ICs 1, 2, 3 and 4; when reset the outputs of these ICs set up the conditions for the remainder of the circuit so that all logic levels are ready for the race to begin.

## Construction

The PCB designed for the Lap Counter (see Figure 3) makes assembly of the electronic parts relatively easy. The board is single sided, with just one wire link running under IC8 — don't forget it! Nearly all components, with the exception of the reset and lap selection switches, power supply and sensor connectors, are mounted on

the board. No special precautions are needed when assembling the PCB, other than the usual CMOS handling procedures and taking care that polarised components (ICs and LEDs only, in this case) are correctly oriented. IC sockets can be used if desired, and the LED leads may need to be extended so that they project at least 10mm above the surface of the board; use Veropins soldered into the PCB and solder the LEDs to the Veropins to reach the correct height.

The PCB bolts onto the front panel of the case, so the next step is to mark out the position of all holes and cut-outs on the panel. Use the full sized PCB mask reproduced on page 64 as a template for this operation: if you are making your own PCB from the mask then trace out the perimeter of the board, the position of the LEDs, dimensions of the display holes and the position of the mounting holes, and use the tracing paper as the template. Also a number of small holes should be drilled in the panel immediately above the piezo sounder, to act as a speaker grille.

The prototype was nicely finished by spray painting the case and labelling the various controls and functions with rub-down lettering; this should be done before mounting the components on the panel.

If the recommended case is used, the PCB must be mounted to one side, leaving space at the other end for the reset and lap-select switches. There is plenty of room under the board for the power supply and lap-sensor connectors.

After completing the PCB and preparing the front panel, the off-board components can be wired in. We used Molex plugs ('PCB connectors') for neatness and convenience, though of course the switches etc can be hard wired; in either case be sure to make the connecting wires long enough (ribbon cable makes a neat job of it).

When this stage is finished the project is more or less complete. Test it by connecting up a power supply (this can be any unregulated DC voltage between 6V and 15V, capable of supplying at least 100mA) and switch on. There should be a short 'beep' and the display will light up with a random number. Reset; select a high lap number and then briefly short out one of the lap sensor inputs, then the other. In each case a short beep should be heard and the relevant lap counter advance from '0' to '1'. Continue to pulse the input by shorting it briefly; the lap counter should advance until the selected number is reached, at which point the appropriate LED will begin to flash and the sounder to beep at 1Hz intervals. Repeat this test with the other input, and then for each input on each of the lap numbers. This checks out every possible variation!



Now the components can all be mounted in the case; the PCB is fixed on 15mm spacers to set the correct distance of the displays and LEDs. The


## How It Works

The Lap Counter can easily be broken down into a number of distinct circuit blocks. Many of these are duplicated, for each car and track.

The inputs from the lap sensor are fed via a normally enabled gate to counter/driver circuits, which feed seven-segment LED display clips producing a lap count for each car. The lap sensors also trigger a one second monostable flip-flop, which sounds an audio tone each time a car completes a lap.

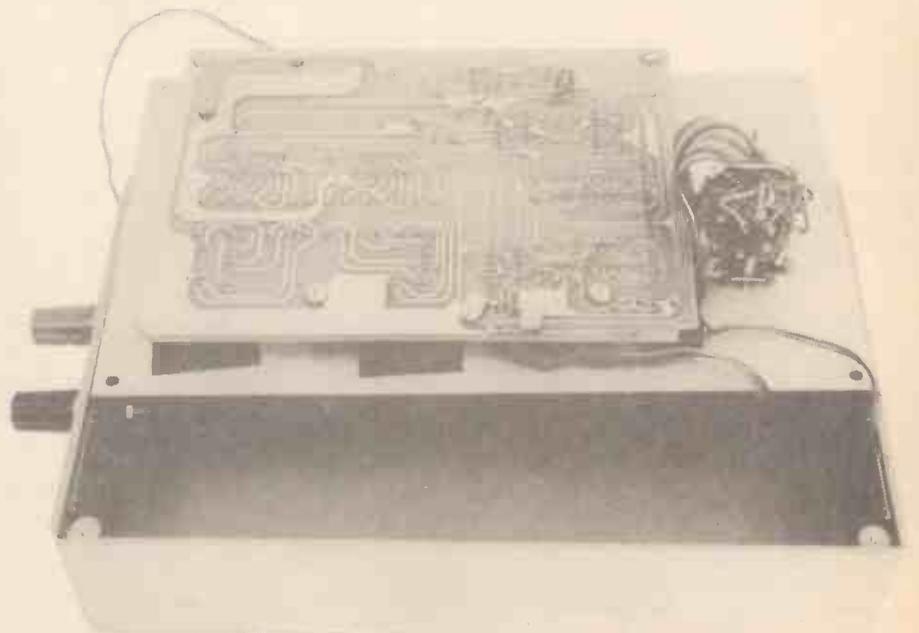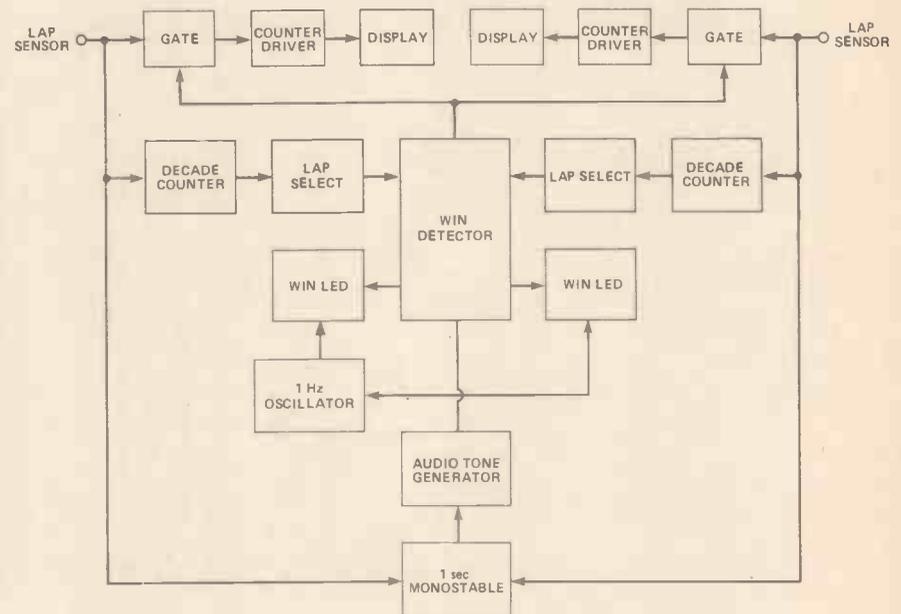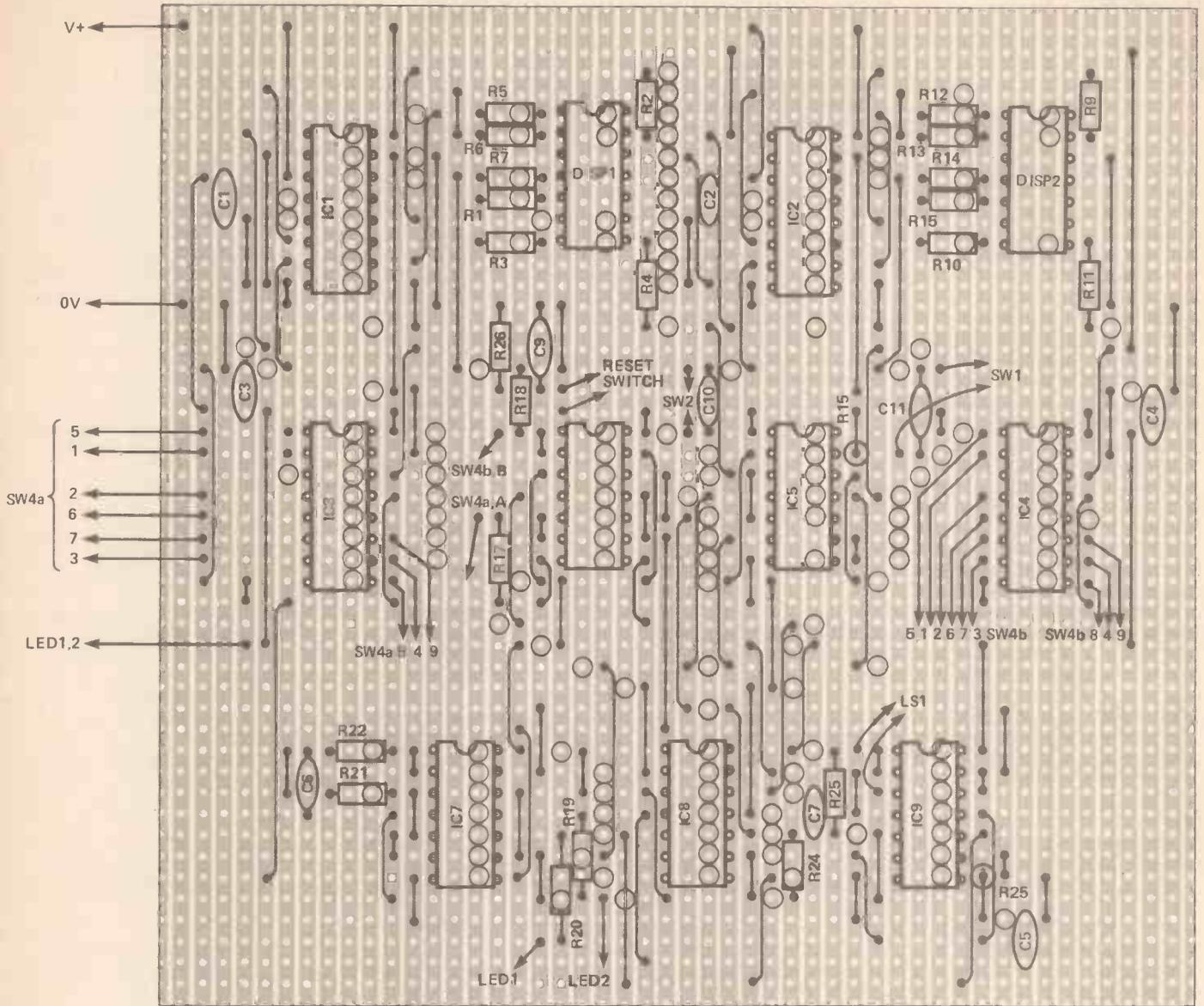At the same time, the lap pulses drive decade counters whose outputs are tapped by the lap-select switches. When the preselected number of laps have been completed, the win detector is triggered; a flashing LED indicates the winning car and a pulsed audio tone signals the end of the race. An output from the win detector is fed back to the input gates so that the pulses from the losing car are locked out.

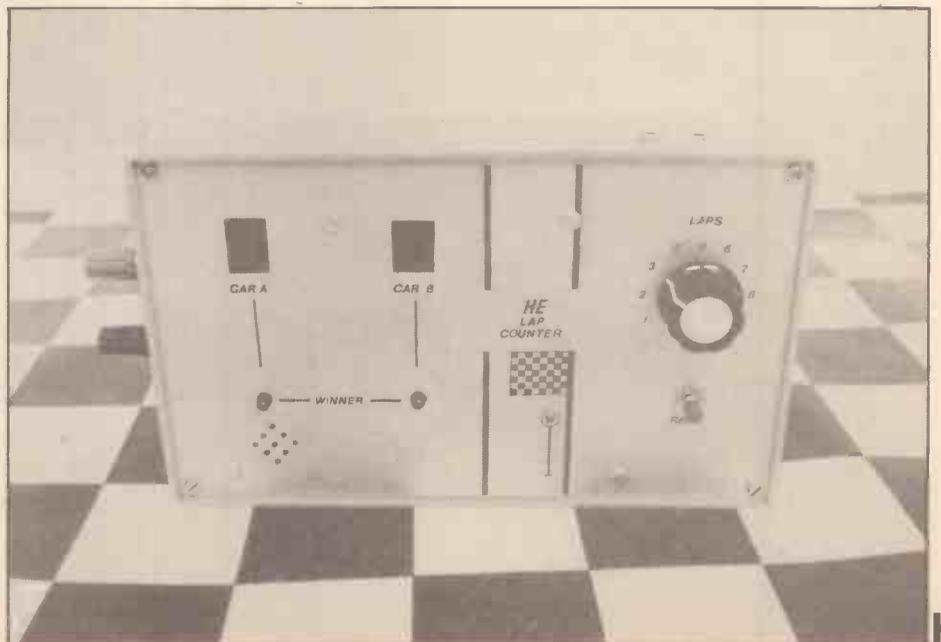




**Figure 4. Veroboard component layout for intrepid experimenters; it has not been constructed and tested, and so cannot be guaranteed to work — see also the note below! Stop Press: C8, which should be connected across the DC supply rails, has been omitted.**

final steps are to mount the reed relays on the slot car tracks and to fix the trip magnets under the racing cars. We have no advice to offer here, as the arrangement will depend entirely on particular cars and layouts. All you need then is the theme music from "Grand Prix"!

*Note: A Veroboard layout for this project has been designed but not tested. It must be regarded as an experimental layout, only, and Hobby Electronics will not be able to advise on constructional problems using the Veroboard. Also more off-board wiring is required and, possibly, a larger case.*




# FREE GREEN CATALOGUE

SEND SAE TODAY
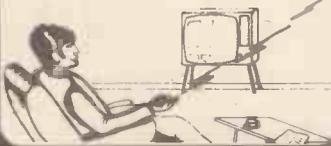
## HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting

- TDR300K Remote Control Dimmer Transmitter for above **£4.20**
- TK6 Touchdimmer **£7.00**
- T5300K Touchswitch **£7.00**
- TDE/K Extension kit for 2-way switching for TD300K **£2.50**



## DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week



Price **£15.50**

# CHRISTMAS PRESENTS GALORE

### 3-NOTE DOOR CHIME

Based on the SA80600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (195 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS. Order as XK102. **£5.00**

### LIGHT DIMMER KIT

Contains all components, including front panel and knob, to make a dimmer for lights up to 300W. **£3.50**

### MW RADIO KIT

Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2 cms. Requires PP3 9V battery. IDEAL FOR BEGINNERS. **£5.00**

### LCD 3 1/2 DIGIT MULTIMETER

16 ranges including DC voltage (200 mv-1000 v) and AC voltage, DC current (200 mA-10 A) and resistance (0.2 M) + NPN & PNP transistor gain and diode check, input impedance 10M. Size 155x88x31 mm. Requires PP3 9V battery. Test leads included. **ONLY £29.00**

## BEGINNERS STARTER PACKS

Containing selection of electronic components including transistors, LEDs, diodes, capacitors, ICs etc. together with a descriptive booklet with 10 easy-to-build projects plus a solderless circuit board enabling the components to be re-used. Requires 9V battery. Discreet component pack (no ICs) **£5.00** Integrated circuit pack **£6.00**

## STOCKING FILLERS All full spec. branded devices.

- PACK (1) 650 Resistors 47 ohm to 10Mohm — 10 per value **£4.00**
- PACK (2) 40 x 16V Electrolytic Capacitors 10µF to 1000µF — 5 per value **£3.25**
- PACK (3) 60 Polyester Capacitors 0.01 to 1µF/250V — 5 per value **£5.55**
- PACK (4) 45 Sub-miniature Presets 100 ohm to 1 Mohm — 5 per value **£2.90**
- PACK (5) 30 Low Profile IC Sockets 8, 14, and 16 pin — 10 of each **£2.40**
- PACK (6) 25 Red LEDs (5mm dia.) **£1.25**

# NOW OPEN COMPUTER SHOWROOM

JUPITER ACE · SPECTRUM  
ORIC 1 · BBC (Model B)  
DRAGON 32

## ELECTRONIC LOCK KIT XK101

This KIT contains a purpose designed lock IC, 10-way keyboard, PCBs and all components to construct a Digital Lock, requiring a 4-key sequence to open and providing over 5000 different combinations. The open sequence may be easily changed by means of a pre-wired plug. Size: 7 x 6 x 3 cms. Supply: 5V to 15V d.c. at 40µA. Output: 750mA max. Hundreds of uses for doors and garages, car anti-theft device, electronic equipment, etc. Will drive most relays direct. Full instructions supplied. **ONLY £10.50**

Electric lock mechanisms for use with latch locks and above kit **£13.50**

## DISCO LIGHTING KITS

DL1000K This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. **£14.60**

DL2100K A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. **Only £8.00**

Optional opto input DLA1 Allowing audio ("beat") —light response. **60p**

DL3000K This 3 channel sound to light kit features zero voltage switching, automatic level control & built in mic. No connections to speaker or amp required. No knobs to adjust — simply connect to mains supply & lamps. (1Kw/Channel) **Only £11.95**

FAST SERVICE · TOP QUALITY · LOW LOW PRICES

No circuit is complete without a call to —

# TK

## ELECTRONICS

11-13 Boston Road  
London W7 3SJ

Add 65p postage & packing + 15% VAT to total Overseas Customers: Add £2.50 (Europe), £6.00 (elsewhere) for p&p Send S.A.E. for further STOCK DETAILS. Goods by return subject to availability.

OPEN

9am to 5pm (Mon to Fri)  
10am to 4pm (Sat)

ALL PRICES EXCLUDE VAT



HE

<p>7 HUGHENDEN ROAD, HASTINGS, SUSSEX. TN34 3TG Telephone: HASTINGS (0424) 436004</p>					
<p>Post &amp; Packing 50p for KS kits, 75p for UK kits, £1.00 for Cabinets. Send 20p S.A.E. for catalogue of our extensive range of kits &amp; Cabinets. Trade, Educational &amp; Export enquiries welcome.</p>					
<p>KS 100</p> <p>MINI VHF SUPER-REGENERATIVE RECEIVER 88-108 MHz 9V D.C. £ 5.27 inc V.A.T.</p>	<p>KS 238</p> <p>3 CHANNEL MICROPHONE OPERATED SOUND TO LIGHT. 300W PER CHANNEL, 240V A.C. £ 11.58 inc V.A.T.</p>	<p>KS 240</p> <p>3 CHANNEL SOUND TO LIGHT, OUTPUT 3 x 1 KW 240V £ 13.70 inc V.A.T.</p>	<p>UK 823/W</p> <p>CAR BURGLAR ALARM. READY ASSEMBLED £ 11.58 inc V.A.T.</p>	<p>UK 875</p> <p>Capacitive Discharge Electronic Ignition £ 17.50 inc V.A.T.</p>	<p>UK 677/A</p> <p>REGULATED SUPPLY 0-20 V, 2.5 A £ 54.23 inc V.A.T.</p>
<p>UK 666</p> <p>0-30V, 2.5A REGULATED SUPPLY WITH DIGITAL DISPLAY £ 76.82 inc V.A.T.</p>	<p>KS 420</p> <p>DIGITAL D.C. VOLT-METER, 999 MV - 999 V, 0.5 V D.C. £ 14.45 inc V.A.T.</p>	<p>UK 558</p> <p>600 MHz PRESCALER + 5 V D.C. £ 19.95 inc V.A.T.</p>	<p>KS 395</p> <p>30 W Hi-Fi-Audio Amplifier £ 11.58 inc V.A.T.</p>	<p>KS 490</p> <p>NICAD BATTERY CHARGER, 10-20-45-100-150 mA, 15 V D.C. MAX 240V A.C. £ 8.42 inc V.A.T.</p>	<p>UK 114/U</p> <p>20 W IC Amplifier £ 8.42 inc V.A.T.</p>

# hobbyboard

The Complete Printed Circuit Workshop

## NEW FULL HOBBYBOARD CATALOGUE & PRICE LIST

Supplies all your PCB needs including Draughting Aids, Process Materials, Hand Tools, Hardware, Instrument Cases etc. Also introducing a choice of PC Prototyping Systems and the Daylight Fototool System for precision photography (no darkroom) and superb label/panel-making. PLUS 2 pages of Add-ons which give your home computer useful "real world" applications and offer fascinating program/hardware development.

Newly Published Full Catalogue - price **£1.50** (Refundable with 1st order over £10)

Easy Add-ons for ZX Spectrum & ACE

- 17 exciting electronic projects to build and run your own micro.
- LIGHT PEN
- WEATHER STATION
- PICTURE DIGITISER
- + OTHER EXCITING & INTERESTING PROJECTS
- KEY PAD
- MODEL CONTROLLER

A newly released book by well known author Owen Bishop, published by Bernard Babani, describes in detail 17 projects to build (using low cost materials) to bring your micro into the real world.

The most complex component (the DECODER) is supplied in kit form ready to assemble with all components and plated through PCB

Order ref HB 2000 "EASY ADD-ONS" BOOK + DECODER KIT	<b>£24.00</b>
Order ref HB 2001 "EASY ADD-ONS" BOOK ONLY	<b>£3.00</b>
Order ref HB 2002 DECODER KIT ONLY	<b>£22.00</b>
Order ref HB 2003 DECODER PCB ONLY	<b>£8.00</b>

Please state computer when ordering.

Prices inclusive of VAT & carriage

hobbyboard

complete P.C.B. workshop

a division of  
KELAN ENGINEERING Ltd  
Hookstone Park  
Harrogate, N. Yorks

HE/1/84



# BUYLINES

## Quizmaster

As a number of separate units are needed to put together a system, particular attention has been paid to keeping the individual cost as low as possible. We calculate the price of the electronics components to be around £5.00, excluding VAT, p&p. None of them are difficult to source and can be obtained from a mail-order supplier such as Cricklewood Electronics; the cost may vary from the figure mentioned above.

A case is recommended for the project, but any box capable of holding all the parts can be used.

The Veroboard layout in the article has neither been built nor tested and must be regarded as experimental. Hobby Electronics cannot answer enquiries concerning constructions based on this layout.

## Lap Counter

A couple of the components for this project, namely the 0.43" common cathode LED display IC and the 2-pole 9-way switch, may be hard to find.

The latter has to be made up from a Mini Wafa switch kit, with two 12-way wafer mechanisms; don't forget to adjust the end stop for nine positions.

All the components, including displays and switch — but not the PB2720 piezo buzzer, are available from Cricklewood Electronics. Unfortunately they do not appear to stock the PB2720, which in the prototype is mounted on the PCB.

The alternatives are to source the device from elsewhere, or accept another type from Cricklewood, which must then be mounted inside the case and wired to the PCB.

The specified case is available from Maplin, though a suitable alternative can be had from Cricklewood.

## Power Reducer

The SC412D triac specified for the circuit is an isolated-tab type, for safety reasons, which may be difficult to obtain. Any triac rated at 8A or better, such as the C146D (10A) can be substituted, but bear in mind that it does not have an isolated tab (most triacs do not) and therefore the heat sink will be live. "Caution: do not touch with the naked foot", as they used to warn on the back of Japanese TV sets!

All the components, including the C146D, are readily available from Maplin Electronics. Cost, excluding case and PCB, should be under £5.00 with VAT, p&p. A suitable case, to the dimensions given in the Parts List, is also available from Maplin.

Incidentally both Cricklewood and Rapid Electronics have new catalogues out at the moment. They are well worth getting as a reference and source for a variety of components.

## Tomorrow's **WORLD** Self-Build Radio Controlled Car Kits

### NOW AVAILABLE!


Complete Car Kit and Transmitter Kit

Clear build-up instructions included  
only **£9.95 + 50p P&P**

Also

Porsche 935 Turbo Kit (2 speed)

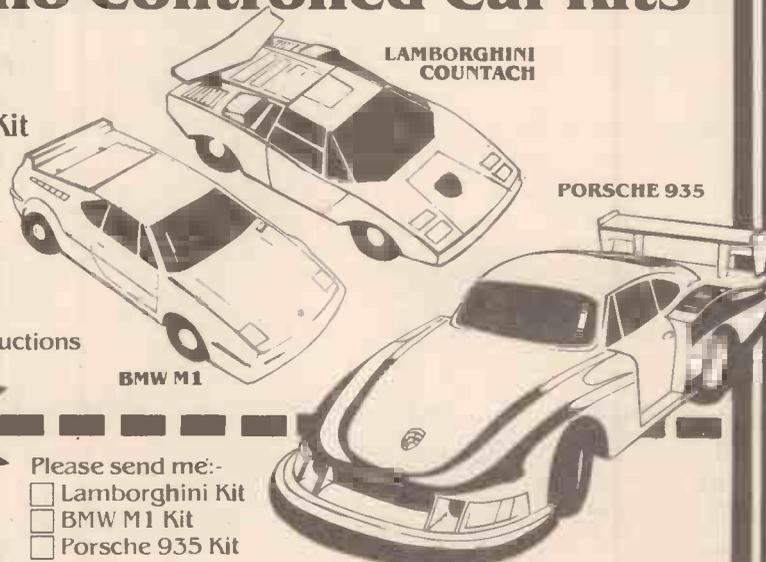Kit includes transmitter and full build-up instructions  
only **£17.00 + 50p P&P**



Order now from:-

Tomorrow's World  
Car Kit Dept.,  
Hadleigh Road Ind. Estate,  
Hadleigh Road,  
Ipswich, Suffolk.

Tel: Ipswich (0473) 59175

Please send me:-

- Lamborghini Kit
- BMW M1 Kit
- Porsche 935 Kit

Name \_\_\_\_\_

Address \_\_\_\_\_

Please allow 14 days delivery in U.K.

# In The FRAME

Hobby Electronics meets the group Mainframe, who take their microcomputers on stage with them.

Helen Armstrong

I WAS INFORMED that Mainframe had recorded their first album in a bedroom.

Was I surprised? Not really. Many a fledgling act puts its demos, or even the finished articles, together in the cosy simplicity of a living room or garret. It took a couple of close encounters with the record itself, listening to its multi-tracked percussion, finely controlled synthesisers and dense sound for it to dawn that 'bedroom' did not necessarily mean amateur.

On the contrary, Mainframe have taken a professional line from the start. The bonus is that they have been able to run an initial career prospect, computing, in tandem with their first love, music, to pursue a project which is unusual in its scope at present, although it must point the direction for things to come.

The players in the band (see the mugshots below) are computer programmer John Molloy, 23, and guitarist-turned- multi-instrumentalist Murray Munro, 20. Murray, who took up music at the age of eight, also writes, sings, produces and engineers their recordings, while John, who can't remember when he started playing (piano, graduating to other keyboards), does arrangements, vocals and percussion, as well as most of the keys, adding a plethora of general ideas, and a big slice of the computer graphics which are the band's special feature.

Just behind the scenes — hardly even behind them — however lurks the rest of the 'band', a team of friends well versed in both the software and hardware side of microcomputing. In a classic case of 'a little help from my friends', the band have created their album and two singles, elaborate computer graphics to complement the music in live performances, an album-length video which they intend to release commercially, plus other shorter videos for stage use, and a percussion synthesiser (alright — drum box) to their own specifications.

All the design and promotion of their album *Tenants Of The Latticework* has been done by — you guessed it — the group, (including a complicated Masquerade-style quest with a £2500 gold "M" as the prize for the first person to unravel the clues), and they have





Mainframe's studio-cum-bedroom in Hemel Hempstead.

logged up a personal first by becoming the first group to release a computer program on a pop record: their first single, *Radio*, had a short program for the Apple II, containing a secret message, and their subsequent single *Talk To Me* has continued the theme, but this time with programs for the Apple, Spectrum, ZX81 and the BBC Micro. And they have material for another album, all laid down (ouch) in that bedroom.

And a bedroom it is — it has a bed in it. And a painting on the wall. Apart from that, the accommodation is dedicated to making music. Recording gear is ranged on one wall, a pile of drums against another. A clump of well-used guitars rests in one corner, and in the other is the wooden frame where the R.S.D. Studiomaster 16:4, a popular small mixing desk nests when it's not being used live.

Where did it begin? John had done some computing at school and technical college. Meeting Murray in a semi-pro band, the pair of them broke away to pursue a different style, and began to incorporate the graphics which they, plus friends, had been working on with their Apple II. The friends — Colin Holgate (who operates the Apples on stage), Dave Green, Jezz West, Martin Poole, Grahame Collins — et al — form a more or less integral part of the

operation.

Working almost entirely on Apple IIs (the band has had as many as four Apples in their stage show at a time) the team devised a visual show that gives their fascination with graphics full rein. The displays became an integral part of the live show, using monitors and, subsequently, a pair of video projectors hired from Rank, with twelve-foot projection screens.

Graphics have also been worked in as part of the video of the album. The record, titled *Tenants Of The Latticework* (it sounds whimsical but is meant literally), tells the story of a business man who is one day told that he is, in fact, a computer program who has been created to explore an artificial landscape by a group of scientists. The hero, Oscar (not your typical rock'n'roll hero), finds a way to emerge from the computer-landscape into the real world. then becomes determined to bring his family out of the computer as well. The story leaves the program-people about to emerge into reality, and the scientists waiting in anticipation.

In the video, the six coloured discs which hold the key to Oscar's ability to move in an out of the program are seen tumbling through a space of advancing stars; the chequered pattern of the latticework floats and expands towards the screen as Oscar 'falls' down into it,

and resolves itself into the form of the piano from his very-average suburban living room; a skeletal globe rotates; geometric forms alter and repeat themselves in kaleidoscopic rhythms, and the band's logo drifts in swarms across the screen. During another song, yet to be recorded, the figures of a deep-sea diver resolves itself line by line into the word 'Diver' in coloured letters.

In the meanwhile, another friend, Andrew Earle, shoots the band and audience through a video camera and onto the screens, juxtaposing live images with the prerecorded sequences, or with projected slides. The stage lighting, a combination of manual and preset control, and sound-to-light, is overseen by Jezz West.

The effect is less that of a band with visuals than of a giant video show incorporating the group.

As they played their first gig in a full-sized hall, the teenage audience, sitting on the floor, watching intently puzzled some members of the team, used to playing discos and clubs and other venues with a shifting population. It wouldn't surprise anyone who (literally) sat through the "getting into it" era in the Sixties, when music was treated with a similar reverence. Not hard to see why: swirling synthesiser riffs, soft-toned harmonic vocals and rich, Pink Floyd-esque lead guitar, along with high-

## Program Preparation

Colin Holgate

AS WE SAID, all the graphics for the video of *Tenants Of The Latticework* were created on the Apple II. Because no animation facilities were available, each sequence had to be displayed in real time and shot with a video camera straight from the monitor screen.

It's easy to overlook the amount of preparation that goes into a particular effect when watching it. The opening scene of the 'Tenants' video shows an aerial view of a blue grid, passing 'beneath' the viewer. The 'viewer's eye' then tilts upwards until the grid has dropped from view at the bottom of the screen. After this, a 3D coloured MAINFRAME logo flies past from right to left, and is then replaced by the stationary *Tenants Of The Latticework* title.

Taking this as an example, we can see the sort of preparation that is required. First of all, a three dimensional image of the logo had to be created. Numbers representing the 500 coordinates and 750 lines that make up the logo had to be entered into a special 3D program called *Apple World*. Having done this, the logo could be viewed from any angle. Fifteen views of the word, as it passed the viewpoint, were saved onto disc.

Each of these wire frames were then treated with a colouring program called *Micro Painter*. At this point any lines that should not be visible had to be changed to the desired background colour.

After this stage, the fifteen frames needed for the flypast were ready, but there was still a major problem. To understand this problem we need to look at some facts and figures on the Apple II. The 64K memory map is not all available as RAM on the Apple, or any other micro. Locations \$9600 to \$FFFF (in Hex) are used for the Apple's disk operating system and Applesoft BASIC.

Locations \$0000 to \$0800 are used for the text page, keyboard buffer, 6502 stack and by BASIC and DOs, all except for about 200 bytes.

In order to replay the prepared frames fast enough to form an animation, all the frames need to be in memory at once. So 28K has been used up; there is more to go.

An Apple hi-res picture occupies 8K of RAM. In order to show the flypast sequence, both of the Apple's hi-res picture

buffers were needed. The next frame to be seen is placed onto the buffer not in view, and then switched over to store the 15 x 8K pictures plus the control program.

Using this method with pictures can be very efficient. The fifteen flypast screens, plus two blank screens, were stored well within the available 20K.

The finished effect is achieved by 'expanding' each frame into the relevant picture buffer.

Whereas Mainframe uses commercial programs to help generate the logo graphics, of all the 'in betweening' programs were written by people associated with the band. One program is used to generate the start and end frames for the change sequence. Another program then uses these to calculate the in-between frames and saves the resultant pictures, in compressed format, onto disk ready for replaying.

The new position for any point of line end is calculated by subtracting the start frame coordinates from the end frame coordinates, dividing the answer by the numbers of frames required and adding this figure to the coordinates of the previous frame. If that is not very clear, the formula for a new x coordinate would be

$$\frac{(LFx - FFx)}{NoF} + PFx$$

where LFx = Last Frame x coordinate, FFx = First Frame x coordinate, NoF = Number of Frames and PFx = Previous Frame x co-ordinate.

Each frame takes on to two seconds to draw, but by using the frame replay, as with the logo, eight frames per second can be achieved.

These difficulties were overcome by 'compressing' the pictures. It is possible to cheat a little by checking through the picture memory looking for repeated values, and storing them in 'shorthand'. The group of letters ppppppaaacd can be expressed as r6pr4acd, where 'r' is a marker to signify a repeat sequence, followed by the number of times that 'p' is repeated. Likewise 'a' is repeated four times, and 'c' and 'd' are without a marker byte and are taken as separate bytes/characters. Should a genuine 'r' be needed, it would have to be stored as r1r.

tech associations are a reminder of that music, but the horror of associating with either pop or heavy metal music which split the field in those days seems — thankfully — to have vanished, and long may it remain so.

But having spared a minute to look at the music, back to the computers. Initially, the group worked entirely on Apple IIs, as this was what they had easiest access to. To write the graphics for the *Tenants* video, they used the Accelerator Card, to increase the speed of all the sequences while keeping the amount of memory to a minimum. The card consists of a 3.58MHz 6502B processor, and 64K of fast access RAM. The programs were run in real time.

The team used software by Appleworld, Micropainter, Bit Stik, Bill Budge's 3D Graphics, EBS and a special American graphics language suited for audio/visual effect, Ceemac, using the *Fire Organ* program, in addition to original software and adaptations written among themselves. They planned to take the video signal directly from the computers to the video tape, but had great difficulty in synchronising the computer's video signal to the video recorder.

While recording the BBC's *Show Me Show*, they had hoped that some super-technician would come to their rescue; however the best solution was to run the signal through a Quantel video effects controller.

The Quantel uses a frame store, capturing a television picture pixel by pixel, digitally — and therefore has synchronizing facilities beyond the pockets of all but full-sized pro video studios.

But alas, the machine had a mind of its own. Finding a single frame of signal which suited its circuits better than any other frame, it 'grabbed' it and refused to accept any other. The operators were stuck. They had one frame in store, but one frame is not much use to a whole visual show. Regretfully, they switched off the recalcitrant controller and resorted to the time-honoured method of taking the image off the monitors via a television camera. This was the technique they used when eventually putting down the complete video for the album.

When making their video, the band had the help of Andrew Earle, another friend, who just happened to be the proprietor of a small pro video company, Gothic Audio Visual. This gave them access to high-band, broadcast-quality video equipment. They tempted him with the prospect of making a video which would be seen at the band's gigs, and potentially on cable television here and in the USA (where the album is released early next year). He spent a number of weekends shooting while the group scripted, acted and produced Oscar's story. Now they are planning to refine the editing of the video and offer it for commercial sale.

The video's backing track, to synchronise it with the video, was DBX encoded, and then run on the soundtrack of the pro-standard U-matic video recorder on which the video had

been recorded.

But the group's 100% first is the release of a computer program on a record. Their first single, *Radio*, had a thirty-second program called The Message on the end of it. If a hi-fi amplifier is connected into an Apple, the program can be played off the record onto the computer — but the contents of the message is kept secret for those who actually run it. The band's second single *Talk To Me* has four programs on the back, one each for the Apple II, Spectrum, ZX81 and BBC Micros. These continue the content of the first 'message'.

Incidentally, on the sleeve of this single, the group recommend that the program is recorded onto cassette tape before loading to save wear on the record grooves — this must be the first record release which actually asks a buyer to copy it, instead of expressly prohibiting such activity! An added benefit of putting computer games and graphics on one side of singles, should it become a common option in the future, is removing the excuse from bands whose attitude is "can't be bothered to put something decent on the B side — let's do a remixed/lyricless/back to front version of the A side and save the studio costs."

Mainframe don't have to worry too much about studio costs as yet; having recorded their album themselves, costs up to pressing stage were £900 plus a few weeks work (after months of planning). They could have spent that in two or three days in a commercial studio.

They have also saved money, and anguish, by paying attention to the technical aspects of recording; for instance, Murray, who engineers the recordings, spends a lot of time getting the recording levels right, and includes a carefully set 1kHz tone prior to each track to give the engineers in the mastering studios a levels reference to work to. Making sure that the equalisation on the recording corresponds to that needed to cut a master disc (as far as possible) is also important and saves later processing (quite apart from getting a better result).

A fundamental problem faced in recording a group is the interference to the sound causes when the signals from one instrument, particularly the bass guitar with its low-frequency sound (which can set up standing waves in the room, instead of dissipating) get onto the recording via another instrument's microphone in a different phase from that which the 'real' recording takes. Use of directional microphones, and careful placing of microphones at the right distances apart avoid this problem. This effect can ruin a recording, and it is expensive and difficult to correct.

Mainframe also point out that, using a four-track tape recorder as they do, the extra expense of a DBX or other noise-reduction unit is worth every penny, as quite apart from improved sound to start with, it doubles (or more) the number of cross-recordings possible from track to track or recorder to recorder, and advantage for any recording group, and



A detail from the cover of Mainframe's album, painted by Murray Monro. The fine details are all clues to the band's "quest".

essential when there are only two people to play half a dozen instruments.

Another personal triumph for Mainframe is their percussion — it's all controlled by the Apple. One of the team, Dave Green, developed the hardware and software for a drum machine which can handle both machine-generated and live-recorded drum sounds (and any other sound which meets the beat). The result is an on-stage drum sound which has much of the sound of live drumming, but with the mechanical drive of a drum machine. Murray augments the sound with Rotosound drums on stage. The sound can also be altered by the drum-box — they are working at connecting up John's Liberation keyboard synthesiser through the device, but early attempts led to Dave blowing up his Apple — so research is still in progress.

Working in the band has led every member and associate member to extend his technical expertise. I asked John whether they hadn't had to spend a great deal on equipment: between them they play Moog Prodigy and Liberation synthesisers (the Liberation is one of those keyboards worn round the neck like a guitar — possibly the world's ugliest musical instrument), Juno 60, Yamaha SK20 organs and Fender Stratocaster guitar, together with their amplification and sundry other guitars/bass/drums bought or borrowed, plus their computers. But the band don't see it as a big investment — the equipment has been built up gradually, much of it before the present band came into existence just over a year ago. (For instance, they make good use of echo and reverb without having access to expensive digital effects unit. One source being an ETI Chorus Unit, built as an 'A' level project at school. That should give hope to those doing

Hobby projects as part of their exams...

The computer bug has proved infectious. When the band began, most of their musical associates had no interest in computing. "Now" says John "Every single person involved with the band has a computer and uses it. They just got interested." Others nod and bear witness to the tenacious grasp of the microcomputer once the owner has investigated it beyond the games-playing stage.

Not deterred by their earlier encounter with the Quantel machine, Mainframe are determined to make their next video with the help of just such a machine, and in the long term they would like to develop their own graphics effects generator. There is no doubt that they will do it, one way or another. The wealth of software and hardware engineering skill within the group puts them in control of their machinery and material, and not only their music.


Having pursued a musical career on the strength of some savings, some freelance computing work, and record sales the most satisfying thing about Mainframe's career so far is that they have succeeded in taking one hobby (computing) and making a career out of it, and then using that to turn another hobby, music into a career as well. Perhaps not everybody has the opportunity, but then again, why not? Family and friends have supported them, but the level of imagination and professionalism they have built up in a short time is not so much a product of their technical or even their musical skills, but their determination to do it rather than just think about it. Their motto could be "Have bedroom, will travel."

MC2 Records can be contacted at 24 Missden Drive, Hemel Hempstead, Herts.


# Hobby Electronics 1982 INDEX



*HEBOT II: November*

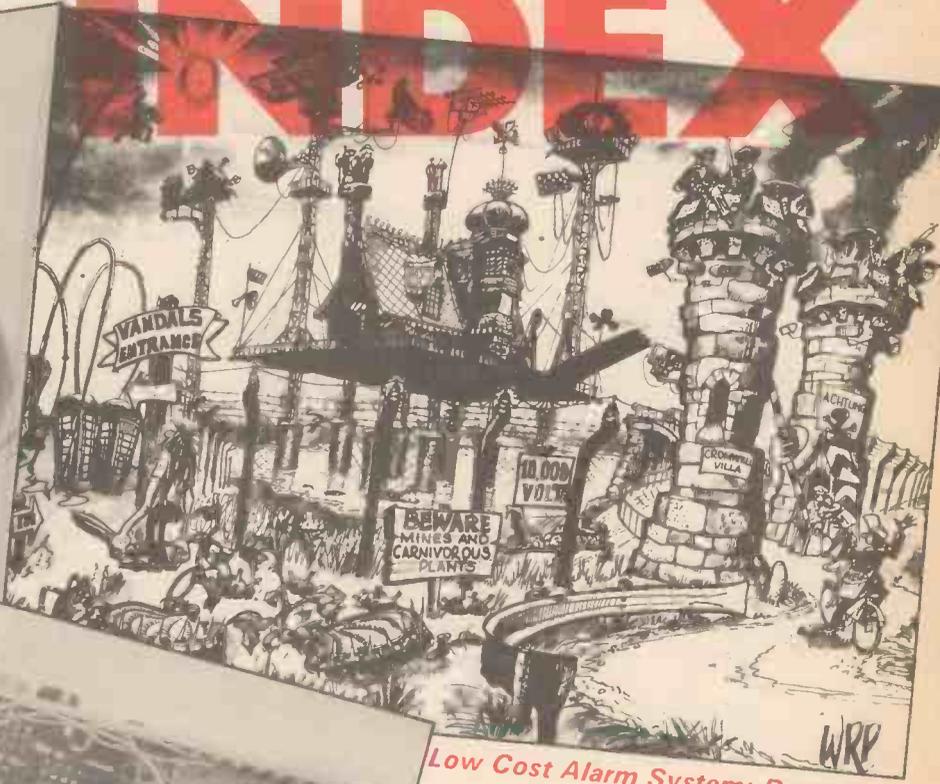

*Low Cost Alarm System: December*

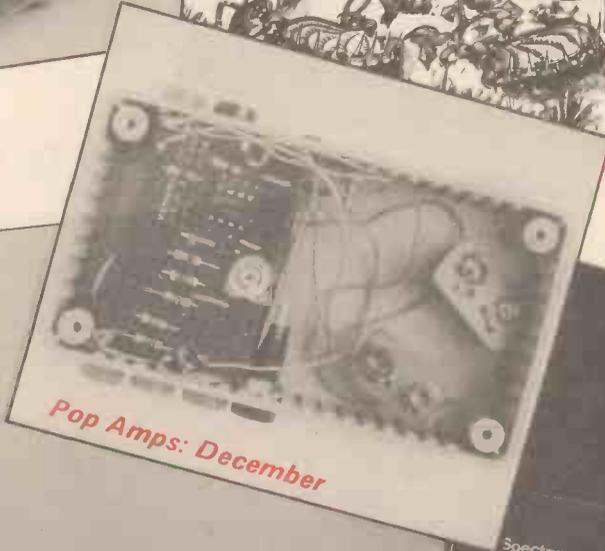

*Pop Amps: December*




*Digital Voltmeter: August*



*ZX Interface Board: September*

## PROJECTS

AF Signal Generator	May 82	49
Audio Analyser	Aug 82	53
Audio Analyser	Sep 82	57
Automatic Greenhouse Sprinkler	Jun 82	48
Auto Wah	Jun 82	25
Big Ear	Dec 82	80
Bike Alarm	Apr 82	72
Bike Siren	Mar 82	28
Breadboard/Audio Phaser	Nov 82	68
Breadboard Tone Controls	Sep 82	34
Cable Tracker	May 82	65
CB Squelch Unit	Oct 82	58
Computer PSU	Jul 82	57
Designing Power Supplies	Jun 82	12
Diana VCO	Nov 82	22
Digital Capacitance Meter	Apr 82	25
Digital Dice	Mar 82	11
Digital Thermometer	May 82	10
Digital Voltmeter	Aug 82	20
Dual Engine Driver	Apr 82	11
Echo-Reverb	May 82	33
Flashpoint Alarm	Oct 82	9
HEBOT II	Nov 82	9
Intelligent Nicad Charger	Jan 82	26
Intruder Confuser	Jan 82	38
"Junior" Slot Car Controller	Sep 82	9
Lofty (Loft Light Alarm)	Dec 82	74
Low Cost Alarm	Dec 82	70
Masthead Amplifier	Feb 82	42
Microlog	Dec 82	9
Microtrainer Part 1	Jun 82	60
Microtrainer Part 3	Jul 82	52
Microtrainer Part 2	Jul 82	52
Microtrainer Part 3	Aug 82	57
Microtraining	Sep 82	25
Negative Voltage Generator	Oct 82	24
Noiseless Fuzzbox	Feb 82	26
Phase Four	Dec 82	37
Pedometer/Odometer	Nov 82	46
Slide-Tape-Synchroniser	Dec 82	56
Solar Radio	Jul 82	20
Stereo Bass Boosters	Mar 82	52
Stereo Noise Gate	Dec 82	20
Switch-Tuned Radio	Jan 82	16
SWR Meter	Aug 82	48
Tanover	July 82	14
Telephone Timer Part 1	Jun 82	9
Telephone Timer Part 2	Jun 82	9
Three Breadboards For Experimenters	Jun 82	31
TV Amp	Dec 82	25
TVI Filter	Jul 82	34
Universal Relay Driver	Feb 82	18
Volume Expander	Jan 82	54
ZX Interface Board	Sep 82	14

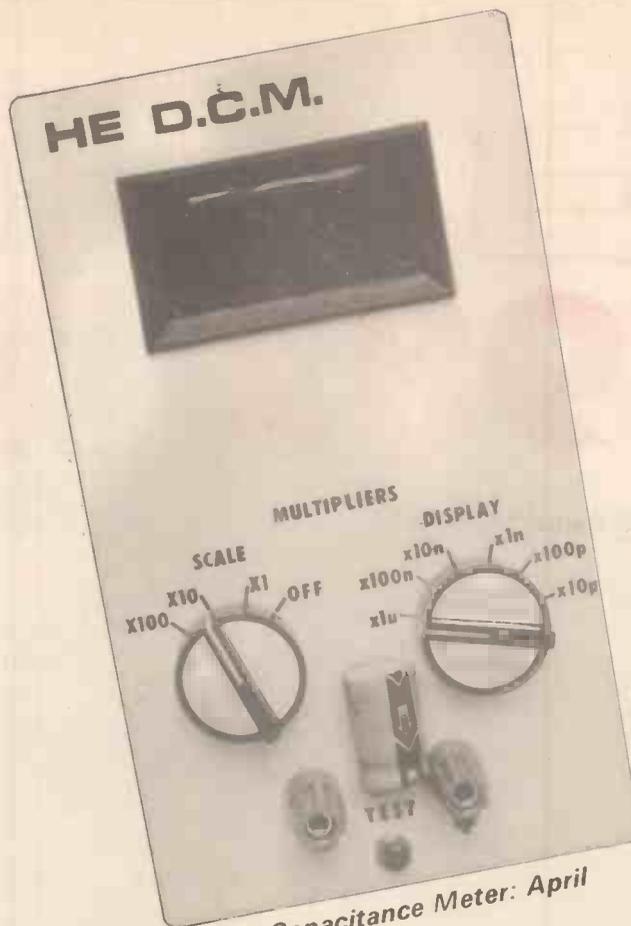

Digital Capacitance Meter: April


## RADIO RULES

Capacitance And Inductance In AC And DC Circuits	Jul 82	29
Capacitance, Resistance And Inductance	Aug 82	43
Classes Of Radio Power	Sep 82	20
Frequency Modulation	Nov 82	63
Radio Stages	Oct 82	68
Oscillator Circuits	May 82	57
Single Sideband	Dec 82	43
Waves And Signals	Apr 82	55
Wave Theory	Jun 82	19


Tape/Slide Synchroniser: December



# Hobby Electronics 1983 INDEX

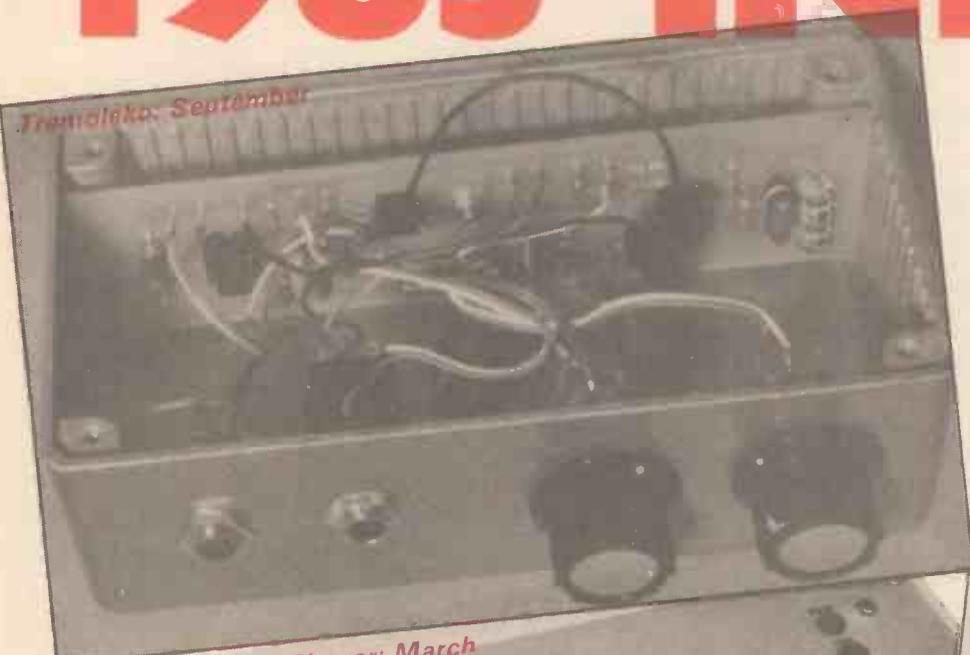


Tremolo: September

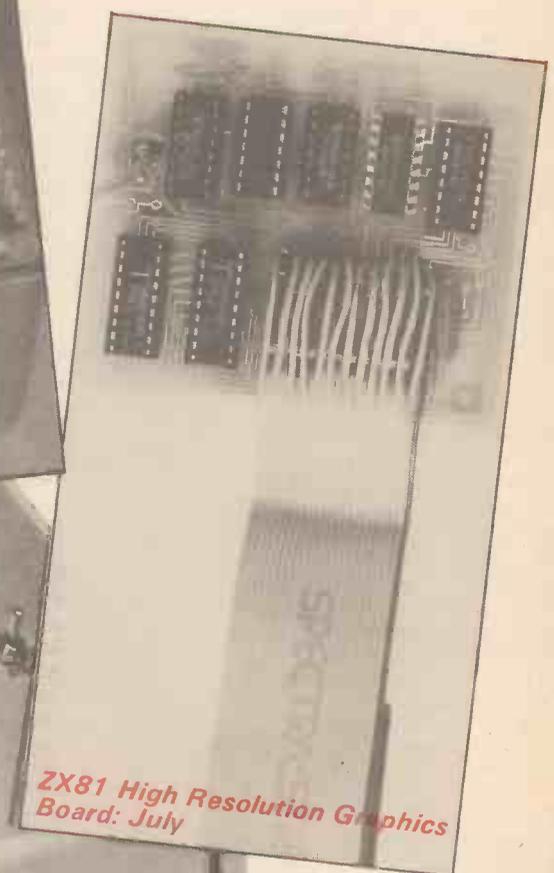

ZX81 High Resolution Graphics Board: July

6502 EPROM Blower: March

HE 6502  
EPROMMER

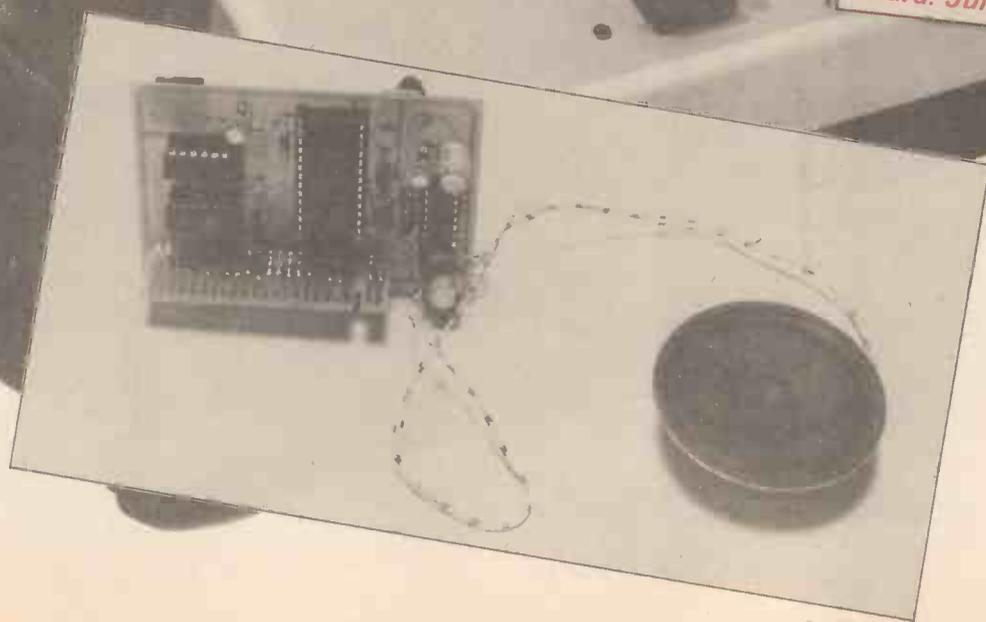

## PROJECTS

Aerial Without Wings	May 83	27
Audio Level Meter	Oct 83	11
Auto Power Down	Apr 83	20
Auto Tester	May 83	28
Auto Winder	Aug 83	56
Battery Warning Device	Jun 83	30
Bassman	Dec 83	29
BBC Micro/HEBOT Interface	May 83	62
Cable And Satellite Television	Sep 83	25
Car Interior Delay Light	Nov 83	26
CB Push To Talk Switch	Jun 83	45
CB Selective Caller	Jan 83	63
Continuity Tester	Dec 83	56
Digitester Part 1	Jan 83	23
Digitester PSU	Feb 83	56
Dual Purpose Power Supply	Nov 83	54
6502-Based EPROM Programmer Part 1	Mar 83	20
EPROM Programmer Part 2	Apr 83	28
Giant Circuit Supplement	Oct 83	34
Gripometer	Sep 83	59
Hi-Voltage Meter	Oct 83	28
Hobby 'Scope Part 1	Jun 83	11
Incremental Timer	Feb 83	12
Light Meter	Dec 83	12
Moisture Gauge	Dec 83	49
Overvoltage Cutout	Mar 83	68
Para-Q	Nov 83	13
Power Supply Unit	Sep 83	54
Programmable Joystick Controller	Aug 83	11
Reader's Project: Enlarger Timer	Aug 83	60
Reader's Project: Simple Stereo Preamp	Nov 83	47
Reader's Project: Simple Tremolo	Jul 83	41
Short Circuits	Nov 83	60
Signal Powered Loudspeaker Protector	Mar 83	50
Soft Fuzz	Jul 83	12
Sound Pressure Level Meter	Sep 83	14
Stall Thief	May 83	20
Stereo Image Expander	Jul 83	52
Stereo Voice-Over Unit	Apr 83	60
Switched Mode Power Supply	Jan 83	15
Traffic Light Toy	Jun 83	65
Tremoleko	Sep 83	36
Trump Card	Oct 83	58
Ultrasonic Intruder Alarm	Oct 83	63
Whistle Switch	Aug 83	36
Windscreen Wiper Delay	Nov 83	36
ZX81 High Resolution Graphics Board	Jul 83	17
ZX Sound Board	Jun 83	20

## POP AMPS

High Impedance AC Millivoltmeter	Jul 83	60
Linear Ohmmeter	Mar 83	30
Long Range Ohmmeter	Mar 83	46
Peak Voltage Detector	Feb 83	52
Single IC Millivoltmeter	Jan 83	30
TTL Logic Tester	Jun 83	36
Very High Impedance Voltmeter	Feb 83	31

## FEATURES

Aces High	May 83	47
Book Reviews	Jan 83	68
Book Reviews	Jun 83	62
Cable And Satellite Television	Sep 83	25
Components And Hardware Directory (Update)	Apr 83	41
Cumulative Index 1978-1982	Jan 83	35
Directory Of Electronic Kits And Modules	Feb 83	37
DIY HI-FI/Speaker Review	May 83	52
Expanding The ACE	Aug 83	42
Finishing Touches	Mar 83	12
FX-Computer Review	Oct 83	16
I Almost Met	Dec 83	42
Junction FETs	Dec 83	44
Light And Power From DC Supplies	Jan 83	10
Look In The Book	Feb 83	59
The Oric 1 Review	Jul 83	36
Radio Controlled Gerbil	APR 83	12
Tools And Test Equipment Survey	Apr 83	36
Tools For The Trade	Apr 83	24
Voyager Car Computer	Mar 83	62
A Zener Diode Primer	Dec 83	20

## COMPONENTS FOR COMPUTING

Randomly Accessing Memory	Feb 83	69
ROMs And EPROMs	Mar 82	16
Interrupts	Apr 82	50
Looking At Displays	Jun 83	38

*The Electronics Revolution: January to May*

*Tools and Test Equipment: April*



## CAREERS IN ELECTRONICS

Basic Qualifications	May 83	12
Technical Writing	Jun 83	52
British Telecom	July 83	48
Radio and TV Transmission	Aug 83	47
In The TV and Radio Studio	Sep 83	40
Customer Service Engineering	Oct 83	16
Working With Microcomputers	Nov 83	48

## FAMOUS NAMES

Charles Wheatstone	Jan 83	20
Herman Hollerith	Mar 83	65
Charles Proteus Steinmetz	May 83	24
Sir John Turton Randall	Jun 83	26
David Sarnoff	Jul 83	55
Alexander Graham Bell	Aug 83	52

## ALL ABOUT ELECTRONICS

Part 1: Basics	Jul 83	28
Electromagnetics And Ohm's Law	Aug 83	20
Resistance And Capacitance	Sept 83	48
Semiconductors	Oct 83	48
Digital Circuits	Nov 83	28
Transistor Circuits	Dec 83	36

## 1983 ERRATA

Auto-Tester (May 83)	Nov 83	41
Battery Warning Device (Jun 83)	Oct 83	26
Tremoleko (Sep 83)	Oct 83	26
ZX81 Hires Graphics Board (Jul 83)	Dec 83	27

## RADIO RULES

Introducing AM Receivers	Jan 83	47
Propagation And Aerials	Mar 83	55
Interference And RF Measurements	Apr 83	66
The RAE	May 83	41

## THE ELECTRONIC REVOLUTION

Wireless At War	Jan 83	52
The Birth Of Broadcasting	Feb 83	22
Pictures From Afar	Mar 83	40
Power In The House	Jun 83	56
The Electronic Age	May 83	57



*Careers in Electronics: May to November*

*ZX81/Spectrum Intelligent Joystick Controller: August*




# HENRY'S AUDIO ELECTRONICS

COMPUTERS • COMMUNICATIONS • TEST EQUIPMENT • COMPONENTS

VISIT OR PHONE • OPEN 6 DAYS A WEEK • ALL PRICES INC VAT

## THERMAL MATRIX & LINE PRINTER

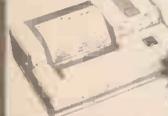

NEARLY 1/2 PRICE

COMPLETE WITH FULL HANDBOOK, 3 ROLLS PAPER  
**£99.95** inc. VAT  
£86.91 - VAT (UK post etc £1.05) (List approx £187)  
150 to 180 LPM • Full 96 CH ASC II • 40 CPL • 280 Dots P/L  
Auto-underline • 50 Graphic Symbols • Back Space • Sell  
Test • VU/HDR TABS • 7 x 10 Matrix • 4.4" Wide Paper  
Bidirectional • 220/240 V AC • Size Approx 9.8 x 2.8 x 7.2"  
SUITABLE FOR: TANDY • 88C • DRIC • NASCOM • GEMINI •  
ACORN • NEW BRAIN • DRAGON • etc. etc.  
(Your enquiries invited).  
(Interface unit with leads £15 - state model)

**PRESTEL ADAPTOR** 3 card set with data etc (P/S +/-, 12V and +5V) **£69.95** inc. VAT

**CHERRY ADD-ON KEYPAD** 16 button pad non-encoded **£5.95**

**MODEM CARD** BT approved ready assembled unit with data and accessories. **£39.95** inc. VAT

**SANYO DM2112 HIGH RESOLUTION MONITOR** 12" green display. Composite video. 1280 characters. Over 15 MHz B/W. 240V AC 34 w. 16 x 11 1/2" x 12 1/2". Alphabetic and Graphic display. Usually **£89.95 - £99.95** incl VAT **£69.95** (UK C/P & ins £2.05)



SAVE £20 TO £30

## I.T.T. 2020 CABINET

Complete PROFES SIGNAL Case beautifully constructed with cut out for one 'CHERRY' keyboard, plus ample room to house a COMPLETE SYSTEM and power supply. Complete with fittings. (Case top detachable). Unit is silver grey in colour. Robust construction. Sloping front with side ventilation ideal for NASCOM, ACORN, TANGENTE or your own system. Size 18" x 15 1/2" x 4 1/2" (front slopes). **£27.50** inc. VAT (UK C/P £2.50)



## LOGIC PROBES

LP10 10 MHz **£26.95**  
DLP50 50 MHz with carry case and accessories **£49.95**



## HIGH VOLTAGE METER

Direct reading 0/40 KV. 20K/Volt. **£23.00** (UK C/P 65p)



## DIGITAL CAPACITANCE METER

(UK C/P 65p)  
0.1 pF to 2000 mfd LCD 8 ranges  
DM6013 **£52.75**



## TRANSISTOR TESTER

Direct reading PNP, NPN, etc. TC1 **£21.95** (UK C/P 65p)




## VARIABLE POWER SUPPLIES

(UK C/P £1.00)  
PP241 0/12/24V, D/1A **£35.00**  
PP243 3 amp version **£59.95**  
PS13075 8/15V 7 amp twin meter **£24.95**


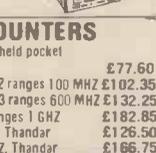
## FREQUENCY COUNTERS

PFM200A 200 MHz hand held pocket 8 digit LED **£77.60**  
MET1008 digit LED bench 2 ranges 100 MHz **£102.35**  
MET6008 digit LED bench 3 ranges 600 MHz **£132.25**  
MET1000 8 digit LED 3 ranges 1 GHz **£182.85**  
TF040 8 digit LCD 40 MHz Thandar **£126.50**  
TF200 3 digit LCD 200 MHz Thandar **£166.75**



## DIGITAL MULTIMETERS



with case (rotary switches)  
+ Side button - case **£2.95**  
KD25C 13 range 6.2A DC, 2 meg ohm **£23.50**  
KD305 16 range 10A DC, 2 meg ohm **£26.95**  
KD30C 26 range 1A AC/DC 20 meg ohm **£29.50**  
KD55C 28 range 10A AC/DC 20 meg ohm **£33.50**

Metex 3000 30 range 10A AC/DC, 20 meg ohm **£33.24**  
6010 28 range 10A AC/DC 20 meg ohm **£34.40**  
7030 4- AS610 high acc. 0.1% basic **£41.30**  
KD615 16 range 10A DC 2 meg plus Hfe tester **£39.95**  
SIFAM 22008 21 range 2A AC/DC 20 meg **£29.95**  
Bench Models  
TM355 29 range LED 10A AC/DC 20 meg, Thandar **£86.25**  
TM356 26 range LCD 10A AC/DC 20 meg, Thandar (Replaces TM353) **£97.75**  
TM351 29 range LCD 10A AC/DC 20 meg, Thandar **£120.75**  
SIFAM 250024 range LCD 2A AC/DC 20 meg **£79.95**  
ALSO IN STOCK Thurlby, Metrix and Beckman. Professional series Incl. True Rms. etc.

## MULTIMETERS (UK C/P 65p)

C7081 50 K/Volt range doubler, 10A DC, Total 36 ranges. Special Offer **£12.50**  
HM102BZ 20K/V 10A DC 22 range & cont. buzzer **£13.50**  
TMK500 23 ranges 30K/V, 12A DC plus cont. buzzer **£23.95**  
MH56R 20K/V, 22 range pocket **£10.95**  
830A 26 range 30K/V, 10A AC/DC overload protection, etc. **£23.95**  
360TR 23 range 100K/V, Large scale 10A AC/DC plus Hfe **£39.95**  
AT2100 31 range 100K/V deluxe, 12A AC/DC **£33.50**  
AT1020 18 range 20K/V, Deluxe plus Hfe tester **£18.95**  
YN360TR 19 range 20K/V plus Hfe tester **£15.95**



## SIGNAL GENERATORS (220/240V AC)

FUNCTION: All sine/square/triangle/TTL etc.  
TG101 0.02HZ-200KHZ **£113.85**  
TG102 0.2HZ-2 MHz **£166.75**  
PULSE  
TG105 Various facilities 5 HZ-5 MHz, **£97.75**  
AUDIO: Multiband Sine/Square  
LAG27 10 HZ to 1 MHz **£90.85**  
AG202A 20 HZ to 200 KHZ (list £94.50) **£83.50**  
LAG 120A 10 HZ-1MHz Low Distortion **£158.85**  
RF  
SG402 100 KHZ to 30 MHz (list £79.50) **£69.50**  
LSG17 100 KHZ to 150 MHz **£79.35**

## OSCILLOSCOPES

Full specification any model on request. SAE by post.  
'HM' Series HAMEG: 'SC'  
'THANDAR: 'CS' TRIO:  
'3' CROTECH: 'HITACHI'  
SINGLE TRACE UK C/P £3.00  
3030 15 MHz 5mV, 95mm tube plus component tester **£177.10**  
SC110A Miniature 10 MHz battery portable Post free **£171.00**  
Optional carry case £6.84 AC adaptor £6.69 Nicads £12.50  
HM103 15 MHz 2mV, 6 x 7 display plus component tester C/P £3.00 **£181.70**  
DUAL TRACE (UK C/P £4.00)  
HM203/4 Dual 20 MHz plus component tester **£303.60**  
CS1562A Dual 10 MHz (list £321.00) **£269.50**  
3131 Dual 15 MHz + component tester **£278.00**  
CS1566A Dual 20 MHz All facilities (list £401.35) **£349.50**  
HM204 Dual 20 MHz plus component tester sweep delay **£419.75**  
HM705 Dual 70 MHz sweep delay **£676.00**  
V212 Dual 20 MHz **£399.25**  
V222 Dual 20 MHz plus extra facilities **£391.00**  
V422 Dual 40 MHz portable **£586.50**  
V203F Dual Trace 20 MHz sweep delay **£408.25**  
V134 Dual Trace 10 MHz storage **£1092.50**  
All HITACHI, CROTECH & TRIO • With probes  
MODELS AVAILABLE



OPTIONAL PROBE KITS  
X1 £7.95 X10 £9.45 X1 - X10 £10.50

Huge stocks of semiconductors, components, tools, etc. Large range of CB equipment and telephones in stock.

CALL IN AND SEE FOR YOURSELF. ORDER BY POST OR PHONE.

ORDER BY POST OR PHONE.

Order by Post with CHEQUES/ACCESS: VISA or you can telephone your orders. All orders despatched within 5 days unless advised.

## FOR HI-FI & ELECTRONICS ENTHUSIASTS CONCEPT ELECTRONICS LTD

51 Tollington Road, London N7 6PB

Mail order only

We are the specialist of electronic kits and rack mounting cabinets. A catalogue with complete range of products including pre-amp modules, power amp modules, pre and power amplifier modules, complete kits of amplifiers, equalizers, reverberation amplifiers (with cases), alarm clocks, appliance timers, CB amplifiers, test equipment, control modules, music generator, battery fluorescent light and high quality rack mounting cabinets etc. with illustrative pictures now available at the cost of 35p + 25p p&p.

### Professional rack mounting cabinet



Panel Size	Rear Box		Price
	WH (inch)	WHD	
19 x 5	17 x 4.5 x 10	27.54	23.54
19 x 4	17 x 3.5 x 10	25.24	21.24
19 x 3.5	17 x 3 x 10	24.09	20.09
19 x 3	17 x 2.5 x 10	24.09	—
19 x 2.5	17 x 2 x 10	22.94	18.94
19 x 6	17 x 5.5 x 12	28.69	24.69
19 x 5	17 x 4.5 x 12	27.54	23.54
19 x 4	17 x 3.5 x 12	25.24	21.24
19 x 3.5	17 x 3 x 12	24.09	20.09
17 x 3.5	15.5 x 3 x 9	21.79	17.79
17 x 2.5	15.5 x 2 x 9	20.64	16.64
17 x 4	15.5 x 3.5 x 12	25.24	21.24
17 x 3	15.5 x 2.5 x 12	24.09	20.09

Please add £2.50 p/p per item

★ Wholly made of black anodised aluminium sheets ★ Suitable for high quality amplifiers and many other purposes ★ Top, side and rear cover removable for access ★ Separate front mounting plate ★ Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles ★ With ventilation slits and plastic feet.

The low cost steel version is also available. The size and features as well as the front panel is the same as the aluminium cabinets except the rear box is manufactured from steel painted in black.

### CONTROL MODULES



TY-7 Electronic touch switch **£2.90 Kit £4.50 Ass.**  
TY-11 Light activated switch **£2.20 Kit £3.50 Ass.**  
TY-18 Sound activated switch (Clap switch) **£4.50 Kit £5.95 Ass.**  
TY-38 Sound activated switch (voice-switch) **£5.50 Kit £7.50 Ass.**  
TY-41 Infra-red remote control (Receiver and transmitter) **£17.20 Kit £21.95 Ass.**

### HI-FI AMPLIFIER MODULES



TA-323A 30W + 30W stereo amplifier **£18.95 Kit £23.95 Ass.**  
TA-820 60W + 60W stereo amplifier **£27.50 Kit £33.50 Ass.**  
TA-920 70W + 70W stereo amplifier **£35.50 Kit £42.50 Ass.**

## FEEL HEALTHIER WITH ZEPHION

Bring fresh clean air into your home with the Zephion Air Ioniser.



Air free from smoke, dust and other pollutants of modern day living can bring to many the relief of breathing comfortably once again.

We are confident that you will be delighted with the Zephion Air Ioniser, but if you are not entirely satisfied a full money back guarantee is available if items are returned in good condition within 28 days.

### BUILD IT YOURSELF!

TO:- Dataplus Developments 81, Cholmeley road Reading, Berks. RG1 3LY TEL:- 0734 67027

PLEASE SEND:-

- ZEPHION KITS • £24.15p (Kits include all parts)
- ZEPHION AIR TONERS BUILT AND TESTED. • £34.50p

clip the coupon

NAME:-

ADDRESS:-

Money immediately refunded if items returned in good condition.

Prices include VAT & postage; allow 14 days for delivery. DATAPLUS:HE

## HENRY'S

404-406 Edgware Road, London, W2 1ED  
Computer: 01-402 6822. Components: 01-723 1008  
Test Equipment & Communications: 01-724 0323

## AUDIO ELECTRONICS

301 Edgware Road, London, W2 1BN  
01-724 3564 (All mail to this address)

Cubegate Limited

ORDER BY POST OR PHONE.

Order by Post with CHEQUES/ACCESS: VISA or you can telephone your orders. All orders despatched within 5 days unless advised.


## FEATURES

The Affordable Computer	Apr 82	45
Beginner's Guide To Construction	Aug 82	28
Breadboard VCO	Oct 82	75
Car Electronics	Jan 82	60
CM100 Circuit Maker Review	Oct 82	63
Components For Computing:		
1/O Ports	Dec 82	46
Computer Talk	Apr 82	41
Creative Recording	Apr 82	76
Digital Counters And Timers	Jun 82	71
Directory Of Electronic		
Components And Hardware		
Suppliers	Oct 82	33
DM 2350 Meter Review	Sep 82	47
The Electronics Revolution:		
Beginnings	May 82	39
Equalisation In Audio	Jul 82	60
Fault-Finding Made Easy	Oct 82	15
Feedback	Mar 82	36
A Good Joint (Soldering Techniques)	Feb 82	53
HC6010 DMM Review	Dec 82	65
Housekeeping For Electronics	Nov 82	26
Inside Colour TV	Apr 82	16
Makin' Tracks (PCB Making)	Feb 82	11
Memotech 64K RAM Pack Review	Jun 82	65
Metertech DVM Review	Aug 82	37
Micro-History	May 82	26
Micro-Mania (Inside Microcomputers)	Apr 82	36
Microprofessor Review	Nov 82	54
The Oscilloscope Revisited	Mar 82	39
Planning On Success	Sep 82	49
Pocket TV	Mar 82	32
Reverb Revealed	Jun 82	38
Solar Cells	Jul 82	9
Spotlight On The Spectrum	Aug 82	14
Transducers	Jun 82	43
Video Discs	Mar 82	24
ZX81 Software Reviewed	Jun 82	66
ZX81 Review	May 82	20
ZX Interfaces Explained	Aug 82	10
ZX Software Reviewed	Jul 82	59

## INTO ELECTRONIC COMPONENTS

Diodes	Jan 82	42
Transistors	Feb 82	46
Transistors	Mar 82	59
741s	Apr 82	61
TTL And CMOS	May 82	61
Understanding Component Values	Jun 82	55
General Hardware	Jul 82	48

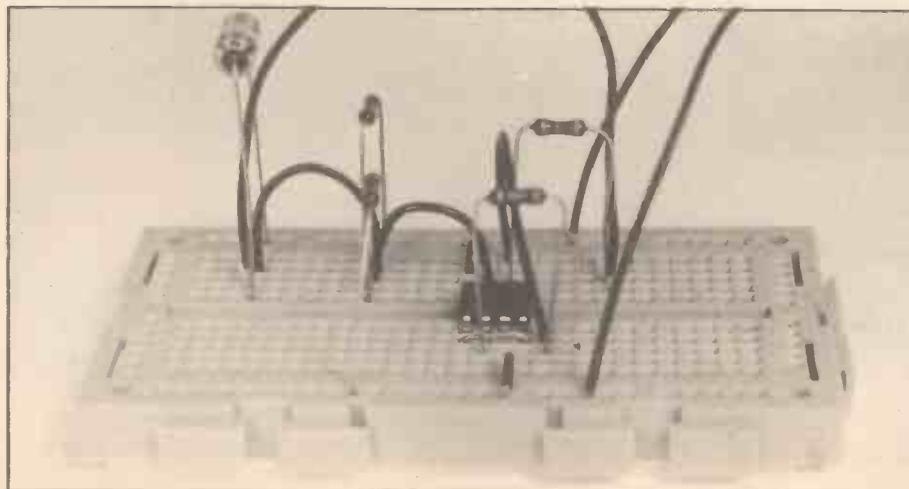*Beginner's Guide To Construction: August*



## POP AMPS

One-Op-Amp Microammeter	Dec 82	52
Voltage Follow And Hold	Dec 82	62

## FAMOUS NAMES

Sir Edward Appleton	Sep 82	37
Charles Babbage	May 82	53
J. M. E. Baudot	Dec 82	33
Sebastian De Ferranti	Jun 82	29
Lee De Forest	Feb 82	45
Allen B. Du Mont	Mar 82	47
Guglielmo Marconi	Apr 82	30
Julius Plucker	Aug 82	39
Valdemar Poulsen	Oct 82	21
William Bradford Shockley	Nov 82	51
Vladimir Zworykin	Jan 82	53

## SCALING THE HI-FI HEIGHTS

Amplifiers	Jan 82	10
Record Decks	Feb 82	37
Loudspeakers	Mar 82	14
Installing And Setting Up		
A System	Apr 82	67
Adding A Cassette Deck	May 82	44


## QUICK PROJECTS

AF/RF Signal Tracer	Apr 82	34
Experiments With Solar Cells	Jul 82	25
Heads And Tails Game	Mar 82	45
Light Seeker	May 82	55
Simple Timer	Jan 82	25
Sound Activated Switch	Feb 82	64

## 1982 ERRATA

Big Ear (Dec 82)	Dec 83	26
Microlog (Dec 82)	Jan 83	6, 72

*Diana VCO: November*

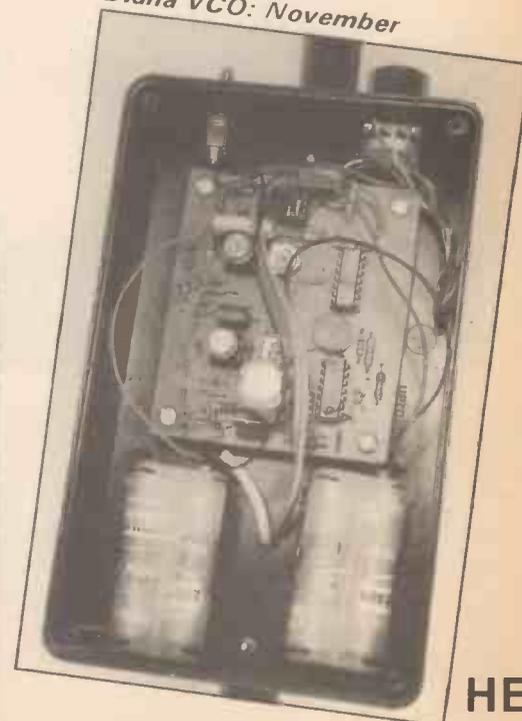

TRANSELE DOT MATRIX PRINTER. Compact. Serial Interface. 230 Volts £65 each.  
 8" MONITOR. CASED Non Standard. With info £20 each.  
 12" MONITOR. CASED. Non Standard. With info. £18 each.  
 CDSOR OSCILLOSCOPE CDU15. Dual Trace 35MHz. Delay Sweep £195 each.  
 SOLARTRON OSCILLOSCOPE CD1400. Dual Beam 15 MHz £95 each.  
 TELEQUIPMENT OSCILLOSCOPE S43 Single Beam 25MHz £95 each.  
 TELEQUIPMENT OSCILLOSCOPE S54 Single Beam 10MHz Solid State £95 each.  
 ADVANCE SIGNAL GENERATOR type 2. 1.50KHz-220MHz CW/Mod £30 each.  
 METRIC WOBBLULATOR type 210. 5-220MHz with manual £25 each.  
 AUTO TRANSDUCER TESTER type TT169 with leads As New. £20 each.

GEARED MOTOR 117/234 50Hz Input 4" dia x 5 1/2" deep. W shaft. NEW. £5 ea. P&P £4.  
 240VOLT AC MOTOR (Turntable style) Size 82 x 75 x 78mm. Shaft 43.4mm dia. £1.50 ea P&P £2.  
 MOTOR 12V DC Input. 3" dia x 4 1/2" deep. W shaft. NEW. £3.50 each P&P £3.  
 SYNCHRONOUS MOTOR 2 Phase 9 volt AC. 375 RPM. Good torque (needs 30 40mfd capacitor) Can be used as DC STEP. PING MOTOR. 8 STEPS PER REV. £1 each.

**STEPPING MOTORS AVAILABLE PLEASE ENQUIRE**

GEARED MOTOR 120V 50Hz 4 Watt 1 rpm 2" dia x 1 1/2" deep. £1.50 each.  
 TORIN SNAIL TYPE BLOWER 230V 22 Watts. Overall size 5 x 1 1/2". £4 each P&P £2.  
 CENTAUR FANS 4 1/2" 115V New. £4.50 ea.  
 MUFFIN 115V 4W. Unused £3 ea. P&P.  
 TRANSFORMERS - All Brand New. All 240 Volts Input. Sec 25.5 Volts 2.5A. Size 3 1/2 x 2 1/2 x 2 1/2". £2.50 each. Sec 115V 1A (Auto) - £1.25 each.  
 Sec 6V 1.6A - £1.50 each.  
 Sec 12V 100mA - 50p each.  
 TRANSFORMER 0-220 - 240V Input. Sec 0-12V & 0-24V 1 Amp (2 windings) £2 each.  
 TRANSFORMER 120V Input. Sec 10-0-10V 1A - 75p each. Sub-Min Transformer 0-120-240V Input. Sec 12-0-12V 4VA - 75p ea. 10 off £8.  
 TOROIDAL TRANSFORMER 0-115-230V Input. Sec 13-0-13.5V 8VA. £1.50 each. 10 off £12.  
 TOROIDAL TRANSFORMER 0-120-240V Input. Sec 0-12V-0-12V 10VA per winding. Encapsulated £4 each. 10 off £35.  
 Sub-Min PULSE TRANSFORMER. Sec centre tapped. Suitable Thyristor triggering. 20p each 10 off £1.80.  
 RAPID DISCHARGE CAPACITOR 8 mfd 4KV £5 each. P&P £2.  
 E.H.T. CAPACITORS 200pF, 500pF, 1000pF 8KV 20p each. 10 off £1.80.  
 ELECTROLYTIC CAPACITOR 15,000 mfd 25V. 20p each. 10 off £1.80.  
 ILLUMINATED ROCKER SWITCH. 2 pole 250V 8 Amp. Change - 50p each. 10 off £4.  
 SLOTTED OPTO SWITCH with data - 50p each. 10 off £4.  
 SPECTRAL RELIANCE TEN TURN POT. 100 ohm. 500 ohm. Brand New. 75p each. 10 off £8.  
 SLIDER POTENTIOMETER Twin Gang 200K. 2M - 35p each. 10 off £3. Swing Gang 10K - 25p each. 10 off £2.  
 PANEL MOUNTING FUSE HOLDER 1 1/2" fuse - 20p each. 10 off £1.50.  
 BELLINGLEE CHASSIS MOUNTING FUSE HOLDER for 1 1/2" fuse - 15p each. 10 off £1.

L.E.C. MAINS LEAD - 2 metre length Heavy duty - 60p each. 10 off £5.  
 4 CORE CURLY WIRE extending to 2 metres - 20p each. 10 off £1.80.  
 MICROPHONE/EARPIECE INSERTS. Brand New 75p each. 30 off £6.  
 TOKIN NOISE FILTER VF215FU. 250VAC 1.5A 50/60Hz. With Ising bracket New - £2 each.  
 CINCOR CONNECTOR STRIP 12 way 4BA Screw connection on both sides - 38p each. 10 off £3.  
 INFRA RED QUARTZ LAMP 230V 620 Watts Size 13 1/2 x 1 1/2" dia - £1.50 each. 10 off £10.  
 FERRANTI PHOTOCELL TYPE MS15 - 50p each. 10 off £4.  
 VU METER Scaled 0-5. Size 1 1/2 x 1 1/2" - 30p each. 10 off £4.  
 I.T. T. LOUD SPEAKER 2 1/2" dia. 50 ohm 0.2 Watt. New - 75p each. 10 off £8.50.  
 PCB KEYBOARD PAD. 16 Push Contacts. 0-8; A-F plus 3 optional - £1.50 each. 10 off £12.  
 KEYBOARD PAD. 12 Alps Reed Switches Push to make 0-9; & blank size 3 1/2 x 2 1/2" high - £4 each. 5 off £15. P&P £3.  
 VARIAC 2 Amp Ex-equipment. Good condition - £12 each. P&P £4.  
 E.H.T. Cable. Overall dia 5mm. - 10p per metre 100 metre drum £7.50. P&P £4.  
 Multi colour RIBBON CABLE 10 way - 50p per metre. 10 metres £4.14 way - 75p per metre. 10 metres £6; 100 metres £40.  
 LED. type TL209 Red with holder - 8p each. 10 off 70p. Dual in Line 8 pin OPTO COUPLER 25p ea. 10 off £2. I.C. SOCKET 16 pin 8p ea. 100 off £8.  
 EPROM. Texas 2564 £3 each. REGULATOR TYPE 7812 - 30p ea. 10 off £3.50.  
 MOSPOWER FET type VMP1 (TO 3) £1.50 each.  
 DIODES - 1N3470. 1N3063. 1S44. 6AX13 - 100 off £1.50. 1000 off £10. 1N4002 - 3p; 1N4003 - 4p.  
 TRANSISTORS - 2N3704 - 8p. 2N3904 - 50p; 2N5449 - 5p. BC107 - 8p; TIP46A - 30p.  
 BRIDGE RECTIFIER - CSC type 8055 - 20p each. 10 off £1.80.  
 TANTALUM BEAD CAPACITORS 0.1mfd 35V. 10 off £1. 100 off £7.50.  
 CAPACITORS - 0.047 25V. 0.005 100V. 0.47 12V. 0.001 200V. 10 off 30p. 100 off £2.  
 TRANSFORMER 240V Input. Sec 2KV 10MA Size 80 x 70x 110mm. Brand New. £4 each P&P £2.  
 BURGESS HEAVY DUTY MICROSCHWITCH with Lever & arm 75p ea. 10 off £8.50.  
 HONEYWELL 1/4 DUTY MICROSCHWITCH with Button 60p each. 10 off £5.  
 SPECTRAL RELIANCE POT 570 ohm. Wire wound 25p each. 10 off £2.  
 WIRE WOUND RESISTOR 11 Watt 27 ohm 10p each. 10 off 80p.  
 CABLE TIES White 8cm Black 12cm 50 for 50p.  
 CARBON FILM RESISTOR 15 ohm 0.5W. 100 off 50p. 1000 off £3.

**BIMBOXES**  
 Part No. Size Grey or Black White  
 BIM2002/12 100x5x25 1.10 1.21  
 BIM2003/13 112x6x23 1.25 1.37  
 BIM2004/14 120x6x24 1.32 1.45  
 BIM2005/15 150x8x56 1.54 1.69  
 BIM2006/16 190x110x60 2.70 2.97  
 BIM2005/25 150x8x76 1.91  
 BIM2006/26 190x110x90 3.20  
 BIM2007/17 112x6x23 0.83  
 Grey Base, Clear Lid  
 Grey Polystyrene, No Guides

**BIMBOXES**  
 4000 Series. ABS Base, Aluminium recessed lid.  
 BIM 4003 85x56x35 1.18 Grey  
 BIM 4004 111x71x48 1.46 or  
 BIM 4005 161x59x96 2.02 Black  
 1000 Series. ABS base, Sloping-Front Aluminium recessed lid.  
 BIM 1005 161x39/57x96 1.78 Grey or  
 BIM 1006 215x47/72x130 2.88 Black

**BIMTOOLS**  
 12v Mini Bimdrill inc collets 8.05  
 Mini Bimdrill Kit inc 20 tools 14.45  
 Mains Bimdrill inc collets 9.55  
 Mains Bimdrill Kit inc 20 tools 15.45  
 Bimiron 17W 6.15  
 Bimiron 27W 5.75  
 Bimpump. Desoldering Tool 6.25

All prices inc VAT. Add 50p per order p&p. SAE for full list. Mail order only.

**BIMSALES**

Dept HE/2, 48a Station Road, Cheadle Hulme, Cheadle, Cheshire, SK8 7AB. Tel: 061-485 6667



**HORIZON ELECTRONICS (Midands)**  
 Charlotte St. Rugby Tel: 781 38  
 Prime quality. TERRIFIC PRICES. Mail order only

<b>REGULATORS</b> 80/100V 25p 1 amp 40v 33p T23 variable 28p	<b>ZENERS</b> 500V 6p 1 watt 17p	<b>CAPACITORS</b> Radial 80V 7p 2.2 mfd 8p 4.7 mfd 8p 10 mfd 10p 22 mfd 12p 47 mfd 13p 100 mfd 14p 220 mfd 15p 470 mfd 55p 1000 mfd 50p	<b>AXIAL 80V</b> 1 mfd 7p 2.2 mfd 7p 4.7 mfd 7p 10 mfd 7p 22 mfd 7p 47 mfd 7p 100 mfd 7p 220 mfd 7p 470 mfd 7p 1000 mfd 7p	<b>LINEAR I.C.s</b> CA 3040 80p DAC 0800 235p CL 741 95p CL 742 180p CM 755 70p CM 755B 130p LF 347 155p LF 351 40p LM 301 24p LM 324 21p LM 339 46p LM 348 80p LM 390 80p	<b>LM 709</b> 440p <b>LM 747</b> 80p <b>LM 749</b> 25p <b>LM 750</b> 58p <b>LM 7805</b> 63p <b>LM 7805A</b> 63p <b>LM 7814</b> 195p <b>LM 301B</b> 215p <b>NE 567</b> 95p <b>NE 581</b> 135p <b>NE 581B</b> 275p <b>NE 581C</b> 275p <b>SN 74023M</b> 275p <b>SN 7414</b> 60p <b>SN 7415</b> 340p	
<b>DIODES</b> 1N 4001 3p 1N 4002 4p 1N 4004 6p 1N 4006 12p 1N 5401 8p 1N 5405 13p 1N 5406 14p	<b>BRIDGE RECTIFIERS</b> 1 amp 50p 2 amp 100p 3 amp 400p 5 amp 400p 8 amp 400p 10 amp 50p 15 amp 100p	<b>TRANSISTORS</b> BC 107 9p BC 108 9p BC 109 10p BC 142 22p BC 160 35p BC 162 7p BC 177 7p BC 212 7p BC 237 9p BC 300 52p BC 301 25p BC 302 38p BC 303 25p BC 307 38p BC 310 35p BC 324 35p BC 327 8p BC 328 15p BC 339 8p BC 347 15p BD 711 15p	<b>OPTO-ISOLATORS</b> TL 112 83p HL 33 117p MOC 300 185p	<b>FUSE HOLDERS</b> 20mm 30p 25mm 35p 30mm 40p 985mm 995p 990mm 1000p	<b>IC CONNECTORS</b> 18 way - 50p 20 way - 50p 25 way - 50p 28 way - 50p 30 way - 50p 32 way - 50p 34 way - 50p 36 way - 50p 38 way - 50p 40 way - 50p 42 way - 50p 44 way - 50p 46 way - 50p 48 way - 50p 50 way - 50p 52 way - 50p 54 way - 50p 56 way - 50p 58 way - 50p 60 way - 50p 62 way - 50p 64 way - 50p 66 way - 50p 68 way - 50p 70 way - 50p 72 way - 50p 74 way - 50p 76 way - 50p 78 way - 50p 80 way - 50p 82 way - 50p 84 way - 50p 86 way - 50p 88 way - 50p 90 way - 50p 92 way - 50p 94 way - 50p 96 way - 50p 98 way - 50p 100 way - 50p	<b>TOGGLE SWITCHES</b> 18 way - 50p 20 way - 50p 25 way - 50p 28 way - 50p 30 way - 50p 32 way - 50p 34 way - 50p 36 way - 50p 38 way - 50p 40 way - 50p 42 way - 50p 44 way - 50p 46 way - 50p 48 way - 50p 50 way - 50p 52 way - 50p 54 way - 50p 56 way - 50p 58 way - 50p 60 way - 50p 62 way - 50p 64 way - 50p 66 way - 50p 68 way - 50p 70 way - 50p 72 way - 50p 74 way - 50p 76 way - 50p 78 way - 50p 80 way - 50p 82 way - 50p 84 way - 50p 86 way - 50p 88 way - 50p 90 way - 50p 92 way - 50p 94 way - 50p 96 way - 50p 98 way - 50p 100 way - 50p

ADD: 65p post/packing to all orders at £15  
 VAT: add 15% VAT to total order value (inc p&p)  
 \*\*\* Comprehensive Catalogue Available: 85p \*\*\*

**STEWART OF READING**

116 WYKEHAM ROAD, READING, BERKS. RG6 1PL  
 Tel: 0734 00011

Callers welcome 9 am-5.30 pm Monday to Saturday Inclusive

**OVERCHARGED FOR YOUR BATTERIES?**

**RECHARGEABLE BATTERIES AND CHARGERS**

For Use in Your

- Personal Stereo
- Transistor
- Torches
- Cassette Recorders
- Metal Detector
- Test Equipment
- Car Kits
- Electronic Projects

**SANDWELL PLANT LTD**

656 Chester Road, Erdington, Birmingham  
 Tel: 021-373 9487 After hours Lichfield 57977  
 Also at Hitchin, Telephone: Hitchin 733254  
 Private enquiries welcome. Send SAE for details

**EDUCATIONAL RADIO KIT**

- For novice or student.
- Three projects in one.
- This T.R.F. AM. radio kit comes complete with instructions, test procedure and theory.
- A complete learning package, showing applications of many components.
- An ideal and useful GIFT for the enthusiast.
- Send only £19.95 to receive your radio kit to:


**HAZZLEWOOD ELECTRONICS EDUCATIONAL**

149 Main Street, Grenolside, Sheffield S30 3PN  
 Tel: 0742 463585


Send S.A.E. for further details. Quantity enquiries welcome.

PAYMENT by cheque or at your local post office by Transcash to account number 62 809 4507.

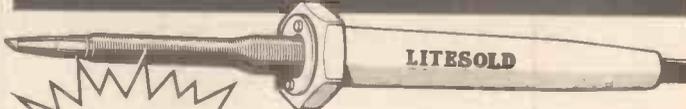**NEW LITESOLD EC50**  
 Electronically controlled Mains Iron



**£26.19** inc. VAT & P.P.  
 Features an advanced electronic temperature control circuit in the handle, with zero-voltage switching to prevent spiking, and proportional band control for spot-on temperature, without swing. Eliminates problems of mechanical thermostats and cost of low-voltage supply - operates 240 v a.c. 50 watt element gives fast heating and recovery. Temperature adjustable from 280 to 400°C. Made in our own works, and offered with burn-proof mains lead and long-life bit, at a special mail-order price of £26.19, including postage and VAT. Send cheque/PO to 'LITESOLD', ring for Access/ Barclaycard sales, or send for leaflet and order form.

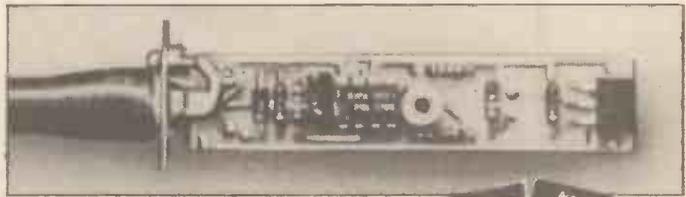

**LITESOLD** LIGHT SOLDERING DEVELOPMENTS LTD  
 Spencer Place, 97-99 Gloucester Road, Croydon CR0 2DN. Surrey. Tel: 01-689 0574

# QUIZ MASTER



All hands on the buzzer . . .

Rory Holmes

THE QUIZMASTER is a design for a universal quiz reaction/lockout system that is capable of being expanded to cope with any number of players. A quiz system generally enables a number of people to react to a question by activating an individual buzzer, preferably giving

some kind of visual indication as well, and should determine who was first to react. This system uses a special technique for indicating the first player to 'buzz'; it is based on a bi-directional busline which links all the quiz stations in use. The first player to 'buzz' sends a signal down the busline

to disable all the other stations, locking them out of the contest. Using this special technique it is possible to expand the system for any number of players or teams simply by linking identical buzzer units into the busline.

The buzzer stations are built into boxes, one for each player, so that as many as required can be linked up in any one of a number of configurations. Each unit naturally includes a pushbutton which activates a variable tone bleeper to indicate a fast reaction.

A bright visual display, which can be a number as illustrated above, is also built into each station; the light stays on for three seconds to allow the successful player to be identified. Each station has preset volume and tone controls, and the circuit draws next to nothing when in the reset state, ie waiting for a 'buzz'.

## All Tied Up

It should be noted that if two players hit their buttons at exactly the same moment then both will 'buzz' and light up, indicating a draw. In the event this will have to be resolved by a further question. Since the individual stations have a three-second 'time out' which resets all stations after that time, it is impossible for any player to cheat!

A number of possible link-ups are illustrated in Figure 1. The versatility of the system allows large school quizzes or games at home for a smaller number of players; it could be used as the ultimate arbiter in Snap or similar card games, or simply as a reaction tester in a contest between any number of people.

Each buzzer station may be powered by an internal battery or, alternatively, a simple external power supply could drive any number of link stations. All can be controlled via the busline from a remote "Master Station", which consists of a simple

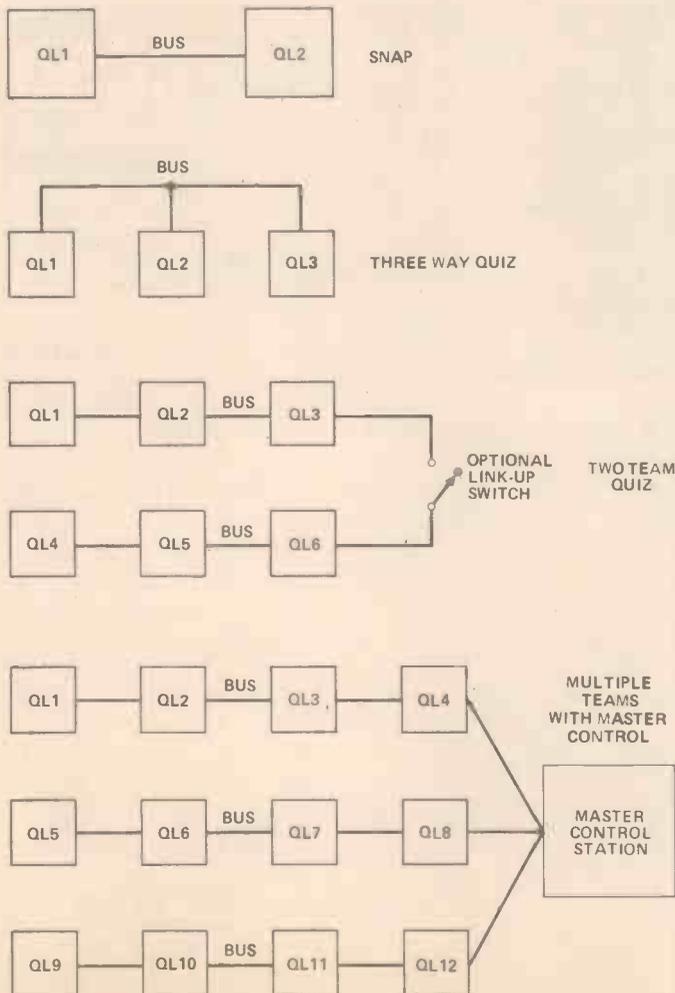


Figure 1. The Quizmaster can be connected up in a versatile variety of ways, including a link-up with a master control station. The method of connecting this up is shown in Figure 2, over the page.

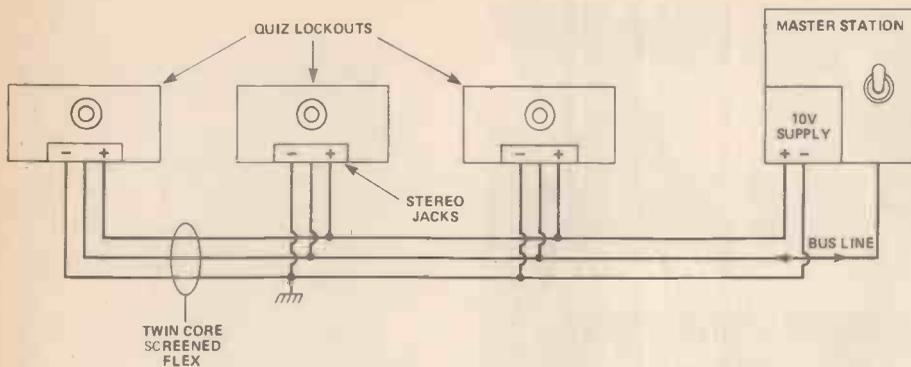


Figure 2. Connecting up a number of Quizmasters to a Master Control switch. See Figure 7 for a suggested circuit.

switch and indicator arrangement as shown in Figure 2. This method would allow timed questions by enabling or disabling the system from a central control point.

## The Circuit?

The pushbutton arrangement is designed to produce a single positive-going pulse to pin 13 of the NAND gate IC1a. This input is normally held low by R2, while R1 ensures that C1 is fully discharged. When the pushbutton is operated both sides of C1 go positive, but then the capacitor rapidly discharges through R2. This positive-going pulse lasts for a few microseconds only, whereupon the pin 13 input is returned to zero volts as C1 discharges.

If all units are in the reset condition the busline is being held high, maintaining a high on the pin 12 input to IC1a via R3 and R4. Thus the positive input pulse appears at the output of the NAND gate as a low-going pulse. This is coupled directly to the pin 1 input of IC1b which, together with IC1c, forms a monostable circuit.

However if another player has got

in first, the busline will be low, holding the output of IC1a at logic 1 until the busline is reset.

Pins 5 and 6 of IC1c are held low, normally, by R5, keeping the output pin 4 at logic high, and this output is also fed back to the other input of IC1b at pin 2. And since the pin 1 input is normally high until a low-going pulse comes from IC1a, IC1b output at pin 3 will normally be low. This keeps the monostable timing capacitor C2 discharged while in the reset condition. But when the negative pulse arrives at IC1b from the pushbutton, the output will immediately go high, taking pins 5 and 6 with it since there is zero voltage drop across C2. Pin 4 of IC1c then goes low, taking pin 2 of IC1b low and disabling the gate by keeping pin 3 at logic 1. The monostable period lasts until R5 discharges C2 below the Schmitt trigger threshold, at which point the monostable resets to its rest state, awaiting another input pulse.

The time period is set by C2 and R5 at about three seconds, and the monostable cannot be re-triggered within this time.

Transistor Q1 is turned on via R6 by

## Parts List

### RESISTORS

(All  $\frac{1}{4}$  watt 5% carbon)

R1, 2	100k
R3	2M2
R4, 6	10k
R5	3M3
R7	100R
R8	4M7
R9	27k
R10	10R

### POTENTIOMETERS

(both miniature horizontal presets)

PR1	470k
PR2	4k7

### CAPACITORS

(Ceramic unless noted)

C1	1n
C2	1u
	35V Tantalum
C3	68n
C4	22n
C5	10n
C6	22u
	16V axial electro

### SEMICONDUCTORS

IC1	4093B
	CMOS Quad 2-in Schmitt trigger NAND
Q1	BC184L
Q2	BC214L
Q3	BFY51
D1, 2	1N4148


### MISCELLANEOUS

SW1	push-to-make
SPK1	8-16R mini speaker
LP1	6V/100mA bulb
J1, 2	2.5mm sockets (see text)

Case, Bimbox 6005; PCB; Veropins; 9V PP7 battery & clips; wire, solder, nuts and bolts etc.

BUYLINES .....page 26

Figure 3. The Circuit. An On/Off switch is not included as power consumption is less than 1mA in the rest state.

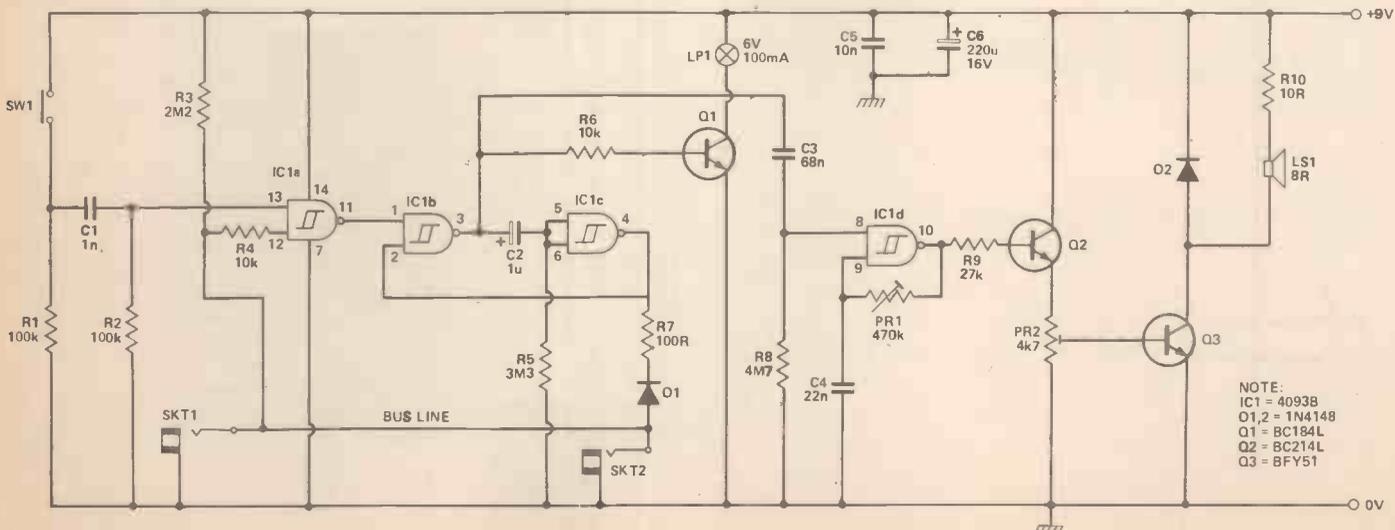

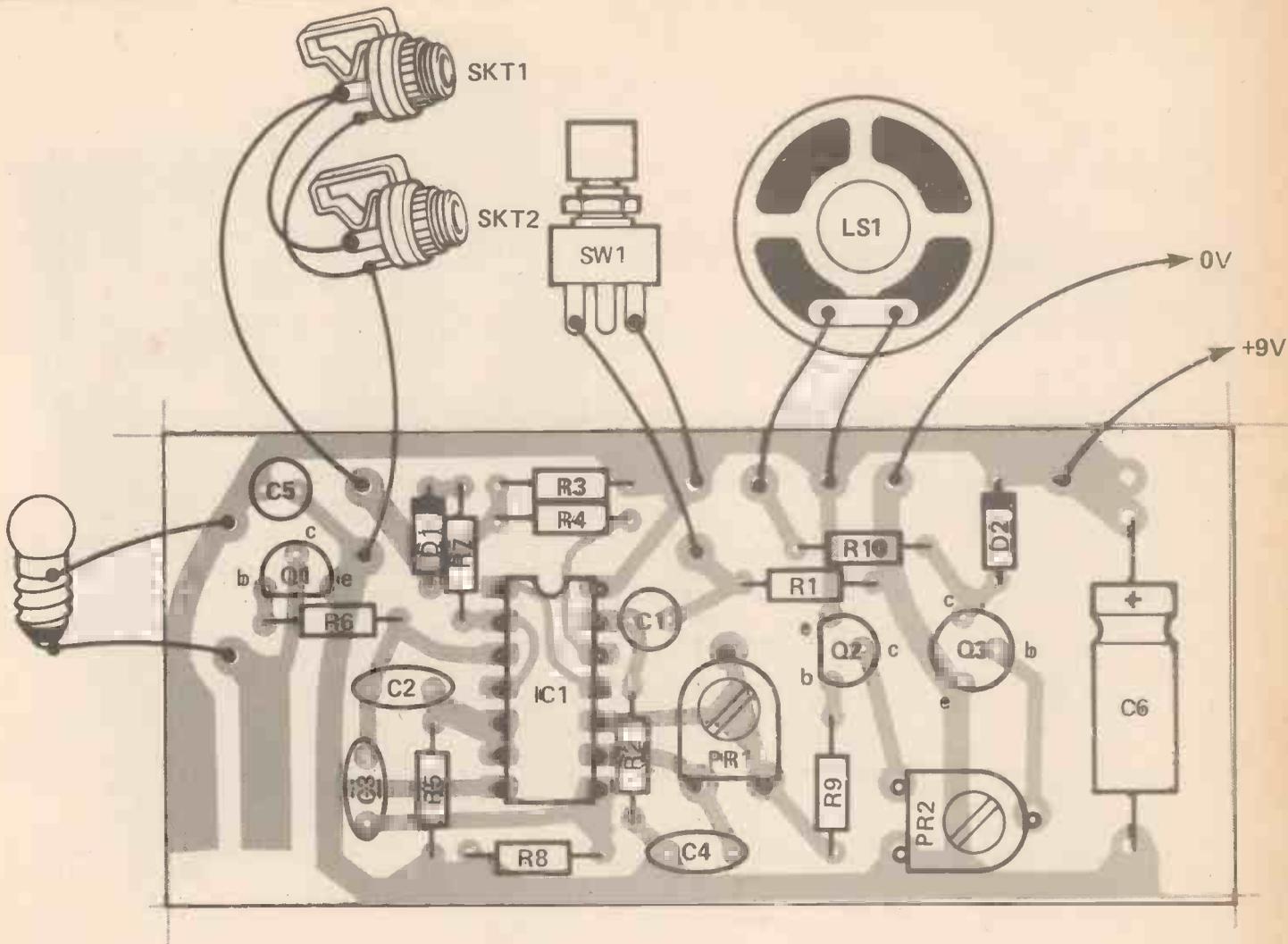


Figure 4. The Component Layout. Note the orientation of D1 and 2, C2 and IC1.

the logic 1 voltage from pin 3 of IC1b, and remains on for the period of the monostable. Q1 supplies up to 200mA for the indicator lamp, LP1.

Meanwhile the low-going signal from the monostable output (pin 4 IC1c), is coupled to the busline via R7 and D1; R7 is there to limit the current on the busline in the event of a short circuit, and D1 allows other stations to take the busline low without affecting the monostable.

At the moment that the first monostable triggers, another monostable based around IC1b is also triggered via C3. IC1d is really a gated squarewave oscillator, with the frequency set by PR1 and C4, to produce an audio tone. When the positive edge of the first monostable pulse is passed via C3 to pin 8 of IC1d the oscillator is gated on, but will turn off after a period determined by the discharge of C3 through R8; this is set

for about one second. Q2 and Q3 are used to amplify the squarewave and drive a small eight Ohm speaker. PR2 adjusts the drive to Q3 and thus the volume; D2 is included to protect Q3 against inductive transients.

Owing to the use of CMOS ICs and the arrangement of the amplifying transistors, the current consumption is held to less than 1mA in the rest state, and so an on/off switch is not included. One could easily be arranged by using, for the busline, a socket with an additional pair of normally-open contacts wired to the power supply, so that power is switched automatically when the unit is connected into a Quizmaster system.

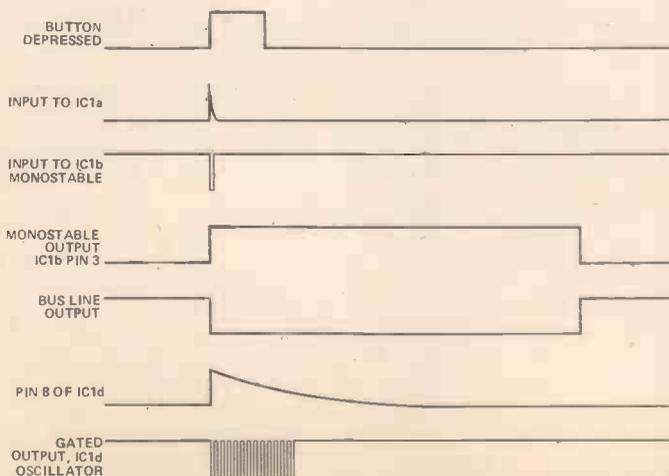



Figure 5. This diagram shows the sequence of signal level changes when the Quizmaster is operated, as described in the text.

### Construction

The circuit layout is not critical and could be built on Veroboard, but we recommend using our PCB for a much simpler and neater construction. The PCB overlay is shown in Figure 3, and there should be no problems with this as long as the orientation of the IC and the two diodes are carefully noted. The tantalum capacitor C2 must also be mounted with correct polarity. The transistors are specified as the 'L' versions to match the



Figure 6. Internal wiring of the Quizmaster.

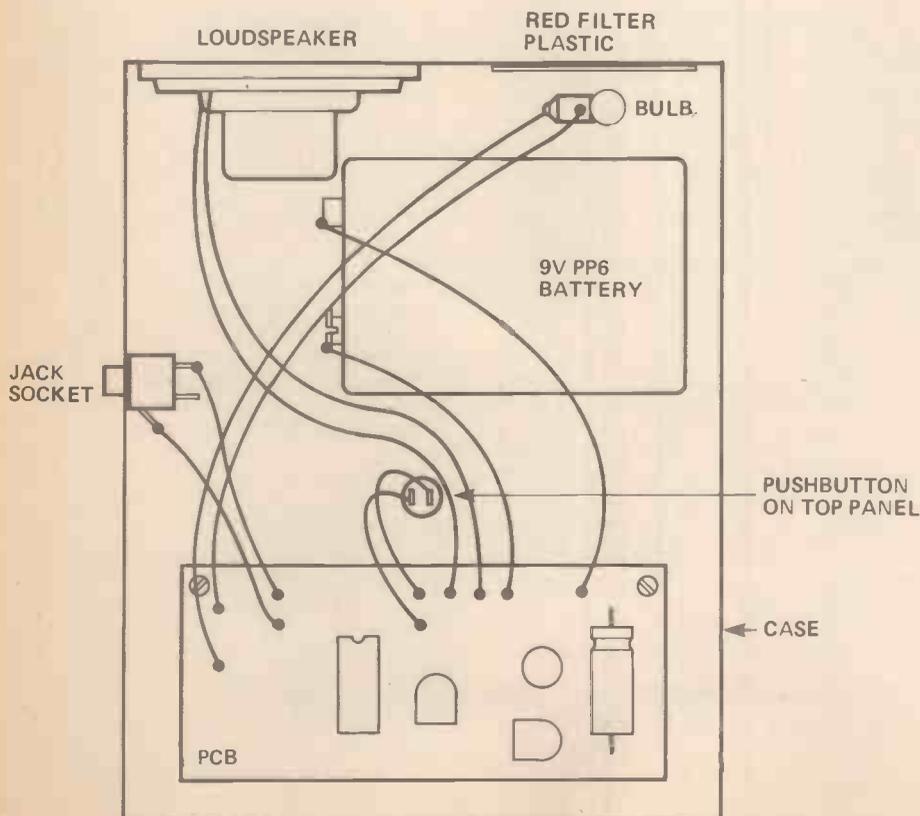

overlay diagram. Different versions may be used, but their pinouts will vary and should be checked before soldering.

Solder in all the components, following the overlay diagram and leaving all the semiconductors to last. It is a good idea to use an IC socket from the CMOS chip. To complete the PCB, solder in ten Veropins at the points marked for external connections to the switches etc (this is not essential, but makes connecting up a great deal easier, particularly when the board has been mounted in the case). Finally, don't forget to check the PCB tracks for solder bridges or bad joints.

The case used for housing each quiz station should ideally have a sloping top panel with sufficient room at the high end of the box for the bulb display and loudspeaker. There should also be room for a PP6 or PP7 9 Volt battery, unless a mains power unit has been opted for.

The box used as seen in our photograph is a BIMBOX 6005, very reasonably priced at about £2, and the ideal size for each station. The internal photographs and diagram show the mounting arrangement for the speaker pushbutton, jack socket and lamp display. The assembled PCB is screwed down in the box and wired

## HOW IT WORKS

The quiz lockout system provides every player with a buzzer station. The block diagram shows the various circuit blocks that are involved in these stations. Each unit is linked to all the others via a common bus rail as shown in the diagram, allowing any number of buzzer stations to be simply incorporated into a complete system. The bus rail carries a single logic level relative to ground and is bidirectional, in that each station can

both send a logic level to all other stations and can also receive a signal from any other station. The bus rail allows the system to determine who buzzed first, from a number of players.


Studying the block diagram from left to right, we start with the player's pushbutton and debouncing circuit. This ensures that we get one brief pulse every time the button is pressed. A disable input on this circuit prevents these pulses appearing

when it's at logic low; it is connected to the bus rail to receive logic signals from the other units.

The push button pulses then trigger a full monostable circuit which goes from low to logic high for three seconds and then back to its rest state of logic low. The high period of this monostable is used to light a lamp, via a sample driver circuit, to indicate that this buzzer station has been successfully activated. At the same time a complementary version of the monostable period goes to the bus rail, transmitting a three second logic low signal to all the other buzzer stations.

In this way the firing action of all the other push buttons is disabled, locking them out for the duration of the monostable period. The first player to buzz will light his display lamp to the exclusion of any other players.

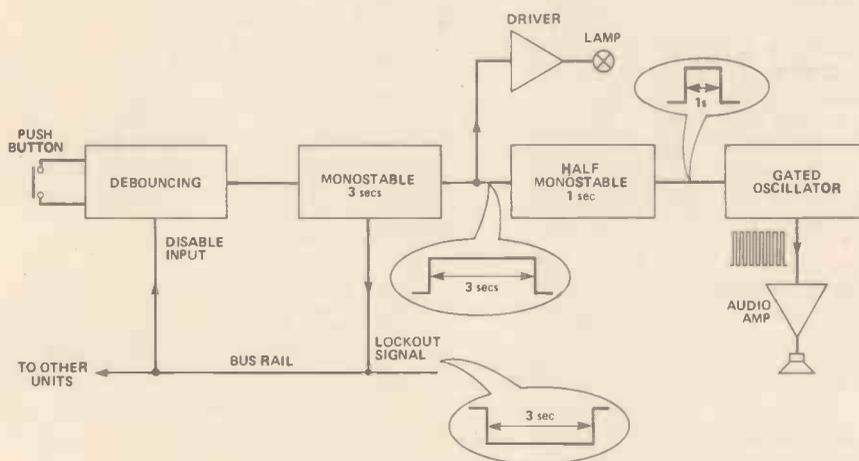A half monostable circuit, triggered as the push button is pressed, is used to provide a loud one second bleep. The monostable turns on a gated audio oscillator to provide a short variable frequency tone which is amplified to drive a loudspeaker. Each buzzer station can be individually adjusted over a wide range of tones and volume, so adding 'personality' to different player's buzzers!




up to the external components from the terminal connections as indicated on the overlay diagram.

If a battery supply is not being used then miniature stereo jacks should be used in place of the mono type to provide an additional inlet for the positive supply rail. The jack connections will then be ground, bus rail, and positive supply. Otherwise, the jack connections would be simply ground, and the bus rail; one or two jack sockets may be provided. In either case, battery or mains, an on-off switch is not required. If a master station for a number of quiz terminals is built, then this could house the mains power supply and would connect up in the same chain via a stereo jack to supply any number of units. A suitable power supply is shown in Figure 1. The loudspeaker was simply glued to the high end of the case with a number of holes drilled in the plastic for sound outlet.

Using a filament bulb as the display indicator allows any number to be displayed by each unit. This is easily achieved by blocking out areas of a piece of red filter plastic with black ink, leaving the desired number outlined, and securing this behind a square hole cut out in the front panel. The display bulb behind this mask will then brightly illuminate your chosen number.



Figure 7. A circuit for a Master Control switch, incorporating a power supply which can replace the Quizmaster's batteries.

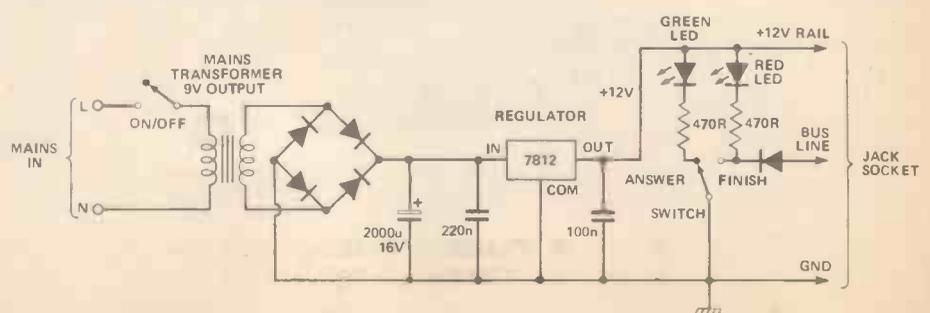

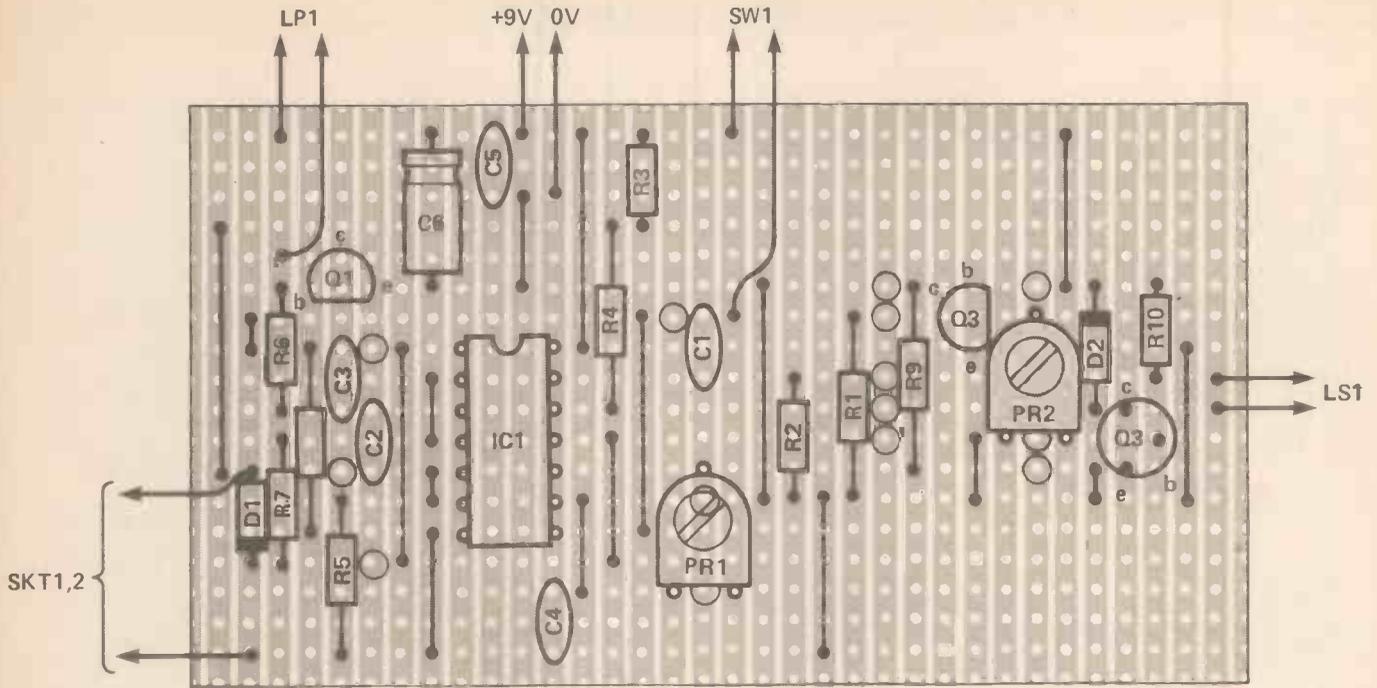


Figure 8. An untested Veroboard layout is given as an alternative to the PCB, for those who prefer building on Vero.

When assembly is finished the buzzer station can be tested. With power applied, and no bus line connections, the unit should emit a loud bleep the pushbutton is pressed and the display light will come on for about three seconds. PR1 can now be adjusted to set the desired buzz tone,

and PR2 will set the volume level. Now connect a jack plug into the bus rail socket and short together the terminals; if the buzzer is now inactive, everything is OK. Releasing the terminals will return the buzzer to its normal mode. Are you ready, then? Your subjects is . . .

# MICROTANIC COMPUTER SYSTEMS LTD.

## MICROTAN 65 NO OTHER COMPUTER IS AS PERSONAL!

For less than £60 you can start building your own Computer that truly suits your needs and, of course, eventually far more superior to any Computer available off-the-shelf.

MICROTAN 65 comes in kit form, complete with manual, full instructions, board with components, (kit form or fully built) our full back-up service, and your own Microtan World Magazine available on subscription.

### FLEXIBLE & EXPANDABLE SYSTEM — 1K to 256K!

Just look at the options:

- |                      |                               |
|----------------------|-------------------------------|
| 1 DISK CONTROLLER    | 7 MASS EPROM STORAGE BOARD    |
| 2 REAL TIME CLOCK    | 8 INDUSTRIAL CONTROLLER BOARD |
| 3 EPROM PROG. CARD   | 9 40K RAM BOARD               |
| 4 SOUND BOARD        | 10 HIGH RES. GRAPHICS 256x256 |
| 5 SERIAL I/O BOARD   | 11 PRINTER FACE BOARD         |
| 6 PARALLEL I/O BOARD | 12 ASC11 KEYBOARD             |

### FULL RANGE OF SOFTWARE


Languages available: Machine Code, Assembly, Basic, Forth, and Pilot



Microtan World Magazine
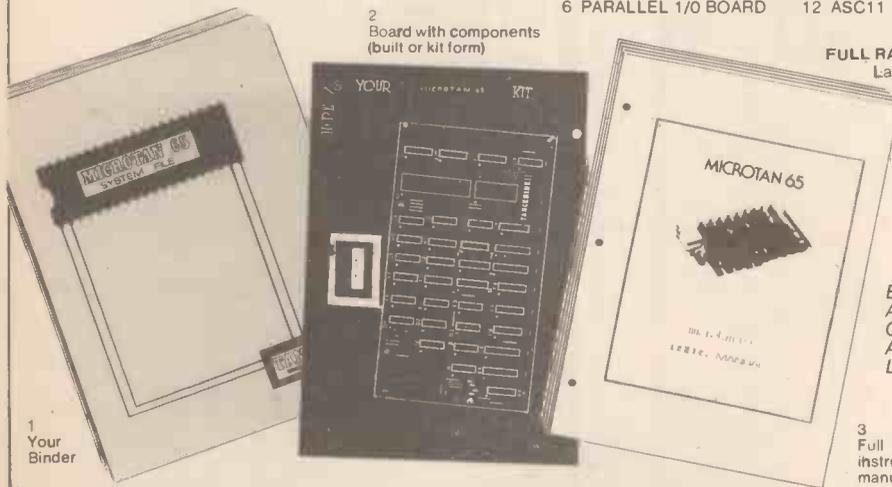
### HOW TO ORDER:

Enter details in the coupon below, enclosing your cheque made payable to: Microtan Computer Systems Ltd. Prices include VAT add £1.50 p&p. Please allow 14 days for delivery.



1 Your Binder

**BUILD AS FAST OR SLOW AS YOU LIKE!**

3 Full instructions manual

**MICROTAN COMPUTER SYSTEMS LTD**  
 SHOWROOM: 16 UPLAND RD  
 DULWICH, LONDON SE22  
 TEL: 01-693-1137

Also available from:  
 Waltham Forest Computer Centre  
 889 Lee Bridge Rd.  
 Nr Whipps Cross, Walthamstow E7  
 Tel: 01-520 7747

Post to:  
**MICROTANIC COMPUTER SYSTEMS LTD**  
 16 UPLAND RD, LONDON SE22  
 Tel No. 01-693 1137

Please rush me my starter kit:  
 (Please tick)

kit form — I will build myself £59.95  
 Fully Built £69.95  
 Complete system wall chart

I enclose my cheque/P.O. for £

Name .....

Company .....

Address .....

Tel (Day) .....

Tel (Eve) .....

# BOOKSHELF

THE HE BOOKSHELF is pleased to offer you a range of top quality electronics paperbacks for you to read and enjoy delivered direct to your door!



**IC PROJECTS FOR BEGINNERS** £1.95  
Especially written for the beginner offering a range of simple projects



**The Art of Programming the ZX81** £1.95  
Shows you how to use the features of the ZX81 in programs that fit into 1K and are still fun to use



**EASY ADD-ON PROJECTS FOR SPECTRUM, ZX81 & ACE** £2.25  
This book describes how to build a number of electronic projects which you can use with your Spectrum, ZX81 or Jupiter Ace microcomputer



**ELECTRONIC PROJECTS FOR CARS AND BOATS** £1.95  
Fifteen fairly simple projects complete with stripboard layouts




**25 SIMPLE AMATEUR BAND AERIALS** £1.95  
This concise book describes how to build amateur band aerials that are simple and inexpensive to construct and perform well



**HOW TO DESIGN AND MAKE YOUR OWN PCBs** £1.95  
The purpose of this book is to familiarise the reader with both simple and more sophisticated methods of producing printed circuit boards (PCBs)



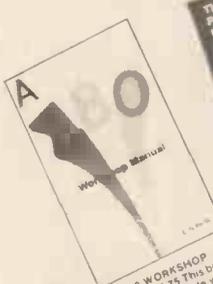**MODEL RAILWAY PROJECTS** £1.95  
Build your own controllers, signals and sound effects etc. and add realism to your model railway



**A Z80 WORKSHOP MANUAL** £2.75  
This book is intended for people who wish to progress beyond the stage of basic programming to topics such as machine-code and assembly language programming or need hardware details of the Z-80 based computer



**THE ART OF PROGRAMMING THE ZX SPECTRUM** £2.50  
Simply helps you get the most out of your Spectrum



**CB PROJECTS** £1.95  
Shows you how to make a number of useful and interesting CB accessories



**THE ART OF PROGRAMMING THE 16K ZX81** £2.50  
Concentrates on good programming style and helps you use your 16K RAM pack and ZX printer to the full




**POPULAR ELECTRONICS PROJECTS** £1.95  
An interesting collection of projects which will appeal to most hobbyists




**AN INTRODUCTION TO VIDEO** £1.95  
For the person who has just, or is just about to buy or rent some video equipment but is not sure what it is all about



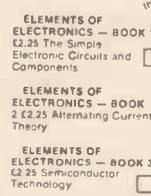
**HOW TO MAKE WALKIE-TALKIES** £1.95  
All you need to know to build your own walkie-talkie



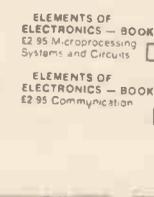
**ELEMENTS OF ELECTRONICS - BOOK 1** £2.25  
The Simple Electronic Circuits and Components



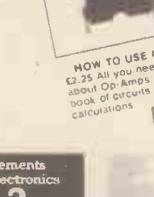
**ELEMENTS OF ELECTRONICS - BOOK 4** £2.95  
Micro-processing Systems and Circuits



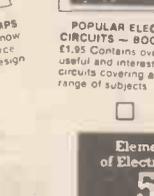**ELEMENTS OF ELECTRONICS - BOOK 2** £2.25  
Alternating Current Theory



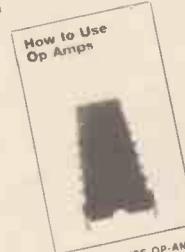**ELEMENTS OF ELECTRONICS - BOOK 5** £2.95  
Communication



**How to Use Op-Amps** £2.25  
All you need to know about Op-Amps: a source book of circuits and design calculations



**POPULAR ELECTRONIC CIRCUITS - BOOK 1** £1.95  
Contains over 70 useful and interesting circuits covering a wide range of subjects



**POPULAR ELECTRONIC CIRCUITS - BOOK 2** £2.25  
Over 140 pages of useful and interesting circuits



**PRACTICAL BUILDING BLOCKS - BOOK 1** £1.95  
Most circuits are built up from building blocks of a standard type. This book shows the reader how to combine these blocks to produce projects of their own design



**PRACTICAL BUILDING BLOCKS - BOOK 2** £1.95  
Most circuits are built up from building blocks of a standard type. This book shows the reader how to combine these blocks to produce projects of their own design

To receive your books you only need ✓ the I  for each title you require and send this page duly completed with your remittance to the address stated.

I enclose my cheque/Postal Order/Money Order (delete as necessary) for £..... (payable to ASP Ltd) OR

Debit my Access/Barclaycard (delete as necessary)

Name (Mr/Mrs/Miss).....

Address.....

Signature

**SEND TO:**  
**HE BOOKSHELF, 513 London Road, Thornton Heath, Surrey CR4 6AR**  
Please use **BLOCK CAPITALS** and include post codes.

Number of books ordered.....  
Total value of books £.....  
Add 75p P&P  
**TOTAL PAYMENT £.....**

# MASTER ELECTRONICS NOW! The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY  
THIS IS THE AGE — OF ELECTRONICS!  
the world's fastest growth industry...

There is a world wide demand for designers/engineers and for men to service and maintain all the electronic equipment on the market today — industrial — commercial and domestic. No unemployment in this walk of life!

Also — the most exciting of all hobbies — especially if you know the basic essentials of the subject. . . .

A few hours a week for less than a year — and the knowledge will be yours. . . .

We have had over 40 years of experience in training men and women successfully in this subject.

Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.



**British National Radio & Electronics School** Reading, Berks. RG1 1BR

**FREE!**

COLOUR BROCHURE



POST NOW TO

Please send your brochure without any obligation to

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

HE/1/841

BLOCK CAPS PLEASE

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS please state below

OR TELEPHONE US  
0734 51515 OR  
TELEX 22758  
(24 HR SERVICE)



**British National Radio & Electronics School** Reading, Berks. RG1 1BR

# CAREERS IN ELECTRONICS

Careers In Electronics begins 1984 with the first in a three-part look at electronics in the Armed Forces. This month we concentrate on the Army, with the Navy and Royal Air Force to follow.


Helen Armstrong

Most readers will be at least passingly familiar with the word 'Milspec'. For those who aren't, 'Milspec' is short for 'Military Specification', and refers to components and hardware whose accuracy and reliability measures up to the demands of military use. If a piece of hifi or a commercial control system breaks down, it can cause anything from mild anguish to heavy financial loss; if a weapon, aircraft or military communications system packs up, lives could be at stake. Add to this that military equipment in active use has to stand up to long hours, rough handling and expeditious maintenance, and it's obvious that it must be designed and built and serviced to very high standards. These standards have to be maintained and improved in peacetime in constant preparation for the possibility (however slight) of real conflict.

When industrial engineers want specially high standards of reliability, they look for Milspec components. The same could be said about military engineers, logically enough: there is no point in having top-grade manufacture and design unless the engineers who are looking after it are also top-class.

While the three 'branches' of the Armed Forces are independent of each other and responsible for their own administration, there are a few generalisations which can be made. They are designed to run like a very well oiled and tuned machine, to respond quickly and efficiently in situations where the results of their actions could be momentous. The men are as much a part of the machinery as the machinery: even at the lowest levels of responsibility, the soldier/sailor/airman is responsible for his personal kit and weaponry, and above this level he is responsible for organising and supervising other men in addition.

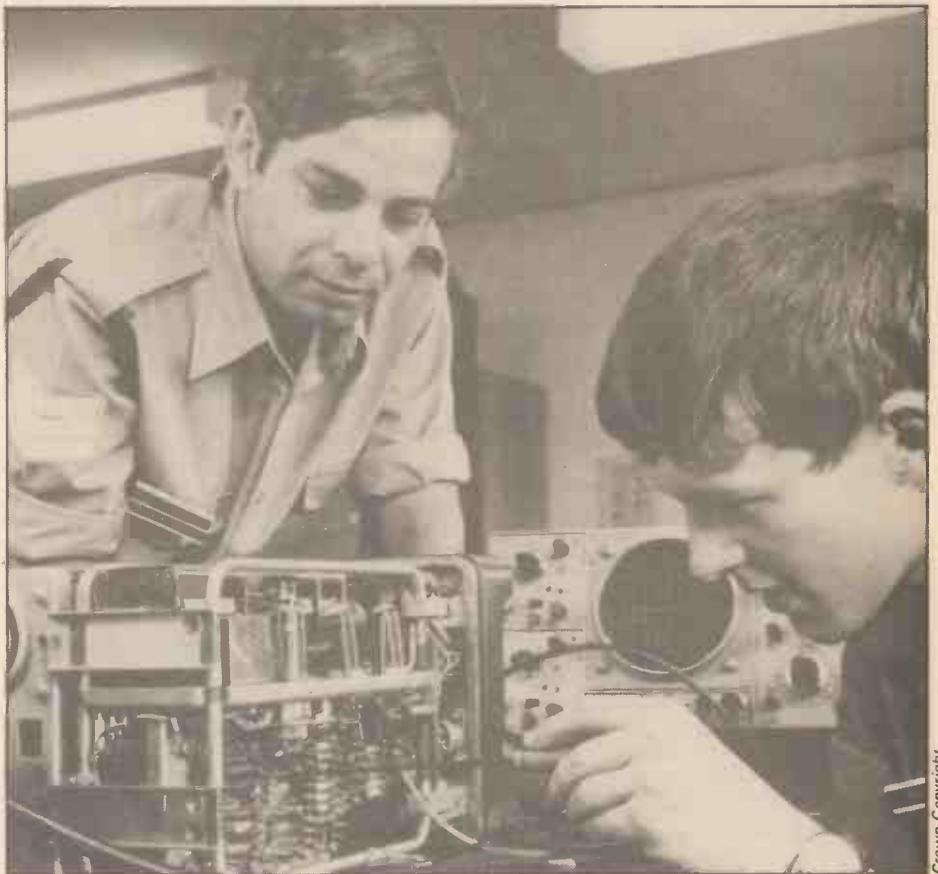Because continuous training is given, you cannot quit for Forces at a moment's notice if you don't get on with the people you work with. So it's not a



comfortable option for anyone who is not happy with the idea of accepting and delegating responsibility while at the same time following instructions (or "orders", as they are known in the trade) and putting a certain amount of implicit faith in the hierarchies above him. It's not a venue for argument or indecision, which is not to say that you are not required to think.

All the services place great emphasis on 'leadership' and 'management', by which they mean the ability to get men and material resources working

effectively, not only by organising them but by being able to demonstrate that you are not asking them to do anything that you would not do yourself. This responsibility means being able to feed back your opinions and assessments to the people above you, without inducing trouble and strife. The trouble and strife is meant to come from the 'other side', not from within: management is the name of the game, with a vengeance. Where does electronics fit in?

The Army, Navy and Air Force need engineering skills at all levels. They set

## Careers In Electronics


An electronics teaching lab. at an Army college.

high standards, and, of more interest to anybody who has not already decided to choose the forces life *per se*, offering thorough training, from basics on to higher degree level, in all relevant engineering subjects, (which are most). Again, because of the 'management' aspect, specialised as it is to Service life, the engineering training has aspects which you wouldn't expect to acquire in civilian life. And yes, these aspects do include 'square bashing' (marching in formation), saying "Yes sir", and negotiating your way on foot across a rain-sodden moor with a pack load of equipment. If you think you can't cope with all this — don't join the forces.

But read on: there's more on offer for the bloke who has electronic aspirations. I say bloke: opportunities for ambitious or technically minded women exist but are limited because the British Services do not accept women in a fighting role. Why not? There are lots of excuses given, which I am not going into. Don't expect that to change until the US Armed Forces get over their own teething troubles integrating women into the fighting forces. Meanwhile, engineer = male, unless otherwise noted.
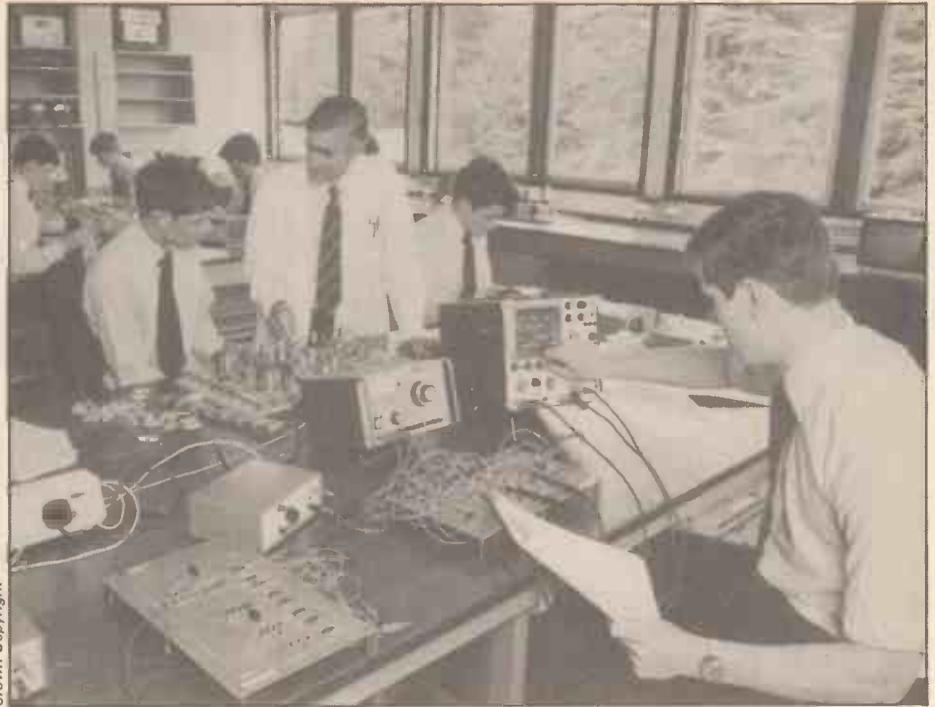
### In The Army Now

In the ARMY there are three corps which train and deploy engineers: The Corps of the Royal Electrical and Mechanical Engineers (REME), the Corps of the Royal Engineers (known as "Sappers") and the Royal Corps of Signals. The Sappers are highly trained combat engineers and their work doesn't involve electronics to any extent; the Royal Corps of Signals are



Crown Copyright

entirely concerned with communications, so there is a certain amount of radio and data processing electronics involved. REME however is the corps which employs most electronics technicians and engineers.

The Army expects to take in recruits from age 17 upwards (or 15¾ for Apprentice Technicians) and train them from scratch at one of their colleges. In the case of REME Electronics Trades the training is at the School of Electronic Engineering at Arborfield. This begins with basic electronic theory, and is followed by more specialised training as a telecommunications technician, radar technician or control equipment technician. This involves familiarity with the equipment being used, the principles on which it works, and fault-finding and repair.

Avionics Technicians, who are trained by the Aircraft Engineering Training Wing at Middle Wallop, follow a similar course, as do Instrument Technicians from the Weapons trades, who are based yet another establishment, the School of Electrical and Mechanical Engineering at Bordon; their specialisation is gunnery.

REME basically accepts men of its own choosing regardless of whether or not they are technically qualified, and then trains them for its specific needs. Between 23 and 35 they may be chosen for an artificer course bringing them up to the rank of Staff Sergeant, where they will act as supervisors or junior managers, and may be registered as technician engineers (CEI) if they attain the right qualifications. The qualifications studied include HNC and City and Guilds Full Technological Certificates (or Technician Education Council Awards).

This is the career route which can lead, eventually, to commissioned rank for some technicians.

In common with all the services, REME and the other Army technical corps have an apprenticeship scheme, which takes entrants between school leaving age and 17 and puts them through a two or three year course involving all their technical training, military training and whatever educational and academic subjects they need to study, putting them a bit ahead of later entrants in their progress through the ranks. They study for the Certificates and Diplomas of the Technician Education Council.

REME trainees have twelve weeks of 'basic military training' before their technical education gets going. This means learning the procedures, rules, regulations and reasons by which the Army operates, and includes learning

Setting up a radio under field conditions with a field regiment.



Crown Copyright

how to look after the uniform and kit, drilling, weaponry, and fitness and survival training. The Royal Corps of Signals come right out and say it: "It's tough. Not everyone enjoys it". Even so, this is the part of the training which people who have been through it remember with a sense of achievement, and it underlines the fact that you are a soldier from day one.

## Qualifications For Life

The Royal Corps of Signals cover such trades as Electronic Warfare Operator, Telecommunications Mechanic, and Data Telegraphists, and all technicians learn basic electrical and electronics theory to start with. Recruits join the field units generally as Class III tradesmen at the end of their training period, and work up from there. Between 15¾ and 17½ you can join as an Apprentice or between 16 and 17 as a Junior Signaller, both of which include an earlier start and extra education. Apprentices study for the BTEC or City and Guilds Certificates; Junior Signaller training follows the same basic career structure, with the added proviso that they are looking for leadership qualities suitable for possible promotion. This is only a difference of emphasis; promotion towards and into officership is possible from any part of the Service.

All the Services emphasise that the courses of training, and qualifications gained are basically the same as those in civilian life, and are recognised by industry and the trade unions.

Combine this with the facts that few men spend their whole working lives in the services, and that there are regular options to leave the service during the basic term of engagement and it is apparent that Army training provides a good technical education for those who do not want to make a long-term career in the Army, as well as those who do. Ex-technicians from these three corps quickly find good jobs in civilian life. Some people join one of the forces specially to get a good education in a particular field, plus the all-round experience of doing a physically as well as a mentally demanding job for a few years.

The same is true for more highly qualified men who can enter the Army as officers at various levels, and on Regular or Short Service commissions.

Non-commissioned members of the Army enlist for twenty-two years, after which they normally have to leave the service, but there are numerous factors governing when they can (or must) leave before that time, quite apart from factors of health and competence (which govern any career, but more so in the services where comparatively high standards are needed just to do the job). A new recruit has a period of about six weeks after joining when he can opt to


leave (or be asked to leave); after this, options to leave come at three, six and nine years; after this, the soldier can re-sign for further set periods, up to the twenty-two years.

REME officers, with the exception of some Short Service officers, must be graduates in a relevant subject. There are various ways of achieving this: you can enter as a graduate, or as an under-graduate, or show that you have the ability to study for a degree under Army sponsorship.

A graduate or imminent graduate going in as a Direct Graduate Entrant attends a four or five month Graduates' course at Sandhurst before going on to the REME Officers School at Arborfield for a Postgraduate course in a chosen specialist discipline. People just going into University, or in their first or second year, can apply to an Army Undergraduate Cadetship, where the Army pays fees and a salary; entrants joining direct from school, on the other hand, spend a year at Sandhurst as an officer cadet and then spend some time in Officers School and REME Engineering schools covering basic REME engineering practice. This is followed by a 'posting' of up to eighteen months as a junior subaltern in an active workshop.

A three year degree course will then be taken, normally at the Royal Military College of Science, Shrivenham, with workshop practice courses and projects to be undertaken in the long vacations.

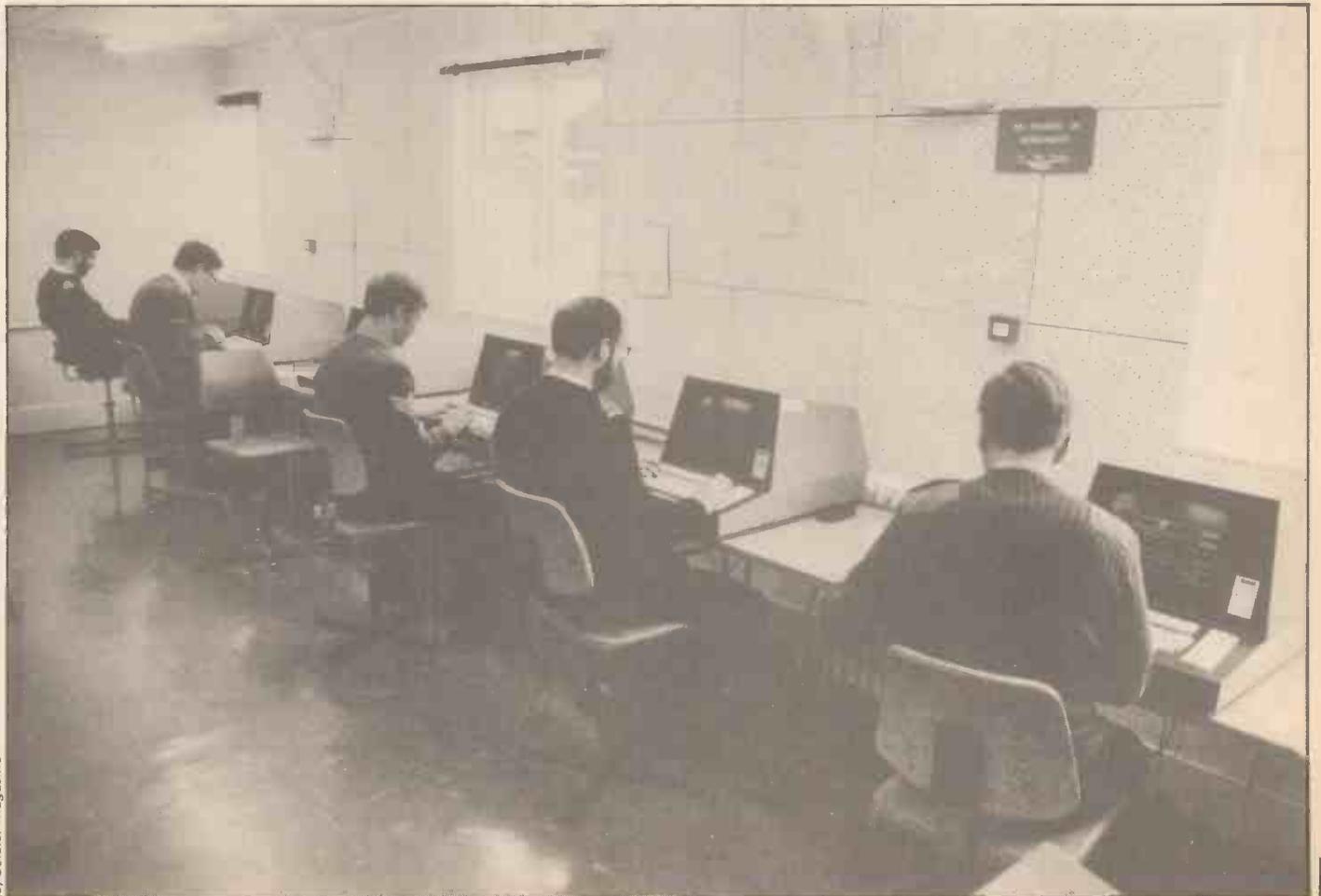A group of Army and Navy trainees taking a computing test at a Data Processing Centre.



(c) Soldier Magazine

## Careers In Electronics

This is very much the course for some one who wants to make a long-term career in the Army, as studies are directed towards the Army's needs from the start, which gives a head start in Army practice.

At some stage in his studies, the officer will begin to work towards one of the three areas — Mechanical, Aeronautical or Electronic Engineering, as described earlier on — which he has chosen to specialise in. Again, the Army has final say in which area you specialise, with the intention of using your abilities to their best advantage.

For Short Service Commissions the routes are very similar. The early undergraduate can apply for an Army Undergraduate Bursary to supplement his local authority grant. Short Service Commissioned officers can also be accepted with an HNC or ONC in Engineering with 60% in maths and two other relevant subjects, or an HNC or Full Technological Certificate in a relevant subject. You can convert to a Regular Commission after a year's active service in REME, but must then study for a degree.

### Field Experience

After degree and postgraduate study, REME officers are sent on a posting as commanding officer on a Light Aid Detachment, a small unit looking after the equipment and vehicles of another division, and responsible to the commanding officer of that division. This is active service experience, giving the officer actual responsibility for commanding a group of men and making certain that the equipment in his charge is fully operational whenever it is needed. In peacetime, this may be the only 'field' experience an engineering officer has, and it is important in that it gives him the experience of organising and motivating a group of men working as near to combat conditions as possible without a war. This is a different proposition entirely from the experience of most civilian engineers: out of doors, in all weather conditions, at short notice, and with expensive and delicate equipment which is expected to work first time, or — in real combat conditions, or even under exercise conditions — cost lives.

The Officer's progress in REME after this will tend to take him to workshops, HQs, research establishments and civilian manufacturers rather than to the front line.

The story is a bit different for a Royal Signals officer, where the work is less theoretical and academic, and more practical. Signals officers do not have to be graduates, and — although they must have a thorough understanding of the equipment they are working with — have less 'hands on' involvement with the insides of equipment. Their business is to keep communications gear connected up, and keep the signals going through, and the officers are



(c) Soldier Magazine

Connecting a Telebrief (ground communications) line to a Harrier in the field.

primarily involved in planning and supervision. The Signals are very much a front line corps, and operate right up to the forward edge of the Battle Area.

Young Signals officers undergo a five-month Communications Qualifying Course at the School of Signals at Blandford. The technical syllabus covers radio and electronics, computers, microprocessors, and audio systems and microwaves, as well as all kinds of transmission techniques and radio and data processing equipment. Instruction is as practical as possible. The course also covers military studies, including tactics, command and control, leadership and equipment management.

From here, the trainee will go to his (or her) squadron or regiment as a working officer. During this time there may be the opportunity to study for a degree, or a Telecommunications Engineering Management course (graduates and a few non-graduates), which will lead to eligibility for possible membership of the IEE (Institute of Electrical Engineers — the main professional body for electrical and electronics engineers). Careers opportunities after this include advancement through the regimental or administrative (Staff) sides of the Army, or a combination.

The basic qualification for a Signals officer is an 'O' level in Maths, English language, a Science subject and two other subjects, but the competition is such that better qualifications are usually needed; however, the Army itself will often put candidates through and extra 'O' and 'A' levels if it thinks they have other qualities which are worth developing.

It is possible to opt for the Army while still at school at a minimum age of 15 years 5 months, by applying for an Army Scholarship. Because of the range of non-combat jobs involved, the Signals is the best Corps to investigate if you are a female with technical aspirations.

There are some general qualifications for entry into the Armed Services which I will mention at the end of the feature — they are mostly to do with nationality. All Army officer candidates have to undergo around three days of leadership and character tests at the Regular Commissions Board at Westbury, and their course from there will be determined by several factors including age, educational and professional attainments, and personal interests and ambitions. Promotion for officers goes in steps determined in part by the officer's age and his length of service, the level he can achieve being determined by merit and the Army's requirement at any given time.


Interested? There is a lot more to find out than the outline I have given here: the first step is to get in touch with an Army careers office, pick up as much paperwork as you can, and ask questions. Then, ask about visiting an Army establishment of the corps you are attracted to, or more than one. Recruitment offices can be found in the telephone directory, or write to one of the addresses given at the foot of the article, asking for brochures and the address of local careers offices.

*Careers In Electronics continues next month with the Royal Navy.*


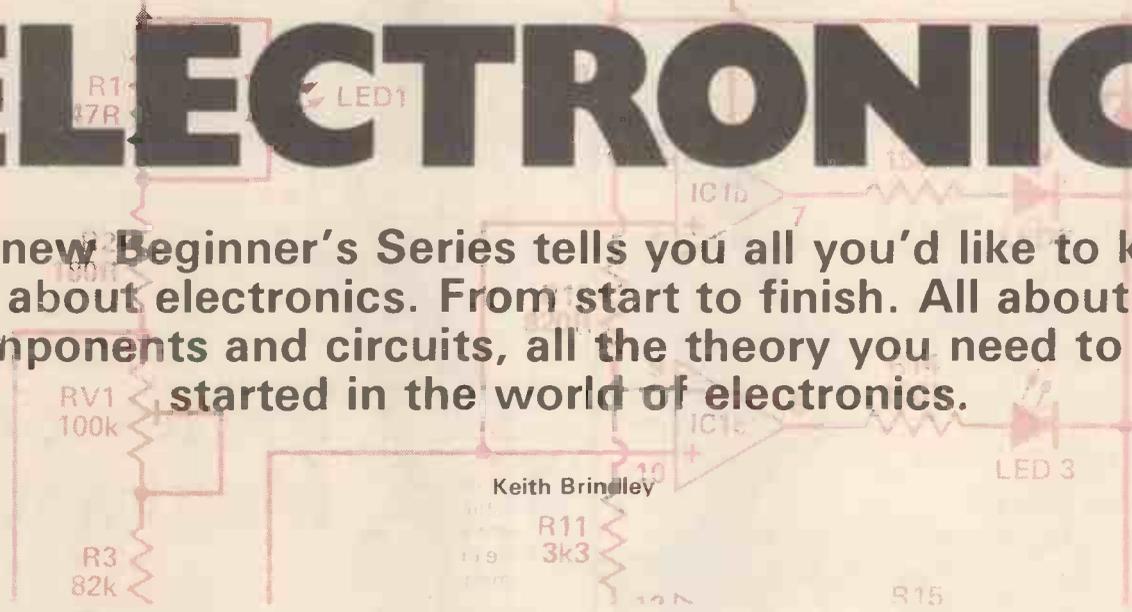
# ALL ABOUT ELECTRONICS

Our new **Beginner's Series** tells you all you'd like to know about electronics. From start to finish. All about components and circuits, all the theory you need to get started in the world of electronics.



IN THIS MONTH'S All About Electronics we are going to take a close look at one of the most important types of linear ICs — the operational amplifier, normally abbreviated to op amp. From now on I will refer to op amps.

Op amps are just what their name implies — amplifiers which can be used (ie, are operational) with only a minimum of extra components. This is not to say that the circuitry inside an op amp is simple. We can, in fact, think of an op amp in block diagram form, an example of such is shown in Figure 1. Here the block diagram shows an amplifier with a voltage gain of ten. This means that whatever voltage is applied to the amplifier input will be increased tenfold ie, if a voltage of 1VDC is applied at the input, 10VDC will be obtained at the output.

Usually, when anyone discusses op amps in modern day terms, the op amp takes the form of an integrated circuit (IC). In days gone past this was not the case and discrete transistors, even valves, were combined together into a complete op amp circuit. The use of ICs simplifies circuit design, and enhances the use of block diagrams in electronics, because the designer no longer needs to think along the lines of complex circuits with components galore but can design quite versatile circuits with only a handful of components.

Probably the most common IC-type op amp is the 741. In its most used form the 741 is an 8-pin DIL IC. The internal circuit of a 741 is shown in Figure 2 and you can see the IC has far more to it than would at first appear. I counted twenty transistors in the circuit so it is obviously quite a complex device. However, its very complexity also makes it extremely versatile.

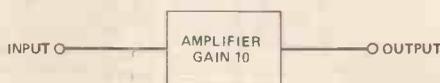


Figure 1. An amplifier shown in block diagram form, with the gain (in this case, x 10) specified.

## Mix And Match


Simply by adding components, say a couple of resistors or capacitors etc., to an op amp can result in very different characteristics, although in essence all that an op amp can do is amplify whatever is at the input. Let's look a bit closer. The circuit symbol for an op amp

is shown in Figure 3. It has two inputs (labelled + and -) and an output. Electric power to operate the amplifier is supplied to the terminals V+ and V-. Note that a 3-rail power supply is used to provide three voltages: V+, 0V, V-.

An op amp is termed more correctly a differential amplifier, ie it will amplify the difference in voltage between the two input terminals. The gain of an op amp connected as in Figure 3 is very, very high (say 10,000).

Now, if the - input (known as the inverting input) is tied to 0V, the amplifier works such that if the voltage applied to the + input (the non-inverting input) is higher than 0V (ie, it is of a positive potential), then the output is also higher than 0V. Likewise, if the

Figure 2. The internal circuit of a 741 op amp.

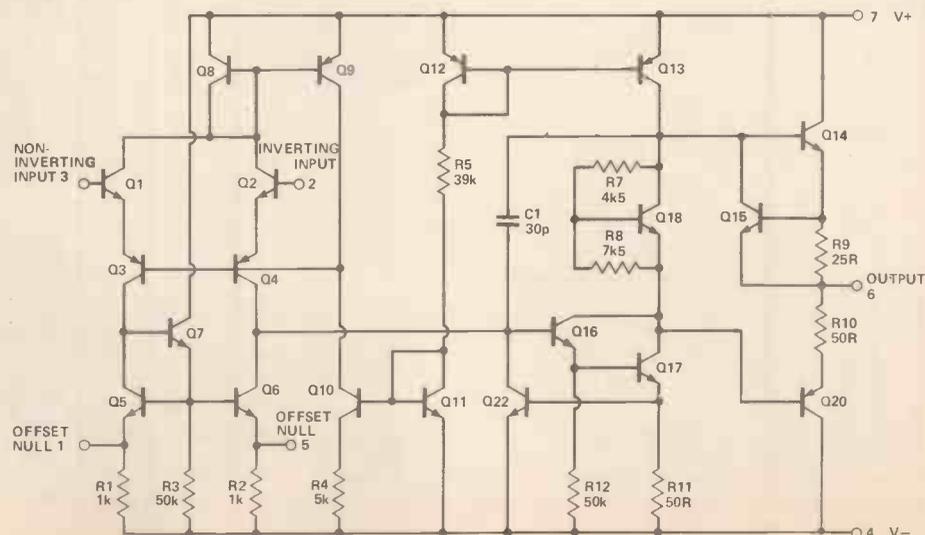

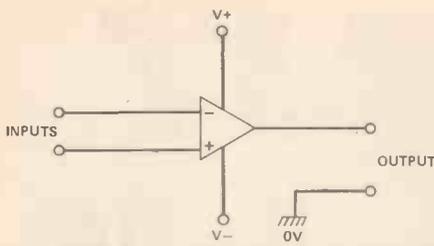


Figure 3. Op amp circuit symbol.

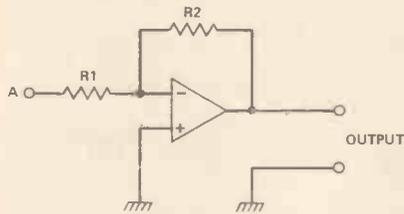


Figure 4. An inverting op amp shown with negative feedback.

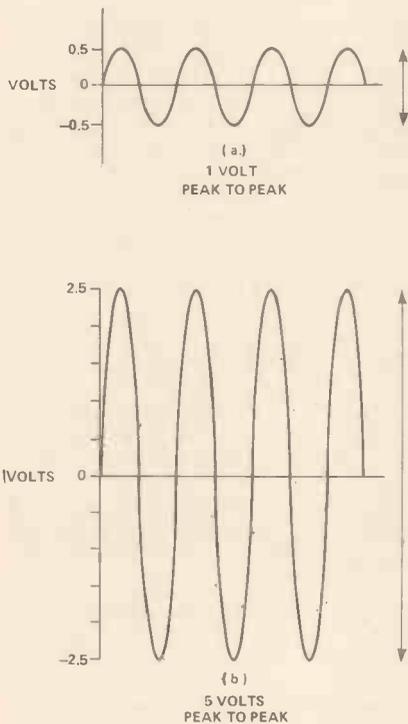


Figure 5. AC input and output voltages to and from an op amp with a gain of five.

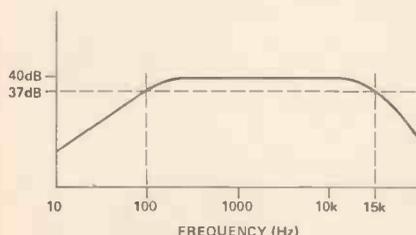


Figure 6. The frequency response of an amplifier with a bandwidth of 100Hz to 15kHz.

non-inverting input voltage is below (ie, negative), the output voltage is negative. It is because of this basic action that the non-inverting input is actually called the non-inverting input.

Similarly, if the non-inverting input is tied to 0V, the inverting action of the op amp is displayed. So, if the voltage applied to the inverting input is above 0V (ie, positive), the output voltage is negative and, if the input voltage is negative the output voltage is positive.

Of course if the gain of the op amp is very high, only a tiny differential input voltage is needed to produce a large output voltage. Although this may be suitable in some instances, the majority of applications will require a much lower gain, say ten, or two etc. We can compare the gain of an op amp in the circuit of Figure 3 with a transistor gain  $\beta$ , back in All About Electronics in the HE November 83. If you remember, Figure 20 of that month shows a transistor amplifier which used a technique known as feedback to control the gain of the common emitter transistor circuit, to a readily definable value. The gain of the circuit simply came down to the ratio between two resistors and by changing one or both of the resistor values the common emitter amplifier gain changed.

Op amp circuits use a similar feedback technique, but with op amps the application is far more apparent than in a transistor circuit. A portion of the output is literally fed back to an input. Because we wish to decrease the value of gain the input chosen to feed back to is the inverting input. The process is called negative feedback. If positive feedback was chosen, ie from the output to the non-inverting input, gain would effectively increase and become uncontrollable, although it can be tamed and then used quite effectively as a later example will show.

### Negative And Positive

Generally speaking, negative feedback is executed with the use of a component connected between output and inverting input, generally passive (but not always). The simplest passive component is the resistor and it is a resistor to which we shall now turn to demonstrate the action of an op amp in a negative feedback circuit.

Figure 4 shows an op amp with a feedback resistor, R2, from output to inverting input. Also shown however, is a resistor connecting the input voltage applied to the circuit to the inverting terminal. This resistor is known as the input resistor, R1. Now it can be proved with some quite complex mathematics that the gain of the circuit equals:

$$\frac{V_{out}}{V_{in}} = -\frac{R2}{R1}$$

The minus sign indicates the amplifier is an inverting amplifier. So, we can control the gain of the amplifier by altering one or both resistor values. For example, if a gain of say, 5, was required

then we could choose resistor values of 10k for R2 and 2k for R1. Or 50k for R2 and 10k for R1. Or 80k for R2 and 16k for R1 etc.

If we now applied a DC voltage of say 1V to point A in the circuit, we would obtain a DC voltage of -5 volts at the output. Similarly, if we applied an AC voltage of 1V peak-to-peak as in Figure 5a to point A, we would get an output of 5V peak-to-peak but inverted in phase by 180° compared with the input (Figure 5b).

From this brief description of op amps you might assume that this would be true whatever frequency is used as the AC input signal voltage. This is not, however, the case because any op amp has what is known as the gain-bandwidth product. I'll explain gain-bandwidth product shortly, but first we need to understand bandwidth.

Now the bandwidth of an amplifier (any amplifier) is defined as the frequency range over which the gain is almost constant — or more correctly speaking it is the frequency range over which the gain does not change by more than a factor of 2 ie, 1.414 times or  $1/1.414 = 0.7$  times the chosen gain.

### A Gain And A Gain

Gain of an op amp (in fact any linear circuit's gain) is often expressed as a ratio of output to input voltages. In electronic terms, the gain can be expressed as a particular number of decibels (dB) where it has been calculated as

$$20 \log_{10} \frac{V_{out}}{V_{in}} \text{ (dB)}$$

So, a numerical gain of 100 is equivalent to a gain of 40dB; a numerical gain of 10 is equivalent to a gain of 20dB; a numerical gain of 1 is equivalent to a gain of 0dB; a numerical gain of 1.414 is equivalent to a gain of 3dB; a numerical gain of 0.7 is equivalent to a gain of -3dB.

So, as the bandwidth of an amplifier is defined as the frequency range over which the gain does not vary by more than 1.414 or 0.7 this automatically means that the gain does not change by more than  $\pm 3$ dB. The bandwidth of an amplifier can be expressed as a frequency range and can be shown on a graph (Figure 6). The X-axis of the graph in Figure 6 shows frequency (in Hertz) on a logarithmic scale but the Y-axis shows gain (in dB) on a linear scale — but the dB is a logarithmic measure of gain anyway. Over the central part of the frequency range amplifier gain is shown as being almost constant at 40dB (ie, a numerical gain of 100). The upper and lower frequencies, where the gain has fallen by 3dB, to 37dB (ie, 15kHz and 100Hz) are known as the corner frequencies, or the 3dB points. These terms are commonly used in electronics so it's worth remembering them, and what they mean.

Now, the gain-bandwidth product of

any op amp is a constant. For the 741 type op amp, the gain-bandwidth product is 1MHz. Thus for an op amp circuit using a 741 IC, if the gain is 100 (ie, 40dB) the maximum bandwidth will be 0Hz to 10KHz.

If the gain is increased by a factor of, say 5, the maximum bandwidth will correspondingly decrease by a factor of 5 (to 0Hz/2KHz). The fact that the figures quoted here for the bandwidth of a 741 op amp go down to 0Hz signify that the 741 can be used to amplify DC input voltages. In certain instances, however, it may be required that a bandwidth having a lower-corner frequency above 0Hz is used. There are ways to do this and we'll see an example later.

## Frequency Response

Gain-bandwidth product of an op amp can be represented as a graph of frequency response (Figure 7) showing how the bandwidth varies with the gain. Figure 7 shows how the bandwidth varies with gain for a 741 op amp and here you can see the effect. If you take a gain of say 40dB, the bandwidth is 10KHz. By reducing the gain for example to one tenth (to 20dB), the bandwidth increases tenfold to 100 KHz.

One very important point which is also displayed in the graph of Figure 7 is the slope of the gain. This slope has a particular angle of 20 dB/decade. In other words the gain decreases by 20 dB for every tenfold increase in frequency.

Another electronic circuit (using only passive components) can produce the same sort of effect. Being passive, such a circuit (shown in Figure 8) cannot amplify an applied signal, and at best can only allow the signal to pass through without reduction in amplitude. The graph of frequency response of the circuit (Figure 9) therefore shows this as a maximum 'gain' of 0 dB ie, a gain of 1, or 'unity gain'.

At the corner frequency the signal amplitude is 3dB down (ie, -3dB) and above this the signal amplitude reduces at a rate of 20dB/decade. Therefore in terms of physical appearance the frequency response is identical to that in Figure 7, only the gain of the circuit is different.

This simple resistor/capacitor circuit is often called a low-pass filter because it passes frequencies lower than the corner frequency and filters out frequencies above the corner frequency. As you would expect, the corner frequency of a resistor/capacitor low pass depends on the values of the resistors and the capacitor used. A simple formula can be used to calculate it:

$$\frac{1}{2\pi RC}$$

and so the resistor and capacitor values shown give a corner frequency of 15KHz.

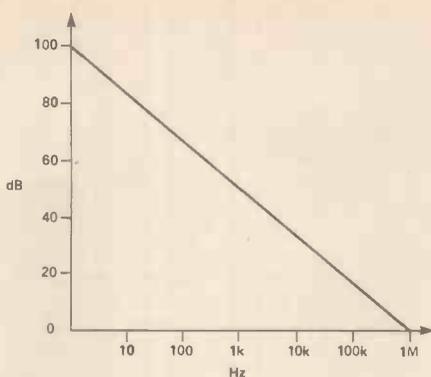


Figure 7. Open loop frequency response of a 741 op amp.

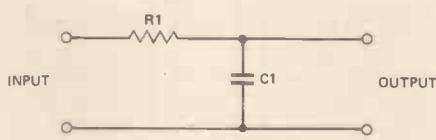


Figure 8. A low pass filter circuit using a resistor and a capacitor.

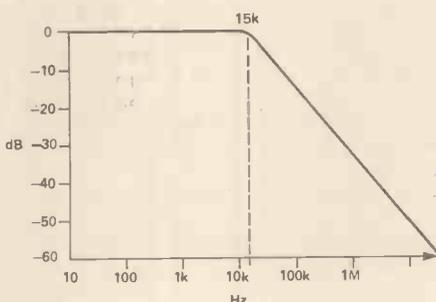


Figure 9. The frequency response of a low pass filter with a corner frequency of 15KHz.

## I Pass

Just as there is such a thing as a low-pass filter, so there is a high-pass filter which allows frequencies above a corner frequency to pass through but filters out frequencies below. The graph of frequency response of such a filter is shown in Figure 10, the circuit of a simple resistor/capacitor network which exhibits this response is shown in Figure 11. The very same formula  $1/2\pi RC$  is used to calculate the corner frequency — so the values shown give a corner frequency of 100Hz.

This circuit should give you a clue to how the frequency response shown in Figure 6 can be obtained. If we simply cascade a low-pass filter and a high-pass filter, ie place one after the other, then an upper and a lower corner frequency will occur above and below which frequencies will be filtered out. But between these two corner frequencies the signal will be passed. Figure 12 shows this using the two

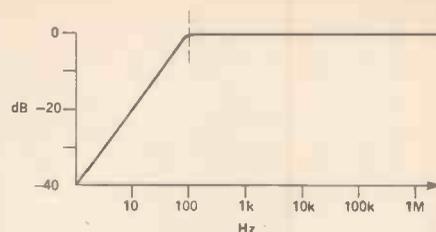


Figure 10. The frequency response of a high pass filter with a corner frequency of 100KHz.

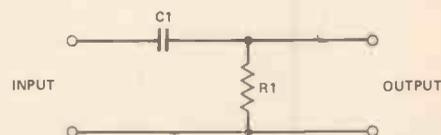


Figure 11. High pass filter using a capacitor and a resistor.

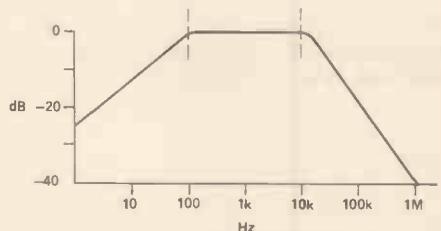


Figure 12. The frequency response of cascaded high pass and low pass filters with corner frequencies of 100 and 15KHz.

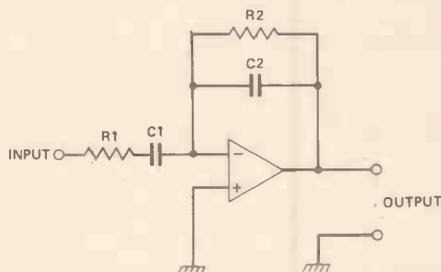


Figure 13. An amplifier bandwidth defined by an op amp with high and low pass filters.

corner frequencies of Figure 9 and 10, but this still has no greater gain than unity over the bandwidth of the response.

To add to the required gain we could simply now include an op amp with a fixed gain into the circuit, that the three networks: amplifier, low-pass filter, high-pass filter are cascaded one after the other. However, a much more elegant way to form a circuit which provides the frequency response of Figure 6 is to use the effect of negative feedback which we already use to control the very gain of the op amp.

Consider Figure 13. The values of R1 and C1 are chosen so that their corner frequency is 100Hz. Above this frequency the signal passes through to the amplifier, but frequencies below are filtered out. The values of R2 and C2 give a corner frequency of 15KHz. Above this frequency more feedback occurs and so the amplifier gain goes down. Thus the combination of the low-

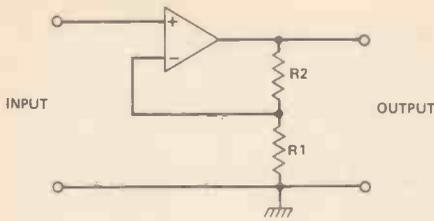


Figure 14. A non-inverting amplifier using an op amp with negative feedback.

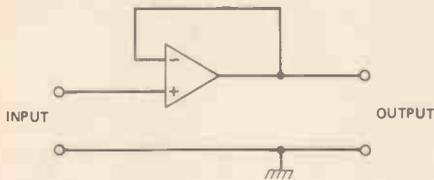


Figure 15. A unity gain buffer using a non-inverting op amp with full negative feedback.

pass and high-pass filters into the feedback circuit of an op amp provide the overall circuit which as the bandwidth we require.

So far we have only studied the op amp in inverting mode. Let's now look at the non-inverting mode. Figure 14 shows the basic non-inverting circuit. Resistors R1 and R2 form the feedback components, (this in essence is a resistive potential divider); the output of which, at the junction between the resistors is fed back to the inverting input of the op amp. Amplifier gain in this mode is calculated from the formula

$$1 + \frac{R2}{R1}$$

From this, you will see that the op amp gain in the non-inverting mode cannot be less than unity — even if the resistor R2 is zero.

### Let's Have Unity

In fact, many applications call for a unity gain amplifier and this mode is often used (Figure 15) as a unity gain buffer. Configured as in Figure 15 an op amp has a very high input impedance and so possesses excellent qualities to be a buffer ie, it does not load a previous circuit. Buffers and loading were explained in last month's All About Electronics.

The same principles we saw with op amps in inverting mode can be used with op amps in non-inverting mode to define their bandwidth.

So, to summarise what we have seen so far: an op amp is simply an amplifier which — with the minimum of external components — can be made functional. It can amplify a wide range of input signals (from 0Hz to many kilohertz) so that the output is either inverted or non-

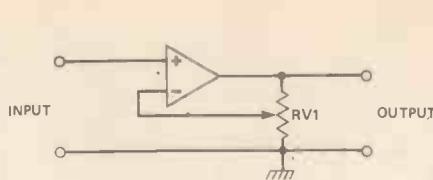


Figure 16. A non-inverting amplifier with variable gain.

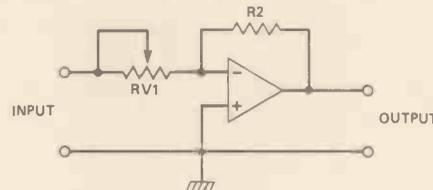


Figure 17. An inverting amplifier with variable gain.

inverted. We can control the level of gain in either inverting or non-inverting mode simply by altering the ratio of two resistors. This is all made possible using the principles of negative feedback.

Now, let's look at some examples of the applications of what we have just summarised. By making one or more of the components in the feedback divider variable the gain of the op amp circuit can be correspondingly varied. Figure 16 shows a non-inverting amplifier with a pot, acting as the potential divider in the feedback circuit. This circuit will provide a large range of gain values depending on the position of the pot wiper.

Figure 17 shows how a pot as the input resistor of an inverting amplifier can be used to give variable gain. In some instances a three-rail power supply may not be desirable (for example, in battery-powered equipment). In such examples we can use a method whereby we trick the op amp into believing that a three-rail power supply exists. Figure 18 shows how. A resistive potential divider at the input terminal provides an artificial earth point about which the op amp functions. DC blocking capacitors at input and output ensure that all DC conditions are

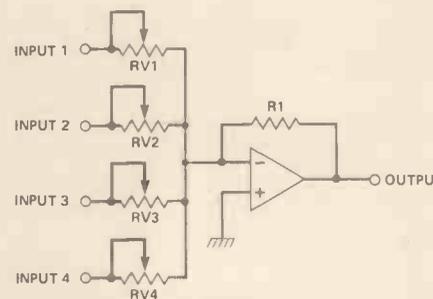


Figure 20. A four channel audio mixer using four potentiometers in the place of four fixed input resistors.

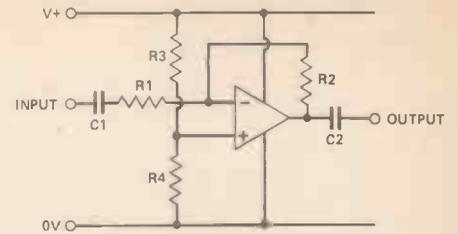


Figure 18. Using an op amp with dual-rail power supply.

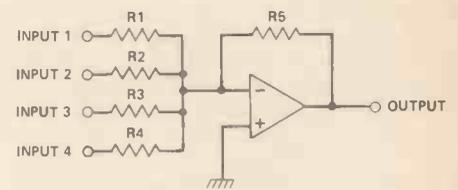


Figure 19. A four input summer amplifier.

maintained while still allowing the AC signal to pass and be amplified. This technique can be used for a non-inverting op amp, too.

A circuit known as a summer is shown in Figure 19. It is shown with no less than four inputs (theoretically, it could have any number). Circuit output is simply an addition of each input multiplied by the amplifier gain — hence the name.

Gain of each individual input signal is the ratio of R5 and that input channel's resistance, so we can very easily turn this into a four channel audio mixer by using pots instead of fixed input resistors (Figure 20). Such a circuit may be used as the basis of a mixer to combine four audio signals before recording the required mix onto, say, a tape recorder.

### Meter Circuit

An op amp can form the basis of a sensitive electronic meter circuit. Because of its high impedance input buffering action, the measured circuit is

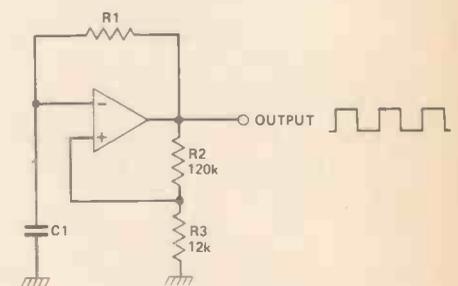


Figure 22. A squarewave generator using an op amp with negative and positive feedback.


## ■ All About Electronics

Figure 21. A 1uA high impedance meter using a 100uA meter movement.

not loaded in any way so the reading will be accurate. Figure 21 for example shows a 741 in an inverting amplifier mode with a gain of 100. The meter mechanism used is a 100-0-100 uA mechanism. Full-scale-deflection of the meter (100 uA or -100 uA) is obtained when a current of 1 uA (or -1 uA) is passed through the input resistor.

One point to note in this circuit which we have not seen before, is pot RV2. This is labelled 'set zero' and is used to make sure the pointer of the meter does actually point to zero when no current is begin measured. This pot is commonly known in op amp circuits as the offset null control and is used to cancel out the output offset which may occur due to minute voltage offset changes at the input. These will vary with temperatures so readjustment will be needed periodically. Use of such an offset null pot is normally only required in circuits with high gain and where high accuracy is demanded.

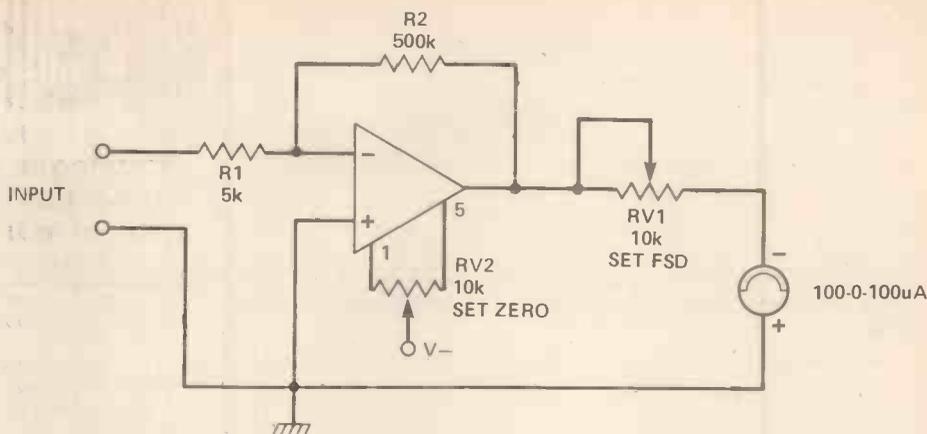Finally, the circuit of Figure 22 (see page 55) uses the principle of positive feedback coupled with usual negtive feedback to produce an oscillator giving a square wave output rather like that of



an astable. Oscillation frequency is dependent on resistor R1 and capacitor C1.

The op amp we have used so far to illustrate all of the applications and principles of op amps is the 741. It just so happens that the 741 is probably the most common op amp available. It is certainly one of the cheapest — a glance through the mail order company advertisements in this issue of Hobby Electronics will show you that a 741 can be bought for as little as 20p. This is a

wonderously small price for such a complex and versatile device and it goes a long way to show why the 741 is the most common op amp.

Other op amps exist, however, for a variety of prices and also a variety of performances. The 741 is a general purpose device and because of its gain-bandwidth product cannot be used for much more than simple audio amplifiers and the like. The principles of all other op amps however, are the same as those we have studied.

HE

# IT LIVES AGAIN!

From the past it came, growing daily, striking terror into the hearts of lesser publications, and spreading its influence across the country in its quest to infiltrate every town, every home, every mind.

Not a horror story, but a success story. And if electronics theory strikes terror into you, then you need the help of **Electronics — It's Easy**. Originally a long-running series in Electronics Today International, **Electronics — It's Easy** was printed as a set of three books. They sold out. It was reprinted as a single volume. It sold out. Now this phenomenally successful publication is available again, in its third reprint. **Electronics — It's Easy** is a comprehensive and simply written guide which explains the theory (and the practice) of electronics step by step. Every aspect of the subject is covered, starting with the basic principles and working through to the how and why of today's technology.

You can obtain your copy of **Electronics — It's Easy** by mail order using the coupon below. Make cheques or postal orders payable to ASP Ltd, alternatively you may pay by Access or Barclaycard.

Send to: Sales Office (Specials),  
513 London Road, Thornton Heath  
Surrey CR4 6AR

Please send me . . . . . copies of **Electronics — It's Easy**. I have enclosed £ . . . . . (£4.95 each including p&p).

NAME . . . . .

ADDRESS . . . . .

Please debit my account

My Access/ Barclaycard No. is . . . . .

Signature . . . . .



## PARNDON ELECTRONICS LTD.

Dept. 22, 44 Paddock Mead, Harlow, Essex. CM18 7RR. Tel: 0279 32700

### RESISTORS: ¼ Watt Carbon Film E24 range ± 5% tolerance

Bandoliered and colour coded. Full Range 1R0-10M.

£1.00 per hundred mixed (Min 10 per value) £8.50 per thousand mixed (Min 50 per value)  
Special stock pack 60 values. 10 of each £5.50

### RECTIFIERS

1 Amp 3 Amp		
50V	3p	14p
100V	4p	14p
200V	5p	14p
400V	6p	19p
600V	8p	20p
1000V	9p	25p

### 3½ Digit LCD Display: 1 colon, 3 decimal points

plus/minus sign and lo bat indicator.

Complete with low power 7106 A/D converter display driver.

Driver set £8.95

Display £3.50 Driver £6.50

### DIODES: IN4148 £1.60 per hundred

### DIL SOCKETS

8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p  
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

### Full List Available — Send SAE

ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS  
MIN ORDER — UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE  
Same Day Despatch

## WHY WRITE TO LONDON

When you can walk to the Midlands largest selection of DIY.

Plugs, sockets, connectors, cable, flex, leads, boxes, Aerials, styli, components, elements, semi-conductors, meters.

In fact the lot!

Spares and repairs for all electronic, electrical and audio.

### H. G. Electronics Co.

1350 Stratford Road, Hall Green,  
Birmingham B28 9EH  
Telephone: 021-777 2369

## Send for my CATALOGUE ONLY 75p

(plus 25p post/packing)

My all-inclusive prices quoted in the Catalogue are the lowest. All below normal trade price — some at only one tenth of manufacturers quantity trade.

Millions of components : thousands of different lines

Rechargeable Nickel Cadmium batteries (ex unused equipment)  
AA(HP7) 1.25volt 500ma. Set of four £2  
Plastic container of ten £5

Watch/Calculator/Lighter etc, Mercury batteries

RW52(PX675) RW54 Made by Ray-O-VAC  
RW56 (DH323,WH8) 31p each or  
RW57, RW58 10 for £2.60, 100 for £21

IN4004 or IN4006 Diodes. 300 for £6.48p  
TO5 or TO18 Heatsinks 7½p, 100 for £6.50, 1000 for £55  
Clipover Heatsink for I/C or TO202 device 21 x 18mm

18p or 100 for £16.50 per 1000 for £155  
Heatsink for TO3 or Plastic Power 19p, 100/£17.50, 1000/£165  
Modern Telephone Handset and lead in white, red, blue, grey, yellow,  
green or black £2

BU508A TV line output transistor, 1,500v, 15A, 125watt  
£1.53p or 40 for £40 or 400 for £300

SEND PAYMENT PLUS 16p SAE OR LABEL ONLY

Prices you would not believe before inflation!

## BRIAN J. REED

TRADE COMPONENTS  
ESTABLISHED 26 YEARS

161 St. Johns Hill, Battersea, London SW11 1TQ

Open 11 am till 6.30pm Tues. to Sat. Telephone: 01-223 5016

# An in-depth series in understanding today's world of electronics. From Texas Instruments.

SPECIAL OFFER  
Order three books and get  
any one of the  
"Understanding" series  
FREE.

The Understanding Electronics Series was specially developed and written to give you an in-depth knowledge of this world.

Each book is comprehensive, yet easy to understand. As informative for the electronics buff as for someone who's simply interested in what's going on today.

Together the library will give you the most complete range of titles available. Take advantage of our special offer and choose the book, or books you want from the titles below. You'll find whole new worlds of advanced technology unfolding before you.

**1. Understanding Electronic Control of Energy Systems.** 1st edition. Ref. LCB 6642. Covers motor, generator, power distribution, heating, air conditioning, internal combustion engine, solar and nuclear systems. *Softbound 272 pages. £4.50.*

**2. Understanding Electronic Security Systems.** 1st edition. Ref. LCB 7201. A complete guide covering the basics of hard wired, photosensitive, infrared, ultrasonic and microwave systems and their use in different applications. *Softbound 128 pages. £2.95.*

**3. Understanding Solid State Electronics.** 3rd edition. Ref. LCC 3361. The principles of solid state theory. It explains electrical movement, with intermediate tuition on the applications of solid state devices. *Softbound 282 pages. £4.50.*

**4. Understanding Digital Electronics.** 1st edition. Ref. LCB 3311. Describes digital electronics in easy-to-follow stages. It covers the main families of digital integrated circuits and data processing systems. *Softbound 260 pages. £4.50.*

**5. Understanding Microprocessors.** 1st edition. Ref. LCB 4023. An in-depth look at the magic of the solid state chip. What they are, what they do. Applications of 8-bit and 16-bit microprocessors; and design from idea to hardware. *Softbound 288 pages. £4.50.*

**6. Understanding Computer Science.** 1st edition. Ref. LCB 5471. This book tells you in everyday English how today's computer has been developed, what goes on inside it, and how you tell it what to do. *Softbound 278 pages. £4.50.*

### 7. Understanding Communications Systems.

1st edition. Ref. LCB 452L. An overview of all types of electronic communications systems. *Softbound 282 pages. £4.50.*

**8. Understanding Calculator Maths.** 1st edition. Ref. LCB 3321. Brings together the basic information—formulae, facts, and mathematical tools—you need to "unlock" the real power of the hand-held calculator. *Softbound 230 pages. £4.50.*

**9. Understanding Optronics.** 1st edition. Ref. LCB 5472. Optronics is the application of light and electronics to perform a wide range of useful tasks. From car headlights to missile guidance systems. *Softbound 270 pages. £4.50.*

**10. Understanding Automotive Electronics.** 1st edition. Ref. LCB 5771. Learn how electronics is being applied to automobiles. How the basic mechanical, electrical and electronic functions and the new microprocessors and microcomputers are being applied in innovative ways for vehicle drive train control, motion control and instrumentation. *Softbound 288 pages. £4.50.*

**11. Understanding Telephone Electronics.** 1st edition. Ref. LCB 7141. The powerful, positive thrust of electronics is making the telephone an even more important communication link. Conventional telephone fundamentals, analog and digital electronics, principles, newer digital techniques and hardware implementation are covered in this book. *Softbound 288 pages. £4.50.*

**12. Understanding Electronic Control of Automation Systems.** 1st edition. Ref. LCB 6641. This book is about automation—explains in simple language the subject of electronic control of automation systems, and to help the reader understand the terms, principles, techniques and effort used to automate processes. *Softbound 280 pages. £4.50.*

### How to order

Fill in the coupon below or if someone else has already used it, simply:

1. List reference numbers and quantities required.
  2. Calculate total order value. Add £1.50 for postage and packing.
  3. Send the list, plus your cheque payable to Texas Instruments Ltd, PO Box 50, Market Harborough, Leicestershire.
- Allow 30 days for delivery.

To: Texas Instruments Limited, PO Box 50, Market Harborough, Leics.  
Please send me the following publications:

REFERENCE NO.	QTY.	REFERENCE NO.	QTY.
1.		7.	
2.		8.	
3.		9.	
4.		10.	
5.		11.	
6.		12.	

Free title choice: Understanding \_\_\_\_\_

I enclose a cheque for £ \_\_\_\_\_

Name \_\_\_\_\_

Company, (if any) \_\_\_\_\_

Address \_\_\_\_\_

Please send me details of TI's range of Technical Books (please tick)

Registered office: Texas Instruments Ltd, Manton Lane, Bedford MK41 7PA.  
Registered number: 574102 England. HE1

# TEXAS INSTRUMENTS



# FORWARD BIAS

Questions, answers and errata from readers and writers.

## COLLECTED BOOBS

Continuing excerpts from the Hobby Electronics Errata Box

### Hobbycom (HE April '80)

On Figures 3 and 4, on the Overlay, the labels 'C2' and 'C3' should be swapped. There is a track missing on both the overlay and the main PCB. Wire a link from the positive side of C6 to the junction of C5 and R5.

### Digital Frequency Meter (HE April '80)

On the Parts List, C1 should be 470n carbonate (not ceramic).

### Short Circuits (HE March '80)


On the Sound Operated Switch (p 33) the unmarked resistor above C3 and C4 is R2, 47k. The junction of R6 and R7 is connected to the base of Q3.

On the Thermostat, (p 52) the capacitor C1 is 1000uF. The resistor next to C2 is R3, 1k2 and the capacitor next to that is C3, 2u2.

On the One Armed Bandit (p 72) IC1 pin 11 should go to IC2 pin 1 but should not be connected to OV. IC1 pin 9 should be connected to OV.
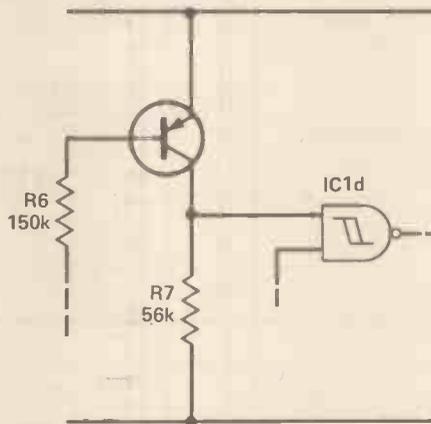
### Miniclocks (HE May '80)

On Figure 5, the circuitry around Q2 is incorrect. It should be:



On Figure 7, the pins of Q1 and Q2 are wrongly labelled. They should read e, c, b from top to bottom.

### The Egg Timer (HE June '80)

On Figure 1, there were several

components missing, also several component values were incorrect. The Parts List gives the correct component values, and the corrected circuit is given here:

In the Parts List, Q1 and 2 must be either BC184 or BC109, and *not* BC184L, as the pins are different on the latter.

### Equitone (HE August '80)

On the Component Overlay, the earth and input connections have been transposed. The top two connections are the input leads.


### Pass The Loop (HE August '80)

On Figure 2, the chip shown as IC3 should be labelled IC2 and vice versa.

### Echo Reverb (HE May '82) Telephone Timer (HE June/July '82)


Both these projects have now been overhauled, and the corrections will be published within the next few issues. Enquiries accompanied by SAEs will be answered shortly, possibly, in fact, before you read this.

### The Egg Timer Circuit

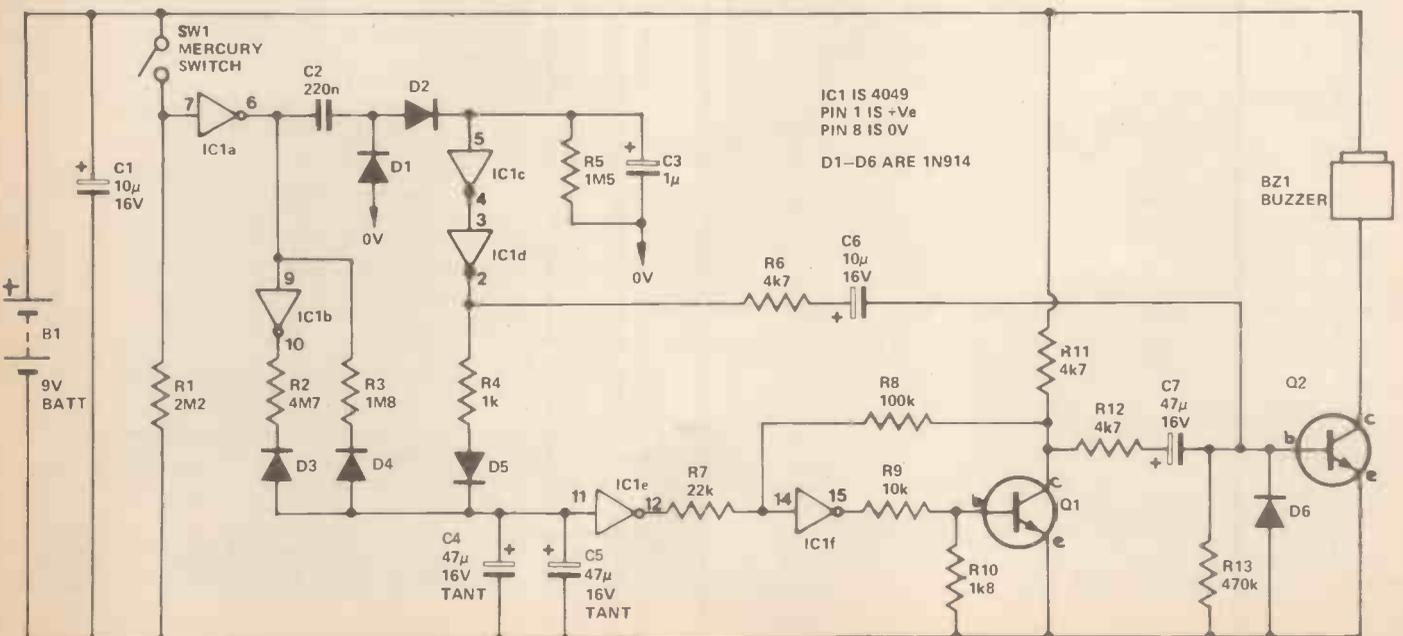

# POWER REDUCER

Andrew Armstrong

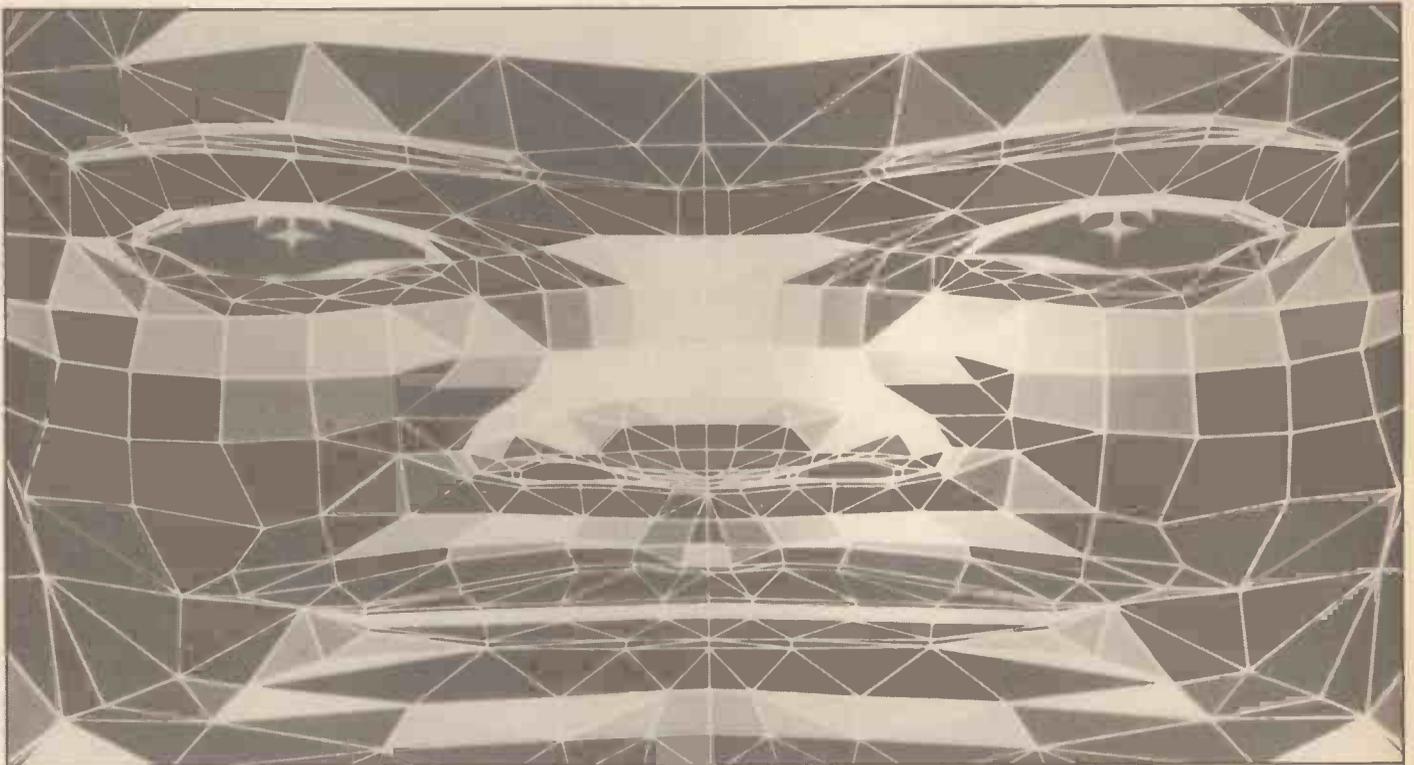

Picture from "Tron" courtesy Walt Disney Productions

Is your 110V/120V gadget being dominated by our 240V mains supply? Cut the power down with this useful project.

## Caution

This project is mains powered: use all caution when testing the device and ensure that all earths are securely connected.

The Power Reducer operates by switching power to a heating coil for only one mains cycle out of four, and so is *not suitable for motor speed*

*control or lamp-dimming applications;* a motor would run very unevenly and a lamp would flicker at the highly noticeable rate of 12.5Hz.

ONE of the lesser known risks of international travel is the possibility of inadvertently picking up an electrical device designed to operate on a foreign mains supply voltage. So when my mother-in-law recently found herself in possession of an American-made coffee perculator, intended to plug into a 110/120 volt supply, she asked me if I could price a suitable transformer for it. I did, and discovered that the transformer would cost £40 — more than the price of the perculator!

Yet this coffee pot has a distinct virtue; it was large enough to satisfy even my thirst for coffee, when we

visit, and I resolved to find a cheaper solution to the problem rather than abandon this paragon of pots.

### I Did It My Way

For a while I considered using something along the lines of a light dimmer (but more powerful) to reduce the power, but two things dissuaded me: first of all the amount of interference radiated by such a powerful phase controller would be a bit anti-social; and second to properly calculate the component values to give the correct power reliably seemed to involve integrating a

function of a function (a painful mathematical manoeuvre I have mercifully forgotten).

The method I finally decided to use is to switch the mains on and off for whole cycles, starting at a zero crossing. The mains voltage in Britain is approximately double the rating of the coffee pot, so if connected straight to the mains it would operate at four times its correct power ( $\text{Power} = V^2/R$ ). Therefore one complete cycle out of four had to be applied to the heating element. The use of a 4039 as a zero crossing detector and a 4013 as a divide-by-four form the heart of a very economical solution.

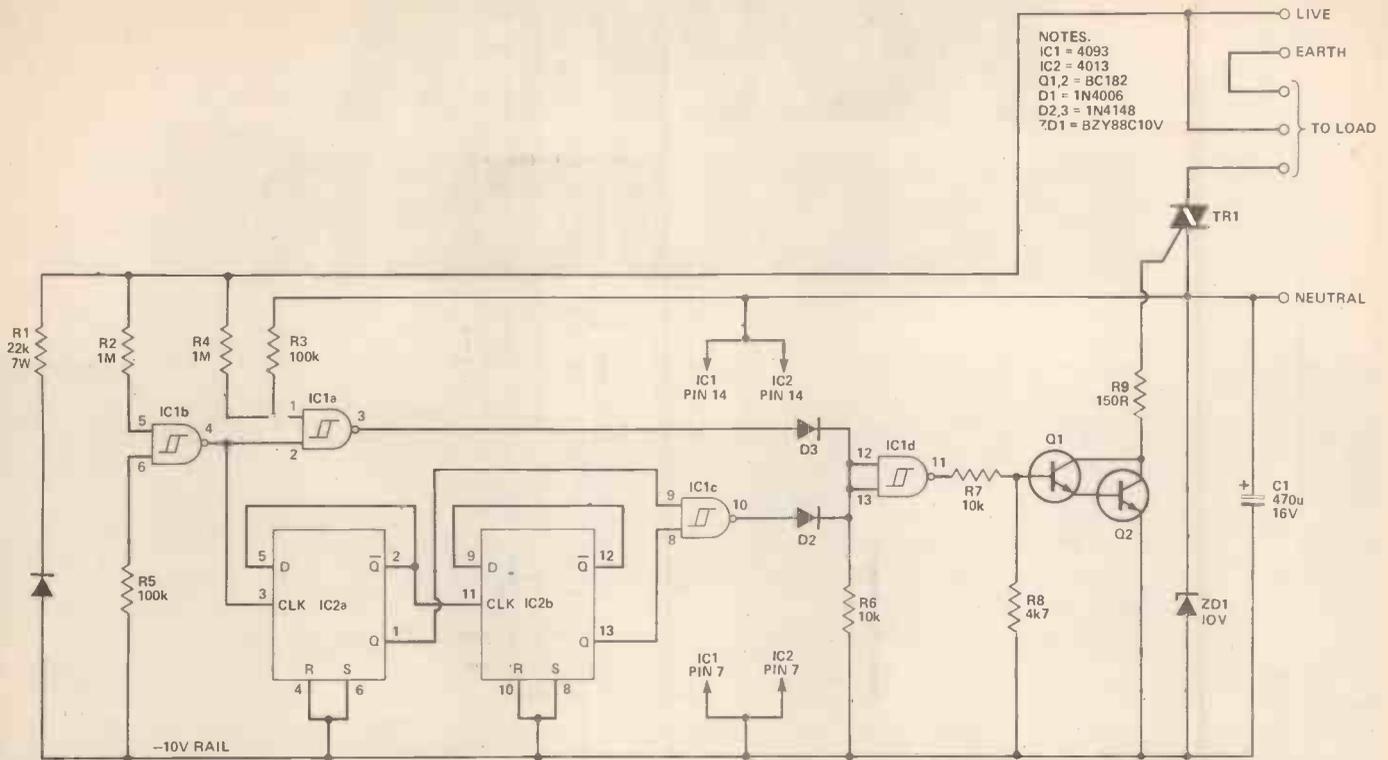


Figure 1. The circuit. The CMOS input protection diodes prevent the inputs from a possible swing to around  $\pm 34V!$

## Design For Power

The design criteria were that the circuit should work without special adjustments, and that the cost of components should be as low as possible, consistent with the first requirement. The obvious requirements of the circuit are:

- 1) something to detect mains zero crossings
- 2) something to count four mains cycles and trigger a triac
- 3) a triac to control the load
- 4) a power supply

Starting with 4, the cheapest power supply can be made using a mains dropper resistor. The fact that the circuit is 'Live' does not matter here as it need not be adjusted once built. Since the other circuit requirements can be carried out with CMOS, the current requirements are low, so I chose the largest conveniently available value to minimise heating. Triacs normally do not trigger reliably with a positive trigger voltage and a negative load voltage (some types are not specified to work under these conditions), so to avoid this problem I chose a negative supply voltage. Nothing in the circuit relies on analogue voltage levels, so bit of ripple on the power supply does not matter; a Zener in parallel with an electrolytic capacitor fulfills this function.

The power dissipated in the resistor can be calculated simply:

$$\text{Power} = \frac{V^2}{R} = \frac{240^2}{22k} = \frac{57600}{22k} = 2.62 \text{ Watts.}$$

Because there is a diode in series

with the resistor, however, this power is applied for only half the time so the power dissipated is 1.31 watts, which is not too serious. The Zener diode ZD1 limits the negative peaks of the power to  $-10V$ , and C1 smooths the voltage somewhat. The current available from this supply is slightly more complicated to calculate — but not beyond the wit of man! See the box headed Programmed Power for the procedure.


Going back, now, to the main circuit Schmitt trigger NAND gates IC1a and IC1b form an economical zero-crossing detector. When the mains voltage is positive, both inputs to IC1b are at logic 1 and its output at pin 4 is therefore logic 0; so with pin 2 low,

IC1a at pin 3 can only be logic 1.

Now as the mains swings down towards zero the voltage will fall below the Schmitt threshold, and pin 4 will switch to logic 1. But because the voltage on pin 1, IC1a, is always 10V more positive than the voltage on pins 5 and 6 (because pin 1 is connected between Live and Neutral whereas pins 5 and 6 are between Live and the  $-10V$  supply rail), both inputs to IC1a will momentarily be at logic 1 and its output will go to logic 0. The pin 1 voltage then rapidly falls below the Schmitt threshold so that, with one input low, IC1a switches back to logic 1.

Conversely when the mains voltage is swinging up from the negative

Figure 2. Modifications to the mains cycle made by the Power Reducer.

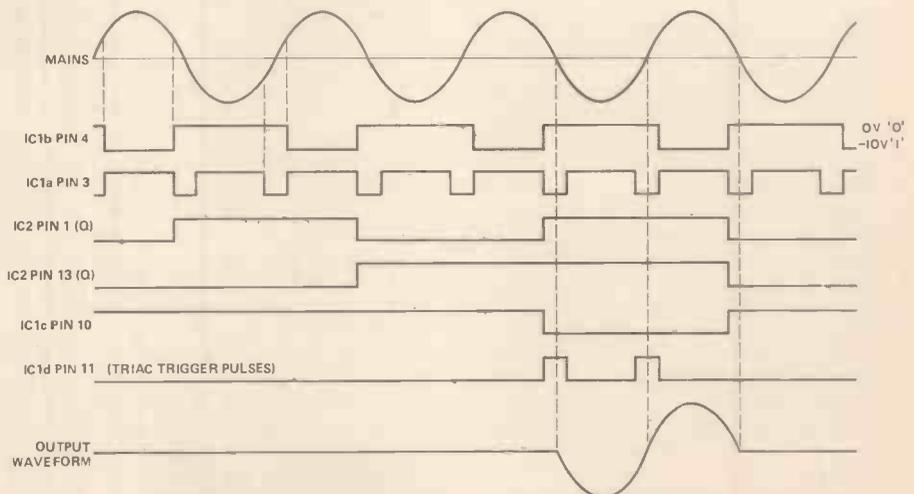

NOTE. SCHMITT TRIGGER GATES ACTUALLY TRIGGER AT DIFFERENT LEVELS, DEPENDING ON WHETHER THE INPUT(S) ARE SWINGING POSITIVE OR NEGATIVE (HYSTERESIS) HOWEVER IN THE INTEREST OF CLARITY THIS DETAIL HAS NOT BEEN SHOWN.

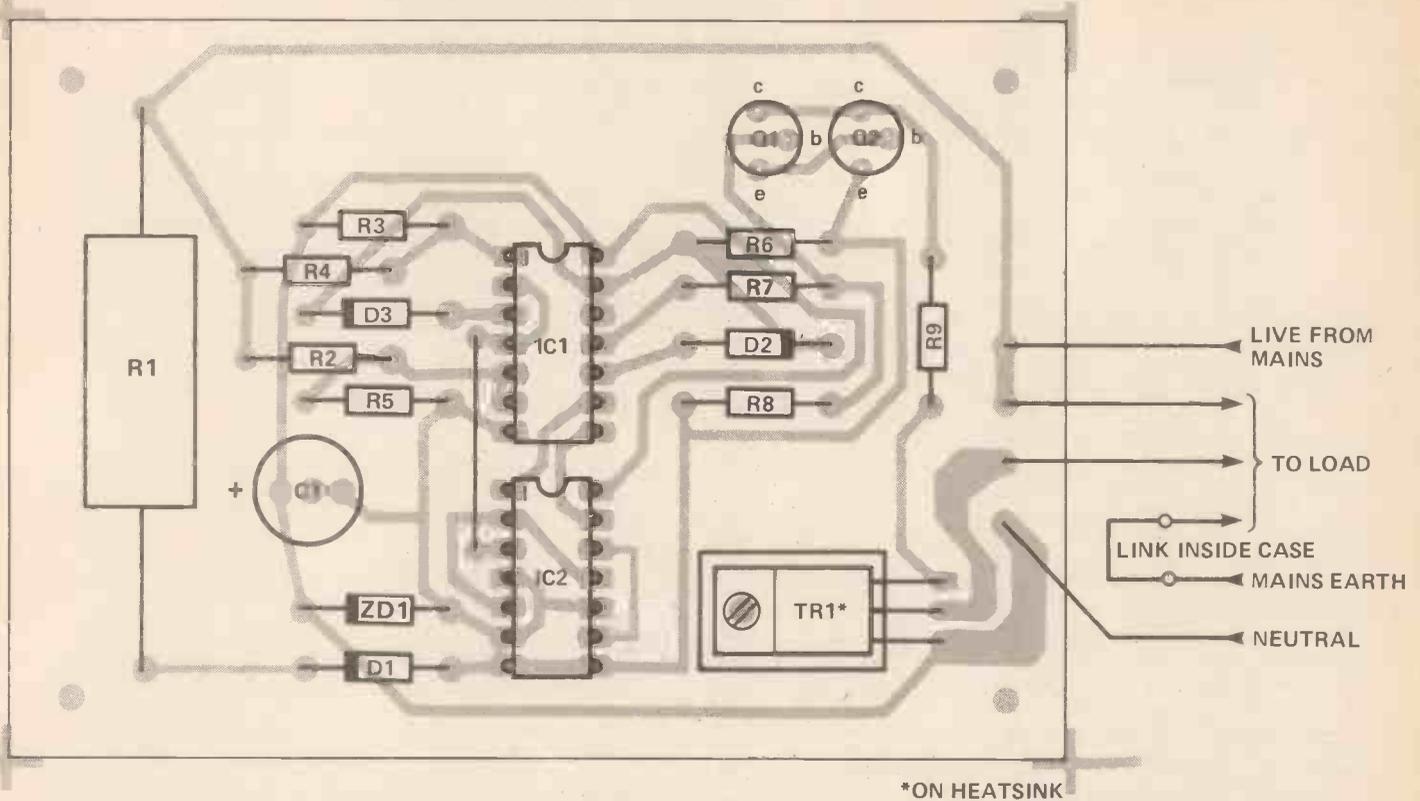


Figure 3. The component layout. Build and test the power supply section first, checking that R1, C2, D1 and ZD1 are the right way round.

peak, the IC1b inputs are both low so pin 4 is high; pin 1, still 10V more positive, will pass through the threshold before pins 5 and 6 so with both inputs momentarily high, IC1a output will go low. Soon after IC1b switches low, restoring IC1a logic 1 output.

The net effect of this action is to generate brief low-going pulses at the output of IC1a, which straddle the mains zero-crossing point. The first few graphs of Figure 2 illustrate the point.

Meanwhile, back to pin 3 of IC1: this gives a signal which goes positive just before negative-going mains zero crossings, so it can conveniently be used to clock a dual D-type flip-flop, a 4013, which is used to count to four whole mains cycles.

The use of a D-type flip-flop as a counter is reasonably common practice and is shown in the timing diagram. Very briefly, on a positive clock edge the Q output takes up the logic state that was on the D input just before the clock edge. If this logic state is fed back from the Q output then the D-type will change state each clock edge.

The Q outputs of the 4013 are decoded by IC1c to give a logic 0 output for one whole mains cycle out of four. This is gated together with the mains zero-crossing signal in IC1d; with the aid of two diodes and a resistor, IC1d performs the function of a NOR gate, so that the transistors can only turn on and trigger the triac when both the aforementioned signals are at logic 0.

This is important, because if the triggering current were to be left on the whole cycle, then the current required would exceed the 4.9mA available! This leads on to another interesting point: when an inadequate power supply is available, CMOS outputs sometimes do silly things. It is quite possible for the 4093 output to switch to logic 1, regardless of what its inputs tell it, if the power supply falls to, say, 2V. If it were possible for the triggering transistors to switch on under these conditions, then the power supply would never reach more than this voltage, and some constructors would be faced with inexplicably non-functioning circuits. Therefore a 4k7 resistor from base to negative supply has been included to prevent the transistors from having any chance of switching on until the logic has enough power to work logically!

Adequate trigger current must be allowed for the triac, too. Assuming that the Darlington pair of transistors switch on so as to drop about 1V, and the triac requires 1V maximum to trigger, then the trigger current is 8V divided by 150R = 53.3mA, adequate for most types of triac.

### Parts List

#### RESISTORS

(All 1/4W 5% unless noted)

R1	22k	7W
R2, 4	1M	
R3, 5	100k	
R6, 7	10k	
R8	4k7	
R9	150R	

#### CAPACITORS

C1	470u	16V radial electro
----	------	--------------------

#### SEMICONDUCTORS

IC1	4093	
-----	------	--

IC2	4013	
Q1, 2	BC182	
D1	IN4006	
D2, 3	IN4148	
ZD1	8ZY88C10V	
TR1	SC142D	

#### MISCELLANEOUS

Plastic case, eg Verobox 3in x 4.5in x 1.25in; small heatsink; four self-adhesive pillars; wire, solder, etc.

BUYLINES ..... page 26

## Power Reducer

Construction of the board may be carried out with reference to the overlay. The power supply should be built first, then tested before other components are added. To do this fit R1, C2, D1 and ZD1 — and carefully check they are the right way round! Then connect a voltmeter across the Zener diode, with the positive end of the voltmeter to the mains neutral side of the Zener. Now plug in and check that the meter reads about 10V. Unplug before touching anything, and if it didn't read correctly check the components. This could avoid an expensive *bang*.

Assuming all was well, complete the construction. It is as well to bolt down the triac before soldering its legs so as not to strain the soldered joint. If the recommended type is used it can be bolted straight away to the heatsink, otherwise insulating washers may be needed.

A plastic case is used to house the unit, with self adhesive plastic pillars to support it (for safety reasons). Self adhesive pillars stick like limpets if the surface is thoroughly clean and grease free, so position them carefully by attaching them to the PCB first. If on the other hand, the surface is not well cleaned they are a pain in the anatomy, so clean the box with washing-up liquid, rinse and dry with kitchen paper before proceeding.

## Testing

The unit should be connected to its load, which can be any heating element — typically a coffee pot or a kettle. For the purposes of the test connect a mains neon or lamp in parallel with the load to indicate proper functioning; the lamp should start to flicker visibly one or two seconds after plugging in. If it comes on at full power then unplug and check that the triac is not shorted out. If it doesn't come on at all, connect a voltmeter to C1, plug in and retest the power supply.


The unit I made caused more than the test lamp to flicker, it was used in a farm house at the end of a long length of supply cable, and every light in the house flickered in sympathy while the coffee percolated!

If the appliance is earthed the earth wires should be connected via and extra insulated terminal block inside the case of the unit. In any event, some thought should be given to the safety of a 120V appliance running on 240V. The coffee pot involved was metallic, but not earthed, but just in case the insulation should ever fail on 240V pulses I added an earth wire.

Once you have taken care of all these points, screw on the lid and the power reducer is finished. Care for a brew?
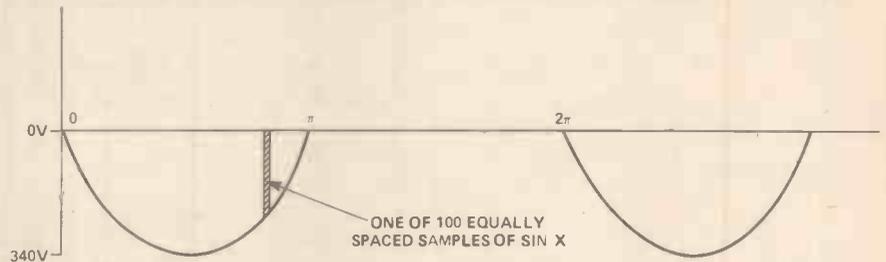
## Programmed Power

The graph below shows the waveform of the voltage on resistor R1 - negative since D1 conducts only on half cycles. At every point on the waveform the current is equal to the instantaneous voltage divided by the resistance (Ohm's Law), but the average current available over the entire waveform is not immediately obvious. It is equal to the area under the curve divided by the resistance and divided by length of the baseline before the cycle repeats itself (in this case  $2\pi$ ). A program can be written to calculate how much current is available, but it does not indicate that it is negative — you know that already!



$$\text{Average current} = \frac{\text{area of curve}}{(\text{total base length})(\text{resistance})} = \frac{\text{Area of curve}}{(2\pi)(22k)}$$

And:

$$\text{Area of curve} \approx \frac{(100 \text{ samples of sin } x)(\text{base length of curve})(\text{height of peak})}{100}$$

Certain of these values are known and are constants in the equation; we can therefore write the constant part:

$$\text{Constant} = \frac{(\text{base length of curve})(\text{height of peak})}{(\text{Total base length})(\text{resistance})} = \frac{340 \cdot \pi}{2\pi \cdot 22k} = 7.72727 \cdot 10^{-3}$$

The program (in ZX81 BASIC) for calculating the average current is:

```

10 LET A = PI/100
20 LET Y = 0
30 FOR N = 1 TO 100
40 LET X = A*N
50 LET B = SIN(X)
60 LET Y = Y + B
70 NEXT N
80 PRINT (Y/100)*7.72727
RUN
4.9189283
    
```

Note that by ignoring the scale factor ( $10^{-3}$ ) in the program we get an answer in milliamps. The more elegant solution is to use calculus to evaluate the area under the curve. The equation is:

$$\frac{340}{(2\pi)(22k)} \int_0^{\pi} -\sin x \, dx = [2.46 \cos x]_0^{\pi} \text{ mA} = 2.46 \cdot -2 = -4.92 \text{ mA}$$

This method also indicates the direction of current flow! The constant part of the equation differs from the program solution because the multiplication by  $\pi$  is included in the integral.

# HE

**Last Month  
at these prices!**

# CB SERVICE

Ready made  
PCBs  
For Readers!

PCB BOARDS (PCBs) for HE projects have often represented an excellent value for money for our readers. Some of you, no doubt, make your own PCBs. Our PCB Service saves you the trouble. You can buy your PCBs direct from HE. All (non-copyright) PCBs will be available to you directly from the HE PCB Service. Each board is produced from the same master as used for the published design and so each will be a true copy, finished to a high standard.

As part from the PCBs for this month's projects, we are making available some of the popular designs from earlier issues. See below for details. *Please note that only boards for projects listed below are available: if it isn't listed we can't supply it.*

<b>December 81</b> HE/8112/1	Pedalboard Organ	£5.64	<b>September 82</b> HE/8209/1&2	Signal lights Main Module	£1.96	<b>May 83</b> HE/8203/1	BBC Interface	£4.82
<b>January 82</b> HE/8201/1	Intelligent NICad Charger	£2.83	HE/8209/3	Junction Module	£1.70	HE/8305/3	Stall Thief	£2.50
<b>February 82</b> HE/8202/1	Relay Driver	£2.07	HE/8209/4	ZX Interface	£3.34	HE/8305/4	Auto-Test	£2.50
HE/8202/2	Mast-Head Amp	£1.08	<b>October 82</b> HE/8210/1	Slot Car Controller	£1.98	<b>June 83</b> HE/8306/1	Sinclair Sound Board	£2.80
<b>March 82</b> HE/8203/1	Digital Dice	£1.40	HE/8210/2	Flash Point Alarm	£2.13	HE/8306/2	CB Rap Latch	£1.65
<b>April 82</b> HE/8204/1	Digital Capacitance Meter	£4.02	HE/8210/3	Negative Voltage Generator	£1.49	HE/8306/3	Bat Light (Car battery monitor)	£2.25
HE/8204/2	Dual Engine Driver	£3.27	HE/8210/3	Squelch Unit	£2.52	HE/8306/4	Traffic Light Toy	£2.56
HE/8204/3	Blke Alarm	£2.45	<b>November 82</b> HE/8211/1	Pedometer/ Odometer	£2.13	<b>July 83</b> HE/8307/1	Soft Fuzz	£2.77
<b>May 82</b> HE/8205/1&2	Digital Thermometer (Set of Two)	£4.62	<b>December 82</b> HE/8212/1	Phase Four	£2.83	<b>August 83</b> HE/8308/1	Whistle Switch	£4.40
HE/8205/3	Echo-Reverb	£5.63	HE/8212/2	Microlog	£3.98	HE/8308/2	Ace Interface	£3.52
HE/8205/4	Cable Tracker	£1.85	HE/8212/3&4	Tape/Slide (Set of Two)	£5.26	HE/8308/3	Enlarger Timer	£2.92
<b>June 82</b> HE/8206/1	Power Supply Design	£2.48	HE/8212/5	TV Amp	£5.70	HE8308/4	Auto-Winder	£2.98
HE/8206/2	Auto-Wah	£3.08	HE/8212/6	Lofty	£2.61	<b>September 83</b> HE 8309 1	Tremoleko	£3.14
HE/8206/3	Auto Greenhouse Sprinkler	£3.45	HE/8212/7	Noise Gate	£3.60	HE 8309 2	SPL Meter	£4.22
HE/8206/4&5	Telephone Timer (Set of Two)	£6.50	HE/8212/8	Low Cost Alarm	£2.30	<b>October 83</b> HE 8310/1	Ultrasonic Alarm	£3.19
<b>July 82</b> HE/8207/1	Tanover	£2.13	<b>January 83</b> HE/8301/1	Chip Probe	£1.82	HE 8310/2	Audio Level Meter	£3.09
HE/8207/2	TVI Filter	£1.78	HE/8301/2	Switched Mode Regulator	£1.96	HE 8310/3	High Voltage Meter	£3.47
HE/8207/3	Computer PSU	£7.68	<b>February 83</b> HE/8302/1	Incremental Timer	£7.13	<b>November 83</b> HE 8311/1	Wiper Delay	£2.80
HE/8207/4	Solar Radio	£1.98	HE/8302/2	DigiTester PSU	£6.70	HE 8311/2	Light Delay	£2.79
<b>August 82</b> HE/8208/1&2	Digital Millivoltmeter (Set of Two)	£4.34	<b>March 83</b> HE/8303/1	Loudspeaker Protector	£2.51	<b>December 83</b> HE 8312/1	Damp Meter	£2.81
HE/8208/3&4	Audio Analyser (Set of Two)	£11.55	HE/8303/2	Overvolt Cutout	£2.25	HE 8312/2	Continuity Tester	£1.21
			<b>April 83</b> HE/8304/1	6502 EPROMMER	£7.18	HE 8312/3	Light Meter	£3.16
			HE/8304/2&3	Ducker		HE 8312/4	Bassman	£2.39
				Main Board	£3.56	<b>January 84</b> HE 8401/01	Power Reducer	£3.21
				Preamp Board	£2.31	HE 8401/02	Lap Counter	£6.09
			HE/8304/4	Power Down	£2.10	HE 8401/03	Quizmaster	£2.81

PLACE an order for your PCBs using the form below (or a piece of plain paper if you prefer not to cut the magazine), then simply wait for your PCBs to drop through your letterbox, protected by a Jiffy bag.

HE PCB Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE

I enclose a cheque/Postal Order made payable to ASP Ltd, for the amount shown below Price.

OR

I wish to pay by Barclaycard. Please charge my account number

VISA

OR

I wish to pay by Access. Please charge to my account number

SIGNATURE

NAME

(BLOCK CAPITALS)

ADDRESS

(BLOCK CAPITALS)

Please allow 21 days for delivery

Boards Required

Price




Add 45p p & p

0.45

Total Enclosed

£

# PCB FOIL PATTERNS

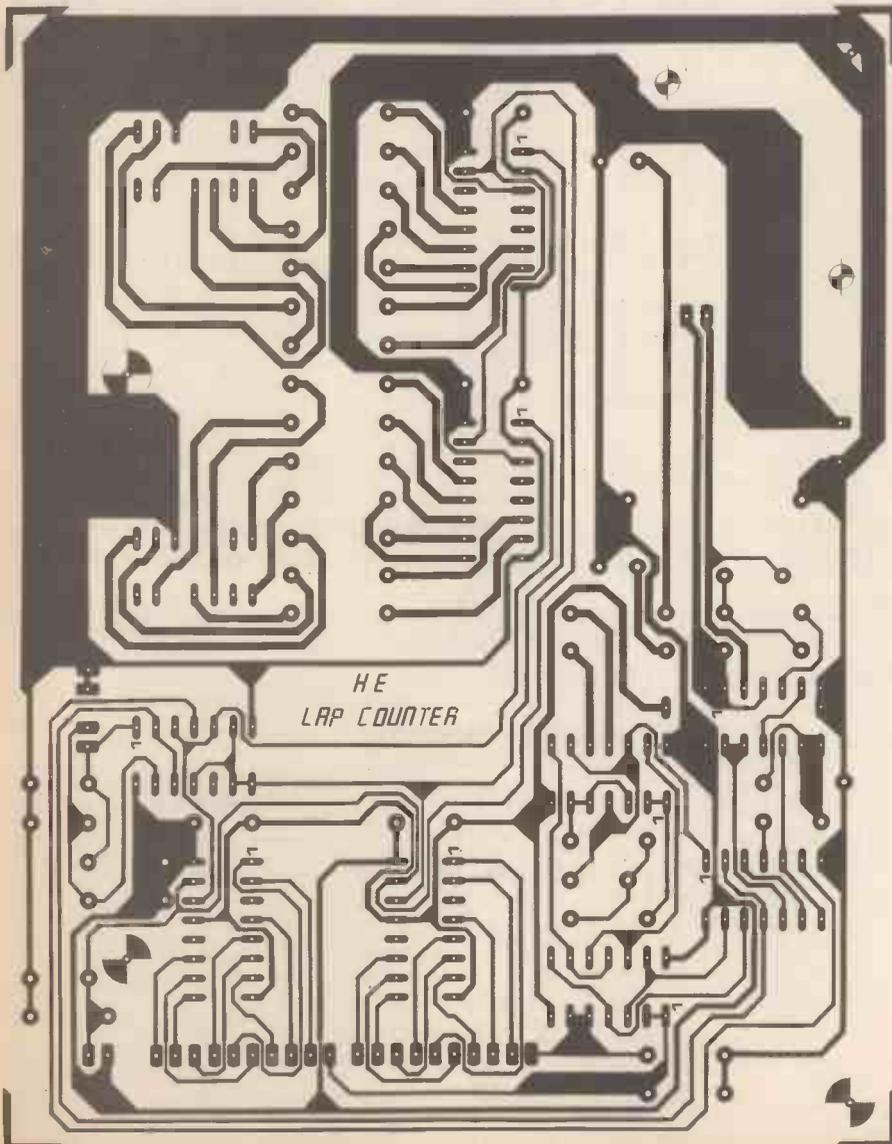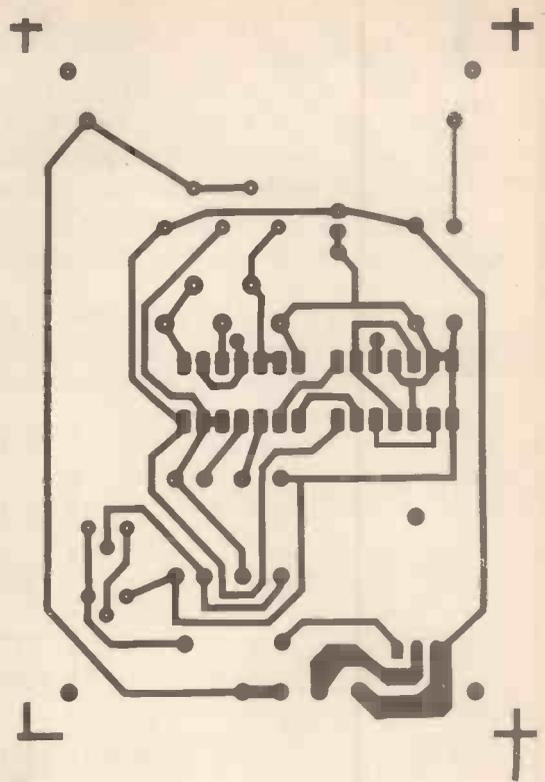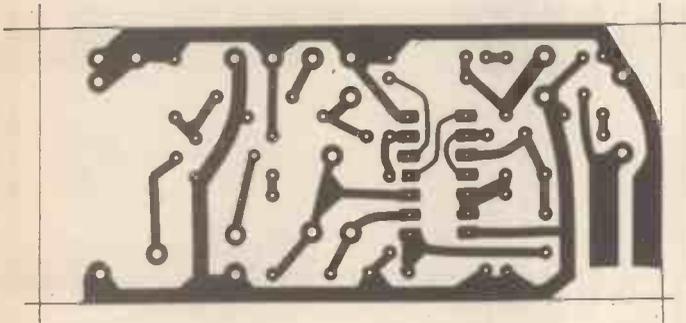

Above left: The PCB Mask for the HE Quizmaster.

Above right: The PCB Mask for the Power Reducer. The IC pin holes have filled in in reproduction so drill them out carefully.

Left: The foil pattern for the HE Lap Counter. A masterpiece of Chinese art by technical expert Ram Chandru.

## Lineage:

30p per word (minimum 15 words)  
Semi-display £7.50 per single column centimetre  
Ring for information on series bookings/discounts



01-437 1002  
EXT 289

Send your requirements to:  
Debbie Miller  
ASP Ltd.,  
145 Charing Cross Road,  
London WC2H 0EF

All advertisements in this section must be prepaid.  
Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)

## KITS

### IS ACCURATE TIMING ESSENTIAL TO YOU?

#### PRECISION DIGITAL TIMER KIT

All solid state.  
No relays.  
Will switch 240V AC @ 8A for time periods from 1 sec to 44 minutes in 1 or 10sec steps. Accurate to better than 1/50sec. For all time periods. NO RC time constants involved.



Ideal for darkroom, UV lamp, egg timing etc. Smart case, D.S. PCB, all components, screws, miniature 3 pin plug & socket AC outlet, wire, incl. 4ft. mains lead. Full circuit & assembly instructions. Can be wired for 240V or 120V. State if to be used on 50 or 60 cycles.  
Price £37.50 + £2.00 P&P.  
Ready built: £12 extra.

Antex Soldering Irons £4.65  
Spare bits all sizes 65p ea.

#### COMPUTERS

VIC-20 starter pack £130.42  
Commodore 64 £199.99  
VIC games cartridges including Sargon Chess all reduced to £8.65 each + P&P.

#### FLOPPY DISKETTES by VERBATIM

5 1/4" S.S. Dual Density  
Box of 10 £21.00 + £1.10 P&P.  
5yr warranty usual price £30+  
+1d 15% V.A.T. to all U.K. orders.

#### GPT ELECTRONICS

63 Cambridge Street  
Godmanchester  
Cambridgeshire PE18 8AY  
Tel: Geoff Miller 0480 56382

**PRINTED CIRCUITS.** Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

**DIGITAL WATCH** replacement parts, batteries, displays, backlights, etc. Also reports publications charts. S.A.E. for full list: Profords Copners Drive, Holmer Green, Bucks HP15 65GE.

## COMPUTERS

### HAVEN HARDWARE

ZX81 £49.90. Inverse Video £4.50. Repeating Keymodule £5.95. ZX Spectrum software: Repulsor fruit machines and Solitar £4.95 each. Mancala and Patience £5.95 each. Jupiter Ace £89.90. Inverse Video £4.95.

Access taken. SAE for details.

#### HAVEN HARDWARE

4 Asby Road, Asby, Workington,  
Cumbria Tel: 094-686 627  
Agency enquiries welcome

## RADIO SOFTWARE

### RADIO SOFTWARE DRAGON AND COCO

RTTY TRANSCIVE. Split screen, type ahead any Baud rate etc. will decode RTTY straight from your Radio.  
MORSE TRANSCIVE. Decodes and sends morse to 150 WPM.  
MORSETUTOR. Any speed, any spacing, includes a send practice facility.  
AMTOR SYSTEM. Available soon.  
Send large SAE for full details and software/hardware price list.

GROSVENOR SOFTWARE  
22 Grosvenor Road, Seaford  
E. Sussex BN25 2BS  
(0323) 893378

## PLANS 'N DESIGN

**AMAZING** electronic plans, lasers, gas, ruby, light shows, high voltage teslas, van de graph, surveillance devices, ultrasonics, pyrotechnics, new solar generator, 150 more projects, catalogue S.A.E., Industrial Centre, Bromyard Road Industrial Estate, Ledbury HR8

Electronic Outja Board  
Personal Self-defence Unit  
Brainwave Simulation  
Pocket air ioniser  
Sounds from Beyond receiver  
Auto-magnetiser  
Experimental bone rejuvenator  
Super-snooper listening device  
Car Stress alarm  
Miniature Directional Finder Receiver  
All above items £2 each

#### THOMPSONS ELECTRONICS

(Dept H.E.)  
Basement Office, N. 5 David Place,  
St. Heller, Jersey

## FOR SALE

**P.C.B. MOUNTED P.S.11** 240V 5V 250ma encapsulated. £7.50 inc. C.W.O. 7 Harehill Crescent, Wingerworth, Chesterfield, Derby.

**KIA** return an ad No. 11... 100 watt slave amplifiers modules—glass/PCB + To3 heatsinking—built, tested... Return advert + £6.95. Now... KIA 8 LS29 9DZ.

## ALARMS

**BURGLAR ALARM** equipment. Ring Bradford (0274) 731532 for our catalogue, or call at our large showrooms opposite Odsal Stadium.

## COMPONENTS

### BUMPER BOX OF BITS

WOW! If we've got so many components in stock, we can't possibly list them all! — So buy a box, in it you'll find resistors, capacitors, displays, switches, panels with transistors, diodes, IC's, etc., coils, pots... and so on. All modern parts — guaranteed at least 1000 items. Minimum weight 10lbs. ONLY £8.50 inc. 48 page catalogue 50p.

ELECTRONICS WORLD  
1F Dews Road, Salisbury  
Wilts SP2 7SN

**250 MIXED ELECTRONIC** components £2.00. Includes resistors, capacitors, diodes, etc. J. Karajar, 42 Priory Rd, Peterborough PE3 6ED.

### SMALL REED SWITCHES

12p. Magnets 17p. Continental 12 VDC relays 2 for £1.25p. 15hr 240V timers £2.95. Postage 25p. Grimsby Electronic Components, Lambert Road, Grimsby.

**IN STOCK** New telephone plugs and sockets also ZX81 plugs and spectrum plugs and wide range of burglar alarm equipment and all accessories for same plus large range of components. Shudehill Supply Co. Ltd., 53 Shudehill, Manchester 4. 061-834 1449.

**BARGAIN** — Semiconductor packs; transistors, IC's 12 items £1.60. Full specification components; BC107 9p; BC108 9p; BC109 11p; 2N3055 55p; BY50 21p; 741 17p; 555 18p; 556 43p. 40 pence p&p. VAT 15%. W.R. Carr, 26 Lawton Road, Roby, Merseyside L36 4HW.

## WANTED

**WANTED.** Handbooks for Phillips GM4114 and Heathkit IT-28 R.C. Bridges. Can copy originals. Tel: 0962 56064.

**TO PLACE AN AD —  
PHONE DEBBIE  
01-437 1002  
Ext 289**

## EQUIPMENT

**AERIAL AMPLIFIERS** Improve weak television reception. Price £6.70. S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire BL0 9AGH.

## ACCESSORIES

**BRITISH TELECOM** plug sockets and leads etc. Tel: C.W.A.S. (0274) 308920. Or visit our showroom opposite Odsal Stadium, Bradford.

## BOOKS & PUBLICATIONS

**PARAPHYSICS JOURNAL** (Russian translations). Psychotronics, Kirlianography, heliphonic music telekinetics. Computer software. SAE 4 x 9"— Parabal, Downton Wilts.

## SERVICES

**ALL ELECTRONIC** components post or phone your requirements to: J.C. Components, 7 Harehill Crescent, Wingerworth, Chesterfield, Derby. Tel: 0246 74003.

## HOBBY SHOP

## DAVENTRY

**EMOS** HIGH MARCH  
DAVENTRY NN11 4HQ  
Tel: (03272) 5523

- ★ Open Mon-Sat 9am-4pm
- ★ Both retailers and wholesalers
- ★ Vast stocks of components
- ★ Large 'walk-round' electronics supermarket

## NEWCASTLE

For the best in  
Electronic Test Equipment  
& Accessories visit

#### MARLBOROUGH ELECTRONICS

15 Waterloo Street  
Newcastle NE1 4DE1  
Tel: 618377

Open 9am-6pm Mon-Sat  
Easy parking

MARLBOROUGH ELECTRONICS

# HOBBY ELECTRONICS

## CLASSIFIED ADVERTISEMENT — ORDER FORM

If you have something to sell now's your chance! Don't turn the page — turn to us!  
**Rates of charge:** 30p per word per issue (minimum of 15 words).  
 and post to **HOBBY ELECTRONICS, CLASSIFIED DEPT., 145 CHARING CROSS ROAD, LONDON WC2**


Please place my advert in **HOBBY ELECTRONICS** for . . . . . issues commencing as soon as possible.  
 I am enclosing my Cheque/Postal Order/International Money Order for: (delete as necessary) £ . . . . . (Made payable to A.S.P. Ltd)  
 Please use **BLOCK CAPITALS** and include post codes.  
**Classification** . . . . .  
**Name (Mr/Mrs/Miss/Ms)** . . . . . (delete accordingly)  
**Address** . . . . .  
 . . . . .  
**Signature** . . . . . **Date** . . . . .  
**Daytime Tel. No.** . . . . .



OR Debit my Access/Barclaycard  
 (Delete as necessary)



--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

All classified advertisements must be paid for in advance.



### FREE CAREER BOOKLET

**Train for success, for a better job, better pay**

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, Through ICS home study, used by over 8 million already! Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your **FREE CAREER BOOKLET** today  
 —no cost or obligation at all.

C & G BASIC ELECTRONICS <input type="checkbox"/>	ELECTRONIC ENGINEERING <input type="checkbox"/>
C & G RADIO AMATEUR'S Exam <input type="checkbox"/>	COMPUTER PROGRAMMING <input type="checkbox"/>
RADIO & AUDIO ENGINEERING <input type="checkbox"/>	TV & AUDIO SERVICING <input type="checkbox"/>
RUNNING YOUR OWN BUSINESS <input type="checkbox"/>	ELECTRICAL INSTALLATIONS/CONTRACTING <input type="checkbox"/>
AUTO MECHANICS <input type="checkbox"/>	C & G BASIC MECHANICAL ENGINEERING <input type="checkbox"/>

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 P.Code \_\_\_\_\_

ICS  
Dept Q261  
160 Stewarts Road,  
London SW8 4UJ

01-622 9911  
(all hours)

### ADVERTISERS INDEX


Ambit International . . . . .	IFC
Amtron UK . . . . .	.25
Audio Electronics . . . . .	.36
Bimsales . . . . .	.38
B.K. Electronics . . . . .	IBC
B.N.R&E.S . . . . .	.46
Brian J Reed . . . . .	.57
J.Bull. . . . .	.4
Concept Electronics . . . . .	.36
Dataplus Developments . . . . .	.36
Electronize Design. . . . .	.5
Hazzlewood Electronics . . . . .	.38
H.G. Electronics . . . . .	.57
Horizon Electronics. . . . .	.38
ICS . . . . .	.66
ILP . . . . .	14,51
Kelan Engineering. . . . .	.25
Litesold . . . . .	.38
Magenta Electronics . . . . .	OBC
Microtan. . . . .	.44
Pantec . . . . .	.51
Parndon Assocs . . . . .	.57
Sandwell Plant. . . . .	.38
Sparkrite . . . . .	.19
Stewarts of Reading . . . . .	.38
Texas Instruments. . . . .	.57
T.K. Electronics . . . . .	.25
Tomorrows World . . . . .	.26


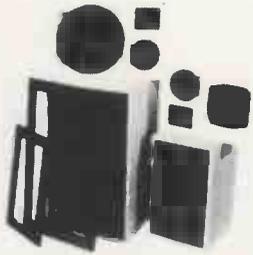
### MULLARD SPEAKER KITS

Purposefully designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer (8" or 5 1/2") with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter. B.K.E. built and tested crossover based on Mullard circuit, combining low loss components, glass fibre board and recessed loudspeaker terminals. SUPERB SOUNDS AT LOW COST. Kits supplied in polystyrene packs complete with instructions. 8" 40W system — recommended cabinet size 240 x 216 x 445mm Price £14.90 each + £2.00 P & P. 5" 30W system — recommended cabinet size 160 x 175 x 295mm Price £13.90 each + £1.50 P & P.


Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self adhesive vinyl etc. 8" system cabinet kit £8.00 each + £2.50 P & P. 5" system cabinet kit £7.00 each + £2.00 P & P.


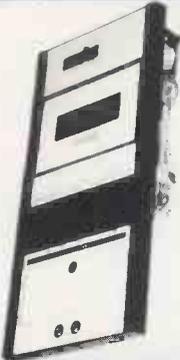
### STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Autostop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Input Sensitivity: 100mV to 2V. Input Impedance: 68K. Output level: 400mV to both left and right hand channels. Output Impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V DC at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2 x 11 1/2 in. Clearance required under top panel 2 1/2 in. Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish. Price £26.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.



### LOUDSPEAKERS POWER RANGE

THREE QUALITY POWER LOUDSPEAKERS (15", 12" and 8" See Photo). Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons. Specification and Prices.


15" 100 watt R.M.S. Impedance 8 ohms. 50oz magnet. 2" aluminium voice coil. Res. Freq. 20 Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. Price: £34.00 each + £3.00 P&P  
12" 100 watt R.M.S. Impedance 8 ohms. 50oz magnet. 2" aluminium voice coil. Res. Freq. 25Hz. Freq. Resp. to 4 KHz. Sens. 95dB. Price: £24.50 each + £3.00 P&P  
8" 50 watt R.M.S. Impedance 8 ohms. 20 oz magnet. 1 1/2" aluminium voice coil. Res. Freq. 40Hz. Freq. Resp. to 6 KHz. Sens. 92dB. Black Cone. Price: £9.50 each. Also available with black protective grille Price: £9.99 each. P&P £1.50.

12" 85 watt R.M.S. MCKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 98dB. Price: £23.00 + £3 carriage.  
12" 85 watt R.M.S. MCKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz. Price £23 + £3 carriage.  
15" 150 watt R.M.S. MCKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price: £47 + £4 carriage.


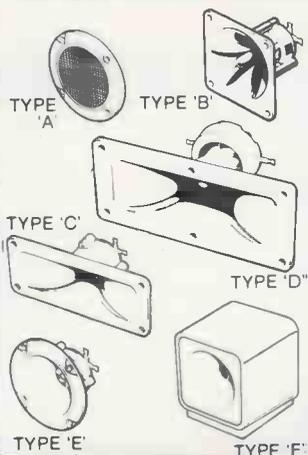
### PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.29 each.


TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £5.99 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £7.99 each.

TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £4.99 each.

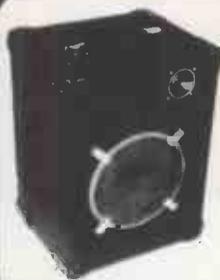TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each P&P 20p ea. (or SAE for Plezo leaflets).



### OMP 80 LOUDSPEAKER

The very best in quality and value.

Ported tuned cabinet in hard-wearing black vinyl with protective corners and carry handle. Built and tested, employing 10in British driver and Piezo tweeter. Spec: 80 watts RMS; 8 ohms; 45Hz-20KHz; Size: 20in x 15in x 12in; Weight: 30 pounds.

Price: £49.00 each  
£90 per pair  
Carriage: £5 each £7 per pair

## BK ELECTRONICS

Prompt Deliveries  
VAT inclusive  
prices  
Audio Equipment  
Test Equipment  
by  
Thandar  
and  
Leader



### HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £7.99p

DIGITAL THERMOMETER -9.9°C to +99.9°C. LED display. Complete with sensor. 70 x 70 mm (9 volt) Price: £27.60p

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled. professional performance. Range up to 3 miles 35 x 84 x 12 mm (12 volt) Price: £12.49p

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22 mm (9/12 volt) Price: £16.49 Transmitter 80 x 50 x 15 mm (9/12 volt) Price £10.29 P&P All Kits +50p. S.A.E. for complete list.




3 watt FM Transmitter

### BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm ● Belt driven ● Aluminium platter ● Precision calibrated counter balance ● Antiskate (bias device) ● Damped cueing lever ● 240 volt AC operation (Hz) ● Cut out template supplied ● Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price £31.35 each. £2.50 P&P

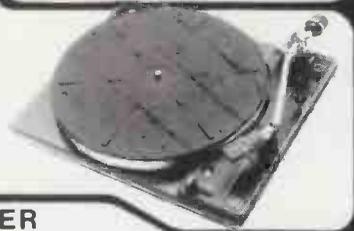

### OMP POWER AMPLIFIER MODULE

READY BUILT



New model.  
Improved specification

MOSFET versions available up to 300W. R.M.S.

NEW OMP100 Mk.II POWER AMPLIFIER MODULE Power Amplifier Module complete with integral heat sink, toroidal transformer power supply and glass fibre p.c.b. assembly. Incorporates drive circuit to power a compatible LED Vu meter. New improved specification makes this amplifier ideal for P.A., Instrumental and Hi-Fi applications.

OUTPUT POWER:— 110 watts R.M.S. Loads:— Open and short circuit proof 4/16 ohms. Frequency Response:— 15Hz - 30KHz -3dB. T.H.D.:— 0.01%. S.N.R. (Unweighted):— -118dB ±3.5dB. Sensitivity for Max Output:— 500mV @ 10K. Size:— 360 x 115 x 72 mm Price:— £31.99 + £2.00 P&P. Vu Meter Price:— £7.00 + 50p P&P.

### HOME PROTECTION SYSTEM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. FULLY GUARANTEED.

Control Unit — Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch — off — test — armed. 30 second exit and entry delay. Indoor alarm — Electronic swept freq. siren. 104dB output.

Outdoor Alarm — Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/250 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £128 Usual price £228.85

BKE's PRICE £99.p&p£4


SAE for colour brochure.


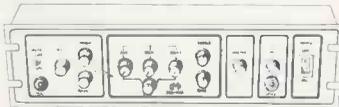
### MIXERS DISCO OMP PRO MIX MONO

OMP PROMIX MONO DISCO MIXER (As illustrated), 4 Inputs: -2 Mag. Disc. 1 Aux plus Mic with override. Active bass and treble tone con'ts. Individual level controls plus master volume. Monitor output (headphone) for all inputs. Output: 775mV Supply 240Vac. Size: 19" x 5 1/2" x 2 1/2". Price: £49.99 + £2.00 P&P

ALSO Stereo Version as above price £69.99 + £2 p&p



READY BUILT & TESTED.

# B.K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR



★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★ All items packed where applicable in special energy absorbing PU foam. ★ Please phone 0702 527572 ★

# H.E. PROJECT KITS

I.C.s  
TRANSISTORS  
CAPACITORS

TOOLS  
RESISTORS  
HARDWARE

CASES  
KITS  
PCBs

# MAGENTA

Full Kits inc. PCBs (or veroboard), hardware, electronics, cases (unless stated). Less batteries. If you do not have the issue of H.E. which includes the project — you will need to order the instruction reprint as an extra — 50p each. Reprints available separately 50p each + p&p 50p.

ULTRASONIC INTRUDER ALARM no case Oct 83	£14.85	IN CAR CASSETTE POWER SUPPLY Dec 81	£4.77
WHISTLE SWITCH Aug 83 less mic	£18.99	SCRATCH FILTER Nov 81 Mono	£5.82
STEREO SPREADER July 83	£5.79	LED VU METER Nov 81 less case	£4.87
SOFT FUZZ July 83	£10.25	SIMPLE STYLUS ORGAN Nov 81 less case	£4.96
SINCLAIR SOUND BOARD Jun 83 less case	£16.98	METRONOME Nov 81	£12.71
BATLIGHT (car battery indicator) June 83 less case	4.96	TELEPHONE BELL REPEATER Oct 81	£13.67
TTL LOGIC PROBE June 83	£7.98	COMBINATION LOCK Oct 81 less solenoid	£16.65
AUTO TESTER May 83	£18.98	BABY ALARM Oct 82	£9.70
STALL THIEF May 83 (inc relay)	£11.72	'DIANA' METAL LOCATOR Sept 82	£34.50
STEREO VOICE OVER UNIT April 83	£17.52	REACTION TESTER GAME Sept 81	£12.81
OPTIONAL MIC PRE AMP April 83 (no case)	£6.26	VARIABLE BENCH POWER SUPPLY Aug 81	£26.98
AUTO POWER DOWN April 83 no case	£8.05	ULTRASOUND BUZZGLAR ALARM July 81	£14.98
LINEAR OHMMETER Mar 83	£13.55	ELECTRONIC DOOR BUZZER July 81	£5.96
LOW RANGE OHMMETER Mar 83	£10.37	ELECTRONIC METRONOME July 81	£4.99
PHASE FOUR Dec 82	£18.71	'CONTINUITY CHECKER June 81	£5.71
STEREO NOISE GATE Dec 82	£15.34	ENVELOPE GENERATOR June 81	£17.96
TAPE/SLIDE SYNCHRONIZER Dec 82	£21.73	AUDIO METER July 81	£5.33
MICROMETER ADAPTOR Dec 82	£4.98	PUBLIC ADDRESS AMPLIFIER March 81	£19.48
OOMETER Nov 82	£14.98	Extras — horn speakers £6.83 each	PA MIC £4.40
DIANA V.C.O. Nov 82	£4.98	FUZZBOX March 81	£10.98
CB SQUELCH UNL Oct 82	£9.19	WINDSCREEN WIPER CONTROLLER March 81	£8.20
'JUNIOR' SLOT CAR CONTROLLERS Sept 82	£5.80 (less case)	STEAM LOCO WHISTLE March 81	£12.96
ZX INTERFACE BOARD Sept 82 inc edge con	£11.33	PHOTOGRAPHIC TIMER March 81	£3.50
T.V.1. FILTER July 82	£5.33	HEATBEAT MONITOR Feb 81	£24.96
AUTO WASH June 82 £18.98 inc case or £12.28 less case	£14.38	TWO-TONE TRAIN HORN Feb 81	£5.60 less case
AUTO GREENHOUSE SPRINKLER June 82	£38.48	MEDIUM WAVE RADIO Feb 81	£8.20
less pump and power supply	£9.96	BENCH AMP Jan 81	£10.98
POWER SUPPLY DESIGN 12V 500MA June 82	£9.96	NICAD CHARGER Jan 81	£8.20
ECHO REVERSE UNIT May 82 Less case	£37.88 extra	CHUFFER Jan 81, less case	£7.53
Economy case W80	£16.90	BATTERY CHARGE MONITOR Dec 82	£6.77
DIGITAL THERMOMETER May 82 excluding case + bezel	£20.96	MEMORY BANK — MINI SYNTHESIZER Nov & Dec 80	£31.48
AUDIO SIGNAL GENERATOR May 82	£20.96	TRANSISTOR TESTER Nov 81	£6.54 inc test leads
CABLE TRACKER May 82	£9.96	GUITAR PRE-AMP Nov 80 £6.65	case extra £2.29
DIGITAL CAPACITANCE METER Apr 82	£21.37	INTRUDER ALARM Oct 80	£20.96
SIGNAL TRACER Apr 82	£3.86	TOUCH SWITCH Sept 80	£2.75 less case & contacts
BIKE ALARM Apr 82	£7.29	QUILT PHASER Sept 80	£16.28
DIGITAL DICE Mar 82	£10.99	SOUND OPERATED FLASH TRIGGER July 80 no skt	£8.33
BICYCLE SIREN Mar 82	£10.45	FOG HORN June 80	£6.64
NOISELESS FUZZBOX Feb 82	£14.74	SPEED CONTROLLER FOR R/C April 80	£17.55 (less case)
MASTHEAD AMPLIFIER Feb 82	£24.37	DIGITAL FREQUENCY METER April 80	£12.92
DRUM SYNTHESIZER Dec 81. Full kit	£3.72	GUITAR TUNER Nov 79	£12.91
GUITAR HEADPHONE AMPLIFIER Dec 81		CAR ALARM Feb 79	

## BOOKS: ELECTRONICS & COMPUTING

205 First Book of Hi-Fi Loudspeaker Enclosures	£0.85	Semiconductor Data Book Newnes	£6.95
228 Tested Transistor Projects	£1.25	Basic Electronics Theory and Practice	£7.98
228 50 Projects Using ICs CA3139	£1.25	Microprocessor for Hobbyist	£4.75
225 A Practical Introduction to Digital IC's	£1.25	Burglar Alarm Systems	£5.55
226 How to Build Advanced Short Wave Receivers	£1.95	Electronic Circuits and Learn	£3.90
228 Essential Theory for the Electronic Hobbyist	£1.95	Electronic Projects in Music	£3.90
BP39 50 (FET) Field Effect Transistor Projects	£1.75	Electronic Projects in Photography	£3.90
BP40 Digital IC Equivalents and Pin Connections	£3.50	Electronic Projects in Home Security	£2.70
BP41 Linear IC Equivalents and Pin Connections	£3.50	Questions and Answers Electronics	£2.70
BP42 50 Simple L.E.D. Circuits	£1.50	Electronic Projects in the Car	£4.80
BP43 How to Make Walkie-Talkies	£1.95	20 Solid State Projects Car and Garage	£4.80
BP45 Projects in Opto-Electronics	£1.95	110 Electronic Alarm Projects	£5.98
BP47 Mobile Discotheque Handbook	£1.35	Computing in the 80's	£1.28
BP48 Electronic Projects for Beginners	£1.95	ZX81 User Handbook	£5.75
BP49 Popular Electronics Projects	£1.95	ZX81 Basic Book	£5.75
BP56 Electronic Security Devices	£1.95	Fun with Electronics	£1.25
BP58 50 Circuits Using 7400 Series IC's	£1.75	24 50 CMOS J.C. Projects	£1.35
BP59 Second Book of CMOS IC Projects	£1.50	BP24 52 Projects Using IC 741	£1.25
BP61 Beginners Guide to Digital Techniques	£0.95	BP44 IC5555 Series	£1.95
BP70 Transistor Radio Fault-Finding Chart	£0.50	BP50 IC LM3900 Projects	£1.35
BP71 Electronic Household Projects	£1.75	BP65 Single IC Projects	£1.50
BP75 Electronic Test Equipment Construction	£1.75	BP69 Electronic Games	£1.75
BP76 Practical Computer Experiments	£1.75	BP72 A Microprocessor Primer	£1.75
BP79 Radio Control for Beginners	£1.75	BP73 Remote Control Projects	£1.95
BP80 Popular Electronic Circuits — Book 1	£1.95	BP74 Electronic Music Projects	£1.75
BP81 Electronic Synthesizer Projects	£1.75	BP76 Power Supply Projects	£1.75
BP82 Electronic Projects Using Solar Cells	£1.85	BP83 V MOS Projects	£1.95
BP85 International Transistor Equivalents Guide	£2.95	BP84 Digital IC Projects	£1.95
BP87 Simple L.E.D. Circuits — Book 2	£1.35	BP88 How to Use OP-Amps	£2.25
BP92 Easy Electronics — Crystal Set Construction	£1.75	BP90 Audio Projects	£1.95
BP94 Electronic Projects for Cars and Boats	£1.95	BP93 Electronic Timer Projects	£1.95
BP98 Popular Electronic Circuits — Book 2	£2.25	BP95 Model Railway Projects	£1.95
BP101 How to Identify Unmarked IC's	£0.85	BP97 IC Projects for Beginners	£1.75
BP103 Multi-Circuit Board Projects	£1.95	BP99 Mini Matrix Board Projects	£1.95
BP108 International Diode Equivalents Guide	£2.25	BP105 Aerial Projects	£1.95
BP109 The Art of Programming the 1K ZX81	£1.95	BP106 Modern OP-AMP Projects	£1.95
BP114 The Art of Programming the 16K ZX81	£2.50	BP115 The Pre Computer Book	£2.25
BP119 The Art of Programming the ZX Spectrum	£2.50	Electronic Science Projects	

Handbook of Integrated Circuits (IC's) Equiv. & Substitutes	£1.95	A33-8912 i.c.	£5.98
Solid State Short Wave Receivers for Beginners	£1.25	ZX81 edge connector	£2.25
Beginners Guide to Building Electronic Projects	£1.95	ZX81 edge plug	£1.50
First Book of Transistor Equivalents and Substitutes	£1.75	ZX Spectrum edge connector	£2.55
Second Book of Transistor Equivalents and Substitutes	50p		
Chart of Radio, Electronic, Semi-conductor and Logic Symbols	£1.95		
How to Build Your Own Metal and Treasure Locators	£1.95		
50 Circuits Using Germanium, Silicon and Zener Diodes	£1.50		
50 Projects Using Relays, SCR's and TRIACS	£1.95		
Electronic Music and Creative Tape Recordings	£1.95		
Practical Electronics Calculations and Formulae	£2.95		
How to Build Your Own Solid State Oscilloscope	£1.95		
Practical Construction of Pre-amps, Tone control Filters & Attn	£1.45		
Beginners Guide to Microprocessors and Computing	£1.75		
Counter, Driver and Numerical Display Projects	£1.75		
An Introduction to BASIC Programming Techniques	£1.95		
30 Solderless Breadboard Projects — book 2	£2.30		
How to Get Your Electronic Projects Working	£1.95		
Practical Electronic Building Blocks — Book 1	£2.25		
Practical Electronic Building Blocks — Book 2	£1.95		
Elementary Electronics. Sladdin. Excellent theory and 35 constructional projects. Uses S-Dec. First steps to CSE level	£3.98		
Interfacing to Microprocessors and Microcomputers	£5.75		

## MEMORY BANK SYNTHESISER

Miniature synthesiser featuring vibrato, envelope, tempo, volume + pitch controls. Uses 24 push button switches in a keyboard style layout. Based on a custom designed L.C. The accessible memory stores a 32 beat length sequence of notes + spaces. Can be played 'live'. Fitted with an internal speaker. Jack socket allows the use of an external amplifier if wished.

**Memory Bank Synthesiser £31.48**

Complete kit inc. case, pcb's etc. Reprint extra 50p. Available separately 50p + 50p p&p

## SOLDERING/TOOLS

ANTEX XS SOLDERING IRON 25W	£5.48
SPARE BITS. Small standard, large. For X5 + X25	£1.84
SOLDER. Handy size	99p
SOLDER CARTON	£1.84
HEAT SINK TWEEZERS	29p
DESOLDER PUMP	£6.48
HOW TO SOLDER LEAFLET	12p
LOW COST CUTTERS	£1.69
LOW COST LONG NOSE PLIERS	£2.98
WIRE STRIPPERS & CUTTERS	£1.98
PRECISION PETITE	
12V P.C.B. DRILL	£11.67
DRILL STAND	£18.98
GRINDING WHEEL	50p
GRINDING WHEEL	50p
SAW BLADE	85p
BRASS WIRE BRUSH	50p
BURR	50p
VERO SPOT FACE CUTTER	£1.48
pin insertion tool	£1.98
VEROPINS (pk of 100) 0.1"	52p
MULTIMETER TYPE 1 (1.00 opv)	£5.48
CROCODILE CLIP TEST LEAD SET. 10 leads with 20 clips	99p
RESISTOR COLOUR CODE CALCULATOR	21p
CONNECTING WIRE PACK TYPE ED. 11 colours	48p
ILLUMINATED MAGNIFIERS	
Small 2" dia. (5 x mag)	£1.14
Large 3" dia. (4 x mag)	£2.98
CAST IRON VICE	£1.98
SCREWDRIVER SET	£3.98
POCKET TOOL SET	£2.85
DENTIST INSPECTION MIRROR	£1.50
JEWELLERS EYEGLASS	69p
PLASTIC TWEEZERS	77p
PAIR OF PROBES WITH LEADS (cc)	
O MAX PUNCHES	
1/4" £2.98; 1/2" £3.06; 3/4" £3.17; 1" £3.24	



MULTIMETER TYPE 2 (V.M.G. 0.01) 20K ohm p.v. with transistor tester. £4.75 AC — DC volts DC current 4 ranges resistance ranges



HELPING HANDS JIG £6.30 Heavy base. Six ball and socket joints allow infinite variation of clips through 360°. Has 2 1/2" diameter (2.5 magnifier attached), used and recommended by our staff.

## CHRISTMAS DECORATIONS

Three project kits — same style as usual H.E. projects. Instructions/reprint included in project price. Please use code when ordering.

CM1. TWINKLING STAR DECORATION

£6.98 Full in power supply extra £3.89

CM2. TABLE DECORATION £9.98

CM3. TREE LIGHTS FLASHER £12.54

## CHRISTMAS DECORATIONS

### \* \* \* \* \* FUN WITH ELECTRONICS

Enjoyable Introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners — children and adults. Only basic tools needed. 64 full colour pages cover all aspects — soldering — fault finding — components (identification and how they work).

Also full details of how to build 6 projects — burglar alarm, radio, games, etc. Requires soldering — 4 pages clearly show you how.

COMPONENTS SUPPLIED ALLOW ALL PROJECTS TO BE BUILT AND KEPT. supplied less batteries & cases.

FUN WITH ELECTRONICS COMPONENT PACK £15.78

BOOK EXTRA £1.25

Book available separately.

## ADVENTURES WITH MICROELECTRONICS

Entertaining and Instructive. Includes details of some digital ICs and 8 projects: shooting gallery, 2 way traffic lights, electronic adder, computer space invaders game etc. No soldering. Adventures with Digital Electronics book £3.25 Component pack including breadboards £42.50 less batteries.

## ADVENTURES WITH DIGITAL ELECTRONICS

Similar to 'Electronics' below. Uses I.C.s. Includes dice, electronic organ, doorbell, reaction timer, radio etc. Based on 'Bimboard 1 bread board. Adventures with Microelectronics £3.20 Component pack £29.64 less battery.

## ADVENTURES WITH ELECTRONICS by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects. Adventures with Electronics £2.85. Component pack £18.98 less battery.

## MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST Price list included with orders or send sae (9 x 4) CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

## ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Send 80p in stamps or add 80p to order. FREE to Schools/Colleges requested on official letterhead.

MAGENTA ELECTRONICS LTD  
HE5, 135 Hunter St, Burton-on-Trent  
Staffs., DE14 2ST. Mail Order Only  
(0283) 65435. S.A.E. enquiries  
Add 50p p&p to all orders. Prices  
include VAT. Access & Visa phone/post

Official school orders welcome.  
OVERSEAS. Payment must be in sterling.  
IRISH REPUBLIC + BFPO — UK PRICES.  
EUROPE: UK PRICES + 10%.  
ELSEWHERE: WRITE FOR QUOTE.  
Goods normally despatched by return of post.