

Hobby

Electronics

Project Electronics For Everyone

90p



OFF-BEAT METRONOME

March to the beat of a different drummer

**Memotech
MTX500
Computer
Reviewed**

High-purity 3Hz-3MHz Sine Wave Generator to build

Lightning Chess Timer Make your move...or lose!

The Hobbit – Tolkien experts ring the changes on this popular game

SPRING HAS SPRUNG!



Ambit's Spring '84 catalogue brings all the parts you need for electronics, radio, audio and computing to your front door.

There's details about an exciting new range of kits and modules being launched into the UK in conjunction with the leading German hobby supplier; full information on our two new regional sales counters in Portsmouth and Broxbourne; new low cost instruments from Black Star - plus all your old favourites:

NiCads, chargers, TOKO coils, filters, and communications ICs, crystal filters, Audio and RF semiconductors - including the biggest range of low cost varicap diodes for all types of electronic tuning.

Available from all good newsagents,
or direct from ambit
Order as Stock Number:
02-00009

More than ever, Ambit's concise 'price on the page' Spring catalogue is the one that you cannot afford to be without. It's fully indexed, precise and up to the minute - get a copy now!

We operate a fully on-line telesales service between 9am and 5.30pm
(Visa, Access, Amex)

ambit
international

all mail order to:

200 North Service Road, Brentwood, Essex
telephone (0277) 230909

Sales counters at:

Park Lane, Broxbourne, Herts
Burrfields Road, Portsmouth

Hobby Electronics

MARCH 1984
Vol 6 No 2

PROJECTS

- ★ OFFBEAT METRONOME 11
A metronome with several differences.
- ★ 3HZ — 3MHZ SINE WAVE GENERATOR 27
A sine for every occasion.
- ★ LIGHTNING CHESS TIMER 54
Don't think — do it now.

FEATURES

- ★ ALL ABOUT ELECTRONICS PART 8 20
Bistables and counters.
- ★ BREADBOARD 24
What we saw at the show.
- ★ CAREERS IN ELECTRONICS 41
The final episode in our three-part series looks at the Royal Air Force.
- ★ REVIEW: MEMOTECH MTX 500/512 MICRO 49
A new micro which continues the trend towards larger memories.
- ★ THE HOBBIT 56
Another look at Melbourne House's revolutionary computer game.
- ★ A LEAP IN THE DARK 44
Sinclair's new QL microcomputer previewed.

SPECIALS

- ★ THE COMPLETE CUMULATIVE INDEX
1978 — 1983 31
Profoundly researched, proven in the field, the final and definitive guide.

REGULARS

- Monitor 6
- Points Of View 16
- Whats On Next 18
- Buylines 26
- HE Bookshelf 46
- Forward Bias 47
- HE PCB Service 63
- HE PCB Page 64

Note: This month Hobby Electronics and Digital & Micro Electronics welcomes Terry Johnson as Technical Editorial Assistant. The gent has extensive experience both in journalism and the components trade and is a long-awaited and much-needed addition to our team. Now, about that box of technical enquiries, Terry...

Editor: Ron Keeley
Deputy Editor: Helen P. Armstrong BA
Technical Editorial Assistant: Terry Johnson
Technical Illustrator: Jerry Fowler
Advertisement Manager: Joanne James
Copy Control: Lynn Collis
Managing Editor: Ron Harris BSc
Chief Executive: T. J. Connell

We are not normally able to deal with technical enquiries by 'phone, so please don't ring. Write to us with an SAE.



Lightning Chess Timer — page 54



Breadboard '83 — page 24



Sinclair QL Micro — page 44

Hobby Electronics is normally published on the second Friday of the month prior to the cover date.
Hobby Electronics, No. 1, Golden Square, London W1R 3AB, 01 437 0626. Telex No 8811869. Published by Argus Specialist Publications Ltd.
Origination by Ebony Typesetting, Trion House, 13 Dean Street, Liskeard, Cornwall PL14 4AB.
Distributed by S. M. Distribution Ltd, 16/18 Trinity Gardens, London SW9 8DX.

Printed by The Garden City Press, Letchworth, Herts SG6 1JS. Covers printed by Alabaster Passmore.


Notice: The contents of this publication including all designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Ltd. All rights conferred by the Law of Copyright and other intellectual property rights by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. All reasonable care is taken in the preparation of the magazine to ensure accuracy, but Argus Specialist Publications Ltd cannot be held responsible legally. ©Copyright 1984 Argus Specialist Publications Ltd. Member of Audit Bureau of Circulation.

PREVIOUSLY ADVERTISED STILL AVAILABLE

Tape punch and reader	£22.50
Beach isolating transformer 250 watt	£7.75
BOAC in-flight stereo unit	£11.50
Drill assortment 4 each 25 sizes between .25mm & 2.5mm	£11.50
Battery condition tester, less box	£1.75
Nicad chargers, mains	£0.75
Flourescent inventor 13 watt from 12v	£3.50
Ten digit stitch pad-pb phone etc.	£1.95
Uniselector 2 pole 25 way	£4.60
Water valve mains operated	£2.50
Counter 6 digit mains operated	£1.15
ditto 12v resettable	£3.45
Double glazing clear PVC sheet, 23 1/2" wide-per running ft.	£0.15
Locking mechanism with 2 keys	£1.15
Magnetic Clutch	£4.50
Mouth operated suck or blow switch	£2.30
Solenoid with slug 8-12v battery op. ditto 230v mains	£1.82
Timer Omron STP NH 110v AC Coil	£2.30
Key switch with 2 keys dp mains	£6.90
Air valve mains operated	£1.75
Latching relay mains operated	£3.50
Dry film lubricant aerosol can	£0.65
Coin op switch, cased with coin tray	£4.60



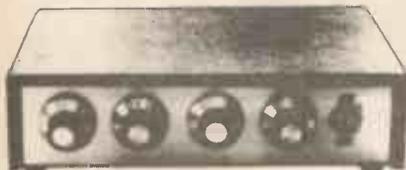8 POWERFUL MODEL MOTORS
(all different)
for robots, meccanos, drills, remote control planes, boats, etc. £2.95.



Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form or £25.00 assembled and tested.

12 volt MOTOR BY SMITHS

Made for use in cars, etc. these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3" dia. They have a good length of 1/4" spindle — Price £3.45.
Ditto, but double ended £4.25.
Ditto, but permanent magnet £3.75.



EXTRA POWERFUL 12v MOTOR

Probably develops up to 1/2 h.p. so it could be used to power a go-kart or to drive a compressor, etc. £7.95 + £1.50 post.

THERMOSTAT ASSORTMENT

10 different thermostats. 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted by in front of the element of a blow heater, the heat would trip the stat if the blower fuses; appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 — 100°C. There is also a thermostatic pad which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 — however, you can have the parcel for £2.50.

MINI MONO AMP

on p.e.b., size 4" x 2" (app.) Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.



— BARGAIN OF THE YEAR — The AMSTRAD Stereo Tuner.

This ready assembled unit is the ideal tuner for a music centre or an amplifier, it can also be quickly made into a personal stereo radio — easy to carry about and which will give you superb reception.

Other uses are a "get you to sleep radio", you could even take it with you to use in the lounge when the rest of the family want to view programmes in which you are not interested. You can listen to some music instead.

Some of the features are: long wave band 115 — 270 KHz, medium wave band 525 — 1650KHz, FM band 87 — 108MHz, mono, stereo & AFC switchable, tuning meter to give you spot on stereo tuning, optional LED wave band indicator, fully assembled and fully aligned. Full wiring up data showing you how to connect to amplifier or headphones and details of suitable FM aerial (note ferrite rod aerial is included for medium and long wave bands. All made up on very compact board.

Offered at a fraction of its cost: **only £6.00**
+ £1.50 post + insurance.

THIS MONTH'S SNIP

WHY PAY £10 OR MORE — Make yourself a Joystick — full details were given in Dec/Jan 'Sinclair Projects'. We will supply complete kit for £2.30. Although designed for the Spectrum or ZX81 It is equally suitable for any home computer.

REVERSIBLE MOTOR with control gear Made by the famous Framco Company this robust motor is approx 7 1/2" long, 3 1/4" dia. 3/8" shaft. Very powerful, almost impossible to stop. Ideal for operating stage curtains, doors, ventilators, etc. Even garage doors if properly balanced. Offered complete with control gear as follows:
1 Framco motor with gear box 1 push to start switch
1 manual reversing & on/off switch 2 limit stop switches
1 circuit diag. of connections **ONLY £11.70 + postage £2.50.**

FOR SOMEONE SPECIAL

Why not make your greeting card play a tune? It could play 'Happy Birthday', 'Merry Christmas', 'Wedding March', etc. or 'Home Sweet Home', etc. Wafer thin 3 part assemblies, for making cards musical. Mini microchip speaker and battery with switch that operates as the card is opened. Please state tune when ordering. Complete, ready to work £1.25.

REEL TO REEL TAPE DECKS

Ex-Langue Teaching School. Second, but we understand these are in good order; any not so would be exchanged. The deck is standard with normal record, replay facilities and an additional feature is tape rev counter. Nicely finished in teak type box. We have 30 only of these. Price £8.50 each + £3 carriage.

TELEPHONE ITEMS

Plug and Wall socket — 4 pin or 5 pin	£3.45
Plugs only 4 pin or 5 pin	£1.15
Modern desk telephone	£7.50
Heavy black old type	£5.50
External bell unit	£6.50
Bell ringing power unit	£4.50
Pick up coil	£1.15

STABILISED POWER SUPPLY (Mains Input)

By LAUDA (USA) — Ideal for computer add-ons, d.c. output. Regulated for line volts and load current. Voltage regulation .1% with input variations up to 20% — load regulation 1% from no load to full load — or full load to no load. Complete in heavy duty case — Models available: 5v - 9A £23.12v - 1.5A £13.25. 15v - 1.2A £13.25. 24v - 2A £23.

PRESTEL UNIT

— brand new and complete except for 7 plug in IC's — Price: £19.75 + £2.00 p&P.

Note: British Telecom may not connect this equipment as there is no manufacturer to guarantee it, however it is well worth buying for its immense breakdown value — sold originally at over £150.



FROZEN PIPES. Can be avoided by winding our heating cable around them — 15 mtrs connected to mains costs only about 10p per week to run. Hundreds of other uses as it is waterproof and very flexible. Resistance 60 ohms/metre. Price 28p/metre or 15m for £3.95.

25A ELECTRICAL PROGRAMMER

'Learn in your sleep.' Have radio playing and kettle boiling as you wake — switch on lights to ward off intruders — have a warmer house to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch. Independent 60 minute memory jogger. A beautiful unit at £2.50.

24 HOUR TIME SWITCH — Made for control of Randall Central Heating Boilers these give 2 on/off per 24 hrs. Equally suitable for control of immersion heaters of heating systems. £4.60.

50 THINGS YOU CAN MAKE

Things you can make include: Multi range meter, Low ohms tester, A.C. amps meter, Alarm clock, Soldering iron minder, Two way telephone, Memory jogger, Live line tester, Continuity checker, etc. etc., and you will still have hundreds of parts for future projects. Our 10kg parcel contains not less than 1,000 items - panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermostats, coils, condensers, resistors, neons, earphone/microphones, nicad charger, power unit, multi-turn pots and notes on the 50 projects.

YOURS FOR ONLY £11.50 plus £3.00 post.

MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument, Jewelled bearings - 2000 o.p.v. mirrored scale. 11 instant range measures:
DC volts 10, 50, 250, 1000.
AC volts 10, 50, 250, 1000.
DC amps 0 — 100 mA.



Continuity and resistance 0 — 1 meg ohms in two ranges. Complete with test leads and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 60p post and insurance.

FREE Amps range kit to enable you to read DC current from 0 — 10 amps, directly on the 0 — 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

J. BULL (Electrical) Ltd.

(Dept. HE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. **Established 30 YEARS**

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £12 add 60p service charge. Monthly account orders accepted from schools and public companies. Access & Barclay orders accepted day or night. Haywards Heath (0444) 454663. Bulk orders: phone for quote. Shop open 9.00 — 6.30, mon to Fri, not Saturday.

STORE CLOSING SALE

All stocks must go from one of our big warehouses. 10,000,000 items, everything from AERIALS to ZENER will be cleared at fantastically low prices - if you are a manufacturer you can save yourself a fortune - send for our Sale List, not for small buyers as minimum order £100.

EXTRACTOR FANS — MAINS OPERATED

Woods extractor.
5" — £5.75, Post £1.25.
6" — £9.95, Post £1.25.
5" Planmak extractor £5.50, Post £1.25.
4" x 4" Muffin 115v. £4.50, Post 75p.
4" x 4" Muffin 230v. £5.75, Post 75p.



All the above ex-computer, those below are unused.
4" x 4" £8.50, Post 75p.
9" American made £11.50, post £2.00.
Tangential Blower 10x3 air outlet, dual speed £4.60, Post 1.50.

TANGENTIAL BLOW HEATER

by British Solartron, as used in best blow heaters. 2Kw approx 9" wide £5.95, 3Kw either 9" or 12" wide (your choice) £5.95 complete with 'cold', 'half' and 'full' heat switch, safety cut out and connection dlg. Please add post £1.50 for 1 or £2.30 for two.



2.5 Kw KIT still available: £4.95 + £1.50 post.



MINIATURE WAFER SWITCHES

2 pole, 2 way — 4 pole, 2 way — 3 pole, 3 way — 4 pole, 3 way — 2 pole, 4 way — 3 pole, 4 way — 2 pole, 6 way — 1 pole, 12 way. All at 25p each.

BLEEP TONE These work off 12v and have an unusual and pleasant bleep. 69p each.

CONNECTING WIRE PACK 48 lengths of connecting wire, each 1 metre long and differently colour coded, a must for those difficult interconnecting jobs. 85p the lot.

RED LEDS 10 for 69p. 100 for £5.75. 1000 for £52.

IN LINE SIMMERSTAT Ideal heat controller for soldering iron and many other hand-held appliances. £2.30. 10 for £17.25.



VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case, but we can supply a plastic case - £1.75 or metal case - £2.95. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder — a complete mains operated kit, case included. £11.95 plus £2.00 post.

OTHER POPULAR PROJECTS

Short Wave Set — covers all the short wave bands using plug-in coils. Kit complete	£14.50
R C Bridge Kit	£9.95
3 Channel Sound to Light — with fully prepared metal case.	£14.95
Ditto — made up	£25.00
Big Ear, listen through walls	£9.50
Robot controller — receiver/transmitter	£9.50
Ignition kit — helps starting, saves petrol, improves performance	£13.95
Silent sentinel Ultra Sonic Transmitter and receiver	£9.50
Car Light 'left on' alarm	£3.50
Secret switch — fools friends and enemies alike	£1.95
3 — 30v Variable Power Supply	£13.80
2 Short & Medium wave Crystal Radio	£3.99
3v to 16v Mains Power Supply Kit	£1.95
Light Chaser — three modes	£17.50
Mullard Unilex HI FI stereo amplifier with speakers	£16.75
Radio stethoscope — fault finding aid	£2.50
Mug stop — emits piercing squawk	£4.80
Morse Trainer — complete with key	£2.99
Drill control kit	£3.95
Drill control kit — made up	£6.95
Interrupted beam kit	£2.50
Transmitter surveillance kit	£2.30
Radio Mike	£5.90
FM receiver kit — for surveillance or normal FM	£3.50
Seat Belt reminder	£3.00
Car Starter Charger Kit	£15.50
Soil heater for plants and seeds	£16.50
Insulation Tester — electronic megger	£7.95
Battery shaver or fluorescent from 12v	£8.90
Matchbox Radio — receives Medium Wave	£2.95
Mixer Pre-amp — disco special with case	£16.00
Aerial Rotator — mains operated	£29.50
Aerial direction indicator	£5.50
40 watt amp — hi-fi 20Hz — 20KHz	£9.50
Microvolt multiplier — measure very low currents with ordinary multimeter	£3.95
Pure Sine Wave Generator	£5.75
Linear Power output meter	£11.50
115 Watt Amplifier 5Hz 25KHz	£13.50
Power supply for 115 watt amps	£8.50
Stereo Bass Booster, most items	£8.95

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite

SELF ASSEMBLY ELECTRONIC KITS

PRICES REDUCED
ON SUPER SAVE
D.I.Y. KITS



SX 1000 Electronic Ignition

- Inductive Discharge ● Extended dwell circuit stores greater energy in coil ● Three position changeover switch ● Patented clip-to-coil fitting ● Easy to assemble, easy to fit ● Contact breaker triggered - includes bounce suppression circuit.


SUPER SAVE

SX 2000 Electronic Ignition

- Reactive Discharge ● Combines inductive & capacitive energy storage ● Gives highest possible spark energy ● Patented clip-to-coil fitting ● Easy assembly sequence ● Contact breaker triggered - includes bounce suppression circuit.



SUPER SAVE

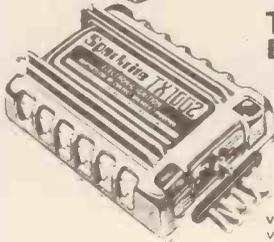


TX 1002 Electronic Ignition

- Inductive discharge ● Extended dwell circuit stores greater energy in coil ● Three position changeover switch ● Contactless or contact breaker triggered ● Clip-to-coil or remote mounting ● Rugged die-cast case ● Contactless adaptors included for majority of 4 & 6 cylinder vehicles ● Easy to build ● For details of vehicles fitted by contactless trigger, ring Technical Service Dept on (0922) 611338-9.

TX2002 Electronic Ignition

- Two separate systems in one unit! ● Reactive Discharge OR Inductive Discharge, with three position changeover switch ● Gives highest possible spark energy ● Clip-to-coil or remote mounting ● Rugged die-cast case ● Contactless or contact breaker triggered ● Contactless adaptors included for majority of 4 & 6 cylinder vehicles ● For details of vehicles fitted by contactless trigger, ring Technical Service Dept on (0922) 611338-9.

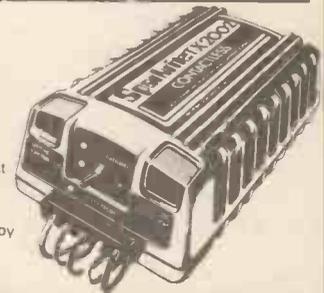

AT-40 Electronic Car Alarm

- Guards doors, boot, bonnet from unauthorised entry ● Armed/disarmed using concealed switch ● 30 second delay-to-arm ● 7 second entry delay ● Can alternatively be wired to exterior key switch ● Flashes headlights & sounds horn intermittently for 60 seconds when activated ● Security loop protects accessories ● Low consumption C-MOS circuitry.



NEW

AT-80 Electronic Car Security System

- Guards doors, boot, bonnet from unauthorised entry ● Armed/disarmed from outside vehicle by magnetic key fob passed across sensor pad adhered to inside of windscreen ● Individually programmable code ● 30 second delay-to-arm ● Flashes headlights and sounds horn intermittently for 60 seconds when activated ● Security loop protects accessories ● Function lights to assist setting-up ● Low consumption C-MOS circuitry.



SUPER SAVE

ULTRASONIC Intruder Detector

- Supplementary to AT 40 & AT-80 ● Will work in conjunction with any door switch input or voltage sensing alarm ● Detects attempted break-in and movement within passenger compartment & triggers alarm ● Includes high efficiency ultrasonic transducers ● Crystal controlled for low drift ● Ingenious sensitivity control allows freedom from false alarms ● Low current consumption



NEW

VOYAGER Car Drive Computer

- 12 functions centred on Fuel, Speed, Distance and Time ● Single chip microprocessor ● Large high brightness fluorescent display with auto-dimming feature ● High accuracy distance & fuel transducers included ● Displays MPG, L/100km and miles/litre at the flick of a switch ● Visual & audible warnings of excess speed, ice, lights-left-on ● Independent LOG & TRIP functions ● Low consumption crystal controlled circuitry.



SPECIAL OFFER
"FREE" MAGIDICE KIT WITH
ALL ORDERS OVER £40.00



MAGIDICE Electronic Dice

- Triggered by waving hand over dice ● Completely random selection ● Bleeps & flashes during 4 sec tumble ● Throw displayed for 10 seconds then flashes to conserve battery ● Low consumption C-MOS circuitry

SUPER SAVE

SPARKRITE (A Division of Stadium Ltd.) 82 Bath Street, Walsall, WS1 3DE England Tel: (0922) 614791

Allow 28 days for delivery

KIT	OLD PRICE	NEW PRICE
SX 1000	£12.95	£11.95
SX 2000	£19.95	£18.95
TX 1002	£22.95	£22.95
TX 2002	£32.95	£32.95
AT-40	—	£9.95
AT-80	£32.95	£24.95
ULTRASONIC	—	£17.95
VOYAGER	£64.95	£64.95
MAGIDICE	£9.95	£6.95

NAME _____ HE 3

ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF. _____

CHEQUE No. _____

PRICES INC. VAT, POSTAGE & PACKING

PHONE YOUR ORDER WITH



BRAND LEADING BRITISH ELECTRONICS
CUT OUT THE COUPON NOW!

MONITOR

On The Counter

The Meteor 600 is the first in a series of digital frequency counters announced by **Black Star**. With typical frequency measurement range of 2Hz-700MHz, sensitivity of <math><25\text{mV}</math> at 600MHz and resolution down to 0Hz1, the Meteor 600 also features 8 x 1/2in bright LED displays, three gate times, two inputs, trigger level control and an integral low pass filter.

The counter is housed in a sturdy, custom-moulded ABS case with a tilt stand. The Meteor 600 can be operated from rechargeable batteries or mains and is supplied complete with mains adaptor/charger and comprehensive instruction manual. A wide range of optional accessories is available.

The combination of high specification and reliability together with low cost plus flexibility of bench or field use makes the Meteor 600 useful for anyone involved in the design or service of CB, audio, communications systems etc. The price (excluding VAT) is £115. A 100MHz and a 1GHz version are also available.

Further details are available from **Black Star Ltd.**, 9A Crown Street, St. Ives, Huntingdon, Cambs PE17 4EB Tel: (0480) 62440.

New Vintage

The **Vintage Wireless Company**, purveyors of obsolete electronics, radio TV and industrial valves, antique wireless equipment, industrial electronics and valve hifi have now established themselves at their new address: **Tudor House, Cossham St., Mangotsfield, Bristol BS17 3EN**. Tel: (0272) 565472 (24hr Ansaphone).


Their new business hours are Monday to Friday 9.5 to 5.30, excepting lunch 1.15 to 2.15, callers by appointment for collection and delivery only till further notice (they are only dealing by mail order at present).

The **Antique Wireless Newsheet**, their newsletter/catalogue is available at twelve issues for £3.50 UK and Eire, £5.00 overseas (air mail).

Putting Pen To Circuit

With the introduction of the new 3211 Pen Digital Multimeter, **Dorman Smith Instruments** reckon they have the last word in portable measuring equipment. The 3211 is built like a pen which can be held in one hand and touched to the circuit to obtain a reading. Advanced design and the "touch-to-circuit" concept has enabled this portable digital multimeter to take readings in previously hard-to-reach locations and with an additional HOLD function a reading can be obtained until the operator is able to record it easily.

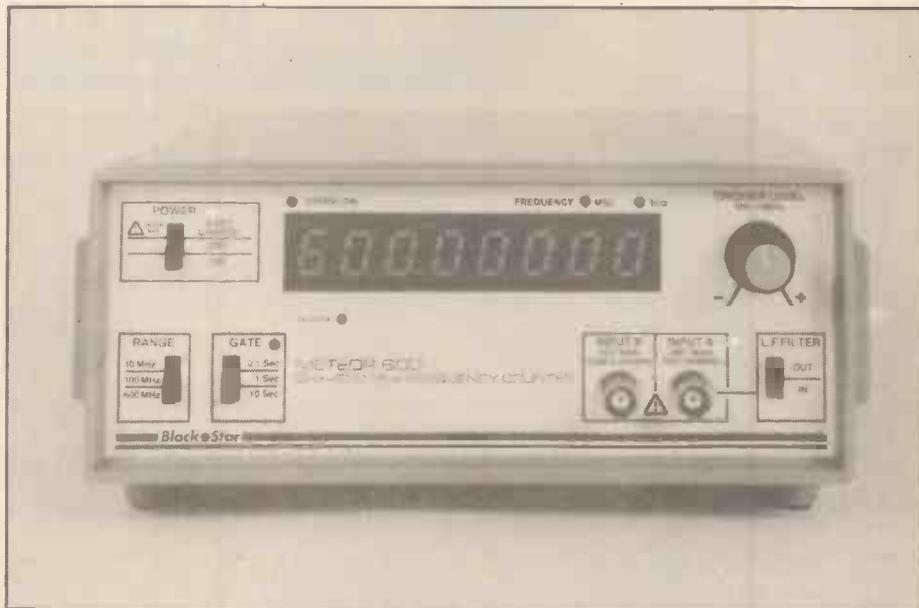All controls are arranged for operational use, including the easy to




read digital display — ideal for troubleshooting and maintenance work on computer systems, the 3211 will also make fast, reliable readings possible on other microcircuits and standard electrical devices. An audible tone of sounds reports the results of the continuity tests, function switching and overrange input.

For further information contact **Dorman Smith Instruments, Group Publicity Department, Blackpool Rd., Preston PR2 2DQ**. Tel: (0772) 728271.

Mighty Mite?

An ultra miniature 50V microswitch with an actuator arm has been announced by **Semiconductor Supplies International**. The switch's dimensions are height 10mm (including the pins, and with the lever compressed), width 8mm and thickness 3mm.

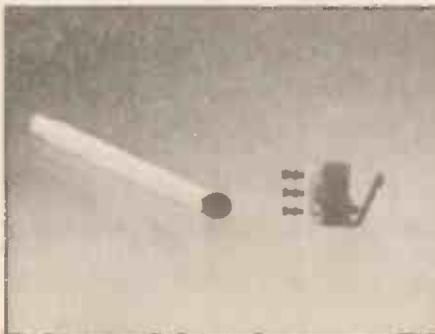The lever on the switch is designed for cam follower applications as well as ordinary compression. Possible uses are tamper proofing or safety switching of small equipment including security equipment such as sensors and for switching scale models and any other miniaturised equipment.



The switch weighs 0.3gm, and is possibly an example of unusually advanced technology, as according to SSI's new release it has a 300mA single pole changeover, which is probably enough to handle the entire national grid. Anyone intending to use it for 300mA applications, however, is probably safe to go ahead without making further enquiries as to specification! The price is £4.00 for ten, p&p inclusive.

Orders and enquiries to **Semiconductor Supplies, 128/130 Carshalton Rd., Sutton, Surrey SM1 4RS**. Tel: 01 643 1126.

Portable Test Gear


Professional test equipment from **Thandar Electronics Ltd.**; the TG101 is a mains-operated **function generator** working from 0.02Hz to 200Hz.

The frequency is selectable via a five-position range switch and a calibrated vernier, or by the sweep input which enables the generator frequency to be adjusted via an external control voltage. Both vernier and sweep input can give more than 1000:1 frequency change within the selected range. A typical external sweep range is 10,000:1.

A variable output of 600R is controlled over a range of more than 80dB up to a maximum of 10V peak to peak via a single vernier plus two position switched attenuator. The DC offset is switch selectable and the vernier provides adjustment of up to ±5V from 6000R.

Square, sine, triangle and the DC waveforms can be selected, and a TTL output is provided. The unit measures 255 x 150 x 50mm in its ABS case and weighs 1200 gms. It will operate from a 50/60Hz supply of 100-120VAC or 200-240VAC. Price is £99 plus VAT.

MONITOR

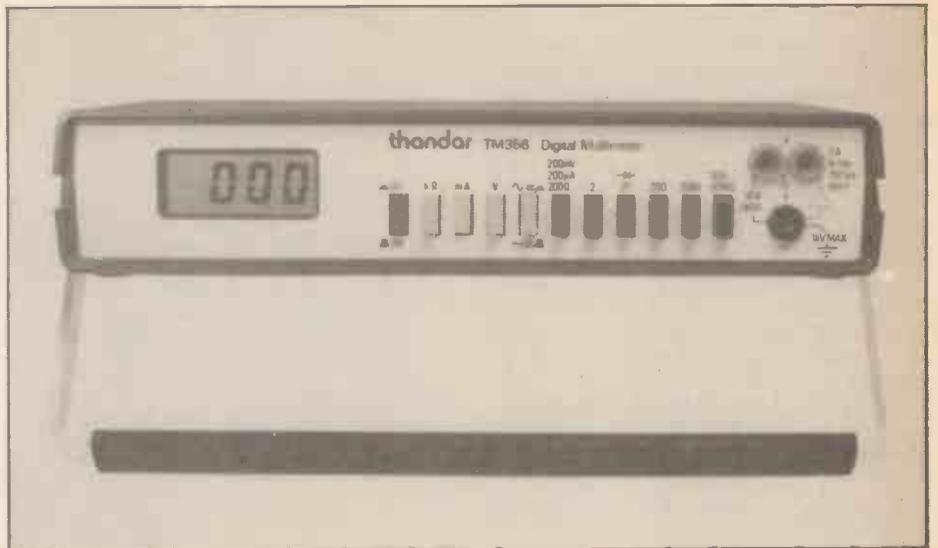

The TM356 is a battery-operated lab multimeter. With twenty nine ranges it can measure voltage from 100uV-1000V (750VAC), current from 100nA-10A and resistance from 100mR to 20MR. Battery life from alkaline 'C' cells is over 3000 hours, and a low-battery indicator shows when 10% battery life remains. The ABS case has a handle and stand for portable and bench use, and the weight is 1200gm with full batteries. The price is £85 plus VAT.

A video head tester, priced at £45 plus VAT, is available in two models, the KNC-909V (for VHS) and LHC-909B (for Betamax) is also available to measure the wear in VCR-heads.

For further information about any of these, contact Thandar Electronics Ltd., London Rd., St. Ives, Huntingdon, Cambs PE17 4HJ. Tel: (0480) 64646.

New For Glue

A new heater called the PTC (Positive Temperature Co-efficient) means that an operating temperature is maintained without a thermostat. This is the new technology incorporated in **Beta Fastening Systems'** latest addition to their range of four hot-melt glue applicators — a new baby, the **BeA Hotfix 180** which brings instant bonding to most materials.

Operating on a 100-240V power supply, it can be used within three or four minutes of being plugged in. By simply feeding glue sticks into the back of the tool and squeezing the trigger, application of hot-melt glue becomes easy, quick and accurate. The adhesive not only bonds, but seals, insulates, fills and reinforces. There is a range of nozzles for the machine and a variety of

glues for different materials. The Hotfix 180 is double insulated, has a power warning light, and a fully enclosed heater housing. The clip-on stand provides stability.

The price is £16.95 plus VAT. Enquiries about the range to **BeA Fastening Systems Ltd.**, Swinemoor Industrial Estate, Beverley, Humberside HU17 0LA. Tel: (0482) 861075.

Clean Screen

The introduction of anti-glare filters, manufactured from nylon or such material and in the form of a very fine mesh to defuse reflected light from VDU screens is an excellent idea but one that presents a cleaning job. These filters, manufactured from man made fibres, are now being fitted in contact with the glass VDU screen which accentuates the build up of static. This fine mesh becomes clogged with contaminants, making the screen even more difficult to see.

If water only is used, some of the water penetrates the filter and deposits water marks and contaminants on the screen. There is also the risk of water running down the front of the filter and seeping into the surrounding cabinet. The new 'Data Care' product Anti Static Screen Cleaner is a specially prepared formula of solvents, with anti-static properties, and is used in such a way as to remove contaminants from meshed surfaces.

Anti-Static Screen Cleaner is available in 340g/400mls aerosols or in kit form, incorporating an anti-static foam cleaner, anti-static screen cleaner and one hundred lint free wipes. To control static build-up, keep filter/screen in good condition and for general cleaning of hard surfaces found in a computer environment.

More information from **Sapona Chemicals Ltd.**, 46-50 Upper Dean St. Birmingham B5 4SG. Tel: 021-622 6442.



MONITOR

Culture Club

The autumn issue of the **British Amateur Electronics Club's** newsletter is mostly taken up with part four of their series by C. Roper, *Electronics A-Z*, which covers Resistor/Capacitor circuits, AC circuits, series circuits and many permutations. There is also the usual letters page and *Notes From An Experimenter's Workshop* by H. F. Howard.

The Winter issue should appear in January. The BAEC, apart from its newsletter provides a loan library of electronics books and periodicals, an annual exhibition, and various other membership benefits. Membership for UK and Eire members is £5.50, overseas surface mail is £7.00, all European memberships £6.00, and other airmail memberships £8.50. Memberships run from January 1st to January 1st, and members receive all the newsletters for the year they join regardless of which month they join in.

Chairman and editor Cyril Bogod and his helpers were much in evidence at **Breadboard** this year. Keep up the good work, chaps. Subscriptions and enquiries should go to the **Chairman, Mr. Cyril Bogod, "Dickens", 26 Forest Rd., Penarth, S. Glam CF6 2DP.**

I Have Seen The Future Of Television, But They Won't Let Me Near It.

We can look forward, in the as-yet-unscheduled future, to being able to watch two television programmes on one screen: either a step closer to heaven or the ultimate horrorshow, depending on what your attitude to television is. Remembering early catfights around the subject of whether we were going to watch *Match Of The Day* or *The Old Grey Whistle Test*, I veer towards the former opinion. At least then you can see what you're fighting about.

The machine in question is a 'new multifunctional digital TV' by Matsushita of Japan, the people who market under the name **National Panasonic** in the UK. By 'multifunctional', they mean



that it's a member of the modern generation which can accommodate teletext, viewdata, video equipment, hifi and all the rest.

The 'second screen' is a digitally processed 6in colour picture which can be inserted in the main 20in screen (see picture). The TV has its own CPU and, being digital, boasts 'crisper, cleaner images due to the reduction of spots, screen flickering and colour saturation which exist in analogue sets'. Panasonic also say that the set has 30% fewer components than the normal analogue set, which increases reliability and reduces cost. As we have no prices to compare, it remains to be seen whether the reduction in cost will be actually or purely relative.

The infra-red remote controller controls sixty-one functions, including both the picture qualities (brightness, saturation etc) of the television, and any other equipment hooked up to it, and, since the control signal is generated by an 11 bit digital system, it is, they say theoretically capable of controlling up to 2,048 functions.

The development of the household television into the home information centre of the future seems to be well under way, though it is still a minority of houses that have teletext, home computers and VCRs, let alone use them for anything more solemn than light entertainment. Mind you, my mother-in-law gave my granda two winners which she saw tipped on the teletext while she was setting up the VCR for Christmas... a few more like that and she'll have covered the cost of the television. Be that as it may, I still remain sceptical that you can afford to budget for more than two people squabbling over the TV (let's be modern and call it a *monitor*) screen at one time. If we're going to have a VCR, video player and a video camera hooked up to the telly, then the games console and the home computer will have to go in the other room with their own monitor, the


hifi will have to go in the cellar or the attic, and we can soundproof the lot while we're about it. Alternatively, the lounge can be fitted out with individual booths for all the family...

So why can't we have the two-screen television right away? If Panasonic don't move soon, every household will have a second telly, or even a third telly, and we won't need one which shows two progs at once. Maybe it's happened already... everyone I know seems to be rescuing discarded black and whites off rubbish tips. We're still looking for a VCR, but no luck yet...

For people who can't afford (or face) even one full-sized TV screen, let alone two in one. Matsushita are also developing a portable 6½in rear-projection colour TV which folds down into an attache case weighing 3kg and measuring 25 x 8.5 x 31cm, about half the size and weight of a normal 7in screen TV, uses 12W and can be used as a monitor for other video equipment. Ideal for closet TV addicts, but you can't fold it in half and put it in your back pocket, or scribble addresses on it, so don't expect multifunctional, digital (all typed by hand) HE to go teletext in the near future.


Feel The Heat

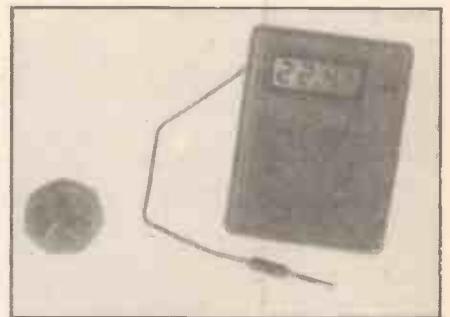Electronic Temperature Instruments have introduced a new all electronic miniature multi purpose thermometer. The Thermotron has two unique features, price and size. At £24.95 it is half the price of the majority of its competitors, and measures up at 82 x 63 x 23mm.



This electronic instrument is an alternative to the glass thermometer for both liquid and air temperature measurement. Its advantages include its easy to read liquid crystal display, long battery life and its waterproof and non corroding sensor. The high impact ABS case is supplied complete with built in wall mounting bracket and table top stand making it truly versatile. This high precision electronic thermometer can measure 0-99°C with an accuracy of 0.1°C.

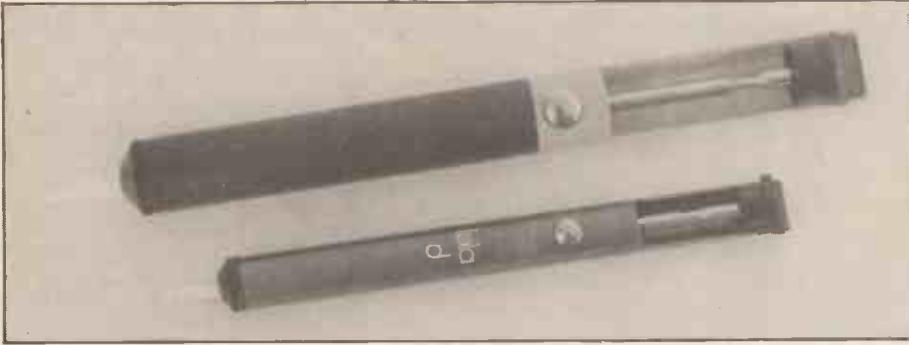The Thermotron is particularly well suited for measuring the exact temperatures of air, liquids and semi solids.



For further information and leaflet please contact **ETI, Highdown Avenue, Worthing, Sussex. Tel: (0903) 692161.**

What? another ETI? Can there be two?

Measure And Dismantle

A pocket-sized **Digital Thermometer** with $\pm 0.1^\circ\text{C}$ accuracy over a temperature range from -200 to $+800^\circ\text{C}$, the Ancom BLR-800 is currently available from **Electronic & Computer Workshop Ltd.** The thermometer offers a one $^\circ\text{C}$, resolution, repeatability and a stability figure of 0.01°C per $^\circ\text{C}$, with a wide range of standard platinum RDT temperature sensor probes. These include air temperature, liquid immersion, surface temperature, hypodermic insertion and fast response types. The sensors are available with conformity to British and DIN standards in grades, A, B, C, D and E and are connected to the instrument by a three-way plug/socket.

The BLR-800 uses a lower power $3\frac{1}{2}$ digit LCD for data display, which also displays a low battery sign. The internal battery will give over 200 hours continuous operation and accuracy is not affected by battery condition. The BLR-800 measures $90 \times 145 \times 28\text{mm}$ and has a single on/off switch. Calibration is carried out by the user, with boiling water and melting ice references, plus screwdriver adjustments.

The Pantec Major 20K, a general purpose **Multimeter**, has a sensitivity of $20\text{k}\Omega/\text{VDC}$ and $4\text{k}\Omega/\text{VDC}$, with a DC voltage range of 0.15 to 1500V and AC from 7.5 to 1500V . Current measurements range from $50\mu\text{A}$ to 2.5ADC and 2.5 to 12.5 AC . Resistance can be measured from 0.5R to 2MR in four ranges, with ballistic capacitance in the range 100 - $1,000\mu\text{f}$ to 10 - 100mf . The multimeter has a 2% accuracy for DC and resistance measurements and 3% for AC.

Full protection is provided with a quick-blow fuse, diode system and neon discharger, and the meter comes with shock-proof case and spare fuse. The Major 20k weighs 600g and dimensions are $130 \times 125 \times 40\text{mm}$.

Effective **de-soldering guns** in standard and miniature sizes are currently available. The standard gun is 19mm in diameter, 220mm long and the

miniature version has a 14mm diameter and is 165mm long. Both guns can be purchased for $\pounds 5.25$ each (plus VAT and P&P).

The guns can be operated with one hand. Used in conjunction with any standard soldering iron the de-soldering operation is simple — the gun is 'charged' by depressing the spring load plunger. On pressing the release button, molten solder is drawn up into the gun where it solidifies.

For further information please contact **Electronic & Computer Workshop Ltd., 171 Broomfield Rd., Chelmsford, Essex CM1 1RY. Tel: (0245) 262149.**

Relay The Message

A low-cost easy-to-use relay board is now available for ZX Spectrum users from **Ness Micro Systems.**

The NMS Relay Controller has four channels each of which has a double pole 5A relay rated at 1kW and 240V AC or 100W at 25V DC and with screw-terminal connections to the relays. Unlike other relay boards it plugs into the Spectrums MIC socket leaving the expansion port free and is powered from the Spectrum supply. The controller is extremely easy to use as any of the four relays may be turned on or off by means of a simple BEEP command, either from within a program or direct from the keyboard. Each relay has an on/off LED indicator.

The board is supplied built into a black plastic case measuring $180 \times 110 \times 55\text{mm}$ together with 1m leads. The controllers may be daisy-chained so that more than one may be operated under the control of one Spectrum.

The NMS Relay Controller is available from **Ness Micro Systems, 100 Drakies Avenue, Inverness IV2 3SD** and costs $\pounds 24.95$ plus $\pounds 1.50$ post and packing.

Big Cat Free

A new electronic hardware catalogue, from **Supercat Electronics Ltd.**, came out in January and is free of charge. There will be a Summer edition later in the year.

Supercat say that the catalogue is

aimed at hobbyists, educational and small industrial users, as well as general industry and research, and the first issue includes test equipment, power supplies, signal sources, meters, kits, connectors, leads and accessories.

Contact **Supercat at PO Box 201, St. Albans, Herts AL1 4FN. Tel: (0727) 62171**, giving your full name and address, and stating whether a business or private user, they say.

Aerial Meter

Not as cheap or simple as our recent HE project, but of possible interest to radio clubs, is **House Of Instruments' TC40**, a field strength meter, from Sadelta, designed to measure the performance of aerials and indicating the prime position for installation.

Aerial signals normally fed to TV or FM receivers are passed to the TC40's 75R coaxial type input connector, where coarse and fine tuning controls give complete and accurate cover over Band I TV 45 to 88MHz , Band II FM 87 to 108MHz , Band III TV 163 to 230MHz and Bands IV and V TV 470 to 862MHz .

Seven level measuring ranges from 100 microvolts full scale to 100 millivolts full scale give accurate indication of on RMS voltage and dB/microvolt calibrated scales, allowing measurement down to 20 microvolt (26dB/microvolt). Audio monitoring of AM and FM is available via an internal detector, amplifier and loudspeaker. An Ohms range, complete with probes, is also fitted for continuity and short circuit tests.

This ultra compact, light field strength meter is fully portable with power being supplied by two internal 4V5 batteries and comes complete with carrying case and accessories. Ideal for applications, say the manufacturers, are for TV and Radio Technicians specialising in aerial installation and alignment, who need one complete reliable portable unit. The UK list price is $\pounds 177$ plus packaging, delivery and VAT.

For further information, please contact **Fred Hutchinson at hil, tel: (0799) 24922**, or write to **Quiswood Ltd., 30 Lancaster Road, St. Albans, Herts AL1 4ET.** A leaflet is available.



BI-PAK BARGAINS

BI-PAK SOLDER - DESOLDER KIT

Kit comprises: ORDER NO. VP80
 1 High Quality 25 watt General Purpose Lightweight Soldering Iron
 240v mains incl 3/16" (4.7mm) bit.
 1 Quality Desoldering Pump High Suction with automatic ejection Knurled anti-corrosive casing and Teflon nozzle
 1.5 metres of De-Soldering braid on plastic dispenser
 2 yds (1.83m) Resin Cored Solder on Card
 1 Heat Shunt tool tweezer Type
 Total Retail Value over £12.00
OUR SPECIAL KIT PRICE £9.95



BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
 1 Expo Mini Drill 10,000RPM 12v DC incl 3 collets & 3 x Twist Bits
 1 Sheet PCB Transfers 210mm x 150mm
 1 Etch Resist Pen
 1 1/2 pack FERRIC CHLORIDE crystals
 3 sheets copper clad board
 2 sheets Fibreglass copper clad board
 Full instructions for making your own PCB boards
 Retail Value over £15.00
OUR BI-PAK SPECIAL KIT PRICE £9.95
 ORDER NO. VP81



DIGITAL VOLT METER MODULE

3 x 7 segment displays Basic Circuit 0-2v± instructions provided to extend voltage & current ranges. Operating voltage 9/12v. Typ. Power Consumption 50mA
 O/No. VP99 Once only price
£9.95

SINGLE SIDED FIBREGLASS BOARD


Order No	Pieces	Size	Sq. Ins	Price
FB1	4	9 x 2 1/2"	100	£1.50
FB2	3	11 x 3"	100	£1.50
FB3	4	13 x 3"	156	£2.00

DOUBLE SIDED FIBREGLASS BOARD

FB4	2	14 x 4"	110	£2.00
-----	---	---------	-----	-------

SILICON BRIDGE RECTIFIERS

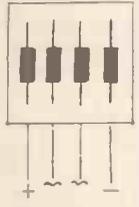Comprising 4 x 1 1/2 Amp rectifiers mounted on PCB. VRM - 150 vits IFM - 1.5 Amps
 Size: 1 inch square
 10 off £1.00
 50 off £4.50
 100 off £7.50
 ORDER NO: 4R1 B Rect.



INTRUSION ALARM

The DOOR BIRD DB 2000 alerts you before your door is opened. Just hang on the inside door knob - alarm is activated as soon as the outside door knob is touched.
ONLY £3.95



OPTO 7-Segment Displays

Brand new 1st Quality LITRONIX DL 707R 14-pin
 Red 0.3" Common Anode Display 0-9 with right hand decimal point TTL compatible 5v DC Supply. Data supplied

IN	5 pieces	£3	(60p each)
PACKS	10 pieces	£5	(50p each)
OF	50 pieces	£20	(40p each)
	100 pieces	£35	(35p each)
	1,000 pieces	£300	(30p each)

THE MORE YOU BUY - THE LESS YOU PAY

TECASBOTY

THE ELECTRONIC COMPONENTS AND SEMICONDUCTOR BARGAIN OF THE YEAR!

This collection of Components and Semiconductors for the hobbyist is probably the most value-packed selection ever offered, it consists of Resistors, carbon and wirewound of various values. Capacitors: All types, sorts and sizes including electrolytics. Potentiometers - single, dual, slider and preset. Switches, Fuses, Heatsinks, Wire, P.C.B. Board, Plugs, Sockets etc., PLUS a selection of Semiconductors for everyday use in popular Hobby Projects. These include: SCR's, Diodes, Rectifiers, Triacs & Bridges as well as a first class mix of Transistors and I.C.'s. In all, we estimate the value of this in current retail catalogues to be over £25! So, help yourself to a great surprise and order a Box TODAY for just £6.50 ONLY at BI-PAK. Remember, stocks are limited so hurry! You can call us on 0920-3182/3412 and order with your Barclaycard or Access Card - 24hrs. Answerphone Service NOW. Order No. V.P. 85.

OUR GREAT NEW CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices. There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

We hold vast stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock. The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

To receive your NEW 1983 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-

BI-PAK

Send your orders to Dept HE3 BI-PAK PO BOX 6 WARE, HERTS
 SHOP AT 3 BALDOCK ST, WARE, HERTS
 TERMS CASH WITH ORDER. SAME DAY DESPATCH ACCESS
 BARCLAYCARD ALSO ACCEPTED TEL (0920) 3182 GIRO 388 7006
 ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING

VALUE PACKS

Pak No.	Qty	Description	Price
VP1	300	Assorted Resistors Mixed Types	£1.00
VP2	300	Carbon Resistors 1/2 Watt Pre-Formed	£1.00
VP3	200		
VP4	150	1/2 Watt Resistors 100 ohm-1M Mixed	£1.00
VP5	200	Assorted Capacitors All Types	£1.00
VP6	200	Ceramic Caps Miniature - Mixed	£1.00
VP7	100	Mixed Ceramic Disc. 1pf - 56pf	£1.00
VP8	100	Mixed Ceramic Disc. 68pf - .015pf	£1.00
VP9	100	Assorted Polyester/Polystyrene Caps	£1.00
VP10	60	C280 Type Caps Metal Foil Mixed	£1.00
VP11	100	Electrolytics - All Sorts	£1.00
VP12	60	Beard Type Polystyrene Min Caps	£1.00
VP13	50	Silver Mica Caps Ass. 5.6pf - 150pf	£1.00
VP14	50	Silver Mica Caps Ass. 180pf - 4700pf	£1.00
VP15	50	High Voltage Disc. Ceramic 750v - 8Kv Mixed	£1.00
VP16	50	Wirewound Res. 9W (avg) Ass. 1 ohm - 12K	£1.00
VP17	50	Metres PVC Covered Single Strand Wire Mixed Colours	£1.00
VP18	30	Metres PVC Covered Multi Strand Wire Mixed Colours	£1.00
VP19	40	Metres PVC Single/Multi Strand Hook-Up Wire Mixed	£1.00
VP20	6	Resistor Switches 5 Amp 240v	£1.00
VP21	20	Pcs. 1 - 2 & 4 mm Plugs & Sockets Matching Sizes	£1.00
VP22	200	Sq. Inches Total, Copper Clad Board Mixed Sizes	£1.00
VP23	20	Assorted Slider Pots. Mixed Values	£1.00
VP24	10	Slider Pots. 40 mm 22K 5 x Log. 5 x Lin	£1.00
VP25	10	Slider Pots. 40 mm 47K 5 x Log. 5 x Lin	£1.00
VP26	20	Small .125" Red LED'S	£1.00
VP27	20	Large 2" Red LED'S	£1.00
VP28	10	Rectangular 2" Green LED'S	£1.00
VP29	30	Ass. Zener Diodes 250mW - 2W Mixed Vits. Coded	£1.00
VP30	10	Ass. 10W Zener Diodes Mixed Vits. Coded	£1.00
VP31	10	5 Amp SCR's T0-66 50-400v Coded	£1.00
VP32	20	3 Amp SCR's T0-66 Up To 400v Uncoded	£1.00
VP33	200	Sil. Diodes Switching Like IN4148 DO-35	£1.00
VP34	200	Sil. Diodes Gen. Purpose Like 0A200/BAX13 16	£1.00
VP35	50	1 Amp IN4000 Series Sil. Diodes Uncoded All Good	£1.00
VP36	8	Bridge Rects. 4 x 1 Amp 4 x 2 Amp Mixed Vits. Coded	£1.00
VP37	8	Black Instrument Type Knobs With Pointer 1/2" Std	£1.00
VP42	10	Black Heatsinks To Fit T0-3, T0-220 Ready Drilled	£1.00
VP43	4	Power-Fin Heatsinks 2 x T0-3 2 x T0-66 Size	£1.00

SEMICONDUCTORS FROM AROUND THE WORLD

100 A collection of Transistors, Diodes, Rectifiers & Bridges SCR's, Triacs, I.C.'s & Opto's all of which are current every-day useable devices.
 Guaranteed Value Over £10 Normal Retail Price.
 Data etc in every pack. Order No. VP56
 Our Price £4.00

BI-PAK'S OPTO SPECIAL

A selection of large and small sized LED's in various shapes, sizes & colours, together with 7 Segment Displays both anode & cathode plus photo transistors emitters and detectors. Cadmium Cell ORP12 and Germ. photo transistor OCP71 included. In all a total of 25 Opto pieces valued over £12 Normal Price
 Order No. VP57
 Our Super Value
 Price Just
£5.00

HYBRID LED COLOUR DISPLAYS



Red, Green, Yellow - .3/.5/.6 inch Mixed types and colours NUMERIC & OVER-FLOW Common Anode/Cathode. GaAsP/GaP. Brand New, Full Data incl.

10 pieces (our mix) ..£4.00
 Normal Retail Value Over £10.00
 Order No. VP58

TRANSISTOR CLEARANCE

All Sorts Transistors. A mixed Bag NPN-PNP Silicon & Germ. Mainly Uncoded You 100 To Sort Pack includes Instructions For Making Simple Transistor Tester. Super Value. Order No. VP60 **£1.00**

POWER SUPPLY OUR PRICE £3.25

Power supply fits directly into 13 amp socket Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug Input - 240V AC 50HZ, Output - 3, 4, 5, 6, 7.5, 9 & 12V DC Rating - 300 ma MW88.

MULTITESTERS

1,000 ohm Including test leads b Battery
 AC volts - 0-15-150-500-1,000
 DC volts - 0-15-150-500-1,000
 DC currents - 0-1ma-150ma
 Resistance - 0-25 K ohms 100 K ohms
 Dims - 90 x 61 x 30mm
 O/No. 1322. OUR PRICE £6.50 ONLY

ELECTRONIC SIREN

12v DC



Red plastic case with adjustable fixing bracket. Emits high-pitched wailing note of varying pitch - 100 cycles per minute. Dims - 90mm (dia) 60mm (depth). Power - 12v DC.
 Our Price: **£5.50**

IC BARGAINS

VP40 30 Assorted 74 Series TTL I.C.'s Gates, Flip-Flops & M.S.I.'s + Data Book. All New. Normal Retail Value Over £6.00. Our price **£2.50**
 VP41. 30 Assorted CMOS I.C.'s CD4000 Series. Pack includes 00/09/12/14/18/21/23/25/28/30/35/44/68 AY/TE Types Plus Data Sheet Value Over £9.00. Normal retail **£2.50**
 YOU MAY ORDER any ONE TYPE of the above CMOS at £2.00 per 25 pieces ORDER AS VP41 + type number required.

RATCHET SCREWDRIVER KIT

Comprises 2 standard screwdriver blades 5 & 7mm size, 2 cross point size 4 & 6. 1 Ratchet handle. 5-in-1 KR. £1.45 each. O/No 3298

REGULATED VARIABLE Stabilised POWER SUPPLY

Variable from 2.30 volts and 0.2 Amps Kit includes -
 1 - VPS30 Module, 1 - 25 volt 2 amp transformer,
 1 - 0.50v 2" Panel Meter, 1 - 0.2 amp 2" Panel Meter,
 1 - 470 ohm wirewound potentiometer, 1 - 4K7 ohm wirewound potentiometer. Wiring Diagram included. Order No. VPS30 KIT **£20**

MINIATURE FM TRANSMITTER

Freq: 95-106MHz. Range: 1/2 mile
 Size: 45 x 20mm. Add: 9v batt. **ONLY £5.50**
 Not licenced in UK.
 Ideal for: 007-M15-FBI-CIA-KGB etc.

Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total Postage add 75p per Total order.


Offbeat Metronome

Andrew Armstrong

A very basic rhythm box for musical practice and improvisation, with a tuning device built in.



Figure 1. The block diagram of the Offbeat Metronome.

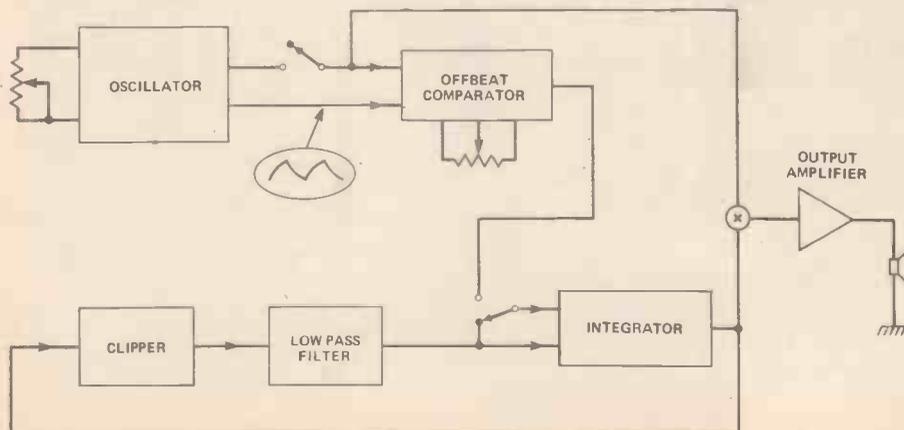

THIS is a metronome with a difference. The initial requirement was for a simple metronome which would enable the musician or musicians to practice playing to an even rhythm, instead of succumbing to the inevitable temptation to play faster and faster until collapse from exhaustion ensues. The project became more ambitious when we decided to add a rhythm accent or offbeat to give a variety of rhythm 'feels' to play against. What was wanted, obviously, was a very simple substitute for a drummer. After all, drummers are usually very simple, aren't they?

The other primary motive was to devise an electronic rhythm box which cost less than the £60 or so demanded for even the cheapest commercial device.

The required variable offbeat was achieved by inserting another note between the regular beats, which can be adjusted to fall anywhere between the two beats, or in unison with one beat to give a stronger accent on that beat, or not to occur at all.

The final embellishment was the addition of a pure "A" tone for tuning purposes.

So the owner of the offbeat metronome has no excuse for being either out of time or out of tune!

Offbeat Circuits

Figure 1 shows the basic functional blocks of the circuit. The oscillator on the top left is one that may be used in any simple metronome project. Next to it is drawn an offbeat comparator block. This is specially designed to add an extra beat between the *tock* and *tick*, so that, with the offbeat, the sound is something like *tick - bok - tock, tick - bok - tock*.

Offbeat Metronome

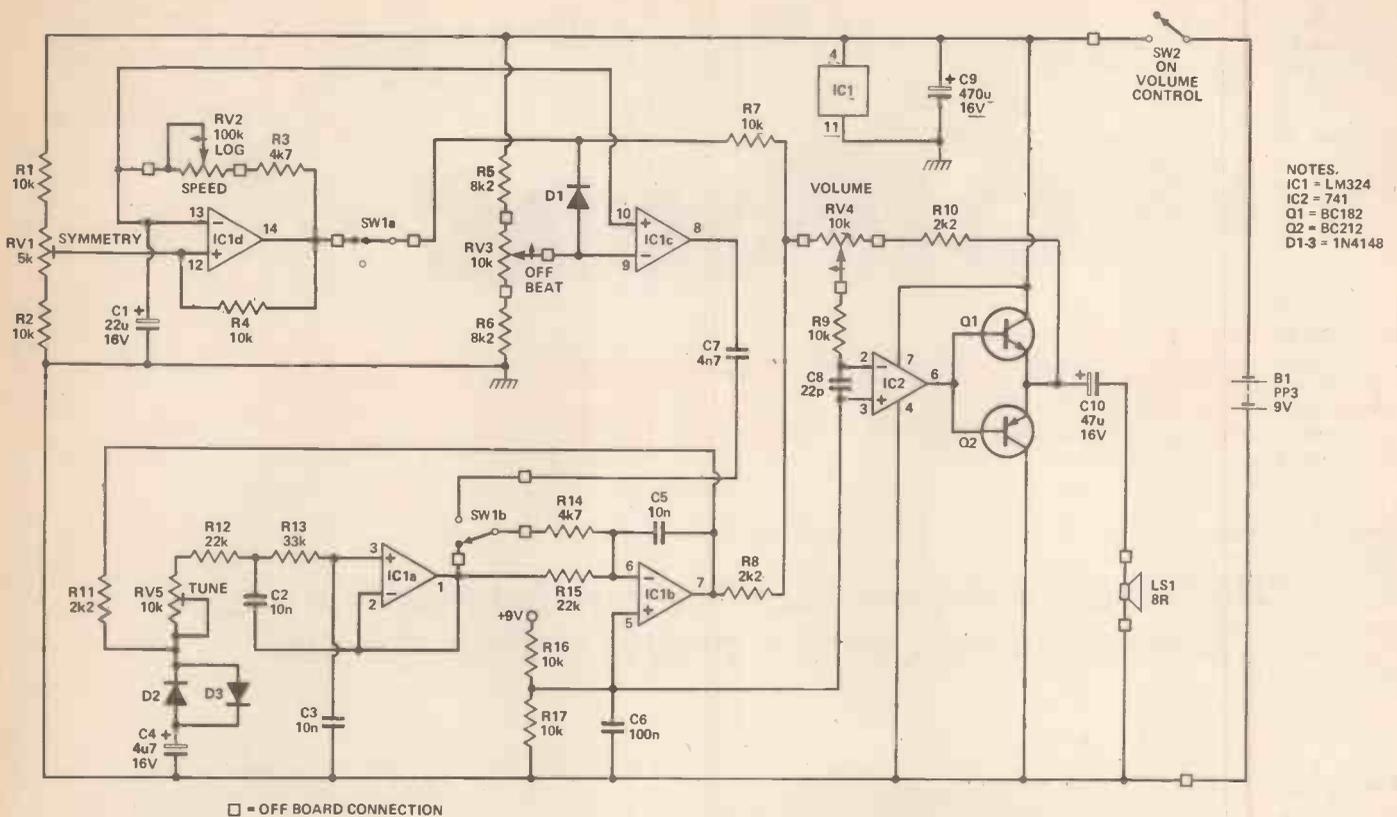


Figure 2. The circuit. The tuning oscillator also modifies the sound from the offbeat comparator.

In order to have a tuning aid available, an accurate sine wave oscillator is included, with the aid of the mode switch the oscillator can be stopped from oscillating and instead used to provide a slightly resonant sound on the signal from the offbeat comparator.

frequency.

So that the filter and the integrator can function without clipping, the feedback is taken via a clipper. The distortion produced by the clipper is filtered out by both the filter and the integrator, so that as long as neither the filter nor the integrator themselves clip, the output sinewave is very pure. Similarly, because the circuit is working in a linear mode,

the frequency is stable and little affected by battery voltage.

IC1a (see Figure 2) forms the filter, which is a very ordinary low pass design, and IC1b forms the integrator. The clipping action is performed by a pair of back to back diodes, D2 and D3, with capacitor C4 preventing DC current through the diodes from upsetting the bias point of the op-amps.

Pull And Twist

The controls (see photograph) are a pot governing the speed of the main rhythm, a small switch which pulls to turn the unit on, and rotates to control the volume; the pot which alters the relative position of the offbeat, and a two position switch which selects either the metronome or the "A" tone. The pull switch for on/off was chosen on the basis that pull switches don't wear out so fast as rotary switches with continual use, but an ordinary rotary on/off pot will do just as well.

First of all, the detailed functioning of the tuning oscillator: in order for a circuit to oscillate, it must receive feedback to its input with a phase shift on it such that the phase change round the entire loop is 360 degrees. In this circuit the 360° phase shift is achieved by one inversion and two 90° phase shifts. The integrator provides both the inversion and 90° phase shift over a wide range of frequencies. The low pass filter has a phase shift which depends on frequency, so it will only provide a 90° phase shift at one specific



Figure 3. The waveform diagram. The symmetry pot is included to compensate for the unequal positive/negative swing of the metronome signal.

Figure 4. The waveform at the output of IC2 (a 741) as it compensates for distortion produced by the transistors Q1 and 2.

The gain of the integrator is switched by switch SW1b. In the low gain position, where some signal is fed into the integrator from the offbeat comparator, the loop gain of the oscillator is insufficient to permit oscillation to occur. However, when the circuit is excited by a sharp pulse, it will ring slightly, producing a somewhat hollow and resonant sound rather like striking a guitar body. In the metronome mode this resonant sound is mixed with the basic metronome tone. Resistors R7 and R8 determine the proportion of signals used.

Time Constant



The metronome oscillator itself uses IC1d. Positive feedback is applied to the op-amp: negative feedback is also applied, delayed by the time constant of C1 and the resistance of RV2 in series with R3.

The time per half cycle of the oscillator is set by the time required for C1 to charge between the voltages which can be obtained on the positive terminal of IC1d, with the output in either of its two states.

This is shown on the waveform diagram, **Figure 3**. Also illustrated on the waveform diagram is the fact that the output stage of the IC used, an LM324, cannot pull equally as close to its positive power supply as to its negative power supply. Thus, in order to maintain symmetry to keep each half cycle of the oscillator the same length, a symmetry adjustment pot has been incorporated.

The waveform on C1 is also fed to IC1c's positive input. This part of the IC works as a comparator to insert the offbeat. When the output of IC1d is high, and C1 is therefore charging towards a positive voltage, and when the voltage on C1 crosses over the voltage set by the offset pot, the output of IC1c switches in a positive direction.

If the offbeat pot is set to a high voltage, so that this switching does not occur before the output of IC1d switches low, then the output of IC1c will switch high at this moment. If the output of IC1c has switched high at all, it will switch low at the same moment that the output of IC1d switches high. Thus, the return stroke of this comparator does not insert an extra offbeat, it merely modifies the sound of the tick slightly. If the offbeat comparator is set at a lower voltage than that attained by C1, then the

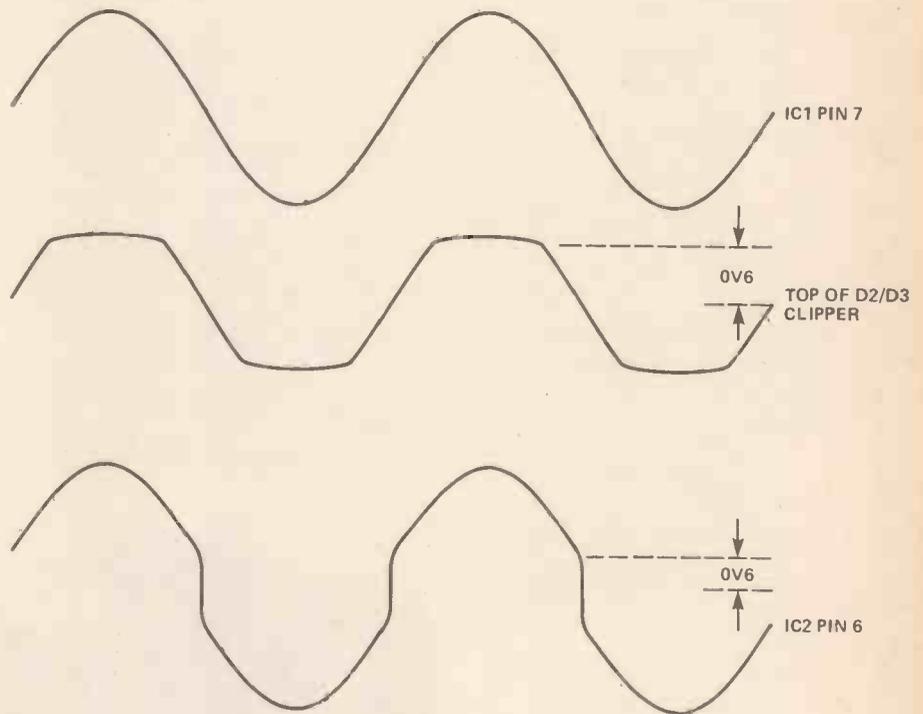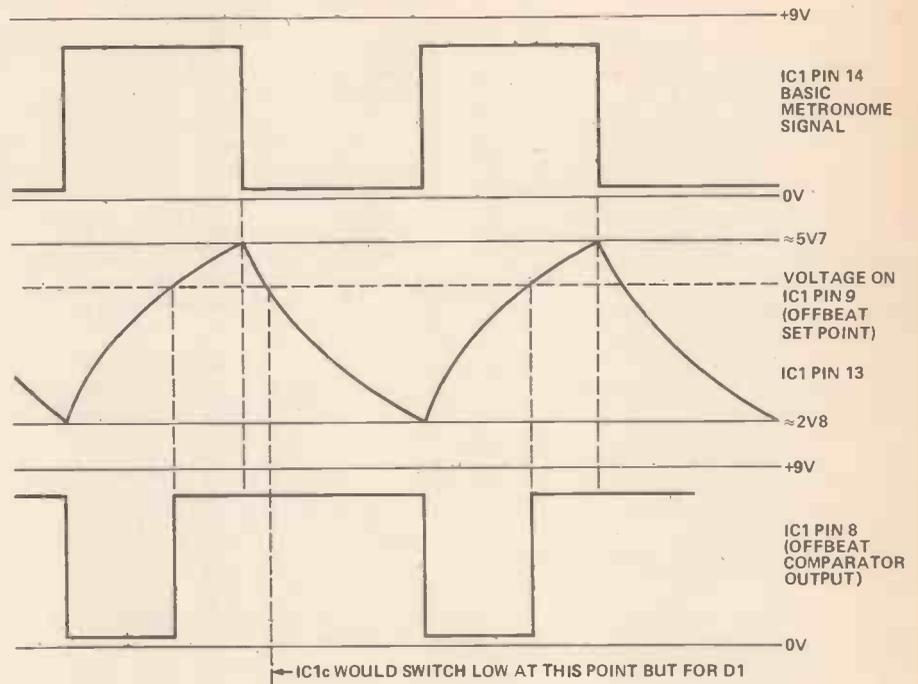

offbeat comparator will not switch at all, and in this mode an unaccented metronome sound is produced.

Output Amplifier

The only part of the circuit not yet described is the output amplifier. This very simple circuit uses a complimentary pair of transistors as emitter followers to increase the output drive available from a 741 op-amp. These transistors are not biased into class A/B, so a certain amount of distortion is produced on the output. This distortion is not significant for the use

to which the circuit is put. However, it does give rise to an interesting waveform on the output of the 741 itself, as the output voltage frantically attempts to compensate for the distortion being introduced by the transistors (see **Figure 4**). As a result of this, the distortion produced is not very severe.

The volume control is of a linear type, and the way in which it is used produces an acceptable control law. Resistors R9 and capacitor C8 are included to prevent the possibility of self oscillation of the circuit due to stray capacitance of the output stage causing pickup on the wire from the wiper of RV4.

Construction

First of all, build up the PCB as shown in Figure 5, inserting the ICs last. Connect the controls to the PCB using suitable lengths of wire. Take great care to make sure that both halves of the mode switch are wired up in the correct sense. Failure to do so could result in the metronome and the tuning note being heard simultaneously! Note that the speed control of the metronome is a logarithmic pot, wired up so that anticlockwise rotation increases the speed. This is done in order to give finer control at the higher speeds.

Once all the controls are connected up, the battery should be connected. Care should be taken to ensure that the polarity is correct! The unit should then be switched on, and then either

a metronome beat or a tuning note should be heard. If the unit does not work properly, first of all check for badly soldered joints or solder bridges. If no such problems are found, but the unit still does not work correctly, then try this list of remedies for likely problems:

1. Metronome does not work at all: check connections to RV2; check that C1 is in the board the right way round; check that the wiring to switch SW1a is correct.
2. Metronome works but offbeat function does not: check connections to RV3; check polarity of D1; check wiring to switch SW1b.
3. Tuning note will not work: check connections to switch SW1c; check polarity of C4; also check polarity of D2 and D3; check that about half the battery voltage can be measured with an ordinary multimeter on IC1 pin 5; if not, check the *bias voltage track* for short circuits.
4. No sound is heard at all: check wiring to battery and switch SW2; check wiring to RV4; check wiring to loudspeaker.

Hopefully, having carried out the checks, any fault will be identified, and you will now be faced with a working unit. The next job is to adjust the symmetry control to make sure that the time between the *tick* and the *tock* and the *tick* on the metronome is the same.

First, set the offbeat control fully clockwise or fully anticlockwise, so that the offbeat is not heard. If you have an oscilloscope, then connect the probe to IC1 pin 14, advance RV2 to maximum speed and temporarily connect a 1k resistor in parallel with R3. You should now see on the oscilloscope a fast squarewave, and this can be adjusted visually by

turning the symmetry pot. If an oscilloscope is not available, then instead turn the speed control to minimum and time the operation of the metronome with the second hand of a watch or the second count of a digital watch and adjust the symmetry pot for equal timings.

Now it is necessary to set the tuning tone. Switch to the "tune" mode, and the tone should be heard. If a frequency counter is available then the note can very easily be adjusted to 440Hz (concert pitch A). If a frequency counter is not available it will be necessary to borrow a tuning fork or to use a musical instrument known to be in tune.

Adjust the tune preset pot till a "zero beat" is heard. It may be that the tone cannot be calibrated due to tolerances of C2 and C3. In this case, R13 should be altered to bring the oscillator to within the correct range. If the frequency was too low, decrease R13 one step at a time. If the frequency was too high, increase R13, again, one E12 step at a time.

The unit is now calibrated, and final assembly can be carried out. A row of four holes needs to be drilled in the front of the case to fit the potentiometers. Four holes should also be drilled in the base of the unit, to fit the mounting bolts of the PC board. The loudspeaker should be mounted on the lid behind a grid of holes, drilled to let the sound out. The best way to make sure that the holes are neatly laid out is to lightly centre-punch the material of the lid through a piece of graph paper: 2.5 or 3mm holes should be suitable.

The loudspeaker is retained in the case by means of two M3 nuts and bolts, fitted with oversize washers, to overlap the rim of the loudspeaker. The convenient way to mount the PP3 battery is to use a couple of double

Parts List

RESISTORS

(All 1/4 watt 5% carbon)

R1, 2, 4, 7, 9, 16, 17	10k
R3, 14	4k7
R5, 6	8k2
R8, 10, 11	2k2
R12, 15	22k
R13	33k

POTENTIOMETERS

RV1	5k
RV2	horiz preset
RV3	100k
RV4	log pot
RV5	10k
RV6	lin pot
RV7	10k
RV8	lin pot with SPST switch
RV9	10k
RV10	horiz preset

CAPACITORS

C1	22u
C2, 3, 5	16V radial electro
C4	10n
C6	polyester
C7	4u7
C8	16V tantalum
C9	100n
C10	polyester
C11	4n7
C12	ceramic disc
C13	22p
C14	ceramic disc
C15	470u
C16	16V radial electro
C17	47u
C18	16V radial electro


SEMICONDUCTORS

IC1	LM324
IC2	741
Q1	BC182 etc
Q2	BC212 etc
D1-3	1N4148

MISCELLANEOUS

LS1	3 1/2" 8R speaker
PCB; case	approximately 120x100 x 45mm; 6 x M3 or 6BA nuts & bolts; wire, solder etc.

BUYLINESpage 26

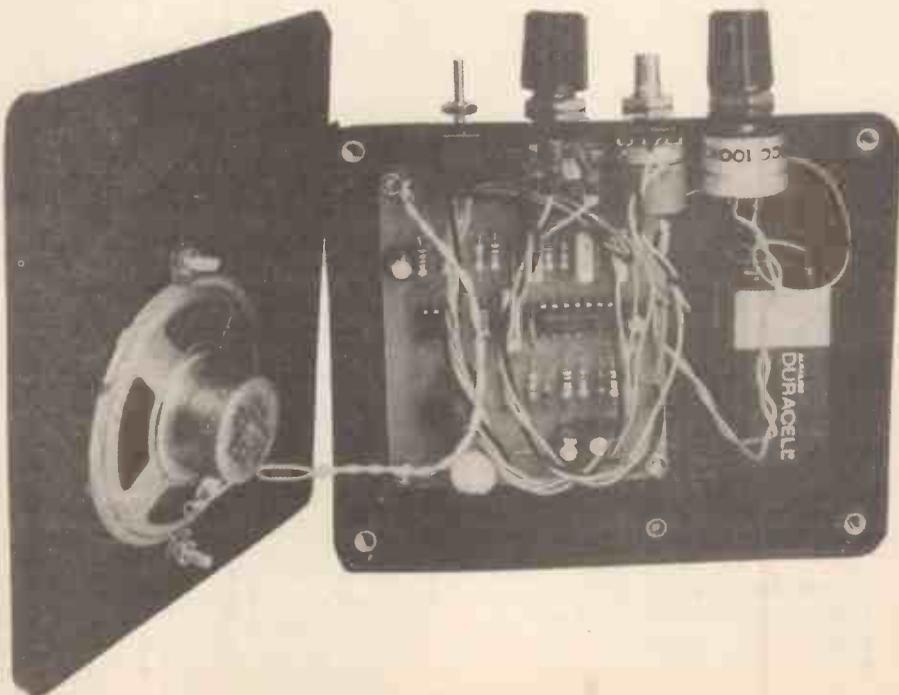

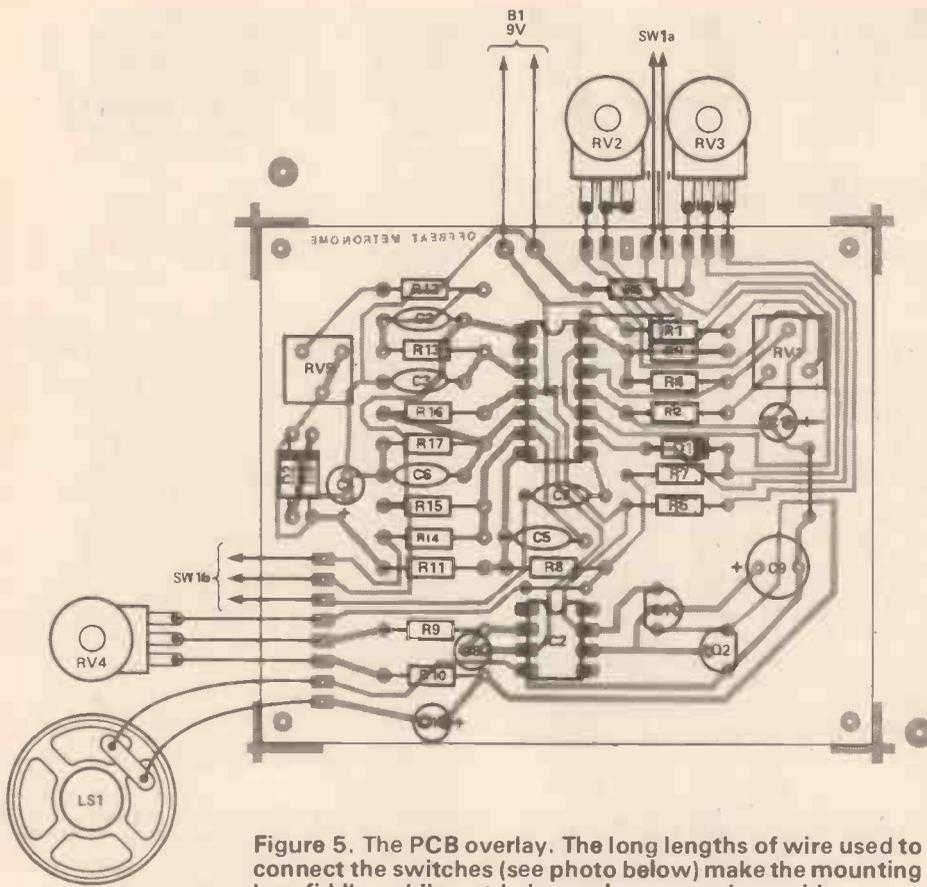


Figure 5. The PCB overlay. The long lengths of wire used to connect the switches (see photo below) make the mounting less fiddly, while not being so long as to be untidy.

sided adhesive pads, and to prise the things off with a screwdriver on the rare occasions at which it needs to be changed. For this reason, an alkaline manganese type of battery is recommended.

Our prototype uses a plastic case for cheapness and lightness; this muffles the sound a little, so if a very robust metronome is wanted, or a maximum volume, a metal case can be used.

Use Of The Metronome

For some purposes a so-called accented beat is required. If the offbeat is not required at the same time, then the offbeat can be set to occur immediately after the tick, thus turning it into a 'double' beat. If the offbeat function is in use, then the tick is automatically accented to a certain extent. If only a basic metronome function is required, without offbeat, but with very slight accent, then setting the offbeat pot fully clockwise will cause a slight accent to be heard.

If the tuning tone does not stop with the switch in either position, first, check the wiring to switch SW1b. If you are completely confident that this is correct, try increasing the value of R15 to reduce the loop gain in the metronome mode. This should cure the problem.

IT LIVES AGAIN!

From the past it came, growing daily, striking terror into the hearts of lesser publications, and spreading its influence across the country in its quest to infiltrate every town, every home, every mind.

Not a horror story, but a success story. And if electronics theory strikes terror into you, then you need the help of **Electronics — It's Easy**. Originally a long-running series in Electronics Today International, **Electronics — It's Easy** was printed as a set of three books. They sold out. It was reprinted as a single volume. It sold out. Now this phenomenally successful publication is available again, in its third reprint. **Electronics — It's Easy** is a comprehensive and simply-written guide which explains the theory (and the practice) of electronics step by step. Every aspect of the subject is covered, starting with the basic principles and working through to the how and why of today's technology.

You can obtain your copy of **Electronics — It's Easy** by mail order using the coupon below. Make cheques or postal orders payable to ASP Ltd, alternatively you may pay by Access or Barclaycard.

Send to: Sales Office (Specials),
513 London Road, Thornton Heath
Surrey CR4 6AR

Please send me copies of Electronics —
It's Easy. I have enclosed £ (£4.95 each
including p&p).

NAME

ADDRESS

Please debit my account

My Access/ Barclaycard No. is

Signature



POINTS OF VIEW

Feel like sounding off?
Then write to the Editor stating your Point of View!

To: The Editor, Hobby Electronics.
Dear Editor,
I have obtained details of a 100W amplifier unit, designed by ETI TOP PROJECTS. I understand that I can obtain printed circuit boards made specially for the amplifier unit, direct from ETI. Unfortunately, I have not found their address anywhere. I would be grateful if you would send me the address, so that I can finish the project.

*Many thanks.
Yours faithfully,
James Bedford,
Halesowen,
West Midlands.*

This gentleman may be having trouble finding ETI's address, but he has the distinction of being the first reader to write direct to our new address at Golden Square. Top marks for observation. The good news is, ETI are at the same address; in fact, they sit in the same corridor. The bad news is, that the PCBs are no longer available for this project. Why not have a go at making your own?

A certain irony is inherent in the sharing of addresses, as is clear from this next letter:

To: The Editor, Electronics Today.
Dear Sir,
I came across a copy of Hobby Electronics the other day, dated December 1982, in which you illustrated a project on phase control called Phase Four, based on the November edition's Breadboard design (a copy of which I do not have).

I would be very much obliged if you could inform me if the components for this project are still available from Newrad Instruments, Tiptoe Road, Wootton, New Milton, Hants, as I am extremely interested in constructing this unit.

I noticed while reading the article that you did not mention if an actual PCB was available, as I have no etching kit at home.

I am writing to Electronics Today about the article in HE because both telex numbers are the same, which led me to believe that HE may have been closed down or amalgamated during 1983. Please accept my apologies if I am incorrect.

*Your assistance in the above matter would be greatly appreciated. Thanking you in anticipation.
Yours faithfully,
Malcolm McKenzie,
Aberdeen,
Scotland.*

Injury to insult! Insult to injury! Pain in my heart! Have you any idea what it does to an Editor's feelings to see a rival Editor (and one who sits in the same corridor, at that) being pressed to accept apologies for the (possible) continued existence of his offspring? While we're on the subject, please will our Aberdeen readers nip into their local newsagents and enquire why Mr. McKenzie could not obtain a December 1983 issue of our beloved HE? In which case he would have observed that the address, distributors and phone number check, as well as the telex number. The Editors don't though. They've begged us on bended knee to let them contribute, but we won't (it's alright. They won't see this till after it's published).

That said, I'm amazed at our readers' powers of observation. We didn't think anyone would actually read the small print at the bottom of the contents page. Well done.

The observation breaks down a bit at this point. Newrad Instruments, in fact, only supplied the case for the prototype: any suitably shaped and constructed case will do. The only criterion, other than being large enough for the works, is that the Phase Four is a foot switch, so the case must be strong enough to stand up to being trodden on.

However, Magenta Electronics Ltd., of 135 Hunter St., Burton-On-Trent, Staffs DE14 2ST do a kit of the Phase Four for £18.71 plus 50p p&p, case included. Magenta do kits for many HE projects, and their advertisement can always be found in current issues of Hobby.

Alternatively, the PCB is still available from Hobby's own PCB Service page.

Flasher Flash

Dear Sir,
*I am currently building the hazzard flashing unit as featured in your publication of Spring 1981, and would be very grateful if you could send me a detailed expansion of how the circuit works.
Yours sincerely,
A. J. Keare,
Ringwood,
Hants.*

I don't have a copy of Electronics Digest Spring 1981 here to refer to, but the Hazard Flasher project also appeared in HE July '80, when it

included the usual construction/How It Works details, along with the circuit, overlay, parts lists, etc. Apart from this (two page's worth only) we can't give any further details. In this case, we don't have any further details (the project is too old) but in general we can't do detailed additional explanations of projects. If anyone is building a circuit and having difficulty getting to grips with one part of it, or making it work, we will as usual do our best to give an explanation.

Computer Careers

Dear Madam,
*After reading your article in careers in electronics in HE October '83 I was extremely interested in the course run by the Polytechnic of Central London with five major computer companies. I would be grateful if you could tell me the address to write to for more information on this course and how to obtain an application form.
Yours faithfully,
K. R. Jones,
Norton,
Cleveland.*

The address to write to with any enquiries is the Engineering And Science School Registry, 115 New Cavendish St., London W1M 8JS. A couple of more companies, incidentally, have entered the sponsorship scheme since we published the article.

Component Crisis

Dear Sirs,
*I have been buying your mag since February 1982 and I can't honestly say that any of the projects have interested me enough to actually build one. But in HE October '83 I did find a project I wanted to build (the Audio Level Meter) after reading in the Buylines that excluding the PCB this project should cost in the region of £6.50. I thought that with my funds being somewhat limited (and whose aren't these days?) this would not only be the ideal project but the ideal price. Or so I thought, because the xxxxxxxxxxxx was £1.75, the bargraph driver £4.39, the LED display £6.50, and the tantalum bead 69p. So far I calculate that at £13.33, twice as much as quoted in the Buylines.
Alright, I know it said 'in the region'*

of £6.50, but there is a somewhat substantial difference between that and £13.50, and I still have other components to get, like presets, axial caps, polycarbonate caps, resistors, diodes, and if those prices are anything to go by it doesn't look like I will be completing this project.

Finally you also say that the TL072 and the LED array are the only things the constructor should have any difficulty in obtaining. Well I managed to get the LED display but the TL072 is not the only thing I've had difficulty in obtaining, in fact most of the components I have found difficult to get hold of.

Yours,
Mr. Watson,
Noddle Hillway,
Hull.

Pardon me for being irrelevant for a moment, but I had a vision of you desperately trying to obtain components from your local greengrocer. Could anything else explain the trouble you're having?

But seriously, and it helps if you plan your buying strategy first like a minor military campaign.

Firstly, we don't know where you're buying your components, and we're not going to ask, believe me, but in that same issue of Hobby Electronics, the LM3915 was advertised for £1.95 from Rapid Electronics, who also sold 10u 26V tantalum capacitors for 20p. Someone has borrowed our Technomatic catalogue, but the most expensive display advertised by them in that issue was £2.00 (they're only £2.50 from RS Components, by the way). Lastly, we can't make out what it was that cost £1.75, but it seems reasonable to assume that it (they?) was overpriced too.

We check off the value of the components used in a project against a recent price list, then add a margin for error or change. We do not generally include the cost of a case or PCB, because there are so many options available. Nor did we include the cost of a power supply for this project, as +9-12V DC should generally be available in the equipment which the level meter is driving.

You should at least change your supplier, and carefully check through the advertisements in the magazine. Contrary to some opinions, we don't print those pages just to fill space: much useful information is there. Essential information, if you want to buy any number of components. Few areas are lucky enough to have a supplier where you can walk into the shop and buy everything you want over the counter at a sensible price. The only other solution is mail order.

There is a payoff between buying your components from several suppliers, at the lowest prices, and the convenience of buying from one or two suppliers at a slightly higher price (ever letter or phone call is part of the expense).

Car Power Boost

Dear Sir or Madam,
Could you please give me the address of West Hyde Developments who produce the Sink Box which you have used in your Car Booster Project (HE July '80). Could you also tell me if you have published any other car stereo boosters since then.
Yours sincerely,
James Bagshawe,
Medical Oncology,
Charing Cross Hospital.

West Hyde Developments were last seen at Unit 8, Park St. Industrial Estate, Aylesbury, Bucks HP20 1ET. Tel: (0292) 20441. Check with them first that they still do the same case or an equivalent.

We haven't published another power booster project, but if you look up the advert from ILP Electronics Ltd., you may find they have what you want.

ZX81 EPROMmer

Dear Sir,
Your magazine has had many great projects over the years and recently some of these have been for the ZX81.

But as a ZX81 user it strikes me that the one project that we really need is an EPROM programmer, a unit specially designed for the ZX computer, complete with a board to connect with the ZX81 for immediate use after programming.

People should be turning to the "PROM" as a more efficient means of storing games, etc. (We have a bad time with tape, you know.) So how about it?

Yours hopefully,
R. Baker,
Trowbridge,
Wilts.

Look out for it in the third edition of our new magazine, **Digital & Micro Electronics**, especially for the computer hardware user, which will be on the newsstands in late March.

Obscured Issue

Dear Editor,
I have begun the 30V PSU project in HE September '83. However upon making my PCB, it seems to be that there is an error involving the connection of the preset to the output.

The circuit diagram shows one side of the preset connected to IC2 pin 2, and emitter of Q3. The wiper arm then feeds the output. The other leg of the preset is then shown connected to the +ve side of the meter.

However, the PCB overlay does not

correspond to this, as the wiper arm is shown to 'feed' the meter instead of the output.

I have been buying HE for a long time, but the clarity of the PCB overlay in the project is diabolical!

Could you please then clarify my query, and even perhaps enlarge or clarify the PCB overlay in the preset and transistor region.

Yours gratefully,
M. S. Higgins,
Hillsborough,
Sheffield.

Unfortunately, the detail of the PCB was obscured in the area of the preset by a line representing the wire joining the emitter of Q1 to the base of Q2. It thus appears that the preset is shorted out!

In fact the lower terminal of PR1 has simply been left open circuit, ie connected as a variable resistor. The wiper of PR1 does feed the meter, but electrically this is equivalent to the arrangement shown in Figure 1, and therefore is of no consequence.

Uncommon Problem

Dear Sir,
I am writing to you about a problem I am having in getting hold of components for the Audio Analyser (HE September '82), because they are such uncommon values.

I am finding it hard to purchase them. I would be grateful if you can help me with this problem, if you can supply me with the components or put me on the right track.

Yours faithfully,
Paul Bridges,
Enfield,
Middx.

If these components cannot be found in the catalogue of the regular mail order suppliers (eg. Maplin, Watford, Rapid etc.) I suggest you ring around until you find someone willing to order them in from RS Components.

However, without going to the trouble of cross checking each and every value, it looks to me as if they're all fairly standard values.

The other point you might like to note is that the Audio Analyser will shortly be the subject of Forward Bias, since certain modifications are required to make it completely reliable.

"Acknowledgements"

Lastly, many thanks to Richard Cartmel of Cheshire — we don't often get thank you letters. Glad to hear the introduction to the HE Tape/Slide Synch was a happy one. By the way, if the PCB and the Circuit Diagram don't exactly correspond, the PCB is likely to be the correct one. We haven't had any problems reported. Cheers!

COMING SOON TO . . .

Hobby Electronics

COPING WITH COMPONENTS

Confused and puzzled by polyester?
Tantalized by tantalum or mystified by metal films?
Then this especially helpful feature will take the worry out of dealing with different types of resistors and capacitors.

THE METRODRIVE

A Hobby Electronics exclusive, lifting the lid on the hidden details of a top secret project from you-know-who.

Faster than a speeding ZX81, more colourful than a Spectrum, flatter than a television and able to leap quanta in a single bound . . . ? All is revealed in next month's Hobby Electronics!

TIME-OUT

A handy easy-to-build project for switching off mains powered appliances after a pre-set time.

The PCB-mounted relay will switch up to 10 amps at 240V, or heavier loads can be handled by an optional off-board heavy duty relay.

The on-time is continuously variable from 10 to 60 minutes, making this a useful device for many household applications.

ANALOGUE TEST SET

An all-in-one test kit for audio components, it includes a one watt audio amplifier for signal tracing, plus a function generator providing sine, square or triangle wave outputs from 10Hz to 100kHz, with the output level variable up to a maximum of one volt RMS.

With the addition of a simple multimeter, the Test Set becomes a universal instrument, capable of most audio tests and measurements, including frequency response and gain.

Please reserve . . . copies of the April issue of

**Hobby
Electronics**

for
Name

Address

.

.



**Hobby
Electronics**

**April issue on sale at
your newsagent from
9th March. Place your
order now!**

Although these articles are being prepared for the next issue, circumstances may alter the final content.

HENRY'S AUDIO ELECTRONICS

COMPUTERS • COMMUNICATIONS • TEST EQUIPMENT • COMPONENTS

VISIT OR PHONE • OPEN 6 DAYS A WEEK • ALL PRICES INC VAT

STEREO TUNER/AMPLIFIER

4 wave-band stereo tuner amplifier by GEC. MW/LW/SW/stereo FM radio. 10 + 10 watt stereo amplifier. Inputs for PU tape in/out. Supplied as two assembled units as illustrated. **£21.95** - easy to connect. (UK C/P £1.50)



THERMAL MATRIX & LINE PRINTER

NEW LOW PRICE

COMPLETE WITH FULL HANDBOOK, 3 ROLLS PAPER (UK post etc £1.05) (Est approx £187) SUITABLE FOR: TANDY • BBC • DRIC • NASCOM • GEMINI • ACORN • NEW BRAIN • DRAGON • etc. etc (Interface unit with leads £15 - stale model). (Your enquiries invited).

£69.95 inc VAT

PRESTEL ADAPTOR 3 card set with data etc (P/S +/- 12V and +5V) **£69.95** inc. VAT

MODEM CARD BT approved ready assembled unit with data and accessories. **£39.95** inc. VAT


SANYO DM21 12 HIGH RESOLUTION MONITOR 12" green display. Composite video. 1280 characters. Over 15 MHz B/W. 240V AC 34 w 15" x 11 1/4" x 12 1/4". Alphabetic and Graphic display. Usually **£89.95 - £99.95** incl VAT **£69.95** (UK C/P & ins £2.05)



I.T.T. 2020 CABINET Professional Computer Case 18" x 15 1/2" x 4 1/2" (front slopes). As previously advertised. **£27.50** inc VAT (UK C/P £2.50)



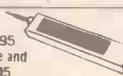LOGIC PROBES LP10 10 MHz **£22.95** DLP50 50 MHz with carry case and accessories **£49.95**



HIGH VOLTAGE METER Direct reading 0/40 KV. 20K/Volt. **£23.00** (UK C/P 65p)



DIGITAL CAPACITANCE METER (UK C/P 65p) 0.1 pF to 2000 mfd LCD 8 ranges **DM6013 £52.75**



VARIABLE POWER SUPPLIES (UK C/P £1.00) PP241 0/12/24V 0/1A **£35.00** PP243 3 amp version **£59.95** 230N 0/30V 1A twin meter **£99.50**



FREQUENCY COUNTERS PFM200A 200 MHz hand held pocket 8 digit LED **£77.60** MET100B digit LED bench 2 ranges 100 MHz £102.35 MET600B digit LED bench 3 ranges 600 MHz £132.25 MET1000 8 digit LED 3 ranges 1 GHz **£182.85** TF040 8 digit LCD 40 MHz Thandar **£126.50** TF200 3 digit LCD 200 MHz Thandar **£166.75**



DIGITAL MULTIMETERS

with case (rotary switches) Side button - case **£2.95** KD25C 13 range 6.2A DC 2 meg ohm **£23.50** K0305 16 range 10A DC 2 meg ohm **£26.95** K030C 26 range 1A AC/DC 20 meg ohm **£29.50** £33.50 Melex 3000 30 range 10A AC/DC 20 meg ohm **£33.24** 6010 - 28 range 10A AC/DC 20 meg ohm **£34.40** 7030 4- AS610 high acc. 0.1% basic **£41.30** KD615 16 range 10A DC 2 meg plus Hfe tester **£39.95** SIFAM 2200B 21 range 2A AC/DC 20 meg Bench Models **£29.95** TM355 29 range LED 10A AC/DC 20 meg, Thandar **£86.25** TM356 26 range LCD 10A AC/DC 20 meg, Thandar (Replaces TM353) **£97.75** TM351 29 range LCD 10A AC/DC 20 meg, Thandar **£120.75**



ALSO IN STOCK Thurby, Metrix and Beckman. Professional series incl. True Rms. etc.

MULTIMETERS (UK C/P 65p)

M200 20K/volt, 30 ranges, AC/DC, 20 KHZ. List **£21.85** **£12.95** HM102BZ 20K/V 10A DC 22 range & cont. buzzer **£13.50** TMS500 23 ranges 30K/V, 12A DC plus cont. buzzer **£23.95** MHS6R 20K/V, 22 range pocket **£10.95** B30A 26 range 30K/V, 10A AC/DC overload protection, etc. **£23.95** 360TR 23 range 100K/V, Large scale 10A AC/DC plus Hfe **£39.95** AT2100 31 range 100K/V deluxe, 12A AC/DC **£33.50** AT1020 18 range 20K/V, Deluxe plus Hfe tester **£18.95** YM360TR 19 range 20K/V plus Hfe tester **£15.95**



SIGNAL GENERATORS (220/240V AC)

FUNCTION: All sine/square/triangle/TTL etc TG101 0.02HZ-200KHZ **£113.85** TG102 0.2HZ-2 MHz **£166.75** PULSE TG105 Various facilities 5HZ-5 MHz **£97.75** AUBD0 Multiband Sine/Square **£90.85** LA627 10 KHZ to 1 MHz **£83.50** A G202A 20 HZ to 200 KHZ (list £94.50) **£159.85** LAG 120A 10 HZ-1MHz Low Distortion **£159.85** RF SG402 100 KHZ to 30 MHz (list £79.50) **£69.50** LSG17 100 KHZ to 150 MHz **£79.35**

OSCILLOSCOPES

Full specification any model on request. SAE by post 'HM' Series HAMEG: 'SC' THANDAR: 'CS' TRIO: '3' CROTECH 'V' HITACHI SINGLE TRACE UK C/P £3.00 3030 15 MHz 5mV 95mm tube plus component tester **£177.10** SC110A = Miniature 10 MHz battery portable Post free **£171.00** Optional carry case £6.84 AC adaptor £6.69 Nicads £12.50 HM103 15 MHz 2mV 6 x 7 display plus component tester C/P £3.00 **£181.70** DUAL TRACE (UK C/P £4.00) HM203/4 Dual 20 MHz plus component tester **£303.60** CS1562A Dual 10 MHz (List £321.00) **£269.50** 3132 Dual 20 MHz - component tester **£325.45** CS1566A Dual 20 MHz All facilities (List £401.35) **£349.50** HM204 Dual 20 MHz plus component tester sweep delay **£419.75** HM705 Dual 70 MHz sweep delay **£676.00** V212 Dual 20 MHz **£399.25** V222 Dual 20 MHz plus extra facilities **£391.00** V422 Dual 40 MHz portable **£586.50** V203F Dual Trace 20 MHz sweep delay **£408.25** V134 Dual Trace 10 MHz storage **£1092.50** All HITACHI, CROTECH TRIO & HAMEG MODELS AVAILABLE • With probes



SCOPE PROBE KITS X1 £7.95 X10 £9.45 X1 - X10 £10.50

ORDER BY POST OR PHONE

HENRY'S 404-406 Edgware Road, London, W2 1ED Computer: 01-402 6822. Components: 01-723 1008 Test Equipment & Communications: 01-724 0323

AUDIO ELECTRONICS 301 Edgware Road, London, W2 1BN 01-724 3564

CATALOGUE Send large S.A.E. (20p UK)

All mail to Cubegate Ltd 1st floor, 406 Edgware Road, London, W2 1ED

JOIN UP WITH LITESOLD

Professional Soldering Equipment at Special Mail-Order Prices.


EC50 Mains Electric Iron. £26.19



proportional electronic temperature control inside the handle. Adjustable 280° to 400°C. Burn-proof 3-wire mains lead. Fitted 3.2mm Long-Life bit. 1.6, 2.4 and 4.7mm available. 240v a.c.

Features spike-free, solid state

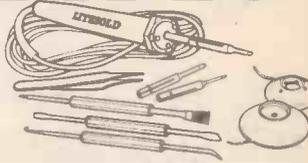SK18 Soldering Kit. £15.24 Build or repair any electronic project. LC18 240v 18w iron with 3.2, 2.4, and 1.6mm bits. Pack of 18 swg flux-cored 60/40 solder. Tweezers. 3 soldering aids. Reel of De-Solder braid. In PVC presentation wallet.



ADAMIN Miniature Iron. £5.97



nylon handle with finger grip. Interchangeable bits available 1.2, 1.6, 2.4, 3.4 and 4.7mm. Fitted with 2.4mm. 240v 12w (12v available). Presentation wallet.

'L' Series Lightweight Irons. 12w £6.23.

High efficiency irons for all electronic hobby work. Non-roll handles with finger guards. Stainless steel element shafts. Screw-connected elements. Slip-on bits available from 1.6 to 4.7mm. LA12



Soldering Iron Stands. £5.11



Designed specially for LITESOLD irons. Heavy, solid-plastic base with non-slip pads. Won't tip over, holds iron safely. With wiping sponge and location for spare (hot) bits. No 5 stand for EC50 iron No 4 stand for ADAMIN miniature iron No 3 stand for LA12 and LC18 Irons All same price

Replacement Bits For all above irons. Non-stick designs, machined from special copper alloy, with Inconel retaining rings. Two types - Chromium plated with copper face (for economy and ease of use) and Iron plated with

	Copper	L/L
EC50	-	£1.58
Adamini 12 and		
LA12	92p	£1.56
LC18	£1.01	£1.70


BRADEWICK De-Solder Braid.



For simple, safe and effective de-soldering of all types of joint, using a standard soldering iron. Handy colour-coded packs of 1.5 metres in 3 widths: Yellow - 1.5mm, Green - 2mm, Blue - 3mm. **£1.05 per Reel**


De-Solder Pumps. £6.19

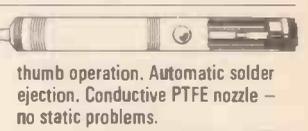High Quality version of increasingly popular type of tool. Precision made anodised aluminium body, plunger guard and high-seal piston. Easy



thumb operation. Automatic solder ejection. Conductive PTFE nozzle - no static problems.

Miniature Tool Sets

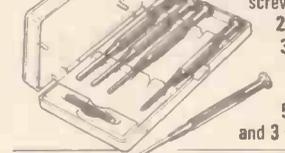

Top quality Japanese metric hardened and tempered tools. Swivel-top chrome plated brass handles. Fitted plastic cases. 113 set - 6 miniature screwdrivers 0.9 to 3.5mm **£2.70** 227 set 5 socket spanners 3 to 5mm **£2.80** 305 set 2 crosspoint and 3 hex wrenches 1.5 to 2.5mm **£2.70** 228 set 20 piece combination: 5 open, 5 skt spanners, 2 crosspoint, 3 hex and 3 plain drivers, scriber, handle/holder **£4.83**

Microcutters. £3.21 Light weight hardened and precision ground. Flush cutting. Screw joint, return spring, cushion-grip handles. Safety wire-retaining clip.



Soldering Aids.




Set of 3 £3.63 Scraper/Knife, Hook/Probe, Brush/Fork. 3 useful double-ended aids to soldering/desoldering/assembly. In plastic wallet.

Solder. £0.90

Top grade resin flux cored 60/40 wire, 18 swg, in handy plastic dispenser. Approximately 3 metres (26gm).



ADAMIN Electric Stylus. £15.04

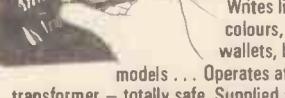

Writes like a ballpoint in Gold, Silver, Copper or 6 colours, on card, plastics, leather etc. Personalise wallets, bags, albums, books, electronic equipment, models... Operates at 4.5v from its own plug/transformer - totally safe. Supplied with coloured foils.

Prices include p&p and VAT. Send order with Cheque/PO. Ring for Access/Visa sales, or ask for order forms. **LIGHT SOLDERING DEVELOPMENTS LTD. DEPT. H 97-99 GLOUCESTER ROAD, CROYDON CR0 2DN. 01 689 0574**

ALL ABOUT ELECTRONICS

Our new **Beginner's Series** tells you all you'd like to know about electronics. From start to finish. All about components and circuits, all the theory you need to get started in the world of electronics.

Two months ago, *All About Electronics* concentrated on devices and circuits formed with logic gates. You saw AND gates, and NAND gates, OR gates, NOR gates and NOT gates (invertors) used individually and in circuits to give particular output logic states which depended totally on the applied input logic states (Figure 1). A logic state consists of either a '1' or a '0' — that is, it can be one of *two* options — hence the general name, *binary logic*, for such circuits.

These binary logic states can be expressed in mathematical terms and written as equations, eg:

$$A = 0$$

or:

$$B = 1$$

or:

$$A \cdot B = C \cdot D = Z$$

where the dot between letters A and B, C and D, in the last equation means AND; and the plus sign means OR. (This is binary or *Boolean algebra*, remember, not conventional algebra.)

Similarly, the logic states can be expressed in electronic terms, as voltages. For example, the logic state 1 could be expressed as the voltage 5VDC, and the state 0 could be defined as 0VDC. The actual voltages used are irrelevant and could be literally any voltages, as long as

1. The voltages, once chosen, are maintained as standard
2. Circuits connected before and after the logic circuit operate satisfactorily with these voltages
3. The electronic logic gates (normally in IC form) which make up the

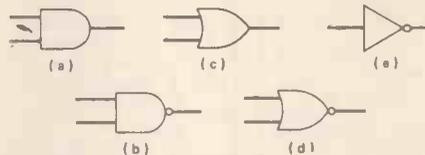


Figure 1. Typical logic gates:

- a) AND gate
- b) NAND gate
- c) OR gate
- d) NOR gate
- e) NOT gate (invertor)

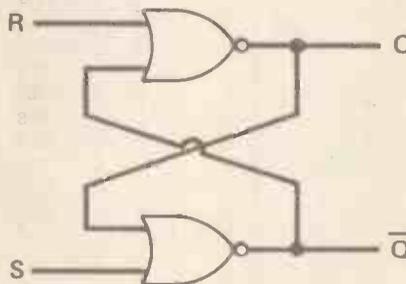


Figure 2. A simple form of electronic memory using two NOR gates — the SR-type bistable.

S	R	Q	Q̄
1	1	H	L
1	0	L	H
0	0	Q ₀	Q̄ ₀
0	0	L	L

Figure 3. Function table for the SR-type bistable of Figure 2. The shaded area indicates an operation-mode not recommended for use.

circuit operate from (and will not be damaged by) the voltages. Two main categories of logic gate ICs where shown to exist: TTL (transistor — transistor logic) and CMOS (complementary metal-oxide semiconductor).

ICs within each category contain individual logic gates, and choosing a particular type of gate, ie AND, NAND, OR, NOR, NOT, is simply a matter of choosing the correct IC within each category.

These types of gates and the circuits we looked at form combinational logic circuits ie, their outputs vary as a definite combination of the inputs. Such circuits, although they may be used in quite complex control equipment, are really no more than electronic switches the output of which depend on the correct combination of inputs. They display no intelligence of any kind, simply doing what is demanded of them — instantly.

Be Smart — Remember This

One of the first aspects of intelligence — whether in the animal world (including humans) or in the electronics world — is memory ie, the ability to decide a course of action dependent not only on the applied inputs but also on a knowledge of what has previously taken place.

Logic circuits can be constructed which remember logic states. We say they can store binary information. The simplest form of logic memory is shown in Figure 2, and is constructed using two NOR gates, cross-coupled so that the output of the first is connected to the input of the second, and the output of the second is connected to the input of the first. There are two inputs to the circuit and also two outputs.

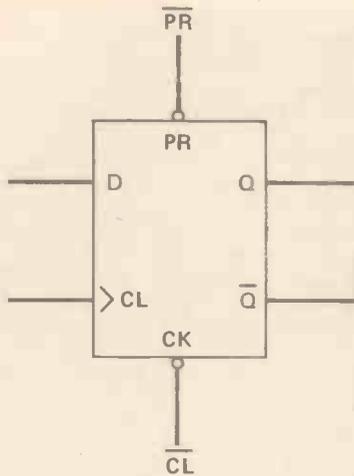


Figure 4. Circuit symbol for D-type bistable.

Now, it so happens that one output is, in most instances, the inverse of the other, so for convenience one output is labelled Q and the other output is \bar{Q} , to show this.

A truth table for the circuit is shown in Figure 3, although more correctly we call this a function table. You see, truth tables are used only for combinational circuits and this circuit, although using combinational gates, is not strictly speaking combinational — you'll see why not, later.

Account has been taken in the function table for changing from one logic state to the other by the symbol: Δ , which indicates that the input state changes from a logic 0 to logic 1. Also, we no longer write the logic states as '1' or '0', but H (meaning high) and L (meaning low).

The outputs indicate what happens as the input states change on these occasions. You can see that if input S goes high (ie, from 0 to 1) while input R is low, then the output Q will be high. If, however, input S then returns low, the output will be Q_0 — which simply means it remains at what it was. If input R then goes high while S remains low, the output changes to low and remains in that state even if R goes low again.

In other words we have constructed a form of memory, called a latch or a bistable, the output of which can be set to a high state by application of a positive-going pulse to input R. You will understand now, why the inputs are labelled S and R (set/reset) and why this type of circuit is called an S-R type bistable.

The last line of the function table is shaded to indicate that this condition is best avoided, because both outputs are the same. Designers of digital circuits would normally ensure that this condition did not occur in their circuits because confusion can arise.

Stable Vibrations

We have met the bistable before, of course. A bistable is one of a group of circuits — the other two types we said

INPUTS				OUTPUTS	
\bar{PR}	\bar{CL}	CK	D	Q	\bar{Q}
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H	H
H	H	Δ	H	H	L
H	H	Δ	L	L	H
H	H	L	X	Q_0	\bar{Q}_0

Figure 5. Function table for a D-type bistable. Shaded area indicates an operation-mode not recommended for use.

Figure 7. Function table for a JK bistable. Shaded area indicates an operation-mode not recommended for use.

INPUTS					OUTPUTS	
\bar{PR}	\bar{CL}	CK	J	K	Q	\bar{Q}
L	H	X	X	X	H	L
H	L	X	X	X	L	H
L	L	X	X	X	H	H
H	H	Δ	L	L	Q_0	\bar{Q}_0
H	H	Δ	H	L	H	L
H	H	Δ	L	H	L	H
H	H	Δ	H	H	TOGGLE	

were monostables and astables — called multivibrators and they can all be built using logic gates.

There is more than just one type of bistable and the S-R type is really only the simplest — the two types I'm going to show now are far more useful and versatile. Instead of showing their construction using separate logic gates, however, they are shown as block. If necessary they could be built using separate gates but you don't need to know how to construct them because, yes you guessed it — they can be bought ready-built in IC form. First is the D-type bistable. Its circuit symbol is shown in Figure 4 and its function table is in Figure 5.

The main difference between D-type and S-R type bistables is that an input is provided for what is called a clock. Now, the clock is the name given to the output of a square-wave oscillator, of any fixed frequency, which produces definite, fixed period, pulses to operate digital circuits. It is an application of a clock pulse that a D-type bistable will perform its function — so for example if a clock is applied with a frequency of 100 Hz, the bistable will perform 100 functions every second.

Note also the S and R inputs of the S-R type bistable have been replaced by the inputs PR (preset) and CL (clear) which perform similar functions. A last input to the D-type bistable is the D (data) input.

You should now be able to understand

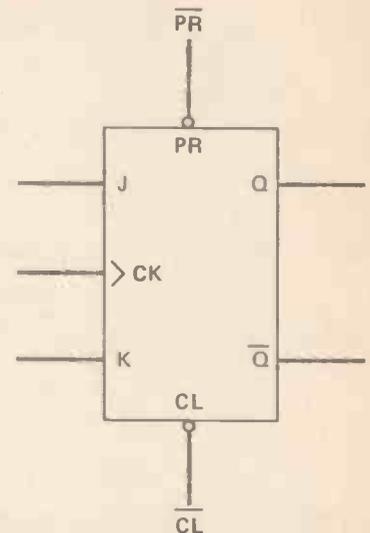


Figure 6. Circuit symbol for a JK master-slave bistable.

the function table. The first three rows indicate that the \bar{PR} and \bar{CL} inputs override all other inputs (that's why the CK and D inputs are shown as X: because X = don't care). Thus the outputs Q and \bar{Q} are dependent primarily upon the logic states of the \bar{PR} and \bar{CL} inputs.

However, when the \bar{PR} and \bar{CL} inputs are both high, control of output becomes the prerogative of the CK and D inputs. For example, when the clock is low the output $Q = Q_0$ ie, it remains the same as it was — no matter what the logic state of the D input (because $D = X$, gerrit?). On the leading edge of the clock pulse, however, output Q follows the logic state of the input D: whether high or low. So a D-type bistable acts like the simpler S-R type but with extra controlling inputs.

Another type of bistable is shown in Figure 6 and is the JK master-slave bistable, it is similar in operation to the D-type bistable but the D type input has been replaced by two separate controlling inputs, J and K. A function table applicable to the J-K master-slave bistable is shown in Figure 7 and you can see how it works from this. The same sort of operations occur as with the D-type bistable but with two main differences:

- the operations take place on the falling edge of the applied clock pulse
- the last row of the function table shows a bistable operation known as toggling ie, the output state changes from whatever state it is, to the other state.

Altogether Now, Vs One At A Time

Underlying the study of bistables which we've looked at so far this month is something far more important than it would first seem. We have actually seen the changeover, from the category of digital electronic circuits known as combinational, to the category of sequential digital circuits. The difference has been that the inputs of

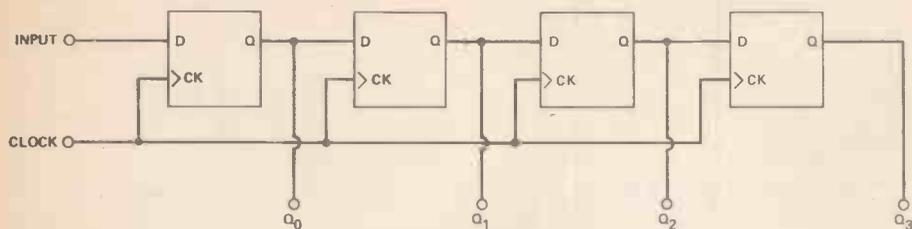


Figure 8. Four-bit shift register using four, D-type bistables.

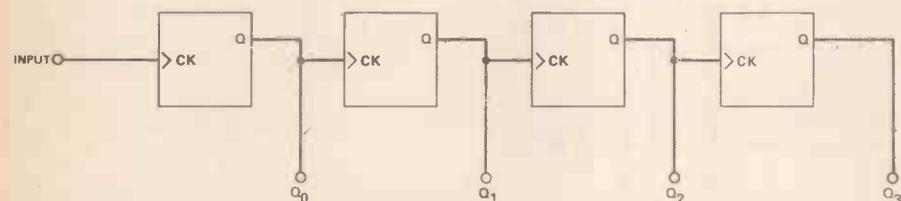


Figure 9. Four-bit binary counter using four, JK-type bistables.

combinational circuits are instantaneous and the outputs occur as a direct consequence of the inputs. In sequential circuits, however, the inputs have to occur at the correct times for the outputs to be correct — ie, they have to occur in a set sequence. It is the combination of the clock pulse (providing the sequence) and memory (to enable inputs to be at the right place at the right time) which allows these sequential circuits to operate. And it is these very bistables which we have seen which form the basis of electronic memory. If you can imagine a network of literally thousands of such bistables then you have pictured a simple memory bank: the information stored inside of which may be changed at will by altering the control inputs.

Of course, things are not quite as simple as that. A collection of bistables gives us a method of storing

information, yes. But such a collection will not necessarily guarantee that the information is organised. For instance if a certain string of binary digits (known as bits) is stored in the memory bank; how do we know when a string is retrieved, that it is the correct one? What we need is some way of ensuring the information out is the same as we fed in.

The way to do this is to store the information in regular formation — rather like a platoon of soldiers. If one line of soldiers is our stored 'information' then that line can move about all over the parade ground and as long as they remain in line ie, soldier 1 before soldier 2, soldier 2 before soldier 3 etc, then the 'information' will not be lost or jumbled. In electronic memory the information we wish to store is entered as a row of bits (called a byte or sometimes a word) and kept within the

memory in that order.

One way of doing this is with a number of D-type bistables, as in Figure 8. By connecting the output of the first bistable to the D input of the second, and the output of the second to the D input of the third etc, a shift register is created. The shift register of Figure 8 has four bistables therefore a byte of four bits can be stored. If a longer byte is required to be stored we use more bistables.

On every clock pulse in the shift register takes the previous state of the bistable to its left. Thus, if a logic 1 was applied to the input, the outputs of all four bistables at each clock pulse is:

after the first pulse	1000
after the second pulse	1100
after the third pulse	1110
after the fourth pulse	1111

Alternatively, if a four-bit type is applied to the input; each bit applied separately, one bit at a time corresponding to each clock pulse (this is known as serial information) then the outputs at each clock pulse will be, for example using an applied serial byte 1001:

Inputs	Outputs
1	1000
0	0100
0	0010
1	1001

That is, after four clock pulses the serial information entered has been stored in the shift register. This information can be retrieved: serially by applying four more clock pulses and taking the information from the last bistable's output or; as a parallel byte by taking the output of all four bistables simultaneously. The latter is known, obviously, as serial-to-parallel

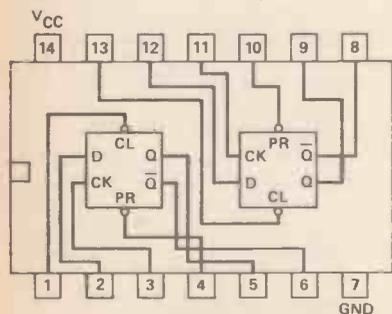


Figure 10. 7474 TTL dual, D-type bistable.

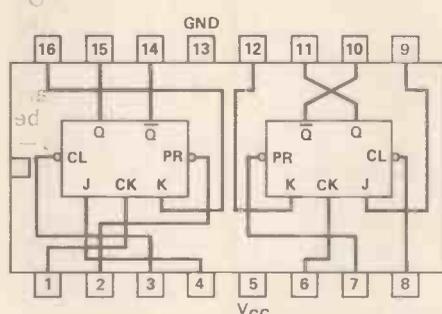


Figure 11. 7476 TTL dual, JK-type bistable.

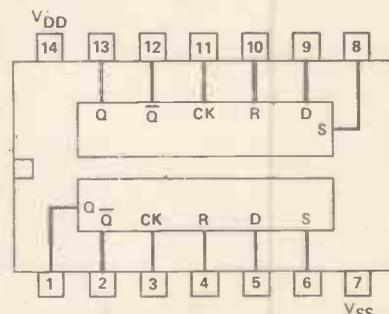


Figure 12. 4013 CMOS dual, D-type bistable.

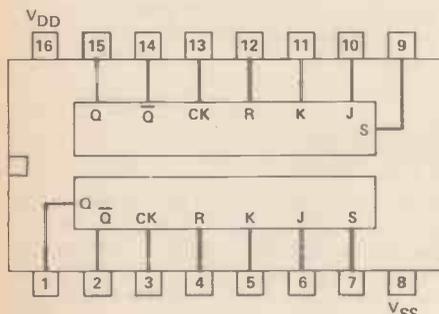


Figure 13. 4027 CMOS dual, JK-type bistable.

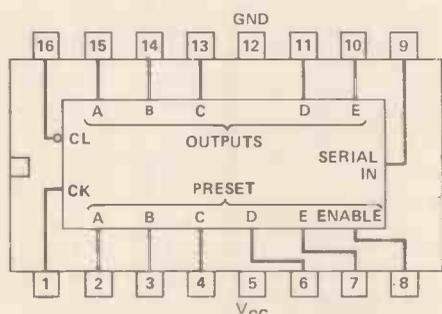


Figure 14. 7496 TTL five-bit shift register.

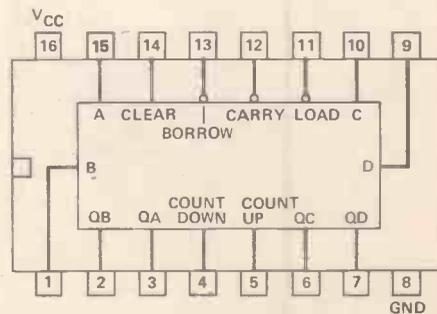


Figure 15. 74193 TTL binary counter.

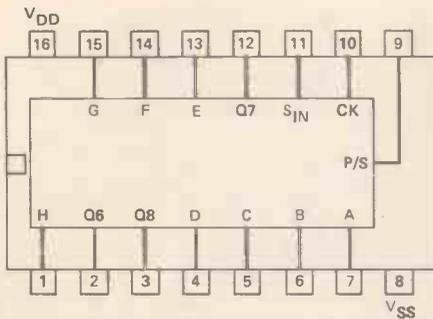


Figure 16. 4014 CMOS eight-bit shift register.

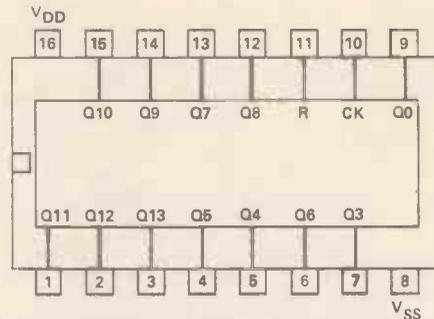


Figure 17. 4020 CMOS 14-bit binary counter.

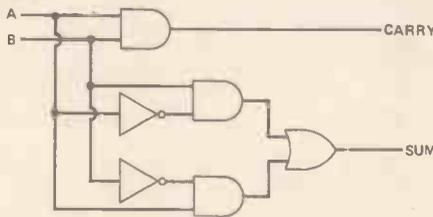


Figure 18. A half-adder circuit using combinational logic gates.

A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Figure 20. A full-adder circuit using two half-adders and an OR gate.

conversion and is an often used procedure in some complex digital circuits.

Counting

Binary mathematics is very similar to ordinary mathematics (ie, denary — to the base of 10) in that there are times when we want to be able to count using it. Simple counters can be made using J-K type bistables and one is shown in Figure 9. In denary, all counting is to the base of 10, ie 0 - 1 - 2 - 3 - 5 - 6 - 7 - 8 - 9 - then go any further we prefix the digits with a 'carry' ie 10 - 11 - 12 - 13 - etc. Then a 'carry 2' ie 20 - 21 - 22 - 23 - etc etc.

However, in binary mathematics the base is 2, so the number system progresses 0 - 1 - 10 - 11 - 100 - 101 - 110 - 111 etc. Figure 9 shows a four-bit counter which can count, for example, input pulses. The corresponding outputs at each input pulse are:

start	0000
after the first pulse	0001
after the second pulse	0010
after the third pulse	0011
after the fourth pulse	0100
etc.	

You will notice that I have reversed the

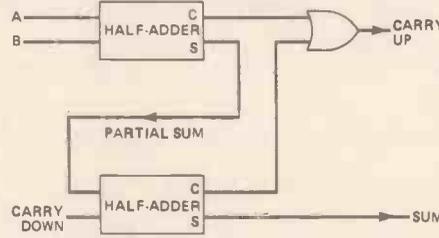


Figure 19. Truth table for a half-adder circuit.

order of the counted bits — this is so the least significant bit (LSB) is on the right as it should be and the most significant bit (MSB) is on the left.

Now, although bistables can be formed with individual gates, it is more usual to see them as part of an IC. For example the layout of the 7474 TTL IC is shown in Figure 10 and consists of two D-type bistables. The 7476 TTL IC is shown in Figure 11 and consists of two J-K master-slave bistables. The CMOS version of both these ICs, the 4013 and the 4027 are shown in Figures 12 and 13.

Likewise, shift registers and binary counters would not normally be constructed using separate bistables — Figures 14 and 15 show a 7496 TTL shift register and a 74193 TTL binary counter, and Figures 16 and 17 show a 4014 CMOS shift register and a 4020 CMOS counter.

Addition and Subtraction

Just as digital circuits can be used to perform functions like counting and storing, they can also be used for other, more usual, mathematical functions like adding and subtracting. For, example, Figure 18 shows a circuit for adding together two bits of binary digits. Now, we should be able to draw up a table from our knowledge of binary numbers giving us the outputs of this circuit and such a table is shown in Figure 19.

This is exactly the same as denary arithmetic where two numbers, say 2 and 3, give a sum 5; but two numbers, say 6 and 4, give a sum 0 and a carry 1 — creating the two-digit number, 10. The circuit of Figure 19 is known as a half-adder because it only performs addition of two inputs. There may be, however,

occasions when three inputs require addition — say if a preceding addition stage has produced a carry output. Well, now we use a full adder as in Figure 20, consisting of two half adders and an OR gate.

Subtraction can be performed using the exact same circuits; after a modification to the number being subtracted. The modification is called "creating the two's complement" of the binary number by inverting every bit and then adding one to that number. In this way, the two's complement of the byte 1010 would be formed.

Number → Invert → Add 1
1010 → 0101 → 0110

So, 0110 is the two's complement of 1010 and the binary subtraction

1101 minus 1010

is the same as

1101 plus 0110

Go Forth And Multiply

Multiplication is easily performed and best demonstrated with denary numbers, but the process is identical in binary. If, say, the two numbers to be multiplied are 60 and 4, we can arrange the statement 60×4 to read $60 + 60 + 60 + 60$, and then use an adder to perform this addition. Division is similar. If the division to be performed is $60/4$, we can re-arrange this to read $60 \times \frac{1}{4} = 60 \times 0.25$, a multiplication, which can be performed as an addition sum, as above.

I haven't spent a lot of time explaining the different mathematical functions in binary, because it isn't necessary that they be learnt. The only thing you need to remember and understand is that all the mathematical functions can be broken down into much simpler steps based on additions and counting. In this way, because digital circuits are very fast in operation, high — speed mathematical calculations are easily performed. We have invented the calculator!

More complex digital circuits have been developed known as arithmetic logic units (ALUs) which performs all the arithmetic functions detailed here plus the standard logic functions of AND, OR, etc. ALUs form the core of the digital computer, and a modern micro-processor IC (yer actual microchip) contains among other things, an ALU within its body, allowing the micro-processor to perform the arithmetical functions according to instructions.

The instructions which a microprocessor follows are collectively known as the program and form, literally, step-by-step recipes for the microprocessor to act upon. This program must be stored in electronic memory for it to be at hand, so the microprocessor can read each instruction as required. Thus, what we have seen in this month's *All About Electronics*, ie bistables, counters, adders, ALUs etc, will form the basis for a future month when we learn about computers themselves.



Bernard Babeni (publishers) Ltd., who supply the HE Bookshelf, ply their trade direct.

"Go West, Young Man" ("Man" being a technical term for a person of either sex and indeterminate age) came the cry from our organisers for 1983, Argus Specialist Exhibitions. So west we went, all the way to Hammersmith and the Cunard International Hotel.

Having attempted to run the gauntlet of the traffic in Hammersmith Broadway, I eventually lost my nerve and went via the underpass — a ten-minute detour. I infiltrated the hotel, waved my pass at the security men, and was confronted at once by a display of computer-controlled railways.

Dave Holladay of Precision Relays Ltd. showed me round his simple, two-track, points-switching system, worked by magnets carried under the trains, and Reed switches embedded in the chipboard beneath the track. Apart from the engines themselves, the most striking aspect of this set-up was the bank of five enormous computer-controlled relays in the centre of the

The HE editorial team hard at work (You distract the editor while I find out what's causing that stripe on the page — d.).



Robots, railways, radio and rockers assemble under Hammersmith Flyover for the electronics exhibition of 1983.

track, and the Commodore 64 which was being used to control them.

The other, more spectacular railway layout was laid out and built by the Fratton Bargain Shop in Portsmouth, using both a Hornby Zero One model railway controller and a Hamant and Morgan 5000 and featuring a two-directional reverse loop. The two control units used constant, but different voltages, and the trains themselves included engines with and without fitted microprocessor control modules.

Heave To

Meanwhile, back on the Electronics stand, we were kept busy heaving fresh bales of December's HE and January's ETI (the lucky blighters were just in time to get their new issues out in time for Breadboard, while we had to keep explaining that Hobby Electronics wasn't due out for another fortnight...)

and flogging back issues and copies of Ham Radio Today and Digital And Micro Electronics — one gent from Sweden bore away almost an entire set of HRT backissues, saving himself quite a few quid compared with postal ordering. Breadboard is, after all, the only place where you can buy the year's backissues still at the cover price — and inspect them into the bargain!

Editor Ron Keeley set up the HE Programmable Joystick on a space-invaders type game, and ETI's technical department, Phil Walker, connected up ETI's Graphic Equaliser to a loud-speaker, and provided sound effects in the form of a computer controlled speech synth which recited "Happy Birthday, Dear Christopher" in an endless loop, more or less loudly depending on who was playing with the equaliser! HE's Quizmaster added a few bleats and flashes to the proceedings, and when one gentleman wanted to know why we didn't have the HE

The ASP computing stand is besieged by earnest enthusiasts ready to have a go on one (or several!) of the micros on trial.



Bassman up and running, we had to explain that it was because we couldn't stock enough batteries to have everything going at once. The real reason may have had something to do with the noise level on the stand.

On the next-door stand, Steve Ireland G3ZZD, Ham Radio's Editor was chiefly engaged in operating the special station, GB4 HRT, which they had set up for the show, along with a band of helpers. Conditions on the first day proved poor for DX calling, so they put the station to good use by calling out to visitors in transit, and guiding them in to the exhibition.

On the other side of the exhibition hall, the Computer magazine staff were manning their own stand, including several micros for visitors to try out for themselves.

Opposite our stand, the British Amateur Electronics Club's stand, courtesy of ASE, featured among other devices a magnificent custom amplifier for keyboards or guitars, complete with flanger, chorus, octave and two kinds of fuzz, with a complete set of equalisation controls for each of the two channels. The builder, Tony Kozary, who had used circuits from various sources, gave us a demonstration using a clef synthesiser and then let me try my guitar on it. This brought a lot of closet guitar players out of the woodwork, including man-of-many talents Phil Walker, ETI's Ian ('I really only play the mandolin') and your own editor, who knew three chords, all very loud!

Anyone interested in the BAEC can find their address in Monitor this month.


Trial And Triumph

BP Oil's display consisted of several winning robots from their **Builderobot Competition 1983**, and a continually-running video showing the actual finals of the competition, a human drama plumbing the depths of despair as complicated and lovingly-crafted pieces of machinery failed to operate to order despite last minute surgery, and the pinnacles of triumph, not to mention incredulity, as the winning robot completed its course, captured the cube and returned to its starting point faster than most eyes could follow it. The winning time was slightly over four seconds. Note for designers: the more closely the robot is tailored to the task designated, the more likely it is to work! While many a sophistication proved fodder for untimely breakdowns.

At the back of the hall, the Micro Robotics Arena set up by the Association of London Computer Club's Micro-Robotics Group showed off a number of small robots in an enclosure, presumably to stop them from escaping and terrorising the crowd (a function amply fulfilled by the Tomorrow's World Radio Controlled car racetrack a few stands away). Alongside, several magnificent fantasy models including a two-foot high Dalek, and the Dalek commander, Davros, in his chariot, sculpted by the King of the Beasties, Robin Hill, were on display.

In the lunch hour the band from the

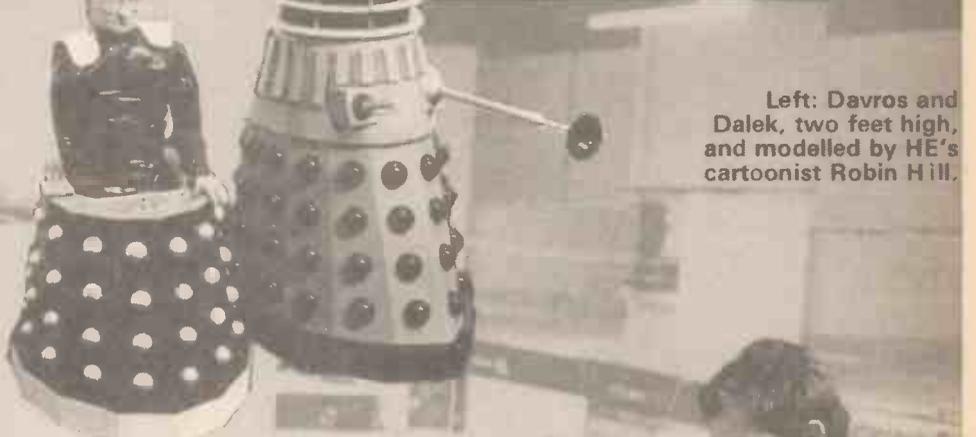Right: The Fratton Bargain Shop's multi-track railway layout, closely watched by its constructors.



Left: Davros and Dalek, two feet high, and modelled by HE's cartoonist Robin Hill.

Right: Trevor Butler G6LPZ drives Ham Radio Today's special station.



stand took it in turns to snack off, grab a sandwich, have a pint, and circulate among the stalls looking out for hardware bargains, tamper with Clef Products' range of keyboard that failed for the second consecutive year to get any recognisably musical sound out of their microsynth, which in other, more skilful hands can sound like a whole band), queue patiently for a go on the bank of arcade games supplied by C.B.S. ColeVision and meet up with visiting authors.

I didn't actually attend any of the lecture program which ran throughout most of each of Breadboard's three days, but others who did tell me that there were plenty of searching questions coming from the audience, and quite a few answers from the blackboard end. Major attractions were electronic music and holographics, and indeed there was a steady hum of music all the time from one or another of the stands with keyboards or musical equipment on show.

On Sunday afternoon, we wiped the

whole business up by offering obsolete ETI and HE projects (as seen) to anyone showing a current issue of the magazine in question. Lucky comers got away with anything from a piece of bench equipment to a miscellaneous circuit board with a few components clinging to it — none of it, of course, supposed to be working, but who knows? One or two people actually bought extra copies to have a second go at the lucky dip. This unannounced extra came about because of the change of offices: we had a lot of cupboards to empty. So don't expect it every year...

What of 1984? Where and when? We don't know yet, but you can expect to see an expanded Breadboard this year, with emphasis on practical demonstrations of hardware, and more electronic bargains — so start planning your November expedition now, because this is our chance to meet the readers unhampered by the paraphernalia of the office, quite apart from any other of numerous benefits. Who says the staff aren't there to enjoy themselves?

BUYLINES

Sinewave Generator

The variable resistor RV1 is specified as having a single-pole single-throw switch. These types are not usually available, but a component with a DPDT switch may be used. Not included in the Parts List is the battery holder; this is a standard type and may be obtained from **Bicc-Vero**.

LP1 is given a type GE 1835: this will be difficult if not impossible to obtain! A near equivalent can be had from **Maplin** under the number WL74R, but it may be necessary to alter the value of R7 to obtain the best results.

The frequency determining capacitors require a special mention. Capacitors C3 — C14 require to have their values matched to within one per cent of the stated value. So for example, take C14: the nominal value is 100pF, which means the value must lie within the range 99 — 101pF if the stated frequency range and

stability is to be achieved. Similarly with the other capacitors. Note that the capacitor tolerance itself need not be small; ten to twenty per cent components would be acceptable.

One source for the components is **Maplin**, and a careful check through the capacitor index page will reveal the types to obtain. For C2, 7, 8, 16, 18, 20, types given as "Monocap" are suitable; for C3 to C6, "reversolytic" may be used. Other capacitors may also be found in this manner. The estimated cost, less case and battery holder (which may be omitted if required), is £5.

Metronome

No real buying problems here. All the components are standard and can be obtained from the majority of suppliers who advertise in HE. For

constructors with shallow pockets, a smaller and cheaper loudspeaker, such as **Maplin** YW53H can be used without losing performance.

Estimated cost is around £5. This figure does not include the case or PCB, and includes the cost for the cheaper loudspeaker. The PCB, as usual, is available from HE's PCB service.

Chess Timer

A number of components require mention but most are not too difficult to obtain. The first is the 4060 type IC. This type is not widely advertised but can be obtained from **Enfield Electronics**.

The **Maplin** piezo buzzer is an unmounted device, which means that wire connections must be made very carefully, to avoid damage. An alternative is to use a ready mounted device such as the PB2720. This is available from **Electrovalue**. The switch used is of the miniature type and generally available.

The cost for the project is estimated at £4, excluding the case and the PCB. The PCB is available from HE's own PCB service, if you care not to make your own.

Tomorrow's Self-Build Radio Controlled Car Kits



NOW AVAILABLE!

Complete Car Kit and Transmitter Kit

Clear build-up instructions included

only **£9.95** + 50p P&P

Also

Porsche 935 Turbo Kit (2 speed)

Kit includes transmitter and full build-up instructions

only **£17.00** + 50p P&P

Order now from:-

Tomorrow's World
Car Kit Dept.,
Hadleigh Road Ind. Estate,
Hadleigh Road,
Ipswich, Suffolk.

Tel: Ipswich (0473) 59175

- Please send me:-
- Lamborghini Kit
 - BMW M1 Kit
 - Porsche 935 Kit

Name _____
Address _____

Please allow 14 days delivery in U.K.

hobbyboard

The Complete Printed Circuit Workshop COMPUTING AND ELECTRONICS Project development materials

COMPUTER ADD-ON / INTERFACE
PROTOTYPING SYSTEM FOR USE
ON MANY HOME COMPUTERS
INCLUDING ZX SPECTRUM & ACE



This system, designed and manufactured by Kelan, provides an attractively styled moulded case, pre-patterned PCB, 28 way connector, can be cut to any size, user port extender, and 9 way PCB mounting 'D' connector to add-ons. Custom designed circuits may be easily built from this kit with a highly professional finish. Order ref HB/2090 £9.50.

HOBBYBOARD CATALOGUE

Newly Published Full Catalogue price £1.50 (refundable with 1st order over £10)

Please send by return:-

QTY	REF	DESCRIPTION	PRICE	TOTAL

Full Catalogue (see above) £1.50

Price inclusive of VAT & carriage (U.K.). Please allow 21 days for delivery. Cheques, PO's or signed Access orders welcomed. Overseas customers please add extra post & packaging. **TOTAL**

NAME _____

ADDRESS _____

HE/3/84



a division of
KELAN ENGINEERING LTD.
Hookstone Park,
Harrogate, N. Yorks.



3Hz—3Mz

Sine Wave

Generator

Based on a Wein bridge, this sine wave oscillator will give you a wide range and clean output in return for easy construction and an economical price. Sounds like a good deal.

J E Aman

PROBABLY the least complicated and most reliable sine wave generator is the Wien bridge type. It incorporates a bridge network, usually in the feedback loop, to determine the frequency of oscillation (f_0).


The bridge itself is an R-C network (Figure 1), which consists of both a series and a parallel R-C circuit. By using a two-stage amplifier to produce a complete phase shift (360°), a circuit can be constructed using a Wien bridge in a positive feedback loop that will oscillate at a frequency determined by the formula $f_0 = 1/2\pi RC$.

A certain amount of attenuation or loss of the positive feedback signal results from the bridge circuit design. The reactive branch of the bridge constitutes an AC voltage divider so that, at the frequency of oscillation, it creates a lead/lag voltage cancellation, and hence no effective phase shift.

But at any other frequency there is a phase shift and, as a result, the attenuation of the positive feedback is too great to sustain oscillation. Since only part of the signal is fed back to the input, the amplifier needs to have

a specific gain that will counteract the effect of the Wien bridge attenuation. The loss in the bridge can be calculated, and it turns out that the network attenuation brings the positive feedback signal to $1/3$ the level

Figure 1. The R-C network which makes up the Wien bridge oscillator.

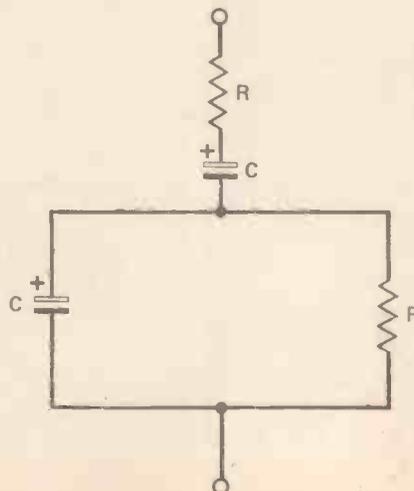

of the output. So, the gain of the amplifier must be at least three to sustain oscillation.

This gain is controlled by means of a second feedback loop. Since the first amplifier has an open loop gain of many hundreds, the second feedback loop is negative and this holds the overall gain at three.

At frequencies other than f_0 , the positive feedback will be too small to sustain oscillation. The negative feedback, which is resistive and always in phase, will then dominate.

The circuit of Figure 2 shows an oscillator that will sweep over a large frequency range up (from below 3Hz to 3MHz) with low distortion (typically less than 0.2% at 1kHz). It operates from a PP3 9V battery and delivers approximately 2.5 volts peak to peak, drawing around 10mA. From the battery the frequencies covered by the six ranges are:

1. 3 — 30Hz
2. 30 — 300Hz
3. 300 — 3kHz
4. 3kHz — 30kHz
5. 30 — 300kHz
6. 300Hz — 3MHz



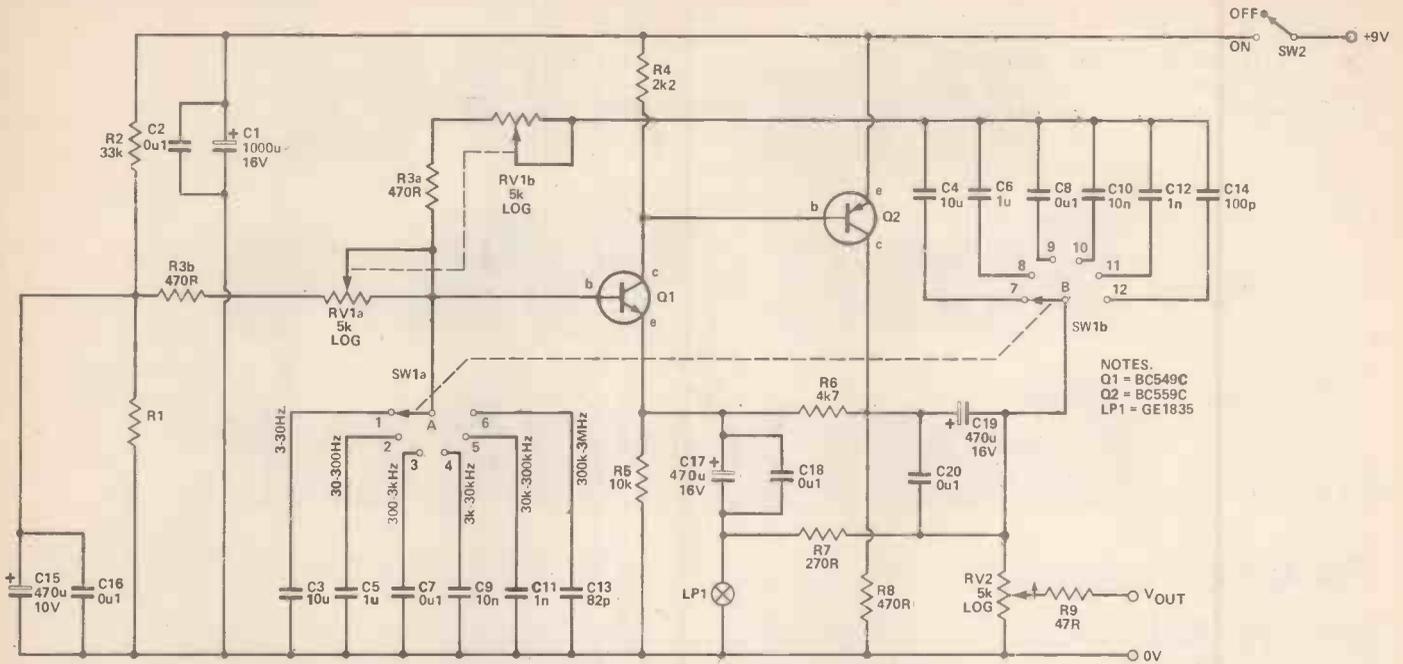


Figure 2. The Circuit. Note that R3a and R3b are two separate resistors. This diagram shows the gain controlled by a filament bulb. See also Figure 3.

Circuit Design

With a 9V supply line in mind, Q2 is selected for power and current capability, together with wide bandwidth and low noise. The BC559C was chosen since it meets all the requirements, ie 200MHz bandwidth, low noise and high gain.

Collector current for Q2 is set by R8, which is chosen to drop half the supply voltage while passing 10mA. This current is low enough to keep noise at a reasonable level and still drives peak currents into, say a 600 ohms load: therefore $4V5/10mA \cong 470R$.

Q1's collector current should be a small fraction of that of Q2, for low noise; say, a few percent. This transistor also wants to be a low noise type. Its collector current, I_c , is again set by its collector resistor, R4. The resistor should not be too large, though, as this would multiply the effects of stray capacitance. A 2k2 seems a good compromise, because since R4 has about 0V6 across it from the base emitter junction of Q2, the collector current is $0V6/2k2 \cong 300uA$, or 3% of Q2. R5 is chosen so that Q1 emitter is a volt or two below Q2 collector, ie 3V, therefore its value is $3V/300uA \cong 10k$.

Considering the current gain of Q1, R1 and R2 are chosen to bias its base at around half the supply. Their values are not critical, but the current through R1 should be five to ten times the base current of Q1. R1 is bypassed with C15, which is large enough to be a virtual AC short circuit at the lowest frequency, while C16 effectively bypasses any inductance that C15 may exhibit at high frequencies. C18 and C20 perform the same function.

R6 provides current feedback to improve stability and is chosen for the lowest value that won't load the output. The negative feedback, and

hence the gain, is controlled by a variable resistance. This variable can take the form of a thermistor, a pair of diodes, a low current lamp filament, or even an FET in more sophisticated circuits. Two arrangements are shown here — the thermistor and the filament lamp. Both work very well by increasing the negative feedback when the output signal increases. The filament is much less expensive than the thermistor but may be harder to find!

The bulb used, a GE 1835 has a cold DC resistance of approximately 110 ohms, and together with R7 (equal to 270 ohms), provides the necessary gain of three to establish oscillation. Both devices change temperature and resistance according to the amount of current flowing through them.


The Rs and Cs of the Wien bridge circuit are chosen to give a 10:1

range on each selected position. A dual 5k pot was chosen to vary the frequency because, as a relatively low impedance, it allows the use of slightly larger capacitors: these, won't be so affected by stray capacitance at the high frequency end. The 470 ohm resistors R3 a, b set the maximum high frequency on each range.

Construction

No great problems here. In fact this project, for its performance, is incredibly easy to build. The PCB helps this, as well as keeping the response more uniform. The capacitors should be close tolerance or selected for the Wien bridge, to keep the frequency dial accurate on all ranges. Leads from the Wien bridge pots and switch should be as short as is practical.

Figure 3. A different method of gain control, where R7 and LP1 are replaced with an R53 thermistor.

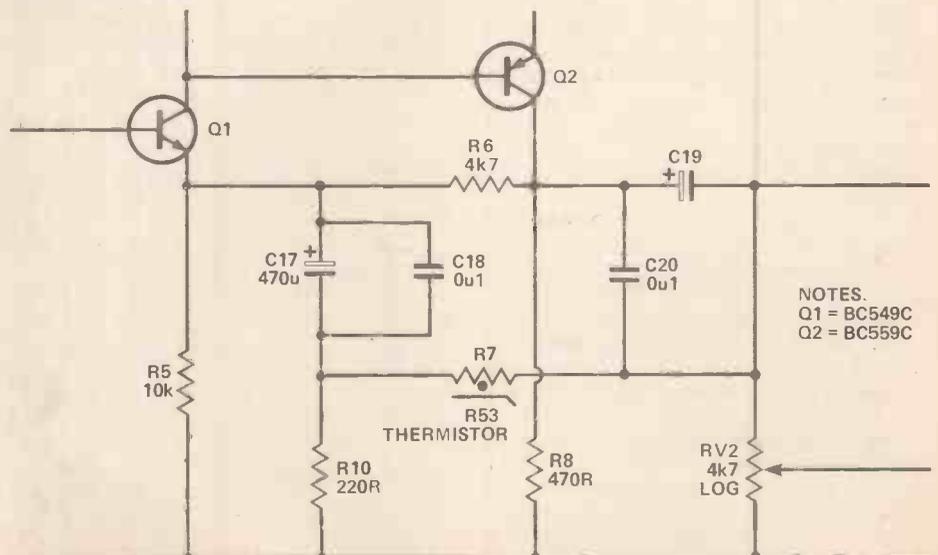

NOTES.
Q1 = BC549C
Q2 = BC559C

Figure 4. The PCB overlay, showing the LP1/R7 arrangement. Note the cluster of components mounted on SW1a, shown in the picture below.

Parts List

RESISTORS

(All 1/4 watt 5% carbon film)

R1	47k
R2	33k
R3a, b, R8	470R
R4	2k2
R5	10k
R6	4k7
R7	270R *
R9	47R
R10	220R *

(* See Figure 3)

POTENTIOMETERS

RV1a, b	5k	dual long pot
RV2	5k	log pot with SPST mains switch

CAPACITORS

C1	1000u	16V radial electro
C2, 7, 8, 16, 18, 20	0u1	ceramic
C3,4	10u	16V non-radial electro
C5, 6	1u	16V non-radial electro
C9, 10	10n	polyester
C11, 12	1n	polyester
C13	82p	ceramic
C14	100p	ceramic
C15, 17, 19	470u	16V radial electro

(NB: Wien bridge capacitors, C3—14, should be selected to values within 1% of that specified.)


SEMICONDUCTORS

Q1	BC549C
Q2	BC559C


MISCELLANEOUS

SW1a, b 2-pole, 6-way rotary
 Case, 159 x 154 x 64mm; PCB;
 knobs; PP3 battery and clips;
 terminals, wire, solder etc.

BUYLINESpage 26

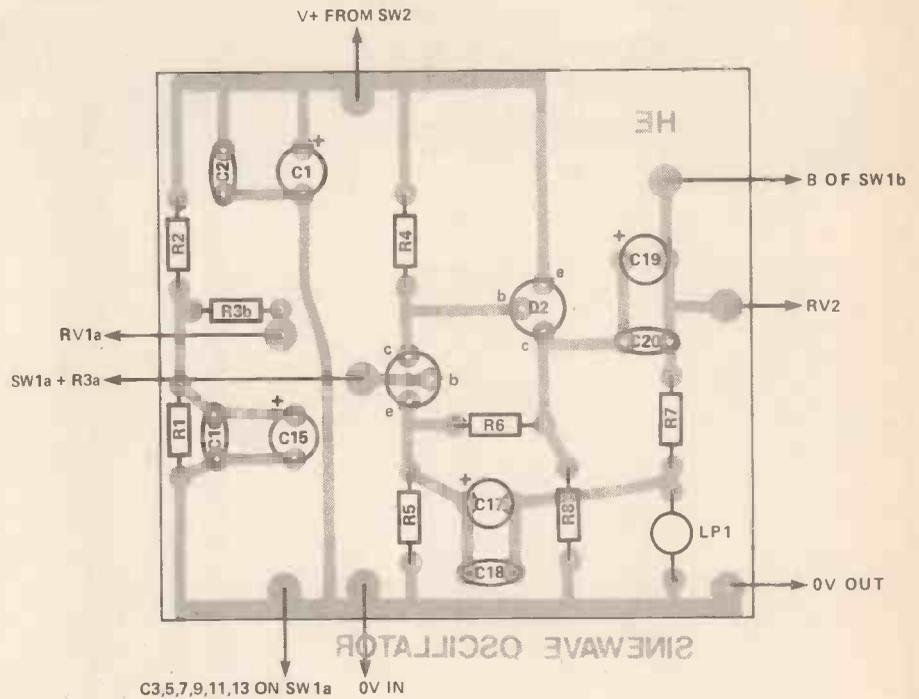

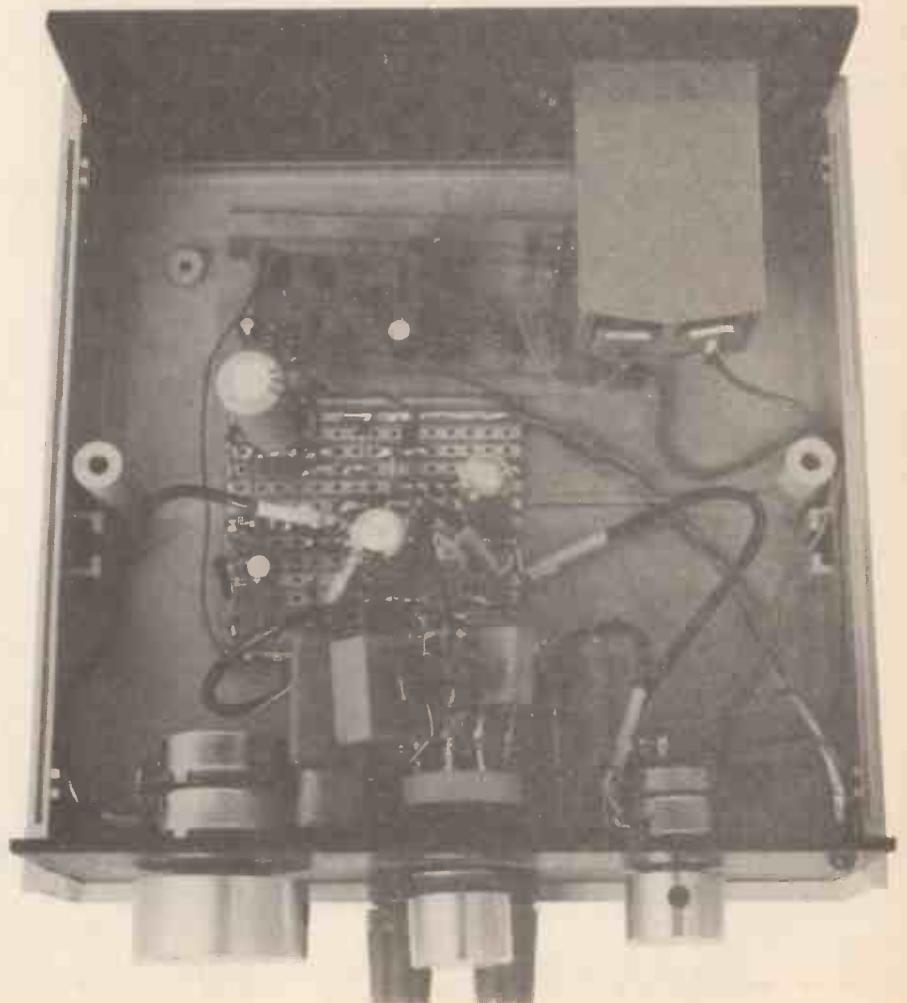This photograph shows the author's sine wave generator, which works for its living. The circuit here is built on Veroboard; the small PCB is an auto power down circuit which we have not included in the project. Note the cluster of Wien bridge components mounted on SW1. The grey box, top right, contains the battery — a simple modification.





ENFIELD ELECTRONICS

208 Baker Street, Enfield,
Middlesex. EN1 3JY. Tel: 01-366 1873



TRANSISTORS

AC125	30p	BC183C	12p	MJE2955	110p	ZTX303	20p	2N1304	80p
AC126	30p	BC183L	12p	MJE3055T	80p	ZTX304	20p	2N1305	80p
AC127	30p	BC183LB	12p	MPSA06	25p	ZTX330	30p	2N1307	70p
AC128	30p	BC184	12p	MPSA96	30p	ZTX500	18p	2N1308	80p
AC132	90p	BC184B	12p	MPSU05	65p	ZTX501	18p	2N1613	36p
AC141	30p	BC184L	12p	OC22	150p	ZTX503	18p	2N2222A	30p
AC142	30p	BC186	30p	OC23	150p	ZTX504	30p	2N2646	68p
AC176	30p	BC187	30p	OC26	200p	ZTX531	30p	2N2904A/5A	30p
AC187	30p	BC212A	14p	OC35	220p	2N686	35p	2N2906A	60p
AC188	30p	BC212L	12p	OC41	75p	2N689	45p	2N2907A	30p
AD149	80p	BC213	12p	OC42	75p	2N699	45p	2N2926B	12p
AD161	45p	BC213B	12p	OC70	60p	2N706A	26p	2N2926R	12p
AD162	45p	BC213L	12p	OC76	60p	2N708	30p	2N3053	30p
BC107	12p	BC214	12p	OC81	60p	BC237	18p	2N3054	75p
BC107A	14p	BC214B	14p	OC82	60p	BC238B	18p	2N3055E	60p
BC107B	14p	BC214L	12p	OC84	50p	BC307	18p	2N3152	20p
BC108	12p	BF194	14p	OC84	50p	BC308	14p	2N3615	200p
BC108A	14p	BF195	14p	OC84	50p	BC327	16p	2N3702	12p
BC108B	14p	BF198	14p	OC84	50p	BC328	16p	2N3703	12p
BC109	12p	BF199	14p	OC84	50p	BC337	16p	2N3704	12p
BC109B	14p	BF200	14p	OC84	50p	BC341	16p	2N3705	12p
BC109C	14p	BF244B	20p	OC84	50p	BC348	16p	2N3706	12p
BC140	35p	BF256	35p	OC84	50p	BC441	16p	2N3707	12p
BC141	35p	BF257	35p	OC84	50p	BC477	40p	2N3708	12p
BC142	35p	BF258	35p	OC84	50p	BC517	40p	2N3711	200p
BC143	35p	BF259	35p	OC84	50p	BC547	15p	2N3717	200p
BC147	12p	BF594	40p	OC84	50p	BC548	15p	2N3722	200p
BC148	12p	BF595	30p	OC84	50p	BC549	40p	2N3726	200p
BC157	12p	BF596	30p	OC84	50p	BC556	20p	2N3819	25p
BC158	12p	BF597	30p	OC84	50p	BC557	16p	2N3820	45p
BC159	12p	BF598	30p	OC84	50p	BC558	16p	2N3823	50p
BC160	50p	BF625	30p	OC84	50p	BC559	16p	2N3826	100p
BC161	45p	BF626	30p	OC84	50p	BC560	16p	2N3827	15p
BC162	15p	BF627	30p	OC84	50p	BC561	16p	2N3828	15p
BC163	15p	BF628	30p	OC84	50p	BC562	16p	2N3829	15p
BC164	15p	BF629	30p	OC84	50p	BC563	16p	2N3830	15p
BC165	15p	BF630	30p	OC84	50p	BC564	16p	2N3831	15p
BC166	15p	BF631	30p	OC84	50p	BC565	16p	2N3832	15p
BC167	15p	BF632	30p	OC84	50p	BC566	16p	2N3833	15p
BC168	15p	BF633	30p	OC84	50p	BC567	16p	2N3834	15p
BC169	15p	BF634	30p	OC84	50p	BC568	16p	2N3835	15p
BC170	20p	BF635	28p	OC84	50p	BC569	16p	2N3836	15p
BC171	13p	BF636	25p	OC84	50p	BC570	20p	2N3837	15p
BC172A	12p	BF637	25p	OC84	50p	BC571	20p	2N3838	15p
BC173	13p	BF638	25p	OC84	50p	BC572	20p	2N3839	15p
BC174	13p	BF639	25p	OC84	50p	BC573	20p	2N3840	15p
BC175	20p	BRV39	40p	OC84	50p	BC574	20p	2N3841	15p
BC176	20p	BSX20	30p	OC84	50p	BC575	20p	2N3842	15p
BC177	25p	BSX21	35p	OC84	50p	BC576	20p	2N3843	15p
BC178	20p	BSX22	30p	OC84	50p	BC577	20p	2N3844	15p
BC179	25p	BSX23	35p	OC84	50p	BC578	20p	2N3845	15p
BC180	25p	BSX24	35p	OC84	50p	BC579	20p	2N3846	15p
BC181	25p	BSX25	35p	OC84	50p	BC580	20p	2N3847	15p
BC255	25p	BSX99	35p	OC84	50p	BC654	20p	2N3921	15p
BC256	25p	BSX00	35p	OC84	50p	BC655	20p	2N3922	15p

The Complete Hobby Electronics Cumulative Index


The definitive key to every article published in
Hobby Electronics from November 1978 to
December 1983.

FEATURES

	Issue	Page		Issue	Page
555 Projects	May 79	38	Deep Space Communications	Dec 78	13
AB Circuits	May 79	33	Dictation Machines	Nov 81	54
Aces High	May 83	47	Digital Counters And Timers	Jun 82	71
A Good Joint Is Hard To Find	Feb 82	53	Digits On Display	Nov 81	14
Aerials	Oct 81	15	Directory Of Electronic Kits And Modules	Feb 83	37
Aerial Tuners	May 79	60	Directory (Update)	Apr 83	41
Affordable Computer, The	Apr 82	45	Display Techniques	Jun 79	13
Anatomy Of A Space Shuttle	Apr 81	16	Edison Effect, The	Nov 78	27
Basic Programming	Jan 79	21	Electronic Aids For The Disabled	Jul 81	15
Beginner's Guide To Construction	Aug 82	28	Electronic Espionage	Jul 80	28
Beginnings Of Real TV (The)	Mar 81	18	Electronic Games	Oct 79	38
Binary Numbers	Jul 79	23	Electronic Housekeeping	Nov 82	26
Book Reviews	Jan 83	68	Electronic Music (1)	May 79	19
Book Reviews	Jun 83	62	Electronic Music (2)	Jun 79	4
Burglar Alarm Installation	Aug 79	14	Electronic Revolution, The	May 82	39
CA3130 Projects	Feb 79	38	Electronic Timekeeping	Sep 79	50
Cable And Satellite Television	Sep 83	25	Electronics From Scratch	Nov 78	9
Capacitors	Apr 79	29	Electronics In Diagnostic Medicine	Sep 81	15
Car Electronics (1)	Dec 81	14	Electronics In Musical Instruments	May 81	18
Car Electronics (2)	Jan 82	60	Electronics In Photography	Jul 80	15
Cassette Decks And Tape	Jul 79	13	Electronics In Warfare	Apr 79	38
Choosing A Calculator	Dec 78	60	Electronics On Wheels	Mar 80	38
Circuit Symbols	Nov 78	40	Equalisation In Audio	Jul 82	60
Citizens Banned	Jun 70	38	Expanding The ACE	Aug 83	42
CMOS Special	Jan 80	23	Fault-Finding Made Easy	Oct 82	15
Computer Glossary	Feb 79	57	Feedback	May 79	15
Computer Talk	Apr 82	41	Feedback	Mar 82	36
Creative Recording	Apr 82	76	FET Special	Sep 79	59
Crossing Your Bridges	Mar 79	13	Finishing Touches	Mar 83	12
Crossover Network	May 80	59	Fixed Resistors	Jul 79	28
Cygnus XI	Nov 78	68	FX-Computer Review	Oct 83	16
Data Supplement Part 1	Nov 79	—	A Good Joint (Soldering Technique)	Feb 82	53
Data Supplement Part 2	Dec 79	—	Hands Off (Meter Review)	Sep 82	47
Decibels	Jul 79	44	HC6010 DMM (Meter Review)	Dec 82	65

Complete Cumulative Index


	Issue	Page		Issue	Page
Hifi Specifications	Nov 78	41	Planning On Success	Sep 82	49
History Of Radioactivity	Feb 79	25	Pocket TV	Mar 82	32
Holograms	Feb 79	46	Project Daedelus	Jan 79	38
Home Computers	Nov 78	60	Project Fault-Finding	Dec 79	41
Home Computing	Nov 79	16	Power From Satellites	Aug 79	38
Home Electronics	Oct 80	44	Power To The People	Feb 80	51
Housekeeping For Electronics	Nov 82	26	Radio (1)	Jun 81	24
How A TV Receiver Works	Dec 81	61	Radio (2)	Jul 81	26
How To Use An Oscilloscope	June 81	15	Radio Control	Aug 81	15
I Almost Met . . .	Dec 83	42	Radio Controlled Gerbil	Apr 83	12
In Car Entertainment	Aug 80	11	Radio Control World	Sep 79	38
Inside Colour TV	Apr 82	16	Radio Servicing Tips	Dec 78	51
Inside Teletext	Sep 80	13	Reverb Revealed	Jun 82	38
Instant Circuit Layout	Feb 79	63	RF Breakthrough	Jun 80	37
Intellivision TV Game	Sep 80	29	Robots	Nov 78	34
Interfering Waves	Mar 79	69	Short Wave Aerials	Mar 79	41
Internal Resistance	Jun 79	31	SI Units	Jul 79	60
Introduction To Test Gear	Mar 79	33	Solar Cells	Jul 82	9
Jargon	Nov 78	70	Solder	Jan 79	63
Junction FETs	Dec 83	44	Spacelab	Jan 80	38
KEZY Does It	Feb 80	38	Spotlight On The Spectrum	Aug 82	14
Lasers	Dec 78	45	Story Behind Stereo	Nov 80	18
Light And Power From DC			Substi-Tutorial	May 81	28
Supplies	Jan 83	10	Synthesiser Secrets	Oct 81	53
Look In The Book	Feb 83	59	Synthesiser Secrets	Nov 81	28
Making PCBs	Dec 78	54	Synthesiser Secrets	Dec 81	29
Makin' Tracks (PCB Making)	Feb 82	11	Telephones	Apr 79	8
Membrane Switches	Oct 81	27	Television Receivers	Dec 79	31
Metal Locators	Nov 78	66	Tesla Controversy, The	Dec 78	70
Metertech DVM Review	Aug 82	37	Thyristors	Sep 79	14
Micro-History	May 82	26	Tools	Aug 78	33
Micro-Mania (Inside			Tools And Test Equipment		
Microcomputers)	Apr 82	36	Survey	Apr 83	36
Microprofessor Review	Nov 82	54	Tools For The Trade	Apr 83	24
Microwave Cooking	Oct 79	50	Top Ten Electronic Games	Jan 81	19
Models Galore At Sandown	Aug 81	20	Transducers	Jan 82	43
Moving Coil Multimeters	May 79	22	Transducers In Audio	Nov 78	55
Narrow Bandwidth Television (1)	Apr 80	40	TV Aerials	Apr 79	19
Narrow Bandwidth Television (2)	May 80	54	TV Broadcasting	Nov 79	42
New Look For Communications			TV Shopping	Mar 79	45
Satellites	Mar 79	63	TV Signal Propagation	Mar 79	21
Next Instalment (Multivibrators)	Apr 79	51	UOSAT Report	Aug 81	56
ORIC 1 Review	Jul 83	36	UOSAT Report	Oct 81	59
Oscilloscope, The	Feb 81	18	Understanding Bias	Dec 78	36
Oscilloscope Revisited, The	Mar 82	39	Understanding Component		
OST Rules OK	Feb 79	70	Values	Jun 82	55
PETing It Together	Mar 80	24	Understanding The Hall		
Photocells	Dec 78	48	Effect	Sep 81	23
Piezo Electricity	Jul 80	56	Unijunction Transistors	Dec 79	19
Pinball Wizards	Jan 79	57	Valdemar Poulsen	Jan 79	14

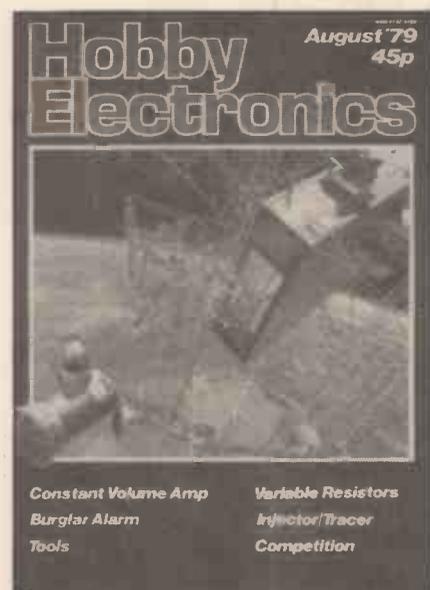

	Issue	Page		Issue	Page
Varicap Diodes	May 79	67	Big Ear, The	Dec 82	80
Variable Resistors	Aug 79	18	Bike Alarm	Apr 82	72
Video Discs	Mar 82	24	Bike Siren	Mar 82	28
Video Tape Recorders	Feb 79	12	Cable And Satellite Television	Sep 83	25
Viewdata	Jan 79	34	Cable Tracker	May 82	65
View Into Video Discs	Dec 80	18	Car Alarm	Feb 79	66
Voyager Car Computer	Mar 83	62	Car Cassette Power Supply	Dec 81	49
A Zener Diode Primer	Dec 83	20	Car Interior Delay Light	Nov 83	26
ZX81 64K RAM Pack (Review)	Jun 82	65	Car Power Booster	Jul 80	23
ZX81 Software Review	Jun 82	66	Car Rev Counter	Jan 81	27
ZX81 Review	May 82	20	Casanova's Candle	Mar 79	16
ZX Interfaces Explained	Aug 82	10	CB Push To Talk Switch	Jun 83	45
ZX Software Reviewed	Jul 82	59	CB Selective Caller	Jan 83	63
			CB Squelch Unit	Oct 82	58
			Chuffer	Jan 81	54
			Cistern Alarm	Apr 79	48
			Crosshatch Generator	Jan 80	31
			Combination Lock	Sep 79	8
			Combination Lock	Oct 81	21
			Computer PSU	Jul 82	57
			Constant Volume Amplifier	Aug 79	61
			Continuity Checker	Jun 81	20
			Continuity Tester	Dec 83	56
			Designing Power Supplies	Jun 82	12
			Development Timer	Sep 80	53
			'Diana' Metal Detector	Sep 81	10
			'Diana' VCO	Nov 82	22
			Digibell	May 79	45
			Digi-Die	Jan 80	47
			Digital Capacitance Meter	Apr 82	25
			Digital Clock	Nov 78	30
			Digital Dice	Mar 82	11
			Digital Frequency Meter	Apr 80	33
			Digital Multivoltmeter	Aug 82	20
			Digital Speedometer (2)	Dec 80	13
			Digital Speedometer (2)	Jan 81	42
			Digital Thermometer	May 82	10
			Digitester Part 1	Jan 83	23
			Digitester PSU	Feb 83	56
			Direct Reading Frequency Meter	Nov 81	38
			Drill Speed Controller	Jun 79	68
			Doorbell Monitor	Apr 81	32
			Doorchime	Dec 81	66
			Doorphone	Oct 81	10
			Double Dice	Nov 80	65
			Dual Engine Driver	Apr 82	11
			Dual Purpose Power Supply	Nov 83	54
			Drum Synthesiser	Dec 81	18
			Echo Reverb Unit	May 82	33
			Egg Timer	Jun 80	43


PROJECTS

Aerial Without Wings	May 83	27			
Amplifier, 2 Watt	Jun 80	54			
Amplifier, 18 Watt Stereo	Jul 80	23			
Amplifier Module, 5080 25 Watt	Mar 80	11			
Analogue Audio Frequency Meter	Oct 79	45			
Audio Analyser (1)	Aug 82	53			
Audio Analyser (2)	Sep 82	57			
Audio Level Meter	Oct 83	11			
Audio Millivoltmeter	May 81	67			
Audio Mixer	Dec 78	40			
Audio Power Meter	Dec 80	59			
Audio Signal Generator	Feb 81	36			
Audio Signal Generator	May 82	49			
Automatic Greenhouse Sprinkler	Jun 82	48			
Auto Power Down	Apr 83	20			
Autoprobe	Sep 80	37			
Auto Tester	May 83	28			
Auto Wah	Jun 82	25			
Auto Winder	Aug 83	56			
Baby Alarm	Jul 79	57			
Baby Alarm	Oct 81	39			
Background Noise Simulator	Feb 81	42			
Bargraph Car Voltmeter	Dec 79	59			
Bassman	Dec 83	29			
Battery Charge Monitor	Dec 80	28			
Battery Eliminator	Nov 80	24			
Battery Warning Device	Jun 83	30			
BBC Micro/HEBOT Interface	May 83	62			
Bedside Radio	Nov 78	45			
Bench Amplifier	Jan 81	37			
Bench PSU	Sep 80	63			
Bicycle Speedometer	Mar 81	37			

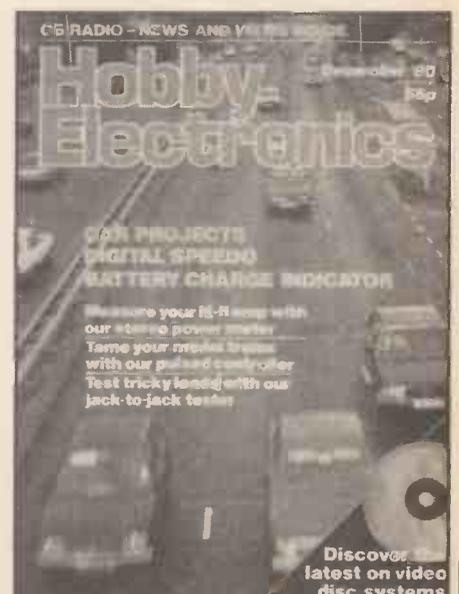


Complete Cumulative Index

	Issue	Page		Issue	Page
Electronic Dice	Dec 78	57	Intelligent NiCad Charger	Jan 82	26
Electronic Doorbuzzer	Jul 81	42	Intruder Alarm	Oct 80	59
Electronic Ignition	Apr 80	11	Intruder Confuser	Jan 82	38
Electronic Ignition	Aug 81	10	Jack Lead Tester	Dec 80	49
Electronic Metronome	Dec 78	10	'Junior' Slot-Car Controller	Sep 82	9
Electronic Organ (1)	May 81	11	Kitchen Timer	Oct 80	13
Electronic Organ (2)	Jun 81	43	Lamp Dimmer	Sep 79	33
Electronic Organ (3)	Jul 81	20	LED Tachometer	Aug 79	24
Electronic Organ (4)	Aug 81	42	LED VU Meter	Nov 81	30
Entryphone	Oct 81	10	Light Beam Telephone	Nov 81	10
Envelope Generator	Jun 79	19	Light Chaser	Mar 79	7
Envelope Generator	Jun 81	51	Light Dimmer	Oct 80	33
EPROM (6502-Based) Programmer			Light Meter	Dec 83	12
Part 1	Mar 83	20	Linear Scale Ohmmeter	Jul 79	20
EPROM Programmer Part 2	Apr 83	28	Lofty	Dec 82	74
Flashpoint Alarm	Oct 82	9	Low Cost Alarm	Dec 82	70
Flash Trigger	Jan 79	59	Low Power Pilot Light	Sep 81	21
Fog Horn	Jun 80	64	Mains Adaptor	Sep 81	42
Freezer Alarm	Oct 80	40	Masthead Amplifier	Feb 82	42
Gas Detector	Aug 80	57	Medium Wave Radio	Feb 81	56
General Purpose Amplifier	Jan 81	37	Metronome	Jun 80	32
Giant Circuit Supplement	Oct 83	34	Metronome	Nov 81	61
Graphic Equalizer	Jan 79	7	Microbe Radio Control Systems	Jun 80	11
Graphic Equalizer, Guitar	Dec 81	10	Microlog	Dec 82	9
Gripometer	Sep 83	59	Micromix	Sep 80	19
GSR Monitor	Jun 79	8	Microtrainer Part 1	Jun 82	60
Guitar Fuzz Box	Mar 81	54	Microtrainer Part 2	Jul 82	52
Guitar Phaser	Sep 80	49	Microtrainer Part 3	Aug 82	57
Guitar Preamplifier	Nov 80	35	Microtraining	Sep 82	25
Guitar Tremolo	Apr 81	39	Miniboard Projects (Vero)	Nov 79	20
Guitar Tuner	Nov 79	61	Miniboard Siren	Mar 80	54
Hazard Flasher	Jul 80	62	Miniclocks	May 80	13
Heartbeat Monitor	Feb 81	13	Minisynth With Memory	Nov 80	13
Hebot (1)	Jun 79	10	Minisynth II	Dec 80	66
Hebot (2)	Dec 79	25	Model Train Controller	Apr 79	15
Hebot (3)	Jan 80	56	Model Train Controller	Dec 80	41
HEBOT II	Nov 82	9	Moisture Gauge	Dec 83	49
High Impedance Voltmeter	Feb 81	26	Movement Alarm	Aug 80	49
Hi-Voltage Meter	Oct 83	28	Multi-Option Siren	Oct 79	58
Hobbycom	Apr 80	17	Negative Voltage Generator	Oct 79	24
Hobby 'Scope Part 1	Jun 83	11	NiCad Battery Charger	Jan 81	50
Hobbytune	Oct 79	23	Nobell Doorbell	Oct 80	67
Home Security System	Aug 79	8	Noiseless Fuzzbox	Feb 82	26
Improved Overload Trip	May 79	71	Odometer, The	Nov 82	46
Incremental Timer	Feb 83	12	Op-Amp Checker	Aug 81	62
Infra-Red Remote Control	Feb 80	27	Overvoltage Circuit	Mar 83	68
Infra-Red Remote Controller	May 81	49	Para-Q	Nov 83	13
Infra-Red Remote Controller			Parking Meter Timer	May 79	27
Part 2	Jun 81	60	Party Grenade	Nov 80	41
Injector/Tracer	Aug 79	48	Passionmeter	Feb 80	10

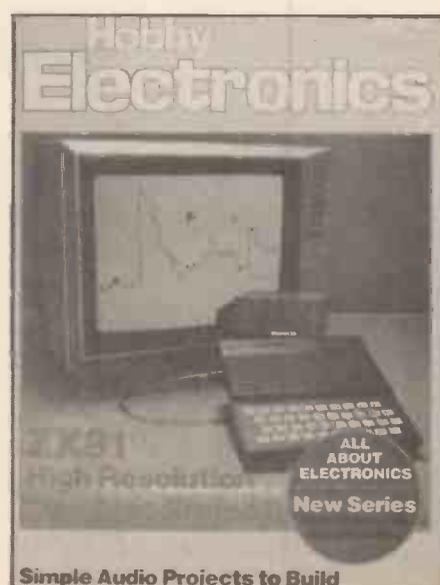

	Issue	Page		Issue	Page
Pass The Loop	Aug 80	41	Sine/Square Wave Generator	Feb 79	19
Pedalboard Organ	Dec 81	32	Slide-Tape-Synchroniser	Dec 82	56
Pedometer/Odometer	Nov 82	46	Slot Car Controller	Dec 79	11
Phase Four	Dec 82	37	Soft Fuzz	Jul 83	12
Photographic Timer	Mar 79	47	Solar Radio	Jul 82	20
Photographic Timer	Mar 81	58	Sound-Into-Light Module	Jan 81	11
Photon Probe	Dec 78	18	Sound Operated Flash Trigger	Jul 80	11
Planning For Success	Sep 82	49	Sound Operated Pressure		
Pocket TV	Mar 82	32	Meter	Sep 83	14
Points Switch	Jul 79	46	Speakers, 5080 System	May 80	64
Pop Amps 1: Microammeter	Jul 79	52	Stall Thief	May 83	20
Pop Amps 2: Follow and Hold	Dec 82	62	Starburst	Sep 79	23
Power Amplifier (1)	May 81	10	Steam Loco Whistle	Mar 81	33
Power Amplifier (2)	Jun 81	49	Stereo Amplifier (Hobit)	Nov 78	20
Power Supply	May 79	9	Stereo Bass Booster	Mar 82	52
Power Supply Unit	Sep 83	54	Stereo Image Expander	Jul 83	52
Preamp, 5080	May 80	28	Stereo Noise Gate	Dec 82	20
Preamplifier (1)	Apr 81	11	Stereo Power Meter	Dec 80	59
Preamplifier (2)	May 81	59	Stereo Voice-Over Unit	Apr 83	60
Programmable Joystick			Switched Mode Power Supply	Jan 83	15
Controller	Aug 83	11	Switched-Tuned Radio	Jan 82	16
PSU Model (5080A)	Mar 80	19	SWR Meter	Aug 82	48
Public Address Amplifier	Mar 81	13	Tanover	July 82	14
Push Button Dice	Dec 78	57	Super-Regenerative VHF		
Push Button Speed Controller	Apr 80	29	Receiver	Nov 81	40
Push Button Volume Control	Apr 80	37	Super Siren	Apr 81	25
Radio Timer	Aug 80	29	Tantrum Stereo Amplifier	Oct 79	10
Railway Track Cleaner	May 80	45	Tape/Slide Synchroniser	Dec 82	56
Reaction Tester Game	Sep 81	58	Telephone Bell Repeater	Oct 81	56
Reaction Timer	Sep 80	25	Telephone Timer (1)	Jun 82	9
Reader's Project: Enlarger Timer	Aug 83	60	Telephone Timer (2)	Jul 82	40
Reader's Project: Simple Stereo			Temperature Controlled Soldering		
Preamp	Nov 83	47	Iron	Oct 80	49
Reader's Project: Simple			Thermometer	Aug 81	23
Tremolo	Jul 83	41	Three-Aspect Signal Lights	Sep 82	39
Rev Counter	Jan 81	27	Ticking Egg-timer	Nov 81	39
RIC Speed Controller	Apr 80	49	Tone Control	Mar 79	27
Ring Modulator	Dec 79	47	Touch Lamp	Oct 81	51
RPM Meter	Aug 81	52	Touch Lamp (continued)	Nov 81	59
Russian Roulette Game	Apr 81	46	Touch Switch	Jan 79	17
RZDZ Radio	Nov 79	51	Touch Switch	Mar 80	44
Scalextric Controller	Dec 79	11	Touch Switch (VMOS)	Sep 80	45
Scalextric Lap Counter	Jan 80	9	Traffic Light Toy	Jun 83	65
Scratch And Rumble Filter	Feb 79	29	Transistor Gain Tester	Apr 79	69
Scratch Filter	Nov 81	19	Transistor Tester	Nov 80	53
Shark	Jul 79	9	Treble Booster	Jul 81	59
Short Wave Radio	Feb 79	8	Tremoleko	Sep 83	36
Short Wave Radio	Mar 80	57	Trump Card	Oct 83	58
Short Wave Receiver	Sep 81	52	TV Amp	Dec 82	25
Signal Powered Loudspeaker Protector	Mar 83	50	TVI Filter	Jul 82	34

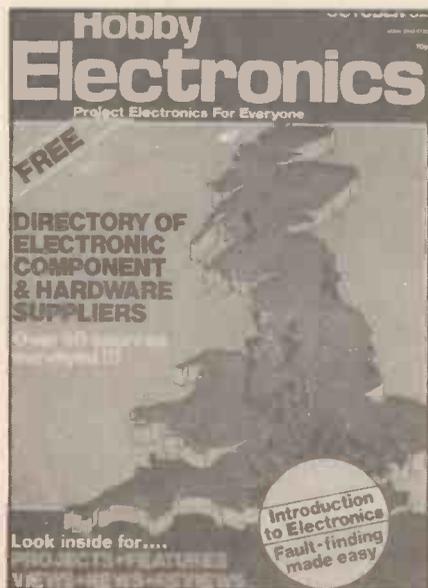

Complete Cumulative Index

	Issue	Page		Issue	Page
Two-Tone Train Horn	Feb 81	48	AF Signal Generator	Dec 79	50
Ultrasonic Burglar Alarm	Jul 81	11	AC Meter Booster	Sep 79	63
Ultrasonic Intruder Alarm	Oct 83	63	Audio Limiter	Jan 80	18
Ultrasonic Switch	Sep 79	45	Automatic Fader	Feb 80	20
Universal Relay Driver	Feb 82	18	Basic Burglar Alarm	Jun 79	53
Variable Bench Power Supply	Aug 81	58	Bedside Radio	Oct 79	72
Variwiper	Jan 79	27	Breadboard/Audio Phaser	Nov 82	68
Voice Operated Switch	May 81	24	Breadboard Tone Controls	Sep 82	34
Volume Expander	Jan 82	54	Breadboard VCO	Oct 82	75
Wah-Wah Pedal	Nov 78	37	CA3080 VCA	Feb 79	32
Watchdog	Oct 80	59	Car Lights Delay	Sep 81	38
Whistle Switch	Aug 83	36	Car Cassette Power Supply	Jan 80	44
White Noise Generator	May 79	63	Cassette-Radio Booster	Jun 80	20
Windscreen Washer Alarm	Apr 81	53	Christmas Tree Lights Flasher	Feb 80	21
Windscreen Wiper Delay	Nov 83	36	Class A Amplifier	Apr 80	23
Windscreen Wiper Controller	Mar 81	30	Clipping Amplifier	May 79	24
Win Indicator	Feb 80	59	CMOS Logic Probe	Apr 79	26
ZX81 High Resolution Graphics Board	Jul 83	17	CMOS Logic Probe	Jul 79	42
ZX Interface Board	Sep 82	14	CMOS Monostable	Dec 79	50
ZX Sound Board	Jun 83	20	Crystal Calibrator	Jun 80	56
			Diode-Transistor Tester	Mar 81	46
			Direct Reading Ohmmeter	Apr 81	45
			Doorbuzzer	Feb 80	17
			Electronic Door Buzzer	Mar 79	25
			Electronic Metronome	Jun 79	41
			Electronic Thermometer	Jun 79	72
			FET Voltmeter	Jul 79	42
			Flash Slave Unit	Aug 79	66
			Gas and Smoke Detector	Aug 79	57
			General Purpose Amplifier	Feb 80	18
			Guitar Practice Amplifier	Aug 79	28
			HF TTL Oscillator	Jan 79	26
			Headlight Warning Indicator	Nov 83	59
			Headphone Amplifier	Sep 79	48
			Heads Or Tails	Jan 80	34
			Home Intercom	Feb 79	28
			Hum Notch Filter	Dec 78	52
			Infra-Red Intruder Alarm	Jul 80	20
			Insect Repellent	Jul 79	41
			Lead Tester	Nov 83	59
			LED VU Meter	Apr 80	48
			Lie Detector	Mar 79	50
			Light Change Detector	Jun 80	46
			Light Sensitive Switch	Dec 78	26
			Linear Scale Ohmmeter	Feb 79	36
			Logic Lock	Jun 79	72
			Low Battery Voltage Indicator	Jun 80	36
			Low Frequency Oscillator	Jan 79	70
			Low Power Flashing Light	Nov 78	71
			Magic Candle	Jul 79	36

QUICK PROJECTS

Audio Mixer	Jun 81	58
Car Light Delay	Sep 81	38
Electronic Metronome	Jul 81	55
Guitar Headphone Amplifier	Dec 81	27
Heads and Tails Game	Mar 82	45
Light Seeker	May 82	55
Light/Water Alarm	Sep 81	28
Seven-Segment Display	Oct 81	45
Signal Tracer	Apr 82	34
Simple Stylus Organ	Nov 81	58
Simple Timer	Jan 82	25
Solar Experiments	Jul 82	25
Sound Switch	Feb 82	64
Substitution Boxes	Nov 81	26
Two-Down-One	May 81	33

SHORT CIRCUITS

555 IC Monostable Circuits	Oct 79	56
555 IC Projects	Mar 79	25
AF Millivoltmeter	Jun 79	49




	Issue	Page		Issue	Page
Mains Interference Suppression	May 79	58	Three Breadboards For	Jun 82	31
Measuring Unknown Capacitors	Nov 78	44	Experimenters	Oct 79	56
Metronome	Feb 80	18	Timer	Mar 80	23
Morse Practice Oscillator	Feb 80	17	Timer, ZN1034E	Apr 79	33
Nanoamp Meter	Apr 79	45	Touch Switch	Jul 79	38
Nanoamp Meter	Jul 79	40	Transistor Checker	Jun 80	62
NiCad Charger	Sep 79	48	Transistor Tester	Nov 78	71
Noise Gate	Jan 80	70	Transistor Tester	Mar 80	33
Noise Limiter	Mar 79	29	Transistor Power Amplifier	Nov 78	49
Noise Limiter	Jul 79	36	Treble Booster	Apr 79	50
One Armed Bandit	Mar 80	72	Treble Booster	Jun 79	40
One Transistor Amplifier	Dec 78	12	Tremolo Unit	Jun 79	11
Phase-Shift Oscillator	Jan 79	70	Tug O' War Game	Oct 80	24
Power Supply With IC			Two Microphone Amplifiers	Jul 79	39
Regulator	Jan 79	33	Two-Tone Alarm	Oct 79	56
Power Supply With Transistor			Two Transistor Noise Source	Dec 78	17
Regulation	Nov 78	64	Two Transistor Radio	Feb 79	32
Pre-Amp with Stepped Gain			Ultrasonic Receiver	Feb 80	19
Control	Jan 79	70	Ultrasonic Transmitter	Feb 80	19
Precision Half Wave Rectifier	Mar 79	19	Unregulated PSU	Nov 78	64
Preselector, 10-30 MHz	Apr 80	23	Voice Operated Fader	Jul 80	45
Power Supply, 5-13V	Feb 79	65	Voltage Controlled Filter	Jul 79	38
PSU with IC Regulation	Jan 79	33	Waa-Waa Unit	Jan 80	44
Quick Transistor Checker	Apr 79	50	Water Alarm	Feb 80	20
Quick Transistor Checker	Jul 79	37	Zener Diode Tester	Sep 79	58
Radio 4 Tuner	Jun 80	36			
Radio Controlled Mixer	Nov 83	58			
Reaction Game	May 79	33			
Regulation Booster	Dec 78	26			
Remote and Touch Volume					
Controls	May 79	35			
RIAA Stereo Pre-Amp	Jan 79	37			
Ringing Tone Monitor	Nov 83	58			
Scratch and Rumble Filter	Aug 79	50			
Signal Injector/Tracer	Jul 79	35			
Simple Amplifier	Mar 79	68			
Simple MW Radio	Feb 80	21			
Simple SW Radio	Feb 80	16			
Simple Timer	Mar 79	68			
Sine To Square Converter	Dec 79	50			
Single IC Organ	May 79	61			
Single IC Power Supply	Dec 79	38			
Single Op-Amp Oscillator	Jan 79	33			
Sound Operated Switch	Mar 80	33			
Sound-Triggered Flash	Jul 79	37			
Speech Processor	Jul 80	26			
Supply Splitter	Apr 80	48			
Suppressor Tester	Feb 81	30			
Sustain Unit	Sep 79	63			
Table Lamp	Jul 80	42			
Thermostat	Jan 80	52			

SERIALS

Famous Names

Edwin Armstrong	Nov 81	23
Sir Edward Appleton	Sep 82	37
Charles Babbage	May 82	53
J. M. E. Baudot	Dec 82	33
Alexander Graham Bell	Aug 83	52
Karl Ferdinand Braun	Oct 81	25
A. A. Campbell-Swinton	Dec 81	26
Allen B. Du Mont	Mar 82	47
Lee De Forest	Feb 82	45
Sebastian De Ferranti	Jun 82	29
Michael Faraday	Apr 81	35
Oliver Heaviside	Sep 81	26
Joseph Henry	Aug 81	26
Heinrich Rudolph Hertz	Jun 81	56
Herman Hollerith	Mar 83	65
Guglielmo Marconi	Apr 82	30
James Clark Maxwell	May 81	63

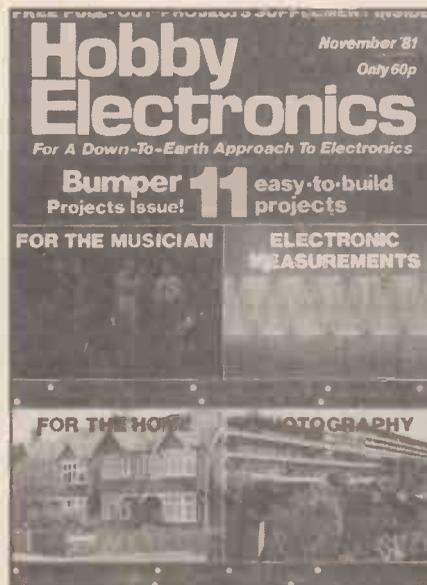

Complete Cumulative Index

	Issue	Page
Julius Plucker	Aug 82	39
Vlademar Poulsen	Oct 82	21
Sir John Turton Randall	Jun 83	26
David Sarnoff	Jul 83	55
William Bradford Shockley	Nov 82	51
Charles Proteus Steinmetz	May 83	24
William Stockley	Nov 82	51
Charles Wheatstone	Jan 83	20
Vladimir Zworykin	Jan 82	53

Into Digital Electronics

Part 1	Sep 80	30
Part 2	Oct 80	17
Part 3	Nov 80	29
Part 4	Dec 80	35
Part 5	Jan 81	45
Part 6	Feb 81	51
Part 7	Mar 81	43

Into Electronic Components

Part 1	Aug 81	47
Part 2	Sep 81	46
Part 3	Oct 81	46
Part 4	Nov 81	48
Part 5	Dec 81	52
Part 6	Jan 82	42
Part 7	Feb 82	46
Part 8	Mar 82	59
Part 9	Apr 82	61
Part 10	May 82	61
Part 11	Jun 82	43
Part 12	Jul 82	48

Into Electronics

Part 1	Nov 78	11
Part 2	Dec 78	27
Part 3	Jan 79	46
Part 4	Feb 79	49
Part 5	Mar 79	51
Part 6	Apr 79	55
Part 7	May 79	49
Part 8	Jun 79	55

Into Electronics Construction

	Issue	Page
Part 1	Feb 80	65
Part 2	Mar 80	67
Part 3	Apr 80	67
Part 4	May 80	67
Part 5	Jun 80	67
Part 6	Jul 80	67

Into Linear ICs

Part 1	Jul 79	49
Part 2	Aug 79	68
Part 3	Sep 79	66
Part 4	Oct 79	66
Part 5	Nov 79	65
Part 6	Dec 79	67
Part 7	Jan 80	65


Radio Rules

Waves And Signals	Apr 82	55
Oscillator Circuits	May 82	57
Wave Theory	Jun 82	19
Capacitance And Inductance In AC And DC Circuits	Jul 82	29
Capacitance, Resistance And Inductance	Aug 82	43
Classes of Radio Power	Sep 82	20
Radio Stages	Oct 82	68
Frequency Modulation	Nov 82	63
Single Sideband	Dec 82	43
Introducing AM Receivers	Jan 83	47
Propagation And Aerials	Mar 83	55
Interference And RF Measurements	Apr 83	66
The RAE	May 83	41

OCCASIONAL SERIES

Synthesizer Secrets

	Oct 81	53
	Nov 81	28
	Dec 81	29

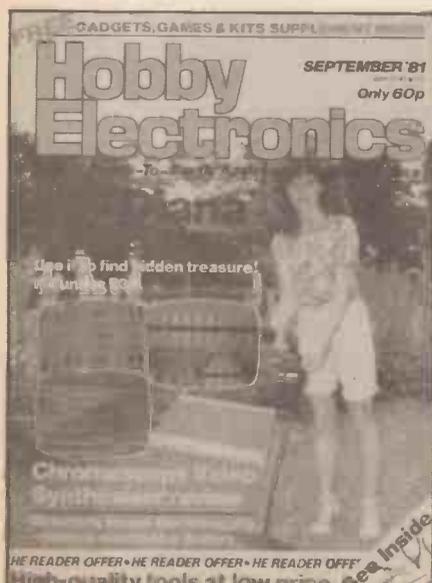

**What's In A Name/
Tech Terms**

	Issue	Page
Loudspeakers	Jan 81	25
Microphones	Feb 81	29
Pressure Sensors	Mar 81	53
The Hall Effect	Oct 81	27

Gadgets, Games And Kits

May 81	35
Jun 81	31
Jul 81	31
Aug 81	31
Sep 81	31
Oct 81	31
Dec 81	35

'O' Level Q & A

Jan 81	32
Feb 81	32
Mar 81	48
Apr 81	48
May 81	53
Jun 81	47
Jul 81	45

Kits

Bio-Activity Translator	Jun 79	51
Car Anti-Theft Alarm	Nov 79	47
Car Clock/Timer	Aug 79	22
CM100 Circuit Maker	Oct 82	63
Digital Panel Meter	Oct 79	27
DIY HiFi/Speaker Review	May 83	52
DM 2350 Meter Review	Sep 82	47
Dora Chime	Nov 78	51
Electronic Ignition	Jul 79	54
Electroni-Kit Construction Kit	Apr 79	24
Memotech 64K RAM Pack		
Review	Jun 82	65
Programagame	Dec 78	67
Power Supply	Feb 79	34
R/C Servo	Feb 80	45
Touch Dimmer	Jul 80	46
Tuner/Amplifier	Mar 80	29
VU Meter	Jul 80	47
Voyager Car Computer	Mar 83	62
Wein Bridge Oscillator	Jan 79	67

Pop Amps

	Issue	Page
High Impedance AC Millivoltmeter	Jul 83	60
Linear Ohmmeter	Mar 83	30
Long Range Ohmmeter	Mar 83	46
One-Op Amp Microammeter	Dec 82	52
Peak Voltage Detector	Feb 83	52
Single IC Millivoltmeter	Jan 83	30
TTL Logic Tester	Jun 83	36
Very High Impedance Voltmeter	Feb 83	31
Voltage Follow And Hold	Dec 82	62

Components For Computing

I/O Ports	Dec 82	46
Randomly Accessing Memory	Feb 83	69
ROMs And EPROMs	Mar 82	16
Interrupts	Apr 82	50
Looking At Displays	Jun 83	38

Careers In Electronics '83


Basic Qualifications	May 82	12
Technical Writing	Jun 83	52
British Telecom	Jul 83	48
Radio and TV Transmission	Aug 83	47
In The TV and Radio Studio	Sep 83	40
Customer Service Engineering	Oct 83	16
Working With Microcomputers	Nov 83	48

All About Electronics

Part 1: Basics	Jul 83	28
Electromagnetics And Ohm's Law	Aug 83	20
Resistance And Capacitance	Sep 83	48
Semiconductors	Oct 83	48
Digital Circuits	Nov 83	28
Transistor Circuits	Dec 83	36

The Electronic Revolution

Beginnings	May 82	39
Wireless At War	Jan 83	52
The Birth Of Broadcasting	Feb 83	22
Pictures From Afar	Mar 83	40
Power In The House	Jun 83	56
The Electronic Age	May 83	57

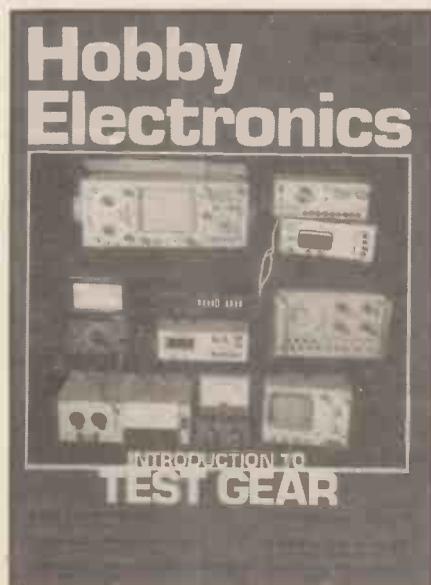

MASTER ELECTRONICS NOW! The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY
THIS IS THE AGE — OF ELECTRONICS!
the world's fastest growth industry...

There is a world wide demand for designers/engineers and for men to service and maintain all the electronic equipment on the market today — industrial — commercial and domestic. No unemployment in this walk of life!

Also — the most exciting of all hobbies — especially if you know the basic essentials of the subject. . . .

A few hours a week for less than a year — and the knowledge will be yours. . . .

We have had over 40 years of experience in training men and women successfully in this subject.

Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.



British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE!

COLOUR BROCHURE



POST NOW TO

Please send your brochure without any obligation to

NAME _____

ADDRESS _____

HE/3/841

BLOCK CAPS PLEASE

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS please state below

OR TELEPHONE US
0734 51515 OR
TELEX 22758
(24 HR SERVICE)



British National Radio & Electronics School Reading, Berks. RG1 1BR

CAREERS IN ELECTRONICS



We conclude our three-part look at electronics in the Armed Forces with the Royal Airforce, and a round up of addresses.

Helen Armstrong

Unsurprisingly, the **ROYAL AIR FORCE** also divides its engineering forces into three sections, in this case known as Aircraft Engineering, including and care and maintenance of the aircraft and heavy weaponry, as well as the electrical systems; Electronics Engineering, which includes the care of all communications equipment, flight simulators, and the fine electronics of flight and navigation systems, and General Engineering, which covers carpentry, workshop crafts, ground equipment servicing and ground and vehicle electrical systems.

For engineering in the RAF, the roles are generally divided into Mechanics (who require no formal qualifications to be accepted for training) and Technicians (most of whom require two or four GCE O levels or the equivalent). Men are accepted at 16½ and women at 17, and most trades are open to both — although, in accordance with the tradition that women do not go into combat, flying jobs are closed to them. As usual, maths and physics are the preferred GCE subjects, and in some cases are essential. Entrants with four

'O' levels, and between 16 and 18½ can apply for Apprenticeship training. The upper age limit for training is 39, a bit higher than for the other two Services. This may reflect the fact that there is less emphasis on personal combat training in the RAF than in the Army or even the Navy: it is highly machine-orientated, the purpose being to get fighting, bombing and reconnaissance aircraft into the air, out to their mission, and safely back again. Even so there is an RAF Regiment whose job is to protect the airfields; all personnel have to undergo military training, and meet basic medical requirements, and some jobs — such as flying — are among the most physically and mentally demanding in any Service.

Technician training lasts from nine to eighteen months, depending on the previous level experience of the trainee (some come straight from school, others from industry) and those entering as Mechanics may be selected according to merit for training as Technicians later. People with, or expecting to get, four good 'O' level passes including Maths and Physics can apply for

Apprenticeship training. This falls into Aircraft Engineering (which is mostly electrics and mechanics), Electronic Engineering (Flight Systems), or Electronic Engineering Technician (Air Communications/Air Radar), which titles are self-explanatory.

Electronic Engineering courses cover three years at RAF Cosford, near Wolverhampton. The first year of study is common to all Electronics students, and includes basic electronics, introductions to radio and computers, plus introductory RAF studies such as physical training, weaponry and RAF history. Work on BTEC studies begin.

In the second year, advanced electronics theory and practice is covered. Students begin to specialise, and learn about the specific equipment they will be working with; they also visit an RAF station to observe engineering in action, and sit BTEC examinations. In the third year, most time is spent in workshop practice and aircraft servicing within the student's specialisation, with more time at an RAF station. There is also a course in Junior Management, which is the first formal step towards

developing the ability to lead and supervise men, which could later lead to officer training to those with the ability.

At the centre of the course the level of BTEC Higher Diploma is achieved, and there are further opportunities to take higher qualifications and more demanding specialisations.

Unlike the Navy and the Army, Engineering Officers in the RAF do not have to be graduates. Acceptable qualifications however are still demanding, and are candidates are classified as "Qualified" or "Intermediately Qualified": Qualified candidates must have a degree in an appropriate subject (engineering, maths or science, to summarise), or membership, or the equivalent, of one of the engineering Institutions or the Royal Aeronautical Society (to the level of Chartered Engineer in the latter case) or a pass in Part 2 of the Council of Engineering Institutions examinations. Intermediately qualified candidates must have an HNC or BTEC Higher Certificate in Engineering or science, or a City and Guilds Full Technological Certificate in one of the four specified engineering subjects — plus 'O' level English.

This is a bald summary; there is a complex system of exemptions and equivalents to be taken into consideration. The RAF like all the Services aim to choose men and women suitable for the service and in the process see that they are qualified, or can be qualified, to do the technical job which will be demanded of them; they are not looking for a sheaf of paper qualifications.

In the RAF equal opportunities exist for men and women in all engineering jobs, except apprenticeships. You'll get more details from their recruiting literature.

Sponsoring Schemes

While they do not have their own degree college, the RAF has a number of schemes for sponsoring. There is a Cadetship scheme for entrants about to go into a University or Polytechnic, and there is also sponsorship for the Air Transport Engineering Course at the City University in London.

The RAF also wants officers who have had experience in industry and, as for the ranks, the upper age limit for entrance is thirty nine.

All officers entering the service have an initial training of eight weeks at the Officer Training Unit at the RAF College, Cranwell. The subjects covered will be familiar to you by now: leadership, service history and knowledge, administration, tactics and defence, physical fitness and survival.

Subsequently, Engineer Officers train at Cranwell, although there are many other RAF training establishments for other branches. Non-graduate engineers receive Lead-in Training, comprising mathematics and electrical science, drawing, workshop practice and other academic subjects. This is followed, for everyone, by eight weeks



A test crew at Marconi Avionics put the tactical systems of a new Nimrod aircraft, due to come into service in the not too distant future, through its paces. This is the kind of equipment which RAF engineers must be able to maintain.

Service Engineering Orientation Course, which covers the technology and management used by the RAF.

After this, officers specialise in either basic aerosystems or basic communications-electronics. Further education in these fields comes in the form of pre-employment training before each tour of employment for C-Es, and familiarisation training on the aircraft they will be working with for Aerosystems (this is similar to the standard pattern of pilot and aircraft engineer training in civil life, where the pilot or engineer must be specifically trained and qualified for one (or more) type of aircraft before he is allowed to work with it).

The initial Professional Training course lasts about twelve months, after which the officer goes into employment, but both technical and management training continues as the officers progress.


As the majority of RAF engineering officers neither fly operationally nor engage in front-line combat, most jobs are open to women as well as men provided they have the same qualifications. But whereas it's fair to say, "Why join the Navy if not to go to sea?", it's not fair to say "Why join the RAF if not to fly?". Comparatively few RAF personnel actually fly, or fly in, the aircraft — the majority of them either service the aircraft, or administrate the

service. It is possible to learn flying, though, as indeed it is in the Navy or the Army.

To join the RAF as an Officer you must be interviewed and selected by either the Air Board (aircrew), the Ground Board (most other personnel) or the Cadetship Board, which selects candidates for University Cadetships. Selection procedures take place at RAF Biggin Hill (home of the Biggin Hill Air Show) and last between three and four days. A permanent commission is initially for sixteen years either from the age of 21 or up to the age of 38 there are also Short Service Commissions of varying length. Promotion is by merit.

Pros And Cons

This article so far has laid out a rough map of the opportunities and commitments which exist in the Armed Forces for people interested in pursuing a career in electronics at any level. I hope I have been able to distinguish between the three services enough. Although they are all run along similar lines and have similar aims I am left with the impression that each has its particular advantages and disadvantages, from small things such as the exact age limits for entry to large

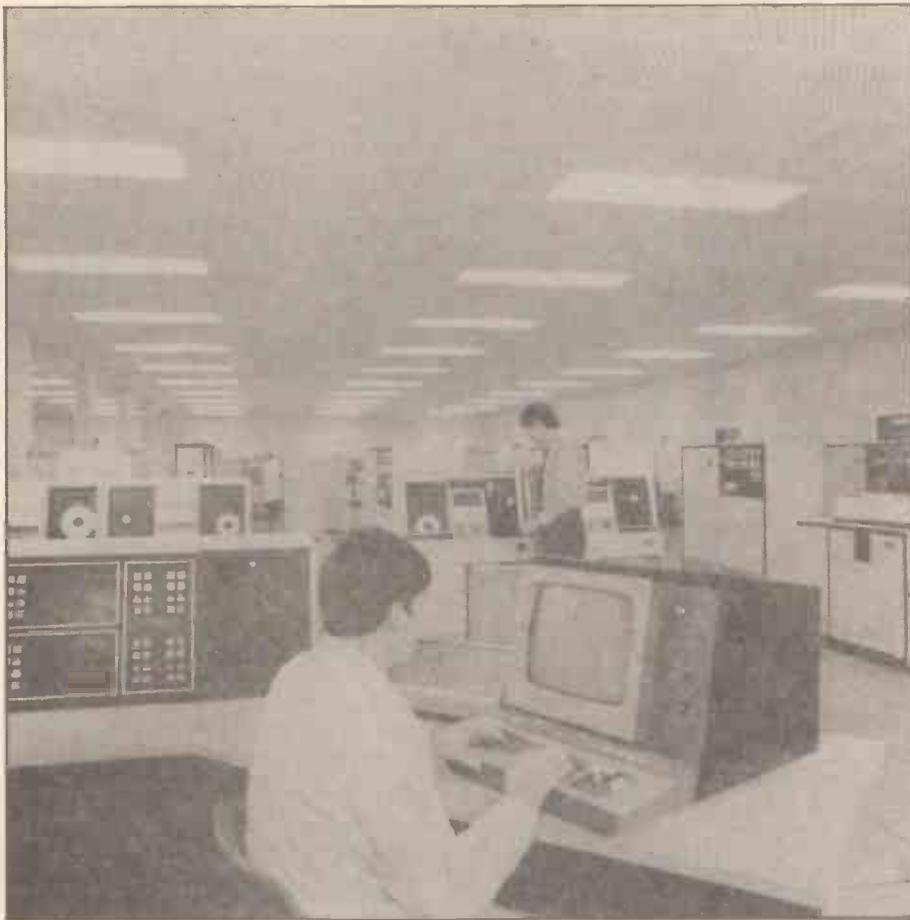

A different aspect of defence work: two operators on the main computer at RAF Brize Norton. Stressing the variety of defence work, operating the administration computer is as far from repairing a fighter aircraft as can be imagined, but it is still a vital part of the defence chain.

matters such as where you would be expected to serve and the opportunity to travel or otherwise.

All the services have the benefits and penalties of a somewhat closed community, as servicemen tend to live on or around bases with other people of the same service. It can be (but does not have to be) rough on family life, as it can involve a good deal of moving around, so that there is not the opportunity to settle into a local community (even a service one) for long periods. Some people find this interesting, others find it disorientating. On the other hand it gives a comparatively well-assured career (although servicemen, especially older ones, are not immune to redundancy; but this does not happen very often) with a good pension for people leaving after a full term career and training and experience (particularly in a technical field such as engineering) which are in demand in civilian employment.

To be eligible for service employment, you must be a British citizen and the child of British citizen parents (which does not mean that you or they have to be born in the UK but does mean that you must have been born within the Commonwealth. Again, as with most Forces regulations, exceptions can be made under the right circumstances. But applicants must be of British nationality on application.

Asking Questions

Career opportunities aside, the Armed Forces exist to defend the UK and territories associated with it against attack; years of peace can suddenly be punctuated by hostilities involving all three Services, as happened with the Falklands war. Engineers even when they are not actually doing the shooting, are occasionally likely to be shot at.

However, the Services are as keen to avoid employing people who are not happy with the conditions of service as those people are to avoid joining them. So it is worth asking questions, if possible visiting services establishments and meeting service people. Joining does not have to be a long-term commitment, so that it is possible to spend a few years in one of the services (the minimum is about three years in most cases) and then decide whether to stay or leave, by which time you will know what is involved and can make the choice with useful experience behind you, and no regrets either way.

Your first step in your investigation is to visit your nearest Services careers office, or to write to one of the addresses listed for brochures, which will tell you roughly what we have told you, and a whole lot more. Then go back to your careers office and start asking questions.

Now, if the RAF will just recognise the

crying need for lady fighter pilots before I get to thirty-nine . . .

To find out more about engineering in the Army, write to:

The Engineer-in-Chief's Recruiting Liaison Office
Royal Engineers
Brompton Barracks
Chatham
Kent ME4 4UG

Lt-Col J. R. Ellis
Officer Recruiting Liaison Staff
School of Signals
Blandford Camp
Dorset DT11 8RH

The Recruiting Liaison Staff
Headquarters
REMEM Training Centre
Arbourfield
Reading
Berks RG2 9NN

These addresses all apply to officer training. For other ranks, locate your nearest Army Careers Office by consulting the Yellow Pages, local telephone directory, or local library. Prospective Naval Officers should write to:

The Officer Entry Section
Naval Careers Service
Old Admiralty Building
Spring Gardens
London SW1A 2BE

For other ranks look for the Royal Navy and Royal Marines Careers Information offices in the phone book (listed under *Naval Establishments*). There are about sixty of these countrywide; you can phone them for initial information and literature.

For the RAF, you will have to refer to the nearest RAF careers office initially.

There are two other options to be considered: one is the Youth Training Scheme, for which the Services are now taking some entrants for twelve month engagements, which is a good chance for likely candidates between sixteen (seventeen for girls) and eighteen. The other is the Forces Reserves. Each Service has a Reserve force made up of ex-personnel and civilians who put a certain amount of their time into Service training every year in return for training and payment. Members acquire rank in the same way as regulars: it's a way of becoming involved in the Service without the full career commitment. Places are often limited. Reservists are the first to be called upon in time of war when the services need more personnel.

That concludes our summary: the rest is up to you. And, yes, the rumours that some trainee officers have been asked to obtain a tassel from a striptease dancer as part of their initiative test have been confirmed by our most reputable (ex-Armed Services) sources.

This feature ends Careers In Electronics '83 as a regular series, but we shall be featuring other electronics careers every so often. Suggestions are welcome from anyone with a special interest that we haven't covered yet.



Sinclair's QL

A giant step forward . . . or a leap in the dark?

CLIVE SINCLAIR has just made a grand slam bid for another lion's share of the computer market. Although not without drawbacks, the new Sinclair QL ("Quantum Leap") is a very powerful machine which Sinclair confidently expects to equal the sales performances of the Spectrum. The QL will retail for just £399, including a set of four software packages from Psion. Mail-order deliveries are due at the end of February 1984, with retail sales planned in the year's third quarter. Ordering a QL should not be a problem, as a wide ranging advertising campaign has already begun.

As pointed out at the launch, there is no other computer offering anything like the power of the QL at anything near the price; the inclusion of four useful and well designed programs is a nice touch, and a sensible precaution against one of the most serious threats to a new computer — lack of software support. This is a marketing lesson which Sinclair has learnt thoroughly but which others absorb only at great cost.

But then marketing is largely what Sinclair Research Ltd are all about. The method is easily grasped, if not so readily followed by companies with less nerve. Somehow Sinclair manage to make and sell tomorrow's computer today, at yesterday's price. It is a leap-frogging process that reverses the normal procedure by which marketing-men take surveys to determine what the public wants, and then produce what they think the public needs. It is a technique (which has worked so far) whereby a new and innovative produce creates its own market: after all, was there really a demand for a small inexpensive home computer until Sinclair released the ZX80? The QL may well follow the same pattern.

The QL is very carefully positioned to bridge the gap (if there is one) between home and business computer users: on the one hand it is cheap enough to compete with the BBC Model B, Commodore 64 and the like, but also powerful enough (at least potentially) to compete with Apple, CBM and even the IBM PC. Yet Sinclair candidly admit that although they see the QL primarily as a business machine, they have no idea what uses the QL will ultimately find in the hands of the target 3.5 million users world wide. In other words having created a supply, they earnestly hope that demand will follow!

Certainly the QL has features to attract interest from all sections of the computer-buying public, and promises to be an interesting machine to explore.

Inside Story

The specification of the QL is worth considering in detail. The main processor is Motorola's MC68008, the baby of the 68000 family but nevertheless a most powerful CPU. It has a 32-bit internal structure and is fully compatible with 68000 code. The 20-bit wide address bus can directly access 1M byte of memory (or memory-mapped I/O), but the most attractive feature to Sinclair must have been its 8-bit data bus, which means the 68008 can be operated with standard byte-wide memories and support chips.

As well as the 68008 the QL includes an Intel 8049 8-bit CPU with 2K ROM and 128 bytes of RAM on the chip. This handles the keyboard, sound generation and the RS232C receive function. In addition, two custom chips are employed: one is dedicated to memory management and the display, while the other looks after the two microdrives, the local

area network and RS232C transmission. A real-time clock is also included, maintained by a back-up battery — a most useful facility which, in the age of digital watches, is inexplicably missing from most computers.

Internal RAM stacks up at a fairly massive 128K, of which 9K is free to the user; an 0.5Mbyte expansion board is promised, which will take total RAM to 640K! The 32K ROM contains the new QDOS operating system, which promises to be very interesting, and an enhanced version of Sinclair BASIC, dubbed SuperBASIC.

QDOS is described as "... a single user multi-tasking, time-sliced system ..." and was developed to take advantage of the power of the 68008 CPU. Multi-tasking (the ability to handle several jobs simultaneously) allows the QL to run several programs at once, each with an independent screen window — a feature normally available only on far more expensive computers.

SuperBASIC offers several improvements over the old Sinclair BASIC. For a start it incorporates the structured PROCEDURE format made popular by BBC BASIC; it is also said to be user-extendable and to run at a constant speed, so that program execution time does not depend on the length of the routine. Other features include easy interfacing to machine code, and access to the QDS operating system.

In And Out

The QL's keyboard has a full sized QWERTY layout with sixty five keys including a space bar, five function keys and four separate cursor controls. It is, apparently and at last, a proper keyboard!

Two microdrive units are built in, and a further six can be daisy-chained onto the expansion socket. However



these may be QL Microdrives; those made for Spectrum cannot be used, though the cassettes themselves are compatible if formatted for the QL.

A port at one end of the computer accepts ROM cartridges up to 32K in capacity, but once more ZX ROM cartridges are not suitable.

The QL offers alternative display outputs. Best quality is obtained from the Monitor port, which will drive either an RGB or a monochrome monitor. Two graphics resolution modes are available: 512 x 256 pixels with a choice of four colours (red, green, black, white, plus a 'stipple' feature) or 256 x 256 with a palette of eight colours. Normal character format on a monitor display is 25 rows x 85 columns.

The UHF TV output display modes are similar, but the use of the stipple feature is not recommended and the character format is typically forty six characters, depending on software.

Other features built into the QL include a local area network (QLAN) providing a link-up for up to sixty-four QLs or Spectrums, two RC232C ports and two joystick ports.

Onwards And Outwards

In addition to the 0.5Mbyte memory expansion, an interesting list of peripherals and extensions is planned for the QL. The most important of these are the 68000 assembler, the analogue/digital interface, Winchester (hard disc) interface, modem and the parallel printer interface.

Finally there is the manual. A preview copy was released to interested journalists at the press launch, and while it would be unfair to criticise it at this stage it is plainly incomplete, with large sections either missing or very skimpy; one hopes that the final style is less opaque than that of the draft version. Bad documentation is unforgivable and a sin which infuriates reviewers and often leads to unfavourable comment on the computer itself.

Software

The 'software suite' supplied with the QL was written and licensed from Psion and consists of four integrated programs: QL Abacus, a spreadsheet; Archive, a data management/filing system; Easel, a graphics design program; and Quill, a wordprocessor.

All four are supplied on Microdrive

cassettes and make extensive use of the QDOS operating system's capability for separate screen windows. At the top of the screen is a Control window, which at all times displays a list of current options available, to the user; few lines of the screen to show information about the work in progress; and the Display window, a large area across the middle of the screen, shows the work.

The screen format is identical in all four programs, as is the command structure, so the learning curve for the complete suite is likely to be quite short. In addition data is transportable from one program to another so that, for example, business graphics can be generated from data imported from the spreadsheet.

Many other tasty features are listed in the documentation, including many found only on up-market business computers, so the indications are that the QL software suit will be a joy and a delight to use — Murphy's Law permitting.


Paper Tigers

Lest readers begin to think that the QL is all things bright and beautiful, a flawless example of computing engineering unmatched by any other, it has to be said that the QL does have a few shortcomings. Indeed the sceptics have already compiled a list of them.

The most serious criticism is the complete lack of a facility found on every computer in the QL's price range... a cassette interface (its worth mentioning that a floppy disc interface is missing, too).

The implication of this is that cheap software is unlikely to be available for some time, because blank Microdrive cassettes currently cost around £5.00 at retail prices, and the medium is not suitable for high speed duplication either. Taking a slightly longer view, though, it will probably not be too long before add-on cassette and/or floppy interfaces are available. Another possibility is that software houses will go for ROM-based programs, though this development must wait on the release of the 68000 assembler.

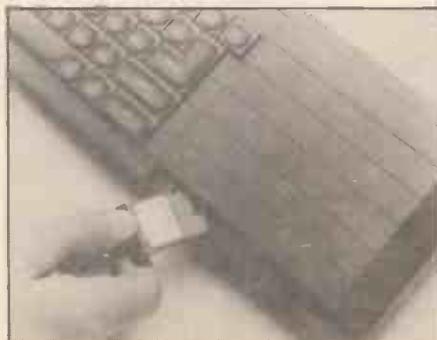The Microdrive system itself is not yet proven to the satisfaction of many buyers. However the QL Microdrives



may prove more efficient than those made for the Spectrum: according to the provisional manual, QDS routinely stores as many files as possible in spare memory, reducing wear and tear on the tape and greatly increasing access time. And the 0.5M byte RAM pack provides a very substantial amount of spare memory! Another serious, albeit temporary problem, is the lack of a parallel printer interface.

The remaining criticism of the QL (so far) have about them a faint aroma of sour grapes. Complaints have been made about the use of the 68008: its data bus is only 8-bits wide rather than 16, so it will be only a quarter as fast as the 68000 because it has to perform four times as many fetches; and with a clock speed of only 7.5MHz the QL will be slower than some of the faster 8-bit computers. Well I wouldn't bet on it.

In fact both the 68000 and the 68008 fetch instruction in pairs of bytes (words), so there is not all that much difference between them, and Motorola data shows that on a 'quick sort' bench-mark test the 68008 clocks in only 10 milliseconds slower (30%) than the 68000 CPU running with a memory management unit. And at first appearances, the 68008 instruction set looks extremely powerful and compact (a point made several times by Motorola in comparing their 68000 family CPUs with other 16-bit processors), so machine code programs should run very quickly on the QL.

The remaining criticism to date concerns the choice — or rather the lack of choice — of colours in high resolution graphics mode. This criticism is relevant only to dedicated games-players, and even so its ultimate strength will depend on the effectiveness of the stipple feature in producing shades and tones.

Of course there will undoubtedly be other valid criticisms of the QL (it would be too much to expect any computer to be perfect) and these will show themselves when review models become available. Then experience will tell whether or not the QL lives up to its specification. The QL will not win kudos for the missing cassette interface, but this is not an insoluble problem: where Sinclair leads, others tend to follow, and if fast performance is any guide the QL and its add-ons will be every bit as successful as earlier Sinclair computers.

FORWARD BIAS

Questions, answers and errata from readers and writers.

Fog Horn (HE June '80)

The PCB (Figure 3) was the wrong one: the correct one is shown here, right size.

The mercury switch mentioned in Buylines was a mistake (this was for the Eggtimer).

Guitar Phaser (HE September '80)

In Figure 1, there should not be a link where R9 to 'orange' crossed C10 to +9V (C10 is a decoupling capacitor across the supply). The resistor from the gate of Q1 should be R14; the capacitor from the link of R6 and R8 to OV is C9.

In Figure 3, Q1 and Q2 are shown with the drain and source reversed. The pin-out diagram beneath Figure 1 is correct.

In the Parts List, RV2 should be 470k antilog as in Figure 1.

Audio PSU (HE February '84)

Last month's Audio Power Supply module had a couple of misprints in it. Under the heading *A Choice Of Power* the four diodes are described as "N4000"; this should read 1N4000. Further down the same section, a "50uF" and a "100uF" capacitor are mentioned: these should be 500 and 1000uFs (as accurately described in the Parts List).

Further down the article, on page 23, an equation is given for the calculation of the output voltage resistor values. This should read: 10V8 x 120R/1V2 gives 1080R as the value for R2.

Heading In The Wrong Direction — Veroboard Warning (HE January '83)

A little mix-up at the type department resulted in all the Veroboards being incorrectly orientated in our Veroboard layouts in last months HE. The tracks should, of course, run across the page, not up and down. Building the projects as shown would result in everything shorting out to everything else, a fact which should normally become abundantly clear before completion of the project.

Short Circuit Authors

Please will contributors G. Foote and B. Adams get in touch with us.

H.E. PROJECT KITS

I.C.s
TRANSISTORS
CAPACITORS

TOOLS
RESISTORS
HARDWARE

CASES
KITS
PCBs

MAGENTA

Full Kits Inc. PCBs, hardware, electronics, cases (unless stated). Less 83.
If you do have the issue of H.E. which includes the project — you will need to order the instruction reprint as an extra — 50p each. Reprints available separately 50p each + p&p 50p.

INFRA-RED CAMERA CONTROL Feb 84	£17.49
C.B. FIELD STRENGTH METER Feb 84	£14.15
BASSMAN Dec 83 (with PCB)	£10.38
CONTINUITY TESTER Dec 83	£5.55
MOISTURE GAUGE Dec 83	£10.98
ULTRASONIC INTRUDER ALARM no case Oct 83	£14.85
WHISTLE SWITCH Aug 83 less mic	£19.98
STEREO SPREADER July 83	£6.36
SINCLAIR SOUND BOARD Jun 83 less case	£18.98
BAT LIGHT (car battery Indicator Jun 83 less case)	£5.48
TTL LOGIC PROBE June 83	£8.78
AUTO TESTER May 83	£7.35
STALL THIEF May 83 (inc relay)	£12.36
STEREO VOICE OVER UNIT April 83	£19.27
OPTIONAL MIC PRE-AMP April 83 (no case)	£4.69
PHASE FOUR Dec 82	£20.58
STEREO NOISE GATE Dec 82	£16.88
TAPE SLIDESHYRONIZER Dec 82	£23.90
ODOMETER Nov 82	£16.48
ZX INTERFACE BOARD Sept 82 inc edge con	£31.246
AUTO WAH June 82 20.88 case £13.51	
AUTO GREENHOUSE SPRINKLER June 82 less nump and power supply	£15.82
ECHO REVERB UNIT May 82 Less case Economy case WB3	£3.75 extra
DIGITAL THERMOMETER May 82 including case + bezel	£18.59
AUDIO SIGNAL GENERATOR May 82	£22.98
CABLE TRACKER May 82	£10.98
DIGITAL CAPACITANCE METER Apr 82	£23.10
SIGNAL TRACER Apr 82	£4.25
BIKE ALARM Apr 82	£13.99
DIGITAL DICE Mar 82	£7.99
NOISELESS FUZZBOX Feb 82	£11.98
MASTHEAD AMPLIFIER Feb 82	£16.10
DRUM SYNTHESIZER Dec 81 Full kit	£25.37
GUITAR HEADPHONE AMPLIFIER Dec 81	£4.12
IN CAR CASSETTE POWER SUPPLY Dec 81	£5.25
SCRATCH FILTER Nov 81 Mono	£6.48
Stereo	£9.80
LED VU METER Nov 81 less case	£5.35
SIMPLY STYLUS ORGAN Nov 81 less case	£5.48
METRONOME Nov 81	£13.98


TELEPHONE BELL REPEATER Oct 81	£15.15
14p meter	
COMBINATION LOCK Oct 81 less case	£19.98
'DIANA' METAL LOCATOR Sept 81	£37.50
VARIABLE BENCH POWER SUPPLY Aug 81	£29.48
ULTRASOUND BURGLAR ALARM July 81	£21.98
ELECTRONIC DOORBELL July 81	£6.48
ELECTRONIC METRONOME July 81	£5.48
CONTINUITY CHECKER June 81	£6.60
ENVELOPE GENERATOR June 81	£19.48
PUBLIC ADDRESS AMPLIFIER March 81	£21.48
Extras — horn speakers £8.35 each PA MIC £4.95	
FUZZ BOX March 81	£11.98
WINDSCREEN WIPER CONTROL March 81	£8.98
STEAM LOC WHISTLE March 81	£14.38
PHOTOGRAPHIC TIMER March 81	£3.95
HEAT BEAT MONITOR Feb 81	£27.50
TWO-TONE TRAIN HORN Feb 81 £6.16 less case	
MEDIUM WAVE RADIO Feb 81	£8.98
CHUFFER Jan 81, less case	£3.25
BATTERY CHARGE MONITOR Dec 82	£8.34
MEMORY BANK—MINI SYNTHESISER Nov & Dec 80	£36.48
TRANSISTOR TESTER Nov 80	£7.25 inc test leads
GUITAR PRE-AMP Nov 80	£7.25
case extra	£2.29
INTRUDER ALARM Oct 80	£23.10
TOUCH SWITCH Sept 80	£2.99 less case & contacts
GUITAR PHAER Sept 80	£17.88
SOUND OPERATED FLASH TRIGGER July 80 no skt	£5.83
FOG HORN June 80	£7.30
SPEED CONTROLLER FOR R/C April 80	£19.20 (less case)
DIGITAL FREQUENCY METER April 80	£43.98
GUITAR TUNER Nov 79	£14.10
CAR ALARM Feb 79	£14.20



HELPING HANDS JIG £8.85
Heavy base. Six ball and socket joints allow infinite variation of clips through 360°. Has 2 1/2" diameter (2.5 magnifier attached), used and recommend by our staff.

SOLDERING/TOOLS

ANTEX X5 SOLDERING IRON 25W	£8.29
SOLDERING IRON STAND	£2.18
SPARE BITS, Small, standard, large, each, For X5+X25	£1.04
SOLDER, Handy size	£1.38
SOLDER CARTON	£2.50
DESOLDER BRAID	69p
HEAT SINK TWEEZERS	35p
DESOLDER PUMP	£6.48
HOW TO SOLDER LEAFLET	13p
LOW COST CUTTERS	£1.99
LOW COST LONG NOSE PLIERS	£1.88
WIRE STRIPPERS & CUTTERS	£2.88
PRECISION PETITE 12V PCB DRIVER	£12.80
DRILL STAND	£8.78
VERO SPOT FACE CUTTER	£1.76
PIN INSERTION TOOL	£2.52
VEROPINS (pk of 100 0.1")	65p
MULTIMETER TYPE 1 (1,000 opv)	£5.85
CROCODILE CLIP TEST LEAD SET, 10 leads with 20 clips	£1.15
RESISTOR COLOUR CODE CALCULATOR 22p	
CONNECTING WIRE PACK TYPE E, 11 colours	40p
ILLUMINATED MAGNIFIERS Small 2" dia. (5 x mag)	£1.32
Large 3" dia. (4 x mag)	£2.52
CORE TRIM TOOL	39p
PRESET TRIM TOOL	60p
FREEZER AEROSOL CONTACT CLEANER AEROSOL	£1.59
ELECOLIT CONDUCTIVE PAINT	£4.99
PVC TAPE (RGB) 3 reels	39p
SCREWDRIVER SET	£1.98
POCKET TOOL SET	£3.98
DENTISTS INSPECTION MIRROR	£2.85
JEWELLERS EYEGLASS	£1.50
PLASTIC TWEEZERS pair of probes with leads (cc)	£6.99
O MAX PUNCHES 3/8" £2.98; 1/2" £3.06; 5/8" £3.17; 3/4" £3.24.	77p

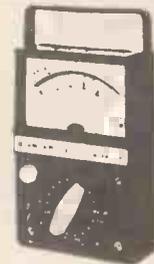

MULTIMETER TYPE 2. (YN360TR) 20K o.p.v. with transistor tester. £14.99
AC+DC volts DC current. 4 very useful resistance ranges. We've used it and we like it.

FUN WITH ELECTRONICS
Enjoyable introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners — children and adults. Only basic tools needed. 64 full colour pages cover all aspects — soldering — fault finding — components (identification and how they work).
Also full details of how to build 6 projects — burglar alarm, radio, games, etc. Requires soldering — 4 pages clearly show you how.
COMPONENTS SUPPLIED ALLOW ALL PROJECTS TO BE BUILT AND KEPT.
Supplied less batteries & cases.
FUN WITH ELECTRONICS COMPONENT PACK £16.48
BOOK EXTRA £1.25.
Book available separately.

Speakers Min 8 ohm 87p; 64 ohm 89p, 80 ohm 90p	£6.48
Crystal earpiece	57p
Magnetic earpiece	19p
Stethoscope attachment	69p
Mono headphones	£3.36
Stereo headphones	£5.49
Telephone pickup coil	69p
Min buzzer 6V 75p. 12V 72p.	
Euro breadboard	£6.20
8 Dec breadboard	£3.98
Bimboard breadboard	£6.39
Verobloc breadboard	£5.88

PCB etching kit	£6.48
ZK81 edge connector	£2.25
Ferrite rod 5 inch	59p
PP3 clips 10p. PP9 clips 11p.	
2 Station Intercomm	£10.53
IC Sockets 8 pin 16p; 14 pin 17p; 16 pin 18p.	
Traditional Style Bell	£1.95
Public Address Mic 50k	£4.95
Mic Insert Crystal	45p
Cassette Mic	£1.29
Pillow Speaker	£1.40
Horn speaker 5 1/2" 8 ohm	£6.98

MORE KITS AND COMPONENTS IN OUR LISTS
FREE PRICE LIST
Price list included with orders or send sae (9 x 4)
CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery.
Send 80p in stamps or add 80p to order.
FREE to Schools/Colleges requested on official letterhead.

MAGENTA ELECTRONICS LTD
HE9, 135 Hunter St., Burton-on-Trent Staffs., DE14 2ST. Mail Order Only. (0283) 65435 S.A.E. enquiries.
Add 50p p&p to all orders. Prices include VAT. Access & Visa phone/post

Official school orders welcome.
OVERSEAS: Payment must be in sterling
IRISH REPUBLIC + BFPO - UK PRICES.
EUROPE: UK PRICES + 10%
ELSEWHERE: WRITE FOR QUOTE.
Goods normally despatched by return of post.

SECURITY

Install your own system and save using built and tested modules

A COMPLETE INTRUDER ALARM

EASILY ASSEMBLED ULTRASONIC UNIT CK 5063

Requires no installation. Easily assembled using our professionally built and tested modules.

- Adjustable range up to 25ft.
- Built-in entrance & exit delay
- Built-in timed alarm
- Key operated switch - Off, Test and Operate
- Provision for an extension speaker
- Fully self-contained
- Uses US 5063, PSL 1865, Key Switch 3901, 3" Speaker 3515

only **£37.00** + V.A.T.



Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built-in LED indicator and test position the unit is easily set-up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 90db's sound, or even 110db's with an additional speaker. All parts included and supplied with full instructions for ease of assembly. Size 200 x 180 x 70mm. Order as CK 5063

DIGITAL ULTRASONIC DETECTOR US 5063



only **£13.95** + V.A.T. **NEW**

- 3 levels of discrimination against false alarms
 - Crystal control for greater stability
 - Adjustable range up to 25ft.
 - Built-in delays
 - 12V operation
- This advanced new module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions. The module has a built-in exit delay and timed alarm period, together with a selectable entrance delay, plus many more outstanding features.

ULTRASONIC MODULE US 4012



£10.95 + V.A.T.

- Adjustable range from 5-25ft.
- This popular low cost ultrasonic detector is already used in a wider range of applications from intruder detectors to automatic light switches and door opening equipment, featuring 2 LED indicators for ease of setting up.

INFRA-RED SYSTEM

IR 1470 only **£25.61** + V.A.T.



Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft, operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications. Size 80 by 50 by 35mm.

POWER SUPPLY & RELAY UNIT PS 4012

Provides stabilised 12V output at 85mA and contains a relay with 3 amp contacts. The unit is designed to operate with up to 2 ultrasonic units or 1 infra-red unit IR 1470. Price **£4.25** + V.A.T.

SIREN MODULE SL 157

Produces a loud penetrating sliding tone which, when coupled to a suitable horn speaker, produces S.P.L.'s of 110db's at 2 metres. Operating from 9-15V. Price **£2.95** + V.A.T.

5 1/2" HORN SPEAKER HS 588

This weather-proof horn speaker provides extremely high sound pressure levels (110db's at 2 metres) when used with the CA 1250, PS 1865 or SL 157. Price **£4.95** + V.A.T.

3-POS. KEY SWITCH 3901

Single pole, 3-pos. key switch intended for use with the CA 1250. Price **£3.43** + V.A.T.

Add 15% VAT to all prices
Add 50p post & packing to all orders
Units on demonstration
Shop hours 9.00 to 5.30 p.m.
Closed Wednesday
Saturday 9.00 to 1.00 p.m.
SAE with all enquiries
Order by telephone or post using your credit card

ALARM CONTROL UNIT CA 1250



Price **£19.95** + V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system whether a highly sophisticated installation or simply controlling a single magnetic switch on the front door.

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charging facility
- Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage
- 2 operating modes - full alarm/anti-tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for external loads
- Test loop facility

SIREN & POWER SUPPLY MODULE PSL 1865



only **£9.95** + V.A.T. **NEW**

A complete siren and power supply module which is capable of providing sound levels of 110db's at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 to form a complete alarm.

HARDWARE KIT HW 1250



only **£9.50** + V.A.T. **NEW**

This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label. Size 200 by 180 by 70mm

ULTRASONIC MODULE ENCLOSURE



only **£2.95** + V.A.T. **NEW**

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063; for US 4012 order SC 4012.

RISCOMP LIMITED

Dept. HE9
21 Duke Street,
Princes Risborough,
Bucks. HP17 0AT
Princes Risborough (084 44) 6326

FEEL HEALTHIER WITH ZEPHION

Bring fresh clean air into your home with the Zephion Air Ioniser.



Air free from smoke, dust and other pollutants of modern day living can bring to many the relief of breathing comfortably once again.

We are confident that you will be delighted with the Zephion Air Ioniser, but if you are not entirely satisfied a full money back guarantee is available if items are returned in good condition within 28 days.

BUILD IT YOURSELF!

clip the coupon

TO:- Dataplus Developments
81, Cholmeley road
Reading, Berks.
RG1 3LY TEL:- 0734 67027

NAME:-

ADDRESS:-

PLEASE TICK

ZEPHION KITS @ £24.15p
(Kits include all parts)

ZEPHION AIR TONERS
BUILT AND TESTED. @ £34.50p

Money immediately refunded if items returned in good condition.

Prices include VAT & postage; allow 14 days for delivery. DATAPLUS HE

Send for my CATALOGUE ONLY 75p (plus 25p post/packing)

My all-inclusive prices quoted in the Catalogue are the lowest. All below normal trade price — some at only one tenth of manufacturers quantity trade.

Millions of components : thousands of different lines

- Rechargeable Nickel Cadmium batteries (ex unused equipment)
 - AA(HP7) 1.25volt 500ma. Set of four £2
 - Plastic container of ten £5
- Watch/Calculator/Lighter etc, Mercury batteries
 - RW52(PX675) RW54 Made by Ray-O-VAC
 - RW56 (DH323,WH8) 31p each or
 - RW57, RW58 10 for £2.60, 100 for £21
- IN4004 or IN4006 Diodes. 300 for £6.48p
- TO5 or TO18 Heatsinks 7 1/2p, 100 for £6.50, 1000 for £55
- Clipover Heatsink for I/C or TO202 device 21 x 18mm 18p or 100 for £16.50 per 1000 for £155
- Heatsink for TO3 or Plastic Power 19p, 100/£17.50, 1000/£165
- Modern Telephone Handset and lead in white, red, blue, grey, yellow, green or black £2
- BU508A TV line output transistor, 1,500v, 15A, 125watt £1.53p or 40 for £40 or 400 for £300

SEND PAYMENT PLUS 16p SAE OR LABEL ONLY

Prices you would not believe before inflation!


BRIAN J. REED
TRADE COMPONENTS
ESTABLISHED 26 YEARS

161 St. Johns Hill, Battersea, London SW11 1TQ
Open 11 am till 6.30pm Tues. to Sat. Telephone: 01-223 5016

A Hobby Electronics Hardware Review

MEMOTECH

500 / 512

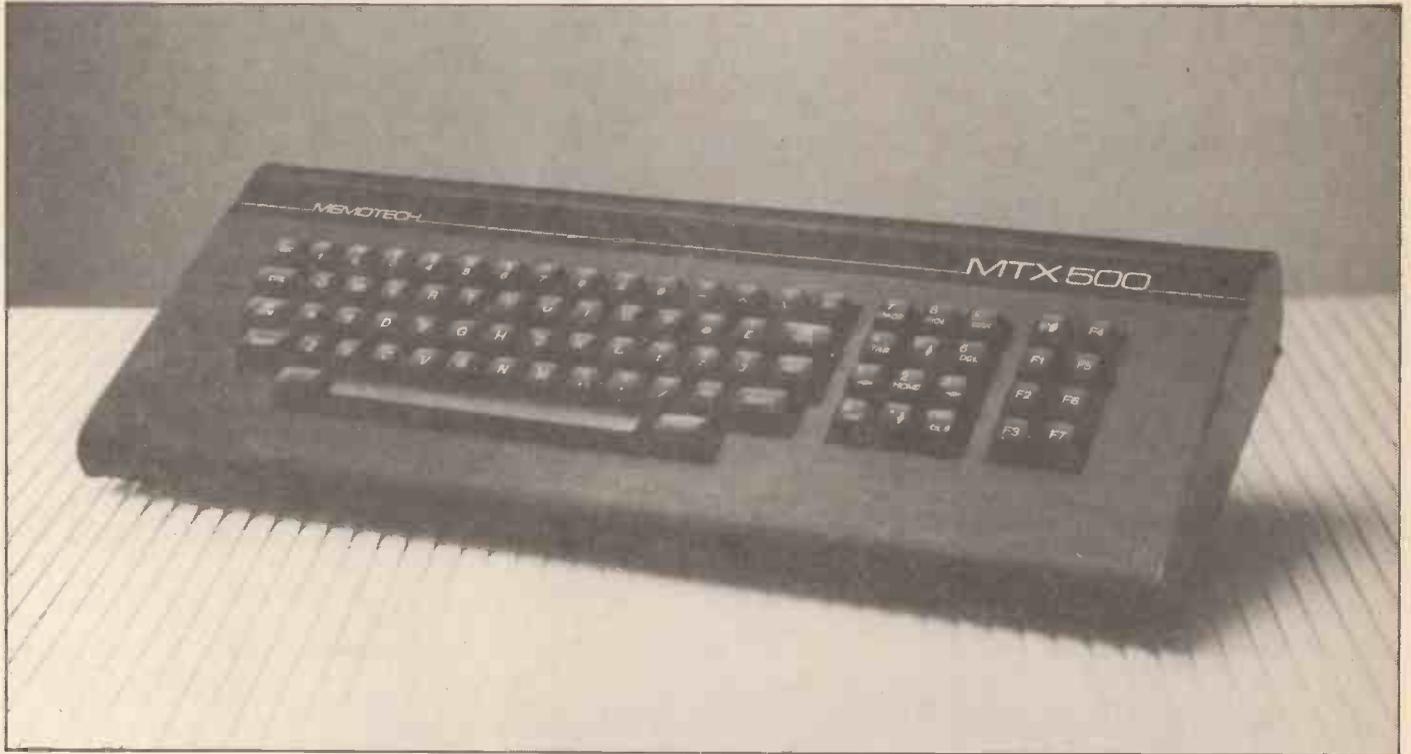

An impressive new computer from a company best known for ZX peripherals.

David Norman

Memotech has served a long apprenticeship in the field of microcomputers as a manufacturer of high quality ZX81 peripherals, and now they are set to take a slice of the home and business market with their MTX range of computers.

The MTX 500 is their basic machine which has an all-inclusive price of £275, which puts it squarely into the highly competitive area presently dominated by the BBC and Commodore machines. The specifications of the MTX look impressive and now that the machine is in the shops the real tests and comparisons will determine if Memotech have got it right.

If first impressions are important, then Memotech have scored highly — their product comes beautifully packed and presented. The micro itself is cased in black anodised aluminium and carries a total of 79 keys which have a crisp and positive feel to them. The

power supply is a separate unit, equally stylish, and rated at 1A. All the usual cables and documentation are in the box but as you dig in deeper you will find no fewer than five cassettes. There is the introductory tape, a cassette-cleaning tape and a C15 blank tape from Memotech, and games tapes "Toado" and "Draughts" from Continental Software who have produced the first batch of games and utility software for the MTX range.

"Toado", which is a very good frog-crossing-dangerous-things type of game, was responsible for delaying this review for an hour or so, but the introductory tape, which I believe is only the first rush version, leaves a great many things to be desired and is way behind the standards set by the Spectrum's introductory tape by Horizon. However, having spent your £275 you are in no danger of having to spend any more

cash on peripherals to compensate for shortcomings in the basic package and that is something you cannot say about some of the Memotech's competitors.

RAM Is RAM

The MTX 500 is a 32K machine, period. No matter what type of graphic mode you choose you have 32K of user RAM; the graphics screen has its own memory and you won't find your precious program space shrinking away to a few kilobytes. However, if 32K is insufficient for your purpose, you have the option of buying the MTX 512 which is identical to the 500 except that it is provided with a 64K of user RAM, or you may buy add-on memory boards for the 500 which fit inside the case. Lack of memory is certainly not going to be a problem for MTX users.



Plenty Of Ports

The MTX is a wide computer — about 19in — so there is plenty of room along the back for a multitude of connectors. They are generally high quality sockets, but deeply recessed and therefore difficult to get at, though this won't matter if the machine is going to stay in one place most of the time. The cassette sockets are the 3.5mm jack type which I think become slack and unreliable after some months of constant use, but they do seem to be popular with computer manufacturers these days. There is a phono socket so that the sound output from the computer can be sent to a hifi. In normal use the sound channels, of which there are four, will pass through the television and can therefore be easily adjusted to the volume of your choice.

Thankfully, the keyboard doesn't beep every time a key is pressed, though doubtless it could be made to do so if you wished. Monitor and printer outputs are present, as are two joystick ports which will accept the popular "Atari" type of joystick. All the important CPU signals are available on an edge connector, though this is normally blanked off in the interests of safety (the machine's safely by the way, not the user's!), and two RS232 interfaces are available as an optional extra. As if this wasn't enough, there is also an uncommitted 8-bit I/O port on the PBC itself, just

sitting there as a 16 way IC socket and waiting for the home constructor to pop in a 16 pin header on some ribbon cable so that the micro can start running that proverbial power station.

Up And Running

Connecting the MTX to cassette and television is straightforward. The DIN power supply connector was a *very* tight fit in its socket, but fortunately once it is in there is no need to disconnect. Not only is there an illuminated switch on the power supply but there is also a reset button on the computer to bring you out from all crashes, infinite loops and other software nightmares. It is as well that there is a light on the power supply since the MTX runs silently, without hums or buzzes. "Toado" loaded easily and quickly from a cheap tape recorder, but loading a program which I had previously saved proved trickier and it took quite a few saves and loads to get the volume levels correct. The cassette baud rate is set at a fast 2400, but since it is under software control it may be changed.

The display on a Hitachi 12in colour TV was steady and the colours true, though the TV did need retuning after a warm-up period of about half-an-hour. There was no "dot-crawl" on either stationary or moving characters. The format of the screen in character mode

is 40 x 24 and in general the text is clear and of pleasing proportions. However, I didn't much care for the lower case g so I used the GENPAT command to redefine it. Any character in the standard ASCII set (codes 32 to 127) can be redefined in this way, and you may also define 26 new characters (or graphics) for codes 128 to 154, and type most of them into the computer using the special function keys marked F1 to F8. In graphics mode there are 32 characters on a line, so there is more space between each character. You can use the keyboard to change the character set to Spanish or German, in which case the specialised European symbols occur in place of the English keyboard's square-brackets and so on.

All the video work is done by one chip, the Texas 9929. This is a standard video Display Processing (VDP) chip capable of producing four display modes, 16 colours and up to 32 sprites, about which more will be said later. It is also responsible for producing oval circles on British televisions, which is a problem first encountered by ORIC. Oric solved the problem eventually, and I have no doubt that Memotech will do so as well, but I daresay they will have to suffer a lot of flak from other computer manufacturers until they get it right. One other possible source of complaint is that the leading character position in each line may be lost in the television

Table 1

ABS	ASC	ATN	LN	CHR\$	CLEAR
CLS	CONT	COS	DATA	DIM	EDIT
EXP	AND	GOSUB	GOTO	INKEY\$	IF-THEN-ELSE
INPUT	INT	LEFT\$	LEN	LET	LIST
LLIST	LOAD	LOG	MID\$	NEW	FOR-STEP-NEXT
OUT	PAUSE	PEEK	POKE	PRINT	ON/GOSUB
RAND	READ	REM	RESTORE	RETURN	ON/GOTO
RIGHT\$	RND	RUN	SAVE	SGN	SIN
SQR	STOP	STR\$	PI	TAN	USR
VAL	VERIFY	OR	NOT	MOD	LPRINT

Table 1. Standard BASIC commands and functions.

TABLE 2

BAUD	CLOCK	INK	PAPER	PAUSE	NODDY
PLOD	CSR	PANEL	SOUND	ASSEM	ATTR
COLOUR	EDITOR	DSI	SDBUF	TIME\$	GR\$
SPK\$	ROM	CRVS	VS		

Table 2. The extended BASIC group.

margin. This is not noticeable at first, since the software places print statements a couple of spaces on from the beginning of a line. I put the MTX UHF output onto an old Ferguson 12in black and white TV and obtained perfect alignment of the screen, with both the start characters and the end characters of each line clearly visible. The general advice must be to try always to buy a TV or monitor with a horizontal hold, accompanied by a plea to the manufacturers to start putting these controls back onto their television sets!


High Command

The MTX has 24K of ROM, so there is plenty of space for some powerful and sophisticated commands. The manual supplied with the review machine is a provisional version: it runs to 250 pages of A4 paper and contains a wealth of technical information, but even so it is evident that a more comprehensive manual or book will be necessary to enable the user to get the best out of this computer. The ROM contains the BASIC, an interactive language called NODDY and a Assembler/Disassembler with powerful debugging facilities. The MTX BASIC has extra commands to enable the user to handle colour, sound, graphics and sprites without recourse to PEEKs and POKEs (Commodore please

note!) and it should please most people. The basic BASIC seems to have most of the standard commands (see Table 1) You may be disappointed to see that PROCEDURES and DO . . . UNTIL constructions are missing, but on the other hand you should be pleased to find that syntax is checked at the time of entry, and that keywords may be entered in a shortened form.

The MTX doesn't like the user to miss out spaces, and requires LET to be used when assigning variables. Listings will therefore look neat and be readable and in any event with so much memory there should be no need to compact the program. To make up for the extra keyboard-bashing, Memotech have provided an AUTO facility whereby your listing has the line numbers entered for you in increments of your choice. In my option this is far more useful than RENUMBER which the MTX doesn't offer, perhaps on the grounds that if you're using a Memotech computer your listings aren't going to get into the messes that RENUMBER sorts out. It is when you are entering and editing BASIC that the MTX auxiliary keypad comes into use. Insertions and deletions can be undertaken with the minimum amount of fuss and bother. It always

Figure 1. The MTX expansion bus.

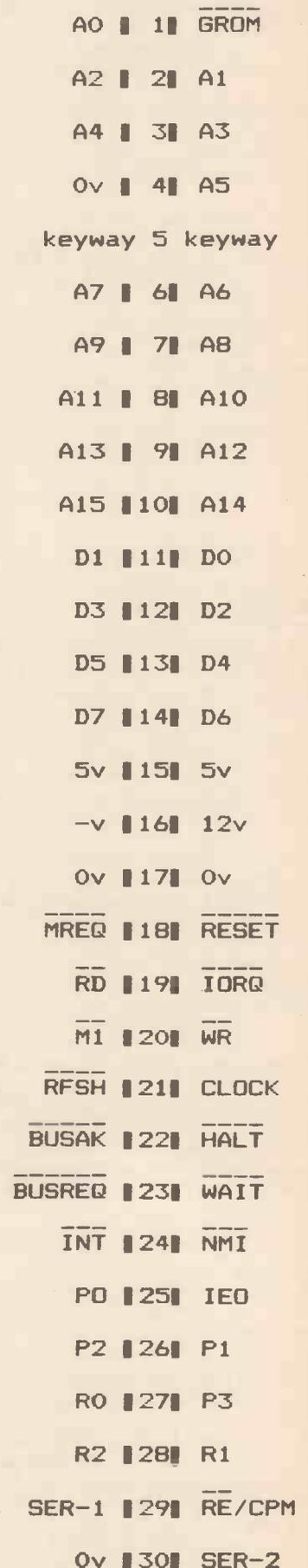

takes some time to get used to a new keyboard, and different users have their own personal preferences. Most touch typists, I am told, would prefer the RETURN key to be larger, but its size doesn't bother me. CLS (clear screen) is more of a problem — like the other editing keys it is available as an unshifted key, yet to press it by accident would wipe as many as 960 characters from the screen, and that could be very annoying.

Looking now at the extra BASIC commands, shown in Table 2 the power of the MTX should begin to become apparent. NODDY, ASSEM and ROM calls up the NODDY language, the assembler and extra ROMs respectively.

The ROM could contain another language such as FORTH and Memotech clearly have the expansion prospects for this machine well planned out: the ROM cartridges are designed to plug into the CPU bus at the side of the machine.

Assemble, Please

The assembler is called from BASIC, and it assembles the code in situ, as part of the BASIC listing. The assembler itself is fairly basic, but it is easy to use and to edit. Numbers may be entered in either hex or decimal, and addresses are printed out in hex. Address labels are obviously accepted, but labels equated to numeric values are not supported. Define Space and Define Byte (incorporating Define String) can be used, but Define Word is absent. The BBC computer has an assembler incorporated in its BASIC which enables easy machine-code programming of the 6502 processor and Memotech have thus created a similar facility which will help programmers get to grips with the Z80 processor.

NODDY is a new language designed to simplify text handling. It has only 11 commands, but can be incorporated into BASIC in such a way that the two languages work together. Coupled with the MTX editing keys it should take the drudgery out of creating programs with a large textual content. Applications are obviously going to suggest themselves in areas of the school curriculum, in the fast-training of personnel in commerce, and in adventure-game writing. Time will tell how useful NODDY will be, and Memotech are to be congratulated for incorporating it into their computer — it's an experiment on their part and a challenge for the software writers to make something of it.

PANEL calls up the front panel display and puts the user directly in control of the MTX monitor at machine code level. There will be many people who have seen a front panel display on the 380Z computer in secondary schools or colleges, and the MTX panel is very similar. Basically it is a window looking in at the registers and memory locations of the computer and it is an invaluable aid to all users interested in writing and debugging program and control of I/O devices at machine code level. To have it already in the machine, and not to have

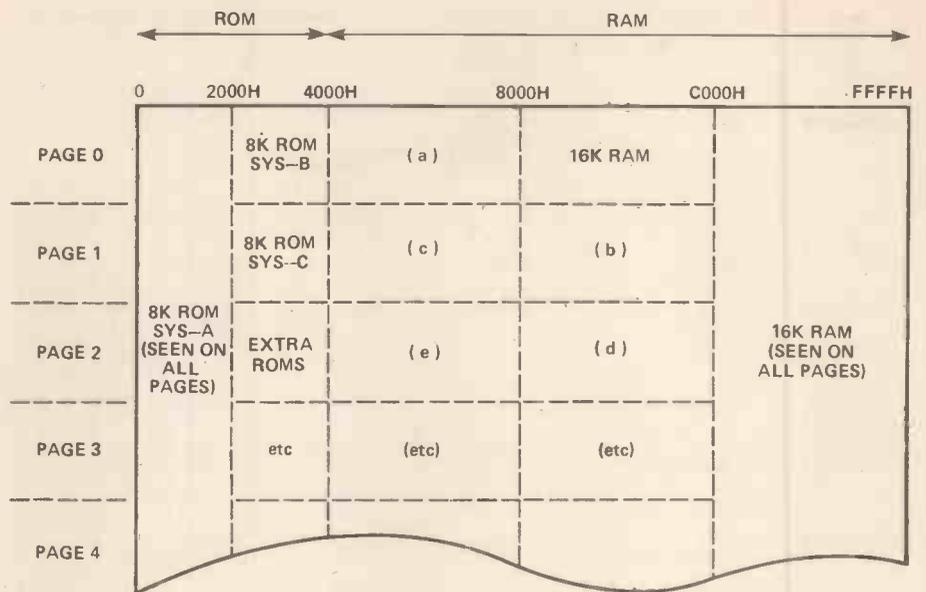


Figure 2. The MTX features a paged memory system, allowing extra ROM and RAM to be added. The diagram shows the basic MTX 500 configuration; RAM is added in the order (a), (b), (c), and so on.

Table 3

CIRCLE	DRAW	PLOT	ARC	LINE	ANGLE	VIEW
PHI	SPRITE	MVSPR	ADJSPR	CTLSPR	GENPAT	

Table 3. The graphic and sprite group; powerful instructions for multi-level, highly mobile screen displays.

Table 4

PAGE	: Toggles scrolling of screen data.
EDL	: Deletes from cursor to end of line.
BRK	: Break out from program.
TAB	: Advance cursor 8 spaces.
DEL	: Delete character at cursor and close up the line.
HOME	: Put cursor to top left of Virtual Screen.
INS	: Insert text, expanding line to suit.
CLS	: Clear screen.
ENT	: Enter (Return).
CURSOR LEFT : CURSOR RIGHT : CURSOR UP : CURSOR DOWN.	

In addition certain controls keys and certain sequences of key presses give other useful functions:

CTL W	tabs in a backwards direction.
CTL	turns the cursor off.
CTL D,n	sets the background colour to n.
ESC,B,2	sets the English character font.
ESC,K	duplicates a line.

Table 4. The MTX provides a number of control and command instructions particularly useful for editing.

```

BD2E      LD A,#01
BD30      LD (#BCD5),A    AF 0000 F3
BD33      JR #BD3B        BC 0000 F3
BD35      LD B,#01        DE 0000 F3
BD37      XOR A           HL 0000 F3
BD38      LD (#BCD5),A    IX 0000 F3
BD3B      PUSH BC         IY 0000 F3
BD3C      LD B,#01        PC >BD3B 32
BD3E      CALL #BD56
BD41      DJNZ #BD3E
BD43      CALL #934B
BD46      POP BC
BD47      DJNZ #BD3B
BD49      RET

LD (#BC5D),A

A180: F5 3E CF D3 06 3E FF D3
A188: 06 3E 0F D3 07 DB 04 E6
A190: 01 20 FA F1 F5 FE 0D 20
A198: 0A CD 2B 0E 3E 0A CD 2B
A1A0: 0E F1 C9 CD 2B 0E F1 C9
A1A8: F6 80 D3 05 E6 7F D3 05

List>BD2E■

```

Figure 3. The MTX "front panel" will be very helpful when de-bugging machine code programs.

to wait until a software house produces a debug/monitor at a price of between £10 and £20, must be a bonus for which Memotech should get considerable credit.

Other interesting commands in this group are the COLOUR, PAPER, INK and ATTRIBUTES which set up the various colour and printing options: the CLOCK and TIMES which handle a real-time clock in hours, minutes and seconds format, and the SOUND command that passes either 3 or 7 parameters to the Texas 76489 sound chip. This, incidentally, is the same chip that is used in the BBC computer so we can, I hope, look forward to hearing the same richness of tones that that computer is capable of producing.

Virtual Screens

The MTX has an inbuilt method to allow you to create smaller screens within your TV screen. These are called virtual screens, and up to eight are allowed. All print commands are relative to the screen you are using. For example, while you are in BASIC, four virtual screens have already been defined for you, and you are in fact using them.

Message errors come up on VS 7, a screen one row deep at the bottom of the TV. BASIC lines which you are entering or editing are constructed as on continuous line in VS 0 which is four rows deep. The program is listed on VS 1 which is the rest of the TV at nineteen rows deep. When you RUN a BASIC program, you default to VS 5, which at 24 rows deep is the entire TV screen. This takes some getting used to when you first encounter the MTX, but it is undoubtedly a useful function to be able to isolate and work on just part of the TV screen. RML's 480Z has such a function but that is a computer which costs considerably more than the MTX 500.

Sprites And Things

The graphics screen has a resolution of 256 x 192 pixels and the graphic commands are listed in Table 3. PLOT, LINE and CIRCLE are fairly standard point and line drawing commands, but there is also ANGLE, PHI, DRAW and ARC and these are used together to determine the direction of lines and patterns drawn in the style of LOGO's TURTLE graphics. The provisional manual gives short examples of how to

handle these advanced graphics, and it is to be hoped that further instructions will be provided in the final version of the manual.

And so now to the Sprites: "Up to 32 independently controllable user definable sprites, plus pattern plane and backdrop plane" to quote the specifications, but what exactly does this mean? Think of the TV screen as a drawing board with a small piece of paper on it. The paper represents the physical size of the video screen, 256 x 192 pixels and can be a colour of your choice. This is the "backdrop-plane". Onto that paper, that screen, goes the text and/or graphics shapes in any ink colour you choose. This is the "pattern-plane". Consider the paper and the ink as a landscape. Now imagine a large piece of cellophane, 8192 x 8192 pixels in size, on which you have placed a small object called a sprite. The cellophane is your "sprite-plane". You can see the landscape beneath the cellophane, except where the sprite obscures it. Furthermore, you can move the sprite across the cellophane (with sprite) relative to the landscape. Finally, imagine that you could have up to thirty-two separate sheets of cellophane all piled on top of the landscape, and each with a moving sprite on it. That's how sprites help to achieve animation effects, and the commands such as MVSPR (move sprite) and CTLSPR (control sprite) help to set up the operating conditions. Once set, the sprites move around independently of the BASIC program, until such time as their parameters are altered. Collisions between sprites are detected, and can be checked upon by a PEEK to a register in the VDP chip.

Conclusion

The MTX 500 is well designed and carefully constructed, and has hardware and software features that make the £275 asking price eminently reasonable. It seems to be suitable for both the home market and the educational market, and to novices and experts alike. If Memotech can correct just a few minor problems, and get their promised CP/M and other extensions along on schedule, they will have an excellent all-purpose machine, and 1984 could be a very good year for them.



Lightning

Chess Timer

Designed for use in chess tournaments, HE's Chess Timer can be set anywhere between 1.5 and 96 seconds for any timed-move game.

AS the only electronics engineer in Leighton Buzzard Chess Club it was natural that I should be asked to make a 'buzzer' for a Lightning Chess Tournament — and thus save £30 to £40 of club funds! But since I had never played in a lightning chess tournament, I first had to try to invigle a detailed definition of the required operation of a chess buzzer. A brief description of how chess is played in a lightning tournament may help those who are as unsure as I was.

A player has to make his move on the 'buzz', leaving the interval to the next 'buzz' as his opponent's thinking time. If a player makes his move late he would be reducing his opponent's thinking time unfairly, and if a player moves prematurely he would be giving his opponent an unnecessary advantage. This enforced rhythm of play is quite unlike anything one meets in normal chess.


A period of about ten seconds between buzzes was requested, but as this seemed rather approximate and arbitrary I decided to provide a wide control range so that it could be adjusted on the night.

Another requirement was that the unit should be small and battery powered, with the battery having a minimum of a ten hour life but preferably much longer.

Overview

For a battery powered unit, low current consumption becomes the prime design consideration. A good choice of an audible output device, with low current consumption and a high output sound level, is one of the many piezoelectric transducers currently available. Whilst glancing through the Maplin catalogue recently I saw a transducer that can be driven by a 3-10kHz square wave and since this sells for about 30p, it seemed ideal.

Figure 1. The block diagram of the Chess Timer.

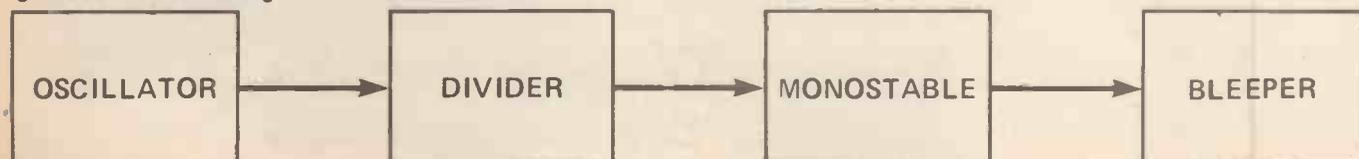

Mike Vince



The block diagram of the basic functions required are shown in Figure 1. An oscillator with a variable period covering the 1.5-12 second range is possible; however, it seemed easier to me to design a circuit using a higher frequency oscillator with its output being divided down to give the required period. The 4060 is a combined CMOS oscillator-and-divider IC available at a reasonable price, and this was the obvious choice for the application. The monostable is used to give a short output pulse whose length is independent of the input frequency.

Circuit Description

The full circuit diagram is shown in

Figure 2, and for clarity the oscillator section has been redrawn in Figure 3 showing some of the internal gates of the 4060.

As can be seen, the oscillator is a standard circuit often used in HE projects, and the values of C2, R1, R2 and RV1 have been chosen to give an output frequency in the range 40-320Hz. The rest of the 4060 is a 14-stage binary counter with the outputs from every stage being available — except for stages 1, 2, 3 and 11.

Since so many outputs are available I chose to provide two speed ranges by utilising the Q9 and Q12 outputs. For the fast range this gives intervals between 'buzzes' of approximately 1.5 — 12 seconds, and for the slow range of approximately 12 — 96 seconds.

Choosing to use different outputs of

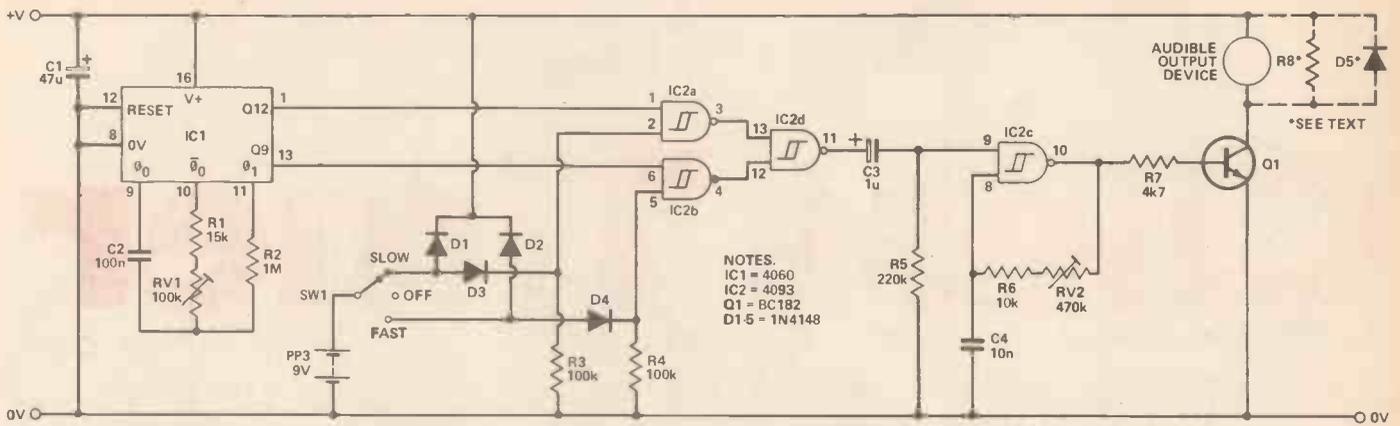


Figure 2. The circuit. R8 and D5 are optional components which may be required according to the exact method used to give the audible tone.

the 4060 one can of course have other ranges if one wished, Q10 giving half the speed between Q9 and Q12 is achieved by IC2a and IC2b.

Diodes D1, D2, D3 and D4 are included so that a single pole centre-off switch can act as both speed-range select and on/off. When the switch is in the slow position power supply current flows through D1 and pin 2 of IC2a is taken to a high logic level via D3.

The truth table for a NAND gate is given in Table 1, and from this it can be seen that if one input of a NAND gate is held high (lines 3 and 4), then the output level is the inverse of the second input. Similarly if the first input is held low (lines 1 and 2), the output is high irrespective of the level on the second input.

Thus IC2a output, pin 3, has the inverse of the waveform from Q12, whilst IC2b output, pin 4, will be high since pin 5 is held low by R4. IC2d then re-inverts the signal and thus its output, pin 11, has the same waveform as Q12.

A similar process applies with the switch in the fast position; in this case IC2d output has the same waveform as Q9.

Next, C3, R7 and IC2c form a monostable circuit, which is triggered on the rising edge, rather than the falling edge, of the divider output square wave.

IC2c, C4, R8 and RV2 form a gated oscillator and when pin 9 is at a logic high level, a short audio tone will appear at pin 10 (Figure 4). RV2 is

Table 1

	A	B	$\overline{A \cdot B}$
1	0	0	1
2	0	1	1
3	1	0	1
4	1	1	0

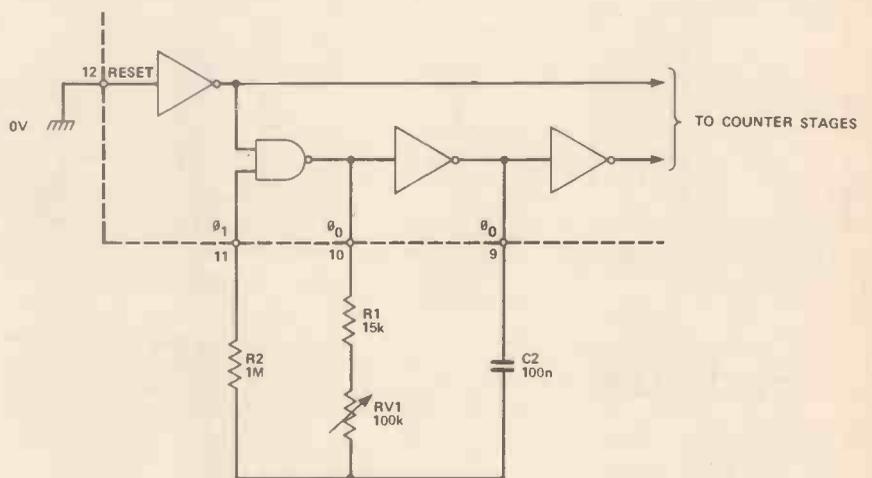


Figure 3. The choice of timer intervals is determined by the outputs of IC1. This is a close-up of some of IC1's internal gates.

required to adjust the frequency of this audio tone, since this type of circuit is very sensitive to component tolerances.

If the output of the unit is to be taken to an external amplifier the output may be taken directly from IC2c pin 10. However, the signal level will be about 8V peak-to-peak, and one should check whether an attenuator is necessary to reduce the signal level.

If a piezoelectric transducer is used it may be necessary to fit R8, and this will have to be chosen by experiment to match the chosen transducer. The other possibility is to use a small loud speaker, and under these circumstances R8 will become diode D5, and will need to be fitted as shown (dotted in Figure 2).

Construction

The circuit may be built on Veroboard, but I recommend using the PCB as this will produce a neater unit. The PCB overlay, Figure 5, shows the position and orientation of all components, and the usual care should be exercised over the orientation of all diodes, C1, C3, Q1


and both ICs. Since semiconductors are the most likely components to be damaged by overheating they should be left to last.

(Normal precautions should be taken when handling the CMOS ICs so as to prevent the possibility of damage due to static; it should be noted that static more often reduces the reliability of CMOS and that complete failure is a rarer problem).

For neatness, Veropins should be used for connecting the wires to the PCB.

The unit can be assembled into any box measuring 4 3/4" x 2 1/2" x 1 1/2" or larger. Before connecting the battery

Figure 4. Output signals from ICs, including the audio tone.

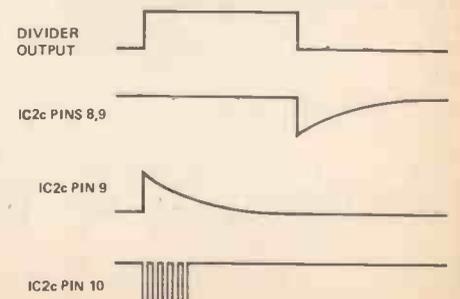

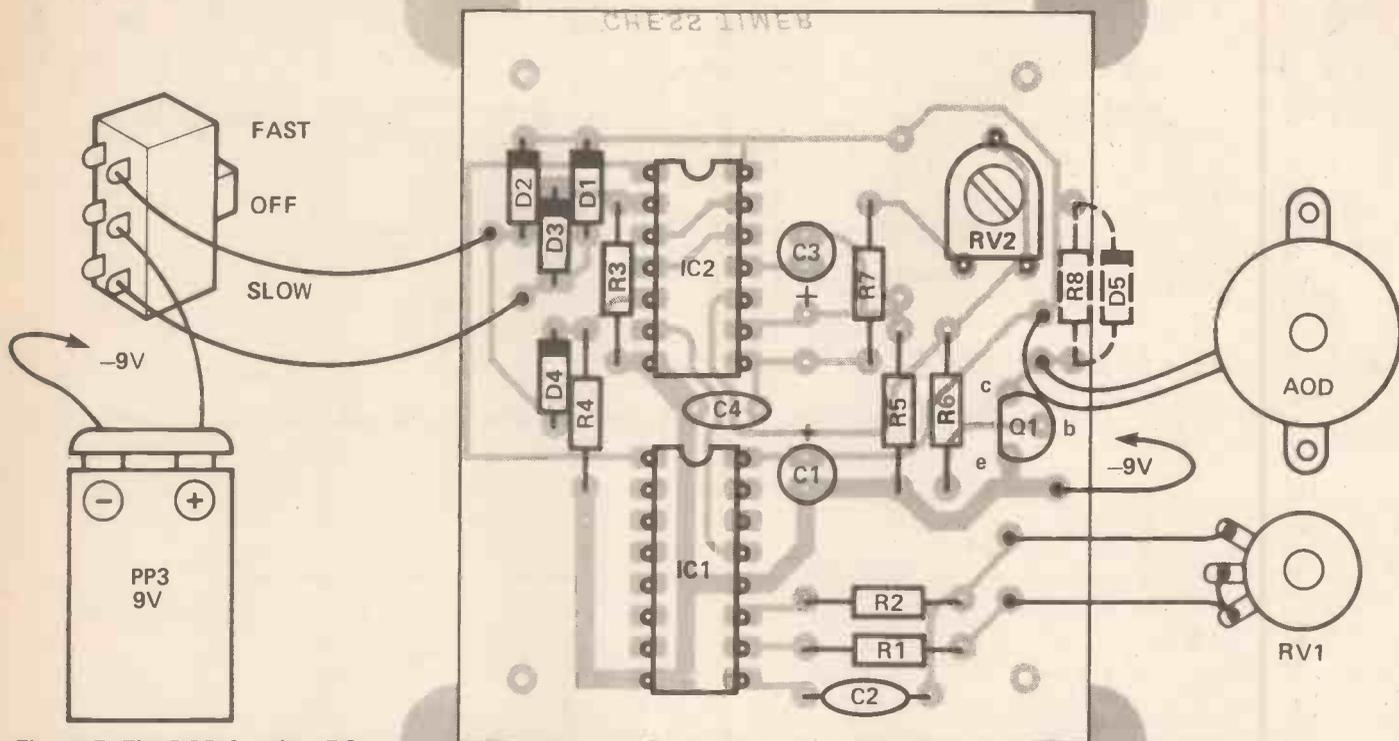


Figure 5. The PCB Overlay. R8 and D5 are optional.

Parts List

RESISTORS

(All 1/4 5% carbon)

R1	15k
R2	1MO
R3, 4	100k
R5	220k
R6	10k
R7	4k7
R8	(see text)

POTENTIOMETERS

RV1	100k	linear
RV2	470k	horiz preset

CAPACITORS

C1	47u	10v radial electro
C2	100n	polyester
C3	1u	10V radial electro
C4	10n	polyester

SEMICONDUCTORS

IC1	4060
IC2	4093
Q1	BC182
D1-5	1N4148

MISCELLANEOUS

SW1	DPDT	centre-off
PCB or Veroboard; case, 4 3/4 x 2 1/2 x 1 1/2 in; piezo buzzer (Maplin QY13P); Veropins, wire, solder etc.			


BUYLINES page 26

and turning on, check again for solder bridges or for components the wrong way round, and do check that the battery connections are correct. If you don't, you may need to buy some new components!

On the prototype the transducer was fixed to the front panel with double sided adhesive tape, but before doing so make sure suitable holes have

been drilled in the box to act as a sound outlet.

When ready to test, set the speed range switch to fast and the speed control to approximately half way. If properly built, the unit will now buzz about every six seconds. Check that both speed ranges work and that the control varies the speed. Now set up the chess board — and good luck!

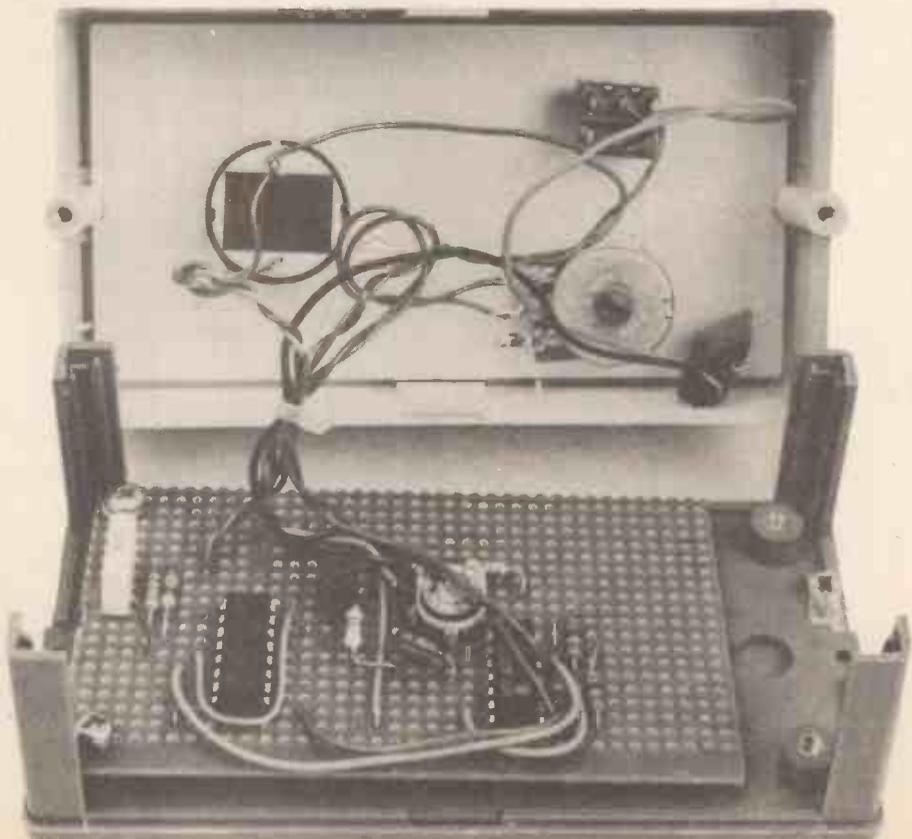


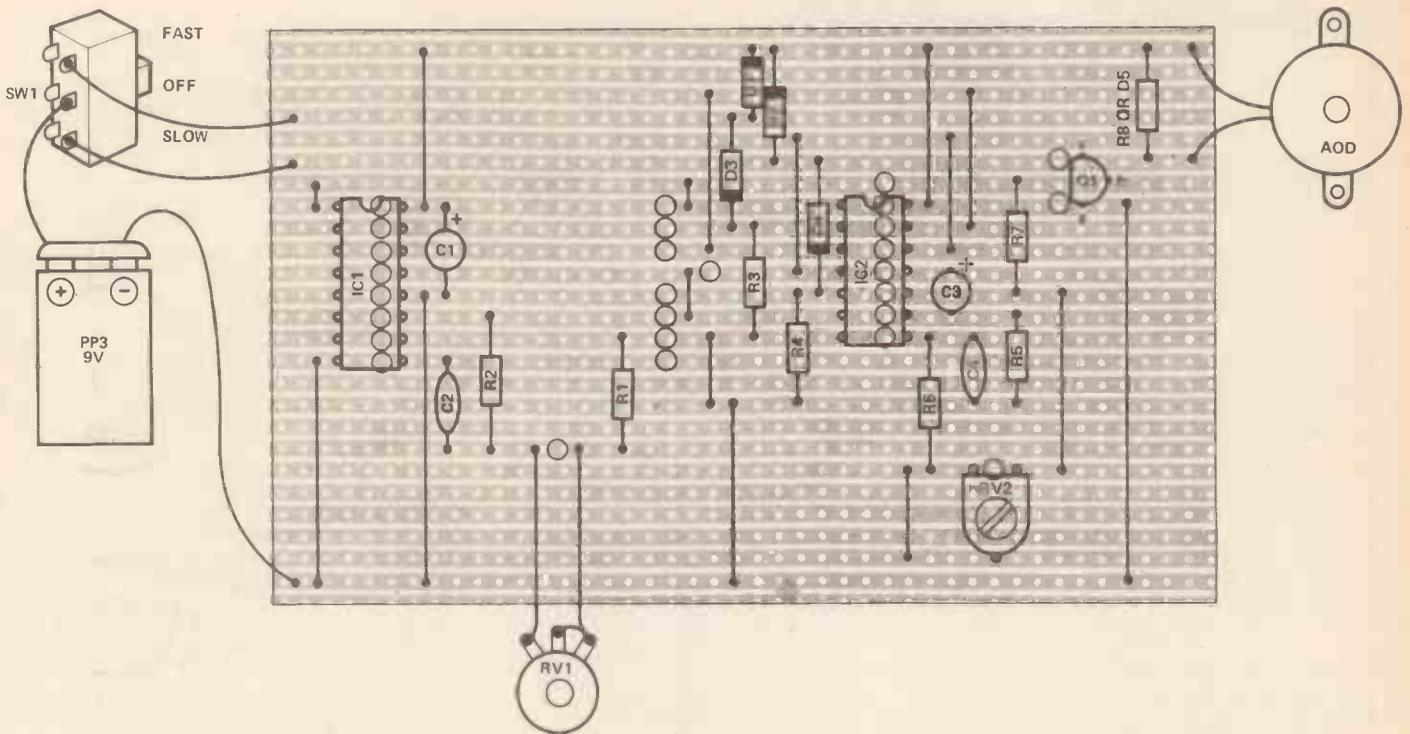


Figure 6. This Veroboard layout is untested and has been laid out without regard to size, to assist experimenters doing their own layouts. It is not the same as the Vero layout used in the original model (see picture, bottom left), which was constructed for a maximum saving on space. Also, the switch wiring in the unmodified model is different from the arrangement used in the project, so don't attempt to copy it. The Verolayout in the photo may offer some clues to anyone doing his own Veroboard.

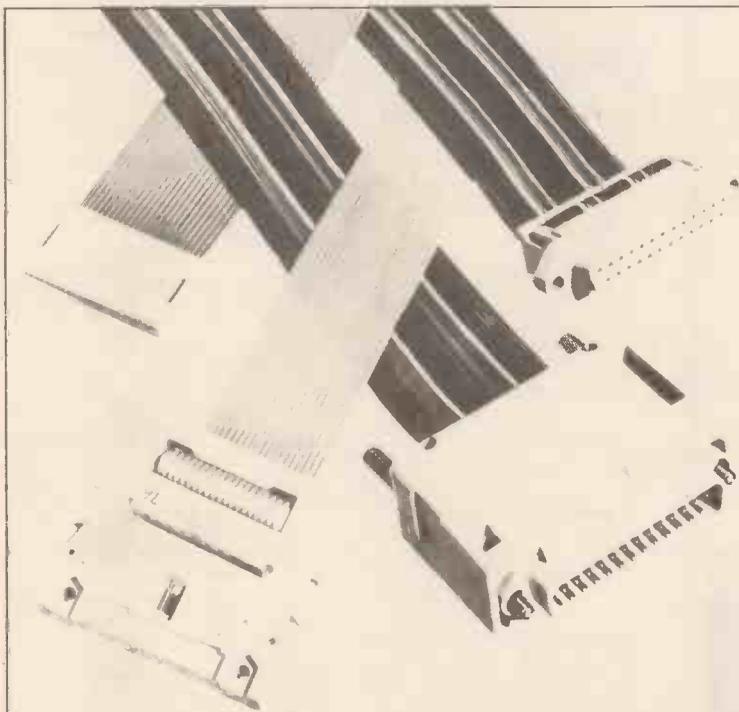

Choose from our M50 range of exciting products all designed to assist the hobbyist in building an interconnection system most suitable for his particular application:

headers; sockets; colour coded cable; DIP connectors; sub-miniature D25 way plug, socket and hood.

With the M50 you get much more than just a good contact. You get a complete interconnection system that includes the cable.

Our new catalogue containing over 150 new products is available now

For further information on these products ring (04215) 62829 or write to:



BICC-VERO ELECTRONICS LIMITED


Retail Dept., Industrial Estate,
Chandlers Ford, Hampshire, SO5 3ZR.

**Your Interconnection
System for the
Microcomputing World**

TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

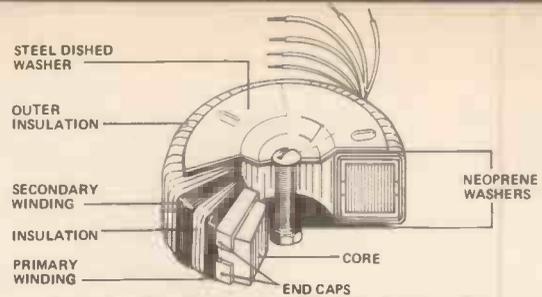Our large standard range is complemented by our **SPECIAL DESIGN** section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



15 VA 62 x 34mm Regulation 19%	50 VA 80 x 35mm Regulation 13%	120 VA 90 x 40mm Regulation 11%	225 VA 110 x 45mm Regulation 7%	500 VA 140 x 60mm Regulation 4%
SERIES SECONDARY No Volts Current RMS	2x010 6+6 4.16 2x011 9+9 2.77 2x012 12+12 2.08 2x013 15+15 1.66 2x014 18+18 1.38 2x015 22+22 1.13 2x016 25+25 1.00 2x017 30+30 0.83 2x028 110 0.45 2x029 220 0.22 2x030 240 0.20	4x010 6+6 10.00 4x011 9+9 6.66 4x012 12+12 5.00 4x013 15+15 4.00 4x014 18+18 3.33 4x015 22+22 2.72 4x016 25+25 2.40 4x017 30+30 2.00 4x018 35+35 1.71 4x028 110 1.09 4x029 220 0.54 4x030 240 0.50	6x012 12+12 9.38 6x013 15+15 7.50 6x014 18+18 6.25 6x015 22+22 5.11 6x016 25+25 4.50 6x017 30+30 3.75 6x018 35+35 3.21 6x026 40+40 2.81 6x025 45+45 2.50 6x033 50+50 2.25 6x028 110 2.04 6x029 220 1.02 6x030 240 0.93	8x016 25+25 10.00 8x017 30+30 8.33 8x018 35+35 7.14 8x025 40+40 6.25 8x025 45+45 5.55 8x033 50+50 5.00 8x042 55+55 4.54 8x028 110 4.54 8x029 220 2.27 8x030 240 2.08
(encased in ABS plastic)	80 VA 90 x 30mm Regulation 12%	160 VA 110 x 40mm Regulation 8%	300 VA 110 x 50mm Regulation 6%	625 VA 140 x 75mm Regulation 4%
70 x 30mm Regulation 18%	3x010 6+6 6.64 3x011 9+9 4.44 3x012 12+12 3.33 3x013 15+15 2.66 3x014 18+18 2.22 3x015 22+22 1.81 3x016 25+25 1.60 3x017 30+30 1.33 3x028 110 0.72 3x029 220 0.36 3x030 240 0.33	5x011 9+9 8.89 5x012 12+12 6.66 5x013 15+15 5.33 5x014 18+18 4.44 5x015 22+22 3.63 5x016 25+25 3.20 5x017 30+30 2.66 5x018 35+35 2.28 5x026 40+40 2.00 5x028 110 1.45 5x029 220 0.72 5x030 240 0.66	7x013 15+15 10.00 7x014 18+18 8.33 7x015 22+22 6.82 7x016 25+25 6.00 7x017 30+30 5.00 7x018 35+35 4.28 7x026 40+40 3.75 7x025 45+45 3.33 7x033 50+50 3.00 7x028 110 2.72 7x029 220 1.36 7x030 240 1.25	9x017 30+30 10.41 9x018 35+35 8.92 9x026 40+40 7.81 9x025 45+45 6.94 9x033 50+50 6.25 9x042 55+55 5.68 9x028 110 5.68 9x029 220 2.84 9x030 240 2.60

Why a Toroid?

- * Smaller size & weight to meet modern 'slimline' requirements.
- * Low electrically induced noise demanded by compact equipment.
- * High efficiency enabling conservative rating whilst maintaining size advantages.
- * Lower operating temperature.

Why ILP?

- * Ex-stock delivery for small quantities.
- * Gold service available. 21 days manufacture for urgent deliveries.
- * 5 year no quibble guarantee.
- * Realistic delivery for volume orders.
- * No price penalty for call off orders.

Prices including P&P and VAT

VA	Size	£	VA	Size	£
15	0	7.43	160	5	12.90
30	1	8.08	225	6	16.30
50	2	10.10	200	7	18.55
80	3	10.81	500	8	25.73
120	4	11.73	625	9	31.63

Mail Order - Please make your crossed cheques or postal orders payable to ILP Electronics Ltd.

Trade - We will open your credit account immediately upon receipt of your first order.

Post to: ILP Electronics Ltd., Dept. 5
Graham Bell House, Roper Close,
Canterbury, Kent. CT2 7EP
Tel: (0227) 54778 Telex: 965780

For 110V primary insert "0" in place of "X" in type number.
For 220V primary (Europe) insert "1" in place of "X" in type number.
For 240V primary (UK) insert "2" in place of "X" in type number.
IMPORTANT: Regulation - All voltages quoted are FULL LOAD.
Please add regulation figure to secondary volt to obtain off load voltage.



ILP ELECTRONICS LTD.

W/P Walmax Processing Ltd

Unit 8, Gateway Trading Estate
Hythe Road, London NW10 6RJ
Telephone: 01-960 8322 Telex: 8952644

ELECTRONIC COMPONENTS FOR SALE

FANS - Woods, Plannair & Muffin all at £2.99 each
MOTORS - £4.99 each

Also Capacitors, Diodes, Resistors, Heat Sinks, Ribbon Wire, Keyboards, Circuit Boards etc. At lowest prices.

Please telephone for further details.

Please mention **HE** when replying to advertisers



7 HUGHENDEN ROAD, HASTINGS, SUSSEX. TN34 3TG
Telephone: HASTINGS (0424) 436004

ELECTRONIC KITS

Post & Packing 50p for KS kits, 75p for UK kits, £1.00 for Cabinets. Send 20p S.A.E. for catalogue of our extensive range of kits & Cabinets. Trade, Educational & Export enquiries welcome.

<p>KS 100</p> <p>MINI VHF SUPER-REGENERATIVE RECEIVER 88-108 MHZ 9V D.C. £ 5.27 inc V.A.T.</p>	<p>KS 238</p> <p>3 CHANNEL MICROPHONE OPERATED SOUND TO LIGHT, 300W PER CHANNEL, 240V A.C. £ 11.58 inc V.A.T.</p>	<p>KS 240</p> <p>3 CHANNEL SOUND TO LIGHT, OUTPUT 3 x 1 KW 240V £ 13.70 inc V.A.T.</p>
<p>UK 823/W</p> <p>CAR BURGLAR ALARM. READY ASSEMBLED £ 13.58 inc V.A.T.</p>	<p>UK 875</p> <p>Capacitive Discharge Electronic Ignition £ 17.50 inc V.A.T.</p>	<p>UK 677/A</p> <p>REGULATED SUPPLY 0-20 V, 2.5 A £ 54.23 inc V.A.T.</p>
<p>UK 666</p> <p>0-30V, 2.5A REGULATED SUPPLY WITH DIGITAL DISPLAY £ 76.82 inc V.A.T.</p>	<p>KS 420</p> <p>DIGITAL D.C. VOLT-METER, 999 MV - 999 V, 0.5 V D.C. £ 14.45 inc V.A.T.</p>	<p>UK 558</p> <p>600 MHz PRESCALER + 5 V D.C. £ 19.95 inc V.A.T.</p>
<p>KS 395</p> <p>30 W HI-FI-Audio Amplifier £ 11.58 inc V.A.T.</p>	<p>KS 490</p> <p>NICAD BATTERY CHARGER, 10-20-45-100-150 mA, 15V D.C. MAX 240V A.C. £ 8.42 inc V.A.T.</p>	<p>UK 114/U</p> <p>20 W IC Amplifier £ 8.42 inc V.A.T.</p>

Getting The Hobbit Habit

Helen Armstrong

A twelvemonth hath passed, and at least some devoted fans of J. R. R. Tolkien are still stuck in the Goblin's Dungeon. How do you rate their chances?

Just over a year and a day ago there appeared in the land a long-awaited adventure game for the Spectrum microcomputer. It was (an awe fell upon me, as the sages would say) based on Prof. J. R. R. Tolkien's fantasy classic *The Hobbit*. Not only "based on" was it, but sanctioned by the official keepers and guardians of *The Hobbit* since the Professor's death ten years ago. The arrival of the new game was hailed as a major advance in the art of computer adventure games, and being an old and proud member of The Tolkien Society, I decided to find out what the fuss was about. With *The Hobbit* now (or imminantly) available for the BBC Micro, Oric and Commodore 64, this seems like a good time to report back. Also, we hear rumours that *The Hobbit's* computer creators, Melbourne House, are starting work on the story's giant sequel, *The Lord Of The Rings* — in multiple parts.

Reactions to *The Hobbit* among my acquaintances depended on their previous experience with computer adventure games. Those who (like me) were used to shooting alien invaders and thinking afterwards were astonished by the sheer patience and calculation needed to make any progress, while underestimating the ingenuity of the program we were communicating with.

Riddles In The Computer

For the uninitiated, an adventure game involves picking your way through a strange landscape in search of treasure, while solving a series of riddles or clues in order to survive. The locations in the landscape are described in text. The player is given a choice of possible routes (usually north, south, east, west, up and down) and, apart from selecting a route, can also give simple commands to the computer to manipulate objects described. For instance, encountering a door, the player could tell the computer to OPEN DOOR. If this doesn't work, which it usually doesn't (that would be too easy) options like UNLOCK DOOR, or



FIND KEY or STRIKE DOOR can be tried. These, normally, are also too easy. The solution might be something like going S (south), to a location where you meet a barbarian warrior, finding a way to KILL WARRIOR who will be carrying a key; you then TAKE KEY, return N and UNLOCK DOOR. This is a simple sequence. You might have to find a sword, first, to kill the warrior and defend yourself from whatever lurks beyond the door. And so on.

The player can also ask the computer for HELP, in which case a cryptic clue might appear. Or might not. It makes the game easier. But not much.

Adventure games require patience.

When *The Hobbit* came out, it was said to be revolutionary, for three reasons: firstly, thirty of the eighty or so locations are displayed in colour-graphic form; secondly, the commands accepted by the games are much closer to real English than usual. Strings of commands can be accepted as long as they are grammatical, and characters in the game can be asked to act for the players. Lastly, the

characters in the game act independently of the player, moving around by themselves and appearing in unexpected places.

Vive La Difference

As a non-initiate into this kind of game, I didn't appreciate what a difference these things make until I had investigated one or two other adventure programs. Whether the difference is a pro or a con depends on your preference. If you don't like unpredictable adventures, don't play *The Hobbit*.

Melbourne House are very proud of the vivid colour graphics used, for which the 48K Spectrum is well suited. These cover the top two thirds of the screen, and were programmed to use much less than two-thirds of a full screen's worth of memory. They appear sketched quickly in line and then filling line by line with colour — a process which, although it does slow the game down, never quite loses its charm, even when



It is apparently advisable to be armed with lunch before facing the perils of the misty mountains. But make sure you eat some, as well.

you have been returned to the Goblin's Dungeon for the fourteenth time in succession.

The language which Melbourne House have developed for the game they call "Inglish" — it looks like English, but isn't, quite, English. One of the ongoing riddles in the game is to find out which words in English are acceptable in Inglish (and when). An unfamiliar word is greeted with the response I DO NOT UNDERSTAND SMITE (for instance). The instruction booklet gives a reasonable guide, but I found that some words listed were not

The Title Graphics, based on the game's cover picture (opposite page).



recognized in some situations.

Others are acceptable in unlikely situations: Chris, a fellow Member of The Society, requested his computer, in a moment of frustration, to KILL LUNCH. His next inventory revealed SOME BROKEN LUNCH — at least it wasn't A DEAD LUNCH, but that would have been no surprise.


The most remarkable feature of the commands is that you can request other characters in the program to act on your

behalf with the command SAY TO (x) "(command)". This process is a vital part of the game. You are, as the manual tells you, only a small Hobbit, and need the aid of a taller, stronger and more powerful character to accomplish your ends. In keeping with the game, the response of other characters is variable. Thus the request SAY TO THORIN "KILL THE GOBLIN" may lead to Thorin attacking the Goblin and killing it, attacking it and being captured, saying "No" and being captured or killed, or merely disregarding you (YOU SPEAK TO THORIN comments the computer), and being captured or killed. Sometimes it is better to ignore the goblins . . .

Try, Try, Try Again

The third feature is the most fascinating/irritating. As with the Inglish, we found we were trying moves just to see what would happen. Many of the characters have the ability to move and pop up randomly around the program. Thus, you may arrive in Rivendell to find

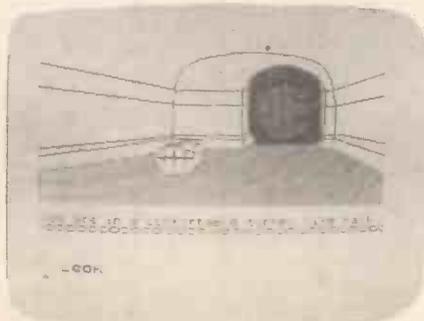
The Hobbit's hallway: probably the most familiar scenario to inexperienced players!



that Elrond has just been killed by a Warg, or meet Gollum unexpectedly at the bottom of the Deep Valley. My spies report that Gandalf has been known to kill Thorin, take Sting and refuse to return it, remove other vital objects and disappear into the program, never to return, or reappear after having earlier been killed. In one reported instance, he picked up the Green Door from Bag End and carried it throughout the game. (SAY TO GANDALF "HIT GOBLIN WITH GREEN DOOR"???) The more bizarre the incident, the less likely it is to occur, but they happen often enough to add interest to/foul up your progress, depending what your attitude is.

Melbourne House includes a note in the instruction manual: "Due to the immense size and complexity of this game it is impossible to guarantee that it will even be completely error free . . . If however any problems are found we would like to know about them so that future versions may be corrected." This

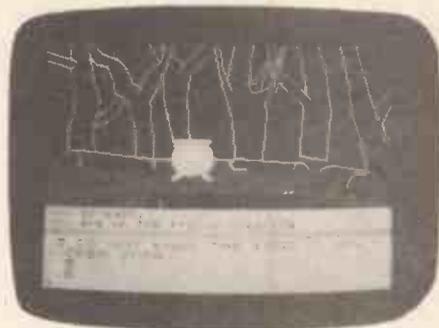The Troll's Clearing appears in red and white for night-time, and blue and white black for daylight.



disclaimer is a bit like the labels in Indian cottons which say that "Variations in the weave and colour are part of the natural beauty of this garment" and musicians who say that bum notes are all part of the spontenaity. As I like Indian cotton and spontenaity (within reason) I normally enjoy the quirks of the program. However, after encountering the DARK in broad daylight as I struggled with another recalcitrant clue, I began to wonder whether I could stand that much natural beauty. As I said, adventures require heroic qualities, like not hurling your Spectrum at the telly.

Wait Or Pause?

Leaving this aside, for those who do not have the facilities to SAVE the game at problems points, it is possible to build up a reliable map and use it to work forward to the stick-point. Once there, put it on PAUSE, quickly; the game goes on playing itself otherwise, and the longer you wait, the more likely something unpleasant is to appear or happen. On the other hand, in some places, waiting is a necessary part of the game process.

The manual gives a number of hints on how to conduct the game. You are told to protect Thorin, as progress is

The sudden appearance of the Troll's footprints on the Troll's Path is the nearest thing to animation in The Hobbit's graphics.



impossible without him (and he will fight enemies who are bigger than you, a mere Hobbit). Choosing the right adverb (QUICKLY or CAREFULLY) with your instructions may be crucial. This sounds fascinating, and it does add interest, but as far as we can work out these factors usually only come into play once or twice during the game. Eventually Thorin became such a pest, purloining objects, running off on wild goose chases, refusing to fight and saying HURRY UP at regular intervals, that we killed him just to shut him up (and were immediately killed by two goblins. Whose side is Thorin on, anyway?). There is one point where Thorin appears to be essential, but one acquaintance regularly disposes of him after this point.

If a disaster such as A DEAD ELROND occurs, at random, there seems to be no way of recouping the loss: for instance, once the DARK appears (normally underground) there seems to be no way of extricating yourself. At least, I have yet to meet anyone who has done so. The logic of the English, often a bit strained, breaks down, so that if THORIN ENTERS and you SAY TO THORIN "FIND LIGHT", the computer merely replies I SEE NO THORIN HERE. IT IS DARK. It dawns that you are not so much pitting your wits against the computer, as trying to catch it in the right mood.

While I applauded the idea of making the computer respond directly to English commands (and it is very time-saving to be able to UNLOCK, OPEN, GO THROUGH DOOR), I found that I quickly started looking for ways to key in

The commands to enter the Troll's Cave can be given in one sequence, instead of three as shown here.




commands as briefly as possible. For instance, SAY TO ELROND, "GIVE ME SOME LUNCH PLEASE" (the manual says you must must be polite) resolved itself into SAY ELR "LUNCH". Elrond didn't seem offended.

By The Book?

At the suggestion of Prof. Tolkien's executors, *The Hobbit* is being sold only with a copy of the novel attached. The idea is that the book will offer clues. This depends on how well you know the book. I found it useless, in fact very misleading. For instance, in the novel, Bilbo and Gollum have a long riddle contest, from which Bilbo escapes, by

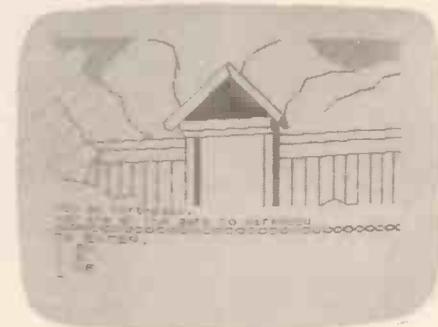In the vicinity of Mirkwood, the Wood Elf appears; travellers report that your chances are better if you are captured.



stragem, without harming Gollum, after obtaining the Ring. In the game, any attempt to converse with Gollum leads to instant strangulation, and the only solution is to take the ring, kill Gollum and run for it.


A number of solutions depend either on keeping someone alive till they have served their purpose, or killing them promptly. It sounds more like Conan than *The Hobbit*, and doesn't actually improve the quality of the game, either.

On the other hand, anyone who does not know the story will find it helpful to know that the Dragon lies to the East, that Elrond and Thorin are goodies and that Goblins are baddies, that Bard the Bowman can shoot dragons and that Sting can be found in a trolls' hoard. Looked at like that, the book is very helpful indeed.

One of our Members has succeeded in getting into the Lonely Mountain, disposing of the Dragon and returning with the treasure to Bag End. He scored 86.5%, so there are still riddles to unravel. He has found no use for the Small Golden Key. Some riddles seem to have no solution, and others, once solved, seem to give no further help in the game.

In their latest bout of publicity, Melbourne House point out that, as *The Hobbit* is so complex, people will discuss it. How right they are: I would say it's better as a conversation piece than it is as a game, because one player's experience is not the same as another's — which was always one of the attractions of Prof. Tolkien's writings. Playing the game is like working out a series of riddles where the rules

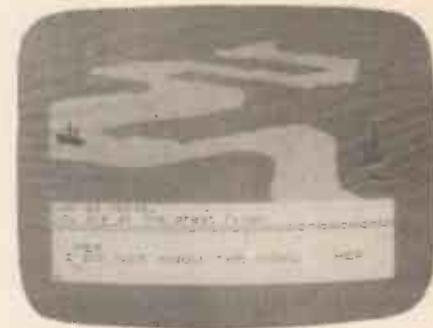An attack of nerves stymies the traveller at the Great River.



occasionally change without warning. The random element makes the adventure something more than a challenge to make a successful map.

The Melbourne House team have expended a great deal of love and care on *The Hobbit*, employing eighteen months and a number of specialists (an artist, a linguistics expert, etc.) to write it, packing as much into 48K of memory as possible. (The recently arrived version for the BBC Micro has, alas, no graphics, as the BBC has only 32K memory). It is going to seem a trifle unsatisfying to anyone who has played an adventure game on a mainframe with hundreds of Ks of memory, but for anyone who plays on micros, *The Hobbit* is unusually complicated.

It's a pioneering work in translating a story into a computer game, as well, and succeeds in capturing some of the flavour of the original. The long gestation period (and the combined sale with the book, no doubt) have bumped the price up to £14.95, but in terms of hours occupied it seems worthwhile.

Indeed, I was eventually driven forth from the Misty Mountains simply because I had no time left to go on searching — such are the demands of a non-hero's life. So I shall leave it to someone else to discover what happens if you THROW ROPE CAREFULLY ACROSS RIVER.

Sadly, the version for the BBC Micro has no colour graphics, owing to lack of memory space.



PERMACON



Proved over many years in commercial use, now available to the hobbyist at competitive prices.

STANDARD CONNECTORS
TWO PITCHES .1 AND .15
FOUR CONTACT STYLES

Further details from:
COLNBROOK ELECTRONICS LTD
Crabbs Abbey, Stowbridge
Kings Lynn, West Norfolk
PE34 3PE

PARNDON ELECTRONICS LTD.

Dept. 22, 44 Paddock Mead, Harlow, Essex. CM18 7RR. Tel: 0279 32700

RESISTORS: ¼ Watt Carbon Film E24 range ± 5% tolerance
Bandolered and colour coded. Full Range 1R0-10M.
£1.00 per hundred mixed (Min 10 per value) **£8.50** per thousand mixed (Min 50 per value)
Special stock pack 60 values. 10 of each **£5.50**

RECTIFIERS 1 Amp 3 Amp 50V 3p 14p 100V 4p 14p 200V 5p 14p 400V 6p 19p 600V 8p 20p 1000V 9p 25p	3½ Digit LCD Display: 1 colon, 3 decimal points plus/minus sign and lo bat indicator. Complete with low power 7106 A/D converter display driver. Driver set £8.95 Display £3.50 Driver £6.50
DIODES: IN4148 £1.60 per hundred	

DIL SOCKETS 8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

Full List Available — Send SAE
ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS
MIN ORDER — UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE
Same Day Despatch

OVERCHARGED FOR YOUR BATTERIES?

RECHARGEABLE BATTERIES AND CHARGERS

For Use in Your

Personal Stereo Metal Detector
Transistor Test Equipment
Torches Car Kits
Cassette Recorders Electronic Projects

SANDWELL PLANT LTD
656 Chester Road, Erdington, Birmingham
Tel: 021-373 9487 After hours Lichfield 57977
Also at Hitchin, Telephone: Hitchin 733254
Private enquiries welcome. Send SAE for details

It's easy to complain about advertisements. But which ones?

Every week millions of advertisements appear in print, on posters or in the cinema. Most of them comply with the rules contained in the British Code of Advertising Practice.

But some of them break the rules and warrant your complaints. If you're not sure about which ones they are, however, drop us a line and we'll send you an abridged copy of the Advertising Code.

Then, if an advertisement bothers you, you'll be justified in bothering us. **The Advertising Standards Authority.** If an advertisement is wrong, we're here to put it right.

ASA Ltd, Dept 2 Brook House, Torrington Place, London WC1E 7HN

This space is donated in the interests of high standards of advertising.

HORIZON ELECTRONICS

(Midlands)
Charlotte St. Rugby Tel: 78138
Prime quality. TERRIFIC PRICES. Mail order only

REGULATORS (5/12/15m) 100ma 25p 1 amp +ve 25p 723 variable 25p	ZENERS (0.7 to 30m) 500mv 6c 1 watt 12p	CAPACITORS Radial 83m 1 mgd 7p 2.2 mgd 7p 4.7 mgd 8p 10 mgd 10p 22 mgd 12p 47 mgd 13p 100 mgd 15p 220 mgd 19p	ANAL 83m 1 mgd 7p 2.2 mgd 7p 4.7 mgd 8p 10 mgd 10p 22 mgd 12p 47 mgd 13p 100 mgd 15p 220 mgd 19p	LINEAR I.C.s CA 3240 95p DAC0800 235p ICL 7811 98p ICL 7821 180p ICM 7558 70p ICM 7558 130p LF 347 158p LF 351 45p LF 353 70p LM 301 75p LM 330 46p LM 348 60p LM 380 68p	LM 709 44p LM 747 60p LM 748 35p LM 1458 43p LM 3000 19p LM 3008 48p LM 3814 199p LM 3815 215p NE 531 133p NE 567 155p SN 78013N 271p SN 78023N 272p ZN 414 45p ZN 425 346p
DIODES 1N 4001 3p 1N 4002 () 4p 1N 4004 6p 1N 4008 8p 1N 5401 12p 1N 5403 13p 1N 5406 14p	BRIDGE RECTIFIERS 1 amp 80v 20p 2 amp 100v 30p 2 amp 400v 30p 6 amp 100v 48p 6 amp 400v 75p 10 amp 80v 17p 10 amp 200v 195p	TRANSISTORS BC 107 9c BC 108 9c BC 109 10p BC 140 25p BC 145 25p BC 180 35p BC 182 7p BC 212 7p BC 237 6p BC 300 52p BC 301 25p BC 302 39p BC 303 25p BC 304 39p BC 305 39p BC 307 25p BC 308 39p BC 309 39p BC 310 39p BC 999 39p BC 1000 39p	TOGGLE SWITCHES Standard 2 amp - SP ST 36p DP DT 48p Miniature 2 amp - SP ST 80p DP DT 100p Sub Min. 2 amp - SP ST 48p DP DT 82p		

ADD: 65p post/packing to all orders under £15

VAT: add 15% VAT to total order value (inc p&p)

*** Comprehensive Catalogue Available : 85p ***


Bimconsoles! — METAL Brown base Beige top	BIMBOARDS Prototype with plug-in breadboards Component support brackets supplied with all except Eurobreadboard.		
Part No	A B C D E	Type	No of Con. Points
BIM 2601	178 51 210 38.5 70	Eurobreadboard	500 6.25
BIM 2602	280 51 210 38.5 70	Eurobreadboard PCB	500 0.75
BIM 2603	381 51 210 38.5 70	Bimboard 1	550 6.55
BIM 2604	483 51 210 38.5 70	Bimboard Strip	80 2.50
BIM 2605	480 51 261 38.5 70	Bimboard PCB	630 1.44
BIM 2701	178 76 210 38.5 70	Bimboard Layout Pad	1422 0.46
BIM 2702	280 102 210 38.5 70	MPU Eurobreadboard	1422 17.25
BIM 2703	381 102 210 38.5 70	Bimboard Designer	77.00
BIM 2704	483 102 210 38.5 70		

Bimconsoles! — ABS Black or Grey base with Grey Aluminium top.	PLAN
BIM 6005	105 555 143 31.5 37.5 2.25
BIM 6006	170 555 143 31.5 37.5 2.80
BIM 6007	170 81.8 21.8 31.5 57.8 3.85


All prices inc VAT. Add 60p per order on Bimboards. £2.50 per order on Bimconsoles for p&p. SAE for full list. Mail Order only.

BIMSALES
Dept HE3, 48a Station Road, Cheadle Hulme, Cheadle, Cheshire, SK8 7AB. Tel: 061 485 6667.


PCB FOIL PATTERNS

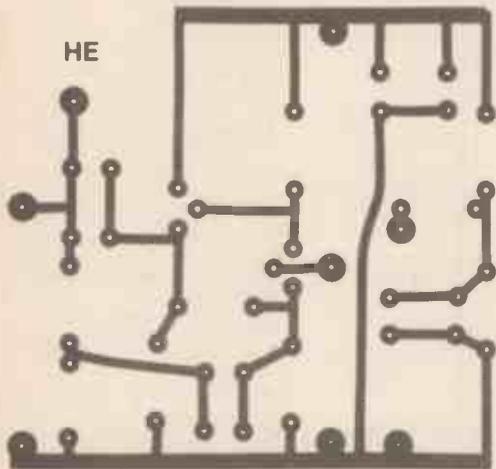

The PCB mask for the Sine Wave Generator

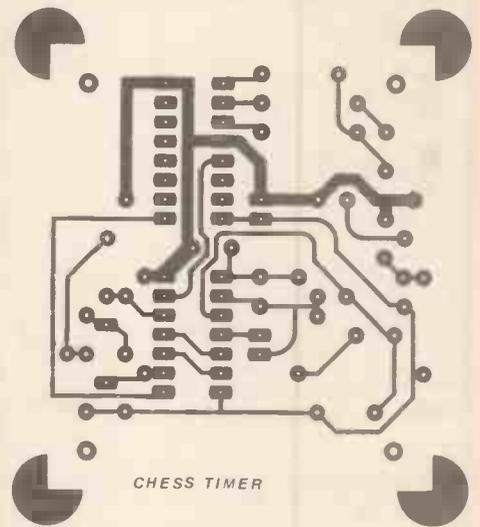

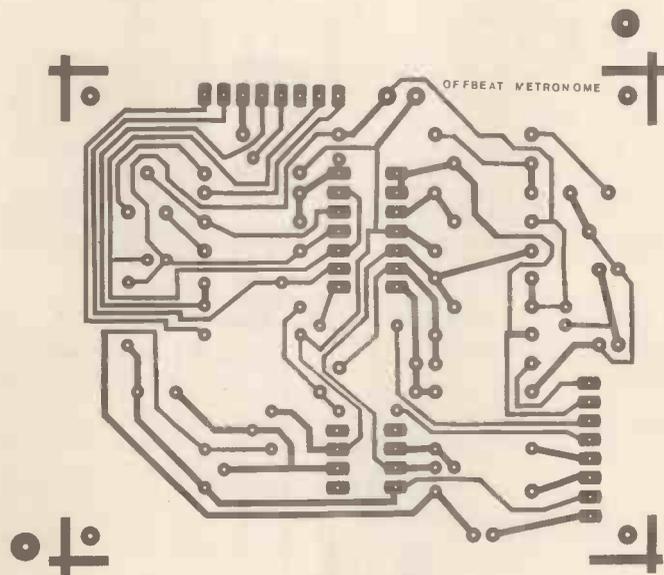The PCB mask for the Lighting Chess Timer.



The PCB foil for the Offbeat Metronome.

Lineage:

30p per word (minimum 15 words)
Semi-display £7.50 per single column centimetre
Ring for information on series bookings/discounts



01-437 0699

All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)

Send your requirements to:
Debbie Miller
ASP Ltd.,
1 Golden Square,
London W1R 3AB

ALARMS

TIMED ENTRY EXIT CONTROL ALARM PANEL

MAINS-BATT.
MODEL 9000E
-ONLY-

2 ZONE - £33-89

£29-50 INC.

- FULL 2 YEAR GUARANTEE
- Adjustable entry-exit with buzzer.
- Regulated power supply (1-2 amp).
- Latching 24 hour circuit.
- Visual & audible walk test.

PLEASE SEND FOR FREE CATALOGUE OF ALARM EQUIPMENT FROM SIMPSONS ELECTRONIC ALARMS 70 PRIORITY ROAD LIVERPOOL L4 2RZ. TRADE SUPPLIED

051-260-0300

LARGEST STOCK OF BURGLAR ALARM EQUIPMENT: As used in the trade. JN Security Centre, 176 Sydenham Rd., London SE26 5JZ. 01-778 1111. Showrooms open 6 days.

BURGLAR ALARM equipment. Ring Bradford (0274) 731532 for our catalogue, or call at our large showrooms opposite Odsal Stadium.

TO FILL
THIS SPACE
PHONE
01-637 0699

A1 INTRUDER ALARMS
Wholesale Alarm Suppliers
Latest D.I.Y. &
Wholesale Published Catalogue
Write off for your copy
86 Derby Lane, Old Swan,
Liverpool 13
Tel: 051-288 3483
or 051-220 0590

PLANS 'N DESIGN

AMAZING electronic plans, lasers, gas, ruby, light shows, high voltage teslas, van de graph, surveillance devices, ultrasonics, pyrotechnics, new solar generator, 150 more projects, catalogue S.A.E., Plan-centre, Bromyard Road Industrial Estate, Ledbury HR8

BOOKS & PUBLICATIONS

PARAPHYSICS JOURNAL (Russian translations). Psychotronics, Kirlianography, heliphonic music tekinetics. Computer software. SAE 4 x 9":— Paralab, Downton Wilts.

PRODUCTS TO
SELL?
USE
HOBBY
CLASSIFIED

COMPONENTS

BUMPER BOX OF BITS
WOW! We've got so many components in stock, we can't possibly list them all! — So buy a box, in it you'll find resistors, capacitors, displays, switches, panels with transistors, diodes, ICs, etc., coils, pots... and so on. All modern parts — guaranteed at least 1000 items. Minimum weight 10lbs. ONLY £8.50 inc. 48 page catalogue 50p.
ELECTRONICS WORLD
1F Dews Road, Salisbury
Wilts SP2 7SN

FREE! Parcel of L.E.D.'s, switches, components worth £10. Send only 80p postage. Horsley, 113 Clare Rd, Braintree, Essex.

COMPONENTS, hobby kits, etc. SAE for free list. PIP Marketing, Two Bridges, Blakeney, Glos.

COMPUTERS

CONTROL
Plug-ins for the DRAGON 32
RELAY OUTPUT UNIT
FITTED 2 RELAYS — £16.75
Space for 6 more
FAST A-D CONVERTER WITH
APPLICATION SOFTWARE
£29.50
Other units available. Please send A4 S.A.S.E. for the full details.
P.N.P. COMMUNICATIONS
(Dept. H.E.)
62 Lawes Avenue, Newhaven
East Sussex BN9 9SB
Tel: 0273 514465

EQUIPMENT

AERIAL AMPLIFIERS Improve weak television reception. Price £6.70. S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire BLO 9AGH.

RESISTOR PACKS FOR ALL PROJECTS

¼ watt carbon film resistors 5% 1 ohm to 10M E24 series. Packs of 10 each value (1690 resistors £10.00. Your choice of qualities/values 25 for £1.00. VAT and Post Free.
GORDON HALLET
20 Bull Lane, Malden, Newton
Dorchester, Dorset DT2 0BQ

BRITISH TELECOM plug sockets and leads, etc. Tel: C.W.A.S (0274) 308920. Or visit our showroom opposite Odsal Stadium, Bradford.

USE THIS SPACE
TO ADVERTISE
YOUR
HOBBY SHOP

HOBBY SHOP

LANCASHIRE

E.E. ETESON ELECTRONICS
158 Lower Green
Poulton-le-Fylde Blackpool
Tel: (0253) 885107
Open 9:30 am—12:30, 1:30—5:30
Closed Wed. & Sun.
Electronic Component Specialists

RADIO SERVICES

VINTAGE WIRELESS COMPANY 1914-1960
Radios, amplifiers, service sheets, valves, vintage components. Books new and used.
Repairs and Restorations.
Mail Order only.
Tudor House, Casoham St.,
Mangotsfield BS17 3EN
Tel: 565472

FOR SALE

100W AMPLIFIER — £9.95 built or use the same board for 50W, 150W, 200W into 4 or 8 ohms etc., by using alternative output transistors and PSU. SAE for full details to — ESS Amplification, Innovation House, Guildhall Road, Hull.

KIA Return An Ad No. 13... New variable automatic protection power supplies... 12-40V/5A/STAB... Return No. 13 + £5.25 — KIA-8, LS-29 9DZ... 1984 Sale Time, 1000 Amplifiers — giveaway prices!!

CABLE TRACKER (HE May 82). Calibrated c/w battery — £15.00. B Cowton, 24 Guisborough Street, Sunderland SR4 7SD.

KITS

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq.ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

Advertising Pays!
TO PLACE AN AD —
PHONE DEBBIE 01-437 0699

HOBBY ELECTRONICS

CLASSIFIED ADVERTISEMENT — ORDER FORM

If you have something to sell now's your chance! Don't turn the page — turn to us!
Rates of charge: 30p per word per issue (minimum of 15 words).
 and post to **HOBBY ELECTRONICS, CLASSIFIED DEPT., 145 CHARING CROSS ROAD, LONDON WC2**

Please place my advert in **HOBBY ELECTRONICS** for issues commencing as soon as possible.
 I am enclosing my Cheque/Postal Order/International Money Order for: (delete as necessary) £ (Made payable to A.S.P. Ltd)
 Please use **BLOCK CAPITALS** and include post codes.
Classification
Name (Mr/Mrs/Miss/Ms) (delete accordingly)
Address
 OR Debit my Access/Barclaycard (Delete as necessary)
 
 Signature Date
 Daytime Tel. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

All classified advertisements must be paid for in advance.

FREE CAREER BOOKLET

Train for success, for a better job, better pay
 Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.
 Learn in your own home, in your own time, at your own pace, Through ICS home study, used by over 8 million already! Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.
 Send for your **FREE CAREER BOOKLET** today —no cost or obligation at all.

C & G BASIC ELECTRONICS <input type="checkbox"/>	ELECTRONIC ENGINEERING <input type="checkbox"/>
C & G RADIO AMATEUR'S Exam <input type="checkbox"/>	COMPUTER PROGRAMMING <input type="checkbox"/>
RADIO & AUDIO ENGINEERING <input type="checkbox"/>	TV & AUDIO SERVICING <input type="checkbox"/>
RUNNING YOUR OWN BUSINESS <input type="checkbox"/>	ELECTRICAL INSTALLATIONS/CONTRACTING <input type="checkbox"/>
AUTO MECHANICS <input type="checkbox"/>	C & G BASIC MECHANICAL ENGINEERING <input type="checkbox"/>

Name _____
 Address _____
 P.Code _____



Dept EA134
 ICS School of Electronics
 160 Stewarts Road
 London SW8 4UJ



01-622 9911
 (all hours)



H.E. Advertisers Index



Abmit International	IFC
Amtron (UK)	58
Audio Electronics	19
Bicc Vero	57
Bimsales	62
Bi-pak	10
B.K. Electronics	IBC
B.N.R. & E.S.	40
Brian J. Reed	48
J. Bull	4
Colnbrook Electronics	62
Dataplus Development	48
Electronize Design	OBC
Enfield Electronics	30
Horizon Electronics	62
ICS	66
ILP	58
Kelan Engineering	26
Litesold	19
Magenta Electronics	47
Parndon Electronics	62
Riscomp	48
Sandwell Plant	62
Sparkrite	5
Tomorrows World	26
Walmax Processing	58



MULLARD SPEAKER KITS

Purposely designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer (8" or 5") with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter. B.K.E. built and tested crossover based on Mullard circuit, combining low loss components, glass fibre board and recessed loudspeaker terminals. SUPERB SOUNDS AT LOW COST. Kits supplied in polystyrene packs complete with instructions. 8" 40W system — recommended cabinet size 240 x 216 x 445mm
Price £14.90 each + £2.00 P & P.
5" 30W system — recommended cabinet size 160 x 175 x 295mm
Price £13.90 each + £1.50 P & P.

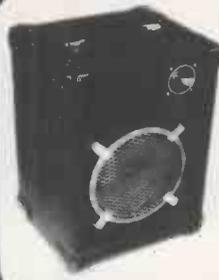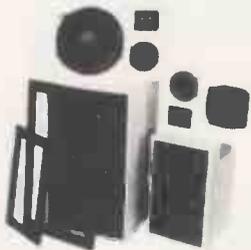Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self adhesive vinyl etc.
8" system cabinet kit £8.00 each + £2.50 P & P.
5" system cabinet kit £7.00 each + £2.00 P & P.



OMP 80 LOUDSPEAKER

The very best in quality and value.
Ported tuned cabinet in hard-wearing black vinylite with protective corners and carry handle. Built and tested, employing 10in British driver and Piezo tweeter. Spec: 80 watts RMS; 8 ohms; 45Hz-20KHz; Size: 20in x 15in x 12in; Weight: 30 pounds.

Price: £49.00 each
£90 per pair
Carriage: £5 each £7 per pair

BK ELECTRONICS


Prompt Deliveries
VAT inclusive
prices
Audio Equipment
Test Equipment
by
Thandar
and
Leader

STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Autostop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Input Sensitivity: 100mV to 2V. Input Impedance: 68K. Output level: 400mV to both left and right hand channels. Output Impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V DC at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2" x 11 1/2". Clearance required under top panel 2 1/2". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

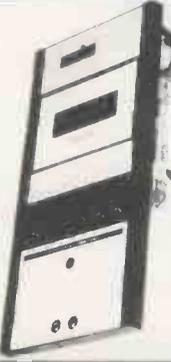Price £26.70 + £2.50 postage and packing.
Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.



PANTEC

HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt)
Price: £7.99p

DIGITAL THERMOMETER -9.9 C to +99.9 C. LED display. Complete with sensor. 70 x 70 mm (9 volt) Price: £27.60p

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled, professional performance. Range up to 3 miles 35 x 84 x 12 mm (12 volt) Price: £12.49p

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22 mm (9/12 volt) Price: £16.49 Transmitter 80 x 50 x 15 mm (9/12 volt) Price: £10.29 P&P All Kits + 75p each. S.A.E. for complete list.



3 watt FM Transmitter

BSR P256 TURNTABLE

P256 turntable chassis • S shaped tone arm • Belt driven • Aluminium platter • Precision calibrated counter balance • Anti skate (bias device) • Damped cueing lever • 240 volt AC operation (Hz) • Cut-out template supplied • Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price £32.35 each. £2.50 P&P



LOUDSPEAKERS POWER RANGE

THREE QUALITY POWER LOUDSPEAKERS (15", 12" and 8" See Photo) Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons. Specification and Prices.

15" 100 watt R.M.S. Impedance 8 ohms. 50oz magnet. 2" aluminium voice coil. Res. Freq. 20 Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. Price: £34.00 each + £3.00 P&P
12" 100 watt R.M.S. Impedance 8 ohms. 50oz magnet. 2" aluminium voice coil. Res. Freq. 25Hz. Freq. Resp. to 4 KHz. Sens. 95dB. Price: £26.00 each + £3.00 P&P
8" 50 watt R.M.S. Impedance 8 ohms. 20 oz magnet. 1 1/2" aluminium voice coil. Res. Freq. 40Hz. Freq. Resp. to 6 KHz. Sens. 92dB. Black Cone. Price: £9.50 each. Also available with black protective grille. Price: £9.99 each P&P £1.50.




12" 85 watt R.M.S. MCKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz. Sens. 98dB. Price £24.00 + £3 carriage.

12" 85 watt R.M.S. MCKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone. 8ohm. imp., Res. Freq. 45Hz. Freq. Resp. to 14KHz. Price £24.00 + £3 carriage.

15" 150 watt R.M.S. MCKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis, 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price £49 + £4 carriage. Cabinets fixings in stock S.A.E.

OMP POWER AMPLIFIER MODULE READY BUILT

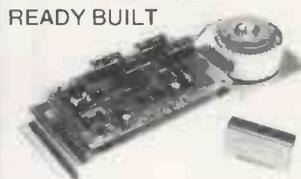

New model.
Improved specification

MOSFET versions available up to 300W. R.M.S.

NEW OMP100 Mk.II POWER AMPLIFIER MODULE Power Amplifier Module complete with integral heat sink, toroidal transformer power supply and glass fibre p.c.b. assembly. Incorporates drive circuit to power a compatible LED Vu meter. New improved specification makes this amplifier ideal for P.A., Instrumental and Hi-Fi applications.
SPECIFICATION
Output Power:— 110 watts R.M.S.
Loads:— Open and short circuit proof 4/16 ohms.
Frequency Response:— 15Hz - 30KHz -3dB.
T.H.D.:— 0.01%
S.N.R. (Unweighted):— -118dB ±3.5dB
Sensitivity for Max Output:— 500mV @ 10K.
Size:— 360 x 115 x 72 mm Price:— £31.99 + £2.50 P&P Vu Meter Price:— £8.50 + 50p P&P.

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.

TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.29 each.


TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £5.99 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £7.99 each.

TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £4.99 each.

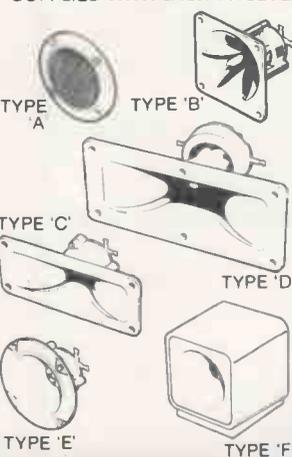TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each
P&P 30p ea. (or SAE for Piezo leaflets).



HOME PROTECTION SYSTEM

Better to be 'Alarmed' than terrified.
Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. FULLY GUARANTEED.

Control Unit — Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch — off — test — armed. 30 second exit and entry delay.

Indoor alarm — Electronic swept freq. siren. 104dB output.

Outdoor Alarm — Electronic swept freq. siren. 98dB Output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions

SAVE £128 Usual price £228.85

BKE'S PRICE £99.00p&p£4

S.A.E. for colour brochure

READY BUILT



STEREO DISCO MIXER

Ready built

STEREO DISCO MIXER with 7 band graphic equaliser and 10 segment L.E.D. Vu Meters. Many outstanding features.

5 Inputs with individual fader controls:— 2 Mag. turntable, 2 Aux. plus Mic. with talk-over switch. Headphone monitor. Master output control with Hi-Low outputs. Compatible with our OMP Power Amplifiers.
Size: 360 x 200 x 120 mm. Supply 240V/50Hz AC.



Price £119.00 + £3.00 P&P.

B.K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★ All items packed where applicable in special energy absorbing PU foam. ★ Please phone 0702 527572 ★



electronize

AUTO-ELECTRONIC PRODUCTS

KITS OR READY BUILT

TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION



IS
YOUR CAR

AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
 - ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains it from service to service.
 - ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs. where the ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engines maximum (even with 8 cylinders).
 - ★ Is the **PERFORMANCE SMOOTH**. The more powerful spark of Total Energy Discharge eliminates the "near misfires" whilst an electronic filter smoothes out the effects of contact bounce etc.
 - ★ Do the **PLUGS** and **POINTS** always need changing to bring the engine back to its best? Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.
 - ★ **TOTAL ENERGY DISCHARGE** is a unique system and the most powerful on the market - 3½ times the power of inductive systems - 3½ times the energy and 3 times the duration of ordinary capacitive systems. These are the facts:
Performance at only 6 volts (max. supply 16 volts)
SPARK POWER — 140W, SPARK ENERGY — 36mJ
SPARK DURATION — 500µS, STORED ENERGY — 135mJ
LOADED OUTPUT VOLTAGE
50pF load — 38kV, 50pF + 500k — 26kV
- We challenge any manufacturer to publish better performance figures. Before you buy any other make, ask for the facts, its probably only an inductive system. But if an inductive system is what you really want, we'll still give you a good deal.
- ★ All **ELECTRONIZE** electronic ignitions feature:
EASY FITTING, STANDARD/ELECTRONIC CHANGEOVER SWITCH, STATIC TIMING LIGHT and DESIGNED IN RELIABILITY (14 years experience and a 3 year guarantee).
 - ★ **IN KIT FORM** it provides a top performance system at less than half the price of comparable ready built units. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2uF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

Most NEW CARS already have electronic ignition. Update YOUR CAR

ELECTRONIZE ELECTRONIC CAR ALARM



HOW SAFE IS YOUR CAR ?

More and more cars are stolen each week and even a steering lock seems little help. But a car thief will avoid a car that will cause him trouble and attract attention. If your car has a good alarm system - well there are plenty of other cars to choose from.

LOOK AT THE PROTECTION AN ELECTRONIZE ALARM CAN GIVE:

- ★ **MINIATURE KEY PLUG** A miniature jack plug attaches to your key ring and is coded to your particular alarm.
- ★ **2025 INDIVIDUAL COMBINATIONS** The key plug contains two 1% tolerance resistors, both must be the correct value and together give 2025 different combinations.
- ★ **ATTRACTS MAXIMUM ATTENTION** This alarm system not only intermittently sounds the horn, but also flashes the headlight and prevents the engine being started.
- ★ **60 SECOND ALARM PERIOD** If triggered the alarm will sound for 60 seconds, unless cancelled by the key plug, before resetting ready to be triggered again.
- ★ **30 SECOND EXIT DELAY** The system is armed by pressing a small button on a dashboard mounted control panel. This starts a 30 second delay period during which the owner can open and close doors without triggering the alarm.
- ★ **10 SECOND ENTRY DELAY** When a door is opened a 10 second delay operates to allow the owner to disarm the system with the coded key plug. Latching circuits are used and once triggered the alarm can only be cancelled by the key plug.
- ★ **L.E.D. FUNCTION INDICATOR** An LED is included in the dashboard unit and indicates the systems operating state. The LED lights continuously to show the system is armed and in the exit delay condition. A flashing LED indicates that the alarm has been triggered and is in the entry delay condition.
- ★ **ACCESSORY LOOP - BONNET/BOOT SWITCH - IGNITION TRIGGER** These operate three separate circuits and will trigger the alarm immediately, regardless of entry and exit delays.
- ★ **SAFETY INTERLOCK** The system cannot be armed by accident when the engine is running and the car is in motion.
- ★ **LOW SUPPLY CURRENT** CMOS IC's and low power operational amplifiers achieve a normal operating current of only 2.5 mA.
- ★ **IN KIT FORM** It provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, random selection resistors to set the code and full set of components etc. In fact everything down to the last washer plus easy to follow instructions.

fill in the coupon and send to:

Please send more information

ELECTRONIZE DESIGN Dept E · Magnus Rd · Wilnecote · Tamworth · B77 5BY · tel 0827 281000

TOTAL ENERGY DISCHARGE (6 or 12 volt negative earth)

- Assembled ready to fit £29.70 £19.95
 D.I.Y. parts kit £15.95 £14.95

TWIN OUTPUT for cars and motor cycles with dual ignition

- Twin, Assembled ready to fit £36.45 £29.95
 Twin, D.I.Y. parts kit £24.55 £22.95
 (positive earth £22.95)

INDUCTIVE DISCHARGE (12 volt only)

- Assembled ready to fit £15.95 £12.75

Prices Include VAT

£1.00 PP(UK) per Unit

CAR ALARM (12 volt negative earth)

- Assembled ready to fit (All wires and connectors incl.) £27.95 £29.95
 D.I.Y. parts kit £24.95 £19.95

I enclose cheque/postal order OR debit my Access/Visa card

VISA

Name _____

Address _____

Code _____

68