

SEPTEMBER TO NOVEMBER 1988

PRICE 85p IR £1.25

Electronics

THE MAPLIN MAGAZINE

**TUNE-IN TO
THE WORLD
WITH THIS
SUPERB
SHORTWAVE
RECEIVER**



Also in this issue:

LOUDSPEAKERS
The first 111 years!

ELECTRONICS
by Experiment!

CALCS
for Engineers!

Plus
Speaker Cabinet Design,
MW/LW radio,
Stripboard Projects!

MAPLIN'S 6 REGIONAL SHOPS

NEW SHOP IN
BRISTOL

HELP SERVE YOU BETTER!

Birmingham:

Sutton New Road, Erdington. Tel: 021 384 8411.

Bristol:

302 Gloucester Road. Tel: 0272 232014.

London:

159-161 King Street, Hammersmith W6.

Tel: 01 748 0926.

Manchester:

8 Oxford Road. Tel: 061 236 0281.

Southampton:

46-48 Bevois Valley Road. Tel: 0703 225831.

Southend-on-Sea:

282-284 London Road, Westcliff-on-Sea, Essex.

Tel: Southend-on-Sea (0702) 554000.

For mail order enquiries,
please *do not* call our shops as they
will be unable to help you.



Before you send your next order to us by post, take a look and see if there's a Maplin shop near you. In our shops you'll find that personal service that even the best mail-order operations cannot match. And you can look at the products before you buy. If you're coming for a particular item, a quick phone call will enable you to be certain the shop has everything you want in stock.

Our shops are pleased to accept Access, Barclaycard, Connect, American Express, Mapcard and cheques up to £50 with a cheque guarantee card. We'll even accept ordinary money as well!

All our shops are close to excellent parking facilities, meters in London and Manchester, and free elsewhere.

The South

In the South our Southampton store is conveniently placed for easy access from all parts of Hampshire and surrounding counties, and is 15 minutes from Portsmouth.

London

Our London store now open 6 full days a week is situated just to the west of the pedestrian shopping centre in Hammersmith, and is just five minutes from the end of the M4 and only a short walk from the District, Piccadilly and Metropolitan lines' Hammersmith station.

The Midlands

In the Midlands, our self service Birmingham store now open 6 full days a week is just 3 minutes from the M6. Turn north at Spaghetti Junction (junction 6), onto the A5127 following the signs to Erdington. As you approach the Erdington roundabout, you'll see the store's 50 space car park directly in front of you.

South-East

Essex and Kent are served by our self-service Southend shop now open 6 full days a week which is right on the A13, just 2 minutes before you reach the centre of Southend. And we're only 30 minutes from the M25 (junction 29) as well.

West

Our West country store in Bristol is open a full 6 days per week. The self-service store can be found on the A38 Gloucester Road, midway between Bristol city centre and the Filton airport.

The North

Our self-service store in Manchester, now open 7 days a week, serves the North and is just off the Mancunian Way, opposite the BBC, about 5 minutes from the end of the M602 or junction 10 on the M63.


All our shops are open from 9a.m. to 5.30p.m. Monday to Saturday (9.30a.m. Wednesday) except Southampton which is closed Mondays. In addition Manchester is open Sundays. All shops are closed on Public Holidays. Shops do *not* close for lunch.

There's a friendly welcome in store for you at any Maplin shop. Our helpful staff may often be able to help with a technical problem or a constructional difficulty.

Call in at a Maplin store and get what you want today. We look forward to serving you.


PROJECTS

Direct Conversion Shortwave Receiver 2

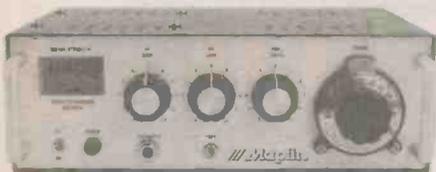

A choice of four tuning kits allow you to listen to speech or morse code from 10 metres to 160 metres. The main features of this easy-to-build unit are a tuned active front end, buffered RF oscillator output, reduction drive 'vernier' tuning and on-board voltage regulator and audio power amplifier.

Bob's Mini Circuits 26

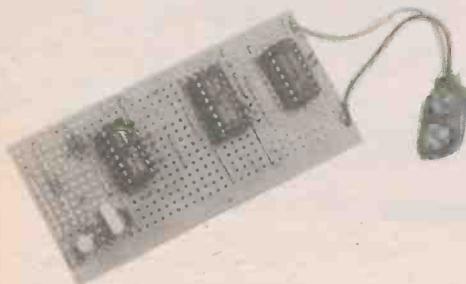

Four useful mini circuits from the prolific pen of Robert Penfold, built on stripboard. You can construct a MIDI thro box, a capacitance meter adaptor, a crystal calibrator and a transistor tester.

2 Way 16 Litre Loudspeaker System 56

Another in our popular series on loudspeaker cabinet designs. Full cabinet construction details are given and the electronics and baffle are available.




FEATURES

Loudspeakers - The first 11 years! 18



The first part of this new series covers the 'early years' of loudspeaker design and includes examples of the work of such 'giants' as S.G. Brown, V.F. Greaves, C. Kyle, Rice and Kellogg, and many others.

Exploring Radio 38

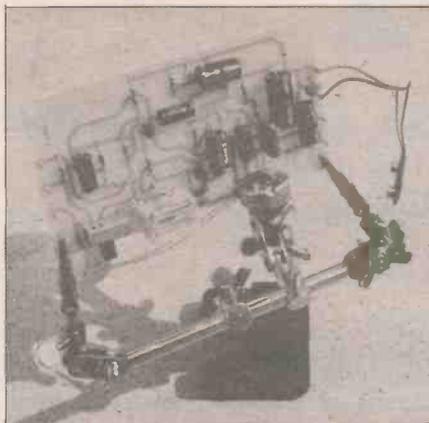

The MW radio in the last issue is expanded to cover the LW band also. A printed circuit board is available so that you can build it for yourself.

Calcs 42

The start of a new series on 'mathematics' with an electronics bias. This first part looks at 'Complex Numbers'.

Not Flat - Just Run Down! 44



Learn how not to treat your ni-cad batteries! Includes monitor program for BBC micro.

Electronics by Experiment 47

Part 4 covers D-type flip-flops, shift registers, the ring counter, and a design for a CRO probe.

'Hello, Who's Calling?' ... 52

Part 2 looks at the Central Battery System and the development of the 'candlestick' telephone.



REGULARS

| | |
|-------------------------------|----|
| Want to Air your Views? | 17 |
| Maplin's Big Heart | 25 |
| Price Changes List | 31 |
| Amendments to Catalogue | 33 |
| New Items Price List | 33 |
| Subscription Form | 34 |
| Order Coupon | 35 |
| Electronics is Changing | 36 |
| 20 Best Selling Books | 37 |
| Calling All Hobbyists | 61 |
| New Books | 62 |
| Classified | 64 |
| Top 20 Kits | 64 |

Mail Order

P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Retail Sales: (0702) 554161. Enquiries: (0702) 552911.
Trade Sales: (0702) 554171. Enquiries: (0702) 552961.
General: (0702) 554155. Cashtel: (0702) 552941.

Shops: See inside front cover.

Editorial & Production

Editor Roy Smith
Production Manager Mike Holmes
Technical Editors Dave Goodman, Chris Barlow
Art Directors Peter Blackmore, Greg Buckley
Art Assistants Andy Nunn, Martin King
Technical Artists John Dudley, Lesley Foster

Published by

Maplin Electronic Supplies Ltd.
Typesetting by Inline Design Systems Ltd.
258A London Road, Hadleigh, Benfleet, Essex SS7 2DE.
Printed by Mayhew McCrimmon Ltd., Star Lane, Great Wakering, Essex.
Distributed by Spotlight Magazine Distribution Ltd., 1-11 Benwell Rd, London N7.

Copyright. All material is subject to world wide copyright protection, and reproduction or imitation in whole or part is expressly forbidden. All reasonable care is taken to ensure accuracy in preparation of the magazine, but Maplin Electronic Supplies Ltd. cannot be held legally responsible for its contents. Where errors occur corrections will be published as soon as possible afterwards. Permission to reproduce printed circuit board layouts commercially or marketing of kits must be sought from the publisher.

© Copyright 1988 Maplin Electronic Supplies Limited.

DIRECT CONVERSION SHORT WAVE RECEIVER



by Chris Barlow

- ★ Receives Speech (SSB, DSB, AM) and Morse (CW)
- ★ Choice of Amateur band, 160 metre – 10 metre
- ★ Reduction drive 'Vernier' tuning
- ★ Tuned Active front end
- ★ Signal strength meter
- ★ Buffered RF Oscillator output
- ★ On-board Voltage regulator and Audio power amplifier

Introduction

The receiver described in this article has been designed to have many of the features found on sophisticated ready-made short wave radios. The cost of such radio equipment is generally quite high and this can discourage newcomers to the hobby. However, good results can be achieved using relatively simple home-constructed receivers of the direct conversion design. This type of receiver has the advantage of simplicity of construction and ease of alignment, with the minimum of test gear.

The frequency range of the short wave bands start as low as 1.7MHz and extends up to 30MHz. To include all these bands on one receiver would present switching and tracking problems that would result in a compromise in its performance. For this reason it was decided that the receiver would cover only one band, but which one? Within the short wave spectrum there are segments allocated to amateur radio operators. These are people located all over the world pursuing the hobby of long distance communication using privately owned radio equipment.

There are six main amateur bands, with the addition of three new ones, and the choice of band is entirely up to you. However, the 80 metre band, admittedly not the best band for long distance reception will provide European stations after dark and British amateurs during daylight hours. When conditions are favour-

Specification of Prototype

RF Specifications (80 Metre version)

Tuning Range: 3.490MHz – 3.810MHz
 Frequency Stability: Less than 100Hz/hour drift after 30 minute warm-up
 Sensitivity: 0.1 μ V for a readable signal
 0.3 μ V or less for 10dB (S+N)/N
 Oscillator Output: 450mV RMS off load
 100mV RMS into 50 Ω load

AF Specifications

Bandpass: 2.8kHz at -6dB (175Hz – 3kHz)
 Dynamic range: 90dB
 Signal to Noise: 40dB
 Power Output into 8 Ω : 1W RMS
 Distortion: 1%
 Tape Output: 100mV RMS into 47k Ω
 Headphone Output: 8 Ω – 32 Ω Mono/Stereo

DC Specifications

Unregulated Power Input: 15 – 20V
 Regulated Power Input: 10.5 – 14V
 Quiescent Current at 12V: 147mA
 Current at full Output: 295mA

able and a suitable aerial is used, stations from further afield can be received, such as America, Africa and Australia. A popular higher frequency band is 20 metres, however this and even higher bands are affected by changes in world wide environmental conditions of the upper atmosphere. This tends to leave them inactive or 'dead' for much of the time and this fact should be taken into consideration when choosing the tuning pack associated with this project. A complete list of the HF amateur bands showing the relevant tuning pack you should use is shown in Table 1. **DON'T FORGET TO ORDER THE TUNING PACK WHEN ORDERING YOUR RECEIVER KIT.**

Direct Conversion

A direct conversion receiver achieves in one signal conversion operation what a superhet achieves in two or more. This is done by mixing the incoming RF signal in a non-linear device with a locally generated RF carrier close to the frequency of the incoming signal. One of the resulting products is the audio modulating frequency when receiving single sideband (SSB) or a beat frequency when receiving morse code (CW). This audio signal is then filtered out from the other unwanted mixer products and amplified, forming the audio output of the receiver.

Circuit Description

In addition to the circuit shown in Figure 2, a block diagram is detailed in Figure 1. This should assist you when following the circuit description or fault finding in the completed unit.

The receiver has two DC power inputs, regulated and unregulated. If using the regulated input, the voltage must be between 10.5 to 14V from an external DC regulated supply or batteries. When using the unregulated input, a mains adaptor such as the unregulated 1A (YM85G), set to its 12V output, will supply the necessary voltage to the regulator RG1. This will be in the order of 15 to 20V and RG1 will stabilise this voltage to 12V. It is most important that the DC supply be connected in the correct polarity, with the positive (+V) going to the centre pin of the DC connector SK1 or SK2.

When the power switch S1 is turned on the supply is connected to the main decoupling capacitor C3 and the front panel indicator LD1. LP1 is a wire-ended filament bulb mounted behind the signal strength meter to provide back illumination. The +12V supply then feeds a second voltage regulator, RG2, which is a variable output type and is set to produce +8V by the resistors R2, 4, 5 and RV1. The preset RV1 is a 22-turn cermet type, which is used when setting up the highly

accurate +8V varicap tuning reference. R3, C6 and C7 provide yet more supply decoupling for the rest of the circuit. For the op-amps to function correctly a half supply reference must be generated, this is provided by one half of IC2. The voltage reference applied to the input of this op-amp is derived from the two resistors R6 and R7 which form a potential divider. The op-amp is merely used as a zero gain buffer to provide a low impedance half supply, its output being de-coupled by C80.

The aerial and earth from SK5 connects to pins P10,11 on the circuit board. To reduce the amount of 'out of band' signals reaching the RF amplifier, a series tuned circuit comprising of T1 and C10 is used. At its resonant frequency this circuit has a low impedance and will allow the RF to pass into the low impedance winding of T2. However, to all other frequencies this circuit appears as a high impedance, thus reducing the level of unwanted RF energy reaching T2. The output of T2 is a parallel tuned circuit, with C12, TC1 and the varicap diode VC1 controlling its resonant frequency. The RF signals across this circuit are then applied to the high impedance 'gate one' input of TR1. The other gate has a variable DC bias applied to it, derived from RV2, R19 and is de-coupled to RF by C14. As the bias voltage is increased,

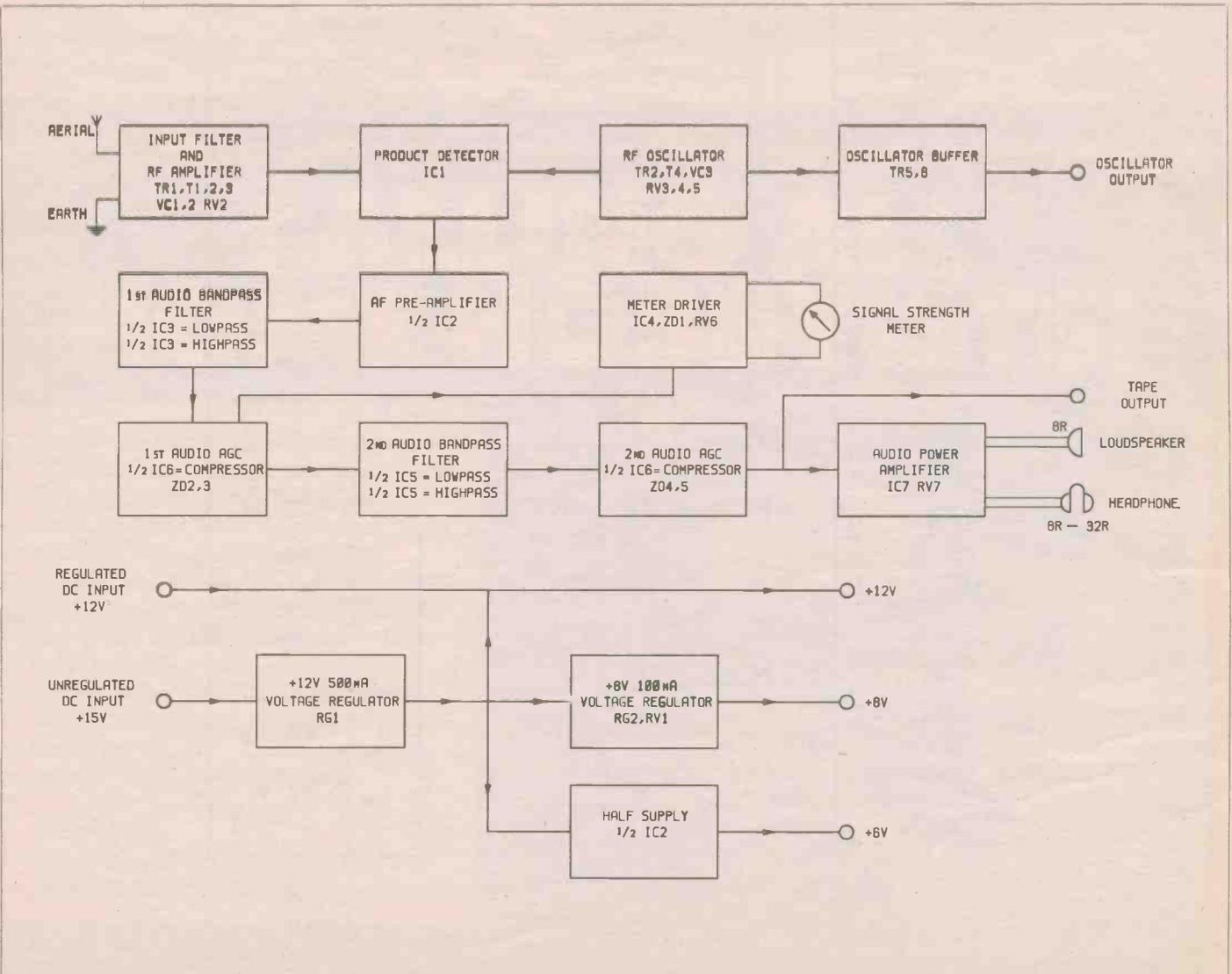


Figure 1. Block diagram.

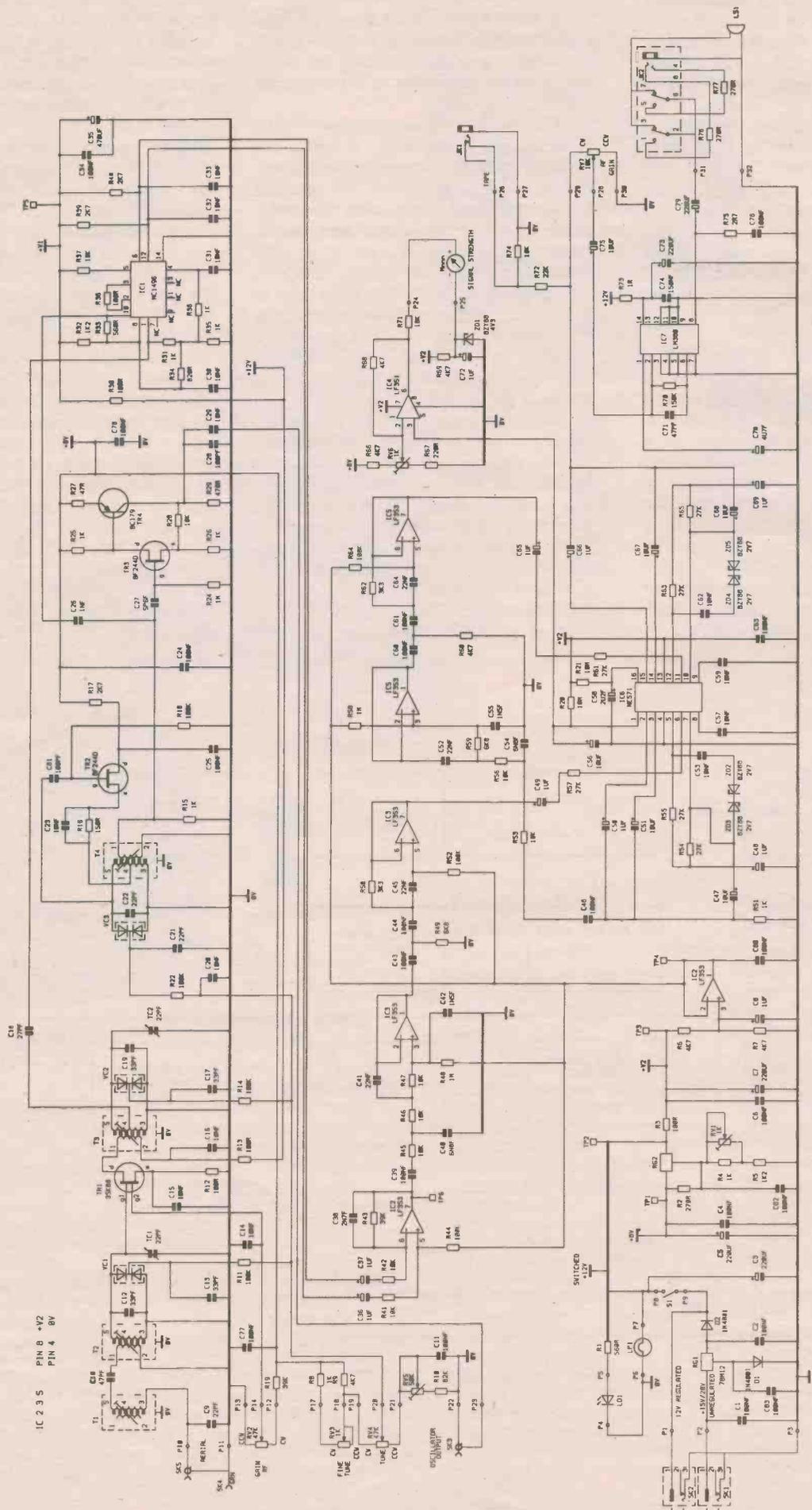


Figure 2. Circuit.

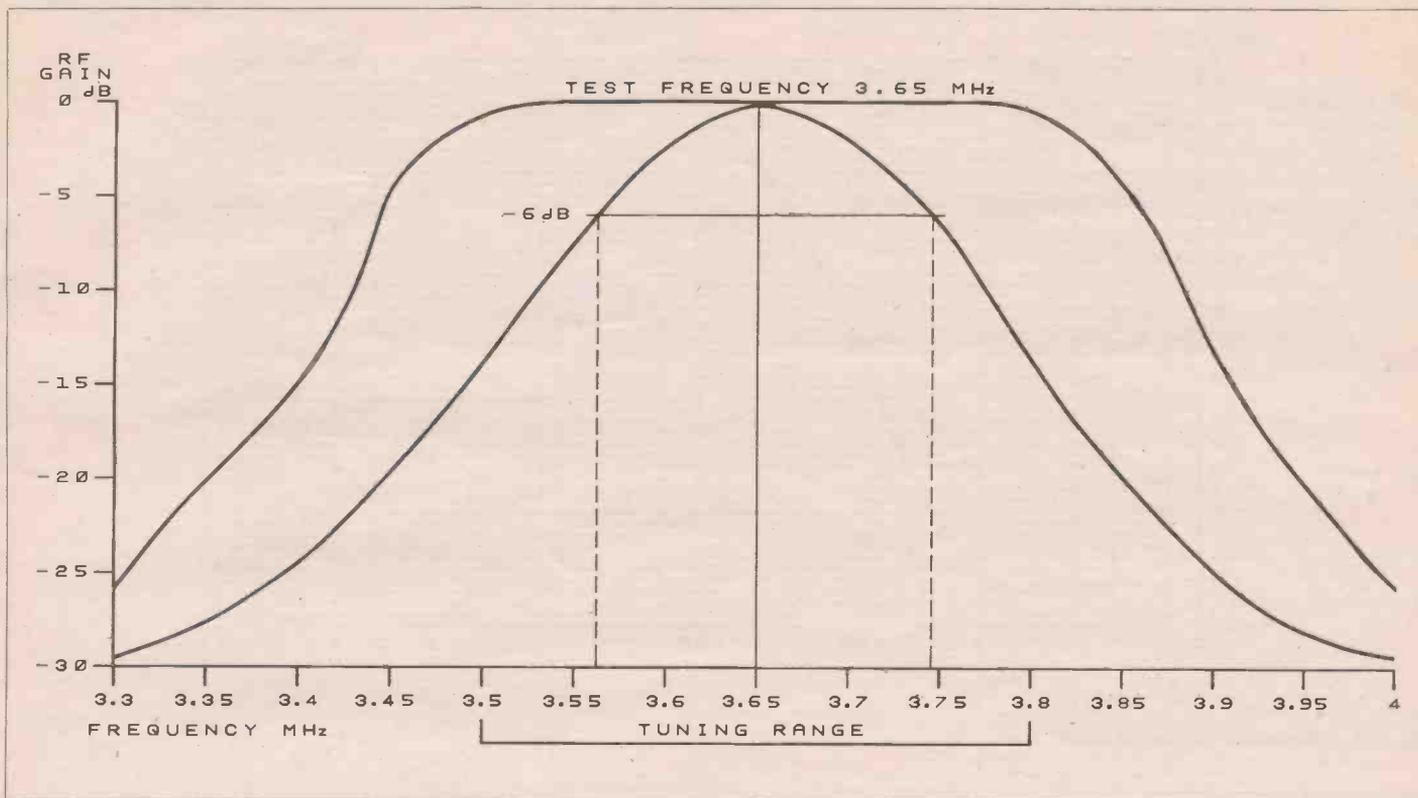


Figure 3. RF filter and amplifier response (80 metre version).

the gain of the amplifier will increase to provide almost 20dB of gain. The low impedance winding of T3 is placed in the drain of TR1 and its output is tuned by C19, TC2 and VC2. The RF signals are then tapped off and fed via C18 to the product detector IC1. A graph showing the tuning and bandpass response of the prototype 80 metre front end is illustrated in Figure 3.

The RF oscillator consists of an FET transistor TR2 and T4 being tuned by C22, VC3, in the Hartley configuration. The output is taken from the low impedance winding of T4 and is fed to the product detector via C26. The output is also taken via C27 to a broad band buffer, comprising of TR3 and TR4. This provides a low impedance output for driving frequency counters or other devices. The DC bias used to tune the oscillator and RF amplifier is generated by a chain of resistors. The high end is set by the value of R8 and fine tuning is provided by RV3. RV4 is used for the main tune control, with the 22-turn preset RV5 and R10 setting the low frequency limit. A plot of the frequency stability of the prototype 80 metre oscillator is shown in Figure 4.

An MC1496 double balanced mixer IC1 is used to produce the sums and differences of the two frequencies applied to pins 1 and 10. The audio output we want is the difference frequency between the RF signals from the input amplifier and the output of the RF oscillator. IC1 produces two audio outputs which are in anti-phase to each other. These signals are fed via C36, C37 to the inverting and non-inverting inputs of IC2. This op-amp is used to produce a high level signal for the bandpass and compressor circuits.

The audio processor comprises of four stages, two bandpass filters and two compressor circuits. Each bandpass filter is made from a lowpass and highpass circuit using a dual op-amp, the first being IC3 and the second IC5. The combined effect of these

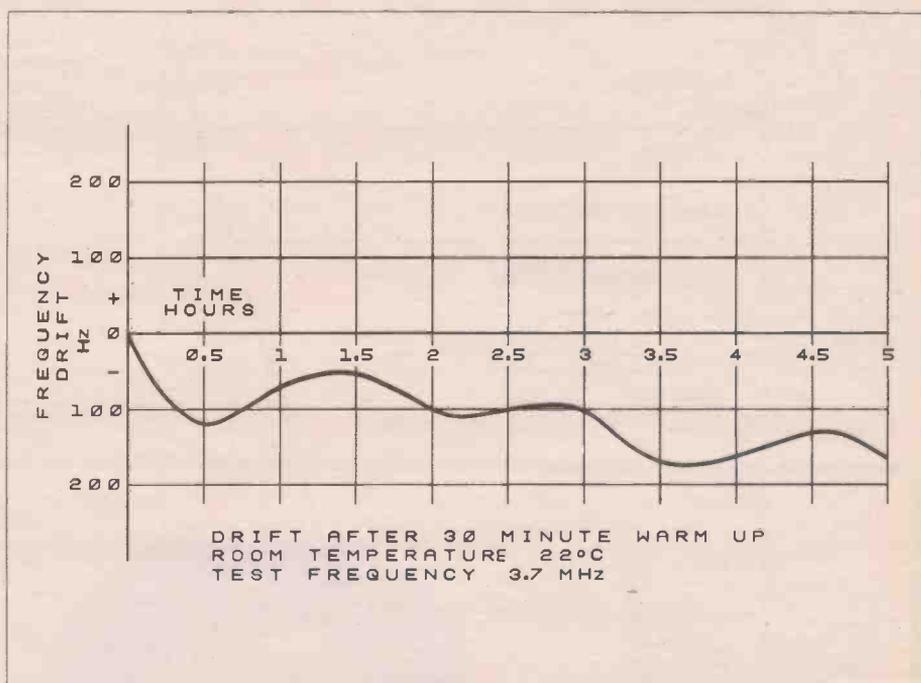


Figure 4. Frequency stability.

filters can be seen in Figure 5. A compressor is used to provide an automatic gain control (AGC) to reduce the volume differences between strong and weak stations. The DC reference produced by the first AGC stage is used by the meter driver IC4 to indicate the strength of the signal. RV6 on pin 2 is used to set the meter zero point and as the voltage on pin 3 progressively increases from the AGC stage the meter will show a steadily rising value. The combined affect of the two compressors is shown in Figure 6 and the signal strength meter response in Figure 7.

The output from the second compressor feeds the final audio product to the tape output and the AF gain control RV7. The sound

output stage IC7, the LM380, is capable of driving an 8Ω loudspeaker or 8 to 32Ω headphones. Stereo or mono phones can be used and when plugged into the quarter inch jack socket JK2 the speaker is automatically switched out.

PCB Assembly

The PCB is a double-sided, plated-through hole type, chosen for maximum reliability and stability. However, removal of a misplaced component is quite difficult with this kind of board so please double-check each component type, value and its polarity where appropriate, before soldering! The PCB has a printed legend to assist you in correctly

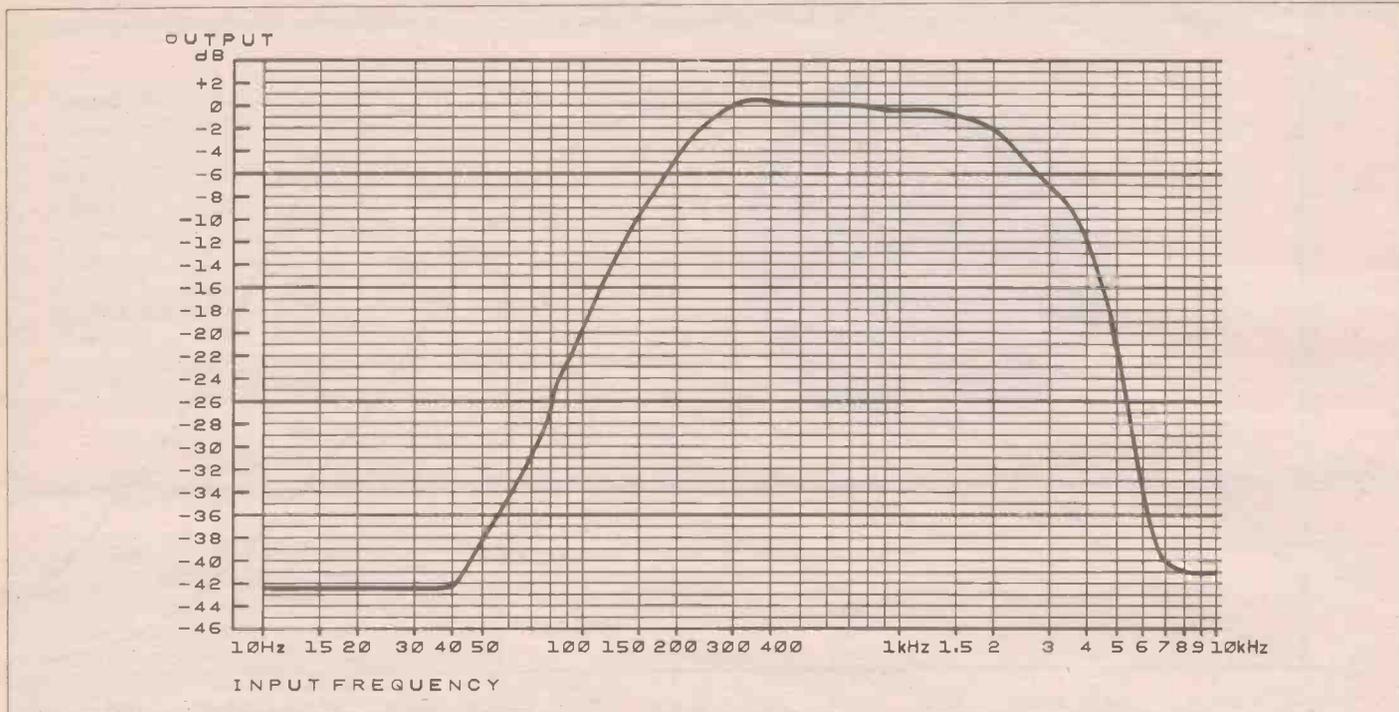


Figure 5. Audio bandpass filter response.

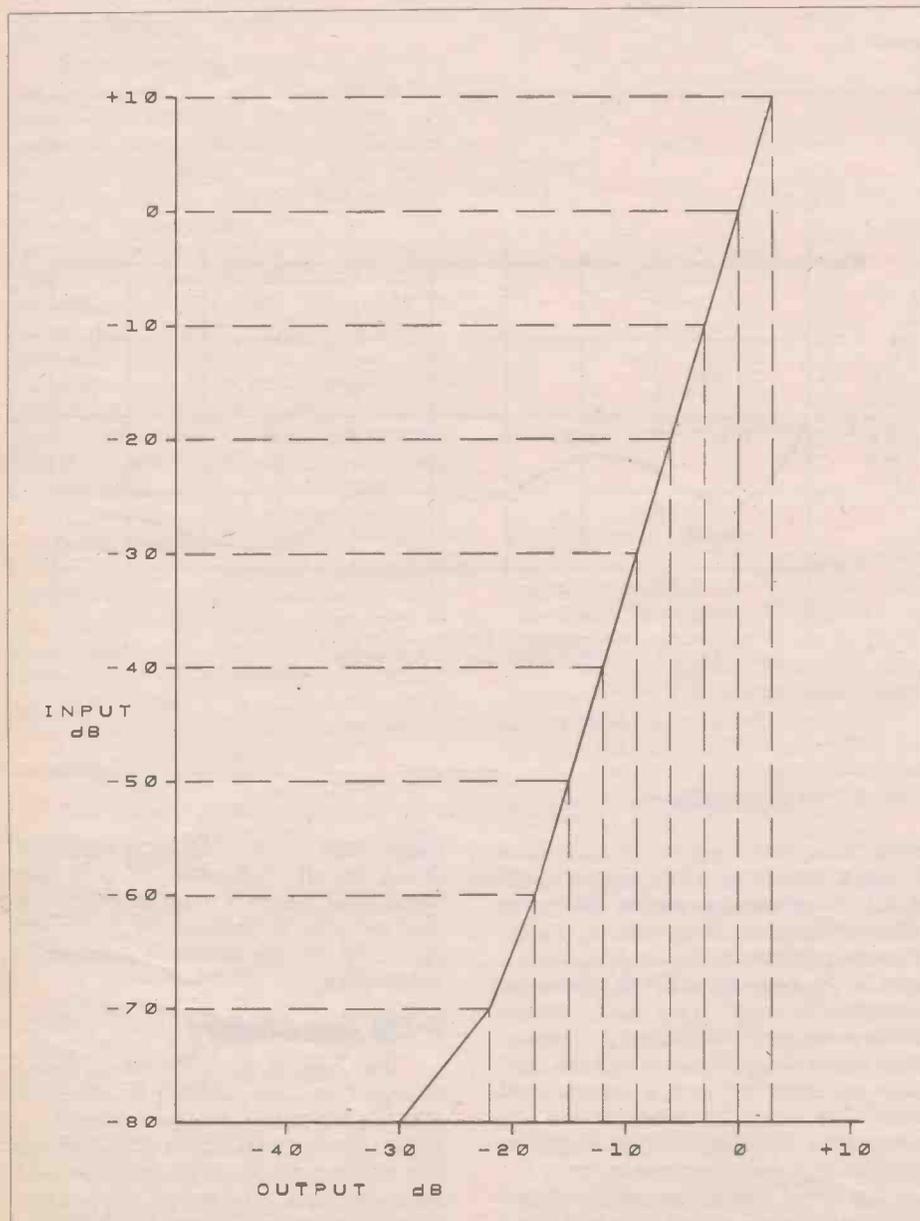


Figure 6. Input/output transfer characteristics.

positioning each item, see Figure 8. The majority of the components are supplied in the main kit (LM60Q), but some RF components have to be selected from the appropriate tuning pack for the desired band, see Table 1.

The sequence in which the components are fitted is not critical. However, the following instructions will be of use in making these tasks as straightforward as possible. It is usually easier to start with the smaller components, such as the resistors. Next mount the ceramic, polyester, polystyrene and electrolytic capacitors. The polarity for the electrolytic capacitors is shown by a plus sign (+) matching that on the PCB legend. However on some capacitors the polarity is designated by a negative symbol (-), in which case the lead nearest this symbol goes away from the positive sign on the legend. All the silicon diodes have a band at one end. Be sure to position them according to the legend, where the appropriate markings are shown. The three varicaps VC1, VC2 and VC3 resemble transistors and you must carefully match the case to the outline shown on the legend. Next install all the transistors, matching each case to its outline. The dual gate MOSFET transistor TR1 is a surface mounting component and is shown in Figure 9. When fitting the IC sockets ensure that you install the appropriate one at each position, matching the notch with the block on the legend. Install IC1 to IC7 making certain that all the pins go into their sockets and the pin one marker is at the notched end. The RF transformers T1, 2, 3 and T4 will only fit one way, but make certain that they are pushed down firmly on to the surface of the PCB. Next install the three preset resistors RV1, 5, 6 and the two trimmer capacitors TC1, 2 and set them all to their half way positions. Install pins at the test points TP1 to TP6 ensuring that you push them fully into the board. When fitting the 'Minicon' connectors ensure that the locking tags are facing inwards, see Photo 1. Finally, mount the two voltage regulators, RG1 and RG2 in their correct positions on the board, ensuring

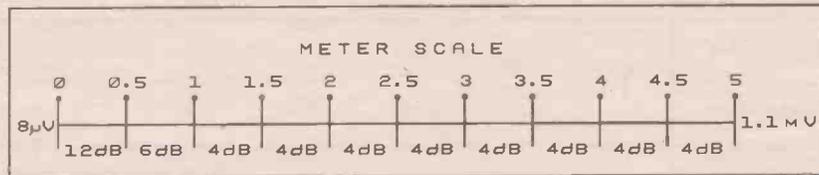


Figure 7. Signal strength meter response.

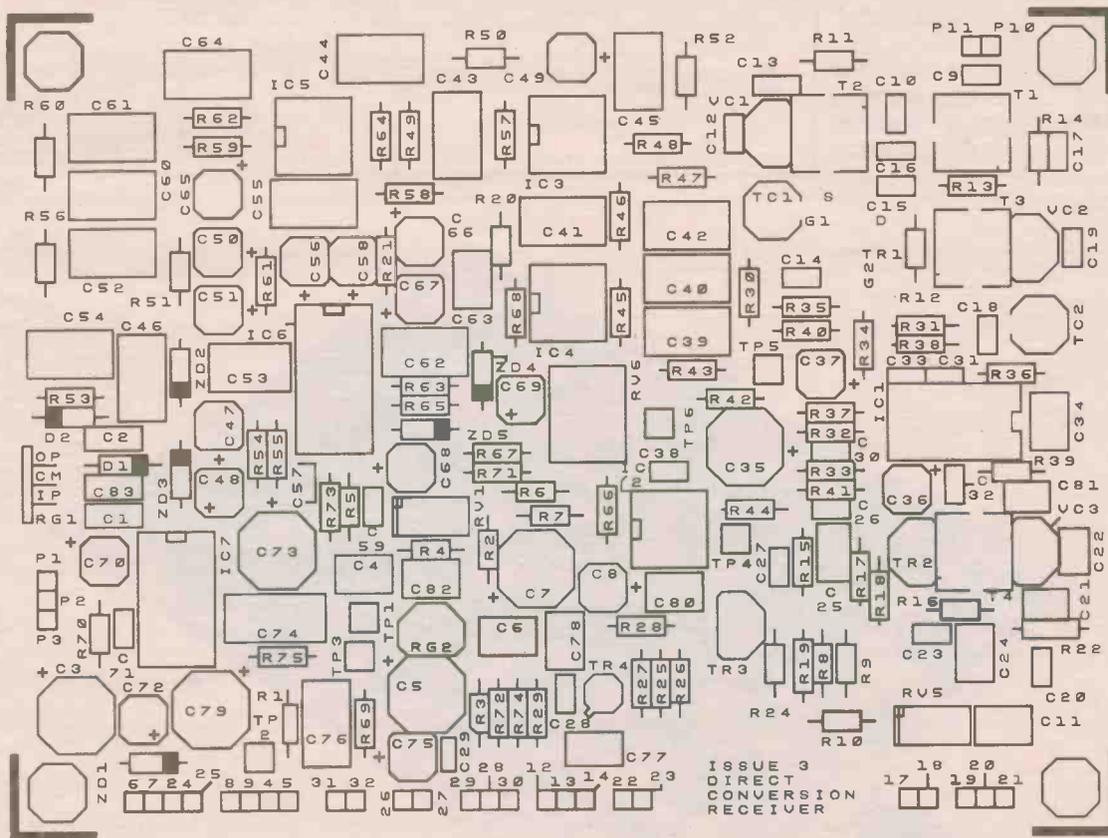


Figure 8. PCB layout.

that you fit RG1 as shown in Figure 15.

This completes the assembly of the PCB and you should now check your work very carefully making sure that all the solder joints are sound. It is also very important that the solder side of the circuit board does not have any trimmed component leads standing proud by more than 3mm, as this may result in a short circuit. Further information on soldering and assembly techniques can be found in the 'Constructors Guide' included in the kit. Photo 2 shows the completed PCB in clear detail.

Final Assembly

The unit is designed to fit in to a metal case type 2408/160 (Maplin code XJ33L) which is also available ready drilled (Maplin

code YT05F). An internal chassis is also available for this box (XJ41U) and indeed this has been incorporated in the design, once again a ready drilled version is available (YT04E). However, if you wish to make up your own box, drilling details for the box and the chassis are given in Figure 10. Also shown in Figure 10 are details of the potentiometer mounting bracket should you wish to make your own, this item too is available ready made (JG47B). Custom made stick-on panels can be purchased to enhance the final look. When fitting ensure that the front and back metal panels of the box are clean then remove the protective backing from the self-adhesive decorative trims. Carefully position and firmly push down using a dry, clean cloth until the

trims are securely in place. Photo 3 shows the rear trim.

Before fitting the headphone jack JK2 remove its forward facing locating tag. When installing the two jack sockets, position a pot washer between the steel chassis and the back of the front panel, see Figure 11. Next prepare the four rotary potentiometers by cutting the shafts to a length of 12mm. When mounting the AF, RF gain and fine tuning pots use two nuts as shown in Figure 12. Before mounting the main tuning control, rotate its shaft to its fully clockwise position. Then back it off a small amount to set the wiper onto the start of the active part of its carbon track. Set the vernier dial to read 100 and remove the small bolt at the rear of the dial. Do not remove

| Amateur Band | Receiver Tuning Range | Tuning Pack | T1,2,3,4 | 1% 0.6W Metal Film | | | Ceramic Plate | | | Polystyrene |
|---------------------------|--|-------------|---------------|--------------------|---------------|------|---------------|-------|--------------|-------------|
| | | | | R8 | R9 | R10 | C10 | C18 | C12,13,17,19 | C21,22 |
| 160M 1.810 – 2.000MHz | 1.800 – 2.010MHz | 1 | KANK 3333R | 22k | NOT FITTED | 22k | 180pF | 100pF | 120pF | 100pF |
| 80M 3.500 – 3.800MHz | 3.490 – 3.810MHz | | | 1k | 4k7 | 82k | 47pF | 27pF | 33pF | 22pF |
| 40M 7.000 – 7.100MHz | 6.690 – 7.150MHz | 2 | KANK 3334R | 10k | NOT FITTED | 180k | 180pF | 27pF | 120pF | 100pF |
| 10.100 – 10.150MHz | 10.000 – 10.500MHz | | | 1k | 2k2 | 150k | 47pF | | 47pF | 33pF |
| 20M 14.000 – 14.350MHz | 13.990 – 14.400MHz | 3 | KANK 3335R | 1k | 4k7 | 180k | 220pF | 27pF | 100pF | 100pF |
| 18.068 – 18.168MHz | 18.000 – 18.500MHz | | | | 2k2 | 220k | 180pF | 15pF | 68pF | 68pF |
| 15M 21.000 – 21.450MHz | 20.990 – 21.500MHz | | | | | 330k | 100pF | | 47pF | 47pF |
| 24.890 – 24.990MHz | 24.540 – 25.000MHz | 4 | KANK 3335R | 1k | 2k2 | 560k | 56pF | 15pF | 22pF | 22pF |
| 10M 28.000 – 29.700MHz | A, 27.975 – 28.525MHz B, 28.475 – 29.025MHz C, 28.975 – 29.525MHz D, 29.475 – 30.025MHz | | | | | | 27pF | | 15pF | 15pF |

Table 1. Band Chart.

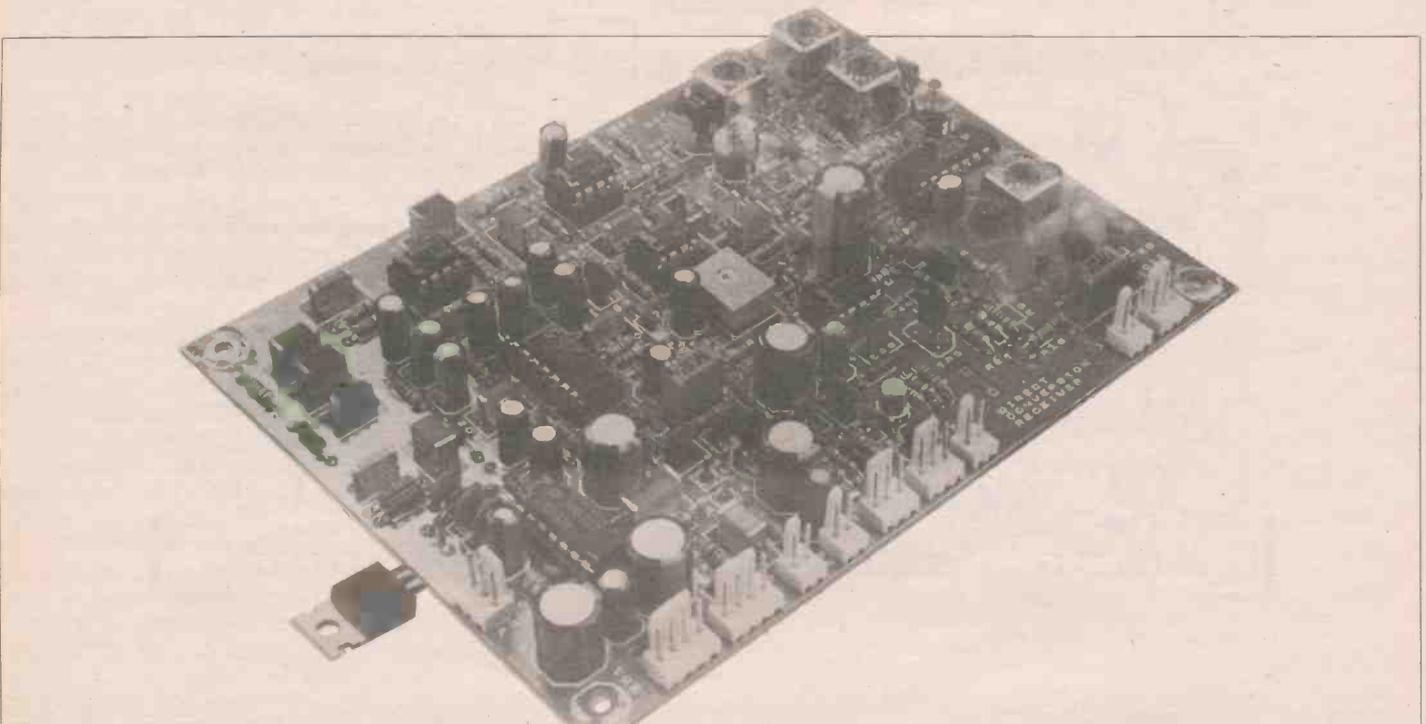


Photo 1. Note that the connector tabs face inboard.

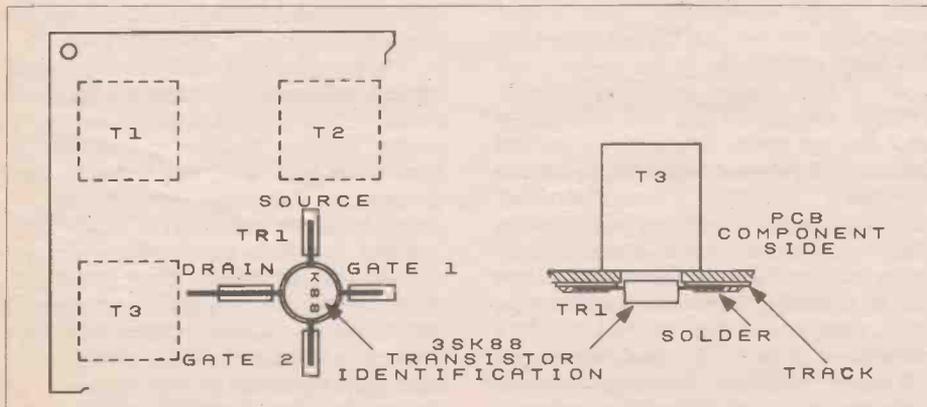


Figure 9. Mounting the dual gate mosfet.

the pot shaft retaining bolt, merely slacken it off enough to allow the shaft to enter the dial. Using M3 hardware, mount the bracket assembly and vernier dial to the front panel, as shown in Figure 13. Next, install the rest of the front panel components and secure the three knobs so that the pointers are at zero when the controls are set fully-anticlockwise.

The EARTH terminal is mounted directly onto the back panel, with the insulating bushes, solder tag and one 4mm washer being discarded, see Figure 14. Fit the two RF connectors; SK3 is the BNC and SK5 is the SO239, ensuring that both are tightly secured. The two 2.5mm power sockets are held in place using M2 bolts and do not require fixing nuts as the mounting holes are threaded.

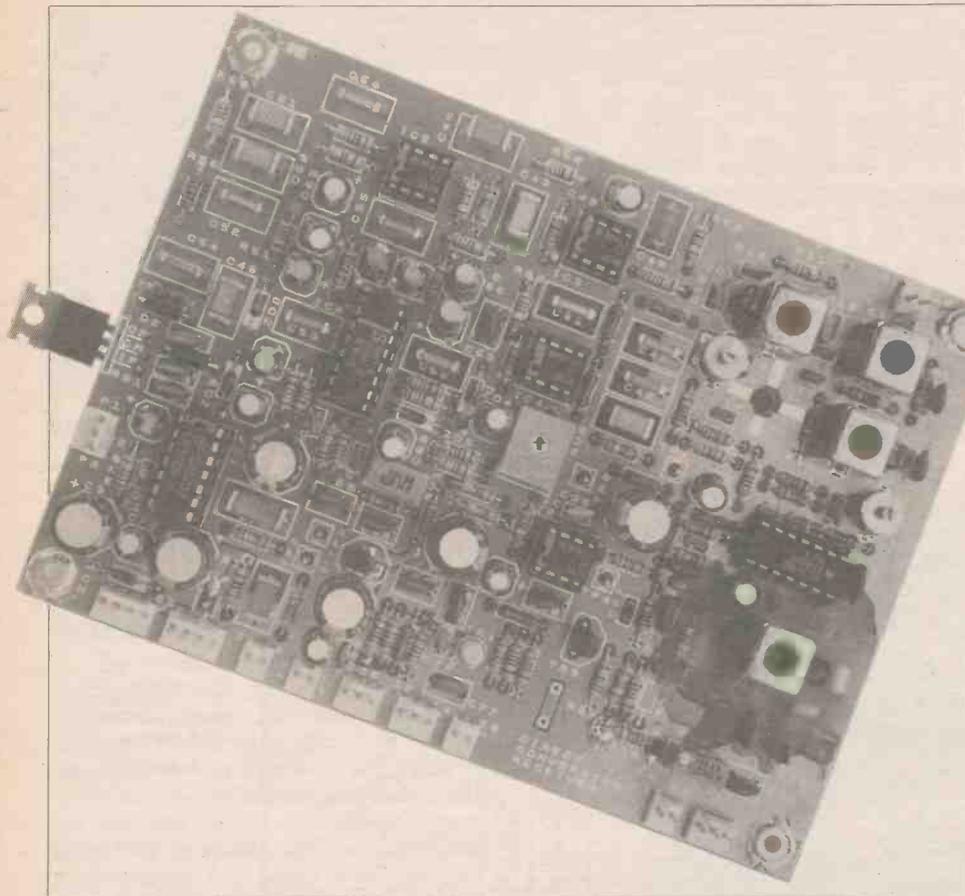


Photo 2. The completed PCB.

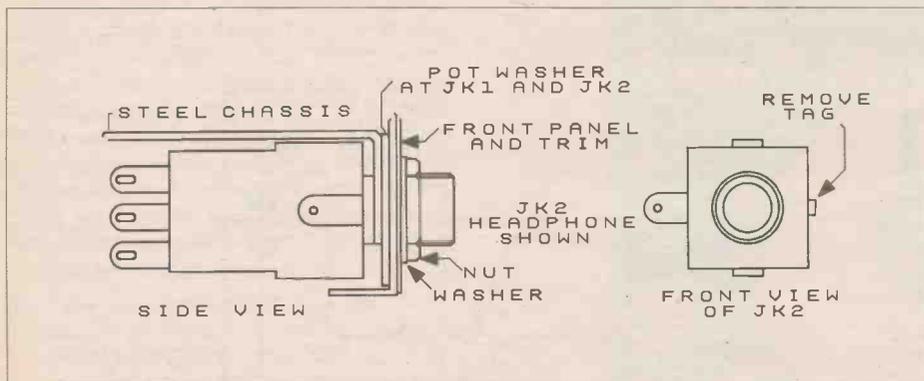


Figure 11. Mounting JK1 and JK2.



Photo 3. Rear view.

The PCB assembly is secured to the steel chassis using 6BA hardware, see Figure 15. When mounting the voltage regulator RG1 ensure that the mica washer and insulating bush are correctly positioned. It is not essential to use heat transfer compound on this device as it is run well within its safe working limits.

The loudspeaker is mounted to the top lid of the case using M4 hardware, as shown in Figure 16. The nut between the speaker and the case is used as a spacer to assist the sound output. This completes the mechanical assembly of the unit and you should now check your work very carefully before proceeding to the wiring stage.

Wiring

If you purchase a complete kit from Maplin it should contain six, one metre lengths of coloured hook-up wire. No specific colour has been designated for each wire connection, it is entirely up to you. The use of coloured wire is to simplify matters, thus making it easier to trace separate connections to off-board components, just in case there is a fault in any given part of the circuit. A wiring diagram showing all the interconnections is given in Figure 17. The wire connections to the PCB are made using 'Minicon' connectors and the method of installing them is shown in Figure 18. All the wires to the front panel components below the internal chassis pass through a small PVC grommet, see Photo 4. The connections to the headphone jack socket JK2 and the loudspeaker LS1 are made using 'figure 8' zip cable. Do not forget to fit the two link wires or the resistors, R76 and R77 on JK2. When wiring the filament bulb LP1 follow the assembly and mounting instructions in Figure 19 which shows construction details for a cardboard shroud which is used to mount the bulb on the rear of the meter, see Photo 5.

The cable used on SK3 and SK5 has a semi-conducting polythene sheath between the braided screen and the inner insulated conductor. It is most important that the semi-conducting sheath should not be able to come into contact with the centre conductor or anything connected to the centre conductor,

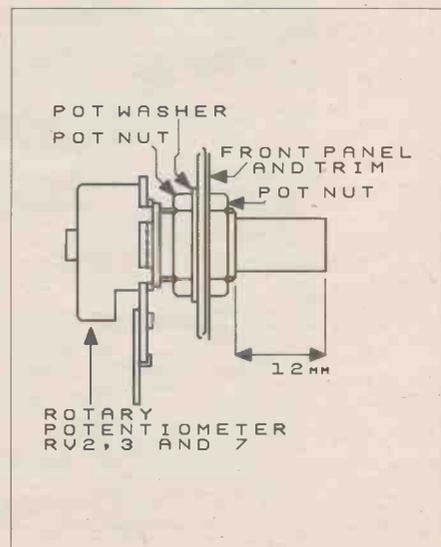


Figure 12. Mounting the AF/RF gain and Fine Tuning pots.

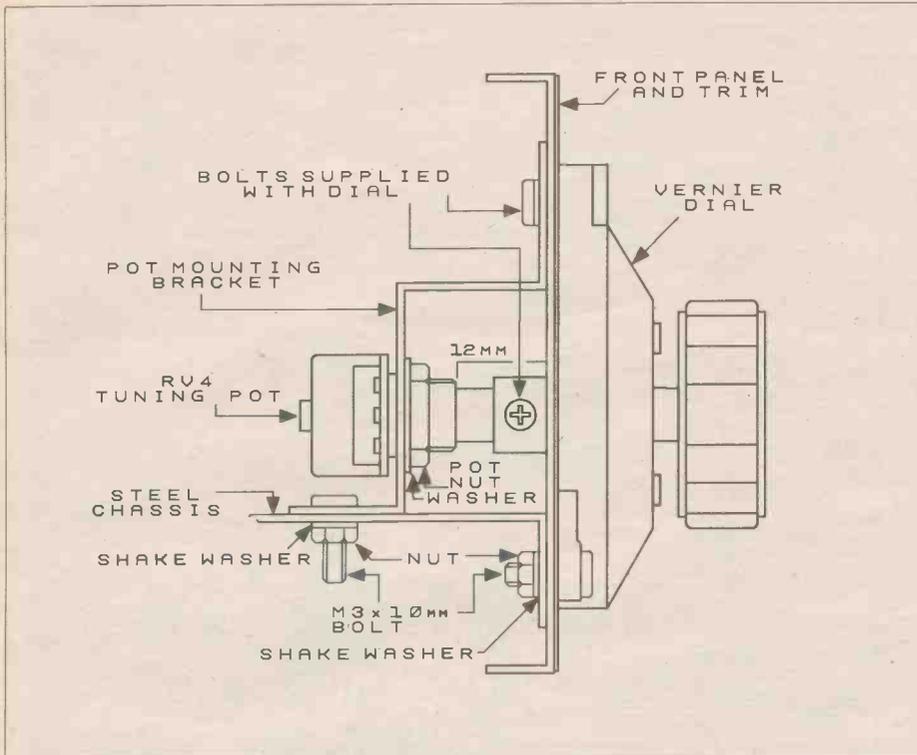


Figure 13. Mounting the Tuning pot.

but that it should be stripped back to the braiding. Photo 6 shows the connections to SK3 and SK5.

This completes the wiring of the receiver and you should now check your work very carefully making sure that all the solder joints are sound.

Testing and Alignment

Before you commence testing the unit set the PCB presets and the front panel controls to the following positions:

On the PCB

RV1, RV5 and RV6 should be set to their half way positions. RV1 and RV5 are 22-turn cermet presets with a slipping clutch which should make an audible clicking sound at each end of their travel. To set them half way, simply rotate the adjustment screw until the clicking sound is heard, then reverse the direction for 11 turns.

On the Front Panel

Set the AF and RF gain controls at zero with the fine tuning set half way to its zero mark. Set the vernier to read 100 on its dial and ensure that the power switch is in the OFF position.

The power supply used during the test procedure was an unregulated 1A mains adaptor type (Maplin code YM85G) and it was set to its 12V output. The polarity switch must be set for positive (+) on the tip of the plug, otherwise damage may be caused to the receiver and power supply when connected. If you intend to use other power supplies, such as rechargeable lead-acid or nickel cadmium batteries, it is STRONGLY recommended that an in-line 1 amp fuse be placed in the positive power line. DO NOT connect the power supply until it is called for during the test procedure.

The aerial used was a 30 metre end fed long wire at approximately 10 metres above



Photo 4. Under the chassis.

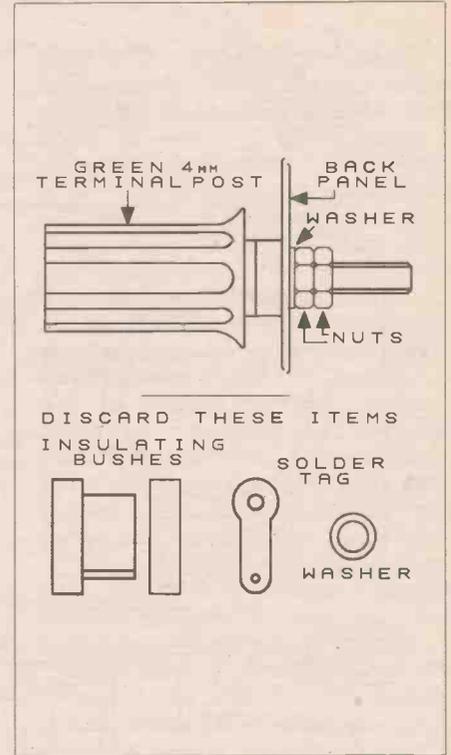


Figure 14. Fixing the earth terminal.

the ground. However, the aerial you use will be determined by the available space and the amateur band you have chosen. The theoretical and practical design of shortwave aerials is an involved topic which can not be covered by this article. However, a list of some of the many books available on this subject is given at the end. DO NOT connect the aerial to the receiver until it is called for.

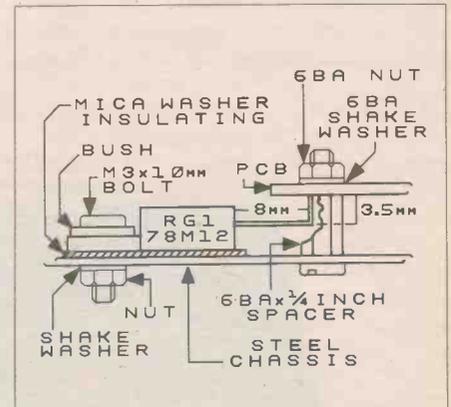


Figure 15. Mounting the PCB and Regulator.

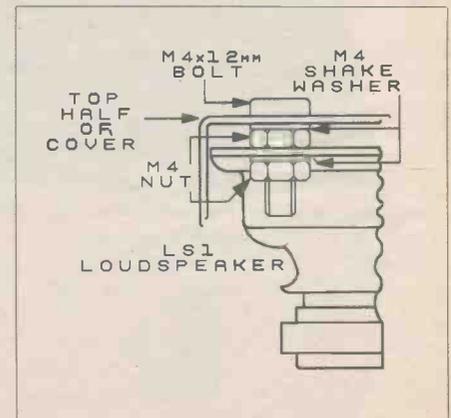


Figure 16. Loudspeaker fixing.

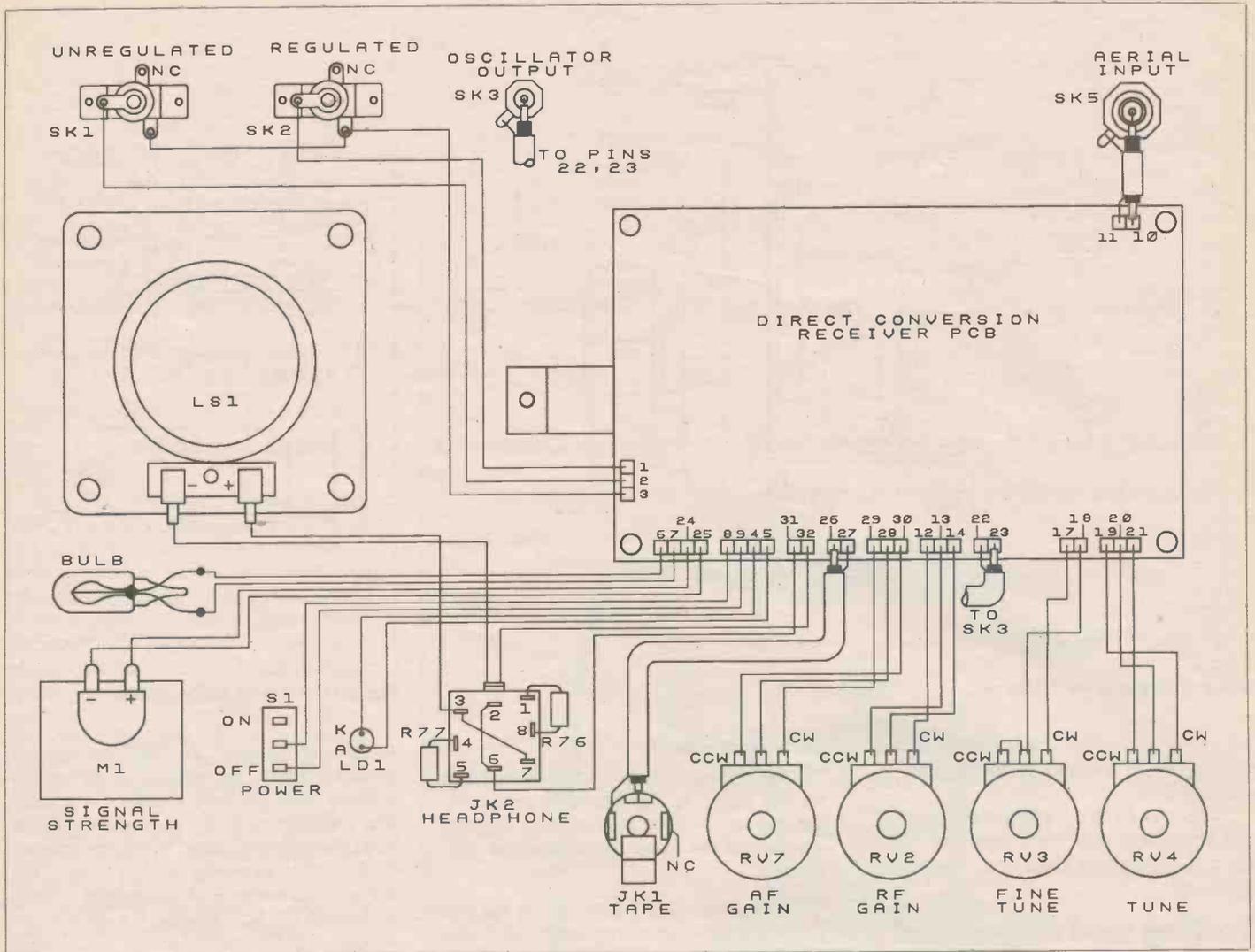


Figure 17. Wiring.

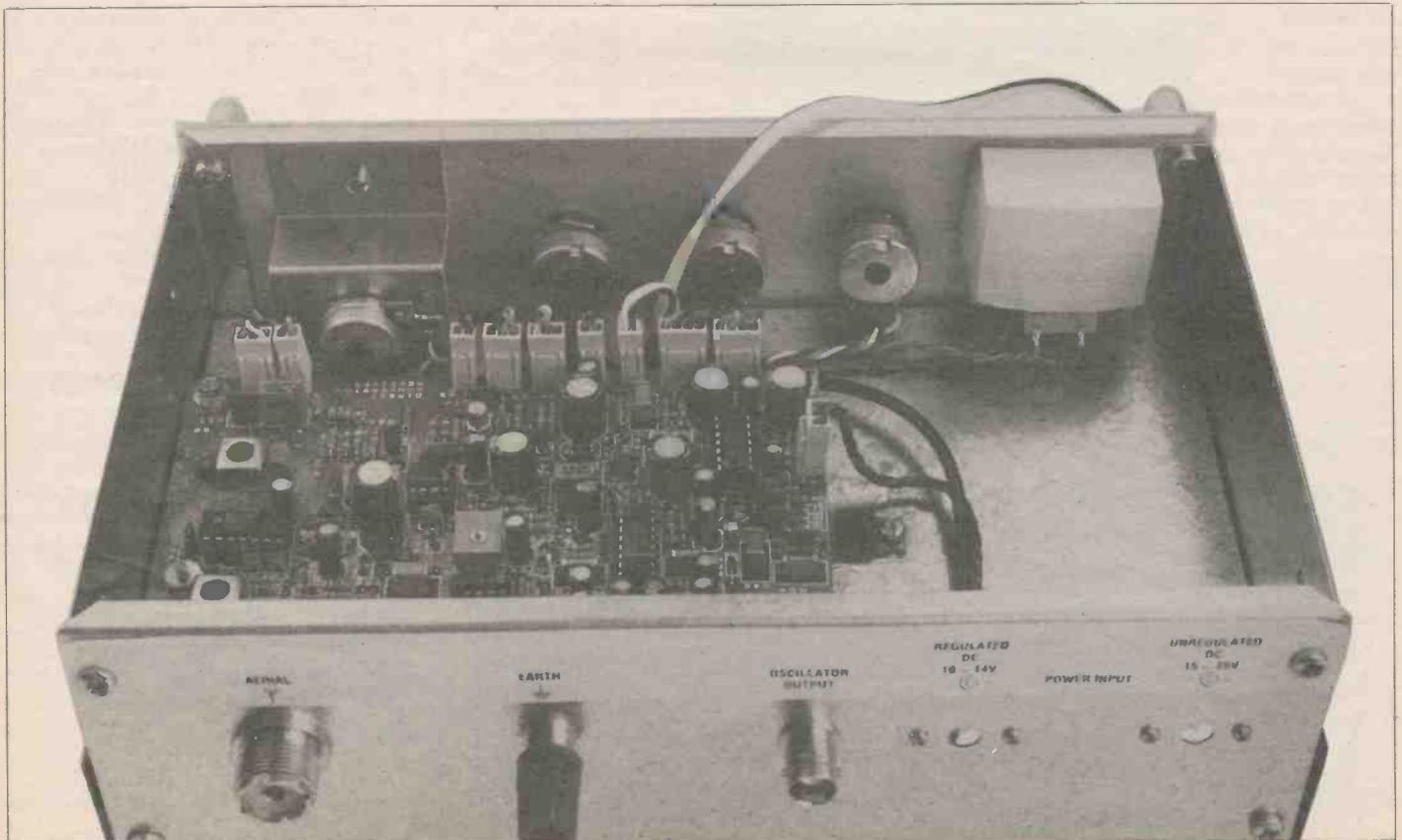


Photo 5. Inside of the front panel.

To measure the DC voltage, current and resistance you will need a digital, or electronic analogue, multimeter with an input impedance of not less than 10MΩ. Other multimeters can be used but some of the readings obtained may vary slightly.

The first test is to measure the resistance at SK1 and SK2. With the meter leads either way round on the centre pin of the unregulated power input socket SK1, a reading of greater than 100kΩ should be present with respect to the chassis. This reading should drop by a small amount when the power on/off switch S1 is activated. Repeat this test on the regulated input SK2, where you should observe the following readings. With the power switch in its OFF position and the test meter leads either way round on the centre pin, an infinite resistance 'open circuit' should be present with respect to the chassis. However, when switched ON this reading should fall to approximately 17Ω. This is mainly due to the low resistance of the filament bulb LP1 and if the Minicon connector in front of ZD1 is temporarily disconnected this reading should rise to greater than 1kΩ if the positive probe is on the centre pin of SK2.

Select a suitable range on your meter that will accommodate a 500mA DC current reading and place it in the positive power line from SK1. Connect the mains adaptor and switch on. The signal strength meter and power indicator LD1 should light up, with a current reading of approximately 147mA being observed. Switch off the receiver, then remove the test meter and reconnect the positive line to SK1.

Now set your multimeter to read DC volts. All voltages are positive with respect to ground, so connect your negative lead to a convenient ground point on the chassis. When the receiver is switched back on, voltages present on the PCB test points should approximately match the following:

TP1 = 8.67V
 TP2 = 12.03V
 TP3 = 10.19V
 TP4 = 5.09V
 TP5 = 11.36V
 TP6 = 5.08V

The voltage at TP1 must now be set to exactly 8.000V by adjusting RV1. Whilst observing the signal strength meter, set RV6 so that the needle is just on the beginning of the zero marker. This completes the DC testing and alignment of the receiver, which must now be left running for a minimum of one hour before commencing the RF adjustments.

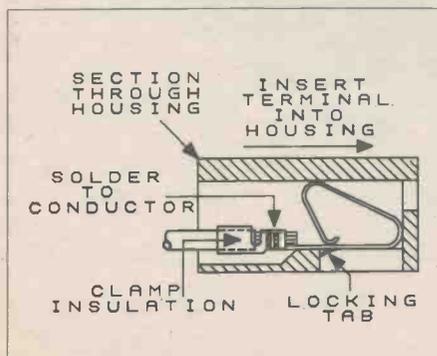


Figure 18. Terminating the wires.

There are three basic methods of RF alignment:

1. The high accuracy approach using an RF signal generator and frequency counter.
2. Medium accuracy using another receiver and aerial on the same band.
3. The 'poke and hope' method using only an aerial.

Method 1

When using a frequency counter to set the tuning range, connect its input to the oscillator output on the back of the receiver and use as short a lead as possible to prevent stray RF pick up. Ensure that the main tuning vernier dial is set to 100 and the fine tune is at the half way zero point. Using a non-metallic trimming tool, carefully adjust the iron dust core of T4 until the top end (high frequency) is set. Then position the main dial to read 0 and

adjust RV5 for the low end of the band. Repeat this procedure until both limits have been set for the required band, as shown in Table 1.

When using an RF signal generator to align the front end, its output is connected to SK5 the aerial input of the receiver. The level of RF injection should be set to produce a half scale deflection on the signal strength meter when the carrier is tuned in. If the AF gain is turned up, an audio tone should be heard whose frequency will change as the receiver is tuned across the incoming signal. At the low end of the band the dust cores of T2 and T3 should be adjusted to give a peak in signal strength. The top end of the tuning range is then peaked using the trimmer capacitors TC1 and TC2. Next set the tuning dial to 50 and adjust the input filter coil T1 for maximum signal reading. Repeat this procedure until no

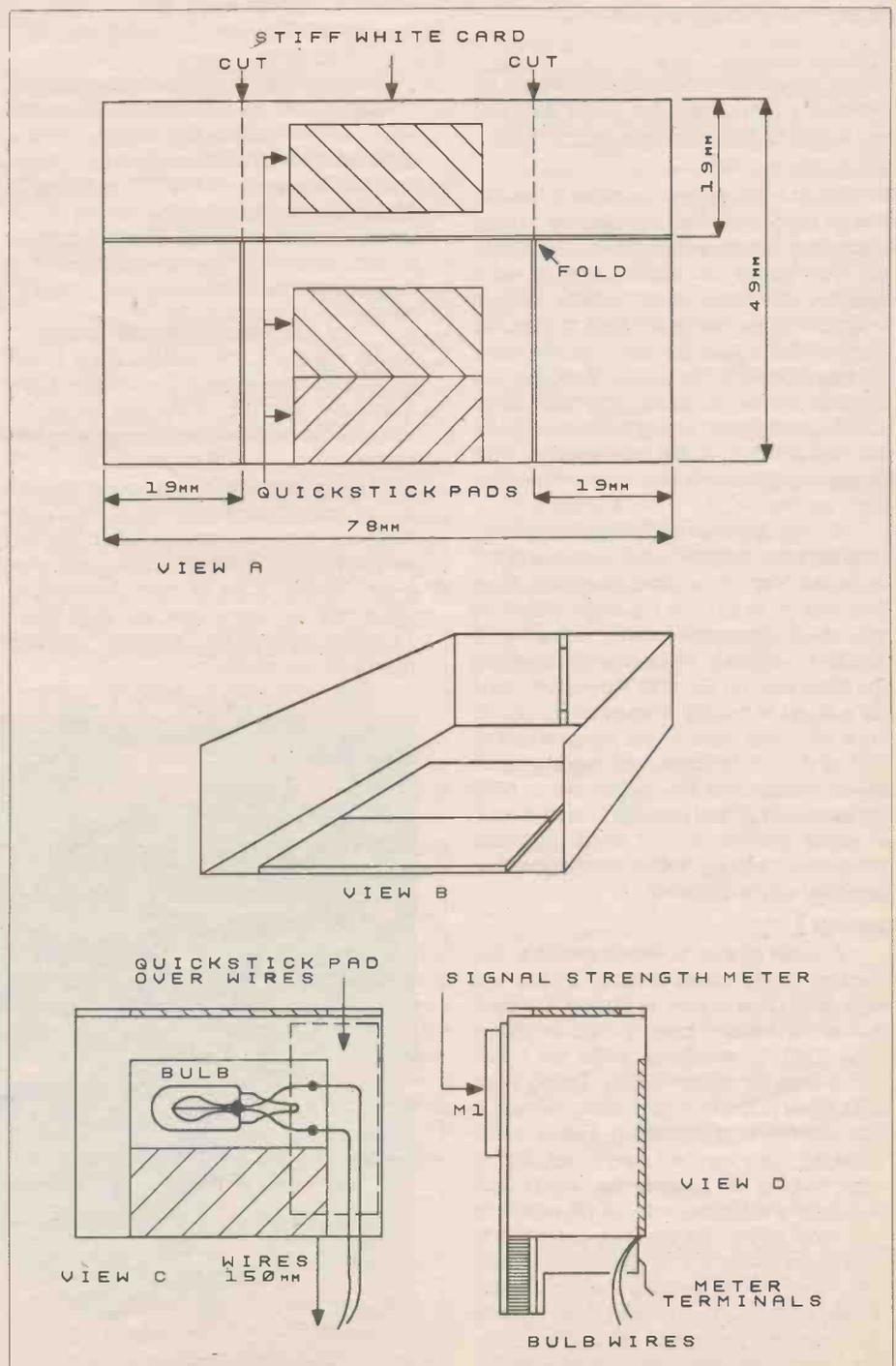


Figure 19. Meter illumination.

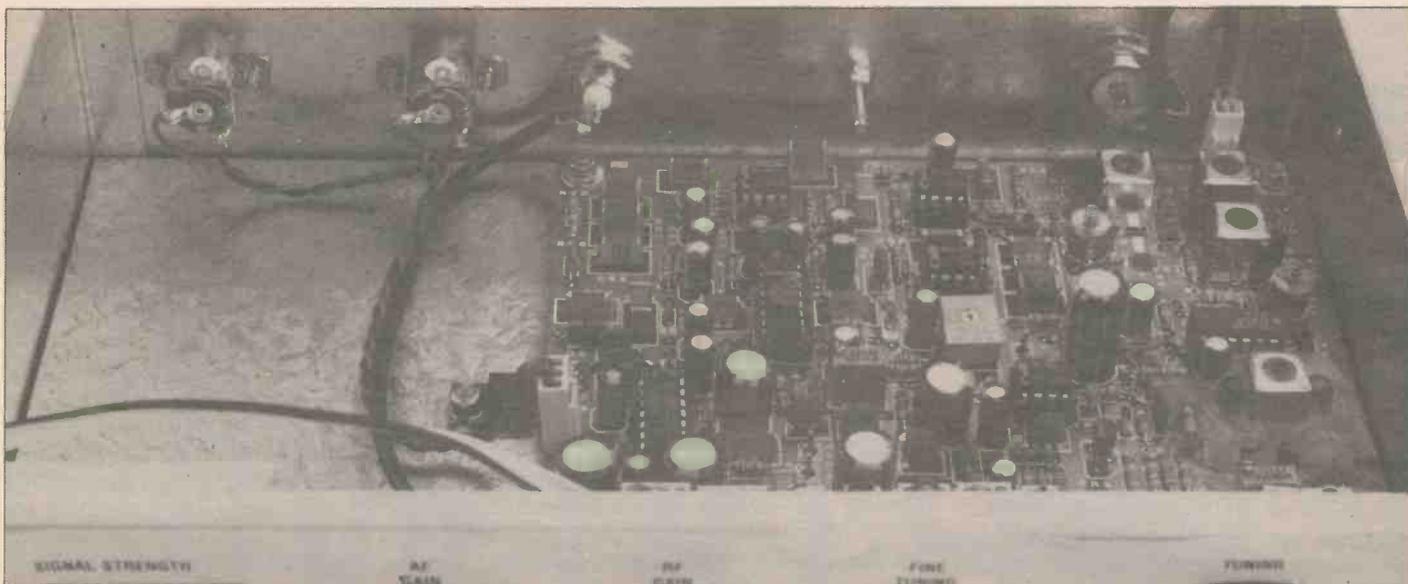


Photo 6. Inside of the rear panel.

further improvement in signal strength can be detected. Finally, check that the RF gain and fine tuning controls are functioning correctly.

Method 2

When using another receiver to set the tuning range of the oscillator no direct connection is made between them. To pick up the RF output, a short piece of wire approximately 200mm (8 inches) long is inserted into the centre terminal of the BNC socket. With a suitable aerial on the other receiver, tune it to the end of the band and listen for the carrier coming from your direct conversion receiver. To adjust this, use T4 for the high and RV5 for the low frequency limit, repeat this procedure until both ends of the band are set.

To align the front end using this method, tune the other receiver into a readable signal at the low end of the band. Swap the aerial over and try to tune for the same station on your direct conversion receiver, adjusting T2 and T3 for a peak in signal strength. Next, put the aerial back on the other receiver and tune for a signal at the high frequency end. Swap back the aerial, tune in the signal adjusting TC1 and TC2 for maximum reading. In a similar manner, set the vernier dial to read approximately 50 and using T1 tune for a peak in signal strength. Repeat these alignment procedures until no further improvement in reception can be obtained.

Method 3

If no test gear or receiver is available, you must set the frequency coverage by trial and error using off air signals. In general, the lower part of the amateur band is used for morse code (CW) transmissions, whilst the upper part is used for speech (SSB). Tuning in an SSB signal properly is quite tricky, but with a little practice it is something that is easily mastered. Very careful tuning is required in order to bring the audio to the correct pitch and the fine tuning control RV3 will make this task much easier. Set the main tuning dial to read 0 and adjust T4 until you start to receive CW transmissions, peaking the signal using T2 and T3. As you tune progressively higher in frequency you should find the SSB transmissions and at the extreme end of the dial TC1 and TC2 are used to peak the signal. If the

SSB stations appear to extend past this point, retune T4 until no more amateur transmissions can be received, then reset the low end of the band using RV5. Next, tune for a station near to the centre of the dial (50) and using T1 adjust for maximum reading on the signal strength meter. Repeat these alignment procedures until no further improvement in reception can be obtained.

Once you have successfully completed the RF alignment, the oscillator stage should be covered in candle wax, see Photo 7. Using a lighted household candle drip the molten wax over the oscillator components being very careful not to get any inside the top of T4. Build up the wax a layer at a time and allow it to cool between applications until the components are completely encapsulated. The wax will cause a shift in oscillator tuning and when it has cooled down to room temperature, which may take some time, you must retune T4 using one of the alignment methods previously described.

Using the Receiver

A good aerial and earth system are essential if the receiver is to be expected to perform at its best, and you should allow it to 'warm up' for at least 30 minutes to obtain frequency stability. The skill of the operator will also play a large part in weeding out the more exotic long distance (DX) stations from the interference (QRM/QRN) on today's crowded bands.

There are two main types of radio signal used by amateurs, morse code (CW) and speech (SSB). When tuning in a CW transmission, the pitch of the dots and dashes start high, then as the receiver is tuned closer to the same RF frequency, the audio pitch will fall. At the dead centre there will be no audio tone as the signal is at the zero beat point. But, if the receiver tuning is continued the pitch of the tone will increase until it goes outside the frequency range of the audio bandpass filter. The final pitch setting will be a matter of personal taste, however 500Hz to

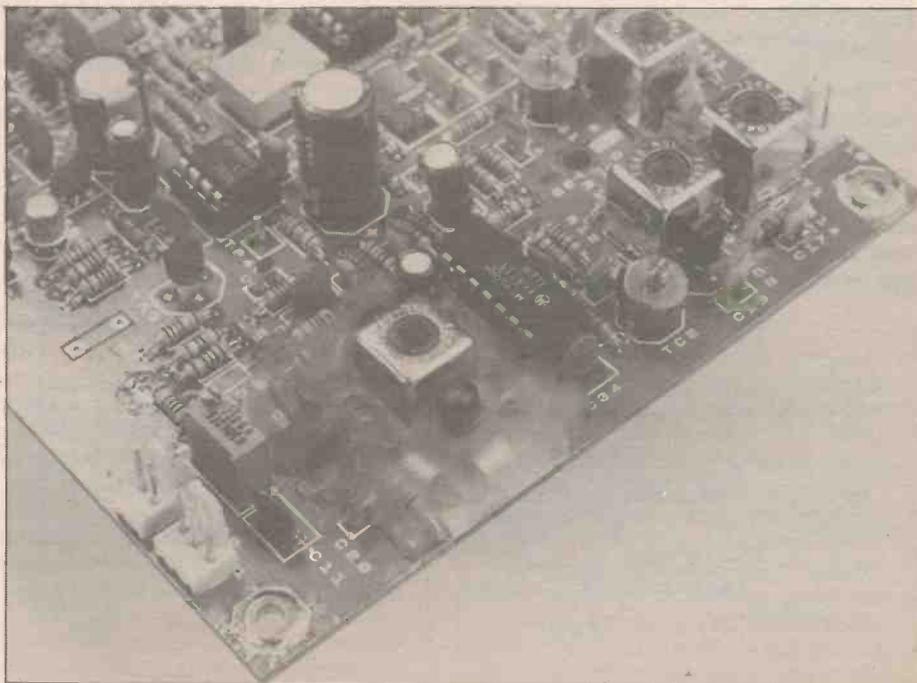


Photo 7. Oscillator section encapsulated in wax.

1kHz is a commonly used range.

The use of single sideband (SSB) for the transmission of speech is preferred by most radio amateurs because of its higher efficiency over ordinary amplitude modulation (AM). In an AM radio signal the level of the RF carrier is modulated by the audio produced by the user. With that type of receiver a small tuning error will probably give no more than a slight loss of audio quality and could even go completely unnoticed. This is not the case when receiving SSB, where the tuning has to be spot on if the station is to be fully resolved. A product of an AM signal is the generation of two sideband signals, lower sideband (LSB) and upper sideband (USB). The sidebands contain the same audio information as the modulated carrier but in a different form. This means that to transmit the information only one of the sidebands needs to be sent and the carrier with the other sideband can be suppressed. However, to resolve the signal the carrier must be re-injected by the product detector in the receiver, which is why the tuning is so critical. The direct conversion receiver principle will permit double sideband signals (DSB) to be received. However, these are not commonly found on the amateur bands where LSB is used up to 40 metres and USB is used on all frequencies above 10MHz. When an SSB station is tuned in on a DSB receiver you will get two places where the signal will be received, but only one sideband will be resolvable. This is the one that matches the original transmitted signal and the overall tone of the audio is set by fine tuning the receiver.

A useful addition to the receiver is a digital frequency counter used to provide an accurate tuning display. The counter should be capable of resolving down to the nearest 100Hz when set to its 0.1 of a second gate time. To prevent the pick up of stray RF signals it should be connected to the oscillator output of the receiver using the shortest

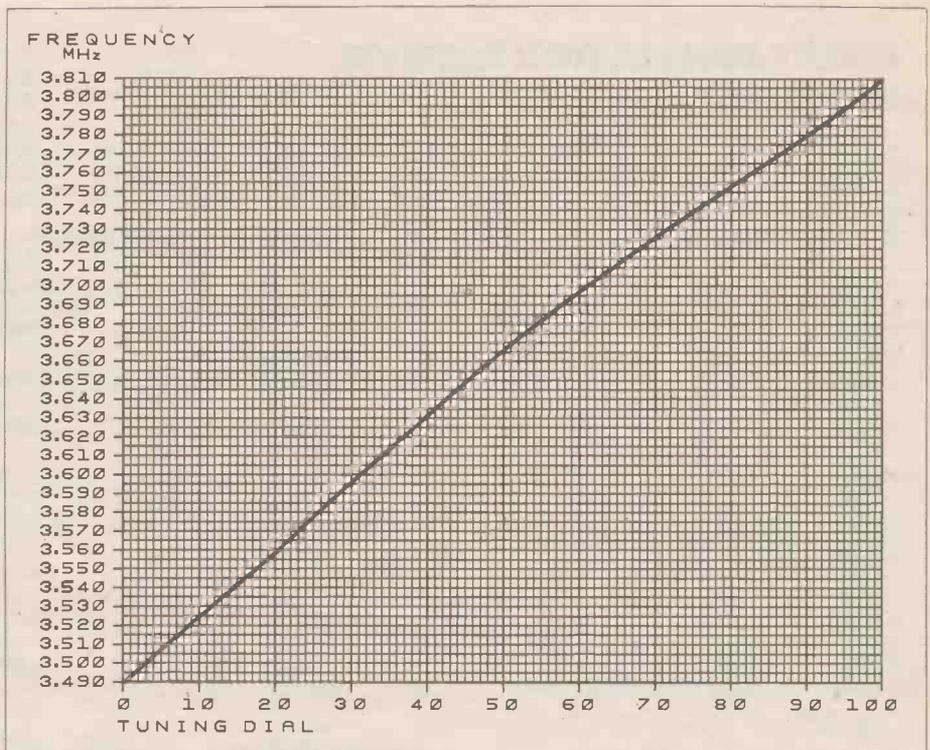


Figure 20. Receiver tuning range (80 metre version).

possible length of cable. If a frequency counter is not permanently available then a tuning chart can be generated using graph paper, see Figure 20. This will help to provide a reasonable tuning accuracy from the vernier dial when the counter is not available.

If the station being received is excessively strong it may start to distort the audio output. This can usually be cured by reducing the RF gain until the reading on the signal strength meter is just below the 5 on the scale.

That wraps it up for this project, I hope you spend many happy hours building your receiver (finished unit shown in Photo 8) and that you find it a pleasure to use once you're

on the air.

Useful Reading

HF Antennas by L.A.Moxon, G6XN. Published by the Radio Society of Great Britain.

Wires and Waves. Published by Practical Wireless.

Radio Wave Propagation (HF Bands) by F.C. Judd.

25 Simple Indoor and Window Aerials by E.M. Noll.

An Introduction to Radio DXing by R.A. Penfold.

Beginner's Guide to Amateur Radio by F.G. Rayer.

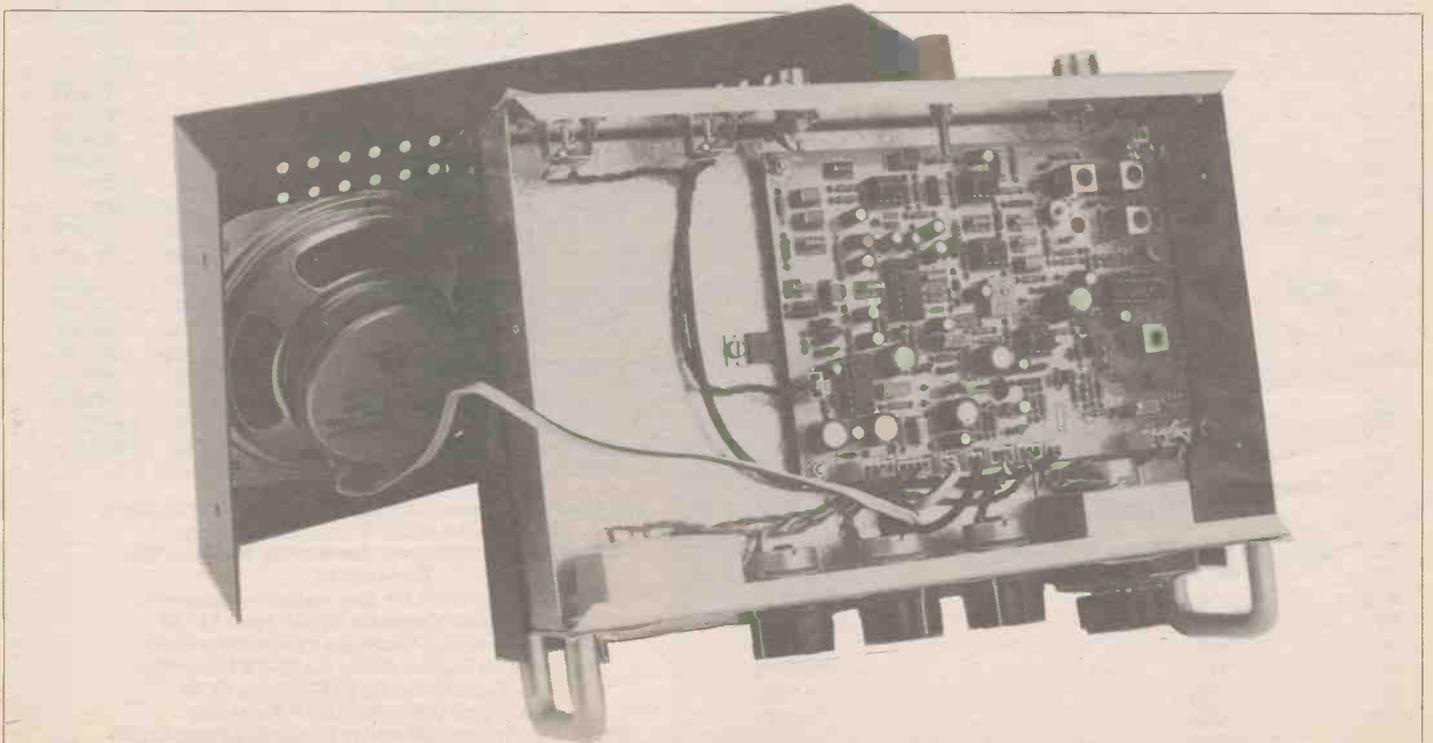


Photo 8. Finished unit.

DIRECT CONVERSION RECEIVER PARTS LIST

RESISTORS: All 0.6W 1% Metal Film

| | | | |
|------------------------------------|----------------|----|---------|
| R1,33 | 560Ω | 2 | (M560R) |
| R2,76,77 | 270Ω | 3 | (M270R) |
| R3,12,13,30, 36 | 100Ω | 5 | (M100R) |
| R4,15,25,26,31,35, 38,51 | 1k | 8 | (M1K) |
| R5,32 | 1k2 | 2 | (M1K2) |
| R6,7,60,66, 68,69 | 4k7 | 6 | (M4K7) |
| R17,39,40 | 2k7 | 3 | (M2K7) |
| R11,14,18,22, 44,52,64 | 100k | 7 | (M100K) |
| R16 | 150Ω | 1 | (M150R) |
| R19,43 | 39k | 2 | (M39K) |
| R20,21 | 10M | 2 | (M10M) |
| R24,48,58 | 1M | 3 | (M1M) |
| R27 | 47Ω | 1 | (M47R) |
| R28,37,41,42,45, 46,47,53,56,74 | 10k | 10 | (M10K) |
| R29 | 470Ω | 1 | (M470R) |
| R34 | 820Ω | 1 | (M820R) |
| R49,69 | 6k8 | 2 | (M6K8) |
| R50,62 | 3k3 | 2 | (M3K3) |
| R54,55,57,61, 63,65 | 27k | 6 | (M27K) |
| R67 | 220Ω | 1 | (M220R) |
| R70 | 150k | 1 | (M150K) |
| R71 | 18k | 1 | (M18K) |
| R72 | 22k | 1 | (M22K) |
| R73 | 1Ω | 1 | (M1R) |
| R75 | 2Ω | 1 | (M2R) |
| RV1 | 1k Cermet 22T | 1 | (UH23A) |
| RV2,4 | 47k Pot Lin | 2 | (FW04E) |
| RV3 | 1k Pot Lin | 1 | (FW00A) |
| RV5 | 50k Cermet 22T | 1 | (UH26D) |
| RV6 | 1k Hor Preset | 1 | (UH00A) |
| RV7 | 10k Pot Log | 1 | (FW22Y) |

CAPACITORS

| | | | |
|--|---------------------------|----|---------|
| C1,2,4,6,11,24,25, 34,63,77,78,80, 82,83 | 100nF Minidisc | 14 | (YR75S) |
| C3,5,7,73,79 | 220μF 16V PC Electrolytic | 5 | (FF13P) |
| C8,36,37,48,49,50, 65,66,69,72 | 1μF 100V PC Electrolytic | 10 | (FF01B) |
| C9 | 22pF Ceramic | 1 | (WX48C) |
| C71 | 47pF Ceramic | 1 | (WX52G) |
| C14,15,16,20,23, 29,30,31,32,33, 57,59 | 10nF Ceramic | 12 | (WX77J) |
| C26 | 1nF Ceramic | 1 | (WX68Y) |
| C27 | 5p6F Ceramic | 1 | (WX41U) |
| C28 | 100pF Ceramic | 1 | (WX56L) |
| C35 | 470μF 16V PC Electrolytic | 1 | (FF15R) |
| C38 | 2n7F Ceramic | 1 | (WX73Q) |
| C39,43,44,46,60, 61,76 | 100nF Polylayer | 7 | (WW41U) |
| C40,54 | 6n8F Polylayer | 2 | (WW27E) |
| C41,45,52,64 | 22nF Polylayer | 4 | (WW33L) |
| C42,55 | 1n5F Polylayer | 2 | (WW23A) |
| C47,51,56,67, 68,75 | 10μF 50V PC Electrolytic | 6 | (FF04E) |
| C53,62 | 10nF Polylayer | 2 | (WW29G) |
| C58 | 2μ2F 100V PC Electrolytic | 1 | (FF02C) |
| C70 | 4μ7F 63V PC Electrolytic | 1 | (FF03D) |
| C74 | 150nF Polylayer | 1 | (WW43W) |
| C81 | 100pF Polystyrene | 1 | (BX28F) |
| TC1,2 | 22pF Trimmer | 2 | (WL70M) |

SEMICONDUCTORS

| | | | |
|---------|--------|---|---------|
| IC1 | MC1496 | 1 | (QH47B) |
| IC2,3,5 | LF353 | 3 | (WQ31J) |
| IC4 | LF351 | 1 | (WQ30H) |
| IC6 | NE571 | 1 | (YY87U) |
| IC7 | LM380 | 1 | (QH40T) |
| D1,2 | 1N4001 | 2 | (QL73Q) |
| TR1 | 3SK88 | 1 | (UH63T) |
| TR2,3 | BF244 | 2 | (QF16S) |

| | | | |
|-----------|---------------|---|---------|
| TR4 | BC179 | 1 | (QB54J) |
| VC1,2,3 | BB212 Varicap | 3 | (YH83E) |
| RG1 | 78M12UC | 1 | (QL29G) |
| RG2 | LM317LZ | 1 | (RA87U) |
| ZD1 | BZY88C4V3 | 1 | (QH05F) |
| ZD2,3,4,8 | BZY88C2V7 | 4 | (QH00A) |
| LD1 | LED Red | 1 | (QY48C) |

MISCELLANEOUS

| | | | |
|-------|-----------------------------|--------|---------|
| S1 | Sub-min Toggle A | 1 | (FH00A) |
| M1 | Signal Strength Meter | 1 | (LB80B) |
| LS1 | 4in. Spkr 8Ω | 1 | (YJ16S) |
| | Pin 2145 | 1 Pkt | (FL24B) |
| | P.C. Board | 1 | (GD78K) |
| LP1 | Wire Bulb 12V | 1 | (WQ13P) |
| SK1,2 | Power Socket 2.5mm | 2 | (HH86T) |
| SK3 | BNC Socket 50Ω | 1 | (HH18U) |
| SK4 | Terminal Post Green 4mm | 1 | (HF05F) |
| SK5 | Socket SO239 | 1 | (BW84F) |
| JK1 | Jack Socket 3.5mm | 1 | (HF82D) |
| JK2 | Switched Jack Socket 1/4in. | 1 | (BW80B) |
| | Vernier Dial Ratio 7.5:1 | 1 | (RX40T) |
| | DIL Socket 8-pin | 4 | (BL17T) |
| | DIL Socket 14-pin | 2 | (BL18U) |
| | DIL Socket 16-pin | 1 | (BL19V) |
| | Minicon Latch Plug 2W | 5 | (RK65V) |
| | Minicon Latch Plug 3W | 4 | (BX96E) |
| | Minicon Latch Plug 4W | 2 | (YW11M) |
| | Minicon Latch Housing 2W | 5 | (HB59P) |
| | Minicon Latch Housing 3W | 4 | (BX97F) |
| | Minicon Latch Housing 4W | 2 | (HB58N) |
| | Minicon Terminal | 3 Pkts | (YW25C) |
| | Kit P Plas | 1 | (WR23A) |
| | Knob K7B | 3 | (YX02C) |
| | Hook-up Wire Black | 1 Pkt | (BL00A) |
| | Hook-up Wire Blue | 1 Pkt | (BL01B) |
| | Hook-up Wire Green | 1 Pkt | (BL04E) |
| | Hook-up Wire Red | 1 Pkt | (BL07H) |
| | Hook-up Wire White | 1 Pkt | (BL09K) |
| | Hook-up Wire Yellow | 1 Pkt | (BL10L) |
| | Zip Wire | 1 Mtr | (XR39N) |
| | Low Noise Screened Cable | 1 Mtr | (XR18U) |
| | Quickstick Pads | 1 Stp | (HB22Y) |
| | Constructor's Guide | 1 | (XH79L) |

OPTIONAL

| | | | |
|--|----------------------------|-------|---------|
| | Power Supply Unregulated | 1 | (YM88G) |
| | Power Plug 2.5mm | 2 | (HH63T) |
| | Fuse Holder In-line | 1 | (RXS1F) |
| | Fuse 1.25in. 1A | 1 | (WR11M) |
| | Trim Tool Set | 1 | (BK34M) |
| | Preset Trim Tool | 1 | (BK49D) |
| | Pot Nut M10 | 1 Pkt | (FP06G) |
| | Pot Washer M10 | 1 Pkt | (FP07H) |
| | Crommet Small | 1 | (FW59P) |
| | Box Pre-drilled | 1 | (YT05F) |
| | Chassis Pre-drilled | 1 | (YT04E) |
| | Pot Mounting Bracket | 1 | (JG47B) |
| | Front Panel Stick-on | 1 | (JG48C) |
| | Back Panel Stick-on | 1 | (JG49D) |
| | Spacer Tapped 6BA x 1/4in. | 1 Pkt | (FD10L) |
| | Bolt 6BA x 1/4in. | 1 Pkt | (BF06G) |
| | Nut 6BA | 1 Pkt | (BF18U) |
| | Shake Washer 6BA | 1 Pkt | (BF26D) |
| | Isobolt M2 x 6mm | 1 Pkt | (JD11M) |
| | Isobolt M3 x 10mm | 1 Pkt | (HY30H) |
| | Isonut M3 | 1 Pkt | (BF58N) |
| | Isoshake M3 | 1 Pkt | (BF44X) |
| | Isobolt M4 x 12mm | 1 Pkt | (BF49D) |
| | Isonut M4 | 1 Pkt | (BF57M) |
| | Isoshake M4 | 1 Pkt | (BF43W) |

The parts listed above, excluding Optional, are available as a kit, but is not shown in our 1988 catalogue:

Order As LM60Q (Direct Conversion Receiver Kit)
Price £69.95

The following items are also available separately:

Box Pre-drilled Order As YT05F Price £17.95

Chassis Pre-drilled Order As YT04E Price £3.95

Pot Mounting Bracket Order As JG47B Price 78p

Front Panel Order As JG48C Price £1.98

Rear Panel Order As JG49D Price 60p

Direct Convrsn Rec PCB Order As GD78K Price £11.95

PARTS LIST TUNING KIT 1

RESISTORS: All 0.6W 1% Metal Film

| | | |
|-----|---|--------|
| 1k | 1 | (M1K) |
| 4k7 | 1 | (M4K7) |
| 22k | 2 | (M22K) |
| 82k | 1 | (M82K) |

CAPACITORS

| | | |
|-------------------|---|---------|
| 27pF Ceramic | 1 | (WX49D) |
| 33pF Ceramic | 4 | (WX50E) |
| 47pF Ceramic | 1 | (WX52G) |
| 100pF Ceramic | 1 | (WX56L) |
| 120pF Ceramic | 4 | (WX57M) |
| 180pF Ceramic | 1 | (WX59P) |
| 22pF Polystyrene | 2 | (BX24B) |
| 100pF Polystyrene | 2 | (BX28F) |

MISCELLANEOUS

| | | |
|---------------------------|---|---------|
| RF Transformer KANK 3333R | 4 | (FD02C) |
|---------------------------|---|---------|

PARTS LIST TUNING KIT 2

RESISTORS: All 0.6W 1% Metal Film

| | | |
|------|---|---------|
| 1k | 1 | (M1K) |
| 2k2 | 1 | (M2K2) |
| 10k | 1 | (M10K) |
| 150k | 1 | (M150K) |
| 180k | 1 | (M180K) |

CAPACITORS

| | | |
|-------------------|---|---------|
| 27pF Ceramic | 1 | (WX49D) |
| 47pF Ceramic | 5 | (WX52G) |
| 120pF Ceramic | 4 | (WX57M) |
| 180pF Ceramic | 1 | (WX59P) |
| 33pF Polystyrene | 2 | (BX25C) |
| 100pF Polystyrene | 2 | (BX28F) |

MISCELLANEOUS

| | | |
|---------------------------|---|---------|
| RF Transformer KANK 3334R | 4 | (FD03D) |
|---------------------------|---|---------|

PARTS LIST TUNING KIT 3

RESISTORS: All 0.6W 1% Metal Film

| | | |
|------|---|---------|
| 1k | 1 | (M1K) |
| 2k2 | 1 | (M2K2) |
| 4k7 | 1 | (M4K7) |
| 180k | 1 | (M180K) |
| 220k | 1 | (M220K) |
| 330k | 1 | (M330K) |

CAPACITORS

| | | |
|-------------------|---|---------|
| 15pF Ceramic | 1 | (WX46A) |
| 27pF Ceramic | 1 | (WX49D) |
| 47pF Ceramic | 4 | (WX52G) |
| 68pF Ceramic | 4 | (WX54J) |
| 100pF Ceramic | 4 | (WX56L) |
| 180pF Ceramic | 1 | (WX59P) |
| 220pF Ceramic | 1 | (WX60Q) |
| 47pF Polystyrene | 2 | (BX26D) |
| 68pF Polystyrene | 2 | (BX27E) |
| 100pF Polystyrene | 2 | (BX28F) |

MISCELLANEOUS

| | | |
|---------------------------|---|---------|
| RF Transformer KANK 3335R | 4 | (FD04E) |
|---------------------------|---|---------|

PARTS LIST TUNING KIT 4

RESISTORS: All 0.6W 1% Metal Film

| | | |
|------|---|---------|
| 1k | 1 | (M1K) |
| 2k2 | 1 | (M2K2) |
| 560k | 1 | (M560K) |

CAPACITORS

| | | |
|------------------|---|---------|
| 15pF Ceramic | 5 | (WX46A) |
| 22pF Ceramic | 4 | (WX48C) |
| 27pF Ceramic | 1 | (WX49D) |
| 56pF Ceramic | 1 | (WX53H) |
| 22pF Polystyrene | 2 | (BX24B) |

MISCELLANEOUS

| | | |
|---------------------------|---|---------|
| RF Transformer KANK 3335R | 4 | (FD04E) |
|---------------------------|---|---------|

All 4 Tuning Kits are available, but are not shown in our 1988 catalogue:

Order As LM61R (Tuning Kit 1) Price £2.95

Order As LM62S (Tuning Kit 2) Price £2.95

Order As LM63T (Tuning Kit 3) Price £2.95

Order As LM64U (Tuning Kit 4) Price £2.95

Want to air your views?

If you have any comments to make about 'Electronics', hints and tips on the projects we have published, points of interest relating to any of the articles we've printed, or you just want to 'air your views' on any electronics related topic, then we would like to hear from you.

Write to the Editor at the address shown below (letters only please, telephone calls will not be accepted), **go on do it NOW!**

The Editor, Maplin Electronics, P.O. Box 3, Rayleigh, Essex SS6 8LR



LOUDSPEAKERS

THE FIRST 111 YEARS

Part 1: The early years

by J.M. Woodgate B.Sc (Eng), A.M.I.E.E., M.A.E.S., M.Inst. S.C.E.

In 1877, patents for moving-coil loudspeakers were issued to E.W. Siemens in Germany, and, almost simultaneously, to Charles Cuttriss and Jerome Redding in the U.S.A. However, this type of loudspeaker had to wait for more than forty-eight years before becoming widely used, and its invention was both preceded and followed by an enormous number of other inventions, some of which actually worked. Nevertheless, the history of the loudspeaker can be considered to begin in the year of this patent. Even today, loudspeakers are one of the most fascinating subjects for the private inventor, and the flow of ingenious (but usually unproven and/or ineffective) devices from dedicated enthusiasts continues unchecked.

Pre-history

Before 1877, most of the eminent physicists of the nineteenth century had investigated, whether purposely or as a side-issue, the production of sound by electrical means. Although it is possible to do this in several ways, almost all the work was based on the electromagnet, invented by Sturgeon, and the dynamo, invented by Michael Faraday. If d.c. is applied to an electromagnet fitted with a springy armature, a most satisfactory clicking sound can be produced as the circuit is made and broken. This, in fact, is the 'Morse sounder', which featured prominently in early Western films. Faraday's early dynamo produced alternating current (before he invented the commutator, which is actually a synchronous mechanical rectifier), and applying alternating current from a hand-turned dynamo to the aforesaid electromagnet CAN produce an unattractive squalling noise. The reason for the emphasis on 'can' is that the actual sound output from different combinations of dynamo and electromagnet varies vastly, and the reasons for this were not well understood at the time. You can repeat this experiment by using a cycle dynamo and a telephone 'receiver' or a pair of headphones, but make sure to connect a 220Ω resistor in series to limit the current, and DON'T WEAR THE HEADPHONES, because the sound may be deafeningly loud. You can extend the

experiment by equipping the receiver or one of the earphones with a conical horn made of rolled-up newspaper. This will make the sound much louder, and this effect has been known from very ancient times. As musical instruments, horns are said to have proved effective weapons of war at the Battle of Jericho (about 1500 BC), and the trumpets of Tutankhamen (1350 BC) have been played and recorded since their rediscovery in 1922.

The Telephone

The slowness of communication by telegraph, using manual Morse, was a considerable spur to the search for a practical telephone, which would convert the human voice into electricity and convert back again at the receiving end of the line. Many inventions were announced before Alexander Graham Bell produced a practical device in 1876. Much of the difficulty, in fact, was concerned with the design of a usable microphone. Both Rie in France and Hughes in England pursued the use of intermittent contacts, which could be made or broken by the vibrations of a diaphragm or other object exposed to the sound waves. Rie used metal contacts, which were unsatisfactory for the purpose but later proved useful as a detector of radio waves, in the 'coherer'. Hughes used carbon, which is very much more suitable, and produced many practical headphones.

Bell, however, used no contacts, his first microphones and receivers were identical and used electromagnetic induction, see Figure 1a. Bell's great contribution, apart from his commercial exploitation of the invention, was to realise that such a device, whether used as a microphone or a receiver, had to have a constant magnetic field, on which, in the receiver, the varying field due to the microphone current was superimposed. It can easily be seen that this constant field is necessary, because if the magnetic field acting on the diaphragm is produced only by the alternating microphone current, the diaphragm will be attracted to the magnet TWICE in each cycle of current, at both the positive and negative peaks. The receiver will thus produce sound at twice the frequency of the incoming

current, i.e. there will be fullwave rectification and 67% second-harmonic distortion, see Figure 1b! A microphone with no constant field will just not work, because there is nothing to generate a current, but it is not so obvious that the continuous field in the receiver not only allows the correct reproduction of the input frequency but also dramatically increases the sensitivity.

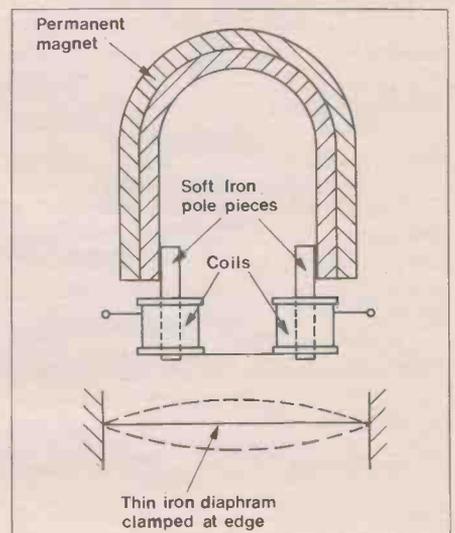


Figure 1a. Bell microphone or receiver with permanent magnet.

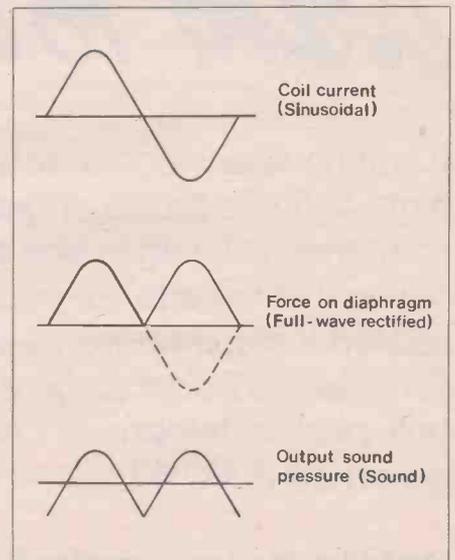


Figure 1b. Distortion produced by non-polarised receiver.

Bell used electromagnets in some early designs of transducer, but later he could make strong permanent magnets, and realised that the elimination of the battery power needed for the electromagnets was highly desirable. However, the best available material for making permanent magnets at that time was glass-hard high-carbon steel, and for the same energy-product, a magnet made of this material has to be far larger than even one made of cobalt steel, which was discovered by Honda and Takei in 1920, so that Bell's microphones and receivers were large and heavy. Their operating principle, however, is the same as that of the diaphragm-type earphone widely used between the World Wars, but the former were much more sensitive; they could be used in a 'sound-powered' system, where the devices were simply connected together, with no battery, and the energy for the system obtained from the sound input.

Later telephones used low-impedance microphones with batteries, and transformer matching to high-impedance receivers. Alternatively (and at that time all alternatives were investigated), a moving-coil receiver could be used with a low impedance microphone. This produced what Sir Oliver Lodge called the 'bellowing telephone', and could be said to be one of the first uses of a loudspeaker. It is used today as a door-answering device. Lodge himself patented a moving-coil loudspeaker in 1898. It must have been sufficiently different from the earlier Siemens device to be patentable. Another early application of the loudspeaker was the relaying of musical concerts to quite large audiences, particularly in France, using Bell-type transducers equipped with horns.

Problems with Bell-type Transducers

The sensitivity of Bell's devices is partly due to the design of their diaphragms. The diaphragm has to be made of ferromagnetic material, and should have a high permeability. But it should also be thin and springy, because it must be positioned very close to the pole-pieces of the magnet system, yet resist the attractive force of the permanent magnet. If the spacing is too small, or the diaphragm too slack, it will collapse in the middle and 'pole', or stick to the pole pieces, causing a great drop in sensitivity and considerable distortion of the sound.

For Bell, the magnetic and mechanical requirements were conflicting, since soft iron had the highest available permeability but not the ideal mechanical properties. Nevertheless, his diaphragms are described as 'soft iron', but are probably not of the purest low-carbon iron (Swedish iron). The thickness, temper and clamping of the edge were arranged, by accident or,



Photo 1a. Sterling 'Baby' horn with diaphragm transducer. About 1924.

most probably, design, to give a high-Q resonance at about 900Hz. This increased the effective sensitivity for speech very considerably. However, the small spacing of the diaphragm from the pole-pieces limited the permissible diaphragm movement (usually termed 'excursion'), and therefore the loudness of the sound produced when the device was used as a loudspeaker. In addition, the mid-band resonance gave an unpleasant coloured and strident sound quality to the reproduction of music, especially as the short, often conical, horn to which it was attached resonated in the same frequency range and would not reproduce lower frequencies properly (Photos 1a, 1b).

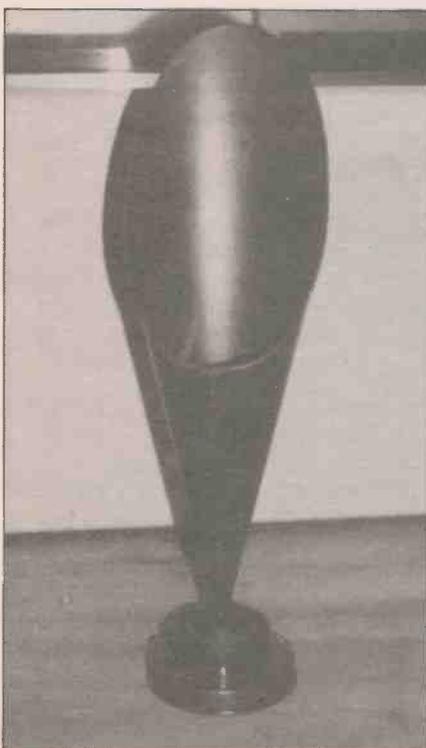


Photo 1b. Early S.G. Brown conical-horn loudspeaker.

The Cantilever Reed-armature Transducer

Based on a 1910 design for an earphone, by S.G. Brown, this device has the advantage of considerable simplicity and robustness, see Figure 2. Unlike the Bell receiver, it can drive a large, preferably conical, diaphragm directly, thus needing no horn (Photo 2a, 2b). Indeed, the mass of the diaphragm is highly desirable, as it lowers the resonant frequency of the reed. Millions of loudspeakers using this principle were made in the early days of broadcasting, and the driver mechanism was also used as a cutting-head for early electrical recordings on (analogue!) disc. Loudspeaker drivers were fitted with a screw adjustment of the spacing between the reed and the pole-pieces, which acts as a very effective volume control, much better than the proverbial sock which was stuffed down a horn to quieten it. However, too close adjustment of the reed results in poling, and the excursion is limited. In addition, as with the Bell transducer, the system is inherently non-linear. The pull on the reed increases when the reed moves towards the pole pieces, and decreases as it moves away, whereas it should be constant. To a certain extent this can be corrected by adjusting the geometry of the system, but it is possible to reduce the non-linearity by modifying the design more fundamentally, leading to the next two variants described below.

A loudspeaker with a large cone radiator can have its low-frequency response improved if a flat baffle-board or a cabinet (now usually called an enclosure) is added, see Figure 3, so that the sound radiated from one side of the cone is separated from the reverse-phase

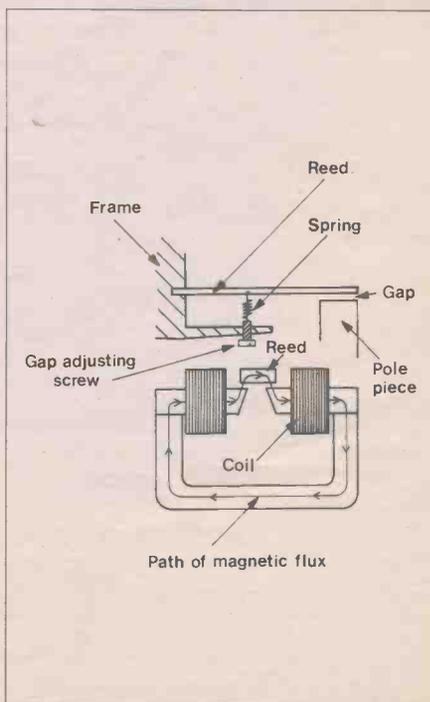


Figure 2. Reed armature driver.

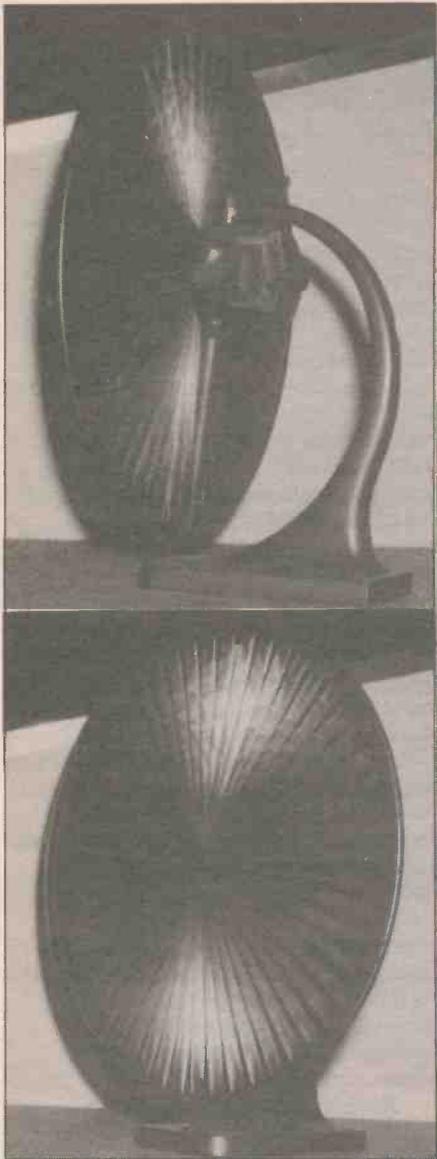


Photo 2a/b. Sterling 'Primax' pleated-diaphragm reed-driven loudspeaker. Contemporary sectioned exhibition model (1927). Many Sterling products were made under licence from The Gramophone Company Ltd., (later to become EMI).

radiation from the other side. While the effect of a very large flat baffle, and those of some other simple geometric shapes, such as a sphere, can be calculated, the effects of a rectangular box are quite complex, especially if the box is partly open at the back, as in the table radios and extension loudspeakers widely marketed in the mid-1920's and for the next forty years (Photo 3). Enclosure design has brought forth more oddities and weird theories than practically any other area of audio engineering. Successful theoretical analyses of the low-frequency response of some well-defined types of driver and enclosure combination were published by A.N. Thiele and R.H. Small in the 1970's.

The Inductor-dynamic Transducer

Developed specifically for loudspeaker applications, this device overcomes a major problem of the reed-armature mechanism, the inability to reproduce low frequencies unless a very low sensitivity is accepted. This is because the spring element of the reed has to be stiff enough to resist the steady pull due to the permanent magnet. This gives a high resonant frequency unless the combined mass of the reed and cone is made large, in which case the device requires a high power input, i.e. the sensitivity is low.

In the inductor-dynamic device (Figure 4), the direct pull and the alternating pull are arranged to be at right-angles, and the direct pull is, in addition, substantially balanced out. The residual direct pull is applied to the spring elements, of which there are two, in such a direction as to stretch them, whereas the alternating pull bends them.



Photo 3. Alphon 4-valve (tube) portable (!) radio with Celestion reed loudspeaker (about

A simple flat spring is very much more difficult to stretch than to bend, so bending can be made easy without risk of poling. Also, the non-linearity is approximately balanced out, if the pole-piece tips are carefully shaped, because the reduction of force on one armature as it moves away from its pole-pieces is compensated by an increasing force on the other armature. This is an example of a push-pull mechanical system, which, like its electrical analogue, is substantially free of even-order non-linearity. With soft springs and a 25cm paper cone having a leather surround at its outer edge, a resonant frequency in the region of 70Hz could be obtained, whereas the resonance of a reed-armature loudspeaker might be above 200Hz. In addition, the inductor-dynamic driver cannot pole, so the amplitude of movement is limited only by the tolerable non-linearity, and can be increased by appropriate armature and pole-tip design. Thus the quality of music reproduction from an inductor-dynamic loudspeaker could be much better than that from a reed-armature type.

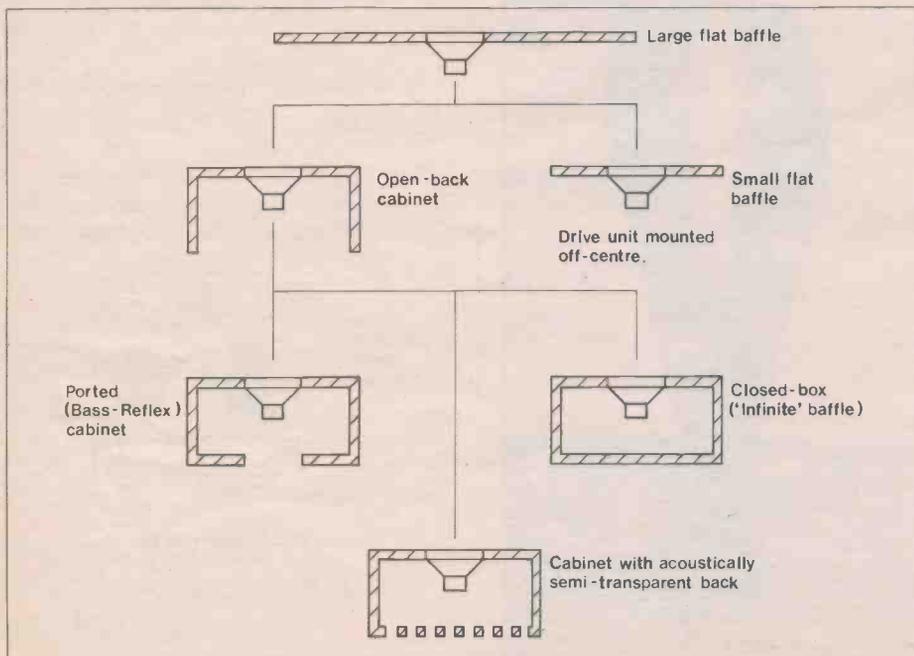


Figure 3. Some types of baffle for direct-radiator loudspeakers (modified and extended from Jordan).

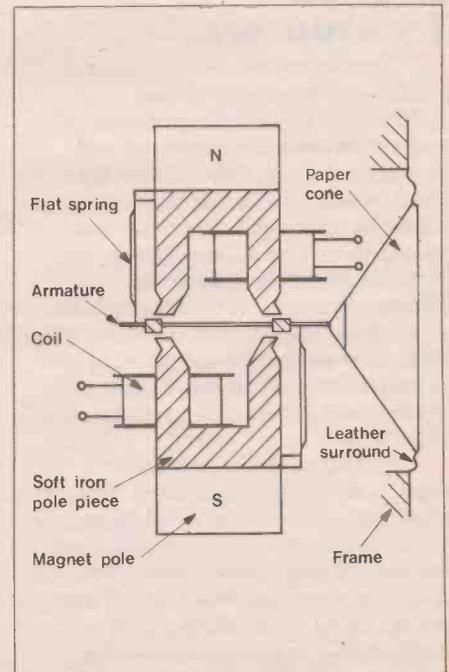


Figure 4. Inductor-dynamic loudspeaker.

The Balanced-armature Driver

This is another way of improving the linearity of the net driving force on the armature system. With the rocking armature (Figure 5) in the exact centre position, there is no net direct pull on it, but it is unstable in this position, like a horizontal see-saw. Consequently, a spring has to be added to prevent poling. This is a pity, because the effective mass of the armature is quite small, so the spring results in a high resonant frequency unless a heavy cone is added. Only the alternating component of the magnetic field passes through the armature, which is therefore not driven close to saturation by the permanent field. The permeability of the armature can therefore be high, with a consequent high sensitivity. This is another push-pull system, and linearity can be similar to that of the inductor-dynamic device. The balanced-armature mechanism may be rather easier to construct, although play in the armature pivot must be prevented.

Electrostatic Loudspeakers

The electrostatic or capacitor microphone predates Bell's telephone by some years, but, because of its high impedance, it could not form part of a practical telephone at that time. Indeed, it is only now, a century later, that this is practicable. The early microphone could also be used as a loudspeaker but required high operating voltages (upwards of 600V) and was not very sensitive. It was not until the end of the 1920's that new materials, such as aluminium foil and thermosetting plastics (Bakelite), became available and new patents for 'condenser loudspeakers' began to appear, in the names of V.F. Greaves *et al.*, C. Kyle, P.E. Edelman and H. Vogt. Greaves, Kyle and their colleagues produced a single-sided unit, see Figure 6a, while Vogt produced a unit with two perforated fixed plates enclosing a stretched moving plate, see Figure 6b. This unit therefore resembled the much later and considerably more successful 'Quad Electrostatic', but did not share the latter's crucial constant-charge drive, and was therefore not very linear in amplitude response, although the frequency response was said to be fairly smooth. The Kyle unit was also said to have a frequency response extending from 100Hz to 10kHz, which was not flat but could be equalised fairly easily. Being single-sided, however, the linearity of the device would be suspect.

Piezo-electric Loudspeakers

The term 'piezo-electric' refers to the property of certain materials to deform mechanically when an electric field is applied, and vice versa to generate a voltage when mechanically stressed. In

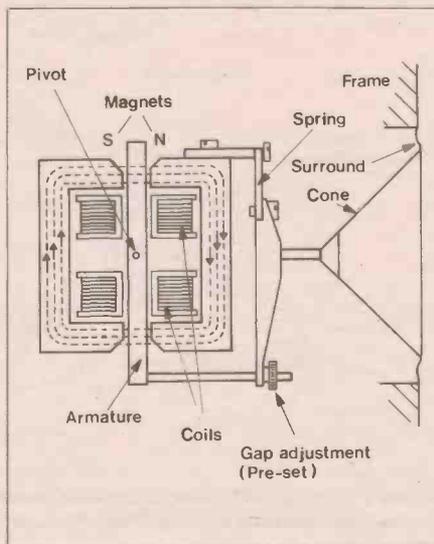


Figure 5. Balanced-armature loudspeaker. Dotted lines show magnetic flux path with no coil current. There is no flux in the armature.

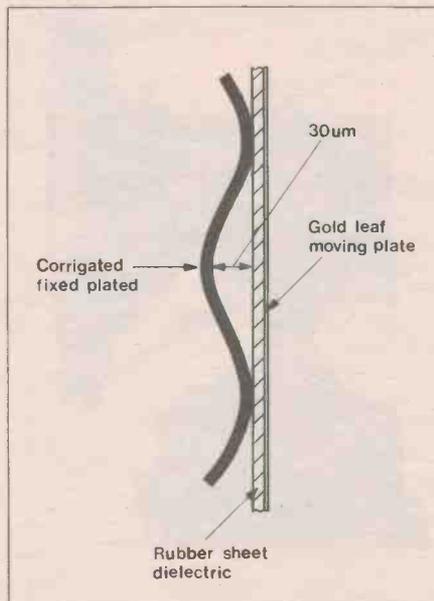


Figure 6a. Modified cross-section of Kyle single-sided electrostatic loudspeaker.

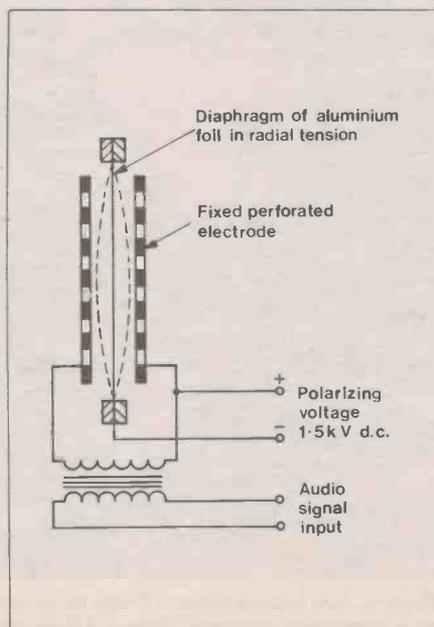


Figure 6b. Cross-section of Vogt double-sided electrostatic loudspeaker.

the early 1930's, loudspeakers, mostly for reproducing frequencies above 5kHz, were described by S. Ballantine, C.B. Sawyer and F. Willms. These used crystals of Rochelle salt (sodium potassium dihydrogen tartrate) as the piezo-electric material. This is very difficult to work with, because it attracts moisture from the air and dissolves in it. Quartz or tourmaline would be much more stable but are much too insensitive for use in loudspeakers. The problems of sealing the crystals against moisture were not solved and the principle was abandoned until the 1950's, when it was briefly revived. New ceramic materials developed since 1970 have allowed the production of reliable piezo-electric high-frequency drivers, but the extension to lower frequencies is difficult. Linearity can be poor, and the capacitive input impedance of the device is not easy to drive.

Friction-driven Loudspeakers

In attempts to produce very sensitive loudspeakers, and/or very high sound levels, electromechanical devices were produced in which the friction between a pad, connected to a conical diaphragm, and a rotating disc or roller was varied electrically. This could be done either by varying directly the force between the pad and the moving part, or by impregnating the moving part (a porous cylinder) with a mixture of chemicals which gave off gas bubbles when electrolysed by the applied electrical signal. Such devices were described by Thomas Alva Edison, Johnson Rahbek and S.G. Brown, but were not very reliable and did not give very good or consistent sound quality. The signal-to-noise ratio was also poor, because the friction introduced noise in the absence of an input signal.

Air-operated Loudspeakers

Another high-power system, developed by Creed and Co. in the 1930's, used a supply of compressed air, the flow of which was controlled by an electrically-operated vane valve. Apart from distortion due to deficiencies in the valve operation, there was considerable non-linearity due to the sound pressure variations at the horn throat being far from negligible compared with atmospheric pressure. This problem also occurs with modern high-power horn loudspeakers, which use moving-coil drivers.

The Moving-coil Driver and Direct-radiator Loudspeaker

By far the most widely used type of driver, the moving-coil system (Figure 7) is surprisingly subtle in its mode of

operation, and it is this which confused the early workers and was partly responsible for the long delay in its exploitation. The other factor is that the construction of a reliable device depends on the use of stable flexible materials and adhesives, neither of which were easily obtained before the 1920's.

The moving coil and cone assembly can be made very light. If provided with a very soft suspension (Photo 4a, 4b and 4c), the result may be a very large coil excursion under some conditions, causing the destruction of the coil by collision with the magnet structure, or by being forced out of the magnet system. On the other hand, a stiff suspension will result in a very high-Q resonance, giving a squawky or strident sound, and low sensitivity except at the resonant frequency. The major contribution of Rice and Kellogg was not the breakfast cereal but the realisation of how to make a moving-coil loudspeaker with a substantially flat frequency response. This involves three steps:

(a) Adjusting the mass of the coil and cone, and the compliance of the suspension, so that they resonate below, or at the lower end of, the working frequency range.

(b) Adjusting the amount of mechanical loss (mainly in the suspension and surround), and the electrical damping, which depends on the output impedance of the driving amplifier and the field strength of the magnet system, so that the main resonance is reasonably well-damped. (Rice and Kellogg may not have fully analysed this: Theile and Small provided a full explanation and quantified the factors involved some 25 years later.)

(c) Allowing, or even encouraging, the cone to cease to vibrate in one piece above a certain frequency, but not to vibrate in sections in several undesirable ways.

Curiously, Siemens' original patent refers to a conical diaphragm with an exponential flare: this shape encourages the correct form of cone break-up and has been used in some of the nicest-sounding commercial (as opposed to high-fidelity, where such simple criteria are inadequate) loudspeakers.

In addition, Rice and Kellogg showed that the diaphragm should be small compared with the wavelength of the sound to be radiated (unless a pronounced directional effect is required), and indicated the need for a baffle or enclosure to prevent destructive interference between front and rear radiation at low frequencies.

Until the late 1930's, permanent magnets were not very suitable for use in moving-coil drivers. The present author remembers dismembering an early example, from a battery radio, in his youth: the magnet was forged from about 30cm of 75mm x 25mm steel bar, rolled into a flattened hoop, welded and fully hardened. It was very heavy indeed, yet not a very strong magnet. The earlier Rice-Kellogg products, made by GE in

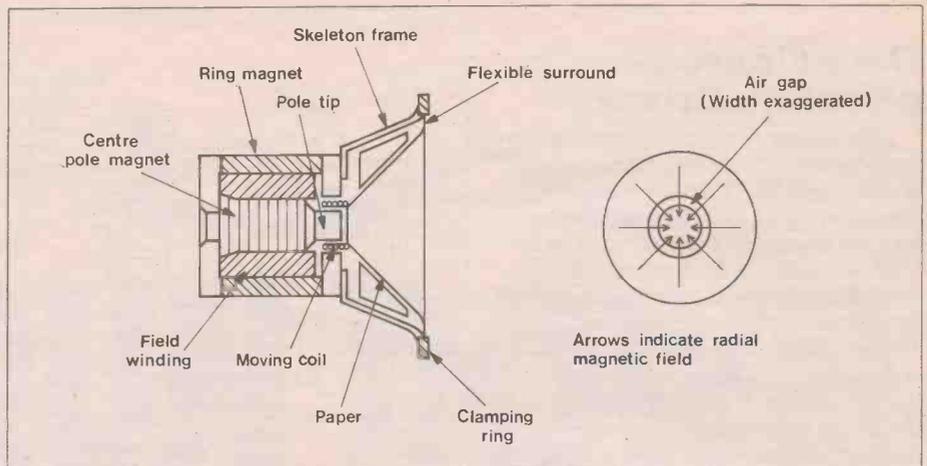


Figure 7. Moving-coil loudspeaker with metal magnet or electromagnet. The two permanent magnets and the field coil are alternatives: whichever magnet is not fitted is replaced by soft iron.



Photo 4a.



Photo 4b.

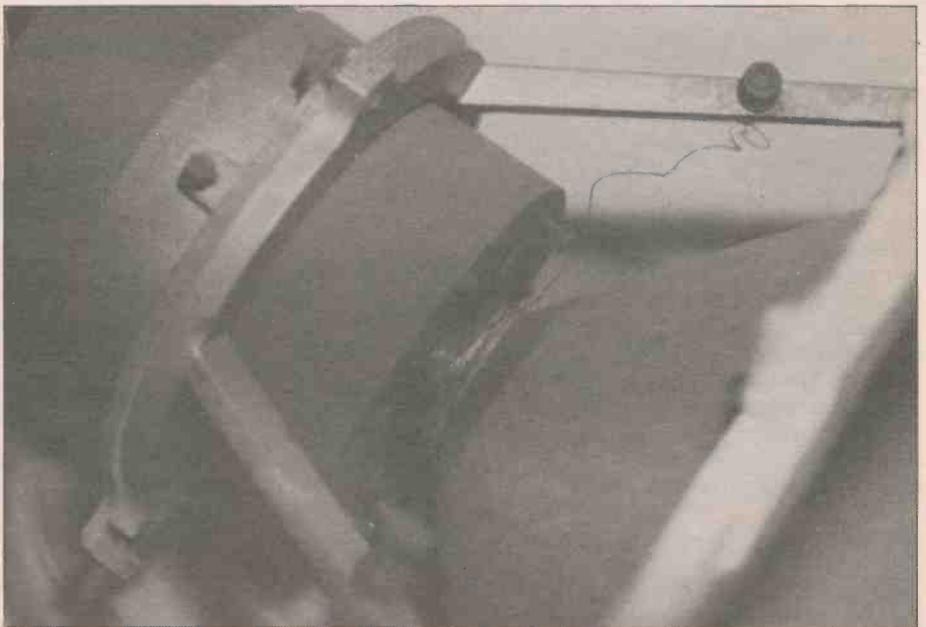


Photo 4a, b, c. Bakers Selhurst Radio 12" moving-coil direct-radiator loudspeaker with a high-impedance voice-coil. This unit has a leather surround and the suspension is formed by two loops of sewing-thread. The resonant frequency is very low, but so is the maximum permissible input.

the USA and marketed in Britain by BTH (Photos 5a, 5b, 5c and 5d), used electromagnets, as did most of the units made at that time. When used in a radio receiver, the field coil served as the smoothing inductor in the power supply. Considerable current at harmonics of the mains supply frequency also flowed through the coil: the reservoir capacitor was only $4\mu\text{F}$ or $8\mu\text{F}$, and the smoothing capacitor, following the inductor, was of the same value. This current would have produced a loud hum from the loudspeaker, so another coil of a few tens of turns was wound next to the field coil and connected in series with the voice-coil. This 'hum-bucking' coil inserted a voltage into the voice-coil circuit which was intended to cancel the effect of the hum current in the field. It did work, but the coil had to be specially designed for each radio, since the number of turns depended on the power supply capacitor values, the anode current drawn by the valves (tubes) and the output source impedance of the output stage.

Flat-diaphragm Moving-coil Loudspeakers

There were some researchers who did not like cones: certainly they are far from ideal, but all other practical shapes have their own disadvantages, which seem to be worse than those of the cone. One of the proponents of the flat diaphragm was J.D. Midgley, who patented several arrangements, including the use of a circular, stretched aluminium foil diaphragm which was driven by a moving coil mounted off-centre (Photo 6a, 6b). The off-centre drive helped to break up the inevitable resonances and spread them out in the frequency domain. Another type of flat radiator was the German Blatthaller (sheet sounder), in which a large corrugated metal sheet (up to several tens of centimetres square) was driven all over its surface by a copper conductor fixed to it at right angles and immersed in the field of a powerful electromagnet. It

was very large, very heavy, and very loud.

Horn-loaded Moving-coil Loudspeakers

Moving-coil drive units were not only used in direct radiators. The talking cinema and the growing sound-reinforcement industry both demanded high sound levels and high quality. It was relatively more difficult in those days to provide more amplifier power than to improve the sensitivity of the loudspeakers. E.C. Wentz and A.L. Thuras (the inventor of the bass-reflex principle) described in 1928 the Western Electric WE555 horn-loaded moving-coil unit. The coil was made of edge-wound aluminium tape, and, whereas most loudspeakers are of the order of 1% efficient (sound power out divided by electrical power in), this unit was about 50% efficient! Modern horn units approach the same performance (with



Photo 5a. B.T.H. Rice-Kellogg 12" energised-field loudspeaker 1931.



Photo 5b. A similar unit from 1929, in the original cabinet with its field power-supply.



Photo 5c. A 12" permanent-magnet unit from the same stable (1931). The slot, one of three in the magnet pot, is not for displaying the interior but a feature of the design.

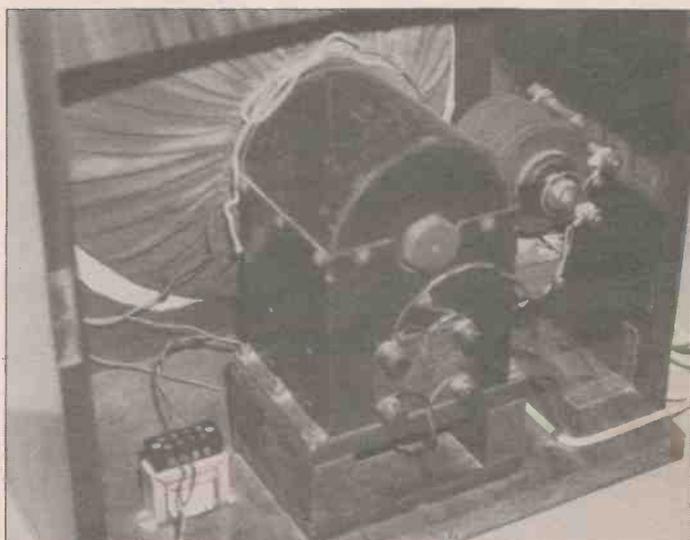


Photo 5d. Rear view of the 1929 unit, showing the mains transformer and copper-oxide rectifier. The transformer on the left is a Wharfedale WMT 1, for $3\Omega:15\Omega$ matching. Many thousands of these were made, from the 1930's until relatively recently. This example is a late model, for it is branded 'Rank-Wharfedale'.

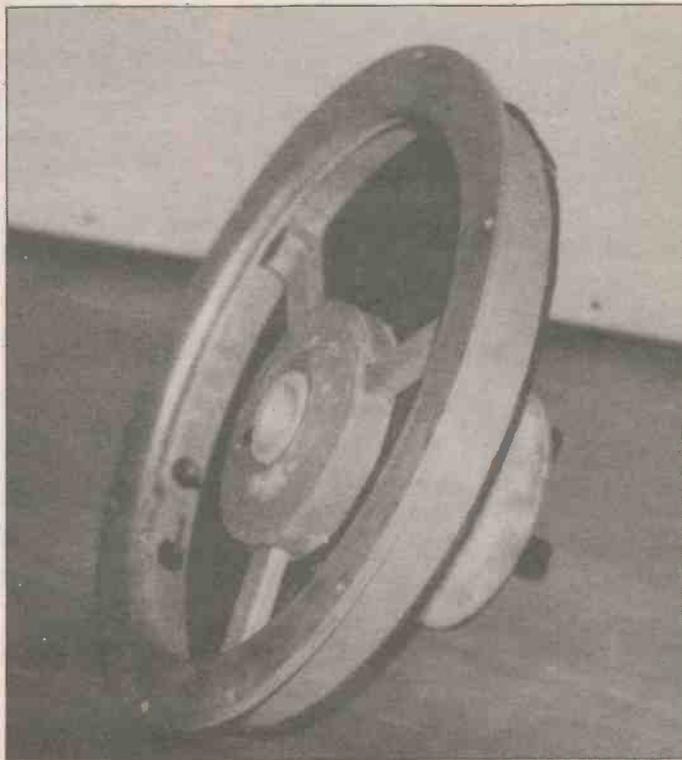
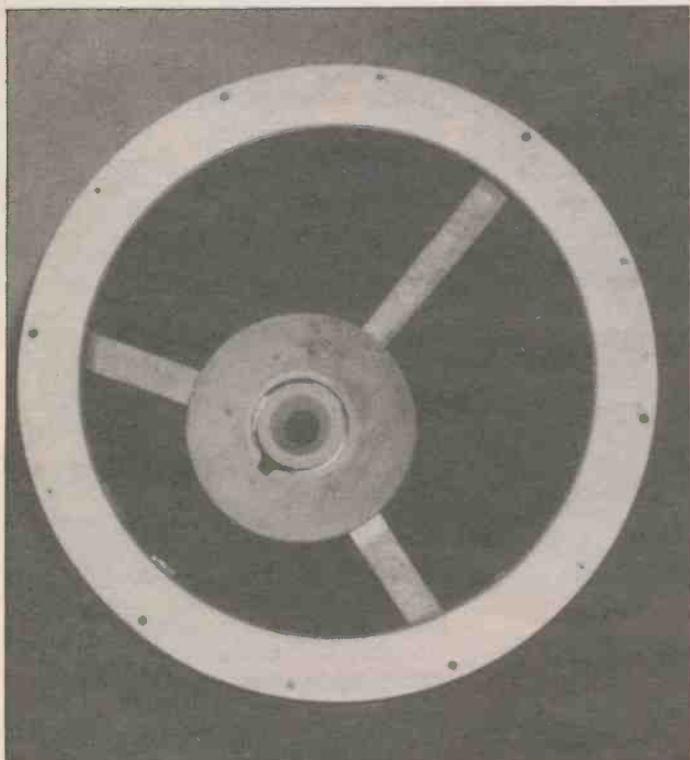


Photo 6a, b. Two views of the chassis of a Midgley flat-diaphragm moving-coil dipole-radiator loudspeaker. Note the off-centre drive, intended to minimise spurious resonances in the thin aluminium diaphragm (absent from this example).

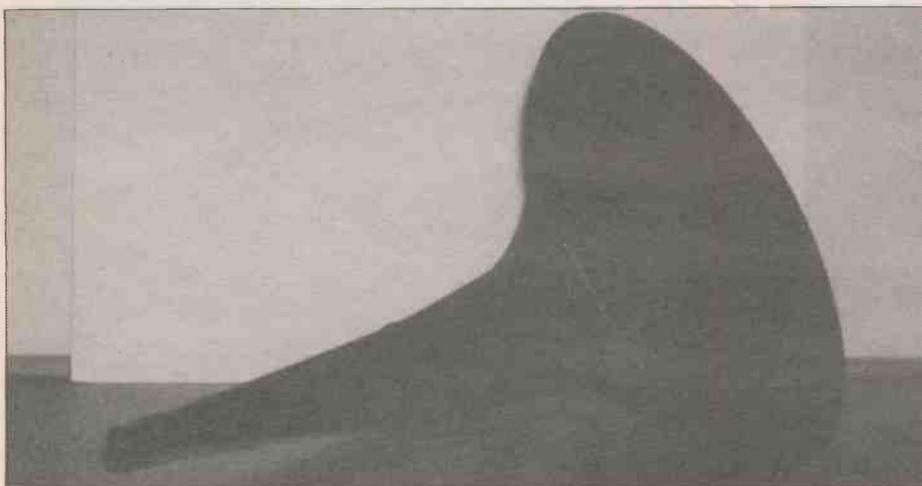


Photo 7. A curved-axis exponential horn, from a Magnavox horn-loaded moving unit of uncertain (but very early) date.

less size and mass and less relative cost) but few indeed exceed it. Mind you, the horn was 10.8 m long! A cross-section of a horn-loaded moving-coil pressure unit is shown in Figure 8. Photo 7 shows a horn from a Magnavox horn-loaded moving-coil unit.

One of the more unusual devices of the day was the 'Crystavox' loudspeaker designed by S.G. Brown, which incorporated a 'microphonic amplifier' (a term with quite a different meaning today!). In photos 8a and 8b, the unit in front of the base of the horn is the amplifier, with its metal cover removed. At the left of the assembly is a reed mechanism which is directly mechanically-coupled to a small carbon microphone cell on the right. This is

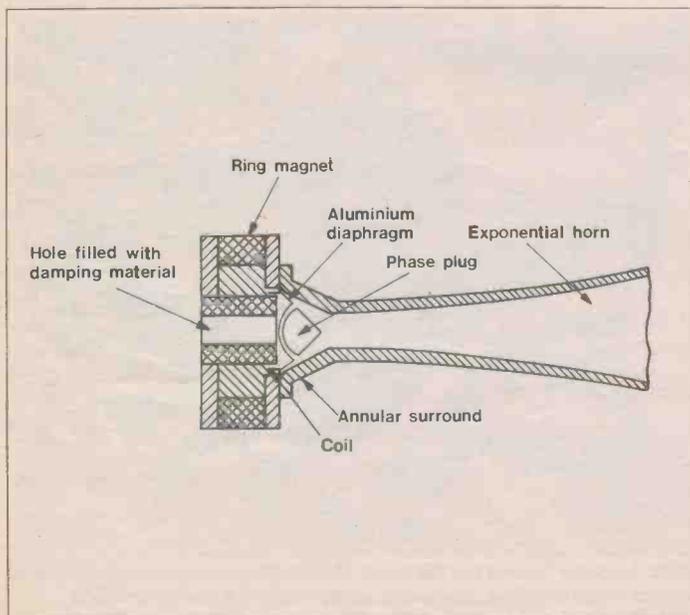


Figure 8. Horn-loaded moving-coil loudspeaker. Early examples used an electromagnet field.



Photo 8a. The 'Crystavox' incorporating a 'microphone amplifier'.

connected in series with an external 3V battery and the low-impedance reed mechanism at the base of the horn. It worked well, and the principle was known and used experimentally before 1900 and certainly long before the triode valve was available as an amplifier.

The End of the Beginning


The start of World War II in 1939 could be regarded as the end of the first stage of the loudspeaker story. Loudspeakers were being produced by the million for mass markets. New magnet materials, iron alloys containing cobalt, nickel and aluminium, and new methods of heat-treatment, were being introduced which would reduce size, weight and, in spite of the exotic metals used in the alloys, cost. The performance of a loudspeaker design could, to a certain extent, be predicted, once the characteristics of the cone to be used had been measured. Cone design was to remain a black art for another thirty years or so, and unpleasant (and even, occasionally, pleasant) surprises still lie in wait for the innocent designer.

Acknowledgement

The assistance of Mr. G.M. Wheeldon of the Science Museum and Ms. J. Marshal of the Science Museum Library is gratefully acknowledged.



Photo 8b. Another view of the 'Crystavox'.

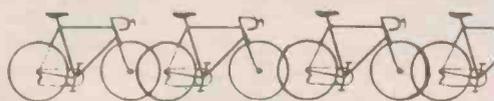

Maplin's Big Heart

By J. Rose

In the last issue I told you about the annual London to Brighton bicycle ride in aid of the British Heart Foundation, this ride has now taken place and was thoroughly enjoyed by all! Over 35,000 cyclists suffered the 56 mile journey with smiles on their faces, joy in their hearts, blisters on their feet and saddle sores on their! The event raised an estimated £1,000,000 which will be used to fund the purchase of much needed equipment and be used for invaluable research work. Maplin contributed over £200 to the Foundation and I would like to thank the staff of the Hammersmith and Birmingham shops particularly and those customers who came forward and donated. Money was also raised at the Head Office in Hadleigh, Essex and my gratitude goes to Hazel and Beryl for their gentle bullying! It is hoped that this will become a Maplin tradition with more support building up each year, as this is a very worthy cause and, let's face it, it only costs Dave Kirk and myself a few aches and pains, not to mention those saddle sores!




Bob's MINI-CIRCUITS

From Robert Penfold

Capacitance Meter Adaptor

A capacitance meter is certainly one of the more useful items of equipment for the home constructor, but even home built instruments tend to be rather expensive. Unfortunately, few multimeters seem to include any capacitance measuring ranges. A low cost but very effective method of capacitance measurement is to use an add-on circuit for an existing multimeter. This avoids the main expense incurred when building a stand-alone unit, which is the cost of the digital display circuit or a good quality panel meter. The capacitance meter add-on described here is primarily intended for operation with a digital multimeter switched to its 1.999 volt range, but it should work quite well with an analogue multimeter having a sensitivity of 20k/volt or more, and a D.C. voltage range of 1 to 2.5 volts full scale. It has four ranges with full scale values (when used with a digital multimeter) of 1.999nF, 19.99nF, 199.9nF, and 1.999 μ F full scale. High value capacitors are beyond the capabilities of this circuit, but its range is quite respectable for such a simple and inexpensive circuit. Anyway, high value capacitors can usually be given a rough check with a multimeter set to a resistance range. The charge current of the capacitor (or lack of it) will be indicated by the meter, and will show whether or not it is basically functional. At the low end of its range, this unit can check capacitors of values down to a few picofarads.

The circuit is based on two 555 timers (IC1 and IC2) which are used in the astable and monostable modes respectively. IC1 provides a clock signal which is a series of very brief negative pulses. These trigger IC2 which provides output pulses of a duration that is controlled by the values of the switched resistors (R2 to R5) and the capacitor under test. The switched resistors provide the unit with its four measuring ranges. With the frequency of the output signal at a fixed rate, the average output voltage of the monostable depends on the duration of the output

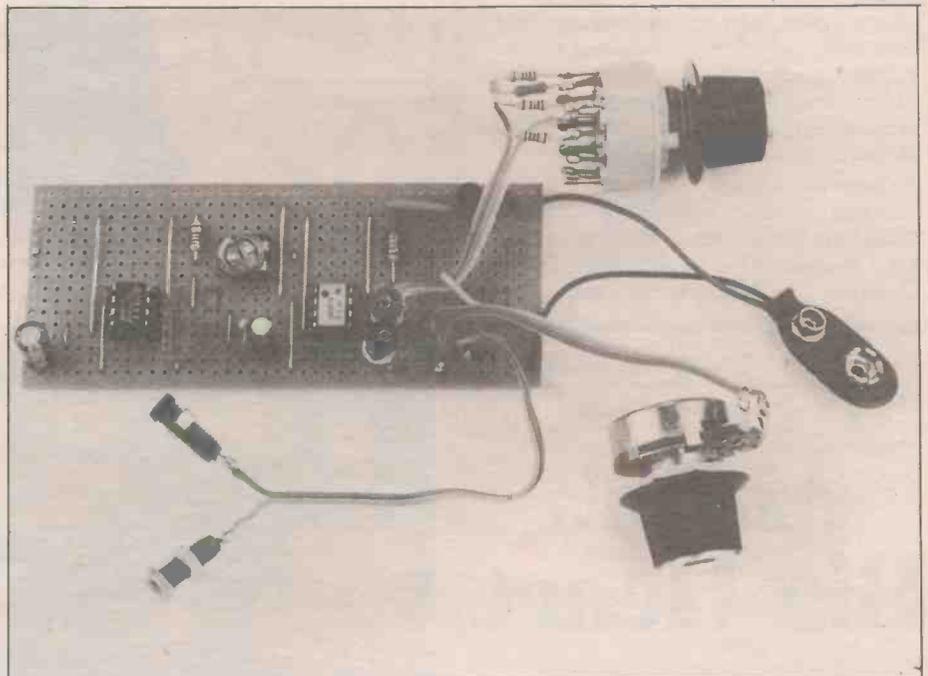

Capacitance Meter Adaptor.

pulses, and is proportional to this duration. This is in turn proportional to the value of the test capacitor. The circuit therefore provides the required capacitance to voltage conversion. RV1 is used to calibrate the unit. R2 to R5 have a tolerance of 1% so that consistent results are obtained from one range to the next. Most multimeters have internal smoothing components, but R6 and C3 will smooth the output to a low ripple D.C. signal in the absence of any built-in smoothing.


There is a problem with simple capacitance measuring circuits of this type in that there is a certain amount of stray capacitance in the monostable which is in parallel with the test capacitor, and adversely affects accuracy. The problem is insignificant on the higher ranges, but can be quite severe on the lower ranges. In this case the problem is eased by the use of the TLC555CP for IC1 and IC2. This has a higher switching speed and lower internal capacitance

than the standard 555, and a quiescent reading of only about 20pF is obtained. The problem is further eased by RV2, which provides a variable offset voltage that can be used to zero the quiescent reading. This enables the unit to measure very low value capacitors.

A stable 5 volt supply is needed, and this is obtained from a 9 volt battery via monolithic voltage regulator IC3. The current consumption of the circuit is only about 4 milliamps.

Reasonable care must be taken with the layout of any circuit of this type, so that the stray capacitance in parallel with test components is kept as low as possible. I originally mounted R2 to R5 on the circuit board, but this boosted the stray capacitance from about 20pF to 80pF. It is much better to mount these resistors on S1. The unit can be calibrated on any range, but for best accuracy use a close tolerance capacitor that has a value which is around 50% to 100% of the full scale value of the


range on which the unit will be calibrated. Zero the unit using RV2 prior to connecting the test component, and then adjust RV1 for the correct reading on the multimeter. Note that changing ranges will require some slight readjustment of RV2 in order to re-zero the unit. Note also that the decimal point of the display is in the wrong position on the middle two ranges, but you will soon get used to converting readings into true capacitance values. The unit is quite accurate, but when testing capacitors you must remember to make allowances for small deficiencies in the accuracy of the unit, and the tolerances of the test components (which can often be some 20%, or even more for ceramic types). As with any capacitance meter, do not connect charged capacitors to it! Always discharge test capacitors before connecting them to the unit.

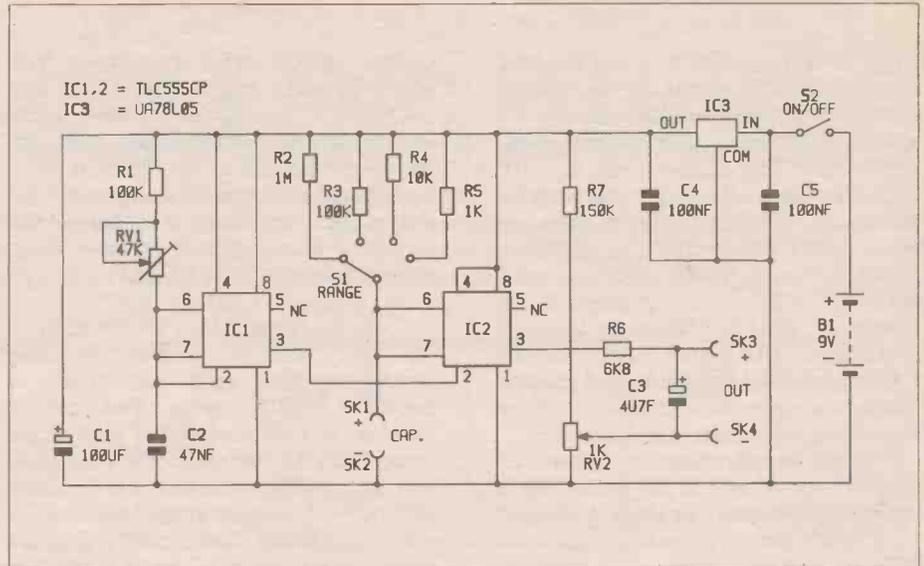

Capacitance Meter Adaptor circuit.

MIDI Thru Box

The standard method of driving pieces of MIDI equipment from a control device is the so-called 'chain' system of connection. This has the 'OUT' socket of the controller connected to the 'IN' socket on one of the other pieces of equipment, and then the 'THRU' socket of this device connects to the 'IN' socket of the next piece of equipment, and so on. In theory, any number of instruments, etc. can be connected together by wiring the 'THRU' socket of one instrument to the 'IN' socket of the next one in the 'chain'. In practice this is not always possible though. There can be problems with what are often called 'delays', but which are more probably problems with smearing of the signal that compromise reliability. At a more basic level, many items of MIDI equipment (especially keyboard instruments) simply do not have a MIDI 'THRU' port, and cannot be used with this method of connection. Actually, if only one instrument lacks a 'THRU' socket it is possible to use the 'chain' system, provided this instrument is placed at the end of the 'chain'. If more than one instrument lacks a 'THRU' port, then the 'star' system must be used.

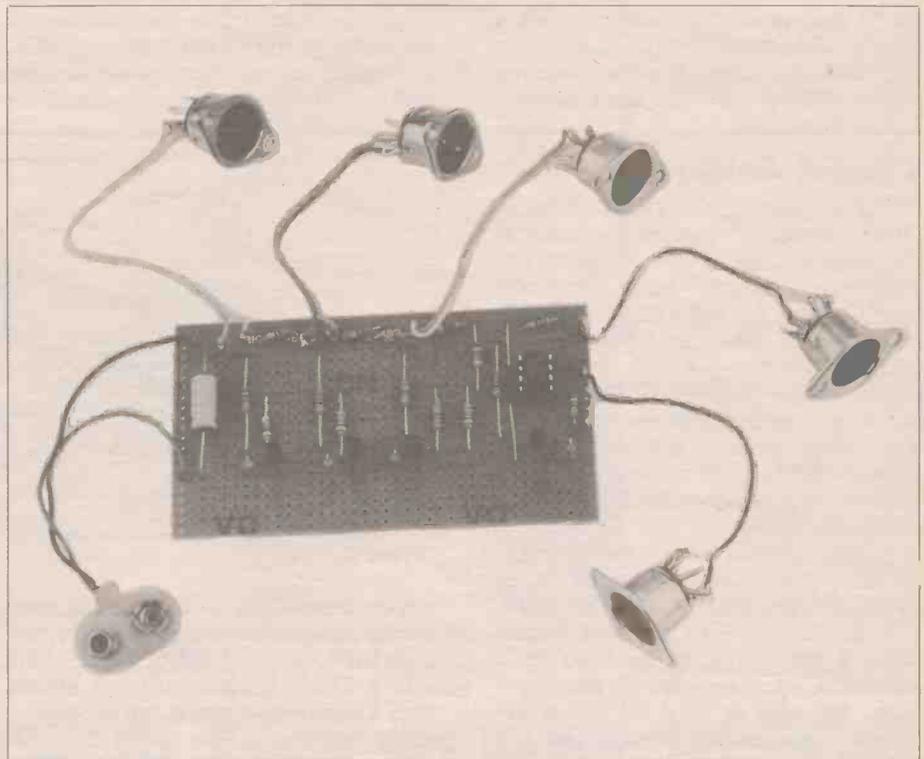

MIDI 'thru' stripboard layout.

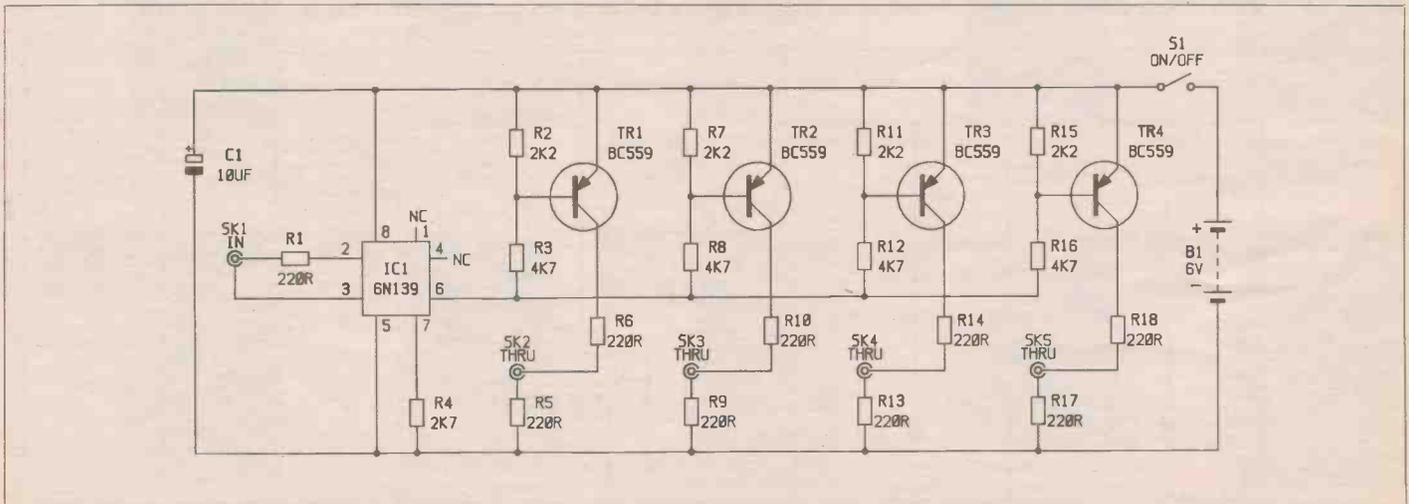


Figure 1. The MIDI 'THRU' circuit.

It is only possible to adopt the 'star' system if the MIDI controller has multiple outputs, or a 'THRU' box is included in the system. This method of connection relies on the controlling device having an 'OUT' socket for each MIDI input that must be driven. A 'THRU' box simply takes the signal from a MIDI output and splits it to give a number of 'THRU' outputs to drive the inputs of the other equipment in the system. A 'THRU' box cannot be a passive device as a MIDI output only provides a drive current of 5 milliamps, and splitting this between several inputs would give an insufficient drive current for each one.

In this circuit, shown in Figure 1, an opto-isolator is used at the input. This is not strictly necessary as there is no need for a 'THRU' box to provide isolation, but MIDI outputs are designed to drive an opto-isolator, and this method ensures reliable operation with any output that properly meets the MIDI standard. The 6N139 used in the IC1 position is not a simple LED/transistor type, but on the output side actually has a photo-diode, an emitter follower transistor, and a common

emitter output stage. This gives high efficiency and fast operating speed. The circuit can comfortably accommodate MIDI's fairly high baud rate of 31250 baud, R4 ensures that the emitter follower stage operates at a reasonable current and that the device achieves a suitable fast switching speed. The 5 milliamp drive current is set partly by R1, and partly by a series resistor in the drive circuit.

On the output side of the circuit there are four common emitter switching transistors, with each one driving a separate 'THRU' socket. Two current limiting resistors are used in each output circuit, and this two resistor system gives better protection to the circuit in the event of a system being incorrectly wired up, or a fault occurring. Four output stages are shown in the circuit diagram, but IC1 is capable of driving several more output stages if necessary. Power is provided by a 6 volt battery (such as four HP7 size cells in a plastic holder). The quiescent current consumption will probably be negligible, but under worse case conditions the average current drain could be as much as

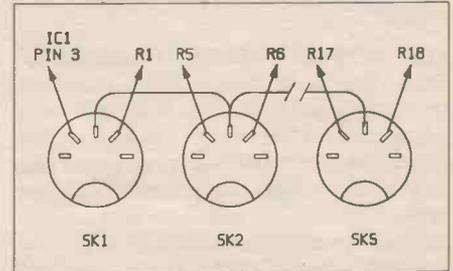


Figure 2. Socket connections.


2.5 milliamps per output that is actually used.

The standard MIDI connectors are 5 way (180 degree) DIN plugs and sockets. Provided you use the appropriate type of socket connected in the manner outlined in Figure 2, the 'THRU' box can be wired into the system using standard MIDI leads. If you make up your own leads, twin screened cable is required. Pins 2, 4, and 5 on one plug are connected to the corresponding pins of the other plug, with the screen carrying the connection between the two pin 2s. Note that some audio 5-way DIN leads use cross coupling and are unsuitable for MIDI applications.

Crystal Calibrator

Some years ago a crystal calibrator offering a wide range of fundamental frequencies was a costly piece of equipment. Things have gradually changed, with the more popular crystals now costing what is in real terms probably less than one tenth of their cost ten or more years ago. Also, logic integrated circuits are now at virtually give away prices, and with digital dividers it is possible to generate a wide range of output frequencies from a single crystal oscillator.


This unit has a fundamental output at 4MHz, with additional outputs at 2MHz, 1MHz, 500kHz, 250kHz, 100kHz, 50kHz, and 25kHz. This may seem of limited value if the unit is to be used as a calibration oscillator for a shortwave radio, but bear in mind that these are only the fundamental signals, and that harmonics are available at frequencies to beyond 30MHz. Thus, for example, the 1MHz output also provides signals at 2MHz, 3MHz, 4MHz, 5MHz and so on. The

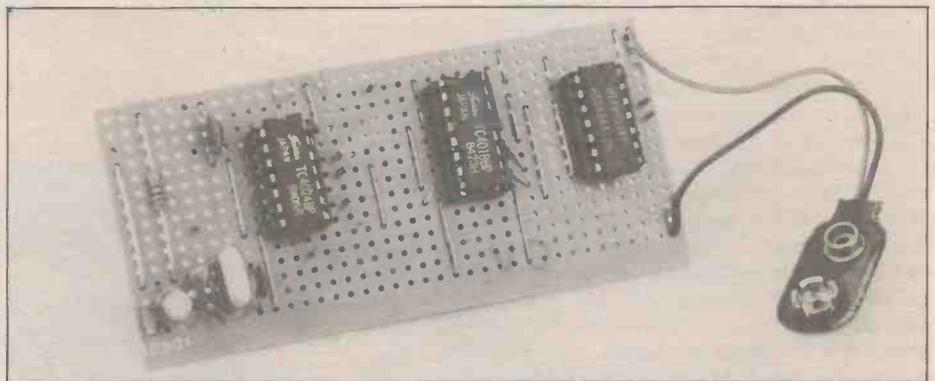

Crystal Calibrator.

outputs from 25kHz to 2MHz are all good quality squarewave types. In theory, the even harmonics (e.g. 2MHz, 4MHz, 6MHz with a 1MHz fundamental) are absent from a squarewave signal, but in practice these frequencies are generally relatively weak rather than absent, due to slight imperfections in the waveform. A pulse shaper could be added at the output in order to give a better spectrum

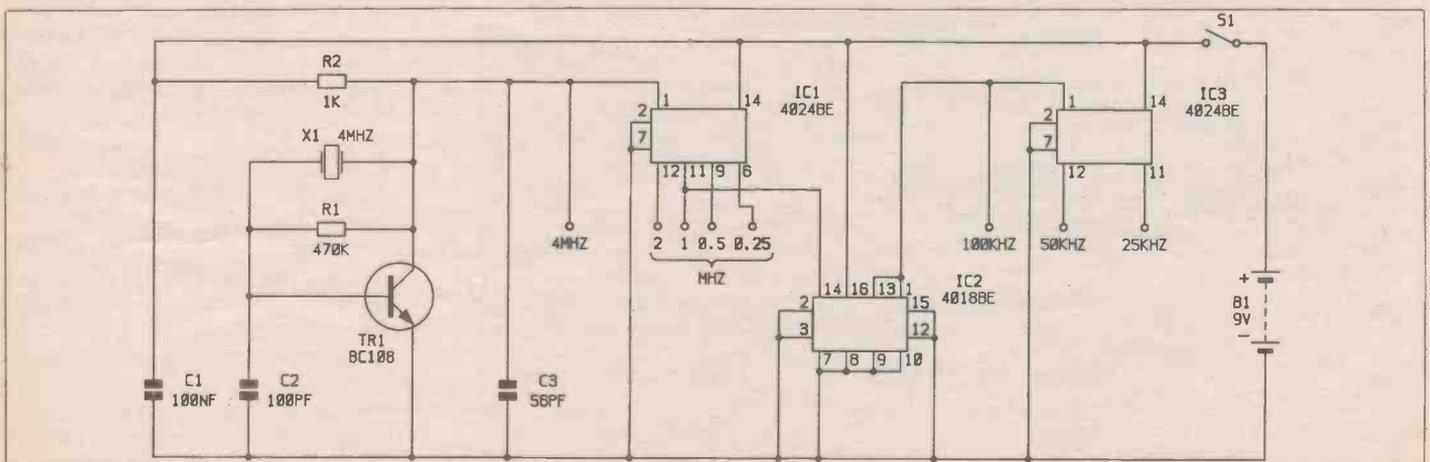of harmonics, but this is probably not worthwhile. The even harmonics will be of more than adequate strength without the aid of any pulse shaping. Because the output is a squarewave, the unit is also well suited to use as a timebase calibrator for an oscilloscope. It gives times ranging from 500ns per cycle at the 2MHz output to 40ms per cycle at the 25kHz output.



Crystal Calibrator Circuit.

The circuit is quite conventional, and has TR1 as a crystal oscillator operating at 4MHz. A non-buffered 4MHz signal is available direct from the collector of TR1. C2 could be changed to a preset type to permit trimming of the output frequency. For most purposes this is unnecessary, as the frequency error is likely to be no more than a couple of Hertz if no trimming is used, and few applications genuinely require even this degree of accuracy. The 4MHz signal is fed to a CMOS 4024BE seven stage binary ripple counter (IC1). Only four stages are actually used in this circuit, and these produce outputs at 2MHz, 1MHz, 500kHz, and 250kHz. The 1MHz output is fed to the input of IC2. This is a CMOS 4018BE divide by 'N' counter, and in this circuit it is connected to give divide by ten

operation. This gives the 100kHz output signal. This signal is also fed to the input of another 4024BE ripple counter (IC3). Only the first two stages of this are used here, and these provide the 50kHz and 25kHz output signals. Of course, the other outputs of IC3 could be used if desired, and they give output frequencies of 12.5kHz, 6.25kHz, etc. However, in practice these lower frequencies are likely to be of limited value. The eight outputs can be taken to separate sockets, or for greater convenience can be taken to a single socket via an eight way switch (which must be a break before make type).

Construction of the unit should not prove to be particularly difficult, but remember that all three integrated circuits are CMOS types, and that as such

they require the standard anti-static handling precautions to be observed. Also, care should be taken when connecting X1, as overheating due to keeping the bit in place on the joints too long could impair the accuracy of the unit.

When coupling the output to a shortwave radio no direct connection should be made between the two units. Apart from possibly overheating the output of the unit, this would almost certainly give an excessive signal level at the receiver. An adequate signal transfer can usually be obtained by connecting a short lead to the output of the calibrator, and placing this close to another lead connected to the aerial input of the receiver.

Transistor Tester

A conventional transistor tester operates by feeding a fixed base current to the test device and then measuring the collector current. The higher the gain of the device under test, the higher the current registered on the meter. The meter can therefore be easily calibrated in terms of current gain, and the collector current is in fact proportional to the gain of the test transistor. In practice this type of tester is very quick and easy to use, but it does have one slight flaw. This is that transistors are tested for gain at an unpredictable collector current, and the gain of most devices varies considerably with changes in collector current. What generally happens is that high gain devices produce a large collector current that means that are tested under good conditions, whereas low gain devices are tested at low currents where they perform relatively badly. This tends to exaggerate the differences between transistors, with slightly above average gain devices showing up as having very high gains. Perhaps of greater importance, transistors with fairly low gains can tend to show up as having inadequate current gains, where they are in fact up to specification in this respect.


This transistor tester was designed to be as easy to use as the conventional tester of the type outlined above, but to operate at a constant collector current so that more reliable results are obtained. Results with the device have been encouraging, and it seems to give what are more accurate results than those obtained with other ultra-simple testers.

The basic method of operation is to feed the collector and emitter terminals from a constant current source. The base terminal is fed from the same source but via a sensitive current meter. With this arrangement the collector current is always equal to the figure set by the current source (or something very close to this figure if we allow for the small amount of current tapped off through the base circuit). The base current is the amount needed to produce this collector current, and therefore decreases as the


level of current gain increases. The meter reading can therefore be translated into a measure of current gain. A minor drawback of this arrangement is that it gives a reverse reading and non-linear scale, which is less convenient in use than the forward reading linear type of a conventional tester. However, taking

readings from this tester is no more difficult than taking readings from the similar scale of an analogue multimeter's resistance ranges.

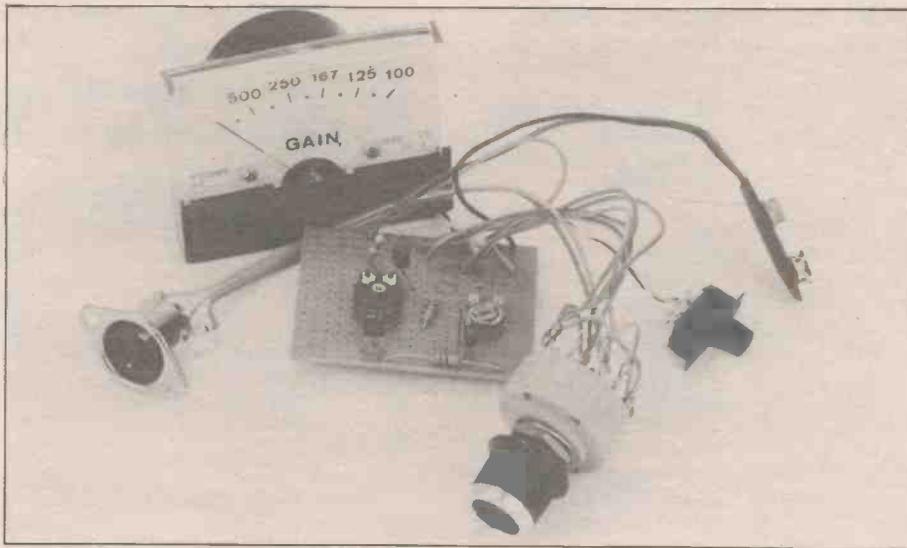There is little more to the circuit than the constant current generator based on TR1 and TR2. RV2 is adjusted to give an output current of 5 milliamps, which is a



Transistor Tester.

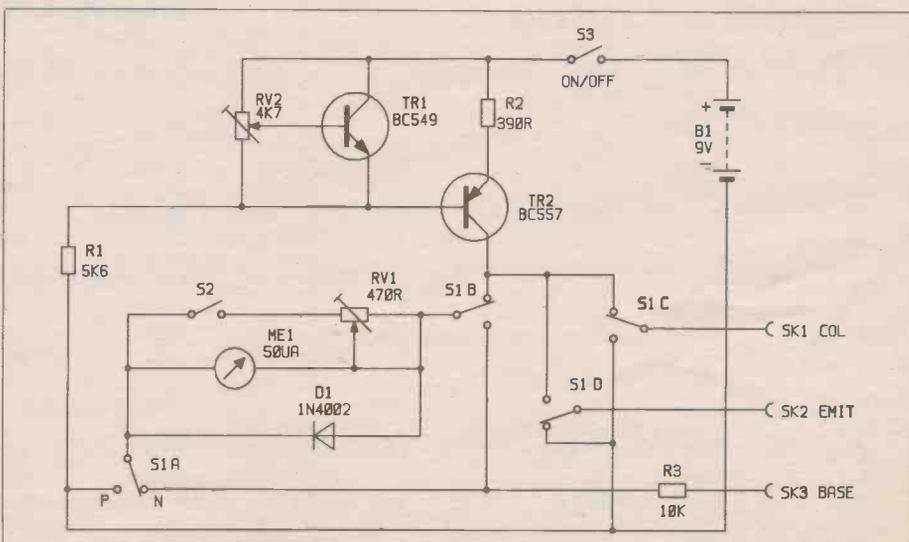

Transistor Tester Circuit.

good compromise value that suits most types of transistor. S1 switches the meter and the test sockets to suit both npn and pnp devices. The meter has a full scale value of 50 microamps, which gives a gain range of one hundred at full scale deflection to infinity at zero deflection. Closing S2 increases the full scale value of the meter to 500 microamps, and the gain range is then ten at full scale deflection, again running through to infinity at zero deflection. R3 and D1 protect the meter against severe overloads, such as would otherwise occur if the base and emitter leads of the test device are connected but the collector is not.

Construction is fairly straightforward, but take care to avoid errors in

the switching. Probably the best type of switch to use for S1 is a 3 way 4 pole rotary type, with the adjustable end-stops set for 2 way operation. SK1 to SK3 can be 1 millimetre sockets grouped close together, and most transistors will then plug into these without any difficulty. Some types (especially power types) will not, and a set of test leads fitted with crocodile clips will be needed to connect these into circuit.

In order to adjust RV2 for a 5 milliamp output current, connect a multi-meter switched to a d.c. current range (about 10 to 25 milliamps full scale) between the negative supply rail and the collector of TR2. Then adjust RV2 for the correct reading of 5 milliamps. To give RV1 the correct setting, close S2 and then

connect the current meter across the base and emitter test sockets via a 15k resistor. Switch the multimeter to a more sensitive range (about 1 to 2.5 milliamps full scale), and then adjust RV1 to match the two readings (bearing in mind that ME1 now reads 500 microamps full scale).

It is more than a little helpful to give the meter a new scale, and this is not too difficult using rub-on transfers. Meter movements are quite delicate though, and due care needs to be taken if you decide to do this. The current gain for points on the scale is obtained by dividing 5000 by the scale value (200 at a value of 25uA for example). When the unit is switched to the lower range, gain levels will be one tenth of the indicated value.

CAPACITANCE METER ADAPTOR PARTS LIST

RESISTORS: All 0.6W 1% Metal Film

| | | | |
|------|------------------------|---|---------|
| R1,3 | 100k | 2 | (M100K) |
| R2 | 1M | 1 | (M1M) |
| R4 | 10k | 1 | (M10K) |
| R5 | 1k | 1 | (M1K) |
| R6 | 6k8 | 1 | (M6K8) |
| R7 | 150k | 1 | (M150K) |
| RV1 | 47k Hor Sub-min Preset | 1 | (WR60Q) |
| RV2 | 1k Lin Pot | 1 | (FW00A) |

CAPACITORS

| | | | |
|------|---------------------------|---|---------|
| C1 | 100µF 10V PC Electrolytic | 1 | (FF10L) |
| C2 | 47nF Polyester | 1 | (WW37S) |
| C3 | 4µF 63V PC Electrolytic | 1 | (FF03D) |
| C4,5 | 100nF Ceramic | 2 | (YR75S) |

SEMICONDUCTORS

| | | | |
|-------|----------|---|---------|
| IC1,2 | TLC555CP | 2 | (RA76H) |
| IC3 | µA78L05 | 1 | (QL26D) |

MISCELLANEOUS

| | | | |
|-----|------------------------------|---|---------|
| SK1 | 1mm Socket Red | 1 | (WL60Q) |
| SK2 | 1mm Socket Black | 1 | (WL59P) |
| SK3 | 2mm Socket Red | 1 | (HF47B) |
| SK4 | 2mm Socket Black | 1 | (HF44X) |
| S1 | 4-way 3-pole Rotary Switch | 1 | (FF75S) |
| S2 | SPST Ultra-min Toggle Switch | 1 | (FH97F) |
| B1 | 9V PP3 Battery | 1 | (FK62S) |
| | Battery Connector | 1 | (HF28F) |
| | 8-pin DIL Socket | 2 | (BL17T) |

TRANSISTOR TESTER PARTS LIST

RESISTORS: All 0.6W 1% Metal Film

| | | | |
|-----|-------------------------|---|---------|
| R1 | 5k6 | 1 | (M5K6) |
| R2 | 390Ω | 1 | (M390R) |
| R3 | 10k | 1 | (M10K) |
| RV1 | 470Ω Sub-min Hor Preset | 1 | (WR54J) |
| RV2 | 4k7 Sub-min Hor Preset | 1 | (WR57M) |

SEMICONDUCTORS

| | | | |
|-----|--------|---|---------|
| TR1 | BC549 | 1 | (QQ15R) |
| TR2 | BC557 | 1 | (QQ16S) |
| D1 | 1N4002 | 1 | (QL74R) |

MISCELLANEOUS

| | | | |
|---------|----------------------------|---|---------|
| S1 | 3 way 4 pole Rotary Switch | 1 | (FF76H) |
| S2,3 | SPST Ultra-min Toggle | 2 | (FH97F) |
| ME1 | 50uA Panel Meter | 1 | (FW98G) |
| B1 | 9 volt PP3 Battery | 1 | (FK62S) |
| SK1,2,3 | 1mm Socket | 3 | (WL59P) |
| | Battery Connector | 1 | (HF28F) |

MIDI THRU BOX PARTS LIST

RESISTORS: All 0.6W 1% Metal Film

| | | | |
|-------------------------|------|---|---------|
| R1,5,6,9,10,13,14,17,18 | 220Ω | 9 | (M220R) |
| R2,7,11,15 | 2k2 | 4 | (M2K2) |
| R3,8,12,16 | 4k7 | 4 | (M4K7) |
| R4 | 2k7 | 1 | (M2K7) |

CAPACITOR

| | | | |
|----|-----------------------------|---|---------|
| C1 | 10µF 25V Axial Electrolytic | 1 | (FB22Y) |
|----|-----------------------------|---|---------|

SEMICONDUCTORS

| | | | |
|-----------|-------|---|---------|
| IC1 | 6N139 | 1 | (RA59P) |
| TR1,2,3,4 | BC559 | 4 | (QQ18U) |

MISCELLANEOUS

| | | | |
|-------------|-------------------------|---|---------|
| SK1,2,3,4,5 | 5-way (180°) DIN Socket | 5 | (HH34M) |
| S1 | SPST Ultra-min Toggle | 1 | (FH97F) |
| B1 | Battery 1.5V | 4 | (FK55K) |
| | 8-pin DIL Socket | 1 | (BL17T) |
| | Battery Holder | 1 | (HF29G) |
| | Battery Connector | 1 | (HF28F) |

CRYSTAL CALIBRATOR PARTS LIST

RESISTORS: All 0.6W 1% Metal Film

| | | | |
|----|------|---|---------|
| R1 | 470k | 1 | (M470K) |
| R2 | 1k | 1 | (M1K) |

CAPACITORS

| | | | |
|----|---------------|---|---------|
| C1 | 100nF Ceramic | 1 | (YR75S) |
| C2 | 100pF Ceramic | 1 | (WX56L) |
| C3 | 56pF Ceramic | 1 | (WX53H) |

SEMICONDUCTORS

| | | | |
|-------|--------|---|---------|
| IC1,3 | 4024BE | 2 | (QX13P) |
| IC2 | 4018BE | 1 | (QX10L) |
| TR1 | BC108C | 1 | (QB32K) |

MISCELLANEOUS

| | | | |
|----|-----------------------|---|---------|
| B1 | 9 volt PP3 Battery | 1 | (FK58N) |
| S1 | SPST Ultra-min Toggle | 1 | (FH97F) |
| X1 | 4MHz HC-18/U | 1 | (FY82D) |
| | Battery Connector | 1 | (HF28F) |
| | DIL IC Holder 14 pin | 2 | (BL18U) |
| | DIL IC Holder 16 pin | 1 | (BL19V) |

1988 CATALOGUE PRICE CHANGES

The price changes shown in this list are valid from 15th August 1988 to 31st November 1988. Prices charged will be those ruling on the day of despatch.

For further details please see 'Prices' on catalogue page 20.

Price Changes

All items whose prices have changed since the publication of the 1988 catalogue are shown in the list below. Those where the price has changed since the last Price Change Leaflet (dated 16th May 1988) are marked * after the price.

A complete Price List is also available free of charge - order as XF08J.

Key
DIS Discontinued.
TEMP Temporarily unobtainable.
FEB Out of stock; new stock expected in month shown.
† An additional £5.50 carriage charge must be added.
/V Indicates that item is zero rated for VAT purposes.
★ See 'Amendments to Catalogue'. Note that not all items that require amendments are shown in this list.

| 1988 Catalogue Page No. | VAT Inclusive Price | 1988 Catalogue Page No. | VAT Inclusive Price | 1988 Catalogue Page No. | VAT Inclusive Price | 1988 Catalogue Page No. | VAT Inclusive Price | 1988 Catalogue Page No. | VAT Inclusive Price |
|-------------------------------------|---------------------|---------------------------------------|---------------------|--|---------------------|---------------------------------|---------------------|-------------------------------------|---------------------|
| Page 38 | | Page 54 | | Page 73 | | Page 98 | | Page 107 | |
| XQ23A Mushkiller FM1083 £13.45 | | Y375 Micro-Cassette 3 Pk. £2.95* | | WP05F Pract Electronics £8.25 NV | | LL11M Verobox 217 £6.95 | | XR79L Flat IDC Cable 50Way 95p | |
| XQ25C Mushkiller FM1085 £21.45 | | Page 55 | | WA24B Understrng Communctns £14.50 NV | | LL12N Verobox 303 £6.95 | | XR80B Cir Cd IDC Cable 16W 47p | |
| XQ29G Trucolour TC10 Grp A £12.65 | | CT140 Scotch XSI-C90 £1.35* | | WK45Y Understrng Phone Ectrn £14.50 NV | | LLH50 Verobox 305 £2.50 | | XR81C Cir Cd IDC Cable 20W 60p | |
| XQ30H Trucolour TC10 Grp B £12.65 | | CT33L Scotch XSMIV-C90 DIS | | WP24B Telecom Circuits £15.50 NV | | LL14Q Verobox 303 £3.30 | | XR82D Cir Cd IDC Cable 26W 75p | |
| XQ31J Trucolour TC10 Grp C/D £12.65 | | CT02C TDK D-60 95p | | WP28F Data Communications £14.50 NV | | LL14Q Verobox 401 96p | | XR83E Cir Cd IDC Cable 34W 98p | |
| XQ32A Trucolour TC10 Grp A £12.85 | | CT03D TDK D-90 £1.20 | | WM59P Linear Electronics £9.50 NV | | LQ030 Flip-Top Box 601 Bk £3.80 | | XR84F Cir Cd IDC Cable 40W £1.10 | |
| XQ32K Trucolour TC10 Grp B £14.30 | | CT08J TDK AD-60 £1.20 | | RL34M Book NB189 £9.95 NV | | LH30H Verobox 705 £7.95 | | XR85G Cir Cd IDC Cable 50W £1.45 | |
| XQ33L Trucolour TC13 Grp A £14.95 | | CT09K TDK AD-90 £1.45 | | RR39N Towers Transistor Bk £14.99 NV | | | | | |
| XQ34M Trucolour TC13 Grp C/D £14.95 | | CT23A TDK SA-60 £1.60 | | RG68Y Book FT338 DIS* | | Page 99 | | | |
| XQ35Q Trucolour TC18 Grp A £18.40 | | CT24B TDK SA-90 £1.98 | | | | F638R Sink 20 74p | | XR47B Twn Mains DS Black £17.65 | |
| XQ36P Trucolour TC18 Grp B £18.40 | | CT26D TDK SA-X60 £1.98 | | Page 74 | | F639N Sink 40 £1.10 | | PA10L 100m Twn Mains Black £1.16 | |
| XQ37S Trucolour TC19 Grp A £18.40 | | CT27E TDK SA-X90 £2.50 | | WP67X Elec Pocket Book £9.95 NV | | | | XR00A Twn Mains DS White £1.16 | |
| XQ38R Trucolour TC19 Grp E £18.40 | | CT31J TDK HXS-90 DIS* | | Page 75 | | | | XR61R Twn 6A Mains Orange 24p | |
| XQ39R Extragain XG5 £19.95 | | CT39N TDK WA-R95 £2.95 | | WA10L TI Linear Circuits £11.00 NV | | | | XR62S Twn 6A Mains White 24p | |
| Page 39 | | CT05F Mexell UL-C90 £1.06* | | WA14Q TI TTL Data Vol 1 £14.95 NV | | | | XR01B Min Mains Black £2.6p | |
| XQ39N Extragain XG8 GroupA £30.95 | | CT10L Mexell UL-C60 £1.08* | | WP31J TI TTL Data Vol 2 £14.95 NV | | CABLES | | PB08J 100m Min Mains Black £17.95 | |
| XQ40T Extragain XG8 GroupB £30.95 | | CT11M Mexell UL-C90 £1.32* | | WG58N Book FT1199 £13.20 NV | | RY06G Acoustic Wadding 80p | | XR02C Min Mains White 26p | |
| XQ41U Extragain XG8 Grp C/D £30.95 | | CT18U Mexell XLI-C90 £1.95* | | | | X510L Square Cloth 0.71m £1.30* | | PB09K 100m Min Mains White £17.95 | |
| XQ42V Extragain XG8 Wdbnd £30.95 | | CT18U Mexell XLI-C90 £1.76* | | Page 76 | | | | XR03D C6A Mains Black 37p | |
| XQ43W Extragain XG14 GroupA £59.50 | | CT25C Mexell XLI-C90 £1.48* | | WG23A Book JW568 DIS* | | | | XR04E C6A Mains White 37p | |
| XQ44X Extragain XG14 GroupB £59.50 | | CT28F Mexell XLI-C60 £1.50* | | WA06G TI MDS Memory Data £12.50 NV | | | | XR05F C6A Mains Orange 37p | |
| XQ45Y Extragain XG14 Grp C/D £59.50 | | CT29G Mexell XLI-C90 £1.94* | | | | | | XR06K C6A Mains Black £36.95 | |
| XQ46A Extragain XG21 Wdbnd £58.50 | | CT41U Mexell XLI-S60 £1.69* | | Page 77 | | | | PA12N 100m HD Mains Black £36.95 | |
| XQ50E Extragain XG21 Wdbnd £84.95 | | CT42V Mexell XLI-S90 £2.22* | | WG01B Book NB447 £7.95 NV | | | | XR10L HD Mains White 56p | |
| XQ56L Hi-Tech TV Ant £10.75 | | CT47Z Mexell MX-C90 £2.36* | | WP50E Intro Electronics £2.95 NV | | | | PA13P 100m HD Mains White £38.75 | |
| XQ51F Super-Set Top £10.35 | | CT37S Mexell MX-C90 £3.36* | | WM60Q Mastering Electronic £4.25 NV | | | | XR11M HD Mains Orange 56p | |
| XQ52G Caratene £12.65 | | Page 57 | | | | | | PA14Q 100m HD Mains Orange £38.75 | |
| XQ53H Mast Bracket Type 3 £9.95 | | XJ11M Video Enhancer 406 £16.95 | | Page 78 | | | | | |
| XQ54J Mast Bracket Type 8 £13.95 | | YP47B Video-Cine Adapter £16.95 | | RH30H Book BP37 £2.95 NV | | | | Page 108 | |
| Page 40 | | Page 58 | | RL05F Book NB074 DIS* | | | | XR49D 1.0mm TE Cable £17p | |
| BW44X Mast Bracket Type 14 £3.95 | | YP84F Surge Protector RS232 £9.95 | | RX53H Cost Effect Constrc £6.95 NV | | | | XR51F 2.5mm TE Cable 31p | |
| BW45Y Loft Bracket EM4 £2.50 | | Page 60 | | Page 79 | | | | XR52G 6mm TE Cable 84p | |
| XQ55K Lashing Kit Type 4 £10.35 | | F782D D/S Q/D Disk 5.25 £1.80 | | WP41U Proj in Microelect DIS* | | | | XR53H 1mm Trpl & ECC Cbl 29p | |
| XQ57M Lashing Kit Type 7 £19.50 | | YJ22P D/O S/D Disk 5.25 £14.95 | | WG54J Book NB535 £5.95 NV | | | | XR15R Min Screened £1.6p | |
| XQ58N Lashing Kit Type 9 £13.75 | | | | RB10L Book NB269 £7.95 NV | | | | PB13P 100m Min Screened £11.95 | |
| XQ60Q Mast D £4.35 | | Page 61 | | Page 80 | | | | XR12N Cable Single Black 18p | |
| Page 41 | | YK37F Minibox 10 DIS* | | WG53H Book NB529 £5.95 NV | | | | XR13P Cable Single Grey 18p | |
| YK730 Indoor Amp X81 £25.95 | | YK87U Minibox 15 £9.95* | | RQ30H Book NB353 £8.95 NV | | | | XR14Q Cable Single White 18p | |
| YP59P Aerial Amp 22.5dB £37.95 | | BATTERIES & POWER SUPPLIES | | XW38R Book NB480 TEMP | | | | XR16S Min Screened £24.95 | |
| YP41U 2 Outlet TV Amp £12.95* | | Page 63 | | RQ66W Book BP59 DIS | | | | PA16S 100m Single Cbl Cable £24.95 | |
| YQ22Y Xtra Set Amp £24.95 | | FK55K Blue Seal R6B 21p | | WP00A Fib Dip Laser Handbk £13.20 NV | | | | XR19V 50m Low C Cable £36p | |
| Page 42 | | FK56L Blue Seal R14B 31p | | Page 81 | | | | XR83T UR67 RF Cable £25.95 | |
| YP42Y 2 Outlet TV/FM Amp £16.95 | | FK57M Blue Seal R20B 40p | | WP77J Build Fibop/Lasr Prj £12.40 NV | | | | XR20W Lapped Pair 20p | |
| BK75S Xtra Set 3 Amp £29.50 | | FK58N Blue Seal P33B 75p | | XW08J Audio Projects AUG 88 | | | | XR23A Cable Quad 56p | |
| YN45Y Xtra Set 4 Amp £36.95 | | FK59P Silver Seal R6S 31p | | Page 82 | | | | PA18U 50m Cable Quad £19.95 | |
| BK76H TV Amp XG12 £16.45 | | FK60D Silver Seal R14S 54p | | WG82D Book FT1364 £8.45 NV | | | | XR22A Lead 4-Core Grey £32p | |
| Page 43 | | FK61R Silver Seal R20S 62p | | XW09K Book NB391 £5.95 NV | | | | PB41U 100m Lap 4-Core Grey £24.95 | |
| YP57M Aerial Combiner A/E £9.95 | | FK62S Silver Seal PPS3 £1.07 | | WG26W Book BP59 DIS | | | | XR19Y Lapped 4-Core Black £32p | |
| YK98V Aerial Combiner AB/CD £9.95 | | FK63R Gold Seal LR1 £.60 | | WP00A Fib Dip Laser Handbk £13.20 NV | | | | PB40T 100m Lap 4-Core Black £24.95 | |
| YK99V Resistor Splitter £2.50 | | FK64A Gold Seal LR16 83p | | Page 83 | | | | Page 110 | |
| YQ23A Inductive Splitter £2.95 | | FK65V Gold Seal LR14 £1.15 | | WG54J Book NB439 £3.95 NV | | | | XR25C Multi-Core 4-Way 70p | |
| HX67U Surface Co-Ax Outlet £1.50 | | FK66W Gold Seal LR20 £1.28 | | Page 84 | | | | BH30H Scr Stretchflex Bk £2.50 | |
| BW55K Flush Co-Ax Outlet £1.99 | | FK67X Gold Seal GLF22 £2.39 | | WG95D Book FT1305 £8.70 NV | | | | BH34M Scr Stretchflex Red £2.50 | |
| BW56L Flush Co-Ax Outlet £2.95 | | FM02D Trans Pwr P91 6V £1.99 | | WG98B Book FT1185 £8.45 NV | | | | HQ49D Twn Stretchflex £3.50 | |
| Page 44 | | FM03D Trans Pwr P95 9V £1.69 | | WP36P Radio Stations Guide £4.95 NV | | | | XR61V Miniature Coax 39p | |
| LB09K 75000 Balun £1.40 | | FM04D Trans Pwr P97 9V £1.69 | | Page 85 | | | | PB20W 100m Miniature Coax £26.95 | |
| FK47B 3dB Attenuator £1.98 | | FM05F Trans Pwr P99 9V £1.69 | | WM95H Satellite TV Guide £9.25 NV | | | | 100m Bal Feeder £39.95 | |
| BW59P Attenuator 6dB £1.98 | | FM07H Photo Batt BLR121 £2.99 | | WG25C Book JW603 £9.95 NV | | | | CAPACITORS | |
| BW60Q Attenuator 12dB £1.98 | | FM08J Photo Batt BLR122 £3.99 | | XW88W Book AG569 £3.95 NV | | | | Page 118 | |
| AUDIO, VIDEO & COMPUTERS | | FM09K Photo Batt BLR154 £2.99 | | YP08J Elect Fault Diagnos £6.95 NV | | | | FF58N 1S Cap 0.47uF 90p | |
| Page 46 | | YQ67Y Photo-Test PX28 £3.64 | | WM86T Elect Servicing £9.50 NV | | | | Page 125 | |
| XG68F 12V Disco Deck DIS | | FK68Y Gen Purpose No. 8 49p | | RL23A Book NB137 DIS* | | | | XJ20W 2m 25W Transceiver £249.95* | |
| FI17T Cartridge Slide MP60 £3.80 | | FK69A Gen Purpose 1289 99p | | WP56L Service Vid Records £20.00 NV | | | | XJ21X 2m 45W Transceiver £299.95* | |
| YW58N BSR Drive Belt £1.98 | | YJ18U Gen Purpose P396 £2.77 | | Page 86 | | | | Page 127 | |
| Page 47 | | YJ19V Gen Purpose P397 £2.75 | | RQ01B Book Sybex C201 £22.95 NV | | | | XJ22Y 70cm 25W Transceiver £289.95* | |
| HR17T Ctrdg Solder V100 £8.95 | | YJ21V Gen Purpose AD28 £2.20 | | XG98G Book FT1070 £15.55 NV | | | | YG16S Mag Mount £11.95 | |
| FQ38R Ctrdg Soldering 800H £12.95 | | YJ22Y Gen Purpose HP1 £12.54 | | WP12N Micro I/F Ckt - Bk2 £2.75 NV | | | | Page 128 | |
| Page 48 | | YJ23A Gen Purpose HP992 £3.99 | | Page 87 | | | | Y9M5D Traveler Clock Radio DIS* | |
| FV16S ME70-B Shure Cart £13.95 | | FK70M Gen Purpose 126 £2.48 | | WP25C 6502 Ref Guide DIS* | | | | Page 129 | |
| FV13P ME75-B5 Shure Cart £14.95 | | FK71N Gen Purpose FLAG £4.53 | | XW80B Book C202 £15.95 NV | | | | YP22Y Clock/Radio Phon Wht £34.95 | |
| FV15R ME75-E2 Shure Cart £19.95 | | Page 64 | | WP63T 68000 Ref Guide DIS | | | | CONNECTORS | |
| FV14Q ME75-ED 2 Shure Cart £23.95 | | FM14Q Merc Batt PX1/RMIN £1.32 | | Page 88 | | | | Page 138 | |
| FV18U ME95-ED Shure Cart £26.95 | | FM18U Merc Batt PX/RM625 89p | | WM76P Programming M68000 £13.95 NV | | | | RK60Q D-Range 9 Way Plug 31p | |
| FV17T ME97-HE Shure Cart £38.50 | | FM20W Merc Batt PXK675 58p | | XW27F Book C280 £20.95 NV | | | | BK58N D-Range 15-Way Plug 43p | |
| HR39N BSR TC8 £1.50 | | FM21X Merc Batt RM104 89p | | Page 89 | | | | YQ48C D-Range 25-Way Plug 51p | |
| HR51F Ronette SF106 £3.95 | | FM24B Merc Batt RM675H DIS* | | WP58N Understanding C £18.95 NV | | | | RK61R D-Range 9 Way Skt 49p | |
| FV27E BSR S14 £2.20 | | FM33L Silver Batt B-SR56L TEMP | | WG29C Book JW603 £9.95 NV | | | | BK59P D-Range 15-Way Skt 63p | |
| HR29S Acos GP91-1SC £2.20 | | F576H Silver Batt B-SR371L DIS* | | XW79L Book C300 £17.95 NV | | | | YQ49D D-Range 25W Socket 74p | |
| HR87U Philips AG3036 £2.20 | | F575S Silver Batt B-SR57L TEMP | | WM77J Working Database II £9.95 NV | | | | Page 140 | |
| HR60D Sonotone 9TAHC £2.20 | | Page 65 | | Page 90 | | | | FS92A Finger Screw Hd 9W 60p | |
| HR22V BSR ST10 £2.20 | | YJ69A 1.2Ah L/Acid Bat 12V £13.50 | | WP13P Easy Prog Atari Micr DIS* | | | | FS53B Finger Screw Hd 15W 64p | |
| YK27E Sony ND15P £7.95 | | Page 66 | | Page 91 | | | | YK48R Finger Screw Hd 25W 61p | |
| VZ6D Acos GP91-1 £2.20 | | FE09K Ni Cad AAA £1.80 | | WA90T 20 ZX81 Projects DIS | | | | FS94C Finger Screw Hd 37W 78p | |
| HR53H Garrard KS40A £2.20 | | YG00A Ni Cad AA £1.36 | | WG61R Book HD192 DIS* | | | | Page 145 | |
| HR13J Acos GP104 £2.20 | | Page 68 | | WM37S Und Auto Syst £14.50 NV | | | | UY37Q Polarising Key IDC 8p | |
| HR78B BSR ST10 £2.20 | | XG88V 13.8V 7A Reg PSU £29.95 | | Page 92 | | | | Page 150 | |
| HR74R BSR ST27 £1.50 | | Page 69 | | FD96E Potting Box Cube 20p | | | | RW350 Plugpak HD Gultar DIS* | |
| FQ45Y Garrard GDD1 £2.20 | | DC/DC Conv + 9V £4.98* | | LH57M Potting Box Small 28p | | | | Page 156 | |
| HR81C Vacco Lux £1.50 | | DC/DC Conv + 15V £4.98* | | F097F Potting Box Medium 38p | | | | HL02C 8-Way Plug £1.98 | |
| HR45Y BSR ST15 £2.20 | | DC/DC Conv -5V £4.98* | | F098E Potting Box Large 46p | | | | YX44X Multicon Skt 36-way 84p | |
| FV24B Fuji Denko £8.95 | | DC/DC Conv -15V £4.98* | | FD98E Potting Box Ex Large 48p | | | | Page 157 | |
| YK22Y Sanyo ST106 £2.20 | | DC/DC Conv +/-12V DIS* | | Page 93 | | | | FG22Y PC Edconn 2x22 way £2.40* | |
| HR90X Philips GP400 £6.95 | | DC/DC Conv +/-15V DIS* | | LH00A Verobox 101 £4.85 | | | | Page 160 | |
| FV37H Hitachi HN-ST6 £2.20 | | BOOKS | | LH01B Verobox 102 £4.40 | | | | JB13P Photo Plug Screened DIS* | |
| FM76L Shure N95-ED £24.95 | | Page 71 | | LH04A Verobox 103 £7.30 | | | | BW67H Photo Socket 6-way 68p | |
| FV20W Tetrad T30MS £2.20 | | RL27E Book NB147 £9.95 NV | | L05F Verobox 201 £7.85 | | | | ELECTRICAL ACCESSORIES | |
| FV24M Shure N87-HE £24.95 | | RL31J Book NB157 £9.95 NV | | L08J Verobox 211 £4.75 | | | | Page 168 | |
| FQ51F Tonnor 2001D £6.95 | | Page 72 | | L10Q Verobox 212 £5.20 | | | | H88Y Single Skt Unswtchd £1.85 | |
| HR89V Philips GP205 £1.50 | | WA44X Understrng Auto Elec £14.50 NV | | LL | | | | | |

1988 CATALOGUE PRICE CHANGES

The price changes shown in this list are valid from 15th August 1988 to 5th November 1988. Prices charged will be those ruling on the day of despatch.

For further details please see 'Prices' on catalogue page 20.

Price Changes

All items whose prices have changed since the publication of the 1988 catalogue are shown in the list below. Those where the price has changed since the last Price Change Leaflet (dated 16th May 1988) are marked * after the price.

A complete Price List is also available free of charge - order as XF08J.

Key
DIS Discontinued.
TEMP Temporarily unobtainable.
FEB Out of stock; new stock expected in month shown.
‡ An additional £5.50 carriage charge must be added.
NV Indicates that item is zero rated for VAT purposes.
***** See 'Amendments To Catalogue'. Note that not all items that require amendments are shown in this list.

| 1988 Catalogue Page No. | VAT Inclusive Price | 1988 Catalogue Page No. | VAT Inclusive Price | 1988 Catalogue Page No. | VAT Inclusive Price | 1988 Catalogue Page No. | VAT Inclusive Price |
|----------------------------|---------------------|---------------------------|---------------------|-----------------------------------|---------------------|--------------------------------|---------------------|
| Page 38 | | Page 54 | | Page 73 | | Page 98 | |
| X025A Mushkiller FM1083 | £13.45 | YF375 Micro-Cassette 3 Pk | £2.95* | W024B Undraining Commun. Circuits | £14.50 NV | LL11M Verobox 217 | £8.95 |
| X025C Mushkiller FM1085 | £21.45 | CT13L Scotch XSI-C90 | £1.35* | W024B Undraining Phone Electr. | £14.50 NV | LL12N Verobox 301 | 84p |
| X027E Mushkiller FM1087 | £33.95 | CT23L Scotch XSMIV-C90 | DIS | W024B Telecom Circuits | £15.50 NV | LH05E Verobox 303 | £2.50 |
| X029G Trucolour TC10 Grp A | £12.85 | CT20C TDK D-80 | 95p | W024B Data Communications | £14.50 NV | LH51F Verobox 305 | £3.30 |
| X029H Trucolour TC10 Grp B | £12.85 | CT23D TDK D-90 | £1.20 | W024B Linear Electronics | £3.50 NV | LL14Q Verobox 401 | 96p |
| X031J Trucolour TC10 Grp C | £12.85 | CT20E TDK AD-80 | £1.20 | R34M Book NB189 | £9.95 NV | L003D Flip-Top Box 601 Blk | £3.80 |
| X032A Trucolour TC13 Grp A | £14.95 | CT23A TDK SA-80 | £1.60 | R393N Towers Transistor Bk. | £14.99 NV | LH30H Verobox 705 | £7.95 |
| X033X Trucolour TC13 Grp B | £14.95 | CT24B TDK SA-90 | £1.98 | R089Y Book FT938 | DIS* | | |
| X034M Trucolour TC13 Grp C | £14.95 | CT24C TDK SA-X80 | £1.98 | | | | |
| X035D Trucolour TC18 Grp A | £18.40 | CT24D TDK SA-X90 | £1.98 | Page 74 | | Page 107 | |
| X036P Trucolour TC18 Grp B | £18.40 | CT27E TDK MA-90 | £2.50 | WP67X Elec Pocket Book | £8.95 NV | XR747B 100m Twm Mains DS Black | 17p |
| X037S Trucolour TC18 Grp C | £18.40 | CT31J TDK HXS-90 | DIS* | | | PA10L 100m Twm Mains White | £11.85 |
| X038R Extragain XG5 | £19.95 | CT39N TDK MA-R90 | £5.95 | | | R000A Twm Mains DS White | 17p |
| | | CT05F Maxell UL-C90 | £1.08* | | | XR02C Min Mains White | £1.85 |
| | | CT10L Maxell UD-C90 | £1.08* | | | XR16R Twm 8A Mains Orange | 24p |
| | | CT11M Maxell UDI-C90 | £1.32* | | | XR82S Twm 6A Mains White | 24p |
| | | CT18U Maxell XLI-C90 | £1.95* | | | X001B Min Mains Black | 28p |
| | | CT20W Maxell XLI-S90 | £1.78* | | | PB08J 100m Min Mains Black | £17.95 |
| | | CT25C Maxell UDI-C90 | £1.48* | | | XR02C Min Mains White | 26p |
| | | CT28F Maxell UDI-C90 | £1.50* | | | PB09K 100m Min Mains White | £17.95 |
| | | CT29G Maxell XLI-C90 | £1.94* | | | R003D C&A Mains Black | 37p |
| | | CT41U Maxell XLI-S90 | £1.89* | | | X040E C&A Mains White | 37p |
| | | CT42V Maxell XLI-S90 | £2.22* | | | XR09J HD Mains Orange | 58p |
| | | CT43W Maxell XLI-S90 | £2.22* | | | XR09K HD Mains Black | 58p |
| | | CT44X Maxell XLI-S90 | £2.22* | | | XR10L HD Mains White | 58p |
| | | CT45Y Maxell XLI-S90 | £2.22* | | | PA13P 100m HD Mains White | £38.75 |
| | | CT46Z Maxell XLI-S90 | £2.22* | | | XR11M HD Mains Orange | 58p |
| | | CT47A Maxell XLI-S90 | £2.22* | | | PA14Q 100m HD Mains Orange | £38.75 |
| | | CT48B Maxell XLI-S90 | £2.22* | | | | |
| | | CT49C Maxell XLI-S90 | £2.22* | | | | |
| | | CT50D Maxell XLI-S90 | £2.22* | | | | |
| | | CT51E Maxell XLI-S90 | £2.22* | | | | |
| | | CT52F Maxell XLI-S90 | £2.22* | | | | |
| | | CT53G Maxell XLI-S90 | £2.22* | | | | |
| | | CT54H Maxell XLI-S90 | £2.22* | | | | |
| | | CT55I Maxell XLI-S90 | £2.22* | | | | |
| | | CT56J Maxell XLI-S90 | £2.22* | | | | |
| | | CT57K Maxell XLI-S90 | £2.22* | | | | |
| | | CT58L Maxell XLI-S90 | £2.22* | | | | |
| | | CT59M Maxell XLI-S90 | £2.22* | | | | |
| | | CT60N Maxell XLI-S90 | £2.22* | | | | |
| | | CT61O Maxell XLI-S90 | £2.22* | | | | |
| | | CT62P Maxell XLI-S90 | £2.22* | | | | |
| | | CT63Q Maxell XLI-S90 | £2.22* | | | | |
| | | CT64R Maxell XLI-S90 | £2.22* | | | | |
| | | CT65S Maxell XLI-S90 | £2.22* | | | | |
| | | CT66T Maxell XLI-S90 | £2.22* | | | | |
| | | CT67U Maxell XLI-S90 | £2.22* | | | | |
| | | CT68V Maxell XLI-S90 | £2.22* | | | | |
| | | CT69W Maxell XLI-S90 | £2.22* | | | | |
| | | CT70X Maxell XLI-S90 | £2.22* | | | | |
| | | CT71Y Maxell XLI-S90 | £2.22* | | | | |
| | | CT72Z Maxell XLI-S90 | £2.22* | | | | |
| | | CT73A Maxell XLI-S90 | £2.22* | | | | |
| | | CT74B Maxell XLI-S90 | £2.22* | | | | |
| | | CT75C Maxell XLI-S90 | £2.22* | | | | |
| | | CT76D Maxell XLI-S90 | £2.22* | | | | |
| | | CT77E Maxell XLI-S90 | £2.22* | | | | |
| | | CT78F Maxell XLI-S90 | £2.22* | | | | |
| | | CT79G Maxell XLI-S90 | £2.22* | | | | |
| | | CT80H Maxell XLI-S90 | £2.22* | | | | |
| | | CT81I Maxell XLI-S90 | £2.22* | | | | |
| | | CT82J Maxell XLI-S90 | £2.22* | | | | |
| | | CT83K Maxell XLI-S90 | £2.22* | | | | |
| | | CT84L Maxell XLI-S90 | £2.22* | | | | |
| | | CT85M Maxell XLI-S90 | £2.22* | | | | |
| | | CT86N Maxell XLI-S90 | £2.22* | | | | |
| | | CT87O Maxell XLI-S90 | £2.22* | | | | |
| | | CT88P Maxell XLI-S90 | £2.22* | | | | |
| | | CT89Q Maxell XLI-S90 | £2.22* | | | | |
| | | CT90R Maxell XLI-S90 | £2.22* | | | | |
| | | CT91S Maxell XLI-S90 | £2.22* | | | | |
| | | CT92T Maxell XLI-S90 | £2.22* | | | | |
| | | CT93U Maxell XLI-S90 | £2.22* | | | | |
| | | CT94V Maxell XLI-S90 | £2.22* | | | | |
| | | CT95W Maxell XLI-S90 | £2.22* | | | | |
| | | CT96X Maxell XLI-S90 | £2.22* | | | | |
| | | CT97Y Maxell XLI-S90 | £2.22* | | | | |
| | | CT98Z Maxell XLI-S90 | £2.22* | | | | |
| | | CT99A Maxell XLI-S90 | £2.22* | | | | |
| | | CT00B Maxell XLI-S90 | £2.22* | | | | |
| | | CT01C Maxell XLI-S90 | £2.22* | | | | |
| | | CT02D Maxell XLI-S90 | £2.22* | | | | |
| | | CT03E Maxell XLI-S90 | £2.22* | | | | |
| | | CT04F Maxell XLI-S90 | £2.22* | | | | |
| | | CT05G Maxell XLI-S90 | £2.22* | | | | |
| | | CT06H Maxell XLI-S90 | £2.22* | | | | |
| | | CT07I Maxell XLI-S90 | £2.22* | | | | |
| | | CT08J Maxell XLI-S90 | £2.22* | | | | |
| | | CT09K Maxell XLI-S90 | £2.22* | | | | |
| | | CT10L Maxell XLI-S90 | £2.22* | | | | |
| | | CT11M Maxell XLI-S90 | £2.22* | | | | |
| | | CT12N Maxell XLI-S90 | £2.22* | | | | |
| | | CT13O Maxell XLI-S90 | £2.22* | | | | |
| | | CT14P Maxell XLI-S90 | £2.22* | | | | |
| | | CT15Q Maxell XLI-S90 | £2.22* | | | | |
| | | CT16R Maxell XLI-S90 | £2.22* | | | | |
| | | CT17S Maxell XLI-S90 | £2.22* | | | | |
| | | CT18T Maxell XLI-S90 | £2.22* | | | | |
| | | CT19U Maxell XLI-S90 | £2.22* | | | | |
| | | CT20V Maxell XLI-S90 | £2.22* | | | | |
| | | CT21W Maxell XLI-S90 | £2.22* | | | | |
| | | CT22X Maxell XLI-S90 | £2.22* | | | | |
| | | CT23Y Maxell XLI-S90 | £2.22* | | | | |
| | | CT24Z Maxell XLI-S90 | £2.22* | | | | |
| | | CT25A Maxell XLI-S90 | £2.22* | | | | |
| | | CT26B Maxell XLI-S90 | £2.22* | | | | |
| | | CT27C Maxell XLI-S90 | £2.22* | | | | |
| | | CT28D Maxell XLI-S90 | £2.22* | | | | |
| | | CT29E Maxell XLI-S90 | £2.22* | | | | |
| | | CT30F Maxell XLI-S90 | £2.22* | | | | |
| | | CT31G Maxell XLI-S90 | £2.22* | | | | |
| | | CT32H Maxell XLI-S90 | £2.22* | | | | |
| | | CT33I Maxell XLI-S90 | £2.22* | | | | |
| | | CT34J Maxell XLI-S90 | £2.22* | | | | |
| | | CT35K Maxell XLI-S90 | £2.22* | | | | |
| | | CT36L Maxell XLI-S90 | £2.22* | | | | |
| | | CT37M Maxell XLI-S90 | £2.22* | | | | |
| | | CT38N Maxell XLI-S90 | £2.22* | | | | |
| | | CT39O Maxell XLI-S90 | £2.22* | | | | |
| | | CT40P Maxell XLI-S90 | £2.22* | | | | |
| | | CT41Q Maxell XLI-S90 | £2.22* | | | | |
| | | CT42R Maxell XLI-S90 | £2.22* | | | | |
| | | CT43S Maxell XLI-S90 | £2.22* | | | | |
| | | CT44T Maxell XLI-S90 | £2.22* | | | | |
| | | CT45U Maxell XLI-S90 | £2.22* | | | | |
| | | CT46V Maxell XLI-S90 | £2.22* | | | | |
| | | CT47W Maxell XLI-S90 | £2.22* | | | | |
| | | CT48X Maxell XLI-S90 | £2.22* | | | | |
| | | CT49Y Maxell XLI-S90 | £2.22* | | | | |
| | | CT50Z Maxell XLI-S90 | £2.22* | | | | |
| | | CT51A Maxell XLI-S90 | £2.22* | | | | |
| | | CT52B Maxell XLI-S90 | £2.22* | | | | |
| | | CT53C Maxell XLI-S90 | £2.22* | | | | |
| | | CT54D Maxell XLI-S90 | £2.22* | | | | |
| | | CT55E Maxell XLI-S90 | £2.22* | | | | |
| | | CT56F Maxell XLI-S90 | £2.22* | | | | |
| | | CT57G Maxell XLI-S90 | £2.22* | | | | |
| | | CT58H Maxell XLI-S90 | £2.22* | | | | |
| | | CT59I Maxell XLI-S90 | £2.22* | | | | |
| | | CT60J Maxell XLI-S90 | £2.22* | | | | |
| | | CT61K Maxell XLI-S90 | £2.22* | | | | |
| | | CT62L Maxell XLI-S90 | £2.22* | | | | |
| | | CT63M Maxell XLI-S90 | £2.22* | | | | |
| | | CT64N Maxell XLI-S90 | £2.22* | | | | |
| | | CT65O Maxell XLI-S90 | £2.22* | | | | |
| | | CT66P Maxell XLI-S90 | £2.22* | | | | |
| | | CT67Q Maxell XLI-S90 | £2.22* | | | | |
| | | CT68R Maxell XLI-S90 | £2.22* | | | | |
| | | CT69S Maxell XLI-S90 | £2.22* | | | | |
| | | CT70T Maxell XLI-S90 | £2.22* | | | | |
| | | CT71U Maxell XLI-S90 | £2.22* | | | | |
| | | CT72V Maxell XLI-S90 | £2.22* | | | | |
| | | CT73W Maxell XLI-S90 | £2.22* | | | | |
| | | CT74X Maxell XLI-S90 | £2.22* | | | | |
| | | CT75Y Maxell XLI-S90 | £2.22* | | | | |
| | | CT76Z Maxell XLI-S90 | £2.22* | | | | |
| | | CT77A Maxell XLI-S90 | £2.22* | | | | |
| | | CT78B Maxell XLI-S90 | £2.22* | | | | |
| | | CT79C Maxell XLI-S90 | £2.22* | | | | |
| | | CT80D Maxell XLI-S90 | £2.22* | | | | |
| | | CT81E Maxell XLI-S90 | £2.22* | | | | |
| | | CT82F Maxell XLI-S90 | £2.22* | | | | |
| | | CT83G Maxell XLI-S90 | £2.22* | | | | |
| | | CT84H Maxell XLI-S90 | £2.22* | | | | |
| | | CT85I Maxell XLI-S90 | £2.22* | | | | |

| 1988 Catalogue Page No. | VAT Inclusive Price | 1988 Catalogue Page No. | VAT Inclusive Price | 1988 Catalogue Page No. | VAT Inclusive Price | 1988 Catalogue Page No. | VAT Inclusive Price | 1988 Catalogue Page No. | VAT Inclusive Price |
|-------------------------------|--------------------------------|-------------------------------|------------------------------------|-------------------------------|----------------------------------|-------------------------------|----------------------------|--------------------------------|---------------------------------|
| HL22P | Double Sw Socket.....£3.99 | BF04E | Bolt 4BA 1in.....41p | FLO6G | Ver0 14354.....45p | BL34M | AD 162.....£0.00 | QW356 | |
| Page 169 | | LR526 | Bolt 4BA 1 1/2in.....52p | FLO8J | Ver0 10346.....£1.80 | YB85W | AY-3-1350.....£4.00 | QW79L | 40257BE.....£1.98 |
| HL26H | Cooker Switch.....£7.50 | BF06E | Bolt 6BA 1/4in.....21p | FLO9K | Ver0 10347.....£1.95 | QB39N | BC142.....29p | UB37S | 74HC153.....69p |
| HL83E | Switched Flex Outlet.....£4.25 | BF07H | Bolt 6BA 1/2in.....26p | FL10L | Ver0 10348.....£2.40 | QB40T | BC143.....29p | UB77J | 74HC356.....£1.40 |
| HL88T | Blanking Plate.....88p | BF07H | Bolt 6BA 1/4in.....26p | | | QB40T | BC441.....39p | | |
| HL87U | 20A Plateswitch.....£2.99 | BF09K | Bolt 8BA 1/2in.....25p | Page 235 | | QB72P | BC461.....39p | Page 358 | |
| HL89W | Light Switch M3.....£1.29 | BF09K | Bolt 8BA 1/4in.....25p | FL20W | Pin 2140.....£1.95 | QB72P | BC461.....39p | QX30H | 4418BE.....DIS |
| HL90X | Light Swch DT Single.....£1.30 | JC29G | 100 Bolt 2BA 1/2in.....£3.00 | HY16S | Wiring Pen.....£5.95 | QY53H | BF173.....29p | | |
| HL91Y | Light Swch Dual.....£2.35 | JC30H | 100 Bolt 2BA 1in.....£3.90 | | | QF17T | BF258.....29p | | |
| | | JC31J | 100 Bolt 4BA 1/4in.....£1.55 | Page 238 | | | | Page 363 | |
| Page 170 | | JC32K | 100 Bolt 4BA 1/2in.....£1.99 | XG20W | CM100 PCB Kit.....DIS | YH94C | BT149B.....DIS | YB85Y | NES534A.....£1.20 |
| YB14Q | Sur Patt 20mm Sngl.....65p | JC33L | 100 Bolt 4BA 1in.....£1.35 | RK40T | Film FFP12.....DIS | WD20W | CA3189E.....£1.72 | Page 365 | |
| YB15S | Sur Patt 29mm Sngl.....69p | JC34M | 100 Bolt 4BA 1 1/2in.....£2.70 | YJ43W | Film Sheet Large.....DIS | WD21X | CA3240E.....£1.15 | QW21X | CA3240E.....£1.15 |
| YB17T | Sur Patt 47mm Dble.....£1.99 | JC35Q | 100 Bolt 6BA 1/4in.....£1.38 | RK42V | PCB006 Pack.....DIS | WH63T | ICM 7655.....88p | | |
| *FD02C | Lampholder 702.....72p | JC36P | 100 Bolt 6BA 1/2in.....£1.77 | YJ40T | Developer FDB.....DIS | QH38R | LM377.....£2.85 | Page 366 | |
| *LB83T | Bayonet LH/DR.....98p | JC37S | 100 Bolt 6BA 1in.....£2.80 | | | WQ35Q | LM397.....£1.98 | QW21X | TL027CP.....69p |
| | | JC38R | 100 Bolt 8B 5/16in.....£1.87 | Page 240 | | | | RA71N | TL082CP.....58p |
| | | JC39N | 100 Bolt 8BA 1/2in.....£1.87 | 9W40T | 1C Pads 200.....£7.95 | Page 326 | | | |
| | | JC40T | 100 Bolt 8BA 3/4in.....£1.95 | | | WQ38R | LM2917.....£3.45 | Page 369 | |
| | | LR54J | C/S Screw 2BA 1/2in.....19p | PROJECTS & MODULES | | RA94C | LM2984C.....£2.99 | QW38R | LM377.....£2.85 |
| | | BF10L | C/S Screw 4BA 1/2in.....14p | Page 245 | | WQ40T | LM3911.....£2.00 | Page 374 | |
| | | BF13P | C/S Screw 6BA 1in.....72p | LW73Q | RTX3 Doppler Kit.....£59.95 | WQ41U | LM3914.....£3.00 | WQ35Q | LM387.....£1.98 |
| | | JC41U | 100 C/S 2BA 1/2in.....£1.29 | Page 246 | | YB96L | LM3915.....£2.00 | Page 377 | |
| | | JC42V | 100 C/S 4BA 1/2in.....86p | LM13P | I/R Prox Detector Kit.....£8.95 | FD92A | MAX232C.....£6.50 | QW49D | MC3340P.....DIS |
| | | JC43W | 100 C/S 6BA 1/4in.....52p | Page 249 | | QH49D | MC3340P.....DIS | Page 379 | |
| | | JC44X | 100 C/S 6BA 1/2in.....58p | GB51F | Power PCB.....£1.98 | QH54J | MC3340P.....45p | YB85Y | NE 566.....£1.60 |
| | | JC45Y | 100 C/S 8BA 1in.....£1.50 | LK34M | 2.5W Pwr Cntrlr Kit.....DIS | QH58P | MF102.....40p | YB85Y | NE534A.....£1.20 |
| | | JC46A | 100 C/S 8BA 1/2in.....95p | LM01B | L/Acid Bat Chrg Kit.....£42.95 | *WQ55K | NE 544.....52p | QY38R | 12A Power Controller.....DIS |
| | | | | Page 251 | | QD12C | SAM77.....DIS | Page 380 | |
| | | Page 174 | | LW82D | Digi-Tel Main Kit.....£144.95 | WQ73Q | TIP122.....80p | UJ45Y | UM3561.....95p |
| | | WH19V | Nylon Nut M3.....5p | Page 253 | | QH58P | TIP3055.....80p | UJ46A | UM3611.....DIS |
| | | Page 175 | | LK42V | Car Batt Monitor.....£8.95 | QD12C | TIP3055.....80p | Page 383 | |
| | | FW13P | Studding 2BA.....40p | Page 254 | | WQ73Q | TIP122.....80p | WQ20W | CA3189E.....£1.72 |
| | | Page 177 | | Page 254 | | YH78K | TL497A.....£2.10 | Page 385 | |
| | | HL13P | Aly Sheet 16 swg.....£3.95 | LK61R | 4 Ch Servo Cntrlr Kit.....£25.95 | UF37S | UA78540.....£2.85 | QL41U | 2N414Z.....92p |
| | | HEATHKIT | | Page 255 | | *UJ45Y | UM3561.....95p | Page 389 | |
| | | Page 178 | | LK45Y | Servo & Driver Kit.....£95.95 | UJ46A | UM3611.....DIS | *WQ55K | NE 544.....£2.80 |
| | | MF27E | Heathkit SB-1000.....£69.95 | Page 262 | | WQ56E | VN66AF.....£1.05 | Page 392 | |
| | | Page 180 | | LK88V | VU Meter Kit.....£8.95 | UH22A | V9398.....£28.95 | WQ40T | LM3911.....£2.00 |
| | | HK24B | HN-31A Antenna Load.....£24.95 | LK89W | Headphone Monitr Kit.....£35.95 | QL41U | ZN414Z.....92p | Page 393 | |
| | | Page 182 | | Page 263 | | QR23A | ZN3053.....29p | WQ41U | LM3914.....£3.00 |
| | | HK45Y | EB-1010 Elect DcInry.....£14.99 NV | XH21X | ME537.....DIS | YH96L | ZN3055.....29p | YB85Y | LM3915.....£3.00 |
| | | HK49E | ES-3140 Hobby Elect.....£34.95 | Page 266 | | QR49D | 2N5458.....DIS | YH30H | 74C917.....£1.36 |
| | | HK32K | EE-3100 Basic Elnry.....£24.99 NV | LM21X | 23 Litre Cabinet Kit.....£30.95 | QD03H | 2SA872.....46p | Page 395 | |
| | | Page 186 | | LMK2D | 40 Litre Cabinet Kit.....£36.95 | QW13P | 2708 250ns.....£8.50 | QH67X | NE 566.....52p |
| | | HK81C | EE-1001 Passive Crs.....£39.95 | Page 272 | | QD07H | 2718 450ns.....£4.50 | Page 396 | |
| | | HK82D | EE-1002 Transr Crs.....£44.95 | LM47T | PA Kit.....£20.95 | *QD08K | 2764 250ns.....£4.50 | QH67X | NE 566.....52p |
| | | HM05F | EE-1003 Amig Dsr Crs.....£44.95 | Page 273 | | UH95D | 27128 250ns.....£8.50 | Page 397 | |
| | | Page 187 | | RK25C | Stereo Amp Heatsink.....£1.20 | QW79L | 40257BE.....£1.98 | YH83T | ICM 7555.....88p |
| | | MD55K | EE-1004 Dig Circuits.....£49.95 | XG16S | Stereo Amp Woodwork.....DIS | QX30H | 4418BE.....DIS | Page 398 | |
| | | HK84F | ETW-1000 Assembled.....£324.95 | XG15R | Stereo Amp Chassis.....£6.95 | UH93B | 4464 150ns.....£8.95 | YH78K | TL497A.....£2.10 |
| | | Page 188 | | GA71N | Stereo Amp PCB.....£7.50 | Page 329 | | Page 399 | |
| | | HK17T | EE-3404 Adv Mic Crs.....DIS | GA78H | Stereo Amp Sw PCB.....80p | QW39Z | 5V Zener 8V2.....98p | UF37S | UA78540.....£2.85 |
| | | Page 189 | | LW71N | 25W Stereo Amp Kit.....DIS | UF33L | 8116 (446) 150ns.....£2.95 | UF34M | 6264 150ns.....£8.95 |
| | | HM15R | EE-2001 Cmptr Fndmnt.....£44.95 | RK36P | Switch Panel.....£1.60 | RA92A | HM85266AP-15.....£9.50 | RA94C | LM2984C.....£2.99 |
| | | MD28D | EE-2002 Cmptr Pprflr.....£49.95 | GA97F | Stereo Amp IR Decodr.....£3.30 | YF00A | 74LS00.....25p | Page 404 | |
| | | Page 190 | | GA99H | Sio Amp IR Cntrlr.....£1.50 | QX74R | 7403.....28p | Page 408 | |
| | | MD31J | EE-2003 Cmptr Mntnce.....£39.95 | LW77J | Am Remote Cntrlr Kit.....£34.95 | QX74R | 7403.....28p | UH22A | V9398.....£28.95 |
| | | HK86T | ET-100 16-Br Trmr.....£899.95 | Page 276 | | QX74R | 7403.....28p | XH18C | Date Manual V9398.....£5.00 |
| | | Page 191 | | LW88V | Volume Pedal Kit.....£29.95 | YF00D | 74LS03.....40p | Page 409 | |
| | | HK21X | EE-1800 Robotics Crs.....£69.95 NV | Page 287 | | YF00D | 74LS03.....40p | FD92A | MAX232C.....£6.50 |
| | | Page 192 | | *GD87X | F/Store PSU/Mod PCB.....£2.50 | YF27E | 74LS51.....18p | Page 411 | |
| | | HK26D | IG-5280 RF Oscilr.....£79.95 | *LM34M | F/Store PSU/Modulatr.....£9.95 | YF27E | 74LS51.....18p | UF33L | 8116 (446) 150ns.....£2.95 |
| | | HK34M | IB-5281 RCL Bridge.....£88.95 | FL15R | Heatsink.....£1.50 | QD88Y | 7493.....40p | UF34M | 6264 150ns.....£8.95 |
| | | HE98G | IE-5230 CRT Tester.....£169.95 | Page 295 | | QX87U | 7496.....58p | RA92A | HM85266AP-15.....£9.50 |
| | | Page 193 | | XG17T | ZX81 Keyboard Case.....£3.95 | UH30H | 74C917.....£1.36 | QY74R | 41256 150ns.....TEMP |
| | | HK33B | IMA-100-10 DC Probe.....DIS | Page 297 | | Page 330 | | Page 412 | |
| | | KNOBS | | GB43W | ZX81 Hi Res Grph PCB.....£12.95 | QB01B | AC128.....50p | UH93B | 4464 150ns.....£8.95 |
| | | Page 195 | | PROTECTION | | QB02C | AC127.....80p | QW13P | 2708 250ns.....£8.50 |
| | | HB34M | Knob K105L.....98p | Page 301 | | BL34M | AD162.....80p | QD07H | 2718 450ns.....£4.50 |
| | | HB36P | Knob K15.....48p | WR95D | Fuse 1/4 50mA.....20p | Page 332 | | *QD08K | 2764 250ns.....£4.50 |
| | | HB40T | Knob K45.....DIS | *WR96E | Fuse 1/4 150mA.....18p | QD03H | 2SA872.....46p | Page 413 | |
| | | Page 196 | | Page 302 | | QB39N | BC142.....29p | YH88V | 27128 250ns.....£5.95 |
| | | WL55K | 15mm Collet Pntr Red.....DIS | YV47B | Surface BA Reed.....£1.20 | QB40T | BC143.....29p | UH95D | 27C128 250ns.....£8.50 |
| | | YG40T | Low-Cost Collet Knob.....38p | FP10L | Surface NSL Reed.....DIS | QB72P | BC461.....39p | Page 418 | |
| | | Page 197 | | Page 305 | | QB72P | BC461.....39p | Page 422 | |
| | | RX94C | Cord Drum Large.....£1.40 | LM15R | Digit-Alarm Extl Sndr.....£19.95 | Page 333 | | FG64U | Coverslide 4Y.....DIS |
| | | MICROPHONES | | YN77J | Ext Sounder Box.....£3.95 | QR23A | 2N3053.....29p | Page 423 | |
| | | Page 199 | | RADIO CONTROL | | QH54J | MCJ340.....45p | FG65V | Coverslide 6W.....38p |
| | | FK45Y | One Point Stereo Mic.....DIS | Page 308 | | WQ73Q | TIP122.....80p | SPEAKERS & SOUNDERS | |
| | | MUSICAL & EFFECTS | | YP25C | Apache Car.....£39.95 | QH58P | TIP2955.....80p | Page 425 | |
| | | Page 211 | | Page 309 | | YH96G | 2N3055.....55p | Page 427 | |
| | | XG30H | BBD Echo EM-006.....£99.95 | XJ19V | Wld Cat Car Kit.....£29.95 | QY53H | BF173.....29p | Page 428 | |
| | | OPTO-ELECTRICAL | | Page 311 | | QF17T | BF258.....29p | YB36T | I/R Stereophone.....£39.95 |
| | | Page 224 | | XJ12N | Killer Kit Car.....£44.95 | QD94D | 2N5458.....DIS | Page 430 | |
| | | HB09K | LDR RPY58A.....£1.20 | Page 312 | | QH58P | TIP2955.....80p | JY03D | Crossed HPX2.....£9.95 |
| | | Page 225 | | JF57M | Killer 2100.....£2.50 | UH93B | 4464 150ns.....£8.95 | WF46A | Controlled Crossover.....£12.95 |
| | | XR56L | Imm Light Guide.....64p | JF58N | Killer 2110.....£2.95 | Page 336 | | Page 431 | |
| | | ORGAN COMPONENTS | | XJ48A | Beagle Car Kit.....£89.95 | QX36P | 5W Zener 8V2.....98p | BK30H | Sprk Fixing Clamp.....20p |
| | | Page 227 | | Page 313 | | Page 337 | | Page 432 | |
| | | QL02C | SAM77.....DIS | JE78K | Beagle BG-17.....£2.50 | YH94C | BT149B.....DIS | WF18U | Elliptical Spkr CM742.....DIS |
| | | Page 228 | | *JF43W | Beagle BG-84.....80p | Page 340 | | *WF12N | Hi-Fi Spkr 40W Binch.....£10.95 |
| | | *XB10L | DM02.....£18.95 | Page 314 | | YF00A | 74LS00.....25p | Page 436 | |
| | | *XB11M | DM02T.....£16.95 | XJ47B | RC Set with Meter.....£39.95 | QX74R | 7403.....28p | YP64U | Personal Spkr Set.....£5.95 |
| | | PANEL METERS | | YF62S | 2 Cnn Prop RC System.....£39.95 | QW73Q | TIP122.....80p | YP72P | Extendable Spkr.....DIS |
| | | Page 231 | | Page 316 | | QR82D | 7438.....38p | SWITCHES & RELAYS | |
| | | RW98G | 2in Ph Mt 100-0-100uA.....£5.95 | YG14D | Servo Mechanism.....£5.95 | UH08J | 74HC10.....35p | Page 441 | |
| | | FM98G | 2in Pan Meter 50uA.....£5.95 | RESISTORS | | Page 343 | | Page 442 | |
| | | RW92A | 2in Pan Meter 100uA.....£5.95 | Page 318 | | YF27E | 74LS51.....18p | WF18U | Elliptical Spkr CM742.....DIS |
| | | RW94C | 2in Pan Meter 1mA.....£5.95 | W | W/W Min 0.22R to 1R.....28p | Page 346 | | *WF12N | Hi-Fi Spkr 40W Binch.....£10.95 |
| | | RX33L | 2in Pan Meter 100mA.....£5.95 | L | 7W W/W.....38p | Page 348 | | Page 436 | |
| | | RX35Q | 2in Pan Meter 1A.....£5.95 | Page 319 | | UB24B | 74HC107.....46p | YP64U | Personal Spkr Set.....£5.95 |

NOW

SUBSCRIBE BEFORE OCT 31st

Cover price will increase after this date!

6 ISSUES A YEAR!

There are 6 tremendous reasons why you should subscribe to Electronics – The Maplin Magazine

- * Every issue is sent to you as soon as it's printed, post free.
- * Packed with interesting and novel projects that you can build with all components easily available.
- * Many features on electronics subjects to keep you up-to-date with latest developments.
- * Minimum advertising space means more pages for you to read.
- * Still far cheaper than the 'Monthlies', most of which are now £1.30 or more per issue.
- * Six times a year means a 50% increase in articles and projects for you to read and build.

To subscribe just send a cheque/postal order for £5.10, made payable to Maplin Electronics, to P.O. Box 3, Rayleigh, Essex SS6 8LR. **OR** you can take advantage of our offer of two free issues by completing the coupon below and agreeing to pay by Credit Card or Direct Debit. The two free issues offer only applies if you use one of these two methods of payment. Simply fill in the 'Payment by Credit Card' or 'Payment by Direct Debiting Mandate' and return it to Maplin. Every time, about 1 month before your subscription is due, we will send you a letter giving details of the subscription rate for the next year and telling you the date on which we will charge your Credit Card or debit your bank account. If you do not wish to continue your subscription, you have until that date to let us know, and we will then cancel your authority to bill your Credit Card or cancel your mandate. Otherwise, if you do nothing, your subscription will continue. The authority or mandate you give us does not allow us to charge anything other than the Maplin Magazine subscription. The benefit to you is that you no longer need to remember to re-new your subscription or send off any more cheques or postal orders. Payment is made automatically.



TAKE THE NEXT TWO ISSUES OF THIS MAGAZINE FREE!!

Because we're so certain that once you've seen the Maplin Magazine you'll want to continue to receive it, we're offering to send you the next two issues free of charge with absolutely no obligation to continue. Just fill in the details below and if after receiving two issues you do not wish to continue, just let us know at least one month before the next issue is due and we will cancel your subscription. The two free issues will be yours to keep whatever you decide. If you already have a subscription, fill in the details below and we'll add two issues free of charge to your current subscription. **SEND NO MONEY NOW.** About 2 weeks before the third issue is due, we will charge you £5.10 for the next six issues, unless you have cancelled. This offer is not available to those already paying by Direct Debit or Continuous Credit Card or those who have stopped payment by either method within the last two years. Please start my subscription with issue 29.

This offer is open until 31st October 1988.

★ PLEASE ADD YOUR ADDRESS, SEE BOTTOM RIGHT ★

PAYMENT BY CREDIT CARD. Please charge my Credit Card Account

Access Visa American Express Mapcard

I authorise you until further notice in writing to debit my CREDIT CARD account with £5.10 and in future, with any amounts which, after notification, MAPLIN ELECTRONIC SUPPLIES LTD. may debit thereto in respect of my subscription to the Maplin Magazine.

| | | | | | | | | | |
|-------------|--|--|--|--|--|--|------|--|--|
| Account No. | | | | | | | | | |
| | | | | | | | | | |
| Signature | | | | | | | Date | | |

OR

PAYMENT BY DIRECT DEBITING MANDATE in favour of Maplin Electronic Supplies Ltd., P.O. Box 3, Rayleigh, Essex SS6 8LR. Direct Debit payment option is only open to customers with bank accounts in the UK including Channel Isles, Isle of Man and N. Ireland. Please note: Instructions cannot be accepted to charge Direct Debits to a Deposit or Savings Account.

| | |
|----------------|---------------------|
| Bank Sort Code | Bank Account Number |
| | |

| |
|-------------------------------|
| Name of Account to be debited |
| |

| |
|-------------|
| The Manager |
| |
| |
| |
| |

I authorise you until further notice in writing to charge my account with you any amounts which MAPLIN ELECTRONIC SUPPLIES LTD. may debit thereto by Direct Debit in respect of my subscription to the Maplin Magazine.

I will inform the bank in writing if I wish to cancel this instruction.

I understand that if any direct debit is paid which breaks the terms of this instruction, the bank will make a refund.

| | |
|-----------|------|
| Signature | Date |
| | |

Enter your address and Maplin customer number, if known.

| | |
|--|-----------|
| | |
| | |
| | |
| | |
| | Post Code |

Electronics is changing!

Good news from Maplin!

From the next issue of Electronics, your favourite hobby magazine will take a giant leap forward. As well as the new style cover, better quality paper and FULL COLOUR sections, Electronics will be published BI-MONTHLY. Yes, 6 times a year will mean a 50% increase in articles and projects for you to read and build, and the quality of the projects will stay just as high as it is now!

Plus

With your first 'New Look' edition you will receive a handy FREE craft knife, a gift from us to help you enjoy your hobby even more!

Now

Is the time to take out a subscription if you haven't done so already! Turn to page 34 and check out the details! Then you'll be sure of receiving your first copy and your FREE craft knife!!



Maplin's 20 BEST SELLING BOOKS!

These are our top twenty best selling books based on mail order and shop sales during April, May and June 1988. Our own magazines and publications are not included. The Maplin order code of each book is shown together with page numbers for our 1988 catalogue. We stock over 250 different titles, covering a wide range of electronics and computing topics.

2



Loudspeaker Enclosure Design and Construction (WM82D) Cat. P82. Previous Position: 1. Price £3.00

3




IC555 Projects, by E.A. Parr. (LY04E) Cat. P80. Previous Position: 6. Price £2.95

4



MIDI Projects, by R.A. Penfold. (WP49D) Cat. P83. Previous Position: 3. Price £2.95

5

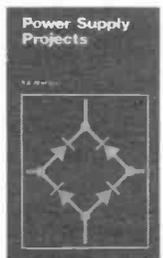

Power Supply Projects, by R.A. Penfold. (XW52G) Cat. P78. Previous Position: 4. Price £2.50

6



Mastering Electronics, by John Watson. (WM60Q) Cat. P77. Previous Position: 2. Price £4.25

Number One

Home Electrics
by Geoffrey Burdett

This book shows you clearly and concisely how to rewire your house, add additional circuits, wire a shower, cooker, immersion heater etc. Clear detailed instructions mean that you can safely rewire your house. (RQ22Y) Cat. P71. Previous Position: New Entry.


Price £4.95

7




Introduction to Electronics, by Pam Beasant. (WP50E) Cat. P77. Previous Position: 7. Price £2.95

10

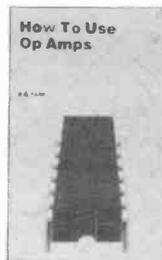

How to Use Op-Amps, by E.A. Parr. (WA29G) Cat. P76. Previous Position: 17. Price £2.25

13

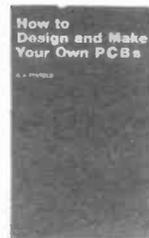


How to Design and Make Your Own PCB's, by R.A. Penfold. (WK63T) Cat. P76. Previous Position: 12. Price £1.95

18



Adventures with Micro-Electronics, by Tom Duncan. (XW63T) Cat. P77. Previous Position: 10. Price £1.95

8

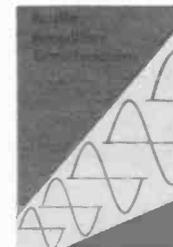

Audio Amplifier Construction, by R.A. Penfold. (WM31J) Cat. P81. Previous Position: New Entry. Price £2.25

11



International Transistor Equivalents Guide, by Adrian Michaels. (WG30H) Cat. P73. Previous Position: 11. Price £3.50

14




50 Projects Using Relays, SCR's and Triacs, by F.G. Rayer. (RH30H) Cat. P78. Previous Position: New Entry. Price £2.95

19



Towers' International Transistor Selector Update 3, by T.D. Towers. (RR39N) Cat. P73. Previous Position: New Entry. Price £14.99

9

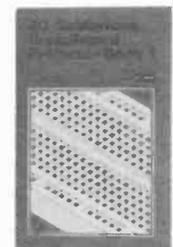

30 Solderless Breadboard Projects Book 1, by R.A. Penfold. (WAS1F) Cat. P77. Previous Position: New Entry. Price £2.45

12




Electronic Security Devices, by R.A. Penfold. (RL43W) Cat. P79. Previous Position: 13. Price £2.50

15



Building Your Own Working Fibre-Optic Infrared and Laser Space-Age Projects, by Robert E. Lannini. (WPT7I) Cat. P81. Previous Position: New Entry. Price £12.40

20

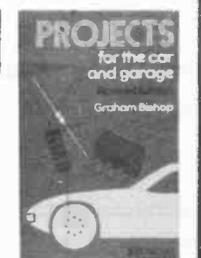

Projects for the Car and Garage, by Graham Bishop. (XW31J) Cat. P79. Previous Position: 8. Price £5.50

16



More Advanced Electronic Music Projects, by R.A. Penfold. (WP44X) Cat. P83. Previous Position: New Entry. Price £2.95

17



Electronic Music Projects, by R.A. Penfold. (XW40T) Cat. P82. Previous Position: New Entry. Price £2.50

Exploring Radio

by *Graham Dixey C. Eng., M.I.E.R.E.* Part 4

Introduction

This radio makes use of the very versatile ZN414 radio chip but, unlike the little personal receiver, whose construction was described in the last issue of 'Electronics', this one has a rather more 'gutsy' output. This is obtained by the use of an audio amplifier chip, the TBA820M. This has a power capability of up to about 1.2 watts of audio power, depending upon the supply voltage and the choice of speaker. It is quite happy with any supply voltage between 3V and a maximum value dependent upon the speaker impedance, as follows.

4 ohm speaker – 9V maximum
8 ohm speaker – 12V maximum
16 ohm speaker – 16V maximum

However, in this design, the d.c. supply has been set at 9V so that any speaker with a coil impedance of 4 ohms or greater can be used. The prototype, shown in Photo 1, used an 8 ohm speaker and gave excellent results. The recommended value of supply voltage should be adhered to because it is related also to the design of the d.c. feed to the ZN414.

A further feature of this receiver is that it is dual waveband, with a choice of either medium-wave or long-wave listening selected with a slide switch. Photo 2 shows the fully assembled pcb.

The Ferrite Rod Aerial

Two separate coils are wound on a 100mm long ferrite rod. The medium wave coil consists of 55 turns of 30 swg enamelled copper wire (E.C.W.). These should be 'close wound', i.e. no gaps between turns. This coil should be wound fairly close to one end of the rod so as to leave plenty of room for the long wave coil. The latter consists of 250 turns which are 'scramble wound'. This means

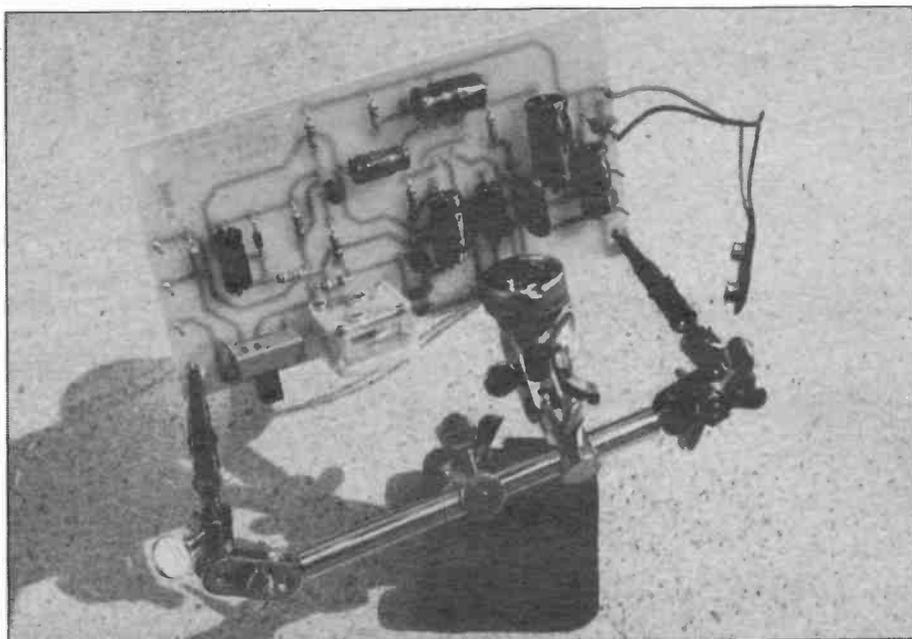


Photo 1. The prototype TRF receiver under construction. A jig of this type greatly helps in handling PCBs.

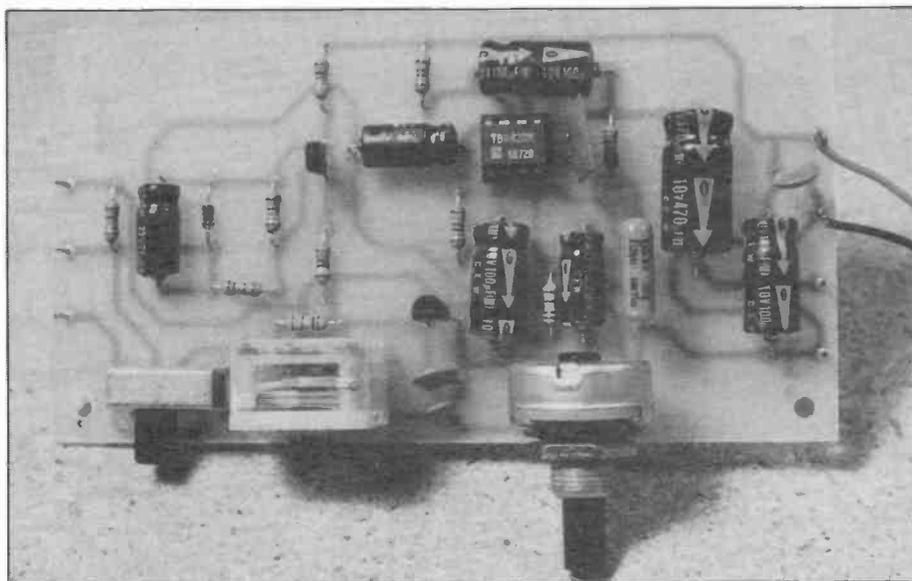


Photo 2. The fully assembled board of the TRF receiver. Note particularly the polarity of the electrolytic capacitors and the placement of other components.

that all attempts at neatness are cast aside (they're impossible anyway without a coil winding machine) and the turns are simply wound tightly over each other. If two or three centimetres of space are allowed for this coil and the turns, as they are laid on, are wound on first in one direction and then in the other, the general result should be a fairly uniform coil with just a hump in the middle (see photograph 3). The coils can be secured with short lengths of PVC tape but, in the example shown, 'superglue' was used instead. The usual precautions should be observed when using this adhesive, of course.

The Radio-Frequency Section

Looking at Figure 1 you can see that each of the coils is selected as required by a slide switch. A 220k resistor is connected across the long wave coil to improve the frequency response. Tuning is by a 150pF variable capacitor, which is provided by using the 'aerial' section of an AM Varitune tuning capacitor assembly. The input stage is decoupled by the usual filter consisting of a 100k resistor and a 10nF ceramic disc capacitor (R2 and C1). A 100nF ceramic disc decouples the output of the ZN414. This output connection also serves as the d.c. feed point for the ZN414 and is provided by a drive circuit, based around the ZTX300 transistor TR1. The supply voltage is dropped from 9V to 4.7V by R6, this value being stabilised by the zener diode ZD1. The emitter resistor, R5, of TR1 also sets the level of the Automatic Gain Control (A.G.C.) for the ZN414.



Photo 3. Compare the neatness of the medium wave coil (secured with glue) and the 'scramble wound' long wave coil (secured with a piece of PVC tape).

The Audio Amplifier

The output of the ZN414 is developed across the volume control RV1 and is coupled to the input of IC2 by C4. This chip has a number of discrete components associated with it, which establish its operating conditions and ensure its stability. The arrangement shown was found to be completely stable and gave an output of acceptable quality, bearing in mind the limitations of the fairly restricted bandwidth of a.m. transmissions anyway. The audio output is coupled to the speaker through a 470µF capacitor, C10. The d.c. supply to the receiver is

decoupled by the capacitors C11 and C12.

General Comments

In the case of the capacitors C11 and C12, some readers may wonder why a small value capacitor (C12 = 100nF) should be included in parallel with a very large value capacitor, in this instance C12, which is 100µF. This is a situation which occurs in many circuits where high frequencies or high speeds (i.e. digital circuits) are used. The low value capacitor will invariably be specified as a 'ceramic disc' type while the larger capacitor will be found to be of a totally

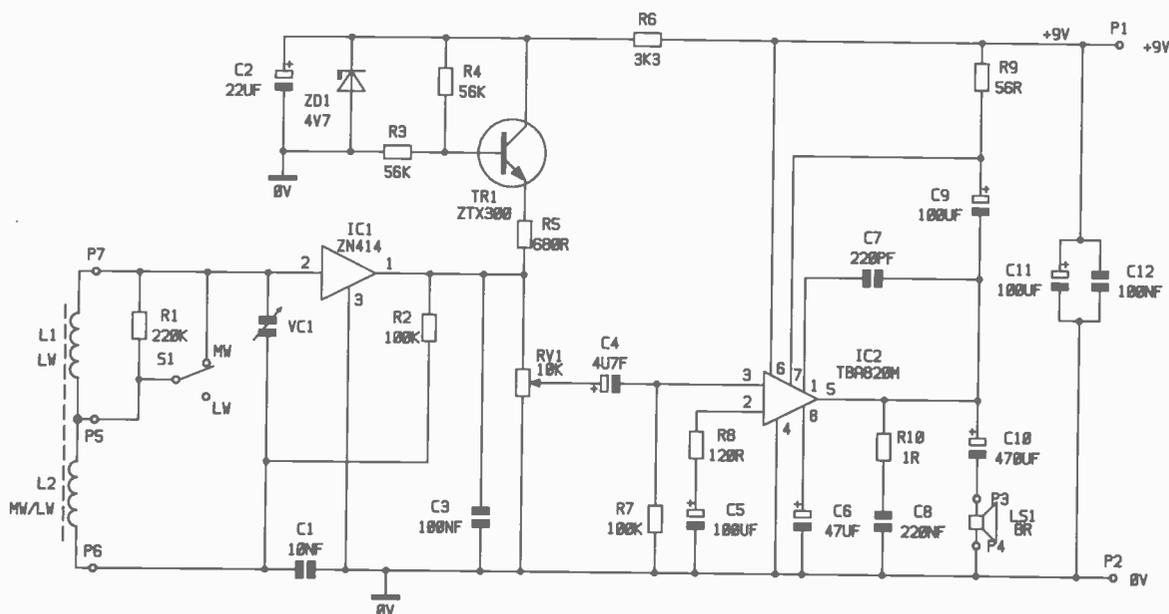


Figure 1. Circuit of the MW/LW TRF Receiver.

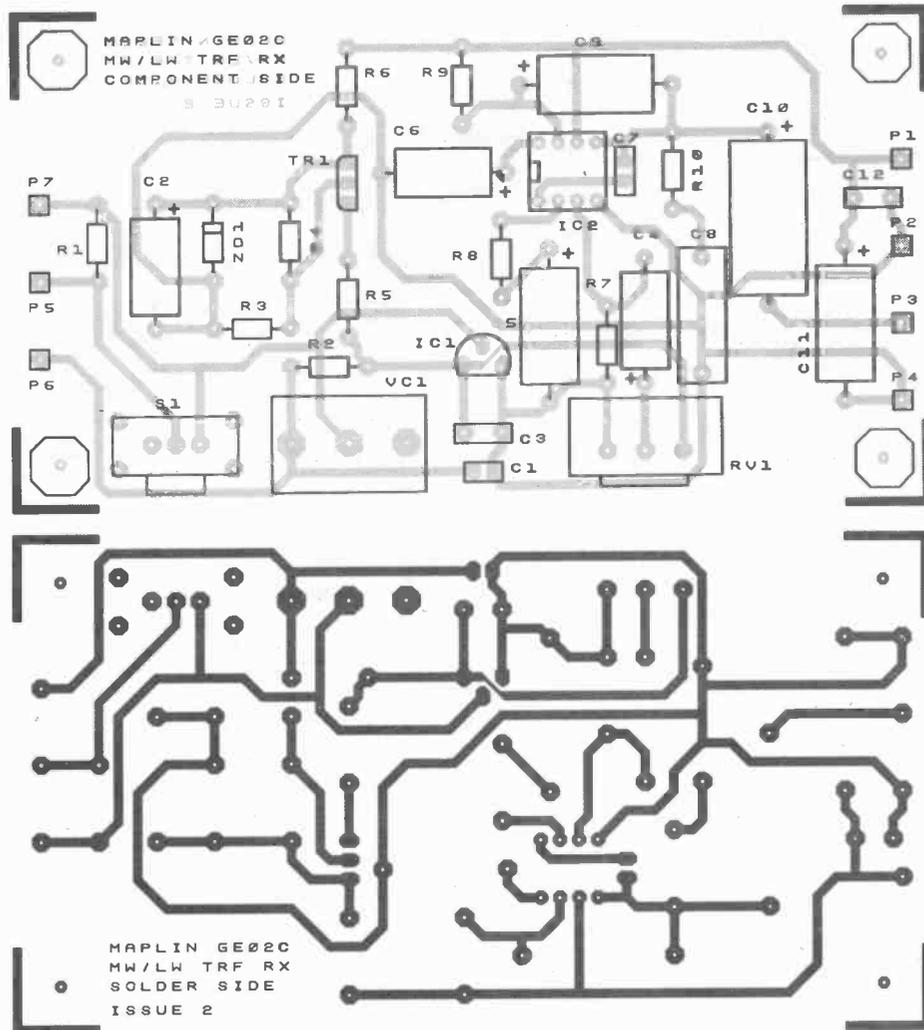


Figure 2. Layout of the PCB.

different type, as in this case where it is an electrolytic. At high frequencies capacitors should be as 'pure' as possible, that is they should exhibit only the properties of capacitance and nothing else. However, because of the way in which electrolytics are made (and this also applies to polyester capacitors), they also have a certain amount of 'self-inductance'. While this would have little effect at audio frequencies, its presence at radio frequencies would prevent the capacitor from acting effectively as a decoupling or r.f. 'bypass' capacitor, simply because it would have too much reactance to the radio signal. For this reason, whenever a ceramic disc capacitor is specified in a circuit, it should never be replaced by a polyester type, just because the value is the same in both cases. One 100nF capacitor is not necessarily the same as another 100nF capacitor!

Assembling and Testing the Receiver

The availability of a PCB for this project, see Figure 2, will ensure both ease of construction and instant success when the power is applied for

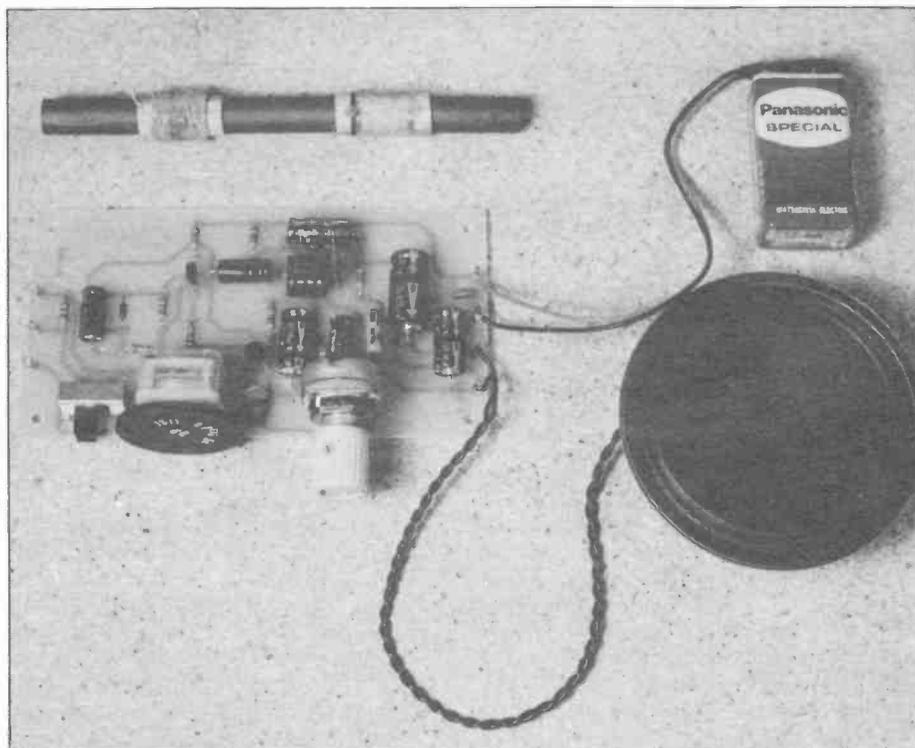


Photo 4. The completed TRF receiver, shown here with the fully assembled 'alternative' ferrite rod aerial.

the first time. It is merely assumed that the builder will check the following.

- the components are inserted in the correct places in the board.
- the polarity of the zener diode and the electrolytic capacitors is observed.
- the base connections of the ZN414 and ZTX300 are correctly noted and these components wired in correctly; check and double check before applying power.
- the TBA820M is plugged into its base the correct way round.
- all soldered joints are made cleanly without any dry joints or 'bridges' between adjacent tracks.

Having observed all of the foregoing points, the power can be applied and the result should be a working radio, Photo 4 shows the completed unit. The only controls are the waveband switch, the tuning capacitor and the volume control, all of which will obviously now be checked.

Should the situation be less than happy, the voltage checks shown in Table 1 can be made. These were made on the prototype, under 'no signal' conditions with a 20k/volt multimeter on the 10V d.c. range. Visual checks should also be made on the components in case one is incorrectly placed.

The readings obtained in practice may differ slightly from those in Table 1 but large variations from these values will indicate a fault condition.

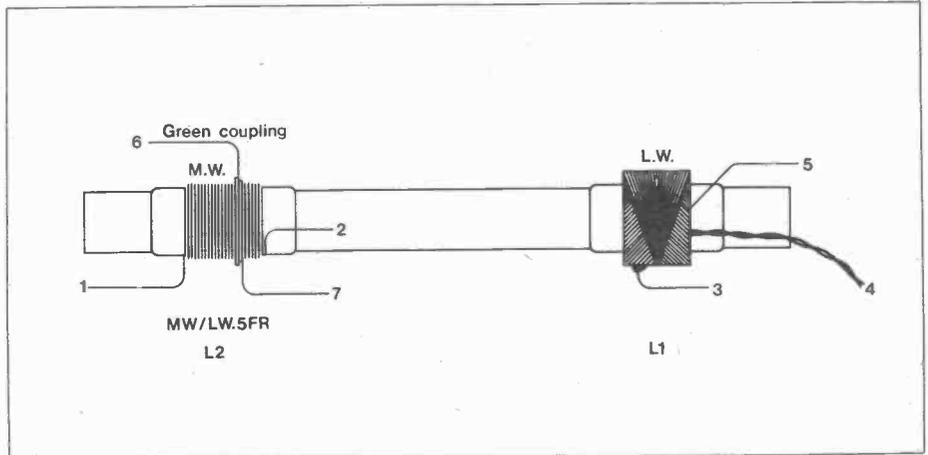


Figure 3. Ferrite rod aerial connections.

| Test Point | Voltmeter Reading |
|---------------------|-------------------|
| Collector of TR1 | 4.0V |
| Base of TR1 | 1.65V |
| Emitter of TR1 | 1.2V |
| Output pin of ZN414 | 0.85V |
| Input pin of ZN414 | 0.6V |
| Pin 1 of TBA820M | 0.6V |
| Pin 2 | 0.5V |
| Pin 3 | 0V |
| Pin 4 | 0V |
| Pin 5 | 4.15V |
| Pin 6 | 9V |
| Pin 7 | 8.8V |
| Pin 8 | 5.6V |

Table 1.

An Alternative Ferrite Rod Aerial

The ferrite rod aerial specified at the start of this article gives an

adequate performance on medium waves but not such a good performance on long waves. This situation can be improved by using a proprietary aerial assembly, such as the one available from Maplin Electronics, and it is listed as an alternative component in the Parts List. It can be used merely by disregarding both the small green coupling coil and the tap on the long wave coil. A drawing of this aerial assembly is included, see Figure 3, and it will be seen that all that needs to be done is to connect the two coils in series by strapping connecting wires 2 to 3 (and taking this junction to pin P5 on the board); wire 1 then goes to pin P6 and wire 5 goes to pin P7. This assembly has the further advantage that it is possible to move the coils along the rod to find the best position; they can then be fixed with a blob of glue.

MW/LW TRF RECEIVER PARTS LIST

RESISTORS: All 0.6W 1% Metal Film

| | | | |
|------|-------------|---|---------|
| R1 | 220k | 1 | (M220K) |
| R2,7 | 100k | 2 | (M100K) |
| R3,4 | 56k | 2 | (M56K) |
| R5 | 680Ω | 1 | (M680R) |
| R6 | 3k3 | 1 | (M3K3) |
| R8 | 120Ω | 1 | (M120R) |
| R9 | 56Ω | 1 | (M56R) |
| R10 | 1Ω | 1 | (M1R) |
| RV1 | 10k Lin Pot | 1 | (FW02C) |

CAPACITORS

| | | | |
|---------|------------------------|---|---------|
| C1 | 10nF Ceramic Disc | 1 | (YR73Q) |
| C2 | 22μF 25V Electrolytic | 1 | (FB30H) |
| C3,12 | 100nF Ceramic Disc | 2 | (YR75S) |
| C4 | 4μF 100V Electrolytic | 1 | (FB18U) |
| C5,9,11 | 100μF 10V Electrolytic | 3 | (FB48C) |
| C6 | 47μF 16V Electrolytic | 1 | (FB38R) |
| C7 | 220pF Ceramic | 1 | (WX60Q) |
| C8 | 220nF Polyester | 1 | (BX78K) |
| C10 | 470μF 10V Electrolytic | 1 | (FB71N) |
| VC1 | AM Varitone | 1 | (FT78K) |

SEMICONDUCTORS

| | | | |
|-----|-----------|---|---------|
| TR1 | ZTX300 | 1 | (QL46A) |
| ZD1 | BZY88C4V7 | 1 | (QH06C) |
| IC1 | ZN414 | 1 | (QL41U) |
| IC2 | TBA820M | 1 | (WQ63T) |

MISCELLANEOUS


| | | | |
|------|------------------|-------|---------|
| L1,2 | Ferrite Rod 810 | 1 | (YG20W) |
| LS1 | 8Ω Speaker | 1 | (YW53H) |
| S1 | Slide Switch R/A | 1 | (FV01B) |
| | PP3 Battery Clip | 1 | (HF28F) |
| | EC Wire 30 swg | 1 | (BL40T) |
| | Pin 2145 | 1 Pkt | (FL24B) |
| | PCB | 1 | (GE02C) |
| | Hook-up Wire | 1 Pkt | (BL00A) |
| | 8-pin DIL Socket | 1 | (BL17T) |

ALTERNATIVE

| | | | |
|------|--------------------|---|---------|
| L1,2 | Ferrite Rod Aerial | 1 | (LB12N) |
|------|--------------------|---|---------|

The following item is available, but is not shown in our 1988 catalogue:
MW/LW TRF Receiver PCB, Order As GE02C
Price £3.95

AVS

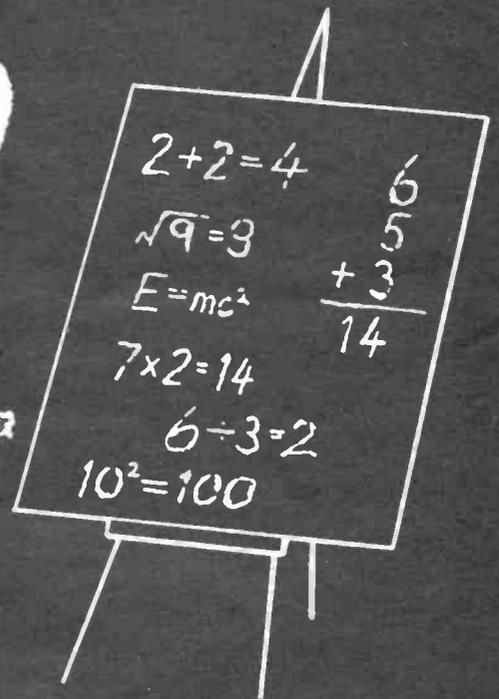

by Jeff Scott Part 1

Complex Numbers

Were you bored by maths at school? Unfortunately, the teaching of maths, not only in schools but also in engineering colleges, tends to be a pure science instead of showing the practical applications to electronics and other branches of engineering.

Mathematics is an exact science with the answers popping out like a pudding out of a pudding bowl, as my teacher used to put it. The frontiers of mathematics, the philosophical side usually predicts the trend that engineering is likely to take.

For instance, the large scale digital processing of signals was shown mathematically long before the technology was available. Fourier analysis showed the components in a waveform much before spectrum analysers were available. Explosions and massive gravitational forces in space, compressing material into a black hole were explained mathematically before the physical phenomena were understood.

Mathematics also serves the purpose of manipulating data into the required form. For example, Laplace transforms transfer an expression from the frequency domain into the time domain. This is useful in electronics since old methods of analogue amplification and filtering were in the frequency domain (frequency division multiplex) whereas modern techniques are in the time domain (time division multiplex).

Complex numbers is an important branch of mathematics with applications to electronic engineering. Mathematicians use the letter 'i' in complex numbers, but 'j' is used in electronics since the letter 'i' in electronics is reserved for current. The 'j' symbol is often called the 'j' operator. The need for a 'j' operator arises for the following reasons. In a circuit that is purely resistive the current is in phase with the voltage, see Figure 1. In a circuit that is reactive, the current may lead or lag the voltage depending on whether the circuit is inductive or capacitive, see Figures 2 and 3.

Argand, a mathematician, was the first to invent the use of 'i' or the imaginary operator. This was useful for explaining the square roots of negative numbers. Consider the equation $x^2 - 16 = 0$. The solution is $x = \pm 4$ which is

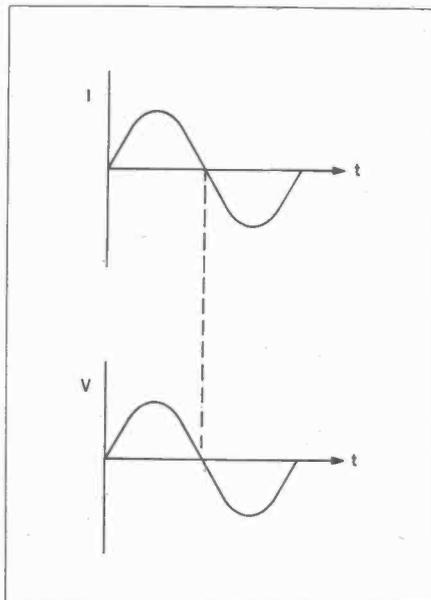


Figure 1. Current in phase with voltage.

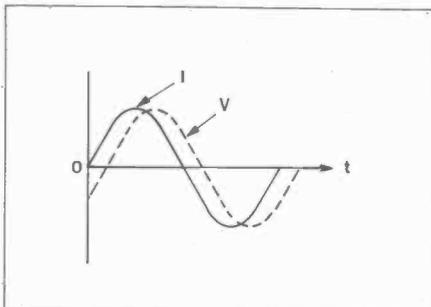


Figure 2. Current leading voltage.

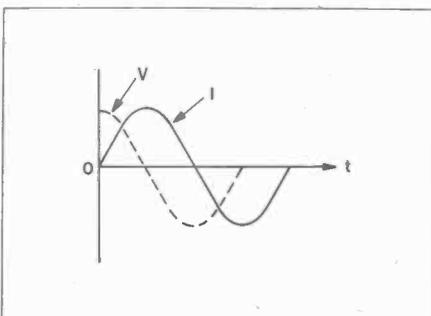


Figure 3. Current lagging voltage.

represented on an Argand diagram as in Figure 4.

But how does one solve the equation $x^2 + 16 = 0$?

$$\text{Here } x^2 = -16$$

$$x = \pm 4 \sqrt{-1}$$

There is no real number which represents the square root of -1 . Argand's solution to this problem was to assign real values along the x axis and imaginary values along the y axis. The solution of $x^2 = -16$ is now shown in Figure 5.

In electrical engineering there are no imaginary values but we call these quadrature

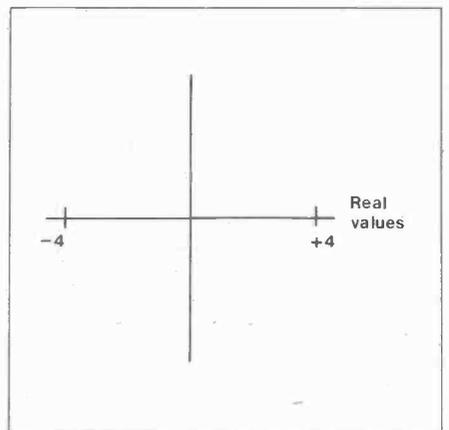


Figure 4. Argand diagram.

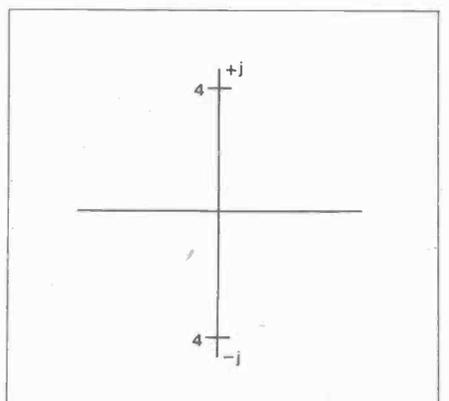


Figure 5. Imaginary (quadrature) components.

components. Therefore a purely resistive circuit will have real components only and a reactive circuit will have quadrature components. An Argand diagram has facilities for describing a circuit that has both real and quadrature components.

From now on we shall use the j symbol and examine the addition and subtraction of complex numbers. An expression that has both real and quadrature components is called a complex number. For instance a number that has 2 units of real value and 4 units of quadrature value would be represented as in Figure 6. The vector P is represented in the general form of: $a + jb$, or $2 + j4$ in this case.

The above method of representing a complex number uses the Cartesian co-ordinates. There is another method of representing complex numbers using polar co-ordinates. In this method, if we define an angle θ (Figure 7) from a reference point then we have one of the attributes defined.

The other attribute must be the length of the vector. Both quantities can be calculated from the cartesian co-ordinates. From Pythagoras' theorem the hypotenuse in Figure 7 is given by:

$$\begin{aligned} & \sqrt{a^2 + b^2} \\ \text{or } & \sqrt{20^2 + 15^2} \\ = & \sqrt{400 + 225} \\ = & \sqrt{625} \\ = & 25 \end{aligned}$$

The tangent of angle θ is $\frac{15}{20} = 0.75$

Therefore $\theta = 36.87^\circ$

The resultant is sometimes called the modulus and the angle is called the argument.

Addition and Subtraction

One of the advantages of the complex notation is that numbers are added and subtracted quickly and easily. This is done by adding or subtracting the real components separately from the quadrature components. The alternative is the tedious method of drawing parallelograms and finding the resultant of only two vectors at a time.

Figure 8 (not to scale) shows three complex numbers $2 + j2$, $-5 + j8$, $-10 - j4$. Adding the real components gives -13 and adding the quadrature components produces $j6$. Therefore the answer is $-13 + j6$. Subtraction is just as easy compared to the parallelogram method of operating on only two vectors each time.

Multiplication and Division of Complex Numbers

Before we deal with the multiplication of complex numbers we must see what happens when we multiply j by itself successively. Since:

$$\begin{aligned} j &= \sqrt{-1} \\ j^2 &= -1 \\ j^3 &= -1 \times j = -j \\ j^4 &= -1 \times -1 = +1 \end{aligned}$$

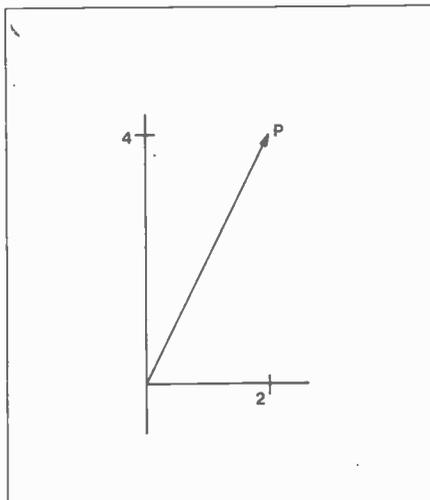


Figure 6. Cartesian co-ordinates.

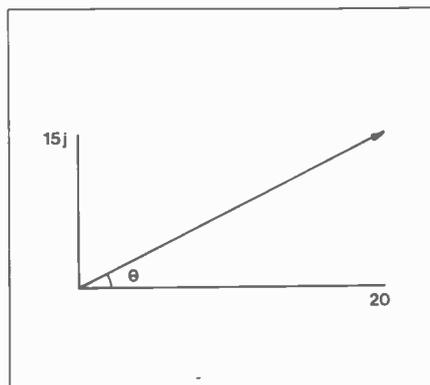


Figure 7. Polar co-ordinates.

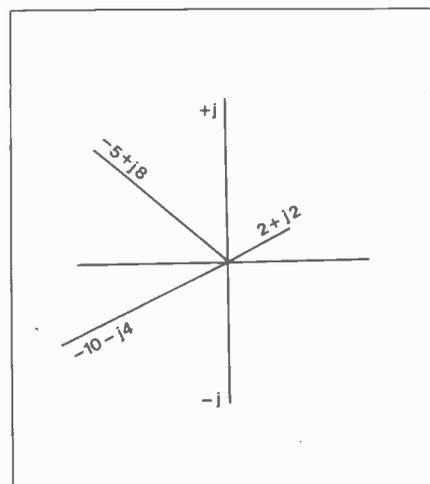


Figure 8. Three complex numbers.

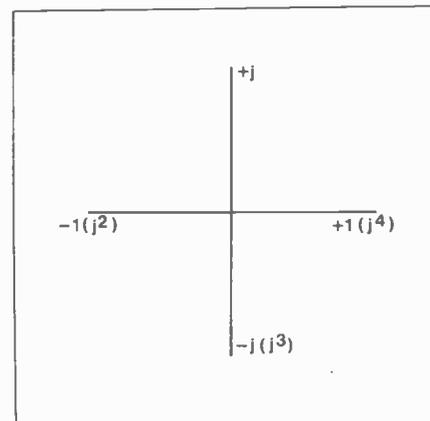


Figure 9. The 'j' operator.

Now we can see why it is called an operator. From Figure 9, each successful multiplication by j has the effect of swinging the value through 90 degrees.

In order to multiply two complex numbers together, we simply expand the brackets in the usual manner.

$$\begin{aligned} \text{For example: } (3 + j^5)(4 - j^2) \\ 12 + j20 - j^22 \end{aligned}$$

$$\begin{aligned} \text{Remembering } j^2 = -1, \\ 12 + j20 + 2 \\ 14 + j20 \text{ is the result.} \end{aligned}$$

Division of complex numbers is just as simple, the answer dropping out like a pudding out of a pudding bowl.

$$\text{For instance } \frac{3 + j5}{4 - j2}$$

First we rationalise the denominator by multiplying it by its conjugate. The conjugate has the same values but opposite phase and has the effect of turning into a wholly real number. The conjugate of $4 - j2$ is $4 + j2$.

$$\begin{aligned} \text{So } & \frac{(3 + j5)(4 + j2)}{(4 - j2)(4 + j2)} \\ = & \frac{12 + j6 + j20 + j^210}{16 + j8 - j8 - j^24} \\ = & \frac{12 + j26 - 10}{16 + 14} \\ = & \frac{2 + j26}{20} \\ = & 0.1 + j1.3 \end{aligned}$$

Multiplication and Division using Polar Co-ordinates

Polar co-ordinates lend themselves quite easily to multiplication and division. The modulus is multiplied separately and the angles (argument) are added together in multiplication:

$$\begin{aligned} r_1 \angle \theta_1 \times r_2 \angle \theta_2 &= r_1 \times r_2 \angle \theta_1 + \theta_2 \\ 6 \angle 35 \times 7 \angle 40 &= 42 \angle 75 \end{aligned}$$

For division the moduli are divided and the angles are subtracted:

Continued on Page 46.

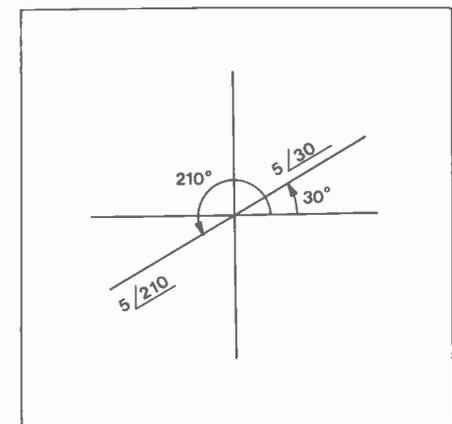


Figure 10. Roots of a number.

NOT FLAT JUST RUN DOWN



by Stephen Potts

Over the past few years the use of Nickel Cadmium or Nicad batteries has become increasingly popular. However, many people are not getting full use from their batteries. This article should help you to understand what the Nicad cell can do when treated properly. It also shows you how to test whether your cell is in a healthy state and if not what can be done about it.

The Nicad cell is a secondary cell because, like a car battery, it can be recharged. The sort of cell that cannot be recharged is known as a primary cell.

Nicads are made in two forms; sintered plate and pocket plate. These are then subdivided into those that are vented and those that are not vented.

Types of Cells

The sintered plate design has the greatest power density. That is, more power can be placed in a small volume and they should last for up to 500 cycles, or 10 years, whichever is the greater. However, they frequently have much shorter lives because of maltreatment and life times of a mere 100 cycles are not uncommon.

The sintered cell Nicad has, like all Nicads, a voltage of 1.25 volts and a capacity that depends on the size of the cell. The capacity is measured in amp-hours and is a product of the time in hours that the cell can deliver a certain current, measured in amps. Thus a cell that is rated at 1.2 amp hours could be expected to deliver 0.6 amps for 2 hours. The typical cell capacities are 0.5 amp-hours for AA cells, 1 to 2.2 amp-hours for C cells and 1.2 to 4 amp-hours for D cells.

Whereas the sintered cell Nicad has active ingredients spread uniformly about the cell, the pocket cell Nicad has the active ingredients in a fine web of pockets. Since these pockets prevent the active material migrating, the cell tends to have a longer life than the sintered glass variety. Coupled with

this is a lower energy density and a higher internal resistance. The pocket cell variety will recharge in a shorter time. If instructions supplied with a battery say; 'recharge for less than three hours', then it is probably a pocket plate cell. If the recharging time is less than 1 hour, then it is definitely a pocket plate cell.

Pocket plate cells are available in C and D sizes, but not usually any smaller. They have a life of 500 to 1000 cycles or 15 years if they are sealed, and a life of 1500 to 2000 cycles or 20 years if vented.

the cell has an output voltage of 1.25 volts which is significantly lower than that of the lead acid cell at 2.2 volts. This may not appear significant, but if you wish to make up a 12 volt pack, it is 6 lead acid cells, but 10 Nicad cells. It is for this reason that many people underestimate the number of cells they are going to need.

Unlike most other cells, the Nicad does not give much warning that it is running down. The voltage will remain approximately 1.25 volts for the full life of the charge and drop very rapidly as it runs



Electrical Characteristics

Having looked at the types of cell available we can now look at the characteristics of the cell. As stated before,

AAA, AA, C, D and PP3 type nicad batteries.

down. The computer program accompanying this article will show this. The point at which voltage drop occurs is usually when around 10% to 20% of the cell capacity is left. Any further discharge - if this

happens on a regular basis – will harm it, shortening its life and lowering its efficiency.

There is a case where it is of use to drain the cell completely, and this is when the cell has 'memory'. Cells that are frequently shallow cycled (that is; fully charged, used for a very short time before being charged again) develop lazy habits and will not deliver more than a shallow capacity. An example of this is the wall mounted torch, often used by the front door of a house. If it is discharged every night as the occupier goes out for about 10 minutes to put the cat out, the result of doing this over a period of time, is that the torch will now deliver no more than 10 minutes of light. A way round this is to exercise the cell. This is achieved by fully discharging the cell at a rate of $C/2$ or more, where C is the capacity of the cell. Thus a 0.5 amp-hour cell will be discharged at 0.25 amps. The cell is then rapidly recharged, with care being taken not to overcharge it. This is repeated 5 times, and in many cases it will rejuvenate tired cells.


There is another cause of tired cells and that is dendritic growth, which is the growth of fine crystals in the cell. These short-out in the cell, and the cell will appear as a dead short and have an output voltage, when charged, of less than 0.8 volts, and less than 1 volt when being charged. The cell can be rejuvenated, but it requires a current of around 200 amps for a fraction of a second with consequent risk of the cell exploding and taking eyes and skin with it. Personally, I would rather throw out the cell and start again.

Correct Charging

The cells can cause injury problems in another way. They can discharge their full capacity in less than a minute, and a cell in your pocket, with some keys and small change, can short circuit and cause burns.

The most frequent cause of cells being damaged is the recharging process. To get the maximum out of the cells they should be recharged as soon as possible. They should either be recharged at a high rate and not overcharged, or alternatively recharged at between $C/4$ and $C/20$. If recharging is done in a very short time, then care should be taken that the cell is not overcharged since this will lead to overheating and permanent damage to the cell because of its low internal resistance. The ideal charging rate is $C/4$ to $C/20$. If $C/20$ is used, then the cell will tolerate overcharging at room temperature since the excess heat is easily lost. The important thing is that the cell is charged at a *constant current and not constant voltage*. Figure 1 shows a possible charging circuit. If the cells to be charged are 2 AA cells, then they could be charged at 0.05 amps for 12 to 14 hours. Since they will have a voltage of 2.5 volts, the net voltage across the cells will be 12 minus 2.5 volts or 9.5 volts. A resistor of 190Ω will provide this.

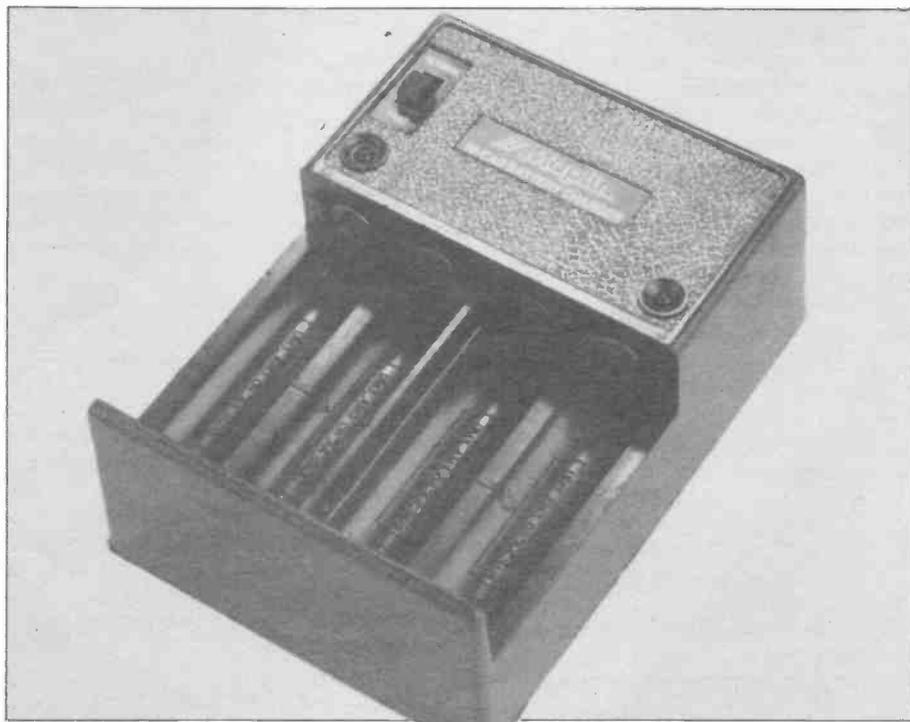Maplin Electronics have several different models of Nicad battery chargers in their catalogue ranging from a simple AA charger to a sophisticated 'deluxe' charger which accepts AAA, AA, C, D, PP3 and Button cells. It is highly recommended that charging of batteries is carried out using this



Charger for AA cells (Maplin Code YN28F).

type of proprietary commercial product as all safety precautions have been built into the units.

Testing Cells

How do you know whether your cells are in a reasonable state or not? This was the problem I had with several AA cells. There were no markings to show which cells were the old ones and which were the new ones. The following computer routine was developed to overcome this problem.

The BBC computer has an analogue to


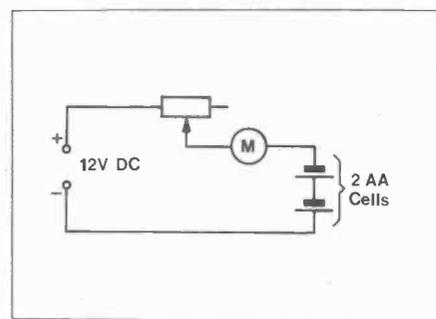


Figure 1. Simple charging circuit.

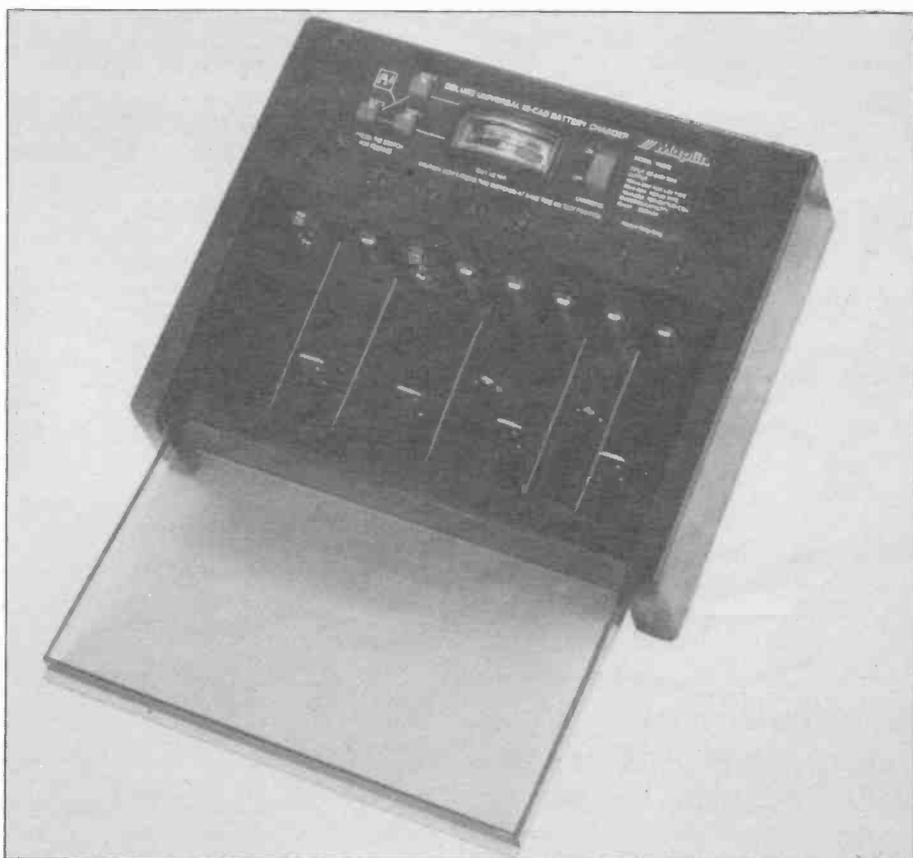

'Deluxe' charger (Maplin code YN27E).

digital converter (the joystick port) which will accept a voltage of up to 1.8 volts and produce a signal in proportion to the voltage. This makes life very easy. The signal from the port will be approximately 35168 for 1 volt input. The advantage of using the computer is that it can store the results and a graph of the results after several hours can be produced. The principle behind the circuit in Figure 2 is that the cell is discharged through a low value resistor and the

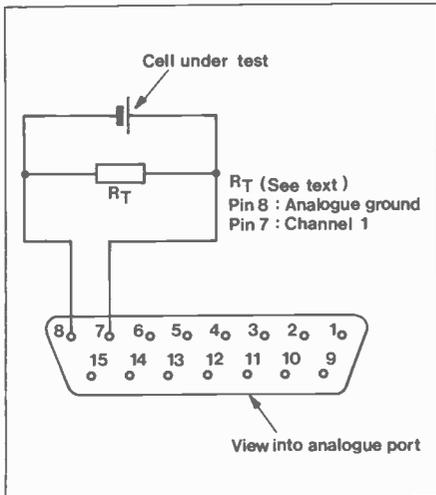


Figure 2. Circuit for BBC micro.

computer is used to monitor the voltage.

The value of the resistor that is used to discharge the cell should be calculated to produce a current of C/2, C/4 and C/8 to give a spread of figures. Thus for an AA cell of capacity 0.5 amp-hours, the discharge rate at C/2 is 0.25 amps, the resistor will have to be 1.25/0.25 or 5Ω. For C/4 the resistor will be 10Ω and so on. In each case, it is a good idea to place an ammeter in the circuit to check that the cell is discharging at the correct rate. In practice, it is often a problem to obtain resistors of these values and it is quite satisfactory to set up a circuit with several resistors wired in parallel to obtain approximately the correct current, as long as the same block of resistors is used when comparisons are made several months later.

The program to check the performance of the cell is shown in Table 1, it is very simple and could be much enhanced. Possible improvements include an automatic graphing routine and a method of storing the information on each cell so that a comparison can be made at a later stage in the cell's life.

Line 150 stops further readings being taken when the voltage drops below approximately 1 volt. It does not stop the cell being further discharged, though by using relays switched from the user port, it could turn off the cell when the voltage drops too low.

```

10 REM Ni Cad cell monitor.
20 DIM Rdg%(1000)
30 REM Readings stored in Rdg%()
40 PRINT "Enter the time interval for
  readings in minutes."
50 INPUT Min
60 Gap=Min*60*100
70 Co=0
80 REPEAT
90   TIME=0
100  Co=Co+1
110  REPEAT
120  UNTIL TIME>Gap
130  Rdg%(Co)=ADVAL(2)
140  PRINT Co*Min,
  INT(Rdg%(Co)/35.168)/1000
150 UNTIL Rdg%(Co)<35000
160 REM This stops the routine when
  the voltage falls too low
170 FOR C=1 TO Co
180 PRINT C*Min,
  INT(Rdg%(Co)/35.168)/1000
190 NEXT C
  
```

Table 1. Monitor program.

I hope this monitor program will be useful to you and that you have learnt something from this article about the correct way of caring for your Nicads.

Calcs continued from Page 43.

$$r_1 \theta_1 \div r_2 \theta_2 = \frac{r_1}{r_2} \theta_1 - \theta_2$$

$$25 \sqrt{60} \div 5 \sqrt{40} = 5 \sqrt{20}$$

Polar co-ordinates are particularly useful in finding square roots. The square root of the modulus is found and the angle divided in half:

$$(r \theta)^{1/2} = \sqrt{r} \theta/2$$

$$(25 \sqrt{60})^{1/2} = 5 \sqrt{30}$$

Now a real number like 25 has two roots 5 and -5.

These are of the same magnitude but opposite sign (phase) to each other. Similarly, a complex number has two roots, one 180 degrees out of phase (opposite phase) to each other.

Hence $(25 \sqrt{60})^{1/2}$ has roots of $5 \sqrt{30}$ and $5 \sqrt{210}$, see Figure 10. To square a number in polar co-ordinates we square the modulus and double the argument.

$$(r \theta)^2 = r^2 \theta \times 2$$

$$(4 \sqrt{20})^2 = 16 \sqrt{40}$$

Application of Complex Numbers to A.C. Bridges

We shall now see how many of the above methods are applied to the solution of

equations for AC bridges. In an equation containing both real and imaginary (quadrature) terms, the real components can be equated separately from the quadrature components.

For instance:

$$R + j\omega L = 13 + j19$$

$$\text{Therefore } R = 13$$

$$\text{and } j\omega L = j19$$

Let us examine a more complicated case like the Maxwell bridge of Figure 11.

$$\text{At balance } Z_1 Z_x = Z_2 Z_3$$

$$\text{where } Z_1 = R_1 \frac{(1)}{(j\omega C_1)} = \frac{R_1}{j\omega C_1 R_1 + 1}$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_x = R_x + j\omega L_x$$

Substituting in $Z_1 Z_x = Z_2 Z_3$:

$$\frac{(R_1)}{(j\omega C_1 R_1 + 1)} (R_x + j\omega L_x) = R_2 R_3$$

Multiplying both sides of the equation by

$$(j\omega C_1 R_1 + 1):$$

$$R_1 (R_x + j\omega L_x) = R_2 R_3 (j\omega C_1 R_1 + 1)$$

$$R_1 R_x + j\omega L_x = j\omega C_1 R_1 R_2 R_3 + R_2 R_3$$

Equating real terms:

$$R_1 R_x = R_2 R_3$$

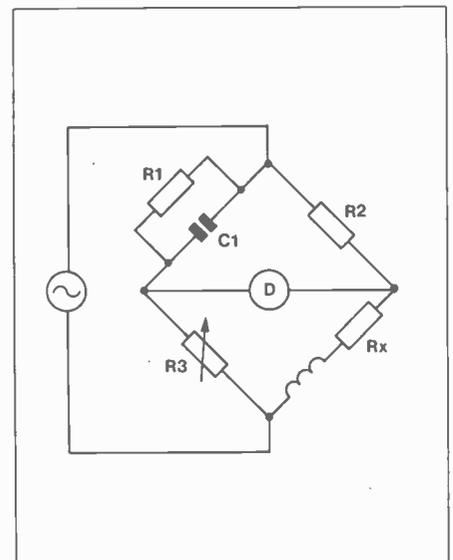


Figure 11. Maxwell bridge.

$$R_x = \frac{R_2 R_3}{R_1}$$

Equating imaginary terms:

$$\omega L_x = \omega C_1 R_1 R_2 R_3$$

$$L_x = C_1 R_1 R_2 R_3$$

This enables one to calculate the value of an unknown inductor L_x and its associated resistance R_x from known values of the other components in the bridge. It is hoped that the above shows how even large mathematical problems can be tackled in small easy steps.

ELECTRONICS

BY

EXPERIMENT

Part 4 by Graham Dixey C. Eng., M.I.E.R.E.

Introduction

A register is also a sequential logic circuit but, whereas a counter is concerned with the process of 'counting' the input data, the register is principally concerned with storing it. However, this bold statement can be a little misleading, since it implies an event that is going on for a substantial period of time, which may not be the case at all. As an example of this consider the familiar electronic calculator. When two numbers are added together, each is deposited into a register and on the command 'add' the two numbers are replaced by their sum. This sum is held in a register that only a moment before held one of the numbers. Thus, the storage of the original number was of very short duration. Another example is when data is being sent from a microcomputer to a printer. It passes out via a register, each byte in turn being held by this register until it is replaced by the next one in the queue. Thus, a register is really a string of flip-flops that can hold a data word for a period of time, no matter how long or short that is. There are also certain other ways in which particular types of register can be useful and they will also be discussed.

To start with the most elementary idea of a register, consider Figure 1, in which the four possible modes of operation are shown. These modes arise because there are two ways in which data can be transmitted from point to point. These ways are known as 'parallel' and 'serial' transmission respectively.

In parallel transmission, there is one line for each bit of the data word and all bits are transmitted at once. Thus an eight-bit word (a byte) requires eight separate lines - an example of parallel data transmission is the well-known Centronics printer interface. Because all bits are sent at once, parallel transmission is fast but requires lots of conductors.

In serial transmission, there is one line only, which all bits have to share. They are therefore sent down it one at a time. Thus, no matter how many bits there are in the data word only one transmission line is used but the process gets slower and

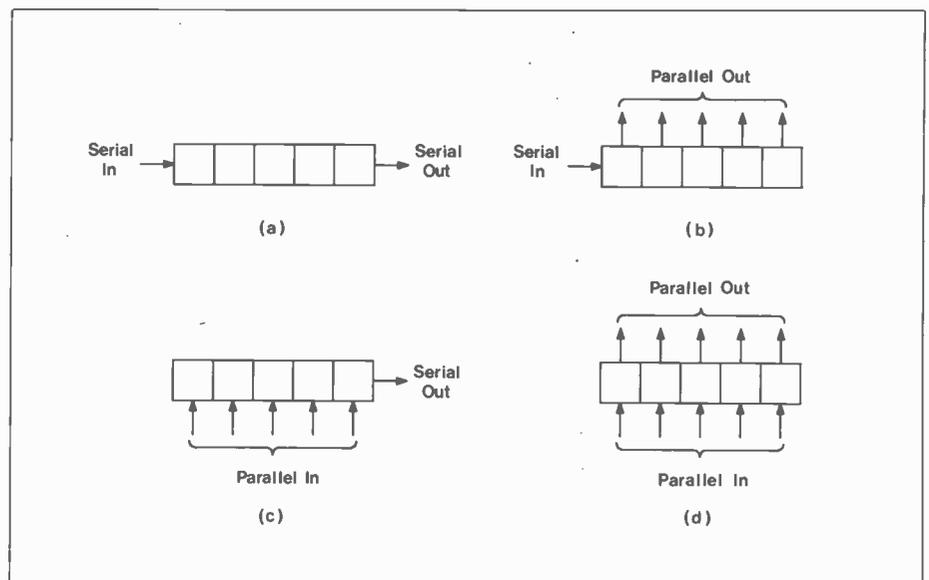


Figure 1. The four main modes of register operation. (a) Serial In, Serial Out (SISO); (b) Serial In, Parallel Out (SIPO); (c) Parallel In, Serial Out (PISO); (d) Parallel In, Parallel Out (PIPO).

slower as the bits queue up for their turn on the line! The advantage is the simplicity of it. An example of serial transmission is the RS232 interface for printers and modems.

How does this relate to registers? Quite simply. Each flip-flop of a register holds just one bit of the data word. Serial or parallel operation refers to the ways in which the data is loaded into the register or sent out from it.

For example, one mode is Serial In Serial Out (SISO). There is only one input line and only one output line. Data bits are 'clocked in' one at a time and then 'clocked out' in a similar fashion. For example, if the register is 'eight bits wide' (meaning it has eight flip-flops), it will take eight clock pulses to store a data word and a further eight clock pulses to 'shift' it out again. Note the use of the word 'shift'. Registers of this type are known as shift registers. In continuous operation a stream of bits flows in at one end and out at the other.

However, it is possible to shift the data in serially until all flip-flops hold one bit of the data word and then access all

bits of the data word at once, so that the output is 'parallel'. Obviously this mode of operation is known as Serial In Parallel Out (SIPO).

Reversing the latter mode is also possible. With one clock pulse the whole register can be loaded with the data word, which can then be shifted out serially. This is known as Parallel In Serial Out (PISO) operation.

A little thought will reveal that the SIPO type is a 'serial to parallel' converter, while the PISO type is a 'parallel to serial' converter. The significance of this can be seen where a computer is connected either to another computer or to a peripheral through a serial connection, i.e. a single line. Since the internal organisation of a computer is on parallel lines (referring to the data bus), there must be a parallel to serial conversion at the sending end and a serial to parallel conversion at the receiving end. It is an ideal function for registers to perform.

Finally, it is possible to load a register by parallel input and access it also by parallel mode. This is Parallel In Parallel Out (PIPO).

The D-type Flip-flop

As a general (but not invariable) rule, counters use JK flip-flops and registers use a type known as the D flip-flop (D stands for Data). The D flip-flop is rather simpler in operation than its JK equivalent. Both its symbol and truth table are shown in Figure 2. It has a single input line, marked D, a CLOCK input and a pair of complementary outputs, of which the Q output is the more useful. The truth table reveals its true simplicity.

The logic level, logic 0 or logic 1, to be stored is first applied to the D input. When a clock pulse is applied this level at D shifts to the Q output, where it will remain until a new data bit is applied to D and a further clock pulse arrives. Thus, the Q output merely copies whatever is at the D input after the arrival of a clock pulse.

As an experiment, try connecting a low-frequency clock oscillator to the clock input of a D flip-flop, say 1Hz (a suitable design appeared in Part Three). At the same time connect a switched logic level to the D input. Connect a logic level indicator to the Q output. Randomly vary the logic level input and note how, on the arrival of the next clock pulse, the logic level applied to D transfers to Q.

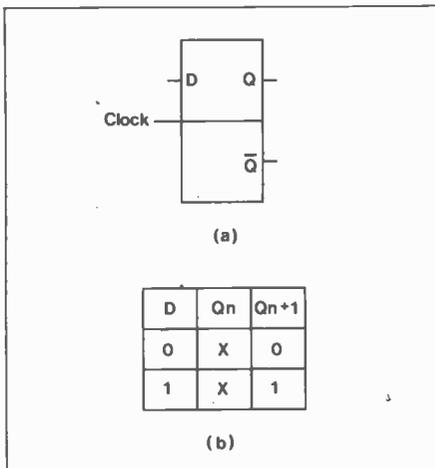


Figure 2. The D type flip-flop. (a) Circuit symbol; (b) Truth Table showing that, after clocking, the output at Q equals the input at D. Note: Q_n = state of Q before clock pulse; Q_{n+1} = state of Q after clock pulse; X = 'Don't care', i.e. can be 0 or 1.

The 7474 D-type Flip-flop

This package contains two D flip-flops and its pin-out diagram appears in Figure 3. This is an example of a 'positive edge triggered flip-flop'. This was mentioned in Part Three but will be repeated here. The clock pulse can be considered as two transitions occurring one after the other. The first is from Logic 0 to Logic 1 (the positive edge) and the second is from Logic 1 back to Logic 0 (the negative edge). In a positive edge triggered flip-flop only the first transition matters. The data transfer from D to Q occurs at this instant only. The duration of the clock pulse is of no importance, nor is the subsequent trailing edge.

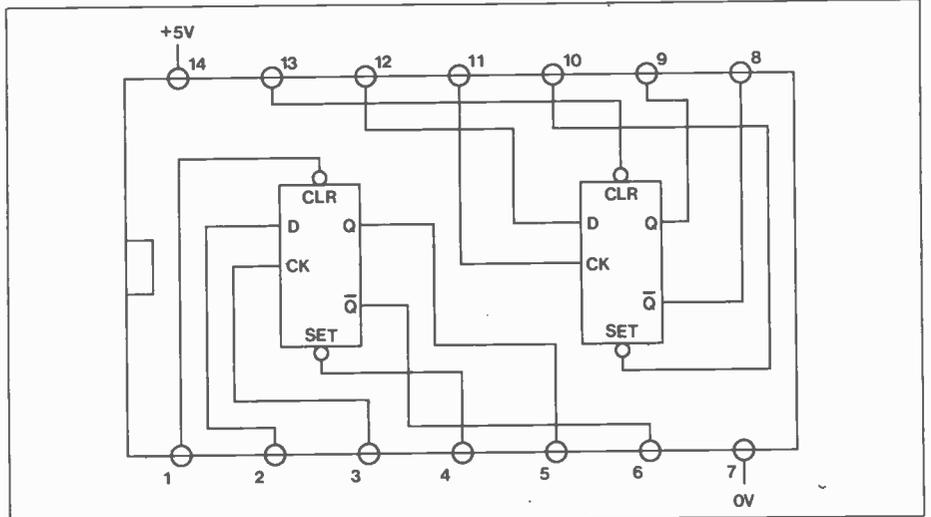


Figure 3. Pinout diagram of the 7474 Dual D type, positive edge triggered, flip-flop.

Each flip-flop has two connections not so far mentioned. These are marked on the 'chips' as SET and CLR and are known usually as 'preset' and 'preclear'. The 'bubble' on each of these indicates that they are 'active low' connections, that is taking the terminal to Logic 0 causes the required action to take place. It is usual to connect all the CLR pins together for all the flip-flops in a register and call this the RESET line. Taking this low, momentarily, clears all the flip-flops, that is all Q outputs go immediately to Logic 0. The SET pins can be used when required to preset a given value into a register, that is to give it a particular state to start off with rather than starting with a clear register. Examples of this use appear later.

Shift Registers

The simplest types of register are the SISO and SIPO types. Their circuit diagrams appear in Figure 4. Basically they are the same; it is only in the way they are used that they differ. The data input to the register is the D input of the first flip-flop;

the data input of any subsequent flip-flop is always the Q output of the preceding one. All flip-flops are clocked at the same time.

Purely for simplicity, only four-bit registers are shown. The same principles apply however many stages there are. To study the mode of operation, connect up this register using two 7474 ICs (Figure 5). Connect all CLR pins together and wire this common line through a switch to the 0V line; leave the switch open for the moment. Connect a de-bounced switch to the clock input and logic level indicators to each of the Q outputs. Finally connect a logic level switch to the data input. Switch on; the Q outputs will be quite arbitrary. Momentarily connect the RESET line to 0V using the switch provided for this purpose. The Q outputs should now all be zero. Set the logic level at the input to Logic 1. No changes should be observed in any of the flip-flops. Leave this level as set and pulse the de-bounced switch four times. The Q outputs should take up the successive

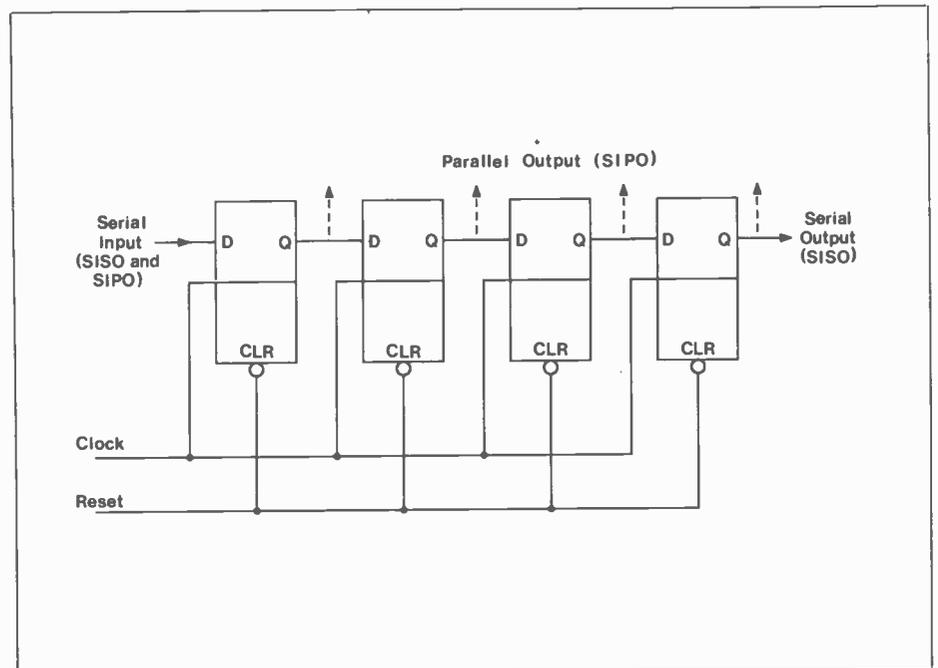


Figure 4. A 4 bit Serial In, Serial Out shift register (SISO), with the simple modification needed to get a parallel output (SIPO).

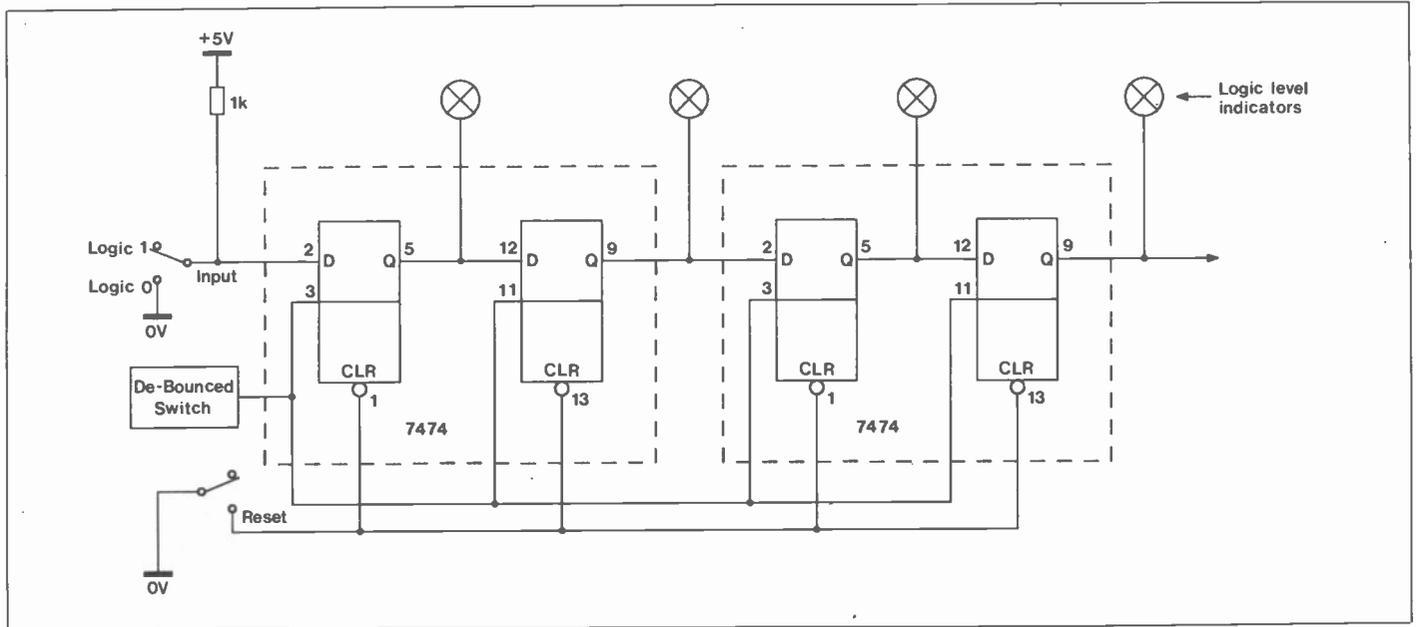


Figure 5. The circuit of Figure 4 implemented with two 7474 ICs and the necessary hardware for evaluating it.

states: 1000, 1100, 1110 and 1111, as shown by the four LEDs of the logic level indicators. If it doesn't do this, check in turn - the circuit wiring, the ICs themselves, the output from the de-bounced switch; finally, "have you left the RESET switch low?"

If all is well, consider the fact that the data word 1111 is shown by the four LED indicators. In other words, not only has it been stored but it is available at the Q outputs if four lines were to be connected to these outputs. Thus, although the data word was entered serially using four clock pulses, it is now available at the Q outputs without any further action being necessary. This is SIPO operation.

But if it is desired to remove the data word serially, four more clock pulses will be needed. This will normally load a new word so set the logic level input switch to Logic 0 and pulse the de-bounced switch four more times. The logic levels at the Q outputs should now take up the successive states: 0111, 0011, 0001 and 0000. Note that the original data word has been progressively shifted to the right until it was replaced by the new word 0000. This is an example of SISO operation. What has not been done in this case is to 'catch' the data word as it left the register. Special provision would have to be done to do this; nonetheless, the basic operation of serial shifting has been shown.

Parallel In Parallel Out and Parallel In Serial Out Registers

These registers, shown in Figure 6, illustrate that sometimes extra gating is needed to get the register to perform in particular ways. In these cases, each flip-flop requires a pair of two-input NAND gates and an inverter. These are concerned with the parallel loading. Once the parallel load has taken place, the contents of the register can be accessed in parallel mode merely by connecting wires to all of the Q outputs, or the data can be obtained serially by clocking the register four times, as already described for the

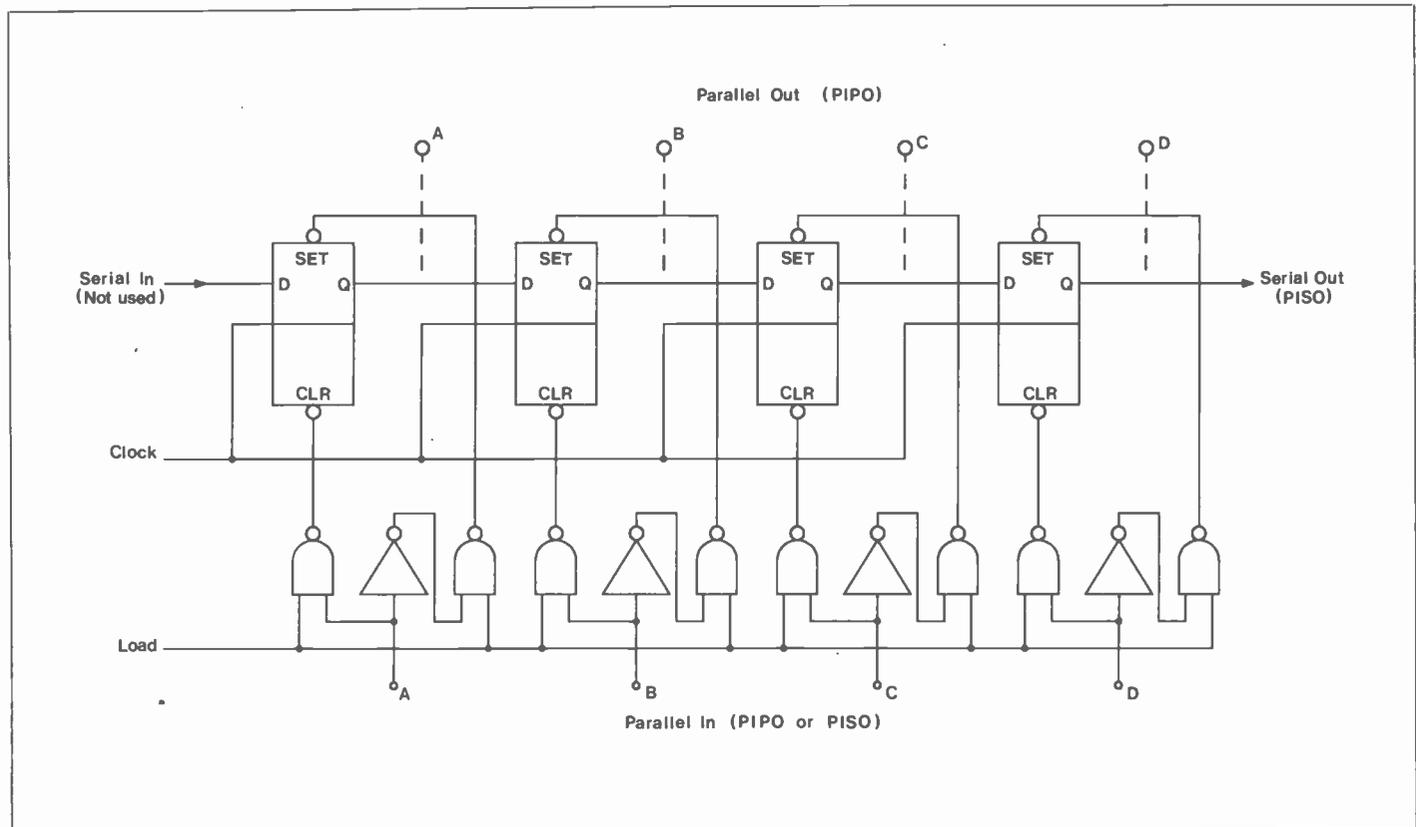


Figure 6. Circuit diagram(s) for the Parallel In, Serial Out (PISO) and the Parallel In, Parallel Out (PIPO) registers.

SISO and SIPO types.

The parallel loading works as follows. The line marked LOAD is normally held at Logic 0. Thus, both NAND gates of each pair associated with each register stage have logic 1 output levels. These drive the SET and CLR pins of the flip-flops; both pins being at logic 1s, nothing happens. Each DATA IN line will have either a Logic 0 or a Logic 1 on it, according to the data to be loaded. This is applied directly to one NAND gate and in inverted form to the other NAND gate. Consequently, one NAND gate of a pair will have Logic 1 and Logic 0 at its inputs, while the other will have both inputs at Logic 0. Now let the LOAD line go to Logic 1. One of each pair of NAND gates will now have two Logic 1 inputs, the condition that causes the output of a NAND gate to go to Logic 0. Since the SET and CLR inputs are negative-acting, each flip-flop will become SET or CLEAR according to the logic level at its DATA IN input. The best way to follow this operation is to connect up the circuit and use a logic probe to look at the logic levels on all pins of the NAND gates and inverters during the load operation.

To connect up the circuit will require an LED logic level indicator at each Q

output, a set of four logic level switches for the four DATA IN lines and a switch for the logic level on the LOAD line. Once the data word has been loaded and the operation fully understood, the shifting operation can be shown by pulsing the clock line with a de-bounced switch.

The Ring Counter

This is an interesting example of a shift register apparently masquerading as a counter, if the title is to be taken literally! It certainly can be used as a particular type of counter but it has a more interesting and useful application. It is frequently used for generating a 'walking one' pattern for scanning keyboards, multiplexing seven-segment displays and generating dot-matrix characters on video displays. It works very simply as follows.

The diagram of Figure 7 shows that the Q output of the last flip-flop is connected back to the D input of the first flip-flop, forming the 'ring' of the title. Thus, there is no actual input apart from the clock. To set it up it is necessary, when it is first switched on, to clear all stages (using a RESET line) and then SET just one of the Q outputs, say the first, to Logic 1. The 'preset' pin is used for this. If it is now clocked the 'Logic 1' shifts to the next

stage to the right, its place being filled by a Logic 0. Every clock pulse performs the same action so that continuous clocking causes the Logic 1 to keep circulating. Naturally, when it reaches the Q output of the last flip-flop it will pass around the ring to the D' input of the first, to keep the process going.

The sequence, for a four-stage ring counter, is 1000, 0100, 0010, 0001, 1000, etc.

Try this circuit out by wiring it up with a pair of 7474 ICs. Connect LED logic level indicators to all Q outputs and a low-frequency clock to the clock input. At about 1Hz it is possible to sit back and watch the 'one' circulate with ease.

The Twisted Ring Counter

This simple derivative of the ring counter just discussed is formed merely by taking the feedback from the not-Q output of the last flip-flop rather than the Q output (Figure 8). It is initialised in the same way - cleared and then a single 'one' put in. What happens when it is successively clocked? Would you be surprised to find out that the sequence is as follows?

1000, 1100, 1110, 1111, 0111, 0011, 0001, 0000, 1000, etc.

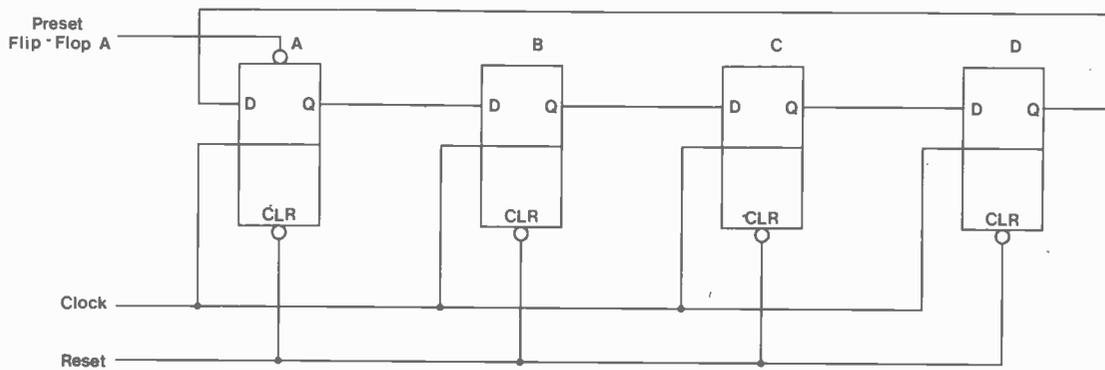


Figure 7. An example of a register with 'feedback', the Ring Counter.

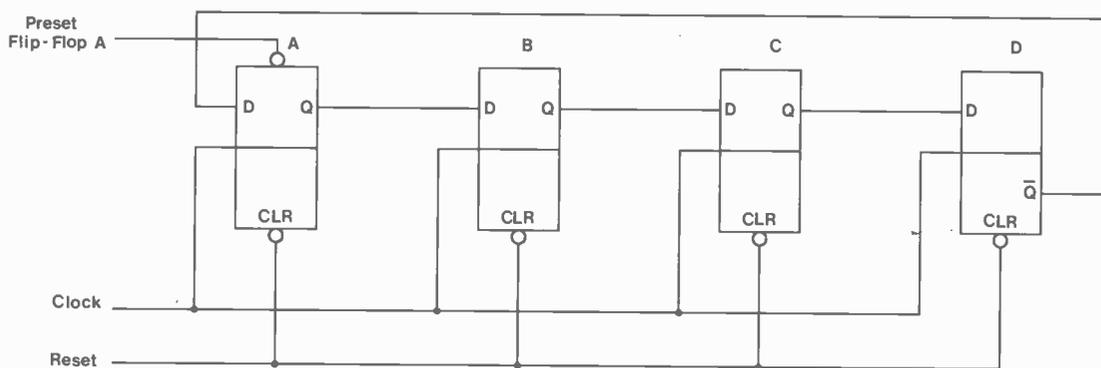


Figure 8. If the feedback is taken from the not Q output of the last flip-flop instead, the circuit of Figure 7 becomes a 'twisted ring' counter, with quite a different sequence.

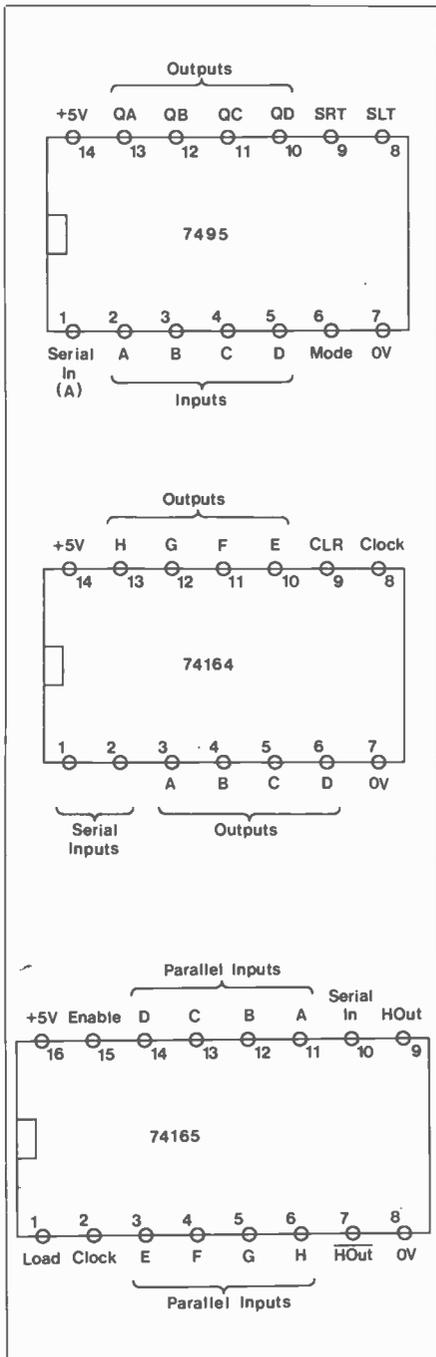


Figure 9. Pinout diagrams for some MSI shift registers.

It is interesting to notice that 'four' flip-flops give rise to 'eight' quite distinct states. In fact the number of states is always twice the number of flip-flops. Therefore, if five flip-flops are used, the number of states are ten – in other words we have a 'decade counter'. The fact that it is not the normal binary sequence for 0-9 is not really important as long as the state of the counter at any instant can be recognised by suitable decoding logic. Thus, if 0000 represents '0', then 1000 represents '1', 1100 represents '2' and so on. This code is called 'Johnson Code' and the twisted ring counter is often known as a 'Johnson Counter'. It has the characteristic of being a very fast synchronous counter, using shift register principles.

Further Work with Registers

The registers discussed so far have

all been assembled from flip-flops and gates in individual IC packages. However there are, of course, fully operational registers contained within single packages. These often offer particular facilities that would be rather tedious to provide by interconnecting flip-flops and gates. A few of these will be discussed now, to round off this feature.

The 7495 Four-Bit Left-Right PIPO Register

This comes in a 14-pin DIL package and the pin-out diagram, together with those for the 74164 and 74165 registers, is shown in Figure 9. It is used as follows.

In this register all D inputs and Q outputs are individually accessible. It is possible to parallel load data into it and then either access it immediately (PIPO mode) or shift it left or right. Reversible registers normally require a fair amount of extra logic so having it 'all on one chip' is a decided advantage. It is possible to cascade these registers to make, for example, an eight-bit register.

There are two modes, known as SHIFT and LOAD. To go into SHIFT mode, the 'mode' input must be taken low. The negative edge of a clock pulse on SRT shifts data one stage 'to the right'. Similarly a negative edge on the other clock pulse, SLT, will shift the data one stage left. Thus, two clocks are needed, though in practice it could be the same clock switched between the SRT and SLT pins. Shifting works exactly as described for previous registers.

To go into LOAD mode, the 'mode' input is taken high and the data presented at the inputs LA – LD is entered into the register when a negative-going transition is made at the shift-left input (SLT). From this it can be seen that the SLT input is dual-purpose, shifting data left in SHIFT mode and loading data in LOAD mode.

The 74164 Eight-Bit SIPO Shift Register

This register, which has a right-shifting ability only, can handle serial-in data in the usual way, but can be pre-loaded with a Logic 0 or Logic 1 input as required. The data may be output in either parallel form or serial form.

For normal operation, one of the Serial Inputs is held high and the other becomes the data input. The Clear pin is also held high (taking it low momentarily clears the register). Data is shifted right one stage on every positive clock edge. To enter a Logic 1 into the register both Serial Inputs must be taken high. Taking either Serial Input low enters a Logic 0. It is essential that the clock is bounceless and noise-free.

The 74165 Eight-Bit PISO Register

This register has the versatility of being able to function as a straightforward Serial In Serial Out shift register or can be loaded with parallel data, which can then

be shifted out serially.

For normal operation, the Enable pin is held low and the Load pin is held high. Data is applied to the Serial In terminal and shifts right one stage on every positive clock edge.

To parallel load the register, the Load pin is momentarily taken low while the data input is applied to the parallel input pins A – H.

Shifting may be disabled at any time by taking the Enable pin high.

With the previous experience of connecting up and testing the other registers mentioned earlier, it shouldn't be too difficult now to devise schemes for testing the above three registers. One learns best by trying out a variety of circuits in this way.

An Oscilloscope Probe

There is sometimes a problem when using an oscilloscope to view the logic waveforms of TTL circuits. The input capacitance of the CRO may 'kill' the waveform at the test point and what is needed is some means of isolating the test circuit from these unwanted effects. This can be achieved quite easily using just two components – a resistor and a capacitor. The resistor is chosen to give attenuation together with the input impedance of the CRO, 10:1 being usual. See Figure 10. The capacitor is wired in parallel with the resistor R1 and is chosen so that the time constant of R1 and C1 equals the time constant of R_{in} and C_{in} for the CRO. This gives the widest possible bandwidth.

To take an example, the typical input impedance of a CRO consists of a parallel combination of a 1M resistance and a capacitance of the order of 10 – 50pF, say 30pF. Therefore, for 10:1 attenuation, R1 should be 9M. This gives the relation that:

$$9M \times C1 = 1M \times 30pF$$

$$\text{From which } C1 = \frac{(1 \times 30)}{9} = 3.3pF$$

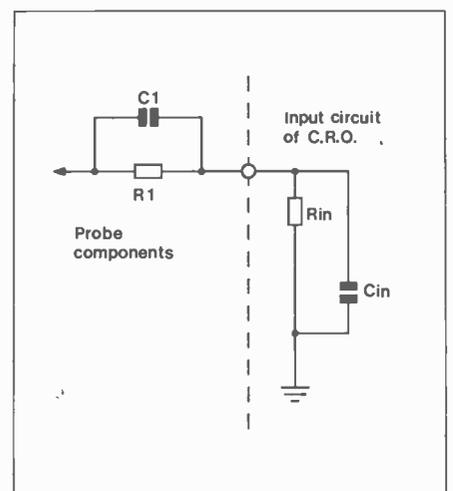


Figure 10. Probe design for a CRO.

It should be quite possible to assemble these two components into a discarded ball-pen case to make a useful probe, using a short length of co-axial cable between the probe and the Y input of the CRO.



'Hello Who's Calling?'

Bell's first telephone

by J.K. Hearfield Part 2

Central Battery Signalling

The earliest telephones were signalled by means of a 'magneto', or hand-cranked generator. Before making a call, the subscriber had to wind the magneto handle energetically several times in order to alert the switchboard operator, who then connected herself to the caller to find out what he wanted. This must have been rather a nuisance, but of course the subscriber had to do it or the call could never be placed. Once the call was finished, the subscriber was supposed to wind the handle again to let the operator know that she could clear the circuit. This procedure was known as 'ringing off', a phrase which survives long after its original meaning has disappeared. If the subscriber forgot, or didn't bother, there wasn't much the telephone company could do about it, and it must have been commonplace for circuits to be tied up long after calls had ended.

An obvious way to improve efficiency was to build into the switchboard some simple means of detecting when a caller finished speaking and hung up, and use this signal to alert the operator instead of relying on the caller to do it. Looking back from the vantage point of

ninety years' steady improvement in technology, it seems perverse that the designers of the day chose to solve the problem in the way they did, but it should be remembered that relays were not always the cheap and reliable components they are today.

The solution chosen was to add what was effectively a third wire to the subscriber pair. Using the earth itself as one of the conductors had already been tried and found to be a bad idea, but using the earth as a third conducting path just for signalling was perfectly feasible, and continued to work well in one guise or another in the UK until at least the 1970s.

The magneto was itself not a low-cost item, and once it was no longer needed for 'ringing off', the way was open to remove it from telephones altogether, provided some equally straightforward way could be found for subscribers to initiate their calls. This proved remarkably easy. A telephone needs dc in order to work, and the earpiece is hung tidily on a hook when the telephone is not actually in use. So if the hook can be attached to a switch so that the circuit is broken when the telephone is 'on-hook' (another phrase from the distant past which inexplicably remains in common use, especially

amongst telecommunications engineers) all the switchboard need do is monitor whether or not a dc path exists through the telephone. The current involved is quite small, because the power to energise the telephone's microphone is still drawn from the local battery, so the central battery need not be prohibitively large and expensive. This system was known as Central (or Common) Battery Signalling, or CBS. The logical next step of replacing thousands of small local batteries with one Central Battery (CB) was still however some way off, and will be discussed in the next article.

The Candlestick Telephone

Voltage detection at the exchange meant that the associated telephones could be smaller and 'portable' (within the limits of their cords). The classic candlestick telephone, typically as shown in Photo 1, exploited this freedom with a radically different shape. The transmitters in the first candlesticks were held in a rigid metal case, and users had the choice of either crouching over the instrument or picking it up (being careful to hold it vertical) in order to talk into the microphone. The user guide, which was engraved around the transmitter casing,



Photo 1. CBS table telephone.



Photo 2. Candlestick telephone, circa 1927.

often included a stern instruction to 'speak closely'. Later versions housed the transmitter in bakelite, an early brittle plastic, designed so that it could be swivelled to face the speaker. The weight of the earpiece operated the hookswitch, and the earpiece shape reflected that of the transmitter stand. The result was a functional and beautiful design which lasted for over fifty years.

The bellset was separate, and could be placed at the subscriber's (or his butler's) most convenient location. As well as housing the bell, it was a convenient termination point for cables from the outside world, the local battery, and of course the telephone itself. These bellsets, usually mounted high on a wall, survived for many years in houses where the telephone itself was modernised, and I was delighted to discover a beautiful example disguised by several layers of paint when I recently moved house.

The candlestick outlived the CBS system in the end, possibly because no-one could find a good reason for scrapping such a manifestly successful design. Candlesticks with dials became commonplace, see Photo 2, and if they were not as elegant as those without, they made up for it by providing a more efficient service.

CBS Telephone Systems

CBS telephones did not have dials, since all calls were still routed through the local manual exchange operator. The early CBS systems were intended for rural exchanges, and this restricted facility was all that was available for many years to some subscribers. And like the colour choice of the early Ford cars, Post Office subscribers could have any colour as long as it was black, though subscribers to the National Telephone Company could choose a nickel plated version.

The normal equipment consisted of a Telephone No.4 and a Bell Set No.5, and the standard CBS No.1 telephone installation is illustrated in Figure 1. The circuit of the telephone itself is shown in Figure 2 as it would have appeared at the time and redrawn with modern symbols. It differed from earlier telephones chiefly in its use of a lower impedance bell, connected not across the A and B wires but from the A wire to earth.

An earth connection on the A wire meant 'clear', because the earth could only be there when the telephone was on-hook. To make a call, the subscriber lifted the receiver earpiece from the hookswitch and the subsequent loop current was sensed at the exchange. In-coming calls were signalled when the exchange applied a large alternating voltage between the A wire and earth, causing the bell to ring. When the subscriber lifted the earpiece, the hookswitch was released, the ringing current path was broken, and the circuit back to the exchange was completed via the A and B wires.

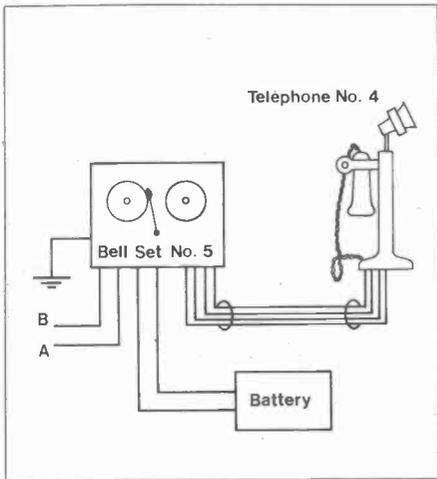


Figure 1. A standard CBS No.1 telephone installation.

There were disadvantages to this system. The bell would never ring if the A and B wires were accidentally reversed anywhere along the route from the exchange to the subscriber's premises (a mistake it was all too easy to make). More importantly, the reliability of the system was governed to an uncomfortable degree by the quality of the earth resistance at the subscriber's premises. Telephone engineers had to explain to disbelieving subscribers that it was vital to water their earth connections in dry weather!

Photo 3 shows another early CB telephone. This elegant instrument not only incorporated its own bell, making a separate bellset unnecessary, but also provided an additional earpiece (for people with two ears, perhaps). The hookswitch design was less impressive, relying as it did on a long leaf-spring inside the handset cradle base which in practice was temperamental and difficult to keep in adjustment.

The simplicity and low cost of the CBS No.1 system ensured its survival for almost half a century, long after fully automatic CB systems had come to be taken for granted by most telephone users. Its disadvantages centred mainly around its use of an earth return path for signalling, and the CBS No.2 system attempted to get round these by introducing a blocking capacitor to separate the ac ringing path from the dc speech path. Figure 3 illustrates the essential difference between the two systems. In CBS No.2, ringing current flows through the $2\mu\text{F}$ capacitor and the bell, whilst dc current flows through the speech circuit. It was necessary to increase the resistance of the bell, which is effectively in parallel with the speech network, but this was easily done by wiring the 500Ω bell coils in series rather than in parallel. Capacitors cost much less by 1940 than they had done in 1900, so the economic effect of the change was not excessive, and CBS No.2 had the great merit of still not requiring a large and costly central battery.

Pay-Phones

Pay-phones for public use were available from an early date. In the 1880s

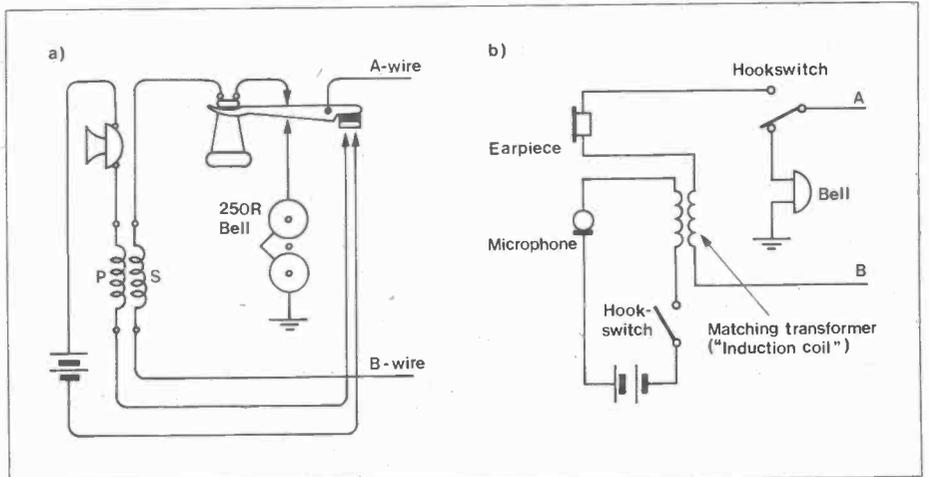


Figure 2. Principle of the CBS No.1 telephone, shown in both contemporary and modern styles.



Photo 3. CBS telephone No.26.

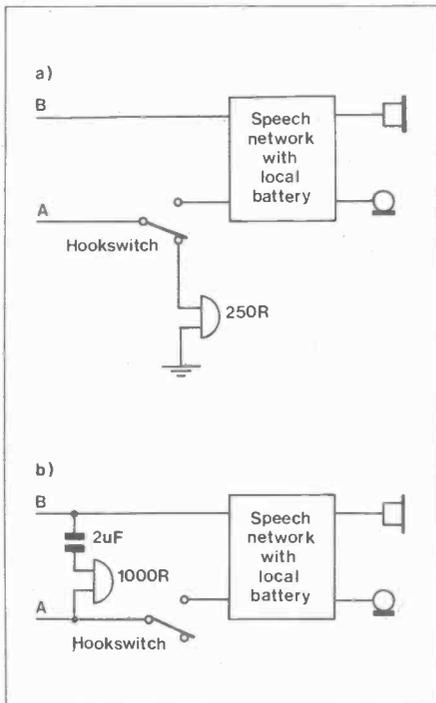


Figure 3. CBS No.2 replaced CBS No.1 about 40 years ago.

there were about twelve thousand private telephones in use, mainly by businesses, and in 1884 the Postmaster General authorised the telephone companies to create public call offices. The early pay-phones were installed in shops, post offices and railway stations, but telephone kiosks arrived in the streets as early as 1900. Some had coin-slots in the door, others had an attendant to collect the money, but whichever method was used it was possible for anyone with 2d to make a telephone call. Such permanent additions to the street also changed its appearance, sometimes to the dismay of the local council. After a number of unsuitable, grotesque or just plain ugly call-boxes had been installed by the various telephone companies, a design competition resulted in Sir Giles Gilbert Scott's classic red telephone box being introduced in 1927.

Style and Applications

Although most people will be familiar with the old types of domestic telephone many different designs were produced for different applications. House telephones and office intercoms used internal wiring to call instruments in another part of the building and were therefore cheaper to use than telephones connected to the public exchange. Railway companies used special telephones which needed little maintenance and could work cheaply over long distances. For many years the railways' private network was as large and complex as the public network. Gasworks and mines used special spark-proof telephones.

With greater use of the telephone, style and fashion became more important. As well as the nickel-plated instrument already mentioned, other inducements were used to persuade the subscriber. One Post Office telephone, similar in style to the Type 26, used

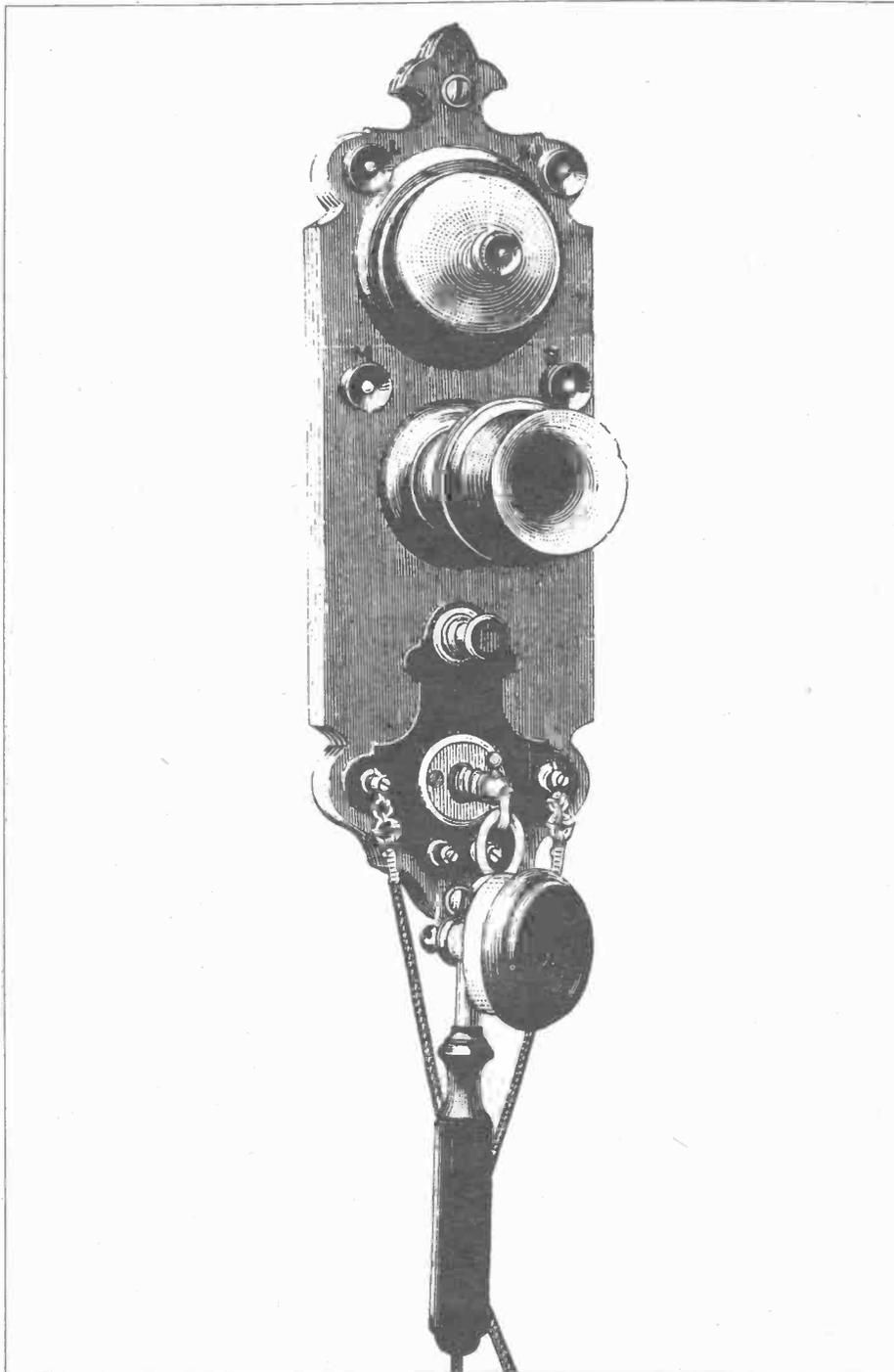


Photo 4. Combined servants call bell and telephone.

stained and varnished wood where possible and printed a woodgrain pattern on the remainder of the metal case. Another early telephone used small cow-gongs instead of bells to summon the subscriber. Some prosaic black telephones were made more up-market by the use of gold filigree transfers. If a household had to have one of these new-fangled instruments, then some effort was made to allow it to be as discreet, or as brash, as the subscriber wanted. In large houses where bellpushes were used to call the staff - see Photo 4 - it was sometimes possible to use the existing wiring to convert the system. 'Ringing for the cook' meant that it was possible to talk to the cook in her kitchen, instead of discussing menus in person, and the subscriber could call for the car without the need for the chauffeur to walk half a

mile from the garage to the study.

Ownership of a telephone was however still rare. The industrialisation which followed the first World War created a much greater demand, which was satisfied by the more reliable mass-produced telephones to be discussed in the next article.

Acknowledgement: All telephone illustrations are reproduced by courtesy of the archivist at The Telecom Technology Showcase.

Further reading: Old Telephones by Andrew Emmerson, published by Shire Publications Ltd., Cromwell House, Church Street, Princes Risborough, Aylesbury, Bucks HP17 9AJ. Cover price £1.25.

2 WAY 16 LITRE LOUDSPEAKER SYSTEM

by Dave Goodman

Introduction

Optimised cabinet designs can be regularly found in the plethora of electronics books and magazines available, and doubtless all have their relative strengths and weaknesses according to latest theories and materials available! We all perceive sound in different ways according to needs, age, personal taste, surroundings and many other variable factors which shape – or cloud – our judgement of what sounds good or bad; therefore, no claims of superiority and geometrical excellence or latest technological marvels are made for this design which is a small 2 way loudspeaker cabinet measuring 25cm x 21cm x 41cm, which is equally suitable for use in home hi-fi and studio or stage monitoring applications. The prototype frequency response, shown in Figure 1, extends from 40Hz to 18kHz with power handling capability up to 40 watts*. Just what the design has to offer however, is:

- A. Ease of construction due to using simple chipboard panels for the box; building the prototype took approximately 2 hours – including sawing and gluing the wood!
- B. Front baffle supplied drilled and pre-cut to take loudspeakers and port tube supplied in the kit.
- C. Very high quality bass/mid range driver with treated fibre glass cone which produces a smooth, clearly defined presence to the sound.
- D. SOA tweeter, active horn loaded and formerless ferro-fluid cooled, offering good transient response and spatial dispersion.

The cabinet dimensions were calculated from T/S data available for the driver and previously published in the March/May 1987 edition of Electronics.

Figures 2 and 3 show the manufacturers response curves for the two speakers both on axis and 30 degrees off axis. The smooth bass response of the driver can be seen from the gradual low frequency roll-off between 100Hz and 20Hz in Figure 2, whereas the slope characteristic changes completely once the driver is fitted into the cabinet as seen in Figure 1.



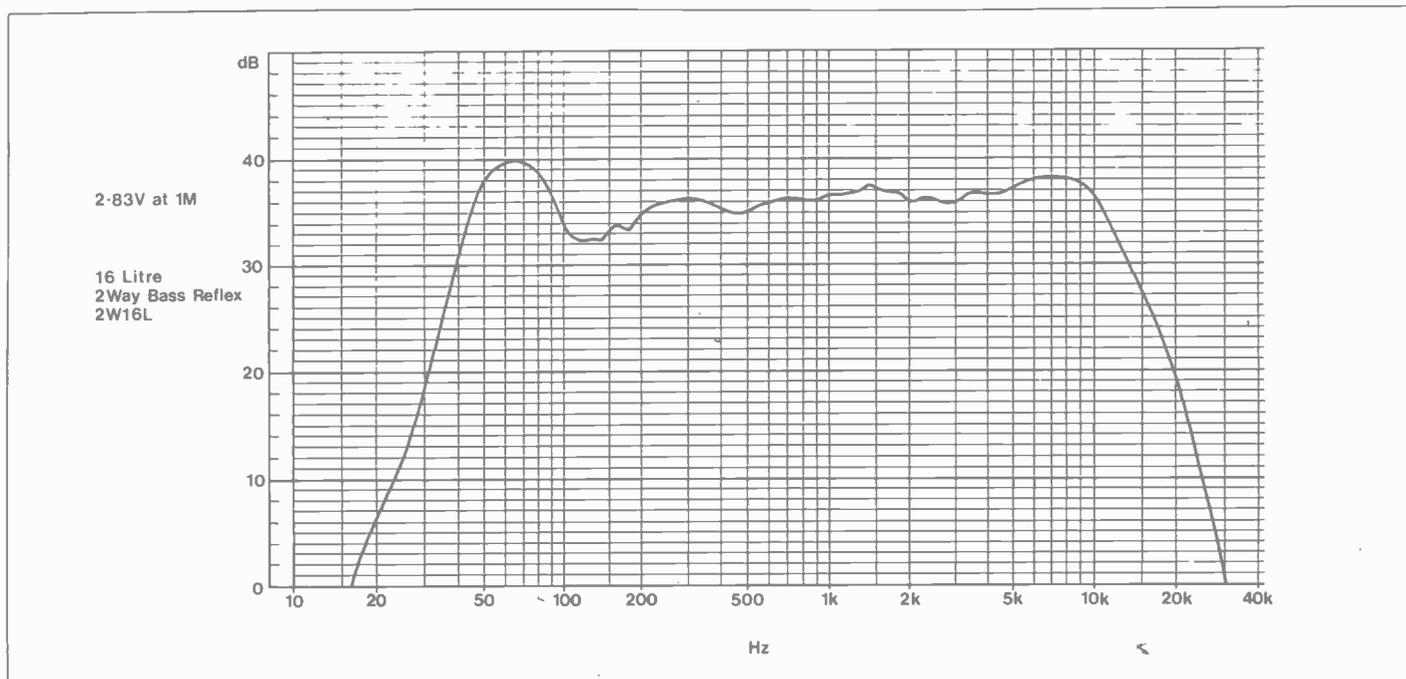


Figure 1. Total system frequency response.

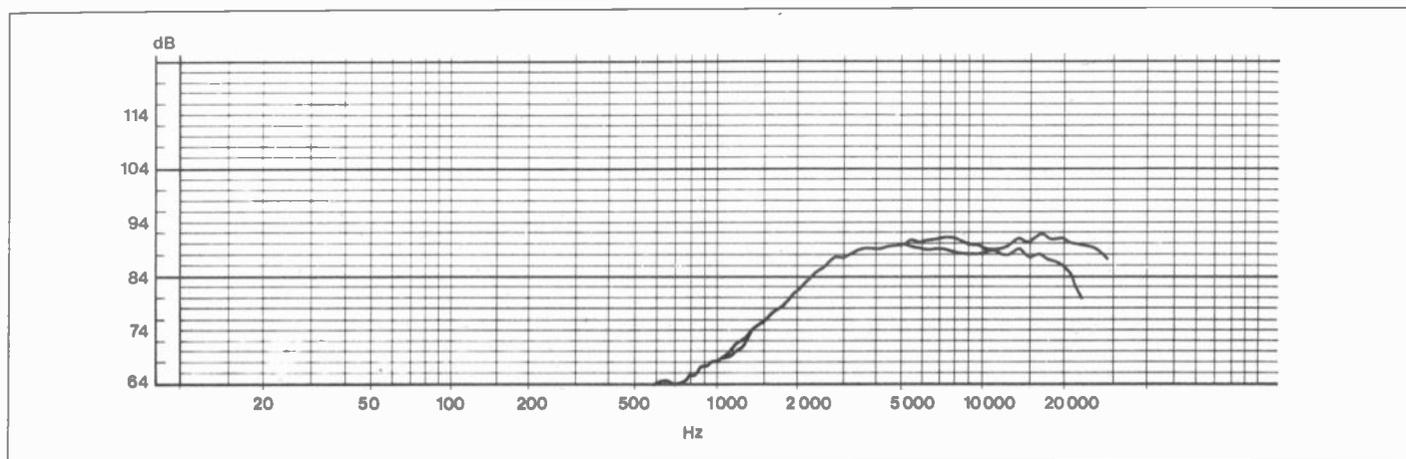


Figure 2. Bass speaker response curve.

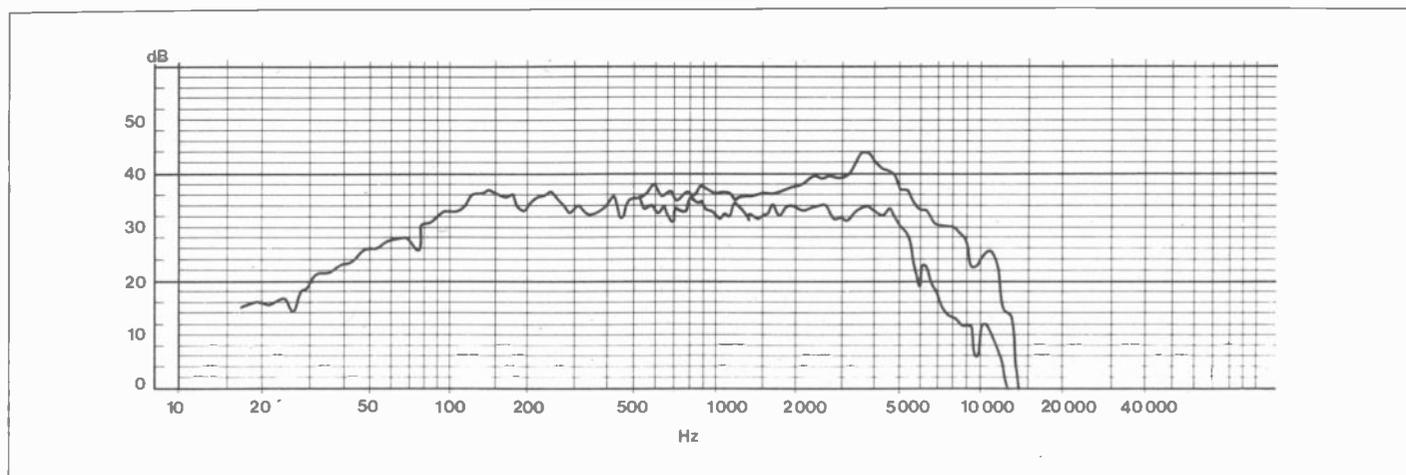


Figure 3. HF tweeter response curve.

Cabinet Construction

Five panels are required for the cabinet as they are *not* supplied in the kit. The cheapest and possibly easiest material to use is 15mm thick, High Density Chipboard of the type used for flooring. Melamine and veneered chipboard is suitable, if the laminate is removed from

butt joints before gluing, or marine plywood can be used. Chipboard is very cheap and can be veneered, painted or wallpapered to taste quite easily.

When cutting panels, particular care should be taken to ensure straight and square edges are formed. At the least, large air gaps will appear along the joints,

at worst – the finished cabinet will not fit together properly. Most large wood yards have power saw facilities and will cut these panels very accurately for you.

Please note that the dimensions shown in Table 1 are based on 15mm thickness material. Any deviation from this thickness will require an alteration to

Cutting List

Material 15mm thick HD chipboard

1 panel 410 x 180mm (1)
2 panels 410 x 250mm (2) & (3)
2 panels 250 x 210mm (4) & (5)

Material 2" x 1" (50mm x 25mm)
prepared

2 horizontals 138mm (6) & (7)
2 verticals 410mm (8) & (9)

Also required are:

18 csk chipboard screws 38mm
6 wire nails 30mm
White wood resin 'W' adhesive
Contact adhesive or glue gun

Table 1. Cutting list.

the 210mm width measurement on panels (4) and (5) only, to allow for the change. Figure 4 gives the panel layout.

Suggested Assembly

If reference is made to Figure 5 panel assembly drawing, it can be seen that panels (2) and (3) require three clearance holes drilled along each of the long edges, for the chipboard screws. Make the holes approximately 7mm in from the edges and counterdrill them to take the screw heads. Note that the larger (68mm) of the two small holes cut out of the front baffle is positioned downward towards the base! Top and base panels (5) and (6) also require 4 clearance holes to be drilled, one positioned centrally along each side and 7mm in from the edge, and these too should be counter drilled as before.

Spread a liberal amount of resin adhesive along the front inside edge of panel (2) and offer it up to the left hand edge of the baffle; insert three screws as shown and tighten them up, ensuring both panels are aligned precisely at the front and ends. Repeat the same procedure as before for the right hand panel (3) and baffle.

Next, fit the back panel (1) temporarily in place using screws only (no glue!) and assemble top and base panels (4) & (5). Apply adhesive to the top edge of panels (2), (3) and baffle only, position panel (4) and insert the four screws. Tighten each screw and with a clean rag, remove any excess glue that may have squeezed out from the joints. Repeat the procedure for base panel (5) as before. Finally, remove all six back panel screws and take out panel (1); you may have to knock the back panel out by inserting a hammer or block of wood through the front speaker cut out and apply a hefty wack!

Framework

A simple framework comprising 4 lengths of 2" x 1", or metric equivalent, is required for bracing the back panel (1). Earlier assembly details suggested that the back panel could be held in place with six screws inserted through side panels (2) & (3). If intending to cover the cabinet after construction and also to allow for the

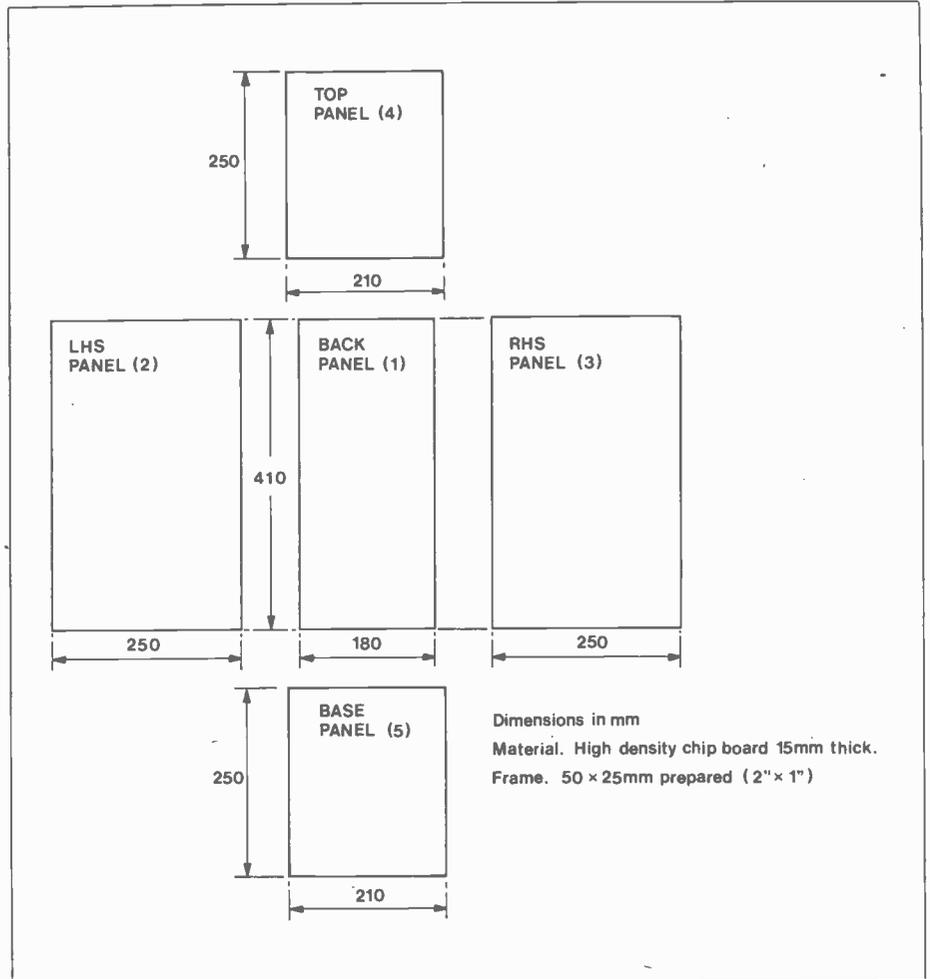


Figure 4. Panel cutting details.

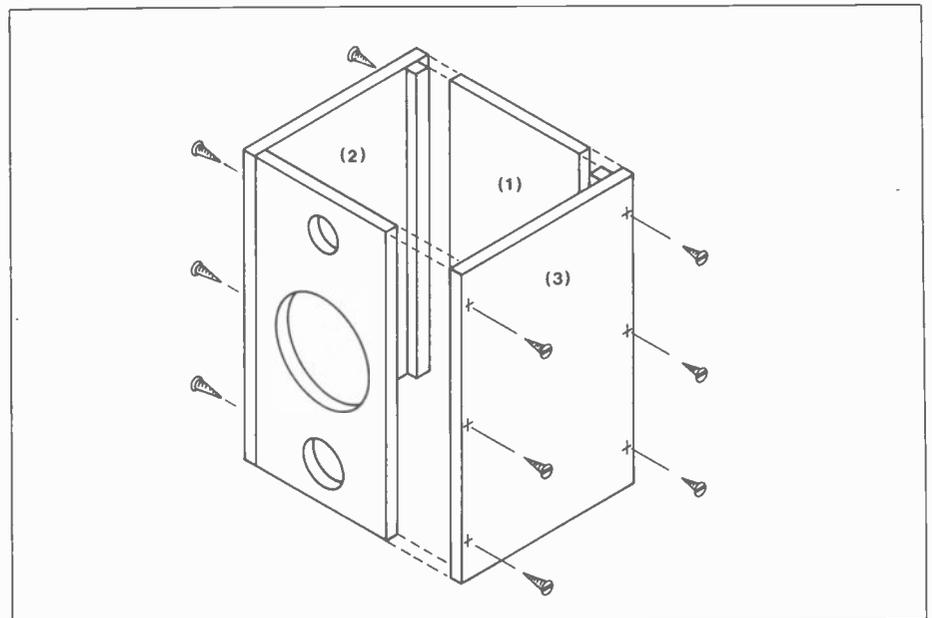


Figure 5. Panel assembly.

back panel to be removable, or perhaps you would not want to damage any external finish on the side panels, then the screws can be inserted through the back panel and into the frame instead.

Figure 6 shows details of the framework assembly and the inset drawing emphasises a 15mm recess to allow for the thickness of the back panel. Both vertical braces (8) & (9) are cut to the same length as the side panels (410mm),

whereas the two horizontal brace (6) & (7) lengths must allow for the particular thickness of material in use. Prepared timber can vary in size, but is usually 21mm for 1 inch, hence the length of 138mm being suggested in the cutting list! Glue the framework in position and use panel pins or wire nails to secure each timber while the assembly dries out and re-check the accuracy of the 15mm recess measurements.

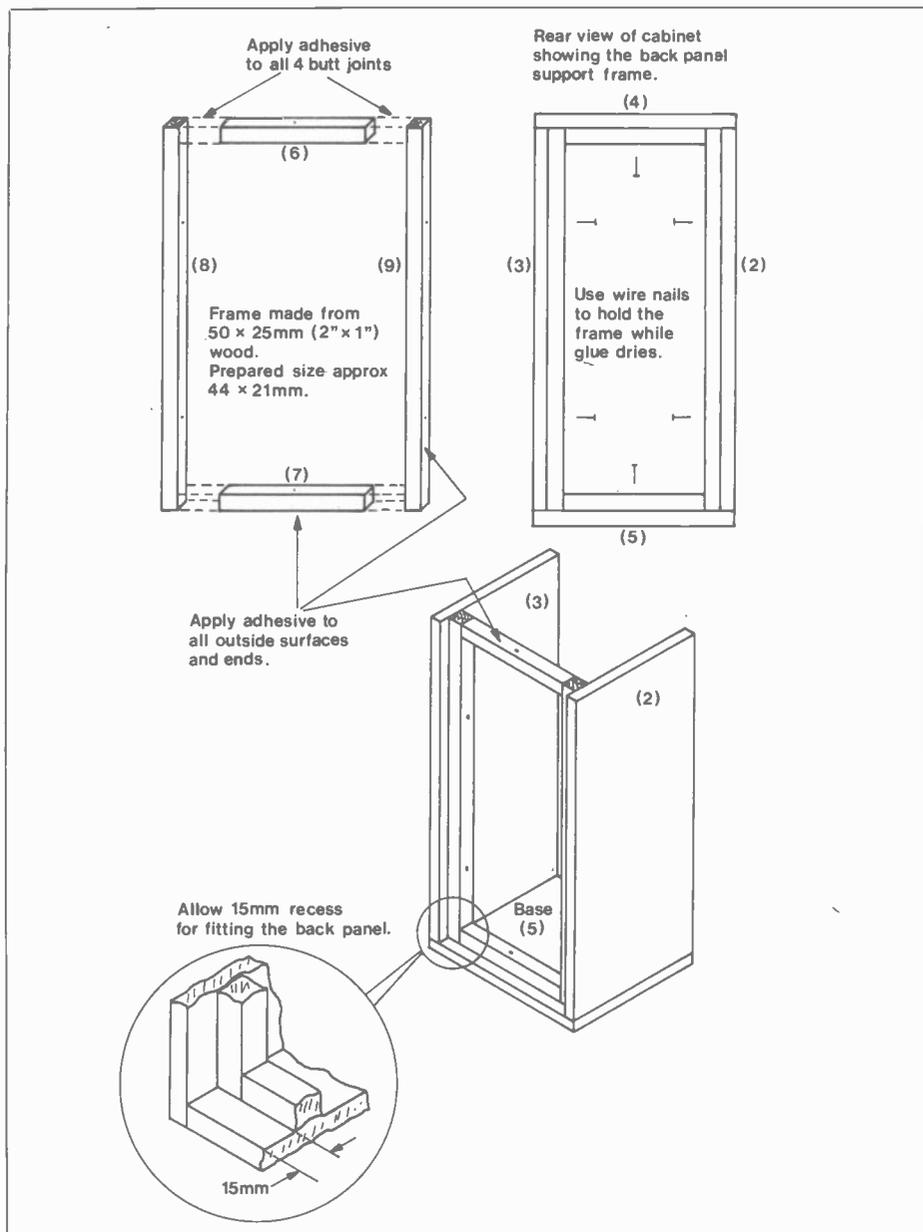


Figure 6. Back panel framework.

Port Tube

A length of plastic tubing is supplied with the kit as a resonator for tuning the cabinet. This 'port', as it is known, relies on the effect of Helmholtz resonance for greater LF acoustic output and lower cut off frequency than would be possible in a sealed box version. The tube is simply inserted into the 68mm cut-out, which should be a tight fit, and secured in place with a suitable adhesive or glue-gun. Apply the adhesive from the inside as shown in Figure 7.

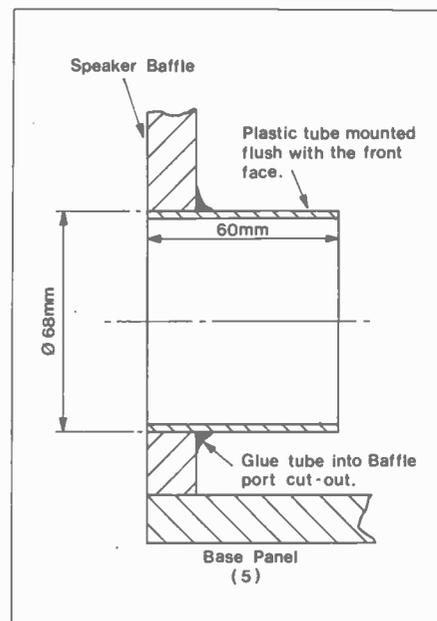


Figure 7. Port tube fitting.

Wadding



Use a sharp knife or scissors to cut out five sections of acoustic wadding. Each piece is glued onto the inside surface of

Specification

Fibre Glass Driver - YN25C

| | |
|---------------------|-----------------|
| Chassis | 173 x 173mm |
| Baffle | 145mm |
| Fixing | 124 x 124mm. |
| | 5mm clear |
| Flux Density | 13000 Gauss |
| Frequency Response | 35Hz to 5kHz |
| Power Handling | 40 Watts * |
| NOM Impedance | 8 Ohm |
| Sensitivity | 91dB (1W at 1m) |
| Coil Diameter | 25mm |
| Free Air Resonance | 40Hz |
| Moving Mass | 0.0114kg |
| Mechanical Q | 1.01 |
| Electrical Q | 0.22 |
| Total Q | 0.18 ** |
| Equivalent Air Load | 30 Litres |

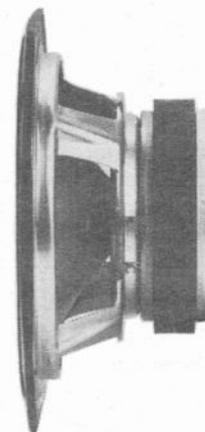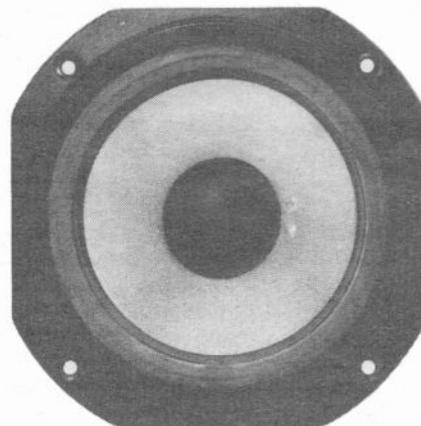* Power specification to DIN 45573. For further reading on this matter, see Electronics, March to May 1988, "Loudspeaker and Amplifier Specifications".




** Tests on the prototype have shown the total Q to be double that specified i.e. Total Q = 0.36. Although this figure may appear insignificant, its relevance

in cabinet design is extremely important and this 16 Litre design is based on the revised figure.

Specification

Miniature Dome Tweeter - FD94C

| | |
|--------------------|-------------------|
| Chassis | 74mm |
| Baffle | 48mm |
| Fixing | 3 x 4.2mm |
| Flux Density | 10600 Gauss |
| Frequency Response | 2500Hz to >25kHz |
| Power Handling | 40W @ 5kHz * |
| NOM Impedance | 8 Ohm |
| Sensitivity | 91.3dB (1W at 1m) |
| Coil Diameter | 10.5mm |
| Free Air Resonance | 2900Hz ± 400Hz |

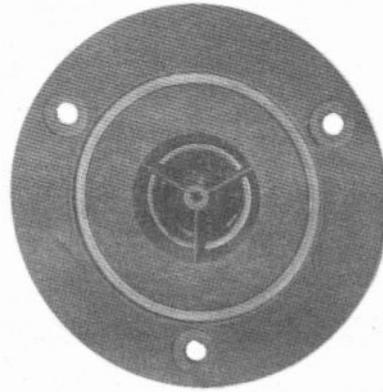

the top, base, side and back panels, but NOT onto the front baffle! Ensure that the piece glued onto the back panel does not foul the framework with the panel in place as this will prevent correct fitting. Also, drill a small hole in the back panel at least 30mm in from one edge and which is just large enough to allow the speaker connecting cable to pass through.

Speakers

Before installing the speakers into the cabinet, check that you can identify the positive (+) terminals on both units. It is important to wire speakers so that they have the same phase relationship, especially when two or more are used in stereo or quad applications. Here, the phase relationship just requires each speaker cone in the system to move in the same direction. If one speaker cone were to move inward while the other cone moved outward, then frequency cancellation takes place; this effect becomes prevalent at low frequencies and results in loss of bass. The tweeter + symbol is stamped into the plastic body moulding and is easy to spot, but the YN25 driver may only have a red dot painted on the chassis, close to the terminal block. If in doubt, connect a 1.5V battery to the speaker terminals so that the cone moves. If the cone moves inward to the speaker, reverse the battery connections so that the cone now moves outward and away from the speaker: the terminal connected to battery positive is now the speaker positive (+) and should be marked for later reference.

Now solder a length of black wire onto the tweeter negative terminal and a length of red wire onto the tweeter positive terminal. Place both wires through the small baffle cut-out, into the cabinet and out again through the driver hole. Insert the tweeter into the baffle from the outside, as shown in Figure 8 and secure in position with 3 x No 6 self tapping screws. It will be found helpful if small pilot holes are first made in the baffle before fitting the screws.

Solder any one end of the 1µF bi-polarised capacitor to the driver speaker positive terminal and the remaining end to the red tweeter wire, keeping the capacitor wires as short as possible to prevent them from shorting out. Solder the remaining black tweeter wire to the driver

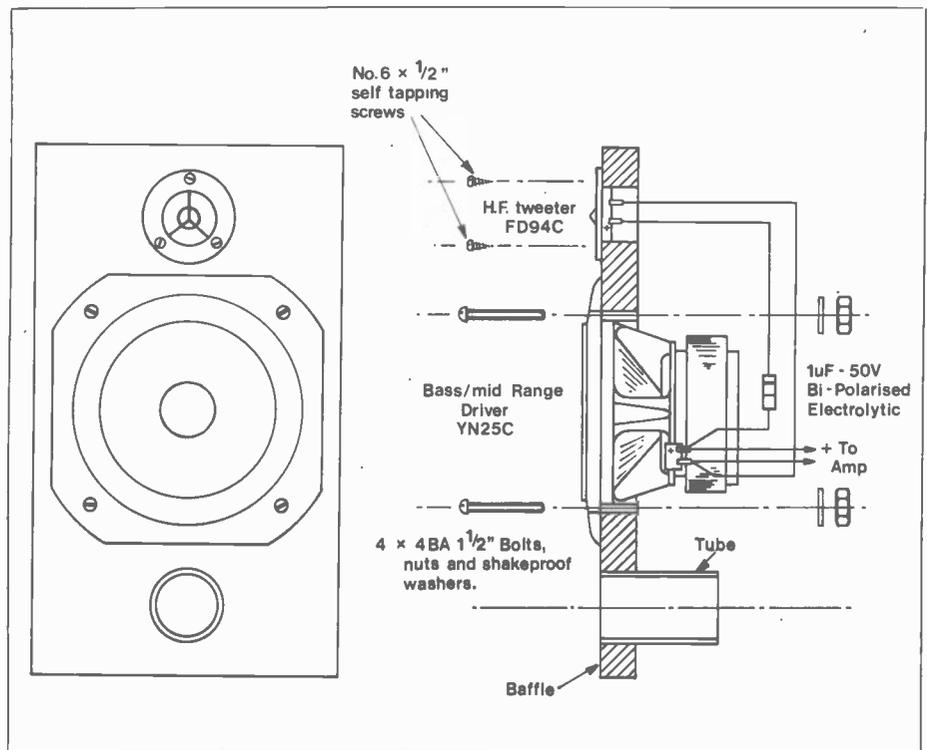


Figure 8. Fitting speakers.

negative terminal. At this time, it is convenient to terminate the cable or wires required for connection to the amplifier. This may be done directly or via a connector terminal as preferred. Whatever method is adopted, remember to identify the positive wire and solder it to the driver +V. Also, connect the negative or return common to the driver -V terminal as shown.

Mount the driver onto the baffle and align the four bolt holes, insert 4 x 4BA 1.5" bolts. Fit a shakeproof washer and nut onto each bolt, from the inside, and tighten each one accordingly. Placing a small blob of glue over these nuts will help prevent them from shaking loose in use and is recommended. Take care that adhesive is not spilt onto the speaker cone whilst doing this.

Final Assembly

Insert the connecting cable through the hole in the back panel and fit the panel in place. If you are using a connector terminal, solder the two speaker wires to

each terminal and mount the block over the wire-hole; otherwise squirt some glue down the wire-hole to seal it off. Screw the panel firmly in place to complete the cabinet as shown in Figure 9. The order in which you carry out the various assemblies is not important and the details are offered as a guide. For instance, if intending to veneer or decorate the cabinet in some way, this should be done before mounting the speakers - for obvious reasons!

Conclusion

A few points to remember are:

- (1) Handle loudspeakers carefully and protect them from contact with adhesive and damage from screwdrivers.
- (2) Ensure polarity markings are found correct before wiring.
- (3) In the cabinet, fill any gap along joints with a mixture of glue and sawdust to make air tight. Silicon rubber could also be used for this purpose, especially around the back panel and wire-hole.

(4) Do not subject the speakers to abuse by continuously over running them. Amplifiers rated 20 to 30 Watts RMS are generally suitable for use with this system.

(5) In a cabinet of this size, low frequency bass performance is very dependent on the size of a room and the position within the room, that is being used. Similarly, high frequency performance

is dependent upon local furnishings and listening positions within the room and is, therefore, worthy of some consideration to obtain the best possible performance.

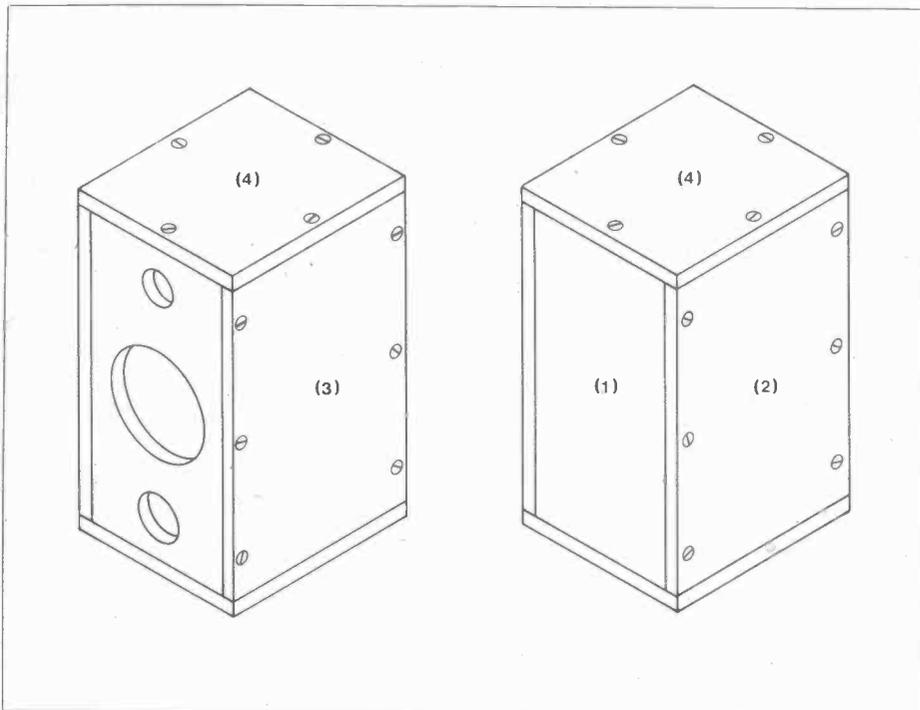


Figure 9. Final assembly.

2W16L CABINET PARTS LIST

| | | |
|----------------------------------|----|---------|
| Bass/Mid range Driver | | (YN25C) |
| Miniature Dome Tweeter | | (FD94C) |
| 1 μ F Reversolytic Capacitor | | (FB97F) |
| No.6 x 0.5in Sif-Tpr | 3 | (BF67X) |
| 4 BA x 1.5 inch Bolt | 4 | (LR52G) |
| 4 BA Nut | 4 | (BF17T) |
| 4 BA Shakeproof | 4 | (BF25C) |
| Wire 3202 Red | 1m | (XR36P) |
| Wire 3202 Black | 1m | (XR32K) |
| Acoustic Wadding | | (RY06C) |
| Port Tube 60 | | (YT03D) |
| 2W16L Baffle | | (XJ69A) |

Optional

| | | |
|------------------------|--|---------|
| Impact Adhesive | | (FL43W) |
| Rubber Sealer | | (YJ91Y) |
| Glue Gun | | (YF71N) |
| Glue Sticks | | (FS97F) |
| Lever Terminal 2-way | | (BW72P) |
| HiFi Loudspeaker Cable | | (XR72P) |

A complete kit, excluding Optional, is available:

Order As LM59P (2W16L Cabinet Kit)

Price £24.95

The following items are also available separately, but are not shown in our 1988 catalogue:

2W16L Baffle **Order As XJ69A Price £2.95**

Port Tube 60 **Order As YT03D Price 48p**

CALLING ALL HOME HOBBYISTS!

Would you like to appear in the pages of 'Electronics - The Maplin Magazine'? Now is your chance! If you are a dedicated electronics enthusiast who has built projects featured in the pages of this magazine, then we would like to meet you. Send brief details of yourself to the Editor, together with a list of projects you have constructed and any other information you feel we would find useful. You could then find one of our reporters calling on you to discuss your favourite hobby!

Write now to:

The Editor, Electronics, P.O. Box 3,
Rayleigh, Essex, SS6 8LR.



NEW BOOKS




Digital Audio and Compact Disc Technology

by Luc Baert, Luc Theunissen and Guido Vergult

The definitive book on the subject of CD players and the technology that goes with them. Essential reading for audio engineers, students and hi-fi enthusiasts, it covers all existing, and proposed, sound transmission and storage systems using digital techniques, specifically Pulse Code Modulation (PCM). DAT (Digital Audio Tape) is also described. This clear and easy to follow introduction has been produced using all the resources and expertise of the Sony Service Centre (Europe). Contents include: principles of Digital Signal Processing, sampling, quantization, A/D conversion, digital magnetic recording, error correction, the Compact Disc and encoding, opto-electronics and more.

1988. 253 pages, 192 x 252mm, illustrated hardback.

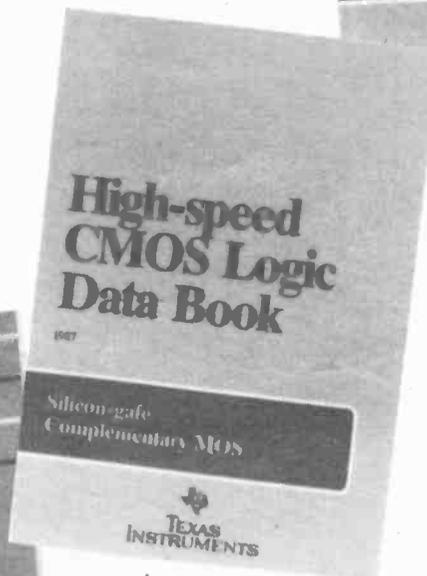Order As WS00A (Comp Disc Tech)
Price £20.00 NV




High Speed CMOS Logic Data Book

Texas Instruments

The high-speed silicon-gate HCMOS logic family ('HC' in the Semiconductors section of our catalogue) offers a range of all the functions of TTL and CMOS, but with the high speed and low power consumption of both. This has come about as the result of improved manufacturing processes, namely reducing the gate size and its overlap across the source and drain, resulting in smaller capacitances and hence faster switching speeds. This comprehensive volume lists all types in common use and offers a wealth of information more than sufficient for the systems designer. Information includes parameter and function tables, pin-outs, logic symbols and internal logic diagrams, and tips on device interfacing and applications for designers.

1987. 943 pages, 210 x 148mm, illustrated.

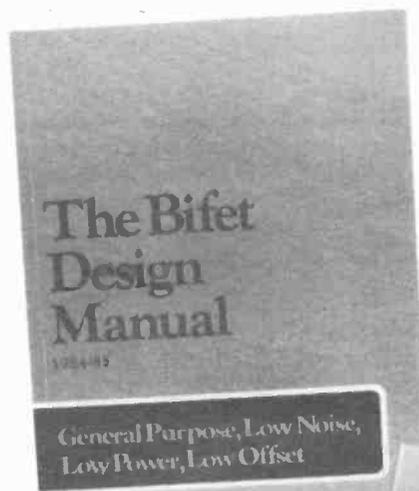Order As WS01B (HCMOS Data Book)
Price £12.50 NV



The Bifet Design Manual

General Purpose, Low Noise, Low Power, Low Offset

TEXAS INSTRUMENTS


The Bifet Design Manual

Texas Instruments

A design reference manual for a wide range of analogue circuit and system designs using the 'TL' series of Bipolar-JFET op-amps, compiled from a large number of individual applications. The book covers amplification, sampling, filter and oscillator circuits as well as data on individual devices and a section on miscellaneous circuits. Full circuit diagrams, design equations and descriptions of each circuit's operation are provided, together with, in many cases, an explanation of how the design equations have been derived, so that circuit operation can be understood more fully. Also these can be used as a basis for modifications to produce a design more compatible with a particular application. The applications circuits could be duplicated using different op-amps, provided that said differences are taken into consideration in the re-worked design equations. The book assumes the reader is familiar with circuit diagrams and general op-amp terminology.

1985. 96 pages, 210 x 148mm, illustrated.

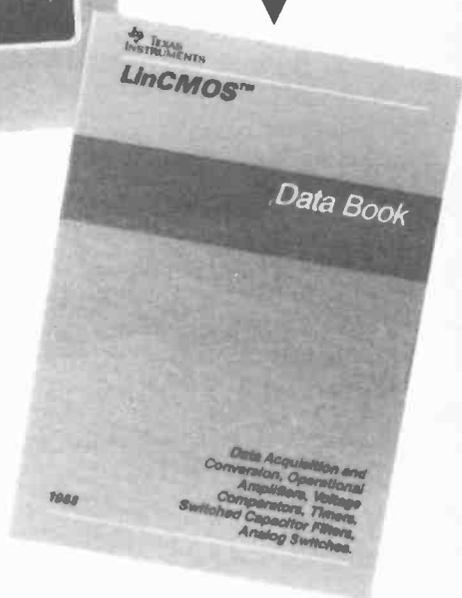Order As WS02C (Bifet Design Manual)
Price £3.95 NV



The LinCMOS Data Book

Texas Instruments





Low power, low voltage, single supply circuits with reduced operating temperature and enhanced reliability have enabled even more compact micro-computers, digital clocks and watches, calculators and the like, thanks to CMOS logic technology. Just recently the analogue side has been able to take advantage of these developments with the introduction of LinCMOS, a true linear technology, that overcame the problems of trying to produce suitable gates for reliable, linear operation. The first devices of this type to appear were op-amps, offering excellent stability with time, temperature and voltage, with single sided supply operation too! Now a complete range of analogue devices has grown up from these, and with the introduction of advanced LinCMOS, Large Scale Integration is possible producing devices containing both digital and analogue circuitry on the one chip.

This data book is a compilation of all the current LinCMOS data sheets, which include parameters tables, pin-outs, internal schematics and applications examples. The devices include operational amplifiers, voltage comparators, timers, A/D and D/A converters, analogue switches, and switched capacitive filters.

1988. 584 pages, 210 x 148mm, illustrated.

Order As WS03D (LinCMOS Data Book)
Price £9.00 NV

BENCHMARKS

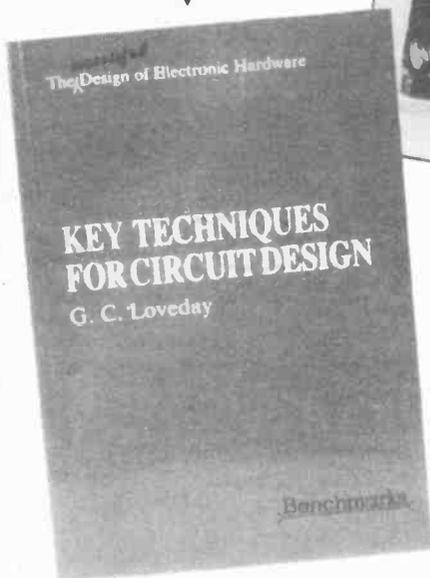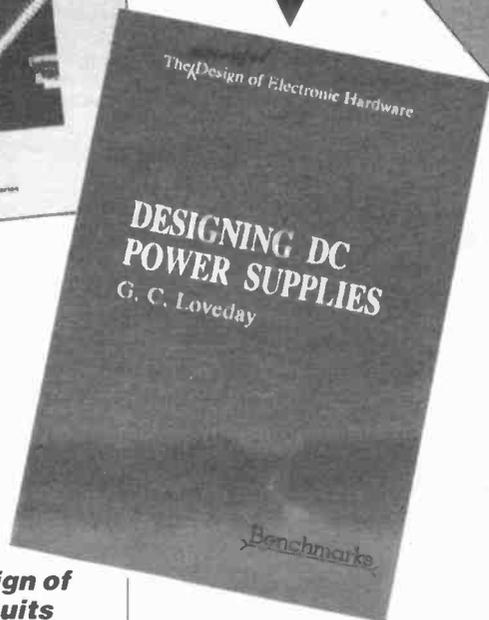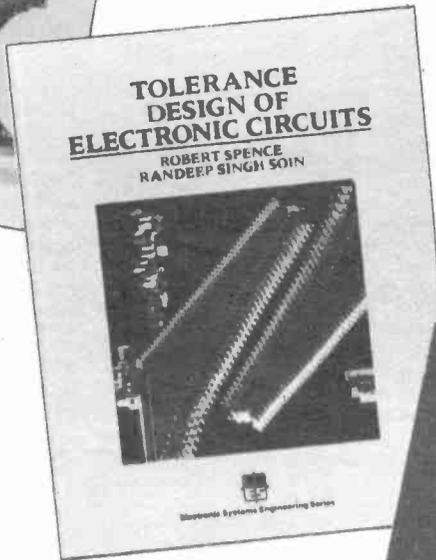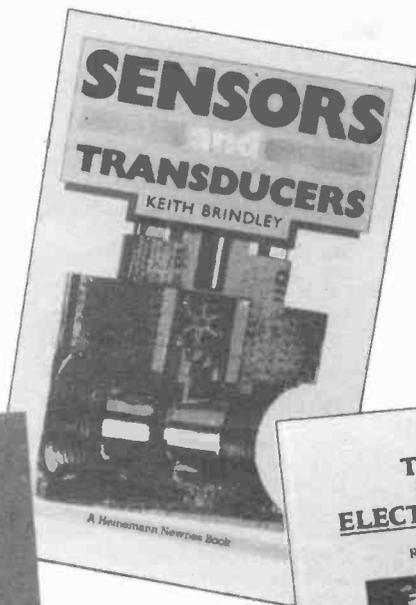

Key Techniques for Circuit Design

G.C. Loveday

Anyone interested in electronics, especially in an amateur way, may sooner or later either wish to or be required to design and build a working circuit or system of their own. Unfortunately this can prove to be a frustrating experience, as several different skills are required, which may on first acquaintance appear to be unrelated. It is all too common to possess either a sound grasp of the theory but be lacking in the practicalities, or to have a good practical aptitude without some of the theory. This book deals with the problems of designing circuits and systems from scratch, introducing the important concepts of drawing up target specifications, the sequence of the design, selecting devices and using equivalent circuits and "rules-of-thumb". All circuits comprise building-block elements, none of which have to be re-invented, only applied. As an aid to the teaching style of this book several design tasks are set with solutions provided at the end. Some basic understanding of electrical and electronic theory is assumed. Subjects include designing, testing, quality and reliability, passive components, inductors and transformers, selecting transistors, FETs and ICs, and equivalent circuits.

1988. 126 pages, 210 x 148mm, illustrated.

Order As WS04E (Key Tech Cct Design) Price £6.95 NV

Sensors and Transducers

by Keith Brindley

There is a considerable variety of transducers to choose from, but that does not necessarily mean that choosing one for a particular application is straightforward. It is often not simply a matter of opting for the likeliest transducer that will be easily interfaced to the measuring system – quite often, in quoted specifications, terms and procedures are stated which may deter an engineer from using a particular transducer when, in fact, it may be best suited to the task required. The problem may be that quite simply a better understanding of all types of transducer is needed before a particular type can be finally chosen. This book aims to provide that information, covering transducer principles, characteristics and engineering considerations, going on to describe transducer types for thermal, solid displacement, fluid, acoustic, optical and chemical measurements.

1988. 163 pages, 215 x 137mm, illustrated.

Order As WS05F (Sens & Trans) Price £12.95 NV

Tolerance Design of Electronic Circuits

by Robert Spence and Randeep Singh Soin

Tolerance design techniques are playing an increasingly important role in maximizing the manufacturing yield of mass produced electronic circuits. This book presents an account of design and analysis methods used to minimize the unwanted effects of component tolerances.

Highlights of the book include: An overview of the concepts of Tolerance Analysis and Design; a detailed discussion of the Statistical Exploration Approach to tolerance design; an engineering discussion of the Monte Carlo statistical method and a presentation of several successful examples of the application of tolerance design.

This book will be highly appropriate for professional electronic designers, computer aided design specialists, electronic engineering undergraduates and graduates taking courses in Advanced Electronic Circuit Design.

215 pages, 192mm x 240mm, illustrated.
Order As WS06G (Tol Design Ccts) Price £18.95 NV

Designing DC Power Supplies

by G. C. Loveday

The power supply is a vital part of an electronic system and its design needs careful consideration if excessive noise, poor stability, crosstalk and other fault conditions are to be avoided. This book deals with all aspects of the design of DC regulated power units, both linear and switched mode types, and is aimed at assisting anyone who wishes to carry out their own design work.

The early chapters discuss specifications, design methods, test strategies and circuit operations. Later chapters deal with transformer, rectifier and filter design and the important area of regulation. Several complete design problems are described and reader exercises, all with solutions, are provided at the end of each chapter.

131 pages, 150mm x 210mm, illustrated.
Order As WS07H (Design DC PSUs) Price £6.95 NV

VARIOUS FOR SALE

Pye Bantam Transceiver Walkie-Talkie. G.W.O. Re-chargeable battery. Leather cased. £70. Tel: 021 - 426 4471.

Kenwood 8400 UHF FM Amateur Radio Transceiver, 430/440MHz, Memories, Scanning, Auto Repeater Shift, Mobile Mounting, Base PSU, Antenna, Boxed, £195 ono. (08864) 588 (Ansaphone).

Thorn EMI 400 Watt Mercury Vapour Area Floodlight. Excellent complete. £95. Tel: 021 - 426 4471.

T.V. Pattern Generator 'Labgear Colourmatch' 625 Lines. £20. Stuttard, 1 St. Mary's Road, Liss. Tel: (0730) 892487.

100W Loudspeaker. Full range system. Custom-built for Lead/Rhythm Guitar but suitable for keyboards, disco, P.A. 41. Excellent condition. 31" x 20" x 12". Offers? 0732 - 832737 evenings.

Resistors. Good selection from 10R to 1M. All 5% or less. Over 700 items in total. £5 post free. Tel: Ashford, Kent 0233 - 27285.

Retired Engineer has for disposal Amplifiers, Tuners, Record Decks, Modules, Components, etc. SAE please to C.J. Gates, 97 Craven Road, Newbury, Berks, RG14 5NL, for details.

Isolation Transformer 250/250V 500 VA. £20. Stepdown Transformer. Split output. 0-115V/0-115V. Input 250V. 300 VA. £15. Transformer. 5" x 3 1/2" x 4".

Input 240V. Output 334-0-334V. 6.4V 4.5A. 4V 2.6A. 2V 1.4A. 4V 7.5A. £5. Carriage extra. Tel: 0424 213479.

Rohde & Schwarz SDR BN41022 Signal Generator 300/1000MHz, Handbook, £75. Will consider exchange with VHF (200MHz) Frequency Counter. Negotiate collection/delivery. Woking 04862 62671.

The Radio & Television Servicing books. Models from 1980 back to the 50's. 25 books at £1 each for the lot. Tel: Lancing 755204.

Project Book Two Maplin Alarm. Ready-built and working. £30.00 ono. Tel: 051 - 677 4079 after 6.00pm and weekends.

Enthusiast, 70 years old clearing out. I have 40 good moving coil milliammeters etc., some Ex.W.D. (1940's) and some new and modern. Would accept £30 for the lot. Also 6 pairs of Ex.W.D. headphones, 1940's, DLRS, very sensitive. Super for crystal sets! Say £15 the lot. SAE for detailed list please. Mr. King, Allet Cottage, Truro, TR4 9DJ.

Tamiya 'Striker' one tenth Radio Controlled Car. Scale speeds of 250mph. Good condition except damaged chassis. Including Acoms Techniplus Radio Control. (Excellent condition.) £60-£65 ono. Many spares. Tel: (0444) 459551.

Night Light Kit. When darkness falls, circuit switches on a light automatically. Any light can be used. Ideal burglar deterrent. All electronics and case. £7.95 inc. P&P. Cheques please to: S. Lord, 6 Stubbing Brink, Hebden Bridge, W. Yorks, HX7 6LR.

Oscilloscope valued, needs attention £5. Nova Computer, small for its age, with manuals £8. Tel: 0689 55965.

CLASSIFIED

If you would like to place an advertisement in this section, here's your chance to tell Maplin's 300,000 customers what you want to buy or sell, or tell them about your club's activities - absolutely free of charge. We will publish as many advertisements as we have space for. To give a fair share of the limited space, we will print 30 words free of charge. Thereafter the charge is 10p per word. Please note that only private individuals will be permitted to advertise. Commercial or trade advertising is

strictly prohibited in the Maplin Magazine. Please print all advertisements in bold capital letters. Box numbers are available at £1.50 each. Please send replies to Box Numbers to the address below. Please send your advertisement with any payment necessary to: Classifieds, Maplin Mag., P.O. Box 3, Rayleigh, Essex SS6 8LR.

For the next issue your advertisement must be in our hands by 3rd October 1988.

Infra Red Remote Control Robot as featured in Maplin Catalogue page 503. Ready-built, tested and working. Very good condition - hardly used. Only £25. Phone Nigel on Hertford (0992) 880588.

Telegquipment Oscilloscope Service Manuals all at £5.00 each including postage. D-31/R. D-43. D-52. S-43. S-51. S-51B/E. Serviscope Minor. Mr. Small, 8 Cherrytree Road, Chinnor, Oxfordshire, OX9 4QY.

Tech TE-20D R.F. Signal Generator £43. Metrix 210 Wobulator (R.F. Sweep Gen) £39. Tech TE-40 Audio Millivoltmeter £24. Heathkit V-7AU Valve Voltmeter £29. Intracopt N7118 Colour-Bar Generator £39.00. Maplin Speech Synthesiser £23. Tel: 0502 566026.

Lots back-issues electronics magazines for sale. Maplin, ETI, HRT, PW, etc. Amstrad mags Amtix, CWA, ACU, AA. SAE for list. Mr. Small, 8 Cherrytree Road, Chinnor, Oxon, OX9 4QY.

Learnaltd Oscilloscope and Manuals for Course, assortment of Resistors, Capacitors, Diodes, Transistors, Chips. Bags of each. Fully-loaded Computer Boards. Bargain at £200.00 the lot ono. Contact Mal at Reading 68278 (evenings).

High Quality Copper Clad Circuit Board 280mm x 216mm, double-sided £1.50. Send cheques to M. Fitch, 56 Hall Green Lane, Hutton, Brentwood, Essex, CM13 2QU.

Oscilloscope Farnell Model DTC12. 5 inch Tube. Size 12" x 11" x 6 3/4". Bandwidth DC-12MHz. Dual Trace, component testing facility. Leads instructions, shoulder carrying case as new. List Price @ £450 + VAT, Sell at £350. Tel: 01-681 5713.

COMPUTERS

Tatung Einstein Colour 80K Computer. 14" colour monitor, internal disk drive, Brother M1009 printer, Radio Shack four colour plotter, spectrum emulator, + many disks. £300. Tel: Reading (0734) 860185.

Tandy TRS 80 Colour Graphic Printer. Type CGP 115, complete with power unit. As new. £25. Tel: 021-426 4471.

Offer on Sirius 1 + software, and Commodore 1541 Disk Drive. Tel: 0732 822959.

BBC Computer Games. Elite £8.50. GAC Disk £18. Siege £1. Tennis £1. Pascal Chips £60 ono + much more. Buy over 25 games + other software for £100. Tel: 0277 228224.

Atari 8-bit Software Disks: Ghostbusters £3.50. Pole-position £3.25. DOS-3 £1.25. Cassettes: Smash Hits 5 £3.00. Atari ST User magazines. March 1986 to March 1987 £5. Tel: (0444) 459551.

Amstrad CPC Maplin ROMboard including Test ROM £30, AMX Mouse and Stop-Press £45 each. Also CPC software on disk, ROM and cassette available. Tel: (0204) 593189.

MUSICAL FOR SALE

Casio MT-205 Electronic Keyboard. 10 months old complete with drum pads, manual and box. Only £100. Tel: 0787 247554 (Sudbury, Suffolk).

MIDitations - easy listening music performed/arranged by David Howard on synthesizers and MIDI. Cassette at £3.50 (inc. P&P) payable to David Howard, 9 Cavendish Drive, Leytonstone, London, E11 1DN.

Casio PT-80 Keyboard 12 rhythms, 8 sounds, ROM pack memory function, auto play. In original box with manual and ROM pack. Any offers 01-789 9954.

One Pioneer PL-3F Stereo Turntable with ARCAM 77 series magnesium body cartridge. Excellent condition £110 ono. Tel: Newcastle, Staffs 680726.

Philips N4504 4-track Tape Deck. 3 speeds, motors, heads, 5 tapes, service, operating manuals. As new. £45, carriage extra. Seon Smyth, 'De Porres' 67 East Princes Street, Helensburgh, C84 TDG. Tel: 0436 71181.

Music Centre Dynatron SRX 30B. Record, Tape and Tuner. Wood Cabinet. All offers considered. 0732 832737 evenings only.

Spectrum Synthesiser constructed with aluminium case and oak end cheeks. Needs Curtis chips and setting up to complete. £75 ono. David Larner, Ct. Yarmouth 721879.

Maplin Ten Channel Stereo Graphic Equaliser, attractive slimline case £50. Full size Equaliser case plus pots £10. Hitachi Tape Deck, dolby, chrome, fully-serviced £60. Tel: Hayward Heath (0444) 892558.

Matinee Organ with stool. Full working order. Very good condition. Quick sale required. Any serious offer accepted. 0732 832737 evenings.

Casio MT600 Keyboard MIDI IN/OUT, 40 voices, 20 rhythms, chord/operation memory, pitch bend, and many other features. Hardly used, with mains adaptor £190. Tel: 01-886 4954.

Unfinished Project: Maplin 61-note Piano Parts. All IC's, PCB's and most components. £40 for quick sale. Tel: 0925 825426.

Pair Hi-Fi Loudspeaker Cabinets 29" x 14" x 11.5", KEF T27, KEF B110, Bass 13" x 8", KEF 3-way XOVER, £50. Tel: 0222 628473.

WANTED
Medium Format Camera outfit. (08864) 588 (Ansaphone).

HELP! I'm converting a small commercial calculator for operation on standard (AA) batteries without any result. Please write to M. Fitch, 56 Hall Green Lane, Hutton, Brentwood, Essex, CM13 2QU.

Service Manual for GEC H.F. Receiver Model RC411. Buy or loan for photocopying. M. Levers, "Waverley", Independent Hill, Alfreton, Derbyshire, DE5 7DG.

Any information/books on interfacing into the Spectrum + 2, especially stepper motors and plotters. Needed for GCSE Project. Tel: 0454 260428.

Maplin Keyboard only complete, with instructions for ZX81. Must be in good condition. Contact: John Squires, 44 St. Marys Road, Wheatley, Doncaster, S. Yorks, DN1 2NP. Tel: 0302 323650.

Mapsat Software - HELP! We need program listings for Amstrad PC1512 and BBC B to demonstrate equipment in schools. Tel: Kevin or Simon on 0769 83930 ext. 26 weekdays 9.30 to 4.30.

Valve Amplifier. Leak TL/50 Plus. Also interested in Quad or Radford Valve Amplifiers. Enthusiast enjoys collecting and restoring. Does anyone have a Williamson Valve Amplifier they wish to sell? Or Williamson Transformers? Contact: D.M. Craig, Tyneside 4886615.

MSX information. User groups, cartridge/expansion port connections, circuit diagrams for disk interface, ROM/RAM cards etc. Mr. I. Moody, 9 Carmel Gardens, Darlington, Co. Durham, DL3 8JD.

Detailed Circuit Diagram and Parts List for a Hearing Loop for a Church. Contact: G.E. Stammers, 10 Ashville Terrace, Leeds, LS6 1LZ.

JVC - CD-4. 4-Channel Demodulator for 4VR 5414 FM-AM 4-Channel Receiver. Spares. (0272) 420516 (day) or (0272) 41227 (evening).

Disassembler/Assembler software on tape for Sinclair ZX81. Originally sold by Bug-Byte, now unavailable. Contact: J. Leech, 60 Broadwaters Road, Lowestoft, Suffolk, NR33 9HS. Tel: 0502 568106.

Pair of Walky Talkies wanted in working order. Contact: Gary Fennal, Hadyn House, Church Street, Hanswell, Gainsborough, Lincs, DN21 5UN.

MAPLIN'S TOP TWENTY KITS

| THIS LAST MONTH | DESCRIPTION OF KIT | ORDER CODE | KIT PRICE | DETAILS IN PROJECT BOOK | | | | | |
|-----------------|--------------------------------|------------|-----------|-------------------------|----------|---------------------------|-------|--------|--------------|
| 1. (1) | ◆◆ Digital Watch | FS18U | £2.00 | Catalogue | 13. (13) | ◆◆ 27MHz Receiver | LK56L | £8.95 | 13 (XA13P) |
| 2. (2) | ◆◆ Live Wire Detector | LK63T | £3.95 | 14 (XA14Q) | 14. (15) | ◆ Car Digital Tacho | LK79L | £19.95 | Best of E&MM |
| 3. (8) | ◆ I/R Prox. Detector | LM13P | £8.95 | 20 (XA20W) | 15. (18) | ◆ Noise Gate | LK43W | £9.95 | Best of E&MM |
| 4. (5) | ◆ 150W Mosfet Amplifier | LW51F | £19.95 | Best of E&MM | 16. (17) | ◆ 50W Amplifier | LW35Q | £17.95 | Catalogue |
| 5. (6) | ◆ U/Sonic Car Alarm | LK75S | £17.95 | 15 (XA15R) | 17. (14) | ◆ 27MHz Transmitter | LK55K | £7.95 | 13 (XA13P) |
| 6. (4) | ◆ Partylite | LW93B | £9.95 | Best of E&MM | 18. (16) | ◆ VHS Video Alarm | LM27E | £11.95 | 24 (XA24B) |
| 7. (7) | ◆ Car Burglar Alarm | LW78K | £7.95 | 4 (XA04E) | 19. (-) | ◆ Frequency Meter Adaptor | LK20W | £7.95 | 9 (XA09K) |
| 8. (11) | ◆ PWM Motor Driver | LK54J | £9.95 | 12 (XA12N) | 20. (19) | ◆ TDA7000 Radio Kit | LK32K | £12.95 | 9 (XA09K) |
| 9. (12) | ◆ Ultrasonic Intruder Detector | LW83E | £11.95 | 4 (XA04E) | | | | | |
| 10. (9) | ◆ 8W Amplifier | LW36P | £5.95 | Catalogue | | | | | |
| 11. (10) | ◆ 15W Amplifier | YQ43W | £5.95 | Catalogue | | | | | |
| 12. (-) | ◆ Logic Probe | LK13P | £13.95 | 8 (XA08J) | | | | | |

Over 150 other kits also available. All kits supplied with instructions. The descriptions above are necessarily short. Please ensure you know exactly what the kit is and what it comprises before ordering, by checking the appropriate Project Book mentioned in the list above - see inside back cover for details.

DID YOU MISS THESE ISSUES?

Project Book 1 Universal Timer. Programmable mains controller. **Combo-Amplifier.** 120W MOSFET power amp. **Temperature Gauge.** 10°C - 100°C, LED readout. **Pass The Bomb!** Pass-The-Parcel with a difference. **Six easy-to-build Projects on Veroboard.** Car batt. monitor; Colour snap game; CMOS Logic Probe; Peak Level meter; Games timer; Multi-colour pendant.

Order As XA01B (Maplin Project Book No. 1)
Price 85p NV.

Project Book 2 Digital Multi-Train Controller. Controls up to 14 model trains. **Home Security System.** Six independent channels. **Digital MPG Meter.** With large LED display, a must for more economical motoring.

Order As XA02C (Maplin Project Book No. 2)
Price 85p NV.

Project Book 3 ZX81 Keyboard. 43 keys, plugs directly into ZX81 with no soldering. **Stereo 25W MOSFET Amp.** 25W r.m.s per channel; Disc, Tape, Tuner & Aux. **Radar Intruder detector.** 20 metres range, may be used with our security system. **Remote Control for Train Controller.** Remote control by infrared, radio or wire.

Order As XA03D (Maplin Project Book No. 3)
Price 85p NV.

Project Book 4 Telephone Exchange. Up to 32 extensions on 2-wire lines. **Remote Control for Amplifier.** Volume, balance and tone controlled via infra-red link. **Frequency Counter.** 8 digit DFM, 10Hz - 600MHz range. **Ultrasonic Intruder Detector.** Areas up to 400 square feet can be covered.

Order As XA04E (Maplin Project Book No. 4)
Price 85p NV.

Project Book 5 Modem. 300 baud transmission speed over normal telephone lines. **Inverter.** 240V AC 60W from 12V car battery. **ZX81 Sound Generator.** 3 tone generators fully controlled from BASIC. **Central Heating Controller.** Optimised performance with this advanced system. **External Horn Timer.** Exterior intruder alarm. **Panic Button.** Add on to our Home Security System. **Model Train Projects.** Add on to our Multi-Train Controller. **Interfacing Micro processors.** How to use parallel I/O ports, with circuits.

Order As XA05F (Maplin Project Book No. 5)
Price 85p NV.

Project Book 6 VIC20 & ZX81 Talkbacks. Speech synthesis projects. **Scratch Filter.** Tunable active circuit 'reclaims' scratched records. **Bridging Module.** Converts two 75W MOSFET amps to one 400W full bridge amplifier. **Moisture Meter.** Finds damp in walls and floors. **ZX81 TV Sound and Normal/Inverse Video.** TV sound and inverse video direct. **Four Simple Veroboard Projects.** Portable Stereo Amp; Sine Generator; Headphone Enhancer and Stylus Organ.

Order As XA06G (Maplin Project Book No. 6)
Price 85p NV.

Project Book 7 CMOS Crystal Calibrator. For amateur radio receiver calibration. **DX'er's Audio Processor.** Improved sound from Communications Receivers. **Enlarger Timer.** An accurate timer for the darkroom. **Sweep Oscillator.** Displays AF frequency response on an oscilloscope screen. **VIC20 and ZX81 Interfaces.** RS232 compatible.

Order As XA07H (Maplin Project Book No. 7)
Price 85p NV.

Project Book 8 Spectrum Modem/RS232 Interface. 2400 baud self contained operating system. **Synchme.** Simulates bells, gongs and other chiming sounds. **Dragon 32 RS232/Modem Interface.** Plugs into ROM expansion port. **Codelock.** Programmable electronic lock. **CMOS Logic Probe.** Digital display shows logic states. **Minilab Power Supply.** Versatile unit for the test bench. **Dragon 32 I/O Ports.** Two 8-bit ports. **Doorbell for The Deaf.** Flashing lamp attracts attention.

Order As XA08J (Maplin Project Book No. 8)
Price 85p NV.

Project Book 9 Spectrum Keyboard. 47 full travel keys. **VIC Extendiboard.** Three expansion ports, one switchable. **Oric Talkback.** Speech synthesiser for the Oric 1. **TDA7000 FM Radio.** Complete FM receiver on a chip. **ZX81 High Resolution Graphics.** 256 x 192 fine pixel display. **Nine Projects!** Personal Stereo Dynamic Noise Limiter; Logic Pulser; TTL/RS232 Converter; Pseudo Stereo AM Radio; and more.

Order As XA09K (Maplin Project Book No. 9)
Price 85p NV.

Project Book 10 Spectrum Easyload. Helps cassette loading with the Spectrum. **80m Receiver.** Simple SSB direct conversion receiver. **Fluorescent Tube Driver.** 8W 12V for camping and caravanning. **Auto-Waa.** Automatic waa-waa effects unit. **Digi-Tel Expansion.**

Expands Maplin Telephone Exchange to 32 extensions. **Oric 1 Modem Interface.** Adapts the Oric 1 to the Maplin Modem. **Dragon 32 Extendiport.** Makes the Dragon's cartridge socket more accessible.

Order As XA10L (Maplin Project Book No. 10)
Price 85p NV.

Project Book 11 Mapmix. Six channel audio mixer. **Xenon Tube Driver.** Xenon flash tube module with strobe. **Enlarger Exposure Meter.** Simple inexpensive tool for the darkroom. **8 Channel Fluid Detector.** Check/control fluid level in up to 8 containers. **Servo & Driver Module.** Servo mechanism with driver module kit. **Mk II Noise Reduction Unit.** Improves signal/noise ratio of tape recordings. **Cautious Ni-Cad Charger.** Controlled charging of ni-cad cells. **Motherboard for The BBC Micro.** Gives easy access to ports.

Order As XA11M (Maplin Project Book No. 11)
Price 85p NV.

Project Book 12 RTTY Unit. The TU1000 receives/transmits Radio Teletype; connects to computer via RS232. **Computadrum.** Use your computer as a drum synthesiser. **Light Pen.** Draw onto the TV screen or select menu options. **PWM Motor Drive.** Reversible model motor driver for 6V and 12V.

Order As XA12N (Maplin Project Book No. 12)
Price 85p NV.

Project Book 13 Explosive Gas Alarm. Flammable gas detector. **Flash Meter.** Get your exposure right when using your flash gun. **Musical Announcer.** A doorbell with a difference. **Mains Controller.** An add-on for the 8-Channel Fluid detector.

Order As XA13P (Maplin Project Book No. 13)
Price 85p NV.

Project Book 14 Live Wire Detector. Invaluable aid for the handyman. **Trundle.** The line follower robot as featured on Channel 4. **4-Channel PWM Controller.** Digital control of motors and servos. **Display Driver Module.** How to use our LED bargraph display ICs. **Control-A-Train.** Full inertia control of model trains. **Spectrum I/O Controller.** Buffered 2-way 8-bit data bus and 8 control lines.

Order As XA14Q (Maplin Project Book No. 14)
Price 85p NV.

Project Book 15 Z80 CPU Module. Expandable CPU based controller. **Sharp MZ-80K Serial Interface.** Get into communications with this project. **Ultrasonic Car Alarm.** Stop car thieves. **Active Crossover.** Includes matched output power amplifiers. **Guitar Equaliser.** Specifically for six string electric guitars. **Fabulous Five.** A selection of interesting circuits.

Order As XA15R (Maplin Project Book No. 15)
Price 85p NV.

Project Book 16 Floodlight Controller. Both power supply and mains switching unit for the Infra-red Intruder Detector Kit. **Spectrum Parallel/Serial Interface.** Provides 8-bit I/P and O/P parallel or serial transfer with programmable UART. **Mains Tx/Rx Data Communications System.** Sends or receives data via the mains wiring. **16-Channel Logic IC Tester.** Simultaneously displays logic states for any logic IC of up to 16 pin-outs on your oscilloscope.

Order As XA16S (Maplin Project Book No. 16)
Price 85p NV.

Project Book 17 Video Digitiser. Interface a TV camera to your computer. **Mixing It.** A comprehensive range of audio amplifier modules. **Hobbyist's Temperature Controller.** General purpose electronic mains power thermostat. **ASCII Keyboard.** Professional computer keyboard with standard ASCII output. **Play Along Mixer.** Play along to your favourite records and tapes on your own instrument.

Order As XA17T (Maplin Project Book 17)
Price 85p NV.

Project Book 18 Weather Satellite Receiver. Display regional weather systems on your TV or monitor. **Mixing It Part 2.** Mono/stereo Hi-Z mic input, mixer and line amplifiers; VU/headphone driver. **Stepper Motor Driver.** How to build and start using the Stepper Motor Kit featured in the Catalogue. **Amstrad Expansion System.** The Maplin Amstrad External ROM Card System for the CPC 464, CPC 664 and 6128.

Sealed Lead Acid Battery Charger. Special high stability output with automatic trickle charge mode for sealed lead acid batteries. **Fantastic Five.** Veroboard projects comprising HF tremelo unit, crystal checker, clap switch, low-Z ohmmeter, snooze timer.

Order As XA18U (Maplin Project Book 18)
Price 85p NV.

Electronics Issue 19 Active Aerial and Aerial Tuning Unit. Get more from SW. **Amstrad Expansion System.** 6 x 8-bit parallel I/O card and PSU. **ADA Digital Echo.** RAM based low cost echo machine. **Mixing It.** Mixer Modules' PSU.

Order As XA19V (Maplin Magazine Volume 5 Issue 19) Price 75p NV.

Project Book 20 Weather Satellite Decoder. Displays output from Satellite Receiver on TV or monitor. **Infra Red Proximity Detector.** Short range heat or movement detector. **Fibre-Optic Link.** Sends AF signals over up to 20m of fibre-optic cable. **Low-Z Microphone Pre-amp.** For 200-600Ω mics plus gain adjustment.

Order As XA20W (Maplin Project Book 20)
Price 85p NV.

Electronics Issue 21 6 Channel Burglar Alarm. Develop a complete security system. **Six Circuits.** Bass Fuzz, Voice-Over Unit, Noise Gate, Envelope Tremolo, RTTY Decoder and Scratch & Rumble Filter on veroboard. **Notch Filter.** AF processor for communications receivers. **12V Public Address System.** 10W per channel from car battery. **Tungsten Lamp Controller.** AC phase control for mains lamps.

Order As XA21X (Maplin Magazine Volume 6 Issue 21) Price 85p NV.

Electronics Issue 22 MIDI Interfacing Techniques. Connect MIDI instruments to the VIC20 or CBM64. **Hi-Fi Speakers & Enclosures.** Two high quality loudspeaker cabinet designs. **Keypad for Z80 CPU.** At last a keypad I/F & ROM for the Z80 CPU kit. **4½ Digit Counter.** Versatile basic counter module to 4½ digits. **Weather Satellite Down Converter Part 1.** Aerial & freq. converter for MAPSAT Receiver to tune into the Meteosat satellite. **Mini Circuits.** Veroboard Audio Level Tester, Sound Triggered Flash, In-Circuit Resistance Meter, I/R Audio Isolator.

Order As XA22Y (Maplin Magazine Volume 6 Issue 22) Price 85p NV.

Electronics Issue 23 MAPSAT Frame Store #1. Z80B CPU controller. **Servo Tester.** Proportional servo tester. **Weather Satellite Down Converter Part 2.** Channel Switching Unit. **Capacitance Tester.** 5 ranges, 3 digit display. **More Mini Circuits.** Movement alarm, Stepper Motor Driver, Pink Noise Generator, Optical Port Data Link, 'Metal Pedal'.

Order As XA23A (Maplin Magazine Volume 6 Issue 23) Price 85p NV.

Electronics Issue 24 Nuclear Radiation Monitor. Alpha, Beta, Gamma & X-ray gieger counter. **VHF Pre-Amp Module.** MAPSAT VHF pre-amp. **External Horn Programmable Timer Update.** Modifying the module for use with other than the Maplin Home Security System. **MAPSAT Frame Store #2.** The Video Graphics Card. **VHS Video Alarm.** Battery powered portable movement alarm built into a VHS Video Cassette.

Order As XA24B (Maplin Magazine Volume 6 Issue 24) Price 85p NV.

Electronics Issue 25 Track side Rapid Charger. Model radio control car ni-cad battery pack charger using 12V car battery as power source. **Slow Charger.** Mains powered trickle charger for model cars. **Temperature Module Expansion.** Relay switching board and serial to parallel converter add-ons. **Disco Partylite.** High quality, 3 channel party lights. **Mini Metal Detector.** Detects ferrous and some non-ferrous metals such as iron wall board nails or brass screws. **Tester for Electrical Domestic Appliances.** Check the safety of any new appliance before you plug it into the mains. **Bob's Mini Circuits.** A pulsed speed controller, a train controller & an electronic lock.

Order As XA25C (Maplin Magazine Volume 7 Issue 25) Price 85p NV.

Electronics Issue 26 1kW High Power Mosfet Amplifier. Superb amp primarily aimed at use in halls, auditoriums, etc. **Simple Melody Generator.** Versatile musical project with four tunes available. **Multi-Tune Generator.** Built around the UM3411A giving 16 tunes etc. **Siren Sound Generator.** Gives 4 different types of siren noises. **Programmable Metronome.** Useful musicians aid.

Order As XA26D (Maplin Magazine Volume 7 Issue 26) Price 85p NV.

Electronics Issue 27 TDA 7000 FM Radio MkII. Complete radio kit including case. **3-Way Loudspeaker System.** 20 litre passive radiator cabinet design. **Watt Watcher.** Check to see if you are overdriving your speakers. **Morse Code Practice Oscillator.** Learn Morse Code the practical way with this excellent project. **Noise Generator.** Make as much noise as you want with this useful piece of test gear. **Bob's Mini Circuits.** Stereo Bargraph, Stereo VU Meter, Simple Fibre-optic link, Serial-Parallel converter and a Games Timer.

Order As XA27E (Maplin Magazine Volume 7 Issue 27) Price 85p NV.

SINGLE-ACTION WIRE-STRIPPERS

Extremely quick and easy to use. Just place wire in jaws and squeeze handles. Wire is neatly stripped in one simple action. Also includes tension adjustment and cutter.

NEW LOW PRICE

£2 95
FY44X



YOU CAN'T BUY CHEAPER

HELPING HANDS

Remarkably low price on this most useful piece of equipment. Two fully adjustable crocodile clips hold pcb's etc. firmly and glass magnifier allows close inspection.



SUPERB VALUE

£4 95
YK53H

Maplin

SUPPLY THE TOOLS! SO YOU CAN FINISH THE JOB WITH EASE!

☎ SALES 0702 554161

HOBBY VICE

Lever operated suction grip base holds tightly to smooth non-porous surfaces. Ideal for holding small components and assemblies. Metal faced jaws 37 x 11mm, open to 35mm. Base 60 x 60mm. Height 68mm.



UNBELIEVABLE PRICE

£1 95
YP38R

ONLY

"The finest soldering irons in the world." - Maplin recommend Antex.

Precision soldering irons that are a pleasure to use. Low leakage currents, ceramic element, shatterproof handle. It all adds up to the number one soldering equipment for the hobbyist. Use CS type for very fine work, XS for general use.



17W TYPE CS
£7 25
FY62S

25W TYPE XS
£7 45
FR12N

SOLDERING IRON STAND

Suitable for most soldering irons.

SUPER LOW PRICE

£2 95
FR20W

SOLDERING IRON KITS

CS or XS Iron complete with stand, solder and 'How To Solder' booklet

IDEAL GIFT



CS KIT
£9 95
FY68Y

XS KIT
£10 15
FY69A

ALL PRICES INCLUDE VAT. PLEASE ADD 50p TOWARDS POSTAGE. IF ORDER BELOW £5 PLEASE ADD 50p

ALL ITEMS SUBJECT TO AVAILABILITY

SOLDER by ADEPTO

INCREDIBLE LOW-PRICE TRIAL OFFER TO LAUNCH OUR NEW BRAND

½kg reel **18 swg**

£6 89
YJ92A

(=£5.99+VAT)
PER REEL

or in boxes of 20 reels (10kg)

£4 99

(=£4.34+VAT)
PER REEL
(SC20W price £99.80).



Top quality standard flux-cored solder designed for hand and machine soldering of electronic components. Manufactured to BS219 Grade KP, BS441 Grade 2 and BS5625 Class 5a. The solder is a 60% tin, 40% lead alloy containing a non-corrosive flux. Solder starts to melt at 183°C and is fully molten at 188°C. Available on ½kg reels in 0.7mm dia. (22 swg) and 1.2mm dia. (18 swg). Perfect for use with all hand soldering irons including Antex, Weller etc.

UNBEATABLE TRIAL OFFER PRICE ON ADEPTO FINE QUALITY SOLDERS.

½kg reel **22 swg**
ONLY

£7 99
FY70M

(=£6.95+VAT)
PER REEL

or in boxes of 20 reels (10kg)

£5 74

(=£4.99+VAT)
PER REEL
(SC21X price £114.80).

DESOLDER PUMP

Powerful pump action and plunger guard.

INCREDIBLE LOW PRICE

NOW ONLY

£2 95
FR26D

Maplin ELECTRONICS

P.O. Box 3, Rayleigh, Essex, SS6 8LR.

MANY MORE PRODUCTS INSIDE!

Pick up a copy of our giant 512 page catalogue from WHSMITH for just £1.60.



Shops at: Sutton New Road, Erdington, Birmingham. 0302 Gloucester Road, Bristol. 0159-161 King Street, Hammersmith, London. 08 Oxford Road, Manchester. 046-48 Bevois Valley Road, Southampton. 0282-284 London Road, Southend-on-Sea.