

**HIGHEST RADIO CIRCULATION IN THE WORLD**

# Popular Wireless

Every Thursday  
PRICE  
3d.

No. 400. Vol. XVI.

INCORPORATING "WIRELESS"

February 1st, 1930.

IN THIS ISSUE

## The "MAGIC" RADIO-GRAM



*OTHER SPECIAL ARTICLES THIS WEEK*

WHERE QUALITY GETS LOST. REACTION CHANGES  
 S.G.'s FOR ORDINARY SETS. USING METERS  
 THE LIFE STORY OF REGINALD FOORT, F.R.C.O.  
 (No. 10 of a very popular "P.W." series)

# Perfect in ALL Elements



Whatever the atmospheric conditions, the Seagull—the most versatile of birds—is perfectly at home on land, sea, and in the air. The Gull is not alone in its ability to conquer the elements, for the Lewcos "X" Coil is renowned for its capacity to separate music from adverse atmospheric conditions. When the ether is vibrant with interfering and jaming transmissions, the Lewcos "X" Coil will enable your set to clarify reception. A fully descriptive leaflet (Ref. R.34) will be sent on request—WRITE FOR IT TO-DAY.

## The LEWCOS "X" COIL

### LEWCOS LITZ WOUND TRIPLE TAPPED "X" COILS.

Nos. 60 and 250 are specified for the "Radio-Gram Magic Three," described in this issue.

#### PRICES

- Ref. X. "60-75" .. 4 9 each
- Ref. X. "200-300" .. 6 6 each

LEWCOS CENTRE TAPPED COILS and the H.F. CHOKE can also be used for this Receiver.

#### PRICES

- Centre Tapped Coils.
- Ref. C.T. "25-75" .. 3 6 each
- Ref. C.T. "200-300" .. 4 6 each
- H.F. Choke .. 7 9 each



THE LONDON ELECTRIC WIRE COMPANY AND SMITHS LIMITED.

Church Road, Leyton, London, E.10

TRADE COUNTER:


7, PLAYHOUSE YARD, GOLDEN LANE, LONDON, E.C.1.

**LEWCOS RADIO PRODUCTS FOR BETTER RECEPTION**
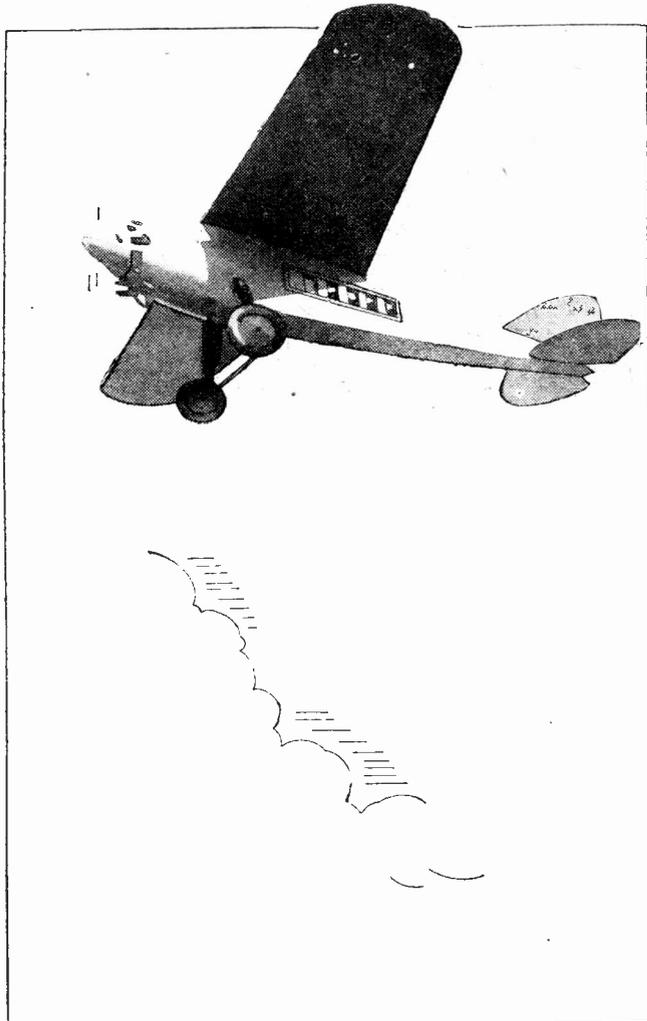
# 3 HOURS — 300 MILES!

10,000 FEET UP! Giant Air Liner roars through clouds. Airport wirelesses warning—"Fog over French Coast." Plane in constant touch — receiving orders, reporting weather conditions—*through Marconi Valves*. All Imperial Airways machines are fitted with Marconi Valves. So is Croydon Control Tower. All British Broadcasting Stations . . . all Trinity House lightships . . . all Trinity House beacon stations . . . most British passenger ships . . . use Marconi Valves. For their reliability. For their long life. For their wide range.

● *In cases like these, when unfailing efficiency is essential, men insist on Marconi Valves*



## FIT

# MARCONI VALVES

## TO YOUR RADIO SET

Give you clearer tone, greater volume, longer range. Cost not a penny more. Fit any set.



***The first and greatest name in wireless***

MARCONIPHONE COMPANY LIMITED, 210-212 Tottenham Court Road, London, W.1

# DUBILIER FOR DURABILITY




MICA CONDENSER, Type B775  
·01 4/1 ·1 8/8 ·5 37/16.  
Intermediate capacities at proportionate prices.

## PAPER CONDENSERS


Up to 1 Each  
·25 and 1/2 ... 2/1  
·4 and 3 ... 2/3  
1 0 and 5 ... 2/5  
2 0 each 3/6  
Prices of higher values on application.



Type 620

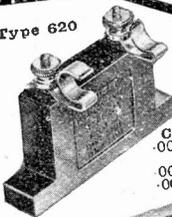

MICA CONDENSER  
·00005 to ·0009  
2/6  
·001 to ·006 3/-  
·007 to ·009 3/6

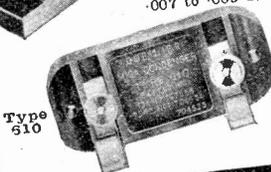

Type 510

Free for the asking—"A Bit about a Battery," There's a copy for you at your dealer's.

DUBILIER  
3/1/30

If unobtainable from your dealer, write direct to us giving his name and address.

# DUBILIER FIXED CONDENSERS

Dubilier Condensers Co. (1925) Ltd., Ducon Works, Victoria Road, North Acton, London, W.3.

Clear

BC277F

## Invaluable to EVERY Amateur and Constructor.

THE  
"POPULAR WIRELESS"

AND  
"MODERN WIRELESS"

# BLUE PRINTS

OF  
TESTED CIRCUITS

PRICE 6d. EACH

The following is a list of the 6d. Blue Prints for Constructors in stock, showing the different circuits available:

### "P.W." BLUE PRINT

Number

1. DETECTOR VALVE WITH REACTION.
2. 1-VALVE L.F. AMPLIFIER.
3. CRYSTAL DETECTOR WITH L.F. AMPLIFIER.
4. H.F. (Tuned Anode) AND CRYSTAL WITH REACTION.
5. H.F. AND CRYSTAL (Transformer Coupled, without Reaction).
6. H.F. AND CRYSTAL (Transformer Coupled, with Reaction).
7. 1-VALVE REFLEX AND CRYSTAL DETECTOR (Tuned Anode).
8. 1-VALVE REFLEX AND CRYSTAL DETECTOR (Employing H.F. Transformer, without Reaction).
9. H.F. AND DETECTOR (Tuned Anode Coupling, with Reaction on Anode).
13. 2-VALVE REFLEX (Employing Valve Detector).
16. H.F. (Tuned Anode), CRYSTAL DETECTOR AND L.F. (With Switch for Last Valve).
17. CRYSTAL DETECTOR WITH TWO L.F. AMPLIFIERS (With Switching).
18. 1-VALVE REFLEX AND CRYSTAL DETECTOR, with 1-VALVE L.F. AMPLIFIER, Controlled by Switch.
21. THE 2-VALVE LODGE "N."
22. "THE GUARANTEED REFLEX."
23. THE 1-VALVE "CHITOS."
24. THE "SPANSACE THREE." Three-Valve Receiver employing 1 Neutralised H.F. Valve, Detector with Non-Radiating Reaction Control, and 1 L.F. Valve.
26. A "STRAIGHT" 4-VALVER (H.F., Det. and 2 L.F. with Switching).
28. A "MODERN WIRELESS" 5-VALVER (H.F., Det. and 3 L.F.).
29. AN H.T. UNIT FOR DIRECT CURRENT MAINS.
30. A REINARTZ ONE-VALVER.
32. THE "CUBE SCREEN" THREE (H.F., Det. and L.F.).
33. A "KNIFE EDGE" CRYSTAL SET.
34. AN H.F. AND DETECTOR TWO-VALVER.
35. THE "UNIVERSAL THREE" (Det. and 2 L.F. stages resistance-coupled).
36. THE "SPANSACE FOUR" (H.F., Det. and 2 L.F.).
37. THE "LONG SHORT" CRYSTAL SET.
38. A TWO-VALVE L.F. AMPLIFIER.
39. THE "SYDNEY" TWO.
40. THE "SUPER SCREEN" THREE.
41. THIS YEAR'S "CHITOS" ONE-VALVER.
42. THE "Q AND A" THREE. A simple set (Det. and 2 L.F.).
43. THE "INEXPENSIVE FOUR."
44. THE "ECONOMY FIVE." For long-range loud-speaker work.
45. A SIMPLE A.C. H.T. UNIT.
46. THE "REGIONAL" THREE.
47. THE "WAVE-CHANGE" ONE.
48. THE "REGIONAL" CRYSTAL SET.

### "M.W." BLUE PRINT



Number

2. A "HIGH POWER" FIVE (A powerful and selective five-valve set incorporating two high frequency stages).
  3. THE "SWITCH-OVER" ONE-VALVER (A little set intended for use in the Regional area. Can be changed over from one station to the other without retuning).
  4. THE "TITAN" TWO (A simple and straightforward wave change Det. and L.F.).
  5. THE "FULL-TONE" TWO-STAGE AMPLIFIER (A powerful two-valve amplifier using two transformer coupled stages).
  6. A "SIMPLE CHANGE" THREE. (A simply made but highly efficient H.F., Det. and L.F. with wave-change switching).
  7. AN "EVERY PURPOSE" THREE (A powerful Det. and 2 L.F. receiver with wave-change switching).
  8. THE "SIMPLE SCREEN" FOUR (A straightforward general purpose four-valver).
- Also THE "ECKERLEY THREE" (A few blue prints of this famous circuit are available, price 1/-).


### ALL BLUE PRINTS 6d. EACH.

All orders for these Blue Prints should be sent direct to the "Popular Wireless" Queries Department, Fleetway House, Farringdon Street, London, E.C.4, enclosing a stamped addressed envelope and a postal order for 6d. for each Blue Print ordered.

**THE TRANSFORMER THAT PUT AI IN RADIO**

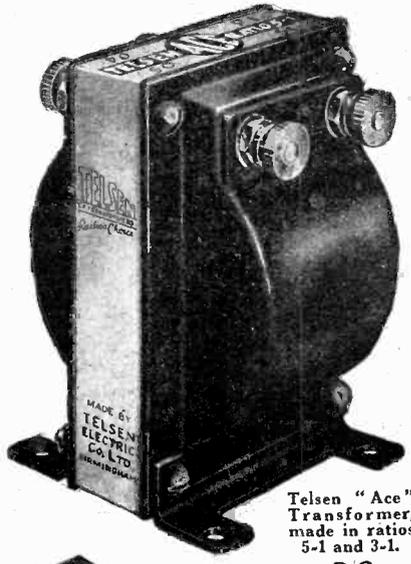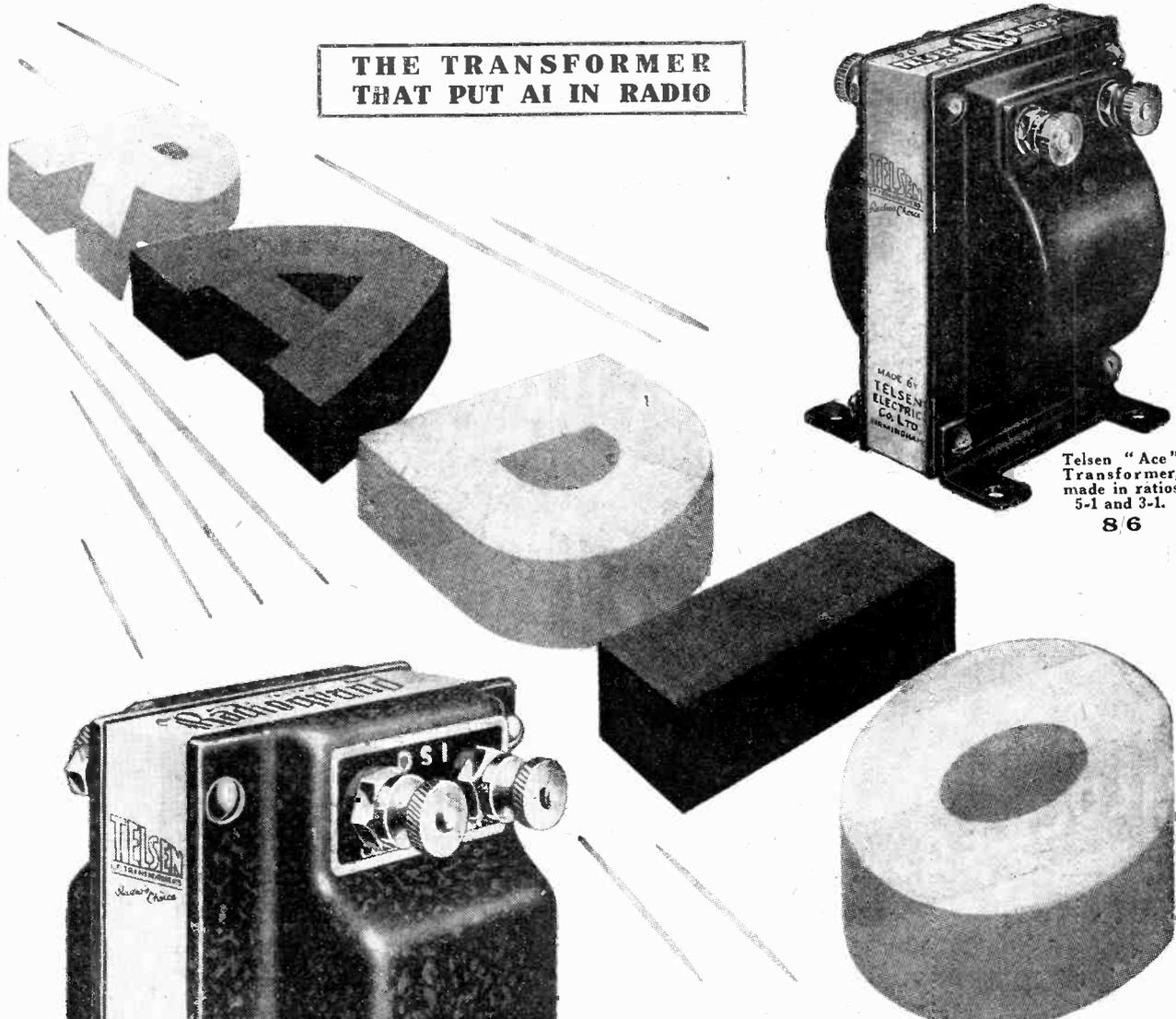

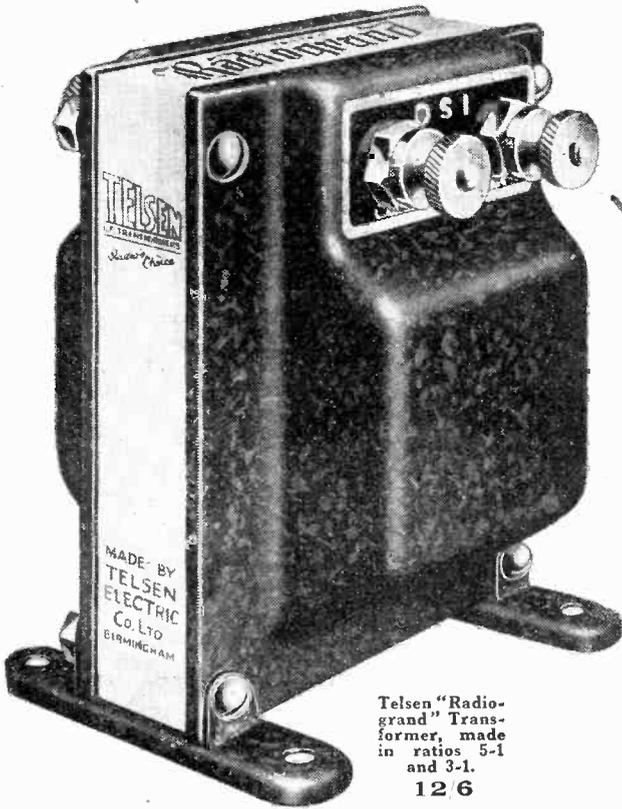Telsen "Ace" Transformer, made in ratios 5-1 and 3-1. 8/6



Telsen "Radiogrand" Transformer, made in ratios 5-1 and 3-1. 12/6

# TELSEN TRANSFORMERS

are the outcome of an endeavour to place upon the market a transformer at a strictly competitive price, yet possessing equal qualities to the most expensive instrument. The choice of experts and set manufacturers too, they can thus be accepted with confidence by all set builders.

Replace your old transformer with a Telsen "Radiogrand" or a Telsen "Ace" for Portables; they give a new life to wireless reception.

**TELSEN ELECTRIC CO., LIMITED,**  
MILLER STREET - - - BIRMINGHAM

**LOCKED for SAFETY!**

**LOCKED for RIGIDITY!**

**LOCKED for LONG LIFE!**



**T**HE *NEW* Cossor Screened Grid Valve is shock-proof, noise-proof and break-proof. Its Interlocked Construction makes it the strongest and most robust Screened Grid Valve ever produced. Its elements are immovably locked in position—vibration is impossible—all risk of microphonic noise is eliminated. And because of the girder-like rigidity of its elements the *NEW* Cossor has exceptional strength, even the hardest blow cannot mar its remarkable performance. Use the *NEW* Cossor Screened Grid in your Receiver—no other make has Interlocked Construction.

The *NEW* Cossor 220 S.G.  
(2 volts, .2 amp.) Impedance  
200,000. Amplification  
Factor 200.  
Anode Volts 22/6  
120-150. Price 22/6


Cossor 4- and 6-volt  
Screened Grid Valves are  
also obtainable from all  
Wireless Dealers.

*The* **NEW**  
**COSSOR**  
**Screened Grid**  
**Valve**
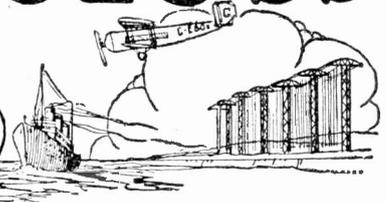
# Popular Wireless



Scientific Adviser:  
 Sir OLIVER LODGE, F.R.S.  
 Chief Radio Consultant:  
 CAPT. P. P. ECKERSLEY, M.I.E.E.  
 Editor: NORMAN EDWARDS.  
 Technical Editor: G. V. DOWDING, Assoc. I.E.E.  
 Assistant Technical Editors: K. D. ROGERS,  
 P. R. BIRD, G. P. KENDALL, B.Sc.,  
 A. JOHNSON RANDALL.



**JUST TOO BAD!**  
**"BACKWARD BRITISH"**  
**THE FOUNDLING**  
**A NEW SOCIETY**

## RADIO NOTES & NEWS

**WHEN TO RECHARGE**  
**A COLD CHESTNUT**  
**RADIO CRITICISM**  
**TEN TO ONE!**

### Impertinent Question.

ONE month gone already—and nothing marvellous happened! Just the old flux of time and weather. Well, plenty more months! Let 'em all come! Specially the warm ones, full of holidays and flowers. All of which gibbering prompts me to wonder what has happened to last year's inventions—all the "x-stoppers," "cold" valves, generators without "input," sets without aeri-als, and so on. All on the hob, warming up, and will be dished up again, no doubt.

### Just Too Bad!

A "RADIO HINTER" called "Phyvenno," who enriches a "daily" and means frightfully well, fires off two shots which I think you ought to know about. No. 1. "An indoor aerial is very seldom any good." This shot made such a bang that "Phyvenno" was scared; he reckoned that folk would contradict it, and he wished he had not put it in italics. So he shoots in the opposite direction. No. 2. "I know you will say to me, 'But I am using an indoor aerial and get wonderful results.' Yes, perhaps you are. But the wonderful results would be very much more wonderful and even more staggering to you if you put the set on an efficient outdoor aerial." And thus he balances the account and is safely back again on thick ice.

### The Backward Britisher.

MR. BRADLEY MARTIN, writing in the "New York Sun" on the subject of "A Picture of British Radio," has evidently got a hair in his brush. Here are some of the smudges which result: "The use of light sockets is out of the question." Quite wrong. "British sets employ very few valves." Has he seen the latest trade catalogues? "There are approximately 2,500,000 receiving sets in England. Of these all but a few are head sets." Yes! There's my loud speaker, and another in Manchester! And Mr. P. R. Bird is trying to save up enough to buy one, because he hears that they really do work

wonderfully! Oh, Mr. Martin! Where did you get it all?

### Radio Club Note.


SOUTH-EAST Londoners may be interested to have particulars of the Faraday Radio Club, which meets at the Walworth Men's Institute, The John Ruskin L.C.C. School, Beresford Street, S.E.5, on Thursdays from 7.45 p.m. till 10 p.m. The

at the back of another in one of those (*hem*) clips) which I have never dealt with. Verily, my name must be Mud upon the lips of Mr. W. F. Wilbee, High Street, Botley, Hants, who wishes to get into touch with E. J. (Portsmouth) who wrote to us some time ago about his "Short-Wave" Two. If E. J. should see this, I hope he will respond and so redeem my reputation.

### The Foundling.

R. S., who lives on the river bank, tells me that during a high tide the basement of his house was flooded, and that after the water had subsided he found on his doorstep a P.M.3 valve covered with mud and grease. He gave the castaway a bath and put it into service, where it "said its piece" quite well. He has since had it furnished up by its makers and now it is leading a respectable and useful life. I hope that R. S. will never have anything worse left at his door.

## OH, NO! HE'S NOT!

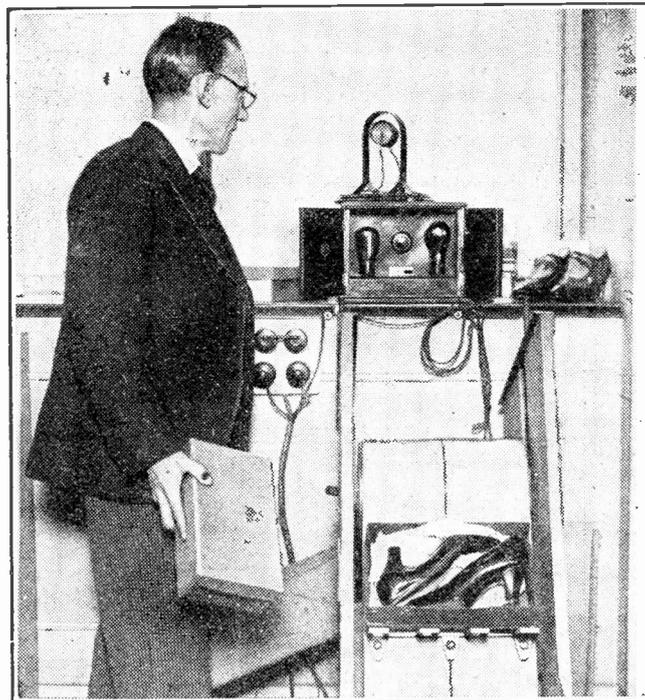

On seeing at this photograph you might think he was going to heave his H.T. battery at his set! Not a bit of it! He's a shoe salesman, and the "set" is a microphone gadget, down which he tells the stock-room all about the kind of shoe he wants. Below the "set" you will see a pair that have just arrived in response to a microphoned request.

hon. sec.—who wants more members—is Mr. J. H. Payton, 39, Penton Place, S.E.17, and the fee for the whole session is one shilling.

### Better Late Than Never.

I KNOW something of what the Post Office ought to feel like when it delivers a letter posted in 1903, for I have just found a letter dated November 3rd. (caught

### Up-to-Date Morticians.

AT a recent meeting of the New Jersey State Funeral Directors Association a resolution was introduced, recommending the establishment of a special radio programme of music for use during funeral services. Surely a somewhat grisly idea! Suppose a wedding-party tuned it in by mistake. The "Telegraph and Telephone Age" flippantly suggests the use of a portable gramophone instead, pointing out that a selection of records could be carried, "suitable to the funeral of any kind of corpse from a bootlegger to a modern saint."

### Proof of the Pudding.

OUR way of controlling and financing broadcasting seems to work about as smoothly as anything can in this wicked world, and it is financially sound at bedrock. But the U.S.A. method of "free for all," though it may suit the American listeners, does not always produce what gold-diggers call "pay dirt." In fact, the  
 (Continued on next page.)

## NOTES AND NEWS.

(Continued from previous page.)

Federal Radio Commission announces that eighty broadcasting stations report an annual loss of £2,000 or more. Well, eighty less stations over there would never even be noticed.

## Larger Hats at Tallis House.

THAT technical gang have been going about recently with an air of mystery and a sort of bloated appearance which seemed to say, "Verily, we are the people and wisdom shall die with us." Having enticed Mr. Rogers out of his vacuum with an old bicycle lamp labelled "Cold Valve," I induced him to divulge the cause of all the bursting hat-bands. It seems that the Research Department has been enlarged and that much new personnel and apparatus has been installed. I suppose it's O.K.—but I wish that poor old "Ariel" could get a little attention sometimes.

## A New Society.

ALWAYS glad to give a "leg up" to a new radio society, I do not hesitate to respond to the request of the Ebbw Vale and District Radio Society

## SHORT WAVES.

TWIN RADIO PROGRAMMES—Likely to prove a howling success.—"Daily Mirror."

## NEED ANY ASSISTANTS?

Wife (awakening her husband). "The early morning radio setting-up exercises are on. You left the radio turned on when you went to bed."

Tired DX Fan (after a hard night): "Please be quiet. I'm doing my daily dozin'."—"Radio News."

"When valves fall sick" runs a headline in the "Leeds Mercury."

Well, who wouldn't?—with all these talks about Economic Potatoes, and so on.

## UNDOUBTEDLY!

We received a letter from a reader the other day, who wrote as follows: "I know my batteries are O.K. as I do not use them, since I run my set from the mains."

It is reported that burglars recently made a big haul of wireless components in a London suburb.

Let's hope this will be a lesson to them.

Mrs. Bangs (confidentially): "Yes, we bought this radio set on instalments last winter."

Mrs. Bings (with some curiosity): "I suppose you've nearly paid for it, then?"

Mrs. Bangs (hesitatingly): "Well, about as far as the second valve."—"Radio News."

"Have you an old set 'parked' away?" we read in the "Bristol Times."

No, but if we had our way we should have—several.

It is said that broadcasting has shortened the lives of several popular songs.

That's one feather in its cap, anyway.

that I mention its advent. It meets on Thursdays at 7.30 p.m. in the Lesser Workman's Hall, Ebbw Vale, and its hon. sec. is Mr. G. R. Scott Farnie, Lloyds Bank House, Ebbw Vale, Mon. I have reason to believe that the society is making great use of "Pentode's" articles. Good luck to them!

## Short-Wave Query Answered.

W.L.S.'s query as to the identity of W2XBH, which works on a wave-length of about 60 metres, has been answered by F. T. C. (Streatham). The

owner of the station is C. G. Unger, 183, Vermont St., Brooklyn, New York. We are much obliged to F. T. C. for his trouble and in future we'll look more carefully in the Radio Amateur Call Book. Can he tell us anything about Turin's nightingale?

## When to Re-Charge.

MY remarks under this heading on January 11th moves "Scot" (Clydebank) to ask how my method of telling whether the L.T. battery needs recharging would work if the set were not filament-controlled. Pretty feebly, I should say! If I had such a set I should use the voltmeter in preference to calculations, or a hydrometer, even though the drop in the discharge curve of an ordinary accumulator is fairly swift. "When this notice is covered by the water it is unsafe to pass across the river," said the signboard. "Yes," said the Scot, "but suppose a monkey can't read!"

## Cold Chestnut.

A GREEK and an Egyptian were boasting about the wisdom of their ancestors. "Why," said the Greek, "during recent excavations in Athens they found copper wires thirty feet below the surface. That proves that the ancient Greeks had telegraphs." "Pooh!" replied the Egyptian. "Why, in digging near Alexandria they found absolutely nothing at a depth of sixty feet. Don't that prove that the ancient Egyptians had wireless?"

## Anti-Noise Invention?

REPORT hath it that Dr. James Robinson, the inventor of the Radiostat, has hit upon a means of rendering rooms sound-proof. Apart from the desirability of such an invention in these days of "Oh, that next-door's radio," the blessings of a still house or office would be tremendous, and I hope that Dr. Robinson will give the Radiostat second place. By the way, a company for the development of the Radiostat has been formed in Canada.

## New Radio Society.

MY attention has been directed to the newly-formed "Ministry of Pensions Radio Society," one of the few societies I have heard of in connection with a Service Department, though probably plenty exist. I understand that the membership is large and enthusiastic, besides being a supporter of "P.W.," which hereby sends the boys its best wishes. Will they let "Ariel" have a list of any "remainders" or "throw-outs" which the Department may have for disposal on easy terms; secondhand pensions not objected to.

## The Great Conversion.

FURTHER evidence that America is softening! First we hear of a company formed for the purpose of ousting jazz, and now here is actually a member of the Federal Radio Commission pleading for the "old songs of country, home, love and romance." (*Loud sobs from the Wall Street gentleman on the right.*) Nay, more! He begs broadcasters not to encourage American boys and girls to smoke cigarettes. Yep! Export those "Camels" and "Lucky Strikes" to European kids. Finally, he pleads that the farmer shall be immune from the perils of jazz. I am glad he did not have to ask for jazz to be eliminated from church music!

## CHEER UP!

Radio needn't be dull. There's no reason why high spirits shouldn't go with the highest technical qualifications. Look at

Capt. P. P. ECKERSLEY, M.I.E.E.

—the man who engineered the B.B.C. from a name into a national service that's a credit to Britain. And remember—he

Writes Exclusively for "P.W."

## Buried Aerials.

W. J. C. (Ventnor, I. of W.), in a letter as pleasant as the lovely island of Vectis, tells me that sets for use in connection with buried aerials are shortly to be placed on the market. This is excellent news for my pup, who fancies himself as a resurrectionist and is already in training. His ambition is to bring up the main sewer, I think. Meantime, one waits.

## And Yet Another Road.

BUT the B.B.C. certainly does provide unknown geniuses with a chance of obtaining public recognition before they are dead, though up to the present no startling discovery has been made—probably because the geniuses are "faddy" and won't broadcast or be broadcast. So the works of dead geniuses continue to be the backbone of the programmes. Talking of music—which I wasn't—will someone kindly tell me what is wrong with my ears? A Stravinsky record got into my house by mistake and was clapped on to the grammy. I had a bad time trying to convince the kids that grammy really was not running backwards.

## Radio Criticism.


RADIO "critics" of professional type are springing up like objectors at a City meeting, and there is in progress quite an amusing competition for pride of place on the scroll of priority in this kind of work. Some of the commentators, being men of ripe experience, unerring good taste, and with a knowledge of the proper functions of a critic, make very good reading; but I notice that much of the so-called criticism is simply a catalogue of the items, arranged under two heads, viz. what the "critic" liked and disliked. We want less references to "I." At random I pick the following specimen of acute criticism: "The Mendelssohn programme was welcome, not forgetting the ever-sweet 'A Midsummer Night's Dream.' *We don't hear this often.*" (My italics).

## Ten to One.

IS it not surprising that in Italy, where the regime is so strict, the "pirates" outnumber the payers by ten to one? According to the "Popolo D'Italia," Milan, there are a million radio receivers working in Italy and one hundred thousand people have paid the licence fee. Evidently there is a chink in the Dictator's armour!

ARIEL.

# WHERE QUALITY GETS LOST

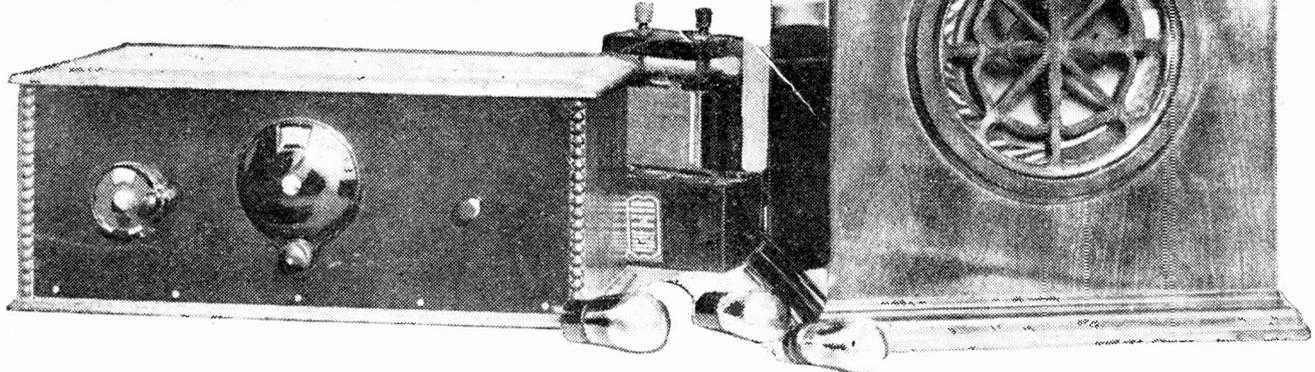

Is your set a sieve? Does it leak notes in every stage, so that you get a mere travesty of the original input by the time it arrives at the loud speaker? You may not realize it, but there are very few sets which can claim to be "note-tight," and to give out in amplified state exactly what is put into them. This article shows the main "holes" through which notes escape on their way through a typical broadcast receiver.

By C. E. FIELD, B.Sc.

THERE must be a very large number of wireless enthusiasts who have purchased loud speakers as a result of a demonstration of excellent reproduction (perhaps at the last Radio Exhibition), but are unable to obtain the same results when

very low or very high notes. This gives rise to distorted speech and music, which differs according to whether it is high or low notes which are suffering from lack of amplification.

We may make a good guess as to what is

wrong with our reproduction, if we know that the speaker is a good one, and that the set is not over-running, for if the results sound high-pitched and "thin," the probability is that the low notes are not being reproduced at full strength, while a muffled, booming tone would indicate that the highest notes were weak or absent.

An absence of high notes is particularly noticeable in the reproduction of speech, for without them sounds such as *s*, *z*, and *th* are almost entirely absent—an effect which is responsible for most of the lack of distinctness in talking-picture reproduction. The characteristic stringy tone of a violin is also lost when high notes are not faithfully reproduced.

An absence of the low notes produces the nasal "gramophony" tone with which we were all too familiar a few years ago (but which is certainly not a feature of a modern gramophone), and gives a twangy quality to a piano, and a metallic note to drums.


## Where the Low Notes Go.

Now, where do these notes get lost?

We will take as examples two or three typical circuits and endeavour to obtain a sort of bird's eye view of what happens to notes on their way through the receiver from the aerial to the loud-speaker.

Look, for instance, at Fig. 1. Here is shown, in simplified form, for reception from a local station a loud-speaker circuit consisting of a detector, low-frequency amplifier, and power valve, transformer-coupled throughout, the output of the last valve being choke-coupled to the speaker.

(Continued on next page.)

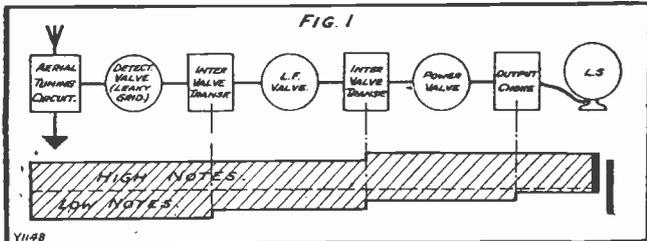

Here is shown an ordinary old-fashioned detector and 2 L.F. transformer-coupled set, which, as you see, has a rooted objection to low notes, and believes the piccolo is the only instrument worth hearing.

they try their newly-acquired speakers on their own sets.

Why is this?

It is almost certainly because their sets are at fault, but there is no reason why every owner of a loud speaker should not be able to do it justice.

As readers are probably all aware, distorted results from a receiving set may be produced by *overloading* (usually the result of employing too small a valve in the last stage, or too little high-tension voltage), or by the *unequal amplification of different notes*.

## High or Low Pitched.

The first form of distortion will not occur providing that the correct types of valves are used, and that the correct high-tension and grid-bias voltages are applied.


The second form, however, is not so easily dismissed.

By the unequal amplification of different notes, we mean, in general, the reproduction of notes round about the middle of the piano-forte range at much greater strength than

The diagnosis of the cause of unnatural reproduction is not quite so straight-

forward as this, for it must be remembered that an absence of "booniness" in results which are not unnaturally high-pitched does not necessarily mean good reproduction, but may, and very often does, indicate an absence of both high and low notes.

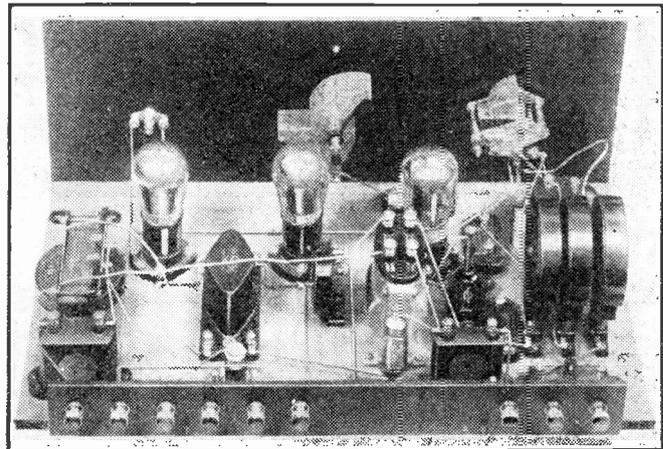Here it should be pointed out that the term "high notes" includes notes which are well above the ordinary musical range, but which are present as part of lower notes, forming what are known as "overtones."



Unless special precautions are taken, as in the case of the "Magic" Three, two transformer-coupled stages may prove very unsatisfactory from the point of view of quality.

## WHERE QUALITY GET'S LOST.

(Continued from previous page.)

Beneath the diagram you will see a chart consisting of two lines with a shaded portion between them.

The distance between these lines represents the range of notes reproduced by the set, a rise in the bottom line indicating a weakening of low notes at that point in the set, and a fall in the top line showing a cutting-off of high notes.

Following the signals through the circuit we see that all goes well until we come to the first intervalve transformer, when there is a weakening of low notes.

### Almost Inevitable.

This is an almost inevitable result of transformer coupling, but with a well-designed modern transformer the effect may be quite negligible. A poor transformer, however, such as has been assumed in this circuit, may completely spoil otherwise good reception.

Many transformers give a little extra amplification to high notes—a feature which is usually advantageous, though not generally very noticeable.

This is assumed to have taken place in the second transformer, in Fig. 1, in addition to a further reduction of low notes. The weakening of low notes is produced when the primary winding of the transformer possesses only a low inductance, i.e. is wound with comparatively few turns of wire, and as transformer wire is very costly, this is usually the way in which the price of a transformer is reduced.

Thus often a cheap transformer will result in high-pitched reproduction.

Returning now to the circuit, we see that after passing the last valve our signals suffer yet another weakening of low notes in the output choke, the cause being exactly the same as in the case of the transformer—too few turns of wire on the winding.

### Nasal Speech Quality.

It is obvious that the final results from this receiver would be very seriously lacking in bass notes, and the effect would be made slightly worse by the extra assistance given to high notes by the second transformer.

Speech from this receiver would be very clear and articulate, but would possess a harsh, nasal quality. Orchestral music would lack body, and the piano and the drums would sound tinny.

In Fig. 2 is shown another circuit. This time the constructor, with the best of intentions has discarded transformers, and

employed resistance-coupling with high-amplification valves. Otherwise the circuit is similar to that shown in Fig. 1.

From the chart below the circuit diagram we see exactly the opposite effect to that obtained in the first circuit. There is a drop in the amplification of high notes at each resistance-capacity coupling.

A good output choke has been assumed, so that low notes are reproduced faithfully throughout.

Speech from the set would be low-pitched, possibly boomy, and would sound "woolly," as if the speaker had a sack tied over his head, while orchestral music would tend to resemble that from a military band on account of the faulty reproduction of stringed instruments.


The reason for this high-note loss is to be found in the very high values of anode resistance and grid leak employed. If, in each case, these two resistances had been 100,000 ohms and 2 megohms respectively, results would have been excellent.

The circuit shown in Fig. 3 is supposed to be constructed for the reception of a few

give the necessary signal strength for loud-speaker operation.

He has employed a really good output choke and intervalve transformer in order to ensure the reproduction of low notes. When we look at the chart, however, we see that first of all the high notes are considerably weakened before the first valve.

This is an effect which is produced when

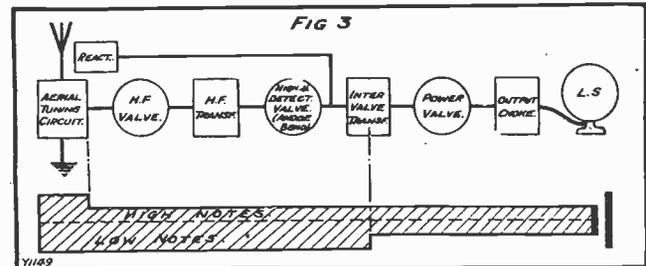

Obtaining better balance. This transformer-coupled set has a better sense of proportion, and although some high and low notes are lost it reproduces the rest of the notes of the musical scale more nearly in their correct relative values.

tuning is made excessively sharp by means of reaction, and can, of course, be avoided by keeping the reaction coupling to a minimum. Whether the required degree of selectivity can be obtained depends, of course, upon the situation of the set with regard to powerful local stations.

Passing on through the receiver we find that, in spite of the fact that a good intervalve transformer is employed, there is at this point a loss of low notes.


### Anode Bend.

The cause of this is the fact that anode-bend rectification by means of a high-impedance valve has been used, for no transformer will give good results when preceded by a valve having a working impedance (as this one might have) of perhaps 60,000 ohms.

Good results would have been obtained if a general-purpose, or low-frequency amplifying valve had been

employed as a leaky grid detector, or if a low-impedance valve specially designed for an anode-bend detector had been used.

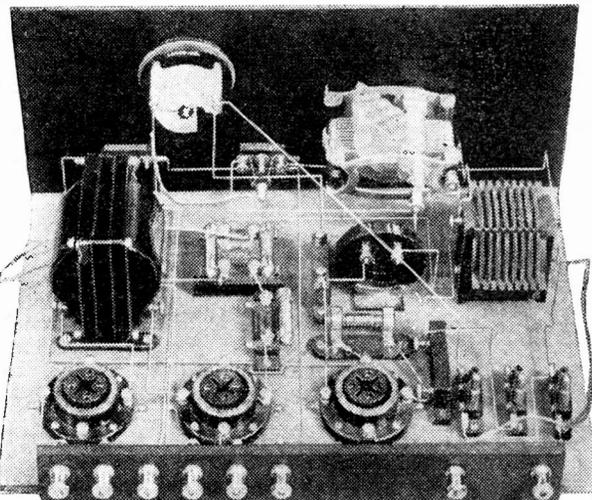These examples may serve to show how easy it is to spoil otherwise good reproduction by a careless selection of components, and in conclusion it may be restated that it is within the power of every amateur to construct a set which will do justice to any loud speaker.




A well-designed set, having resistance and transformer coupling, which is scientifically designed will give quite a good response curve.

Continental stations, or for the cutting-out of a powerful local station.
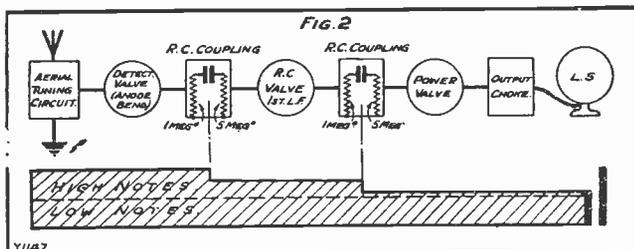
### Where the Set Fails.

It consists of a high-frequency valve, detector, and power-valve, reaction being employed to provide selectivity. The constructor has argued, we will suppose, that, since he is employing a high-frequency stage, the signals received by the detector will be strong enough to allow him to use anode-bend rectification, while as he is not employing an intermediate stage between the detector and the power-valve, a transformer should be employed, rather than resistance coupling, to



"Good stuff this bass" is the slogan of this set, which has no time for any form of high-note instrument, and turns a deaf ear to the harmonics of the piano, violin, flute, etc.


## FOR YOUR NOTEBOOK.

\* \* \*

It is often a good plan to connect the mounting of an electrical pick-up to earth.

\* \* \*

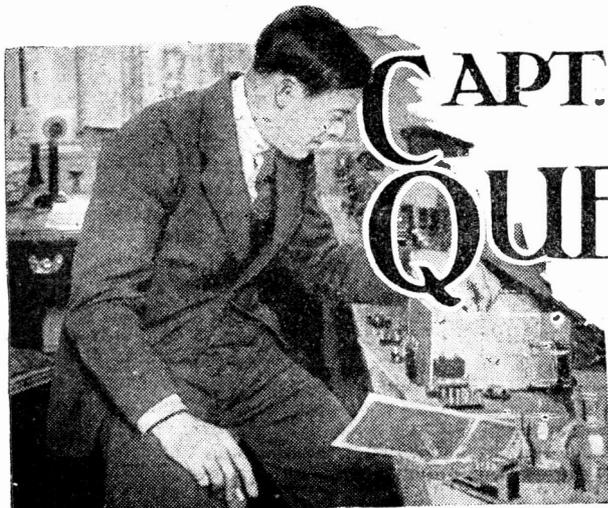Bell wire or fairly stout insulated D.C.C. wire such as No. 22 gauge, is more suitable for long loud-speaker leads than the flex which is so frequently used.



# CAPT ECKERSLEY'S QUERY CORNER

Under the above title, week by week, Captain P. P. Eckersley, M.I.E.E., late Chief Engineer of the B.B.C., and now our Chief Radio Consultant, will comment upon radio queries submitted by "P.W." readers. But don't address your queries to Captain Eckersley—a selection of those coming to the Query Department in the ordinary way will be dealt with by him.

### M.C. Loud-Speaker Limits.

P. D. (West Drayton).—"Is there any limit (apart from the current-carrying capacity of the wire in the pot) to the sensitivity which can be obtained in a moving-coil loud speaker by increasing the strength of the field?"

No! I suppose there's no limit to the field you could get if the wire could carry the current.

But, of course, in practice, the limit is the heating of the wire.

### "Heterodyning Orchestras."

P. S. (Davenport).—"If two orchestras were to play together in one room, the result, while perhaps unpleasant, would not be distorted, nor would the music be accompanied by a high-pitched whistle.

"Why then should signals be distorted, or heterodyned as it is called, when two neighbouring radio stations transmit items, for surely this amounts to the same thing, except for the radio link?"

What do you mean by distorted? With wireless, and if two stations are too close together, then the upper frequencies of one get muddled with the upper frequencies of the other and produce more frequencies. This produces a nasty noise, and people call it distortion.

It would be just the same listening to one of these stations as if you had one orchestra going while the upper wind, strings, piccolos, etc., of another orchestra were played (playing a different tune) on top of the orchestra you wanted to hear.

Just the same you would get a horrid noise, and if you call it distortion it is distortion. If you call it anything it's the same in both cases!

### Why Foreigners Fade.

L. W. (Ipswich).—"Is there any theory explaining the reason for distant stations fading?"

Yes, rather—but do you want me to do it all again? All right!

Above the earth there's a layer of charged particles which acts as a reflector to wireless waves. The transmitting aerial sends out rays parallel and rays at an angle to the earth's surface.

The ray parallel which does not fade is the one you get from your local station. The rays shooting upwards hit the electrical layer and are bent down to earth to come in at distant stations.

But the reflecting power of the layer varies, and is sometimes good, sometimes poor, and so the down-coming ray is weaker and stronger, depending on how the layer's feeling about it! Hence fading.

In broadcast waves the layer is ineffective in day-time, and so one gets better—albeit fading—signals at night. See the B.B.C. handbook, which has a very good article on the subject—I wrote it!

### Wave-length and Service Area.

N. C. M. (Harrow).—"Why is the 'service' area of a long-wave broadcasting

But the earth has a finite conductivity, and energy is lost by its effect and things on the earth, houses, hills, trees, mountains, etc., etc., so that the waves may be of strength 1 at 10 miles,  $\frac{1}{2}$  at 20,  $\frac{1}{4}$  at 40, and so on.

If the wave-length is made shorter and shorter the losses in the earth are greater and greater, and so a wave dies away not only more quickly than by the inverse distance law but more quickly as it is shorter. So the service area of long-wave stations is greater.

### The Effects of Rain.

P. T. S. (Manchester).—"Does rain affect reception?"

Yes, with an outdoor aerial, and in Manchester especially, because it deposits soot on the insulators.

Some rain is charged with electricity, too, and makes crackles when it falls on a bare aerial, but this is rare. Rain on a dry earth improves things, but, in general, rain does not (except indirectly and after a long time) affect reception.

### Copper or Iron for the Aerial Wire?


P. T. (Norwich).—"Is it essential to use stranded copper wire for an aerial? I have a quantity of galvanised iron wire. Would there be any objection to my using this?"

Stranded copper wire is useful for acrials because it will stand a lot of swaying about in the wind without mechanical breakage.

Galvanised iron wire would not only be liable to chafe, get hard-drawn, and break if used out-of-doors, but wherever it is used would be electrically less efficient than copper wire, because of its much higher electrical resistance.

When uncoiling the new wire, keep it free from kinks if you can. Use stranded copper or phosphor-bronze wire for an outdoor aerial, make it all up ship-shape, and don't bother about it any more in spite of the gales!

## DON'T KILL THAT COIL!

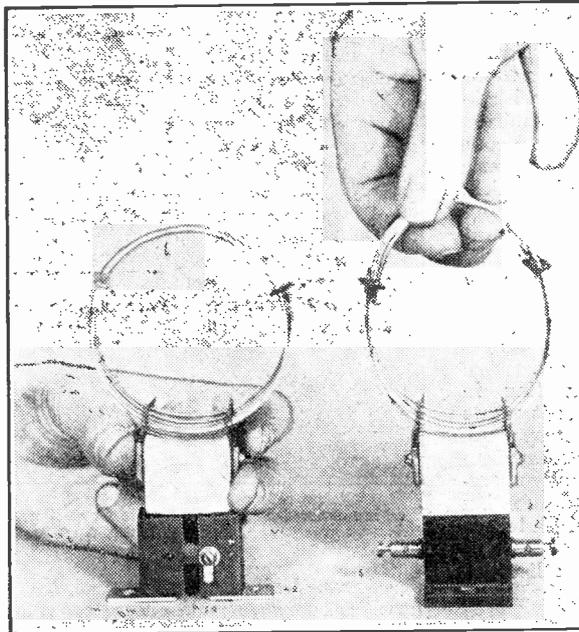

Attention! There is a right and a wrong way of pulling out a coil. ON THE RIGHT—WRONG! ON THE LEFT—RIGHT! You can't expect a coil to "keep in shape" unless you put the pressure on the holder, and not on the wire.

station greater than that of a low-wave station using the same power?"

Any wave travelling over the surface of the earth gets feebler and feebler as it travels away from the station. Its rate of decay, if the earth had a very large effective conductivity, would be simply according to inverse distance—i.e. if the strength was 1 at 10 miles it would be  $\frac{1}{2}$  at 20,  $\frac{1}{4}$  at 40, and so on.

# WHAT THE PUBLIC WANTS.

A trenchant article discussing the policy of the B.B.C.

By THE EDITOR.

THE question of "what the public wants" is one which will always exercise the minds of those who have to cater for the public, whether it be in connection with newspapers, books, theatres, food, or broadcasting. There is one school of thought which has for its slogan: "Give the public what it wants," and there is another school of thought which has for its slogan: "Give the public what's best for it."

## The American Way.

The former slogan is chiefly in evidence in the United States, where everything possible is done to pander to the taste of the public. Especially is this noticeable in American ideas of theatrical entertainment. But while, on the one hand, it would not be an exaggeration to say that American business men who cater for a public which patronise cinemas, theatres and newspapers, provide—on the average—entertainment which does not primarily aim at improving public taste, either by forceful or persuasive measures, there are other organisations in America which doggedly persist in endeavouring, if not by persuasive, then by forceful measures, to make the American public take something which it doesn't want.

Uplift societies are admittedly more numerous in America than they are in Great Britain; and although we have no wish to be unduly controversial, it is an admitted fact that Prohibition was brought about in the United States by the energetic propagandist methods of a minority which, because of its very methods, eventually brought about probably one of the most amazing pieces of legislature which the world has ever known. Hundreds of thousands of people—in fact, millions would not be an exaggeration—were made to tolerate—or, at least, to put up with—something which they did not want.

In connection with broadcasting in America, giving the public what it wants is a policy which has pretty full sway; and, consequently, observant critics of American broadcasting methods are practically unanimous in saying that American broadcasting is not on such a high level as British broadcasting. Whether American broadcasting is more popular with American listeners than British broadcasting is with British listeners is a moot point.

## Sir John Reith's View.

The above views have occurred to us after reading an article by Sir John Reith, the Director-General of the B.B.C., on "The Business Management of Public Services," which he wrote recently for the journal of the Institute of Public Administration. In the course of his article, Sir John deals with the policy which he admits has caused a good deal of friction with the listening public; in short, the policy of giving the public not what it wants, but what it should have.

"To set out to give the public what it wants," writes Sir John, "is a dangerous and fallacious policy, involving almost always an under-estimate of the public's intelligence and a continual lowering of standards."

Sir John frankly expresses his preference for the monopoly system in British broadcasting, though he is careful to add "subject to certain safeguards in the public interest."

"In some cases," he states, "it is essential; in others, at least highly desirable. Its absence is often unfortunate and even

or, at any rate, it is so to the right kind of people.

Sir John considers that, paradoxically enough, the policy of giving the public what it wants, although a dangerous and fallacious policy (involving, as we have already stated, an under-estimate of the public's intelligence and a continual lowering of standards) turns out to be not the monopolistic system but the competitive system that is obliged to play for safety.

## A Wise Policy.

It is not insistent autocracy (says Sir John), but wisdom that suggests the policy of prosecuting carefully and persistently a basis of giving people what you believe they should like and will come to like, granting, of course, discretion and understanding on the part of those who carry out the policy.

As our readers know, that has been Sir John Reith's policy ever since the early days of broadcasting. It would have been easy enough to have given way to all the critics of broadcasting and to have followed

the line of least resistance by giving the public what it wants. Undoubtedly, by not following that line, the B.B.C. has incurred at times storms of displeasure and disapproval, but after a period of years we can sit back and take stock of the situation and, with some pride, realise that the policy of not kow-towing to the public has been, on the whole, justified.

## The Best.

Mr. Aylesworth, the President of the National Broadcasting Company of America, himself admitted that British broadcasting methods were superior in many ways to American ones. From a progressive standpoint at any rate, and certainly from an educational standpoint, British programmes are probably the best in the world.

What is the alternative? Giving the public what it wants! But how can we ascertain definitely

what the public really wants?

The only way is by noting whether the patronage of the public increases or decreases; and the evidence points indubitably to the fact that, year by year, the listening public grows; that, on the whole, it does like what the B.B.C. provides in the way of entertainment, education, etc., and that Sir John Reith's policy, although tinged with that *bele noir* of every Britisher, autocracy, is nevertheless one which, in practice, has certainly turned out to be reasonably satisfactory and definitely better than the American policy of pandering indiscriminately to a noisy public minority.

## COLD COMFORT?



This wireless set was taken by the Hon. Mrs. Victor Bruce to accompany her on her motor-dash from Lapland to Monte Carlo. She is here shown warmly clad for the first stages of the run.


disastrous. Unified central control, if it be absolute enough, should ensure concentration and preservation of effort, and the most economic administration. It should, in fact, imply and supply the highest degree of efficiency in every sense of the term."

Sir John draws as an example the fact that one hears a good deal that is absurd about the advantages of competition as a stimulus to effort. Some advantages of competition are obvious and, in his view, much more so are its disadvantages in waste, undercutting and overbidding. There are other forms of stimulus which bear heavily upon the monopolist. The very fact of monopoly is a stimulus, believes Sir John,

# LIFE STORIES OF FAMOUS BROADCAST STARS N° 10

## TRYING TO SUIT BOTH THE EAR AND THE EYE

By REGINALD FOORT

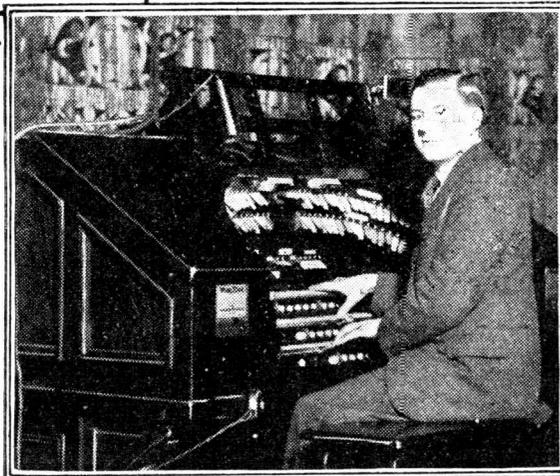

MANY wireless listeners seem to think that learning to play the cinema organ has taken me years. In reality, it took me only a day, or rather, a night.

Before I turned to the cinema, I had for many years played the organ in a London church. Then, after a time, I tired of the routine and monotony of this, and looked round for fresh fields to conquer.

A friend suggested the cinema organ, I made a few enquiries, and was eventually engaged to play at the opening of a new cinema in the North.

I arrived at the hall four days before the public were to be admitted, and found to my astonishment that the organ had not yet been erected.

### The First Experience.

It was not ready for me to play upon it until twenty-four hours before the performance, and then I sat down to master what was to me an entirely new instrument as speedily as I could.

On the opening night I was able to play perfectly. Within nine weeks they transferred me to the West End of London.

My previous organ experience had stood me in good stead, but I think it was my being a pianist as well that counted in the end, for the American cinema organ as little resembles its church sister as a trumpet does a saxophone.

I had studied under a pupil of Paderewski, and for some time had made my living by playing at concerts and by teaching. Then, finding piano playing not very lucrative, I thought I would try the organ.

My present work is truly fascinating, and especially so when I am aware that the "mike" overhead is alive and listening.

### Realistic Railway Effects.

Playing for the wireless makes one feel a superman. Not only is there the knowledge of an incredibly vast audience, but even the organ makes one feel rather regal.

I sit at a console that has hundreds of stop keys arranged in a semi-circle above the four manuals or key-boards, played by the hands and feet.

We have all seen a cat playing the piano by walking up and down; I do very much the same thing, although not so discordantly.

Wonderful though the console is, with its pistons, gauges, stops and electric lights, it is but a very small part of the organ's entire mechanism.

Hidden behind the grilles the audience sees and listeners imagine, are numbers of large chambers packed with pipes, bellows,

a motor, a blower, and action parts of every description.

The organist controls all these in effect, and the effects and music as well. With various keys and stops, I am able to imitate steamboat whistles, surf, wind, rain, thunder, aeroplanes, motors, horses hooves, fire bells, telephone bells, klaxon horns, pistol shots, crockery smashing, birds, and practically every other outstanding sound of the world.

A short time ago, I discovered a new way of imitating the sound of an express train leaving a station, and it must have been good, for when I gave it for the first time the

In this notable contribution to a very popular "P.W." series, the well-known cinema organist, Mr. Reginald Foort, F.R.C.O., describes the incidents that led to his being heard by millions of listeners, and some of his experiences as an "outside broadcaster."

audience burst into a salvo of applause, and the next day several letters of praise were forwarded from Savoy Hill.

Again, with the organ, one is able to play anything from an overture to a fox trot with a freedom and completeness unknown to any other solo musician. I can play from memory or improvise as I please.

But, as I have already indicated, my greatest pleasure lies in playing to a wire-



Mr. Reginald Foort.

less audience. when I forget those in the cinema and play to the unseen ones alone. Incidentally, preparing my broadcast programmes is my most difficult job. I am now beginning to get accustomed to it, but in my early days, when I was

the first and only organist to broadcast, the strain was terrible.

The music played in the cinema must fit the picture, and the advent of the talkies

has in no way altered my own personal position.

A death scene demands a sad tune, a ballroom scene a foxtrot, and so on. In the ordinary way, cinema music is made up from little snips of hundreds of pieces, but for the wireless audience this would never do.

### Time and the Pictures.

A listener cannot see the picture: he wants to hear a piece of music right through. And searching for material that will suit the picture when played at length is a nerve-racking task.

As a rule, I succeed. Only on two occasions can I remember anything going wrong.

When "La Bohème" was being shown, I found that the Overture to "William Tell" exactly fitted some of the scenes, so I included the piece in my programme.

Unfortunately, at the time of my broadcast, the film was either running too fast, or had started a minute too late—it was out of place.

I was just in the middle of the tempestuous finale when I glanced at the screen. I have never felt so foolish in all my life. I was playing that uproarious music as an accompaniment to the death scene!

### Buster Keaton and "Carmen"!

One evening, in order that the main film in the cinema should not be spoilt by the accompaniment, it was arranged that two interest pictures—whose allied music did not matter so much—should be shown, and the main picture, a Buster Keaton comedy, kept until after the broadcast.

Unfortunately, on the day of this particular relay, the management decided to have four programmes instead of three, and so, to make the programmes shorter, the interest pictures were cut out, and my musical arrangement ruined.

The programmes having been published, the B.B.C. refused to allow any alterations. I could do nothing but carry on, and so listeners heard nothing of that broadcast save laughter. But it was more at me than at the film.

While Buster Keaton was falling off trains and generally fooling about, I was playing the "Flower Song" from "Carmen!"

## LATEST BROADCASTING NEWS.

REGIONAL SCHEME  
PROGRESS.

**AN ARCHBISHOP'S POINT OF VIEW—BIRMINGHAM FEATURES—DIGNITY IN THE CHILDREN'S HOUR—LANCASHIRE COTTON FAIR—A PRACTICAL TALK.**

It is understood that the full alternative programme service will begin from Brookmans Park in the second week of March. At the same time 5 G B will drop its title of Daventry Experimental, and assume that of Midlands Transmitter.

Negotiations between the B.B.C. and Birmingham civic authorities about the orchestra are still going on. The general position in the Midlands is also claiming special B.B.C. attention. It is reported that Mr. Gladstone Murray, the Information chief at Savoy Hill, has recently visited Birmingham, Nottingham, Leicester, Wolverhampton, Shrewsbury, Coventry and Leamington.

**An Archbishop's Point of View.**

The Archbishop of York is to open a new series of "Points of View" talks in the London studio on Monday, February 10th. He will be followed a week later by Lord Grey of Falloden. Another notable speaker is coming to the microphone on Sunday, February 9th, in the person of Mr. Frank Hodges, M.P., who is to make an appeal to Welsh listeners on behalf of the Aber-tillery and District Hospital.

**Birmingham Features.**

An important musical programme will be performed for 5 G B listeners in the Birmingham Studio on Sunday evening, February 9th, when a performance of Berlioz's Oratorio "The Childhood of Christ," will be given by the Studio Chorus and Symphony Orchestra, under the direction of Joseph Lewis, with Kate Winter (soprano), Eric Greene (tenor), Robert Maitland (baritone), Joseph Farrington (bass) taking the solo parts.

This work, which was first broadcast about two years ago, is rarely presented to the public. It is an expansion from a shorter work known as "The Flight into Egypt" which was originally a complete work, but now forms the second part of the whole work which has been arranged as a trilogy.

Another musical event in the same week worthy of mention is a symphony concert to be relayed from the Town Hall, Birmingham, on Thursday, February 13th, when Dr. Adrian Boult will be the conductor. The programme includes the overture to Mozart's opera, "The Magic Flute" and Gustav Mahler's "Song of the Earth." The soloists will be Astra Desmond and Stuart Wilson (tenor).

**Dignity in the Children's Hour.**

For some reason or another the happy and successful little functions arranged by those who run the Children's Hour at the

various stations of the B.B.C. to mark important occasions such as Christmas, the anniversary of the opening of stations, etc., have been discontinued, without enhancing the dignity of the officials whom the children were so proud to meet on those occasions.

It has been left to Scotland to reintroduce these children's parties for members of their Radio Circles, and one has already taken place in the Cowdray Hall, Aberdeen: Glasgow's Radio Circle is giving a party in the Albert Palais de Danse on Saturday, February 15th; while Edinburgh has planned theirs to come off at the Albyn Rooms in March.

**Lancashire Cotton Fair.**

From the earliest days the B.B.C. has consistently displayed a desire to help any cause which has for its object the advancement of national progress.

Such an example is the Lancashire Cotton Fair, which is to be opened in the City Hall, Manchester, on Tuesday, February 11th, when, and during the following three

weeks, attention will be drawn to the activities of one of the principal industries not only in the north, but of the whole country.

The fair has been arranged by a committee representative of all sections of the industry—including mill-owners and trade union representatives—whose prosperity affects the wellbeing of such important centres as Oldham, Bury, Blackburn, Preston, Bolton, Rochdale and Burnley, to mention but a few of the chief towns around which the cotton mills of Lancashire are clustered.

The opening speeches of the Fair, on Tuesday, February 11th, will be broadcast throughout the Northern Region, and also from 5 G B, and further attention will be called to it by the inclusion of several evening talks and special programmes which are to be broadcast during the first week of the event.

One such special programme includes a play entitled "Progress and the Builder," which depicts the work of Samuel Crompton, whose name is famous for the improve-


ments which he devised to the spinning jenny which brought so much prosperity to Lancashire.

**A Practical Talk.**

A good deal of importance is attached in certain quarters to a talk to be broadcast from the London studio on Thursday morning, February 13th, on the subject of bread made from English National Mark flour.

It has the approbation of the Ministry of Agriculture which will supply all applicants with information as to the nearest place from which National Mark flour can be obtained.

## TWO HUNDRED FROM ONE SET!

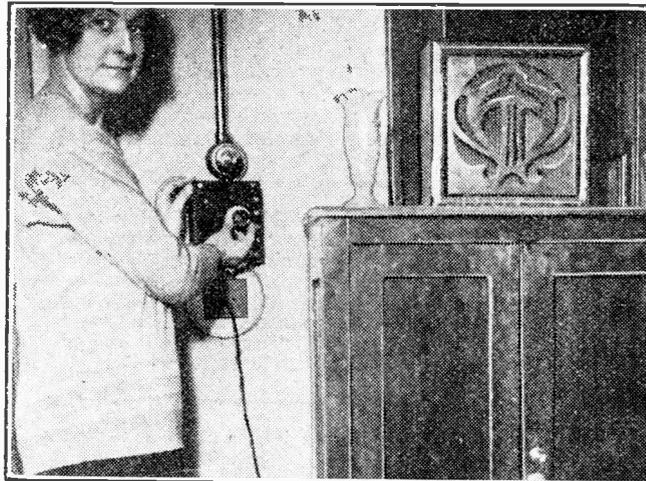

No less than two hundred families are supplied with radio from a set installed near Baker Street, London, W., and here one of the loud speakers is shown being plugged in to work from this super programme-provider.

## TECHNICAL NOTES.

By Dr. J. H. T. Roberts, F.Inst.P.

## NOVEL RECORDING METHODS.

USE OF MAGNETISED WIRE—THE TELEGRAPHONE, ETC.

SOME time ago I mentioned the use of a magnetised wire for the purpose of recording and reproducing sound, and as this seems to have been a matter of general interest to readers, you will probably like to have some further details of this system, particularly as it is being rapidly improved and is to be adapted for use with talking pictures.

The idea of recording sound by converting the sound variations into magnetic variations and impressing these upon a steel wire or tape is generally believed to be due to Poulsen, the arrangement being originally known as the "telegraphone."

Although a certain amount of progress was made with the telegraphone, it never got really very far, because of the difficulty

of amplifying the very feeble reproduction obtained from the magnetised wire; you will bear in mind that all this was long before the invention of the thermionic amplifying valve.

It appeared at that time, therefore, that there was a natural limitation to the practical use of the telegraphone, and investigations along these lines practically ceased.

**Renewed Interest.**

With the coming of the wireless valve, however, and the general developments in methods of sound recording and reproduction, attention was again turned to the

(Continued on page 1102.)



# "M.W." and Sir John Reith

THE DIRECTOR-GENERAL OF THE B.B.C.

Contributes a series of special and exclusive articles to "Modern Wireless" on the problems of British Broadcasting, and his first article appears in the February issue, on sale Feb. 1st.



*Other Special Features include:*

Is Radio Realism Possible?  
by Capt. P. P. Eckersley, M.I.E.E.  
Humour via Radio by "Philemon"  
A Revolution in Selectivity  
Microphone Mannerisms  
Television in 1930?  
etc., etc.

*Three Fine Sets for Constructors*

The "B.P." Five  
(A special high quality set)

The "Eckersley" A.C. Three  
(For all-mains working)  
and

The "Electric" Two  
(Another fine mains set)

## "Leasing Out Britain's Ether"

IS THE TITLE OF SIR JOHN'S FIRST ARTICLE  
IN THE FEBRUARY ISSUE OF

# "MODERN WIRELESS"


ON SALE FEB. 1st.

PRICE 1/-

ON SALE FEB. 1st.

**EXCLUSIVE TO "M.W."**

# REACTION CHANGES

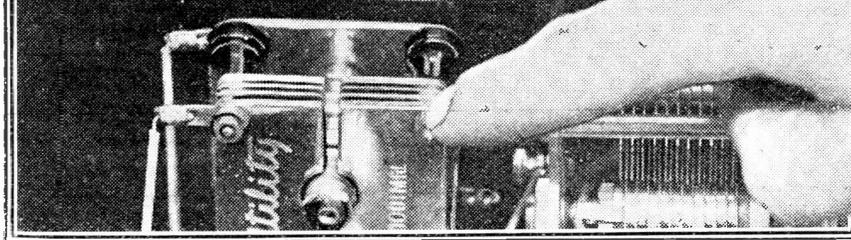

By  
A. S. CLARK.


THERE are still many receivers that employ the original swinging-coil method of obtaining reaction. Some amateurs consider that this scheme is better than capacity control, while others prefer the latter.

Leaving personal partialities out of the question, capacity reaction certainly scores over magnetic reaction control on several points. These are such as to be of particular interest to those not very skilled in making delicate adjustments of tuning, and condenser control is consequently preferable for domestic receivers.
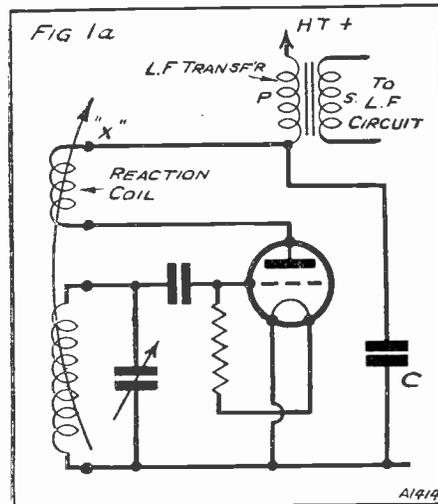
### Easy Alteration.

It is an easy matter to convert a set with swinging-coil reaction to capacity control, and the conversion is well worth trying. The following details should make it quite clear how one can do it. They apply equally to sets using ordinary plug-in coils, and those in which all-wave tuners of the tapped variety are employed.

The type of aerial circuit does not matter. It will not make any difference whether it is direct-coupled, auto-coupled by means of a tap on the tuned circuit, or whether



A typical circuit employing swinging-coil reaction.

a separate semi-aperiodic aerial coil is provided. No alterations have to be made to the tuned circuit.

Fig. 1a shows the reaction scheme which is almost universal in swinging-reaction-coil receivers. The aerial and earth are omitted since, as already indicated, different methods of coupling may be employed, and

It is not difficult to arrange a swinging-coil reaction set to be capacity-controlled, and the alterations are described in this article.

it is also possible that the detector valve may be preceded by one or more H.F. stages.

The primary of an L.F. transformer is shown connected in the plate circuit of the detector valve, but it must be appreciated that in some cases it will be replaced by telephones, or the anode resistance of an R.C. unit. Whatever it is, is immaterial so far as the details for converting to capacity-controlled reaction are concerned, and we will assume it is an L.F. transformer for purposes of description.

### For Extra Parts.

Fig. 1b shows the circuit of Fig. 1a altered to capacity-controlled reaction. The only extra components required are an H.F. choke and a reaction condenser. The value of the reaction condenser is not very important, and .0003 will do for any circuit, but in some cases a .0001 will be large enough, particularly when plug-in coils are employed.

Mount the H.F. choke on the baseboard near the plate terminal of the detector valve holder, and fix the reaction condenser in a convenient position on the panel. The wiring alterations to make are as follows. Break the wire that runs from one side of the reaction coil to the L.F. transformer.

The point is marked "X" on the diagram of Fig. 1a. Now connect one side of the H.F. choke to the plate of the detector valve and the other to the wire running from the L.F. transformer and which was previously joined to the reaction coil.

The other side of the reaction coil (which is now free), is joined to the fixed vanes of the reaction condenser, the moving vanes going to L.T. —. (The condenser C may be omitted.) This completes all the alterations.

### Final Adjustments.

You will appreciate that there are now two means of controlling reaction, the reaction condenser and the original coil holder or reaction knob.


The latter must now be considered merely as a rough control only. It should be

adjusted as follows: Set the reaction condenser vanes about one-third the way in, and then adjust the reaction coil so that there is just sufficient reaction to make the set oscillate at any part of the tuning dial.

This applies to both wave-bands in the case of all-wave tuners. The set is now tuned in the usual way, the new condenser being used instead of the original reaction control. As its capacity is increased so reaction will increase, and vice versa.
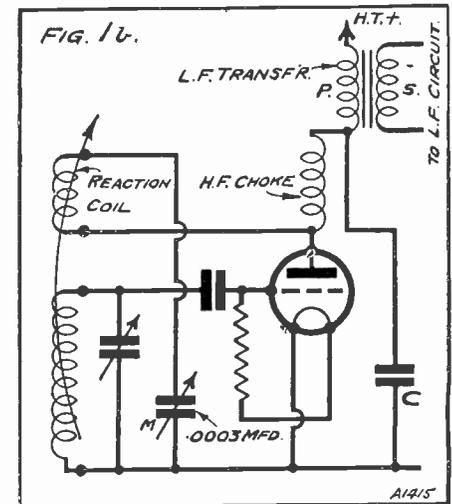
### Hints on Handling.

Sometimes hand capacity is experienced on the reaction condenser of a Reinartz circuit, and a few hints on overcoming this will not be out of place. Usually the fact of having the moving vanes of the



The circuit of Fig. 1a changed to capacity-controlled reaction.

reaction condenser connected to L.T. — obviates the trouble.

If, however, it is present in spite of this, it will probably be accompanied by a "ploppy" control of reaction, and the following hints will help to put the matter right.

Use a smaller reaction coil. (This applies chiefly when plug-in coils are employed.)

Lower the value of the H.T. on the detector valve.

Use a higher value of grid leak for the detector valve.

Fit a .0002 series fixed condenser in the aerial lead. (In some sets this will already be incorporated.)

Make sure the L.T. accumulator is not running down.

## THE "MAGIC" THREE.

The Editor, POPULAR WIRELESS.

Dear Sir,—G. E. B. of Port Talbot would have saved himself much trouble, and probably a lot of expense, had he adhered to the value of resistance specified by the designers of The "Magic" Three, i.e. 25,000 ohms. In his letter he states that a 100,000-ohm resistance was used, and that a 300-turn coil is necessary for reaction.

The reason for such a big coil is obvious, for assuming his supply is 120 volts, the voltage on the detector anode when using 100,000-ohm decoupling resistance, and an ordinary L.F. valve may quite possibly be less than 30 volts, when the D.C. resistance of a Ferranti A.F.3 (2,000 ohms) is also taken into account. If G. E. B. will substitute a 20,000 or 25,000-ohm resistance for that mentioned in his letter, he will get all the reaction he requires with the coils recommended, and the results will certainly be more amazing than he is getting at present.

Yours faithfully,

M. E. CHAPLIN.

Ipswich.

The Editor, POPULAR WIRELESS.

Dear Sir,—I built the "Magic" Three about four weeks ago, and the results are amazing. I am only using the spring mattress of the bedstead for an aerial at present, and I can get a good number of stations, loud-speaker strength.

I am very grateful to POPULAR WIRELESS for bringing into existence such a fine set.

I have since constructed the H.F. unit, and would be pleased if you would inform me just how to connect to the "Magic" Three.

With all good wishes to you and your paper,  
Yours truly,

J. B. LEWIS.

Ipswich, Suffolk.

[ED. NOTE: Full details for the connection of the H.F. unit will shortly be given in the "Radiatorial" columns.]

The Editor, POPULAR WIRELESS.

Dear Sir,—As an old reader of your paper, I feel I must write to say how much I appreciate the "Magic" Three. I have built a good few sets in my time, but this is the best. But to those who wish to hear it at its best, I would advise them to use a super-power valve with output filter in the last stage, using 150 volts on its plate and 224 grid volts.

I wrote this letter for another purpose as well, and that is as regards the connections to the coil holders. I happened to build an identical set to my own (the "Magic" Three of course), but found on switching on that the X coil didn't tune all the wave-lengths from 230, or thereabouts, to 500 as my own did, and, of course, I was a bit puzzled and sat down to think it out a bit. Then it struck me that the coil holders were mounted differently, and on rectifying this everything was O.K.

Anyone who has built this wonderful set and cannot tune from 230 to 500 metres with a 60 X coil should try reversing the leads to both coil holders,

## CORRESPONDENCE.

## The "MAGIC" THREE.

A FURTHER SELECTION FROM THE HOSTS OF LETTERS FROM READERS WHO HAVE BUILT THIS REMARKABLE RECEIVER.

Letters from readers discussing interesting and topical wireless events or recording unusual experiences are always welcomed; but it must be clearly understood that the publication of such does in no way indicate that we associate ourselves with the views expressed by our correspondents, and we cannot accept any responsibility for information given.—EDITOR.

viz., aerial side of coil holder to earth side and vice-versa, and the plate side of reaction coil holder to the side connected from the H.F. choke and vice-versa. I always make a rule of remembering that the plate side of reaction coil is connected on the same side as the earth is on the aerial coil holder.

This may not be a very clear letter, but I have endeavoured to explain to the best of my ability, and I think there may be many people who have overlooked this point and have been disappointed with results.

Another point of interest is that of working on the long waves. Well, not having a large enough reaction coil to work Daventry 5 X X properly, I tried shunting a '0001 fixed condenser from one side of H.F. choke (the one nearest the reaction condenser and connected to same) to any point connected to earth. With 250 X coil and 50 or 60 reaction, I found I could oscillate and tune in all the long-wave stations, so I left it in, and found that on going over to the broadcast band again I needed less H.T. and only a 25 or 30 reaction coil, without any sacrifice of volume or tone. I may have bored you stiff with all this, but if my experience will benefit anyone else, I shall be satisfied.

Yours faithfully,

H. W. COOK.

Manchester.

The Editor, POPULAR WIRELESS.

Dear Sir,—Having put the "Magic" Three to a strong test during the last three weeks, I am thoroughly convinced that its capabilities have no limit.

So far, so good. But I must admit that there is one "snag," and this is undoubtedly shared by many others. In this I refer to the irksome business of opening the cabinet in order to change coils on the broadcast band.

I have, after a few interesting experiments, overcome this difficulty by means of a double-throw three-pole switch, working on large diameter coils of my own construction.

## SHORT-WAVE NOTES.

By W. L. S.

it has not yet been noticeable on headphones).

So many readers send in queries of various kinds about the use of A.C. mains units in conjunction with short-wavers that the Editor has asked me to contribute a separate article on this subject.

I must apologise for not answering the letters individually, but hope that the various points will be cleared up in the article referred to.

The "Dorchester" telephony station, reported by several readers as working at various times with the yacht "Elettra," is apparently causing quite a stir in the Antipodes. I have the card from New Zealand which I have, I believe, mentioned previously, and I have had reports by radio from several of the New Zealand enthusiasts, all to the effect that he is stronger than 5 SW and altogether puts out a very fine transmission.

Another new telephony station is Rugby, G B U, who is reported by quite a shoal of readers. He apparently works at irregular

The medium wave, 2 L O, 5 G B, etc., etc., has a tapped coil, and the long wave, 5 X X, Radio Paris, F L, and Hilversum, run on an untapped coil. The same reaction is in use, but naturally with a much tighter coupling on the long wave. Whichever coil is not in use is completely put out of circuit.

Believe me, yours truly,

Maidstone.

J. W. KNIGHT.

The Editor, POPULAR WIRELESS.

Dear Sir,—Having heard quite a few good remarks about the "Magic" Three, I decided to build same a few evenings ago. I was really astonished when I switched on to hear the new high-power station at Rome coming in on the loud speaker at tremendous volume. Up to the time of writing I have received about fifty stations on the loud speaker, and hope for more. I have built at least twenty three-valve sets, but not one of these came up to the "Magic" Three in either volume or purity. I have not tested this set on short waves yet, but hope to do so in the course of a day or so.

Thanking you for such a remarkable set, and wishing your paper every success.

Yours faithfully,

F. G. BARNES.

P.S.—I can cut Liverpool, my local station, out within a few degrees of the dial without a wave-trap. Liverpool.

## THE "ANTIPODES ADAPTOR."

The Editor, POPULAR WIRELESS.

Dear Sir,—I have much pleasure in writing to you about the "Antipodes Adaptor." I built the "A. A." a few months ago, and so far I have logged some two dozen stations all over the world. Some of them are 2 X A F, K D K A on 26 metres, G 5 S W, Zeesou, P C J, 7 L O, P C L, 2 P J; Bangkok, Radio Manila, 6 A G, 2 M E, G B X, 1 A B Singapore, etc. The unit works excellently well with the ordinary set. We in Ceylon are unlucky for we are unable to get the proper components from the local dealers.

About 5 S W we here are unable to appreciate its transmissions, for we have to keep up till midnight to hear it, and even after waiting till midnight we are sometimes disappointed. P C J and Zeesou comes here very loud as early as 8.30 p.m., I.S.T., but 5 S W cannot be received so well as 2 X A F on early mornings.

Listeners in Ceylon are eagerly waiting for a day when the B.B.C. will open an Empire S.W. station for the British Colonies. The new Brookmans Park station can be received here after about 11 p.m., I.S.T. at good strength, but atmospherics are very troublesome. At present I am using an S.G. four-valve set, which is very similar to the "Magic" Four which we received by the last mail, only the reaction is different. I will change the circuit when I get a differential condenser. I have been a regular reader of the "P.W." for the last year and a half, and have learnt many things by the help of the "P.W."

Thanking the "P.W." staff, and wishing it success.

Yours faithfully,

Moratuwa, Ceylon.

W. T. FERNANDO.

I HAVE several times been asked my opinion as to the best type of detector valve to use for short-wave work, and have invariably replied that it depends largely upon the coupling following the detector, but that my own personal preference is for one of the excellent "H L" type general-purpose valves.

No one seems to have worried, though, about the other valve or valves in the receiver, and I think it worthy of mention that I am using at present as my output valve also one of this type, with an impedance of 30,000 and an amplification factor of 30. Failing this, I often use a "DEL" type with an impedance of about 7,500, in preference to a small power valve.

## Signals Sharpened-up.

This only applies, naturally, to a receiver intended for use with headphones only; quality of reproduction suffers considerably, but signals are considerably improved in strength, and in the case of C. W. (which happens to be what I am keenest on for the next month or so) the signal is "sharpened up" quite a lot. In addition to this we have the advantage of the low anode current taken by the output valve.

Naturally, for loud-speaker work such an arrangement is strongly to be deprecated; the grid-swing that these valves will handle is rather small, and considerable distortion must occur on strong telephony (although

times on 33 or 34 metres, and has been responsible, it is believed, for burning out one listener's best pair of headphones.

One of these (a Plymouth reader) is in trouble because he can do anything he likes down to 30 metres, and there he is stuck. He can in no circumstances get lower. A common trouble at first, R. C. A.! Probably you have not quite got the hang yet of the best layouts for short-wavers, and your wiring is too long or too complicated.

## Keep the Wiring Short.

If you use a series-fed circuit the trouble can't possibly be due to H.F. chokes or anything of that kind. I take it you have tried other valves as detectors? Persevere with improving the general layout and "smartness" of the set, and shorten the wiring as much as you possibly can, and success will arrive all of a sudden.

A Loughborough reader reports hearing a station calling W O O on 24.6 metres and announcing "This is G 2 G N calling from the 'Olympic,'" and afterwards the station was heard working with F 8 B Z. Can anyone else throw any light upon this?

Another transmission that has been responsible for a lot of correspondence is that of "Buttercup." This man has been heard working with "Yellow File" now, and with "Buffalo Red" on other occasions. Any further information on any of the above transmissions will be welcomed.

# HOW TO GET RED HOT RHYTHM FROM POPULAR BROADCAST DANCE TUNES 'MY SONG OF THE NILE'


PURE CURRENT  
FOR LIVELY RADIO



There is a thrill and a throb in every bar of this syncopated song when you put a Lissen New Process Battery into your set. For the pure current it delivers throws up the rhythm of this dance into sharp relief and makes it enjoyable to listen to and alluring to dance to.

There is a Secret Process used in the Lissen Battery which generates pure D.C. current. There is never any ripple in it, never any hum. It puts smooth, noiseless power into your set—which will last for months and months of use, and Safe Power, safe for the children and all at home.

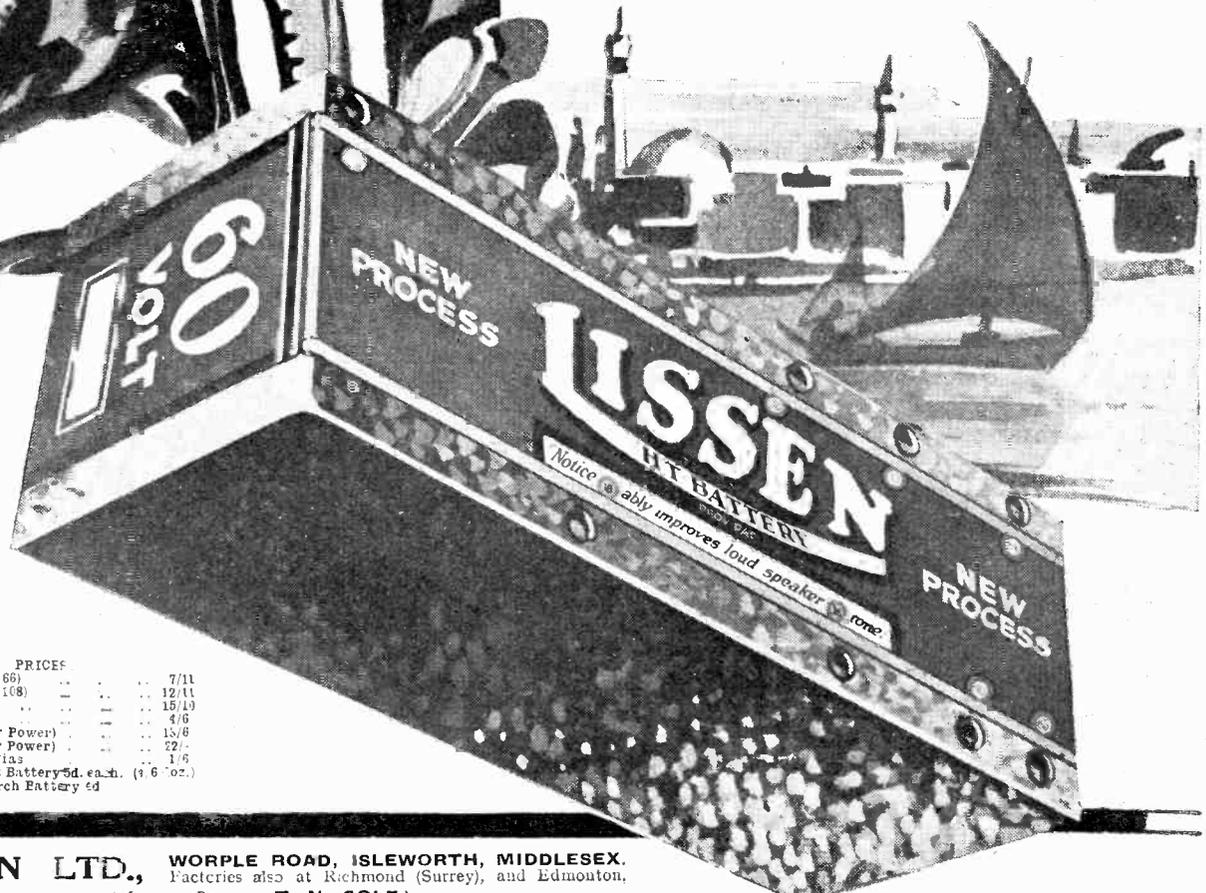*Put a Lissen Battery into your set. It brings from your loud speaker music that keeps you listening and sets the feet tingling to the rhythm.*





PRICES

60 volt (reads 66)	7/11
60 volt (reads 108)	12/11
20 volt	15/10
6 volt	4/6
60 volt (Super Power)	15/6
60 volt (Super Power)	22/-
9 volt Grid Bias	1/6
4 volt Pocket Battery 5d. each. (1/6 doz.)	
Single Cell Torch Battery 1d	

**LISSEN LTD.,** WORPLE ROAD, ISLEWORTH, MIDDLESEX.  
Factories also at Richmond (Surrey), and Edmonton,  
Managing Director: T. N. COLE.

# Use the MORE-MUSIC LESS-WEAR PICK-UP

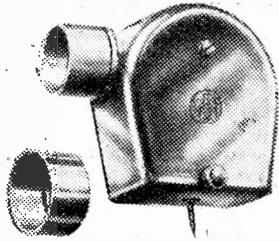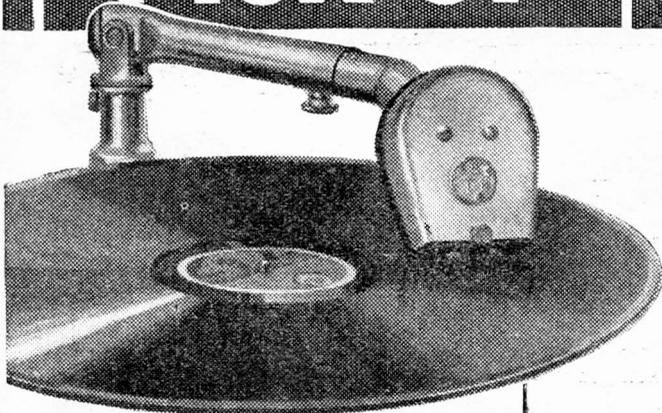

Pick-up with adaptor for use with standard Gramophone tone arms—price 27/6 complete. Gives equally good results.

A record is made electrically—unless it is reproduced electrically a great deal of its beauty may be lost. Use a B.T.H. pick-up with your radio set and hear record music as you've never heard it before.

Pick-up and Tone Arm—Price 45/- complete.



## PICK-UP and TONE ARM




THE EDISON SWAN ELECTRIC CO., LTD.,  
Radio Division,  
1a, Newman Street, Oxford Street, W.1  
Branches in all the Principal Towns.


# EDISWAN
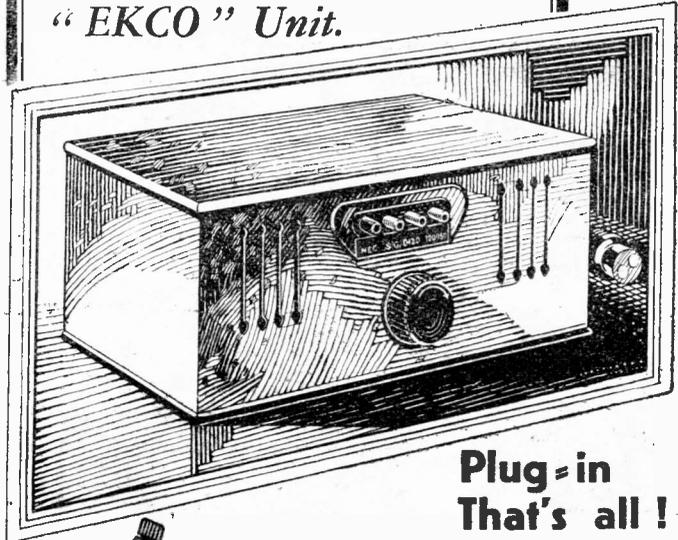
# BRITAIN'S FAVOURITE TRIO . . . .

*works better, cheaper  
and simpler with an  
"EKCO" Unit.*



**Plug-in  
That's all!**

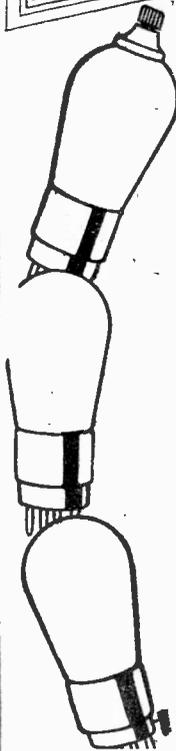

Fully 75% of radio receivers in the British Isles are of the three-valve type—Screen Grid, Detector, Pentode—a combination that eats up current like a hungry lion. For trouble-free, pure reception with this type of set you must use an "EKCO" Power Supply Unit—the most reliable, the cheapest and the simplest source of current. An "EKCO" All-Power Unit abolishes all batteries, accumulators and grid bias, whilst an "EKCO" H.T. or L.T. Unit eliminates H.T. or L.T. batteries respectively.

The H.T. Unit, illustrated above, is Model IV.20 for A.C. Mains. Suitable for use with all well-known portable sets and other receivers from one to five valves. Tapping for S.G. Valve, also at 0-120 and 120/150 volts. Output up to 20 m/a (Size 7 3/4" x 6 3/4" x 4 1/2").

£4 : 12 : 6

D.C. Model (7 1/2" x 3 1/2" x 3 1/2")

£2 : 10 : 0

"EKCO" Power Supply Units are obtainable for D.C. as well as A.C. Mains. Westinghouse Valveless Rectification in A.C. Models.

# EKCO

## POWER SUPPLY UNITS

Write for details of Easy Payments and Free Booklet on "All-Electric Radio," containing full particulars of the above Units, and "EKCO-LECTRIC" Radio Receivers, radio's supreme achievements.

E. K. COLE LTD., DEPT. A. "EKCO" WORKS, LEIGH - ON - SEA.

THIS week we are presenting to our readers that famous receiver, the "Magic" Three, in a new guise. We have already given it in a simple standard form, and also with various refinements which could be added to make it into something of a "de luxe" receiver, and now comes the turn of those readers who are interested in electrical gramophone reproduction.

For them we have designed a radio-gram version of the "Magic" Three, and we have taken the opportunity of incorporating in it many of those special little refinements we have discussed in the past, since no doubt such users will wish to make it something of a "last word" outfit.


At the same time, since it is now some little while since the original appeared, we are taking the opportunity of repeating the design more or less in full, so that those who have not previously tried the "Magic" Three can, if they so desire, make it up like any other new receiver.

Since there may be some of our readers who did not see the original design at all we may as well just run briefly over the circuit details of the receiver portion proper. We will endeavour to do this in as little space as possible, and then go on to the special new arrangements which will no doubt interest all those who have already constructed the set.

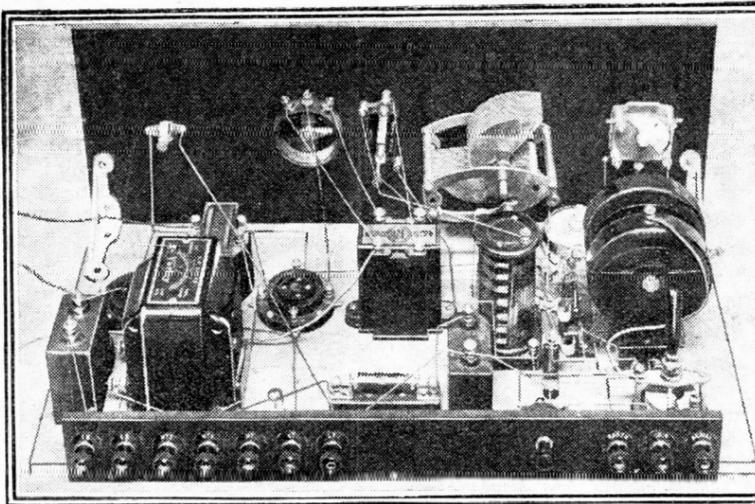**Converting Your Own "Magic."**



We should like to explain at this point, by the way, that it is quite an easy matter to add the pick-up arrangement to the existing standard version, as you will see as you go on. In the interests of those who already possess an example of the "Magic" Three in standard form, we have taken care to make the pick-up arrangements as simple and as easy to add as we could, and we actually produced the present receiver by taking the original model and converting it.

The special secrets of the "Magic" Three circuit are chiefly located in the tuning and reaction arrangements of the



No matter how you look at it—back view, front view, or any other way—the "Magic" Radio-gram is a winner!

# The "MAGIC" RADIO-GRAM

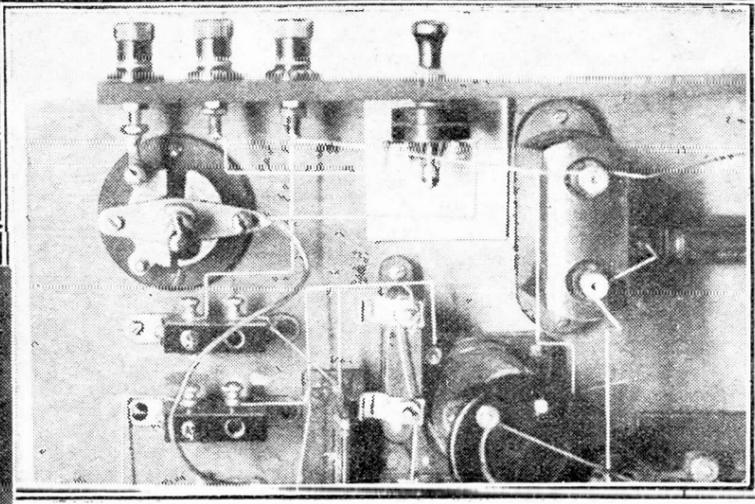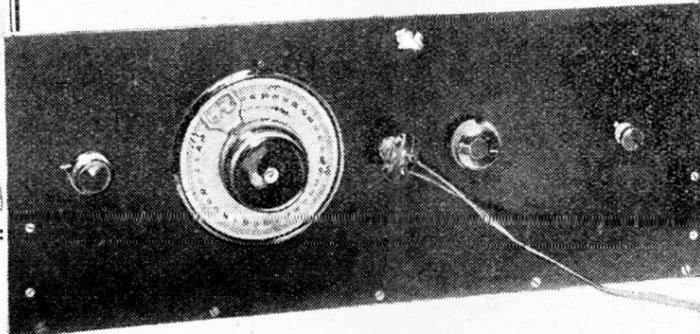

You can look down on to the baseboard—but you've simply got to look up to the set when you hear it!

detector valve. First of all, there is a tuned circuit composed of a standard type of "X" coil tuned by the usual .0005 mfd. variable condenser. This in itself is a good standard method of getting a satisfactory degree of selectivity, which is further enhanced by the special reaction scheme and also by an adjustment of the grid potential of the detector valve to the best working point by means of a potentiometer.

Then, to make the set suitable for use on short waves without the tuning becoming unduly difficult, there is a fixed condenser of .0005 mfd. which is arranged for insertion in series with the tuning condenser when required. This is put out of action when not required, in a fashion which you will understand when you look at the photographs and wiring diagram.

This condenser is the one marked C<sub>6</sub> and you will observe that it is fitted with grid-leak

clips. The idea is that when you do not require the condenser in circuit you insert in these clips a short piece of brass or copper rod or tube of about the same dimension as a grid leak, or failing that a short piece of pencil or wooden rod wrapped in tinfoil, so short-circuiting the fixed condenser and thereby leaving the

variable condenser alone in circuit.

When the condenser C<sub>6</sub> is "unshorted," so to speak, it has the effect of reducing the maximum tuning capacity to half its

normal value and so renders tuning very much easier on the shorter waves.

We have already mentioned that there is a device provided for the correct biasing

of the grid of the detector valve, and you will observe that this takes the form of the potentiometer marked P<sub>1</sub> on the diagram.

**Special Reaction Circuit.**

With the aid of this you are enabled to find a grid voltage for the detector valve which gives you the smoothest possible reaction, and since this is usually somewhere half-way between negative and positive, there is a consequent improvement in selectivity for technical reasons with which we will not trouble you at this point.

The reaction arrangement is a special


form of the differential method which we introduced especially for use in the "Magic" Three. As the reader is probably aware, differential reaction has the very great merit of having practically no effect in upsetting the tuning when it is adjusted, and the

**Power and Stability.**

Following upon the detector we have the other main important feature of the "Magic" Three, namely an unusually powerful yet stable L.F. amplifying side consisting of two transformer-coupled stages. In this way enormous amplification is obtained with suitable valves.


Adequate precautions are of course taken to ensure stability. In the first place, there is what is commonly called an anti-motor boating filter at the detector stage, (Continued on next page.)

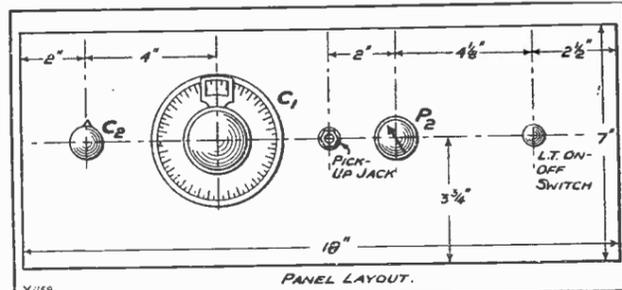Here's a set that not only beats Records but plays Records as well! Literally packed with programmes, it is another triumph for THE "P.W." RESEARCH DEPARTMENT.



The panel is just like the "Magic" Three's, except for the pick-up jack and the volume control (P<sub>2</sub>).

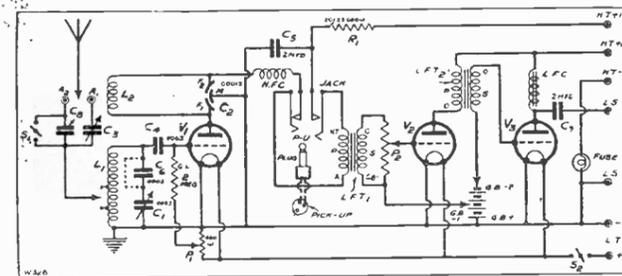Your old Gramophone will be as pleased as yourself with THE "MAGIC" RADIO-GRAM and you can carry on after every station in Europe has closed down!




As the original "Magic" circuit couldn't be beaten we "de-luxe-ified" it a bit, and the above diagram shows every detail of the system of connections.

**COMPONENTS AND MATERIALS.**


- 1 Panel, 18 in. x 7 in. (Resiston, Becol, Trolite, "Kay-Ray," Trelleborg, etc.).
- 1 Cabinet to fit, and baseboard 9 in. or 10 in. deep (Pickett, Raymond, Cameo, Gilbert, Lock, etc.).
- 1 .0005-mfd. variable condenser, slow-motion type or with Vernier dial (Lissen, J.B., Lotus, Igranic, Raymond, Burton, Gecophone, Ormond, Utility, Dubilier, Bowyer-Lowe, Cylton, Formo, Colvern, etc.).
- 1 Vernier dial, if condenser not of slow-motion type (Utility, Lissen, Igranic, J.B., Lotus, Brownie, Formo, Ormond).
- 1 .0001-, .00013-, or .00015-mfd. differential reaction condenser (Lotus, Ready Radio, Lissen, Dubilier, Pye, Burton, Utility, Wearite, Ormond, Magnum).
- 1 L.T. on-off switch (Benjamin, Lissen, Igranic, Lotus, Bulgin, Wearite, Keystone, Burton, Raymond, etc.).
- 3 Sprung valve holders (Lotus, Igranic, W.B., Benjamin, Formo, Magnum, Wearite, Burton, Bowyer-Lowe, etc.).
- 2 Single-coil sockets (Lotus, Raymond, Wearite, Keystone, etc.).
- 1 400- or 200-ohm baseboard-mounting potentiometer (Igranic, Lissen, Ready Radio, etc.).
- 1 Baseboard-mounting neutrodyne type condenser (for use as series aerial condenser on short waves, not for neutralising). (Magnum, J.B., Lissen, Keystone, Bulgin, etc.).
- 1 H.F. choke (Varley, Lewcos, Ready Radio, Dubilier, Igranic, Lissen, R.I., Climax, Raymond, Bowyer-Lowe, Bulgin, Magnum, Wearite, Colvern, etc.).
- 2 L.F. transformers of low ratio, preferably of different makes or types. (R.I. "Hypermu" and Igranic "J" in set). Any good makes. A few

- other examples are these: Ferranti, Lissen, Brown, Telsen, Cossor, Varley, Lotus, Lewcos, Philips, Mullard, etc.).
- 1 .0003-mfd. fixed condenser (Igranic, T.C.C., Dubilier, Lissen, Clarke, Graham-Farish, Goltone, etc.).
- 1 2-mfd. Mansbridge type condenser (Lissen, Ferranti, Dubilier, T.C.C., Hydra, Mullard, etc.).
- 1 2-megohm grid leak and holder (Ediswan, Lissen, Dubilier, Igranic, Carborundum, Loewe, Mullard, etc.).
- 1 25,000- or 20,000-ohm resistance and holder (any resistance of 20,000-60,000 ohms will serve). (Ready Radio, Dubilier, Ferranti, Lissen, Varley, Precision, R.I., Mullard, Igranic, etc.).
- 1 Terminal strip, 16 in. x 2 in. x 1/4 in.
- 10 Terminals (Igranic, Belling and Lee, Eelex, Clix, etc.).

- Wire, Screws, G.B. plugs, fuse, etc.
- The list above is that for the standard version. For the "Radio-Gram" form the following additional parts will be needed:
- 1 Combined series aerial condenser and shorting switch (Wearite).
- 1 "Double-circuit jack" (Lotus J.K.3, Igranic, Ormond, etc.).
- 1 1/2- or 1-meg. volume control, 3 terminal type (R.I., Gambrell, Varley, Igranic, Rothermel, etc.).
- 1 .0005-mfd. fixed condenser with grid-leak clips (T.C.C., Lissen, Dubilier, Mullard, Goltone, Graham-Farish, Clarke, etc.).
- 1 Output filter choke (Varley, Ferranti, R.I., Igranic, Wearite, Magnum, etc.).
- 1 2-mfd. condenser (T.C.C., Lissen, Dubilier, etc.).

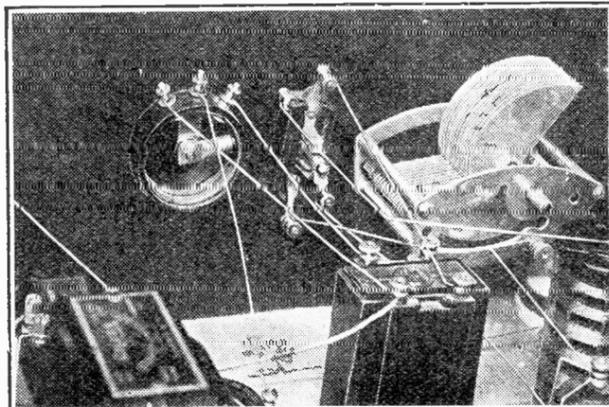

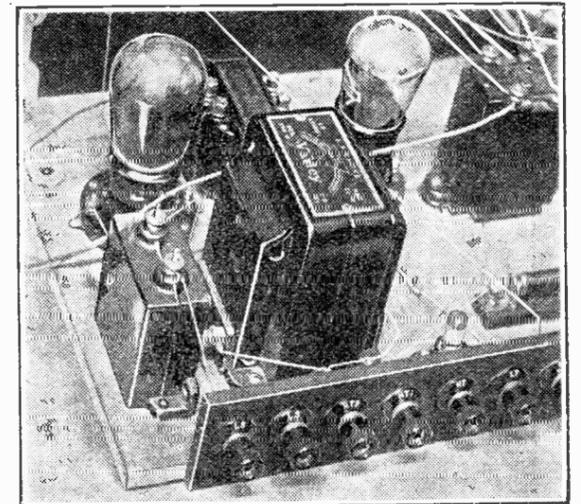Perhaps the "P.W." photographer took special care to show these wires clearly, for he runs a "Magic" Three himself, and wants to adapt it for gramophone work as well. Anyhow, every wire to the jack and volume control is very clearly shown on this photograph.



On the original "Magic" Three this corner of the baseboard was left comparatively empty, in case it was desired to fit a filter circuit later. And here the necessary choke and condenser are shown in position, forming yet another valuable feature of the "Magic" series.

# THE "MAGIC" RADIO-GRAM.

(Continued from previous page.)

consisting of the resistance  $R_1$  of 25,000 ohms, or thereabouts, and the 2-mfd. condenser  $C_5$ . This is a most valuable aid in preventing battery coupling troubles, and practically removes the risk of howling under normal conditions.

The careful layout of the L.F. side to prevent interaction also plays its part in promoting stability, as also does another little device in the second stage. We refer to the fact that we have provided a connection to earth from the core of the second L.F. transformer, which helps to stabilise the receiver still further.

This is done by taking the lead which

runs between two of the filament connections of the valve holders  $V_2$  and  $V_3$  to the earthing tag provided on the second transformer, which point is marked X on the wiring diagram. Of course, this is not absolutely essential, and with those transformers not provided with an earthing point should be ignored.

### Special New Features.


Those are the details of the "Magic" Three main portion common to all of its various versions. Now let us just run over very briefly the special features of the particular form. In the first place, we have incorporated two of the special refinements suggested in later articles—namely, an output filter for the loud speaker and a volume control.

Both these features are very desirable in a radio-gram outfit. The volume control is almost a necessity, because with a sensitive pick-up you are likely to find yourself

overloading the last valve in the absence of a volume control, and there would be nothing you could do about it. With the aid of the control you can adjust the volume to a nicety, and give your last valve just as much as it can carry without distortion setting in.

Although not so necessary, the output filter is nevertheless decidedly desirable. A radio-gram outfit is presumably one arranged with considerable regard to the best possible quality, and that means plenty of H.T. on the last valve, which will no doubt be a super power. In such cases an output filter is a great help.

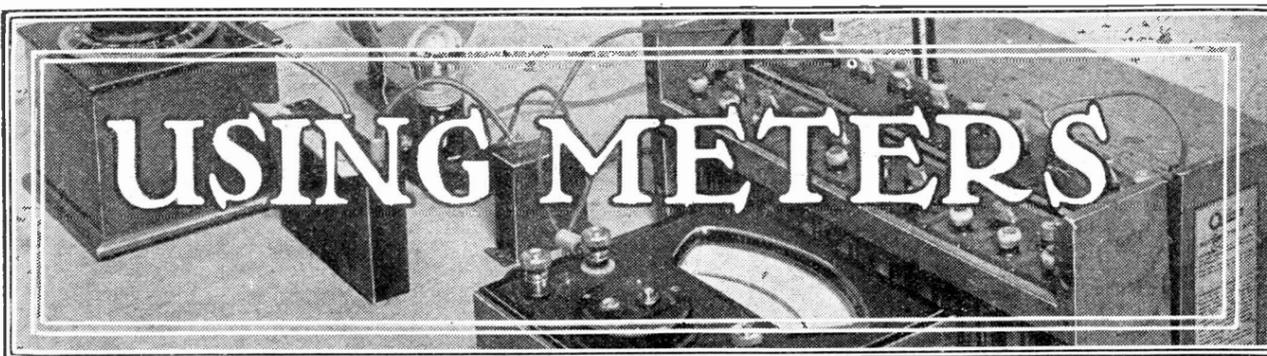In the detector circuit you will find one further little refinement which we have not previously shown in a "Magic" design, namely, an optional series aerial condenser provided with a switch for cutting it out of the aerial circuit when not required, but these and other points we must reserve for next week's article.



**T**HERE are two ways in which a milliammeter can be used. You can connect it up to show you how much H.T. current the set is using, or you can make it show you whether a valve is overloading, or in some other way distortion is occurring. The two things are not the same.


In the second case you want the H.T. current of only the one valve to pass through the milliammeter.

For either task a meter giving readings from 0 to 20 or 30 milliamps will be necessary if your set uses a power or super-power valve. Such a meter will cost anything from about 2s. 6d. up to £7.
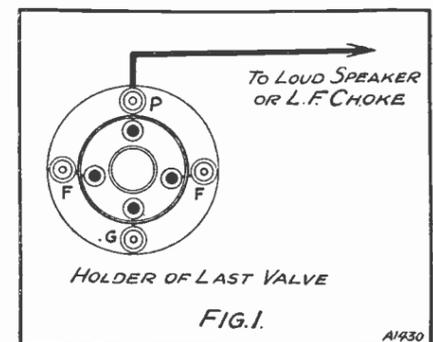
### Three Points to Note.

The cheapest kind may answer your purpose, for you will not want laboratory accuracy of measurement.

To determine the total current that is flowing from your H.T. battery or mains unit you connect the device between the negative terminal of the H.T. supply and the negative H.T. terminal of the set.



This is the wire you have to disconnect in order to insert the milliammeter when you use it to check the power valve's activities.

That is, you disconnect the negative H.T. lead from the set, and join this to one terminal of the meter. The other terminal of the meter is then connected to the H.T. negative terminal of the mains unit or H.T. battery with a short length of wire.

The reading given indicates the total current passing from the H.T. battery or mains unit. There are three points to note. The set must not be in an oscillating condition (turn your reaction back to zero) or more current than usual may be passing.

If the meter is connected up the wrong way round no reading may be given. And finally, if the resistance of the meter is unduly high the set may howl because a common coupling between its anode circuits has been introduced.

**The listener who operates his set without meters is working in the dark. Meters can tell you exactly what is happening to a receiver and exactly where there is likely to be distortion. And this article explains in the simplest possible way how to choose and use one of the most important of all meters.**  
**By G. V. DOWDING, Assoc.I.E.E.**

By the way, don't forget that a tiny meter with a small scale and a thick needle cannot show you anything but approximations. The bigger the scale and the thinner the needle the closer the readings you can take.

In order to test the H.T. current passing to one particular valve in order to test this valve for distortion you must proceed as follows:

If this valve has a positive H.T. tapping on the H.T. supply all to itself you can connect the meter in series with the H.T. lead concerned. But it often happens that the very valve you want to test shares its H.T. tapping with some other valve or valves.

In such a case, or perhaps in any case, it is best to start right at the plate terminal of the valve holder.

Supposing you want to test the last stage. (This is the valve that is more often badly overloaded or working under incorrect conditions.)

You disconnect the wire that is on the plate (anode) terminal of the valve holder, and join this wire to the one terminal of the meter. The other terminal of the meter is then connected to the plate terminal of the valve holder.

### Mind Those Filaments!

Of course, it won't matter if you have to lengthen the existing wire by temporarily joining another piece of wire to it in order to place the meter in a comfortable position for reading its needle movements.

But do be careful that you do not short-circuit anything and burn out the valves. This can only too easily happen, perhaps by touching the plate valve lead against a filament wire or terminal or something else or by touching the metal case of the meter against something. Please note that last point very carefully.


Practically, any type of milliammeter can be left permanently in circuit in order to give you indications the whole time the set is in use. The exceptions are those of high resistance (these would drop your H.T.

voltage and mess up your anode circuit characteristics) and those of the watch type not having terminals.

Panel-mounting milliammeters suitable for permanent connection can be obtained from Messrs. Bulgin, Ferranti, Sifam, Ward & Goldstone, and other well-known firms.
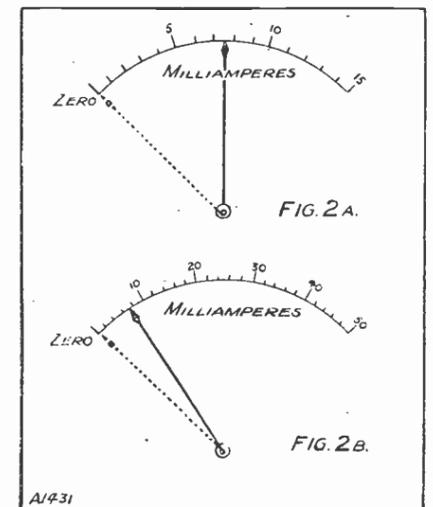
### Scale Sizes.

An extremely useful type, but one that is rather more expensive than the simple kind, is the one that has three ranges, 0-5, 0-10 and 0-25 milliamps. These three ranges are valuable because while the first gives you a wide needle movement for smaller H.T. currents (such as with a detector valve) you have another range (the third) capable of getting in the currents handled by the smaller super-power valves. Actually you must have a meter having a maximum on its scale at least 25 per cent




This drawing illustrates the importance of the relative sizes of the scales of meters. Notice the distances covered by each of the needles to indicate the same one or two milliampers.

greater than the greatest H.T. current you ever expect to use.

Don't purchase a meter reading to much greater figures, as the relative needle movements will be so much smaller.

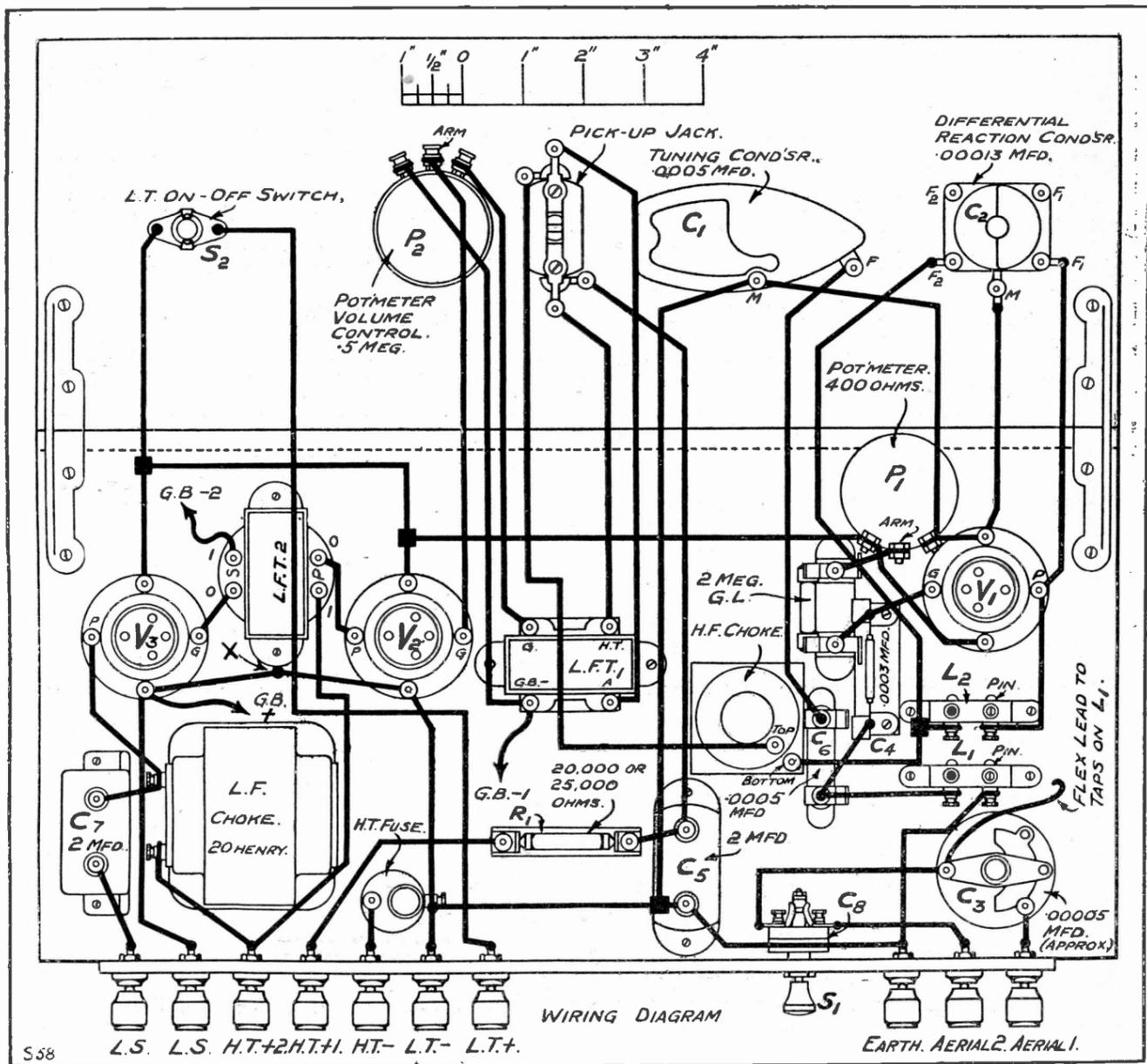Would you notice a 1 milliamp decrease with Fig. 2B as easily as you would with Fig. 2A? Finally, your object will be to keep the needle of the meter practically stationary when the loudest noises are coming through the loud speaker. But the actual interpretation of milliammeter needle movements has been dealt with quite recently in "P.W."



# Ready Radio

## FOR THE "MAGIC" THREE

OUR COMPLETE KITS ARE OFFICIALLY APPROVED BY "POPULAR WIRELESS"

- KIT A less valves and cabinet £6: 13: 0
- KIT B with valves less cabinet £8: 6: 6
- KIT C with valves and cabinet £9: 16: 6

All Kits include special Ready Radio connecting links.

Official Blue Print and full wiring and operating instructions free of charge with all kits.

**NO SOLDERING REQUIRED!**

## EASY PAYMENTS

NO DEPOSIT SYSTEM

## COMPLETE SET "MAGIC" THREE

All parts as specified, including Valves, Cabinet, Short-Wave Coils, Ready Radio connecting links and official Blue Print with full wiring and operating instructions.

**12** equal monthly payments of **18/3**

### CASH, C.O.D. or EASY PAYMENTS

A new addition to the well-known Ready Radio Service is our Hire-Purchase **NO DEPOSIT SYSTEM** for complete Kits of parts, etc., etc. Our close attention to customers detailed requirements and the well-known Ready Radio After Sales Service ensure complete satisfaction whichever way you buy.

Telephone No.  
Hop 5555  
Private Exchange.

# Mullard ORGO RECEIVER

NOW AVAILABLE FOR IMMEDIATE DESPATCH IN SEALED CARTONS

- KIT A (excluding cabinet) £6: 11: 5
- KIT B (with valves) £9: 9: 5
- KIT C (with valves and cabinet) £10: 16: 11

## EASY PAYMENTS

All PARTS as specified in "Radio for the Million" INCLUDING:— VALVES and CABINET

**12** equal monthly payments of **19/9**

## BROOKMANS

TWIN-WAVE

## REJECTOR

COMPLETE KITS AVAILABLE FOR

IMMEDIATE DESPATCH

- KIT A WITHOUT COILS £0: 18: 3
- KIT B INCLUDING COILS £1: 6: 6

## BROOKMANS

TWIN-WAVE

## CONDENSERS

SET OF 3 CONDENSERS AS USED BY THE DESIGNER **10/6**

These condensers enable you to obtain the fine control essential for the ELIMINATION of EITHER or BOTH Brookmans Park stations.

# Ready Radio

## FOR THE "MAGIC" FOUR

OUR COMPLETE KITS ARE OFFICIALLY APPROVED BY "POPULAR WIRELESS"

- KIT A less valves and cabinet £9: 19: 6
- KIT B with valves less cabinet £12: 15: 6
- KIT C with valves and cabinet £14: 8: 0

All Kits include special Ready Radio connecting links.

1 Set of Short-Wave Coils (20-50 metres) can be supplied separately if desired. Price 7/10.

For full list of approved components see issue dated November 30th.

**NO SOLDERING REQUIRED!**

## EASY PAYMENTS

NO DEPOSIT SYSTEM

## COMPLETE SET "MAGIC" FOUR

All parts as specified including Valves, Cabinet, **SHORT-WAVE COILS**, and Ready Radio connecting links.

**12** equal monthly payments of **27/3**

### READY RADIO IMMEDIATE DESPATCH SERVICE

When you buy radio parts you naturally want them quickly. You also would be happier with the knowledge that in the event of subsequent difficulties you can obtain technical advice without trouble.

#### TO HOME CUSTOMERS

Your goods are despatched post free in sealed cartons or carriage paid by rail. Note.—You can if you desire avail yourself of the C.O.D. system.

#### TO OVERSEAS CUSTOMERS


All your goods are very carefully packed for export and insured, all charges forward.

# Ready Radio

Telegrams:  
Ready Hop 5555  
London.

159, BOROUGH HIGH STREET, LONDON BRIDGE, S.E.1

# A Vote of Confidence in the T.C.C.

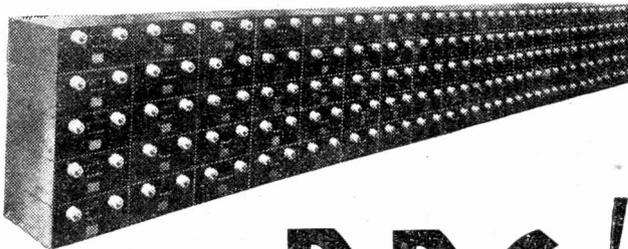

by the **B.B.C.**!


HERE is a testimony of the confidence placed, by those who *know*, in T.C.C. The British Broadcasting Corporation specified T.C.C. Condensers for use in their high power Brookmans Park transmitter. For such a job, only condensers having an extremely high standard of efficiency, of accuracy, of dependability could be considered and T.C.C. condensers were installed. Whether it's a bank of condensers illustrated above or just a small 2 mfd. condenser for eliminator smoothing T.C.C. are to-day the recognised standard. Consider this when *you* need a condenser.

The illustration above shows the bank of smoothing condensers tested to 24,000 V.D.C., for working at 12,000 V.D.C., installed at Brookman's Park.



A Ltd. Telegraph Condenser Co. Ltd., Wales Farm Road, N. Acton, London, W.3.

3373

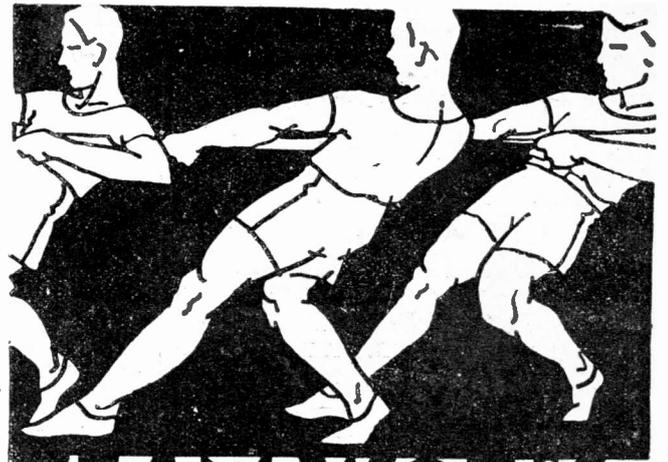

**TEAM WORK-**

## A PERFECT COMBINATION!

Team work—every part pulling its weight—is the foundation of success in a wireless set—just as much as in a tug-of-war. The colossal success of BurTon's "Empire 3" is due to team work. Every part a BurTon part—every part doing its job to perfection—all pulling together—that's team work!


**£5. 10**

*Valves, Batteries and Royalties extra.*
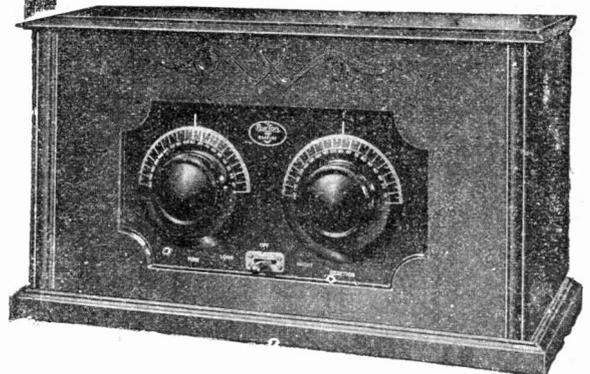
### ALL MAINS MODEL

*(self-contained)*  
Price of Set - £11 : 5 : 0  
Price of Valves (Mullard A.C.) £3 : 10 : 0  
*(Royalty extra)*


*Identical in appearance to the Battery Model.*



# THE BURTON EMPIRE 3

EVERY PART A BURTON PART

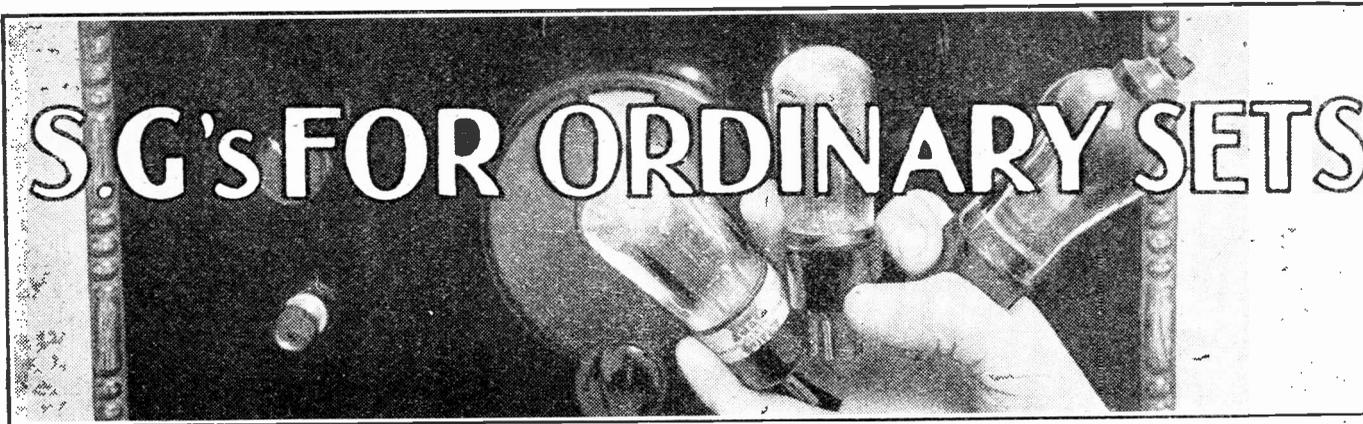C. F. & H. BURTON, PROGRESS WORKS, WALSALL, ENGLAND



**H**AVE you ever considered the possibility of using an S.G. valve in place of the present valve in the H.F. stage of your receiver, and do you know what alterations are necessary to the circuit in order to make this possible?

Perhaps you are even wondering why it should be necessary to have to make alterations at all when it is desired to change over to a screened-grid valve.

**Preventing Feed-back.**

In these circumstances it is reasonable to suppose that a few words of explanation will not be altogether amiss, although it should perhaps be explained that the main object of the present article is to deal with the practical, rather than with the theoretical, side of the question, and that in consequence the "theory" part of the business must be kept short.

When designing the H.F. stage of a set on the ordinary neutralised principle, the coils, wiring, etc., are so arranged that as far as possible no coupling shall take place when the set is working between the grid and anode circuits of the H.F. valve.

The distance separating the coils is based to a large extent upon the degree of amplification given by the valve, since the strength of the "fields" round the coils is very largely governed by this factor. The S.G. type of H.F. valve differs from the ordinary variety in that it has a very much higher amplification factor although, of course, this is not the only essential difference between the two valves.

Consequently, when an S.G. valve is used to replace a valve of the ordinary H.F. type in a set, the coil "fields" increase due to the much greater degree of amplification given by the S.G. valve, and as a result, there is a danger of the set becoming unstable through coupling effects.

**Alterations Essential.**

Quite apart from the question of coils, there are, of course, other contributory reasons for the tendency towards instability, such as, for instance, coupling between the wiring. Thus, in point of fact, there are very few sets with ordinary neutralised H.F. stages into which an S.G. valve can be placed, without in some way modifying the existing layout and arrangement.

In attempting to deal with the practical side, one is faced with the difficulty that there are literally dozens of different ways in which to couple the H.F. valve to the detector, although I do not think there is

In response to numerous requests we are giving full details for the easy conversion of an ordinary set so that it can take one of those wonderful screened-grid valves. The example chosen uses a very popular type of circuit.

By G. T. KELSEY.

very much doubt as to the arrangement most generally in use.

It is obviously quite impossible in the scope of a single article to give directions which will be applicable to all receivers, and since, to deal with the subject at all

thoroughly, it will be necessary to limit the subject to one particular type of set, I propose to deal with those employing the popular split-primary-transformer method.

The H.F. side of a typical set employing the split-primary-transformer scheme is shown in Fig. 1, and although in this particular example a coil of the plug-in "X" type is shown in the grid circuit of the H.F. valve, it is quite feasible that in many sets the grid coil will be one of the six-pin variety or possibly even two separate plug-in coils.

The actual method of aerial coupling is quite immaterial, and the part of the circuit with which we are most concerned is that associated with the anode circuit of the H.F. valve, in other words, the split-primary transformer.

**The Best Way.**


Perhaps the most helpful way in which to deal with the subject of alterations would be by mentioning as a start the components it is necessary to remove. I use the plural, although, as a matter of fact, there is only one which has to be removed entirely, and that is the neutralising condenser.

In order to carry out the alterations you will require in addition to the screened-grid valve one H.F. choke (a good quality choke is strongly to be recommended for use here), one .001 fixed condenser, two .25 Mansbridge condensers and two more terminals.

**Not Difficult.**

These components are all mounted in position to the right of the vertical screen, and since there is nothing particularly complicated in this part of the work, there is not much

(Continued on next page.)

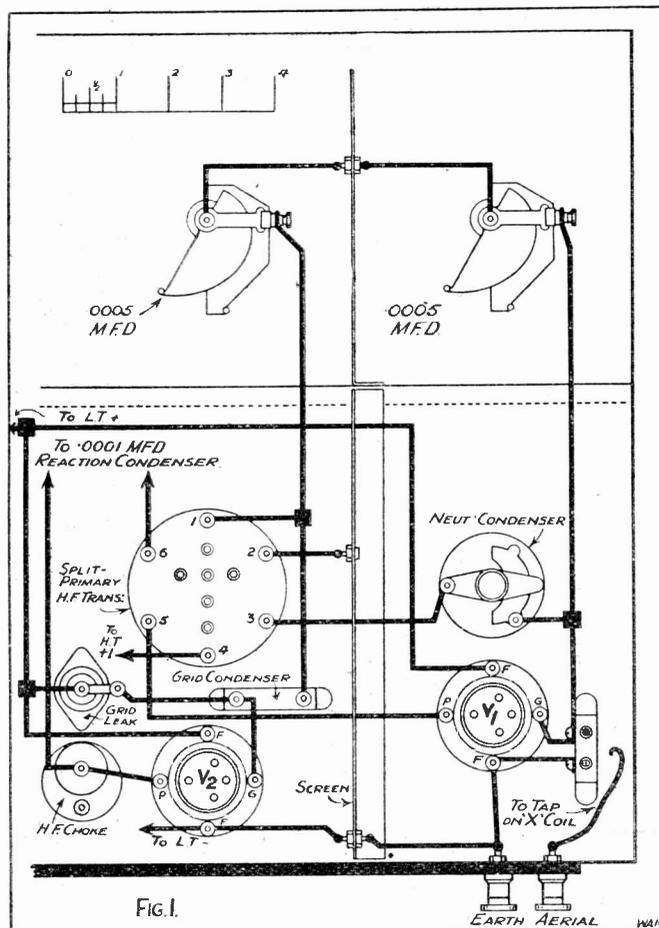

The H.F. side of a set employing a straightforward circuit, which can be modified quite easily to accommodate a screened-grid valve.

THE following brief account of a recent visit to the Varley Works, at Woolwich, will be of interest to our readers.

After inspecting all the various departments, the modern machines and testing devices, one can quite understand how this firm has reached its present high position in the Radio industry.

The manufactured articles are standardized on a quantity production basis, which enables them to be produced at really competitive prices. Each department has its own special costing system.

The Machine Shop is equipped with the most modern automatic machines, capstan lathes, etc. These enable very accurate machine work and intricate thread-cutting to be carried out.

**Everything Carefully Tested.**

The Coil Winding Shop is probably one of the best in the country, and over 300 girls are employed in it. Many types of coils apart from those for wireless are wound in this department.

Incidentally, the machines in this shop are all designed by Varley themselves, and are made in their own machine shop under their own patents. This is the shop where the well-known Bi-duplex Winding is done, in which every coil of wire is separated by pure silk. In addition, there is a complete Impregnating Department and Finishing Shop.

\* \* \* \* \*

## A VISIT TO THE VARLEY WORKS.

By  
A SPECIAL CORRESPONDENT.

\* \* \* \* \*

All coils are thoroughly tested before being sent out, even to the extent of being tested for a single short-circuited turn.

Special attention is paid to efficient packing of all products. The Packing De-

partment is quite separate from all others, and each member is trained for his particular job.

A test of each of the parts of a component is made before it is assembled, and a final thorough test is given on completion.


**Building the Sets.**

The components themselves are all tested before they go into sets, and the sets are subjected to preliminary tests during construction, afterwards being finally tested before leaving the works.


A test is made on actual broadcasting to see that each set obtains all the stations for which the manufacturers guarantee it.

The Test Department itself is equipped with up-to-date measuring instruments capable of testing all components, sets, coils and other radio equipment. Where necessary, coils, etc., are subjected to a flash test up to 2,000 volts A.C.

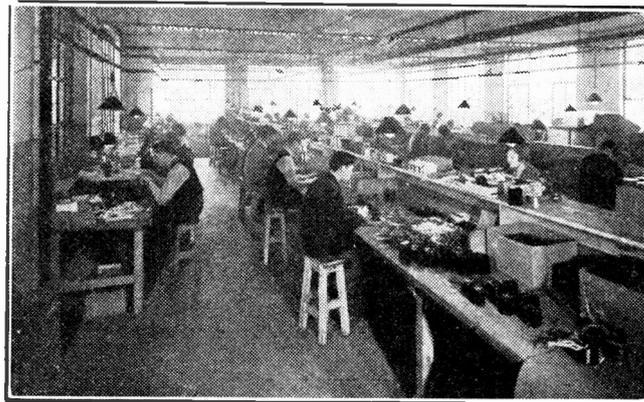Continual additions are being made to the testing department to ensure that it is always up to date.



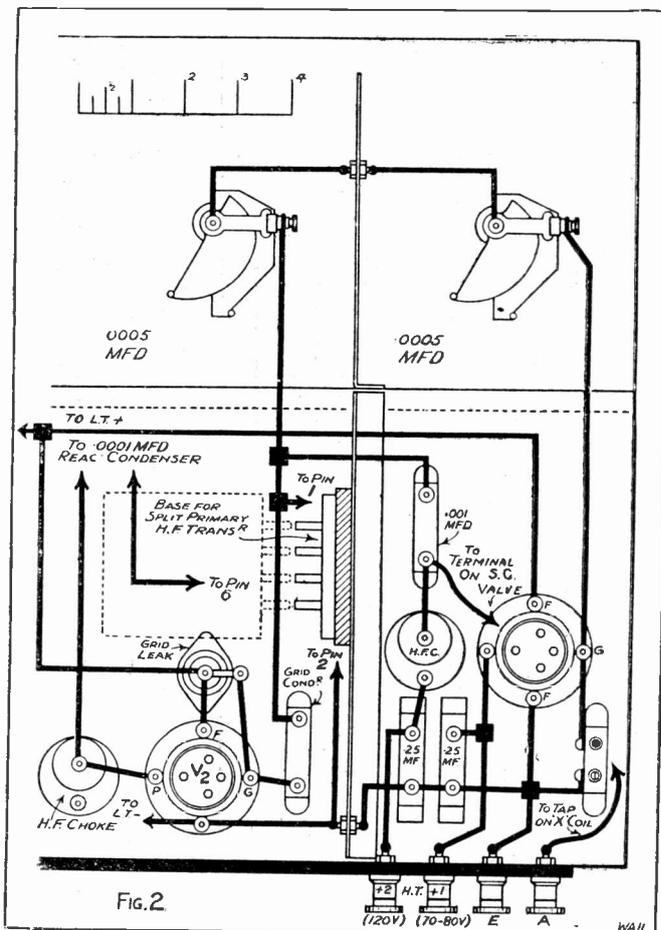The component assembly department where the famous Varley chokes, transformers, etc., reach completion.



Here is a diagram showing how the new connections run.

\* \* \* \* \*

## S.G.'s FOR ORDINARY SETS.

(Continued from  
previous page.)

\* \* \* \* \*

point in going over what is already shown quite clearly in the diagram (Fig. 2).

The portion of the set to the left of the vertical screen, however, is not quite so straightforward, although as far as the wiring is concerned this part of the circuit will be even more simple than it was before. The H.F. transformer in its present position is not satisfactory, and if left as it is would in all probability produce instability. If, however, you do not particularly wish to move the six-pin base, it can be left where it is, providing, instead of the present six-pin split-

primary transformer, you use a binocular coil of the same type.

I expect, however, that most of you will desire to use up your existing components in preference to purchasing new ones, and it will therefore be necessary for you to mount the six-pin base against the side of the screen. For this purpose the best plan is first to mount against the screen a piece of wood, and it then becomes a simple matter to fix the six-pin base in position.

Full details of the wiring alterations involved are clearly shown in Fig. 2, and perhaps I need only mention that the pins 3, 4 and 5 on the six-pin base are not now used.

**New H.T. Voltages.**

When the wiring alterations have been completed, it only remains to put the S.G. valve in the first holder, and to connect to the top of the valve the flex connection from the .001 condenser. With regard to the new H.T. plus terminals, the one on the right (marked + 1) should be joined to a position on the existing H.T. battery at about 70 or 80 volts, and the other terminal requires about 120 volts (also from the same H.T. battery). If a separate H.T. plus terminal was used for supplying the H.F. valve in the original set, only one new terminal will, of course, be necessary.

\* \* \* \* \*

### REMEMBER THAT .

\* \* \* \* \*

The long strip of a dry cell represents the negative pole and the short strip the positive.

\* \* \* \* \*

The actual plate or output connection of an S.G. valve is the terminal on the top of the bulb and that leg of the valve which is joined to the P terminal of the valve holder is joined inside the valve to its screening grid, not to its plate.

# FERRANTI RADIO IN THE HOME



*“That’s beautiful! don’t alter it, Betty—”*

The Ferranti A.C. Mains Receiver is designed with recognition of the fact that Radio is now an accepted part of the equipment of the home. Beautiful in design and workmanship, it provides entertainment of very high quality. The cost of running—entirely from the mains—is negligible, and manipulation is the simplest possible.

Available for Alternating Current only, 200/250 volts, 40 cycles or over.

PRICE, including Valves:

In Oak - - - £25

In Mahogany - - £26


In Walnut - - - £26

Royalty £1 extra.

Ready for immediate delivery.

FERRANTI LTD.  
HOLLINWOOD  
LANCASHIRE

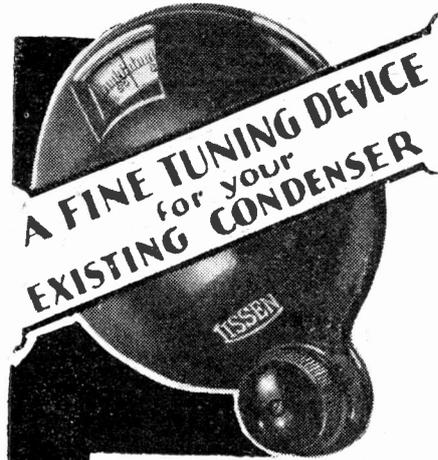*The*  
**FERRANTI**  
**A.C. MAINS RECEIVER**




**A FINE TUNING DEVICE**  
for your  
**EXISTING CONDENSER**

Fit a Lissen Slow Motion Dial to your existing condenser and get a new smoothness and ease of control in tuning. This Lissen Slow Motion Dial gives a handsome finish to any panel. In dustproof black moulded case; ratio 8 to 1; control knob rotates in same direction as dial; scale seen through window, with hair-line for accurate reading. Fits 1/4-in. spindles, but can be adjusted for use with spindles of any diameter up to 3/8 in. One extra hole only for fixing. Price **3/6**

**LISSEN**

VERNIER DIAL

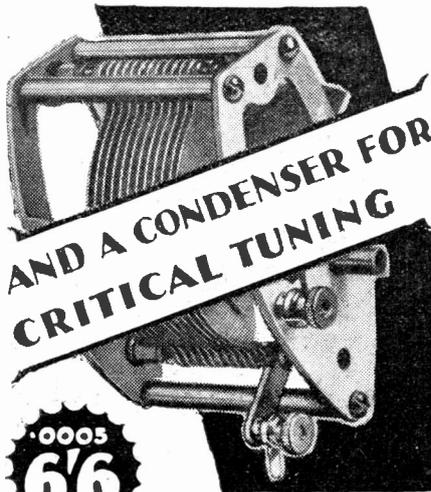

**AND A CONDENSER FOR CRITICAL TUNING**

•0005  
**6/6**

- 0001 mfd. cap. 5/9
- 0002 mfd. cap. 6/-
- 0003 mfd. cap. 6/-
- 00035 mfd. cap. 6/3
- 0005 mfd. cap. 6/6

The new Lissen Variable Condenser enables you to enjoy a new standard of tuning—a new sense of smooth control—a new ease in separating stations close together—*simply because there is no condenser loss and incoming signals are retained at full strength.* See the unmistakable rigidity of its construction; see the long bearing and the extended spindle for gauging purposes. Notice that there is no old pressure, no tendency to distortion of the vanes. The fixed vane terminal is in a new and convenient position well away from the end plates. There are feet for baseboard mounting, or standard one-hole-fixing for panel mounting.

**LISSEN**  
LOW LOSS

VARIABLE CONDENSER  
**LISSEN LIMITED**  
WORPLE ROAD, ISLEWORTH, MIDDLESEX

FROM THE  
TECHNICAL EDITOR'S NOTEBOOK.

**TESTED AND FOUND—?**


**CONDENSERS FOR OUR REJECTORS.**

THE enormous popularity achieved by every one of the several "P.W." "Brookmans" Rejectors that has been described, caused, and still is causing, a very widespread demand for the components peculiar to the designs.

It is a moot point as to whether the Rejectors beat even the "Magic" sets in this regard.

However, the fact remains that those little compression condensers needed for the Rejectors are now to be seen in all radio stores in the land that are not sold out (and there are hundreds periodically finding themselves in this condition).

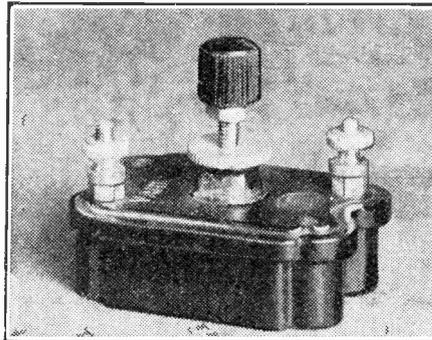The reasons are obvious. The Rejectors do the trick as nothing else except the most



The new R.I. Varicap Condenser.

intricate apparatus can, and they are, in fact, exceptionally cheap and remarkably easy to make.

Undoubtedly they are one of "P.W.'s" greatest triumphs. Moreover their arrival coincided with the new broadcasting conditions—conditions that would otherwise have been death to old and well-tried (and well-loved!) sets.

Remembering all this, let us give a hearty welcome to the R.I. Varicap condensers, which have just made their debut and which are now available in any numbers to meet fresh demands made by Rejector enthusiasts.

The Varicap sells at 2s. 6d. and is an excellent job—Radio Instruments have done nothing better and that is saying something.

Particularly do I like the wide range they cover, •0002 to •0014 mfd. is fine for such a compact little instrument.

There is, too, a lock screw that runs down and permanently holds a setting just as a good lock screw should.

And the casing is a most pleasing moulding of a high-class character.

Internally, the device, with its wide mica sheets and tough springy brass plates, is absolutely up to scratch—no rough workmanship at any point within sight or hidden to the eye. It is an honest production that a "P.W." Rejector should be pleased to meet!

(Continued on next page.)



**DELIVERS ALL ITS STORED-UP ENERGY!**

**LISSEN**  
GRID LEAKS

These are resistances that never vary; they are absolutely silent in use, and their values remain unchanged. All values,

**1/-**  
each;

With Terminals, 1/3 each.

When you buy a Lissen Fixed Condenser you can be sure that it will never leak, never vary in capacity, never break down in use, and will deliver all its stored-up energy all the time.


For whatever purpose you require a fixed condenser—whatever circuit you are building, and no matter what is specified—use Lissen with absolute confidence. They are accurate to within 5% of stated capacity, and will remain constant throughout the life of the receiver.

- 0001 to •001 - - - 1/-
- 002 to •006 - - - 1/6
- 01 - - - - - 2/-



**LISSEN**

FIXED CONDENSER

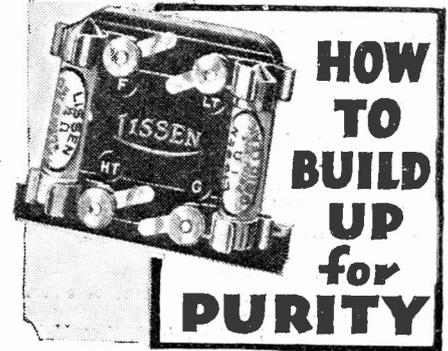

**HOW TO BUILD UP for PURITY**

Lissen Resistance Capacity Coupling Unit embodies a •01 Lissen Fixed Condenser, which is leak-proof and unvarying in capacity and which delivers all its stored-up energy. There is therefore no loss of volume, no loss of purity. The Lissen Fixed Resistances are silent; they never vary, no matter what the current load. Values incorporated have been selected as the most suitable for general use, but the resistances are easily inter-changeable. May be mounted upright or flat. PRICE **4/-**

**LISSEN**

R.C.C. UNIT

**LISSEN LIMITED**  
WORPLE ROAD, ISLEWORTH, MIDDLESEX

**NOW YOU CAN USE AN ELIMINATOR JUST LIKE A BATTERY**




**27/6**

Lissen H.T. Eliminators deliver smooth steady current from your house electric supply, and cheaply. The Lissen Eliminators can be put into your set as easily as any battery. From the four types made there will be one to suit you. Send a deposit of 5/- and we will arrange for delivery of the Eliminator to suit you and for it to be properly installed. Send 5/- only. Leave the rest to us. You pay the balance in one sum after installation or by extended instalments.

D.C. MODEL "A" 100-110 or 200-250 v. Cash price 27/6, or 5/- down and 5 monthly payments of 5/6.  
 D.C. MODEL "B" 100-110 or 200-250 v. Cash price 39/6, or 5/- down and 8 monthly payments of 5/6.  
 A.C. MODEL "A" 100-110, 200-210, 220-230, 240-250 v. Cash price 60/- or 5/- down and 10 monthly payments of 6/6.  
 A.C. MODEL "B" 100-110, 200-210, 220-230, 240-250 v. Cash price 75/-, or 5/- down and 10 monthly payments of 8/-.

**LISSEN**  
ELIMINATORS

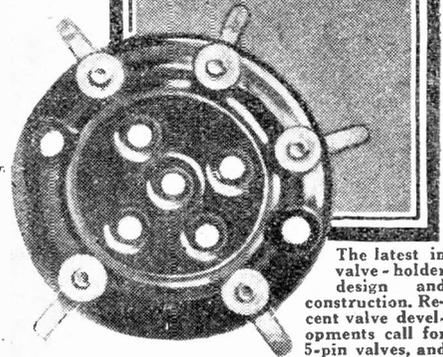**LISSEN'S NEW 5-PIN VALVE-HOLDER suits all valves!**



The latest in valve-holder design and construction. Recent valve developments call for 5-pin valves, and this tendency will without doubt be extended. Save expense by fitting 5-pin holders now. Exceptionally strong, with springs entirely independent and cannot short-circuit. A glove-like fit to any standard valve, with positive terminal connection to valve pins.

IN BROWN MOULDED CASE

**LISSEN**  
FIVE-PIN  
VALVE-HOLDER

LISSEN LTD., Worples Road, Isleworth, Middlesex.

**TESTED AND FOUND—?**

(Continued from previous page.)

**THE CHLORIDE CHRONICLE.**

This is the journal of the Chloride Electrical Storage Co., Ltd., and it sells for 2d. The cost of printing and publication is borne by the company and the proceeds of sales go to the Chloride Sick Club. I thought the recent number extra specially good.

**FROM LISSEN LTD.**

Messrs. Lissen Ltd., recently sent me a selection of their recently published literature. It is an assembly of leaflets and catalogues all very excellently produced, covering the comprehensive range of radio apparatus that Lissens now manufacture.

When one realises that every portion of every one of the components and accessories described is built by Lissen themselves, one begins to realise something of the enormous organisation that this enterprising concern has grown into.

**TRELLEBORG EBONITE.**

One meets so much brittle composition material in the cheaper radio components that it is quite a pleasure to examine some first-class ebonite—and this, Trelleborg Genuine Ebonite, certainly is.

Trelleborg Ebonite Works, Ltd., recently sent me a sample panel, glossy black on the one side and mahogany grained on the other.

Traders and manufacturers are invited to submit radio sets, components, and accessories to the "P.W." Technical Department for test. All tests are carried out with strict impartiality under the personal supervision of the Technical Editor, and readers are asked to note that this weekly feature is intended as a reliable and unbiased guide as to what to buy and what to avoid.

It has a specific gravity of 1.25 which, in itself, is an excellent indication of its quality, and a resistance test amply confirmed this. It cuts cleanly and drills without cracking and, altogether, is a material of first-class nature.

**EKCO MAINS UNITS.**

So great has been the demand for Ekco main unit and sets that E. K. Cole, Ltd., have had to erect an immense new factory. It is built on some ten acres of land and is said to be a most impressive affair.

**A MULLARD LOUD SPEAKER.**

What do you think of this?

"A cabinet type instrument possessing all the good technical features of the well-known pure music range of speakers has now been placed on the market by the Mullard Wireless Service Company, Ltd.

"The speaker, which is known as Type 'K,' consists of a balanced-armature, movement driving a 13-in. diameter cone, the whole being mounted in a polished oak cabinet, 19 in. square, with a handsome fretted front. By means of sockets at the back of the instrument either one-third, two-thirds, or the whole of the speech coil can be utilised, so that the impedance of the speaker can be adjusted to suit the output circuit of the receiver.


(Continued on next page.)

**HAVE YOU HEARD**

The **LISSEN** ADJUSTABLE

**BALANCED ARMATURE SPEAKER**

WITH MOVING COIL TONE!

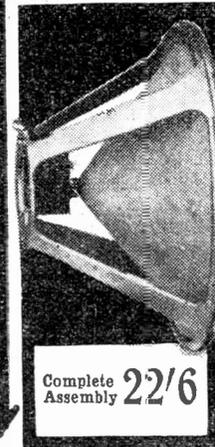

Complete Assembly 22/6

In brown moulded case with attachment for fitting to any type of cone.

Price 12/6

Cast aluminium Chassis, specially designed to give the best results from the Unit.

Price 7/6


13 in. Cone for use with the above. 2/6

The Lissen 4-Pole Balanced Armature Unit brings something approaching loud speaker perfection within the reach of everybody who owns a radio set. You can build any type of cone loud speaker with it; you can use it with a big baffle board, or put it in a cabinet. You can build a linen diaphragm loud speaker with it, or you can buy it completely assembled and ready to connect up to your set. It has a fine adjustment, and you therefore get the utmost volume from it without chatter.

**LISSEN** ADJUSTABLE

BALANCED ARMATURE UNIT

**SWITCHES** for EVERY PURPOSE!

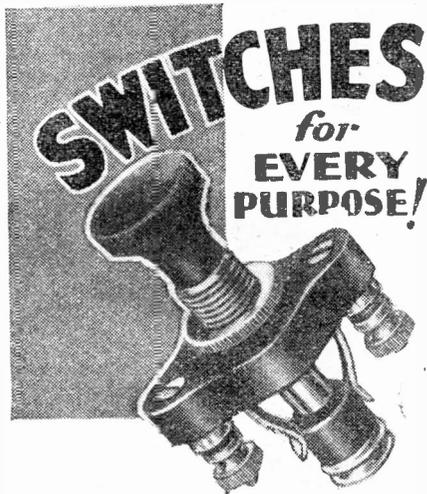

**PRICES**

Filament Switch,	1/-
3 Point Wave-Change Switch,	1/6
2-way Switch,	1/6
5-point Switch	2/6
D.P.D.T. Switch,	2/6

There is a Lissen Switch for every radio switching purpose. All Lissen Switches are fitted with terminals for convenience in wiring, and all contacts are positive and self-cleaning. Whatever purpose you want a switch for, consider value for money and you will decide upon these low-loss Lissen Switches.

**LISSEN**  
SWITCHES


LISSEN LTD., Worples Road, Isleworth, Middlesex.

## TESTED AND FOUND—?

(Continued from previous page.)

"The front fret has been designed to present the minimum obstruction to the sound waves, and the back of the instrument is also of open construction, so that the natural reproduction from the balanced-armature unit is in no way impaired by the presence of the cabinet. The movement is, of course, protected against dust by silk screens at back and front.

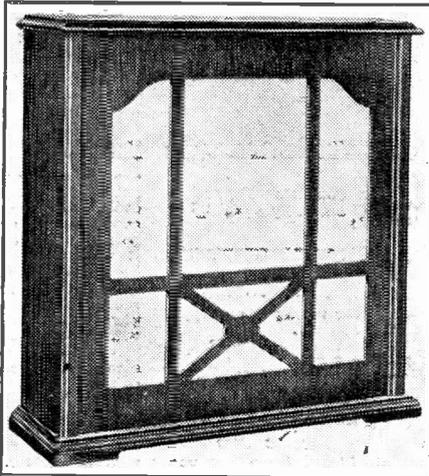"Sold at the popular price of £6 15s. 0d., which includes a 6-ft. flexible lead, the new Mullard Type 'K' speaker is already proving a good selling line."



The Type "K" Mullard Loud Speaker.

It is the Mullard people's own description of their product, and I should say for straightforwardness, lucidity and freedom from padding, it would take some beating. I do not think anyone could describe the instrument better.

It is a fine-looking loud speaker, much larger than the average, although it is far from being clumsy or awkward. Indeed, it appeals to me rather more than anything that I have seen for some time and it gives good results, results that are, in my opinion, slightly better than the other Pure Music loud speaker I reviewed a little while ago, and that is saying something. It has the alertness of the moving-coil variety with an excellent high note response. It works comparatively as well with a small two-valve as with a five-valve outfit.

### IGRANIC Q.M.B. SWITCH.

A few weeks ago I dealt with the Igranic Q.M.B. Switch but did not make it clear that there are two models available.

The one is the L.T. type, and this retails at 2s. 6d. and is excellent value for money.

The other can deal with voltages up to 250 or carry currents up to 5 amperes. This type retails at 3s. 6d. and also is a fine proposition.

### THE VALUE OF THE PENTODE.

I have received the following interesting notes from the Mullard people.

Owing to the more general use of "super" power valves in recent years, which necessitates, of course, the acceptance of the limitations of the three-electrode valve, a large grid bias has come to be associated, in the minds of the large majority of listeners, with a good power valve.

But a large grid bias simply means that the amplification factor of the valve is so low that a large signal voltage swing must be applied to the grid in order to obtain the maximum output of audio-

frequency power, and that, in order to obtain this larger signal voltage, a very considerable degree of low-frequency amplification is necessary preceding the power stage.

The best power valve is the valve which will give the desired power output for the smallest grid voltage swing, and the qualities in a valve determining its performance in this direction are its amplification factor and mutual conductance, both of which should be high, combined of course, with adequate emission.

This is one reason for the growing popularity of the pentode type of amplifying valve. The amplification factors of these valves are high, and the mutual conductances highly satisfactory. For example, the figures for the Mullard P.M.24 4-volts "Pentone" are 62 and 2.3 respectively, as compared with 4.2 and 2.1 for the super-power valve P.M.254 of similar output.

This means that with a given input signal strength, and in order to obtain the same output, a receiver or amplifier fitted with a pentode output valve need supply far less low-frequency voltage amplification than a set using a triode in the output stage. In fact, in many domestic receivers, if a pentode is employed, no intermediate low-frequency stage between the detector and pentode is required. Thus a substantial saving is effected in the initial cost of the equipment, and in addition the risk of introducing distortion is greatly reduced.

But this does not complete the tale of the advantages to be gained from the use of the pentode. If correctly applied and operated, the five-electrode valve may result in a very considerable improvement in the quality of reproduction.

To understand this, it should be realised that the output stage of a receiver, that is to say, the power valve and the speaker, must be considered as a combined unit, the performance of which depends upon the design and selection of both components.

Now the earlier types of speaker—horn-type instruments and certain forms of cone speaker—tended to over-accentuate the higher audio-frequencies—i.e. the treble notes, with the result that reproduction was apt to be high-pitched. More recent designs of speaker give a more even response to the different frequencies within the audio-frequency band, and some even err on the other side and give over-accentuated bass reproduction, a fault which is aggravated by the fact that the output of a three-electrode power valve at the higher frequencies falls off very severely.

As a result, the reproduction in modern radio equipment is usually characterised by an over-preponderance of bass, which is not only pronounced, but has become fashionable and even identified with "good quality." Now, deficiency in the higher frequencies is fatal to fidelity of reproduction,

All who prefer Quality  
in Cigarettes

Say  
Player's  
Please




5 for 3d. 10 for 6d.  
20 for 11½d.



N.C.C.722
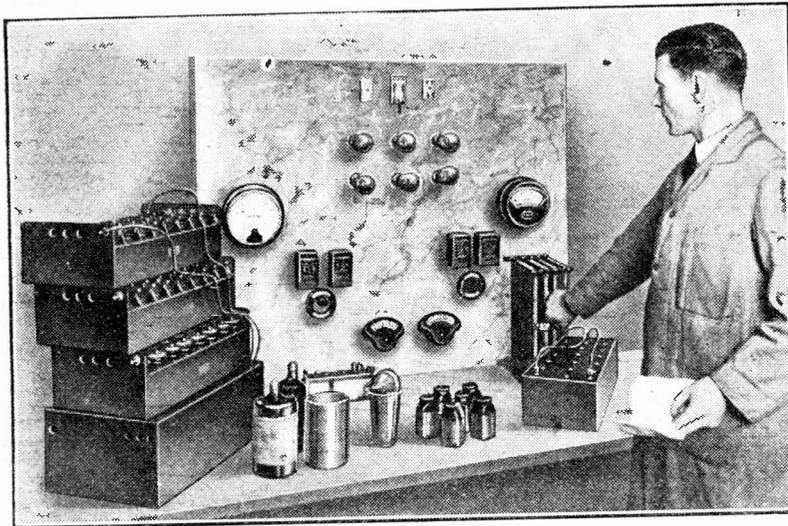
# COMPARATIVE TESTS REVEAL REMARKABLE FACTS REMARKABLE TESTIMONY



These testimonials are unsolicited and the originals can be inspected at our offices.

**VASTLY SUPERIOR TO DRY BATTERIES** *3/10/28*  
C. S. F. (Brighton)

**BEST H.T. I HAVE EVER HAD** *19/2/29*  
H. B. (S.W.8)

**SURPRISINGLY TROUBLE FREE** *13/7/29*  
C. H. T. (Caterham)

**PREVIOUSLY SPENT POUNDS ON DRY BATTERIES** *10.1.29*  
F. S. D. (Wood Green)

Why waste money on costly and obsolete sources of H.T. supply, when you will be faced with periodical renewals at further cost? In addition to giving you longer initial service, the "Standard" H.T. can be re-charged simply at home, merely by replacing the used-up Cartridges with Refills.

## The STANDARD Battery 57% CHEAPER in operation THAN DRY BATTERIES

**AMAZING OUT-PUT. 21,000 M.A. RESULT OF  
69 WEEKS' TEST**


Comparative tests carried out on a 96 cell No. 3 Standard Battery, under average working conditions, have revealed conclusively that it is overwhelmingly superior both for economy and results than the average dry battery.

**30 HOURS' USE PER WEEK FOR  
16 MONTHS.**

The battery was in service from July, 1928, to 1st December, 1929, a period of 69 weeks, on an average of 30 hours per week on a set taking 10 M.A. The output of the battery was 309 M.A. or, on this basis, a total output of 21,000 M.A. hours.

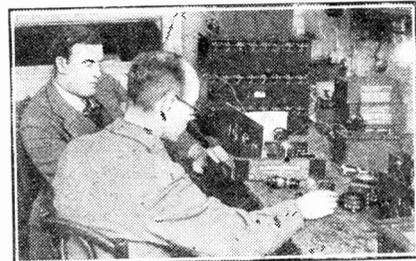**PROVED 57% CHEAPER TO RUN.**

The test shows that, apart from maintaining a steady and constant pressure of current, the battery was remarkably economical. Comparing an average size dry H.T. battery, costing approximately 12/- per 100 volts, the maximum economical output is 5 M.A., and the average life cannot be considered to exceed 5 months on the weekly running of 30 hours. Taking 20 weeks as a fair life, the cost per 100 M.A. hours equals 7.5 pence. Then take the cost of a set of refills and chemical, of the Standard battery, plus one-third of the initial cost, the cost of running equals 3.2 pence per 100 M.A. hours—57% cheaper than the dry battery.



**LEADING EXPERTS USE "STANDARD" FOR LABORATORY WORK.**

The recognition of the Standard Battery by such well-known experts as Capt. Eckerley and Mr. G. P. Kendall, B.Sc., shewn experimenting with the aid of the Standard Battery in the "Modern Wireless" Research Laboratory, is indeed an indication of its great efficiency and economy.



## GREAT ADVERTISING OFFER

**USE THIS  
COUPON**

To THE STANDARD BATTERY CO.,  
184-188, Shaftesbury Avenue, London, W.C.2

Please send me your free book fully describing and illustrating how the Standard Battery improves reception and saves money.

Name.....

Address.....

Complete batteries assembled. Cash or on our famous "No Deposit, No Refills" terms. Obtainable from all good dealers, Curry's or Hullford's.

**H.2.** 10,000 M.A. capacity, 48 No. 3 cells, 72 volts, in 2 trays with lid. Cash £2.3.6 or 5/- down and 5 monthly payments of 8/2.

**5!**  
DOWN

**H.4.** Over 10,000 M.A. capacity, 72 cells, 108 volts, in 3 trays with lid. Cash £3.4.0 or 10/- down and 5 monthly payments of 11.8. **10/- DOWN**

**J.6.** Over 20,000 M.A. capacity, 96 No. 4 cells, 144 volts in 3 trays, with lid. Cash £3.10.3 or £1 down and 5 monthly payments of 19.2. **£1 DOWN**



All Editorial communications to be addressed to the Editor, POPULAR WIRELESS, Tallis House, Tallis Street, London, E.C.4.

The Editor will be pleased to consider articles and photographs dealing with all subjects appertaining to wireless work. The Editor cannot accept responsibility for manuscripts or photos. Every care will be taken to return MSS. not accepted for publication. A stamped and addressed envelope must be sent with every article. All inquiries concerning advertising rates, etc., to be addressed to the Sole Agents, Messrs. John H. Lile, Ltd., 4, Ludgate Circus, London, E.C.4.

The constructional articles which appear from time to time in this journal are the outcome of research and experimental work carried out with a view to improving the technique of wireless reception. As much of the information given in the columns of this paper concerns the most recent developments in the radio world, some of the arrangements and specialities described may be the subject of Letters Patent, and the amateur and the trader would be well advised to obtain permission of the patenters to use the patents before doing so.

## QUESTIONS AND ANSWERS.

### DO YOU GET ANGRY WITH YOUR SET ?

"Troubled Wife."—"My husband is what would be termed an amateur wireless enthusiast. He has a two-valve set and on the whole gets very good results.

"We have a home with every comfort, and could be very happy, but at times it is made a veritable hell if anything goes wrong with the accumulator, or with the eliminator,

or in fact with anything connected with the wireless. The most dreadful accusations are made.

"No matter how careful I am the wind is raised every time anything goes wrong, and I should like to know if there is any other person who has the same thing to contend with, or is he an exception? If so, what is the best way of getting rid of it?"

We are very sorry to hear that wireless is the cause of any unpleasantness, because there is really no need for this at all. It is, alas, perfectly true that other cases have occurred, and in the great majority of those we have investigated the trouble has all been due to faulty maintenance.

The set itself may be all right, but in order to give results it must have a good "broadcasting" input

from the aerial, and a good energy input from the accumulator eliminator, etc. You can always rely on the B.B.C. for putting out a good standard of quality and strength, so if your aerial is O.K. and is kept in good condition by a monthly inspection and overhaul you can be reasonably sure that the actual broadcasting is entering the set correctly.

Next you want proper L.T. and H.T. voltages and current, and for this purpose a voltmeter is invaluable to check the power supply. One of the two-scale kind is perfectly satisfactory, as one scale will enable a check to be kept on H.T. voltages, and the other scale enables you to check the low tension.

If these two power supplies are kept up to scratch the probability is that most of your troubles will disappear, as faulty maintenance (run-down batteries, etc.) is the chief cause of poor reception.

(After you have had your valves in use for about a year or so, there is a possibility of one of them "kinking out," or "losing emission," as it is called, and this is generally indicated by a sudden falling off in strength and quality, even though the battery voltages are all O.K. A new valve is the only cure in such a case, but as we have pointed out, this should only happen say once a year at the most, and you can easily tell when this trouble arises, if you are able to borrow a valve similar to the one you are using, and substitute it, as the set will instantly be restored to life by this means.)

We feel pretty sure that in your case the bad results are due to voltage drop which should be shown up by the voltmeter, so if possible we should certainly obtain one of these invaluable instruments.

If we may venture to add another word it would be to say that irritability or impatience with a set will generally vanish when more knowledge of its working is gained. Can you not get him interested in "Pentode's" articles dealing with the working of wireless currents, so that he understands what a delicate thing a set is, and how easily some unsuspected cause may throw it out of operation unless a watch is kept on it?

It is not generally carelessness, or other people, that put it out of action, and fortunately, when all the voltages, etc., are maintained properly, it will give such regular and reliable service that to have a little fault come on it, to look for this and put it right, will be an enjoyable rather than an annoying experience!


### TRANSFORMER CONNECTIONS.

J. L. B. (Yorks).—"I have just completed the construction of the 'P.W.' 'Holiday' Two, and I think it is a wonderful little set. I have constructed it for home use, still having the


(Continued on page 1098.)

# Run YOUR Set—any Set — even a Portable

## OFF THE ELECTRIC LIGHT

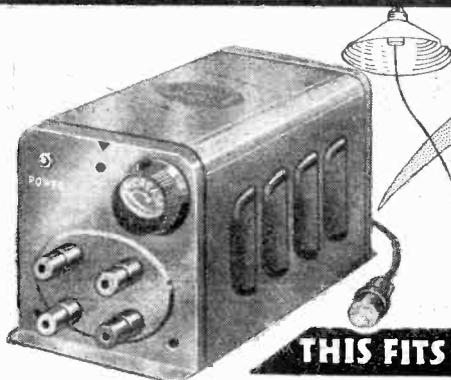

THIS FITS HERE

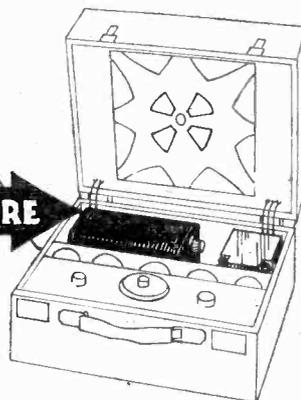

Here's the new Regentone 'Portable' H.T. Mains Unit—SPECIALLY designed for Portables—which to-day is being used all over the British Isles, not only for Portables but for ordinary 3- and 4-Valve Receivers.

Size 8½ x 4 x 4. Output 120-v. at 18 m/a. £4/5/0  
A.C. MODEL  
or 17/6 down and 6 monthly instalments of 12/6

D.C. MODEL £2/15/0  
or 10/- down and 5 monthly instalments of 10/-  
3 Tappings—1 Variable, 1 Screened Grid, 1 Power.

Insist on Regentone—the simple, trouble-free way to All-Electric Radio. No Valves, no liquids, no moving parts—nothing to get out of order. Costs practically nothing to run—guaranteed for 12 months.

All Regentone A.C. Models incorporate Westinghouse Metal Rectifier. Write for FREE ART BOOKLET "Radio from the Mains," and for particulars of Regentone Hire Purchase Terms.



For Radio from the Mains

REGENT RADIO SUPPLY CO. 21, Bartlett's Bldgs, Holborn Circus, London, E.C.4. Telephone CENTRAL 900.

# BEWARE IMITATIONS

THERE IS  
**ONLY ONE GENUINE  
FORMO-DENSOR "G"**

See name on Article and Carton

Types "G" & "J" as used by designer  
and specified for **THE BROOKMANS**

**REJECTOR**

**THE  
WAVE-CHANGE  
REJECTOR**

**THE  
KENDALL  
REJECTOR**



**BE WISE!**

Refuse Unspecified Substitutes and  
thus avoid Disappointing Results.

Full Catalogue sent post free on receipt of post card.

The **FORMO Co.** Crown Works Cricklewood Lane, N.W.

# APOLOGY

To Messrs. Impex Electrical Ltd.,  
538, High Road,  
Leytonstone.

With reference to the recent notice which has appeared in the window of our premises situate at 278, High Street, Stratford, E.15, wherein we have stated that "DARIO VALVES ARE NO LONGER GOOD," I regret that I have caused such notice to appear and appreciate that such notice would lead the public to believe that valves sold under the name of "Dario" were not good, which is contrary to fact.

I UNDERTAKE that neither I, my servants or agents will in future repeat this notice or any similar notice or make any statement either by word of mouth, advertisement or notice detrimental to your goods, and I apologise to you for having given prominence to such notice which I now realise was entirely untrue.


(Signature) R. H. COSKY,

Trading as **WIRELESS SUPPLIES UNLIMITED,**  
278, High Street, Stratford.

# WARNING

Messrs. Impex Electrical Ltd., will take proceedings against any person or firm who in any way libel the articles sold under the name of "Dario."

# NO OTHER SET IS SUCH SPLENDID VALUE

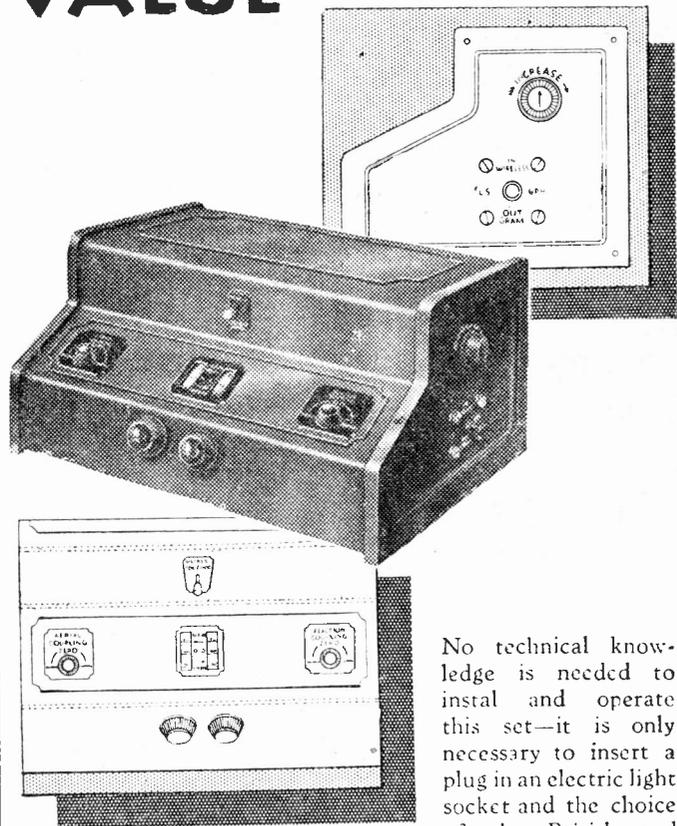

PRICE  
**20 GUINEAS**  
(including valves)

"Pay as you use" terms may be  
arranged with your dealer.

No technical knowledge is needed to instal and operate this set—it is only necessary to insert a plug in an electric light socket and the choice of the British and foreign programmes is at your command.

The price is low and a few shillings are sufficient to cover a year's running costs.

Ask your dealer to demonstrate.

# EDISWAN

All British All Electric

# RECEIVERS



THE EDISON SWAN ELECTRICAL CO., LTD.,  
Radio Division,  
1a, Newman Street, Oxford Street, W.1.  
Showrooms and Trade Counters in all the  
Principal Towns.

W.40

# RAYMOND'S

27 & 28a, LISLE ST., LONDON, W.C.2  
Come to LEICESTER SQUARE TUBE  
This address is at the back of Daly's Theatre  
Phones: Gerrard 4637 and 2821

**HOURS OF BUSINESS** EVERY DAY 9 to 8  
SATURDAY 9 to 9  
SUN MORN. 11 to 1

## COMPARE OUR PRICES

**RAYMOND'S**  
FOR THE "MAGIC" 2 KIT OF PARTS

Panel 14 x 7, .0005 S.M. Condenser, Differential Reaction, 0 to Switch, 2 Spring V.H., 2 B.B. Coil Holders, H.F. Choke, Lotus or Telsen Radiogrand 12/6 (add balance any other make), 400-ohm B.B. Pot., Neutralising Condenser, .0003 and .0005 Fixed, 2 meg. and Holder, Strip, 10 Terminals, Wire, Screws, Clips, Flex. Plugs and Baseboard.

**CASH PRICE**  
**55/-**  
Post U.K. 1/-

**KITS OF PARTS** of your own selection  
Quoted for at a special cash price where possible on receipt of detailed list.  
**OVER 25/-** in value

## AMAZING VALUE IN 3-VALVE LOUDSPEAKER RECEIVERS

RECEIVES LOCAL, BROOKMAN'S PARK, NEW ALTERNATIVE, 5 G.B., AND MANY CONTINENTAL STATIONS.



**DE LUXE MODEL** ASSEMBLED IN CABINET READY TO FIX TO AERIAL  
**A WONDERFUL SET FOR DISTANCE, SPEECH AND MUSIC.** ALL PARTS ENCLOSED TRANSFORMER COUPLED NETT. CASH NO COILS TO CHANGE

RECEIVER (as shown) with 3 D.E. Valves, (one Power), Dual Range Coil 200/2000, Battery Leads, and 9 volt Grid Bias.  
**69/6** BATTERIES and SPEAKER EXTRA Carriage 5/-

**EASY TERMS** 12 MONTHLY PAYMENTS OF 7/9

OR COMPLETE RECEIVER (AS ABOVE) WITH THE LOT  
100-volt H.T., 2 v. 40 L.T., Amplion Cone Speaker Aerial Equipment.  
**£5-12-6** Carriage 7/6.

**EASY TERMS** (the lot) 12 MONTHLY PAYMENTS OF 13/11  
EASY PAYMENT FORM FREE IF FLAT OR HOUSEHOLDER.

**SOVEREIGN WE STOCK**  
CONDENSERS J.B. Condensers, R.I. Chokes, Transformers and all usual products, Lowcoils Coils, Chokes, etc. Ekco Mains Units, Amplion Speakers, Brown Speakers, and all components, phones, etc. Ferranti L.F. Transformers, Chokes, Anode Resistances, Cossor, Mullard, Oram Ediswan, Marconi Valves, Varley Chokes and Transformers, Ormond Condensers, Dials, etc.

"F" .0001 2/-  
"G" .001  
"J" .0003 Post 3d.

**EASY TERMS** ON KITS OF PARTS ETC. OVER £3

**"MAGIC" 3 (P.W.) Our Parts Approved edit r.**  
KIT OF PARTS.—18 x 7 Panel, .0005 Variable S.M. Dial, Reaction (Differential), 20/2,000 L.T. Switch, 3 Spring V.H., 2 Coil Sockets, 400-ohm B.M. Potentiometer, Neutrodyne B.B., Lewcoils H.F. Choke (or R.I. Dual), Hypermu and Igranio "J" 40, 60X, L.F., .0003 Fixed, 2 mid., 2-meg. Leak and Holder, 25,000-ohm Wirewound, 16 x 2 Strip, 10 Terminals, Wire, Screws, Baseboard Carriage and Packing, 2/- (U.K.) Nett Cash  
**79/6** CABINET 17/6

Ultra Short including: 3 Mullard 33/6 Wave Coils Dario 2, 4, 6, 9 Triotron 18/6 6/6 Set. Tungram Set Post 6d.

**For "MAGIC" 3 RADIO-GRAM**  
EXTRAS REQUIRED. Wearite Aerial Switch, 2/3. Lotus No. 4, 2/6. Vol. Control, 6/6. .0005 and clips, 2/-. Wearite Output Filter Choke, 21/-. 2 mid., 3/6. Post 3d. under 5/.

## RADIOTORIAL QUESTIONS AND ANSWERS

(Continued from page 1096.)

batteries, etc., inside the cabinet as the original. The terminals are on a strip at the back, thus giving the set a better appearance.

"When I first wired the set I got no results, but after checking every component and wiring, I found that my L.F. transformer was connected the wrong way. You will remember that the connections on the diagram are marked G, Plate, + B, - C.

"My transformer is marked IS, OS, etc. To anyone not knowing that IS is connected to G.B. — OS to grid of valve, IP to plate, and OP to H.T. +, I think that this is liable to cause trouble, and suggest therefore that the markings should be made standard."

As a matter of fact, the markings IS, OS, etc., are rather old-fashioned ones that appear to be rapidly going out. Nearly all the British manufacturers now mark the terminals according to the points where they can be connected, i.e. G for grid, G B for G.B. —, P (or A) for Plate (or Anode), and H.T. + for H.T. +

## "P.W." TECHNICAL QUERY DEPARTMENT

Is Your Set "Going Good" ?

Perhaps some mysterious noise has appeared, and is spoiling your radio reception?—Or one of the batteries seems to run down much faster than formerly?—Or you want a Blue Print?

Whatever your radio problem may be, remember that the Technical Query Department is thoroughly equipped to assist our readers, and offers an unrivalled service.

Full details, including scale of charges, can be obtained direct from the Technical Query Dept., POPULAR WIRELESS, The Fleetway House, Farringdon Street, London, E.C.4.

A postcard will do. On receipt of this an Application Form will be sent to you free and post free immediately. This application will place you under no obligation whatever, but having the form you will know exactly what information we require to have before us in order to solve your problems.

**LONDON READERS PLEASE NOTE:** Inquiries should NOT be made in person at Fleetway House or Tallis House.

## MAKING A THREE-VALVER SELECTIVE.

A. F. F. (Enfield Highway).—"Before I ask my question, I should like to say 'Thank-You-Three-Bags-Full' for the circuit and wiring diagram you sent me last year. Right from the first it was a winner, and the variety of programmes I could get is about as amazing to my friends as the purity and strength with which I fill the room.

"Being lazy, I have not written to thank you for it, though I have often thought of doing so, but all my friends have heard about it, you can bet!

"As you will gather, I would be very loath to alter the circuit much, but I should like more selectivity now the Regional scheme is going. As there is plenty of room in the receiver, what I should like to do is to put another circuit in front of the detector, either with or without an H.F. valve; preferably without.

"I am still using plug-in tuning coils, because I have found them absolutely satisfactory, and there is plenty of room on the panel for another tuning condenser and on the baseboard for another valve, unless it wants very elaborate screening. My idea is to strip everything from in front of the detector, and re-wire it, so as to make it much more selective than the centre-tapped aerial coil. I do not really want an H.F. valve, as there are plenty of stations to satisfy anybody on the present arrangements.

(Continued on page 1100.)

# POPULAR TRANSFORMER

The Brownie POPULAR Transformer is every bit as good as it looks. Its purity of amplification gives vivid clarity throughout the full musical range, while its sturdy British construction ensures that it will give this quality of reproduction not just now and then, but always. It costs only 9/6, and does the work of transformers at double its price.

BROWNIE WIRELESS CO. (G.B.) LTD.  
Nelson Street Works, London, N.W.1



**"BUILD YOUR OWN DRY BATTERIES"**  
A NEW WIRELESS HOBBY.  
We supply super capacity Dry Cells and all parts for building your own dry battery at home. This is the best and cheapest form of H.T. yet offered. Super Capacity Cells, each 1.5 volts, 22 milliamps. 3/6 per doz. Send 1d. stamp for Booklet, "How to Build a Dry Battery at Home," to THE LEYTON BATTERY CO., 305, Church Road, Leyton, E.10.

**GRAMOPHONES.** Latest Horns and parts. Catalogue free. Cash or terms. Build £12 model for £3. Instructions 3d. **V. BURT, 185, High St., London, S.E.8.**

## WIRELESS

A NEW WIRELESS WONDER  
**THE "TROUBLE TRACKER"**

Will find that fault in a flash. Keep your set always in perfect working order. Invaluable if you are building your own set. The surest way of testing valves and other components.

**5/-** POST FREE (with full instructions)

Absolutely reliable and foolproof.

**BRODELL & CO.,**  
(Dept. P.W.) 16, PRAED STREET, LONDON, W.2.



PLEASE MENTION "POPULAR WIRELESS" WHEN REPLYING TO ADVERTISEMENTS.

Your panel should be PAXOLIN. The appearance and performance of your set will then give you the satisfaction you deserve.


# WEARITE COMPONENTS

An improved line.


Rheostats 1/6 to 2/-  
 Potentiometers .. 2/6  
 Volume Controls 4/-  
 Can also be supplied for base-board mounting. 3d. extra.



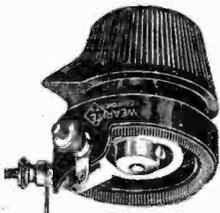A.C. Valve Holder  
 also for 3 electrode  
 valves, 1/3 each



Wave  
 Change  
 Switch,  
 1/6 each

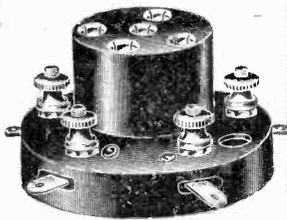

Write for illustrated lists.

**WRIGHT & WEIRE LTD.,**  
 740, High Rd., Tottenham, N.17

143

## The Men who fail and why!

By J. A. R. CAIRNS

For this week's ANSWERS London's most experienced and human magistrate has written the most helpful article of the year.

There is also time to enter for ANSWERS record **£12 A WEEK FOR LIFE CONTEST** Rules, Free Coupon and Full Particulars in TO-DAY'S

# ANSWERS

Buy Your Copy TO-DAY - - 2d.


## DOUBLE THE VOLUME of your LOUD-SPEAKER

Fit a P.R. Moulded Paper Cone to your speaker and you will be positively amazed at the difference. Double the volume and much greater purity in tone. All the notes come out in their correct value. No resonance—no "drumming"—just pure and real music.

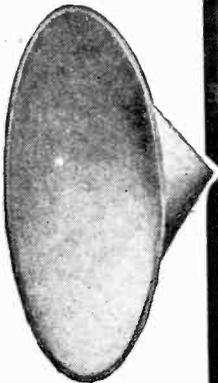
**3/6**

Post 4d.  
 THE PAPER WHICH HAS IMPROVED SPEAKERS ALL OVER THE WORLD.

The P.R. Cone is the only one which correctly reproduces the human voice as well as instrumental music. That is why it will improve any cone speaker, no matter the make or price 11 in. diameter, correctly proportioned, ready to fit, complete with washers and screws. Can be adjusted instantly. No cutting, sticking or wash leather required.



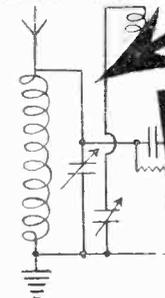Sent C.O.D. if desired. Telephone: City 378  
**P.R. PRODUCTS** (Dept. C7), P.R. House, Newgate Street, London, E.C.4. Opposite Post Office tube



**"GOLSTONE" 1930 DUAL WAVE COIL**  
**MOST EFFICIENT PRODUCED**  
**Price 8/- Each**

Designed and recommended to obtain maximum selectivity, to comply with new Regional requirements. More efficient and convenient than old-fashioned Plug-in coils. Just switch over from High to Low Wave band. Reaction on High and Low Wave lengths is fully obtained. Range 200-600 and 1000-2000 metres.

No. D.W/8 8/- each.


From all first-class Radio Dealers. Refuse substitutes. If any difficulty write direct.

**Ward & Goldstone**  
PENDLETON & MANCHESTER LTD.

Full particulars see Radio Catalogue just issued. FREE on request.



## it's easy as A.B.C.

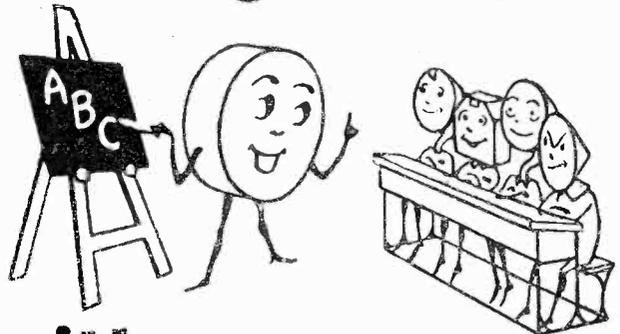

# with FLUXITE

FLUXITE is sold in tins, price 8d., 1/4 and 2/8. **SOLDERING SET Complete**


Another use for Fluxite: **Hardening Tools and Case Hardening.**

Ask for leaflet on improved methods.

**7/6** or LAMP only

**FLUXITE LTD.**

(Dept. 324), Rotherhithe, S.E.16.

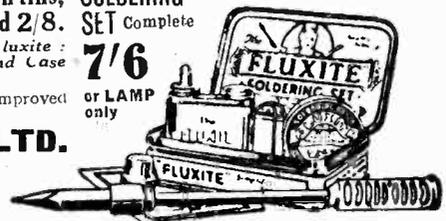

**- IT SIMPLIFIES ALL SOLDERING**



# BULGIN

BRITISH MADE




*The choice of critics*

## CIRCUIT DIAGRAMS!

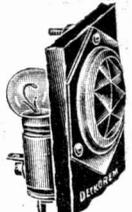
**CHOKES.**

We make H.F. and L.F. Chokes of the highest efficiency, the inside construction of which will bear the closest investigation. All necessary concealed parts are of the same high quality workmanship as the exteriors.


Our catalogue contains 24 diagrams of connections dealing with our components, also helpful hints to constructors.



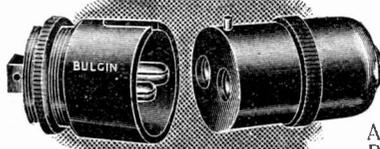**SIGNAL LAMP.**  
A brilliant Ruby Reflector with highly nickel-plated mount and lamp-holder fitting. Indicates when set is switched "On" 1/6 or "Off." Pair 1/6. 06 Bulbs 6d. each.



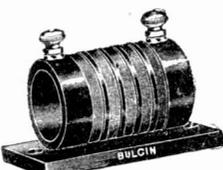**SAFETY MAINS PLUG.**  
A foolproof mains connection of polished bakelite, entirely shock proof, non-reversible, and made to correct electrical specifications. Suitable for eliminators and other mains apparatus. Complete 2/6



**SHORT WAVE CHOKE.**  
8 to 80 METRES. GUARANTEED 3/-. Complete 2/6

Send 2d stamps for our new 56 page illustrated catalogue and radio manual.

**A. F. BULGIN & CO.,** 9, 10, 11, CURSITOR STREET, CHANCERY LANE, LONDON, E.C.4.  
— Radio Manufacturers — Telephone: Holborn 1072 and 2072


## RADIOTORIAL QUESTIONS AND ANSWERS

(Continued from page 1098.)

"Having proved what 'P.W.' Query Department has done in the past, I put myself entirely in your hands, hoping that you will use as many of my own components as possible, of which I include a list. (I am also returning the theoretical diagram you sent me which shows the circuit is a det-2 L.F. and gives the date if you want to refer to other diagram.)"

## POPULAR "WIRELETS"

Here is the answer to No. 1

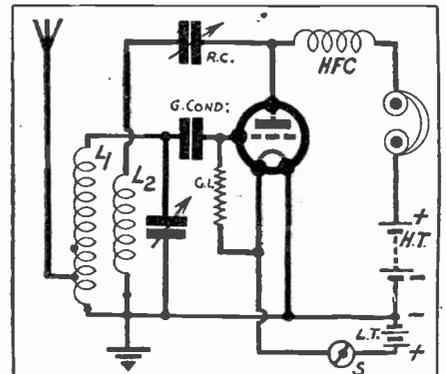

**DID YOU GET IT RIGHT?**  
(Wirelet No. 2 appears next week.)

## SATISFIED?

Are you satisfied with the results of your Set? If not, why not reconstruct or build a new Set?

### EVERYTHING WIRELESS ON EASY TERMS

Mullard Orgola, Cossor Melody Maker, "P.W." Kits, Climax H.T. Units, and all Components. Cut out interference with the WATMEL WAVE TRAP. Price 8/6 post free by return. Call or send list of requirements.

QUOTATIONS OF OUR best monthly terms  
by return of post. Catalogue on request.

**The P.D.P. Co. Ltd.** (Dept. P.W.)  
121, CHEAPSIDE, LONDON, E.C.2.  
Telephone: National 9846



### KAY'S CABINETS

This Cabinet soundly constructed of Oak and equipped with Baseboard Runners. Fall Front, Hinged Top Polished rich Jacobean, 36" high. For panels up to 18" wide 45/-. Also made to accommodate any Popular Set. Greatest Range of Wireless Cabinets. Illustrated Lists Free

**H. KAY Cabinet Manufacturer,**  
Mount Pleasant Road, London, N.17  
Phone: WALTHAMSTOW 1626

**UNWANTED RADIO PARTS** taken in part payment for new. A fair cash balance must be paid. State absolute lowest price acceptable for your goods, as offers cannot be made, and new goods required. We guarantee to supply only brand-new goods. No risk with—  
**RYALLS RADIO, 182, Kennington Rd., London.**



### WET H.T. BATTERIES

Solve all H.T. Troubles.  
**SELF-CHARGING, SILENT, ECONOMICAL JARS** (waxed), 2 1/2" x 1 1/2" sq. 1/3 doz. ZINCS, new type 10d. doz. Sacs 1/2 doz. Sample doz. (18 volts), complete with bands and electrolyte, 4/1. post 3d. Sample unit, 6d. illus. booklet free. Bargain list free.

**AMPLIFIERS, 30/-.** 3-VALVE SET, 25/-.  
**P. TAYLOR, 57, Studley Road,**  
570-KWELL LONDON

**PLEASE MENTION "POPULAR WIRELESS"  
WHEN REPLYING TO ADVERTISEMENTS.**

## Receiver Sale

**Electradix Clearance Bargains of Broadcast Receivers and Speakers at a fraction of cost. Cannot be sent on approval at these sacrifice prices. Valves and Batteries extra. Cannot be repeated when stock sold.**

- One-valve Sterling, steel-clad units with coil holders, 139/153, 15/-. Valve, 3/6.
- Marconiphone 1 Valve and Detector RB10 with valve, 17/6. 1 Valve TMC and Etesca, 17/6. Valve, 3/6.
- 2 Valve Ditto, RB10 H.F. and L.F., enclosed in leatherette covered Cabinet, 35/-. Ditto, 2 L.F. 35/-. Valves, 7/-.  
2 V. Trench BMKII short-wave, 30/-. Valves, 7/-.  
3 V. R.A.F. Aircraft, portable, 27/6. Valves, 7/-.  
3 V. Sterling, Desk type, 50/-. Valves, 10/6.
- 4 Valve Polar, H.F., Det., and 2 L.F., vertical pol. Maho, 70/-. Valves, 14/-. 5 Valve R.A.F. 10, with valves, oak American type Cabinet, 80/-. Aircraft model, 40/-. Ditto without remote control, 40/-. R.A.F. 7v. Receiver-Amplifier, 60/-. Marconi No. 55 7-valve H.F. screened No. 39, 60/-.  
**Power Amplifiers for grammo-motors and Western Electric 2-valve mahogany case, 45/-. Sterling ditto, 45/-. W.D. M.K.IV, 40/-. Sterling 1-valve, 15/-. Panatropes for D.C. mains, 65/-.  
**Loud Speakers, Horn, Small NK, 5/-. Assorted, all sizes, 10/-, 15/-, and 20/-. Amplion AR58, new, minus horn, 12/6. Brown's H3 Loud Speakers, List £3. Sale 27/6. Brown's H3Q Speakers, List £3 5s. Sale 30/-. Brown's Disc Speakers, List £5 5s. Sale 45/-. Brown's Cabinet Speakers, List £6 6s. Sale 48/6. Western Electric, 12/-. Exponential curled in Tone Chamber, 10 in. by 8 in. Sale 28/-. Reed-diaphragm Balanced Units to match, 17/6. Gilman & Zampa Cone and Chassis, 7/6.****

**300 CABINET LOUD SPEAKERS.** The famous Violina, all mahogany, 2,000 ohms. Perfect reproduction high to bass. All new List £5 5s. Sale 22/6. Baker Texas Cone Speakers, plated frame, 17/6. Hegra, 14/-. Reed type Units, for Portables, 5/-. Skinder, 5/6. Cones, 2/6. Powerful 4-pole Double Acting Magnetic Units 8/6; usually 12/6.

**ELECTRADIX RADIOS,**  
218, Upper Thames Street, E.C.  
Blackfriars Sta., Met. Rly. City 0191.

We do not think there is any need in your case for an extra valve, as you should be able to get all the selectivity required by means of one extra tuning circuit. You will need your present aerial coil-holder and aerial tuning condenser left in position, and, in addition, you will require another .0005-mfd. variable condenser, another tuning coil, and two neutralising condensers, all of which are included in your list of parts on hand.

Arrange the new tuning condenser well away from the aerial condenser, and place the new coil-holder behind it, so that the two circuits are not magnetically coupled. Put a new aerial terminal near to this new tuned circuit, and mount the two neutralising condensers between the old aerial coil-holder and the new one.


Now wire up as follows: From the old earth terminal of the receiver (which will still remain the earth terminal) run a wire to one side of the new

(Continued on page 1101.)

## RADIOLA

for YOUR SET!

## SPEAKER and batteries

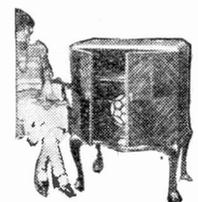

NOTE.—Improved Baffle and sound chamber as used in "P.F.5." "All-Electric Two," etc.

**For ALL Sets or Radio-Gram**  
The sort that people desire to possess and keep. Graceful design—sound construction—hand finished (piano finish), snug, compact, adding to the life of your set.

Over 3,000 delighted clients.  
(Used by Radio Press—by W. James, Percy Harris, etc.)

**For your own set!**  
"Radiola" de luxe, from £5 50 to £11 11 0  
"Popular" Oak Model, from £3 15 0  
Cash or easy payments.  
Sent ON APPROVAL—direct from the makers  
If you wish to part with it we will willingly refund FULL MONEY.  
Photographs and full particulars FREE!

**PICKETT'S, RADIO FURNITURE MAKERS,**  
"P.W." WORKS, BEXLEY HEATH, KENT  
Established since the beginning of Broadcasting.

## RADIOTORIAL QUESTIONS AND ANSWERS

(Continued from previous page.)

coil holder and to the moving vanes of the new condenser. The remaining side of the new variable condenser is joined to the new aerial terminal and also to the vacant side of the new coil holder and to the first neutralising condenser.

The other side of the neutralising condenser is joined to the second neutralising condenser, and finally the remaining terminal on the second neutralising condenser is taken to that side of the old aerial coil and aerial tuning condenser which is connected to the grid condenser.

This completes the new wiring, and you can vary the selectivity of the arrangement and the sharpness of tuning by adjusting the size of the neutralising condenser. If the arrangement seems too sharp, cut out one of these neutralising condensers by means of

### WHAT DO YOU THINK ABOUT THIS?

Here is a problem that puzzled a Brighton reader of "P.W."

The set was a home-made 3-valver (Det. and 2 L.F., 1 stage Resistance, 1 Transformer), and had been in use for 18 months, with no trouble.

Quality had always been good until one day it "went off," the set got very weak, and reaction failed to act.

Checked all plate voltages—O.K.

Checked all fil. voltages—O.K.

Grid bias, earth and aerial, loud speaker, condensers, coils, and all leads, etc., in perfect order. All joints, etc., inside set tested and found O.K.

### WHERE WAS THE FAULT?

N.B.—There is no prize for answering this, but from time to time we shall give a radio problem (followed the next week by the answer) in the hope that readers will find them both interesting and instructive. (Look out for the solution to above next week.)

*The fault in the Birmingham reader's outfit, that was described last week, was found to be in the loud speaker. It had merely gone out of adjustment and our reader tested everything except that!*

a shorting link or plug, and try the effect of using only one of them. But situated as you are, we expect that two will be necessary.


By means of a little juggling with coils, you should be able to get the two tuning dials to read alike, so that readjustment for any given station will be quite easy, and you will still have a big bag of programmes which now will be easily separable from one another

### DON'T BUY ANOTHER RAZOR BLADE!

Money & postage returned if **MINIT STROPER** will not sharpen perfectly one Gillette blade 500 times 1/6 post free—**RAZORS (P)**, 125, Heathfield Rd. Birmingham

### PARAMOUNT TRIPLE CONE

WITH TUNABLE CONES

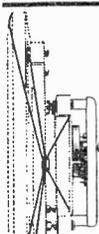

16 • 18 • 6	Chassis .....	2 5 0
	and Unit .....	3 10 0
	Complete in Oak Cabinet	4 10 0
BEAUTIFUL NATURAL REPRODUCTION.	Chassis .....	3 0 0
	and Unit .....	4 10 0
22 22 8	Complete in Oak Cabinet	5 10 0
	Console Cabinet	10 10 0

Chassis Model takes any Unit. All Chassis Safe Covered.

Prov. Pat. No. 33457 29 FROM YOUR DEALER OR

**PARAMOUNT REPRODUCERS**  
153 Devonshire St. Sheffield



## KITS AND SETS

### Our Test Room is Yours

Every Pilot Kit contains a leaflet describing our special free Test Room Service, available to all Pilot customers. Buy from the pioneer firm who guarantee good results.

### We Guarantee You Perfect Results

**PILOT KITS INCLUDE** all specified components, necessary coils, drilled panels and requisite connecting wires, screws, etc. "A" Kits include also specified valves and cabinet, whilst "B" Kits exclude these items.

	A KITS		B KITS	
	CASH PRICE	Or 12 monthly instalments of	CASH PRICE	Or 12 monthly instalments of
MAGIC THREE	£9 8 1	17/3	£6 9 7	11/10
MAGIC FOUR	£13 11 0	25/8	£9 6 8	17/1
TWIN WAVE THREE	£9 13 9	17/6	£6 3 3	11/3

Any parts supplied separately. Details lists on application

### IMMEDIATE DELIVERY to all approved orders

**FINISHED INSTRUMENTS.** All the most popular "P.W." sets—including the above—are available as finished receivers, built in our own factory and aerial tested and guaranteed. Full details on application.

## The MAGIC RADIOGRAM

(See this issue.)

### Build your MAGIC THREE into the ADAPTARAM

Specification: Garrard double-spring motor, with twelve-inch turntable, B.T.H. pick-up, double balance armature speaker, handsome oak cabinet, French polished, antique finish. Height, 5 ft.; width, 23 in.; depth, 17 in.

**Price £12 • 19 • 6**

or first payment of 39/6 and eleven monthly payments of 12/-. Can be supplied without loud speaker if desired.



# Peto-Scott

1920-1930

Co., Ltd.

Qualified engineers in attendance at all our branches.

77, City Road, London, E.C.1. Telephone: Clerkenwell 9406-7-8. 82, High Holborn, London, W.C. Telephone: Chancery 8266. 4 Manchester St., Liverpool. Telephone: Central 2131. 33, White-low Road, Chorlton-Cum-Hardy, Manchester. Telephone: Chorlton-Cum-Hardy 2028.

Mail coupon in unsealed envelope under gd. stamp.

### COUPON.

Please send me your 48-page Illustrated Catalogue, describing the 1929-30 products of all the leading makers.

NAME.....


ADDRESS.....

P.W., 1/2.

## The Easy Way

TO PERFECT RADIO

**BUILD YOUR KIT INTO**

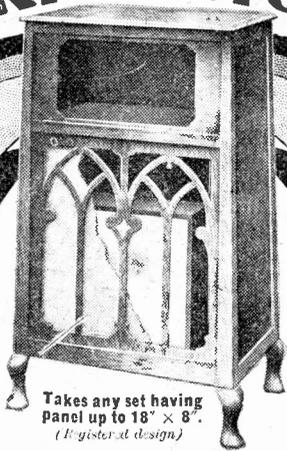

Takes any set having panel up to 18" x 8".  
(Registeral design)

**THIS MAGNIFICENT VOX KIT CONSOLE**

**Holds both Speaker and Set!**

Combines this advantage with unusually attractive appearance. Handsome overlays are supplied to suit almost any receiver. With or without speaker. Attractive art brown silk is fitted in either case. When ordering, specify type of set you propose fitting into cabinet. The speaker is the famous ULTRA Double Line Diaphragm Air Chrome type K. Chassis giving superb results at all frequencies.

**PRICES:**

With Speaker.	Without Speaker.
Oak - - £8 17 6	Oak - - £4 4 0
Mahogany 7 7 0	Mahogany 4 13 6


Stockists all over England. Write for full details and name of nearest stockist to:

**THE BRITISH RADIO GRAMOPHONE CO., LTD.,**  
77, City Road, LONDON, E.C.1.

**-EASY PAYMENTS**

The first firm to supply Wireless parts on easy payments. Five years advertiser in "Popular Wireless." Thousands of satisfied customers. Send us a list of the parts you require, and the payments that will suit your convenience, and we will send you a definite quotation. Anything wireless.

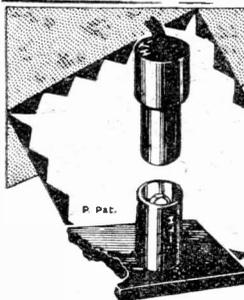**H. W. HOLMES, 29, FOLEY STREET**  
Phone: Museum 1414 Gt. Portland St., W.1



**BOTH PLUG & SOCKET COMPLETELY INSULATED**

Shocks impossible—the essential Plug and Socket for Mains-operated sets, and wherever fool-proof connections are needed. Engraved name on both parts—ample contacts—ease of fixing. Equip your set or eliminator with them.

The first Plug and Socket in which both parts are engraved and entirely insulated when connected or disconnected.

9d.  
(Panel portion, 3d. Flex portion, 6d.)  
Ask your dealer, or send to us, for Belling-Lee Handbook, "Radio Connections."

**BELLING-LEE**  
FOR EVERY RADIO CONNECTION

Advt. of Belling & Lee, Ltd., Queensway Works, Ponders End, Middlesex.

**TECHNICAL NOTES.**

(Continued from page 1076.)

telegraphone, and very great improvements were made in it. The principal experimenter in this direction being a German scientist Dr. Stille.

This inventor has produced a totally new type of recording and reproducing machine for the magnetic wire or tape, and has brought the telegraphone system to a state in which it can be, and indeed has been, used for talking pictures.

The wire passes through the machine from one spool to another, in somewhat the same way as the film in a cinematograph projector, the actual speed of the wire being about 6 ft. per second. During its progress from the one spool to the other it passes between the poles of an electro-magnet; the speech currents to be recorded are fed into the windings of this electro-magnet.

In this way, as you will see at once, the wire is magnetised at each point to an intensity depending upon the strength of the speech currents in the magnet windings, at the moment when that particular part of the wire was in transit between the poles.

It is easy to see that by passing the wire through again in the same way currents will be induced in the windings of the electro-magnet (exactly as in an electrical "pick-up"), and these currents are led away, amplified in the usual manner, and reproduced through a loud speaker.

**Using the Record Again.**

The same wire may be used repeatedly and the magnetic "impression" may be removed by running the wire past a suitable magnetic arrangement which "washes out" the magnetic impressions already upon it.

This is a feature which makes the arrangement very suitable for the talking-picture studio, since the record obtained is instantly ready for reproduction. The director, therefore, can tell at once whether the recording conditions are to his liking.

The reproduction from the wire or tape is claimed to be superior to that from other more conventional types of record, and a particular claim is made with regard to the recording and reproduction of very high and very low frequencies which, of course, have so important an effect upon the quality of the reproduced sound.

If the wire or tape should happen to be broken, or if it is desired to piece together different recorded selections, joints can easily be made by a simple soldering process.


**Permanent Magnetism.**

You might think that when the wire was wound upon a spool with the turns touching one another, the magnetisation would be destroyed, but apparently this is not the case. A still more simple feature is that the wire or tape, after being magnetically "recorded," can actually be heated to a high temperature without obliterating the magnetic record.

Naturally this is not a matter of any great practical importance—I mean the heating—as it pre-supposes a condition not likely to arise in practice; at the same time it indicates how tenaciously the magnetic effect is retained.

(Continued on next page.)

**PORTABLE CASES**

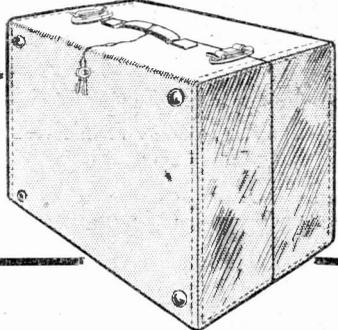

**BEST QUALITY**  
ALL FITTED WITH PAKAWA HANDLES, PATENT FASTENERS AND LOCKS


14 1/2" x 12" x 4 1/2". LID 4 1/2" DEEP  
**LEATHER - - 34/-**  
**REXINE - - 22/6**

14" x 14" x 5". LID 4" DEEP  
**BLACK REXINE - - 20/-**  
Carriage Extra.

**HENRI & CO.**  
79, ROCHESTER ROW, VICTORIA, S.W.1.  
Tel.: VICTORIA 436r.

**NEW SUPER-MICROPHONE CRYSTAL AMPLIFIER**

(Patent applied for)

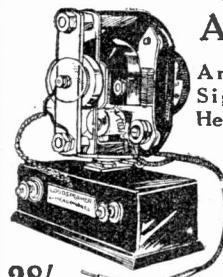

Amplifies weak Signals to good Headphone Strength and good Headphone Strength to good Loudspeaker Volume.

Requires only one or two Dry Cells to work. No other Accessories needed. Robust Construction. No Fragile Parts.

Initial Cost and Upkeep very much less than a Valve Amplifier of the same Volume.

Directions for use, free.

**FREDK. ADOLPH, Actual Maker** Phone: Museum 8329.  
27, Fitzroy Street, London, W.1.

**"TWIN MAG" 29/6**



A Double Magnet super permanently balanced armature unit—giving magnificent reproduction. Ideal for linen diaphragm speakers. If your dealer does not stock it do not accept a substitute—we will send C.O.D.

Write for fully descriptive leaflet.

**GOODMANS**  
27 FARRINGTON ST. LONDON, E.C.4  
Telephone: City 4472.

PLEASE MENTION "POPULAR WIRELESS" WHEN REPLYING TO ADVERTISEMENTS.

**TECHNICAL NOTES.**

(Continued from previous page.)

**Improving Selectivity.**

In connection with the improvement of the selectivity of a set, a matter to which I have referred once or twice lately, probably you know that with the grid-leak method of rectification there is usually a tendency for the tuning to be flatter, that is, to lack selectivity. In the usual way the detector is connected to the top of the grid coil, and when this is the case the voltages arising in the detector circuit are to some extent reduced. This is due, of course, to the damping which is in this way introduced into the circuit.

If, however, the connection to the detector is shifted from the end of the grid coil to some other point on that coil, it will probably be possible, after a certain amount of trial, to find a position where, without much interference with the signal strength, a much improved selectivity is obtained.

The improvement obtainable in this way will naturally depend upon the capabilities of the set when it is working under the most efficient conditions: if the set is inherently inefficient (owing to bad design, bad components or what not) the improvement obtainable either in the above-mentioned way or any other way may not be significant.

For instance, in the present case, if the grid coil is not functioning properly, no doubt you will get very little, if any, improvement in selectivity by the little dodge which I have mentioned. But under certain conditions this little alteration of the circuit may prove worth while.

**Leaks and Condensers.**

Talking about grid leaks and condensers, I should add that it is not always possible to say offhand what will be the best value for the resistance of a grid leak and the capacity of the grid condenser in any particular case.

I know that certain standard or average values are commonly recommended, but it is clear that the values must depend upon circumstances and, therefore, that a little experimenting will be necessary to determine the best possible values.

For instance, with the conventional 2-megohms grid-leak and .0003 mfd. for the condenser the quality of the reproduction may not be so good as when the capacity of the condenser is somewhat reduced.

Again, the value of the grid leak depends upon the strength of signals which it is intended to handle, and for strong signals you should certainly use a lower value of grid-leak. It is a well-known fact that if strong signals are being handled with high value of grid leak there is a tendency for the detector to become badly choked.

**Effect of Signal Strength.**

Another reason why it is impossible to make any hard-and-fast rule with regard to grid-leak and condenser values is because, even for a given circuit and given components, there are slight variations in the characteristics of the components, particularly the valves.

Even in these days of scientific valve manufacture it is impossible to turn out valves of absolutely constant characteristics, and slight variations in characteristics may necessitate corresponding adjustments in

(Continued on next page)

**GET PENTODE VOLUME FROM BATTERY POWER**

**AMPLIFICATION FACTOR 90**

**AMPLIFICATION FACTOR 90**

**AMPLIFICATION FACTOR 90**

**Use the New Lissen Power Pentode Valve for L.F. Amplification**

**LISSENS NEW POWER PENTODE BATTERY DRIVEN 176**

P.T. 225.

The new conception in valve design. The big volume valve, yet working off dry batteries. Giving tremendous volume from small incoming signals—with purity. Any set with one stage of L.F. amplification is vastly improved by the new Lissen Power Pentode. No alteration of wiring necessary. Put it in the L.F. stage (its amplification is so great that it is not recommended when there are two L.F. stages in any set). It takes only 7 milliamps of current, therefore imposes no heavier drain on your batteries than any ordinary L.F. valve, yet gives tremendous volume.

Instead of buying a Power Valve, next time buy one of the new Lissen Power Pentode Valves—it will improve your set out of all recognition. It goes straight into your set without alteration.

**OTHER TYPES AND PRICES.**

- H.210 R.C. and H.F., 10 6.
- H.L.210 General Purpose, 10 6.
- L.210 L.F. Amplifier, 1st stage, 10 6.
- P.220 Power Valve, 12 6.

**LISSEN LTD.**

**Worple Road, Isleworth, Middlesex.**  
 Factories also at Richmond (Surrey) and Edmonton. (Managing Director: T. N. COLE)

# The Easy Way TO PERFECT RADIO

In addition to their own extensive range, PETO SCOTT offer YOU Every Known Radio Receiver or Component—all on

## EASY TERMS with SERVICE AFTER SALES

The following list is merely representative, and we ask you to fill in the coupon below, or send us a list of your requirements.

- OSRAM MUSIC MAGNET. Cash £9 0s. 0d., or 12 monthly payments of 16/6. Valves included.
- COSSOR 1930 THREE-VALVE KIT. Cash £8 15s., or 12 monthly payments of 16/-.  
EXIDE 120-volt H.T. Accumulator TYPE W.J., in crates. Cash £3 15s. 0d., or 12 monthly payments of 6/11. TYPE W.H., 120 volts, in crates. Cash £4 13s. 0d., or 12 monthly payments of 8/6.
- REGENTONE W.I.B. S.G. (A.C. Mains). For S.G. and Pentode Sets. Cash £4 19s. 6d., or 12 monthly payments of 9/2.
- CELESTION C.12 LOUD SPEAKER, in oak. Cash £5 12s. 6d., or 12 monthly payments of 10/4; in Mahogany, £5 17s. 6d., or 12 monthly payments of 10/9.

### SPECIAL OFFER

Double linen diaphragm air chrome speakers in oak or mahogany table model cabinets of handsome appearance. These speakers have been specially made for us, and the cabinets are so designed that they ensure the utmost purity and depth of tone from the ULTRA Type K Chassis, which is incorporated.

SPECIAL PRICE **£4-4-0**

or send only 7/6 and balance by 11 monthly instalments of 7/6.

STANDARD WET H.T. 144-volt Battery. 10,000 m/a, absolutely complete. Cash £4 0s. 0d. or 12 monthly payments of 7/4. All parts for these batteries available.

## PETO SCOTT LTD.

Free Demonstrations and advice by Qualified Engineers at our Shops—  
77, CITY ROAD, LONDON, E.C.1. Telephone: Clerkenwell 9406-7-8.  
62, HIGH HOLBORN, LONDON, W.C.1. Telephone: Chancery 8266.  
4, Manchester Street, Liverpool. Telephone: Central 2134.  
33, Whitelaw Road, Chorlton-cum-Hardy, Manchester. Telephone: Chorlton-cum-Hardy 2028.  
Mail coupon in unsealed envelope under 1d. stamp.

### COUPON

Please send me your 48-page Illustrated Catalogue, describing the 1929-30 products of all the leading makers.

NAME.....  
ADDRESS.....

F.W. 1/2

### REPAIRS

Any make of L.F. Transformer, Loudspeaker or Headphones repaired and despatched within 48 HOURS—TWELVE MONTHS' GUARANTEE with each repair. 4/- post free.

Transformer Repair Co.,  
"Repairs" Dept.,  
214, High Street, Colliers Wood, London, S.W.19.

### "KLEER-KUT" COILS

FOR WAVE-TRAPS OR ANY POSITION WHERE PLUG-IN COILS ARE SPECIFIED.  
"Equal to any I have had—many at 3 times the price."  
"I am thoroughly satisfied. They are very strongly made."  
"I have tuned in 20 stations on the loud speaker, using the coils you supplied, in my 'Magic' 3."  
25. 30. 35. 1/-, 40. 50. 1/2, 60. 75. 1/3, 100. 125. 150. 1/6, 175. 1/9, 200. 2/-, 250. 2/3, 300. 2/6.  
Centre Tapped 6d., "X" Coils 1/- extra.

THEY SAVE YOU MONEY.  
FREE! FREE! Wiring diagram and instructions for making 2 Wave-traps sent free with all orders for Plug-in Coils.  
L. BRUCE, 99, King Henry's Rd., LONDON, N.W.3  
6 years coil maker to the Wireless Trade.  
Phone: Primrose 1303. Trade supplied

## TECHNICAL NOTES.

(Continued from previous page.)

the circuit such as, in the case we are considering, a somewhat different value of grid leak and condenser.

### Anode-Bend Rectification.

Following the above remarks on grid-leak rectification, I should like to say something about anode-bend detection and the question of overloading.

One of the simplest ways of noting whether the anode-bend detector is being overloaded is to introduce into the output circuit a suitable milliammeter; this meter may be one reading up to, say, 5 milliamps, although, of course, the current actually registered in the case in question will be much less than this maximum amount.

It is important to choose the grid bias so that the current passing through the detector anode circuit when no signals are being received is as small as possible. Then when signals are tuned in, the current will increase very considerably, and this increase depends naturally upon the strength of the transmission which is being received.

### Watch the Meter.

Whilst you have the station tuned in, you should note very carefully not only the current indicated on the milliammeter but also the behaviour of the needle. As you tune in nearer and nearer to resonance you will find the current increase, but you may reach a point where the needle of the milliammeter begins to show unsteadiness and, in particular, where it gives little kicks as different sounds come through.

If this state of affairs is reached it indicates definitely that the anode-bend detector is being overloaded and, therefore, that the rectified signals are losing their quality and distortion is being introduced.

## EASY TERMS

We SPECIALISE in the supply of all Good Quality Radio Sets, Components and accessories on Easy Terms. We will give you efficient service. Send us your list of requirements and a quotation will be sent by return.

LONDON RADIO SUPPLY COMPANY  
11, Oat Lane, Noble St., London, E.C.2  
NATIONAL, 1927.

## "RED DIAMOND"


THE RECOGNISED DETECTOR FOR ALL CIRCUITS USING CRYSTAL RECTIFICATION.

RD 40

2/-



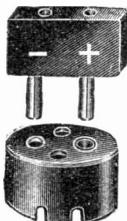Not affected by vibration. Each one is tested on broadcast before despatch, and is perfect.



## "RED DIAMOND" WALL PLUG

RD 29

2/-


Solid Ebonite, Highly Finished, Perfect Insulation. Two size plugs and sockets, so that it is impossible to insert plugs in reverse.

JEWEL PEN Co., Ltd.

(Radio Dept. 46), 21-22, Great Sutton St., LONDON, E.C.1.



## CLIX 21 VARIETIES

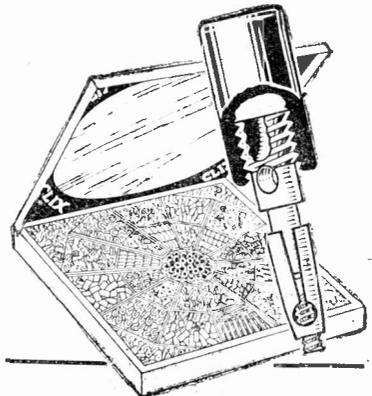

### No. 10. CLIX-LOX WANDER PLUG

Adjustable to fit any socket. A turn of the insulator locks it. Special short insulator. Red, Black, and Green 2 1/2 d.

The above is one of the many useful lines displayed in the Clix Showcase.

Supplied with engraved insulators




for 1d. extra. Full range of markings.

Look for the Clix Showcase on your dealer's counter. Write for descriptive leaflet: "A Matter of Connection."

LECTRO LINX LTD.,  
254, Vauxhall Bridge Road, S.W.1

## ELEX

### MOISTURE RETAINING EARTH BOWL

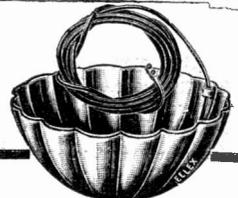

Collects and retains all available moisture—improves with age—immune from atmospheric conditions—that is the Elex "earth!" Supplied with 9 ft. rubber-covered lead and connector. Price 5/6 each. Write for list 'T' 89.

J. J. EASTICK & SONS,  
Elex House, 118, Bunhill Row, LONDON, E.C.1

### HEADPHONES REPAIRED 4/-

Transformers 5/-. Loudspeakers 4/-. All repairs re-magnetised free. Tested, guaranteed and ready for delivery in 24 hours.

Discount for Trade. Clerkenwell 9069.  
E. MASON, 44, East Rd., City Rd., N.1.

### CABINETS AT BARGAIN PRICES

Solid Oak Cabinets, well made and highly polished. American Type, Open Top, complete with Baseboard.  
12" x 8" x 8" 9/6 18" x 7" x 10"  
14" x 8" x 8" 21" x 7" x 10"  
16" x 8" x 8" 21" x 7" x 10" 12/6  
Postage and Packing 1/3 extra.  
Any size and shape made to order within 7 days.  
SEND NOW FOR NEW BARGAIN LIST.  
POST FREE. Phone: Terminus 6777.  
WEST CENTRAL RADIO SUPPLIES,  
259, Gray's Inn Rd., King's X, London, W.C.1

## EXACT TUNERS

250 to 2,000 metres. Thousands of these tuners are in use, and we can strongly recommend them. No further coils are required. Send P.C. for particulars and circuits, FREE.

THE EXACT MANUFACTURING CO.,  
Croft Works, Priory Place, Coventry.

PLEASE MENTION "POPULAR WIRELESS" WHEN REPLYING TO ADVERTISEMENTS.




**Certainly-  
experiment  
with your set**

**BUT NOT WITH  
the COMPONENTS**

*Always use the best—*

**BENJAMIN**

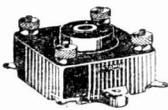

**VALVEHOLDERS.**

Clearer Tone .. .. .	2/-
Vibroholder .. .. .	1.6
5-Pin Holder .. .. .	1.9
Pentode .. .. .	2.3

**SWITCHES.**

Push-Pull .. .. .	1.3
Rotary .. .. .	1.9



**TURNTABLE.**



Full-bearing and equipped with hinged and folding legs .. 7/6

Send P.C. for fully illustrated 'cuffe' No. 2003.

**THE BENJAMIN ELECTRIC LTD.**  
BRANTWOOD WORKS, LONDON, N.17

**MAZDA  
P.625A**

**EFFICIENCY  
AND  
ECONOMY**

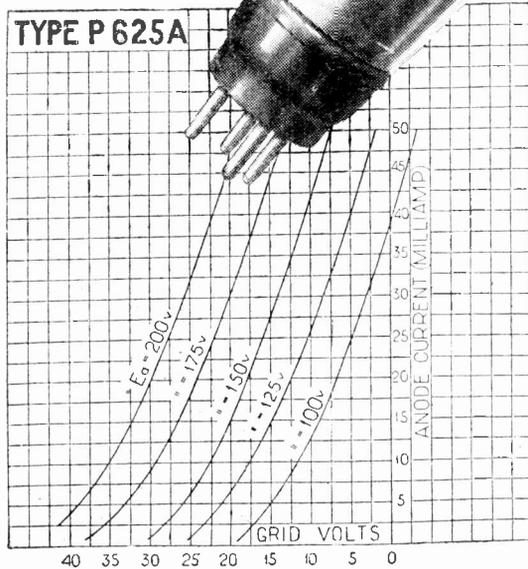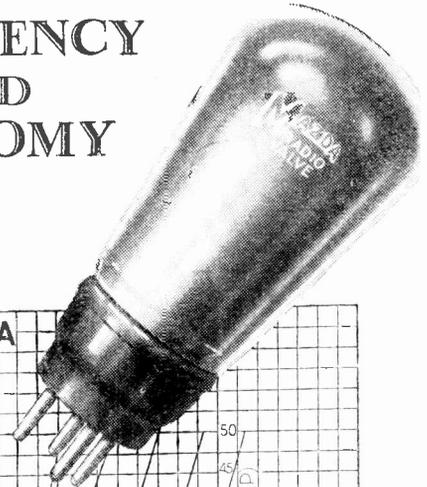

**MAZDA P.625a**

Type P625A is a super-power valve, and is capable of giving a high power output without distortion. It has been designed for operating cone and moving-coil type loud speakers. The volume obtained with this valve when used in the final L.F. stage is sufficient for most purposes, whilst the quality of reproduction over the whole of the musical range is bound to please all lovers of good music.

Those who desire a large volume of sound and better quality of reproduction should fit the valve in the final stage of their receivers.

These valves can be supplied matched for push-pull work.

**PRICE 15/-**  
The AMAZING


**MAZDA  
RADIO  
VALVES**

**THE EDISON SWAN ELECTRIC CO., LTD.**  
Ediswan Radio Showrooms:  
1a, NEWMAN STREET, OXFORD STREET, W.1.  
(\*Phone: Museum 9801.)  
Showrooms in all the Principal Towns. V.20.

The

# HYPERMITE

## L.F. TRANSFORMER

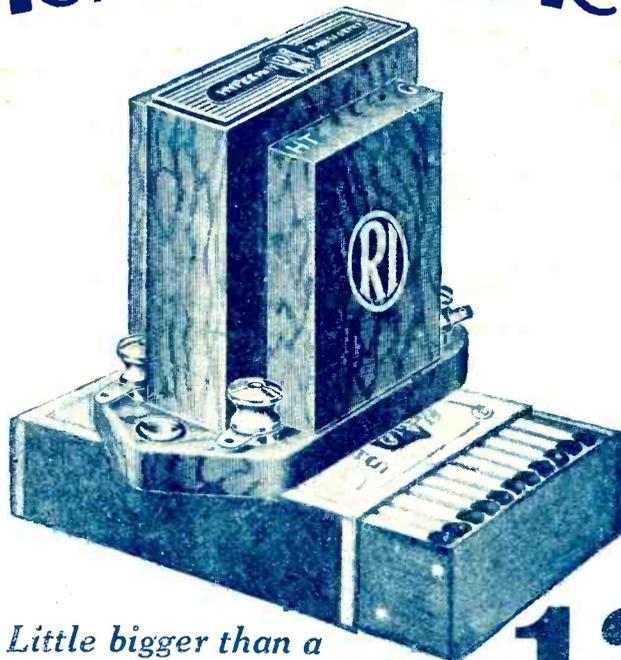

*Little bigger than a  
matchbox & weighs  
ONLY 7 OUNCES*

# 12/6

### PRIMARY INDUCTANCE OVER 50 HENRIES

Here at last is a transformer built with a CORE OF A NEW NICKEL ALLOY of enormous permeability, yet sold at a price which places it within the reach of the average home constructor.

The "Hypermu" at 21/- is, of course, the best transformer it is possible to buy, but the "Hypermite" gives an opportunity of acquiring at the popular price of 12/6 a modern transformer with a high inductance, which GUARANTEES THE RETENTION OF THE LOW FREQUENCIES WITHOUT SACRIFICING THE HIGH.

*A "Hypermite" leaflet with full diagrams, will tell you all about it. Ask your dealer for a free copy or send direct to the manufacturers.*

The name  on radio products is a guarantee of excellence throughout the world, and a comparison of this transformer with any of the bulky, expensive transformers will definitely establish its value.

A NICKEL ALLOY CORE is now recognised as an essential feature of modern intervalve transformer design. The "Hypermite" is an absolute boon to SET MAKERS, who are most enthusiastic with its performance. They have already placed contracts for the 1930 Season for PORTABLE SETS.



*The "Hypermite" will be one of the outstanding features of progress in Radio during the 1930 Season. Try it in your set. It justifies our claims.*

12, HYDE STREET, LTD LONDON, W.C.1.