

FREE SUPPLEMENT CHRISTMAS PROJECTS

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EVERYDAY

DECEMBER 2000

PRACTICAL

ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL £2.75

FREE CHRISTMAS PROJECTS SUPPLEMENT
Enhance your decorations with these four festive designs

NOW AVAILABLE TO BUY ON THE WEB
EPE
www.epemag.com



DUAL-PSU
A microcontroller in charge

Starter Project
STATIC FIELD DETECTOR
Check the charge on your friends/TV/car etc.



PLUS
News • Schmitt Triggers Part 2
Circuit Surgery • Ingenuity Unlimited



<http://www.epemag.wimborne.co.uk>

12v 18Ah SEALED LEAD ACID BATTERIES, new and boxed, unused pack of 4 £39.95 ref CYC7 or £15 each ref CYC6

AUTOMATIC CHARGER For the above batteries charges 2 at or re-charge level indicator circuitry 6 hour charge £10 ref CYC8

A new range of 12v to 240v INVERTERS

IV400S (400 watt) £89
IV800S (800 watt) £159
IV1200S (1200 watt) £219

ECG MACHINES 76v 10Ah BATT/24V 8A TX EX govt. ECG machines! Measures 390x320x120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connections on the rear including video out etc. On the front panel are two DIN sockets for connecting the body sensors to. Sensors not included. Inside 2 x 6V 10Ah lead acid cells (not in good condition), PCB's and a 8A/24V toroidal transformer (mains in, sold as seen, may have one or two broken knobs etc due to poor storage. £15.99 ref VP2

SODIUM LAMP SYSTEMS £75.70 Complete system with 250w or 400 watt SON-T Agro bulb, reflector with bulb holder and remote ballast and starter (uncased) all you need is wire. 250W system ref SLS1, 400W system SLS2.

PC SUPPORT HANDBOOK The ultimate technical guide to building and maintaining PCs. Over 460 AA pages packed with technical data and diagrams just £10 ref PCBK. If you want 4 copies for £33 ref PCBK2. Also available is a CD packed with diagnostic programmes to use with the book £5 ref PCBK1

D SIZE NICADS Tagged, 1200mA, 1.2v pack of 4 for £6 ref CYC9 or as a pack of 24 for £22 ref CYC10

D SIZE SEALED LEAD ACID BATTERIES

2v 2.5Ah rechargeable sealed lead acid battery made by Cyclon 60x45mm (standard D size) supplied as a pack of 12 or 20 giving you options for battery configurations eg 12v at 5Ah 24v at 2.5Ah 6v at 10Ah. These batteries are particularly useful in that you can arrange them in your project to optimise space etc (eg boat ballast etc) Pack of 12 £10 ref CYC4, pack of 20 £16 ref CYC5

HYDROPONICS DO YOU GROW YOUR OWN?

We have a full colour hydroponics catalogue available containing nutrients, pumps, fittings, environmental control light fittings plants, test equipment etc Ring for your free copy.

PC COMBINED UPS AND PSU The unit has a total power of 292 watts, standard mother board connectors and 12 peripheral power leads for drives etc. Inside is 3 12v 7.2Ah sealed lead acid batteries. Backup time is 8 mins at full load or 30 mins at half load. Made in the UK by Magnum, 110 or 240vac input, +5v at 35A, -5v at 5A, +12v at 9A, -12v at 5A outputs. 170x260x220mm, new and boxed £29.95 ref PCUPS2

ALTERNATIVE ENERGY CD, PACKED WITH HUNDREDS OF ALTERNATIVE ENERGY RELATED ARTICLES, PLANS AND INFORMATION ETC £14.50 REF CD56

AERIAL PHOTOGRAPHY KIT This rocket comes with a built in camera! It flies up to 500 feet (150 m) turns over, and takes an aerial photograph of the ground below. The rocket then returns with its film via its parachute. Takes 110 film. Supplied complete with everything including a launch pad and 3 motors (no film) £29.98 ref astro

PROJECT BOXES Another bargain for you are these smart ABS project boxes, smart two piece screw together case measuring approx 6"x5"x2" complete with panel mounted LED. Inside you will find loads of free bits, tape heads, motors, chips resistors, transistors etc. Pack of 20 £19.95 ref MD2

TELEPHONES Just in this week is a huge delivery of telephones, all brand new and boxed. Two piece construction - illuminated keypad tone or pulse (switchable) recall redial and pause high/low and off ringer switch and quality construction. Off white colour and is supplied with a standard international lead (same as US or moderns) if you wish to have a BT lead supplied to convert the phones these are £1.55 each ref BTLX. Phones £4.99 each ref PH210 off £30 ref SS2

3HP MAINS MOTORS Single phase 240v, brand new 2 pole 340x180mm 2850 rpm, built in automatic reset overload protector, keyed shaft (40x16mm) Made by Leeson £99 each ref LEE1

BUILD YOUR OWN WINDFARM FROM SCRAP New publication gives step by step guide to building wind generators and propellers. Armed with this publication and a good local scrap yard could make you self sufficient in electricity! £12 ref LOT81

CHIEFTAN TANK DOUBLE LASERS 9 WATT + 3 WATT + LASER OPTICS Could be adapted for laser listener long range comms etc. Double beam units designed to fit in the barrel of a tank, each unit has 2 semiconductor lasers and motor drive units for alignment 7 mile range, no circuit diagrams due to MOD, new price £50 000? us? £199. Each unit has two gallium Arsenide injector lasers, 1 x 9 watt 1 x 3 watt 900nm wavelength, 28vdc, 600hz pulse freq. The units also contain a receiver to detect reflected signals from targets. £99 ref LOT4

MAGNETIC CREDIT CARD READERS AND ENCODING MANUAL £9.95 Cased with flyleads designed to read standard credit cards! complete with control electronics PCB and manual covering everything you could want to know about what's hidden in that magnetic strip on your card! just £9.95 ref BAR31

SOLAR POWER LAB SPECIAL 2x 6"x6" 6v 130mA cells, 4 LED's wire buzzer switch + relay motor £7.99 REF SA27

SOLAR NICAD CHARGERS 4x AA size £9.99 ref 6P476

2 x C size £9.99 ref 6P477

BRAND NEW MILITARY ISSUE DOSE METERS

Current NATO issue Standard emergency services unit Used by most of the worlds Military personnel New and boxed Normal retail price £400. BULLS bargain price just £99! The PDRM 82 M is a portable lightweight water resistant gamma radiation survey meter to measure radiological dose rate in the range 0.1 to 300 centigrays per hour in air. The Geiger Muller (G M) tube detecting unit is energy and polar response corrected. The radiation level is displayed on a Liquid Crystal Display. The microcomputer corrects for the non-linearity of the G M tube response. The instrument is powered by three international C size batteries giving typically 400 hours operation in normal conditions. The dose rate meter PDRM 82M designed and selected for the United Kingdom Government, has been fully evaluated to satisfy a wide range of environmental conditions and is nuclear hard. The construction enables the instrument to be easily decontaminated. The instrument is designed for radiation surveys for post incident monitoring. Used in a mobile role, either carried by troops or in military vehicles for rapid deployment enabling radiation hot spots to be quickly located. Range 0 - 300 cGy/h in 0.1 cGy/h increments. Over range to 1500 cGy/h - indicates flashing 300. Accuracy 20% of true dose rate +0.1 cGy/h, 0 - 100 cGy/h 130% of true dose rate, 100 - 300 cGy/h Energy Response 0.3 MeV to 3 MeV - within 120% (Ra 226) 80 KeV to 300 KeV - within 140% (Ra 226) Detector Energy compensated Halogen quenched Geiger Muller Tube. Controls Combined battery access and ON/OFF switch. Batteries 3 International standard C cells. Weight 560 grams Operating Temperature Range -30deg C to +60 deg C indicators High contrast 4 digit LCD. Battery low indication Dose rate Rising/Falling £99 ref PDRM

Hydrogen fuel cells Our new Hydrogen fuel cells are 1v at up to 1A output, Hydrogen input, easily driven from a small electrocatalysis assembly or from a hydrogen source, our demo model uses a solar panel with the output leads in a glass of salt water to produce the hydrogen! Each cell is designed to be completely taken apart, put back together and expanded to what ever capacity you like, (up to 10watts and 12v per assembly. Cells cost £49 ref HFC11

PHILIPS VP406 LASER DISC PLAYERS, SCART OUTPUT, JUST PUT YOUR VIDEO DISK IN AND PRESS PLAY, STANDARD AUDIO AND VIDEO OUTPUTS, £14.95 REF VP406

SMOKE ALARMS Mains powered made by the famous Gent company, easy fit next to light fittings, power point. Pack of 5 £15 ref SS23 pack of 12 £24 ref SS24

4AH D SIZE NICADS pack of 4 £10 ref 4AHPK SENDER KIT Contains all components to build a A/V transmitter complete with case £35 ref VSXX2

10 WATT SOLAR PANEL Amorphous silicon panel fitted in a anodized aluminium frame. Panel measures 3' by 1' with screw terminals for easy connection. 3' x 1' solar panel £56 ref MAG46

12V SOLAR POWERED WATER PUMP Perfect for many 12v DC uses, from solar fountains to hydroponics! Small and compact yet powerful works direct from our 10 watt solar panel in bright sun. Max hd 17 ft Max flow = 8 l.p.m 1.5A Ref AC8 £18.99

SOLAR ENERGY BANK KIT 50x 6"x12" 6v solar panels (amorphous) +50 diodes £99 ref EF112 PINHOLE CAMERA MODULE WITH AUDIO!

Superb board camera with on board sound! extra small just 28mm square (including microphone) ideal for covert surveillance. Can be hidden inside anything, even a matchbox! Complete with 15 metre cable, psu and tv/r connector. £49.95 ref CC6J

SOLAR MOTORS Tiny motors which run quite happily on voltages from 3-12vdc. Works on our 6v amorphous 6" panels and you can run them from the sun! 32mm dia 20mm thick £1.50 each **WALKIE TALKIES 1 MILE RANGE £37/PAIR REF MAG30**

LIQUID CRYSTAL DISPLAY Bargain prices, 40 character 1 line 154x16mm £6.00 ref SMC4011A **YOUR HOME COULD BE SELF SUFFICIENT IN ELECTRICITY** Comprehensive plans with loads of info on designing systems, panels, control electronics, etc £7 ref PV1

AUTO SUNCHARGER 155x300mm solar panel with diode and 3 metre lead and cigar plug 12v 2w £12.99 REF AUG10P3

SOLAR POWER LAB SPECIAL 2x 6"x6" 6v 130mA cells, 4 LED's, wire buzzer switch + relay motor £7.99 REF SA27

SOLAR NICAD CHARGERS 4 x AA size £9.99 ref 6P476 2 x C size £9.99 ref 6P477

MINATURE TOGGLE SWITCHES These top quality Japanese panel mount toggle switches measure 35x13x12mm, are 2 pole changeover and will switch 1A at 250vac, or 3 A at 125vac. Complete with mounting washers and nuts. Supplied as a box of 100 switches for £29.95 ref SWT35 or a bag of 15 for £4.99 ref SWT34

VOICE CHANGERS Hold one of these units over your phone mouth piece and you can adjust your voice using the controls on the unit! Battery operated £15 ref CC3

BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.
BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE WITH ORDER PLUS £4.00 P&P PLUS VAT.
24 HOUR SERVICE £6.50 PLUS VAT.

OVERSEAS ORDERS AT COST PLUS £3.50 (ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

phone orders : 01273 203500
FAX 01273 323077
Sales@bull-electrical.com

30 WATTS OF SOLAR POWER for just £69, 4 panels each one 3'x1' and producing 8w, 13v. PACK OF FOUR £69 ref SOLX

200 WATT INVERTERS plugs straight into your car cigarette lighter socket and is fitted with a 13A socket so you can run your mains operated devices from your car battery. £49.95 ref SS66

THE TRUTH MACHINE Tells if someone is lying by micro tremors in their voice, battery operated, works in general conversation and on the phone and TV as well! £42.49 ref TD3

INFRA RED FILM 6" square piece of flexible infra red film that will only allow IR light through. Perfect for converting ordinary torches, lights, headlights etc to infra red output only using standard light bulbs. Easily cut to shape. 6" square £15 ref IRF2

33 KILO LIFT MAGNET Neodymium 32mm diameter with a fixing bolt on the back for easy mounting. Each magnet will lift 33 kilos. 4 magnets bolted to a plate will lift an incredible 132 kilos! £15 ref MAG33 Pack of 4 just £39 ref MAG33AA

HYDROGEN FUEL CELL PLANS Loads of information on hydrogen storage and production. Practical plans to build a Hydrogen fuel cell (good workshop facilities required) £8 set ref FCP1

STIRLING ENGINE PLANS Interesting information pack covering all aspects of Stirling engines, pictures of home made engines made from an aerosol can running on a candle! £12 ref STIR2

ENERGY SAVER PLUGS Saves up to 15% electricity when used with fridges motors up to 2A, light bulbs, soldering irons etc. £9 ea ref LOT71, 10 pack £69 ref LOT72

12V OPERATED SMOKE BOMBS Type 3 is a 12v trigger and 3 smoke canisters. Each canister will fill a room in a very short space of time! £14.99 ref SB3. Type 2 is 20 smaller canisters (suitable for mock equipment fires etc) and 1 trigger module for £29 ref SB2. Type 1 is a 12v trigger and 20 large canisters. £49 ref SB1

HIPOWER ZENON VARIABLE STROBES Useful 12v PCB fitted with hi power strobe tube and control electronics and speed control potentiometer. Perfect for interesting projects. etc 70x55mm 12vdc operation. £6 ea ref FLS1, pack of 10 £49 ref FLS2

NEW LASER POINTERS 4.5mw 75 metre range hand held unit runs on two AA batteries (supplied) 670nm £29 ref DEC49J

HOW TO PRODUCE 35 BOTTLES OF WHISKY FROM A SACK OF POTATOES Comprehensive 270 page book covers all aspects of spirit production from everyday materials. Includes construction details of simple stills. £12 ref MS3

NEW HIGH POWER MINI BUG With a range of up to 800 metres and a 3 days use from a PP3 this is our top selling bug! less than 1" square and a 10m voice pickup range. £28 ref LOT102

IR LAMP KIT Suitable for CCTV cameras, enables the camera to be used in total darkness! £6 ref EF138

INFRA RED POWER BEAM Hand held battery powered lamp, 4 inch reflector, gives out powerful pure infrared light! perfect for CCTV use, night sights etc. £29 ref PB1

SUPER WIDEBAND RADAR DETECTOR Detects both radar and laser. X K and KA bands, speed cameras, and all known speed detection systems. 360 degree coverage, front & rear waveguides, 1.1"x2.7"x4.6" fits on visor or dash. £149

LOPTX Made by Samsung for colour TV. £3 each ref SS52

LAPTOP LCD SCREENS 240x175mm £12 ref SS51

WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA? We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell!) the manuals as much as you like! £14 ref EP74

ELECTRONIC SPEED CONTROLLER KIT For the above motor is £19 ref MAG17. Save £5 if you buy them both together. 1 motor plus speed controller rrp is £41, offer price £36 ref MOT5A

INFRA RED REMOTE CONTROLS made for TVs but may have other uses pack of 100 £39 ref IREM

RCB UNITS In line IEC lead with fitted RC breaker. Installed in seconds. Pack of 3 £9.98 ref LOT5A

On our web sites you can



1. Order online.
2. Check your premium bonds.
3. Enter our auction or build your own.
4. Add E-commerce to your own site.
5. Discover our software site, optical site, hydroponics site, holiday home exchange site, inkjet site, hotels site.
6. View our web camera.
7. Invest in our future.

<http://www.bullnet.co.uk>

YOUR HOME COULD BE SELF SUFFICIENT IN ELECTRICITY Comprehensive plans with loads of info on designing systems, panels, control electronics, etc £7 ref PV1

AUTO SUNCHARGER 155x300mm solar panel with diode and 3 metre lead and cigar plug 12v 2w £12.99 REF AUG10P3

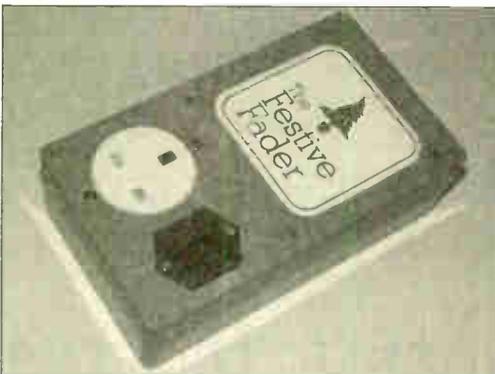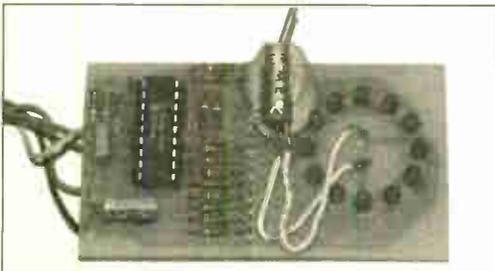STEPPER MOTORS Brand new stepper motors, 4mm fixing holes with 47.14mm fixing centres, 20mm shaft, 6.35mm diameter, 5v phase, 0.7A/phase, 1.8 deg step (200 step). Body 56x36mm £14.99 ea ref STEP6, pack of 4 for £49.95. PIC based variable speed controller kit £15 ref STEP7



NOTE NEW PUBLISHING DATE
 January issue on sale
 Thursday December 14

© Wimborne Publishing Ltd 2000. Copyright in all drawings, photographs and articles published in EVERYDAY PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our January 2001 issue will be published on Thursday, 14 December 2000. See page 875 for details

Projects and Circuits

PIC-MONITORED DUAL PSU - 1 by John Becker	884
Workshop power supply with multiple options and monitoring of voltage and current using PIC microcontroller plus l.c.d. readout	
STATIC FIELD DETECTOR by Robert Penfold	894
An amusing "electroscope" starter project that reveals if your friends are "highly charged"!	
INGENUITY UNLIMITED hosted by Alan Winstanley	902
Car Wash-Wipe Latch; Missed Call Indicator; Scissors, Paper, Stone	
MOTORIST'S BUZZ-BOX by Terry de Vaux-Balbirnie	930
A multipurpose test instrument for the intrepid car owner	
CHRISTMAS SUPPLEMENT Between pages 912 and 913	
TWINKLING STAR by Bart Trepak	1
Twinkle twinkle little LED, brighten our festives as we're fed!	
CHRISTMAS BUBBLE by Owen Bishop	4
Keep the party balloons intact, watch light bubbles burst instead!	
FESTIVE FADER by Steve Dellow	7
Relax your Noelistic senses with smoothly changing lighting effects!	
PICTOGRAM by Andy Flind	13
Become a novelty flasher at the Mad Hatter's (or other's) Xmas party!	

Series and Features

CIRCUIT SURGERY by Alan Winstanley and Ian Bell	908
Switched-Mode Power Supplies	
THE SCHMITT TRIGGER - 2.	
Op.amp and comparator trlggers by Anthony H. Smith	913
A designer's guide to investigating and using Schmitt triggers	
NEW TECHNOLOGY UPDATE by Ian Poole	924
Inkjet and optical technologies combine to provide greater comms bandwidth	
INTERFACE by Robert Penfold	926
Extended temperature PC Interface software	
NET WORK - THE INTERNET PAGE surfed by Alan Winstanley	929
Freemove - and other "unmetered" servers	
QUASAR KITS REVIEW by Robert Penfold	938
Examining the merits of a dozen electronic kits from Quasar	

Regulars and Services

EDITORIAL	883
NEWS - Barry Fox highlights technology's leading edge	892
Plus everyday news from the world of electronics	
BACK ISSUES Did you miss these? Some now on CD-ROM!	899
READOUT John Becker addresses general points arising	905
ELECTRONICS MANUALS	922
Essential reference works for hobbyists, students and service engineers	
SHOPTALK with David Barrington	920
The <i>essential</i> guide to component buying for <i>EPE</i> projects	
CD-ROMS FOR ELECTRONICS	940
Electronic Projects; Filters; Digital Works 3.0; Parts Gallery + Electronic Circuits and Components; Digital Electronics; Analogue Electronics; PICtutor; Modular Circuit Design; Electronic Components Photos.	
DIRECT BOOK SERVICE	943
A wide range of technical books available by mail order, plus more CD-ROMs	
PRINTED CIRCUIT BOARD AND SOFTWARE SERVICE	946
PCBs for <i>EPE</i> projects. Plus <i>EPE</i> software	
ELECTRONICS VIDEOS Our range of educational videos	949
ANNUAL INDEX 2000	947
ADVERTISERS INDEX	952

Readers Services • Editorial and Advertisement Departments 883

Visit our website
www.distel.co.uk


THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

THE AMAZING TELEBOX

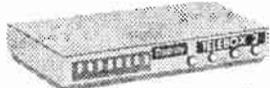Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND &
VIDEO TUNER
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems 3 PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95
TELEBOX STL as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
For overseas PAL versions state 5.5 or 6 MHz sound specification.
*For cable / hyperband signal reception TELEBOX MB should be connected to a cable type service. Shipping on all Telebox's code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite 1V pp video and NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate.
BRAND NEW - Order as MY00. Only £49.95 code (B)
See www.distel.co.uk/data_my00.htm for picture + full details

FLOPPY DISK DRIVES 2 1/2" - 8"

All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call or see our web site www.distel.co.uk for over 2000 unlisted drives for spares or repair

- 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only £25.95(B)
- 3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop £18.95(B)
- 5 1/4" Teac FD-55GR 1.2 Meg (for IBM pc's) RFE £18.95(B)
- 5 1/4" Teac FD-55F-03U 720K 40/80 (for BBC's etc) RFE £29.95(B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 360K £22.95(B)
- Table top case with integral PSU for HH 5 1/4" Floppy / HD £29.95(B)
- 8" Shugart 800/801 8" SS refurbished & tested £210.00(E)
- 8" Shugart 810 8" SS HH Brand New £195.00(E)
- 8" Shugart 851 8" double sided refurbished & tested £260.00(E)
- 8" Mitsubishi M2894-63 double sided NEW £295.00(E)
- 8" Mitsubishi M2894-63-02U DS slimline NEW £295.00(E)
- Dual 8" cased drives with integral power supply 2 Mb £499.00(E)

HARD DISK DRIVES 2 1/2" - 14"

- 2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H) New £79.95
 - 2 1/2" TOSHIBA MK2101MAN 2.16 Gb laptop (19 mm H) New £89.50
 - 2 1/2" TOSHIBA MK4309MAT 4.3Gb laptop (8.2 mm H) New £105.00
 - 2 1/2" TOSHIBA MK409MAV 6.1Gb laptop (12.7 mm H) New £190.00
 - 2 1/2" to 3 1/2" conversion kit for PCs, complete with connectors £14.95
 - 3 1/2" FUJII FK-309-26 20Mb MF/ RFE £59.95
 - 3 1/2" CONNER CP3024 20 Mb IDE /RFE (or equiv) RFE £59.95
 - 3 1/2" CONNER CP3044 40 Mb IDE /RFE (or equiv) RFE £69.00
 - 3 1/2" QUANTUM 40S Prodr/ve 42Mb SCSI /RFE, New RFE £49.00
 - 5 1/4" MINISCRIBE 3425 20Mb MF/ RFE (or equiv) RFE £49.95
 - 5 1/4" SEAGATE ST-238R 30 Mb RLL /RFE Refurb £69.95
 - 5 1/4" CDC 94205-51 40Mb HH MF/ RFE RFE tested £69.95
 - 5 1/4" HP 97548 850 Mb SCSI RFE tested £99.00
 - 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
 - 8" NEC D2246 85 Mb SMD interface. New £199.00
 - 8" FUJITSU M2322K 160Mb SMD /RFE RFE tested £195.00
 - 8" FUJITSU M2329K 2 Gb SMD /RFE RFE tested £345.00
- Many other drives in stock - Shipping on all drives is code (C1)

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

- 3MITS. FA3445ETKL 14" Industrial spec SVGA monitors £245
- FARNELL O-60V DC @ 50 Amps, bench Power Supply £995
- FARNELL AP3080 O-30V DC @ 80 Amps, bench Supply £1850
- 1KW to 400 kW - 400 Hz 3 phase power sources - ex stock EPOA
- IBM 8230 Type 1, Token ring base unit driver £760
- Wayne Kerr RA200 Audio frequency response analyser £2500
- IBM 53F5501 Token Ring ICS 20 port lobe modules £750
- IBM MAU Token ring distribution panel 8228-23-5050N £95
- AIM 501 Low distortion Oscillator 9Hz to 30KHz, IEE £250
- ALLGON 8360.1 1805-1880 MHz hybrid power combiners £250
- Trend DSA 274 Data Analyser with G703(2M) 64 v/c EPOA
- Marconi 6313 Programmable 2 to 22 GHz sweep generator £6500
- Marconi 2022C 10KHz-1GHz RF signal generator £1550
- Marconi 2030 opt 03 10KHz-1.3 GHz signal generator, New £4995
- HP1650B Logic Analyser £3750
- HP3781A Pattern generator & HP3782A Error Detector EPOA
- HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
- HP6264 Rack mount variable 0-20V @ 20A metered PSU £675
- HP54121A DC to 22 GHz four channel test set EPOA
- HP8130A opt 020 300 MHz pulse generator, GPIB etc £7900
- HP A1, A0 8 pen HPGL high speed drum plotters from HP DRAFTMASTER 1 8 pen high speed plotter £550
- EG+G Brookdeal 95035C Precision lock in amp £1800
- View Eng. Mod 1200 computerised inspection system EPOA
- Sony DXC-3000A High quality CCD colour TV camera £995
- Keithley 590 CV capacitor / voltage analyser £3750
- Racal ICR40 dual 40 channel video recorder system £3750
- Fiskers 45KVA 3 ph On Line UPS - Now batteries £9500
- Emerson AP130 2.5KVA industrial spec UPS £2100
- Mann Tally MT645 High speed line printer £2200
- Intel SBC 486/133SE Multibus 486 system 8Mb Ram £945
- Siemens K4400 64Kb to 140Mb demux analyser £2950

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK
10,000,000 items EX STOCK

For MAJOR SAVINGS
CALL OR SEE OUR WEB SITE www.distel.co.uk

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see -
At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, least switching and LOW RADIATION MPR specification. Fully guaranteed, in EXCELLENT little

used condition.
TIN & Swivel Base £4.75
VGA cable for IBM PC included.
External cables for other types of computers available - CALL

Ex demo 17" 0.28 SVGA Mitsubishi Diamond Pro monitors, Full multisync etc.
Full 90 day guarantee. Only £199.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for Info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed fan controls, VCR correction button etc. Good used condition - fully tested - guaranteed
Dimensions: W14" x H12 3/4" x 15 1/2" D.
Only £99.00 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen bums). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered.
Only £79.00 (D)

KME 10" 15M1009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 kHz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.
Only £125 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. Pill all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)


We probably have the largest range of video monitors in Europe. All sizes and types from 4" to 42" call for info.

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock
Call or see our web site.

- HP6030A 0-200V DC @ 17 Amps bench power supply £1950
- Intel SBC 486/125C08 Enhanced Multibus (MSA) New £1150
- Nikon HF-X11 (Ephiphot) exposure control unit £1450
- PHILIPS PM5518 pro. TV signal generator £1250
- Motorola VME Bus Boards & Components List. SAE / CALL EPOA
- Trio 0-18 vdc linear, metered 30 amp bench PSU. New £550
- Fujitsu M3041R 600 LPM high speed band printer £1950
- Fujitsu M3041D 600 LPM printer with network interface £1250
- Perkin Elmer 299B Infrared spectrophotometer £500
- Perkin Elmer 597 Infrared spectrophotometer £3500
- VG Electronics 1035 TELETEXT Decoding Margin Meter £495
- LightBand 60 output high spec 2u rack mount Video VDA's £1995
- Sekonic SD 150H 18 channel digital hybrid chat recorder £300
- B&K 2633 Microphone pre amp £750
- Taylor Hobson Talysurf amplifier / recorder £1450
- ADC S5200 Carbon dioxide gas detector / monitor £75
- BBC AM20/3 PPM Meter (Ernest Turner) + drive electronics £5650
- ANRITSU 9654A Optical DC-2.5Gb waveform monitor EPOA
- ANRITSU M9001B1 0.6-1.7 uM optical spectrum analyser EPOA
- ANRITSU ML93A optical power meter £990
- ANRITSU Fibre optic characteristic test set EPOA
- R&S FTDZ Dual sound unit £650
- R&S SBUF-E1 Vision modulator £775
- WILTRON 6630B 12 4 / 20GHz RF sweep generator £5750
- TEK 2445 150 MHz 4 trace oscilloscope £1250
- TEK 2465 300 MHz 300 MHz oscilloscope rack mount £1955
- TEK TDS380 400MHz digital realtime + disk driver, FFT etc £2900
- TEK TDS524A 500MHz digital realtime + colour display etc £5100
- HP3585A Opt 907 20Hz to 40MHz spectrum analyser £3950
- PHILIPS PW1730/10 60KX XRAY generator & accessories £1995
- CLAUDE LYONS 12A 240V single phase auto. volt. regs £325
- CLAUDE LYONS 100A 240V/15V 3 phase auto. volt. regs £2900

19" RACK CABINETS

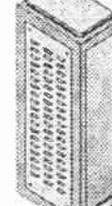

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half covered back door and lowered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:
OPT Rack 1 Complete with removable side panels. £345.00 (G)
OPT Rack 2 Back. Less side panels. £245.00 (G)

Over 1000 racks, shelves, accessories
19" 22" & 24" wide 3 to 46 U high.
Available from stock !!

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, pre-punched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys Colour Royal Blue. External dimensions mm=1625H x 635D x 603 W (64" H x 25" D x 23 1/2" W)



Sold at LESS than a third of makers price !!

A superb buy at only £245.00 (G)

42U version of the above only £345 - CALL

12V BATTERY SCOOP - 60% off !!

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12v DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type SB515 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS6290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £70 each. Our Price £35 each (C) or 4 for £99 (E)

RELAYS - 200,000 FROM STOCK

Save ££££'s by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting etc. CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save ££££'s

COLOUR CCD CAMERAS

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full autolight sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART) socket, and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available.



Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100% of applications including Security, Home Video, Web TV, Web Cams etc, etc.

Web ref = LK33 ONLY £99.00 or 2 for £180.00 (B)

SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. ONLY £89.00 (B)
ENCARTA 95 - CDROM, Not the latest - But at this price! £7.95
DOS 5.0 on 3 1/2" disks with concise books c/w QBasic. £14.95
Windows for Workgroups 3.11 + Dos 6.22 on 3 1/2" disks £55.00
Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95
shipping charges for software is code B

DISTEL on the web !! - Over 16,000,000 items from stock - www.distel.co.uk

Display
-ELECTRONICS

ALL MAIL TO
Dept PE, 29/35 Osborne Rd
Thornton Heath
Surrey CR7 8PD
Open Mon - Fri 9.00 - 5:30

LONDON SHOP
Open Mon - Sat 9.00 - 5.30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
N. Thornton Heath &
Selhurst Park SR Rail Stations

NEW DISTEL
Visit our web site
www.distel.co.uk
email = admin@distel.co.uk

ALL ENQUIRIES
0208 653 3333
FAX 0208 653 8888

All prices for UK Mainland UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £150. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)-£3.00, (A1)-£4.00, (B)-£5.50, (C)-£8.50, (C1)-£12.50, (D)-£15.00, (E)-£18.00, (F)-£20.00. (G)=CALL. Allow approx 6 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to charge prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices part for surplus goods. All trademarks, tradenames etc acknowledged © Display Electronics 1999 E & O E. 0799

NEXT MONTH

UFO DETECTOR AND EVENT RECORDER


Although some ancient texts are said to contain references to spacecraft, the UFO enigma really began on the afternoon of 24 June, 1947, when aircraft pilot Kenneth Arnold reported nine crescent-shaped objects crossing the sky at great speed near Mount Rainier in the State of Washington, USA. Since then there have been countless sightings, world-wide, and private and government organisations have been set up to investigate and report on the phenomena.

And there's been no shortage of encounters to fill the researchers' files. Whilst many incidents have been shown to have a terrestrial origin, there remains a solid core of cases where inexplicable phenomena and reliable witnesses combine to challenge our disbelief.

One thing running like a thread through many of the reports is the powerful magnetic disturbance which accompanies the craft. Car and aircraft ignition systems falter or fail (presumably the ignition coil core becomes saturated), and dashboard and navigation instruments behave erratically.

As recently as 30 March this year, a family travelling along the Klondike Highway in Canada claim to have observed a saucer-shaped UFO closing in on their car. Headlights dimmed, the tape recorder stopped playing and battery operated watches malfunctioned.

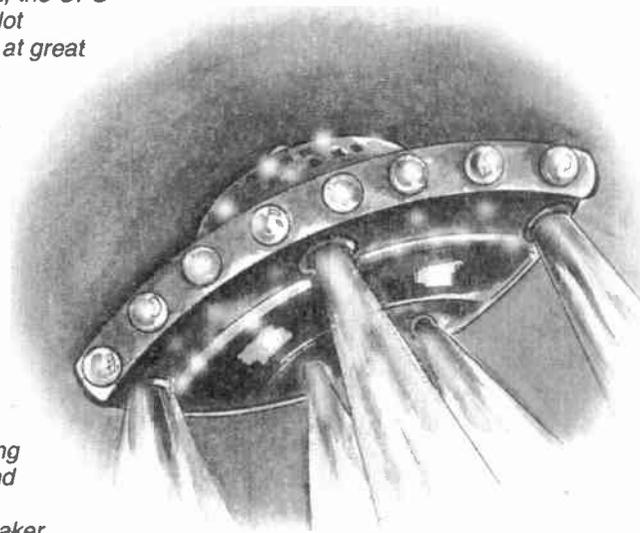The equipment to be described next month will detect and record far weaker magnetic perturbations than these. Stand-by current is extremely low, and the battery powered units can be operated economically in remote locations. Go out and find your alien!



A TWO-WAY INTERCOM

Intercom projects used to be part of the staple diet of electronic construction enthusiasts with at least one appearing somewhere every year. Over time they seem to have become less common, perhaps because they can be bought quite cheaply nowadays, so when a reader asked if EPE had recently published one, editorial eyebrows rose at the discovery that some eight years had passed since the last appeared. It seemed timely, therefore, to present a new intercom design.

It might be asked why anyone would build an intercom when they can be bought quite cheaply. In fact there are several reasons. A home-built design can be customised, built into other projects, modified and used in ways its original design never intended. Parts of the circuit might be adapted for use in other projects. The constructor can easily repair it if it goes wrong and an intercom is a good starter project for those seeking electronic experience. Last, but by no means least, constructors with children will probably find that an intercom's entertainment potential will earn them lots of brownie points with the kids! Given all this, a new design seems well worthwhile.

VERSATILE OPTICAL TRIGGER

This is a circuit that is flexible enough to cater for many different applications. In its basic form, the Versatile Optical Trigger switches a load on or off, depending on the amount of light falling on its sensor. It can be set to respond in reasonably bright conditions or in dim light. It can be adapted to work either way round, switching on when the light gets brighter, or when it becomes dimmer. Applications for the basic circuit include switching on a porch lamp at dusk, briefly sounding a buzzer when someone's shadow falls on the sensor (or when the cat leaves the house by the cat door), or to switch on a lamp in a cupboard when the door is opened. We leave it to the imagination of the reader to find other interesting things to do with this circuit.

PLUS ALL THE REGULAR FEATURES

NO ONE DOES IT BETTER

EVERYDAY
PRACTICAL
ELECTRONICS
INCORPORATING **ELECTRONICS TODAY INTERNATIONAL**

**DON'T MISS AN
ISSUE – PLACE YOUR
ORDER NOW!**
Demand is bound to be high

JANUARY 2001 ISSUE ON SALE THURSDAY, DECEMBER 14

KITMASTER EDUCATIONAL KITS FROM GREENWELD

RADIO CLUBS - NOVICES - COLLEGES - SCHOOLS

www.greenweld.co.uk

SOLID STATE KITS

ALL KITS BUILT ON TRIPAD PCB BUILD AS YOU SEE SYSTEM

FULL KIT & INSTRUCTIONS

KMX1	2-C MK484 MW RADIO	£11.50
KMX3	1-C + TRAN MW RADIO	£11.50
KMX5	MK484 + 2030 MW RADIO	£21.95
KMX7	MK484 TUNER MW, NO AMP	£7.50
KMB2	BASIC CRYSTAL SET AMPLIFIED	£11.50
KMB4	WORKSHOP AMPLIFIER	£11.50
KMX11	S. METER	£11.95
KMB44	SIMPLE HF MW ATU	£9.25
KMB8	SW TUNER GENERAL	£11.50
KMC1	BASIC CRYSTAL SET MW	£7.95
KMB61	MW SIGNAL BOOSTER	£14.99
KMB9	FAKE CAR ALARM FLASHER	£6.30
KMB10	2 L.E.D. FLASHER	£5.95
KMB11	LOW VOLTS L.E.D. ALARM 9-12V	£6.30
KMB12	LIE DETECTOR WITH METER	£11.50
KMB13	TOY ORGAN	£7.95
KMB14	METRONOME IC CONTROL	£5.30
KMB15	TOUCH SWITCH	£6.30
KMB16	HEADS OR TAILS GAME	£6.30
KMB17	SIREN	£5.95
KMB18	RAIN DETECTOR	£5.95
KMB19	CONTINUITY TESTER	£5.50
KMB20	MORSE CODE OSCILLATOR	£5.95
KMB21	BURGLAR ALARM L.E.D. & SPEAKER	£6.30
KMB22	LOOP SECURITY ALARM	£6.30
KMB23	VIBRATION ALARM	£5.95
KMB25	HAND TREMOR GAME	£5.95
KMB26	RAIN SYNTHESISER - NOISE	£11.95
KMB27	AUTO LIGHT DARK INDICATOR	£5.95
KMB28	ADJ. LOW LIGHT INDICATOR	£5.95
KMB29	DARK ACTIVATED L.E.D. FLASHER	£5.95
KMB30	LIGHT ACTIVATED TONE ALARM	£5.95
KMB31	CAR ELECTRIC PROBE	£5.75
KMB32	SIGNAL INJECTOR	£5.75
KMB33	MOISTURE METER - L.E.D.	£5.95
KMB34	L.E.D. TRANSISTOR TESTER NPN	£5.75
KMB35	DIODE TESTER - L.E.D.	£5.75
KMB36	L.E.D. TRANSISTOR TESTER PNP	£5.75
KMB37	IC 555 TESTER - L.E.D.	£6.75
KMB38	0-18 MIN TIMER L.E.D. & SPEAKER	£6.75
KMB39	TOY THERAMIN MUSIC	£8.25
KMB40	AMPLIFIED RF PROBE + METER	£11.95
KMB41	TRANSMITTER RF INDICATOR L.E.D.	£5.95

PERFECT FOR NOVICE FIRST TIME BUILDERS IN ELECTRONICS

KMB43	AUDIO NOISE GENERATOR	£11.50
KMB45	GENERAL 3 TRANSISTOR AMP	£6.75
KMB46	LM386 AMPLIFIER GENERAL	£6.75
KMB48	COMMON PRE-AMP RADIO	£6.75
KMB49	PEST SCARER HIGH PITCH	£14.99
KMB50	VARIABLE FREQ. OSCILLATOR	£6.75
KMB51	AUTOMATIC NIGHT LIGHT	£6.75
KMB52	FROST ALARM	£6.99
KMB53	PRESSURE MAT & ALARM	£16.50
KMB54	GUITAR TUNER	£11.50
KMB55	TOUCH ALARM	£6.99
KMB56	SIMPLE LIGHT METER	£16.50
KMB57	L.E.D. CONTINUITY METER	£5.50
KMB58	SOUND-OPERATED SWITCH	£7.95
KMB58A	8 FLASHING L.E.D.s	£8.25
KMB59	TBA 820M AUDIO AMP	£12.75
KMB60	TDA 2030 AUDIO AMP	£11.50
KMB62	ELECTRONIC DICE GAME	£10.30
KMB63	ADVANCED THERAMIN-MUSIC	£12.75
KMB64	TOUCH DELAY LAMP	£7.95
KMB65	FISHERMAN'S ROD BITE ALARM	£5.99
KMB66	BEAM BREAK DETECTOR ALARM	£9.75
KMB67	LATCHING BURGLAR ALARM	£9.25
KMB68	LIGHT-OPERATED RELAY	£9.25
KMB69	MICROPHONE PRE-AMP	£9.25
KMB70	MAGNETIC ALARM-MODELS	£9.25
KMB72	BATH OR WATER BUTT ALARM	£8.25
KMB73	0-18 VOLT POWER SUPPLY UNIT	£8.25
KMB74	FM BUG POWER SUPPLY 0-9V	£7.99
KMB75	1 TRANSISTOR FM BUG	£7.95
KMB76	2 TRANSISTOR FM BUG	£8.95
KMB77	CHIRP GENERATOR	£8.25
KMB78	TONE BURST GENERATOR	£8.25
KMB79	SOUND EFFECTS GENERATOR	£11.95
KMB80	LIGHT METER - PHOTOGRAPHY	£11.95
KMB81	LIGHT OSCILLATOR - PHOTOGRAPHY	£11.50
KMB82	LIGHT-ACTIVATED RELAY	£11.50
KMB83	DARK-ACTIVATED RELAY	£11.50
KMB84	SOUND SIREN + LOUD AMPLIFIER	£13.95
KMX12	AUDIO PROBE	£11.95
KMX14	CHILD SPEAK LAMP	£8.25
KMZ1	SW GEN RECEIVER	£16.50

NEW RADIO VALVE KITS

LOW PRICED ECONOMY RANGE

ALL ESSENTIAL PARTS SUPPLIED - VALVES - TRANSFORMERS - SPEAKERS - TAGSTRIP - POTENTIOMETERS - KNOBS - TUNING CAPACITORS - AERIAL FORMERS - VALVE HOLDERS - RADIO CHASSIS - CAPACITORS - RESISTORS - SOLDER - WIRE - PLUS FULL INSTRUCTIONS

PLEASE NOTE: CASES ARE NOT INCLUDED

KMK1	VALVE RADIO POWER SUPPLY UNIT, IDEAL FOR MOST OF OUR KITS. HT 210 VOLTS D.C. AND LT 6-3 VOLTS A.C.	£26.00
KMK2	VALVE PSU HIGHER OUTPUT, OK FOR MOST OF OUR KITS. HT 250 VOLTS D.C. AND LT 6-3 VOLTS A.C. BOTH PSUs HAVE 100 mA TRANSFORMERS	£28.00
KMK3	TWO VALVE RADIO, WORKS ON MW OR SW INTERCHANGEABLE AERIAL COIL FORMER. COMES WITH SPEAKER - OUR BEST SELLER	£31.50
KMK4	ONE VALVE AMPLIFIER USES THE EL84 VALVE STILL MADE TODAY. IDEAL SHACK PROJECT. EASY TO BUILD, GOOD SPEAKER VOLUME	£16.50
KMK6	ONE VALVE REGEN RADIO. THIS KIT COMES WITH GOOD QUALITY EARPIECE. CAN BE USED EITHER MW OR SW. GIVES GOOD RESULTS	£18.50
KMK7	THIS VERY GOOD AMPLIFIER USES THE EL84 AND ECL83 VALVES. A VERY VALUABLE TWO VALVE AMP IN THE SHACK. GOOD SPEAKER VOLUME	£23.00
KMK8	ONE VALVE EXPERIMENTAL CRYSTAL SET WITH SOLID STATE INCORPORATED. IDEAL FOR HAM EXPERIMENTS. GOOD SPEAKER VOLUME	£22.00
KMK9	ONE VALVE MW RADIO THIS ONE IS NOT REGEN. INSTEAD IT HAS SOLID STATE AS WELL. GOOD SPEAKER VOLUME, EASY TO BUILD	£26.00
KMK10	MODERN TWO VALVE MW RADIO WITH SOLID STATE. USES TWO VALVES MADE TODAY. NO COILS TO WIND, GOOD SPEAKER VOLUME	£31.50
KMK11	ANOTHER TYPE OF DESIGN TWO VALVE SW RADIO. OPERATES APPROX. 6MHz TO 14MHz. IDEAL GENERAL SW SET, GOOD SPEAKER VOLUME	£33.50
KMK12	TWO VALVE AMPLIFIED CRYSTAL SET, MW OR SW. IDEAL HAM KIT INCORPORATES OA90 DIODE WITH EL84 AND ECC83 VALVES, LOUDSPEAKER	£31.50
KMK13	TRY BUILDING THIS TWO VALVE REGEN RADIO. USES THE EF91 AND ECL80 VALVES, GOOD SPEAKER VOLUME, REGEN MW OR SW	£31.50
KMK14	LOOK AT THIS ONE, IT'S A THREE VALVE MW OR SW REGEN SET WITH RF STAGE, GOOD SELECTIVITY, GOOD SPEAKER VOLUME	£39.95
KMK15	MW OR SW THREE VALVE REGEN RADIO USING A DIFFERENT SYSTEM, THIS USES EF91, EF80, EL84, VERY LOUD SPEAKER	£39.95
KMK16	FOUR VALVE MW OR SW TOP OF THE RANGE, DESIGNED FOR EASY BUILDING NOVICES, GOOD SELECTIVITY, GOOD SPEAKER VOLUME	£49.95

LOOK! NEW BATTERY VALVE KITS - RADIOS - AMPLIFIERS

ALL THESE BATTERY KITS WORK AT JUST 90 VOLTS D.C.

KMT1	BATTERY ELIMINATOR - DON'T WANT TO USE A BATTERY? USE OUR PSU, GIVES 90 VOLTS D.C. AND 1-5 VOLTS D.C. FOR ALL BATTERY KITS	£27.95
KMT2	BATTERY MW THREE VALVER AND A GOOD ONE, USES TWO IT4 VALVES WITH A DL96, VERY LOUD SPEAKER, GOOD PROJECT	£39.95
KMT3	SHORT WAVE BATTERY THREE VALVER, COMES WITH THREE AERIAL FORMERS, IDEAL HAM PROJECT, GOOD SPEAKER VOLUME	£44.99
KMT4	WANT A BATTERY VALVE AMPLIFIER? TRY THIS TWO VALVE AMPLIFIER, IDEAL FOR THE SHACK, MANY USES, VERY LOUD SPEAKER	£26.50
KMT5	BATTERY TWO VALVE MW CRYSTAL SET, STRICTLY FOR THE HAM EXPERIMENTER. USES IT4 AND DL96 WITH OA90, GOOD SPEAKER VOLUME	£33.95
KMT6	BATTERY TWO VALVE MW RADIO INCORPORATING SOLID STATE, NO OUTSIDE AERIAL NEEDED, GOOD SPEAKER VOLUME, GOOD PROJECT	£39.99
KMT7	BATTERY TWO VALVE GENERAL SW RADIO, 6MHz TO 14MHz APPROX. NO REGEN, VERY LOUD SPEAKER, EASY TO BUILD	£39.95

ALL RADIO CHASSIS PRE-DRILLED AND VALVE BASES FITTED READY FOR QUICK ASSEMBLY

Visit our new web site: <http://www.kit-master.co.uk>
<http://www.greenweld.co.uk>

For our FREE catalogue E-mail: service@greenweld.co.uk

P&P £3.00
£10 OVERSEAS AND NEXT DAY

MAIL ORDER ONLY
PLEASE ALLOW UP TO
28 DAYS FOR DELIVERY

ALL KITMASTER KITS DESIGNED



BY DAVID JOHNS



FREE CATALOGUE

GREENWELD OFFERS A MASSIVE RANGE OF LOW COST ELECTRONIC COMPONENTS, NEW AND SURPLUS. WHETHER YOUR INTEREST IS IN ELECTRONICS, MODEL ENGINEERING, AUDIO, COMPUTERS OR ROBOTS, WE HAVE SOMETHING FOR YOU.

LOOK! NEW BATTERY VALVE KITS YES, THEY'RE HERE. IF YOU'RE LIKE US AND DON'T WANT TO BOTHER WITH BATTERIES, WE SUGGEST YOU BUILD T1 BATTERY ELIMINATOR FIRST THEN YOU CAN CHOOSE WHICH RADIO TO START ON. WE WILL ADD THAT T2 IS AN EXCELLENT LITTLE MEDIUM WAVE SET, IT'S WORTH CONSIDERING AND IT'S GOT GOOD VOLUME, EASY TO BUILD.

Send now for our comprehensive
FREE catalogue



WE ACCEPT PAYMENT BY
CHEQUE, POSTAL ORDER
AND CREDIT CARD




UNIT 24, WEST HORNDON
INDUSTRIAL PARK
WEST HORNDON, BRENTWOOD,
ESSEX CM13 3XD



TEL: 01277 811042
FAX: 01277 812419

The science lab in a PC

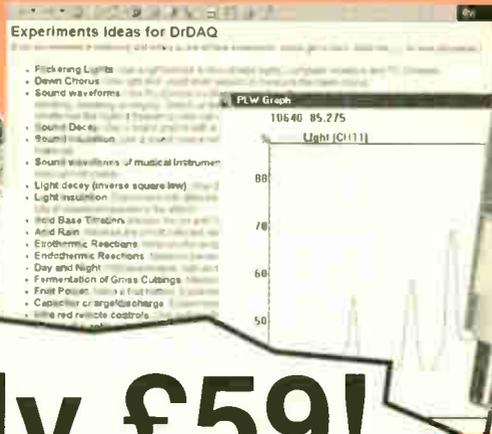

- Output
- Voltage
- Resistance
- Light level
- Temperature
- External sensors
- pH
- Microphone

Only £59!
+VAT

The DrDAQ is a low cost data logger from Pico Technology. It is supplied ready to use with all cables, software and example science experiments.

DrDAQ represents a breakthrough in data logging. Simply plug DrDAQ into any Windows PC, run the supplied software and you are ready to collect and display data. DrDAQ draws its power from the parallel port, so no batteries or power supplies are required.

- ✓ Very low cost
- ✓ Built in sensors for light, sound (level and waveforms) and temperature
- ✓ Use DrDAQ to capture fast signals (eg sound waveforms)
- ✓ Outputs for control experiments
- ✓ Supplied with both PicoScope (oscilloscope) and PicoLog (data logging) software

FREE Science Experiments Over The Web!

The Pico Technology Library of Science Experiments contains a number of educational experiments suitable for use with oscilloscope and data logging products.

The experiments are written by science teachers and industry experts. So that you can find an experiment of interest easily, we have divided them into five subjects: biology, chemistry, physics, electronics and general science. You can find these experiments at: www.picotech.com/experiments/index.html



To order the DrDAQ please choose one of the following guidelines:

- i) Fill out the order form and either fax it, or post it back to Pico Technology.
- ii) Visit our web site and place an order over the internet, or,
- iii) Place an order over the phone by ringing the number below.

DrDAQ Order Form:			
Quantity	Package	Price inc VAT	Total
	DrDAQ + Software	£69.32	
	DrDAQ + 2 Temperature Sensors	£92.85	
	DrDAQ + 2 Temperature Sensors + pH Electrode	£116.32	
	Delivery (per item)	£4 11	
Grand Total		£	

Name			
Address			
Post code			
Phone			
Credit Card	Visa / Mastercard / Switch / Amex		
Card Number			
Expiry Date	/	Start Date & or issue No.	
Cheque with order	<input type="checkbox"/>		

EPE

Pico Technology Ltd, The Mill House, Cambridge Street, St Neots, Cambridgeshire. PE19 1QB
Tel: 01480 396395, Fax: 01480 396296, E-mail: post@picotech.com, Web: www.drdaq.com




PIC LOGICATOR™

The fully graphical environment for designing control systems for PICmicros


Draw the system as an on-screen flowchart, test it in the software, and download it directly to the PICmicro.

- Fast and easy
- Ideal for new PICmicro users
- Great for robotics and animatronics projects

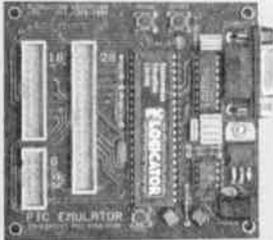Primarily designed for use with FLASH reprogrammable microcontrollers (e.g. PIC16F84 and PIC16F873). Also supports OTP devices. A separate software application is provided to allow the Programmer to download hex files generated from assembler code or C.



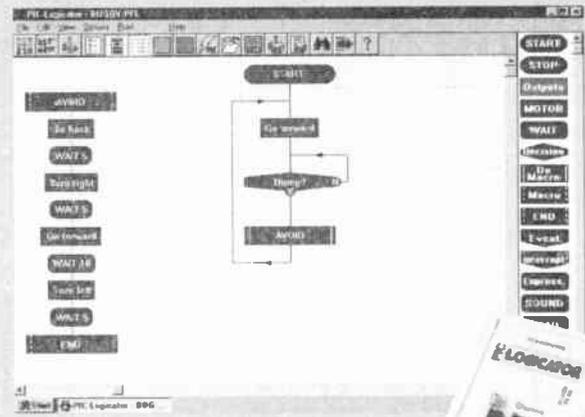PIC-Logicator Emulator
Allows in-circuit emulation of the PICmicro, either in real time or responding directly to an on-screen simulation.
PIC-EM £119.95



PIC-Logicator Pack
PIC-Logicator Software for PCs running Windows 95/98, and Programmer complete with serial lead, power supply and user manual.
PIC-L £149.95



www.pic-logicator.com
• Interactive software demo • Direct purchase

Prices include UK carriage and VAT.

PIC-Logicator, Economatics(Education)Ltd, Epic House, Darnall Rd, Sheffield S95AA UK.
Tel 0114 281 3311. Email: education@economatics.co.uk

SQUIRES

MODEL & CRAFT TOOLS

A COMPREHENSIVE RANGE OF MINIATURE HAND AND POWER TOOLS AND AN EXTENSIVE RANGE OF ELECTRONIC COMPONENTS
FEATURED IN A FULLY ILLUSTRATED
432-PAGE MAIL ORDER CATALOGUE

2001 ISSUE

**SAME DAY DESPATCH
FREE POST AND PACKAGING**

Catalogues: FREE OF CHARGE to addressed in the UK.
Overseas: CATALOGUE FREE, postage at cost charged to credit card

**Squires, 100 London Road,
Bognor Regis, West Sussex, PO21 1DD**

TEL: 01243 842424

FAX: 01243 842525

SHOP NOW OPEN



Bell College
Almada Street
Hamilton
Scotland ML3 0JB
Tel: 01698 283100
Fax: 01698 282131



Make your Expertise pay!

In today's world you need qualifications to obtain and keep employment. Our open learning courses make obtaining those qualifications as convenient as possible.

Choose from our dozens of SQA accredited units, either singly to **update your skills** or as a group to obtain a **Higher National Certificate**.

- **Learn at your own pace in your own home**
- **Support from professional engineers via phone, FAX and the Internet**
- **Courses from Introductory Bridging Modules to HNC Electronics**
- **Units from Programmable Logic Controllers to Engineering Computing**

DONT DELAY – we are waiting to hear from you.

Contact Laura Murdoch, Open Learning Co-ordinator
Tel 01698 283100 Ext. 214.
E-mail l.murdoch@bell.ac.uk
Web: http://floti.bell.ac.uk/openlearning

Member of the British Association for Open Learning
Preview Centre for FT Knowledge



Bell College of Technology
is a registered charity No. Sc 021179,
providing quality Higher Education and
Training opportunities for all.





**8 CAVANS WAY,
BINLEY INDUSTRIAL
ESTATE,
COVENTRY CV3 2SF**
Tel: 01203 650702
Fax: 01203 650773
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M45 and M69)

OSCILLOSCOPES

Beckman 9020 - 20MHz - Dual Channel.....	£180
Gold 06 245A/250/255/300/300C/3351/4000.....	from £125
Hewlett Packard 180A/180C/181A/182C.....	from £180
Hewlett Packard 1740A, 1741A, 1744A 100MHz Dual Channel.....	from £300
Hewlett Packard 841000 - 1 GHz Digitizing.....	£1280
Hewlett Packard 84200A - 50 MHz Digitizing.....	£500
Hewlett Packard 84201A - 300MHz - 1GS/s 4-Channel.....	£2250
Hewlett Packard 84512B - 300MHz - 1GS/s 4-Channel.....	£1250
Hewlett Packard 84501A - 100MHz - 100Ms/s 4-Channel.....	from £105
Hitachi V182F/V302B/V302F/V323F/V580B/V680F.....	£200
Hitachi V1100A - 100MHz 4-Channel.....	£250
Intron 2020 - 20MHz Digital Storage (NEW).....	£450
Intron 8867/10/886702 - 20MHz.....	from £125
Meguro - M80 1270A - 20 MHz Digital Storage (NEW).....	£450
Lecroy 8304 AM - 200MHz - 100 Ms/s 4-Channel.....	£3000
Lecroy 8450A - 300MHz/400 Ms/s D.S.O. 2-Channel.....	£2250
Philips PM 3055 - 50MHz Dual Trace.....	£450
Philips PM 3211/PM 3212/PM 3214/PM 3217/PM 3234/PM 3240/PM 3243/PM 3244/PM 3261/PM 3262/PM 3263/PM 3540.....	from £125
Philips PM 3295A - 400MHz Dual Channel.....	£1800
Philips PM 3335 - 50MHz/20 Ms/s D.S.O. 2-Channel.....	£350
Tektronix 481 - 50MHz Dual Channel.....	£200
Tektronix 484/486 - 100MHz Analogue Storage.....	from £200
Tektronix 486/485B - 100MHz Dual Channel.....	from £200
Tektronix 486 - 100MHz D.S.O.....	£200
Tektronix 7AS 478 - 100MHz - 4-Channel.....	£285
Tektronix 478/478A - 200MHz/250MHz Dual Channel.....	from £400
Tektronix 486 - 350MHz - 2-Channel.....	£250
Tektronix 2211 - Digital Storage - 50MHz.....	£200
Tektronix 2213 - 60MHz Dual Channel.....	£260
Tektronix 2215 - 60MHz Dual Trace.....	£275
Tektronix 2220 - 60MHz Dual Channel D.S.O.....	£260
Tektronix 2221 - 60MHz Digital Storage 2-Channel.....	£260
Tektronix 2225 - 50MHz Dual Channel.....	£200
Tektronix 2235 - 100MHz Dual trace.....	£200
Tektronix 2335 - Dual Trace 100MHz (portable).....	£200
Tektronix 2440 - 300MHz/500 Ms/s D.S.O. 2-Channel.....	£2500
Tektronix 2445 - 150MHz - 4-Channel+DMH.....	£200
Tektronix 2445A - 100MHz - 4-Channel.....	£250
Tektronix 2478B - 400MHz - 4-Channel.....	£2600
Tektronix 8403 - 60MHz - 2 or 4-Channel.....	from £180
Tektronix 7313, 7993, 7823, 7633 - 100MHz 4-Channel.....	from £225
Tektronix 7704 - 250MHz 4-Channel.....	from £250
Tektronix 790 - 20MHz Dual Channel.....	from £240
Trfo CB-1022 - 20MHz - Dual Channel.....	£125

Other scopes available too

SPECIAL OFFER

HITACHI V212 - 20MHz DWAL TRAC.....	£100
HITACHI V222 - 20MHz DWAL TRACE+ALTERNATE MAGNIFY.....	£100

Ando AC8211 - Spectrum Analyser 1-7G.....	£1995
Anritsu MS828 - 10kHz-1700MHz.....	£3500+
Anritsu MS3401A+MS3401B - (10Hz-30MHz).....	£3500+
Anritsu MS810B - 10kHz-2GHz - (Mint).....	£3500+
Anritsu MS710F - 100kHz-23GHz Spectrum Analy.....	£3500+
Avcom P8A858 - 100MHz - port.....	£250
Hamco 8028/8038 - Spectrum Analyser/Tracking Gen+100MHz Oscilloscope.....	£2500
Hewlett Packard 1821 with 8558A (10MHz-21GHz).....	£2500
Hewlett Packard 1821-8558B - 0-1 to 1500M.....	£2500
Hewlett Packard 852A-8558B - 0-1 to 1500M.....	£2500
Hewlett Packard 3882A - Dual Channel Dynamic Sig. Analyser.....	£200
Hewlett Packard 3850A - 5Hz-50k.....	£2000
Hewlett Packard 382A - 0-02Hz-25-6kHz (Dual Channel).....	£4000
Hewlett Packard 385A - 20Hz-40M.....	£4250
Hewlett Packard 8508B - (0-01 to 22GHz).....	£2500
Hewlett Packard 8504A - 'S' Parameter Test Set.....	from £3000
Hewlett Packard 8733A - Network Analyser.....	from £4500
Hewlett Packard 8733B - Network Analyser.....	£2500
IFR 7750 - 10kHz-1G.....	£750
Meguro M8A 4001 - 1-300GHz (AS NEW).....	£1000
Meguro M8A 4012 - 1-1GHz (AS NEW).....	£1500
Rohde & Schwarz - SWOB 5 Polyskop 0-1-1300M.....	£2100
Tekeda Filken 4132 - 1-0GHz Spectrum Analyser.....	£2500
Tektronix 7L1B with mainframe (1-60GHz with external mixers).....	£4500
Tektronix 486P - 100MHz-1.8GHz prog.....	£4250
Tektronix 486P - 1kHz-1.8GHz Spectrum Analyser.....	£4250

Adret 740A - 100kHz-1120MHz Synthesised Signal Generator.....	£300
Anritsu MG 3801A Signal Generator 0.1-1040MHz.....	£1250
Anritsu MIE 462B DF3 Transmission Analyser.....	£2500
Anritsu MG 645B Signal Generator 0-05-1.....	£750
Boonton 82C R/F Mill.....	£195
Boonton 83A True RMS Voltmeter.....	£195
Dranzetz 830 - AC/DC - Multifunction Analyser.....	£450
EIP 331 - Frequency Counter 18G.....	£1250
EIP 645 - Frequency Counter 18G.....	£450
EIP 575 - Frequency Counter 18G.....	£1450
Etek 888PB - Power Supply 60V-30V.....	£200
Farnell TV9 MK18 Power Supply (70V - 5A or 35V - 10A).....	£125
Farnell D8Q-1 Synthesised Signal Generator.....	£1750
Farnell AP 30250A Power Supply 3V.....	£150
Feedback PFG 805 Power Function Generator.....	£1850
Fluke 5100A - Calibrator.....	£2500
GN ELMI EPP31 PCM Signalling Recorder.....	£2000
Guidance 9182 - T12 Battery Standard Cell.....	£500
Hewlett Packard 1630D - Logic Analyser (43 Channels).....	£500
Hewlett Packard 16500A/B and C - Fitted with 16510A/1651A/16530A/16531A - Logic Analyser.....	from £2000
Hewlett Packard 331A - Distortion Analyser.....	£300
Hewlett Packard 333A - Distortion Analyser.....	£300
Hewlett Packard 334A - Distortion Analyser.....	£300
Hewlett Packard 3328A - 21MHz Synthesiser/Function Generator.....	£300
Hewlett Packard 3338A - Synthesised Signal Generator (200Hz-81MHz).....	£2750
Hewlett Packard 3338C - Synthesised Signal Generator (10Hz-21MHz).....	£300
Hewlett Packard 3455A - 8% Digi Multimeter (Autocal).....	£300
Hewlett Packard 3455A - Digital Voltmeter.....	£300
Hewlett Packard 3488A - HP - 1B Switch Control Unit (various Plug-Ins available).....	£350
Hewlett Packard 35600A - Dual Channel Dynamic Signal Analyser.....	£3750
Hewlett Packard 3585A - Selective Level Meter.....	£300
Hewlett Packard 3711A/3712A/3713/3713B - Microwave Link Analyser.....	500
Hewlett Packard 3746A - Selective Measuring.....	£300
Hewlett Packard 3746A - Selective Measuring PCM Terminal Test Set.....	£1000
Hewlett Packard 3779A/3779C - Primary Mux Analyser.....	from £400

Hewlett Packard 3784A - Digital Transmission Analyser.....	£5000
Hewlett Packard 37900B - Jitter Generator+Receiver.....	£1250
Hewlett Packard 37900B - Signalling Test Set (No. 7 and ISDN).....	£4250
Hewlett Packard P982A - Variable Attenuator.....	£250
Hewlett Packard 4192A - LF Impedance Analyser.....	£5800
Hewlett Packard 4282A - Digital LCR Meter.....	£360
Hewlett Packard 4342A - 'Q' Meter.....	£300
Hewlett Packard 435A or B Power Meter (with 8481A/8484A).....	from £400
Hewlett Packard 436A and 437B - Power Meter and Sensor.....	from £200
Hewlett Packard 4848A - (TIMS) Transmission Impairment M/Set.....	£1000
Hewlett Packard 4972A - Lan Protocol Analyser.....	£1280
Hewlett Packard 5183 - Waveform Recorder.....	£1280
Hewlett Packard 5338A - Frequency Counter 100MHz.....	£280
Hewlett Packard 5314A - (NEW) 100MHz Universal Counter.....	£280
Hewlett Packard 5318A - Universal Counter (IEEE).....	£280
Hewlett Packard 5338A - 200MHz High Performance Systems Counter.....	£300
Hewlett Packard 5324A - Microwave Frequency Counter (500MHz-18GHz) Opts 1+3.....	£300
Hewlett Packard 5368A - High Resolution Time Synthesiser.....	£280
Hewlett Packard 5370B - Universal Timer/Counter.....	£2000
Hewlett Packard 5384 - 225MHz Frequency Counter.....	£300
Hewlett Packard 5385A - Frequency Counter - 1GHz - (HP1B) with OPTS 001/003/004/005.....	£750
Hewlett Packard 6033A - Power Supply Autoranging (20V - 30A).....	£750
Hewlett Packard 6283A - Power Supply 20V - 3A Twin.....	£200
Hewlett Packard 6285A - Power Supply 40V - 1.5A Twin.....	£200

HEWLETT PACKARD 8261B
Power Supply 20V - 50A £350 Discount for Quantities

Hewlett Packard 6264B - Power Supply (0-20V, 0-25A).....	£300
Hewlett Packard 6271B - Power Supply 60V - 3A.....	£220
Hewlett Packard 6824A - Quad Power Supply.....	£200
Hewlett Packard 6832A - Power Supply (20V - 5A).....	£300
Hewlett Packard 6982A - 20V - 25A System P.S.U.....	£750
Hewlett Packard 747B - 8 Pen Plotter.....	£250
Hewlett Packard 7560A - 8 Pen Plotter.....	£250
Hewlett Packard 7760 - Coax Dual Directional Coupler.....	£300
Hewlett Packard 8018A - 50MHz Pulse Generator.....	£300
Hewlett Packard 8188A - 50MHz Programmable Signal Source.....	£1250
Hewlett Packard 8180A - Data Generator.....	£1800
Hewlett Packard 8182 - Data Analyser.....	£250
Hewlett Packard 8360B - Sweep Oscillator Mainframe (various plug-in options available).....	£2500
Hewlett Packard 8385A - Wave Source Module 26-5 to 40GHz.....	£2600
Hewlett Packard 8385A - Millimeter - Wave Source Module 33-50GHz.....	£2450
Hewlett Packard 8408A - Vector Voltmeter.....	£350
Hewlett Packard 8620C - Sweep Oscillator Mainframe.....	from £280
Hewlett Packard 8640B - Signal Generator (512MHz-1024MHz).....	from £350
Hewlett Packard 8642A - Signal Generator (0-01 to 1050MHz) High Performance Synthesiser.....	£280
Hewlett Packard 8656A - Synthesised Signal Generator (950MHz).....	£280
Hewlett Packard 8656B - Synthesised Signal Generator.....	£1450
Hewlett Packard 8657A - Signal Generator (100kHz-1040MHz).....	£1800
Hewlett Packard 8658A - Synthesised Signal Generator (10kHz-2600MHz).....	£2250
Hewlett Packard 8750A - Storage Network Analyser.....	£1500
Hewlett Packard 8756A - Scalar Network Analyser.....	£2250
Hewlett Packard 8757A - Scalar Network Analyser.....	£1000
Hewlett Packard 8901A - Modulation Analyser.....	£2000
Hewlett Packard 8901B - Modulation Analyser.....	£1600
Hewlett Packard 8903B - Distortion Analyser (Mint).....	£1500
Hewlett Packard 8920A - R/F Comms Test Set.....	£2500
Hewlett Packard 8922B/G/H - Radio Comms Test Sets (G.S.M.).....	from £8000
Hewlett Packard 8988A - Cellular Radio Interface.....	£1000
Hewlett Packard 8988B - Miniature 15KV Hand-held ESD Simulator.....	£1750
Krohn-Hite 2200 - Lin/Log Sweep Generator.....	£250
Krohn-Hite 4024A - Oscillator.....	£250
Krohn-Hite 6200 - Sweep, Function Generator.....	£250
Krohn-Hite 6500 - Phase Meter.....	£250
Leader LDM-170 Distortion Meter.....	£350
Leader 3216 - Signal Generator (100kHz-140kHz) AM/FM/CW with built-in FM stereo modulator (mint).....	£395
Marconi 1095B - Demultiplexer and Frame Alignment Monitor (new).....	EPOA
Marconi 2019 - 80kHz-1040MHz Synthesised Signal Generator.....	£750
Marconi 2019A - 80kHz-1040MHz Synthesised Signal Generator.....	£1000
Marconi 2111 - UHF Synthesiser (new).....	EPOA
Marconi 2185 - 1.5GHz Programmable Attenuator (new).....	EPOA
Marconi 2305 - Modulation Meter.....	750
Marconi 2337A - Automatic Distortion Meter.....	£180
Marconi 2610 - True RMS Voltmeter.....	£700
Marconi 2671 - Data Comms Analyser.....	£500
Marconi 2685 - Radio Comms Test Set.....	£2500
Marconi 6310 - Sweep Generator - Programmable - new (2-20GHz).....	£2500
Marconi 6950/6960 - Power Meter & Sensor.....	from £500
Marconi 6960 - Power Meter & Sensor.....	from £380
Marconi 893 - A/F Power Meter.....	£250
Philips PM5 67 Mixt Function Generator.....	£400
Philips 5190 - L.F. Synthesiser (G.P.I.B.).....	£1500
Philips 6518 - Synthesised Function Generator.....	£1800
Philips PM5519 - TV Pattern Generator.....	£2500
Philips PM5710 - 50MHz Pulse Generator.....	£235
Primo 4000 - 6 Digit Multimeter (NEW).....	£250
Quadrant 2A - On-Air Frequency Sta.....	£200
Racal 1992 - 1.3GHz Frequency Counter.....	£200
Racal 6111/6181 - GSM Radio Comms Test.....	EPOA
Racal Dana 9081/9082 - Synthesised Signal Generator 520M.....	from £400
Racal Dana 9084 - Synthesised Signal Generator 104M.....	£480
Racal 9201A - True RMS R/F Multivoltmeter.....	£375
Racal Dana 9302A - R/F Multivoltmeter (new version).....	£270
Racal Dana 9303 - R/F Level Meter &.....	£75
Racal Dana 9617 - UHF Frequency Meter 500M.....	£360
Rohde & Schwarz LF42 - 60MHz Group Delay Sweep Generator.....	£995
Rohde & Schwarz CM1A 84 - GSM Radio Comms Analyser.....	£750
Schaffner NS9 203A - Line Voltage Variation Simulator.....	£700
Schaffner NS9 222A - Interference Simulator.....	£700
Schaffner NS9 223 - Interference Generator.....	£400
Schubmberger 4031 - 1GHz Radio Comms Test.....	£495
Schubmberger Stablock 4040 - Radio Comms Test.....	£1995
Schubmberger 7090/7098/7075 - M.....	from £280
Stanford Research DS 340 - 15MHz Synthesised Function (NEW) and Arbitrary Waveform Generator.....	£1200
Syston Donner 6030 - Microwave Frequency Counter (26-5GHz).....	£1995
Tektronix PJ8503+TM801+PE302 - Current Probe Amplifier.....	£300
Tektronix PG806+TG801+G8603+TM803 - Oscilloscope Calibrator.....	£195
Tektronix 577 - Curve Tracer.....	£180
Tektronix 1240 - Logic Analyser.....	£500
Tektronix 141A - PAL Test Signal Generator.....	£250
Tektronix AA801 & TM8008 M/F - Programmable Distortion Analyser.....	£1995
Tektronix TM8003+AFQ 5101 - Arbitrary Function Generator.....	£1800
Tektronix - Plug-ins - many available such as SC504, SW503, SG502, PG508, FG504, FG503, TG501, TR503+many.....	
Time 9611 - Programmable R.....	£400
Time 9614 - Voltage Calibrator.....	£550
Valhalla Scientific - 272A Programmable Resistance.....	EPOA
Wandel & Gottmann PFJ-8 - Error/Jitter Test.....	£1800
Wandel & Gottmann PC44 - Options.....	£3000
Wandel & Gottmann MU30 - Test Point Scanner.....	£1800
Wayne Kerr 4225 - LCR Bridge.....	£300
Wavetek 171 - Synthesised Function Generator.....	£250
Wavetek 172B - Programmable Signal Source (0-0001Hz-13MHz).....	EPOA
Wavetek 184 - Sweep Generator 5M.....	£280
Wavetek 3010 - 1-1GHz Signal Generator.....	£1250
Witron 8408 - RF Analysers (1MHz-2GHz).....	EPOA
Witron 8620B - Programmable Sweep Generator (3-6GHz-6.5GHz).....	£650
Witron 6747-20 - Swept Frequency Synthesiser (10MHz-20GHz).....	£380
Yokogawa 3885 - Analysing Recorder.....	EPOA

MAIL ORDER ONLY • CALLERS BY APPOINTMENT

EPE MICROCONTROLLER P.I. TREASURE HUNTER

The latest MAGENTA DESIGN - highly stable & sensitive - with I.C. control of all timing functions and advanced pulse separation techniques.

- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

KIT 847£63.95

PORTABLE ULTRASONIC PEST SCARER

A powerful 23kHz ultrasound generator in a compact hand-held case. MOSFET output drives a special sealed transducer with intense pulses via a special tuned transformer. Sweeping frequency output is designed to give maximum output without any special setting up.

KIT 842.....£22.56

68000 DEVELOPMENT TRAINING KIT

- NEW PCB DESIGN
- 8MHz 68000 16-BIT BUS
- MANUAL AND SOFTWARE
- 2 SERIAL PORTS
- PIT AND I/O PORT OPTIONS
- 12C PORT OPTIONS

KIT 621

£99.95

- ON BOARD 5V REGULATOR
- PSU £6.99
- SERIAL LEAD £3.99

Stepping Motors

MD38...Mini 48 step...£8.65

MD35...Std 48 step...£9.99

MD200...200 step...£12.99

MD24...Large 200 step...£22.95



PIC PIPE DESCALER

- SIMPLE TO BUILD
- HIGH POWER OUTPUT
- AUDIO & VISUAL MONITORING
- SWEPT FREQUENCY

An affordable circuit which sweeps the incoming water supply with variable frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve lathering ability by altering the way salts in the water behave. Kit includes case, P.C.B., coupling coil and all components. High coil current ensures maximum effect. L.E.D. monitor.



KIT 868 £22.95 POWER UNIT.....£3.99

MICRO PEST SCARER

Our latest design - The ultimate scarer for the garden. Uses special microchip to give random delay and pulse time. Easy to build reliable circuit. Keeps pets/pests away from newly sown areas, play areas, etc. uses power source from 9 to 24 volts.

- RANDOM PULSES
- HIGH POWER
- DUAL OPTION



Plug-in power supply £4.99

KIT 867.....£19.99

KIT + SLAVE UNIT.....£32.50

WINDICATOR

A novel wind speed indicator with LED readout. Kit comes complete with sensor cups, and weatherproof sensing head. Mains power unit £5.99 extra.

KIT 856.....£28.00

★ TENS UNIT ★

DUAL OUTPUT TENS UNIT

As featured in March '97 issue.

Magenta have prepared a FULL KIT for this, excellent new project. All components, PCB, hardware and electrodes are included. Designed for simple assembly and testing and providing high level dual output drive.

KIT 866. . Full kit including four electrodes £32.90

Set of 4 spare electrodes £6.50

1000V & 500V INSULATION TESTER



Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms.

Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

KIT 848.....£32.95

EPE TEACH-IN 2000

Full set of top quality NEW components for this educational series. All parts as specified by EPE. Kit includes breadboard, wire, croc clips, pins and all components for experiments, as listed in introduction to Part 1.

*Batteries and tools not included.

TEACH-IN 2000 -

KIT 879 £44.95

MULTIMETER £14.45

SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube plus instructions for message loading.

KIT 849.....£16.99

12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMS at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

KIT 790.....£29.90

SUPER BAT DETECTOR

1 WATT O/P, BUILT IN SPEAKER, COMPACT CASE 20kHz-140kHz

NEW DESIGN WITH 40kHz MIC.

A new circuit using a 'full-bridge' audio amplifier i.c., internal speaker, and headphone/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.

KIT 861.....£24.99

ALSO AVAILABLE Built & Tested...£39.99



MOSFET MKII VARIABLE BENCH POWER SUPPLY 0-25V 2-5A

Based on our Mk1 design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.



Kit No. 845£64.95

EPE PROJECT PICS

Programmed PICs for all* EPE Projects 16C84/18F84/16C71 All **£5.90** each PIC16F877 now in stock **£10** inc. VAT & postage

(*some projects are copyright)

ULTRASONIC PEST SCARER

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.



- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS
- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

KIT 812.....£15.00

SIMPLE PIC PROGRAMMER

INCREDIBLE LOW PRICE! Kit 857 **£12.99**

INCLUDES 1-PIC16F84 CHIP
SOFTWARE DISK, LEAD
CONNECTOR, PROFESSIONAL
PC BOARD & INSTRUCTIONS

Power Supply £3.99

EXTRA CHIPS:
PIC 16F84 £4.84

Based on February '96 EPE. Magenta designed PCB and kit. PCB with 'Reset' switch, Program switch, 5V regulator and test L.E.D.s, and connection points for access to all A and B port pins.

PIC 16C84 DISPLAY DRIVER

INCLUDES 1-PIC16F84 WITH
DEMO PROGRAM SOFTWARE
DISK, PCB, INSTRUCTIONS
AND 16-CHARACTER 2-LINE
LCD DISPLAY

Kit 860 **£19.99**

Power Supply £3.99

FULL PROGRAM SOURCE
CODE SUPPLIED - DEVELOP
YOUR OWN APPLICATION!

Another super PIC project from Magenta. Supplied with PCB, industry standard 2-LINE x 16-character display, data, all components, and software to include in your own programs. Ideal development base for meters, terminals, calculators, counters, timers - Just waiting for your application!

PIC 16F84 MAINS POWER 4-CHANNEL CONTROLLER & LIGHT CHASER

- WITH PROGRAMMED 16F84 AND DISK WITH SOURCE CODE IN MPASM
- ZERO VOLT SWITCHING
- MULTIPLE CHASE PATTERNS
- OPTO ISOLATED
- 5 AMP OUTPUTS
- 12 KEYPAD CONTROL
- SPEED/DIMMING POT.
- HARD-FIRED TRIACS


Kit 855 **£39.95**

LOTS OF OTHER APPLICATIONS

Now features full 4-channel chaser software on DISK and pre-programmed PIC16F84 chip. Easily re-programmed for your own applications. Software source code is fully 'commented' so that it can be followed easily.

ICEBREAKER

□□□□□□□□□□

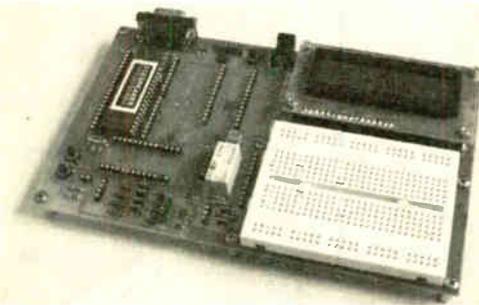

PIC Real Time In-Circuit Emulator

- Icebreaker uses PIC16F877 in circuit debugger
- Links to Standard PC Serial Port (lead supplied)
- Windows™ (95+) Software included
- Works with MPASM and MPLAB Microchip software
- 16 x 2 L.C.D., Breadboard, Relay, I/O devices and patch leads supplied

As featured in March '00 EPE. Ideal for beginners AND advanced users. Programs can be written, assembled, downloaded into the microcontroller and run at full speed (up to 20MHz), or one step at a time. Full emulation means that all I/O ports respond exactly and immediately, reading and driving external hardware.

Features include: Reset; Halt on external pulse; Set Breakpoint; Examine and Change registers, EEPROM and program memory; Load program, Single Step with display of Status, W register, Program counter, and user selected 'Watch Window' registers.

Kit 900 . . . **£34.99**

POWER SUPPLY £3.99 STEPPING MOTOR £5.99

EPE PIC Tutorial

At last! A Real, Practical, Hands-On Series

- Learn Programming from scratch using PIC16F84
- Start by lighting I.e.d.s and do 30 tutorials to Sound Generation, Data Display, and a Security System.
- PIC TUTOR Board with Switches, I.e.d.s, and on board programmer

PIC TUTOR BOARD KIT

Includes: PIC16F84 Chip, TOP Quality PCB printed with Component Layout and all components* (*not ZIF Socket or Displays). Included with the Magenta Kit is a disk with Test and Demonstration routines.

Kit 870 **£27.95, Built & Tested £42.95**

Optional: Power Supply - **£3.99, ZIF Socket - £9.99**

LCD Display **£7.99** LED Display **£6.99**

Reprints Mar/Apr/May 98 - **£3.00 set 3**

PIC TOOLKIT V2

- SUPER UPGRADE FROM V1
- 18, 28 AND 40-PIN CHIPS
- READ, WRITE, ASSEMBLE & DISASSEMBLE PICS
- SIMPLE POWER SUPPLY OPTIONS 5V-20V
- ALL SWITCHING UNDER SOFTWARE CONTROL
- MAGENTA DESIGNED PCB HAS TERMINAL PINS AND OSCILLATOR CONNECTIONS FOR ALL CHIPS
- INCLUDES SOFTWARE AND PIC CHIP

Kit 878 . . . **£22.99** with 16F84 . . . **£29.99** with 16F877

SUPER PIC PROGRAMMER

- READS, PROGRAMS, AND VERIFIES
- WINDOWS® SOFTWARE
- PIC16C6X, 7X, AND 8X
- USES ANY PC PARALLEL PORT
- USES STANDARD MICROCHIP
- HEX FILES
- OPTIONAL DISASSEMBLER SOFTWARE (EXTRA)
- PCB, LEAD, ALL COMPONENTS, TURNED-PIN SOCKETS FOR 18, 28, AND 40 PIN ICs

- SEND FOR DETAILED INFORMATION - A SUPERB PRODUCT AT AN UNBEATABLE LOW PRICE.

Kit 862 **£29.99**

Power Supply £3.99

DISASSEMBLER SOFTWARE **£11.75**

PIC STEPPING MOTOR DRIVER

INCLUDES PCB, PIC16F84 WITH DEMO PROGRAM, SOFTWARE DISC, INSTRUCTIONS AND MOTOR.

Kit 863 **£18.99**

FULL SOURCE CODE SUPPLIED ALSO USE FOR DRIVING OTHER POWER DEVICES e.g. SOLENOIDS

Another NEW Magenta PIC project. Drives any 4-phase unipolar motor - up to 24V and 1A. Kit includes all components and 48 step motor. Chip is pre-programmed with demo software, then write your own, and re-program the same chip! Circuit accepts inputs from switches etc and drives motor in response. Also runs standard demo sequence from memory.

8-CHANNEL DATA LOGGER

As featured in Aug./Sept. '99 EPE. Full kit with Magenta redesigned PCB - LCD fits directly on board. Use as Data Logger or as a test bed for many other 16F877 projects. Kit includes programmed chip, 8 EEPROMs, PCB, case and all components.

Kit 877 **£49.95** inc. 8 x 256K EEPROMS

MAGENTA

All prices include VAT. Add £3.00 p&p. Next day **£6.99**

Tel: 01283 565435 Fax: 01283 546932 E-mail: sales@magenta2000.co.uk

122000



Station Road, Cullercoats, Tyne & Wear, NE30 4PQ



All Major Credit cards Accepted... Prices Exclude Vat @17.5%. Add £1.25 (UK) carriage & Vat to all orders.

See Next / Last Months Ad. for COMPONENT ACCESSORIES

Table listing electronic components such as 4000 Series, 74HC Series, and 74LS Series with part numbers and prices.

Table listing electronic components including EPROMs, RAM, Bridge Rectifiers, A/D Converters, Data Acquisition, Thyristors, uControllers, Voltage Regulators, Diodes, and Linear ICs.

Table listing electronic components including Transistors, Diac, Electrolytic Radial, Electrolytic Axial, Resistors - Pleasa State Value Required, and Potentiometers - Pleasa State Value Required.

Table listing electronic components including Enclosed, 10mm Square, Potentiometers - Pleasa State Value Required, and Hardware & Tools Pack.

Quality Components Quantity Discounts Available

Tel: 0191 2514363 Fax: 0191 2522296 Email: sales@esr.co.uk http://www.esr.co.uk

EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

VOL. 29 No. 12 DECEMBER 2000

BUMPER

A bumper issue this month with the extra 16 pages devoted to Christmas projects. We have a regular problem with trying to fit everything into each issue, and I try to balance the content to appeal to a wide range of readers. With regular series like *Teach-In 2000* (Nov 1999 to Oct 2000) and now *The Schmitt Trigger*, plus a range of constructional projects and the regular features it's always a bit of a tight squeeze and sometimes it's difficult to know what to leave out. Only occasionally can we afford to go "over the top" with the number of pages to bring you extra content, we are, however, planning a couple more bumper issues for the Spring.

Incidentally, our educational series are always very popular and we are presently working at putting *Teach-In 2000* on a mini CD-ROM. The complete course, together with all the software, should soon be available in this form, hopefully there will be more news on this in the next issue.

DESIGN

We are often asked by readers how to design circuits and sometimes more specifically to tell them how we arrived at the values of each component in a particular circuit design – not something we can offer to provide, I'm afraid.

As an insight to the variations and complexity of circuit design the present *Schmitt Trigger* series should be an eye-opener for many readers. One *EPE* contributor has already commented that he did not realise there was so much to say about Schmitt Triggers – and that was after Part 1! This series is a little above the general level of theory we normally carry in *EPE*, but should interest those of you who are above the beginner level and who want to understand more about circuit design.

We can't promise to tell you everything there is to know about Schmitt Triggers, but you will certainly learn a lot.



AVAILABILITY

Copies of *EPE* are available on subscription anywhere in the world (see below), from all UK newsagents (distributed by COMAG) and from the following electronic component retailers: Omni Electronics and Yebo Electronics in S. Africa. *EPE* can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased for just \$9.99(US) per year available from www.epemag.com

SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the

UK: 6 months £14.50, 12 months £27.50, two years £50; Overseas: 6 months £17.50 standard air service or £27 express airmail, 12 months £33.50 standard air service or £51 express airmail, 24 months £62 standard air service or £97 express airmail.

Online subscriptions, for downloading the magazine via the Internet, \$9.99(US) for one year available from www.epemag.com.

Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Sub. Dept., Allen House, East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749. Fax: 01202 841692. E-mail: subs@epemag.wimborne.co.uk. Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard or Visa. (For past issues see the *Back Issues* page.)

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £5.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). *Normally sent within seven days but please allow 28 days for delivery – more for overseas.*

Payment in £ sterling only please. Visa and MasterCard accepted, minimum credit card order £5. Send, fax or phone your card number and card expiry date with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

Editorial Offices:

EVERYDAY PRACTICAL ELECTRONICS EDITORIAL
ALLEN HOUSE, EAST BOROUGH, WIMBORNE
DORSET BH21 1PF
Phone: Wimborne (01202) 881749
Fax: (01202) 841692.

E-mail: editorial@epemag.wimborne.co.uk
Web Site: <http://www.epemag.wimborne.co.uk>
EPE Online www.epemag.com

See notes on Readers' Enquiries below – we regret lengthy technical enquiries cannot be answered over the telephone.

Advertisement Offices:

EVERYDAY PRACTICAL ELECTRONICS ADVERTISEMENTS
MILL LODGE, MILL LANE
THORPE-LE-SOKEN, ESSEX CO16 0ED
Phone/Fax: (01255) 861161

Editor: MIKE KENWARD

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Administration: FAY KENWARD

Editorial/Admin: Wimborne (01202) 881749

Advertisement Manager:

PETER J. MEW, Frinton (01255) 861161

Advertisement Copy Controller:

PETER SHERIDAN, Wimborne (01202) 882299

On-Line Editor: ALAN WINSTANLEY

EPE Online (Internet version) Editors:

CLIVE (MAX) MAXFIELD and ALVIN BROWN

READERS' ENQUIRIES

E-mail: techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a **stamped self-addressed envelope or a self-addressed envelope and international reply coupons**. All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers (see *Shoptalk*). We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

E-mail: adverts@epemag.wimborne.co.uk

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.



PIC-MONITORED DUAL PSU



JOHN BECKER

Part One

Ever keen to add tools to the workshop, the author designs yet another, and finds more uses for a PIC16F877!

THE dual power supply unit (PSU) described here can be built in several forms.

At the simplest level it can be built with a single d.c. output switched for 5V or variable between about 6V and 9V. This shortened version is probably an ideal starter power supply for those who have been following the recent *Teach-In 2000* series and now wish to start adding workshop equipment.

This version will be described in Part 2, as will other constructional options. Some aspects of the main PSU have also been described in such a way as to reinforce the understanding of power supplies by *Teach-In 2000* readers.

It is emphasised that mains a.c. electrical power is dangerous and that construction of any of the versions of this power supply should only be undertaken (or supervised) by those who are suitably qualified or experienced.

FULL VERSION

The full version of the dual power supply provides PIC microcontroller monitoring of voltage and current, displaying the data on a liquid crystal display (l.c.d.). It has the specifications shown opposite.

Specifications

● **Dual channel**, switchable for series or parallel operation:

Two outputs per channel (four outputs total).

Output 1 switchable for fixed voltages of 5V, 6V, 9V, 12V, 15V or 18V.

Output 2 fully variable from about 0V up to 1V less than the switch-selected fixed voltage.

In series connection mode, the common rail of Channel B is connected to the selected fixed voltage of Channel A, providing a maximum output of +18V from Channel A and +36V from Channel B, or -18V from Channel A and +18V from Channel B.

All outputs are "floating" with respect to mains earth (ground) and any output can be regarded as the 0V (common) level.

● **Output monitoring:**

PIC16F877 microcontroller simultaneously monitors voltage and current for both outputs of both channels (four outputs).

Monitored data is output to a 2-line 16-character (per line) alphanumeric l.c.d.

The PIC controls l.e.d.s and buzzer in response to preset current limits being exceeded.

● **Display modes:**

1. Each channel's data shown individually, stating output voltage, output current, preset alarm-trip current. Channels switch-selectable on a cycle of four.

2. All four monitored voltages shown simultaneously.

3. All four monitored currents shown simultaneously.

● **Maximum output currents:**

Output 1 (switched voltage), 1A but see text and Table 6 later.

Output 2 (variable voltage), 350mA but see text in Part 2.

● **Current limiting:**

Output 2 can be set to limit the power supplied to the load circuit, using a panel control.



Each of the four outputs can have a maximum current limit set via pushbutton switches. If the preset current is exceeded, a light emitting diode (l.e.d.) indicates which channel is overloaded. A buzzer sounds if the total current drawn from either channel exceeds 1A. Physical limitation of the current supplied is *not* controlled by this option.

The PIC's EEPROM data memory retains the limit value set even when the power supply unit is switched off.

The basic block diagram for the power supply is shown in Fig.1. All controls are omitted except for the Series/Parallel switch.

TRANSFORMER

Illustrated in Fig.2 is the circuit diagram for the mains a.c. input and transformer. For use in the UK, transformer T1 should have the primary winding rated for 230V a.c. For the USA, the primary winding should be rated for 110V a.c. Readers from other countries should select the primary

It should be noted, though, that the output of the op.amp (a type LM358) can never fall to 0V. More typically the minimum output voltage available will be about 0.5V. Consequently, the minimum regulated voltage that can be set by VR1 will be about 5.5V. The maximum voltage will about 2V below the rectified voltage fed into the input of regulator IC1.

In Fig.3, switch S2 selects whether IC1's common pin is connected to 0V (for fixed 5V output) or to the op.amp's output (for variable voltage control).

SWITCHED SUPPLY

For the full power supply design, the circuit of Fig.3 is expanded to become that in Fig.4.

Here the single potentiometer of Fig.4 has been replaced by a chain of six resistors, providing a tapped potential divider whose nodes are selected by rotary switch S2a. The reason for the inclusion of resistor R3 will be stated presently.

Capacitor C4 and resistor R2 are included to minimise voltage surges when the voltage range is switched. A smoothing capacitor is NOT connected between the op.amp's output and the 0V line since it was found that this could cause oscillation in the regulated supply.

Switch S2b replaces S2 of Fig.3, selecting between 5V and the preset output voltage from the buffering op.amp.

POTENTIAL CALCULATIONS

When considering the design of this power supply, the author originally believed that the tapped controlling voltages fed to the op.amp would need to be provided via individual preset potentiometers, each set for a different bias voltage, 5V below the required output from the regulator. The first constructed model actually used presets.

Initial calculations for a fixed multi-node potential divider had showed that the required resistors would have unusual values. The calculations were based on a total resistance across the divider of 10kΩ (as used for the basic potentiometer control).

As an example, and referring to Fig.5, consider the situation for $V_{out} = 6V$:

$$R_{total} = R_x + R_y = 10k\Omega$$

$$V_{out} = 6V$$

$$V_{bias} = V_{out} - 5V = 1V$$

(5V is the voltage differential between IC1's output and common pins)

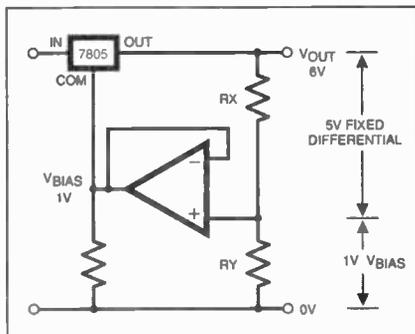


Fig.5. Potential divider use to control the voltage output from regulator IC1 at 6V.

Using the potential divider formula of:

$$V_{bias} = V_{out} \times (R_y / R_{total})$$

the equation can be stated as:

$$1V = 6V \times (R_y / 10k)$$

Making R_y the subject produces the equation:

$$R_y = (1V / 6V) \times 10k = 1.666667k$$

Thus R_x becomes:

$$R_{total} - R_y = 10k - 1.666667k = 8.333333k$$

Table 1 shows the individual resistor values in the divider chain of Fig.6 calculated for all five required output voltages. The calculations were produced by the QBasic program in Listing 1, in which R_{total} is the total resistance set at 10 (the "k" factor being omitted).

Table 1

IDEAL VALUES for $R_{total} = 10k$		
Vout	Vbias	Resistor
6V	1V	R1 1.666667k
9V	4V	R2 2.777778k
12V	7V	R3 3.388889k
15V	10V	R4 8.333332k
18V	13V	R5 5.555557k
$R6 = R_{total} - (R1 + R2 + R3 + R4 + R5) = 2.777778k$		

The calculations were originally done by hand without the computer program. However, in an idle moment some weeks after building the power supply, the author gave the problem to the computer, using Listing 1. Calculations were made for several different values of R_{total} . A value for R_{total} of 11(k) produced the results shown in Table 2.

Table 2

IDEAL VALUES for $R_{total} = 11k$		
Vout	Vbias	Resistor
6V	1V	R1 1.833333k
9V	4V	R2 3.055556k
12V	7V	R3 5.277778k
15V	10V	R4 9.166668k
18V	13V	R5 6.111109k
$R6 = R_{total} - (R1 + R2 + R3 + R4 + R5) = 3.055555k$		

Since these values appeared to be close to the available E24 series values, a second program was written (Listing 2). In the program, the calculated output voltages were derived for a divider chain comprised of E24 values nearest to those in Table 2, i.e. 1k8, 3k, 1k5, 910Ω, 620Ω, 3k. The results are shown in Table 3.

Table 3

E24	Values	Vout
R1	1k8	5.996678V
R2	3k	8.9801V
R3	1k5	11.95364V
R4	910Ω	14.95856V
R5	620Ω	18.05V
R6	3k	
$R_{total} = 10.83k$		

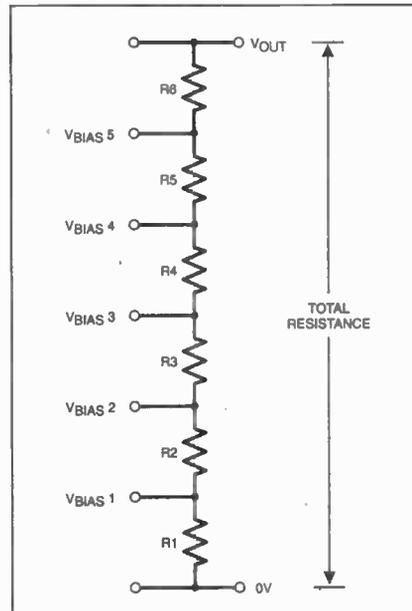


Fig.6. Basic potential divider chain used for voltage control selection.

LISTING 1

```
DATA 6,9,12,15,18: ' required Vout
rtotal = 10: m = 0
PRINT "IDEAL VALUES for Rtotal";
PRINT " = "; rtotal; "k"
PRINT "Vout"; TAB(10); "Vbias";
PRINT TAB(20); "Resistor"
FOR a = 1 TO 5: READ vout
vbias = vout - 5
r(a) = ((vbias / vout) * rtotal) - m.
rn = rn + r(a)
PRINT vout; "V"; TAB(10); vbias;
PRINT "V"; TAB(20); "R";
PRINT LTRIM$(STR$(a));
PRINT r(a); "k": NEXT
PRINT "R6 =
Rtotal-(R1+R2+R3+R4+R5)";
PRINT " = "; rtotal - rn; "k"
```

LISTING 2

```
DATA 1.8,3.0,1.5,910,620,3.0
PRINT : PRINT "E24 VALUES";
PRINT TAB(16); "CURRENT";
PRINT TAB(31); "Vout"
FOR a = 1 TO 6: READ r(a)
t = t + r(a): NEXT
ry = 0: rx = t
FOR a = 1 TO 5
rx = rx - r(a)
ry = ry + r(a)
I = 5000 / rx
v = (I * ry) / 1000 + 5
PRINT "R"; a; " = "; r(a); "k";
PRINT TAB(15); I; "mA";
PRINT TAB(30); v; "V": NEXT
PRINT "R"; a; " = "; r(a); "k";
PRINT TAB(20); "Rtotal = "; t; "k"
```

Table 4

Ideal	Chan 1	Chan 2
5V	4.97V	4.98V
6V	5.97V	5.98V
9V	8.93V	8.94V
12V	11.86V	11.87V
15V	14.84V	14.74V
18V	17.91V	17.82V

The values in Table 3 were considered to be close enough to the ideal for them to be acceptable. In practice, they will differ slightly because of resistor tolerance factors. Those obtained with the prototype are given in Table 4 (note that even the "fixed" 5V output of the two regulator i.c.s is not exactly 5V).

The basic formulae used in the programs are those for potential dividers, as given earlier (Listing 1), and Ohm's Law (Listing 2), $V = I \times R$.

Referring to Fig.5, the voltage (call it V_b) across R_x is automatically specified as 5V, and thus the current (I) flowing through R_x is calculated as:

$$I = V_b / R_x$$

The current flowing through a potential divider chain is constant at whatever point in the chain it is measured. Consequently, the same current flows through R_y as flows through R_x .

Therefore the voltage drop across R_y (V_{bias}) simply equals $I \times R_y$, and so the regulated output voltage (V_{out}) for the specified values of R_x and R_y is V_{bias} plus 5V.

As an example, and referring to Fig.6 and the resistor values in Table 3, to find V_{out} when V_{bias} at the junction of R_5 and R_6 is selected (V_{bias5}), the following reasoning is used:

Since a voltage of 5V exists across R_6 (3k), then a current of $5V/3k = 1.666667mA$ flows through R_6 (Ohm's Law derivative $I = V/R$). Consequently the voltage drop (V_{bias}) across the total of $R_1 + R_2 + R_3 + R_4 + R_5$ (7.83k) is calculated as $1.666667mA \times 7.83k = 13.05V$. Thus the regulated output voltage $V_{out} = V_{bias} + 5V = 18.05V$, as listed in Table 3.

As a result of these calculations, the pre-sets were dropped from the prototype and a resistor chain substituted instead, as shown in Fig.4 earlier. (All of which confirms the author's belief that a computer is one of his most important workshop tools!)

The two programs listed can be modified to calculate other tapped potential divider characteristics, for as many nodes are required.

CURRENT MONITORING

The switched voltage from IC1 (Fig.4) is taken to the output sockets (SK1 to SK5) via a 1Ω resistor, R_3 . This allows current flow to be monitored, according to the voltage drop across R_3 caused by the amount of current flowing (Ohm's Law again). The resistor is included in the bias setting (potential divider) chain to maintain the correct output voltage irrespective of load currents.

Op.amp IC2b is configured as a differential amplifier. The voltage to either side of R_3 is fed to the op.amp's inputs (pins 5 and 6) and the amplified difference is routed to the PIC microcontroller (discussed later) from point V2. The gain as seen by changes in voltage on the non-inverting input is about ten, as set by R_{10} and R_{11} ($R_{11} / R_{10} + 1$).

If current monitoring is not required, the circuit around IC2b may be omitted and the switched voltage fed to the output sockets, SK1 to SK5, from point V1. R_3 must be replaced by a wire link.

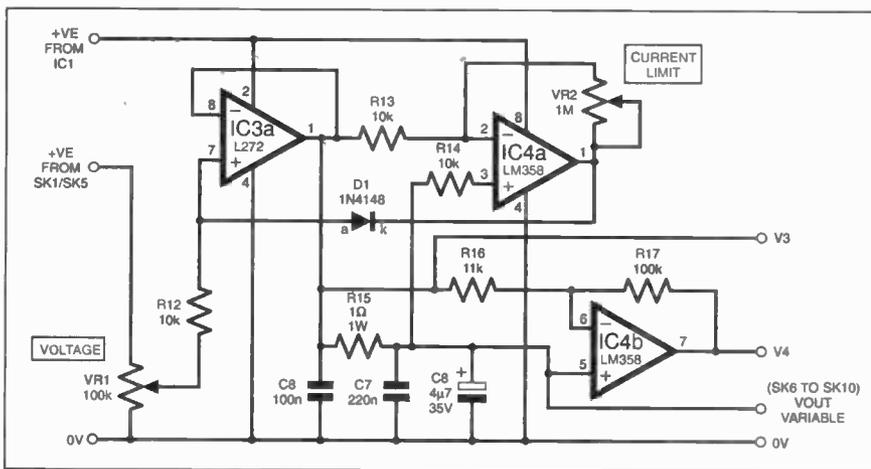


Fig.7. Variable voltage and current limiting circuit.

VARIABLE SUPPLY

As it stands, the circuit in Fig.4 is perfectly usable on its own, with or without current monitoring. However, the author frequently has the need for a control voltage that can be varied from 0V upwards. Whilst a potentiometer across a fixed supply can provide such a voltage via its wiper, the current available is limited by the resistance at the wiper.

Consequently, this power supply has had a buffer circuit added, the circuit diagram for which is shown in Fig.7.

The buffer is formed around op.amp IC3a, one half of an L272 dual power op.amp (the other half is unused). The L272 is capable of supplying a current of 1A, but there are limitations imposed by the circuit, as discussed presently.

Power for the op.amp is taken from the switch-selected voltage output from regulator IC1. Potentiometer VR1 is also connected across the same supply, but following resistor R_3 , and its wiper voltage is fed via resistor R_{12} to the non-inverting input of IC3a, pin 7.

The op.amp's output from pin 1 could be used directly as a variable voltage supply via the connection marked V3. However, as with the switched supply, it has a 1Ω resistor (R_{15}) in series with it, through which the voltage is fed to the output sockets (SK6 to SK10). This allows current flow to be monitored via differential amplifier IC4b, which has the same function as IC2b, outputting an amplified current-dependent voltage to the PIC.

CURRENT LIMITING

The variable supply has been given a simple current limiting facility, via the circuit around IC4a.

This circuit is also configured as a differential amplifier, monitoring the voltage across R_{15} and amplifying it according to the ratio of R_{13} and the resistance across potentiometer VR2.

The output of IC4a is connected back to the non-inverting input of IC3a via diode D1. If the current through R_{15} causes the amplified output voltage from IC4a to fall 0.7V (the "diode drop" voltage for a silicon diode) below the voltage on IC3a pin 7, the latter will be pulled down across resistor R_{12} . The result is that the output voltage from IC3a will fall by the same amount, so limiting the power fed to the load circuit.

Potentiometer VR2 permits the threshold gain to be varied from roughly unity ($VR_2 = 0\Omega$) to about 100 (VR_2 at maximum resistance). By test on the prototype, with VR2 at zero resistance, a current flow of about 350mA through R_{15} causes the threshold to be reached, beyond which the input to IC3a is progressively reduced. With VR2 at maximum resistance, 5mA across R_{15} has the same effect.

Any circuit powered from the variable supply must have a smoothing capacitor across its input power lines in order to prevent the current limiting circuit from oscillating when the threshold is reached. Without the capacitor, when the threshold is reached the output voltage falls, and so the current flow decreases, causing the voltage to rise again, etc.

Note that the presence of R_{15} on its own will also cause a voltage drop at the output sockets in response to increasing current, simply according to Ohm's Law (100mA causes a 0.1V drop).

PIC MONITOR

The PIC microcontroller, IC6 in Fig.8, monitors the voltages input to it from the four power supply circuits, outputting data to the l.e.d.s. and the l.c.d. It interprets and displays the data according to factors input to it from switches S3 to S6. It does not actually control the power supply in any way.

As discussed in previous published PIC16F87x designs, this family of devices has several inputs which can be used for analogue-to-digital conversion. The PIC16F877 used here has eight A/D inputs, allowing the twin voltage levels from all channels to be monitored.

For each channel, the twin voltages are tapped prior to the 1Ω current sensing resistor and at the output of the respective differential amplifier.

The voltages can be several times greater than the PIC can safely handle and are attenuated by eight 20k/2k2 potential dividers, formed around R_8 to R_{33} . The attenuation ratio is 1:10, which at first sight may seem high.

The reason is that Channel B can be connected in series with Channel A (refer back to Fig.1). In this situation, Channel B can produce a possible maximum voltage of 36V with reference to the PIC's 0V line. The 1:10 attenuation thus results in 3.6V at the input to PIC. Whilst a ratio of 5:36 (1:7.2) would allow slightly greater

precision of the digital conversion, a ratio of 1:10 makes the software processing somewhat easier.

The software repeatedly samples the eight inputs, and produces 10-bit conversion values. From these it calculates the source voltages prior to the attenuators. The value of the voltage prior to each 1Ω resistor is stored for output to the l.c.d.

This value is also compared with the voltage from the respective differential amplifier and a value for the current being drawn by the load circuit is calculated. This too is stored for subsequent output to the l.c.d.

The current values are additionally compared with the current limit values preset via switches S3 to S5. If the limit is being exceeded, the appropriate l.e.d. (D3 to D6) is turned on. Resistors R39 to R42 are the l.e.d. ballast resistors.

If the total current being supplied by a channel, via either or both of its outputs, exceeds 1A then both l.e.d.s for that channel are turned on, as is buzzer WD1.

The current being drawn must be reduced below the limits before the l.e.d.s and buzzer are turned off.

Remember that the PIC does not control the power supply in response to these limits being reached.

L.C.D. MODULE

Data is sent to the l.c.d. module (X2) in 4-bit mode, with the same physical pin connection order as used with all the author's l.c.d. controlling designs over the last couple of years.

Readers who already have l.c.d.s with connectors that match those designs can simply plug them straight in to this Power Supply's monitor p.c.b. via the matching terminal pins (notated as TB1).

Preset potentiometer VR3 adjusts the l.c.d. screen contrast.

A point worth considering is whether or not to use a back-lit l.c.d. The author's workshop is well lit and the screen of the normal reflective type of l.c.d. used can be clearly seen.

In a less well-lit situation, however, the use of a (slightly more expensive) back-lit version could be beneficial, because the screen is on the front panel and faces forwards, rather than upwards as with the majority of published designs using l.c.d.s.

Typically, back-lit l.c.d.s have illumination provided by internal l.e.d.s. It is possible that the l.e.d.s can be powered from the monitor board's 5V supply (check the l.c.d. data sheet for the backlighting power requirements and connections). If this is the case, it would be prudent to use a 7805 1A regulator for IC5, instead of the 78L05 100mA device listed.

CONTROL SWITCHES

Pushbutton switches S3 to S5 allow the PIC's current limiting data to be changed as required. S6 selects which of three display modes is shown: full data for one output, voltage data for all four outputs, or current data for all four outputs. Each push of S6 steps the display through the modes, on a repeating cycle.

When in the mode for single-output full data display, switch S5 steps the display through each output, on a repeating cycle of four. Typical displays are shown in Part 2.

Top left of the screen shows the output identity. This is notated in the form Ch1 to Ch4, where:

- Ch1 = Channel A switched output
- Ch2 = Channel A variable output
- Ch3 = Channel B switched output
- Ch4 = Channel B variable output

Top right of the screen shows the preset current limit for that output. It can be increased by S4 or decreased by S3. The limit is changed in steps of 10mA, with a minimum of 10mA and a maximum of 1A.

When S3 or S4 are released, the value displayed is stored in the PIC's EEPROM data memory. It remains there even after power has been switched off. It is recalled when the unit is again switched on.

Bottom left of the screen shows the voltage presently supplying the selected output (before the 1Ω resistor), in steps of 0.05V.

Bottom right of the screen shows the current being drawn from the output, in steps of 5mA.

Be mindful of the fact that the monitored voltage and current details on the l.c.d. screen are not as precise as those which a multimeter will display. They should be treated only as an approximate guide to prevailing conditions.

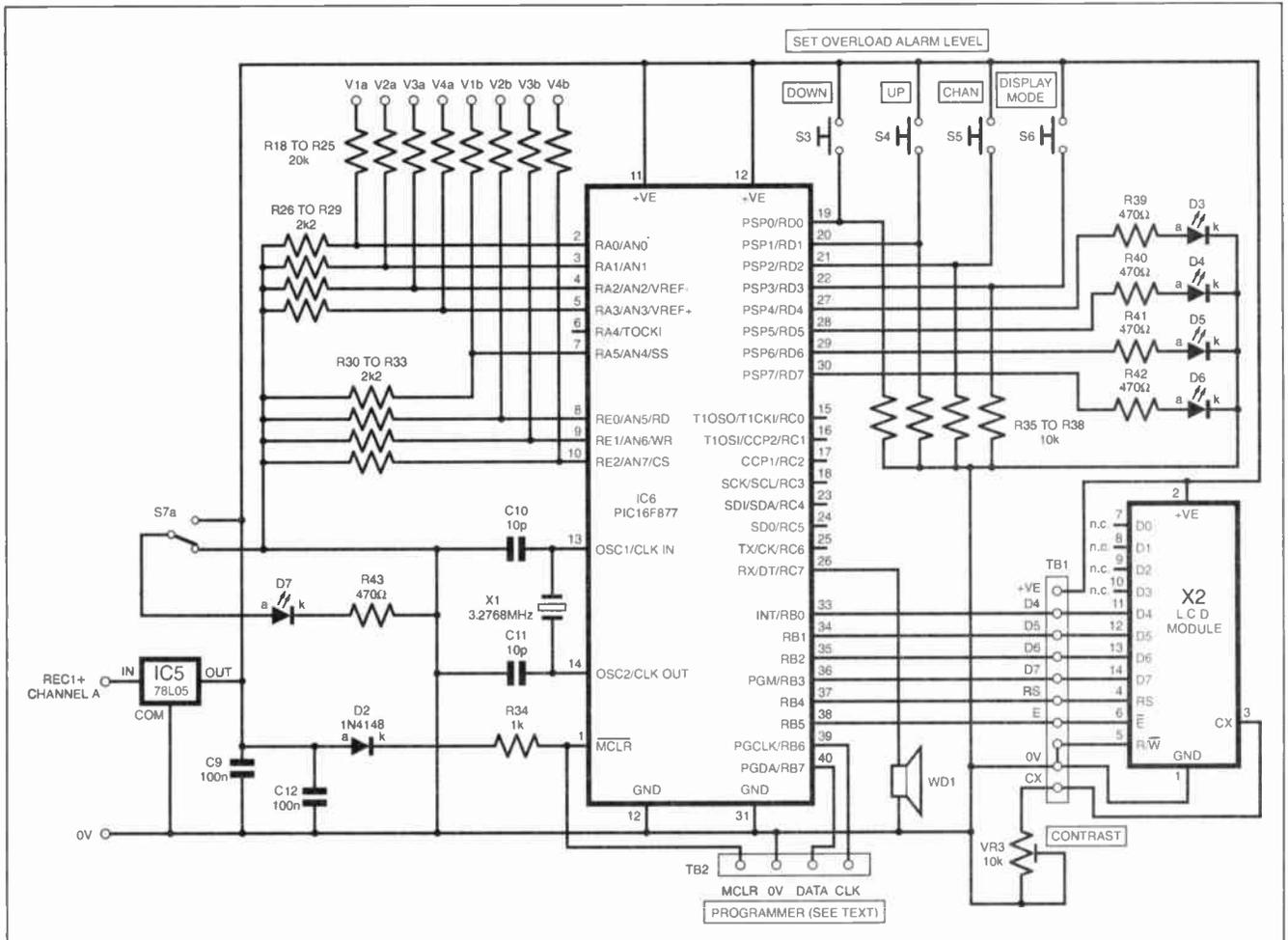


Fig.8. Circuit diagram for the PIC-monitoring option of the full power supply.

COMPONENTS

SINGLE FULL PSU CHANNEL Excluding the PIC monitoring circuit

Resistors

R1	1k 0.25W 5%
R2	1M 0.25W 5%
R3, R15	1Ω 1W 5% (or better) (2 off)
R4, R8	3k 0.25W 1% (2 off)
R5	620Ω 0.25W 1%
R6	910Ω 0.25W 1%
R7	1k5 0.25W 1%
R9	1k8 0.25W 1%
R10, R16	11k 0.25W 1% (2 off)
R11, R17	100k 0.25W 1% (2 off)
R12 to R14	10k 0.25W 5% (3 off)

Potentiometers

VR1	100k lin rotary
VR2	1M lin rotary

Capacitors

C1	4700μF radial elect. (see text)
C2, C7	220n ceramic disc, 5mm pitch (2 off)
C3 to C6	100n ceramic disc, 5mm pitch (4 off)
C8	4μ7 radial elect. 35V

Semiconductors

D1	1N4148 silicon signal diode
IC1	7805 +5V 1A voltage regulator
IC2, IC4	LM358 dual op.amp (2 off)
IC3	L272 dual power op.amp

Miscellaneous

REC1	W005 50V 1A bridge rectifier, or similar
S1	s.p.d.t. switch, mains rated
S2	2-pole 6-way rotary switch
SK1 to SK15	2mm socket, 3 colours, 5 off each (see text)

Printed circuit board (power supply), available from the *EPE PCB Service* code 280; knob (3 off); TO220 insulating washer kit for IC1; 8-pin d.i.l. socket (3 off)

All above parts repeated for second channel.

Also required

FS1	20mm fuseholder, panel mounting, with 1A 20mm fuse, slow blow
T1	mains transformer, 0-15V, 0-15V secondaries, 50VA (25VA per winding)

Metal case, 255mm × 160mm × 196mm (see text); heatsink compound (see text); eyelet tag; mains cable clamping grommet; nuts and bolts for mounting transformer (2 off each); cable ties; 1mm terminal pins; 3-core mains cable, 5A; connecting wire; solder, etc

Approx. Cost
Guidance Only

£30
excluding case


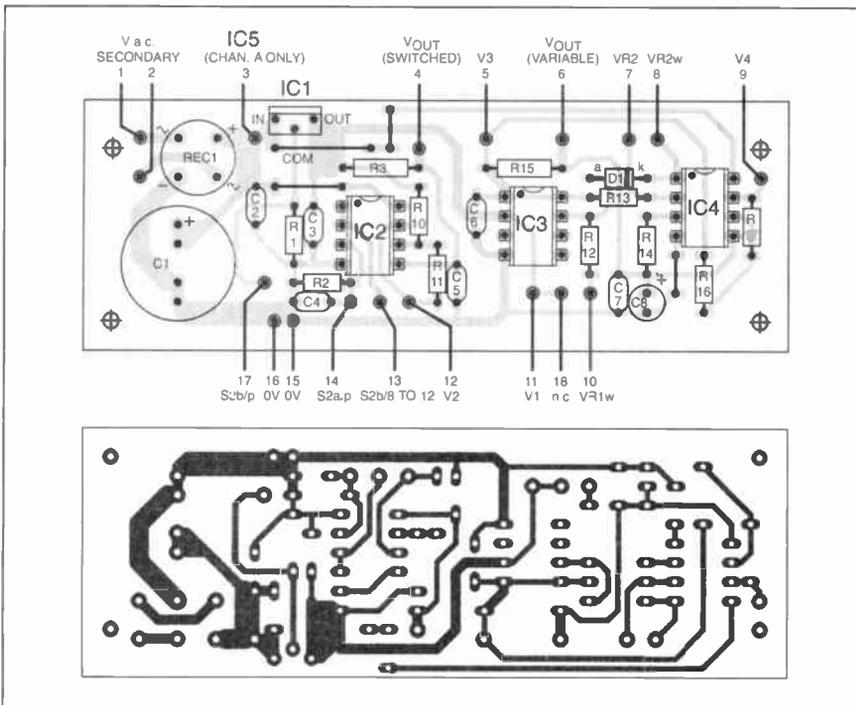


Fig.9. Printed circuit board component layout and full size copper foil master track pattern for the power supply in Fig.4.

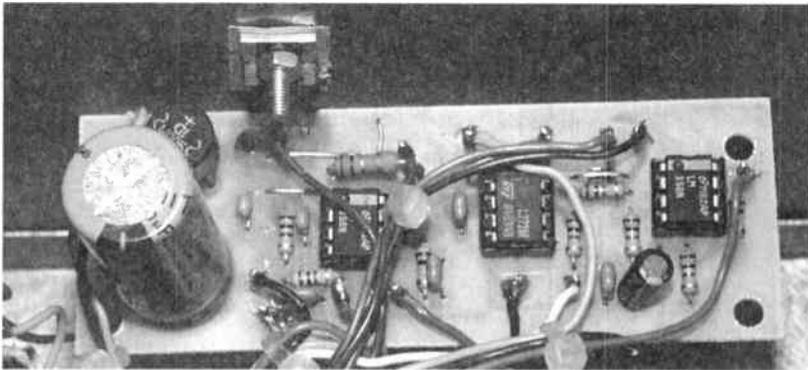

MISCELLANY

The PIC and I.c.d. are powered at 5V. This is provided by regulator IC5, whose input is connected directly to the rectified voltage at capacitor C1 (approximately 20V) of Channel A. The current drawn, with the I.e.d.s inactive, is a little under 6mA.

Crystal X1 sets the PIC's clock frequency at 3.2768MHz.

Selection of parallel or serial connection of Channels A and B is made by switch S7b in Fig.1 earlier. In Fig.8, S7a is the second half of the same switch and turns on I.e.d. D7 when the channels are connected in series.

CONSTRUCTION

There are two printed circuit boards, one for the PIC monitoring circuit, the other for the power supply components of a single channel (two are needed if both channels are required).

Their constructional and track layout details are shown in Fig.9 and Fig.10. The boards are available from the *EPE PCB Service*, code 281 for the monitor and 280 for the power supply.

Preferably assemble the components in ascending order of size, commencing with the on-board link wires. Use sockets for IC2, IC3, IC4 and IC6. Do not insert IC6 (the PIC) into its socket until a few circuit

tests have been made later. Ensure the correct orientation of all other semiconductors and the electrolytic capacitors.

Mount the rectifier (REC1) and 1Ω resistors (R3 and R15) so that their bodies stand a bit above the p.c.b., allowing air to circulate around them. Also mount regulator IC1 somewhat above the p.c.b. to allow it to be easily bolted to the side of the case during the final stages of connecting up.

For terminal pin blocks TB1 and TB2 use 1mm pin-header strips. For the other off-board connection points insert 1mm terminal pins.

CASE PREPARATION

The case used in the prototype and shown in the photographs is one which the author has had for some years. Regrettably it has been discontinued by the supplier, but an alternative case of a similar size is quoted in *Shoptalk*. The size of the original is 255mm × 160mm × 196mm (l × h × d). The detachable front and rear panels measure 245mm × 135mm. They are made from aluminium, whilst the rest of the case is mild steel.

Referring to the photographs, plan and drill your chosen case with care. Allow ample clearance between all mains powered connections and other items. Use a clamping cable grommet for the mains input lead.

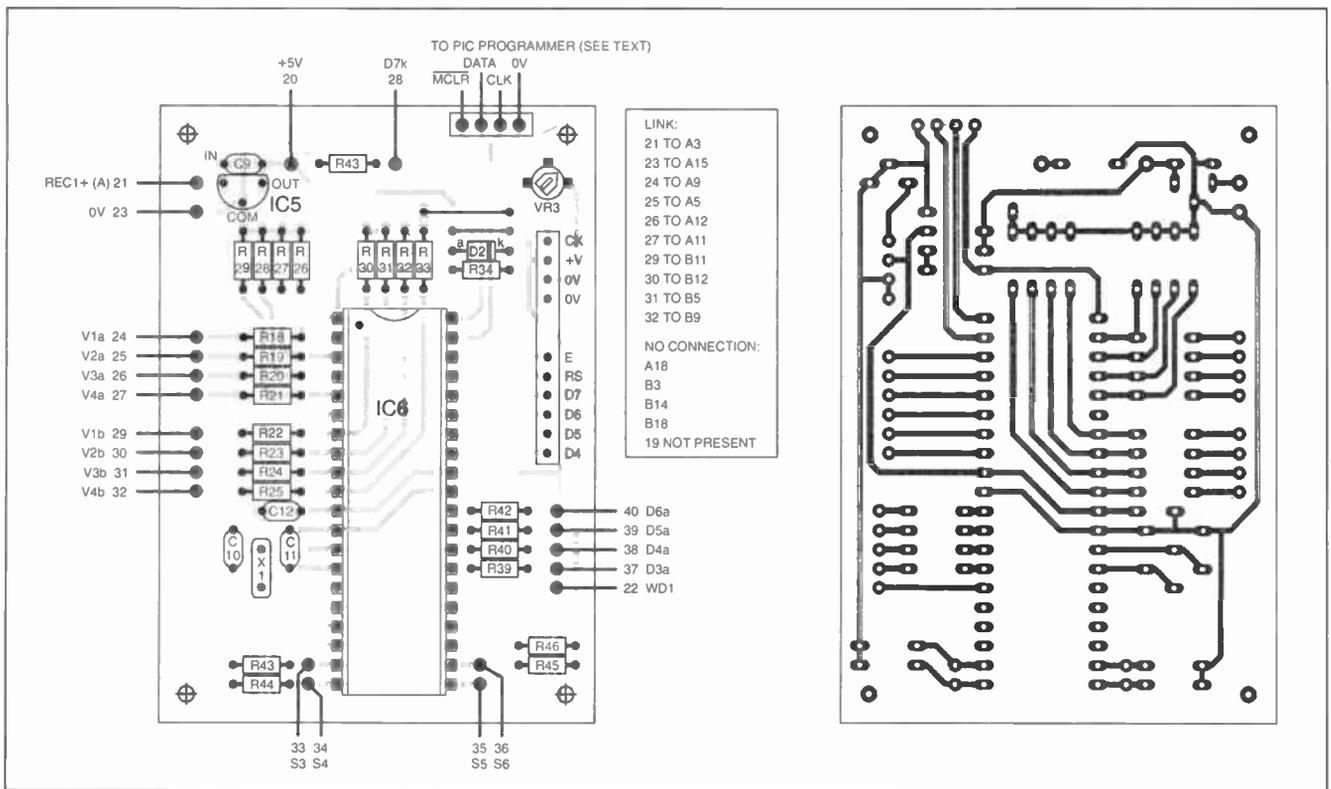


Fig. 10. Component layout and full size copper foil master track pattern for the PIC-monitoring circuit in Fig.8.



If you prefer to use output sockets of a larger size to the 2mm type used in the prototype, you may not have room for the same quantity. The author prefers having several sockets connected to a single power supply output, allowing several circuits to be powered simultaneously from the same source.

Allow reasonable space for the control knobs to be rotated.

Mark the i.c.d. position carefully, then drill a succession of holes inside the perimeter of its screen position to ease the sawed removal of the oblong cut-out. Finish off with a file.

The i.e.d.s in the prototype were purchased as panel mounting components complete with pre-connected leads. Conventional i.e.d.s and mounting clips may be used instead. The wiring diagram in Part 2 shows the connections for the latter type.

Drill a hole in each side panel through which the IC1 regulators have to be bolted, attached to their p.c.b. Insulating washers and bushes should be used with the regulators, together with heatsink compound (some types of washer do not require the compound – consult your supplier when ordering the washers).

It is essential to check that there is no electrical connection between the case and the tabs of the regulators.

NEXT MONTH

In the concluding part next month the wiring up of the full power supply is detailed, heat sinking is discussed, and operation of the software is described. Details of constructing simpler versions will also be given.

See this month's *Shoptalk* page for information on obtaining the software, and general information on buying the components.

COMPONENTS		Approx. Cost Guidance Only	£30 excluding case
MONITOR UNIT			
Resistors	See SHOP TALK page	D3 to D7 red i.e.d. (5 off) (see text)	
R18 to		IC5	78L05 +5V 100mA voltage regulator (see text)
R25		IC6	PIC16F877-4 microcontroller, pre-programmed (see text)
R26 to		Miscellaneous	S3 to S6 s.p. min. push-to-make switch (4 off)
R33		S7	d.p.d.t. min. toggle switch
R34		TB1, TB2	1mm pin header strips (see text)
R35 to		WD1	5V to 9V active buzzer
R38		X1	3.2768MHz crystal
R39 to		X2	2-line, 16-character (per line) liquid crystal display (see text)
R43			
Capacitors			
C9, C12			
C10, C11			
Potentiometer			
VR3			
Semiconductors			
D2			

Printed circuit board, available from the *EPE PCB Service*, code 281 (monitor); 40-pin d.i.l. socket; nuts and bolts for i.c.d. (4 off each); cable ties; connecting wire; solder, etc.

The FED PIC C Compiler - Rapid, Efficient, High level development


FED PIC C Compiler – Version 3.0 now available

- Designed to ANSI C Standards
- Complete development environment includes Editor, assembler, simulator, waveform analyser and terminal emulator (see screenshot below)
- Libraries include serial interfaces, 12C, LCD, keypads, delays, string handling, hardware etc.
- Simulator runs up to 10 times faster than MPLAB, allows inputs to be defined, multiple breakpoint types, single stepping, step over etc.
- Supports all 14-bit core PIC's – 12C67x, 16C55x, 16C6x, 16C7x, 16C8x, 16C87x, etc.
- Will produce code for MPLAB

LEARN to Program PIC's in C with FED!

With the FED introductory manual:
"Learn to program PIC's with FED PIC C"


- Suitable for complete beginners to PIC's or to the C programming language
- Leads through example
- Introduces simple C programs, then covers variables and casting, pointers, structures and unions, functions, etc.
- All examples will run fully within the simulator, or on the FED 16F84 and 16F877 development boards
- Covers use of interrupts and programming for real time applications
- Hints and tips on good programming practice with the PIC
- Full examples of debugging using FED PIC C are included
- Included FREE on our PIC C Compiler CD ROM, or available in paper copy
- Available only to existing or new customers for our C Compiler.

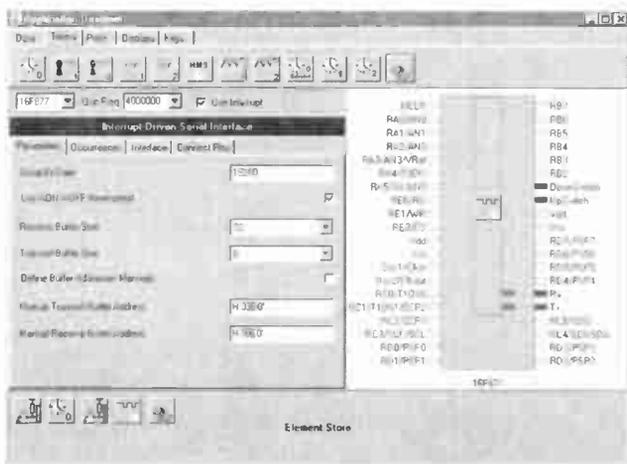

Prices (reductions for PICDESIM/WIZPIC users)
C Compiler with all manuals on CD ROM £60. CD ROM with printed manuals £75.
Upgrade – PICDESIM/WIZPIC users £45.00 CD ROM.
"Learn to program PIC's with FED PIC C" – £7.50.

Programmers for PIC & AVR

PIC Serial Programmer (Left)

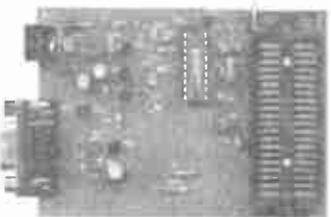

Handles serially programmed PIC devices in a 40-pin multi-width ZIF socket. 16C55X, 16C6X, 16C7X, 16C8x, 16F8X, 12C508, 12C509, 16C72XPIC 14000, 16F87X, etc.

Also In-Circuit programming. Operates on PC serial port

Price : £45/kit
£50/built & tested

PIC Introductory – Programs 8 & 18 pin devices : 16C505, 16C55X, 16C61, 16C62X, 16C71, 16C71X, 16C8X, 16F8X, 12C508/9, 12C671/2 etc. **£25/kit.**

AVR – AVR – 1200,2313,4144,8515, 8535, 4434 etc. in ZIF. 4.5V battery powered. **Price : £40 for the kit or £45 built & tested.**

All our Programmers operate on PC serial interface. No hard to handle parallel cable swapping ! Programmers supplied with instructions, + Windows 3.1/95/98/NT software.

Upgrade programmers from our web site !

WIZPIC

PIC Visual Development



- Rapid Application Development for the PIC microcontroller
- Drag and drop your software component selections on to your design

- Included components support timers, serial interfaces, I2C, LCD, 7-Seg displays, keypads, switches, port controls, and many more.
- Connect software components to PIC pins by point & click using the mouse
- Set parameters for each component from drop down list boxes, check boxes, or text entry
- Links your code automatically into library events (e.g. Button Pressed, Byte Received etc)
- Up to 10 times faster than MPLAB
- Supports all 14-bit core PIC's -12C67x, 16C55x, 16C6x, 16C7x, 16C8x, 16C87x etc.

Cost – CD-ROM with Data sheets and application notes – £35.00, Floppy version £30.00.

Forest Electronic Developments

60 Walkford Road, Christchurch, Dorset, BH23 5QG.

E-mail – info@fored.co.uk, or sales@fored.co.uk

Web Site – <http://www.fored.co.uk>

01425-274068 (Voice/Fax)

Prices are fully inclusive. Add £3.00 for P&P and handling to each order. Cheques/POs payable to Forest Electronic Developments, or phone with credit card details.



16F877

Fully supported by WIZPIC, PICDESIM, the serial programmer and our C Compiler.

16F877-04 £5.50
16F877-20 £6.00

MOBILE PROMISES . . . PROMISES . . .

Can Packet Radio make marketplace headway if it does not fulfil promised expectations? Barry Fox reports.

THE cellphone industry risks crippling the fledgling market for GPRS by making the same kind of undeliverable promises that turned users off WAP.

GPRS, the new General Packet Radio Service due for consumer launch this Christmas, is already being wildly overhyped. It will deliver much slower data speeds than promised and looks sure to disappoint – like WAP before it.

"Who needs 3G (the third generation cellphone system due in a few years), when GPRS is here now," asks Motorola, the first company to deliver GPRS handsets. BT, now trialling the first commercial GPRS service, says "accessing video and multimedia applications on your mobile phone is now a reality."

"GPRS opens the mobile market to wireless multimedia," promises Motorola's web site, "with streaming and live video content."

Technical and medical issues make even the theoretical speeds unattainable.

TIME SLOTS

The European GSM digital cellphone system is now used in most countries. Channels 25kHz wide are sliced into eight time slots. Each slot carries a separate conversation, or data, at 9.6Kbps, one sixth the speed of a fixed phone line and modem. Users are charged for the time they use a slot.

GPRS lets users share time slots, with charges levied for data moved, not time on line. Several coding systems are used to protect against transmission errors. CS-1 has the most powerful error correction, but delivers only 9.05Kbps per slot. Where the radio signal is strong, CS-2 coding delivers 13.4Kbps.

Some of this data is wasted on "headers" needed to label Internet data. The data rate also varies depending on how many people are sharing slots. Most important, four or five slots can eventually be used for reception, a handset or PC card can transmit only one or two slots before the chips get too hot and burn out. Above two slots there is a health risk from excessive radiation (Specific Absorption Rate). Battery drain doubles for two slot working, so life halves.

Motorola's first GPRS phones, such as the Timeport, will handle only one time slot out of the phone and two into the phone. New phones next year will work with one slot out and four down. The first models are not upgradeable. Ericsson will wait and launch with one out and four down.

EXPERT OPINIONS

Rainer Lischetzki of Motorola says, "The realistic maximum rates we can get from GPRS are 64Kbps into the handset and 30Kbps out. We have known for ages about these limitations. We regret the sales talk, and data rate exaggeration."

A BT Cellnet engineer was privately even more conservative, promising only between 7Kbps and 10Kbps per slot, or a best case scenario next year of 10Kbps transmit and 40Kbps receive.

But Motorola's own web site and technical briefing documents promise speeds up to 171.2Kbps with "streaming and live video content", while BT's

publicity literature promises the chance to "send and receive data up to five times faster than is currently possible . . . and speeds will increase up to ten times faster in the coming months."

Because GPRS is an always-on system, with charges for the quantity or quality of data handled, rather than time on line, it becomes the ideal tool for receiving E-mail on the move. But people who believe the publicity and buy GPRS as a mobile multimedia tool will be sorely disappointed. Even low quality mono sound needs two time slots; MPEG-4 videophone links can manage only one or two coarse video pictures a second.

IT SUCKS – IN STYLE!




THE new Shesto Pal range of suction pick-up tools is invaluable for model making, craft and hobby uses, and they work without batteries.

Held like a pen, a gentle press of the button or bulb creates the correct amount of pressure to pick up, rotate and easily place small objects. To release them simply press the button again. The tools easily handle electronic components and a variety of other materials without risk of damage or blemish.

There are two models: the Model Pal at £7.95, comprising suction bulb and three cups, and the Hobby Pal at £14.95, which includes suction generator, four cups, two straight holders and two angled holders. The prices are quoted as *post free*.

For more information contact Shesto Ltd., Dept EPE, Unit 2, Sapcote Trading Centre, 374 High Road, Willesden, London NW10 2DH. Tel: 020 8451 6188. Fax: 020 8451 5450. E-mail: sales@shesto.co.uk. Web: www.shesto.com.

GREENWELD AND KITMASTER

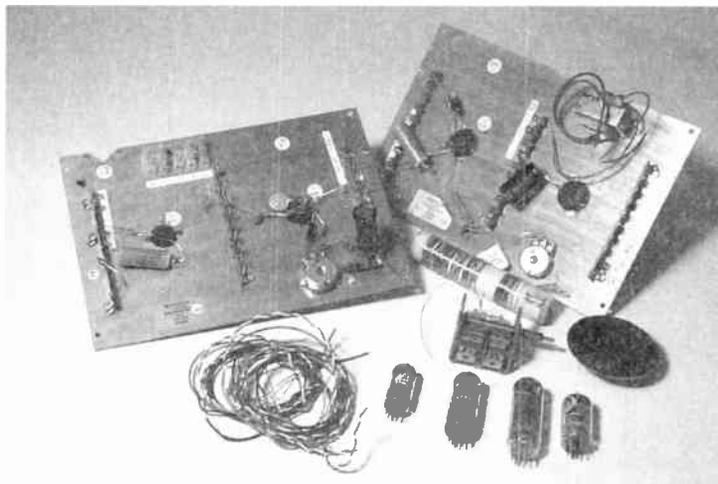

TWO well known companies, Greenweld and Kitmaster, have announced that they are to combine.

Greenweld, having been successfully resurrected after the closure of the old company in 1999, have seen high levels of demand for their new and surplus range of electronic bargain buys. During the same period, the arrival of Kitmaster by David Johns has brought back the era of valve radios.

Recently, Greenweld have been featuring Kitmaster products for sale through their own mail order and online shopping services. Realising the potential offered by these popular designs, Greenweld are combining their established mail order infrastructure with David John's expertise in electronics and valve radio design.

Geoffrey Carter of Greenweld tells us that Kitmaster's novel approach to electronic kit building has revived interest in valve technology assembly for both novices and experienced users alike. Models such as the popular Four Valve Regeneration Unit are selling at a high rate. Recent introductions include a range of battery-operated valve radios, which are becoming even more sought after. Each kit contains all the necessary parts, together with a detailed and comprehensive manual.

Greenweld will continue their commitment to offering a huge range of electronic components, together with frequent purchases of surplus electronic equipment of every type which is, as usual, offered at bargain prices. David Johns will continue to develop new products.

For a free catalogue contact Greenweld Ltd, Dept EPE, Unit 24, Horndon Industrial Park, West Horndon, Brentwood, Essex CM13 3XD. Tel: 01277 811042. Fax: 01277 812419. E-mail: service@greenweld.co.uk. Web: www.greenweld.co.uk.

EWB WITH PCB CAD

ELECTRONICS Workbench devotees will be pleased to learn that this superb circuit design and simulation software package has now had printed circuit design facilities added to its pedigree. The sense of making such an addition will be obvious to anyone who is familiar with EWB.

EWB multiSIM is a complete system design tool which offers schematic entry, comprehensive component database, SPICE simulation, VHDL/Verilog entry and simulation, waveform analysis, r.f. capabilities and "seamless" transfer to p.c.b. layout. It is said to offer a unique combination of advanced functionality and exceptional ease of use.

Many of you will recall that we featured the basic EWB software in Mike Tooley's excellent *Electronics from the Ground Up* series of Oct '94 to Jun '95.

For more information contact Adept Scientific plc, Dept EPE, Amor Way, Letchworth, Herts SG6 1ZA. Tel: 01462 480055. Fax: 01462 480213.

E-mail: ewb@adeptscience.co.uk.
Web: www.adeptscience.co.uk.

MAPLIN 2000/2001 CAT

MAPLIN Electronics have launched their new 2000/2001 catalogue with a huge range of products, over £100 worth of money-off vouchers and many brand new lines.

Maplin comment that their catalogue is "widely regarded as *the* electronics product bible." Now in its 28th year, it contains products ranging from individual components to state-of-the-art electronic equipment. It is available in traditional format (cost £3.99) or on a CD-ROM (£1.99).

The products can also be found at 57 Maplin stores nationwide, where specialist staff are available to help with technical and product enquiries. The Maplin website also features full product range details and a secure on-line ordering service with stock checking facilities.

For more catalogue information contact Maplin Electronics, Dept EPE, Valley Road, Wombwell, Barnsley S73 0BS. Tel: 0870 264 6002.

Web: www.maplin.co.uk.

Sparing DVD Egg-spense?

By Barry Fox

TECHNICS launched DVD-Audio at the Hammersmith HiFi show. Consumers now have the chance to spend £900 on a new format player with no new format software to play on it. The only discs at the show were DVD-R dubs from Universal. None exploited the full DVD-Audio specification of 192kHz.

"It's chicken and egg," says Technics.

Most people may prefer to wait until there are eggs to go with their £900 chickens.

Talking Signs

ON a number of occasions we have mentioned NXT, the inventors of Surface Sound flat panel loudspeaker technology. They tell us that they have unveiled a multilingual talking sign incorporating this revolutionary technology.

Using the latest digital audio techniques (MP3), the sign speaks in nine languages and is installed at the Whittington Hospital in Highgate, London. Research had shown that many public areas encounter a growing number of ethnic issues, including the variety of languages spoken and the need for simple spoken information.

Simply touching the panel gives the user instant access to customised information in a selection of languages. The combination of colourful graphics and clear high quality sound allows a wide range of messages and information to be imparted in a concise and friendly manner to both English and non-English speakers.

A spokesman for the Whittington Hospital said "This is a very exciting development for us, and we are pleased to be the first hospital in the UK with this particular initiative. We serve a culturally mixed community and we are always striving to improve our standards of health and ethnic issues."

For further information contact New Transducer Ltd., Dept EPE, 37 Ixworth Place, London SW3 3QH. Tel: 020 7343 5050. Fax: 020 7343 5055.

E-mail: marketing@nxtsound.com.
Web: www.nxtsound.com.

Patents Rising

APPLICATIONS for patents have risen by six per cent to over 30,000 for 1999, according to figures released by the UK Patent Office. Most patents were granted in the telecomms sector, 865 patents, but electric circuitry also came high, at 429 patents.


The Patent Office web site (www.patent.gov.uk) is receiving 50,000 hits daily (up from 20,000 a day last year), signifying that more people are wanting to find out how to protect their ideas and inventions.

The DTI (Department of Trade and Industry) also tells us that 27 per cent of UK businesses are now trading on-line. This puts the UK on a par with the USA and Canada, and ahead of Germany and Sweden (see www.ukonlineforbusiness.gov.uk).

Starter Project

STATIC FIELD DETECTOR

ROBERT PENFOLD

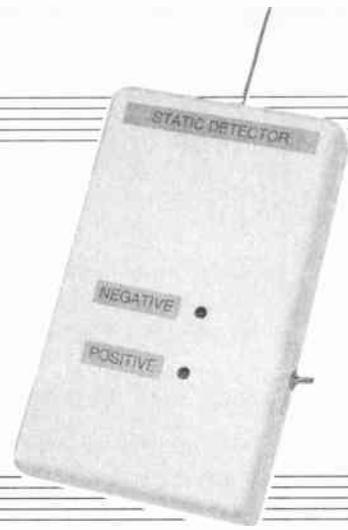

Amuse your friends and family with this novel "electroscope" starter project. – See if they are highly charged characters!

THIS ultra-simple device was designed as a low cost project for complete beginners, but it should also be of interest to those who like to experiment with unusual gadgets. It is a form of electroscope, which is a device that detects static electricity.

No doubt most readers have seen demonstration of purely mechanical devices that use electrostatic forces to show the presence of high static voltages. This device uses some simple electronics to detect much smaller potentials, with a twin l.e.d. display showing any increase or decrease in the detected voltage.

It has to be emphasised that this very simple unit is only intended to be a "fun" project, and it is not suitable for serious scientific purposes. Those with a serious interest in the subject of atmospheric electricity should refer to the recent *EPE* articles (*Atmospheric Electricity Detector* – June/July 2000) on this subject by Keith Garwell.

BASICS

What is the difference between static electricity and the regular variety, and why is it not possible to measure static electricity using ordinary test equipment?

In normal electronics we are concerned with a flow of electricity, with electrons moving along wires or into and out of components. Static electricity is not fundamentally different to the electrical signals we normally deal with in that it is still comprised of electrons. The difference is that the electrons are not going anywhere.

Although normal matter contains electrons, it does not necessarily have a static charge. Matter has a positive charge when it has fewer electrons than normal, or a negative charge if it has an excess of electrons.

As most readers will be aware, static charges can be generated by friction, and rubbing many plastics will generate quite high voltages. The fact that static charges are present in most environments is probably less well known. Where you are right now there could well be a potential of 50V to 100V between the air near the floor and the air about two metres higher up.

On the face of it, measuring voltages of this order should be easy enough and any multimeter should be able to handle the task. In practice matters are more complicated due to the nature of the signals involved. The voltages may be quite high, but the available current is quite low. To be more precise, an appreciable current is available, but only very briefly.

Although a digital multimeter has a high input resistance of typically over 10 megohms, this will still rapidly leak away the charge being measured. In fact, it will leak it away before a meaningful measurement can be made.

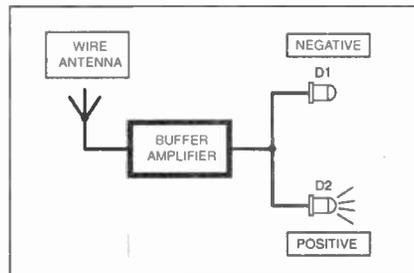


Fig.1. The static detector is basically just a buffer amplifier and two l.e.d.s.

A voltmeter having an extremely high input resistance is needed in order to measure static charges. The amount of current drawn by the test instrument is then so low that it does not significantly reduce the charge voltage during the measurement process.

Obtaining a suitably high input resistance is not difficult, since this is a natural characteristic of field effect transistors (f.e.t.s). It is also an attribute of many operational amplifiers (op.amps) which use field effect devices in their input stages. Op.amps having input resistances of one million megohms or more are commonplace, and this is more than adequate for the present application.

SYSTEM OPERATION

This Static Field Detector uses the simple arrangement shown in Fig.1. An antenna consisting of a short piece of wire is connected to the input of a buffer amplifier that

has an ultra-high input resistance. This amplifier has no voltage gain, and its sole purpose is to provide the circuit with an ultra-high input resistance. There are no bias resistors or other components at the input of the amplifier, which is therefore free to float to whatever potential the antenna assumes.

The output of the amplifier drives two l.e.d. indicators. With the output of the amplifier at about half the supply potential both l.e.d.s are switched on fairly brightly.

If the output potential rises, the brightness of l.e.d. D2 increases but l.e.d. D1 becomes dimmer and will switch off if the output potential becomes high enough. A decrease in the output voltage has the opposite effect, with D1 becoming brighter and D2 going dimmer or even switching off altogether. This method is very simple and inexpensive, but it clearly shows any variations in the detected voltage.

MEASURING WHAT?

When measuring voltages in a circuit you do not simply place one test prod on a test point and read its voltage. Most equipment is of the negative earth variety, and voltages are therefore measured relative to the negative supply rail. One test prod is connected to the earth rail (0V), and the other is placed on the test points.

Here we are effectively using a single test prod in the form of the antenna, with voltage measurements being made relative to nothing. Although it might seem as though the same middle reading will always be obtained, this is not actually the case.

When the unit is first switched on the two l.e.d.s will switch on to indicate a middle voltage. If the unit is moved around the l.e.d.s should soon start to indicate changes in potential. The unit is registering changes in voltage relative to the antenna's starting potential. It would be possible to connect the negative supply rail of the unit to an earth and then make measurements relative to the earth's potential.

However, a simple circuit such as this can only handle an input voltage range of about 0V to 9V, whereas signals of either polarity and up to a few hundred volts in magnitude might be encountered. Also, using an earth is relatively awkward and restrictive. The method used here is freer, easier, and works quite well.

CIRCUIT OPERATION

The full circuit diagram for the Static Field Detector appears in Fig.2. The

operational amplifier, IC1, is the buffer amplifier, and is a bi-f.e.t. device that uses junction gate field effect transistors in its input stage. A device having a MOSFET input stage should work equally well on the input side of things, as should any other bi-f.e.t. op.amp.

The specified TL061CP op.amp has an output stage that will drive both l.e.d.s from fully switched off to fully switched on, whereas most other op.amps will fail to do this. Consequently, the use of alternative devices is not recommended.

No voltage gain is required in this application, so 100 per cent negative feedback is provided by coupling the output of the amplifier (pin 6) to the inverting input (pin 2) via resistor R1. The output adopts the same voltage as the non-inverting input at pin 3, but there is a massive current gain through IC1.

The input current is probably a few nanoamps or even picoamps, but the output can provide a few milliamps to drive the l.e.d.s at good brightness. Resistors R2 and R3 limit the current fed to l.e.d.s D1 and D2 to a safe level.

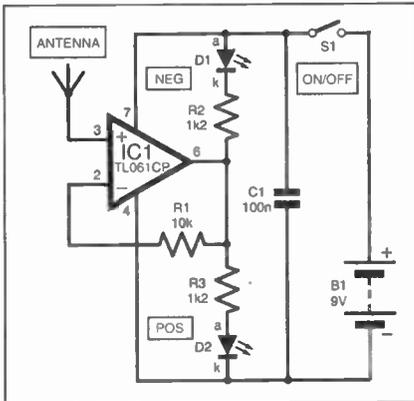


Fig.2. Complete circuit diagram for the Static Field Detector.

The maximum drive current is about 5mA. The TL061CP used for IC1 is a low current device, and the current consumption of the circuit as a whole is never much more than about 5mA.

CONSTRUCTION

The construction of the Static Field Detector is based on the *EPE* multi-project printed circuit board. This board is available from the *EPE PCB Service*, code 932. The component layout, wiring and the actual size foil master pattern are shown in Fig.3.

Although there are very few components to fit onto the circuit board, the usual warning is still in order here. Unlike a normal custom printed circuit board, this board does not have one hole per component lead. It has many holes that are left unused, and the small number of components used in this circuit means that the vast majority of them are not used.

The low component count actually makes it easier to make a mistake, so it is essential to take more care than normal when fitting the components. Also, carefully check the completed board for errors.

In all other respects construction of the board offers nothing out of the ordinary. The TL061CP used for IC1 is not a device that is vulnerable to damage from static charges, but it is still advisable to mount it on the board via an i.c. socket.

There are two ways of dealing with the l.e.d.s. One is to mount them in panel holders and then hard wire them to the circuit board. The board should be fitted with single-sided solder pins at the points where the connections to the two l.e.d.s will be made. Incidentally, it should also be fitted with pins at the points where connections will be made to on/off switch S1, the battery, and the antenna.


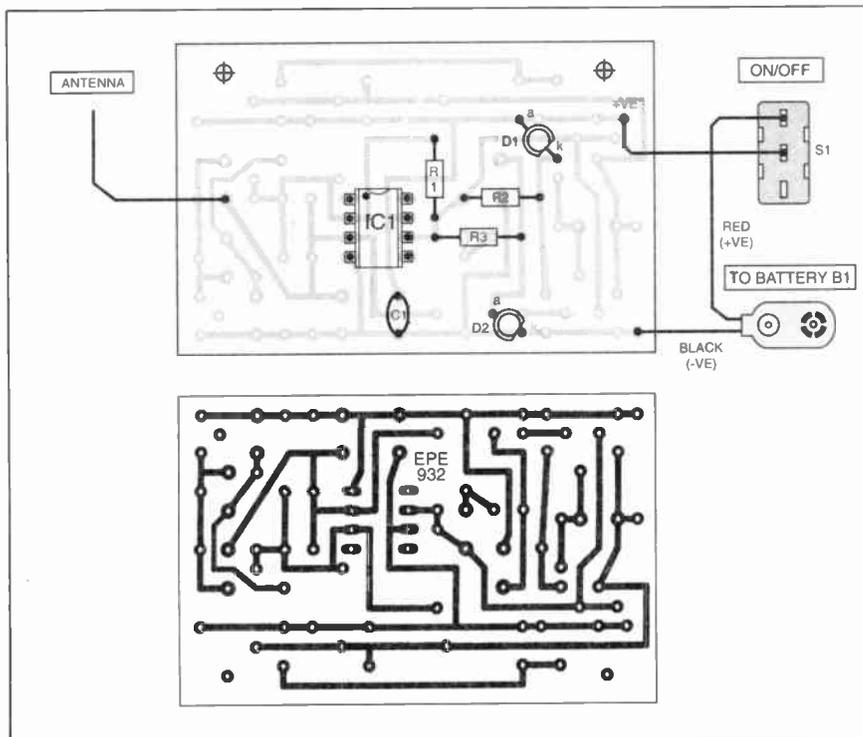


Fig.3. Component layout on the multi-project printed circuit board and full-size copper foil master. Double-check layout as not all holes are used.

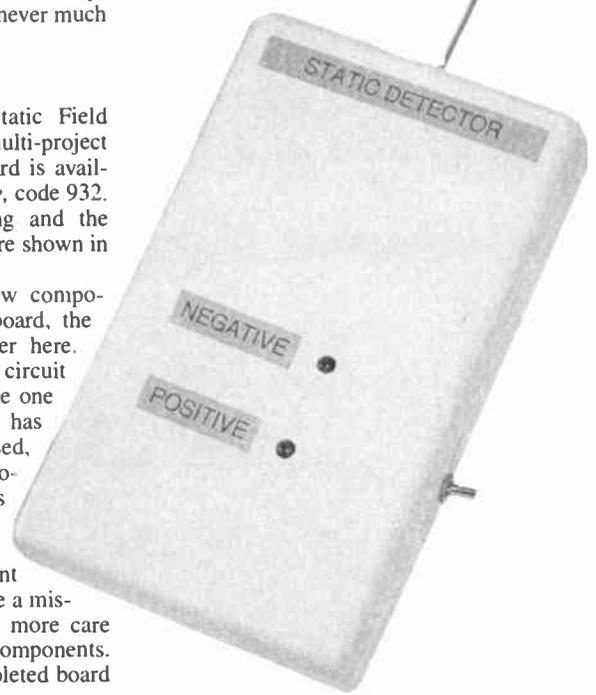Finished handheld detector showing labelling of the two "static" l.e.d.s.



The alternative method is to mount the l.e.d.s D1 and D2 on the printed circuit board, and to leave the leadout wires quite long. With the printed circuit board mounted on the base panel of the case, the l.e.d.s will then fit into two 5mm dia. holes drilled at the appropriate positions in the top panel.

Note that l.e.d.s, unlike filament bulbs, will only operate if they are connected with the correct polarity. The cathode (k) lead-out wire is normally shorter than the anode (a) lead. Also, most l.e.d.s have a "flat" on the component's body, next to the cathode lead.

COMPONENTS

Resistors
R1 10k
R2, R3 1k2 (2 off)
All 0.25W 5% carbon film

Capacitor
C1 100n ceramic

Semiconductors
D1, D2 5mm panel l.e.d.s, red
IC1 TL061CP (see text)

Miscellaneous
S1 s.p.s.t. min toggle switch
B1 9V battery (PP3 size)

Small plastic case, size to choice; printed circuit board available from the *EPE PCB Service*, code 932; battery connector; stout tinned copper wire for antenna; plastic stand-off pillars or M3 nuts and bolts (see text); single-sided solder pins (3 off); solder, etc.

Approx. Cost
Guidance Only

£10

CASING-UP

Any small to medium size plastic case is suitable for this project. It is best not to use a metal box as it could interfere with the correct operation of the device, and would complicate fitting the antenna.

The completed printed circuit board is mounted inside the case using either plastic stand-offs or metric M3 bolts and fixing nuts. If bolts are used, spacers a few millimetres long must be fitted between the case and the board.

On/off switch S1 is mounted at any convenient point on the case, and a hole about 2mm dia. is drilled in the top side panel of the case, see photographs. This hole is for the antenna, which is merely a piece of tinned copper wire that protrudes about 75mm to 100mm beyond the front of the case. This wire should be fairly thick, but anything from about 0.7mm to 1.6mm (22 to 16s.w.g.) is suitable.

To complete the unit add the battery connector, fit the antenna, and add the wire from S1 to the circuit board.

TESTING

Start with the lid of the case removed so that you have access to the circuit board.


Both l.e.d.s should light up quite brightly when the unit is switched on. Try touching the antenna and the solder pin on the circuit board that takes the connection from the negative (black) battery lead. This should result in l.e.d. D2 switching off and D1 increasing in brightness.

Next touch the antenna and the solder pin that takes the lead from S1. This should have the opposite effect, with l.e.d. D1 switching off and D2 lighting more brightly. If there is any sign of a malfunction switch off at once and recheck the circuit board, etc.


If all is well, refit the lid of the case and make some initial tests with the detector. In general, there is more to detect in a dry atmosphere than in a humid one where charges tend to leak away. Up and down movement will usually produce some change in the display.

Placing the unit near the ground invariably produces a strong positive indication, as will placing the antenna near anything that is earthed. This includes things like the metal case of a computer, a radiator, or the walls of a house.

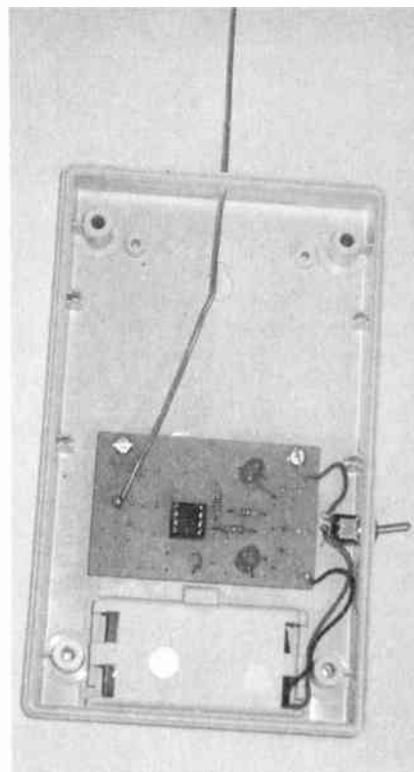You can amuse your friends and family by checking to see if they are highly charge



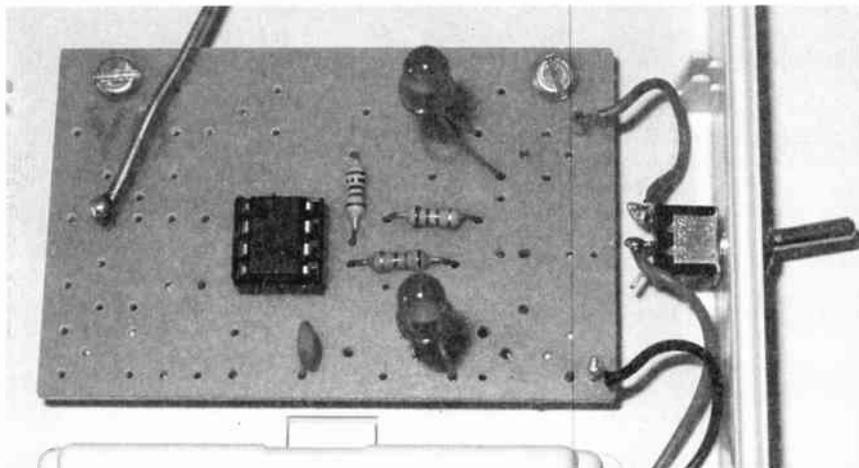The simple layout of components inside the handheld case.



Completed circuit board. Note the unused holes.

characters, and whether they emit positive or negative energy. Get them to rub their clothes and then try again to see if different results are obtained.

The device used for ICI has built-in protection circuitry that should prevent the input voltage from going outside the range that the unit can handle. If the l.e.d.s seem to get stuck showing a fully positive or negative indication try switching off, waiting a second or two, and then switching on again.

Attempts to deliberately "zap" ICI by placing the antenna near known sources of high static voltages such as television screens proved fruitless. This suggests that the unit is reasonably "zap" resistant, but large static charges can destroy most modern semiconductors, so you try this sort of thing at your own risk.

★ MAKE IT A SPECIAL GIFT EVERY MONTH ★

EVERYDAY
PRACTICAL
ELECTRONICS

INCORPORATING **ELECTRONICS TODAY INTERNATIONAL**

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

Annual subscription rates (2000/2001):

6 Months: UK £14.50, Overseas £17.50 (standard air service),
£27 (express airmail)

1 Year: UK £27.50, Overseas £33.50 (standard air service)
£51 (express airmail)

2 Years: UK £50.00, Overseas £62.00 (standard air service)
£97 (express airmail)

To: Everyday Practical Electronics,
Allen House, East Borough, Wimborne, Dorset BH21 1PF
Tel: 01202 881749 Fax: 01202 841692
E-mail: subs@epemag.wimborne.co.uk

Name

Address

Post code

SUBSCRIPTION ORDER FORM



I enclose payment of £..... (cheque/PO in £ sterling only),

payable to Everyday Practical Electronics



Access or Visa No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Signature

Card Ex. Date

Please supply name and address of cardholder if different from the subscription address shown below. Subscriptions can only start with the next available issue. For back numbers see the Editorial page.

12/00

from
£60 (inc)
Shareware Version
Download & Order Online!

PROTEUS VSM


Virtual System Modelling

Build It In Cyberspace

www.labcenter.co.uk

Develop and test complete micro-controller designs without building a physical prototype. PROTEUS VSM simulates the CPU and any additional electronics used in your designs. And it does so in real time. *

- CPU models for PIC and 8051 and series micro-controllers available now. 68HC11 coming soon. More CPU models under development. See website for latest info.
- Interactive device models include LCD displays, RS232 terminal, universal keypad plus a range of switches, buttons, pots, LEDs, 7 segment displays and much more.
- Extensive debugging facilities including register and memory contents, breakpoints and single step modes.
- Source level debugging supported for selected development tools.
- Integrated 'make' utility - compile and simulate with one keystroke.
- Over 4000 standard SPICE models included. Fully compatible with manufacturers' SPICE models.
- DLL interfaces provided for application specific models.
- Based on SPICE3F5 mixed mode circuit simulator.
- CPU and interactive device models are sold separately - build up your VSM system in affordable stages.
- ARES Lite PCB Layout also available.

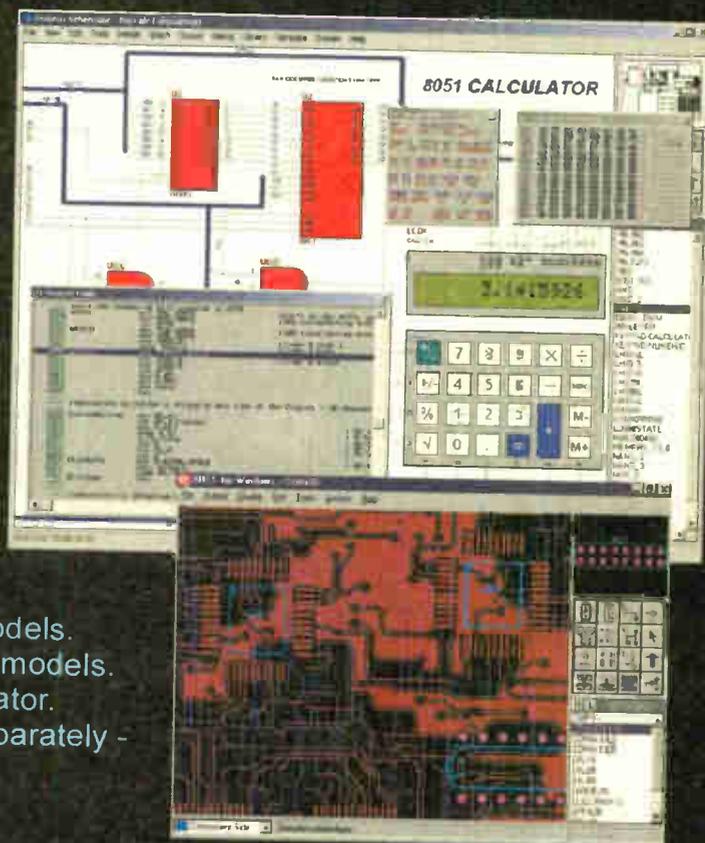

labcenter
Electronics

*E.g. PROTEUS VSM can simulate an 8051 clocked at 12MHz on a 300MHz Pentium II

Write, phone or fax for your free demo CD - or email info@labcenter.co.uk.
Tel: 01756 753440. Fax: 01756 752857. 53-55 Main St, Grassington. BD23 5AA.

FRUSTRATED!

Looking for ICs TRANSISTORS?

A phone call to us could get a result. We offer an extensive range and with a world-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD
ADC AN AM AY BA BC BD BDT BDV BDW BDX BF
BFR BFS BFT BFX BFY BLY BLX BS BR BRX BRY BS
BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUY
BUW BUX BUY BUZ CA CD CX CXA DAC DG DM DS
DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA
KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB
MC MDAJ MJE MJF MM MN MPS MPSA MPSH MPSU
MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB
SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD
STRM STRS SVI T TA TAA TAG TBA TC TCA TDA TDB
TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA
UAA UC UDN ULN UM UP A UPC UPD VN X XR Z ZN
ZTS + many others

We can also offer equivalents (at customers' risk)

We also stock a full range of other electronic components
Mail, phone, Fax Credit Card orders and callers welcome



Connect

Cricklewood Electronics Ltd

40-42 Cricklewood Broadway London NW2 3ET
Tel: 0181 452 0161 Fax: 0181 208 1441



DISTANCE LEARNING COURSES in:

Analogue and Digital Electronics, Fibre Optics, Fault Diagnosis, Mechanics, Mathematics and Programmable Logic Controllers leading to a

BTEC PROFESSIONAL DEVELOPMENT CERTIFICATE

- Suitable for beginners and those wishing to update their knowledge and practical skills
- Courses are very practical and delivered as self contained kits
- No travelling or college attendance
- Learning is at your own pace
- Each course can stand alone or be part of a modular study programme
- Tutor supported and BTEC certified

For information contact:

NCT Ltd., P.O. Box 11
Wendover, Bucks HP22 6XA
Telephone 01296 624270; Fax 01296 625299
Web: <http://www.nct.ltd.uk>

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220V/240V AC 50/60Hz OUTPUT 0V-260V

PANEL MOUNTING

	Price	P&P
0.5KVA 2.5 amp max	£33.00	£6.00
		(£45.84 inc VAT)
1KVA 5 amp max	£45.25	£7.00
		(£61.39 inc VAT)

SHROUDED

0.5KVA 2.5 amp max	£34.00	£6.00
		(£47.00 inc VAT)
1KVA 5 amp max	£46.25	£7.00
		(£62.57 inc VAT)
2KVA 10 amp max	£65.00	£8.50
		(£86.36 inc VAT)
3KVA 15 amp max	£86.50	£8.50
		(£111.63 inc VAT)
5KVA 25 amp max	£150.00 (+ Carriage & VAT)	

Buy direct from the Importers. Keenest prices in the country.

500VA ISOLATION TRANSFORMER

Input lead 240V AC. Output via 3-pin 13A socket. 240V AC continuously rated, mounted in fibreglass case with handle. Internally fused. Price £35.00 carriage paid + VAT (£41.13)

TOROIDAL L.T. TRANSFORMER

Primary 0-240V AC. Secondary 0-30V + 0-30V 600VA. Fixing bolt supplied. Price £25.00 carriage paid + VAT (£29.38)

COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO

110V-240V Auto transformer either cased with American socket and mains lead or open frame type. Available for immediate delivery.

ULTRA VIOLET BLACK LIGHT BLUE FLUORESCENT TUBES

4ft. 40 watt	£14.00 (callers only)	(£16.45 inc VAT)
2ft. 20 watt	£9.00 (callers only)	(£10.58 inc VAT)
12in 8 watt	£4.80 + 75p p&p	(£6.52 inc VAT)
6in 6 watt	£3.96 + 50p p&p	(£5.24 inc VAT)
6in 4 watt	£3.96 + 50p p&p	(£5.24 inc VAT)

230V AC BALLAST KIT

For either 6in, 9in or 12in tubes £8.05+£1.40 p&p (£9.75 inc VAT)
The above Tubes are 3500/4000 angstrom (350-400nm) ideal for detecting security markings, effects lighting & Chemical applications.
Other Wavelengths of UV TUBE available for Germdical & Photo Sensitive applications. Please telephone your enquiries

400 WATT BLACK LIGHT BLUE UV LAMP

GES Mercury Vapour lamp suitable for use with a 400W P.F. Ballast. Only £39.95 incl p&p & VAT



5 KVA ISOLATION TRANSFORMER

As New. Ex-Equipment, fully shrouded, Line Noise Suppression, Ultra Isolation Transformer with terminal covers and knock-out cable entries. Primary 120V/240V, Secondary 120V/240V, 50/60Hz, 0.005pF Capacitance. Size, L 37cm x W 19cm x H 16cm, Weight 42 kilos. Price £120 + VAT. Ex-warehouse. Carriage on request.

24V DC SIEMENS CONTACTOR

Type 3TH8022-0B 2 x NO and 2 x NC 230V AC 10A. Contacts. Screw or Din Rail fixing. Size H 120mm x W 45mm x D 75mm. Brand New Price £7.63 inc. p&p and VAT.

240V AC WESTOOL SOLENOIDS

Model TT2 Max. stroke 16mm, 5lb. pull. Base mounting. Rating 1. Model TT6 Max. stroke 25mm, 15lb. pull. Base mounting. Rating 1. Series 400 Max. stroke 28mm, 15lb. pull. Front mounting. Rating 2. Prices inc. p&p & VAT. TT2 £5.88, TT6 £8.81, Series 400 £8.64.

AXIAL COOLING FAN

230V AC 120mm square x 38mm 3 blade 10 watt Low Noise fan. Price £7.29 incl. p&p and VAT. Other voltages and sizes available from stock. Please telephone your enquiries.

INSTRUMENT CASE

Brand new. Manufactured by Imhof. L 31cm x H 18cm x 19cm Deep. Removable front and rear panel for easy assembly of your components. Grey textured finish, complete with case feet. Price £16.45 incl. p&p and VAT. 2 off £28.20 inclusive.

DIECAST ALUMINIUM BOX

with internal PCB guides. Internal size 265mm x 165mm x 50mm deep. Price £9.93 incl. p&p & VAT. 2 off £17.80 incl.

230V AC SYNCHRONOUS GEARED MOTORS

Brand new Ovoid Gearbox Crozet type motors. H 65mm x W 55mm x D 35mm, 4mm dia. shaft x 10mm long, 6 RPM anti cw. £9.99 incl. p&p & VAT. 20 RPM anti cw. Depth 40mm. £11.16 incl. p&p & VAT.

16 RPM REVERSIBLE Crouzet 220V/230V

50Hz geared motor with ovoid geared box. 4mm dia. shaft. New manuf. surplus. Sold complete with reversing capacitor connecting block and circ. Overall size: h 68mm x w 52mm x 43mm deep. PRICE incl. P&P & VAT £9.99

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit. Kit of parts less case includes 12in. 8watt 2537. Angst Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £15.00+£2.00 p&p. (£19.98 inc VAT)


WASHING MACHINE WATER PUMP

Brand new 240V AC fan cooled. Can be used for a variety of purposes. Inlet 1 1/2" dia., outlet tin. dia. Price includes p&p & VAT. £11.20 each or 2 for £20.50 inclusive.

Watch Slides on TV.

Make videos of your slides. Digitise your slides (using a video capture card)

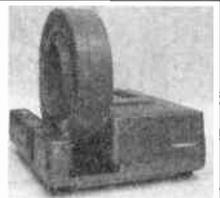"Liesgang diatv" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. More details see www.diatv.co.uk. £91.91 + VAT = £108.00



Board cameras all with 512 x 582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10V and 12V DC 150mA. 47MIR size 60 x 36 x 27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye) £37.00 + VAT = £43.48 30MP size 32 x 32 x 14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole £35.00 + VAT = £41.13 40MC size 39 x 38 x 27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses £32.00 + VAT = £37.60 Economy C mount lenses all fixed focus & fixed iris

VSL1220F 12mm F1.6 12 x 15 degrees viewing angle £15.97 + VAT £18.76
VSL4022F 4mm F1.22 63 x 47 degrees viewing angle £17.65 + VAT £20.74
VSL6022F 6mm F1.22 42 x 32 degrees viewing angle £19.05 + VAT £22.38
VSL8020F 8mm F1.22 32 x 24 degrees viewing angle £19.90 + VAT £23.38

Better quality C Mount lenses

VSL1614F 16mm F1.6 30 x 24 degrees viewing angle £26.43 + VAT £31.06
VWL813M 8mm F1.3 with iris 56 x 42 degrees viewing angle £77.45 + VAT = £91.00
1206 surface mount resistors E12 values 10 ohm to 1M ohm
100 of 1 value £1.00 + VAT 1000 of 1 value £5.00 + VAT

866 battery pack originally intended to be used with an orbitel mobile telephone it contains 10 1-6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily £7.46 + VAT = £8.77



Please add £1.66 + vat = £1.95 postage & packing per order

JPG Electronics

276-278 Chatsworth Road, Chesterfield, S40 2BH.

Tel 01246 211202 Fax 01246 550959

Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

We can supply back issues of *EPE* by post, most issues from the past five years are available. An *EPE* index for the last five years is also available – see order form. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photostat of any *one article* (or *one part* of a series) can be purchased for the same price. Issues from Nov. 98 onwards are also available to download from www.epemag.com.

DID YOU MISS THESE?

JULY '99

PROJECTS • 12V Lead-acid Battery Tester • L.E.D. Stroboscope • EPE Mood Picker • Intruder Deterrent.
FEATURES • Practical Oscillator Designs-1 • Practically Speaking • Circuit Surgery • Ingenuity Unlimited • New Technology Update • Net Work – The Internet.

AUG '99

PROJECTS • Ultrasonic Puncture Finder • Magnetic Field Detective • Freezer Alarm • 8-Channel Analogue Data Logger-1 • Sound Activated Switch.
FEATURES • Practical Oscillator Designs-2 • Power Generation from Pipelines to Pyons-1 • Ingenuity Unlimited • Circuit Surgery • Interface • Net Work – The Internet.

SEPT '99

PROJECTS • Loop Aerial SW Receiver • Child Guard • 8-Channel Analogue Data Logger-2 • Variable Dual Power Supply.
FEATURES • Practical Oscillator Designs-3 • Power Generation from Pipelines to Pylons-2 • Practically Speaking • Circuit Surgery • Ingenuity Unlimited • New Technology Update • Net Work.

OCT '99

PROJECTS • Interior Lamp Delay • Mains Cable Detector • QWL Loudspeaker System • Micro Power Supply.
FEATURES • PIC16F87x Mini Tutorial • Practical Oscillator Designs-4 • Circuit Surgery • Interface • Ingenuity Unlimited • Net Work – The Internet.

NOV '99

PROJECTS • Acoustic Probe • Vibralarm • Ginormous Stopwatch-1 • Demister One-Shot.
FEATURES • Teach-In 2000-Part 1 • Ingenuity Unlimited • Practically Speaking • Practical Oscillator Designs-5 • Circuit Surgery • New Technology Update • Net Work – The Internet
FREE Identifying Electronic Components booklet.



DEC '99

PROJECTS • PIC Micro-Probe • Magnetic Field Detector • Loft Guard • Ginormous Stopwatch – Giant Display-2.
FEATURES • Teach-In 2000-Part 2 • Practical Oscillator Designs-6 • Interface • Ingenuity Unlimited (Special) • Circuit Surgery • Net Work-The Internet • 1999 Annual Index.

JAN '00

PROJECTS • Scratch Blanker • Versatile Burglar Alarm • Flashing Snowman • Vehicle Frost Box.
FEATURES • Ingenuity Unlimited • Teach-In 2000-Part 3 • Circuit Surgery • Practically Speaking • Tina Pro Review • Net Work – The Internet.

FEB '00 Photostats Only

PROJECTS • PIC Video Cleaner • Voltage Monitor • Easy-Typist Tape Controller • Find It – Don't Lose It!
FEATURES • Technology Timelines-1 • Circuit Surgery • Teach-In 2000-Part 4 • Ingenuity Unlimited • Interface • Net Work – The Internet.

MAR '00

PROJECTS • EPE ICEbreaker • High Performance Regenerative Receiver-1 • Parking Warning System • Automatic Train Signal.
FEATURES • Teach-In 2000 – Part 5 • Practically Speaking • Technology Timelines-2 • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Net Work – The Internet.

APRIL '00

PROJECTS • Flash Slave • Garage Link • Micro-PICscope • High Performance Regenerative Receiver-2.
FEATURES • Teach-In 2000-Part 6 • Ingenuity Unlimited • Technology Timelines-3 • Circuit Surgery • Interface • Telcan Home Video • Net Work – The Internet.



MAY '00

PROJECTS • Versatile Mic/Audio Preamplifier • PIR Light Checker • Low-Cost Capacitance Meter • Multi-Channel Transmission System-1.
FEATURES • Teach-In 2000-Part 7 • Technology Timelines-4 • Circuit Surgery • Practically Speaking • Ingenuity Unlimited • Net Work – The Internet • **FREE** Giant Technology Timelines Chart.

JUNE '00

PROJECTS • Atmospheric Electricity Detector-1 • Canute Tide Predictor • Multi-Channel Transmission System-2 • Automatic Nightlight.
FEATURES • Teach-In 2000 – Part 8 • Technology Timelines-5 • Circuit Surgery • Interface • New Technology Update • Ingenuity Unlimited • Net Work – The Internet.



JULY '00

PROJECTS • g-Meter • Camera Shutter Timer • PIC-Gen Frequency Generator/Counter • Atmospheric Electricity Detector-2.
FEATURES • Teach-In 2000-Part 9 • Practically Speaking • Ingenuity Unlimited • Circuit Surgery • PICO DrDAQ Reviewed • Net Work – The Internet.

AUG '00

PROJECTS • Handy-Amp • EPE Moodloop • Quiz Game Indicator • Door Protector
FEATURES • Teach-In 2000-Part 10 • Cave Electronics • Ingenuity Unlimited • Circuit Surgery • Interface • New Technology Update • Net Work – The Internet.

SEPT '00

PROJECTS • Active Ferrite Loop Aerial • Steeplechase Game • Remote Control IR Decoder • EPE Moodloop Power Supply.
FEATURES • Teach-In 2000-Part 11 • New Technology Update • Circuit Surgery • Ingenuity Unlimited • Practically Speaking • Net Work – The Internet Page.

OCT '00

PROJECTS • Wind-Up Torch • PIC Dual-Chan Virtual Scope • Fridge/Freezer Alarm • EPE Moodloop Field Strength Indicator.
FEATURES • Teach-In 2000-Part 12 • Interface • Ingenuity Unlimited • New Technology Update • Circuit Surgery • Peak Atlas Component Analyser Review • Net Work – The Internet Page.

NOV '00

PROJECTS • PIC Pulsometer • Opto-Alarm System • Sample-and-Hold • Handclap Switch.
FEATURES • The Schmitt Trigger-Part 1 • Ingenuity Unlimited • PIC Toolkit Mk2 Update V2.4 • Circuit Surgery • New Technology Update • Net Work – The Internet • **FREE** Transistor Data Chart.

BACK ISSUES ONLY £3.00 each inc. UK p&p.

Overseas prices £3.50 each surface mail, £4.95 each airmail.

We can also supply issues from earlier years: 1992 (except March, April, June to Sept. and Dec.), 1993 (except Jan. to March, May, Aug., Dec.), 1994 (except April to June, Aug., Oct. to Dec.), 1995 (No Issues), 1996 (except Jan. to May, July, Aug., Nov.), 1997 (except Feb. and March), 1998 (except Jan., March to May, July, Nov., Dec.), 1999.

We can also supply back issues of *ETI* (prior to the merger of the two magazines) for 1998/9 – Vol. 27 Nos 1 to 13 and Vol. 28 No. 1. We are not able to supply any material from *ETI* prior to 1996. Please put *ETI* clearly on your order form if you require *ETI* issues.

Where we do not have an issue a photostat of any *one article* or *one part* of a series can be provided at the same price.

ORDER FORM – BACK ISSUES – PHOTOSTATS– INDEXES

- Send back issues dates
 Send photostats of (article title and issues date)
 Send copies of last five years indexes (£3.00 for five inc. p&p – Overseas £3.50 surface, £4.95 airmail)

Name

Address

I enclose cheque/P.O./bank draft to the value of £

Please charge my Visa/Mastercard £

Card No. Card Expiry Date

Note: Minimum order for credit cards £5. Please supply name and address of cardholder if different from that shown above.

SEND TO: Everyday Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF.

Tel: 01202 881749. Fax: 01202 841692.


E-mail: orders@epemag.wimborne.co.uk

Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.


M12/00

STORE YOUR BACK ISSUES IN YOUR WALLET!

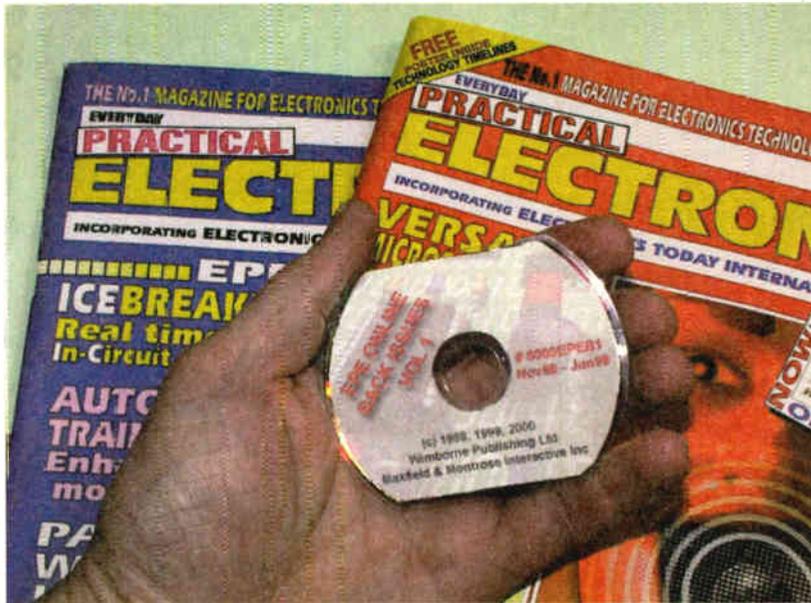

**VOL 2
NOW AVAILABLE**

**ONLY
£12.45**
including VAT
and p&p

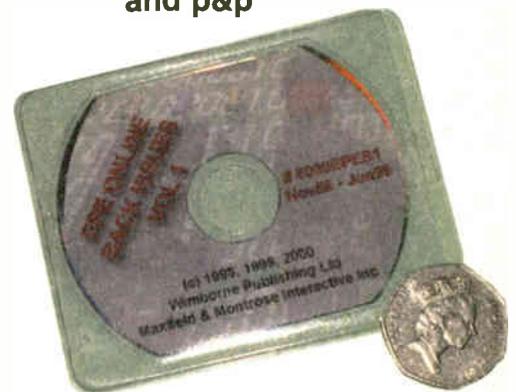

A new way to buy *EPE* Back Issues – our wallet-sized CD-ROMs contain back issues from our *EPE Online* website plus bonus articles, all the relevant PIC software and web links. All this for just £12.45 including postage and packing.

VOL 1 CONTENTS

BACK ISSUES – November 1998 to June 1999 (all the projects, features, news, IUs etc. from all eight issues). Note: No advertisements or Free Gifts are included.

PIC PROJECT CODES – All the available codes for the PIC based projects published in issues from November 1998 to June 1999.

EPE ONLINE STORE – Books, PCBs, Subscriptions, etc.

VOL 2 CONTENTS

BACK ISSUES – July 1999 to December 1999 (all the projects, features, news, IUs, etc. from all six issues). Note: No advertisements or Free Gifts are included.

PIC PROJECT CODES – All the available codes for the PIC-based projects published in issues from July to December 1999.

EPE ONLINE STORE – Books, PCBs, Subscriptions, etc.

EXTRA ARTICLES – ON ALL VOLUMES

THE LIFE & WORKS OF KONRAD ZUSE – a brilliant pioneer in the evolution of computers. A bonus article on his life and work written by his eldest son, including many previously unpublished photographs.

BASIC SOLDERING GUIDE – Alan Winstanley's internationally acclaimed fully illustrated guide.

UNDERSTANDING PASSIVE COMPONENTS – Introduction to the basic principles of passive components.

HOW TO USE INTELLIGENT L.C.D.s, By Julyan Ilett – An utterly practical guide to interfacing and programming intelligent liquid crystal display modules.

Phyzyb COMPUTERS BONUS ARTICLE 1 – Signed and Unsigned Binary Numbers. By Clive "Max" Maxfield and Alvin Brown.

Phyzyb COMPUTERS BONUS ARTICLE 2 – Creating an Event Counter. By Clive "Max" Maxfield and Alvin Brown.

INTERGRAPH COMPUTER SYSTEMS 3D GRAPHICS – A chapter from Intergraph's book that explains computer graphics technology in an interesting and understandable way with full colour graphics.

NOTE: This mini CD-ROM is suitable for use on any PC with a CD-ROM drive. It requires Adobe Acrobat Reader (available free from the Internet – www.adobe.com/acrobat)

Order on-line from www.epemag.com or by Phone, Fax, E-mail or Post

BACK ISSUES CD-ROM ORDER FORM

Please send me (quantity) BACK ISSUES CD-ROM VOL 1

Please send me (quantity) BACK ISSUES CD-ROM VOL 2
Price £12.45 (approx \$20) each – includes postage to anywhere in the world.

Name

Address

..... Post Code

I enclose cheque/P.O./bank draft to the value of £

Please charge my Visa/Mastercard £

Card No. Expiry Date

Note: Minimum order for credit cards £5. Please supply name and address of cardholder if different from that shown above.

SEND TO: Everyday Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF.

Tel: 01202 881749. Fax: 01202 841692.

E-mail: orders@epemag.wimborne.co.uk

Payments must be by credit card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

Sorry girls - party's over!
My new Antex Gas
Soldering Iron has just
arrived!



A compact, pocket sized kit with an iron and accessories to cope with a multitude of soldering/hot air applications.

Antex Gas Soldering Iron Kit

This kit includes:

- Gascat 70 soldering iron
- Soldering iron stand
- Solder
- Cleaning sponge
- Hot air tip
- Gas torch tip
- Hot knife tip
- Carry case

Order Code: AJ97F



SAVE £7
WAS £36.99

£29.99

GAS SOLDERING
IRON KIT

MAPLIN
ELECTRONICS


Order yours today! call

0870 264 6000


quoting ref A0045. Also available from Maplin stores and from our web site at www.maplin.co.uk. We accept the following cards for telephone orders



INGENUITY UNLIMITED

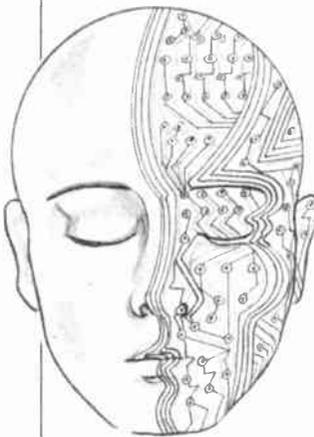

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas *must be the reader's own work and must not have been submitted for publication elsewhere*. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and full circuit diagram showing all relevant component values. **Please draw all circuit schematics as clearly as possible.** Send your circuit ideas to: Alan Winstanley, *Ingenuity Unlimited*, Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset BH21 1PF. (We do not accept submissions for IU via E-mail.) Your ideas could earn you some cash and a prize!

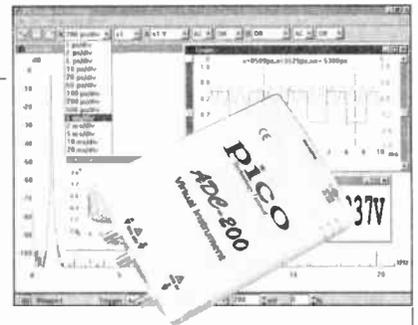

WIN A PICO PC BASED OSCILLOSCOPE

- 50MSPS Dual Channel Storage Oscilloscope
- 25MHz Spectrum Analyser
- Multimeter • Frequency Meter
- Signal Generator

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC based oscilloscope could be yours. Every six months, Pico Technology will be awarding an ADC200-50 digital storage oscilloscope for the best IU submission. In addition, two single channel ADC-40s will be presented to the runners-up.

Car Wash-Wipe Latch – More Delays

FOR cars which have only a simple rear wash-wipe control giving a single sweep of the wiper each time the switch is operated, the latching circuit of Fig. 1 will additionally provide a sweep automatically every few seconds, for use in continuous spray conditions. No extra switches are needed and the normal single-sweep operation can still be used at any time.

In the circuit diagram of Fig.1, IC1a is one half of a 556 dual timer, with the reset terminal (pin 4) connected unusually to the output (pin 5) via resistor R6 to form a latch. This can be set or reset depending on the duration of the wiper switch closure. When power is first applied (probably by switching on the car ignition), capacitor C2 briefly pulls the reset terminal high which enables the timer.

The trigger terminal (pin 6) voltage is low, so the output goes high and maintains the

reset terminal high. The timing capacitor C1 charges from the output via R4, R5 and R6, but because of resistor R7 it does not reach the timer's threshold voltage (two-thirds of the supply voltage).

When the wiper switch is closed, capacitor C1 charges further via resistor R2, and will reach the threshold voltage in about 0.4 seconds, at which point the timer output will go low. (If the switch is opened before this, C1 simply discharges again.) The output then holds the reset terminal low after the wiper switch is opened, and C1 then discharges through R7. The latch remains in this state until the wiper switch is closed again, which takes the reset high and allows the output to go high again.

If the wiper switch is then held closed for more than 0.4 seconds capacitor C1 will have charged above the threshold voltage and so when the switch is opened the

output will go low, resetting the latch. Releasing the switch in less than 0.4 seconds sets the latch.

While the output of the latch is low it enables IC1b, which is an astable multivibrator with a duty cycle of 5 per cent. The inclusion of diode D3 enables the on and off times to be set independently by resistors R9 and R10 respectively. The output at IC1b pin 9 drives the existing transistorised wiper relay to give one sweep every ten seconds.

The circuit is powered from the car battery via resistor R1 and Zener diode D1 which provide a regulated 6.2V. To prevent damage to the i.c. from any voltage spikes from the wiper switch, the signal from R2 is clamped to the regulated supply rail by diode D2.

N. Jewell,
Ilfracombe,
Devon.

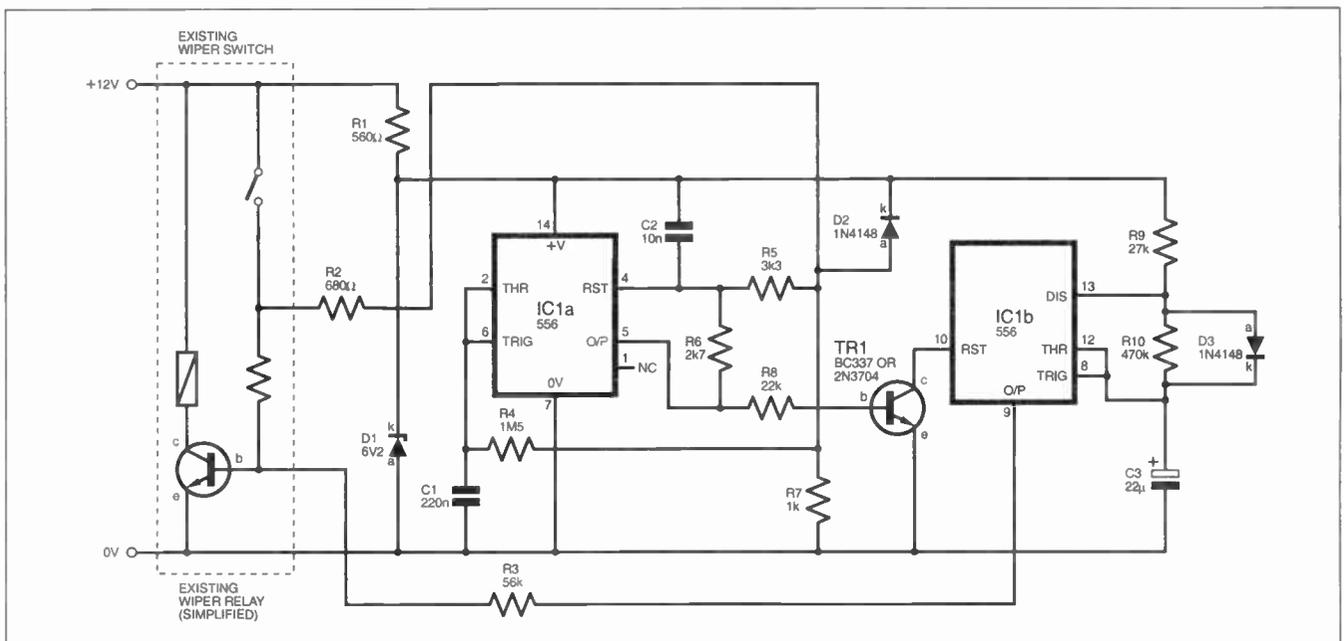


Fig.1. Circuit diagram for the Car Wash-Wipe Latch.

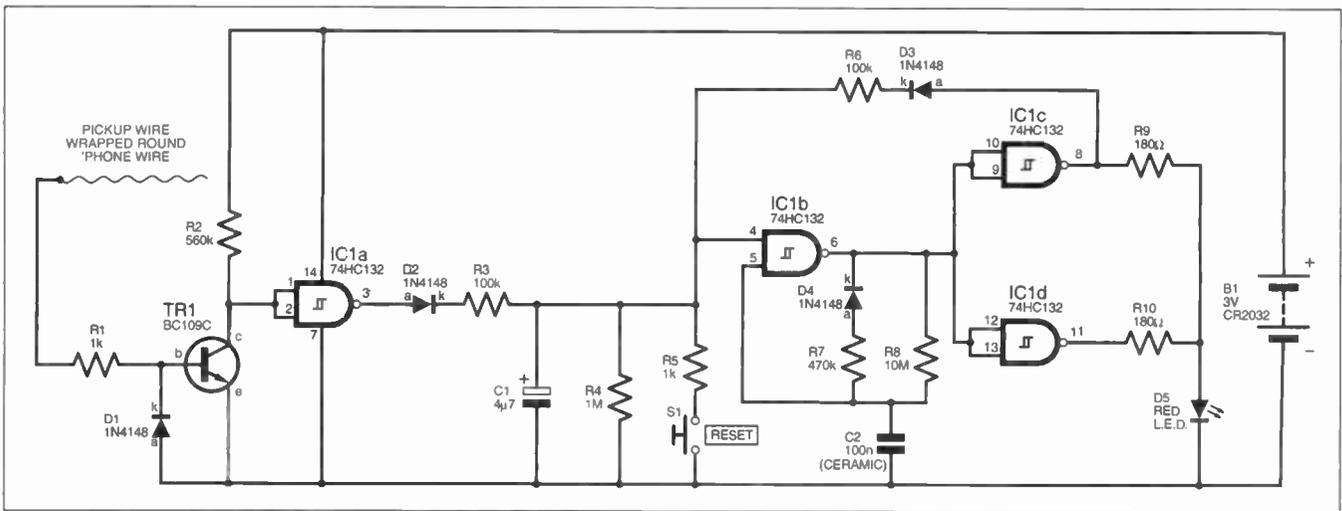


Fig.2. Circuit diagram for a Missed Call Indicator.

Missed Call Indicator – Call Back In A Flash

THIS project can provide an immediate visual indication that a telephone call has been missed. This is particularly useful when services such as the 1471 last call or automated call answer are used, since there is no way of telling if a new call has been missed without actually using the phone to check.

The circuit diagram shown in Fig.2 is designed to avoid the need for any direct connection to the phone line and to be battery operated. When not triggered, the quiescent current is near zero to ensure long battery life.

To avoid the need for a direct connection to the phone line, in accordance with UK regulations, a pick-up wire is instead, wrapped around the wire to the phone. This is connected to a high input impedance amplifier to detect the ringing voltage on the line.

A transistor TR1 with no bias, followed by a Schmitt trigger IC1a, provides sufficient amplification to trigger the circuit from the


ringing voltage. Unlike more traditional methods of detecting the phone ring with a microphone and amplifier, this method draws negligible quiescent current.

A second Schmitt trigger gate IC1b is used to implement a gated oscillator to generate the l.e.d. flash rate. An RC network formed by R3 and C1 at the input to this gated oscillator helps to prevent false triggering by requiring the equivalent of around three rings before the oscillator triggers. The two remaining gates are used as buffers to drive the l.e.d. and also to provide a feedback signal, via diode D3 and resistor R6, to latch the circuit once triggered.

The project can be built on stripboard and housed in a small plastic case. A 3V lithium cell or two 1.5V cells provides the power supply (B1) and the use of a 74HC series Schmitt trigger ensures that the circuit operates at 3V.

David Corder,
Loughborough, Leics.

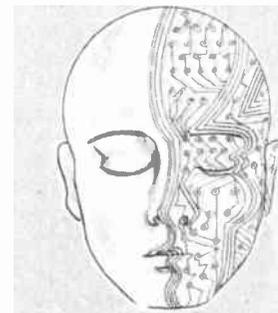**WHY NOT
SEND US YOUR
CIRCUIT IDEA
Earn some extra
cash and possibly
a prize!**



Scissors, Paper, Stone – The Game's Up

AN electronic variation of the Scissors, Paper, Stone game, designed for one player versus a machine, is shown in circuit diagram Fig.3. With pushswitches S1, S2 and S3 open, timer IC2 operates as an astable at approximately 30kHz with its output (pin 3) driving the clock (pin 14) of decade counter IC1. This counts to "3" and then resets so giving three viable outputs "1," "0" and "2".

On closing any one of the switches, one of the l.e.d.s D4, D5 or D6 illuminates and IC2 output is reset by lowering the voltage of pin 4. This stops the astable and the clock of the 4017 (IC1). Now one of the output pins 2, 3 or 4 of IC1 will be held high and the corresponding l.e.d. D1, D2 or D3 connected to it lights up. The machine's "response" to the player's selected diode D4, D5, D6 can therefore be observed.

Diode D7 has a dual purpose. Its primary function is to raise the voltage of IC2 so that when one of the switches S1 to S3 is selected, the input at the Reset pin (4) is low enough to operate the reset function and drive the IC2 output low. It also provides a power-on indicator.

George A. Vicary,
Swayfield,
Grantham.

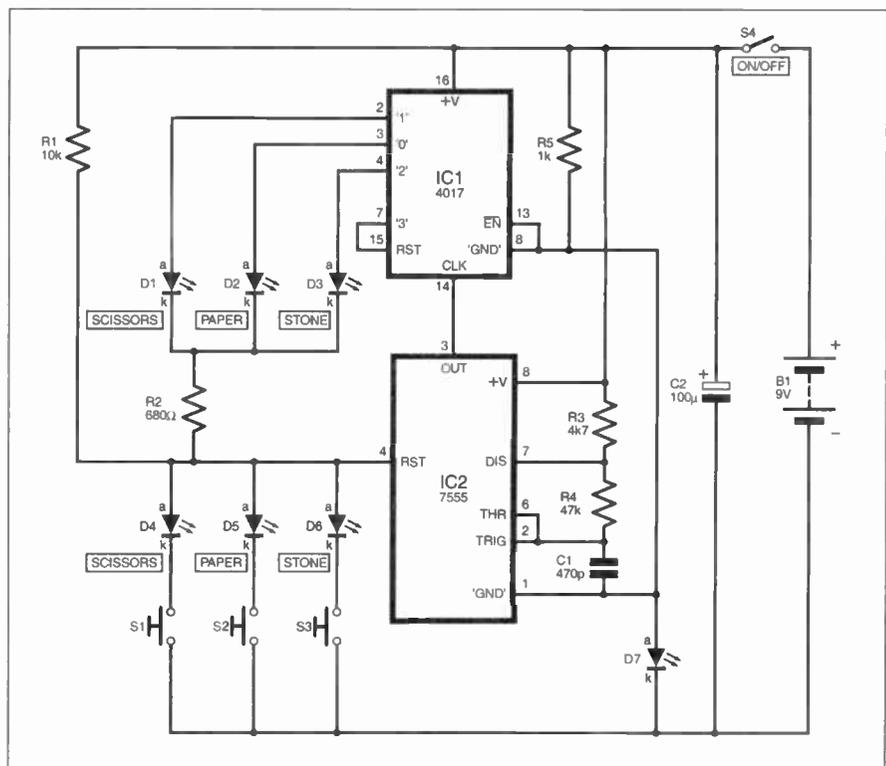


Fig.3. Scissors, Paper, Stone game circuit diagram.

LET PIC Basic

At last, a true BASIC compiler for the PIC micro
at an affordable price!

Download your FREE copy of LET PIC Basic lite from:
[Http://www.letbasic.com](http://www.letbasic.com)

Full LET PIC BASIC MANUAL available on-line

LET PIC Basic Professional £25
LET PIC Basic Plus £FREE with Professional

LET PIC Basic provides a seamless Windows development environment, with LET PIC Basic, you write, debug and compile your BASIC program within one Windows application, and by using a compatible programmer, just one key press allows you to program and verify the resulting code in the PIC of your choice! The Windows based Let PIC Basic programming environment comprises of Text Editor (with automatic syntax checker), Compiler and Programmer interface. When used with the LET PIC Programmer compilation and programming is achieved with just one mouse click!. LET PICBASIC produces .asm files compatible with MPLAB for use with most PIC Programmers.

Write code in true BASIC and compile for the popular PIC devices 12C508, 12C509, 16C54, 55, 56, 57, 16C71 and 16C84. The accompanying LET PICBASIC Plus allows programs to be compiled for the new 16F877 range of devices.

DOWNLOAD LET PICBASIC LITE FREE!

[Http://www.letbasic.com](http://www.letbasic.com)

FREE!

LET PIC BASIC

UNLEASHED!

By Les Johnson




£19.95

Les Johnson's Latest Book
Download an example chapter from
<http://www.letbasic.com>

LET PIC Programmer and LET PIC BASIC

Complete Package! £69.95

100% compatible with LET PIC BASIC

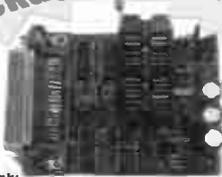

- ☑ Includes Power supply
- ☑ Includes Parallel port PC connection cable
- ☑ Windows and DOS software (Including LET PIC BASIC)
- ☑ High Quality ZIF socket
- ☑ Programs Parallel and serial PIC devices
- ☑ Programs popular serial memory devices
- ☑ Compatible with all popular file formats

Programs all popular PIC devices including 12c508, 509, 16F84 and parallel 16c54, 55, 56 & 57. Memory devices 24c and 24lc
See web page <http://www.letbasic.com/letpicprog3.htm> for the full list of devices, too long to list here!

This machine represents exceptionally good value for money, nothing else is required to enable you to write, compile and program your PIC BASIC program into popular PIC devices.

All prices are subject to VAT @ 17.5%



- PIC 16F84 /04p - £1.90
- PIC 16F84 /04so - £2.00
- PIC 16F84 /10p - £3.95
- PIC 16C622 /04p - £2.50
- PIC 16F877 /04p - £5.50
- PIC 16F877 /20p - £6.00
- PIC 16F876 /04p - £4.50
- PIC 16F874 /04p - £4.50
- PIC 16F873 /04p - £4.50

- PIC 12C508A - £0.63
- PIC 12C509A - £0.63
- 24LC16 - £0.75
- 24LC16 so - £0.95
- 24LC32 - £1.50
- 24LC64 - £1.50
- 24LC65 - £1.50

All prices are subject to VAT @ 17.5%

2 x PIC Micro CD-ROM's

packed with over 1.2Gb of info £10 inc P&P and VAT

Packed with information, data sheets, application notes, programs diagrams and tutorials. Includes TETRIS and PING PONG with sound and video out of a single PIC 16F84. Basic language assembly routines and macros for hundreds of commands. Data sheets on thousands of devices, micro's, memory and support chips.

Xtals and Resonators

4Mhz and 20Mhz from 45p




LCD DISPLAYS

16x2 line super twlst displays - £7.50 ea



SMARTCARD DEVELOPMENT SYSTEM

Smart Cards Included

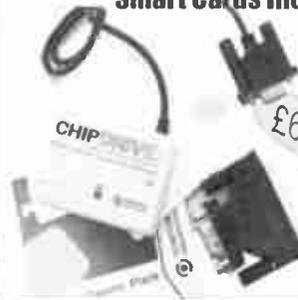

ChipDrive StarterKit + Windows Software

Read and Write data on Smart Cards and Memory cards

Microsoft PCSC compatible!

Package Includes:

Professional card Reader Writer (ChipDrive Micro),

Assorted Smart Cards (3 pairs),

Samples of source code in VB3,4,5+6, C and Delphi.

Examples Apps to Read and Write to Smart Cards and GSM cards

Documentation and detailed Windows DLL description.

Secure Online Ordering

www.crownhill.co.uk/itm00024

Free working Source code

£69.95

Crownhill Associates Limited

32 Broad Street Ely Cambridge Cb7 4PW



Tel: 01353 666709 Fax: 01353 666710



ORDER ON-LINE

www.crownhill.co.uk

LET products offered are wholly owned by Crownhill Associates Limited

LET was a trade mark of Leading Edge Technology (Malta) Ltd

All products are subject to post and packing unless otherwise stated

READOUT

E-mail: editorial@epemag.wimborne.co.uk

John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

WIN A DIGITAL MULTIMETER

A 3½ digit pocket-sized I.c.d. multimeter which measures a.c. and d.c. voltage, d.c. current and resistance. It can also test diodes and bipolar transistors.

Every month we will give a Digital Multimeter to the author of the best Readout letter.



★ LETTER OF THE MONTH ★

BASE-32 CODE

Dear EPE,

Your extension of base-16 (so-called *hexadecimal*) code to provide a compact date/time code for file names in the *PIC Dual-Channel Virtual Scope* project (Oct '00), is easily extended further to provide a full base-32 code and allow even more compactness.

As you point out, the month requires only one digit in base-16 code, and by extending the code as you have done, hours from 0 to 24 can also be represented by only one digit. With a further extension of the code to base 32, the day of the month could also be represented by only one digit, and three digits would suffice to represent any year up to 32,767 AD.

I have been using such a base-32 code for some time, with some modifications (dare I emulate Microsoft and call them *enhancements*?) that I find useful. These are:

1. Leaving out I (eye) and O (oh), which can be confused with 1 (one) and 0 (zero)

2. For those, like me, who prefer to use lower-case letters, also leaving out l (el), easily confused with 1 (one).

So with the above, the code sequence is: 0 to 9, a to f (as in the commonly used base-16 code), g h j k m n, p to y. This leaves z for use as a dummy symbol.

3. I considered devising a base-64 code to represent minutes and seconds, but decided that it would be more bother than it was worth, so like you I have retained base-10 for these.

4. The most significant digit is placed first, i.e. the date and time are expressed as year + month + day + hour + minute + second. This simplifies sorting and arithmetical operations.

5. The code may have uses beyond incorporating date and time information in file names. So for, say, astronomical events, dates BC are expressed by prefixing a minus sign, and the BC/AD discontinuity smoothed out by assigning 000 to 1 BC. Examples:

1. My E-mail user name (pk1V7) comprises my initials and my birth year (yes, 1927 in base-10 code) 1x0 means 1984; this year (2000) is 1xg = 1984 + 16

2. The inventor of the Julian calendar made his first attempt to invade Britain in -01p

To conform with the DOS file-name and extension format of up-to-eight + up-to-three characters, the code for the seconds is placed in the extension. This leaves room to include the Admiralty time-zone designation as well: z for GMT, a for BST, k for my part of Oz. Your example of 7 Sep 2000 at 1:37:13 a.m., which you code as 07913713.Y00, then becomes 1xg97137.13a

The advantages of this coding scheme, it seems to me, are its generality and its versatility. There can be a trade-off between time span and precision, with the code truncated at one or both ends to suit the application, thereby leaving room within file-naming conventions for other information.

**Peter Kelly,
Woombye, Queensland, Australia**

Many thanks Peter for raising this discussion. Your comments are interesting for several reasons.

First, you highlight the problem of differentiating between several characters. It has long bugged me that some programmers insist on using the letter l (or i) as a variable name. For example: FOR A = I TO K, which if seen in print could be taken as FOR A = (ONE) TO K when in fact it means FOR A = (the value stored in the variable represented by letter l) TO K, a misinterpretation that could have a profound effect on the successful running of the program.

To me, programming use of characters i, l and l (eye, EYE, el) should be prohibited by cosmic edict (or at least common sense)! I'm currently getting to grips with VisualBASIC and even in its demo software there are frequent instances where I am not immediately sure which of the three characters is meant. (Oh, alright, I've been known to use them myself in my own software!)

Incidentally, my OCR scanner can also be confused by these characters, plus ' / \ and ! (lefthand single quote, apostrophe, forward slash, backslash, exclamation) and 5 and S (five, ESS).

You are quite right about using base-32 for coding. For characters that have to be read by a human eye, as in a file name within a computer directory (folder) for example, base-32 seems a reasonable limit. However, if it is only the computer that has to read coded data, almost the full extent of base-256 can be used.

Some years ago, I wrote a fixtures allocation program for a local Sunday football league. This was written for a very low powered machine (Commodore PET) and to economise on memory space (32K bytes) I succeeded in coding each data item within single bytes, one each for date, venue, teams, home/away, score points etc. These bytes only needed to be read by the computer from a single string of characters within a data file, it then translated them according to calculation and lookup tables.

Whilst a few ASCII values within the possible 0 to 255 range could not be used (comma, semicolon, ASCII 0 and 13, for instance) because the computer had its own ideas of their use in a string of characters, most could be used, and were.

*On using the file name extension for seconds coding, I avoided this option in order to simplify file name searching (and possible interpretation by the computer as having a different significance). Using the dot-suffix of .Y allows a more ready search for file types. For example keying in DIR *.Y0? immediately calls up all PSCOPE (and VSCOPE) files for the years 2000 to 2009 (I don't think I actually coded the year number).*

Lastly, I was interested to read that time zones have officially (Admiralty) allocated letter designations.

BASIC AND DELPHI

Dear EPE,

I would like to make some comments on replacements for GWBasic, QBASIC interpreters and the QuickBASIC compiler for use in simple interfacing projects, and to comment on Delphi.

FirstBASIC, which is shareware and for DOS, can be downloaded from www.powerbasic.com and registered within the UK for £30.55, see www.greymatter.co.uk for this. It is a very good BASIC compiler with a simple Integrated Development Environment (IDE) and, in the registered version, on-screen help.

Like QBASIC and QuickBASIC it has all the constructs for structured programming and the syntax is easy to learn, but the IDE does not support the use of the mouse. See PowerBASIC website for comparisons and some help with translating between Basics.

Having written a number of large programs in QuickBASIC for student use, some of which need to write to or poll the printer port to examine the hardware connected to it, I'm now trying to move them to Delphi. I think this is essential if I'm going to be able to run them under future operating systems.

Until recently all the books and articles I have come across have concentrated almost exclusively on the "components" used to build the various types of windows. This approach quickly allows you to build a "gee whiz" user interface, but to use Delphi seriously it is necessary to learn to use Object Pascal, which in turn requires an understanding of standard Pascal program structure.

Computer Programming in Pascal by David Lightfoot, *Teach Yourself Series*, is old, 1983, but adequate for understanding Pascal program structure. *Delphi in a Nutshell* by Ray Lischner is a new, 2000, desktop quick reference to Object Pascal, and is very comprehensive, 560pp, but it assumes some knowledge of Pascal. It also mentions that Delphi is being ported to Linux.

Delphi 1 is still available from Greymatter for £57.68p (see above) as *Learn to Program with Delphi 1*. This is a thick, 900pp, self-study manual and CD-ROM containing Delphi 1. It covers both the components and the Object Pascal language, though you have to dig a little to find what you want to know about the latter and there are some mistakes and ambiguities in the text. The "hidden gem" tucked away on the CD-ROM is the 300 page Object Pascal manual which can be printed from Adobe Acrobat.

Having no previous knowledge of Pascal, I almost gave up on Delphi because I could not figure out how to store, retrieve and manipulate data. Now I'm hooked. I've concluded that a rule of thumb is to ignore any book with less than 300 pages as it will be too superficial. It's a steep learning curve and I'm still in the foothills, but I'm still climbing!

**Dr Les May,
Rochdale, Lancs**

Interesting. Thank you Dr Les. It's an aspect that some readers may find it worthwhile looking into. Personally, I'm now just about coming to grips with VisualBASIC 6 and, despite finding the documentation inadequate, believe that this, with its Windows base, is the route to pursue.

BCD CHALLENGE ACCEPTED

Dear EPE,

I was very intrigued by the Binary to BCD conversion routine given in September 2000 *EPE*, as I had always seen this done by some method involving division by ten.

After a lot of thought, I managed to come up with what I think is an improved version. The procedure used to do the conversion is: "Start with a Partial Result (PR) of zero. For each bit in the binary, starting at the left hand end, multiply the PR by two and add the bit."

By doing this arithmetic in decimal, the PR at the end has the converted value which holds the digits as binary coded decimal (BCD) in the lower four bits of each of a succession of bytes, bits 4 to 7 are zeroes (Unpacked BCD). You could also, with a different program, use Packed BCD with two digits in a byte, one in each nibble.

Throughout the process, decimal adjustment (DecAdj) of the PR is necessary to maintain its BCD nature, so that 0 to 9 are unchanged but a result in the range 10 to 15, which is stored as hex 0A to 0F, is converted to 0 to 5 with a 1 carry ready to go in the next BCD, i.e. 0A to 0F become 10 to 15 hex.

The actual process is to add six to the unadjusted result. If this causes a 1 in the fifth bit (bit 4) then the changed pattern is used, other-

wise the original unadjusted pattern is retained. For Unpacked BCD the state of bit 4 can be used as the test.

The algorithm in Sep '00 uses "Add 3" before the "times 2" shift. This is best when Packed BCD is converted since for the "top" nibble there is no bit corresponding to bit 4. By "Adding 3" before the shift instead of "Add 6" after, the same effect is obtained using bit 7. However, in this case the carry into the decimal cannot be done until after the shift, hence the two passes through the digits for each bit.

The following is a version using one pass, for Unpacked BCD. I have used the locations BIN0 to BIN2 to hold the three bytes of binary, with the most significant (m.s.) byte in BIN2. The PR goes in the eight bytes DIGIT0 to DIGIT7, with the m.s. digit in DIGIT7. BINCNT and DECCNT hold counts for the two nested loops.

Harry West, via the Net

Congrats on picking up the challenge Harry! In fact I'd already seen in our Chat Zone that you'd been in contact with Peter Hemsley (who started it all off) and that he'd accepted your improvement. Well done. You now hold the BCD Place of Honour - can you be deposed we wonder? Well, readers, what do you think?

BINDEC:

CALL CLRDIG : Clear decimal digits
MOVLW 24 : Decimal count
MOVWF BINCNT

BITLP:

RLF BIN0,F : Shift binary left
RLF BIN1,F
RLF BIN2,F
MOVLW DIGIT0
MOVWF FSR
MOVLW 8 : Count for the decimal digits
MOVWF DECCNT
MOVLW 6 : The Working Register holds 6 throughout. For each bit the inner loop is repeated 8 times, with shift in of the next bit, "times 2" and DecAdj of each digit

ADJLP:

RLF INDF,F : 2*digit, then shift in "next bit" for DIGIT0 or else the carry from the previous digit
ADDWF INDF,F : Add 6, clears Cf and gives 1 in bit 4 if the

BTFSS INDF,4 : addition is needed; zero if not, when

SUBWF INDF,F : we subtract it again. Sets Cf

BSF STATUS,C : Cf could be 0 or 1, so make it 1 as default

BTFSS INDF,4 : Bit 4 is the carry to the next digit

BCF STATUS,C : Reset Cf to zero if bit 4 is clear

BCF INDF,4 : For BCD clear bit 4 in case it's one

INCF FSR,F : Go to next digit, (Cf not affected)

DECFSZ DECCNT,F : End of inner loop. check digit count and

GOTO ADJLP : round again if it's not zero

DECFSZ BINCNT,F : End of outer loop, one pass through digits.

GOTO BITLP : check bit count and repeat if necessary.

RETURN

E-MAIL VIRUSES

Dear EPE,

Barry Fox's article in *News* of September '00 raised the question of whether a virus can hide in plain text E-mails. He is essentially correct in saying that a computer-executable program cannot be transmitted through a text-only E-mail.

However, viruses are more than just computer programs. A virus is an entity that uses its host to replicate itself. If a text E-mail simply says "Copy this E-mail to everybody you know", it is a virus. It utilises the human user as the host to replicate itself. In 1994 an E-mail virus "Good Times" infected thousands of people's E-mail systems, as detailed in <http://www.mdfnsnet.f9.co.uk/Docs/Comp/Viruses/GoodTimes>.

It was essentially a chain letter containing a hoax warning about a virus, recommending that the reader E-mail it on to all their friends. As Clay Skirky on alt.folklore.urban put it: "It works by finding hosts with defective parsing apparatus which prevents them from understanding that a piece of E-mail which says there is an E-mail virus, and then asking them to remail the message to all their friends, is the virus itself."

P.S. A super computer is a machine that runs an endless loop in just two minutes.

Councillor Jonathan G. Harston,
Sheffield, via the Net

Editor Mike comments that we recently received a "self-executing" virus of the type you refer to. It trusted the user to delete all the files on his hard disk and then send on the E-mail!

We wonder whether by publishing your letter through so many thousands of EPE copies that it too has persuaded human hosts to perpetuate it as a virus?

NEW ELECTRONICS eGROUP

Dear EPE,

I wish to inform you of a new electronics egroup which has been set up specifically to address the needs of persons involved in all forms and branches of electronics in the UK, but particularly enthusiasts and students, whatever their experience. The main emphasis is on the sharing of information, designs, advice and support.

Further information, and joining instructions can be found at:

www.egroups.com/group/Electronics-UK, or from: Electronics-UK-owner@egroups.com.

I warmly invite your friends and colleagues to join.

Ross Currie,
Belfast, Northern Ireland, UK,
via the Net

Thanks Ross. We hope readers will flock to join your worthwhile enterprise.

BINARY TO DECIMAL

Dear EPE,

Thanks for publishing Peter Hemsley's BINDEC routine in Sept '00 *Readout*. However, the second instruction could better be written `MOVLW D'24`. If the default radix happens to be hexadecimal, as in MPASM, the program won't work right as written unless the radix is changed to decimal.

Stan Ockers, via the Net

Thanks Stan. Yes, that would be the case with MPASM, although TASM automatically recognises the value as decimal, not having a facility for setting the radix. In TASM, hex is expressed with a \$ (dollar) symbol before the value.

DATA SHEETS

Dear EPE,

I refer to *Readout* of Sept '00 and Roger Nightingale's query regarding data sheet availability on the web. Since I work in a computer workshop at the University of Dundee, information is a prime requirement to efficiency and fault finding and data sheets are crucially important. Having 24 hours a day access to the web I have been able to find numerous sites for data sheets but none to rival the one at www.bgs.nu/sdw/a.html.

If Roger can't find his required data sheet on this site, then he is in deep trouble.

Sandy Smith,
Dundee, via the Net

Most useful info Sandy, thanks.

PIC PULSOMETER

Dear EPE,

You published my *PIC Pulsometer* project in the Nov '00 issue. It was written in TASM and I owe you a word of thanks. This was my first PIC project, and your *PIC Tutorial* (Mar-May '98) and excellent *Toolkit Mk1* (Jul '98) programmer gave me an easy route into picking up the basics to add to my previous if different experience.

Richard Hinckley,
Congleton, Cheshire

Thank you Richard. We are sure that many readers will appreciate the result your of efforts! Why not give Toolkit Mk2 (May-Jun '99) a try now? It has even more facilities and the software has been updated again (see Nov '00 issue).

ANTI-TAMPER LOOP

Dear EPE,

In the application of Alan Bradley's *Anti-Tamper Loop Alarm* in *Ingenuity Unlimited* Oct '00, particularly when being deployed for the protection of a bicycle, motorcycle or car steering wheel, a good practice is to use coaxial cable such as RG58 or similar for the loop. This cable is then threaded through a chain with links of a suitable diameter, leaving several links at either end for the purpose of securing the chain with a padlock.

The cable may then be terminated with BNC connectors, which offer not only good connection reliability, but also, from the point of reducing false alarms, would be unlikely to become inadvertently disconnected through, for example, vibration or innocent, inadvertent movement of the protected item.

In this situation, good security is provided by not only having the security factor of the loop alarm, but also the physical security of the chain, which, if the loop is assembled within it correctly, will be very difficult to cut without cutting the loop and therefore activating the alarm. It also restricts access to the loop for bypass measures.

Ross Currie,
Belfast, Northern Ireland,
via the Net

Ah, hello again Ross! As a cyclist (in good weather only!) I agree with your suggestion. Also see Please Take Note this month.

SURVEILLANCE

Electronic Surveillance Equipment Kits from the UK's No.1 Supplier

SUMA DESIGNS has been supplying professional quality electronic surveillance equipment kits for over 20 years. Whether your requirement is hobbyist, amateur or professional you can be sure that you are buying from a company that knows the business. We ONLY sell surveillance products, no alarms, disco lights or computer bits. All of our kits are designed for self assembly and are well tried, tested and proven. All kits are supplied complete with top grade components, fibreglass PCB, full instructions, circuit diagrams and assembly details. Unless otherwise stated all transmitter kits are tuneable and can be received using an ordinary VHF FM radio.

UTX Ultra-miniature Room Transmitter

At less than 1/2 the size of a postage stamp the UTX is the smallest room transmitter kit in the world! Incredible 10mm x 20mm including microphone, 3-12V operation. Range up to 500m **£13.95**

MTX Micro-miniature Room Transmitter

Our best selling room transmitter kit. Just 17mm x 17mm including mic. Extremely sensitive. 3-12V operation. Range up to 1000m. ... **£14.95**

STX High-performance Room Transmitter

High performance transmitter with buffered output for greater stability and range. Measures just 22mm x 22mm including mic. 6-12V operation. Range up to 1500m. **£16.95**

VT500 High-power Room Transmitter

Our most powerful room transmitter with around 250mW of output power. Excellent range and penetration. Size 20mm x 40mm, 6-12V operation. Range up to 3000m. **£17.95**

VXT Voice-activated Room Transmitter

Triggers only when sounds are detected by on-board mic. Variable trigger sensitivity and on-time with LED trigger indicator. Very low standby current. Size 20mm x 67mm, 9V operation, range up to 1000m. **£21.95**

HVX400 Mains Powered Room Transmitter

Connects directly to 240V AC supply. Ideal for long-term monitoring. Size 30mm x 35mm, range up to 500m. **£21.95**

SCRX Subcarrier Scrambled Room Transmitter

To increase the security of the transmission the audio is subcarrier modulated. Receiver now requires the decoder module (SCDM) connected to allow monitoring. Size 20mm x 67mm, 9V operation, up to 1000m range. **£24.95**

SCDM Subcarrier Decoder for SCRX

Connects to earphone socket on receiver and provides decoded audio output to headphones. Size 32mm x 70mm, 9-12V operation. ... **£27.95**

UTLX Ultra-miniature Telephone Transmitter

Smallest kit available. Connects onto telephone line, switches on and off automatically as phone is used. All conversations transmitted. Size 10mm x 20mm, powered from line, up to 500m range. **£13.95**

TLX700 Micro-miniature Telephone Transmitter

Best selling kit. Performance as UTLX but easier to assemble as PCB is 20mm x 20mm. **£14.95**

STLX High-performance Telephone Transmitter

High-performance transmitter with buffered output for greater stability and range. Connects onto telephone line and switches on and off automatically as phone is used. Both sides of conversation transmitted up to 1000m. Powered from line. Size 22mm x 22mm. **£16.95**

PTS7 Automatic Telephone Recording Interface

Connects between telephone line (anywhere) and normal cassette recorder. Automatically switches recorder on and off as phone is used. Both sides of any conversation recorded. 9V operation, size 20mm x 67mm. **£21.95**

CD400 Pocket Size Bug Detector/Locator

LED and piezo bleeper pulse slowly. Pulse rate and tone pitch increase as signal source is approached. Variable sensitivity allows pinpointing of signal source. 9V operation, size 45mm x 54mm. **£34.95**

CD600 Professional Bug Detector/Locator

Multicolour bargraph LED readout of signal strength with variable rate bleeper and variable sensitivity allows pinpointing of any signal source. When found, unit is switched into AUDIO CONFIRM mode to distinguish between bugging devices and legitimate signals such as pagers, cellphones etc. Size 70mm x 100mm. 9V operation. **£59.95**

QTX180 Crystal Controlled Room Transmitter

Narrow band FM crystal transmitter for ultimate in privacy. Output frequency 173.225 MHz. Designed for use with QRX180 receiver unit. Size 20mm x 67mm, 9V operation, range up to 1000m **£44.95**

QLX180 Crystal Controlled Telephone Transmitter

Specifications as per QTX180 but connects onto telephone line to allow monitoring of both sides of conversations. **£44.95**

QSX180 Line Powered Crystal Telephone Transmitter

Connects onto telephone line, switches on and off as phone is used. Power is drawn from line. Output frequency 173.225 MHz. Designed for use with QRX180 receiver. Size 32mm x 37mm. Range up to 500m. **£39.95**

QRX180 Crystal Controlled FM Receiver

Specifically designed for use with any of the SUMA 'O' range kits. High sensitivity design. Complex RF front end section supplied as pre-built and aligned sub-assembly so no difficult setting up. Headphone output. PCB size 60mm x 75mm. 9V operation. **£69.95**

TKX900 Signalling/Tracking Transmitter

Transmits a continuous stream of audio bleeps. Variable pitch and bleep rate. Ideal for signalling, alarm or basic tracking uses. High power output. Size 25mm x 63mm, 9-12V operation, up to 2000m range. **£23.95**

MBX-1 Hi-Fi Micro Broadcaster

Connects to headphone socket of CD player, Walkman or Hi-Fi and broadcasts your favourite music around house and garden up to 250m. Size 27mm x 60mm, 9V operation. **£22.95**

DLTX/RX Radio Remote Switch System

Two kits, transmitter sends a coded signal (256 selectable codes) when button pressed. Receiver detects signal, checks code and activates relay. Can be set to be momentary or toggle (on/off) operation. Range up to 100m, 9V operation on both units. TX 45mm x 45mm, RX 35mm x 90mm. **£44.95**

TO ORDER:

Post, fax or telephone your order direct to our sales office. Payment can be Credit card (Visa or Mastercard), Postal Order, cash (please send registered) or cheques. Kits despatched same day (cheques need clearing). All orders sent by recorded or registered post. Please add postage as follows:

ORDER UP TO £30.00: To UK £2.50 To EUROPE £5.50 All other £7.50
ORDERS OVER £30.00: To UK £3.65 To EUROPE £7.50 All others call

Overseas customers please use credit cards or send sterling cheque or bank draft.



VISA

SEND 2 x 1st CLASS STAMPS FOR OUR 2000 KIT CATALOGUE CONTAINING FULL DETAILS OF THESE AND OTHER KITS.

A BUILD-UP SERVICE IS AVAILABLE ON ALL OF OUR KITS, DETAILS IN CATALOGUE. VISIT OUR WEBSITE: www.suma-designs.co.uk

Please note: Some of our part numbers are being unscrupulously used by other companies selling kits eg. MTX, VXT. DO NOT BE MISLEAD! These are NOT GENUINE SUMA KITS which are only available direct from us or our appointed distributors.

If you wish to collect kits direct from our office
PLEASE TELEPHONE


SUMA DESIGNS

Dept. EE, The Workshops, 95 Main Road,
Baxterley, Warwickshire, CV9 2LE, U.K.
Website: www.suma-designs.co.uk

TEL/FAX: 01827 714476
(24 HOUR ORDERLINE)
email: sales@suma-designs.co.uk

CIRCUIT SURGERY

ALAN WINSTANLEY
and IAN BELL

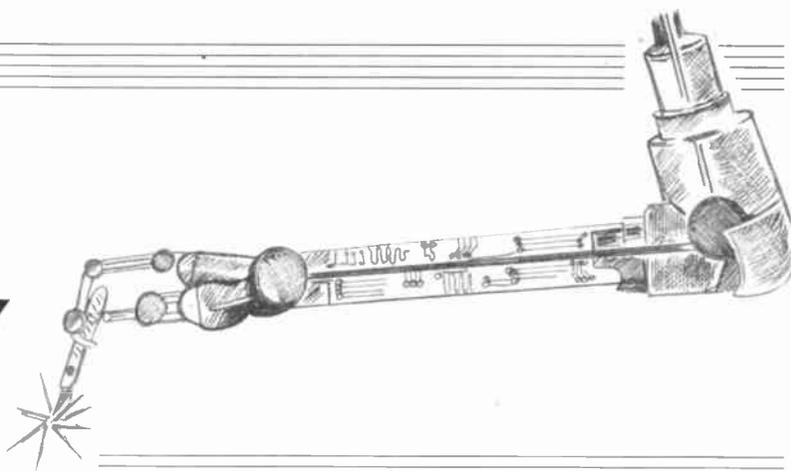

Our intrepid circuit surgeons explore switched-mode power supplies, whilst under heavy sedation!

Switched Mode Supplies

Richard Torpey of Merseyside writes by E-mail, asking for advice about designing step-up voltage regulators:

A friend of mine has recently asked me to construct a microphone pre-amplifier for portable use, running from a 9V PP3 cell. The microphone he's using requires a +48V (in practice, anything from +40V to +50V) supply (phantom powering) to operate.

I have identified a circuit which provides the necessary gain and d.c. blocking to satisfy this function, and it runs quite happily off a bench PSU. However, I cannot find an easy solution for obtaining a +48V supply.

A method considered was generating a sine wave to feed a step up transformer primary, and rectifying and smoothing the secondary output, but finding a suitable transformer for this application seems difficult.

I have heard of a solution involving use of a "Cockroft Ladder" voltage-doubling network, but am unsure as to how such a system would be put into practice for the desired application. The most important considerations are, primarily, obtaining a clean, steady +48V output, and also efficiency to preserve battery life. Current consumption will be in the order of milliamps.

As Richard indicates, there are a number of possible approaches to this problem. We will look at a number of solutions to step-up voltage converter design in general over the next couple of months, hopefully Richard will then be able to select a circuit suitable for his application. But before we start, let's check some basic concepts.

Efficiency is often a key parameter in power conversion. Power is given by voltage multiplied by current ($V \times I$), so if a power converter is 100 per cent efficient then $P_{in} = V_{in}I_{in} = P_{out} = V_{out}I_{out}$. If the converter is less than 100 per cent efficient, then P_{out} will be less than P_{in} by the efficiency factor.

In this application we need a high efficiency so that the battery is not drained too

quickly. The ideal situation of $V_{in}I_{in} = V_{out}I_{out}$ also shows us that if we increase the voltage ($V_{out} > V_{in}$), the current available at the output will be proportionally less than I_{in} . With a perfect converter, 5mA at 48V output would draw 27mA from a 9V input. A real converter would draw more current, which should be borne in mind when considering battery life.

Regulation

Another important power supply specification is regulation. In fact, there are two factors to consider here – *line regulation* and *load regulation*. Line regulation indicates how much the output voltage changes as the input voltage changes, and it's calculated using:

$$\text{Line regulation} = \frac{V_{out} \text{ at max input} - V_{out} \text{ at min input}}{V_{out} \text{ required}} \times 100\%$$

Load regulation indicates how much the output varies with varying load and is calculated using:

$$\text{Load regulation} = \frac{V_{out} \text{ at 50\% load} - V_{out} \text{ at full load}}{V_{out} \text{ required}} \times 100\%$$

There may be a small a.c. signal superimposed on the d.c. output of a supply. This is known as a "ripple voltage" and is usually expressed simply in volts, but could also be given a percentage of the supply voltage.

Richard suggests the use of a sine wave generator feeding a transformer as a possible approach. The transformer provides the voltage step-up in accordance with its turns ratio and must be driven by a varying voltage (only a.c. signals are coupled to the secondaries of transformers).

In mains power supplies the input to the transformer primary is a 50Hz or 60Hz sine wave, depending where you live. For d.c. to d.c. "converters" (a power supply circuit that raises a lower d.c. voltage to a higher one), neither a sine wave nor a frequency as low as this need be used. Higher frequencies enable smaller transformers to

be used, and furthermore if it operates above audio frequencies, then it will allow for silent operation (otherwise some transformers may emit an annoying whine or whistle).

Pulsed inputs to the transformer (or other type of inductor) are commonly used in "switching power supplies" (ones which use an oscillator to generate pulses which can be converted into a higher voltage output), as they are relatively easy to generate using control logic. This logic often uses pulse modulation (switching pulses on or off, or modifying their length) to control the output voltage as the load varies.

Royer Converter

A classic power converter circuit in which the transformer input is a switched waveform rather than a sine wave, is the "Royer Converter" described by G.H. Royer in 1954. This is shown in its basic form in Fig.1.

The circuit is self-oscillating, with feedback provided from a transformer winding. The oscillation is "square wave" in nature rather than sinusoidal because the transformer is driven into saturation (an appropriate transformer must be used to achieve efficient operation).

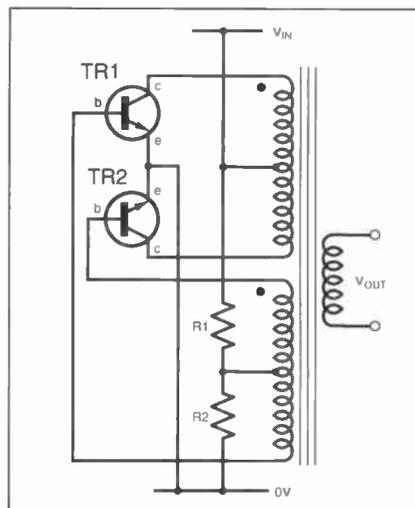


Fig.1. Basic Royer power converter.

The resistor network provides bias and ensures that the circuit starts oscillating when power is applied. The transistors switch on and off out of phase with each another, with a duty cycle of 50 per cent. The voltage induced in the secondary winding depends on V_{in} and the transformer turns ratio. Appropriate transistors should be used which have a high gain (h_{FE}), low $V_{CE(sat)}$, low on-resistance ($R_{CE(sat)}$) and high collector-base breakdown voltage. Transistors specifically designed for high current switching applications should be used.

In Fig.2 is shown a modified Royer converter based on a circuit from a design note by Zetex (www.zetex.com), who are renowned for high current, high performance transistors including the ZTX650, ZTX849 and ZTX449, which are suitable for use in these circuits. The circuit is a slight modification of Fig. 1, which itself does not need a centre-tapped feedback winding.

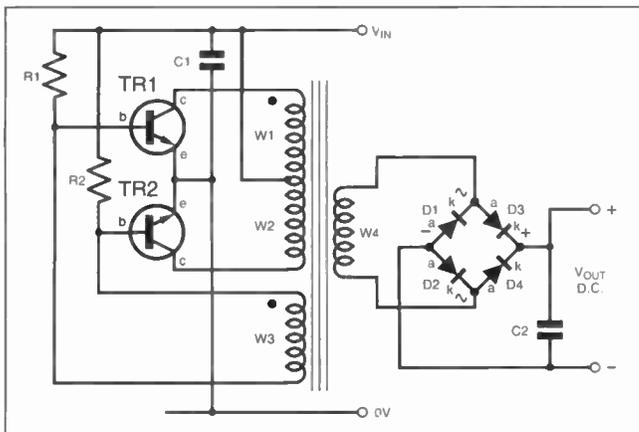


Fig.2. Royer step-up d.c. to d.c. converter.

The Zetex circuit uses two ZTX449 transistors, two 560 ohm resistors and two ceramic 100nF decoupling capacitors, together with a suggested toroidal transformer, with windings W1 and W2 (primary) having 10 turns, W3 (feedback) at 4 turns and W4 (secondary) at 28 turns. Note that this circuit has not been proven by us: if you decide to wind your own toroid, simply wind the correct number of turns using as thick an enamelled copper wire as can be accommodated by the ferrite core.

The output is 12V at 2W from a 5V supply at 77 per cent efficiency, and has an operating frequency of over 80kHz. Increasing the input voltage or number of secondary windings will give a higher output voltage (adjust the resistors and capacitors to suit).

Other Zetex switching transistors (or equivalent) may be used in more demanding versions of the circuit. We have shown the rectifier and smoothing capacitor in Fig. 2, but will not do so in all the circuits in order to save space. As Zetex says, circuits like this look deceptively simple, but many components interact in a complex way.

Having said that "the use of sinewaves is not necessary", there are step-up converters that *do* use sinusoidal oscillation, which can be useful at times. The use of sinewaves cuts the level of harmonics of the basic switching frequency, which can otherwise be responsible for radio frequency noise and

interference (r.f.i.). A modified Royer circuit, in which sinusoidal operation occurs due to the presence of the inductor L1 and capacitor C1, is shown in Fig.3.

Switch Mode

Finding a suitable transformer for a particular step-up power supply design can be very difficult; it is possible to wind your own transformer using the various ferrite core kits etc. which are sold for this purpose, but this adds another dimension to the design problem that not everyone would want to tackle. Useful results can often be obtained by experimenting to optimise the circuit.

However, it is not necessary to use a transformer to produce a step-up converter – some switch mode power supply (SMPS) configurations only require an inductor, and certain voltage multiplier and charge-pump circuits achieve step-up neatly by using capacitors (but voltage multipliers are usually driven from a transformer secondary). We will look at each of these options next, and also in next month's column.

An example SMPS circuit, using a National Semiconductor LM2586-ADJ device, is shown in Fig.4. An SMPS design is often regarded as being quite difficult – which is true if you do not follow manufacturer's design guidelines, and also because they are demanding circuits requiring the use of appropriately specified components together with high quality construction. At this point it should be mentioned that the higher voltages generated with ease by these efficient circuits must be treated with due respect, using suitably-rated parts, with good insulation and reasonable standards of assembly.

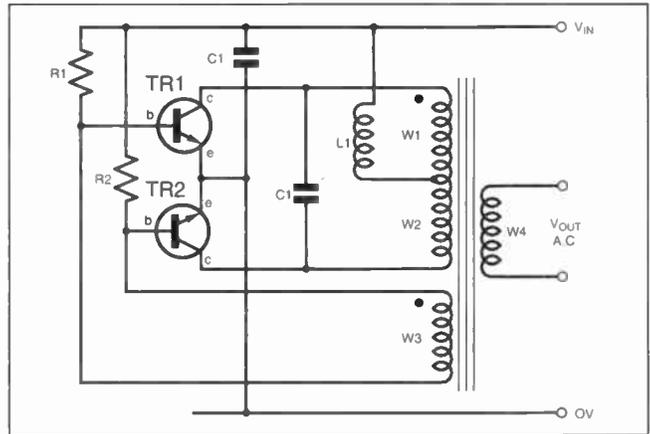


Fig.3. Version of Royer circuit with sinusoidal operation.

Design On-line

Rather than struggle, we took the easy, modern route and obtained this circuit using on-line tools available on National Semiconductor's Power Web Site at www.national.com/appinfo/power/. This is a particularly interesting site which allows you to design and simulate SMPSs on-line using National's versatile WebBench^(tm) and WebSIM^(tm) tools. The web site even allows you to organize your designs with secure password protected storage. Design details including your specifications, bill of materials, schematic, and simulations results are stored on the server, and are available on-line.

Note that the WebSIM simulation tools are installed on a server owned by National Semiconductor, not on the user's machine, as would be the case with most simulators. The user gains access to the simulator using a browser, executing the simulation on the server instead of on their own machine.

This enables very large amounts of computing power and memory to be used by the simulator environment. The simulation tools can be constantly upgraded, ensuring that users always have the most up-to-date version.

We created an SMPS for an 8V to 10V input and 47V output using National's on-line tools, and we simulated the steady state output from the circuit using WebSIM to obtain the results shown in Fig.5. Note that there is about 400mV of ripple on the supply. Using a large value for C_{out} could reduce this.


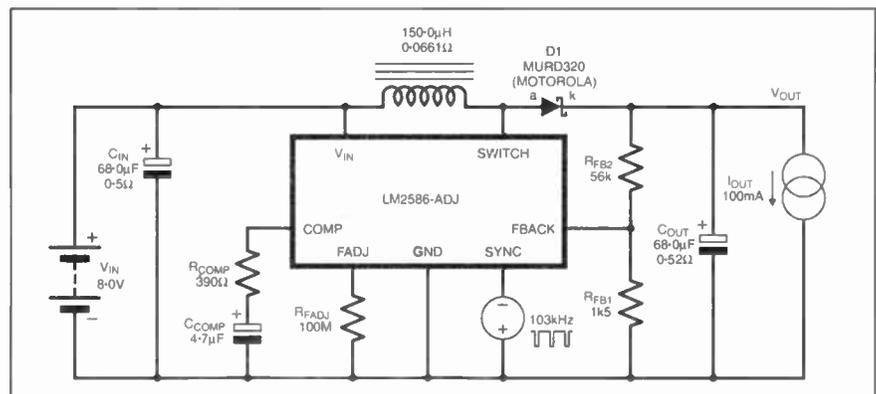


Fig.4. Switched-mode step-up converter for 8V to 10V input giving 47V output. Courtesy National Semiconductor's web site (see text).

Learn The Easy Way!

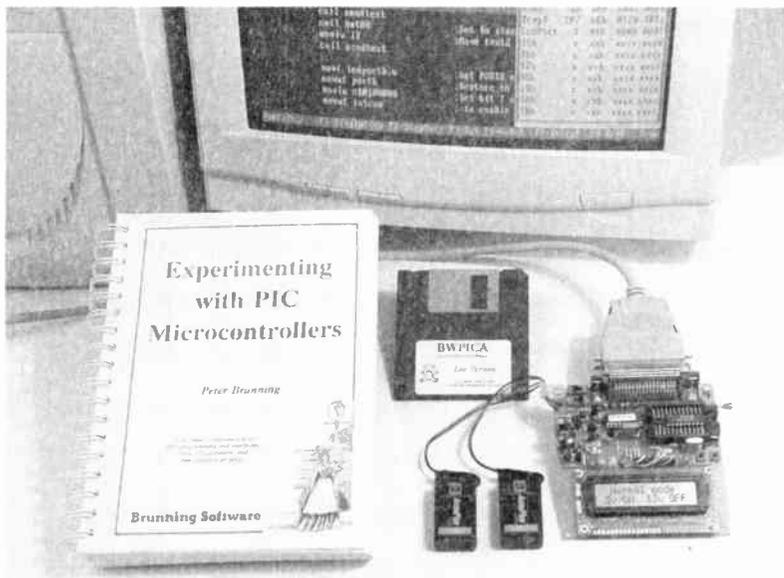

Experimenting with PIC Microcontrollers

This is the easiest way to start programming and interfacing the PIC16F84 and PIC16C711 microcontrollers. The system consists of the book, a programmer/experimental module, and an integrated suite of programmes to run on a PC.

The importance of the information being in a real book rather than given as computer files cannot be over emphasised. The book lies open on your desk while you use the computer to work through the experiments, but that is just the beginning of the ease of use of this system. We start with the simplest possible experiment and the book gives step by step instructions. As we finish typing each line it is tested by the programme to ensure that it can be assembled and the machine code is displayed at the top right of the screen. Then without leaving the programme we assemble the text into PIC code, and use the simulator to single step the programme. Watching the data in the registers change and seeing this in decimal, binary and hexadecimal numbers at the same time solves the problems at a stroke. You see it happen and understand what you have done, and when our programmes use the alphanumeric liquid crystal display the simulator shows what will be displayed. Then without leaving the programme we write the code into the test PIC and run the programme in the real world. BWPICA does it all there are not three programmes to continually swap between.

The 24 experiments are all performed using the programmer/experimental module. Flashing LEDs, text display, real time clock, period timer, beeps and music, including a rendition of Beethoven's *Für Elise*. Then there are two projects to work through; building a sinewave generator covering 0.2Hz to 20kHz, and investigating measurement of the power taken by domestic appliances. The system works through from absolute beginner to experienced engineer level.

Programming PICs

The assembler understands normal PIC terminology. This has two distinct advantages for beginners over the usual system; it is not necessary to start programmes with a list of definitions, and the assembler recognises errors such as *call intcon* because it knows that *INTCON* is a register not a subroutine name.

The programmer module uses its own PIC to control the timing and voltages required to programme the test PIC. The programming is performed and verified at normal 5 volts, then verified with $\pm 10\%$ volts applied to ensure that the device is programmed with a good margin and not poised on the edge of failure. The system will also programme similar PICs (83, 710, 71, 620, 621 etc).

The module is supplied with a test PIC fitted, and requires two PP3 batteries which are not supplied.

Assembler

The first book *Experimenting with PC Computers* with its kit is the easiest way ever to learn assembly language programming, simple circuit design and interfacing to a PC. If you have enough intelligence to understand the English language and you can operate a PC computer then you have all the necessary background knowledge. Flashing LEDs, digital to analogue converters, simple oscilloscope, charging curves, temperature graphs and audio digitising.

C & C++

The second book *Experimenting with C & C++ Programmes* uses a similar approach. It teaches the user to programme by using C to drive the simple hardware circuits built using the materials supplied in the kit of parts. The experimental circuits build up to a storage oscilloscope using relatively simple C techniques to construct a programme that is by no means simple. When approached in this way C is only marginally more difficult than BASIC and infinitely more powerful. C programmers are always in demand. Ideal for absolute beginners and experienced programmers.

The Kits

The kits contain the prototyping board, lead assemblies, components and programming software to do all the experiments. The 'made up' kits are supplied ready to start the first experiment. The 'unmade' Kits require the prototyping board and leads to be assembled and soldered before you can start. The 'top up' kit CP2t is for readers who have purchased a kit to go with the first book, and contains all the components and programming software but not the prototyping board or leads. The kits do not include the book.

Hardware required

All three systems assume you have a PC (386 or better) and a printer lead.

Mail Order Form

Please make your cheque/PO payable to *Brunning Software* and send with this form to *Brunning Software*, 138 The Street, Little Clacton, Clacton-on-sea, Essex, CO16 9LS. Your order will be processed as soon as your cheque arrives. Despatch is usually the same day. Software supplied on 3.5" HD discs. *The kits do not include the book.*

Book <i>Experimenting with PCs</i>	£21.50
Kit 1a 'made up' with software and ready to start.	£45.00
Kit 1u 'unmade' with software, needs assembling.	£38.00
Book <i>Experimenting with C & C++</i>	£24.99
Kit CP2a 'made up' with software and ready to start.	£32.51
Kit CP2u 'unmade' with software, needs assembling.	£26.51
Kit CP2t 'top up' with software, to add to kit 1.	£12.99
Book <i>Experimenting with PIC Microcontrollers</i>	£23.99
PIC Programmer/experimental module with software.	£62.51

Prices include VAT if applicable. Postage charges must be added to all orders.
UK postage £2.50 per book and £1.00 per kit. Maximum charge £7.50.
Europe postage £3.50 per book, £1.50 per kit. Rest of world £6.50 per book, £2.50 per kit.

Name.....
Address.....
.....
.....
.....
Postcode..... Date.....

Telephone for full details.

Mail order address:-

Brunning Software

138 The Street, Little Clacton, Clacton-on-sea,
Essex, CO16 9LS. Tel 01255 862308.




ICEBREAKER
 OOOOOOOOOO

20MHz full speed operation
 PC Serial port connection
 Use With Microchip MPLAB
 Standard MPASM Language
 PCB with solder mask & component ID
 Kit with all components, PIC16F877
 Solderless Breadboard, Icd,
 Serial Lead, and Software
 Kit 900 £34.99

MAGENTA
 ELECTRONICS LTD

PIC Real Time In-Circuit Emulator

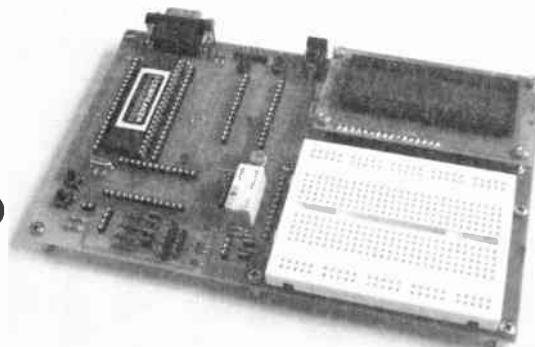

Stepping Motor & Power Supply Extra

135 Hunter Street, Burton-on-Trent, Staffs. DE14 2ST
 Tel: 01283 565435 Fax: 546932
 http://www.magenta2000.co.uk
 E-mail: sales@magenta2000.co.uk
 All Prices include VAT. Add £3.00 p&p. £6.99 next day

MARCONI 2019A



AM/FM SYNTHESISED SIGNAL
 GENERATOR
 80 kHz - 1040MHz
 NOW ONLY **£400**

H.P. 3312A Function Gen. 0-1Hz-13MHz, AM/FM Sweep/Tri/Gate/Burst etc £300
 H.P. 3310A Function Gen. 0-0.05Hz-5MHz, Sine/Saw/Tri/Ramp/Pulse £125
 FARNELL LFM4 Sine/Sq Oscillator, 10Hz-1MHz, low distortion, TTL output, Amplitude Meter £125
 H.P. 545A Logic Probe with 546A Logic Pulsar and 547A Current Tracer £90
 FLUKE 77 Multimeter, 3½-digit, handheld £70
 FLUKE 77 Series 11 £60
 HEME 1000 L.C.D. Clamp Meter, 00-1000A, in carrying case £60

RACAL 9008

Automatic Modulation Meter, AM/FM 1-5MHz-2GHz



ONLY **£95**

H.P. 8494A Attenuator, DC-4GHz, 0-11dB, N/SMA £250
 H.P. 8492A Attenuator, DC-18GHz, 0-6dB, APC7 £95
 MANY OTHER ATTENUATORS, LOADS, COUPLERS ETC. AVAILABLE

DATRON 1061

HIGH QUALITY 5½-DIGIT BENCH MULTIMETER True RMS/4 wire Res/Current Converter/IEEE

£150

TIME 1051 LOW OHM RES. BOX

0-01 ohm to 1Mohm in 0-01 ohm steps.

£100

STILL AVAILABLE AS PREVIOUSLY ADVERTISED WITH PHOTOS

MARCONI 893C AF Power Meter, Sinad Measurement Unused £100, Used £60
 MARCONI 893B, No Sinad £30
 MARCONI 2610 True RMS Voltmeter, Autoranging, 5Hz-25MHz £195
 GOULD J3B Sine/Sq Osc., 10Hz-100kHz, low distortion £75-£125
 AVO 8 Mk 6 in Every Ready case, with leads etc £80
 Other AVOs from £50
 GOODWILL GFC8010G Freq. Counter, 1Hz-120MHz, unused £75
 GOODWILL GVT427 Dual Ch AC Millivoltmeter, 10mV-300V in 12 ranges, Freq. 10Hz-1MHz £100-£125
 SOLARTRON 7150 DVM 6½-digit Tru RMS-IEEE £95-£150
 SOLARTRON 7150 Plus £200
RACAL TRUE RMS VOLTMETERS
 9300 5Hz-20MHz usable to 60MHz, 10V-316V £95
 9300B Version £150
 9301/9302 RF Version to 1.5Hz from £200-£300
HIGH QUALITY RACAL COUNTERS
 9904 Universal Timer Counter, 50MHz £50
 9916 Counter, 10Hz-520MHz £75
 9918 Counter, 10Hz-560MHz 9-digit £50
 FARNELL AMM255 Automatic Mod Meter, 1-5MHz-2GHz, unused £400

CLASSIC AVOMETER DA116

Digital 3 5 Digit Complete with batteries and leads



ONLY **£30**

SOLARTRON 7045 BENCH MULTIMETER

4½-Digit bright I.e.d. with leads It's so cheap you should have it as a spare

ONLY **£30**

MARCONI TF2015 AM/FM sig gen. 10-520MHz £175
 RACAL 9008 Auto Mod Meter, 1-5MHz-2GHz £200
 LEVELL TG2000MP RC Oscillator, 1Hz-1MHz £50
 Sine/Sq. Meter, battery operated (batts. not supplied) £75
 FARNELL LF1 Sine/Sq. Oscillator, 10Hz-1MHz £125
 RACAL/AMI 9343M LCR Databridge Digital Auto measurement of R, C, L, Q, D £200
 HUNTRON TRACKER Model 1000 £125
 H.P. 5315A Universal Counter, 1GHz, 2-ch £80
 FLUKE 8050A DMM 4½-digit 2A True RMS £75
 FLUKE 8010A DMM 3½-digit 10A £50

RADIO COMMUNICATIONS TEST SETS

MARCONI 2955/2995B £2000
 MARCONI 2955A/2950 £2500
 MARCONI 2022E Synth AM/FM sig gen 10kHz-1.01GHz i.c.d. display etc £525-£750
 H.P. 8672A Synth 2-18GHz sig gen £4000
 H.P. 8657A Synth sig gen, 100kHz-1040MHz £2000
 H.P. 8656B Synth sig gen, 100kHz-960MHz £1350
 H.P. 8656A Synth sig gen 100kHz-960MHz £395
 H.P. 8640A AM/FM sig gen 500kHz-512MHz £400
 H.P. 8640A AM/FM sig gen 500kHz-512MHz £250
 PHILIPS PMS328 sig gen, 100kHz-160MHz with 200MHz freq counter, IEEE £550
 RACAL 9081 Synth AM/FM sig gen 5-520MHz £250
 H.P. 3325A Synth function gen 21MHz £600
 MARCONI 6500 Amplitude Analyser £1500
 H.P. 4275A LCR Meter 10kHz-10MHz £2750
 H.P. 8903A Distortion Analyser £1000
 WAYNE KERR 3245 Inductance Analyser £2000
 H.P. 8112A Pulse Generator 50MHz £1250
 DATRON AutoCal Multimeter 5½-7½-digit, 10E5/10E1A, 1071 from £300-£500

MARCONI 2400 Frequency Counter 20GHz £1000
 H.P. 5350B Frequency Counter 20GHz £2000
 H.P. 5342A 10Hz-18GHz Frequency Counter £800
 FARNELL AP10030 Power Supply £1000
 FARNELL AP7030 Power Supply £800
 PHILIPS PMS418TH Colour TV Pattern Generator £1750
 PHILIPS PMS418TK Colour TV Pattern Generator £2000
 B&K Accelerometer, type 4366 £350
 H.P. 11692D Dual Directional Coupler 2MHz-18GHz £1600
 H.P. 11691D Dual Directional Coupler 2MHz-18GHz £1250
 TEKTRONIX P6109B Probe 100MHz readout unused £60
 TEKTRONIX P6106A Probe 250MHz readout unused £85
 FARNELL AMM2000 Auto Mod Meter, 10Hz-2.4GHz Unused £950
 MARCONI 2035 Mod Meter 500kHz-2GHz from £750
 TEKTRONIX 577 Transistor Curve Tracer £500

ROHDE & SCHWARZ APN 62

Synthesised 1Hz-260kHz Signal Generator Balanced unbalanced output LCD display

£425

H.P. 6012B DC PSU, C-60V 0-50A 1000W £1000
 FARNELL AP9650 1kW Autotransforming £1000
 FARNELL H6050 0-60V 0-50A £750
 FARNELL H6025 0-60V 0-25A £400
 Power Supply HPS3010 0-30V 0-10A £140
 FARNELL L30-2 0-30V 0-2A £60
 FARNELL L30-1 0-30V 0-1A £60
 Many other Power Supplies available
 Isolating Transformer 250V In/Out 500VA £40

WELLER EC3100A

Temperature controlled Soldering Station 200 C-450 C Unused

£125

SPECTRUM ANALYSERS

TEKTRONIX 492 50kHz-18GHz £3500
 EATON/AILTECH 757 0.001-22GHz £2500
 ADVANTEST R3261A 9kHz-2.6GHz synthesised £4000
 H.P. 853A (Dig Frame) with 8559A 100kHz-21GHz £2750
 H.P. 8558B with main frame 100kHz-1500MHz £1250
 H.P. 3580A Audio Analyser 5Hz-50kHz as new £1000
 MARCONI 2382 100Hz-400MHz high resolution £2000
 B&K 2033R Signal Analyser £1500
 ADVANTEST TR4131 10kHz-3.5GHz £2750
 MARCONI 2370 30Hz-110MHz from £500
 H.P. 141 SYSTEMS £550
 8553 1kHz-110MHz from £500
 8554 500kHz-1250MHz from £750
 8555 10MHz-18GHz from £1000

UNUSED OSCILLOSCOPES

TEKTRONIX TDS640A 4-ch 500MHz 2GS £4000
 TEKTRONIX TDS380 dual trace 400MHz 2GS £2000
 TEKTRONIX TDS350 dual trace 200MHz 1GS £1250
 TEKTRONIX TA5485, 4-ch 200MHz etc £900
 H.P. 54600B dual trace 100MHz 20MS £900

OSCILLOSCOPES

PHILIPS PM3092 2-2-ch 200MHz delay etc £800 as new £950
 PHILIPS PM3082 2-2-ch 100MHz delay etc £700 as new £800
 TEKTRONIX TA5465 dual trace 100MHz delay etc £1800
 TEKTRONIX 2465B 4-ch 400MHz delay cursors etc £2500
 TEKTRONIX 2465A 4-ch 300MHz delay cursors etc £900
 TEKTRONIX 2445A/B 4-ch 150MHz delay cursors etc £500-£900
 TEKTRONIX 468 dig storage dual trace 100MHz delay £450
 TEKTRONIX TDS350 dual trace 200MHz 1GS £250
 TEKTRONIX 485 dual trace 350MHz delay sweep £600
 TEKTRONIX 475 dual trace 200MHz delay sweep £400
 TEKTRONIX 465B dual trace 100MHz delay sweep £325
 PHILIPS PM3217 dual trace 50MHz delay £250-£300
 GOULD OS1100 dual trace 30MHz delay £200

JUST IN

HAMEG HM303 4 dual trace 30MHz component tester £325
 HAMEG HM303 dual trace 30MHz component tester £300
 HAMEG HM203 7 dual trace 20MHz component tester £250
 FARNELL DTV20 dual trace 20MHz component tester £180



GOULD OS 300
 Dual Trace 200MHz
£160

MANY OTHER OSCILLOSCOPES AVAILABLE

PORTABLE APPLIANCE TESTER

Megger Pat 2 ONLY **£180**

STEWART of READING

110 WYKEHAM ROAD, READING, BERKS. RG6 1PL
 Telephone: (0118) 9268041. Fax: (0118) 9351696

Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

Used Equipment - GUARANTEED. Manuals supplied

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage

Christmas Project

TWINKLING STAR



BART TREPAK

Add a "sparkle" to your festive decorations.

If you are tired with the old star which usually decorates your Christmas tree and would prefer something more eye catching, then this Twinkling Star circuit could be just what you need!

The star itself can be bought or made from tinsel stuck onto cardboard or a sheet of polystyrene sprayed gold or silver, or indeed simply your old star if it is suitable. The details of this are left to you, this article concerns itself only with the electronics!

TWINKLE TWINKLE

The easiest way to add some interest to the star is to simply light it up and for this light emitting diodes (l.e.d.s) are eminently suitable. They are available in a wide variety of colours and a festive display can be made without resorting to lamps and coloured lenses.

A static display is not very interesting and a flashing display is far more attractive. Rather than simply connecting all the l.e.d.s to an oscillator to make them all flash together, a twinkling effect is more effective and desirable. Twinkling, by its nature of course, suggests some sort of random flashing and this could be achieved by building a number of oscillators each driving its own l.e.d. or group of l.e.d.s.

With a 5-pointed star for example, five separate oscillators would be required each running at a slightly different rate. This would produce an overall random effect but it would be obvious that each l.e.d. was in fact switching on and off quite regularly.

With digital circuits, where the output is a logical function determined by the current inputs (and perhaps even previous states), it is impossible to produce a truly random output where the occurrence of the next state cannot be predicted with any certainty. In these circumstances, a pseudo random code generator (PRCG) based on shift registers is normally used. As the name suggests, this is a circuit which produces a seemingly random series of pulses, although on closer inspection the series is found to repeat at regular intervals.

How long the sequence takes to repeat depends on the number of shift register stages used. By having a suitably large number, the sequence can be made random enough for the application. Such circuits are used extensively in the generation of audio white noise and input signals for logic systems for test purposes, as well as in computer games to introduce the element of chance. They are even used in secure remote controls, which send a different code each time they are used, thus preventing the infra-red transmission being copied and used later by an unauthorised person.

PSEUDO RANDOM

To get an idea of how a PRCG works, it is best to consider the simple arrangement of the 4-stage shift register with XNOR (exclusive-NOR) feedback shown in Fig. 1.

Each shift register stage has an output which can be either 0 or 1. With each successive clock pulse, the output of each stage assumes the state of the preceding stage.

The output of an XNOR gate is high when the inputs have equal logic values. If the values are unequal, however, the output will go low. In Fig. 1, the inputs of the gate are connected to stage outputs Q3 and Q4. The gate's output feeds into the data input (D) of the first stage. Consequently, input D is continually changing its logic state in response to the logic on outputs Q3 and Q4.

Assuming that initially all the stage outputs are each set at 0, the sequence for the shift register is as shown in Table 1.

Table 1. Logic sequence for Fig. 1.

STEP	Q1	Q2	Q3	Q4	D
0	0	0	0	0	1
1	1	0	0	0	1
2	1	1	0	0	1
3	1	1	1	0	0
4	0	1	1	1	1
5	1	0	1	1	1
6	1	1	0	1	0
7	0	1	1	0	0
8	0	0	1	1	1
9	1	0	0	1	0
10	0	1	0	0	1
11	1	0	1	0	0
12	0	1	0	1	0
13	0	0	1	0	0
14	0	0	0	1	0
15	0	0	0	0	1

It will be seen that after 15 clock pulses, the outputs again contain all 0s and the sequence will then repeat. Thus, if l.e.d.s are connected to each of the Q outputs, they will be on for the periods marked 1, and off for those marked 0. To a casual observer each l.e.d. will appear to be switching randomly, although with a short


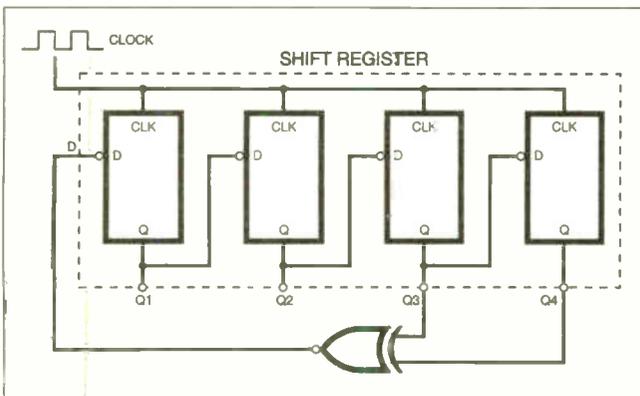


Fig. 1. A four-stage pseudo random code generator based on shift registers and an exclusive-NOR gate.

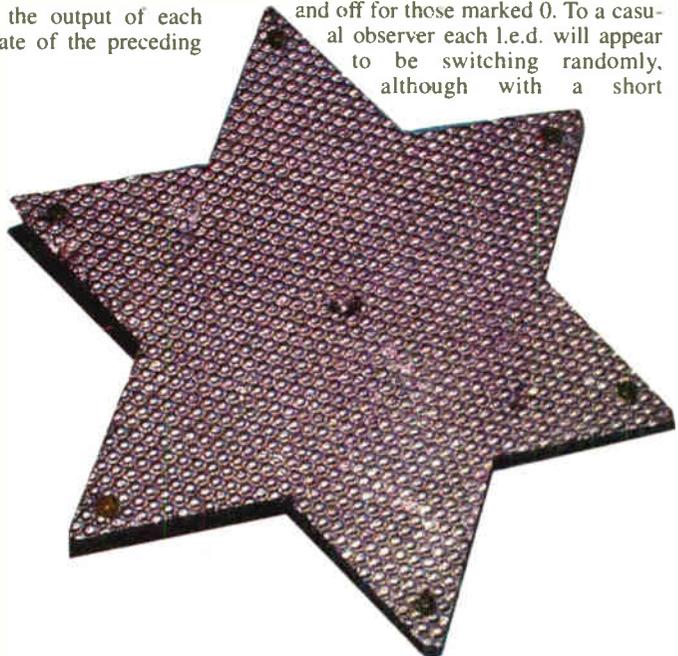

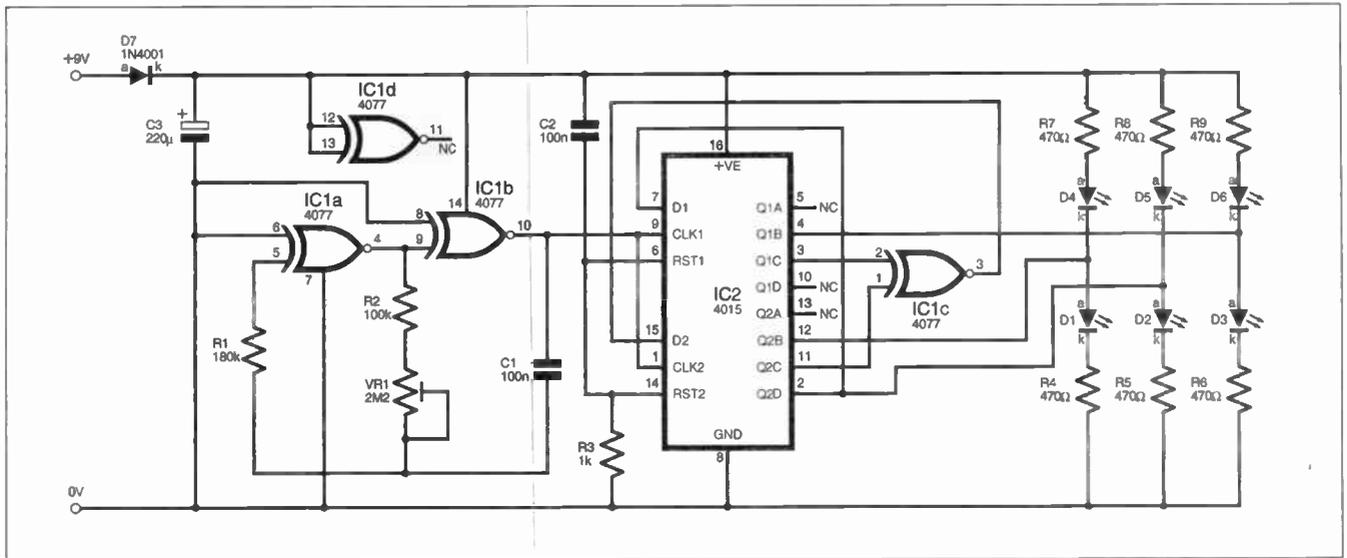


Fig.2. Complete circuit diagram for the Twinkling Star.

sequence like this, a pattern may soon be spotted.

The theory of pseudo random generators is quite complex but a few simple rules can be discerned. It will be noticed, for example, that the switching pattern for each output is the same, except that it is delayed by a certain number of clock periods. Thus the second stage is the same as the first but delayed by one clock period, while the fourth stage is the same but delayed by three periods.

In general, the maximum number of states will be given by $2^n - 1$, where n is the number of stages. In the above example where $n = 4$, the number of different states is $2^4 - 1 = 16 - 1 = 15$.

To increase the maximum number of states, the additional stages must be connected "within" the XNOR feedback loop. Adding them on the end of the shift register "outside" the feedback loop would, of course, only repeat the same patterns again.

The above sequence is known as a "maximum length sequence" and to obtain this, the feedback connections must be chosen carefully. If the outputs had been taken from the second and fourth stages, for example, the sequence would repeat after only six clock pulses. However, if the first and fourth stages were used, the output pattern would also happen to be a maximum length of 15.

You can prove this for yourself if you can run the short QBASIC program in Listing 1. The length of the sequence can be extended by adding more zeros to the length of A\$. The XNOR gate inputs A and B can be "connected" to any Q output by changing the

Listing 1.

```
'TWINKLE TEST
CLS : A$ = "0000": B = LEN(A$) - 1
INPUTA = 3: INPUTB = 4
LOOPIT:
IF MID$(A$, INPUTA, 1) = MID$(
  A$, INPUTB, 1) THEN D$ = "1"
ELSE D$ = "0"
IF VAL(A$) = 0 THEN PRINT
  "START SEQUENCE"
PRINT A, A$, D$: A$ = D$ + LEFT$(
  A$, B): A = A + 1
HOLD: IF INKEY$ = "" THEN
  GOTO HOLD
GOTO LOOPIT
```

number allocated to them in variables INPUTA and INPUTB. The sequence is stepped through pressing any key.

As the program proves, if more stages are used, the feedback will need to be taken from other outputs to obtain a maximum length sequence. Sometimes even more than two outputs are needed (try modifying the program for this), which then requires the use of a network of XNOR gates.

Thus an 8-stage shift-register, for example, happens to require more than two outputs to be used while a seven stage shift-register requires only two outputs to be connected (1 and 7, or 3 and 7) and produces a sequence of 127 states before repeating.

The mathematics for determining the feedback connections are beyond the scope of this article (or of the simple program) but for those interested, the feedback connections for various length shift registers required to obtain maximal length sequences are shown in Table 2.

Note that only those requiring two input feedback are shown.

Table 2: Maximum length sequences

Number of Stages	Feedback Taps	Sequence Length
3	1 and 3	7
4	1 and 4	15
5	3 and 5	31
6	1 and 6	63
7	1 and 7	127
	or 3 and 7	
9	4 and 9	511
10	3 and 10	1,023
11	2 and 11	2,047
15	1 and 15	32,767
	or 4 and 15	
	or 7 and 15	
17	3 and 17	131,071
	or 5 and 17	
	or 6 and 17	
18	7 and 18	262,143
20	3 and 20	1,048,575
21	2 and 21	2,097,151
22	1 and 22	4,194,303
23	5 and 23	8,388,607
	or 9 and 23	
25	3 and 25	32,554,431
	or 7 and 25	
39	4 and 39	5.5×10^{11}

FORBIDDEN STATE

In the previous example, the initial shift-register state was assumed to be all zeros. This was done not only because this was an easily recognised state, enabling the repeating pattern to be more easily seen, but also for a much more important reason. The "all-ones" state would also give an easily recognised condition but this is a "forbidden state" because it would simply cause 1s to be continually shifted along the register and provide no output at all (try it with the program).

In practical circuits this state must therefore be prevented from occurring as it is quite possible that it might occur at switch on.

In this Twinkling Star circuit, however, the problem is side-stepped by using a simple power-on reset circuit.

CIRCUIT DIAGRAM

The complete circuit diagram for the Twinkling Star is shown in Fig.2.

Two XNOR gates, IC1a and IC1b form an oscillator whose frequency is determined by the values of capacitor C1 and the total resistance of resistor R2 in series with preset potentiometer VR1. The latter is used to alter the frequency.

IC2 is a dual 4-bit shift-register. The two registers are connected in series to produce an 8-bit register. XNOR gate IC1c provides the feedback and is connected to the third and seventh stages of the register to give a total of 127 different output states.

The outputs chosen for driving the l.e.d.s are taken from the second, fourth and sixth stages. These provide exactly the same states but separated in time by two clock cycles so that all the l.e.d.s will appear to be switching randomly.

To ensure that there are no periods when all the l.e.d.s are off, each output drives two l.e.d.s., which require opposite logic states to turn them on and off.

Any colour can be chosen for the l.e.d.s, although it may be necessary to change the values of some of the ballast resistors if a uniform brightness between different colours is required.

As the current consumption is fairly high, the circuit should be powered by a small mains adaptor delivering about 9V d.c. Also see later.

COMPONENTS

Resistors

R1	180k
R2	100k
R3	1k
R4 to R9	470Ω (6 off)

See
SHOP
TALK
page

Potentiometer

VR1	2M2 min. vertical preset
-----	--------------------------

Capacitors

C1, C2	100n ceramic, 5mm spacing (2 off)
C3	220μ radial elect. 16V

Semiconductors

D1 to D6	l.e.d., colour of choice (6 off)
D7	1N4001 rectifier diode
IC1	4077 quad XNOR gate
IC2	4015 dual 4-bit shift register

Miscellaneous

Printed circuit board, available from the *EPE PCB Service*, code 276; d.i.l. 14-pin socket; d.i.l. 16-pin socket; 2-pin screw-terminal block, p.c.b. mounting; "star" material (see text); connecting wire; solder, etc.

Approx. Cost
Guidance Only

£14

excluding case

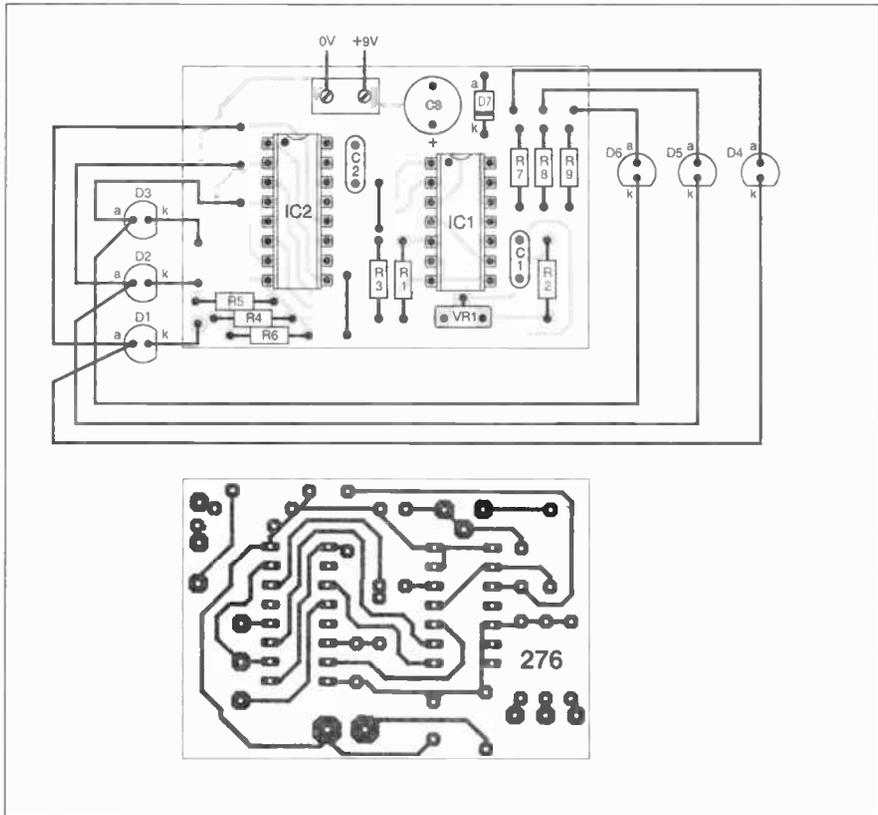


Fig.3. Printed circuit board component layout, interwiring to off-board l.e.d.s and full-size copper foil master.

CONSTRUCTION

The circuit is constructed on a printed circuit board whose details are shown in Fig.3. This board is available from the *EPE PCB Service*, code 276.

Construction should begin with the lowest profile components (i.e. resistors and diode), and then proceed to the capacitors and i.c.s. The latter should be fitted with sockets as they are CMOS devices and prone to damage if mishandled. Touch a grounded (earthed) item before handling them.

In use, the p.c.b. is mounted on the back of the star. This could be cut out from card, polystyrene or some other sheet material on which the l.e.d.s can be mounted. To obtain the maximum flexibility in positioning the l.e.d.s and the size of the star, these are mounted off the p.c.b. and connected to it with suitable lengths of insulated wire.

It is probably best to construct the star first and then mount the l.e.d.s and p.c.b. The wiring details are shown in Fig.3. Care should be taken to ensure that the l.e.d.s are connected the right way around as reversal could cause them not to light.

If you choose to use a 12V d.c. supply, two or three l.e.d.s could be wired in series in place of each l.e.d. shown. This would enable a larger number of l.e.d.s to be mounted on the star, although all l.e.d.s in the same group would light simultaneously, of course. The values of the series resistors would then also have to be adjusted to maintain a suitable level of brightness, and without overloading the output capability of IC2. The l.e.d.s should *not* be connected in parallel.

When complete, there should be a total of nine wires coming from the star for connection to the p.c.b. These should be colour


coded so that there is no confusion about which should be connected to the positive and negative (0V) lines.

Provided the circuit has been wired correctly, it should work without any adjustments. Resistors R4 to R9, however, may need selecting depending on the relative

brightness of the l.e.d.s used. The speed of the flashing can be adjusted according to taste by means of preset VR1.

Finally, there is no reason why this circuit should not be used with some other kind of tree top ornament, a twinkling fairy, snowman or Father Christmas. □

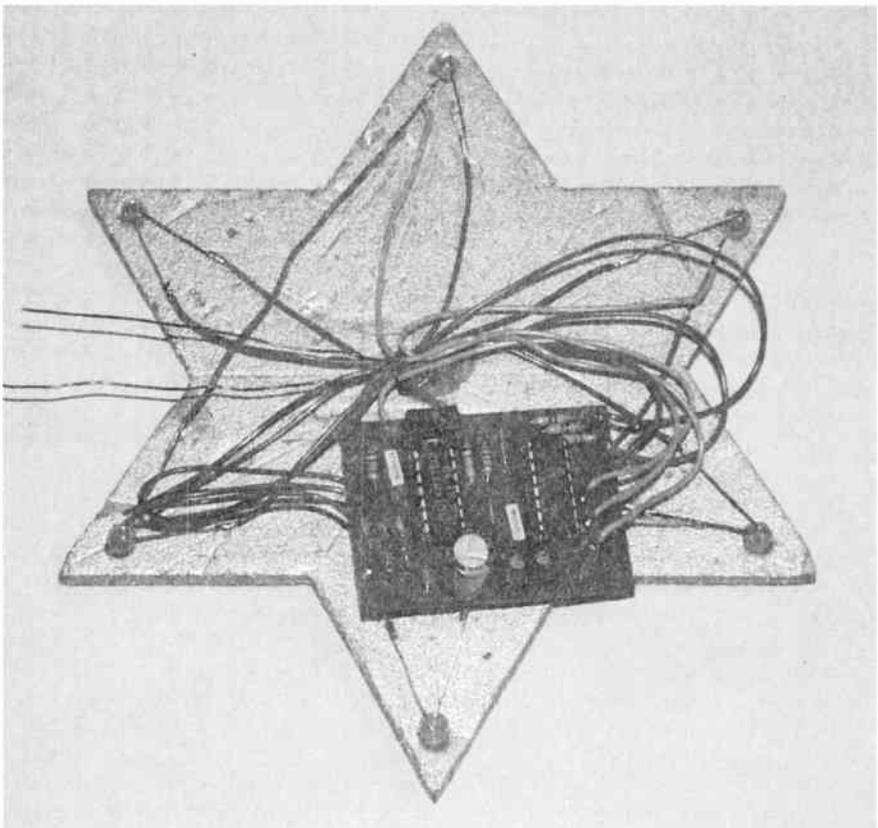
Completed prototype "star" with p.c.b. mounted on the back.



CHRISTMAS BUBBLE

OWEN BISHOP

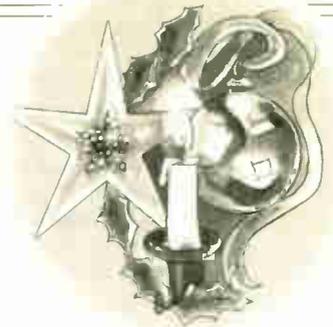Keep the party balloons intact, watch light bubbles burst instead!



Festive Supplement

THIS project gets its name because it looks like a large bubble, repeatedly swelling up and bursting. The effect is produced by arrays of l.e.d.s arranged in three concentric circles with a jumbo l.e.d. in the centre. First the central l.e.d. lights, then the rings around it light up in order, expanding outward until the bubble finally "bursts" then swells again.

This is a flexible project that can be "programmed" for a wide range of effects. There is more than one way to burst a bubble and there are more things to do with any of the l.e.d. arrays. By varying the connections and the layout of the l.e.d.s. all manner of repeating displays may be realised.

Effects can include spinning lights and travelling lights. There is also a spare area of the board on which, for little extra cost, you can set up a more elaborate display or install another complete display driven by the same counter circuit. This simply entails adding two more sets of components repeating those from IC3 onwards.

HOW IT WORKS

The circuit is quite a simple one, for which the schematic diagram is shown in Fig.1. An oscillator, IC1, generates pulses

at about 5Hz. This rate is suitable for producing a lively display. The pulses go to a decade counter, IC2. Its ten outputs repeatedly go high one at a time, in order from 0 to 9.

The next stage consists of four 4-input NOR gates, IC3a/b and IC4a/b, which are connected variously to the counter outputs. If any one or more inputs of a particular NOR gate is high, the output of the gate is low. The output from each gate goes to one of four *pnp* transistors, TR1 to TR4. Pulling low the base (b) of the respective transistor turns it on and current flows to the l.e.d. group, causing the group to light.

For example, as connected in Fig.1, l.e.d. D1 comes on for counts 0 to 4 and goes out for counts 5 to 9. The l.e.d.s in the second group, D2 to D5, are wired in parallel. They come on for counts 1 to 4 and are out for the other counts.

The full sequence for all four groups is shown in Table 1. To make the action clear, it only indicates when l.e.d.s are switched on. They are switched off if not marked.

Other combinations of inputs could alternatively be connected instead to produce other effects, which is why a wide range of lighting sequences is possible with this project.

The breadboard layout in Fig.5 shows the connections required to correspond with Table 1 and the circuit in Fig.1. You may choose different connections if you prefer.

Since different numbers of l.e.d.s are switched, the values of resistors R3 to R10 are chosen accordingly. Table 2 shows the details and selection criteria in relation to a 6V d.c. power supply. The values must be changed if other quantities of l.e.d.s are used should you choose to modify the circuit, or if a different power supply voltage is used.

The groups of l.e.d.s are arranged as shown in Fig.2. All the l.e.d.s in a ring are connected together in parallel. The bubble spreads during counts 0 to 4. The central l.e.d. goes out at count 5. It "bursts" at counts 6 and 7, briefly reappears in outline at count 8 and is gone again at count 9. The sequence then repeats indefinitely, taking about two seconds for each repeat.

Table 1: L.E.D. Switching Sequence.

Count	Centre	Inner ring	Middle ring	Outer ring
0	ON			
1	ON	ON		
2	ON	ON	ON	
3	ON	ON	ON	ON
4		ON	ON	ON
5		ON	ON	
6				
7				
8				ON
9				

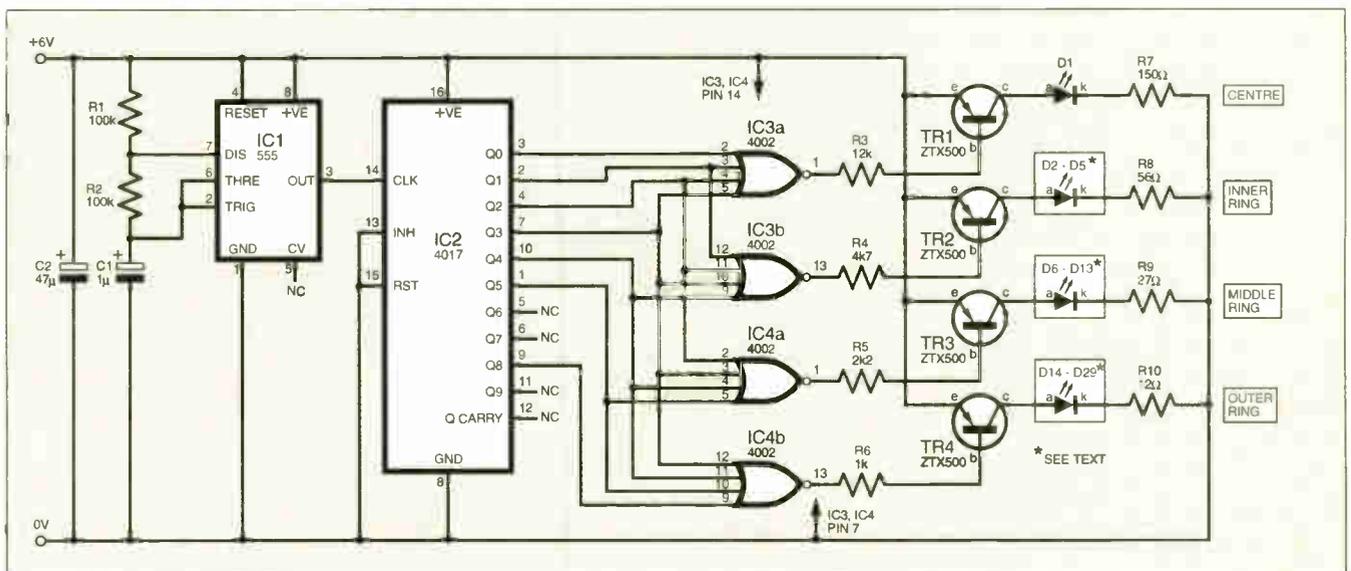


Fig.1. Full circuit diagram for the Christmas Bubble.

As the project is a decoration for Christmas and other festivities, it is likely to be run for several hours at a time. It is powered either by a mains-powered 6V d.c. battery eliminator, which should be capable of supplying at least 500mA. Alternatively, use four D-type cells.

DISPLAY CONSTRUCTION

The display is assembled on a piece of thin card about 120mm square. To make it more decorative, use coloured card or stick coloured paper or cutouts on it.

The l.e.d.s are mounted by pushing their leads through holes in the card (see Fig.3) as far as the lugs will allow. Mark out the circles on the rear of the card and use a stout pin to make pairs of holes about 2.5mm apart, as in Fig.4.

Working on one ring at a time, push the leads of the l.e.d.s through the holes from the front. Make sure that the cathodes (k) of all the l.e.d.s are toward the centre of the circle. Cut each lead to



about half-length, then bend it back to touch the rear of the card. Take a length of solid-strand connecting wire and strip off the insulation. Run the wire around the circle leaving a gap as shown.

Tuck the wire under the bent cathode wires and then use fine pliers to kink the cathode wire more sharply to grip the circular wire. Solder each joint, working as quickly as possible to avoid damaging the

l.e.d.s. Repeat this operation with another wire to join the anodes (a). Repeat the whole operation for each ring and for the central l.e.d.

CONTROL BOARD ASSEMBLY

The component requirements depend on the numbers of l.e.d.s used and the patterns in which they are switched. The components list caters for the Bursting Bubble as illustrated in Fig.1, Fig.2, and Table 1.

The control board shown in Fig.5 carries everything except the battery and the l.e.d.s. Assemble the circuit around IC1, for which a socket should be used. Check your connections and then apply power. Confirm that the output from pin 3 is a series of pulses at about 5Hz.

Assemble the circuit for IC2, again using a socket and checking your soldering. When power is applied, each output gives a 0.2s pulse every two seconds.

Next make the connections between IC2 and IC3/IC4, again using sockets for the latter. Link the like-notation points together, e.g. link Q1 at IC2 to Q1 at both IC3 and IC4. Although only one connection per "Q" is shown at IC2, the horizontally adjacent holes may be used as well for the same notation.

Table 2: Resistor selection detail for a 6V d.c. supply.

Group	Number of L.E.D.s	Total current (mA)	Base resistor	Series resistor
Centre	1 jumbo	20	R3 12k	R7 150Ω
Inner ring	4	60	R4 4k7	R8 56Ω
Middle ring	8	120	R5 2k2	R9 27Ω
Outer ring	16	240	R6 1k	R10 12Ω

COMPONENTS

Resistors

- R1, R2 100k (2 off)
- R3 12k
- R4 4k7
- R5 2k2
- R6 1k
- R7 150Ω
- R8 56Ω
- R9 27Ω
- R10 12Ω

See **SHOP**
TALK
page

All 0.25W, 5% carbon film or better

Capacitors

- C1 1μ radial elect. 10V
- C2 47μ axial elect. 10V

Semiconductors

- D1 l.e.d., 10mm, any colour
- D2 to D29 l.e.d., 5mm, any colour, any shape (28 off)
- IC1 555 timer
- IC2 4017 decade counter
- IC3, IC4 4002 4-input NOR gate (2 off)
- TR1 to TR4 ZTX500 pnp transistor (4 off)

Miscellaneous

Stripboard 29 strips x 39 holes; 1mm terminal pins (6 off), 8-pin d.i.l. socket; 14-pin d.i.l. socket (2 off), 16-pin d.i.l. socket; min. crocodile clip; battery holder for four D-type cells; connecting wire (single-strand and multistrand); solder; card and materials for decoration.

Approx Cost
Guidance Only

£10
excluding batts

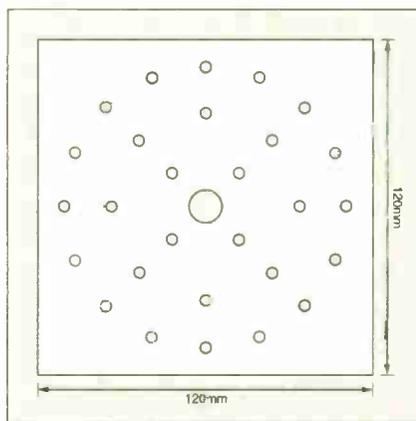


Fig.2 (above left). Front panel display layout and measurements.

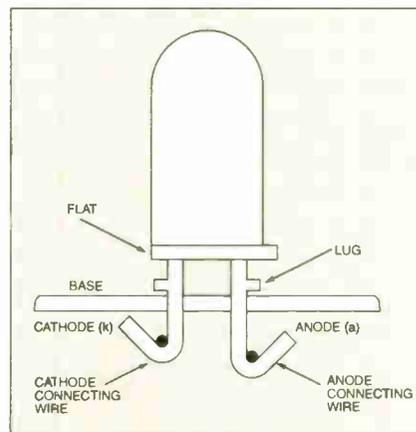


Fig.3 (above right). Suggested method of mounting l.e.d.s on the display wire rings.



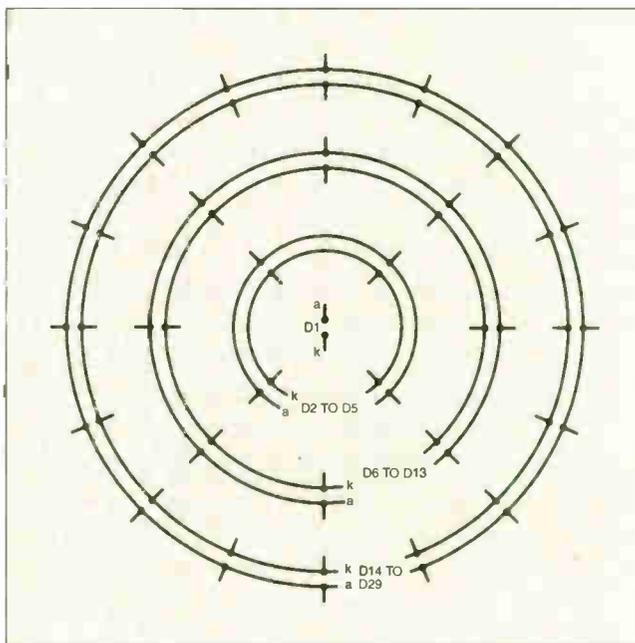


Fig.4 (right). Connecting up the l.e.d.s in groups.

Festive Supplement

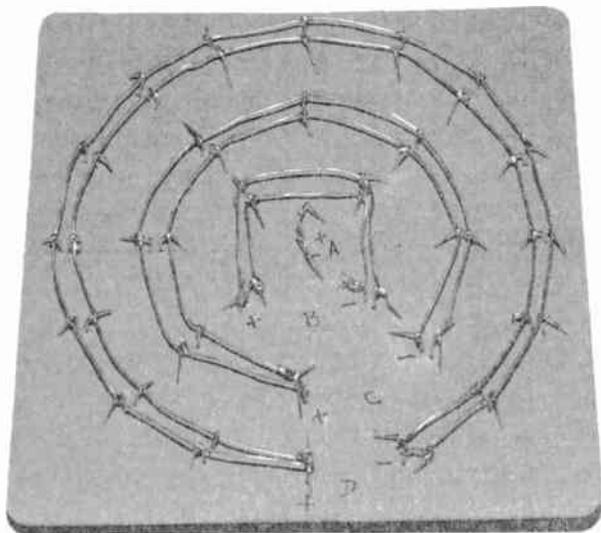

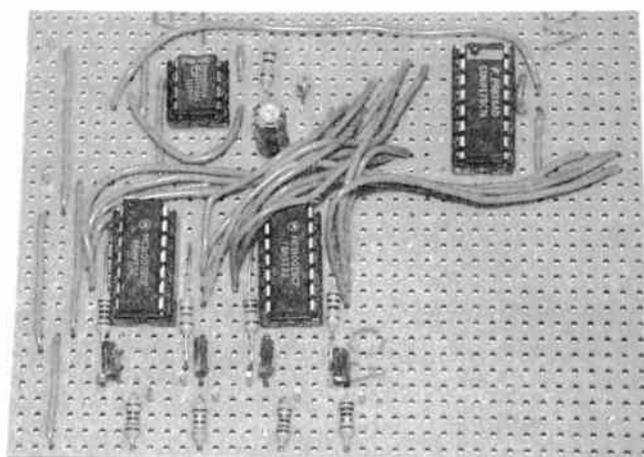The l.e.d.s soldered to the display wire rings.



Completed prototype stripboard component layout.

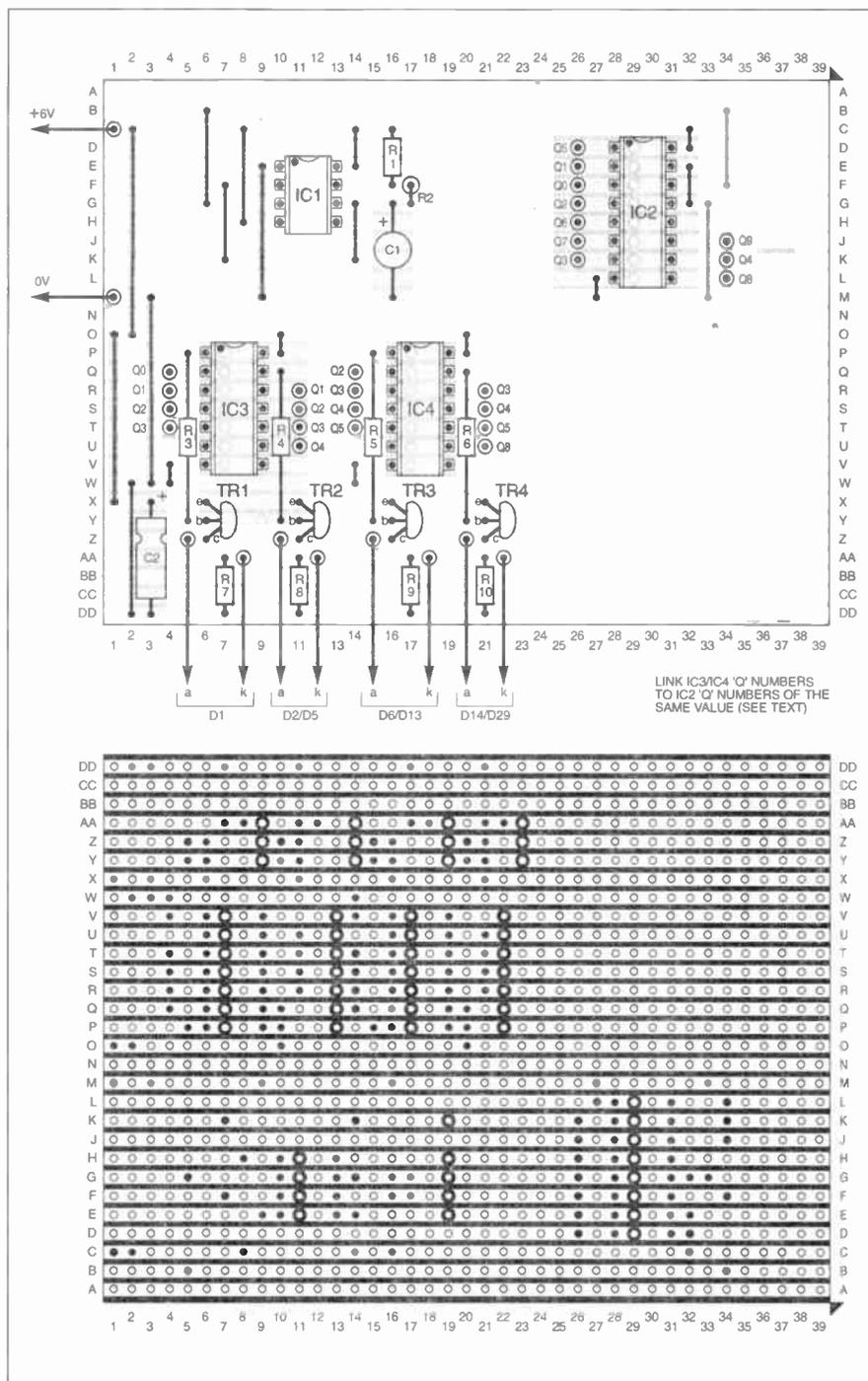


Fig.5. Stripboard component layout and underside copper break details.

Using thin flexible wire, join the ends of the l.e.d. rings to the notated points on the control board. The cathode (k) rings connect to the dropper resistors (pins on row AA) and the anode rings to the collectors (c) of the transistors (pins on row Z), as marked.

You are now ready to view the effect. If any of the l.e.d.s fail to light, check the soldering. Also, check that the l.e.d.s are mounted the right way round, with the "flat" on the rim indicating the cathode pin. If the rows light up out of sequence or at the wrong times, carefully check the connections between IC2 and the inputs of the gates.

A power switch is not really essential for this project. The 0V power line is soldered directly to the negative tag of the battery holder. Make the lead long enough so that the battery can be sited in some inconspicuous place away from the control board and display. Solder a crocodile clip to the positive supply lead. This just clips on to the positive tag of the battery box when power is required.

WRAPPING UP

The final step is to make the project more presentable as an object to hang on the Christmas tree, over the mantleshelf, or outside the front door. The battery box may be camouflaged by wrapping it with Christmas wrapping paper, to that it looks like a present on the tree. Lodge the "parcel" in the angle of a stout branch.

The control box is hidden behind the display panel and may be attached to it by large blobs of Blu-Tack or a double-sided adhesive pad. Beware of creating short-circuits. To improve the appearance further, make a shallow tray of thin cardboard to mount on the back of the display panel to cover the control board.

There are several different sequences that can be devised with the rings of l.e.d.s as in Fig.4. It is also possible to connect them in other ways. For instance the l.e.d.s of the outer two rings can be re-connected in eight sectors of three l.e.d.s each, with opposite sectors connected. Suitable "programming" would give the effect of a rotating fan.

As said earlier, different connections between the counter and the NOR gates could also be made. Make sure that the soldering of any relocated wires is satisfactory before re-applying power.

A Happy and Scintillating Christmas to all readers! □

Christmas Project

FESTIVE

FADER

STEVE DELLOW

Relax your Noelistic senses with smoothly changing lighting effects.

EVERY electronics hobbyist fantasizes about the festive season – it's the greatest opportunity of the year to show off your talents and prove that you can actually build something useful! The reason? The "Christmas Tree Lights Controller", of course! It's your annual chance to dazzle your friends and family with your skills . . . maybe.

Unfortunately, most of the options seem to have been explored by the mass manufacturers. Lights that flash in every conceivable type of sequence and pattern, playing medleys of the most obscure carols ever composed. Not exactly guaranteed to sustain the Christmas cheer.

DESIGN BASIS

The design concept of the circuit described here was to cater for the other end of the market – something a bit more subtle (if that's possible).

Consider the atmosphere late on Boxing Day when the trifle's just been round for the umpteenth time, and the Best Value multipack of beer is proving a little difficult to dispose of.

As you're finally dozing off, the mother-in-law breezes in and crows "Why aren't the Tree Lights on?". And before you can get a cushion over your head, *BattleStar Gallactica* erupts in the corner!

Bad news! What you'd prefer is something a bit gentler on the senses – a display that gently fades up and down over a period of time to assist in generating a more relaxed atmosphere.

Specifically, the circuit uses automatic phase-angle control to produce the slow cycling of a mains load backwards and forwards between the extremes of fully off and fully on.

In our application here, we have chosen to connect a set of Christmas Tree Lights as the load, but the concept can be extended to a wide variety of applications, providing an interesting insight into how low-voltage electronics can be used to safely control substantial amounts of power.

MAINS WAVEFORM

To understand the circuit operation, we must first look at the mains waveform which is available to power the load. The mains electricity supply delivers an a.c. signal to our houses, generally in the shape of a sine wave, as illustrated in Fig. 1.

The size of the potential difference at any moment in time is directly proportional to how much power we can extract from the supply. As you can see, this varies between the peak when we can get a lot of power, and the



zero-crossing points when no power is delivered.

When we switch the lights under normal circumstances we apply the full waveform cycle to our load, and they run at full power. However, in this case, we want to have control of how much power is applied to the load, so we can dim the lights up and down. So in effect we need to have some control over the amount of the mains waveform that is applied.

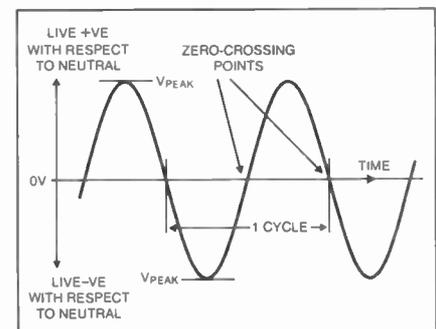


Fig. 1. Mains a.c. waveform.

The two main ways of achieving this are *burst-fire control* and *phase-angle switching*. Both are employed extensively in industrial and domestic equipment to achieve power control. Burst firing is used mainly for loads with a large "inertia" such as heaters, and lets through the a.c. waveform in bursts of complete cycles. In other words, it applies a measured number of full cycles depending on how much power is to be delivered, see Fig. 2.

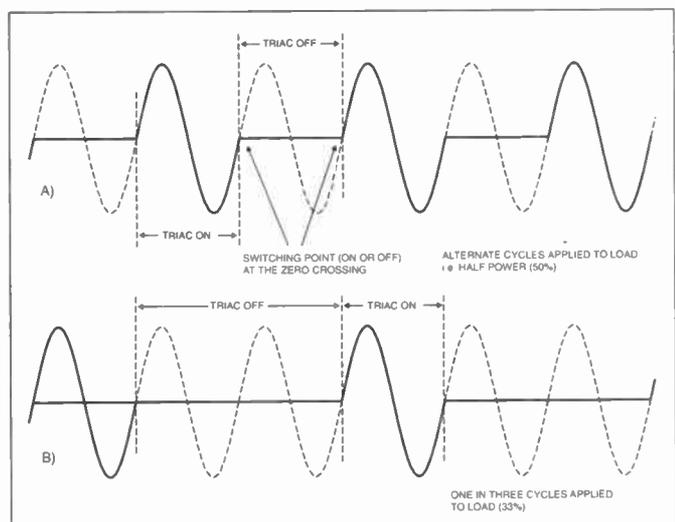


Fig. 2. Burst fire control.



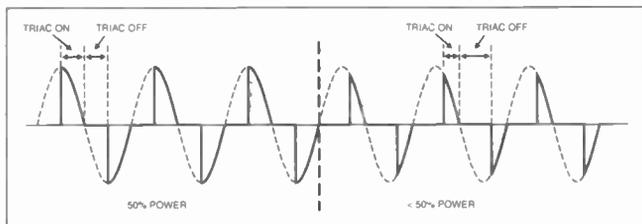


Fig.4 (above). Phase angle control.

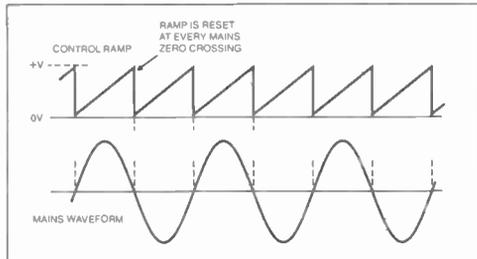


Fig.5 (left). Synchronised control ramp alongside mains waveform.

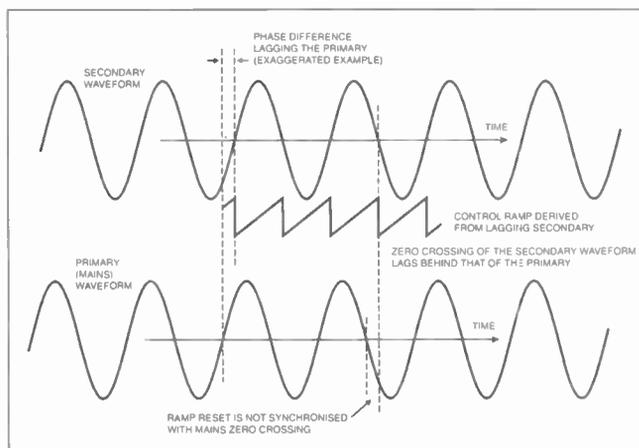


Fig.6. Transformer phase shift problems.

The cycle “blocks” always begin and end at zero-crossing points to reduce switching interference to a minimum. This is fine for large loads but not so for lights, which tend to flicker annoyingly when controlled in such a way – not what we really want.

The alternative is phase-angle control which “chops” up the a.c. waveform, as illustrated in Fig.4. By choosing the point where we apply our “chop” we can accurately control how much energy is passed through into the load, and so we have a means of controlling the brightness of our lights.

There is a risk of interference with this style of switching, but the lights are generally quite low power systems, so it’s not normally a problem.

CIRCUIT DESCRIPTION

Referring to the Festive Fader circuit diagram in Fig.3, power for the system is taken via a small mains transformer, T1, a 3VA type being sufficient to supply the circuit’s needs. The secondaries are joined together in series and fed through a full-wave bridge rectifier, REC1, to convert the a.c. signal to d.c. for the internal power supply.

This raw d.c. is smoothed by capacitors C1 and C2 to give about 9V across each component. The voltage regulator configuration that follows the smoothing capacitors may be a little confusing at first – creating a +10V d.c. supply, but using two regulators to do it! Why not use just a single one and save money?

The reason is that it is necessary to maintain everything symmetrical about the centre tapping of the transformer secondary, so that our zero voltage detection system works.

Since we are using phase angle switching, we need to have a reference that tells us exactly where we are in the mains signal to permit accurate switching of the mains-controlling triac (CSR1).

The chosen method here is to create a rising voltage ramp (or sawtooth) that starts from 0V at the beginning of each half cycle of the mains. This ramp rises linearly until it is reset at the end of the period – see Fig.5.

This will give us the means to control the lamps from fully off to fully on – if we switch the triac on at the far left hand end of the ramp, the lamps will get most of the energy from the associated mains cycle i.e. be very bright. However, if we switch them

when the ramp is a lot “higher”, then less energy is delivered and the lamps are proportionally dimmer. It’s so easy!

ZERO CROSSING

To start (and reset) this synchronising ramp we need to find the zero crossing points of the mains waveform. There are a number of ways of doing this, and a large proportion involve making direct connections to the primary of the transformer. This results in there being a number of “live” components on the circuit board – which can be quite hair-raising when you’re trying to do fault finding!

The argument in favour is that the mains signal in the secondary windings on most cheap transformers cannot be guaranteed to be in-phase with that of the primary. This means that the ramp would be “shifted” in time with respect to the actual mains signal, and we wouldn’t be switching things at the right moment, see Fig.6.

To understand the information in Fig.6, read it in the following manner:

1. Look at the primary waveform
2. Compare it with the secondary waveform (note that it lags behind the primary)
3. The control ramp is derived from the secondary waveform and its zero crossings
4. Compare the ramp reset points with the zero crossings of the primary waveform
5. Start again.

SAFETY RAMP


A “Safety First” approach has been taken with this design, and the ramp waveform has been derived from the transformer secondary. Consequently money is saved on mains-rated components, not to mention rubber gloves! If there does appear to be a phase shift problem there is a simple modification to the circuit to cure this.

A sample of the a.c. signal from the secondary is coupled through C3 and R1, and clipped by diodes D1 and D2 to protect the inputs of op.amps IC3a and IC3b (in Fig.1).

If the signal at pin 2 of IC3a is displayed on an oscilloscope (with reference to 0V), you will see that the waveform is sitting nice and symmetrical between the supply rails. This has come about as a result of the split regulator arrangement, which has made sure that the zero crossing points occur as close as possible to the half supply voltage (5V).

We now make use of the two op.amps IC3a and IC3b to create a zero-crossing detector. The op.amps are both configured as simple voltage comparators. When the non-inverting (+) input is higher than the inverting (-) input, the output is near the supply rail (10V), and when the conditions are reversed, the output switches to ground (0V).

By setting the switching threshold at half the supply voltage, we can use these comparators for zero-voltage crossing

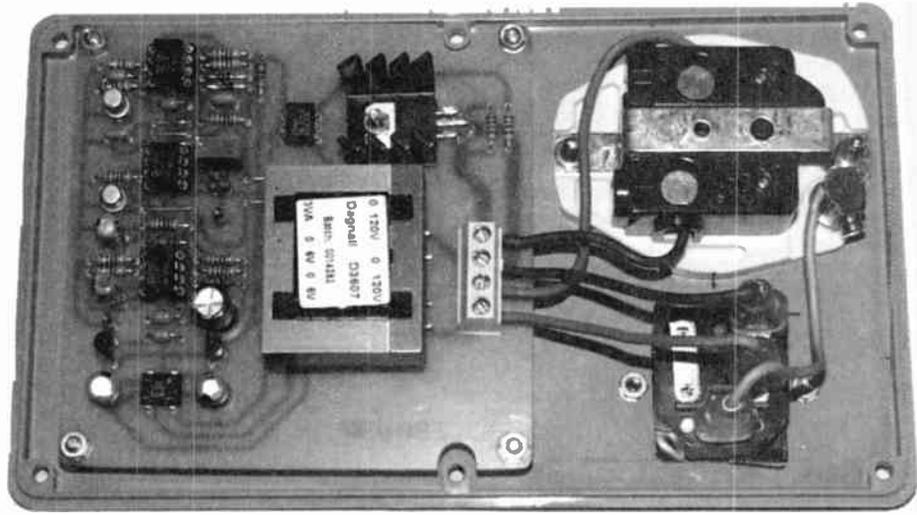

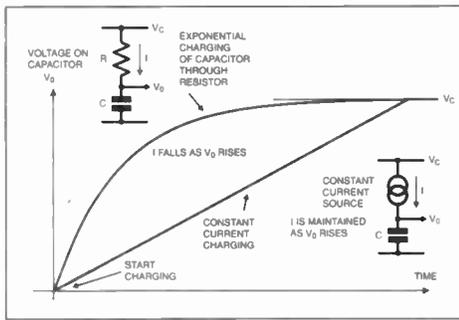


Fig. 7. Constant current charging of a capacitor.

point detection. Their outputs switch between “high” and “low” every time the input signal crosses the threshold (which is effectively the zero-crossing point) and produce a square wave signal at the outputs.

If you look carefully at the connections to the inputs, you will see that this results in the two generated square waves being in anti-phase. When the signal voltage rises through the threshold, IC3a output switches high, but IC3b output goes low, and vice versa when the signal input falls back through the threshold.

So, having created a zero-crossing detector circuit we need to consider how it can be used to synchronise the timing ramp.

RAMP SYNCHRONISATION

The ramp is created by charging up a capacitor under controlled conditions. Generally, we tend to charge up these devices through a resistor connected to a fixed voltage source. This produces the classic exponential curve, because the charging voltage across the resistor falls as the voltage on the capacitor rises. In other words, as time progresses, there's less “push” to force more charge onto the capacitor. See Fig. 7.

However, if we were able to maintain a steady push then the voltage would rise, not in a curve but in a straight line. This steady push is known as a constant current, and is created by adding circuitry that maintains a fixed voltage across the charging resistor. In this circuit, op.amps IC4a and IC4b plus variable-voltage regulator IC5 and preset VR1 are used for this task.

They combine to produce a constant current to charge capacitor C6, and the result is a rising voltage ramp, the height of which is ultimately limited by the supply rail. Op.amp IC4a is wired simply as a unity gain buffer to make sure that the charge (and therefore voltage) on C6 is undisturbed by the operation of the regulator.

The process is relatively simple. Regulator IC5 is used to create a constant voltage across VR1. Because there is a constant voltage across this resistance, there must be a constant current through it. This current pushes charge into C6 and as it does so, the voltage on the capacitor rises.

The regulator responds to this and maintains the voltage across VR1 so that the current is kept flowing at the same rate. The resistance is made variable to allow the ramp to be optimised, and a test point is included to allow it to be displayed on an oscilloscope.

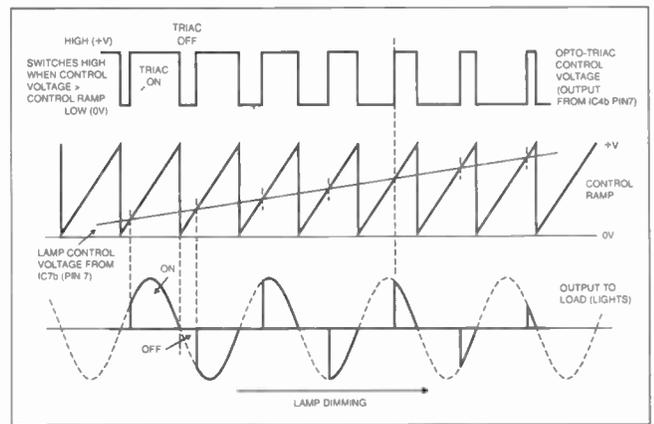


Fig. 8. Opto-triac control voltage.

We have created a ramp, then, but we need to reset it to 0V at the start of each mains half-cycle. This is where we bring in the zero-crossing signal created earlier. A transistor is connected across the ramp capacitor, C6, and by switching this on very briefly at the zero-crossing point, the charge on the top of the capacitor is removed, thus returning the ramp to 0V.

The transistor switching signal is created by differentiating the waveforms from the outputs of IC3a/b. Nice, short switching pulses are produced by the action of capacitors C4 and C5, which allow only the a.c. component of the signal through, i.e. when the voltage changes. The transistor responds only to the positive going pulses and the result is a good, clean reset.

FADE CONTROL

Now that we have a synchronised ramp, the next step is to create some sort of control signal that will command the triac to fade the lights up and down. The simplest method has got to be voltage control – when the voltage is at one extreme, say 0V, we want the lamps to be fully on, and at the other, fully off.


This works in well with the ramp voltage, which is also moving between the

supply rails. Lighting experts may at this juncture remind us that the brightness of an incandescent lamp is not linearly related to the point at which you switch it on during the mains cycle. It's not even a simple matter of doing a mathematical integration, as there are other physical effects that come into play.

For this application it was decided to keep things simple, and the “error” is not really noticeable unless you're sitting right under the Christmas tree with a light meter!

Op.amps IC7a and IC7b are used to produce a slow linear ramp which moves backwards and forwards between 0V and the supply rail – it's really a triangle wave. The rate is set so slow that the signal actually spends time clamped to supply or ground at the top and the bottom before it starts to move back again. These are the points where the lights would be fully on or fully off.

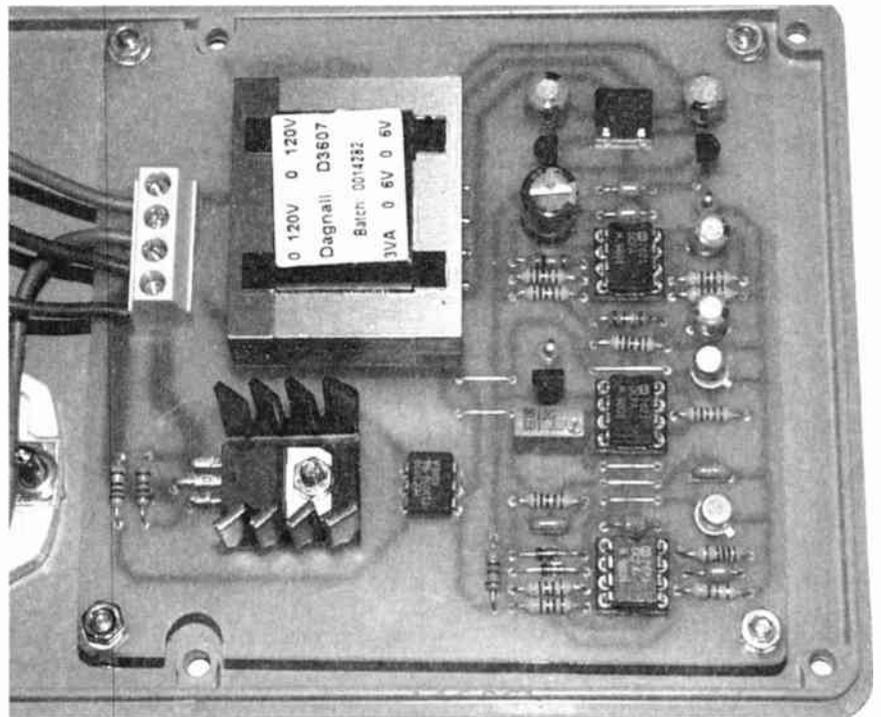The first op.amp, IC7a, is set up as a slow square-wave oscillator. You can see the output switching simply by using a voltmeter. The rate is set by resistor R14



Finished circuit board. It is essential to use an insulating kit to mount the triac heatsink on the p.c.b.

and capacitor C9. Their values could be modified to speed things up a bit, or slow them down even further!

The second stage (op.amp IC7b) operates as an active integrator, turning the square wave input into a ramp. Here, the total value of capacitors C7 and C8 in relation to the value of resistor R12 control the gradient of the ramp, i.e. how fast the lights fade.

TRIAC CONTROL

The final step is to apply a control signal to the triac, and we return to the comparator function of an op.amp to help us here. By applying the zero-crossing ramp and the control voltage to the inputs of op.amp IC4b, we produce a switching waveform, as shown in Fig.8.

Whenever the half-cycle ramp is greater than the control voltage, the op.amp's output switches high and transistor TR2 turns on. This turns on the light emitting diode (i.e.d.) inside the opto-triac package of IC6, which triggers the integral triac into conduction.

The current capability of IC6's triac is limited, so an external device with greater capacity is added to cope with a real load such as our lights. The specified triac will cope with loads up to about 1kW.

So, if the triac is conducting, this means that mains current will flow – and the lights will be on; but only for that half-cycle! When the mains goes back through zero, the triacs stop conducting – so we have to trigger them *every* half cycle. This is why we keep resetting the ramp – we have to keep retriggering the triacs to keep the lights working! Consequently, the circuit is kept very busy while we relax to the gentle fading of the lights . . .

CONSTRUCTION

Since there are mains connections involved in this design it is strongly recommended that the published printed circuit board (p.c.b.) is used rather than stripboard (which isn't voltage rated for such work anyway). The p.c.b. assembly and tracking details are shown in Fig.9. The board is available from the *EPE PCB Service*, code 277.

This circuit should only be constructed by those who are adequately familiar with constructing mains operated circuits.

Before beginning any construction work, get yourself well prepared! Make sure the soldering iron tip is nice and clean, all your tools are close at hand, then find a really quiet spot away from any likely disturbances. Close reference to the circuit layout is essential – time spent here will save much grief later on.

Start by soldering in the wire links – there are six of them in all – plus the two test points. Then move on through the following sequence – resistors, capacitors, bridge rectifiers, and diodes. Then onto the transistors and regulators taking care to get their orientation absolutely right.

If it's all looking good, fit the transformer to the board – which may need a firm push to get its pins snugly down through the holes.

FIRST TEST

Test that the power supply is up and running before fitting the more expensive bits! First, make a careful check of all your soldering – look out for solder splashes, dry joints, solder bridges between tracks, etc. Once again, time spent here can save money . . . use a good magnifying glass to be absolutely sure.

When you've finished, carefully wire up a fused mains supply (one that's Residual

Current Circuit Breaker (RCCB) protected is best) to the inputs marked L and N (Live and Neutral), then make sure that the board is firmly supported on an insulating surface.

Keeping well clear of the live parts, switch on. The check here is to confirm that the 10V d.c. supply is correctly running – there are a number of points in the circuit where this can be measured using a multimeter. Be sure that you know where you're putting your probes before you try

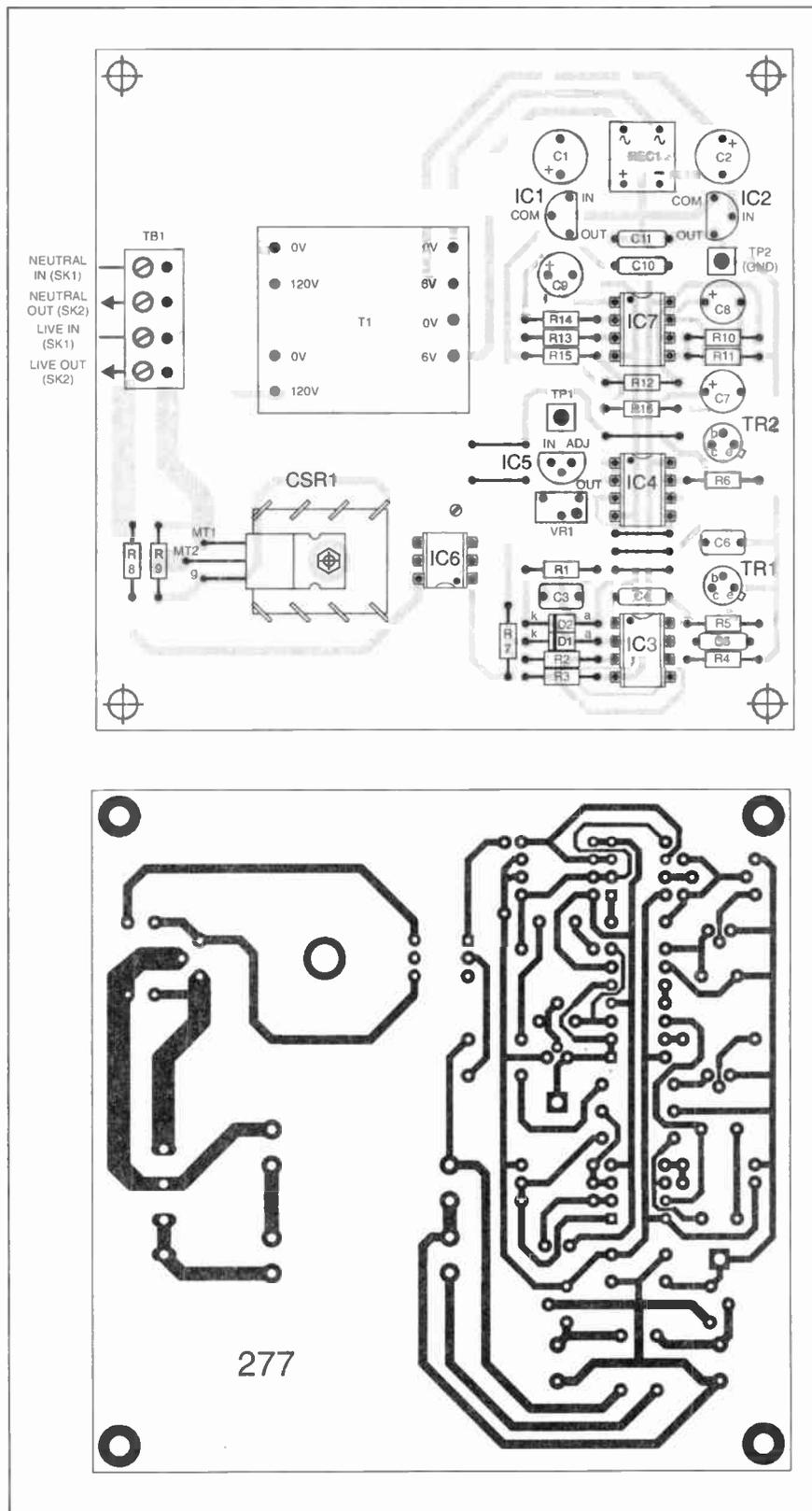


Fig.9. Festive Fader printed circuit board component layout and full-size underside copper foil master pattern. Beware some tracks carry the mains supply.

Festive Supplement

and make a measurement. Always keep your other hand in your pocket to avoid short-circuits through your body.

TRIAC MOUNTING

Once you're confident that everything's getting power, switch off and disconnect the mains connections completely. The integrated circuits (IC3 to IC7) and triac CSR1 can now be soldered into the board. As usual, check carefully that you're putting them in the right way round.

With mains loads up to 60W, the triac can be mounted vertically into the board, but if heavier loads are planned, there's space for it to be bolted down with a small TO220 heatsink. In this case, it is essential that you use an insulating kit, otherwise the heatsink body will be at mains potential!

ALIGNMENT

With everything now in place, it's time for some real action! Another visual check of the installation is definitely worthwhile, then wire up to the mains once again, this time connecting a small mains lamp (60W is fine) to the *Live out* and *Neutral out* terminals.

It would be sensible at this stage to secure the board to some firm surface using mounting pillars in conjunction with the holes provided in the p.c.b. This will keep everything under control while setting up the circuit.

It helps if an oscilloscope is available, but it isn't essential. Adjust preset VR1 to mid-travel, check your mains connections again, then switch on. After about ten seconds, everything should have settled, and the lamp will be fading slowly up and down. The scope is useful to check what shape the ramp is, and this can be done by using the test points.

Ground the 'scope to the 0V point at the edge of the board, and then hook onto test point TP1 for the signal. The ramp should start from 0V, rise to about 9V or 10V then reset to 0V again, repeating every 10ms, so set your scope's gain and timebase accordingly, and check whether this is the case.


Adjust preset VR1 and see what happens to the shape of the ramp – leave it at a setting where the lamp seems to fade at a consistent rate between its two extremes, and spends about the same time at those limits.

If you're feeling adventurous, look at the output waveform on IC4b (pin 7), and you'll see that when this is permanently high the lamp is fully on, but in the low state the lamp is off. When the lamp is fading, you'll see two abrupt waveform edges appear. The falling edge coincides with the reset of the ramp, but the rising edge defines the point in the mains half cycle at which the triac is turned on.

Set the 'scope to trigger on the falling edge, watch the sequence, and see how it relates to what state the lamp is in. It's not the end of the world if you haven't got a 'scope – the ramp can be set just as effectively by watching how the lamp responds – it shouldn't take long.

PHASE CORRECTION

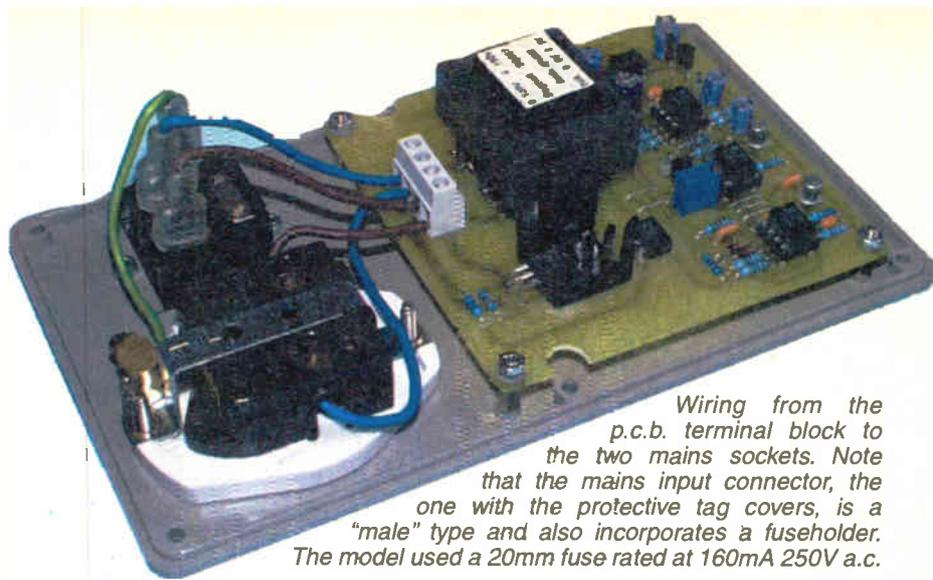It was mentioned earlier that there is a remote chance that the transformer secondary may be sufficiently out of phase with the primary to cause control problems. This could be a lead or a lag error – one will cause the lamp to suddenly go to



Wiring from the p.c.b. terminal block to the two mains sockets. Note that the mains input connector, the one with the protective tag covers, is a "male" type and also incorporates a fuseholder. The model used a 20mm fuse rated at 160mA 250V a.c.

full on at the end of its fade down, and the other will result in the opposite effect.

The simple fix for this is to make some adjustments to the values of resistors R2 and R3. If you're sure that you've got a problem, remove these resistors and substitute a 100k Ω potentiometer, connect its outer terminals to the respective d.c. supply lines and its wiper to the board at the R2/R3 junction point.

Adjust the potentiometer to find a suitable voltage that takes account of the lead or lag error. Then measure its resistances to either side of the wiper to find the new values and fit resistors of about the same value (within the usual E24 series range). Basically, by changing the reference voltage, you're moving the zero-detection point backwards and forwards in time to take account of the error.


ENCLOSURE

Once you're happy with the operation of the circuit, it's time to start putting everything safely in a box. As mentioned earlier, mounting holes are provided to allow the board to be fixed down and pillars are recommended to allow it to stand away from the surface.

For all mains connections, make sure that the cable is overrated for the job – 6A type is probably best. If you decide to use a direct cable connection for the mains input to the terminal connector, make sure that some good strain relief is included inside the box. A single cable tie round the cable is NOT good practice – a P-clip installation is far more professional (and lasts longer)!

The mains earth must be connected to both mains input and output connections. If a metal enclosure is used this *must* also be earthed.

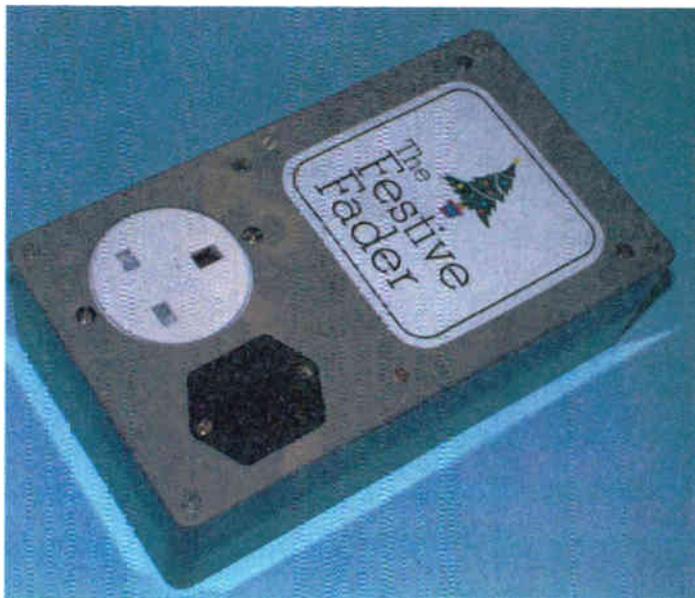Completed unit showing the two mains sockets. The input connector is the "male" type.



For the output side of things a commercial mains socket would appear to be the order of the day, and a chassis mounted type is recommended so as to keep everything compact. As shown in the photographs, connect the earth from the input mains cable directly across to the output socket. If a metal case is being used, make sure that this gets a good earth connection too.


IN USE

This Christmas Tree Lights Controller has proved to be a useful and interesting addition to the festive display. Note that it is intended for use with light sets that connect *direct* to the mains, and *not* via a transformer, so check before you connect up.

As mentioned earlier, there's no need to restrict it to seasonal use, and it probably has a wide variety of other applications, maybe not even using lights as the load. Multiple units would produce a subtle but interesting light-show, and it would be quite easy to extend the basic circuit to a multi-channel system by adding extra control stages.

The other option is to create a totally manual controller by using a potentiometer that gives 0V to +10V into pin 6 of IC4b. Whatever circuit you decide to go with, remember that there's mains power around, so be absolutely sure before you change things! □

PICTOGRAM

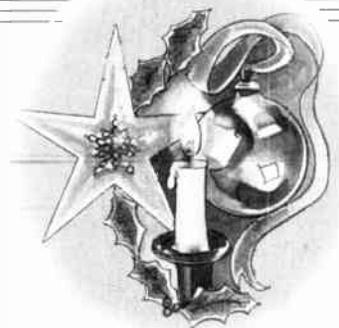

ANDY FLIND

*Become a novelty flasher at the Mad Hatter's (or other's) Xmas party!
(Andy caps it nicely!)*

THE idea for this project germinated around the time the author's son announced forthcoming nuptials. As the groom's father, yours truly was expected to take a fairly prominent part in the proceedings, and those in key roles were requested by the happy couple to wear full traditional dress including, for the men, top hats.

It wasn't long before the notion of a ring of flashing light emitting diodes (l.e.d.s) around this spectacular piece of headgear was conceived. Well, some of us never quite grow up, as our wives frequently tell us.

The resulting display could, of course, equally well be applied to a belt or headband, or to almost any festive decoration.

PIC-TURE THIS!

The task seemed ideally suited to a design using a PIC microcontroller. It's easy enough to make a bunch of l.e.d.s flash with some CMOS logic, but with a PIC the circuit becomes even simpler, and seemingly endless flashing and chasing patterns can be generated with very simple software. Before the advent of these devices these sequences would have required whole boardfuls of components, and would have been almost impossible to implement for this application.

The prototype was practically "thrown together" on stripboard. After all, there are many other matters to be attended to before a wedding and time for such frivolous activities as electronics was in chronically short supply.

HAT TRICK

As the hat was obtained from a dress hire service a way of attaching it without causing damage had to be found, which will be described later.

After the event it was realised that the circuit had almost unlimited possibilities for amusing and eye-catching displays and decorations so it was re-designed onto a small printed circuit board and provided with an optional built-in display. The software was improved and tidied up, and the final result is now suitable for general release to other constructors.

Port A, to drive 12 l.e.d.s. Each has a current limiting resistor, R3 to R14, to control the l.e.d. current. The l.e.d.s used are rated at 2mA, but they are slightly over-driven in this circuit, which results in their being bright enough for most indoor situations.

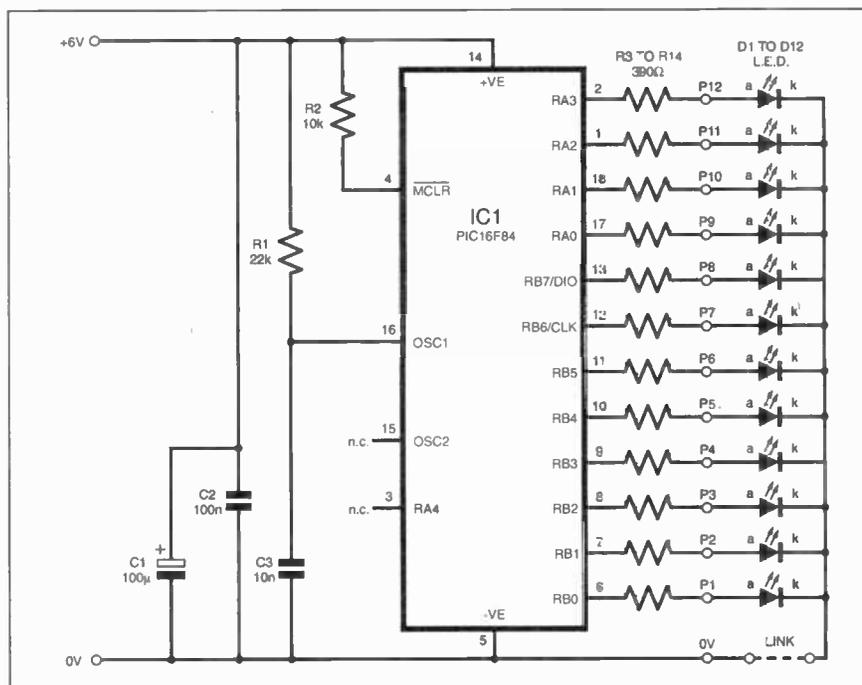


Fig.1. Complete circuit diagram for the PICtogram.

The full circuit for the PICtogram novelty project appears in Fig.1. For the greatest simplicity and lowest cost the PIC's RC (resistor-capacitor) clock option is used with a frequency set by resistor R1 and capacitor C3 to about 4kHz. Since the PIC divides the oscillator frequency by a factor of four, this results in processing taking place at about 1ms per step, which may help to make program timing simple to calculate.

In practice, the effects of the patterns are very subjective, it's easier to just "fiddle" with the timing factors until it "looks right". The MCLR connection is pulled high by resistor R2, which has a higher than usual value to allow it to be programmed "in circuit" by John Becker's excellent PIC Toolkit Mk2 programmer. The high value is needed to allow the 12V programming voltage to pull this pin high enough to obtain programming mode.

Twelve outputs are used, consisting of the whole of Port B and the first four of

It was found necessary to reduce the loading on pins RB6 and RB7 for in-circuit programming. An easy, single-connection way to achieve this is by disconnecting the common-cathode connection to all the l.e.d.s via the link shown in Fig.1.

For extended programming sessions a switch can be connected across this point so that it can be easily disconnected whilst programming actually takes place. The link also allows the built-in l.e.d. display to be easily disabled if the unit is programmed with the help of this and then connected to an external display.

Capacitors C1 and C2 are the usual supply decouplers used in battery operated circuits of this type.

There is a choice of methods for mounting the l.e.d.s. The printed circuit board holds the PIC and its components, plus facilities for mounting 12 l.e.d.s in a small circle.

As discussed later, the l.e.d.s could alternatively be mounted on a separate plastic

strip and connected back to the p.c.b. by a ribbon cable. In this case the ring of l.e.d.s on the p.c.b. would be omitted.

CONSTRUCTION

The PICtogram project is built up on a small printed circuit board (p.c.b.), which also accommodates a ring of programming/display l.e.d.s. This board is available from the *EPE PCB Service*, code 279.

The p.c.b.'s assembly and layout details are shown in Fig.2. It has the built-in ring of l.e.d.s with the common-cathode disconnection link at their centre. A line of connections for external output to the optional l.e.d. assembly is included (terminals P1 to P12, 0V).

Construction of this board is carried out by fitting the link wire, resistors, ceramic capacitors, and then the electrolytic capacitor C1. This capacitor is positioned horizontally on the board to achieve a low profile.

Ideally, a socket should be used for the PIC IC1, but this makes it the tallest component on the board! For the lowest possible profile IC1 could, perhaps, be simply soldered in place if it is to be programmed in situ. However, note that soldering a commercially pre-programmed PIC would probably negate its guarantee.

The l.e.d.s for this board are fitted with their cathodes (k) all facing towards the centre of the circle.

PROGRAMMING TIME

Following construction, it's programming time! A ready-programmed PIC is available for this project with a total of eighteen flashing, rotating and special patterns which are invoked in a sequence which it is hoped will be found both interesting and pleasant. This PIC can be simply fitted into place and the unit powered up, when it should operate with no problems.

COMPONENTS

Resistors

- R1 22k
- R2 10k
- R3 to R14 390Ω (12 off)

See
SHOP
TALK
page

Capacitors

- C1 100μ radial elect. 10V
- C2 100n ceramic
- C3 10n resin-dipped ceramic

Semiconductors

- D1 to D12 red l.e.d., 2mA type (12 off)
- IC1 PIC16F84 microcontroller preprogrammed (see text)

Miscellaneous

Printed circuit board, available from the *EPE PCB Service*, code 279; optional min. s.p.s.t. switch (see text); solder pins; connecting wire; solder etc.

Approx. Cost
Guidance Only

£15


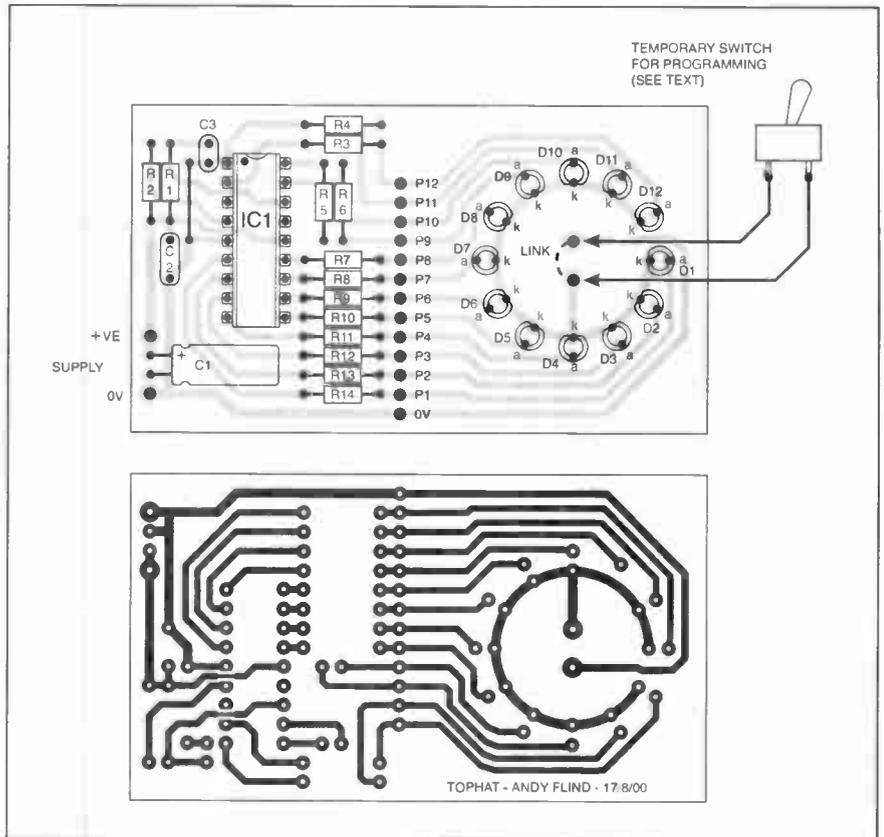


Fig.2. PICtogram printed circuit board (p.c.b.) component layout and full-size copper foil pattern. The completed p.c.b. with the "programming" switch attached to the board is shown below.

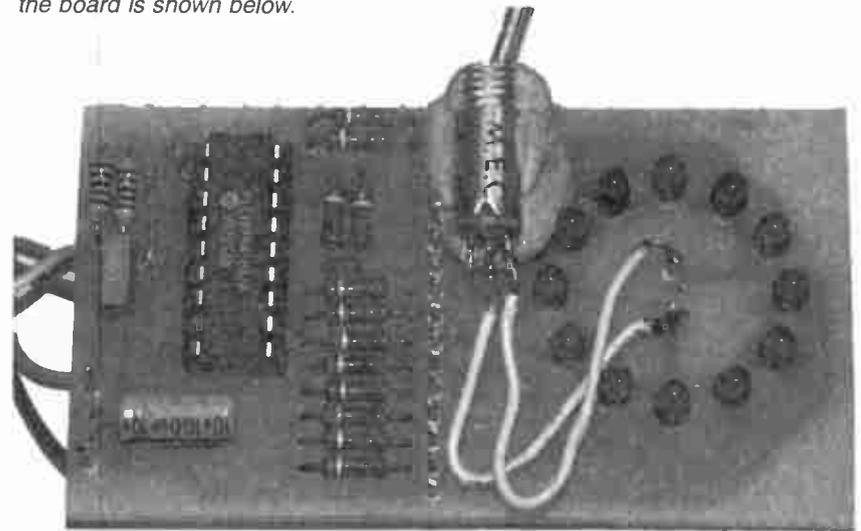

Producing an illuminated plaque or wheel by placing the l.e.d.s around the perimeter of a cardboard disc.

However, the real fun is to be had in writing the programs for a project of this kind and hopefully this is what many readers will choose to do. As mentioned earlier the author used John Becker's *Toolkit Mk2* for programming, though it has to be admitted that the one used had been modified to include, amongst other things, a beefier 5V regulator.

If a "standard" *Toolkit Mk2* is used, it would be advisable to keep an eye on the temperature of the regulator when the i.e.d.s are being driven, or to use an external supply for this project.

The connections for in-circuit programming are shown in Fig.3. *Toolkit Mk2* makes programming a very simple operation since the 12V programming voltage and reset pulses to MCLR, plus most other housekeeping jobs, are carried out automatically by the associated software.

It will be necessary to disconnect the link to the i.e.d. cathodes whilst programming is taking place though, and the temporary connection of a switch for this is shown in Fig.2.

Most constructors will probably start by obtaining an unprogrammed PIC and a copy of the software source code, most of which should be fairly simple to follow.

As this is an ideal project to hone initial programming skills, some notes on the methods used may be helpful. The original was written as TASM assembly source code but it shouldn't be too difficult for MPASM users to follow and modify as desired (*Toolkit Mk2* can translate between TASM and MPASM).

ROUTINE EVENTS

The program uses three basic types of routine. One consists of loading a pattern onto the output, implementing a delay, then loading another pattern. Or, perhaps, just turning all the i.e.d.s off and doing another delay, at a set speed for a set number of times, using a loop. This is the simple flashing routine, and there are eight of these in the original program.

Another routine consists of loading a pattern and then causing it to rotate clockwise or anti-clockwise with a simple procedure to rotate the bits in the output files which can be used in a repeating loop. There are three of these patterns, in both clockwise and anti-clockwise versions, a total of six in all.

Finally, there are the more complicated patterns, where bits are turned on and off individually, which give the most pleasing results of all but produce a lot more code. There are four of these.

All these routines are written as self-contained subroutines so that a "program" can be built up simply using a string of "calls". Timing is carried out by a simple loop called "dly" placed right at the end of the program. This uses a variable called "rate" which is loaded before "dly" is called. Another variable called appropriately "reps" controls the number of times each pattern will repeat.

The effect generated by the flashing i.e.d. patterns is highly subjective so there really is no real alternative to testing each

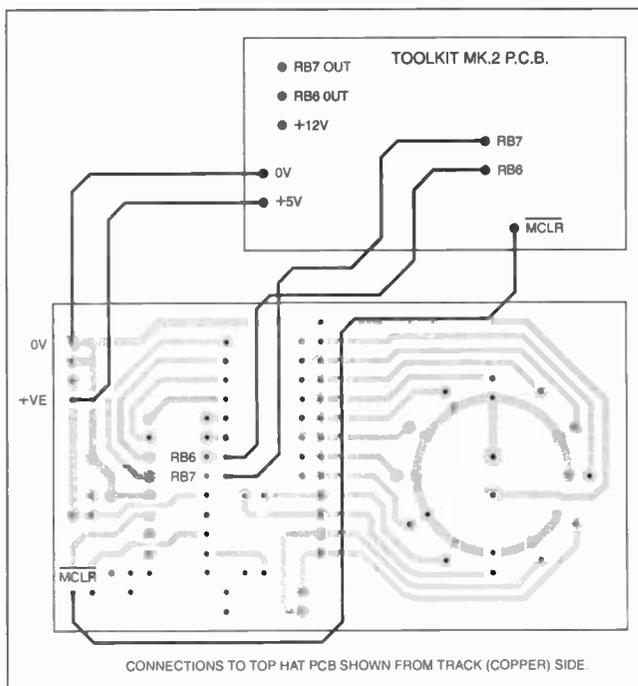


Fig.3. In-circuit programming set-up using the Toolkit Mk2 programmer.

one as it is written to see what it looks like, and then adjusting the timing and repeats to get the preferred effect.

A glance at the full source code will show that the routines, when assembled into a full program, take up a lot of space. This creates problems simply of scrolling through them all in the edit screen during the trial-and-error creation process, and for those of us who do this sort of work with

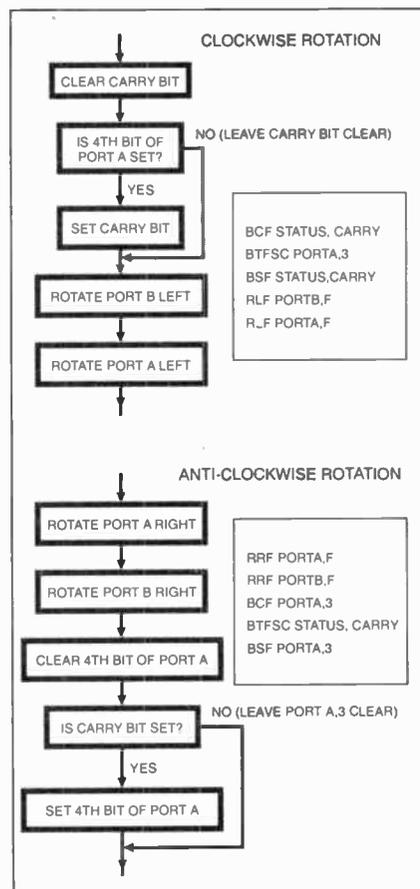


Fig.4. Flow diagram for rotating a "file-and-a-half" left and right.

ancient computers that have been relegated to the workshop, whilst keeping the gigahertz Pentium mega-machine elsewhere for web surfing, it can lead to slow processing and programming.

John Becker has recently released a new version of *Toolkit Mk2* software (discussed in *EPE* Nov '00) which provides the incredibly useful "include" directive to overcome this difficulty.

Let's say a piece of code, perhaps a complete flash routine, has been tested and is working perfectly. It can be saved on its own under a filename, perhaps "flash_1.asm", and replaced in the main program with the statement ".include flash_1.asm" (or "\$include flash_1.asm"). At assembly time, the assembler will simply add the code into the main program and convert it into object code as if it were there in full.

The advantages of this are twofold. First, there will be far less to scroll through when entering the text editor and navigating to the section currently under development. Secondly, an

"include" can be excluded from the assembly process with a single ";" (semicolon) placed before it, making it much easier to turn whole chunks of program on and off and, in the case of older computers, speeding assembly and programming times.

MPASM will have similar commands and directives, and programmers not familiar with them should investigate as they are incredibly helpful. Their inclusion (sorry!) in the latest *Toolkit* software is most welcome.

Rotating bits around a file and a half, Port B and the first four bits of Port A, may appear difficult to beginners in programming. In fact, the procedure is quite simple and involves only a few lines of code. The trick is to read and set the status carry bit at the appropriate points so that the desired value is read in on the next rotation command. Flow diagrams and some code for this are shown in Fig.4.

Hopefully these notes will encourage would-be programmers to dip their toes in the water, as this is an ideal project to experiment with. It helps to have a picture of the i.e.d. layout labelled with their port and bit assignments whilst designing the

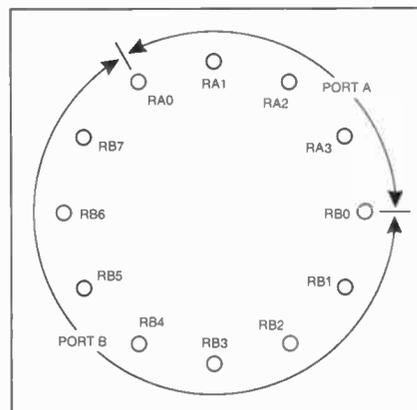


Fig.5. Circuit board i.e.d. layout, with their port and bit assignments.

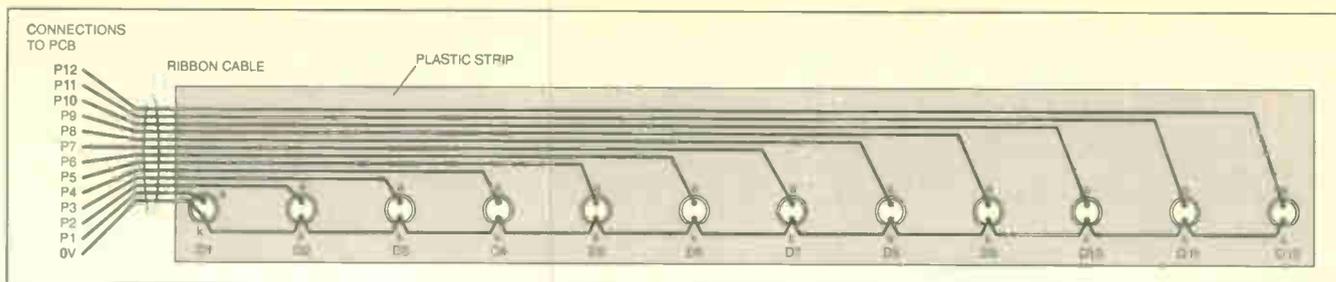


Fig.6. Interwiring between the I.e.d.s in the hat or head band.

more complex patterns, so this is shown in Fig.5.

The number of patterns and sequences that can be developed is practically endless; perhaps we should hold a competition for the most spectacular one produced! (Well, perhaps not. But the code might be worthy of a mention in Readout!. Ed.)

Incidentally, John Becker's PICtutor is probably still the best introduction around for the complete newcomer to the PIC and would easily enable anyone to learn how to program this project.

ON DISPLAY

The original top hat display was constructed using plastic shelf-edging strip obtained from a DIY store. A piece of this was cut just long enough to go around the hat and be secured in place with elastic. This strip was drilled with a line of holes which were a tight fit for the I.e.d.s, which were pressed in and connected to the board with ribbon cable as shown in Fig.6.

The board was taped into some bubble-wrap packaging with the battery connector hanging out of one side, and this was pressed onto the connector of a holder containing four AAA cells; there was no on-off switch. The battery and board sat in the rim of the hat and, like the I.e.d. band, were kept in place with elastic. This was, after all, a serious rush job!

Readers possessing their own top hat could install the board and I.e.d.s directly into the hat with some kind of secret switch, where it would be almost invisible until switched on, for a far better effect. Those attending a lot of weddings might like to consider this option! (But do be



The two ends of the I.e.d. carrying plastic strip are secured with elastic to form a headband, hatband, belt etc: Take your PIC!

aware that these days proper top hats are quite valuable.)


Other possibilities for this project are limited only by the constructor's imagination, though as a suggestion for a very simple method the board could be installed in a small case of some kind using its built in I.e.d. display to make a very unusual brooch, badge, or decoration. The I.e.d.s don't have to be all red, by the way, any other colour could be used instead.

If you are programming your own PIC, note that it needs to be initialised for RC

oscillator, Watchdog off, Start-up Timer on (Power on Reset).

Finally, for readers with the question on their lips, the answer is *No*. this project was not actually worn when walking up the aisle in the church!

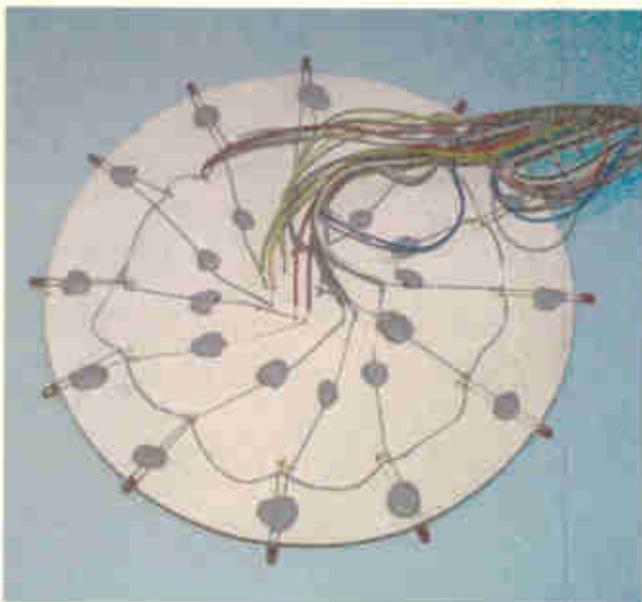The author has been asked this, several times, so the answer has to be provided! It was used late in the evening when the disco was in full swing, the lights were low, and most of the guests were sufficiently well lubricated to appreciate the novelty. □



Off-board I.e.d.s arranged around a cardboard disc.



Programming switch soldered to the "link" pins on the p.c.b.


Special Series

THE SCHMITT TRIGGER

ANTHONY H. SMITH

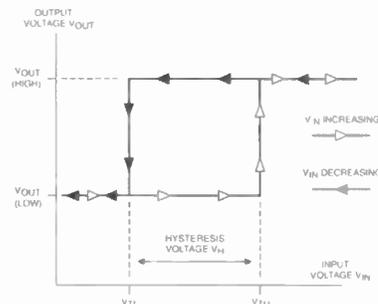Part 2

In this short series, we investigate the Schmitt trigger's operation; explore the various ways of implementing its special characteristics and also look at how we can use it to create oscillators and pulse width modulators.



Op.amp and Comparator Triggers

In the first part of this series, we looked at discrete Schmitt triggers based on bipolar transistors. Although effective and flexible, we saw how they could be somewhat difficult to design, especially where the interconnection of several transistors demanded careful attention to biasing levels and resistance values.

In this article, we look at Schmitt triggers based on operational amplifiers (op.amps) and comparators, devices which free us from most of the effort required in designing discrete, transistor-based circuits. By considering the op.amp or comparator as a "black box" having just input and output terminals and power supply pins, we can ignore its inner workings to a large degree, and instead concentrate on using it as a highly versatile circuit building block.

However, designing with op.amps and comparators is not a trivial undertaking: they bring their own set of requirements, terminology, and design rules, and if not applied correctly they will either malfunction or suffer permanent damage. The practice of designing with op.amps and comparators is a vast subject that is way beyond the scope of this article. Nevertheless, we'll deal with the main points and examine several practical circuits that illustrate different aspects of Schmitt triggers based on them.

INVERTING SCHMITT TRIGGER

In Fig.2.1a (next page) is shown a simple, inverting Schmitt trigger requiring only two resistors (R_1 and R_2), an op.amp (IC1), and an optional voltage reference (V_{REF}). In some cases, a small "speed-up" capacitor, C_S , may be connected across R_2 to improve the transient response. Before examining the operation of the circuit, we'll deal with some basic op.amp behaviour

The op.amp's input terminals are denoted "+" for the *non-inverting* input, and "-" for the *inverting* input. The term *non-inverting* implies that a voltage applied to that terminal will cause the output voltage to "move" in the same direction, i.e., with the same polarity.

For example, applying a small negative voltage to the non-inverting input will result in a much larger negative voltage at the output. The opposite is true of the inverting input, where a small negative voltage would be "inverted" at the output and result in a much larger positive voltage.

The op.amp is a *differential* amplifier, meaning that it amplifies the voltage *difference* between the input terminals. Ideally, an op.amp would have infinite open-loop differential gain. In practice, this can never be achieved, but most op.amps do have very high differential gain, usually in the order of 100,000 or more. The venerable 741, for example, has a typical open-loop gain of around 200,000, meaning that a differential voltage of just $10\mu\text{V}$ will swing the output by 2V.

If the input terminals of an ideal op.amp were shorted together to make the differential input voltage zero, the output voltage would also be zero. In practice, however, all op.amps feature a small "input offset voltage" (usually denoted V_{IO} , or sometimes V_{OS}) which results in a non-zero output voltage when the inputs are shorted together.

For example, an input offset voltage of +2mV would require applying an actual differential voltage of -2mV in order to

"neutralise" the offset and make the output voltage zero. General-purpose op.amps like the 741, LM358 and MC33171 have V_{IO} in the millivolt range, whereas precision devices such as the OP177 have offsets that are a thousand times smaller, typically just $10\mu\text{V}$.

For the circuits we'll be examining in this article, we can assume V_{IO} is negligible, although for precision Schmitt triggers it must be taken into account.

One thing we cannot ignore, however, is the effect of input bias currents. Ideally, an op.amp's input terminals would have an infinitely large impedance, such that they would draw no current from an input voltage source. In practice, all op.amps exhibit an "input bias current" which, as the name suggests, is the current necessary to bias the input transistors.

Usually denoted I_B , the input bias current may flow into or out of the input, depending on the op.amp type, and tends to be larger for devices fabricated using a bipolar process.

For example, the inputs of bipolar op.amps like the LM358 and MC33078 draw bias currents of a few tens or hundreds of nano-amperes. Devices fabricated using JFET or MOSFET technology, on the other hand, exhibit much smaller bias currents. The TLC271, for example, has a MOSFET input stage with typical input bias currents of just 0.7 picoampere at room temperature. More about input bias currents later.

POWER SUPPLIES

The diagram in Fig.2.1a shows the op.amp connected to positive and negative power rails, $+V_S$ and $-V_S$, respectively. Typically, dual supplies like this may range from $\pm 5\text{V}$ to $\pm 15\text{V}$, depending on the application, although some op.amps and comparators can operate on rails as low as $\pm 1\text{V}$.

For dual rail (sometimes called "split supply") circuits, it's important to remember that there is a third power supply connection, namely 0V (or "ground"). Although the op.amp is not usually connected directly to 0V, the power supply, the input voltage source(s) and the output load usually are connected to 0V in some way, and the input and output voltages are almost always measured with respect to 0V.

A slight variation on this arrangement is found in "single rail" applications, where the negative rail is omitted and the op.amp's negative supply terminal is connected to 0V. Single rail circuits are increasingly used in applications where an analogue signal of some kind must interface with digital logic operating on a single rail, typically +5V or +3.3V. The Schmitt trigger provides an extremely powerful way of interfacing analogue and digital circuits, and we shall look at single rail Schmitt triggers later.

COMMON MODE

We've mentioned that the op.amp amplifies *differential* signals: ideally, any *common-mode* voltage will be totally rejected and will have no effect on the output. A common-mode voltage is one which appears in common to both inputs.

Suppose, for example, we shorted both inputs together and connected them to +2.5V (with respect to 0V), the common-mode

voltage would be +2.5V. If we then connected one input to -1V and the other to -2V, the differential voltage would be 1V, and the common-mode voltage would be the mean voltage between the inputs, in this case -1.5V.

In practical circuits, op.amps do not provide total rejection of the common-mode voltage, although the *common-mode rejection* (the degree to which the common-mode signal is rejected) is usually so good that common-mode effects can be ignored.

Still on the subject of common-mode signals, the "common-mode input voltage range" defines the range of common-mode voltages that can be tolerated by a given op.amp. This is not usually the same as the "differential voltage range" which defines the range of voltage that can appear between the inputs without causing malfunction or damage.

Both of these parameters depend on the supply voltage. The LM741, for example, has a maximum differential input voltage rating of $\pm 30V$. Exceeding this limit could cause permanent damage. When operating on $\pm 15V$ supply rails, the common-mode input voltage range is typically $\pm 13V$, which means that the voltage at each input must not go within 2V of either supply rail or the op.amp might not function properly.

The LM358, however, is specifically intended for single rail applications. For example, when operating on a single +5V rail, the common-mode input voltage may go as high as +3.5V and may go all the way down to 0V. Modern op.amps and comparators frequently offer "rail-to-rail" performance. This means that the input voltage range, or output voltage range, or sometimes both, may cover the entire range from one supply rail to the other.

The LMC6482, for example, is a "Rail-to-Rail Input and Output" op.amp. When operated on, say, $\pm 5V$ rails, the input voltage may be permitted to take any value between -5V and +5V, and the output voltage will typically swing to within 20mV of each rail (i.e., $\pm 4.98V$) for load resistances greater than 100k Ω .

When used in "linear" applications (i.e., applications in which negative feedback is applied to keep the op.amp within its linear range), the op.amp's input voltage ratings are often not excessively taxed. However, when used in Schmitt trigger circuits, the positive feedback frequently forces the inputs to cover a wide range, resulting in large common-mode and differential voltages.

Consequently, it's essential to check the worst-case, maximum input voltage range for a given application to ensure the op.amp or comparator will function correctly.

POSITIVE FEEDBACK

Having discussed basic op.amp theory, we can now return to Fig.2.1a and examine the operation of the inverting Schmitt trigger.

To simplify the analysis, assume the reference voltage V_{REF} is zero (i.e., R1 connected to 0V) and that V_{IN} is at some negative voltage, such that the voltage at the op.amp's inverting input is lower (more negative) than that at the non-inverting input, denoted $V+$. If the resulting positive differential input voltage is greater than a few millivolts, the op.amp's output will be in positive saturation, V_{SAT+} , i.e., the output will be at its maximum positive level.

The non-inverting input voltage, $V+$, will sit at a value determined by the ratio of R1 and R2, and by the value of V_{SAT+} . If V_{IN} now rises above the level of $V+$, the differential input voltage becomes negative forcing V_{OUT} also to go negative. This causes $V+$ to go negative, which increases the negative differential voltage, and ultimately forces V_{OUT} into negative saturation, V_{SAT-} .

As with the discrete Schmitt triggers described in Part One, the positive feedback via R2 causes *regenerative* behaviour which reinforces the switching action, causing a rapid transition from one output state to the other.

The value of V_{IN} required to "trigger" this change of state is denoted the "upper threshold voltage", V_{TU} , and is given by:

$$\text{Upper Threshold Voltage, } V_{TU} = \frac{R1 \times V_{SAT+}}{R1 + R2} \quad (\text{volts})$$

Since V_{OUT} has gone into negative saturation, $V+$ now sits at a negative voltage. If V_{IN} , and hence the inverting input terminal, is now taken more negative than $V+$, the differential voltage will again become positive and regenerative action will force V_{OUT} into positive saturation, V_{SAT+} . The value of V_{IN} required to initiate this opposite change of state is denoted the "lower threshold voltage", V_{TL} , and is given by:

$$\text{Lower Threshold Voltage, } V_{TL} = \frac{R1 \times V_{SAT-}}{R1 + R2} \quad (\text{volts})$$

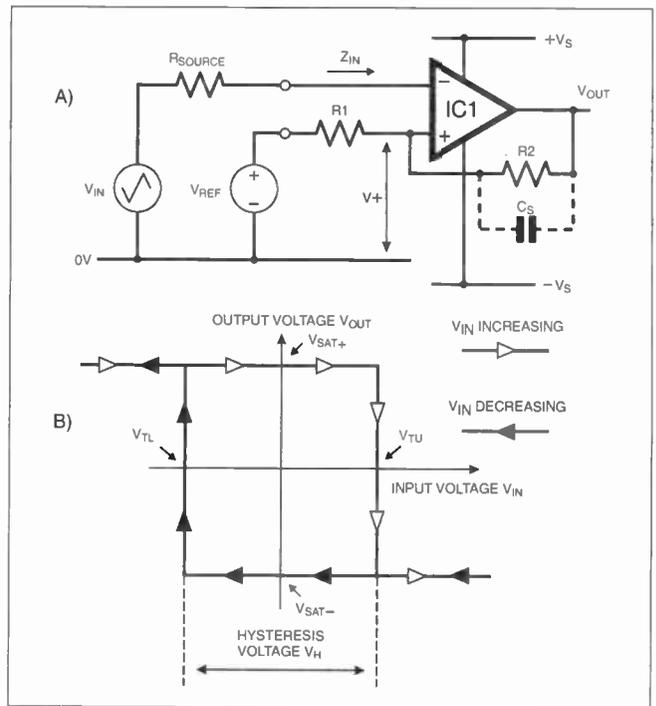


Fig.2.1. Circuit diagram for an Inverting Schmitt Trigger (a) and its voltage transfer characteristic (b).

Note that when V_{IN} goes positive and crosses the upper threshold, the output goes negative, hence the term *inverting* Schmitt trigger. We can see at a glance that the circuit is inverting because V_{IN} is applied to the op.amp's inverting input terminal.

The diagram in Fig.2.1b shows the circuit's "voltage transfer characteristic", i.e., the relationship between input and output voltage. Starting at the top left-hand corner and following the white arrows as the input voltage increases, we see that the output remains at V_{SAT+} until V_{IN} crosses the upper threshold, V_{TU} , at which point the output rapidly changes state and goes into negative saturation, V_{SAT-} .

Rapidly increases in V_{IN} have no effect on V_{OUT} . As V_{IN} decreases (shown by the black arrows), V_{OUT} remains at V_{SAT-} until V_{IN} crosses the lower threshold, V_{TL} , where V_{OUT} abruptly changes state and goes back into positive saturation.

The transfer characteristic shown assumes that V_{SAT+} is equal and opposite to V_{SAT-} and that V_{TU} is equal and opposite to V_{TL} , resulting in a "hysteresis loop" that is symmetrical about the origin. However, this is not always the case: depending on the application, it may be necessary to make the magnitude of the thresholds unequal, or to make them both positive or both negative. Also, as we shall see shortly, V_{SAT+} is not always equal and opposite to V_{SAT-} .

The thresholds can be varied by appropriate choice of R1 and R2, and by introducing a non-zero reference voltage (so far, we have assumed that $V_{REF} = 0$).

Referring again to Fig.2.1a, assume we apply a positive value of V_{REF} : whatever the value of V_{OUT} , this will result in $V+$ becoming more positive. The effect of making V_{REF} positive is to shift the thresholds "upward", i.e., more positive. Similarly, making V_{REF} negative would shift the thresholds negative. To incorporate the effect of V_{REF} , the threshold equations become:

$$\text{Upper Threshold Voltage, } V_{TU} = \frac{(V_{REF} \times R2) + (R1 \times V_{SAT+})}{R1 + R2} \quad (\text{volts})$$

and:

$$\text{Lower Threshold Voltage, } V_{TL} = \frac{(V_{REF} \times R2) + (R1 \times V_{SAT-})}{R1 + R2} \quad (\text{volts})$$

The "hysteresis" voltage is the difference between the thresholds:

$$\text{Hysteresis voltage, } V_H = V_{TU} - V_{TL} = \frac{R1 \times (V_{SAT+} - V_{SAT-})}{R1 + R2} \quad (\text{volts})$$

Note that V_H is completely independent of V_{REF} : this is an important aspect of the circuit, since it allows the thresholds to be shifted by varying V_{REF} without affecting the hysteresis voltage.

The circuit's response to a triangle wave input voltage is shown in Fig.2.2a. V_{REF} has been set to a sufficiently large positive voltage, such that both thresholds are also positive; in Fig.2.2b, a negative value of V_{REF} has shifted both thresholds negative.

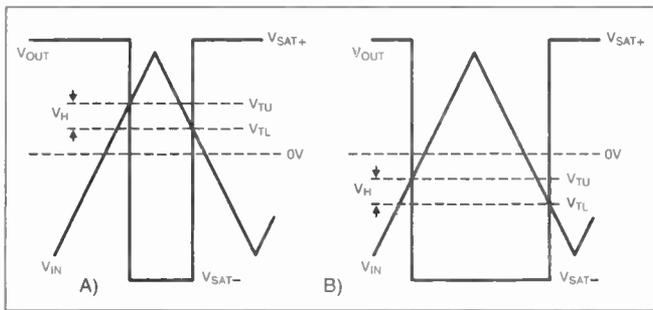


Fig.2.2. Response to a triangle wave input for positive (a) and negative (b) V_{REF} .

Varying V_{REF} allows the thresholds to be shifted over a wide range of positive and negative values. This can be a particularly useful feature: having chosen R1 and R2 to set the desired hysteresis voltage, V_{REF} may then be selected to set the mid point of the hysteresis band equal to the quiescent value of the input signal, such that the circuit can accommodate small-amplitude input signals whilst providing maximum noise immunity.

INPUT IMPEDANCE

Our analysis of the circuit has ignored the effects of input offset voltage, V_{IO} ; this is a reasonable approach provided the circuit does not demand absolute precision. However, the op.amp's input impedance cannot always be neglected.

Generally, the impedance Z_{IN} seen "looking into" the inverting input can be represented by the same kind of model introduced in Part One, namely a parallel combination of resistance, capacitance, and a current sink (or source) to represent the input bias current.

At low frequencies we can usually ignore the effects of input capacitance, and if we assume the input resistance is large (several megohms) we can concentrate on the effects of input bias current.

For example, consider the LM6171, a high speed op.amp capable of operation at frequencies in excess of 10MHz. The input bias current, I_B , is typically $1\mu A$, but can be as high as $3\mu A$. If the input voltage source resistance, R_{SOURCE} , is very small, I_B will have negligible effect.

However, for a source resistance of, say, $100k\Omega$, a bias current of $2\mu A$ would drop $0.2V$ across R_{SOURCE} , resulting in significant errors in the threshold levels.

Even if R_{SOURCE} is zero, we must still consider the effects of I_B at the non-inverting input: if R1 and R2 are relatively large, the input bias current will cause a voltage drop across them which again will offset the threshold levels. To avoid these problems, either use small values for R1 and R2, or select an op.amp (or comparator) that has very small input bias currents.

TESTING THE CIRCUIT'S PERFORMANCE

To demonstrate the circuit's performance, it was decided to use an LF351 op.amp. As well as offering fast response, the LF351 has a JFET input stage with typical input bias currents of just 50 picoamperes, allowing it to accommodate large resistance values without affecting the thresholds.

With $R1 = 10k\Omega \pm 1\%$, $R2 = 100k\Omega \pm 1\%$, and with the supply rails set to precisely $\pm 15.00V$, the circuit's response to a 100Hz triangle wave input voltage was measured. It was found that the op.amp's output saturation levels were $V_{SAT+} = +14.25V$ and $V_{SAT-} = -13.55V$.

Therefore, with $V_{REF} = 0$, the thresholds should be $V_{TU} = +1.30V$ and $V_{TL} = -1.23V$. The actual, measured values were $V_{TU} = +1.31V$ and $V_{TL} = -1.21V$. Pretty good!

Next, a reference voltage was introduced. With $V_{REF} = +5.00V$, the thresholds were $V_{TU} = +5.88V$ and $V_{TL} = +3.36V$, very close to their theoretical values of $V_{TU} = +5.84V$ and $V_{TL} = +3.31V$.

Finally, with $V_{REF} = -5.00V$, the thresholds were $V_{TU} = -3.26V$ and $V_{TL} = -5.80V$, again in close agreement with their theoretical values of $V_{TU} = -3.25V$ and $V_{TL} = -5.78V$.

Note that for each value of V_{REF} , the hysteresis voltage, V_H , remains fairly constant at $\approx 2.5V$.

ZENER CLAMP OUTPUT SCHEME

We see from the previous example that the output saturation levels are not equal in magnitude, i.e., $|V_{SAT+}| \neq |V_{SAT-}|$, which results in an asymmetry in the thresholds. Furthermore, the output saturation levels may change from part to part, and may also vary with temperature and load.

Since V_{TU} and V_{TL} depend directly on V_{SAT+} and V_{SAT-} , this can make it difficult to establish the thresholds precisely and repeatedly. To some extent, this problem can be resolved by using an op.amp (or comparator) with rail-to-rail output swing, but even then the saturation levels would be affected by any variation in the supply voltages.

In Fig.2.3 are shown two methods which can be used to establish greater control over the output voltage levels. In Fig.2.3a, a back-to-back Zener "clamp" has been added to the output and feedback is now taken from the clamp via R2, rather than from the op.amp's output.

The Zener clamp is "bi-directional": as the op.amp output swings between its positive and negative saturation levels, the output voltage, V_{OUT} , at the junction of R3 and ZD1 also swings positive and negative. We can define these levels V_{Z+} and V_{Z-} , such that $V_{Z+} = V_{Z1} + V_{D2}$ and $V_{Z-} = V_{Z2} + V_{D1}$, where V_{Z1} and V_{Z2} are the reverse Zener voltages, and V_{D1} and V_{D2} are the Zeners' forward diode drops.

If the Zeners are well matched, i.e., if $V_{Z1} = V_{Z2}$ and $V_{D1} = V_{D2}$, the magnitude of V_{Z+} and V_{Z-} will be equal.

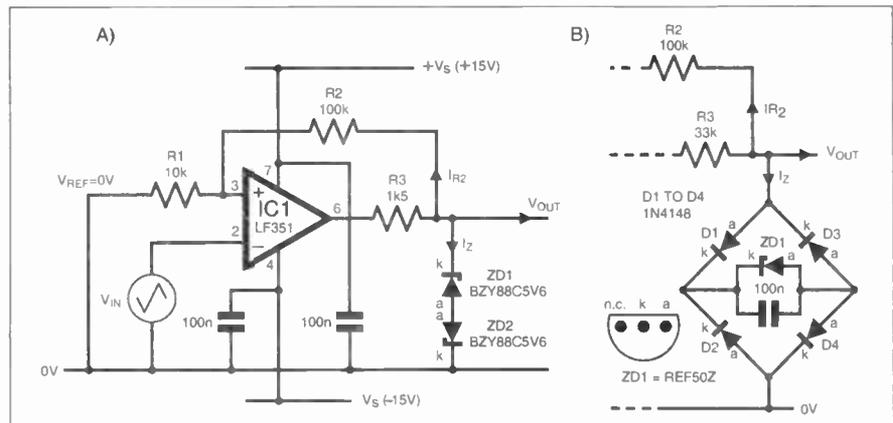


Fig.2.3. Two methods which can be used to give greater control over output voltage levels, (a) using a back-to-back Zener clamp and (b) using a diode bridge.

For example, using 5.6V Zeners as shown in Fig.2.3a, it was found that the voltage at V_{OUT} was perfectly symmetrical at $\pm 6.0V$, and with $R1 = 10k\Omega \pm 1\%$ and $R2 = 100k\Omega \pm 1\%$ as before, and with $V_{REF} = 0$, the thresholds were also symmetrical at $\pm 0.63V$.

Note that R3 must be small enough to provide adequate current, I_Z , to bias the Zeners properly, and must also provide the feedback current, I_{R2} , that flows in R2. Provided R3 is chosen carefully, this technique will provide a relatively constant, symmetrical bipolar voltage swing at V_{OUT} .

A STABLE BRIDGE

The output clamp method can be improved still further using the scheme shown in Fig.2.3b. Here, the D1-D4 diode bridge maintains a positive potential at the cathode of regulator diode ZD1 for both positive and negative swings at V_{OUT} . If we assume the forward voltage drops across each of the bridge diodes are equal and denoted V_D , the output voltage swing is $V_{OUT} = \pm(2V_D + V_Z)$, where V_Z is ZD1's reverse voltage.

Although ZD1 could be a Zener, even better performance can be obtained using a precision shunt voltage reference diode. Here a choice was made to use the REF50Z, a micropower 5.0V reference diode, although other devices such as the REF12Z (1.26V) and REF25Z (2.5V) could be used to provide different clamping voltages.

Note that R3 has been increased from $1.5k\Omega$ to $33k\Omega$, since the REF50Z requires much less bias current than the back-to-back Zeners.

This "reference-in-a-bridge" approach generated an output voltage swing of $\pm 6.02V$, and with $R1 = 10k\Omega \pm 1\%$, $R2 = 100k\Omega \pm 1\%$ and $V_{REF} = 0$ as before, the thresholds were $V_{TU} = \pm 0.575V$ and $V_{TL} = -0.570V$.

USING COMPARATORS AND SINGLE RAILS

The examples so far have focused on a circuit using an op.amp working on dual supply rails. However, in many applications, it may be better to take advantage of the superior switching qualities offered by a comparator (see panel "Comparator Essentials"). We must also consider the biasing requirements of single rail applications and the use of "open-collector" (or "open-drain") outputs.

In Fig.2.4a is shown an inverting Schmitt trigger using one half of the popular LM393 comparator. Although the LM393 can work on dual supplies from $\pm 1\text{V}$ to $\pm 18\text{V}$, it is particularly suited to single rail operation since the common-mode input range goes all the way down to the negative rail (0V for single rail applications).

The reference voltage is generated by the potential divider comprising resistors R1a, R1b and the positive supply:

$$V_{\text{REF}} = \frac{+V_s \times R1b}{R1a + R1b} \quad (\text{volts})$$

For dual rail applications, a negative reference may be generated by connecting R1a to $-V_s$.

Since the LM393 has an open-collector output, pull-up resistor R_{PU} is required to pull the output voltage up toward $+V_s$ when the output transistor turns off. However, R_{PU} must be included in the expression for V_{TU} since it effectively appears in series with R2.

The thresholds are given by:

Upper Threshold Voltage,

$$V_{\text{TU}} = \frac{V_{\text{REF}} \times (R2 + R_{\text{PU}}) + R_{\text{TH}} \times (+V_s)}{R_{\text{TH}} + R2 + R_{\text{PU}}} \quad (\text{volts})$$

and: Lower Threshold Voltage,

$$V_{\text{TL}} = \frac{(V_{\text{REF}} \times R2) + (R_{\text{TH}} \times V_{\text{SAT-}})}{R_{\text{TH}} + R2} \quad (\text{volts})$$

R_{TH} is the Thévenin equivalent resistance of the R1a-R1b potential divider:

$$R_{\text{TH}} = \frac{R1a \times R1b}{R1a + R1b} \quad (\text{ohms})$$

Note that the expression for V_{TU} is only true for a lightly loaded output (for example, driving a CMOS logic gate). For heavier loads which prevent R_{PU} pulling the output all the way up to $+V_s$, the expression must be modified by removing R_{PU} and replacing $+V_s$ with $V_{\text{SAT+}}$, the maximum positive output voltage, which must be determined for the particular application.

CUT THE CHATTER

A problem sometimes encountered when comparators are misapplied is "chatter" at the output. With slowly varying input signals, comparators tend to produce multiple output transitions when the input signal crosses the reference potential.

As the input traverses the linear region, the comparator behaves as a very high gain, open-loop amplifier. The slightest noise on the input is amplified by the enormous gain of the comparator causing "chatter" at the output.

For example, the LM393 has a typical open-loop voltage gain of 200V/mV (i.e., 200,000), so to cause a 5V output transition requires an input noise amplitude of only $5/200,000 = 25\mu\text{V}$.

Stray capacitances around the comparator can result in a.c. feedback from output to input causing oscillation around the threshold, another source of output chatter.

Fortunately, hysteresis may be used to eliminate these problems. Usually, applying just a little positive feedback, say a few millivolts, may be enough to prevent the chatter. Naturally, for signals with larger noise content, the hysteresis, and hence the positive feedback, must be increased.

Chatter can sometimes be difficult to spot on an oscilloscope, but causes unacceptable errors in counting circuits.

SINGLE RAIL TESTS

A single rail version of the circuit in Fig.2.4a was built by connecting the comparator's negative supply terminal (pin 4) to 0V. Resistance values were selected for $R1a = R1b = 36\text{k}\Omega \pm 1\%$ to give $R_{\text{TH}} = 18\text{k}\Omega \pm 1\%$. With $R2 = 100\text{k}\Omega \pm 1\%$, $R_{\text{PU}} = 10\text{k}\Omega \pm 1\%$, and $+V_s = +5.00\text{V}$, the "negative" saturation voltage, $V_{\text{SAT-}}$, was measured as +50mV. The thresholds were $V_{\text{TU}} = 2.82\text{V}$ and $V_{\text{TL}} = 2.10\text{V}$, in close agreement with the theoretical values, namely $V_{\text{TU}} = 2.85\text{V}$ and $V_{\text{TL}} = 2.13\text{V}$.

The value of $V_{\text{SAT-}}$ is so small that it can almost be ignored and eliminated from the expression for V_{TL} which reduces to:

$$V_{\text{TL}} = (V_{\text{REF}} \times R2) / (R_{\text{TH}} + R2)$$

Bear in mind, however, that $V_{\text{SAT-}}$ will tend to increase as R_{PU} is reduced. For example, if R_{PU} is reduced to, say, $1\text{k}\Omega$, the LM393's output transistor will sink around 4mA when it turns on, and the corresponding saturation voltage may be as large as 400mV.

HIGH FREQUENCY RESPONSE

So far, we've looked at circuit response using low frequency signals, on the order of 100Hz. However, at high frequencies, where the input signal has a very fast rate of change, the comparator's response time causes an apparent shift in the thresholds.

The waveforms in Fig.2.5 illustrate those obtained from the single rail LM393 circuit when a 250kHz triangle wave input was applied. Initially, the non-inverting input, V_+ , sits at a potential equal to V_{TU} , but when V_{IN} crosses this threshold the output does not change state immediately. Instead, there is a delay denoted $t_{\text{PD-}}$ (for "negative-going propagation delay") before the output leaves its positive saturation level and starts to head negative.

However, it cannot change from positive to negative saturation instantaneously, but takes a finite time to "slew" from $V_{\text{SAT+}}$ to $V_{\text{SAT-}}$. The combined effects of propagation delay and slew rate constitute the response time, and result in the *apparent* value of V_{TU} being significantly higher than the real value of V_{TU} .

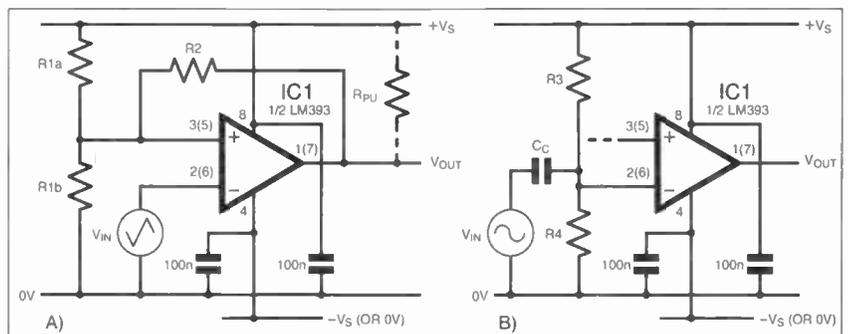


Fig.2.4. A single rail Schmitt trigger circuit using an "open-collector" comparator.

A similar effect occurs when the input signal crosses the lower value of V_+ , i.e., V_{TL} . Again, there is a delay denoted $t_{\text{PD+}}$ (for "positive-going propagation delay") before the output leaves its negative saturation level and starts to move positive. However, this time, the slew-rate effects are more pronounced since the open-collector output depends on the pull-up resistor to swing the output positive.

Since the resistor must charge the comparator's output capacitance plus any stray and load capacitance, the output waveform now acquires an exponential shape. By the time the output waveform crosses the input signal, the *apparent* value of V_{TL} is considerably lower than the real level of V_{TL} .

At low frequencies, where the input signal changes at a relatively slow rate, the effects of comparator response time are usually negligible. However, you should be aware of these effects at high frequencies since they limit the Schmitt trigger's ability to respond to rapidly changing signals.

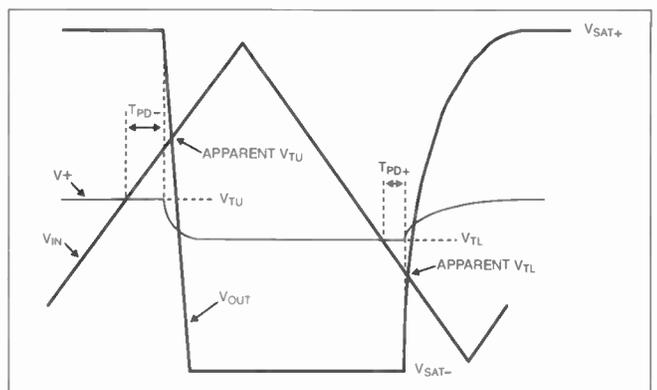


Fig.2.5. Effects of comparator response time on apparent thresholds.

Comparator Essentials

Although op.amps can be used to compare one voltage level with another, the *voltage comparator* is often the better choice. Like the op.amp, the comparator is essentially a high-gain differential amplifier, in that a very small differential input voltage will drive the output into positive or negative saturation.

However, by enhancing certain characteristics such as gain and slew rate, the comparator is optimised for non-linear applications in which the main function is to compare rather than to amplify voltages.

An important comparator a.c. parameter is *response time*, the time delay between an input step voltage and the resulting large-scale change in output voltage. Response time includes the propagation delay through the i.c. and the effects of output slew rate, and varies considerably from one type of comparator to another. For example, the typical response time for the National Semiconductor LM393 is 1.3µs, whereas for the LM360 it is just 14ns.

Comparators are expected to be operated with non-zero differential voltages; this is not necessarily so with op.amps which are mainly intended to be operated "closed-loop" where the differential voltage is close to zero. For example, the TLC372 dual comparator has a differential input range equal to the supply voltage (which can be as high as 18V), whereas the OP97 precision op.amp has input protection diodes which limit the differential input voltage to just ±1V. Always read the data sheet thoroughly to check that a given device is being used properly.

OUTPUT STAGE

Although comparators occasionally feature "push-pull" output stages like op.amps, they often have "open-collector" (or "open-drain") outputs. For example, the NE521 (a high speed, dual comparator) has a push-pull output stage, which means the output voltage is constrained to lie between ground (0V) and the positive supply.

The dual LM393, on the other hand, has an open-collector output (emitter connected to ground), which allows it to drive loads connected to rails higher than its own supply voltage.

The output stage of the LM311 is even more flexible, since both the collector and emitter of the output transistor are "floating", such that it can drive loads referred to ground, to the positive supply or to the negative supply. With the emitter grounded, the collector can drive loads connected to voltages as high as 40V and can sink currents up to 50mA.

Open-collector outputs can be very flexible when interfacing to logic devices, and are also suited to "wired-OR" operation, rather like open-collector TTL gates.

INPUT PARAMETERS

Input bias current, I_B , can vary considerably from one comparator type to another. For example, the LM393 has $I_B = 25nA$ (typical) at 25°C, whereas the TLC393 (dual, open drain) has $I_B = 5pA$ (typical) at 25°C – five thousand times less! Also, note that the TLC393 supply current is approximately one-twentieth that of the LM393, even though the devices are functionally equivalent.

For certain devices, bias current can vary with differential input voltage. The LM311, for example, has a typical input bias current of 100nA at 25°C for zero differential input voltage, but this can vary by ±75nA if the differential input is taken beyond ±8V. Note that 100nA will drop 10mV across a 100kΩ input resistance.

Always check the common-mode input range: this is not necessarily equal to the supply voltages, and is often significantly less. For example, when working on ±15V supplies, the LM311's input voltage range is -14.5V to +13.0V.

WIDE VARIETY

Like op.amps, comparators come in a many different "flavours". Speed (response time), input offset voltage and bias current are some of the parameters to be considered when choosing a suitable device, although supply current, output type and cost can often be equally important. Table 1 lists some of the most popular comparators and details some of the main parameters. Note that this is not an exhaustive list and there are many others to choose from!

If you would rather use an op.amp as a comparator, consider its speed (bandwidth and slew-rate), its ability to drive loads, and its output swing (especially if interfacing to logic circuits). Lastly, remember that comparators are not meant to be operated in linear mode, and so are not internally frequency compensated. Generally, therefore, comparators do not make good op.amps and should not be used as such!

Table 1: Popular Comparators and Their Main Characteristics

Part Number	Manufacturer	Single/Dual/Quad	t_R (typ.)	I_B max.	V_{IO} max. (mV)	I_S max.	Total Supply Voltage (V)		Single Rail Operation?	Output Type	Comments
							min	max			
CA3290	Harris	D	1.2µs	40pA	20	3mA	5	36	Yes	OC	BiMOS design
LM311	National Semiconductor	S	200ns	250nA	7.5	7.5mA	5	36	Yes	OC	popular; inexpensive; flexible output stage
LM319	National Semiconductor	D	80ns	1µA	8	12.5mA	5	36	Yes	OC	fast, but input current is high
LM339	National Semiconductor	Q	1.3µs	250nA	5	2.5mA	2	36	Yes	OC	popular; inexpensive; very low operating voltage
LM361	National Semiconductor	S	1.4ns	30µA	5	20mA	11	30	No	PP	very fast, but input and supply currents are high; differential output may be strobed
LM393	National Semiconductor	D	1.3µs	250nA	5	2.5mA	2	36	Yes	OC	popular; inexpensive; dual version of LM339
LMC6762	National Semiconductor	D	10µs	0.04pA (typ.)	15	20µA	2.7	15	Yes	PP	input and output voltage range is rail-to-rail; very low power; extremely low input current
LT1016	Linear Technology	S	10ns	10µA	3	35mA	5	10	Yes	PP	very fast, but power hungry; differential outputs may be latched.
LT1017	Linear Technology	D	20µs	15nA	1	90µA	1.2	40	Yes	PP	micropower; very low operating voltage
LT1018	Linear Technology	D	6µs	75nA	1	250µA	1.2	40	Yes	PP	low power; very low operating voltage
MAX931	Maxim	S	12µs	1nA	10	3.2µA	2.5	11	Yes	PP	micropower; includes 1.18V bandgap voltage reference; comparator has adjustable hysteresis
MAX941	Maxim	S	80ns	300nA	2	700µA	2.7	6	Yes	PP	fast; low power; rail-to-rail input voltage range
NE521	Philips Semiconductors	D	10ns	20µA	7.5	35mA	9	11	No	PP	very fast; outputs may be strobed
NE529	Philips Semiconductors	S	15ns	20µA	6	25mA	10	20	No	PP	very fast; differential outputs may be strobed
TLC372	Texas Instruments	D	650ns	5pA	5	300µA	2	18	Yes	OD	low power; very low supply voltage and input current
TLC393	Texas Instruments	D	2.5µs	5pA	5	40µA	3	16	Yes	OD	micropower; very low supply voltage and input current; compare with LM393
TLC3702	Texas Instruments	D	2.7µs	5pA	5	40µA	3	16	Yes	PP	push-pull output version of TLC393
TLC3704	Texas Instruments	Q	2.7µs	5pA	5	80µA	3	16	Yes	PP	quad version of TLC3702

NOTES: All specifications are given for an operating temperature of +25°C. t_R = Response Time (depends on input overdrive). I_B = Input Bias Current
 V_{IO} = Input Offset Voltage. I_S = Supply Current. Total Supply Voltage = difference between positive and negative supply rails.
 OC = Open Collector; OD = Open Drain; PP = Push-Pull.

A.C. COUPLING

We've seen how the Schmitt trigger's reference voltage can be set to match the mid-point of the hysteresis band to the quiescent, or average, voltage level of the input signal. However, for signals that lie outside the common-mode range of the comparator, a.c. coupling can be used to remove the d.c. level and thus bring the a.c. content of the signal within the comparator's input range.

The circuit diagram in Fig.2.4b shows how the single rail Schmitt trigger can be modified for a.c. coupling. Resistors R3 and R4 establish a suitable d.c. potential at the comparator's inverting input. Usually, it is best to make this potential equal to the mid-point of the comparator's common-mode input range.

For example, when operating on a single +5V rail, the LM393's common-mode input range is zero to 3.5V, so R3 and R4 would be selected to set the d.c. level at the inverting input to 1.75V. The a.c. signal is capacitively coupled via C_C to the inverting input, allowing the circuit to accept a.c. signals up to $\pm 1.75V$ in amplitude, or 3.5V peak-to-peak.

Resistors R1a and R1b would be chosen to set the mid point of the hysteresis band equal to 1.75V, and by selecting R2 and R_{PU} to set the hysteresis voltage just less than the minimum peak-to-peak amplitude of the input signal, the Schmitt trigger will provide maximum noise immunity.

A word of warning, though. When dealing with a.c. signals such as pulse trains whose duty cycle can vary enormously, capacitive coupling can cause problems: as the duty cycle changes, so, too, does the average d.c. level of the waveform, such that the waveform at the inverting input tends to shift up and down. If this shift is excessive, the signal fails to cross one of the thresholds, and the circuit doesn't trigger. Always check that the circuit will respond properly at the extremes of the input signal's duty cycle.

NON-INVERTING SCHMITT TRIGGER

By swapping over the input voltage and reference voltage connections of the inverting Schmitt trigger (Fig.2.1), we obtain the non-inverting Schmitt trigger shown in Fig.2.6a.

The voltage $V+$ at the non-inverting input now depends not only on V_{OUT} , R1 and R2, but also on V_{IN} . We can understand the circuit's operation by referring to the voltage transfer characteristic in Fig.2.6b, which shows the case for $V_{REF} = 0$ and assumes V_{SAT+} is equal and opposite to V_{SAT-} .

Starting at the bottom left-hand corner, where V_{IN} is at its most negative value, the output is in negative saturation and so $V+$ is also a negative voltage. As V_{IN} increases (shown by the white arrows) it eventually reaches a positive level where $V+$ just rises above 0V, causing the comparator output to change state. The value of V_{IN} where the output rapidly changes from V_{SAT-} to V_{SAT+} is the upper threshold voltage, V_{TU} .

If V_{IN} is now reduced (shown by the black arrows), the output remains in positive saturation until V_{IN} has gone sufficiently negative to make $V+$ go just below 0V. At this point, where $V_{IN} = V_{TL}$, the output abruptly changes from positive to negative saturation, V_{SAT-} .

Notice how the hysteresis loop moves in an "anti-clockwise" direction, whereas that of the inverting Schmitt trigger (Fig.2.1b) follows a clockwise path.

By introducing the reference voltage, V_{REF} , we can shift the thresholds up or down: when V_{REF} is positive, the thresholds are moved in a positive direction, and vice-versa. The expressions for the thresholds (assuming $R_{SOURCE} = 0$) are:

Upper Threshold Voltage,

$$V_{TU} = \frac{V_{REF} \times (R1 + R2) - (R1 \times V_{SAT-})}{R2} \quad (\text{volts})$$

and:

Lower Threshold Voltage,

$$V_{TL} = \frac{V_{REF} \times (R1 + R2) - (R1 \times V_{SAT+})}{R2} \quad (\text{volts})$$

The "hysteresis" voltage, the difference between the thresholds, is:

Hysteresis voltage,

$$V_H = V_{TU} - V_{TL} = \frac{R1 \times (V_{SAT+} - V_{SAT-})}{R2} \quad (\text{volts})$$

Again, like the inverting Schmitt trigger, we see that V_H is completely independent of V_{REF} .

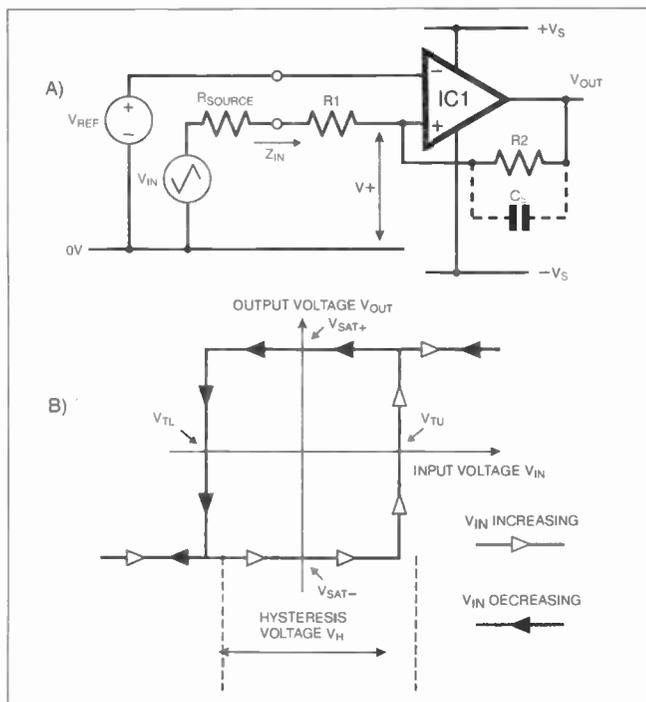


Fig.2.6. Circuit for a non-inverting Schmitt trigger (a) and its voltage transfer characteristic (b).

POSITIVE AND NEGATIVE RESISTANCE

We saw that the inverting Schmitt trigger's input impedance was dominated by the input bias current of the op.amp or comparator. For the non-inverting circuit, the impedance Z_{IN} seen by the voltage source depends largely on R1, R2 and V_{OUT} , and appears as either a positive or negative resistance.

For example, when V_{IN} is above V_{TU} , V_{OUT} is in positive saturation and current flows from IC1's output, through R2 and R1 and into V_{IN} . Thus, Z_{IN} appears as a *negative* resistance.

On the other hand, when V_{IN} is below V_{TL} , V_{OUT} is in negative saturation, and current flows from V_{IN} , through R1 and R2 and into IC1's output, such that Z_{IN} now behaves like a *positive* resistance.

If R_{SOURCE} , the output resistance of the voltage source, is very small or zero, the changing nature of Z_{IN} has negligible effect on circuit behaviour. However, if R_{SOURCE} is similar, or greater, in size to R1 and R2, the changing input current will cause a changing voltage drop across it, causing the apparent thresholds to shift relative to their nominal values.

In these circumstances, it is necessary to modify the threshold and hysteresis voltage equations by replacing R1 with $(R_{SOURCE} + R1)$, since R_{SOURCE} effectively appears in series with R1.

NON-INVERTING DESIGN PROCEDURE

The values for V_{SAT+} and V_{SAT-} can be obtained from the data sheet or determined from in-circuit measurements: the latter can often be more accurate, especially where saturation levels are heavily dependent on output loading.

For a desired hysteresis voltage, R1 and R2 can be selected by rearranging the expression for V_H :

$$R2 = R1 \times (V_{SAT+} - V_{SAT-}) / V_H$$

Then, knowing the desired value for V_{TU} , the appropriate reference voltage may be evaluated from:

Reference Voltage,

$$V_{REF} = \frac{V_{TU} \times (V_{SAT+} - V_{SAT-}) + (V_H \times V_{SAT-})}{V_H + V_{SAT+} - V_{SAT-}} \quad (\text{volts})$$

We'll follow a design example based on the LM6482, a dual, rail-to-rail input and output op.amp. Let's assume we require a hysteresis voltage of 1.0V and $V_{TU} = 1.5V$, and the circuit is to run on a single 5V supply.

With the output lightly loaded, it was found from in-circuit measurements that $V_{SAT+} = 5.00V$ and $V_{SAT-} = 20mV$. Using the above equations, we find that $R2 = 4.98 \times R1$, and $V_{REF} = 1.253V$.

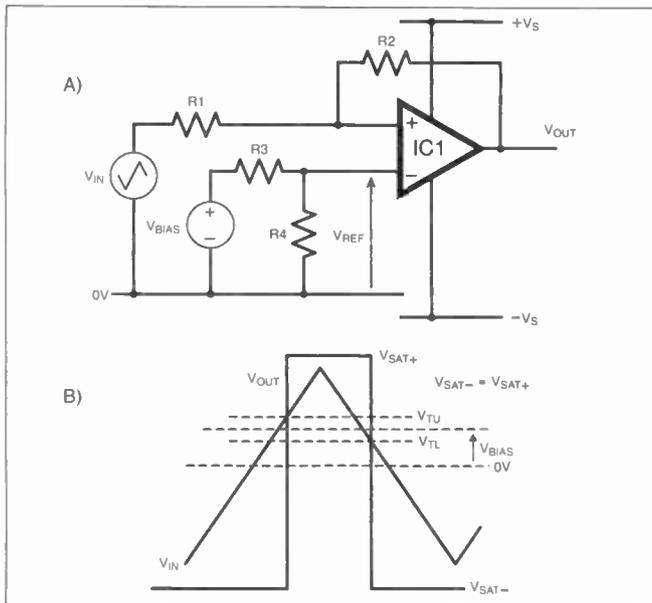


Fig.2.7. Using a bias voltage to control the mid-hysteresis level.

Using $R1 = 20k\Omega \pm 1\%$, $R2 = 100k\Omega \pm 1\%$, and with the supply voltage set to precisely 5.00V and V_{REF} set to 1.25V, measurements showed the upper threshold voltage as $V_{TU} = 1.53V$ and the hysteresis voltage as $V_H = 1.06V$.

Note that these results were obtained using a 200Hz triangular input waveform. It was found that performance was good up to around 2kHz: at higher frequencies, the op.amp's response time started to affect the thresholds in the manner described earlier.

For example, with V_{REF} increased to 2.5V, the nominal thresholds are $V_{TL} = 2.00V$ and $V_{TU} = 3.00V$. At 2kHz, the measured values were $V_{TL} = 1.87V$ and $V_{TU} = 3.09V$, whereas at 20kHz the apparent thresholds were $V_{TL} = 1.50V$ and $V_{TU} = 3.45V$. Clearly, if accurate performance were to be required at frequencies above 2kHz, it would be necessary to use a faster op.amp.

MID-HYSTERESIS LEVEL

We saw earlier that the hysteresis voltage $V_H = R1 \times (V_{SAT+} - V_{SAT-}) / R2$. If we can arrange for the output saturation levels to be equal and opposite, i.e., if $V_{SAT+} = -V_{SAT-}$, the expression can be written $V_H = (2 \times R1 \times V_{SAT+}) / R2$.

Now, the mid-point of the hysteresis band is simply the lower threshold plus half of the hysteresis voltage, or $V_{TL} + (V_H/2)$. So, for the case when $V_{SAT+} = -V_{SAT-}$ (and assuming $R_{SOURCE} = 0$), we find that:

$$\text{Mid-point of Hysteresis Voltage} = V_{TL} + (V_H/2) = \frac{V_{REF} \times (R1 + R2) - (R1 \times V_{SAT+})}{R2} + \frac{(R1 \times V_{SAT+})}{R2} \quad (\text{volts})$$

which simplifies nicely to:

$$V_{TL} + (V_H/2) = V_{REF} \times \frac{(R1 + R2)}{R2} \quad (\text{volts})$$

If we apply a d.c. bias voltage, V_{BIAS} , to the inverting input using the R3-R4 potential divider as shown in Fig.7a, we see that $V_{REF} = (V_{BIAS} \times R4) / (R3+R4)$, and so:

$$V_{TL} + (V_H/2) = V_{BIAS} \times \frac{R4}{(R3 + R4)} \times \frac{(R1 + R2)}{R2} \quad (\text{volts})$$

Therefore, if we make the ratio of $R2 / R1 = R4 / R3$, we get:

$$V_{TL} + (V_H/2) = V_{BIAS}$$

In other words, the mid-point of the hysteresis band will equal the bias voltage V_{BIAS} , as shown in Fig.2.7b for a positive value of V_{BIAS} .

This technique can be useful where the average level of the a.c. input signal changes unpredictably, a problem that can make it difficult or impossible to set appropriate thresholds using the simple Schmitt trigger of Fig.2.6.

By using the circuit of Fig.2.7a, and by arranging for V_{BIAS} to track the average level of the input signal, the thresholds will shift automatically such that the hysteresis band will always be centred

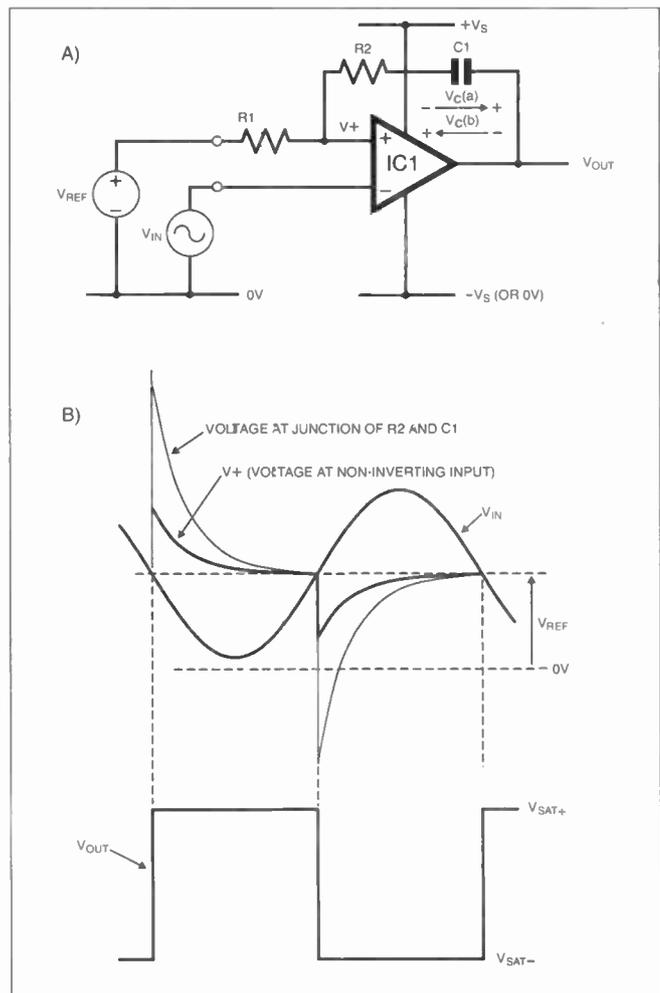


Fig.2.8. Using capacitive feedback provides temporal hysteresis.

on the a.c. signal. Remember, however, that this technique can only be used when the output saturation levels are equal and opposite.

SINGLE THRESHOLD VOLTAGE

For applications that demand only a single threshold voltage and yet still require noise rejection, we must find a way of introducing hysteresis without having two separate thresholds. This apparent paradox is achieved using "temporal" hysteresis, usually implemented with capacitive positive feedback as shown in the inverting Schmitt trigger of Fig.2.8a. The circuit works as follows:

Assume that V_{IN} is lower than $V+$, the voltage at the non-inverting terminal, such that V_{OUT} is in positive saturation. Capacitor C1 charges via R1 and R2 until its voltage, $V_C(a)$ equals $(V_{SAT+} - V_{REF})$.

When C1 is fully charged, no current flows through R1 and so $V+ = V_{REF}$. If V_{IN} now rises above $V+$, V_{OUT} abruptly changes state from V_{SAT+} to V_{SAT-} , causing the voltage at the R2-C1 junction to go to $V_{SAT-} - V_C(a) = V_{SAT-} - V_{SAT+} + V_{REF}$.

Thus, $V+$ is suddenly pulled down to a voltage lower than V_{REF} , resulting in the regenerative action needed for proper Schmitt trigger operation. (The actual voltage that $V+$ goes to depends on the ratio of R1 and R2).

However, $V+$ does not stay at this low level because C1 starts to charge via R1 and R2 until its voltage, $V_C(b)$ equals $(V_{REF} - V_{SAT-})$. Once C1 is fully charged, $V+$ again settles back to equal V_{REF} .

If V_{IN} now falls below $V+$, V_{OUT} snaps into positive saturation, and $V+$ is rapidly pulled to a voltage greater than V_{REF} . Once again, positive feedback causes the required regenerative action. C1 now charges until its voltage, $V_C(a)$ equals $(V_{SAT+} - V_{REF})$, at which point $V+$ again falls back to equal V_{REF} .

The waveforms in Fig.2.8b are those typically occurring in response to a sinusoidal input voltage, where $V_{REF} = V_{SAT+} / 2$ and $V_{SAT-} = 0$ (i.e., a single rail application).

Notice that when V_{IN} crosses the V_{REF} threshold, $V+$ jumps above or below V_{REF} and then decays back to a level equal to V_{REF} . Provided the $(R1 + R2) \times C1$ time constant is less than one-tenth the period of V_{IN} , $V+$ will always return to V_{REF} before V_{IN} next crosses the V_{REF} threshold.

Knowing the maximum input signal frequency, the appropriate $(R1 + R2) \times C1$ time constant may be determined. Then, having chosen $C1$, the ratio of $R1$ and $R2$ must be selected to maximise the voltage swing at the non-inverting input (thereby maximising the circuit's noise rejection properties) whilst ensuring that $V+$ remains within the common-mode input limits for the op.amp or comparator used.

Temporal hysteresis can be demonstrated using the circuit of Fig.2.9, a single rail circuit which again uses one half of an LMC6482 op.amp (although other op.amps or comparators with rail-to-rail input and output capability could be used).

Making $R1a$ and $R1b$ both equal to $100k\Omega$ sets $V_{REF} = 2.5V$ and provides an effective (Thévenin) value of $R1 = 50k\Omega$. With $R2 = 100k\Omega$ and $C1 = 6.8nF$, the feedback network's time constant is $1ms$, allowing the circuit to accommodate input signal frequencies as high as $100Hz$.

The maximum voltage swing at the non-inverting input is $V_{REF} \pm 1.7V$, i.e., $0.8V$ to $4.2V$, well within the op.amp's common-mode input limits.

The circuit's response to a noisy input signal is illustrated in Fig.2.10. The top trace shows the input signal, a sine wave containing over 30 per cent of "triangular" noise.

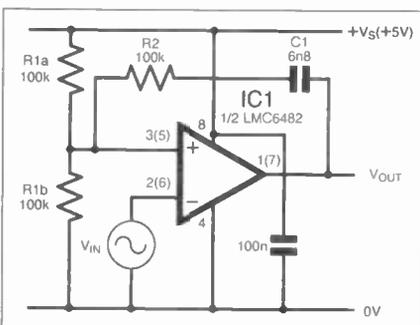


Fig.2.9. Single rail Schmitt trigger with temporal hysteresis.

The middle trace is the output of the circuit in Fig.2.9. Notice how there is only one transition each time the sinusoid crosses the $2.5V$ reference threshold.

The bottom trace shows the circuit's output with $R2$ and $C1$ removed (i.e., no positive feedback at all). The circuit now

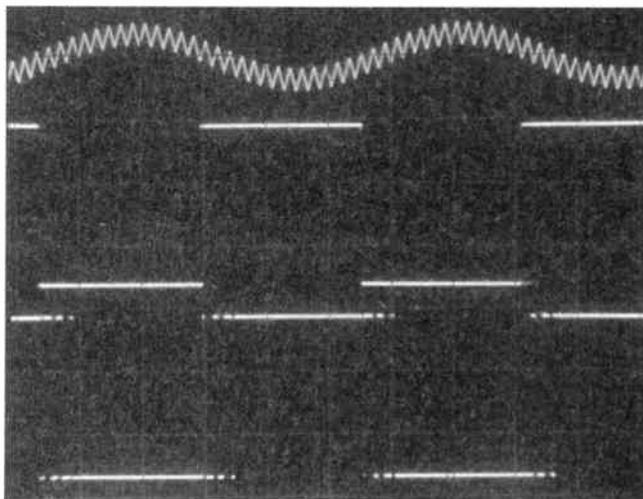


Fig.2.10. Waveforms showing that temporal hysteresis provides noise rejection. Top trace: V_{IN} ($5V/div.$). Middle trace: Output waveform of circuit with temporal hysteresis ($2V/div.$). Bottom trace: Output waveform with no positive feedback ($2V/div.$). Timebase: $2ms/div.$

behaves as a simple comparator, such that its input is triggered each time the noise crosses the $2.5V$ reference: the multiple transitions caused by the noise can clearly be seen on the output wave-form.

PRECISION AND VERSATILITY

In Part Three of this series, we'll examine methods for improving the Schmitt trigger's precision and flexibility. We'll also see how this versatile circuit element is used as the basis for other circuit functions, such as oscillators and pulse generators.

SHOP TALK

with David Barrington

PIC-Monitored Dual PSU

We have a minor problem concerning the metal case for the *PIC-Monitored PSU*. The original one used in the author's model is no longer stocked. However, although the dimensions are not exactly the same, our investigations have thrown up two possibilities and they are both RS types.

The first one measures $305mm \times 178mm \times 177mm$, is coded 223-972 and listed at $\pounds 19.55$. The other one is coded 671-242, measures $254mm \times 197mm \times 159mm$ and is listed at $\pounds 40.21$. Readers should be able to order these through any *bona-fide* RS stockists in their area. Alternatively, they can be ordered through **Electromail** (☎ **01536 304555** or <http://rswww.com>), their mail order outlet. No doubt, readers will have their own ideas regarding the case.

The $50VA$ mains transformer, code 805-142, and the L272 dual power op.amp, code 635-167, also came from the above source.

Regarding the monitor section. The alphanumeric 2-line 16-character per line liquid display module used in the prototype has an integral cable and connector. It was purchased from **Magenta Electronics** (☎ **01283 565435** or www.magenta2000.co.uk). Other advertisers will no doubt be able to offer something similar, without cable.

For those readers unable to program their own PICs, a ready-programmed PIC16F877-4P can be purchased from Magenta (see above) for the inclusive price of $\pounds 10$ (overseas readers add $\pounds 1$ for postage). Software for the *PIC-Monitored Dual PSU* is available on a 3.5-in. PC-compatible disk from the *EPE* Editorial Office – see *PCB Service* page 946. It is also available free via the *EPE* web site: [ftp://epemag.wimborne.co.uk/pubs/PICS/PICmonpsu](http://epemag.wimborne.co.uk/pubs/PICS/PICmonpsu).

The two printed circuit boards are available from the *EPE PCB Service*, codes 280 (Power Supply, of which two are needed for the full PSU) and 281 (Monitor).

Static Field Detector

This month's Starter Project is a low-cost *Static Field Detector* and we do not expect any "sticky" component problems.

The specified TL061CP op.amp has an output stage that will drive both i.e.d.s from fully switched off to fully on, whereas many other op.amps will fail to do this. Therefore, the use of alternative devices is not really recommended. The TL061CP should be readily available from component advertisers.

The printed circuit board for the "Detector" is the Multi-project board available from our *PCB Service*, code 932.

Motorists' Buzz-Box

Prices for panel meters tend to vary quite considerably and it may pay you to shop around when collecting together parts for the *Motorists' Buzz-Box* project.

The LM334N adjustable current source chip came from Maplin (☎ **0870 264 6000** or www.maplin.co.uk), code WQ32K. They also have a "large" $50\mu A$ panel

meter, code RX54J, but you will need a larger plastic box for this one. The printed circuit board is available from the *EPE PCB Service*, code 278.

Festive Fader

The $3VA$ mains transformer, with twin primary and secondary windings, and the MOC3020 opto-isolated triac for the *Festive Fader* were purchased from **Farnell** (☎ **0113 263 6311** or www.farnell.com), codes 159-438 and 280-320. They also supplied the $1\mu F$ multilayer ceramic capacitor, but you will probably have to buy in multiples of 5. It is also listed by **Electromail** (☎ **01536 304555** or <http://rswww.com>), code 264-4977 (packs of 5).

The printed circuit board is available from the *EPE PCB Service*, code 277 (see page 946). The Euro mains connector, with fuseholder, should be widely stocked.

PICtogram

All of the components called up for the *PICtogram* project appear to be "off-the-shelf" items except, of course, a ready-programmed PIC16F84 microcontroller. The $2mA$ i.e.d.s certainly seem to be in abundant supply, in various colours.

For those readers unable to program their own PICs, the author is able to supply ready-programmed PIC16F84 microcontrollers for the sum of $\pounds 6$ each, inclusive of postage (overseas add $\pounds 1$ per order). Orders should be sent to: **Andy Flind, 22 Holway Hill, Taunton, Somerset, TA1 2HB**. Payments should be made out to *A. Flind*. For those who wish to program their own PICs, the software is available from the Editorial offices on a 3.5-in. PC-compatible disk, see *PCB Service* page 946. It is also available free via the *EPE* web site: [ftp://epemag.wimborne.co.uk/pubs/PICS/PICtogram](http://epemag.wimborne.co.uk/pubs/PICS/PICtogram).

Finally, the printed circuit board is available from the *EPE PCB Service*, code 271 (see page 946).

Christmas Bubble and Twinkling Star

Regarding the *Christmas Bubble* and *Twinkling Star* projects, both sets of components appear to be "run of the mill" items and should not cause any sourcing problems.

Jumbo i.e.d.s ($10mm$) should cost you just under $\pounds 1$ on average. You may also be able to buy the standard i.e.d.s at quantity discounts from some advertisers, it's worth trying.

If you must run these two projects using mains adaptors, most of our components advertisers seem to stock good quality, multi-voltage types. The small printed circuit board for the *Twinkling Star* is available from the *EPE PCB Service*, code 276 (see page 946).

PLEASE TAKE NOTE

Anti-Tamper Alarm (Ingenuity Unlimited)

Page 766. The i.c.s should be types 4001 and not as shown on the circuit. Also, note capacitor $C1$ should be $10n$ (nano) and not as shown. Oct '00

Versatile Mic/Audio Preamplifier


It would appear that supplies of the SSM2166P mic. preamp chip have now "dried-up". If any readers know of a source please let us know so that we can pass it on. May '00

CONTROL & ROBOTICS


Milford Instruments

BASIC Stamp Microcontrollers

Still the simplest and easiest way to get your project or development work done. BASIC Stamps are small computers that run BASIC programmes. With either 8 or 16 Input-Output pins they may be connected directly to push-buttons, LEDs, speakers, potentiometers and integrated circuits such as digital thermometers, real-time clocks and analog-digital converters. BASIC Stamps are programmed using an ordinary PC running DOS or Windows. The language has familiar, easy-to-read instructions such as FOR...NEXT, IF...THEN and GOTO. Built-in syntax make it easy to measure and generate pulses, read push-buttons, send/receive serial data etc. Stamps from **£25** (single quantities), Full development kits from **£79**

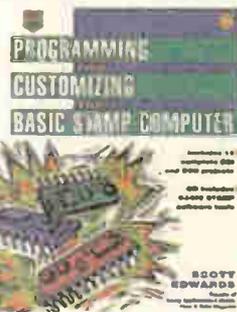

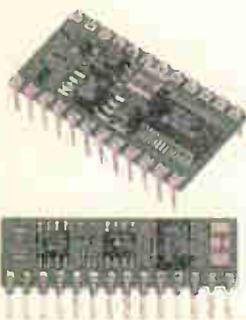Full information on using BASIC Stamps plus lots of worked projects and practical electronics help. CD-ROM also includes 30+ past magazine articles and Stamp software. **£29.95**



New to PICs or just wanting to learn more tricks? We stock the excellent PIC primer books from David Benson - suitable for the complete beginner to the advanced user.



SERIAL LCDs

Banish the hassle of interfacing to LCD displays. We stock a comprehensive range of alphanumeric and Graphic LCDs - all with an easy-to-use standard RS232 serial interface. Sizes from 2x16 to 4x40 plus 128x64 graphic panels. Prices start at **£25** (single quantity)



Stamp2 based 3-axis machine
Stepper drive to X, Y and Z axes with 0.1mm (4thou) resolution. Kit contains pre-machined frame components. Complete with Windows software for drilling pcbs. **Full kit at £249, Part kit at £189**

StampBug

Stamp1 based walking insect. Forwards, backwards and left/right turn when feelers detect object in path. Up to 2 hours roving from 4xAA Nicads. Chips pre-programmed but programme may be changed (software supplied). Body parts pre-cut. **Full kit £68**



TecArm4

New range of robotic arms for educational and hobbyist use with super powerful servos. Controlled from PC (Windows freeware provided) or from optional keypad. Stands about 450mm high when fully extended. Kit includes all pre-cut body parts, servo controller board, servos and software. Requires 9v Dc. Kits start of **£189**



Alex- Animated Head

Stamp2 based controller with voice record-playback capability, PIR input and/or random playback. 4-servo actions are recorded/edited one track at a time. May also be controlled from PC. **Head kits start at £29. Controllers from £29**

BigFoot

Stamp1 based walking humanoid. Walks forwards/backwards with left and right turn when detects obstacles. Electronics pcb pre-built and tested. Programme pre-loaded but may be changed with supplied software. **Full kit £68**



On Screen Display
Superimpose text onto standard CCTV from simple RS232 serial line. Ready built/tested of **£59**

IR Decoder Board

Control your project using a standard domestic IR remote. 7 Output lines (5v @ 20mA) may be set to momentary or toggle action. Simple teaching routine. Requires 9-12vDC. Supplied built and tested. **£29 single quantity**



Servo Driver Board

Control up to 8 standard hobby servos from an RS232 serial data line using this controller board. Simple command structure holds servos in position until update is received. Fully built and tested- requires 9vDC and servos. Supplied with Windows freeware. **£29 single quantity. Optional keypad available.**



Milford Instruments


120 High Street, South Milford, LEEDS LS25 5AQ
Tel: 01977 683665 Fax: 01977 681465

All prices exclude VAT and shipping.

BASIC Stamp is the registered trademark of Parallax Inc. For further details on the above and other interesting products, please see our web site www.milinst.demon.co.uk

**WHETHER ELECTRONICS IS YOUR HOBBY
OR YOUR LIVELIHOOD . . .
YOU NEED THE MODERN ELECTRONICS MANUAL
and the ELECTRONICS SERVICE MANUAL**

THE MODERN ELECTRONICS MANUAL

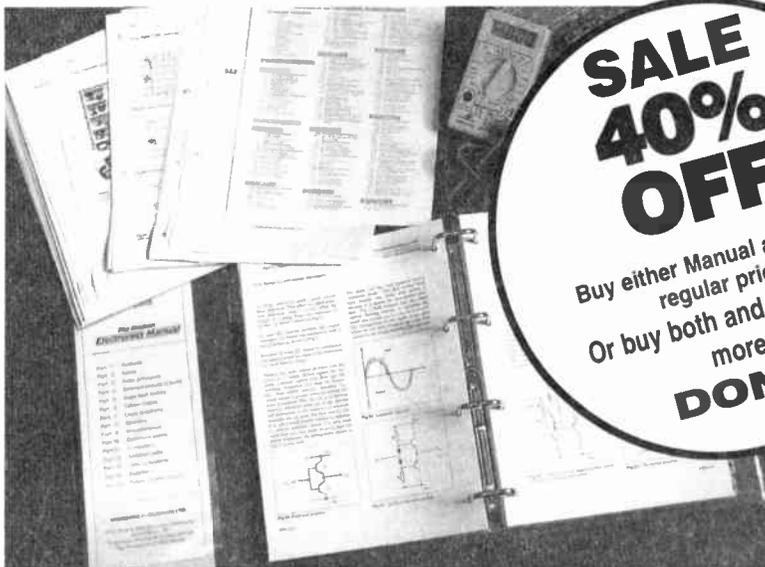

**SALE
40%
OFF**
Buy either Manual at 40% off
regular price.
Or buy both and save even
more.
DON'T

*The essential reference
work for everyone
studying electronics*

- Over 900 pages
- In-depth theory
- Projects to build
- Detailed assembly instructions
- Full components checklists
- Extensive data tables
- Detailed supply information
- Easy-to-use format
- Clear and simple layout
- Comprehensive subject range
- Professionally written
- Regular Supplements
- Sturdy gold blocked ring-binder

EVERYTHING YOU NEED TO GET STARTED AND GO FURTHER IN ELECTRONICS!

The revised edition of the Modern Electronics Base Manual contains practical, easy-to-follow information on the following subjects:

BASIC PRINCIPLES: Electronic Components and their Characteristics (16 sections from Resistors and Potentiometers to Crystals, Crystal Modules and Resonators), Circuits Using Passive Components (9 sections), Power Supplies, The Amateur Electronics Workshop, The Uses of Semiconductors, Digital Electronics (6 sections), Operational Amplifiers, Introduction to Physics, Semiconductors (6 sections) and Digital Instruments (5 sections).

CIRCUITS TO BUILD: There's nothing to beat the satisfaction of creating your own project. From basic principles, like soldering and making printed circuit boards, to circuit-building, the Modern Electronics Manual and its Supplements describe clearly, with appropriate diagrams, how to assemble radios, loudspeakers,

amplifiers, car projects, computer interfaces, measuring instruments, workshop equipment, security systems, etc. The Base Manual describes 13 projects including a Theremin and a Simple TENS Unit.

ESSENTIAL DATA: Extensive tables on diodes, transistors, thyristors and triacs, digital and linear i.c.s.

EXTENSIVE GLOSSARY: Should you come across a technical word, phrase or abbreviation you're not familiar with, simply turn to the glossary included in the Manual and you'll find a comprehensive definition in plain English.

The Manual also covers **Safety and Suppliers**. The most comprehensive reference work ever produced at a price you can afford, the revised edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the *essential* information you need.

THE MODERN ELECTRONICS MANUAL

Revised Edition of Basic Work: Contains over 900 pages of information. Edited by John Becker.

Regular Supplements: Approximately 160-page Supplements of additional information which, if requested, are forwarded to you immediately on publication (four times a year). These are billed separately and can be discontinued at any time.

Presentation: Durable looseleaf system in large A4 format

Price of the Basic Work: ~~£39.95~~ **SALE PRICE £23.97** (to include a recent Supplement **FREE**)

Guarantee

Our 30 day money back guarantee gives you **complete peace of mind**. If you are not entirely happy with either Manual, for whatever reason, simply return it to us in good condition within 30 days and we will make a **full refund of your payment** – no small print and no questions asked.
(Overseas buyers do have to pay the overseas postage charge)

ELECTRONICS SERVICE MANUAL

EVERYTHING YOU NEED TO KNOW TO GET STARTED IN REPAIRING AND SERVICING ELECTRONIC EQUIPMENT

SAFETY: Be knowledgeable about Safety Regulations, Electrical Safety and First Aid.

UNDERPINNING KNOWLEDGE: Specific sections enable you to Understand Electrical and Electronic Principles, Active and Passive Components, Circuit Diagrams, Circuit Measurements, Radio, Computers, Valves and manufacturers' Data, etc.

PRACTICAL SKILLS: Learn how to identify Electronic Components, Avoid Static Hazards, Carry Out Soldering and Wiring, Remove and Replace Components.

TEST EQUIPMENT: How to Choose and Use Test Equipment, Assemble a Toolkit, Set Up a Workshop, and Get the Most from Your Multimeter and Oscilloscope, etc.

SERVICING TECHNIQUES: The regular Supplements include vital guidelines on how to Service Audio Amplifiers, Radio Receivers, TV Receivers, Cassette Recorders, Video Recorders, Personal Computers, etc.

TECHNICAL NOTES: Commencing with the IBM PC, this section and the regular Supplements deal with a very wide range of specific types of equipment – radios, TVs, cassette recorders, amplifiers, video recorders etc..

REFERENCE DATA: Detailing vital parameters for Diodes, Small-Signal Transistors, Power Transistors, Thyristors, Triacs and Field Effect Transistors. Supplements include Operational Amplifiers, Logic Circuits, Optoelectronic Devices, etc.

The essential work for servicing and repairing electronic equipment

- Around 900 pages
- Fundamental principles
- Troubleshooting techniques
- Servicing techniques
- Choosing and using test equipment
- Reference data
- Easy-to-use format
- Clear and simple layout
- Vital safety precautions
- Professionally written
- Regular Supplements
- Sturdy gold blocked ring-binder

ELECTRONICS SERVICE MANUAL

Basic Work: Contains around 900 pages of information. Edited by Mike Tooley BA

Regular Supplements: Approximately 160-page Supplements of additional information which, if requested, are forwarded to you immediately on publication (four times a year). These are billed separately and can be discontinued at any time.

Presentation: Durable looseleaf system in large A4 format

Price of the Basic Work: ~~£39.95~~ SALE PRICE £23.97 (to include a recent Supplement FREE)

ORDER BOTH MANUALS TOGETHER AND SAVE ANOTHER £8

A mass of well-organised and clearly explained information is brought to you by expert editorial teams whose combined experience ensures the widest coverage
Regular Supplements to these unique publications, each around 160 pages, keep you abreast of the latest technology and techniques if required

REGULAR SUPPLEMENTS

Unlike a book or encyclopedia, these Manuals are living works – continuously extended with new material. If requested, Supplements are sent to you approximately every three months. Each Supplement contains around 160 pages – all for only £23.50+£2.50 p&p. You can, of course, return any Supplement (within ten days) which

you feel is superfluous to your needs. You can also purchase a range of past Supplements to extend your Base Manual on subjects of particular interest to you.

RESPONDING TO YOUR NEEDS

We are able to provide you with the most important and popular, up to date, features in our

Supplements. Our unique system is augmented by readers' requests for new information. Through this service you are able to let us know exactly what information you require in your Manuals.

You can also contact the editors directly in writing if you have a specific technical request or query relating to the Manuals.

PLEASE send me

THE MODERN ELECTRONICS MANUAL plus a FREE SUPPLEMENT

ELECTRONICS SERVICE MANUAL plus a FREE SUPPLEMENT

I enclose payment of £23.97 (for one Manual) or £39.94 for both Manuals (saving another £8 by ordering both together) plus postage if applicable.

I also require the appropriate Supplements four times a year. These are billed separately and can be discontinued at any time. *(Please delete if not required.)*

Should I decide not to keep the Manual/s I will return it/them to you within 30 days for a full refund.

FULL NAME
(PLEASE PRINT)

ADDRESS

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

ORDER FORM

Simply complete and return the order form with your payment to the following address:

Wimborne Publishing Ltd, Dept. Y12, Allen House, East Borough, Wimborne, Dorset BH21 1PF

We offer a 30 day MONEY BACK GUARANTEE

– if you are not happy with either Manual simply return it to us in good condition within 30 days for a full refund.

Overseas buyers do have to pay the overseas postage – see below

POSTAGE CHARGES

Postal Region	Price PER MANUAL	
	Surface	Air
Mainland UK	FREE	–
Scottish Highlands, UK Islands & Eire	£5.50 each	–
Europe (EU)	–	£20 each
Europe (Non-EU)	£20 each	£26 each
USA & Canada	£25 each	£33 each
Far East & Australasia	£31 each	£35 each
Rest of World	£25 each	£45 each

Please allow four working days for UK delivery.

NOTE: Surface mail can take over 10 weeks to some parts of the world. Each Manual weighs about 4kg when packed.

esm2

New Technology Update

Inkjet and optical technologies combine to provide greater comms bandwidth. Ian Poole reports.

THE telecommunications industry is one of the major growth areas in today's business arena. Increasing amounts of information are required and they are needed faster than ever before. Much of this has been fuelled by the phenomenal growth of the Internet, with applications like e-commerce and the transmission of audio and video providing ever-increasing levels of traffic.

Such is the growth that it has been predicted that the capacity required will have risen by a factor of thirty-six in the eight years from 1995.

Optical Data Rates

Many of the transmission paths use optical technologies. New techniques like Dense Wavelength Division Multiplexing (DWDM) are being used more widely. In this, a single fibre is used to carry several channels, each having a different wavelength.

Optical fibre data rates are also increasing, with transmission speeds set to quadruple in the next two years. This will enable network builders to move from the existing backbones running at 10 Gigabits per second to 40 Gigabits.

To ensure that the required speeds can be met, many organisations are moving to all-optical networks. This alleviates a number of the problems found in mixed technology systems. It also gives additional levels of flexibility, for example allowing operators to lease a wavelength, whereby the entire wavelength channel is leased out to a user.

This gives the potential of desk-top to desk-top optical communications, which can be very attractive to the system provider as there could be many thousands of optical channels available within a single fibre.

Switched Solution

To achieve these goals, optical devices need to be developed further. At the moment many are very expensive, but there are a number of developments that are under way that are likely to resolve many of the problems being encountered.

One of these areas is in optical switching, where Agilent (formerly the non-computer related areas of Hewlett Packard) have developed an optical switch. This uses a combination of inkjet activators and optical planar waveguides to give a simple and scalable optical switch with no moving parts.

Agilent's new switch is the N3565A, which provides a 32 x 32 photonic switching platform. It innovatively uses inkjet printer technology, combined with planar

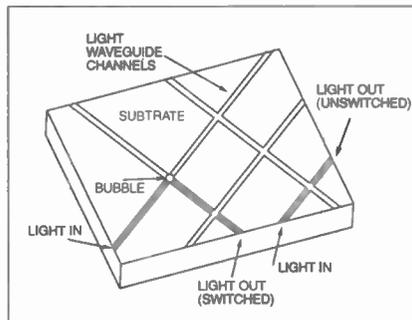


Fig.1. The light waveguide switching platform.

lightwave circuit technologies.

The switch consists of intersecting silica waveguides as shown in Fig.1. At each intersection a trench is etched into the waveguide. This is filled with a fluid that has a refractive index matching that of the light path, and accordingly it allows unimpeded transmission of the light across the intersection.

When a command to switch is issued, a bubble is created at the intersection and this causes the light to be reflected down the intersecting light path by total internal reflection (Fig.2). It is this bubble that is formed using inkjet printer technology.

Switching Technique

Switching is performed using the piezo-electric actuators that are based on those found in inkjet printers. These are solid state devices that are comprised of a pump chamber, inlet mechanism and a bubble nozzle. When a voltage is applied to the piezo-electric actuator, it contracts and

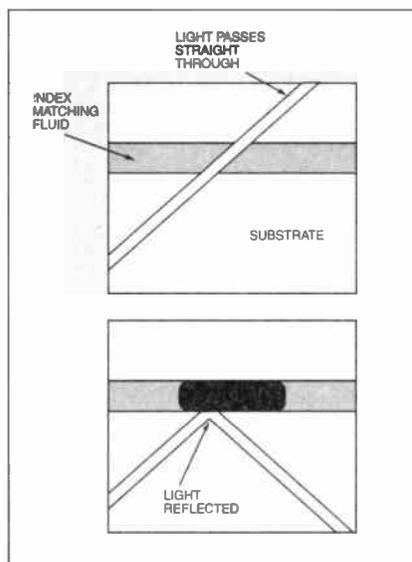


Fig.2. Principle of switching.

then relaxes when the voltage is removed. This action increases and then reduces the pump chamber volume, drawing in liquid and ejecting droplets under pulsed control.

Using this system, switching can occur in less than ten milliseconds, and this is sufficiently fast for the systems on which it is anticipated the switch will be used.

The absence of moving parts is the key to the reliability of the system. The inkjet elements have been switched many millions of times in tests and have been shown to be exceedingly reliable. Additionally, the fluid that is used is non-corrosive and stable, which are key elements in the reliability of the whole system.

System Aspects

The basic principle can be used to create very large switching matrices that enable a considerable amount of flexibility to be introduced into optical data systems. Whilst there is about 5dB of loss from one fibre, through the switch, into the output fibre, for what is termed a wavelength selective cross-connect, this is quite acceptable, especially when it is compared to other technologies.

Crosstalk is surprisingly low at -50dB, demonstrating the very high level of isolation that is achieved. This is particularly important where large numbers of optical paths are switched, because if the levels were higher then it would also lead to high levels of interfering noise that would result in data errors.

Future

This development is likely to achieve widespread use. It is flexible, cheap and effective. It shows that optical technology for data transmission can now be used even in small installations.

The development is also indicative of the growing use of optical technology. It has several advantages, even for the small user. Not only are much higher data rates possible than for an electrical wire system, but it also has greater immunity to electrical noise. For those interested in security, the optical fibres do not radiate the signals in the same way that wired systems do, thereby making eavesdropping much more difficult.

In view of all these advantages, many commentators anticipate that optical technology will grow considerably in importance in the coming years.

Further information about these optical switches can be found on the Agilent website at www.agilent.com.

Information about radio and electronics in general can be found at www.radio-

*All in all, it can be
thoroughly recommended.*

Everyday Practical Electronics - 10/2000


A must-try product

Farnell - 9/2000



What does it offer?

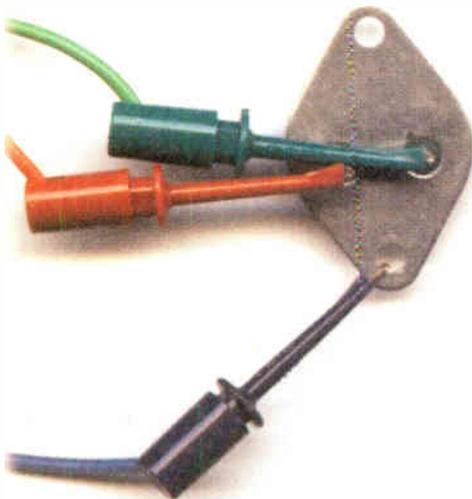- Automatic component identification
- Pinout identification
- Important parameter measurement
- Clear scrollable pages
- No nonsense simplicity and power



What components are supported?

- Bipolar transistors
- Darlington transistors
- Diode protected transistors
- Resistor shunted transistors
- Enhancement mode MOSFETs
- Depletion mode MOSFETs
- Junction FETs
- Low power triacs and thyristors
- Diodes and diode networks
- LEDs including 2 lead and 3 lead bicolours

We just know you will fall in love with this thing.

We Guarantee it!!

Contact us for a comprehensive data pack. Alternatively, order a Peak Atlas and you can just send it back to us for a full refund if you are not happy for any reason.

You can pay using a cheque, postal order, credit or debit card. Please contact us for overseas or volume orders - you will be pleasantly surprised.

peak electronic design limited

From UK
Tel. 01298 70012
Fax. 01298 22044

From Outside UK
Tel. +44 1298 70012
Fax. +44 1298 22044

Internet
Web: www.peakelec.co.uk
Email: sales@peakelec.co.uk

West Road House,
West Road,
Buxton, Derbyshire,
SK17 6HF, UK.

INTERFACE

Robert Penfold



EXTENDED TEMPERATURE PC INTERFACE SOFTWARE

As pointed out in the past, this series is primarily concerned with the hardware side of add-on projects for PCs. However, without software the projects are of no use, and the software topics have to be considered from time to time.

Interestingly, it is the software that tends to bring the most feedback from readers. Over the last year software matters seem to have generated three or four times as many letters and E-mails as hardware related topics.

Some of the letters contain suggestions for better ways of doing things. Thanks to those who have made suggestions, some of which have been incorporated into the software featured in recent months.

Others are interested in using improved software to extend the capabilities of the projects featured in this series. Arrays and data logging is a topic that turns up from time to time, and is one that has not been covered significantly in this series.

Arrays

Usually the software has to do nothing more than take a reading from a port, do some simple arithmetic on the returned value, and then display the value on the screen. This is achieved by storing the reading in a variable, doing any necessary mathematics with the result being stored back in the variable, and then writing the contents of the variable to the screen via a label or text box.

Data logging is more complex in that it requires what could be hundreds or even thousands of readings to be taken and stored in the computer's memory. The results can then be read via a text box, printed out, or presented on the screen in some graphic form.

Arrays are used to store blocks of data, and each element of an array is just a special form of variable. The exact way in which arrays are handled varies slightly from one programming language to another, but here we will consider the Visual BASIC 6 version, which is fairly typical.

Each element in an array has the same name, but a number in parentheses (brackets) follows this name. This number gives each element in the array a unique identity. In the normal scheme of things the numbering starts at 0 and goes up to the number that is specified when the array is dimensioned. In Visual BASIC you can declare variables or simply make them up as you go along.

This same flexibility is not available when using arrays, and they must be declared and dimensioned before they are used. By telling the programming

language the type of variable used in the array and the number of elements, it is then able to reserve a suitably sized block of memory to store the data.

Going Public

When declaring variables and arrays in Visual BASIC it has to be borne in mind that there are public and private variables. If the declaration is made within a subroutine, the variable can only be used within that routine.

This can be very useful, but with interfacing software it is often the public version that is of more use. By declaring a variable outside a subroutine it becomes a public type that can be accessed by any part of the program. The following line, for example, would declare an array containing 100 elements, with each element an integer:

```
Dim Reading(99) As Integer
```

Note that there are 100 and not 99 cells in this array, because the numbering starts at 0 and not 1. In order to read a set of data into an array a loop is used, together with a variable that acts as a counter. For example, the followings routine would read the printer port data lines at address 888 one hundred times, placing the readings in the elements of the array called Reading:

```
Dim Reading(99) As Integer
```

```
Out 890,32
```

```
For Counter = 0 To 99
```

```
Reading(Counter) = Inp(888)
```

```
Next Counter
```

The first line dimensions the array, and the second one sets the printer port data

Listing 1: Extended Temperature Interface Program

```
Dim Port1 As Integer
Dim Port2 As Integer
Dim Port3 As Integer
Dim Reading As Integer
Dim Counter As Integer
Dim Readings(99) As Integer

Private Sub Command1_Click()
Port1 = 632
Port2 = 633
Port3 = 634
Timer1.Enabled = True
End Sub

Private Sub Command2_Click()
Port1 = 888
Port2 = 889
Port3 = 890
Timer1.Enabled = True
End Sub

Private Sub Command3_Click()
Label1.Caption = Readings(Text1.Text)
End Sub

Private Sub Form_Load()
Counter = 0
End Sub

Private Sub Timer1_Timer()
Out Port3, 1
Out Port3, 3
Out Port3, 2
For D = 1 To 2000
Next D
Dta = Inp(Port2) And 8
If Dta = 8 Then Reading = 128
Else Reading = 0
Out Port3, 3
Out Port3, 2
Dta = Inp(Port2) And 8
If Dta = 8 Then Reading = Reading + 64
Out Port3, 3
Out Port3, 2
Dta = Inp(Port2) And 8
If Dta = 8 Then Reading = Reading + 32
Out Port3, 3
Out Port3, 2
Dta = Inp(Port2) And 8
If Dta = 8 Then Reading = Reading + 16
Out Port3, 3
Out Port3, 2
Dta = Inp(Port2) And 8
If Dta = 8 Then Reading = Reading + 8
Out Port3, 3
Out Port3, 2
Dta = Inp(Port2) And 8
If Dta = 8 Then Reading = Reading + 4
Out Port3, 3
Out Port3, 2
Dta = Inp(Port2) And 8
If Dta = 8 Then Reading = Reading + 2
Out Port3, 3
Out Port3, 2
Dta = Inp(Port2) And 8
If Dta = 8 Then Reading = Reading + 1
Out Port3, 3
Label1.Caption = Reading / 2
Readings(Counter) = Reading / 2
Counter = Counter + 1
If Counter = 100 Then Label1.Caption =
"STOPPED"
If Counter = 100 Then Timer1.Enabled =
False
End Sub
```

lines as inputs. The port must obviously be a bidirectional type for this to work. Note that Visual BASIC does not have built-in Inp and Out commands, and that these must be added using Inpout32.dll, as described in previous *Interface* articles. The rest of the routine is a For...Next loop that executes 100 times, incrementing the variable called Counter from 0 to 99 in the process. Counter is used as the element number in the program line that reads the printer port and the result into the array.

Therefore, on the first loop the returned value is read into Reading(0), on the next it is placed into Reading(1), and so on until the value read from the port is placed in Reading(99) on the one hundredth loop.

Perfect Timing

In practical applications the readings will usually have to be taken at regular intervals, and it may be necessary to have a substantial gap from one reading to the next. This could be achieved by adding a delay routine in the For...Next loop, but

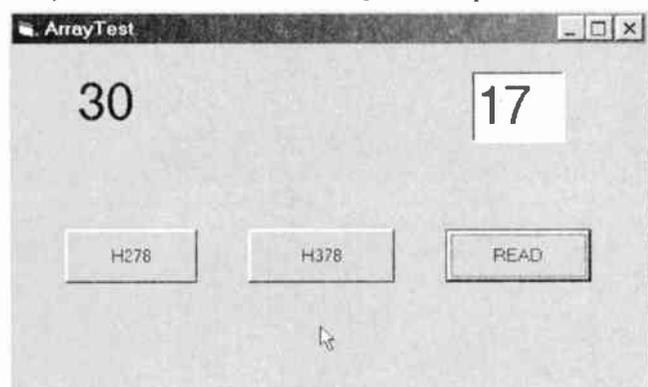


Fig.1. Screen shot showing display text box window and READ "button".

with Visual BASIC the obvious way of handling things is to assign the routine that reads the port to a timer component.

Readings are then taken at whatever interval is used for the timer. The method used to obtain readings might be more complex than simply reading a port, but the basic method outlined here can still be applied.

Program Listing 1 is an extension of the thermometer program featured in the previous *Interface* article. It takes 100 temperature readings at one-second intervals and places them in an array. See the October 2000 issue for details of the Temperature Interface.

As in the original program, operating either the button marked H278 or the one captioned H378 selects the required base address and starts the timer. The routine that reads the analogue-to-digital converter is relatively long because the data is read one bit at a time and then reconstituted into an 8-bit value. However, once the final value has been obtained it is displayed on Label1 and placed in the array.

Numbers Count

A variable called Counter is used to provide the element number, and this

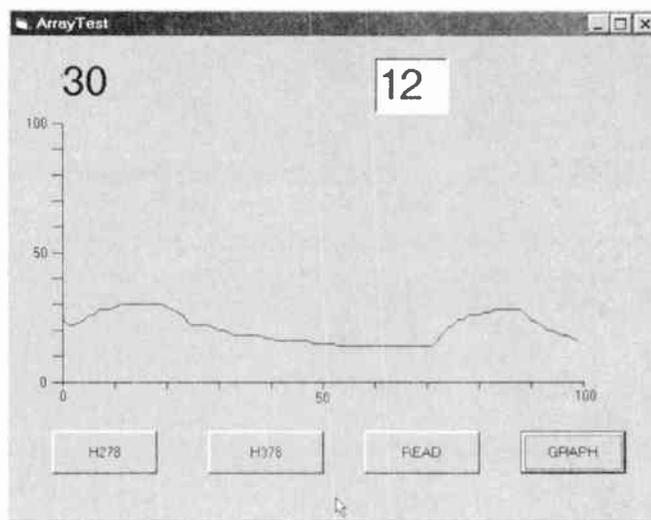


Fig.2. Extended program in action. Some simple calibration marks have been added to the graph to make it easier to interpret results.

variable is incremented by one each time the routine is performed. Eventually the value of Counter reaches 100, and the last line in the routine then switches off the timer so that no further readings are taken and stored. The penultimate line prints STOPPED on Label1 so that you know that things have come to a halt.

Once the data has been safely stored in an array the PC can manipulate it in a variety of ways. This program simply has a third button and a text box that enable individual samples to be displayed on the screen. Just type a number from 0 to 99 into the text box and then press the READ button. The relevant reading will then be displayed on Label1, as in the screen dump

that is shown in Fig.1.

There are plenty of other possibilities. The PC can be used to find and display the maximum and minimum readings, calculate and display various types of mean reading, and so on.

Graphics

A modern PC is also well equipped to display various types of graph and chart. The following routine can be applied to a fourth command button, and it draws a simple graph on the screen once a set of readings have been taken. The form must be large enough to accommodate the graph, and the middle section that the graph occupies must be left free of other components.

```
Private Sub Command4_Click()
Counter = 0
T1 = 600
T2 = 660
For Loops = 0 To 98
Lft = Readings(Counter)
Counter2 = Counter + 1
Rght = Readings(Counter2)
Lft = Lft * 30
```

```
Rght = Rght * 30
Lft = Lft + 1000
Rght = Rght + 1000
Lft = 5000 - Lft
Rght = 5000 - Rght
Line (T1, Lft) - (T2, Rght)
Counter = Counter + 1
T1 = T1 + 60
T2 = T2 + 60
Next Loops
End Sub
```

An enlarged version of the program in action is depicted in the screen dump of Fig.2. Some simple calibration marks have been added to make it easier to interpret results.

The routine starts by setting three variables at their initial values. T1 and T2 are variables used to provide the X1 and X2 co-ordinates for each section of the graph. Counter is used to select

the required element of the array, and is initially set at 0. The routine then goes into a For...Next loop that actually draws the graph.

The first and second readings are used to provide the Y1 and Y2 co-ordinates for the first section of the graph. Both require some mathematical manipulation in order to match up with the Visual BASIC co-ordinate system. Incidentally, the graphics area extends from 600,4000 at the bottom left corner to 6600,10000 at the top right hand corner.

A Line command is then used to actually draw the line, and this operates in much the same way as the QBASIC Line command. Counter is then incremented by 1, and T1 plus T2 are incremented by 60 (one second's worth of co-ordinates). The loop causes this process to be repeated a further 98 times until all 99 sections of the graph have been completed.

The routines provided here are quite basic, and do not contain any error trapping for example. However, they do demonstrate that reading data into an array is very straightforward. Processing the captured data and displaying it on the screen in various ways is then just a matter of using conventional programming techniques.

On Disk

Should you wish to experiment with them, the source files for the graph program are available on the EPE web site, as is the compiled version of the program. It is also available on the EPE *Interface* Disk 1, see EPE PCB Service page elsewhere in this issue for details.



Our
**Hot
 Rods**
*won't burn a hole
 in your pocket*

ANTEX

NOT JUST ANY OLD IRON

Antex have a great track record of offering high quality soldering irons at a low price. So race off with a 'fixed temperature' iron or take the 'In Handle' temperature controlled model for a burn.

Both offer total safety with a choice of a PVC or burn-proof silicone lead, and every model has been manufactured in the UK and meets CE conformity.

And with Antex you get loads of extras from a wide variety of long life bits to state-of-the art soldering stations.

So visit our web site or your electronics retailer and take one for a test drive



YOU CAN NOW BUY ANTEX EQUIPMENT ON-LINE
 ALL SOLDERING IRONS PURCHASED ON-LINE BEFORE CHRISTMAS WILL RECEIVE A FREE DESOLDER PUMP

www.antex.co.uk



**A COMPLETE RANGE OF
 INVERTERS**

150W TO 1000W - 12V & 24V

A complete range of regulated inverters to power 220V and 240V AC equipment via a car, lorry or boat battery. Due to their high performance (>90%) the inverters generate very little heat. The high stability of the output frequency ($\pm 1\%$) makes them equally suitable to power sensitive devices.

These inverters generate a modified sine wave, which are considerably superior to the square waves which are produced by most other inverters. Due to this superior feature they are capable of powering electrical equipment such as TVs, videos, microwave ovens, electrical lamps, pumps, battery chargers, etc.

Low Battery Alarm

The inverters give an audible warning signal when the battery voltage is lower than 10.5V (21V for the 24V version). The inverter automatically shuts off when the battery voltage drops below 10V (20V for the 24V version). Fuse protected input circuitry.

Order Code	Power	Voltage	Price
651.581	150W Continuous	12V	£38.49
651.578	150W Continuous	24V	£38.49
651.582	300W Continuous	12V	£54.36
651.585	300W Continuous	24V	£54.36
651.583	600W Continuous	12V	£118.42
651.593	600W Continuous	24V	£118.42
651.587	1000W Continuous	12V	£174.60
651.597	1000W Continuous	24V	£174.60



All prices are inclusive of V.A.T. Carriage £6.00 Per Order

Many uses include:- Festes • Fairgrounds • Shows • Picnics • Camping • Caravans • Boats • Carnivals • Field Research and • Amateur Radio field days.

DELIVERY CHARGES ARE £6.00 PER ORDER. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLC'S ETC. PRICES ARE INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX, OR EMAIL US AT SALES@BKELEC.COM ALTERNATIVELY SEND CHEQUE OR POSTAL ORDERS MADE PAYABLE TO BK ELECTRONICS.



B.K. ELECTRONICS




UNIT 11, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TP
 TEL: +44(0)1702-527572 FAX: +44(0)1702-420243

For Full Specifications View our web site at:-
WWW.BKELEC.COM/INVERTERS.HTM

SURFING THE INTERNET

NET WORK

ALAN WINSTANLEY

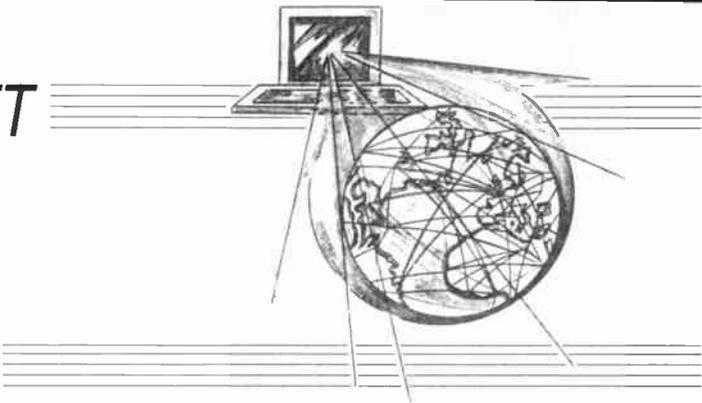

ONE of the downsides of writing a column dated several months ahead of reality is that it doesn't half make time fly. Here I am in early October already writing for the December 2000 issue, with the year 2001 arriving "next month"! This year started on an optimistic note, with promises of unmetered Internet access and broadband services wetting our appetites. Spring 2000 saw the attempt by Alta Vista UK to pre-empt the market by promising an unmetered package. Other unmetered tariffs have come and gone since then, all of them proving a financial drain for their operators, or in the case of Ezesurf, ruining them altogether.

Freeserve (www.freeserve.net) was amongst the very first to offer BT Surftime unmetered tariffs in Summer 2000, but has gone underground with its advertising, apparently having been heavily subscribed, even more so when other users, finding themselves turfed off other failed unmetered packages, migrated to Freeserve instead. Users were soon complaining of slow connections, engaged tones and poor bandwidth as the networks creaked under the strain.

On the Hog

Predictably, a minority of Freeserve incumbents decided to hog some lines to themselves, therefore spoiling the show for everyone else. More than 750 customers have since been served with a month's written notice because of their disproportionate drain – said to be up to 10% – on Freeserve's bandwidth.

The UK Consumer's Association said in October: "ISPs offering an unmetered service have seemed more interested in increasing their customer numbers than in delivering the services that consumers were originally promised when they signed up."

"Recent press reports suggesting that Freeserve would withdraw its unmetered access service from heavy users seems like another example of an unmetered offer that can't live up to the hype. If Freeserve has found itself caught out by the heavy usage of its customers it should accept its share of the blame."

"The ISPs have got themselves into a mess" says the CA. "Rather than luring consumers in and then kicking them off schemes, what is needed on their part is better planning, realistic projections of customer usage and clearer advertising for new schemes."

However, no ISP can reasonably cater for, say, a quarter of a million users all suddenly commandeering a cheap leased line 24x7, because the capacity just isn't there and probably never will be. Expectations are still running unrealistically high on both sides: consumers demand "excessive" levels of bandwidth on the cheap, and ISPs hope their customers will show restraint when using it.

The times are a'changing

I decided the time was ripe to review my Internet provision, if only to see what could be done to bring the cost down from its interstellar trajectory. I soon saw that confusion marketing reigned supreme. I started by checking my regular ISP, Demon Internet, who pioneered the flat-rate "TAM" (tenner-a-month) account in the early 1990's. Recently Demon felt sufficiently moved to incorporate a BT Surftime package, the idea being that the BT portion of the cost would be charged directly to your phone bill to provide for unmetered tariffs.

Under Surftime the standard TAM account will then benefit from reduced call costs – 2p/minute daytimes, 0-6p evenings, 0-5p weekends. For its proposed evenings and weekends package, Demon offers the standard Surftime £5.99 monthly rate paid direct to BT. This provides 100 per cent discount on all evening and weekend Internet calls, remembering Demon's £11.75 monthly subscription is extra.

Demon also proposes an enhanced package called *Premier Connect Plus* which costs nearly twice the standard account rate.

For a monthly sum of £19.99, the Surftime numbers can be used throughout the working day as well as during evenings and weekends. Under this package, call costs drop to 1p/min. weekday daytimes, 0-6p evenings and 0-5p weekends.

Demon continues: "Again, if you make a fixed extra payment to BT (a further £19.99 per month) you can get a 100 per cent discount on some or all of your Surftime calls so that they become 'free'. . . or you can pay £5.99 per month to cover evening and weekend calls only." Demon puts a price of £119.94 (\$167) per quarter on 100 per cent unmetered access. This service was due to roll out on 9 October.

This typifies the sort of stuff most users have to grapple with when comparing the best deals. Your cable operator may have packages comparable with any BT service (*ntl* hasn't replied to my query about cable modems). Personally, I sought a credible Surftime ISP offering a reasonable compromise to help slash daytime access costs, and maybe provide free calls in the evening and weekends.

As mentioned in previous columns, the choice of Surftime-enabled ISPs listed on BT's web site is meagre. A glitch with my Demon dial-in access – Demon changed their access software which rendered my modem obsolete – finally caused me to start shopping around.

Enter an ISP which bowed out from offering unmetered access earlier this year: LineOne (www.lineone.net). Their new Surftime tariff is simple and to the point: for a fee of £9.99 added to your phone bill – £5.99 is BT's Surftime evening and weekend portion, £4 is LineOne's ISP subscription – I could enjoy 1p a minute during the business daytime and completely free access during the evenings and weekends.

LineOne's on-line sign-up was soon completed and three days later an E-mail confirmed that my BT account had been updated for LineOne Surftime. This will cost £29.97 per quarter including VAT. Quickly dialling in via the new 0844 number, I was soon in business at 1p/minute or completely free altogether, and have high hopes of dramatically cutting costs. Note that LineOne telephone support costs 50p/minute, whilst Demon's is free, but this won't worry proficient users.

On your bike, ET

I was feeling quite pleased at this point. However, there's just enough room left this month to describe a perverse coincidence which rained on my parade. On the very same day I started to celebrate new lower prices, I spied a BT engineer shinning up the telegraph pole outside. In giving a neighbour a second line, the engineer did something to my own Internet access line which has resulted in my line speed being crippled to 33-6Kbps maximum, and it now takes several noisy attempts of my new modem to access any ISP at all, and connection speeds are suddenly 40 per cent slower.

This has all the makings of having a phone line "DACSeD" (Digital Access Carrier Service), multiplexing two signals down a copper wire where no new circuits are available, to channel two phone lines down one wire. It's a common BT trick.

A maximum line speed of 33-6K every time is a dead give-away that something is wrong, but my problem makes no sense as two separate properties are involved. I have already had the "we don't guarantee any modem speeds down a voice line" argument with several unsympathetic BT reps.

I am therefore, at a single stroke, back to the sort of line speed I endured half a decade ago. British Telecom uses E.T. the Extra Terrestrial as their TV advertising mascot and I can tell you that at the time of writing, I am more incandescent than E.T.'s finger-end.

You can E-mail me at alan@epemag.demon.co.uk. See you next month.

Constructional Project

MOTORISTS'

BUZZ-BOX



TERRY de VAUX-BALBIRNIE

A multi-purpose test instrument for the intrepid car owner.

It also provides a "crank test". This gives a battery "goodness" check by measuring the voltage under the heavy load over the starter motor.

THIS easy-build Buzz-Box is a test instrument having six useful functions. It would be ideal for anyone involved with fitting car accessories and for checking bulbs, fuses, switches, ignition leads and "earth" points. Since the unit receives power from the car electrical system, it does not need any internal batteries so will always be ready to use.

One particular advantage of this circuit is that most of the tests are provided by audible signals. This means that the user can concentrate on the task in hand without having to look at a display!

NEGATIVE ONLY

The Buzz-Box is suitable only for vehicles having a 12V *negative earth* system. That is, the negative terminal of the car battery is connected directly to the vehicle's metal structure ("earth" or "ground"). It is usual for the car body to provide the return path for the various circuits and this saves a lot of wiring.


Practically all cars in use today use the negative earth system although certain old models are "positive earth" (where the positive terminal of the battery is connected to the chassis). It is a simple matter to check this point if in doubt. **Damage will be caused to the unit if it is connected with incorrect polarity.**

OVERVIEW

The instrument is built in a small plastic box. On top there is a meter, a rotary control with scale, a pair of terminals, pair of sockets and two metal contact "rails" (see photograph). On the side, there is a further socket which accepts a test meter type probe. A long piece of twin wire is used to connect the unit to the car cigar lighter socket for powering it.

The Buzz-Box provides the following functions:

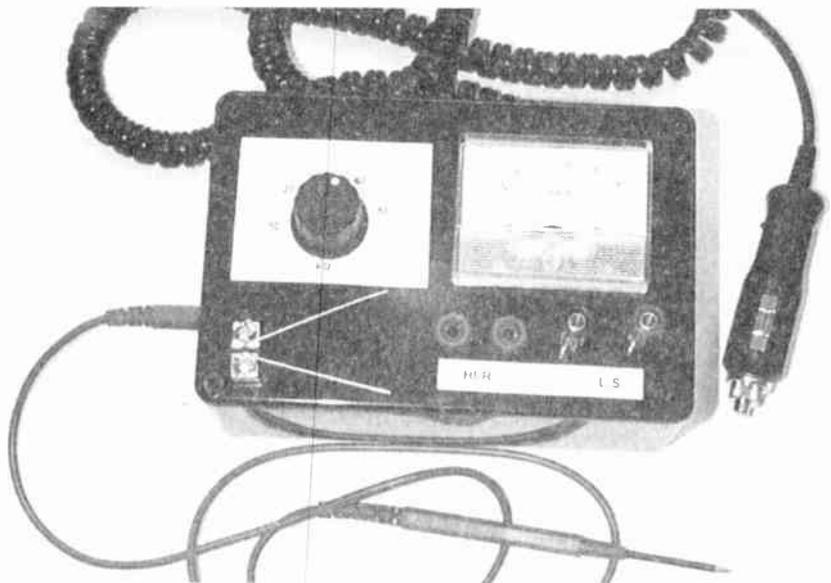1. Earth Test. When the probe is applied to some point which has a small resistance with respect to the car chassis, an internal buzzer will emit a short bleep. This will be found useful for finding a good "earth" point when wiring an accessory or for checking the quality of an existing connection. Rust at a securing screw is a common problem and will result in increased resistance.



2. 12V Test. When the probe is touched on to some point which is within approximately 300mV of supply voltage (nominally 11.7V), the buzzer will emit a long bleep.

3. Low Resistance Test (20Ω). When the terminals of a low-resistance component bridge the test rails, the buzzer will sound continuously providing its resistance lies between zero and 20 ohms approximately. Several items associated with the car electrical system have near-zero resistance. Examples include fuses, pieces of wire and "closed" switch contacts.

However, the "cold" resistance of a low-power bulb may exceed ten ohms. A facility for giving a bleep with a resistance less than 20 ohms or thereabouts is therefore useful. This may be used as a quick "continuity" check on any low-resistance item.

4. Ignition Lead Test (Hi-R). The lead is connected to the Hi-R (high resistance) test position. The knob on the rotary control is turned until the buzzer just sounds and the resistance read off on a scale from ten kilohms (10kΩ) to 50 kilohms (50kΩ).

5. Battery Voltmeter. While the unit is connected to the car system, a narrow-scale analogue meter gives a read-out of the battery voltage from 10V to 14V. This may be used to check the charge state of the battery.

6. Loudspeaker Test. When loudspeaker leads are connected to the terminals, the loudspeaker will emit an audible tone. This is useful when it is not known which set of loudspeaker leads is which. It will also identify faulty units and connections. *Note that this test does not determine how well the loudspeaker is working.*

In order to set up the voltmeter section at the end of construction, you will need brief access to a good-quality test meter.

Since the circuit receives current from the car system, the 0V line will be automatically connected to the car chassis through the low resistance of the feed wire. The positive line will be at whatever voltage exists across the car battery terminals. This will be approximately 12V but will vary to some extent depending on the state of charge of the battery.

HOW IT WORKS

The full circuit diagram for the Motorists' Buzz-Box is shown in Fig.1. In the descriptions which follow, the supply voltage is assumed to be 12V. However, it turns out that the exact value of the voltage (within operating limits) does not matter and this point will be explained later.

Note that there is *no* reverse-polarity protection provided. This would introduce

a voltage drop which would interfere with correct operation of the circuit.

However, providing the unit is correctly wired to the cigar lighter plug, the circuit cannot be connected incorrectly. Fuse FS1 provides some protection against overheating if a short-circuit were to occur. However, it does not provide any protection against reverse-polarity.

DOWN TO EARTH

The "earth test" centres around IC1a which is one section of quad op.amp (operational amplifier), IC1. This contains four identical units – the other three are associated with other tests.

The non-inverting input (pin 3) of IC1a is connected to a potential divider having fixed resistor R1 as the top arm. Resistor R2 appears in series with the resistance between the probe and the 0V line. This is labelled "R" (the "earth resistance") in Fig.1. Resistor R2 and R form the lower arm of the potential divider.

It will be noted that resistors R7 and R8 connected in series, appear in parallel with

R. When the probe is connected to an earth point there will be only a very small resistance between itself and the 0V line so the effect of resistors R7 and R8 (having a combined resistance much higher than R) is negligible.

When the probe is left unconnected, the non-inverting input (pin 3) will be at 9.7V approximately. This is due to the potential divider which now consists of resistor R1 in the top arm and R2 in series with R7 and R8 in the lower one.

When the probe is connected to an "earth" point, R will have a very low value. Assume for the moment that this is zero. The upper and lower arms of the potential divider connected to IC1a non-inverting input will now be equal. The voltage here will then be one-half that of the supply – that is, 6V approximately.

However, if the earth resistance was, say, 0.5 ohm the lower arm would have a greater resistance than the upper one. In this case, calculation shows that the voltage at IC1a non-inverting input would be 6.03V, 30mV more than before.

POTENTIALLY MORE

The inverting input of IC1a (pin 2) is also connected to a potential divider. This comprises resistor R3 (the top arm) and the network of resistors R4, R5 and preset potentiometer VR1 connected in series (the bottom one). When preset VR1 is set to minimum, the voltage at the inverting input will be 5.8V and when at maximum, 6.1V approximately.

By adjusting preset VR1 at the end of construction, the inverting input voltage can be made to exceed that at the non-inverting one when R is between zero and some chosen value. The op.amp will then have its output (pin 1) low.

Some adjustment is needed to provide the required "low" point taking account of component tolerances and the resistance already existing in the connecting wires. In the prototype unit, the low point was set at 0.3 ohm approximately.

With the probe unconnected, the voltage at IC1a pin 3 (9.7V) exceeds that at pin 2 (6V approx.) so the op.amp output is high. This has no further effect.

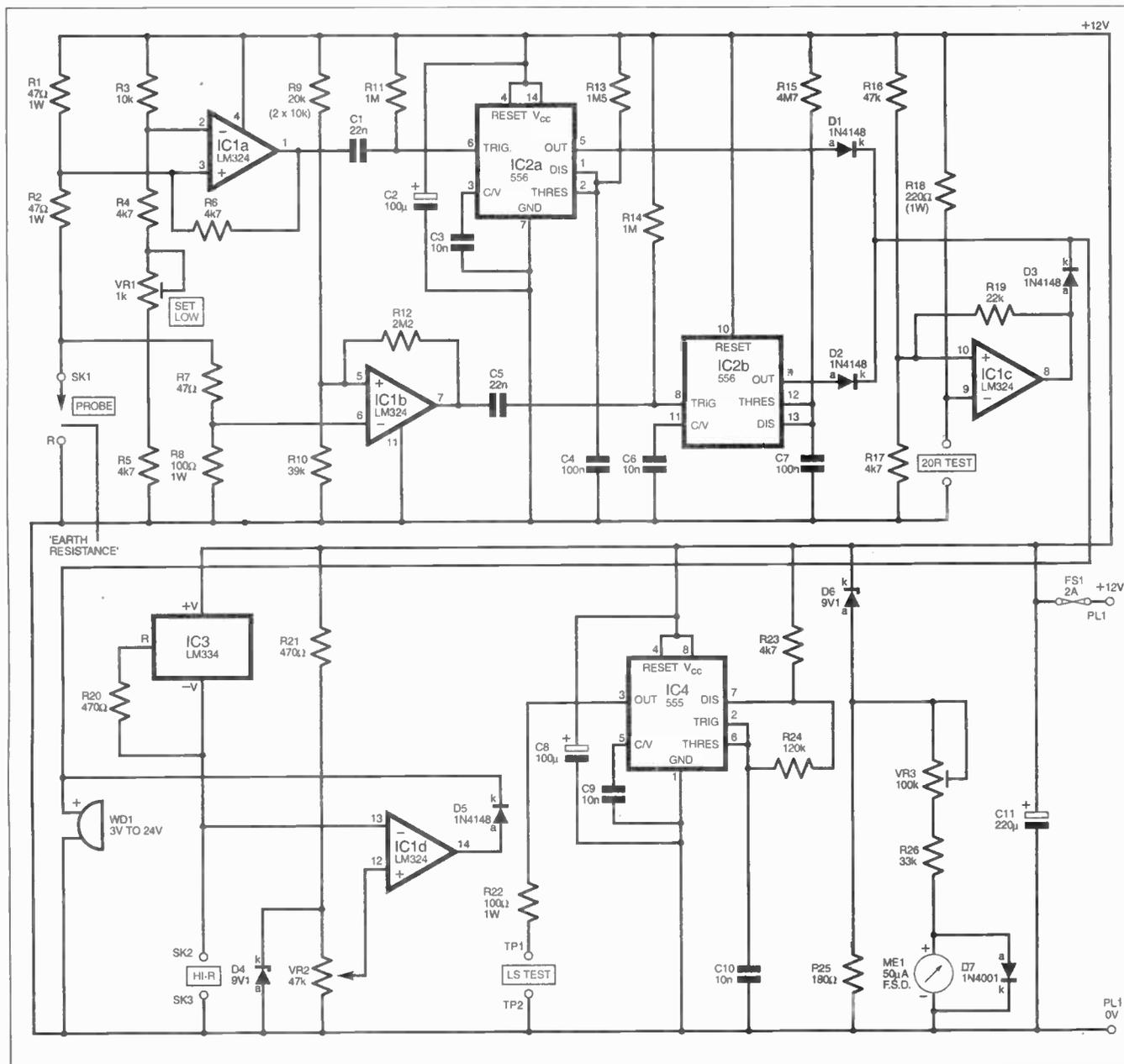


Fig.1. Complete circuit diagram for the Motorists' Buzz-Box. Note that some resistors must be rated at 1W.

GOOD ENOUGH!

When the probe detects a sufficiently "good" (that is, low resistance) earth point, the low logic state of IC1a output (pin 1) applies a short duration low pulse to IC2a pin 6 (the trigger input) via capacitor C1. IC2 is a dual timer with both sections, IC2a and IC2b configured as monostables.

In the case of IC2a, the time period is set by the value of resistor R13 and capacitor C4 and with those used here, it will be rather less than 0.2 second. During this time, the output (pin 5) goes high then reverts to low. While high, current flows through diode D1 to buzzer WD1, which gives a *short* bleep.

Resistor R11 maintains IC2a pin 6 in a high state in the absence of a trigger pulse and this prevents false operation. Resistor R6 applies a little positive feedback to the op.amp (IC1a) system and this sharpens the switching action.

12 VOLT TEST

For the 12V Test, op.amp IC1b (another section of quad op.amp, IC1) and IC2b (the other section of dual timer IC2) are used. It will be noted that the same probe is used for both the "Earth" and "12V" tests and this is particularly convenient when making checks.

The action of the 12V test is best described by considering what voltage exists at IC1b inverting input (pin 6) when the probe is (a) connected to a point at +12V, (b) unconnected and (c) when connected to 0V (that is, while performing an earth test).

In the case of (a), IC1b pin 6 may be considered to be connected to a potential divider having resistors R7 in the upper arm and R8 in the lower one (remembering that the top end of R7 is now connected to +12V). This gives a voltage of 8.16V.

In the case of (b) pin 6 is connected to the potential divider comprising resistors R1, R2 and R7 in series in the upper arm and R8 in the lower one. This provides a voltage of almost 5V. In the case of (c) the top end of R7 and the bottom end of R8 are both connected to 0V so the voltage at pin 6 is zero.

MORE POTENTIAL

The non-inverting input of IC1b is connected to another potential divider comprising resistor R9 in the upper arm and R10 in the lower one. With the values specified, the voltage applied to this input will be 7.93V.

If the probe is touched on a point within about 0.3V of the positive supply voltage, the inverting input voltage will exceed the non-inverting one. The output at pin 7 will then go low. This low state is applied, via capacitor C5, to the trigger input (pin 8) of the monostable based on IC2b.

The time period of this section is related to the values of resistor R15 and capacitor C7, and with those specified it will be 0.5 second approximately. During this time, the output at pin 9 goes high and current passes via diode D2 to the buzzer. This then emits a *long* bleep.

The trigger input at pin 8 of IC2b is maintained in a normally-high state using resistor R14. Resistor R12 provides a little positive feedback to op.amp IC1b and this sharpens the switching action.

COMPONENTS

Approx. Cost
Guidance Only
£15
excluding case & meter

Resistors

R1, R2	47Ω 1W (2 off)
R3	10k
R4 to R6,	
R17, R23	4k7 (5 off)
R7	47Ω
R8, R22	100Ω 1W (2 off)
R9	20k (2 off 10k units – see text).
R10	39k
R11, R14	1M (2 off)
R12	2M2
R13	1M5
R15	4M7
R16	47k
R18	220Ω 1 watt
R19	22k
R20, R21	470Ω (2 off)
R24	120k
R25	180Ω
R26	33k

Plus 0.22W test resistor – see test. Also 10kΩ and 47kΩ test resistors.

All resistors, apart from the 0.22W test resistor, are of the 1% metal film type. Unless otherwise indicated, they should be rated at 0.6W. The 0.22W test resistor may be of any type.

Potentiometers

VR1	1k min. preset, vert.
VR2	47k min. rotary carbon, lin.
VR3	100k min. preset, vert.

Capacitors

C1, C5	22n polyester, 5mm pin spacing (2 off)
C2, C8	100μ radial elect. 25V (2 off)

See
SHOP
TALK
page

C3, C6	
C9, C10	10n polyester, 5mm pin spacing (4 off)
C4, C7	100n polyester, 5mm pin spacing (2 off)
C11	220μ radial elect. 25V

Semiconductors

D1 to D3,	1N4148 signal diode (4 off)
D4, D6	9V1 Zener diode (2 off)
D7	1N4001 50V 1A rect. diode
IC1	LM324N dual op.amp
IC2	556N dual timer
IC3	LM334N adjustable current source
IC4	555 timer

Miscellaneous

ME1	50μA full-scale deflection (f.s.d.), moving coil panel meter – see text
SK1, SK2,	4mm chassis sockets SK3 (3 off) matching plugs (2 off) – see text.
TP1, TP2	small terminal posts (2 off)

Printed circuit board available from the *EPE PCB Service*, code 278; plastic box, size 150mm x 100mm x 60mm external; 8-pin d.i.l. socket; 14-pin d.i.l. socket (2 off); test meter probe to fit SK1; screw terminals (2 off); 5A terminal block (2 sections); 5A flexible twin wire (or ready-made cigar lighter extension lead (PL1)) – see text; materials for test rails; strain relief bush; control knob for VR2; self-adhesive p.c.b. stand-off pillar (2 off); solder etc.

TWENTY OHM TEST

The 20 Ohm Test or "low resistance test" is centred on IC1c, the third section of quad op.amp IC1. The non-inverting input (pin 10) is held at a potential of just over 1V due to the potential divider R16/R17. The inverting input (pin 9) is held at +12V due to resistor R18.

The metal rails on top of the unit form the "20R test" position. When a low-resistance item bridges the rails, this becomes the lower arm of a potential divider with resistor R18 as the upper one.

If the component on test has a resistance less than 22 ohms approximately, the inverting input voltage will fall below that at the non-inverting one. The output at IC1c pin 8 will then go high. The high state will pass, via diode D3, to the buzzer, which will sound.

When the test position is not occupied, the inverting input voltage exceeds the non-inverting one and the output will be low. This state is blocked by diode D3 and has no effect.

Timer IC2 is a robust bipolar device. It needs small-value capacitors connected between the control voltage pins (pin 3 and pin 11) and the 0V line (C3 and C6 respectively). Also, because momentary large current "spikes" occur on the supply rails, capacitor C2 is included to provide a charge reservoir.

In the Earth Test, 12V Test and 20 Ohm Test, both inputs of the op.amp involved

have applied voltages which are derived from potential dividers. These are connected to the same supply lines. Thus, as the supply voltage rises or falls, the voltages at both op.amp inputs will rise or fall in sympathy. It, therefore, does not matter what battery voltage actually exists within operating limits.

TAKING THE LEAD

Ignition leads have a relatively high resistance and this is built into the design to suppress RFI (radio-frequency interference). This would otherwise cause severe noise in the loudspeaker connected to audio equipment and it would even affect radios in nearby cars.

The voltage used in the ignition system is very high (tens of kilovolts) so the relatively high resistance of the leads still enables sufficient current to flow to provide an effective spark at each plug gap.

However, if the resistance rises too much mis-firing occurs. This usually varies with factors such as engine speed and load. If the lead becomes open-circuit, the corresponding cylinder will not fire at all. Any such faults will play havoc with a catalytic converter.

Unfortunately, problems with ignition leads are fairly common so some means of quickly measuring their resistance is useful. This enables the user to check how the resistance of the various leads compare and to determine whether or not they fall within

manufactures' tolerances if this data is available. By "wiggling" the leads as the tests are made, it is possible to check for intermittent faults.

The High Resistance test is centred on IC1d, the fourth section of the quad op.amp. The lead is connected between the inverting input, pin 13, and the 0V line. A fixed current is now passed through it from the adjustable current source device IC3. This is programmed using resistor R20 and with the specified value, will be some 140µA.

With a constant current flowing through the lead, the voltage across its ends will be proportional to its resistance. It turns out that with a resistance of 64kΩ, the voltage across it will be nearly 9V and, of course, with zero ohms it is 0V. With no lead connected, virtually no current flows so IC3 obviously cannot maintain its regulation. However, this is of no consequence.

RESISTANCE TRACKING

Operational amplifier IC1d non-inverting input (pin 12) is connected to the sliding contact of panel-mounted potentiometer VR2. The track is connected in series with fixed resistor R21 across the supply.

Zener diode D4 operates in conjunction with R21 to provide a stable 9.1V (regarded as 9V) across VR2 track despite changes in supply voltage (down to around 9.5V). The difference between these two voltages appears across resistor R21. Since VR2 is a linear device, its angle of rotation will be approximately proportional to the voltage at the sliding contact rising from zero to 9V.

With the ignition lead in "Hi-R" position, VR2 control knob is slowly rotated. At some point, the voltage at the non-inverting input will exceed that at the inverting one. The output at pin 14 of IC1d will then go high and provide a feed to the buzzer WD1 through diode D5.


By adjusting the control knob, the position can be found where the buzzer just sounds. The resistance of the lead may then be read off a scale. Marking the scale 0 to 50kΩ (50 kilohms) is a simple matter and will be carried out at the end.

LOUDSPEAKER TEST

For the Loudspeaker Test a single 555 timer, IC4, is used. This is of the same type as the dual unit used for IC2. However, here it is configured as an astable. Thus, as long as a supply exists, the output at pin 3 of IC4 will provide a continuous train of on-off pulses.

The output from IC4 pin 3 is connected to one of the loudspeaker terminals (TP1), via resistor R22, while the other one (TP2) is connected to 0V. Providing the pulse frequency lies within the audible range, a loudspeaker connected to the terminals will produce a sound. Remembering the description of IC2, capacitor C9 is the control voltage capacitor and C8 provides a charge reservoir.

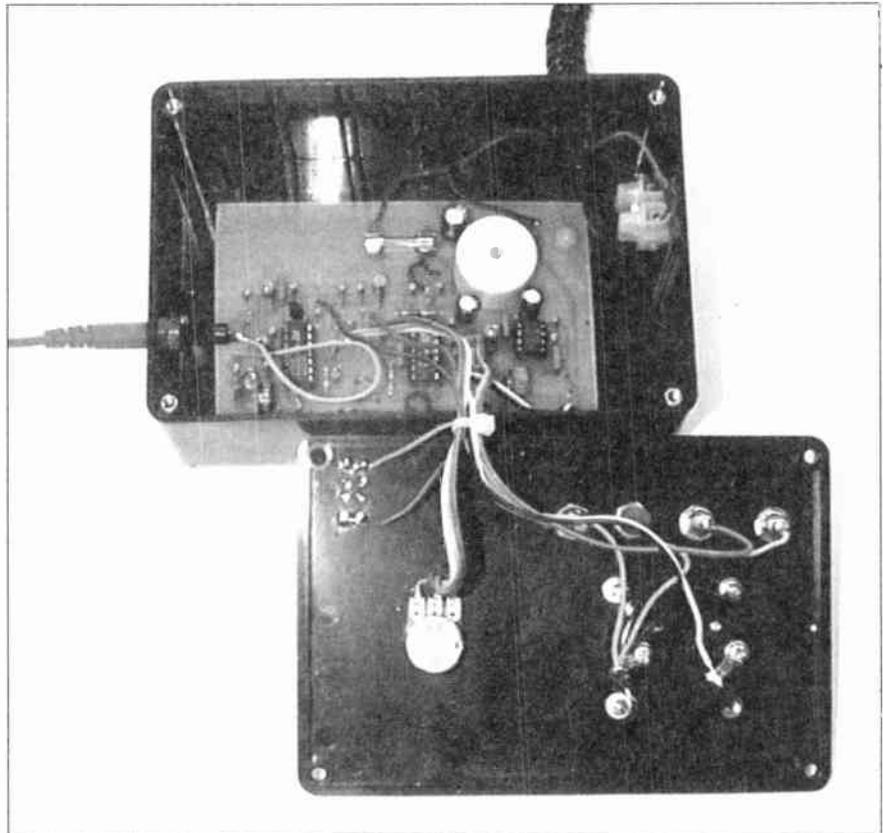The components which determine the pulse frequency are resistors R23, R24 and capacitor C10. Using the specified values, this frequency will be 600Hz approximately. The ears are sensitive to this frequency and the loudspeaker will reproduce the sound well.



Layout of components inside the plastic box and wiring to components mounted on the lid.

Because the signal is a simple square wave, the power has been kept low to prevent possible damage. This is the reason for including resistor R22 in series with the output. This limits the peak current to 120mA or thereabouts.

This is not a precision signal designed to assess the performance of the loudspeaker. It is used simply to find which pair of leads is which and to identify non-working units, loose connections and so on.

VOLTMETER

The read-out of the supply voltage is provided by panel meter ME1. This is scaled 0 to 50µA but it is modified to show a d.c. range voltage from 10V to 14V.

The supply is connected to a 9.1V (regarded as 9V) Zener diode, D6, connected in series with fixed resistor R25. As long as the supply is a little more than the Zener breakdown voltage, the diode will conduct and this voltage will appear across it. The difference between the supply voltage and 9V will then appear across R25.

If the supply voltage is less than the Zener breakdown voltage, the diode will not conduct and therefore the voltage across resistor R25 will be zero. With a supply voltage of 14V (the maximum value in practice), the voltage across R25 will be 5V.

Meter ME1 operates in conjunction with preset potentiometer VR3 and fixed resistor R26 to provide a voltmeter having a full-scale reading of 14V. With an applied voltage less than about 9.5V, it will read zero.

The region between 9V and 10V must be regarded as a "grey area". This depends on exactly when the Zener diode begins to conduct. Also, at the beginning it does not do this sharply.

Values below 10V are therefore not known with any accuracy. At 10V the Zener diode will be behaving as it should and the scale after that will be more-or-less linear (equal changes in voltage producing equal steps on the scale). This is why there is space between the rest position of the pointer and 10V (see photograph).

METER CHOICE

The values of components have been chosen for a meter having a full-scale deflection of 50µA (although a 100µA unit would also work). Preset VR3 will be adjusted to give the correct full-scale reading at the end of construction. The internal resistance of the meter itself will be a few kilohms. However, the exact value does not matter because it is taken into account when VR3 is adjusted.

Diode D7 is connected in parallel with the meter movement as a protection device. Thus, if due to a fault an excessive current would otherwise flow through the meter, the voltage across it would be limited to 0.7V approximately (the forward voltage drop).

Normally, a smaller voltage than this exists across the meter (with the specified device carrying 50µA it is about 0.2V). Under normal conditions, therefore, the diode will have no effect. Under fault conditions, the current will be around 200µA but the meter will probably not be damaged.

CONSTRUCTION

Construction is based on a single-sided printed circuit board (p.c.b.). The topside component layout and full size underside copper track foil master are shown in Fig. 2. This board is available from the EPE PCB Service, code 278.

Begin construction by drilling the two fixing holes then solder the sockets for IC1, IC2 and IC4 in position (but do not insert the i.c.s themselves yet). Solder the fuse clips in place. If these are not available, you could use a small fuse block instead. If necessary, this could be mounted off board and hard-wired to the FS1 points on the p.c.b. later. Solder in position the single link wire, just above IC2 socket.

Add all resistors and the preset potentiometers. Note that some of the fixed resistors *must* have a power rating of one watt minimum. This is because they can become quite warm in prolonged tests.

Although five per cent tolerance would be sufficient for some of the resistors, some must have a tolerance of one per cent. To avoid confusion, one per cent tolerance resistors have therefore been specified throughout.

Resistor R9 must have a value of 20k Ω . It will probably be easier to use two 10k Ω units connected in series. Space has been left for two such resistors on the p.c.b. Note that they are *both* labelled R9 on the component layout, Fig.2.

Solder the capacitors in place. It is essential to place the electrolytic

capacitors – C2, C8 and C11 – with the correct polarity. Solder all diodes in position taking care over their polarity, noting particularly the orientation of Zener diodes (D4 and D6). Add the audible warning device (WD1), taking note of its polarity (which is marked on top).

Next, solder 15cm pieces of light-duty stranded connecting wire to the following points on the p.c.b.: +12V; 0V; ME1 (2 off); VR2 (3 off); Probe; TP1; TP2; HI-R and 20 Ω . By using different coloured wires (pieces of "rainbow" ribbon cable), problems will be avoided later.

Solder IC3 in position (the flat face is towards the left-hand side of the p.c.b.) keeping its end leads at least 5mm in length. Solder it quickly to avoid damage. If necessary, use a simple heat shunt – this may be nothing more than a pair of fine-nose pliers. These are used to grip each lead between the body of the device and the p.c.b. as it is soldered.

BOXING-UP

Begin the boxing-up procedure by making the holes for the meter. Mark out the large one and the small fixing ones using

the template supplied with it. The large hole can be made by drilling a series of small holes around the outline. These are then joined together using a small hacksaw blade. The holes will be covered by the meter face so there is no point in trying to make a perfect job.

Place the p.c.b. in position on the base of the box. Mark through the fixing holes. Remove the p.c.b. and drill these through.

Decide on positions and drill holes for VR2 bush, also for terminals TP1/TP2 (for the loudspeaker test) and sockets SK2/SK3 (for the HI-R test). Place the control knob on the potentiometer spindle and measure how much needs to be cut off. Mark this, remove the knob and cut off the excess using a small hacksaw.

While doing this, hold the spindle (not the potentiometer body) in the vice. *Gripping the body of the device is likely to damage it.* File the cut edge smooth.

Place the potentiometer bush through its hole and secure it loosely. Mark a suitable position for the anti-rotation lug on the inside. Remove the potentiometer again and drill a small hole to be a tight fit with the lug.


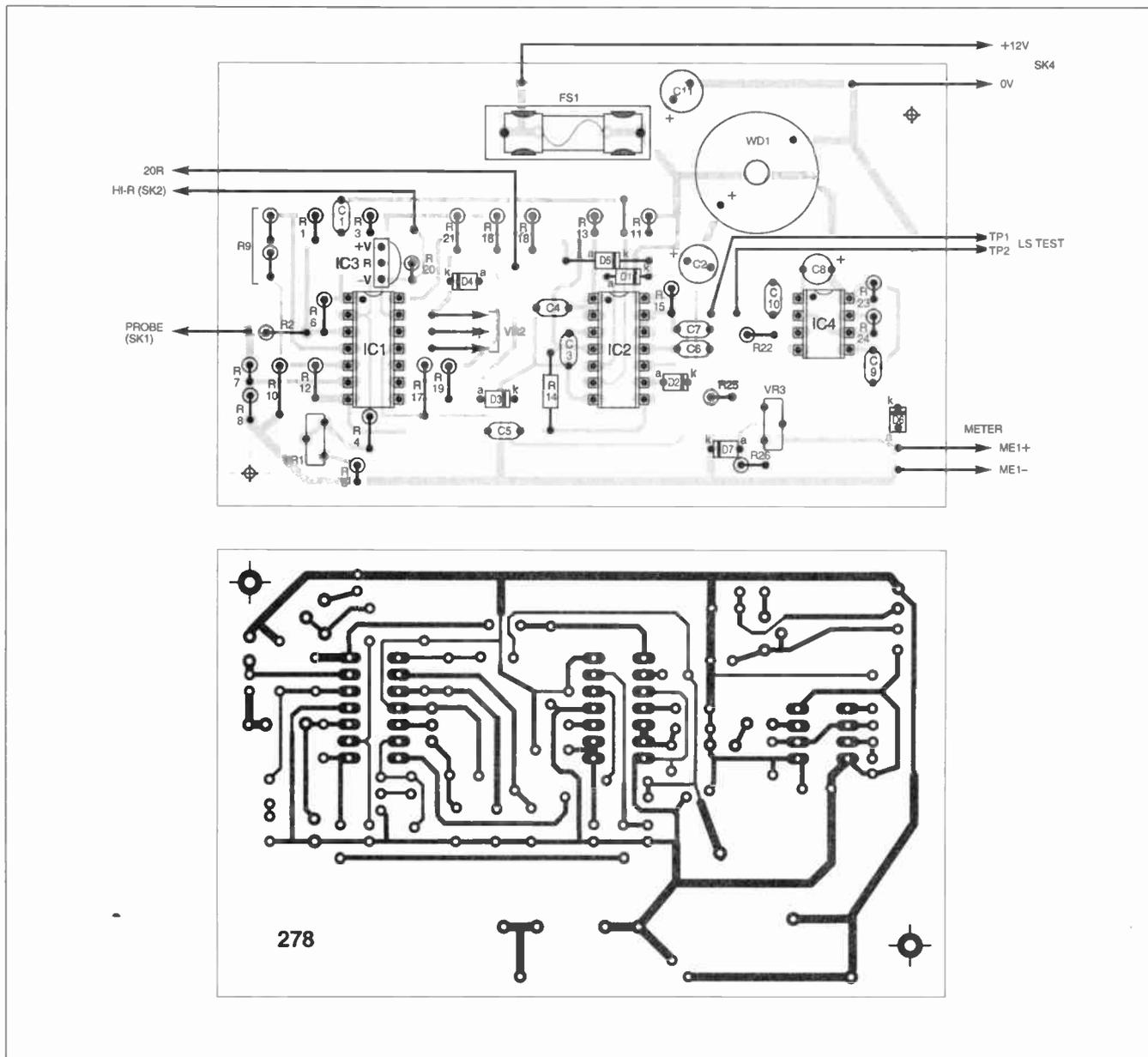


Fig.2. Printed circuit board topside component layout and full-size copper foil master for the Motorists' Buzz-Box.

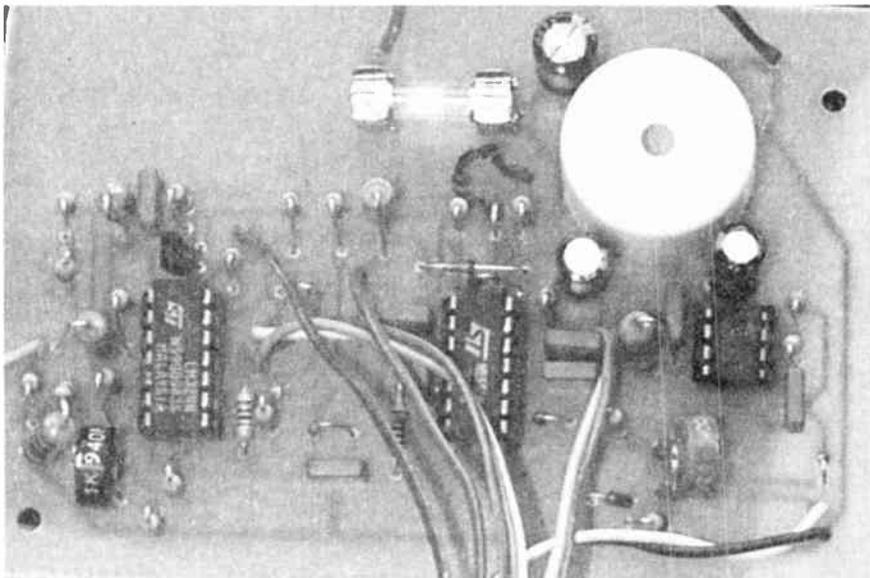


Completed prototype circuit board. Use different coloured wires (rainbow ribbon cable) to ease identification.

Drill the hole for probe the socket, SK1, in one side panel of the box and attach it. Drill a hole in the rear of the box for entry of the input wire. This must be large enough to accommodate the strain relief grommet.

ON THE RAILS

Refer to the photographs and make the test "Rails". In the prototype unit, these were constructed using paper clips which were secured in place using screw terminals of the type shown. This method gives a neat finish and also allows the rail wires to be easily replaced if they become damaged in use.

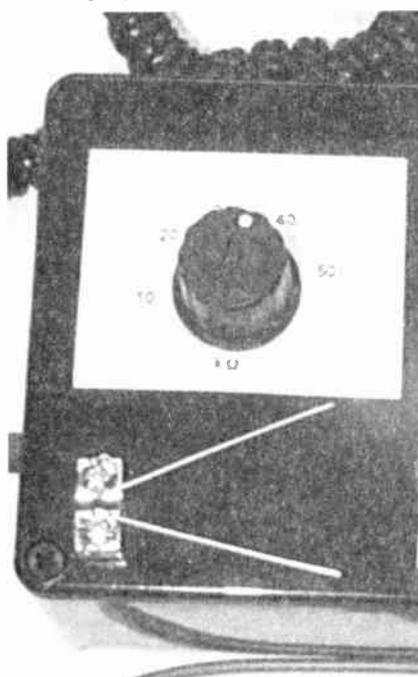The screw terminals used in the prototype were of the p.c.b. mounting type. These had four lugs which were made to be pushed through holes in a panel and soldered into position. However, if tight holes are drilled in the box, the lugs may be pushed through then secured by bending them slightly.



The "test" rails made from paper clips and the cardboard "resistance" scale.

The narrow end of the rails should be only a few millimetres apart (to allow for the testing of small bulbs) and about 35mm apart at the other end to enable testing of 1/4in fuses. The suggested method raises the rails above the top face of the case and this allows for the easy testing of small bulbs.

Attach potentiometer VR2 securely with the anti-rotation lug engaged in its hole. This lug prevents the body from possibly rotating in service (due to harsh use or loosening of the fixing nut). This would

result in incorrect readings and could even snap off the connecting wires. Mount the p.c.b. on short plastic spacers and all remaining components.

Refer to Fig.3 and complete all the interwiring between the p.c.b. and off-board components. This should be done slowly to avoid errors in view of the fact that there are several components involved. Note particularly which wire from the p.c.b. connects to which VR2 tag (the diagram gives a rear view). Only if they are correct will the high resistance (Hi-R) section work properly with clockwise rotation corresponding with increasing resistance.

SUPPLY LEAD

The cable used for the supply voltage input lead *must be rated at 5A minimum*. This will avoid excessive voltage drops due to resistance. In the prototype, a ready-made "curly" extension lead was used with the line socket end cut off.

Fit the 2-core cable wire through the strain relief bush. *Make sure it is secure*. Leaving a little slack, connect the ends to a 2-section piece of screw terminal block mounted inside the case. Connect the p.c.b. wires to this making certain that the polarity is correct.

Adjust preset VR1 fully clockwise (with respect to the left-hand side of the p.c.b.) and preset VR3 to approximately mid-track position.

TESTING

Double-check that the polarity to the circuit is correct before plugging in.

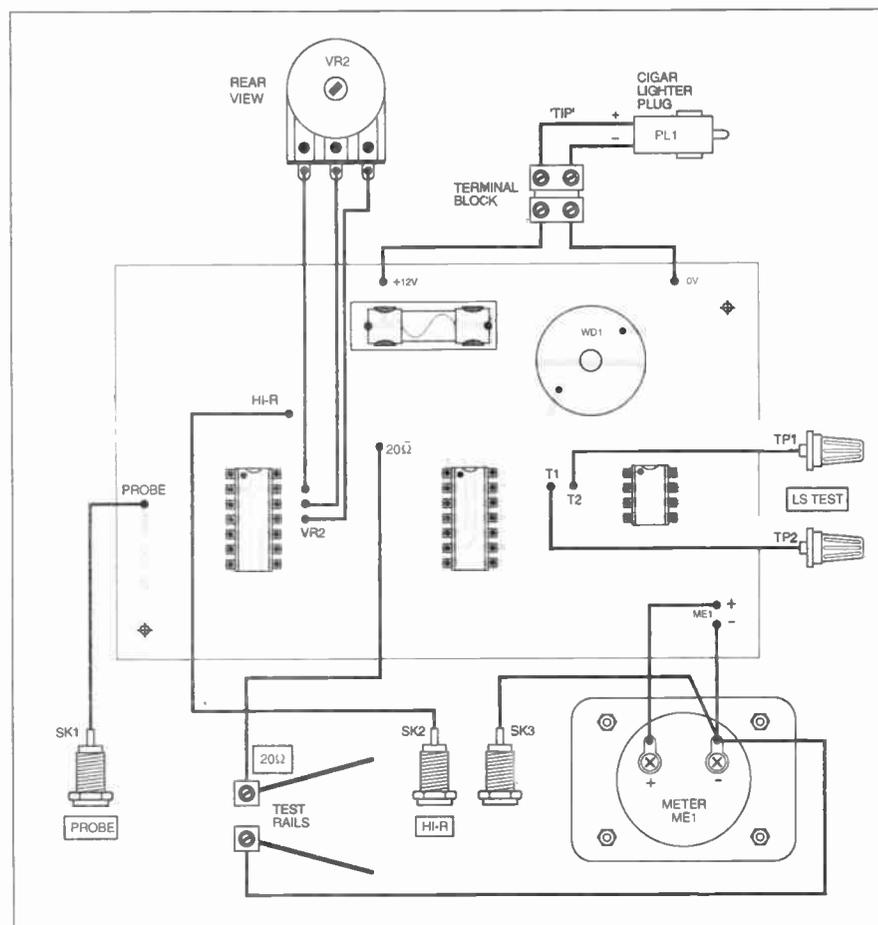


Fig.3. Interwiring from the printed circuit board to off-board components. The general layout within the case can be seen in the photographs.

Connect the unit to the lighter socket. In some cars the ignition must be switched on for this to operate. The monostables will probably self-trigger and the buzzer give a bleep. The meter should read somewhere on the scale. Adjust preset VR3 slightly if necessary.

Plug the probe into socket SK1. Touch this on an "earth" point. The buzzer should give a short bleep. If not, adjust preset VR1 so that it does. Touch the probe on a point at positive supply voltage. The buzzer should give a longer bleep.

Check that the 20Ω test works by bridging the rails with a piece of wire. The buzzer should sound continuously.

METER SCALE

Remove the front cover from the meter by gently pulling or careful levering using a thin knife blade. Exercising great care, remove the scale fixing screws using a small screwdriver. Slide out the scale taking care not to touch the pointer.

Cut out a paper scale to glue on top of the existing one. By pressing them in contact, you will see through sufficiently to mark with a pencil the positions of 10μA, 20μA, 30μA, 40μA and 50μA. Mark these 10V, 11V, 12V, 13V and 14V respectively using dry print lettering. Put a light pencil dot at the zero position.

You can, if you wish, "Tippex" or white-out the old scale (so that it does not show through the paper). Glue the new scale over it and re-assemble the meter. Attach the front taking care that the adjustment peg engages with the fork in the movement.

Check that the pointer rests at the zero dot. If not, adjust the screw on the top face until it does.

MAKING ADJUSTMENTS

Start the adjustment procedure with the Voltmeter. If you have access to a variable voltage power supply unit, you could use that to set VR3 to give a full-scale reading when 14V is applied. You will then find that the other markings correspond fairly well. Adjust preset VR3 to give the best compromise on these figures.

However, if you do not have access to a suitable power supply, plug the unit into the cigar lighter, measure the battery terminal voltage and adjust preset VR3 to correspond. The whole of the scale will then be reasonably accurate.

GOOD OLE' EARTH

To adjust the Earth Test low point, take the 0.22 ohm test resistor (or some other chosen value) and connect the probe to one end of this. Connect the other end to the negative terminal of the battery or a good earth point. Adjust preset VR1 until the buzzer just sounds.

R-SCALE CALIBRATION

Now for potentiometer VR2's front panel "resistance" scale and calibration. Make a thin cardboard scale and secure it temporarily behind the control knob. Pencil in the zero position (knob turned full anti-clockwise).

There is no point in marking the scale with great accuracy. It may be assumed that this is linear – that is, equal increases in resistance correspond with equal steps.



Testing an ignition (plug) lead. The new meter scaling can also be seen here.

Take the 10kΩ test resistor and connect it to the Hi-R test position. Rotate VR2 control knob to the point where the buzzer just sounds. Make a pencil mark. Repeat using the 47kΩ (regarded as 50kΩ) test resistor, again, making a mark.

Remove the scale and, by measurement, make marks for each 10kΩ step from 10 to 50. Mark these permanently. Label the scale "kΩ" then attach the scale in its original position. Check that the "zero" point is still correct.

USING THE BUZZ-BOX

There are several points to observe when using the test probe. *This must be applied with care and with reference to the car wiring diagram. It may be used on items which carry supply current direct to some accessory (e.g. at a fuse, switch or connector) or an earth point. Do not probe around indiscriminately.*

On no account use it inside pieces of electronic equipment. If, for example, it was used inside an electronic control unit severe damage could result to the control unit.

Do not apply it to any connector associated with an engine management system, ABS unit or any other electronic system or sensor. Do not apply it to any wires inter-connecting such circuits.

Do not apply it to points on any diagnostic socket. Do not use it in the engine compartment with the engine running.

When using the loudspeaker test, disconnect both of the wires involved before connecting them to the unit.

CRANK TEST

The unit is not really designed to be used with the engine running except for a "crank test". To do this, watch the voltmeter as the starter motor is operated. If the needle drops immediately below 10V and the battery is known to be well charged, it is likely to be at the end of its useful life.

It would be worth checking the battery connectors (for tightness and lack of corrosion) and the connection of the earth strap to the car chassis since trouble here could produce a similar result. A good battery should be capable of maintaining a voltage of 10V or more for a few seconds until the engine fires.

STATE OF CHARGE

The charge state of the battery is found by measuring the voltage but this needs some interpretation. It will only be meaningful if the battery has not been charged for a few hours before the test is made.

A terminal voltage less than 11.5V indicates a battery which is "flat" (possibly irreversibly so). A voltage of 12.5V or more indicates a good state of charge and near 13V indicates full charge.

Take great care to avoid touching the probe on a +12V point and the car chassis or other earth point at the same time. *If you did, there would be a short circuit and damage could be caused.* In the prototype unit, the end of the probe was insulated using heat-shrinkable sleeving so that only a little bare tip remained. This reduced the likelihood of causing a short circuit.

UP TO YOU

Ignition leads could be connected to the test position in various ways. The method used in the prototype was to solder short pieces of stiff wire to the 4mm plugs. The other ends of the wire were bent into a loop to make contact with the connectors when inserted in the ends of the leads (see photograph).

Several ignition leads were tested and these had a resistance between 5kΩ and 20kΩ. Without specific data, compare the resistances of the leads. If one has a markedly higher value than the rest, it should be replaced and, preferably, the whole set renewed. □

ADD £2.00 P&P to all orders (or 1st Class Recommended E4 Next day (Insured £250) Europe £4.00 Rest of World £5.00). We accept all major credit cards. Make cheques/PO payable to Quasar Electronics. Please include 17.5% VAT. MAIL ORDER ONLY FREE CATALOGUE with order or send 2 x 1st class stamps (refundable) for details of over 150 kits & publications.



PROJECT KITS

Our electronic kits are supplied complete with all components, high quality PCBs (NOT cheap Tripad strip board!) and detailed assembly/operating instructions


- **2 x 25W CAR BOOSTER AMPLIFIER** Connects to the output of an existing car stereo cassette player, CD player or radio. Heatsinks provided PCB 75x75mm 1046KT £27.95
- **3-CHANNEL WIRELESS LIGHT MODULATOR** No electrical connection with amplifier. Light modulation achieved via a sensitive electret microphone. Separate sensitivity control per channel. Power handling 400W/channel. PCB 54x112mm. Mains powered. Box provided 6014KT £27.95
- **12 RUNNING LIGHT EFFECT** Exciting 12 LED light effect ideal for parties, discos, shop-windows, & eye-catching signs. PCB design allows replacement of LEDs with 220V bulbs by inserting 3 TRIACs. Adjustable rotation speed & direction. PCB 54x112mm. 1028KT £17.95; BOX (for mains operation) 2026BX £10.00
- **DISCO STROBE LIGHT** Probably the most exciting of all light effects. Very bright strobe tube. Adjustable strobe frequency 1-60Hz. Mains powered. PCB: 60x68mm. Box provided 6037KT £31.95
- **ANIMAL SOUNDS** Cat, dog, chicken & cow. Ideal for kids farmyard toys & schools. SG10M £6.95
- **1/2 DIGIT LED PANEL METER** Use for basic voltage/current displays or customise to measure temperature, light, weight, movement, sound levels, etc. with appropriate sensors (not supplied). Various input circuit designs provided 3061KT £13.95
- **IR REMOTE TOGGLE SWITCH** Use any TV/VCR remote control unit to switch onboard 12V/1A relay on/off 3058KT £10.95
- **SPEED CONTROLLER** for any common DC motor up to 100V/5A. Pulse width modulation gives maximum torque at all speeds. 5-15VDC. Box provided 3067KT £12.95
- **3 x 8 CHANNEL IR RELAY BOARD** Control eight 12V/1A relays by Infra Red (IR) remote control over a 20m range in sunlight. 6 relays turn on only, the other 2 toggle on/off. 3 operation ranges determined by jumpers. Transmitter case & all components provided. Receiver PCB 76x89mm 3072KT £52.95

PRODUCT FEATURE

4 WATT FM TRANSMITTER

Small but powerful 4 Watt 88-108MHz FM transmitter with an audio preamplifier stage and 3 RF stages. Accepts a wide variety of input sources - the electret microphone supplied, a tape player or for more professional results, a separate audio mixer (like our 3-Input Mono Mixer kit 1052). Can be used with an open dipole or ground plane antenna. Supply: 12-15V DC/0.5A. PCB: 45 x 145mm.

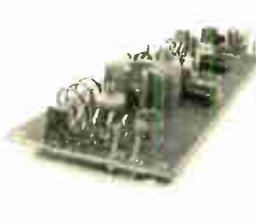ORDERING INFO: Kit 1028KT £24.95.
OPTIONAL EXTRAS: 3-Input Mono Mixer Kit 1052KT £17.95. AS1028 £39.95.



- **SOUND EFFECTS GENERATOR** Easy to build. Create an almost infinite variety of interesting, unique sound effects from birds chirping to sirens. 9VDC. PCB 54x85mm 1045KT £9.95
- **ROBOT VOICE EFFECT** Make your voice sound similar to a robot or Darlek. Great fun for discos, school plays, theatre productions, radio stations & playing jokes on your friends when answering the phone! PCB 42x71mm. 1131KT £9.95
- **AUDIO TO LIGHT MODULATOR** Controls intensity of one or more lights in response to an audio input. Safe, modern opto-coupler design. Mains voltage experience required 3012KT £8.95
- **MUSIC BOX** Activated by light. Plays 8 Christmas songs and 5 other tunes. 3104KT £7.95
- **20 SECOND VOICE RECORDER** Uses non-volatile memory - no battery backup needed. Record/replay messages over & over. Playback as required to greet customers etc. Volume control & built-in mic. 6VDC. PCB 50x73mm 3131KT £12.95
- **TRAIN SOUNDS** 4 selectable sounds: whistle, crossing bell, 'chickety-clack' & 4 in sequence. SG01M £6.95
- **PC CONTROLLED RELAY BOARD** Convert any 286 upward PC into a dedicated automatic controller to independently turn on/off up to eight lights, motors & other devices around the home, office, laboratory or factory using 8 240VAC/12A onboard relays, DOS utilities, sample test program, full-featured Windows utility & all components (except cable) provided 12VDC. PCB 70x200mm 3074KT £31.95
- **2 CHANNEL UHF RELAY SWITCH** Contains the same transmitter/receiver pair as 30A15 below plus the components and PCB to control two 240VAC/10A relays (also supplied). Ultra bright LEDs used to indicate relay status 3082KT £27.95
- **TRANSMITTER RECEIVER PAIR** 2-button keyboard style 300-375MHz Tx with 30m range. Receiver encoder module with matched decoder IC. Components must be built into a circuit like kit 3082 above 30A15 £14.95
- **PC DATA ACQUISITION/CONTROL UNIT** Use your PC to monitor physical variables (e.g. pressure, temperature, light, weight, switch state, movement, relays, etc.), process the information & use results to control physical devices like motors, sirens, relays, servo & stepper motors. Inputs: 16 digital & 11 analogue. Outputs: 8 digital & 1 analogue. Plastic case with printed front/rear panels, software utilities, programming examples & all components (except sensors & cable) provided 12VDC 3093KT £99.95
- **PIC 16C71 FOUR SERVO MOTOR DRIVER** Simultaneously control up to 4 servo motors. Software & all components (except sensors/control pots) supplied 5VDC. PCB 50x70mm 3102KT £15.95
- **PC SERIAL PORT ISOLATED I/O BOARD** Provides eight 240VAC/10A relay outputs & 4 optically isolated inputs. Designed for use in various control & sensing applications. e.g. load switching, external switch input sensing, contact closure & external voltage sensing. Controlled via serial port & a terminal emulator program (built into Windows). Can be used with ANY computer/operating system. Plastic case with printed front/rear panels & all components (except cable) provided 3108KT £54.95
- **UNIPOLAR STEPPER MOTOR DRIVER** for any 5/6/8 lead motor. Fast/slow & single step rates. Direction control & on/off switch. Wave, 2-phase & half-wave step modes. 4 LED indicators. PCB 50x65mm 3109KT £14.95
- **PC CONTROLLED STEPPER MOTOR DRIVER** Control two unipolar stepper motors (3A max each) via PC printer port. Wave, 2-phase & half-wave step modes. Software accepts 4 digital inputs from external switches & will single step motors. PCB fits in D-shell case provided. 3113KT £17.95
- **12-BIT PC DATA ACQUISITION/CONTROL UNIT** Similar to kit 3093 above but uses a 12 bit Analogue-to-Digital Converter (ADC) with internal analogue multiplexer. Reads 8 single ended channels or 4 differential inputs or a mixture of both. Analogue inputs read 0-4V. Four TTL/CMOS compatible digital input/outputs. ADC conversion time <10µs. Software (C, QB & Win), extended D shell case & all components (except sensors & cable) provided 3118KT £52.95

X FACTOR PUBLICATIONS

THE EXPERTS IN RARE & UNUSUAL INFORMATION!

Full details of all X-FACTOR PUBLICATIONS can be found in our catalogue. NB Minimum order charge for reports and plans is £5.00 PLUS normal P&P.

- **SUPER-EAR LISTENING DEVICE** Complete plans to build your own parabolic dish microphone. Listen to distant voices and sounds through open windows and even walls! Made from readily available parts. R002 £3.50
- **TELEPHONE BUG PLANS** Build your own micro-belt telephone bug. Suitable for any phone. Transmits over 250 metres - more with good receiver. Made from easy to obtain cheap components. R006 £2.50
- **LOCKS** - How they work and how to pick them. This fact filled report will teach you more about locks and the art of lock picking than many books we have seen at 4 times the price. Packed with information and illustrations. R008 £4.50
- **RADIO & TV JOKER PLANS** We show you how to build three different circuits for disrupting TV picture and sound plus FM radio! May upset your neighbours & the authorities! DISCRETION REQUIRED! R017 £3.50
- **INFINITY TRANSMITTER PLANS** Complete plans for building the famous Infinity Transmitter. Once installed, on the target phone, device acts like a room bug. Just call the target phone & activate the unit to hear all room sounds. Great for home office security! R019 £3.50
- **THE OTHER BOX CALL INTERCEPTOR PLANS** Grabs telephone calls out of them all! No need to wire a phone bug. Simply place the device near the phone lines to 'wear the conversations taking place! R025 £3.00
- **CASH CREATOR BUSINESS REPORTS** Need ideas for making some cash? Well this could be just what you need! You get 40 reports (approx 800 pages) on floppy disk that give you information on setting up different businesses. You also get valuable reproduction and duplication rights so that you can sell the manuals as you like. R030 £7.50

SURVEILLANCE

High performance surveillance bugs. Room transmitters supplied with sensitive electret microphone & battery holder etc. All transmitters can be received on an ordinary VHF/FM radio between 88-108MHz. Available in Kit Form (KIT) or Assembled & Tested (AST).

ROOM SURVEILLANCE

- **MTX - MINIATURE 3V TRANSMITTER** Easy to build & guaranteed to transmit 300m @ 3V Long battery life. 3-5V operation. Only 45x18mm ● 3007KT £6.95
- **AS3007 £11.95**
- **MRTX - MINIATURE 9V TRANSMITTER** Our best selling bug. Super sensitive high power - 500m range @ 9V (over 1km with 18V supply and better aerial). 45x19mm 3018KT £7.95 AS3018 £12.95
- **HPTX - HIGH POWER TRANSMITTER** High performance 2 stage transmitter gives greater stability & higher quality reception 1000m range @ 12V DC operation. Size 70x15mm 3032KT £9.95
- **AS3032 £18.95**
- **MMTX - MICRO-MINIATURE 9V TRANSMITTER** The ultimate bug for its size, performance and price. Just 15x25mm 500m range @ 9V. Good stability 6-18V operation 3051KT £8.95 AS3051 £14.95
- **VTX - VOICE ACTIVATED TRANSMITTER** Operates only when sounds detected. Low standby current. Variable trigger sensitivity 500m range. Peaking circuit supplied for maximum RF output. On/off switch 6V operation. Only 63x30mm 3028KT £12.95 AS3028 £21.95
- **HARD-WIRED BUG/TWO STATION INTERCOM** Each station has its own amplifier, speaker and mic. Can be set up as either a hard-wired bug or two-station intercom. 10m x 2-core cable supplied 3021KT £15.95 (kit form only)
- **TRVS - TAPE RECORDER VOX SWITCH** Used to automatically operate a tape recorder (not supplied) via its REMOTE socket when sounds are detected. All conversations recorded. Adjustable sensitivity & turn-off delay 115x19mm 3013KT £9.95 AS3013 £21.95

LIQUID LEVEL SENSOR/RAIN ALARM

Will indicate fluid levels or simply the presence of fluid. Relay output to control a pump to add/remove water when it reaches a certain level 1080KT £6.95

● **STEREO VU METER** Shows peak music power using 2 rows of 10 LEDs (mixed green & red) moving bar display. 0-30db. 3089KT £11.95

● **AM RADIO KIT** 1 Tuned Radio Frequency front-end, single chip AM radio IC & 2 stages of audio amplification. All components inc. speaker provided. PCB 92x102mm 3063KT £10.95

● **DRILL SPEED CONTROLLER** Adjust the speed of your electric drill according to the job at hand. Suitable for 240V AC mains powered drills up to 700W power. PCB: 48mm x 65mm. Box provided 6074KT £18.95

● **3 INPUT MONO MIXER** Independent level control for each input and separate bass/treble controls. Input sensitivity 240mV 18V DC. PCB 60mm x 165mm 1052KT £17.95

● **NEGATIVE POSITIVE ION GENERATOR** Standard Cockcroft-Walton multiplier circuit. Mains voltage experience required 3057KT £10.95

● **LED DICE** Classic intro to electronics & circuit analysis. 7 LEDs simulate dice roll, slow down & land on a number at random. 555 IC circuit. 3003KT £9.95

● **STAIRWAY TO HEAVEN** Tests hand-eye co-ordination. Press switch when green segment of LED lights to climb the stairway - miss & start again! Good intro to several basic circuits 3005KT £9.95

● **ROULETTE LED Ball** Spins round the wheel. Slow down & drops into a slot 10 LEDs Good intro to CMOS decade counters & Op-Amps 3006KT £10.95

● **9V XENON BATTERY FLASHER** Transformer circuit steps up 9V battery to flash a 25mm Xenon tube. Adjustable flash rate (0.25-2 Secs) 3022KT £11.95

● **LED FLASHER 1** 5 ultra bright red LEDs flash in 7 selectable patterns 3037MKT £5.95

● **LED FLASHER 2** Similar to above but flash in sequence or randomly. Ideal for model railways 3052MKT £5.95

● **INTRODUCTION TO PIC PROGRAMMING** Learn programming from scratch. Programming hardware, a P16F84 chip and a two-part practical hands-on tutorial series are provided 3081KT £22.95

● **SERIAL PIC PROGRAMMER** for all 818/2840 pin DIP serial programmed PICs. Shareware software supplied. Limited to programming 256 bytes (registration costs £14.95) 3096KT £13.95

● **PICALL SERIAL & PARALLEL PIC PROGRAMMER** for all 818/2840 pin DIP parallel AND serial PICs. Includes fully functional & registered software (DOS, W3.1, W95/98) 3117KT £59.95

● **ATMEL 89C051 PROGRAMMER** Simple-to-use yet powerful programmer for the Atmel 89C1051, 89C2051 & 89C4051 uC's. Programmer does NOT require special software other than a terminal emulator program (built into Windows). Can be used with ANY computer/operating system. 3121KT £24.95

● **3V/1.5V TO 9V BATTERY CONVERTER** Replace expensive 9V batteries with economic 1.5V batteries. IC based circuit steps up 1 or 2 'AA' batteries to give 9V/16mA 3035KT £5.95

TELEPHONE SURVEILLANCE

● **MTTX - MINIATURE TELEPHONE TRANSMITTER** Attaches anywhere to phone line. Transmits only when phone is used. Time your radio and hear both parties. 300m range. Uses line as antenna & power source. 20x45mm 3016KT £8.95 AS3016 £14.95

● **TRT - TELEPHONE RECORDING INTERFACE** Automatically records all conversations. Connects between phone line & tape recorder (not supplied). Operates on either 1.5-2V battery systems. Powered from line. 80x33mm 3033KT £9.95 AS3033 £18.95

● **TPA - TELEPHONE PICK-UP AMPLIFIER/WIRELESS PHONE BUG** Place pickup coil on the phone line or near phone earpiece and hear both sides of the conversation 3055KT £11.95 AS3055 £20.95

● **1 WATT FM TRANSMITTER** Easy to construct. Delivers a crisp clear signal. Two-stage circuit. Kit includes microphone and requires a simple open dipole aerial. 44x30mm PCB 42x55mm 1009KT £14.95

● **4 WATT FM TRANSMITTER** Comprises three RF stages and an audio preamplifier stage. Piezo-electric microphone supplied or you can use a separate preamplifier circuit. Antenna can be an open dipole or Ground Plane. Ideal project for those who wish to get started in the fascinating world of FM broadcasting and want a good basic circuit to experiment with. 12 18VDC PCB 44x146mm 1028KT £24.95 AS1028 £39.95

● **15 WATT FM TRANSMITTER (PRE-ASSEMBLED & TESTED)** Four transistor based stages with Philips BLY 88 in final stage. 15 Watts RF power on the air. 88-108MHz. Accepts open dipole Ground Plane, 5B J or YAGI configuration antennas. 12-18VDC. PCB 70x220mm. SWS meter needed for alignment. 1021KT £74.95

● **SIMILAR TO ABOVE BUT 25W Output.** 1031KT £84.95

● **STABILISED POWER SUPPLY 3-30V/2.5A** Ideal for hobbyist & professional laboratory. Very reliable & versatile design at an extremely reasonable price. Short circuit protection. Variable DC voltages (3-30V). Rated output 2.5 Amps. Large heatsink supplied. You just supply a 24VAC/3A transformer. PCB 55x112mm. Mains operation 1007KT £18.95.

● **STABILISED POWER SUPPLY 2-30V/5A** As kit 1007 above but rated at 5Amp. Requires a 24VAC/5A transformer. 1096KT £32.95.

● **MOTORBIKE ALARM** Uses a reliable vibration sensor (adjustable sensitivity) to detect movement of the bike to trigger the alarm & switch the output relay to which a siren, bikes horn, indicators or other warning device can be attached. Auto-reset. 6 12VDC PCB 57x64mm 1011KT £12.95. Box 2011BX £7.00

● **CAR ALARM SYSTEM** Protect your car from theft. Features vibration sensor, courtesy boot light sensor, door sensor and bonnet/bulb earth switch sensor. Entry/exit delays. Auto reset and adjustable alarm duration. 6 12V DC PCB 47mm x 55mm 1019KT £12.95. Box 2019BX £8.00

● **PIEZO SCREAMER** 110db of ear piercing noise. Fits in bulb with 2 x 35mm piezo elements built into their own resonant cavity. Use as an alarm siren or just for fun! 6-9VDC 3015KT £10.95

● **COMBINATION LOCK** Versatile electronic lock comprising main circuit & separate keypad for remote opening of lock. Relay supplied 3029KT £10.95

● **ULTRASONIC MOVEMENT DETECTOR** Crystal locked detector frequency for stability & reliability. PCB 75x40mm houses all components 4-7m range. Adjustable sensitivity. Output will drive external relays/circuits 9VDC 3049KT £13.95

● **PIR DETECTOR MODULE** 3-lead assembled unit just 25x35mm as used in commercial burglar alarm systems 3076KT £8.95

● **INFRARED SECURITY BEAM** When the invisible IR beam is broken a relay is tripped that can be used to sound a bell or alarm. 25 metre range. Mains rated relays provided 12VDC operation 3130KT £12.95

● **SQUARE WAVE OSCILLATOR** Generates square waves at 6 preset frequencies in factors of 10 from 1Hz-100kHz. Visual output indicator. 5-18VDC. Box provided 3111KT £8.95

● **PC DRIVEN POCKET SAMPLER/DATA LOGGER** Analogue voltage sampler records voltages up to 2V or 20V over periods from milli-seconds to months. Can also be used as a simple digital scope to examine audio & other signals up to about 5kHz. Software & D-shell case provided 3122KT £18.95

● **20 MHz FUNCTION GENERATOR** Square triangular and sine waveform up to 20MHz over 3 ranges using 'coarse' and 'fine' frequency adjust ment controls. Adjustable output from 0.2V p-p A TTL output is also provided for connection to a frequency meter. Uses MAX938 IC. Plastic case with printed front/rear panels & all components provided 7-12VAC 3101KT £69.95

BARGAIN BUY!!

30-in-ONE Electronic Projects Lab

Great introduction to electronics. Ideal for the budding electronics expert! Build a radio, burglar alarm, water detector, Morse code practice circuit, simple computer circuits and much more! NO soldering, tools or previous electronics knowledge required. Circuits can be built and unassembled repeatedly. Comprehensive 68-page manual with explanations, schematics and assembly diagrams. Suitable for age 10+. Excellent for schools. Requires 2 x AA batteries. 10x £14.95 (phone for bulk discounts)




WEB: <http://www.QuasarElectronics.com>
email: epesales@QuasarElectronics.com

Secure Online Ordering Facilities
Full Kit Listing, Descriptions & Photos
Kit Documentation & Software Downloads

www.QuasarElectronics.com

Credit Card Sales: 01279 306504

QUASAR KITS REVIEW

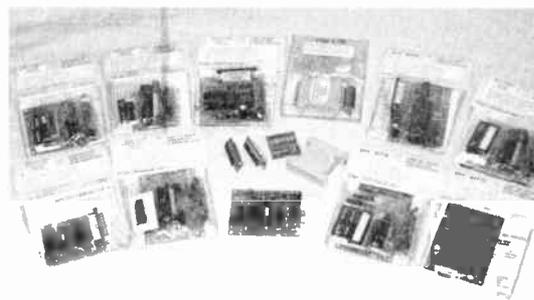

ROBERT PENFOLD

Examining the merits of a dozen electronic kits from Quasar.

WHILE I NORMALLY receive things for review one or two at a time, but no less than a dozen units are under consideration in this review. This is perhaps a slight exaggeration since there are only six different units, but each one has been supplied in kit form and ready-made. All marketed by Quasar Electronics.

It is not practical to consider every device in detail, so we will take a detailed look at one kit and then consider the other units in more general terms. It is kit number 3113, the PC-based dual stepper motor driver that will receive the in-depth coverage.

STEP-BY-STEP

A stepper motor has two centre-tapped coils, effectively giving four solenoids for the driver circuit to control. By pulsing the solenoids in the correct fashion the motor can be made to rotate in either direction in small steps of typically about 15 degrees.

Stepper motors produce little torque, but are used in applications that require precise positioning rather than high power. One way of driving a stepper motor is to use a special integrated circuit to simplify control. With this method there are two control inputs, one of which controls the direction of rotation. The other input is pulsed each time the motor must be moved on by one step.

The more simple method, and the one adopted in this case, is to control the solenoids from four output lines of the computer. Software is then used to generate the appropriate control pulses for whatever actions are required. This slightly complicates the software side of things, but direct control of a stepper motor is not that difficult.

This dual stepper motor interface is basically just eight open collector driver transistors controlled by the data outputs of a PC printer port, plus an MS-DOS program to make the unit operate as a dual stepper motor driver.


The interface takes the form of a small box having a 25-way D-type connector at each end. The male connector plugs into the PC's printer port, or it can be connected via a "straight" 25-way D connector cable (not supplied). Connections to the motors and power source are by way of the female connector at the other end of the case, and the supplied male connector. You have to supply your own connecting wires. The electronics fits on a tiny printed circuit board that fits between the two D connectors.

GETTING IT TOGETHER


Two A4 size sheets contain the building instructions, notes on use, the circuit diagram, etc. Quite a lot of information is crammed onto these two sheets, and it is definitely advisable to read through them once or twice before starting construction.

The fibreglass printed circuit board is a good quality double-sided type that is printed with a component overlay. Construction starts by fitting the two D connectors, and then the 32 small components are added.

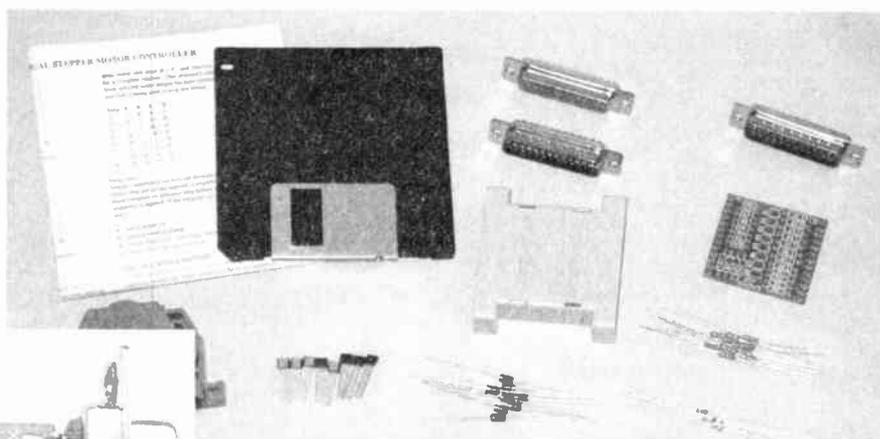There is no problem in identifying the components, and it is fairly obvious where everything fits. One slight problem is that the board is designed to take eight resistors in the form of a 16-pin



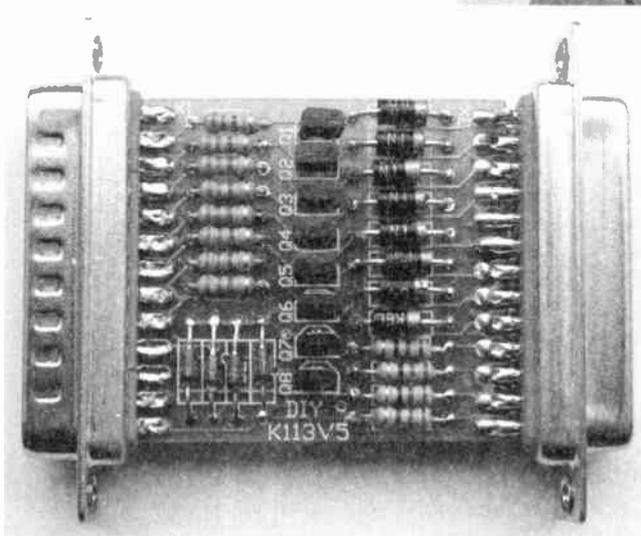The contents of the stepper motor driver kit.



Completed twin stepper motor driver unit.

d.i.l. package, but the kit is supplied with eight individual resistors. However, the instruction sheets do point out this discrepancy, and make it clear where the resistors are fitted. (The p.c.b. has now been redesigned to overcome this - Ed.)

Having some 32 components squeezed into about nine square centimetres makes construction fiddly rather than difficult. The situation is eased somewhat by the solder resist on the board which helps to avoid accidental short circuits. Also, the board is through-plated so there is no need for any pins to carry connections from one layer to the other.

It is still necessary to take reasonable care to avoid short circuits, and a magnifying glass is as essential as a soldering iron when building this type of board.

The instruction sheets give advice about using the interface with various types of stepper motor. It acknowledges the fact that many

of the motors used by electronics hobbyists are surplus components that are supplied with little or no technical data.

Having sorted out some basic information about the motors it is often a matter of using some trial and error to get everything working properly. I tried the interface with an old Maplin stepper motor for which I did still have the connection data, and I am pleased to say that the unit worked first time.

SOFTWARE

The only supplied software is a DOS program on a 3.5-inch floppy disk. This did not work properly when run in a DOS window under Windows 98, but it worked fine when the computer was rebooted in DOS mode, or when the computer was booted into DOS from a floppy disk.

The program provides a command line interpreter that can be used to issue various commands to the motors, such as spin, stop, dir (direction) and wait. The commands seem to work well enough, and the program is easy to use.

It is possible to have the software process a series of commands contained in a text file, rather like running a DOS batch file. This enables what is effectively a simple program to be written and executed, but for many purposes something more sophisticated than this will be needed. It should not be too difficult to control the motor using a Windows programming language such as Delphi or Visual BASIC.

The output port of the interface also provides access to four handshake inputs of the printer port, which makes it possible to have control of the motor to some extent dependent on feedback from sensors. However, you are completely on your own with this type of thing.

CONCLUSION

Although this is a fairly simple kit, it is not really suitable for beginners, and is not aimed at those of limited experience. Constructing the kit is actually quite easy, but a fair amount of technical expertise is needed to get the finished unit do anything worthwhile.

Considering the simplicity of the unit, at a VAT inclusive cost of £17.95 it is not particularly cheap, but the price is reasonable considering the quality of the components. The printed circuit board is as good as any I have seen, and better than most. As the ready-made interface costs some £29.95 including VAT, it seems to be well worthwhile spending half an hour or so building the kit version.

PIC/ATMEL PROGRAMMERS


The other kits and ready-made boards received for review are for programming PIC or ATMEL microcontrollers. The Quasar kits seem to be based on designs that are available on the Internet. The original instruction leaflets were quite brief at just one A4 sheet with printing on one side, but these have now been updated and improved. Further assistance is often available from one or more web sites, as are more recent versions of the software. The latter is shareware, although in some cases the full registered version is supplied in the kit price. In general, the kits seem to be quite easy to put together.

The printed circuit boards are good quality fibreglass boards, but are mostly single-sided types that require some link-wires. The boards have a solder resist layer that helps to avoid short circuits due to excess solder, and this makes it much easier to get things working first time.

Some of the kits have attractively low prices, but bear in mind that all you get is a kit of parts to build the board, together with a floppy disk containing the software. The cable to connect the board to the computer and the mains adapter are optional extras at £4.95 and £5.95 each.

The kit versions of the programmers are supplied with an ordinary 40-pin d.i.l. socket, and a universal ZIF socket costs an additional £15.95. The ZIF socket has to be regarded as an essential buy. Apart from other considerations, many PIC chips will simply not fit an ordinary 40-pin holder with its 0.6-inch row spacing.

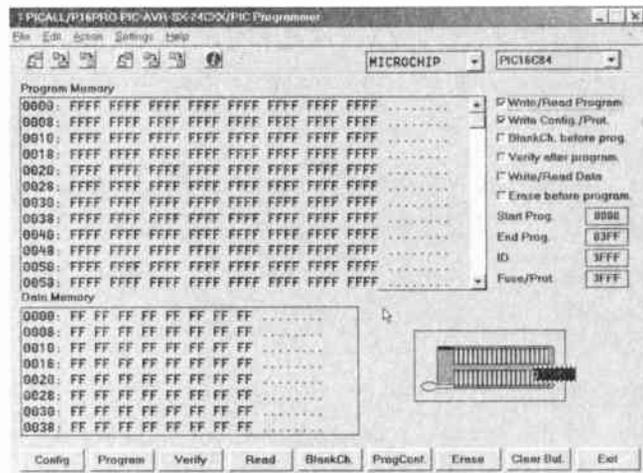As already pointed out, there is also a software registration fee with some kits if the full version is required, and this adds a further £14.95 to the cost. These extras can



Windows version of the PICALL software.

substantially boost the basic kit price, although the overall cost still seems to be reasonable.

The programmers are mostly quite easy to use. The P16PRO serial PIC programmer supports a range of PIC microcontrollers and has MS-DOS software, but it is very simple and straightforward to use. The PICALL programmer supports a wide range of PIC microcontrollers, plus a limited range of non-PIC devices, and has the option of MS-DOS or Windows software. The Windows version of the program is easier to use, but the diagram showing how to connect the selected device to the ZIF socket makes things "as clear as mud". It is best to resort to the MS-DOS version for connection details.


FINAL CONCLUSION

Building any of these kits should not present any major problems for someone who has a small amount of experience at electronic project building. However, none of the kits can really be recommended for beginners, since a fair amount of technical know-how is needed in order to utilize the finished units. For the same reason, the ready-made boards are only suitable for those who know what they are doing.

It is a pity that neither the kits nor the ready-made units are supplied with more documentation as this would substantially broaden their appeal. (This point has now been addressed with new documents plus an electronic manual that is provided with the software - Ed.) As things stand, the kits and ready-made units are of excellent quality, represent reasonably good value for money, and represent a worthwhile proposition for someone having the requisite technical expertise and an Internet connection.

For more information contact Quasar Electronics, Unit 14 Sunningdale, Bishop's Stortford, Herts CM23 2PA. Tel: 01279 306504. Fax: 08707 064222.

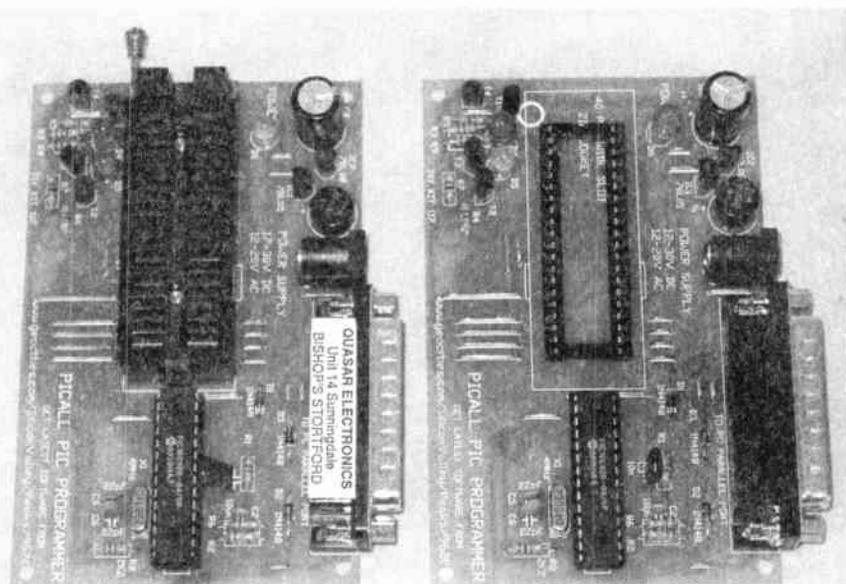
Email: epesales@QuasarElectronics.com.
Web: www.QuasarElectronics.com. □




The ready-made (left) and kit version of the PICALL programmer.

Everyday Practical Electronics are pleased to be able to offer all readers these **ELECTRONICS CD-ROMS**

NEW ELECTRONICS PROJECTS

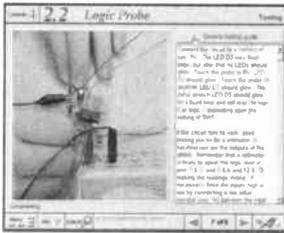

Logic Probe testing

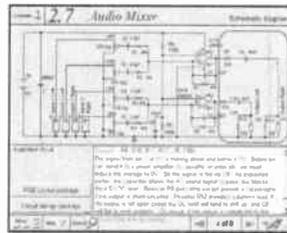


Audio Mixer circuit description


Electronic Projects is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included.

The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.

ANALOGUE ELECTRONICS

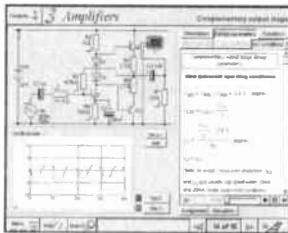

Complimentary output stage

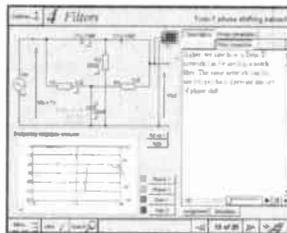


Twin-T phase shifting network


Analogue Electronics is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits.

Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections). **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections). **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections). **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

DIGITAL ELECTRONICS

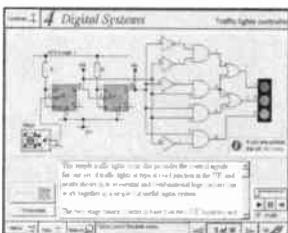

Virtual laboratory – Traffic Lights

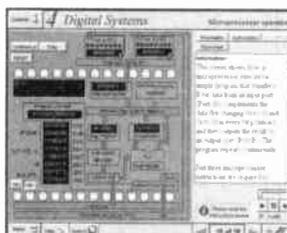


Microprocessor


Digital Electronics builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (opposite), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen.

Covers binary and hexadecimal numbering systems, ASCII, basic logic gates and their operation, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters and their parameters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units.

FILTERS

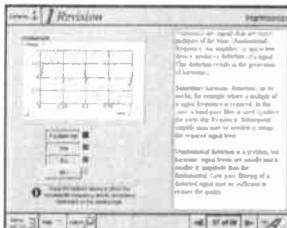


Filter Theory

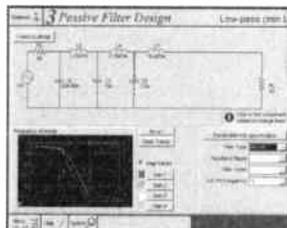


Active filter synthesis

Filters is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev op.amp filters.

DIGITAL WORKS 3.0

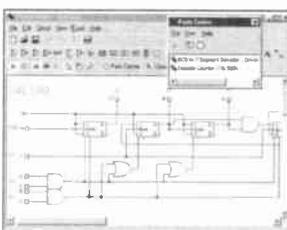

Macro screen

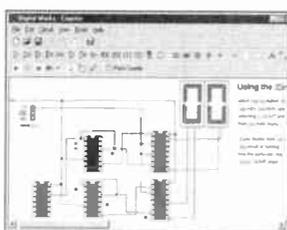

Counter project

Digital Works Version 3.0 is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability.


- Software for simulating digital logic circuits
- Create your own macros – highly scalable
- Create your own circuits, components, and i.c.s
- Easy-to-use digital interface
- Animation brings circuits to life
- Vast library of logic macros and 74 series i.c.s with data sheets
- Powerful tool for designing and learning

PRICES
Prices for each of the CD-ROMs above are:


Hobbyist/Student£45 inc VAT
Institutional (Schools/HE/FE/Industry).....£99 plus VAT
Institutional 10 user (Network Licence)£199 plus VAT

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

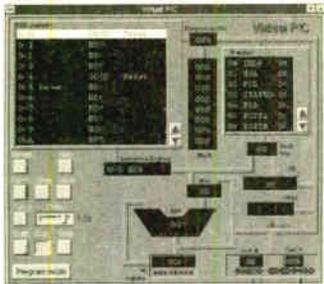Interested in programming PIC microcontrollers? Learn with **PICtutor** by John Becker



The Virtual PIC

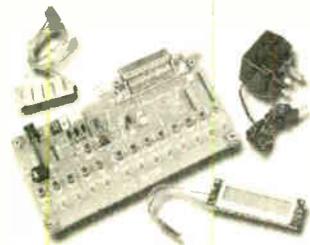

Deluxe PICtutor Hardware

This highly acclaimed CD-ROM, together with the PICtutor experimental and development board, will teach you how to use PIC microcontrollers with special emphasis on the PIC16x84 devices. The board will also act as a development test bed and programmer for future projects as your programming skills develop. This interactive presentation uses the specially developed **Virtual PIC Simulator** to show exactly what is happening as you run, or step through, a program. In this way the CD provides the easiest and best ever introduction to the subject.

Nearly 40 Tutorials cover virtually every aspect of PIC programming in an easy to follow logical sequence.

HARDWARE

Whilst the CD-ROM can be used on its own, the physical demonstration provided by the **PICtutor Development Kit**, plus the ability to program and test your own PIC16x84s, really reinforces the lessons learned. The hardware will also be an invaluable development and programming tool for future work. Two levels of PICtutor hardware are available – Standard and Deluxe. The **Standard** unit comes with a battery holder, a reduced number of switches and no displays. This version will allow users to complete 25 of the 39 Tutorials. The **Deluxe Development Kit** is supplied with a plug-top power supply (the **Export** Version has a battery holder), all switches for both PIC ports plus I.C.D. and 4-digit 7-segment I.E.D. displays. It allows users to program and control all functions and both ports of the PIC. All hardware is supplied **fully built and tested** and includes a PIC16F84.

PICtutor CD-ROM

Hobbyist/Student£45 inc. VAT
 Institutional (Schools/HE/FE Industry) ...£99 plus VAT
 Institutional 10 user (Network Licence) .£199 plus VAT

HARDWARE

Standard PICtutor Development Kit£47 inc. VAT
 Deluxe PICtutor Development Kit£99 plus VAT
 Deluxe Export Version£96 plus VAT

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)



ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 JPG images of electronic components. This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details). Also contains a FREE 30-day evaluation of Paint Shop Pro 6 – Paint Shop Pro image editing tips and on-line help included!

Price **£19.95 inc. VAT**

ELECTRONIC CIRCUITS & COMPONENTS + THE PARTS GALLERY

Provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Sections include: **Fundamentals:** units & multiples, electricity, electric circuits, alternating circuits. **Passive Components:** resistors, capacitors, inductors, transformers. **Semiconductors:** diodes, transistors, op.amps, logic gates. **Passive Circuits . Active Circuits**

The Parts Gallery will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Selections include: **Components, Components Quiz, Symbols, Symbols Quiz, Circuit Technology**

Hobbyist/Student.....£34 inc VAT
 Institutional (Schools/HE/FE/Industry).....£89 plus VAT
 Institutional 10 user (Network Licence).....£169 plus VAT

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

MODULAR CIRCUIT DESIGN

This CD-ROM contains a range of tried and tested analogue and digital circuit modules, together with the knowledge to use and interface them. Thus allowing anyone with a basic understanding of circuit symbols to design and build their own projects.

Essential information for anyone undertaking GCSE or "A" level electronics or technology and for hobbyists who want to get to grips with project design. Over seventy different Input, Processor and Output modules are illustrated and fully described, together with detailed information on construction, fault finding and components, including circuit symbols, pinouts, power supplies, decoupling etc.

Single User Version **£19.95 inc. VAT**

Multiple User Version **£34 plus VAT**

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Minimum system requirements for these CD-ROMs: PC with 486/166MHz, VGA+256 colours, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 95/98, mouse, sound card, web browser.

Please send me:

CD-ROM ORDER FORM

- Electronic Projects
- Analogue Electronics
- Digital Electronics
- Filters
- Digital Works 3.0
- PICtutor
- Electronic Circuits & Components +The Parts Gallery

Version required:

- Hobbyist/Student
- Institutional
- Institutional 10 user

Note: The software on each version is the same, only the licence for use varies.

- PICtutor Development Kit – Standard
- PICtutor Development Kit – Deluxe

Deluxe Export

Note: The PICtutor CD-ROM is not included in the Kit prices.

- Electronic Components Photos
- Modular Circuit Design – Single User
- Modular Circuit Design – Multiple User

Note: The software on each version is the same, only the licence for use varies.

Full name:

Address:

Post code:Tel. No:

Signature:

I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

Please charge my Visa/Mastercard: £Card expiry date:

Card No:

Please supply name and address of cardholder if different to the delivery address.

ORDERING

ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world
 EU residents outside the UK add £5 for airmail postage per order

Institutional, Multiple User and Deluxe Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU country, then add 17½% VAT or provide your official VAT registration number).

Send your order to:

Direct Book Service

Allen House, East Borough, Wimborne Dorset BH21 1PF

Direct Book Service is a division of Wimborne Publishing Ltd. To order by phone ring

01202 881749. Fax: 01202 841692


Goods are normally sent within seven days
 E-mail: orders@epemag.wimborne.co.uk

SMART HIGH QUALITY ELECTRONIC KITS

CAT. NO.	DESCRIPTION	PRICE £
1005	Touch Switch	2.87
1010	5-input stereo mixer with monitor output	
19.31		
1016	Loudspeaker protection unit	3.22
1023	Dynamic head preamp	2.50
1024	Microphone preamplifier	2.07
1025	7 watt hi-fi power amplifier	2.53
1026	Running lights	4.60
1027	NiCad battery charger	3.91
1030	Light dimmer	2.53
1039	Stereo VU meter	4.60
1042	AF generator 250Hz-16kHz	1.70
1043	Loudness stereo unit	3.22
1047	Sound switch	5.29
1048	Electronic thermostat	3.68
1050	3-input hi-fi stereo preamplifier	12.42
1052	3-input mono mixer	6.21
1054	4-input instrument mixer	2.76
1059	Telephone amplifier	4.60
1062	5V 0.5A stabilised supply for TTL	2.30
1064	12V 0.5A stabilised supply	3.22
1067	Stereo VU meter with leads	9.20
1068	18V 0.5A stabilised power supply	2.53
1071	4-input selector	6.90
1080	Liquid level sensor, rain alarm	2.30
1082	Car voltmeter with l.e.d.s	7.36
1083	Video signal amplifier	2.76
1085	DC converter 12V to 6V or 7.5V or 9V	2.53
1093	Windscreen wiper controller	3.68
1094	Home alarm system	12.42
1098	Digital thermometer with l.c.d. display	11.50
1101	Dollar tester	4.60
1102	Stereo VU meter with 14 l.e.d.s	6.67
1106	Thermometer with l.e.d.s	6.90
1107	Electronics to help win the pools	3.68
1112	Loudspeaker protection with delay	4.60
1115	Courtesy light delay	2.07
1118	Time switch with triac 0-10 mins	4.14
1122	Telephone call relay	3.68
1123	Morse code generator	1.84
1126	Microphone preamplifier	4.60
1127	Microphone tone control	4.60
1128a	Power flasher 12V d.c.	2.53
1133	Stereo sound to light	5.26

DO YOU NEED ALL ROUND AIR MOVEMENT?

A simple fan will move air in one direction only. Even an oscillating fan will only blow just over halfway round, but if you need to blow all round, then our boxer fans, Order Ref: 4P114, could give you just this. Six of these placed as the sketch could be operated from our transformer, Order Ref: 4P24. The fans have their own mounting frames and the transformer has a frame so they could all be assembled on a table-top or plywood base, and if you wanted to blow hot air then a heater could also be placed in the centre. We are making a special offer of six fans and the transformer for £20 the lot, including VAT. Order Ref: 20P41.

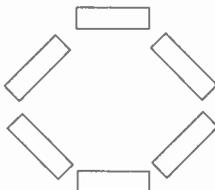

ANOTHER USEFUL FAN

This is a 12V d.c. brushless fan. It is very small, in fact only just under 60mm square including fixings. Being brushless this fan consumes very little current, in fact it is only 150mA. It is very quiet running and we can supply a transformer and full wave rectifier which would operate it for just £1. Price of the fan £5. Order Ref: 5P291.

TWO MORE POST OFFICE INSTRUMENTS

Both instruments contain lots of useful parts, including sub-min toggle switch sold by many at £1 each. They are both in extremely nice cases, with battery compartment and flexible carrying handles so if you don't need the instruments themselves, the case may be just right for a project you have in mind.

The first is Oscillator 87F. This has an output, continuous or interrupted, of 1KHz. It is in a plastic box size 115mm wide, 145mm high and 50mm deep. Price only £1. Order Ref: 7R1.

The other is Amplifier Ref. No. 109G. This is in a case size 80mm wide, 130mm high and 35mm deep. Price £1. Order Ref: 7R2.

HEAVY DUTY POT


Rated at 25W, this is 20 ohm resistance so it could be just right for speed controlling a d.c. motor or device or to control the output of a high current amplifier. Price £1. Order Ref: 1/33L1.

STEPPER MOTOR

Made by Philips as specified for the wind-up torch in the Oct 100 Practical Electronics is still available, price £2. Order Ref: 2P457. Sorry, but the other item which Practical Electronics Shop Talk suggests we might supply is the IF Memory Back-up Capacitor, sorry we have no stocks of this item.

THIS MONTH'S SPECIAL

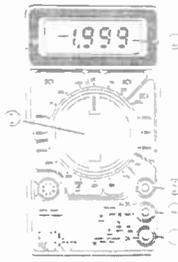IT IS A DIGITAL MULTI-TESTER, complete with backrest to stand it and hands-free test prod holder. This tester measures d.c. volts up to 1,000 and a.c. volts up to 750; d.c. current up to 10A and resistance up to 2 megs. Also tests transistors and diodes and has an internal buzzer for continuity tests. Comes complete with test prods, battery and instructions. Price £6.99. Order Ref: 7P29.



YOUR CHANCE TO BUY SOME POPULAR LINES AT BARGAIN PRICES

250W WOOFER. Made by Challenger, this is 10in. 4 ohm, very high quality make. Our normal price £29, we are reducing to £20, which is almost a third off. Order Ref: 29P7L.

200W WOOFER. Again by Challenger, this is 8in. 4 ohm, our normal price £18 but it is reduced to £14 making it a terrific bargain. Order Ref: 18P81.

9in. PHILIPS MONITOR. In a Metal frame, made for the OPD computer, our normal price £15, now reduced to £12. Order Ref: 15P1L.

100A TIME SWITCH. Ex-electricity board, this is extra useful because it has a mechanism to keep it going should there be a power failure, and although 100A it will operate quite happily on 5A. Regular price £10, now reduced to £8. Order Ref: 10P14L.

MOTORISED DISPLAY. This could control up to 120A of lighting or other equipment. The mains operated motor drives 12 x 10A microswitches, each of which can be set to come on at a different time, so giving running lights or other interesting displays. Regular price £10, reduced to £8. Order Ref: 1P191L.

BRUSH TYPE MAINS MOTOR. Probably 1/4hp but being brush type it is easily speed controllable. Normal price £5, special offer price £4. Order Ref: 5P275L.

SOLAR KITS. To make an old fashioned gramophone which will operate in sunlight or under a light bulb. Normal price £7.50, reduced to £6. Order Ref: 7P16L.

A SIMILAR SOLAR KIT. This one makes a monoplane, again £6. Order Ref: 7P18L.

MOST USEFUL MAINS TRANSFORMER. This is a 12V-0-12V 35W rated, has mounting legs so can stand directly on base panel, price £2.50. Order Ref: 2.5P15.

PROJECT BOX BARGAIN. Colour beige and size approximately 250mm x 130mm wide and 50mm deep. Divides into 2 halves, held together by screws. It has ventilators in the top and bottom corners, but these are quite a decoration and give the box a pleasing look. Price £1. Order Ref: D201.

5A BRIDGE RECTIFIER FOR 12V or 24V CHARGER. With heatsink coupler if used on full current, 2 for £1. Order Ref: 1070.

ENGINEERS BENCH PANEL. This has 2 x 13A mains sockets which are switched and illuminated, thus saving you having to keep pulling out the plugs. Nicely cased, only £2. Order Ref: 2P461.

OVEN THERMOSTAT with knob calibrated so you can set it to cut out at any temperature up to 600 degrees F. Price £3. Order Ref: 3P229.

BUY ONE GET ONE FREE

ULTRASONIC MOVEMENT DETECTOR. Nicely cased, free standing, has internal alarm which can be silenced. Also has connections for external speaker or light. Price £10. Order Ref: 10P154.

CASED POWER SUPPLIES which, with a few small extra components and a bit of modifying, would give 12V at 10A. Originally £9.50 each, now 2 for £9.50. Order Ref: 9.5P4.

3-OCTAVE KEYBOARDS with piano size keys, brand new, previous price £9.50, now 2 for the price of one. Order Ref: 9.5P5.

RECHARGEABLE 12V JELLY ACID BATTERIES.

Yuasa 12V 2.3AH. These are 7in. long, 3in. high and 1 1/2in. wide with robust terminals protruding through the top. Price £3.50. Order Ref: 3.5P11.

DITTO, but 12V 18AH. This is 7in. long, 7in. high and 3in. wide. Brand new with 12 months guarantee, price £12.50 or pack of 4 for £48, including VAT and carriage. Order Ref: 12.5P3.

Note - This battery will start a car and is ideal for golf trolleys, etc.

CHARGER for these batteries and other sealed lead acid batteries, £5. Order Ref: 5P269.

RECHARGEABLE NICAD BATTERIES. AA size, 25p each, which is a real bargain considering many firms charge as much as £2 each. These are in packs of 10, coupled together with an output lead so are a 12V unit but easily divideable into 2 x 6V or 10 x 1.2V. £2.50 per pack, 10 packs for £25 including carriage. Order Ref: 2.5P34.

FOR QUICK HOOK-UPS.

You can't beat leads with a croc clip each end. You can have a set of 10 leads, 2 each of 5 assorted colours with insulated crocodile clips on each end. Lead length 36cm, £2 per set. Order Ref: 2P459.



1mA PANEL METER.

Approximately 80mm x 55mm, front engraved 0-100. Price £1.50 each. Order Ref: 1/16R2.

VERY THIN DRILLS. 12 assorted sizes vary between 0.6mm and 1.6mm. Price £1. Order Ref: 128.

EVEN THINNER DRILLS. 12 that vary between 0.1 and 0.5mm. Price £1. Order Ref: 129.

TWIN TELEPHONE PLUG. Enables you to plug 2 telephones into the one socket for all normal BT plugs. Price £1.50. Order Ref: 1.5P67.

D.C. MOTOR WITH GEARBOX. Size 60mm long, 30mm diameter. Very powerful, operates off any voltage between 6 and 24 D.C. Speed at 6V is 200 rpm, speed controller available. Special price £3 each. Order Ref: 3P108.

MOST USEFUL POWER SUPPLY. Rated at 9V 1A, this plugs into a 13A socket, is really nicely boxed. £2. Order Ref: 2P733.

BT TELEPHONE EXTENSION WIRE. This is proper heavy duty cable for running around the skirting board when you want to make a permanent extension, 4 cores properly colour coded, 25m length. Only £1. Order Ref: 1067.

12V 8A DC POWER SUPPLY. Totally enclosed with its own cooling fan. Normal mains operation. Price £11. Order Ref: 11P6.

TWIN 13A SWITCHED SOCKET. Standard in all respects and complete with fixing screws. White, standard size and suitable for flush mounting or in a surface box. Price £1.50. Order Ref: 1.5P61.

BIG 12V TRANSFORMER. It is 55VA so that is over 4A which is normal working, intermittently it would be a much higher amperage. Beautiful transformer, well made and very well insulated, terminals are in a plastic frame so can't be accidentally touched. Price £3.50. Order Ref: 3.5P20.

RELAYS

We have thousands of relays of various sorts in stock, so if you need anything special give us a ring. A few new ones that have just arrived are special in that they are plug-in and come complete with a special base which enables you to check voltages of connections of it without having to go underneath. We have 6 different types with varying coil voltages and contact arrangements. All contacts are rated at 10A 250V AC.

Coil Voltage	Contacts	Price	Order Ref:
12V DC	4-pole changeover	£2.00	FR10
12V DC	2-pole changeover	£1.50	FR11
24V DC	2-pole changeover	£1.50	FR12
24V DC	4-pole changeover	£2.00	FR13
240V AC	1-pole changeover	£1.50	FR14
240V AC	4-pole changeover	£2.00	FR15

Prices include base
NOT MUCH BIGGER THAN AN OXO CUBE. Another relay just arrived is extra small with a 12V coil and 6A changeover contacts. It is sealed so it can be mounted in any position or on a p.c.b. Price 75p each, 10 for £6 or 100 for £50. Order Ref: FR16.

TERMS

Send cash, PO, cheque or quote credit card number - orders under £25 add £3.50 service charge.

J & N FACTORS
Pilgrim Works (Dept.E.E.)
Stairbridge Lane, Bolney
Sussex RH17 5PA
Telephone: 01444 881965

DIRECT BOOK SERVICE

Circuits and Design



ELECTRONICS TEACH-IN No. 7 ANALOGUE AND DIGITAL ELECTRONICS COURSE

(published by *Everyday Practical Electronics*)

Alan Winstanley and Keith Dye B.Eng(Tech)AMIEE

This highly acclaimed *EPE Teach-In* series, which included the construction and use of the *Mini Lab* and *Micro Lab* test and development units, has been put together in book form.

An interesting and thorough tutorial series aimed specifically at the novice or complete beginner in electronics. The series is designed to support those undertaking either GCSE Electronics or GCE Advanced Levels, and starts with fundamental principles.

If you are taking electronics or technology at school or college, this book is for you. If you just want to learn the basics of electronics or technology you must make sure you see it. *Teach-In No. 7* will be invaluable if you are considering a career in electronics or even if you are already training in one. The *Mini Lab* and software enable the construction and testing of both demonstration and development circuits. These learning aids bring electronics to life in an enjoyable and interesting way; you will both see and hear the electron in action! The *Micro Lab* microprocessor add-on system will appeal to higher level students and those developing microprocessor projects.

160 pages

Order code T17

£3.95

ELECTRONICS PROJECTS USING ELECTRONICS WORKBENCH plus FREE CD-ROM

M. P. Horsey

This book offers a wide range of tested circuit modules which can be used as electronics projects, part of an electronics course, or as a hands-on way of getting better acquainted with Electronics Workbench. With circuits ranging from 'bulbs and batteries' to complex systems using integrated circuits, the projects will appeal to novices, students and practitioners alike.

Electronics Workbench is a highly versatile computer simulation package which enables the user to design, test and modify their circuits before building them, and to plan PCB layouts on-screen. All the circuits in the book are provided as runnable Electronic Workbench files on the enclosed CD-ROM, and a selection of 15 representative circuits can be explored using the free demo version of the application.

Contents: Some basic concepts; Projects with switches, LEDs, relays and diodes; Transistors; Power supplies; Op.amp projects; Further op.amp circuits; Logic gates; Real logic circuits; Logic gate multivibrators; The 555 timer; Flip-flops, counters and shift registers; Adders, comparators and multiplexers; Field effect transistors; Thyristors, triacs and diacs; Constructing your circuit; Index.

227 pages

Order code NE29

£14.99

A BEGINNER'S GUIDE TO MODERN ELECTRONIC COMPONENTS

R. A. Penfold

The purpose of this book is to provide practical information to help the reader sort out the bewildering array of components currently on offer. An advanced knowledge of the theory of electronics is not needed, and this book is not intended to be a course in electronic theory. The main aim is to explain the differences between components of the same basic type (e.g. carbon, carbon film, metal film, and wire-wound resistors) so that the right component for a given application can be selected. A wide range of components are included, with the emphasis firmly on those components that are used a great deal in projects for the home constructor.

170 pages

Order code BP285

£4.99

FREE
CD-ROM

PRACTICAL REMOTE CONTROL PROJECTS

Owen Bishop

Provides a wealth of circuits and circuit modules for use in remote control systems of all kinds; ultrasonic, infra-red, optical fibre, cable and radio. There are instructions for building fourteen novel and practical remote control projects. But this is not all, as each of these projects provides a model for building dozens of other related circuits by simply modifying parts of the design slightly to suit your own requirements. This book tells you how.

Also included are techniques for connecting a PC to a remote control system, the use of a microcontroller in remote control, as exemplified by the BASIC Stamp, and the application of ready-made type-approved 418MHz radio transmitter and receiver modules to remote control systems.

160 pages

Order code BP413

£5.99

DISCOVERING ELECTRONIC CLOCKS

W. D. Phillips

This is a whole book about designing and making electronic clocks. You start by connecting HIGH and LOW logic signals to logic gates. You find out about and then build and test bistables, crystal-controlled astables, counters, decoders and displays. All of these subsystems are carefully explained, with practical work supported by easy to follow prototype board layouts.

Full constructional details, including circuit diagrams and a printed circuit board pattern, are given for a digital electronic clock. The circuit for the First Clock is modified and developed to produce additional designs which include a Big Digit Clock, Binary Clock, Linear Clock, Andrew's Clock (with a semi-analogue display), and a Circles Clock. All of these designs are unusual and distinctive.

This is an ideal resource for project work in GCSE Design and Technology; Electronics Product, and for project work in AS-Level and A-Level Electronics and Technology.

194 pages, A4 spiral bound

Order code DEP1

£16.50

DOMESTIC SECURITY SYSTEMS

A. L. Brown

This book shows you how, with common sense and basic do-it-yourself skills, you can protect your home. It also gives tips and ideas which will help you to maintain and improve your home security, even if you already have an alarm. Every circuit in this book is clearly described and illustrated, and contains components that are easy to source. Advice and guidance are based on the real experience of the author who is an alarm installer, and the designs themselves have been rigorously put to use on some of the most crime-ridden streets in the world.

The designs include all elements, including sensors, -detectors, alarms, controls, lights, video and door entry systems. Chapters cover installation, testing, maintenance and upgrading.

192 pages

Order code NE25

£14.99

MICROCONTROLLER COOKBOOK

Mike James

The practical solutions to real problems shown in this cookbook provide the basis to make PIC and 8051 devices really work. Capabilities of the variants are examined, and ways to enhance these are shown. A survey of common interface devices, and a description of programming models, lead on to a section on development techniques. The cookbook offers an introduction that will allow any user, novice or experienced, to make the most of microcontrollers.

240 pages

Order code NE26

£19.99

A BEGINNER'S GUIDE TO TTL DIGITAL ICs

R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip/flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in the 'real world'.

142 pages

Order code BP332

£4.95

ELECTRONIC MODULES AND SYSTEMS FOR BEGINNERS

Owen Bishop

This book describes over 60 modular electronic circuits, how they work, how to build them, and how to use them. The modules may be wired together to make hundreds of different electronic systems, both analogue and digital. To show the reader how to begin building systems from modules, a selection of over 25 electronic systems are described in detail, covering such widely differing applications as timing, home security, measurement, audio (including a simple radio receiver), games and remote control.

200 pages

Temporarily out of print

PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Bridges the gap between complicated technical theory, and 'cut-and-try' methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias - tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-Current Circuits, Passive Components, Alternating-Current Circuits, Networks and Theorems, Measurements.

256 pages

Order code BP53

£4.99

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order to your door. Full ordering details are given on the last book page.

FOR ANOTHER SELECTION OF BOOKS SEE
THE NEXT TWO MONTHS' ISSUES.

Note our UK postage costs just £2.00 no matter how
many books you order!

Computing & Robotics

WINDOWS 95 EXPLAINED

P. R. M. Oliver and N. Kantaris

If you would like to get up and running, as soon as possible, with the Windows 95 operating system, then this is the book for you.

The book was written with the non-expert, busy person in mind. It explains the hardware that you need in order to run Windows 95 successfully, and how to install and optimize your system's resources. It presents an overview of the Windows 95 environment.

Later chapters cover how to work with programs, folders and documents; how to control Windows 95 and use the many accessories that come with it; how to use DOS programs and, if necessary, DOS commands and how to communicate with the rest of the electronic world.

170 pages

Order code BP400

£5.95

INTRODUCING ROBOTICS WITH LEGO MINDSTORMS

Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various 'click-together' components supplied in the basic RIS kit. Explains in simple terms how the 'brain' of the robot may be programmed on screen using a PC and 'zapped' to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Detailed building and programming instructions provided, including numerous step-by-step photographs.

288 pages - large format

Order code BP901

£12.99

INTRODUCTION TO MICROPROCESSORS

John Crisp

If you are, or soon will be, involved in the use of microprocessors, this practical introduction is essential reading. This book provides a thoroughly readable introduction to microprocessors, assuming no previous knowledge of the subject, nor a technical or mathematical background. It is suitable for students, technicians, engineers and hobbyists, and covers the full range of modern microprocessors.

After a thorough introduction to the subject, ideas are developed progressively in a well-structured format. All technical terms are carefully introduced and subjects which have proved difficult, for example 2's complement, are clearly explained. John Crisp covers the complete range of microprocessors from the popular 4-bit and 8-bit designs to today's super-fast 32-bit and 64-bit versions that power PCs and engine management systems etc.

Contents: The world changed in 1971; Microprocessors don't have ten fingers; More counting; Mathematical micros; It's all a matter of logic; Registers and memories; A microprocessor based system; A typical 8-bit microprocessor; Programming, High level languages; Micros are getting bigger and faster; The Pentium; The PowerPC; The Alpha 21164 microprocessor; Interfacing; Test equipment and fault finding.

222 pages

Order code NE31

£16.99

Theory and Reference

Bebop To The Boolean Boogie

By Clive (call me Max)
Maxfield

ORDER CODE BEB1
£24.95


470 pages. Large format
*Specially imported by EPE –
Excellent value*

An Unconventional Guide to
Electronics Fundamentals,
Components and Processes

This book gives the "big picture" of digital electronics. This indepth, highly readable, up-to-the-minute guide shows you how electronic devices work and how they're made. You'll discover how transistors operate, how printed circuit boards are fabricated, and what the innards of memory ICs look like. You'll also gain a working knowledge of Boolean Algebra and Karnaugh Maps, and understand what Reed-Muller logic is and how it's used. And there's much, MUCH more (including a recipe for a truly great seafood gumbo!).

Hundreds of carefully drawn illustrations clearly show the important points of each topic. The author's tongue-in-cheek British humor makes it a delight to read, but this is a REAL technical book, extremely detailed and accurate. A great reference for your own shelf, and also an ideal gift for a friend or family member who wants to understand what it is you do all day. . . .

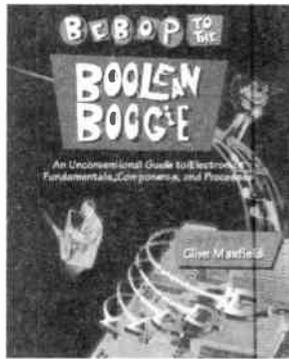470 pages – large format **Order code BEB1** **£24.95**



Bebop Bytes Back

By Clive "Max" Maxfield
and Alvin Brown

ORDER CODE BEB2
£29.95

Over 500 pages. Large
format


*Specially imported by
EPE – Excellent value*

An Unconventional Guide
To Computers

Plus FREE CD-ROM which
includes: Fully Functional
Internet-Ready Virtual
Computer with Interactive
Labs

This follow-on to *Bebop to the Boolean Boogie* is a multimedia extravaganza of information about how computers work. It picks up where "Bebop I" left off, guiding you through the fascinating world of computer design . . . and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the accompanying CD-ROM (for Windows 95 machines only) contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the book contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this one!

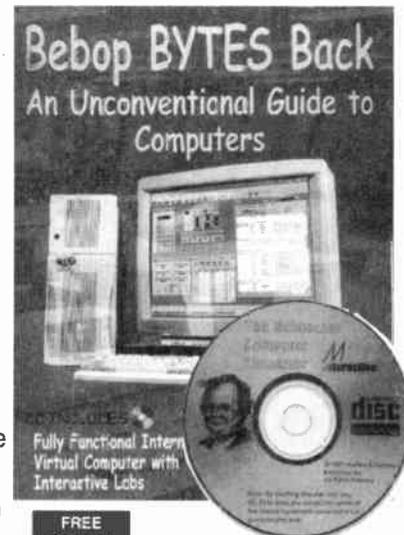Over 500 pages – large format **Order code BEB2** **£29.95**



DIGITAL ELECTRONICS – A PRACTICAL APPROACH
With FREE Software: Number One Systems – EASY-PC
Professional XM and Pulsar (Limited Functionality)

Richard Monk

Covers binary arithmetic, Boolean algebra and logic gates, combination logic, sequential logic including the design and construction of asynchronous and synchronous circuits and register circuits. Together with a considerable practical content plus the additional attraction of its close association with computer-aided design including the FREE software.

There is a 'blow-by-blow' guide to the use of EASY-PC Professional XM (a schematic drawing and printed circuit board design computer package). The guide also conducts the reader through logic circuit simulation using Pulsar software. Chapters on p.c.b. physics and p.c.b. production techniques make the book unique, and with its host of project ideas make it an ideal companion for the integrative assignment and common skills components required by BTEC and the key skills demanded by GNVQ. The principal aim of the book is to provide a straightforward approach to the understanding of digital electronics.

Those who prefer the 'Teach-In' approach or would rather experiment with some simple circuits should find the book's final chapters on printed circuit board production and project ideas especially useful.

250 pages **Order code NE28** **£16.99**

DIGITAL GATES AND FLIP-FLOPS

Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important tripole counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of micro-processor techniques as applied to digital logic.

200 pages **Order code PC106** **£8.95**

FREE
SOFTWARE

NEWNES INTERACTIVE ELECTRONIC CIRCUITS CD-ROM **CD-ROM**
Edited by Owen Bishop

An expert adviser, an encyclopedia, an analytical tool and a source of real design data, all in one CD-ROM. Written by leading electronics experts, the collected wisdom of the electronics world is at your fingertips. The simple and attractive Circuits Environment™ is designed to allow you to find the circuit or advice notes of your choice quickly and easily using the search facility. The text is written by leading experts as if they were explaining the points to you face to face. Over 1,000 circuit diagrams are presented in a standardised form, and you are given the option to analyse them by clicking on the Action icon. The circuit groups covered are: Amplifiers, Oscillators, Power, Sensing, Signal Processing, Filters, Measurement, Timing, Logic Circuits, Telecommunications.

The analysis tool chosen is SpiceAge for Windows, a powerful and intuitive application, a simple version of which automatically bursts into action when selected.

Newnes Interactive Electronic Circuits allows you to: analyse circuits using top simulation program SpiceAge; test your design skills on a selection of problem circuits; clip comments to any page and define bookmarks; modify component values within the circuits; call up and display useful formulae which remain on screen; look up over 100 electronic terms in the glossary; print and export netlists.

System Requirements: PC running Windows 3.x, 95 or NT on a 386 or better processor. 4MB RAM, 8MB disk space.

Order code NE-CD1

Audio and Music

AN INTRODUCTION TO LOUSPEAKERS AND ENCLOSURE DESIGN

V. Capei

This book explores the various features, good points and snags of speaker designs. It examines the whys and wherefores so that the reader can understand the principles involved and so make an informed choice of design, or even design loudspeaker enclosures for him – or herself. Crossover units are also explained, the various types, how they work, the distortions they produce and how to avoid them. Finally there is a step-by-step description of the construction of the Kapellmeister loudspeaker enclosure.

148 pages **Order code BP256** **£3.99**

PREAMPLIFIER AND FILTER CIRCUITS

R. A. Penfold

This book provides circuits and background information for a range of amplifiers, plus tone controls, filters, mixers, etc. The use of modern low noise operational amplifiers and a specialist high performance audio preamplifier i.c. results in circuits that have excellent performance, but which are still quite simple. All the circuits featured can be built at quite low cost (just a few pounds in most cases). The preamplifier circuits featured include: Microphone preamplifiers (low

impedance, high impedance, and crystal). Magnetic cartridge pick-up preamplifiers with R.I.A.A. equalisation. Crystal/ceramic pick-up preamplifier. Guitar pick-up preamplifier. Tape head preamplifier (for use with compact cassette systems).

Other circuits include: Audio limiter to prevent overloading of power amplifiers. Passive tone controls. Active tone controls. PA filters: (highpass and lowpass). Scratch and rumble filters. Loudness filter. Audio mixers. Volume and balance controls.

92 pages **Order code BP309** **£3.99**

HIGH POWER AUDIO AMPLIFIER CONSTRUCTION

R. A. Penfold

Practical construction details of how to build a number of audio power amplifiers ranging from about 50 to 300/400 watts r.m.s. includes MOSFET and bipolar transistor designs.

96 pages **Order code BP277** **£3.99**

ELECTRONIC MUSIC AND MIDI PROJECTS

R. A. Penfold

Whether you wish to save money, boldly go where no

musician has gone before, rekindle the pioneering spirit, or simply have fun building some electronic music gadgets, the designs featured in this book should suit your needs. The projects are all easy to build, and some are so simple that even complete beginners at electronic project construction can tackle them with ease. Stripboard layouts are provided for every project, together with a wiring diagram. The mechanical side of construction has largely been left to the individual constructors to sort out, simply because the vast majority of project builders prefer to do their own thing in this respect.

None of the designs requires the use of any test equipment in order to get them set up properly. Where any setting up is required, the procedures are very straightforward, and they are described in detail.

Projects covered: Simple MIDI tester. Message grabber, Byte grabber, THRU box, MIDI auto switcher, Auto-manual switcher, Manual switcher, MIDI patchbay, MIDI controlled switcher, MIDI lead tester, Program change pedal, Improved program change pedal, Basic mixer, Stereo mixer, Electronic swell pedal, Metronome, Analogue echo unit.

138 pages **Order code PC116** **£9.95**

Testing, Theory, Data and Reference

SCROGGIE'S FOUNDATIONS OF WIRELESS AND ELECTRONICS - ELEVENTH EDITION

S. W. Amos and Roger Amos

Scroggie's Foundations is a classic text for anyone working with electronics, who needs to know the art and craft of the subject. It covers both the theory and practical aspects of a huge range of topics from valve and tube technology, and the application of cathode ray tubes to radar, to digital tape systems and optical recording techniques.

Since *Foundations of Wireless* was first published over 60 years ago, it has helped many thousands of readers to become familiar with the principles of radio and electronics. The original author Sowerby was succeeded by Scroggie in the 1940s, whose name became synonymous with this classic primer for practitioners and students alike. Stan Amos, one of the fathers of modern electronics and the author of many well-known books in the area, took over the revision of this book in the 1980s and it is he, with his son, who have produced this latest version.

400 pages **Order code NE27** £19.99

ELECTRONICS MADE SIMPLE

Ian Sinclair

Assuming no prior knowledge, *Electronics Made Simple* presents an outline of modern electronics with an emphasis on understanding how systems work rather than on details of circuit diagrams and calculations. It is ideal for students on a range of courses in electronics, including GCSE, C&G and GNVQ, and for students of other subjects who will be using electronic instruments and methods.

Contents: waves and pulses, passive components, active components and ICs, linear circuits, block and circuit diagrams, how radio works, disc and tape recording, elements of TV and radar, digital signals, gating and logic circuits, counting and correcting, microprocessors, calculators and computers, miscellaneous systems.

199 pages (large format) **Order code NE23** £12.99

TRANSISTOR DATA TABLES

Hans-Günther Steidle

The tables in this book contain information about the package shape, pin connections and basic electrical data for each of the many thousands of transistors listed. The data includes maximum reverse voltage, forward current and power dissipation, current gain and forward transmittance and resistance, cut-off frequency and details of applications.

A book of this size is of necessity restricted in its scope, and the individual transistor types cannot therefore be described in the sort of detail that maybe found in some larger and considerably more expensive data books. However, the list of manufacturers' addresses will make it easier for the prospective user to obtain further information, if necessary.

Lists over 8,000 different transistors, including f.e.t.s.
200 pages **Order code BP401** £5.95

ELECTRONIC TEST EQUIPMENT HANDBOOK

Steve Money

The principles of operation of the various types of test instrument are explained in simple terms with a minimum of mathematical analysis. The book covers analogue and digital meters, bridges, oscilloscopes, signal generators, counters, timers and frequency measurement. The practical uses of the instruments are also examined.

Everything from Oscillators, through R, C & L measurements (and much more) to Waveform Generators and testing Zeners.

206 pages **Order code PC109** £8.95

GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

96 pages **Order code BP239** £2.95

NEWNES ELECTRONICS TOOLKIT - SECOND EDITION

Geoff Phillips

The author has used his 30 years experience in industry to draw together the basic information that is constantly demanded. Facts, formulae, data and charts are presented to help the engineer when designing, developing, evaluating, fault finding and repairing electronic circuits. The result is this handy workmate volume: a memory aid, tutor and reference source which is recommended to all electronics engineers, students and technicians.

Have you ever wished for a concise and comprehensive guide to electronics concepts and rules of thumb? Have you ever been unable to source a component, or choose between two alternatives for a particular application? How much time do you spend searching for basic facts or manufacturer's specifications? This book is the answer, it covers resistors, capacitors, inductors, semiconductors, logic circuits, EMC, audio, electronics and music, telephones, electronics in lighting, thermal considerations, connections, reference data.

158 pages **Order code NE20** £14.99

PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING

Robin Pain

This is not a book of theory. It is a book of practical tips, hints, and rules of thumb, all of which will equip the reader to tackle any job. You may be an engineer or technician in search of information and guidance, a college student, a hobbyist building a project from a magazine, or simply a keen self-taught amateur who is interested in electronic fault finding but finds books on the subject too mathematical or specialized.

The book covers: Basics - Voltage, current and resistance; Capacitance, inductance and impedance; Diodes and transistors; Op-amps and negative feedback; Fault finding - Analogue fault finding, Digital fault finding; Memory; Binary and hexadecimal; Addressing; Discrete logic; Microprocessor action; I/O control; CRT control; Dynamic RAM; Fault finding digital systems; Dual trace oscilloscope; IC replacement.

274 pages **Order code NE22** £18.99

AN INTRODUCTION TO LIGHT IN ELECTRONICS

F. A. Wilson

This book is not for the expert but neither is it for the completely uninitiated. It is assumed the reader has

some basic knowledge of electronics. After dealing with subjects like Fundamentals, Waves and Particles and The Nature of Light such things as Emitters, Detectors and Displays are discussed. Chapter 7 details four different types of Lasers before concluding with a chapter on Fibre Optics.

161 pages **Order code BP359** £4.95

UNDERSTANDING DIGITAL TECHNOLOGY

F. A. Wilson C.G.I.A., C.Eng., F.I.E.E., F.I. Mgt.

This book examines what digital technology has to offer and then considers its arithmetic and how it can be arranged for making decisions in so many processes. It then looks at the part digital has to play in the ever expanding Information Technology, especially in modern transmission systems and television. It avoids getting deeply involved in mathematics.

Various chapters cover: Digital Arithmetic, Electronic Logic, Conversions between Analogue and Digital Structures, Transmission Systems. Several Appendices explain some of the concepts more fully and a glossary of terms is included.

183 pages **Order code BP376** £4.95

Project Building

ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering; making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby.

135 pages **Order code BP392** £4.95

45 SIMPLE ELECTRONIC TERMINAL BLOCK PROJECTS

R. Bebbington

Contains 45 easy-to-build electronic projects that can be constructed, by an absolute beginner, on terminal blocks using only a screwdriver and other simple hand tools. No soldering is needed.

Most of the projects can be simply screwed together, by following the layout diagrams, in a matter of minutes and readily unscrewed if desired to make new circuits. A theoretical circuit diagram is also included with each project to help broaden the constructor's knowledge.

The projects included in this book cover a wide range of interests under the chapter headings: Connections and Components, Sound and Music, Entertainment, Security Devices, Communication, Test and Measuring.

163 pages **Order code BP378** £4.95

30 SIMPLE IC TERMINAL BLOCK PROJECTS

R. Bebbington

Follow on from BP378 using ICs.

117 pages **Order code BP379** £4.99

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.S.

R. A. Penfold

Deals with the simple methods of copying printed circuit board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.

80 pages **Order code BP121** £3.99

IC555 PROJECTS

E. A. Parr

Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. It was first manufactured by Signetics, but is now manufactured by almost every semiconductor manufacturer in the world and is inexpensive and very easily obtainable.

Included in this book are over 70 circuit diagrams and descriptions covering basic and general circuits, motor car and model railway circuits, alarms and noise makers as well as a section on 556, 558 and 559 timers. (Note. No construction details are given.)

A reference book of invaluable use to all those who have any interest in electronics, be they professional engineers or designers, students of hobbyists.

167 pages **Order code BP44** £3.99

BOOK ORDERING DETAILS

Our postage price is the same no matter how many books you order, just add £2.00 to your total order for postage and packing (overseas readers add £4 for countries in the EEC, or add £7 for all countries outside the EEC, surface mail postage) and send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or credit card details, Visa or Mastercard - minimum credit card order is £5 - to: **DIRECT BOOK SERVICE, ALLEN HOUSE, EAST BOROUGH, WIMBORNE, DORSET BH21 1PF.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery - more for overseas orders. *Please check price and availability (see latest issue of Everyday Practical Electronics) before ordering from old lists.*

For a further selection of books see the next two issues of *EPE*.
DIRECT BOOK SERVICE IS A DIVISION OF WIMBORNE PUBLISHING LTD.

Tel 01202 881749 Fax 01202 841692.

E-mail: dbs@epemag.wimborne.co.uk

BOOK ORDER FORM

Full name:

Address:

.....

.....

..... Post code: Telephone No:

Signature:

I enclose cheque/PO payable to DIRECT BOOK SERVICE for £

Please charge my Visa/Mastercard £ Card expiry date

Card Number

Please send book order codes:

.....

Please continue on separate sheet of paper if necessary

PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749; Fax 01202 841692; E-mail: orders@epemag.wimborne.co.uk.** Cheques should be crossed and made payable to *Everyday Practical Electronics (Payment in £ sterling only).*

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery - overseas readers allow extra if ordered by surface mail. Back numbers or photostats of articles are available if required - see the Back Issues page for details.

Please check price and availability in the latest issue. Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
★ <i>EPE</i> PIC Tutorial	MAR '98	182 £7.99
The Handy Thing (Double-Sided)	183	£6.58
Lighting-Up Reminder	184	£5.90
★ Audio System Remote Controller - PSU Main Board	185	£7.05
	186	£8.29
Simple Metal Detector (Multi-project PCB)	APR '98	932 £3.00
★ RC-Meter	188	£7.66
Security Auto-Light	MAY '98	189 £8.10
Stereo Tone Control plus 20W Stereo Amplifier		
Tone Control	190	£7.78
20W Amplifier	191	£8.58
★ Dice Lott	192	£8.05
<i>EPE</i> Mood Changer	JUNE '98	193 £7.75
★ AT89C2051/1051 Programmer		
Main Board	194	£8.50
Test Board	195	£8.69
★ Reaction Timer Software only		-
★ PIC16x84 Toolkit	JULY '98	196 £6.96
★ Greenhouse Computer Control Board	197	£9.08
PSU Board	198	£8.10
Float Charger	AUG '98	199 £6.59
Lightbulb Saver	202	£3.00
Personal Stereo Amplifier (Multi-project PCB)	SEPT '98	932 £3.00
★ Greenhouse Radio Link	200	£8.32
★ PIC Altimeter	201	£8.15
Voice Processor	OCT '98	203 £7.18
★ Digiserv R/C Expander	204	£7.69
IR Remote Control - Transmitter	205	£3.00
- Receiver	206	£3.50
★ PIC Tape Measure	NOV '98	207 £6.82
Electronic Thermostat - T-Stat	208	£4.00
PhizzyB		£14.95
A - PCB B - CD-ROM C - Prog. Microcontroller	Bee (A)(B)(C)	each
15-Way IR Remote Control	211	£3.00
Switch Matrix	212	£4.00
15-Way Rec/Decoder	209	£4.50
Damp Stat	DEC '98	213 £4.00
Handheld Function Generator	215	£5.16
★ Fading Christmas Lights	216	£3.95
PhizzyB I/O Board (4-section)	JAN '99	210 £7.55
★ <i>EPE</i> Mind PICKler	214	£6.30
PhizzyB I/O Board (4-section)	216	£3.95
Alternative Courtesy Light Controller	217	£6.72
Light Alarm	FEB '99	218 £6.78
★ Wireless Monitoring System Transmitter	219+a	£9.92
Receiver	220+a	£8.56
★ PIC MIDI Sustain Pedal Software only		-
★ Wireless Monitoring System-2 F.M. Trans/Rec Adaptors	MAR '99	219a/220a See Feb '99
★ Time and Date Generator	221	£7.37
Auto Cupboard Light	222	£6.36
Smoke Absorber	223	£5.94
Ironing Board Saver	APR '99	224 £5.15
Voice Record/Playback Module	225	£5.12
Mechanical Radio (pair)	226A&B	£7.40
★ Versatile Event Counter	207	£6.82
PIC Toolkit MK2	MAY '99	227 £8.95
A.M./F.M. Radio Remote Control		
Transmitter	228	£3.00
Receiver	229	£3.20
★ Musical Sundial	JUNE '99	231 £9.51
PC Audio Frequency Meter	232	£8.79
★ <i>EPE</i> Mood PICKler	JULY '99	233 £6.78
12V Battery Tester	234	£6.72
Intruder Deterrent	235	£7.10
L.E.D. Stroboscope (Multi-project PCB)	932	£3.00
Ultrasonic Puncture Finder	AUG '99	236 £5.00
★ 8-Channel Analogue Data Logger	237	£8.88
Buffer Amplifier (Oscillators Pt 2)	238	£6.96
Magnetic Field Detective	239	£6.77
Sound Activated Switch	240	£6.53
Freezer Alarm (Multi-project PCB)	932	£3.00
Child Guard	SEPT '99	241 £7.51
Variable Dual Power Supply	242	£7.64

PROJECT TITLE	Order Code	Cost
Micro Power Supply	OCT '99	243 £3.50
★ Interior Lamp Delay	244	£7.88
Mains Cable Locator (Multi-project PCB)	932	£3.00
Vibralarm	NOV '99	230 £6.93
Demister One-Shot	245	£6.78
★ Ginormous Stopwatch - Part 1		246 £7.82
★ Ginormous Stopwatch - Part 2	DEC '99	
Giant Display	247	£7.85
Serial Port Converter	248	£3.96
Loft Guard	249	£4.44
Scratch Blanker	JAN '00	250 £4.83
Flashing Snowman (Multi-project PCB)	932	£3.00
★ Video Cleaner	FEB '00	251 £5.63
Find It	252	£4.20
★ Teach-In 2000 - Part 4		253 £4.52
High Performance Regenerative Receiver	MAR '00	254, 255 } £5.49
★ <i>EPE</i> Icebreaker - PCB257, programmed PIC16F877 and floppy disc		Set Only £22.99
Parking Warning System		258 £5.08
★ Micro-PICscope	APR '00	259 £4.99
Garage Link - Transmitter		261 } £5.87
Receiver		262 Set
Versatile Mic/Audio Preamplifier	MAY '00	260 £3.33
PIR Light Checker	263	£3.17
★ Multi-Channel Transmission System		
Transmitter	264	} Set £6.34
Receiver	265	
Interface	266	
★ Canute Tide Predictor	JUNE '00	267 £3.05
★ PIC-Gen Frequency Generator/Counter	JULY '00	268 £5.07
Q-Meter	269	£4.36
★ <i>EPE</i> Moodloop	AUG '00	271 £5.47
Quiz Game Indicator	272	£4.52
Handy Amp		273 £4.52
Active Ferrite Loop Aerial	SEPT '00	274 £4.67
★ Remote Control IR Decoder Software only		-
★ PIC Dual-Channel Virtual Scope	OCT '00	275 £5.15
Handclap Switch	NOV '00	270 £3.96
★ PIC Pulsometer Software only		-
Twinkling Star	DEC '00	276 £4.28
Festive Fader	277	£5.71
Motorists' Buzz-Box	278	£5.39
★ PIClogram	279	£4.91
★ PIC-Monitored Dual PSU-1		
PSU	280	£4.75
Monitor Unit	281	£5.23
Static Field Detector (Multi-project PCB)	932	£3.00

EPE SOFTWARE

Software programs for *EPE* projects marked with an asterisk * are available on 3.5 inch PC-compatible disks or free from our Internet site. The following disks are available: *PIC Tutorial* (Mar-May '98 issues); *PIC Toolkit Mk2* (May-Jun '99 issues); *EPE Disk 1* (Apr '95-Dec '98 issues); *EPE Disk 2* (Jan-Dec '99); *EPE Disk 3* (Jan '00 issue to current cover date); *EPE Teach-In 2000*; *EPE Interface Disk 1* (October '00 issue to current cover date). The disks are obtainable from the *EPE PCB Service* at £3.00 each (UK) to cover our admin costs (the software itself is free). Overseas (each): £3.50 surface mail, £4.95 each airmail. All files can be downloaded free from our Internet FTP site: <ftp://ftp.epemag.wimborne.co.uk>.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code Project Quantity Price

Name

Address

I enclose payment of £..... (cheque/PO in £ sterling only) to:

Everyday Practical Electronics
 MasterCard or Visa No.
 Minimum order for credit cards £5

Signature..... Card Exp. Date.....

Please supply name and address of cardholder if different from the address shown

NOTE: You can also order p.c.b.s by phone, Fax, E-mail or via our Internet site on a secure server:

Pages	Issue	Pages	Issue
1-80	January	481-560	July
81-152	February	561-640	August
153-232	March	641-712	September
233-320	April	713-792	October
3211-400	May	793-8722	November
401-480	June	873-952	December

CONSTRUCTIONAL PROJECTS

ACTIVE FERRITE LOOP AERIAL <i>by Raymond Haigh</i>	672	METER, g-	504
AERIAL, ACTIVE FERRITE LOOP	672	METER, LOW-COST CAPACITANCE	344
ALARM, FRIDGE/FREEZER	764	MIC/AUDIO PREAMPLIFIER, VERSATILE	332
ALARM, OPTO-, SYSTEM	820	MICRO-PICSCOPE <i>by John Becker</i>	274
AMP, HANDY	572	MONITOR, VOLTAGE	102
ATMOSPHERIC ELECTRICITY DETECTOR <i>by Keith Garwell</i>	412, 546	MOODLOOP FIELD STRENGTH INDICATOR, EPE	781
AUDIO PREAMPLIFIER, VERSATILE MIC/	332	MOODLOOP POWER SUPPLY, EPE	682
AUTOMATIC NIGHTLIGHT <i>by Robert Penfold</i>	430	MOODLOOP, EPE	602
AUTOMATIC TRAIN SIGNAL <i>by Robert Penfold</i>	188	MOTORISTS' BUZZ-BOX <i>by Terry de Vaux-Balbirnie</i>	930
BLANKER, SCRATCH	38	MULTI-CHANNEL TRANSMISSION SYSTEM <i>by Andy Flind</i>	360, 464
BURGLAR ALARM, VERSATILE	22	NIGHTLIGHT, AUTOMATIC	430
BUZZ-BOX, MOTORISTS'	930	OPTO-ALARM SYSTEM <i>by Stephen Spencer</i>	820
CAMERA SHUTTER TIMER <i>by Robert Penfold</i>	492	PARKING WARNING SYSTEM <i>by Tom Webb</i>	164
CANUTE TIDE PREDICTOR <i>by John Becker</i>	440	PERFORMANCE REGENERATIVE RECEIVER, HIGH	174, 300
CAPACITANCE METER, LOW-COST	344	PIC DUAL-CHAN VIRTUAL SCOPE <i>by John Becker</i>	752
CHECKER, PIR LIGHT	374	PIC-GEN FREQUENCY GENERATOR/COUNTER <i>by John Becker</i>	515
CHRISTMAS BUBBLE <i>by Owen Bishop</i>	(Dec '00 Supp. 5)	PIC-MONITORED DUAL PSU Part 1 <i>by John Becker</i>	884
CHRISTMAS TREE LIGHTS FADER	(Dec '00 Supp. 7)	PIC PULSOMETER <i>by Richard Hinckley</i>	828
CLEANER, PIC VIDEO	114	PICSCOPE, MICRO-	274
CONTROL, IR DECODER, REMOTE	698	PICTOGRAM <i>by Andy Flind</i>	(Dec '00 Supp. 13)
CONTROLLER, EASY-TYPIST TAPE	92	PIC TOOLKIT MK2 UPDATE V2.4 <i>by John Becker</i>	838
COUNTER, PIC-GEN FREQUENCY GENERATOR/	515	PIC VIDEO CLEANER <i>by Mike Delaney</i>	114
DECODER, REMOTE CONTROL IR	698	PIR LIGHT CHECKER <i>by Terry de Vaux-Balbirnie</i>	374
DETECTOR, ATMOSPHERIC ELECTRICITY	412, 546	POWER SUPPLY, EPE MOODLOOP	682
DETECTOR, STATIC FIELD	894	POWER SUPPLY UNIT, PIC-MONITORED DUAL	884
DON'T LOSE IT!, FIND IT	140	PREAMPLIFIER, VERSATILE MIC/ AUDIO	332
DOOR PROTECTOR <i>by Owen Bishop</i>	624	PREDICTOR, CANUTE TIDE	440
DUAL-CHAN VIRTUAL SCOPE, PIC	752	PROTECTOR, DOOR	624
EASY-TYPIST TAPE CONTROLLER <i>by Andy Flind</i>	92	PULSOMETER, PIC	828
ELECTRICITY DETECTOR, ATMOSPHERIC	412, 546	QUIZ GAME INDICATOR <i>by Max Horsey and Tom Webb</i>	598
EPE ICEBREAKER <i>by Mark Stuart</i>	193	RECEIVER, HIGH PERFORMANCE REGENERATIVE	174, 300
EPE MOODLOOP <i>by Andy Flind</i>	602	REGENERATIVE RECEIVER, HIGH PERFORMANCE	174, 300
EPE MOODLOOP FIELD STRENGTH INDICATOR <i>by Andy Flind</i>	781	REMOTE CONTROL IR DECODER <i>by Roger Thomas</i>	698
EPE MOODLOOP POWER SUPPLY <i>by Andy Flind</i>	682	SAMPLE-AND-HOLD <i>by Owen Bishop</i>	804
FERRITE LOOP AERIAL, ACTIVE	672	SCOPE, PIC DUAL-CHAN VIRTUAL	752
FESTIVE FADER <i>by Steve Dellow</i>	(Dec '00 Supp. 7)	SCRATCH BLANKER <i>by Robert Penfold</i>	38
FIELD DETECTOR, STATIC	894	SHUTTER TIMER, CAMERA	492
FIELD STRENGTH INDICATOR, EPE MOODLOOP	781	SIGNAL, AUTOMATIC TRAIN	188
FIND IT - DON'T LOSE IT! <i>by Terry de Vaux-Balbirnie</i>	140	SLAVE, FLASH	246
FLASH SLAVE <i>by Robert Penfold</i>	246	SNOWMAN, FLASHING	12
FLASHING SNOWMAN <i>by Robert Penfold</i>	12	STAR, TWINKLING	(Dec '00 Supp. 1)
FREQUENCY GENERATOR/COUNTER, PIC-GEN	515	STATIC FIELD DETECTOR <i>by Robert Penfold</i>	894
FRIDGE/FREEZER ALARM <i>by Owen Bishop</i>	764	STEEPLECHASE GAME <i>by Owen Bishop</i>	652
FROST BOX, VEHICLE	66	SWITCH, HANDCLAP	864
g-METER <i>by Bill Mooney</i>	504	SYSTEM, MULTI-CHANNEL TRANSMISSION	360, 464
GAME INDICATOR, QUIZ	598	SYSTEM, PARKING WARNING	164
GAME, STEEPLCHASE	652	TAPE CONTROLLER, EASY-TYPIST	92
GARAGE LINK <i>by Terry de Vaux-Balbirnie</i>	255	TIDE PREDICTOR, CANUTE	440
GENERATOR/COUNTER, PIC-GEN FREQUENCY	515	TIMER, CAMERA SHUTTER	492
HANDCLAP SWITCH <i>by Tom Webb</i>	864	TOOLKIT MK2 UPDATE V2.4, PIC	838
HANDY-AMP <i>by Terry de Vaux-Balbirnie</i>	572	TORCH, WIND-UP	724
HIGH PERFORMANCE REGENERATIVE RECEIVER <i>by Raymond Haigh</i>	174, 300	TRAIN SIGNAL, AUTOMATIC	188
ICEBREAKER, EPE	193	TRANSMISSION SYSTEM, MULTI-CHANNEL	360, 464
INDICATOR, EPE MOODLOOP FIELD STRENGTH	781	TWINKLING STAR <i>by Bart Trepak</i>	(Dec '00 Supp. 1)
INDICATOR, QUIZ GAME	598	VEHICLE FROST BOX <i>by Steve Dellow</i>	66
IR DECODER, REMOTE CONTROL	698	VERSATILE BURGLAR ALARM <i>by Ian March</i>	22
L.E.D. FLASHER, PICTOGRAM	(Dec '00 Supp. 13)	VERSATILE MIC/AUDIO PREAMPLIFIER <i>by Raymond Haigh</i>	332
LIGHT CHECKER, PIR	374	VIDEO CLEANER, PIC	114
LIGHT, AUTOMATIC NIGHT	430	VIRTUAL SCOPE, PIC DUAL-CHAN	752
LINK, GARAGE	255	VOLTAGE MONITOR <i>by Robert Penfold</i>	102
LOOP AERIAL, ACTIVE FERRITE	672	WARNING SYSTEM, PARKING	164
LOSE IT!, FIND IT - DON'T	140	WIND-UP TORCH <i>by Thomas Scarborough</i>	724
LOW-COST CAPACITANCE METER <i>by Robert Penfold</i>	344		

GENERAL FEATURES

CAVE ELECTRONICS <i>by Mike Bedford</i>	610	QUASAR KITS REVIEW <i>by Robert Penfold</i>	938
PEAK ATLAS COMPONENT ANALYSER REVIEW <i>by Andy Flind</i>	770	TELCAN HOME VIDEO <i>by Barrie Blake-Coleman</i>	314
PIC LOGICATOR REVIEW <i>by Robert Penfold</i>	858	TINA PRO REVIEW <i>by Mike Tooley BA</i>	54
PICO DrDAQ REVIEWED <i>by Robert Penfold</i>	526		

SPECIAL SERIES

<p>CIRCUIT SURGERY by Alan Winstanley and Ian Bell 75, 122, 219, 306, 380, 470, 502, 617, 686, 747, 814, 908</p> <p>Assault and Ni-Cad Battery 687</p> <p>Battery Flattery 382</p> <p>Beginner's Questions 686</p> <p>Biased Approach 306</p> <p>Bistable Switches 122</p> <p>Checking the Chips 502</p> <p>Circuit Breakers 814</p> <p>Common Ground 686</p> <p>Conventional Current Flow 221</p> <p>Down with Heavy Metal 687</p> <p>Earthy Feelings 748</p> <p>Fault Finding 470</p> <p>Ferric Disposal 687</p> <p>Gas Gauge Chips 687</p> <p>Get Wise about Piecewise and Lambda 617</p> <p>Hot Regulator 220</p> <p>Keep Soldering On 747</p> <p>Low Voltage Detector 503</p> <p>More on Op.amps – Electrical Ratings 76</p> <p>Noise Source 123</p> <p>Op.amp Differentials 219</p> <p>Op.amps – Getting Loaded 306</p> <p>Op.amps – Outputs and short-circuit protection 380</p> <p>Op.amps – Signal Handling 123</p> <p>P.C.B. track widths 815</p> <p>RAM your Batteries 687</p> <p>Royer Converter 908</p> <p>Shocking Stuff 686</p> <p>Socket to Me 307</p> <p>Surface-Mount Selection 308</p> <p>Switched Mode Supplies 908</p> <p>Teach-In Amplifiers 75</p> <p>Testing transistors the quick and easy way 747</p> <p>INTERFACE by Robert Penfold 120, 272, 424, 630, 734, 926</p> <p>Bidirectional Printer Ports 272</p> <p>Digital and Analogue Temperature PC Interface 734</p> <p>Extended Temperature PC Interface Software 926</p> <p>Four-Range Resistance Meter PC Interface 630</p> <p>Obtaining power from a PC's serial and parallel ports 424</p> <p>12-Bit serial ADC using the AD7896 120</p> <p>INGENUITY UNLIMITED hosted by Alan Winstanley 61, 143, 201, 280, 342, 422, 523, 582, 678, 766, 810, 902</p> <p>Air-Flow Detector 423</p> <p>Anti-Tamper Loop Alarm 766</p> <p>Auditory Illusion 343</p> <p>Bidirectional Printer Port 202</p> <p>Brushless Fan Speed Control 283</p> <p>Car Wash-Wipe Latch 902</p> <p>Clock Detector 423</p> <p>Colour TV Tester Add-On 768</p> <p>Cool Controller 582</p> <p>Delay-On Timer 201</p> <p>Doorbell Extension and Entry/Exit Indicator 767</p> <p>Electric Garage Door Status Indicator 62</p> <p>Experimenter's Power Supply 343</p> <p>Infra-red Remote Tester 342</p> <p>Loudener 678</p>	<p>Low Cost AA to PP3 Converter 61</p> <p>Macrovision Blanker 811</p> <p>Mini Disc Optical Interface 143</p> <p>Mini Photo Slave Flash 768</p> <p>Missed Call Indicator 903</p> <p>Multi-Purpose A.C. Detector/Switch 523</p> <p>Musical Chip Amplifier 524</p> <p>Narrow SCSI Active Terminator 525</p> <p>Omnidirectional Pendulum 281</p> <p>Paper, Stone, Scissors Game 903</p> <p>PC Controlled D.C. Motor 280</p> <p>PIC Adaptor Socket 201</p> <p>PIC UPS 678</p> <p>PICO Prize Winners 423</p> <p>Radio Sleep Timer 679</p> <p>Scissors, Paper, Stone Game 903</p> <p>'Scope Synchroniser 679</p> <p>Sensitive Hall Effect Switch 342</p> <p>Shaky Dice 202</p> <p>Single-Phase Power Regulator 810</p> <p>Square Wave Circuit 583</p> <p>Stone, Paper, Scissors Game 903</p> <p>VCO Generator 143</p> <p>Versatile Car Interior Light Delay 524</p> <p>Voltage Booster 422</p> <p>VOM Continuity Buzzer 583</p> <p>555 Power Supply 201</p> <p>PRACTICALLY SPEAKING by Robert Penfold 58, 227, 390, 510, 694</p> <p>Front panel labels for projects 510</p> <p>Mains power projects 58</p> <p>Project building 694</p> <p>Resistors and potentiometers 227</p> <p>Using stripboard 390</p> <p>SCHMITT TRIGGERS by Anthony H. Smith 842, 913</p> <p>1. Bipolar Transistor triggers 842</p> <p>2. Op.Amp and Comparator triggers 913</p> <p>TEACH-IN 2000 by John Becker 30, 128, 206, 290, 384, 465, 534, 584, 662, 736</p> <p>3 – Potentiometers, Sensor Resistors, Ohm's Law 30</p> <p>4 – Diodes and L.E.D.s 128</p> <p>5 – Waveforms, Frequency and Time 206</p> <p>6 – Logic Gates, Binary and Hex Logic 290</p> <p>7 – Op.amps 384</p> <p>8 – Comparators, Mixers, Audio and Sensor Amplifier 465</p> <p>9 – Transistors 534</p> <p>10 – Transformers and Rectifiers 584</p> <p>11 – Voltage Regulation, Integration, Differentiation 662</p> <p>12 – 7-Segment Displays, L.C.D.s, Digital-to-Analogue, Miscellany 736</p> <p>TECHNOLOGY TIMELINES by Clive "Max" Maxfield and Alvin Brown 106, 182, 266, 350, 434</p> <p>1 – Days of Yore 106</p> <p>2 – Days of Later Yore, plus Fundamental 20th Century Electronics 182</p> <p>3 – Communications and Related Technologies 1900 – 1999 266</p> <p>4 – Computing – 1900 to 2000 350</p> <p>5 – Crystal Balls! 434</p>
---	--

REGULAR FEATURES

<p>EDITORIAL 11, 91, 163, 245, 331, 411, 491, 571, 661, 723, 803, 883</p> <p>NET WORK – THE INTERNET PAGE surf'd by Alan Winstanley 28, 148, 214, 264, 348, 428, 512, 592, 702, 774, 841, 929</p> <p>NEW TECHNOLOGY UPDATE by Ian Poole 16, 96, 168, 252, 358, 426, 530, 580, 660, 744, 812, 924</p>	<p>NEWS – plus reports by Barry Fox 19, 99, 171, 249, 339, 419, 499, 578, 655, 730, 807, 892</p> <p>READOUT addressed by John Becker 49, 105, 179, 285, 369, 449, 549, 622, 658, 761, 817, 905</p> <p>SHOPTALK with David Barrington 15, 136, 202, 283, 382, 468, 521, 627, 688, 728, 854</p>
---	--

SPECIAL OFFERS AND SERVICES

<p>ADVERTISERS INDEX 80,192, 232, 320, 480, 400, 560, 640, 712, 792, 872, 952</p> <p>BACK ISSUES Some now on CD-ROM 26, 146, 222, 262, 366, 462, 544, 595, 696, 776, 856, 899</p> <p>CD-ROMS FOR ELECTRONICS 52, 126, 254, 288, 372, 452, 532, 620, 692, 772, 852, 940</p> <p>CHRISTMAS PROJECTS SUPPLEMENT (Dec '00) between pages 912/913</p> <p>DIRECT BOOK SERVICE 72, 144, 223, 310, 394, 474, 551, 634, 704, 785, 861, 943</p>	<p>ELECTRONICS MANUALS 64, 138, 216, 304, 392, 472, 554, 628, 670, 778, 850, 922</p> <p>ELECTRONICS VIDEOS 70, 147, 226, 313, 368, 469, 556, 594, 690, 746, 806, 949</p> <p>PRINTED CIRCUIT BOARD AND SOFTWARE SERVICE 77, 149, 229, 308, 397, 477, 557, 637, 709, 788, 868, 946</p> <p>GIANT TECHNOLOGY TIMELINES CHART between pages 360/361</p> <p>GIANT TRANSISTOR DATA CHART between pages 832/833</p>
---	--

VIDEOS ON ELECTRONICS

A range of videos selected by *EPE* and designed to provide instruction on electronics theory. Each video gives a sound introduction and grounding in a specialised area of the subject. The tapes make learning both easier and more enjoyable than pure textbook or magazine study. They have proved particularly useful in schools, colleges, training departments and electronics clubs as well as to general hobbyists and those following distance learning courses etc



BASICS

VT201 to VT206 is a basic electronics course and is designed to be used as a complete series, if required.

VT201 54 minutes. Part One; D.C. Circuits. This video is an absolute must for the beginner. Series circuits, parallel circuits, Ohms law, how to use the digital multimeter and much more.


Order Code VT201

VT202 62 minutes. Part Two; A.C. Circuits. This is your next step in understanding the basics of electronics. You will learn about how coils, transformers, capacitors, etc are used in common circuits.

Order Code VT202

VT203 57 minutes. Part Three; Semiconductors. Gives you an exciting look into the world of semiconductors. With basic semiconductor theory. Plus 15 different semiconductor devices explained.

Order Code VT203

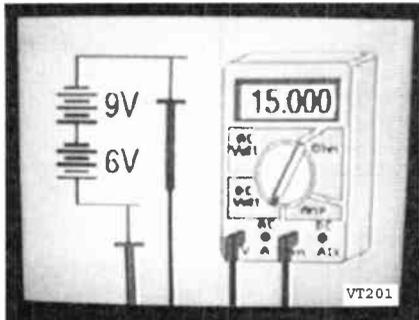

VT204 56 minutes. Part Four; Power Supplies. Guides you step-by-step through different sections of a power supply.

Order Code VT204

VT205 57 minutes. Part Five; Amplifiers. Shows you how amplifiers work as you have never seen them before. Class A, class B, class C, op.amps. etc.

Order Code VT205

VT206 54 minutes. Part Six; Oscillators. Oscillators are found in both linear and digital circuits. Gives a good basic background in oscillator circuits.

Order Code VT206

£34.95 each
inc. VAT & postage

Order 8 or more get one extra FREE
Order 16 get two extra FREE

VCR MAINTENANCE

VT102 84 minutes: Introduction to VCR Repair. Warning, not for the beginner. Through the use of block diagrams this video will take you through the various circuits found in the NTSC VHS system. You will follow the signal from the input to the audio/video heads then from the heads back to the output.

Order Code VT102

VT103 35 minutes: A step-by-step easy to follow procedure for professionally cleaning the tape path and replacing many of the belts in most VHS VCR's. The viewer will also become familiar with the various parts found in the tape path.

Order Code VT103

DIGITAL

Now for the digital series of six videos. This series is designed to provide a good grounding in digital and computer technology.

VT301 54 minutes. Digital One; Gates begins with the basics as you learn about seven of the most common gates which are used in almost every digital circuit, plus Binary notation.

Order Code VT301

VT302 55 minutes. Digital Two; Flip Flops will further enhance your knowledge of digital basics. You will learn about Octal and Hexadecimal notation groups, flip-flops, counters, etc.

Order Code VT302

VT303 54 minutes. Digital Three; Registers and Displays is your next step in obtaining a solid understanding of the basic circuits found in today's digital designs. Gets into multiplexers, registers, display devices, etc.

Order Code VT303

VT304 59 minutes. Digital Four; DAC and ADC shows you how the computer is able to communicate with the real world. You will learn about digital-to-analogue and analogue-to-digital converter circuits.

Order Code VT304

VT305 56 minutes. Digital Five; Memory Devices introduces you to the technology used in many of today's memory devices. You will learn all about ROM devices and then proceed into PROM, EPROM, EEPROM, SRAM, DRAM, and MBM devices.

Order Code VT305

VT306 56 minutes. Digital Six; The CPU gives you a thorough understanding in the basics of the central processing unit and the input/output circuits used to make the system work.

Order Code VT306


RADIO

VT401 61 minutes. A.M. Radio Theory. The most complete video ever produced on a.m. radio. Begins with the basics of a.m. transmission and proceeds to the five major stages of a.m. reception. Learn how the signal is detected, converted and reproduced. Also covers the Motorola C-QUAM a.m. stereo system.

Order Code VT401

VT402 58 minutes. F.M. Radio Part 1. F.M. basics including the functional blocks of a receiver. Plus r.f. amplifier, mixer oscillator, i.f. amplifier, limiter and f.m. decoder stages of a typical f.m. receiver.

Order Code VT402

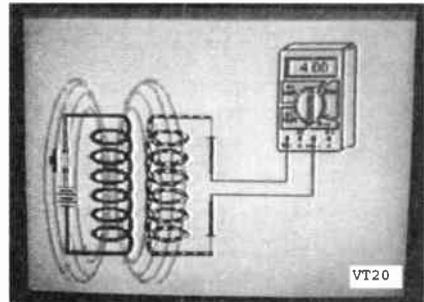

VT403 58 minutes. F.M. Radio Part 2. A continuation of f.m. technology from Part 1. Begins with the detector stage output, proceeds to the 19kHz amplifier, frequency doubler, stereo demultiplexer and audio amplifier stages. Also covers RDS digital data encoding and decoding.

Order Code VT403


MISCELLANEOUS

VT501 58 minutes. Fibre Optics. From the fundamentals of fibre optic technology through cable manufacture to connectors, transmitters and receivers.

Order Code VT501

VT502 57 minutes. Laser Technology A basic introduction covering some of the common uses of laser devices, plus the operation of the Ruby Rod laser, HeNe laser, CO₂ gas laser and semiconductor laser devices. Also covers the basics of CD and bar code scanning.

Order Code VT502

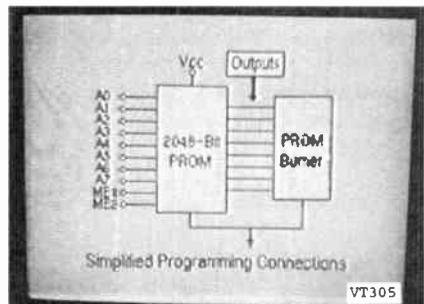

Each video uses a mixture of animated current flow in circuits plus text, plus cartoon instruction etc., and a very full commentary to get the points across. The tapes are imported by us and originate from VCR Educational Products Co, an American supplier. We are the worldwide distributors of the PAL and SECAM versions of these tapes. (All videos are to the UK PAL standard on VHS tapes unless you specifically request SECAM versions.)

ORDERING: Price includes postage to anywhere in the world.

OVERSEAS ORDERS: We use the VAT portion of the price to pay for *airmail* postage and packing, wherever you live in the world. Just send £34.95 per tape. All payments in £ sterling only (send cheque or money order drawn on a UK bank). Make cheques payable to Direct Book Service.

Visa and Mastercard orders accepted – please give card number, card expiry date and cardholder's address if different from the delivery address.

Orders are normally sent within seven days but please allow a maximum of 28 days, longer for overseas orders.

Send your order to: Direct Book Service, Allen House, East Borough, Wimborne, Dorset BH21 1PF

Direct Book Service is a division of Wimborne Publishing Ltd., Publishers of *EPE*
Tel: 01202 881749. Fax: 01202 841692

Due to the cost we cannot reply to overseas orders or queries by Fax.

E-mail: dbs@epemag.wimborne.co.uk

Everyday Practical Electronics reaches twice as many UK readers as any other UK monthly hobby electronics magazine, our audited sales figures prove it. We have been the leading independent monthly magazine in this market for the last fifteen years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. VAT must be added. Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, Mill Lodge, Mill Lane, Thorpe-le-Soken, Essex CO16 0ED. Phone/Fax (01255) 861161.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

Valve Output Transformers: Single ended 50mA, £4.50; push/pull 15W, £27; 30W, £32; 50W, £38; 100W, £53. Mains Transformers: Sec 220V 30mA 6V 1A, £3; 250V 60mA 6V 2A, £5; 250V 80mA 6V 2A, £6. High Voltage Caps: 50µF 350V, 68µF 500V, 150µF 385V, 330µF 400V, 470µF 385V, all £3 ea., 32+32µF 450V £5. Postage extra.
Record Decks and Spares: BSR, Garrard, Goldring, motors, arms, wheels, headshells, spindles, etc. Send or phone your want list for quote.

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON
SURREY, CR0 2HS. Tel: (020) 8684 1666
Lots of transformers, high volt caps, valves, output transformers, speakers, in stock. Phone or send your wants list for quote.

Z88 NOW AVAILABLE WITH
128K AND 512K - OZ4

**ALSO SPECTRUM
AND QL PARTS**

W. N. RICHARDSON & CO.
PHONE/FAX 01494 8713196
RAVENSMEAD, CHALFONT ST PETER,
BUCKS, SL9 0NB

TIS - Midlinbank Farm
Ryeland, Strathaven ML10 6RD
Manuals on anything electronic

Circuits - VCR £8, CTV £6
Service Manuals from £10
Repair Manuals from £5
P&P any order £2.50

Write, or ring 01357 440280 for full details
of our lending service and FREE quote for
any data

**BTEC ELECTRONICS
TECHNICIAN TRAINING**

GNVQ ADVANCED ENGINEERING
(ELECTRONIC) - PART-TIME
HND ELECTRONICS - FULL-TIME
B.Eng FOUNDATION - FULL-TIME

Next course commences
Monday 29th January 2001
FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE
(Dept EPE) 20 PENYWERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: (020) 7373 8721

**THE BRITISH AMATEUR
ELECTRONICS CLUB**

exists to help electronics enthusiasts by
personal contact and through a quarterly
Newsletter.

For membership details, write to the
Secretary:

Mr. M. P. Moses,
5 Park View, Cwmaman,
Aberdare CF44 6PP

Space donated by
Everyday Practical Electronics

Miscellaneous

PRINTED CIRCUIT BOARDS - QUICK SERVICE. Prototype and production artwork raised from magazines or draft designs at low cost. PCBs designed from schematics. Production assembly, wiring and software programming. For details contact Patrick at Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast, BT5 4GX. Phone 028 9073 8897, Fax 028 9073 1802, E-mail agar@argonet.co.uk.

PROTOTYPE PRINTED CIRCUIT BOARDS one offs and quantities, for details send s.a.e. to B. M. Ansbro, 38 Poynings Drive, Hove, Sussex BN3 8GR, or phone/fax Brighton 883871, Mobile 07949 598309. E-mail b.m.a@cwctv.net.

X-10® Home Automation
We put you in control™

Why tolerate when you can automate?

An extensive range of 230V X-10 products and starter kits available. Uses proven Power Line Carrier technology, no wires required. Products Catalogue available Online. Worldwide delivery.

Philips Pronto Intelligent Remote now available!

Laser Business Systems Ltd.

E-Mail: info@laser.com
http://www.laser.com
Tel: (020) 8441 9788
Fax: (020) 8449 0430



FREE PROTOTYPE PRINTED CIRCUIT BOARDS! Free prototype p.c.b. with quantity orders. Call Patrick on 028 9073 8897 for details. Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast BT5 4GX.

G.C.S.E. ELECTRONIC KITS, at pocket money prices. S.A.E. for FREE catalogue. SIR-KIT Electronics, 52 Severn Road, Clacton, CO15 3RB.

VALVE ENTHUSIASTS: Capacitors and other parts in stock. For free advice/lists please ring, Geoff Davies (Radio), Tel. 01788 574774.

DETECT ATMOSPHERIC ACTIVITY. Unique Designs. Self-addressed envelope: PO Box 694, Saint Helier, JE4 9PZ, Jersey, CI.

FOR SALE: E-PROMS, 27128A-2, 27256-2, 2764, 27C011, 27C256-15, 27C512, a total of 247 devices; also Dataman Designs Softy 3 programmer emulator, Gang of Eight copier, UV eraser. Prefer to sell as one lot, £600. E-mail MCW@cwcom.net or tel: 01234 781300.

K.I.A. CATALOGUE, s.a.e. Projects, offers plus bargains and component samples . . . lots from Santa! K.I.A., 1 Regent Road, Ilkley LS29.

FLUKE SCOPEMETER, Model 92, combines the functions of a rugged dual-channel oscilloscope with multimeter functions. Boxed, as new, cost £1,250, nearest cash offer to £350 secures. For further details tel: 01884 258272 (Devon).

EPE NET ADDRESSES

EPE FTP site: <ftp://ftp.epemag.wimborne.co.uk>

Access the FTP site by typing the above into your web browser, or by setting up an FTP session using appropriate FTP software, then go into quoted sub-directories:

PIC-project source code files: **/pub/PICS**

PIC projects each have their own folder; navigate to the correct folder and open it, then fetch all the files contained within. *Do not try to download the folder itself!*

EPE text files: **/pub/docs**

Basic Soldering Guide: **solder.txt**

EPE TENS Unit user advice: **tens.doc** and **tens.txt**

Ingenuity Unlimited submission guidance: **ing_unlt.txt**

New readers and subscribers info: **epe_info.txt**

Newsgroups or Usenet users advice: **usenet.txt**

Ni-Cad discussion: **nicadfaq.zip** and **nicad2.zip**

Writing for EPE advice: **write4us.txt**

On-line readers! Try the EPE Chat Zone - a virtually real-time Internet "discussion board" in a simple to use web-based forum!

<http://www.epemag.wimborne.co.uk/wwwboard>

Or buy EPE Online: www.epemag.com

Ensure you set your FTP software to ASCII transfer when fetching text files, or they may be unreadable.

Note that any file which ends in .zip needs unzipping before use. Unzip utilities can be downloaded from:

<http://www.winzip.com> or
<http://www.pkware.com>

TRAIN TODAY FOR A BETTER FUTURE

Now you can get the skills and qualifications you need for career success with an ICS Home Study Course. Learn in the comfort of your own home at the pace and times that suit you. ICS is the world's largest, most experienced home study school. Over the past 100 years ICS have helped nearly 10 million people to improve their job prospects. Find out how we can help YOU. Post or phone today for FREE INFORMATION on the course of your choice

Electrical Contracting & Installation
Electrical Engineering
C&G/ICS Basic Electronic Engineering
C&G/ICS Basic Mechanical Engineering
TV and Video Servicing
Radio and Hi-Fi Servicing
Refrigeration Heating & Air Conditioning
Motorcycle Maintenance

FREEPHONE 0500 581 557

Or write to: International Correspondence Schools, FREEPOST 882, 8 Elliot Place, Clydeaway Skypark, Glasgow, G3 8BR. Tel: 0500 581 557 or Tel/Fax: Dublin 285 2533

Please send me my Free information on your Electronics Courses.

Mr/Mrs/Ms/Miss
(BLOCK CAPITALS PLEASE) Date of Birth / /

Address

Postcode

Occupation Tel. No.

From time to time, we permit other carefully screened organisations to write to you about products and services. If you would prefer not to hear from such organisations please tick box Dept. ZEEVC1K0

Professional 88-108MHz FM Broadcasting Kits


All Our Kits Include

Detailed Instructions with Schematics
High Quality Screen Printed PCBs
High Quality Components

Our Product Range Includes

Transmitters from 0.05W to 35W
FM Stereo Coders
Audio Compressor Limiters
Antennas
RF Power Amps

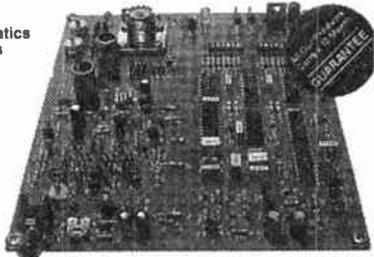Our Kits Are Also Available
Fully Assembled And Tested



1W Professional PLL FM Transmitter for Licenced Use in the UK

Visit our Website at <http://www.veronica.co.uk>

WE DELIVER WORLD-WIDE AND
ACCEPT MAJOR CREDIT CARDS

Contact Us Now For A Free Brochure

Tel 01274 883434 Fax 01274 428665

email info@veronica.co.uk

Unit 5/6 1A Sandbeds/Albert Rd Queensbury BRADFORD BD13 1AA



ELECTRONICS SURPLUS CLEARANCE SALE

SCOOP PURCHASE:

FLUKE HAND HELD DIGITAL MULTIMETER, MODEL 8024B

Cancelled export order 750V AC/DC 2 amp AC/DC Resistance 20Megohm plus Siemens range. Also measures temperature -20°C to +1265°C. Temp. probe not included. Calibrated for K-type thermocouple. Peak hold facility. Supplied brand new and boxed but with original purchasing organisation's small identifying mark on case. Test leads and handbook included.

Offered at a fraction of original price: £47.50, p&p £6.50

THE ELECTRONICS SURPLUS TRADER - This is a listing of new first class components, books and electronic items at below trade prices. Includes manufacturers' surplus and overstocks. Also obsolete semiconductors, valves and high voltage caps and components. Send two first class stamps for large catalogue.

(Dept E) CHEVET SUPPLIES LTD

157 Dickson Road, BLACKPOOL FY1 2EU

Tel: (01253) 751858. Fax: (01253) 302979

E-mail: chevet@globalnet.co.uk Telephone Orders Accepted
Callers welcome Tues, Thurs, Fri and Sat.



COVERT VIDEO CAMERAS

Black and White Pin Hole Board Cameras with Audio. Cameras in P.I.R., Radios, Clocks, Briefcases etc. Transmitting Cameras with Receiver (Wireless).

Cameras as above with colour.
Audio Surveillance Kits and Ready Built Units, Bug Detector etc.

A.L. ELECTRONICS

Please phone 0181 203 6008 for free catalogue.

Fax 0181 201 5359

E-mail: surveillance@btclick.com www.uspy.com

New DTI approved Video Transmitters and Receivers (Wireless)

Major credit cards now taken



MANUFACTURER OF HI-FI AUDIO MODULES AND
TOROIDAL TRANSFORMERS SINCE 1971

CONTACT US NOW FOR A FREE CATALOGUE

ILP DIRECT LTD.

SPONG LANE, ELMSTED, ASHFORD, KENT TN25 5JU

TEL +44 1233 750481 FAX +44 1233 750578

VISA



2001 CATALOGUE

NOW AVAILABLE, FREE OF CHARGE, PLEASE SEND SAE.
KITS AVAILABLE FOR MOST EPE PROJECTS. PLEASE SEND SAE
FOR DETAILS OF ANY KIT THAT INTERESTS YOU.

SPECIAL £1 OFFER PACKS IN OUR 2001 CATALOGUE NOW INCLUDE:

2	BB104 VARICAP DIODE	7	2N2926 YELLOW TRANSISTOR
3	BC107 TRANSISTOR	10	2N3704 TRANSISTOR
4	BC108 TRANSISTOR	16	16-PIN DIL SOCKET
5	BC109 TRANSISTOR	8	18-PIN DIL SOCKET
6	BC117 TRANSISTOR	3	6 x AA BATTERY HOLDER 61 x 45 x 28mm
7	BC142 TRANSISTOR	5	STRIPBOARD 25 x 64MM (9T x 25H)
8	BC167 TRANSISTOR	10	13A 1in. MAINS PLUG TOP FUSES
9	BC168 TRANSISTOR	10	2-PIN DIN LOUDSPEAKER CHASSIS SOCKET
10	BC213LB TRANSISTOR	10	2-PIN DIN LOUDSPEAKER CHASSIS SOCKET
11	BC303-5 TRANSISTOR	10	ASSORTED FUSES
12	BC413 TRANSISTOR	20M	ASSORTED WIRE PACK
13	TC206D TRIAC 400V 4A		SEE LAST/NEXT MONTH'S EPE FOR MORE BARGAINS

PRICE INCLUDES VAT. CLAIM YOUR FREE GIFT WITH ALL ORDERS OVER £10 IN VALUE WITH THIS ADVERT.
MAJOR CREDIT CARDS, CHEQUES AND PO'S ACCEPTED. MAIL ORDER ONLY.
UK MAINLAND P&P ONLY £1 (EXPORT AT COST MIN. £2).

FML ELECTRONICS

FREEPOST NEA 3627, BEDALE, NORTH YORKSHIRE DL8 2BR

TEL: 01677 425840

N. R. BARDWELL LTD (EPE)


100	Signal Diodes 1N4148	£1.00	200	Asstd. disc ceramic capacitors	£1.00
75	Rectifier Diodes 1N4001	£1.00	50	Asstd. Sikal Presets (sm, stand, cermet)	£1.00
50	Rectifier Diodes 1N4007	£1.00	50	Asstd. RF chokes (inductors)	£1.00
10	W01 Bridge Rectifiers	£1.00	50	Asstd. grommets	£1.00
10	555 Timer I.C.s	£1.00	80	Asstd. solder lags, p/conn, terminals	£1.00
4	741 Op Amps	£1.00	10	Asstd. crystals - plug in	£1.00
50	Assorted Zener Diodes 400mW	£1.00	24	Asstd. coil formers	£1.00
12	Assorted 7-segment Displays	£1.00	8	Asstd. di. switches	£1.00
25	5mm l.e.d.s. red, green or yellow	£1.00	20	Miniature slide switches sp/co	£1.00
25	3mm l.e.d.s. red, green or yellow	£1.00	10	Standard slide switches dp/dt	£1.00
50	Axial l.e.d.s. 2mcd red Diode Package	£1.00	100	Asstd. beads (ceramic, teflon, fish spine)	£1.00
25	Asstd. High Brightness l.e.d.s., var coils	£1.00	80	Asstd. small stand offs, 1/throughs etc	£1.00
20	BC182L Transistors	£1.00	30	Asstd. di. sockets up to 40 way	£1.00
25	BC212L Transistors	£1.00	10	TV coax plugs, plastic	£1.00
30	BC237 Transistors	£1.00	40	metres very thin connecting wire, red	£1.00
20	BC327 Transistors	£1.00	20	1in. glass reed switches	£1.00
30	BC328 Transistors	£1.00	20	Magnetic ear pipes with lead and plug	£1.00
30	BC547 Transistors	£1.00	100	Any one value 1/4W 5% cf resistors range	£0.45
30	BC548 Transistors	£1.00	1R to 10M		£0.45
30	BC549 Transistors	£1.00	10	7812 Voltage Regulators	£1.00
25	BC557 Transistors	£1.00			
30	BC558 Transistors	£1.00			
30	BC559 Transistors	£1.00			
20	2N3904 Transistors	£1.00			
100	1nf 50V wkg Axial Capacitors	£1.00			
100	4N7 50V wkg Axial Capacitors	£1.00			
12	1uf 250V encapsulated radial plastic cased capacitors	£1.00			
80	Asstd capacitors electrolytic-	£1.00			
80	Asstd. capacitors 1nF to 1µF	£1.00			

288 Abbeydale Road, Sheffield S7 1FL

Phone: 0114 255 2886 ★ Fax: 0114 250 0689

e-mail: sales@bardwells.co.uk ★ Web: www.bardwells.co.uk

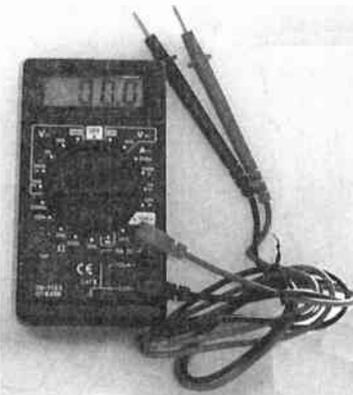Prices include VAT. Postage £1.65
44p stamp for lists or disk



DIGITAL TEST METER

Built-in transistor test socket and diode test position.
DC volts 200mV to 1000V.
AC volts 200V to 750V.
DC current 200mA to 10A.
Resistance 200 ohms to 2000K ohms.

£6.99 incl. VAT

**FREE 240-page
colour catalogue**

Great value for Speakers, Microphones, Headphones, Aerials, Transmitters, TV Amps, Plugs, Sockets, Leads, CD Storage Cases, CCTV, Security, Connectors, Adaptors, Switch Boxes, Gadgets, Disco Lighting & Effects, Mixers, Amplifiers, Turntables, Musicians' Leads, Car Audio, Test Equipment, Hobby Kits, Computer Leads & Accessories, Power Supplies, Inverters, Transformers, Battery Chargers, Tools, Soldering, Switches, Fuses, Indicators, Cable & Wire, Crossovers, Speaker Hardware, PA Amps, and a great deal more... all for the price of a stamp.

SKY ELECTRONICS
Tel: 020 8450 0995
Fax: 020 8208 1441

Sky Electronics

40-42 Cricklewood Broadway London NW2 3ET
Tel: 020 8450 0995 Fax: 020 8208 1441
www.skyelectronics.co.uk

The Catalogue is FREE to callers or send stamps to the value of £1.35 to cover postage.

ELECTRONICS 2001

SHERWOOD ELECTRONICS

FREE COMPONENTS

Buy 10 x £1 Special Packs and choose another one FREE

SP1 15 x 5mm Red LEDs	SP131 2 x TL071 Op.Amps
SP2 12 x 5mm Green LEDs	SP133 20 x 1N4004 diodes
SP3 12 x 5mm Yellow LEDs	SP134 15 x 1N4007 diodes
SP6 15 x 3mm Red LEDs	SP135 6 x Min. slide switches
SP7 12 x 3mm Green LEDs	SP136 3 x BFY50 transistors
SP10 100 x 1N4148 diodes	SP137 4 x W005 1.5A bridge rectifiers
SP11 30 x 1N4001 diodes	SP138 20 x 2.2/63V radial elect. caps.
SP12 30 x 1N4002 diodes	SP140 3 x W04 1.5A bridge rectifiers
SP18 20 x BC182 transistors	SP142 2 x CMOS 4017
SP20 20 x BC184 transistors	SP143 5 Pairs min. crocodile clips (Red & Black)
SP21 20 x BC212 transistors	SP145 6 x ZTX300 transistors
SP23 20 x BC549 transistors	SP146 10 x 2N3704 transistors
SP24 4 x CMOS 4001	SP147 5 x Stripboard 9 strips x 25 holes
SP25 4 x 555 timers	SP151 4 x 8mm Red LEDs
SP26 4 x 741 Op.Amps	SP152 4 x 8mm Green LEDs
SP28 4 x CMOS 4011	SP153 4 x 8mm Yellow LEDs
SP29 3 x CMOS 4013	SP154 15 x BC548 transistors
SP31 4 x CMOS 4071	SP156 3 x Stripboard, 14 strips x 27 holes
SP34 20 x 1N914 diodes	SP160 10 x 2N3904 transistors
SP36 25 x 10/25V radial elect. caps.	SP161 10 x 2N3906 transistors
SP37 15 x 100/35V radial elect. caps.	SP165 2 x LF351 Op.Amps
SP39 10 x 470/16V radial elect. caps.	SP167 6 x BC107 transistors
SP40 15 x BC237 transistors	SP168 6 x BC108 transistors
SP41 20 x Mixed Ic transistors	SP175 20 x 1/63V radial elect. caps.
SP42 200 x Mixed 0.25W C.F. resistors	SP177 10 x 1A 20mm quick blow fuses
SP47 5 x Min. PB switches	SP182 20 x 4-7/63V radial elect. caps.
SP102 20 x 8-pin DIL sockets	SP183 20 x BC547 transistors
SP103 15 x 14-pin DIL sockets	SP187 15 x BC239 transistors
SP104 15 x 16-pin D.L sockets	SP191 3 x CMOS 4023
SP105 4 x 74LS00	SP192 3 x CMOS 4056
SP109 15 x BC557 transistors	SP193 20 x BC213 transistors
SP112 4 x CMOS 4093	SP194 8 x OA94 diodes
SP114 5 x ZTX500 transistors	SP195 3 x 10mm Yellow LEDs
SP115 3 x 10mm Red LEDs	SP197 6 x 20 pin DIL sockets
SP116 3 x 10mm Green LEDs	SP198 5 x 24 pin DIL sockets
SP118 2 x CMOS 4047	
SP120 3 x 74LS93	
SP124 20 x Assorted ceramic disc caps	
SP130 100 x Mixed 0.5W C.F. resistors	

RESISTOR PACKS - C.Film

RP3 5 each value - total 365 0.25W	£2 85
RP7 10 each value - total 730 0.25W	£4 10
RP10 1000 popular values: 0.25W	£5 85
RP4 5 each value-total 365 0.5W	£4 80
RP9 10 each value-total 730 0.5W	£4 45
RP11 1000 popular values: 0.5W	£4 15

2000 Catalogue now available £1 inc. P&P or FREE with first order.

P&P £1.25 per order. NO VAT

Orders to:

Sherwood Electronics,
7 Williamson St., Mansfield,
Notts. NG19 6TD.

Millions of quality components at lowest ever prices!

Plus anything from bankruptcy - theft recovery
- frustrated orders - over productions etc.
Send 54p stamped self-addressed label or
envelope for clearance lists.

Brian J Reed

**6 Queensmead Avenue, East Ewell,
Epsom, Surrey KT17 3EQ
Tel: 07775 945386 or 0208 393 9055
Mail Order UK only.**

Lists are updated and only 40 are sent out every 2 weeks. This normally ensures that orders can be fulfilled where only a few thousands of an item is available. (Payment is returned if sold out. I do not deal in credit notes).

ADVERTISERS INDEX

A.L. ELECTRONICS	951
ANTEX	928
N. R. BARDWELL	951
BELL COLLEGE OF TECHNOLOGY	878
B.K. ELECTRONICS	Cover (iii)/928
BRIAN J. REED	952
BRUNNING SOFTWARE	911
BULL ELECTRICAL	Cover (ii)
CHEVET SUPPLIES	951
CRICKLEWOOD ELECTRONICS	898
CROWNHILL ASSOCIATES	904
DISPLAY ELECTRONICS	874
ECONOMATICS (EDUCATION)	878
EPTSOFT	Cover (iv)
ESR ELECTRONIC COMPONENTS	882
FML ELECTRONICS	951
FOREST ELECTRONIC DEVELOPMENTS	891
GREENWELD	876
ICS	951
ILP DIRECT	951
J&N FACTORS	942
JPG ELECTRONICS	898
LABCENTER ELECTRONICS	897
MAGENTA ELECTRONICS	880/881/912
MAPLIN ELECTRONICS	901
MILFORD INSTRUMENTS	921
NATIONAL COLLEGE OF TECHNOLOGY	898
PEAK ELECTRONIC DESIGN	925
PICO TECHNOLOGY	877
QUASAR ELECTRONICS	937
SERVICE TRADING CO	898
SHERWOOD ELECTRONICS	952
SKY ELECTRONICS	952
SQUIRES	878
STEWART OF READING	912
SUMA DESIGNS	907
TELNET	879
VERONICA KITS	951

ADVERTISEMENT MANAGER: PETER J. MEW

ADVERTISEMENT OFFICES:

EVERYDAY PRACTICAL ELECTRONICS, ADVERTISEMENTS,
MILL LODGE, MILL LANE, THORPE-LE-SOKEN,
ESSEX CO16 0ED.

Phone/Fax: (01255) 861161

For Editorial address and phone numbers see page 883



POWER AMPLIFIER MODULES-LOUDSPEAKERS-MIXERS 19 INCH STEREO AMPLIFIERS-ACTIVE CROSS/OVERS.

* PRICES INCLUDE V.A.T.
* PROMPT DELIVERY

OMP MOS-FET POWER AMPLIFIERS HIGH POWER. TWO CHANNEL 19 INCH RACK

10,000's
SOLD
TO PRO
USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W - 200W)
MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS ARE R.M.S. INTO 4 OHMS, WITH BOTH CHANNELS DRIVEN
FEATURES:- * Independent power supplies with two toroidal transformers
* Twin L.E.D. Vu Meters * Level controls * Illuminated on/off switch * Jack / XLR inputs
* Speakon Outputs * Standard 775mv inputs * Open and Short circuit proof * Latest Mos-Fets
for stress free delivery into virtually any load * High slew rate * Very low distortion * Aluminium
cases * MXF600 & MXF900 fan cooled with D.C. Loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC

SIZES:-
MXF200 W19" D11" H3 1/2" (2U)
MXF400 W19" D12" H5 1/2" (3U)
MXF600 W19" D13" H5 1/2" (3U)
MXF900 W19" D14" H5 1/2" (3U)

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL £12.50 Each



OMP XO3-S STEREO 3 WAY ACTIVE CROSSOVER SWITCHABLE 2-WAY




BASS MID TOP BASS/MID TOP BASS MID/TOP
CONFIGURED 3 WAY 2 WAY BASS/MID COMBINED 2 WAY MID/TOP COMBINED

FEATURES:-

Advanced 3-Way Stereo Active Cross-Over (Switchable two way), housed in a 19" x 1U case. Each channel has three level controls: Bass, Mid & Top. The removable front facia allows access to the programmable DIL switches to adjust the cross-over frequency: There are two versions available:-
XO3-S Bass-Mid 125/250/500Hz, Mid-Top 1.8/3/5kHz, all at 24 dB per octave.
XO3 Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5kHz, all at 24 dB per Octave.
Please make sure you ask for the correct model when ordering.
The 2/3 way selector switches are also accessed by removing the front facia. Each stereo channel can be configured separately. Bass Invert Switches are incorporated on each channel. Nominal 775mV input/output. Fully compatible with the OMP Rack Amplifier and Modules.

BOTH MODELS PRICED AT :- £117.44 + £5.00 P&P

STEREO DISCO MIXER MPX 2005

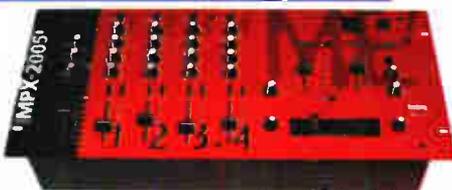

- * 4 STEREO INPUT CHANNELS
- * 2 DJ MIC INPUTS
- * SEPARATE TONE CONTROLS FOR EACH CHANNEL
- * HEADPHONE MONITOR WITH PFL
- * ASSIGNABLE CROSSFADE
- * 2 MASTER OUTPUTS WITH INDIVIDUAL GAIN CONTROLS
- * REMOVABLE CROSSFADE

STEREO DISCO MIXER WITH:- * SEPARATE TONE CONTROLS FOR EACH CHANNEL * 2 DJ MIC INPUTS * DJ MIC HAS ITS OWN TONE CONTROL, GAIN AND AUTO TALK OVER * 4 STEREO CHANNELS WITH INDIVIDUAL FADERS AND ASSIGNABLE CROSSFADE * CHANNELS SWITCHABLE TURNTABLE * MAG CARTRIDGE * CD, LINE, TAPE ETC. * HEADPHONE MONITOR WITH PREFADE LISTEN * 2 X LED VU METERS * SEPARATE GAIN CONTROLS * EFFECTS SEND AND RETURN * 2 X LED VU METERS CAN MONITOR MASTER CHANNELS A OR B OR PFL LEVEL
SIZE : 482 X 222 X 110mm PRICE :- £169.00 + £5.00 P&P

100 WATT ACTIVE SUB BASS AMPLIFIER PANEL



AN ACTIVE SUB BASS AMPLIFIER WITH A TRUE 100W RMS OUTPUT SUPERB CONSTRUCTION WITH THE FACILITIES TO INTEGRATE SEEMLESSLY INTO MOST HI-FI OR HOME CINEMA SETUPS. USE THIS PANEL PLUS ONE OF OUR LOUDSPEAKERS TO MAKE YOUR OWN SUB WOOFER THAT WILL MATCH OR BEAT MOST COMMERCIALY AVAILABLE SUB WOOFERS.

FEATURES:- * 100W RMS INTO 8 OHMS * HIGH AND LOW LEVEL INPUTS * TOROIDAL TRANSFORMER * SHORT CIRCUIT PROTECTION * D.C. SPEAKER PROTECTION * FREQUENCY ROLL OFF, LOWER 10Hz, UPPER 60Hz TO 240Hz (FULLY ADJUSTABLE) * AC3 COMPATIBLE FILTER CAN BE BYPASSED FOR 5-1 FORMATS. * A TIGHT CONSTRUCTION * TENS OF THOUSANDS OF OUR PANELS ALREADY IN USE. * COMPLETE WITH LEADS

SPECIFICATIONS:- * POWER 100W RMS @ 8 OHMS * FREQ RESP. 10Hz 15KHz -3dB * DAMPING FACTOR >200 * DISTORTION 0.05% * S/N A WEIGHTED >100dB * SUPPLY 230V A.C. * WEIGHT 2.7Kg * SIZE H254 X W254 X D94mm

THERE ARE 2 VERSIONS OF THE ABOVE PANEL AVAILABLE :- BSB100/8 8 OHM VERSION BSB100/4 4 OHM VERSION BOTH PANELS ARE PRICED AT £117.44 + £5.00 P&P INCL. V.A.T

FLIGHTCASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of latest loudspeaker technology and enclosure designs. All models utilise high quality studio cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands. The FC15-300 incorporates a large 16 X 6 inch horn. All cabinets are fitted with the latest Speakon connectors for your convenience and safety. Five models to choose from.

Woofer
Monitor
Tweeter



PLEASE NOTE:- POWER RATINGS QUOTED ARE IN WATTS R.M.S. FOR EACH INDIVIDUAL CABINET ALL ENCLOSURES ARE 8 OHMS

15=15 Inch speaker
12=12 Inch speaker

- ibl FC15-300 WATTS Freq Range 35Hz-20kHz, Sens 101dB, Size H695 W502 D415mm Price:- £299.00 per pair
- ibl FC12-300 WATTS Freq Range 45Hz-20kHz, Sens 96dB, Size H600 W405 D300mm Price:- £249.00 per pair
- ibl FC12-200 WATTS Freq Range 40Hz-20kHz, Sens 97dB, Size H600 W405 D300mm Price:- £199.00 per pair
- ibl FC12-100 WATTS Freq Range 45Hz-20kHz, Sens 100dB, Size H546 W380 D300mm Price:- £179.00 per pair
- ibl WM12-200 WATTS Freq Range 40Hz-20kHz, Sens 97dB, Size H418 W600 D385mm Price:- £125.00 Each

SPECIALIST CARRIER DEL. £12.50 per pair, wedge monitor £7.00 each
Optional Metal Stands PRICE £49.00 per pair Delivery £6.00

10 INCH AND 12 INCH 100W RMS SUB BASS LOUDSPEAKERS

TWO SUPERB SUB WOOFER LOUDSPEAKER DRIVERS TO ACCOMPANY OUR SUB BASS AMPLIFIER PANEL BELOW. BOTH DRIVERS OFFER GOOD BASS RESPONSE AT A REASONABLE COST. THE BSB12-100 HAS BEEN USED FOR MANY YEARS IN AN AWARD WINNING SUB BASS SYSTEM

FOR TH/SM SPECIFICATIONS VIEW OUR WEB SITE AT <http://www.bkelec.com>

12 INCH LOUDSPEAKER	BSB12-100	10 INCH LOUDSPEAKER	BSB10-100
	POWER 100W IMPEDANCE 8 OHMS SENSITIVITY 90dB WEIGHT 3.0Kg PRICE £24.95 CARRIAGE £5.00		POWER 100W IMPEDANCE 8 OHMS SENSITIVITY 89dB WEIGHT 2.3Kg PRICE £19.99 CARRIAGE £5.00

OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market, ie. Industry, Leisure, instrumental and Hi-Fi etc. When comparing prices: NOTE that all models include toroidal power supply, integral heatsink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output Power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. 110dB, Size 300 x 123 x 60mm. Price:- £42.85 + £4.00 P&P



OMP/MF 200 Mos-Fet Output Power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Size 300 x 155 x 100mm. Price:- £66.35 + £4.00 P&P



OMP/MF 300 Mos-Fet Output Power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Size 330 x 175 x 100mm. Price:- £83.75 + £5.00 P&P



OMP/MF 450 Mos-Fet Output Power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti Thump Delay, Size 385 x 210 x 105mm. Price:- £135.85 + £6.00 P&P



OMP/MF 1000 Mos-Fet Output Power 1000 watts R.M.S. into 2 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti Thump Delay, Size 422 x 300 x 125mm. Price:- £261.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BANDWIDTH 100kHz OR PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BANDWIDTH 50kHz ORDER STANDARD OR PEC

B.K. ELECTRONICS
UNIT 1 COMET WAY, SOUTHEND-ON-SEA,
ESSEX, SS2 6TR.

TEL.: 01702-527572 FAX.: 01702-420243
Web:- <http://www.bkelec.com> E-Mail sales@bkelec.com

REF D2

'Electronics and Computing Principles V7'

New version for 2000

Principles V7'

Studying electronics or computing or just want to keep up-to-date in a easy and enjoyable way, then this is the software for you.

eptsoft.com

Including all the previous version six topics, many of which are revised and updated, from DC and AC theory, transistors, OpAmps, electrical, filters, digital techniques, microprocessors, programming the PIC micro controller, where the architecture and full instruction set can be explored. More than a thousand interactive electronics, electrical, mathematics topics (just five shown above), now including computer science. V7 (developed in the UK) is a huge source of electronic and computing information.

Our software is used in colleges and universities at home and overseas to support electronics and computing courses from GCSE, A' Level, City & Guilds, BTEC to Degree level. It's extremely easy to use, making it ideally suited to the novice just starting out, up to the qualified engineer who is looking to access hundreds of formula covering practically every aspect of electronics. Telephone for a full list.

ADDITIONAL TOPICS: Computer Science from how a CD-ROM works to calculating the placement of data on a hard disk drive, to file handling and data management systems, Component Testing, Physical Science, More Electronics, Self Assessment Questions, Electronics Lab software and a completely new Component and Equipment Dictionary. A 700 slide PowerPoint presentation is included on the CD-ROM.

PLUS: Changes to graphical presentation, function selection toolbar, number formatting and printing.

eptsoft limited. Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ.

Tel: +44 (0)1376 514008. Fax: +44 (0)870 0509660 Email: info@eptsoft.com

Switch, Delta, Visa and MasterCard payments accepted.

Cheques and P.O. made payable to eptsoft limited. UK and OVERSEAS POSTAGE ARE FREE