

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EVERYDAY

SEPTEMBER 2001

**PRACTICAL**

# ELECTRONICS

£2.75

## WATER MONITOR

Measures & controls water usage

## HI-TECH L.E.D. TORCHES

Economical illumination



**NOW AVAILABLE TO BUY ON THE WEB**  
**EP**  
www.epemag.co.uk

### PERPETUAL PROJECTS-3

- Burglar Alarm
- Door Light
- Rain Alarm

### PLUS

New Technology Update •  
Readout • Network



<http://www.epemag.wimborne.co.uk>

World Radio History

**PIR OPERATED WATER VALVES.** These brand new units consist of a control box with integral PIR and a water valve fitted with 15mm compression fittings. The valve is 6V d.c. operation and latches, e.g. 6V pulse will open it, 6V negative pulse will release it. Originally made to control urinals (flush when someone comes in) they have many other uses in cat scarers, automatic watering systems etc. They have built-in adjustable time delays and settings and run quite happily for months on just a 9V battery. The valve alone could have many uses in garden features, solar systems, etc. Current retail price for the complete unit is £120, we can offer them at just £19.95 while stocks last! Ref PIRVAL2.

**EMMINENCE LOUDSPEAKERS.** 12in. diameter, 50 watts nominal, 100 watts peak, 16 ohm Imp. Pack of 4 just £39.95. Ref SPEAK39.

**PIR SECURITY SWITCHES.** These brand new swivel mounting PIR units will switch up to 2 kilowatts. Adjustable sensitivity, light level and time delay (9 seconds to 10 minutes), 15m detection range, mains operated, waterproof. £5.95. Ref PIR1PACK or a pack of 5 for £22.95. Ref PIR5PACK or 10 for £39.95 Ref PIR10PACK.

**12V 18Ah SEALED LEAD-ACID BATTERIES, new and boxed, unused, pack of 4 £44.95, Ref CYC7 or £15.95 each, Ref CYC6.**

**12V 6-5Ah SEALED LEAD ACID BATTERIES, new and boxed, pack of 5 £34.95, Ref CYC65A, or individually at £8.99, Ref CYC65B.**

## A new range of 12V to 240V INVERTERS

**IV400S (400 watt) £89**

**IV800S (800 watt) £159**

**IV1200S (1200 watt) £219**

**SODIUM LAMP SYSTEMS, £75.70.** Complete system with 250W or 400W SON-T Agro bulb, reflector with bulbholder and remote ballast and starter (uncased), all you need is wire. 250W system Ref SLS1. 400W system SLS2.

**HYDROPONICS – DO YOU GROW YOUR OWN?** Check our web site at [www.bullnet.co.uk](http://www.bullnet.co.uk).

**PC COMBINED UPS AND PSU.** The unit has a total power of 292 watts, standard motherboard connectors and 12 peripheral power leads for drives etc. Inside are three 12V 7.2Ah sealed lead-acid batteries. Backup time is 8 mins at full load or 30 mins at half load. Made in the UK by Magnum, 110V or 240V a.c. input, +5V at 35A, -5V at 0.5A, +12V at 9A, -12V at 0.5A outputs. 170mm x 260mm x 220mm, new and boxed, £29.95. Ref PCUPS2.

**AERIAL PHOTOGRAPHY KIT.** This rocket comes with a built-in camera, it flies up to 500 feet (150m), turns over, and takes an aerial photograph of the ground below. The rocket then returns, with its film, via its parachute. Takes 110 film. Supplied complete with everything, including a launch pad and three motors (no film). £29.98. Ref ASTRO.

**3HP MAINS MOTORS.** Single-phase 240V, brand new, 2-pole, 340mm x 180mm, 2,850 rpm, built-in automatic reset over-load protector, keyed shaft (40mm x 16mm). Made by Leeson. £99 each. Ref LEE1.

**BUILD YOUR OWN WINDFARM FROM SCRAP.** New publication gives step-by-step guide to building wind generators and propellers. Armed with this publication and a good local scrapyard could make you self-sufficient in electricity! £12. Ref LOT81.

**MAGNETIC CREDIT CARD READERS AND ENCODING MANUAL, £9.95.** Cased with fly-leads, designed to read standard credit cards! Complete with control electronics p.c.b. and manual covering everything you could want to know about what's hidden in that magnetic strip on your card! Just £9.95. Ref BAR31.

**SOLAR POWER LAB SPECIAL.** 2in. x 6in. x 6in., 6V 130mA cells, 4 l.e.d.s, wire, buzzer, switch plus relay or motor. £7.99. Ref SA27.

**SOLAR NiCAD CHARGERS.** 4 x AA-size, £9.99. Ref 6P476, 2 x C-size, £9.99. Ref 6P477.

**LOCKPICKS.** We sell a full range of lockpicks and lockpicking books on our website: [www.lockpicks.co.uk](http://www.lockpicks.co.uk).

**SHUT THE BOX.** Check out [www.bullybeef.co.uk](http://www.bullybeef.co.uk) for a range of pub games and magic tricks.

**AIR RIFLES FROM LESS THAN £40, CROSSBOWS, WIDE RANGE OF BB GUNS, AMMO, TARGETS, PISTOLS, REPLICA GUNS, UZI MACHINE GUN REPLICAS (BB), REPEATERS, LASER SIGHTS, ELECTRIC BB, GAS BB**  
[www.airpistol.co.uk](http://www.airpistol.co.uk)

**INKJET CARTRIDGES FROM JUST £3 AT**  
[www.officebits.co.uk](http://www.officebits.co.uk)

## GIANT WEATHER BALLOONS NEW, BOXED, NATO, TOTEX 7 FOOT DIAMETER, £13.99

## ONE MILLION HITS A MONTH [WWW.BULLNET.CO.UK](http://WWW.BULLNET.CO.UK)

Hydrogen fuel cells. Our new Hydrogen fuel cells are 1V at up to 1A output. Hydrogen Input, easily driven from a small electrolysis assembly or from a hydrogen source, our demo model uses a solar panel with the output leads in a glass of salt water to produce the hydrogen! Each cell is designed to be completely taken apart, put back together and expanded to whatever capacity you like (up to 10 watts and 12V per assembly). Cells cost £49. Ref HFC11.

**PHILIPS VP406 LASER DISC PLAYERS, SALE PRICE JUST £9.95. SCART OUTPUT, JUST PUT YOUR VIDEO DISC IN AND PRESS PLAY. STANDARD AUDIO AND VIDEO OUTPUTS. £9.95. REF VP406.**

**SMOKE ALARMS.** Mains powered, made by the famous Gent company, easy fit next to light fittings, power point. Pack of 5 £15, Ref SS23. Pack of 12 £24, Ref SS24.

**SENDER KIT.** Contains all components to build a A/V transmitter complete with case, £35. Ref VSXX2.

**CCTV CAMERAS FROM £22.** Check out our web site at [www.cctvstuff.co.uk](http://www.cctvstuff.co.uk).

**MAMOD STEAM ENGINES AND A FULL RANGE OF SPARE PARTS.**

CHECK OUT [www.mamodspares.co.uk](http://www.mamodspares.co.uk).

**14 WATT SOLAR PANEL.** Amorphous silicon panel fitted in an anodised aluminium frame. Panel measures 3ft. by 1ft. with screw terminals for easy connection. 3ft. x 1ft. solar panel £69. Ref MAG45. Unframed 4 pack (3ft. x 1ft.) £69. Ref SOLX.

**12V SOLAR POWERED WATER PUMP.** Perfect for many 12V d.c. uses, from solar fountains to hydroponics! Small and compact, yet powerful, works direct from our 10 watt solar panel in bright sun. Max hd: 17ft., max flow = 8l.p.m., 1.5A. Ref AC8. £18.99

**SOLAR MOTORS.** Tiny motors which run quite happily on voltages from 3V to 12V d.c. Works on our 6V amorphous 6in. panels, and you can run them from the sun! 32mm dia., 20mm thick. £1.50 each.

**WALKIE TALKIES. 1 MILE RANGE, £37/PAIR. REF MAG30.**

**LIQUID CRYSTAL DISPLAY.** Bargain prices, 40-character 1-line 154mm x 16mm, £6.00. Ref SMC4011A.

**YOUR HOME COULD BE SELF-SUFFICIENT IN ELECTRICITY.** Comprehensive plans with loads of info on designing systems, panels, control electronics, etc. £7. Ref PV1.

**SOLAR POWER LAB SPECIAL.** 2in. x 6in. x 6in., 6V 130mA cells, 4 l.e.d.s, wire, buzzer, switch plus relay or motor. £7.99. Ref SA27.

**SOLAR NiCAD CHARGERS.** 4 x AA-size, £9.99. Ref 6P476, 2 x C-size, £9.99. Ref 6P477.

**BRAND NEW NATO ISSUE RADIATION DETECTORS, SALE PRICE JUST £39.95.** Current NATO issue standard emergency services unit used by most of the world's military personnel. New and boxed. Normal retail price £400, BULL'S bargain price just £99. Ref PDRM.

**PC COMBINED UPS AND PSU.** The unit has a total power of 292 watts, standard motherboard connectors and 12 peripheral power leads for drives etc. Inside are three 12V 7.2Ah sealed lead-acid batteries. Back-up time is 8 mins at full load or 30 mins at half load. Made in the UK by Magnum, 110V or 240V a.c. input, +5 at 35A, -5V at 0.5A, +12V at 9A, -12V at 0.5A outputs. 170mm x 260mm x 220mm, new and boxed, £29.95. Ref PCUPS2.

**BASIC GUIDE TO BIO DIESEL. HOW TO MAKE DIESEL FUEL FROM USED KITCHEN OIL, £6. REF BIOF.**

**SPECIAL OFFER! SAVE ££££££££, RCB UNITS.** In-line IEC lead with fitted RC breaker. Installed in seconds. Fit to any computer, monitor, office equipment and make it safe! Pack of 10 just £9.98. Ref LOT5B.

**INFRA-RED REMOTE CONTROL WATCHES, £16.99;** vibrating watches, vibrate when your phone rings, £16.99; pulse watches, display your pulse, £16.99.

**ALTERNATIVE ENERGY CD,** packed with hundreds of alternative energy related articles, plans and information etc. £14.50. Ref CD56.

## BULL ELECTRICAL

UNIT D, HENFIELD BUSINESS PARK,  
SHOREHAM ROAD, HENFIELD, SUSSEX  
BN5 9SL (ESTABLISHED 50 YEARS)  
MAIL ORDER TERMS: CASH, PO  
OR CHEQUE WITH ORDER  
PLUS £5.00 P&P PLUS VAT

24 HOUR SERVICE £7.50 PLUS VAT  
OVERSEAS ORDERS AT COST PLUS £3.50  
(ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

'phone orders: 0871 871 1300  
FAX 0871 871 1301

Sales@bull-electrical.com

**BASIC GUIDE TO LOCKPICKING.** New publication gives you an insight! £6. Ref LPK.

**30 WATTS OF SOLAR POWER** for just £69, 4 panels, each one 3ft. x 1ft. and producing 8W, 13V. Pack of four £69. Ref SOLX.

**200 WATT INVERTERS,** plugs straight into your car cigarette lighter socket and is fitted with a 13A socket so you can run your mains-operated devices from your car battery. £49.95. Ref SS66.

**THE TRUTH MACHINE.** Tells if someone is lying by micro tremors in their voice, battery operated, works in general conversation and on the phone and TV as well! £42.49. Ref TD3.

**INFRA-RED FILM.** 6in. square piece of flexible infra-red film that will only allow IR light through. Perfect for converting ordinary torches, lights, headlights etc. to infra-red output only using standard light bulbs. Easily cut to shape. 6in. square. £15. Ref IRF2.

**33 KILO LIFT MAGNET.** Neodymium, 32mm diameter with a fixing bolt on the back for easy mounting. Each magnet will lift 33 kilos, 4 magnets bolted to a plate will lift an incredible 132 kilos! £15. Ref MAG33. Pack of 4 just £39. Ref MAG33AA.

**77 KILO LIFT MAGNET.** These Samarium magnets measure 57mm x 20mm and have a threaded hole (5/16th UNF) in the centre and a magnetic strength of 2.2 gauss. We have tested these on a steel beam running through the offices and found that they will take more than 77kg (170lb) in weight before being pulled off. Supplied with keeper. £19.95 each. Ref MAG77.

**HYDROGEN FUEL CELL PLANS.** Loads of information on hydrogen storage and production. Practical plans to build a hydrogen fuel cell (good workshop facilities required). £8 set. Ref FCP1.

**STIRLING ENGINE PLANS.** Interesting information pack covering all aspects of Stirling engines, pictures of home made engines made from an aerosol can running on a candle! £12. Ref STIR2.

**ENERGY SAVER PLUGS.** Saves up to 15% electricity when used with fridges, motors up to 2A, light bulbs, soldering irons etc. £9 each. Ref LOT71. 10 pack, £69. Ref LOT72.

**12V OPERATED SMOKE BOMBS.** Type 3 is a 12V trigger and three smoke cannisters, each cannister will fill a room in a very short space of time! £14.99. Ref SB3. Type 2 is 20 smaller cannisters (suitable for mock equipment fires etc.) and one trigger module for £29. Ref SB2. Type 1 is a 12V trigger and 20 large cannisters. £49. Ref SB1.

**HI-POWER ZENON VARIABLE STROBES.** Useful 12V p.c.b. fitted with hi-power strobe tube and control electronics and speed control potentiometer. Perfect for interesting projects etc. 70mm x 55mm 12V d.c. operation. £6 each. Ref FLS1. Pack of 10 £49. Ref FLS2.

**HOW TO PRODUCE 35 BOTTLES OF WHISKY FROM A SACK OF POTATOES.** Comprehensive 270 page book covers all aspects of spirit production from everyday materials. Includes construction details of simple stills. £12. Ref MS3.

**NEW HIGH POWER MINI BUG.** With a range of up to 800 metres and 3 days use from a PP3 battery this is our top selling bug! Less than 1in. square and a 10m voice pick-up range. £28. Ref LOT102.

**IR LAMP KIT.** Suitable for CCTV cameras, enables the camera to be used in total darkness! £6. Ref EF138.

**INFRA-RED POWER BEAM.** Handheld battery powered lamp, 4 inch reflector, gives out powerful pure infra-red light! Perfect for CCTV use, night sights etc. £29. Ref PB1.

**SUPER WIDEBAND RADAR DETECTOR.** Whistler 1630. Detects both radar and laser, XK and KA bands, speed cameras, and all known speed detection systems. 360 degree coverage, front and rear waveguides. 1.1in. x 2.7in. x 4.6in., fits on visor or dash. New low price £99. Ref WH1630. Other models available at [www.radargun.co.uk](http://www.radargun.co.uk).

**LOPTX.** Made by Samsung for colour TV. £3 each. Ref SS52.

**WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA?** We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14. Ref EP74.

**ELECTRONIC SPEED CONTROLLER KIT.** For the above motor is £19. Ref MAG17. Save £5 if you buy them both together. one motor plus speed controller rrp is £41. Offer price £36. Ref MOT5A.

**INFRA-RED REMOTE CONTROLS.** Made for TVs but may have other uses. Pack of 100 £39. Ref IREM.

**RCB UNITS.** In-line IEC lead with fitted RC breaker. Installed in seconds. Pack of 3 £9.98. Ref LOT5A.

**STEPPER MOTORS.** Brand new stepper motors, 4mm fixing holes with 47.14mm fixing centres, 20mm shaft, 6-35mm diameter, 5V/phase, 0-7A/phase, 1-8 deg. step (200 step), body 56mm x 36mm. £14.99 each. Ref STEP6. Pack of 4 for £49.95.

## On our web sites you can:

1. Order online.
2. Check your premium bonds.
3. Enter our auction or build your own.
4. Add E-commerce to your own site.
5. Discover our software site, optical site, hydroponics site, holiday home exchange site, inkjet site, radar detectors, hotels site.

<http://www.bullnet.co.uk>

ISSN 0262 3617  
PROJECTS ... THEORY ... NEWS ...  
COMMENTS ... POPULAR FEATURES ...



VOL. 30. No. 9 SEPTEMBER 2001

Cover illustration by Jonathan Robertson
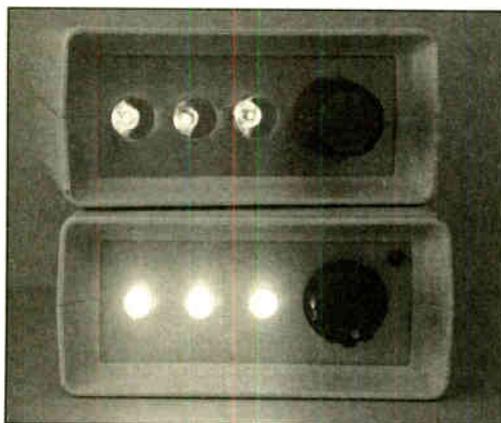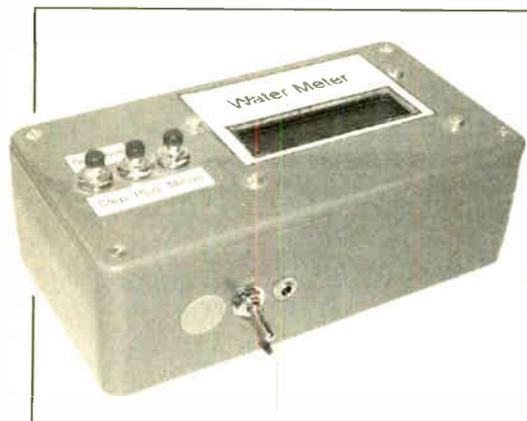
# EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

[www.epemag.wimborne.co.uk](http://www.epemag.wimborne.co.uk)  
**EPE Online: [www.epemag.com](http://www.epemag.com)**



## WE HAVE MOVED!

Please note our new address and  
phone/fax numbers – see page 615

© Wimborne Publishing Ltd 2001. Copyright in all drawings, photographs and articles published in EVERYDAY PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

## Projects and Circuits

- WATER MONITOR** by John Becker 616  
How costly is it to keep your garden watered?  
Find out and control it
- INGENUITY UNLIMITED** hosted by Alan Winstanley 626  
Wien Bridge Audio Generator; Precision Stereo Volume Control
- L.E.D. SUPER TORCHES** by Andy Flind 628  
Two hi-tech (one super-hi-tech!) designs to brighten your nights
- PERPETUAL PROJECTS – 3** by Thomas Scarborough 644  
Three more solar-powered projects – **Loop Burglar Alarm, Touch-Switch Door-Light, Solar-Powered Rain Alarm** – plus seven suggestions for variants
- SYNCHRONOUS CLOCK DRIVER** by Andy Flind 660  
By popular request – a dual-frequency, 50Hz-60Hz converter for mains operated synchronous clocks

## Series and Features

- NEW TECHNOLOGY UPDATE** by Ian Poole 622  
Small is efficient when it comes to packaging
- CONTROLLING FLIGHT** by Owen Bishop 638  
An insight into how electronics helps to maintain aircraft safety
- PRACTICALLY SPEAKING** by Robert Penfold 654  
A novice's guide to why some pins can be left unconnected
- NET WORK – THE INTERNET PAGE** surfed by Alan Winstanley 658
- CIRCUIT SURGERY** by Alan Winstanley and Ian Bell 666  
Curious Decoupling; Some Like it Hot

## Regulars and Services

- EDITORIAL** 615
- NEWS** – Barry Fox highlights technology's leading edge 623  
Plus everyday news from the world of electronics
- READOUT** John Becker addresses general points arising 635
- ELECTRONICS VIDEOS** Our range of educational videos 642
- SHOPTALK** with David Barrington 650  
The *essential* guide to component buying for *EPE* projects
- PLEASE TAKE NOTE** Shortwave Loop Aerial 650
- BACK ISSUES** Did you miss these? Some now on CD-ROM! 652
- CD-ROMS FOR ELECTRONICS** 656  
Electronic Projects; Filters; Digital Works 3.0; Electronic Circuits and Components V2.0; Digital Electronics; Analogue Electronics; PICtutor; Modular Circuit Design; Electronic Components Photos; C for PIC Micros; CAD Pack
- ELECTRONICS MANUALS** 668  
Essential reference works for hobbyists, students and service engineers
- DIRECT BOOK SERVICE** 670  
A wide range of technical books available by mail order
- PRINTED CIRCUIT BOARD AND SOFTWARE SERVICE** 673  
PCBs for *EPE* projects. Plus *EPE* software
- ADVERTISERS INDEX** 676

Our October 2001 issue will be published on Thursday,  
13 September 2001. See page 607 for details

**Readers Services • Editorial and Advertisement Departments 615**

Visit our website  
www.distel.co.uk

# THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always  
wanted for cash!

## THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!



TV SOUND &  
VIDEO TUNER  
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers\* (TELEBOX MR). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95  
TELEBOX STL as ST but fitted with integral speaker £39.50  
TELEBOX MR Multiband VHF/UHF/Cable/Hyperband tuner £69.95  
For overseas PAL versions state 5.5 or 6 MHz sound specification.  
\*For cable / hyperband signal reception TELEBOX MB should be connected to a cable type service. Shipping on all Telebox's, code (B)

**NEW** State of the art PAL (UK spec) UHF TV tuner module with composite 1V pp video and NICAM Hi Fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £49.95 code (B)**  
See www.distel.co.uk/data\_my00.htm for picture + full details

## FLOPPY DISK DRIVES 2 1/2" - 8"

All units (unless stated) are **BRAND NEW** or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call or see our web site www.distel.co.uk for over 2000 unlisted drives for spares or repair.

- 3 1/2" Mitsubishi MF355C-L 1.4 Meg Laptops only £25.95(B)
- 3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop £18.95(B)
- 5 1/4" Teac FD-55FR 1.2 Meg (for IBM pcs) RFE £18.95(B)
- 5 1/4" Teac FD-55F-0U 720K 40/80 (for BBC's etc) RFE £29.95(B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 360K £22.95(B)
- Table top case with integral PSU for HH 5 1/4" Floppy / HD £29.95(B)
- 8" Shugart 800/801 8" SS refurbished & tested £210.00(E)
- 8" Shugart 810 8" SS HH Brand New £260.00(E)
- 8" Shugart 851 8" double sided refurbished & tested £295.00(E)
- 8" Mitsubishi M2894-63 double sided NEW £295.00(E)
- 8" Mitsubishi M2896-63-02U DS slimline NEW £295.00(E)
- Dual 8" casad drives with integral power supply 2 Mb £499.00(E)

## HARD DISK DRIVES 2 1/2" - 14"

- 2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H) New £79.95
  - 2 1/2" TOSHIBA MK2101MAN 2.16 Gb laptop (19 mm H) New £89.50
  - 2 1/2" TOSHIBA MK4309MAT 4.3Gb laptop (8.2 mm H) New £105.00
  - 2 1/2" TOSHIBA MK6409MAV 6.1Gb laptop (12.7 mm H) New £190.00
  - 2 1/2" to 3 1/2" conversion kit for PCs, complete with connectors £14.95
  - 3 1/2" FUJI FC-309-26 20mb MFM I/F RFE £59.95
  - 3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE £59.95
  - 3 1/2" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE £69.00
  - 3 1/2" QUANTUM 405 Prodr II w/ 42mb SCSI I/F, New RFE £49.00
  - 5 1/4" MINISCRIIBE 3425 20mb MFM I/F (or equiv.) RFE £49.95
  - 5 1/4" SEAGATE ST-238R 30 mb IFL I/F Refurb £69.95
  - 5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested £69.95
  - 5 1/4" HP 97546 850 Mb SCSI RFE tested £99.00
  - 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
  - 8" NEC D2246 85 Mb SMD interface. New £199.00
  - 8" FUJITSU M2322K 160Mb SMD I/F RFE tested £195.00
  - 8" FUJITSU M2392K 2 Gb SMD I/F RFE tested £345.00
- Many other drives in stock - Shipping on all drives is code (C1)

## TEST EQUIPMENT & SPECIAL INTEREST ITEMS

- MITS. FA3445ETKL 14" Industrial spec SVGA monitors £245
- FARNELL 0-60V DC @ 50 Amps, bench Power Supplies £995
- FARNELL AP3080 0-30V DC @ 80 Amps, bench Supply £1850
- 1kW to 400 kW - 400 Hz 3 phase power sources - ex stock £POA
- IBM 8230 Type 1, Token ring base unit driver £760
- Wayne Kerr RA200 Audio frequency response analyser £2500
- IBM S3F5501 Token Ring ICS 20 port lobe modules £750
- IBM MAU Token ring distribution panel 8228-23-5050N £95
- AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE £550
- ALLGON 8360, 11805-1880 MHz hybrid power combiners £250
- Trend DSA 274 Data Analyser with G703(2M) 64 v/o £POA
- Marconi 6310 Programmable 2 to 22 GHz sweep generator £6500
- Marconi 2022C 10KHz-1GHz RF signal generator £1550
- Marconi 2030 opt 03 10KHz-1.3 GHz signal generator, New £4995
- HP1650B Logic Analyser £3750
- HP3781A Pattern generator & HP3782A Error Detector £POA
- HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
- HP6264 Rack mount variable 0-20V @ 20A metered PSU £675
- HP54121A DC to 22 GHz four channel test set £7900
- HP8130A opt 020 300 MHz pulse generator, GPIB etc £550
- HP A1, A0 8 pen HPGL high speed drum plotters - from £750
- HP DRAFTMASTER 1 8 pen high speed plotter £1800
- EG+G Brookdale 95035C Precision lock in amp £1800
- Vony Eng. Mod 1200 computerised inspection system £POA
- Sony DXC-3000A High quality CCD colour TV camera £995
- Keithley 590 CV capacitor / voltage analyser £POA
- Racal ICR40 dual 40 channel voice recorder system £3750
- Fiskers 45KVA 3 ph On Line UPS - Now batteries £9500
- Emerson AP130 2.5KVA industrial spec UPS £2100
- Mann Tally M7645 High speed line printer £2200
- Intel SBC 486/133SE Multibus 486 system 8Mb Ram £945
- Siemens K4400 64Kb to 140Mb demux analyser £2950

## IC'S - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK  
10,000,000 items EX STOCK

For MAJOR SAVINGS  
CALL OR SEE OUR WEB SITE www.distel.co.uk

## VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see -  
At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PCs in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPPR specification. Fully guaranteed, in EXCELLENT little used condition.

Tilt & Swivel Base £1.75  
VGA cable for IBM PC included.  
Only £119 (E) Order as MITS-SVGA

External cables for other types of computers available - CALL  
Ex demo 17" 0.28 SVGA Mitsubishi Diamond Pro monitors, Full multisync etc.  
Full 90 day guarantee. Only £199.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested & guaranteed Only £99.00 (E)  
Dimensions: W14" x H12 1/4" x 15 1/2" D.

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered. Only £79.00 (D)

KME 10" 15M1009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition. Only £125 (E)

## 20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. Pill all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.


20"....£135 22"....£155 26"....£185 (F)  
We probably have the largest range of video monitors in Europe. All sizes and types from 4" to 42" call for info.

## DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock  
Call or see our web site.

- HP6030A 0-200V DC @ 17 Amps bench power supply £1950
- Intel SBC 486/125C08 Enhanced Multibus (MSA) New £1150
- Nikon HF-X11 (Ephiphon) exposure control unit £1450
- PHILIPS PM5518 pro. TV signal generator £1250
- Motorola VME Bus Boards & Components List. SAE / CAL £POA
- Trio 0-18 vdc linear, metered 30 amp bench PSU. New £550
- Fujitsu M3041R 600 LPM high speed band printer £1950
- Fujitsu M3041D 600 LPM printer with network interface £1250
- Perkin Elmer 299B Infrared spectrophotometer £500
- Perkin Elmer 597 Infrared spectrophotometer £3500
- VG Electronics 1035 TELE TEXT Decoding Margin Meter £3250
- LightBand 60 output high spec 2u rack mount Video VDA's £495
- Seikon SD 150H 18 channel digital Hybrid chart recorder £1995
- B&K 2633 Microphone pre amp £300
- Taylor Hobson Tallysur amplifier / recorder £750
- ADC S5200 Carbon dioxide gas detector / monitor £1450
- BBC AM203 PPM Meter (Ernest Turner) + drive electronics £75
- ANRITSU 9654A Optical DC-2.5Gb/w wavelorn monitor £6500
- ANRITSU MS9001B1 0.6-1.7 uM optical spectrum analyser £POA
- ANRITSU ML93A optical power meter £990
- ANRITSU Fibre optic characterisic test set £EPOA
- R&S FTDZ Dual sound unit £650
- R&S SBUF-E1 Vision modulator £775
- WILTRON 6630B 12 4 / 20GHz RF sweep generator £5750
- TEK 2445 150 MHz 4 trace oscilloscope £1250
- TEK 2465 300 MHz 300 MHz oscilloscope rack mount £1950
- TEK TDS380 400MHz digital realtime + disk driver, FFT etc £2900
- TEK TDS524A 500MHz digital realtime + colour display etc £5100
- HP3585A Opt 907 20Hz to 40 MHz spectrum analyser £3950
- PHILIPS PW1730/10 60KV XRAY generator & accessories £POA
- CLAUDE LYONS 12A 240V single phase auto volt. regs £325
- CLAUDE LYONS 100A 240/415V 3 phase auto. volt. regs £2900

## 19" RACK CABINETS

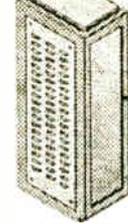


Superb quality 6 foot 40U  
Virtually New, Ultra Smart  
Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting, plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are 77 1/2" H x 32 1/2" D x 22" W. Order as:

OPT Rack 1 Complete with removable side panels. £345.00 (G)  
OPT Rack 2 Black. Less side panels. £245.00 (G)  
Over 1000 racks, shelves, accessories  
19" 22" & 24" wide 3 to 46 U high.  
Available from stock !!
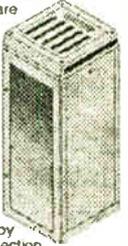
## 32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, pre-punched utility panel at lower rear for cable / connector access. Supplied in excellent, slightly used condition with keys Colour Royal blue. External dimensions mm=1625H x 635D x 603 W (64" H x 25" D x 23 1/2" W)



Sold at LESS than a third of makers price !!  
A superb buy at only £245.00 (G)  
42U version of the above only £345 - CALL

## 12V BATTERY SCOOP - 60% off !!

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12v DC 14Ah rechargeable batteries. Made by Hawker Energy Ltd, type SB515 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS6290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £70 each. Our Price £35 each (C) or 4 for £99 (E)

## RELAYS - 200,000 FROM STOCK

Save ££££'s by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradles, Hermetically Sealed, Continental, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting etc. CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save ££££'s

## COLOUR CCD CAMERAS

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full autolight sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available. Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cam's etc.

Web ref = LK33 ONLY £99.00 or 2 for £180.00 (E)

## SOFTWARE SPECIALS

- NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. ONLY £89.00 (B)
  - ENCARTA 95 - CDROM, Not the latest - but at this price! £7.95
  - DOS 5.0 on 3 1/2" disks with concise books c/w OBasic £14.95
  - Windows for Workgroups 3.11 + Dos 6.22 on 3 1/2" disks £55.00
  - Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95
- shipping charges for software is code B

## DISTEL on the web !! - Over 16,000,000 items from stock - www.distel.co.uk



ALL MAIL TO  
Dept PE, 29/35 Osborne Rd  
Thornton Heath  
Surrey CR7 8PD  
Open Mon - Fri 9.00 - 5.30

LONDON SHOP  
Open Mon - Sat 9.00 - 5.30  
215 Whitehorse Lane  
South Norwood  
On 68A Bus Route  
N. Thornton Heath & Selhurst Park SR Rail Stations

NEW DISTEL  
Visit our web site  
www.distel.co.uk  
email = admin@distel.co.uk

ALL ENQUIRIES  
0208 653 3333  
FAX 0208 653 8888

All prices for UK Mainland. UK customers add 17.5% VAT to total order amount. Minimum order £10. Bond 5-10% account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)-£3.00, (A1)-£4.00, (B)-£5.50, (C)-£8.50, (C1)-£12.50, (D)-£15.00, (F)-£18.00, (F)-£20.00, (G)-CALL. Allow approx 6 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All quantities on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASI prices paid for surplus goods. All trademarks, tradenames etc acknowledged © Display Electronics 1999. T. & O. E. 0799.



# NEXT MONTH


## PIC TOOLKIT TK3 FOR WINDOWS

Designed explicitly for running in the "desk-top PC" environments of Windows 95 and 98, the software for Toolkit TK3 is intuitively easy to use, fast in operation, has many extra features that are probably not found elsewhere, and is the ideal programming aid for all who love to play with reprogrammable PICs. It is equally suited to TASM and MPASM programming dialects.

The accompanying p.c.b. caters for 8-, 18-, 28- and 40-pin PIC sizes. These can be hard-wired not only to integral on-board hardware, but also to external components in conjunction with a plug-in breadboard. In this context, it is not only a programmer, but its options are also closely allied to the facilities available on the highly successful EPE PIC Tutorial board of March to May '98.

The PIC families catered for are principally the PIC16x84 and PIC16F87x EEPROM-based series. It is likely that the system can be used with other PICs that also have 14-bit program codes.

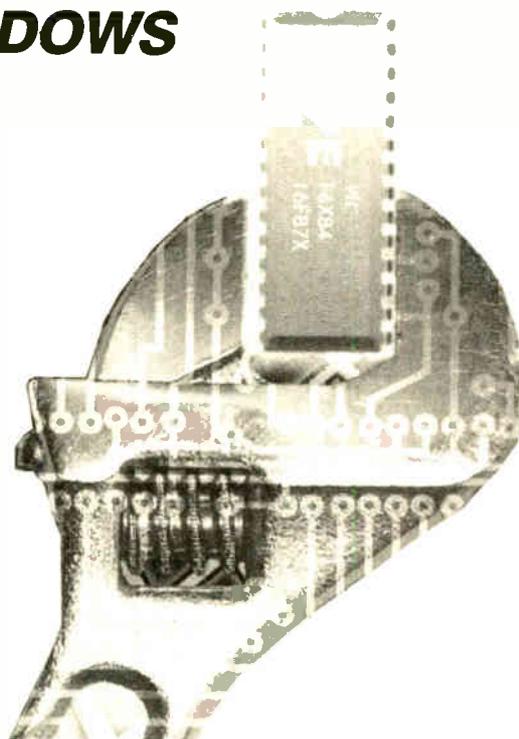The new software can also be used with the Toolkit V2.4 board, originally released in May/June '99.



## TRAFFIC CONTROL

We hear much about air traffic controllers, but more important to our daily lives are those relatively inconspicuous systems and people who control the flow of traffic in our busy cities. This article describes how electronics and computers are used to make their work possible.

For instance, vehicles approaching many junctions are detected by inductive loops. Changes in inductance change the input to the control computer that is located beside the road junction. Information from the inductive loops can tell the computer the length of the traffic queue at the lights and also the speed and approximate size of vehicles approaching them. It's all explained in this feature article.

## TWO-VALVE SW RECEIVER

Never let us be accused of lagging behind the times. Get right up to date with this Two-Valve Shortwave Receiver.

Well maybe it's not the very latest technology but this fascinating retro project is fun to build and use, and the components are still easy to obtain.

This battery powered set is of the type that was the norm in the 60s. It covers the range 5MHz to 30MHz and, although a bit of "chassis bashing" is involved, it is easy to build and use.

Go back in time next month – it will give you a warm glow!

**PLUS ALL THE REGULAR FEATURES**

**NO ONE DOES IT BETTER**

EVERYDAY  
**PRACTICAL**  
**ELECTRONICS**

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

**DON'T MISS AN  
ISSUE – PLACE YOUR  
ORDER NOW!**

Demand is bound to be high

**OCTOBER 2001 ISSUE ON SALE THURSDAY, SEPTEMBER 13**

# QUASAR ELECTRONICS LIMITED

Unit 14 Sunningdale, BISHOPS STORTFORD, Herts. CM23 2PA

TEL: 01279 306504 FAX: 07092 203496

ADD £2.00 P&P to all orders (for 1st Class Registered £4, Non day (1st and £250) £7, Europe £5.00, Rest of World £10.00. We accept all major credit cards. Make cheques/P.O.s payable to Quasar Electronics. Prices include 17.5% VAT. MAIL ORDER ONLY. FREE CATALOGUE with order or send 2 x 1st class stamps (refundable) for details of over 150 kits & publications.



## PROJECT KITS


Our electronic kits are supplied complete with all components, high quality PCBs (NOT cheap Tripad strip board!) and detailed assembly/operating instructions

- **2x 25W CAR BOOSTER AMPLIFIER** Connects to the output of an existing car stereo cassette player, CD player or radio. Heatsinks provided. PCB 76x75mm 1046KT £24.95
- **3-CHANNEL WIRELESS LIGHT MODULATOR** No electrical connection with amplifier. Light modulation achieved via a sensitive electret microphone. Separate sensitivity control per channel. Power handling 400W/channel. PCB 54x112mm. Mains powered Box provided 6014KT £24.95
- **12 RUNNING LIGHT EFFECT** Exciting 12 LED light effect ideal for parties, discos, shop windows & eye-catching signs. PCB design allows replacement of LEDs with 220V bulbs by inserting 3 TRIACS. Adjustable rotation speed & direction. PCB 54x112mm. 1026KT £15.95; BOX (for mains operation) 2026BX £9.00
- **DISCO STROBE LIGHT** Probably the most exciting of all light effects. Very bright strobe tube. Adjustable strobe frequency 1-60Hz. Mains powered. PCB: 60x88mm. Box provided. 6037KT £28.95
- **ANIMAL SOUNDS** Cat, dog, chicken & cow. Ideal for kids farmyard toys & schools. SG10M £5.95
- **3 1/2 DIGIT LED PANEL METER** Use for basic voltage/current displays or customise to measure temperature, light, weight, movement, sound levels, etc. with appropriate sensors (not supplied). Various input circuit designs provided. 3061KT £13.95
- **IR REMOTE TOGGLE SWITCH** Use any TV/CR remote control unit to switch onboard 12V/1A relay. 3058KT £10.95
- **SPEED CONTROLLER** for any common DC motor up to 100V/5A. Pulse width modulation gives maximum torque at all speeds. 5-15VDC. Box provided 3067KT £12.95
- **3 x 8 CHANNEL IR RELAY BOARD** Control eight 12V/1A relays by Infra Red (IR) remote control over a 20m range in sunlight. 6 relays turn on only, the other 2 toggle on/off 3 operation ranges determined by jumpers. Transmitter case & all components provided Receiver PCB 76x89mm 3072KT £52.95

## PRODUCT FEATURE
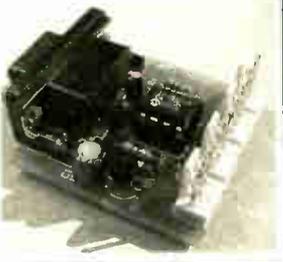
### COMPUTER TEMPERATURE DATA LOGGER

PC serial port controlled 4-channel temperature meter (either deg C or F). Requires no external power. Allows continuous temperature data logging of up to four temperature sensors located 200m+ from motherboard/PC. Ideal use for old 386/486 computers. Users can tailor input data stream to suit their purpose (dump it to a spreadsheet or write your own BASIC programs using the INPUT command to grab the readings). PCB just 38mm x 38mm. Sensors connect via four 3-pin headers. 4 header cables supplied but only one DS18S20 sensor. Kit software available free from our website. ORDERING: 3145KT £23.95 (kit form); AS3145 £28.95 (assembled); Additional DS18S20 sensors £4.95 each



- **SOUND EFFECTS GENERATOR** Easy to build. Create an almost infinite variety of interesting/unusual sound effects from birds chirping to sirens. 9VDC. PCB 54x85mm. 1045KT £8.95
- **ROBOT VOICE EFFECT** Make your voice sound similar to a robot or Darteik. Great fun for discos, school plays, theatre productions, radio stations & playing jokes on your friends when answering the phone! PCB 42x71mm. 1131KT £8.95
- **AUDIO TO LIGHT MODULATOR** Controls intensity of one or more lights in response to an audio input. Safe, modern opto-coupler design. Mains voltage experience required. 3012KT £8.95
- **MUSIC BOX** Activated by light. Plays 8 Christmas songs and 5 other tunes. 3104KT £7.95
- **20 SECOND VOICE RECORDER** Uses non-volatile memory - no battery backup needed. Record/replay messages over & over. Playback as required to greet customers etc. Volume control & built-in mic. 6VDC. PCB 50x73mm. 3131KT £12.95
- **TRAIN SOUNDS** 4 selectable sounds: whistle blowing, level crossing bell, 'clickety-click' & 4 in sequence SG01M £6.95
- **PC CONTROLLED RELAY BOARD** Convert any 286 upward PC into a dedicated automatic controller to independently turn on/off up to eight lights, motors & other devices around the home, office, laboratory or factory using 8 240VAC/12A onboard relays. DOS utilities, sample test program, full-featured Windows utility & all components (except cable) provided. 12VDC. PCB 70x200mm. 3074KT £31.95
- **2 CHANNEL UHF RELAY SWITCH** Contains the same transmitter/receiver pair as 30A15 below plus the components and PCB to control two 240VAC/10A relays (also supplied). Ultra bright LEDs used to indicate relay status. 3082KT £27.95
- **TRANSMITTER RECEIVER PAIR** 2-button keyfob style 300-375MHz Tx with 30m range. Receiver encoder module with matched decoder IC. Components must be built into a circuit like kit 3082 above. 30A15 £14.95
- **PIC 16C71 FOUR SERVO MOTOR DRIVER** Simultaneously control up to 4 servo motors. Software & all components (except sensor/control pots) supplied. 5VDC. PCB 50x70mm 3102KT £15.95
- **UNIPOLAR STEPPER MOTOR DRIVER** for any 5/6/8 lead motor. Fast/slow & single step rates. Direction control & on/off switch. Wave, 2-phase & half-wave step modes. 4 LED indicators. PCB 50x65mm 3109KT £14.95
- **PC CONTROLLED STEPPER MOTOR DRIVER** Control two unipolar stepper motors (3A max. each) via PC printer port. Wave, 2-phase & half-wave step modes. Software accepts 4 digital inputs from external switches & will single step motors. PCB fits in D-shell case provided. 3113KT £17.95
- **12-BIT PC DATA ACQUISITION/CONTROL UNIT** Similar to kit 3093 above but uses a 12 bit Analogue-to-Digital Converter (ADC) with internal analogue multiplexer. Reads 8 single ended channels or 4 differential inputs or a mixture of both. Analogue inputs read 0-4V. Four TTL/CMOS compatible digital input/outputs. ADC conversion time <10µs. Software (C, QB & Win), extended D shell case & all components (except sensors & cable) provided. 3118KT £52.95
- **LIQUID LEVEL SENSOR/RAIN ALARM** Will indicate fluid levels or simply the presence of fluid. Relay output to control a pump to add/remove water when it reaches a certain level. 1080KT £5.95
- **AM RADIO KIT 1 Tuned Radio Frequency front-end, single chip AM radio IC & 2 stages of audio amplification.** All components inc. speaker provided. PCB 32x102mm. 3063KT £10.95
- **DRILL SPEED CONTROLLER** Adjust the speed of your electric drill according to the job at hand. Suitable for 240V AC mains powered drills up to

## X-FACTOR PUBLICATIONS

THE EXPERTS IN RARE & UNUSUAL INFORMATION!

Full details of all X-FACTOR PUBLICATIONS can be found in our catalogue. NB Minimum order charge for reports and plans is £5.00 PLUS normal P&P

- **SUPER-EAR LISTENING DEVICE** Complete plans to build your own parabolic dish microphone. Listen to distant voices and sounds through open windows and even walls! Made from readily available parts. R002 £3.50
- **LOCKS** - How they work and how to pick them. This fact filled report will teach you more about locks and the art of lock picking than many books we have seen at 4 times the price. Priced with information and illustrations. R008 £3.50
- **RAID & TV JOKER PLANS** We show you how to build three different circuits for disrupting TV picture and sound plus FM radio! May upset your neighbours & the authorities! DISCRETION REQUIRED. R017 £3.50
- **INFINITY TRANSMITTER PLANS** Complete plans for building the famous Infinity Transmitter. Once installed on the target phone, device acts like a room bug. Just call the target phone & activate the unit to hear all room sounds. Great for 'home/office security'. R019 £3.50
- **THE ETHER BOX CALL INTERCEPTOR PLANS** Grabs telephone calls out of thin air! No need to wire-in a phone bug. Simply place this device near the phone lines to hear the conversations taking place! R025 £3.00
- **CASH CREATOR BUSINESS REPORTS** Need ideas for making some cash? Well this could be just what you need! You get 40 reports (approx. 800 pages) on floppy disk that give you information on setting up different businesses. You also get valuable reproduction and duplication rights so that you can sell the manuals as you like. R030 £7.50

# SURVEILLANCE

High performance surveillance bugs. Room transmitters supplied with sensitive electret microphone & battery holder/clip. All transmitters can be received on an ordinary VHF/FM radio between 88-108MHz. Available in Kit Form (KT) or Assembled & Tested (AS).

## ROOM SURVEILLANCE

- **MTX - MINIATURE 3V TRANSMITTER** Easy to build & guaranteed to transmit 300m @ 3V. Long battery life. 3-5V operation. Only 45x19mm. B 3007KT £6.95 AS3007 £11.95
- **MRTX - MINIATURE 9V TRANSMITTER** Our best selling bug. Super sensitive, high power - 500m range @ 9V (over 1km with 18V supply and better aerial). 45x19mm. 3018KT £7.95 AS3018 £12.95
- **HPTX - HIGH POWER TRANSMITTER** High performance, 2 stage transmitter gives greater stability & higher quality reception. 1000m range. 6-12V DC operation. Size 70x15mm. 3032KT £9.95
- **MMTX - MICRO-MINIATURE 9V TRANSMITTER** The ultimate bug for its size, performance and price. Just 15x25mm. 500m range @ 9V. Good stability. 6-18V operation. 3051KT £8.95 AS3051 £14.95
- **VTX - VOICE ACTIVATED TRANSMITTER** Operates only when sounds detected. Low standby current. Variable trigger sensitivity. 500m range. Peaking circuit supplied for maximum RF output. On/off switch. 6V operation. Only 63x38mm. 3028KT £12.95 AS3028 £21.95
- **HARDWIRED BUG/TWO STATION INTERCOM** Each station has its own amplifier, speaker and mic. Can be set up as either a hard-wired bug or two-station intercom. 10m x 2-core cable supplied. 9V operation. 3021KT £15.95 (kit form only)
- **TRYS - TAPE RECORDER VOX SWITCH** Used to automatically operate a tape recorder (not supplied) via its REMOTE socket when sounds are detected. All conversations recorded. Adjustable sensitivity & turn-off delay. 115x19mm. 3013KT £9.95 AS3013 £21.95



## TELEPHONE SURVEILLANCE

- **MTTX - MINIATURE TELEPHONE TRANSMITTER** Attaches anywhere to your line. Transmits only when phone is used! Tune-in your radio and hear both parties. 300m range. Uses line as aerial & power source. 20x45mm. 3016KT £8.95 AS3016 £14.95
- **TRT - TELEPHONE RECORDING INTERFACE** Automatically records all conversations. Connects between phone line & tape recorder (not supplied). Operates recorders with 1.5-12V battery systems. Powered from line. 50x33mm. 3033KT £9.95 AS3033 £18.95
- **TPA - TELEPHONE PICK-UP AMPLIFIER/WIRELESS PHONE BUG** Place pick-up coil on the phone line & hear phone earpiece and hear both sides of the conversation. 3055KT £11.95 AS3055 £20.95

## HIGH POWER TRANSMITTERS

- **1 WATT FM TRANSMITTER** Easy to construct. Delivers a crisp, clear signal. Two-stage circuit. Kit includes microphone and requires a simple open dipole aerial. 8-30VDC. PCB 42x45mm. 1009KT £14.95
- **4 WATT FM TRANSMITTER** Comprises three RF stages and an audio preamplifier stage. Piezoelectric microphone supplied or you can use a separate preamplifier circuit. Antenna can be an open dipole or Ground Plane. Ideal project for those who wish to get started in the fascinating world of FM broadcasting and want a good basic circuit to experiment with. 12-18VDC. PCB 44x146mm. 1028KT £22.95 AS1028 £34.95
- **15 WATT FM TRANSMITTER (PRE-ASSEMBLED & TESTED)** Four transistor based stages with Philips BLY 88 in final stage. 15 Watts RF power on the air. 88-108MHz. Accepts open dipole, Ground Plane, 5/8, J, or YAGI antennas. 12-18VDC. PCB 70x220mm. SWS meter needed for alignment. 1021KT £99.95
- **SIMILAR TO ABOVE BUT 25W** Output. 1031KT £109.95

- 700W power. PCB: 48mm x 65mm. Box provided. 6074KT £17.95
- **3 INPUT MONO MIXER** Independent level control for each input and separate bass/treble controls. Input sensitivity: 240mV. 18V DC. PCB: 60mm x 185mm. 1052KT £16.95
- **NEGATIVE POSITIVE ION GENERATOR** Standard Cockcroft-Walton multiplier circuit. Mains voltage experience required. 3057KT £10.95
- **LED DICE** Classic intro to electronics & circuit analysis. 7 LEDs simulate dice roll, slow down & land on a number at random. 555 IC circuit. 3003KT £9.95
- **STAIRWAY TO HEAVEN** Tests hand-eye co-ordination. Press switch when green segment of LED lights to climb the stairway - miss & start again! Good intro to several basic circuits. 3005KT £9.95
- **ROULETTE LED 'Ball'** spins round the wheel, slows down & drops into a slot. 10 LEDs. Good intro to CMOS decade counters & Op-Amps. 3006KT £10.95
- **9V XENON TUBE FLASHER** Transformer circuit steps up 9V battery to flash a 25mm. Xenon tube. Adjustable flash rate (0.25-2 Sec's). 3022KT £11.95
- **LED FLASHER 1** 5 ultra bright red LEDs flash in 7 selectable patterns. 3037MKT £5.95
- **LED FLASHER 2** Similar to above but flash in sequence or randomly. Ideal for model railways. 3052MKT £5.95
- **INTRODUCTION TO PIC PROGRAMMING.** Learn programming from scratch. Programming hardware, a 16F84 chip and a two-part, practical, hands-on tutorial series are provided. 3081KT £22.95
- **SERIAL PIC PROGRAMMER** for all 8/18/28/40 pin DIP serial programmed PICs. Shareware software supplied limited to programming 256 bytes (registration costs £14.95). 3096KT £13.95
- **ATMEL 89C051 PROGRAMMER** Simple-to-use yet powerful programmer for the Atmel 89C1051, 89C2051 & 89C4051 uC's. Programmer does NOT require special software other than a terminal emulator program (built into Windows). Can be used with ANY computer/operating system. 3121KT £24.95
- **3V/1.5V TO 9V BATTERY CONVERTER** Replace expensive 9V batteries with economic 1.5V batteries. IC based circuit steps up 1 or 2 'AA' batteries to give 9V/18mA. 3035KT £5.95
- **STABILISED POWER SUPPLY 3-30V/2.5A** Ideal for hobbyist & professional laboratory. Very reliable & versatile design at an extremely reasonable price. Short circuit protection. Variable DC voltages (3-30V). Rated output 2.5 Amps. Large heatsink supplied. You just supply a 24VAC/3A transformer. PCB 55x112mm. Mains operation. 1007KT £16.95.

- **STABILISED POWER SUPPLY 2-30V/5A** As kit 1007 above but rated at 5Amp. Requires a 24VAC/5A transformer. 1096KT £27.95.
- **MOTORBIKE ALARM** Uses a reliable vibration sensor (adjustable sensitivity) to detect movement of the bike to trigger the alarm & switch the output relay to which a siren, bikes horn, indicators or other warning device can be attached. Auto-reset. 6-12VDC. PCB 57x64mm. 1011KT £11.95. Box 2011BX £7.00
- **CAR ALARM SYSTEM** Protect your car from theft. Features vibration sensor, courtesy/booth light voltage drop sensor and bonnet/boot latch switch sensor. Entry/exit delays, auto-reset and adjustable alarm duration. 6-12V DC. PCB: 47mm x 55mm. 1019KT £11.95. Box 2019BX £8.00
- **PIEZO SCREAMER** 1100dB of ear piercing noise. Fits in box with 2 x 35mm piezo elements built into their own resonant cavity. Use as an alarm siren or just for fun! 6-9VDC. 3015KT £10.95
- **COMBINATION LOCK** Versatile electronic lock comprising main circuit & separate keypad for remote opening of lock. Relay supplied. 3029KT £10.95
- **ULTRASONIC MOVEMENT DETECTOR** Crystal locked detector frequency for stability & reliability. PCB 75x40mm houses all components. 4-7m range. Adjustable sensitivity. Output will drive external relay/circuits. 9VDC. 3049KT £13.95
- **PIR DETECTOR MODULE** 3-lead assembled unit just 25x35mm as used in commercial burglar alarm systems. 3076KT £8.95
- **INFRARED SECURITY BEAM** When the invisible IR beam is broken a relay is tripped that can be used to sound a bell or alarm. 25 metre range. Mains rated relays provided. 12VDC operation. 3130KT £12.95
- **SQUARE WAVE OSCILLATOR** Generates square waves at 6 preset frequencies in factors of 10 from 1Hz-100KHz. Visual output indicator. 5-18VDC. Box provided. 3111KT £8.95
- **PC DRIVEN POCKET SAMPLER/DATA LOGGER** Analogue voltage sampler records voltages up to 2V or 20V over periods from milli-seconds to months. Can also be used as a simple digital scope to examine audio & other signals up to about 5KHz. Software & D-shell case provided. 3112KT £18.95
- **20 MHz FUNCTION GENERATOR** Square, triangular and sine waveform up to 20MHz with 3 ranges using 'coarse' and 'fine' frequency adjustment controls. Adjustable output from 0-2V p-p. A TTL output is also provided for connection to a frequency meter. Uses MAX038 IC. Plastic case with printed front/rear panels & all components provided. 7-12VAC. 3101KT £69.95

BARGAIN BUY!

Great introduction to electronics. Ideal for the budding electronics expert! Build a radio, burglar alarm, water detector, Morse code practice circuit, simple computer circuits, and much more! NO soldering, tools or previous electronics knowledge required. Circuits can be built and unassembled repeatedly. Comprehensive 68-page manual with explanations, schematics and assembly diagrams. Suitable for age 10+. Excellent for schools. Requires 2 x AA batteries. ONLY £14.95 (phone for bulk discounts).



## 30-IN-ONE Electronic Projects Lab

WEB: <http://www.QuasarElectronics.com>  
email: [epesales@QuasarElectronics.com](mailto:epesales@QuasarElectronics.com)

Secure Online Ordering Facilities  
Full Kit Listing, Descriptions & Photos  
Kit Documentation & Software Downloads

www.QuasarElectronics.com

Credit Card Sales: 01279 306504


## 'PICALL' PIC Programmer

Kit will program ALL 8\*, 18\*, 28 and 40 pin serial AND parallel programmed PIC micro controllers. Connects to PC parallel port. Supplied with fully functional pre-registered PICALL DOS and WINDOWS AVR software packages, all components and high quality DSPTH PCB. Also programs certain ATMEL AVR, serial EPROM 24C and SCENIX SX devices. New PIC's can be added to the software as they are released. Software shows you where to place your PIC chip on the board for programming. Now has blank chip auto sensing feature for super-fast bulk programming. \*A 40 pin wide ZIF socket is required to program 8 & 18 pin devices (available at £15.95).



3117KT	'PICALL' PIC Programmer Kit	£59.95
AS3117	Assembled 'PICALL' PIC Programmer	£69.95
AS3117ZIF	Assembled 'PICALL' PIC Programmer c/w ZIF socket	£84.95

## ATMEL AVR Programmer

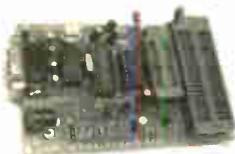

Powerful programmer for Atmel AT90Sxxx (AVR) micro controller family. All fuse and lock bits are programmable. Connects to serial port. Can be used with ANY computer and operating system. Two LEDs to indicate programming status. Supports 20-pin DIP AT90S1200 & AT90S2313 and 40-pin

DIP AT90S4414 & AT90S8515 devices. NO special software required - uses any terminal emulator program (built into Windows). The programmer is supported by BASCOM-AVR Basic Compiler software (see website for details).

**NB ZIF sockets not included.**

3122KT	ATMEL AVR Programmer	£24.95
AS3122	Assembled 3122	£39.95

Atmel 89Cx051 and 89xxx programmers also available.

## PC Data Acquisition & Control Unit

With this kit you can use a PC parallel port as a real world interface. Unit can be connected to a mixture of analogue and digital inputs from pressure, temperature, movement, sound light intensity, weight sensors, etc. (not supplied) to sensing switch and relay states. It can then process the input data and use the information to control up to 11 physical devices such as motors, sirens, other relays, servo motors & two-stepper motors.



### FEATURES:

- 8 Digital Outputs: Open collector, 500mA, 33V max.
  - 16 Digital Inputs 20V max. Protection 1K in series, 5-1V Zener to ground.
  - 11 Analogue Inputs: 0-5V, 10 bit (5mV/step.)
  - 1 Analogue Output: 0-2.5V or 0-10V. 8 bit (20mV/step.)
- All components provided including a plastic case (140mm x 110mm x 35mm) with pre-punched and silk screened front/rear panels to give a professional and attractive finish (see photo) with screen printed front & rear panels supplied. Software utilities & programming examples supplied.

3093KT	PC Data Acquisition & Control Unit	£99.95
AS3093	Assembled 3093	£124.95

See opposite page for ordering information on these kits

## ABC Mini 'Hotchip' Board




Currently learning about microcontrollers? Need to do something more than flash a LED or sound a buzzer? The ABC Mini 'Hotchip' Board is based on Atmel's AVR 8535 RISC technology and will interest both the beginner and expert alike. Beginners will find that they can write and test a simple program, using the BASIC programming language, within an hour or two of connecting it up.

Experts will like the power and flexibility of the ATMEL microcontroller, as well as the ease with which the little Hot Chip board can be "designed-in" to a project. The ABC Mini Board 'Starter Pack' includes just about everything you need to get up and experimenting right away. On the hardware side, there's a pre-assembled micro controller PC board with both parallel and serial cables for connection to your PC. Windows software included on CD-ROM features an Assembler, BASIC compiler and in-system programmer. The pre-assembled boards only are also available separately.

ABCMINISP	ABC MINI Starter Pack	£64.95
ABCMINIB	ABC MINI Board Only	£39.95
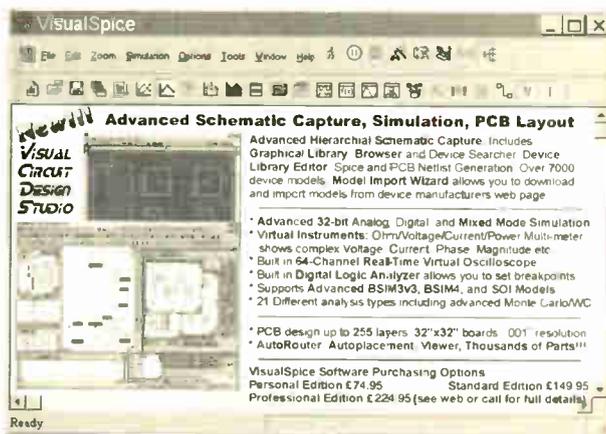
## Advanced Schematic Capture and Simulation Software



## Serial Port Isolated I/O Controller

Kit provides eight 240VAC/12A (110VAC/15A) rated relay outputs and four optically isolated inputs. Can be used in a variety of control and sensing applications including load switching, external switch input sensing, contact closure and external voltage sensing. Programmed via a computer serial port, it is compatible with ANY computer & operating system. After programming, PC can be disconnected. Serial cable can be up to 35m long, allowing 'remote' control. User can easily write batch file programs to control the kit using simple text commands. NO special software required - uses any terminal emulator program (built into Windows). All components provided including a plastic case with pre-punched and silk screened front/rear panels to give a professional and attractive finish (see photo).



3108KT	Serial Port Isolated I/O Controller Kit	£54.95
AS3108	Assembled Serial Port Isolated I/O Controller	£69.95

### MARCONI 2019A



AM/FM SYNTHESISED SIGNAL GENERATOR  
80 kHz - 1040MHz  
**£400**  
NOW ONLY

H.P. 3312A Function Gen., 0-1Hz-13MHz, AM/FM Sweep/Tri/Gate/Burst etc. £300  
H.P. 3310A Function Gen., 0-005Hz-5MHz, Sine/Sq/Tri/Ramp/Pulse £125  
FARNELL LFM4 Sine/Sq Oscillator, 10Hz-1MHz, low distortion, TTL output, Amplitude Meter £125  
H.P. 545A Logic Probe with 546A Logic Pulsar and 547A Current Tracer £90  
FLUKE 77 Multimeter, 3½-digit, handheld £60  
FLUKE 77 Series 11 £70  
HEME 1000 L.C.D. Clamp Meter, 00-1000A, in carrying case £60

### RACAL 9008

Automatic Modulation Meter, AM/FM  
1-5MHz-2GHz  
**£95**  
ONLY



H.P. 8494A Attenuator, DC-4GHz, 0-11dB, N/SMA £250  
H.P. 8492A Attenuator, DC-18GHz, 0-6dB, APC7 £95  
MANY OTHER ATTENUATORS, LOADS, COUPLERS ETC. AVAILABLE

### DATRON 1061

HIGH QUALITY 5½-DIGIT BENCH MULTIMETER  
True RMS/4 wire Res/Current Converter/IEEE  
**£150**

### TIME 1051 LOW OHM RES. BOX

0-01 ohm to 1Mohm in  
0-01 ohm steps.  
**£100**  
UNUSED

### STILL AVAILABLE AS PREVIOUSLY ADVERTISED WITH PHOTOS

MARCONI 893C AF Power Meter, Sinad Measurement Unused £100, Used £60  
MARCONI 893B, No Sinad, Unused £30  
MARCONI 2610 True RMS Voltmeter, Autorange, 5Hz-25MHz £195  
GOULD J3B Sine/Sq Osc., 10Hz-100kHz, low distortion £75-£125  
AVO 8 Mk. 6 in Every Ready case, with leads etc. £80  
Other AVOs from £50  
GOODWILL GFC8010G Freq. Counter, 1Hz-120MHz, unused £75  
GOODWILL GVT427 Dual Ch AC Millivoltmeter, 10mV-300V in 12 ranges, Freq. 10Hz-1MHz £100-£125  
SOLARTRON 7150 DMM 6½-digit Tru RMS-IEEE £95-£150  
SOLARTRON 7150 Plus RACAL TRUE RMS VOLTMETERS 9300 5Hz-20MHz usable to 60MHz, 10V-316V £95  
9300B Version £150  
9301/9302 RF Version to 1.5Hz from £200-£300  
HIGH QUALITY RACAL COUNTERS 9904 Universal Timer Counter, 50MHz £75  
9916 Counter, 10Hz-520MHz £75  
9918 Counter, 10Hz-560MHz, 9-digit £50  
FARNELL AMM255 Automatic Mod Meter, 1-5MHz-2GHz, unused £400

### CLASSIC AVOMETER DA116

Digital 3-5 Digit Complete with batteries and leads  
**£30**  
ONLY



### SOLARTRON 7045

BENCH MULTIMETER  
4½-Digit bright l.e.d. with leads  
It's so cheap you should have it as a spare  
**£30**  
ONLY



MARCONI TF2015 AM/FM sig gen. 10-520MHz £175  
RACAL 9008 Auto Mod Meter, 1-5MHz-2GHz £200  
LEVELL TG200DMP RC Oscillator, 1Hz-1MHz £50  
Sine/Sq. Meter, battery operated (batts. not supplied)  
FARNELL LF1 Sine/Sq. Oscillator, 10Hz-1MHz £75  
RACAL/JAM 9343M LCR Databridge, Digital Auto measurement of R, C, L, Q, D £200  
HUNTRON TRACKER Model 1000 £125  
H.P. 5315A Universal Counter, 1GHz, 2-ch £80  
FLUKE 8050A DMM 4½-digit 2A True RMS £75  
FLUKE 8010A DMM 3½-digit 10A £50

### RADIO COMMUNICATIONS TEST SETS

MARCONI 2955/2955 £200  
MARCONI 2955A/2960 £250  
MARCONI 2022E Synth AM/FM sig gen 10kHz-1.01GHz l.c.d. display etc. £525-£750  
H.P. 8672A Synth 2-18GHz sig gen £4000  
H.P. 8674A Synth sig gen, 100kHz-1040MHz £2000  
H.P. 8658B Synth sig gen, 100kHz-990MHz £1350  
H.P. 8656A Synth sig gen, 100kHz-990MHz £995  
H.P. 8640A AM/FM sig gen, 500kHz-1024MHz £400  
H.P. 8640A AM/FM sig gen, 500kHz-512MHz £250  
PHILIPS PM5328 sig gen, 100kHz-180MHz with 200MHz, freq. counter, IEEE £550  
RACAL 9081 Synth AM/FM sig gen, 5-520MHz £250  
H.P. 3325A Synth function gen, 21MHz £900  
MARCONI 6500 Amplitude Analyser £1500  
H.P. 4275A LCR Meter, 10kHz-10MHz £2750  
H.P. 8903A Distortion Analyser £1000  
WAYNE KERR 3245 Inductance Analyser £2000  
H.P. 8112A Pulse Generator, 50MHz £1250  
DATRON AutoCal Multimeter, 5½-7½-digit, 1065/1061A/1071 from £300-£900  
MARCONI 2400 Frequency Counter, 20GHz £1000  
H.P. 5350B Frequency Counter, 20GHz £2000  
H.P. 8637A 10Hz-18GHz Frequency Counter £300  
FARNELL AP10030 Power Supply £1000  
FARNELL AP7030 Power Supply £900  
PHILIPS PM5418TH Colour TV Pattern Generator £1750  
PHILIPS PM5418TX Colour TV Pattern Generator £2000  
B&K Accelerometer, type 4365 £300  
H.P. 11692D Dual Directional Coupler, 2MHz-18GHz £1600  
H.P. 11691D Dual Directional Coupler, 2MHz-18GHz £1250  
TEKTRONIX P61098 Probe, 100MHz readout, unused £90  
TEKTRONIX P61064 Probe, 250MHz readout, unused £35  
FARNELL AMM2000 Auto Mod Meter, 10Hz-2.4GHz Unused £950  
MARCONI 2035 Mod Meter, 500kHz-2GHz from £750  
TEKTRONIX 577 Transistor Curve Tracer £500

### ROHDE & SCHWARZ APN 62

Synthesised 1Hz-260kHz Signal Generator  
Balanced/unbalanced output LCD display  
**£425**

H.P. 6012B DC PSU, 0-60V, 0-50A, 1000W £1000  
FARNELL AP6050 1kW Autorange £1000  
FARNELL H9050 0-60V, 0-50A £750  
FARNELL H9025 0-60V, 0-25A £400  
Power Supply HPS3010 0-30V, 0-10A £140  
L30-2 0-30V, 0-2A £80  
FARNELL L30-1 0-30V, 0-1A £60  
Many other Power Supplies available  
Isolating Transformer 250V In/Out 500VA £40

### WELLER EC3100A

Temperature controlled Soldering Station  
200°C-450°C, Unused  
**£125**

### PORTABLE APPLIANCE TESTER

Megger Pat 2 ONLY  
**£180**

### SCOPE FOR IMPROVEMENT



### GOULD OS 300

Dual Trace, 20MHz  
Tested with Manual  
**£95**  
FOR THE FIRST TIME EVER ONLY  
It's so cheap you should replace that old scope

### SPECTRUM ANALYSERS

TEKTRONIX 492 50kHz-18GHz £3500  
EATON/WALTECH 757 0-001-22GHz £2500  
H.P. 853A (Dig. Frame) with 8559A 100kHz-21GHz £2750  
H.P. 8558B with main frame, 100kHz-1500MHz £1250  
H.P. 3580A Audio Analyser 5Hz-50kHz, as new £1000  
MARCONI Z382 100Hz-400MHz, high resolution £2000  
B&K 2033R Signal Analyser £1500  
H.P. 182 with 8557 10kHz-350MHz £500  
MARCONI 2370 30Hz-110MHz from £500  
H.P. 141 SYSTEMS  
8553 1kHz-110MHz from £500  
8554 500kHz-1250MHz from £750  
8555 10MHz-18GHz from £1000

### UNUSED OSCILLOSCOPES

TEKTRONIX TAS 485 4-ch., 200MHz, etc. £900  
TEKTRONIX THS70A dual trace, l.c.d., 100MHz, 500MS. £900  
TEKTRONIX THS710 dual trace, 60MHz, 250MS. £750  
HITACHI VC6523, dual trace, 20MHz, 20MS, delay etc. £600

### OSCILLOSCOPES

PHILIPS PM3092 2+2-ch., 200MHz, delay etc., £900 as new £950  
PHILIPS PM3082 2+2-ch., 100MHz, delay etc., £700 as new £800  
TEKTRONIX TAS465 dual trace, 100MHz, delay etc. £800  
TEKTRONIX 2465B 4-ch., 400MHz, delay cursors etc. £1250  
TEKTRONIX 2465 4-ch., 300MHz, delay cursors etc. £900  
TEKTRONIX 2445A/B 4-ch 150MHz, delay cursors etc. £500-£900  
TEKTRONIX 468 dig. storage, dual trace, 100MHz, delay £450  
TEKTRONIX 466 Analogue storage, dual trace, 100MHz £250  
TEKTRONIX 485 dual trace, 350MHz, delay sweep £600  
TEKTRONIX 475 dual trace, 200MHz, delay sweep £400  
TEKTRONIX 465B dual trace, 100MHz, delay sweep £325  
PHILIPS PM3217 dual trace, 50MHz delay £250-£300  
GOULD OS1100 dual trace, 30MHz delay £200  
HAMEG HM3034 dual trace, 30MHz component testerm £325  
HAMEG HM3033 dual trace, 30MHz component tester £300  
HAMEG HM2037 dual trace, 20MHz component tester £250  
FARNELL OTV20 dual trace, 20MHz component tester £180

### RACAL RECEIVER RA1772

50kHz - 30 MHz LED Display  
Basically working  
**£250**

## STEWART of READING



110 WYKEHAM ROAD, READING, BERKS. RG6 1PL

Telephone: (0118) 9268041. Fax: (0118) 9351696

Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)



# PLASTIC BOXES & ENCLOSURES

Contact us for your free catalogue

S.L.M. (Model) Engineers Ltd  
Chiltern Road  
Prestbury  
Cheltenham  
GL52 5JQ

Website: www.slm.uk.com  
Telephone 01242 525488  
Fax 01242 226288

# SQUIRES

## MODEL & CRAFT TOOLS

A COMPREHENSIVE RANGE OF MINIATURE HAND AND POWER TOOLS AND AN EXTENSIVE RANGE OF

### ELECTRONIC COMPONENTS

FEATURED IN A FULLY ILLUSTRATED

### MAIL ORDER CATALOGUE

### 2002 COPY DUE FOR RELEASE

SEPTEMBER 2001

Note: If you have ordered from 2001 copy you will receive the new catalogue automatically

### SAME DAY DESPATCH FREE POST AND PACKAGING

Catalogues: FREE OF CHARGE to addresses in the UK.  
Overseas: CATALOGUE FREE, postage at cost charged to credit card

Squires, 100 London Road,  
Bognor Regis, West Sussex, PO21 1DD

TEL: 01243 842424

FAX: 01243 842525

SHOP NOW OPEN



## £1 BARGAIN PACKS Selected Items

**PIEZO ELECTRIC SOUNDER**, also operates efficiently as a microphone. Approximately 30mm diameter, easily mountable, 2 for £1. Order Ref: 1084.

**LIQUID CRYSTAL DISPLAY** on p.c.b. with i.c.s etc. to drive it to give 2 rows of 8 figures or letters with data. Order Ref: 1085.

**30A PANEL MOUNTING TOGGLE SWITCH**. Double-pole. Order Ref: 166.

**SUB MIN TOGGLE SWITCHES**. Pack of 3. Order Ref: 214.

**HIGH POWER 3in. SPEAKER** (1W 8ohm). Order Ref: 246.

**MEDIUM WAVE PERMEABILITY TUNER**. It's almost a complete radio with circuit. Order Ref: 247.

**HEATING ELEMENT**, mains voltage 100W, brass encased. Order Ref: 8.

**MAINS MOTOR** with gearbox giving 1 rev per 24 hours. Order Ref: 89.

**ROUND POINTER KNOBS** for flatted 1/4in. spindles. Pack of 10. Order Ref: 295.

**CERAMIC WAVE-CHANGE SWITCH**. 12-pole, 3-way with 1/4in. spindle. Order Ref: 303.

**REVERSING SWITCH**. 20A double-pole or 40A single pole. Order Ref: 343.

**LUMINOUS PUSH-ON PUSH-OFF SWITCHES**. Pack of 3. Order Ref: 373.

**SLIDE SWITCHES**. Single pole changeover. Pack of 10. Order Ref: 1053.

**PAXOLIN PANEL**. Approximately 12in. x 12in. Order Ref: 1033.

**CLOCKWORK MOTOR**. Suitable for up to 6 hours. Order Ref: 1038.

**TRANSISTOR DRIVER TRANSFORMER**. Maker's ref. no. LT44, impedance ratio 20k ohm to 1k ohm; centre tapped, 50p. Order Ref: 1/23R4.

**HIGH CURRENT RELAY**, 12V d.c. or 24V a.c., operates changeover contacts. Order Ref: 1026.

**3-CONTACT MICROSWITCHES**, operated with slightest touch, pack of 2. Order Ref: 861.

**HIVAC NUMICATOR TUBE**, Hivac ref XN3. Order Ref: 865 or XN11 Order Ref: 866.

**2IN. ROUND LOUDSPEAKERS**. 50Ω coil. Pack of 2. Order Ref: 908.

**5K POT**, standard size with DP switch, good length 1/4in. spindle, pack of 2. Order Ref: 11R24.

**13A PLUG**, fully legal with insulated legs, pack of 3. Order Ref: GR19.

**OPTO-SWITCH** on p.c.b., size 2in. x 1in., pack of 2. Order Ref: GR21.

**COMPONENT MOUNTING PANEL**, heavy paxolin 10in. x 2in., 32 pairs of brass pillars for soldering binding components. Order Ref: 7RC26.

**HIGH AMP THYRISTOR**, normal 2 contacts from top, heavy threaded fixing underneath, think amperage to be at least 25A, pack of 2. Order Ref: 7FC43.

**BRIDGE RECTIFIER**, ideal for 12V to 24V charger at 5A, pack of 2. Order Ref: 1070.

**TEST PRODS FOR MULTIMETER** with 4mm sockets. Good length flexible lead. Order Ref: D86.

**LUMINOUS ROCKER SWITCH**, approximately 30mm square, pack of 2. Order Ref: D64.

**MES LAMPHOLDERS** slide on to 1/4in. tag, pack of 10. Order Ref: 1054.

**HALL EFFECT DEVICES**, mounted on small heatsink, pack of 2. Order Ref: 1022.

**12V POLARISED RELAY**, 2 changeover contacts. Order Ref: 1032.

**PROJECT CASE**, 95mm x 66mm x 23mm with removable lid held by 4 screws, pack of 2. Order Ref: 876.

**LARGE MICROSWITCHES**, 20mm x 6mm x 10mm, changeover contacts, pack of 2. Order Ref: 826.

**MAINS RELAY** with 15A changeover contacts. Order Ref: 965.

**COPPER CLAD PANELS**, size 7in. x 4in., pack of 2. Order Ref: 973.

**100M COIL OF CONNECTING WIRE**. Order Ref: 685.

**WHITE PROJECT BOX**, 78mm x 115mm x 35mm. Order Ref: 106.

**LEVER-OPERATED MICROSWITCHES**, ex-equipment, batch tested, any faulty would be replaced, pack of 10. Order Ref: 755.

**MAINS TRANSFORMER**, 12V-0V-12V, 6W. Order Ref: 811.

## THIS MONTH'S SPECIAL

IT IS A DIGITAL MULTITESTER, complete with backrest to stand it and hands-free test prod holder. This tester measures d.c. volts up to 1,000 and a.c. volts up to 750; d.c. current up to 10A and resistance up to 2 megs. Also tests transistors and diodes and has an internal buzzer for continuity tests. Comes complete with test prods, battery and instructions. Price £6.99. Order Ref: 7P29.



**1mA PANEL METER**. Approximately 80mm x 55mm, front engraved 0-100. Price £1.50 each. Order Ref: 1/16R2.

**VERY THIN DRILLS**. 12 assorted sizes vary between 0.6mm and 1.6mm. Price £1. Order Ref: 128.

**EVEN THINNER DRILLS**. 12 that vary between 0.1mm and 0.5mm. Price £1. Order Ref: 129.

**BT PLUG WITH TWIN SOCKET**. Enables you to plug 2 telephones into the one socket for all normal BT plugs. Price £1.50. Order Ref: 1.5P50.

**D.C. MOTOR WITH GEARBOX**. Size 60mm long, 30mm diameter. Very powerful, operates off any voltage between 6V and 24V D.C. Speed at 6V is 200 rpm, speed controller available. Special price £3 each. Order Ref: 3P108.

**FLASHING BEACON**. Ideal for putting on a van, a tractor or any vehicle that should always be seen. Uses a Xenon tube and has an amber coloured dome. Separate fixing base is included so unit can be put away if desirable. Price £5. Order Ref: 5P267.

**MOST USEFUL POWER SUPPLY**. Rated at 9V 1A, this plugs into a 13A socket, is really nicely boxed. £2. Order Ref: 2P733.

**MOTOR SPEED CONTROLLER**. These are suitable for D.C. motors for voltages up to 12V and any power up to 1/6h.p. They reduce the speed by intermittent full voltage pulses so there should be no loss of power. In kit form these are £12. Order Ref: 12P34. Or made up and tested, £20. Order Ref: 20P39.

**BT TELEPHONE EXTENSION WIRE**. This is proper heavy duty cable for running around the skirting board when you want to make a permanent extension. 4 cores properly colour coded, 25m length. Only £1. Order Ref: 1067.

**LARGE TYPE MICROSWITCH** with 2in. lever, changeover contacts rated at 15A at 250V, 2 for £1. Order Ref: 1/2R7.

**BALANCE ASSEMBLY KITS**. Japanese made, when assembled ideal for chemical experiments, complete with tweezers and 6 weights 0.5 to 5 grams. Price £2. Order Ref: 2P44.

**CYCLE LAMP BARGAIN**. You can have 100 6V 0.5A MES bulbs for just £2.50 or 1,000 for £20. They are beautifully made, slightly larger than the standard 6.3V pilot bulb so they would be ideal for making displays for night lights and similar applications.

**DOORBELL PSU**. This has AC voltage output so is ideal for operating most doorbells. The unit is totally enclosed so perfectly safe and it plugs into a 13A socket. Price only £1. Order Ref: 1/30R1.

**INSULATION TESTER WITH MULTIMETER**. Internally generates voltages which enable you to read insulation directly in megohms. The multi-meter has four ranges, AC/DC volts, 3 ranges DC milliamps, 3 ranges resistance and 5 amp range. These instruments are ex-British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50 each, yours for only £7.50 with leads, carrying case £2 extra. Order Ref: 7.5P4.

**REPAIRABLE METERS**. We have some of the above testers but slightly faulty, not working on all ranges, should be repairable, we supply diagram, £3. Order Ref: 3P176.

### TWO MORE POST OFFICE INSTRUMENTS

Both instruments contain lots of useful parts, including sub-min toggle switch sold by many at £1 each. They are both in extremely nice cases, with battery compartment and flexible carrying handles, so if you don't need the instruments themselves, the case may be just right for a project you have in mind.

The first is **Oscillator 87F**. This has an output, continuous or interrupted, of 1kHz. It is in a plastic box size 115mm wide, 145mm high and 50mm deep. Price only £1. Order Ref: 7R1.

The other is **Amplifier Ref. No. 109G**. This is in a case size 80mm wide, 130mm high and 35mm deep. Price £1. Order Ref: 7R2.

### HEAVY DUTY POT

Rated at 25W, this is 20 ohm resistance so it could be just right for speed controlling a d.c. motor or device or to control the output of a high current amplifier. Price £1. Order Ref: 1/33L1.

### STEPPER MOTOR

Made by Philips as specified for the wind-up torch in the Oct '00 Practical Electronics is still available, price £2. Order Ref: 2P457.

**SOLDERING IRON**, super mains powered with long-life ceramic element, heavy duty 40W for the extra special job, complete with plated wire stand and 245mm lead, £3. Order Ref: 3P221.

## RELAYS

We have thousands of relays of various sorts in stock, so if you need anything special give us a ring. A few new ones that have just arrived are special in that they are plug-in and come complete with a special base which enables you to check voltages of connections of it without having to go underneath. We have 6 different types with varying coil voltages and contact arrangements. All contacts are rated at 10A 250V AC.



Coil Voltage	Contacts	Price	Order Ref:
12V DC	4-pole changeover	£2.00	FR10
24V DC	2-pole changeover	£1.50	FR12
24V DC	4-pole changeover	£2.00	FR13
240V AC	1-pole changeover	£1.50	FR14
240V AC	4-pole changeover	£2.00	FR15

Prices include base

### MINI POWER RELAYS

For p.c.b. mounting, size 28mm x 25mm x 12mm, all have 16A changeover contacts for up to 250V. Four versions available, they all look the same but have different coils:

6V Order Ref: FR17  
12V Order Ref: FR18  
24V Order Ref: FR19  
48V Order Ref: FR20

Price £1 each less 10% if ordered in quantities of 10, same or mixed values.

**NOT MUCH BIGGER THAN AN OXO CUBE**. Another relay just arrived is extra small with a 12V coil and 6A changeover contacts. It is sealed so it can be mounted in any position or on a p.c.b. Price 75p each, 10 for £6 or 100 for £50. Order Ref: FR16.

**RECHARGEABLE NICAD BATTERIES**. AA size, 25p each, which is a real bargain considering many firms charge as much as £2 each. These are in packs of 10, coupled together with an output lead so are a 12V unit but easily dividable into 2 x 6V or 10 x 1.2V. £2.50 per pack, 10 packs for £25 including carriage. Order Ref: 2.5P34.

**FOR QUICK HOOK-UPS**. You can't beat leads with a croc clip each end. You can have a set of 10 leads, 2 each of 5 assorted colours with insulated crocodile clips on each end. Lead length 36cm, £2 per set. Order Ref: 2P459.



**BIG 12V TRANSFORMER**. It is 55VA so that is over 4A which is normal working, intermittently it would be a much higher amperage. Beautiful transformer, well made and very well insulated, terminals are in a plastic frame so can't be accidentally touched. Price £3.50. Order Ref: 3.5P20.


## BUY ONE GET ONE FREE

**ULTRASONIC MOVEMENT DETECTOR**. Nicely cased, free standing, has internal alarm which can be silenced. Also has connections for external speaker or light. Price £10. Order Ref: 10P154.

**CASED POWER SUPPLIES** which, with a few small extra components and a bit of modifying, would give 12V at 10A. Originally £9.50 each, now 2 for £9.50. Order Ref: 9.5P4.

**3-OCTAVE KEYBOARDS** with piano size keys, brand new, previous price £9.50, now 2 for the price of one. Order Ref: 9.5P5.

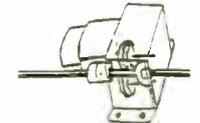**1.5V-6V MOTOR WITH GEARBOX**. Motor is mounted on the gearbox which has interchangeable gears giving a range of speeds and motor torques. Comes with full instructions for changing gears and calculating speeds, £7. Order Ref: 7P26.



### MINI BLOWER HEATER.

1kW, ideal for under desk or airing cupboard, etc., needs only a simple mounting frame, price £5. Order Ref: 5P23.

### TERMS

Send cash, PO, cheque or quote credit card number - orders under £25 add £4.50 service charge.

## J & N FACTORS

Pilgrim Works (Dept.E.E.)

Stairbridge Lane, Bolney

Sussex RH17 5PA

Telephone: 01444 881965

E-mail: jnfactors@aol.com

**MAIL ORDER ONLY • CALLERS BY APPOINTMENT**

**EPE MICROCONTROLLER P.I. TREASURE HUNTER**

The latest MAGENTA DESIGN – highly stable & sensitive – with I.C. control of all timing functions and advanced pulse separation techniques.

- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

**KIT 847 ..... £63.95**

**PORTABLE ULTRASONIC PEST SCARER**

A powerful 23kHz ultrasound generator in a compact hand-held case. MOSFET output drives a special sealed transducer with intense pulses via a special tuned transformer. Sweeping frequency output is designed to give maximum output without any special setting up.

**KIT 842.....£22.56**

**68000 DEVELOPMENT TRAINING KIT**

- NEW PCB DESIGN
- 8MHz 68000 16-BIT BUS
- MANUAL AND SOFTWARE
- 2 SERIAL PORTS
- PIT AND I/O PORT OPTIONS
- 12C PORT OPTIONS

**KIT 621**

**£99.95**

- ON BOARD 5V REGULATOR
- PSU £6.99
- SERIAL LEAD £3.99

**Stepping Motors**

MD38...Mini 48 step...£8.65

MD35...Std 48 step...£9.99

MD200...200 step...£12.99

MD24...Large 200 step...£22.95



**PIC PIPE DESCALER**

- SIMPLE TO BUILD
- HIGH POWER OUTPUT
- AUDIO & VISUAL MONITORING
- SWEPT FREQUENCY

An affordable circuit which sweeps the incoming water supply with variable frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve lathering ability by altering the way salts in the water behave. Kit includes case, P.C.B., coupling coil and all components. High coil current ensures maximum effect. L.E.D. monitor.

**KIT 868 ..... £22.95 POWER UNIT.....£3.99**



**MICRO PEST SCARER**

Our latest design – The ultimate scarer for the garden. Uses special microchip to give random delay and pulse time. Easy to build reliable circuit. Keeps pets/pests away from newly sown areas, play areas, etc. uses power source from 9 to 24 volts.

- RANDOM PULSES
- HIGH POWER
- DUAL OPTION

**KIT 867.....£19.99**

**KIT + SLAVE UNIT.....£32.50**



Plug-in power supply £4.99

**WINDICATOR**

A novel wind speed indicator with LED readout. Kit comes complete with sensor cups, and weatherproof sensing head. Mains power unit £5.99 extra.

**KIT 856.....£28.00**

**★ TENS UNIT ★**

**DUAL OUTPUT TENS UNIT**

As featured in March '97 issue.

Magenta have prepared a FULL KIT for this excellent new project. All components, PCB, hardware and electrodes are included. Designed for simple assembly and testing and providing high level dual output drive.

**KIT 866. . Full kit including four electrodes £32.90**

Set of 4 spare electrodes £6.50

**1000V & 500V INSULATION TESTER**



Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms.

Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

**KIT 848..... £32.95**

**EPE TEACH-IN 2000**

Full set of top quality NEW components for this educational series. All parts as specified by EPE. Kit includes breadboard, wire, croc clips, pins and all components for experiments, as listed in introduction to Part 1.

\*Batteries and tools not included.

**TEACH-IN 2000 -**

**KIT 879 £44.95**

**MULTIMETER £14.45**

**SPACEWRITER**

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube plus instructions for message loading.

**KIT 849 .....£16.99**

**12V EPROM ERASER**

A safe low cost eraser for up to 4 EPROMS at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

**KIT 790 .....£29.90**

**SUPER BAT DETECTOR**

1 WATT O/P, BUILT IN SPEAKER, COMPACT CASE 20kHz-140kHz NEW DESIGN WITH 40kHz MIC.

A new circuit using a 'full-bridge' audio amplifier i.c., internal speaker, and headphone/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.

**KIT 861 .....£24.99**

ALSO AVAILABLE Built & Tested... £39.99



**MOSFET MKII VARIABLE BENCH POWER SUPPLY 0-25V 2-5A**

Based on our Mk1 design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.



**Kit No. 845 ..... £64.95**

**EPE PROJECT PICS**

Programmed PICs for all\* EPE Projects 16C84/18F84/16C71 All **£5.90 each** PIC16F877 now in stock **£10 inc. VAT & postage** (\*some projects are copyright)

**ULTRASONIC PEST SCARER**

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS

- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

**KIT 812.....£15.00**



## SIMPLE PIC PROGRAMMER

INCREDIBLE LOW PRICE! Kit 857 **£12.99**

INCLUDES 1-PIC16F84 CHIP  
SOFTWARE DISK, LEAD  
CONNECTOR, PROFESSIONAL  
PC BOARD & INSTRUCTIONS

Power Supply £3.99

EXTRA CHIPS:

PIC 16F84 £4.84

Based on February '96 EPE. Magenta designed PCB and kit. PCB with 'Reset' switch, Program switch, 5V regulator and test L.E.D.s, and connection points for access to all A and B port pins.

## PIC 16C84 DISPLAY DRIVER

INCLUDES 1-PIC16F84 WITH  
DEMO PROGRAM SOFTWARE  
DISK, PCB, INSTRUCTIONS  
AND 16-CHARACTER 2-LINE  
LCD DISPLAY

Kit 860 **£19.99**

Power Supply £3.99

FULL PROGRAM SOURCE  
CODE SUPPLIED - DEVELOP  
YOUR OWN APPLICATION!

Another super PIC project from Magenta. Supplied with PCB, industry standard 2-LINE x 16-character display, data, all components, and software to include in your own programs. Ideal development base for meters, terminals, calculators, counters, timers - Just waiting for your application!

## PIC 16F84 MAINS POWER 4-CHANNEL CONTROLLER & LIGHT CHASER

- WITH PROGRAMMED 16F84 AND DISK WITH SOURCE CODE IN MPASM
- ZERO VOLT SWITCHING MULTIPLE CHASE PATTERNS
- OPTO ISOLATED 5 AMP OUTPUTS
- 12 KEYPAD CONTROL
- SPEED/DIMMING POT.
- HARD-FIRED TRIACS


Kit 855 **£39.95**

LOTS OF OTHER APPLICATIONS

Now features full 4-channel chaser software on DISK and pre-programmed PIC16F84 chip. Easily re-programmed for your own applications. Software source code is fully 'commented' so that it can be followed easily.

## ICEBREAKER

□□□□□□□□□□

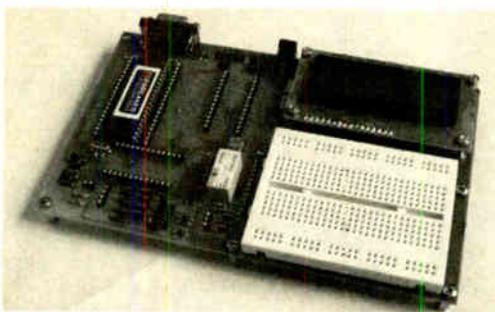

## PIC Real Time In-Circuit Emulator

- Icebreaker uses PIC16F877 in circuit debugger
- Links to Standard PC Serial Port (lead supplied)
- Windows™ (95+) Software included
- Works with MPASM and MPLAB Microchip software
- 16 x 2 L.C.D., Breadboard, Relay, I/O devices and patch leads supplied

As featured in March '00 EPE. Ideal for beginners AND advanced users. Programs can be written, assembled, downloaded into the microcontroller and run at full speed (up to 20MHz), or one step at a time. Full emulation means that all I/O ports respond exactly and immediately, reading and driving external hardware.

Features include: Reset; Halt on external pulse; Set Breakpoint; Examine and Change registers, EEPROM and program memory; Load program, Single Step with display of Status, W register, Program counter, and user selected 'Watch Window' registers.

Kit 900 . . . **£34.99**

POWER SUPPLY £3.99 STEPPING MOTOR £5.99

## EPE PIC Tutorial

At last! A Real, Practical, Hands-On Series

- Learn Programming from scratch using PIC16F84
- Start by lighting I.e.d.s and do 30 tutorials to Sound Generation, Data Display, and a Security System.
- PIC TUTOR Board with Switches, I.e.d.s, and on board programmer

### PIC TUTOR BOARD KIT

Includes: PIC16F84 Chip, TOP Quality PCB printed with Component Layout and all components\* (\*not ZIF Socket or Displays). Included with the Magenta Kit is a disk with Test and Demonstration routines.

KIT 870 .... **£27.95, Built & Tested .... £42.95**

Optional: Power Supply - £3.99, ZIF Socket - £9.99

LCD Display ..... **£7.99** LED Display ..... **£6.99**

Reprints Mar/Apr/May 98 - £3.00 set 3

## PIC TOOLKIT V2

- SUPER UPGRADE FROM V1 • 18, 28 AND 40-PIN CHIPS
- READ, WRITE, ASSEMBLE & DISASSEMBLE PICS
- SIMPLE POWER SUPPLY OPTIONS 5V-20V
- ALL SWITCHING UNDER SOFTWARE CONTROL
- MAGENTA DESIGNED PCB HAS TERMINAL PINS AND OSCILLATOR CONNECTIONS FOR ALL CHIPS
- INCLUDES SOFTWARE AND PIC CHIP

KIT 878 . . . **£22.99** with 16F84 . . . **£29.99** with 16F877

## SUPER PIC PROGRAMMER

- READS, PROGRAMS, AND VERIFIES
- WINDOWS® SOFTWARE
- PIC16C6X, 7X, AND 8X
- USES ANY PC PARALLEL PORT
- USES STANDARD MICROCHIP • HEX FILES
- OPTIONAL DISASSEMBLER SOFTWARE (EXTRA)
- PCB, LEAD, ALL COMPONENTS, TURNED-PIN SOCKETS FOR 18, 28, AND 40 PIN ICs

- SEND FOR DETAILED INFORMATION - A SUPERB PRODUCT AT AN UNBEATABLE LOW PRICE.

Kit 862 **£29.99**

Power Supply £3.99

DISASSEMBLER SOFTWARE **£11.75**

## PIC STEPPING MOTOR DRIVER

INCLUDES PCB, PIC16F84 WITH DEMO PROGRAM, SOFTWARE DISC, INSTRUCTIONS AND MOTOR.

Kit 863 **£18.99**

FULL SOURCE CODE SUPPLIED ALSO USE FOR DRIVING OTHER POWER DEVICES e.g. SOLENOIDS

Another NEW Magenta PIC project. Drives any 4-phase unipolar motor - up to 24V and 1A. Kit includes all components and 48 step motor. Chip is pre-programmed with demo software, then write your own, and re-program the same chip! Circuit accepts inputs from switches etc and drives motor in response. Also runs standard demo sequence from memory.

## 8-CHANNEL DATA LOGGER

As featured in Aug./Sept. '99 EPE. Full kit with Magenta redesigned PCB - LCD fits directly on board. Use as Data Logger or as a test bed for many other 16F877 projects. Kit includes programmed chip, 8 EEPROMs, PCB, case and all components.

KIT 877 **£49.95** inc. 8 x 256K EEPROMS

# MAGENTA

All prices include VAT. Add £3.00 p&p. Next day £6.99

Tel: 01283 565435 Fax: 01283 546932 E-mail: sales@magenta2000.co.uk

092001



Station Road, Cullercoats, Tyne & Wear, NE30 4PQ

Prices Exclude Vat @ 17.5%... UK Carriage £1.50 (less than 1kg) £3.50 greater than 1kg

See Next / Last Months Ad. for ELECTRONIC COMPONENTS

DIL Sockets table with columns for pin count and price

Stamped Pin table with columns for pin count and price

ZIF Sockets table with columns for pin count and price

Transistor Sockets table with columns for pin count and price

IDC Cable Sockets table with columns for pin count and price

IDC Cable Plugs table with columns for pin count and price

PCB Box Headers table with columns for pin count and price

10 Way Straight table with columns for pin count and price

PCB Patch Headers table with columns for pin count and price

DIL Headers table with columns for pin count and price

Transition Headers table with columns for pin count and price

D Type Connectors table with columns for pin count and price

Solder Bucket table with columns for pin count and price

IDC Ribbon Mounting table with columns for pin count and price

Right Angled PCB table with columns for pin count and price

9 Way Male Plug table with columns for pin count and price

Plastic D Covers table with columns for pin count and price

Audio Connectors table with columns for pin count and price

Red Line Plug table with columns for pin count and price

XLR Series - metal table with columns for pin count and price

3 Pin Line Plug table with columns for pin count and price

3 Pin Chassis Plug table with columns for pin count and price

RF Connectors table with columns for type and price

Terminals table with columns for type and price

Power Connectors table with columns for type and price

IEC Mains 6A 250Vac table with columns for type and price

3 Pin IEC Line Socket table with columns for type and price

8 Way Bulgin table with columns for type and price

8 Pin Line Plug P551 table with columns for type and price

Toggle Switches table with columns for type and price

Sub-Miniature table with columns for type and price

Miniature table with columns for type and price

Standard table with columns for type and price

Slide Switches table with columns for type and price

Miniature table with columns for type and price

Standard table with columns for type and price

Rotary Switches table with columns for type and price

150mA 250V Make before table with columns for type and price

Break 22mm Ø table with columns for type and price

Push Switches table with columns for type and price

Miniature Round table with columns for type and price

Standard Square table with columns for type and price

1A 250V table with columns for type and price

Rocker Switches table with columns for type and price

Miniature table with columns for type and price

Standard table with columns for type and price

Relays table with columns for type and price

Computer Accessories table with columns for type and price

9M Gender Changer table with columns for type and price

25M Gender Changer table with columns for type and price

Yesters / Patch Boxes table with columns for type and price

Leads & Cables table with columns for type and price

1.5m Printer Lead table with columns for type and price

2m BD Printer Lead table with columns for type and price

5m IEEE1284 Printer L table with columns for type and price

25Mole to 25Femole table with columns for type and price

PC Link Leads table with columns for type and price

Patch Lead table with columns for type and price

Internal Leads table with columns for type and price

Networking table with columns for type and price

Boxes & Cases table with columns for type and price

General Purpose Plastic table with columns for type and price

Dilecast Aluminium table with columns for type and price

Wire & Cable Ribbon Cable table with columns for type and price

Unannealed Copper Wire table with columns for type and price

Tinned Copper Wire table with columns for type and price

Equipment Wire table with columns for type and price

Extra Flex Cable table with columns for type and price

Crystals table with columns for type and price

HC-49/U Case table with columns for type and price

CMOS Black & White table with columns for type and price

660-800 £23.75 + vol table with columns for type and price

660-812 £29.21 + vol table with columns for type and price

660-816 £32.18 + vol table with columns for type and price

660-812 £29.21 + vol table with columns for type and price

660-816 £32.18 + vol table with columns for type and price

660-812 £29.21 + vol table with columns for type and price

660-816 £32.18 + vol table with columns for type and price

660-812 £29.21 + vol table with columns for type and price

660-816 £32.18 + vol table with columns for type and price

660-812 £29.21 + vol table with columns for type and price

3.2768MHz table with columns for type and price

Low Profile Crystals, 2 & 3 Pin Ceramic Resonators table with columns for type and price

Opto Electronics LEDs table with columns for type and price

7 Segment Displays table with columns for type and price

Infra Red Diodes table with columns for type and price

3mm IR Emitter table with columns for type and price

5mm IR Emitter table with columns for type and price

5mm Photo-Transistor table with columns for type and price

Photo Diode table with columns for type and price

4N26 Opto-Coupler table with columns for type and price

4N32 Opto-Coupler table with columns for type and price

6N135 Opto-Coupler table with columns for type and price

6N136 Opto-Coupler table with columns for type and price

6N137 Opto-Coupler table with columns for type and price

6N138 Opto-Coupler table with columns for type and price

6N139 Opto-Coupler table with columns for type and price

CNY17-1 O-Coupler table with columns for type and price

CNY17-2 O-Coupler table with columns for type and price

IS-74 Opto-Coupler table with columns for type and price

ISD-74 Opto-Coupler table with columns for type and price

CCTV Camera Modules & Systems

CMOS Black & White Sub-Miniature (24 x 24 x 27mm) 110k Pixel

CMOS Colour Miniature + Audio (31 x 31 x 28mm) Sensor 270k Pixel >7 Lux

Full range & detailed specs. available upon request. Complete outdoor systems also stocked.

Technical books & CD ROMs

Full details of UK, European or World-wide Order information on our web site.

# EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

## VOL. 30 No. 9 SEPTEMBER 2001

### VARIETY

I have commented on the variety this job offers in past Editorials, what is also of interest is the variety of projects we are able to offer. We can take little responsibility for the wide range of designs – these are mostly down to the inventiveness of contributors. Sometimes we will ask authors for a particular project, but very often the ideas will come from them and, as you can tell, they are an inventive lot.

This month is no exception – one project, from our long-standing regular contributor Andy Flind, has been designed following a request from a reader, this is the *Synchronous Clock Driver*. Andy also designed the *L.E.D. Torches* for his own use – see his introduction in the article. John Becker, our Technical Editor, has come up with another PIC-based project which develops some previously published designs. In addition to these, Thomas Scarborough has come up with a range of solar-powered projects as part of the *Perpetual Projects* series.

### NEXT MONTH

Next month the variety is stretched even further with a *Two-Valve Shortwave Receiver* from Robert Penfold and perhaps the ultimate, up-to-the-minute design of *PIC Toolkit TK3 for Windows* from John Becker; together with new Visual Basic software with extensive facilities. There will also be some more *Perpetual Projects*.

### THERE'S MORE

Just to whet your appetite even further we have the following unusual projects in the pipeline: *Ghost Buster* – experimental device for detecting low frequency standing waves; *Virus Zapper* – can a simple circuit kill the common cold? *Forever Flasher* – free power for an l.e.d. flashing circuit. Don't miss them.

And, oh yes, we have *Teach-In 2002* starting in the November issue, it's a bit different to previous series and will be of interest to a very wide range of readers – more details next month.



### AVAILABILITY

Copies of *EPE* are available on subscription anywhere in the world (see below), from all UK newsagents (distributed by COMAG) and from the following electronic component retailers: Omni Electronics and Yebo Electronics (S. Africa). *EPE* can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased and downloaded for just \$9.99(US) per year available from [www.epemag.com](http://www.epemag.com)

### SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the

UK: 6 months £14.50, 12 months £27.50, two years £50; Overseas: 6 months £17.50 standard air service or £27 express airmail, 12 months £33.50 standard air service or £51 express airmail, 24 months £62 standard air service or £97 express airmail.

Online subscriptions, for downloading the magazine via the Internet, \$9.99(US) for one year available from [www.epemag.com](http://www.epemag.com).

Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subs. Dept., Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. E-mail: [subs@epemag.wimborne.co.uk](mailto:subs@epemag.wimborne.co.uk). Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Switch or Visa. (For past issues see the *Back Issues* page.)

### BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £5.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Amex, Diners Club, Switch and MasterCard accepted, minimum card order £5. Send, fax or phone your card number and card expiry date with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

### Editorial Offices:

EVERYDAY PRACTICAL ELECTRONICS EDITORIAL  
WIMBORNE PUBLISHING LTD., 408 WIMBORNE ROAD EAST,  
FERNDOWN, DORSET BH22 9ND  
Phone: (01202) 873872. Fax: (01202) 874562.

E-mail: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk)

Web Site: <http://www.epemag.wimborne.co.uk>

EPE Online [www.epemag.com](http://www.epemag.com)

EPE Online Shop: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

See notes on Readers' Enquiries below – we regret lengthy technical enquiries cannot be answered over the telephone.

### Advertisement Offices:

EVERYDAY PRACTICAL ELECTRONICS ADVERTISEMENTS

MILL LODGE, MILL LANE

THORPE-LE-SOKEN, ESSEX CO16 0ED

Phone/Fax: (01255) 861161

E-mail: [epeads@aol.com](mailto:epeads@aol.com)

Editor: MIKE KENWARD

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Administration: FAY KENWARD

Editorial/Admin: (01202) 873872

Advertisement Manager:

PETER J. MEW, Frinton (01255) 861161

Advertisement Copy Controller:

PETER SHERIDAN, (01202) 873872

On-Line Editor: ALAN WINSTANLEY

EPE Online (Internet version) Editors:

CLIVE (MAX) MAXFIELD and ALVIN BROWN

### READERS' ENQUIRIES

E-mail: [techdept@epemag.wimborne.co.uk](mailto:techdept@epemag.wimborne.co.uk)

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons. All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

### COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers (see *Shoptalk*). We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

### ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

### TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.



# Constructional Project

# WATER MONITOR



**JOHN BECKER**

*How costly is it to keep your garden watered? Find out, and control it!*

**M**UCH water has “flowed under the bridge” since the author’s original *Digital Water Meter* was published in *EPE* June 1994. Indeed, in many parts of the UK, probably far too much has flowed this year!

Interestingly, that meter was designed at a time of great drought in Southern England and there were concerns that water should be conserved for ecological reasons. This too was a time when UK households were in the process of going over to paying for water by quantity used rather than according to a fixed annual charge.

In this respect, people were wondering whether they would be better or worse off by going over to Water Company metering. The meter was designed to enable readers to pre-assess their consumption before taking the irreversible step of allowing the Water Company to install their own meter.

These days most households probably have water metering installed as standard. It is still beneficial, though, to keep track of how much the water bill has been clocked up by watering the garden.

## WATER CONSUMPTION

It is worth noting, however, that garden watering is not the only cause of significant water use. The UK Government’s Office of Water Services (OFWAT) quotes the following domestic water supply statistics:

Appliance	Average use (litres)	Percentage of average total use
Household per day	380	100%
Washing machine	110	12%
Dishwasher	55	1%
Bath	80	17%
Shower	35	
WC	9.5	32%
Garden hose	540 per hour	3%
Drinking/cooking	–	2.5%
Miscellaneous	–	32.5%

## WATER MONITOR

Terry de Vaux-Balbirnie tackled one aspect of garden watering consumption

with his *Hosepipe Controller* of June ‘01. His design allowed watering to be automatically cut-off after a preset period.

The Water Monitor presented now also allows preset water cut-off, but has the additional benefit of actually telling you the cost of the water that has been used to keep the grass green.

The design is PIC controlled and includes a 32-digit alphanumeric liquid crystal display (l.c.d.). The Water Company’s charge per cubic metre of water used is entered via pushbutton switches and is automatically stored for future recall. The l.c.d. shows the elapsed time since watering started (24-hour clock), the number of litres used (99999 max.) and their cumulative cost (£99.99 – or \$ etc. – max.).

The original intention had been to provide only this information. Editor Mike, however, made the valid suggestion that it would be useful if the meter could also control the duration of water flow. This facility has been added as a simple optional extra, although it is not used in the author’s prototype shown in the photographs.

The duration can be set in steps of 10 minutes up to a total period of nine hours

50 minutes. It can be manually terminated earlier than the preset period if desired. The facility can be bypassed to allow unlimited water flow. The preset time is also stored for future recall.

Additionally, the meter allows the litres and cost count to be reset each time it is used, or to continue counting from the previous values reached when the meter was last used.

Cut-off duration and Water Company price per cubic metre can be changed as often as you require.


## CIRCUIT DESCRIPTION

Not only has the UK experienced a change from drought to frequent flood conditions since the author’s original water meter was published, but electronics technology has improved dramatically. This has allowed a much simpler and yet more sophisticated design to be published now – it is also cheaper to build!

The original meter used 14 integrated circuits and a 4-digit 7-segment l.c.d. The new design uses two i.c.s (the PIC microcontroller and a voltage regulator) and an “intelligent” alphanumeric l.c.d. The water flow sensor is the same as previously used.

Whereas the original cost about £70 to build, the new one costs about £35.

The circuit diagram for the Water Monitor, without the optional water control feature, is shown in Fig.1.

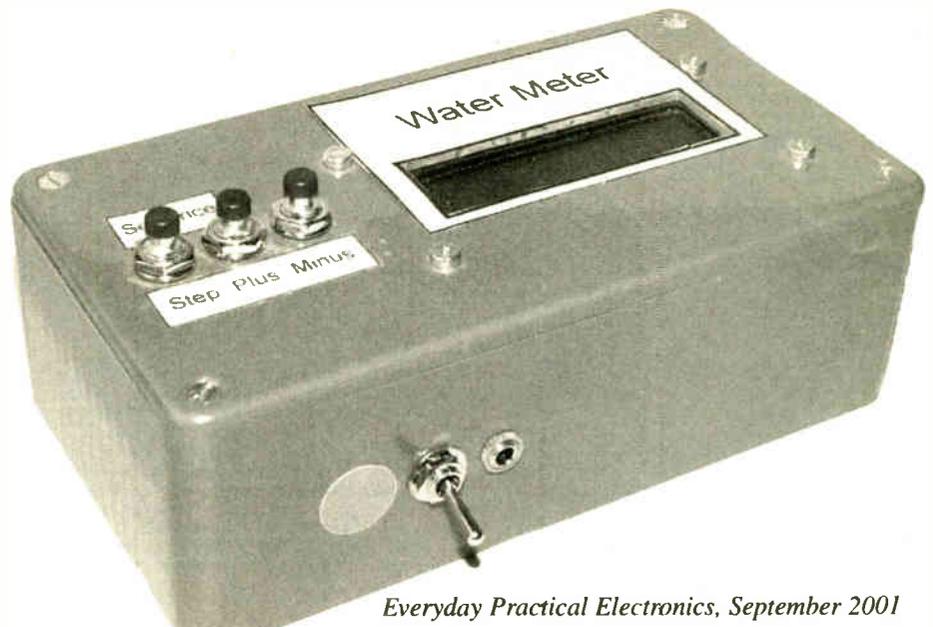

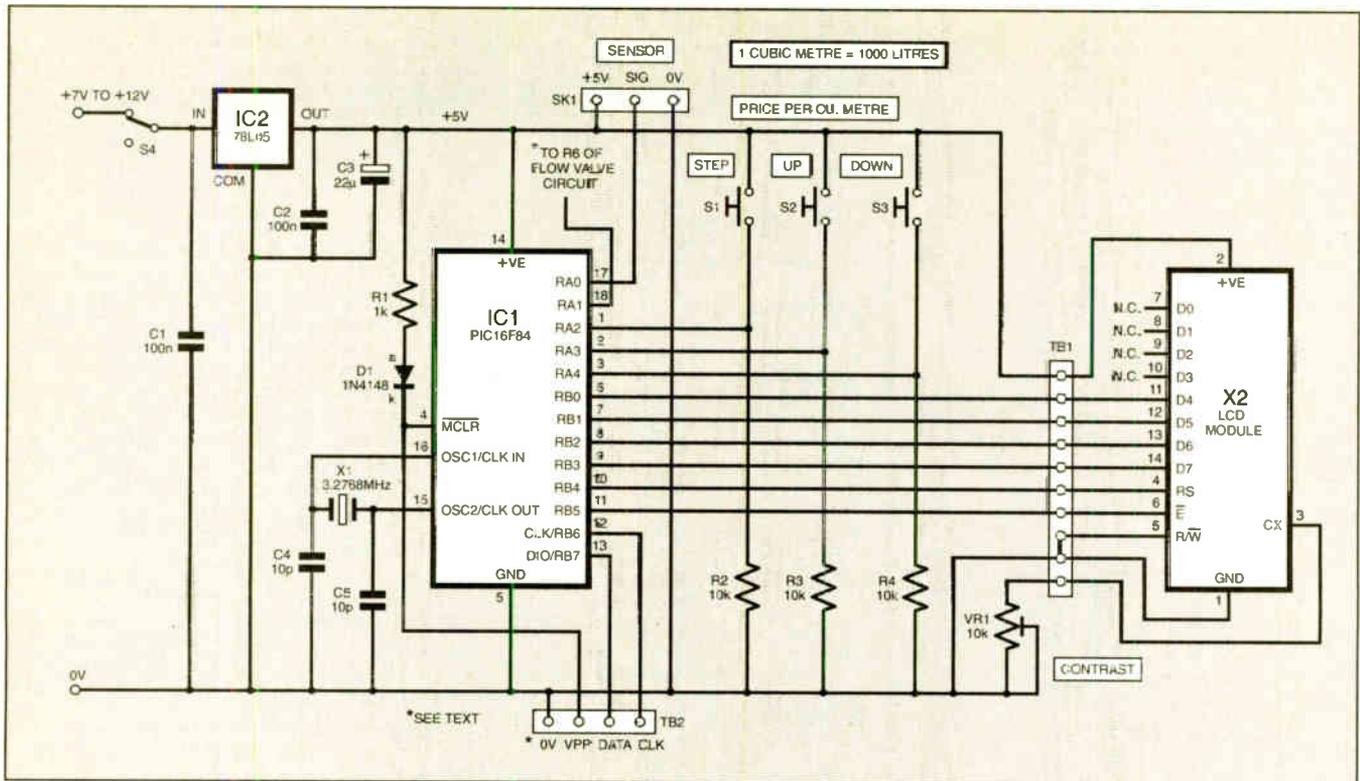


Fig. 1. Circuit diagram for the Water Monitor control and display.

A PIC16F84 microcontroller is used, designated as IC1. It is operated at 3.2768MHz, as set by crystal X1. Pulses are input to the PIC from the water sensor (discussed presently) via socket SK1 to port pin RA0. Processed data is output to the l.c.d., X2, which is operated under conventional 4-bit mode. Preset VR1 allows for l.c.d. contrast adjustment.

Switches S1 to S3 are used to set the cost per cubic metre and the water cut-off duration. They are operated in push-to-make mode, with PIC pins RA2 to RA4 normally biased to 0V via resistors R2 to R4. When the switches are pressed, the relevant PIC pin is taken high (+5V). Port pin RA1 is used to control the optional water flow valve described later.

The PIC may be programmed *in situ* via connector TB2. The pins are in the author's standard order for use with *EPE* PIC programmer *Toolkit Mk2*. Resistor R1 and diode D1 prevent regulator IC2 from being "distressed" by the voltages involved during programming.

The unit may be powered at between about 7V and 15V d.c. The prototype draws 32.5mA with the sensor connected, 8.7mA without. It is not intended to be battery operated (unless a heavy duty battery is used, external to the unit). The prototype is powered from a bench power supply, although a mains powered d.c. "battery adaptor" may be used instead.

**DO NOT use the control unit outdoors or anywhere near the water supply if it is in any way connected to the electrical mains, however remotely. Normal mains electricity safety considerations must be observed.**

The controlling PIC software is available on 3.5-inch disk (for which a nominal handling charge applies) or free via the *EPE* web site. The files include the source code (TASM grammar) and both OBJ (TASM) and HEX (MPASM) format program codes. Pre-programmed PICs are

available through an independent supplier. See this month's *Shoptalk* column for details of all options.

### WATER FLOW SENSOR

As previously said, the water flow sensor (transducer) is the same as used in the original design. It is manufactured for use with heating and mains water supplies up to a temperature of about 70°C. It *must not*, however, be used to monitor drainage water sources, such as the outputs from kitchen sinks, baths, washing machines or similar, since it could become blocked.

In essence, the sensor comprises a pipe containing a small turbine mounted on sapphire bearings. Attached to the turbine, in a water-resistant housing, is a small electronic circuit, as shown in Fig.2.

Water flowing through the pipe causes the turbine to rotate at a rate proportional to the flow. Within the housing are a light emitting diode (l.e.d.) and a light sensitive diode. As the turbine blades rotate, they repeatedly interrupt the light path between the l.e.d. and the photodiode. The resulting voltage changes across the diode are amplified by the sensor's op.amp, shaped by the Schmitt trigger buffer and output at the transistor's collector.

The maximum output pulse level is that of the supply line which, in other applications, may be between about +4.5V and +16V d.c. For this monitor, the level is nominally +5V. An internal regulator drops the supply voltage to a fixed level suitable for the photodiode, op.amp and Schmitt trigger. The transistor's

collector load resistor is connected to the supply line, so in this application, the pulsed output swings between +5V and 0V.

The sensor's l.e.d. has to be used with an external series resistor, R5, whose value is chosen to suit the supply line. The maximum l.e.d. current is 30mA, although with the test model a current of about 22mA, as set by R5 at 220 ohms, was satisfactory.

Note that the sensor's circuit housing is not totally light-proof and that too high an l.e.d. current in the presence of high ambient light levels could cause the output to stay high.

A graph of the sensor's output pulse rates plotted against water flow is shown in Fig.3. It also shows the typical output pulse waveform which, it should be noted, does not have an equal mark-space ratio, i.e. it is not a square wave.

The sensor is capable of monitoring flow rates of about 1.5 to 30 litres per minute. Full scale frequency output is approximately 600Hz. Typically, the number of pulses per litre of flow is 1200. It is this figure that is used in the calculations made by the PIC microcontroller.

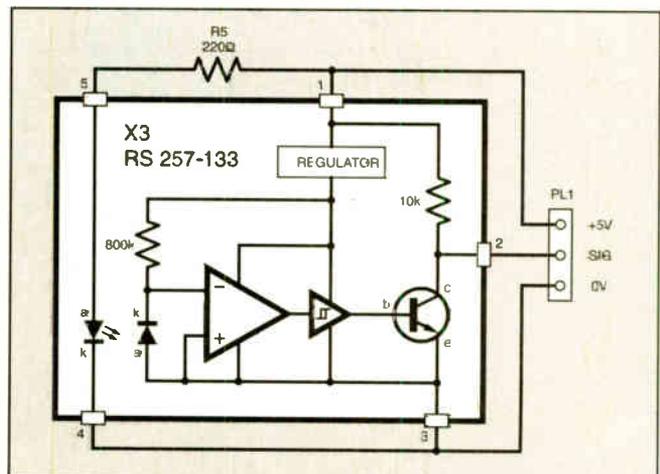


Fig.2. Diagram for the flow sensor's integral circuit.

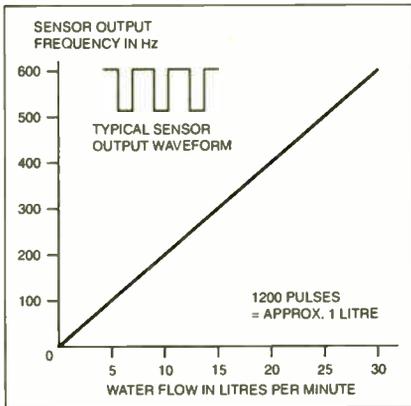


Fig.3. Sensor output pulse rates in relation to water flow.

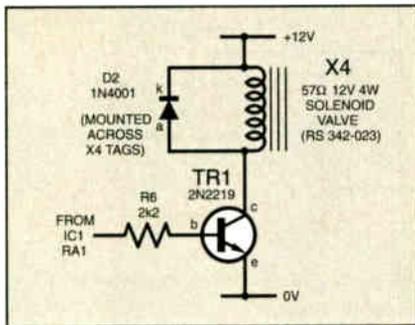


Fig.4. Optional water flow duration control circuit.

## SOLENOID VALVE

The optional facility which allows water flow to be switched on and off by the PIC is shown in Fig.4.

It consists of the solenoid valve, X4, and a controlling transistor, TR1. A high output level from PIC pin RA1 turns on the transistor via current limiting resistor R6. This causes the solenoid valve to turn on, allowing water to flow. When pin RA1 goes low, the valve is closed and water flow ceases.

The maximum flow rate for the valve is 17 litres per minute and its input water

# COMPONENTS

**Approx. Cost**  
**Guidance Only**  
**£35**  
*excl. case and solenoid*

### MONITORING UNIT

<b>Resistors</b>	R1 1k	<b>See SHOP TALK page</b>
	R2 to R4 10k (3 off)	
	R5 220Ω	
	All 0.25W 5% carbon film	
<b>Potentiometer</b>	VR1 10k min. round preset	
<b>Capacitors</b>	C1, C2 100n ceramic disc, 5mm pitch (2 off)	
	C3 22μ radial elect. 10V	
	C4, C5 10p ceramic disc, 5mm pitch	
<b>Semiconductors</b>	D1 1N4148 signal diode	
	IC1 PIC16F84-4 microcontroller (pre-programmed)	
	IC2 78L05 +5V 100mA voltage regulator	
<b>Miscellaneous</b>	S1 to S3 min. push-to-make switch (3 off)	
	S4 min s.p.d.t. toggle switch	
	SK1 3.5mm stereo jack socket (see text)	
	PL1 3.5mm stereo jack plug (see text)	
	TB1 10-way 1mm pin-header strip	
	TB2 4-way 1mm pin-header strip	
	X1 3.2768MHz crystal	
	X2 2-line 16-character (per line) alphanumeric I.c.d. module	
	X3 flow sensor module (RS 257-133 - see text)	

Printed circuit board, available from the *EPE PCB Service*, code 317; plastic case, 150mm x 80mm x 50mm; 3-way sensor connecting cable, small diameter, length to suit application; power input socket to suit; 18-way d.i.l. socket; p.c.b. supports, self-adhesive (4 off); nuts and bolts to suit I.c.d. module (4 off); plumbing connectors to suit (see text); connecting wire; solder, etc.

### FLOW CONTROL

<b>Resistor</b>	R6 2k2 0.25W 5% carbon film
<b>Semiconductors</b>	D2 1N4001 rectifier diode
	TR1 2N2219 npn transistor (see text)
<b>Miscellaneous</b>	X4 flow control solenoid valve 12V d.c. 57Ω coil (RS 342-023 - see text)

Cable, plug and socket, plus plumbing connectors to suit (see text); connecting wire; solder etc.

pressure must be between 0.2 and 10 bars (the author's domestic water pressure is about four bars).

Diode D2 is connected across the solenoid's coil to inhibit the generation of high voltage pulses (back-e.m.f.) at the moment of switching off the solenoid.

The solenoid requires a d.c. power supply of between 11.8V and 13.5V. It is nominally rated at 4W and has a coil resistance of 57Ω ±10 per cent. Typically, it will draw about 330mA.

A 2N2219 npn transistor is suggested for TR1 as this can switch a current of about 800mA. Any other similar transistor can be used instead. It is not in the least bit critical.

*This control facility must only be used in conjunction with garden hose monitoring. It could cause damage to other water-fed equipment.*

## CONSTRUCTION

Printed circuit board (p.c.b.) component and track layout details are shown in Fig.5.



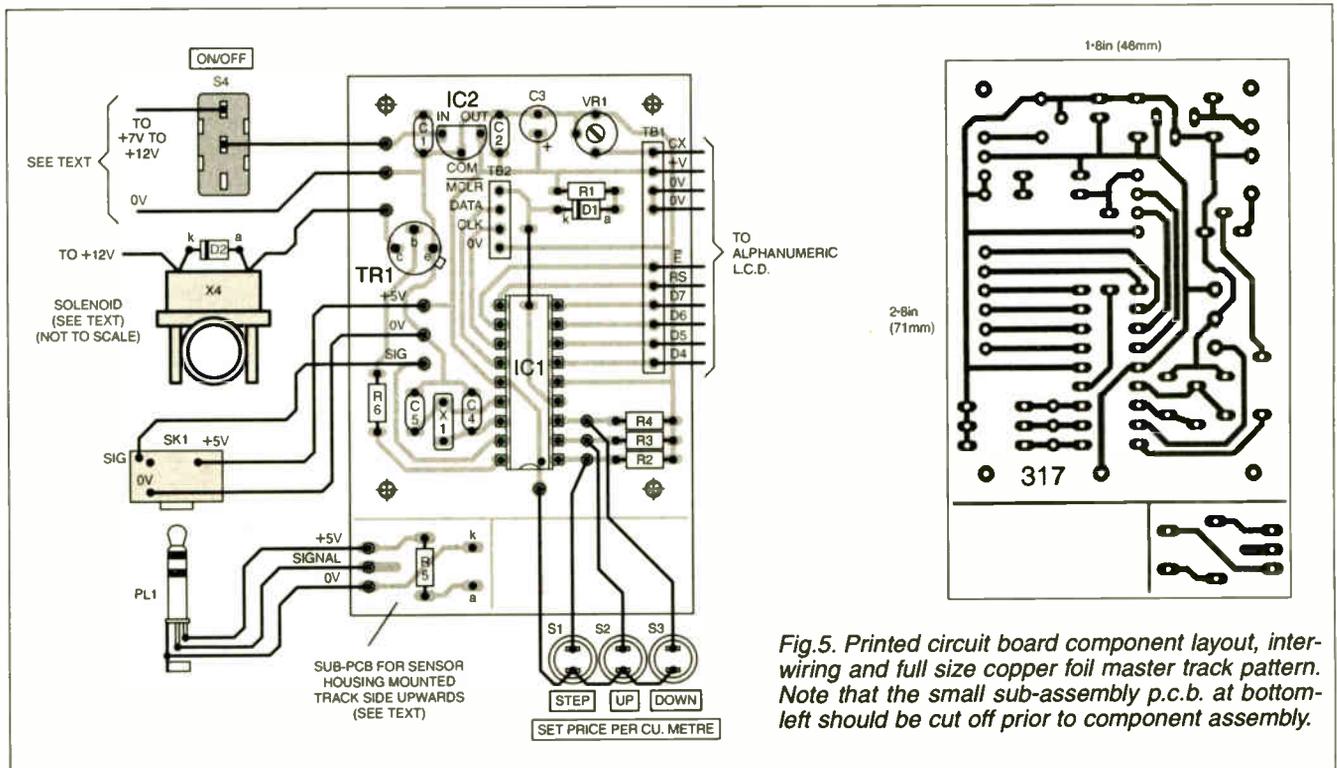


Fig.5. Printed circuit board component layout, inter-wiring and full size copper foil master track pattern. Note that the small sub-assembly p.c.b. at bottom-left should be cut off prior to component assembly.

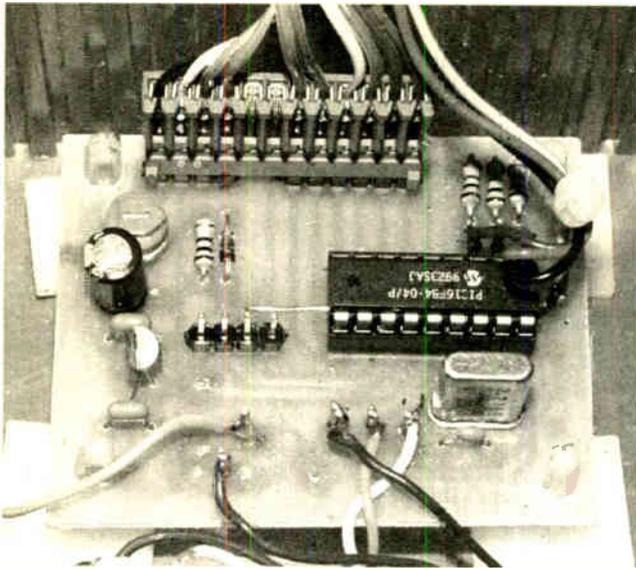

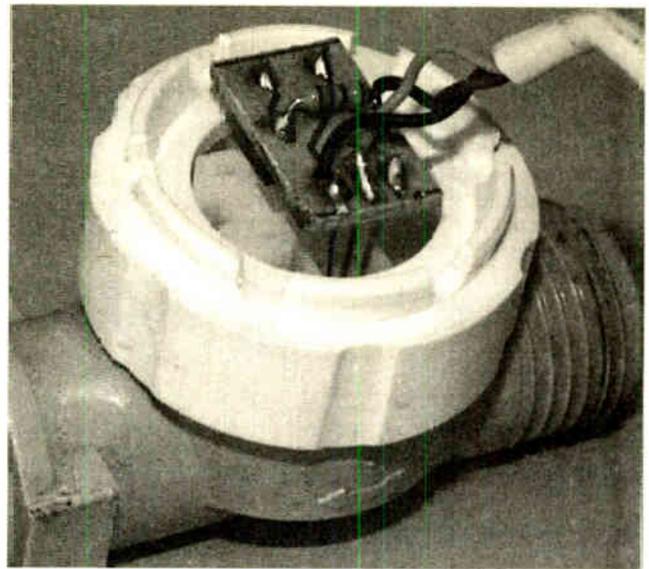Main p.c.b. in the prototype. The pin-header connector shown is optional and l.c.d. connections may be soldered if preferred.



Sub-assembly p.c.b. mounted inside the water flow sensor module.

This board is available from the *EPE PCB Service*, code 317.

At one corner of the p.c.b. is a small sub-assembly board which is for use with the water flow sensor. It should be carefully cut off before component assembly.

Assemble the main board in any component order you wish, but note that a link wire must be inserted before mounting the (essential) socket for IC1. Do not insert IC1 or the l.c.d. until you have checked that the output voltage from regulator IC2 is at +5V (within a few per cent).

The l.c.d. connections to the p.c.b. are, as usual, in the author's "standard" order. Connections to the l.c.d. itself could take one of two possible formats, as shown in Fig.6. The most likely is that on the left.

A schematic drawing of the sensor housing is shown in Fig.7. Gently, but firmly, prise off the cap on the housing using a thin-bladed tool. Inside will be seen five rigid wires. Carefully push these into the holes of the small sub-p.c.b., which should be trackside upwards, and solder them in position.

Now solder resistor R5 to the trackside, having first pushed its trimmed leads through the holes (see photo).

The sensor, of course, will be outdoors and the control unit some distance away indoors. Solder a suitable length of 3-core cable to the board and solder plug PL1 to the other end.

Do not connect the sensor to the water supply or main p.c.b. yet.

## CHECKING OUT

With the programmed PIC in place and the l.c.d. connected, switch on the power supply. Adjust l.c.d. preset VR1 until a reasonable display contrast is shown. At this time the information displayed will be "garbage", having been generated in relation to unknown values within the PIC's data EEPROM.

The first thing you need to do is to get some sensible data into the EEPROM. The process about to be described is that required whenever you wish to change the water price or flow duration, or to reset the cumulative values to zero.

Switch off the power supply, and wait a few moments to allow the capacitors to fully discharge. Now press switch S1

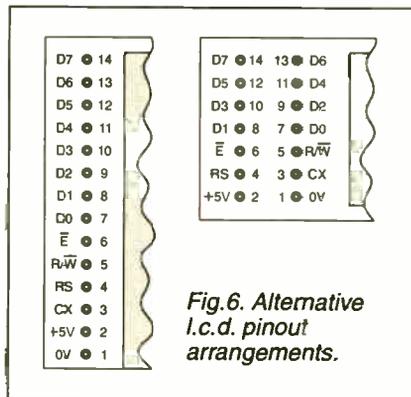


Fig.6. Alternative l.c.d. pinout arrangements.

(Step) and hold it down while you again switch on the power. Once the display is again active, release S1.

On the display's top line should be seen the message "SET PERIOD" towards the right. At the left, the first and third digits could be anything (actually the l.c.d.'s interpretation of any ASCII value between 48 and 63). Digits 2, 4 and 5 should show *h* (for hours), *0* units of minutes, and *m* (for minutes)

On line two below this digit will be seen a flashing asterisk. This indicates the digit that can be changed, in this case the first digit.

Pressing S2 (Up) will cause the first digit's value to increment, rolling over to 0 after 9. The rate of change while the switch is pressed is about twice per second. Pressing S3 (Down) causes the value to decrement, rolling over to 9 following 0.

This digit sets the number of hours for which you want the water turned on once the unit is activated. Set it for zero at the moment.

To select the next digit, press switch S1 again to cause the asterisk to move under digit 3. This shows the tens of minutes for which the water should remain on. It too can be varied between 0 and 9 using S2 and S3. Try it, but return to 0 for now.

That completes the water-on duration setting. In this particular instance the duration has been set for zero. The PIC has been programmed to never turn off water if the value is zero.

For a non-zero value, the PIC monitors a clock routine which commences when the unit is powered and any value changes (if any) have been completed.

## PRICE SETTING

Next the Water Company's cost per cubic metre value has to be entered. Press S1 again, causing the display to change.

The top line will now show the message "SET PRICE" at the left, and four random values plus a decimal point to the right. This asterisk will now be seen under the first random digit.

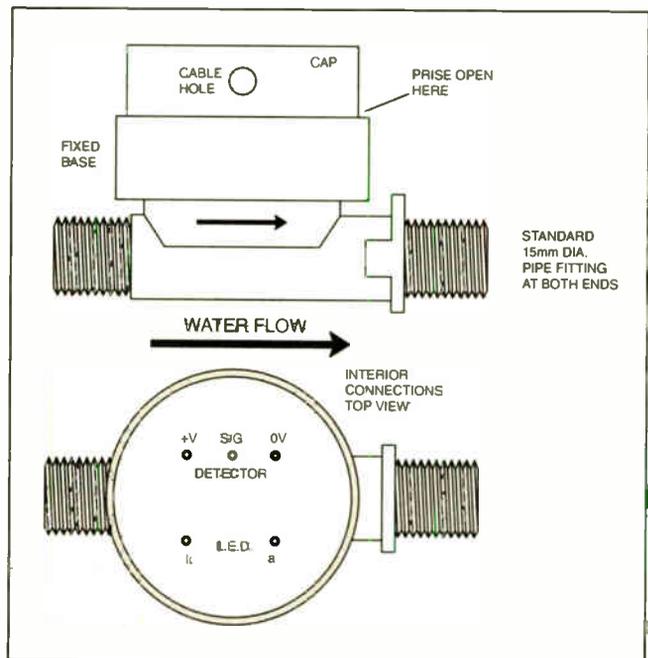


Fig.7. Schematic details of the water flow sensor module.

The righthand values show the price per cubic metre, in pence (or cents etc.) to the left of the decimal point, and tenths of a pence after it. The maximum value that can be set is 999.9 pence (or cents etc.) per cubic metre.

At the time of writing the author's Water Company charges 60.9 pence per cubic metre. The company actually shows the price on its invoices as having three decimal places. Such fine detail in this application seemed irrelevant and the last two digits of the Company's price are ignored. Remember that one cubic metre is 1000 litres, a lot of liquid! In this instance, one litre costs a mere 0.0609 pence (compare that to your petrol costs – or your bar bill!).

Again the digits can be changed using S2 and S3, with S1 causing the asterisk to step to the next digit. Refer to your last water bill and enter the cubic metre price shown.


At the final digit position, the next press of S1 ends the value setting routine, storing the values in the data EEPROM for subsequent use and recall. They remain there until changed, even after the power has been switched off.

The confirmation word "STORED" briefly appears on the top line when the data has been stored. Then the monitoring commences, turning on the solenoid valve if in use.
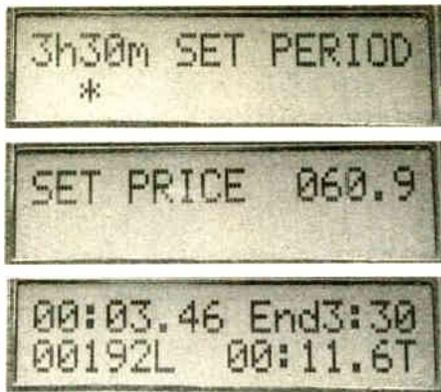
### RUN-MODE DISPLAY

The screen then shows its run-mode display, an hours-minutes-seconds count top left and the litres-consumed count bottom left, followed by letter L. Top right shows the word "End" plus the duration for which the water has been set to flow.

At the bottom right the cumulative cost of the litres used is shown, in the form "xx.yy.zT" where xx = pounds (or dollars etc.), yy = pence (or cents etc.) and z = tenths of a pence. Letter T simply means Total.



*Example displays: Setting water flow duration period; setting price per cubic metre; during monitoring.*

At present, only the clock value will be seen to be changing. There are no sensor pulses being input to affect the litres and cost values. These can be simulated, though, using a signal generator.

### PULSE TESTING

Connect the output of a digital signal generator (0V/5V square wave) to the unit's Signal input point on the p.c.b. Set the frequency to around 1200Hz (the number of pulses per litre).

Power up the unit again and observe the litres count incrementing at roughly once per second. Varying the frequency will vary the litre rate. The total cost value will be seen to change in relation to this.

Restart the unit as described earlier. This time set the water-on period for 10 minutes. Repeatedly press S1 to bypass the digit settings for cost, and allow monitoring to restart.

It will be seen that the clock, litres count and cost have started from zero. This reset always occurs when the unit is powered up with S1 pressed. The function causes the

cumulative flow and cost values to be reset and you can step past the preset duration and price values without changing them if you wish by using S1.

Observe the cumulative factors counting upwards again, until the clock reaches an elapsed time of 10 minutes. The PIC constantly monitors the clock in relation to the water-on duration set. When the two match, the message "FINISHED" is shown top right, monitoring stops, and port pin RA1 goes low, so shutting off the water solenoid if in use.

The litres count and cost values are automatically stored into the data EEPROM at this point. The software remains in this holding condition until power is switched off.

### REPETITION

On next switch-on, the stored values are all recalled, but the clock value is always reset to zero. This allows watering to be started each time the unit is switched on and to continue for the same preset duration, day after day if required.

Note that the unit only goes into Reset mode if switch S1 is held pressed while power is being switched on. It otherwise goes straight into monitoring mode.

At any time during monitoring, you can store the current cumulative counts by pressing any of switches S1 to S3 and then to switch off manually before the preset duration ends. If you switch off without storing the data, the existing cumulative values will be lost and those stored previously will be recalled on next power-up.

### PLUMBING

The water sensor has standard 15mm diameter plumbing fittings. It must be connected so that the water flows in the direction of the arrow moulded into its body. Use standard compression fittings when connecting the sensor to your water supply.

The solenoid valve has 0.5in B.S.P. connections. Compression


adaptors that allow this size to be connected to standard 15mm diameter pipes are available from the same source as the valve, or from plumbing retailers. The valve also has a water flow direction arrow moulded into its body and which must be followed.

Having "plumbed-up", electrically connect the solenoid to the control unit, via a suitable length of colour-coded cable plus its own plug and socket (not illustrated).

Alternatively, the entire system may be operated at 12V d.c., in which case it would be acceptable to connect the solenoid and water sensor to the unit via a single 4-core cable (+12V, 0V, signal, coil control), using a 4-pin plug and socket.

Solder diode D2 directly across the solenoid coil's terminals, ensuring the correct polarity. Wrap waterproof tape around the electrical connections.

The unit is now ready for use.

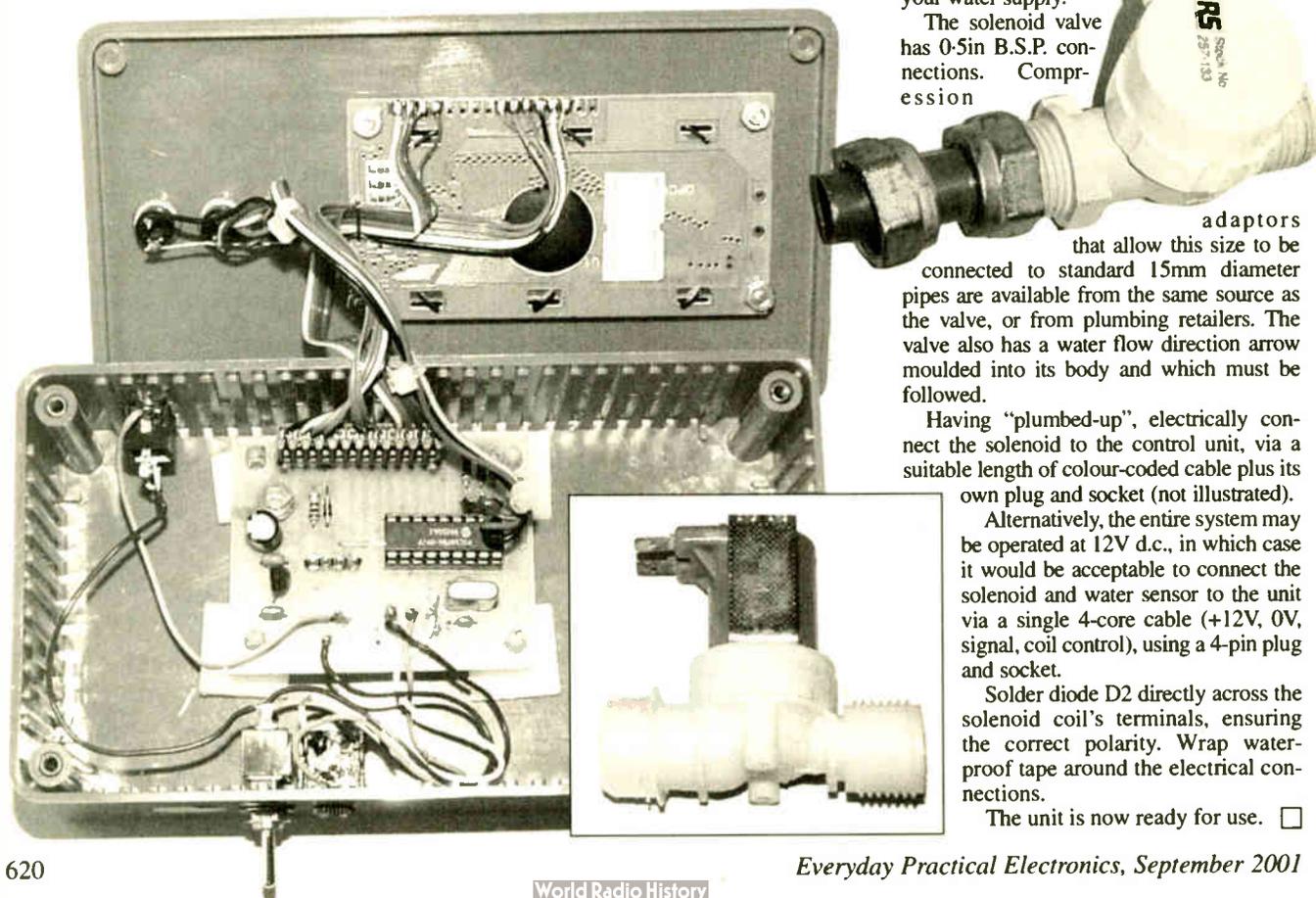

**SPECIAL  
READER -  
SEE WEBSITE  
FOR DETAILS**

# PROTEUS

## VSM


Virtual System Modelling

Build It In Cyberspace

[www.labcenter.co.uk](http://www.labcenter.co.uk)

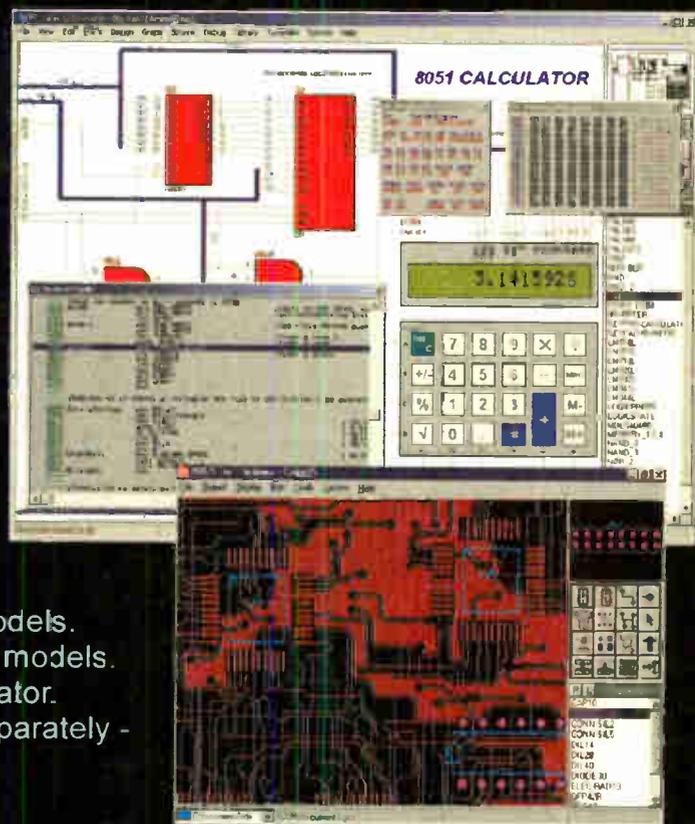**Develop and test complete micro-controller designs without building a physical prototype. PROTEUS VSM simulates the CPU and any additional electronics used in your designs. And it does so in real time. \***

- CPU models for PIC and 8051 and series micro-controllers available now. 68HC11 coming soon. More CPU models under development. See website for latest info.
- Interactive device models include LCD displays, RS232 terminal, universal keypad plus a range of switches, buttons, pots, LEDs, 7 segment displays and much more
- Extensive debugging facilities including register and memory contents, breakpoints and single step modes.
- Source level debugging supported for selected development tools.
- Integrated 'make' utility - compile and simulate with one keystroke.
- Over 4000 standard SPICE models included. Fully compatible with manufacturers' SPICE models.
- DLL interfaces provided for application specific models.
- Based on SPICE3F5 mixed mode circuit simulator.
- CPU and interactive device models are sold separately - build up your VSM system in affordable stages.
- ARES Lite PCB Layout also available.



**labcenter**  
Electronics

\*E.g. PROTEUS VSM can simulate an 8051 clocked at 12MHz on a 300MHz Pentium II

Write, phone or fax for your free demo CD or email [info@labcenter.co.uk](mailto:info@labcenter.co.uk).  
Tel: 01756 753440. Fax: 01756 752857. 53-55 Main St, Grassington. BD23 5AA.

# New Technology Update

*Not only do smaller i.c. packages reduce overall equipment sizes, but also help to reduce heat generation, reports Ian Poole.*

**C**OMPONENT packaging is a vitally important issue for electronics technology. It has been investigated in this column before (see May 2000). Whilst component packages may seem on the surface to be comparatively low tech when compared to the silicon that is mounted inside them, they are equally important, and surprisingly high tech.

It has been said that the package itself is not the limiting factor in terms of performance, but it can be considered that it enables the full performance to be realised. As a result, much development is invested by manufacturers to ensure that packaging technology keeps up with the improvements being made in the silicon itself.

These developments span the whole breadth of the semiconductor industry ranging from the simple discrete devices right up to the large high-speed processors.

## Small Packages

There is a steady trend to reduce the size of packages. To many people the fundamental driver for this is to reduce the size of electronic printed circuit boards. By reducing the area covered by the components it should be possible to reduce the board area required. However, the size reduction does not bear a linear relationship to the reduction in component size. Track routing becomes more difficult and if the same printed circuit board design rules are adopted there is a diminishing return on using smaller components.

There are other benefits of using smaller components. The main one is the increase in performance. This can manifest itself in a number of ways. One is an increase in speed. This is brought about by the fact that lead lengths are smaller and levels of stray inductance (ESL – equivalent series inductance), and to a lesser extent capacitance, are much reduced.

There are also other advantages. Thermal resistance can be reduced with careful package design, again because distances are smaller. In some instances optimised devices are able to dissipate over 50 per cent more in a smaller package purely as a result of the package design. In fact, over the past few years power devices have shrunk in size to the extent where many engineers who have been in the business for some time wonder whether these new components can handle the stated power!

A further advantage for power devices is that smaller packages bring shorter lead lengths and this can assist in reducing the levels of  $R_{DS(ON)}$ . A further reduction can be brought about by using multiple bond wires in the package. In many packages it is found that the internal bond wires

contribute significantly to the overall value of the ON resistance. Again this assists in the power handling capacity of the device because it means that the power dissipation within the device package is reduced.

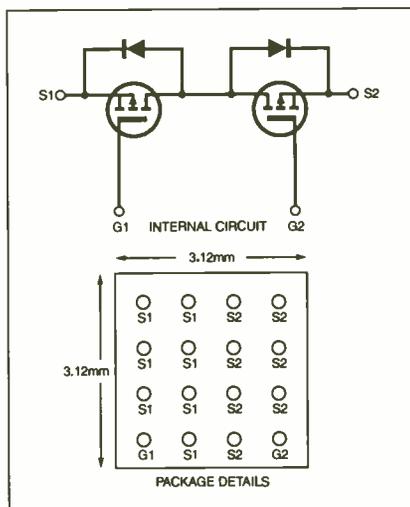


Fig.1. An example of a dual p-channel MOSFET in a chip scale package.

## Other Aspects

Further improvements can be brought about by the current trend towards chip scale packages (CSP). These are particularly useful for power MOSFETs. Whilst they are not full scale integrated circuits in the traditional sense of the term, several components can be integrated onto a single chip. This has the advantage of saving a considerable amount of board space because only one package is needed instead of two or more.

One example of this is where a back-to-back MOS switch is encapsulated in a 16-bump CSP, as shown in Fig.1. This device is aimed at use in a battery pack to provide switching and protection. The chip scale package occupies only 3.2mm x 3.1mm and contains all the interconnections, whereas a traditional package would require connections between the internal drain and source.

Typically this might be contained in a TSSOP (thin shrink small outline package) measuring about 3mm x 6mm, but additional tracks would be required on the printed circuit board that would take up additional space.

## Integrated Circuits

Not only are developments occurring in the discrete component arena but, as would be expected, there are many major initiatives being undertaken that will improve i.c. technology.

One of the major areas where problems are being encountered is with the

interconnections to the chip. No longer can the pin assignments be made to conform to what is easiest for the chip designer. With speed considerations being critical, a balance has to be made to find the best overall solution for the chip and printed circuit board design. Often the more critical inputs and outputs are allocated to areas that are more accessible to the tracks on the boards. In this way interference, ringing and other associated issues can be controlled.

## Leadless Packages

Thermal issues are again of great importance. With the massive levels of heat that are generated in many chips, it is imperative that all the thermal issues are fully addressed to ensure full performance and long term reliability.

One area of concern is associated with the thermal coefficients of expansion of the different materials used, particularly between silicon and board or substrate materials. With leaded components this was not a major concern because sufficient expansion could be taken up in the leads. However, with leadless packages the stress must be taken up in other areas.

To overcome this problem, Fairchild mounts its die onto a substrate that has an almost equivalent thermal coefficient of expansion to that of silicon. Wire bonds are then taken to the external pads and then the package is encapsulated using an organic material. Using this concept any strain occurs at the substrate/encapsulant interface and this affects neither the performance nor the reliability.

## Undercover

With chips becoming considerably more complex, far greater numbers of interconnects are required. In some cases 1000 or more may be needed, and this creates enormous problems as the chips become "pad bound". To overcome this, pads are placed under the chip to enable connections to be brought out from anywhere under the chip itself. This relieves the problems caused by having to bring out the connections to external bond points near the edge of the chip.

By removing the limitation of connection pad placement to be on the perimeter of the chip, or at least near to the edge, chip designers gain a considerable amount of flexibility, both in terms of the design itself and the number of connections that can be made.

Making connections under the chip is accomplished by a process involving the use of conductive "bumps" under the die. These bumps connect to equivalent connections on the carrier which can then be routed as required.

### YEDA 2001



The Young Electronics Designer Awards (YEDA) were made on 6 July at the Science Museum in London, during a special celebration dinner attended by 220 guests, including prizewinners, parents, teachers, local dignitaries and members of the business community.

Martin Rosinski (16) of Ponteland Community High School, Ponteland, Newcastle upon Tyne, scooped both the The Duke of York's Award and First Prize in the Intermediate category for the second year running, with his rail axle safety assessment device. This tiny unit has already attracted the interest of Railtrack and other major international rail network operators. Martin's device has the potential to prevent tragic accidents occurring as the result of broken or buckled rails, by using sophisticated electronics.

The Duke's Award resulted in cheque for £1000 to be shared between Martin and his school, together with a crystal trophy to be retained for one year and a hand painted certificate signed by His Royal Highness, plus a DVD player courtesy of Philips Electronics UK Ltd. Martin's Intermediate Prize was £750 plus a YEDA Trophy.

Amongst the other winners were Johnny Will and Harry Mustard (both 14) of Murchiston School, Edinburgh. Their childproof lock for power tools was deemed to be the most commercially viable project which earned them and their school £1000. Johnny and Harry also won the Junior Category (under 15 years) with their design, receiving a further £500 and a YEDA trophy.

The IEE Award for the best new entrant to YEDA went to Michael Porton (16) of Fitzalan High School, Leckwith, Cardiff, again with £1000 to be shared by himself and his school. Also highly motivated by safety aspects was Tammy Crawford-Rolt (16) of St Margaret's Senior School, Midhurst, West Sussex, who invented a variable temperature alarm for use with cooking and won £150.

The YEDA competition is open to students between the ages of 12 to 25 in secondary schools, colleges and universities. It challenges young designers to produce a novel electronic device that meets an everyday need. The overall objective is for contestants to have fun putting their ideas into practice and in doing so discover the exciting opportunities which a career in the electronics, communications and IT industries can offer.

More information and the full list of winners and their designs can be obtained from The YEDA Trust, 60 Lower Street, Pulborough, West Sussex RH20 2BW. Tel: 01798 875559. Fax: 01798 873550. E-mail: [yeda@cix.co.uk](mailto:yeda@cix.co.uk).

### B.A.E.C. SEEKS AUTHORS

Some while ago we reported that the British Amateur Electronics Club was in need of authors. Seemingly the situation has not been resolved and recently received B.A.E.C. information states that "continued publication of the Newsletter is in doubt" through shortage of articles.

The Club requires articles telling members what you know, passing on information which you may have acquired in years of experience or recently acquired in college. Any electronics-related subject will be of interest.

If an adequate supply of articles is not forthcoming, the Club says that it will have no choice except to wind up. That would be a great shame for an organisation that has existed for many decades and provided help, advice, information and interest for many hobbyists.

If you have knowledge to share and can put more than two words together on paper, for goodness' sake write something for the Club and help its continued existence!

For more details about the Club contact George Burton, Editor and Chairman, 581 Fishponds Road, Fishponds, Bristol BS16 3AA. Tel: 0117 965 4800. E-mail: [prontaprint.bristol@cablenet.co.uk](mailto:prontaprint.bristol@cablenet.co.uk). Mention *EPE* when contacting him.

### Bowood Cat

Bowood Electronics have sent us their 28-page A4 mail-order catalogue. It includes batteries, telephone accessories, boxes, buzzers and connectors, along with passive components such as capacitors and resistors. There is a useful selection of p.c.b. manufacturing materials and a pretty substantial list of semi-conductors. It appears to be well worthwhile having this "catalist" on your bookshelf.

For more information contact Bowood Electronics Ltd., Dept EPE, 7 Bakewell Road, Baslow, Derbyshire DE45 1RE. Tel/Fax: 01246 583777.

E-mail: [sales@bowood-electronics.co.uk](mailto:sales@bowood-electronics.co.uk).

Web: [www.bowood-electronics.co.uk](http://www.bowood-electronics.co.uk).

### ILP Disk Cat

ILP, who are renowned for their high-power amplifier modules, have sent us a disk containing the datasheets and prices for their HY2000 series. These cover eight modules ranging from HY2000 30W to HY2007 240W. They typically include their own power supply and heatsinks, can be used with 4Ω or 8Ω loads and have automatic adjustment of input sensitivity. Usefully, the data sheets include mounting dimensions and connection details.

A selection of ILP transformer prices is given, and the company have also advised us that they are a source for customised toroidal transformers as well. ILP have been manufacturers of hi-fi audio modules and toroidal transformers since 1971. Their catalogue is free.

For more information contact ILP Direct Ltd., Dept EPE, Spong Lane, Elmsted, Ashford, Kent TN25 5JU. Tel: 01233 750481. Fax: 01233 750578. E-mail: [ilp@btinternet.com](mailto:ilp@btinternet.com).

# OPEN-SKY FOR HOME VIDEOS

Barry Fox reveals how you could become renowned as a film director, with your home movies.

Nothing on TV tonight? Don't want to pay for a subscription movie channel? Soon you will be able to surf the Internet with a satellite dish to watch someone's home movies.

The catchy idea of Personal Broadcasting comes from European satellite organisation Eutelsat. Trials of the service, called Open-Sky, started in Italy this July. If the trials are a success Eutelsat will switch on the rest of Europe, North Africa and the Middle East next year. Eutelsat hit on the idea because many people now use digital camcorders and computer editing equipment to craft mini-epics which they would love more people to see.

Europe's Digital Video Broadcasting standard was designed to deliver a stream of high quality video and audio, encoded to the MPEG-2 standard and travelling at many megabits per second. Home satellite receivers can only decode MPEG-2 signals.

Home computers access the Internet by phone line using the quite different Internet Protocol, which splits data into small packets running at tens or hundreds of kilobits a second. Even the new and much more powerful MPEG-4 compression standard cannot deliver clear video pictures and sound at these low speeds.

Open-Sky builds a bridge between the two very different technologies by slotting packets of MPEG-4 video into the DVB bit-stream so they can be broadcast by satellite to a home dish. The dish is connected to a Windows PC which is fitted with a DVD-IP decoder card, costing around 200 Euros (£125). The card strips IP packets from the DVB video signal; a conventional Web browser, with Windows Media Player, then decodes the video. Data speeds of 256 or 512Kbps – far faster than available from conventional phone lines – are used to deliver full screen video.

Because the PC cannot transmit signals back to the satellite, a conventional low speed modem and phone line are used to access the Internet and trigger the high speed delivery of selected material. Eutelsat will soon invite home movie makers to upload their videos at slow speed to a central server, using a modem and phone line, with the invitation that anyone with a dish and PC can stream and watch them, like a TV programme.

Eutelsat privatised in July and the populist idea steals a march on rival satellite operator Astra which has so far promoted its Astra-Net data service mainly as a business tool, for staff training and shareholder conferences. Astra says it is also now moving into the consumer market, with satellite Internet transmission of the Italian version of TV programme *Big Brother*.

## ULTIBOARD 2001

Adept Scientific has announced the latest release of the p.c.b. layout software from Electronics Workbench, Ultiboard 2001. It is said to give "unprecedented functionality at unmatched prices".

Ultiboard has been specifically redesigned after an extensive R&D programme in response to user feedback. The specific improvements includes a function known as Tight Integration with Software Capture, which works with Multisim, Electronics Workbench or Ulticap. There is a fully customizable user interface which makes it easier to view and navigate p.c.b. designs. A useful new facility is Push and Shove component placement, allowing users to place components in densely populated areas by automatically moving interfering parts aside.

For more information contact Adept Scientific plc, Dept EPE, Amor Way, Letchworth, Herts SG6 1ZA. Tel: 01462 480055. Fax: 01462 480213. E-mail: info@adeptscience.co.uk. Web: [www.adeptscience.co.uk](http://www.adeptscience.co.uk).

## SMART METERS

The Minister for E-commerce has announced that a new generation of "smart meters" could allow domestic users of electricity and gas to reduce their spending on fuel and connect homes to the Internet and cable TV.

"The Internet of the future will connect all kinds of services, not only PCs and TVs", says the Minister. "Technology already exists to allow telephone and TV services through utilities meters that could provide an Internet under the stairs".

**Our**  
**Hot Rods**  
**Come in a variety of models**

Antex thermally balanced soldering irons are fast, easy to handle and very safe. Plus you get a wide range of different voltages and wattages. So race off with a 'fixed temperature' iron or try the 'In Handle' temperature controlled model. Each one comes with a choice of a PVC or a burn-proof silicon lead, has been manufactured in the UK and meets CE conformity. And with Antex you get a big choice of soldering bits to suit every need. But while our irons sell faster than a dragster, they come at a price that won't burn a hole in your pocket. So visit our web site or your electronics retailer and take one for a test drive

**ANTEX**  
**NOT JUST ANY OLD IRON**


**YOU CAN NOW BUY ANTEX EQUIPMENT ON-LINE**  
**[www.antex.co.uk](http://www.antex.co.uk)**

# CONTROL & ROBOTICS


Milford Instruments
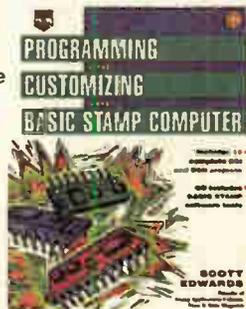
## BASIC Stamp Microcontrollers

Still the simplest and easiest way to get your project or development work done. BASIC Stamps are small computers that run BASIC programmes. With either 8 or 16 Input-Output pins they may be connected directly to push-buttons, LEDs, speakers, potentiometers and integrated circuits such as digital thermometers, real-time clocks and analog-digital converters. BASIC Stamps are programmed using an ordinary PC running DOS or Windows. The language has familiar, easy-to-read instructions such as FOR...NEXT, IF...THEN and GOTO. Built-in syntax make it easy to measure and generate pulses, read push-buttons, send/receive serial data etc. Stamps from **£25** (single quantities), Full development kits from **£79**



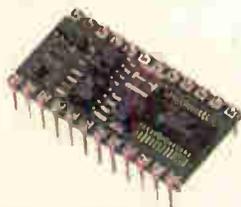Full information on using BASIC Stamps plus lots of worked projects and practical electronics help. CD-ROM also includes 30+ past magazine articles and Stamp software. **£29.95**




New to PICs or just wanting to learn more tricks? We stock the excellent PIC primer books from David Benson - suitable for the complete beginner to the advanced user.


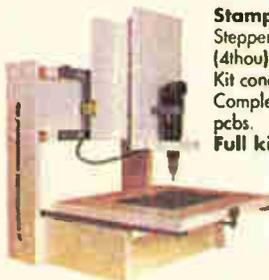
### SERIAL LCDs


Bonnie's the hassle of interfacing to LCD displays. We stock a comprehensive range of alphanumeric and Graphic LCDs - all with an easy-to-use standard RS232 serial Interface. Sizes from 2x16 to 4x40 plus 128x64 graphic panels. Prices start at **£25** (single quantity)



**Stamp2 based 3-axis machine**  
Stepper drive to X, Y and Z axes with 0.1mm (4thou) resolution. Kit contains pre-machined frame components. Complete with Windows software for drilling PCBs. **Full kit at £249, Part kit at £189**
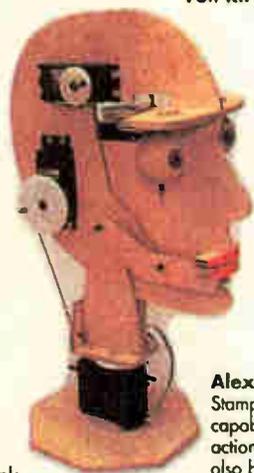
### TecArm4

New range of robotic arms for educational and hobbyist use with super powerful servos. Controlled from PC (Windows freeware provided) or from optional keypad. Stands about 450mm high when fully extended. Kit includes all pre-cut body parts, servo controller board, servos and software. Requires 9v Dc. Kits start at **£189**



### StampBug

Stamp1 based walking insect. Forwards, backwards and left/right turn when feelers detect object in path. Up to 2 hours roving from 4xAA Nicads. Chips pre-programmed but programme may be changed (software supplied). Body parts pre-cut. **Full kit £68**



### BigFoot

Stamp1 based walking humanoid. Walks forwards/backwards with left and right turn when detects obstacles. Electronics PCB pre-built and tested. Programme pre-loaded but may be changed with supplied software. **Full kit £68**



### On Screen Display

Superimpose text onto standard CCTV from simple RS232 serial line. Ready built/tested at **£59**



### IR Decoder Board

Control your project using a standard domestic IR remote. 7 Output lines (5v @ 20mA) may be set to momentary or toggle action. Simple teaching routine. Requires 9-12vDC. Supplied built and tested. **£29 single quantity**




### Alex- Animated Head

Stamp2 based controller with voice record-playback capability, PIR input and/or random playback. 4-servo actions are recorded/edited one track at a time. May also be controlled from PC. **Head kits start at £29. Controllers from £29**
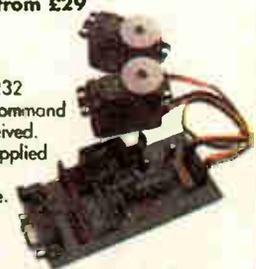
### Servo Driver Board

Control up to 8 standard hobby servos from an RS232 serial data line using this controller board. Simple command structure holds servos in position until update is received. Fully built and tested - requires 9vDC and servos. Supplied with Windows freeware. **£29 single quantity. Optional keypad available.**




## Milford Instruments

120 High Street, South Milford, LEEDS LS25 5AQ  
Tel: 01977 683665 Fax: 01977 681465

All prices exclude VAT and shipping.

**BASIC Stamp** is the registered trademark of Parallax Inc. For further details on the above and other interesting products, please see our web site - [www.milinst.demon.co.uk](http://www.milinst.demon.co.uk)

# INGENUITY UNLIMITED

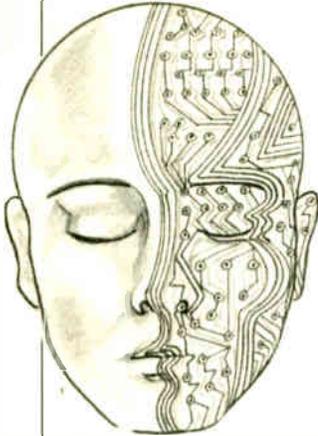

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas *must be the reader's own work and must not have been submitted for publication elsewhere.* The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and full circuit diagram showing all relevant component values. **Please draw all circuit schematics as clearly as possible.** Send your circuit ideas to: Alan Winstanley, *Ingenuity Unlimited*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown Dorset BH22 9ND. (We do not accept submissions for *IU* via E-mail.) Your ideas could earn you some cash and a prize!



## WIN A PICO PC BASED OSCILLOSCOPE

- 50MSPS Dual Channel Storage Oscilloscope
- 25MHz Spectrum Analyser
- Multimeter • Frequency Meter
- Signal Generator

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC based oscilloscope could be yours. Every six months, Pico Technology will be awarding an ADC200-50 digital storage oscilloscope for the best *IU* submission. In addition, two single channel ADC-40s will be presented to the runners-up.

## Wien Bridge Audio Generator – Spot On

**W**HEN testing audio amplifier and filter circuits, a source of high quality sinewaves is needed. The Wien Bridge oscillator is a suitable sinewave source, but its gain must be held at exactly three. Any less and the oscillation will die away, and any more and the oscillation amplitude will increase until the circuit clips the waveform to produce a square wave.

The usual method of stabilising the amplitude is to use a thermistor. Unfortunately, suitable devices are expensive, can be difficult to obtain and are temperature sensitive. It was, therefore, decided to try a different

approach and use an automatic gain control (a.g.c.) loop to stabilise the oscillator, as shown in the circuit diagram of Fig. 1.

The op.amp IC1a is the oscillator proper. Positive feedback is provided through the Wien network comprising of the dual-ganged potentiometer, wired as a variable resistor, VR1a and VR1b, and the switched capacitor network (C1 to C8). The capacitors used came from an old, commercial signal generator, hence the odd values. Good quality, close tolerance (5% or better) capacitors are needed. The values specified cover the frequency range 5Hz to 50kHz.

Negative feedback is provided from pin 1 to pin 2 of IC1a. When the junction f.e.t. TR1 is biased off, the feedback resistors set the feedback at a value of 2.47. When TR1 is biased on, resistor R3 is in parallel with resistor R5 and the gain increases to 3.47. As the bias on the transistor changes it appears as a variable resistance. At the correct bias point a gain of exactly 3 will be achieved.

The circuitry around IC1c controls the j.f.e.t. bias. The oscillator output is rectified by the diode D1 and charges capacitor C9. The resultant negative voltage is amplified by IC1c and is applied to the gate (g) of TR1.

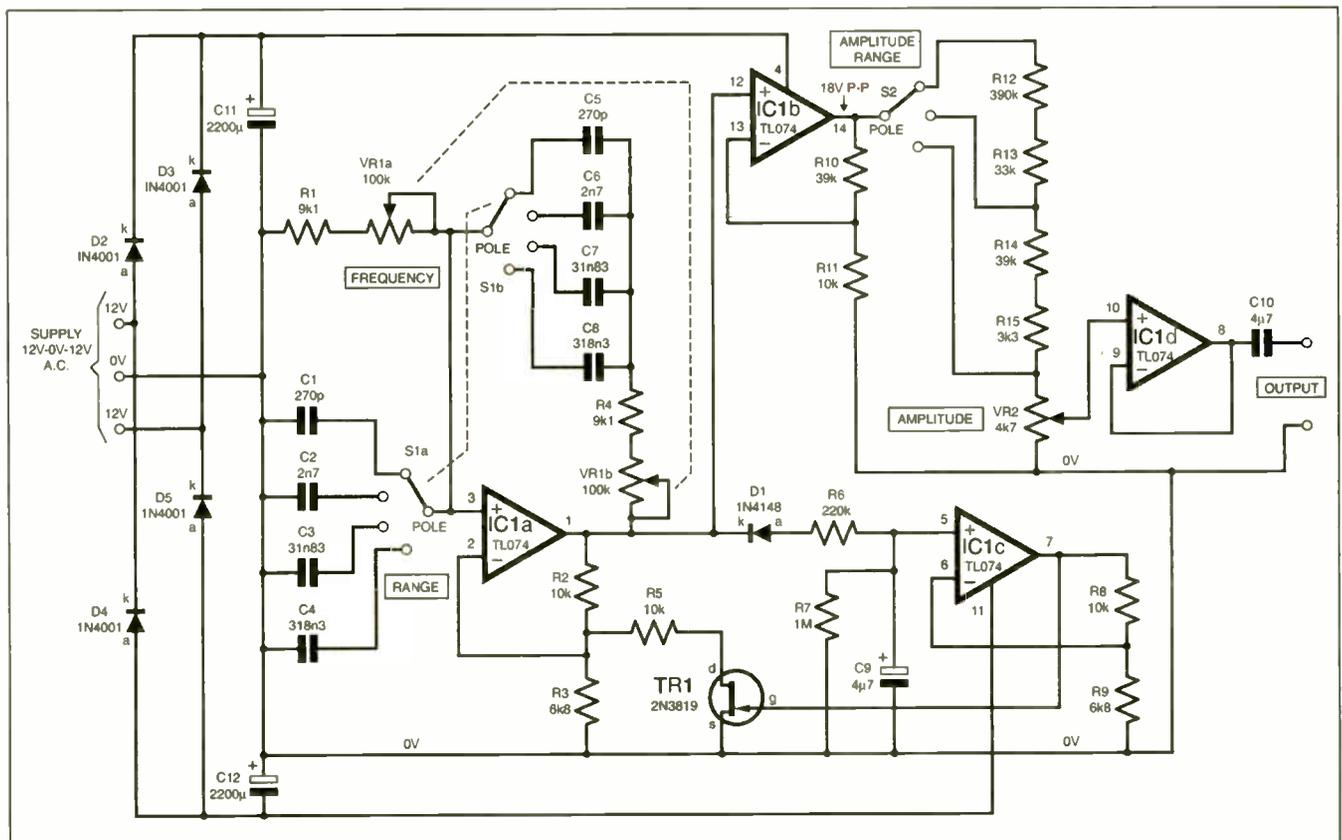


Fig.1. Circuit diagram for the Wien Bridge Audio Generator. Note capacitor C10 should be a non-polarised type.

Note the long time constants for charging and discharging capacitor C9: this stops the a.g.c. circuit from trying to follow the waveform and ensures any amplitude variations take place very slowly. It also means the oscillator takes about 15 seconds to settle down on start up but this is a small price to pay.

The sinewave output is amplified by IC1b to approximately 18V peak-to-peak and then applied to the attenuator selected by switch S2 which gives 1, 10, 100 attenuation steps while the Amplitude potentiometer VR2 allows fine adjustment of the output level. Op.amp IC1d buffers the attenuator output and feeds the output terminals via a non-polarised d.c. blocking capacitor C10.

The author's circuit shares a  $\pm 12V$  d.c. regulated supply with several other items of test gear. The bridge rectifier, D2 to D5, and smoothing capacitors C11 and C12 shown are present on all the test items to prevent interference from being carried along the supply lines.

There is no reason why the unit should not have its own internal power supply but the power circuits must be kept well away from the signal circuits to prevent pickup of hum.

*Paul Fellingham,  
Brighton, East Sussex.*

## INGENUITY UNLIMITED

### BE INTERACTIVE

IU is *your* forum where you can offer other readers the benefit of your Ingenuity. Share those ideas, earn some cash and possibly a prize!



## Precision Stereo Volume Control

### - Well Balanced

WHILST working on a hi-fi preamplifier project, the subject of potentiometers used as variable resistors for volume control arose. The specifications of available dual potentiometers were a bit disappointing for my application. The "gang error", the difference in level from each track resistance, was in the region of 2dB to 3dB (26% to 41%), which is unusable in a hi-fi application without a balance control.

For audio applications, variable resistors with a log resistance profile are required. This is hard to achieve in manufacture, so generally the log profile is made up from two or more linear profiles. This means that log conformance is not very good, and this is essentially the reason behind the poor gang error.

To obtain true balance from our hi-fi systems, it seems necessary to compensate by fiddling with the balance control every time the volume control is changed - not very practical. For my project I decided to use a ganged pair of 12-way switches to make my own variable resistor in the circuit of Fig.2.

The log conformance of this arrangement is better than 0.2dB and the gang error comes down to the tolerance of the resistors used. The overall value of the resistance is 47k and the step size is 4dB.

**Duncan Boyd, Blackburn, W. Lothian.**

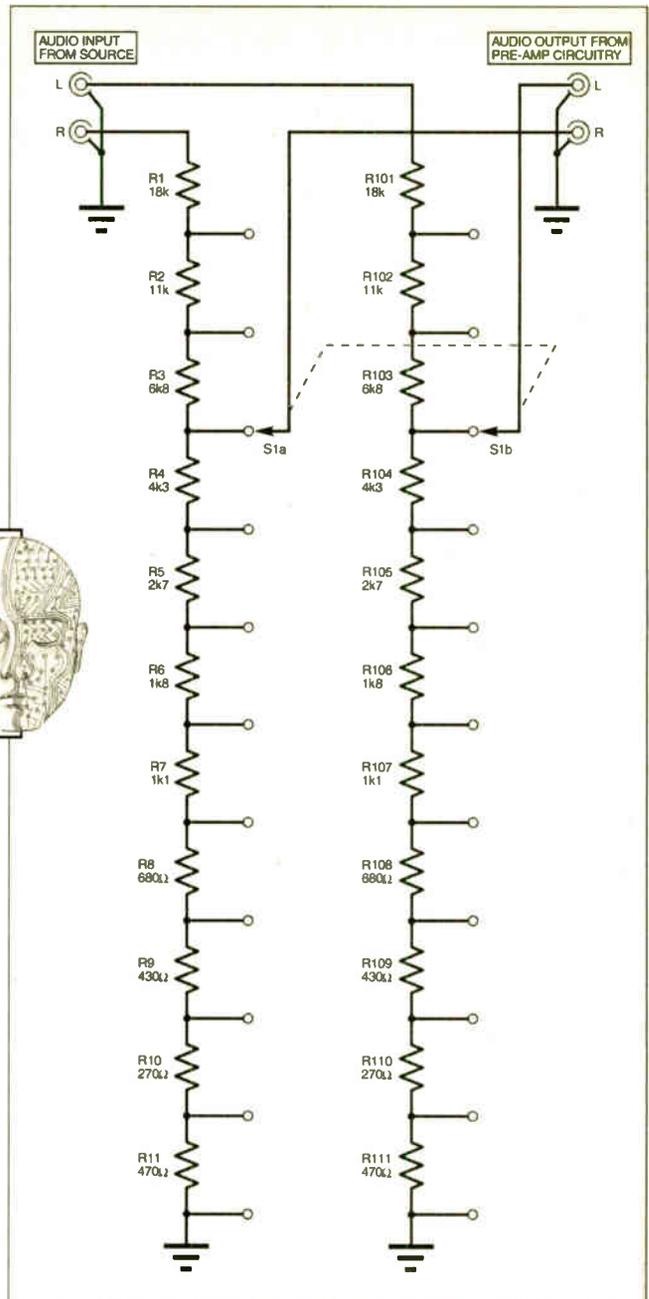


Fig.2. Circuit diagram for a Precision Stereo Volume Control.

## ORDER YOUR COPY NOW

NEXT MONTH: ★ PIC TOOLKIT TK3 FOR WINDOWS ★ 2-VALVE SW RECEIVER ★



Signed.....

Name and Address.....

.....

.....

## NEWSAGENTS ORDER FORM

Please reserve/deliver a copy of *Everyday Practical Electronics* for me each month


Post Code.....

*Everyday Practical Electronics* is published on the second Thursday of each month and distributed S.O.R. by COMAG. Make sure of your copy of *EPE* each month - cut out or photostat this form, fill it in and hand it to your newsagent.

## Constructional Project

# L.E.D. SUPER TORCHES

ANDY FLIND

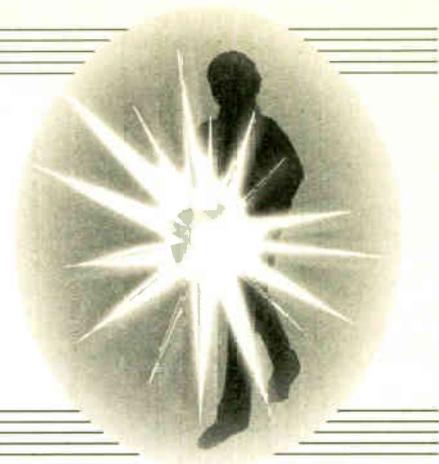

*Two brilliant ways of lightening your darkness – one of them really “state-of-the-art”!*

**T**HE idea for the first of these two torches took hold last summer whilst the author was contemplating a camping trip to Scotland. The Scottish weather and insect life can lead to long evenings confined to the tent (especially if the campsite doesn't have a bar!) so it was felt that an economical reading light might prove useful.

The first design was put together using parts which happened to be available in the workshop. Many readers will have similar components to hand, with the possible exception of the very bright red l.e.d.s which were left over from the construction of goggles for a “Mind Machine” project.

The resulting torch subsequently proved very useful as some unpleasant weather was indeed encountered north of the border. Readers acquainted with the famous Scottish midge will know how swarms of these can also prevent any kind of outdoor activity, and the ability to read for long periods without incurring heavy battery replacement expenses was well worth the constructional effort.

### HI-TECH UPGRADE

On return it was felt that the torch might make a useful constructional project. However, *EPE*, as we all know, is right at the cutting edge of technology and our Editor indicated that it would only be acceptable if it used the latest and brightest white l.e.d.s.

Unfortunately this was not just a case of replacing the original ones as the new high intensity white types exhibit around twice the forward voltage of the familiar red ones and required the development of a circuit capable of handling this.

The resulting torch using white l.e.d.s is impressive though, as it really is extraordinarily bright for l.e.d.s and with three brilliant sources of cold, bluish-white light it looks like no other torch currently on the market. It definitely has novelty value, as well as being very useful.

However, it is more expensive to construct and slightly more difficult to test if problems are encountered following construction, so it would seem that both designs have applications. Because of this it was decided to present both versions so prospective constructors can make a choice.

### RED L.E.D.

The Red L.E.D. Torch is relatively cheap and simple to construct using inexpensive l.e.d.s and semiconductors. The circuit is easy to follow and faults can be traced and cured readily. The red light may be more pleasing to some users as it has a “warmth” which is lacking in the white version.

It's actually better as a reading light since the pure red light heightens the apparent contrast between black print and

a white page. Although not so bright as the white version it is more than sufficient for many purposes.

Finally, for those who like to listen to shortwave radios in bed, it doesn't produce any r.f. (radio frequency) noise. The white l.e.d. version does to a small extent, for reasons that will be explained. One small disadvantage is that it can be difficult to distinguish colours with the pure red light. Red text on a white page, for example, is practically invisible.

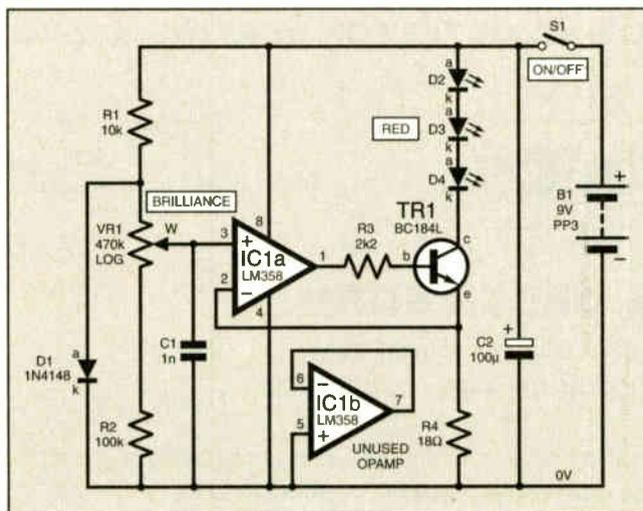
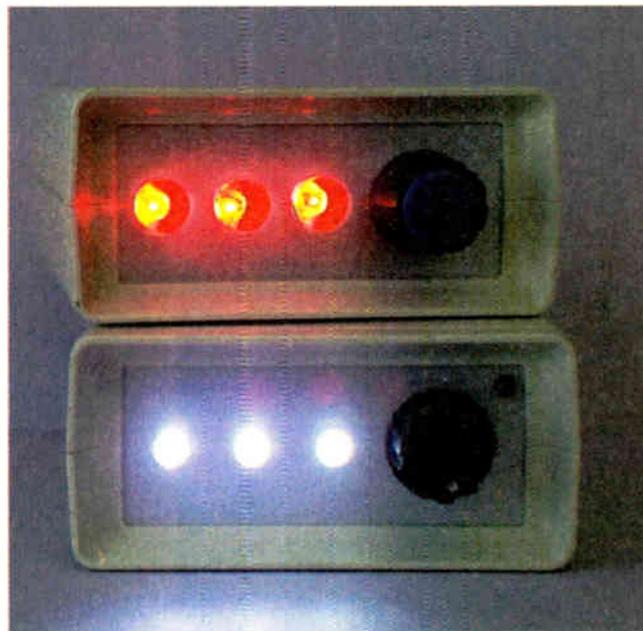


Fig. 1. Full circuit diagram for the Red L.E.D. Torch.

### RED CIRCUIT

The circuit diagram for the Red L.E.D. Torch is shown in Fig. 1. In principle, it is simply an adjustable constant current circuit driving the three l.e.d.s, D2, D3 and D4 in series. Resistor R1 and diode D1 place a constant voltage of about 0.6V, the forward voltage drop of D1, across the “brilliance” control VR1 and resistor R2, which sets the minimum output.

Op.amp IC1a drives transistor TR1 until the voltage from the wiper of VR1 appears at TR1's emitter, causing a corresponding current to flow through the emitter resistor R4. Nearly all of this current is drawn from TR1's collector, passing through the three l.e.d.s on the way, so the current

through these is effectively set by the control voltage from VR1.

Since the eye, like the ear, has a logarithmic response to stimulus intensity VR1 is a "log law" type.

An LM358 op.amp is used for IC1a in this circuit since its output voltage ranges right down to the negative rail. Many op.amps cannot go far enough in this direction to be used for directly controlling a transistor in the manner used here. The LM358 actually contains two op.amps, of which only one is used by this circuit.


The l.e.d.s have a typical forward voltage of less than 2V, usually about 1.7V so battery B1 will operate the circuit until its output drops to around 6V to 7V, by which time replacement is usually advisable anyway to avoid leakage.

An alkaline PP3 battery has a typical capacity of around 550mAh (mA-hours), so the full output current of about 35mA consumed by this circuit means that it will operate for about fifteen hours. At the other end of the scale it is perfectly possible to read by it with a current of less than 10mA, when the battery should last for over fifty hours!

Many older readers will remember childhood longings for a torch with performance like this for reading beneath the bedclothes!
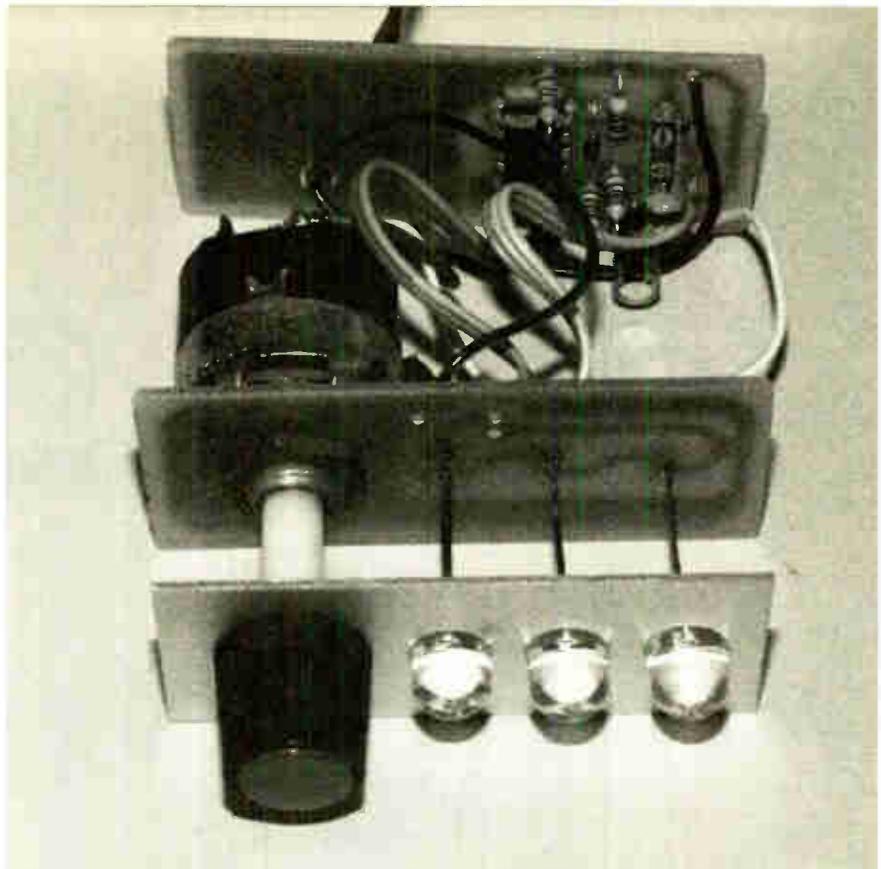
## HARDWARE CONSIDERATIONS

The general layout of this version of the torch can be seen from the photographs. The case used is not the cheapest available but it has the advantage of being compact, with a separate battery compartment having a snap-on cover and a recessed front



The "sandwich" of p.c.b.s and front panel removed from the case showing the method of mounting the l.e.d.s by using the full length of their leads.

panel which provides useful protection for the clear l.e.d. lenses

Two small p.c.b.s were made to fit into the internal slots provided. One of these contains the circuit whilst the other provides mounting for the l.e.d.s and the brilliance control VR1, together with on-off switch S1. These boards are available from the *EPE PCB Service*, codes 313 (Main Red) and 314 (Display Red).

The boards should first be fitted temporarily to the case and trimmed with a file if necessary until the case fits neatly together over them.

The front panel should be drilled for the l.e.d.s and the shaft of VR1 using the template shown in Fig.2. The leads of the l.e.d.s used in the prototype were long

## COMPONENTS

### RED L E D TORCH

#### Resistors

R1	10k
R2	100k
R3	2k2
R4	18Ω

All 0.6W 1% metal film.

See  
**SHOP**  
**TALK**  
page

#### Potentiometer

VR1	470k rotary carbon, with switch, log
-----	--------------------------------------

#### Capacitors

C1	1n ceramic, resin-dipped
C2	100μ radial elect. 25V

#### Semiconductors

D1	1N4148 signal diode
D2 to D4	ultrabright 8mm red l.e.d. (3 off)
TR1	BC184L npn silicon transistor
IC1	LM358 dual op.amp

#### Miscellaneous


Printed circuit boards, available from the *EPE PCB Service*, codes 313 (Main Red) and 314 (Display Red); 8-pin d.i.l. socket; PP3 battery connector; control knob, 15mm diameter; plastic case, 114mm x 72mm x 33mm with integral battery compartment; connecting wire; solder, etc.

Approx. Cost  
Guidance Only


**£11**

excluding case.

Fig.2 (right). Front panel drilling template, with dimensions.

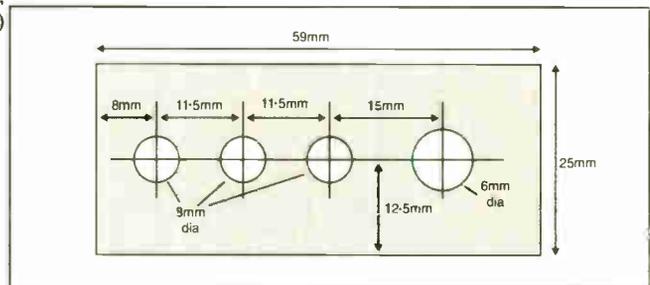

(Below) The two p.c.b.s slotted into their guides.

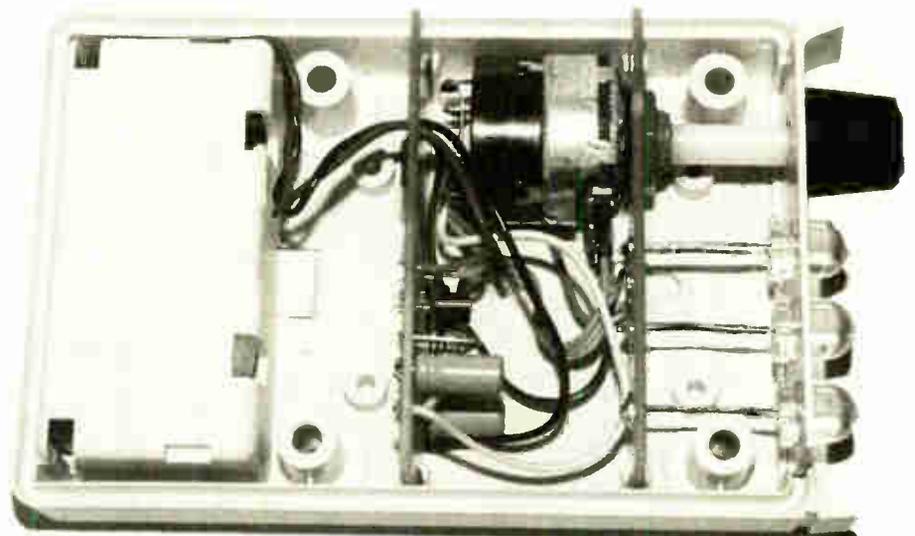

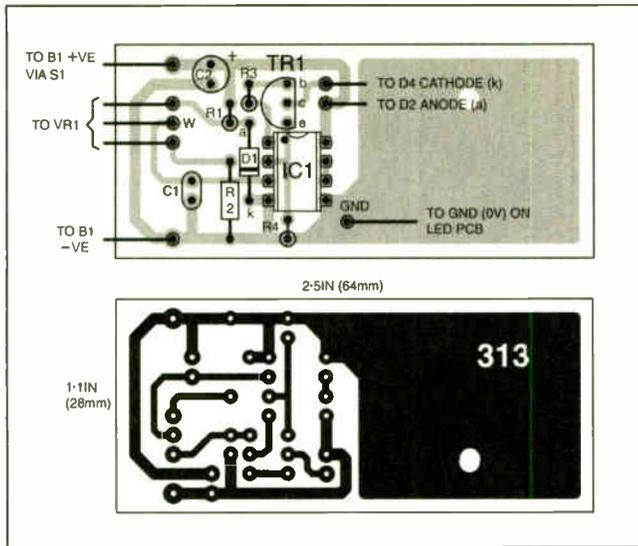


Fig.3. Red L.E.D. Torch main p.c.b. component layout and full-size copper foil master.


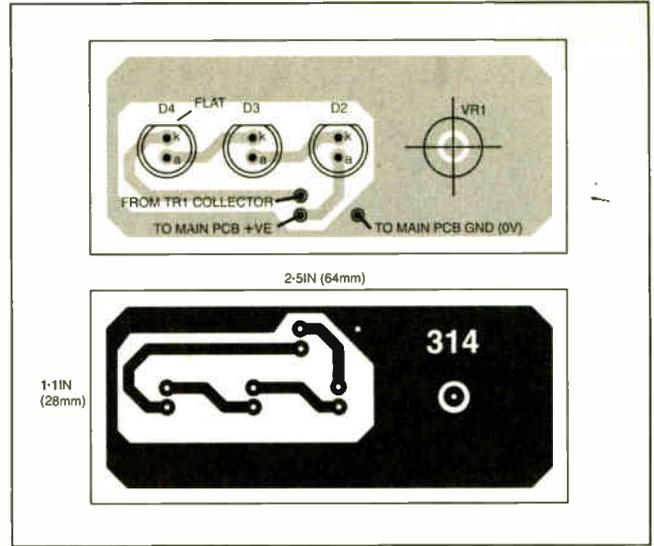


Fig.4. Red L.E.D. Display board component layout and copper foil master.

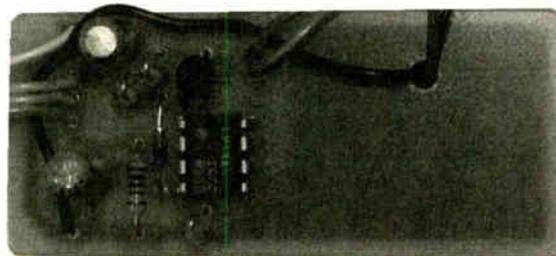enough to extend back to the p.c.b. behind them so this was used as their mounting. If this is not the case, they can be glued to the panel and their connections made locally as shown for the second, white version of the torch.



Completed circuit board for the Red L.E.D. Torch.

### CONSTRUCTION

Most of the remaining components for this project are fitted to the p.c.b. as shown in Fig.3. There should be no problems in assembling this little circuit, but it should be noted that three of the resistors, R1, R3 and R4, are mounted in a vertical manner to save space. An 8-pin dual-in-line socket is recommended for IC1.

The method of fitting the three l.e.d.s D2, D3 and D4 is shown in Fig.4. It is useful to place the l.e.d. board and front panel into the case to hold the l.e.d.s in place for soldering, allowing them to project adequately through the case holes.

Connections between the various parts are shown in Fig.5. A hole in the main p.c.b. allows leads to be passed through it where necessary.

Testing should be just a matter of connecting a supply and checking that everything works, though if problems are encountered it should be simple enough to find and rectify them with a meter. If the l.e.d.s fail to light they can be checked by driving them directly in series from the battery using a 220 ohms resistor to limit the current to a safe value.

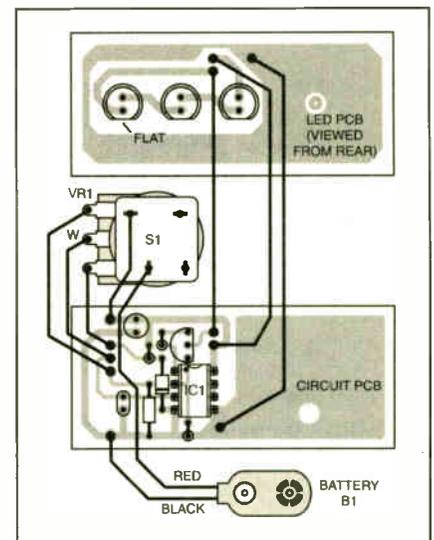


Fig.5. Interwiring between the p.c.b.s and the brightness control.

## WHITE L.E.D. SUPER TORCH

*A bright idea for lighting your way at night*

### WHITE L.E.D.S

THE NEW white l.e.d.s operate in a different way to the older red, yellow and green ones that have been around for some time. They are not a mixture of colours to obtain white as might at first be thought. Instead they consist of very high intensity blue l.e.d.s backed by a phosphor which glows brilliantly white under the stimulation of the intense blue light.

The resulting output is very bright for an l.e.d., in fact it's quite painful to look directly into one of these devices at full power, but it's a very "cold" light with a high blue content, unlike the warmer colour of a conventional white filament lamp. These l.e.d.s have a typical forward voltage of about 4V, around twice that of a red type.



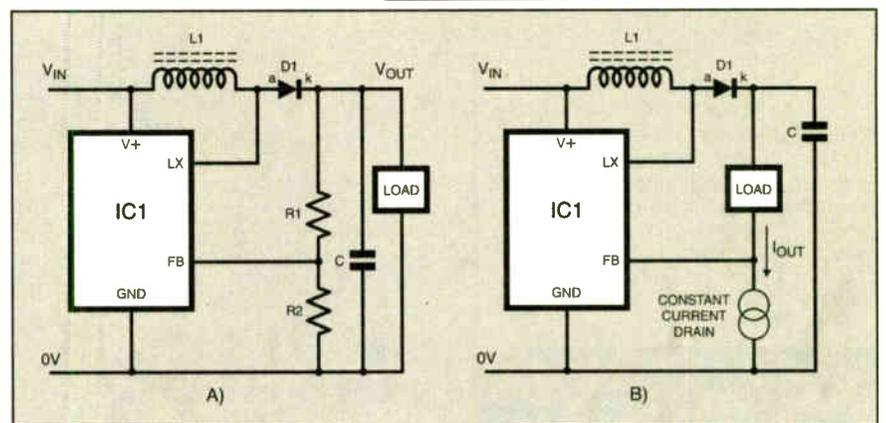
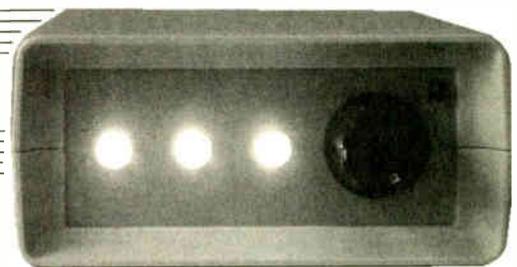
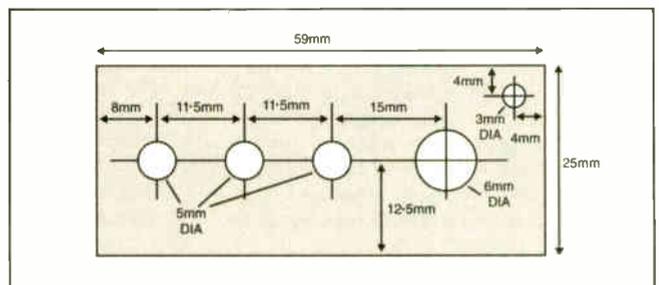
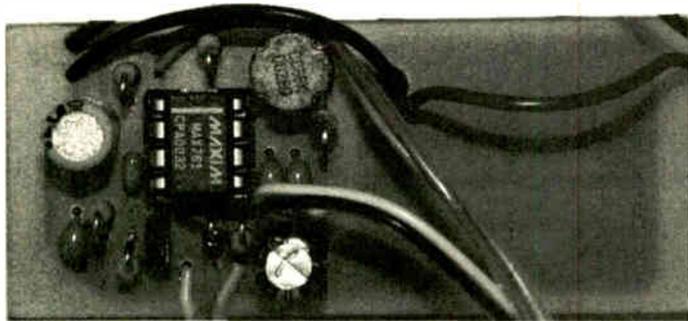


Fig.6. Operating principle of the White L.E.D. Super Torch circuit.

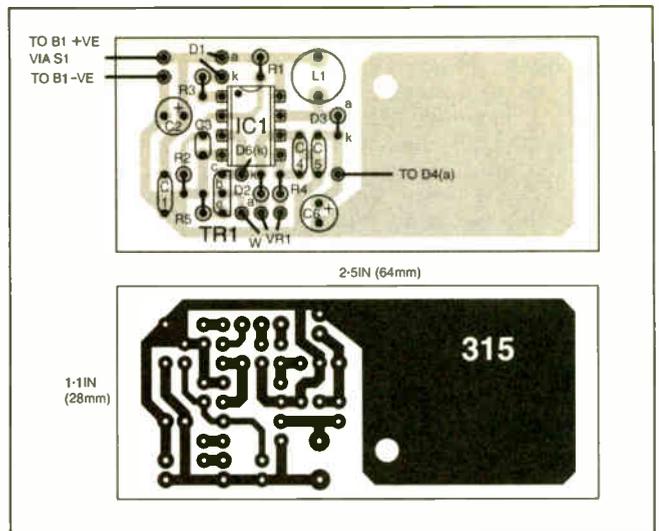

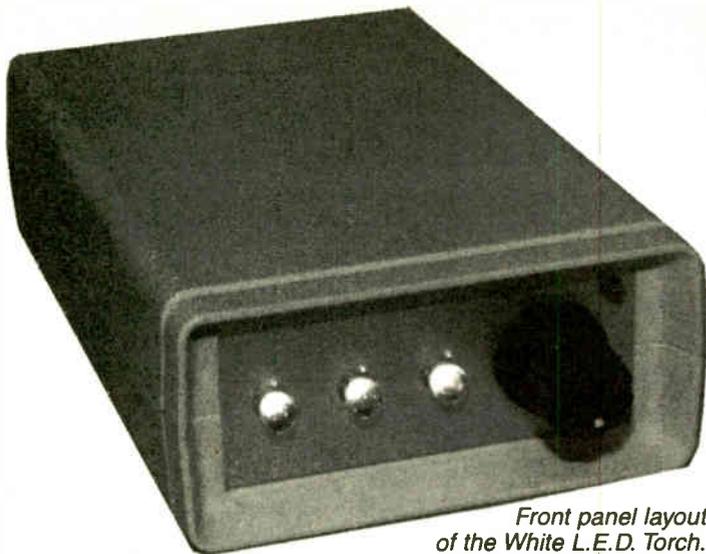

## COLD BRILLIANCE

The light produced is somewhat cold in nature, as it contains a lot of blue light. The clear lens casing tends to separate the colours slightly, so that a circle of bluish light can sometimes be seen in the output beam.

The current drain depends on the supply voltage as IC1 draws more current to supply the output as the input voltage falls. However, at full power it takes about 50mA, so an alkaline PP3 should manage over ten hours at this setting. It is possible to read with the torch quite comfortably at supply currents of little more than 10mA, making for a very long battery life.

The torch is much brighter than the red version and it really would be possible to walk along a rural footpath at night with it, and it would be far more economical to run than a conventional torch. Unlike the red version, colours are clearly visible in its light.


Finally, white l.e.d.s are still "state-of-the-art" so many people have not actually seen one and are usually astonished by their brilliance. This is the version to build if you want to impress your friends!

## CONSTRUCTION

The printed circuit board for this version is also available from the *EPE PCB Service*, code 315.

Once again, the board should be checked for a fit in the case first, and adjusted by filing the edges if necessary.

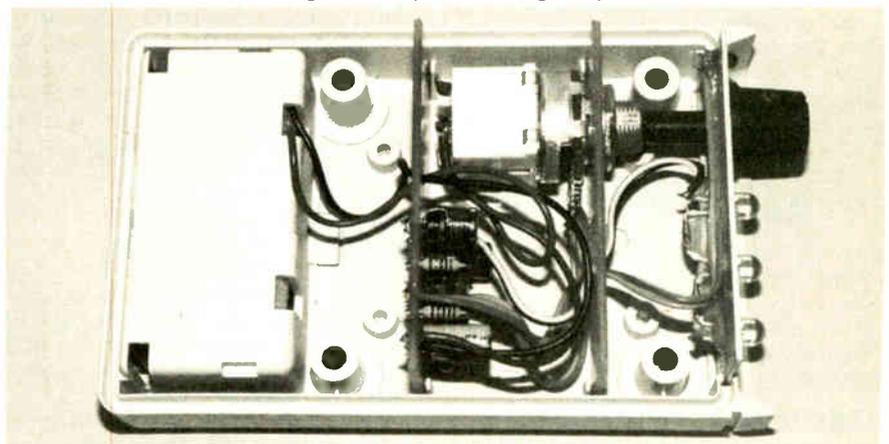Following this all the components can be fitted as shown in Fig.8. The board is rather compact, with all the axial-leaded resistors and diodes mounted vertically to save space, so some care will be needed in assembly. An 8-pin d.i.l. socket should be used for IC1.




Completed unit showing the internal layout of the torch.

Testing should be carried out with care since if it is not correctly loaded on power up, the output voltage may exceed the rating for the output transistor "behind" IC1 LX and cause damage. It is suggested that the board is tested with a 330 ohms resistor in place of the l.e.d.s.

The supply current should vary between 2mA and 45mA depending on the setting of VR1, and the voltage across the test resistor which, unlike the l.e.d.s, is directly dependant on the current, will vary from 0V to about 10-25V.

A second p.c.b. is not used in this project as the l.e.d. leads were not long enough. A spare piece of fibreglass p.c.b. material was used for mounting the brilliance control VR1, but a piece of aluminium sheet would do as well. A hole should be drilled in this for the wires to the l.e.d.s to pass through from the circuit p.c.b.

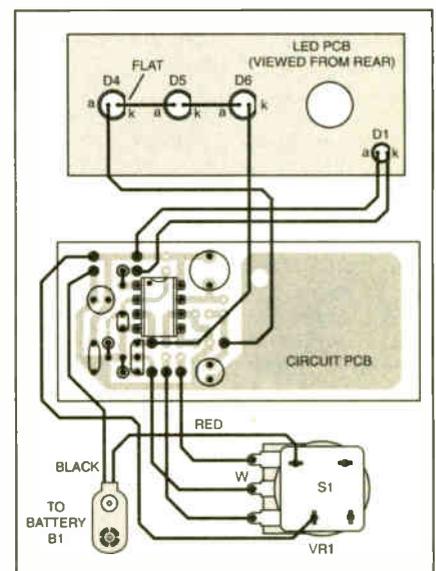Once again the front panel was drilled to take the shaft of VR1 and the l.e.d.s, but in



this version there is also a 3mm red l.e.d. for the low battery indication. This is placed in a corner by the control, away from the main l.e.d.s. to make it more visible. A template that can be used for drilling the panel is given in Fig.9.

The l.e.d.s are connected as shown in Fig.10 and secured with two applications of Evostik, although an epoxy adhesive might be better.

### TESTING AND ASSEMBLY


The l.e.d.s can be tested if a suitable supply is available to ensure the correct path for the current exists through them. Two PP3 batteries in series will provide an 18V supply which can be applied through a series resistor of 560 ohms to limit their current to just over 10mA for testing. If they all illuminate it's a safe bet they are connected correctly and working.

Following this, the project can be assembled into the case for a final operational check. Adjustment of VR1 should control the brilliance from almost zero to full power. On switch-off the three white l.e.d.s will glow for a short period as capacitors C2 and C6 discharge, and the low battery l.e.d. D1 should flash briefly as the supply drops through 6V, showing this feature is working correctly.

If a variable voltage bench supply is available this can be used to check the action more precisely.
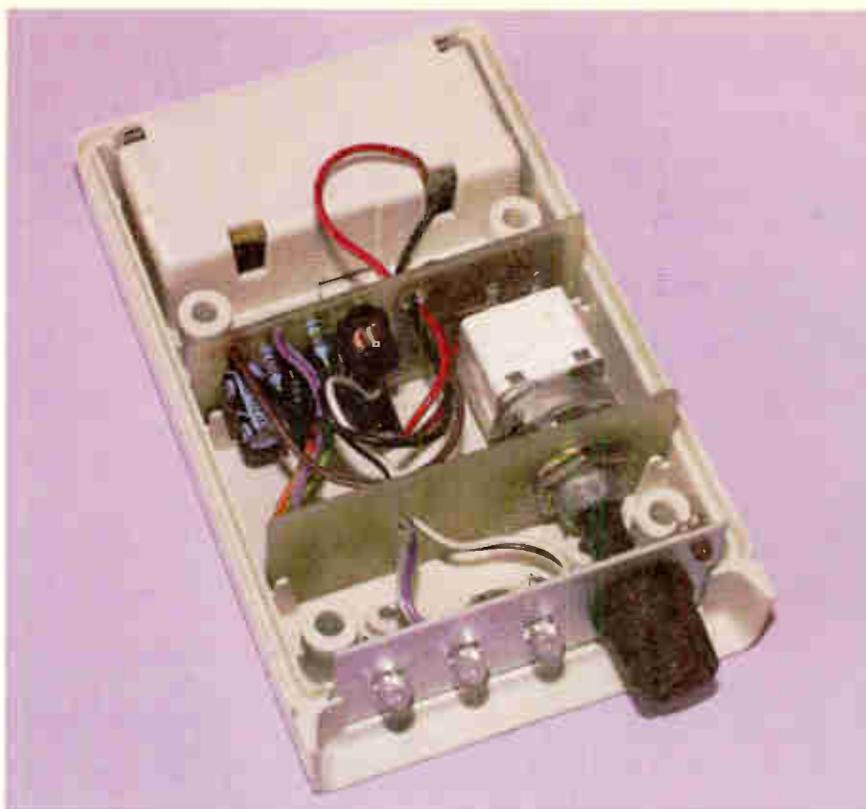
### IDEALLY SUITED

Both these torches make ideal reading lights with low battery consumption. The red one is cheap to construct and has a pleasant



Completed White L.E.D. Super Torch. Note the 3mm "low battery" monitor l.e.d. in the top right-hand corner of the front panel.

warm light. The white one is more expensive (principally due to the cost of the l.e.d.s), but just as cheap to run and considerably brighter, and quite unique in appearance.

It is also a better replacement for a normal incandescent lamp torch. They both have their advantages, so the choice is a matter of individual preference. □



## A COMPLETE RANGE OF INVERTERS

150W TO 2500W - 12V & 24V

A Complete range of regulated inverters to power 220V and 240V AC equipment via a car, lorry or boat battery. Due to their high performance (>90%) the inverters generate very little heat. The high stability of the output frequency (+/-1%) makes them equally suitable to power sensitive devices.

These inverters generate a modified sine wave, which are considerably superior to the square waves which are produced by most other inverters. Due to this superior feature they are capable of powering electrical equipment such as TV,s, videos, desktop & notepad computers, microwave ovens, electrical lamps, pumps, battery chargers, etc.

### Low Battery Alarm

The inverters give an audible warning signal when the battery voltage is lower than 10.5V (21V for the 24V version). The inverter automatically shuts off when the battery voltage drops below 10V (20V for the 24V version). Fuse protected input circuitry.

Order Code	Power	Voltage	Price
651.581	150W Continuous	12V	£36.39
651.578	150W Continuous	24V	£36.39
651.582	300W Continuous	12V	£50.64
651.585	300W Continuous	24V	£50.64
651.583	600W Continuous	12V	£101.59
651.593	600W Continuous	24V	£101.59
651.587	1000W Continuous	12V	£177.18
651.597	1000W Continuous	24V	£177.18
651.602	1500W Continuous	12V	£314.52
651.605	1500W Continuous	24V	£314.52
651.589	2500W Continuous	12V	£490.54
651.599	2500W Continuous	24V	£490.54



All prices are inclusive of V.A.T. Carriage £5.00 per Order

Many uses include:- Fetes . Fairgrounds . Airshows . Picnics . Camping . Caravans . Boats . Carnivals . Field Research and . Amateur Radio field days \* Powering Desktop & Notepad Computers.

DELIVERY CHARGES ARE £6.00 PER ORDER. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLC,S ETC. PRICES ARE INCLUSIVE OF V.A.T. SALES COUNTER. VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX, OR EMAIL US AT SALES@BKELEC.COM ALTERNATIVELY SEND CHEQUE OR POSTAL ORDERS MADE PAYABLE TO BK ELECTRONICS.



**B.K. ELECTRONICS**




UNIT 1, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR  
TEL.: +44(0)1702-527572 FAX.: +44(0)1702-420243

For Full Specifications View our web site at:-

[WWW.BKELEC.COM/INVERTERS.HTM](http://WWW.BKELEC.COM/INVERTERS.HTM)
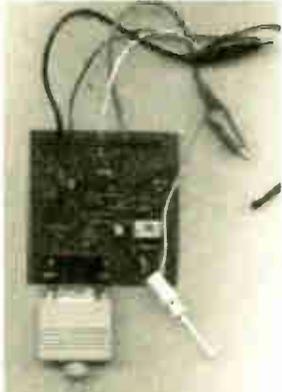
## NEW From FED – In Circuit Debugging for PIC 16F87x series

Operates with all FED PIC Development applications (PIXIE, WIZPIC, PICDESIM, C Compiler)



**In Circuit Debugger Board**

### What is In-Circuit Debugging (ICD) ?

In Circuit Debugging is a technique where a monitor program runs on the PIC in the application circuit. The ICD board connects to the PIC and to the PC. From any of our applications it is then possible to set breakpoints on the PIC, run code, single step, examine registers on the real device and change their values. The ICD makes debugging real time applications faster, easier and more accurate than simulation tools available for the PIC.

### Features

- Allows real hardware to be examined & programs to be debugged and to be *run in real time* on your application
- Powered from the application circuit (3.3V to 5V)
- The FED ICD requires only *one data I/O* pin on the PIC which can be chosen from any of ports B, C or D.
- Can *program and re-program* applications in circuit
- Up to **3 breakpoints**
- Run, single step and step over, run to cursor line, set PC to any value in the program
- Trace execution in the original C or Assembler source files
- *Animate* operation to trace variables at breakpoints or watch the program executing
- Auto Run application if ICD not connected
- *View and change values* of PIC special function and general purpose registers, W and the ports.
- Uses a standard (3 wire) serial interface to a PC

### Prices

**In Circuit Debugger Board - £30.00**

You will also need a copy of PICDESIM, WIZPIC, our C Compiler, or PIXIE, all of which operate with the ICD board.

## PIXIE

### Visual Development for the FED PIC C Compiler

- An application designer for the FED PIC C Compiler FULLY including the PIC C Compiler
- Drag a software component on to your design & set up the parameters using check boxes, drop down boxes and edit boxes (see shot right).
- Connect the component to the PIC pins using the mouse
- Select your own C functions to be triggered when events occur (e.g. Byte received, timer overflow etc.)
- Simulate. Trace at up to 10x the speed of MPLAB
- Generate the base application automatically and then add your own functional code in C or assembler
- Supports 14/16 bit core PICS - 16F87x, 16C55x, 16C6x, 16F8x, 16C7xx 18Cxx
- C Compiler designed to ANSI C Standards




### Prices

PIXIE with Introductory manual (C Manuals on CD) - £70

PIXIE with WIZPIC, Serial Programmer, or Development Board £50.00 CD-ROM

## PIC & AVR Programmings

## NEW - PIC Development Board

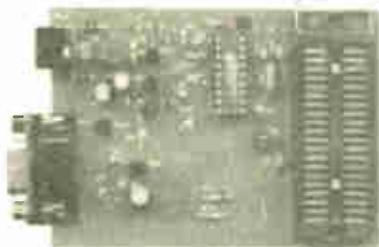

### PIC Serial Programmer (Left) including 18Cxxx

Handles serially programmed PIC devices in a 40 pin multi-width ZIF socket. 16C55X, 16C6X, 16C7X, 16C8x, 16F8X, 12C508, 12C509, 16C72XPIC 14000, 16F87X, 18Cxxx etc. Also In-Circuit programming. Operates on PC serial port

Price : £45/kit  
£50/built & tested

**PIC Introductory** – Programs 8 & 18 pin devices : 16C505, 16C55X, 16C61, 16C62X, 16C71 16C71X, 16C8X, 16F8X, 12C508/9, 12C671/2 **£25/kit.**

**AVR** – AVR1200,2313,4144,8515, 8535, 4434 etc. in ZIF. 4.5V battery powered. Price : **£40 for the kit or £45 built & tested.**

All our Programmings operate on PC serial interface. No hard to handle parallel cable swapping ! Programmings supplied with instructions, + Windows 3.1/95/98/NT software. Upgrade programmings from our web site !



For ALL 40 pin PICS from 16cxxx, 16Fxxx and 18cxxx

- Includes In-Circuit Programmer – NO separate programmer required
- LCD module interface (1:1) plus contrast control
- Hex keypad interface
- 4 LED's and driver
- 32 I/O pins available on IDC headers
- Variable resistor for A/D
- Socket for 12C EEPROM
- 1A 5V regulator on board
- 2 serial interfaces
- CD-ROM supplied with FED PIC BASIC and Compiler
- Peripherals operate only on port D and E leaving others free

Manual on CD-ROM or download free from our web site

### Prices

Kit with integrated programmer hardware **£35.00**

**CD-ROM** including FED PIC BASIC compiler **£5.00**

**Other options** available – please ring or see web site

### Forest Electronic Developments

60 Walkford Road, Christchurch, Dorset, BH23 5QG.

Email – info@fored.co.uk or sales@fored.co.uk

Web Site – <http://www.fored.co.uk>

01425-274068 (Voice/Fax)

Prices are fully inclusive, Add £3.00 for P&P and handling to each order.

Cheques/POs payable to Forest Electronic Developments, or phone with credit card details



## 18C452

New architecture (more instructions + Hardware multiply), 40MHz clock, 16K program words, 1536 bytes RAM. Easy to upgrade from 16F877

18C452/JW £20.00  
18C452/OTP £8.00

# READOUT

E-mail: editorial@epemag.wimborne.co.uk

**John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!**

## WIN A DIGITAL MULTIMETER

A 3½ digit pocket-sized I.c.d. multimeter which measures a.c. and d.c. voltage, d.c. current and resistance. It can also test diodes and bipolar transistors.

Every month we will give a Digital Multimeter to the author of the best Readout letter.



## ★ LETTER OF THE MONTH ★

### CONTROL PLATFORMS

Dear EPE,

First, let me congratulate you and Owen Bishop for an excellent article in the June '01 issue, *Controlling Jodrell Bank*. I personally find articles like this most enlightening and hope you continue to publish similar articles in the future. The side bars on Grey and incremental encoders were most fascinating, especially if you've ever wondered how a PC mouse works.

I'd also like to throw my penny's worth into the development language/operating system debate. I've read with interest peoples' comments, their pros and cons for each respective environment and am of the conclusion that there is no "perfect" solution. Price, performance, cost, ease of use and minimum hardware specifications etc., all play a factor in people choosing which is the better environment for them and their specific project.

I'm sure that some readers, myself included, have written their own versions of software for some of your projects for various reasons, and I would like to suggest that EPE make available a web page so that software developers could either post their versions of software or perhaps links to web sites where alternative versions of software can be found. Perhaps this way people can try out different versions of software that they feel are more appropriate to their situations.

If developers included the source code there would be no need to place executables on the site and problems with viruses could be eliminated. Also, some development languages, like Visual Basic, require quite hefty runtimes. However, if you only store the source code on

the site, then perspective users of the software would require the actual development environment to compile the code so you wouldn't need to store rather larger runtime files or setup kits.

As a professional Visual Basic software developer, I feel that the above approach would eliminate a lot of the problems some seem to encounter. EPE project authors could continue to develop software in their preferred development toolset and the EPE community would port the software to other platforms giving the less experienced developers chance to use different versions.

Joe Farr, via the Net

*Thank you Joe. Owen's article in this issue should interest you just as much.*

*We have previously discussed having a reader's software portal on our site but the problem is that someone at our end has to monitor and regulate it, time which none of us have available on a regular basis, although we can certainly see the merits of the idea.*

*However, we have just introduced a PIC TRICKS folder on the ftp site that contains some useful code sections that have been published in Readout.*

*Regarding source code provision, we already do this (and it is one of the requirements of project acceptance that authors must provide source code for general dissemination to readers who require it).*

*Executables we shall continue to provide for the sake of those who do not wish to modify code, allowing them to directly make use of the code as it stands. All software is checked for viruses before being placed on our ftp site.*

Alan, who is Master of Ceremonies for IU comments:

Nice story Nigel. Well, that's one way of fulfilling the design requirement I suppose, though it's a bit unofficial!

It also proves there is plenty of mileage to be had out of good old discrete logic without having to program a PIC microcontroller, though I fear the MCU is the way everything will go.

Alan Winstanley

### PIC16F877 AND PICTUTOR

Dear EPE,

Can I plug a 16F877 into the PICTutor board, given I make an appropriate plug adaptor, in order to program it? I assume the high programming voltage is the same as that for the PIC16F84.

John Waller, via the Net

*Yes, John, it is certainly possible to program other PICs using PICTutor. Simply connect leads from PICTutor for +5V, 0V, RB6 and RB7 to the other PIC's appropriate pins. However, you must be aware that the PICTutor guarantee becomes invalid if you do so.*

### PIC BANKS AND INTERRUPTS

Dear EPE,

I have just read through John Becker's PIC16F87x *Extended Memory* piece in June's EPE. Very good – explaining things so thoroughly and simply for beginners, with all the useful tables etc.

The thing I missed in the article was any mention of interrupts. If you're both using interrupts and playing with different banks then you have to be additionally careful because you can find yourself in interrupt code (ISR) with RP0/RP1 and/or the IRP/FSR bit 7 incorrectly set for accessing the ISR's data locations.

Thus it is necessary to locate (at least) the ISR's state saving locations in the \$70 to \$7F region so that they can be accessed independently of the RPx bit settings before the ISR has been able to set them up how it wants.

Resetting of RPx and IRP on exit from the ISR will generally happen automatically as a consequence of preserving the STATUS register by means of the standard ISR entry/exit sequence, but in the (probably unlikely) case that the ISR changes FSR bit 7, this will need to be saved and restored specially.

Malc Wiles, via the Net

*Hello again Malc, and thank you!*

*Readers, Malc makes a very valid point and indeed interrupts are something that has not been significantly discussed in EPE. In fact, Malc and I have since been in frequent discussion about this. The upshot is that Malc has written a "semi-tutorial" on interrupt use with PICs.*

*We know there are many PIC users who will appreciate more insights into using interrupts and the potential problems if they are not used correctly. As a programmer familiar with many software disciplines and dialects, Malc is well qualified in this matter. His script is excellent and we look forward to publishing the final version in due course – no date fixed yet.*

### C TUTOR?

Dear EPE,

I get the impression that in the commercial world programming of PICs in C is becoming the norm. Microchip's most recent range of microcontrollers, the PIC18Cxx2, consist of a "C-compiler optimised architecture/instruction set", with "Source code compatible with the PIC16Cxx instruction set".

Whilst general tutorials on the all purpose programming languages Visual Basic or C would be inappropriate in EPE, I would welcome an introduction to this field by someone who has investigated the available compilers, and settled for one at a hobbyist price.

Michael Stewart, via the Net

*Thanks Michael, and you will no doubt be interested by Alan Bradley's informative "C Source" letter published in Readout June '01, and in Mike Kenyon's letter on the next page.*

*You will probably also find our "C" for PICmicro Microcontrollers CD-ROM will be of great interest (see the CD-ROM pages). It also includes a "virtual" code development screen.*

### TUNING FORK

Dear EPE,

I was very interested in the *Electronic Tuning Fork* in May's IU.

Some years ago, I bought some ancient Moog synthesisers and needed to build a crystal based 440Hz sounder to tune them by. It needed to be stable and all the back issues off EE I had only showed RC oscillators, which I presumed would drift as much as the old synths. So I had to build my own gadget. However, I couldn't work out how to divide a crystal generated frequency into the required 440Hz.

So, remembering how one used to tune organ circuits by filing a notch in a resistor, I took a 400Hz ceramic resonator from a dead VCR, built a standard oscillator circuit around it followed by three 4017 divide-by-tens. Then, I opened up the ceramic resonator and very carefully filed down the sliver of material inside on all four sides, which increased the resonant frequency, replacing it and repeating until I got the required reading on my frequency meter.

Amazingly, this actually worked. I had wondered if air getting to a once sealed component would affect stability but it still works properly!

Nigel Rushbrook, via the Net

## C POWER

Dear EPE,

Whilst I must applaud the desires of several of your readers to learn "C" programming, I must agree with the sentiments you expressed in the May edition. Furthermore, C (and C++) is a complex and extremely powerful language with the capability to do horrible (and nice!) things to not only the operating system but indeed to the BIOS. It gives access to all aspects of the computer but relies heavily on the programmer keeping very close tabs on what he (or she) is doing at all times. A misplaced comma or semicolon could easily bring the operating system down with the resultant mess being sprayed around the hard drive!

Having said that, please don't be put off (just be careful!) - I understand that the Microsoft team wrote the various versions of Windows in C - an indication of the versatility of the language.

If anyone wants to learn C programming, an excellent primer is *Learning to Program in C* by Noel Kantaris (B. Babani - ISBN 0-85934-203-4). I feel that in any subject, knowing the tools and materials available is half the battle, and to this end I have no hesitation in recommending *C The Complete Reference* or the newer version *C++ The Complete Reference* - both by Herbert Schildt (Osborne Books ISBN 0-07-881538-X and 0-07-882123-L respectively).

I believe that Kemighan and Ritchie (the inventors of the language) have also written tutorial books on the subject. The various PC magazines give away versions of C compilers (and Linux software!) from time to time on their cover disks, in addition to running tutorials, and there are many C and C++ programming forums (fora?) on the web. No excuses!

With reference to your question about the USB, most new PCs are equipped with USB capability, simply requiring the addition of a hub card, while others will already have the port built in to the main board. A (limited) power supply is available, though the necessary driver software may be a problem for the home constructor.

Mike Kenyon, via the Net

*You have provided some very useful advice, Mike, thank you.*

## SNUG BUG SENSOR

Dear EPE,

I noticed the *Snug Bug* article (April '01) mentions that the active temperature sensors used have the disadvantage of requiring three wires. One which does not is the IC590kH (RS order code 308-809). This a current source whose current is proportional to temperature ( $1\mu A/^{\circ}C$ ) and so is resistant to the problems of long cables and only requires a two-wire cable. A simple op.amp current-to-voltage converter circuit will read it.

Alan Bradley, via the Net

Thanks Alan.

## SOLDER TYPES

Dear EPE,

Having read Alan Winstanley's *Basic Soldering Guide* (downloaded from your web site), and as a service-technician constantly trying to improve his soldering, I would like to ask what the advantages are of using solder containing two per cent silver or two per cent copper over the usual 60/40 tin/lead alloys. When and where are they best used?

Erik Hens, via the Net

Alan replies:

Solder containing silver (two per cent typical) tends to produce better quality results when soldering by hand. It has a better "wetting" characteristic, meaning that it flows more easily over the joint than ordinary Sn/Pb solder does. It also has better conductivity, which might be important with low power, high frequency circuits. I know an engineer who exclusively uses silver-loaded solder for all his manual soldering.

The only copper-based solder I know of, is 99.7 per cent tin, 0.3 per cent copper. Such solders are described as "lead-free" which is supposedly better for the environment. Some countries are banning the use of lead solder altogether, so everyone is actively looking for alternatives. Water-based fluxes are also becoming popular for environmental reasons. For more info browse [www.weller.com](http://www.weller.com).

## NOTETAB TEXT EDITOR

Dear EPE,

Regarding text editors and file sizes, I too have had problems with Windows Notepad (and similar). May I recommend NoteTab, available as a free download from [www.notetab.com](http://www.notetab.com). The highly featured, freeware version is excellent. It is a text editor (as opposed to a wordprocessor), and is very fast. It also has a huge host of other clever features... well worth a try.

I have used it with a PIC '871 datalogger project that I am working on, both for the ASM source code (too large for Notepad), and to view/edit the data files the PIC generates, which are 2.5MB in size.

Richard Niell, via the Net

*You are right, Richard, it is good. I downloaded it when I first read your E-mail and am very impressed. So much so, that I have actually put a link to the NoteTab site into my forthcoming Toolkit TK3 For Windows so that users can import the editor and use it through TK3 (which allows programmers to use any text editor of their choice).*

*Incidentally, I was amused to see the vast quantity of web "smilies" that NotePad has as "library" symbols for use in text messages - I had no idea there were so many! Interestingly, NoteTab also has hyperlinking facilities.*

## PCB MASTERS

*We have several times discussed the merits of various techniques of outputting CAD-generated p.c.b. artwork to a form suitable for use as the track master when making p.c.b.s via photosensitive copper-clad fibreglass.*

*Such techniques have included the use of sprays that transparentise paper printouts (including the use of WD40 - actually very successful as long as track thicknesses and spacings are adequate).*

*Until recently, I have favoured the use of translucent (but not transparent) drafting film. This works best with dot-matrix printers but can be difficult with inks unless good quality (and expensive) ink is used. It is still prone to smudging before it dries, and on occasions can "spread" across the film (especially if the wrong side of the film is used).*

*However, let me share with you my pleasure at discovering Overhead Projection (OHP) film. This clear film has been manufactured for use when creating computer generated colour images that are suitable for overhead projection displays, which are commonplace when "presentations" are made by Public Relations departments in a multitude of industries.*

*PC World was my own source and there are several manufacturers. Not knowing what I was destined to achieve with it, I bought from a cheaper range, but which was said to be suitable for Epson inkjet printers. It is brilliant to use!*

*Subsequent exposure time in my UV printer, using Mega photosensitive board, is down to two and half minutes, whereas it had been four minutes with the drafting film. The definition is great and even tracks a mere "15 thou" (about 0.4mm) wide retained their width perfectly. The image is the best I have had since I ceased using a plate camera to photograph hand-drafted tape and pad masters (before CAD became affordable).*

*I heartily recommend OHP film to anyone making their own track masters using an inkjet printer (as I write, another EPE author has also discovered it, sending his latest p.c.b. design printed on it).*

## ELECTRONICS SHORTAGE

Dear EPE,

Reading the News item in June's issue about the Electronics Labour Shortage, I could not help but laugh out aloud. I have been trying to get a job in the electronics industry for the past twenty years but to no avail. At first I would phone for jobs and send for application forms and would get some replies stating that they need people with qualifications. This was back in the late 70s.

I thought, OK, go to college and get some qualifications. So for four years I attended my local college and gained the City & Guilds 2240 Electronic Servicing and various other certificates, but having these qualifications did not make any impact on prospective employers.

I was also interested in the assembling side of electronics. I trained at various establishments to gain experience and knowledge to increase my chances of gaining work in this field. It did not make any difference to the outcome. My last interview was several weeks ago at a large Japanese company that makes electronic parts for the automotive industry. Despite the experience I had obtained working on a full time placement for an electronic scales builder, I was turned down again. So how can you state there's a skills shortage when companies are so picky?

Brian Wintle, via the Net

*We are sorry to learn of your difficulties, Brian, but it is very difficult for us to comment. The item was a News report about a survey by KPMG - we did not produce the results they reported from the electronics industry.*

*We do hope you have better success with your next application.*

## ACTIVE JAVA

Dear EPE,

While C is certainly one of the dominant languages for embedded systems today, Java is definitely getting in on the act, being suitable for PC-side user interface applications, and there is a lot of activity on making Java runtime environments small enough for microcontroller applications.

Java has a number of advantages for the hobbyist, the main one is that it is free and available on all the common platforms including Windows and Linux - write the application for one and it will run on all. Compare this with C which varies slightly across different platforms and Delphi which I believe may only be available on Windows.

One potential drawback is that Java is interpreted and so slower than C, for example. However, it is fast enough compared with Visual Basic and compilers are available, GCJ for instance, to support more demanding applications. Having programmed in C++ I've also found object oriented programming is far easier and more intuitive with Java than C++ to the extent that I now use Java almost exclusively.

Java has a very active community developing both the language and application libraries and there are numerous books at all levels. The best place to start is [www.java-soft.com](http://www.java-soft.com), this is the home of Java and the source for all API documentation, software development kits and an excellent on-line/downloadable tutorial.

Other useful sites include: Gamalan at [softwaredev.earthweb.com/java](http://softwaredev.earthweb.com/java) and *The Java Developer's Journal* at [www.svs-con.com/java/index2.html](http://www.svs-con.com/java/index2.html)

David Price, Reading, Berkshire, via the Net

*Interesting, David, but we are not sure that Java is actually a language that would suit the type of projects that we publish.*

*Opinions, anyone?*

*Personally, having got to grips with VisualBasic (VB6), I find it superb to use and love playing with it. (Watch out for my Spectrum Analyser that I've written in VB6!)*

# L.E.T PIC BASIC PRO COMPILER

The Fast and Easy way to Program the PIC Microcontroller

Write and Compile your first Program in under 5 minutes  
Distribute your applications ROYALTY FREE  
Technical Support direct from the authors  
Dedicated user group mailing list  
Easy to navigate Windows (GUI)  
CDROM Includes software and example programs  
Book Includes worked examples and Projects  
Supports the popular PIC micro's including Flash devices

## INCLUDES:


LET PIC BASIC Pro Compiler on CD-ROM  
LET PIC BASIC User Guide on CD-ROM  
Data Sheets and support documents on CD-ROM  
Adobe Acrobat reader on CD-ROM  
StampPlot Lite  
LET PIC BASIC Unleashed Book  
Printed User Guide

Includes  
CD-ROM

L.E.T. PIC  
BASIC PLUS  
NOW AVAILABLE  
**£99.95**  
+ £5.50 p+p  
+VAT

Download StampPlot

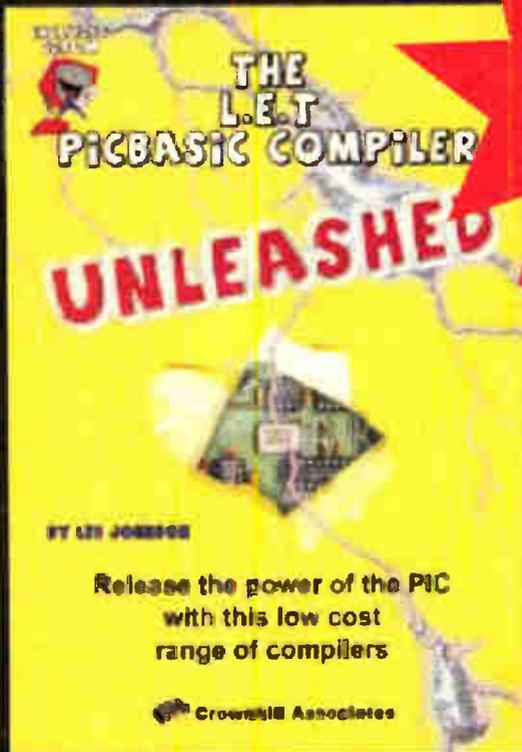
Free at [www.letbasic.com](http://www.letbasic.com)



LET PIC BASIC Unleashed by Les Johnson

Covering the following subjects:  
Interfacing to LCD and LED Displays  
Interfacing to Keypads  
Infrared Remote Control  
Using the 433Mhz Transmitter/Receiver Modules  
Interfacing to Serial Devices  
Temperature Measurement  
Downloading the computer's time  
Using the on board A to D Converter  
Advanced Programming Techniques  
RS232 serial communications demystified  
Implementing interrupts in BASIC  
Temperature data Logging Project

LET PICBASIC produces tight concise code from your program written in the easy to learn yet powerful BASIC language. You no longer have to struggle to learn machine code to use the popular PIC Microcontrollers, the compiler will produce code for both the 12 bit and 14 bit micros, therefore it can be used to produce code for any of the popular PIC devices including the 12C508 and 12C509 and the 16F84 and 16F877 and other popular Flash Devices.

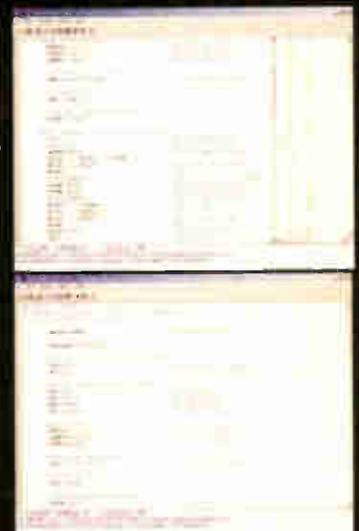

**FREE Download**  
**L.E.T PIC BASIC LITE**  
[www.letbasic.com](http://www.letbasic.com)

**Crownhill Associates Limited**

32 Broad Street Ely Cambridge CB7 4AH  
Tel:01353 666709 Fax:01353 666710



ORDER ONLINE [www.crownhill.co.uk](http://www.crownhill.co.uk)  
All prices are subject to a delivery charge + VAT@17.5%

# CONTROLLING FLIGHT

OWEN BISHOP



*An insight into how electronics helps to maintain aircraft safety.*

**A**IRCRAFT safety is of paramount importance to us all, whether we are flight passengers or simply ground-based below a flight path. This article highlights how electronics is used to control and monitor aircraft performance and help to ensure safety.

## FLIGHT SURFACES

The primary flight surfaces that control the attitude and direction of an aircraft are the ailerons on the trailing edge of the wings, the elevators at the trailing edge of the tailplanes (which may themselves be trimmable) and the rudder behind the tail fin.

The secondary flight surfaces include the flaps or slots, which are narrow strips at the leading or trailing edges that are moved out from the wing when the aircraft is flying at low speed so as to prevent the aircraft from stalling. Also included with the secondary flight surfaces are the spoilers or speed brakes. You can often see these rather wider strips angled sharply up from the upper wing surface just after a landing. They are used to decelerate the aircraft rapidly prior to taxiing to the terminal.

In the early days of flying, the primary flight surfaces were moved into position by a purely mechanical system of levers, cranks and cables. The pilot physically wrestled with the joystick and the foot-propelled rudder bar. Later, hydraulic systems were introduced so that the safety of the aircraft was no longer dependent on the brute strength of the pilot. Nowadays there is still a joystick in the cockpit, but it is reduced in size and delicately adjustable. It is very similar in appearance to the joystick commonly used for computer games.

## MOVING A SURFACE

A flight surface is usually moved by an electric motor with reduction gearing to decrease the rate of rotation and to correspondingly increase the torque. Alternatively, the surface is moved by electro-hydraulic actuators, consisting of solenoid-operated valves and an assemblage of pistons and levers.

Moving an aileron, for example, is not just a matter of switching on the motor and

then switching it off again when the aileron has reached the required angle. Flight surfaces are subject to strong forces from air streams and their motion must be closely monitored and tightly controlled. Feedback from position sensors is used to ensure that the surface has actually moved to where it should be.

Another requirement is that the motion from the current position to the new position must take place as quickly as possible. Fig.1 shows a profile of the kind of motion needed. At time A, the aileron is at a given angle to the wing. During the period A to B it is accelerated at the maximum rate (a rate that will not cause it or the mechanism any mechanical damage) until it reaches its maximum angular velocity.

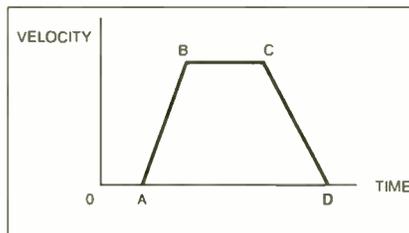


Fig.1. A plot of a trapezoidal velocity profile.

The curve is level for the period B to C, showing that the aileron is now turning as fast as possible. The final stage is to decelerate it, again at the maximum safe rate, so that it comes to rest (that is its velocity is zero) at the exact moment at which it reaches the desired new angle. The length of the curve from B to C has to be calculated so as to bring this about.

Deceleration begins at time C and the aileron comes to rest at time D. Because of the shape of the curve, this is known as a trapezoidal control profile. If the change of angle is small and the aileron has to start decelerating before it has attained maximum angular velocity, the profile becomes a triangle.

## MECHANICAL INERTIA

There are mechanical problems to be dealt with as well as electronic ones. However robust the control mechanism,

there is always a certain amount of inertia to be taken care of. It is impossible to stop motion without exerting some mechanical counter-force.

In the case of an aileron or other movable flight surface, it is essential for it to stop dead when it lines up with the fixed surface of the wing. To allow it to move even as little as 1mm beyond the stopping point is to invite distortion of the moving surface or of the wing itself. Various materials have been tried to absorb the closing impact but none have been found satisfactory. The current solution is to incorporate a slipping clutch into the drive.

The algorithm for calculating the required angular velocity moment by moment is moderately complex. It depends on the original and required aileron angles and on certain parameters such as the maximum allowable acceleration and deceleration and the maximum allowable velocity. Variations in airflow over the wings will exert forces on the aileron. The calculations must compensate for these.

## MICROCONTROLLING MOTORS

Calculations of this degree of complexity need a microcontroller or microprocessor. Then, putting the calculated motion into effect is not simply a matter of switching the motor on or off. The torque required from the motor must be calculated on a continuous basis in terms of current to be sent to its coils. This stage too needs a processor of some kind.

Motors used in these LEMACs (Large Electro-Mechanical Actuating Systems) are generally of the variable reluctance type. A variable reluctance motor comprises a coil-less multipoled rotor, spinning within a multipoled stator, which has electromagnetic coils.

The number of poles of the rotor differs from that of the stator. Typically, the rotor has six poles angled 60° apart, and the stator has eight poles angled 45° apart. This means that only one pair of poles of the rotor can be aligned with a pair of poles of the stator at any one time.

The rotor is made to turn by applying a sequence of pulses to the coils of the stator. The action is similar to that of a stepper motor but it is not a stepping action. It is a continuous action, and the driving circuits are required to supply a sequence of precisely timed and carefully shaped pulses to the coils. A microcontroller is used to produce these pulses.

## SLAVE PROCESSORS

As explained, there are several operations in moving a flight surface that can be achieved only with the help of a processor. In the most up-to-date systems, the processor is a microcontroller and is situated very close to the actuator. The microcontroller receives a general instruction from the flight computer to move the aileron to a specified new angle. From then on, the microcontroller takes over the control of the aileron, leaving the flight computer free to deal with other flight surfaces or with other aspects of flying the aircraft.

Using stored data and feedback from sensors in the wing, the microcontroller moves the aileron to its new position. Then it reports back to the flight control computer that the task has been completed. It may also report back at intermediate stages, if interrogated by the flight computer.

Many of the sensors referred to above incorporate a microcontroller to supervise their activities and to process the data they produce. For example, the angular position of a mechanical part, such as an aileron, may be sensed by a linear inductive position sensor (LIPS).

The input to the sensor is a 1MHz signal of fixed amplitude. The amplitude of the output signal is proportional to the present position of the moving part. The output signal is sampled at the same phase in each cycle, giving a d.c. voltage proportional to the position of the part. The interface circuit is small enough to be contained within the casing of the sensor.

## FLY-BY-WIRE


The control of flight surfaces as described in the previous paragraphs is part of the "fly-by-wire" system developed by Lucas Aerospace for the Airbus 320 and 330. The official name for this system is Integrated Modular Avionics (IMA). The dictionary defines avionics as the application of electronics to aviation.

The concept of localising much of the computing within the wings does a lot to simplify the cabling of the system. It also leads to a modular approach to the flight systems. There are many such systems in the Airbus, each functioning autonomously, yet each sharing data with certain other systems so that the control of the aircraft as a whole is coordinated. The controllers for most of these systems are located in a special hold below the flight deck – see photograph above.

The whole fly-by-wire system is digital except in the final links connecting it to the sensors and actuators. The modular approach includes specialised processing cards for handling the data and gateway cards for routing data through the system.

One of the more recent developments is the use of multi-purpose modules. These are able to perform a wide range of functions. When a multi-purpose card is plugged into the rack, it automatically reads the configuration of the contact terminals in the socket. From this information it is able to deduce what function it is expected to perform there. It then configures itself to perform that function.

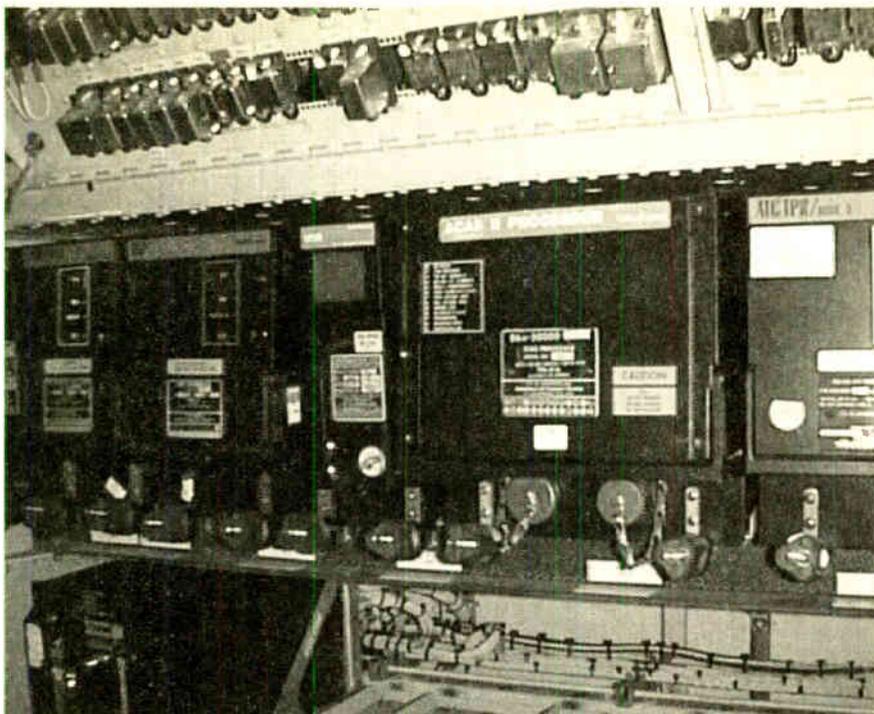These Generic Smart Actuator Controllers (GSACs) greatly simplify the



Control cabinets below the flight deck of an Airbus 330.

problem of stocking spares, since only one type of module need be stocked.

## SAFETY

As might be expected, safety aspects loom large in all the systems and routines connected with flight. At one time, avionics circuits were built from devices having military specifications. These have the advantage of high reliability and guaranteed performance, but are very expensive and often difficult to obtain. Now the trend is to use the standard specification types that are readily available commercially. Circuit builders rely on rigorous design of the circuit to provide the required reliability and margins of safety.

Redundancy is a widespread way of making a system reliable. Redundancy on the small scale is exemplified by replacing a single component by two or three identical components, usually wired in parallel. If one fails, the others continue to operate.

For example, if a voltage is to be regulated by a Zener diode, three such diodes wired in parallel will give virtually the same regulation, even if two of the three fail. The laws of probability show that if the chance of one component failing in a given period is one per cent, the chance of all three failing at the same time is one per cent of one per cent of one per cent, which is one in a million.

Another example of redundancy is the use of two or three sensors to measure the same quantity. If their outputs agree, all is well. If there is a discrepancy between their outputs, a warning is generated to call attention to the failure.

## MULTIPLE MEASUREMENTS

A more subtle approach is to use different techniques to measure the same quantity. For example, the speed of a motor may be measured by using a magnetic or optical sensor driving a tachometer circuit. At the same time, the speed may be calcu-

lated from measurements of the back e.m.f. of the motor. The output of the tachometer circuit is compared with the back e.m.f. measurements and any disagreement results in an alarm signal or corrective action by the computer.

An example of large-scale redundancy is illustrated in the photograph on the next page. Toward the top of the photograph there are duplicate control panels. The panel on the right is normally used by the pilot while that on the left is used by the co-pilot. If they should accidentally try to operate their controls differently, a warning signal is heard and the pilot's panel takes priority. If either panel fails, the aircraft can be flown using the other panel. If both fail, the third panel at the bottom of the photograph can be used.


With more and more control functions being implemented in software, it is not only the avionics that must be reliable. Software must not fail to act as expected. For this reason, the software is often written in a rigorous high-level language, such as ADA. A proprietary language known as LUCOL is used by Lucas Aerospace and, for the control of Rolls Royce engines, they have cooperated with Rolls Royce to produce a language known as FADEC (Full Authority Digital Engine Control).

## TESTING

Thorough testing at the design stage is another contributor to safety. When testing the mechanical parts of an aircraft, it is no longer a matter of "taking her up for a spin". Every part of a modern aircraft is exhaustively tested well before the day of the first take-off.

An example of the close scrutiny given to all the parts of the mechanism is the test bed designed and built by Machines and Systems (Design) Ltd. for testing a gearbox made by Lucas Aerospace (Fig.2).

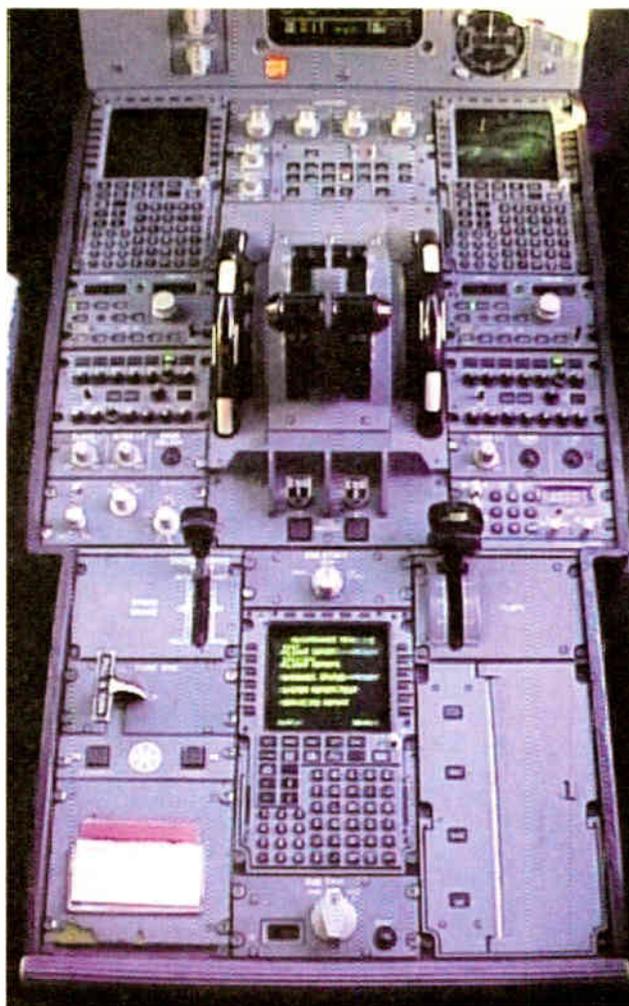The gearbox being tested is a tee gear used for linking a motor with an aileron. Motor 2 is the motor normally used as the



Triplicate control panels on the flight deck of an Airbus 330.

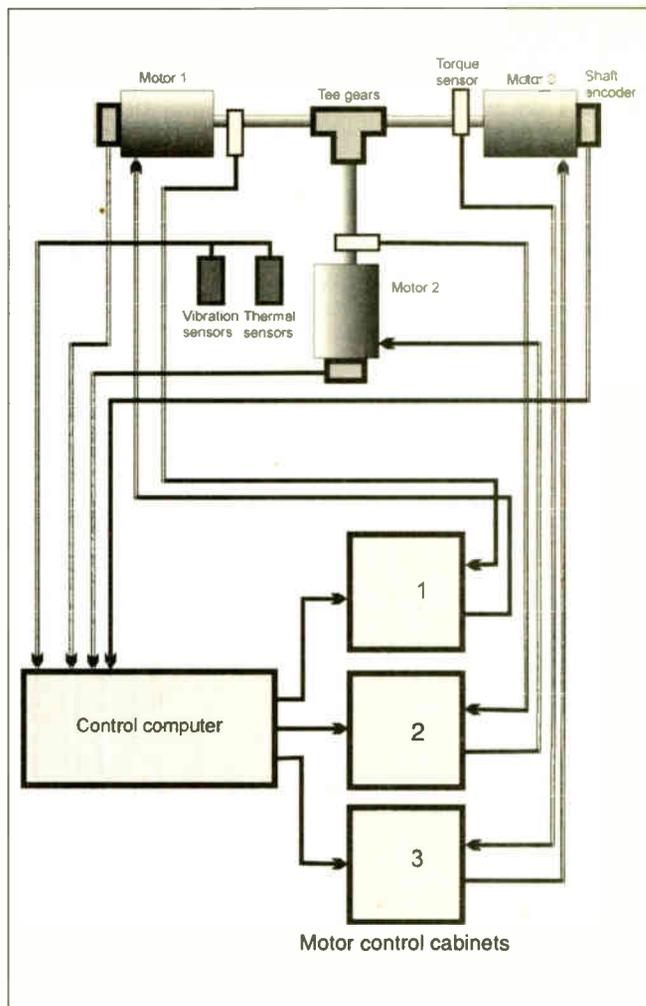


Fig.2. A block diagram of a test-bed designed for testing actuator gearboxes.

aileron actuator. Motors 1 and 3 drive the cross-shaft and are intended to simulate the action of airflow on the aileron.

Each motor has its own control circuitry housed in a motor control cabinet. The whole system is under computer control. The computer is normally programmed in VEE, a language specially intended for control systems. This is a visual language by Hewlett Packard in which the programmer drags symbols representing functional blocks on to the screen, and joins them by "wires". VEE then produces the program to give the required control action.

The motors receive a d.c. drive current from their control cabinets and data from each motor is fed back to the cabinets and to the computer from a shaft encoder and a torque sensor. The shaft encoder is similar to those used in the Lovell telescope, described in the June '01 issue. This gives a measure of the angular position of the shaft.

### TORQUE SENSING

Two types of torque sensor have been used in this test bed. The simplest and cheapest consists of a double flanged shaft with strain gauges set at 45° so as to measure the shear stress in the shaft. The principle of the strain gauge is that its resistance changes when the thin metal foil of the gauge is subjected to strain. The filaments of the gauge become stretched, and thus become longer and thinner.

As a result, their resistance increases.

The change in resistance is relatively small so a sensitive measuring circuit is required. This usually takes the form of a bridge, with a gauge in each arm.

In the case of the torque sensors, the bridge must have an electrical connection for the alternating drive current and a connection to the instrumentation circuit that buffers and amplifies the output signal. The connections are made by way of silver contact slip rings to allow the shaft to rotate freely while torque is being measured.

More recently, a new type of sensor dispenses with the slip rings. The supply current is generated in the bridge electromagnetically, using an inductive loop. On the output side, an f.m. signal is transmitted to a loop receiver. There are integrated electronics on both the stator and rotor to deal with signal processing. These new sensors are more expensive but are more robust and can deal with very high rates of revolution.

Most of the signal links in this system are by optical fibre to avoid electromagnetic interference from the motors. The system also includes sensors to detect overheating and excessive vibration. These are connected to the main computer by one-bit digital lines. In an emergency, signals from these sensors can automatically shut down the system.

Under computer control, and in real time, the gearbox can be taken through a prescribed regime of driving force and

the resulting reaction from simulated effects of airflow. The computer records the torque and angular position of the shafts at each stage. In this way, the ability of the gearbox to function correctly under all possible operating conditions is exhaustively tested.


### ACKNOWLEDGEMENTS

The author thanks the following for helpful advice and information used in this article. At Lucas Aerospace Ltd., Actuators Division, Wolverhampton: Carl Maxwell, Principal Electronics Systems Engineer and R&D Team Leader, Chris Whitley, Principal Electronics Systems Engineer, and Karl Barker, Electronic Systems Engineer. At Machines and Systems (Design) Ltd.: Roger Doyle and John Bugge, Engineering Directors. At Cathay Pacific Airways, Perth International Airport, Western Australia: Colin Myers, Engineering Manager. □

### TRAFFIC CONTROL

Whilst air traffic control in relation to electronics and computing is too complex to discuss simply, road traffic control is a subject of equal importance (and arguably more so) to our daily lives, and which will be highlighted in a future article.
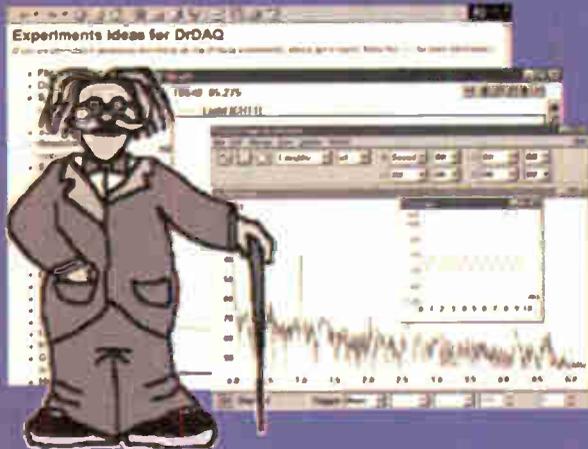
# Measure pH, Voltage, Humidity, Sound & Light, on your PC!




- ✓ Very low cost
- ✓ Built in sensors for light, sound (level and waveforms) and temperature
- ✓ Use DrDAQ to capture fast signals (eg sound waveforms)
- ✓ Outputs for control experiments
- ✓ Supplied with both PicoScope (oscilloscope) and PicoLog (data logging) software

**Only £59!**  
+ VAT

The DrDAQ is a low cost data logger from Pico Technology. It is supplied ready to use with all cables, software and example science experiments.

DrDAQ represents a breakthrough in data logging. Simply plug DrDAQ into any Windows PC, run the supplied software and you are ready to collect and display data. DrDAQ draws its power from the parallel port, so no batteries or power supplies are required.

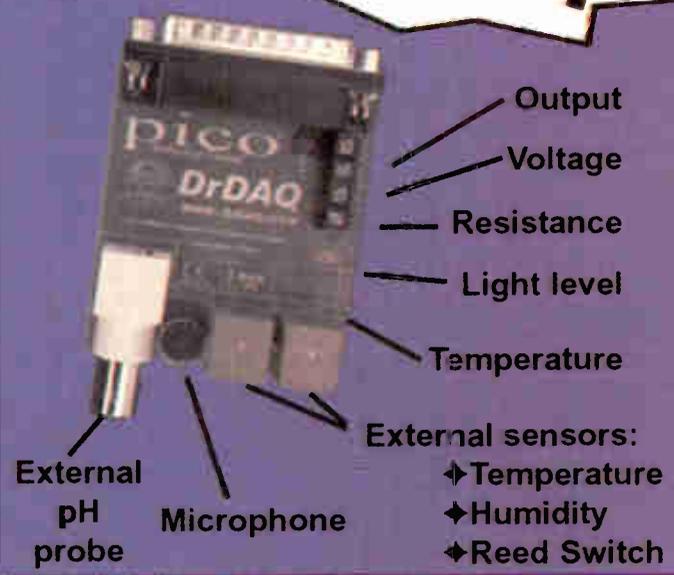As well as the built in sensors, DrDAQ has two sockets for external sensors. When a sensor is plugged in, the software detects it and automatically scales readings. For example, if a temperature sensor is plugged in, readings are displayed in °C. Details are provided to allow users to develop their own sensors.



To order the DrDAQ please choose one of the following options:

- i) Visit our web site and place an order over the Internet,
- ii) Place an order over the phone by ringing the number below, or,
- iii) Fill out the order form and either fax it, or post it back to Pico Technology.

DrDAQ Order Form:			
Quantity	Package	Price inc VAT	Total
	DrDAQ + Software	£69.32	
	DrDAQ + 2 Temp Sensors	£92.85	
	DrDAQ + 2 Temp, pH Electrode, Humidity + Reed Switch Sensors	£175.08	
Delivery		£4.11	£4.11
Grand Total		£	

Name			
Address			
Post code			
Phone			
Credit Card	Visa / Mastercard / Switch / Amex		
Card Number			
Expiry Date	/	Start Date & or Issue No.	
Cheque with order	<input type="checkbox"/>		

PICO A Data Logging Breakthrough

# VIDEOS ON ELECTRONICS

A range of videos selected by *EPE* and designed to provide instruction on electronics theory. Each video gives a sound introduction and grounding in a specialised area of the subject. The tapes make learning both easier and more enjoyable than pure textbook or magazine study. They have proved particularly useful in schools, colleges, training departments and electronics clubs as well as to general hobbyists and those following distance learning courses etc



## BASICS

VT201 to VT206 is a basic electronics course and is designed to be used as a complete series, if required.

**VT201** 54 minutes. Part One; D.C. Circuits. This video is an absolute must for the beginner. Series circuits, parallel circuits, Ohms law, how to use the digital multimeter and much more.


Order Code VT201

**VT202** 62 minutes. Part Two; A.C. Circuits. This is your next step in understanding the basics of electronics. You will learn about how coils, transformers, capacitors, etc are used in common circuits.

Order Code VT202

**VT203** 57 minutes. Part Three; Semiconductors. Gives you an exciting look into the world of semiconductors. With basic semiconductor theory. Plus 15 different semiconductor devices explained.

Order Code VT203

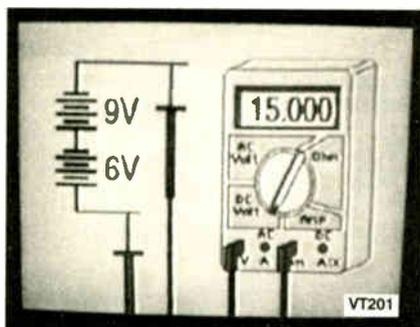

VT201

**VT204** 56 minutes. Part Four; Power Supplies. Guides you step-by-step through different sections of a power supply.

Order Code VT204

**VT205** 57 minutes. Part Five; Amplifiers. Shows you how amplifiers work as you have never seen them before. Class A, class B, class C, op.amps. etc.

Order Code VT205

**VT206** 54 minutes. Part Six; Oscillators. Oscillators are found in both linear and digital circuits. Gives a good basic background in oscillator circuits.

Order Code VT206

**£34.95** each  
inc. VAT & postage

Order 8 or more get one extra FREE  
Order 16 get two extra FREE

## VCR MAINTENANCE

**VT102** 84 minutes: Introduction to VCR Repair. Warning, not for the beginner. Through the use of block diagrams this video will take you through the various circuits found in the NTSC VHS system. You will follow the signal from the input to the audio/video heads then from the heads back to the output.

Order Code VT102

**VT103** 35 minutes: A step-by-step easy to follow procedure for professionally cleaning the tape path and replacing many of the belts in most VHS VCR's. The viewer will also become familiar with the various parts found in the tape path.

Order Code VT103

## DIGITAL

Now for the digital series of six videos. This series is designed to provide a good grounding in digital and computer technology.

**VT301** 54 minutes. Digital One; Gates begins with the basics as you learn about seven of the most common gates which are used in almost every digital circuit, plus Binary notation.

Order Code VT301

**VT302** 55 minutes. Digital Two; Flip Flops will further enhance your knowledge of digital basics. You will learn about Octal and Hexadecimal notation groups, flip-flops, counters, etc.

Order Code VT302

**VT303** 54 minutes. Digital Three; Registers and Displays is your next step in obtaining a solid understanding of the basic circuits found in today's digital designs. Gets into multiplexers, registers, display devices, etc.

Order Code VT303

**VT304** 59 minutes. Digital Four; DAC and ADC shows you how the computer is able to communicate with the real world. You will learn about digital-to-analogue and analogue-to-digital converter circuits.

Order Code VT304

**VT305** 56 minutes. Digital Five; Memory Devices introduces you to the technology used in many of today's memory devices. You will learn all about ROM devices and then proceed into PROM, EPROM, EEPROM, SRAM, DRAM, and MBM devices.

Order Code VT305

**VT306** 56 minutes. Digital Six; The CPU gives you a thorough understanding in the basics of the central processing unit and the input/output circuits used to make the system work.

Order Code VT306


## RADIO

**VT401** 61 minutes. A.M. Radio Theory. The most complete video ever produced on a.m. radio. Begins with the basics of a.m. transmission and proceeds to the five major stages of a.m. reception. Learn how the signal is detected, converted and reproduced. Also covers the Motorola C-QUAM a.m. stereo system.

Order Code VT401

**VT402** 58 minutes. F.M. Radio Part 1. F.M. basics including the functional blocks of a receiver. Plus r.f. amplifier, mixer oscillator, i.f. amplifier, limiter and f.m. decoder stages of a typical f.m. receiver.

Order Code VT402

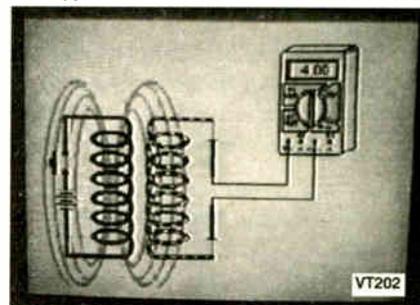

VT202

**VT403** 58 minutes. F.M. Radio Part 2. A continuation of f.m. technology from Part 1. Begins with the detector stage output, proceeds to the 19kHz amplifier, frequency doubler, stereo demultiplexer and audio amplifier stages. Also covers RDS digital data encoding and decoding.

Order Code VT403


## MISCELLANEOUS

**VT501** 58 minutes. Fibre Optics. From the fundamentals of fibre optic technology through cable manufacture to connectors, transmitters and receivers.

Order Code VT501

**VT502** 57 minutes. Laser Technology A basic introduction covering some of the common uses of laser devices, plus the operation of the Ruby Rod laser, HeNe laser, CO<sub>2</sub> gas laser and semiconductor laser devices. Also covers the basics of CD and bar code scanning.

Order Code VT502

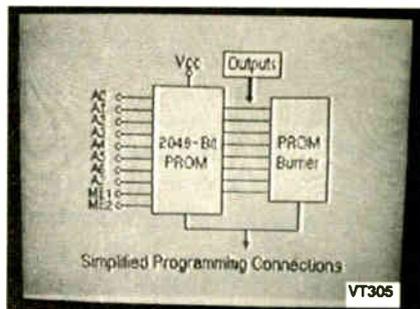

VT305

Each video uses a mixture of animated current flow in circuits plus text, plus cartoon instruction etc., and a very full commentary to get the points across. The tapes are imported by us and originate from VCR Educational Products Co, an American supplier. We are the worldwide distributors of the PAL and SECAM versions of these tapes. (All videos are to the UK PAL standard on VHS tapes unless you specifically request SECAM versions.)

## ORDERING: Price includes postage to anywhere in the world.

**OVERSEAS ORDERS:** We use the VAT portion of the price to pay for airmail postage and packing, wherever you live in the world. Just send £34.95 per tape. All payments in £ sterling only (send cheque or money order drawn on a UK bank). Make cheques payable to Direct Book Service.

Visa, Mastercard, Amex, Diners Club and Switch orders accepted - please give card number, card expiry date and Switch Issue No.

Orders are normally sent within seven days but please allow a maximum of 28 days, longer for overseas orders.

Send your order to: Direct Book Service, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND

Tel: 01202 873872. Fax: 01202 874562. E-mail: [dbs@epemag.wimborne.co.uk](mailto:dbs@epemag.wimborne.co.uk)

Online store: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

# Radio Bygones

The leading magazine for vintage radio enthusiasts

Now Also Available to **BUY ONLINE**  
[www.radiobygones.com](http://www.radiobygones.com)  
 Log on, pay by credit card and download the magazine to your PC  
**ONLY \$9.99 (US dollars) FOR 6 ISSUES**  
 A free issue is available

ARTICLES on restoration and repair, history, circuit techniques, personalities, reminiscences and just plain nostalgia – you'll find them all. Plus features on museums and private collections and a full-colour photo-feature in every issue.

ITS MOSTLY about valves, of course, but 'solid-state' – whether of the coherer and spark-gap variety or early transistors – also has a place.

FROM THE DAYS of Maxwell, Hertz, Lodge and Marconi to what was the state-of-the-art just a few short years ago . . .

THERE IS ALSO a selection of free readers' For Sale and Wanted advertisements in every issue.

## Radio Bygones covers it all!

THE MAGAZINE is published six times a year, and is only available by postal subscription. It is not available at newsagents.

TO TAKE OUT a subscription, or to request a sample copy, please complete the form below and return it to:

**RADIO BYGONES, Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.**

Tel: 01202 873872. Fax: 01202 874562. Web sites: [www.radiobygones.co.uk](http://www.radiobygones.co.uk) [www.radiobygones.com](http://www.radiobygones.com)



## RADIO BYGONES ORDER FORM



A SAMPLE COPY of Radio Bygones . . . . . £3.25  
 (Add 70p for overseas Airmail postage)

SUBSCRIPTIONS (post paid):	<b>1 YEAR</b>	<b>2 YEAR</b>
UNITED KINGDOM	£18.50	£35.00
REST OF EUROPE (AIRMAIL)	£20.50	£39.00
REST OF THE WORLD (AIRMAIL)	£24.50	£47.00

- Yes, I would like a sample copy of RADIO BYGONES
- Yes, I would like to take out a subscription for:
- One year (6 issues)     Two years (12 issues)
- I enclose a cheque/Eurocheque/PO for £ . . . . . payable to Wimborne Publishing Ltd
- Please debit my Visa/Mastercard/Switch card
- NOTE *Minimum credit card payment is £5*

My card number is:

.....  
*Please print clearly, and check that you have the number correct*

The card is valid from: ..... Switch Issue No: .....

My name is .....

My address .....

Post Code/Zip ..... Tel .....

Signed .....

If you do not wish to cut your issue, send a letter or a copy of this form.

## SAVE UP TO 66p AN ISSUE !

DON'T MISS THE WINDOW OF OPPORTUNITY – MAKE SURE OF YOUR COPY NOW!

### ★ PIC TOOLKIT TK3 FOR WINDOWS ★

Annual subscription rates:

Note: Prices will go up next month.

6 Months: UK £14.50, Overseas £17.50 (standard air service),  
 £27 (express airmail)

1 Year: UK £27.50, Overseas £33.50 (standard air service)  
 £51 (express airmail)

2 Years: UK £50.00, Overseas £62.00 (standard air service)  
 £97 (express airmail)

To: **Everyday Practical Electronics,**  
 Wimborne Publishing Ltd., 408 Wimborne Road East,  
 Ferndown, Dorset BH22 9ND

Tel: 01202 873872 Fax: 01202 874562

E-mail: [subs@epemag.wimborne.co.uk](mailto:subs@epemag.wimborne.co.uk)

Order from our online shop at:  
[www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)



## SUBSCRIPTION ORDER FORM



I enclose payment of £ .....  
 (cheque/PO in £ sterling only),

payable to Everyday Practical Electronics



Name .....

My card number is: .....

*Please print clearly, and check that you have the number correct*

Address .....

Signature .....

Card Ex. Date ..... Switch Issue No. ....

Post code ..... Tel. ....

Subscriptions can only start with the next available issue.  
 For back numbers see the Back Issues page.

If you do not wish to cut your issue, send a letter or a copy of this form.

09/01

## LOOP BURGLAR ALARM

### THOMAS SCARBOROUGH



- Solar-Powered - no batteries
- Uses a common - Uniboard - p.c.b.
- Will run indefinitely, without attention
- Ideal for the novice

**T**HIS month, in the penultimate of our four-part series of "perpetual" projects, we give details of a further three circuits that will find many possible uses in and around the home. We also include suggestions for some interesting variations.

All are based on the same Uniboard p.c.b. introduced in Part One (July '01) and are all powered by the *Solar-Powered Power Supply and Voltage Regulator* described in the same issue. Each is designed to run unattended for months at a time without attention - in fact for years!

It only remains for you to select which of the following solar-powered Perpetual Projects most appeals to you! You can, of course, elect to build all the projects, provided you purchase additional p.c.b.s.

☆ **Loop Burglar Alarm** ☆

☆ **Touch-Switch Door-Light** ☆

☆ **Rain Alarm** ☆

Besides these projects, suggestions are made for seven variations - a Broken Beam Beeper, a Power Failure Alarm, a Soil Moisture Monitor, a Thermostat, a Timer, a Liquid-Level Alarm, and a Wake-up Alarm.

In all the projects which follow, only the specifications of IC1 and the l.e.d. are critical. Rough equivalents should work in most other instances without trouble.

### LOOP ALARM CIRCUIT

The simple Loop Burglar Alarm circuit diagram is shown in Fig.1. Note that the component references follow on from the *Solar-Powered Power Supply and Voltage Regulator* circuit published in the July '01 issue.

There are various manufacturers of the 4093 i.c., and the one used throughout this series is the Motorola MC14093BCP. This does make a difference - the make significantly affects both the power consumption and characteristics of the 4093 i.c.

Any unused inputs of IC1 should not be left "floating" (unconnected), otherwise an input may not know what to do, and is likely to behave erratically. By "tying inputs high", a significant amount of power (as much as one third) can be saved.

The circuit works on the principle that when a continuous electrical loop is broken, an alarm is triggered. The loop may include a thin wire snare which would be snapped by an intruder or by the removal of an object through which the loop-wire is threaded.

The "loop" in Fig.1 could also include contacts which would be broken by, for example, a gate or a window opening. Normally-open magnetic switches (closes when a magnet is brought into close proximity to the switch), or microswitches (which are cheaper), would also serve well as contacts for doors or windows (these are wired in series).

However, it should be remembered that such switches can be closed again as quickly as they were opened! They might thus best be used to indicate, for instance, when a shop door has been opened. (See next month for a circuit which adds a *delay* before switching off the oscillator).

Normally-closed switches may be used if you swap the positions of resistor R5 and the loop in the circuit diagram. Such switches are then wired in *parallel*.

### PUSH-PULL

In the circuit diagram of Fig.1, the oscillator (IC1a) causes an audible tone to be produced by piezo disc WD1. Note that instead of wiring the alarm's piezo disc between IC1b's output terminal and the 0V or +V<sub>E</sub> rails (which would work perfectly well), it is wired instead between the two output terminals (pins 3 and 4) of IC1a and IC1b.

Consider that IC1b inverts the output of IC1a. Therefore when IC1a's output goes high, IC1b's output will go low, and vice versa. This, in effect, constantly reverses the voltage across the leads of piezo disc WD1 in a push-pull fashion, and substantially increases the volume of the alarm.

While not sufficient to wake the neighbourhood, the break-contact alarm would hopefully be sufficient to unnerve a would-be intruder/thief!

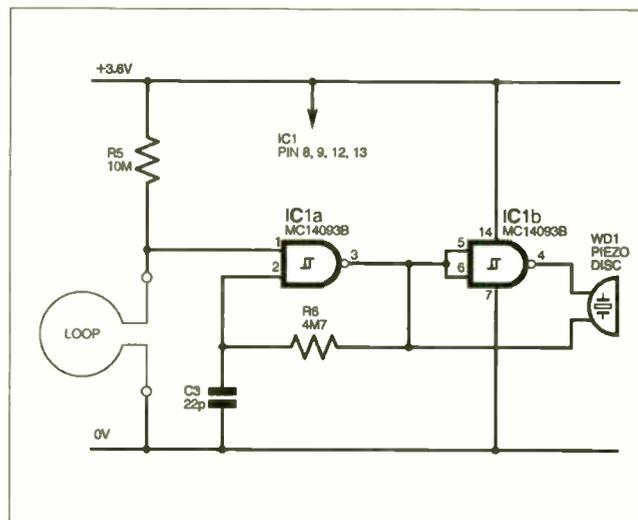
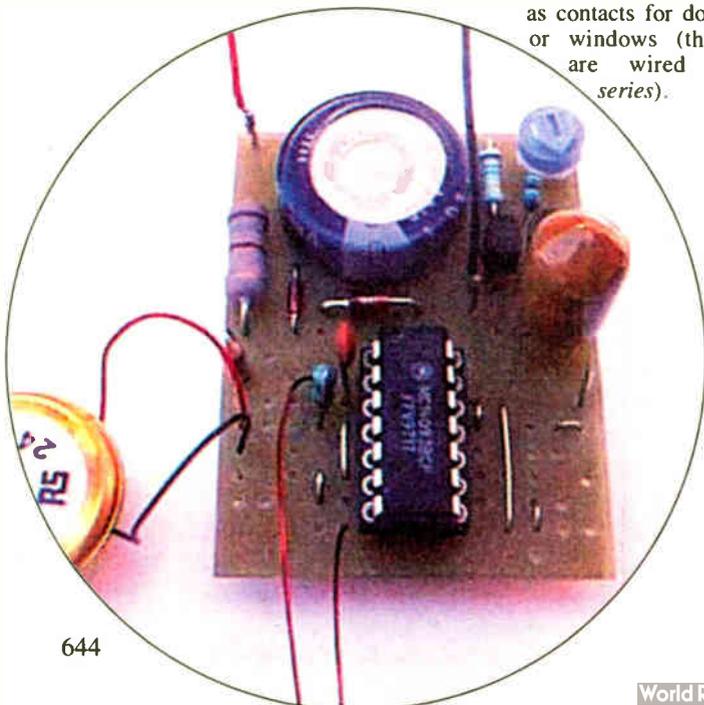


Fig.1. Circuit diagram for the Loop Burglar Alarm. Component numbering continues on from the *Solar-Powered Power Supply and Voltage Regulator* published in the July '01 issue.

## CONSTRUCTION


The Loop Burglar Alarm is built up on the Uniboard p.c.b. as shown in the topside component layout details of Fig.2, together with the copper foil master. This board (minus components) is available from the *EPE PCB Service*, code 305.

Commence construction by soldering the link wires and the resistors in position, continuing with capacitor C3 and attaching the piezo disc WD1 as shown.

Finally, insert IC1 in its d.i.l. socket, being careful again to observe the correct polarity, as well as anti-static precautions. A one megohm (1M) resistor may be wired in series with the loop to protect the input at IC1 pin 1 from possible static, although in practice the circuit is unlikely to miss this.
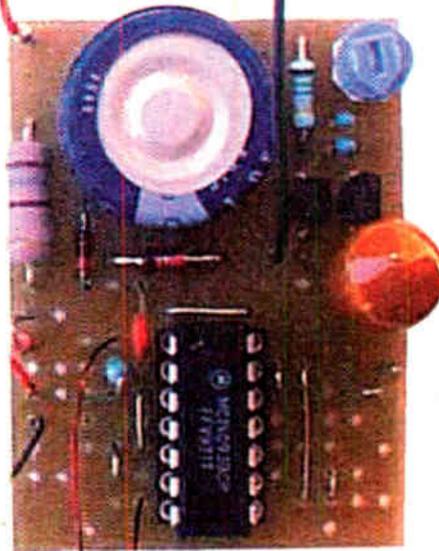
## SETTING UP

Once the power supply capacitor C1 has been fully charged in the sun, via the solar cell (see Part One), adjust the regulator's preset trimmer VR1 until 3.6V is measured



Completed loop alarm circuit board. Also includes solar-powered power supply components.

## COMPONENTS

### LOOP BURGLAR ALARM

#### Resistors

R5 10M  
R6 4M7  
All 0.25W 5% carbon film

See  
**SHOP**  
**TALK**  
page

#### Capacitor

C3 22p ceramic plate

#### Semiconductor

IC1 MC14093BCP quad  
2-input NAND  
Schmitt trigger

#### Miscellaneous

WD1 low profile wire-ended  
piezo sounder

Printed circuit board (Uniboard) available from the *EPE PCB Service*, code 305; multistrand connecting wire; link wires; solder pins; solder etc.

Note: Component designations run on from the Solar-Powered Power Supply and Voltage Regulator described in the July '01 issue.

Approx. Cost  
Guidance Only

£4

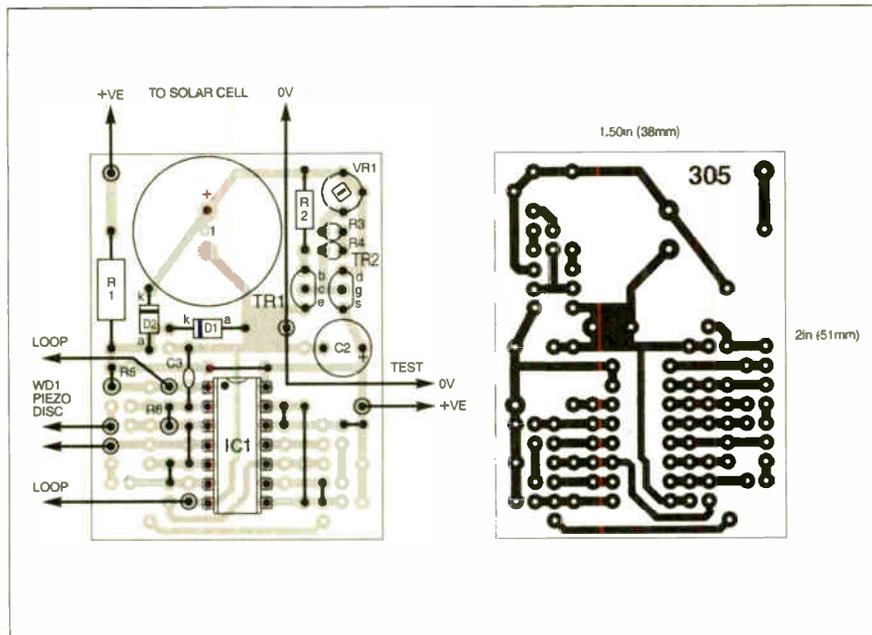


Fig.2. Uniboard component layout and full-size foil master for the Loop Burglar Alarm. Includes components for the solar-powered power supply (July '01).

## SUGGESTION 1 – BROKEN BEAM BEEPER

Try making a Broken Beam Beeper. This will sound when a person breaks a beam of light which shines across (for instance) a doorway. Use the Loop Burglar Alarm as a guide.

Unlike the Loop Burglar Alarm, this circuit draws about 10µA when on standby. If triggering is unreliable, experiment with the value of resistor R5 – a higher value for greater sensitivity to light, and vice versa.

- Substitute an *npn* phototransistor for the loop wire, mounting the phototransistor in a black tube so that it is not affected by ambient light. Wire the emitter (e) to the 0V rail, and the collector (c) to IC1 pin 1 and R5.
- Illuminate the phototransistor with a focussed light-beam.
- Change the value of resistor R5 to 270 kilohms (270k) (this will suit most phototransistors and conditions).

When the resistance of the phototransistor rises above about 540 kilohms (this occurs when the light-beam is broken), the alarm beeps.

## IT'S A LIGHT TOUCH

## SUGGESTION 2 – POWER FAILURE ALARM

Mains voltages are lethal – do not attempt this unless you have a thorough experience of mains wiring.

A distinct advantage of this Power Failure Alarm is that it will never suffer power failure itself – it is perpetual. Wire up the Broken Beam Beeper (Suggestion 1) – but instead of using a light beam as a light source, use a miniature neon lamp which is powered by the mains. House both the miniature neon bulb and the phototransistor in a small dark enclosure.

- For 200V to 250V mains supplies, wire a 270 kilohm 0.5W resistor in series with the miniature neon lamp.
- For 110V mains supplies, wire a 100 kilohm 0.5W resistor in series with the miniature neon lamp.
- Wire a 1nF capacitor in parallel with the phototransistor


### SUGGESTION 3 – SOIL MOISTURE MONITOR

Try modifying the Loop Burglar Alarm to become a Soil Moisture Monitor. Note that since current consumption in this case is up to about 60µA on standby (this was explained in *Part 1* of the series), the circuit is likely to shut down before sunrise. Nevertheless, it should serve its purpose well.

- Substitute two probes for the loop.
- Change resistor R5 to one megohm (1M).
- Wire a 10µF capacitor in parallel with resistor R5.

As the soil dries out, this “breaks the contact” between the two probes which are inserted a short distance from each other in the soil. The capacitor helps when you reset the alarm after triggering.

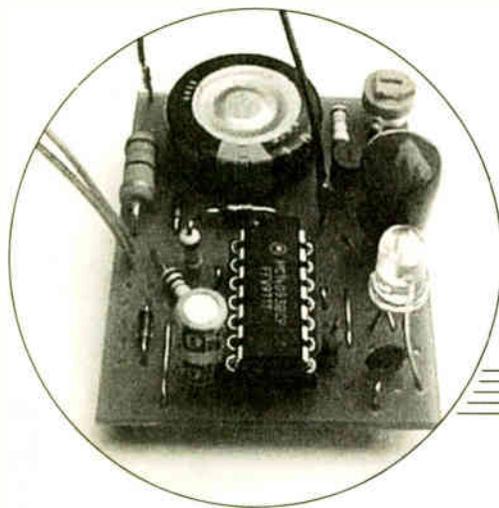Can you see how it functions? When the alarm triggers, water the soil – remove the two probes from the soil, click them together to reset the alarm, and re-insert in the soil.



### SUGGESTION 4 – THERMOSTAT

You might like to try designing a Thermostat to warn of impending frost. Once again, current consumption is up to about 60µA on standby, so that the circuit is likely to shut down before sunrise – this might defeat the purpose of this circuit in some applications. Use the Loop Burglar Alarm as a guide.

- Substitute a thermistor for the loop.
- Wire a 100pF capacitor in parallel with the thermistor (this effectively reduces the source impedance presented to the input, thus reducing current consumption – the “trick” is referred to in *Part 1*).
- Choose a value for resistor R5 to suit (refer to “potential dividers” covered in last month’s Double Door-Buzzer project for guidance).
- If you would like the Thermostat to trigger on *rising* temperature (e.g. for a Freezer Alarm), swap the positions of the thermistor and resistor R5.

Choose a high value for the thermistor (e.g. 100 kilohms at 25°C) to conserve power. What is the thermistor’s rated value at 0°C? What value is required for resistor R5? Refer to last month’s issue for help.

Note that if the potential at IC1 pin 1 needs to rise to about *two-thirds* of the supply voltage to trigger IC1a, it will need to fall to about *one-third* to reset it. How will you reset the gate when the thermostat triggers? Can you do it without a mechanical switch?

## TOUCH-SWITCH DOOR-LIGHT

*A light touch is all you need to show you the way*

**T**HE CIRCUIT diagram for the Touch-Switch Door-Light shown in Fig.3 has several possible applications – among them being to light an entrance upon entering, to illuminate a switchboard during a power failure, or to help you find a keyhole on approaching a door at night.

Once the door-light is triggered, by the touch switch S1, it shines for roughly half a minute at a time. It could be used more than 10 times in the darkness before the regulator’s capacitor C1 is exhausted.

The door-light employs a 5mm extreme brightness white I.e.d. (D4) with a narrow

viewing angle, which provides a good light in a confined space. The I.e.d. D4 is pulsed by the oscillator IC1c, so as to conserve power. No ballast resistor is required, since the effective current flow is limited by the regulator (the white I.e.d. being rated at 3-6V – any other I.e.d. type would need a suitable ballast resistor.).

Capacitor C3 is charged through resistor R6. When the touch-switch S1 is touched, IC1a conducts, and C3 is discharged through diode D3. The output (pin 4) of IC1b then goes high, so that the oscillator (IC1c) is activated, to pulse I.e.d. D4 via IC1d.

When C3 has again charged to two-thirds of the supply voltage, the I.e.d. extinguishes. Diode D3 prevents C3 from being re-charged through IC1a. The on-time of the Door-Light may be lengthened by increasing the value of capacitor C3, and vice versa.

### TOUCH SWITCH

It was decided to use touch-switches throughout this series, since the symbolism of the “perpetual” might be compromised if any mechanical switches were included.

A touch-switch was constructed by the author from the pieces of a broken ultrasonic transducer, the cavity between the “switch” contacts being filled with quick-set putty. It should be constructed in such a way that a finger is sure to close the gap across the two contacts.

Ready-made touch contacts are available from some component suppliers and which could be used instead.

It would be worth noting that touch-switches can pick up static. A recommended simple means of protecting all the circuits in this series against static would be to wire a one megohm resistor in series with each touch-switch. This would be desirable especially if there is an expanse of carpeting near the touch-switch.

If you would prefer a mechanical switch, remember that all touch-switches in this “Uniboard” series may be replaced with pushbutton switches (push-to-make, release-to-break), the accompanying 22 megohms (22M) resistor R5 being exchanged for one of 100 kilohms (100k) value.

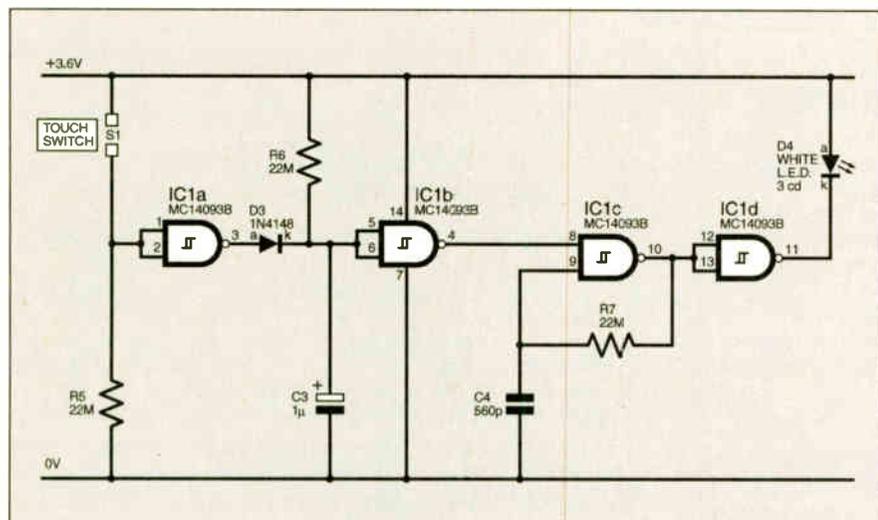


Fig.3. Circuit diagram for the Touch-Switch Door-Light. Note the component references follow on from the power supply published in the July '01 issue.

# COMPONENTS

## TOUCH-SWITCH DOOR-LIGHT

### Resistors

R5, R6, R7 22M (3 off)  
All 0.25W 5% metal film

See  
**SHOP**  
**TALK**  
page

### Capacitor

C3 1 $\mu$  min. radial elec. 10V  
C4 560p min. ceramic plate

### Semiconductors

D3 1N4148 signal diode  
D4 5mm 20° extreme  
brightness white l.e.d.  
IC1 MC14093BCP quad  
2-input NAND Schmitt  
trigger

### Miscellaneous

S1 touch-switch – see text

Printed circuit board (Uniboard) available from the *EPE PCB Service*, code 305; multistrand connecting wire; link wires; solder pins; solder etc.

Note: Component designations run on from the Solar-Powered Power Supply and Voltage Regulator described in the July '01 issue.

Approx. Cost  
Guidance Only

**£7**

Once C1 has been fully charged by the solar cell, adjust the regulator's preset VR1 until 3-6V is measured across capacitor C2 – while the l.e.d. is shining.

Current consumption should be virtually nil on standby, and rises to about 1.4mA when l.e.d. D4 is shining.

The Touch-Switch Door-Light could, if you wish, be detached from the solar cell and used as a make-shift torch (a jack plug and socket could make the connection) – which could be the closest thing yet to the proverbial sun-powered torch! (If you're really serious, then why not build the White L.E.D. Super Torch elsewhere in this issue – Ed.)

**DON'T BE RAINED OFF**


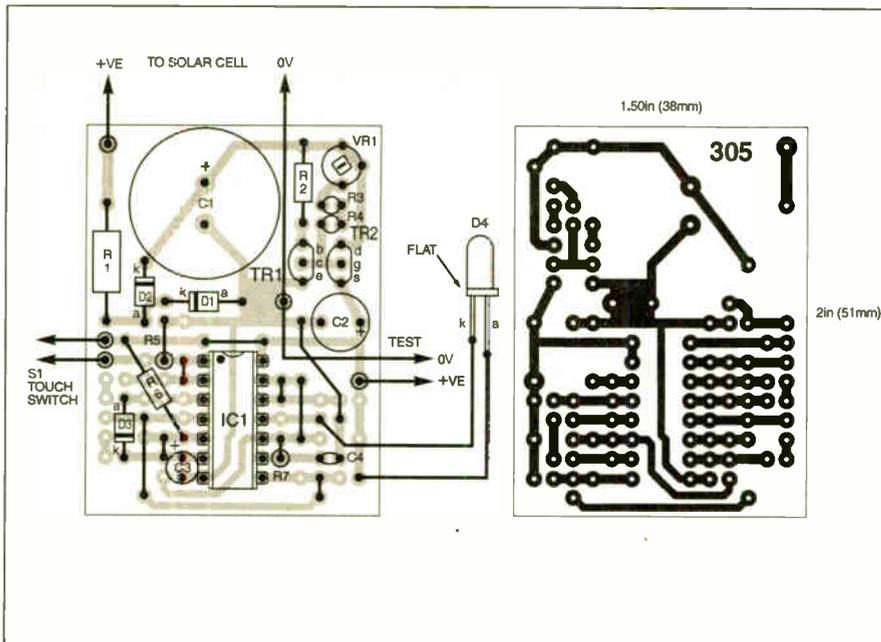


Fig.4. Uniboard component layout and full-size foil master for the Touch-Switch Door-Light. Includes power supply from July '01 issue.
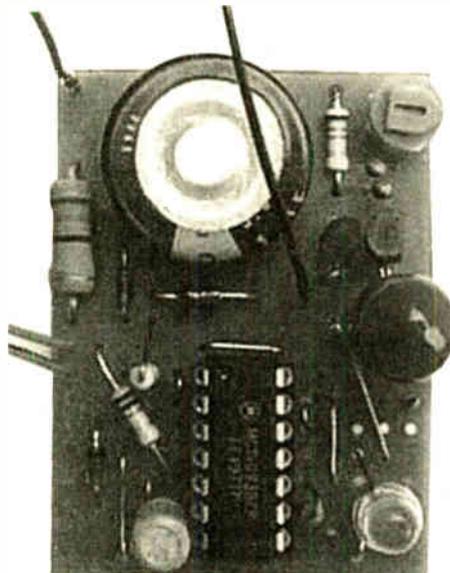
## CONSTRUCTION


The Touch-Switch Door-Light is built up on the Uniboard p.c.b., which may or may not already hold the regulator and d.i.l. socket (see July issue, Fig.2) – as shown in the topside component layout details of Fig.4. This board (minus components) is available from the *EPE PCB Service*, code 305.

Follow the same procedures as previously described, soldering the components to the board in sequence, and finally inserting IC1, observing anti-static precautions. The white light l.e.d. D4 is also static sensitive,



Completed "touch-light" circuit board.

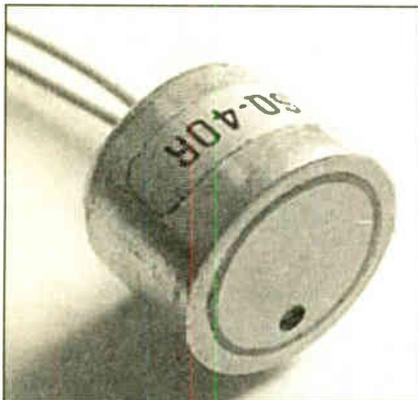so observe anti-static precautions – careful handling could prevent an expensive mistake.




The author's "touch-switch" was made from a broken ultrasonic transducer.

## SUGGESTION 5 – TIMER

You might wish to build a simple Timer. Use the circuit of the Touch-Switch Door-Light. Note that this Timer sounds *while* timing, and falls silent at the end of the timing period. It would thus best be suited to shorter timing periods, where the activity being timed will not slip one's mind.

A value of about 10 $\mu$ F for capacitor C3 will provide a timing period of about four minutes. The Timer produces an unobtrusive tone rather than the higher tone used in alarm circuits in the series.

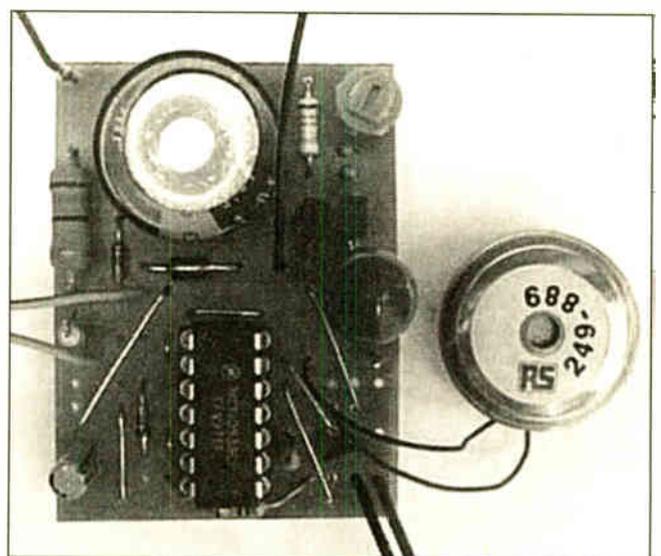- Substitute a piezoelectric disc for the l.e.d. D4
- Substitute a 270pF capacitor for C4.



# SOLAR-POWERED RAIN ALARM



Why not let the sun keep guard over your washing or give you an "early morning" call!

**T**HE FIRST electronic project which the author ever constructed was a *Rain Alarm*, published in *Everyday Electronics* (June 1973). As simple as it was, he was very chuffed with the result!

The Rain Alarm in this Uniboard series is significantly different to that old rain alarm in at least one respect – there would have been no obvious way then to power such an alarm around the clock without batteries.

## CIRCUIT DETAILS

The full circuit diagram for the Solar-Powered Rain Alarm is shown in Fig.5 and involves the most complicated logic of the series (as far as we can call it "complicated")! This is because the user would probably want to switch it *off* again when it is triggered by falling rain. How is this to be achieved without a mechanical switch?

It was decided that, when the alarm sounded, the touch of a finger would put it to sleep again for an hour or so. By that time, the sensor can have been rubbed down with a towel and given time to dry.

Note that oscillator IC1c continues to oscillate "in the background" while the sensor is wet. Therefore if the sensor does not dry within an hour or two, the regulator's "power" capacitor C1 may be exhausted until the sun again strikes the solar panel.

## AUTO SNOOZE

The "off switch" action works as follows. When the touch-switch S1 is touched, IC1a is triggered and its output (pin 3) goes *high*. This charges capacitor C3, via diode

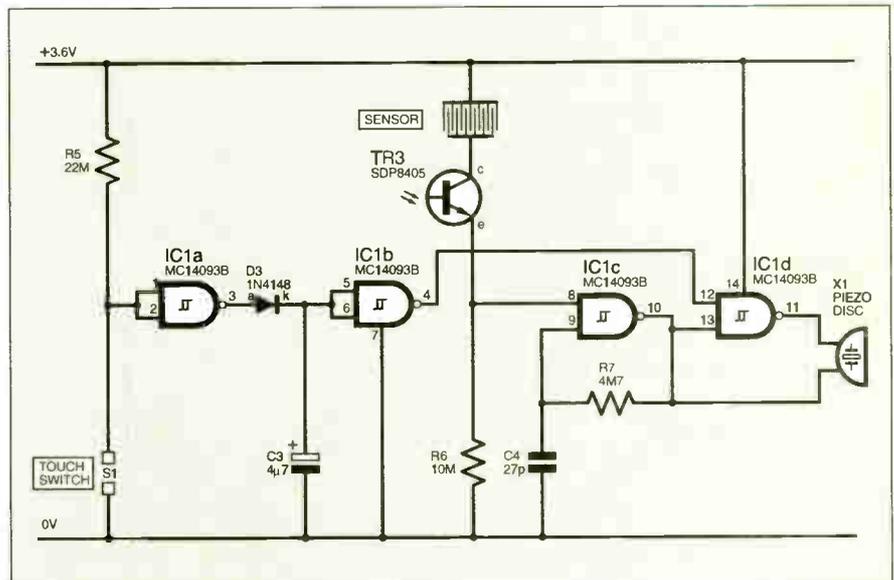


Fig.5. Circuit diagram of the Solar-Powered Rain Alarm. The component annotations run on from the power supply (July '01).

D3, which causes gate IC1b's output, pin 4, to go *low*, switching off the buffer (IC1d) of oscillator IC1c.

Diode D3 is included to prevent discharge of capacitor C3 once it has been charged. Once charged, C3 discharges through various leakage currents in the circuit. The value of C3 may be increased to increase the timing period, and vice versa.


The rain alarm also incorporates a phototransistor TR3, so that the circuit will switch off at night (washing is more often than not taken off the line by nightfall, and you would probably not want to be woken up in the early hours)! In this case, the

phototransistor is wired in series with the sensor, being mounted on the sensor strip-board as shown in Fig.7. If triggering is unreliable, experiment with the value of resistor R6 – a higher value for greater sensitivity to light (and rain), and vice versa.

The oscillator IC1c is activated when a build-up of rain droplets spread (short circuit) across two copper sensor strips.
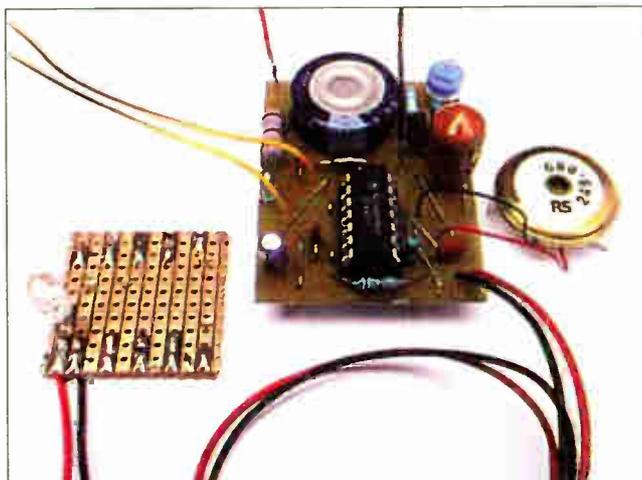
## CONSTRUCTION

The rain alarm is built up on the Uniboard p.c.b., as shown in the topside component layout details of Fig.6. This board (*minus components*) is available from the *EPE PCB Service*, code 305. Once again, the *Solar-Powered Power Supply and Voltage Regulator* components are included in this diagram.



Completed Solar-Powered Rain Alarm with the warning sounder and small rain sensor attached.

## SUGGESTION 6 – LIQUID-LEVEL ALARM

Use the circuit of the Rain Alarm. For an alarm that senses a *rising* liquid level, just one modification is required.

- Substitute *two probes* for the stripboard sensor. These trigger the alarm when they are bridged simultaneously by water.
- If you would like the Liquid-Level Alarm to be triggered by *falling* liquid level (e.g. an empty-tank alarm), swap the positions of the probes and resistor R6.

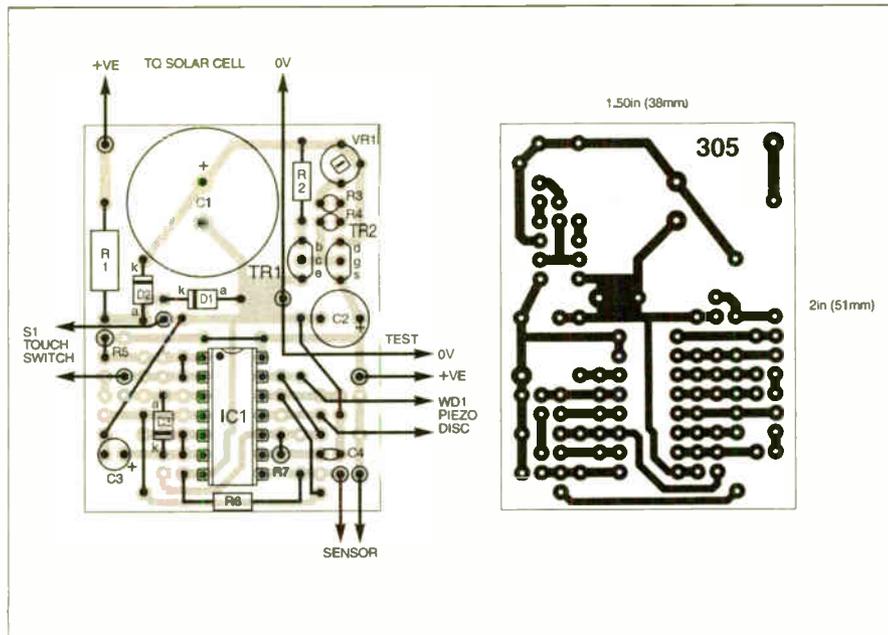


Fig. 6. Uniboard component layout and full-size foil master for the Solar-Powered Rain Alarm. Includes the power supply from Part One (July '01).

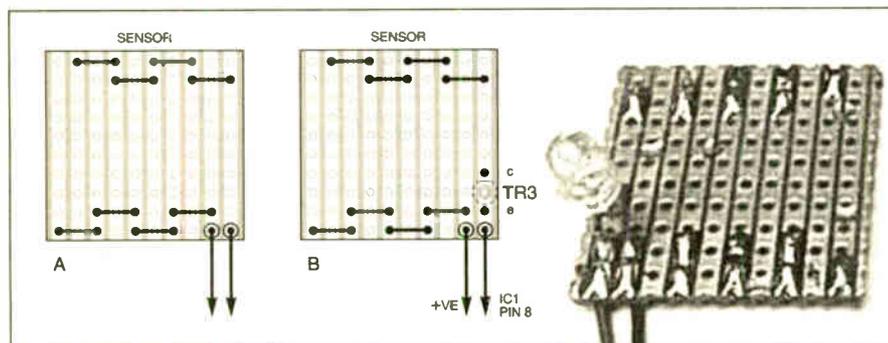


Fig. 7. Rain alarm sensor topside (a) without and (b) with a phototransistor, mounted on the track side. (Right) Stripboard rain sensor with phototransistor soldered directly to the copper tracks.

Follow the same procedures as previously described, soldering the components to the board in sequence, finally inserting IC1, taking anti-static precautions. Take special care with the construction of this project, since a number of diagonal link wires are used.

The Sensor is made from a small piece of stripboard, as shown in the topside layout details of Fig. 7. Alternate copper strips are wired together, so that each adjacent strip forms a bridge to its neighbour when droplets of rain fall into the gaps. The sensor is attached to the circuit by means of a

length of twin-flex wire, so that the p.c.b. itself may be kept in a dry place.

Phototransistor TR3 is mounted on the sensor stripboard (Fig. 7b) on the same side as the copper tracks, with a break being cut in the copper track between the collector (c) and emitter (e) leads. It should be placed where it will not be affected by any night-time light source such as a street lamp.

### SETTING UP

The sensor should be sited where it will be struck by any falling rain or drizzle.

## SUGGESTION 7 – WAKE-UP ALARM

Another variation on the Rain Alarm would be a Wake-up Alarm, to wake you at dawn (but no guarantees that this will get you to work on time)! An *npn* phototransistor is used to trigger the alarm at dawn.

The touch-switch S1 now serves as a “snooze” button. The value of C3 may be increased to give a longer snooze (even to switch it off all day), and vice versa.

- Substitute an *npn* phototransistor for the stripboard Sensor (if you have built a sensor with a phototransistor mounted on it, you may simply short the tracks of the sensor). Wire the phototransistor's emitter (e) to IC1 pin 8 (and R6), and collector (c) to the +3-6V rail.
- Change the value of resistor R6 to 2M2.

## COMPONENTS

### SOLAR-POWERED RAIN ALARM

#### Resistors

- |    |                 |
|----|-----------------|
| R5 | 22M metal film  |
| R6 | 10M carbon film |
| R7 | 4M7 carbon film |

See  
**SHOP**  
**TALK**  
page

All 0.25W 5%

#### Capacitor

- |    |                                |
|----|--------------------------------|
| C3 | 4μ7 sub-min. radial elect. 10V |
| C4 | 27p min. ceramic plate         |

#### Semiconductors

- |     |   |
|-----|---|
| D3  | 1N4148 signal diode                           |
| TR3 | SDP8405 <i>npn</i> phototransistor (optional) |
| IC1 | MC14093BCP quad 2-input NAND Schmitt trigger  |

#### Miscellaneous

- |     |                                      |
|-----|--------------------------------------|
| WD1 | low profile wire-ended piezo sounder |
| S1  | touch-switch – see text              |

Printed circuit board (Uniboard) available from the *EPE PCB Service*, code 305; piece of 0.1in. matrix stripboard, 10 strips x 10 holes, for sensor; multistrand connecting wire; link wires; solder pins; solder etc.

Note: Component designations run on from the Solar-Powered Power Supply and Voltage Regulator described last month (July '01)

Approx. Cost  
Guidance Only


£5

This project needs a supply of 3-6V, so the regulator's voltage should be adjusted to give this voltage – while the circuit is sounding.

Current consumption is virtually nil on standby, and about 500μA when the circuit is sounding. A moist finger on the sensor board will cause the Rain Alarm to sound.
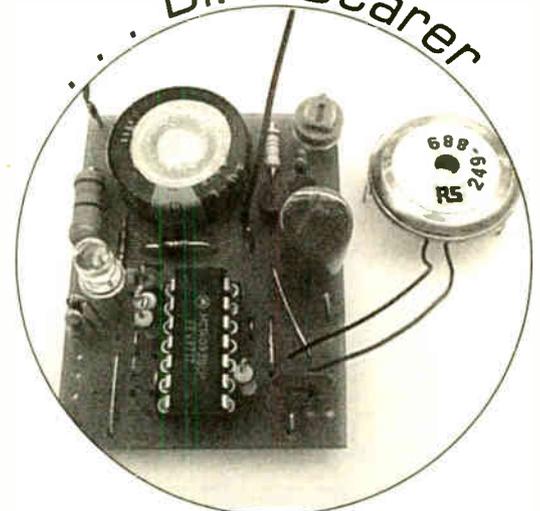
## Bird Scarer

Next month we conclude this short “solar-powered” series with a *Gate Sentinel*, a *Register* and a *Bird Scarer* project. Plus a suggestion for a *Break Contact Alarm*.



# SHOP TALK

with David Barrington

## Water Monitor

Two of the components called up for the *Water Monitor* project are RS components and any local *bona fide* stockist, including many of our advertisers, will be able to obtain them for readers. The 12V d.c. water solenoid valve used in the prototype was ordered from their mail order outlet, **Electromail** (☎ 01536 204555 or <http://rswww.com>), code 342-023. They also supplied the water flow sensor module, code 257-133.

There should not be any problems finding a suitable 2-line 16-character per line alphanumeric I.c.d. module as connection details are included for two possible formats. The one used in the author's model came from **Magenta Electronics** (☎ 01283 565435 or [www.magenta2000.co.uk](http://www.magenta2000.co.uk)). You should specify that you wish to purchase one with a pin connector attached.

For those readers unable to program their own PICs, a ready-programmed PIC16F84 microcontroller can be obtained from **Magenta** (see above) for the inclusive price of £5.90 each (overseas add £1 p&p). The software is available on a 3.5in. PC-compatible disk (*EPE* Disk 4) from the *EPE* Editorial Office for the sum of £3 each (UK), to cover admin costs (for overseas see page 673). It is also available *Free* from the *EPE* web site: <ftp://ftp.epemag.wimborne.co.uk/pub/PICS/WaterMonitor>.

The printed circuit board is obtainable from the *EPE PCB Service*, code 317 (see page 673).

## L.E.D. Super Torches

One or two problems could arise when "shopping" for parts for the *L.E.D. Super Torches*, particularly the red and white l.e.d.s and the ferrite r.f. choke.

The 8mm ultrabright red l.e.d. used in the *Red L.E.D. Torch* came from **Maplin** (☎ 0870 264 6000 or [www.maplin.co.uk](http://www.maplin.co.uk)), code UK24B. The rest of the semiconductors for the "red" version should be readily available. Watch out for the BC184L transistor, other versions have a different pinout line-up. You must specify a "log" type for the Brilliance control VR1.

Both the 5mm extreme brightness (400-mcd) white l.e.d. (code NR73Q) and the MAX761 5V to 12V d.c.-to-d.c. step-up switching regulator (code NR61R) came from the above mentioned company. The MAX761 is also listed by **Electromail** (☎ 01536 204555 or <http://rswww.com>), code 299-553. They also supplied the 47µH 1-2A ferrite bobbin r.f. choke, code 228-450.

The printed circuit boards for the torches are available from the *EPE PCB Service*, codes 313 (Main Red), 314 (Display Red) and 315 (White L.E.D.). The case used by the author for both torches is not the cheapest, but it does have a separate battery compartment and was obtained from **Electromail**, code 583-195.

## Perpetual Projects 3 – Loop Burglar Alarm, Touch-Switch Door-Light and Solar-Powered Rain Alarm

As pointed out in the first instalment (July '01) of this short "solar-powered" series, the Motorola MC14093BCP quad 2-input NAND Schmitt trigger i.c.

should be used in all these projects. It was obtained from **Electromail** (☎ 01536 204555) or <http://rswww.com> code 640-765. In fact, most of the "special" items came from this source.

The 5mm extreme brightness (3cd, 20° viewing) white l.e.d. used in the *Touch-Switch Door-Light* carries the code 310-6690 and the optional SDP8405 phototransistor for the Solar-Powered Rain Alarm is coded 122-267.

The low-profile piezo sounder also came from them, code 249-889, as did the solar cell, code 194-098. you could try using one of the standard disc type piezoelectric sounders.

All three of these projects, plus the additional suggestions, can be built on the special Uniboard p.c.b., which is available from the *EPE PCB Service*, code 305 (see page 673).

## Synchronous Clock Driver

The main cause of concern regarding parts for the *Synchronous Clock Driver* is likely to be finding mains transformers which will fit on the circuit board. Once again, these are RS component types and local *bona-fide* stockists should be able to help.

All of the following were ordered through **Electromail** (☎ 01536 204555), their mail order operation: p.c.b. mounting mains transformers, 0V-9V 6VA twin secondaries (code 805-669) and 0V-15V 6VA twin secondaries (code 805-681); 100µH 2-6A toroidal inductor (306-8605); class X2 275V a.c. suppression capacitor (124-5591) and the 5p to 65p trimmer capacitor (125-660).

The original supplier of the IRF540 n-channel MOSFET has now stopped stocking it. However, we have found the above company has two listings (codes 655-486 and 244-9536) and also that **Farnell** (☎ 0113 263 6311 or [www.farnell.com](http://www.farnell.com)) carry two entries (354-375 and 260-204) for it.

A pre-programmed PIC16F84 microcontroller can be purchased from the author for the sum of £6 (add £1 for overseas). Orders (mail only) should be sent to **Andy Flind, 22 Holway Hill, Taunton, Somerset, TA1 2HB**. Payments should be made out to *A. Flind*. For those who wish to program their own PICs, the software is available from the Editorial offices on a 3.5in. PC-compatible disk (*EPE* Disk 4), see *PCB Service* page 637. It is also available *Free* via the *EPE* web site: <ftp://epemag.wimborne.co.uk/pub/PICS/synclock>.

Finally, the printed circuit board is available from the *EPE PCB Service*, code 316 (see page 637).


## PLEASE TAKE NOTE

### Compact Shortwave Loop Aerial

(August '01)

Some readers have reported problems in obtaining the varicap diode for the loop aerial. Peter Thomas of JAB has confirmed that he is holding good stocks of the KV1235 and KV1236. The prices are £3.80 for the KV1235 and £2.25 for the KV1236. Postage is £2.00 for orders under £5.00 and £1.20 for orders between £5 and £20. Orders should be placed by fax (☎ 0121 681 1329) or E-mail ([Peter@JAB.Demon.co.uk](mailto:Peter@JAB.Demon.co.uk)). Mail orders should be sent to: **JAB Electronic Components** (☎ 0121 682 7045), PO Box 5774, Birmingham, B44 8PJ.

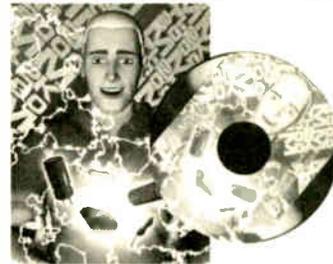**Cricklewood Electronics** (see their ad on page 659) have offered the BB112 single varicap diode as an alternative. This should be OK but has not been tried in the model.



# EPE TEACH-IN 2000

## Now on CD-ROM

The whole of the 12-part *Teach-In 2000* series by John Becker (published in *EPE* Nov '99 to Oct 2000) is now available on CD-ROM. Plus the *Teach-In 2000* software covering all aspects of the series and Alan Winstanley's *Basic Soldering Guide* (including illustrations and *Desoldering*).

*Teach-in 2000* covers all the basic principles of electronics from Ohm's Law to Displays, including Op.Amps, Logic Gates etc. Each part has its own section on the interactive PC software where you can also change component values in the various on-screen demonstration circuits.

The series gives a hands-on approach to electronics with numerous breadboarded circuits to try out, plus a simple computer interface which allows a PC to be used as a basic oscilloscope.

**ONLY £12.45** including VAT and p&p

We accept Visa, Mastercard, Amex, Diners Club and Switch cards.

NOTE: This mini CD-ROM is suitable for use on any PC with a CD-ROM drive. It requires Adobe Acrobat Reader (available free from the Internet – [www.adobe.com/acrobat](http://www.adobe.com/acrobat))

### TEACH-IN 2000 CD-ROM ORDER FORM

Please send me ..... (quantity) TEACH-IN 2000 CD-ROM  
Price £12.45 (approx \$20) each – includes postage to anywhere in the world.

Name .....

Address .....

Post Code ..... Tel. ....

I enclose cheque/P.O./bank draft to the value of £ .....

Please charge my card £ .....

Card No. ....

Expiry Date ..... Switch Issue No. ....

Note: Minimum order for cards £5.

SEND TO: **Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.**

Tel: 01202 873872. Fax: 01202 874562.

E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)

Online store: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.

# SURVEILLANCE

## Electronic Surveillance Equipment Kits from the UK's No.1 Supplier

SUMA DESIGNS has been supplying professional quality electronic surveillance equipment kits for over 20 years. Whether your requirement is hobbyist, amateur or professional you can be sure that you are buying from a company that knows the business. We ONLY sell surveillance products, no alarms, disco lights or computer bits. All of our kits are designed for self assembly and are well tried, tested and proven. All kits are supplied complete with top grade components, fibreglass PCB, full instructions, circuit diagrams and assembly details. Unless otherwise stated all transmitter kits are tuneable and can be received using an ordinary VHF FM radio.

### UTX Ultra-miniature Room Transmitter

At less than 1/2 the size of a postage stamp the UTX is the smallest room transmitter kit in the world! Incredible 10mm x 20mm including microphone, 3-12V operation. Range up to 500m ..... **£13.95**

### MTX Micro-miniature Room Transmitter

Our best selling room transmitter kit. Just 17mm x 17mm including mic. Extremely sensitive. 3-12V operation. Range up to 1000m. .... **£14.95**

### STX High-performance Room Transmitter

High performance transmitter with buffered output for greater stability and range. Measures just 22mm x 22mm including mic. 6-12V operation. Range up to 1500m. .... **£16.95**

### VT500 High-power Room Transmitter

Our most powerful room transmitter with around 250mW of output power. Excellent range and penetration. Size 20mm x 40mm, 6-12V operation. Range up to 3000m. .... **£17.95**

### VXT Voice-activated Room Transmitter

Triggers only when sounds are detected by on-board mic. Variable trigger sensitivity and on-time with LED trigger indicator. Very low standby current. Size 20mm x 67mm, 9V operation, range up to 1000m. .... **£21.95**

### HVX400 Mains Powered Room Transmitter

Connects directly to 240V AC supply. Ideal for long-term monitoring. Size 30mm x 35mm, range up to 500m. .... **£21.95**

### SCRX Subcarrier Scrambled Room Transmitter

To increase the security of the transmission the audio is subcarrier modulated. Receiver now requires the decoder module (SCDM) connected to allow monitoring. Size 20mm x 67mm, 9V operation, up to 1000m range. .... **£24.95**

### SCDM Subcarrier Decoder for SCRX

Connects to earphone socket on receiver and provides decoded audio output to headphones. Size 32mm x 70mm, 9-12V operation. .... **£27.95**

### UTLX Ultra-miniature Telephone Transmitter

Smallest kit available. Connects onto telephone line, switches on and off automatically as phone is used. All conversations transmitted. Size 10mm x 20mm, powered from line, up to 500m range. .... **£13.95**

### TLX700 Micro-miniature Telephone Transmitter

Best selling kit. Performance as UTLX but easier to assemble as PCB is 20mm x 20mm. .... **£14.95**

### STLX High-performance Telephone Transmitter

High-performance transmitter with buffered output for greater stability and range. Connects onto telephone line and switches on and off automatically as phone is used. Both sides of conversation transmitted up to 1000m. Powered from line. Size 22mm x 22mm. .... **£16.95**

### PTS7 Automatic Telephone Recording Interface

Connects between telephone line (anywhere) and normal cassette recorder. Automatically switches recorder on and off as phone is used. Both sides of any conversation recorded. 9V operation, size 20mm x 67mm. .... **£21.95**

### CD400 Pocket Size Bug Detector/Locator

LED and piezo bleeper pulse slowly. Pulse rate and tone pitch increase as signal source is approached. Variable sensitivity allows pinpointing of signal source. 9V operation, size 45mm x 54mm. .... **£34.95**

### CD600 Professional Bug Detector/Locator

Multicolour bargraph LED readout of signal strength with variable rate bleeper and variable sensitivity allows pinpointing of any signal source. When found, unit is switched into AUDIO CONFIRM mode to distinguish between bugging devices and legitimate signals such as pagers, cellphones etc. Size 70mm x 100mm. 9V operation. .... **£59.95**

### QTX180 Crystal Controlled Room Transmitter

Narrow band FM crystal transmitter for ultimate in privacy. Output frequency 173.225 MHz. Designed for use with QRX180 receiver unit. Size 20mm x 67mm, 9V operation, range up to 1000m ..... **£44.95**

### QLX180 Crystal Controlled Telephone Transmitter

Specifications as per QTX180 but connects onto telephone line to allow monitoring of both sides of conversations. .... **£44.95**

### QSX180 Line Powered Crystal Telephone Transmitter

Connects onto telephone line, switches on and off as phone is used. Power is drawn from line. Output frequency 173.225 MHz. Designed for use with QRX180 receiver. Size 32mm x 37mm. Range up to 500m. .... **£39.95**

### QRX180 Crystal Controlled FM Receiver

Specifically designed for use with any of the SUMA 'O' range kits. High sensitivity design. Complex RF front end section supplied as pre-built and aligned sub-assembly so no difficult setting up. Headphone output. PCB size 60mm x 75mm. 9V operation. .... **£69.95**

### TKX900 Signalling/Tracking Transmitter

Transmits a continuous stream of audio beeps. Variable pitch and beep rate. Ideal for signalling, alarm or basic tracking uses. High power output. Size 25mm x 63mm, 9-12V operation, up to 2000m range. .... **£23.95**

### MBX-1 Hi-Fi Micro Broadcaster

Connects to headphone socket of CD player, Walkman or Hi-Fi and broadcasts your favourite music around house and garden up to 250m. Size 27mm x 60mm, 9V operation. .... **£22.95**

### DLTX/RX Radio Remote Switch System

Two kits, transmitter sends a coded signal (256 selectable codes) when button pressed. Receiver detects signal, checks code and activates relay. Can be set to be momentary or toggle (on/off) operation. Range up to 100m, 9V operation on both units. TX 45mm x 45mm, RX 35mm x 90mm. .... **£44.95**

#### TO ORDER:

Post, fax or telephone your order direct to our sales office. Payment can be Credit card (Visa or Mastercard), Postal Order, cash (please send registered) or cheques. Kits despatched same day (cheques need clearing). All orders sent by recorded or registered post. Please add postage as follows:

ORDER UP TO £30.00: To UK £2.50 To EUROPE £5.50 All other £7.50

ORDERS OVER £30.00: To UK £3.65 To EUROPE £7.50 All others call

Overseas customers please use credit cards or send sterling cheque or bank draft.



VISA

#### SEND 2 x 1st CLASS STAMPS FOR OUR 2000 KIT CATALOGUE CONTAINING FULL DETAILS OF THESE AND OTHER KITS.

A BUILD-UP SERVICE IS AVAILABLE ON ALL OF OUR KITS, DETAILS IN CATALOGUE. VISIT OUR WEBSITE: [www.suma-designs.co.uk](http://www.suma-designs.co.uk)

Please note: Some of our part numbers are being unscrupulously used by other companies selling kits eg. MTX, VXT. DO NOT BE MISLEAD! These are NOT GENUINE SUMA KITS which are only available direct from us or our appointed distributors.

If you wish to collect kits direct from our office PLEASE TELEPHONE

# SUMA DESIGNS

Dept. EE, The Workshops, 95 Main Road,  
Baxterley, Warwickshire, CV9 2LE, U.K.  
Website: [www.suma-designs.co.uk](http://www.suma-designs.co.uk)

TEL/FAX: 01827 714476  
(24 HOUR ORDERLINE)  
email: [sales@suma-designs.co.uk](mailto:sales@suma-designs.co.uk)

We can supply back issues of *EPE* by post, most issues from the past three years are available. An *EPE* index for the last five years is also available – see order form. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photostat of any *one article* (or *one part* of a series) can be purchased for the same price. Issues from Jan. 2001 onwards are also available to download from [www.epemag.com](http://www.epemag.com).

## DID YOU MISS THESE?

### MAY '00

**PROJECTS** • Versatile Mic/Audio Preamplifier • PIR Light Checker • Low-Cost Capacitance Meter • Multi-Channel Transmission System-1.  
**FEATURES** • Teach-In 2000-Part 7 • Technology Timelines-4 • Circuit Surgery • Practically Speaking • Ingenuity Unlimited • Net Work – The Internet • **FREE** Giant Technology Timelines Chart.

### JUNE '00

**PROJECTS** • Atmospheric Electricity Detector-1 • Canute Tide Predictor • Multi-Channel Transmission System-2 • Automatic Nightlight.  
**FEATURES** • Teach-In 2000 – Part 8 • Technology Timelines-5 • Circuit Surgery • Interface • New Technology Update • Ingenuity Unlimited • Net Work – The Internet.

### JULY '00

**PROJECTS** • G-Meter • Camera Shutter Timer PIC-Gen Frequency Generator/Counter • Atmospheric Electricity Detector-2.  
**FEATURES** • Teach-In 2000-Part 9 • Practically Speaking • Ingenuity Unlimited • Circuit Surgery • PICO DrDAQ Reviewed • Net Work – The Internet.



### AUG '00

**PROJECTS** • Handy-Amp • EPE Moodloop • Quiz Game Indicator • Door Protector  
**FEATURES** • Teach-In 2000-Part 10 • Cave Electronics • Ingenuity Unlimited • Circuit Surgery • Interface • New Technology Update • Net Work – The Internet.

### SEPT '00

**PROJECTS** • Active Ferrite Loop Aerial • Steeplechase Game • Remote Control IR Decoder • EPE Moodloop Power Supply.  
**FEATURES** • Teach-In 2000-Part 11 • New Technology Update • Circuit Surgery • Ingenuity Unlimited • Practically Speaking • Net Work – The Internet Page.

### OCT '00

**PROJECTS** • Wind-Up Torch • PIC Dual-Chan Virtual Scope • Fridge/Freezer Alarm • EPE Moodloop Field Strength Indicator.  
**FEATURES** • Teach-In 2000-Part 12 • Interface • Ingenuity Unlimited • New Technology Update • Circuit Surgery • Peak Atlas Component Analyser Review • Net Work – The Internet Page.

### NOV '00

**PROJECTS** • PIC Pulsometer • Opto-Alarm System • Sample-and-Hold • Handclap Switch.  
**FEATURES** • The Schmitt Trigger-Part 1 • Ingenuity Unlimited • PIC Toolkit Mk2 Update V2.4 • Circuit Surgery • New Technology Update • Net Work – The Internet • **FREE** Transistor Data Chart.

### DEC '00

**PROJECTS** • PIC-Monitored Dual PSU-Part 1 • Static Field Detector • Motorists' Buzz-Box • Twinkling Star • Christmas Bubble • Festive Fader • PICtogram.  
**FEATURES** • The Schmitt Trigger-Part 2 • Ingenuity Unlimited • Interface • Circuit Surgery • New Technology Update • Quasar Kits Review • Net Work – The Internet • 2000 Annual Index.

### JAN '01

**PROJECTS** • Versatile Optical Trigger • UFO Detector and Event Recorder • Two-Way Intercom • PIC-Monitored Dual PSU-Part 2.  
**FEATURES** • Using PICs and Keypads • The Schmitt Trigger-Part 3 • New Technology Update • Circuit Surgery • Practically Speaking • Ingenuity Unlimited • CIRSIM Shareware Review • Net Work – The Internet.



### FEB '01

**PROJECTS** • Ice Alert • Using LM3914-6 Bargraph Drivers • Simple Metronome • PC Audio Power Meter.  
**FEATURES** • The Schmitt Trigger-Part 4 • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Net Work – The Internet • **Free** 16-page supplement – How To Use Graphics L.C.D.s With PICs.

### MAR '01

**PROJECTS** • Doorbell Extender • Body Detector • DIY Tesla Lightning • Circuit Tester  
**FEATURES** • Understanding Inductors • The Schmitt Trigger-Part 5 • Circuit Surgery • Interface • New Technology Update • Net Work – The Internet Page.

### APRIL '01

**PROJECTS** • Wave Sound Effect • Intruder Alarm Control Panel-Part 1 • Sound Trigger • EPE Snug-Bug Pet Heating Control Centre.  
**FEATURES** • The Schmitt Trigger-Part 6 • Practically Speaking • Ingenuity Unlimited • Circuit Surgery • Net Work – The Internet Page • **FREE** supplement – An End To All Disease.

### MAY '01

**PROJECTS** • Camcorder Mixer • PIC Graphics L.C.D. Scope • D.C. Motor Controller • Intruder Alarm Control Panel-Part 2.  
**FEATURES** • The Schmitt Trigger-Part 7 • Interface • Circuit Surgery • Ingenuity Unlimited • New Technology Update • Net Work – The Internet Page.

### JUNE '01

**PROJECTS** • Hosepipe Controller • In-Circuit Ohmmeter • Dummy PIR Detector • Magfield Monitor.  
**FEATURES** • Controlling Jodrell Bank • PIC1687x Extended Memory Use • Practically Speaking • Ingenuity Unlimited • New Technology Update • Circuit Surgery • Net Work – The Internet Page.



### JULY '01

**PROJECTS** • Stereo/Surround Sound Amplifier • PIC to Printer Interface • Perpetual Projects 1- Solar-Powered Power Supply and Voltage Regulator • MSF Signal Repeater and Indicator.  
**FEATURES** • The World of PLCs • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Net Work – The Internet Page.

### AUG '01

**PROJECTS** • Digitimer • Lead-Acid Battery Charger • Compact Shortwave Loop Aerial • Perpetual Projects 2 – L.E.D. Flasher • Double Door-Buzzer.  
**FEATURES** • Controlling Power Generation • Ingenuity Unlimited • Interface • Circuit Surgery • New Technology Update • Net Work – The Internet page.

## BACK ISSUES ONLY £3.00 each inc. UK p&p.

Overseas prices £3.50 each surface mail, £4.95 each airmail.

We can also supply issues from earlier years: 1998 (except Jan. to May, July, Nov., Dec.), 1999, 2000 (except Feb.). Where we do not have an issue a photostat of any *one article* or *one part* of a series can be provided at the same price.

### ORDER FORM – BACK ISSUES – PHOTOSTATS– INDEXES

Send back issues dates .....

Send photostats of (article title and issues date) .....

Send copies of last five years indexes (£3.00 for five inc. p&p – Overseas £3.50 surface, £4.95 airmail)

Name .....

Address .....

..... Tel: .....

I enclose cheque/P.O./bank draft to the value of £ .....

Please charge my Visa/Mastercard/Amex/Diners Club/Switch £ ..... Switch Issue No. ....

Card No. .... Card Expiry Date .....

Note: Minimum order for credit cards £5.


SEND TO: Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.  
Tel: 01202 873872. Fax: 01202 874562.

E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk) On-line Shop: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)  
Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.


M09/01

# STORE YOUR BACK ISSUES IN YOUR WALLET!

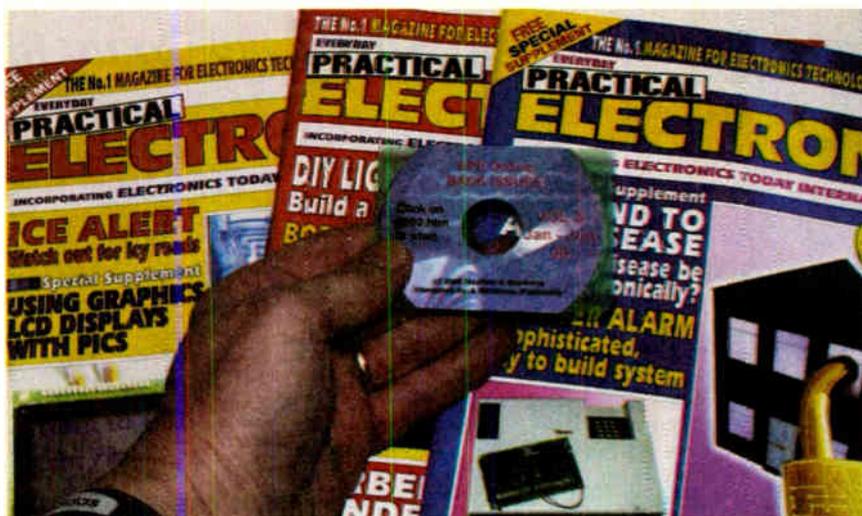

**VOL 4  
NOW AVAILABLE**

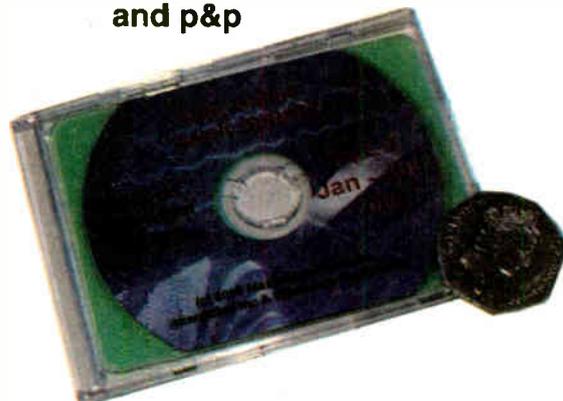**ONLY  
£12.45** each  
including VAT  
and p&p



A great way to buy *EPE* Back Issues – our wallet-sized CD-ROMs contain back issues from our *EPE Online* website plus bonus articles, all the relevant PIC software and web links. All this for just £12.45 each including postage and packing.

## VOL 1 CONTENTS

**BACK ISSUES** – November 1998 to June 1999 (all the projects, features, news, IUs etc. from all eight issues). Note: No advertisements or Free Gifts are included.

**PIC PROJECT CODES** – All the available codes for the PIC based projects published in issues from November 1998 to June 1999.

## VOL 2 CONTENTS

**BACK ISSUES** – July 1999 to December 1999 (all the projects, features, news, IUs, etc. from all six issues). Note: No advertisements or Free Gifts are included.

**PIC PROJECT CODES** – All the available codes for the PIC-based projects published in issues from July to December 1999.

## VOL 3 CONTENTS

**BACK ISSUES** – January 2000 to June 2000 (all the projects, features, news, IUs, etc. from all six issues). Note: No advertisements or Free Gifts are included.

**PIC PROJECT CODES** – All the available codes for the PIC-based projects published in issues from January to June 2000.

## VOL 4 CONTENTS

**BACK ISSUES** – July 2000 to Dec. 2000 (all the projects, features, news, IUs etc. from all six issues). Note: No Free Gifts are included.

**PROJECT CODES** – All the available codes for the programmable projects from July to Dec. 2000.

## EXTRA ARTICLES – ON ALL VOLUMES

**BASIC SOLDERING GUIDE** – Alan Winstanley's internationally acclaimed fully illustrated guide.

**UNDERSTANDING PASSIVE COMPONENTS** – Introduction to the basic principles of passive components.

**HOW TO USE INTELLIGENT L.C.D.s**, By Julyan Ilett – An utterly practical guide to interfacing and programming intelligent liquid crystal display modules.

**Phyzyb COMPUTERS BONUS ARTICLE 1** – Signed and Unsigned Binary Numbers. By Clive "Max" Maxfield and Alvin Brown.

**Phyzyb COMPUTERS BONUS ARTICLE 2** – Creating an Event Counter. By Clive "Max" Maxfield and Alvin Brown.

**INTERGRAPH COMPUTER SYSTEMS 3D GRAPHICS** – A chapter from Intergraph's book that explains computer graphics technology in an interesting and understandable way with full colour graphics.

## EXTRA ARTICLE ON VOL 1 & 2

**THE LIFE & WORKS OF KONRAD ZUSE** – a brilliant pioneer in the evolution of computers. A bonus article on his life and work written by his eldest son, including many previously unpublished photographs.

NOTE: This mini CD-ROM is suitable for use on any PC with a CD-ROM drive. It requires Adobe Acrobat Reader (available free from the Internet – [www.adobe.com/acrobat](http://www.adobe.com/acrobat))

Order on-line from

[www.epemag.wimborne.cc.uk/shopdoor.htm](http://www.epemag.wimborne.cc.uk/shopdoor.htm)

or [www.epemag.com](http://www.epemag.com) (USA \$ prices)

or by phone, Fax, E-mail or Post

### BACK ISSUES CD-ROM ORDER FORM

Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 1

Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 2

Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 3

Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 4

Price £12.45 each – includes postage to anywhere in the world.

Name .....

Address .....

.....

..... Post Code .....

I enclose cheque/P.O./bank draft to the value of £ .....

Please charge my Visa/Mastercard/Amex/

Diners Club/Switch

£ .....

Card No. ....

Expiry Date ..... Switch Issue No. ....

SEND TO: **Everyday Practical Electronics,  
Wimborne Publishing Ltd.,**

**408 Wimborne Road East, Ferndown, Dorset BH22 9ND.**

Tel: 01202 873872. Fax: 01202 874562.

E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

# PRACTICALLY SPEAKING

Robert Penfold looks at the Techniques of Actually Doing It!

THE TOPIC of this month's article could be described as "loose ends". Beginners at electronic project construction are often fazed when they find the construction diagrams for a project have one or more tags, pins or leads unconnected. Surely the project cannot possibly work with one or more of the components only partially connected?

## Spare Capacity

The simple answer to this is that most projects can and do work even though some of the components have these "loose ends". There are two main reasons for some of the tags, etc. not connecting to anything. One is the use of standard encapsulations for some types of component, and integrated circuits (i.c.s) are the most common example of this.

Integrated circuits are available in standard case sizes and styles having from six to 40 or more pins. All the normal types of encapsulation have an even number of pins, but some devices require an odd number of pins. If an operational amplifier (op.amp) only requires seven pins, it will therefore be housed in an 8-pin type with one terminal having no internal connection.

In the past it was quite common for some integrated circuits, but op.amps in particular, to be produced in various eight and fourteen pin versions. Why the 14-pin versions were produced is not too clear, but it meant that these devices had about six or seven pins that did not have internal connections.

This practice has now largely ended, but there are still a few integrated circuits that have far more pins than are actually needed. The number that have one unused pin is much more substantial.

## Pinouts

If you look at pinout diagrams for some integrated circuits you will probably find some of the pins marked "n.c.". These are the ones that are unused, and "n.c." simply stands for no connection. Fig.1 shows the pinout diagram for the 741C op.amp and the many pin compatible types. Pin 8 is marked "n.c.", and is therefore unused.

Occasionally there may be a pin that is designated "IC" (internal connection), "Test", or something of this type. This indicates that there is an internal connection to the pin, but that no external connection is made in normal use. It is provided for use in the manufacturer's final testing procedure.

It is usually quite easy to eliminate unused integrated circuit pins as a source of problems. Checking the circuit diagram should show that the pin or pins in question do not connect to

anything. Either the pins in question will be included on the circuit diagram but there will be no "wires" connected to them, or the pins will simply not be shown at all.

In the unlikely event that there is a definite discrepancy between the circuit diagram and other diagrams in the book or article, the publisher of the material should be able to provide corrections. If there is a strong possibility of an error in a construction diagram, do not simply press on and hope for the best. There is a risk that components could be damaged if you do, and there could be safety issues as well.

## Part-time Components

The second cause of unused connections is components that are not fully utilized. This is quite common with integrated circuits that contain two or more elements, such as logic devices that contain several gate circuits or amplifier packages that contain several op.amps.

If a design requires (say) two CMOS 2-input NOR gates, a quad 2-input NOR gate has to be used because a twin version is not manufactured.

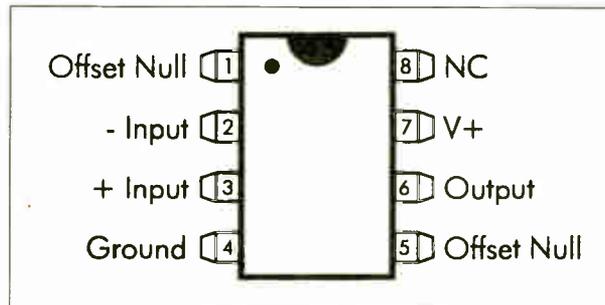


Fig.1. The 741C op.amp pinout details. There is no internal connection to pin 8, and pin 1 and pin 5 are little used in practice.

Depending on the device in question, unused sections may simply be ignored, or unused inputs could be connected to one or other of the supply rails.

However, with most MOS input devices there can be problems if unused inputs are left unconnected. They are vulnerable to damage from static charges and can be operated by stray signals, producing an unnecessary increase in current consumption.

Connecting the inputs to one or other of the supply rails avoids these problems. This still leaves any unused outputs unconnected though. Again, checking the circuit diagram should show whether or not there are any missing connections on the layout diagrams, or simply some unused pins.

Integrated circuits often have one or two pins that are not utilized because they provide functions that are unnecessary in most applications. Returning to the 741C op.amp (Fig.1), pin 1 and

pin 5 provide an offset null facility. This enables better accuracy to be obtained in precision d.c. applications. Although originally designed for applications of this type, op.amps now have a wide range of uses. Consequently, in the vast majority of applications any offset null pins are left unused.

## Transformers

The transformer is another type of component that is often only partially utilized. Whether a project requires a radio frequency (r.f.), audio frequency (a.f.) or mains transformer, designs for the home constructor do not usually have the luxury of a custom component. Instead the designer usually has to do the best he or she can with an "off the shelf" component.

Rationalisation by manufacturers and retailers means that only a limited range of transformers is readily available these days. It is often necessary for the designer to settle for a component that is less than ideal. Where there are three or four connection points on a winding, only two might actually be used. In some cases a complete winding is left unused.

Where an audio or mains transformer with flying leads has one or two spare leads, do not simply leave the leads flapping around inside the case. It is best to cut the leads quite short and then insulate the ends with p.v.c. sleeving or insulation tape. This ensures that there can be no accidental connections to other parts of the circuit. It is a good idea to tape the leads to the case, or chassis rather than just leaving them dangling.

## Rotary Switches

Switches represent another type of component where the designer has to make the best of what is available to the home constructor. This is not usually a problem where the more simple switches are required, but there can sometimes be one or two tags left unconnected.

There can be and often are many unused tags where multi-way rotary switches are involved. I must have used multiway rotary switches hundreds of times over the years, but you could probably count on the fingers of one hand the number of times that all the tags were used. The multiway rotary switches used in most designs for the home constructor are supplied in four types, which are 3-way 4-pole, 4-way 3-pole, 6-way 2-pole, and 12-way 1-pole.

Modern switches of this type invariably have an adjustable end-stop (Fig.2). If a design required (say) a 5-way 2-pole switch, it is actually a 6-way 2-pole switch that would be used, with the end-stop set for 5-way operation.

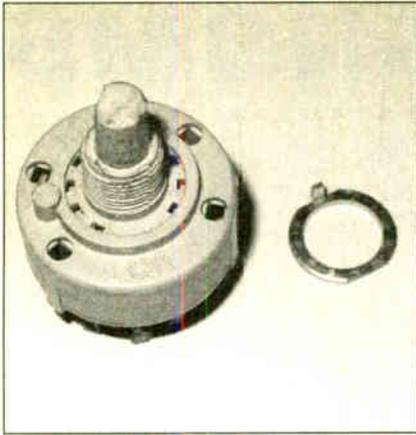


Fig.2. Multiway rotary switches have an end-stop that fits over the mounting bush.

Where a 3-way 2-pole switch is required, the designer would probably opt for a 3-way 4-pole type with two poles left unused. Alternatively, a 6-way 2-pole type set for 3-way operation could be used. Either way, something like half the tags would be left unused.

The pole tags of rotary switches are usually labelled A, B, etc., and the other tags are numbered from 1 to 12. In the case of a 6-way 2-pole switch for example, tag A is used with tags 1 to 6, and tag B is used with tags 7 to 12. This makes it much easier to get these switches connected correctly.

### Relays

It is perhaps worth mentioning relays. A relay is a two-way switch that is operated via an electromagnet. For maximum versatility relays often have two or four sets of changeover contacts.

Many practical applications require a basic on/off action. A changeover switch can be used as an on/off type by using the pole tag and one of the other two. This often results in two tags being used and four or 10 tags being left unused.

### Connectors

The connectors used with computer projects often have a number of unused pins. This is partially due to the use of standard connectors that do not always have the exact number of terminals required, and the compromises this requires. Also, a computer interface may have twenty input and output lines, but many practical applications require something like two inputs and three outputs.

It is not uncommon for about half a dozen connections to be made to a 25-way connector. The other pins are either totally unused or are not required in that particular application.

There are also plenty of examples where all but one or two pins are left unused, and it is these that tend to get inexperienced constructors worried. With only one or two pins unused it looks as if something has been overlooked, but it is likely that everything is actually present and correct.

"Spare" pins are less common when dealing with audio connectors, although

you may occasionally encounter DIN plugs and sockets that have some unused terminals. This stems from the use of 5-way connectors that act as stereo inputs and outputs. Two pins are left unused where only an input or an output is required.

### Jack Connectors

Jack sockets are the more common cause of problems. Mono jack sockets are 2-way connectors, but the 2.5mm and 3.5mm types often have three tags, and many standard types sport four tags! The reason for the extra tag or tags is that the socket incorporates a switch.

Jack connectors are used in a variety of audio applications, but one of their most common uses is with headphones and earphones. The switch contacts are normally closed, but open when a plug is inserted into the socket. The switch is used to automatically switch off the internal loudspeaker when the earphone or headphones are in use. These days most applications do not require any built-in switch, and one or two tags are often left unused.

The correct method of connection for switched versions of standard (6.35mm) and 3.5mm sockets is shown in Fig.3. Switched 2.5mm jack sockets are the same as the 3.5mm type incidentally, but scaled down slightly. There is an extra tag on the standard jack socket because it has two sets of switch contacts. The loudspeaker is totally disconnected when the plug is inserted.

A 3.5mm jack socket has only one built-in switch, and one lead to the loudspeaker is not switched. Of course, disconnecting one lead is sufficient to mute the loudspeaker. If the switching action is not required, the two leads to the loudspeaker are omitted.

Not all jack sockets have the integral switch contacts, so make sure you obtain a socket of the correct type where a design does require automatic switching. The switched sockets shown in Fig.3 are the most common types, but there are some variations. Some 3.5mm sockets are a sort of

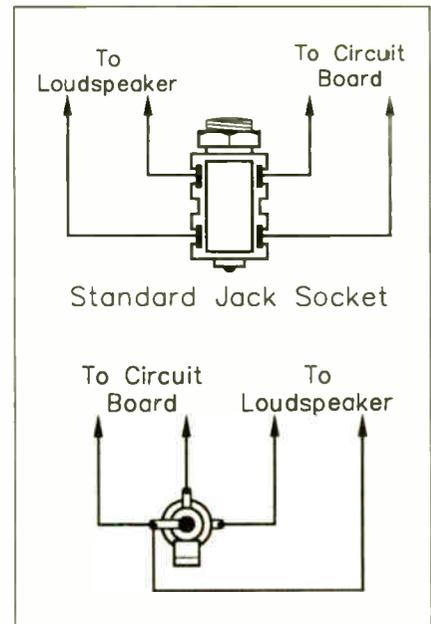


Fig.3. Using jack sockets to provide automatic muting of a loudspeaker.

miniature version of the standard type for example.

Retailers' catalogues sometimes provide diagrams that show the functions of the tags on the more exotic jack sockets. Failing that, the most basic of continuity testers plus some simple checks will soon show which tags connect to the plug, and the connections between tags when the plug is removed.



## DISTANCE LEARNING SHORT COURSES with BTEC CERTIFICATION


Analogue and Digital Electronics, Fibre Optics, Fault Diagnosis, Mechanics, Mathematics and Programmable Logic Controllers

- Suitable for beginners and those wishing to update their knowledge and practical skills
- Courses are very practical and delivered as self contained kits
- No travelling or college attendance
- Learning is at your own pace
- Each course can stand alone or be part of a modular study programme
- Tutor supported and BTEC certified

For information contact:  
NCT Ltd., P.O. Box 11  
Wendover, Bucks HP22 6XA  
Telephone 01296 624270; Fax 01296 625299  
Web: <http://www.nct.ltd.uk>

# ELECTRONICS CD-ROMS


## ELECTRONICS PROJECTS

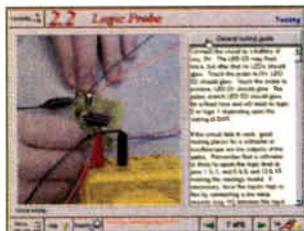

Logic Probe testing

*Electronic Projects* is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included. The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.


## ELECTRONICS CAD PACK

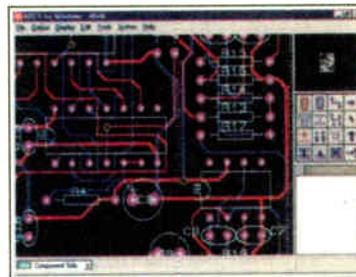

PCB Layout

Electronics CADPACK allows users to design complex circuit schematics, to view circuit animations using a unique SPICE-based simulation tool, and to design printed circuit boards. CADPACK is made up of three separate software modules: **ISIS Lite** which provides full schematic drawing features including full control of drawing appearance, automatic wire routing, and over 6,000 parts. **PROSPICE Lite** (integrated into ISIS Lite) which uses unique animation to show the operation of any circuit with mouse-operated switches, pots, etc. The animation is compiled using a full mixed mode SPICE simulator. **ARES Lite** PCB layout software allows professional quality PCBs to be designed and includes advanced features such as 16-layer boards, SMT components, and even a **fully functional autorouter**.


## ANALOGUE ELECTRONICS

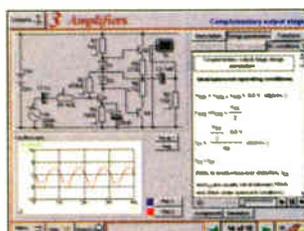

Complimentary output stage

*Analogue Electronics* is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits. Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections). **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections). **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections). **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.


## DIGITAL ELECTRONICS

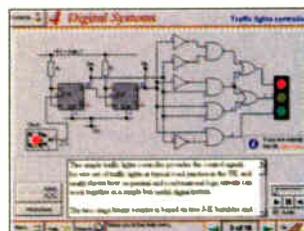

Virtual laboratory – Traffic Lights

*Digital Electronics* builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (opposite), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen. Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units.


## FILTERS

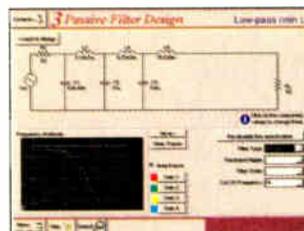

Filter synthesis

*Filters* is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev op.amp filters.

## DIGITAL WORKS 3.0

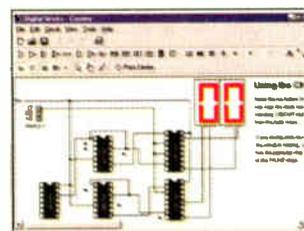

Counter project

*Digital Works Version 3.0* is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability.

- Software for simulating digital logic circuits
- Create your own macros – highly scalable
- Create your own circuits, components, and i.c.s
- Easy-to-use digital interface
- Animation brings circuits to life
- Vast library of logic macros and 74 series i.c.s with data sheets
- Powerful tool for designing and learning

## “C” FOR PICMICRO MICROCONTROLLERS



**C for PICmicro Microcontrollers** is designed for students and professionals who need to learn how to use C to program embedded microcontrollers. This product contains a complete course in C that makes use of a virtual C PICmicro which allows students to see code execution step-by-step. Tutorials, exercises and practical projects are included to allow students to test their C programming capabilities. Also includes a complete Integrated Development Environment, a full C compiler, Arizona Microchip's MPLAB assembler, and software that will program a PIC16F84 via the parallel printer port on your PC. (Can be used with the *PICtutor* hardware – see opposite.) Although the course focuses on the use of the PICmicro series of microcontrollers, this product will provide a relevant background in C programming for any microcontroller.


## PRICES

Prices for each of the CD-ROMs above are:


Hobbyist/Student .....£45 inc VAT  
 Institutional (Schools/HE/FE/Industry).....£99 plus VAT  
 Institutional 10 user (Network Licence) .....£199 plus VAT

(UK and EU customers add VAT at 17.5% to “plus VAT” prices)
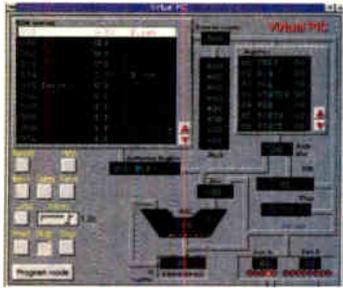
# Interested in programming PIC microcontrollers? Learn with **PICtutor** by John Becker



The Virtual PIC

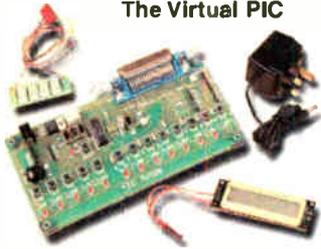

Deluxe PICtutor Hardware

This highly acclaimed CD-ROM, together with the PICtutor experimental and development board, will teach you how to use PIC microcontrollers with special emphasis on the PIC16x84 devices. The board will also act as a development test bed and programmer for future projects as your programming skills develop. This interactive presentation uses the specially developed **Virtual PIC Simulator** to show exactly what is happening as you run, or step through, a program. In this way the CD provides the easiest and best ever introduction to the subject.

Nearly 40 Tutorials cover virtually every aspect of PIC programming in an easy to follow logical sequence.

## HARDWARE

Whilst the CD-ROM can be used on its own, the physical demonstration provided by the **PICtutor Development Kit**, plus the ability to program and test your own PIC16x84s, really reinforces the lessons learned. The hardware will also be an invaluable development and programming tool for future work.

Two levels of PICtutor hardware are available – Standard and Deluxe. The **Standard** unit comes with a battery holder, a reduced number of switches and no displays. This version will allow users to complete 25 of the 39 Tutorials. The **Deluxe** Development Kit is supplied with a plug-top power supply (the **Export** Version has a battery holder), all switches for both PIC ports plus I.c.d. and 4-digit 7-segment I.e.d. displays. It allows users to program and control all functions and both ports of the PIC. All hardware is supplied **fully built and tested** and includes a PIC16F84.

## PICtutor CD-ROM

Hobbyist/Student ..... £45 inc. VAT  
 Institutional (Schools/HE/FE Industry) ... £99 plus VAT  
 Institutional 10 user (Network Licence) .£199 plus VAT

## HARDWARE

Standard PICtutor Development Kit ..... £47 inc. VAT  
 Deluxe PICtutor Development Kit ..... £99 plus VAT  
 Deluxe Export Version ..... £96 plus VAT

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

**NEW VERSION 2**

## ELECTRONIC CIRCUITS & COMPONENTS V2.0



Circuit simulation screen

Provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals**: units & multiples, electricity, electric circuits, alternating circuits. **Passive Components**: resistors, capacitors, inductors, transformers. **Semiconductors**: diodes, transistors,

op.amps, logic gates. **Passive Circuits**, **Active Circuits**, **The Parts Gallery** will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Selections include: **Components**, **Components Quiz**, **Symbols**, **Symbols Quiz**, **Circuit Technology**.

Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.

Hobbyist/Student ..... £45 inc VAT  
 Institutional (Schools/HE/FE/Industry) ..... £99 plus VAT  
 Institutional Site Licence ..... £499 plus VAT

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

## ELECTRONIC COMPONENTS PHOTOS



A high quality selection of over 200 JPG images of electronic components. This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details). Also contains a **FREE** 30-day evaluation of Paint Shop Pro 6 – Paint Shop Pro image editing tips and on-line help included!

Price **£19.95 inc. VAT**

## MODULAR CIRCUIT DESIGN

This CD-ROM contains a range of tried and tested analogue and digital circuit modules, together with the knowledge to use and interface them. Thus allowing anyone with a basic understanding of circuit symbols to design and build their own projects.

Essential information for anyone undertaking GCSE or "A" level electronics or technology and for hobbyists who want to get to grips with project design. Over seventy different Input, Processor and Output modules are illustrated and fully described, together with detailed information on construction, fault finding and components, including circuit symbols, pinouts, power supplies, decoupling etc.

Single User Version **£19.95 inc. VAT**  
 Multiple User Version **£34 plus VAT**

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 95/98/NT/2000/ME, mouse, sound card, web browser.

### CD-ROM ORDER FORM

Please send me:

Electronic Projects  
 Analogue Electronics  
 Digital Electronics  
 Filters  
 Digital Works 3.0  
 Electronics CAD Pack  
 C For PICmicro Microcontrollers  
 PICtutor  
 Electronic Circuits & Components V2.0

PICtutor Development Kit – Standard  
 PICtutor Development Kit – Deluxe

Electronic Components Photos  
 Modular Circuit Design – Single User  
 Modular Circuit Design – Multiple User

Full name: .....  
 Address: .....  
 .....  
 ..... Post code: ..... Tel. No: .....

Signature: .....

I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £ .....  
 Please charge my Visa/Mastercard/Amex/Diners Club/Switch: £ ..... Card expiry date: .....

Card No: ..... Switch Issue No. ....

**Version required:**

Hobbyist/Student  
 Institutional  
 Institutional 10 user  
 Institutional site licence

Deluxe Export

Note: The software on each version is the same (unless stated otherwise above), only the licence for use varies.

Note: The CD-ROM is not included in the Development Kit prices.

## ORDERING

ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world

EU residents outside the UK add £5 for airmail postage per order

Institutional, Multiple User and Deluxe Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU (European Union) country, then add 17½% VAT or provide your official VAT registration number).

Send your order to:  
**Direct Book Service**  
**Wimborne Publishing Ltd**  
**408 Wimborne Road East**  
**Ferndown, Dorset BH22 9ND**


To order by phone ring  
**01202 873872. Fax: 01202 874562**

Goods are normally sent within seven days  
 E-mail: [orders@wimborne.co.uk](mailto:orders@wimborne.co.uk)  
 Online shop:  
[www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

# SURFING THE INTERNET

# NET WORK

## ALAN WINSTANLEY

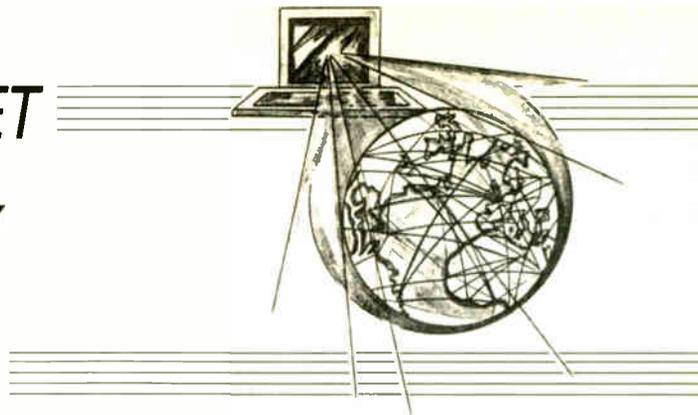

### Windows Shopping

**I**N MY ten years' experience of internet usage, including five years or so of shopping over the internet, I have purchased many items from the USA at prices considerably cheaper than any available in the UK. However, my internet shopping experiences had not been entirely trouble-free: a small order placed with the Exploratorium Online Store in the US resulted in over a dozen inexplicable debits and credits being made on my credit card account; then the goods were delivered twice.

Shipping companies such as DHL and UPS have also gained a new market, as they can pocket a £10 documentation fee merely for collecting a few pounds of import duty from the consignee. The courier UPS in the UK received a major blackmark from the writer, for threatening to sue him for import costs related to an American import which he had already paid, cash on delivery.

After ordering a new PC online last year, Dell Computers UK delivered it three weeks late, missing the year end, which has cost the writer £1,800 (\$2,700) in postponed tax allowances. It would also appear that internet orders placed with Dell UK were re-input by human beings: how else would it become a desktop PC (I ordered a mini tower) fitted with a much cheaper graphics card as well? Only an expert would have noticed that the required video card had not been fitted.

Of course problems like these are not limited to internet orders and generally the internet provides an easy, quick and efficient way of buying, as our own transactions with readers buying from the *EPE* online shop at <http://www.epemag.wimborne.co.uk/shopdoor.htm> proves.

Everything I have bought has been transacted in US dollars or Pounds Sterling. In fact, I have to say that the Euro currency, or any other currency (apart from one transaction for SAustralian 400), has never featured on the internet landscape although I fear the Euro soon might. Nevertheless it is towards mainland Europe that I now look as regards the future of broadband Internet services.

### Satellite Links

For a regular internet user like myself, who has become tired of BT's confusing and constantly changing array of tariffs, who is fed up of squawking modems, who gets nowhere trying to get a cable modem installed (NTL laid a CATV cable in the pavement just yards away years ago, but never switched it on), or for whom DSL will never happen – then help may be at hand towards the end of 2001.

Tiscali International ([www.tiscali.com](http://www.tiscali.com)) is the Italian ISP and telco that now owns the major UK ISP LineOne ([www.lineone.net](http://www.lineone.net)) and France's Liberty Surf. Tiscali's avowed intention is to become one of the top three ISP's in every major European country.

Interestingly, Tiscali is aiming to roll out satellite internet services across Europe and South Africa through their TiscaliSat subsidiary (<http://satellite.tiscali.com>). That's right – install a small satellite dish and you have unlimited usage, always-on bi-directional internet access with no cable worries, no tie-ins to local telephone or cable TV services nor any complicated tariffs – almost anywhere in the country. It may be the ultimate "wireless" internet service for the regular-to-heavy internet user and it will also have a flat-rate monthly fee.

TiscaliSat claims download at speeds up to ten times faster than dial-up services. It is claimed that speeds will often reach 400kbps with targeted peak-time speeds in excess of 150kbps, with current upload speeds ranging between 40kbps and 140kbps. You can register your interest on their web site, and a pan-European service is promised by the end of the year. I am keeping a close watch.

### May the farce be with you

My faithful Nokia 8100 mobile phone had served me well for half a decade but it was recently traded in for a new Nokia 6210. Actually, the phone upgrade was prompted by a recent mishap, when a

high-sided lorry ripped down all my overhead phone lines, leaving me completely "wire-less" for several days. If only I had satellite....

However, the new phone does have infra red. Although IR communications are tediously slow, at least you can communicate in "black and white" by sending plain text emails from a laptop computer. Or you could try sending mail through a WAP phone, which is a hideously slow and cumbersome process.

Wireless Application Protocol promised much but has failed to live up to anyone's expectations: this is the industry's fault to start with, as the service has been hyped to death, not helped by TV adverts that imply that all manner of information is available instantly on tap – what they don't show of course, is the chronic process of logging in and tapping away on a small keypad in order to access the WAP service at all. Then there's the waiting!

My WAP service was to be enabled after three working days (Wednesday), but a week later it was still inoperative. I was told that in order to enable the service, I had to call BT Cellnet myself to arrange it. I did this several times. On the Saturday, they finally provided me with data and fax numbers that I needed to configure the new phone, adding that I would need to speak to Genie ([www.genie.co.uk](http://www.genie.co.uk)), the mobile internet service, to get the WAP service set up.

A few hours later, BT called back to say that actually, I needed to enter some different fax/data numbers instead – I explained that writing them down could be difficult because I was driving down the motorway at a fair rate of knots at that time. They suggested I call them back – which I did, except the number turned out to be that of Syncordia, a marketing call centre that closes at the weekends.

Back to BT Cellnet. A terse BT call centre worker insisted that their call centre never closes ("well that one was," I exclaimed) and that I should be talking to BT Cellnet's main office anyway. But no, to switch on the WAP service they insisted that I speak to Genie again. Genie charges 50p/minute for these calls but their operator, in turn, knew nothing about setting up a mobile phone for WAP, as they only handle PC desktop services at that call centre.

Back to BT Cellnet yet again!, where BT still refused to have anything to do with WAP phones, least of all enabling it on mine. "Call Genie again," said the BT Cellnet agent "and tell them you want something called the 'con-fig-ur-ation' settings for your WAP phone". Oh, right....

Before giving it up as a bad job, the last resort was to speak to Genie yet again (50p/minute remember); actually, an extremely helpful Genie operator explained that BT Cellnet were supposed to be handling all such WAP configuration queries now, or at least that's what they had been told. Nevertheless he looked up my model of phone and went through all the set-up pages. My phone suddenly beeped as we spoke: WAP had finally been enabled. The moment of truth had arrived.

### A Genial Genie

Only, there was a bug in the system, explained the genial man from Genie – the password setup doesn't work properly, so I would have to enter that manually, and then re-enter it to confirm. It was at that point that I had my first taste of typing text into a WAP phone, and I can tell you that the convoluted process almost put me off using a WAP phone for good.

Nevertheless, I did manage to login, create a new account and send one tiny E-mail, a few words that took a good four or five minutes to prepare and send. Somehow I don't think that 100 free minutes a month will go very far: I think I'll stick to my laptop and infra red. Or wait for satellite. You can check out WAP set-up issues for your model of phone at the Genie web site.

You can E-mail me at [alan@epemag.co.uk](mailto:alan@epemag.co.uk) but not by WAP, please!

# FRUSTRATED!

## Looking for ICs TRANSISTORS?

A phone call to us could get a result. We offer an extensive range and with a world-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD  
 ADC AN AM AY BA BC BD BDT BDV BDW BDX BF  
 BFR BFS BFT BFX BFY BLY BLX BS BR BRX BRY BS  
 BSS BSV BSW BSX BT BTA BTB BW BU BUK BUT BUY  
 BUW BUX BUY BUZ CA CD CX CXA DAC DG DM DS  
 DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA  
 KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB  
 MC MDAJ MJE MJF MM MN MPS MPSA MPSP MPSP  
 MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB  
 SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD  
 STRM STRS SVI T TA TAA TAG TBA TC TCA TDA TDB  
 TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA  
 UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN  
 ZTS + many others

We can also offer equivalents (at customers' risk)

We also stock a full range of other electronic components  
 Mail, phone, Fax Credit Card orders and callers welcome



Connect


## Cricklewood Electronics Ltd

40-42 Cricklewood Broadway London NW2 3ET  
 Tel: 020 8452 0161 Fax: 020 8208 1441
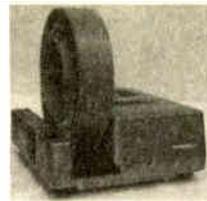
## Watch Slides on TV.

Make videos of your slides. Digitise your slides (using a video capture card)

"Liesgang diatv" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. More details see [www.diatv.co.uk](http://www.diatv.co.uk).  
 £91.91 + VAT = £108.00



Board cameras all with 512 x 582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10V and 12V DC 150mA.  
 47MIR size 60 x 36 x 27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye) £37.00 + VAT = £43.48  
 30MP size 32 x 32 x 14mm spy camera with a fixed focus pin hole lens for hid-ning behind a very small hole £35.00 + VAT = £41.13  
 40MC size 39 x 38 x 27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses £32.00 + VAT = £37.60  
 Economy C mount lenses all fixed focus & fixed iris  
 VSL1220F 12mm F1.6 12 x 15 degrees viewing angle £15.97 + VAT £18.76  
 VSL4022F 4mm F1.22 63 x 47 degrees viewing angle £17.65 + VAT £20.74  
 VSL6022F 6mm F1.22 42 x 32 degrees viewing angle £19.05 + VAT £22.38  
 VSL8020F 8mm F1.22 32 x 24 degrees viewing angle £19.90 + VAT £23.38

## Better quality C Mount lenses

VSL1614F 16mm F1.6 30 x 24 degrees viewing angle £26.43 + VAT £31.06  
 VWL813M 8mm F1.3 with iris 56 x 42 degrees viewing angle £77.45 + VAT = £91.00  
 1206 surface mount resistors E12 values 10 ohm to 1M ohm  
 100 of 1 value £1.00 + VAT 1000 of 1 value £5.00 + VAT

866 battery pack originally intended to be used with an orbitel mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily  
 £7.46 + VAT = £8.77



Please add £1.66 + vat = £1.95 postage & packing per order

## JPG Electronics

Shaws Row, Old Road, Chesterfield, S40 2RB.

Tel 01246 211202 Fax 01246 550959

Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

## VARIABLE VOLTAGE TRANSFORMERS

INPUT 220V/240V AC 50/60Hz OUTPUT 0V-260V  
 PANEL MOUNTING

	Price	P&P
0.5KVA 2.5 amp max	£33.00	£8.00 (£45.84 inc VAT)
1KVA 5 amp max	£45.25	£7.00 (£51.39 inc VAT)

### SHROUDED

0.5KVA 2.5 amp max	£34.00	£8.00 (£47.00 inc VAT)
1KVA 5 amp max	£46.25	£7.00 (£52.57 inc VAT)
2KVA 10 amp max	£85.00	£8.50 (£93.36 inc VAT)
3KVA 15 amp max	£86.50	£8.50 (£111.63 inc VAT)
5KVA 25 amp max	£150.00 (+ Carriage & VAT)	

Buy direct from the Importers. Cheapest prices in the country

### 500VA ISOLATION TRANSFORMER

Input lead 240V AC. Output via 3-pin 13A socket. 240V AC continuously rated. mounted in fibreglass case with handle. Internally fused. Price £35.00 carriage paid + VAT (£41.13)

### TOROIDAL L.T. TRANSFORMER

Primary 0-240V AC. Secondary 0-30V + 0-30V 600VA. Flaming bolt supplied. Price £25.00 carriage paid + VAT (£29.38)

### COMPREHENSIVE RANGE OF TRANSFORMERS- LIT- ISOLATION & AUTO

110V-240V Auto transfer either cased with American socket and mains lead or open frame type. Available for immediate delivery

### ULTRA VIOLET BLACK LIGHT BLUE FLUORESCENT TUBES

4ft. 40 watt £14.00 (callers only)	(£18.45 inc VAT)
2ft 20 watt £9.00 (callers only)	(£10.58 inc VAT)
12in 8 watt £4.80 + 75p p&p	(£5.52 inc VAT)
9in 6 watt £3.96 + 50p p&p	(£5.24 inc VAT)
6in 4 watt £3.96 + 50p p&p	(£5.24 inc VAT)

### 230V AC BALLAST KIT

For either 6in, 9in or 12in tubes £8.05+£1.40 p&p (£9.75 inc VAT)  
 The above Tubes are 3500/4000 angst. (350-400nm) ideal for detecting security markings, effects lighting & Chemical applications.  
 Other Wavelengths of UV TUBE available for Germicidal & Photo Sensitive applications. Please telephone your enquiries.

### 400 WATT BLACK LIGHT BLUE UV LAMP

GES Mercury Vapour lamp suitable for use with a 400W PF. Ballast. Only £39.95 incl. p&p & VAT



### 5 KVA ISOLATION TRANSFORMER

As New. Ex-Equipment, fully shrouded, Line Noise Suppression, Ultra Isolation Transformer with terminal covers and knock-out cable entries. Primary 120V/240V, Secondary 120V/240V, 50/60Hz, 0.005pF Capacitance. Size, L 37cm x W 19cm x H 16cm, Weight 42 kilos. Price £120 + VAT. Ex-warehouse. Carriage on request.

### 24V DC SIEMENS CONTACTOR

Type 3TH9022-0B 2 x 1NO and 2 x NC 230V AC 10A. Contacts: Screw or Din Rail fixing. Size H 120mm x W 45mm x D 75mm. Brand New Price £7.63 inc. p&p and VAT.

### 240V AC WESTOOL SOLENOIDS

Model TT2 Max. stroke 18mm, 5lb. pull. Base mounting. Rating 1. Model TT6 Max. stroke 25mm, 15lb. pull. Base mounting. Rating 1. Series 400 Max. stroke 26mm, 15lb. pull. Front mounting. Rating 2. Prices inc. p&p & VAT: TT2 £5.88, TT6 £8.81, Series 400 £8.84.

### AXIAL COOLING FAN

230V AC 120mm square x 38mm 3 blade 10 watt Low Noise fan. Price £7.29 incl. p&p and VAT  
 Other voltages and sizes available from stock. Please telephone your enquiries.

### INSTRUMENT CASE

Brand new. Manufactured by Imhof. L 31cm x H 18cm x 19cm Deep. Removable front and rear panel for easy assembly of your components. Grey textured finish, complete with case feet. Price £16.45 incl. p&p and VAT. 2 off £28.20 inclusive.

### DIECAST ALUMINIUM BOX

with internal PCB guides. Internal size 265mm x 165mm x 50mm deep. Price £9.93 incl. p&p & VAT. 2 off £17.80 incl.

### 230V AC SYNCHRONOUS GEARED MOTORS

Brand new Ovoid Gearbox Crouzet type motors. EI 65mm x W 55mm x D 35mm, 4mm dia. shaft x 10mm long. 6 RPM anti cw. £9.99 incl. p&p & VAT.  
 20 RPM anti cw. Depth 40mm. £11.16 incl. p&p & VAT.

### 16 RPM REVERSIBLE Crouzet 220V/230V

50Hz geared motor with ovoid geared box. 4mm dia. shaft. New manuf. surplus. Sold complete with reversing capacitor, cord, connecting block and circ. Overall size: h 68mm x w 52mm x 43mm deep  
 PRICE incl. P&P & VAT £9.99

### EPROM ERASURE KIT

Build your own EPROM ERASURE KIT for a fraction of the price of a made-up unit. Kit of parts less case includes: 12in. 8watt 2537, Angst Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £15.00+£2.00 p&p. (£19.98 inc. VAT)

### WASHING MACHINE WATER PUMP

Brand new 240V AC fan cooled. Can be used for a variety of purposes. Inlet 1 1/2 in., outlet 1 in. dia. Price includes p&p & VAT. £11.20 each or 2 for £20.50 inclusive.

## ELECTRONICS SURPLUS CLEARANCE SALE

### SCOOP PURCHASE:

### FLUKE HAND HELD DIGITAL MULTIMETER, MODEL 8024B

Cancelled export order 750V AC/DC 2 amp AC/DC Resistance 20Megohm plus Siemens range. Also measures temperature -20°C to +1265°C. Temp. probe not included. Calibrated for K-type thermocouple. Peak hold facility. Supplied brand new and boxed but with original purchasing organisation's small identifying mark on case. Test leads and handbook included.

Offered at a fraction of original price: £47.50, p&p £6.50

A DIGITAL HANDHELD LCR METER. Measuring inductance, capacitance and resistance. 3.5 digit, 1999 count, l.c.d. display, inductance range 2MH to 20H, capacitance range 2000pF to 200uF, resistance range 200Ω to 20 megohms. Brand new and boxed with test alligator clip leads and user manual. £44 including postage.

MAGNETIC CREDIT CARD READER. Keyboard and laptop display system. Point of sale unit. Cost over £150, our price £12.50, carriage £6.50. Two units for £35 including carriage. To be used for experimental purposes only. No info.



OC42 VINTAGE TRANSISTORS. Individually wrapped, military spec. 10 for £2.50 including post.

### BOOKS:

ELECTRIC UFOs by Albert Budden. A chilling exposure of electromagnetic pollution and its effects on the environment and health including fireballs, UFOs and abnormal states. Many case studies and field investigations and experiments. 286 pages, photos. £7.50, p&p £2.50.

THE GUINNESS BOOK OF ESPIONAGE by Lloyd Mark. This unique book shines a revealing light on the furtive clandestine business of the art of spying and traces the technical development of spying with particular emphasis on WW2. Includes photos and details of spy sets. Enigma equipment and clandestine devices. 256 pages. £12.50, p&p £3.75.

THE ELECTRONICS SURPLUS TRADER - This is a listing of new first class components, books and electronic items at below trade prices. Includes manufacturers' surplus and overstocks. Also obsolete semiconductors, valves and high voltage caps and components. Send two first class stamps for large catalogue.

## (Dept E) CHEVET SUPPLIES LTD

157 Dickson Road, BLACKPOOL FY1 2EU

Tel: (01253) 751858. Fax: (01253) 302979

E-mail: [chevet@globalnet.co.uk](mailto:chevet@globalnet.co.uk) Telephone Orders Accepted

Callers welcome Tues, Thurs, Fri and Sat.



## SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB

Tel: 020 8995 1560 FAX: 020 8995 0549




Ample Parking Space



# SYNCHRONOUS CLOCK DRIVER

ANDY FLIND

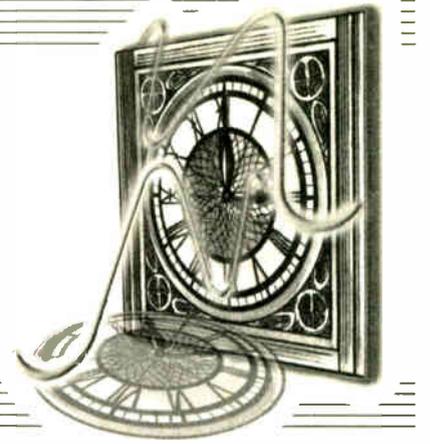

*By popular request – a dual-frequency, 50Hz/60Hz converter for mains operated synchronous clocks.*

**T**HIS project took shape following a request for advice from UK reader Chris Betts with a rather attractive American synchronous clock, which naturally enough he wanted to see in operation.

Many readers will know that these clocks rely upon accurate frequency of the a.c. mains supply for their timekeeping, and that the supply across the pond is 60Hz, whereas ours here in Britain is 50Hz. This means that even if the voltage were to be transformed down to the US standard of 115 volts, the clock would still lose ten minutes per hour in the UK. The fact that this would be a very accurate ten minutes is not really much compensation!

A reply of a fairly general nature was given in *Readout* (April '01), to the effect that the solution would be to construct a sinewave source of suitable frequency and power and transform it up to the required voltage. Whilst basically correct, this is not very helpful to someone with insufficient experience to design such a circuit.

## MEETING TIME

As a fellow clock enthusiast, the present author asked to be put in touch with the reader and a meeting, complete with the clock, was duly arranged. The possibility of a constructional feature for *EPE* wasn't overlooked of course.

The clock was purchased through an internet auction so there must be others like it which need a suitable driver. Some of our British synchronous clocks are becoming collectible nowadays too, and it is likely that some of these will have found their way to America.

A circuit designed to supply 60Hz here could easily be modified to provide 50Hz over there, where *EPE* is well known through the internet. A further application for a 50Hz circuit can be found in the operation of public clocks from an uninterruptible battery-backed supply.

Most modern public clocks are simply convex dials that can be fixed to an

external surface, with space behind the centre for a robust synchronous movement which operates the hands. If the mains supply fails for a few minutes it's often necessary to call the expert with a ladder!

Because of this, it is possible to purchase commercially produced "synchronisers" which work by monitoring the total mains failure time. When this exceeds around thirty seconds the device stops the clock for exactly eleven hours, fifty nine minutes and thirty seconds before starting it again!

This is hardly an ideal solution, especially when it is known that the price of such equipment is typically several hundred pounds.

## MYSTERY CLOCK

The clock in this project is a Jefferson "mystery" clock, so called because it is not immediately obvious how it works. As can be seen in the photograph, it has a gold lacquered base to house the motor and a gold metal outer dial surround with the numerals. This holds a circular glass panel, to the centre of which the hands are attached.

There is no apparent mechanical connection to the hands, so the "mystery" is how power from the motor is transmitted to them. Readers can ponder this question for the present (answer at the end of the article!) It's certainly a good looking clock so it's owner's desire to see it working is easy to understand.

## PIC THE FREQUENCY

Moving to the design, a PIC microcontroller was chosen as the basis for the design since it already has a robust crystal oscillator circuit and can be programmed to divide this by almost any factor of one's choice.

Considering this for a moment, it should be apparent that to generate an output of a given frequency, the PIC must perform the minimum action of switching an output on for half a cycle, then off for half a cycle, so the period of half a cycle of the desired output must be exactly divisible by an integer number of periods of the PIC instruction cycle, remembering of course that the PIC divides its crystal frequency by four to get the instruction cycle frequency.

Clear as mud? Well, try dividing the crystal frequency by eight times the desired output frequency. If there's a fraction in the answer that frequency isn't available. This explains the choice of a 3-6864MHz crystal for this project, as these are readily available and their



frequency can be divided easily to obtain 60Hz.

Experiments began with the synthesis of a fairly good sinewave with the PIC and driving the output transformer – a mains type used “backwards” – with a power amplifier i.c. intended for in-car audio power-boosting applications.

This worked but the use of linear power circuitry resulted in rather wasteful heat generation, mostly from the power amplifier stage. It also led to a fairly complex circuit so a large case with external heatsinking would have been required.

## WAVEFORM UNIMPORTANT

When the clock was tested however, it was found that so long as the frequency was correct and sufficient voltage was available, the waveform was unimportant. This led rapidly to a circuit using switching outputs, which is much simpler, generates practically no heat and is consequently physically smaller and far more efficient. The principle of this is shown in Fig.1.

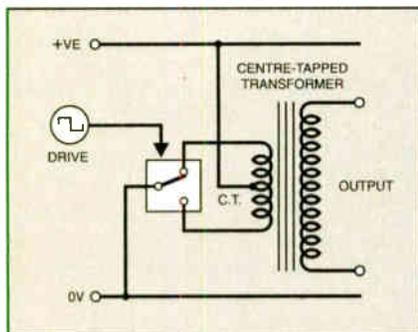


Fig.1. Switch-mode voltage conversion.

A centre-tapped transformer has the tap connected to the positive supply. The two ends of the winding are connected alternately to ground at the required output frequency by a switch, effectively creating an a.c. drive. In practice, power MOSFET devices replace the switch and are driven with pulses from the PIC.

Most synchronous clocks can operate from much less than their rated voltage. In the present case, the 115V clock motor started reliably from 70V, so 100V was considered perfectly adequate. Lower voltage means lower power consumption and less heat generation within the clock motor, which should reduce drying out of the lubricants and therefore less wear and tear.

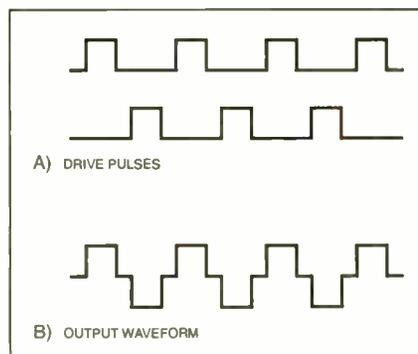


Fig.2. Combining two pulses to create a variable output waveform.

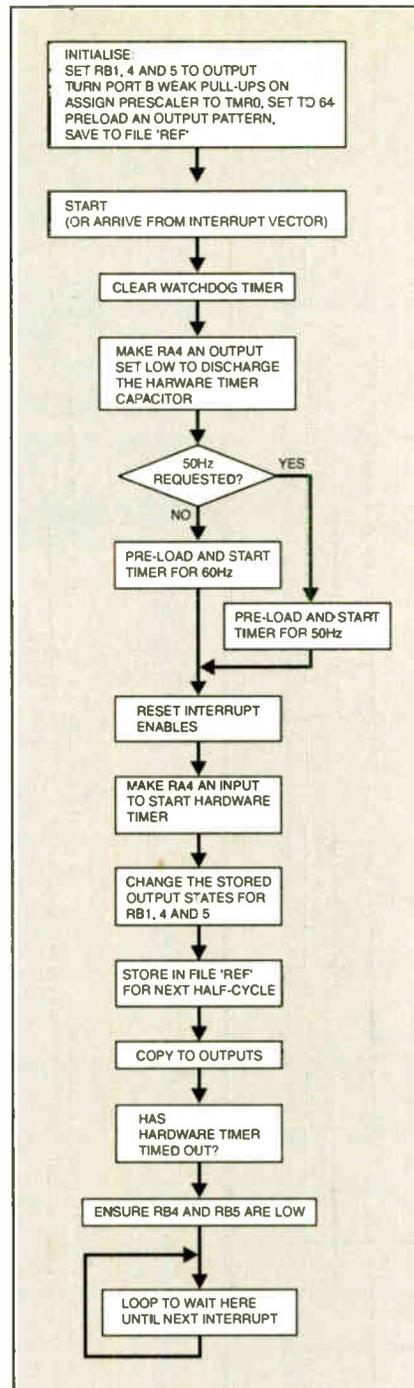


Fig.3. Flow chart for the PIC-based control program.

The output voltage of the switching circuit may be easily controlled by adjusting the width of the output pulses to the MOSFETs, keeping each of them “on” for only part of a half cycle, as shown in Fig.2. This can be made user-adjustable with a preset control.

## FLOWCHART

The operation of the PIC software is shown in the flowchart of Fig.3. This has been arranged to provide either 50Hz or 60Hz, the former being obtainable by shorting a couple of adjacent points on the printed circuit board (p.c.b.).

The interrupt facility of the internal timer is primarily used to control frequency, though readers examining the software will find a couple of small timing loops and “NOPs” used to fine-tune to the exact number of cycles required.

The usual initialisation is carried out, setting RB1, RB4 and RB5 as outputs, turning on the internal Port B pull-up resistors (for the pins used as inputs) and assigning a prescaler set to a factor of 64 to the timer.

A register named REF is used to hold the current states of the three outputs and is pre-loaded at this stage. Program flow then reaches the point to which it will return following each interrupt. The watchdog timer is enabled in this design, so first this is cleared (*nice to see WDT being used in a project! Ed*).

## HARDWARE TIMING

Next we come to the hardware timer used to control the output pulse width. This consists of a small-value capacitor connected to RA4, with a preset resistance to charge it from the positive supply. RA4 is made an output and set low to discharge the capacitor, then it is made an input and monitors the capacitor voltage until it deems this to be high for a period adjustable with the preset.

As an input, RA4 has Schmitt characteristics so it is particularly suitable for this task. With RA4 having been put into the discharge state, RB3 is checked to see if it is low to decide whether the program is going to proceed with timing for 60Hz or branch to that for 50Hz.

In each case some fine tuning delays are executed and then the timer, TMR0, is pre-loaded with the necessary factor for the appropriate interrupt time. The interrupt enable bits are then reset, and RA4 is changed back to an input since by now the capacitor should be sufficiently discharged. The Timer Interrupts panel later details how precise software timing is achieved.


The XOR instruction is used to change the state of the three output bits in register REF, the new values are stored and applied to the outputs. Then the program waits for the hardware timer to complete, ensures both the MOSFET drives are off, and waits in a loop for the next interrupt before repeating these actions. If the hardware timer never times out it won't matter since the output drives will be switched by the next run through this procedure anyway, giving full alternate half cycles of drive.

## CIRCUIT DIAGRAM

Moving to the full circuit of Fig.4, the current required by this circuit can be up to three or four hundred milliamps so the supply section has to be capable of this, although in most cases the supply current will be closer to 250mA. Transformer T1 is therefore a dual 6VA type, with two 0-9V secondaries capable of over 500mA.

This is slightly “over the top”, but more copper and iron in the transformers was found to improve efficiency, especially on the output side. The type used is compact, p.c.b. mounting and inexpensive, so is well suited to this design.

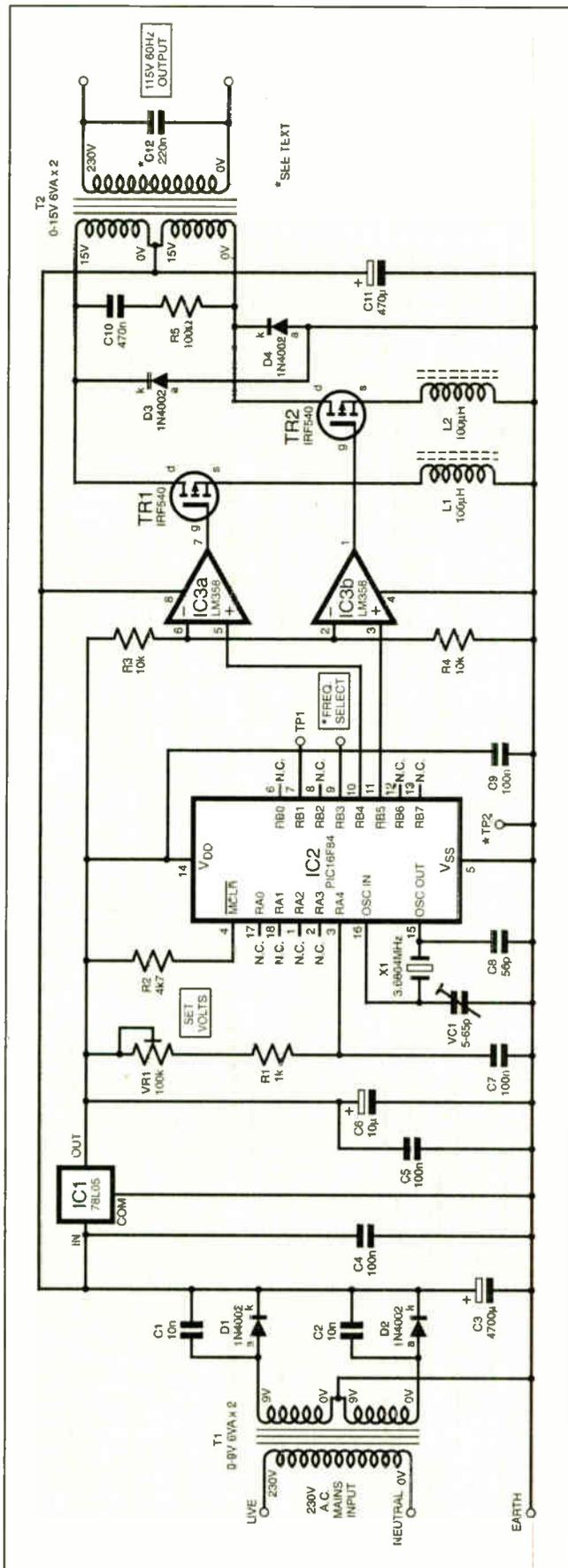The classic two-diode full-wave rectifier circuit is used, with diodes D1 and D2 and reservoir capacitor C3 developing around 12V d.c. A lot of care went into minimising radio frequency (r.f.) emission from this circuit. It is likely to be operated continuously so interference caused by it could be particularly troublesome.



Eventually the "noises" were suppressed to the point where a loud buzz still detectable by a radio at close range proved to be coming from this rectifier stage. The reason for this is that silicon diodes have a small forward voltage drop, of typically about 0.6V, leading to kinks in the output around the zero-crossing points, as shown in exaggerated form in Fig.5.

Small capacitors are sometimes used to suppress this noise so the feature was included in this circuit with C1 and C2, which cured the problem completely.

A standard 78L05 +5V 100mA voltage regulator, IC1, is used to provide power for the PIC, IC2.

The 3.6864MHz crystal, X1, has a 5-65pF trimmer on the input side, VC1, for


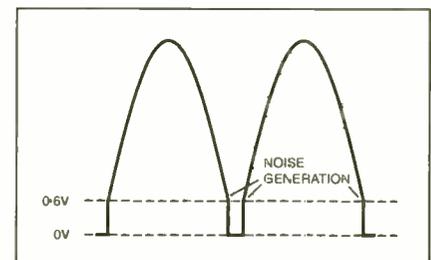


Fig.4 (left). Complete circuit diagram for the Synchronous Clock Driver.

Fig.5 (right). Noise generation across a rectifier diode.

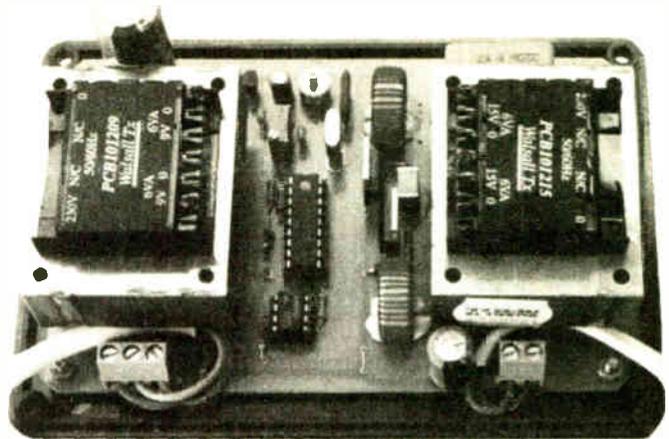

## COMPONENTS

Approx. Cost  
Guidance Only **£32**  
excluding case.

### Resistors

R1	1k
R2	4k7
R3, R4	10k (2 off)
R5	100Ω

All 0-6W 1% metal film.

### Potentiometers

VR1	100k multiturn cermet preset, vertical
-----	--

### Capacitors

C1, C2	10n ceramic, resin-dipped (2 off)
C3	4700μ radial elect. 25V
C4, C5,	100n ceramic,
C7, C9	resin-dipped (4 off)
C6	10μ radial elect. 25V
C8	56p silver-mica
C10	470n polyester, 100V
C11	470μ radial elect. 25V
C12	220n X2 suppression type, 275V a.c.
VC1	5p-65p trimmer

### Semiconductors

D1 to D4	1N4002 rectifier diode (4 off)
TR1, TR2	IRF540 n-channel MOSFET (2 off)
IC1	78L05 +5V 100mA voltage regulator
IC2	PIC16F84 microcontroller, preprogrammed (see text)
IC3	LM358 dual op.amp

### Miscellaneous

L1, L2	100μH 2-6A toroidal inductor (2 off)
T1	mains transformer, p.c.b. mounting, with dual 9V, 6VA per winding, secondaries
T2	mains transformer, p.c.b. mounting, with dual 15V, 6VA per winding, secondaries (see text)
X1	3.6864MHz crystal (see text)

Printed circuit board, available from the EPE PCB Service, code 316; plastic size case, 150mm x 100mm x 60mm; 8-pin d.i.l. socket; 18-pin d.i.l. socket; p.c.b. mounting terminal block 2-way, 5.08mm pitch; p.c.b. mounting terminal block 3-way, 5.08mm pitch; mains connectors and cable to suit; connecting wire; solder etc.

See  
**SHOP**  
**TALK**  
page

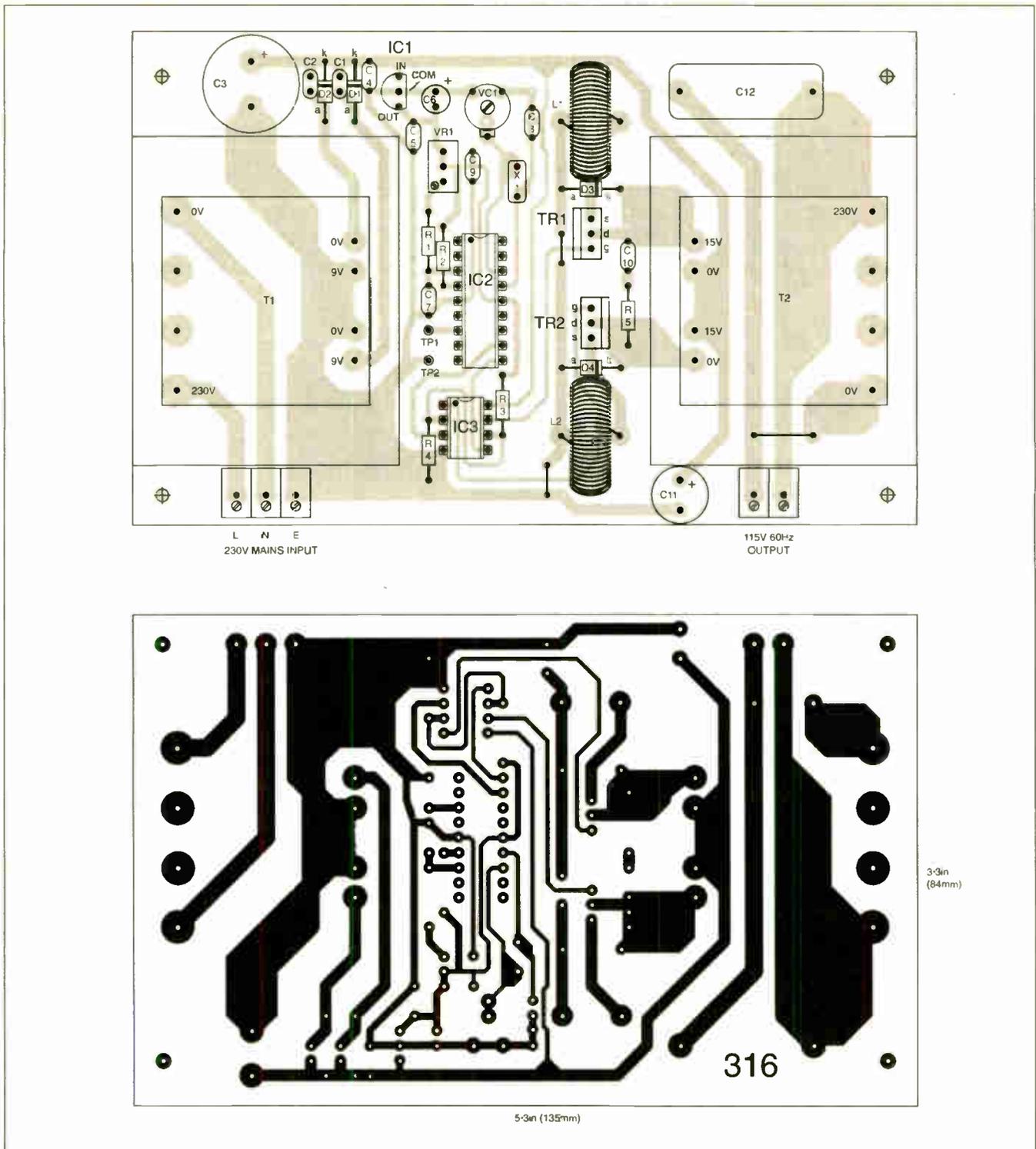


Fig.6. Printed circuit board component layout and full size copper foil master track pattern for the Synchronous Clock Driver.

If a different type is used some adjustment of the values of these capacitors may be needed.

The adjustable hardware timer referred to above is implemented with capacitor C7 plus resistor R1 and preset potentiometer VR1 connected to RA4, pin 3 of IC2.

The "frequency select" pin was chosen as RB3, pin 9, simply because in the physical layout it is adjacent to a 0V track to which it may conveniently be connected if 50Hz is required.

### SQUARE WAVE CONVERSION

RB1, pin 7, provides a square wave output to test point TP1 for use with a frequency meter, if one is available, for use during setting up.

RB4 and RB5, pins 10 and 11, are the outputs to drive the two power MOSFETs TR1 and TR2, though they do so through the two op.amps of IC3, an LM358 dual type. Power MOSFETs often require rather more than five volts to ensure full turn-on, so these two devices, used simply as comparators, provide drive voltage close to the main positive supply instead of the five volts available from IC2.

The two chokes, L1 and L2, reduce the rate of rise of current as TR1 and TR2 switch on, which results in a large drop in interference radiated by the circuit. The "snubber" network of R5 and C10 also contributes to interference control.

Transformer T2 is a 2 x 0-15V 6VA type, connected as a centre-tapped winding and used "backwards". This was found to

give comfortably in excess of 115 volts if required. For 230V output a 9V-0-9V transformer may be suitable, more about this later.

Finally, capacitor C12 "rounds" the corners of the output waveform just a little, which was found to be necessary to prevent a slight "buzzing" from the clock motor. Its value of 220nF is a compromise since it increases current consumption slightly. As little as was necessary to prevent the buzz was applied. Due to the high a.c. voltage at this point this capacitor *must* be a mains suppression type.

### SAFETY WARNING

Before commencing description of construction and testing it must be pointed out that this circuit involves hazardous

voltages at both input and output. Constructors should therefore be experienced enough to avoid harmful contact with these by taking appropriate precautions whilst testing and setting up the circuit. If in doubt consult a suitably experienced person.

The "live" bits are confined to small areas of track around the two transformers and the terminal blocks which should be covered with insulation material. When properly connected to the supply all the low-voltage circuitry will be earthed and safe to handle or connect with test equipment.

## CONSTRUCTION

Printed circuit board layout details are shown in Fig.6. This board is available from the *EPE PCB Service*, code 316.

Construction can commence with the fitting of the three links and the two pins for testing, followed by the resistors, diodes and small capacitors. Next two d.i.l. (dual-in-line) sockets, essential for IC2 and recommended for IC3, should be fitted, followed by VR1, VC1 and the remaining passive components, except capacitors C3, C11 and C12 for the moment.

The 5V regulator IC1, crystal X1, two chokes L1 and L2 and transformers T1 and T2 can be fitted next. The chokes used in the prototype were toroidal types with no support save for their leads. This seemed insufficient so each was provided with a blob of silicone sealant, the sort of stuff used around the edges of baths and showers, to help hold it in place. The leads were pulled through and bent over to hold them in place for soldering. This worked well and is recommended to constructors of this design.

## BENCH TESTING

It is best to test this circuit in stages with a bench power supply, ideally with a current limit, since this is always preferable to simply turning on a transformer capable of supplying over half an ampere and hoping for the best!

Hopefully, such a supply will be available, which should be set for 12V and connected with 0V to the Earth connection and +12V to a lead temporarily connected to the cathode (k) side of diodes D1 and D2. The current drawn at this stage should be about 4mA. The presence of the regulated 5V supply can be checked at pin 14 of the socket for the PIC, IC2.

Variable capacitor VC1 should now be set to about half-travel and a programmed PIC inserted into the socket. The average d.c. voltage at test point TP1 should be about 2.5V, indicating that the 60Hz squarewave output is present. This can be checked with a 'scope or frequency meter if available.

Following this, preset VR1 should be wound completely clockwise and the average d.c. voltage at pins 3 and 5 of IC3's socket checked. With VR1 fully clockwise they should be receiving square wave cycles of 60Hz, so will measure about 2.5V, as with TP1.

Turning VR1 in an anti-clockwise direction, should have the effect of lowering the measured voltages as the pulse widths are narrowed. Leave them set for about 1V average.

## TIMER INTERRUPTS

If a 3-6864MHz crystal is employed, the frequency of the PIC's internal clock will be  $3-6864 \times 10^6 / 4$  or 921600Hz. The period therefore is  $1/921600$ secs.

A square wave output state is changed twice per cycle when generating a frequency, therefore if interrupts are used these must be at 100Hz for a 50Hz output and 120Hz for a 60Hz output. These, therefore, correspond to  $921600/100 = 9216$  and  $921600/120 = 7680$  clock cycles respectively.

For 50Hz, the interrupt period must be 9216 PIC instruction cycles.

For 60Hz, the interrupt period must be 7680 PIC instruction cycles.

Since TMR0 is "pre-loaded" each time, and there are other functions involved such as coming out of the interrupt vector, there will be overheads to allow for and in most cases it will prove impossible to obtain the exact period required from TMR0. Consequently there will be a short timing loop and perhaps also some "NOPs" for fine tuning of each frequency.

In the program, taking 50Hz, the instruction cycle count is as follows:

The GOTO from interrupt vector to start of program	2
Clear the watchdog timer	1
Start the output pulse timer capacitor discharging	4
Test RB3 to see if 50Hz requested	1
GOTO the 50Hz TMR0 routine	2
Load a fine-tuning loop (single) with value of 15	2
Execute the loop	46
NOPs	2
Pre-load TMR0	2
Time for TMR0 to begin running	2
Total overhead so far:	64

The TMR0 prescaler is set for 64

TMR0 is pre-loaded with 113 and counts up, so the total clock cycles taken before interrupt occurs will be  $(256 - 113) \times 64 = 9152$

**The total number of instruction cycles taken is therefore  $9152 + 64 = 9216$**

The equivalent for 60Hz is as follows:

The GOTO from interrupt vector to start of program	2
Clear the watchdog timer	1
Start the output pulse timer capacitor discharging	4
Test RB3 to see if 50Hz requested	2 (it isn't, so this becomes a 2-cycle instruction)
Load a fine tuning loop (single) with value of 16	2
Execute the loop	49
NOPs	0 (None used in this routine)
Pre-load TMR0	2
Time for TMR0 to begin running	2
Total overhead so far:	64 (same as above, but this is a coincidence!)

The TMR0 prescaler is set for 64

TMR0 is pre-loaded with 137 and counts up, so the total clock cycles taken before interrupt occurs will be  $(256 - 137) \times 64 = 7616$

**The total number of instruction cycles taken is therefore  $7616 + 64 = 7680$**

The interrupts, loaded with these factors and used with the appropriate crystal, will enable the precise generation of 50Hz and 60Hz output frequencies by the PIC program, while leaving the program free to perform other functions such as updating the output states and timing the output drive pulses for most of its operating time.

## OUTPUT TESTING

Next op.amp IC3 can be fitted, taking the supply current to around 6mA. The outputs from IC3, pins 3 and 5, should measure around 2V average; if so, they are operating correctly.

The two power MOSFETs TR1 and TR2 and the two large electrolytics C3 and C11 should be fitted now, observing correct orientation.

An a.c. voltmeter with a range of 200V or more should be connected to the output and the circuit powered again, still from a bench supply if possible. With VR1 left set as above, the prototype's output voltage measured about 78V, though the measured value may depend on how individual meters interpret the output waveform.

The supply current, as yet with no output load, measured about 30mA. Fitting

capacitor C12 raised the measured output to about 95V and the supply current to around 50mA. Finally, the clock can be connected and the output voltage set to its final value.

As mentioned earlier, the clock used with the prototype started reliably at about 70V so the circuit was set to provide 100V. The voltage of this project is quite heavily dependent on the load so the final voltage must be adjusted with it connected. The Jefferson clock had a coil resistance of about  $4k\Omega$  and was rated at 2.5W. With the voltage adjusted to a measured 100V a.c., the supply drain was about 270mA.

With the circuit connected to the mains, and obviously taking necessary precautions to prevent shock, the output voltage was re-checked and adjusted as necessary. A frequency meter was connected to TP1 to set the output to exactly 60Hz.

## ENCLOSING TIME

The size of case shown in the components list fits almost perfectly, just a tiny bevel being needed at the corners of the p.c.b. for clearance. Four 3mm nylon screws were used to secure the board, using 4mm nuts as spacers. Other enclosures could be used, of course, according to the preference of the constructor. *If a metal case is used it must be earthed.*

The 9V transformer runs slightly warm – transformers seem to be designed to run warm nowadays. Otherwise there is no heat dissipation from the circuit at all so no heatsinking or ventilation holes are required.

## CUSTOMISING

Almost finally, here are some details of modifications and customising:

If it is required to operate a 50Hz 230V clock, pin 9 (bottom left) of IC2 should be connected to the earth point to the left of it, notated as TP2. This is easily done on the copper track side of the board. The software will recognise this connection and switch to 50Hz operation.

The input and output transformer voltage ratios may also need changing for 230V output and/or 115V input operation.

Incidentally, if the crystal trimmer has been adjusted to the correct value for one frequency it will automatically be correct at the other so it is possible to use a switch here.

During design work, testing was carried out with two 50Hz clock motors, both of which had coil resistances of about 4k $\Omega$ . One was a large, old movement of the type which has to be manually started with a "flicking" mechanism. This was actually removed from a tower clock by a



clockmaker who became tired of call-outs to restart it every time the mains failed!

The other came from a cooker timer and appeared to be of the shaded-pole type rather than the more familiar "toothed wheel" construction commonly found in clock motors.

These two very different motors both ran happily with this circuit and required much less than 200V to operate. A 9V-0-9V transformer for T2 just about managed 200V output. A 6V-0-6V could easily exceed 230V but was less efficient, suggesting that in most cases a 9V type would be the better choice.

Where the specified type of transformer is not available, other types of suitable rating can be used, using wires to connect them to the p.c.b. if necessary.

## BATTERY POWER

If a battery-backed supply is to be used, diodes D1, D2 and capacitors C1 and C2 should be omitted, along with transformer T1. A supply of about 12V capable of around 500mA can then be connected across C3. This can be backed by batteries of suitable type, the small sealed lead acid types common nowadays would be ideal. The float-charge voltage of these is around 13.8V, which will be OK for use with this circuit.

One final modification that some constructors may like to consider is replacement of variable capacitor VC1 with a smaller value in parallel with a fixed capacitor to make it less critical to adjust. On an early prototype a 1-10pf was used together with a 47pF ceramic, though a 15pF or 22pF might be better.

Although a silver mica type was used for capacitor C8, a ceramic should be OK as the effect of temperature will probably have little effect with the crystal as the primary timekeeper.




## REVOLVING TIME

And now the answer you've been eagerly awaiting . . . how does the clock work? The glass rotates! The minute hand is attached by a friction mechanism to allow time setting, and the hour hand is operated from it with an ingenious counterbalance and some gears. The overall effect is very pleasing to look at, and the way it works is not at all obvious to those who haven't met such clocks before. □
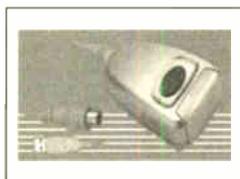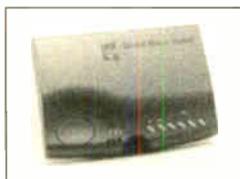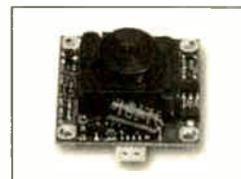
# Video Surveillance



- C-MOS B/W Camera 15mm/15mm £29.00
- C-MOS Colour Camera 15mm/15mm £65.00
- PCB B/W Camera 32mm/32mm £24.00
- PCB Colour Camera w/Audio 32mm/32mm £65.00
- 23cm (1.3GHz) Video/Audio Transmitter £35.00
- 13cm (2.4GHz) Video/Audio Transmitter £35.00
- 1.2 Watt 2.4GHz Video/Audio Transmitter £120.00
- 4" TFT Boxed Colour Monitor w/Audio £110.00
- Video to VGA Converter £65.00
- VGA to Video Converter £90.00
- External USB Video Capture Box £55.00




All prices exclude VAT.

Many more products on our website:

[WWW.BITZTECHNOLOGY.COM](http://WWW.BITZTECHNOLOGY.COM)

Tel: 01753 522 902 Fax: 01753 571 657

# CIRCUIT SURGERY

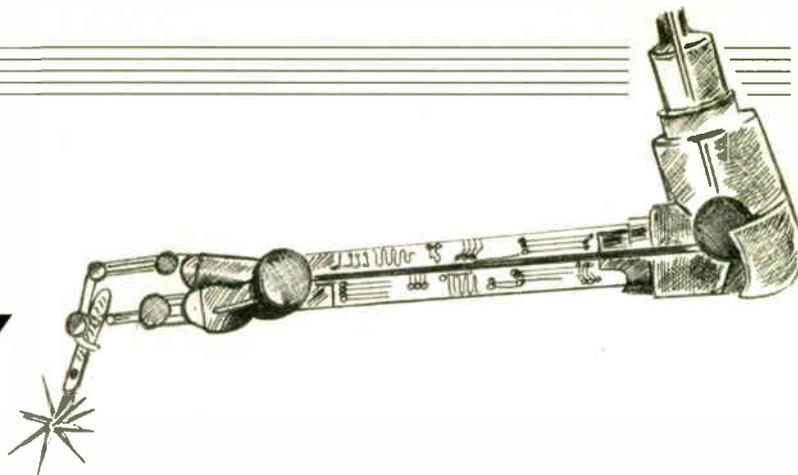

**ALAN WINSTANLEY  
and IAN BELL**

*Our monthly feature of readers' queries examines the use of differing types of decoupling capacitors and investigates the operating temperatures of electronic components*

## Curious Decoupling

*"As a beginner at electronics I am repeatedly baffled by the following: many times, usually on power supply circuits, I see two or more capacitors in parallel used for "decoupling" the supply line. One is usually big (say 100µF), and one smaller (100nF). What is the reason for using two capacitors?"*

*All I know about capacitors in parallel is that their total capacitance is the sum of their individual capacitances. I assume that this is not the reason for their use . . . namely to obtain a capacitance of 100.1µF!*

*Also if capacitive reactance is inversely proportional to frequency, then a large capacitor should be able to bypass the low frequencies and the high frequencies alike so why need the smaller capacitor? Also, how are the values for a suitable decoupling capacitor arrived at? Thanks in anticipation." Gerard Galvin by E-mail.*

Welcome to the real world! Your argument would be completely correct if the capacitors and power supply wires and tracks we used were *ideal*, but of course they are not. In particular, real capacitors have *inductance* due to the way they are made – as a spiral of material – which means that their impedance does not continue to fall off as frequency rises, in fact it may well *increase* again.

Larger value capacitors tend to have a larger inductance and hence poorer performance at high frequencies. Smaller value capacitors are made from materials that have better performance at high frequencies. Thus, *two* capacitors are often used in order to cover the full range of frequencies we have to deal with.

So why are decoupling capacitors used at all? The answer is to try to keep the power supply voltage as steady and as "clean" as possible. Many analogue circuits have poor **power supply rejection**, that is, if you vary the power supply voltage this variation will show up (as noise) in the signal at the circuit's output.

Digital circuits have a finite **noise margin**, which indicates how much you can shift a good logic output voltage by before the next

gate will not longer recognise it as a valid logic state. If you vary the power supply voltage then gate output voltages and input thresholds shift. If this shift exceeds the noise margin you may get a logic error.

We get variations in power supply voltage as a circuit operates because the power supply circuitry and the wiring between it is not ideal – it has a finite rather than zero impedance. As the current taken by the circuit (or various parts of it) changes, the voltage dropped across the supply's internal impedance and the power supply wires (p.c.b. tracks etc) varies. It is not just the positive rail voltage that can vary, the ground voltage (ideally zero) may vary too.

## Crosstalk

One of the problems this causes is **crosstalk**. Imagine an analogue circuit board processing multiple channels (e.g. amplifying several audio signals). As the signal in one channel varies, so will the current taken by that amplifier from the power supply; this will cause a variation of the power supply voltage in sympathy with the signal.

Thus, the other channels will have a power supply with voltage variations that follow the signal in the first channel! This will cause a variation in their output voltage that follows the signal in the first channel, so the signal from the first channel has "crossed" to the other via the power supply. Hopefully this signal will be very small compared to the proper signals for those channels.

However, crosstalk can also occur in digital circuits. As a gate (or set of gates and flip-flops) switches over, current is taken from the supply causing a voltage change on supply or ground rail (or both). If this voltage shift is large enough to overcome the noise margin of a gate elsewhere in the circuit (on the same supply line), then the logic state in the second sub-circuit may become erroneous. Thus the switching of one block of logic has caused another part of the circuit to react when it should not have done so.

A power supply voltage should be d.c. The unwanted effects we have just

discussed are effectively a.c. signals superimposed on the supply's d.c. voltage. If we "short out" the supply for a.c. signals we should be able to reduce the magnitude of these troublesome signals. That's why we use capacitors across the supply. They have infinite impedance at d.c., but low impedance at a.c.

What values should be used? First you need to know what the largest voltage change you can tolerate is likely to be. For digital circuits the main problem is caused by *changes* in current demand from the power supply going through the supply line inductance.

So to calculate the capacitor value, find the worse case step change in current you are likely to have. Then, the maximum voltage change divided by the maximum current change gives you the maximum supply line impedance. You also need to know the supply line resistance and series inductance (not necessarily very easy . . .).

From this and maximum impedance value you can use the usual impedance formula to find the frequency at which the supply impedance exceeds your required maximum. Then find the capacitance value that equals the maximum impedance value at this frequency to give the minimum capacitance you need. This calculation is straightforward but finding the values to go in it may not be!

## We Value Decoupling


For a reasonably sized digital circuit this may be a value in the region of tens or hundreds of microfarads. Such capacitors, as mentioned above, have inductance and will not provide supply decoupling at higher frequencies (check the effective series resistance and inductance of the capacitor you are using if you can).

The large capacitor is suitable for the board, but we also need smaller capacitors near to individual i.c.s to take care of the higher frequencies. The small capacitors have to be kept very close to the i.c.s they are decoupling, in order to keep the supply impedance between them and the i.c.s as small as possible. That's why you often see

ceramic capacitors close to the chips on large logic boards (see photograph below).

Supply decoupling is particularly demanding for high-speed logic. This is because of the very fast step changes in current demanded from the supply as logic lines switch. Often many lines switch at once.

From the defining equation for inductance  $V=(dI/dt)L$  we see that the voltage is determined by the rate of change of current ( $dI/dt$ ). Fast logic switching edges therefore result in large supply voltage changes due to supply line inductance. The faster the edges then the higher the frequencies which have to be handled by the decoupling and the larger the voltage drops become. For example, for a logic rise time of four nanoseconds (the waveform edge takes this time to go from 10% to 90% of its final value) frequencies of 250MHz will have to be dealt with by the decoupling.

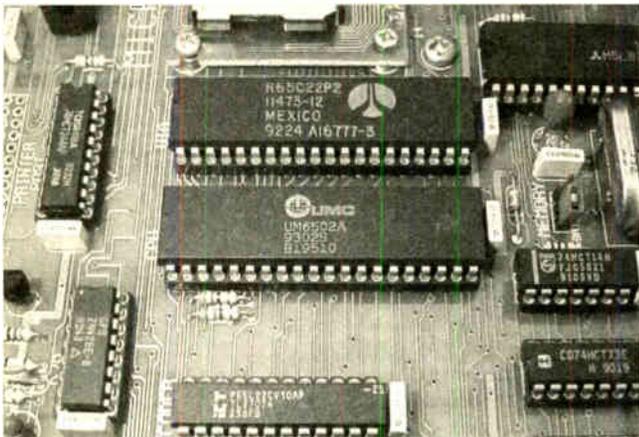

Decoupling capacitors positioned close to the logic chips on a microprocessor circuit board. Polyester types are used here

## Going Critical

In the electronics industry, decoupling and supply line characteristics are of critical importance in the design of state-of-the-art logic boards. Digital circuits are now so fast that hundreds of megahertz to gigahertz frequencies have to be considered.

Another problem associated with digital switching is the generation of radio frequency interference. Poorly designed p.c.b.s can result in the loops being formed via the decoupling capacitors and i.c. supplies acting like little radio transmitters. Just designing the power supply tracks on modern high speed digital boards can be a major feat of radio frequency engineering!

However, in modest hobby projects, you will often see just an electrolytic – say 220µF to 470µF – strapped across the supply, which helps to remove ripple in battery supply rails. This becomes more important as the battery begins to age. Elsewhere you may see a 100nF polyester capacitor in parallel, to catch high frequency noise.

Even with the simplest of circuits (let's say a 556 twin oscillator, operating from a single supply), placing decoupling capacitors near to the chip's supply pins can cure strange interaction amongst the oscillators, which will stabilise their operation. This is a classic case of a circuit that should work correctly "on paper" but it's only with a bit more experience that you learn some of the

tricks needed to coax them into operation in reality. *I.M.B.*

## Some Like it Hot


Reader *D. Lee* from the Wirral writes about hot components: "How hot should a component be when it is working normally? I have an alarm control panel and the transformer can be described as belching heat, measured at a constant 30°C. The 12V regulator heatsink was also very hot with some discolouring of nearby plastics.

The panel is in good working order, but the heat generated is astronomical. It is the same for a battery fast charger. Even the video recorder on standby seems to give off lots of heat from heatsinks."

Power is dissipated by the action of electronic circuitry, which in turn leads to increased temperature of the components and their immediate surroundings. That heat has

the properties of the materials in which it is embedded (e.g. whether they are thermal insulators or thermal conductors). Materials can be described by their *thermal resistance*, which indicates the ease with which heat flows through them. If we assume that the component's surroundings can absorb all the heat from it without changing temperature then we can calculate the difference between the surrounding temperature (known as ambient temperature) and the component.

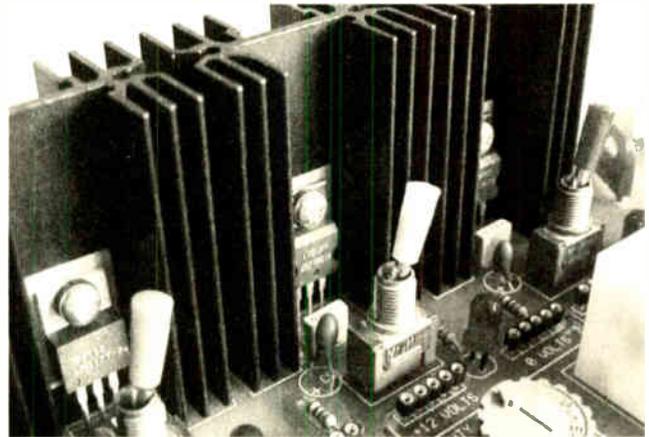From the point where the heat is generated in the component to the surroundings there may be a number of "layers", such as the component's packaging and a heatsink. We need to know the thermal resistance to heat flow between each of these layers (e.g. component to package, package to heatsink, heatsink to surroundings) in order to calculate the temperature of the component. Manufacturers of power



Heatsinks help to maintain the temperature of devices within their operating limits. Also note the decoupling capacitors close by – tantalum and polyester types are both used near these regulators

to go somewhere: the purpose of heatsinks is to remove excess heat energy from components to keep their temperature within bounds, so when you feel heat coming off a heatsink, it is only doing its intended job!

The real question is, how hot should a component be when working? This depends on the component of course, but it is possible to calculate thermal requirements for components and temperature data is often included in datasheets (especially those of semiconductors) and catalogues.

A component's maximum working temperature will be set either by degradation of the materials used to construct the component, or by onset of unacceptable changes in operating characteristics. In operation, components dissipate power, that is they produce a "continuous stream" of thermal energy.

If the thermal energy stays more or less where it is (i.e. in the component) the temperature of the component will continue to rise. However if the energy flows away from the component, a point will be reached where the energy leaving it equals the energy produced by the component, and it is this "balance" which determines the working temperature.

## Thermal Resistance

The flow of heat away from a component depends on the difference in temperature between it and its surroundings as well as

semiconductors publish thermal resistance data for their products, as do heatsink manufacturers, so we can obtain these figures.

## Power Dissipation

We also need the power dissipation in watts in the component, which the circuit designer should of course know. Then the temperature above ambient is found by multiplying the series thermal resistance (i.e. the sum of thermal resistances) by the power dissipated.


The fact that power dissipation causes a rise in temperature relative to ambient temperature, means that ambient temperature is an important consideration in the thermal design of electronics. This can be affected by ventilation in the system. Some systems, such as personal computers, need fans to keep the ambient temperature inside the case reasonably low.

For power transistors, the key issue is the junction temperature, which may typically have a maximum value of 100°C to 200°C. Specific temperature and thermal resistance figures are often published for power devices where it is assumed that heatsinks will be used and thermal calculations will be made by designers. For other components it is typical to be given maximum power ratings and ambient temperatures.

Next month we'll show you how to calculate heatsink ratings for a typical semiconductor application. *I.M.B.*

**WHETHER ELECTRONICS IS YOUR HOBBY  
OR YOUR LIVELIHOOD . . .  
YOU NEED THE MODERN ELECTRONICS MANUAL  
and the ELECTRONICS SERVICE MANUAL**

## THE MODERN ELECTRONICS MANUAL

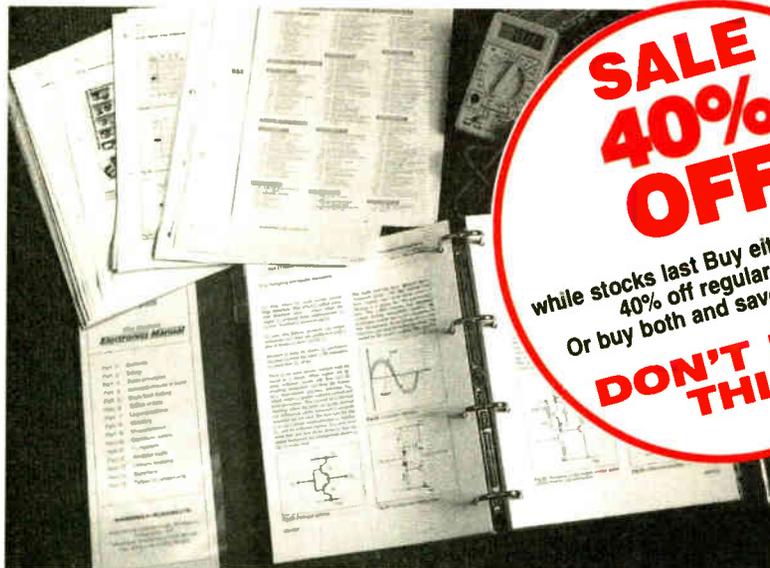

**SALE  
40%  
OFF**  
while stocks last Buy either Manual at  
40% off regular price.  
Or buy both and save even more.  
**DON'T MISS  
THIS!**

*The essential reference  
work for everyone  
studying electronics*

- Over 900 pages
- In-depth theory
- Projects to build
- Detailed assembly instructions
- Full components checklists
- Extensive data tables
- Detailed supply information
- Easy-to-use format
- Clear and simple layout
- Comprehensive subject range
- Professionally written
- Regular Supplements
- Sturdy gold blocked ring-binder

## EVERYTHING YOU NEED TO GET STARTED AND GO FURTHER IN ELECTRONICS!

The revised edition of the Modern Electronics Base Manual contains practical, easy-to-follow information on the following subjects:

**BASIC PRINCIPLES:** Electronic Components and their Characteristics (16 sections from Resistors and Potentiometers to Crystals, Crystal Modules and Resonators), Circuits Using Passive Components (9 sections), Power Supplies. The Amateur Electronics Workshop, The Uses of Semiconductors, Digital Electronics (6 sections), Operational Amplifiers, Introduction to Physics, Semiconductors (6 sections) and Digital Instruments (5 sections).

**CIRCUITS TO BUILD:** There's nothing to beat the satisfaction of creating your own project. From basic principles, like soldering and making printed circuit boards, to circuit-building, the Modern Electronics Manual and its Supplements describe clearly, with appropriate diagrams, how to assemble radios, loudspeakers,

amplifiers, car projects, computer interfaces, measuring instruments, workshop equipment, security systems, etc. The Base Manual describes 13 projects including a Theremin and a Simple TENS Unit.

**ESSENTIAL DATA:** Extensive tables on diodes, transistors, thyristors and triacs, digital and linear i.c.s.

**EXTENSIVE GLOSSARY:** Should you come across a technical word, phrase or abbreviation you're not familiar with, simply turn to the glossary included in the Manual and you'll find a comprehensive definition in plain English.

The Manual also covers **Safety** and **Suppliers**. The most comprehensive reference work ever produced at a price you can afford, the revised edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the *essential* information you need.

## THE MODERN ELECTRONICS MANUAL

**Revised Edition of Basic Work:** Contains over 900 pages of information. Edited by John Becker.

**Regular Supplements:** Approximately 160-page Supplements of additional information which, if requested, are forwarded to you immediately on publication (four times a year). These are billed separately and can be discontinued at any time.

**Presentation:** Durable looseleaf system in large A4 format

**Price of the Basic Work:** ~~£39.95~~ **SALE PRICE £23.97** (to include a recent Supplement **FREE**)

### Guarantee

Our 30 day money back guarantee gives you **complete peace of mind**. If you are not entirely happy with either Manual, for whatever reason, simply return it to us in good condition within 30 days and we will make a **full refund of your payment** – no small print and no questions asked.  
(Overseas buyers do have to pay the overseas postage charge)

# ELECTRONICS SERVICE MANUAL

## EVERYTHING YOU NEED TO KNOW TO GET STARTED IN REPAIRING AND SERVICING ELECTRONIC EQUIPMENT

**SAFETY:** Be knowledgeable about Safety Regulations, Electrical Safety and First Aid.

**UNDERPINNING KNOWLEDGE:** Specific sections enable you to Understand Electrical and Electronic Principles, Active and Passive Components, Circuit Diagrams, Circuit Measurements, Radio, Computers, Valves and manufacturers' Data, etc.

**PRACTICAL SKILLS:** Learn how to identify Electronic Components, Avoid Static Hazards, Carry Out Soldering and Wiring, Remove and Replace Components.

**TEST EQUIPMENT:** How to Choose and Use Test Equipment, Assemble a Toolkit, Set Up a Workshop, and Get the Most from Your Multimeter and Oscilloscope, etc.

**SERVICING TECHNIQUES:** The regular Supplements include vital guidelines on how to Service Audio Amplifiers, Radio Receivers, TV Receivers, Cassette Recorders, Video Recorders, Personal Computers, etc.

**TECHNICAL NOTES:** Commencing with the IBM PC, this section and the regular Supplements deal with a very wide range of specific types of equipment – radios, TVs, cassette recorders, amplifiers, video recorders etc..

**REFERENCE DATA:** Detailing vital parameters for Diodes, Small-Signal Transistors, Power Transistors, Thyristors, Triacs and Field Effect Transistors. Supplements include Operational Amplifiers, Logic Circuits, Optoelectronic Devices, etc.

## The essential work for servicing and repairing electronic equipment

- Around 900 pages
- Fundamental principles
- Troubleshooting techniques
- Servicing techniques
- Choosing and using test equipment
- Reference data
- Easy-to-use format
- Clear and simple layout
- Vital safety precautions
- Professionally written
- Regular Supplements
- Sturdy gold blocked ring-binder

## ELECTRONICS SERVICE MANUAL

**Basic Work:** Contains around 900 pages of information. Edited by Mike Tooley BA

**Regular Supplements:** Approximately 160-page Supplements of additional information which, if requested, are forwarded to you immediately on publication (four times a year). These are billed separately and can be discontinued at any time.

**Presentation:** Durable looseleaf system: in large A4 format

**Price of the Basic Work:** ~~£39.95~~ **SALE PRICE £23.97** (to include a recent Supplement FREE)

## ORDER BOTH MANUALS TOGETHER AND SAVE ANOTHER £8

*A mass of well-organised and clearly explained information is brought to you by expert editorial teams whose combined experience ensures the widest coverage*  
*Regular Supplements to these unique publications, each around 160 pages, keep you abreast of the latest technology and techniques if required*

### REGULAR SUPPLEMENTS

Unlike a book or encyclopedia, these Manuals are living works – continuously extended with new material. If requested, Supplements are sent to you approximately every three months. Each Supplement contains around 160 pages – all for only £23.50+£2.50 p&p. You can, of course, return any Supplement (within ten days) which

you feel is superfluous to your needs. You can also purchase a range of past Supplements to extend your Base Manual on subjects of particular interest to you.

### RESPONDING TO YOUR NEEDS

We are able to provide you with the most important and popular, up to date, features in our

Supplements. Our unique system is augmented by readers' requests for new information. Through this service you are able to let us know exactly what information you require in your Manuals.

You can also contact the editors directly in writing if you have a specific technical request or query relating to the Manuals.

**PLEASE** send me



- THE MODERN ELECTRONICS MANUAL plus a FREE SUPPLEMENT
- ELECTRONICS SERVICE MANUAL plus a FREE SUPPLEMENT

I enclose payment of £23.97 (for one Manual) or £39.94 for both Manuals (saving another £8 by ordering both together) plus postage if applicable.

I also require the appropriate Supplements four times a year. These are billed separately and can be discontinued at any time. (Please delete if not required.)

Should I decide not to keep the Manual/s I will return it/them to you within 30 days for a full refund.

FULL NAME .....  
 (PLEASE PRINT)

ADDRESS .....

.....POSTCODE .....

SIGNATURE .....

I enclose cheque/PO payable to Wimborne Publishing Ltd.

Please charge my Visa/Mastercard/Amex/Diners Club/Switch Switch Issue No.....

Card No. .... Card Exp. Date .....

### ORDER FORM

Simply complete and return the order form with your payment to the following address:

**Wimborne Publishing Ltd, Dept. Y9, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND**

**We offer a 30 day MONEY BACK GUARANTEE**

– if you are not happy with either Manual simply return it to us in good condition within 30 days for a full refund.

Overseas buyers do have to pay the overseas postage – see below.

### POSTAGE CHARGES

Postal Region	Price PER MANUAL	
	Surface	Air
Mainland UK	FREE	–
Scottish Highlands, UK Islands & Eire	£5.50 each	–
Europe (EU)	–	£20 each
Europe (Non-EU)	£20 each	£26 each
USA & Canada	£25 each	£33 each
Far East & Australasia	£31 each	£35 each
Rest of World	£25 each	£45 each

Please allow four working days for UK delivery.  
 NOTE: Surface mail can take over 10 weeks to some parts of the world. Each Manual weighs about 4kg when packed.

esm2

# DIRECT BOOK SERVICE

NOTE: ALL PRICES INCLUDE UK POSTAGE



## EPE TEACH-IN 2000 CD-ROM

The whole of the 12-part *Teach-In 2000* series by John Becker (published in *EPE* Nov '99 to Oct 2000) is now available on CD-ROM. Plus the *Teach-In 2000* interactive software covering all aspects of the series and Alan Winstanley's *Basic Soldering Guide* (including illustrations and Desoldering).

*Teach-In 2000* covers all the basic principles of electronics from Ohm's Law to Displays, including Op.Amps, Logic Gates etc. Each part has its own section on the interactive software where you can also change component values in the various on-screen demonstration circuits.

The series gives a hands-on approach to electronics with numerous breadboard circuits to try out, plus a simple computer interface which allows a PC to be used as a basic oscilloscope.

**ONLY £12.45** including VAT and p&p

Order code Teach-In CD-ROM

### PRACTICAL REMOTE CONTROL PROJECTS

Owen Bishop

Provides a wealth of circuits and circuit modules for use in remote control systems of all kinds; ultrasonic, infra-red, optical fibre, cable and radio. There are instructions for building fourteen novel and practical remote control projects. But this is not all, as each of these projects provides a model for building dozens of other related circuits by simply modifying parts of the design slightly to suit your own requirements. This book tells you how.

Also included are techniques for connecting a PC to a remote control system, the use of a microcontroller in remote control, as exemplified by the BASIC Stamp, and the application of ready-made type-approved 418MHz

## Computing & Robotics

### INTRODUCING ROBOTICS WITH LEGO MINDSTORMS

Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various "click-together" components supplied in the basic RIS kit. Explains in simple terms how the "brain" of the robot may be programmed on screen using a PC and "zapped" to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Detailed building and programming instructions provided, including numerous step-by-step photographs.

288 pages - large format Order code BP901 £14.99

### MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS - Robert Penfold

Covers the Vision Command System

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using Lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with 'waiter service' when you clap your hands, perform tricks, 'see' and avoid objects by using 'bats radar', or accurately follow a line marked on the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit.OCX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an 'intelligent' sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

298 pages Order code BP902 £14.99

radio transmitter and receiver modules to remote control systems.

160 pages Order code BP413 £6.49

### ELECTRONICS PROJECTS USING ELECTRONICS WORKBENCH plus FREE CD-ROM

M. P. Horsey

This book offers a wide range of tested circuit modules which can be used as electronics projects, part of an electronics course, or as a hands-on way of getting better acquainted with Electronics Workbench. With circuits ranging from 'bulbs and batteries' to complex systems using integrated circuits, the projects will appeal to novices, students and practitioners alike.

Electronics Workbench is a highly versatile computer simulation package which enables the user to design, test and modify their circuits before building them, and to plan PCB layouts on-screen. All the circuits in the book are provided as runnable Electronic Workbench files on the enclosed CD-ROM, and a selection of 15 representative circuits can be explored using the free demo version of the application.

Contents: Some basic concepts; Projects with switches, LEDs, relays and diodes; Transistors; Power supplies; Op.amp projects; Further op.amp circuits; Logic gates; Real logic circuits; Logic gate multivibrators; The 555 timer; Flip-flops, counters and shift registers; Adders, comparators and multipliers; Field effect transistors; Thyristors, triacs and diacs; Constructing your circuit; Index.

227 pages Order code NE29 £16.99

### A BEGINNER'S GUIDE TO MODERN ELECTRONIC COMPONENTS

R. A. Penfold

The purpose of this book is to provide practical information to help the reader sort out the bewildering array of components currently on offer. An advanced knowledge of the theory of electronics is not needed, and this book is not intended to be a course in electronic theory. The main aim is to explain the differences between components of the same basic type (e.g. carbon, carbon film, metal film, and wire-wound resistors) so that the right component for a given application can be selected. A wide range of components are included, with the emphasis firmly on those components that are used a great deal in projects for the home constructor.

170 pages Temporarily out of print

### DISCOVERING ELECTRONIC CLOCKS

W. D. Phillips

This is a whole book about designing and making electronic clocks. You start by connecting HIGH and LOW logic signals to logic gates. You find out about and then build and test bistables, crystal-controlled astables, counters, decoders and displays. All of these subsystems are

### PIC YOUR PERSONAL INTRODUCTORY COURSE

SECOND EDITION John Morton

Discover the potential of the PIC microcontroller through graded projects - this book could revolutionise your electronics construction work!

A uniquely concise and practical guide to getting up and running with the PIC Microcontroller. The PIC is one of the most popular of the microcontrollers that are transforming electronic project work and product design.

Assuming no prior knowledge of microcontrollers and introducing the PICs capabilities through simple projects, this book is ideal for use in schools and colleges. It is the ideal introduction for students, teachers, technicians and electronics enthusiasts. The step-by-step explanations make it ideal for self-study too; this is not a reference book - you start work with the PIC straight away.

The revised second edition covers the popular reprogrammable EEPROM PICs: P16C84/16F84 as well as the P54 and P71 families.

270 pages Order code NE36 £13.99

### INTRODUCTION TO MICROPROCESSORS

John Crisp

If you are, or soon will be, involved in the use of microprocessors, this practical introduction is essential reading. This book provides a thoroughly readable introduction to microprocessors, assuming no previous knowledge of the subject, nor a technical or mathematical background. It is suitable for students, technicians, engineers and hobbyists, and covers the full range of modern microprocessors.

After a thorough introduction to the subject, ideas are developed progressively in a well-structured format. All technical terms are carefully introduced and subjects which have proved difficult, for example 2's complement, are clearly explained. John Crisp covers the complete range of microprocessors from the popular 4-bit and 8-bit designs to today's super-fast 32-bit and 64-bit versions that power PCs and engine management systems etc.

222 pages Order code NE31 £18.99

## Circuits and Design

carefully explained, with practical work supported by easy to follow prototype board layouts.

Full constructional details, including circuit diagrams and a printed circuit board pattern, are given for a digital electronic clock. The circuit for the First Clock is modified and developed to produce additional designs which include a Big Digi Clock, Binary Clock, Linear Clock, Andrew's Clock (with a semi-analogue display), and a Circles Clock. All of these designs are unusual and distinctive.

This is an ideal resource for project work in GCSE Design and Technology: Electronics Product, and for project work in AS-Level and A-Level Electronics and Technology.

194 pages, A4 spiral bound Order code DEP1 £17.50

### 50 SIMPLE LED CIRCUITS

R. N. Soar

Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components - the Light Emitting Diode (or L.E.D.). Also includes circuits for the 707 Common Anode Display.

A useful book for the library of both beginner and more advanced enthusiasts alike.

62 pages Order code BP42 £3.49

### 50 SIMPLE LED CIRCUITS BOOK 2

R. N. Soar

Following the tremendous success of book number BP42, 50 SIMPLE LED CIRCUITS, the author has devised and developed a further series of useful applications and circuits, covering many different branches of electronics, using the simple Light Emitting Diode (L.E.D.) and these are now published as Book 2.

Book 2 in no way supersedes or replaces the original book but complements it, offering many more ideas and circuits to the reader. A useful book for the library of both beginner and more advanced enthusiasts alike.

57 pages Order code BP87 £3.49

### DOMESTIC SECURITY SYSTEMS

A. L. Brown

This book shows you how, with common sense and basic do-it-yourself skills, you can protect your home. It also gives tips and ideas which will help you to maintain and improve your home security, even if you already have an alarm. Every circuit in this book is clearly described and illustrated, and contains components that are easy to source. Advice and guidance are based on the real experience of the author who is an alarm installer, and the designs themselves have been rigorously put to use on some of the most crime-ridden streets in the world.

The designs include all elements, including sensors, -detectors, alarms, controls, lights, video and door entry systems. Chapters cover installation, testing, maintenance and upgrading.

192 pages Order code NE25 £15.99

### MICROCONTROLLER COOKBOOK

Mike James

The practical solutions to real problems shown in this cookbook provide the basis to make PIC and 8051 devices really work. Capabilities of the variants are examined, and ways to enhance these are shown. A survey of common interface devices, and a description of programming models, lead on to a section on development techniques. The cookbook offers an introduction that will allow any user, novice or experienced, to make the most of microcontrollers.

240 pages Order code NE26 £21.99

### A BEGINNER'S GUIDE TO TTL DIGITAL ICs

R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip/flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in the "real world".

142 pages Order code BP332 £5.45

### ELECTRONIC MODULES AND SYSTEMS FOR BEGINNERS

Owen Bishop

This book describes over 60 modular electronic circuits, how they work, how to build them, and how to use them. The modules may be wired together to make hundreds of different electronic systems, both analogue and digital. To show the reader how to begin building systems from modules, a selection of over 25 electronic systems are described in detail, covering such widely differing applications as timing, home security, measurement, audio (including a simple radio receiver), games and remote control.

200 pages Order code BP266 £4.45

### PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Bridges the gap between complicated technical theory, and "cut-and-try" methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias - tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-Current Circuits, Passive Components, Alternating-Current Circuits, Networks and Theorems, Measurements.

256 pages Order code BP53 £5.49

# Theory and Reference

## Bebop To The Boolean Boogie


By Clive (call me Max)  
Maxfield

ORDER CODE BEB1

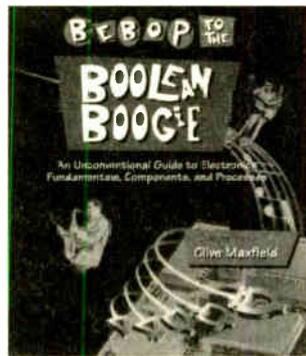**£26.95**

**470 pages. Large format**  
**Specially imported by EPE –**  
**Excellent value**

**An Unconventional Guide to**  
**Electronics Fundamentals,**  
**Components and Processes**



This book gives the "big picture" of digital electronics. This indepth, highly readable, up-to-the-minute guide shows you how electronic devices work and how they're made. You'll discover how transistors operate, how printed circuit boards are fabricated, and what the innards of memory ICs look like. You'll also gain a working knowledge of Boolean Algebra and Karnaugh Maps, and understand what Reed-Muller logic is and how it's used. And there's much, MUCH more (including a recipe for a truly great seafood gumbo!).

Hundreds of carefully drawn illustrations clearly show the important points of each topic. The author's tongue-in-cheek British humor makes it a delight to read, but this is a REAL technical book, extremely detailed and accurate. A great reference for your own shelf, and also an ideal gift for a friend or family member who wants to understand what it is you do all day. . . .

470 pages – large format **Order code BEB1** **£26.95**

**DIGITAL ELECTRONICS – A PRACTICAL APPROACH**  
**With FREE Software: Number One Systems – EASY-PC**  
**Professional XM and Pulsar (Limited Functionality)**

**Richard Monk**

Covers binary arithmetic, Boolean algebra and logic gates, combination logic, sequential logic including the design and construction of asynchronous and synchronous circuits and register circuits. Together with a considerable practical content plus the additional attraction of its close association with computer-aided design including the FREE software.

There is a 'blow-by-blow' guide to the use of EASY-PC Professional XM (a schematic drawing and printed circuit board design computer package). The guide also conducts the reader through logic circuit simulation using Pulsar software. Chapters on p.c.b. physics and p.c.b. production techniques make the book unique, and with its host of project ideas make it an ideal companion for the integrative assignment and common skills components required by BTEC and the key skills demanded by GNVQ. The principal aim of the book is to provide a straightforward approach to the understanding of digital electronics.

Those who prefer the 'Teach-In' approach or would rather experiment with some simple circuits should find the book's final chapters on printed circuit board production and project ideas especially useful.

250 pages **Order code NE28** **£17.99**

**DIGITAL GATES AND FLIP-FLOPS**

**Ian R. Sinclair**

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of micro-processor techniques as applied to digital logic.

200 pages **Order code PC106** **£9.95**

**FREE**  
**SOFTWARE**

## Bebop Bytes Back

By Clive "Max" Maxfield  
and Alvin Brown

ORDER CODE BEB2


**£31.95**

**Over 500 pages. Large**  
**format**

**Specially imported by**  
**EPE – Excellent value**

**An Unconventional Guide**  
**To Computers**

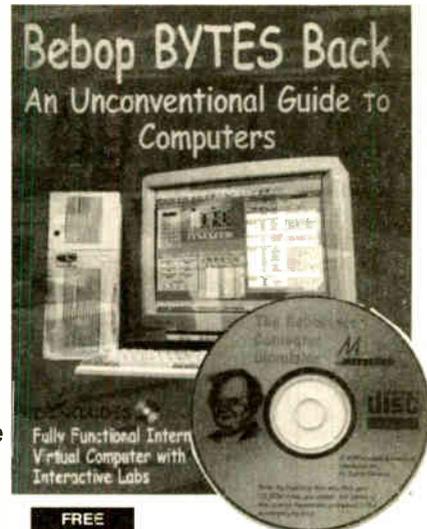**Plus FREE CD-ROM which**  
**includes: Fully Functional**  
**Internet-Ready Virtual**  
**Computer with Interactive**  
**Labs**



**FREE**  
**CD-ROM**

This follow-on to *Bebop to the Boolean Boogie* is a multimedia extravaganza of information about how computers work. It picks up where "Bebop I" left off, guiding you through the fascinating world of computer design . . . and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the accompanying CD-ROM (for Windows 95 machines only) contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the book contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this one!

Over 500 pages – large format **Order code BEB2** **£31.95**

**UNDERSTANDING ELECTRONIC CONTROL SYSTEMS**

**Owen Bishop**

Owen Bishop has produced a concise, readable text to introduce a wide range of students, technicians and professionals to an important area of electronics. Control is a highly mathematical subject, but here maths is kept to a minimum, with flow charts to illustrate principles and techniques instead of equations.

Cutting edge topics such as microcontrollers, neural networks and fuzzy control are all here, making this an ideal refresher course for those working in industry. Basic principles, control algorithms and hardwired control systems are also fully covered so the resulting book is a comprehensive text and well suited to college courses or background reading for university students.

The text is supported by questions under the headings Keeping Up and Test Your Knowledge so that the reader can develop a sound understanding and the ability to apply the techniques they are learning.

228 pages

**Order code NE35**

**£17.99**

**All prices**  
**INCLUDE UK POSTAGE**

# Audio and Music

**AN INTRODUCTION TO LOUSPEAKERS AND**  
**ENCLOSURE DESIGN**

**V. Capel**

This book explores the various features, good points and snags of speaker designs. It examines the whys and wherefores so that the reader can understand the principles involved and so make an informed choice of design, or even design loudspeaker enclosures for him – or herself. Crossover units are also explained, the various types, how they work, the distortions they produce and how to avoid them. Finally there is a step-by-step description of the construction of the Kapellmeister loudspeaker enclosure.

148 pages

**Temporarily out of print**

**PREAMPLIFIER AND FILTER CIRCUITS**

**R. A. Penfold**

This book provides circuits and background information for a range of preamplifiers, plus tone controls, filters, mixers, etc. The use of modern low noise operational amplifiers and a specialist high performance audio preamplifier i.c. results in circuits that have excellent performance, but which are still quite simple. All the circuits featured can be built at quite low cost (just a few pounds in most cases). The preamplifier circuits featured include: Microphone preamplifiers (low

impedance, high impedance, and crystal). Magnetic cartridge pick-up preamplifiers with R.I.A.A. equalisation. Crystal/ceramic pick-up preamplifier. Guitar pick-up preamplifier. Tape head preamplifier (for use with compact cassette systems).

Other circuits include: Audio limiter to prevent overloading of power amplifiers. Passive tone controls. Active tone controls. PA filters (highpass and lowpass). Scratch and rumble filters. Loudness filter. Audio mixers. Volume and balance controls.

92 pages

**Order code BP309**

**£4.49**

**HIGH POWER AUDIO AMPLIFIER CONSTRUCTION**

**R. A. Penfold**

Practical construction details of how to build a number of audio power amplifiers ranging from about 50 to 300/400 watts r.m.s. includes MOSFET and bipolar transistor designs.

96 pages

**Order code BP277**

**£4.49**

**ELECTRONIC MUSIC AND MIDI PROJECTS**

**R. A. Penfold**

Whether you wish to save money, boldly go where no

musician has gone before, rekindle the pioneering spirit, or simply have fun building some electronic music gadgets, the designs featured in this book should suit your needs. The projects are all easy to build, and some are so simple that even complete beginners at electronic project construction can tackle them with ease. Stripboard layouts are provided for every project, together with a wiring diagram. The mechanical side of construction has largely been left to the individual constructors to sort out, simply because the vast majority of project builders prefer to do their own thing in this respect.

None of the designs requires the use of any test equipment in order to get them set up properly. Where any setting up is required, the procedures are very straightforward, and they are described in detail.

Projects covered: Simple MIDI tester, Message grabber, Byte grabber, THRU box, MIDI auto switcher, Auto/manual switcher, Manual switcher, MIDI patchbay, MIDI controlled switcher, MIDI lead tester, Program change pedal, Improved program change pedal, Basic mixer, Stereo mixer, Electronic swell pedal, Metronome, Analogue echo unit.

138 pages

**Order code PC116**

**£10.95**

# Testing, Theory, Data and Reference

## SCROGGIE'S FOUNDATIONS OF WIRELESS AND ELECTRONICS - ELEVENTH EDITION

S.W. Amos and Roger Amos

Scroggie's Foundations is a classic text for anyone working with electronics, who needs to know the art and craft of the subject. It covers both the theory and practical aspects of a huge range of topics from valve and tube technology, and the application of cathode ray tubes to radar, to digital tape systems and optical recording techniques.

Since *Foundations of Wireless* was first published over 60 years ago, it has helped many thousands of readers to become familiar with the principles of radio and electronics. The original author Sowerby was succeeded by Scroggie in the 1940s, whose name became synonymous with this classic primer for practitioners and students alike. Stan Amos, one of the fathers of modern electronics and the author of many well-known books in the area, took over the revision of this book in the 1980s and it is he, with his son, who have produced this latest version.

400 pages **Order code NE27** £21.99

## ELECTRONICS MADE SIMPLE

Ian Sinclair

Assuming no prior knowledge, *Electronics Made Simple* presents an outline of modern electronics with an emphasis on understanding how systems work rather than on details of circuit diagrams and calculations. It is ideal for students on a range of courses in electronics, including GCSE, C&G and GNVQ, and for students of other subjects who will be using electronic instruments and methods.

Contents: waves and pulses, passive components, active components and ICs, linear circuits, block and circuit diagrams, how radio works, disc and tape recording, elements of TV and radar, digital signals, gating and logic circuits, counting and correcting, microprocessors, calculators and computers, miscellaneous systems.

199 pages (large format) **Order code NE23** £13.99

## TRANSISTOR DATA TABLES

Hans-Günther Steidle

The tables in this book contain information about the package shape, pin connections and basic electrical data for each of the many thousands of transistors listed. The data includes maximum reverse voltage, forward current and power dissipation, current gain and forward transmittance and resistance, cut-off frequency and details of applications.

A book of this size is of necessity restricted in its scope, and the individual transistor types cannot therefore be described in the sort of detail that maybe found in some larger and considerably more expensive data books. However, the list of manufacturers' addresses will make it easier for the prospective user to obtain further information, if necessary.

Lists over 8,000 different transistors, including f.e.t.s.  
200 pages **Order code BP401** £6.45

## ELECTRONIC TEST EQUIPMENT HANDBOOK

Steve Money

The principles of operation of the various types of test instrument are explained in simple terms with a minimum of mathematical analysis. The book covers analogue and digital meters, bridges, oscilloscopes, signal generators, counters, timers and frequency measurement. The practical uses of the instruments are also examined.

Everything from Oscillators, through R, C & L measurements (and much more) to Waveform Generators and testing Zeners.

206 pages **Order code PC109** £9.95

## GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic products.

96 pages **Order code BP239** £3.45

## NEWNES ELECTRONICS TOOLKIT - SECOND EDITION

Geoff Phillips

The author has used his 30 years experience in industry to draw together the basic information that is constantly demanded. Facts, formulae, data and charts are presented to help the engineer when designing, developing, evaluating, fault finding and repairing electronic circuits. The result is this handy workmate volume: a memory aid, tutor and reference source which is recommended to all electronics engineers, students and technicians.

Have you ever wished for a concise and comprehensive guide to electronics concepts and rules of thumb? Have you ever been unable to source a component, or choose between two alternatives for a particular application? How much time do you spend searching for basic facts or manufacturer's specifications? This book is the answer, it covers resistors, capacitors, inductors, semiconductors, logic circuits, EMC, audio, electronics and music, telephones, electronics in lighting, thermal considerations, connections, reference data.

158 pages **Order code NE20** £15.99

## PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING

Robin Pain

This is not a book of theory. It is a book of practical tips, hints, and rules of thumb, all of which will equip the reader to tackle any job. You may be an engineer or technician in search of information and guidance, a college student, a hobbyist building a project from a magazine, or simply a keen self-taught amateur who is interested in electronic fault finding but finds books on the subject too mathematical or specialized.

The book covers: Basics - Voltage, current and resistance; Capacitance, inductance and impedance; Diodes and transistors; Op-amps and negative feedback; Fault finding - Analogue fault finding, Digital fault finding; Memory; Binary and hexadecimal; Addressing; Discrete logic; Microprocessor action; I/O control; CRT control; Dynamic RAM; Fault finding digital systems; Dual trace oscilloscope; IC replacement.

274 pages **Order code NE22** £20.99

## AN INTRODUCTION TO LIGHT IN ELECTRONICS

F. A. Wilson

This book is not for the expert but neither is it for the completely uninitiated. It is assumed the reader has

some basic knowledge of electronics. After dealing with subjects like Fundamentals, Waves and Particles and The Nature of Light such things as Emitters, Detectors and Displays are discussed. Chapter 7 details four different types of Lasers before concluding with a chapter on Fibre Optics.

161 pages **Order code BP359** £5.45

## UNDERSTANDING DIGITAL TECHNOLOGY

F. A. Wilson C.G.I.A., C.Eng., F.I.E.E., F.I. Mgt.

This book examines what digital technology has to offer and then considers its arithmetic and how it can be arranged for making decisions in so many processes. It then looks at the part digital has to play in the ever expanding Information Technology, especially in modern transmission systems and television. It avoids getting deeply involved in mathematics.

Various chapters cover: Digital Arithmetic, Electronic Logic, Conversions between Analogue and Digital Structures, Transmission Systems. Several Appendices explain some of the concepts more fully and a glossary of terms is included.

183 pages **Order code BP376** £5.45

# Project Building

## ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering; making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby.

135 pages **Order code BP392** £5.45

## 45 SIMPLE ELECTRONIC TERMINAL BLOCK PROJECTS

R. Bebington

Contains 45 easy-to-build electronic projects that can be constructed, by an absolute beginner, on terminal blocks using only a screwdriver and other simple hand tools. No soldering is needed.

Most of the projects can be simply screwed together, by following the layout diagrams, in a matter of minutes and readily unscrewed if desired to make new circuits. A theoretical circuit diagram is also included with each project to help broaden the constructor's knowledge.

The projects included in this book cover a wide range of interests under the chapter headings: Connections and Components, Sound and Music, Entertainment, Security Devices, Communication, Test and Measuring.

163 pages **Order code BP378** £5.45

## 30 SIMPLE IC TERMINAL BLOCK PROJECTS

R. Bebington

Follow on from BP378 using ICs.

117 pages **Order code BP379** £5.49

## HOW TO DESIGN AND MAKE YOUR OWN P.C.B.S

R. A. Penfold

Deals with the simple methods of copying printed circuit board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.

80 pages **Order code BP121** £4.49

## IC555 PROJECTS

E. A. Parr

Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. It was first manufactured by Signetics, but is now manufactured by almost every semiconductor manufacturer in the world and is inexpensive and very easily obtainable.

Included in this book are over 70 circuit diagrams and descriptions covering basic and general circuits, motor car and model railway circuits, alarms and noise makers as well as a section on 556, 558 and 559 timers. (Note. No construction details are given.)

A reference book of invaluable use to all those who have any interest in electronics, be they professional engineers or designers, students of hobbyists.

167 pages **Order code BP44** £4.49

# BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £1 per book. For the rest of the world airmail add £2 per book. Send a PO, cheque, international money order (£ sterling only) made payable to **DIRECT BOOK SERVICE** or card details, Visa, Mastercard, Amex, Diners Club or Switch - minimum card order is £5 - to: **DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LIMITED, 408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery - more for overseas orders. *Please check price and availability (see latest issue of Everyday Practical Electronics) before ordering from old lists.*

For a further selection of books see the next two issues of *EPE*.

Tel 01202 873872 Fax 01202 874562. E-mail: [dbs@epemag.wimborne.co.uk](mailto:dbs@epemag.wimborne.co.uk)

Order from our online shop at: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

# BOOK ORDER FORM

Full name: .....

Address: .....

Post code: ..... Telephone No: .....

Signature: .....

I enclose cheque/PO payable to DIRECT BOOK SERVICE for £ .....

Please charge my card £ ..... Card expiry date .....

Card Number ..... Switch Issue No.....

Please send book order codes: .....

Please continue on separate sheet of paper if necessary

# PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to The PCB Service, *Everyday Practical Electronics*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872; Fax 01202 874562; E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk). On-line Shop: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm). Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).  
**NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery - overseas readers allow extra if ordered by surface mail. Back numbers or photostats of articles are available if required - see the Back Issues page for details.**

**Please check price and availability in the latest issue.**  
**Boards can only be supplied on a payment with order basis.**

PROJECT TITLE	Order Code	Cost
Handheld Function Generator	DEC '98 213	£4.00
★ Fading Christmas Lights	215	£5.16
PhizzyB I/O Board (4-section)	216	£3.95
Twinkle Twinkle Reaction Game	JAN '99 210	£7.55
★ EPE Mind PICkler	214	£6.30
PhizzyB I/O Board (4-section)	216	£3.95
Alternative Courtesy Light Controller	217	£6.72
Light Alarm	FEB '99 218	£6.78
★ Wireless Monitoring System	219+a	£9.92
Receiver	220+a	£8.56
★ PIC MIDI Sustain Pedal	Software only	-
★ Wireless Monitoring System-2	MAR '99 219a/220a	Feb '99
F.M. Trans/Rec Adaptors	221	£7.37
★ Time and Date Generator	222	£6.36
Auto Cupboard Light	224	£5.15
Ironing Board Saver	APR '99 225	£5.12
Voice Record/Playback Module	226A&B	£7.40
Mechanical Radio (pair)	207	£6.82
★ Versatile Event Counter	MAY '99 227	£8.95
PIC Toolkit Mk2	228	£3.00
A.M./F.M. Radio Remote Control - Transmitter	229	£3.20
Receiver	231	£9.51
★ Musical Sundial	JUNE '99 232	£8.79
PC Audio Frequency Meter	233	£6.78
★ EPE Mood PICkler	JULY '99 234	£6.72
12V Battery Tester	235	£7.10
Intruder Deterrent	932	£3.00
L.E.D. Stroboscope (Multi-project PCB)	AUG '99 236	£5.00
Ultrasonic Puncture Finder	237	£8.88
★ 8-Channel Analogue Data Logger	238	£6.96
Buffer Amplifier (Oscillators Pt 2)	239	£6.77
Magnetic Field Detective	240	£6.53
Sound Activated Switch	932	£3.00
Freezer Alarm (Multi-project PCB)	SEPT '99 241	£7.51
Child Guard	242	£7.64
Variable Dual Power Supply	OCT '99 243	£3.50
Micro Power Supply	244	£7.88
★ Interior Lamp Delay	932	£3.00
Mains Cable Locator (Multi-project PCB)	NOV '99 230	£6.93
Vibralarm	245	£6.78
Demister One-Shot	246	£7.82
★ Ginormous Stopwatch - Part 1	DEC '99 247	£7.85
★ Ginormous Stopwatch - Part 2	248	£3.96
Giant Display	249	£4.44
Serial Port Converter	250	£4.83
Loft Guard	932	£3.00
Scratch Blanker	JAN '00 251	£5.63
Flashing Snowman (Multi-project PCB)	252	£4.20
★ Video Cleaner	253	£4.52
Find It	MAR '00 254, 255	£5.49
★ Teach-In 2000 - Part 4	256	Set
High Performance Regenerative Receiver	Set only	£22.99
★ EPE Icebreaker - PCB257, programmed PIC16F877 and floppy disc	258	£5.08
Parking Warning System	APR '00 259	£4.99
★ Micro-PICscope	261	Set
Garage Link - Transmitter	262	£5.87
Receiver	MAY '00 260	£3.33
Versatile Mic/Audio Preamplifier	263	£3.17
PIR Light Checker	264	Set
★ Multi-Channel Transmission System - Transmitter	265	£6.34
Receiver	266	Set
Interface	JUNE '00 267	£3.05
★ Canute Tide Predictor	JULY '00 268	£5.07
★ PIC-Gen Frequency Generator/Counter	269	£4.36
G-Meter	AUG '00 271	£5.47
★ EPE Moodloop	272	£4.52
Quiz Game Indicator	273	£4.52
Handy-Amp	SEPT '00 274	£4.67
Active Ferrite Loop Aerial	Software only	-
★ Remote Control IR Decoder	OCT '00 275	£5.15
★ PIC Dual-Channel Virtual Scope	NOV '00 270	£3.96
Handclap Switch	Software only	-
★ PIC Pulsometer	DEC '00 276	£4.28
Twinkling Star	277	£5.71
Festive Fader	278	£5.39
Motorists' Buzz-Box	279	£4.91
★ PICtogram	280	£4.75
★ PIC-Monitored Dual PSU-1 PSU	281	£5.23
Monitor Unit	932	£3.00
Static Field Detector (Multi-project PCB)		

PROJECT TITLE	Order Code	Cost
Two-Way Intercom	JAN '01 282	£4.76
UFO Detector and Event Recorder	283	} Set £6.19
Magnetic Anomaly Detector	284	
Event Recorder	285	
Audio Alarm	-	-
★ Using PICs and Keypads	Software only	-
Ice Alarm	FEB '01 287	£4.60
★ Graphics L.C.D. Display with PICs (Supp)	288	£5.23
Using the LM3914-6 L.E.D. Bargraph Drivers	289	} Set £7.14
Multi-purpose Main p.c.b.	290	
Relay Control	291	
L.E.D. Display	-	-
★ PC Audio Power Meter	Software only	-
Doorbell Extender: Transmitter	MAR '01 292	£4.20
Receiver	293	£4.60
Trans/Remote	294	£4.28
Rec./Relay	295	£4.92
EPE Snug-bug Heat Control for Pets	APR '01 296	£6.50
Intruder Alarm Control Panel	297	£6.97
Main Board	298	£4.76
External Bell Unit	MAY '01 299	£6.34
Camcorder Mixer	300	£5.07
★ PIC Graphics L.C.D. Scope	JUNE '01 301	£5.14
Hosepipe Controller	302	£4.91
Magfield Monitor (Sensor Board)	303	£4.36
Dummy PIR Detector	-	-
★ PIC16F87x Extended Memory	Software only	-
Stereo/Surround Sound Amplifier	JULY '01 304	£4.75
Perpetual Projects Uniboard	305	£3.00
Solar-Powered Power Supply & Voltage Reg.	306	£4.75
MSF Signal Repeater and Indicator	307	£4.44
Repeater Board	308	£5.39
Meter Board	309	£4.99
★ PIC to Printer Interface	AUG '01 310	£5.07
Lead/Acid Battery Charger	311	£6.50
Shortwave Loop Aerial	312	£4.36
★ Digitimer - Main Board	-	-
- R.F. Board	305	£3.00
Perpetual Projects Uniboard-2	SEPT '01 305	£3.00
L.E.D. Flasher - Double Door-Buzzer	313	} Set £6.10
Perpetual Projects Uniboard - Loop Burglar Alarm, Touch-Switch Door-Light and Solar-Powered Rain Alarm	314	
L.E.D. Super Torches - Red Main	315	
- Display Red	316	£5.94
- White L.E.D.	317	£4.91
★ Sync Clock Driver		
★ Water Monitor		

## EPE SOFTWARE

Software programs for *EPE* projects marked with an asterisk \* are available on 3.5 inch PC-compatible disks or free from our Internet site. The following disks are available: *PIC Tutorial* (Mar-May '98 issues); *PIC Toolkit Mk2 V2-4d* (May-Jun '99 issues); *EPE Disk 1* (Apr '95-Dec '98 issues); *EPE Disk 2* (Jan-Dec '99); *EPE Disk 3* (Jan-Dec '00); *EPE Disk 4* (Jan '01 issue to current cover date); *EPE Teach-In 2000*; *EPE Interface Disk 1* (October '00 issue to current cover date). The disks are obtainable from the *EPE PCB Service* at £3.00 each (UK) to cover our admin costs (the software itself is free). Overseas (each): £3.50 surface mail, £4.95 each airmail. All files can be downloaded free from our Internet FTP site: [ftp://ftp.epemag.wimborne.co.uk](http://ftp.epemag.wimborne.co.uk).

## EPE PRINTED CIRCUIT BOARD SERVICE

Order Code	Project	Quantity	Price
Name .....			
Address .....			
Tel. No. ....			
I enclose payment of £..... (cheque/PO in £ sterling only) to:			
 <b>Everyday Practical Electronics</b> 		 <b>MasterCard, Amex, Diners Club, Visa or Switch</b> 	
Minimum order for cards £5		Switch Issue No. ....	
Card No. ....			
Signature..... Card Exp. Date.....			
<p><b>NOTE: You can also order p.c.b.s by phone, Fax, E-mail or via our Internet site on a secure server:</b>  <a href="http://www.epemag.wimborne.co.uk/shopdoor.htm">http://www.epemag.wimborne.co.uk/shopdoor.htm</a></p>			

Everyday Practical Electronics reaches twice as many UK readers as any other UK monthly hobby electronics magazine, our audited sales figures prove it. We have been the leading monthly magazine in this market for the last sixteen years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. VAT must be added. Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, Mill Lodge, Mill Lane, Thorpe-le-Soken, Essex CO16 0ED. Phone/Fax (01255) 861161.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

Valve Output Transformers: Single ended 50mA, £4.50; push/pull 15W, £27; 30W, £32; 50W, £38; 100W, £53. Mains Transformers: Sec 220V 30mA 6V 1A, £3; 250V 60mA 6V 2A, £5; 250V 80mA 6V 2A, £6. High Voltage Caps: 50µF 350V, 68µF 500V, 150µF 385V, 330µF 400V, 470µF 385V, all £3 ea., 32+32µF 450V £5, 4µF 800V oil filled paper block, £10. Postage extra.  
Record Decks and Spares: BSR, Garrard, Goldring, motors, arms, wheels, headshells, spindles, etc. Send or phone your want list for quote.

**RADIO COMPONENT SPECIALISTS**

**337 WHITEHORSE ROAD, CROYDON**  
**SURREY, CR0 2HS. Tel: (020) 8684 1685**

Lots of transformers, high volt caps, valves, output transformers, speakers, in stock. Phone or send your wants list for quote.

**Z88** NOW AVAILABLE WITH  
128K AND 512K - OZ4

**ALSO SPECTRUM  
AND QL PARTS**

**W. N. RICHARDSON & CO.**  
PHONE/FAX 01494 871319  
E-mail: wnr@compuserve.com  
RAVENSMOOR, CHALFONT ST PETER, BUCKS, SL9 0NB

**TIS - Midlinbank Farm**  
**Ryeland, Strathaven ML10 6RD**

*Manuals on anything electronic*

Circuits - VCR £8, CTV £6  
Service Manuals from £10  
Repair Manuals from £5  
P&P any order £2.50

*Write, or ring 01357 440280 for full details  
of our lending service and FREE quote for  
any data*

**BTEC ELECTRONICS  
TECHNICIAN TRAINING**

VCE ADVANCED ENGINEERING  
ELECTRONICS AND ICT  
HNC AND HND ELECTRONICS  
NVQ ENGINEERING AND IT  
*Next course commences  
SEPTEMBER 2001*  
FULL PROSPECTUS FROM

**LONDON ELECTRONICS COLLEGE**  
(Dept EPE) 20 PENYWERN ROAD  
EARLS COURT, LONDON SW5 9SU  
TEL: (020) 7373 8721

**THE BRITISH AMATEUR  
ELECTRONICS CLUB**

exists to help electronics enthusiasts by personal contact and through a quarterly Newsletter.

For membership details, write to the Secretary:  
**Mr. M. P. Moses,**  
5 Park View, Cwmaman,  
Aberdare CF44 6PP  
Space donated by  
**Everyday Practical Electronics**

**Miscellaneous**

**X-10<sup>®</sup> Home Automation**  
**We put you in control™**

**Why tolerate when you can automate?**

An extensive range of 230V X-10 products and starter kits available. Uses proven Power Line Carrier technology, no wires required.

Products Catalogue available Online.  
Worldwide delivery.

**Laser Business Systems Ltd.**

E-Mail: info@laser.com  
http://www.laser.com  
Tel: (020) 8441 9788  
Fax: (020) 8449 0430


**Test Equipment**



**Service Manuals.**

Contact  
[www.cooke-int.com](http://www.cooke-int.com)  
Tel: +44 01243 55 55 90

**PRINTED CIRCUIT BOARDS - QUICK SERVICE.** Prototype and production artwork raised from magazines or draft designs at low cost. PCBs designed from schematics. Production assembly, wiring and software programming. For details contact Patrick at Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast, BT5 4GX. Phone 028 9073 8897, Fax 028 9073 1802, E-mail agar@argonet.co.uk.

**FREE PROTOTYPE PRINTED CIRCUIT BOARDS!** Free prototype p.c.b. with quantity orders. Call Patrick on 028 9073 8897 for details. Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast BT5 4GX.

**WANTED OLD JVC 7300EK TOP LOAD VCR** for clock/timer parts. Phone 01202 432973.

- Prototype PCB manufacture
- PCB's designed from schematics
- Circuit design & construction
- Ideas developed & turned into reality
- Software written for PIC, PC, etc.

**Circuit Innovations** 24 Leasmires Avenue  
Easingwold  
York YO61 3DU  
[www.circuit-innovations.co.uk](http://www.circuit-innovations.co.uk)

**G.C.S.E. ELECTRONIC KITS**, at pocket money prices. S.A.E. for FREE catalogue. SIR-KIT Electronics, 52 Severn Road, Clacton, CO15 3RB, <http://www.geocities.com/sirkituk/index.htm>.

**EDUCATIONAL ELECTRONIC KITS**, GCSE, Physics, Hobbyist. 2 x 1st class stamps for catalogue. Electroteach, PO Box 2594, Cannock, WS12 4YH.  
[www.electroteach.com](http://www.electroteach.com).

**PURCHASING AN AUDIO MIXING DESK.** Specialists in custom built, fully modular mixing desks. For hospital radio, talking newspapers, shopping centres, amateur dramatic groups, theatres etc. To see our products visit us at <http://www.partridgeelectronics.co.uk> or contact us for our latest catalogue including all sub-units for self-build. Partridge Electronics, 54-56 Fleet Road, Benfleet, Essex, SS7 5JN. Phone 01268 793256. Fax 01268 565759.

**BUMPER COMPONENT PARCEL**, can contain l.e.d.s, transistors, switches, i.c.s etc. £3.95 + £1.35 postage; large parcel £5.65 + £1.65 postage. TM Industries, 2 The Square, Skillington, Grantham NG33 5HB.

**VALVES AND ALLIED COMPONENTS IN STOCK** - please ring for free list. Valve equipment repaired. Geoff Davies (Radio). Phone 01788 574774.

**1995 - 1999 EVERYDAY PRACTICAL ELECTRONICS MAGAZINES** for sale including folders, plus some spare magazines. Some missing. £150. Contact Tony, 93 Galloway Road, Hamworthy, Poole, Dorset.

**WANTED: SL561 AUDIO PRE-AMP CHIP.** Probably Plessey, Adrian, 6 Aidan Grove, Ellington, NE61 5HJ.

**EPE NET ADDRESSES**

**EPE FTP site:** <ftp://ftp.epemag.wimbome.co.uk>  
Access the FTP site by typing the above into your web browser, or by setting up an FTP session using appropriate FTP software, then go into quoted sub-directories:  
PIC-project source code files: /pub/PICS  
PIC projects each have their own folder; navigate to the correct folder and open it, then fetch all the files contained within. *Do not try to download the folder itself!*  
EPE text files: /pub/docs  
*Basic Soldering Guide:* solder.txt  
*Ingenuity Unlimited* submission guidance: ing\_unit.txt  
New readers and subscribers info: epe\_info.txt  
Newsgroups or Usenet users advice: usenet.txt  
Ni-Cad discussion: nicadfaq.zip and nicad2.zip  
Writing for EPE advice: write4us.txt

You can also enter the FTP site via the link at the top of the main page of our home site at: <http://www.epemag.wimbome.co.uk>  
Shop now on-line: [www.epemag.wimbome.co.uk/shopdoor.htm](http://www.epemag.wimbome.co.uk/shopdoor.htm)

Ensure you set your FTP software to ASCII transfer when fetching text files, or they may be unreadable.  
Note that any file which ends in .zip needs unzipping before use. Unzip utilities can be downloaded from:  
<http://www.winzip.com> or  
<http://www.pkware.com>

## TRAIN TODAY FOR A BETTER FUTURE

Now you can get the skills and qualifications you need for career success with an ICS Home Study Course. Learn in the comfort of your own home at the pace and times that suit you. ICS is the world's largest, most experienced home study school. Over the past 100 years ICS have helped nearly 10 million people to improve their job prospects. Find out how we can help YOU. Post or phone today for FREE INFORMATION on the course of your choice

Electrical Contracting & Installation  
Electrical Engineering  
C&G/ICS Basic Electronic Engineering  
C&G/ICS Basic Mechanical Engineering  
TV and Video Servicing  
Radio and Hi-Fi Servicing  
Refrigeration Heating & Air Conditioning  
Motorcycle Maintenance

**FREEPHONE 0500 581 557**

Or write to: International Correspondence Schools, FREEPOST 882, 8 Elliot Place, Clydeside Skypark, Glasgow, G3 8PR. Tel: 0500 581 557 or Tel/Fax: Dublin 285 2533

Please send me my Free Information on your Electronics Courses.

Mr/Ms/Ms/Miss (BLOCK CAPITALS PLEASE) \_\_\_\_\_ Date of Birth / /

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Occupation \_\_\_\_\_ Tel. No. \_\_\_\_\_

From time to time, we permit other carefully screened organisations to write to you about products and services. If you would prefer not to hear from such organisations please tick box  Dept. ZEEVC1H1



MANUFACTURER OF HIFI AUDIO MODULES AND TOROIDAL TRANSFORMERS SINCE 1971

CONTACT US NOW FOR A FREE CATALOGUE

**ILP DIRECT LTD.**

SPONG LANE, ELMSTED, ASHFORD, KENT TN25 5JU  
TEL +44 1233 750481 FAX +44 1233 750578

VISA



## Bowood Electronics Ltd

Suppliers of Electronic Components

Batteries, Buzzers, Capacitors, Connectors, Diodes, Cases, Ferrites, Fuses, Heatshrink, ICs, Inverters, L.E.D.s, P.C.B., Potentiometers, Power Supplies, Presets, Rectifiers, Relays, Resistors, Soldering Equipment, Stripboard, Switches, Test Meters, Thermistors, Thyristors, Tools, Transistors, Triacs...

Catalogue available NOW

Send 41p stamp or visit our website

Website: <http://www.bowood-electronics.co.uk>  
sales@bowood-electronics.co.uk



Mail Order Only  
7 Bakewell Road, Baslow, Derbyshire, DE45 1RE, UK  
Telephone/Fax: 01246 583777

## Crotech POWER Value for Money

•European Design  
•IEC 1010-1 & CE

•>50K units sold  
•Prices that Please

### ZEBRA

DC Lab Supplies  
(With Two 3Digit DPM's)

ZS3202	0-32V / 0-2A	£ 93/-
ZS3203	0-32V / 0-3A	£ 112/-
ZS3205	0-32V / 0-5A	£ 136/-
ZT3203	0-32V / 0-3A	£ 232/-
	0-32V / 0-2A	£ 232/-
	5V/3A	
ZT3205	0-32V / 0-5A	£ 323/-
	0-32V / 0-5A	£ 323/-
	5V/3A	

### 1KW

DC Lab Supplies  
3U High 19" Rack Adaptable  
(With Two 3Digit DPM's)

L1650	0-16V / 0-50A	£ 645/-
L3220	0-32V / 0-20A	£ 593/-
L3230	0-32V / 0-30A	£ 904/-
L6410	0-64V / 0-10A	£ 645/-
L6415	0-64V / 0-15A	£ 1122/-
L1285	0-128V / 0-5A	£ 818/-
L1288	0-128V / 0-8A	£ 1232/-

Prices are excluding VAT & Delivery Custom Units Available on Request

Crotech Instruments Ltd.  
Unit A1, Faraday Road, Newbury, Berks, RG14 2AD  
Tel: 01635 550789 Email: sales@crotech.co.uk

[www.crotech.co.uk](http://www.crotech.co.uk)

**Area Distributors Wanted**

## SSE ADJUSTABLE MULTIMETER TESTER STAND

Solid State Electronics (UK)

Does your meter keep on falling over - even if it is fitted with a plastic holster? Then get a sturdy, metal SSE Test Meter Holder TMH2001

SAFE & SECURE • EASY TO USE • CONVENIENT SUPPORT

PATENT PENDING



For FREE information contact:  
Solid State Electronics (UK)  
6 The Orchard  
Bassett Green Village  
Southampton  
SO16 3MA  
Tel: 023 80769598  
Fax: 023 80768315  
solidstate@ssejim.co.uk  
www.ssejim.co.uk

PAYMENT ONLY BY:  
Cash, Postal Order or  
Cheque (prices include P & P)

**INTRODUCTORY SPECIAL PRICE**

Two Models Available:  
LARGE £13.00  
SMALL £12.00

We stock thousands of products - send now for our FREE catalogue. Telephone, fax, email or write today!



LOW PRICES!

## Specialist Mail Order Supplier Of Electronic Components

Power Supplies • Surplus Bargains  
Electronic Components & Equipment  
Tools • Valve Radio Kits • Etc

Delivered direct from our new warehouse and distribution facility in Brentwood, Essex

48 pages filled with useful tools, electronic kits, books, hardware, batteries, etc, etc

Visit our website: [www.greenweld.co.uk](http://www.greenweld.co.uk)


**GREENWELD**

Greenweld Limited  
Unit 24 Horndon Industrial Park  
West Horndon - Brentwood  
Essex CM13 3XD  
Tel: 01277 811042 Fax: 01277 812419  
Email: [service@greenweld.co.uk](mailto:service@greenweld.co.uk)  
Office Hours: Monday - Friday 08.00 to 17.00

## N. R. BARDWELL LTD (Est. 1948)

100	Signal Diodes 1N4148	£1.00	80	Asstd capacitors electrolytic	£1.00
75	Rectifier Diodes 1N4001	£1.00	80	Asstd. capacitors 1nF to 1µF	£1.00
50	Rectifier Diodes 1N4007	£1.00	200	Asstd. disc ceramic capacitors	£1.00
10	WOT Bridge Rectifiers	£1.00	50	Asstd. Steel Presets (sm, stand, ceramic)	£1.00
10	555 Timer I.C.s	£1.00	50	Asstd. RF chokes (inductors)	£1.00
4	741 Op Amps	£1.00	50	Asstd. grommets	£1.00
50	Assorted Zener Diodes 400mW	£1.00	80	Asstd. solder tags, p/conn, terminals	£1.00
12	Assorted 7-segment Displays	£1.00	10	Asstd. crystals - plug in	£1.00
25	5mm l.e.d.s, red, green or yellow	£1.00	8	Asstd. diil switches	£1.00
25	3mm l.e.d.s, red, green or yellow	£1.00	20	Miniature slide switches sp/co	£1.00
75	5mm l.e.d.s, green, 6-5mm eggs	£1.00	100	Asstd. beads (ceramic, teflon, fish spine)	£1.00
50	Axial l.e.d.s, 2mcd red Diode Package	£1.00	80	Asstd. small stand offs, lithroughs etc	£1.00
25	Asstd. High Brightness l.e.d.s, var coats	£1.00	30	Asstd. diil sockets up to 40 way	£1.00
20	BC182L Transistors	£1.00	10	TV coax plugs, plastic	£1.00
25	BC212L Transistors	£1.00	40	metres very thin connecting wire, red	£1.00
30	BC237 Transistors	£1.00	20	1in. glass reed switches	£1.00
20	BC327 Transistors	£1.00	100	Any one value 1/4W 5% cf resistors range	£1.00
30	BC328 Transistors	£1.00	1R to 10M		£0.45
30	BC547 Transistors	£1.00	10	7912 Voltage Regulators	£1.00
20	BC547B Transistor	£1.00			
30	BC548 Transistors	£1.00			
30	BC549 Transistors	£1.00			
25	BC557 Transistors	£1.00			
30	BC558 Transistors	£1.00			
30	BC559 Transistors	£1.00			
20	2N3904 Transistors	£1.00			
100	1nf 50V wkg Axial Capacitors	£1.00			
100	4N7 50V wkg Axial Capacitors	£1.00			

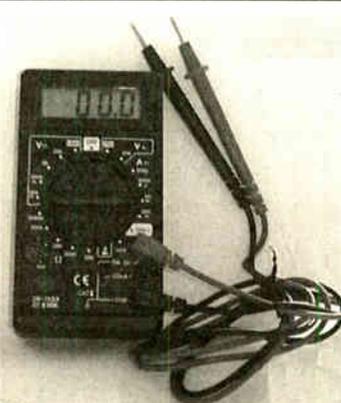288 Abbeydale Road, Sheffield S7 1FL  
Phone: 0114 255 2886 ★ Fax: 0114 255 5039  
e-mail: [sales@bardwells.co.uk](mailto:sales@bardwells.co.uk) ★ Web: [www.bardwells.co.uk](http://www.bardwells.co.uk)  
Prices include VAT. Postage £1.65  
44p stamp for lists or disk



## DIGITAL TEST METER

Built-in transistor test socket and diode test position.  
DC volts 200mV to 1000V.  
AC volts 200V to 750V.  
DC current 200mA to 10A.  
Resistance 200 ohms to 2000K ohms.

**£5.99** incl. VAT

**FREE 240-page  
colour catalogue**

Great value for Speakers, Microphones, Headphones, Aerials, Transmitters, TV Amps, Plugs, Sockets, Leads, CD Storage Cases, CCTV, Security, Connectors, Adaptors, Switch Boxes, Gadgets, Disco Lighting & Effects, Mixers, Amplifiers, Turntables, Musicians' Leads, Car Audio, Test Equipment, Hobby Kits, Computer Leads & Accessories, Power Supplies, Inverters, Transformers, Battery Chargers, Tools, Soldering, Switches, Fuses, Indicators, Cable & Wire, Crossovers, Speaker Hardware, PA Amps, and a great deal more... all for the price of a stamp.


**SKY ELECTRONICS**  
Tel: 020 8450 0995  
Fax: 020 8208 1441

## Sky Electronics

40-42 Cricklewood Broadway London NW2 3ET  
Tel: 020 8450 0995 Fax: 020 8208 1441  
[www.skyelectronics.co.uk](http://www.skyelectronics.co.uk)

The Catalogue is FREE to callers or send stamps to the value of £1.85 to cover postage.

# ELECTRONICS 2001

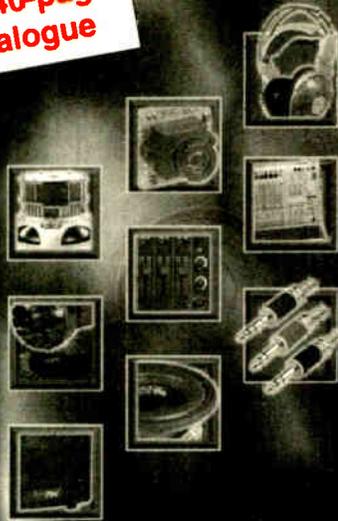

2000  
2001

## SHERWOOD ELECTRONICS

**FREE COMPONENTS**

Buy 10 x £1 Special Packs and choose another one FREE

SP1	15 x 5mm Red LEDs	SP133	20 x 1N4004 diodes
SP2	12 x 5mm Green LEDs	SP134	15 x 1N4007 diodes
SP3	12 x 5mm Yellow LEDs	SP136	3 x BFY50 transistors
SP6	15 x 3mm Red LEDs	SP137	4 x W005 1.5A bridge rectifiers
SP7	12 x 3mm Green LEDs	SP138	20 x 2.2/63V radial elect. caps.
SP8	10 x 3mm Yellow LEDs	SP140	3 x W04 1.5A bridge rectifiers
SP10	100 x 1N4148 diodes	SP142	2 x CMOS 4017
SP11	30 x 1N4001 diodes	SP143	5 Pairs min. crocodile clips (Red & Black)
SP12	30 x 1N4002 diodes	SP145	6 x ZTX300 transistors
SP20	20 x BC184 transistors	SP146	10 x 2N3704 transistors
SP21	20 x BC212 transistors	SP147	5 x Stripboard 9 strips x 25 holes
SP23	20 x BC549 transistors	SP151	4 x 8mm Red LEDs
SP24	4 x CMOS 4001	SP152	4 x 8mm Green LEDs
SP25	4 x 555 timers	SP153	4 x 8mm Yellow LEDs
SP26	4 x 741 Op.Amps	SP154	15 x BC548 transistors
SP28	4 x CMOS 4011	SP156	3 x Stripboard, 14 strips x 27 holes
SP29	3 x CMOS 4013	SP160	10 x 2N3904 transistors
SP31	4 x CMOS 4071	SP161	10 x 2N3906 transistors
SP36	25 x 10/25V radial elect. caps.	SP165	2 x LF351 Op.Amps
SP37	15 x 100/35V radial elect. caps.	SP166	20 x 1N4003 diodes
SP39	10 x 470/16V radial elect. caps.	SP167	6 x BC107 transistors
SP40	15 x BC237 transistors	SP168	6 x BC108 transistors
SP41	20 x Mixed transistors	SP172	4 x Standard slide switches
SP42	200 x Mixed 0.25W C.F. resistors	SP175	20 x 1/63V radial elect. caps.
SP47	5 x Min. PB switches	SP177	10 x 1A 20mm quick blow fuses
SP102	20 x 8-pin DIL sockets	SP182	20 x 4.7/63V radial elect. caps.
SP103	15 x 14-pin DIL sockets	SP183	20 x BC547 transistors
SP104	15 x 16-pin DIL sockets	SP187	15 x BC239 transistors
SP105	4 x 74LS00	SP191	3 x CMOS 4023
SP109	15 x BC557 transistors	SP192	3 x CMOS 4066
SP111	12 x Assorted polyester caps	SP193	20 x BC213 transistors
SP112	4 x CMOS 4093	SP195	3 x 10mm Yellow LEDs
SP115	3 x 10mm Red LEDs	SP197	6 x 20 pin DIL sockets
SP116	3 x 10mm Green LEDs	SP198	5 x 24 pin DIL sockets
SP118	2 x CMOS 4047	SP199	5 x 2.5mm mono jack plugs
SP120	3 x 74LS93		
SP124	20 x Assorted ceramic disc caps		
SP130	100 x Mixed 0.5W C.F. resistors		
SP131	2 x TL071 Op.Amps		

**RESISTOR PACKS - C.Film**

RP3	5 each value - total 365 0.25W	£2.95
RP7	10 each value - total 730 0.25W	£4.20
RP10	1000 popular values 0.25W	£5.95
RP4	5 each value-total 365 0.5W	£3.90
RP8	10 each value-total 730 0.5W	£6.55
RP11	1000 popular values 0.5W	£8.25

**2001 Catalogue now available £1 inc. P&P or FREE with first order. P&P £1.25 per order. NO VAT**  
Orders to:  
**Sherwood Electronics,**  
7 Williamson St., Mansfield,  
Notts. NG19 6TD.

## COVERT VIDEO CAMERAS

Black and White Pin Hole Board Cameras with Audio. Cameras in P.I.R., Radios, Clocks, Briefcases etc. Transmitting Cameras with Receiver (Wireless).  
Cameras as above with colour.  
Audio Surveillance Kits and Ready Built Units, Bug Detector etc.

## A.L. ELECTRONICS

Please phone **0181 203 6008** for free catalogue.  
Fax **0181 201 5359**

E-mail: [surveillance@btclick.com](mailto:surveillance@btclick.com) [www.uspy.com](http://www.uspy.com)  
New DTI approved Video Transmitters and Receivers (Wireless)  
Major credit cards now taken

## ADVERTISERS INDEX

A.L. ELECTRONICS	676
ANTEX	624
N. R. BARDWELL	675
BITZ TECHNOLOGY	665
B.K. ELECTRONICS	Cover (iii)/633
BOWOOD ELECTRONICS	675
BULL ELECTRICAL	Cover (ii)
CHEVET SUPPLIES	659
CRICKLEWOOD ELECTRONICS	659
CROTECH INSTRUMENTS	675
CROWN HILL ASSOCIATES	637
DISPLAY ELECTRONICS	606
EPTSOFT	Cover (iv)
ESR ELECTRONIC COMPONENTS	614
FOREST ELECTRONIC DEVELOPMENTS	634
GREENWELD	675
ICS	675
ILP DIRECT	675
J&N FACTORS	611
JPG ELECTRONICS	659
LABCENTER	621
MAGENTA ELECTRONICS	612/613
MILFORD INSTRUMENTS	625
NATIONAL COLLEGE OF TECHNOLOGY	655
PICO TECHNOLOGY	641
QUASAR ELECTRONICS	608/609
SERVICE TRADING CO	659
SHERWOOD ELECTRONICS	676
SKY ELECTRONICS	676
SLM (MODEL) ENGINEERS	610
SOLID STATE ELECTRONICS (UK)	675
SQUIRES	610
STEWART OF READING	610
SUMA DESIGNS	651

**ADVERTISEMENT MANAGER: PETER J. MEW**  
**ADVERTISEMENT OFFICES:**

EVERYDAY PRACTICAL ELECTRONICS, ADVERTISEMENTS,  
MILL LODGE, MILL LANE, THORPE-LE-SOKEN,  
ESSEX CO16 0ED.  
Phone/Fax: (01255) 861161

For Editorial address and phone numbers see page 615



# POWER AMPLIFIER MODULES-LOUDSPEAKERS-MIXERS 19 INCH STEREO AMPLIFIERS-ACTIVE CROSS/OVERS.

\* PRICES INCLUDE V.A.T.  
\* PROMPT DELIVERY

## OMP MOS-FET POWER AMPLIFIERS HIGH POWER, TWO CHANNEL 19 INCH RACK

10,000's  
SOLD  
TO PRO  
USERS



### THE RENOWNED MXF SERIES OF POWER AMPLIFIERS

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)

MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS ARE R.M.S. INTO 4 OHMS, WITH BOTH CHANNELS DRIVEN.  
FEATURES:- \* Independent power supplies with two toroidal transformers  
\* Twin L.E.D. Vu Meters \* Level controls \* Illuminated on/off switch \* Jack / XLR inputs  
\* Speakon Outputs \* Standard 775mV inputs \* Open and Short circuit proof \* Latest Mos-Fets  
for stress free delivery into virtually any load \* High slew rate \* Very low distortion \* Aluminium cases \* MXF600 & MXF900 fan cooled with D.C. Loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC

SIZES:-  
MXF200 W19" D11" H3 1/2" (2U)  
MXF400 W19" D12" H5 1/2" (3U)  
MXF600 W19" D13" H5 1/2" (3U)  
MXF900 W19" D14" H5 1/2" (3U)

PRICES:- MXF200 £175.00 MXF400 £233.85  
MXF600 £329.00 MXF900 £449.15  
SPECIALIST CARRIER DEL £12.50 Each



## OMP XO3-S STEREO 3 WAY ACTIVE CROSSOVER SWITCHABLE 2-WAY



BASS MID TOP CONFIGURED 3 WAY  
BASS/MID TOP 2 WAY BASS/MID COMBINED  
BASS MID/TOP 2 WAY MID/TOP COMBINED

### FEATURES:-

Advanced 3-Way Stereo Active Cross-Over (Switchable two way), housed in a 19" x 1U case. Each channel has three level controls: Bass, Mid & Top. The removable front face allows access to the programmable DIL switches to adjust the cross-over frequency. There are two versions available: -XO3-S Bass-Mid 125/250/500Hz, Mid-Top 1.8/3/5kHz, all at 24 dB per octave. XO3 Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5kHz, all at 24 dB per Octave. Please make sure you ask for the correct model when ordering. The 2/3 way selector switches are also accessed by removing the front face. Each stereo channel can be configured separately. Bass Invert Switches are incorporated on each channel. Nominal 775mV input/output. Fully compatible with the OMP Rack Amplifier and Modules.

BOTH MODELS PRICED AT :- £117.44 + £5.00 P&P

## TEST AND MEASUREMENT Kenwood CS-4125 20Mhz Oscilloscope



Inheriting the design concept of the higher-version models the CS-4100 series 2-channel oscilloscopes provide excellent performance for general purpose applications. They feature high quality components ensuring long term reliability plus relay attenuators which minimise the need for re-calibration. The CS-4100 Series with excellent cost efficiency were designed to meet the needs of engineers over the widest range of applications. CS-4125 Price : £351.33 Free Delivery

## Kenwood FGE-1202 Programmable function generator

The FGE-1202 is a microprocessor controlled programmable function generator providing a full featured, accurate generator in compact low cost instrument. The design incorporates an LED back lite 16x2 LCD giving clear easily read characters. The main output has wave-shapes of sine, square, triangle and DC. The output frequency is continuously displayed along with the current edit parameters. As standard an RS-232 interface allowing remote control via a computer. Output has offset, amplitude and symmetry control. An external input allows for external sweep and modulation (AM and FM). Internal sweep is also provided with a sweep rate of 20mS to 20Seconds with sweep modes log and lin.



FGE-1202  
Price : £280.83  
Free Delivery

For full specifications and more equipment view our web site at [www.bkelec.com](http://www.bkelec.com) and press the Test & Measurement button

## 100 WATT ACTIVE SUB BASS AMPLIFIER PANEL



AN ACTIVE SUB BASS AMPLIFIER WITH A TRUE 100W RMS OUTPUT. SUPERB CONSTRUCTION WITH THE FACILITIES TO INTEGRATE SEEMLESSLY INTO MOST HI-FI OR HOME CINEMA SETUPS. USE THIS PANEL PLUS ONE OF OUR LOUDSPEAKERS TO MAKE YOUR OWN SUB WOOFER THAT WILL MATCH OR BEAT MOST COMMERCIALY AVAILABLE SUB WOOFERS.

FEATURES:- \* 100W RMS INTO 8 OHMS \* HIGH AND LOW LEVEL INPUTS \* TOROIDAL TRANSFORMER \* SHORT CIRCUIT PROTECTION \* D.C. SPEAKER PROTECTION \* FREQUENCY ROLL OFF, LOWER 10Hz, UPPER 60Hz TO 240Hz (FULLY ADJUSTABLE) \* AC3 COMPATIBLE FILTER CAN BE BYPASSED FOR 5-1 FORMATS. \* AIRTIGHT CONSTRUCTION \* TENS OF THOUSANDS OF OUR PANELS ALREADY IN USE. \* COMPLETE WITH LEADS

SPECIFICATIONS:- \* POWER 100W RMS @ 8 OHMS \* FREQ RESP. 10Hz 15KHz -3dB \* DAMPING FACTOR >200 \* DISTORTION 0.05% \* S/N A WEIGHTED >100dB \* SUPPLY 230V A.C. \* WEIGHT 2.7Kg \* SIZE H254 X W254 X D94mm

THERE ARE 2 VERSIONS OF THE ABOVE PANEL AVAILABLE :- **BSB100/8 8 OHM VERSION** BSB100/4 4 OHM VERSION BOTH PANELS ARE PRICED AT £117.44 + £5.00 P&P INCL. V.A.T

## FLIGHTCASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of latest loudspeaker technology and enclosure designs. All models utilise high quality studio cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands. The FC15-300 incorporates a large 16 X 6 inch horn. All cabinets are fitted with the latest Speakon connectors for your convenience and safety. Five models to choose from.

WEDGE MONITOR



PLEASE NOTE POWER RATINGS QUOTED ARE IN WATTS R.M.S. FOR EACH INDIVIDUAL CABINET ALL ENCLOSURES ARE 8 OHMS

15-15 Inch speaker  
12-12 Inch speaker

ibl FC15-300 WATTS Freq Range 35Hz-20kHz, Sens 101dB, Size H695 W502 D415mm

Price:- £299.00 per pair

ibl FC12-300 WATTS Freq Range 45Hz-20kHz, Sens 96dB, Size H600 W405 D300mm

Price:- £249.00 per pair

ibl FC12-200 WATTS Freq Range 40Hz-20kHz, Sens 97dB, Size H600 W405 D300mm

Price:- £199.00 per pair

ibl FC12-100 WATTS Freq Range 45Hz-20kHz, Sens 100dB, Size H546 W380 D300mm

Price:- £179.00 per pair

ibl WM12-200 WATTS Freq Range 40Hz-20kHz, Sens 97dB, Size H418 W600 D385mm

Price:- £125.00 Each

SPECIALIST CARRIER DEL:- £12.50 per pair, wedge monitor £7.00 each  
Optional Metal Stands PRICE:- £49.00 per pair Delivery:- £6.00

## 10 INCH AND 12 INCH 100W RMS SUB BASS LOUDSPEAKERS

TWO SUPERB SUB WOOFER LOUDSPEAKER DRIVERS TO ACCOMPANY OUR SUB BASS AMPLIFIER PANEL BELOW. BOTH DRIVERS OFFER GOOD BASS RESPONSE AT A REASONABLE COST. THE BSB12-100 HAS BEEN USED FOR MANY YEARS IN AN AWARD WINNING SUB BASS SYSTEM

FOR THSM SPECIFICATIONS VIEW OUR WEB SITE AT <http://www.bkelec.com>

12 INCH LOUDSPEAKER BSB12-100 10 INCH LOUDSPEAKER BSB10-100

12 INCH LOUDSPEAKER	BSB12-100	10 INCH LOUDSPEAKER	BSB10-100
POWER	100W	POWER	100W
IMPEDANCE	8 OHMS	IMPEDANCE	8 OHMS
SENSITIVITY	90dB	SENSITIVITY	89dB
WEIGHT	3.0Kg	WEIGHT	2.3Kg
PRICE	£24.95	PRICE	£19.99
CARRIAGE	£5.00	CARRIAGE	£5.00

## OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc.. When comparing prices, NOTE that all models include toroidal power supply, integral heatsink glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

### THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS

OMP/MF 100 Mos-Fet Output Power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. 110dB, Size 300 x 123 x 60mm. Price:- £42.85 + £4.00 P&P

OMP/MF 200 Mos-Fet Output Power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Size 300 x 155 x 100mm. Price:- £66.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output Power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Size 330 x 175 x 100mm. Price:- £83.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output Power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti Thump Delay, Size 385 x 210 x 105mm. Price:- £135.85 + £6.00 P&P

OMP/MF 1000 Mos-Fet Output Power 1000 watts R.M.S. into 2 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti Thump Delay, Size 422 x 300 x 125mm. Price:- £261.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS. STANDARD - INPUT SENS 500mV/BANDWIDTH 100kHz OR PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BANDWIDTH 50kHz ORDER STANDARD OR PEC

DELIVERY CHARGES:- PLEASE INCLUDE AS ABOVE, TO A MAXIMUM AMOUNT £30.00. OFFICIAL ORDERS FROM SCHOOL, COLLEGES, GOVT. PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER. CREDIT CARD ORDERS ACCEPTED BY POST PHONE OR FAX.



# B.K. ELECTRONICS

UNIT 1 COMET WAY, SOUTHEND-ON-SEA,  
ESSEX. SS2 6TR.

TEL.: 01702-527572 FAX.: 01702-420243

Web:- <http://www.bkelec.com> E-Mail sales@bkelec.com

REF D4

# 'Electronics and Computing Principles V7'

## '95, '98, NT or 2000 Principles V7'

Interested in PIC micro controllers, this is the software for you!

The screenshot displays the 'Electronics and Computing Principles V7' software interface. The main window is titled 'PIC16F84 ARCHITECTURE: PIC16F84 Block Diagrams'. It features a schematic of the PIC16F84 microcontroller on the left, showing pins RB0-RB7, RA0-RA4, and oscillators Osci and Osci2. The central window is titled 'PIC16F84 BYTE-ORIENTATED INSTRUCTIONS: MOVF f,d: Move f'. It shows the instruction syntax '[label] MOVF f,d', its encoding (00 1000 dff ffff), and a description: 'The contents of register 'f' are moved to destination 'd'. If 'd' is 0, destination is W register. If 'd' is 1, the destination is file register 'f' itself. d = 1 is useful to test a file register since status flag 'Z' is affected.' Below this, it shows the W register (0Dh) and the status register (Zero = 0). An example shows the instruction 'MOVF FSR, 0' being executed, resulting in 'F = 0Dh'. The right-hand window shows a memory map with addresses from 00h to 15h and a register window showing 'BR 7 d = 1'. The bottom of the window shows a table of RETLW instructions and their effects on the W register.

Visit [www.eptsoft.com](http://www.eptsoft.com) or telephone for full details, including a description by Robert Penfold.

Electronics and Computing Principles V7 comprises more than a thousand main topics, covering AC and DC theory, Transistors, Op-Amps, Electrical, Digital techniques, Micro processors and Mathematics. PLUS: Components and Equipment Picture dictionary, SAQ's, Electronics toolbox etc, and more...

Also included is an enormous amount of interactive technical information about PIC micro controllers and the full instruction set.

Schools, colleges and industry use V7 alongside their own programmers enabling students and engineers to play with ALL the Byte, Bit and Literal instructions to explore their effect. V7 is listed on the Microchip university web site as a training resource for PICs.

FREE programming software to accompany EPV7 is available from the Microchip web site. Details provided.

Personal user £99.95 +VAT  
Education\* £299.95 +VAT  
(\* Includes unlimited multi-user site licence.)

For beginners our PIC topics start with an interactive introduction to the PIC program structure and basic operation with a summary of the complete instruction set and code examples.

PIC16F84 Architecture is shown whereby a context sensitive description of its action is displayed. Every PIC operation is discussed (even the more advanced are explained). Just as it occurs inside a PIC, we show it in colour on the screen.

PIC16C71 A/D functions are given the same treatment, along with a full explanation of the A/D conversion process, even the calculations.

A visually attractive set of Windows designed to help you quickly and easily get started in the development of your own PIC programs.

More than 80 PIC topics and it's still only a tiny part of the complete V7 package.

eptsoft limited. Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ.  
Tel: +44 (0)1376 514008. Fax: +44 (0)870 0509660. Email: [info@eptsoft.com](mailto:info@eptsoft.com).  
Switch, Delta, Visa and MasterCard accepted.  
No additional postage or airmail charges.