

**THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS**

**EVERYDAY**

**MAY 2002**

**PRACTICAL**

# **ELECTRONICS**

**£2.85**

**PIC  
BIG DIGIT  
DISPLAY**  
For score-boards, etc.

Special Series  
**SIMPLE AUDIO  
CIRCUITS**  
A selection of  
pick-n-mix  
projects



**WASHING  
READY INDICATOR**  
Has the machine finished?

PLUS  
**New Technology Update  
Net Work • News**



<http://www.epemag.wimborne.co.uk>

**YUASA ENDURANCE 6V 100AH** sealed lead acid batteries, £59 each or 10 for £499.  
**GAS MASKS RUSSIAN**, new and boxed standard NATO filter, £39.  
**LOW COST NIGHT VISION** system, Russian handheld complete with infra-red illuminator, 100m range. Runs on 2 AA batteries, just £109.95.  
**COBRA NIGHT VISION** equipment also stocked, more info on our web site at [www.cobra-optics.co.uk](http://www.cobra-optics.co.uk).

**ELECTRIC SCOOTERS** 18hp, 24V motor, 6 hour charge time, 22kg weight, max load 90kg, running time up to 1 hour, range 15km, 8.5A motor, 24V, direct drive. Our Price £229.95. Ref ESCOOT.  
**VOICE CHANGERS** Hold one of these units over your phone mouthpiece and you can adjust your voice using the controls on the unit. Battery operated, £15. Ref CC3.  
**EMMINENCE LOUDSPEAKERS** 12in. dia., 50W nom, 100W peak, 16 ohm impedance. Pack of 4 just £39.95. Ref SPEAK39.  
**PIR SECURITY SWITCHES** These brand new swivel mounting PIR units will switch up to 2 kilowatts. Adjustable sensitivity, light level and time delay (9 seconds to 10 minutes), 15m detection range, mains operated, waterproof, £5.99 Ref PIR1PACK or a pack of 5 for £22.95 Ref PIR5PACK or 10 for £39.95 Ref PIR10PACK.

**12V 18AH SEALED LEAD-ACID BATTERIES**, new and boxed, unused, pack of 4 £69.95 Ref CYC7 or £21.95 each Ref CYC6.  
**12V 6.5AH SEALED LEAD-ACID BATTERIES**, new and boxed, pack of 5 £34.95 Ref CYC65A or individually at £8.99 Ref CYC65B.

**12V 12Ah SEALED LEAD-ACID BATTERIES**, 100mm x 150mm x 95mm, 4kg, £15 each Ref SSLB.  
**6V 100AH SEALED LEAD-ACID BATTERIES**, 200mm x 208mm x 238mm, £59.

**SEALED LEAD-ACID CHARGER AND FLOAT CHARGER**. Complete unit will charge 12V lead acids and maintain them with an automatic trickle charge. Charger on its own is £15 Ref LAC or charger and a 12V 12Ah battery (all fully cased) is £25 Ref ACB.  
**AERIAL PHOTOGRAPHY KIT**. This rocket comes with a built-in camera! It flies up to 500 feet (150m), turns over and takes an aerial photograph of the ground below. The rocket then returns with its film via its parachute. Takes 110 film. Supplied with everything including a launch pad and 3 motors (no film). £29.98 Ref Astro.

**BUILD YOUR OWN WINDFARM FROM SCRAP**. New publication gives step-by-step guide to building wind generators and propellers. Armed with this publication and a good local scrapyard could make you self-sufficient in electricity! £12. Ref LOT81.  
**MAGNETIC CREDIT CARD READERS AND ENCODING INFO**, £9.95. Cased with filelays, designed to read standard credit cards! Complete with control electronics p.c.b. and manual covering everything you could want to know about what's hidden in that magnetic strip on your card! Just £9.95 Ref BAR31.

**77 KILO LIFT MAGNET**. These Samarium magnets measure 57mm x 20mm and have a threaded hole (5/16th UNF) in the centre and a magnetic strength of 2.2 gauss. We have tested these on a steel beam running through the offices and found that they will take more than 170lb. (77kg) in weight before being pulled off. Supplied with keeper. £19.95 ea. Ref MAG77.

**HYDROGEN FUEL CELL PLANS**. Loads of information on hydrogen storage and production. Practical plans to build hydrogen fuel cell (good workshop facilities required). £8 set. Ref FCP1.  
**STIRLING ENGINE PLANS**. Interesting information pack covering all aspects of Stirling engines, pictures of home made engines made from an aerosol can running on a candle! £12 STIR2.

**12V OPERATED SMOKE BOMBS**. Type 3 is a 12V trigger and 3 smoke canisters, each canister will fill a room in a very short space of time! £14.99. Ref SB3. Type 2 is 20 smaller canisters (suitable for mock equipment fires etc.) and 1 trigger module for £29. Ref SB2. Type 1 is a 12V trigger and 20 large canisters. £49. Ref SB1.

**BRAND NEW NATO ISSUE RADIATION DETECTORS, SALE PRICE JUST £69.95**. Current NATO issue standard emergency services unit. Used by most of the world's military personnel. New and boxed. Normal retail price £400. Bull's bargain price just £69.95. Ref PDRM.  
**BASIC GUIDE TO BIO DIESEL**. How to make diesel fuel from used kitchen oil. £6. Ref B10F.

**SAVE ££££s. RCB UNITS**. In-line IEC lead with fitted RC breaker. Installed in seconds. Fit to any computer, monitor, office equipment and make it safe! Pack of 10 just £9.98. Ref LOT5B.  
**INFRA-RED REMOTE CONTROL WATCHES**, £16.99.  
**VIBRATING WATCHES**, vibrate when your phone rings, £16.99.  
**PULSE WATCHES**, display your pulse, £16.99.

[www.quemex.co.uk](http://www.quemex.co.uk)  
**MINIATURE TOGGLE SWITCHES**. These top quality Japanese panel mounting toggle switches measure 35mm x 13mm x 12mm, are 2-pole changeover and will switch 1A at 250V a.c., or 3A at 125V a.c. Complete with mounting washers and nuts. Supplied as a box of 100 switches for £29.95. Ref SWT35 or a bag of 15 for £4.99. Ref SWT34.

**STEPPER MOTORS**. Brand new stepper motors, 4mm fixing holes with 47.14mm fixing centres, 20mm shaft, 6.35mm diameter, 5V/phase, 0.7A/phase, 1.8 deg. step (200 step). Body 56mm x 36mm, £14.99 each. Ref STEP6, pack of 4 for £49.95.  
**BASIC GUIDE TO LOCKPICKING**. New publication gives you an insight! £6. Ref LPK.

**NEW HIGH POWER MINI BUG**. With a range of up to 800 metres and 3 days use from a PP3 this is our top selling bug! Less than 1in. square and a 10m voice pick-up range. £26. Ref LOT102.  
**IR LAMP KIT**. Suitable for CCTV cameras, enables the camera to be used in total darkness! £6. Ref EF138.

**INFRA-RED POWERBEAM**. Handheld battery powered lamp, 4in. reflector, gives out powerful pure infra-red light! Perfect for CCTV use, night sights, etc. £29. Ref PB1.  
**YOUR HOME COULD BE SELF-SUFFICIENT IN ELECTRICITY**. Comprehensive plans with loads of info on designing systems, panels, control electronics etc. £7. Ref PV1.

**200 WATT INVERTERS**, plugs straight into your car cigarette lighter socket and is fitted with a 13A socket so you can run your mains operated devices from your car battery. £49.95. Ref SS66.  
**THE TRUTH MACHINE**. Tells if someone is lying by micro tremors in their voice. battery operated, works in general conversation and on the 'phone and TV as well! £42.49. Ref TD3.

**INFRA-RED FILM**. 6in. square piece of flexible infra-red film that will only allow IR light through. Perfect for converting ordinary torches, lights, headlights etc. to infra-red output using only standard light bulbs. Easily cut to shape. 6in. square. £15. Ref IRF2 or a 12in. square for £29.95. Ref IRF2A.  
**HYDROGEN FUEL CELLS**. Our new hydrogen fuel cells are 1V at up to 1A output, hydrogen input, easily driven from a small electrolysis assembly or from a hydrogen source, our demo model uses a solar panel with the output leads in a glass of salt water to produce the hydrogen! Each cell is designed to be completely taken apart, put back together and expanded to whatever capacity you like (up to 10 watts and 12V per assembly). Cells cost £49. Ref HFC11.

**SMOKE ALARMS**. Mains powered, made by the famous Gent company, easy fit next to light fittings, power point. Pack of 5 £15. Ref SS23, pack of 12 £24. Ref SS24.  
**CCTV CAMERAS FROM £25**. Check out our web site at [www.ctctvstuf.co.uk](http://www.ctctvstuf.co.uk) and [www.home-cctv.co.uk](http://www.home-cctv.co.uk).

**14 WATT SOLAR PANELS**. Amorphous silicon panel fitted in an anodised aluminium frame. Panel measures 3ft. by 1ft. with 3m leads for easy connection. 3ft. x 1ft. solar panel £79. Ref MAG45. Unframed 4 pack, 8-9W (3ft. x 1ft.) £99. Ref SOLX. 35 watts of solar power for just £99. 4 panels, each one 3ft. x 1ft. and producing 8W min., 13V. Pack of four £99. Ref SOLX.

**NEW 12V 12in. SQUARE SOLAR PANEL**. Kevalar backed, 3 watt output, copper strips for easy solder connections. £14.99 Ref 15P42. Pack of four just £39.95. Ref 15P42SP.  
**NEW UNIVERSAL SOLAR CHARGER**. Charges AAAs, AAs, Cs and D-type NiCads. £9.99. Ref UNISOL.

**12V SOLAR POWER WATER PUMP**. Perfect for many 12V d.c. uses, from solar fountains to hydroponics! Small and compact yet powerful, works direct from our 10W solar panel in bright sun. Max HD: 17ft, max flow = 8 Lpm, 1.5A. Ref AC88, £18.99.  
**SOLAR MOTORS**. Tiny motors which run quite happily on voltages from 3V-12V d.c. Works on our 6V amorphous 6in. panels and you can run them from the sun! 32mm dia., 20mm thick. £1.50 each.  
**MAMOD STEAM ENGINES** and a full range of spare parts. Check out [www.mamodspares.co.uk](http://www.mamodspares.co.uk).

**SUPER WIDEBAND RADAR DETECTOR**. Whistler 1630. Detects both radar and laser. X, K and KA bands, speed cameras and all known speed detection systems, 360 degree coverage, front and rear waveguides, 1.1in. x 2.7in. x 4.6in., fits on visor or dash, new low price £99. Ref WH1630. Other models available at [www.radarjunk.co.uk](http://www.radarjunk.co.uk).

**BUG DETECTORS**. A new detector at a sensible price! Detects bugs hidden in rooms, computers etc., between 1-200MHz, adjustable sensitivity, 9V PP3 battery required. £29.95. Ref BDET2.  
**GIANT WEATHER BALLOONS** made by Totex, we blew one up to 7ft, diameter then it popped due to stones on the ground! £13.99. Ref TOTEX.

**PHILIPS VP406 LASER DISC PLAYERS**, sale price just £9.95. Scart output, just put your video disk in and press play, standard audio and video outputs. £9.95. Ref VP406.  
**12V DC SIRENS**. Very loud, suitable for indoors or outdoors, two-tone, 160mm x 135mm, finished in white with bracket. £4.99. Ref SIR2A.

**FREEZER/MAINS FAIL ALARMS**. Designed to fit around the mains cable on a freezer this alarm will sound if the device is unplugged from the mains supply, battery operated, cased, built-in sounder, ideal for TVs, Hi-Fi equipment etc. £7.01. Ref FRE2.  
**BARNET CROSSBOWS**. We stock the entire range of crossbows, check out our web site at [www.xbows.co.uk](http://www.xbows.co.uk).

**HOT AIR BALLOON KITS**. Everything you need to build a 1.7m high, 4.5m in circum, hot air balloon, launch over a small burner or heater. £112.49. Ref HA1.  
**CROOKES RADIOMETER**. Fascinating glass bulb contains blades driven around by the sun. £9.99. Ref SC120BB.  
**GIANT TV OR PC VIEWING SCREEN**. Turn your TV into a super-size screen, converts small screens into a super size 26in. £26.99. Ref SVGA2.

**RADIOSONDES**. Made by Valsala, unused, they measure pressure, temperature and humidity. Model RS80, good stripper at £15. Ref SONDE.  
**AIR WIND POWER MODULE**. Produces nearly 400 watts of power from the wind, 1.4m blade, 12V d.c. output, 3 year warranty, built-in battery regulator. £549. Ref AIR1.

**WORMERIES**. The ideal solution for your kitchen waste! Supplied complete with worms. Turn your rubbish into liquid feed! Two sizes available, small (ideal for 1-2 people), £25.45. Ref WM2, and a large one (ideal for 4 or more), £42.44. Ref WM1.  
**COMPLETE WIRELESS CCTV SYSTEM**. Includes monitor, camera, up to 100m range, audio and video, UK legal, complete with infra-red lights. £169. Ref WMS333.

**PELTIER MODULES**. 56W, 40mm x 40mm, 16V, sealed edges, new and boxed. Supplied with 18-page PelTier design manual featuring circuit designs, design information etc. 1 module and manual is £29.99. Ref PELT1, pack of 4 modules and manual is £99.99. Ref PELT2. The manual on its own is £4. Ref PELT3.  
**DC MOTOR**. 12V d.c., general purpose model motor, 70mm x 50mm, 12V d.c., permanent magnet, 4mm x 25mm shaft. £6. Ref GPM1, pack of 10 is just £40. Ref GPM2.

**180R.P.M. MAINS MOTOR**. Induction type, 90mm x 70mm, 50mm x 5mm shaft, 12A continuous rating, thermal protected. £22. Ref MGM1.  
**LOGIC STATE RELAYS**. P.C.B. mounting, these relays require 3-32V d.c. to operate but will switch up to 3A a.c. mains. Pack of 4 £5. Ref SPEC1B.  
**12V RELAYS**. 2 x 2 c/o 16A contacts p.c.b. mount (will fit Vero), tray of 25 relays for just £9.95. Ref SPEC1.

**VENNER TIME CONTROLS**. Designed to be wired in permanently they will switch up to 16A 240V a.c. motorised with dial and pins. New and boxed. £15. Ref VTS.  
**GYROSCOPES**. We still sell original 1917 design, hours of fun for all the family, complete with stand, string, box and info. £6. Ref EP70.

**INNOVATIONS**. We also sell a wide range of innovative products for the home, these are at [www.seemans.com](http://www.seemans.com).  
**INVERTERS**. Convert 12V d.c. into 240V mains (modified sine wave), 300 watt (150 watt continuous). £59.95. Ref VER3. 600 watt model (330 watt continuous). £79.97. Ref VER4.  
**10 WATT SILICON SOLAR PANEL**, 10 year life, waterproof, 365mm x 365mm x 26mm, 14V, 10W, 1.8kg, framed. £84.99. Ref PAN.

**STICKY LABELS**. Small address labels etc. are very useful and can be ordered online at [www.stickon.co.uk](http://www.stickon.co.uk).  
**RED L.E.D.s**. Hewlett Packard red l.e.d.s, 5V operation, available in a pack of 50 for £8. Ref SS200, or 500 for £29.95. Ref SS201.  
**MICROSOFT TRACKBALL AND MOUSE**. Called the Microsoft Ballpoint this has 4 buttons, a trackball and PS2 connector. Will work with most PCs. £5.99. Ref EP50.

**MAXON WALKIE TALKIES**, up to 2 mile range. UK legal, 300 channel, 2 x walkie talkies, £74.95. Ref Maxon1. Chargers £14. Ref. Maxon, battery packs £12. Ref. Maxonb (otherwise uses AAA batteries).  
**2-WAY MIRROR KIT**. Contains enough material to make up to a 500mm x 2200mm mirror (excl. glass), full instructions. £19.95. Ref WF001.

**.22 AIR RIFLE**. Under lever type, powerful Chinese training rifle, £38.26. Ref A1047, 500 pellets, £2.68. Ref A1091.  
**.22 AIR RIFLE STANDARD TYPE**. Chinese training rifle, on legal limit for air rifles, £29.75. Ref A1040. Pellets £2.68. Ref A1091.  
**SHUT THE BOX**. Check out [www.bullybeef.co.uk](http://www.bullybeef.co.uk) for a range of pub games and magic tricks.

**WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA?** We have collated 1400 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14. Ref EP74.  
**ANICS CO2 GAS POWERED PISTOL**. Russian handheld pistol powered by Sparkies CO2 cylinders (give approx. 70 shots), fires steel BB. Pistol £58.22. Ref AGA101, tub of 1,500 BB shot £5.10. Ref A1015, pack of 5 CO2 cartridges £3.50. Ref GASS.

**33 KILO LIFT MAGNET**. Neodymium, 32mm diameter with a fixing bolt on the back for easy mounting. Each magnet will lift 33 kilos, 4 magnets bolted to a plate will lift an incredible 132 kilos! £15. Ref MAG33. Pack of 4 just £39. Ref MAG33AA.  
**BSA METEOR AIR RIFLE**. UK made. 22 rifle, top quality professional air rifle. £84.15. Ref BSAMET 500 Lazapell pellets £5. Ref LAZAPELL.

**MAMOD 1313 TEIA TRACTION ENGINE**. Attractive working model of traditional steam engine. £85. Ref 1313.  
**MAMOD STEAM ROADSTER** (white), magnificent working steam model car. £112. Ref 1319.  
**MAMOD STEAM WAGON**. Working model steam wagon finished in blue. £112. Ref 1318. Brown version (with barrels), £122. Ref 1450.

**POCKET SPY MONOCULAR**. Clever folding monocular with 8 x 21 magnification, made by Helios, with case. £14.99. Ref MONOC.  
**KEVLAR BRITISH ARMY HATS**. Broken or missing straps, hence just £8 each. Ref KEV99.  
**CCTV SYSTEMS**, £24.99. Complete with camera, 20 metres of cable, p.s.u. and info simple connection to scart. £24.99. Ref CCTVCAM2.

**FM BROADCAST BAND HIGH POWER TRANSMITTERS** can be viewed and bought online at [www.veronica-kits.co.uk](http://www.veronica-kits.co.uk).  
**TONER CARTRIDGES FOR COPIERS AND PRINTERS** can be bought online at [www.nationaltoners.co.uk](http://www.nationaltoners.co.uk).  
**VELOSOLEX**. Traditional French style two-stroke moped (engine over front wheels), black only. £695. Ref VELO. Delivered direct in a box, you need to fit the pedals etc. then register it with your local DVLC.

**HYDROPONIC GROWING SYSTEMS**. Complete, everything you need apart from plants and light, contains grow tank, nutrients, pump, tester etc. GT205 710mm x 390mm, NFT system, £31.45. Ref GT205. GT424 1070mm x 500mm, NFT system, £58.65. Ref GT424.

**ELECTRIC BIKES**, £679. Viking, built-in indicators, radio, lights, 13mph, 5 hour charge. Shimano gears, up to 50 mile range, horn, 26in. wheels, suspension, no licence needed, key operated. £679. Ref VIKING.

**PIR PCBs**. These contain a standard PIR detector circuit with all components, easy to wire up and use. Pack of 4 £6. Ref PIRB.  
**NEBULISER, WATER ATOMISER**. Ultrasonic module that you place in water, atomises the water into a very fine mist, many applications from special effects to scientific. £69. Ref NEB6.  
**PORTABLE X-RAY MACHINE PLANS**. Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £6/set. Ref F/XP1.

**TELEKINETIC ENHANCER PLANS**. Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks yet produces positive motion and effect. Excellent for science projects, magic shows, part demonstrations or serious research and development of this strange and amazing psychic phenomenon. £4/set. Ref F/TKE1.

**ELECTRONIC HYPNOSIS PLANS & DATA**. This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc only, by those experienced in its use. £15/set. Ref F/EH2.  
**GRAVITY GENERATOR PLANS**. This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of simple materials and without any visible means cause it to levitate. £10/set. Ref F/GRA1.

**TESLA COIL/LIGHTNING DISPLAY GLOBE PLANS**. Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects. 'Plasma in a jar', St Elmo's fire, corona, excellent science project or conversation piece. £5/set. Ref F/BTC1/LG5.  
**COPPER VAPOUR LASER PLANS**. Produces 100mW of visible green light. High coherency and spectral quality similar to argon laser but easier and less costly to build, yet far more efficient. This particular design was developed at the Atomic Energy Commission of NEGEV in Israel. £10/set. Ref F/CVL1.

**VOICE SCRAMBLER PLANS**. Miniature solid-state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £6/set. Ref F/V59.  
**PULSED TV JOKER PLANS**. Little handheld device utilises pulse techniques that will completely disrupt TV picture and sound! Works on FM too! *Discretion advised* £8/set. Ref F/TJ5.

**BODYHEAT TELESCOPE PLANS**. Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development etc. Excellent security device or very interesting science project. £8/set. Ref F/BHT1.




**BURNING, CUTTING CO2 LASER PLANS**. Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials, but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground etc. Burning and etching wood, cutting, plastics, textiles etc. £12/set, Ref F/LC7.

**AIR RIFLES FROM LESS THAN £40, CROSSBOWS, WIDE RANGE OF BB GUNS, AMMO, TARGETS, PISTOLS, REPLICAS, LASER SIGHTS, ELECTRIC BB, GAS BB**  
[www.alrpistol.co.uk](http://www.alrpistol.co.uk)

**INKJET CARTRIDGES FROM JUST £3 AT**  
[www.officebits.co.uk](http://www.officebits.co.uk)

**BULL ELECTRICAL**  
UNIT D, HENFIELD BUSINESS PARK,  
HENFIELD, SUSSEX BN5 9SL  
TERMS: CASH, PO OR CHEQUE WITH  
ORDER PLUS £5.00 P&P (UK) PLUS VAT  
24 HOUR SERVICE £7.50 (UK) PLUS VAT  
OVERSEAS ORDERS AT COST PLUS £3.50  
(ACCESS/VISA/SWITCH ACCEPTED)  
'phone: 01273 491490 Fax 491813  
Sales@bull-electrical.com

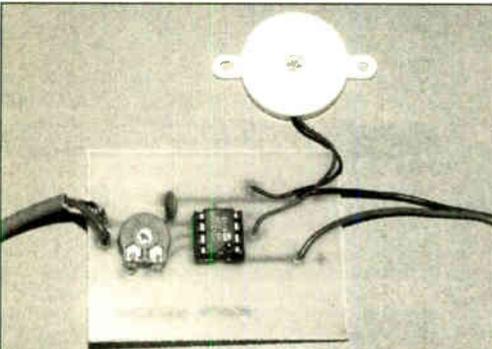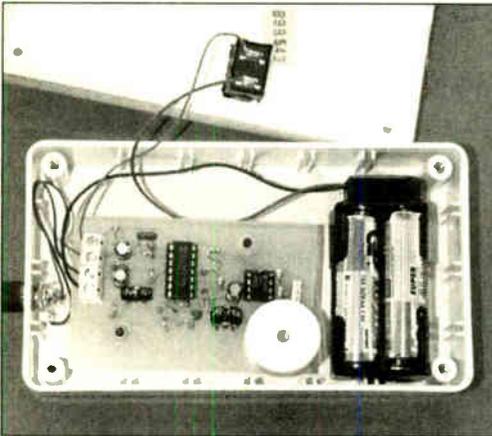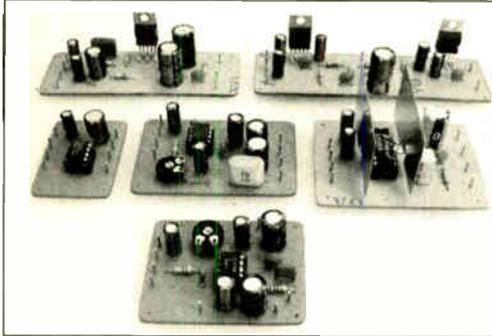[www.bullnet.co.uk](http://www.bullnet.co.uk)



## Projects and Circuits

- FREEZER ALARM** by Humphrey Berridge **316**  
 How to prevent your food from defrosting unexpectedly
- PIC BIG-DIGIT DISPLAY** by John Becker **325**  
 Control the giant ex-British Rail platform clock 7-segment digits that are now available on the surplus market
- INGENUITY UNLIMITED** hosted by Alan Winstanley **338**  
 Battery Discharger; Emergency Light
- SIMPLE AUDIO CIRCUITS – 1. Power Amplifiers** by Raymond Haigh **340**  
 A compendium of useful audio amplifier circuits for the experimenting constructor
- WASHING READY INDICATOR** by Terry de Vaux-Balbirnie **356**  
 Has the washing machine finished? – Avoid those washday blues

## Series and Features

- NEW TECHNOLOGY UPDATE** by Ian Poole **320**  
 Dye molecules improve solar cell efficiency
- PRACTICALLY SPEAKING** by Robert Penfold **335**  
 A general look at using enclosures with your projects
- NET WORK – THE INTERNET PAGE** surfed by Alan Winstanley **360**  
 Stripboard designing software
- CIRCUIT SURGERY** by Alan Winstanley and Ian Bell **362**  
 Linear opto-coupling; Dog and Cat Scarer circuit details
- TEACH-IN 2002 – 7. Comparators and digital optical sensing, plus more on Noise, with experiments** by Ian Bell and Dave Chesmore **368**

## Regulars and Services

- ELECTRONICS MANUALS** **310**  
 Essential reference works for hobbyists, students and service engineers
- EDITORIAL** **315**
- NEWS** – Barry Fox highlights technology's leading edge **322**  
 Plus everyday news from the world of electronics
- BACK ISSUES** Did you miss these? Many now on CD-ROM! **350**
- READOUT** John Becker addresses general points arising **353**
- CD-ROMS FOR ELECTRONICS** **364**  
 A wide range of CD-ROMs for hobbyists, students and engineers
- SHOPTALK** with David Barrington, **367**  
 The *essential* guide to component buying for *EPE* projects
- ELECTRONIC VIDEOS** Our range of educational videos **378**
- PRINTED CIRCUIT BOARD AND SOFTWARE SERVICE** **379**  
 PCBs for *EPE* projects. Plus *EPE* software
- DIRECT BOOK SERVICE** **380**  
 A wide range of technical books available by mail order
- ADVERTISERS INDEX** **384**

© Wimborne Publishing Ltd 2002. Copyright in all drawings, photographs and articles published in **EVERYDAY PRACTICAL ELECTRONICS** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our June 2002 issue will be published on Thursday, 9 May 2002. See page 307 for details

**Readers Services • Editorial and Advertisement Departments 315**

Visit our website  
www.distel.co.uk

# THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always  
wanted for cash!

## GIANT 10" 7-SEGMENT DISPLAYS

A bulk purchase enables us to bring to you these GIANT 7-segment digital displays at a now affordable price!! The 10" character size gives exceptional readability at long distances and enables a host of applications including, score boards, digital clocks, counters, event timers etc. As the units are a simple electromechanical device and operate from 12V DC, simple switching via switches, relays, PIC or PC may be used to control single or multiple digits. Units feature integral 'Zero Power' memory which greatly simplifies design. For an excellent DIY practice article, see the May issue of 'Everyday Practical Electronics' magazine. Ideal School / College construction project. Supplied in good RFE condition, complete with data sheet.



Less than 30% of makers price! Only £29.95(B) or 4 / £99.00(D)  
Order RW44 Order PH26

## THE AMAZING TELEBOX



TV SOUND & VIDEO TUNER  
CABLE COMPATIBLE

Converts your colour monitor into a QUALITY COLOUR TV!!  
The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers\* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95  
TELEBOX STL as ST but fitted with integral speaker £39.50  
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95  
For overseas PAL versions state 5.5 or 6 mHz sound specification.  
\*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Teleboxes, code (B)

**NEW** State of the art PAL (UK spec) UHF TV tuner module with composite 1V pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate.  
**BRAND NEW - Order as MY00. Only £39.95 code (B)**  
See www.distel.co.uk/data\_my00.htm for picture + full details

## HARD DISK DRIVES 2 1/2" - 14"

2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H) New £59.95  
2 1/2" TOSHIBA MK4313MAT 4.3Gb laptop (8.2 mm H) New £105.00  
2 1/2" TOSHIBA MK6409MAV 6.1Gb laptop (12.7 mm H) New £98.00  
2 1/2" TOSHIBA MK1614GAV 18 Gb laptop (12 mm H) New £149.95  
2 1/2" to 3 1/2" conversion kit for PC's, complete with connectors £15.95  
3 1/2" COMPAQ 313706-B21 (IBM) 9 gb ULT/SCSI3 New £199.00  
3 1/2" FUJII FK-309-26 20mb MFM I/F RFE £59.95  
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE £59.95  
3 1/2" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE £69.00  
3 1/2" QUANTUM 40S Prodriv ve 42mb SCSI I/F, New RFE £49.00  
5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE £49.95  
5 1/4" SEAGATE ST-238R 8 mb RLL I/F Refurb £69.95  
5 1/4" CDC 94205-51 40mb H MFM I/F RFE tested £69.95  
5 1/4" HP 97548 850 Mb SCSI RFE tested £99.00  
5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00  
8" NEC D2246 85 Mb SMD interface. New £99.00  
8" FUJITSU M2322K 160Mb SMD I/F RFE tested £195.00  
8" FUJITSU M2392K 2 Gb SMD I/F RFE tested £345.00  
Many other floppy & H drives, IDE, SCSI, ESDI etc from stock, see website for full stock list. Shipping on all drives is code (C)

## IC's - TRANSISTORS - DIODES

OBSELETE - SHORT SUPPLY - BULK  
10,000,000 items EX STOCK  
For MAJOR SAVINGS  
CALL or see web site www.distel.co.uk

## COMPUTER MONITOR SPECIALS

Legacy products  
High spec genuine multisync.  
CGA, EGA, VGA, SVGA

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes. BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched facplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, in EXCELLENT little used condition. TR & Swivel Base £4.75

VGA cable for IBM PC included. Only £129 (E) Order as CG73

External cables for other types of computers available - CALL

## Generic LOW COST SVGA Monitors

We choose the make, which includes Compaq, Mitsubishi, IBM, etc. Supplied ready to run with all cables, Standard RTB 90 day guarantee.

14" £59.00 15" £69.00 17" £79.00  
Supplied in good used condition. Shipping code (D)

## VIDEO MONITORS

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed  
Dimensions: W14" x H12 3/4" x 15 1/2" D. (E)  
Only £99.00

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen bums). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered.  
Only £79.00 (D)

## INDUSTRIAL COMPUTERS

Tiny shoebox sized industrial 40 Mhz 386 PC system measuring only (mm) 266 w x 88 h x 272 d. Ideal for dedicated control applications running DOS, Linux or even Windows I Steel case contains 85 to 265 V AC 50 / 60 Hz Watt PSU, a 3 slot ISA passive backplane and a Rocky 318 (PC104) standard, single board computer with 8 MByte NON VOLATILE solid state 'Disk On Chip' RAMDISK. System comprises: Rocky 318 (PC104) SBC ISA card with 40MHz ALI 386SX CPU, 72 pin SIMM slot with 16 Mbyte SIMM, AMI BIOS, battery backed up real time clock, 2 x 9 pin D 16550 serial ports, EPP/ECP printer port, mini DIN keyboard connector, floppy port, IDE port for hard drives up to 528 MByte capacity, watchdog timer and PC/104 bus socket. The 8 MByte solid state 'disk on a chip' has its own BIOS, and can be fdisked, formatted & booted. Supplied BRAND NEW fully tested and guaranteed. For full data see featured item on website. Order as QG36  
100's of applications inc: firewalls, routers, robotics etc  
Only £99.00 (D)

## 19" RACK CABINETS

Save £££'s  
Europe's Largest Stocks of quality rack cabinets, enclosures and accessories. Over 1000 Racks from stock

This month's special  
33 / 42 / 47 U - High Quality  
All steel Rack Cabinets

BIG £ SAVER

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvres. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue, some grey available - CALL - Can be supplied in many other configurations.



<b>33U</b> Order as BC44 External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W) Only <b>£245</b>	<b>42U</b> Order as DT20 External dimensions mm=2019H x 635D x 603 W. (79.5" H x 25" D x 23 3/4" W) Only <b>£345</b>	<b>47U</b> Order as RV36 External dimensions mm=2019H x 635D x 603 W. (88" H x 25" D x 23 3/4" W) Only <b>£410</b>
--	--	--

Call for shipping quotation

## COLOUR CCD CAMERAS

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full auto light sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available.



Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cams etc, etc.  
Order as LK33 ONLY £79.00 or 2 for £149.00 (B)

## SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. ONLY £89.00 (B)  
ENCARTA 95 - CDROM, Not the latest - but at this price! £7.95  
DOS 5.0 on 3 1/2" disks with concise books c/w QBasic £14.95  
Windows for Workgroups 3.11 + Dos 6.22 on 3.5" disks £55.00  
Windows 95 CDROM Only - No Licence - £19.95  
Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95  
shipping charges for software is code B

## SOLID STATE LASERS

Visible red, 670nm laser diode assembly. Unit runs from 5 V DC at approx 50 mA. Originally made for continuous use in industrial barcode scanners, the laser is mounted in a removable solid aluminium block, which functions as a heatsink and rigid optical mount. Dims of block are 50 x 50 x 15 mm. Integral features include over temperature shutdown, current control, laser OK output, and gated TTL ON / OFF. Many uses for experimental optics, comms & lightshows etc. Supplied complete with data sheet.  
Order as TD91 ONLY £24.95 (A)

## DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock - Call or see our web site.

## RELAYS - 200,000 FROM STOCK

Save £££'s by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting etc. CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save £££'s

## TEST EQUIPMENT & SPECIAL INTEREST ITEMS

MITSUBUSHI FA3445ETKL 14" Ind. spec SVGA monitors £245  
FARNELL 0-60V DC @ 50 Amps, bench Power Supplies £995  
FARNELL AP3080 0-30V DC @ 80 Amps, bench Supply £1850  
KINGSHILL CZ4031 0-50V @ DC 200 Amps - NEW £3950  
1kW to 400 kW - 400 Hz 3 phase power sources - ex stock £760  
IBM 8230 Type 1, Token ring base unit driver £2500  
Wayne Kerr RA200 Audio frequency response analyser £49  
INFODEC 1U, 24 port, RJ45 network patchpanels. #TH93 £49  
3COM 16670 12 Port Ethernet hub - RJ45 connectors #LD97 £69  
3COM 16671 24 Port Ethernet hub - RJ45 connectors £89  
3COM 16700 8 Port Ethernet hub - RJ45 connectors NEW £39  
IBM 53F501 Token Ring ICS 20 port lobe modules £POA  
IBM MAU Token ring distribution panel 8228-23-5050N £45  
AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE I/O £550  
ALLGON 8360, 11805-1880 MHz hybrid power combiners £250  
Trend DSA 274 Data Analyser with G703(2M) 64 I/O £POA  
Marconi 6310 Programmable 2 to 22 GHz sweep generator £4500  
Marconi 2022C 10KHz-1GHz RF signal generator £1550  
HP1650B Logic Analyser £3750  
HP3781A Pattern generator & HP3782A Error Detector £POA  
HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800  
HP6264 Rack mount variable 0-20V @ 20A metered PSU £475  
HP54121A DC to 22 GHz four channel test set £POA  
HP8130A opt 020 300 MHz pulse generator, GPIB etc £7900  
HP A1, A0 8 pen HPGL high speed drum plotters - from HP DRAFTMASTER 1 8 pen high speed plotter £550  
EG-G Brookdeal 95035C Precision lock in amp £1800  
Keithley 590 CV capacitor / voltage analyser £POA  
Racal ICR40 dual 40 channel video recorder system £3750  
Fliskera 45KVA 3 ph On Line UPS - New batteries £4500  
Emerson AP130 2.5KVA industrial spec. UPS £1499  
Mann Tally MT645 High speed line printer £2200  
Intel SBC 486/133SE Multibus 486 system. 8Mb Ram £945

HP6030A 0-200V DC @ 17 Amps bench power supply £1950  
Nitel SBC 486/125C08 Enhanced Multibus (MSA) New £1150  
Intel HFX-11 (Ephiphot) exposure control unit £1450  
PHILIPS PM5518 pro. TV signal generator £1250  
Motorola VME Bus Boards & Components List. SAE / CALL £POA  
Trio 0-18 vdc linear, metered 30 amp bench PSU. New £550  
Fujitsu M3041R 600 LPM high speed band printer £1950  
Fujitsu M3041D 600 LPM printer with network interface £1250  
Siemens K4400 64Kb to 140Mb demux analyzer £2950  
Perkin Elmer 299B Infrared spectrophotometer £500  
Perkin Elmer 597 Infrared spectrophotometer £3500  
Vig Electronics 1035 TELETXT Decoding Margin Meter £3250  
LightBand 60 output high spec 2u rack mount Video VDA's £495  
Sekonic SD 150H 18 channel digital Hybrid chart recorder £1995  
B&K 2633 Microphone pre amp £300  
Taylor Hobson Tallysurf amplifier / recorder £750  
ADC SS200 Carbon dioxide gas detector / monitor £1450  
BBC AM203 PPM Meter (Ernest Turner) - drive electronics £75  
ANRITSU 9654A Optical DC-2.5Gb/s wavform monitor £5650  
ANRITSU ML93A optical power meter £990  
ANRITSU Fibre optic characteristic test set £POA  
R&S FT0Z Dual sound unit £650  
R&S SBUF-E1 Vision modulator £775  
WILTRON 6630B 12.4 / 20GHz RF sweep generator £5750  
TEK 2445 150 MHz 4 trace oscilloscope £1250  
TEK 2465 300 MHz 300 MHz oscilloscope rack mount £1955  
TEK TDS380 400MHz digital realtime + disk drive, FFT etc £2900  
TEK TDS524A 500MHz digital realtime + colour display etc £5100  
HP3585A Opt 907 20Hz to 40 MHz spectrum analyser £3950  
PHILIPS PW1730/10 60KV XRAY generator & accessories £POA  
VARIACS - Large range from stock - call or see our website  
CLAUDE LYONS 12A 240V single phase auto. volt. regs £325  
CLAUDE LYONS 100A 240/415V 3 phase auto. volt. regs £2900

Display Electronics  
-ELECTRONICS-

ALL MAIL TO  
Dept PE, 29 / 35 Osborne Rd  
Thornton Heath  
Surrey CR7 8PD  
Open Mon - Fri 9.00 - 5:30

18 Million Items On Line Now!  
Secure ordering, Pictures, Information  
www.distel.co.uk  
email = admin@distel.co.uk

ALL ENQUIRIES  
0208 653 3333  
FAX 0208 653 8888



All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 7 working days clearance. Carriage charges (A)=£3.50, (B)=£6.50, (C)=£10, (D)=£15.00, (E)=£18.00, (F)=CALL. Allow approx 3 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale which can be viewed at our website and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Display Electronics 2002. E & O E..


# NEXT MONTH

## BIOPIC HEARTBEAT MONITOR

The Biopic monitors heartbeats across the chest using simple electrodes and outputs the display to a PC-compatible computer via an electrically-isolated serial data link. Pulse rates can be monitored separately by a handheld sensor that detects the opacity of the thumb, which changes as blood pulses through it. Based on a PIC16F876 microcontroller, the design uses only five i.c.s. The probes and contact pads used are those sold inexpensively by major chemists for use with proprietary TENS (pain relief) machines.

It can also be used as a handheld unit without a PC. In this role, an l.c.d. shows the heart rate as a graphical waveform, and provides a beats per minute count, plus a real-time pulse beat via a flashing asterisk.

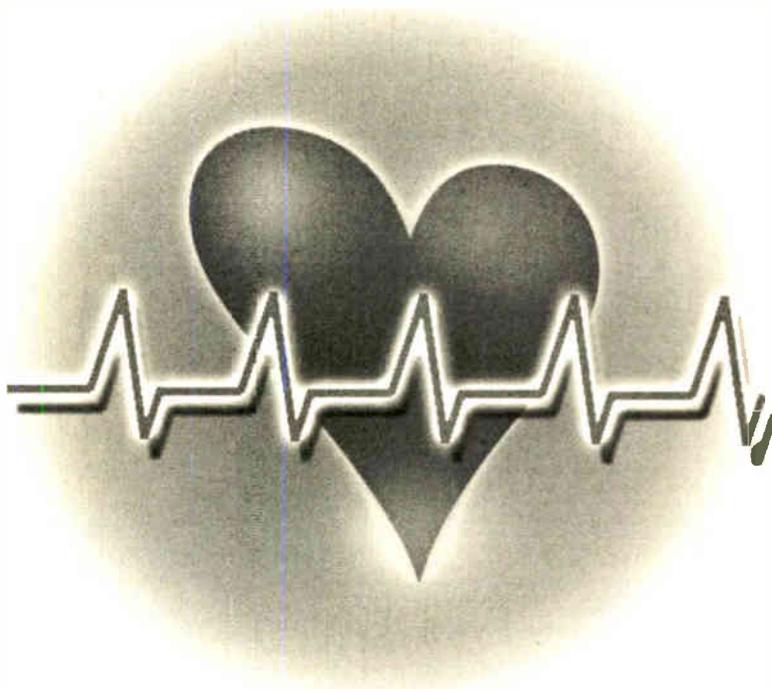The Biopic's PC software is written in QBasic, but is self-contained and does not require QB itself to be installed. It can be run in DOS mode or under Windows 3.1, 95, 98 and ME.



## WORLD LAMP

THE quest for a battery-powered lamp for lighting in poorer areas has presented an interesting and important design challenge for many years. Such a lamp should ideally be cheap, simple, efficient, and flexible – all at the same time.

With this in mind, the authors have designed a lamp that is made from inexpensive readily-available stock parts and runs off a nominal 12V d.c. supply. This is converted to a p.w.m. (pulse width modulated) a.c. supply which will power any ordinary fluorescent lamp between 100mW and 15W. It will power the equivalent of a 60W incandescent lamp for about 80 hours off a standard 12V car battery and can provide low cost lighting whenever or wherever there's no mains supply available.

## FREQUENCY STANDARD GENERATOR

A high-precision selectable 1kHz to 100kHz frequency source derived from BBC Radio Four's transmission signal which has a Rubidium frequency source as its reference and has an accuracy of one part in  $10^{11}$ .

The primary virtue of this design is its phenomenal accuracy and stability. There will not usually be many really accurate standards of any kind in the workshop of a home constructor since they are usually prohibitively expensive. This design provides an exception to this rule by bringing a national frequency standard right onto the amateur's bench. It should prove useful for checking and adjusting the calibration of frequency meters, oscilloscopes, and any other equipment used for measuring or generating frequency of any kind.

# NO ONE DOES IT BETTER

EVERYDAY  
**PRACTICAL**  
**ELECTRONICS**

INCORPORATING **ELECTRONICS TODAY INTERNATIONAL**

**DON'T MISS AN  
ISSUE – PLACE YOUR  
ORDER NOW!**  
Demand is bound to be high

**JUNE 2002 ISSUE ON SALE THURSDAY, MAY 9**

# QUASAR ELECTRONICS LIMITED

PO Box 6935, BISHOPS STORTFORD, Herts. CM23 4WP

TEL: 01279 467799 FAX: 07092 203496

ADD £3.00 P&P to all orders. \* Class Recorded £4. Next day (add £25.00) £7. Express £5.00. R% of World £10.00. We accept all major credit cards. Make cheques/POs payable to Quasar Electronics. Prices include 17.5% VAT MAIL ORDER ONLY. FREE CATALOGUE with order or send 2 x 1st class stamps (refundable) for details of over 150 kits & publications.



## PROJECT KITS

Our electronic kits are supplied complete with all components, high quality PCBs (NOT cheap Tripad strip board!) and detailed assembly/operating instructions

- **2 x 25W CAR BOOSTER AMPLIFIER** Connects to the output of an existing car stereo cassette player, CD player or radio. Heatsinks provided. PCB 76x75mm. 1046KT £24.95
- **3 CHANNEL WIRELESS LIGHT MODULATOR** No electrical connection with amplifier. Light modulation achieved via a sensitive electret microphone. Separate sensitivity control per channel. Power handling 400W/channel. PCB 54x112mm. Mains powered. Box provided. 6014KT £24.95
- **12 RUNNING LIGHT EFFECT** Exciting 12 LED light effect ideal for parties, discos, shop-windows & eye-catching signs. PCB design allows replacement of LEDs with 220V bulbs by inserting 3 TRIACs. Adjustable rotation speed & direction. PCB 54x112mm. 1026KT £15.95; BOX (for mains operation) 2026BX £30.00
- **DISCO STROBE LIGHT** Probably the most exciting of all light effects. Very bright strobe tube. Adjustable strobe frequency. 1-60Hz. Mains powered. PCB: 60x68mm. Box provided. 6037KT £28.95
- **ANIMAL SOUNDS** Cat, dog, chicken & cow. Ideal for kids farmyard toys & schools. SG10M £5.95
- **1/2 DIGIT LED PANEL METER** Use for basic voltage/current displays or customise to measure temperature, light, weight, movement, sound levels, etc. with appropriate sensors (not supplied). Various input circuit designs provided. 3061KT £13.95
- **IR REMOTE TOGGLE SWITCH** Use any TV/VCR remote control unit to switch onboard 12V/1A relay on/off. 3058KT £10.95
- **SPEED CONTROLLER** for any common DC motor up to 100V/5A. Pulse width modulation gives maximum torque at all speeds. 5-15VDC. Box provided. 3067KT £12.95
- **3 x 8 CHANNEL IR RELAY BOARD** Control eight 12V/1A relays by infra red (IR) remote control over a 20m range in sunlight. 6 relays turn on only, the other 2 toggle on/off. 3 operation ranges determined by jumpers. Transmitter case & all components provided. Receiver PCB 76x89mm 3072KT £52.95

## PRODUCT FEATURE

### COMPUTER TEMPERATURE DATA LOGGER

PC serial port controlled 4-channel temperature meter (either deg C or F). Requires no external power. Allows continuous temperature data logging of up to four temperature sensors located 200m+ from motherboard/PC. Ideal use for old 386/486 computers. Users can tailor input data stream to suit their purpose (dump it to a spreadsheet or write your own BASIC programs using the INPUT command to grab the readings). PCB just 38mm x 38mm. Sensors connect via four 3-pin headers. 4 header cables supplied but only one DS18S20 sensor. Kit software available free from our website.

ORDERING: 3145KT £23.95 (kit form); AS3145 £29.95 (assembled); Additional DS18S20 sensors £4.95 each



- **SOUND EFFECTS GENERATOR** Easy to build. Create an almost infinite variety of interesting/unusual sound effects from birds chirping to sirens. 9VDC. PCB 54x85mm. 1045KT £8.95
- **ROBOT VOICE EFFECT** Make your voice sound similar to a robot or Darlek. Great fun for discos, school plays, theatre productions, radio stations & playing jokes on your friends when answering the phone! PCB 42x71mm. 1131KT £8.95
- **AUDIO TO LIGHT MODULATOR** Controls intensity of one or more lights in response to an audio input. Sale, modern opto-coupler design. Mains voltage experience required. 3012KT £8.95
- **MUSIC BOX** Activated by light. Plays 8 Christmas songs and 5 other tunes. 3104KT £7.95
- **20 SECOND VOICE RECORDER** Uses non-volatile memory - no battery backup needed. Record/replay messages over & over. Playback as required to greet customers etc. Volume control & built-in mc. 6VDC. PCB 50x73mm. 3131KT £12.95
- **TRAIN SOUNDS** 4 selectable sounds: whistle blowing, level crossing bell, 'clicky-clack' & 4 in sequence. SG01M £6.95

### PC CONTROLLED RELAY BOARD

Convert any 286 upward PC into a dedicated automatic controller to independently turn on/off up to eight lights, motors & other devices around the home, office, laboratory or factory. Each relay output is capable of switching 250VAC/4A. A suite of DOS and Windows control programs are provided together with all components (except box and PC cable). 12VDC. PCB 70x200mm 3074KT £31.95

- **2 CHANNEL UHF RELAY SWITCH** Contains the same transmitter/receiver pair as 30A15 plus the components and PCB to control two 240VAC/10A relays (also supplied). Ultra bright LEDs used to indicate relay status. 3082KT £27.95
- **TRANSMITTER RECEIVER PAIR** 2-button keyboard style 300-375MHz Tx with 30m range. Receiver encoder module with matched decoder IC. Components must be built into a circuit like kit 3082 above. 30A15 £14.95
- **PIC 16C71 FOUR SERVO MOTOR DRIVER** Simultaneously control up to 4 servo motors. Software & all components (except servos/control pots) supplied. 5VDC PCB 50x70mm. 3102KT £15.95

- **UNIPOLAR STEPPER MOTOR DRIVER** for any 5/6/8 lead motor. Fast/slow & single step rates. Direction control & on/off switch. Wave, 2-phase & half-wave step modes. 4 LED indicators. PCB 50x65mm. 3109KT £14.95
- **PC CONTROLLED STEPPER MOTOR DRIVER** Control two unipolar stepper motors (3A max. each) via PC printer port. Wave, 2-phase & half-wave step modes. Software accepts 4 digital inputs from external switches & will single step motors. PCB fits in D-shell case provided. 3113KT £17.95

- **12-BIT PC DATA ACQUISITION/CONTROL UNIT** Similar to kit 3093 above but uses a 12 bit Analogue-to-Digital Converter (ADC) with internal analogue multiplexer. Reads 8 single ended channels or 4 differential inputs or a mixture of both. Analogue inputs read 0-4V. Four TTL/CMOS compatible digital input/outputs. ADC conversion time <10µs. Software (C, QB & Win), extended D shell case & all components (except sensors & cable) provided. 3118KT £52.95
- **LIQUID LEVEL SENSOR/RAIN ALARM** Will indicate fluid levels or simply the presence of fluid. Relay output to control a pump to add/remove water when it reaches a certain level. 1080KT £5.95
- **AM RADIO KIT 1** Tuned Radio Frequency front-end, single chip AM radio IC & 2 stages of audio amplification. All components inc. speaker provided. PCB 32x102mm. 3063KT £10.95
- **DRILL SPEED CONTROLLER** Adjust the speed of your electric drill according to the job at hand. Suitable for 240V AC mains powered drills up to

## X FACTOR PUBLICATIONS

THE EXPERTS IN RARE & UNUSUAL INFORMATION!

Full details of all X-FACTOR PUBLICATIONS can be found in our catalogue. N.B. Minimum order charge for reports and plans is £5.00 PLUS normal P&P.

- **SUPER-EAR LISTENING DEVICE** Complete plans to build your own parabolic dish microphone. Listen to distant voices and sounds through open windows and even walls! Made from readily available parts. R002 £3.50
- **LOCKS** - How they work and how to pick them. This fact filled report will teach you more about locks and the art of lock picking than many books we have seen at 4 times the price. Packed with information and illustrations. R008 £3.50
- **RADIO & TV JOKER PLANS** We show you how to build three different circuits for disrupting TV picture and sound plus FM radio! May upset your neighbours & the authorities! DISCRETION REQUIRED. R017 £3.50
- **INFINITY TRANSMITTER PLANS** Complete plans for building the famous Infinity Transmitter. Once installed on the target phone, device acts like a room bug. Just call the target phone & activate the unit to hear all room sounds. Great for home/office security! R019 £3.50
- **THE ETHER BOX CALL INTERCEPTOR PLANS** Grabs telephone calls out of thin air! No need to wire-in a phone bug. Simply place this device near the phone lines to hear the conversations taking place! R025 £3.00
- **CASH CREATOR BUSINESS REPORTS** Need ideas for making some cash? Well this could be just what you need! You get 40 reports (approx. 800 pages) on floppy disk that give you information on setting up different businesses. You also get valuable reproduction and duplication rights so that you can sell the manuals as you like. R030 £7.50

# SURVEILLANCE

High performance surveillance bugs. Room transmitters supplied with sensitive electret microphone & battery holder/cap. All transmitters can be received on an ordinary VHF/FM radio between 88-108MHz. Available in Kit Form (KT) or Assembled & Tested (AT).

## ROOM SURVEILLANCE

● **MTX - MINIATURE 3V TRANSMITTER** Easy to build & guaranteed to transmit 300m @ 3V Long battery life 3-5V operation. Only 45x18mm. B 3007KT £6.95 AS3007 £11.95

● **MRTX - MINIATURE 9V TRANSMITTER** Our best selling bug. Super sensitive high power - 500m range @ 9V (over 1km with 18V supply and better aerial) 45x19mm 3018KT £7.95 AS3018 £12.95

● **HPTX - HIGH POWER TRANSMITTER** High performance, 2 stage transmitter gives greater stability & higher quality reception 1000m range 6-12V DC operation. Size 70x15mm 3032KT £9.95 AS3032 £18.95

● **MMTX - MICRO-MINIATURE 9V TRANSMITTER** The ultimate bug for its size, performance and price. Just 15x25mm 500m range @ 9V. Good stability. 6-18V operation. 3051KT £8.95 AS3051 £14.95

● **VTX - VOICE ACTIVATED TRANSMITTER** Operates only when sounds detected. Low standby current. Variable trigger sensitivity. 500m range. Peaking circuit supplied for maximum RF output. On/off switch. 6V operation. Only 63x38mm 3028KT £12.95 AS3028 £21.95

● **HARDWIRED BUG/TWO STATION INTERCOM** Each station has its own amplifier, speaker and mic. Can be set up as either a hard-wired bug or two-station intercom. 10m x 2-core cable supplied. 9V operation. 3021KT £15.95 (kit form only)

● **TRVS - TAPE RECORDER VOX SWITCH** Used to automatically activate a tape recorder (not supplied) via its REMOTE socket when sounds are detected. All conversions recorded. Adjustable sensitivity & turn-off delay. 115x19mm 3013KT £9.95 AS3013 £21.95

700W power. PCB: 48mm x 65mm. Box provided. 6074KT £17.95

● **3 INPUT MONO MIXER** Independent level control for each input and separate bass/treble controls. Input sensitivity: 240mV. 18V OC. PCB: 60mm x 185mm 1052KT £16.95

● **NEGATIVE/POSITIVE ION GENERATOR** Standard Cockcroft-Walton multiplier circuit. Mains voltage experience required. 3057KT £10.95

● **LED DICE** Classic intro to electronics & circuit analysis. 7 LEDs simulate dice roll, slow down & land on a number at random. 555 IC circuit. 3003KT £9.95

● **STAIRWAY TO HEAVEN** Tests hand-eye co-ordination. Press switch when green segment of LED lights to climb the stairway - miss & start again! Good intro to several basic circuits. 3005KT £9.95

● **ROULETTE LED 'Ball'** spins round the wheel, slows down & drops into a slot. 10 LEDs. Good intro to CMOS decade counters & Op-Amps. 3006KT £10.95

● **12V XENON TUBE FLASHER TRANSFORMER** steps up a 12V supply to flash a 25mm Xenon tube. Adjustable flash rate. 3163KT £13.95

● **LED FLASHER 1** 5 ultra bright red LEDs flash in 7 selectable patterns. 3037MKT £5.95

● **LED FLASHER 2** Similar to above but flash in sequence or randomly. Ideal for model railways. 3052MKT £5.95

● **INTRODUCTION TO PIC PROGRAMMING.** Learn programming from scratch. Programming hardware, a P16F84 chip and a two-part, practical, hands-on tutorial series are provided. 3081KT £21.95

● **SERIAL PIC PROGRAMMER** for all 818/28/40 pin DIP serial programmed PICs. Shareware software supplied limited to programming 256 bytes (registration costs £14.95). 3096KT £12.95

● **ATMEL 89C051 PROGRAMMER** Simple-to-use yet powerful programmer for the Atmel 89C1051, 89C2051 & 89C4051 uCs. Programmer does NOT require special software other than a terminal emulator program (built into Windows). Can be used with ANY computer/operating system. 3121KT £24.95

● **3V/1-5V 9V BATTERY CONVERTER** Replace expensive 9V batteries with economic 1.5V batteries. IC based circuit steps up 1 or 2 'AA' batteries to give 9V/18mA. 3035KT £5.95

● **STABILISED POWER SUPPLY 3-30V/2.5A** Ideal for hobbyist & professional laboratory. Very reliable & versatile design at an extremely reasonable price. Short circuit protection. Variable DC voltages (3-30V). Rated output 2.5 Amps. Large heatsink supplied. You just supply a 24VAC/3A transformer. PCB 55x112mm. Mains operation. 1007KT £16.95.

## TELEPHONE SURVEILLANCE

● **M7TX - MINIATURE TELEPHONE TRANSMITTER** Attached anywhere to phone line. Transmits only when phone is used. Tune-in your radio and hear both parties. 300m range. Uses line as aerial & power source. 20x45mm 3016KT £8.95 AS3016 £14.95

● **TRF - TELEPHONE RECORDING INTERFACE** Automatically record all conversations. Connects between phone line & tape recorder (not supplied). Operates recorders with 1.5-12V battery systems. Powered from line. 50x33mm 3033KT £9.95 AS3033 £18.95

● **TPA - TELEPHONE PICK-UP AMPLIFIER/WIRELESS PHONE BUG** Place pick-up coil on the phone line or near phone earpiece and hear both sides of the conversation. 3055KT £11.95 AS3055 £20.95

## HIGH POWER TRANSMITTERS

● **1 WATT FM TRANSMITTER** Easy to construct. Delivers a crisp, clear signal. Two-stage circuit. Kit includes microphone and requires a simple open dipole aerial. 8-30VDC. PCB 42x45mm. 1009KT £14.95

● **4 WATT FM TRANSMITTER** Comprises three RF stages and an audio preamplifier stage. Piezoelectric microphone supplied or you can use a separate preamplifier circuit. Antenna can be an open dipole or Ground Plane. Ideal project for those who wish to get started in the fascinating world of FM broadcasting and want a good basic circuit to experiment with. 12-18VDC. PCB 44x146mm. 1028KT £22.95 AS1028 £34.95

● **15 WATT FM TRANSMITTER (PRE-ASSEMBLED & TESTED)** Four transistor based stages with Philips BL88 in final stage. 15 Watts RF power on the air. 88-108MHz. Accepts open dipole. Ground Plane, 5/8, J, or YAGI antennas. 12-18VDC. PCB 70x220mm. SWS meter needed for alignment. 1021KT £99.95

● **SIMILAR TO ABOVE BUT 25W Output** 1031KT £109.95

● **STABILISED POWER SUPPLY 2-30V/5A** As kit 1007 above but rated at 5Amp. Requires a 24VAC/5A transformer. 1096KT £27.95.

● **MOTORBIKE ALARM** Uses a reliable vibration sensor (adjustable sensitivity) to detect movement of the bike to trigger the alarm & switch the output relay to which a siren, bikes horn, indicators or other warning device can be attached. Auto-reset. 6-12VDC. PCB 57x64mm. 1011KT £11.95. Box 2011BX £7.00

● **CAR ALARM SYSTEM** Protect your car from theft. Features vibration sensor, courtesy/boot light voltage drop sensor and bonnet/boot earth switch sensor. Entry/exit delays, auto-reset and adjustable alarm duration. 6-12V DC PCB 47mm x 55mm 1019KT £11.95. Box 2019BX £8.00

● **PIEZO SCREAMER** 110dB of ear piercing noise. Fits in box with 2 x 35mm piezo elements built into their own resonant cavity. Use as an alarm siren or just for fun! 6-9VDC. 3015KT £10.95

● **COMBINATION LOCK** Versatile electronic lock comprising main circuit & separate keypad for remote opening of lock. Relay supplied. 3029KT £10.95

● **ULTRASONIC MOVEMENT DETECTOR** Crystal locked detector frequency for stability & reliability. PCB 75x40mm houses all components 4-7m range. Adjustable sensitivity. Output will drive external relay/circuits. 9VDC 3049KT £13.95

● **PIR DETECTOR MODULE** 3-lead assembled unit just 25x35mm as used in commercial burglar alarm systems. 3076KT £8.95

● **INFRARED SECURITY BEAM** When the invisible IR beam is broken a relay is tripped that can be used to sound a bell or alarm. 25 metre range. Mains rated relays provided. 12VDC operation. 3130KT £12.95

● **SQUARE WAVE OSCILLATOR** Generates square waves at 6 preset frequencies in factors of 10 from 1Hz-100KHz. Visual output indicator. 5-18VDC. Box provided. 3111KT £8.95

● **PC DRIVEN POCKET SAMPLER/OATA LOGGER** Analogue voltage sampler records voltages up to 2V or 20V over periods from milli-seconds to months. Can also be used as a simple digital scope to examine audio & other signals up to about 5KHz. Software & D-shell case provided. 3123KT £18.95

● **20 MHZ FUNCTION GENERATOR** Square, triangular and sine waveform up to 20MHz over 3 ranges using 'coarse' and 'fine' frequency adjustment controls. Adjustable output from 0-2V p-p. A TTL output is also provided for connection to a frequency meter. Uses MAX038 IC. Plastic case with printed front/rear panels & all components provided. 7-12VAC. 3101KT £69.95

**BARGAIN BUY!!**

## 30-in-ONE Electronic Projects Lab

Great introduction to electronics. Ideal for the budding electronics expert! Build a radio, burglar alarm, water detector, Morse code practice circuit, simple computer circuits, and much more! NO soldering, tools or previous electronics knowledge required. Circuits can be built and unassembled repeatedly. Comprehensive 68-page manual with explanations, schematics and assembly diagrams. Suitable for age 10+. Excellent for schools. Requires 2 x AA batteries. Order Code EP.030 ONLY £19.95 (phone for bulk discounts).



WEB: <http://www.QuasarElectronics.com>  
email: [epesales@QuasarElectronics.com](mailto:epesales@QuasarElectronics.com)

Secure Online Ordering Facilities  
Full Kit Listing, Descriptions & Photos  
Kit Documentation & Software Downloads

Credit Card Sales: 01279 467799

## Enhanced 'PICALL' ISP PIC Programmer

Kit will program virtually ALL 8 to 40 pin serial and parallel programmed PIC micro-controllers. Connects to PC parallel port. Supplied with fully functional pre-registered PICALL DOS and WINDOWS AVR software packages, all components and high quality DSPTH board. Also programs certain ATMEL AVR, SCENIX SX and EEPROM 24C devices. New devices can be added to the software as they are released. Blank chip auto detect feature for superb bulk programming. Hardware now supports ISP programming. \*A 40 pin wide ZIF socket is required to program 0-3in. devices (Order Code AZIF40 @ £15.00).



3144KT	Enhanced 'PICALL' ISP PIC Programmer	£64.95
AS3144	Assembled Enhanced 'PICALL' ISP PIC Programmer	£74.95
AS3144ZIF	Assembled Enhanced 'PICALL' ISP PIC Programmer c/w ZIF socket	£89.95

## ATMEL AVR Programmer




Powerful programmer for Atmel AT90Sxxxx (AVR) micro controller family. All fuse and lock bits are programmable. Connects to serial port. Can be used with ANY computer and operating system. Two LEDs to indicate programming status. Supports 20-pin DIP AT90S1200 & AT90S2313 and 40-pin DIP AT90S4414 & AT90S8515 devices. NO special software required - uses any terminal emulator program (built into Windows). The programmer is supported by BASCOM-AVR Basic Compiler software (see website for details).

3122KT	ATMEL AVR Programmer	£24.95
AS3122	Assembled 3122	£39.95

Atmel 89Cx051 and 89xxx programmers also available.
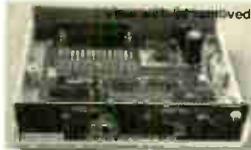
## PC Data Acquisition & Control Unit

With this kit you can use a PC parallel port as a real world interface. Unit can be connected to a mixture of analogue and digital inputs from pressure, temperature, movement, sound, light intensity, weight sensors, etc. (not supplied) to sensing switch and relay states. It can then process the input data and use the information to control up to 11 physical devices such as motors, sirens, other relays, servo motors & two-stepper motors.



### FEATURES:

- 8 Digital Outputs: Open collector, 500mA, 33V max.
  - 16 Digital Inputs: 20V max. Protection 1K in series, 5-1V Zener to ground.
  - 11 Analogue Inputs: 0-5V, 10 bit (5mV/step.)
  - 1 Analogue Output: 0-2.5V or 0-10V. 8 bit (20mV/step.)
- All components provided including a plastic case (140mm x 110mm x 35mm) with pre-punched and silk screened front/rear panels to give a professional and attractive finish (see photo) with screen printed front & rear panels supplied. Software utilities & programming examples supplied.

3093KT	PC Data Acquisition & Control Unit	£99.95
AS3093	Assembled 3093	£124.95

See opposite page for ordering information on these kits

## ABC Mini 'Hotchip' Board




Currently learning about microcontrollers? Need to do something more than flash a LED or sound a buzzer? The ABC Mini 'Hotchip' Board is based on Atmel's AVR 8535 RISC technology and will interest both the beginner and expert alike. Beginners will find that they can write and test a simple program, using the BASIC programming language, within an hour or two of connecting it up.

Experts will like the power and flexibility of the ATMEL microcontroller, as well as the ease with which the little Hot Chip board can be "designed-in" to a project. The ABC Mini Board 'Starter Pack' includes just about everything you need to get up and experimenting right away. On the hardware side, there's a pre-assembled micro controller PC board with both parallel and serial cables for connection to your PC. Windows software included on CD-ROM features an Assembler, BASIC compiler and in-system programmer. The pre-assembled boards only are also available separately.


ABCMINISP	ABC MINI Starter Pack	£64.95
ABCMINIB	ABC MINI Board Only	£39.95
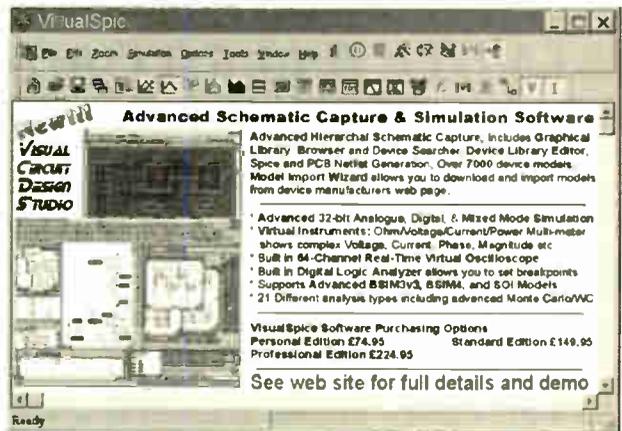
## Advanced 32-bit Schematic Capture and Simulation Visual Design Studio


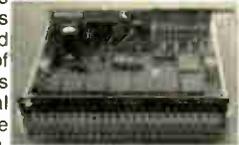
## Serial Port Isolated I/O Controller

Kit provides eight relay outputs capable of switching 4 amps at mains voltages and four optically isolated inputs. Can be used in a variety of control and sensing applications including load switching, external switch input sensing, contact closure and external voltage sensing. Programmed via a computer serial port, it is compatible with ANY computer & operating system. After programming, PC can be disconnected. Serial cable can be up to 35m long, allowing 'remote' control. User can easily write batch file programs to control the kit using simple text commands. NO special software required - uses any terminal emulator program (built into Windows). All components provided including a plastic case with pre-punched and silk screened front/rear panels to give a professional and attractive finish (see photo).



3108KT	Serial Port Isolated I/O Controller Kit	£54.95
AS3108	Assembled Serial Port Isolated I/O Controller	£69.95

**WHETHER ELECTRONICS IS YOUR HOBBY  
OR YOUR LIVELIHOOD . . .  
YOU NEED THE MODERN ELECTRONICS MANUAL  
and the ELECTRONICS SERVICE MANUAL**

## **THE MODERN ELECTRONICS MANUAL (CD-ROM VERSION ONLY)**



*The essential reference  
work for everyone  
studying electronics*

- Over 800 pages
- In-depth theory
- Projects to build
- Detailed assembly instructions
- Full components checklists
- Extensive data tables
- Manufacturers' web links
- Easy-to-use Adobe Acrobat format
- Clear and simple layout
- Comprehensive subject range
- Professionally written
- Regular Supplements

## **EVERYTHING YOU NEED TO GET STARTED AND GO FURTHER IN ELECTRONICS!**

The revised CD-ROM edition of the Modern Electronics Base Manual (MEM) contains practical, easy-to-follow information on the following subjects:

**BASIC PRINCIPLES:** Electronic Components and their Characteristics (16 sections from Resistors and Potentiometers to Crystals, Crystal Modules and Resonators); Circuits Using Passive Components (10 sections); Power Supplies; The Amateur Electronics Workshop; The Uses of Semiconductors; Digital Electronics (6 sections); Operational Amplifiers; Introduction to Physics, including practical experiments; Semiconductors (5 sections) and Digital Instruments (3 sections).

**CIRCUITS TO BUILD:** There's nothing to beat the satisfaction of creating your own projects. From basic principles, like soldering and making printed circuit boards, to the tools needed for circuit-building, the Modern Electronics Manual and its Supplements describe clearly, with appropriate diagrams, how to assemble a radio, loudspeaker circuits, amplifiers, car projects,

a computer interface, measuring instruments, workshop equipment, security systems, medical and musical circuits, etc. The Base Manual describes 12 projects including a Theremin and a Simple TENS Unit.

**ESSENTIAL DATA:** Extensive tables on diodes, transistors, thyristors and triacs, digital and linear i.c.s.

**EXTENSIVE GLOSSARY:** Should you come across a technical word, phrase or abbreviation you're not familiar with, simply look up the glossary included in the Manual and you'll find a comprehensive definition in plain English.

The Manual also covers **Safety** and provides web links to component and equipment **Manufacturers and Suppliers**. The most comprehensive reference work ever produced at a price you can afford, the CD-ROM edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the *essential* information you need.

## **THE MODERN ELECTRONICS MANUAL (MEM – CD-ROM version only)**

**Revised CD-ROM Edition of Basic Work:** Contains over 800 pages of information in Adobe Acrobat format. Edited by John Becker.

**Regular Supplements:** Additional CD-ROMs each containing approximately 500 pages of additional information on specific areas of electronics will be available for £19.95 each. Information on the availability and content of each Supplement CD-ROM will be sent to you as they become available.

**Presentation:** CD-ROM suitable for any modern PC. Requires Adobe Acrobat Reader which is included on the MEM CD-ROM.

**Price of the Basic Work:** ~~£29.95~~ OFFER PRICE £24.95 POST FREE. Offer ends May 31st 2002

## **ORDER BOTH MANUALS TOGETHER AND SAVE ANOTHER £10**

*A mass of well-organised and clearly explained information is brought to you by expert editorial teams whose combined experience ensures the widest coverage  
Regular Supplements to these unique publications, keep you abreast of the latest technology and techniques if required*

# ELECTRONICS SERVICE MANUAL

(PRINTED VERSION ONLY)

## EVERYTHING YOU NEED TO KNOW TO GET STARTED IN REPAIRING AND SERVICING ELECTRONIC EQUIPMENT

**SAFETY:** Be knowledgeable about Safety Regulations, Electrical Safety and First Aid.

**UNDERPINNING KNOWLEDGE:** Specific sections enable you to Understand Electrical and Electronic Principles, Active and Passive Components, Circuit Diagrams, Circuit Measurements, Radio, Computers, Valves and Manufacturers' Data, etc.

**PRACTICAL SKILLS:** Learn how to identify Electronic Components, Avoid Static Hazards, Carry Out Soldering and Wiring, Remove and Replace Components.

**TEST EQUIPMENT:** How to Choose and Use Test Equipment, Assemble a Toolkit, Set Up a Workshop, and Get the Most from Your Multimeter and Oscilloscope, etc.

**SERVICING TECHNIQUES:** The regular Supplements include vital guidelines on how to Service Audio Amplifiers, Radio Receivers, TV Receivers, Cassette Recorders, Video Recorders, Personal Computers, etc.

**TECHNICAL NOTES:** Commencing with the IBM PC, this section and the regular Supplements deal with a very wide range of specific types of equipment – radios, TVs, cassette recorders, amplifiers, video recorders etc..

**REFERENCE DATA:** Detailing vital parameters for Diodes, Small-Signal Transistors, Power Transistors, Thyristors, Triacs and Field Effect Transistors. Supplements include Operational Amplifiers, Logic Circuits, Optoelectronic Devices, etc.

## ELECTRONICS SERVICE MANUAL

(ESM – Printed version only)

**Basic Work:** Contains around 900 pages of information. Edited by Mike Tooley BA

**Regular Supplements:** Unlike a book or encyclopedia, this Manual is a living work – continuously extended with new material. If requested, Supplements are sent to you on approval approximately every three months. Each Supplement contains around 160 pages – all for only £23.50+£2.50 p&p. You can, of course, return any Supplement (within ten days) which you feel is superfluous to your needs. You can also purchase a range of past Supplements to extend your Base Manual on subjects of particular interest to you.

**Presentation:** Durable looseleaf system in large A4 format

**Price of the Basic Work:** ~~£39.95~~ **SALE PRICE £24.95**  
(to include a recent Supplement FREE). Offer ends May 31st 2002.

## The essential work for servicing and repairing electronic equipment

- Around 900 pages
- Fundamental principles
- Troubleshooting techniques
- Servicing techniques
- Choosing and using test equipment
- Reference data
- Easy-to-use format
- Clear and simple layout
- Vital safety precautions
- Professionally written
- Regular Supplements
- Sturdy gold blocked ring-binder



### Guarantee

Our 30 day money back guarantee gives you complete peace of mind. If you are not entirely happy with the *Electronics Service Manual*, for whatever reason, simply return it to us in good condition within 30 days and we will make a full refund of your payment – no small print and no questions asked. All we ask is that you pay the return postage. (Overseas buyers also have to pay our overseas postage charge). Sorry, but we can only make exchanges on the *Modern Electronics Manual* (CD-ROM version) if the CD-ROM is faulty, we cannot offer a money back guarantee on this product as the content can be printed out.

Wimborne Publishing Ltd., Dept Y5, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562.  
Online shop: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

PLEASE send me



- THE MODERN ELECTRONICS MANUAL (CD-ROM version only)
- ELECTRONICS SERVICE MANUAL plus a FREE SUPPLEMENT (Printed version only)
- I enclose payment of £24.95 (for one Manual) or £39.90 for both Manuals (saving another £10 by ordering both together) plus postage if applicable. (Offers end May 31st 2002)
- I also require the appropriate Supplements four times a year. These are billed separately and can be discontinued at any time. (Please delete if not required.)

FULL NAME .....  
(PLEASE PRINT)

ADDRESS .....

.....POSTCODE .....

SIGNATURE .....

- I enclose cheque/PO in UK pounds payable to Wimborne Publishing Ltd.
- Please charge my Visa/Mastercard/Amex/Diners Club/Switch Switch Issue No.....

Card No. .... Card Exp. Date .....

### ORDER FORM

Simply complete and return the order form with your payment to the following address:  
Wimborne Publishing Ltd, Dept. Y5, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND  
We offer a 30 day MONEY BACK GUARANTEE on ESM – see the panel above for details.

### POSTAGE CHARGES FOR ESM

MEM CD-ROM POST FREE TO ALL COUNTRIES  
(Note we use the VAT portion of the MEM CD-ROM payment to pay for overseas postage)

Postal Region	Price PER ESM PRINTED MANUAL	
	Surface	Air
Mainland UK	FREE	-
Scottish Highlands, UK Islands & Eire	£7 each	-
Europe (EU)	-	£23 each
Europe (Non-EU)	£23 each	£30 each
USA & Canada	£28 each	£39 each
Far East & Australasia	£35 each	£43 each
Rest of World	£28 each	£52 each

Please allow four working days for UK delivery.  
NOTE: Surface mail can take over 10 weeks to some parts of the world. Each ESM weighs about 4kg when packed.

mem-cd

**MAIL ORDER ONLY • CALLERS BY APPOINTMENT**

**EPE MICROCONTROLLER P.I. TREASURE HUNTER**

The latest MAGENTA DESIGN - highly stable & sensitive - with I.C. control of all timing functions and advanced pulse separation techniques.

- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

**KIT 847 .....£63.95**


**PORTABLE ULTRASONIC PEST SCARER**

A powerful 23kHz ultrasound generator in a compact hand-held case. MOSFET output drives a special sealed transducer with intense pulses via a special tuned transformer. Sweeping frequency output is designed to give maximum output without any special setting up.

**KIT 842.....£22.56**

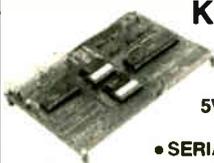**68000 DEVELOPMENT TRAINING KIT**

- NEW PCB DESIGN
- 8MHz 68000 16-BIT BUS
- MANUAL AND SOFTWARE
- 2 SERIAL PORTS
- PIT AND I/O PORT OPTIONS
- 12C PORT OPTIONS



**KIT 621 £99.95**

- ON BOARD 5V REGULATOR
- PSU £6.99
- SERIAL LEAD £3.99

**Stepping Motors**

- MD38...Mini 48 step...£8.65
- MD35...Std 48 step...£9.99
- MD200...200 step...£12.99
- MD24...Large 200 step...£22.95



**PIC PIPE DESCALER**

- SIMPLE TO BUILD
- HIGH POWER OUTPUT
- AUDIO & VISUAL MONITORING
- SWEPT FREQUENCY

An affordable circuit which sweeps the incoming water supply with variable frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve lathering ability by altering the way salts in the water behave. Kit includes case, P.C.B., coupling coil and all components. High coil current ensures maximum effect. L.E.D. monitor.



**KIT 868 ..... £22.95 POWER UNIT.....£3.99**

**MICRO PEST SCARER**

Our latest design - The ultimate scarer for the garden. Uses special microchip to give random delay and pulse time. Easy to build reliable circuit. Keeps pets/pests away from newly sown areas, play areas, etc. uses power source from 9 to 24 volts.

- RANDOM PULSES
- HIGH POWER
- DUAL OPTION



Plug-in power supply £4.99

**KIT 867.....£19.99**

**KIT + SLAVE UNIT.....£32.50**

**WINDICATOR**

A novel wind speed indicator with LED readout. Kit comes complete with sensor cups, and weatherproof sensing head. Mains power unit £5.99 extra.

**KIT 856.....£28.00**

**★ TENS UNIT ★**

**DUAL OUTPUT TENS UNIT**

As featured in March '97 issue.

Magenta have prepared a FULL KIT for this excellent new project. All components, PCB, hardware and electrodes are included. Designed for simple assembly and testing and providing high level dual output drive.

**KIT 866.. Full kit including four electrodes £32.90**

Set of 4 spare electrodes £6.50

**1000V & 500V INSULATION TESTER**



Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms.

Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

**KIT 848..... £32.95**

**EPE TEACH-IN 2000**

Full set of top quality NEW components for this educational series. All parts as specified by EPE. Kit includes breadboard, wire, croc clips, pins and all components for experiments, as listed in introduction to Part 1.

\*Batteries and tools not included.

**TEACH-IN 2000 -**

**KIT 879 £44.95**

**MULTIMETER £14.45**

**SPACEWRITER**

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube plus instructions for message loading.

**KIT 849 .....£16.99**

**12V EPROM ERASER**

A safe low cost eraser for up to 4 EPROMS at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

**KIT 790 .....£29.90**

**SUPER BAT DETECTOR**

1 WATT O/P, BUILT IN SPEAKER, COMPACT CASE 20kHz-140kHz

NEW DESIGN WITH 40kHz MIC.

A new circuit using a 'full-bridge' audio amplifier i.c., internal speaker, and headphone/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.



**KIT 861 .....£24.99**

ALSO AVAILABLE Built & Tested... £39.99

**MOSFET MKII VARIABLE BENCH POWER SUPPLY 0-25V 2.5A**

Based on our Mk1 design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.



Kit No. 845 .....£64.95

**EPE PROJECT PICS**

Programmed PICs for all\* EPE Projects 16C84/18F84/16C71 All **£5.90 each** PIC16F877 now in stock **£10 inc. VAT & postage**

(\*some projects are copyright)

**ULTRASONIC PEST SCARER**

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS



- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

**KIT 812.....£15.00**

## SIMPLE PIC PROGRAMMER

INCREDIBLE LOW PRICE! Kit 857 **£12.99**

INCLUDES 1-PIC16F84 CHIP  
SOFTWARE DISK, LEAD  
CONNECTOR, PROFESSIONAL  
PC BOARD & INSTRUCTIONS

Power Supply £3.99

EXTRA CHIPS:  
PIC 16F84 £4.84

Based on February '96 EPE. Magenta designed PCB and kit. PCB with 'Reset' switch, Program switch, 5V regulator and test L.E.D.s, and connection points for access to all A and B port pins.

## PIC 16C84 DISPLAY DRIVER

INCLUDES 1-PIC16F84 WITH DEMO  
PROGRAM SOFTWARE DISK, PCB,  
INSTRUCTIONS AND 16-CHARAC-  
TER 2-LINE  
LCD DISPLAY

Kit 860 **£19.99**

Power Supply £3.99

FULL PROGRAM SOURCE CODE  
SUPPLIED - DEVELOP  
YOUR OWN APPLICATION!

Another super PIC project from Magenta. Supplied with PCB, industry standard 2-LINE x 16-character display, data, all components, and software to include in your own programs. Ideal development base for meters, terminals, calculators, counters, timers - Just waiting for your application!

## PIC 16F84 MAINS POWER 4-CHANNEL CONTROLLER & LIGHT CHASER

- WITH PROGRAMMED 16F84 AND DISK WITH SOURCE CODE IN MPASM
- ZERO VOLT SWITCHING
- MULTIPLE CHASE PATTERNS
- OPTO ISOLATED
- 5 AMP OUTPUTS
- 12 KEYPAD CONTROL
- SPEED/DIMMING POT.
- HARD-FIRED TRIACS

Kit 855 **£39.95**

LOTS OF OTHER APPLICATIONS


Now features full 4-channel chaser software on DISK and pre-programmed PIC16F84 chip. Easily re-programmed for your own applications. Software source code is fully 'commented' so that it can be followed easily.

## 8-CHANNEL DATA LOGGER

As featured in Aug./Sept. '99 EPE. Full kit with Magenta redesigned PCB - LCD fits directly on board. Use as Data Logger or as a test bed for many other 16F877 projects. Kit includes programmed chip, 8 EEPROMs, PCB, case and all components.

Kit 877 **£49.95** inc. 8 x 256K EEPROMS

## ICEBREAKER

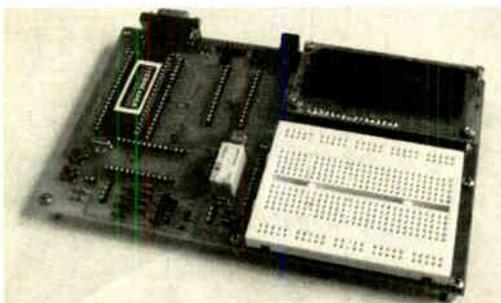

## PIC Real Time In-Circuit Emulator

- Icebreaker uses PIC16F877 in circuit debugger
- Links to Standard PC Serial Port (lead supplied)
- Windows™ (95+) Software included
- Works with MPASM and MPLAB Microchip software
- 16 x 2 L.C.D., Breadboard, Relay, I/O devices and patch leads supplied

As featured in March '00 EPE. Ideal for beginners AND advanced users. Programs can be written, assembled, downloaded into the microcontroller and run at full speed (up to 20MHz), or one step at a time.

Full emulation means that all I/O ports respond exactly and immediately, reading and driving external hardware.

Features include: Reset; Halt on external pulse; Set Breakpoint; Examine and Change registers, EEPROM and program memory; Load program, Single Step with display of Status, W register, Program counter, and user selected 'Watch Window' registers.

Kit 900 . . . **£34.99**

POWER SUPPLY £3.99 STEPPING MOTOR £5.99

## EPE PIC TOOLKIT 3

**NEW**

- THE LATEST TOOLKIT BOARD - 8, 18, 28 AND 40-PIN CHIPS
- MAGENTA DESIGNED P.C.B. WITH COMPONENT LAYOUT AND EXTRAS
- L.C.D., BREADBOARD AND PIC CHIP INCLUDED
- ALL TOP QUALITY COMPONENTS AND SOFTWARE SUPPLIED

Kit 880 . . . **£34.99** with 16F84 . . . **£39.99** with 16F877

## PIC TOOLKIT V2

- SUPER UPGRADE FROM V1 • 18, 28 AND 40-PIN CHIPS
- READ, WRITE, ASSEMBLE & DISASSEMBLE PICS
- SIMPLE POWER SUPPLY OPTIONS 5V-20V
- ALL SWITCHING UNDER SOFTWARE CONTROL
- MAGENTA DESIGNED PCB HAS TERMINAL PINS AND OSCILLATOR CONNECTIONS FOR ALL CHIPS
- INCLUDES SOFTWARE AND PIC CHIP

Kit 878 . . . **£22.99** with 16F84 . . . **£29.99** with 16F877

## EPE PIC Tutorial

At last! A Real, Practical, Hands-On Series

- Learn Programming from scratch using PIC16F84
- Start by lighting l.e.d.s and do 30 tutorials to Sound Generation, Data Display, and a Security System.
- PIC TUTOR Board with Switches, l.e.d.s, and on board programmer

## PIC TUTOR BOARD KIT

Includes: PIC16F84 Chip, TOP Quality PCB printed with Component Layout and all components\* (\*not ZIF Socket or Displays). Included with the Magenta Kit is a disk with Test and Demonstration routines.

Kit 870 .... **£27.95**, Built & Tested .... **£42.95**

Optional: Power Supply - **£3.99**, ZIF Socket - **£9.99**

LCD Display ..... **£7.99** LED Display ..... **£6.99**

Reprints Mar/Apr/May 98 - **£3.00** set 3

## SUPER PIC PROGRAMMER

- READS, PROGRAMS, AND VERIFIES
- WINDOWS® SOFTWARE
- PIC16C6X, 7X, AND 8X
- USES ANY PC PARALLEL PORT
- USES STANDARD MICROCHIP • HEX FILES
- OPTIONAL DISASSEMBLER SOFTWARE (EXTRA)
- PCB, LEAD, ALL COMPONENTS, TURNED-PIN SOCKETS FOR 18, 28, AND 40 PIN ICs

• SEND FOR DETAILED INFORMATION - A SUPERB PRODUCT AT AN UNBEATABLE LOW PRICE.

Kit 862 **£29.99**

Power Supply £3.99

DISASSEMBLER SOFTWARE **£11.75**

## PIC STEPPING MOTOR DRIVER

INCLUDES PCB, PIC16F84 WITH DEMO PROGRAM, SOFTWARE DISC, INSTRUCTIONS AND MOTOR.

Kit 863 **£18.99**

FULL SOURCE CODE SUPPLIED ALSO USE FOR DRIVING OTHER POWER DEVICES e.g. SOLENOIDS

Another NEW Magenta PIC project. Drives any 4-phase unipolar motor - up to 24V and 1A. Kit includes all components and 48 step motor. Chip is pre-programmed with demo software, then write your own, and re-program the same chip! Circuit accepts inputs from switches etc and drives motor in response. Also runs standard demo sequence from memory.

# MAGENTA

All prices include VAT. Add £3.00 p&p. Next day **£6.99**

Tel: 01283 565435 Fax: 01283 546932 E-mail: sales@magenta2000.co.uk

052002



**Station Road, Cullercoats, Tyne & Wear, NE30 4PQ**

Prices Exclude Vat @17.5%.  
UK Carriage £1.50 (less than 1kg)  
£3.50 greater than 1kg  
Cheques / Postal orders payable to  
ESR Electronic Components.  
PLEASE ADD CARRIAGE & VAT TO ALL ORDERS

See Next / Last Months Ad. for ELECTRONIC COMPONENTS

**DIL Sockets**

6 Pin DIL 0.3"	£0.07
8 Pin DIL 0.3"	£0.06
14 Pin DIL 0.3"	£0.11
16 Pin DIL 0.3"	£0.11
18 Pin DIL 0.3"	£0.12
20 Pin DIL 0.3"	£0.12
24 Pin DIL 0.6"	£0.13
28 Pin DIL 0.6"	£0.13
40 Pin DIL 0.6"	£0.19

**Stamped Pin**

6 Pin DIL 0.3"	£0.07
8 Pin DIL 0.3"	£0.06
14 Pin DIL 0.3"	£0.11
16 Pin DIL 0.3"	£0.11
18 Pin DIL 0.3"	£0.12
20 Pin DIL 0.3"	£0.12
24 Pin DIL 0.6"	£0.13
28 Pin DIL 0.6"	£0.13
40 Pin DIL 0.6"	£0.19

**Turned Pin**

8 Pin DIL 0.3"	£0.11
14 Pin DIL 0.3"	£0.20
16 Pin DIL 0.3"	£0.23
18 Pin DIL 0.3"	£0.25
20 Pin DIL 0.3"	£0.28
24 Pin DIL 0.6"	£0.35
28 Pin DIL 0.6"	£0.39

**ZIF Sockets**

Universal ZIF DIL Sockets	
24 Way 0.3-0.6"	£5.78
28 Way 0.3-0.6"	£6.60
32 Way 0.3-0.6"	£7.50
40 Way 0.3-0.6"	£8.93

**Transistor Sockets**

T018-4 Base Socket	£0.24
T05 Base Socket	£0.24

**ICD Cable Sockets**

10 Way Socket	£0.23
14 Way Socket	£0.35
16 Way Socket	£0.37
20 Way Socket	£0.37
26 Way Socket	£0.38
34 Way Socket	£0.39
40 Way Socket	£0.55
50 Way Socket	£0.80

**ICD Cable Plugs**

10 Way Plug	£0.52
14 Way Plug	£0.58
16 Way Plug	£0.62
20 Way Plug	£0.66
26 Way Plug	£0.70
34 Way Plug	£0.80
40 Way Plug	£0.92
50 Way Plug	£1.12

**PCB Box Headers**

10 Way Straight	£0.23
14 Way Straight	£0.33
16 Way Straight	£0.32
20 Way Straight	£0.41
26 Way Straight	£0.55
34 Way Straight	£0.68
40 Way Straight	£1.03
50 Way Straight	£1.03
10 Way 90°	£0.39
14 Way 90°	£0.32
16 Way 90°	£0.42
20 Way 90°	£0.63
26 Way 90°	£0.82
34 Way 90°	£0.81
40 Way 90°	£1.17
50 Way 90°	£1.14

**PCB Latch Headers**

10 Way Straight	£0.41
14 Way Straight	£0.45
16 Way Straight	£0.51
20 Way Straight	£0.55
26 Way Straight	£0.73
34 Way Straight	£0.88
40 Way Straight	£0.92
50 Way Straight	£1.27
10 Way 90°	£0.46
14 Way 90°	£0.48
16 Way 90°	£0.54
20 Way 90°	£0.59
26 Way 90°	£0.81
34 Way 90°	£1.03
40 Way 90°	£1.23
50 Way 90°	£1.41

**DIL Headers**

14 Way DIL	£0.51
16 Way DIL	£0.53
24 Way DIL	£0.90
40 Way DIL	£1.37

**Transistion Headers**

10 Way Transistion	£0.42
14 Way Transistion	£0.42
16 Way Transistion	£0.48
20 Way Transistion	£0.48
26 Way Transistion	£0.52
34 Way Transistion	£0.56
40 Way Transistion	£0.63
50 Way Transistion	£0.84

Large Range of Connectors in stock - Fully illustrated details on our web site inc. quantity discounts.

**D Type Connectors**

9 Way Male Plug	£0.20
9 Way Female Socket	£0.20
15 Way Male Plug	£0.28
15 Way Female Socket	£0.29
15 Way H.D. Plug	£0.48
15 Way H.D. Socket	£0.64
23 Way Male Plug	£0.44
23 Way Female Socket	£0.50
25 Way Male Plug	£0.30
25 Way Female Skt	£0.35

**Solder Bucket**

9 Way Male Plug	£0.20
9 Way Female Socket	£0.20
15 Way Male Plug	£0.28
15 Way Female Socket	£0.29
15 Way H.D. Plug	£0.48
15 Way H.D. Socket	£0.64
23 Way Male Plug	£0.44
23 Way Female Socket	£0.50
25 Way Male Plug	£0.30
25 Way Female Skt	£0.35

**ICD Ribbon Mounting**

9 Way Male Plug	£1.08
9 Way Female Socket	£0.93
15 Way Male Plug	£1.30
15 Way Female Socket	£1.32
25 Way Male Plug	£1.10
25 Way Female Socket	£1.13
ICD Crimp Tool	£11.80

**Right Angled PCB**

9 Way Male Plug	£0.33
9 Way Female Socket	£0.33
15 Way Male Plug	£0.39
15 Way Female Socket	£0.39
15 Way H.D. Socket	£0.58
25 Way Male Plug	£0.58
25 Way Female Socket	£0.50

**Plastic D Covers**

9 Way Cover - Grey	£0.29
9 Way Cover - Black	£0.30
15 Way Cover - Grey	£0.32
15 Way Cover - Black	£0.38
25 Way Cover - Grey	£0.34
25 Way Cover - Black	£0.37
9 to 9 Cover / Case	£0.80
25 to 25 Cover / Case	£0.84
9 to 25 Cover / Case	£0.80

**Audio Connectors**

2.5mm Jack Plug	£0.25
2.5mm Line Socket	£0.16
2.5mm Chassis Socket	£0.20
3.5mm Mono Plug	£0.20
3.5mm Mono Line Skt	£0.20
3.5mm Mono Chassis	£0.14
3.5mm Stereo Plug	£0.35
3.5mm Stereo Line Skt	£0.37
3.5mm Stereo Chassis	£0.22
1/4" Mono Plug	£0.34
1/4" Mono Line Socket	£0.35
1/4" Mono Chassis Skt	£0.37
1/4" Stereo Plug	£0.40
1/4" Stereo Line Socket	£0.38
1/4" Stereo Chassis Skt	£0.38
MUSIC Speakon Plug	£2.81

**Phono Series**

Red Line Plug	£0.20
Black Line Plug	£0.20
Yellow Line Plug	£0.20
White Line Plug	£0.20
Red Line Socket	£0.20
Black Line Socket	£0.20
Yellow Line Socket	£0.20
White Line Socket	£0.20
Red Chassis Socket	£0.20
Black Chassis Socket	£0.20
Gold Plated Plug Red	£0.66
Gold Plated Plug Black	£0.66

**XLR Series - metal**

3 Pin Line Plug	£0.96
3 Pin Line Socket	£0.96
3 Pin Chassis Plug	£1.50
3 Pin Chassis Socket	£1.49
Neutrik Line Plug	£1.79
Neutrik Line Socket	£1.99
Neutrik Chassis Plug	£2.13
Neutrik Chassis Socket	£2.37

**RF Connectors**

BNC Plug 50Ω Solder	£0.99
BNC Plug 50Ω Crimp	£0.68
BNC Plug 75Ω Solder	£1.08
BNC Plug 75Ω Crimp	£0.68
BNC Chassis Socket	£0.81
F Plug - Twist	£0.24
F Plug - Crimp	£0.26
TNC Plug 50Ω Solder	£1.24
TNC Plug 50Ω Crimp	£0.85
TNC Plug 75Ω Solder	£1.40
TNC Plug 75Ω Crimp	£1.16
UHF Plug 5mm Cable	£0.63
UHF Plug 11mm Cable	£0.75
UHF Chassis Skt - Sqr	£0.54
UHF Chassis Skt - Rnd	£0.73

**Terminals**

Colours Red, Black, Green, Blue, White or Yellow	
2mm Solder Plugs	£0.18
2mm Chassis Sockets	£0.28
4mm Plugs - Solder	£0.33
4mm Plugs - Screw	£0.38
4mm Stackable Plugs	£0.40
4mm Shrouded Plugs	£0.74
4mm Chassis Sockets	£0.24
4mm Binding Posts	£0.46
33mm Crocodile Clips	£0.10

**Power Connectors**

DC Plug 0.71D 2.35OD	£0.47
DC Plug 1.71D 3.40D	£0.32
DC Plug 1.71D 4.00D	£0.47
DC Plug 1.71D 4.75D	£0.47
DC Plug 2.11D 5.00D	£0.25
DC Plug 2.11D 5.00D	£0.24
DC Plug 3.11D 6.30D	£0.46
DC Line Socket 2.1mm	£0.57
DC Line Socket 2.5mm	£0.68
DC Chassis Skt 2.1mm	£0.44
DC Chassis Skt 2.5mm	£0.41

**IEC Mains 6A 250Vac**

3 Pin IEC Line Socket	£1.08
3 Pin IEC Line Plug	£1.78
3 Pin Chassis Socket	£0.55
3 Pin Chassis Plug	£0.72

**8 Way Bulgin**

8 Pin Line Plug P551	£3.58
8 Pin Chassis Skt P552	£1.08

**Toggle Switches**

Sub-Miniature 3A 125V 1A 250V	
6.2mm Ø Mounting Hole	
5mm Ø Mounting Hole	
SPST 5 x 10mm	£0.53
SPDT 5 x 10mm	£0.53
SPDT C/O 5 x 10mm	£1.01
DPDT 9.2 x 10mm	£0.63

**Miniature**

6A 125V 3A 250V	
6.2mm Ø Mounting Hole	
SPST 8 x 13mm	£0.58
SPDT 8 x 13mm	£0.55
SPDT C/O 8 x 13mm	£0.65
SPDT c/o Biased 2 way 1.18	£1.18
SPDT c/o Biased 1 way 1.15	£0.65
DPDT 12 x 13mm	£0.65
DPDT C/O 12 x 13mm	£0.88
DPDT c/o Biased 2W	£1.20
DPDT c/o Biased 1W	£1.28

**Standard**

1A 125V	
5.5 x 12mm Mounting Hole	
DPDT 12 x 35mm	£0.27
DPDT C/O 12 x 35mm	£0.25

**Rotary Switches**

150mA 250V Moke before Break 22mm Ø	
9.8mm Ø Mounting Hole	
1 Pole 12 Way	£0.84
2 Pole 6 Way	£0.84
3 Pole 4 Way	£0.84
4 Pole 3 Way	£0.84

**Push Switches**

Miniature Round 250mA 125V 28 x 10mm 7mm Ø Mounting Hole	
Non Latching Push to Make	
Black, Red, Yellow, Green, Blue or White	£0.23
Non Latching Push to Break	
Black P78	£0.24

**Standard Square**

1A 250V 39 x 15MM 12mm Ø Mounting Hole	
Non Latching Push to Make	
Black, Red, Blue or White	£0.60
Latching -push On push Off	
Black, Red, Blue or White	£0.65

**Rocker Switches**

Miniature 13 x 19mm Mounting Hole	
SPST 4A 250V	£0.57
SPST 6A Red Neon	£1.65
SPST 3A Red LED	£1.92
SPDT 6A 250V	£0.75
DPST 4A 250V	£0.81
DPST 4A Red Neon	£1.10
DPST 3A Amber Neon	£1.40
DPST 3A Green Neon	£1.32

**Standard**

10(SP,22)(DP) x 30mm Mounting Hole	
SPST 10A 250V	£0.60
SPST 16A 250V	£0.75
SPST 15A Red Neon	£0.90
SPDT 16A 250V	£0.75
DPST 10A 250V	£0.90
DPST 15A Red Neon	£1.18
DPST Amber Neon	£1.25
DPST Green Neon	£1.25
DPDT 10A 250V	£0.90

**Relays**

PCB Mounting 1A 24Vdc DPDT 5V	£1.38
1A 24Vdc DPDT 12V	£1.35
3A 110V SPDT 6V	£0.58
3A 110V SPDT 12V	£0.60
5A 110V SPDT 6V	£0.72
5A 110V SPDT 12V	£0.72
5A 110V DPDT 6V	£0.93
5A 110V DPDT 12V	£0.93
5A 240V DPDT 6V	£1.76
5A 240V DPDT 12V	£1.55
10A 240V SPDT 6V	£1.20
10A 240V SPDT 12V	£1.44
10A 240V SPDT 24V	£1.44

**Computer Accessories Adapters**

9M Gender Changer	£1.73
9F Gender Changer	£1.73
25M Gender Changer	£2.20
25F Gender Changer	£2.43
9 Male - 25 Female	£1.73
9 Female - 25 Male	£1.73
9M - 6 Mini Din Male	£2.48
9F - 6 Mini Din Female	£2.48
5M Din - 6F Mini Din	£1.73
5F Din - 6M Mini Din	£1.73

**Testers / Patch Boxes**

Mini Tester 7 LEDs	£4.72
Check Tester 18 LEDs	£6.32
Enhanced+ Switches	£15.18
25D Patch Box M-F	£2.64
Anti-Static Wrist Strap	£4.76
RS232 Surge Protector	£5.43
5A Surge Protector	£5.20
13A Surge Protector	£10.00
4 Gang Surge Block	£10.50

**Leads & Cables**

1.5m Printer Lead	£2.55
2m BD Printer Lead	£2.98
5m BD Printer Lead	£4.98
10m BD Printer Lead	£9.88
2m IEEE1284 Printer L	£4.38
5m IEEE1284 Printer L	£8.90
10m IEEE1284 Printer L	£16.13
Serial Printer 25M-9F	£4.88
Serial Printer 25M-25F	£4.38

**Null Modem Leads**

9 Female - 9 Female	£4.38
25 Male - 25 Female	£6.48
9 Female - 25 Female	£4.38
9&25F to 9&25F	£4.88

**Modem Leads**

25Male to 9Female	£4.08
25Male to 25Female	£3.78

**PC Link Leads**

Interlink 25M to 25M	£3.88
----------------------	-------

# EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

**VOL. 31 No. 5 MAY 2002**

## MAGIC POWERS

The start of this month's new series on *Simple Audio Circuits* raises a question that always annoys me – I guess it is a pet hate of mine. To put it in simple terms, I hate to see audio output powers quoted by manufacturers that are frankly fairy tales. If you see a set of small computer speakers with internal amplifiers quoted as having 100W or greater output then I suggest you simply buy from a more honest manufacturer.

How do manufacturers dream up these totally unrealistic figures? Well this is how it's done, courtesy of Jake Rothman writing for our *Modern Electronics Manual*:

Say the true r.m.s. output of an amplifier is 10W (this expresses the power of an unclipped sinewave as a d.c. voltage producing the same power into a given – say 8 ohm resistance). The first stage of the trick is to use the term "peak power" which derives the power from the peak voltage so our 10W becomes 20W. The next stage is to specify the output into 4 ohms so now we have 40W (note that 90 per cent of speakers are 8 ohm impedance). Step 3 is to call it music power which, because music is not continuous (like a sinewave), allows the output to be doubled again giving 80W. Finally, the two stereo channel outputs are added together to give 160W peak music power (stereo) you will usually see this quoted simply as 160W PMPO (peak music power output).

As you can see, it's a con, try dividing it by 16 to get the true output! In some cases manufacturers have gone even further and I have seen claims like 480W PMPO qualified by 12W + 12W r.m.s. output – at least they quoted the r.m.s. figure.

So if you see audio output specifications that are not based on continuous sinewave r.m.s. figures at a stated level of distortion then I suggest that you simply do not believe them.

You can tell the quality manufacturers by the way they quote their output figures. There is basically no way that miniature amplified computer speakers will provide a true 100W (or more) output, if you don't believe me just take a look at the output available from the plug top power supply they normally use and ask yourself if you can get 100W output with less than 10W (12V, 800mA) input? Nice trick if you could really do it.

It is, of course, all a marketing con. trick.



## AVAILABILITY

Copies of *EPE* are available on subscription anywhere in the world (see below), from all UK newsagents (distributed by COMAG) and from the following electronic component retailers: Omni Electronics and Yebo Electronics (S. Africa). *EPE* can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased and downloaded for just \$9.99(US – approx £7.70) per year available from [www.epemag.com](http://www.epemag.com)

## SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £15, 12 months £28.50, two years £52; Overseas: 6 months £18 standard air service or £27 express airmail, 12 months £34.50 standard air service or £52 express airmail, 24 months £64 standard air service or £99 express airmail.

Online subscriptions, for downloading the magazine via the Internet, \$9.99(US – approx £7.70) for one year available from [www.epemag.com](http://www.epemag.com).

Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subs. Dept., Wimborne Publishing Ltd. 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: [subs@epemag.wimborne.co.uk](mailto:subs@epemag.wimborne.co.uk). Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Switch or Visa. (For past issues see the *Back Issues* page.)

## BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £5.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Amex, Diners Club, Switch and MasterCard accepted. Send, fax or phone your card number and card expiry date with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

## Editorial Offices:

EVERYDAY PRACTICAL ELECTRONICS EDITORIAL  
WIMBORNE PUBLISHING LTD, 408 WIMBORNE ROAD EAST,  
FERNDOWN, DORSET BH22 9ND  
Phone: (01202) 873872. Fax: (01202) 874562.

Email: [epe@wimborne.co.uk](mailto:epe@wimborne.co.uk)

Web Site: <http://www.epemag.wimborne.co.uk>

EPE Online [www.epemag.com](http://www.epemag.com)

EPE Online Shop: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

See notes on Readers' Enquiries below – we regret lengthy technical enquiries cannot be answered over the telephone.

## Advertisement Offices:

EVERYDAY PRACTICAL ELECTRONICS ADVERTISEMENTS

MILL LODGE, MILL LANE

THORPE-LE-SOKEN, ESSEX CO16 0ED

Phone/Fax: (01255) 861161

Email: [epeads@aol.com](mailto:epeads@aol.com)

Editor: MIKE KENWARD

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Administration: FAY KENWARD

Editorial/Admin: (01202) 873872

Advertisement Manager:

PETER J. MEW, Frinton (01255) 861161

Advertisement Copy Controller:

PETER SHERIDAN, (01202) 873872

On-Line Editor: ALAN WINSTANLEY

EPE Online (Internet version) Editors:

CLIVE (MAX) MAXFIELD and ALVIN BROWN

## READERS' ENQUIRIES

E-mail: [techdept@epemag.wimborne.co.uk](mailto:techdept@epemag.wimborne.co.uk)

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a **stamped self-addressed envelope or a self-addressed envelope and international reply coupons**. All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

## COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers (see *Shoptalk*). We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

## ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

## TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.



# Constructional Project

# FREEZER ALARM

## HUMPHREY BERRIDGE



Simply protect your food, learn about using the 8-pin PIC12C508, and about applying the Watchdog Timer.

**S**OME modern freezers contain alarms which sound if you leave the door open and allow the internal space to warm up. However, they do not work if the freezer suffers a power failure, which is a bit of a drawback.

Making a temperature-sensitive circuit which can sound an alarm is not too difficult (a typical example was the *Ice Alert* in Feb '01) but what is required here is a low-cost circuit which can run on batteries for a very long time.

This design uses a circuit based on a PIC, using a feature about which little has been written, namely the ability to send it to sleep! The circuit is extremely simple, and the software uses several techniques which could be useful in other projects.

### BABY PIC

The design uses the "baby" of the PIC family, the PIC12C508. This is an extraordinarily versatile device, and in its OTP (one-time-programmable) version is very inexpensive. It is housed in an 8-pin d.i.l. package (see Fig.1), and has the same set of 33 RISC instructions as its big brothers.

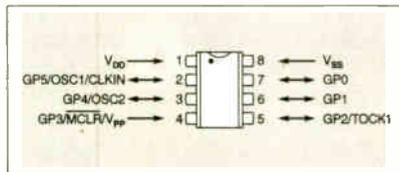


Fig.1 (above). The pin diagram for the PIC12C508 microcontroller.

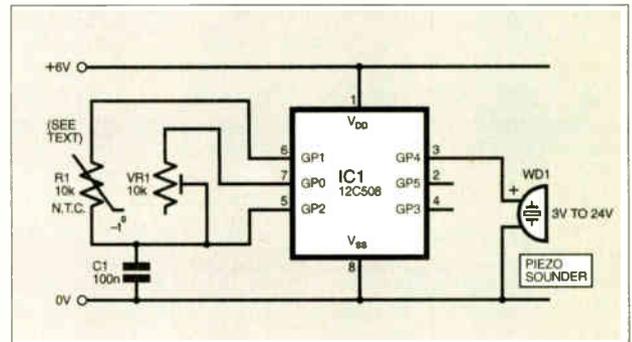


Fig.2 (right). Circuit diagram for the Freezer Alarm.

Two pins are used for power (between 2.5V and 5.5V), the remainder can be configured as five I/O (input-output) pins and one input-only pin.

An in-built oscillator runs at 4MHz – i.e. an instruction every 1 $\mu$ s. It has 25 bytes of

data RAM available, program memory is 512 bytes. There are two internal timers, one of which is a "Watchdog", and it can drive output devices with currents up to 50mA.

This little PIC is extraordinarily versatile, and for many applications provides adequate microcontroller power. Of course, the more powerful versions such as the PIC16F84 can be programmed to operate in just the same way with few changes to the software, but why use a sledge-hammer to crack a nut?

### CIRCUIT DESCRIPTION

If you are the sort of person who enjoys the challenge of constructing complex circuits, you will be disappointed! The complete circuit contains only five components, as shown in Fig.2. The clever stuff, of course, is provided by the PIC.


The temperature sensor used is a low-cost disc thermistor, R1, which can be attached via a length of 2-core cable. A small preset variable resistor, VR1 is used to set the operating point, the temperature threshold at which the alarm sounds.

Capacitor C1 is used to make the input circuit time-dependant, as described in the next section. For the alarm, a piezo sounder (WD1) is used because it can make a relatively large amount of noise whilst using a very small amount of electrical power. The whole circuit will conveniently run off a 6V battery.
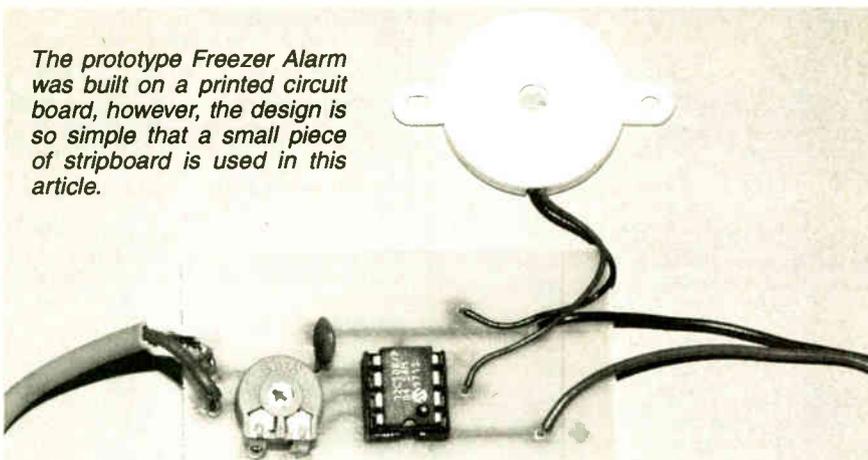
### HOW IT WORKS

Thermistors are basically temperature sensitive resistors – normal n.t.c. (negative temperature coefficient) ones have a high resistance when cold, and a low resistance when hot, and the change of resistance is a very large effect.

The prototype Freezer Alarm was built on a printed circuit board, however, the design is so simple that a small piece of stripboard is used in this article.



An easy way to test a thermistor is to place it in a freezer (which is normally at about  $-18^{\circ}\text{C}$ ) and connect it to a multimeter via leads of suitable length. After a few minutes the thermistor will reach the temperature of the freezer, and with the meter on its resistance range you will be able to measure the approximate value of resistance at this temperature.

The thermistor used here has a resistance of around  $1\text{k}\Omega$  at room temperature (see Table 1). Other types of N.T.C. thermistor could equally well be used with minor alterations to the circuit which are explained later.

**Table 1. Thermistor temperature/resistance**

	Temperature	Resistance
Room	$22^{\circ}\text{C}$	$900\Omega$
Fridge	$2^{\circ}\text{C}$	$2\text{k}\Omega$
Freezer	$-20^{\circ}\text{C}$	$11\text{k}\Omega$


The microcontroller circuit needs to "measure" this resistance in order to evaluate whether the thermistor is too warm – we do not need to know its actual value, just whether it is higher or lower than a preset value. This can conveniently be done by comparing the resistance of the thermistor to that of a preset resistor, VR1.

The PIC12C508 is basically a digital device, so we need a cunning plan to make it capable of measuring resistance. The method is to use the PIC as a timer which can count how long it takes a small capacitor C1 to charge up to a certain voltage.


If we consider a very simple circuit (Fig.3) consisting of just a capacitor C and a resistor R, we can see that if the switch is closed, the voltage V across the capacitor is zero and it is uncharged. As soon as the switch is opened, the capacitor charges via the resistor, and the voltage rises along an exponential curve (Fig.4).

In our circuit, we time how long it takes to go from zero to the logic threshold of the PIC (the point at which a logic 0 changes to a logic 1), which is about 3.0V, say.


The mathematics of this charging process produces a very simple relationship, namely that the time taken to reach a certain voltage is directly proportional to the value of R, so the time we have counted out until the voltage rises to 3.0V is an accurate representation of the value of the resistor. So all we need to do is to time how long it takes for the capacitor to charge via the thermistor, then time how long it takes to charge via the preset resistor. If the first time is shorter than the second, the thermistor is too warm and we ought to sound the alarm!

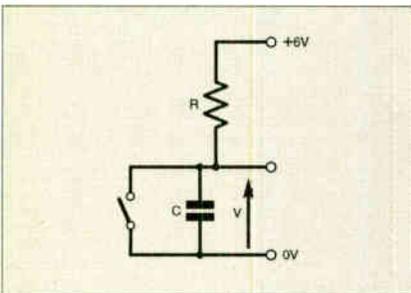

**Fig.3. Simple circuit to demonstrate capacitor charging.**

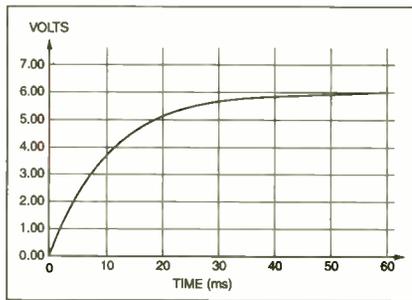

**Fig.4. Capacitor charging curve.**

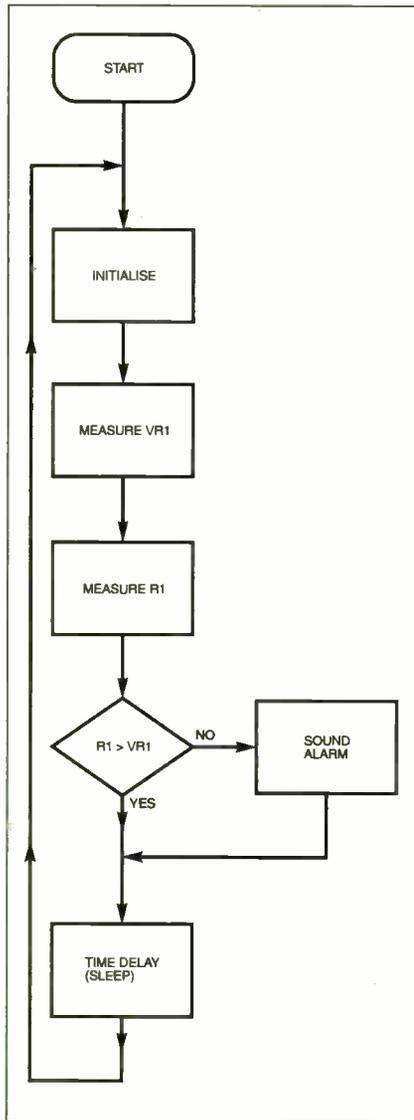

**Fig.5. Flow chart for the main program.**

What makes it possible for the PIC to do this is that not only can we force pins to go high or low, but we can also change whether a pin is an output or an input as the program is running. Using this fact we can both switch between the two resistors, and discharge the capacitor between our readings. This is described in the section on programming.

### MAIN PROGRAM

The way the program operates is straightforward, as illustrated by the flow-chart in Fig.5. First the PIC is initialised in that pins are set up either as outputs or inputs. We then have to measure the charging times of the capacitor first for the preset resistor VR1, then for the thermistor R1.

In order to give a reasonable number of steps to do the counting and improve the range of accuracy of the measurement, two registers are used together to form a 16-bit value.

The technique used for measuring resistance is shown in Fig.6, and involves the following:

1. First the capacitor needs to be completely discharged. To do this, pin 5 is set as an output, and then set at logic 0 (zero volts). This effectively shorts the capacitor. A delay of approximately 5ms makes sure it is fully discharged.

2. Next the two registers used to store the count time for the thermistor are set to zero.

3. Then pin 6 is set as an output, and reset to logic 0. Pin 5 is swapped to being an input pin, and then pin 6 taken to logic 1. At this moment the capacitor begins to charge up.

4. The program now starts to loop, incrementing the counter registers as it goes. Each time around the loop pin 5 is checked for having reached the voltage threshold at which it is considered to be at logic 1.

5. As soon as this happens, the routine ends, and the counter registers then contain the final time count. This process is repeated for the variable resistor VR1 using a different set of counter registers and pin 7 instead of pin 6.

After both measurements have been made, the two answers are compared: all we need to do is to subtract one number from another – we just want to know which process took the longer. Depending upon the outcome, we either go directly into the Sleep mode, or sound the alarm for a short time before again going to sleep.

### ALARMING

Generally speaking, a piezo device is not a buzzer – it has to be driven by an oscillating signal to make the alarm

## COMPONENTS

<b>Resistor</b>	R1 n.t.c. disc thermistor, 10k (1k at room temperature)	See SHOP TALK page
<b>Potentiometer</b>	VR1 10k min. enclosed carbon skeleton preset, horiz	
<b>Capacitor</b>	C1 100n ceramic disc	
<b>Semiconductor</b>	IC1 PIC12C508 preprogrammed microcontroller (see text)	
<b>Miscellaneous</b>	WD1 piezo sounder, 3V to 24V	

Stripboard, 10 strips x 17 holes; plastic case, size and type to choice; battery holder; AA-size batteries (4 off); battery clip; 8-pin d.i.l. socket; connecting wire; solder, etc.

Approx. Cost  
Guidance Only
£9

excluding case & batts.

sounds. There are two reasons for using a "swept frequency" alarm sound using the software:

a. Changing sounds such as beepers, sirens, etc. stand out much better from background noises, and

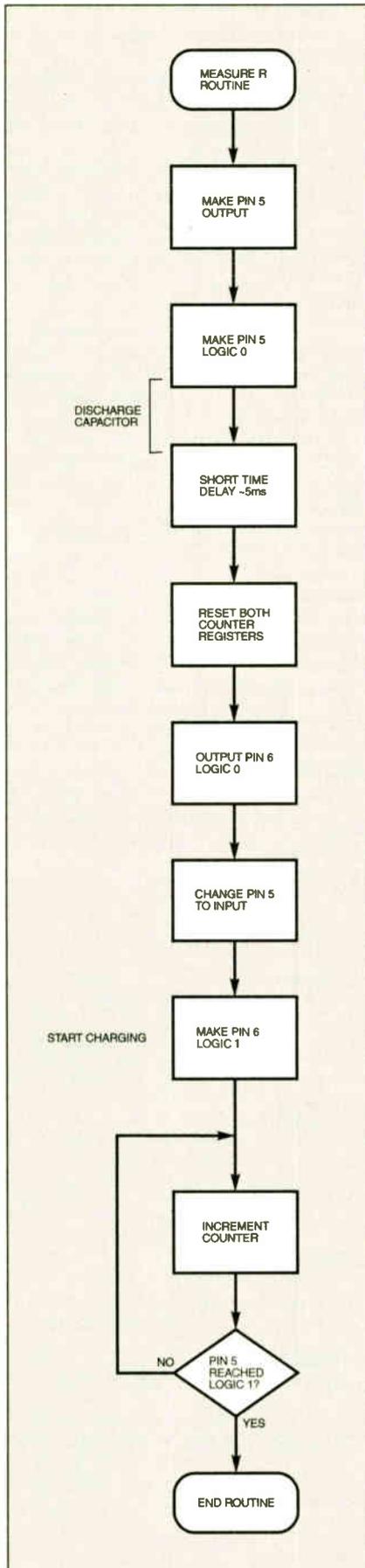


Fig.6. Measuring the resistance of the thermistor.

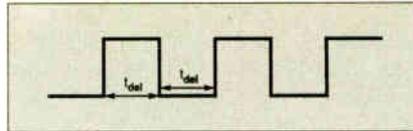


Fig.7. Output waveform.

b. the piezo device used here has a very sharp resonance – i.e. the sound output is very much higher at a specific frequency than at others. Different devices have different resonances, and even those tested of the same type had frequencies which varied quite a bit. By sweeping the frequency through the resonance one can be sure of making the most irritating noise! In this design, the frequency sweeps from approximately 2kHz to 8kHz.

To make a PIC generate an oscillating signal is quite simple. Referring to the waveform in Fig.7, you take the output high, wait for a short time ( $t_{del}$ ), take the output low, wait for a short time ( $t_{del}$ ), and then repeat the process.

The result is a square wave driving the piezo sounder. If, for instance, we made  $t_{del} = 0.5ms$ , the period would be  $2 \times t_{del} = 1.0ms$ , and the sound would have a frequency of 1kHz.

Sweeping the frequency may be accomplished by gradually changing the value of  $t_{del}$  which can be done using the fact that delays in microcontroller systems are often made by "time-waster" loops where a counter counts down to zero.

By changing the value loaded into a register in the first place, the time taken can be varied. Fig.8 shows the program segment responsible. For each specific frequency, eight cycles are generated. The whole process takes approximately 130ms.

### WATCHDOG

Not many published projects seem to use a PIC's Watchdog Timer (WDT), but when it comes to conserving power using the Sleep mode, it is very useful. Information can be found in Microchip's data sheets and other publications.

When a PIC is given the Sleep command, it shuts down nearly all its functions and as a result consumes a very tiny amount of power – it only draws about  $4\mu A$  from the supply.

There are three ways in which it can wake up again:

- by a logic change on a pre-defined pin
- when the WDT times-out, and
- by an external master Reset

It is the second of these options that is used in this project. Inside the PIC12C508, the WDT function has its own internal oscillator and counter, and these continue to run even if the PIC is asleep. When the WDT times out, a system Reset is generated, and the program restarts.

It should be noted that one bit of the configuration word of the PIC enables or disables the WDT, and this bit must be set when the chip is programmed.

So, if we reset the WDT, it will then start counting and when it times-out (18ms later), the program goes through a Reset and starts again. That is not a very long time, but fortunately we can use the internal pre-scaler which can be used in conjunction with the WDT. To do this, we use the OPTION register to extend the time-out period to approximately 2-3 seconds.

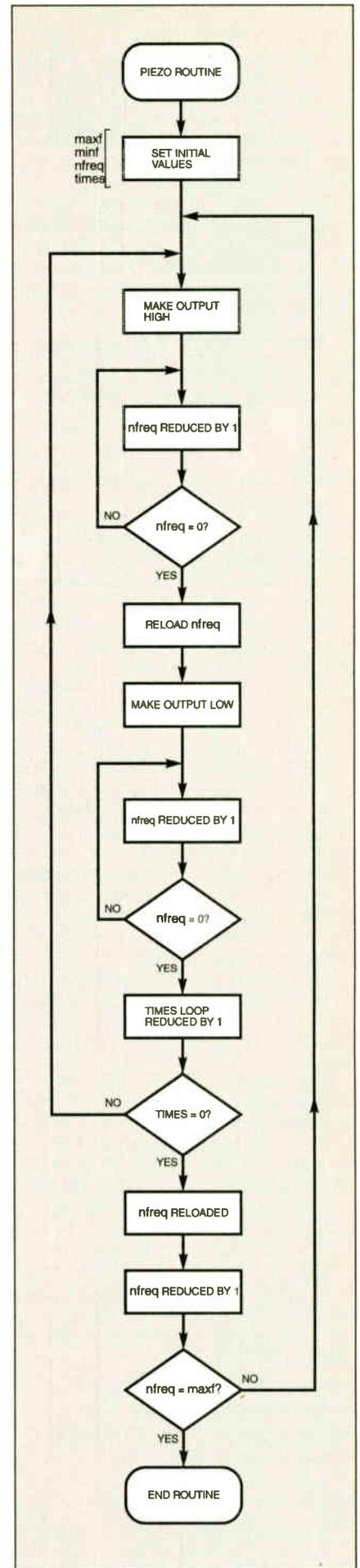


Fig.8. Flowchart for the piezo sweeper. The whole sequence takes approximately 130ms.

This may not seem very long, but what matters in conserving power is the ratio of the time taken to run the measurements compared and the time remaining asleep. If, for instance, it takes 50ms to take the measurements, the circuit is asleep for 98 per cent of the time with a resulting extension of battery life.

The OPTION register has eight bits which must be set up in order to control the WDT and prescaler. The functions are shown in Table 2. For this application, the OPTION register must be set to contain the binary byte 11001111. The short main program section is shown in Fig.9.

Note that during a Sleep period, the I/O ports maintain the same conditions that they had immediately beforehand. Therefore, to minimise the current drawn, all the pins are made inputs (high impedance) before the Sleep command.

## CONSTRUCTION

Construction is very simple. The suggested stripboard component layout and track cut details are shown in Fig.10.

The thermistor can be soldered to a short length of wire such as thin audio coax. An improvement would be to waterproof the thermistor connections by dunking it in polyurethane varnish. The wire can be fed into the freezer via the door seal.

It is important to resist the temptation to add a light emitting diode as a battery indicator – the l.e.d. would take about a thousand times more power than the rest of the circuit!

The PIC should be plugged into the board via an 8-pin d.i.l. socket. The circuit and batteries can be housed in a plastic box to sit outside the freezer, a small hole being provided to glue the piezo sounder behind. You should not need to replace batteries very often.

Software and pre-programmed PICs are available as stated in this month's *Shoptalk*.

## TESTING

The circuit will work quite happily at room temperature. Once the batteries are connected (it seems to work well on 6V although this is higher than the maximum recommended).

Gently rotate preset VR1 until the threshold is found between the alarm bleating or not. Set it so that the alarm is just off. Then hold the thermistor in your fingers to warm it up, and the alarm

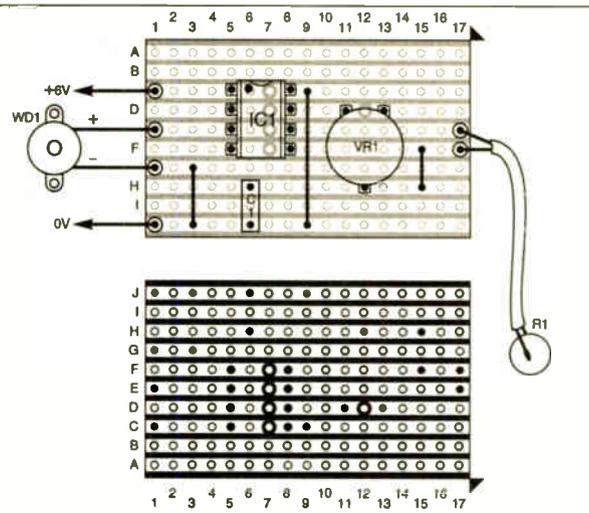


Fig. 10. Stripboard layout for the Freezer Alarm.

Fig. 9. Main program

```

; Main program start
start
  clrw dt          ; initialise I/O
  clrf  gpio
  movlw b'00001111'
  tris  gpio
  movlw b'11001111'
  option          ; wdt and prescaler
                  setup

  call  delay     ; settle down
  call  measureR
  call  measureT
  call  compare
  xorlw 0FFH     ; check if resT <
                  resR
  btsc  z         ; if so, set off alarm!
  call  alarm
  movlw b'11111111'
  tris  gpio     ; all pins high
                  impedance

  clrw dt
  sleep          ; until reawakened
                  by wdt
                  ; with a reset kiss

  goto start    ; should never reach
                  here!

```

Table 2. Option Register Bits

Bit 7	GPWU	Enable (0) or disable (1) wave-up on pin change
Bit 6	GPPU	Enable (0) or disable (1) weak pull-up resistors
Bit 5	TOCS	Timer 0 clock source
Bit 4	TOSE	Timer 0 edge select
Bit 3	PSA	Prescaler assignment: Assigned to WDT (1), or to Timer 0 (0)
Bits 2-0		Prescaler rate – division ratio (111 for WDT ratio of 1:128)

should sound; let go to allow the thermistor to cool again to room temperature, and the alarm should stop.

Once you are convinced all is well, put the thermistor in the freezer, and after allowing time for the temperature to stabilise, increase the resistance on the preset so that the alarm threshold is set where you would like it.

In fact, the best way to find out if the batteries are OK is to let the thermistor warm up a bit when you open the freezer – if it is working and the alarm sounds, the batteries are fine!

## MODIFICATIONS

As mentioned earlier, the techniques explained allow simple modifications to change how the circuit operates:

a. To make the alarm work if something is too cold rather than too warm (for example as a greenhouse frost alarm), simply swap over the connections to pins 6 and 7. Alternatively, make the appropriate swaps in the software.


b. The method can be adapted for any resistance changes – for example, the alarm could be made light-sensitive by using an l.d.r. (light dependent resistor) instead of a thermistor. Whatever thermistor or other device is used, VR1 needs to have a resistance which can be set to the same that the device has at its operating threshold.

c. An important design consideration concerns the value of the capacitor C1. Once the resistance of the appropriate sensor is known, the variable preset resistor needs to have the same value. However, the counter which waits for the capacitor to charge to its threshold must not overflow. This will happen after 320ms with this design's value for C1. Therefore, ensure that  $C(\mu F) \times R(k\Omega) < 320ms$ .

d. The circuit is remarkably accurate and stable. Because of the timing method of comparing the two resistors, any changes in the supply voltage (within the parameters above), or changes in the capacitance value caused by temperature or ageing, have virtually no effect.
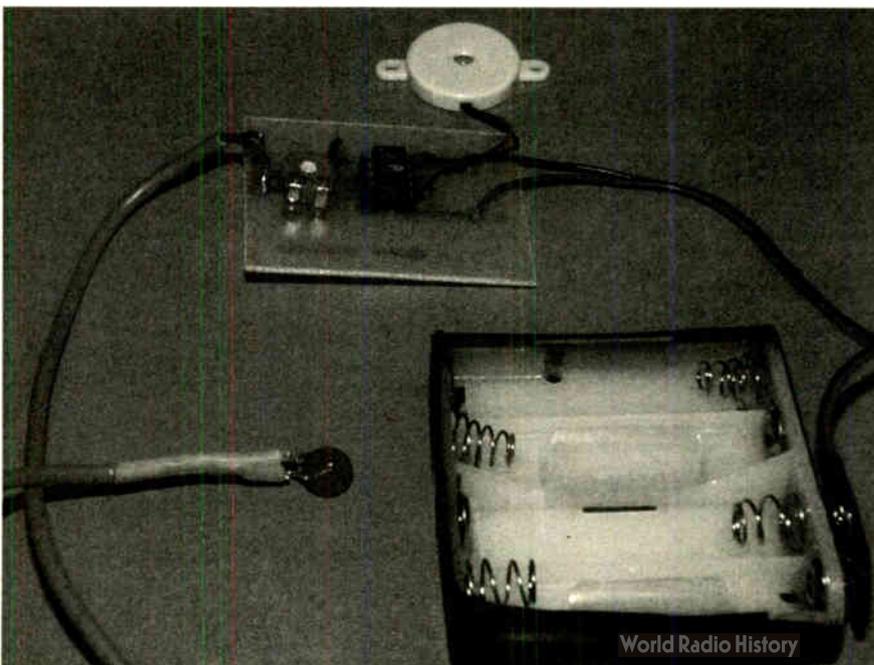
## ACKNOWLEDGEMENTS

The author expresses his thanks to Mrs Jan Edwards for her help in this project. □



# New Technology Update

*With a growing awareness of global warming, scientists are looking at ways of using dye molecules to produce more efficient solar cells, reports Ian Poole*

**S**olar cells might seem to be an ideal way of generating electricity. They convert the plentiful supply of sunlight that is freely available in many areas of the world into useful electricity.

Whilst this may seem to be an excellent idea in theory, reality has been quite different and very few solar cells are used. The main reason for this is that a large area needs to be covered by solar cells to enable a useful amount of electricity to be generated. This means that the costs are prohibitively high for most applications.

The raw silicon from which the solar cells are made is plentiful and cheap. Unfortunately the processing costs mean that the completed cells are expensive, especially considering the areas that have to be covered to collect a useful amount of light for conversion. If solar generated electricity is to become common, then cheaper methods of converting the sunlight into electricity are needed.

## Photosynthesis

In the search for more efficient and cost effective methods of converting sunlight into electrical energy, scientists have investigated the way in which plants convert solar energy into chemical energy to explore any leads that could be followed and utilised for electrical energy conversion. This line of research was first investigated in the 1970s.

The basic idea that was adopted was to use a layer of dye molecules that are highly absorbent to light. This is placed onto the surface of a semiconductor and once the dye is excited it delivers an electron into the conduction band. By adopting this approach the operation of the device is no longer dependent upon the absorption level of the semiconductor but the dye, over which there is more control.

The drawback of using this approach is that the electrons move very slowly through the dye layer, and this reduces the efficiency of these devices considerably, even if the dye layer is made very thin. Initially efficiency levels of only 0.01% were achieved, and this is far less than that achieved by the traditional semiconductor techniques.

## New Concept

To overcome this problem a new approach was adopted by the Swiss Federal Institute of Technology. Using their method they believe the new cells will offer the possibility of a significant reduction in the cost of solar generated electricity due to the very simple construction of the cell.

In the new cell, light absorption occurs in what is termed a mono-layer of dye. This is adsorbed chemically at the surface of a semiconductor forming a layer that is only 1µm thick. Instead of using one continuous

layer, the new cell uses small particles that are held in a colloidal solution.

When the dye is excited by a photon of light, the dye is able to transfer an electron to the semiconductor. If an external circuit is connected to the cell a current will flow as a result of the potential that is created by the transfer of the electrons. The potential is a function of the structure of the semiconductor and of the dye.

## Cell Structure

The solar cell itself consists of two conducting glass electrodes in a sandwich configuration with an electrolyte separating the two, see Fig.1. During the fabrication of the cell a layer of titanium dioxide is deposited onto one of the electrodes. This is achieved by using a colloidal preparation of mono-dispersed particles. The resultant layer of titanium dioxide is very porous and has a high surface area. This allows the distribution of dye molecules into the titanium dioxide.

The layer is heat treated to enable the resistivity of the film to reduce to a sufficiently low level to ensure resistance losses are within acceptable limits. Then the electrode with the oxide layer is immersed in the dye solution for several hours. The porous oxide absorbs the dye very efficiently giving an intense colour to the film.

The dye coated electrode is put together with another conducting glass electrode and the space between them is filled with an organic electrolyte. This second glass plate has a reflecting platinum plate to ensure light reaching it is reflected back into the cell. After making provision for the electrical contacts with the two electrodes the assembly is sealed.

## Greater Efficiency

The absorption of light using only a single molecular thickness of dye would be very low if it was not for the construction technique used. The fact that a very rough porous structure is used instead, allows for much greater levels of efficiency to be achieved because there is a far higher surface area presented to the light. A further advantage is gained from the fact that the semiconductor structure is nano-crystalline and this spreads the light over the whole area, further increasing the efficiency.

It might be thought that the heterogeneous structure of the semiconductor

would lead to a high level of resistance within the device and large losses. However, the reverse is true and electrons are able to diffuse in the bulk matter towards the supporting conductor with almost no energy loss.

Also, it does not suffer the same problem of a reduced percentage efficiency under low light conditions that traditional semiconductor cells suffer. Traditional cells suffer from hole-electron recombination in the semiconductor, and this reduces the efficiency, particularly when light levels are low.

## Other Research

Now that the basic idea has been proven, more research is ongoing to find some solid-state substitutes for the liquid electrolyte as this will make its manufacture much easier. It will also enable the complete solar cell to be far more robust than it can currently be made. Some ideas have already been tried and results using conductive polymers such as those used in light emitting diodes may prove to be promising.

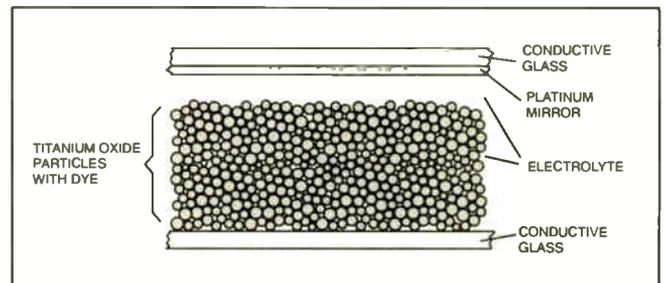


Fig.1. Structure of the solar cell using organic dye and titanium oxide particles.

Another problem that is facing the researchers is that purifying some of the materials used in the new processes is neither cheap nor easy at the moment. After ten years of research into the new cell there is still plenty that needs to be done. However, success will bring with it large returns because there is a growing awareness of global warming and new initiatives like these are likely to pay off the research and development costs many times over.

Other groups are also investigating similar technologies. For example, Bell Labs have produced a solar cell that is based around pentacene, an organic semiconductor. Reports indicate that this achieved efficiency levels of around 4%, but they still need to investigate many aspects such as the effect of ultraviolet light on the organic semiconductor.

These new developments often take ten to fifteen years to be completed but reports indicate that the new solar cells could be available in five years or so.

# CROWNHILL PIC BASIC

Write and compile your first program in under 5 minutes  
Distribute your applications ROYALTY FREE  
Technical Support direct from the author  
Dedicated user group mailing list  
Easy to navigate Windows IDE  
CDROM includes software and example programs  
Book Includes worked examples and projects  
Supports the popular PIC micro's including Flash devices



Crownhill PIC BASIC PRO produces tight concise code from your programs, written in the easy to learn yet powerful BASIC language. The compiler will produce code for the popular 12-bit and 14-bit micros.

For a FREE LITE version of PIC BASIC PRO visit [www.letbasic.com](http://www.letbasic.com)

The PICBASIC PLUS Compiler presents a range of interfacing solutions for the most exotic peripherals. Such as the I2C bus, Alphanumeric and Graphic types of LCD, and 2 or 3-wire SPI.

A FREE Lite version of PIC BASIC Plus! is available from [www.letbasic.com](http://www.letbasic.com)



For more in-depth information about our products please visit our website at [www.letbasic.com](http://www.letbasic.com)


LITE versions of both products are available from [www.letbasic.com](http://www.letbasic.com)

all prices exclude delivery and VAT @ 17.5%

Crownhill Associates Ltd  
32 Broad Street Ely Cambridge CB7 4AH  
Tel: 01353 666709 Fax: 01353 666710  
Order Online: [www.letbasic.com](http://www.letbasic.com)

Free Download @ [www.letbasic.com](http://www.letbasic.com)

## PICS BREAK 1MB BARRIER.

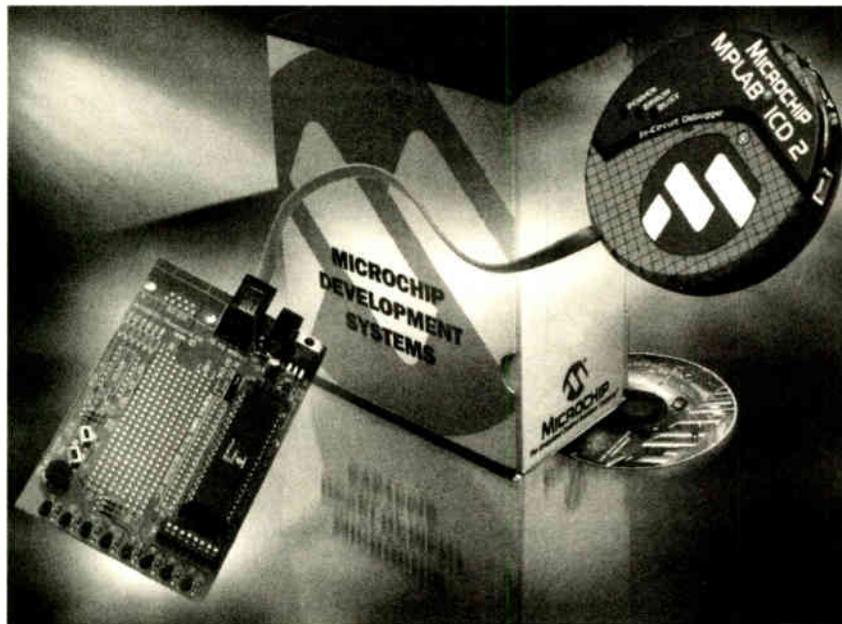

MICROCHIP'S new Flash microcontrollers are the first to break the one megabit memory barrier. The PIC18F6620, PIC18F8620, PIC18F6720 and PIC18F8720 offer field programmability, larger memory, a higher pin count and the most feature-rich peripheral set that Microchip has produced so far.

Programming times allow a 1-megabit array to be fully erased and programmed in under two seconds. The '620s feature 64K bytes of Flash memory, while the '720s have 128K bytes (1Mbit). The '8620 and '8720 also have a linear address capability of 2Mbytes.

Microchip has also released a low-cost, in-circuit debugger and programmer. The PC-based MPLAB ICD 2 supports the PIC16F and PIC18F devices. As new devices become available, users will be able to download new software into MPLAB ICD 2, at no cost, creating a highly adaptable tool.

MPLAB ICD2 is available as a stand-alone unit or as an evaluation kit that includes a demonstration board and samples of the '18F452 and '16F877. The board features a 2 x 16 l.c.d., temperature sensor, EEPROM memory, i.e.d.s, piezo sounder and RS232 interface.

For more information browse [www.microchip.com](http://www.microchip.com).

## FARNELL COMBATS OBSOLESCENCE

COMPONENT distributors Farnell have launched Product Watch, an "obsolescence service", which gives customers advance notice of when components are about to become obsolete, and of any end-of-line and end-of-stock items.

It sounds an excellent innovation. Few of us can claim to have never been afflicted by designing a circuit whose components become obsolete or no longer attainable on the day the design is completed!

For more information email Farnell at [productwatch@farnell.com](mailto:productwatch@farnell.com).

## WCN SUPPLIES CAT

THE 32-page catalogue from WCN Supplies is another that enterprising hobbyists should have in their library. Component categories run from audio, batteries, cables, chargers and connectors, through the alphabet via models (including some delightful ones from Humbro), motors, passive components (resistors, etc), power supplies, relays, semiconductors, and right on to Zircon drill sets.

For more information contact WCN Supplies, Dept EPE, The Old Grain Store, Rear of 62 Rumbridge Street, Totton, Southampton SO40 9DS.

Tel/Fax: 023 8066 0700.

Email: [info@wcnsupplies.fsnet.co.uk](mailto:info@wcnsupplies.fsnet.co.uk).

## EPSON RADIO FAIR

SUNDAY 16 June 2002, is the date for *Epsom Radio and Electronics Fair*, at Epsom Downs Racecourse Grandstand, 10am to 5pm. The organisers, Radio Fairs, tell us that it had been perceived that there was a need for a major radio rally to be staged south of the Thames in the North Surrey area, ostensibly to replace the Sandown Rally which is no longer held due to commercial restrictions.

The Epsom fair is a one day event and will consist of private and trade stalls with added attractions throughout the day. Epsom Downs is considered to be an excellent venue as it is easy to get to from any direction.

A car boot sale and a bring and buy sale will be incorporated into the rally. Ken Macintosh and his band will provide entertainment during the day. As an added attraction to the event, morse testing facilities will be available. It is hoped that Dr Bob Whelan, president of the RSGB, will open this new style event. Refreshments and light meals are available. Car parking is free.

Free admission tickets will be made available to schools and colleges in the south east, to encourage new people to come into the hobby. Normal entry is £3, although concessions for wheelchair disabled and children will be priced at £2.50.

For more information contact Brian Cannon G8DIU, 38 Sandringham Road, Worcester Park, Surrey KT4 8UJ. Tel: 020 833 0092 (10am-6pm Mon-Fri).

Fax: 01737 279108 (24 hours).

Email: [Brian.Cannon@btinternet.com](mailto:Brian.Cannon@btinternet.com).

## MAPLIN'S C3 CAT

MAPLIN Electronics have introduced a mini-variant of their large paper-based catalogue. It is free and is described as being their new specialist catalogue focusing on their most popular lines from the world of components, cables and connectors. The C3 is said to contain all the essential items for your hobbyist projects or commercial applications.

David O'Reilly, Maplin's Marketing Director, says "I would like to draw your attention to a number of new features: firstly the extended price breaks for volume enquires . . . plus the launch of our new information centre which will help you with some key technical principles and calculations for your specific application".

For more information contact Maplin Electronics through any one their nationwide stores, or telephone 0870 264 6000. Fax: 0870 264 6001.

Email: [customerservice@maplin.co.uk](mailto:customerservice@maplin.co.uk).

Web: [www.maplin.co.uk](http://www.maplin.co.uk).

# R.F. SOLUTIONS



RADIO communications modules in various forms are at the heart of the product range for R.F. Solutions Ltd. Their latest catalogue consists of 70 A4-size pages in a ring-binder, and details a broad selection of remote control systems, including Microchip's Keeloq encoders and decoders, radio telemetry systems, pager control, r.f. modems, and radio modules principally based on the standard frequencies of 315/433MHz, although modules operating at other frequencies are available.

Amongst the other products offered are Microchip PIC emulator tools, compilers and programmers, an r.f. pocket meter and radio evaluation boards. There is also a 150-page book entitled *An Introduction to Low Power Radio*, which is aimed at the practical engineer and concentrates on discussing theoretical radio matters in an easy to understand manner.

It is interesting to note that R.F. Solutions has complimented its range of PIC emulation products with the introduction of a compact low-cost programmer. The MEL-EPICA enables quick and easy programming of 8-pin and 18-pin mid-range PIC devices. It runs within Win95/98/NT or DOS and is able to integrate with MPLAB. There is also a C compiler for "quick and easy coding" of PICs.

For more information, contact R.F. Solutions Ltd., Unit 21, Cliffe Industrial Estate, South Street, Lewes, E.Sussex BN8 6JL. Tel: 01273 488880. Fax: 01273 480661. Email: sales@rfsolutions.co.uk. Web: www.rfsolutions.co.uk.

## BUBBLE-TIME

By Barry Fox

CALTECH, the Californian Institute of Technology, is patenting a new, eye-catching method of billboard advertising, using bubbles (W0 01/35379) which is sure to set constructors thinking.

The system can be scaled down to display time on a domestic clock. A container, like a very thin fish tank, is filled with transparent viscous liquid. On the rear side of the tank, a matrix of piezoelectric pump holes release globs of coloured liquid with slightly different viscosity. As the globs escape they float slowly up or down, like bubbles.

The pump holes are in groups, like the light sources of a digital display, to create alphanumeric characters or graphics. Caltec says the system works well with coloured detergents. Experimenters will doubtless come up with their own variations on the new theme.

## PLUG IN AND FLASHGO

By Barry Fox

THE computer industry uses five different miniature memory card formats for digital cameras, handheld computers, PDAs and MP3 players; Compact Flash, Smart Media, Multimedia Card, Secure Digital and Memory Stick, as well as IBM's tiny Microdrive hard disk. Users must use proprietary leads and software to connect each device to a PC. The law of cussedness ensures the right lead for the job is the one lead you have not got.

Imation – a spin-off from 3M – is now selling a reader with a single slot and matrix of contacts that mates with any known card. The reader connects to a PC by single USB lead and all-purpose control software. FlashGo costs around £60. If more formats emerge, Imation will sell matching adaptors that plug into the reader slot.

## Music On Time

By Barry Fox

RECORD companies want radio and club DJs to have new releases ready to play on official release day. But if records go out in advance, some DJs break the embargo. So Warner Music in the US has patented a system for enforcing the embargo electronically (W0 01/15428). A batch of music CDs for DJs will be encrypted so they play back only on a modified player.

The encryption is time-coded and the key tied to the official release date. To stop DJs cheating by advancing the player clock, the time code comes from GPS satellites. So everyone in the world gets to play their records for the first time, at the same time.

## National Vintage Communications Fair

THE *National Vintage Communications Fair* will be held at N.E.C. Birmingham on Sunday 5 May 2002. It is the Tenth Anniversary Special and doors open from 10.30am to 4.00pm at an entry price of £5. Do come and have a chat with our sister publication *Radio Bygones* on their stand!

All visitors will receive a free copy of the *Sound & Vision Yearbook's Collector's Guide*. This useful directory is really "the book of the show" but contains information that will be useful long after the show has closed.

For more information contact N.V.C.F., 13 Belmont Road, Exeter, Devon EX1 2HF. Tel: 01392 411565.

Email: sun.press@btinternet.com.

Web: www.anglefire.com/tx/sunpress/index.html.

## Mainline's Cats

THE latest Jackson Brothers catalogue of variable capacitors and drives has been received from Mainline Electronics. These 30 pages will be a highly useful source of information when looking for that vital radio component. Prices are quoted as a separate 4-page supplement.


Also received is Mainline's "Flyer", a 32-page catalogue of over 850 new products on offer. They say they have bought over 250 pallets of new surplus stock and have "many very unusual items, plus the usual freebies". The components are varied too categorise here, so get a copy of the two cats!

Contact Mainline Electronics, Dept EPE, Unit 1A Cutters Close, Coventry Road, Narborough, Leicester LE19 2FZ. Tel: 0116 286 5373. Fax: 0116 286 7797. Email: surplus@mainlinegroup.co.uk.


## Smaller DVD Cassettes

By Barry Fox


SONY thinks the world needs a new video format. At the IFA electronics show in Berlin, Sony unveiled MicroMV, a tape cassette 70 per cent smaller than existing Mini DV digital video cassettes. The tape runs for an hour and the cassette has 64KB of onboard solid state memory that automatically indexes every shot and tells what is on a tape by instantly displaying still images taken from the start of the shots.

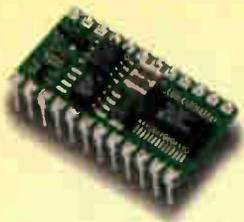


BS2-IC

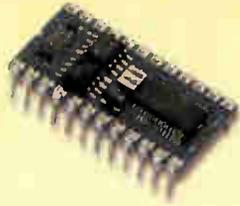


BS2-SX

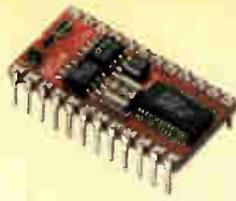

BS2E-IC

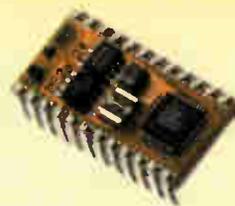


BS2P/24

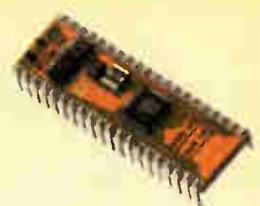

BS2P/40

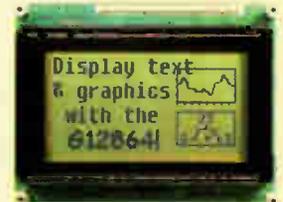**Parallax BASIC Stamps - still the easy way to get your project up and running!**



**Serial Alphanumeric and Graphic Displays, Mini-Terminals and Bezel kits**

# www.milinst.com




Animated Head



3-Axis Machine



Six-Legged Walkers

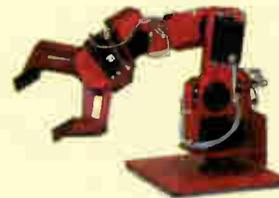

Robotic Arms




Bipeds

**Robotic models for both the beginner and the advanced hobbyist**



Servo Drivers

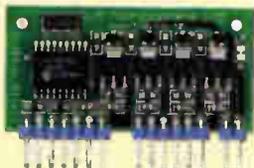

Motor Drivers



On-Screen Displays



DMX Protocol



U/Sound Ranging

**Animatronics and Specialist Interface-Control Modules**



Quadravox MP3 & Speech Systems



SensoryInc Voice Recognition



Parallax Ubicom Tool Kits



Tech-Tools PIC & Rom Emulators



BASICMicro PIC BASIC Compilers

**Development Tools**

Milford Instruments Limited Tel 01977 683665, Fax 01977 681465, sales@milinst.com

# PIC BIG DIGIT DISPLAY



JOHN BECKER

Microcontrolling giant 7-segment displays

**R**ECENTLY Dave Fisher of Display Electronics told *EPE* that he had acquired several thousand electro-mechanical "big digits". These had previously graced the platforms of British Rail as 6-digit 7-segment clocks. Yes, they were the familiar "click... click..." digits that surely any would-be passenger has watched mesmerised while waiting for that (*where IS it?*) train to arrive.

In the course of conversation, the question of *EPE* designing a suitable electronic interface for these digits came up. Would Tech Ed be interested? *Certainly*, was the author's timely response to a novel design idea.

## DISPLAY RESULTS

The resulting basic design is capable of driving from one to eight digits, with expansion up to 64 digits possible, as discussed later. They can be controlled via a standard 4 x 4 data entry keypad, or via a PC-compatible computer running under MS-DOS or Win95/98/ME.

A PIC16F84 microcontroller is the controlling device between the PC or keypad and the multiplexed digits. The PC software is written in QBASIC/QuickBASIC but can be run as a standalone program without the need for QB to be installed.

The digits are ideal for use in any situation that requires a large electronically controlled display where the data is to be input intermittently. Applications that

come to mind are sporting scoreboards, ticket draw results, display of outdoor temperature in public arenas – well, you've seen where large digits can be used, think up your own applications!

## MONSTERS

Since the digits were only large versions of 7-segment displays, reasoned the author before starting the design, they could be simply driven by a PIC through a minimal bit of multiplexing. No problem – or so it seemed until two arrived!

The digits are monsters in several senses. Overall, they measure 12in high, 9in wide and 2.25in deep (30.5cm x 23cm x 5.5cm). The angled display area is effectively 10in high x 7in wide (25.5 x 18cm) and comprises seven bright-yellow hinged segments.

In the absence of fully informative data, the first task was to establish some criteria about controlling the display segments. Basically all that was known from a rudimentary data sheet was that a pulse of 12V d.c. for about 0.25secs was required to turn segments on and off, and that the pinouts of a built-in connector were shown. There was no mention of the current required, although there was a warning not to connect d.c. to the segments for long periods otherwise damage/heating will occur.

The original manufacturer's name was printed on the rear of the digits, Bodet,

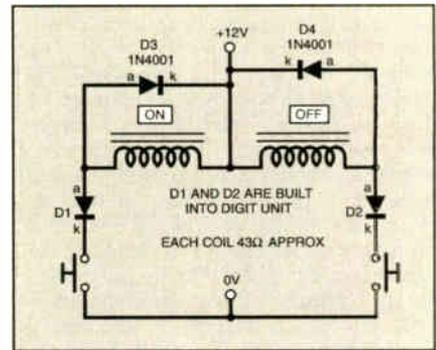


Fig.1. Basic circuit for controlling one segment.

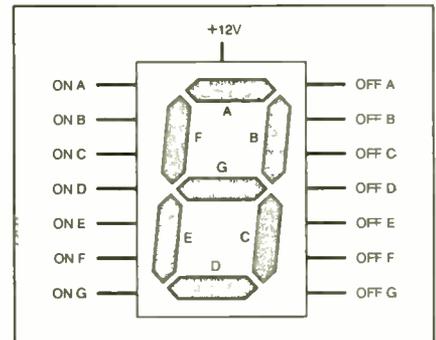


Fig.2. Each digit has 15 connections, 12V power input and two on-off controls for each segment.



along with the message Made in France. Doing a [www.google.com](http://www.google.com) search revealed the company at [www.bodet.com](http://www.bodet.com), but no electronic specifications could be located, other than a schematic for one segment (see Fig.1 and Fig.2). An email to Bodet for data produced no response. Time for experiments!

Briefly connecting an ammeter between a segment and a 12V power supply revealed the current required to activate the mechanical flap – around 280mA. What?! Surely not? An ohms check across the various controlling coils showed a typical d.c. resistance of 43Ω. Wow, yes indeed, that unscientific test had shown a current figure in the right ballpark!

Furthermore, there were seven segments to be controlled – about 2A per digit, and users would probably need several digits. More used to dealing with liquid crystal displays needing only a handful of milliamps, rather than two thousand milliamps, the

author recognised that the digits were more than just monsters in size.

## RESEARCHING DESIGN

Having numerous data books and CD-ROMs is always to be recommended. These days, so is Internet access. Using a mixture of sources, a couple of evenings were spent researching the type of semiconductors that were available to handle such currents in a multiplexed situation. It was a foregone conclusion that they needed to be capable of being PIC-controlled.

Any idea of using any form of discrete transistor, power-FET or otherwise, was rejected. Such techniques were fine years ago, but hardly today's technology when multiplexing – even less so regarding any suggestion of relay control. No, it had to be semiconductors in integrated circuit form.

Anyone familiar with controlling 4-digit 7-segment light emitting diode displays will know that they can easily be controlled by multiplexed signals – a common 7-line "bus" feeding identically to all segments of all digits, and then separate power supply lines, each feeding to its own digit. The technique required then is to send out segment control data along the common bus, and to only turn on digit power lines individually at the appropriate moment.

However, data sheet browsing suggested that switching seven segments simultaneously at a total of 2A or so could present a significant problem. Perhaps switching segments individually at about 280mA would be more sensible?

There are many chips that can provide 1-of-8 output selection in response to a 3-bit control code. Such chips include the 74HC138, whose outputs are normally high, but go low individually when selected by the appropriate control code. The 74HC237 operates with the opposite output logic, normally low but going high when selected.

Although the outputs of these devices cannot handle the sinking or sourcing of 280mA, or a voltage of 12V, they are capable of driving intermediate high-current buffers. The question then became one of which buffers were available?

## LINE DRIVER

After considerable research, it was decided to use the 7-stage line driver type ULN2004A to activate the segments. It can sink 500mA per stage, and is capable of handling voltages up to 50V.

This device also has the benefit of having built-in diodes across each output which inhibit back-e.m.f. generation when switching inductive loads, such as the segment coils (see Fig.3).

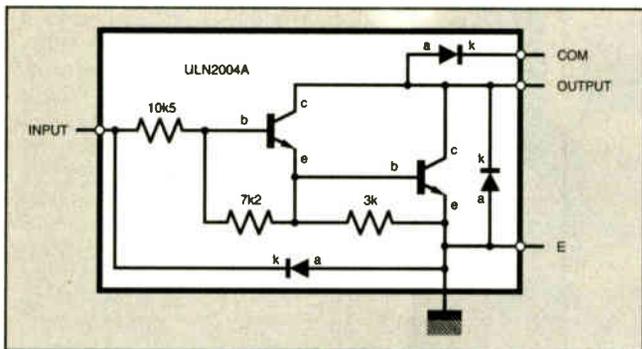


Fig.3. Schematic of one stage within a ULN 2004A 7-stage line driver.

It is a bipolar-fabricated Darlingtion device that requires a positive voltage at each input to turn on the respective open-collector output. Conveniently, each input has its own 10.5kΩ series resistor, removing the need for external resistors (such as required in the control line feeding into the base of a "normal" discrete transistor). The inputs are also diode-protected.

Using a 74HC237 multiplexer, the seven segments can readily be controlled directly through the ULN2004A driver.

## COMMON ANODE

That took care of current sinking through the segments. The problem then became that of providing multiplexed power to each digit. If you relate the concept to a common-anode 7-segment i.e.d. matrix, the individual segment cathodes had now been catered for – it was the common-anode current control that was now required. In other words, a current source was needed, at a minimum of 280mA.

It had been expected that as multiple high-current sinking paths were available in one i.c., as with the ULN2004A, so multiple high current sourcing devices would be equally common.

It was found that there were many options available if a source current of no more than 100mA were required, especially as the current would be pulsed intermittently. However, the requirement for at least 280mA presented a seemingly unsolvable problem, unless discrete transistors were used – which the author was determined not to resort to. Quite simply, no ideal i.c. devices could be found.

Briefly, power op.amps such as the L272 dual device seemed a possible solution, but that was not deemed "tidy"! Eventually, it was decided to accept a less-than-optimum option, to use an L293DN quadruple Half-H driver.

This has four devices that can each be set to sink or source a current of up to 1A at a voltage from 4.5V to 36V. It also has two enable inputs which allow pairs of drivers to have their outputs placed into a high-impedance state (see Fig.4). Additionally, it too has in-built diode protection.

The device is intended for reversible motor and solenoid control. The term Half-H refers to the bridge configuration in which the pairs of drivers can be operated. It seemed suitable for this application since no other appropriate device format could be found. Consequently, two L293DN devices are used in the main circuit, each providing power for four multiplexed digits. They are under combined control of another 74HC237 1-of-8 controller.

The L293DN, however, has the unfortunate side effect of consuming around 20mA even when the outputs are in a high impedance state. The "enable" inputs do not place the device into a quiescent state in high-impedance mode, unlike many logic devices that you may be familiar with. Regrettably, it is not cheap.

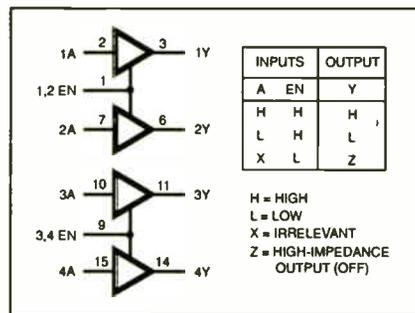


Fig.4. L293DN pinouts and logic table.

Do not use any other type of L293 device. The L293DN (note the DN suffix), is a 16-pin device with diode protection. Other L293 device types may not have the same characteristics (the L293E, for instance, has 20 pins and cannot be used).

## MULTIPLEX CIRCUIT

A simplified block diagram of the control requirement is shown in Fig.5.

The circuit diagram showing the multiplexing and digit drive devices is given in Fig.6. Control data originates from a PIC16F84 microcontroller (discussed presently in relation to Fig.7). Through multiplexer IC1, 3-bit control data selects which digit is to be powered via source drivers IC2 or IC3.

As shown in Fig.6, and designed on the printed circuit board to be described later, eight digits (one "bank") can be controlled by these two drivers. Additional digit source drivers can be added separately if required (on stripboard for example, although no constructional details on this are offered).

If fewer than five digits are to be controlled, IC3 can be omitted.

The eight outputs of IC1 are common to all digit drivers, and IC1 does not need to be repeated if additional banks of drivers are added.

The software allows two additional banks of eight digits (a total of 24 digits) to be controlled without modification to the program. Readers who are familiar with PIC and QB programming could modify the software to cope with multiplexing up to 64 digits if an additional 74HC237 multiplexer is used (see later).

Segment selection is provided by a 3-bit code fed to multiplexers IC4 and IC5. These in turn control segment sink drivers IC6 and IC7, respectively. Only seven outputs of these multiplexers are used.

The two multiplexers are under "chip select" (CS) control by separate CS1 lines (pins 6), so that segment On or Off control is achieved not only in respect of the 3-bit code, but also in terms of current-sinking pulse duration (more later).

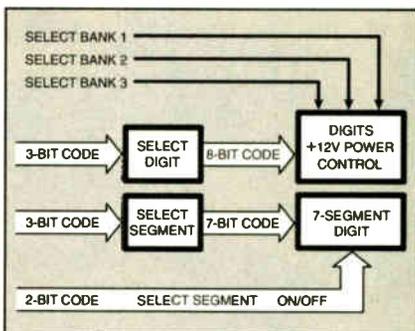


Fig.5. Multiplexed control logic.

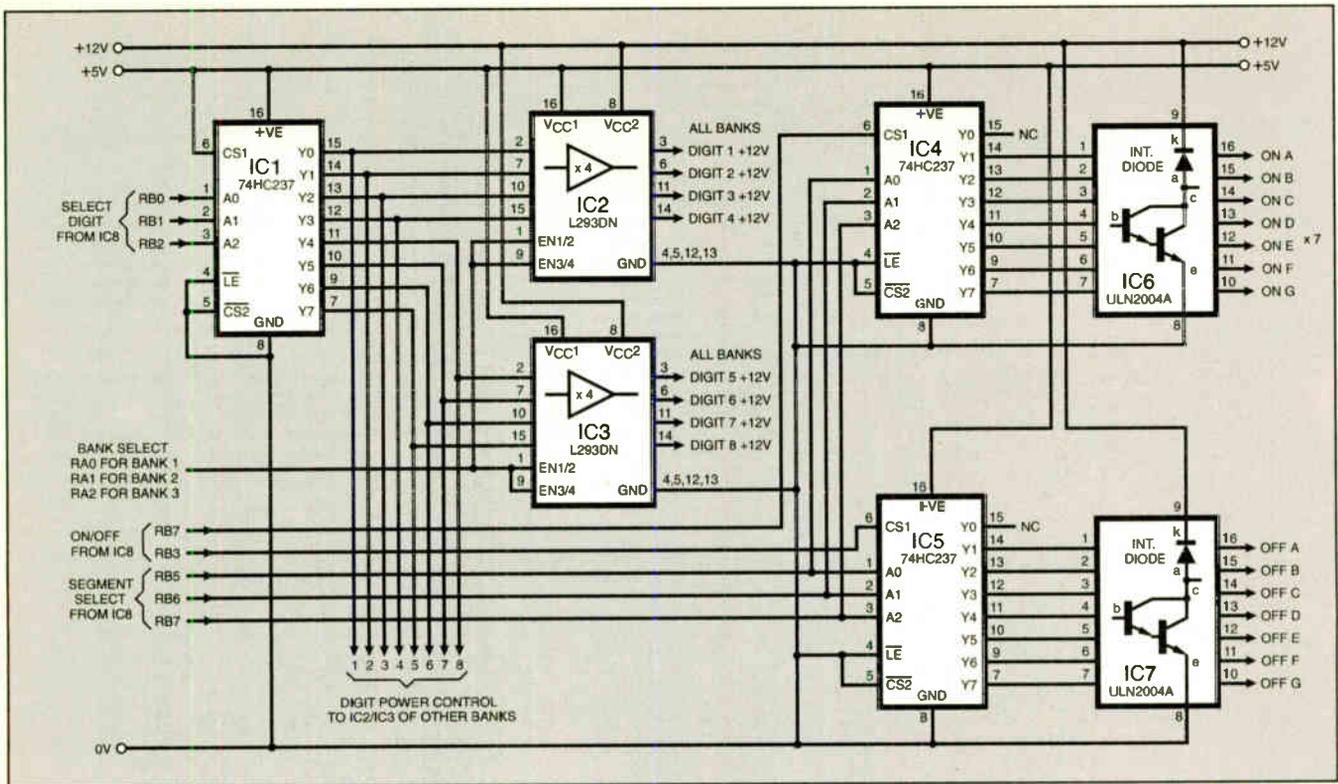


Fig.6. Circuit diagram for the multiplexed control of the digits, basically for eight, but can be modified to control 64 digits.

## MICROCONTROLLER

Because of the multiplexing arrangement, a PIC16F84 microcontroller is readily suitable for this design, see Fig.7. It is capable of being user-controlled either via a 16-key (4 x 4) data entry keypad, or via a PC-compatible computer, running under MS-DOS or Win95/98/ME.

The PIC is run at 4MHz, as set by crystal X1. Port pins RB0 to RB2 control digit selection via IC1 (Fig.6), pins RB4 to RB6 control segment selection via IC4 and IC5, RB7 controls selection of IC4 (segment On control), and RB3 controls selection of IC5 (segment Off control).

Port pins RA0 to RA2 perform "bank" selection. As shown, they can control up to three banks of eight digits. If they are used to control another 74HC237 1-of-8 multiplexer, however, they could control eight banks (with suitable software modification).

Port B pins are also used for inputting data from a 16-key keypad, or from a PC. Note that it is unwise to connect a keypad and PC simultaneously since one might adversely affect the other. The PIC itself is protected against its Port B pins being undesirably affected by external PC/keypad control by the inclusion of buffer resistors R1 to R8.

Pins RA3 and RB7 are used by the software to achieve "handshaking" with the PC when the unit is under computer control.

Pin RA4 is used in a manner possibly not seen by readers before. It is used in oscillatory mode under software control and at a rate set by preset VR1 and capacitor C5. It allows the segment control pulse width to be varied. The controlling software routine will be discussed towards the end of this article.

As usual with the author's PIC designs, on-board programming can be performed via a 4-pin connection (TB1). Adverse

effects on the +5V power line are prevented during programming control by the inclusion of resistor R9 and diode D1.

## POWER SUPPLY

Power for the digits needs to be 12V d.c. This may be provided from any source capable of supplying at least 500mA (to provide "headroom" when a segment is activated). It does not need to be stabilised. A 12V car battery is suitable.

The prototype was found to operate with a supply voltage as low as 9V (with resultant reduction in current consumption).

Whilst the 13.5V (or so) of a fully charged battery seems acceptable, it would appear to be unwise to allow the supply to significantly exceed this voltage. The voltage, current and pulse duration limits for the digits are not known since Bodid did not respond to the author's request for information.

The digital control i.c.s require to be powered at +5V d.c. (which *must not* be exceeded). This is provided from the 12V line via regulator IC9, which can supply up to 100mA of sustained current. Be aware, though, that on the prototype it was

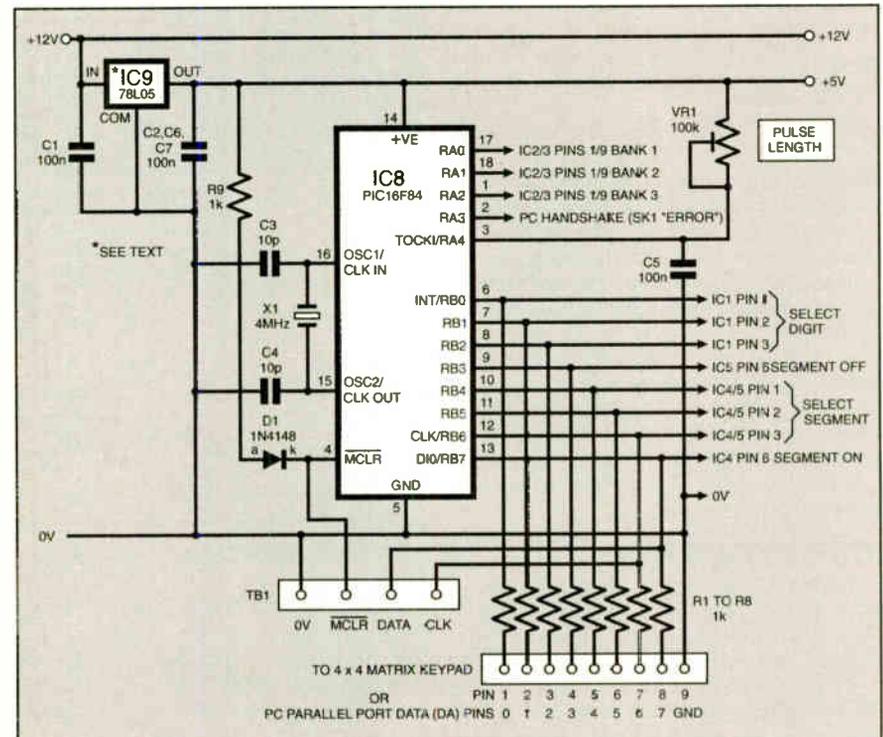


Fig.7. Circuit diagram showing the PIC16F84 control connections, plus power supply.

# COMPONENTS

## Resistors

R1 to R9 1k (9 off)  
All 0.25W 5% carbon film

See  
**SHOP  
TALK**  
page

## Potentiometer

VR1 100k min.  
preset,  
round

## Capacitors

C1, C2,  
C5 to C7 100n ceramic, 0.2in pitch  
(5 off)  
C3, C4 10p ceramic, 0.2in pitch  
(2 off)

## Semiconductors

IC1, IC4,  
IC5 74HC237 1-to-8  
multiplexer (see text)  
(3 off)  
IC2, IC3 L293DN 16-pin Half-H  
driver (see text) (2 off)  
IC6, IC7 ULN2004A 7-way  
Darlington line driver  
(see text) (2 off)  
IC8 PIC16F84  
microcontroller,  
preprogrammed  
(see text)  
IC9 78L05 +5V 100mA (or  
7805 +5V 1A) regulator  
(see text)

## Miscellaneous

X1 4MHz crystal

Printed circuit board, available from the *EPE PCB Service*, code 341; RW44 10-inch 7-segment electromechanical display (big digit), quantity to suit (see text); 4 x 4 data entry keypad (optional - see text); stranded colour-coded connecting wire (individual wires or ribbon cable); 12V d.c. power source, min. 500mA output; 1mm terminal pins or pin headers; 16-pin d.i.l. socket (7 off, see text); 18-pin d.i.l. socket; printer port connectors to suit (optional - see text); solder, etc.

Approx. Cost  
Guidance Only

**£20**  
excluding hardware

required to constantly provide around 40mA (due to the two L293DN devices). It is thus likely to get a bit warm, especially if the source power is 12V or greater.

If it is found to shut down through excessive heat (it is thermally regulated), change it to a standard 7805 +5V 1A device. It is perhaps prudent to switch off power during long periods of digit inactivity.

Note that the digits themselves only consume power during the brief pulse that changes their segment display position.

Capacitors C1, C2, C6 and C7 help to maintain powerline stability.

## CONSTRUCTION

Printed circuit board component and track layout details are shown in Fig.8. This board is available from the *EPE PCB Service*, code 341.

Assemble in order of link wires first, including the one marked "Bank 1 Link" - this will be discussed under "Expansion". Note that some links go under the i.c.


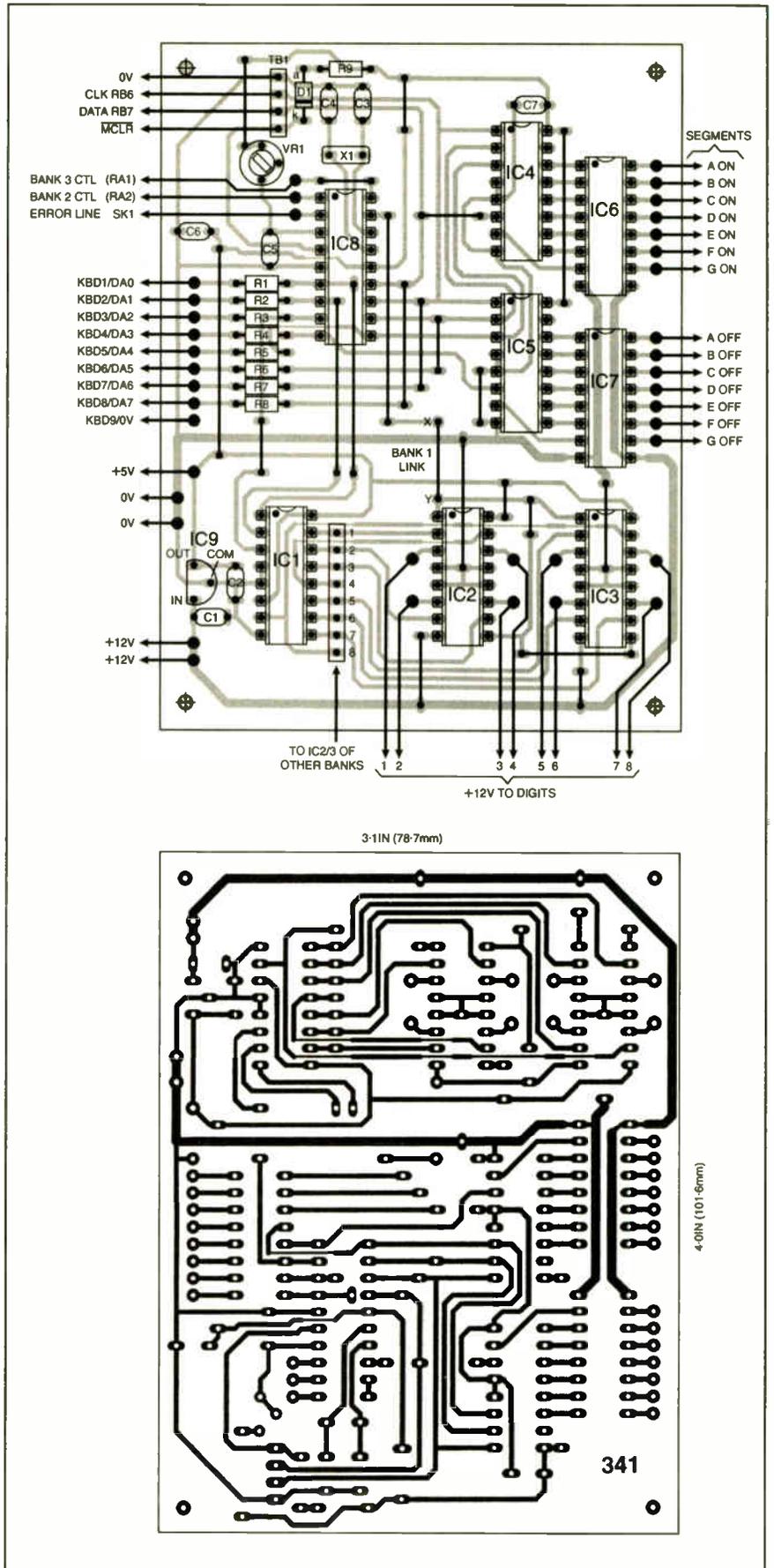


Fig.8. Component layout and full-size underside copper foil master track pattern.

positions. Follow with the d.i.l. (dual-inline) i.c. sockets and then continue in any convenient order. Insert 1mm terminal pins at the external connection points, but omit those alongside IC1 which are only needed if more than eight digits are to be controlled.

There are two choices of data input, as said earlier. They are connected to the board at the pins to the left of resistors R1 to R8.

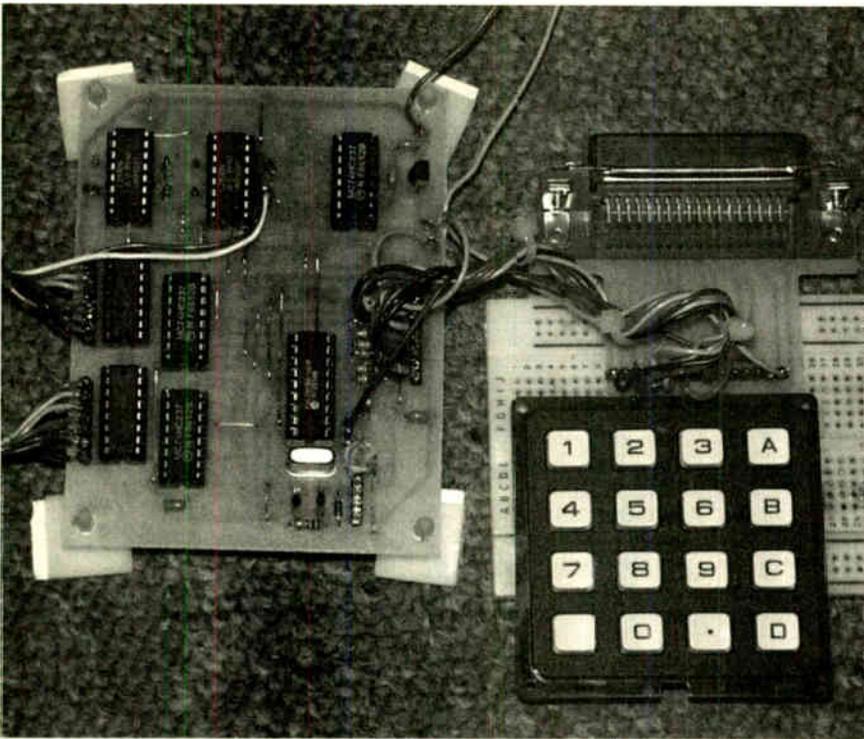If using the data entry keypad, connect its pins, as shown in Fig.9, to the similarly numbered points on the board. Keyboard



Prototype display controller board during development testing using a plug-in breadboard to temporarily connect a data keypad and a PC via a Centronics connector (mounted on the p.c.b. used with Teach-In 2000 Part 4 – Feb '00).

pin 9 is a ground (0V) connection for the pad's frame.

If using a PC as the data source, it needs to be connected from its parallel printer port to the board. The easiest way is to use a standard printer cable with pre-attached connectors. The "printer end" of the cable has a 36-way male D-type Centronics connector which requires a matching female type at the unit end. The latter should be hardwired to the board at the designated points using short lengths of insulated stranded wire. The pinouts for a right-angled female connector are shown in Fig.10.

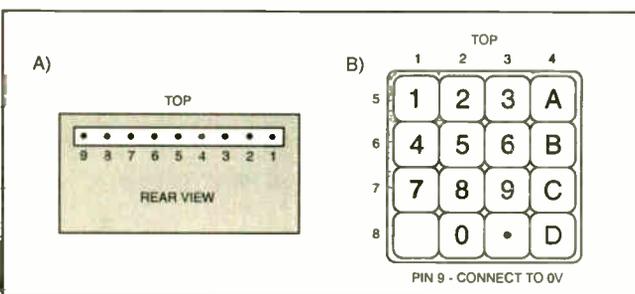


Fig.9. Keypad connection details.

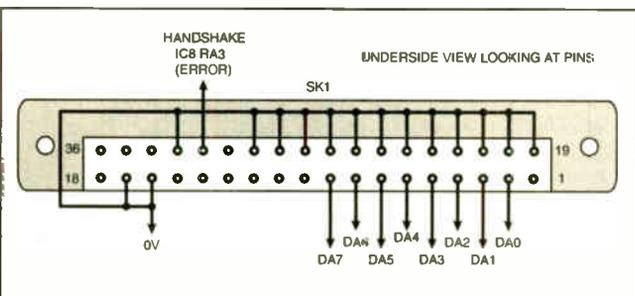


Fig.10. Connections to a 36-way D-type Centronics female connector used in conjunction with a standard PC parallel port cable.

Alternatively, the unit can be hardwired to a separate 25-way D-type male connector plugged into the back of the computer – 10-way ribbon cable would be ideal. The connector's pinouts are shown in Fig.11. Note that the "Error" line connects to the board pin situated near IC8. ("Error" is the name given in respect of that line's normal purpose when interfaced to a printer.)

Before inserting the d.i.l. i.c.s, do a thorough examination of the board for faulty assembly and soldering. Then only insert them after you have established that regulator IC9 is correctly supplying +5V at its output. Check this again once the i.c.s have been inserted.

Be aware that they are CMOS devices and require the normal handling precautions, discharging static electricity from your body by touching the bare metal of something earthed before handling them.

Adjust preset VR1 to a fully-clockwise setting (maximum pulse length) before testing the system.

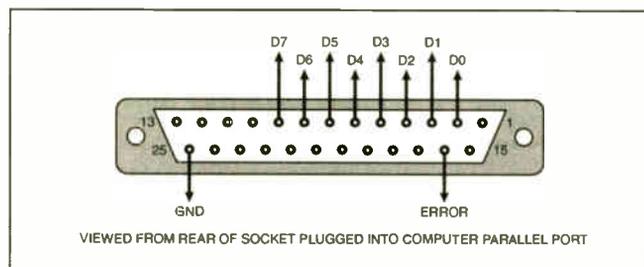


Fig.11. Alternative connections via a 25-way male D-type connector.

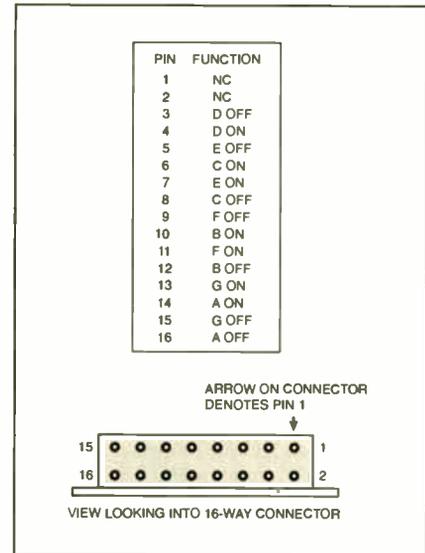


Fig.12. Pinouts for the connector mounted as part of the digit assembly.

## DIGIT WIRING

Monstrous is again a term that can be used in respect of the digit connection requirements. The digits need to be wired in parallel back to the control board. However, although the manufacturers have provided a single connector on each digit, this only allows for one set of the 15 connection wires needed.

One would have expected two connectors, one for the cable harness arriving from the control board, another for the harness that then has to be connected serially to the next digit.

The author offers no recommendations about using the digit's own connector, although for the sake of good order, its pinouts are shown in Fig.12.

It was decided that it was easier to hardwire the connections to solder pads at various positions on the back of the digits. They are the pads to which the manufacturer's rectifier diodes (mounted inside the digit box) are soldered. The correct connection points were found experimentally and are shown in Fig.13. Ignore the unused pads.

Whereas the 14 segment wires of each harness are connected in parallel to each digit, each digit needs its own separate +12V power supply wire, originating from the control unit p.c.b. as shown in Fig.8. Make the +12V connections in numerical order in relation to the digit positions in the proposed display.

Before you fully interwire the digits, though, it is recommended that you just wire-up for the first one and check out the system.

## KEYPAD OPERATION

The software has been written so that on power being switched on the PIC sets its Port B for input with the input pull-up resistors active. A check is then made to see if the inputs are connected to any source that pulls them low.

Under keypad control (with no keys pressed) there is nothing to pull the pins low and so the PIC assumes that a keypad is the data entry source.

Having established that fact, the software goes into a perpetual loop scanning the keypad for keypresses. The software routine used is a variant of that described in the author's *Using PICs with Keypads* of Jan '01.

In response to any keypresses, look-up tables are used to relate that input value to the data to be sent to the digits. The first table (VALUE) allocates the keypress data to a numerical value between 0 and 15. Another table (TABLE) then relates that value to a binary sequence in respect of the digit segments to be turned on.

The sequence is in the right-to-left order (bit 0 to bit 7) of segment A to segment G. For example, binary 01111111 turns on all segments, resulting in the 7-segment display of numeral 8. Binary 00000110, on the other hand, only turns on segments B and C, resulting in numeral 1 being displayed. The full table is shown in Listing 1.

### LISTING 1

TABLE:

```

addwf PCL,F
retlw %00111111 ; 0
retlw %00000110 ; 1
retlw %01011011 ; 2
retlw %01001111 ; 3
retlw %01100110 ; 4
retlw %01101101 ; 5
retlw %01111101 ; 6
retlw %00000111 ; 7
retlw %01111111 ; 8
retlw %01100111 ; 9
retlw %01110111 ; 10 A
retlw %01111100 ; 11 b
retlw %00111001 ; 12 C
retlw %01011110 ; 13 d
retlw %10000000 ; 14 blank
retlw %01000000 ; 15 -
GFEDCBA
    
```

Note that bit 7 in the 14th jump is set at 1. This prevents the PIC from returning a zero value from this location, which would otherwise be recognised as "no data entered from keypad".

Whilst it is suggested that decimal display values from 0 to 9 are retained, other segment arrangements could be provided for the other six positions by readers having their own PIC assembly-programming facilities, such as the author's *Toolkit Mk3/TK3* (Oct/Nov '01).

It is also worth recognising that 7-segment displays cannot in many instances be used to represent alphabet characters. For example, capital letter A can be represented, but lower case a cannot. Conversely, b can be, but B cannot (it would just look like an 8).

Also note that any letters having diagonals cannot be represented, such as K, M, N, Z, nor can T. It is worth experimenting to see what characters can be represented, and what compromises you might have to


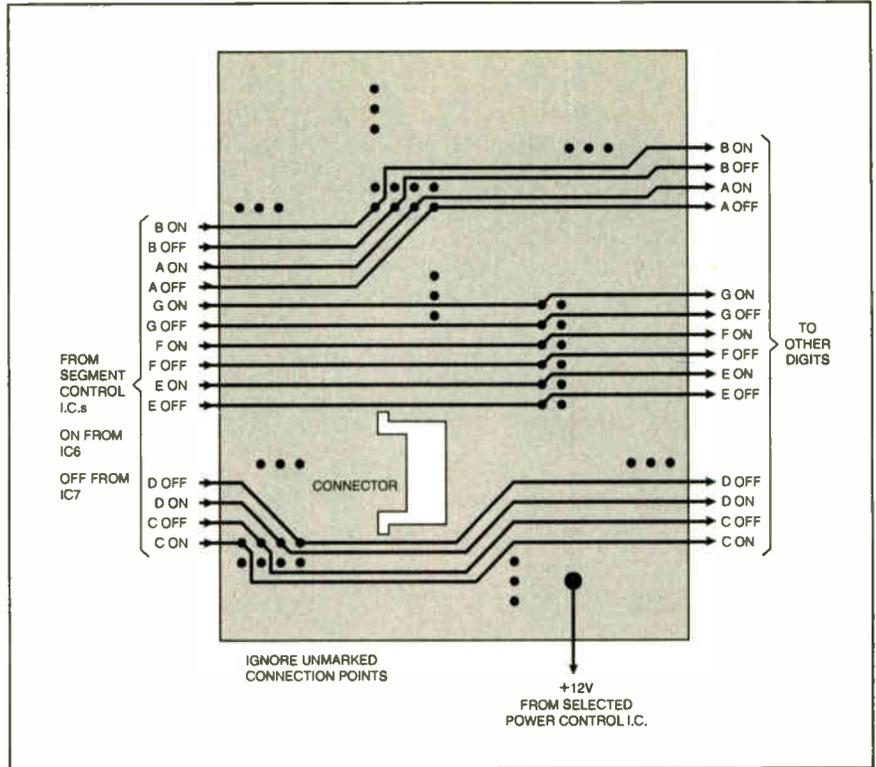


Fig.13. Wiring details for a single digit.

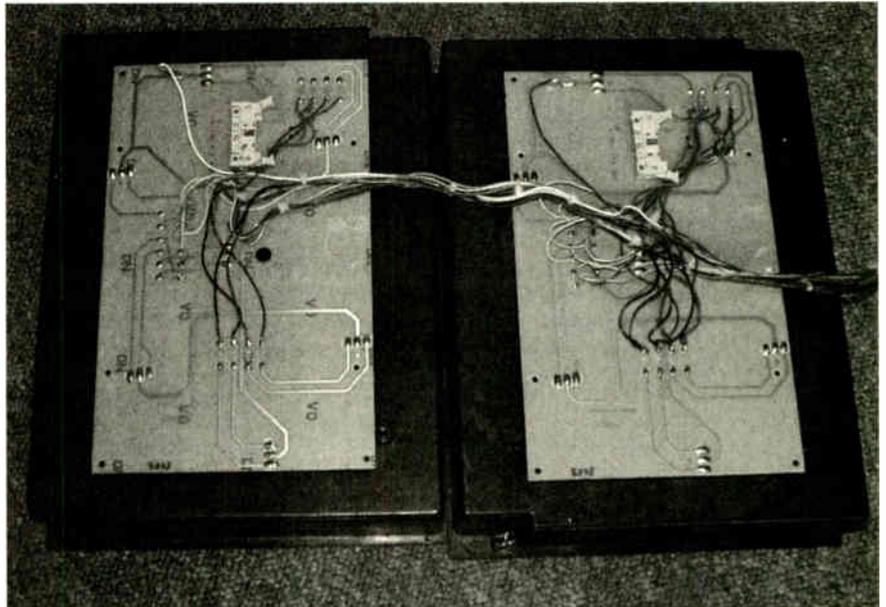

Interwiring between the two digits used during development.

make. You may recall that the author's *Teach-In 2000* series demonstration software illustrated the principle of 7-segment control.

Having established the segment code required, the PIC then has to send the corresponding data to the segments individually. From within a loop, the PIC reads each data bit position to see whether a segment should be On or Off. At each position it uses another look-up table (TABLE2 – see Listing 2) for the code needed to send to multiplexers IC4 and IC5 in order to control that bit.

The code also takes into account that the p.c.b. tracks are connected to the three control pins in the opposite order than might normally be expected (this was done for p.c.b. design simplicity). Only bits 6 to 4 are of importance in this table.

### LISTING 2

TABLE2:

```

addwf PCL,F
retlw %01000000 ; a
retlw %00100000 ; b
retlw %01100000 ; c
retlw %00010000 ; d
retlw %01010000 ; e
retlw %00110000 ; f
retlw %01110000 ; g
retlw %00000000 ; -
    
```

The code is output on the 3-line common bus feeding to IC4 and IC5. Which of these i.c.s is activated depends on whether the segment needs to be turned on or turned off. To turn on IC4 (segment On), bit 7 in the code is set high. If IC5 is required (segment Off) bit 3 is set high.

It is also necessary to specify which of the digits is the target for the segment information. This data is set into the code's bits 0 to 2, representing the number (1 to 8) of the digit in the allocated bank, and destined for IC1 (see Fig.6).

## DIGIT SELECTION VIA KEYPAD

Because the digits might be located away from the controlling keypad, and not be visible to the user, it was decided to allocate two keypad keys as digit stepping controls. At switch-on digit 1 is the default target, and any numeric data keyed in continues to be routed to it.

To choose Digit 2 instead, press keypad "D" (Digit step). This changes the control code fed to IC1, incrementing it from binary 000 to binary 001, so selecting digit 2. Display data is now repeatedly fed to this digit. Pressing "D" repeatedly steps through each digit position in turn, irrespective of whether the digit physically exists in the system.

To return to Digit 1 at any time press "C" (Clear back to start). It is not possible to step back individually from digit to digit. This, though, is a facility for which PIC-wise users could write a software routine. In this case it is suggested that key "B" is intercepted (Backwards) in a similar way to which letters "C" and "D" are intercepted.

Each time the digit number is stepped forward, the software increments a 24-value counter (rolling over to 1 again following 24). This not only provides information on which digit is selected (from 1 to 8), but also on which Bank it is in (Bank 0 to 2), using yet another look-up table. This results in Port A pins RA0, RA1 or RA2 being selected as appropriate (in Bank order).

Referring back to Fig.6 again, it will be seen that IC2 and IC3 are shown to be under selection control by pin RA0. If additional IC2 and IC3 devices are used they would be allocated to one of the other Port A pins, RA1 or RA2, in that order of Bank.

In this way, 24 digits can be stepped through by pressing key "D" the required number of times. Yes, it tests the user's counting ability, but seemed the best solution considering the limited number of keys available.

The provision of monitoring via an alphanumeric liquid crystal display was considered, but was rejected on the grounds of adding complexity to a moderately simple design.

PIC-knowledgeable readers could probably add l.c.d. facilities if needed. There are numerous examples of l.c.d. control in many of the published *EPE* PIC projects (especially in the author's designs). Such a routine could be integrated almost as a "library" file.

It is suggested that l.c.d. control is basically via Port B with the exception of the l.c.d. E line, which is better suited to control by the otherwise unused pin RA3 (it is only used when under PC control).

Line E cannot be satisfactorily controlled by Port B as all pins are in use for other purposes, which would cause undesirable l.c.d. response. It is only Line E that is critical in this context.

## COMPUTER CONTROL

When under computer control, data is fed to the PIC via the same connections as

the keypad (but preferably in the keypad's absence). It is in a different coding format to that used with the keypad, however.

Because of the full range of keys on a PC keyboard, is it possible to send a much greater variety of data to the digits. On recognition by the PIC that a PC is connected to it (see earlier), it goes into a different monitoring routine (COMPROG).

Synchronisation between the PIC and PC is maintained by using two handshake lines at the PIC end of the system, pins RA3 and RA7 as mentioned earlier. Port B pull-up resistors are turned off in this mode.

The first significant handshake action the PIC takes following switch on for PC mode, is to set pin RA3 high. This indicates to the PC that the PIC is ready to receive data. The PIC then sits in a holding loop until acknowledgement from the PC is received.

The PC software in its turn holds its printer port output DA7 low and waits for the RA3 = high signal to arrive via its printer port "Error" line. Having received this signal, however, it takes no immediate action, but waits for a keyboard key to be pressed.

Having received a keypress, the PC relates it to a lengthy look-up table that holds segment data in respect of keypresses. If segment data has been allocated to that key, it is output as seven bits (same relationship as with keypad data) plus bit 7 set high. It then remains in another holding loop until the "Error" line goes low.

The PIC, recognising that its RB7 pin has gone high, accepts the incoming 7-bits of RB0-RB6 data as valid. It immediately acknowledges this to the PC by setting line RA3 low.

The PC, having accepted this acknowledgement, is now free to wait for another keypress, but will not send it until the PIC signals that it is ready.

Between accepting bytes of data, the PIC sends the segment data serially to the selected digit in a similar fashion to that described earlier. On completion of each digit's output, the PIC again sets handshake line RA3 high, asking for more PC data.

## DIGIT COUNT SELECTION

The PC program has been written so that it can be set to the exact number of digits in use, unlike the keypad software which always expects 24 digits. It also provides the facility to select which printer port register address is used.

On running the program, the screen shown in Fig.14a will be displayed. The three possible printer port registers addresses are displayed at the top. It is necessary to select the one appropriate to your PC's configuration. Most likely it will be address 378 hex, but could be hex 278 or 3BC. Select the

address by pressing 0, 1 or 2 (pressing any other key, including <ENTER>, always selects 0, i.e. address 378).

If you do not know which address your PC uses, try all three. The system will show you have the correct one when it proves that it can send data to the displays. (The PIC board must be free of assembly errors of course!)

Having selected the register, the screen changes to that in Fig.14b. Underneath the main title you are asked to enter the number of digits that you wish to be controlled, with a range of 1 to 24. Values outside this range are not accepted.

At the bottom of the screen are displayed the characters which can be sent for display via the 7-segment digits. With the exception of the control keys mentioned next, this represents the full range of keys that are functional. Any others will be ignored by the program (although you can add to the range as discussed later).

To either side of the screen are quoted the commands available when the program is in full control mode. The <ESC> (escape) key causes the program to restart from its beginning and may be used at any time. Pressing the <CTRL> and <BRK> keys simultaneously causes the program to end. This is the only way in which it can be halted and exited.

Otherwise, all keyboard characters shown in the bottom line are available for output to the digits. Acceptable keypresses are responded to immediately, and data is output to the digits in sequence, the PIC's digit count being incremented following receipt of each character. When the final digit in the sequence has been triggered, the count automatically recommences from Digit 1.

When entering data for output to the digits, pressing <ENTER> causes the PIC to reset the digit count back to Digit 1. Pressing the space bar causes the next digit to be cleared (no segments showing).

## PC FIRST, PIC SECOND

In the mid-switch area you are told that you should switch on the PIC unit "now". As said earlier, when the PIC program is first switched on, the PIC examines Port B to see whether its pins are high or low. If high, keypad control is assumed. On running the PC program, however, its first activity is to set its printer port lines low. On reading Port B being low, the PIC knows that PC control is required.

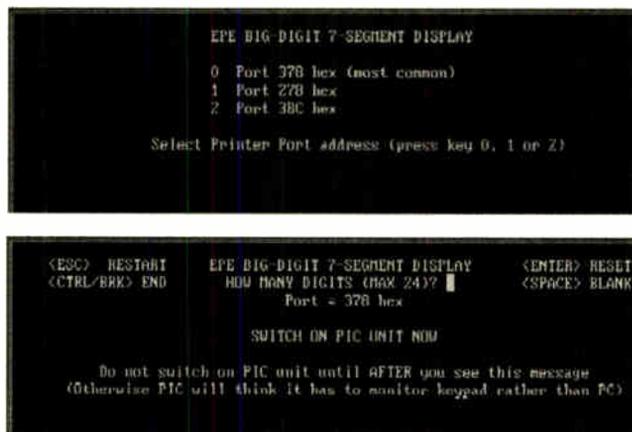


Fig.14. Sections of Big Digit PC program setup screens, (a) printer port selection, (b) digit quantity selections.



Fig.15. Example of PC screen during digit control.

Consequently, do not switch on the PIC unit until you see the screen now being discussed. When you have switched on the PIC, then enter the number of digits to be controlled and press <ENTER>.

The program then enters its full operational mode, first drawing on screen the same number of boxes as the number of digits specified. These boxes represent the 7-segment digits and display the same characters.

Next the program sends data for numeral 8 to all digits required. It then sends a reset command to the PIC, resetting it for Digit 1, after which it sends data to clear all required digits, again followed by a reset command.

This action has three functions, to synchronise the PIC with the computer's order of digits, to prime the PIC so that it knows which segments are in which state, and thirdly to clear any existing display data.

In the latter context it is worth recognising that the segments can be set by hand without damaging them. They are only balanced on light-duty pivots, freely responding to the electromagnetic fields generated by their coils. It is quite possible that someone could have set them by hand to random positions. (In a "field" situation, it is advisable to enclose the digits to prevent this happening – and of course to protect them from the "elements".)

From this point onwards, pressing any recognised key causes the data to be displayed sequentially, with the count returning to zero (Digit 1) after the final digit (or on pressing <ENTER> as described earlier). An example PC screen display is shown in Fig.15.

## PC CONTROL DATA OPTIONS

Because of the greater variety of segment codes that can be generated via the PC than with the keypad, there is the option to program the PC software with any segment combination required.

The data is held in a look-up table which can be added to by readers who have QBASIC or QuickBASIC resident on their PC. The data is held as in the format extract example shown in Listing 3, in the bit order of segments ABCDEFG (the opposite order used by the PIC software's table).

## LISTING 3

```
DATA 01111110
DATA 10110000
DATA 21101101
DATA C1001110
DATA c0001101
DATA D0000000
DATA d0111101
DATA K0000000
DATA k0000000
DATA " 0000000"
DATA "^1100011"
```

When the program is started, all data statements are "Read" and analysed. The first character in each data string holds the keyboard character that represents the following 7-bit segment data. Its ASCII value is taken and the remaining seven bits in the data are stored in a string array, seg\$(x), at the address corresponding to the ASCII value.

For example, in the first case, "01111110", the leading "0" is the first character. Its ASCII value is 48 and so the rest of the data string ("1111110") is stored at string array position seg\$(48). In the fourth case, "C" is the character, having the ASCII value 67, so its 7-bit string data is stored at seg\$(67).

Note that some data statements have had to be enclosed in quotes so that the program recognises the associated character correctly (the last character in the above list cause the "degrees" symbol to be displayed when the "A" is pressed (as in 20°C). The one before it is for the space bar (turns off all segments in a digit).

You will see instances where the character may be in upper or lower case, and in some cases both. If the value following the character contains one or more "1"s, the equivalent character *can* be generated on a 7-segment display. In the other cases, all zeros, the character *cannot* be formed using a 7-segment display.

If a character is not included in the table, a value of zero is returned if its key is pressed. All unacceptable keypresses are ignored.

## ALLOCATING SEGMENTS

For such "unacceptable" keys, however, a segment or PIC control code can be allocated separately. For instance, the program allocates the code "00000001" when the <ENTER> key (ASCII 13) is pressed. The PIC has been programmed to recognise this bit combination as the command to reset the digit number count to Digit 1, in a similar way to that in which it responds when the "D" key on the 4 x 4 data keypad is pressed.

You could, for example, allocate specific codes for the PC's forwards/backwards cursor keys. The PIC could then be told to step the digit count value backwards or forwards without causing the display data to change. Then, on pressing another key, its character would be displayed at the new digit address.

Such a facility would be of help in a display having many digits and where only one or two might need to be changed at any time. This would remove the need to key in data for all digits in the full display when only a few might need changing.

Another option open to those who are familiar with QB programming is to write a code routine that allows a string of characters to be entered via the keyboard as a sentence (using INPUT instead of INKEY\$). This would not be transmitted to the PIC until the <ENTER> key had been pressed. Each character would then be sent automatically in sequence to successive digits as required.

## SETTING PULSE LENGTH

So far the discussion has assumed that the length of the control pulse that activates the segment coils is correct. Setting preset VR1 earlier to a fully clockwise position sets the length to the maximum design limit. It is likely that the pulse can be shortened, so speeding segment changes.

The simple data sheet received indicated that a pulse length of about 0.25 seconds was required. Experiments with the digits showed that it could be much shorter. Although there was a slight variation in minimum operational pulse length for the various segments, the requirements were typically found to be about 70 milliseconds, but cannot be guaranteed in other assemblies (hence the need for user-adjustment rather than specifying the length as an accurate timing within the software).

A 70ms pulse length is generated with preset VR1 at a roughly midway setting. The maximum pulse length that can be set is about twice that. These figures are based on the PIC being run at 4MHz.

Once you have ascertained the correct response of the segments using a long pulse set via VR1, it is worth experimenting to find the lowest VR1 setting at which the segments will respond. This will speed the rate at which the displays can be changed.

The digits will not respond if the resistance is set too low. An intermediate stage may also be found in which some digits respond but not others. Avoid setting VR1 to a nil resistance position which will overload RA4 when it is in output-low mode (the PIC is internally protected against brief overloads – but do not sustain this condition).

It is worth noting that the software has also been written to speed segment changing. The status of each segment is recorded in the PIC's memory. When a new character is to be displayed on a particular digit, the digit's current segment status is checked against the segment requirement for the new character. If any segments match, they are ignored by the output routine, so saving one pulse duration – which can be a significant saving when many digits are in use.

## SCHMITT PULSING

This now brings us to a software/hardware aspect that has not been used before in an EPE project – analogue control of frequency via a digital input.

You are no doubt familiar with the type of circuit in which a single Schmitt trigger inverter is used with a resistor and capacitor in order to generate a frequency (an RC oscillator). The technique used in Big Digit is similar.

The PIC16F84 has a Schmitt trigger input, pin RA4. Referring to Fig.7, the

resistance is provided by preset VR1, and the capacitance by C5. Initially software sets RA4 as an output set for logic 0. This discharges C5. RA4 is then set as an input, allowing current to charge up C5 via VR1.

When the Schmitt threshold is reached, the software responds to this as an input change from logic 0 to logic 1. It immediately sets RA4 as an output at logic 0 again, discharging C5, and then resets RA4 as an input once more, and so the cycle can continue for as long as the software requires it.

In this design, 16 waveform cycles are used, which allows a lower value capacitor to be used than with a single cycle. It also increases the capacitor's discharge rate and reduces current flow when RA4 is briefly set low. Listing 1 shows the full pulse delay generation routine.

The frequency of oscillation can be changed by varying VR1 or by using a different value for C5.

## EXPANSION

As said earlier, additional banks of eight digits can be controlled. In this case IC2 and IC3 need to be duplicated on a strip-board layout. Their pins should be connected identically to those in Bank 1, referring to Fig.6. The connection points on the p.c.b. are those alongside IC1, previously left unused.

The difference is that their enable pins (1 and 9) need to be controlled by a different Port A pin, RA1 for Bank 2, and RA2 for Bank 3. It is permissible to omit IC3 in the final bank if the digit count does not require it.

If more than three Banks are needed (more than 24 digits), pins RA0 to RA3 should be wired into another 74HC237, mounted on stripboard, at its pins A0 to A2. The outputs would then be used as the Bank Select lines for up to eight pairs of IC2 and IC3.

If using the extra 74HC237, remove the p.c.b. link wire marked Bank 1 Link. Connect point Y to pin Y0 of the new multiplexer. Point X then becomes the point to be regarded as the RA0 connection.

The software for the PIC and the PC will need to be modified to cope with more than three banks of digits. For this reason, only readers highly familiar with programming in both PIC and QB languages should undertake this option.

To such experienced programmers, the changes required should be obvious, but the author cannot offer advice on it. Nor can advice be offered on a breadboard layout for any additional chips added.

Note that it will be necessary to change regulator IC9 to a standard 7805 +5V 1A type if additional copies of IC2/IC3 are added (each extra chip adds about 20mA to the power drawn from the +5V line – see earlier).

QB programmers will recognise that the multiplexing circuit could be controlled directly from the PC's printer port data lines, omitting the PIC entirely. The port's other control lines could then be used in place of the RA0 to RA2 connections. The QB software would largely need to be rewritten, of course.

## VALEDICTUM DIGITALIS!

Two digits were sent to the author for experimentation. As described in this article, the resulting design is intended to drive up to at least 24 digits, and up to 64 with modification. Obviously this ability has not been fully proved in practice. However, extensive bench-tests and simulations have been made using the two digits and it is believed that the claims are valid. If you find any aspect that does not justify this belief, let the author know via EPE HQ (NOT via the Chat Zone as messages posted there may be overlooked).

The author hopes that readers will find ways in which the PIC and QB programs can be enhanced and write additional routines to suit their own needs. His intention has been to show with this design how the Big Digits can be controlled, and to provide an elementary framework within which readers can work to suit their own needs and the number of digits actually used.

Readers who do not wish to tailor the programs, though, will find that the software is perfectly usable as it stands, and that it

## LISTING 4 Send pulse to segment control

```
PULSE1:
    movlw %00010000    ; number of cycles required
    movwf PULSECNT
PULSE2:
    btfss PORTA,4      ; has bit 4 gone high (cap charged
                        ; up enough)?
                        ; no, repeat check
    goto PULSE2        ; yes, set bit 4 low to discharge cap
                        ; again
    PAGE1
    bcf TRISA,4        ; set bit 4 as output
    PAGE0
    nop                ; brief wait discharge capacitor
    PAGE1
    bsf TRISA,4        ; set bit 4 as input
    PAGE0
    decfsz PULSECNT,F  ; repeat for set delay loop time
    goto PULSE2
    return
```

provides a reasonable method of controlling the digits, whether just one is used, or many more. We would be interested to know how many you use and in what applications.

## RESOURCES

The software for this design is available on 3.5in disk (for which a nominal handling charge applies) from EPE Editorial office, or free via the EPE ftp site (path PUB/PICS/bigdigit). The easiest route to the ftp site is via the link at the top of the main EPE web page at [www.epemag.wimborne.co.uk](http://www.epemag.wimborne.co.uk).

The PIC software is supplied as a source code (ASM – TASM grammar), HEX code (MPASM) and OBJ code (TASM). It was developed using EPE Toolkit Mk3/TK3. The PC program is supplied as a stand-alone program (EXE) and as QBasic/Quick-BASIC source code (BAS).

The PIC configuration required is XTAL XS, POR on, WDT off. This is embedded in the ASM and HEX codes, but readers using the TASM OBJ code must configure the PIC in the usual separate manner.

Ensure that you read this month's Shoptalk page for details of component buying for this project.

## ACKNOWLEDGEMENT

The author thanks Display Electronics ([www.distel.co.uk](http://www.distel.co.uk)) for providing the Big Digits for experimental use in the development of this project.

**EVERYDAY  
PRACTICAL  
ELECTRONICS**

## NEWSAGENTS ORDER FORM

Please reserve/deliver a copy of *Everyday Practical Electronics* for me each month

Post Code .....

*Everyday Practical Electronics* is published on the second Thursday of each month and distributed S.O.R. by COMAG  
Make sure of your copy of *EPE* each month – cut out or photostat this form, fill it in and hand it to your newsagent.

Signed.....

Name and Address.....

.....


.....

# New – Professional versions of WIZ-C and our PIC C Compiler

*WIZ – C, The new name for FED's PIXIE development system*
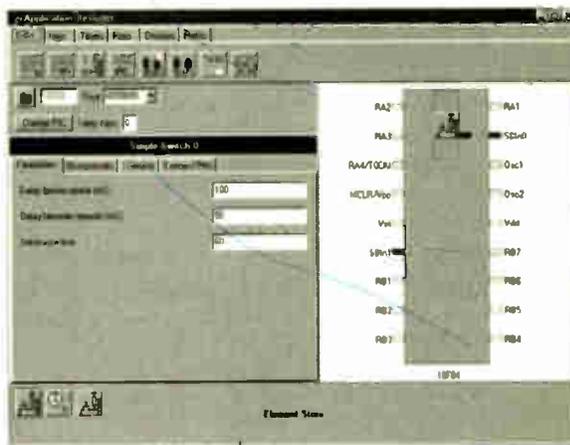
## What is the WIZ-C Rapid Application Environment ?

- Our PIC C compiler including a new front end.
- An application designer for the FED PIC C Compiler
- Drag a software component on to your design & set up the parameters using check boxes, drop down boxes and edit boxes (see shot right).
- Connect the component to the PIC pins using the mouse
- Select your own C functions to be triggered when events occur (e.g. Byte received, timer overflow etc.)
- Generate the base application automatically and then add your own functional code in C or assembler
- Simulate, Trace at up to 10x the speed of MPLAB
- Supports 14/16 bit core PICs  
16F87x, 16C55x, 16C6x, 16F8x, 16C7xx 18Cxx etc.
- C Compiler designed to ANSI C Standards



## Professional Version Enhancements to our C Compiler and WIZ-C Rapid Application Environment


- Manage and simulate multiple projects together
- Connect PIC pins across projects to allow simulated devices to communicate
- Handle assembler and C projects
- View and inspect variables in native C format
- Inspect all local variables and their values in native C format
- Maintain a history within simulation to back track and determine the past leading up to an event

### Prices

WIZ – C Standard - £70.00,  
Professional £100.00. Upgrade for existing WIZ-C owners £30.00  
PIC C Compiler Standard - £60.00,  
Professional £90.00. Upgrade for existing Compiler owners £30.00  
Other upgrade options are available together with reduced price bundled packages – see our web site for details
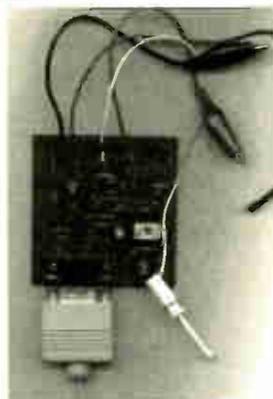
## In Circuit Debugger

Operates with FED PIC Development apps (WIZ-C, WIZASM, C Compiler)



### What is In-Circuit Debugging (ICD) ?

In Circuit Debugging is a technique where a monitor program runs on the PIC in the application circuit. The ICD board connects to the PIC and to the PC. From any of our applications it is then possible to set breakpoints on the PIC, run code, single step, examine registers on the real device and change their values. The ICD makes debugging real time applications faster, easier and more accurate than simulation tools available for the PIC.

### Features

- Allows real hardware to be examined & programs to be debugged and to be run in real time on your application

- Powered from the application circuit (3.3V to 5V)
- The FED ICD requires only one data I/O pin on the PIC which can be chosen from any of ports B, C or D.
- Can program and re-program applications in circuit
- Up to 3 breakpoints
- Run, single step and step over, run to cursor line, set PC to any value in the program
- Trace execution in the original C or Assembler source files
- Animate operation to trace variables at breakpoints or watch the program executing
- Auto Run application if ICD not connected
- View and change values of PIC special function and general purpose registers, W and the ports.
- Uses a standard (3 wire) serial interface to a PC
- Operates on our development board (right)

Price - £30.00. Requires a copy of WIZASM, our PIC C Compiler, or the WIZ-C applications

## Other PIC Products

### Development Board

- Handles 40 pin PIC devices
- Includes on board Programmer – no separate programmer required
- 4 LED's on board, Analogue on trimpot, 2 duplex serial ports
- 1A 5V regulator
- 20MHz crystal
- Interfaces for LCD, hex keypad, 32 I/O pins on IDC connectors
- Will run FED PIC BASIC (included on CD)
- 12C EEPROM socket





Price - £45.00 Built and Tested. 16F877-20P £6.00,  
18C452/JW £30.00, CD with BASIC & Programmer £5.00
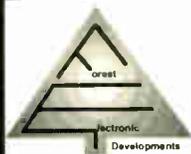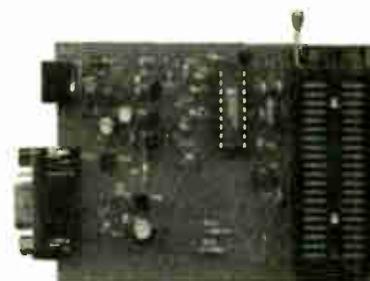
### PIC Serial Programmer including 18Cxxx

Handles serially programmed PIC devices in a 40 pin multi-width ZIF socket.  
16C55X, 16C6X,  
16C7X, 16C8x, 16F8X,  
12C508, 12C509,  
16C72XPIC 14000,  
16F87X, 18Cxxx etc

Also In-Circuit programming. Operates on PC serial port.  
Price : £45/kit £50/built & tested



**Forest Electronic Developments 01590-681511 (Voice/Fax)**

12 Buldowne Walk, Sway, LYMINGTON, HAMPSHIRE, SO41 6DU.

Email – info@fored.co.uk, or sales@fored.co.uk

Web Site – http://www.fored.co.uk

Prices are fully inclusive, Add £3.00 for P&P and handling to each order.

Cheques/POs payable to Forest Electronic Developments, or phone with credit card or Switch details.



# PRACTICALLY SPEAKING

*Robert Penfold looks at the Techniques of Actually Doing It!*

**E**LECTRONIC project construction is certainly a technical hobby, but it is not only a matter of test equipment, PIC programming, and electronic theory. It is not just soldering irons, electronic components, and circuit boards either. There is also a "nuts and bolts" side to the hobby. Having completed a circuit board successfully you are by no means "home and dry". There is usually a fair amount of work to do before you are ready to show off your new masterpiece. You should not find things too difficult if you have a reasonable selection of tools and often undertake DIY jobs around the house. On the other hand, project construction and general DIY jobs are certainly different.

Electronic project construction requires a more gentle approach. The "hammer and tongs" approach usually ends in disaster, with a lot of time and materials being wasted. Most projects are housed in plastic or aluminium cases that are easily damaged. Some cases are actually quite tough, but many of the plastic cases are prone to cracking, and it is easy to dent or distort most aluminium cases. Bear in mind that most cases have finishes that are easily spoiled. With the "nuts and bolts" side of construction it is definitely advisable to proceed carefully and always use the minimum amount of force.

## Look Before You . . .

If you look through a selection of project articles you will find detailed instructions for building the circuit boards and completing the hard wiring. Articles are usually more sketchy about the mechanical side of construction. This is simply because most constructors prefer to "do their own thing" with this aspect of project building. You can try to produce an exact copy of the original each time you build a project, but it is more interesting and satisfying if you do things your own way. You

have greater freedom when "doing your own thing", but the chances of ending up with a complete mess are greatly increased.

It is fair to say that careful planning is important when building anything, and electronic projects are certainly no exception. Simply making it up as you go along is likely to produce an end result that looks muddled and badly thought out. It might even produce a 90 per cent complete project that can be taken no further.

Without planning it is easy to produce projects that are fine, apart from the fact there is insufficient space for the battery, or the lid of the case can not be fitted into place. Another popular mistake is to miss out a control or socket which then has to be fitted in as best you can. At best this produces some odd-looking panel layouts. At worst you find that one or two controls cannot be adjusted when the headphones are plugged in, or something of this nature.

## Project Cases

Although there are many different types of project cases in use at present, they break down into two main categories. The cheapest are the simple boxes that are normally of plastic construction, but can be made of metal or a mixture of plastic and metal. Instrument cases are generally larger and more expensive.

The simple boxes consist of a five-sided main section plus a removable lid, although the latter is often used as the front panel. The more expensive metal types are of diecast aluminium construction and are very tough. They also have good screening properties that prevent radio signals from entering or exiting. The cheaper metal boxes use folded aluminium construction. While nothing like as tough as the diecast variety, they are more than adequate for most projects.

Simple boxes are fine for projects that require a small to medium size enclosure, but they are often a bit awkward when applied to larger projects. Instrument cases are usually the better option for larger projects. Apart from the fact that they "look the part", they generally provide better access to the interior of the case which makes it easier to work on larger and more complex projects.

Instrument cases vary considerably in design, but many have a base section combined with front and rear panels. The lid and sides are combined in another section. Ideally, the case should have removable front and rear panels, as this makes working on the panels very much easier.


While it is normally acceptable to use any case that is large enough, it is as well to read the construction notes in the article. There may be other considerations, and in some applications plastic cases are not suitable while in others a metal case must not be used.

Some projects rely on the metal casing to act as a heatsink or to provide screening, or earthing. Other projects, such as radios, require plastic cases that do not provide screening. It is important to heed the advice when an article stipulates a certain type of case.


In most instances the exact type of case used is unimportant, and it is then a matter of choosing one that is big enough and within your price range. In general, simple boxes are substantially cheaper than instrument cases, and they are perfectly adequate for most small projects. For larger projects it is probably worthwhile paying the extra for an instrument case. The finished unit will probably look much better in an instrument case, and it will be easier to build as well.
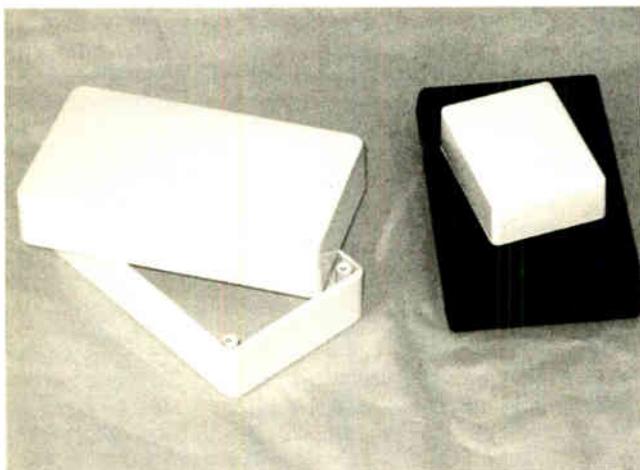
## Size Is Important

How do you work out whether or not a likely looking case will actually



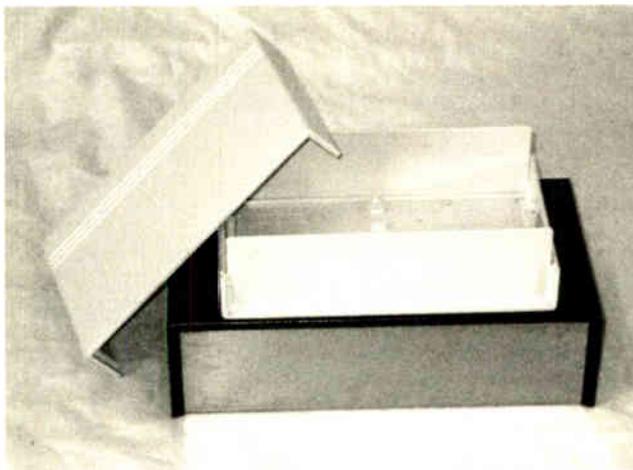*A wide range of inexpensive plastic boxes are available, they are well suited to most small projects.*



*Instrument cases are a better choice for larger projects.*

accommodate your latest project? Measurements taken from the circuit board and other large components might give some guidance, but even this early in the proceedings it is really advisable to give some thought to the general layout of the project. There is otherwise a risk of buying a case that is big enough to take the components, but not with the components positioned sensibly.

Most component catalogues give both the internal and external dimensions for cases. It is the internal dimensions that are of most importance. Where no internal size is given, deducting about 8 millimetres from the external dimensions usually provides figures that are quite close to the internal ones. There is a slight problem in that most cases have internal obstructions that effectively reduce their internal dimensions. For example, most cases have mounting pillars and (or) guide-rails for printed circuit boards, and threaded pillars for the lid mounting screws.

Many cases have mouldings that seem to serve no purpose at all, and make it difficult to fit in even the simplest of projects. Be especially careful with cases having fixing screws that penetrate several millimetres into the open area inside the case. Many metal instrument cases fall into this category.


It is easy to produce a plausible looking layout that actually results in a fixing screw going straight into the battery or a circuit board when the lid of the case is fitted in place. Where a case is supplied with fixing screws that are clearly longer than necessary, it is probably worthwhile replacing them with shorter ones.

It is not a good idea to make every project as small as possible. If a project really needs to be of diminutive proportions, then try to work out a layout that will give a really compact finished article. It is otherwise better to err on the side of caution and choose a case that seems to be slightly too large. This avoids making construction unnecessarily awkward, and will probably result in a finished unit that looks neater and is easier to use.

It is certainly a good idea to place the circuit board, battery, and any other large components inside the case before you start the cutting and drilling. Alternatively, make some careful measurements and some drawings. This should enable you to establish that everything fits, and that the controls, circuit board, etc., are not vying for the same space.
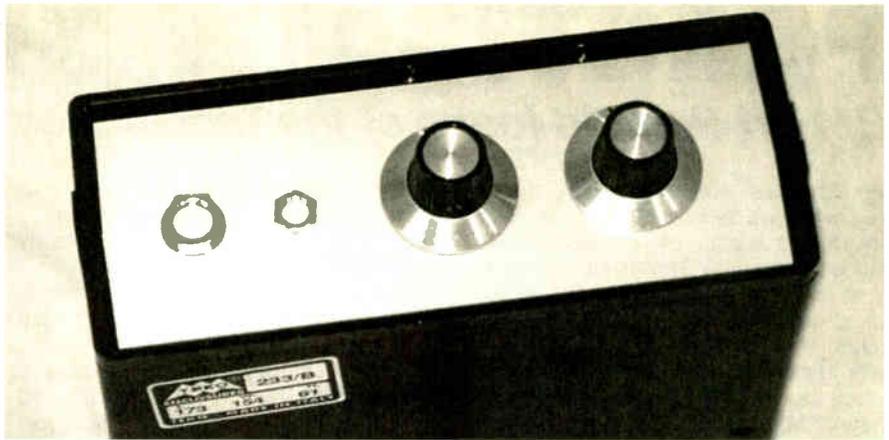
### Long and Short of it

When designing layouts you are often faced with conflicting requirements. You would like to place controls and sockets to give a neat and usable layout, but such a layout might not be very practical. It is best to avoid layouts that have long wires running all over the place. This is not simply because layouts of this type tend to look rather scrappy. With many projects it is best to keep the wiring short in order to minimise problems with stray pick up of "hum" and other signals, and to keep stray feedback to a minimum. The article



*Position control knobs, etc., on the front panel and move them around to find the best layout.*

should point out any restrictions on the layout, such as leads that have to be kept very short, or components that should be mounted well apart. It is advisable to keep inputs and outputs well separated.

Layouts normally look neater if the spacing between control knobs of the same size is constant. On the other hand, a purely mathematical approach to front panel layouts will not necessarily produce the best looking results. The neatest layout is the one that looks best "in the flesh", and not the one that looks best "on paper".

The best way to try out layouts is to place the control knobs onto the front panel, together with fixing nuts to represent things like toggle switches or sockets. This way you get a very accurate impression of what the finished project will look like. When everything looks just right, make careful measurements so that a plan of the layout can be drawn up.

### Perfect Marks

Always check the final layout to make sure you have not overlooked something. When you are sure everything is correct, transfer the layout to the front panel, but take due care when doing this. Most project cases are made from soft plastics or aluminium that is easily worked, but they are also easily chipped and scratched.

Mark the drilling points using something like a fibre-tip pen that will not scar the case for life. It is advisable not to use spirit-based inks on plastic panels. The spirit in the ink might dissolve and seriously damage the case. If in doubt, try the pen on the inner surface of the panel, where any damage will be of no consequence. Very soft pencils (about 5B or 6B) work well on aluminium panels and should not cause any damage. The lines can be removed using an ordinary eraser.

Some plastic panels are resistant to virtually all inks. One option is to scratch the design onto the panel, making sure you only place marks in areas that will be cut or drilled away. The more popular option is to fix paper onto the panel with double-sided tape or a Pritt-Stick. This method is quite a good one using any case, since it is easy to mark the layout very accurately, and the

paper gives some protection to the panel. The paper is peeled off once work on the panel has been completed, and any adhesive or paper that remains is easily washed off.

Use a centre punch to mark the centres of all holes in metal cases prior to drilling them. The small indentations guide the drill bit and make accurate drilling much easier. An automatic punch works well with aluminium. Go carefully when using an ordinary punch with aluminium panels. These buckle and distort quite easily, as you will soon discover if due care is not taken. Centre punches are unsuitable for many plastic cases, which could easily be cracked or more seriously damaged. An indentation is still needed to stop the drill bit from wandering, and this can be made using a pointed tool such as a bradawl, together with a minimum of pressure.

### Drilling Holes

It is then a matter of using standard do-it-yourself tools to drill the holes, file cutouts, or whatever. Due to the softness of the materials used for most cases it is best to drill slowly and very carefully. If you use an electric drill that has some sort of speed control, a low speed is best. A hand drill is perfectly adequate for most project construction.

With an awkward case it might be necessary to enlist the services of a helper to keep it in place while the holes are drilled. Normal clamping techniques can be used with most cases, but use some cloth to protect the panels from damage. Do not rely on any paper or plastic coverings to protect panels from clamps.




Always have a piece of scrap timber, MDF, etc. under the work piece. This supports the panel so that there is less risk of it buckling and it gives "cleaner" holes that require less deburring. With metal panels you will still need to do a certain amount of deburring using a miniature file, or there are special tools for this task.

Be careful when dealing with steel panels. Any raised edges around holes are likely to be quite sharp, so do not feel for them using a fingertip! Look carefully for any projections and immediately remove any that are found.
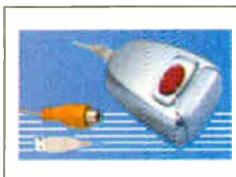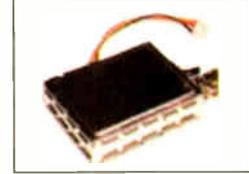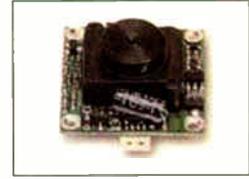
# Video Surveillance



- C-MOS B/W Camera 15mm/15mm £29.00
- C-MOS Colour Camera 15mm/15mm £65.00
- PCB B/W Camera 32mm/32mm £24.00
- PCB Colour Camera w/Audio 32mm/32mm £65.00
- 23cm (1.3GHz) Video/Audio Transmitter £35.00
- 13cm (2.4GHz) Video/Audio Transmitter £35.00
- 1.2 Watt 2.4GHz Video/Audio Transmitter £120.00
- 4" TFT Boxed Colour Monitor w/Audio £110.00
- Video to VGA Converter £65.00
- VGA to Video Converter £90.00
- External USB Video Capture Box £55.00



All prices exclude VAT.

Many more products on our website:

[WWW.BITZTECHNOLOGY.COM](http://WWW.BITZTECHNOLOGY.COM)

Tel: 01753 522 902 Fax: 01753 571 657

## Wireless Remote Controls



**RC-11**  
3 channels RC-11 Key fob  
Control Transmitter with  
Rolling Code technology.

RC-11 Price: £14.99



**UC-216**  
3 channels receiver with 2 relays  
output working from 9V to 12Vdc  
UC-216 with learning mode and  
rolling code technology.

UC-216 9-12Vdc £29.00  
UC-222 240 Vac £29.00

Also


Wireless pager alarm PG-4W	£125.00
Wireless PIR alarm JA-60S	£49.00
Wireless door magnet alarm	£39.00
Wireless smoke alarm	£49.00
Wireless glass break alarm	£49.00
Wireless alarm control panel	£99.00
Wireless alarm control panel with digital /voice dialler	£149.00

Distributors Welcome.

All prices exclude VAT and carriage. All transmitters are licence exempt working on 433.92Mhz. All transmitters work with rolling code technology.

**Bitz Technology Ltd**  
[sales@bitztechnology.com](mailto:sales@bitztechnology.com)  
+44 (0) 1753 522 902

# INGENUITY UNLIMITED

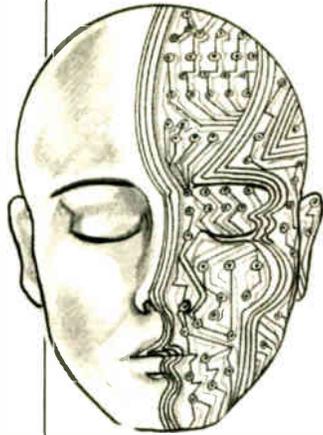

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas *must be the reader's own work and must not have been submitted for publication elsewhere*. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and full circuit diagram showing all relevant component values. **Please draw all circuit schematics as clearly as possible.** Send your circuit ideas to: Alan Winstanley, *Ingenuity Unlimited*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown Dorset BH22 9ND. (We do not accept submissions for *IU* via E-mail.) Your ideas could earn you some cash and a prize!

## WIN A PICO PC BASED OSCILLOSCOPE WORTH £586

- 100MS/s Dual Channel Storage Oscilloscope
- 50MHz Spectrum Analyser
- Multimeter • Frequency Meter
- Signal Generator

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC based oscilloscope could be yours. Every 12 months, Pico Technology will be awarding an ADC200-100 digital storage oscilloscope for the best *IU* submission. In addition, a DrDAQ Data Logger/Scope worth £69 will be presented to the runner up.

## Battery Discharger – Out in a Flash

THE circuit diagram of Fig.1 discharges any rechargeable 1.5V cell and the light-emitting diode D3 starts to flash when the battery connected across the "test" terminal is sufficiently discharged. The design uses a two-transistor astable multivibrator operating at a frequency of about 25kHz. When transistor TR2 conducts, a current flows through the 4.7mH inductor L1, whereupon energy is stored in the resulting electromagnetic field.

When TR2 is cut off, the surrounding electromagnetic field collapses which produces a back-e.m.f. at a level that exceeds the forward voltage (about 1.6V) of the l.e.d. D3. A current then flows through the l.e.d. which appears to be continually alight in normal operation. Diode D2 prevents the current flowing through resistor R6 and capacitor C2. This process is halted only when the battery voltage no longer provides a sufficient base potential for the transistors, and the battery can now be removed.

However, the addition of the forward bias of D1 (about 0.3V) means that the final "discharge voltage" of the battery is raised to 0.9V to 1.0V. Additional resistors R3 and R5 ensure that sufficient current flows through D1.

It should be noted that the battery is discharged sufficiently when the l.e.d. begins to flash. When the discharge is complete (i.e. to 0.9V), the l.e.d. goes out altogether. (*Total discharge may damage Nickel Cadmium or Nickel Metal Hydride cells and is not recommended – ARW.*)

The flashing of l.e.d. D3 when the battery is nearing the recommended discharge level is caused by the increasing internal resistance of the battery lowering the terminal voltage to below the threshold level. Then when no current flows, the internal resistance is of no consequence since the terminal voltage rises to the threshold voltage by taking some energy from the battery.

Liao Jian Mei,  
Singapore.

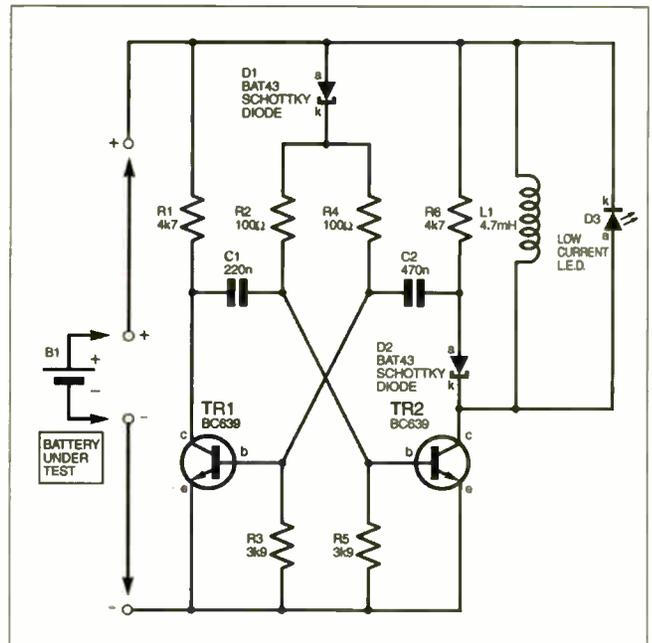


Fig.1. Circuit diagram for the Battery Discharger.

## Emergency Light – A Wind-up

THE circuit diagram shown in Fig.2 offers a stepper-motor powered Emergency Light.

When spun rapidly between the fingers, a small four-phase stepper motor will produce an a.c. voltage of around 5V at 25mA per phase. If all four windings are paralleled, up to 100mA can therefore be produced.

If this is stepped up with a small 230V to 6V-0V-6V centre tapped mains transformer, a small stepper motor is capable of powering a 6 inch 4W fluorescent tube. The transformer must be a small one (around 250mA) or so, otherwise efficiency is compromised.

Once the stepper motor's common lead or leads have been identified, the others can be identified through trial and error. First take the common lead(s) to one terminal of the transformer's primary windings, and try combinations of two wires on the other terminal until the tube lights up. Then connect the remaining wires.

To obtain a good level of light for shorter term use, consider using gears on the motor to avoid the need for any undue exertion.

## INGENUITY UNLIMITED

**BE INTERACTIVE**

IU is your forum where you can offer other readers the benefit of your Ingenuity. Share those ideas, earn some cash and possibly a prize!

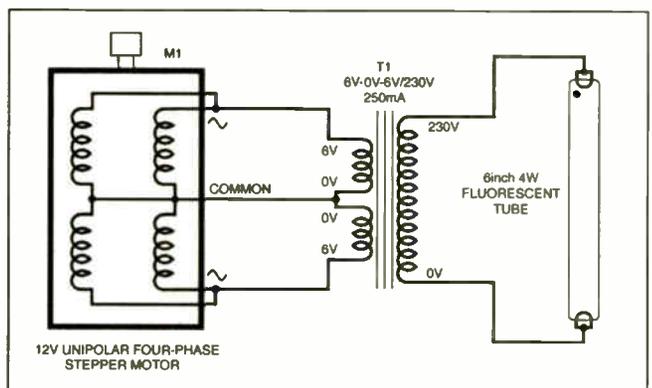


Fig.2. Emergency Light circuit diagram.

**SPECIAL OFFERS**



**TEKTRONIX 2445A**  
4-ch 150MHz delay,  
J-probe etc. Supplied  
with 2 Tektronix probes.  
ONLY **£425**

**TEKTRONIX 2232** Digital Storage Scope  
Dual Trace, 100MHz, 100MS with probes ..... £525  
H.P. 54501A Dig. Oscilloscope, 100MHz 4-Ch ..... £425  
H.P. 3312A Function Gen., 0-1Hz-13MHz, ..... £300  
AM/FM Sweep/TriGate/Burst etc.  
FARNELL Dual PSU XA35-2T, 0-35V, 0-2A, ..... £180  
Twice QMD, I.c.d. Display  
CIRRUS CRL254 Sound Level Meter  
with Calibrator 80-120dB, LEQ ..... £150  
EDDYSTONE 1002 Receiver, 150kHz-30MHz  
+ Broadcast FM, unused ..... £125  
FARNELL AMM255 Automatic Mo  
Meter, 1-5MHz-2GHz, unused ..... £300  
FARNELL D5G1 Low Frequency Syn Sig. Gen.,  
0-001Hz-99.99kHz, low distortion,  
TTL/Square/Pulse Outputs etc. .... £95  
FLUKE 8060A Handheld True RMS, DMM,  
4 1/2 digit. As new £130, Used £95  
BECKMAN HD110 Handheld 3 1/2 digit DMM, 28  
ranges, with battery, leads and carrying case. £40

H.P. 3310A Function Gen., 0-005Hz-5MHz,  
Sine/Sq/Tri/Ramp/Pulse ..... £125  
FARNELL LFM4 Sine/Sq Oscillator, 10Hz-1MHz,  
low distortion, TTL output, Amplitude Meter. £125  
H.P. 545A Logic Probe with 546A Logic  
Pulsar and 547A Current Tracer ..... £90  
FLUKE 77 Multimeter, 3 1/2-digit, handheld ..... £60  
FLUKE 77 Series 11 ..... £70  
HEME 1000 L.C.D. Clamp Meter, 00-1000A,  
in carrying case ..... £60

**Racal 9008** ONLY **£95**  
Automatic Modulation Meter, AM/FM 1.5MHz-2GHz

**Datron 1061** **£150**  
High Quality 5-5 Digit Bench  
Multimeter  
True RMS/4 wire/Current Converter/IEEE

**Datron 1061A** **£225**  
High Quality 6 1/2 digit Bench  
Multimeter  
True RMS/4 wire/Current Converter

**Racal Receiver RA1772** **£250**  
10kHz-30MHz  
L.E.D. Display. Basically working.

**MARCONI 2019A**



**AM/FM SYNTHESISED SIGNAL  
GENERATOR**  
80 kHz - 1040MHz  
NOW ONLY **£400**

**MARCONI 893C** AF Power Meter, Sinad Measurement  
Unused £100, Used £80  
**MARCONI 893B**, No Sinad  
**MARCONI 2510** True RMS Voltmeter, Autoranging,  
5Hz-25MHz ..... £195  
**GOULD J3B** Sine/Sq Osc., 10Hz-100kHz,  
low distortion ..... £75-£125  
AVO 8 Mk. 6 in Every Ready case, with leads etc. £80  
Other AVOs from ..... £50  
**GOODWILL GVT427** Dual Ch AC Millivoltmeter,  
10mV-300V in 12 ranges, Freq. 10Hz-1MHz ..... £100-£125  
**SOLARTRON 7150** DMM 6 1/2-digit  
Tri RMS-IEEE ..... £95-£150  
**SOLARTRON 7150 Plus** ..... £290

**HIGH QUALITY RACAL COUNTERS**  
9904 Universal Timer Counter, 50MHz ..... £80  
9916 Counter, 10Hz-520MHz ..... £75  
9918 Counter, 10Hz-560MHz, 9-digit ..... £50  
**WAYNE KERR B424** Component Bridge  
Digital/AIM 9343M LCR Databridge,  
Digital Automeasurement of R, C, L, Q, D ..... £200  
**HUNTRON TRACKER Model 1000** ..... £125  
**FLUKE 8050A** 4-5 Digit, 2A, True RMS ..... £75  
**FLUKE 8010A** 3-5 Digit, 10A ..... £50  
**FLUKE 8012A** 3-5 Digit, 2A ..... £40

**SOLARTRON 7045**  
Bench Multimeter ONLY **£30**  
4-5 Digit Bright L.E.D. with leads.

**Portable Appliance Tester** **£180**  
Megger Pat 2

H.P. 8012B DC PSU 0-60V, 0-50A, 1000W ..... £1000  
FARNELL AP60/50 1KW Autoranging ..... £1000  
FARNELL H60/50 0-60V 0-50A ..... £750  
FARNELL H60/25 0-60V, 0-25A ..... £480  
Power Supply HPS3010, 0-30V, 0-10A ..... £140  
FARNELL L30-2 0-30V, 0-2A ..... £80  
FARNELL L30-1 0-30V, 0-1A ..... £60  
Many other Power Supplies available  
Isolating Transformer, 240V In/Out 500VA ..... £40



**GOULD OS300**  
Dual Trace, 20MHz  
Tested with Manual  
ONLY **£95**

**OSCILLOSCOPES**

**TEKTRONIX TDS390** dual trace, 200MHz, 1GS/..... Unused £1500  
**TEKTRONIX TDS320** dual trace, 100MHz, 500MS ..... £1200  
**TEKTRONIX TDS310** dual trace, 50MHz, 200MS ..... £950  
**LECROY 9400A** dual trace, 175MHz, 5GS ..... £1500  
**HITACHI VC6523**, 4trace, 20MHz, 20MS, delay etc. Unused £900  
**PHILIPS PM3082** 2+2-ch., 200MHz, delay etc., £700 as new £300  
**PHILIPS PM3082** 2+2-ch., 100MHz, delay etc., £700 as new £300  
**TEKTRONIX TAS465** dual trace, 100MHz, delay etc. .... £750  
**TEKTRONIX 2465B** 4-ch., 400MHz, delay cursors etc ..... £1500  
**TEKTRONIX 2465** 4-ch., 300MHz, delay cursors etc ..... £900  
**TEKTRONIX 2465A/B** 4-ch 150MHz, delay cursors etc. £500-£900  
**TEKTRONIX 468** Dig. Storage, dual trace, 100MHz, delay ..... £450  
**TEKTRONIX 468** Analogue Storage, dual trace, 100MHz ..... £250  
**TEKTRONIX 468** dual trace, 350MHz, delay sweep ..... £350  
**TEKTRONIX 475** dual trace, 200MHz, delay sweep ..... £400  
**TEKTRONIX 465B** dual trace, 100MHz, delay sweep ..... £325  
**PHILIPS PM3217** dual trace, 50MHz delay ..... £200-£250  
**GOULD OS1100** dual trace, 30MHz delay ..... £150  
**HAMEG HM303** dual trace, 30MHz component tester ..... £275  
**HAMEG HM203.7** dual trace, 20MHz component tester ..... £200  
**FERNEL D1720** dual trace, 20MHz component tester ..... £125  
Many other Oscilloscopes available

**MARCONI 2022E** Synth AM/FM Sig Gen  
10kHz-1.01GHz L.c.d. display etc ..... £525-£750  
H.P. 8657A Synth sig gen, 10kHz-1040MHz ..... £2000  
H.P. 8658B Synth sig gen, 100kHz-990MHz ..... £1350  
H.P. 8658A Synth sig gen, 100kHz-990MHz ..... £995  
**RAS APN82** Synth, 1Hz-200kHz sig. gen.,  
balanced/unbalanced output, L.c.d. display ..... £425  
**PHILIPS PM6328** sig gen, 100kHz-180MHz with  
20MHz, trig. counter, IEEE ..... £550  
**RACAL 9001** Synth AM/FM sig gen, 5kHz-1024MHz ..... £250  
H.P. 3325A Synth function gen, 21MHz ..... £800  
**MARCONI 8600** Amplitude Analyser ..... £1500  
H.P. 4192A Impedance Analyser ..... £5000  
H.P. 4275A LCR Meter, 10kHz-10MHz ..... £2750  
H.P. 8603A Distortion Analyser ..... £1000  
**WAYNE KERR 3540** Inductance Analyser ..... £2000  
H.P. 8112A Pulse Generator, 50MHz ..... £1250  
**MARCONI 2440** Frequency Counter, 20GHz ..... £1000  
H.P. 3320B Frequency Counter, 20GHz ..... £2000  
H.P. 3342A 10Hz-19GHz Frequency Counter ..... £900  
H.P. 1660B Logic Analyser, 80-channels ..... £1000  
**MARCONI 2058** Mod Meter, 500kHz-2GHz ..... £750

**RADIO COMMUNICATIONS TEST SETS**  
**MARCONI 2865/2895A** ..... From £1900  
**ROHDE & SCHWARZ CMT 0-1-1000MHz** ..... £2600  
**SCHLUMBERGER 4040** ..... £900

**JUST IN**

H.P. 8063B DC Electronic Load, 3-240V/0-10A, 250W ..... £04  
H.P. 86312A PSU, 0-20V/0-2A ..... £400  
H.P. 86311B PSU, 0-15V/0-3A ..... £400  
H.P. 8630B PSU Dual, 0-15, 0-3A/0-12, 0-1-5A ..... £750  
H.P. 8632B PSU, 0-20V/0-5A ..... £500  
H.P. 8623A PSU, triple output ranging from 0-7V 0-5A to  
0-20V 0-4A ..... £850  
H.P./GIGILENT 34401A DMM 6 1/2 digit ..... £400/£450  
H.P. 3478A DMM 5 1/2 digit ..... £275  
FLUKE 45 DMM dual display ..... £400  
KEITHLEY 2010 DMM 7 1/2 digit ..... £950  
KEITHLEY 617 Programmable Electrometer ..... £1250  
H.P. 4339B MilliOhm Meter ..... £1500  
RACAL Counter type 1999 2.6GHz ..... £500  
H.P. Counter type 33131A 3GHz ..... £1050  
H.P./GIGILENT 33120A Func. Gen/ARB, 100kHz-15MHz ..... £300/£250  
SOMY/TEKTRONIX AFG320 Arbitrary Func. Gen ..... £1250  
H.P. 8604A Syn. Function Gen, DC-60MHz ..... £1000/£1250  
BLACK STAR JUPITOR 2010 Func. Gen, 0-2Hz-2MHz with  
frequency counter ..... £140  
H.P. 8116A Pulse Generator, 1mH-50MHz ..... £1950  
H.P. 8657B Syn Sig. Gen, 0-1-2080MHz ..... £2500  
CO-AXIAL SWITCH, 1-5GHz ..... £40  
IEEE CABLES ..... £10

**SPECTRUM ANALYSERS**

H.P. 8561B 50Hz-6.5GHz ..... £6500  
H.P. 8560A 50Hz-2.9GHz synthesised ..... £5000  
H.P. 8594E 9kHz-2.9GHz ..... £4500/£5000  
H.P. 8591E 1MHz-1.8GHz, 75 Ohm ..... £3500  
H.P. 853A with 859A 100kHz-21GHz ..... £3250  
H.P. 8558B with Main Frame, 100kHz-1500MHz ..... £1250  
H.P. 365A 20Hz-40MHz ..... £2000  
H.P. 3500A 5Hz-50MHz ..... £3000  
ADVANTEST RA131B 10kHz-3.5GHz ..... £3600  
EATON/ARL/TECH 757 0-001-22GHz ..... £1500  
**MARCONI 2382** 100Hz-400MHz, high resolution ..... £2000  
**MARCONI 2370** 30Hz-110MHz ..... £5000  
H.P. 102 with 8557 10kHz-350MHz ..... £500  
H.P. 141T SYSTEMS  
8553 1kHz-110MHz ..... from £500  
8554 500kHz-1250MHz ..... from £750  
8555 10MHz-19GHz ..... from £1000  
TEKTRONIX 81 10MHz-12.4GHz ..... £500  
H.P. 8443 Tracking Gen/Counter, 110MHz ..... £250  
H.P. 8444 OPT 050 ..... £750  
B&K 2033R Signal Analyser ..... £750  
H.P. 5372A Frequency & Time Interval Analyser ..... £2250  
H.P. 8754A Network Analyser, 4MHz-1300MHz ..... £1250  
H.P. 3557A Network Analyser, 5Hz-200MHz ..... £3000  
H.P. 53310A Mod Domain Analyser Opt 001/003 ..... £5000  
ONO SOKKI CF300 Portable FFT Analyser ..... £1500

**STEWART OF READING**

110 WYKEHAM ROAD, READING, BERKS. RG6 1PL  
Telephone: (0118) 9269041. Fax: (0118) 9361696  
www.stewart-of-reading.co.uk

Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

Used Equipment - GUARANTEED. Manuals supplied

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists.  
Please check availability before ordering.  
CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage

**FRUSTRATED!**

Looking for ICs TRANSISTORS?  
A phone call to us could get a result. We offer an extensive range and with a world-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD  
ADC AN AM AY BA BC BD BDT BDV BDW BDX BF  
BFR BFS BFT BFX BFY BLY BLX BS BR BRX BRY BS  
BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUY  
BUW BUX BUY BUZ CA CD CX CZA DAC DG DM DS  
DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA  
KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB  
MC MDAJ MJE MJF MM MN MPS MPSA MPM MPMH MPSP  
MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB  
SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD  
STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB  
TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA  
UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN  
ZTS + many others

We can also offer equivalents (at customers' risk)  
We also stock a full range of other electronic components  
Mail, phone, Fax Credit Card orders and callers welcome



**Cricklewood Electronics Ltd**  
40-42 Cricklewood Broadway London NW2 3ET  
Tel: 020 8452 0161 Fax: 020 8208 1441

**SQUIRES**

**MODEL & CRAFT TOOLS**  
A COMPREHENSIVE RANGE OF MINIATURE HAND AND  
POWER TOOLS AND AN EXTENSIVE RANGE OF  
**ELECTRONIC COMPONENTS**

FEATURED IN A FULLY ILLUSTRATED  
**528 PAGE MAIL ORDER CATALOGUE**  
**2002 ISSUE**

**SAME DAY DESPATCH**  
**FREE POST AND PACKAGING**

Catalogues: FREE OF CHARGE to addresses in the UK.  
Overseas: CATALOGUE FREE, postage at cost charged  
to credit card

**NEW SHOP EXTENSION OPENING SOON**  
**Squires, 100 London Road,**  
**Bognor Regis, West Sussex, PO21 1DD**

TEL: 01243 842424  
FAX: 01243 842525  
**SHOP NOW OPEN**



# SIMPLE AUDIO CIRCUITS



## Part 1 – Introduction and Power Amplifiers

RAYMOND HAIGH

*A selection of "pic-n-mix" low-cost audio circuits – from preamplifier to speaker!*

**W**HATEVER their particular area of interest, most electronics enthusiasts encounter the need to amplify and reproduce audio signals. The final stages of radio receivers, intercom units, security and surveillance installations, or just a hankering for a big sound from a Walkman or portable CD player, all involve audio amplification and a speaker system. And the amplification usually goes hand-in-hand with some form of signal processing.

Music reproduction calls for a wide frequency response and tone-control circuitry. Speech communication, especially

under difficult conditions, is greatly clarified if the frequency response is curtailed.

This short series of articles describes simple, but effective, ways of meeting these different requirements. Although the circuits are capable of a good standard of reproduction, they will particularly interest the constructor who looks for plenty of performance per pound or dollar.

We begin with the power amplifier. Six alternatives are given and, with the requirement of maximum performance for minimum cost and effort, they are all based on widely available integrated circuits (i.c.s):


### HOW MUCH POWER?

Before considering the various circuits, it is worthwhile to reflect on the amount of power actually needed.

Clear reproduction in Walkman type earphones of reasonable sensitivity can be achieved with a miserly milliwatt (0.001W). When listening to talk programmes in a quiet domestic setting, the power fed to the speaker will hover around 50mW (0.05W), and this is ample for the operator of a communications receiver whose ears are closer to the sound source.

During the valve era, ten watts was considered adequate for the realistic reproduction of orchestral music, and some experts suggested a figure as low as five. One watt of power delivered to a

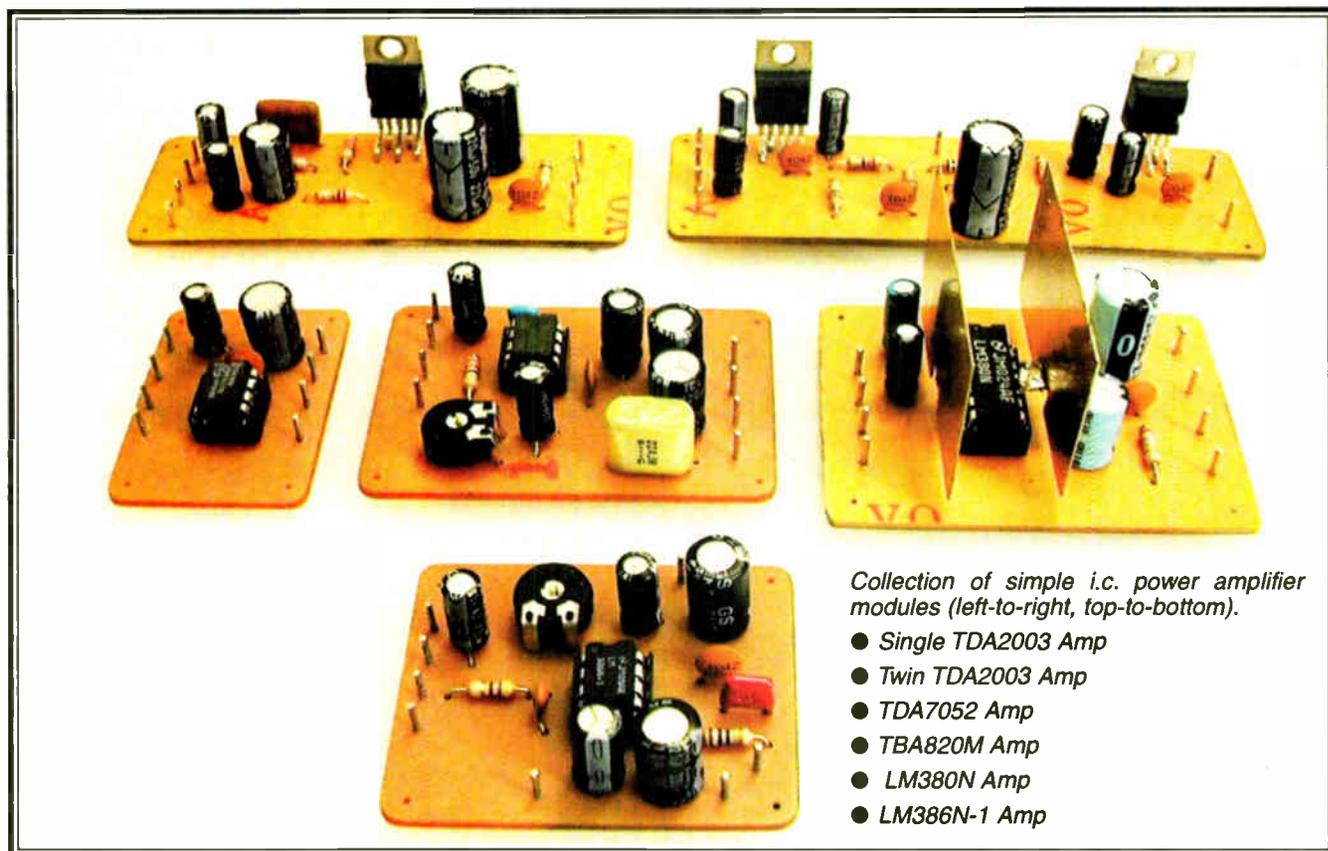- LM386N-1
- TDA7052
- TBA820M
- LM380N
- TDA2003.



reasonably efficient speaker will produce a loud sound, a *continuous* five watts is becoming deafening, and ten will rattle windows. This assumes single channel, or mono, reproduction in a normal living room. The impact is, of course, greater with a stereo system.

This is at odds with the high power ratings of many of the quality amplifiers currently advertised. The desire for a big reserve of power, the low efficiency of some modern speakers, and different ways of measuring output, may account for the difference.

Output is variously rated as music power, sustained music, speech and music, and sinewave power. To add to the confusion, the figures are quoted at different distortion levels. The standard most often used when valves were commonplace, and the one adopted in this article, is the r.m.s. (root mean square) value of a continuous sinewave. This gives the lowest rating and is the most realistic expression of the amplifier's ability to deliver power into a load (speaker).

An increase in output power is reflected as much, if not more, in the cost of the power supply as it is in the actual amplifier. Because the theme of this article is good performance at modest cost, the most powerful amplifier described is rated at 12.5W r.m.s.

## DISTORTION

Manufacturers of power-amplifier integrated circuits and modestly priced hi-fi systems (which invariably incorporate devices of this kind) usually rate the maximum power output at 10 per cent distortion. At this level there is a very noticeable roughness to the sound and clipping of the waveform on loud passages.

The power output levels quoted here have been measured just before the onset of clipping or any noticeable distortion of the output waveform. They are somewhat lower than the figures quoted by the i.c. manufacturers, but they do represent the highest output, free from audible distortion, that the device can deliver for a particular supply voltage and load.

## NOISE

Modern power amplifier i.c.s have a very low noise level. Manufacturers usually define this internally generated electrical noise as an equivalent signal voltage at the input, but this doesn't give the average experimenter an immediate impression of its audible effect.

Accordingly, the devices described here were tested by disconnecting the signal source, turning the input or volume control to maximum, and then listening to the output on a pair of sensitive, Walkman type earphones.

In all cases the noise was no more than barely audible. The two devices which can be configured for high gain (LM386N and TBA820M) did produce a faint, but audible, hiss when the gain was set at maximum. The hiss was also noticeable with a loudspeaker connected.

However, when the gain preset was turned back a little, these i.c.s became as silent as the rest. Some constructors may need the highest possible gain, and details will be given later of measures which can be taken to eliminate the noise.

## STABILITY

Provided a few basic precautions are observed, the amplifiers are all unconditionally stable. Most i.c.s of this kind have a ground connection for the input circuitry and a *separate* ground pin for the output stage.

The printed circuit board (p.c.b.) layouts have been designed to maintain this isolation, and care should be taken to ground the signal inputs and connect the negative power supply lead to the designated points on the board. Failure to do this could result in "motor boating" (low frequency instability).

Input leads should be *screened* to avoid mains hum and radio frequency (r.f.) signal pick up. Speaker leads should be twisted together to minimise external fields. Input and output leads should be spaced as far apart as possible: this is particularly important when the LM386N and TBA820M are set for high gain.

All of the circuits include high and low frequency bypass capacitors across the supply rails. The former minimise the possibility of r.f. oscillation: the latter avoid low frequency instability when long power supply leads are used, or when batteries are ageing.

## HIGH FREQUENCY RESPONSE

The bandwidth of the amplifiers extends into the r.f. spectrum, and this makes the devices vulnerable


overloads them, causing distortion and loss of clarity.

Indeed, if the amplifier is being used primarily for speech, clarity can be much improved by rolling-off the frequency response below 300Hz, and an even lower value of coupling capacitor, say 100 $\mu$ F or even 47 $\mu$ F, would be of benefit. Readers seeking quality music reproduction at low power, via a speaker of reasonable size, should increase the coupling capacitor to say 1000 $\mu$ F.

This relationship between coupling capacitors and frequency response will be considered more fully in the next article.
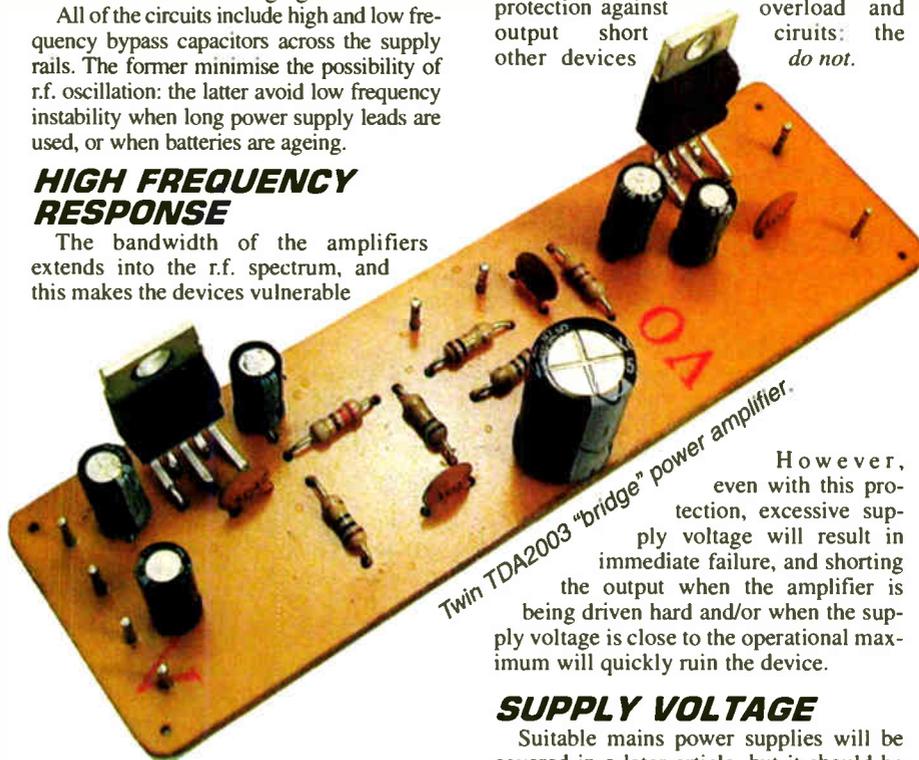
## DEVICE PROTECTION

The integrated circuits covered here are electrically robust but they are by no means indestructible. The TDA7052, LM380, and the TDA2003 incorporate protection against output short circuits: the other devices *do not*.



However, even with this protection, excessive supply voltage will result in immediate failure, and shorting the output when the amplifier is being driven hard and/or when the supply voltage is close to the operational maximum will quickly ruin the device.

## SUPPLY VOLTAGE

Suitable mains power supplies will be covered in a later article, but it should be mentioned now that, off-load, d.c. output voltages rise to 1.4 times the a.c. voltage delivered by transformer secondaries. When using unregulated mains power supplies care should, therefore, be taken to ensure that the off-load voltage is always less than the maximum safe working voltage of the amplifier. *Never connect a working power supply to an amplifier without first checking its output voltage.*

## ELECTRICAL CHARACTERISTICS

The electrical characteristics of the various devices are tabulated alongside the circuit diagrams (except one) for easy reference. Power output figures are based on measurements taken on a single, randomly purchased sample. For reasons already given, they are somewhat lower than the figures quoted by the manufacturers.

Recommendations are made regarding the speaker impedances to use with various supply voltages in order to keep the dissipation of the devices within reasonable limits.

The input resistance, maximum voltage ratings, and frequency response details are those supplied by the manufacturers.

to r.f. interference. Some of the i.c.s provide for the connection of an external capacitor in a negative feedback loop to "roll-off" the high frequency response. Selecting an appropriate value for this component will help to make the device immune.

The problem of r.f. pick up invariably manifests itself when a high value (more than 10 kilohms) input potentiometer (VR1) is used to match the amplifier to the impedance of a signal source. If the potentiometer or volume control must have a high resistance, connecting a 1nF or, at most, 10nF capacitor across its track will shunt unwanted r.f. to ground.

## LOW FREQUENCY RESPONSE

The low frequency response of three of the lower powered amplifiers has been curtailed a little by fitting a 220 $\mu$ F speaker coupling capacitor. Amplifiers of this kind are invariably used with small, inexpensive speakers which are incapable of producing an audible output at frequencies below 150Hz or so. Feeding low frequencies to speakers of this kind only

## AMPLIFIER PROJECTS

In use, there is little to distinguish between the four, low powered amplifiers, all perform well. There are, however, differences which make one device more suitable than another for a particular application.

Low current consumption is important when equipment is powered from dry batteries. Quiescent current drawn by the small amplifiers is in the region of 6mA (13mA for the LM380).

In the case of the LM386N, TBA820M and LM380, current rises to around 120mA when 500mW is being delivered into an 8 ohm load. Current consumed by the TDA7052 is approximately 220mA, or almost double, under these conditions.

In all cases, the signal input pin has been connected to the slider (moving contact) of the Volume control potentiometer (via a blocking capacitor in the case of the TDA2003). This minimises hum and noise and ensures that a more or less constant impedance is presented to the signal

source. Potentiometers of 4700 ohms or 10 kilohms (10k) are usual, but the value can be increased to 100k to raise input impedance.

This will, however, make the circuits more vulnerable to mains hum, r.f. interference and instability, and the value should be kept as low as the signal source impedance permits. This applies particularly to the TDA7052, where the value of the Volume control should, if possible, be no more than 10k. Earlier comments regarding stability are of relevance here.

## LM386N-1 AMPLIFIER

A circuit diagram for a simple amplifier using the low-voltage LM386N-1 power amplifier i.c. is shown in Fig.1. Also shown are the general performance and electrical characteristics of the circuit.

Blocking capacitor C1 prevents any disturbance of the d.c. conditions in the signal source and potentiometer VR1 (the Volume control) sets the input level. The manufacturers of the chip, National Semiconductor, suggest an input network to roll-off high frequencies and resistor R1 and capacitor C2 perform this function.

The unused non-inverting input (pin 3) is grounded to avoid instability when gain is set high. Capacitors C3 and C4, connected across the supply rails, prevent low and high frequency instability.

### FEEDBACK

An internal negative feedback path can be accessed via pin 1 and pin 8. Bypass capacitor C5 reduces the feedback and increases the gain of the chip from 23 to 170 times (as measured: samples will vary). Preset potentiometer VR2 (wired as a variable resistor) controls the bypassing effect of C5 and enables the gain to be set within these limits.

Bypass capacitor C6 makes the device more immune to supply line ripple, and C8 couples the output to the speaker LS1. The Zobel network, formed by resistor R2 and capacitor C7, ensures that the speaker always presents a resistive load to the amplifier. Without these components there is a risk of high level transients causing damage to the output transistors.

Tabulated power output levels for various supply voltages and speaker impedances are included below the circuit diagram. Sustained operation at more than 300mW is not recommended.

### CIRCUIT BOARD

The printed circuit board component layout, wiring details and full-size copper foil master pattern are shown in Fig.2. This board is available from the *EPE PCB Service*, code 343 (LM386N-1).


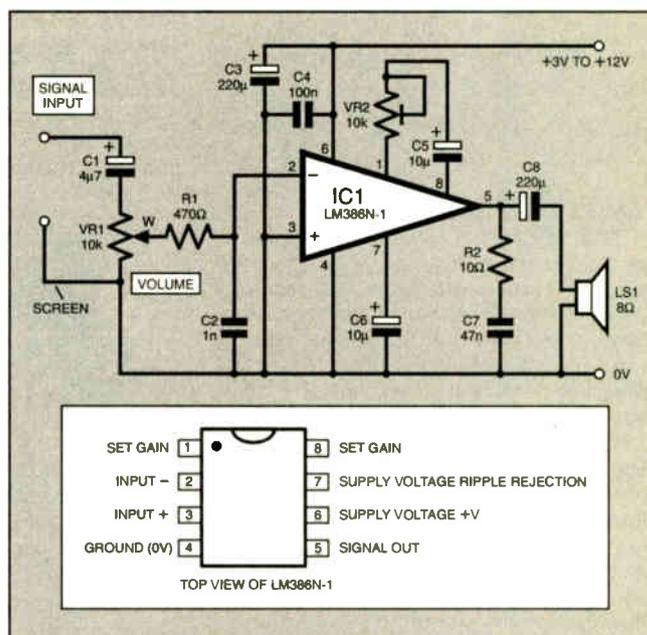


Fig.1. Circuit diagram and pinout details for the LM386N-1 Power Amplifier.

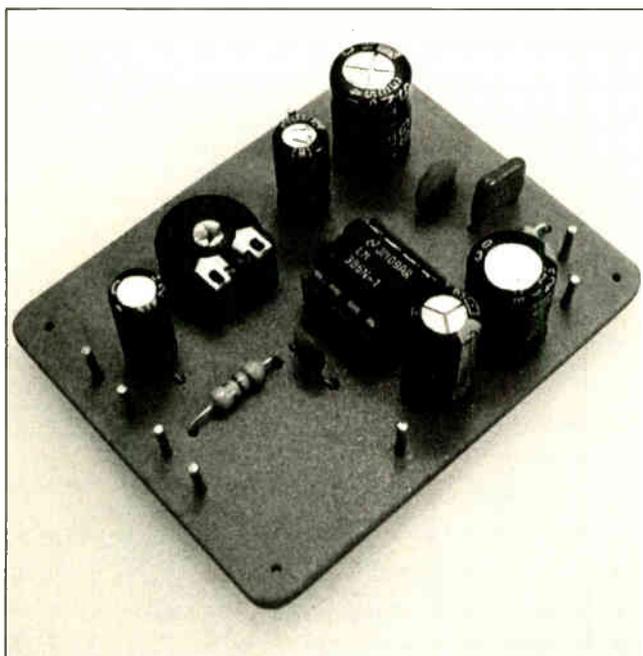

Completed LM386N-1 circuit board.

### LM386N-1 POWER AMPLIFIER R.M.S. power output just before the onset of waveform clipping

Speaker impedance ohms	Supply Voltage				
	3V	4.5V	6V	9V	12V
4	60mW	150mW	320mW	500mW	-
8	26mW	105mW	200mW	560mW	900mW
16	15mW	60mW	110mW	320mW	605mW
32	-	35mW	62mW	170mW	330mW

Quiescent current:	6mA
Input resistance:	50k ohms
Input sensitivity for 560mW output (8 ohm load, 9V supply),	
(a) VR2 set for maximum resistance:	90mV r.m.s. (gain 23)
(b) VR2 set for minimum resistance:	12mV r.m.s. (gain 170)
Absolute maximum supply voltage, beyond which damage will occur:	15V
Suggested maximum supply voltage with a 4 ohm speaker	6V
Frequency response	up to 300kHz

# COMPONENTS

## LM386N-1 AMPLIFIER

### Resistors

R1 470Ω R2 10Ω  
All 0.25W 5% carbon film

### Potentiometers

VR1 10k min. rotary carbon, log.  
VR2 10k enclosed carbon preset

### Capacitors

C1 4μ7 radial elect. 25V  
C2 1n disc ceramic  
C3, C8 220μ radial elect. 25V (2 off)  
C4 100n disc ceramic  
C5, C6 10μ radial elect. 25V (2 off)  
C7 47n polyester

### Semiconductor

IC1 LM386N-1 audio power amp i.c.

### Miscellaneous

LS1 4 to 32 ohm loudspeaker (see text)

Printed circuit board available from the *EPE PCB Service*, code 343 (LM386N-1); case (optional), size and type to choice; 8-pin d.i.l. socket; multistrand connecting wire; audio screened cable; solder pins; solder etc.

Approx. Cost  
Guidance Only

**£10.50**  
excluding case & speaker

See  
**SHOP**  
**TALK**  
page

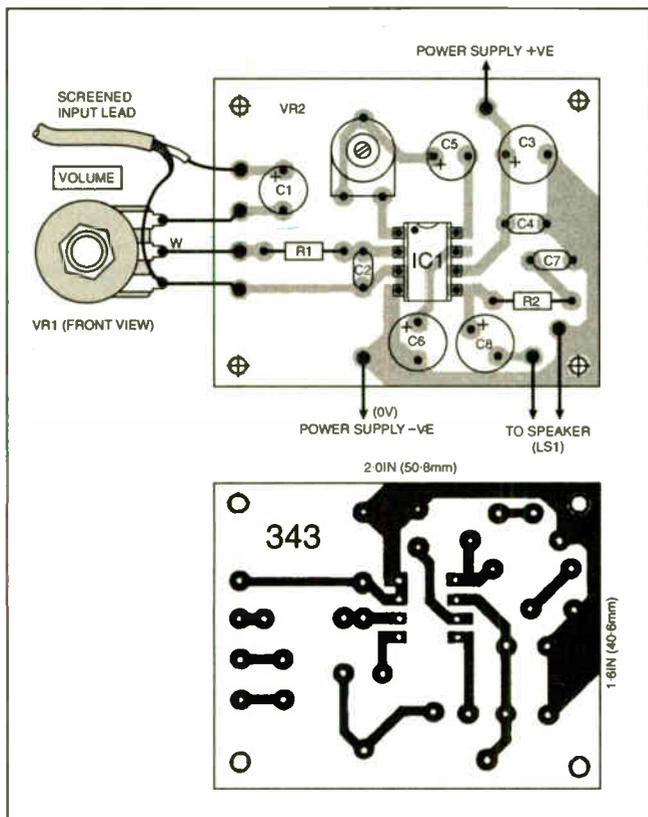


Fig. 2. Printed circuit board, component layout, full-size copper foil master and interwiring for the LM386N-1 Amp.

## TDA7052 AMPLIFIER

Philips have adopted a bridge arrangement for the TDA7052's output stage. This enables the chip to maintain a good output at low supply voltages and eliminates the need for a speaker coupling capacitor.

Gain is fixed internally, no provision is made for ripple rejection, and there is no Zobel network. This reduces the external component count to the d.c. blocking capacitor C1, Volume control VR1 and the supply line bypass capacitors, C2 and C3. The full circuit diagram, together with a

specification guide, for the TDA7052 amplifier is shown in Fig. 3.

Protection against output short circuits is built in and the device shuts down when the dissipation becomes excessive. This explains the small rise in sustainable output when the speaker impedance is increased to 16 ohms with a 9V supply.

Although usually costing a little more than the other low-power chips, this is the device of choice when the supply voltage

has to be low, a good output is required, and high gain is not important. Current consumption for a given output power is, however, almost twice that of the LM386N and the TBA820M.

### CIRCUIT BOARD

The printed circuit board component layout, wiring details and full-size copper foil master pattern are shown in Fig. 4. This board is available from the *EPE PCB Service*, code 344 (TDA7052).

### TDA7052 POWER AMPLIFIER

R.M.S. Power output just before the onset of waveform clipping

Speaker Impedance Ohms	Supply Voltage				
	3V	4.5V	6V	9V	12V
4	70mW	500mW	780mW	—	—
8	60mW	455mW	640mW	1W	—
16	40mW	235mW	450mW	1.12W	—
32	24mW	145mW	250mW	600mW	1.26W

Quiescent current	5mA
Input resistance	100k ohms
Input sensitivity for 1W output (8 ohm load, 9V supply)	40mV r.m.s. (gain 70)
Absolute maximum supply voltage beyond which damage will occur	18V
Suggested maximum supply voltage:	
with a 4 ohm speaker	6V
with 8 or 16 ohm speakers	9V
Frequency response at the -3dB points	25Hz - 20kHz

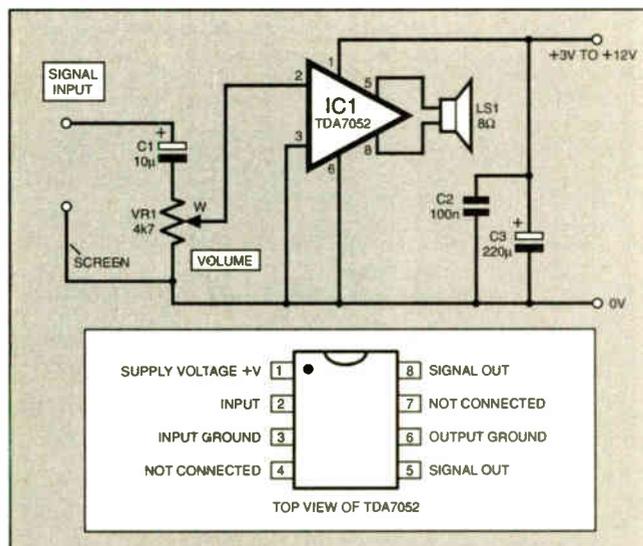


Fig. 3. Circuit diagram and pinout details for the TDA7052 Amp. See left for performance data.

# COMPONENTS

## TDA7052 AMPLIFIER

### Capacitors

- C1 10 $\mu$  radial elect. 25V
- C2 100n disc ceramic
- C3 220 $\mu$  radial elect. 25V

See  
**SHOP**  
**TALK**  
page

### Potentiometers

- VR1 4k7 min. rotary carbon, log.

### Semiconductor


- IC1 TDA7052 power amp i.c.

### Miscellaneous

- LS1 4 to 32 ohm loudspeaker (see text)


Printed circuit board available from the *EPE PCB Service*, code 344 (TDA7052); case (optional), size and type to choice; 8-pin d.i.l. socket; multistrand connecting wire; audio screened cable; solder pins; solder etc.

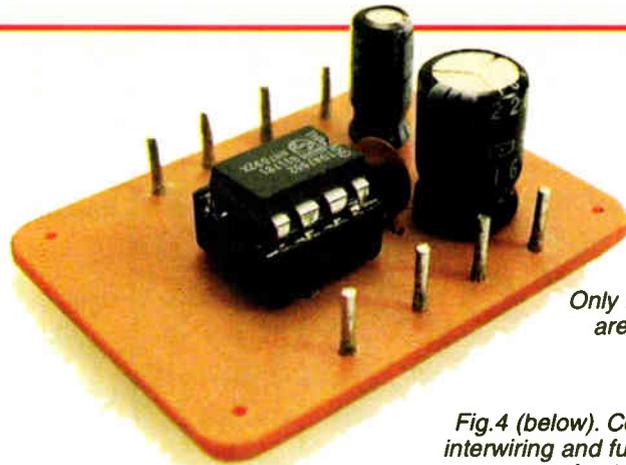**Approx. Cost**  
**Guidance Only** **£9.50**  
excluding case & speaker



Only four components are mounted on the TDA7052 p.c.b.


Fig.4 (below). Component layout, interwiring and full-size copper foil master for the TDA7052 Amp.

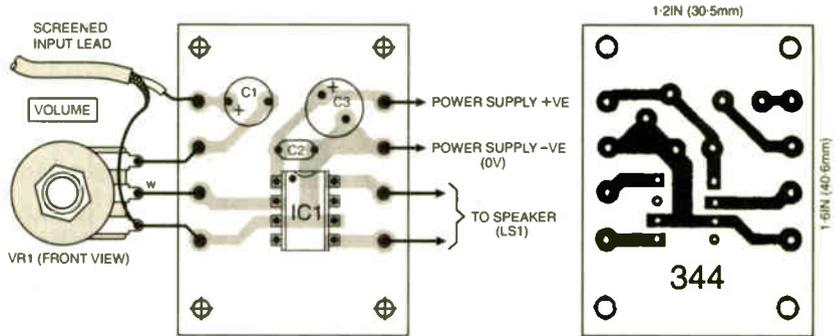
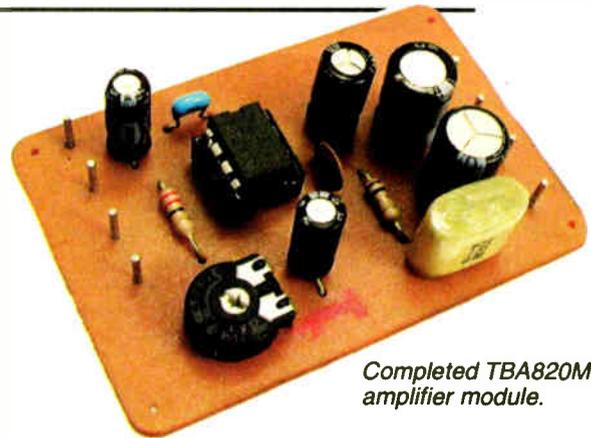
## TBA820M AMPLIFIER

A circuit diagram incorporating the TBA820M audio amp i.c., which is manufactured by SGS-Thomson, together with a general performance guide, is given in Fig.5. The input arrangements, supply line bypassing, speaker coupling and Zobel network are conventional, and the relevant components can be identified from previous circuit descriptions.

Gain can be controlled by shunting an internal negative feedback loop, which is accessed at pin 2. Preset potentiometer VR2, placed in



Completed TBA820M amplifier module.

### TBA820M POWER AMPLIFIER

R.M.S. power output just before the onset of waveform clipping

Speaker Impedance Ohms	Supply Voltage				
	3V	4.5V	6V	9V	12V
4	10mW	320mW	405mW	980mW	-
8	20mW	200mW	300mW	680mW	1.1W
16	30mW	115mW	180mW	405mW	720mW
32	20mW	60mW	90mW	225mW	390mW

Quiescent current

6mA

Input resistance

5M ohms

Input sensitivity for 680mW

output (8 ohm load, 9V supply):

(a) VR2 set for maximum resistance

56mV r.m.s. (gain 40)

(b) VR2 set for minimum resistance

10mV r.m.s. (gain 230)

Absolute maximum supply voltage

beyond which damage will occur

16V

Suggested maximum supply voltage:

with a 4 ohm speaker

9V

with an 8 ohm speaker

12V

High frequency response at -3dB point:

with C6 220pF

20kHz

with C6 680pF

7kHz

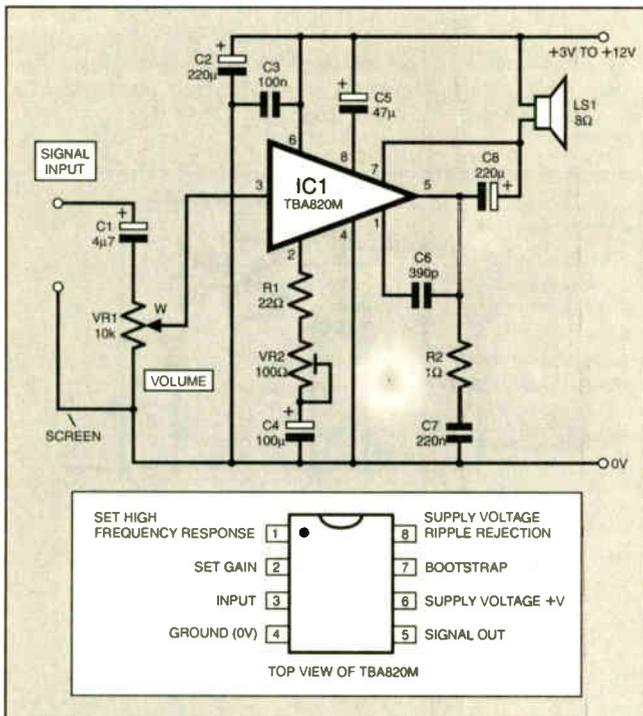


Fig.5. Circuit diagram and pinout details for the TBA820M power amplifier. See right for general performance details.

# COMPONENTS

## TBA820M AMPLIFIER

### Resistors

R1 22Ω  
R2 1Ω

All 0.25W 5% carbon film

See  
**SHOP**

**TALK**  
page

### Potentiometers

VR1 10k min. rotary carbon, log.  
VR2 100Ω enclosed carbon preset

### Capacitors

C1 4μ7 radial elect. 25V  
C2, C8 220μ radial elect. 25V (2 off)  
C3, 100n disc ceramic  
C4 100μ radial elect. 25V  
C5 47μ radial elect. 25V  
C6 390p ceramic  
C7 220n polyester

### Semiconductor

IC1 TBA820M audio power amp i.c.

### Miscellaneous

LS1 4 to 32 ohm loudspeaker (see text)

Printed circuit board available from the *EPE PCB Service*, code 345 (TBA820M); case (optional), size and type to choice; 8-pin d.i.l. socket; multistrand connecting wire; audio screened cable; solder pins; solder etc.

Approx. Cost  
Guidance Only

**£10**

excluding case & speaker

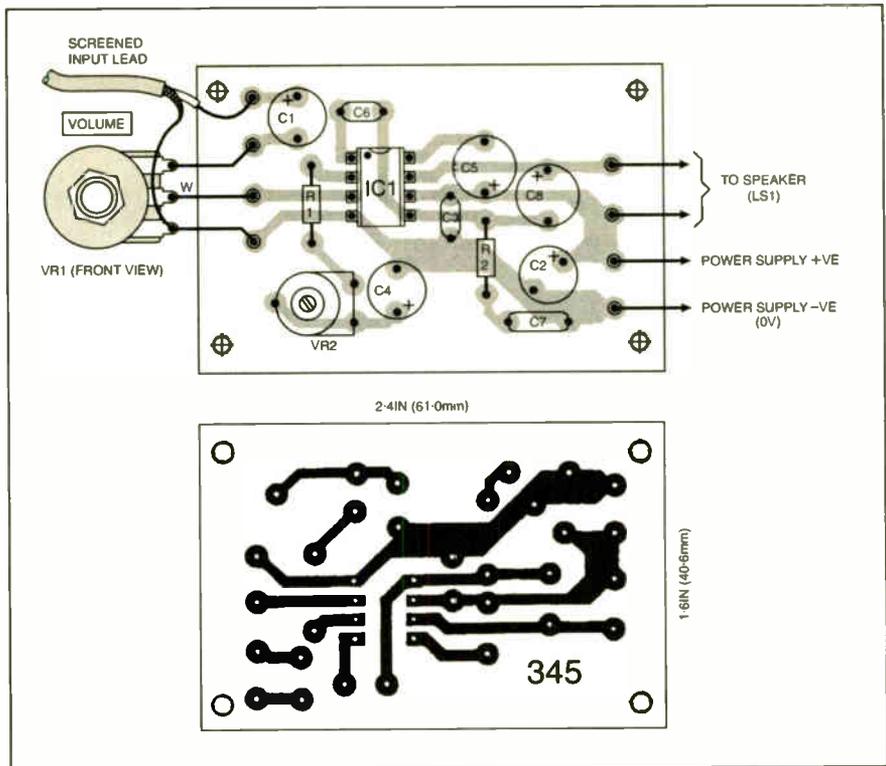


Fig.6. Topside component layout, off-board wiring details and full-size copper foil master for the TBA820M Amplifier.

series with capacitor C4, controls the shunting effect and, with the sample tested, gain could be set between 40 and 230.

High frequency response is determined by capacitor C6. The response at the -3dB points for different capacitor values is also listed in the table. If desired, the value of C6 can be increased to reduce the upper frequency response even more.

In this application, the speaker LS1 is

connected to the positive supply rail as this reduces the component count (a capacitor and resistor are saved).

## CIRCUIT BOARD

The printed circuit board component layout, wiring details and full-size copper foil master pattern are shown in Fig.6. This board is available from the *EPE PCB Service*, code 345 (TBA820M).

# LM380N AMPLIFIER

An amplifier circuit diagram incorporating the LM380N audio i.c. is shown in Fig.7. A general specification guide is shown below.

The manufacturers, National Semiconductor, have made provision for optional heatsinking via some of the pins, and this makes the package larger (14-pin). The output is short-circuit proofed and there is dissipation limiting. Gain is fixed.


Again, the purpose of the various components will be evident from earlier descriptions. In this version of the circuit, the signal

## LM380N POWER AMPLIFIER

R.M.S. power output just before the onset of waveform clipping

Speaker Impedance Ohms	Supply Voltage			
	9V	12V	15V	18V
4	400mW	1.12W	1.62W	-
8	275mW	720mW	1.32W	2.25W
16	137mW	405mW	720mW	1.32W
32	68mW	202mW	360mW	765mW

Quiescent current	13mA
Input resistance	150k ohms
Input sensitivity for 720mW output (8 ohm load, 12V supply)	50mV r.m.s. (gain 50)
Absolute maximum supply voltage beyond which damage will occur	22V

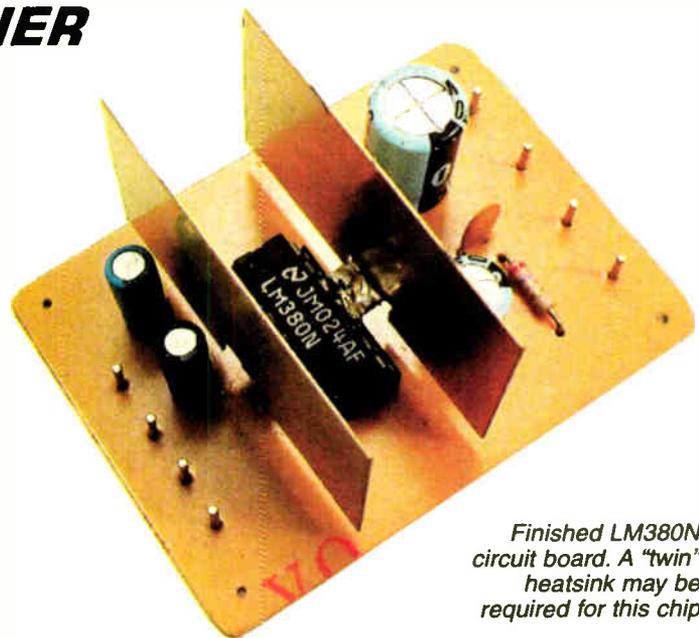

Finished LM380N circuit board. A "twin" heatsink may be required for this chip

A heatsink should be fitted if the device is to be operated, other than intermittently, at output levels in excess of 1W.

Without a heatsink, the suggested maximum supply voltages are:

with a 4 ohm speaker	12V
with an 8 ohm speaker	15V
Frequency response	up to 100kHz

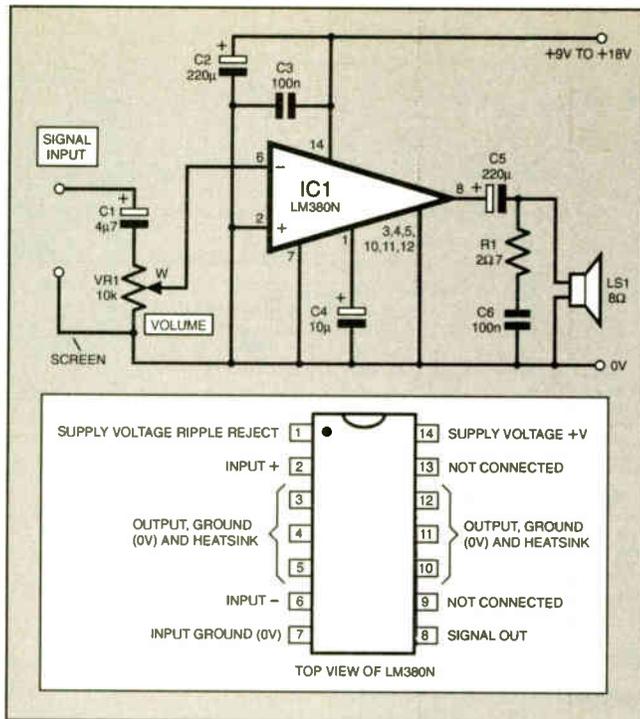


Fig.7. Circuit diagram for the LM380N Amplifier.

is applied to the inverting input (pin 6) and, to avoid instability, the non-inverting input (pin 2) is grounded (0V).

The manufacturers quote a minimum supply voltage of 10V. The sample tested worked with a 9V supply, but performance became erratic at lower voltages. Quiescent current, although modest, is

double that of the other low-power devices, and this, together with the higher operating voltage, makes the i.c. more suitable for mains-powered equipment.

### CIRCUIT BOARD

Details of the printed circuit board

## COMPONENTS

### LM380N AMPLIFIER

#### Resistors

R1 2Ω 0.25W 5% carbon film

#### Potentiometers

VR1 10k rotary carbon, log.

#### Capacitors

C1 4µ7 radial elect. 50V  
C2, C5 220µ radial elect. 50V (2 off)  
C3, C6 100n disc ceramic (2 off)  
C4 10µ radial elect. 50V

#### Semiconductor

IC1 LM380N audio power amp i.c.

#### Miscellaneous

LS1 4 to 32 ohm loudspeaker (see text)

Printed circuit board available from the *EPE PCB Service*, code 346 (LM380N); case (optional), size and type to choice; 14-pin d.i.l. socket; heatsink (see text); multistrand connecting wire; audio screened cable; solder pins; solder etc.

Approx. Cost  
Guidance Only

See  
**SHOP**  
**TALK**  
page

**£11**  
excluding case & speaker

component layout, wiring and copper foil master are given in Fig.8. This board is also available from the *EPE PCB Service*, code 346 (LM380N).

Although the board has been kept small, as much copper as possible has been retained to afford some heatsinking.

## TDA2003 AMPLIFIER

Produced by SGS-Thomson, the TDA2003 low-cost i.c. is mainly for use in car radios. Although chips designed specifically for "hi-fi" amplifiers are available, they usually require higher voltage and/or split rail power supplies. This makes them less easy and more expensive to use.


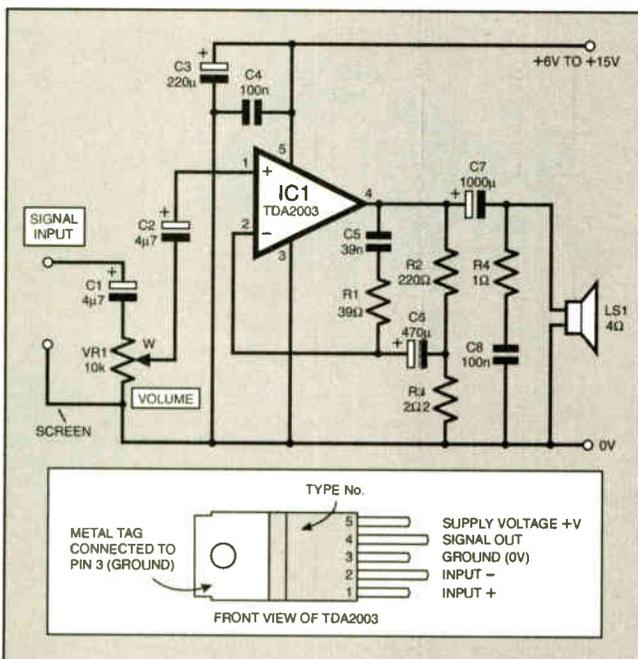


Fig.9. Circuit diagram for a single TDA2003 Amp.

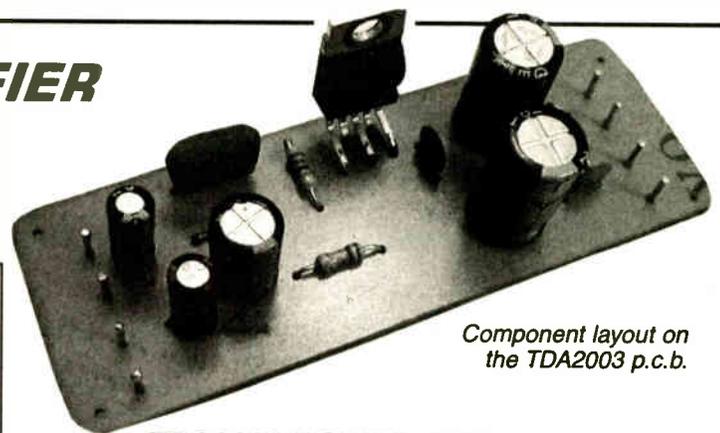

Component layout on the TDA2003 p.c.b.

### TDA2003 POWER AMPLIFIER

R.M.S. power output just before the onset of waveform clipping

Speaker Impedance Ohms	Supply Voltage		
	9V	12V	15V
2	2.25W	4W	5.75W
4	1.28W	2.6W	3.9W
8	720mW	1.44W	2.1W

Quiescent current 45mA  
Input sensitivity for 2.6W output (4 ohm load, 12V supply) 42mV r.m.s. (gain 80)  
Absolute maximum supply voltage beyond which damage will occur 28V  
Absolute maximum operating voltage 18V  
Frequency response: 40Hz to 15kHz at the -3dB points.  
The upper frequency limit can be extended by reducing the value of C5.

# COMPONENTS

## TDA2003 AUDIO AMPLIFIER

### Resistors

R1	39Ω
R2	220Ω
R3	2Ω
R4	1Ω

All 0.25W 5% carbon film

### Potentiometers

VR1	10k rotary carbon, log.
-----	-------------------------

### Capacitors

C1, C2	4μ7 radial elect. 50V (2 off)
C3	220μ radial elect. 50V
C4	100n disc ceramic
C5	39n polyester
C6	470μ radial elect. 50V
C7	1000μ radial elect. 50V
C8	100n polyester

### Semiconductor

IC1	TDA2003 audio power amp i.c.
-----	------------------------------

### Miscellaneous

LS1	4 to 32 ohm loudspeaker (see text)
-----	---------------------------------------

Printed circuit board available from the EPE PCB Service, code 347 (TDA2003); case (optional), size and type to choice; heatsink (see text); audio screened cable; multistrand connecting wire; solder pins; solder etc.

Approx. Cost  
Guidance Only

**£11**

excluding case & speaker

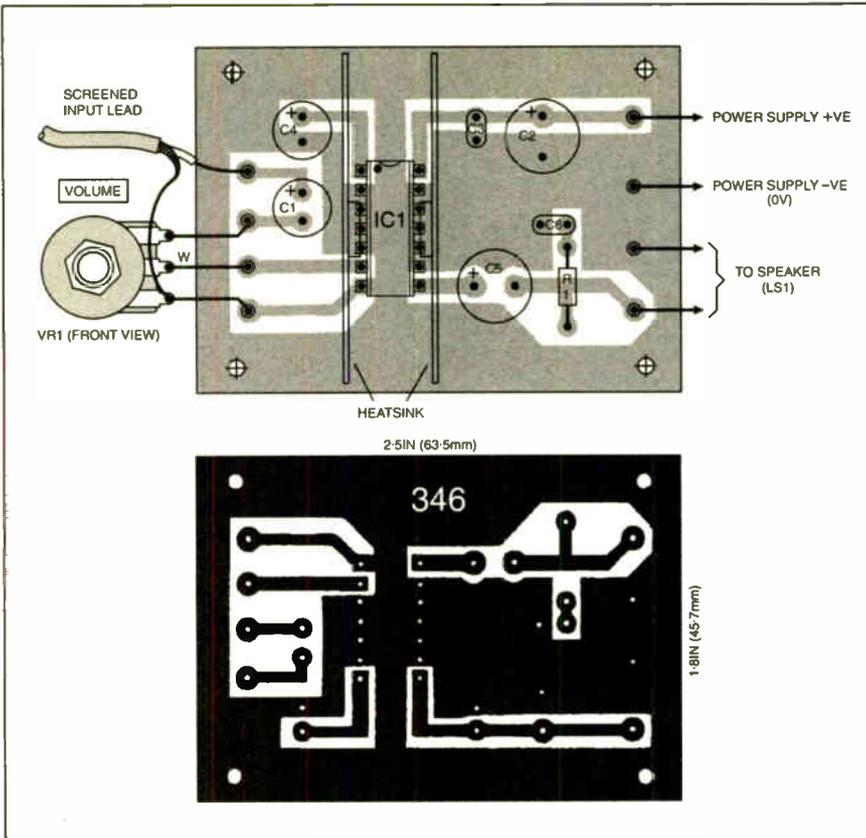


Fig. 8. The LM380N printed circuit board component layout, off-board interwiring and full-size copper foil master pattern. Note the heatsinks.

## HEATSINKS

For those readers who wish to get the most out of the chip, a suitable heatsink for the LM380 (Fig. 7 and Fig. 8) can be formed from two, 40mm (1<sup>5</sup>/<sub>8</sub>in.) lengths

of 25mm x 0.4mm (1in. x 1/64in.) brass strip. Make two shallow cuts, 5mm (3/16in.) apart, close to the centre, and bend out a tag which can be soldered to the relevant pins of the i.c. Thin brass strip can be purchased from almost all model shops.

The TDA2003 incorporates short circuit and overload protection, and is extremely rugged. It will deliver a worthwhile output at modest supply voltages, and the suitability of car batteries as a power source may make it of particular interest to some readers. The

circuit diagram of a single chip TDA2003 audio amplifier is given in Fig. 9.

Grounding the input (pin 1) of this device would upset the internal biasing arrangements, so a second blocking capacitor C2 must be provided. The high

frequency response is set by capacitor C5 in conjunction with resistor R1. The response can be extended by reducing the value of C5. Supply line ripple rejection is afforded by capacitor C6.

The outputs which can be delivered at various supply voltages are tabulated in the accompanying table. The current drawn from a 15V supply when 4W are dissipated into a 4 ohm load is around 500mA. The 2 ohm load is obtained by connecting two 4 ohm speakers in parallel.

At these power levels, the device must, of course, be connected to an adequate heatsink, and this is discussed later.

The printed circuit board component layout, wiring and full-size copper foil master pattern for the single chip TDA2003 amplifier are shown in Fig. 10. This board is available from the EPE PCB Service, code 347 (TDA2003).

## TWIN TDA2003 AMPLIFIER

A circuit diagram using two TDA2003 chips in a bridge configuration is shown in Fig. 11, together with a general performance guide.

Drawing around 1.7A from a 15V supply, this combination will deliver a clean 12.5W into a 4 ohm load. The case for this being adequate for domestic listening has already been argued, but individual constructors will, of course, decide whether or not it will meet their needs.

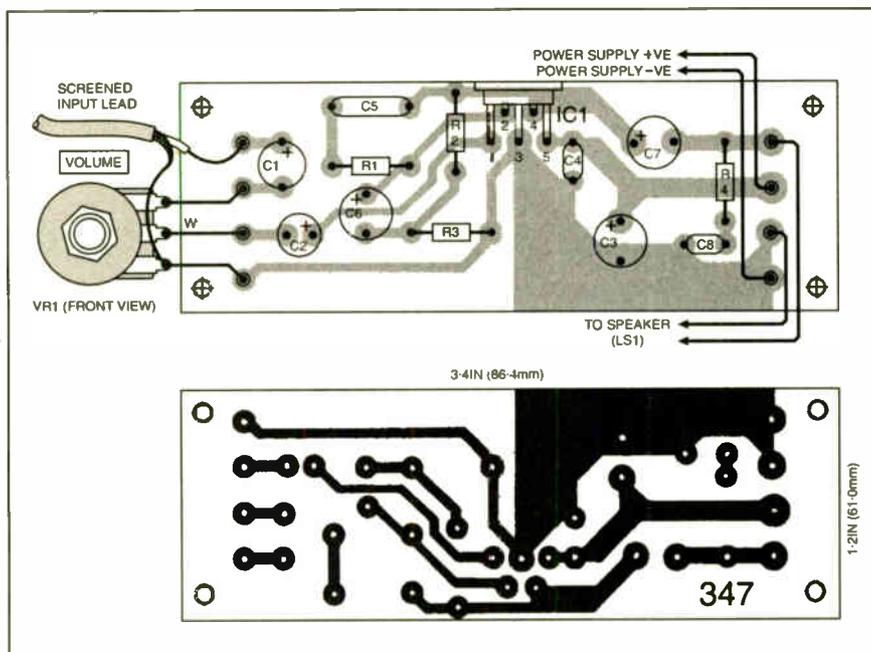


Fig. 10. Printed circuit board component layout, full-size foil master and off-board wiring for the single TDA2003 Amplifier.

# TWIN TDA2003 AMPLIFIER

## COMPONENTS

### TWIN TDA2003 POWER AMP

#### Resistors

- R1, R4 1Ω (2 off)  
 R2 220Ω  
 R3, R5 10Ω (2 off)  
 R6 470Ω

See **SHOP TALK** page

All 0.25W 5% carbon film

#### Potentiometers

- VR1 10k rotary carbon

#### Capacitors

- C1, C2  
 C9 4μ7 radial elect. 50V (3 off)  
 C3, C8 100n disc ceramic (2 off)  
 C4 22μ radial elect. 50V  
 C5, C6 100n polyester (2 off)  
 C7 10μ radial elect. 50V  
 C10 220μ radial elect. 50V

#### Semiconductor

- IC1, IC2 TDA2003 audio power amp i.c. (2 off)

#### Miscellaneous


- LS1 2 to 8 ohm loudspeaker (see text)

Printed circuit board available from the *EPE PCB Service*, code 348 (TDA2003); case (optional), size and type to choice; heatsink (see text); audio screened cable; multistrand connecting wire; solder pins;

Approx. Cost Guidance Only

**£14**

excluding case & speaker

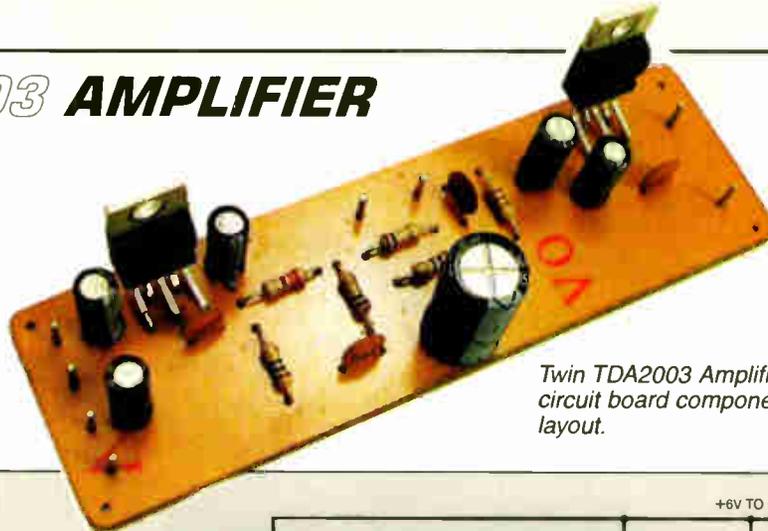

Twin TDA2003 Amplifier circuit board component layout.

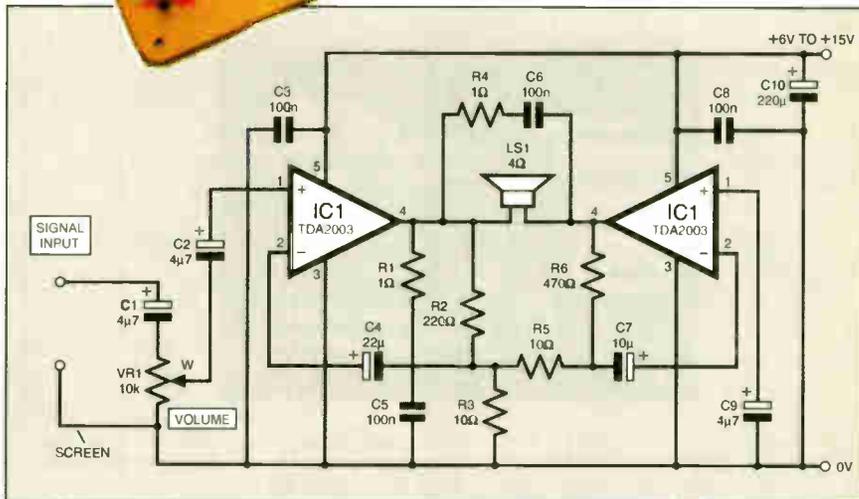


Fig. 11 (above). Circuit diagram for the Twin TDA2003 Power Amplifier.

### TWO TDA2003 BRIDGE CONFIGURATION POWER AMP

R.M.S. power output just before the onset of waveform clipping


Speaker Impedance Ohms	Supply Voltage		
	9V	12V	15V
2	6.25W	10.5W	—
4	3.78W	8W	12.5W
8	2W	5W	8.2W

Quiescent current 80mA

Input sensitivity for 8W output (4 ohm load, 12V supply) 70mV r.m.s. (gain 40)

See single TDA2003 for details of absolute maximum ratings.

Fig. 12 (below). Component layout, off-board interwiring and full-size copper foil master for the Twin TDA2003 Amp. You will need a heatsink for these devices.

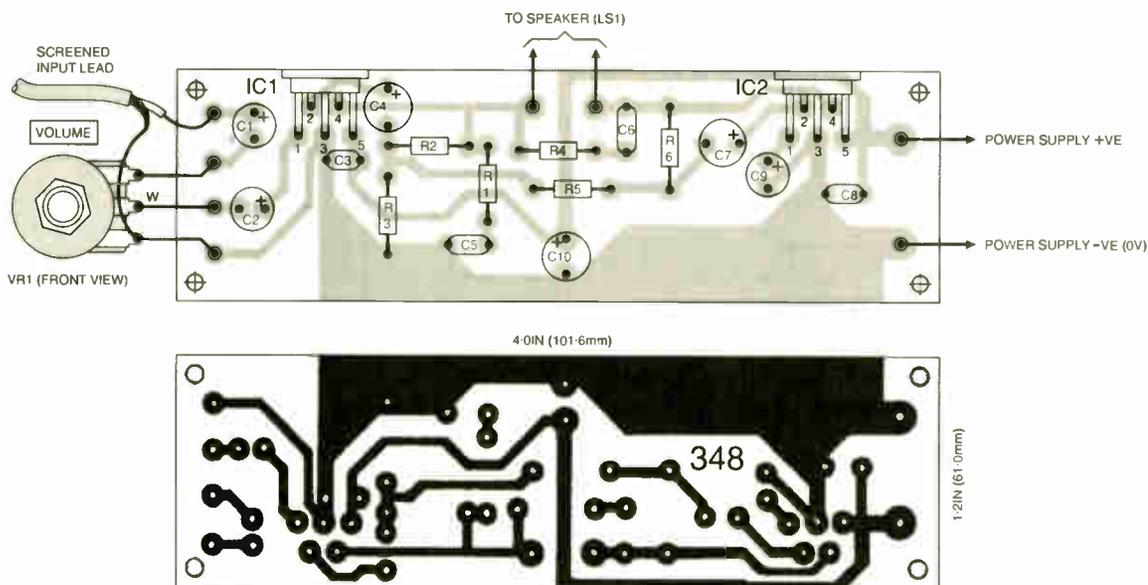

The printed circuit board component layout, wiring and copper foil master are detailed in Fig.12. Again, combined or separate heatsinks must be fitted to the integrated circuit's metal tabs. The p.c.b. is obtainable from the *EPE PCB Service*, code 348 (Twin TDA22003).

## HEATSINKS

A large area metal heatsink is required for the TDA2003 (Fig.9 and Fig.11). Because the device incorporates overload protection, the actual size is not too critical (the i.c. will shut down when it begins to overheat), but sustained high output will only be developed if the heatsink is adequate. At the very least use 40sq. cm (6.5sq. in.) of 16s.w.g. aluminium per chip, or fit a proprietary heatsink with a thermal resistance not greater than 7°C per watt.

The i.c.s are arranged on the p.c.b. (see Fig.10 and Fig.12) so that they can be bolted to the back of a metal case by their metal tabs. A 50mm x 150mm x 200mm (2in. x 6in. x 8in.) aluminium box would be more than adequate as a heatsink. Insulating washers are not required, but a smear of heat transfer compound should be applied.

## COMPONENTS

Slight differences in the i.c. type numbers can cause confusion. The LM386N-1 has the lowest power rating of this group of devices. The suffixes "N-3" and "N-4" indicate devices rated at 700mW and 1W respectively. The suffix "M" indicates surface mounting. Suppliers offering the

LM386 are usually referring to the N-1 version.

The TDA7052 is sometimes given the suffix "A". This indicates that the chip contains a d.c. volume control and is *not* suitable for the circuit described here.

Some suppliers give the LM380 the suffix "14" to indicate the 2.5W 14-pin version, and the suffix "8" for the 8-pin 600mW alternative. When ordering, make it clear that the 14-pin chip is required.

The suffix "P" or "V" is sometimes added by suppliers to the TDA2003 to indicate that it is for vertical, and "H" for horizontal, mounting. There is no electrical difference, but the p.c.b.s illustrated here have been designed for vertical chips.

## CONSTRUCTION

All the amplifiers covered in this part are assembled on printed circuit boards and construction is reasonably straightforward. The use of an i.c. holder will permit the substitution and checking of the low power amplifiers. However, if reliance is to be placed on the p.c.b. foil for minimal heatsinking of the LM380, the device should be soldered directly in place. Solder pins, inserted at the lead-out points, will simplify off-board wiring.

It may help to start construction of the chosen circuit board by first placing and soldering the i.c. holder


on the p.c.b. to act as an "orientation" guide. This should be followed by the lead-off solder pins, and then the smallest components (resistors) working up to the largest, electrolytic capacitors and presets. Finally, the lead-off wires (including the screened input cable), off-board Volume control and loudspeaker should be attached to the p.c.b.

On completion, check the board for poor soldered joints or bridged tracks. Check the orientation of the electrolytic capacitors and the i.c.(s).

If using a mains power supply, make sure the voltage delivered does not exceed the safe working voltage of the amplifier for the load impedance being used.

If all is in order, connect the power supply and check the quiescent current consumption. Inject a signal and re-check the current drain and supply voltage.

### Next Month: Transistor preamplifiers

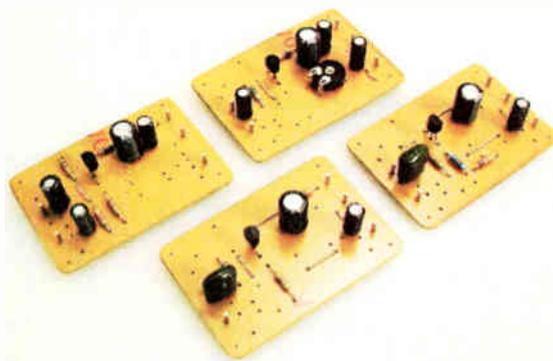

## A COMPLETE RANGE OF INVERTERS

150W TO 2500W - 12V & 24V

A Complete range of regulated inverters to power 220V and 240V AC equipment via a car, lorry or boat battery. Due to their high performance (>90%) the inverters generate very little heat. The high stability of the output frequency (+/-1%) makes them equally suitable to power sensitive devices.

These inverters generate a modified sine wave, which are considerably superior to the square waves which are produced by most other inverters. Due to this superior feature they are capable of powering electrical equipment such as TV,s, videos, desktop & notepad computers, microwave ovens, electrical lamps, pumps, battery chargers, etc.

### Low Battery Alarm

The inverters give an audible warning signal when the battery voltage is lower than 10.5V (21V for the 24V version). The inverter automatically shuts off when the battery voltage drops below 10V (20V for the 24V version). Fuse protected input circuitry.

Order Code	Power	Voltage	Price
651.581	150W Continuous	12V	£36.39
651.578	150W Continuous	24V	£36.39
651.582	300W Continuous	12V	£50.64
651.585	300W Continuous	24V	£50.64
651.583	600W Continuous	12V	£101.59
651.593	600W Continuous	24V	£101.59
651.587	1000W Continuous	12V	£177.18
651.597	1000W Continuous	24V	£177.18
651.602	1500W Continuous	12V	£314.52
651.605	1500W Continuous	24V	£314.52
651.589	2500W Continuous	12V	£490.54
651.599	2500W Continuous	24V	£490.54

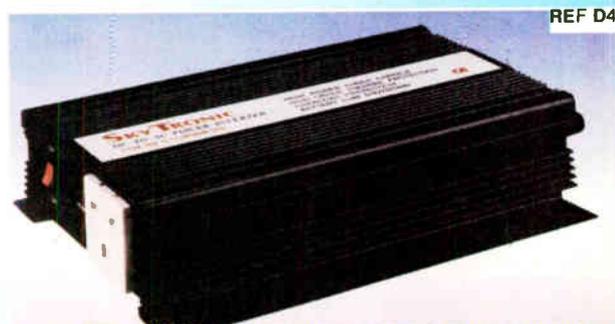


ILLUSTRATION SHOWN IS 651.583 600W VERSION.

All prices are inclusive of V.A.T. Carriage £2.00 Per Order

Many uses include:- Fetes . Fairgrounds . Airshows . Picnics . Camping . Caravans . Boats . Carnivals . Field Research and . Amateur Radio field days \* Powering Desktop & Notepad Computers.

DELIVERY CHARGES ARE £6.00 PER ORDER. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLC.S ETC. PRICES ARE INCLUSIVE OF V.A.T. SALES COUNTER. VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX, OR EMAIL US AT SALES@BKELEC.COM ALTERNATIVELY SEND CHEQUE OR POSTAL ORDERS MADE PAYABLE TO BK ELECTRONICS.



**B.K. ELECTRONICS**



UNIT 1, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR  
TEL.: +44(0)1702-527572 FAX.:+44(0)1702-420243

For Full Specifications View our web site at:-  
**WWW.BKELEC.COM/INVERTERS.HTM**

We can supply back issues of *EPE* by post, most issues from the past three years are available. An *EPE* index for the last five years is also available – see order form. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photostat of any *one article* (or *one part* of a series) can be purchased for the same price. Issues from Jan. 2001 onwards are also available to download from [www.epemag.com](http://www.epemag.com).

# BACK ISSUES

## DID YOU MISS THESE?

### JAN '01

**PROJECTS** • Versatile Optical Trigger • UFO Detector and Event Recorder • Two-Way Intercom • PIC-Monitored Dual PSU-Part 2.  
**FEATURES** • Using PICs and Keypads • The Schmitt Trigger-Part 3 • New Technology Update • Circuit Surgery • Practically Speaking • Ingenuity Unlimited • CIRSIM Shareware Review • Net Work – The Internet.

### FEB '01

**PROJECTS** • Ice Alert • Using LM3914-6 Bargraph Drivers • Simple Metronome • PC Audio Power Meter.  
**FEATURES** • The Schmitt Trigger-Part 4 • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Net Work – The Internet • Free 16-page supplement – How To Use Graphics L.C.D.s With PICs.

### MAR '01

**PROJECTS** • Doorbell Extender • Body Detector • DIY Tesla Lightning • Circuit Tester  
**FEATURES** • Understanding Inductors • The Schmitt Trigger-Part 5 • Circuit Surgery • Interface • New Technology Update • Net Work – The Internet Page.



### APRIL '01

**PROJECTS** • Wave Sound Effect • Intruder Alarm Control Panel-Part 1 • Sound Trigger • EPE Snug-Bug Pet Heating Control Centre.  
**FEATURES** • The Schmitt Trigger-Part 6 • Practically Speaking • Ingenuity Unlimited • Circuit Surgery • Net Work – The Internet Page • FREE supplement – An End To All Disease.

### MAY '01

**PROJECTS** • Camcorder Mixer • PIC Graphics L.C.D. Scope • D.C. Motor Controller • Intruder Alarm Control Panel-Part 2.  
**FEATURES** • The Schmitt Trigger-Part 7 • Interface • Circuit Surgery • Ingenuity Unlimited • New Technology Update • Net Work – The Internet Page.

### JUNE '01

**PROJECTS** • Hosepipe Controller • In-Circuit Ohmmeter • Dummy PIR Detector • Magfield Monitor.  
**FEATURES** • Controlling Jodrell Bank • PIC1687x Extended Memory Use • Practically Speaking • Ingenuity Unlimited • New Technology Update • Circuit Surgery • Net Work – The Internet Page.

### JULY '01

**PROJECTS** • Stereo/Surround Sound Amplifier • PIC to Printer Interface • Perpetual Projects 1 – Solar-Powered Power Supply and Voltage Regulator • MSF Signal Repeater and Indicator.  
**FEATURES** • The World of PLCs • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Net Work – The Internet Page.

### AUG '01

**PROJECTS** • Digitimer • Lead-Acid Battery Charger • Compact Shortwave Loop Aerial • Perpetual Projects 2 – L.E.D. Flasher – Double Door-Buzzer.  
**FEATURES** • Controlling Power Generation • Ingenuity Unlimited • Interface • Circuit Surgery • New Technology Update • Net Work – The Internet Page.

### SEPT '01

**PROJECTS** • Water Monitor • L.E.D. Super Torches • Synchronous Clock Driver • Perpetual Projects 3 – Loop Burglar Alarm – Touch-Switch Door-Light – Solar-Powered Rain Alarm.  
**FEATURES** • Controlling Flight • Ingenuity Unlimited • Practically Speaking • Circuit Surgery • New Technology Update • Net Work – The Internet Page.



### OCT '01 Photostats only

**PROJECTS** • PIC Toolkit Mk3 • Camcorder Power Supply • 2-Valve SW Receiver • Perpetual Projects 4 – Gate Sentinel – Bird Scarer – In-Out Register.  
**FEATURES** • Traffic Control • Ingenuity Unlimited • New Technology Update • Circuit Surgery • Interface • Net Work – The Internet Page • Free 2 CD-ROMs – Microchip 2001 Tech Library.

### NOV '01

**PROJECTS** • Capacitance Meter • Pitch Switch • Lights Needed Alert • Teach-In 2002 Power Supply.  
**FEATURES** • Teach-In 2002 – Part 1 • Practically Speaking • Circuit Surgery • New Technology Update • Ingenuity Unlimited • Net Work – The Internet Page • Free 16-page Supplement – PIC Toolkit TK3 For Windows

### DEC '01

**PROJECTS** • Ghost Buster • PIC Polywhatsit • Twinkling Lights • Mains Failure Alarm.  
**FEATURES** • Teach-In 2002 – Part 2 • Marconi – The Father of Radio • Interface • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Net Work – The Internet Page • 2001 Annual Index.

### JAN '02

**PROJECTS** • PIC Magick Musick • Time Delay Touch Switch • Versatile Bench Power Supply • Forever Flasher.  
**FEATURES** • Teach-In 2002 – Part 3 • Practically Speaking • Ingenuity Unlimited • New Technology Update • Circuit Surgery • Net Work – The Internet Page.

### FEB '02

**PROJECTS** • PIC Spectrum Analyser • Guitar Practice Amp • HT Power Supply • Versatile Current Monitor.  
**FEATURES** • Teach-In 2002 – Part 4 • Ingenuity Unlimited • Russian Space Shuttle Revisited • Circuit Surgery • Interface • New Technology Update • Net Work – The Internet Page.



### MAR '02

**PROJECTS** • MK484 Shortwave Radio • PIC Virus Zapper • RH Meter • PIC Mini-Enigma.  
**FEATURES** • Teach-In 2002 – Part 5 • Ingenuity Unlimited • Programming PIC Interrupts-1 • Circuit Surgery • Practically Speaking • New Technology Update • Net Work – The Internet Page.

### APR '02

**PROJECTS** • Electric Guitar Tuner • PIC Controlled Intruder Alarm • Solar Charge and Go • Manual Stepper Motor Controller.  
**FEATURES** • Teach-In 2002 – Part 6 • Interface • Programming PIC Interrupts-2 • Circuit Surgery • Ingenuity Unlimited • New Technology Update • Net Work – The Internet Page • FREE Giant Op.Amp Data Chart.

**BACK ISSUES ONLY £3.30 each inc. UK p&p.**

Overseas prices £3.80 each surface mail, £5.25 each airmail.

We can also supply issues from earlier years: 1998 (except Jan. to May, July, Nov., Dec.), 1999, 2000 (except Feb., July), 2001 (except Oct). Where we do not have an issue a photostat of any *one article* or *one part* of a series can be provided at the same price.

#### ORDER FORM – BACK ISSUES – PHOTOSTATS– INDEXES

- Send back issues dates .....
- Send photostats of (article title and issues date) .....
- Send copies of last five years indexes (£3.30 for five inc. p&p – Overseas £3.80 surface, £5.25 airmail)

Name .....

Address .....

.....Tel: .....

I enclose cheque/P.O./bank draft to the value of £ .....


Please charge my Visa/Mastercard/Amex/Diners Club/Switch £ ..... Switch Issue No. ....

Card No. .... Card Expiry Date .....

SEND TO: Everyday Practical Electronics, Wimborne Publishing Ltd., 406 Wimborne Road East, Ferndown, Dorset BH22 9ND.  
Tel: 01202 873872, Fax: 01202 874562.  
E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk) On-line Shop: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)  
Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.  
Send a copy of this form, or order by letter if you do not wish to cut your issue.


M05/02

# STORE YOUR BACK ISSUES ON MINI CD-ROMS

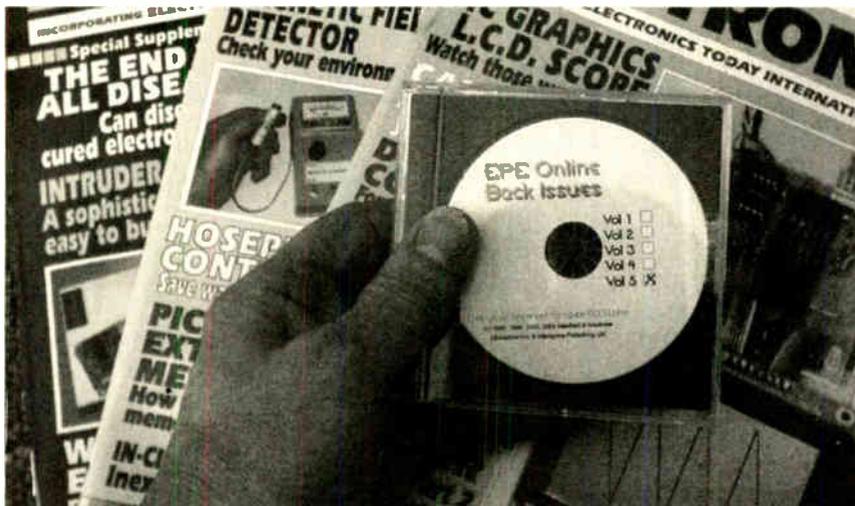

**VOL 5  
NOW AVAILABLE**

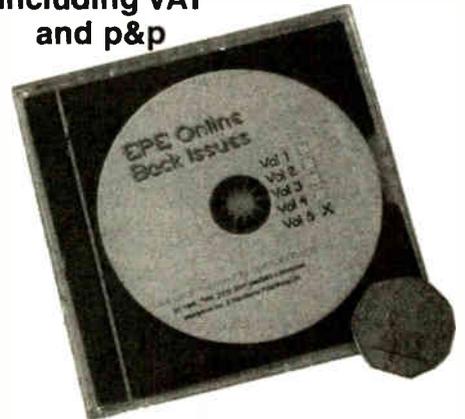**ONLY  
£12.45** each  
including VAT  
and p&p



A great way to buy **EPE Back Issues** – our mini CD-ROMs contain back issues from our **EPE Online** website plus bonus articles, all the relevant PIC software and web links. Note: no free gifts are included. All this for just **£12.45** each including postage and packing.

## VOL 1 CONTENTS

**BACK ISSUES** – November 1998 to June 1999 (all the projects, features, news, IUs etc. from all eight issues). Note: No advertisements are included. **PIC PROJECT CODES** – All the available codes for the PIC based projects published in these issues.

## VOL 2 CONTENTS

**BACK ISSUES** – July 1999 to December 1999 (all the projects, features, news, IUs, etc. from all six issues). Note: No advertisements are included. **PIC PROJECT CODES** – All the available codes for the PIC-based projects published in these issues.

## VOL 3 CONTENTS

**BACK ISSUES** – January 2000 to June 2000 (all the projects, features, news, IUs, etc. from all six issues). **PIC PROJECT CODES** – All the available codes for the PIC-based projects published in these issues.

## VOL 4 CONTENTS

**BACK ISSUES** – July 2000 to Dec. 2000 (all the projects, features, news, IUs etc. from all six issues). **PROJECT CODES** – All the available codes for the programmable projects in these issues.

## VOL 5 CONTENTS

**BACK ISSUES** – January 2001 to June 2001 (all the projects, features, news, IUs etc. from all six issues). **PROJECT CODES** – All the available codes for the programmable projects in these issues, including those for *Interface*.

## EXTRA ARTICLES – ON ALL VOLUMES

**BASIC SOLDERING GUIDE** – Alan Winstanley's internationally acclaimed fully illustrated guide.

**UNDERSTANDING PASSIVE COMPONENTS** – Introduction to the basic principles of passive components.

**HOW TO USE INTELLIGENT L.C.D.s**, By Julyan Ilett – An utterly practical guide to interfacing and programming intelligent liquid crystal display modules.

**PhyzyB COMPUTERS BONUS ARTICLE 1** – Signed and Unsigned Binary Numbers. By Clive "Max" Maxfield and Alvin Brown.

**PhyzyB COMPUTERS BONUS ARTICLE 2** – Creating an Event Counter. By Clive "Max" Maxfield and Alvin Brown.

**INTERGRAPH COMPUTER SYSTEMS 3D GRAPHICS** – A chapter from Intergraph's book that explains computer graphics technology in an interesting and understandable way with full colour graphics.

## EXTRA ARTICLE ON VOL 1 & 2

**THE LIFE & WORKS OF KONRAD ZUSE** – a brilliant pioneer in the evolution of computers. A bonus article on his life and work written by his eldest son, including many previously unpublished photographs.

**NOTE:** These mini CD-ROMs are suitable for use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader (available free from the Internet – [www.adobe.com/acrobat](http://www.adobe.com/acrobat))

Order on-line from  
[www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)  
or [www.epemag.com](http://www.epemag.com) (USA \$ prices)  
or by phone, Fax, E-mail or Post

### BACK ISSUES MINI CD-ROM ORDER FORM

Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 1**

Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 2**

Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 3**

Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 3**

Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 5**

Price £12.45 each – includes postage to anywhere in the world.

Name .....

Address .....

.....

..... Post Code .....

I enclose cheque/P.O./bank draft to the value of £ .....

Please charge my Visa/Mastercard/Amex/

Diners Club/Switch

£ .....

Card No. ....

Expiry Date ..... Switch Issue No. ....

**SEND TO: Everyday Practical Electronics,  
Wimborne Publishing Ltd.,**

**408 Wimborne Road East, Ferndown, Dorset BH22 9ND.**

Tel: 01202 873872. Fax: 01202 874562.


**E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)**

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.
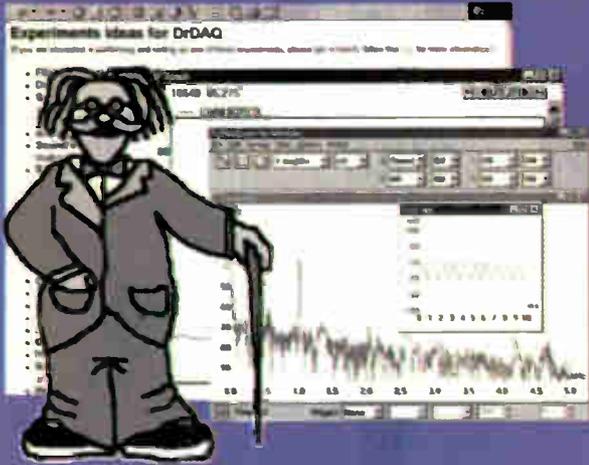
# Measure pH, Voltage, Humidity, Sound & Light, on your PC!




- ✓ Very low cost
- ✓ Built in sensors for light, sound (level and waveforms) and temperature
- ✓ Use DrDAQ to capture fast signals (eg sound waveforms)
- ✓ Outputs for control experiments
- ✓ Supplied with both PicoScope (oscilloscope) and PicoLog (data logging) software

**Only £59!**  
+ VAT

The DrDAQ is a low cost data logger from Pico Technology. It is supplied ready to use with all cables, software and example science experiments.

**DrDAQ represents a breakthrough in data logging.** Simply plug DrDAQ into any Windows PC, run the supplied software and you are ready to collect and display data. DrDAQ draws its power from the parallel port, so no batteries or power supplies are required.

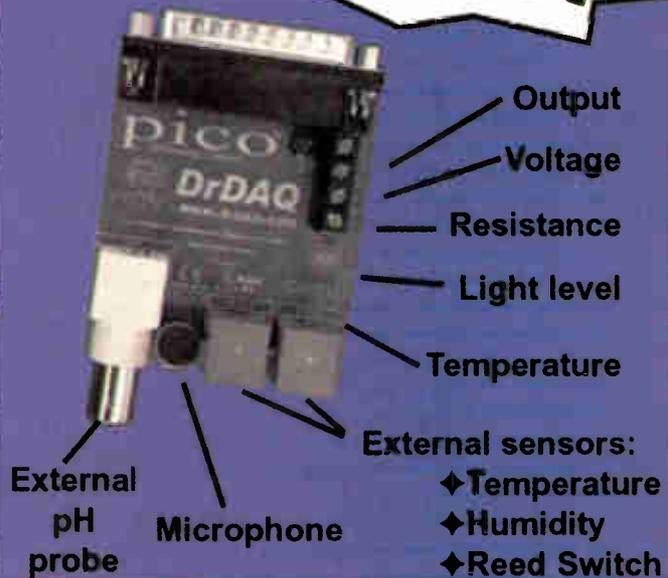As well as the built in sensors, DrDAQ has two sockets for external sensors. When a sensor is plugged in, the software detects it and automatically scales readings. For example, if a temperature sensor is plugged in, readings are displayed in °C. Details are provided to allow users to develop their own sensors.



To order the DrDAQ please choose one of the following options:

- i) Visit our web site and place an order over the Internet,
- ii) Place an order over the phone by ringing the number below, or,
- iii) Fill out the order form and either fax it, or post it back to Pico Technology.

## DrDAQ Order Form:

Quantity	Package	Price inc VAT	Total
	DrDAQ + Software	£69.32	
	DrDAQ + 2 Temp Sensors	£92.85	
	DrDAQ + 2 Temp, pH Electrode, Humidity + Reed Switch Sensors	£175.08	
	Delivery	£4.11	£4.11
	<b>Grand Total</b>	£	

Name			
Address			
Post code			
Phone			
Credit Card	Visa / Mastercard / Switch / Amex		
Card Number			
Expiry Date	/	Start Date & or Issue No.	
Cheque with order	<input type="checkbox"/>		

A Data Logging Breakthrough

**PICO**  
Technology Limited

# READOUT

E-mail: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk)

**John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!**

## WIN A DIGITAL MULTIMETER

A 3 $\frac{1}{2}$  digit pocket-sized I.c.d. multimeter which measures a.c. and d.c. voltage, d.c. current and resistance. It can also test diodes and bipolar transistors.

Every month we will give a Digital Multimeter to the author of the best *Readout* letter.



## ★ LETTER OF THE MONTH ★

### ANALYSING NYQUIST

Dear EPE,

I read with interest the email from Mr Nick de Smith in *EPE* March '02, concerning the *PIC Spectrum Analyser*.

What he says about the lack of anti-aliasing filters and the problems with signals greater in frequency than half the sampling rate (Nyquist frequency) causing aliasing of the signals is absolutely correct.

It has been accepted as a fact that in signal analysis it is not possible to retrieve signals which are greater than half of the sampling frequency. This premise is clearly stated in all textbooks on this subject as the "Nyquist Criteria" or as "Shannon's Sampling Theory".

For example, with a sampling frequency of 2kHz it is not possible to retrieve signals in excess of 1kHz. Any frequencies greater than this 1kHz value will appear as a false or aliased signal and a considerable amount of research and commercial activity has emerged to eliminate such signals by filtering them out from the signal presentation.

However, it has now been proved through a research program (undertaken by myself and Dr R. F. McLean) that the above premise is false and that the limitation of the Nyquist Criteria can easily be overcome. A theoretical study along with a simple capturing device has been developed which can retrieve signals in excess of 2000 times this hitherto limitation in frequency. The system also dispenses with the need for any form of filtering of the incoming signal. For example, by sampling at no greater than 2kHz, frequencies of up to 2.4GHz are unambiguously retrievable.

The technique has been used in vibration condition monitoring and it removes the need for the analyst to predict the maximum frequency of interest in a signal, and thus removes the need to predict the maximum sampling frequency, nor does the analyst need to consider filtering, which could inadvertently filter out the signals of interest. It therefore ensures greater accuracy in diagnosing machinery defects. Also, with its high frequency potential, it will be suitable for use in the field of communication, data encryption and associated disciplines.

The above technique and equipment has already been successfully used within industry. There is a patent pending on this technique and more information can be seen on our web site at [www.HolisticSignals.co.uk](http://www.HolisticSignals.co.uk).

**Stephen H Alsop,  
Sands Systems Ltd, Sheffield,  
via email**

*Thanks, Stephen. Historically, I understand that Nyquist was a radio engineer investigating the most economically reliable method for transmitting speech data. It was in this context that his ratios were established, with 2:1 being the absolute minimum but 3:1 being considered better for adequate intelligibility.*

*Although I know that stable waveforms can be accurately sampled at frequencies well below their fundamental, I assume your techniques are far superior. In which case you have an amazing breakthrough – a bit like breaking the light barrier, or turning the arrow of time backwards!*

### PIC MINI-ENIGMA

Dear EPE,

The *Mini-Enigma* (Mar '02) is an intriguing idea from Nick Dossis, but please bear in mind that your encryption is not as secure as the original Enigma. It is (worst case figures) eight times more complex than a simple substitution cipher. Like the original Enigma, no letter codes to itself, so for each of the first eight characters there are 25 possible resulting encryptions (these eight being the maximum codeword length). This gives rise to 25<sup>8</sup> possibilities. Daunting perhaps, but not outside the scope of modern computing equipment.

The example BYEBYE only appears to have no repetition as the codeword in your article is four characters, ABCD. If, instead, a 3-character codeword was applied, then repetition would be immediately apparent – bad news for attempted secrecy!

I found a software emulation of the original machine, on the Internet, at:  
[www.ugrad.cs.jhu.edu/~russell/classes/enigma/](http://www.ugrad.cs.jhu.edu/~russell/classes/enigma/).

**Godfrey Manning,  
Edgware, Middlesex, via email**

*Hello again Godfrey. You are reading more into Nick's design than you should. Don't you recall passing coded messages on paper between*

*you and your classmates at school, probably even written using "invisible" lemon juice ink? That's how we felt Mini-Enigma would find appeal – as a modern equivalent!*

*Nick himself replies:*

It is nice to hear from someone who also takes an interest in encryption techniques.

I appreciate your comments pointing out that the encryption technique used in the project does not match that of the original Enigma machine. As mentioned in the article, my design was never meant to be a simulation of the original, however to the untrained eye the coded message would still be difficult to crack. I am sure that if you wanted to make the encryption technique more secure it would be quite straightforward to alter the software. I would certainly be interested to know if anybody tries it.

Don't forget that the message could be made more secure if the user transfers the encrypted message into the match-box memory unit. By using this method, the would-be cracker would first need to know how to retrieve the data out of the PIC's EEPROM memory (which, of course, is in encrypted binary format) and then attempt to decipher the message. How this affects the possibility of cracking the code is practically immeasurable.

**Nick Dossis**

### WEATHER MONITORING

Dear EPE,

I came across your magazine quite by chance with the February issue. For some time now I have been wanting to put together a weather station, just for my own records. I am more mechanical/hydraulic orientated but have sort of taught myself a bit about the electrical side. Am currently doing a course with Colu to make me Mech/Elect. Have looked at some of the off the shelf jobs, just plug in as it were but my goodness what a price! Wonder if NASA can afford them?

Do you perhaps know where I can purchase stand-alone units/senders or where to get kits or plans to build my own units. The parameters I am interested in are: barometric pressure; min/max temperature, including windchill (wet bulb thermometer); wind speed/direction; rainfall; humidity. I plan to download this info say every six hours into a datalogger (if feasible) or direct to PC and would also want the results output as graphs.

I am also busy setting up to capture images from satellite to show what the sky is doing. Maybe there are future articles planned? I really enjoy reading the mag.

**Albin Draper, via email**

*Well Albin, my Met Office weather station was published in *EPE* issues Dec '95, Jan '96. However, I am working on a sophisticated update for publication later this year, PIC controlled complete with logger and PC interface. It will do all you mention, except windchill (which I'd not thought about, but might look into). Wind sensing will be solid-state. I regret that I don't know of commercial sources, although a general search via the web may help you. No, we've nothing astronomical in the pipeline.*

### PICtutor AND TK3

Dear EPE,

I recently bought a *PICmicro* development board and the *PIC Toolkit TK3 V1.1*. I was under the impression that with these two I would be able to program the PICMicro on the board and run my own programs. I also have Windows 2000.

When I got the CD it told me that the *Toolkit* will not run on Windows 2000 and it also seems that I need to order more software in order to use the *PICmicro* development board. I also now notice that the *PICtutor* software does not appear to work on Windows 2000 either.

**Chris Ringrow,  
Linden, Alhampton, Somerset,  
via email**

*Chris, you have misunderstood – PICtutor and Toolkit are not related to each other. PICtutor is to teach about PICs, with reference to the PIC16F84 (which the Tutor board will handle). Toolkit 3 is for those who are experienced PIC programmers for use in developing their own programs. As said in the article, Toolkit does not run under Win2000 (although we have an article in the pipeline which gives details of using it with 2000 and XP). PICtutor runs under any Windows format, but if you have problems you should contact the manufacturers, Matrix Multimedia.*

## MSF, WWVB AND BBC

Dear EPE,

Andy Flind's answer to Steve Davenport's email (Mar '02) prompted me to look up the original article (which was July '01 not July '98 as quoted!). Since WWVB broadcasts on the same frequency as MSF (60kHz), there seems every chance that the MSF repeater will work with WWVB without modification.

I wonder if Steve is aware of [www.boulder.nist.gov/timefreq/stations/wwvb.htm](http://www.boulder.nist.gov/timefreq/stations/wwvb.htm) It wasn't until I did a Google search on WWVB and spent 30 minutes trawling through this splendid site, which although not totally relevant unless you live in the US, has some excellent info about time and related topics.

Barry Taylor,  
Rickmansworth,  
via email

Thanks Barry, nice to hear from you again. And, yes, July '01!

Incidentally, folks, Barry also drew our attention to a web site devoted to the history of BBC equipment and those who helped run it, of whom Barry was one. The site is well worth a visit and is at:

[www.roger.beckwith.btinternet.co.uk/bh/menu.htm](http://www.roger.beckwith.btinternet.co.uk/bh/menu.htm).

## INTERRUPTING THE Z BIT

Dear EPE

The article by Malcolm Wiles on *Programming PIC Interrupts* (Mar-Apr '02) was of interest and I was surprised to see the query raised over the use of the instruction MOVF Status,W i.e. what will be the bit in W corresponding to the Z bit of the Status register. Will it be the value in the Status register at the start of the instruction or the value at the end of the instruction? A simple consideration of the hardware of registers will indicate what happens.

The flip-flops of W will have the Status register routed to it and it will be clocked into the flip-flops at the same time that the output of the Zero detection logic is being clocked into the Status register. Hence the old value of the Status register is clocked into W and the zero condition of the old value of the Status register is reflected in the new Z bit which is clocked into the Status register.

Ken Naylor, via email

Malcolm replies:

As a software engineer I would never presume to guess or assume how Microchip have implemented their hardware.

Just because there is a simple, or obvious, maybe even textbook, way of doing something, does it necessarily follow that every implementation does it that way? If the spec or data sheet doesn't explicitly state something, I think it is safest, from a software point of view, not to make any assumptions.

The situation is almost identical with instructions in which W is both the source of data and its destination e.g. SUBWF f,W. The hardware functions as required because the old value of W at the start is processed with the contents of 'f' and the result clocked back into W to give a new value. Hence the new value does not circulate round giving another 'new' value in the same clock cycle.

Malcolm Wiles

## INTERRUPTS CONTEXT

Dear EPE,

I wonder if I have misunderstood the concept of changing memory bank as part of the "context" in Malcolm Wiles' *Using PIC Interrupts*.

Referring to Listing 2 (page 171) it is necessary to select BANK1 prior to initiating the reading of EEPROM by instruction BSF EECON1,RD. Now, what if the interrupt is activated between these two instructions? One of the actions inside the interrupt service routine at ISR is to set its own context and select BANK0. I

can't see how the bank selected by the main program is reinstated prior to return at the RETFIE instruction. It looks as though the return continues to thread main program code but with BANK0 still selected. Is there some implicit re-selection of the main program's required BANK, for example, through the STATUS word?

As an aside, and as I've said before, it's been a revelation starting to read *EPE* again – keep up the good work and don't change any of it! Let me also put in a good word for BBC Basic for Windows (not just because it's developed by a fellow licensed radio amateur!). Limitations it has, just as with any language, but its use must not be underestimated and its new lease of life under Windows is a boon. At its quoted price, it's also excellent value.

Godfrey Manning, G4GLM

Thanks Godfrey for your continued appreciative interest in us. Malcolm Wiles replies to your question:

Reference to the PIC data sheets will show that the Bank select bits (RP0 and RP1) are physically part of the STATUS register (bits 5 and 6 respectively). So their setting on entry to the ISR is preserved (along with Z, C, DC, TO, PD, and IRP) when the STATUS register is saved by the SWAPF STATUS,W . . . MOVWF SAVES sequence at the beginning of the ISR.

After that has been done, the ISR can safely change any of these flags, because they will all be reinstated to the values they had on entry to the ISR by the POP: SWAPF SAVES,W . . . MOVWF STATUS instructions at the end of the ISR. This reinstatement includes the values of RP0 and RP1, so at this point Bank 1 will again be selected if it was the setting on entry to the ISR.

Clearly the ISR must not subsequently contain any code which depends on Bank or other STATUS register flag settings made in the ISR itself. (Recall the discussion in the article which noted that once STATUS has been so restored, only non-STATUS affecting instructions (e.g. SWAPF) can be used in any further ISR code.)

Malcolm Wiles

## NOTABLY SENIOR

Dear EPE,

This year I will become an official Senior Citizen, and although a long-time reader of *EPE* and *PE* before that, I have never written to the magazine before, so would you indulge me for a moment and allow me to say:

Thank you and all contributors for a splendid magazine, I have had many hours of pleasure, education and also some frustration – due to my shortcomings, not *EPE*'s! In particular, the (relatively) recent interest in PIC's has certainly given my grey matter a bashing – that's not a bad thing! – and your *Toolkit Mk3* is a joy. Following the *PIC Tutorials* has enabled me to modify Bart Trepak's excellent *Xmas Lights Dimmer* (a wonderfully informative article, Dec '98) to suit my taste – you are definitely never too old to learn!

My circumstances are such that I am not able to buy *EPE* every month, and this sometimes leaves me with a problem regarding the *Please Take Note* messages. Of course gremlins creep in occasionally, that is understood, but if I can't afford to buy the mag for a month or two after I've built a project, I miss any error corrections that appear.

Would it be possible for all error correction notes to be put onto the Web site? Of course it would be best if I could buy the mag every month – I wish! – but I expect some other readers may have the same problem, and using the already excellent site would really help.

I now intend to construct the *EPE Virtual Scope* (Jan/Feb '98). Without asking you to give too much away, should I go ahead, or do you have any news of an updated version in the pipeline (perhaps using your mastery of VB? – is flattery ok?)!

Derek Waite, via email

*I wholeheartedly agree, Derek, that keeping the grey cells active is vital (and enjoyable!). I'm pleased to know we've helped to inspire you, and flattery is always welcome! We shall actively consider putting Please Take Note on our FTP site, thanks for the suggestion.*

*My Virtual Scope is the most advanced of all those I've done. There have been some simpler versions based around PICs since then but they are more limited than the VS. I've no plans to do another scope unless technology takes a quantum leap forward again in some way regarding the hardware – VB would only offer a cosmetic advantage, not a physical one.*

## WHEELS A-TURNING?

Dear EPE,

We need to measure distances on archeological sites. Did I see a project for a measuring wheel in *EPE* some time ago?

Philip Vallis,  
via the net

*I replied to Philip that I had designed a PIC unit for use on my pushbike for distance etc, and that it was published as PICagoras in two parts Apr/May '97. Philip came back saying:*

*I am not allowed to ride a bike after a heart attack. We need a machine that we can carry around and measure distances accurately. We use 30-metre tapes at present. I built the Earth Resistivity Meter (Jan/Feb '97), but the archeologist that wanted it has not yet built the frame. I built a magnetometer last year that worked first time! We have used it but found nothing so far. If you can design a measuring wheel I would appreciate it.*

*That reminds me of a tale when I was in local government. White lines were paid for by the yard. One day an engineer had to measure a road about one mile long, using the measuring wheel. On that day he had been in the pub for lunch. He was somewhat incapable so he called on a van driver to let him lay down in the back and he put the wheel down at the start of each line and lifted it off at the end. Unfortunately the driver decided that he was going too slow and the wheel started going faster and faster. When they got to the end of the road they had measured enough white lines to stretch from London to Brighton.*

*Philip, I'm sorry to hear you can't enjoy the pleasures(?) of pushbikes, although I'm on the verge of feeling that age is gradually putting a spoke in my wheels!*

*My PICagoras, though, can be used with any wheel and its diameter can be easily programmed into the unit using a signal generator. I still think it might do for you, but regret I can't offer to do it for you.*

*What a delightful tale! It reminds of when my wife and I were in Zante, one of the Greek islands. Cycling along a main road that had recently been white lined, the painting gang had not bothered to avoid a snake in their path, which was now also painted, but dead of course!*

*Incidentally, I'm soon to start testing an Earth Resistivity Logger that (I think!) I have designed for archeology.*

## TK3 AND PIC16F74


Dear EPE,

Is it possible to modify the TK3 software to incorporate the PIC16F74? I have several for my private use, but no means to program them as yet. It would seem they are not as popular as their 8K cousins.

Peter Barratt, Australia,  
via email

*It appears to be pin-compatible with the F874/7 series and should program OK in TK3 – just treat it as being from that family, although its configuration bits may not be the same. Reading its data sheet via [www.microchip.com](http://www.microchip.com) should give you the '74's full details.*

# Learn About Microcontrollers

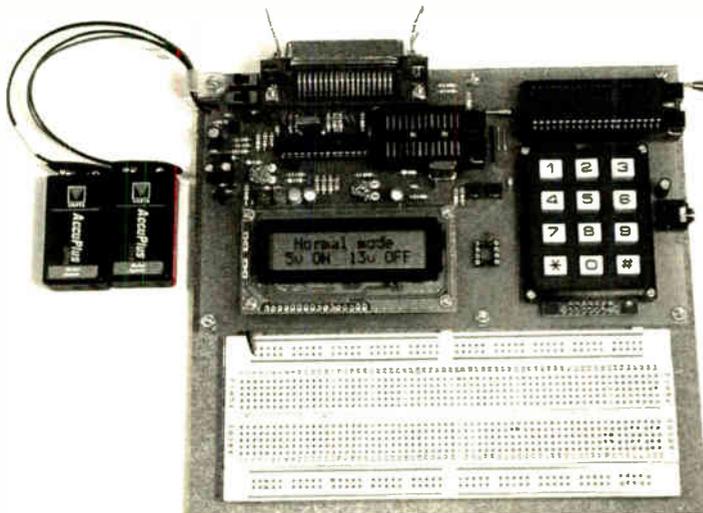

## PIC Training & Development System

The best place to start learning about microcontrollers is the PIC16F84. This is easy to understand and very popular with construction projects. Then continue on using the more sophisticated PIC16F877 family.

The heart of our system is a real book which lies open on your desk while you use your computer to type in the programme and control the hardware. Start with four very simple programmes. Run the simulator to see how they work. Test them with real hardware. Follow on with a little theory.....

Our complete PIC training and development system consists of our universal mid range PIC programmer, a 306 page book covering the PIC16F84, a 212 page book introducing the PIC16F877 family, and a suite of programmes to run on a PC. The module is an advanced design using a 28 pin PIC16F872 to handle the timing, programming and voltage switching requirements. The module has two ZIF sockets and an 8 pin socket which between them allow most mid range 8, 18, 28 and 40 pin PICs to be programmed. The plugboard is wired with a 5 volt supply. The software is an integrated system comprising a text editor, assembler disassembler, simulator and programming software. The programming is performed at normal 5 volts and then verified with plus and minus 10% applied to ensure that the device is programmed with a good margin and not poised on the edge of failure. Requires two PP3 batteries which are not supplied.

- Universal mid range PIC programmer module
  - + Book Experimenting with PIC Microcontrollers
  - + Book Experimenting with the PIC16F877 (2nd edition)
  - + Universal mid range PIC software suite
- .....+ PIC16F84 and PIC16F872 test PICs. . . . . £157.41
- UK Postage and insurance. . . . . £ 7.50
- (Europe postage & Insurance. . £13.00. Rest of world. £22.00)

## Experimenting with PIC Microcontrollers

This book introduces the PIC16F84 and PIC16C711, and is the easy way to get started for anyone who is new to PIC programming. We begin with four simple experiments, the first of which is explained over ten and a half pages assuming no starting knowledge except the ability to operate a PC. Then having gained some practical experience we study the basic principles of PIC programming, learn about the 8 bit timer, how to drive the liquid crystal display, create a real time clock, experiment with the watchdog timer, sleep mode, beeps and music, including a rendition of Beethoven's *Für Elise*. Finally there are two projects to work through, using the PIC16F84 to create a sinewave generator and investigating the power taken by domestic appliances. In the space of 24 experiments, two projects and 56 exercises the book works through from absolute beginner to experienced engineer level.

### Ordering Information

Telephone with Visa, Mastercard or Switch, or send cheque/PO for immediate despatch. All prices include VAT if applicable. Postage must be added to all orders. UK postage £2.50 per book, £1.00 per kit, maximum £7.50. Europe postage £3.50 per book, £1.50 per kit. Rest of World £6.50 per book, £2.50 per kit.  
Web site:- [www.brunningssoftware.co.uk](http://www.brunningssoftware.co.uk)

## NEW 32 bit PC Assembler

*Experimenting with PC Computers* with its kit is the easiest way ever to learn assembly language programming. If you have enough intelligence to understand the English language and you can operate a PC computer then you have all the necessary background knowledge. Flashing LEDs, digital to analogue converters, simple oscilloscope, charging curves, temperature graphs and audio digitising.

Kit now supplied with our 32 bit assembler with 84 page supplement detailing the new features and including 7 experiments PC to PIC communication. Flashing LEDs, writing to LCD and two way data using 3 wires from PC's parallel port to PIC16F84.

- Book *Experimenting with PCs* ..... £21.50
- Kit 1a 'made up' with software ..... £52.00
- Kit 1u 'unmade' with software ..... £45.00

## C & C++ for the PC

*Experimenting with C & C++ Programmes* teaches us to programme by using C to drive the simple hardware circuits built using the materials supplied in the kit. The circuits build up to a storage oscilloscope using relatively simple C techniques to construct a programme that is by no means simple. When approached in this way C is only marginally more difficult than BASIC and infinitely more powerful. C programmers are always in demand. Ideal for absolute beginners and experienced programmers.


- Book *Experimenting with C & C++* ..... £24.99
- Kit CP2a 'made up' with software ..... £32.51
- Kit CP2u 'unmade' with software ..... £26.51
- Kit CP2t 'top up' with software ..... £12.99

## The Kits

The assembler and C & C++ kits contain the prototyping board, lead assemblies, components and programming software to do all the experiments. The 'made up' kits are supplied ready to start. The 'top up' kit is for readers who have already purchased kit 1a or 1u. The kits do not include the book.
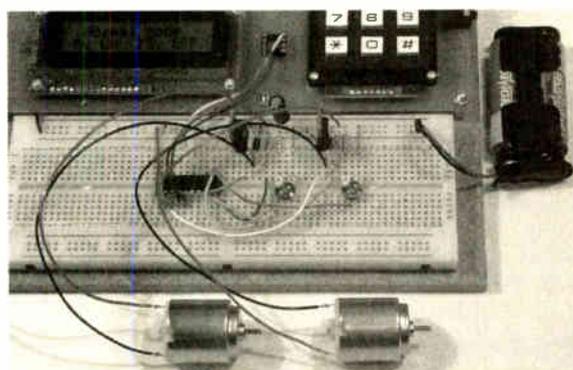
## Hardware required

All systems in this advertisement assume you have a PC (386 or better) and a printer lead. The experiments require no soldering.



## Experimenting with the PIC16F877

The second PIC book starts with the simplest of experiments to give us a basic understanding of the PIC16F877 family. Then we look at the 16 bit timer, efficient storage and display of text messages, simple frequency counter, use a keypad for numbers, letters and security codes, and examine the 10 bit A/D converter.

The 2nd edition has two new chapters. The PIC16F627 is introduced as a low cost PIC16F84. We use the PIC16F627 as a step up switching regulator, and to control the speed of a DC motor with maximum torque still available. Then we study how to use a PIC to switch mains power using an optoisolated triac driving a high current triac.

Mail order address:

**Brunning Software** 138 The Street, Little Clacton, Clacton-on-sea, Essex, CO16 9LS. Tel 01255 862308

# WASHING READY INDICATOR



## TERRY DE VAUX-BALBIRNIE

*Has the washing machine finished?  
– Avoid those washday blues!*

**O**UR OLD washing machine gave long and faithful service. Unfortunately, when it did eventually fail, it was not possible to repair it economically.

### DREAM MACHINE

The replacement washing machine is a famous brand, renowned for its high quality and long life. However, after using it for the first time, it became apparent that something that “old faithful” had was lacking in its successor. This was a lamp that came on when it had completed the washing.

The only way of knowing whether it has finished or not is to look closely at the program switch or listen until the machine has not made a sound for some time. Taking the washing out promptly is important if you wish to re-load the machine or if you want to dry the laundry as quickly as possible.

A further point is that if the washing machine is situated in a garage or other place remote from the house, even a warning light will be of little help. You would have to visit it periodically to check whether it had finished its work.

### LAUNDRY DONE

The washing machine alarm circuit described here will give an audible signal (in the form of high-pitched beeping) when the washing cycle has finished. If the machine has been left on a “rinse hold”

setting, it will give a signal when the program has reached this point.

This will prevent the user from forgetting about it and leaving the washing overnight in a machine filled with water. Readers may find the circuit useful for other similar appliances and it has been tested successfully with tumble driers.

However, if the washing machine is situated in some place remote from the house, the buzzer could be placed somewhere else – in the kitchen, for example. For this to be done, you would need to route a length of light-duty twin wire between the main unit and buzzer position.

While operating under standby conditions, the prototype required just  $500\mu\text{A}$ , which may be regarded as negligible. While actually sounding, the current rises to a few milliamps depending on the



Fig. 1. Block schematic diagram for the Washing Ready Indicator.

Being battery-operated, the circuit is safe to construct and in operation. Also, because no modifications are made to the appliance itself, using the device will not invalidate any manufacturer's warranty.

The circuit consists of a main unit (see photographs) which is placed near the washing machine. This contains the circuit panel and a 6V battery pack. There is an on-off switch on the front of the case and a socket on the side which is used to connect a sensor. This is placed so as to make mechanical contact with some part of the washing machine.

The warning device (a small piezo buzzer) will normally be mounted on the circuit board with a hole drilled in the box to allow the sound to pass through.

buzzer used. The internal 6V battery pack will provide several hundred operating hours and will probably give more than one year of service.

### OVERVIEW

The Washing Ready Indicator works by responding to the sound and/or vibration that occurs while the washing machine motor is operating. When correctly adjusted, other sources of sound have only a minimal effect unless they are particularly loud. Even if they do have some temporary effect, this should not prevent the circuit from giving a proper warning.

The sensor consists of an electret microphone insert (that is, the working part without the external case). While the motor is turning, this provides an electrical signal which is passed to the main unit.

While the machine vibrations continue, the warning does not sound. When it stops, the warning continues to be held off for a further preset time and after that the buzzer sounds.

### HOLD-OFF TIME

This hold-off time is necessary because the motor in a washing machine is not operating all the time during the washing cycle. The drum turns in alternate directions to prevent the clothes tangling and there will be several seconds of silence between each movement.

There may also be longer “quiet” times when the machine is filling with water. The hold-off time must be sufficient to take account of all these factors and will be set by the user for best effect at the testing stage.



## LONG SILENCE

To prevent the warning being given while the washing machine is not in use (obviously a long period of silence!), the unit must be switched on and off manually. The user is unlikely to forget to switch it off because the buzzer will continue to sound until this has been done. However, he or she will need to remember to switch it on at the beginning of the washing cycle whenever a warning is required.

## HOW IT WORKS

Basic operation of the Washing Ready Indicator is best illustrated by the block diagram shown in Fig.1. It will be seen that this comprises seven main parts: vibration sensor; audio amplifier; level detector; integrator; Schmitt trigger inverter; slow astable (low-frequency oscillator) and piezo buzzer.

The complete circuit diagram is shown in Fig.2. MIC1 is the electret microphone insert of the type specified in the parts list. This has an inbuilt f.e.t. preamplifier which requires its own power supply. This is derived from the 6V battery pack, B1, through resistor R1.


Operational amplifier (op.amp), IC1 is a quad device – it contains four identical units IC1a, IC1b, IC1c and IC1d (although only three of these are actually used). IC1a is used for the audio amplifier, IC2b for the level detector and IC1c for the Schmitt trigger inverter.

Taking IC1a first, this is used in a.c. inverting mode. For this, the signal arriving from the sensor MIC1 is applied, via coupling capacitor C1 and input resistor R2, to the inverting input (pin 2).

Capacitor C1 allows the alternating current (a.c.) component (that is, the signal) to pass while blocking the passage of direct current (d.c.) This prevents it interfering with the d.c. conditions of the op.amp.
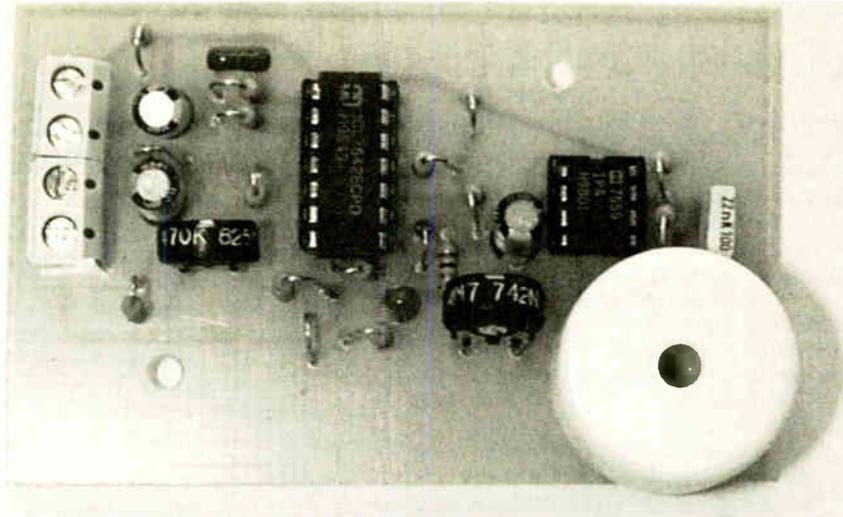
## STANDING CONDITIONS

As far as d.c. is concerned, the op.amp non-inverting input (pin 3) is held at one-half of supply voltage (3V nominally) by the potential divider action of equal-value resistors R3 and R4. Regarding the a.c. signal, it is at 0V since the impedance of



Component layout on the finished circuit board.

capacitor C2 is very small at the audio frequencies involved. The standing d.c. voltage at the output (pin 1) is equal to that at the non-inverting input – that is, nominally 3V.

The gain of the amplifier is determined by the ratio of feedback resistance (R5) to input resistance (R2). In fact, the gain is negative but this has no practical consequence here.

With the values specified, the gain is therefore fixed at (-)220. The result is that a voltage of some 1V peak-to-peak will exist at the output, pin 1, and this will be superimposed on the standing d.c. voltage.

Capacitor C3, connected in parallel with the feedback resistor R5, provides a low impedance path at higher frequencies but a much higher one at the typical frequencies of vibration. It thus has little effect at the "intended" frequencies but the gain is much reduced at higher ones. The circuit is therefore less sensitive to much of the "normal" sound in the vicinity of the washing machine.

## ON THE LEVEL

The level detector based on IC1b "looks at" the voltages applied to its inverting (-) and non-inverting (+) inputs (pin 6 and

pin 5 respectively). If the voltage at pin 5 exceeds that at pin 6 the op.amp will be on with the output (pin 7) high. Otherwise it remains low.

The signal provided by the output of the audio amplifier (IC1a pin 1) is applied direct to IC1b inverting input (pin 6). A certain preset voltage is applied to the non-inverting input, pin 5, by the potential divider network made up of R6/VR1/R7.

Preset potentiometer VR1 will be adjusted at the end so that the voltage at pin 5 is slightly lower than that at pin 6 (that is, less than 3V) when no vibration is detected. The state of the level detector output (pin 7) will therefore be low when no vibration exists.

Fixed resistors R6 and R7 narrow the range of adjustment of VR1 to the middle one-third of the voltage range (nominally 2V to 4V) and this simplifies setting-up at the end.

## RAPID SWITCHING

When vibration is detected, the voltage at IC1b pin 6 rises on the positive half-cycles and falls on the negative ones. The former have no effect.

However, on the negative excursions, the voltage at pin 6 will fall below that at

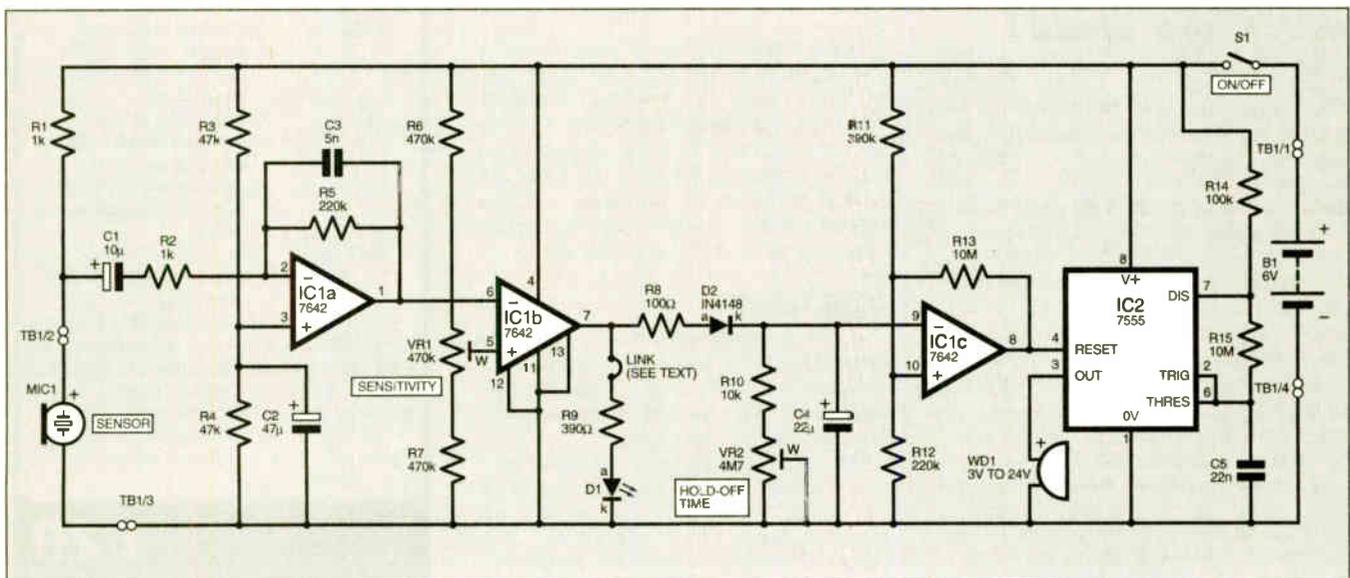


Fig.2. Complete circuit diagram for the Washing Ready Indicator. The battery pack B1 is made up of 4 x AA alkaline cells.

pin 5 and this will result in the output (pin 7) switching between high and low states at the frequency of vibration. The length of the on times will depend on how much the a.c. wave falls below the voltage at pin 5 as set by preset VR1. This preset therefore provides the Sensitivity control.

Note that, as the supply voltage falls in the process of battery ageing, this makes no difference to the operating point. This is because the voltages applied to both IC1b inputs vary in the same proportion.

Ignoring the connection from the output of IC1b at pin 7 to resistor R8 for the moment, the signal from the output of the level detector can be directed to the light-emitting diode (l.e.d.) D1 using a "jumper wire" on the circuit board. The operating current is limited to some 10mA by series resistor R9.

The l.e.d. is used to check operation of the circuit up to this point because it will flash when vibration is picked up. It is also used to make a reasonably correct adjustment to preset VR1. At the end of testing, the jumper wire will be cut to prevent the l.e.d. from working and so reduce the current requirement of the circuit.

## INTEGRATION

Returning now to the output from the level detector IC1b at pin 7, consider the current flowing through fixed resistor R8 and diode D2. This allows capacitor C4 to charge up and provides the "integrator" aspect of the circuit.

While pulses are given by IC1b output (pin 7), the relatively small value of resistor R8 allows the capacitor to charge to almost supply voltage in a very short time. In fact, it will not quite reach this value because it is being constantly drained by the network comprising fixed resistor R10 and preset VR2.

When the pulses stop, the capacitor gradually discharges in a time dependent on the adjustment of VR2. It cannot drain back into IC1b pin 7 because diode D2 is reverse biased.

Note that without R10 and VR2, capacitor C4 could only discharge by leakage and this would take a very long time. This is because the input resistance of op.amp IC1c (whose purpose will be explained presently) is extremely high.

## INVERTING EFFECT

Op.amp section, IC1c gives a Schmitt trigger inverting effect. It works like this. The voltage existing across capacitor C4 is applied to the inverting input (pin 9). The non-inverting input (pin 10) is maintained at approximately 2V by the potential divider action of resistors R11 and R12.

While pulses are detected, the inverting input voltage (which is close to supply positive voltage) will exceed the non-inverting one and IC1c output (pin 8) will be low. When the pulses stop and sufficient time has elapsed to discharge C4 below the 2V level, the conditions reverse and pin 8 will go high. Resistor R13 provides some positive feedback and sharpens the switching between the output on and off states.

When the "machine" vibration stops for a short time, the voltage across capacitor C4 does not fall sufficiently for IC1c output pin 8 to go high. When vibration is detected again, the capacitor rapidly charges to its former value.

## TIME ADJUSTMENT

The hold-off time can be adjusted using preset VR2 between limits of almost zero and two minutes approximately. The shortest timing is provided simply for testing purposes. The maximum timing could be extended if required by raising the value of capacitor C4.

A CMOS version of the 555 timer i.e., IC2, is configured as a low frequency astable. While vibration is detected, the low state of IC1c output (pin 8) applies a similar state to IC2 reset input (pin 4). This disables the device and it does nothing.

When the hold-off time expires, IC1c pin 8 goes high and, with IC2 reset input also high, a stream of pulses are passed to IC2 output at pin 3 and hence to buzzer WD1. The frequency of oscillation is determined by the value of fixed resistors R14 and R15 in conjunction with capacitor C5 and with the values used, this should be some 3kHz.

In fact, it appears to vary with operating conditions and was much slower in the prototype. This may be seen as a benefit because it reduces the current requirement. The buzzer connected to IC2 output, pin 3, therefore bleeps in sympathy.

## CONSTRUCTION

Construction of the Washing Ready Indicator is based on a single-sided printed circuit board (p.c.b.). This board is available from the *EPE PCB Service*, code 342. The topside component layout, interwiring to off-board switch and jack socket, and full-size underside copper foil master pattern are shown in Fig.3.

Begin construction by drilling the two mounting holes and soldering the i.c. sockets and p.c.b. mounting terminal block (TB1) in position. Solder the jumper wire to link points A and B. Follow with the resistors and capacitors (including preset potentiometers VR1 and VR2).


Now, add the polarity-sensitive components which are the electrolytic capacitors, l.e.d. D1, diode D2 and buzzer WD1 (if this is to be mounted on-board) taking care over the orientation of these components. Adjust preset VR1 to approximately mid-track position and VR2 fully anti-clockwise (as viewed from the bottom edge of the p.c.b.). This gives a near-zero hold-off time.

Finish construction of the circuit board by inserting IC1 (but not IC2 at this stage) into its socket taking care with the orientation. Since this is a CMOS component, it is vulnerable to damage by static charge which may be present on the body. To avoid any such problems, touch something which is earthed (such as a metal water tap) before removing the i.c. from its packaging.
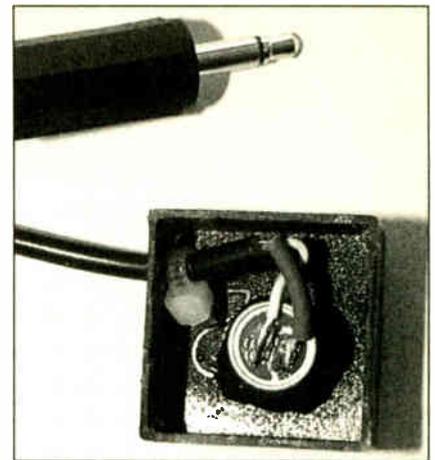
## TESTING

It will be found convenient to make a basic test on the unit before the p.c.b. is mounted in its box. In this way, errors are more easily corrected and the preset potentiometers are more accessible.

Cut off a short piece of light-duty twin wire to connect the microphone insert sensor (MIC1) temporarily to the terminal block at points TB1/2 and TB1/3. Look carefully at the microphone connecting pads. The one which is connected to the metal case of the device must be taken to



Using screened audio cable to connect the electret microphone to the main unit.

## COMPONENTS

### Resistors

R1, R2	1k (2 off)
R3, R4	47k (2 off)
R5, R12	220k (2 off)
R6, R7	470k (2 off)
R8	100Ω
R9	390Ω
R10	10k
R11	390k
R13, R15	10M (2 off)
R14	100k

All 0-25W 5% carbon film.

See  
**SHOP  
TALK**  
page

### Potentiometers

VR1	470k sub-min. enclosed carbon preset, vert.
VR2	4M7 sub-min. enclosed carbon preset, vert.

### Capacitors

C1	10μ radial elect. 16V
C2	47μ radial elect. 16V
C3	5n ceramic
C4	22μ radial elect. 16V
C5	22n ceramic

### Semiconductors

D1	3mm red l.e.d.
D2	1N4148 signal diode
IC1	ICL7642 quad op.amp
IC2	ICM75551PA CMOS timer

### Miscellaneous

WD1	miniature solid-state buzzer - 3V to 24V operation at 10mA maximum
TB1	4-way p.c.b. screw terminal block - 5mm pin spacing
MIC1	miniature two-terminal electret microphone insert
SK1/PL1	3.5mm mono panel mounting jack socket, with plug

Printed circuit board available from the *EPE PCB Service*, code 342; plastic box, size 143mm x 82mm x 44mm; 8-pin i.c. socket; 14-pin i.c. socket; battery holder and four AA size alkaline cells; PP3 type battery snap (or as required); light-duty screened wire; multistrand connecting wire; solder, etc.

Approx. Cost  
Guidance Only

**£20**  
excluding batt

the negative (0V) of the supply – that is to TB1/3. The other one is connected to TB1/2.

Connect the PP3 battery snap (or as appropriate) to TB1/1 and TB1/4 taking care over the polarity. Insert the cells in their holder, apply the battery snap and switch on.

Adjust Sensitivity preset VR1 to the point where the “test” l.e.d. D1 is just off. If the microphone is touched, or the table top is tapped, the l.e.d. should flash momentarily. Adjust VR1 so that this happens reliably.

The battery should now be disconnected and IC2 inserted into its socket observing the anti-static precautions mentioned earlier for IC1. It is best to leave the l.e.d. in circuit for the moment.


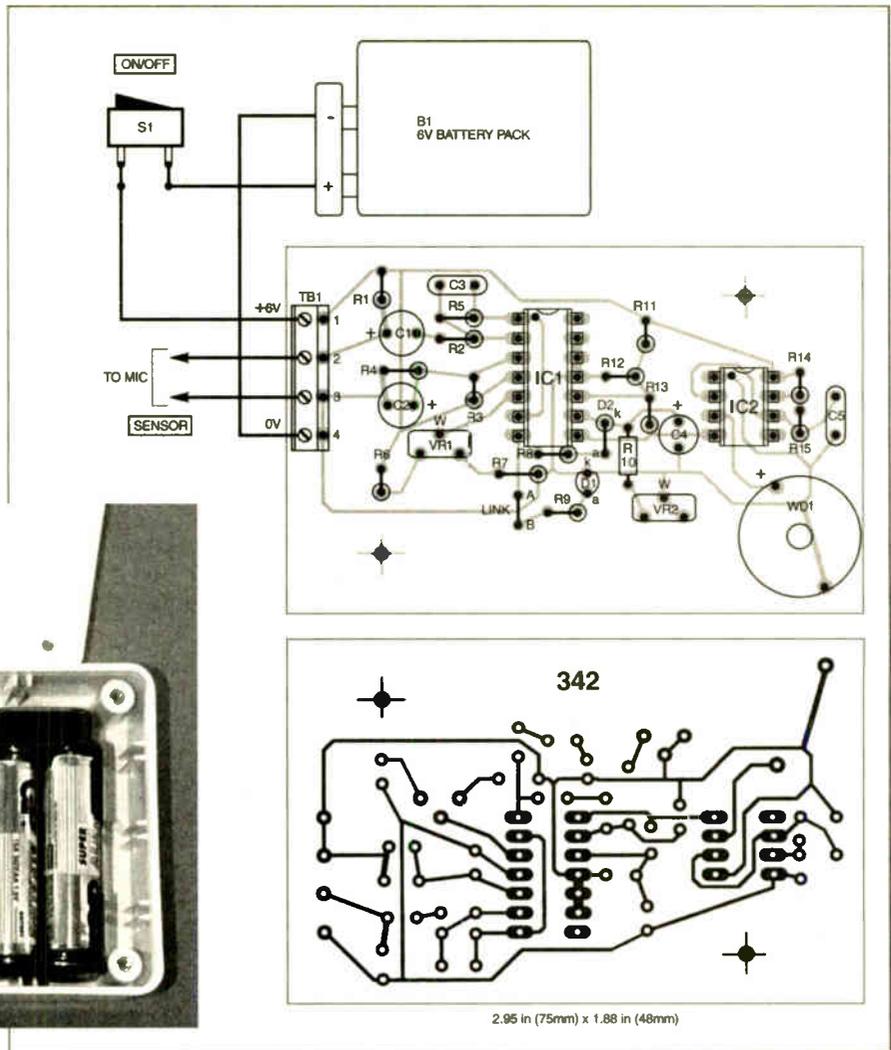


Fig.3. Printed circuit board component layout, full-size copper foil master and wiring to off-board components.

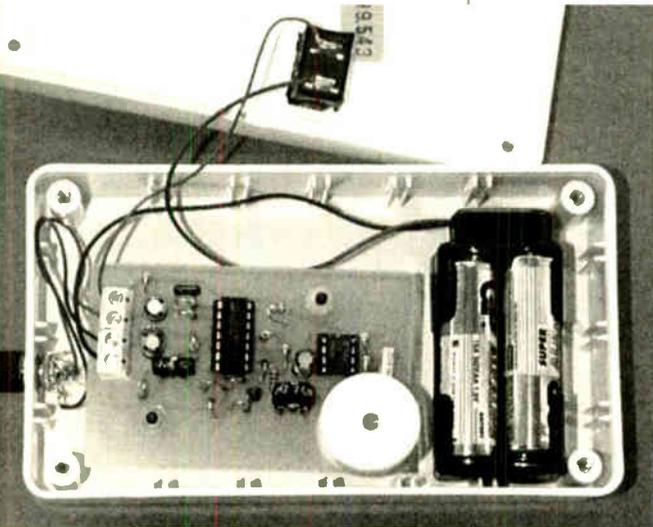

Positioning of components inside the plastic case.

With no sound detected, buzzer WD1 should operate. Sound should make the buzzer stop but begin again as soon as it stops. This might not work properly unless preset VR2 is adjusted slightly clockwise to give a small hold-off time. If that works, adjust VR2 to provide a longer hold-off time of, say, 30 seconds.

Check that if sounds are made periodically within this time, the sound is held off. This will provide an approximate setting but final adjustments to the presets can only be made with the unit under actual operating conditions.

### BOXING UP

Remove the temporary sensor wires from terminal block TB1. Place the p.c.b. and battery holder on the bottom of the box to find their best positions. If the unit is to be wall-mounted, remember to allow space for the holes which will be used to attach it.

Mark through the holes for the various parts, also mark positions for on-off switch (S1) and the 3.5mm mono jack socket which is used for sensor MIC1 connection. Measure the buzzer position and drill a hole in the lid directly above this. If the buzzer is to be mounted remotely, mark the position for a further socket (say, a small “power-in” or a 2.5mm mono jack type) for this to be connected.

Remove all these parts, drill the holes and attach them. Use plastic stand-off insulators for p.c.b. mounting to bring the buzzer up to level of the hole in the lid.

Refer to Fig.3 and complete the wiring using light-duty stranded connecting wire. If buzzer WD1 is mounted remotely, connect the buzzer pads on the p.c.b. to the buzzer output socket taking account of the polarity.

### SITING THE UNIT

Decide on a suitable position for the main unit. This should be placed fairly close to the washing machine (say, within 4 metres). Make the sensor connection using light-duty single screened wire (microphone cable). This is because ordinary wire could pick-up stray mains “hum” and could result in the injection of unwanted signals into the circuit. It is possible that this could hold off the warning in the absence of any vibration. When connecting the jack plug to the sensor wire, solder the outer (sleeve) terminal to the screening.

Mount the microphone insert inside a small plastic box (a potting box was used in the prototype). To do this, drill a hole to make a push fit for the microphone insert. Secure it using a little quick-setting adhesive.

Drill a further hole in the side of the box for the connecting wire to pass through. Pass the wire through the hole and, allowing a little slack apply a tight cable tie to provide strain relief.

Twist and sleeve some of the screening braid and solder the wires to the microphone pads. The pad which is connected to the

metal case of the microphone should be the one which is connected to the screening.

If the buzzer is to be mounted remotely, the connecting wire may be of any convenient length and be of any light-duty stranded twin type.

### FINAL TESTS

With the main unit in position, route the screened sensor wire between it and the washing machine and plug it in. Make some tests with the sensor in various positions observing the l.e.d. A suitable place should be found where the drumming noises of the washing machine case cause the l.e.d. to flash brightly. When satisfied about this, make further adjustments to preset VR1 as required.

In some cases it will not be found necessary for the sensor to touch the washing machine at all – just placed close enough for it to pick up the noise. However, if doing this, you may need to set the sensitivity somewhat higher and this may make the unit more susceptible to the pick-up of stray random noise.


Make some tests under real operating conditions. Adjust preset VR2 for a suitable hold-off time so that the buzzer is prevented from operating under all “silent” conditions on all washing programs. When satisfied about all aspects of operation, cut the jumper wire on the p.c.b. to prevent the l.e.d. operating.

Happy washday! □

# SURFING THE INTERNET

# NET WORK

## ALAN WINSTANLEY

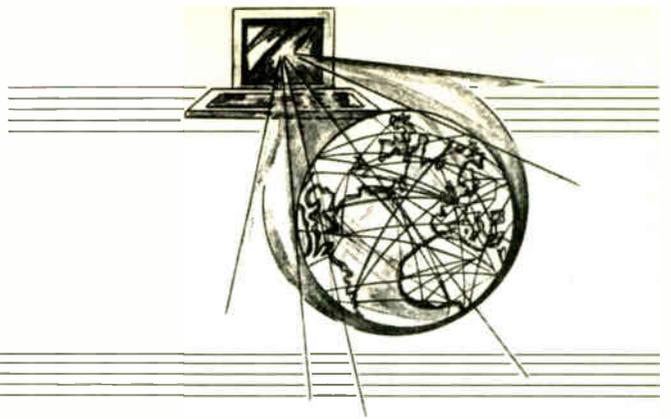

WELCOME to *Net Work*, our monthly column written for Internet users. Have you visited our web site at [www.epemag.wimborne.co.uk](http://www.epemag.wimborne.co.uk) recently? You can view a summary of all issues of *EPE* dating back several years, with colour photographs and indexes of projects also available together with any *Please Take Note* corrections for that year. You can buy back issues, books, CD-ROMs, videos and p.c.b.s online via our online shop ([shopdoor.htm](http://shopdoor.htm)). You can also download copies of the magazine from [www.epemag.com](http://www.epemag.com) (our Online issue priced in US dollars).

Our "Chat Zone" message board is proving to be increasingly popular, and is an easy way of posting plain text messages into a forum where you can communicate with other readers; if you are looking for advice or help from fellow electronics enthusiasts, why not ask them by posting your message into the *EPE* Chat Zone? We are very grateful to the regular readers who support us and help out with queries in the Chat Zone.

### Strip Teaser

In the March '02 issue of *EPE Net Work* I pointed the way to a simple Stripboard Designer graphics program that is available as shareware from [www.geocities.com/stripboarddesigner](http://www.geocities.com/stripboarddesigner). The principle of shareware is very simple – you download the demo for free and if you like the product, you buy it! If you don't like it, you haven't lost anything! Some of the world's best programs such as JASC Paint Shop Pro started out as modest shareware, so by supporting shareware honestly you encourage software authors to develop their ideas further.

One of the tasks I still enjoy is the creation of stripboard layouts, which I always found to be a stimulating mental exercise (followed by all the troubleshooting afterwards!). For decades I used quadrille (squared) paper and after some frenetic scribbling and erasing I would finally develop a layout that I could take to the workbench. Nowadays, computers can help a lot by allowing layouts to be created and edited on-screen, also the design can be saved and printed for future reference.

Probably the first commercial program to help with this task was Ambyr's *Stripboard Magic*, which my fellow contributor Andy Flind (who creates many of *EPE*'s drawings) reviewed in *EPE* March 1998 issue. The program could create automatically from a circuit diagram a layout either for stripboard or a plug-in solderless breadboard.


I occasionally get emails asking me what happened to *Stripboard Magic*. Well, just as the program was starting to gain acceptance, it is believed that Ambyr sold the exclusive distributorship to a mail order company. The program and its web site sank without trace and Ambyr Ltd. was dissolved in December 1999 (according to Companies House Online at [www.companieshouse.gov.uk](http://www.companieshouse.gov.uk)).

### Lochmaster 2.0

However, I am very grateful to reader *Branko Zupan* in Slovenia who has brought to my attention a German stripboard design package called *Lochmaster*. This is produced by Abacom and an English version is downloadable from [www.abacom-online.de](http://www.abacom-online.de). The demo allows ten elements to be positioned, and print and save functions have been disabled. It appears to be a very good tool for helping to design layouts by hand, although it does not automate the total design process as *Stripboard Magic* did.

The component library is comprehensive and incorporates all the usual discrete and integrated devices, semiconductors, plus a good range of hardware, including fasteners, pin headers and d.i.l. sockets. New components can also be added to the library.

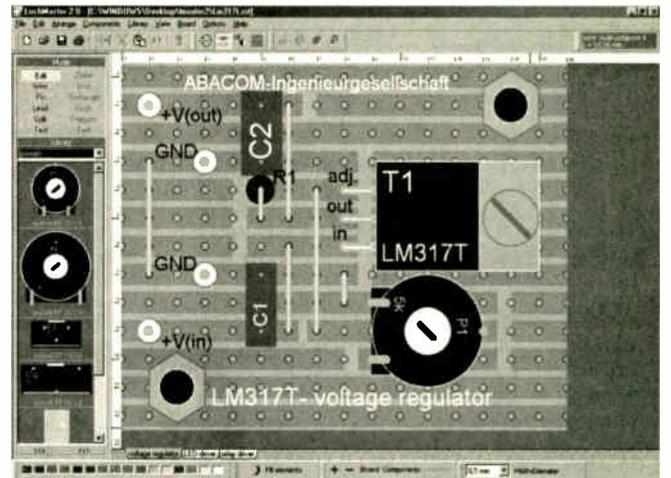
Stripboards are designed by placing components on the board, rotating and linking as necessary and making breaks in the copper track using the Split command. Different views are available – the component side of course, plus an X-ray mode and a solder-side (flipped) view. The views are zoomable and, usefully, a Components List can be created and printed from the board design.



Top view of a small sample board created in Lochmaster 2.0.

New pages can be added to a project design, each page having its own "tab". A very handy feature is the Test command, which literally highlights a route taken by a conductor throughout the board, including wire jumper links (but not through components). You can, therefore, reveal a path of interconnections to prevent unwanted short circuits to other components or strips.

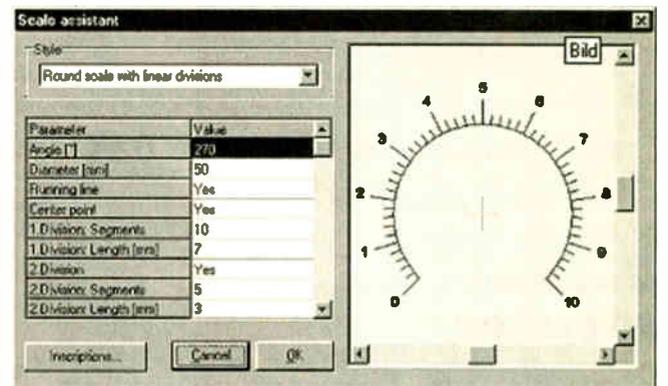You still need rather an agile mind to create stripboard layouts, but this technique will suit many electronics enthusiasts absolutely fine. Lochmaster 2.0 is available direct from Abacom for 35.28 (about £22 or US\$30).



Scale Assistant, part of the Front Designer package, creates complex scales for rotary controls.

### Front Line


Also worth checking out is Abacom's Front Designer package for drafting front panel layouts for your projects. Amongst other things, its "Scale Assistant" helps with the divisional markings for those pesky rotary switches and volume controls. You can then print out the final design onto transparent film or photopaper (or consider large Avery "invisible" clear inkjet labels?) and affix it to your project. The whole point of such software packages, of course, is that you can play around on-screen to your heart's content without doing any damage to that precious anodised aluminium panel.

See you next month – you can email Alan at [alan@epemag.co.uk](mailto:alan@epemag.co.uk) or visit his web site at:

<http://homepages.tcp.co.uk/~alanwin>.

Experience the magic of

# NEON STRING

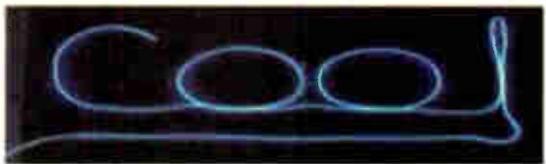

Neon string uses the principle of Electroluminescence. At just 2.5mm in diameter it produces a bright, crisp light, but no heat.

## IMAGINE THE POSSIBILITIES!

Safety illumination. Disco. Signs. Special effects.

It is so flexible you can tie it in knots! Choose between 1 metre green or 1 metre blue string. Supplied ready fitted with all connectors including 9V battery clip. Can operate at 12V for automotive use.

1 metre of string with connector, power pack with fitted input and output connector.

includes delivery **£29.99** includes VAT

Cheque with order. Payable to Inntact Electronics  
**Inntact Electronics, Unit 5, Butterley Croft,  
Whiteley Road,  
Ripley, Derbyshire DE5 3QL**

01773 570008 inntact@aol.com

Most credit cards accepted

## Mail Order Suppliers of ELECTRONIC COMPONENTS & SURPLUS STOCK

### Mains Power Away From Home

YOU CAN POWER UP MAINS EQUIPMENT FROM A CAR, LORRY OR BOAT

Ideal for camping, caravanning, boats, motor caravans and of course cars.

Power up your laptop computers, TV's, lamps, recharge your mobile phone - dozens of uses!

PHONE 01277 811042

HOW TO ORDER

ST0110B1	12V, 100W	£65.00	ST0110B7	12V, 600W	£150.00
ST0110B3	24V, 500W	£65.00	ST0110B2	24V, 600W	£100.00
ST0110B2	12V, 300W	£55.00	ST0110B4	24V, 1000W	£175.00
ST0110B4	24V, 300W	£55.00	ST0110B5	24V, 1000W	£175.00

We stock thousands of products. Low cost electronic components, bargains and great value surplus stock!

- SOLID STATE KITS
- TOOLS • BATTERIES
- POWER SUPPLIES
- VALVE RADIO KITS
- HOBBY BOOKS • ETC.



All Prices include VAT  
Carriage £3.50 Per Order

Visit our website: [www.greenweld.co.uk](http://www.greenweld.co.uk)

**GREENWELD**

Greenweld Limited  
Unit 24 Pennine Business Park - West Horsham  
Bosham Road - Emsay - GU15 3XD  
Tel: 01277 811042 - Fax: 01277 812419  
Email: [service@greenweld.co.uk](mailto:service@greenweld.co.uk)

Office Hours: Mon - Fri 9.00 to 17.00 & Sat 9.00 to 12.00



NATIONAL  
COLLEGE OF  
TECHNOLOGY

## DISTANCE LEARNING SHORT COURSES with BTEC CERTIFICATION

Analogue and Digital Electronics, Fibre Optics, Fault Diagnosis, Mechanics, Mathematics and Programmable Logic Controllers

- Suitable for beginners and those wishing to update their knowledge and practical skills
- Courses are very practical and delivered as self contained kits
- No travelling or college attendance
- Learning is at your own pace
- Each course can stand alone or be part of a modular study programme
- Tutor supported and BTEC certified

For information contact  
NCT Ltd., P.O. Box 11  
Wendover, Bucks HP22 6XA  
Telephone 01296 624270: Fax 01296 625299  
Web: <http://www.nct.ltd.uk>

## FREE 304-page colour catalogue

Great value for Speakers, Microphones, Headphones, Aerials, Transmitters, TV Amps, Plugs, Sockets, Leads, CD Storage Cases, CCTV, Security, Connectors, Adaptors, Switch Boxes, Gadgets, Disc Lighting & Effects, Mixers, Amplifiers, Turntables, Musicians' Leads, Car Audio, Test Equipment, Hobby Kits, Computer Leads & Accessories, Power Supplies, Inverters, Transformers, Battery Chargers, Tools, Soldering, Switches, Fuses, Indicators, Cable & Wire, Crossovers, Speaker Hardware, PA Amps, and a great deal more... all for the price of a stamp.

### Sky Electronics

40-42 Cricklewood Broadway,  
London, NW2 3ET

Tel: 020 8450 0995

Fax: 020 8208 1441


Email: [sales@cricklewoodelectronics.com](mailto:sales@cricklewoodelectronics.com)

[www.skyelectronics.co.uk](http://www.skyelectronics.co.uk)

**ELECTRONICS 2002**

The Catalogue is FREE to shop callers or send stamps to the value of £1.85 to cover postage.

# CIRCUIT SURGERY

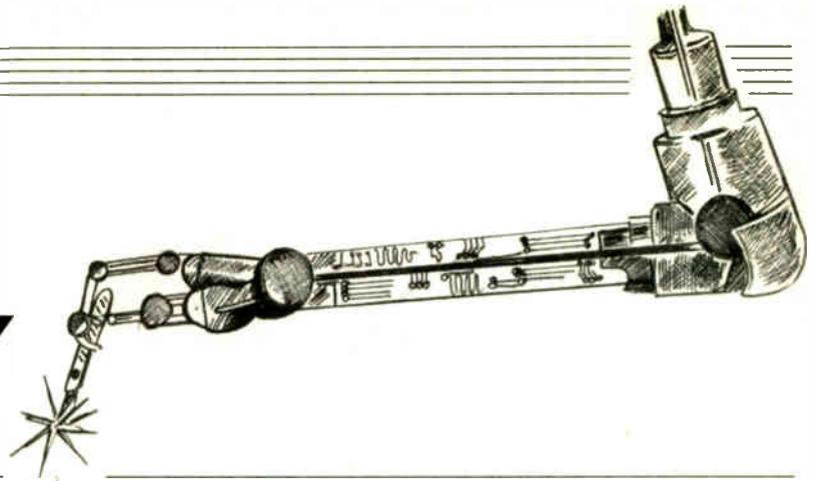

**ALAN WINSTANLEY  
and IAN BELL**

*Our monthly feature of readers' queries looks at analogue opto-couplers and a timely problem*

## Linear Opto-coupler

My thanks to *Dave Lerner* who writes by email;

*I found the March instalment of Teach-In 2002 with the practicalities of the instrumentation amplifier very informative and helpful. I wondered if you could give me a pointer of where to look for a linear opto-coupler. I have been experimenting with some of the biofeedback circuits dating back to Practical Electronics May 1987!*

*I would like to connect these to my oscilloscope or maybe some kind of recorder. This would leave the biofeedback circuit battery powered for reasons of safety and electrical noise. I have tracked down a number of data sheets but the applications all seem to be for coupling digital circuits. Are there specialist types available?*

We're pleased you're enjoying *Teach-In 2002 Making Sense of the Real World*, our multi-part series created to help constructors adapt and use many types of environmental sensors within their own projects. We hope that there is something in this *Teach-In 2002* series to suit everyone: as we said right at the beginning, "one often gets the impression that the world has gone completely digital in nature, with telephones, television, music, photography and radio all following this trend.

None of this allows us to escape the fact that the real world is actually *analogue* – a world in which many electronics applications must obtain information from their environment and condition it correctly, before it can be handed over for digital processing." Our series outlines many fundamental principles of operational amplifiers, instrumentation amplifiers, low noise techniques, including a lot of material not covered before in *EPE*.

## In Isolation

How to optically isolate an analogue signal is something I put to Dr David Chesmore, one of the *Teach-In 2002* co-writers and closely involved with the Biomedical Engineering Research Group at the University of York. Dave has produced most of the environmental monitoring material of our series, and he suggested that most opto-isolators can be operated linearly since they contain I.e.d.s and (usually) phototransistors.

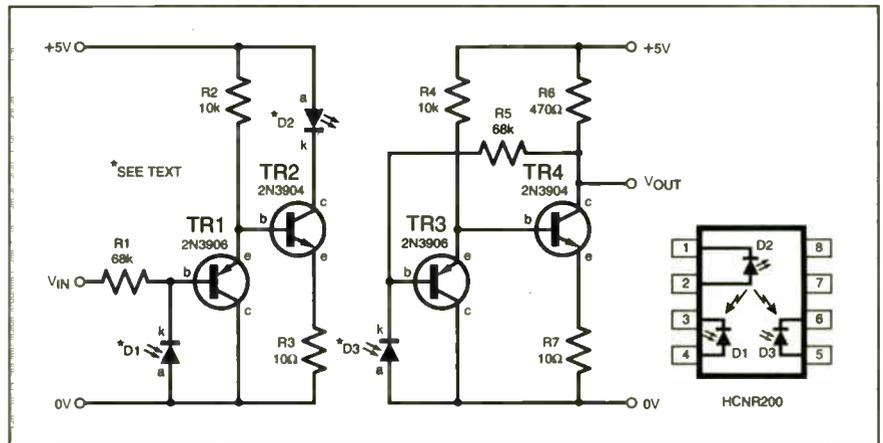


Fig.1. Circuit for a high speed, low-cost analogue opto-isolator using the HCNR200. (Courtesy Agilent.)

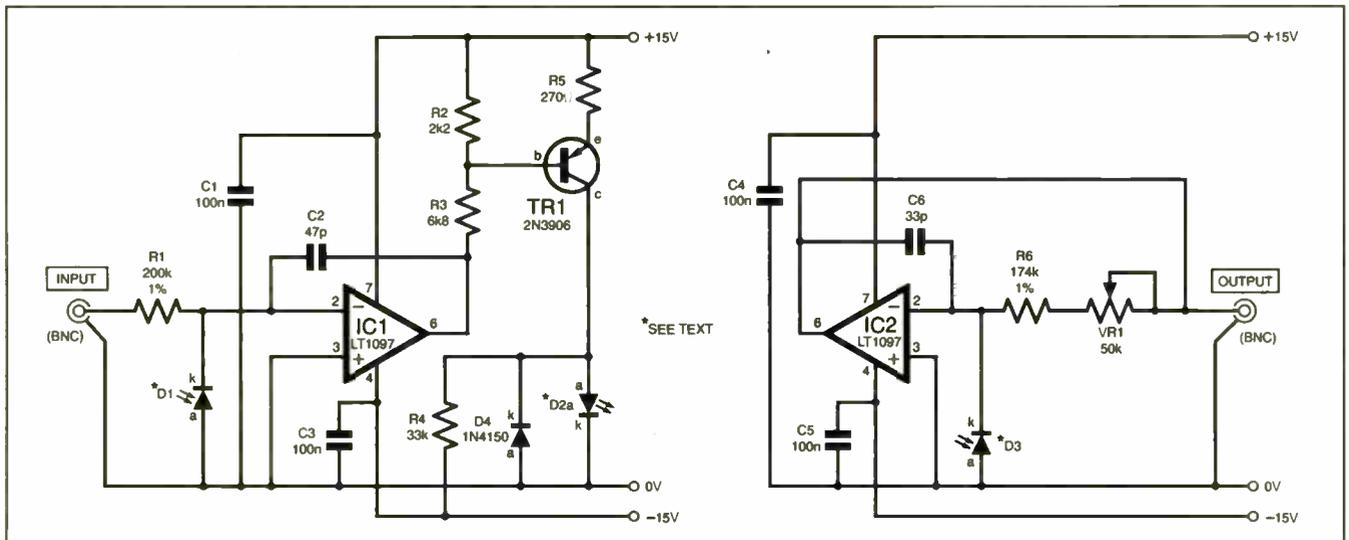


Fig.2. Circuit for a precision analogue isolation amplifier based on the HCNR200. (Courtesy Agilent.)

It would be worth putting a variable voltage onto such an l.e.d. and observing the output. The Toshiba 4N29, for example, has an l.e.d. and a photo-Darlington transistor which means the transistor output (with load resistor from emitter to ground and collector to positive supply) will produce an output proportional to the l.e.d.'s drive current.

Subsequently, Mr. Larner reverted with more details of an interesting device he had found after consulting Agilent (the optoelectronics offshoot of Hewlett Packard). The Agilent HCNR200 is a high linearity analogue opto-coupler containing a high efficiency l.e.d. that illuminates two closely matched photodiodes (see Fig.1). The "input side" photodiode (D1) can be used to stabilise the light output of the l.e.d. (D2), so that the non-linearity and drift of the l.e.d. can be eliminated.

The Agilent HCNR200 claims 0.25% non-linearity and the higher spec. HCNR201 0.05% maximum non-linearity. You can download the data sheet from [www.agilent.com](http://www.agilent.com). They are available from RS Components ([rswww.com](http://rswww.com)) e.g. the HCNR200 Part No. 801-465 is listed at £2.47, excluding VAT and P&P. Other linear opto-couplers are also available from RS including the IL300 which may be worth investigating.

A practical example of a low cost analogue isolator is shown in Fig.1, while Fig.2 shows a suggested precision analogue isolation amplifier. Low noise and shielding techniques using BNC and tri-axial connectors are also covered in *Teach-In 2002* and may be helpful in applications like these. The Agilent data sheet contains more practical circuits and detailed theory.

Thanks for letting us know! ARW.

## Dog and Cat Scarer

An interesting circuit recently appeared in our readers' circuits feature – *Ingenuity Unlimited*, March 2002 (p163). *The Dog and Cat Scarer* prompted a letter from reader Martin Stubbs who emails:

*A device such as the Dog and Cat Scarer would be extremely useful to us as we enjoy walking, particularly on holiday as last year we were harassed by dogs in Greece. I am intrigued to know how the two 555 timers used in the circuit work. I cannot determine how IC1 is set up as an oscillator or IC2 as a buffer amplifier. Perhaps Circuit Surgery could dedicate a few lines of explanation as to how it works.*

Referring back to the March *I/U*, first of all an unfortunate error crept into the circuit diagram: note that the connections to pin 2 and pin 3 of IC2 should be reversed. The circuit's operation then makes a whole lot more sense! We also stated that it should NOT be relied upon as a defence against aggressive dogs.

First, IC1 is configured as an oscillator using a method that is often overlooked by constructors. It utilises one feedback timing resistor between the output (pin 3) and the threshold (pin 6) and a capacitor to control the frequency.

If the CMOS 7555 version is used, then the fact that it switches from rail-to-rail means that you can obtain a 50 per cent duty cycle (the main advantage of this type of circuit). The result is a square wave appearing at pin 3.

Turning to the H-bridge arrangement, this uses four power transistors wired in complementary pairs. When IC1 output goes high, this turns on the npn transistor TR1, but the pnp transistor TR3 does not conduct. The output of IC1 also triggers the monostable IC2 – the trigger pin (2) needs to be taken low for the timer to trigger.

So, with IC1 output high, IC2 trigger input is pulled high, so IC2 output remains low. This allows the pnp transistor TR4 to conduct because its base is pulled low – so with the pair TR1 and TR4 conducting hard, current flows through the ultrasonic sound transducer LS1 as shown in Fig.3.

The designer mentioned a current flow of 4 amps when using a bench power supply which I can well believe; the *Power Siren* shown in *Circuit Surgery* June 1997 uses a ZSD100 siren chip and an H-bridge driver to produce an ear-splitting and highly efficient loudspeaker siren.

When IC1 output goes low then TR3 conducts instead of TR1, and IC2 is now triggered at pin 2. The monostable timer output goes high which supplies base current to TR2. Current therefore passes through TR2, LS1 and TR3 to 0V.

Thus, two opposing transistors are switched alternately in order to supply high currents through LS1. Exactly the same principle is often used to control the direction and speed of powerful d.c. motors, and special driver chips are available for this.

## Buffered Solution

You asked how IC2 works as a buffer amplifier. It is wired as a monostable (single shot timer) with a short period. Once triggered by IC1, the monostable will start timing and it will ignore any more trigger signals until it times out. However, if a trigger signal is present when the monostable tries to time out, then a 555 will carry on timing until the trigger is removed, when the output will go low at the same time.

A quick 555 breadboard experiment will demonstrate this – build the monostable of Fig.4, briefly trigger it and watch the l.e.d. time out automatically after a second or two. Then keep it triggered for several seconds – the output will go low as soon as the trigger is removed.

Taking a brief look at the timing of the circuit, in theory the on-time of IC2 is calculated approximately by  $1.1 R_2 C_4$  which is  $11\mu\text{s}$ . If IC1 is said to run at 40kHz then by using frequency =  $1/t$  the period (t) of its output is  $25\mu\text{s}$ . These figures do not allow for component or formula tolerances and are only for illustration.

Let's think about this a bit more. If we assume the astable has a 50% duty cycle then it is high for (say)  $12.5\mu\text{s}$  and low for  $12.5\mu\text{s}$ , see Fig.5. Each negative-going edge triggers the monostable for  $11\mu\text{s}$ , after which the monostable wants to time out but the trigger voltage is still there (with  $1.5\mu\text{s}$  still to go): so the monostable

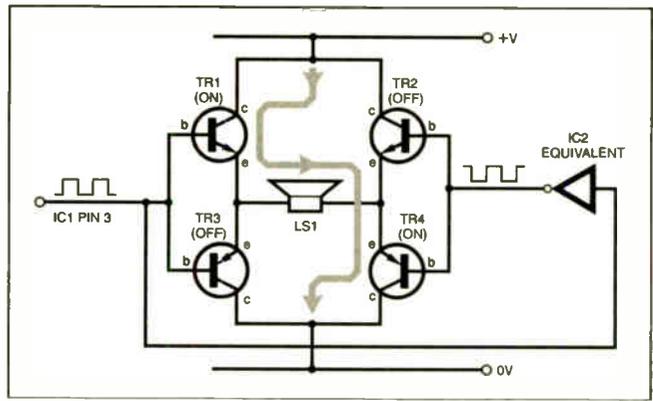


Fig.3. In an H-bridge driver, opposing pairs of complementary transistors drive the load as shown by the path (tint) taken by the current. (One phase of full circuit is shown.)

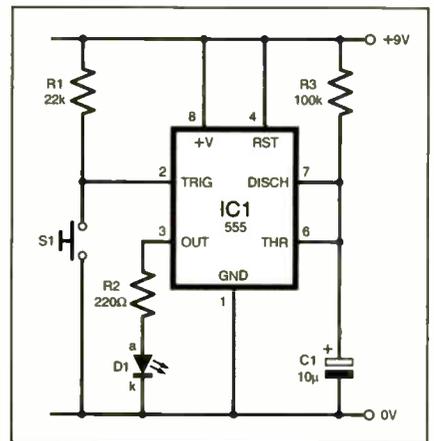


Fig.4. Circuit for testing the re-triggerability of a 555 monostable. Keep switch S1 closed for several seconds and observe the l.e.d. D1.

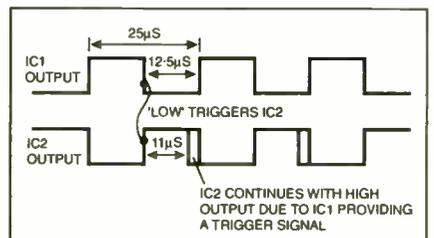


Fig.5. The monostable IC2 will continue to give a High output for as long as its trigger pin is held low by IC1. IC2 can therefore be used as an inverter.


carries on timing until the trigger is removed, when the monostable output will go low at the same time. After a further  $12.5\mu\text{s}$  the monostable is triggered once again. These timing values may not be quite the same in practice, but you get the general idea.

The overall result is that the monostable simply inverts the astable's square wave. It provides base current to both transistors TR2 and TR4, because the bipolar 555 is able to sink up to 200mA current into its input and source current out when it's high.

You could perhaps "force" the inverter operation more by ensuring the monostable period is even shorter still. Overall, it's quite a cunning design and I look forward to constructing one myself. My thanks to *Dave Stringwell* in Scunthorpe for submitting the design. ARW.

# ELECTRONICS CD-ROMS


## ELECTRONICS PROJECTS

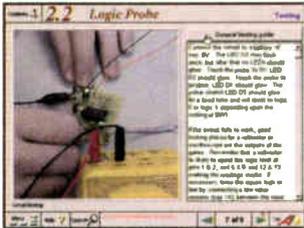

Logic Probe testing

*Electronic Projects* is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK **schematic capture, circuit simulation and p.c.b. design** software is included. The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.


## ELECTRONICS CAD PACK

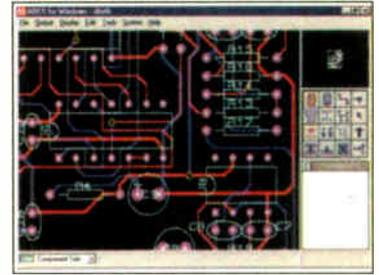

PCB Layout

Electronics CADPACK allows users to design complex circuit schematics, to view circuit animations using a unique SPICE-based simulation tool, and to design printed circuit boards. CADPACK is made up of three separate software modules. (These are restricted versions of the full Labcenter software.) **ISIS Lite** which provides full schematic drawing features including full control of drawing appearance, automatic wire routing, and over 6,000 parts. **PROSPICE Lite** (integrated into ISIS Lite) which uses unique animation to show the operation of any circuit with mouse-operated switches, pots, etc. The animation is compiled using a full mixed mode SPICE simulator. **ARES Lite** PCB layout software allows professional quality PCBs to be designed and includes advanced features such as 16-layer boards, SMT components, and an autorouter operating on user generated Net Lists.

## ANALOGUE ELECTRONICS

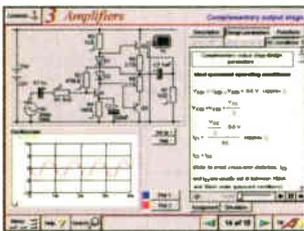


Complimentary output stage

*Analogue Electronics* is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits. Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections). **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections). **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections). **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

## DIGITAL ELECTRONICS V2.0


NEW VERSION 2

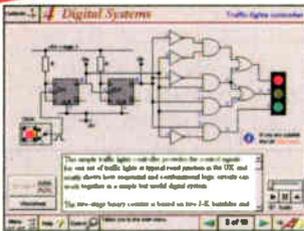

Virtual laboratory – Traffic Lights

*Digital Electronics* builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (opposite), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen. Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units. Sections on Boolean Logic and Venn diagrams, displays and chip types have been expanded in Version 2 and new sections include shift registers, digital fault finding, programmable logic controllers, and microcontrollers and microprocessors. The Institutional versions now also include several types of assessment for supervisors, including worksheets, multiple choice tests, fault finding exercises and examination questions.


## FILTERS

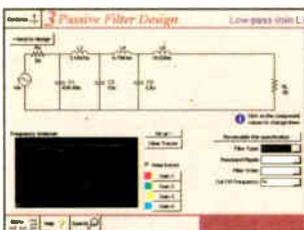

Filter synthesis

*Filters* is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev op.amp filters.

## DIGITAL WORKS 3.0

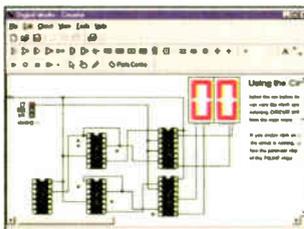

Counter project

*Digital Works Version 3.0* is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability. ● Software for simulating digital logic circuits. ● Create your own macros – highly scalable. ● Create your own circuits, components, and i.c.s. ● Easy-to-use digital interface. ● Animation brings circuits to life. ● Vast library of logic macros and 74 series i.c.s with data sheets. ● Powerful tool for designing and learning.

## “C” FOR PICMICRO MICROCONTROLLERS



**C for PICmicro Microcontrollers** is designed for students and professionals who need to learn how to use C to program embedded microcontrollers. This product contains a complete course in C that makes use of a virtual C PICmicro which allows students to see code execution step-by-step. Tutorials, exercises and practical projects are included to allow students to test their C programming capabilities. Also includes a complete Integrated Development Environment, a full C compiler, Arizona Microchip's MPLAB assembler, and software that will program a PIC16F84 via the parallel printer port on your PC. (Can be used with the *PICtutor* hardware – see opposite.) Although the course focuses on the use of the PICmicro series of microcontrollers, this product will provide a relevant background in C programming for any microcontroller.


## PRICES

Prices for each of the CD-ROMs above are:

Hobbyist/Student .....	£45 inc VAT
Institutional (Schools/HE/FE/Industry).....	£99 plus VAT
Institutional 10 user (Network Licence) .....	£199 plus VAT
Site Licence.....	£499 plus VAT

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)
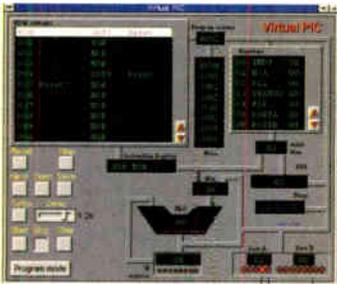
## Interested in programming PIC microcontrollers? Learn with **PICtutor**




The Virtual PIC

This highly acclaimed CD-ROM by John Becker, together with the PICtutor experimental and development board, will teach you how to use PIC microcontrollers with special emphasis on the PIC16x84 devices. The board will also act as a development test bed and programmer for future projects as your programming skills develop. This interactive presentation uses the specially developed **Virtual PIC Simulator** to show exactly what is happening as you run, or step through, a program. In this way the CD provides the easiest and best ever introduction to the subject. Nearly 40 Tutorials cover virtually every aspect of PIC programming in an easy to follow logical sequence.
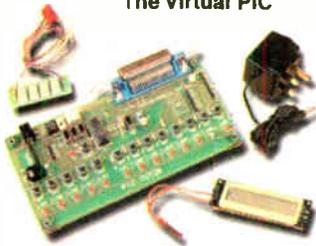
### HARDWARE

Whilst the CD-ROM can be used on its own, the physical demonstration provided by the **PICtutor Development Kit**, plus the ability to program and test your own PIC16x84s, really reinforces the lessons learned. The hardware will also be an invaluable development and programming tool for future work.

Two levels of PICtutor hardware are available – Standard and Deluxe. The Standard unit comes with a battery holder, a reduced number of switches and no displays. This version will allow users to complete 25 of the 39 Tutorials. The **Deluxe Development Kit** is supplied with a plug-top power supply (the **Export Version** has a battery holder), all switches for both PIC ports plus I.C.D. and 4-digit 7-segment I.E.D. displays. It allows users to program and control all functions and both ports of the PIC. All hardware is supplied **fully built and tested** and includes a PIC16F84.



Deluxe PICtutor Hardware

### PICtutor CD-ROM

Hobbyist/Student .....£45 inc. VAT  
 Institutional (Schools/HE/FE Industry) ...£99 plus VAT  
 Institutional 10 user (Network Licence) .£199 plus VAT

### HARDWARE

Standard Development Kit ....£47 inc. VAT  
 Deluxe Development Kit .....£99 plus VAT  
 Deluxe Export Version .....£96 plus VAT

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

## ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 JPG images of electronic components.

This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details).

Also contains a **FREE** 30-day evaluation of Paint Shop Pro 6 – Paint Shop Pro image editing tips and on-line help included!

Price **£19.95 inc. VAT**



**VERSION 2**

## ELECTRONIC CIRCUITS & COMPONENTS V2.0

Provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals:** units & multiples, electricity, electric circuits, alternating circuits. **Passive Components:** resistors, capacitors, inductors, transformers. **Semiconductors:** diodes, transistors, op.amps, logic gates. **Active Circuits. The Parts Gallery** will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Selections include: **Components, Components Quiz, Symbols, Symbols Quiz, Circuit Technology.**

Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.

Hobbyist/Student .....£45 inc. VAT  
 Institutional (Schools/HE/FE/Industry) .....£99 plus VAT  
 Institutional 10 user (Network Licence) .....£199 plus VAT  
 Institutional Site Licence .....£499 plus VAT

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

## ELECTRONICS IN CONTROL

Two colourful animated courses for students on one CD-ROM. These cover Key Stage 3 and GCSE syllabuses. **Key Stage 3:** A pictorial look at the Electronics section featuring animations and video clips. Provides an ideal introduction or revision guide, including multi-choice questions with feedback. **GCSE:** Aimed at the Electronics in many Design & Technology courses, it covers many sections of GCSE Electronics. Provides an ideal revision guide with Homework Questions on each chapter. Worked answers with an access code are provided on a special website.

Single User **£29 inc. VAT. Multiple User £39 plus VAT**  
 Student copies (available only with a multiple user copy) **£6 plus VAT**  
 (UK and EU customers add VAT at 17.5% to "plus VAT" prices)

## MODULAR CIRCUIT DESIGN

Contains a range of tried and tested analogue and digital circuit modules, together with the knowledge to use and interface them. Thus allowing anyone with a basic understanding of circuit symbols to design and build their own projects. Version 3 includes data and circuit modules for a range of popular PICs; includes PICAXE circuits, the system which enables a PIC to be programmed without a programmer, and without removing it from the circuit. Shows where to obtain free software downloads to enable BASIC programming. Essential information for anyone undertaking GCSE or "A" level electronics or technology and for hobbyists who want to get to grips with project design. Over seventy different Input, Processor and Output modules are illustrated and fully described, together with detailed information on construction, fault finding and components, including circuit symbols, pinouts, power supplies, decoupling etc.

Single User **£19.95 inc. VAT. Multiple User £34 plus VAT**  
 (UK and EU customers add VAT at 17.5% to "plus VAT" prices)

**VERSION 3**

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 95/98/NT/2000/ME/XP, mouse, sound card, web browser.

## CD-ROM ORDER FORM

Please send me:

- Electronic Projects
- Analogue Electronics
- Digital Electronics V2.0
- Filters
- Digital Works 3.0
- Electronics CAD Pack
- C For PICmicro Microcontrollers
- PICtutor
- Electronic Circuits & Components V2.0

Version required:

- Hobbyist/Student
- Institutional
- Institutional 10 user
- Institutional site licence

Note: The software on each version is the same (unless stated otherwise), only the licence for use varies.



- PICtutor Development Kit – Standard
- PICtutor Development Kit – Deluxe

Deluxe Export

Note: The CD-ROM is not included in the Development Kit prices.

- Electronic Components Photos
- Electronics In Control – Single User
- Electronics In Control – Multiple User
- Modular Circuit Design – Single User
- Modular Circuit Design – Multiple User

Note: The software on each version is the same, only the licence for use varies.

Full name: .....

Address: .....

Post code: ..... Tel. No: .....

Signature: .....

I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £ .....

Please charge my Visa/Mastercard/Amex/Diners Club/Switch: £ ..... Card expiry date: .....

Card No: ..... Switch Issue No. ....

## ORDERING

ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world  
 EU residents outside the UK add £5 for airmail postage per order

Institutional, Multiple User and Deluxe Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU (European Union) country, then add 17½% VAT or provide your official VAT registration number).

Send your order to:

Direct Book Service  
 Wimborne Publishing Ltd  
 408 Wimborne Road East  
 Ferndown, Dorset BH22 9ND

To order by phone ring

01202 873872. Fax: 01202 874562

Goods are normally sent within seven days

E-mail: orders@wimborne.co.uk


Online shop:

www.epemag.wimborne.co.uk/shopdoor.htm
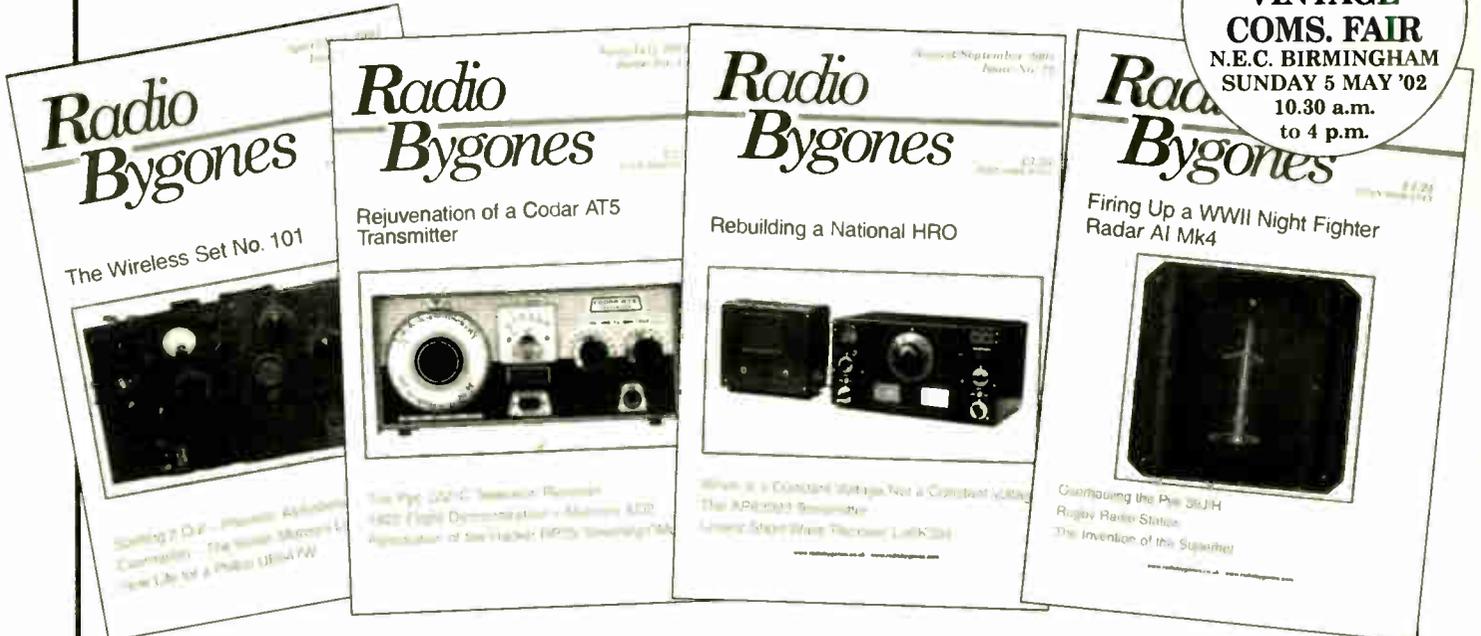
# Radio Bygones

The leading magazine  
for vintage radio  
enthusiasts

MEET US  
AT THE  
**NATIONAL  
VINTAGE  
COMS. FAIR**  
N.E.C. BIRMINGHAM  
SUNDAY 5 MAY '02  
10.30 a.m.  
to 4 p.m.



WHETHER your interest is in domestic radio and TV or in amateur radio, in military, aeronautical or marine communications, in radar and radio navigation, in instruments, in broadcasting, in audio and recording, or in professional radio systems fixed or mobile, RADIO BYGONES is the magazine for you.

ARTICLES on restoration and repair, history, circuit techniques, personalities, reminiscences and just plain nostalgia – you'll find them all. Plus features on museums and private collections and a full-colour photo-feature in every issue.

IT'S MOSTLY about valves, of course, but 'solid-state' – whether of the coherer and spark-gap variety or early transistors – also has a place.

FROM THE DAYS of Maxwell, Hertz, Lodge and Marconi to what was the state-of-the-art just a few short years ago . . .

There is also a selection of free readers' For Sale and Wanted advertisements in every issue.

## Radio Bygones covers it all!

THE MAGAZINE is published six times a year, and is available by postal subscription. It is not available at newsagents.

TO TAKE OUT a subscription, or to request a sample copy, please complete the form below and return it to:  
**RADIO BYGONES, Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.**

Tel: 01202 873872. Fax 01202 874562. Web sites: [www.radiobygones.co.uk](http://www.radiobygones.co.uk) [www.radiobygones.com](http://www.radiobygones.com)

### RADIO BYGONES ORDER FORM

A SAMPLE COPY of Radio Bygones . . . . . £3.25  
(Add 70p for overseas Airmail postage)

SUBSCRIPTIONS (post paid):      1 YEAR    2 YEAR  
UNITED KINGDOM                      £18.50    £35.00  
REST OF EUROPE (AIRMAIL)        £20.50    £39.00  
REST OF THE WORLD (AIRMAIL)    £24.50    £47.00

- Yes, I would like a sample copy of RADIO BYGONES  
 Yes, I would like to take out a subscription for:  
 One year (6 issues)     Two years (12 issues)  
 I enclose a cheque/Eurocheque/PO for £ . . . . . payable to Wimborne Publishing Ltd  
 Please debit my card

My card number is:

.....  
Please print clearly, and check that you have the number correct

Expiry date . . . . . Switch Issue No. . . . .

My name is . . . . .

My address . . . . .

Post Code/Zip . . . . . Tel: . . . . .

Signed . . . . .

*If you do not wish to cut your magazine, send a letter or a copy of this form*

# SHOP TALK

with David Barrington

## PIC Big Digit Display

It is important that constructors keep to the specified semiconductor devices when putting together parts of the *PIC Big Digit Display* project. The L293DN 16-pin Half-H driver chip (also known as a stepper motor driver i.c.) was purchased from **Rapid Electronics** (☎ 01206 751166 or [www.rapidelectronics.co.uk](http://www.rapidelectronics.co.uk)), code 82-0192. The "D" denotes it is a 16-pin device and has diode protection. Do not use other L293 device types as they may not have the same characteristics – for instance, the L293E has 20 pins and cannot be used. (Check out the Texas web site at: [www.ti.com](http://www.ti.com)).

Bulk purchasing has enabled **Display Electronics** (☎ 0208 653 3333 or [www.distel.co.uk](http://www.distel.co.uk)) to offer the "British Rail" giant 10 inch 7-segment electromechanical display at a very reasonable price; claimed to be less than 30 per cent of the original. A single display module (code RW44) cost just £29.95 plus VAT and £99 plus VAT for four units (code PH26). A carriage charge will need to be added to these prices – see their advertisement in this issue for details.

The 7-stage Darlington line driver type ULN2004A was also purchased from **Rapid** (see above), code 82-0622. It is also listed by **RS** (☎ 01536 444079 or [rswww.com](http://rswww.com)), code 652-825.

For those readers unable to program their own PICs, a ready-programmed PIC16F84 microcontroller can be purchased from **Magenta Electronics** (☎ 01283 565435 or [www.magenta2000.co.uk](http://www.magenta2000.co.uk)) for the inclusive price of £5.90 each (overseas add £1 p&p). The software is available on a 3.5in. PC-compatible disk (EPE Disk 5) from the *EPE* Editorial Office for the sum of £3 each (UK), to cover admin costs (for overseas charges see page 379). It is also available Free from the *EPE* web site: [ftp://ftp.epemag.wimborne.co.uk/pub/PICS/PICbigdigit](http://ftp.epemag.wimborne.co.uk/pub/PICS/PICbigdigit).

The printed circuit board is available from the *EPE PCB Service*, code 341 (see page 379). Finally, the optional 4x4 matrix data entry keypad came from **RS** (see earlier), code 331-304.

## Washing Ready Indicator

Some readers may experience difficulty in tracking down the specified quad op.amp used in the *Washing Ready Indicator* project. We have found that the Harris Semiconductors CMOS ICL7642ECPD quad op.amp is stocked by **RS** (code 630-623) and can be ordered through any *bona fide* stockists, including some of our advertisers. You can order direct (credit card only) from **RS** on 01536 444079 or through the web at [rswww.com](http://rswww.com). A post and handling charge will be made.

The sub-miniature, omni-directional electret microphone insert used in the model was obtained from **Maplin** (☎ 01283 565435 or [www.maplin.co.uk](http://www.maplin.co.uk)), code FS43W. You could possibly use their ultra-miniature version, code QY62S. This has not been tried in the unit.

The same company also supplied the 3V to 24V d.c. 10mA max. piezoelectric buzzer, code KU56L. Most of our components advertisers should be in a position to offer an identical buzzer.

The small printed circuit board is available from the *EPE PCB Service*, code 342 (see page 379).

## Teach-In 2002 – Lab 7

Like most of the *Lab Works* in the *Teach-In 2002* series, it's the sensor elements that are usually "specials" and cause most purchasing problems. However, this is not the case with the first simple comparator demonstration circuits, Lab 7.1, where the light-dependent resistor (l.d.r.) type ORP12 is needed. This is widely stocked and advertisers such as **ESR**, **Bardwell**, **Bowood**, **Cricklewood** and **Sherwood Electronics** should be able to supply.

For the Anemometer (Wind Speed/Force) – Lab 7.2 and the Wind Direction Indicator – Lab 7.3, the miniature reflective opto-switch type SG2BC was ordered from **Farnell** (☎ 0113 263 6311 or [www.farnell.com](http://www.farnell.com)) code 491-366. They also supplied the TLC7524 8-bit DAC chip, code 397-246.

It may be well worth investigating the possibility of using the "wind cup" hardware stocked by **Magenta Electronics** (☎ 01283 565435 or [www.magenta2000.co.uk](http://www.magenta2000.co.uk)).

## Freezer Alarm

The circuit for the *Freezer Alarm* project uses the "baby" of the PIC family, the "one-time-programmable" PIC12C508 microcontroller. The rest of the components should be readily available.

For those readers unable to program this type of PIC, a ready-programmed PIC12C508 microcontroller can be purchased from **Magenta Electronics** (☎ 01283 565435 or [www.magenta2000.co.uk](http://www.magenta2000.co.uk)) for the inclusive price of £5.90 each (overseas add £1 p&p). The software is available on a 3.5in. disk (EPE Disk 5) from the *EPE* Editorial Office for the sum of £3 each (UK), to cover admin costs (for overseas charges see page 379). It is also available Free from the *EPE* web site: [ftp://ftp.epemag.wimborne.co.uk/pub/PICS/PICfreezer](http://ftp.epemag.wimborne.co.uk/pub/PICS/PICfreezer).

## Simple Audio Circuits – 1

We do not expect any component buying problems to be encountered when shopping for parts for the various amplifier modules called-up in this month's *Simple Audio Circuits* projects. All the audio amp i.c.s should be "shelf" items.

All the small printed circuit boards are available from the *EPE PCB Service*. See page 379 for individual ordering codes and prices.

MAKE IT A GIFT EVERY MONTH – AND SAVE UP TO 68p AN ISSUE

NEXT MONTH – DON'T MISS OUT  
 ★ BIOPIC HEARTBEAT MONITOR ★  
 ★ WORLD LAMP ★  
 ★ SIMPLE AUDIO CIRCUITS-2 ★

### Annual subscription rates:

- 6 Months: UK £15, Overseas £18 (standard air service), £27 (express airmail)
- 1 Year: UK £28.50, Overseas £34.50 (standard air service) £52 (express airmail)
- 2 Years: UK £52.00, Overseas £64.00 (standard air service) £99 (express airmail)

To: Everyday Practical Electronics,  
 Wimborne Publishing Ltd., 408 Wimborne Road East,  
 Ferndown, Dorset BH22 9ND

Tel: 01202 873872 Fax: 01202 874562

E-mail: [subs@epemag.wimborne.co.uk](mailto:subs@epemag.wimborne.co.uk)

Order from our online shop at:  
[www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

Name .....

Address .....

Post code ..... Tel. ....

MAKE SURE OF YOUR COPY NOW!



### SUBSCRIPTION ORDER FORM



I enclose payment of £ .....  
 (cheque/PO in £ sterling only),



payable to Everyday Practical Electronics



My card number is: .....

Please print clearly, and check that you have the number correct

Signature .....

Card Ex. Date ..... Switch Issue No. ....

Subscriptions can only start with the next available issue.  
 For back numbers see the Back Issues page.


If you do not wish to cut your issue, send a letter or a copy of this form.

05/02

# TEACH-IN 2002

Part Seven – More on Noise, plus Comparators and Digital Optical Sensing

IAN BELL AND DAVE CHESMORE

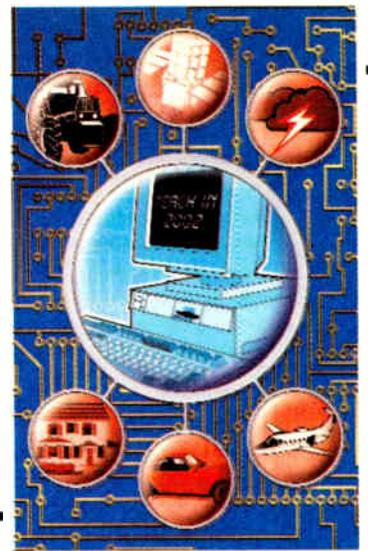

## Making Sense of the Real World: Electronics to Measure the Environment

**I**N many applications we use sensors to measure the quantity that they are sensitive to – temperature, humidity, strain etc. We may simply be interested in monitoring or recording this value (e.g. the temperature of a room) or we may be using it in a more complex way – for example, to control the environment of an enclosure.

This may require sophisticated manipulation of the sensor data using a microcontroller or PC. In other cases we do not need to know the value measured by the sensor, but simply have to switch an output when the level crosses a preset threshold (e.g. to switch on lights at night).

### COMPARABLE

Such applications often require comparators which will form one of the topics of our discussion this month. The sensor/comparator combination provides a digital signal which has uses beyond that of the simple level-switching just mentioned, and provides a means of measuring quantities other than those directly detected by the sensor.

The most common use of this approach is in motion sensing – e.g. position, direction and speed and the sensors most commonly used are optical sensors (hence the phrase *Digital Optical Sensing* in this part's sub-title). Although magnetic sensors are also used in this way, digital optical sensing is our main sensor topic this month and we will be building wind speed and direction instruments.

You may be thinking that digital sensing and use of comparators rather than accurate amplification and measurement of a sensor signal means that we can relax and forget about the nasty problems of noise and errors that we have discussed in the last few parts. Unfortunately this is not the case.

### NOISE RETURNS

As we will see later, noise may cause a comparator to switch multiple times as a threshold is crossed. Furthermore, offsets and other errors may shift the threshold level.

Last month we introduced the fact that there is noise that originates from within the components themselves. We now move

on to see that there is a variety of types of noise generated within electronic sensors and associated circuitry, these are **thermal noise**, **shot noise**, **flicker noise**, **burst noise** and **avalanche noise**.

We will have a quick look at each of them in turn.

### THERMAL NOISE

Thermal noise (also known as **Johnson noise**) is a fundamental property of resistors (including the internal resistances of sensors and semiconductor devices), which results in a **white-noise** voltage across its in-circuit terminals.

This is a fundamental property of any resistor and therefore sets the lower limit of the noise from any sensor – whatever we do, we cannot get lower noise than the thermal noise.

Thermal noise cannot be reduced by improved component manufacture. However, as it is temperature-dependent, reducing the temperature will reduce the noise. Cooling sensors to very low temperatures may be appropriate for some situations, such as physics experiments, but in most cases it would be too difficult and expensive to be justifiable.

The thermal noise r.m.s. voltage across a resistor is given by:

$$V_{N,rms} = \sqrt{4kTR\Delta f}$$

Where:

$k$  is a physical constant known as **Boltzmann's Constant** ( $1.38 \times 10^{-23} \text{JK}^{-1}$ ) (Joules per Kelvin)

$T$  is the temperature in Kelvin (K)

$R$  is the resistance in ohms ( $\Omega$ )

$\Delta f$  is the bandwidth of interest in Hertz (Hz), i.e. the range of frequencies over which you are measuring the noise.

$\Delta f$  is pronounced "delta f", the delta symbol means "change in" and so  $\Delta f$  represents a range of frequencies.

The fact that a bandwidth has to be specified in order to get a noise voltage means that noise figures are often expressed in "volts per bandwidth unit" form, rather than simply as voltages (have a look on data sheets for i.c.s. such as op.amps and you will see noise figures expressed this way). This value is known as **noise density**.

If we divide both sides of the first equation by the square root of the bandwidth ( $\sqrt{\Delta f}$ ) we get:

$$\frac{V_{N,rms}}{\sqrt{\Delta f}} = \sqrt{4kTR}$$

The value  $\sqrt{4kTR}$  has units "volts per root Hertz", often written as  $\text{V}/\text{Hz}^{1/2}$  or  $\text{V}/\sqrt{\text{Hz}}$ . So, for example, the noise from a  $100\text{k}\Omega$  resistor at  $20^\circ\text{C}$  (293K) is:

$$\sqrt{4 \times 1.38 \times 10^{-23} \times 293 \times 100 \times 10^3} = 40\text{nV}/\text{Hz}^{1/2}$$

If we were interested in a bandwidth of say 20kHz, the thermal noise voltage from this resistor would be  $40\text{nV} \times \sqrt{20 \times 10^3} = 5.7\mu\text{V}$ . Statistical analysis of the properties of thermal noise shows that the instantaneous peak noise voltage will be less than five times the r.m.s. (average) value for 99 per cent of the time.

The equation for thermal noise indicates that we can reduce noise voltage by reducing resistance (source or internal resistance in the case of a sensor) or by reducing bandwidth. Reducing source resistance may not be possible, as it will often be fixed for a particular sensor. However, effective reduction in bandwidth can be achieved by making many measurements and averaging, or measurement over a longer period of time.

Why does making multiple measurements reduce effective  $\Delta f$ ? If we make a measurement over a certain period of time those random variations which occur many times during this period will be averaged out. However, variations much longer than our period of making measurements will not "be seen" by our measurement process. Thus we have effectively removed some of the noise in the high frequency end of  $\Delta f$ , reducing its range and hence reducing the noise.

This approach is useful, but of course we pay for it by reduction in the speed with which we make our measurement. We also cannot extend our measurement period for longer than the time for which the quantity being measured will have a "constant" value, and as we increase measurement time other errors such as drift become more significant.

## SHOT NOISE

When current flows through a resistance it will generate additional white noise above the thermal noise due to the quantum nature of electric current at the atomic level. Electric current is the flow of discrete charge carriers (e.g. electrons), rather than a "continuous" flow. This noise is known as **shot noise** and like thermal noise is due to fundamental physics and cannot be reduced. For an applied current of  $I$  in amps (A) the shot noise is given by:

$$I_{N,rms} = \sqrt{2eI\Delta f}$$

where  $e$  is the electronic charge (charge on one electron =  $1.6 \times 10^{-19}$ C (Coulombs)) and  $\Delta f$  is the bandwidth as before. For a current of  $1\mu\text{A}$  this is  $0.57\text{pA}/\text{Hz}^{1/2}$ , which is about  $80\text{pA}$  over a  $20\text{kHz}$  bandwidth.  $80\text{pA}$  noise on  $1\mu\text{A}$  is a variation of  $0.008\%$ , which is an SNR (signal-to-noise-ratio) of around  $82\text{dB}$ .

For very low currents the effect of shot noise becomes increasingly significant, limiting the accuracy of low-level measurements. Shot noise is an important source of noise in semiconductor devices such as diodes and transistors.

## YET MORE NOISE

In addition to thermal noise and shot noise, resistors and active devices produce yet more noise for various and often complex reasons. This noise is called **flicker noise**, also known as **1/f noise** or **pink noise**, as it typically has a  $1/f$  relationship with frequency ( $f$ ) (as defined last month).

Unlike thermal and shot noise, flicker noise in resistors (and other devices) depends on the component type and manufacture, and can even vary quite widely for components of same type. For a decade bandwidth (frequency range of 1 to 10 times) the flicker noise for typical resistors varies from tens of nanovolts to a few microvolts, depending on type and quality.

Carbon composition resistors produce the highest flicker noise and wirewound resistors the lowest. As flicker noise is more prominent at lower frequencies, unlike white noise, its effect is not reduced by longer sampling times.

**Burst noise** (also known as **popcorn noise**) occurs in transistors and results in pulses often in the audio frequency range,

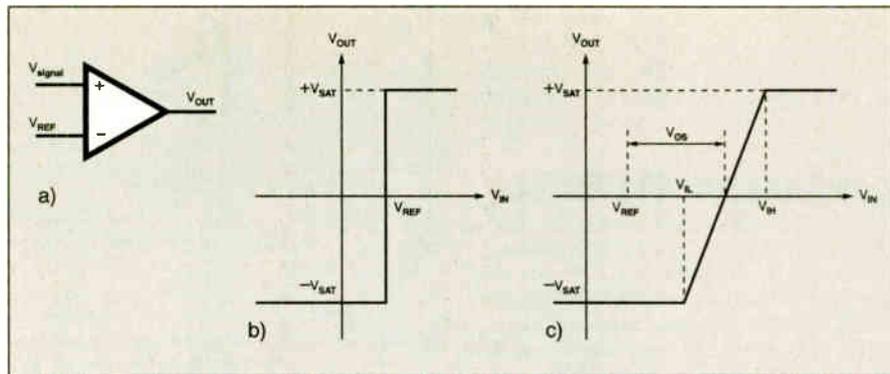


Fig.7.1. Comparator input-output characteristics, (a) schematic, (b) ideal response, (c) realistic response.

which can lead to a popping sound (hence the name *popcorn noise*).

**Avalanche noise** is produced by Zener diodes (or other diode junctions undergoing Zener or avalanche reverse breakdown). Avalanche noise is much larger than shot noise and so Zener diodes can introduce a lot of noise into a circuit. For this reason they should be avoided in low noise circuits even though they are a temptingly easy way to produce a stable voltage reference.

## COMPARATORS

Earlier in the series we discussed how an op.amp that is used without negative feedback has very high gain. Thus, for all but a small range of input voltage differences, the output will be saturated (see Fig.7.1). These two voltages (e.g.  $-V_{sat}$  and  $+V_{sat}$ ) may represent logic 0 and 1 and will indicate which of the two inputs is at the higher voltage. An op.amp used in this way is known as a **comparator**.

One input of the comparator is usually connected to a fixed reference level ( $V_{REF}$  in Fig.7.1, sometimes called the **threshold**) and the other input is connected to the signal of interest (e.g. from a sensor). A real op.amp may not switch when the input is at exactly  $V_{REF}$  due to offsets. Furthermore, for a range of input voltages, the op.amp will be in normal "linear" mode and will output intermediate voltages (see Fig.7.1c). This range of inputs is very small, however, and the situation is much better using an op.amp than, say, a single transistor, as we will see in this month's *Lab Work*.

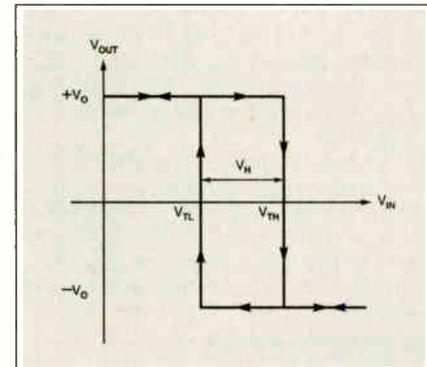


Fig.7.2. Response of an inverting regenerative comparator.

The simplest use of a comparator with a sensor is to switch a load on or off when the sensor output goes above or below a particular level. For example, to produce an over- or under-temperature alarm. A **window comparator** uses two comparators to indicate when a signal is between two levels. These circuits are often used to determine if a measured value is between acceptable limits.

An ideal comparator would switch instantaneously when the *input* signals cross the comparison threshold. A real comparator takes a finite time before it reacts. This time is known as the **propagation delay**.

An ideal comparator's *output* voltage switches between its two possible output states instantaneously. Again, a real comparator takes a finite time. The rate of

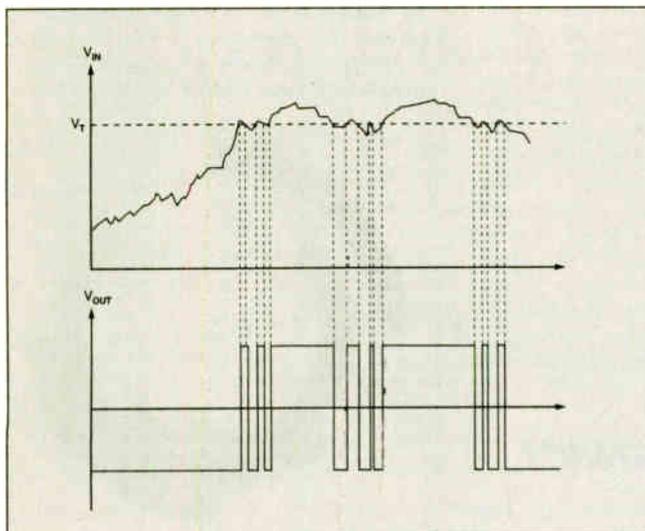


Fig.7.3. Comparator without hysteresis.

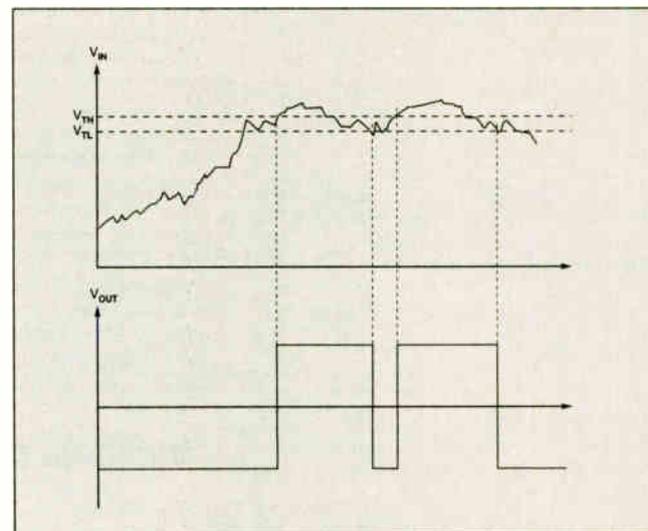


Fig.7.4. Comparator with hysteresis.

change of the comparator's output voltage as it switches is known as its **slew rate**.

Any op.amp may be used as a comparator, but the best performance is obtained by using devices that have been *specifically designed* as comparators.

### COMPARATOR HYSTERESIS

A comparator with a single threshold value may switch states many times as a noisy, slowly changing input crosses the threshold. This is often undesirable, for example, if the number of threshold-crossings is to be counted. The problem may be overcome by using two thresholds, e.g.  $V_{TH}$  and  $V_{TL}$ .

The difference between  $V_{TH}$  and  $V_{TL}$  is called the **hysteresis**. When the input increases past  $V_{TH}$  the comparator switches, but it does not switch if the input *decreases* past  $V_{TH}$ . The input must decrease past a lower threshold,  $V_{TL}$ , before the comparator switches again. This is illustrated in Fig.7.2.

If the input noise level is known, the hysteresis can be set slightly larger than this. The comparator will then not switch as a result of the noise. Fig.7.3 and Fig.7.4 show the result of applying the same noisy signal to a simple comparator and one with hysteresis.

### REGENERATIVE COMPARATORS

Comparators with hysteresis are also known as **regenerative comparators** and **Schmitt triggers**. A comparator with hysteresis can be made using a single-threshold comparator by setting the threshold depending on the comparator's present output state. The comparator has two output states so these can be used to set the two thresholds as required, by using **positive feedback** (hence the name *regenerative*).

A regenerative comparator can be made using an op.amp as shown in Fig.7.5. The switching point,  $V_{comp}$  depends on  $V_{REF}$  and  $V_{out}$ .  $V_{REF}$  will usually be fixed, but  $V_{out}$  depends on the current state of the comparator. One of two values can be taken by  $V_{out}$ , that is,  $\pm V_O$  (basically the op.amp positive and negative saturation voltages, which for simplicity we will assume to have the same magnitude).

To follow the operation of the circuit start by assuming that  $V_{in}$  is less than  $v_{comp}$  so  $V_{out} = +V_O$ . As  $V_{in}$  is slowly increased, this condition remains until  $V_{in} = V_{comp} = V_{TH}$  (upper threshold), where:

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{ref} + \frac{R_1}{R_1 + R_2} V_o$$

On switching at  $V_{comp} = V_{TH}$  the output changes to  $V_{out} = -V_O$ . Changing the threshold to a new value,  $V_{comp} = V_{TL}$  (lower threshold), where:

$$V_{TL} = \frac{R_2}{R_1 + R_2} V_{ref} - \frac{R_1}{R_1 + R_2} V_o$$

$V_{out}$  will now stay at  $-V_O$  until the input falls below the new  $V_{comp}$  value. The difference in the switching points, i.e. the hysteresis,  $V_H$ , is:

$$V_H = V_{TH} - V_{TL} = \frac{2R_1}{R_1 + R_2} V_o$$

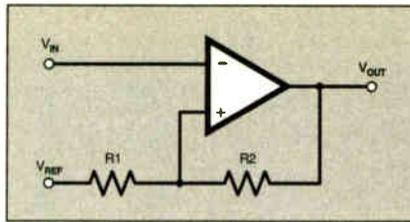


Fig.7.5. Inverting regenerative comparator circuit.

An inverting version of the circuit is shown in Fig.7.5. A non-inverting version can also be made. The equations are slightly different, but the basic operation of the circuit is the same.

### OPTICAL MOTION SENSING

Consider a rotating disc marked with black and white sections above which an optical sensor has been placed (see Fig.7.6). Assume that light is shining onto the disc so that when the sensor is above a white area we get a relatively large signal compared to when it is above a black area.

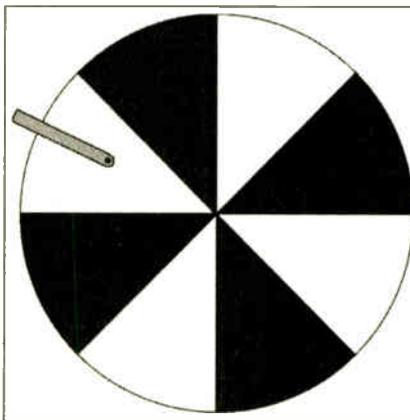


Fig.7.6. Optical sensing of motion. The grey bar represents the fixed sensor mounting and the black dot indicates the location of the sensor. The disc is free to rotate past the sensor.

Assume that this signal is passed through a suitable comparator circuit so that a clean digital output signal is obtained, with 0 representing a black area and 1 a white area. As the disc rotates we will get an alternating 1 and 0, the frequency of this pulsed signal indicating the speed of rotation.

We are not restricted to rotary motion with this technique - we can pattern a linear bar and measure movement in a similar way. We can also use holes in the disc, or bar, or other object rather than black and white areas to switch the level of light falling on the sensor as movement occurs.

More sophisticated measurement of the disc's movement can be achieved by using more complex patterns on the disk and multiple sensors. If we use several sensors and arrange the black and white areas appropriately, we can provide a binary coded output that indicates the location (angle of rotation) of the disc. Fig.7.7 provides an example of this using a 3-bit number, giving us an angular resolution of 45 degrees.

### AVOIDING UNCERTAINTY

This seems fine, but actually it is not a sensible way of patterning the disc. The problem is that, unless the sensors are perfectly aligned, as we move from one

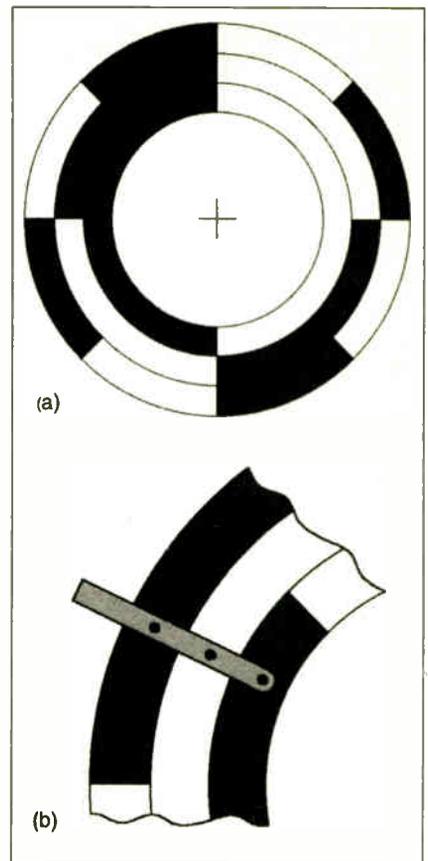


Fig.7.7. (a) Disc patterned with binary code, (b) arrangement of sensors.

segment to the next the bits which change may not do so at the same instant, leading to unwanted "intermediate" codes.

The worse case in the Fig.7.7 example is the change from 000 to 111 or vice versa, where any 3-bit number (or even a sequence of two numbers) could appear as an intermediate code. The solution is to pattern the disc so that only one bit changes as we move from one segment to the next, as shown in Fig.7.8.

This type of binary code is called a **Gray code** and a 3-bit Gray code is shown in Table 7.1. We can use a logic circuit to convert it to standard binary numbers as shown in Fig.7.9.

Using code-patterned discs is useful where the disc position is simply an angle, but if the movement of the disc over multiple revolutions must be measured it is less useful. Furthermore if high resolution is required the printing of the disc becomes complex and difficult, and a potentially large number of sensors is required (one per bit).

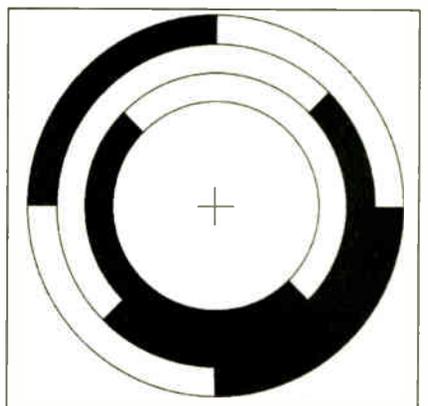


Fig.7.8. Gray coded disc.

**Table 7.1. 3-bit Gray Code**

Output Codes		
A	B	C
0	0	0
0	0	1
0	1	1
0	1	0
1	1	0
1	1	1
1	0	1
1	0	0

A = inner ring of Fig.7.8  
 B = middle ring of Fig.7.8  
 C = outer ring of Fig.7.8

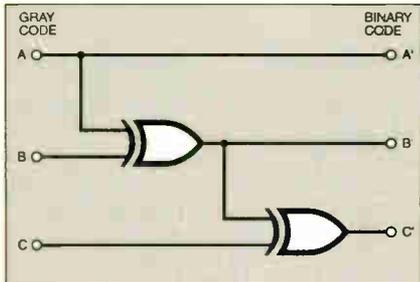


Fig.7.9. Gray code to binary code converter.

### INCREMENTAL ENCODING

An alternative approach, called an **incremental encoder**, uses two sensors that generate a quadrature signal – that is, two waveforms offset by a 90 degree phase shift. Movement is indicated by the output of either sensor switching and direction is indicated by the relative phase (plus or minus 90 degrees) of the signals.

These signals can be used to control a counter to obtain a binary representation of position. As this approach, unlike the Gray code disc, does not directly indicate absolute location, a third sensor may be used to provide an index or reference point.

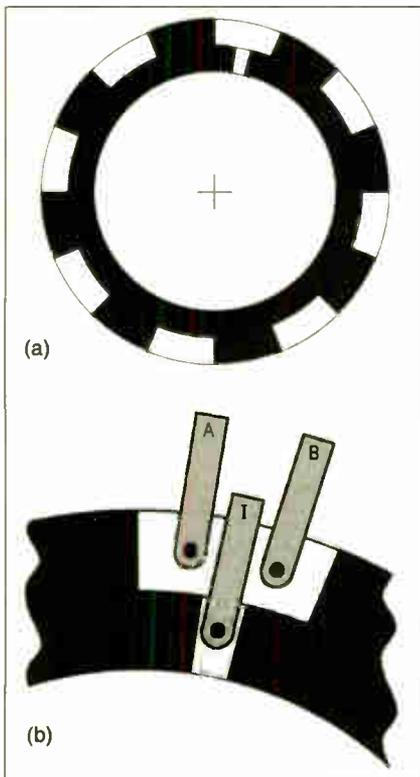


Fig.7.10. Incremental encoder for motion sensing (a) disc pattern, (b) sensor locations.

An incremental encoder disc pattern and its sensor locations are shown in Fig.7.10. The quadrature signal is obtained from sensors A and B and the reference signal from sensor I.

The spacing of the alternate black and white zones determines the resolution with which location can be measured. The separation distance between sensors A and B is half the length of the black and white sections. The waveforms obtained from the sensors are shown in Fig.7.11.

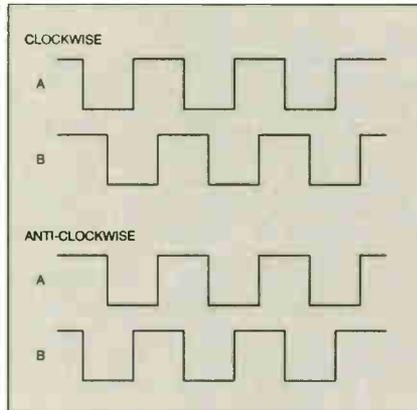


Fig.7.11. Quadrature signals from the incremental encoder in Fig.7.10.

We can build logic circuits to determine the direction of movement from the A and B signals in Fig.7.11. The simplest approach is to look at the level of (say) B when there is a positive edge on A (i.e. at the *instant* that it changes from low to high). Checking Fig.7.11 will show that a 0 indicates clockwise and a 1 indicates anti-clockwise in this arrangement.

We can check the direction at any of the edges of the two waveforms in this way. Each edge also represents a definite indication of movement and can therefore be used to increment or decrement a counter circuit depending on the direction. The binary value in the counter will then represent the relative movement of the disc since the counter was last set to a particular value (e.g. reset).

### RESPONSE TIME

The logic design for an incremental encoder can be a little tricky due to the need to prevent races between the direction discrimination and the counting. It is further complicated by the need to distinguish between definite movement in a particular direction and vibration about a basically fixed point, which can continuously switch one of the sensors.

The latter problem prevents us from using the simple solution of connecting (say) A to the clock of an up/down counter and B to the up/down control. The best approach is to sample the quadrature waveform using an external clock running at a faster rate than the fastest possible input signals and use a state machine to work out what is going on. The state machine then controls the position counter.

A state machine is a sequential logic system whose outputs depend on the previous and present inputs (as in a counter, for instance) as opposed to processes that are functions of present inputs alone.

Fortunately, incremental position sensor decoder i.c.s are available, for example the HCTL-200xx series from Agilent

Technologies (formerly Hewlett Packard). These chips also include simple digital filters to remove glitches from the input waveforms. Specialist motion control processors, such as the LM628 from National Semiconductor, also have built-in quadrature decoders and counters.

### OPTICAL ENCODING SENSORS

As we have seen, it is possible to detect the rate and angle of rotation using specially designed discs and optical sensors. There are several techniques and a number of readily available sensors that we can use:

- **Photodiode (or phototransistor) and I.e.d.** As shown in Fig.7.12, the I.e.d. and photosensor are mounted on opposite sides of the encoding disc that has alternating transparent and opaque areas. The photosensor will detect light shining through the transparent area.

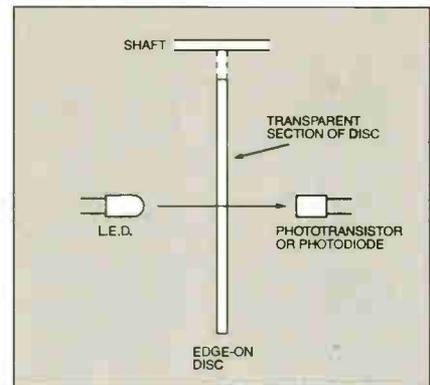


Fig.7.12. Sensing using a separate I.e.d. and photosensor.

- **Slotted optosensors.** A slotted optosensor has a built-in phototransistor and I.e.d. mounted facing each other across a small gap, as indicated in Fig.7.13. Again a disc that has alternating transparent and opaque areas is used. The sensor is mounted at the edge of the disc so that the light beam is interrupted when the disc rotates. Another name given to this type of sensor is a **photointerrupter**.

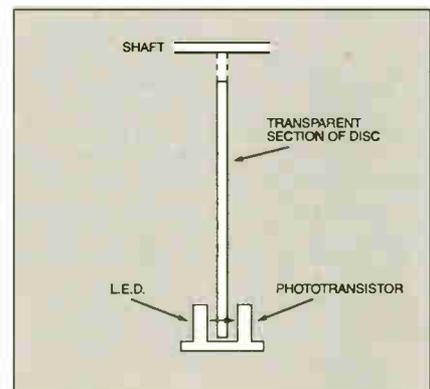


Fig.7.13. Slotted photosensor.

- **Reflective optosensors.** These also have a built-in I.e.d. and phototransistor but which are mounted side by side on one side of the disc only, which does not need to be transparent. Light is reflected back to the phototransistor by a reflective surface placed close to the sensor as shown in

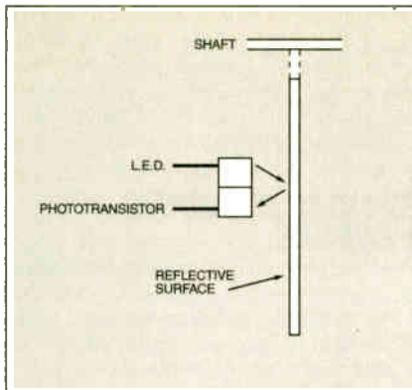


Fig.7.14. Reflective photosensor.


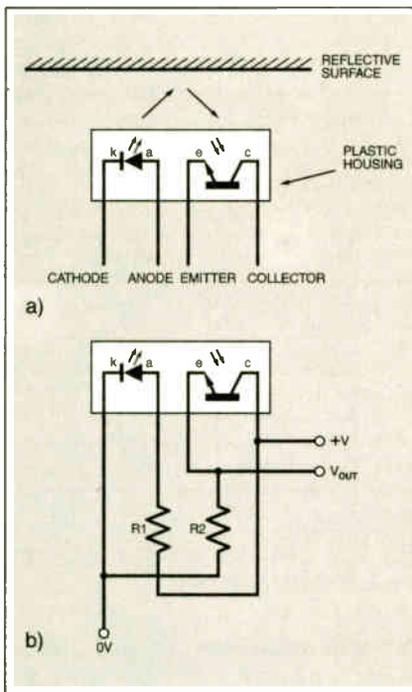


Fig.7.15. (a) Schematic of slotted optosensor and (b) connections.

Fig.7.14. We use this type of sensor in the *Lab Work* experiments this month. Another application of reflective optosensors is for proximity sensing, i.e. to sense when an object is close to the sensor.

The schematic diagram of a typical reflective optosensor which consists of an infra-red (IR) l.e.d. and a phototransistor is shown in Fig.7.15a. The components are mounted in a plastic that is transparent to IR so as to reduce interference from ambient light (e.g. a.c. powered room lighting).

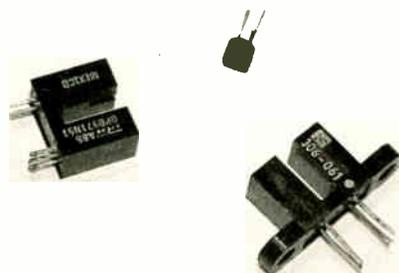This does not mean that they are totally immune to ambient light since there is quite a lot of IR around, especially in tungsten



Typical examples of slotted and reflective photosensors.

lamps, so precautions must still be taken to reduce ambient light as much as possible.

A typical circuit for operating an optosensor is shown in Fig.7.15b, where the l.e.d. is forward biased via resistor R1, the value of which depends on the required current for the l.e.d. (typically 5mA to 20mA). The phototransistor can be used with its collector connected to the power supply voltage and the emitter to ground via resistor R2, as shown.

The value of R2 can be calculated from datasheets – the relevant data for the reflective device we will be using this month is given in Table 7.2.

In Lab Work, we illustrate the use of optosensors, and describe a rotation sensor that uses one in a circuit for measuring wind speed. Before that, though, let's discuss a few basics about wind sensing.

## WIND SPEED MEASUREMENT

The speed of the wind is measured in distance per unit time, such as miles per hour (mph), kilometres per hour (kph), metres per second ( $\text{ms}^{-1}$ ) or knots. Another, subjective, measurement uses the Beaufort Scale, a numbering system that goes from 0 representing calm, to 12 representing hurricane force. The scale actually goes to 17 (126mph to 136mph) but such high wind speeds are extremely rare.

Table 7.3 gives the basic Beaufort Scale and corresponding wind speeds in miles per hours. It is often useful to be able to convert between the other different wind speed units; this is given in Table 7.4. To use the table, choose the units, e.g. 30mph to change to kph, read the FROM-TO multiplication factor (1.609) and multiply – 30mph = 48.3kph. To convert back use the TO-FROM multiplier, e.g. 100kph = 360 $\text{ms}^{-1}$ .

There are many commercial wind speed meters available (anemometers) which fall into three categories:

Table 7.2. Data for the SG-2BC Reflective Photointerrupter

	Parameter	Value
L.E.D.	Forward Voltage ( $I = 4\text{mA}$ )	1.2V (max)
	Power Dissipation	75mW (max)
	Peak Wavelength	940nm
Phototransistor	Collector Dark Current	0.1 $\mu\text{A}$
	Light Current (diode current = 4mA)	100 $\mu\text{A}$
	Leakage Current	0.1 $\mu\text{A}$
	Risetime ( $V_{CC} = 2\text{V}$ , $I_c = 100\mu\text{A}$ )	30 $\mu\text{s}$
	$R_L = 1\text{k}\Omega$	
	Falltime (as above)	30 $\mu\text{s}$
	Collector Current	20mA (max)
	Collector-emitter Voltage	30V (max)
Emitter-collector Voltage	3V (max)	

- **Cup anemometers.** These are probably the most familiar and operate by the wind blowing three or sometimes four cups around on a spindle. In a variation on the separate cups concept, the cups are replaced by an S-shaped arrangement. Cup anemometers suffer from stalling at very low speed due to friction, i.e. they will not start until a particular minimum wind speed.

- **Hot-wire anemometers.** If a wire is heated to a given temperature and air is allowed to flow across the wire, some of the heat will be removed. Hot-wire anemometers use this principle and can be extremely sensitive. They are, however, quite fragile since the wire is very thin.

- **Acoustic anemometers.** The speed of sound in air depends on the relative direction of the sound in relation to the direction of the wind, and to a lesser degree on temperature and barometric pressure.

It is possible to use ultrasonic pulses to measure changes in sound velocity and hence determine wind speed. These can be highly sensitive and have no moving parts, thus making them robust. It is also possible to have three or four sensors mounted at fixed angles to each other to obtain the wind's direction.

## OPTICALLY MONITORED ANEMOMETER

Last month we designed a simple rotation speed circuit using a magnetic sensor and a pulse width-to-voltage converter.

This suffers from two disadvantages:

- One pulse per revolution means that low speeds are difficult to measure as the voltage on the capacitor in the frequency-to-voltage converter will decay and the output will not be a linear function of rotation rate.

- The frequency-to-voltage converter does not follow rapid changes in rotation rate.

We can overcome these problems by increasing the number of pulses per revolution and using a different

Table 7.3. Beaufort Scale for Wind Speed

Beaufort Scale	Description	mph
0	calm	1
1	light air	1-3
2	slight breeze	4-7
3	gentle breeze	8-12
4	moderate breeze	13-18
5	fresh breeze	19-24
6	strong breeze	25-31
7	near gale	32-38
8	gale	39-46
9	strong gale	47-54
10	storm	55-63
11	violent storm	64-72
12	hurricane	73-82

Table 7.4. Conversion between Wind Speed Units

Unit 1	Unit 2	From-To	To-From
mph	kph	1.609	0.621
mph	$\text{ms}^{-1}$	0.447	2.237
mph	knots	0.869	1.151
$\text{ms}^{-1}$	knots	1.944	0.514
$\text{ms}^{-1}$	kph	3.6	0.278
knots	kph	1.852	0.54

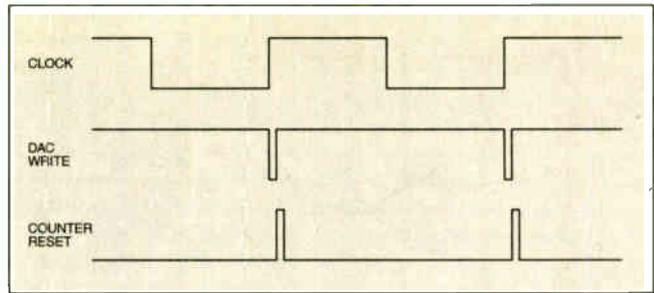
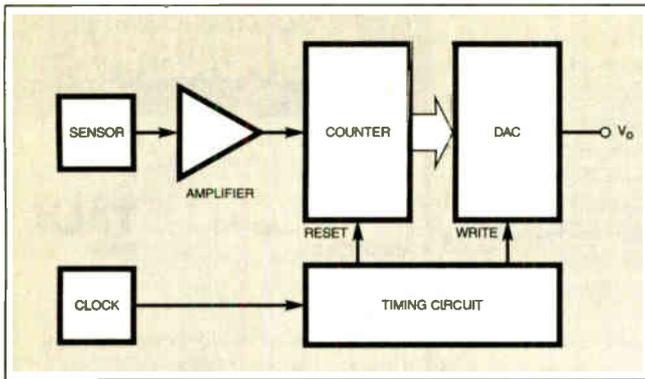


Fig.7.17 (above). Timing diagram of anemometer circuit.

Fig.7.16 (left). Block diagram of anemometer circuit.

type of frequency-to-voltage converter employing a counter and a digital-to-analogue converter (DAC).

To illustrate the theory (that we put into practice in *Lab Work*), we can use a reflective optosensor and the disc shown in Fig.7.10 to create eight pulses per revolution. These are counted over a defined interval by an 8-bit binary counter and the count is converted into a voltage using a DAC as indicated in the block diagram in Fig.7.16.

We need to control the counter and DAC so that at the end of each timing period (e.g. one second) the value on the counter outputs is transferred to the DAC, after which the counter is reset ready for the next counting interval, as shown in Fig.7.17.

A well-designed circuit can produce a stable voltage output as a linear function of shaft rotation speed which changes at regular intervals.

However, we need to work out several values before the circuit can be finalised. These will depend on the intended output (e.g.  $\text{ms}^{-1}$ , mph or kph), the design of the anemometer cups (number of cups, relative size, etc) and the relationship between output voltage and wind speed.

In the *Lab Work* design, we produce an output voltage of 3.0V for a wind speed of  $30\text{ms}^{-1}$ . From comparative measurements using the 3-cup anemometer and a commercial device, the number of pulses per

second (pps) obtained from the circuit is 30.3pps for a wind speed of  $6\text{ms}^{-1}$ , which gives 5.05pps per  $\text{ms}^{-1}$ . At the maximum wind speed of  $30\text{ms}^{-1}$  (67mph) we get 151.5pps.

The output of the DAC is determined by:

$$V \times (D / N)$$

where:

$V$  is the maximum voltage that the DAC can output (frequently, but not always, the same voltage as on the positive supply line)

$D$  is the digital input value, usually in binary form

$N$  is the number of input bits that the DAC has been designed to accept, typically having a decimal value range of 0 to 255 (8-bit), although DACs having other input ranges are available.

Using an 8-bit DAC (as we do in *Lab Work*), to achieve an output voltage of 3.0V for  $30\text{ms}^{-1}$ , the input value required is  $D = 3 \times 256 / 5 = 154$ , to the nearest integer. This means we need to count 154 pulses every interval to make the output read 3.0V at  $30\text{ms}^{-1}$  which makes the interval very close to one second, precisely calculated as 1.016s.

### WIND SPEED CALCULATION

Unfortunately, wind speed is not the easiest parameter to calibrate unless you possess a wind tunnel! The main reason for

this is that the relationship between cup design and rotation speed with wind speed is not straightforward, so we cannot perform simple calculations. There are two main options for calibration:

- Compare with a commercial anemometer. This is the way we determined the number of pulses per second in the *Lab Work* design.
- Place the anemometer on a long pole and put it (vertically!) out of a car window and drive at a known speed. The anemometer needs to be away from the slip stream of the vehicle. This requires considerable care (*remember you are not jousting. Ed!*)

### WIND DIRECTION SENSING

Measuring wind direction requires a binary or Gray coded disc and multiple sensors – the more bits in the code, the higher the resolution but the more complex the circuit. The main part of a wind direction sensor is a vane and counter weight (to ensure balance).

The vane points into the wind and turns a coded disc. All one needs to do is ensure the code's origin is aligned with North and the instrument can be calibrated in relation to the number of bits and the angular displacement that each represents.

We discuss wind sensing in a practical sense in Labs 7.2 and 7.3. First, though, we experiment with comparators.

# TEACH-IN 2002 – Lab Work 7

DAVE CHESMORE

## Comparator and Optosensing Experiments, plus Anemometer Assembly

### Lab 7.1 Comparators

In this Lab we examine the characteristics of comparators by building an op.amp version of the light switch in Part 2. Fig.7.18 shows the circuit diagram using an OP177 op.amp and a light dependent resistor (l.d.r.).

Since we are using a single +5V supply rail (rather than a dual  $\pm 5\text{V}$  supply), we

need to generate a reference voltage. This is achieved using Zener diode D1 to give a 2.7V reference. Resistor R2 provides sufficient current for the Zener diode to reach its Zener voltage.

Build the circuit on your breadboard and connect the Picoscope to the op.amp's output. You should be able to see the output change state when the light level changes

sufficiently for the voltage at the op.amp's non-inverting input (pin 3) to cross the reference threshold voltage at the inverting input (pin 2).

Use the Picoscope on a small sampling interval and see if the output changes like that shown in Fig.7.19. This rapid changing of state at the switching point is obviously not a good thing!

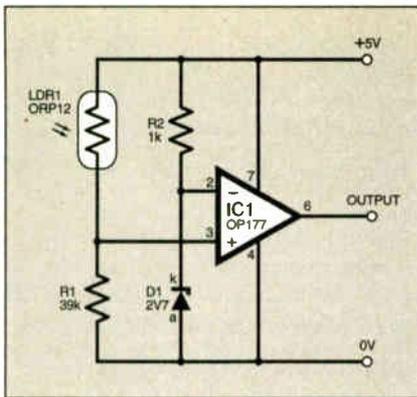


Fig.7.18. Comparator circuit without hysteresis.

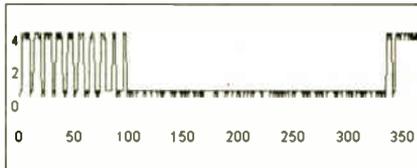


Fig.7.19. Typical noisy output from circuit in Fig.7.18.

Now modify the circuit in Fig.7.18 to become that in Fig.7.20 and repeat the above experiments. The multiple switching should have disappeared (see Fig.7.21). You should also notice that the point at which the output changes state will be different when the light level increases to that when it decreases – this is due to the hysteresis now introduced by the inclusion of resistors R3 and R4.

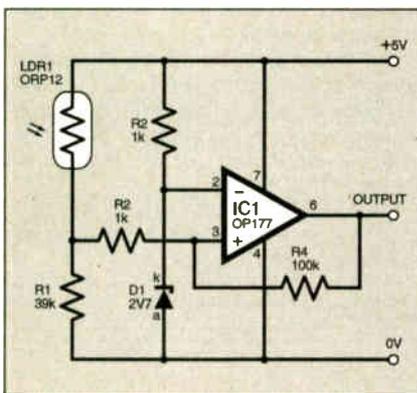


Fig.7.20. Comparator circuit with hysteresis.



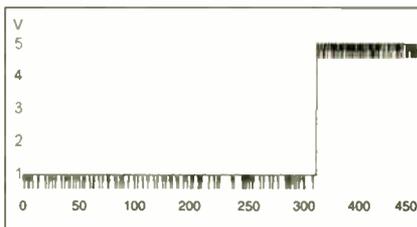


Fig.7.21. Typical clean switching output from circuit in Fig.7.20.

You can vary the amount of hysteresis by changing the values of these resistors as described in this month's tutorial section. Try increasing R4 to 1M $\Omega$  and then R3 to 100k $\Omega$  and see the difference. You may be able to see the hysteresis better by replacing the l.d.r. with a 100k $\Omega$  variable resistor (potentiometer) which will allow you to vary the input voltage in a controlled way.

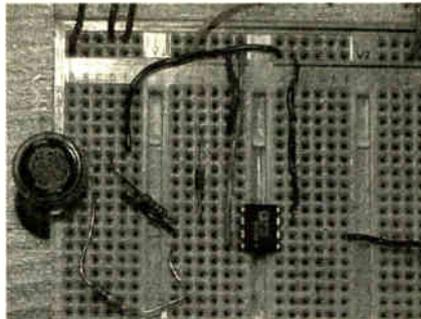

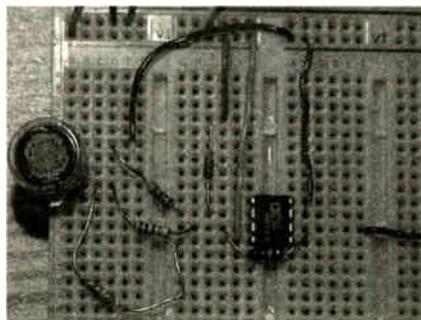Breadboard assembly for circuit in Fig.7.18.



Breadboard assembly for circuit in Fig.7.20.

If you compare the results from this experiment with the transistor-based light switch in Part 2, then it is obvious that a well-designed comparator is much better.

### Lab 7.2 Anemometer using an Optical Sensor

For this anemometer we use the incremental encoder disc in Fig.7.10 and a single reflective optosensor to measure wind speed in a similar manner to that used with the magnetic sensor design in last month's *Teach-In*.

The general principle of operation was illustrated in Fig.7.16, where a counter is used to accumulate pulses over a known period of time and then the count is converted into an analogue voltage using a digital-to-analogue converter (DAC). The complete circuit diagram of the anemometer is shown in Fig.7.22.

The output of the photosensor (X1) is amplified by transistor TR1 and then input to an 8-bit binary counter formed using the two 4-bit counters, IC1a and IC1b. The counter increments on the positive-going edges received at IC1a's clock input CPOA (pin 1). When IC1a rolls over from 15 to 0 (overflow), the negative-going output at OA3 (pin 6) triggers the second counter, IC1b, via its CPTB input (pin 10), causing it to increment.

The eight outputs are connected to a TLC7524 8-bit DAC (IC2) connected to produce an output voltage at its pin 15 (REF). As discussed in the tutorial section, the output voltage is  $5V \times D / 256$  where D is the digital input value (between 0 and 255).

In the prototype, the photosensor used was a type SG-2BC, chosen for its small size. Other common reflective optosensors that could be used include the SY-CR102 and OPB706B.

### TIMING

The circuit based around the four 2-input Schmitt NAND gates within IC3 performs all timing logic.

## COMPONENTS

N.B. Some components are repeated between Lab Works

See **SHOP TALK** page

### Lab 7.1

Resistors	
R1	39k
R2, R3	1k (2 off)
R4	100k
LDR1	ORP12 light dependent resistor

Resistors R1 to R4 0.25W 5% carbon film.

### Semiconductors

D1	BZY88C 2.7V Zener diode
IC1	OP177 op.amp

### Lab 7.2

Resistors	
R1	560 $\Omega$
R2	56k
R3	390 $\Omega$
R4	4k7
R5	10k
R6, R7	39k (2 off)

All 0.25W 5% carbon film.

### Potentiometer

VR1	22k preset, min. round
-----	------------------------

### Capacitors

C1	47 $\mu$ tantalum 16V
C2, C3	10n ceramic (2 off)

### Semiconductors

TR1	BC548 or similar small signal npn transistor
IC1	4520 dual binary counter
IC2	TLC7524 8-bit digital-to-analogue converter
IC3	4093 quad 2-input Schmitt NAND gate

### Miscellaneous

X1	SG-2BC reflective photointerrupter (see text)
----	---

### Lab 7.3

Resistors	
R1 to R3	560 $\Omega$ (3 off)
R4 to R6	56k (3 off)
R7 to R9	390 $\Omega$ (3 off)
R10 to R12	4k7 (3 off)
R13 to R20	470 $\Omega$ (8 off)

All 0.25W 5% carbon film.

### Semiconductors

D1 to D8	red l.e.d. (8 off) (see text)
TR1 to TR3	BC548 or similar small signal npn transistor (3 off)
IC1	74HC138 or 74LS138 3-to-8 line decode

### Miscellaneous

Materials for wind cups and vane (see text).

Approx. Cost Guidance Only

**£15**  
excl. hardware

IC3a is configured as an oscillator with a period of one to three seconds, controllable by preset VR1 (a fixed resistor was used in the test model). Its output is passed to IC3b via a pulse-shaping C-R (capacitor-resistor) network formed by C2 and R6. This causes the output of IC3b to go low for a short period (about 5ms) when the input to C2 goes high – this is the Write signal for DAC IC2.


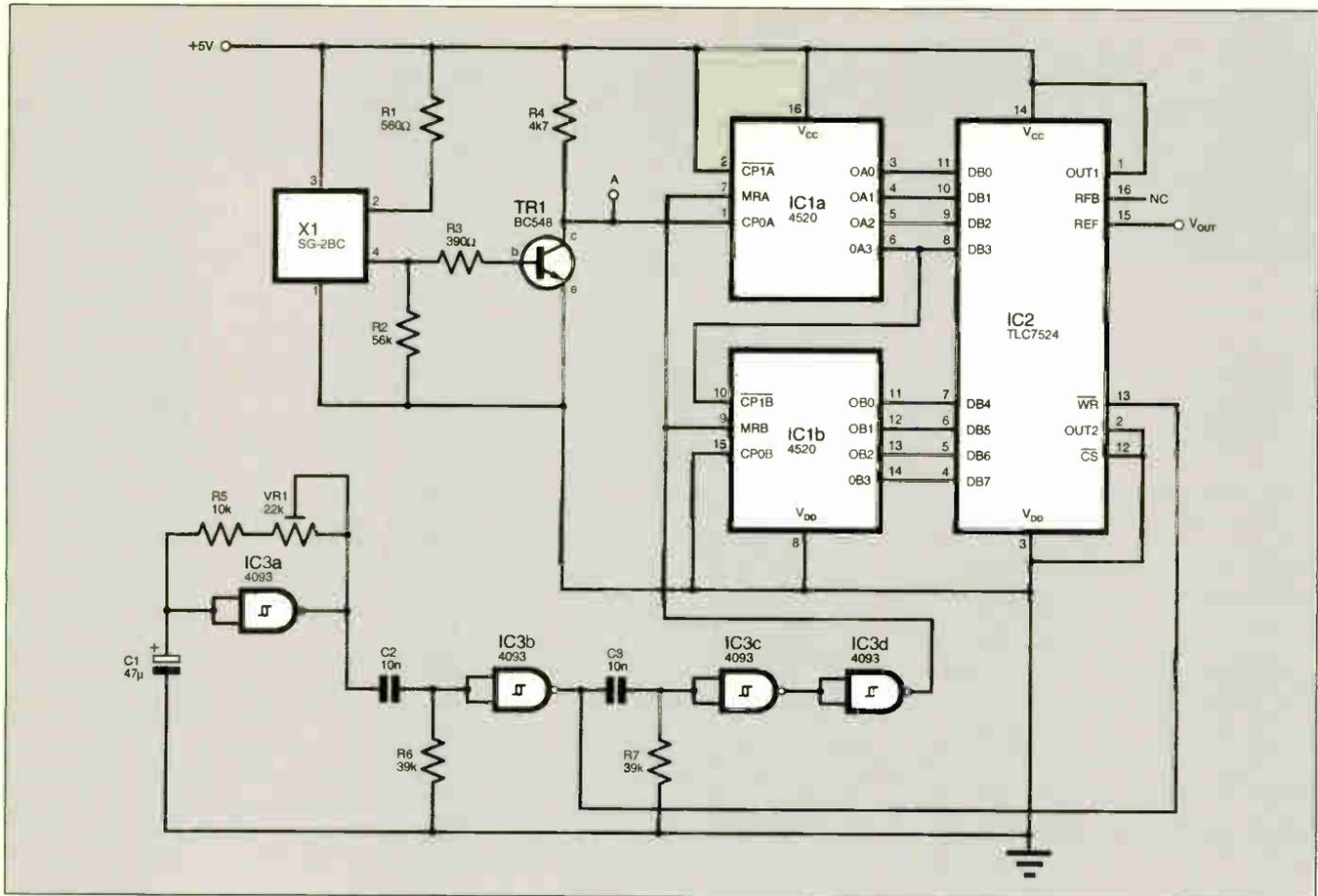


Fig.7.22. Circuit diagram for the anemometer.

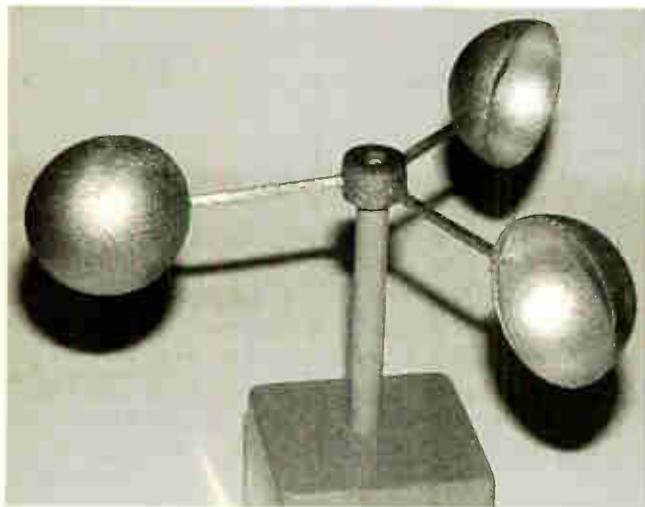

Prototype "homemade" anemometer assembly.

Similarly, IC3c produces a short negative-going pulse, having a period set by C3 and R7, when the output of IC3b goes high. This is inverted by IC3d and produces the Reset pulse for the counters.

### ANEMOMETER MECHANICS

The anemometer is constructed using three half ping-pong balls to make the cups (they can easily be cut using a hacksaw) connected to a central hub with short lengths of plastic as shown in Fig.7.23. Larger cups may be used if you require.

One suggestion is to use plastic scoops available with washing powder. The basic rule for calculating how far the cups should be away from the hub is that the distance from the hub to the centre of the cup should be equal to the cup's diameter.

The hub is attached to a length of plastic or aluminium rod which passes through the barrel of an old felt pen. If the hub is made of plastic then it should ride on the pen with little friction. The pen is attached to a box which contains the disc and electronics. The bottom of the shaft should reach the base of the box and

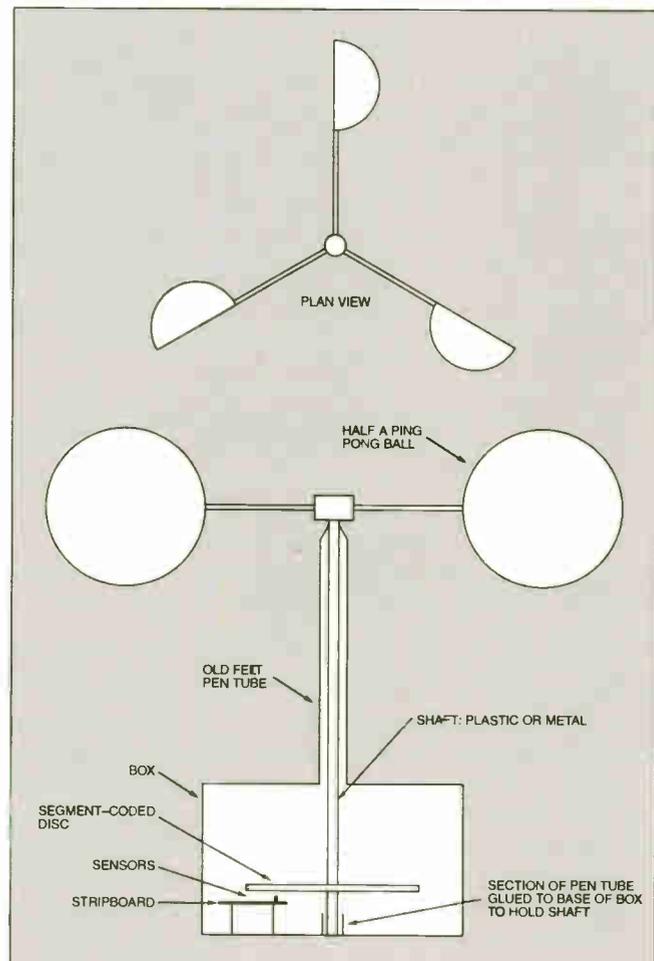


Fig.7.23. Basic format for a suggested anemometer assembly (see text).



Mounting of the sensor in the prototype anemometer.

a short length of pen tube is used to stop the shaft from moving sideways. The encoded disc is secured to the shaft at a position a couple of millimetres away from the top of the sensor.

You should note that the design is very crude and many modifications can be made. For example, using a ball race as the top bearing to ensure that the friction is low and the shaft is secured (in our design, the cup assembly can simply be lifted off the rest).

### SENSOR DISK

Since the sensor is a reflective type, we can use a black and white disc such as that in Fig.7.10. We suggest you get an enlarged photocopy of the disc and paste it onto a piece of stiff card. The sensor needs to be within a few millimetres of the surface of the disc.

Build the circuit on breadboard (but with the sensor mounted on a small bit of strip-board) and set the oscillator period to about one second using VR1. Use the Picoscope to measure the period. Monitor the voltage at point A in Fig.7.22 and rotate the disc. The output should be similar to that in Fig.7.24. If it is not then try moving the sensor closer to the disc.

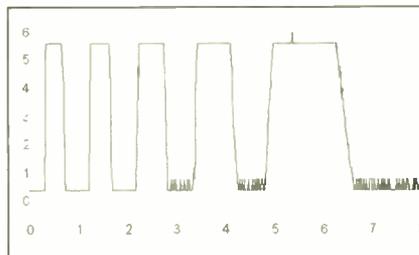


Fig.7.24. Example of output pulses at point A in Fig.7.22.

Once you get a good series of pulses at point A, connect a voltmeter (or the Picoscope) to the output of the circuit. You should get a voltage which changes approximately once per second and which is proportional to the speed of rotation. Fig.7.25

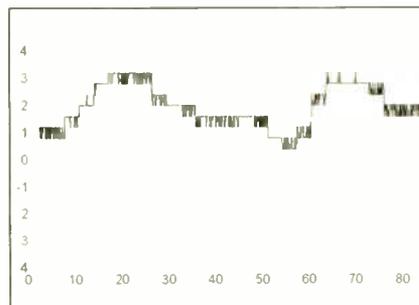


Fig.7.25. Output of anemometer showing wind speed variation.

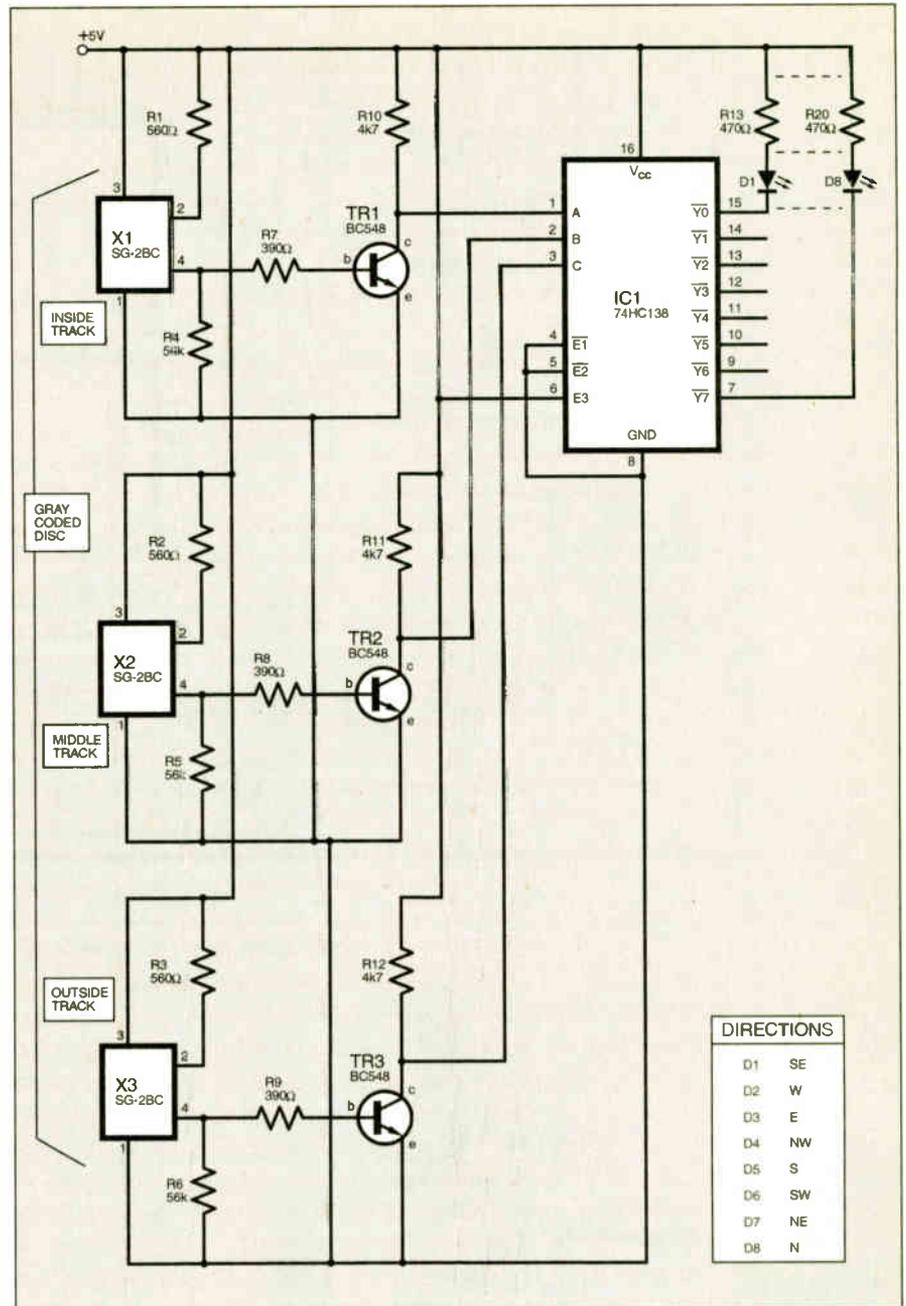


Fig.7.26. Circuit diagram for the wind direction sensor.

shows a typical output captured using the Picoscope (note that the "noise" is due to the limited resolution of the Picoscope ADC-40 and not the DAC).

If the oscillator is set to 1.016s then 0.1V at the DAC's output should be roughly equal to  $1\text{ms}^{-1}$  (i.e. 3.0V equals  $30\text{ms}^{-1}$ ). Accurate calibration is not easy, as discussed earlier in the theory section.

### Lab 7.3 Wind Direction Meter

Measuring wind direction can be done using a binary or Gray coded disc and multiple sensors. In this Lab we show you how to build an instrument to indicate eight points on the compass – north, north-east, east, etc, so we need a 3-bit Gray coded disc.

The circuit diagram is shown in Fig.7.26. The outputs of the sensors are amplified by transistors TR1 to TR3 and input to a 3-to-8 line decoder, IC1. The decoder takes a 3-bit binary input and sets the corresponding output low. For example, if the input is binary 000, output Y0 goes low; an input of binary 110 causes output Y6 to go low.

Table 7.5. Relationship between Outputs and Compass Points for Lab 7.3


Output/L.E.D.	Compass point
Y0-D1	South East
Y1-D2	West
Y2-D3	East
Y3-D4	North West
Y4-D5	South
Y5-D6	South West
Y6-D7	North East
Y7-D8	North

The decoder has three enables, two active low and one active high. In this circuit they are set to permanently enable the device. Each output is connected to an l.e.d. to indicate whether or not it is low. Since the disc is Gray coded, the outputs Y0-Y7 do not correspond to successive points on the compass as they would if the disc were binary coded. Use Table 7.5 to connect the l.e.d.s in the correct order.

Photocopy the disc in Fig.7.8. Mount the sensors in a similar manner to Lab 7.1.



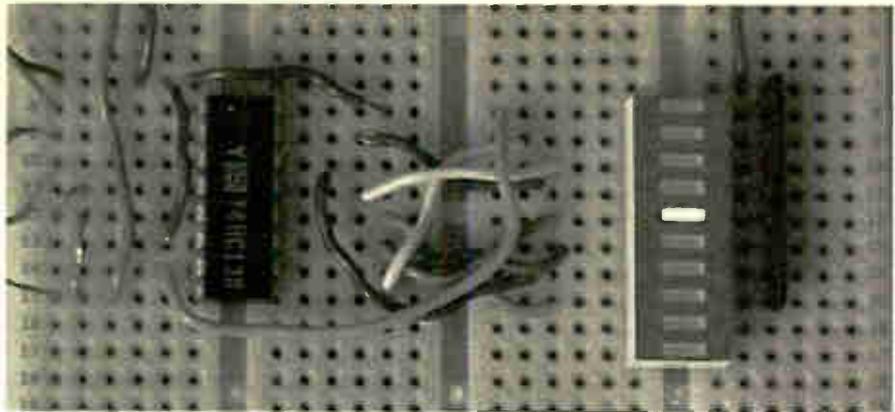Example of a reflective sensor, as used in the wind vane.




Breadboard assembly for the display circuit in Fig.7.26. Individual I.e.d.s may be used in place of the bargraph display and discrete resistors in place of the resistor module.



Above: Stripboard assembly mounting for the wind vane.

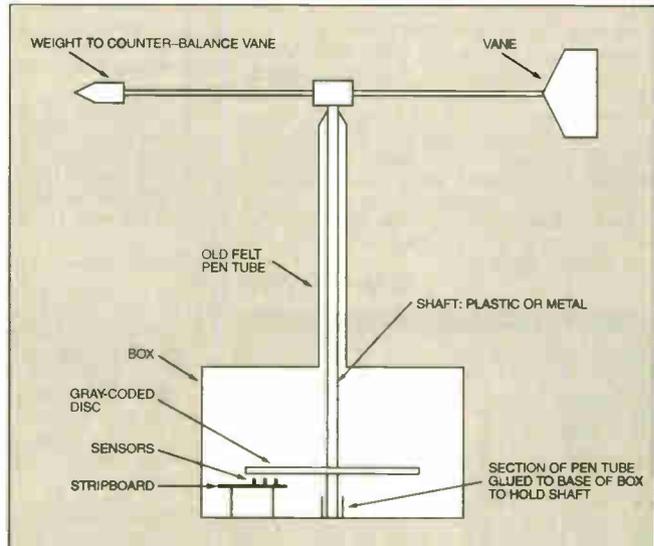Right: Fig.7.27. Basic format for a suggested wind vane assembly (see text).



There are three points to note in this particular design:

1. The outputs from the sensors are inverted by the transistors so that the black areas correspond to a logic 1. This may not be correct if you use different sensors.

2. The disc in our design faced upwards when the sensor was completed thus making everything occur in the opposite way. If your disc faces down, swap west for east, north west for north east, and south west for south east in Table 7.5.

3. In our prototype we demonstrated the direction indicating principle using an I.e.d. bargraph, but if you choose to use individual I.e.d.s instead, we suggest you arrange them in a circle.

Most of the construction of the wind

vane is the same as for the anemometer, but using the Gray coded disc instead. The vane itself is a horizontal length of aluminium or plastic rod to which is attached a vertical vane at one end and a counter-balance weight at the other. The photograph of a commercial vane should give you a good idea of the design.

Having completed construction, the only thing left to do is use a compass to align north on the disc (centre of the black-black area) to magnetic north.

### NEXT MONTH

In Part 8 next month, we examine control-feedback closed-loop systems, filters, sensor actuator combinations, with reference to smoke and gas detectors.



Example of a commercial wind vane.



## EPE BINDERS



### KEEP YOUR MAGAZINES SAFE – RING US NOW!

This ring binder uses a special system to allow the issues to be easily removed and re-inserted without any damage. A nylon strip slips over each issue and this passes over the four rings in the binder, thus holding the magazine in place.

The binders are finished in hard-wearing royal blue p.v.c. with the magazine logo in gold on the spine. They will keep your issues neat and tidy but allow you to remove them for use easily.

The price is £5.95 plus £3.50 post and packing. If you order more than one binder add £1 postage for each binder after the initial £3.50 postage charge (overseas readers the postage is £6.00 each to everywhere except Australia and Papua New Guinea which costs £10.50 each).

Send your payment in £'s sterling cheque or PO (Overseas readers send £ sterling bank draft, or cheque drawn on a UK bank or pay by card), to **Everyday Practical Electronics, Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562.**

E-mail: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk). Web site: <http://www.epemag.wimborne.co.uk>

Order on-line from [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)



We also accept card payments. Mastercard, Visa, Amex, Diners Club or Switch (minimum card order £5). Send your card number and card expiry date plus Switch Issue No. with your order.



# VIDEOS ON ELECTRONICS

A range of videos selected by *EPE* and designed to provide instruction on electronics theory. Each video gives a sound introduction and grounding in a specialised area of the subject. The tapes make learning both easier and more enjoyable than pure textbook or magazine study. They have proved particularly useful in schools, colleges, training departments and electronics clubs as well as to general hobbyists and those following distance learning courses etc




## BASICS

VT201 to VT206 is a basic electronics course and is designed to be used as a complete series, if required.

**VT201** 54 minutes. Part One; D.C. Circuits. This video is an absolute must for the beginner. Series circuits, parallel circuits, Ohms law, how to use the digital multimeter and much more. **Order Code VT201**

**VT202** 62 minutes. Part Two; A.C. Circuits. This is your next step in understanding the basics of electronics. You will learn about how coils, transformers, capacitors, etc are used in common circuits. **Order Code VT202**

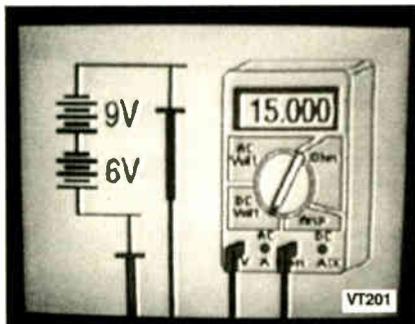**VT203** 57 minutes. Part Three; Semiconductors. Gives you an exciting look into the world of semiconductors. With basic semiconductor theory. Plus 15 different semiconductor devices explained. **Order Code VT203**



**VT204** 56 minutes. Part Four; Power Supplies. Guides you step-by-step through different sections of a power supply. **Order Code VT204**

**VT205** 57 minutes. Part Five; Amplifiers. Shows you how amplifiers work as you have never seen them before. Class A, class B, class C, op.amps. etc. **Order Code VT205**

**VT206** 54 minutes. Part Six; Oscillators. Oscillators are found in both linear and digital circuits. Gives a good basic background in oscillator circuits. **Order Code VT206**

**£34.95** each  
inc. VAT & postage

Order 8 or more get one extra FREE  
Order 16 get two extra FREE

## VCR MAINTENANCE

**VT102** 84 minutes: Introduction to VCR Repair. Warning, not for the beginner. Through the use of block diagrams this video will take you through the various circuits found in the NTSC VHS system. You will follow the signal from the input to the audio/video heads then from the heads back to the output. **Order Code VT102**

**VT103** 35 minutes: A step-by-step easy to follow procedure for professionally cleaning the tape path and replacing many of the belts in most VHS VCR's. The viewer will also become familiar with the various parts found in the tape path. **Order Code VT103**

## DIGITAL

Now for the digital series of six videos. This series is designed to provide a good grounding in digital and computer technology.

**VT301** 54 minutes. Digital One; Gates begins with the basics as you learn about seven of the most common gates which are used in almost every digital circuit, plus Binary notation. **Order Code VT301**

**VT302** 55 minutes. Digital Two; Flip Flops will further enhance your knowledge of digital basics. You will learn about Octal and Hexadecimal notation groups, flip-flops, counters, etc. **Order Code VT302**

**VT303** 54 minutes. Digital Three; Registers and Displays is your next step in obtaining a solid understanding of the basic circuits found in today's digital designs. Gets into multiplexers, registers, display devices, etc. **Order Code VT303**

**VT304** 59 minutes. Digital Four; DAC and ADC shows you how the computer is able to communicate with the real world. You will learn about digital-to-analogue and analogue-to-digital converter circuits. **Order Code VT304**


**VT305** 56 minutes. Digital Five; Memory Devices introduces you to the technology used in many of today's memory devices. You will learn all about ROM devices and then proceed into PROM, EPROM, EEPROM, SRAM, DRAM, and MBM devices. **Order Code VT305**

**VT306** 56 minutes. Digital Six; The CPU gives you a thorough understanding in the basics of the central processing unit and the input/output circuits used to make the system work. **Order Code VT306**

## RADIO

**VT401** 61 minutes. A.M. Radio Theory. The most complete video ever produced on a.m. radio. Begins with the basics of a.m. transmission and proceeds to the five major stages of a.m. reception. Learn how the signal is detected, converted and reproduced. Also covers the Motorola C-QUAM a.m. stereo system. **Order Code VT401**

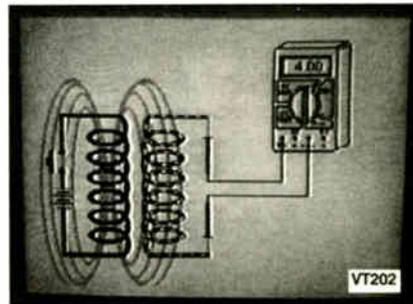**VT402** 58 minutes. F.M. Radio Part 1. F.M. basics including the functional blocks of a receiver. Plus r.f. amplifier, mixer oscillator, i.f. amplifier, limiter and f.m. decoder stages of a typical f.m. receiver. **Order Code VT402**




**VT403** 58 minutes. F.M. Radio Part 2. A continuation of f.m. technology from Part 1. Begins with the detector stage output, proceeds to the 19kHz amplifier, frequency doubler, stereo demultiplexer and audio amplifier stages. Also covers RDS digital data encoding and decoding. **Order Code VT403**

## MISCELLANEOUS

**VT501** 58 minutes. Fibre Optics. From the fundamentals of fibre optic technology through cable manufacture to connectors, transmitters and receivers. **Order Code VT501**

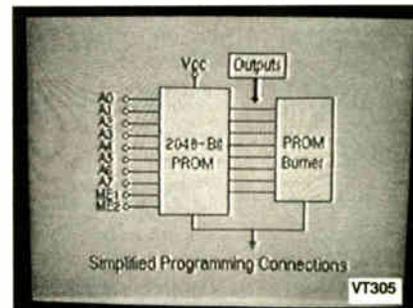**VT502** 57 minutes. Laser Technology A basic introduction covering some of the common uses of laser devices, plus the operation of the Ruby Rod laser, HeNe laser, CO<sub>2</sub> gas laser and semiconductor laser devices. Also covers the basics of CD and bar code scanning. **Order Code VT502**



Each video uses a mixture of animated current flow in circuits plus text, plus cartoon instruction etc., and a very full commentary to get the points across. The tapes are imported by us and originate from VCR Educational Products Co, an American supplier. We are the worldwide distributors of the PAL and SECAM versions of these tapes. (All videos are to the UK PAL standard on VHS tapes unless you specifically request SECAM versions.)

**ORDERING:** Price includes postage to anywhere in the world.

**OVERSEAS ORDERS:** We use the VAT portion of the price to pay for airmail postage and packing, wherever you live in the world. Just send £34.95 per tape. All payments in £ sterling only (send cheque or money order drawn on a UK bank). Make cheques payable to Direct Book Service.

Visa, Mastercard, Amex, Diners Club and Switch orders accepted – please give card number, card expiry date and Switch Issue No.

Orders are normally sent within seven days but please allow a maximum of 28 days, longer for overseas orders.

Send your order to: Direct Book Service, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND

Tel: 01202 873872. Fax: 01202 874562. E-mail: [dbs@epemag.wimborne.co.uk](mailto:dbs@epemag.wimborne.co.uk)

Online store: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

# PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872; Fax 01202 874562; E-mail: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm.** Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

**NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail. Back numbers or photostats of articles are available if required – see the Back Issues page for details.**

**Please check price and availability in the latest issue. Boards can only be supplied on a payment with order basis.**

PROJECT TITLE	Order Code	Cost
Vibralarm	NOV '99 230	£6.93
Demister One-Shot	245	£6.78
★ Ginormous Stopwatch – Part 1	246	£7.82
★ Ginormous Stopwatch – Part 2	DEC '99	
Giant Display	247	£7.85
Serial Port Converter	248	£3.96
Loft Guard	249	£4.44
Scratch Blanker	JAN '00 250	£4.83
Flashing Snowman (Multi-project PCB)	932	£3.00
★ Video Cleaner	FEB '00 251	£5.63
Find It	252	£4.20
★ Teach-In 2000 – Part 4	253	£4.52
High Performance Regenerative Receiver	MAR '00 254, 255	£5.49
★ <i>EPE</i> Icebreaker – PCB257, programmed PIC16F877 and floppy disc	256	Set
Parking Warning System	Set only	£22.99
★ Micro-PICscope	258	£5.08
Garage Link – Transmitter	259	£4.99
Receiver	261	Set
262	262	£5.87
Versatile Mic/Audio Preamp	MAY '00 260	£3.33
PIR Light Checker	263	£3.17
★ Multi-Channel Transmission System – Transmitter	264	Set
Receiver	265	£6.34
Interface	266	
★ Canute Tide Predictor	JUNE '00 267	£3.05
★ PIC-Gen Frequency Generator/Counter	JULY '00 268	£5.07
g-Meter	269	£4.36
★ <i>EPE</i> Moodloop	AUG '00 271	£5.47
Quiz Game Indicator	272	£4.52
Handy-Amp	273	£4.52
Active Ferrite Loop Aerial	SEPT '00 274	£4.67
★ Remote Control IR Decoder	Software only	–
★ PIC Dual-Channel Virtual Scope	OCT '00 275	£5.15
Handclap Switch	NOV '00 270	£3.96
★ PIC Pulsometer	Software only	–
Twinkling Star	DEC '00 276	£4.28
Festive Fader	277	£5.71
Motorists' Buzz-Box	278	£5.39
★ PICtogram	279	£4.91
★ PIC-Monitored Dual PSU-1	280	£4.75
Monitor Unit	281	£5.23
Static Field Detector (Multi-project PCB)	932	£3.00
Two-Way Intercom	JAN '01 282	£4.76
UFO Detector and Event Recorder		
Magnetic Anomaly Detector	283	Set
Event Recorder	284	£6.19
Audio Alarm	285	
★ Using PICs and Keypads	Software only	–
Ice Alarm	FEB '01 287	£4.60
★ Graphics L.C.D. Display with PICs (Supp)	288	£5.23
Using the LM3914-6 L.E.D. Bargraph Drivers		
Multi-purpose Main p.c.b.	289	Set
Relay Control	290	£7.14
L.E.D. Display	291	
★ PC Audio Power Meter	Software only	–
Doorbell Extender: Transmitter	MAR '01 292	£4.20
Receiver	293	£4.60
Trans/Remote	294	£4.28
Rec./Relay	295	£4.92
<i>EPE</i> Snug-bug Heat Control for Pets	APR '01 296	£6.50
Intruder Alarm Control Panel		
Main Board	297	£6.97
External Bell Unit	298	£4.76
Camcorder Mixer	MAY '01 299	£6.34
★ PIC Graphics L.C.D. Scope	300	£5.07
Hosepipe Controller	JUNE '01 301	£5.14
Magfield Monitor (Sensor Board)	302	£4.91
Dummy PIR Detector	303	£4.36
★ PIC16F87x Extended Memory	Software only	–
Stereo/Surround Sound Amplifier	JULY '01 304	£4.75
Perpetual Projects Uniboard-1	305	£3.00
Solar-Powered Power Supply & Voltage Reg.		
MSF Signal Repeater and Indicator		
Repeater Board	306	£4.75
Meter Board	307	£4.44
★ PIC to Printer Interface	308	£5.39

PROJECT TITLE	Order Code	Cost
Lead/Acid Battery Charger	AUG '01 309	£4.99
Shortwave Loop Aerial	310	£5.07
★ Digitimer – Main Board	311	£6.50
– R.F. Board	312	£4.36
Perpetual Projects Uniboard-2		
L.E.D. Flasher – Double Door-Buzzer	305	£3.00
Perpetual Projects Uniboard-3	SEPT '01 305	£3.00
Loop Burglar Alarm, Touch-Switch Door-Light and Solar-Powered Rain Alarm		
L.E.D. Super Torches – Red Main	313	Set
– Display Red	314	£6.10
– White L.E.D.	315	£4.28
★ Sync Clock Driver	316	£5.94
★ Water Monitor	317	£4.91
Camcorder Power Supply	OCT '01 318	£5.94
PIC Toolkit Mk3	319	£8.24
Perpetual Projects Uniboard-4. Gate Sentinel, Solar-powered Bird Scarer and Solar-Powered Register	305	£3.00
Teach-In 2002 Power Supply	NOV '01 320	£4.28
Lights Needed Alert	321	£5.39
Pitch Switch	322	£5.87
Capacitance Meter – Main Board (double-sided)	323	Set
– Display Board (double-sided)	324	£12.00
★ ★ PIC Toolkit TK3 – Software only	–	–
4-Channel Twinkling Lights	DEC '01 325	£6.82
Ghost Buster – Mic	326	Set
– Main	327	£5.78
★ PIC Polywhatsit – Digital	328	Set
– Analogue	329	£7.61
Forever Flasher	JAN '02 330	£4.44
Time Delay Touch Switch	331	£4.60
★ PIC Magick Musick	332	£5.87
Versatile Bench Power Supply	333	£5.71
★ PIC Spectrum Analyser	FEB '02 334	£7.13
Versatile Current Monitor	335	£4.75
Guitar Practice Amp	336	£5.39
★ PIC Virus Zapper	MAR '02 337	£4.75
RH Meter	338	£4.28
★ PIC Mini-Enigma – Software only	–	–
★ Programming PIC Interrupts – Software only	–	–
★ PIC Controlled Intruder Alarm	APR '02 339	£6.50
★ PIC Big Digit Display	MAY '02 341	£6.02
Washing Ready Indicator	342	£4.75
Audio Circuits-1 – LM386N-1	343	£4.28
– TDA7052	344	£4.12
– TBA820M	345	£4.44
– LM380N	346	£4.44
– TDA2003	347	£4.60
– Twin TDA2003	348	£4.75

## EPE SOFTWARE

Software programs for *EPE* projects marked with a single asterisk \* are available on 3.5 inch PC-compatible disks or free from our internet site. The following disks are available: **PIC Tutorial** (Mar-May '98); **PIC Toolkit Mk2 V2-4d** (May-Jun '99); ***EPE* Disk 1** (Apr '95-Dec '98); ***EPE* Disk 2** (1999); ***EPE* Disk 3** (2000); ***EPE* Disk 4** (2001); ***EPE* Disk 5** (Jan 2002 issue to current cover date); ***EPE* Teach-In 2000**; ***EPE* Spectrum**; ***EPE* Interface Disk 1** (October '00 issue to current cover date). ★ **PIC Toolkit TK3** software (Nov '01) is on CD-ROM. The 3.5 inch disks are £3.00 each (UK), the CD-ROM is £6.95 (UK). Add 50p each for overseas surface mail, and £1 each for airmail. All are available from the *EPE PCB Service*. All files can be downloaded free from our internet FTP site: <ftp://ftp.epemag.wimborne.co.uk>.

## EPE PRINTED CIRCUIT BOARD SERVICE

Order Code	Project	Quantity	Price
Name .....	.....		
Address .....	.....		
Tel. No. ....	.....		
I enclose payment of £..... (cheque/PO in £ sterling only) to:			
		<b>Everyday Practical Electronics</b>	
		<b>MasterCard, Amex, Diners Club, Visa or Switch</b>	
Card No. ....	.....		
Card Exp. Date.....	Switch Issue No.....		
Signature.....	.....		
<b>NOTE: You can also order p.c.b.s by phone, Fax, E-mail or via our internet site on a secure server:</b>			
<a href="http://www.epemag.wimborne.co.uk/shopdoor.htm">http://www.epemag.wimborne.co.uk/shopdoor.htm</a>			



## EPE TEACH-IN 2000 CD-ROM

The whole of the 12-part *Teach-In 2000* series by John Becker (published in *EPE* Nov '99 to Oct 2000) is now available on CD-ROM. Plus the *Teach-In 2000* interactive software covering all aspects of the series and Alan Winstanley's *Basic Soldering Guide* (including illustrations and Desoldering).

*Teach-In 2000* covers all the basic principles of electronics from Ohm's Law to Displays, including Op.Amps, Logic Gates etc. Each part has its own section on the interactive software where you can also change component values in the various on-screen demonstration circuits.

The series gives a hands-on approach to electronics with numerous breadboard circuits to try out, plus a simple computer interface which allows a PC to be used as a basic oscilloscope.

**ONLY £12.45** including VAT and p&p

Order code Teach-In CD-ROM

## PROJECT CONSTRUCTION

### PRACTICAL REMOTE CONTROL PROJECTS Owen Bishop

Provides a wealth of circuits and circuit modules for use in remote control systems of all kinds; ultrasonic, infra-red, optical fibre, cable and radio. There are instructions for building fourteen novel and practical remote control projects. But this is not all, as each of these projects provides a model for building dozens of other related circuits by simply modifying parts of the design slightly to suit your own requirements. This book tells you how.

Also included are techniques for connecting a PC to a remote control system, the use of a microcontroller in remote control, as exemplified by the BASIC Stamp, and the application of ready-made type-approved 418MHz radio transmitter and receiver modules to remote control systems.

160 pages **Order code BP413** £6.49

### PRACTICAL ELECTRONIC MODEL RAILWAY PROJECTS R. A. Penfold

The aim of this book is to provide the model railway enthusiast with a number of useful but reasonably simple projects that are easily constructed from readily available components. Stripboard layouts and wiring diagrams are provided for each project. The projects covered include: constant voltage controller; pulsed controller; pushbutton pulsed controller; pulsed controller with simulated inertia, momentum and braking; automatic signals; steam whistle sound effect; two-tone horn sound effect; automatic two-tone horn effect; automatic chuffer.

The final chapter covers the increasingly popular subject of using a computer to control a model railway layout, including circuits for computer-based controllers and signalling systems.

151 pages **Order code BP384** £5.49

### A PRACTICAL INTRODUCTION TO SURFACE MOUNT DEVICES Bill Mooney

This book takes you from the simplest possible starting point to a high level of competence in handworking with surface mount devices (SMD's). The wider subject of SM technology is also introduced, so giving a feeling for its depth and fascination.

Subjects such as p.c.b. design, chip control, soldering techniques and specialist tools for SM are fully explained and developed as the book progresses. Some useful constructional projects are also included.

Whilst the book is mainly intended as an introduction it is also an invaluable reference book, and the browser should find it engrossing.

120 pages **Order code BP411** £5.49

### FAULT-FINDING ELECTRONIC PROJECTS

R. A. Penfold

Starting with mechanical faults such as dry joints, short-circuits etc. coverage includes linear circuits, using a meter to make voltage checks, signal tracing techniques and fault finding on logic circuits. The final chapter covers ways of testing a wide

# DIRECT BOOK SERVICE

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

**FOR A FURTHER SELECTION OF BOOKS  
SEE THE NEXT TWO ISSUES OF EPE.**

**All prices include UK postage**

range of electronic components, such as resistors, capacitors, operational amplifiers, diodes, transistors, SCRs and triacs, with the aid of only a limited amount of test equipment.

The construction and use of a Tristate Continuity Tester, a Signal Tracer, a Logic Probe and a CMOS Tester are also included.

136 pages **Order code BP391** £5.49

### TEST EQUIPMENT CONSTRUCTION

R. A. Penfold

This book describes in detail how to construct some simple and inexpensive but extremely useful, pieces of test equipment. Stripboard layouts are provided for all designs, together with wiring diagrams where appropriate, plus notes on construction and use.

The following designs are included:- AF Generator, Capacitance Meter, Test Bench Amplifier, AF Frequency Meter, Audio Multivoltmeter, Analogue Probe, High Resistance Voltmeter, CMOS Probe, Transistor Tester, TTL Probe. The designs are suitable for both newcomers and more experienced hobbyists.

104 pages **Order code BP248** £4.49

## AUDIO AND MUSIC

### VALVE & TRANSISTOR AUDIO AMPLIFIERS John Linsley Hood

This is John Linsley Hood's greatest work yet, describing the milestones that have marked the development of audio amplifiers since the earliest days to the latest systems. Including classic amps with valves at their heart and exciting new designs using the latest components, this book is the complete world guide to audio amp design.

Contents: Active components; Valves or vacuum tubes; Solid-state devices; Passive components; Inductors and transformers; Capacitors, Resistors, Switches and electrical contacts; Voltage amplifier stages using valves; Valve audio amplifier layouts; Negative feedback; Valve operated power amplifiers; Solid state voltage amplifiers; Early solid-state audio amplifiers; Contemporary power amplifier designs; Preamplifiers; Power supplies (PSUs); Index.

250 pages **Order code NE24** £21.99

### AUDIO AMPLIFIER PROJECTS R. A. Penfold

A wide range of useful audio amplifier projects, each project features a circuit diagram, an explanation of the circuit operation and a stripboard layout diagram. All constructional details are provided along with a shopping list of components, and none of the designs requires the use of any test equipment in order to set up properly. All the projects are designed for straightforward assembly on simple circuit boards.

Circuits include: High impedance mic preamp, Low impedance mic preamp, Crystal mic preamp, Guitar and GP preamplifier, Scratch and rumble filter, RIAA preamplifier, Tape preamplifier, Audio limiter, Bass and treble tone controls, Loudness filter, Loudness control, Simple graphic equaliser, Basic audio mixer, Small (300mW) audio power amp, 6 watt audio power amp, 20/32 watt power amp and power supply, Dynamic noise limiter.

A must for audio enthusiasts with more sense than money!

116 pages **Order code PC113** £10.95

## RADIO / TV VIDEO

### ELECTRONIC PROJECTS FOR VIDEO ENTHUSIASTS R. A. Penfold

This book provides a number of practical designs for video accessories that will help you get the best results from your camcorder and VCR. All the projects use inexpensive components that are readily available, and they are easy to construct. Full construction details are provided, including stripboard layouts and wiring diagrams. Where appropriate, simple setting up procedures are described in detail; no test equipment is needed.

The projects covered in this book include: Four channel audio mixer, Four channel stereo mixer, Dynamic noise limiter (DNL), Automatic audio fader, Video faders, Video wipers, Video crispener, Mains power supply unit.

109 pages **Order code BP356** £5.45

### SETTING UP AN AMATEUR RADIO STATION I. D. Poole

The aim of this book is to give guidance on the decisions which have to be made when setting up any amateur radio or short wave listening station. Often the experience which is needed is learned by one's mistakes, however, this can be expensive. To help overcome this, guidance is given on many aspects of setting up and running an efficient station. It then proceeds to the steps that need to be taken in gaining a full transmitting licence.

Topics covered include: The equipment that is needed; Setting up the shack; Which aerials to use; Methods of construction; Preparing for the licence.

An essential addition to the library of all those taking their first steps in amateur radio.

86 pages **Order code BP300** £4.45

### EXPERIMENTAL ANTENNA TOPICS H. C. Wright

Although nearly a century has passed since Marconi's first demonstration of radio communication, there is still research and experiment to be carried out in the field of antenna design and behaviour.

The aim of the experimenter will be to make a measurement or confirm a principle, and this can be done with relatively fragile, short-life apparatus. Because of this, devices described in this book make liberal use of cardboard, cooking foil, plastic bottles, cat food tins, etc. These materials are, in general, cheap to obtain and easily worked with simple tools, encouraging the trial-and-error philosophy which leads to innovation and discovery.

Although primarily a practical book with text closely supported by diagrams, some formulae which can be used by straightforward substitution and some simple graphs have also been included.

72 pages **Order code BP278** £4.00

### 25 SIMPLE INDOOR AND WINDOW AERIALS E. M. Noel

Many people live in flats and apartments or other types of accommodation where outdoor aerials are prohibited, or a lack of garden space etc. prevents aerials from being erected. This does not mean you have to forgo shortwave-listening, for even a 20-foot length of wire stretched out along the skirting board of a room can produce acceptable results. However, with some additional effort and experimentation one may well be able to improve performance further.

This concise book tells the story, and shows the reader how to construct and use 25 indoor and window aerials that the author has proven to be sure performers. Much information is also given on shortwave bands, aerial directivity, time zones, dimensions etc.

50 pages **Order code BP136** £2.25

# CIRCUITS AND DESIGN

## AN INTRODUCTION TO PIC MICROCONTROLLERS

Robert Penfold

Designing your own PIC based projects may seem a daunting task, but it is really not too difficult providing you have some previous experience of electronics.

The PIC processors have plenty of useful features, but they are still reasonably simple and straightforward to use. This book should contain everything you need to know.

Topics covered include: the PIC register set; numbering systems; bitwise operations and rotation; the PIC instruction set; using interrupts; using the analogue to digital converter; clock circuits; using the real time clock counter (RTCC); using subroutines; driving seven segment displays.

166 pages

Order code BP394

£6.49

## PRACTICAL OSCILLATOR CIRCUITS

A. Flind

Extensive coverage is given to circuits using capacitors and resistors to control frequency. Designs using CMOS, timer i.c.s and op.amps are all described in detail, with a special chapter on "waveform generator" i.c.s. Reliable "white" and "pink" noise generator circuits are also included.

Various circuits using inductors and capacitors are covered, with emphasis on stable low frequency generation. Some of these are amazingly simple, but are still very useful signal sources.

Crystal oscillators have their own chapter. Many of the circuits shown are readily available special i.c.s for simplicity and reliability, and offer several output frequencies. Finally, complete constructional details are given for an audio sinewave generator.

133 pages

Order code BP393

£5.49

## PRACTICAL ELECTRONIC CONTROL PROJECTS

Owen Bishop

Explains electronic control theory in simple, non-mathematical terms and is illustrated by 30 practical designs suitable for the student or hobbyist to build. Shows how to use sensors as input to the control system, and how to provide output to lamps, heaters, solenoids, relays and motors.

Computer based control is explained by practical examples that can be run on a PC. For stand-alone systems, the projects use microcontrollers, such as the inexpensive and easy-to-use Stamp BASIC microcontroller.

198 pages

Temporarily out of print

## PRACTICAL ELECTRONICS HANDBOOK -

Fifth Edition, Ian Sinclair

Contains all of the everyday information that anyone working in electronics will need.

It provides a practical and comprehensive collection of circuits, rules of thumb and design data for professional engineers, students and enthusiasts, and therefore enough background to allow the understanding and development of a range of basic circuits.

Contents: Passive components, Active discrete components, Circuits, Linear I.C.s, Energy conversion components, Digital I.C.s, Microprocessors and microprocessor

systems, Transferring digital data, Digital-analogue conversions, Computer aids in electronics, Hardware components and practical work, Microcontrollers and PLCs, Digital broadcasting, Electronic security.

440 pages

Order code NE21

£16.99

## COIL DESIGN AND CONSTRUCTIONAL MANUAL

B. B. Babani

A complete book for the home constructor on "how to make" RF, IF, audio and power coils, chokes and transformers. Practically every possible type is discussed and calculations necessary are given and explained in detail. Although this book is now twenty years old, with the exception of toroids and pulse transformers little has changed in coil design since it was written.

96 pages

Order code 160

£4.49

## OPTOELECTRONICS CIRCUITS MANUAL

R. M. Marston

A useful single-volume guide to the optoelectronics device user, specifically aimed at the practical design engineer, technician, and the experimenter, as well as the electronics student and amateur. It deals with the subject in an easy-to-read, down-to-earth, and non-mathematical yet comprehensive manner, explaining the basic principles and characteristics of the best known devices, and presenting the reader with many practical applications and over 200 circuits. Most of the i.c.s and other devices used are inexpensive and readily available types, with universally recognised type numbers.

182 pages

Order code NE14

£15.99

## OPERATIONAL AMPLIFIER USER'S HANDBOOK

R. A. Penfold

The first part of this book covers standard operational amplifier based "building blocks" (integrator, precision rectifier, function generator, amplifiers, etc), and considers the ways in which modern devices can be used to give superior performance in each one. The second part describes a number of practical circuits that exploit modern operational amplifiers, such as high slew-rate, ultra low noise, and low input offset devices. The projects include: Low noise tape preamplifier, low noise RIAA preamplifier, audio power amplifiers, d.c. power controllers, opto-isolator audio link, audio millivolt meter, temperature monitor, low distortion audio signal generator, simple video fader, and many more.

120 pages

Order code BP335

£5.45

## A BEGINNERS GUIDE TO CMOS DIGITAL ICs

R. A. Penfold

Getting started with logic circuits can be difficult, since many of the fundamental concepts of digital design tend to seem rather abstract, and remote from obviously useful applications. This book covers the basic theory of digital electronics and the use of CMOS integrated circuits, but does not lose sight of the fact that digital electronics has numerous "real world" applications.

The topics covered in this book include: the basic concepts of logic circuits; the functions of gates, inverters and other logic "building blocks"; CMOS logic i.c. characteristics, and their advantages in practical circuit design; oscillators and monostables (timers); flip/flops, binary dividers and binary counters; decade counters and display drivers.

119 pages

Order code BP333

£5.45

# AUDIO AND MUSIC

## INTRODUCTION TO DIGITAL AUDIO

(Second Edition) Ian Sinclair

The compact disc (CD) was the first device to bring digital audio methods into the home.

This development has involved methods and circuits that are totally alien to the technician or keen amateur who has previously worked with audio circuits. The principles and practices of digital audio owe little or nothing to the traditional linear circuits of the past, and are much more comprehensible to today's computer engineer than the older generation of audio engineers.

This book is intended to bridge the gap of understanding for the technician and enthusiast. The principles and methods are explained, but the mathematical background and theory is avoided, other than to state the end product.

128 pages

Order code PC102

£8.95

## PROJECTS FOR THE ELECTRIC GUITAR

J. Chatwin

This book is for anyone interested in the electric guitar. It explains how the electronic functions of the instrument work together, and includes information on

the various pickups and transducers that can be fitted. There are complete circuit diagrams for the major types of instrument, as well as a selection of wiring modifications and pickup switching circuits. These can be used to help you create your own custom wiring.

Along with the electric guitar, sections are also included relating to acoustic instruments. The function of specialised piezoelectric pickups is explained and there are detailed instructions on how to make your own contact and bridge transducers. The projects range from simple preamps and tone boosters, to complete active controls and equaliser units.

92 pages

Order code BP358

£5.45

## VALVE AMPLIFIERS

Second Edition, Morgan Jones

This book allows those with a limited knowledge of the field to understand both the theory and practice of valve audio amplifier design, such that they can analyse and modify circuits, and build or restore an amplifier. Design principles and construction techniques are provided so readers can devise and build from scratch, designs that actually work.

The second edition of this popular book builds on its main strength - exploring and illustrating theory with practical applications. Numerous new sections include: output transformer problems; heater regulators; phase splitter analysis; and component technology. In addition to the numerous amplifier and preamplifier circuits, three major new designs are included: a low-noise single-ended LP stage, and a pair of high voltage amplifiers for driving electrostatic transducers directly - one for headphones, one for loudspeakers.

488 pages

Order code NE33

£26.99

## VALVE RADIO AND AUDIO REPAIR HANDBOOK

Chas Miller

This book is not only an essential read for every professional working with antique radio and gramophone equipment, but also dealers, collectors and valve technology enthusiasts the world over. The emphasis is firmly on the practicalities of repairing and restoring, so technical content is kept to a minimum, and always explained in a way that can be followed by readers with no background in electronics. Those who have a good grounding in electronics, but wish to learn more about the practical aspects, will benefit from the emphasis given to hands-on repair work, covering mechanical as well as electrical aspects of servicing. Repair techniques are also illustrated throughout.

A large reference section provides a range of information compiled from many contemporary sources, and includes specialist dealers for valves, components and complete receivers.

288 pages

Order code NE34

£20.99

## LOUDSPEAKERS FOR MUSICIANS

Vivan Capel

This book contains all that a working musician needs to know about loudspeakers; the different types, how they work, the most suitable for different instruments, for cabaret work, and for vocals. It gives tips on constructing cabinets, wiring up, when and where to use wadding, and when not to, what fittings are available, finishing, how to ensure they travel well, how to connect multi-speaker arrays and much more.

Ten practical enclosure designs with plans and comments are given in the last chapter, but by the time you've read that far you should be able to design your own!

164 pages

Order code BP297

£5.49

## BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £1 per book. For the rest of the world airmail add £2 per book. Send a PO, cheque, international money order (£ sterling only) made payable to Direct Book Service or card details, Visa, Mastercard, Amex, Diners Club or Switch to: DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LIMITED, 408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND.

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery - more for overseas orders. Please check price and availability (see latest issue of Everyday Practical Electronics) before ordering from old lists.

For a further selection of books see the next two issues of EPE.

Tel 01202 873872 Fax 01202 874562. E-mail: [dbs@epemag.wimbome.co.uk](mailto:dbs@epemag.wimbome.co.uk)

Order from our online shop at: [www.epemag.wimbome.co.uk/shopdoor.htm](http://www.epemag.wimbome.co.uk/shopdoor.htm)

## BOOK ORDER FORM

Full name: .....

Address: .....

..... Post code: ..... Telephone No: .....

Signature: .....

I enclose cheque/PO payable to DIRECT BOOK SERVICE for £ .....

Please charge my card £ ..... Card expiry date: .....

Card Number ..... Switch Issue No. ....

Please send book order codes: .....

Please continue on separate sheet of paper if necessary

Everyday Practical Electronics reaches twice as many UK readers as any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last seventeen years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. VAT must be added. Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, Mill Lodge, Mill Lane, Thorpe-le-Soken, Essex CO16 0ED. Phone/Fax (01255) 861161.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

Valve Output Transformers: Single ended 50mA, £4.50; push/pull 50W, £38; 100W, £53. Mains Transformers: Sec 220V 30mA 6V 1A, £3; 250V 60mA 6V 2A, £5; 250V 80mA 6V 2A, £6. High Voltage Caps: 50µF 350V, 68µF 500V, 150µF 385V, 220µF 400V, 330µF 400V, 470µF 385V, all £3 ea., 32+32µF 450V £5, 4µF 800V oil filled paper block £10, 10H 200mA choke £14. Postage extra.  
Record Decks and Spares: BSR, Garrard, Goldring, motors, arms, wheels, headshells, spindles, etc. Send or phone your

**RADIO COMPONENT SPECIALISTS**

for quote.  
337 WHITEHORSE ROAD, CROYDON  
SURREY, CR0 2HS. Tel: (020) 8684 1666

**Test Equipment**



**Service Manuals.**

Contact  
[www.cooke-int.com](http://www.cooke-int.com)  
Tel: +44 01243 55 55 90

**IS THIS YOUR COMPUTER?**

Random Crashes, Data Loss,  
Premature Component Failure



The demand for a faster PC is turning up the heat inside your PC. Monitor and protect it with the PC Thermometer. Features: Temperature display, Fan control & monitor, Audible alarm, Fits Drive Bay.

**Circuit Innovations**  
24 Leasmires Avenue  
Easingwold  
York YO61 3DU  
[www.circuit-innovations.co.uk](http://www.circuit-innovations.co.uk)  
Other Design, Manufacturing & PCB Services too!

**Z88** NOW AVAILABLE WITH  
128K AND 512K - OZ4


**ALSO SPECTRUM  
AND QL PARTS**

**W. N. RICHARDSON & CO.**  
PHONE/FAX 01494 871319  
E-mail: [wnr@compuserve.com](mailto:wnr@compuserve.com)  
RAVENSMED, CHALFONT ST PETER, BUCKS, SL9 0NB

**X-10® Home Automation**  
We put you in control™

Why tolerate when you can automate?  
An extensive range of 230V X-10 products and starter kits available. Uses proven Power Line Carrier technology, no wires required.  
Products Catalogue available Online.  
Worldwide delivery.

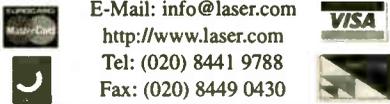**Laser Business Systems Ltd.**  
E-Mail: [info@laser.com](mailto:info@laser.com)  
<http://www.laser.com>  
Tel: (020) 8441 9788  
Fax: (020) 8449 0430



**BTEC ELECTRONICS  
TECHNICIAN TRAINING**

VCE ADVANCED ENGINEERING  
ELECTRONICS AND ICT  
HNC AND HND ELECTRONICS  
NVQ ENGINEERING AND IT  
Next course commences  
16th SEPTEMBER 2002  
FULL PROSPECTUS FROM

**LONDON ELECTRONICS COLLEGE**  
(Dept EPE) 20 PENYWERN ROAD  
EARLS COURT, LONDON SW5 9SU  
TEL: (020) 7373 8721

**2002 CATALOGUE**  
PLEASE SEND SAE FOR A FREE COPY TO

**FML ELECTRONICS**  
FREEPOST NEA 3627 BEDALE  
NORTH YORKSHIRE DL8 2BR  
TEL: 01677 425840

SPECIALIST SUPPLIERS OF SEMICONDUCTORS, RESISTORS,  
CAPACITORS AND OTHER ELECTRONIC COMPONENTS AT  
COMPETITIVE PRICES.

**OLIMEX**  
<http://www.olimex.com/pcb>

**PCB prototypes for \$26**

FR-4, 1.5 mm, 35/35 um copper,  
160x100 mm, double side, PTH,  
soldermask, component silkscreen  
production in 3-5 working days  
made in Bulgaria  
no import tax to Europe, UK and US

**THE BRITISH AMATEUR  
ELECTRONICS CLUB**

exists to help electronics enthusiasts by personal contact and through a quarterly Newsletter.  
For membership details, write to the Secretary:  
**Mr. M. P. Moses,**  
5 Park View, Cwmaman,  
Aberdare CF44 6PP  
Space donated by Everyday Practical Electronics

**Miscellaneous**

**FREE PROTOTYPE PRINTED CIRCUIT  
BOARDS!** Free prototype p.c.b. with quantity orders. Call Patrick on 028 9073 8897 for details. Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast BT5 4GX.

**EDUCATIONAL ELECTRONIC KITS,** GCSE, Physics, Hobbyist. 2 x 1st class stamps for catalogue. Electroteach, PO Box 2594, Cannock, WS12 4YH.

[www.electroteach.com](http://www.electroteach.com).

**PRINTED CIRCUIT BOARDS - QUICK SERVICE.** Prototype and production artwork raised from magazines or draft designs at low cost. PCBs designed from schematics. Production assembly, wiring and software programming. For details contact Patrick at Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast, BT5 4GX. Phone 028 9073 8897, Fax 028 9073 1802, Email [agar@argonet.co.uk](mailto:agar@argonet.co.uk).

**G.C.S.E. ELECTRONICS KITS,** at pocket money prices. S.A.E. for FREE catalogue. SIR-KIT Electronics, 52 Severn Road, Clacton, CO15 3RB. [www.geocities.com/sirkituk](http://www.geocities.com/sirkituk).

**VALVES AND ALLIED COMPONENTS IN STOCK** - please ring for free list. Valve equipment repaired. Geoff Davies (Radio). Phone 01788 574774.

**BACK ISSUES OF EVERYDAY PRACTICAL ELECTRONICS,** Oct. 1977 to Dec. 1990. Enquiries to [yymij@bigfoot.com](mailto:yymij@bigfoot.com). Tel. 01582 834840.

**EPE NET ADDRESSES**

**EPE FTP site:** <ftp://ftp.epemag.wimborne.co.uk>  
Access the FTP site by typing the above into your web browser, or by setting up an FTP session using appropriate FTP software, then go into quoted sub-directories:  
PIC-project source code files: /pub/PICS  
PIC projects each have their own folder; navigate to the correct folder and open it, then fetch all the files contained within. Do not try to download the folder itself!  
EPE text files: /pub/docs  
Basic Soldering Guide: solder.txt  
Ingenuity Unlimited submission guidance: lng\_unlt.txt  
New readers and subscribers info: epe\_info.txt  
Newsgroups or Usenet users advice: usenet.txt  
Ni-Cad discussion: nlcadfaq.zip and nlcad2.zip  
Writing for EPE advice: write4us.txt  
You can also enter the FTP site via the link at the top of the main page of our home site at:  
<http://www.epemag.wimborne.co.uk>  
Shop now on-line:  
[www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

Ensure you set your FTP software to ASCII transfer when fetching text files, or they may be unreadable.  
Note that any file which ends in .zip needs unzipping before use. Unzip utilities can be downloaded from:  
<http://www.winzip.com>  
Ensure you use the latest version

## TRAIN TODAY FOR A BETTER FUTURE

Now you can get the skills and qualifications you need for career success with an ICS Home Study Course. Learn in the comfort of your own home at the pace and times that suit you. ICS is the world's largest, most experienced home study school. Over the past 100 years ICS have helped nearly 10 million people to improve their job prospects. Find out how we can help YOU. Post or phone today for FREE INFORMATION on the course of your choice

Electrical Contracting & Installation  
Electrical Engineering  
C&G/ICS Basic Electronic Engineering  
C&G/ICS Basic Mechanical Engineering  
TV and Video Servicing  
Radio and Hi-Fi Servicing  
Refrigeration Heating & Air Conditioning  
Motorcycle Maintenance

**FREEPHONE 0500 581 557**

Or write to: International Correspondence Schools, FREEPOST 882, 8 Elliot Place, Clydeaway Skypark, Glasgow, G3 8BR. Tel: 0500 581 557 or Tel/Fax: Dublin 285 2533.

Please send me my Free Information on your Electronics Courses.

Mr/Ms/Ms/Miss (BLOCK CAPITALS PLEASE) \_\_\_\_\_ Date of Birth / /

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Occupation \_\_\_\_\_ Tel. No. \_\_\_\_\_

From time to time, we permit other carefully screened organisations to write to you about products and services. If you would prefer not to hear from such organisations please tick box:  Dept. ZEEVC1D2

## EPE TEACH-IN 2000 Now on CD-ROM

The whole of the 12-part *Teach-In 2000* series by John Becker (published in *EPE* Nov '99 to Oct 2000) is now available on CD-ROM. Plus the *Teach-In 2000* demonstration software covering all aspects of the series and Alan Winstanley's *Basic Soldering Guide* (including illustrations and *Desoldering*).

*Teach-in 2000* covers all the basic principles of electronics from Ohm's Law to Displays, including Op.Amps, Logic Gates etc. Each part has its own section on the interactive PC software where you can also change component values in the various on-screen demonstration circuits.

The series gives a hands-on approach to electronics with numerous breadboarded circuits to try out, plus a simple computer interface which allows a PC to be used as a basic oscilloscope.

**ONLY £12.45** including VAT and p&p

We accept Visa, Mastercard, Amex, Diners Club and Switch cards.

NOTE: This mini CD-ROM is suitable for use on any PC with a CD-ROM drive. It requires Adobe Acrobat Reader (available free from the Internet - [www.adobe.com/acrobat](http://www.adobe.com/acrobat))

### TEACH-IN 2000 CD-ROM ORDER FORM

Please send me ..... (quantity) TEACH-IN 2000 CD-ROM  
Price £12.45 (approx \$20) each - includes postage to anywhere in the world.

Name .....

Address .....

Post Code ..... Tel. ....

I enclose cheque/P.O./bank draft to the value of £ .....

Please charge my card £ .....

Card No. ....

Expiry Date ..... Switch Issue No. ....

SEND TO: **Everyday Practical Electronics, Wimborne Publishing Ltd.,**  
408 Wimborne Road East, Ferndown, Dorset BH22 9ND.  
Tel: 01202 873872. Fax: 01202 874562.  
E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)  
Online store: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)  
Payments must be by card or in £ Sterling - cheque or bank draft drawn on a UK bank.

## Watch Slides on TV.

Make videos of your slides. Digitise your slides (using a video capture card)  
"Liesgang diatv" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. More details see [www.diatv.co.uk](http://www.diatv.co.uk).  
£91.91 + VAT = £108.00



Board cameras all with 512 x 582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10V and 12V DC 150mA.  
47MIR size 60 x 36 x 27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye) £37.00 + VAT = £43.48  
30MP size 32 x 32 x 14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole £35.00 + VAT = £41.13  
40MC size 39 x 38 x 27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses £32.00 + VAT = £37.60  
Economy C mount lenses all fixed focus & fixed iris  
VSL1220F 12mm F1.6 12 x 15 degrees viewing angle £15.97 + VAT £18.76  
VSL4022F 4mm F1.22 63 x 47 degrees viewing angle £17.65 + VAT £20.74  
VSL6022F 6mm F1.22 42 x 32 degrees viewing angle £19.05 + VAT £22.38  
VSL8020F 8mm F1.22 32 x 24 degrees viewing angle £19.90 + VAT £23.38

## Better quality C Mount lenses

VSL1614F 16mm F1.6 30 x 24 degrees viewing angle £26.43 + VAT £31.06  
VWL813M 8mm F1.3 with iris 56 x 42 degrees viewing angle £77.45 + VAT = £91.00  
1206 surface mount resistors E12 values 10 ohm to 1M ohm  
100 of 1 value £1.00 + VAT 1000 of 1 value £5.00 + VAT

866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily  
£7.46 + VAT = £8.77



Please add £1.66 + vat = £1.95 postage & packing per order

## JPG Electronics

Shaws Row, Old Road, Chesterfield, S40 2RB.

Tel 01246 211202 Fax 01246 550959

Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

## ELECTRONICS SURPLUS CLEARANCE SALE

FLUKE HANDHELD DIGITAL MULTIMETER MODEL 8024B. Cancelled export order. Brand new and boxed but with original purchasing organisation's small identifying mark on case With test leads and handbook. List price £150. Our price £47.50. P&P £6.50.

A DIGITAL HANDHELD LCR METER. Measuring inductance, capacitance, resistance. LCD display. Range 2mH to 20H inductance. 2000pF to 200µF capacitance. 200 ohm to 20 megohm resistance. Brand new with test leads and manual. £44.00. P&P £3.50.

12V D.C. TO 240V A.C. 300WATT POWER INVERTER. Ideal for use in your caravan, car, boat, to run TV, lighting, fridges, recharge your mobile phone, etc. Compact size, brand new and boxed, fully guaranteed. £49.50, p&p £6.50.

250 ¼ watt metal/carbon film resistors	£1	<b>VALVE ASSOCIATED ITEMS</b>	
30 5mm red l.e.d.s	£1	5 High voltage capacitors, 0.1µF 1000V axial	£3
30 BCY71	£1	5 0.05µF 600V axial	£3
30 BCY72	£1	50 Vintage carbon one watt resistors. Useful values	£3
30 BFX30	£1	15 100 ohm wirewound resistors. 3W	£1
30 BC640	£1	5 Valveholders, Octal, B7G, B9A (state which)	£2.50
30 BC558	£1	3 68µF 450V wkg electrolytics, 1¼in. x ¼in. dia.	£2.50
10 OC42 Military spec	£2.50	radial	
30 2N4393	£1	3 47µF 400V wkg electrolytic, ¼in. x ¼in. dia.	£2.50
10 555 Timer chips	£1	radial	
4 IEC 3-pin mains input chassis socket	£1	4 22µF 250V wkg electrolytic, 1in. x ¼in. dia. axial	£1
		4 47µF mixed dielectric axial capacitors, 250V wkg	£1
		5 10µF 400V electrolytic, 1in. x ¼in. dia. axial	£2
		5 Terminal block 4 screw terminals, 2¼in. length with fixing holes	£1

### BOOKS:

ELECTRIC UFOs by Albert Budden. The effects of electromagnetic pollution, UFOs, fireballs, abnormal states. 286 pages, photos. £10.

MULLARD HIGH QUALITY SOUND REPRODUCTION. A constructional manual for building valve amplifiers, pre-amps, tuners, circa 1958. 48 large format pages, facsimile copy. £12.50.

MULLARD VALVE DATA AND EQUIVALENTS HANDBOOK. Over 300 pages of valve data, base connections, characteristics and operating conditions for Mullard valves and their equivalent makes. Facsimile reprint. £16.50, p&p £2.25.

Send 2 first class stamps for the *Electronic Surplus Trader* - our latest catalogue full of component bargains, valves, high voltage capacitors, obsolete semiconductors etc.

P&P £1.60 under £10. Over Free unless otherwise stated.

## (Dept E) CHEVET SUPPLIES LTD

157 Dickson Road, BLACKPOOL FY1 2EU  
Tel: (01253) 751858. Fax: (01253) 302979

E-mail: [chevet@globalnet.co.uk](mailto:chevet@globalnet.co.uk) Telephone Orders Accepted



# N. R. BARDWELL LTD (Est. 1948)

100	Signal Diodes 1N4148	£1.00
75	Rectifier Diodes 1N4001	£1.00
50	Rectifier Diodes 1N4007	£1.00
10	W01 Bridge Rectifiers	£1.00
10	555 Timer I.C.s	£1.00
4	741 Op Amps	£1.00
50	Assorted Zener Diodes 400mW	£1.00
12	Assorted 7-segment Displays	£1.00
25	5mm I.e.d.s, red, green or yellow	£1.00
25	3mm I.e.d.s, red, green or yellow	£1.00
75	5mm I.e.d.s, green, 6-5mm legs	£1.00
50	Axial I.e.d.s, 2mcd red Diode Package	£1.00
25	Asstd. High Brightness I.e.d.s, var cols	£1.00
20	BC182 Transistors	£1.00
25	BC212 Transistors	£1.00
30	BC237 Transistors	£1.00
20	BC327 Transistors	£1.00
30	BC328 Transistors	£1.00
30	BC547 Transistors	£1.00
20	BC547B Transistor	£1.00
30	BC548 Transistors	£1.00
30	BC549 Transistors	£1.00
25	BC557 Transistors	£1.00
30	BC558 Transistors	£1.00
30	BC559 Transistors	£1.00
20	2N3904 Transistors	£1.00
100	1nf 50V wkg Axial Capacitors	£1.00
100	4N7 50V wkg Axial Capacitors	£1.00
80	Asstd capacitors electrolytic	£1.00
80	Asstd. capacitors 1nF to 1µF	£1.00

200	Asstd. disc ceramic capacitors	£1.00
50	Asstd. Sikel Presets (am, stand, cermet)	£1.00
50	Asstd. RF chokes (inductors)	£1.00
50	Asstd. grommets	£1.00
80	Asstd. solder tags, p/conn, terminals	£1.00
10	Asstd. crystals - plug in	£1.00
8	Asstd. di switches	£1.00
20	Miniature slide switches sp/co	£1.00
100	Asstd. beads (ceramic, teflon, fish spine)	£1.00
30	Asstd. di sockets up to 40 way	£1.00
10	TV coax plugs, plastic	£1.00
40	metres very thin connecting wire, red	£1.00
20	1in. glass reed switches	£1.00
100	Any one value 1/4W 5% of resistors range	£0.45
1R to 10M		£0.45
10	7812 Voltage Regulators	£1.00
300	Asstd. resistors, 1/4W/1/2W, mostly on tapes	£1.00
8	Asstd. push-button switches, multi-bank, multi-pole	£1.00

288 Abbeydale Road, Sheffield S7 1FL  
 Phone: 0114 255 2886 ★ Fax: 0114 255 5039  
 e-mail: sales@bardwells.co.uk ★ Web: www.bardwells.co.uk  
 Prices include VAT. Postage £1.65  
 44p stamp for lists or disk  
**POs, Cheques and Credit Cards accepted**



## DIGITAL TEST METER

Built-in transistor test socket and diode test position.  
 DC volts 200mV to 1000V.  
 AC volts 200V to 750V.  
 DC current 200mA to 10A.  
 Resistance 200 ohms to 2000K ohms.

**£5.99** incl. VAT

SEE OUR WEB PAGES FOR MORE COMPONENTS AND SPECIAL OFFERS  
[www.bardwells.co.uk](http://www.bardwells.co.uk)

## Bowood Electronics Ltd

### Suppliers of Electronic Components

Batteries, Buzzers, Capacitors, Connectors, Diodes, Cases, Ferrites, Fuses, Heatshrink, ICs, Inverters, L.E.D.s, P.C.B., Potentiometers, Power Supplies, Presets, Rectifiers, Relays, Resistors, Soldering Equipment, Stripboard, Switches, Test Meters, Thermistors, Thyristors, Tools, Transistors, Triacs . . .

**Catalogue available NOW**

Send 41p stamp or visit our website

Website: <http://www.bowood-electronics.co.uk>  
 sales@bowood-electronics.co.uk



Mail Order Only  
 7 Bakewell Road, Baslow, Derbyshire, DE45 1RE, UK  
 Telephone/Fax: 01246 583777

## SHERWOOD ELECTRONICS

### FREE COMPONENTS

Buy 10 x £1 Special Packs and choose another one FREE

SP1	15 x 5mm Red LEDs	SP135	6 x Miniature slide switches
SP2	12 x 5mm Green LEDs	SP136	3 x BFY50 transistors
SP3	12 x 5mm Yellow LEDs	SP137	4 x W005 1.5A bridge rectifiers
SP6	15 x 3mm Red LEDs	SP138	20 x 2.2/63V radial elect. caps.
SP7	12 x 3mm Green LEDs	SP140	3 x W04 1.5A bridge rectifiers
SP8	10 x 3mm Yellow LEDs	SP142	2 x CMOS 4017
SP10	100 x 1N4148 diodes	SP143	5 Pairs min. crocodile clips (Red & Black)
SP11	30 x 1N4001 diodes	SP145	6 x ZTX300 transistors
SP12	30 x 1N4002 diodes	SP146	10 x 2N3704 transistors
SP20	20 x BC184 transistors	SP147	5 x Stripboard 9 strips x 25 holes
SP21	20 x BC212 transistors	SP151	4 x 8mm Red LEDs
SP23	20 x BC549 transistors	SP152	4 x 8mm Green LEDs
SP24	4 x CMOS 4001	SP153	4 x 8mm Yellow LEDs
SP25	4 x 555 timers	SP154	15 x BC548 transistors
SP26	4 x 741 Op.Amps	SP156	3 x Stripboard, 14 strips x 27 holes
SP28	4 x CMOS 4011	SP160	10 x 2N3904 transistors
SP29	3 x CMOS 4013	SP161	10 x 2N3906 transistors
SP34	20 x 1N914 diodes	SP165	2 x LF351 Op.Amps
SP36	25 x 10/25V radial elect. caps.	SP166	20 x 1N4003 diodes
SP37	12 x 100/35V radial elect. caps.	SP167	6 x BC107 transistors
SP39	10 x 470/16V radial elect. caps.	SP168	6 x BC108 transistors
SP40	15 x BC237 transistors	SP172	4 x Standard slide switches
SP41	20 x Mixed transistors	SP175	20 x 1/63V radial elect. caps.
SP42	200 x Mixed 0.25W C.F. resistors	SP177	10 x 1A 20mm quick blow fuses
SP47	5 x Min. PB switches	SP182	20 x 4.7/63V radial elect. caps.
SP49	4 x 5 metres stranded core wire	SP183	20 x BC547 transistors
SP102	20 x 8-pin DIL sockets	SP187	15 x BC239 transistors
SP103	15 x 14-pin DIL sockets	SP189	4 x 5 metres solid core wire
SP104	15 x 16-pin DIL sockets	SP192	3 x CMOS 4066
SP109	15 x BC557 transistors	SP193	20 x BC213 transistors
SP112	4 x CMOS 4093	SP195	3 x 10mm Yellow LEDs
SP115	3 x 10mm Red LEDs	SP197	6 x 20 pin DIL sockets
SP116	3 x 10mm Green LEDs	SP198	5 x 24 pin DIL sockets
SP124	20 x Assorted ceramic disc caps	SP199	5 x 2.5mm mono jack plugs
SP126	8 x Battery clips - 4 ea. PP3 + PP9	SP200	5 x 2.5mm mono jack sockets
SP130	100 x Mixed 0.5W C.F. resistors		
SP131	2 x TL071 Op.Amps		
SP133	20 x 1N4004 diodes		
SP134	15 x 1N4007 diodes		

RESISTOR PACKS - C.Film	
RP3	5 each value - total 365 0.25W £3.00
RP7	10 each value - total 730 0.25W £4.25
RP10	1000 popular values 0.25W £6.15
RP4	5 each value-total 365 0.5W £4.00
RP8	10 each value-total 730 0.5W £6.65
RP11	1000 popular values 0.5W £8.40

2002 Catalogue now available £1 inc. P&P or FREE with first order.  
 P&P £1.25 per order. NO VAT  
 Orders to:  
**Sherwood Electronics,**  
 7 Williamson St., Mansfield,  
 Notts. NG19 6TD.

## ADVERTISERS INDEX

N. R. BARDWELL	384
BITZ TECHNOLOGY	337
B.K. ELECTRONICS	Cover (iv)/349
BOWOOD ELECTRONICS	384
BRUNNING SOFTWARE	355
BULL ELECTRICAL	Cover (ii)
CHEVET SUPPLIES	383
CRICKLEWOOD ELECTRONICS	339
CROWNHILL ASSOCIATES	321
DISPLAY ELECTRONICS	306
ESR ELECTRONIC COMPONENTS	314
FOREST ELECTRONIC DEVELOPMENTS	334
GREENWELD	361
ICS	383
INNTACT ELECTRONICS	361
JPG ELECTRONICS	383
LABCENTER	Cover (iii)
MAGENTA ELECTRONICS	312/313
MILFORD INSTRUMENTS	324
NATIONAL COLLEGE OF TECHNOLOGY	361
PICO TECHNOLOGY	352
QUASAR ELECTRONICS	308/309
SHERWOOD ELECTRONICS	384
SKY ELECTRONICS	361
SQUIRES	339
STEWART OF READING	339

ADVERTISEMENT MANAGER: PETER J. MEW

ADVERTISEMENT OFFICES:

EVERYDAY PRACTICAL ELECTRONICS, ADVERTISEMENTS,  
 MILL LODGE, MILL LANE, THORPE-LE-SOKEN,  
 ESSEX CO16 0ED.

Phone/Fax: (01255) 861161

For Editorial address and phone numbers see page 315

**SPECIAL  
READER -  
SEE WEBSITE  
FOR DETAILS**

# PROTEUS

## VSM



Virtual System Modelling

Build It In Cyberspace

[www.labcenter.co.uk](http://www.labcenter.co.uk)

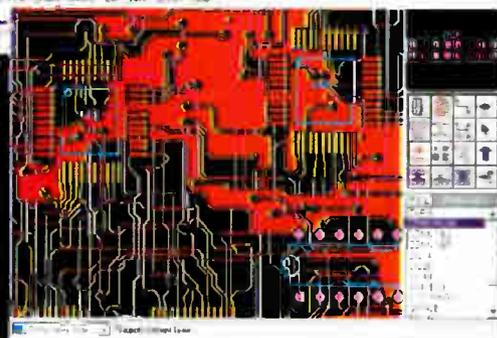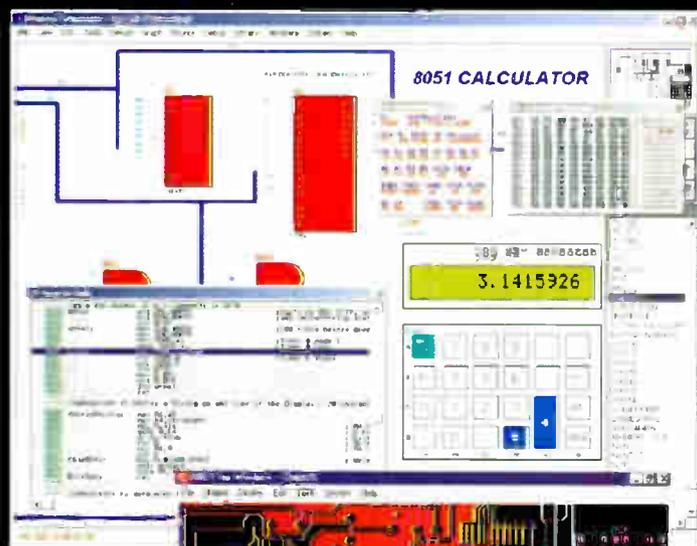**Develop and test complete micro-controller designs without building a physical prototype. PROTEUS VSM simulates the CPU and any additional electronics used in your designs. And it does so in real time. \***

- CPU models for PIC and 8051 and series micro-controllers available now. 68HC11 coming soon. More CPU models under development. See website for latest info.
- Interactive device models include LCD displays, RS232 terminal, universal keypad plus a range of switches, buttons, pots, LEDs, 7 segment displays and much more.
- Extensive debugging facilities including register and memory contents, breakpoints and single step modes.
- Source level debugging supported for selected development tools.
- Integrated 'make' utility - compile and simulate with one keystroke.
- Over 4000 standard SPICE models included. Fully compatible with manufacturers' SPICE models.
- DLL interfaces provided for application specific models.
- Based on SPICE3F5 mixed mode circuit simulator.
- CPU and interactive device models are sold separately - build up your VSM system in affordable stages.
- ARES Lite PCB Layout also available.



**labcenter**  
Electronics

\*E.g. PROTEUS VSM can simulate an 8051 clocked at 12MHz on a 300MHz Pentium II.

Write, phone or fax for your free demo CD - or email [info@labcenter.co.uk](mailto:info@labcenter.co.uk).  
Tel: 01756 753440. Fax: 01756 752857. 53-55 Main St, Grassington. BD23 5AA.



**POWER AMPLIFIER MODULES-LOUDSPEAKERS-MIXERS  
19 INCH STEREO AMPLIFIERS-ACTIVE CROSS/OVERS.**

\* PRICES INCLUDE V.A.T.  
\* PROMPT DELIVERY

**OMP MOS-FET POWER AMPLIFIERS  
HIGH POWER, TWO CHANNEL 19 INCH RACK**

10,000's  
SOLD  
TO PRO  
USERS



**THE RENOWNED MXF SERIES OF POWER AMPLIFIERS**

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)  
MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS ARE R.M.S. INTO 4 OHMS, WITH BOTH CHANNELS DRIVEN  
FEATURES:- \* Independent power supplies with two toroidal transformers  
\* Twin L.E.D. Vu Meters \* Level controls \* Illuminated on/off switch \* Jack / XLR inputs  
\* Speakon Outputs \* Standard 775mv inputs \* Open and Short circuit proof \* Latest Mos-Fets  
for stress free delivery into virtually any load \* High slew rate \* Very low distortion \* Aluminium  
cases \* MXF600 & MXF900 fan cooled with D.C. Loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC

SIZES:-	MXF200 W19"	D11"	H3 1/2"	(2U)
	MXF400 W19"	D12"	H5 1/2"	(3U)
	MXF600 W19"	D13"	H5 1/2"	(3U)
	MXF900 W19"	D14"	H5 1/2"	(3U)

PRICES:- MXF200 £175.00 MXF400 £233.85  
MXF600 £329.00 MXF900 £449.15  
SPECIALIST CARRIER DEL £12.50 Each



**ibl FLIGHTCASED  
LOUDSPEAKERS**

A new range of quality loudspeakers, designed to take advantage of latest loudspeaker technology and enclosure designs. All models utilise high quality studio cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands. The FC15-300 incorporates a large 16 X 6 inch horn. All cabinets are fitted with the latest Speakon connectors for your convenience and safety. Five models to choose from.

WEDGEMONITOR



PLEASE NOTE:- POWER RATINGS  
QUOTED ARE IN WATTS R.M.S. FOR  
EACH INDIVIDUAL CABINET ALL  
ENCLOSURES ARE 8 OHMS

15-15 Inch speaker  
12-12 Inch speaker

- ibl FC15-300 WATTS Freq Range 35Hz-20kHz, Sens 101dB, Size H695 W502 D415mm  
Price:- £299.00 per pair
- ibl FC12-300 WATTS Freq Range 45Hz-20kHz, Sens 96dB, Size H600 W405 D300mm  
Price:- £249.00 per pair
- ibl FC12-200 WATTS Freq Range 40Hz-20kHz, Sens 97dB, Size H600 W405 D300mm  
Price:- £199.00 per pair
- ibl FC12-100 WATTS Freq Range 45Hz-20kHz, Sens 100dB, Size H546 W380 D300mm  
Price:- £179.00 per pair
- ibl WM12-200 WATTS Freq Range 40Hz-20kHz, Sens 97dB, Size H418 W600 D385mm  
Price:- £125.00 Each

SPECIALIST CARRIER DEL:- £12.50 per pair, wedge monitor £7.00 each  
Optional Metal Stands PRICE:- £49.00 per pair Delivery:- £6.00

**CATALOGUE 2001 2002**

Robots  
Test & Teals  
Electronic Kits  
The Sky's The Limit  
Catalogue  
Communication  
Security  
Accessories

**B.K. Electronics**  
Unit 1, Comet Way, Southend-on-Sea, Essex, SS2 6TR  
Tel:- 01702-527572 Fax:- 01702-420243  
E-Mail: sales@bkelec.com Web Site: www.bkelec.com

FREE Our Sky over 3000 items  
The catalogue is free with any order placed from this advert  
and to personal callers or £3.00 to cover P&P if ordered by mail.  
This is a fully refundable gift you will love.

**100 WATT ACTIVE SUB BASS AMPLIFIER PANEL**



AN ACTIVE SUB BASS AMPLIFIER WITH A TRUE 100W RMS OUTPUT. SUPERB CONSTRUCTION WITH THE FACILITIES TO INTEGRATE SEEMLESSLY INTO MOST HI-FI OR HOME CINEMA SETUPS. USE THIS PANEL PLUS ONE OF OUR LOUDSPEAKERS TO MAKE YOUR OWN SUB WOOFER THAT WILL MATCH OR BEAT MOST COMMERCIALY AVAILABLE SUB WOOFERS.

FEATURES:- \* 100W RMS INTO 8 OHMS \* HIGH AND LOW LEVEL INPUTS \* TOROIDAL TRANSFORMER \* SHORT CIRCUIT PROTECTION \* D.C. SPEAKER PROTECTION \* FREQUENCY ROLL OFF, LOWER 10Hz, UPPER 60Hz TO 240Hz (FULLY ADJUSTABLE) \* AC3 COMPATIBLE FILTER CAN BE BYPASSED FOR 5-1 FORMATS. \* AIRTIGHT CONSTRUCTION \* TENS OF THOUSANDS OF OUR PANELS ALREADY IN USE. \* COMPLETE WITH LEADS

SPECIFICATIONS:- \* POWER 100W RMS @ 8 OHMS \* FREQ RESP. 10Hz 15kHz -3dB \* DAMPING FACTOR >200 \* DISTORTION 0.05% \* S/N A WEIGHTED >100dB \* SUPPLY 230V A.C. \* WEIGHT 2.7Kg \* SIZE H254 X W254 X D94mm

THERE ARE 2 VERSIONS OF THE ABOVE PANEL AVAILABLE :- **BSB100/8 8 OHM VERSION** BSB100/4 4 OHM VERSION BOTH PANELS ARE PRICED AT £117.44 + £5.00 P&P INCL. V.A.T. CHECK WEBSITE FOR PANELS UP TO 900W

**OMP X03-S STEREO 3 WAY ACTIVE CROSSOVER SWITCHABLE 2-WAY**



**FEATURES:-**

Advanced 3-Way Stereo Active Cross-Over (Switchable two way), housed in a 19" x 1U case. Each channel has three level controls: Bass, Mid & Top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency. There are two versions available:- X03-S Bass-Mid 125/250/500Hz, Mid-Top 1.8/3/5kHz, all at 24 dB per octave. X03 Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5kHz, all at 24 dB per Octave. Please make sure you ask for the correct model when ordering. The 2/3 way selector switches are also accessed by removing the front fascia. Each stereo channel can be configured separately. Bass Invert Switches are incorporated on each channel. Nominal 775mV input/output. Fully compatible with the OMP Rack Amplifier and Modules.

BOTH MODELS PRICED AT :- £117.44 + £5.00 P&P

**OMP MOS-FET POWER AMPLIFIER MODULES**

SUPPLIED READY BUILT AND TESTED

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices: NOTE that all models include toroidal power supply, integral heatsink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

**THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS**

OMP/MF 100 Mos-Fet Output Power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. 110dB. Size 300 x 60mm.  
Price:- £42.85 + £4.00 P&P

OMP/MF 200 Mos-Fet Output Power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB. Size 300 x 155 x 100mm.  
Price:- £66.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output Power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB. Size 330 x 175 x 100mm.  
Price:- £83.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output Power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB. Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti Thump Delay. Size 385 x 210 x 105mm.  
Price:- £135.85 + £6.00 P&P

OMP/MF 1000 Mos-Fet Output Power 1000 watts R.M.S. into 2 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB. Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti Thump Delay. Size 422 x 300 x 125mm.  
Price:- £261.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV BANDWIDTH 100kHz OR PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV BANDWIDTH 50kHz ORDER STANDARD OR PEC

**B.K. ELECTRONICS** REF 05  
UNIT 1 COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR.  
TEL.: 01702-527572 FAX.: 01702-420243  
Web:- <http://www.bkelec.com> E-Mail sales@bkelec.com

DELIVERY CHARGES:- PLEASE INCLUDE AS ABOVE, TO A MAXIMUM AMOUNT £30.00. OFFICIAL ORDERS FROM SCHOOL, COLLEGES, GOVT. PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER. CREDIT CARD ORDERS ACCEPTED BY POST PHONE OR FAX.

