

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EVERYDAY

JULY 2002


PRACTICAL

ELECTRONICS

£2.85

STYLOPIC


A hand-held musical instrument

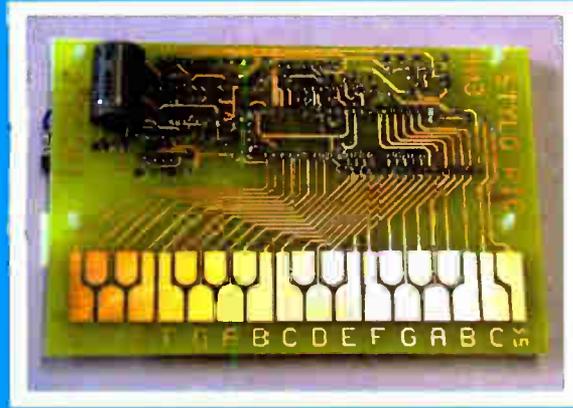

INFRA-RED AUTOSWITCH
An easy to build project

AUDIO CIRCUITS - 3
Power supplies, loudspeakers & signal filtering

PLUS
USING THE PIC's PCLATH COMMAND

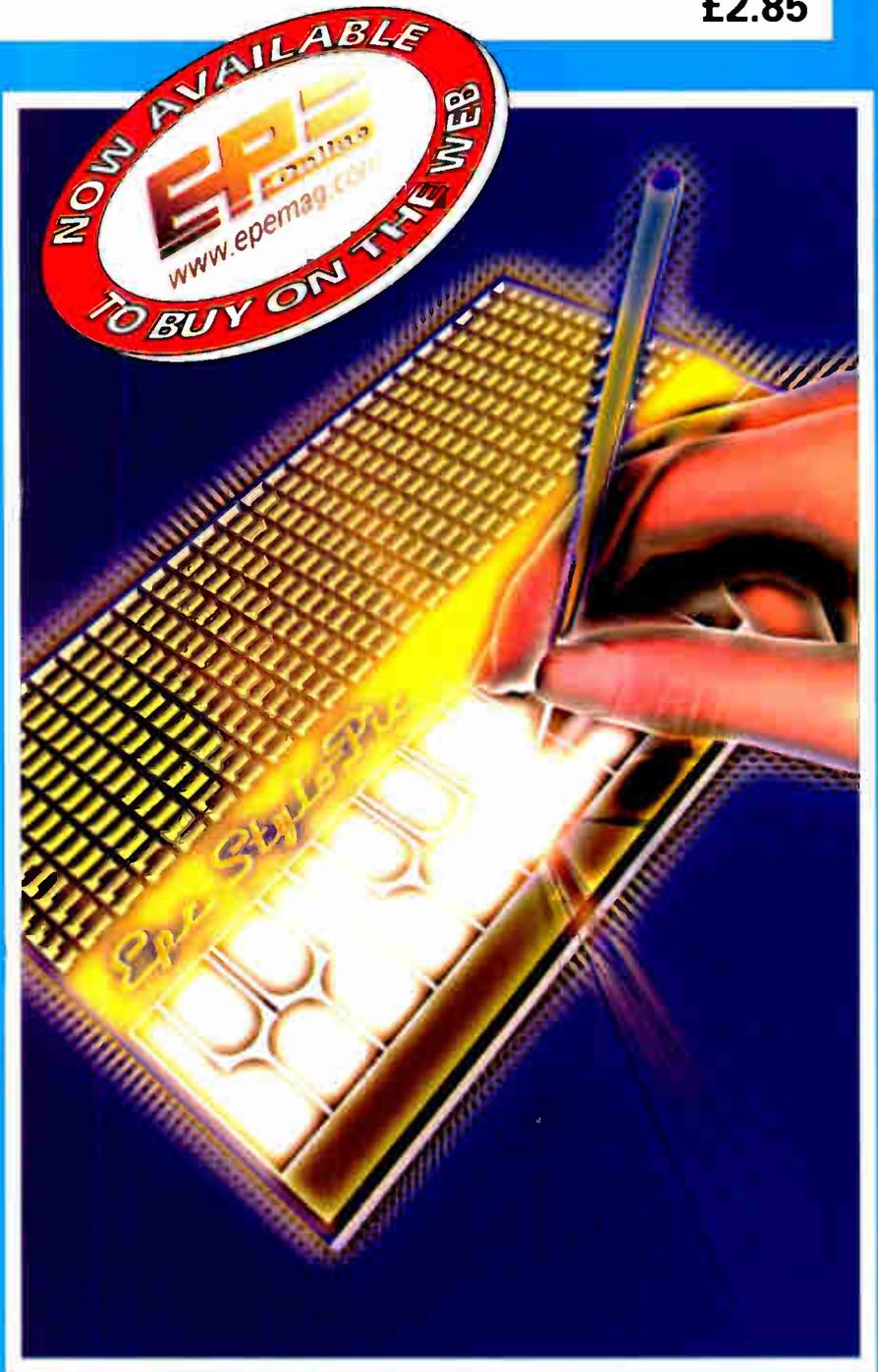

<http://www.epemag.wimborne.co.uk>

GAS MASKS RUSSIAN, new and boxed, NATO filter, £39.
LOW COST NIGHT VISION system. Russian handheld complete with infra-red illuminator, 100m range. Runs on 2 AA batteries, just £109.95.

COBRA NIGHT VISION equipment also stocked, more info on our web site at www.vibra-optical.co.uk.

ELECTRIC SCOOTERS 18kph, 24V motor, 6 hour charge time, 22kg weight, max load 90kg, running time up to 1 hour, range 15km, 8.5A motor, 24V, direct drive. Our Price £229.95. Ref ES00T.

VOICE CHANGERS Hold one of these units over your phone mouthpiece and you can adjust your voice using the controls on the unit. Battery operated, £15. Ref CC3.

EMMINENCE LOUDSPEAKERS 12in. dia., 50W nom, 100W peak, 16 ohm impedance. Pack of 4 just £39.95. Ref SPEAK39.

PIR SECURITY SWITCHES These brand new swivel mounting PIR units will switch up to 2 kilowatts. Adjustable sensitivity, light level and time delay (9 seconds to 10 minutes), 15m detection range, mains operated, waterproof £5.99 Ref PIR1PACK or a pack of 5 for £22.95 Ref PIR5PACK or 10 for £39.95 Ref PIR10PACK.

12V 12Ah SEALED LEAD ACID BATTERIES, 100mm x 150mm x 95mm, 4in. £15 each. Ref SSLB.

SEALED LEAD-ACID CHARGER AND FLOAT CHARGER. Complete unit will charge 12V lead acids and maintain them with an automatic trickle charge. Charger on its own is £15 Ref LAC or charger and a 12V 12Ah battery (all fully charged) is £25 Ref ACB.

AERIAL PHOTOGRAPHY KIT. This rocket comes with a built-in camera! It flies up to 500 feet (150m), turns over and takes an aerial photograph of the ground below. The rocket then returns with its film via its parachute. Takes 110 film. Supplied with everything including a launch pad and 3 motors (no film). £29.98 Ref Astro.

BUILD YOUR OWN WINDFARM FROM SCRAP. New publication gives step-by-step guide to building wind generators and propellers. Armed with this publication and a good local scrapyard could make you self-sufficient in electricity! £12. Ref LOT81.

MAGNETIC CREDIT CARD READERS AND ENCODING INFO, £9.95. Cased with flyleads, designed to read standard credit cards! Complete with control electronics p.c.b. and manual covering everything you could want to know about what's hidden in that magnetic strip on your card! Just £9.95 Ref BAR31.

77 KILO LIFT MAGNET. These Samarium magnets measure 57mm x 20mm and have a threaded hole (5/16th UNF) in the centre and a magnetic strength of 2.2 gauss. We have tested these on a steel beam running through the offices and found that they will take more than 170lb. (77kg) in weight before being pulled off. Supplied with keeper. £19.95 ea. Ref MAG77.

HYDROGEN FUEL CELL PLANS. Loads of information on hydrogen storage and production. Practical plans to build hydrogen fuel cell (good workshop facilities required), £8 set. Ref FCP1.

STIRLING ENGINE PLANS. Interesting information pack covering all aspects of Stirling engines, pictures of home made engines made from an aerosol can running on a candle! £12 STIR2.

12V OPERATED SMOKE BOMBS. Type 3 is a 12V trigger and 3 smoke canisters, each canister will fill a room in a very short space of time! £14.99. Ref SB3. Type 2 is 20 smaller canisters (suitable for mock equipment fires etc.) and 1 trigger module for £29. Ref SB2. Type 1 is a 12V trigger and 20 large canisters. £49. Ref SB1.

BRAND NEW NATO ISSUE RADIATION DETECTORS, SALE PRICE JUST £69.95. Current NATO issue standard emergency services unit. Used by most of the world's military personnel. New and boxed. Normal retail price £400. Bull's bargain price just £69.95. Ref PDRM.

BASIC GUIDE TO BIO DIESEL. How to make diesel fuel from used kitchen oil, £6. Ref BIOF.

SAVE £££££. RCb UNITS. In-line IEC lead with fitted RC breaker. Installed in seconds. Fit to any computer, monitor, office equipment and make it safe! Pack of 10 just £9.99. Ref LOT5B.

INFRA-RED REMOTE CONTROL WATCHES, £16.99.

VIBRATING WATCHES, vibrate when your phone rings, £16.99.

PULSE WATCHES, display your pulse, £16.99.

www.quemex.co.uk

STEPPER MOTORS. Brand new stepper motors, 4mm fixing holes with 47-14mm fixing centres, 20mm shaft, 6-35mm diameter, 5V/phase, 0.7A/phase, 1-8 deg. step (200 step). Body 56mm x 36mm, £14.99 each. Ref STEP6. pack of 4 for £49.95.

BASIC GUIDE TO LOCKPICKING. New publication gives you an insight! £6. Ref LPK.

NEW HIGH POWER MINI BUG. With a range of up to 800 metres and 3 days use from a PP3 this is our top selling bug! Less than 1in. square and a 10m voice pick-up range. £28. Ref LOT102.

IR LAMP KIT. Suitable for CCTV cameras, enables the camera to be used in total darkness! £6. Ref EF138.

INFRA-RED POWERBEAM. Handheld battery powered lamp, 4in. reflector, gives out powerful pure infra-red light! Perfect for CCTV use, night sights, etc. £29. Ref PB1.

YOUR HOME COULD BE SELF-SUFFICIENT IN ELECTRICITY. Comprehensive plans with loads of info on designing systems, panels, control electronics etc. £7. Ref PV1.

200 WATT INVERTERS, plugs straight into your car cigarette lighter socket and is fitted with a 13A socket so you can run your mains operated devices from your car battery. £49.95. Ref SS66.

THE TRUTH MACHINE. Tells if someone is lying by micro tremors in their voice, battery operated, works in general conversation and on the phone and TV as well! £42.49. Ref TD3.

INFRA-RED FILM. 6in. square piece of flexible infra-red film that will only allow IR light through. Perfect for converting ordinary torches, lights, headlights etc. to infra-red using only standard light bulbs. Easily cut to shape. 6in. square. £15. Ref IRF2 or a 12in. square for £29.95. Ref IRF2A.

SMOKE ALARMS. Mains powered, made by the famous Gent company, easy fit next to light fittings, power point. Pack of 5 £15. Ref SS23, pack of 12 £24. Ref SS24.

CCTV CAMERAS FROM £25. Check out our web site at www.cctvistuff.co.uk and www.home-cctv.co.uk.

14 WATT SOLAR PANELS. Amorphous silicon panel fitted in an anodised aluminium frame. Panel measures 3ft. by 1ft. with 3m leads for easy connection, 3ft. x 1ft. solar panel £79. Ref MAG45.

Unframed 4 pack, 6-9W (3ft. x 1ft.) £99. Ref SOLX. 35 watts of solar power for just £99. 4 panels, each one 3ft. x 1ft. and producing 8W min., 13V. Pack of four £99. Ref SOLX.

POWERSAFE DEEP CYCLE BATTERIES



6V 100AH £39 EACH

NEW 12V 12in. SQUARE SOLAR PANEL. Kevlar backed, 3 watt output, copper strips for easy solder connections. £14.99 Ref 15P42. Pack of four just £39.95. Ref 15P42SP.

NEW UNIVERSAL SOLAR CHARGER. Charges AAAs, AAs, Cs and D-type NiCads. £9.99. Ref UNISOL.

12V SOLAR POWER WATER PUMP. Perfect for many 12V d.c. uses, from solar fountains to hydroponics! Small and compact yet powerful, works direct from our 10W solar panel in bright sun. Max HD: 17ft, max flow = 8 Lpm, 1-5A. Ref AC88. £18.99.

SOLAR MOTORS. Tiny motors which run quite happily on voltages from 3V-12V d.c. Works on our 6V amorphous 6in. panels and you can run them from the sun! 32mm dia., 20mm thick. £1.50 each.

MAMOD STEAM ENGINES and a full range of spare parts. Check out www.mamodspares.co.uk.

SUPER WIDEBAND RADAR DETECTOR. Whistler 1630. Detects both radar and laser, X, K and KA bands, speed cameras and all known speed detection systems. 360 degree coverage, front and rear waveguides, 1.1in. x 2.7in. x 4.6in., fits on visor or dash, new low price £99. Ref WH1630. Other models available at www.rsdargun.co.uk.

BUG DETECTORS. A new detector at a sensible price! Detects bugs hidden in rooms, computers etc., between 1-200MHz, adjustable sensitivity, 9V PP3 battery required. £29.95. Ref BDET2.

GIANT WEATHER BALLOONS made by Tolex, we blew one up to 7ft. diameter then it popped due to stones on the ground! £13.99. Ref TOTEX.

PHILIPS VP406 LASER DISC PLAYERS, sale price just £9.95. Start out, just put your video disk in and press play, standard audio and video outputs. £9.95. Ref VP406.

12V DC SIRENS. Very loud, suitable for indoors or outdoors, two-tone, 160mm x 135mm, finished in white with bracket. £4.99. Ref SIRVA2.

FREEZER/MAINS FAIL ALARMS. Designed to fit around the mains cable on a freezer this alarm will sound if the device is unplugged from the mains supply, battery operated, cased, built-in sounder. Ideal for TVs, Hi-Fi equipment etc. £7.01. Ref FRE2.

BARNET CROSSBOWS. We stock the entire range of crossbows, check out our web site at www.xbows.co.uk.

HOT AIR BALLOON KITS. Everything you need to build a 1.7m high, 4.5m in circum, hot air balloon, launch over a small burner or heater. £12.49. Ref HA1.

CROOKES RADIOMETER. Fascinating glass bulb contains blades driven around by the sun, £9.99. Ref SC120B.

GIANT TV OR PC VIEWING SCREEN. Turn your TV into a super-size screen, converts small screens into a super size 26in. £26.99. Ref SVGA2.

RADIOSONDES. Made by Valsala, unused, they measure pressure, temperature and humidity. Model RS80, good stripper at £15. Ref SONDE.

AIR WIND POWER MODULE. Produces nearly 400 watts of power from the wind, 1.14m blade, 12V d.c. output, 3 year warranty, built-in battery regulator. £549. Ref AIR1.

WORMERIES. The ideal solution for your kitchen waste! Supplied complete with worms. Turn your rubbish into liquid feed! Two sizes available, small (ideal for 1-2 people), £25.45. Ref WM2, and a large one (ideal for 4 or more), £42.44. Ref WM1.

COMPLETE WIRELESS CCTV SYSTEM. Includes monitor, camera, up to 100m range, audio and video, UK legal, complete with infra-red lights. £169. Ref WMS333.

PELTIER MODULES. 56W, 40mm x 40mm, 16V, sealed edges. New and boxed. Supplied with 18-page PelTier design manual featuring circuit designs, design information etc. 1 module and manual is £29.99. Ref PELT1, pack of 4 modules and manual is £99.99. Ref PELT2. The manual on its own is £4. Ref PELT3.

DC MOTOR. 12V d.c., general purpose model motor, 70mm x 50mm, 12V d.c., permanent magnet, 4mm x 25mm shaft. £6. Ref GPM1, pack of 10 is just £40. Ref GPM2.

180R.P.M. MAINS MOTOR. Induction type, 90mm x 70mm, 50mm x 5mm shaft, 12A continuous rating, thermal protected. £22. Ref MG1.

SOLID STATE RELAYS. P.C.B. mounting, these relays require 3-32V d.c. to operate but will switch up to 3A a.c. ma.ins. Pack of 4 £5. Ref SPEC1B.

12V RELAYS. 2 x 2 c/o 16A contacts p.c.b. mount (will fit Ver0), 12V of 25 relays for just £9.95. Ref SPEC1.

VENNER TIME CONTROLS. Designed to be wired in permanently they will switch up to 16A 240V a.c. motorised with dial and pins. New and boxed £15. Ref VTS.

GYROSCOPES. We still sell original 1917 design, hours of fun for all the family, complete with stand, string, box and info. £6. Ref EP70.

INNOVATIONS. We also sell a wide range of innovative products for the home, these are at www.seemans.com.

INVERTERS. Convert 12V d.c. into 240V mains (modified sine wave), 300 watt (150 watt continuous), £59.95. Ref VER3. 600 watt model (330 watt continuous), £79.97. Ref VER4.

10 WATT SILICON SOLAR PANEL, 10 year life, waterproof, 365mm x 365mm x 26mm, 14V, 10W, 1.8kg, framed. £84.99. Ref PAN.

STICKY LABELS. Small address labels etc. are very useful and can be ordered online at www.stickon.co.uk.

MICROSOFT TRACKBALL AND MOUSE. Called the Microsoft Ballpoint this has 4 buttons, a trackball and PS2 connector. Will work with most PCs. £5.99. Ref EP50.

MAXON WALKIE TALKIES, up to 2 mile range, UK legal, 300 channel, 2 x walkie talkies, £74.95. Ref. Maxon1. Chargers £14. Ref. Maxonc. battery packs £12. Ref. Maxonb (otherwise uses AAA batteries).

2-WAY MIRROR KIT. Contains enough material to make up to a 500mm x 2200mm mirror (excl. glass), full instructions. £19.95. Ref WF001.

.22 AIR RIFLE. Under lever type, powerful Chinese training rifle, £38.26. Ref A1047. 500 pellets, £2.68. Ref A1091.

.22 AIR RIFLE STANDARD TYPE. Chinese training rifle, on legal limit for air rifles, £29.75. Ref A1040. Pellets £2.68. Ref A1091.

SHUT THE BOX. Check out www.bullybeef.co.uk for a range of pub games and magic tricks.

WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA? We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14. Ref EP74.

ANICS CO2 GAS POWERED PISTOL. Russian hand pump pistol powered by Sparklets CO2 cylinders (give approx. 70 shots), fires steel BB. Pistol £58.22. Ref AGA101. tub of 1,500 BB shot £5.10. Ref A1015. pack of 5 CO2 cartridges £3.50. Ref GAS5.

33 KILO LIFT MAGNET. Neodymium, 32mm diameter with a fixing bolt on the back for easy mounting. Each magnet will lift 33 kilos, 4 magnets bolted to a plate will lift an incredible 132 kilos! £15. Ref MAG33. Pack of 4 just £39. Ref MAG33AA.

BSA METEOR AIR RIFLE. UK made. 22 rifle, top quality professional air rifle, £84.15. Ref BSAMET 500 Lazapell pellets £5. Ref LAZAPELL.

MAMOD 1313 TE1A TRACTION ENGINE. Attractive working model of traditional steam engine, £85. Ref 1313.

MAMOD STEAM ROADSTER (white), magnificent working steam model car, £112. Ref 1319.

MAMOD STEAM WAGON. Working model steam wagon finished in blue. £112. Ref 1318. Brown version (with barrels), £122. Ref 1450.

POCKET SPY MONOCULAR. Clever folding monocular with 8 x 21 magnification, made by Helios, with case. £14.99. Ref MONOC.

KEVLAR BRITISH ARMY HATS. Broken or missing straps, hence just £8 each. Ref KEV99.

CCTV SYSTEMS, £24.99. Complete with camera, 20 metres of cable, p.s.u. and info simple connection to scart. £24.99. Ref CCTVCAM2.

FM BROADCAST BAND HIGH POWER TRANSMITTERS can be viewed and bought online at www.veronica-kifs.co.uk.

TONER CARTRIDGES FOR COPIERS AND PRINTERS can be bought online at www.nationaltoners.co.uk.

VELOSOLEX. Traditional French style two-stroke moped (engine over front wheels), black only, £695. Ref VELO. Delivered direct in a box, you need to fit the pedals etc. then register it with your local DVLC.

HYDROPONIC GROWING SYSTEMS. Complete, everything you need apart from plants and light, contains grow tank, nutrients, pump, tester etc. GT205 710mm x 390mm, NFT system, £31.45. Ref GT205. GT424 1070mm x 500mm, NFT system, £58.65. Ref GT424.

ELECTRIC BIKES, £679. Viking, built-in indicators, radio, lights, 13mph, 5 hour charge, Shimano gears, up to 50 mile range, horn, 26in. wheels, suspension, no licence needed, key operated, £679. Ref VIKING.

PIR PCBs. These contain a standard PIR detector circuit with all components, easy to wire up and use. Pack of 4 £6. Ref PIRB.

NEBULISER, WATER ATOMISER. Ultrasonic module that you place in water, atomises the water into a very fine mist, many applications from special effects to scientific. £69. Ref NEB6.

PORTABLE X-RAY MACHINE PLANS. Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £6/set. Ref FXP1.

TELEKINETIC ENHANCER PLANS. Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks yet produces positive motion and effect. Excellent for science projects, magic shows, part demonstrations or serious research and development of this strange and amazing psychic phenomenon. £4/set. Ref FTKE1.

ELECTRONIC HYPNOSIS PLANS & DATA. This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc. only, by those experienced in its use. £15/set. Ref F/EH2.

GRAVITY GENERATOR PLANS. This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of simple materials and without any visible means cause it to levitate. £10/set. Ref F/GRA1.

TESLA COIL/LIGHTNING DISPLAY GLOBE PLANS. Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects. 'Plasma in a jar', St Elmo's fire, corona, excellent science project or conversation piece. £5/set. Ref F/BTC1/LG5.

COPPER VAPOUR LASER PLANS. Produces 100mW of visible green light. High coherency and spectral quality similar to argon laser but easier and less costly to build, yet far more efficient. This particular design was developed at the Atomic Energy Commission of NEgev in Israel. £10/set. Ref F/CVL1.

VOICE SCRAMBLER PLANS. Miniature solid-state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £6/set. Ref F/V59.

PULSED TV JOKER PLANS. Little handheld device utilises pulse techniques that will completely disrupt TV picture and sound! Works on FM too! Discretion advised. £8/set. Ref F/TJ5.

BODYHEAT TELESCOPE PLANS. Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development etc. Excellent security device or very interesting science project. £8/set. Ref F/BHT1.

BURNING, CUTTING CO2 LASER PLANS. Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials, but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground etc. Burning and etching wood, cutting, plastics, textiles etc. £12/set. Ref F/LC7.

AIR RIFLES FROM LESS THAN £40, CROSSBOWS, WIDE RANGE OF BB GUNS, AMMO, TARGETS, PISTOLS, REPLICAS GUNS, UZI MACHINE GUN REPLICAS (BB), REPEATERS, LASER SIGHTS, ELECTRIC BB, GAS BB
www.airplstol.co.uk

INKJET CARTRIDGES FROM JUST £3 AT
www.officebits.co.uk

BULL ELECTRICAL
 UNIT D, HENFIELD BUSINESS PARK,
 HENFIELD, SUSSEX BN5 9SL
 TERMS: CASH, PO OR CHEQUE WITH
 ORDER PLUS £5.00 P&P (UK) PLUS VAT
 24 HOUR SERVICE £7.50 (UK) PLUS VAT
 OVERSEAS ORDERS AT COST PLUS £3.50
 (ACCESS/VISA/SWITCH ACCEPTED)
 'phone: 01273 491490 Fax 491813
 Sales@bull-electrical.co.uk

www.bullnet.co.uk





ISSN 0262 3617
PROJECTS ... THEORY ... NEWS ...
COMMENTS ... POPULAR FEATURES ...

VOL. 31. No. 7 JULY 2002
Cover illustration by Jonathan Robertson

EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

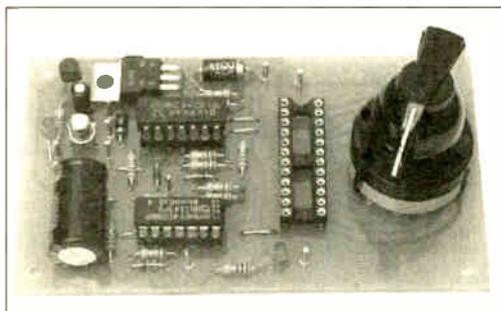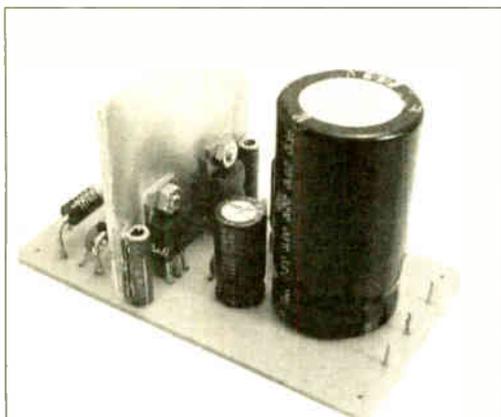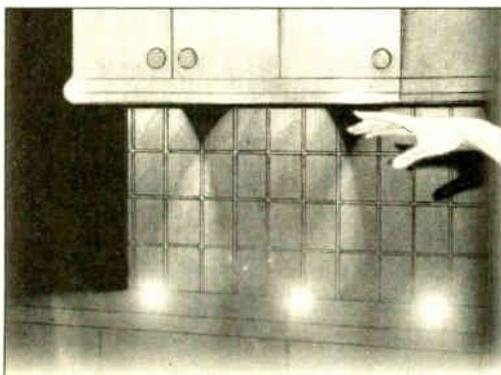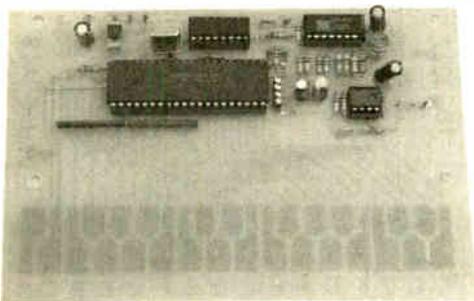www.epemag.wimborne.co.uk
EPE Online: www.epemag.com



© Wimborne Publishing Ltd 2002. Copyright in all drawings, photographs and articles published in EVERYDAY PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our August 2002 issue will be published on Thursday, 11 July 2002. See page 467 for details

Projects and Circuits

- INFRA-RED AUTOSWITCH** by Max Horsey 476
Keeps work-surface lights turned on only while you are near to them
- INGENUITY UNLIMITED** hosted by Alan Winstanley 486
Velocity Detector; Car Battery Trickle Charger
- EPE STYLOPIC** by John Becker 488
Have fun with a modern interpretation of a classic musical instrument!
- SIMPLE AUDIO CIRCUITS – 3. Power Supplies, Loudspeakers, Crossover Networks and Filters** by Raymond Haigh 500
A compendium of useful audio amplifier circuits for the experimenting constructor
- ROTARY COMBINATION LOCK** by Thomas Scarborough 512
Pure logic and a "stack of cards" function enhance security

Series and Features

- NEW TECHNOLOGY UPDATE** by Ian Poole 484
Holographic techniques could revolutionise computer data storage
- USING THE PIC'S PCLATH COMMAND** by John Waller 509
How to access PIC addresses beyond 2K and place tables outside the basic 256 byte block
- CIRCUIT SURGERY** by Alan Winstanley and Ian Bell 519
Bandgap Voltages; More on X and Y capacitors; Yaesu Battery Charger again
- PRACTICALLY SPEAKING** by Robert Penfold 522
A practical look at interpreting component codings
- NET WORK – THE INTERNET PAGE** surfed by Alan Winstanley 527
Search Engines; Tiscali 10.0
- TEACH-IN 2002 – 9. Filters, Analogue-to-Digital Conversion, Sampling and Nuclear Radiation Sensing** by Ian Bell and Dave Chesmore 528

Regulars and Services

- EDITORIAL** 475
- NEWS** – Barry Fox highlights technology's leading edge 482
Plus everyday news from the world of electronics
- READOUT** John Becker addresses general points arising 495
- BACK ISSUES** Did you miss these? Many now on CD-ROM! 498
- SHOPTALK** with David Barrington, 507
The *essential* guide to component buying for EPE projects
- PLEASE TAKE NOTE** 507
World Lamp; L.E.D. Sequencer; Toolkit TK3
- CD-ROMS FOR ELECTRONICS** 524
A wide range of CD-ROMs for hobbyists, students and engineers
- DIRECT BOOK SERVICE** 536
A wide range of technical books available by mail order
- PRINTED CIRCUIT BOARD AND SOFTWARE SERVICE** 539
PCBs for EPE projects. Plus EPE software
- ELECTRONICS MANUALS** 540
Essential reference works for hobbyists, students and service engineers
- ADVERTISERS INDEX** 544

Readers Services • Editorial and Advertisement Departments 475

Visit our website
www.distel.co.uk

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

GIANT 10" 7-SEGMENT DISPLAYS

A bulk purchase enables us to bring to you these GIANT 7-segment digital displays at a now affordable price! The 10" character size gives exceptional readability at long distances and enables a host of applications including score boards, digital clocks, counters, event timers etc. As the units are a simple electromechanical device and operate from 12V DC, simple switching via switches, relays, PIC or PC may be used to control single or multiple digits. Units feature integral Zero Power memory which greatly simplifies design. For an excellent DIY practical article, see the May issue of "Everyday Practical Electronics" magazine. Ideal School / College construction project. Supplied in good RFE condition, complete with data sheet.



Less than 30% of makers price! Only £29.95(B) or 4 / £99.00(D)
Order RW44 Order PH26

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!
The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tunable off air UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95
TELEBOX STL as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
For overseas PAL versions state 5.5 or 6 mHz sound specification.
For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Telebox's, code (B)

TELEBOX ST for composite video input type monitors £36.95
TELEBOX STL as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
For overseas PAL versions state 5.5 or 6 mHz sound specification.
For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Telebox's, code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite TV pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate.
BRAND NEW - Order as MY00. Only £39.95 code (B)
See www.distel.co.uk/data/my00.htm for picture + full details

HARD DISK DRIVES 2 1/2" - 14"

2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H) New £59.95
2 1/2" TOSHIBA MK4313MAT 4.3Gb laptop (8.2 mm H) New £105.00
2 1/2" TOSHIBA MK6409MAV 6.1Gb laptop (12.7 mm H) New £98.00
2 1/2" TOSHIBA MK1614GAV 18 Gb laptop (12 mm H) New £149.95
3 1/2" to 3 1/2" conversion kit for PCs, complete with connectors £15.95
3 1/2" COMPAQ 313706-B21 (IBM) 9 gb ULT/SCSI3 New £199.00
3 1/2" FUJI FK-309-26 20mb MFH I/F RFE £59.95
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE £59.95
3 1/2" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE £69.00
3 1/2" QUANTUM 405 Prodriv 18 Gb SCSI I/F, New RFE £49.00
5 1/4" MINISCRIBE 3425 20mb MFH I/F (or equiv.) RFE £49.95
5 1/4" SEAGATE ST-238R 30 mb RLL I/F Return £69.95
5 1/4" CDC 94205 5 1/4" 40mb HH MFH I/F RFE tested £69.95
5 1/4" HP 97548 850 Mb SCSI RFE tested £99.00
5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
8" NEC D2246 85 Mb SMD interface. New £99.00
8" FUJITSU M2322K 160Mb SMD I/F RFE tested £195.00
8" FUJITSU M2392K 2 Gb SMD I/F RFE tested £345.00
Many other floppy & H drives, IDE, SCSI, ESDI etc from stock, see website for full stock list. Shipping on all drives is code (C)

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK
10,000,000 items EX STOCK
For MAJOR SAVINGS
CALL or see web site www.distel.co.uk

COMPUTER MONITOR SPECIALS

Legacy products
High spec genuine multisync.
CGA, EGA, VGA, SVGA

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Main features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, in EXCELLENT like used condition. Tilt & Swivel Base £4.75
VGA cable for IBM PC included. Order as CG73

Only £129 (E)

External cables for other types of computers available - CALL

Generic LOW COST SVGA Monitors

We choose the make, which includes Compaq, Mitsubishi, IBM, etc. Supplied ready to run with all cables, Standard RTB 90 day guarantee.

14" £59.00
15" £69.00
17" £79.00
Supplied in good used condition. Shipping code (D)

VIDEO MONITORS

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls. VCR correction button etc. Good used condition - fully tested & guaranteed
Dimensions: W14" x H12 3/4" x 15 1/2" D.
Only £99.00 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen bums). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered.
Only £79.00 (D)

INDUSTRIAL COMPUTERS

Tiny shoebox sized industrial 40 Mhz 386 PC system measuring only (mm) 266 w X 88 h X 272 d. Ideal for dedicated control applications running DOS, Linux or even Windows! Steel case contains 85 to 265 V AC 50 / 60 Hz 70 Watt PSU, a 3 slot ISA passive backplane and a Rocky 318 (PC104) standard, single board computer with 8 Mbyte NON VOLATILE solid state 'Disk On Chip' RAMDISK. System comprises: Rocky 318 (PC104) SBC ISA card with 40MHz ALI 386SX CPU, 72 pin SIMM slot with 16 Mbyte SIMM, AMI BIOS, battery backed up real time clock, 2 x 9 pin D 16550 serial ports, EPP/ECP printer port, mini DIN keyboard connector, floppy port, IDE port for hard drives up to 528 Mbyte capacity, watchdog timer and PC/104 bus socket. The 8 Mbyte solid state 'disk on a chip' has its own BIOS, and can be formatted, formatted & booted. Supplied BRAND NEW fully tested and guaranteed. For full data see featured item on website. Order as QG36
100's of applications inc: firewalls, routers, robotics etc
Only £99.00 (D)

19" RACK CABINETS

Europe's Largest Stocks of quality rack cabinets, enclosures and accessories. Over 1000 Racks from stock

This month's special
33 / 42 / 47 U - High Quality
All steel Rack Cabinets

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remains unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A main distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue, some gray available - CALL - Can be supplied in many other configurations.



33U Order as BC44 External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W) Only £245
42U Order as DT20 External dimensions mm=2019H x 635D x 603 W. (79.5" H x 25" D x 23 3/4" W) Only £345
47U Order as RV36 External dimensions mm=2019H x 635D x 603 W. (88" H x 25" D x 23 3/4" W) Only £410

Call for shipping quotation

COLOUR CCD CAMERAS

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full autolight sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available. BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cams etc.



Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cams etc.
Order as LK33 ONLY £79.00 or 2 for £149.00 (B)

SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. ONLY £89.00 (B)
ENCARTA 95 - CDROM, Not the latest - but at this price! £7.95
DOS 5.0 on 3 1/2" disks with concise books o/w QBasic £14.95
Windows for Workgroups 3.11+ on 3.5" disks £55.00
Windows 95 CDROM Only - No Licence £19.95
Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95
shipping charges for software is code B

SOLID STATE LASERS

Visible red, 670nm laser diode assembly. Unit runs from 3 V DC at approx 50 mA. Originally made for continuous use in industrial barcode scanners, the laser is mounted in a removable solid aluminium block, which functions as a heatsink and rigid optical mount. Dims of block are 50 w x 50 d x 15 mm. Integral features include over temperature shutdown, current control, laser OK output, and gated TTL ON / OFF. Many uses for experimental optics, comms & lightshows etc. Supplied complete with data sheet.
Order as TD91 ONLY £24.95 (A)

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock - Call or see our web site.

RELAYS - 200,000 FROM STOCK

Save ££££'s by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contractors, Time Delay, Relay, Mercury Wetted, Solid State, Printed Circuit Mounting etc., CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save ££££'s

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

MITSUBISHI FA3445ETKL 14" Ind. spec SVGA monitors £245
FARNELL 0-60V DC @ 50Amps, bench Power Supplies £995
FARNELL AP3080 0-30V DC @ 80 Amps, bench Supply £1850
KINGSHILL CZ403/1 0-50V @ DC 200 Amps - NEW £3950
1KW to 400 KW - 400 Hz 3 phase power sources - ex stock EPOA £760
Wayne Kerr RA200 Audio frequency response analyser £2500
INFODEC 1U, 24 port, RJ45 network patchpanels. #TH93 £49
3COM 16670 12 Port Ethernet hub - RJ45 connectors #LD97 £69
3COM 16671 24 Port Ethernet hub - RJ45 connectors £89
3COM 16700 8 Port Ethernet hub - RJ45 connectors NEW £39
IBM 53F5501 Token Ring IC5 20 port lobe modules EPOA £45
IBM MAU Token ring distribution panel 3202B-23-5050N £45
AIM 50 Low distortion Oscillator 9Hz to 330KHz, IEEE I/O £550
ALLGON 8360.11805-1880 MHz hybrid power combiners £250
Trend DSA 274 Data Analyser with G703(2M) 64 I/O £4500
Marconi 6310 Programmable 2 to 22 GHz sweep generator £1550
Marconi 2022C 10KHz-1GHz RF signal generator £3750
HP1650B Logic Analyser EPOA £1800
HP3781A Pattern generator & HP3782A Error Detector £475
HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
HP6264 Rack mount variable 0-20V @ 20A metered PSU £475
HP54121A DC to 22 GHz four channel test set EPOA £7900
WHL130A opt 020 300 MHz pulse generator, GPIB etc £550
HP A1, A0 8 pen HPGL high speed drum plotters - from HP DRAFTMASTER 1 8 pen high speed plotter £750
EG+G Brookdale 95035C Precision lock in amp £1800
Keithley 590 CV capacitor / voltage analyser EPOA £3750
Racal CR40 dual 40 channel video recorder system £4500
Fluke 45KVA 3 ph On Line UPS - New batteries £1499
Emerson AP130 2.5KVA industrial spec UPS £2200
Mann Tally MT645 High speed line printer £2200
Intel SBC 486/133SE Multibus 486 system. 8Mb Ram £945

Unless marked NEW, items in this section are pre owned.

HP6030A 0-200V DC @ 17 Amps bench power supply £1950
Intel SBC 486/125C08 Enhanced Multibus (MSA) New £1150
Nikon HF-X11 (Ephobot) exposure control unit £1450
PHILIPS PM5518 pro. TV signal generator £1250
Motorola VME Bus Boards & Components List. SAE / CALL EPOA £550
Trilo 0-18 vdc linear, metered 30 amp bench PSU. New £1950
Fujitsu M3041R 600 LPM high speed band printer £1250
Fujitsu M3041D 600 LPM printer with network interface £2950
Siemens K4400 64Kb to 140Mb demux analyser £500
Perkin Elmer 299B infrared spectrophotometer £500
YG Electronics 1035 TELETEC Decoding Margin Meter £3250
LightBand 60 optical high spec 2u rack mount Video VDA's £495
Sekonic SD 150M 18 channel digital Hybrid card recorder £1995
BK 2633 Microphone pre amp £300
Taylor Hobson Tallysurp amplifier / recorder £750
ADC SS200 Carbon dioxide gas detector / monitor £1450
BBC AN203 PPM Meter (Ernest Turner) + drive electronics £75
ANRITSU 9654A Optical DC-2.5Gb waveform monitor £5650
ANRITSU ML93A optical power meter £990
ANRITSU Fibre optic characteristic test set EPOA £650
R&S FTDZ Dual sound unit £775
R&S SBUE-1 Vision modulator £5750
WILTRON 6630B 12.4 / 20GHz RF sweep generator £1250
TEK 2445 150 MHz 4 trace oscilloscope £1955
TEK 2465 300 Mhz 300 MHz oscilloscope rack mount £2900
TEK TD5380 400MHz digital real time + disk drive, FFT etc £5100
TEK TDS524A 500MHz digital realtime + colour display etc £3950
HP3585A Opt 907 20Hz to 40 Mhz spectrum analyser £3950
PHILIPS PW1730/10 60KV XRAY generator & accessories EPOA £1499
VARIACS - Large range from stock - call or see our website £325
CLAUDE LYONS 12A 240V single phase auto. volt. regs £2900
CLAUDE LYONS 100A 240/415V 3 phase auto. volt. regs £2900



ALL MAIL TO
Dept PE, 29 / 35 Osborne Rd
Thornton Heath
Surrey CR7 8PD
Open Mon - Fri 9.00 - 5:30

18 Million Items On Line Now!
Secure ordering, Pictures, Information
www.distel.co.uk
email = admin@distel.co.uk

ALL ENQUIRIES
0208 653 3333
FAX 0208 653 8888


All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 7 working days clearance. Carriage charges (A)=£3.50, (B)=£6.50, (C)=£10, (D)=£15.00, (E)=£18.00, (F)=CALL. Allow approx 3 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale which can be viewed at our website and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Distel Electronics 2002. E & O.E.

NEXT MONTH

PIC WORLD CLOCK

Inspired by a display originally seen in a hotel lobby, this design graphically shows calendar, clock and global timezone data. Based on a PIC16F877 microcontroller and a graphics I.c.d., the following functions are available:

- Simplified World map
- Current UK clock and calendar data
- Clock data for any other timezone, adjustable via switches
- Flashing marker for sun's current highest position, i.e. true noon at that longitude (angle in relation to 0°, GMT)
- Marker's position vertically (latitude) varies with the weeks and months throughout the year, spanning the Tropics of Capricorn and Cancer
- Multi-paged text display of 150 major cities and their timezone displacements in relation to GMT (e.g. New York -5 hours, Sydney +11 hours)
- Additional city timezones can be readily added by readers who have PIC Toolkit Mk2 or Mk3 (TK3 V1.2)
- Accuracy of clock time-keeping adjustable via switches
- Principal clock and calendar data stored in the PIC's non-volatile EEPROM for recall in the event of power failure.
- Runs from a mains powered 9V battery adaptor, plus standby battery back-up.

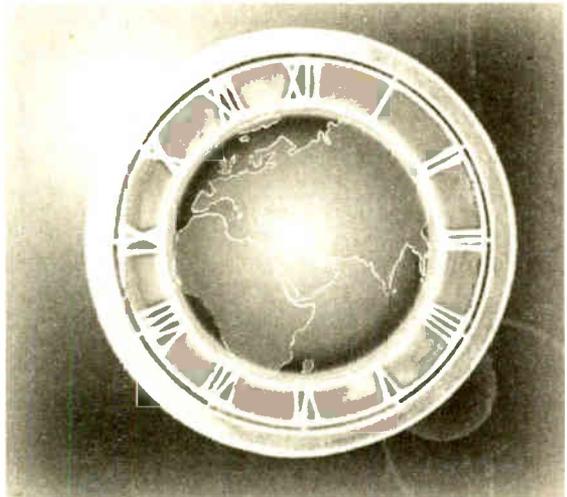


A REVOLUTION IN EVOLUTION

We hear about advances in electronics all the time – smaller circuits, faster chips, new devices and technologies. But there's another revolution happening, one that in a few years may change electronics forever and perhaps even lead to the development of the first truly intelligent machines. This new revolution is called Evolutionary Electronics. One of the most interesting and unusual attributes of this revolution is its accessibility to hobbyists. The answers to the big questions aren't clear yet and the rewards for getting it right are immense. The experiments don't need million dollar machines or laboratories, just access to some good computing equipment and a degree of ingenuity.

We all know what evolution is: it is a simple and elegant concept. If you take a population of animals which have random genes and leave them in a particular environment, those with good traits will survive and those that are not as fit will die. The better-suited members of the population survive to breed and to mix and pass on their good traits to the next generation. So, why not do the same with circuits? Set them up randomly, test how good they are (their fitness), and allow the best ones to survive and mix their traits (to breed!). Well, this can be done and it has been done with some very interesting results, as you will see next month.

BIG-EARS BUGGY

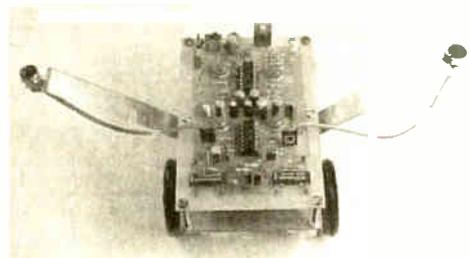A simple fun buggy that will move towards a sound – speak to it and it will turn and move towards you. Uses inexpensive circuitry bolted to a simple chassis. The circuit could find a number of other applications where the direction of sound needs to be monitored.



NO ONE DOES IT BETTER

EVERYDAY
PRACTICAL
ELECTRONICS

**DON'T MISS AN
ISSUE – PLACE YOUR
ORDER NOW!**
Demand is bound to be high

AUGUST 2002 ISSUE ON SALE THURSDAY, JULY 11

QUASAR ELECTRONICS LIMITED

PO Box 6935, BISHOPS STORTFORD, Herts. CM23 4WP

TEL: 01279 467799 FAX: 07092 203496

ADD £2.00 P&P to all orders (or 1st Class Recorded £4, Next day Recorded £2.50) in Europe only. Rest of World £10.00. We accept all major credit cards. Make cheques/POs payable to Quasar Electronics. Prices include 17.5% VAT. MAIL ORDER ONLY. FREE CATALOGUE with order or send 2 x 1st class stamps (refundable) for details of over 150 kits & publications.



PROJECT KITS

Our electronic kits are supplied complete with all components, high quality PCBs (NOT cheap Tripad strip board!) and detailed assembly/operating instructions


- **2 x 25W CAR BOOSTER AMPLIFIER** Connects to the output of an existing car stereo cassette player, CD player or radio. Heatsinks provided. PCB 76x75mm. 1045KT £24.95
- **3-CHANNEL WIRELESS LIGHT MODULATOR** No electrical connection with amplifier. Light modulation achieved via a sensitive electret microphone. Separate sensitivity control per channel. Power handling 400W/channel. PCB 54x112mm. Mains powered. Box provided. 6014KT £24.95
- **12 RUNNING LIGHT EFFECT** Exciting 12 LED light effect ideal for parties, discos, shop-windows & eye-catching signs. PCB design allows replacement of LEDs with 220V bulbs by inserting 3 TRIACs. Adjustable rotation speed & direction. PCB 54x112mm. 1026KT £15.95; BOX (for mains operation) 2026BX £30.00
- **DISCO STROBE LIGHT** Probably the most exciting of all light effects. Very bright strobe tube. Adjustable strobe frequency 1-60Hz. Mains powered. PCB: 60x68mm. Box provided. 6037KT £28.95

- **ANIMAL SOUNDS** Cat, dog, chicken & cow. Ideal for kids farmyard toys & schools. SG10M £5.95
- **3 1/2 DIGIT LED PANEL METER** Use for basic voltage/current displays or customise to measure temperature, light, weight, movement, sound levels, etc. with appropriate sensors (not supplied). Various input circuit designs provided. 3061KT £13.95
- **IR REMOTE TOGGLE SWITCH** Use any TV/VCR remote control unit to switch on/off a 12V/1A relay on/off. 3058KT £10.95
- **SPEED CONTROLLER** for any common DC motor up to 100V/5A. Pulse width modulation gives maximum torque at all speeds. 5-15VDC. Box provided. 3067KT £12.95
- **3 x 8 CHANNEL IR RELAY BOARD** Control eight 12V/1A relays by Infra Red (IR) remote control over a 20m range in sunlight. 8 relays turn on only, the other 2 toggle on/off. 3 operation ranges determined by jumpers. Transmitter case & all components provided. Receiver PCB 76x89mm. 3072KT £52.95

PRODUCT FEATURE

COMPUTER TEMPERATURE DATA LOGGER

PC serial port controlled 4-channel temperature meter (either deg C or F). Requires no external power. Allows continuous temperature data logging of up to four temperature sensors located 200m+ from motherboard/PC. Ideal use for old 386/486 computers. Users can tailor input data stream to suit their purpose (dump it to a spreadsheet or write your own BASIC programs using the INPUT command to grab the readings). PCB just 38mm x 38mm. Sensors connect via four 3-pin headers. 4 header cables supplied but only one DS18S20 sensor. Kit software available free from our website. ORDERING: 3145KT £23.95 (kit form); AS3145 £29.95 (assembled); Additional DS18S20 sensors £4.95 each

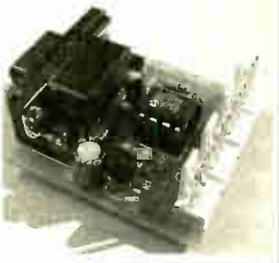

- **SOUND EFFECTS GENERATOR** Easy to build. Create an almost infinite variety of interesting/unusual sound effects from birds chirping to sirens. 9VDC. PCB 54x85mm. 1045KT £8.95
- **ROBOT VOICE EFFECT** Make your voice sound similar to a robot or Daria! Great fun for discos, school plays, theatre productions, radio stations & playing jokes on your friends when answering the phone! PCB 42x71mm. 1131KT £8.95
- **AUDIO TO LIGHT MODULATOR** Controls intensity of one or more lights in response to an audio input. Safe, modern opto-coupler design. Mains voltage experience required. 3012KT £8.95
- **MUSIC BOX** Activated by light. Plays 8 Christmas songs and 5 other tunes. 3104KT £7.95
- **20 SECOND VOICE RECORDER** Uses non-volatile memory - no battery backup needed. Record/replay messages over & over. Playback as required to greet customers etc. Volume control & built-in mic. 5VDC. PCB 50x73mm. 3131KT £12.95
- **TRAIN SOUNDS** 4 selectable sounds: whistle blowing, level crossing bell, 'clackety-clack' & 4 in sequence. SG01M £6.95

- **PC CONTROLLED RELAY BOARD** Convert any 286 upward PC into a dedicated automatic controller to independently turn on/off up to eight lights, motors & other devices around the home, office, laboratory or factory. Each relay output is capable of switching 250VAC/4A. A suite of DOS and Windows control programs are provided together with all components (except box and PC cable). 12VDC. PCB 70x200mm. 3074KT £31.95
- **2 CHANNEL UHF RELAY SWITCH** Contains the same transmitter/receiver pair as 30A15 below plus the components and PCB to control two 240VAC/10A relays (also supplied) Ultra bright LEDs used to indicate relay status. 3082KT £27.95
- **TRANSMITTER RECEIVER PAIR 2-button keyfob** style 300-375MHz Tx with 30m range. Receiver encoder module with matched decoder IC. Components must be built into a circuit like kit 3082 above. 30A15 £14.95
- **PIC 16C71 FOUR SERVO MOTOR DRIVER** Simultaneously control up to 4 servo motors. Software & all components (except servo/control pots) supplied. 5VDC. PCB 50x70mm. 3102KT £15.95
- **UNIPOLAR STEPPER MOTOR DRIVER** for any 5/6/8 lead motor. Fast/slow & single step rates. Direction control & on/off switch. Wave, 2-phase & half-wave step modes. 4 LED indicators. PCB 50x65mm. 3109KT £14.95
- **PC CONTROLLED STEPPER MOTOR DRIVER** Control two unipolar stepper motors (3A max. each) via PC printer port. Wave, 2-phase & half-wave step modes. Software accepts 4 digital inputs from external switches & will single step motors. PCB fits in D-shell case provided. 3113KT £17.95
- **12-BIT PC DATA ACQUISITION/CONTROL UNIT** Similar to kit 3093 above but uses a 12 bit Analogue-to-Digital Converter (ADC) with internal analogue multiplexer. Reads 8 single ended channels or 4 differential inputs or a mixture of both. Analogue inputs read 0-4V. Four TTL/CMOS compatible digital inputs/outputs. ADC conversion time <10us. Software (C, QB & Wln), extended D shell case & all components (except sensors & cable) provided. 3118KT £52.95
- **LIQUID LEVEL SENSOR/RAIN ALARM** Will indicate fluid levels or simply the presence of fluid. Relay output to control a pump to add/remove water when it reaches a certain level. 1080KT £5.95
- **AM RADIO KIT 1** Tuned Radio Frequency front-end, single chip AM radio IC & 2 stages of audio amplification. All components inc. speaker provided. PCB 32x102mm. 3063KT £10.95
- **DRILL SPEED CONTROLLER** Adjust the speed of your electric drill according to the job at hand. Suitable for 240V AC mains powered drills up to

X FACTOR PUBLICATIONS

THE EXPERTS IN RARE & UNUSUAL INFORMATION!

Full details of all X-FACTOR PUBLICATIONS can be found in our catalogue. NB: Minimum order charge for reports and plans is £5.00 PLUS normal P&P.

- **SUPER-EAR LISTENING DEVICE** Complete plans to build your own parabolic dish microphone. Listen to distant voices and sounds through open windows and even walls! Made from readily available parts. R002 £3.50
- **LOCKS** - How they work and how to pick them. This fact filled report will teach you more about locks and the art of lock picking than many books we have seen at 4 times the price. Packed with information and illustrations. R008 £3.50
- **RADIO & TV JOKER PLANS** We show you how to build three different circuits for disrupting TV picture and sound plus FM radio! May upset your neighbours & the authorities! DISCRETION REQUIRED. R017 £3.50
- **INFINITY TRANSMITTER PLANS** Complete plans for building the famous Infinity Transmitter. Once installed on the target phone, device acts like a room bug. Just call the target phone & activate the unit to hear all room sounds. Great for home/office security! R019 £3.50
- **THE ETHER BDX CALL INTERCEPT PLANS** Grabs telephone calls out of thin air! No need to wire-in a phone bug. Simply place this device near the phone lines to hear the conversations taking place! R025 £3.00
- **CASH CREATOR BUSINESS REPORTS** Need ideas for making some cash? Well this could be just what you need! You get 40 reports (approx. 800 pages) on floppy disk that give you information on setting up different businesses. You also get valuable reproduction and duplication rights so that you can sell the manuals as you like. R030 £7.50

SURVEILLANCE

High performance surveillance bugs. Room transmitters supplied with sensitive electret microphone & battery holder/cell. All transmitters can be received on an ordinary VHF/FM radio between 88-108MHz. Available in Kit Form (KIT) or Assembled & Tested (AS).

ROOM SURVEILLANCE

- **MTX - MINIATURE 3V TRANSMITTER** Easy to build & guaranteed to transmit 300m @ 3V. Long battery life. 3-5V operation. Only 45x18mm. B 3007KT £6.95 AS3007 £11.95
- **MRTX - MINIATURE 9V TRANSMITTER** Our best selling bug. Super sensitive, high power - 500m range @ 9V (over 1km with 18V supply and better aerial). 45x19mm. 3018KT £7.95 AS3018 £12.95
- **HPTX - HIGH POWER TRANSMITTER** High performance, 2 stage transmitter gives greater stability & higher quality reception. 1000m range. 6-12V DC operation. Size 70x15mm. 3032KT £9.95 AS3032 £18.95
- **MMTX - MICRO-MINIATURE 9V TRANSMITTER** The ultimate bug for its size, performance and price. Just 15x25mm. 500m range @ 9V. Good stability. 6-18V operation. 3051KT £8.95 AS3051 £14.95
- **VTX - VOICE ACTIVATED TRANSMITTER** Operates only when sounds detected. Low standby current. Variable trigger sensitivity. 500m range. Peaking circuit supplied for maximum RF output. On/off switch. 6V operation. Only 63x38mm. 3028KT £12.95 AS3028 £24.95



TELEPHONE SURVEILLANCE

- **M7TX - MINIATURE TELEPHONE TRANSMITTER** Attaches anywhere to phone line. Transmits only when phone is used! Tune-in your radio and hear both parties. 300m range. Uses line as aerial & power source. 20x45mm. 3016KT £8.95 AS3016 £14.95
- **TRF - TELEPHONE RECORDING INTERFACE** Automatically calls all conversions. Connects between phone line & tape recorder (not supplied). Operates recorders with 1.5-12V battery systems. Powered from line. 50x33mm. 3033KT £9.95 AS3033 £18.95
- **TPA - TELEPHONE PICK-UP AMPLIFIER/WIRELESS PHONE BUG** Place pick-up coil on the phone line or near phone earpiece and hear both sides of the conversation. 3055KT £11.95 AS3055 £20.95

HIGH POWER TRANSMITTERS

- **1 WATT FM TRANSMITTER** Easy to construct. Delivers a crisp, clear signal. Two-stage circuit. Kit includes microphone and requires a simple open dipole aerial. 8-30VDC. PCB 42x45mm. 1009KT £14.95
- **4 WATT FM TRANSMITTER** Comprises three RF stages and an audio preamplifier stage. Piezoelectric microphone supplied or you can use a separate preamplifier circuit. Antenna can be an open dipole or Ground Plane. Ideal project for those who wish to get started in the fascinating world of FM broadcasting and want a good basic circuit to experiment with. 12-18VDC. PCB 44x146mm. 1028KT £22.95 AS1028 £34.95
- **15 WATT FM TRANSMITTER (PRE-ASSEMBLED & TESTED)** Four transistor based stages with Philips BL8 in final stage. 15 Watts RF power on the air. 80-108MHz. Accepts open dipole, Ground Plane, 5/8, J or YAGI antennas. 12-18VDC. PCB 70x220mm. SWS meter needed for alignment. 1021KT £99.95
- **SIMILAR TO ABOVE BUT 25W Output.** 1031KT £109.95

700W power. PCB: 48mm x 65mm. Box provided. 6074KT £17.95

- **3 INPUT MONO MIXER** Independent level control for each input and separate bass/treble controls. Input sensitivity: 240mV. 18V DC. PCB: 60mm x 185mm. 1052KT £16.95
- **NEGATIVE/POSITIVE ION GENERATOR** Standard Cockcroft-Walton multiplier circuit. Mains voltage experience required. 3057KT £10.95
- **LED DICE** Classic intro to electronics & circuit analysis. 7 LEDs simulate dice roll, slow down & land on a number at random. 555 IC circuit. 3003KT £9.95
- **STAIRWAY TO HEAVEN** Tests hand-eye co-ordination. Press switch when green segment of LED lights to climb the stairway - miss & start again! Good intro to several basic circuits. 3005KT £9.95
- **ROULETTE LED 'Ball'** spins round the wheel, slows down & drops into a slot. 10 LEDs. Good intro to CMOS decade counters & Op-Amps. 3006KT £10.95
- **12V XENON TUBE FLASHER TRANSFORMER** steps up a 12V supply to flash a 25mm Xenon tube. Adjustable flash rate. 3163KT £13.95
- **LED FLASHER 1** 5 ultra bright red LEDs flash in 7 selectable patterns. 3037MKT £5.95
- **LED FLASHER 2** Similar to above but flash in sequence or randomly. Ideal for model railways. 3052MKT £5.95
- **INTRODUCTION TO PIC PROGRAMMING.** Learn programming from scratch. Programming hardware, a P16F84 chip and a two-part, practical, hands-on tutorial series are provided. 3081KT £21.95
- **SERIAL PIC PROGRAMMER** for all 8/18/28/40 pin DIP serial programmed PICs. Shareware software supplied limited to programming 256 bytes (registration costs £14.95). 3096KT £12.95
- **ATMEL 89C051 PROGRAMMER** Simple-to-use yet powerful programmer for the Atmel 89C1051, 89C2051 & 89C4051 uCs. Programmer does NOT require special software other than a terminal emulator program (built into Windows). Can be used with ANY computer/operating system. 3121KT £24.95
- **3V/1.5V TO 9V BATTERY CONVERTER** Replace expensive 9V batteries with economic 1.5V batteries. IC based circuit steps up 1 or 2 'AA' batteries to give 9V/18mA. 3035KT £5.95
- **STABILISED POWER SUPPLY 3-30V/2.5A** Ideal for hobbyist & professional laboratory. Very reliable & versatile design at an extremely reasonable price. Short circuit protection. Variable DC voltages (3-30V). Rated output 2.5 Amps. Large heatsink supplied. You just supply a 24VAC/3A transformer. PCB 55x112mm. Mains operation. 1007KT £16.95.

- **STABILISED POWER SUPPLY 2-30V/5A** As kit 1007 above but rated at 5Amp. Requires a 24VAC/5A transformer. 1096KT £27.95.
- **MOTORBIKE ALARM** Uses a reliable vibration sensor (adjustable sensitivity) to detect movement of the bike to trigger the alarm & switch the output relay to which a siren, bikes horn, indicators or other warning device can be attached. Auto-reset. 6-12VDC. PCB 57x64mm. 1011KT £11.95. Box 2011BX £7.00
- **CAR ALARM SYSTEM** Protect your car from theft. Features vibration sensor, courtesy/boot light voltage drop sensor and bonnet/boot earth switch sensor. Entry/exit delays, auto-reset and adjustable alarm duration. 6-12V DC. PCB: 47mm x 55mm. 1019KT £11.95. Box 2019BX £8.00
- **PIEZO SCREAMER** 110dB of ear piercing noise. Fits in box with 2 x 35mm piezo elements built into their own resonant cavity. Use as an alarm siren or just for fun! 6-9VDC. 3015KT £10.95
- **COMBINATION LOCK** Versatile electronic lock comprising main circuit & separate keypad for remote opening of lock. Relay supplied. 3029KT £10.95
- **ULTRASONIC MOVEMENT DETECTOR** Crystal locked detector frequency for stability & reliability. PCB 75x40mm houses all components. 4-7m range. Adjustable sensitivity. Output will drive external relay/circuits. 9VDC. 3049KT £13.95
- **PIR DETECTOR MODULE** 3-lead assembled unit just 25x35mm as used in commercial burglar alarm systems. 3076KT £8.95
- **INFRARED SECURITY BEAM** When the invisible IR beam is broken a relay is tripped that can be used to sound a bell or alarm. 25 metre range. Mains rated relays provided. 12VDC operation. 3100KT £12.95
- **SQUARE WAVE OSCILLATOR** Generates square waves at 6 preset frequencies in factors of 10 from 1Hz-100KHz. Visual output indicator. 5-18VDC. Box provided. 3111KT £8.95
- **PC DRIVEN POCKET SAMPLER/DATA LOGGER** Analogue voltage sampler records voltages up to 2V or 20V over periods from milli-seconds to months. Can also be used as a simple digital scope to examine audio & other signals up to about 5KHz. Software & D-shell case provided. 3112KT £18.95
- **20 MHz FUNCTION GENERATOR** Square, triangular and sine waveform up to 20MHz over 3 ranges using 'coarse' and 'fine' frequency adjustment controls. Adjustable output from 0-2V p-p. A TTL output is also provided for connection to a frequency meter. Uses MAX038 IC. Plastic case with printed front/rear panels & all components provided. 7-12VAC. 3101KT £69.95

BARGAIN BUY!!

30-In-ONE Electronic Projects Lab

Great introduction to electronics. Ideal for the budding electronics expert! Build a radio, burglar alarm, water detector, Morse code practice circuit, simple computer circuits, and much more! NO soldering, tools or previous electronics knowledge required. Circuits can be built and unassembled repeatedly. Comprehensive 68-page manual with explanations, schematics and assembly diagrams. Suitable for age 10+. Excellent for schools. Requires 2 x AA batteries. Order Code EPL030 ONLY £14.95 (phone for bulk discounts). 130, 300 and 500-in-ONE also available.



WEB: <http://www.QuasarElectronics.com>
email: epesales@QuasarElectronics.com

Secure Online Ordering Facilities
Full Kit Listing, Descriptions & Photos
Kit Documentation & Software Downloads

Credit Card Sales! 01279 467799

Enhanced 'PICALL' ISP PIC Programmer

Kit will program virtually ALL 8 to 40 pin* serial and parallel programmed PIC micro-controllers. Connects to PC parallel port. Supplied with fully functional pre-registered PICALL DOS and WINDOWS AVR software packages, all components and high quality DSPTH board. Also programs certain ATMEL AVR, SCENIX SX and EEPROM 24C devices. New devices can be added to the software as they are released. Blank chip auto detect feature for super-fast bulk programming. Hardware now supports ISP programming. *A 40 pin wide ZIF socket is required to program 0-3in. devices (Order Code AZIF40 @ £15.00).



3144KT	Enhanced 'PICALL' ISP PIC Programmer	£64.95
AS3144	Assembled Enhanced 'PICALL' ISP PIC Programmer	£74.95
AS3144ZIF	Assembled Enhanced 'PICALL' ISP PIC Programmer c/w ZIF socket	£89.95

ATMEL AVR Programmer




Powerful programmer for Atmel AT90Sxxxx (AVR) micro controller family. All fuse and lock bits are programmable. Connects to serial port. Can be used with ANY computer and operating system. Two LEDs to indicate programming status. Supports 20-pin DIP AT90S1200 & AT90S2313 and 40-pin DIP AT90S4414 & AT90S8515 devices. NO special software required – uses any terminal emulator program (built into Windows). The programmer is supported by BASCOM-AVR Basic Compiler software (see website for details).

3122KT	ATMEL AVR Programmer	£24.95
AS3122	Assembled 3122	£39.95

Atmel 89Cx051 and 89xxx programmers also available.

PC Data Acquisition & Control Unit

With this kit you can use a PC parallel port as a real world interface. Unit can be connected to a mixture of analogue and digital inputs from pressure, temperature, movement, sound, light intensity, weight sensors, etc (not supplied) to sensing switch and relay states. It can then process the input data and use the information to control up to 11 physical devices such as motors, sirens, other relays, servo motors & two-stepper motors.

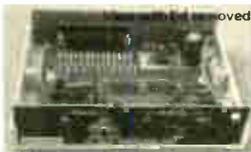

FEATURES:

- 8 Digital Outputs: Open collector, 500mA, 33V max.
- 16 Digital Inputs: 20V max. Protection 1K in series, 5-1V Zener to ground.
- 11 Analogue Inputs: 0-5V, 10 bit (5mV/step.)
- 1 Analogue Output: 0-2.5V or 0-10V. 8 bit (20mV/step.)

All components provided including a plastic case (140mm x 110mm x 35mm) with pre-punched and silk screened front/rear panels to give a professional and attractive finish (see photo) with screen printed front & rear panels supplied. Software utilities & programming examples supplied.

3093KT	PC Data Acquisition & Control Unit	£99.95
AS3093	Assembled 3093	£124.95

See opposite page for ordering information on these kits

ABC Mini 'Hotchip' Board



Currently learning about microcontrollers? Need to do something more than flash a LED or sound a buzzer? The ABC Mini 'Hotchip' Board is based on Atmel's AVR 8535 RISC technology and will interest both the beginner and expert alike. Beginners will find that they can write and test a simple program, using the BASIC programming language, within an hour or two of connecting it up.

Experts will like the power and flexibility of the ATMEL microcontroller, as well as the ease with which the little Hot Chip board can be "designed-in" to a project. The ABC Mini Board 'Starter Pack' includes just about everything you need to get up and experimenting right away. On the hardware side, there's a pre-assembled micro controller PC board with both parallel and serial cables for connection to your PC. Windows software included on CD-ROM features an Assembler, BASIC compiler and in-system programmer. The pre-assembled boards only are also available separately.

ABCMINISP	ABC MINI Starter Pack	£64.95
ABCMINIB	ABC MINI Board Only	£39.95

Advanced 32-bit Schematic Capture and Simulation Visual Design Studio



Serial Port Isolated I/O Controller

Kit provides eight relay outputs capable of switching 4 amps at mains voltages and four optically isolated inputs. Can be used in a variety of control and sensing applications including load switching, external switch input sensing, contact closure and external voltage sensing.



Programmed via a computer serial port, it is compatible with ANY computer & operating system. After programming, PC can be disconnected. Serial cable can be up to 35m long, allowing 'remote' control. User can easily write batch file programs to control the kit using simple text commands. NO special software required – uses any terminal emulator program (built into Windows). All components provided including a plastic case with pre-punched and silk screened front/rear panels to give a professional and attractive finish (see photo).

3108KT	Serial Port Isolated I/O Controller Kit	£54.95
AS3108	Assembled Serial Port Isolated I/O Controller	£69.95

SPECIAL OFFERS



TEKTRONIX 2445A
4-ch 150MHz delay,
cursors etc. Supplied
with 2 Tektronix probes.
ONLY **£425**

TEKTRONIX 2232 Digital Storage Scope. £252
Dual Trace, 100MHz, 100MS with probes. £425
H.P. 54501A Dig. Oscilloscope, 100MHz 4-Ch £425
H.P. 3312A Function Gen., 0-1Hz-13MHz,
AM/FM Sweep/Tri/Gate/Burst etc. £300
FARNELL Dual PSU XA35-2T, 0-35V, 0-2A,
Twice QMD, I.c.d. Display £180
CIRIUS CRL254 Sound Level Meter
with Calibrator 80-120dB, LEO £150
FARNELL AMM255 Automatic Mo
Meter, 1-5MHz-2GHz, unused £300
FARNELL DSG1 Low Frequency Syn Sig. Gen.,
0-001Hz-99.99kHz, low distortion, £95
TTU/Square/Pulse Outputs etc. £125
FLUKE 8060A Handheld True RMS, DMM,
4 1/2 digit. As new £150, used £95
BECKMAN HD110 Handheld 3 1/2 digit DMM, 28
ranges, with battery, leads and carrying case. £60

H.P. 3310A Function Gen., 0-005Hz-5MHz,
Sine/Sq/Tri/Ramp/Pulse £125
FARNELL LF44 Sine/Sq Oscillator, 10Hz-1MHz,
low distortion, TTL output, Amplifier Meter £125
H.P. 545A Logic Probe with 546A Logic
Pulsar and 547A Current Tracer. £90
FLUKE 77 Multimeter, 3 1/2-digit, handheld £60
FLUKE 77 Series 11 £70
HEME 1000 L.C.D. Clamp Meter, 00-1000A,
in carrying case £60

BLACK STAR ORION PAL/TV Colour Pattern
Generator, from £75-£125
THURLBY/THANDER TG210 Function Generator,
0-002Hz-2MHz, TTL etc. £80-£95
THURLBY THANDER P.S.U. PL320QMD, 0V-32V,
0A-2A Twice (late colours) £200

Datron 1061 **£150**
High Quality 5.5 Digit Bench
Multimeter
True RMS/4 wire Res/Current Converter/IEEE

Datron 1061A **£225**
High Quality 6 1/2 digit Bench
Multimeter
True RMS/4 wire/Current Converter

Racal Receiver RA1772 **£250**
50kHz-30MHz
L.E.D. Display, Basically working.

MARCONI 2019A



**AM/FM SYNTHESISED SIGNAL
GENERATOR**
80 kHz - 1040MHz
NOW ONLY **£400**

MARCONI 893C AF Power Meter, Sinad Measurement
Unused £100, Used £50
MARCONI 893B, No Sinad £30
MARCONI 2610 True RMS Voltmeter, Autorangeing,
5Hz-25MHz £195
GOULD J3B Sine/Sq Osc., 10Hz-100kHz,
low distortion £75-£125
AVO 8 Mk. 6 in Every Ready case, with leads etc. £80
Other AVOs from £50
GOODWILL GVT427 Dual Ch AC Millivoltmeter,
10mV-300V in 12 ranges, Freq 10Hz-1MHz £100-£125
SOLARTRON 7150 DMM 6 1/2-digit
Tri RMS-IEEE £95-£150
SOLARTRON 7150 Plus £200

HIGH QUALITY RACAL COUNTERS
9904 Universal Timer Counter, 50MHz £50
9916 Counter, 10Hz-520MHz £75
9918 Counter, 10Hz-560MHz, 9-digit £50
WAYNE KERR 8424 Component Bridge £125
RACAL/AIM 9343M LCR Datebridge.
Digital Automeasurement of R, C, L, Q, D £200
HUNTRON TRACKER Model 1000 £125
FLUKE 8050A 4.5 Digit, 2A True RMS £75
FLUKE 8010A 3.5 Digit, 10A £50
FLUKE 8012A 3.5 Digit, 2A £40

Racal 9008 ONLY **£95**
Automatic Modulation Meter,
AM/FM 1-5MHz-2GHz

Portable Appliance Tester **£180**
Megger Pat 2

H.P. 6012B DC PSU 0-60V, 0-50A, 1000W £1000
FARNELL AP60/50 1kW Autorangeing £1000
FARNELL H60/50 0-60V 0-50A £750
FARNELL H60/25 0-60V, 0-25A £400
Power Supply HPS3010, 0-30V, 0-10A £140
FARNELL L30-2 0-30V, 0-2A £80
FARNELL L30-1 0-30V, 0-1A £60
Many other Power Supplies available

GOULD OS300



Dual Trace, 20MHz
Tested with Manual
ONLY **£95**

OSCILLOSCOPES
TEKTRONIX TDS350 dual trace, 200MHz, 1G/S Unused £1500
TEKTRONIX TDS320 dual trace, 100MHz, 500MS/£1200
TEKTRONIX TDS310 dual trace, 50MHz, 200MS/£950
LECROY 9400A dual trace, 175MHz, 5GS £1500
HITACHI VC6523, d/trace, 20MHz, 20MS, delay etc Unused £800
PHILIPS PM3092 2-2-ch, 200MHz, delay etc £800 as new £950
PHILIPS PM3062 2-2-ch, 100MHz, delay etc £700 as new £800
TEKTRONIX TA5455 dual trace, 100MHz, delay etc £750
TEKTRONIX 2465B 4-ch, 400MHz, delay cursors etc £1500
TEKTRONIX 2465 4-ch, 300MHz, delay cursors etc £900
TEKTRONIX 2445A/B 4-ch 150MHz, delay cursors etc £500-£900
TEKTRONIX 468 Dig Storage, dual trace, 100MHz, delay £450
TEKTRONIX 466 Analogous Storage, dual trace, 100MHz £250
TEKTRONIX 465 dual trace, 350MHz, delay sweep £550
TEKTRONIX 475 dual trace, 200MHz, delay sweep £400
TEKTRONIX 468B dual trace, 100MHz, delay sweep £325
PHILIPS PM3217 dual trace, 50MHz, delay £200-£250
GOULD OS1100 dual trace, 30MHz, delay £150
HAMEG HM303 dual trace, 30MHz component tester £275
HAMEG HM203.7 dual trace, 20MHz component tester £200
FARNELL OTV20 dual trace, 20MHz component tester £125
Many other Oscilloscopes available

MARCONI 2022E Synth AM/FM Sig Gen £325-£750
10kHz-1.01GHz i.c.d. display etc
H.P. 8657A Synth sig gen, 100kHz-1040MHz £2000
H.P. 8656B Synth sig gen, 100kHz-990MHz £1350
H.P. 8656A Synth sig gen, 100kHz-990MHz £995
RAS APN62 Synth, 1Hz-260kHz sig. gen.,
balanced/unbalanced output, I.c.d display £425
PHILIPS PM3328 sig gen, 100kHz-180MHz with
200MHz, freq counter, IEEE £550
RACAL 9081 Synth AM/FM sig gen, 5kHz-1024MHz £1500
H.P. 3325A Synth function gen, 21MHz £600
MARCONI 6500 Amplitude Analyser £1500
H.P. 4192A Impedance Analyser £5000
H.P. 4275A LCR Meter, 10kHz-10MHz £2750
H.P. 8605A Distortion Analyser £1000
WAYNE KERR 3245 Inductance Analyser £2000
H.P. 8112A Pulse Generator, 50MHz £1250
MARCONI 2440 Frequency Counter, 20GHz £1000
H.P. 5330B Frequency Counter, 20GHz £2000
H.P. 5342A 10Hz-18GHz Frequency Counter £800
H.P. 1650B Logic Analyser, 80-channel £1000
MARCONI 2035 Mod Meter, 500kHz-2GHz £750

RADIO COMMUNICATIONS TEST SETS
MARCONI 2955/2955A From £1500
RHODE & SCHWARZ CMT 0-1-1000MHz £2000
SCHLUMBERGER 4040 £300

JUST IN

H.P. 8063B DC Electronic Load, 3-240V0-10A, 250W £400
H.P. 86312A PSU, 0-20V0-2A £400
H.P. 86311B PSU, 0-15V0-3A £750
H.P. 86309D PSU Dual, 0-15, 0-3A0-12, 0-1-5A £500
H.P. 8632B PSU, 0-20V0-5A £850
H.P. 8623A PSU, triple output ranging from 0-7V 0-5A to
0-20V 0-4A £300/£450
H.P./AGILENT 34401A DMM 6 1/2 digit £275
H.P. 3478A DMM 5 1/2 digit £400
FLUKE 45 DMM dual display £950
KETHLEY 2010 DMM 7 1/2 digit £1250
KETHLEY 617 Programmable Electrometer £1500
H.P. 4338B Milliohmmeter £500
RACAL Counter type 1999 2 6GHz £380
H.P. Counter type 33131A 3GHz £1250
H.P./AGILENT 33120A Func Gen/ARB, 100Hz-15MHz

SONY/TEKTRONIX AFG320 Arbitrary Func. Gen £1250
H.P. 8694A Syn. Function Gen. DC-600kHz £1000/£1250
BLACK STAR JUPITOR 2010 Func. Gen, 0.2Hz-2MHz with
frequency counter £140
H.P. 8116A Pulse Generator, 1mV-50MHz £1950
H.P. 8657B Syn Sig. Gen, 0-1-2080MHz £2500
CO-AXIAL SWITCH, 1-5GHz £40
IEEE CABLES £10

SPECTRUM ANALYSERS

H.P. 8561B 50Hz-6.5GHz £3500
H.P. 8560A 50Hz-2.9GHz synthesised £4500/£5000
H.P. 8594E 9kHz-2.9GHz £3500
H.P. 8591E 1MHz-1.8GHz, 75 Ohm £2250
H.P. 8591A 1MHz-1.8GHz, 50 Ohm £1250
H.P. 8558A with Main Frame, 100kHz-1500MHz £3000
H.P. 3585A 20Hz-40MHz £800
H.P. 3580A 5Hz-50MHz £300
ADVANTEST RA131B 10kHz-3.5GHz £1500
EATON/ALTECH 757 0-001-22GHz £2000
MARCONI Z382 100Hz-400MHz, high resolution from £500
MARCONI Z370 30Hz-110MHz £500
H.P. 182 with 8557 10kHz-350MHz £500
H.P. 141T SYSTEMS from £500
8553 1kHz-110MHz from £750
8554 500kHz-1250MHz from £1000
8555 10MHz-18GHz £500
TEKTRONIX 491 10MHz-12.4GHz £250
H.P. 8443 Tracking Gen/Counter, 110MHz £750
H.P. 8444 OPT 059 £750
B&K 2033R Signal Analyser £2250
H.P. 5372A Frequency & Time Interval Analyser £1250
H.P. 8754A Network Analyser, 4MHz-1300MHz £3000
H.P. 3557A Network Analyser, 5Hz-200MHz £5000
H.P. 53310A Mod Domain Analyser Opt 001/003 £5000
ONO SOKKI CF300 Portable FFT Analyser £1500

STEWART of READING


110 WYKEHAM ROAD, READING, BERKS. RG6 1PL
Telephone: (0118) 9268041. Fax: (0118) 9351696
www.stewart-of-reading.co.uk

Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

Used Equipment – GUARANTEED. Manuals supplied

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists.
Please check availability before ordering.
CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage

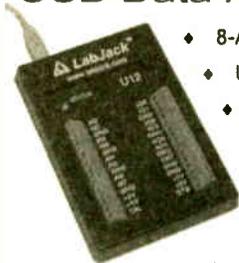The LabJack U12
USB Data Acquisition & Control




- ◆ 8-Analogue in, 2-out, 20 digital I/O, counter
- ◆ USB plug-and-play - no PSU needed
- ◆ FREE scope and logger software
- ◆ Write data to disk, a web page or email
- ◆ Temp/humidity probes, relay boards available
- ◆ Connect 80 LabJacks to one USB port



DAQLab Software

Data Acquisition, Control, HMI, analysis

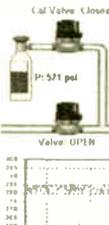

- ◆ Data acquisition and logging
- ◆ User screens with components in text form, on a graph or an animated image.
- ◆ An industrial symbol library with over 3800 images
- ◆ Data analysis features
- ◆ Sequences for automation and control

DAQLAB LITE £49! - DAQLAB FOR LABJACK £89!

All prices exclude VAT and delivery. Order on-line: major credit/debit cards accepted.



AUDON Electronics

www.audon.co.uk +44 (0)115 925 8412 ◊ Fax (0)115 925 9757

FRUSTRATED!

Looking for ICs TRANSISTORS?

A phone call to us could get a result. We offer an extensive range and with a world-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD
ADC AN AM AY BA BC BD BDT BDV BDW BDX BF
BFR BFS BFT BFX BFY BLY BLX BS BR BRX BRY BS
BSS BSV BSW BSX BT BTA BTB BRW BU BUK BT BUY
BUW BUX BUY BUZ CA CD CX CXA DAC DG DM DS
DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA
KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB
MC MDAJ MJE MJF MM MN MPS MPSA MPSP MPSP
MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB
SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD
STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB
TEA TIC TIR TIPL TEA TL TLC TMP TMS TPU U UA
UAA UC UDN ULN UM UPA UPC UPD VNX XR Z ZN
ZTS + many others

We can also offer equivalents (at customers' risk)

We also stock a full range of other electronic components
Mail, phone, Fax Credit Card orders and callers welcome



Connect


Cricklewood Electronics Ltd
40-42 Cricklewood Broadway London NW2 3ET
Tel: 020 8452 0161 Fax: 020 8208 1441

New – Professional versions of WIZ-C and our PIC C Compiler

WIZ – C, The new name for FED's PIXIE development system

What is the WIZ-C Rapid Application Environment ?

- Our PIC C compiler including a new front end.
- An application designer for the FED PIC C Compiler
- Drag a software component on to your design & set up the parameters using check boxes, drop down boxes and edit boxes (see shot right).
- Connect the component to the PIC pins using the mouse
- Select your own C functions to be triggered when events occur (e.g. Byte received, timer overflow etc.)
- Generate the base application automatically and then add your own functional code in C or assembler
- Simulate, Trace at up to 10x the speed of MPLAB
- Supports 14/16 bit core PICS
16F87x, 16C55x, 16C6x, 16F8x, 16C7xx 18Cxx etc.
- C Compiler designed to ANSI C Standards

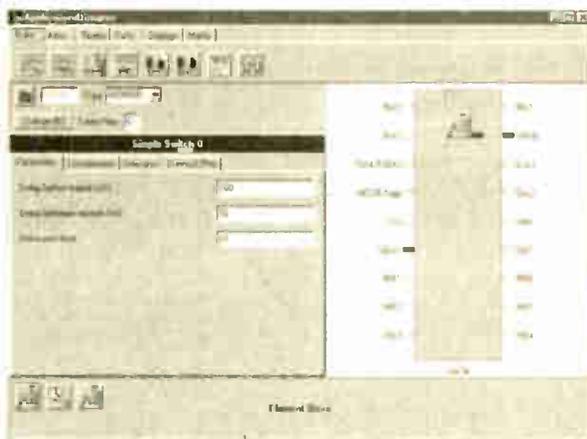

Professional Version Enhancements to our C Compiler and WIZ-C Rapid Application Environment


- Manage and simulate multiple projects together
- Connect PIC pins across projects to allow simulated devices to communicate
- Handle assembler and C projects
- View and inspect variables in native C format
- Inspect all local variables and their values in native C format
- Maintain a history within simulation to back track and determine the past leading up to an event

Prices

WIZ – C Standard - £70.00,
Professional £100.00. Upgrade for existing WIZ-C owners £30.00
PIC C Compiler Standard - £60.00,
Professional £90.00. Upgrade for existing Compiler owners £30.00
Other upgrade options are available together with reduced price bundled packages – see our web site for details

In Circuit Debugger

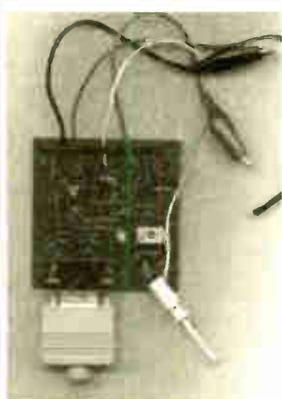Operates with FED PIC Development apps (WIZ-C, WIZASM, C Compiler)



What is In-Circuit Debugging (ICD) ?

In Circuit Debugging is a technique where a monitor program runs on the PIC in the application circuit. The ICD board connects to the PIC and to the PC. From any of our applications it is then possible to set breakpoints on the PIC, run code, single step, examine registers on the real device and change their values. The ICD makes debugging real time applications faster, easier and more accurate than simulation tools available for the PIC.

Features

- Allows real hardware to be examined & programs to be debugged and to be run in real time on your application
- Powered from the application circuit (3.3V to 5V)
- The FED ICD requires only one data I/O pin on the PIC which can be chosen from any of ports B, C or D.
- Can program and re-program applications in circuit
- Up to 3 breakpoints
- Run, single step and step over, run to cursor line, set PC to any value in the program
- Trace execution in the original C or Assembler source files
- Animate operation to trace variables at breakpoints or watch the program executing
- Auto Run application if ICD not connected
- View and change values of PIC special function and general purpose registers, W and the ports.
- Uses a standard (3 wire) serial interface to a PC
- Operates on our development board (right)

Price - £30.00, Requires a copy of WIZASM, our PIC C Compiler, or the WIZ-C applications

Other PIC Products

Development Board





- Handles 40 pin PIC devices
- Includes on board Programmer – no separate programmer required
- 4 LED's on board, Analogue on trimpot, 2 duplex serial ports
- 1A 5V regulator
- 20MHz crystal
- Interfaces for LCD, hex keypad, 32 I/O pins on IDC connectors
- Will run FED PIC BASIC (included on CD)
- I2C EEPROM socket

Price - £45.00 Built and Tested. 16F877-20P £6.00, 18C452/JW £30.00. CD with BASIC & Programmer £5.00

PIC Serial Programmer including 18Cxxx

Handles serially programmed PIC devices in a 40 pin multi-width ZIF socket.
16C55X, 16C6X
16C7X, 16C8x, 16F8X,
12C508, 12C509,
16C72XPIC 14000,
16F87X, 18Cxxx etc

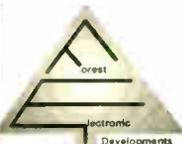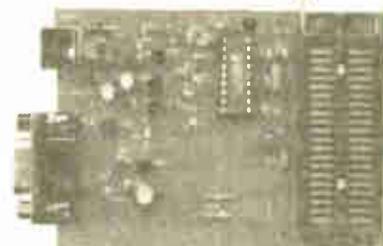Also In-Circuit programming. Operates on PC serial port.
Price : £45/kit £50/built & tested



Forest Electronic Developments 01590-681511 (Voice/Fax)

12 Buldowne Walk, Sway, LYMINGTON, HAMPSHIRE, S041 6DU.

Email – info@fored.co.uk, or sales@fored.co.uk

Web Site – <http://www.fored.co.uk>

Prices are fully inclusive, Add £3.00 for P&P and handling to each order.

Cheques/POs payable to Forest Electronic Developments, or phone with credit card or Switch details.

MAIL ORDER ONLY • CALLERS BY APPOINTMENT

EPE MICROCONTROLLER P.I. TREASURE HUNTER

The latest MAGENTA DESIGN - highly stable & sensitive - with I.C. control of all timing functions and advanced pulse separation techniques.

- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

KIT 847 £63.95

PORTABLE ULTRASONIC PEST SCARER

A powerful 23kHz ultrasound generator in a compact hand-held case. MOSFET output drives a special sealed transducer with intense pulses via a special tuned transformer. Sweeping frequency output is designed to give maximum output without any special setting up.

KIT 842.....£22.56


68000 DEVELOPMENT TRAINING KIT

- NEW PCB DESIGN
- 8MHz 68000 16-BIT BUS
- MANUAL AND SOFTWARE
- 2 SERIAL PORTS
- PIT AND I/O PORT OPTIONS
- 12C PORT OPTIONS

KIT 621

£99.95

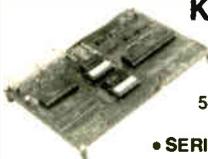- ON BOARD 5V REGULATOR
- PSU £6.99
- SERIAL LEAD £3.99



Stepping Motors

MD38...Mini 48 step...£8.65

MD35...Std 48 step...£9.99

MD200...200 step...£12.99

MD24...Large 200 step...£22.95



PIC PIPE DESCALER

- SIMPLE TO BUILD
- HIGH POWER OUTPUT
- AUDIO & VISUAL MONITORING
- SWEPT FREQUENCY

An affordable circuit which sweeps the incoming water supply with variable frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve lathering ability by altering the way salts in the water behave. Kit includes case, P.C.B., coupling coil and all components. High coil current ensures maximum effect. L.E.D. monitor.



KIT 868 £22.95 POWER UNIT.....£3.99

MICRO PEST SCARER

Our latest design - The ultimate scarer for the garden. Uses special microchip to give random delay and pulse time. Easy to build reliable circuit. Keeps pets/pests away from newly sown areas, play areas, etc. uses power source from 9 to 24 volts.

- RANDOM PULSES
- HIGH POWER
- DUAL OPTION



Plug-in power supply £4.99

KIT 867. £19.99

KIT + SLAVE UNIT. £32.50

WINDICATOR

A novel wind speed indicator with LED readout. Kit comes complete with sensor cups, and weatherproof sensing head. Mains power unit £5.99 extra.

KIT 856. £28.00

★ TENS UNIT ★

DUAL OUTPUT TENS UNIT

As featured in March '97 issue.

Magenta have prepared a FULL KIT for this excellent new project. All components, PCB, hardware and electrodes are included. Designed for simple assembly and testing and providing high level dual output drive.

KIT 866. . Full kit including four electrodes £32.90

Set of 4 spare electrodes £6.50

1000V & 500V INSULATION TESTER



Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms. Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

KIT 848. £32.95

EPE TEACH-IN 2000

Full set of top quality NEW components for this educational series. All parts as specified by EPE. Kit includes breadboard, wire, croc clips, pins and all components for experiments, as listed in introduction to Part 1.

*Batteries and tools not included.

TEACH-IN 2000 -

KIT 879 £44.95

MULTIMETER £14.45

SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube plus instructions for message loading.

KIT 849 £16.99

12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMS at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

KIT 790 £29.90

SUPER BAT DETECTOR

1 WATT O/P, BUILT IN SPEAKER, COMPACT CASE 20kHz-140kHz NEW DESIGN WITH 40kHz MIC.

A new circuit using a 'full-bridge' audio amplifier i.c., internal speaker, and headphone/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.



KIT 861 £24.99

ALSO AVAILABLE Built & Tested. . . £39.99

MOSFET MkII VARIABLE BENCH POWER SUPPLY 0-25V 2.5A

Based on our Mk1 design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.



Kit No. 845 £64.95

EPE PROJECT PICS

Programmed PICs for all* EPE Projects 16C84/18F84/16C71 All **£5.90 each** PIC16F877 now in stock **£10 inc. VAT & postage** (*some projects are copyright)

ULTRASONIC PEST SCARER

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS



- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

KIT 812. £15.00

SIMPLE PIC PROGRAMMER

INCREDIBLE LOW PRICE! Kit 857 **£12.99**

INCLUDES 1-PIC16F84 CHIP
SOFTWARE DISK, LEAD
CONNECTOR, PROFESSIONAL
PC BOARD & INSTRUCTIONS

Power Supply £3.99

EXTRA CHIPS:
PIC 16F84 £4.84

Based on February '96 EPE. Magenta designed PCB and kit. PCB with 'Reset' switch, Program switch, 5V regulator and test L.E.D.s, and connection points for access to all A and B port pins.

PIC 16C84 DISPLAY DRIVER

INCLUDES 1-PIC16F84 WITH DEMO
PROGRAM SOFTWARE DISK, PCB,
INSTRUCTIONS AND 16-CHARAC-
TER 2-LINE
LCD DISPLAY

Kit 860 **£19.99**

Power Supply £3.99

FULL PROGRAM SOURCE CODE
SUPPLIED - DEVELOP
YOUR OWN APPLICATION!

Another super PIC project from Magenta. Supplied with PCB, industry standard 2-LINE x 16-character display, data, all components, and software to include in your own programs. Ideal development base for meters, terminals, calculators, counters, timers - Just waiting for your application!

PIC 16F84 MAINS POWER 4-CHANNEL CONTROLLER & LIGHT CHASER

- WITH PROGRAMMED 16F84 AND DISK WITH SOURCE CODE IN MPASM
- ZERO VOLT SWITCHING MULTIPLE CHASE PATTERNS
- OPTO ISOLATED 5 AMP OUTPUTS
- 12 KEYPAD CONTROL
- SPEED/DIMMING POT.
- HARD-FIRED TRIACS

Now features full 4-channel chaser software on DISK and pre-programmed PIC16F84 chip. Easily re-programmed for your own applications. Software source code is fully 'commented' so that it can be followed easily.

Kit 855 **£39.95**

LOTS OF OTHER APPLICATIONS


8-CHANNEL DATA LOGGER

As featured in Aug./Sept. '99 EPE. Full kit with Magenta redesigned PCB - LCD fits directly on board. Use as Data Logger or as a test bed for many other 16F877 projects. Kit includes programmed chip, 8 EEPROMs, PCB, case and all components.

Kit 877 **£49.95** inc. 8 x 256K EEPROMS

ICEBREAKER

□□□□□□□□□□

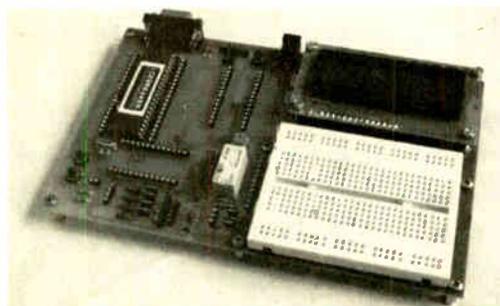

PIC Real Time In-Circuit Emulator

- Icebreaker uses PIC16F877 in circuit debugger
- Links to Standard PC Serial Port (lead supplied)
- Windows™ (95+) Software included
- Works with MPASM and MPLAB Microchip software
- 16 x 2 L.C.D., Breadboard, Relay, I/O devices and patch leads supplied

As featured in March '00 EPE. Ideal for beginners AND advanced users. Programs can be written, assembled, downloaded into the microcontroller and run at full speed (up to 20MHz), or one step at a time.

Full emulation means that all I/O ports respond exactly and immediately, reading and driving external hardware.

Features include: Reset; Halt on external pulse, Set Breakpoint; Examine and Change registers, EEPROM and program memory; Load program, Single Step with display of Status, W register, Program counter, and user selected 'Watch Window' registers.

Kit 900 . . . **£34.99**

POWER SUPPLY £3.99 STEPPING MOTOR £5.99

EPE PIC TOOLKIT 3

NEW

- THE LATEST TOOLKIT BOARD - 8, 18, 28 AND 40-PIN CHIPS
- MAGENTA DESIGNED P.C.B. WITH COMPONENT LAYOUT AND EXTRAS
- L.C.D., BREADBOARD AND PIC CHIP INCLUDED
- ALL TOP QUALITY COMPONENTS AND SOFTWARE SUPPLIED

Kit 880 . . . **£34.99** with 16F84 . . . **£39.99** with 16F877

PIC TOOLKIT V2

- SUPER UPGRADE FROM V1 • 18, 28 AND 40-PIN CHIPS
- READ, WRITE, ASSEMBLE & DISASSEMBLE PICS
- SIMPLE POWER SUPPLY OPTIONS 5V-20V
- ALL SWITCHING UNDER SOFTWARE CONTROL
- MAGENTA DESIGNED PCB HAS TERMINAL PINS AND OSCILLATOR CONNECTIONS FOR ALL CHIPS
- INCLUDES SOFTWARE AND PIC CHIP

Kit 878 . . . **£22.99** with 16F84 . . . **£29.99** with 16F877

EPE PIC Tutorial

At last! A Real, Practical, Hands-On Series

- Learn Programming from scratch using PIC16F84
- Start by lighting l.e.d.s and do 30 tutorials to Sound Generation, Data Display, and a Security System.
- PIC TUTOR Board with Switches, l.e.d.s, and on board programmer

PIC TUTOR BOARD KIT

Includes: PIC16F84 Chip, TOP Quality PCB printed with Component Layout and all components* (*not ZIF Socket or Displays). Included with the Magenta Kit is a disk with Test and Demonstration routines.

Kit 870 **£27.95**, Built & Tested **£42.95**

Optional: Power Supply - **£3.99**, ZIF Socket - **£9.99**

LCD Display **£7.99** LED Display **£6.99**

Reprints Mar/Apr/May 98 - **£3.00** set 3

SUPER PIC PROGRAMMER

- READS, PROGRAMS, AND VERIFIES
- WINDOWS® SOFTWARE
- PIC16C6X, 7X, AND 8X
- USES ANY PC PARALLEL PORT
- USES STANDARD MICROCHIP • HEX FILES
- OPTIONAL DISASSEMBLER SOFTWARE (EXTRA)
- PCB, LEAD, ALL COMPONENTS, TURNED-PIN SOCKETS FOR 18, 28, AND 40 PIN ICs

• SEND FOR DETAILED INFORMATION - A SUPERB PRODUCT AT AN UNBEATABLE LOW PRICE.

Kit 862 **£29.99**

Power Supply £3.99

DISASSEMBLER SOFTWARE **£11.75**

PIC STEPPING MOTOR DRIVER

INCLUDES PCB, PIC16F84 WITH DEMO PROGRAM, SOFTWARE DISC, INSTRUCTIONS AND MOTOR.

Kit 863 **£18.99**

FULL SOURCE CODE SUPPLIED ALSO USE FOR DRIVING OTHER POWER DEVICES e.g. SOLENOIDS

Another NEW Magenta PIC project. Drives any 4-phase unipolar motor - up to 24V and 1A. Kit includes all components and 48 step motor. Chip is pre-programmed with demo software, then write your own, and re-program the same chip! Circuit accepts inputs from switches etc and drives motor in response. Also runs standard demo sequence from memory.

MAGENTA

All prices include VAT. Add £3.00 p&p. Next day **£6.99**

Tel: 01283 565435 Fax: 01283 546932 E-mail: sales@magenta2000.co.uk



Station Road, Cullercoats, Tyne & Wear, NE30 4PQ

Prices Exclude Vat @17.5%
UK Carriage £1.50 (less than 1kg)
£3.50 greater than 1kg
Cheques / Postal orders payable to
ESR Electronic Components
PLEASE ADD CARRIAGE & VAT TO ALL ORDERS

See Next / Last Months Ad for
ELECTRONIC COMPONENTS

DIL Sockets

6 Pin DIL 0.3"	£0.07
8 Pin DIL 0.3"	£0.06
14 Pin DIL 0.3"	£0.11
16 Pin DIL 0.3"	£0.11
18 Pin DIL 0.3"	£0.12
20 Pin DIL 0.3"	£0.12
24 Pin DIL 0.6"	£0.12
28 Pin DIL 0.6"	£0.13
40 Pin DIL 0.6"	£0.19

Stamped Pin

6 Pin DIL 0.3"	£0.11
14 Pin DIL 0.3"	£0.20
16 Pin DIL 0.3"	£0.23
18 Pin DIL 0.3"	£0.25
20 Pin DIL 0.3"	£0.28
24 Pin DIL 0.6"	£0.35
28 Pin DIL 0.6"	£0.39

ZIF Sockets

Universal ZIF DIL Sockets	
24 Way 0.3-0.6"	£5.78
28 Way 0.3-0.6"	£6.60
32 Way 0.3-0.6"	£7.50
40 Way 0.3-0.6"	£8.93

Transistor Sockets

T018-4 Base Socket	£0.24
T05 Base Socket	£0.24

IDC Cable Sockets

10 Way Socket	£0.23
14 Way Socket	£0.35
16 Way Socket	£0.37
20 Way Socket	£0.37
24 Way Socket	£0.38
26 Way Socket	£0.39
40 Way Socket	£0.55
50 Way Socket	£0.80

IDC Cable Plugs

10 Way Plug	£0.52
14 Way Plug	£0.58
16 Way Plug	£0.62
20 Way Plug	£0.66
26 Way Plug	£0.70
34 Way Plug	£0.80
40 Way Plug	£0.92
50 Way Plug	£1.12

PCB Box Headers

10 Way Straight	£0.23
14 Way Straight	£0.33
16 Way Straight	£0.32
20 Way Straight	£0.41
26 Way Straight	£0.55
34 Way Straight	£0.68
40 Way Straight	£0.68
50 Way Straight	£1.03
10 Way 90	£0.32
14 Way 90	£0.39
16 Way 90	£0.42
20 Way 90	£0.50
26 Way 90	£0.63
34 Way 90	£0.81
40 Way 90	£1.17
50 Way 90	£1.14

PCB Latch Headers

10 Way Straight	£0.41
14 Way Straight	£0.45
16 Way Straight	£0.51
20 Way Straight	£0.55
26 Way Straight	£0.73
34 Way Straight	£0.88
40 Way Straight	£0.92
50 Way Straight	£1.27
10 Way 90	£0.46
14 Way 90	£0.48
16 Way 90	£0.54
20 Way 90	£0.59
26 Way 90	£0.81
34 Way 90	£1.03
40 Way 90	£1.23
50 Way 90	£1.41

DIL Headers

14 Way DIL	£0.51
16 Way DIL	£0.53
24 Way DIL	£0.90
40 Way DIL	£1.37

Transistor Headers

10 Way Transistor	£0.42
14 Way Transistor	£0.42
16 Way Transistor	£0.48
20 Way Transistor	£0.48
26 Way Transistor	£0.52
34 Way Transistor	£0.56
40 Way Transistor	£0.63
50 Way Transistor	£0.84

D Type Connectors

9 Way Mole Plug	£0.20
9 Way Female Socket	£0.20
15 Way Mole Plug	£0.28
15 Way Female Socket	£0.29
15 Way H.D. Plug	£0.48
15 Way H.D. Socket	£0.44
23 Way Female Socket	£0.50
25 Way Mole Plug	£0.30
25 Way Female Skt	£0.35

Solder Bucket

9 Way Mole Plug	£0.20
9 Way Female Socket	£0.20
15 Way Mole Plug	£0.28
15 Way Female Socket	£0.29
15 Way H.D. Plug	£0.48
15 Way H.D. Socket	£0.44
23 Way Female Socket	£0.50
25 Way Mole Plug	£0.30
25 Way Female Skt	£0.35

IC Ribbon Mounting

9 Way Mole Plug	£1.08
9 Way Female Socket	£0.93
15 Way Mole Plug	£1.30
15 Way Female Socket	£1.32
25 Way Mole Plug	£1.10
25 Way Female Socket	£1.13
IDC Crimp Tool	£11.80

Right Angled PCB

9 Way Mole Plug	£0.33
9 Way Female Socket	£0.33
15 Way Male Plug	£0.39
15 Way Female Socket	£0.39
15 Way H.D. Socket	£0.58
25 Way Male Plug	£0.50
25 Way Female Socket	£0.50

Plastic D Covers

9 Way Cover - Grey	£0.29
9 Way Cover - Black	£0.30
15 Way Cover - Grey	£0.32
15 Way Cover - Black	£0.38
23 Way Cover - Grey	£0.34
23 Way Cover - Black	£0.34
25 Way Cover - Grey	£0.34
25 Way Cover - Black	£0.37
9 to 9 Cover / Case	£0.80
25 to 25 Cover / Case	£0.84
9 to 25 Cover / Case	£0.80

Audio Connectors

2.5mm Jack Plug	£0.25
2.5mm Line Socket	£0.16
2.5mm Chassis Socket	£0.20
3.5mm Mono Plug	£0.20
3.5mm Mono Line Skt	£0.30
3.5mm Mono Chassis	£0.14
3.5mm Stereo Plug	£0.35
3.5mm Stereo Line Skt	£0.37
3.5mm Stereo Chassis	£0.22
4" Mono Plug	£0.34
4" Mono Line Socket	£0.35
4" Mono Chassis Skt	£0.37
4" Stereo Plug	£0.40
4" Stereo Line Socket	£0.38
4" Stereo Chassis Skt	£0.38

Phono Series

Red Line Plug	£0.20
Black Line Plug	£0.20
Yellow Line Plug	£0.20
White Line Plug	£0.20
Red Line Socket	£0.20
Black Line Socket	£0.20
Yellow Line Socket	£0.20
White Line Socket	£0.20
Red Chassis Socket	£0.20
Black Chassis Socket	£0.20
Gold Plated Plug Red	£0.66
Gold Plated Plug Black	£0.66

XLR Series - metal

3 Pin Line Plug	£0.96
3 Pin Line Socket	£0.96
3 Pin Chassis Plug	£1.50
3 Pin Chassis Socket	£1.49
Neutrik Line Plug	£1.79
Neutrik Line Socket	£1.99
Neutrik Chassis Plug	£2.13
Neutrik Chassis Socket	£2.32

RF Connectors

BNC Plug 50Ω Solder	£0.99
BNC Plug 50Ω Crimp	£0.68
BNC Plug 75Ω Solder	£1.08
BNC Plug 75Ω Crimp	£0.68
BNC Chassis Socket	£0.81
F Plug - Twist	£0.24
F Plug - Crimp	£0.26
TNC Plug 50Ω Solder	£1.24
TNC Plug 50Ω Crimp	£0.85
TNC Plug 75Ω Solder	£1.40
TNC Plug 75Ω Crimp	£1.16
UHF Plug 5mm Cable	£0.63
UHF Plug 11mm Cable	£0.75
UHF Chassis Skt	£0.54
UHF Chassis Skt	£0.73

Terminals

Colours Red, Black, Green, Blue, White or Yellow	
2mm Solder Plugs	£0.18
2mm Chassis Sockets	£0.28
4mm Plugs - Solder	£0.33
4mm Plugs - Screw	£0.81
4mm Stockable Plugs	£0.40
4mm Shrouded Plugs	£0.74
4mm Chassis Sockets	£0.24
4mm Binding Posts	£0.46
33mm Crocodile Clips	£0.10

Power Connectors

DC Plug 0.7ID 2.35OD	£0.47
DC Plug 1.3ID 3.4OD	£0.32
DC Plug 1.7ID 4.0OD	£0.47
DC Plug 1.7ID 4.75OD	£0.47
DC Plug 2.1ID 5.0OD	£0.25
DC Plug 2.5ID 5.0OD	£0.24
DC Plug 3.1ID 6.3OD	£0.46
DC Line Socket 2.1mm	£0.57
DC Line Socket 2.5mm	£0.68
DC Chassis Skt 2.1mm	£0.44
DC Chassis Skt 2.5mm	£0.41

IEC Mains 6A 250Vac

3 Pin IEC Line Socket	£1.08
3 Pin IEC Line Plug	£1.78
3 Pin Chassis Socket	£0.55
3 Pin Chassis Plug	£0.72

8 Way Bulgin

8 Pin Line Plug P551	£3.58
8 Pin Chassis Skt P552	£1.08

Toggle Switches

Sub-Miniature	
3A 125V 1A 250V	
5mm Ø Mounting Hole	
SPST 5 x 10mm	£0.53
SPDT 5 x 10mm	£0.53
SPDT c/Off 5 x 10mm	£1.01
DPDT 9.2 x 10mm	£0.63

Miniature

6A 125V 3A 250V	
6.2mm Ø Mounting Hole	
SPST 8 x 13mm	£0.58
SPDT c/Off 8 x 13mm	£0.65
SPDT c/o Biased 2 way	£1.18
SPDT c/o Biased 1 way	£1.15
DPDT 12 x 13mm	£0.65
DPDT c/Off 12 x 13mm	£0.88
DPDT c/o Biased 2W	£1.20
DPDT c/o Biased 1W	£1.28

Standard

10A 250V Push on terminals	
12mm Ø Mounting Hole	
SPST 18 x 30mm	£1.05
SPDT 18 x 30mm	£1.18
SPDT c/Off 18 x 30mm	£1.78
DPDT 21 x 30mm	£1.78
DPDT c/Off 21 x 30mm	£1.78

Slide Switches

Miniature	
300mA 125V	
7 x 15mm Mounting Hole	
DPDT 7 x 23mm	£0.17

Standard

1A 125V	
5.5 x 12mm Mounting Hole	
DPDT 12 x 35mm	£0.27
DPDT c/o 12 x 35mm	£0.25

Rotary Switches

150mA 250V Make before Break 22mm Ø	
9.8mm Ø Mounting Hole	
1 Pole 12 Way	£0.84
2 Pole 6 Way	£0.84
3 Pole 4 Way	£0.84
4 Pole 3 Way	£0.84

Push Switches

Miniature Round	
250mA 125V 28 x 10mm	
7mm Ø Mounting Hole	
Non Latching Push to Make	
Black, Red, Yellow, Green, Blue or White	£0.23
Non Latching Push to Break	£0.24
Black PTB	£0.24

Standard Square

1A 250V	
39 x 15MM	
12mm Ø Mounting Hole	
Non Latching Push to Make	
Black, Red, Blue or White	£0.60
Latching - push On push Off	£0.65
Black, Red, Blue or White	£0.65

Rocker Switches

Miniature	
13 x 19mm Mounting Hole	
SPST 4A 250V	£0.57
SPST 6A Red Neon	£1.65
SPST 3A Red LED	£1.92
SPDT 6A 250V	£0.75
DPST 4A 250V	£0.81
DPST 4A Red Neon	£1.10
DPST 3A Amber Neon	£1.40
DPST 3A Green Neon	£1.32

Standard

(SPST, 22(DP) x 30mm Mounting Hole	
SPST 10A 250V	£0.60
SPST 16A 250V	£0.75
SPST 15A Red Neon	£0.90
SPDT 16A 250V	£0.75
DPST 10A 250V	£0.90
DPST 15A Red Neon	£1.18
DPST Amber Neon	£1.25
DPST Green Neon	£1.25
DPST 10A 250V	£0.90

Relays

PCB Mounting	
1A 24Vdc DPDT 5V	£1.38
1A 24Vdc DPDT 12V	£1.35
3A 110V SPDT 6V	£0.58
3A 110V SPDT 12V	£0.72
5A 110V SPDT 6V	£0.72
5A 110V SPDT 12V	£0.72
5A 110V DPDT 6V	£0.93
5A 110V DPDT 12V	£0.93
5A 240V DPDT 6V	£1.76
5A 240V DPDT 12V	£1.55
10A 240V SPDT 6V	£1.20
10A 240V SPDT 12V	£1.44
10A 240V SPDT 24V	£1.44

Computer Accessories

Adaptors	
9M Gender Changer	£1.73
9F Gender Changer	£1.73
25M Gender Changer	£2.20
25F Gender Changer	£2.43
9 Male - 25 Female	£1.73
9 Female - 25 Male	£1.73
9M - 6 Mini Din Mole	£2.48
9F - 6 Mini Din Female	£2.23
1M Din - 6 Mini Din	£1.73
5F Din - 6 Mini Din	£1.73

Testers / Patch Boxes

Mini Tester 7 LEDs	£4.72
Check Tester 18 LEDs	£6.32
Enhanced+ Switches	£15.18
25D Patch Box M-F	£2.64
Anti-Static Wrist Strap	£4.76
R5232 Surge Protector	£5.43
5A Surge Protector	£5.20
13A Surge Protector	£10.00
4 Gang Surge Block	£10.50

Leads & Cables

1.5m Printer Lead	£2.55
2m BD Printer Lead	£2.98
5m BD Printer Lead	£4.98
10m BD Printer Lead	£9.88
2m IEEE1284 Printer L	£4.38
5m IEEE1284 Printer L	£8.90
10m IEEE1284 Printer L	£16.13
Serial Printer 25M-9F	£4.88
Serial Printer 25M-25F	£4.38
9 Female - 9 Female	£4.38
25 Female - 25 Female	£6.48
9 Female - 25 Female	£4.38
9.25F to 9.25M	£4.88

Modem Leads

25Male to 9Female	£4.08
25Male to 25Female	£3.78

PC Link Leads

Interlink 25M to 25M	£3.88
25Male to 25Male	£3.60
36Male to 36Male	£2.60

EVERYDAY PRACTICAL ELECTRONICS

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

VOL. 31 No. 7 JUNE 2002

RIP OFF!

It's a pity when a few spoil it for everyone – we see it all too often in modern society with football hooligans, young vandals, hackers and virus writers and, of course, those that are prepared to rip someone else off for their own gain and glorification. Why is this relevant to *EPE*, well, of course, it should not be – but then we exist in today's world just like everyone else.

SERIOUS OFFENCE

Over the last twenty years or so we have had just one or two instances where items we have published have turned out to have been copied from other magazines, but this month two such items have come to light – both have been published in our *Ingenuity Unlimited* column and both have been copied from other magazines. This has happened even though both readers have signed a legal form to say: "I hereby confirm that the above-mentioned submission for publication in the *Ingenuity Unlimited* column is my/our own work and has not been published or currently submitted for publication elsewhere. I have read and understand the Notice appearing below." The Notice referred to reads: "This is a legally-binding agreement. Breach of copyright is now a serious offence. Material which is accepted for inclusion in *Ingenuity Unlimited* must not have been published or be currently submitted for publication elsewhere. In signing this form you agree to indemnify us from any damages and costs arising as a consequence of any breach of copyrights held by any other parties."

So these *EPE* readers are apparently quite happy to commit a serious offence and to take all of us for a ride.

The items in question were previously published in *Practical Wireless* and *Elektor* magazines and we apologise to them for breaching their copyright. Fortunately, the Editors of both magazines have been very understanding – possibly because they, too, are well aware of the problems caused by a few unscrupulous readers, so hopefully we will not need to go after these readers for damages, although that might make others think before they copy. In one case the reader has not been paid and in the other we are taking steps to recover the payment made.

REVIEW

We are now in the process of reviewing the future of our *IU* page, a pity but then, as I have said, so often the few spoil it for everyone. I hope those responsible are suitably shamed – you will find a special notice on our *IU* page this month.

I guess after 30-odd years on *PE/EE* and *EPE* I should not be surprised, but I am rather sad.



AVAILABILITY

Copies of *EPE* are available on subscription anywhere in the world (see below), from all UK newsagents (distributed by COMAG) and from the following electronic component retailers: Omni Electronics and Yebo Electronics (S. Africa). *EPE* can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased and downloaded for just \$9.99 (US – approx £7.70) per year available from www.epemag.com

SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £15, 12 months £28.50, two years £52; Overseas: 6 months £18 standard air service or £27 express airmail, 12 months £34.50 standard air service or £52 express airmail, 24 months £64 standard air service or £99 express airmail.

Online subscriptions, for downloading the magazine via the Internet, \$9.99 (US – approx £7.70) for one year available from www.epemag.com.

Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subs. Dept., Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Switch or Visa. (For past issues see the *Back Issues* page.)

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £5.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Amex, Diners Club, Switch and MasterCard accepted. Send, fax or phone your card number and card expiry date with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

Editorial Offices:

EVERYDAY PRACTICAL ELECTRONICS EDITORIAL
WIMBORNE PUBLISHING LTD., 408 WIMBORNE ROAD EAST,
FERNDOWN, DORSET BH22 9ND
Phone: (01202) 873872. Fax: (01202) 874562.

Email: enquiries@epemag.wimborne.co.uk

Web Site: <http://www.epemag.wimborne.co.uk>

EPE Online www.epemag.com

EPE Online Shop: www.epemag.wimborne.co.uk/shopdoor.htm

See notes on **Readers' Technical Enquiries** below – we regret lengthy technical enquiries cannot be answered over the telephone.

Advertisement Offices:

EVERYDAY PRACTICAL ELECTRONICS ADVERTISEMENTS
MILL LODGE, MILL LANE
THORPE-LE-SOKEN, ESSEX CO16 0ED
Phone/Fax: (01255) 861161

Editor: MIKE KENWARD

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Administration: FAY KENWARD

Editorial/Admin: (01202) 873872

Advertisement Manager:

PETER J. MEW, Frinton (01255) 861161

Advertisement Copy Controller:

PETER SHERIDAN, (01202) 873872

On-Line Editor: ALAN WINSTANLEY

EPE Online (Internet version) Editors:

CLIVE (MAX) MAXFIELD and ALVIN BROWN

READERS' TECHNICAL ENQUIRIES

E-mail: techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply must be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons. All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers (see *Shoptalk*). We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are bona fide, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.



Constructional Project

INFRA-RED AUTOSWITCH

MAX HORSEY



Simply waving your hand near this versatile IR switch will cause lights to switch on for a timed period. If you stay in the area the unit will remain triggered.

THE Infra-Red Autoswitch described here will, no doubt, find many applications, but it was designed initially to switch on the concealed lighting around a set of kitchen units. Simply waving your hand near the unit will cause the lights to switch on for a timed period. Also, if you stay in the area the unit will remain triggered.

The sensor employed here is similar to the auto-switches used in up-market public wash handbasins and handdriers, where the water or air is switched on when your hand is in place.

It is important not to make the unit too sensitive otherwise false triggering will occur. The system is triggered when your hand is about 30cm from the unit. The prototype was concealed underneath a kitchen cupboard, the distance between the unit and the worksurface being too large to cause false triggering.

The project was designed for maximum ease of assembly and fitting, with all components including the transformer being housed on a printed circuit board (p.c.b.). The only connections required are the mains supply input, and lighting output.

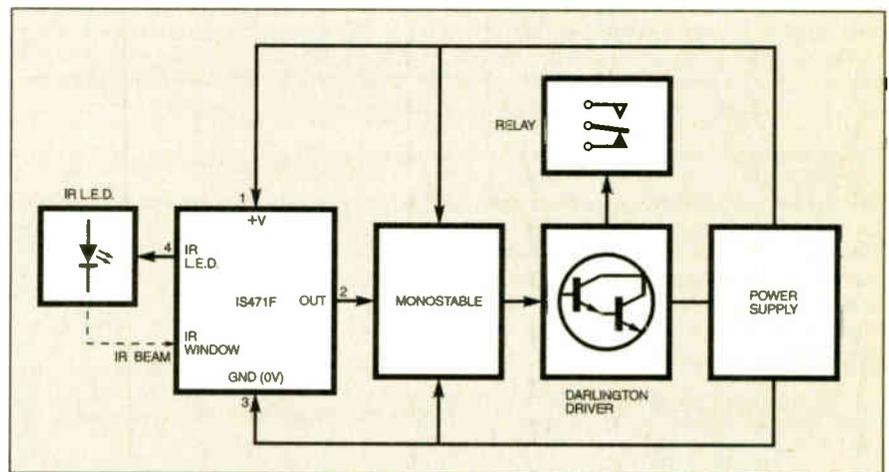


Fig. 1. Block schematic diagram for the Infra-Red Autoswitch.

INTELLIGENT SENSOR

The infra-red system is based on the inexpensive but intelligent IS471F infra-red sensor i.c. This i.c. provides a signal, which may be used to directly drive one or two infra-red l.e.d.s.

A coded signal is applied to the IR l.e.d.s, and having transmitted the beam,


the i.c. waits for the signal to be reflected. The reflected signal is detected by a window built into the i.c., and when the signal is received the output switches from positive to zero volts.

A basic block schematic diagram is shown in Fig.1. The IS471F is a 4-pin device; pin 1 and pin 3 connect to the power supply, which should be between 4.5V and 16V. Pin 4 acts as a sink to provide the coded signal for the IR l.e.d.s. and pin 2 is the output.

When a reflected signal is detected, the output at pin 2 switches from positive to 0V. This is used to trigger a monostable (timer). The monostable switches on a transistor and relay, which in turn switches on the lights or any other device.

CIRCUIT DETAILS

The full circuit diagram for the Infra-Red Autoswitch is shown in Fig.2. The IS471F infra-red sensor (IC1) is connected to a pair of infra-red l.e.d.s D1 and D2 as shown. Note that no series resistor is required since the current is regulated by the i.c. In tests, two l.e.d.s provided a longer detection range than one, but three made no difference. If a shorter range is required a single l.e.d. could be employed, it is also possible to reduce the range by adding a resistor in series with the l.e.d.s.

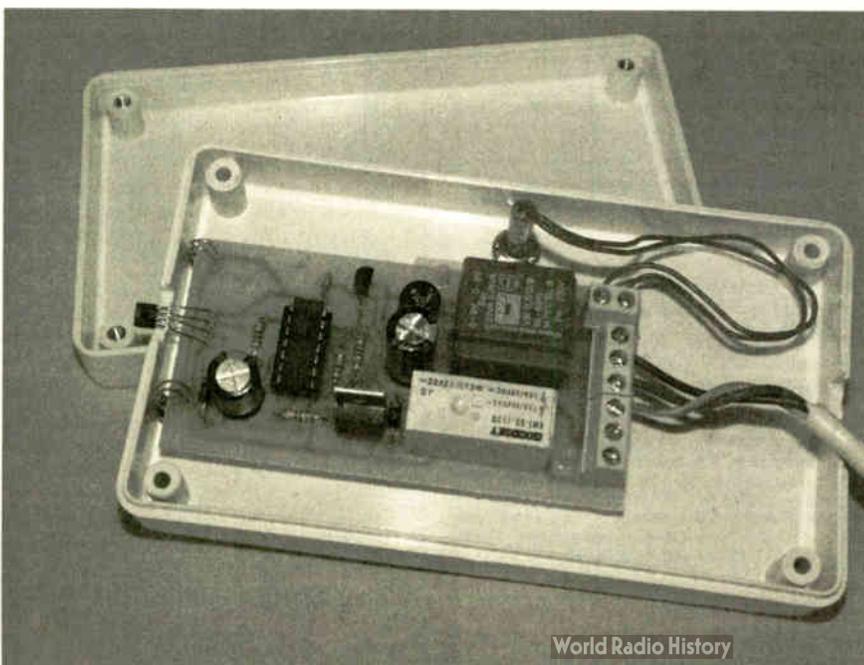

The monostable is based around the well-tried-and-tested CMOS 4001B chip, which houses four NOR gates. Gates IC2b and IC2c are configured as a monostable and a positive signal is required at pin 5 of gate IC2b to trigger the time period.

As stated, IC1 provides an output which switches to 0V when an object is detected. So it is necessary to invert this signal, and this is achieved by means of gate IC2a, whose inputs (pin 1 and pin 2) are connected together thus making it behave as a NOT gate or inverter.

When an object is detected, pin 2 of IC1 switches to 0V, and this causes output pin 3 of IC2a to switch to positive (high). This signal is fed to input pin 5 of IC2b, so triggering the monostable formed by IC2b and IC2c.

When triggered, pin 4 of IC2b switches to 0V, and this sudden change of voltage is transferred to the other side of capacitor C1, so reducing the voltage at pin 8 and pin 9 to 0V. Hence output pin 10 of IC2c switches to positive, and this is fed back to input pin 6 of IC2b, so latching the monostable into its new state.

output pin 2 of IC1 switches to 0V (object detected), capacitor C1 is discharged.

With this addition, timing is from the last time that an object was detected. So, if you stand near the sensor, the lights will remain on. Diode D3 prevents current flowing towards capacitor C1 when IC1 pin 2 is positive, and resistor R1 is needed to reduce the surge of current that might damage IC1.

When the circuit is being tested, a time period of more than five minutes can be tedious! So resistor R3 was included together with solder pads P1 and P2. Terminal pins or a wire link may be soldered to these pads so that at the testing stage the time period can be reduced to just a few seconds. When the system is working, the link can be cut, so reverting to the full time period.

If you wish to have a variable time period, then resistor R2 may be omitted, and a variable resistor (potentiometer) can be connected across pads P1 and P2. A value of 1 megohm will provide a sufficient range of times.

COMPONENTS

Resistors

R1	680Ω
R2	680k
R3	10k
R4	4k7

All 0.25W 5% carbon film

See
**SHOP
TALK**
page

Capacitors

C1, C3	1000μ radial elect. 25V (2 off)
C2	100n disc ceramic

Semiconductors

D1, D2	infra-red light-emitting diode (2 off)
D3, D4	1N4001 1A 50V rect. diode (2 off)
TR1	TIP122 npn Darlington transistor
IC1	IS471F infra-red sensor
IC2	4001 quad 2-input NOR gate
IC3	78L12 +12V voltage regulator
REC1	W005 1.5A 50V bridge rectifier

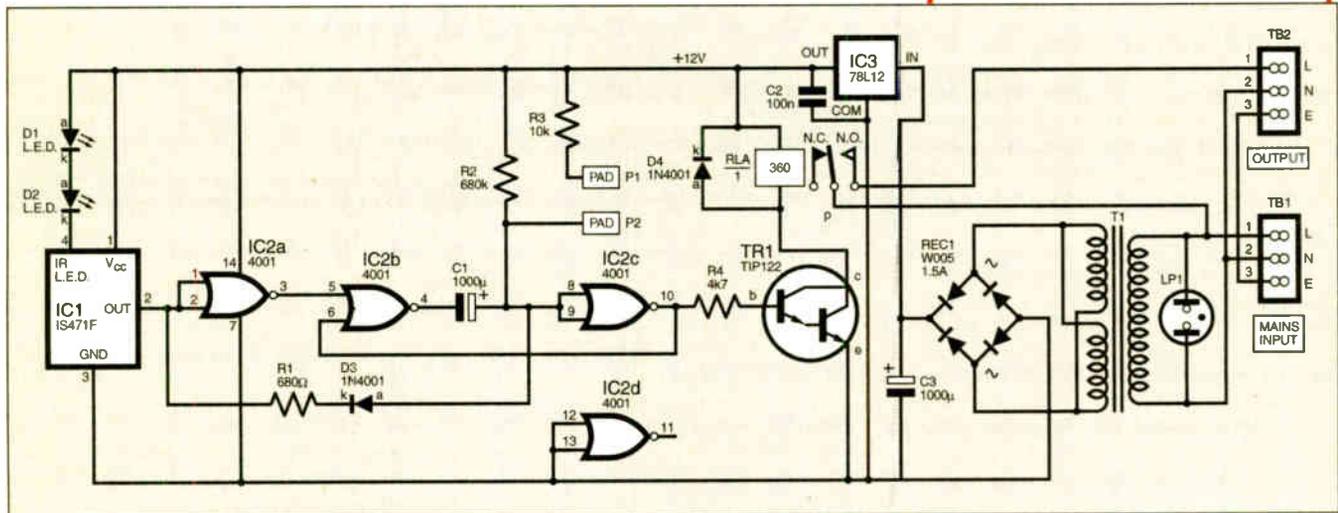


Fig.2. Complete circuit diagram, including mains power supply, for the Infra-Red Autoswitch.

The monostable is not stable in its new state, since there is a voltage difference across resistor R2. Current therefore flows through R2, slowly charging up capacitor C1. So the voltage rises at IC2c pin 8 and pin 9 and as it crosses the half-way point, gate IC2c changes state and completes the time period.

Now the change of logic level is fed back to IC2b pin 6 which causes IC2b output pin 4 to switch back to positive. This change of voltage is transferred across capacitor C1, so reinforcing the change already taking place. All this happens very quickly so producing a clean change of state to 0V at pin 10 of IC2c.

Once the monostable is triggered, further triggering has no effect, and the time period is fixed from the first moment that triggering occurred. This can be irritating in this application, since the lights will switch off even if your hand is still near the sensor.

Although they will be re-triggered immediately, this is not ideal, especially since kitchen units are generally fitted with fluorescent lights which flicker as they switch on. Hence resistor R1 and diode D3 were added so that every time

OUTPUT DRIVER

Little current is available from the output of a CMOS gate, and so transistor TR1 is employed to amplify the current available. In fact, Darlington transistors cost little more than normal ones, and so a Darlington transistor was used in the prototype. The massive gain and power rating of a Darlington allows the use of almost any type of low voltage relay, and allows the value of resistor R4 to be sufficiently high not to adversely affect the logic level at the output.

A relay with a 12V coil voltage should be employed for the output, and its contacts must be rated at 230V a.c., 5A or more. Note that many relays on sale have contacts rated at 120V. These are likely to burn out or fuse together in a short time.

It is much easier and safer to house the relay directly on the p.c.b., and so check that the type obtained will fit. There seem to be two slightly different pin spacings in common use, and the p.c.b. has been designed to accommodate either. Diode D4 removes any back e.m.f. produced by the relay.

Miscellaneous

T1	230V a.c. mains transformer, p.c.b. mounting, with twin 9V 0.028A secondaries; total rating 0.5VA
RLA	mains p.c.b. mounting, low-profile relay with 12V d.c. 360 ohm coil and 12A 250V a.c. single-pole change-over contacts. The relay height should be 19mm or less to fit inside the specified case
LP1	mains neon indicator, with integral resistor

Printed circuit board available from the EPE PCB Service, code 358; plastic case, size 143mm x 82mm x 30mm; 14-pin d.i.l. socket; 3-way, p.c.b. mounting screw terminal block (2 off); multistrand connecting wire; mains cable; nylon self-adhesive p.c.b. supports (3 off); solder pins; solder etc.

Approx. Cost
Guidance Only

£19
excluding case

POWER SUPPLY

A regulated mains power supply is included in the circuit diagram of Fig.1 and is made up of the components to the right of relay RLA1 contacts. The supply was included to simplify installation of the system. The main components are the mains transformer T1, bridge rectifier REC1, smoothing capacitor C3 and the +12V voltage regulator IC3.

The Autoswitch circuit consumes very little power and so a fully encapsulated p.c.b. mounting mains transformer was employed. The specified transformer supplies a limited current and its secondary can be short-circuited without the transformer being damaged. Note that there are two separate secondary windings, and these are connected in *parallel* to double the current available. Select the transformer with care, so that its pins fit the p.c.b..

When the a.c. supply from transformer T1 secondaries is full-wave rectified by REC1, and smoothed by capacitor C3, the resulting d.c. voltage is increased by a factor of about 1.4 times, though this is subject to a voltage drop caused by the "bridge" diodes. The current available is reduced by the same percentage.

So a transformer rated at 9V 28mA per secondary winding was employed, the two coils being connected in parallel to achieve 9V 56mA. After rectification and smoothing the voltage available is around 12V and the current around 40mA.

REGULATION

The original prototype design used this unregulated supply to drive the circuit, and all was well. However, the *actual* voltage produced by the transformer depends upon the current flowing, and when the circuit is in standby mode, the current is very small and so the voltage rises well above its nominal value. Small transformers of the type employed here are particularly bad in this respect.

The i.c.s in the circuit can tolerate up to 16V, but there was a danger that the voltage may rise beyond this when in standby mode. So a +12V voltage regulator, IC3, was added. This limits the supply to 12V regardless of whether the circuit is in standby mode, or activated.

The current required by the relay coil when activated will make the regulated supply dip a little below 12V, but this should not be a problem since a 12V relay should be capable of operating on 9V or less. Capacitor C2 is needed to remove any spikes from the supply line.

No fuse was included though it is assumed that the circuit is driven from a fused supply. If this is not the case, then a fuse *must* be added in series with the Live connection on the mains input side; terminal block TB1. Neon indicator (with integral resistor) LP1 is included on the mains input side to provide a warning that the system is live.

TIME OUT

The period for which the output of the monostable (IC2b/IC2c) is positive is set by resistor R2 and capacitor C1. The formula is:

$$\text{Time (secs)} = R \text{ (ohms)} \times C \text{ (farads)} \times 0.7$$

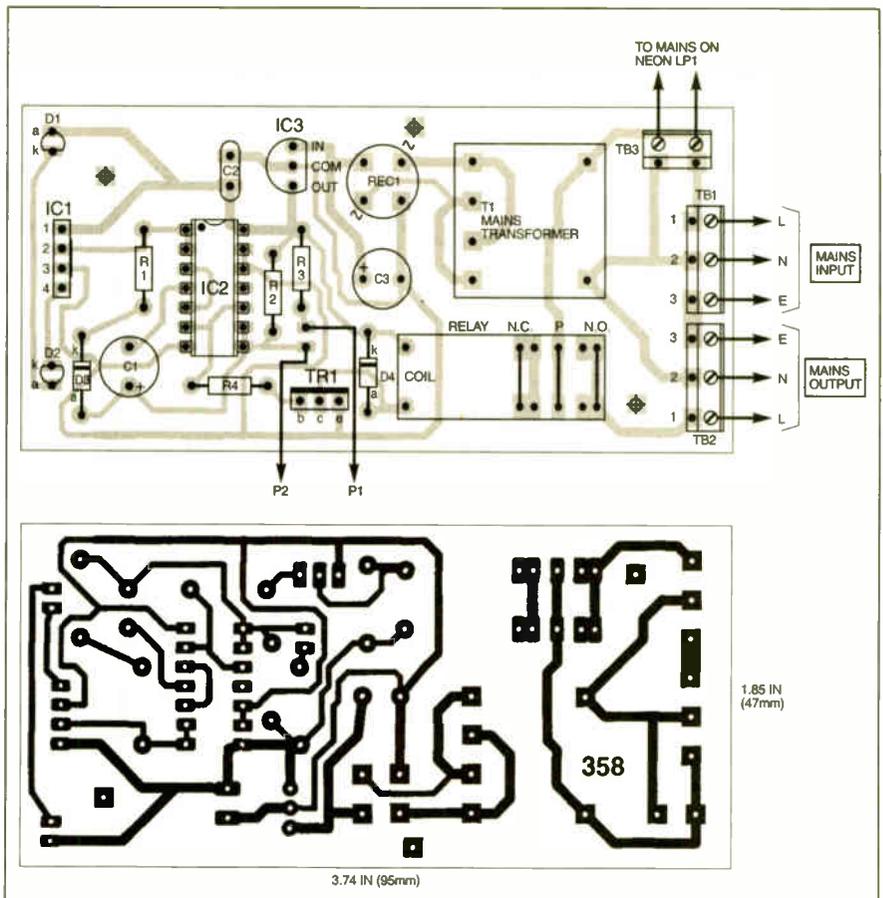


Fig.3. Printed circuit board topside component layout, lead-off wires and full-size underside copper foil master.

The numbers can be simplified by taking R in megohms and C in microfarads μF .

Hence using the values in the circuit diagram (Fig.2):

$$\text{Time} = 0.68 \times 1000 \times 0.7 = 476 \text{ secs.} = \text{almost 8 minutes.}$$

Remember that this is the time for which the switch remains on, after the last time it was triggered. If the pads P1 and P2 on the p.c.b. are joined with a wire link, then resistor R3 reduces the time period considerably. Resistor R3 is so much lower than R2 that R2 can be ignored in the calculation, so the time is given by:

$$\text{Time} = 0.01 \times 1000 \times 0.7 = 7 \text{ secs.}$$

Note that all these times are approximate as they depend upon the accuracy of the components used, particularly the capacitor. Some electrolytic capacitors may have a tolerance (error) of as much as 50 per cent, though most modern ones can do better!

As stated earlier, if precise times are required, a potentiometer (wired as a variable resistor) could be employed so that the exact time may be set. The "variable resistor" should be connected to the p.c.b. pads P1 and P2 so that it is in series with resistor R3; this ensures that if the variable resistor is reduced to zero, there is not a direct link to the positive supply.

The value of resistor R3 could be reduced to 1k if shorter times are required. The maximum resistance permitted is 1M, beyond that, timings may be unstable.

If very long timings are required the value of capacitor C1 could be increased, though be cautious, as large value electrolytics can be very "leaky" and you may find that C1 never charges sufficiently to complete the timing cycle. Some experimentation may be necessary.

CONSTRUCTION


Apart from the mains neon indicator LP1, all the components for the Infra-Red Autoswitch are mounted on a small single-sided printed circuit board. The topside component layout and full-size copper foil master pattern are shown in Fig.3. This board is available from the *EPE PCB Service*, code 358.

Begin construction by soldering in position the 14-pin i.c. socket followed by the resistors and diodes D3 and D4, checking that the diodes are fitted the correct way round.

Now fit the larger components including bridge rectifier REC1 and the capacitors. Again, all must be fitted the correct way round, except C2 which may be either way. Fit transistor TR1 with its metal tab away from the edge of the board, and regulator IC3 with the flat side the way shown.

Fit solder terminal pins into copper pads P1 and P2, or use a wire link (which will later be cut) to join these two pads together. This will help with testing as explained later.

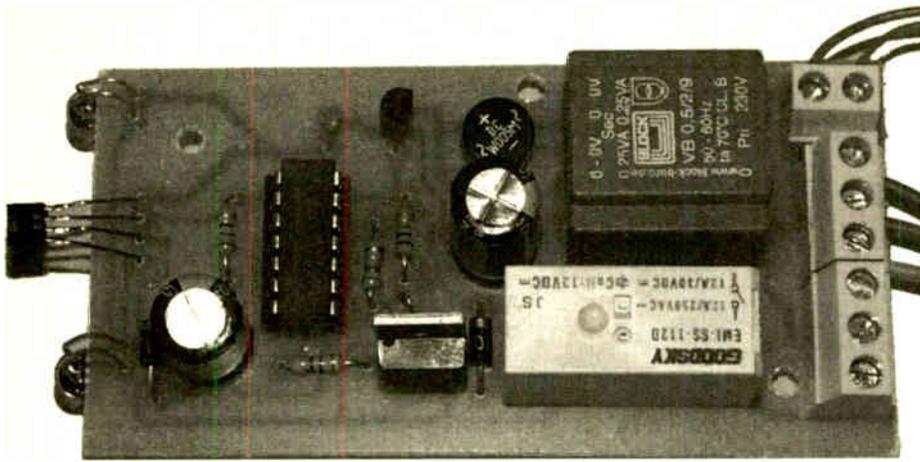The infra-red l.e.d.s D1 and D2 must be fitted the correct way round (see Fig.3), and must stand proud of the board so that they may be bent over the edge later. Leave their wires as long as possible.



Component layout on the completed printed circuit board. The infra-red sensor and diode emitters are mounted on the lefthand edge. Note the two infra-red light-emitting diodes are "looped" over the edge of the p.c.b.

WARNING: The IR I.e.d.s used in the prototype were supplied with their longer leads indicating cathode (k). This is very unusual, normally long indicates anode (a). So take care with the orientation of the I.e.d.s.

Round I.e.d.s have a flat mark on the base of the plastic, and this also indicates cathode. In the prototype the flat mark was – correctly – on the cathode side. If you only require a single IR I.e.d. (for a shorter detection range) then fit a wire link in place of the I.e.d. not required.

The infra-red sensor IC1 must also be fitted correctly. The "bump" on the surface of the I.C. indicates the rear (non-sensing) side (see Fig.4). Hence, it should be fitted with the smooth flat side towards the edge of the p.c.b.

Touch an earthed surface (such as the case of a metal appliance which is plugged into the mains) in order to remove any static electricity in your body before handling IC1. Fit the sensor, allowing it to stand proud of the p.c.b. so that it can be folded over the edge later.

Now fit the relay to the p.c.b., noting that double holes are provided for some of the relay tags, since – annoyingly – relays do not always conform to a standard layout. Similarly the transformer should be soldered into place. Neither the specified relay nor transformer will fit the wrong way round.

If you employ a relay or transformer which is not designed for p.c.b. mounting, then you must use insulated wires to make the appropriate connections. However,

using the components specified will be easier and safer.

The mains and lighting cables are connected via 3-way terminal blocks (TB1 and TB2). These are soldered to the p.c.b., and provide a convenient way of connecting leads at a later stage. Likewise a 2-way block (TB3) can be used to connect the mains neon indicator LP1. Alternatively, the mains neon may be soldered directly to the appropriate p.c.b. pads, but before fitting the neon, check which way it passes through the case; if fitted from the outside, you will need to attach it to the case before soldering or screwing in its leads.

Finally, fit IC2 into its socket, checking that its notch (or dot) is at the correct end, and taking the same anti-static precautions as described earlier.

TESTING

It is strongly recommended that the circuit board should first be tested on a separate 9V or 12V battery supply before connecting it to the mains, otherwise, house the circuit in its case first, and return to testing later.

Connect a separate battery supply by clipping a pair of leads to the appropriate tracks on the circuit board. Check that the correct polarity is observed. The track at the top, leading to IR diode D1 is the positive supply, and the track at the very bottom of the p.c.b. is the negative (0V) supply line. If terminal pins have been fitted to pads P1 and P2, then join these together for testing.

Switch on. The relay should click on. Assuming that you have not connected a mains supply, you can verify that the relay is working by connecting a multimeter set to "resistance" to the terminals marked "L" on TB1 and "L" on TB2. When the relay contacts close, the meter should give a reading of about zero, or bleep.

When power is first applied to the board the relay should switch on. Assuming that pads P1 and P2 are joined together, the relay should remain on for about 7 seconds. If the relay remains on for longer, it may be because the IR receiver IC1 is being triggered by the IR I.e.d.s. Try shielding the sensor with thick paper, card or Blu-Tack.

If all is well, disconnect the multimeter and temporary low voltage supply. Do not connect the mains supply until the p.c.b. is safely housed and secured into its case.

FAULT FINDING

Fault finding should *only* be carried out if the circuit is powered from a separate 9V or 12V battery supply as described earlier, i.e. do not connect the circuit to a mains supply. A voltmeter is the only test instrument required; connect the negative lead of the voltmeter to the 0V track (the very bottom) on the p.c.b.

Begin at the sensor (IC1) end of the circuit, and take readings with the positive lead of the voltmeter, starting with the power pins of IC1, pin 1 (positive) and 3 (0V). Now test pin 2 (output) of IC1. This should be positive when a signal is *not* received, switching to 0V when the IR beam is reflected from an object. A constant 0V signal may indicate that the beam is reaching the sensor directly, so try covering D1 and D2 with thick paper or Blu-Tack (front, sides and back) to find out whether this is the case.

Remember that when the circuit is housed in its case, direct transmission from infra-red I.e.d.s D1 and D2 to sensor IC1 should not be a problem. A constant positive signal may indicate that the I.e.d.s are not working at all. Check their connections carefully, and remember that the longer lead indicates cathode (k) on certain infrared I.e.d.s. If you have employed only one I.e.d., you should have fitted a wire link in place of the other one.

If the output pin (2) of IC1 is working correctly, its logic levels should be copied to pin 1 and pin 2 of IC2. Pin 3 of IC1 should do the opposite.

The best test point on the monostable IC2b/IC2c is pin 10. This should normally be around 0V switching to positive during the timed period. If its input side is working, but the output fails, check carefully the values of the components, and whether diode D3 is fitted the correct way round.

If you have joined pads P1 and P2 then the timed period should be about 7 seconds. If the monostable never completes its timed period, try using a smaller capacitor for C1 since some electrolytic capacitors leak current. The value suggested should not suffer in this way, unless very old or connected the wrong way round.

If the voltage at IC2c pin 10 is near positive, then TR1 and the relay should switch on. Failure at this point suggests that the transistor may be the wrong way round, or



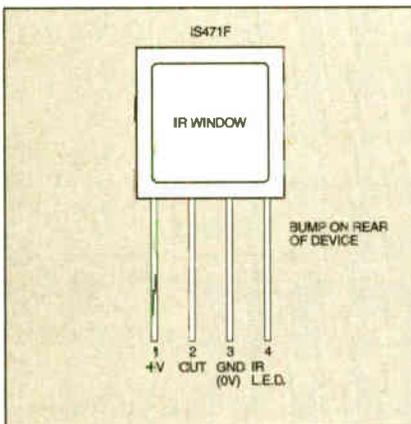


Fig.4. Pinout details for the IS471F infra-red sensor.

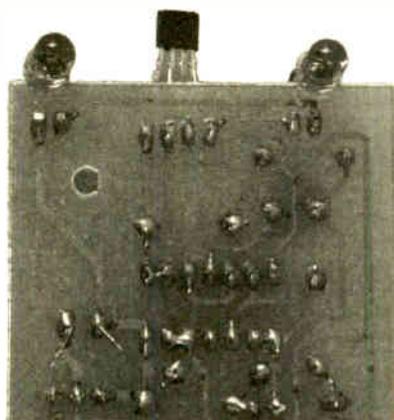

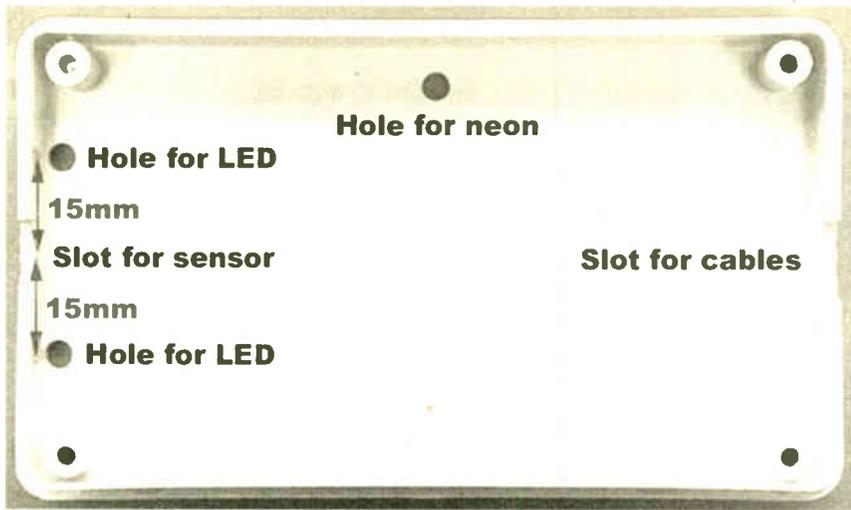IR sensor (centre) and diodes mounted at one end of the p.c.b.



Suggested drilling and component positioning details for the case lid.

the wrong type etc. You can check the operation of the relay by shorting together the two right hand pins (c and e) of TR1. This should trigger the relay.

CASING UP

A neat white plastic case, measuring 140mm x 80mm x 30mm, was used in the prototype as shown in the photographs. Decide which of the two halves will be used to house the circuit. If required for a kitchen unit, it is best to fit the p.c.b. in the lid i.e. the side where you can see the lid retaining screws. The base of the case can be fastened to the underside of a kitchen cupboard by means of one or two small wood screws. Begin case preparation by drilling holes for these screws in the base of the case.

Turning your attention to the lid, cut a slot in the end for the sensor IC1. The use of a slot at the side of the case ensures that the IR beam cannot be received from the rear of the l.e.d.s, or by reflections inside the case. If you change the design, do ensure that this point is observed, otherwise use large amounts of Blu-Tack to protect the sensor from stray reflections!

Now drill two holes for the IR l.e.d.s near the edge of the case as shown in the above photograph, plus a hole for the

mains neon LP1. The latter can fit anywhere providing it does not foul the p.c.b. Check the position of the p.c.b. before drilling. You will also need a slot for the mains input and light output cables.

The printed circuit board may be housed by means of nylon self-adhesive p.c.b. supports. Before removing the protective

cover on these supports, check that the sensor and l.e.d.s will fit into place. The l.e.d.s D1 and D2 should be neatly folded over the edge of the p.c.b. as shown in the photograph, so that they fit into the holes.


You could have soldered the l.e.d.s to the copper side of the board, but exact alignment is much more difficult and it is hard to judge how long the leads should be to make a good fit. The method suggested is much easier.

Having fixed the p.c.b., the mains wiring can be completed, but do not plug in, until the base is fixed to the lid.

FINAL TESTING

When the two halves of the case are screwed together, connect the unit to a fused mains supply. On switch-on, the relay should switch on with a click. If pads P1 and P2 are still joined, the timed period will be about 7 seconds. Test the system to ensure that the "trigger" range is satisfactory.

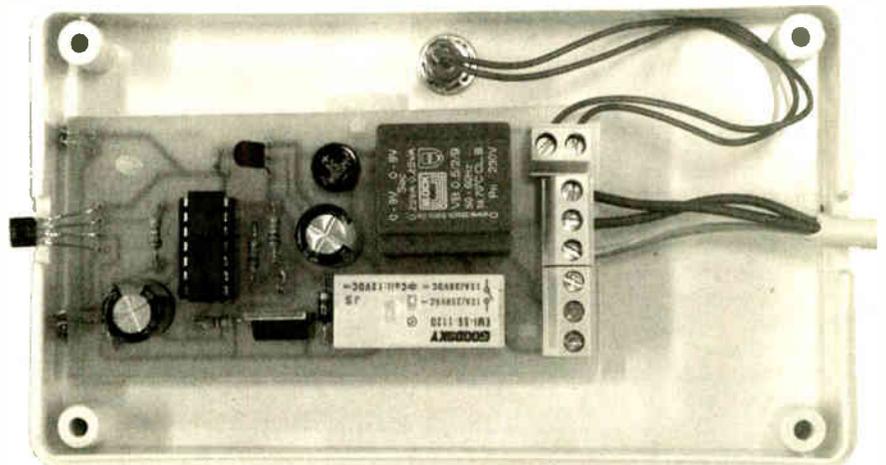Now disconnect from the mains supply, and remove or cut the link between pads P1 and P2. The timed period will now be about 8 minutes. When the case is safely back together, re-connect the mains supply.



The printed circuit board should be positioned in the lid of the case using nylon self-adhesive pillars. Note the cutout slot for the IR sensor.

EVERYDAY PRACTICAL ELECTRONICS

NEWSAGENTS ORDER FORM

Please reserve/deliver a copy of *Everyday Practical Electronics* for me each month

Signed.....

Name and Address.....

.....

.....

Post Code

Everyday Practical Electronics is published on the second Thursday of each month and distributed S.O.R. by COMAG. Make sure of your copy of *EPE* each month – cut out or photostat this form, fill it in and hand it to your newsagent.

SPECIAL
READER -
SEE WEBSITE
FOR DETAILS

PROTEUS VSM


Virtual System Modelling

Build It In Cyberspace

www.labcenter.co.uk

Develop and test complete micro-controller designs without building a physical prototype. PROTEUS VSM simulates the CPU and any additional electronics used in your designs. And it does so in real time. *

- CPU models for PIC and 8051 and series micro-controllers available now. 68HC11 coming soon. More CPU models under development. See website for latest info.
- Interactive device models include LCD displays, RS232 terminal, universal keypad plus a range of switches, buttons, pots, LEDs, 7 segment displays and much more.
- Extensive debugging facilities including register and memory contents, breakpoints and single step modes.
- Source level debugging supported for selected development tools.
- Integrated 'make' utility - compile and simulate with one keystroke.
- Over 4000 standard SPICE models included. Fully compatible with manufacturers' SPICE models.
- DLL interfaces provided for application specific models.
- Based on SPICE3F5 mixed mode circuit simulator.
- CPU and interactive device models are sold separately - build up your VSM system in affordable stages.
- ARES Lite PCB Layout also available.

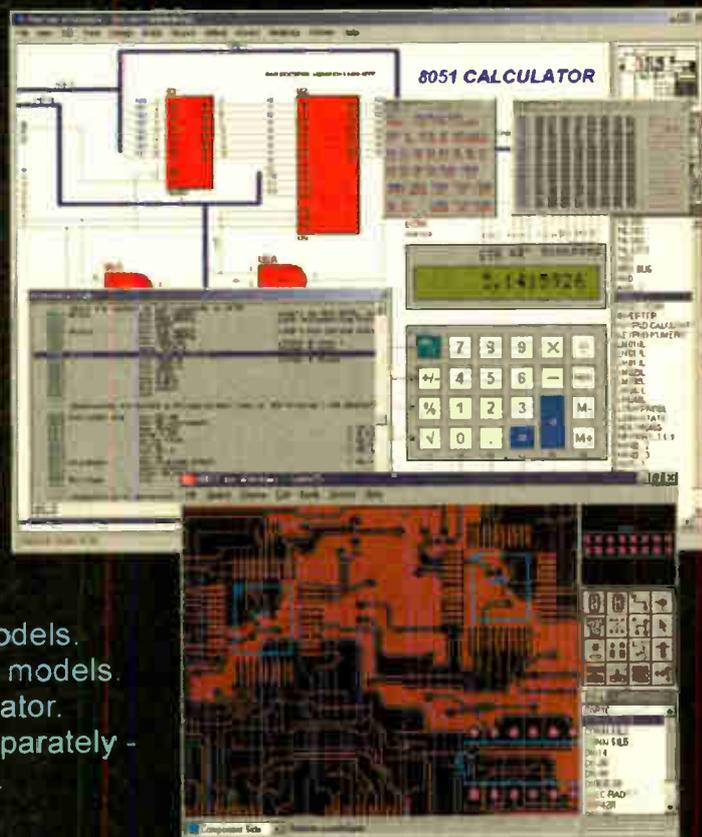

labcenter

Electronics

*E.g. PROTEUS VSM can simulate an 8051 clocked at 12MHz on a 300MHz Pentium II

Write, phone or fax for your free demo CD - or email info@labcenter.co.uk.
Tel: 01756 753440. Fax: 01756 752857. 53-55 Main St, Grassington, BD23 5AA.

TV HISTORY REVISITED

Big business ethics do not always favour the creative inventor, as Barry Fox reports.

CONTRARY to popular belief, the world very seldom beats a path to an inventor's door, waving a cheque book; pioneers die broke and forgotten, and big business lawyers make mincemeat of lone inventors.

The tragic story of how Edwin Howard Armstrong invented FM radio in 1933, and committed suicide in 1954 out of despair, is well documented in *Man of High Fidelity* by Lawrence Lessing, Bantam Books (although, be warned, the book is a eulogy and lacks any index). Armstrong struggled first to win frequencies for FM broadcasting from the Federal Communications Commission and then to win royalties on radio equipment from the giant RCA and its ruthless Chairman, David Sarnoff.

Boy Genius

The equally bitter struggle between David Sarnoff and US TV pioneer Philo Farnsworth, has so far been a lot less well documented. But a new book by Daniel Stashower just published in the USA (*The Boy Genius and the Mogul, the Untold Story of Television*, Broadway Books, ISBN 0-7679-0759-0), fills the gap. And of course the Internet now makes it much easier to buy books internationally.

Stashower's book also provides a useful reminder that no-one really invented television; the technology emerged as two competing streams of development, mechanical and all-electronic, converged. Although the mechanical systems were all doomed to failure, they put pictures on screen much earlier than the electronic systems could do, and so whetted the public's appetite for "seeing by radio".

Paul Nipkow began it all with his 1884 idea for a spinning disc to scan an image. This was taken up by Charles Francis Jenkins in the USA in 1922, John Logie Baird in the UK in 1926 and Bell Labs in 1927. In 1928 Ernst Alexanderson at RCA switched from disc to mirrored drum.

It was 1908 when A. A. Campbell Swinton proposed a cathode ray tube and inspired Edouard Belin who was experimenting in Paris by 1921. Karl Ferdinand Braun, Boris Rosing and Vladimir Zworykin took up the idea of displaying pictures on a CRT. Philo Farnsworth was a fifteen year old Idaho farm boy when, in 1922, he started to formulate plans for a television set with no moving parts while ploughing fields with a raster of furrows. Farnsworth filed

his key patents (USP 1,773,980 and 981) in 1927.

Jenkins died in poverty in 1934 and although Baird lived until 1946, his mechanical system had long since been ousted in the UK by the all-electronic technology developed by EMI and Marconi, with a team including Alan Blumlein, the inventor of stereo sound recording.

Baird had called on Farnsworth in 1934 to help him convert his mechanical system to an electronic one. The deal collapsed, because Baird's operation was shut down by a disastrous fire at his Crystal Palace research labs in South London in 1936.

At the time Farnsworth was also working with German broadcasters on televising the Berlin Olympics. And by then Philo Farnsworth and his small, under-funded company, were in head-on confrontation with David Sarnoff and RCA, who were backing Vladimir Zworykin's approach. Zworykin had told RCA in 1929 it would cost \$10,000 and take two years to make electronic television work. Sarnoff was later to complain it had taken ten years and cost \$50 million.

Breaking Patents

RCA's policy under Sarnoff was that RCA collected royalties, and did not pay them. So although Farnsworth's Image Dissector camera worked better than Zworykin's Iconoscope (while Zworykin's Kinescope display worked better than Farnsworth's tube) Sarnoff was not willing to cut a deal. Instead, after Zworykin visited Edouard Belin in 1928 and Farnsworth in 1930, Sarnoff set out to break Farnsworth's patents.

RCA had vast financial resources from the pool of several thousand radio patents the company had accumulated through the 1920s, so could afford prolonged legal action, with the best lawyers. When Farnsworth won a round they just appealed. In 1935 RCA had hardened its commitment to television, instead of FM radio. RCA's PR machine swung into action to tell the public what RCA was achieving. At the World's Fair in New York in 1939, RCA made the headlines, with Farnsworth and his system nowhere to be seen.

Farnsworth's research had been starved of funds, despite a deal with Bell and AT&T in 1937; the inventor was on the breadline and in mental and physical decline. Sarnoff was earning \$100,000 a year. In 1939, after ten years of legal battle, RCA finally took a licence from

Farnsworth, the first ever for the company. But war was coming and by the time it was over, Farnsworth's patents were dead.

Ten years later, ITT took over what was left of the Farnsworth company and the inventor lived on until 1971 dreaming up ideas for nuclear power generation. Stashower's story makes a good read and a timely antidote to some of today's adverts for invention brokerage agencies which can lead the innocent into expecting too much, too easily from filing a patent.

But although the story hangs on patents, they are not identified by number; this is a surprising omission. It is also clear that the author is much better at telling a story than analysing and explaining competing technologies. He would have benefited from some technical assistance. And I would add a final irony: some of the original mechanical technology has recently found a new life; the digital micro-mirror projectors which use a Texas Instrument chip often rely on a spinning filter wheel to add colour to the picture.

WELLBERRY CASES



MOST of you are no doubt familiar with the "WB" range of project cases that has been around for many years. Wellberry Cases have reminded us that in fact it was in 1971 that these aluminium/steel cases with simulated leatherette texture finish were first introduced. In 1974 the same company also introduced the familiar EB range that so many readers have used for instrumentation-type housings.


The good news is that not only are the cases still available after all these years, but that they are now available direct from the manufacturer, Wellberry, at a good price advantage! Not only that, Wellberry will also punch panels to your design if you have a requirement for at least 50 of them (kit suppliers take note!), and at a low price.

For more information contact Wellberry Cases, Dept. EPE, Ion Farm, Lower Gravenhurst, Bedfordshire MK45 4HH. Tel: 01462 814788.

Fax: 01525 860081.

Web: www.wellberry.co.uk.

PICtutor V2

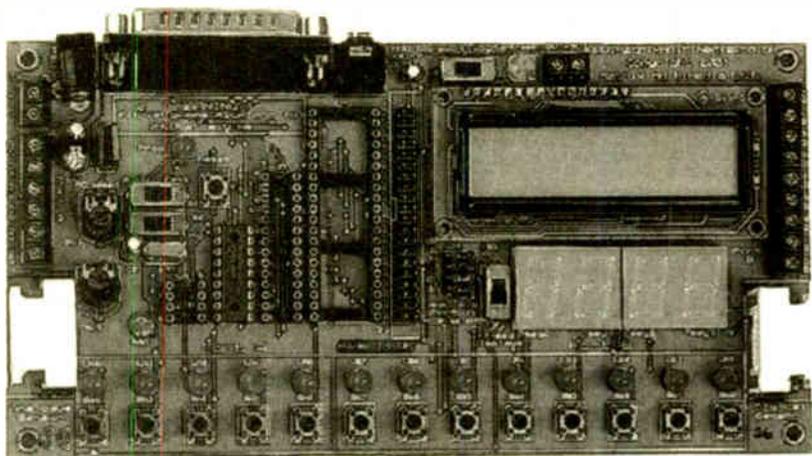

BACK in '98 we published John Becker's well-acclaimed *PIC Tutorial* series of articles explaining to newcomers how to understand and use PIC microcontrollers. The success of that series led to the production of a CD-ROM based version in conjunction with Matrix Multimedia Ltd, and known as *PICtutor*, complete with its own simulator and development board.

A new version of *PICtutor* has been introduced with many beneficially enhanced features. First, whereas the original was based on the TASM assembly dialect, John has revised V2 so that it is totally based upon the industry-standard MPASM dialect, giving a much more universal appeal to the tutorials, demonstrations and development exercises.

Secondly, the development board through which PICs can be programmed during the tutorials, and in the user's own later applications, has been totally redesigned with many new interface features, and allowing four different PIC sizes to be programmed. Of great significance, too, is the improvement that does away with the programming switches of V1. All program downloading is now fully under control of the PC computer, via a specially developed suite of software that is included on the CD.

We are extremely pleased that Microchip, the manufacturers of PICs, has given its support to the new version. To suit their marketing recommendations, it has been renamed as *Assembly for PICmicro Microcontrollers V2.0*. For further details see the *CD-ROMs for Electronics* pages in this issue.

Weather Instruments

IT is well known that in the UK we are pretty much obsessed with the weather. Hardly surprising, perhaps, as despite the worthy efforts of our met forecasters, it is so irrationally changeable and seemingly unpredictable. Mindful of this, no doubt, American company Davis Instruments have sent a catalogue of their Precision Weather Instruments that will delight the heart of any weather watcher.

Davis Instruments is a California-based manufacturer of high quality marine, weather and automotive products. They have a wide range of weather stations and accessories for many purposes, from education, agriculture, industry and expeditions, to "just for the hobbyist".

The Weather Wizard III Station, for example, is said to be "everything you need for measuring inside and outside temperature, wind speed and direction, wind chill, and daily and accumulative rainfall". It is priced at US \$250, although there are other units from \$195 to \$995.

In the higher price range are included advanced stations that are solar powered and have radio links to a base station, which can include a PC interface and a suite of analytical software.

For more information contact Davis Instruments, 3465 Diablo Ave., Hayward, CA 94545, USA. Tel: (510)732-9229. Fax: (510)732-9188. Web www.davisnet.com. Also browse www.sierracom.com and www.icselectronics.co.uk/icsnet.

Everyday Practical Electronics, July 2002

Greenweld E-bargains

GREENWELD Electronics, who are noted for their bargain offers, tell us that their E-Newsletters may become a more regular item "thanks to a new member of staff who has got it into her head that we ought to actually tell all our customers about the latest bargains when they come in, instead of just sitting here drooling over them!"

So, readers, get yourselves on Greenweld's E-newslist and get to the bargains before they are snapped up by those just sitting at home waiting for the postman to deliver news about them through snail-mail!

For more information email: bargains@greenweld.co.uk, or browse www.greenweld.co.uk.


Networks Expo

NETWORKS *Telecom Europe 2002* takes place at Birmingham NEC from 25 to 27 June 2002 and provides a platform to explore new products, network with leading vendors and keep abreast of the latest issues facing the networking industry.

There will be over 200 exhibitors, offering demonstrations and advice relating to new products and services.

For more information visit: www.networks-telecom.com.

Attractive Connections

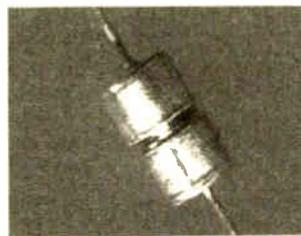

THE new Magtrix Connectors caused a bit of a stir on the newsdesk! They are magnetic and are said to be "an irresistible connection". Indeed so, for their size they probably have the strongest permanent magnet we've encountered.

A pair of them is shown in the photo, in which the two end surfaces are in strong magnetic connection to each other. The other ends have rigid wires attached to enable the magnets to be p.c.b. mounted so that they make strong electrical and physical contact with ferrous-based components, such as fuses and some types of battery casing, for instance.

They really have an extremely powerful semi-permanent bonding effect, allowing components to be securely retained yet removed from a circuit without desoldering. They can even pick up two D-type batteries weighing in at 300g!

The Magtrix connectors can also be used as the component part of actuators, Hall effect devices and generators. It seems that they must have many more applications in a hobbyist's workshop as well! They are supplied as five pairs to a pack (code MC/53GNS) for £3.75.

For more information contact Magtrix Connectors, Dept. EPE, 17 Larch Drive, Brinscall, Chorley PR6 8QN. Tel: 01254 830761. Fax: 01254 830408.

Email: sales@victorignition.co.uk.

Magnifico

FOR a bigger view of those tiny electronic components and their identities, you should "look into" Magnifico UK Ltd. They tell us they offer Britain's best online selection of magnifiers, loupes and low-vision aids.

On their website are over 100 products in six key categories, including handheld, illuminated, desk, sheet and handsfree. There is also a useful guide, *Choosing A Magnifier* to help with your selection.

Prices range from £2.75 to £120, so there's bound to be something for everyone. Prices include free delivery to any mainland UK address.

For more information contact Magnifico UK Ltd., Dept. EPE, 12 Sussex Road, Harrow HA1 4LX. Tel/fax: 020 8891 6966.

Web: www.magnifyingglasses.co.uk.

Email: sales@magnifyingglasses.co.uk.

Magfield Sensors

OVER recent years we have published three constructional projects that use the FGM-3 magnetic field sensor from Speake & Co. Bill Speake, the proprietor, tells us that he now has a website through which you can browse the company's full range of products. It can be accessed by either of the following:

www.speakesensors.co.uk, or
www.speakesensors.com.

New Technology Update

Holographic data storage promises to revolutionise the way the computer industry stores data and could even spell the end for the trusty disk drive, reports Ian Poole.

MEMORY and in particular long term memory such as that supplied by disk drives, tape drives and the like is a key element in electronics technology. Storage is being used at an ever increasing rate as software becomes more complicated and takes up more storage space. Also with the growing reliance on computer technology there is a greater need to take back-ups and have long term archive systems.

Instead of requiring disk sizes in megabytes, the storage sizes will be measured in terabytes. Whilst there is plenty of room for development using today's technologies, new ideas will be required for years into the future.

Many of these new ideas are emerging even now. This is a necessity as often they require many years of development before they can be made successfully on a commercial scale.

A company that is making some very significant inroads into storage developments that offer a quantum leap increase is called Polight Technologies. A Cambridge University spin-out, it has some interesting ideas that, it is claimed, are capable of revolutionising the way in which data is stored.

In fact, its ideas could sound the death knell for some existing forms of mass storage and may even spell the end for the trusty disk drive that has been at the centre of computer technology for so many years.

New Technology

The idea is based around a group of semiconducting glasses known as chalcogenides that contain Group VI elements. These exhibit some significant changes when they are illuminated by a particular form of light. These can include changes in structure, volume, and various optical properties including the refractive index and level of light absorption. As a demonstration of some of the effects that can be created, it has been shown that a bi-layer cantilever can be deflected up and down by exposing it to polarised light.

However, it is the change in refractive index that is of particular importance as this can be used to enable vast amounts of data to be stored. Up until now it has not been possible to use this form of optical storage commercially as a result of material problems.

Holographic storage

Now with the introduction of the new chalcogenides, a way forward is available and it is expected that it will be possible to commercialise this form of data storage using holographic techniques. This

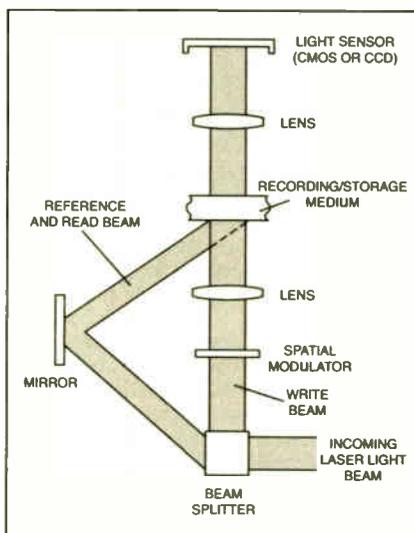


Fig.1. Basic concept of the new data storage system being developed by Polight Technologies.

involves optically writing data into a volume of photosensitive material.

This is achieved using a laser. The data is encoded into the laser beam using what is known as a spatial light modulator. This beam is combined with a reference beam and the combined light is then projected into the material.

To read the data the reference beam is projected into the material and emerging light contains the data that was written into the material and this can be converted into an electrical format using a CCD or CMOS sensor (see Fig.1).

The amount of data that can be stored is enormous. This is due to the fact that multiple images can be stored in the recording material.

This can be achieved because of the holographic nature of the images and the fact that the material has a very large dynamic range, each of the individual images uses up a portion of this range. To enable multiple images to be stored the angle of the reference beam is changed.

Only when the angle of the reference beam used to read the data matches the angle of the reference beam used to write the data match can the data be retrieved. By enabling a large variety of angles to be used, the amount of data that can be stored can be multiplied many times.

Work

A wide variety of work is being undertaken to fully investigate the new materials. Computer simulations of the atomic vibrational characteristics of real glasses

and of the new chalcogenides are being performed.

Thus a greater understanding of the way in which light phonons are related to the vibrational modes can be gained. In turn this can be used to gain a better understanding of the way data can be stored using these materials.

It is interesting to note that the early thermionic valve developments were greatly hindered by a lack of understanding of the way in which valves worked. This team are aiming to gain as full an understanding as possible.

First units

Polight's first storage product is being developed with investment partners. Called the Holodisc, this first product is a 500 Gbyte storage unit and uses a 250 to 500 micron thick element of chalcogenide. This gives it a memory data density of around 110Gbit/cm², a figure which is many times that of current disk drive technology.

It is expected that it will revolutionise the corporate back-up and archive storage markets. The unit offers read and write speeds of 750Mbytes per second in comparison to a DVD which offers a capacity of only 4-7Gbytes and speeds of 3Mbytes per second.

The market for the new product is expected to be huge, with sales in excess of \$25 billion by the year 2005. This shows the potential that can be realised when investors and academia come together.

Indeed, Professor Stephen Elliott commented: "This is an excellent example of Cambridge University and investors coming together to turn academic research into a real business opportunity. I'm delighted to see Polight complete this round: this company has a very exciting future in front of it".


Future

For the future, holographic data storage is highlighted by industry experts as offering the prospect of a revolution in data storage. Until now commercialisation has not been possible for lack of a suitable media. Now Polight has the challenge to resolve the last problems with its inorganic glasses that are given the name "Holonide".


Michael Ledzion, Polight's CEO commented: "Holographic data storage is the next big step forward for the removable data storage industry". It will now be very interesting to see how this new and exciting technology develops over the next few years, and the impact it makes on the computer industry.




BS2-IC

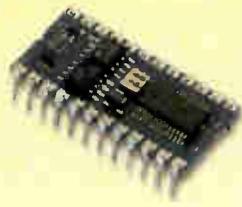


BS2-SX

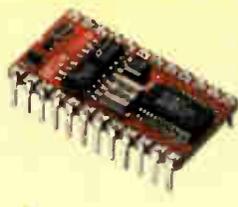

BS2E-IC

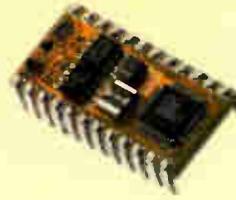


BS2P/24

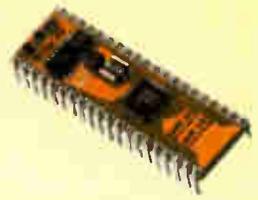

BS2P/40

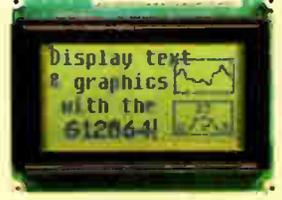Parallax BASIC Stamps - still the easy way to get your project up and running!




Serial Alphanumeric and Graphic Displays, Mini-Terminals and Bezel kits

www.milinst.com




Animated Head

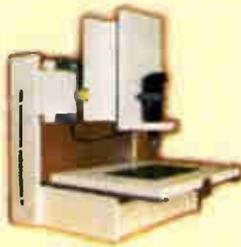

3-Axis Machine



Six-Legged Walkers

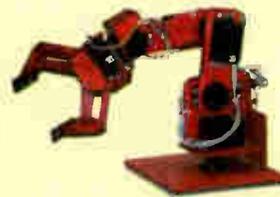


Robotic Arms




Bipeds

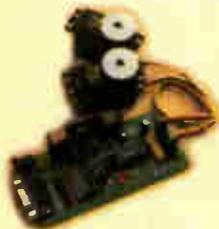Robotic models for both the beginner and the advanced hobbyist



Servo Drivers

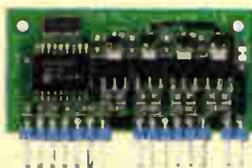


Motor Drivers



On-Screen Displays



DMX Protocol

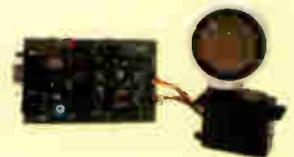

U/Sound Ranging

Animatronics and Specialist Interface-Control Modules



Quadvox MP3 & Speech Systems



SensoryInc Voice Recognition



Parallax Ubicom Tool Kits



Tech-Tools PIC & Rom Emulators



BASICMicro PIC BASIC Compilers

Development Tools

Milford Instruments Limited Tel 01977 683665, Fax 01977 681465, sales@milinst.com

Car Battery Trickle Charger

- A Sure Start

WORKING away out of the country for long periods often resulted in the writer returning home to find his car battery "dead". Whilst proprietary trickle chargers are available, they tend to be rather expensive and very bulky. The simple trickle charger shown in the circuit diagram of Fig.2 was made from scrap components for just a couple of pounds. The prototype has been in use for 18 months and has provided "first time" starts to a 3.5 litre sports car after standing for a 2½ month period, and a diesel saloon after six weeks in winter.

A discarded mains adapter from an old answering machine formed the heart of the unit, which produced an (unregulated) d.c. output of 17V at 500mA. An LM317 voltage regulator IC1 was built into the adapter casing, the device then being connected to the car via the cigar lighter socket.

The regulator provides a constant voltage under all conditions, and therefore a charging current inversely proportional to battery terminal voltage. A state of equilibrium is eventually reached between the charger output and the trickle charge requirement of the battery along with any loads formed by the car clock, alarm etc. A 200mA fuse near the cigar plug guards against shorts.

The prototype was set up by connecting an ammeter in the output circuit, connecting to car and mains supply and advancing the preset trimmer VR1 until a current of approximately 60mA was displayed. This corresponded to an output voltage of

approximately 14V. This value will need to be altered to suit the standing current drain from any car accessories permanently connected to the battery, but in practice a trickle current of around 50mA into the battery was found to be sufficient.

Not all cigar lighter sockets may allow such a connection, so consider a direct connection to the battery as an alternative,

observing all the usual precautions when dealing with lead acid batteries.

David-John Gibbs,
Southport.

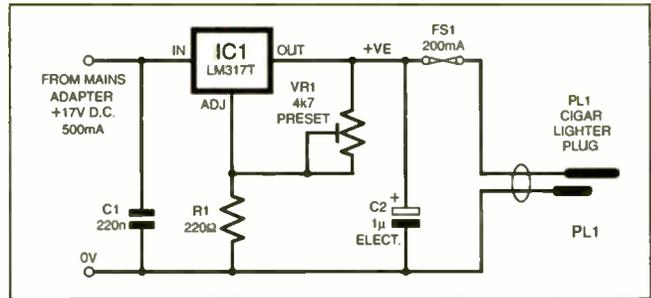


Fig.2. Circuit diagram for the Car Battery Trickle Charger. A novel application of a standard circuit.

APOLOGY

We regret to say that the item *Battery Discharger* (EPE May 2002 issue) was not an original item. EPE has since received an apology from Liao Jian Mei, the author concerned. Our thanks to the reader who notified us promptly and EPE duly apologises to the publishers of *Elektor* magazine who published the original circuit.

Additionally we are told that the item *Emergency Light Unit* by Steve Cartwright shown in the November 2001 issue is the same as a circuit devised by Alan Ainslie in *Practical Wireless* January 1976 and for this we apologise to *PW Publishing*.

Everyday Practical Electronics publishes readers' own circuits in good faith with a view to encouraging more efforts in circuit design, providing an outlet for ideas and

inspiring readers to develop ideas for themselves. EPE does everything possible to authenticate the circuits and contributors are required to sign a written legal disclaimer and confirmation of originality. Copyright infringement is a serious matter and readers who copy material and claim it is their own could be prosecuted.

Those who would attempt to defraud the column would do well to remember that EPE has many tens of thousands of very loyal readers around the world, some of them with extremely long memories. Any attempt to pass off a deliberately copied circuit as "original" will be exposed without mercy - both by upset readers as well as EPE.

NOTE: The *Emergency Light* circuit in the May 2002 issue (which is original) was sent in by Thomas Scarborough.



80-046 Electronic digital caliper for both imperial (0-6 inches) and metric (0-150mm). Accuracy +/-0.001". Simple touch button facility to change from metric to imperial (and vice versa). On/off and zero button, inside and outside measuring plus locking screw to hold measurement. Uses a standard watch battery (included). Metal construction. Supplied in a neat plastic storage case. **£34.95**



56-067 CR2016 lithium battery. 3V. 20mm diameter x 1.6mm high. **£1.00**
56-068 CR2025 lithium battery. 3V. 20mm diameter x 2.5mm high. **£1.00**
42-544 Lithium button cell, CR2032. 3V, 20mm diameter x 3.2mm thick. Brand new (not surplus). **£1.00**



80-078 Mains PSU, 220-240V AC input, 15V DC, 800mA output. Plug in the wall type. 2m flying lead to a 2.1mm power socket. **£3.95**



80-045 12V, 17Ah, lead acid, sealed rechargeable battery. Gel type. Brand new. 180 x 165 x 75mm. These are usually around £45.00 each to buy. **£14.95**



80-042 Switch mode PSU (ATX type) for computers. Mains input to DC output. +5V @ 32A, +3.3V @ 25A, +12V @ 8.5A, -5V @ 0.4A, -12V @ 0.7A, +5V (aux) @ 0.75A, maximum 330W. Made by AC Bel, Part No. API7506. Case size 150 x 145 x 105mm. Fan cooled. **£12.95**




48-111 Vibrating motor designed for pagers and mobile phones. 20mm long x 7mm diameter. Works between 3V and 6V. Very small and excellent quality. **£2.50**




80-102 IDE hard disk drive cable with 3 x 40 way IDC sockets so you can have two hard drives running off the same motherboard. 580mm long. **£1.50**



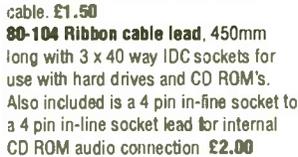80-103 Floppy disk drive cable to enable the use of up to 2 floppy disk drives. Has 3 x 34 way IDC sockets and 2 x 34 way card edge connectors mounted on a 650mm long ribbon cable. **£1.50**



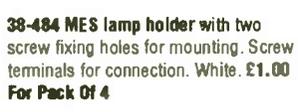
80-104 Ribbon cable lead, 450mm long with 3 x 40 way IDC sockets for use with hard drives and CD ROM's. Also included is a 4 pin in-line socket to a 4 pin in-line socket lead for internal CD ROM audio connection. **£2.00**



38-484 MES lamp holder with two screw fixing holes for mounting. Screw terminals for connection. White. **£1.00**
For Pack Of 4



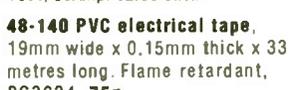56-155 KBPC3501 bridge rectifier 100V, 35Amp. **£2.50 each**



48-140 PVC electrical tape, 19mm wide x 0.15mm thick x 33 metres long. Flame retardant, BS3924. **75p**



56-006 Brand new 12V DC fan. 80 x 80 x 25mm with 10" red and black lead. **£2.95**



WON SUPPLIES


WON Supplies
 Dept EE · The Old Grain Store
 Rear Of 62 Rumbidge Street
 Totton · Southampton · SO40 9DS
 Telephone or Fax On
 Southampton 023 8066 0700
 Email: info@wonsupplies.fsnet.co.uk

SEND FOR OUR FREE CATALOGUE CONTAINING EVEN MORE BARGAIN ITEMS!

**ALL PRICES INCLUDE VAT
ADD £2.25 FOR P & P**

EPE STYLOPIC

JOHN BECKER

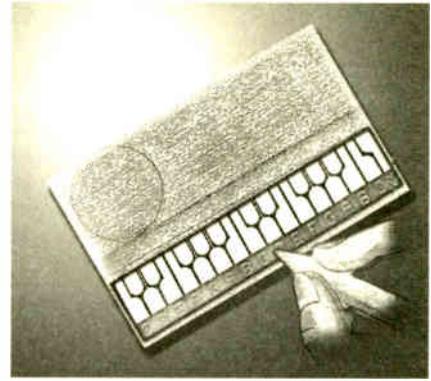

Have fun with a modern interpretation of a classic musical instrument!

ROLF Harris is well known these days for his concern for sick animals. Back in the 1970s (and later) though, he was popular as an entertainer who would delight his audience by (amongst many other activities) playing the didgeridoo, wobble-board and the *Stylophone*. The latter was a compact hand-held electronic musical instrument having a built-in keyboard which was activated by an electrically conductive stylus.

The *EPE StyloPIC* pays homage to this classic design, which is now relegated to the depths of history and enthusiast's web sites (although we know some readers still have the real thing, and second-hand ones can still be found!). It is really simple in its concept, yet remarkably fun to play!

HISTORY

Some of you familiar with the original *Stylophone* can be forgiven for perhaps thinking that Rolf Harris actually invented this superb little instrument. In fact, his involvement was purely promotional, but this was to prove crucial to the *Stylophone*'s success.

The *Stylophone* came about as a result of a certain Brian Jarvis having been asked to repair his young niece's toy piano. Not only did he do so, but added a modification that led to the idea of a completely new hand-held electronic instrument.



Rolf and the *Stylophone* – “The greatest little instrument of the century!” Courtesy www.stylophone.fsnet.co.uk

Brian was one of a team who in 1967 had founded a company providing dubbing and recording services to the broadcast and film industry, from which services the company name Dubreq was derived.

Brian and his partners, Bert and Ted Coleman, recognised that this instrument had great potential, if only it could be marketed effectively, with television being the obvious medium.

With this in mind, the team also recognised that the popularity of Rolf Harris made him the ideal celebrity to help promote their innovative instrument. Bert demonstrated the *Stylophone* to Rolf, who is said to have been “very impressed”.

This ultimately led to the instrument making its debut on Rolf's BBC TV *Saturday Show*, in which a renowned support troupe of the era, *The Young Generation*, played along with Rolf on six additional *Stylophones*. The Rolf Harris connection was to lead to the *Stylophone* becoming known as the “greatest little instrument of the century”!

EXPANSION

Initially, *Stylophones* were hand-made and (in “pre-decimal money”) sold at £8 18s 6d (£8.92 “modern”), which is estimated to be the equivalent of £95 in today's money. Production soon expanded and a move was made from Dubreq's basement premises to a proper factory in Cricklewood, London. Staff numbers would eventually grow to around 75 during the company's full production life.

The original *Stylophone* was a monophonic instrument which comprised a metal keyboard, a stylus to play the notes, vibrato and on-off switches, plus a line-out socket. There was also a spindle underneath for fine tuning. Although there were only two basic models made, there

were many variants, including the components used, and in the finish, colour, keyboard and packaging.

Dubreq licensed the *Stylophone* to America, Germany, France and Hong Kong. Its major success, though, brought the inevitable copies and copyright infringements. During its production lifetime approximately four million units were sold in the UK alone.

Developments in technology eventually caused the demise of the *Stylophone* in the early 1980s. The simple electronics around which it was based were superseded by the far more sophisticated technology being used in instruments originating from the Far East.

Dubreq ceased manufacture in 1977 and was wound up in 1980. The original prototype *Stylophone* is said to still exist!

STYLOPIC CONCEPT

Whereas the original *Stylophone* had 20 keypad zones, the *EPE StyloPIC* has been extended to cover two full octaves – 25 notes including sharps and flats (C to C – 261Hz to 1046Hz). It too, of course, is activated by a stylus, which makes contact with the integral keyboard-style printed circuit board that also holds the electronic components. Its tuning accuracy is superb, the software making use of a technique hitherto unpublicised through *EPE*.

Apart from the PIC microcontroller, there are only three active integrated circuits – a waveform converter, an envelope shaper and an amplifier. The circuit diagram in Fig.1 shows the detailed connections between the *StyloPIC*'s keyboard and the microcontroller, IC1, along with the waveform converter, IC2, and the simple regulated power supply, derived via IC3. The envelope shaper and amplifier are discussed later, referring to Fig.2.

The keyboard contacts are formed on the printed circuit board (p.c.b.) in the style of a 25-note keyboard, plus an additional “mode-change” contact which causes a change in the tonal quality of the notes produced. All contacts are connected to individual inputs of the PIC16F877 microcontroller.

Note that in Fig.1, the keyboard notation is shown in the order best suited to illustrating the PIC's port connections in an appropriate visual order. On the p.c.b., of course, the keyboard connections are in the correct musical order!


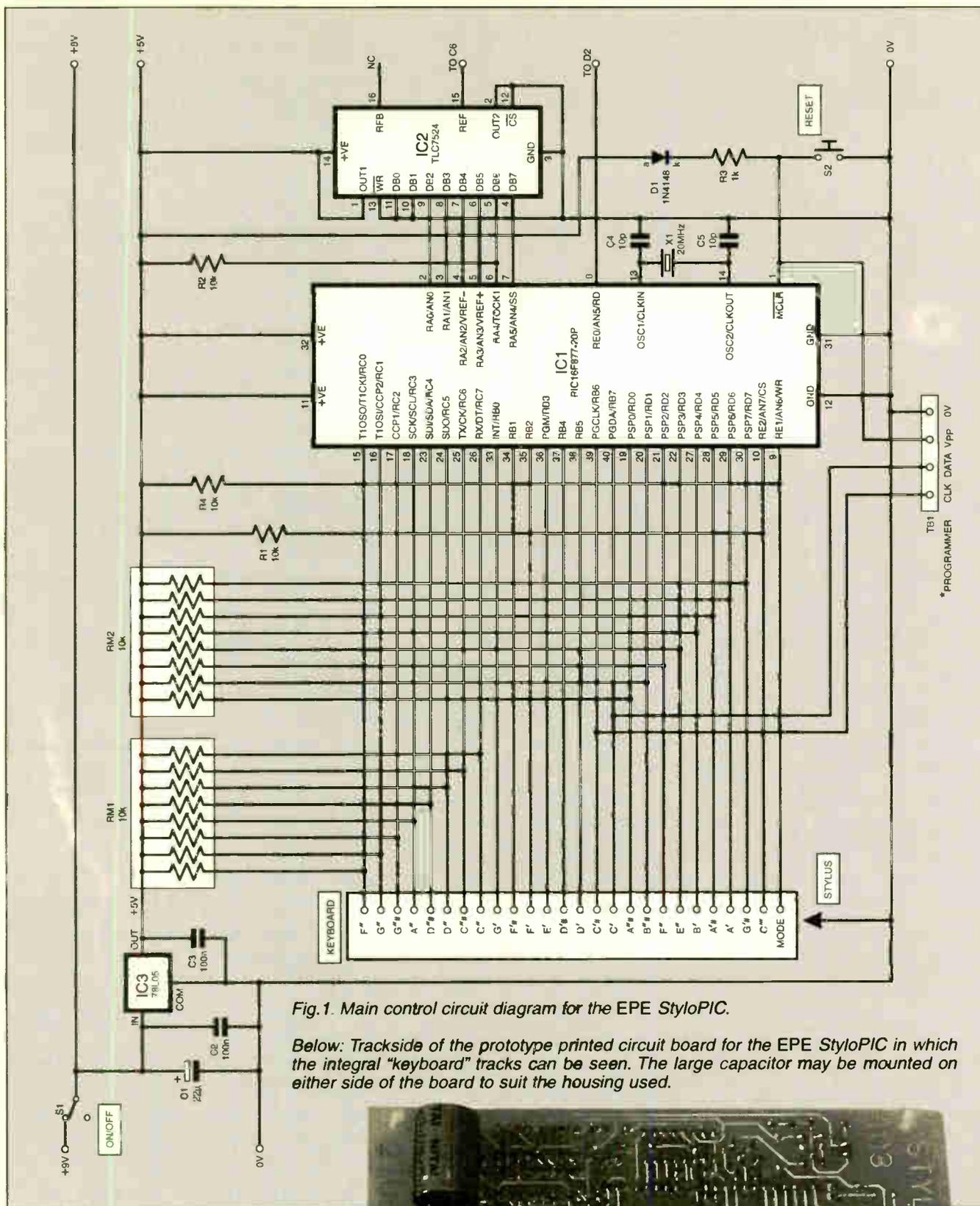


Fig.1. Main control circuit diagram for the EPE StyloPIC.

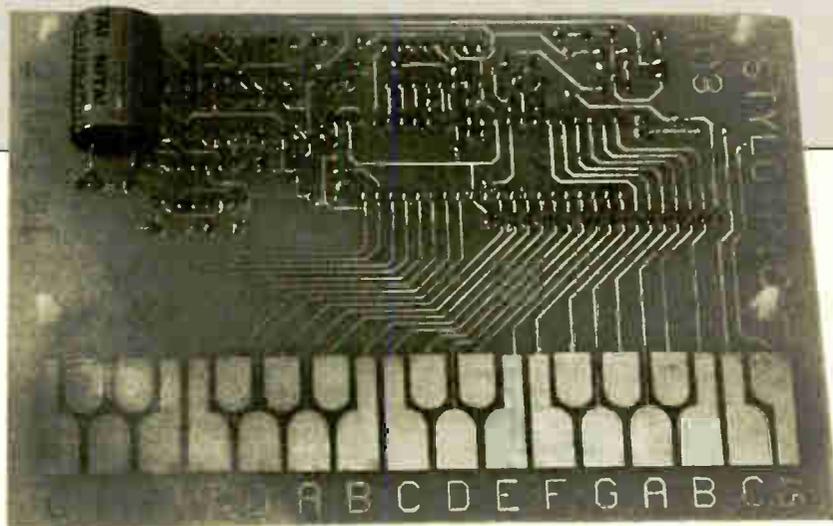Below: Trackside of the prototype printed circuit board for the EPE StyloPIC in which the integral "keyboard" tracks can be seen. The large capacitor may be mounted on either side of the board to suit the housing used.



All contacts except for the eight connected to the PIC's Port B are biased normally-high via individual resistors, eight within each of resistor modules RM1 and RM2, plus two designated as R1 and R4. The connections to Port B (RB0 to RB7) are held normally-high by the PIC's eight internal pull-up resistors.

The stylus which causes the notes to be triggered is connected to the 0V line. When it connects with a note key, the respective PIC line is taken low, the PIC responding according to which line has been affected.

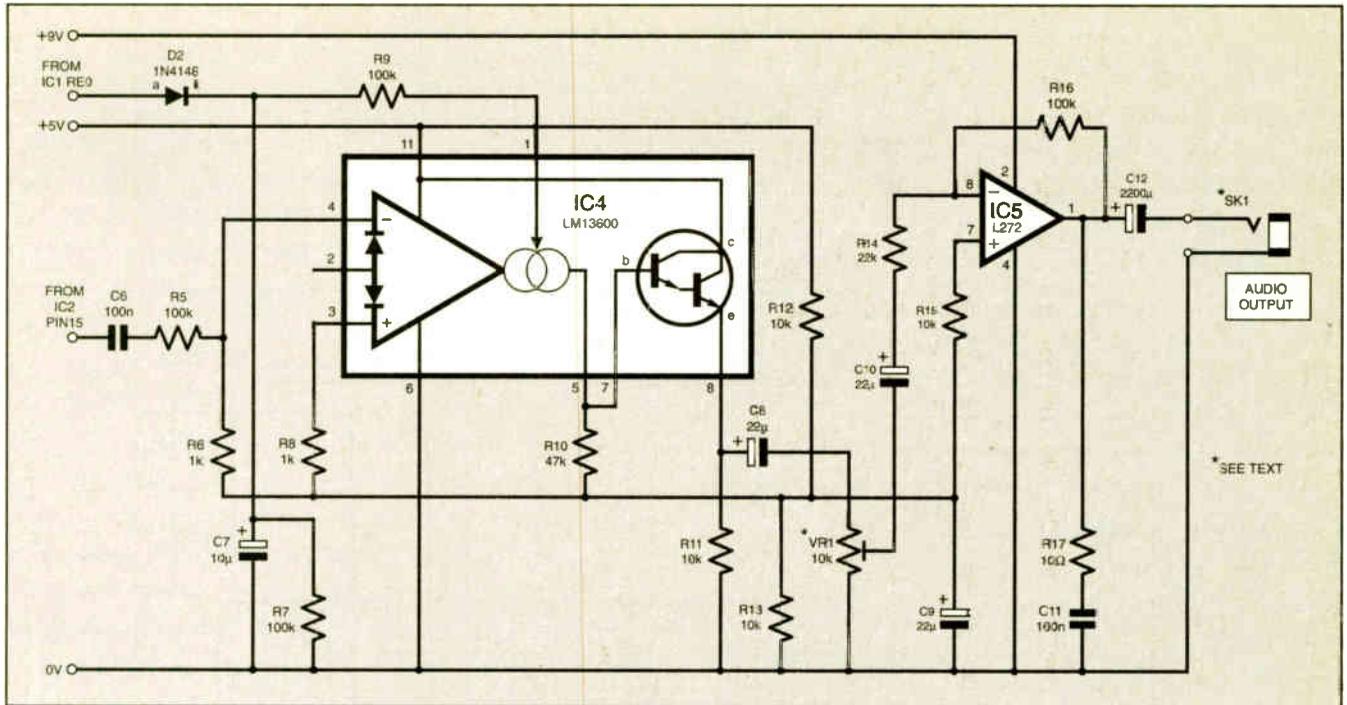


Fig.2. Circuit diagram for the envelope shaper and output amplifier.

In response to music keys being activated (as opposed to activating the Mode Change key) the PIC increments an internal counter at a rate related to the note frequency required. The counter's value is output via Port A (RA0 to RA5) to six inputs of the 8-bit digital-to-analogue converter (DAC) IC2, whose other two inputs are held permanently low.

The manner in which the counter's value is output determines the tone of the note produced. This stage and the subsequent envelope and amplifier stages are essentially the same as used in the author's *PIC Magick Musick* design of *EPE Jan '02*. However, whereas that design always generated a rising ramp waveform via the DAC, the option to output a square waveform has been provided here.

This tone-change function is triggered via the Mode key feeding into PIC pin RE1. Each time the key is activated the mode changes, alternating between the ramp and square options.

It is believed that the original *Strylphone* probably output a squarewave, but the author finds the ramp (sawtooth) waveform more harmonious to the ear. Indeed, as shown through *Magick Musick*, when envelope shaping is applied as well, a very piano-like sound is created.

The DAC is used in the mode which allows a voltage-related output to be generated in respect of digital input values (it can also generate current related outputs). In the voltage output mode, the voltage signal is taken from the device's REF (reference) pin, with the two "normal" outputs (OUT1 and OUT2) connected to +5V and 0V respectively. If you wish to explore this

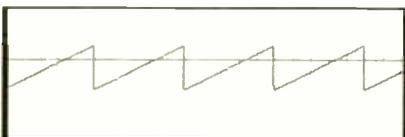


Fig.3. Sawtooth waveform created via DAC IC2.

device's attributes in detail, its datasheet can be download free from www.ti.com.

An example of the ramp waveform generated is shown in Fig.3.

ENVELOPE SHAPING

Referring now to Fig.2, envelope shaping is performed by transconductance amplifier IC4, an LM13600 device, whose datasheet can be download from www.nsc.com (it was also discussed in *Circuit Surgery Dec '01*).

As in *Magick Musick*, it is used as a voltage controlled amplifier (VCA) that is under pulsed control as an envelope shaper (varying the amplitude of a frequency signal across a specific period). In this application, the pulse control is applied from PIC pin RE0 to IC4 pin 1.

The pulse is modified by the action of diode D2, capacitor C7 and the combined resistance of R7 and R9. As will be seen from the waveform in Fig.4, the voltage at IC4 pin 1 rises rapidly when the pulse arrives from RE0. When it ceases, the voltage across C7 decays at a rate determined by the current flowing through R7 and R9.

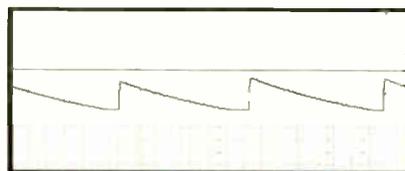


Fig.4. The envelope shaping pulse at capacitor C7

It is the current that flows into IC4 pin 1 that determines the amplitude of the audio signal "transconducted" through IC4, from pin 4 to pin 5, and secondarily governed by the value of resistor R10. The signal at R10 is then buffered by IC4's internal Darlington transistor and output via capacitor C8 to potentiometer VR1, and thence to the audio amplifier stage around IC5.

A typical waveform as seen at IC4 pin 8 is shown in Fig.5. It clearly illustrates the

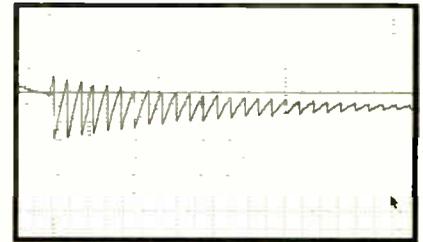


Fig.5. The attack and decay of a note as controlled by the envelope shaper.

"attack" as a note is triggered by a pulse from the PIC, and the subsequent "decay" of the amplitude when the pulse has ended. Note that the software has been written so that the PIC's trigger pulse remains high for as long as stylus contact with the key is maintained. This allows a certain amount of "colour" to be introduced to the musician's playing.

Whilst VR1 is shown as a preset potentiometer (mounted on the p.c.b.) an external rotary pot could be used instead, mounted in the chosen case. In this instance, a logarithmic (log) potentiometer is recommended.

An L272 audio amplifier (IC5) is used for the final output stage. This device is capable of outputting about 1W and is suitable for coupling into loudspeakers or headphones having impedances as low as 8Ω.

The output is a.c. coupled via capacitor C12 and may also be fed to the line-input of a normal domestic amplifier.

The device has been given a gain of about x5 and the maximum output level is around 3V peak-to-peak. Resistor R17 and capacitor C11 give stability to this power op.amp (which is actually a dual channel device, although only one channel is used).

POWER SUPPLY

The circuit is basically run at 5V as regulated by IC3 (Fig.1), except for the power amp IC5, which is powered at the full voltage of the power supply. The latter may be any d.c. source between about 7V and 15V.

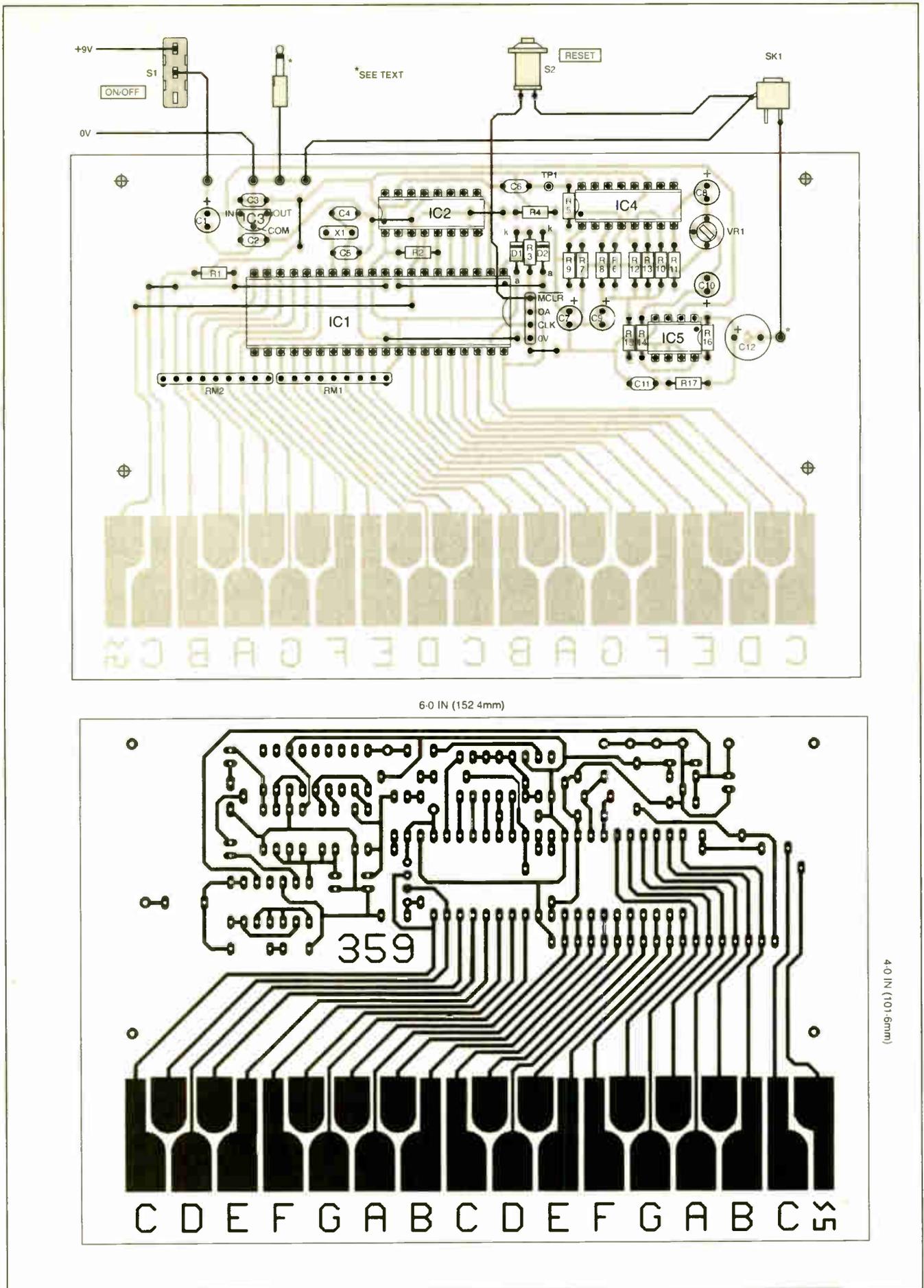


Fig.6. Component layout and full-size master track pattern for the EPE StyloPIC printed circuit board. Note that capacitor C12 may be mounted on either surface of the board to suit the housing used, and is best positioned "lying down" rather than vertically. Also note that several on-board link wires are required below the i.c. sockets, and that resistor modules RM1 and RM2 have "orientation" marks on their bodies which must correspond in position to the indications in the top figure.

A 9V battery may be used (e.g. PP3). Capacitor C1's voltage rating should be increased to 25V for supply voltages above 12V.

Maximum current consumption will depend on the amplitude output from the power amp. In the prototype, the current was about 14.5mA with no audio output, rising to about 80mA when driving an 8Ω speaker at full amplitude with IC5 powered at 9V.

CONSTRUCTION

The printed circuit board component layout and tracking details are shown in Fig.5. This board is available from the *EPE PCB Service*, code 359. Assemble in any convenient order you prefer, using sockets for the d.i.l. (dual-in-line) i.c.s, and observe the correct orientation for the polarity sensitive components (including resistor modules RM1 and RM2).

Note that capacitor C12 is physically large. It may be mounted flat on either side of the board to suit the type of housing in which the StyloPIC is housed. It seems likely that in most instances mounting on the trackside would be more suitable (as done with the test model).

Treat all i.c.s as static sensitive and discharge static electricity from your body before handling them (touch a water pipe or the bare metal of a grounded item of workshop equipment). Do not insert them until the correctness of the regulated 5V power supply has been proved.

If you intend programming your PIC *in situ* (see later) do not connect Reset switch S2 until you have done so (it uses one of the programming terminals).

STYLOPIC CASING

The test model was not mounted in a case and is simply enjoyed as an unprotected fun instrument on the author's workbench. No definitive suggestions for housing your own are offered, but you may find inspiration from the earlier photograph of an original *Stylophone*.

A plastic slim-line case measuring about 180mm × 120mm × 40mm might also be considered. In this instance, the p.c.b. could perhaps be mounted so that it slides in and out of the front aperture, protruding just so far as is required when actually playing the keyboard.

It is strongly recommended that the outer corners of the keyboard should be filed so that they are rounded and smoothed to avoid damage to your playing hand as it frantically keys-out *Tie me Kangaroo Down Sport*, or some other "Rolfarian refrain" or similar!

You may need to glue a wooden or plastic support under the front of the keyboard area to prevent the board from tilting while playing.

If using an internal speaker, the size of the above mentioned case would probably allow it to be mounted either under the lid, or above the base, with suitable holes drilled to let the sound out adequately. A rotary volume control and jack socket for external sound output could be mounted on the rear panel, along with switches S1 and S2.

It seems likely that a PP3 battery will fit comfortably to the side of the p.c.b. Those are just idle thoughts, though – let not the author impose his will on your creativity!


A word of caution, though. It is unusual for a p.c.b. to be used trackside upwards. Do ensure that the tracks around the i.c.s. cannot be shorted by inadvertent contact with anything conductive. However, the keyboard tracks themselves may (and must!) remain open and electrical shorts between them are permissible (and unavoidable when playing glissando).

It is also important that undesirable external voltage sources are not applied to the unit, which could cause a safety hazard. If you are plugging the unit into another item of equipment, full consideration must be given to whether or not that equipment could potentially cause high voltages (e.g. mains a.c.) to be applied to the StyloPIC tracks.

DURABILITY

With the prototype, the stylus principally used is a round-ended probe from a multimeter. Occasionally the rounded tip of a 3.5mm jack plug has been used. Whatever your choice of stylus, ensure that the contact area is as smooth as possible to avoid damage to the p.c.b.

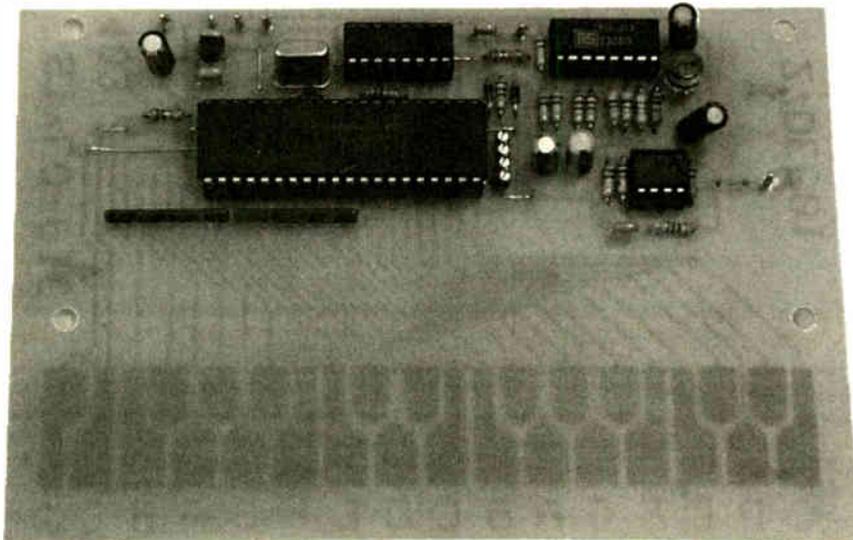It is acknowledged that the long-term durability of the p.c.b. tracks will be significantly lower than that provided by the



Component side of the StyloPIC. It is turned the "other-way-up" to play the keyboard!

COMPONENTS

Resistors

R1, R2,		See SHOP TALK page
R4, R11 to		
R13, R15	10k (7 off)	
R3, R6, R8	1k (3 off)	
R5, R7,		
R9, R16	100k (4 off)	
R10	47k	
R14	22k	
R17	10Ω	
RM1, RM2	10k, 8-common resistor module (2 off)	

All 0.25W 5% carbon film except RM1 and RM2.

Potentiometer

VR1	10k min. preset, round, or rotary log (see text)
-----	--

Capacitors

C1, C8	
to C10	22μ radial elect. 16V (4 off)
C2, C3,	
C6, C11	100n ceramic, 5mm pitch (4 off)
C4, C5	10p ceramic, 5mm pitch (2 off)
C7	10μ radial elect. 16V
C12	2200μ radial elect. 25V

Semiconductors

D1, D2	1N4148 signal diode (2 off)
IC1	PIC16F877-20 microcontroller (20MHz), preprogrammed (see text)
IC2	TLC7524 digital-to-analogue converter
IC3	78L05 +5V 100mA voltage regulator
IC4	LM13600 transconductance amplifier
IC5	L272 dual power op.amp

Miscellaneous

S1	min. s.p.d.t. switch
S2	min. push-to-make switch
SK1	3.5mm mono jack socket (see text)
TB1	1mm terminal pins or pin-header (optional)
X1	20MHz crystal

Printed circuit board, available from the *EPE PCB Service*, code 359; 8-pin d.i.l. socket; 16-pin d.i.l. socket (2 off); 40-pin d.i.l. socket; stylus (see text); loud-speaker or headphones (see text); case to suit (see text); supports for p.c.b. (see text); connecting wire; solder etc.

Approx. Cost
Guidance Only
excluding speaker, case & batts

£25

steel-based keyboard of the *Stylophone*. Readers using the ready-made board from the *EPE PCB Service* should fare better in this respect since the boards are roller-tinned, unlike the bare copper boards that (usually) result from making your own.

Nonetheless, whilst you will periodically get carried away with rapid glissandos and staccato keying, try not to dig holes into the keyboard pads, and certainly avoid contact with the connections leading from

them to the PIC. Probably, though, a touch of the soldering iron will repair minor damage.

SOFTWARE HIGHLIGHT

It was mentioned earlier that the tuning accuracy of the StyloPIC surpasses that for any PIC-controlled music design previously published in *EPE*.

You may recall that in *PIC Magick Musick* there was a brief discussion about the difficulty of accurately generating exact frequencies when using a PIC. That discussion related to "conventional" frequency generation in a which a counter is incremented by whole values (minimum of one unit) within a loop whose length is varied to change the resultant output frequency.

There is another technique whose principle has been used by the author in other non-musical PIC applications in which fractional values can be added in the loop. Once such instance was with his bike computer (*PIC-Agoras*) of April '87 in which distance was calculated in relation to precise wheel diameters, and required the use of binary fractions.

However, the author had not thought to relate this technique to music generation until Peter Hemsley (of renown for his many *PIC Tricks*) pointed out the possibility. Thank you, Peter, it's a superb way of achieving accuracy, and is used here in the StyloPIC!

To achieve it, though, a much higher clock frequency is required to control the PIC than is usually employed for many designs. As you will see from Fig.1, the rate used here is 20MHz – effectively the top rate at which a PIC16F877 is designed to operate (although as many readers will have found, PICs can often be driven at rates in excess of their specifications – but we would be reluctant to actually publish over-driven designs).

In "conventional" frequency-generating PIC software the following technique is typically used:

```
START:    clrf COUNTER
FREQ:    movf COUNTER,W
          movwf PORTB
          nop
          incf COUNTER,F
          goto FREQ
```

In this routine the value of COUNTER is repeatedly incremented and output to one of the ports, Port B in this instance. The rate at which Port B bit 0 oscillates would be the highest frequency available from this loop. That at Port B bit 7 would be the slowest, at eight octaves below that at bit 0 (i.e. 256 times slower). The actual frequency range would be controlled by the number of NOP instructions included in the loop.

In the "fractional" technique, a binary word (two bytes) holds a constant 16-bit value which is repeatedly added to a 3-byte counter (23 bits) within a loop. It is the value of the most significant byte (counter bits 16 to 23) which is output to the port. This technique provides a far greater potential for tuning accuracy due to the ability to change the additive value by as little as 1/65536.

TUNING ADJUSTMENT

In the StyloPIC tuning values for all 25 notes are held in two blocks within the PIC's data Eeprom. When the PIC has been

newly programmed, the two blocks are identical, the second being regarded as holding the "author's default" values, i.e. those which held true with the prototype unit.

There will be slight differences between clock rates of individual versions of the StyloPIC due to the crystal-generated frequency not being at exactly 20MHz. This is a perfectly natural situation with crystals. As with other component types, crystal values have a manufacturing tolerance spread.

Not only that, if the StyloPIC is to be used alongside other instruments, it may be desirable to change its pitch to suit the pitch set for the other instruments. Consequently, a pitch adjustment option has been provided within the software.

Pitch tuning can be shifted symmetrically across all 25 notes, both upwards and downwards. The author's default values can also be recalled to replace the user's own values should the need arise. Tuning of individual notes is not allowed for, nor is it desirable since the frequency relationship between each note is mathematically derived (ideal note frequencies are shown in Table 1). Consequently, any frequency shift has to be applied equally relative to each note's mathematical ideal.

Table 1. Mathematically calculated ideal frequency values for the notes covered by the StyloPIC.

Note	Frequency (Hz)
C'	261-625
C#	277-182
D'	293-664
D#	311-126
E'	329-627
F'	349-229
F#	369-994
G'	391-995
G#	415-304
A"	440-000
A#	466-163
B"	493-883
C"	523-251
C#	554-364
D"	587-328
D#	622-252
E"	659-254
F"	698-458
F#	739-988
G"	783-990
G#	830-608
A"	880-000
A#	932-326
B"	987-766
C"	1046-50

Thus, if you increase note Concert A from 440Hz to 441Hz, A at the next octave up is automatically increased to 882Hz, exactly twice that of the lower note.

To change the pitch of the entire 25-note block, Reset switch S2 is pressed (while the unit is fully powered) and the stylus applied to one of three keys. Keeping the stylus on the selected key. Reset is released and the program restarts from the beginning. During the initialisation it recognises which key is active and the program jumps to an appropriate correction routine. The interception routing is shown in Listing 1.

As you will see, if top C is keyed, an increase in pitch is required. Keying bottom C causes a reduction in pitch, while

LISTING 1

```
btfss PORTE,2      ; is increase in tuning
                    ; freq needed?
                    ; (top C keyed)
call TUNEUP         ; yes
btfss PORTB,7      ; is decrease in
                    ; tuning freq need-
                    ; ed? (bot C keyed)
call TUNEDOWN      ; yes
btfss PORTD,6      ; is restore of orig
                    ; tuning freq need-
                    ; ed? (A 440 key)
call RESTORETUNE   ; yes
call GETNOTES
```

keying Concert A 440Hz (A nearest to the left of the keyboard) results in the author's defaults being restored.

Readers having TK3 and its board could actually change the pitch by as little as one least significant bit via the MSG file amendment/programming option.

RESTORING

Any changes actioned are automatically stored back to the first block in the Eeprom, where they remain even after power has been switched off, being recalled again when the unit is next switched on.

Tuning adjustment is in relation to the value held in the MSB (most significant byte) of the 2-byte tuning value in the author's default block. For example, if tuning upwards is needed, the author's MSB is retrieved from the Eeprom, halved and added to the LSB (least significant byte) of the value for the equivalent note in the user's block, automatically incrementing the user's note MSB if a Carry (roll over of the LSB) results from the addition. The process is automatically repeated by the software routine for all 25 notes.

Similarly, if a decrease in pitch is required, half the value of the author's MSB is subtracted from the user's LSB/MSB. Restoration of the author's defaults simply entails copying these values into the user's data Eeprom block.

Each adjustment is only performed once for any call via the Reset option. As soon as the adjustment has been made, the PIC waits until the stylus has been removed from the selected key. It then stores the new values back to the user's Eeprom block.

Having done so, and even if adjustment has not been called, the software extracts all values from the user's Eeprom (GETNOTES routine called in Listing 1) and stores them into a 50-byte wide block (25 pairs of note values) of the normal data registers (NOTEVAL, commencing at \$30). These are the tuning values then accessed by the software when the StyloPIC is in normal use.

When the values have been extracted following switch-on or Reset, Concert A 440Hz is triggered, and will be heard from the loudspeaker or headphones as a hard-attack, slow decay audio output (assuming you have turned up volume control VR1!). Although the audio output decays, the note itself continues to be generated at the pin 15 output of DAC IC2. This may be monitored by a frequency counter at test point TP1. To establish its true accuracy, use a frequency counter that shows the result to at least one decimal place. The frequency

for *true* Concert A should be exactly 440.0Hz.

Should you decide that a further adjustment of the pitch is required, repeat the Reset procedure as just described.

GENERATION GAME

The software has been written so that all lines from the keyboard are constantly scanned to see if any is being touched by the stylus. If one has, a lookup table is used to determine which note frequency it refers to. If the note is different to the previous one called, that note's 2-byte tuning value is then copied from the NOTEVAL block and stored into registers *FREQHI* and *FREQLO* (MSB and LSB respectively). Simultaneously, the envelope shaper is triggered via PIC output *RE0*.

It is the *FREQHI/LO* value that is added to the frequency generation counter pair *WAVEHI* and *WAVELO* in routine *PLAYIT*. Each time the added value causes *WAVEHI* to rollover (Carry flag set), another counter, *OUTPUT* is incremented. It is the value of this counter that is output to Port A and DAC IC2. Listing 2 shows the structure of the *PLAYIT* routine.

There are two points especially worth noting in Listing 2. First, it will be seen that the status of the Carry flag is not actually tested (e.g. *BTFSS STATUS,C*), but its status is extracted as a value which is then added to *WAVEHI*, regardless of whether the answer is 0 or 1.

One of the most import aspects of music generation software is that all functions are absolutely consistent in their timings, irrespective of any intermediate actions that have to be performed during them. To have actually tested the Carry flag would have resulted in different loop timings, depending on the result of the test. This would probably be heard as a brief "hiccup" (unevenness) in the note. The process shown in Listing 2 avoids this brief deviation.

Secondly, it is in the *PLAYIT* routine that the output waveform is set to either ramp or squarewave. Towards the end of Listing 2 is the command *BTFSC MASK,0*. Register *MASK* is that which holds the waveshape flag as triggered by touching the stylus on the keyboard's right-hand pad (marked with a triangle and squarewave) below it.

If *MASK* bit 0 is set (= 1) then the ramp waveform is required and the routine jumps to label *PLAY2* and then at *OUTIT* outputs the full value of the *OUTPUT* counter to Port A.

If *MASK* bit 0 is not set (= 0), the squarewave output is required. This is generated by outputting a value of 0 or 31 (binary 00111111), depending on the state of the count. If bit 5 of *COUNTER* is high then 31 is output, otherwise the output value is 0. In both instances the four *NOP* commands at *PLAY2* are bypassed.

The *NOPs* are again there for timing balance, this time between the different times it takes to process the ramp waveform compared to the squarewave.

If you study the full listing for the *StyloPIC* you will find numerous *NOP* commands inserted, all to maintain the timing balance between various stage aspects. **IT IS IMPERATIVE that you do NOT change the number of *NOPs*.** You will lose tuning consistency if you do.

LISTING 2

```
PLAYIT:  movf FREQLO,W      ; get freq LSB and add it to WAVE LSB
         addwf WAVELO,F
         movf STATUS,W     ; add Carry (if any) to WAVE MSB
         andlw 1
         addwf WAVEHI,F
         movf STATUS,W     ; add Carry (if any) to OUTPUT register
         andlw 1
         addwf OUTPUT,F
         movf FREQHI,W     ; get freq MSB and add it to WAVE MSB
         addwf WAVEHI,F
         movf STATUS,W     ; add Carry (if any) to OUTPUT register
         andlw 1
         addwf OUTPUT,F
         movf OUTPUT,W
         btfsc MASK,0      ; is MASK = 1 (ramp)?
         goto PLAY2       ; yes
         movlw 0           ; no, so square needed
         btfsc OUTPUT,5    ; should output be low?
         movlw %00111111  ; no, it should be high
         goto OUTIT
PLAY2:   nop               ; timing balance delay
         nop
         nop
         nop
OUTIT:   movwf PORTA      ; output value to PORTA
         goto MAIN
```

SOFTWARE

The *StyloPIC* software was written in TASM grammar on *Toolkit TK3*, through which it can be translated to MPASM grammar for use with such software as MPLAB, for example. It is available on 3.5in disk (for which a small handling charge applies) from the *EPE* Editorial office, or by free download from the *EPE* ftp site.

The easiest access to the ftp site is via our main web site at www.epemag.wimborne.co.uk. At the top of the main page click on the ftp option, then select in order of PUB - PICS - *StyloPIC*.

There are four files involved: *ASM* (TASM), *OBJ* (TASM), *HEX* (MPASM) and *MSG*. The latter holds the data Eeprom tuning values in the format specific to *Toolkit TK3* (whose software is also available for free download via our ftp site). Non-*TK3* users will need to incorporate these values into the *HEX* file so that during programming they are loaded into the PIC's data Eeprom commencing at location 0.

PIC configuration is embedded into the *HEX* file. *OBJ* users should configure the *PIC* for HS crystal, *WDT* off, *POR* on.

The printed circuit board includes connections through which the *PIC* can be programmed using *TK3* and its *MK3* board. The connections are in the author's standard order (via *TB1*, see Fig.1). Remember to connect switch *S2* after you have completed the programming.

Programmed *PICs* are available as discussed in this month's *Shoptalk* column (which also provides essential information on component sourcing for the *StyloPIC*).

STYLOPHONE WEBSITES

Doing a search on *Stylophone* via www.google.com revealed that at the time of writing it provides access to 2260 *Stylophone*-related sites, while www.yahoo.com has 1610 sites available.

Some other sites not only offer history and other information about the

Stylophone, but also offer second-hand ones for sale (for about US \$70 on one site). There are also sites that allow you to download and play with simulations of the *Stylophone* on your PC.

Other sites deal with the spin-offs that resulted from the *Stylophone* craze, including information on the musicians and groups who used the instrument on their recordings, such as David Bowie, for example, on his *Space Oddity* (spelled *Odyssey* on some sites - never mind, it's a superb track whatever its name!).


There are too many sites for the author to provide a list of the most interesting ones, but one in particular is worth highlighting:

www.stylophone.fsnet.co.uk

which the author found especially fascinating, and from which the earlier "history" paragraphs were distilled (there is much more, and very interesting, information in the original - browse it!). The images of a *Stylophone* also came from this site.

PUTTING ON THE STYLE

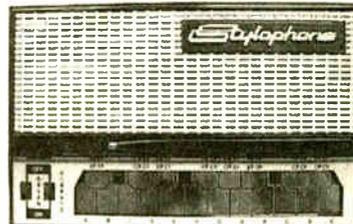Whilst the heyday of the *Stylophone* is long gone, it continues to live on as an excellent example of how someone's innovative brainwave materialised as a product that really caught people's imagination. It is hoped that many of you will find enjoyment through playing with the author's modern re-interpretation of the original simple yet very effective idea. □



READOUT

E-mail: editorial@epemag.wimborne.co.uk

John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

WIN A DIGITAL MULTIMETER

A 3½ digit pocket-sized l.c.d. multimeter which measures a.c. and d.c. voltage, d.c. current and resistance. It can also test diodes and bipolar transistors.

Every month we will give a Digital Multimeter to the author of the best *Readout* letter.



★ LETTER OF THE MONTH ★

P.C.B. SIZES AGAIN

Dear EPE,

Regarding the enquiry by Dave Stacey on p.c.b. sizes (*Readout* June '02), I have also had re-sizing problems with pdf file p.c.b. sizes, and with trying to import pdf files into Photo Suite, Photo Studio and Photo Plus for editing. The ubiquitous free Adobe Acrobat Reader unfortunately allows no graphics editing. Not only that, but scanning poor quality paper magazine layouts produces unwanted image artifacts, and can cause closely placed tracks and pads to merge on the final printout, making the scan unusable as a p.c.b. master image.

I have found a solution: it is so simple, quick and easy, and produces such accurate and high quality p.c.b. masters from both pdf files and scanned images, that at first I could not believe that it worked. It is also free!

Obtain a copy of Paint Shop Pro (PSP). I use version 4.15 but an evaluation copy of Paint Shop Pro 3.0 may be downloaded from www.jasc.com, and works just as well, although the toolbars are better on V4.15. (Other graphics packages may work with the following procedure, but I have no such experience. Maybe other readers can advise.)

Install PSP, open to full screen size, and minimise. Open Acrobat to full screen size, load the relevant p.c.b. layout page and centralise the layout on the screen. Press the Print Screen key on the keyboard (this sends the screen image to the clipboard). Minimise Acrobat and maximise PSP and make it the active window. Press Ctrl-V (simultaneously), which pastes the clipboard to PSP.

Select the p.c.b. layout, crop and zoom to 10:1. A bit map image in pixels is produced which may be manipulated in all forms. Pixels can be deleted or added as required

by the various tools available, tracks and pads can be removed, or added to make minor additions to the layout, the printout can be re-sized and even specified for placement on the page (which can save valuable acetate). Don't forget to save regularly while editing. My 1280 x 1024 screen gives a resolution in PSP of about 150 pixels/inch which is adequate for good resolution printouts with a manageable number of pixels to edit.

Poorly reproduced magazine layouts are as simple, and the cheapest scanner should be adequate. Open PSP, go to File, Acquire and use the TWAIN interface to scan the magazine copy. Use Lineart, Resolution 200. Then edit the layout as above.

Three additional points for making best p.c.b. production:

1. Mirror the layout before printing on acetate to allow the printed tracks to be in intimate contact with the photosensitive layer when exposing the board.

2. Special ink-jet (sand finish) acetate can produce acceptable masters with ink jet printers, but the cartridge and printer must be perfect. Any missing scan lines will etch hair line track breaks on the final board.

3. For consistent high quality masters a cheap 600 lines-per-inch laser printer is worth the investment.

I also recommend *Paint Shop Pro in Easy Steps* by Stephen Copestake, £8.99. The publisher in UK is Computer Step - tel: 01926 817999.

**Roger Lucas,
via email**

That appears to be very useful info, Roger. Whilst I have not tried it, it seems that the technique should also work with the standard Paint program supplied in the Accessories folder of all Windows-based PCs.

PIC627/8 DEVICES

Dear EPE,

I assume you're aware that the price of the PIC16F84 and 16F84A has recently increased quite dramatically.

Checking Farnell's web site, I found that the 16F627 (and 628) were, by comparison, a bargain. If the price differential is likely to persist (which, I suspect, will be the case), then might it be time to make the cheaper 16F627/8 the entry-level PIC in *EPE*?

However I'm well aware that the additional complexity of these PICs might put beginners off. The 16F84(A) is, at least, fairly simple.

Phil Cadman, via email

The differential is likely to continue and I have experimented with the F627 and found that at its simplest level it can readily be used in place of the F84, with a simple software modification if Port A is to be used as normal I/O:

First, add the equates:

```
CMCON EQU H'1F'
```

Then prior to the initialising commands for the ports etc, make the statement (within Page 0):

```
MOVLW 7  
MOVWF CMCON
```

Port A will then behave in the normal way. You must also ensure that all variables (user registers) start at H'20' or later, not at H'0C' as allowed by the C84 and F84.

Toolkit TK3 software has been upgraded to handle F627/8 and is now on our web site as V1.3. A short article looking at basic F627/8 use and various mods made to TK3 to handle them will be published in the near future. TK3 has also been modified to allow users to add their own specified PICs (14-bit command types) to the list of those it handles.

TK3 AND PIC12C508

Dear EPE,

Here's a handy tip for readers who have built the Toolkit TK3 programmer board and want to program 12C508 or other 12-bit code PICs. TK3 software only programs 14-bit code.

First go to www.ic-prog.com and download the free programmer software and helpfile. Now the hard bit, on the TK3 circuit board you must cut the track between printer connector pin 6 (DA4) and TP4. Then unsolder the ends of resistors R7 and R3 connected to TP3 and lift them off the board. Now connect TP3 to TP4. I also took out the wire link connecting TP6 to IC2c pin 2 (but maybe not needed, try leaving it in first).

Now run the ICPROG programmer you downloaded and under hardware select PROPIC2. ICPROG will treat TK3 like PROPIC2, and can program PICs TK3 software cannot. It's easy to reverse these circuit changes.

Stanley Cartwright, via email

That's useful Stanley, thanks. I have not yet found a situation where I wanted to use a 12C device. Should I ever do so I'll probably upgrade TK3 to cope with it.

DIGITAL MULTIMETER

Dear EPE,

Could you please send me any information you might have on digital multimeters. I am building a multimeter and I heard your magazine did an issue several years ago. I do not have this particular magazine and you not do back issues. Thank you for your support and great magazine.

Meme, via email

We have not done anything on them in many years and cannot offer you any info. However, they are so cheap that it seems hardly worthwhile building one.

But why do you believe we do not sell back issues? We certainly do, as our regular Back Issues pages prove. We also sell back issues on CD-ROMs. Even if we no longer have a back issue containing a particular project, we can provide a photocopy of that article, providing it is less than five years old. See the Back Issues page in this issue for prices.

FED WIZPIC

Dear EPE,

I have been learning PIC assembler over the last few months with a regard to several projects I have been wanting to design/build for years. Last month, I came across Forest Electronic Developments (www.fored.co.uk) who sell a PIC development/simulation system, for Windows, called WIZ-ASM. This product is fantastic value for money, and it has allowed me to move on in leaps-and-bounds.

I now write code and test it (with appropriate simulated hardware) before I get near a programmer or a single "real" component. Fantastic. I rate this product 10/10 for value and usefulness. Well done, FED.

**Geoff Sim,
via email**

Yes, Geoff, we know that FED do good products, and that they are a very helpful company.

VIRUS ZAPPING

Dear EPE,

I have used a virus zapper of the type designed by Andy Flind and published in your March '02 issue, but do not know whether or not it helped a virus infection I had for several weeks in an ear canal last year. I like to keep an open mind on these matters. Antibiotics had not been able to heal this infection.

However, I recently had an identical infection in the same ear canal, and it hurt just the same, too much to ignore! So it happened with this new infection that a highly experimental "brain wave stimulator" I designed and built about 15 years ago forcibly came out of retirement to act as a source of capacitor-discharge spikes for a six-inch diameter coil I hurriedly wound. (Andy Flind's *Moodloop*, Aug '00 - Andy is a good source of information on brainwaves and why you would want to stimulate them.)

I did this because I wanted a Rife-type of "magnetic pulser" and I was in too much discomfort to bother with making a proper one, with a proper frequency feed of squarewave a.c. (as per Aubrey Scoon's *The End to all Disease*, April '01).

I knew from years earlier that my brain wave machine when fed into a one-turn room loop coil could influence the mood of people in the room. I was hoping that the d.c. spikes from it at 16.7Hz when fed into my small coil held close to my ear, would be powerful enough to ease possible weeks of pain such as I had last year. And it worked. The pain was mostly gone within 24 hours and in 48 hours I was a happy man.

Why 16.7Hz? That's the only Rife frequency that any brain wave machine can reach (it's in the "beta" brain wave range). Allegedly (from Rife supporters) that frequency is totally wrong for infections but I was - again - hoping that it would work. It wasn't a forlorn hope, as readers who follow alternative electrotherapy will realize that, while Rife has large numbers of frequencies, one for each ailment, a certain Dr Robert Beck offers a similar coil-type magnetic pulser, but in Beck's case one 4Hz squarewave frequency does the lot!

So now I have just helped myself with a d.c. train of spikes, not a.c., at an "unapproved" frequency!

Which leaves me thinking: many people in the Rife and Beck camps apparently swear that their system is the right one. Therefore one must conclude that the choice of frequency is/isn't important. And when I put my pennyworth in, we also understand that the supply should be a.c./d.c. Yes, they are silly statements, but how can they be refuted? I am not lying, and I am sure that the Rife and Beck supporters are not lying either! Are we mistaken then, as to what really heals us? Could be. I look forward to other readers' opinions.

May I also comment that the *EPE PIC Virus Zapper* carries no health warning and point out that Dr Hulda Clark in her book states "Do not zap if you are pregnant or wearing a pacemaker".

**Stan Hood,
Christchurch, New Zealand,
via email**

Andy Flind replies:

I recently had two really bad colds in quick succession. My original zapper has been loaned to a chap in Scotland, so I knocked up a generator for a zapper output, only this one can do both 2.5kHz and 20kHz. I applied it through adhesive electrodes on my wrists, and manually timed the sessions, not having a PIC programmed for this.

The sore throat cleared up overnight, and on the day after the first treatment I felt a bit thick-headed (no, really!) as they say you sometimes will when you first use a zapper on a problem. Like Stan, I can't say whether I'd have got better anyhow or the zapper did the job, but something fixed my problems.

The first zapper circuit I built was Hulda's original, from her book. It has a truly horrible

output waveform, and ran at about 18kHz if I recall. I used the bipolar 555 in case the rise and fall times of the output were significant, being faster than CMOS types. However, I've since found that the body appears to behave a bit like a capacitor, if the output drive current isn't available it'll slow the rise and fall times significantly. Hulda's design has a 1kΩ resistor in its output, which would be enough to cause the problem.

Frequencies . . . I've used both, and didn't notice any significant difference between them. One commercial supplier now claims that they work by achieving resonance with the target organisms and "bursting" them, but I think there's some confusion with Rife here. They offer a unit which sweeps its output between 10kHz and 100kHz, though if it's swept as fast as their 'scope picture suggests, it misses most of the intermediate ones.

Yes, we should have had warnings.

Andy Flind

PIC INTERRUPTS

Dear EPE,

Referring to Malcolm Wiles' *Using PIC Interrupts* articles (Mar/Apr '02), the RETFIE instruction is by no means the only possible return from an ISR, RETURN and RETLW can also be used but will not set the GIE bit. This proved useful to me on one occasion when I needed to measure the width of an external pulse. The ISR in conjunction with TMR0 measured the pulse width and returned to the main program using a RETURN instruction. The main then tested GIE to be clear indicating a valid reading was available.

Malcolm's Listing 6 highlights the problem of reading a 2-byte value that is continually changing. Here is a solution that does not require interrupts to be disabled. Read and save the high byte, read and save the low byte, re-read the high byte and check if it is the same as the previous read, if not start over again. This translates to the following pic code.

```
LOOP MOVF ISRCH,W
      MOVWF COUNTH
      MOVF ISRCL,W
      MOVWF COUNTL
      MOVF ISRCH,W
      XORWF COUNTH,W
      BTFSF STATUS,Z
      GOTO LOOP
```

Malcolm is correct in respect of Microchip having fixed Murphy's last trick. Here is an extract from the document 31008a.pdf which, as far as I know, does not appear elsewhere:

"When an instruction that clears the GIE bit is executed, any interrupts that were pending for execution in the next cycle are ignored. The CPU will execute a NOP in the cycle immediately following the instruction which clears the GIE bit. The interrupts which were ignored are still pending to be serviced when the GIE bit is set again."

So if you clear GIE and are also counting instruction cycles for a timing critical section, beware! - the CPU may slip in an extra NOP instruction. The moral of this story? Read every Microchip document you can find, and read it very carefully!

Finally, despite a few minor shortcomings an AVR is a programmer's dream when compared to a PIC.

**Peter Hemsley,
via email**

That's useful, Peter, thanks.

AVRs - that's another story. A while ago we tried readers on an Atmel microcontroller design and no-one was significantly interested. Also, despite AVRs periodically being discussed in Readout, there's not a great deal of interest coming in on correspondence. We have therefore concluded that PICs, which do have a good following, are the microcontroller that we should principally support.

PIC, SHIFT REG AND L.C.D.

Dear EPE,

Thanks to John Becker for all his hard work in producing *TK3*. There are many expensive programmers and tutors etc. that fall far short of what *TK3* will do, a confusing minefield for people who wish to start using PICs. How about a comparison feature in *EPE*? I have used *TK3* with John's excellent *PIC Tutorial* text downloaded with the *TK3* software, with a bit of thought most tutorial examples can be run on the *TK3* board. I found ASM easier to pick up this way than Basic.

My own projects are being slowly thought out, worked out and programmed. The splendid *Teach-In* series is helping me with a weather station project, and an inverter project is also under way. Both have small programs that need only a 16F84. I did not want to use (waste) an F87x or buy a serial l.c.d. (too dear for alphanumeric) so I extended a routine for 8-bit shift registers I developed, added some of your l.c.d. bits and ended up with a routine to talk to intelligent l.c.d.s. it only uses three I/O pins and although not optimised, works ok.

I would recommend *TK3*, as a tutor and development tool, excellent value, well done, many thanks. Thanks also to Malcolm Wiles for a very informative and (for me) timely article on interrupts.

**Graham Card,
via email**

Very many thanks for the kind words and software offering - it looks interesting. It's too long to quote in Readout, but I have put the code in the PIC Tricks folder on our FTP site.

Regarding comparison articles - that would be extremely difficult for us to do in a meaningful manner since it would require someone to acquire and learn the various programmers that are available. No-one is realistically ever going to have the time to do this, nor would it be cost-effective in respect of the research and equipment costs. It's a nice idea, and a pity we could not undertake it.

HIGH VOLTAGE GENERATORS

Dear EPE,

I want to build a high voltage generator of sufficient power and voltage to kill rodents. I built something in kit form some years back using a Darlingtion circuit which was used as a car ignition amplifier. Perhaps I could follow the same tack, but what I really want is a unit powered by about 6V to 12V d.c., storing voltage of the maximum that could be generated from this source, but perhaps not exceeding 30kV, until it is delivered through a short circuit that occurs when a rodent treads on a plate (earth) and the voltage discharged from an electrode through the rodent. I envisage something in solid state form.

At present I am using mains voltage for this purpose. It fries the rodents, but each time I have to reset the 6A circuit breaker, and the unit is inconvenient as it cannot be used out of doors. Any idea where I can look for information?

Anthony Bankside, via email

Goodness, Anthony, I dread to think what animal (and human) welfare organisations might think of your extermination practice and intent! I will refrain from comment on this, but if you wish to investigate high voltage generation in a broad sense, the technology used in the Tesla coil generator for the DIY Tesla Lightning of March '01 might be of interest to you. There are also many web sites devoted to Tesla coils - do a search on Tesla via www.google.com. Such voltages aare, of course, highly dangerous.

RUGBY CLOCK


Dear EPE,

I am thinking of decoding the time-signals from Rugby to use in a data logger. Has anybody made a program for a PIC?

Dave, via email

My PIC Time Machine (Nov '97 plus Aug '98) does it. The software's on our FTP site.

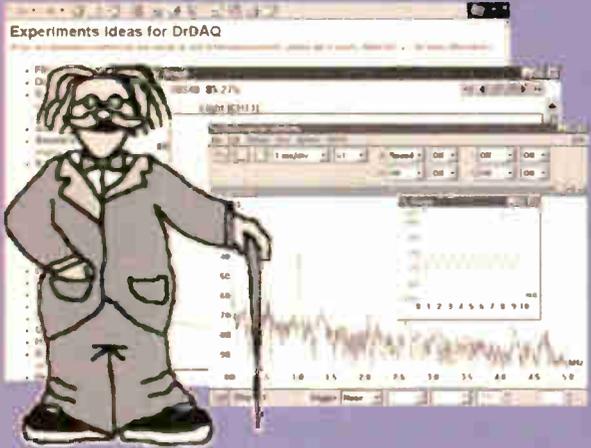Measure pH, Voltage, Humidity, Sound & Light, on your PC!




- ✓ Very low cost
- ✓ Built in sensors for light, sound (level and waveforms) and temperature
- ✓ Use DrDAQ to capture fast signals (eg sound waveforms)
- ✓ Outputs for control experiments
- ✓ Supplied with both PicoScope (oscilloscope) and PicoLog (data logging) software

Only £59!
+ VAT

The DrDAQ is a low cost data logger from Pico Technology. It is supplied ready to use with all cables, software and example science experiments.

DrDAQ represents a breakthrough in data logging. Simply plug DrDAQ into any Windows PC, run the supplied software and you are ready to collect and display data. DrDAQ draws its power from the parallel port, so no batteries or power supplies are required.

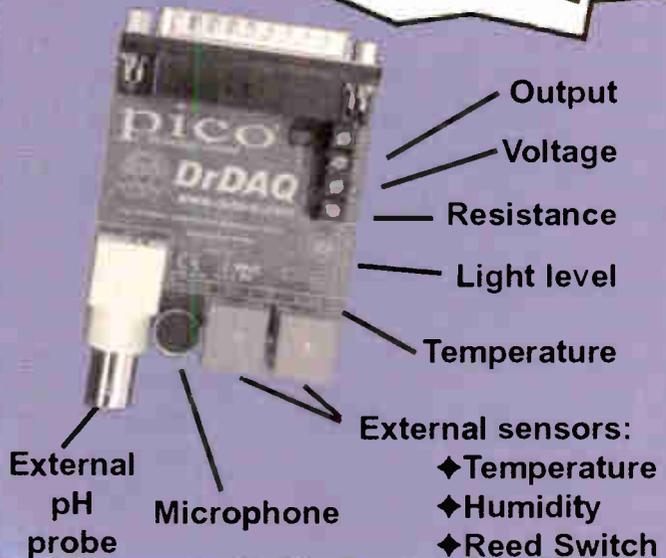As well as the built in sensors, DrDAQ has two sockets for external sensors. When a sensor is plugged in, the software detects it and automatically scales readings. For example, if a temperature sensor is plugged in, readings are displayed in °C. Details are provided to allow users to develop their own sensors.



To order the DrDAQ please choose one of the following options:

- i) Visit our web site and place an order over the Internet,
- ii) Place an order over the phone by ringing the number below, or,
- iii) Fill out the order form and either fax it, or post it back to Pico Technology.

DrDAQ Order Form:

Quantity	Package	Price inc VAT	Total
	DrDAQ + Software	£69.32	
	DrDAQ + 2 Temp Sensors	£92.85	
	DrDAQ + 2 Temp, pH Electrode, Humidity + Reed Switch Sensors	£175.08	
	Delivery	£4.11	£4.11
Grand Total		£	

Name			
Address			
Post code			
Phone			
Credit Card	<input type="checkbox"/> Visa / Mastercard / Switch / Amex		
Card Number			
Expiry Date	/	Start Date & or Issue No.	
Cheque with order	<input type="checkbox"/>		

Pico Technology Ltd, The Mill House, Cambridge Street, St Neots, Cambridgeshire. PE19 1QB
Tel: 01480 396395, Fax: 01480 396296, E-mail: post@picotech.com, Web: www.drdaq.com

World Radio History

A Data Logging Breakthrough

PICO
Technology Limited

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

We can supply back issues of *EPE* by post, most issues from the past three years are available. An *EPE* index for the last five years is also available – see order form. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photocopy of any *one* article (or *one* part of a series) can be purchased for the same price. Issues from Jan. 2002 onwards are also available to download from www.epemag.com.

DID YOU MISS THESE?

MAR '01

PROJECTS • Doorbell Extender • Body Detector • DIY Tesla Lightning • Circuit Tester
FEATURES • Understanding Inductors • The Schmitt Trigger-Part 5 • Circuit Surgery • Interface • New Technology Update • Net Work – The Internet Page.

APRIL '01

PROJECTS • Wave Sound Effect • Intruder Alarm Control Panel-Part 1 • Sound Trigger • EPE Snug-Bug Pet Heating Control Centre.
FEATURES • The Schmitt Trigger-Part 6 • Practically Speaking • Ingenuity Unlimited • Circuit Surgery • Net Work – The Internet Page • **FREE** supplement – An End To All Disease.



MAY '01

Photostats only

PROJECTS • Camcorder Mixer • PIC Graphics L.C.D. Scope • D.C. Motor Controller • Intruder Alarm Control Panel-Part 2.
FEATURES • The Schmitt Trigger-Part 7 • Interface • Circuit Surgery • Ingenuity Unlimited • New Technology Update • Net Work – The Internet Page.

JUNE '01

PROJECTS • Hosepipe Controller • In-Circuit Ohmmeter • Dummy PIR Detector • Magfield Monitor.
FEATURES • Controlling Jodrell Bank • PIC1687x Extended Memory Use • Practically Speaking • Ingenuity Unlimited • New Technology Update • Circuit Surgery • Net Work – The Internet Page.

JULY '01

PROJECTS • Stereo/Surround Sound Amplifier • PIC to Printer Interface • Perpetual Projects 1 – Solar-Powered Power Supply and Voltage Regulator • MSF Signal Repeater and Indicator.
FEATURES • The World of PLCs • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Net Work – The Internet Page.

AUG '01

PROJECTS • Digitimer • Lead-Acid Battery Charger • Compact Shortwave Loop Aerial • Perpetual Projects 2 – L.E.D. Flasher – Double Door-Buzzer.
FEATURES • Controlling Power Generation • Ingenuity Unlimited • Interface • Circuit Surgery • New Technology Update • Net Work – The Internet Page.

SEPT '01

PROJECTS • Water Monitor • L.E.D. Super Torches • Synchronous Clock Driver • Perpetual Projects 3 – Loop Burglar Alarm – Touch-Switch Door-Light – Solar-Powered Rain Alarm.
FEATURES • Controlling Flight • Ingenuity Unlimited • Practically Speaking • Circuit Surgery • New Technology Update • Net Work – The Internet Page.

OCT '01

Photostats only

PROJECTS • PIC Toolkit Mk3 • Camcorder Power Supply • 2-Valve SW Receiver • Perpetual Projects 4 – Gate Sentinel – Bird Scarer – In-Out Register.
FEATURES • Traffic Control • Ingenuity Unlimited • New Technology Update • Circuit Surgery • Interface • Net Work – The Internet Page • **Free** 2 CD-ROMs – Microchip 2001 Tech Library.



NOV '01

PROJECTS • Capacitance Meter • Pitch Switch • Lights Needed Alert • Teach-In 2002 Power Supply.
FEATURES • Teach-In 2002 – Part 1 • Practically Speaking • Circuit Surgery • New Technology Update • Ingenuity Unlimited • Net Work – The Internet Page • **Free** 16-page Supplement – PIC Toolkit TK3 For Windows

DEC '01

PROJECTS • Ghost Buster • PIC Polywhatsit • Twinkling Lights • Mains Failure Alarm.
FEATURES • Teach-In 2002 – Part 2 • Marconi – The Father of Radio • Interface • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Net Work – The Internet Page • 2001 Annual Index.

JAN '02

PROJECTS • PIC Magick Musick • Time Delay Touch Switch • Versatile Bench Power Supply • Forever Flasher.
FEATURES • Teach-In 2002 – Part 3 • Practically Speaking • Ingenuity Unlimited • New Technology Update • Circuit Surgery • Net Work – The Internet Page.

FEB '02

PROJECTS • PIC Spectrum Analyser • Guitar Practice Amp • HT Power Supply • Versatile Current Monitor.
FEATURES • Teach-In 2002 – Part 4 • Ingenuity Unlimited • Russian Space Shuttle Revisited • Circuit Surgery • Interface • New Technology Update • Net Work – The Internet Page.

MAR '02

PROJECTS • MK484 Shortwave Radio • PIC Virus Zapper • RH Meter • PIC Mini-Enigma.
FEATURES • Teach-In 2002 – Part 5 • Ingenuity Unlimited • Programming PIC Interrupts-1 • Circuit Surgery • Practically Speaking • New Technology Update • Net Work – The Internet Page.

APR '02

PROJECTS • Electric Guitar Tuner • PIC Controlled Intruder Alarm • Solar Charge and Go • Manual Stepper Motor Controller.
FEATURES • Teach-In 2002 – Part 6 • Interface • Programming PIC Interrupts-2 • Circuit Surgery • Ingenuity Unlimited • New Technology Update • Net Work – The Internet Page • **FREE** Giant Op.Amp Data Chart.



MAY '02

PROJECTS • PIC Big-Digit Display • Simple Audio Circuits – 1 • Freezer Alarm • Washing Ready Indicator.
FEATURES • Teach-In 2002 – Part 7 • Ingenuity Unlimited • Practically Speaking • New Technology Update • Circuit Surgery • Net Work – The Internet Page.

JUNE '02

PROJECTS • Biopic Heartbeat Monitor • Frequency Standard Generator • Simple Audio Circuits – 2 • World Lamp.
FEATURES • Teach-In 2002 – Part 8 • Interface • New Technology Update • Circuit Surgery • Ingenuity Unlimited • Net Work – The Internet Page.

BACK ISSUES ONLY £3.30 each inc. UK p&p.
Overseas prices £3.80 each surface mail, £5.25 each airmail.

We can also supply issues from earlier years: 1998 (except Jan. to May, July, Nov., Dec.), 1999, 2000 (except Feb., July), 2001 (except May, Oct.). Where we do not have an issue a photocopy of any *one* article or *one* part of a series can be provided at the same price.

ORDER FORM – BACK ISSUES – PHOTOCOPIES– INDEXES

- Send back issues dated
- Send photocopies of (article title and issue date)
- Send copies of last five years indexes (£3.30 for five inc. p&p – Overseas £3.80 surface, £5.25 airmail)

Name

Address

.....Tel:

I enclose cheque/P.O./bank draft to the value of £

Please charge my Visa/Mastercard/Amex/Diners Club/Switch £ Switch Issue No.

Card No. Card Expiry Date

SEND TO: Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.
Tel: 01202 873872. Fax: 01202 874562.


E-mail: croers@epemag.wimborne.co.uk On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm

Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.


M07/02

STORE YOUR BACK ISSUES ON MINI CD-ROMS

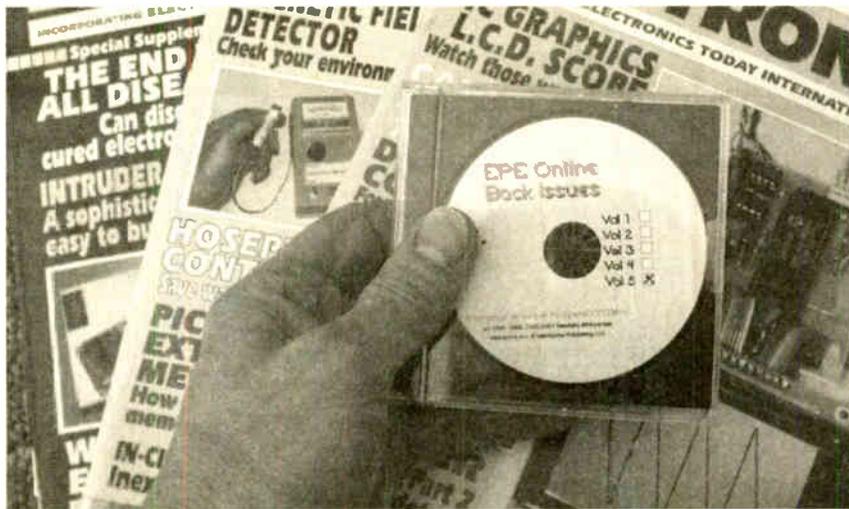

**VOL 6
NOW AVAILABLE**

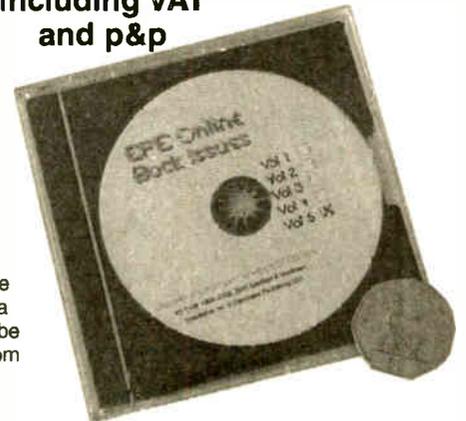**ONLY
£12.45 each**
including VAT
and p&p



A great way to buy *EPE* Back Issues – our mini CD-ROMs contain back issues from our *EPE Online* website plus bonus articles, all the relevant PIC software and web links. Note: no free gifts are included. All this for just £12.45 each including postage and packing.

VOL 1 CONTENTS

BACK ISSUES – November 1998 to June 1999 (all the projects, features, news, IUs etc. from all eight issues). Note: No advertisements are included. **PIC PROJECT CODES** – All the available codes for the PIC based projects published in these issues.

VOL 2 CONTENTS

BACK ISSUES – July 1999 to December 1999 (all the projects, features, news, IUs, etc. from all six issues). Note: No advertisements are included. **PIC PROJECT CODES** – All the available codes for the PIC-based projects published in these issues.

VOL 3 CONTENTS

BACK ISSUES – January 2000 to June 2000 (all the projects, features, news, IUs, etc. from all six issues). **PIC PROJECT CODES** – All the available codes for the PIC-based projects published in these issues.

VOL 4 CONTENTS

BACK ISSUES – July 2000 to Dec. 2000 (all the projects, features, news, IUs etc. from all six issues). **PROJECT CODES** – All the available codes for the programmable projects in these issues.

VOL 5 CONTENTS

BACK ISSUES – January 2001 to June 2001 (all the projects, features, news, IUs etc. from all six issues). **PROJECT CODES** – All the available codes for the programmable projects in these issues, including those for *Interface*.

VOL 6 CONTENTS

BACK ISSUES – July 2001 to December 2001 (all the projects, features, news, IUs etc. from all six issues). **PROJECT CODES** – All the available codes for the programmable projects in these issues, including those for *Interface*.

EXTRA ARTICLES – ON ALL VOLUMES

BASIC SOLDERING GUIDE – Alan Winstanley's internationally acclaimed fully illustrated guide. **UNDERSTANDING PASSIVE COMPONENTS** – Introduction to the basic principles of passive components. **HOW TO USE INTELLIGENT L.C.D.s**, By Julyan Ilett – An utterly practical guide to interfacing and programming intelligent liquid crystal display modules. **PhyzyB COMPUTERS BONUS ARTICLE 1** – Signed and Unsigned Binary Numbers. By Clive "Max" Maxfield and Alvin Brown. **PhyzyB COMPUTERS BONUS ARTICLE 2** – Creating an Event Counter. By Clive "Max" Maxfield and Alvin Brown. **INTERGRAPH COMPUTER SYSTEMS 3D GRAPHICS** – A chapter from Intergraph's book that explains computer graphics technology in an interesting and understandable way with full colour graphics.

EXTRA ARTICLE ON VOL 1 & 2

THE LIFE & WORKS OF KONRAD ZUSE – a brilliant pioneer in the evolution of computers. A bonus article on his life and work written by his eldest son, including many previously unpublished photographs.

NOTE: These mini CD-ROMs are suitable for use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader (available free from the Internet – www.adobe.com/acrobat)

Order on-line from
www.epemag.wimborne.co.uk/shopdoor.htm
or www.epemag.com (USA \$ prices)
or by phone, Fax, E-mail or Post

BACK ISSUES MINI CD-ROM ORDER FORM

Please send me (quantity) BACK ISSUES CD-ROM VOL 1
Please send me (quantity) BACK ISSUES CD-ROM VOL 2
Please send me (quantity) BACK ISSUES CD-ROM VOL 3
Please send me (quantity) BACK ISSUES CD-ROM VOL 3
Please send me (quantity) BACK ISSUES CD-ROM VOL 5
Please send me (quantity) BACK ISSUES CD-ROM VOL 6

Price £12.45 each – includes postage to anywhere in the world.

Name

Address

.....

Post Code

I enclose cheque/P.O./bank draft to the value of £

Please charge my Visa/Mastercard/Amex/
Diners Club/Switch

£

Card No.

Expiry Date Switch Issue No.

SEND TO: **Everyday Practical Electronics,
Wimborne Publishing Ltd.,**

408 Wimborne Road East, Ferndown, Dorset BH22 9ND.

Tel: 01202 873872. Fax: 01202 874562.

E-mail: orders@epemag.wimborne.co.uk

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

SIMPLE AUDIO CIRCUITS



Part 3 – Power Supplies, Loudspeakers, Crossover Networks and Filters

RAYMOND HAIGH

A selection of "pic-n-mix" low-cost audio circuits – from preamplifier to speaker!

If a modest output from one of the smaller power amplifiers (May '02) is all that is required, dry batteries represent a suitable power supply. However, when the output is expected to exceed the half-watt level for sustained periods, a mains power unit is more appropriate. Savings in the cost of batteries will quickly cover expenditure on components.

Compromises, inherent in the design of loudspeakers, give rise to limitations which are normally overcome by the use of two or more units and a crossover.

Power supplies, loudspeakers and associated networks are the topics to be covered this month.

SUPPLY REGULATION

A simple mains power supply comprising a full-wave rectifier and capacitor input filter will deliver an off-load voltage of around 1.4 times the transformer secondary voltage.

With a secondary rated at 12V a.c., the off-load d.c. output voltage will, therefore,

be almost 17V. If the power supply output is close to the maximum safe operating voltage of the amplifier i.c., there is a danger that, under no-signal conditions, the device will be ruined.

When fully loaded, the d.c. output voltage will fall to around 14V with an adequately rated transformer; lower when the transformer specification has been skimped. Voltage will, therefore, be low at the very moments when the power amplifier is being called upon to deliver a high output.

These voltage variations are a cause of distortion and impair the performance of the power amplifier. Moreover, when high-gain preamplifiers or radio tuners are fed from the same supply, the variations can also result in instability, even when substantial decoupling is provided.

POWER SUPPLY

These problems can be avoided by regulating the output of the power supply, and a versatile circuit, which can be adapted

for single or stereo pairs of any of the amplifiers described in Part 1 (May '02), is given in Fig.1. The mains voltage is stepped down by transformer T1, and a full-wave bridge rectifier arrangement, D1 to D4, produces the d.c. output. Reservoir capacitor C5 reduces supply ripple.

Voltage regulators IC1 and IC2 virtually eliminate any voltage swings caused by load variations. The regulators also remove any residual 100Hz ripple on the supply voltage rails and permit the use of a lower value reservoir capacitor (C5). Low level electrical noise, extending into the r.f. spectrum, is present in the output of the i.c.s, and bypass capacitors, C6, C7, C8 and C9, shunt this to the 0V rail.

The voltages required by amplifiers, preamplifiers and auxiliary equipment are often different, and provision is made for two regulated outputs. Alternatively, each output can supply a separate channel of a stereo system in order to double the current rating.

The switching action of the rectifier diodes (D1 to D4) modulates any r.f. (radio frequencies) present in the mains input. This modulated r.f. can be picked up by radio receivers connected to the supply and it manifests itself as a 100Hz hum which only appears when a station is tuned in. Capacitors C1 to C4, connected across the diodes, suppress this interference, which is known as modulation hum. If radio tuners are to be powered from this circuit, these capacitors must be fitted.


COMPONENT RATINGS

Fuse

It is good practice to protect the equipment with an internal fuse of the lowest possible rating. Because of the nature of the load, this should be of the anti-surge or slow-blow type, and a component rated at one amp (1A) would be suitable for power supplies serving the amplifiers described in this series of articles.

Transformer

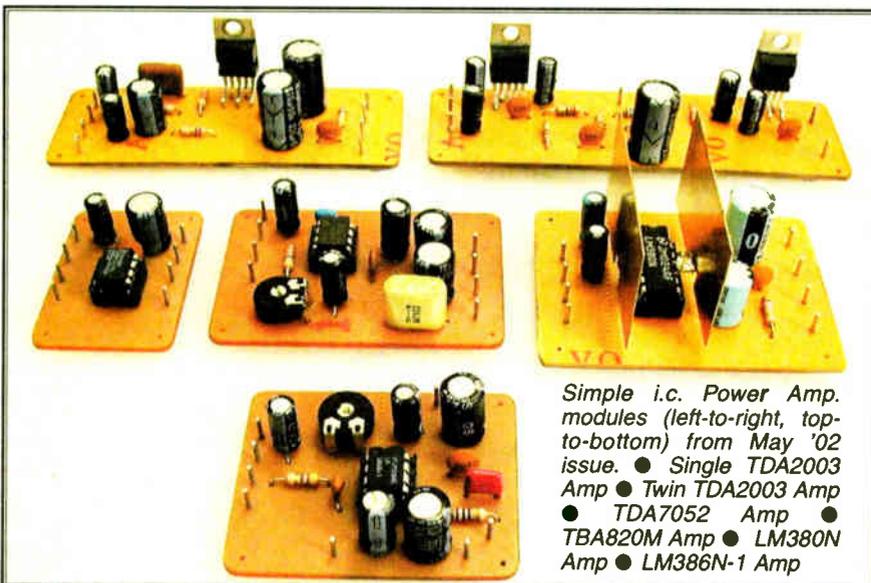The rectified d.c. voltage across the reservoir capacitor (C5) must be at least 3V more than the regulator output when



Simple i.c. Power Amp. modules (left-to-right, top-to-bottom) from May '02 issue. ● Single TDA2003 Amp ● Twin TDA2003 Amp ● TDA7052 Amp ● TBA820M Amp ● LM380N Amp ● LM386N-1 Amp

maximum current is being drawn from the supply. Further, the maximum input voltage to the regulator i.c., which is usually 35V for devices with a 2A rating, *must not* be exceeded. It is also desirable for the voltage drop across it to be no more than 10V or so, or power dissipation within the chip will be increased and more elaborate heatsinking will be required.

These requirements can best be met if the mains transformer secondary voltage is 3V more than the regulated d.c. output.

To determine the required current rating of the secondary winding, add together the demands of the amplifiers and ancillary equipment to be connected to the power supply, and increase this by at least 25 per cent to allow for the reactive load presented by the reservoir capacitor (C5). The current requirements of the power amplifiers were given in Part 1. For convenience, they are repeated here in Table 2.

Manufacturers usually indicate the current delivering capacity of their mains transformers by quoting a VA rating. This is, of course, the secondary output voltage multiplied by the maximum current which the transformer can supply.

In Europe, mains transformers often have two 115V primary windings and two identical secondary windings. The primary windings must be series or parallel connected to suit the local supply voltage, and the secondary connected to deliver the desired output. Parallel connecting the secondary will, of course, double the current available. *Connect the windings in phase or the transformer will be short circuited.*

Rectifiers

With a capacitor input filter, the rectifiers (D1 to D4) must have a p.i.v. (peak inverse voltage) rating at least three times the secondary voltage of the mains transformer. Their current rating should be at least 50 per cent greater than the maximum load on the power supply.

Reservoir Capacitor

The value of the reservoir capacitor, in microfarads (μF), should be at least 2500 times the maximum load current in amps when the supply is regulated, and double this value when unregulated. The working voltage should be at least double the secondary voltage of the mains transformer.

Regulators

The current rating of the voltage regulators (IC1 and IC2) must, of course, be equal to or greater than the maximum current demand on the power supply. The maximum input voltage rating (usually 30V to 35V) must be at least 1.5 times the secondary voltage of the mains transformer.

Regulator i.c.s are available in a range of output voltages suitable for the audio amplifiers (May'02) and preamplifiers (June'02) described in this

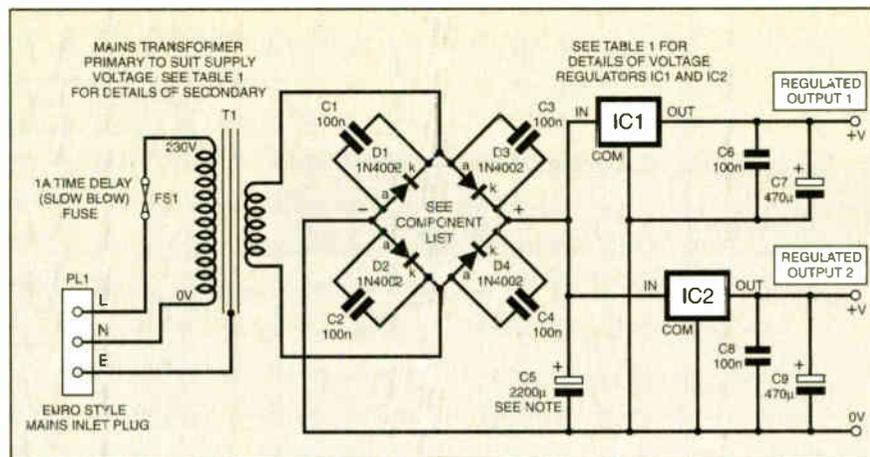



Fig. 1. Circuit diagram for a Dual Output Regulated Power Supply.

Table 1: Component Ratings

Regulated Output V d.c.	Transformer Sec. V r.m.s.	Regulator I.C. (1A max output)	C5 Working Voltage
6	9	L7806	25
9	12	L7809	25
12	15	L7812	35
15	18	L7815	35

NOTES:

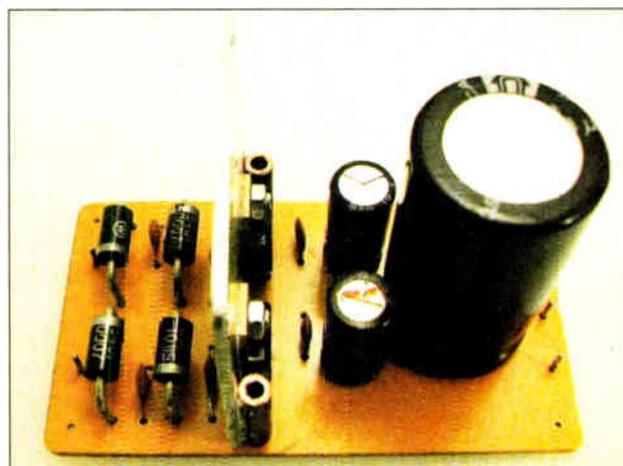- (1) To determine the transformer current rating, add together the current demands of pre and power amplifiers and any ancillary equipment, then increase the total by at least 25% to allow for the reactive load presented by C5.
- (2) A bridge-connected pair of TDA2003 i.c.s with a 4 ohm load will draw 1.7A from a 15V supply and the ratings of the rectifiers, regulator and reservoir capacitor must be increased. Use 1N5401 rectifiers, an L78S15 regulator and a 4700 μF capacitor for C5 (35V working).
- (3) For two, bridge-connected pairs of TDA2003 i.c.s in a stereo combination, fit a 10000 μF (or two 4700 μF) 35V reservoir capacitor, two L78S15 regulators, (one for each stereo channel) and use P600D rectifiers.



Completed power supply board.

Table 2: Power Amplifier Current Requirements

Power Amp I.C.	Speaker Imp Ohms	Supply volts V d.c.	Current drain A	Power output W
LM386N-1	4	6	0.13	0.32
LM386N-1	8	9	0.12	0.56
TDA7052	4	6	0.42	0.78
TDA7052	8	9	0.39	1
TBA820M	4	9	0.23	0.98
TBA820M	8	12	0.17	1.1
LM380N	4	12	0.23	1.12
LM380N	8	15	0.19	1.32
TDA2003	4	15	0.5	3.92
TDA2003	8	15	0.27	2.1
TDA2003 x 2	4	15	1.7	12.5
TDA2003 x 2	8	15	0.96	8.2

Current drain and power output measured just before the onset of clipping.

series. Maximum current ratings are 5A for 12V and 3A for 15V units, but chips rated at more than 2A can be difficult to obtain. When the current demand exceeds 2A; e.g. when two, bridge-connected, pairs of TDA2003 audio power amplifier modules are used in a stereo combination, fit a 2A regulator to each output of the power supply and use one for each stereo channel.

Suppressor Capacitors

The working voltage of capacitors C1 to C4, connected across the rectifier diodes, should be at least four times the secondary voltage of the mains transformer. Bypass capacitors C6, C7, C8 and C9, should have a working voltage at least 1.5 times the transformer secondary voltage to protect them in the event of regulator failure.

DUAL OUTPUT REGULATED POWER SUPPLY

COMPONENTS

POWER SUPPLY

Capacitors

- C1 to C4 100n ceramic, 100V (4 off)
- C5 2200 μ radial elect. (see Table 1)
- C6, C8 100n ceramic, 50V (2 off)
- C7, C9 470 μ radial elect. 50V (2 off)

See
**SHOP
TALK**
page

Semiconductors

- D1 to D4 1N4002 rect. diode for 1A max. output (4 off)
- 1N5401 rect. diode for 3A max. output (4 off)
- P60D rect. diode for 4A max. output, limited by regulators (4 off)
- IC1, IC2 78 series for 1A; 78S series for 2A maximum output. See Table 1 (2 off)

Miscellaneous

- T1 mains transformer – see text and Table 1
- FS1 1A 20mm slow-blow fuse to suit holder
- PL1 Euro fused mains inlet, chassis mounting, plug with line socket

Printed circuit board available from the EPE PCB Service, code 356 (PSU); metal case, size and type to choice; multistrand connecting wire; mains cable; aluminium sheet or proprietary heatsink and heatsink compound; solder pins; nuts, bolts and washers; stand-off pillars (4 off); solder etc.

Approx. Cost
Guidance Only

£20
excluding case

CONSTRUCTION

Any readers who have no experience of building or commissioning mains-powered equipment are reminded that the voltages involved can kill! Anyone who feels unsure of his or her ability to complete a project of this kind **MUST** seek help and guidance from an experienced constructor.

The small components are assembled on the printed circuit board (p.c.b.) as illustrated in Fig.2, together with a full-size copper foil master and the interwiring to off-board components. This board is available from the *EPE PCB Service*, code 356.

Commence construction by first soldering in position on the p.c.b. the rectifier diodes and non-electrolytic capacitors. This can be

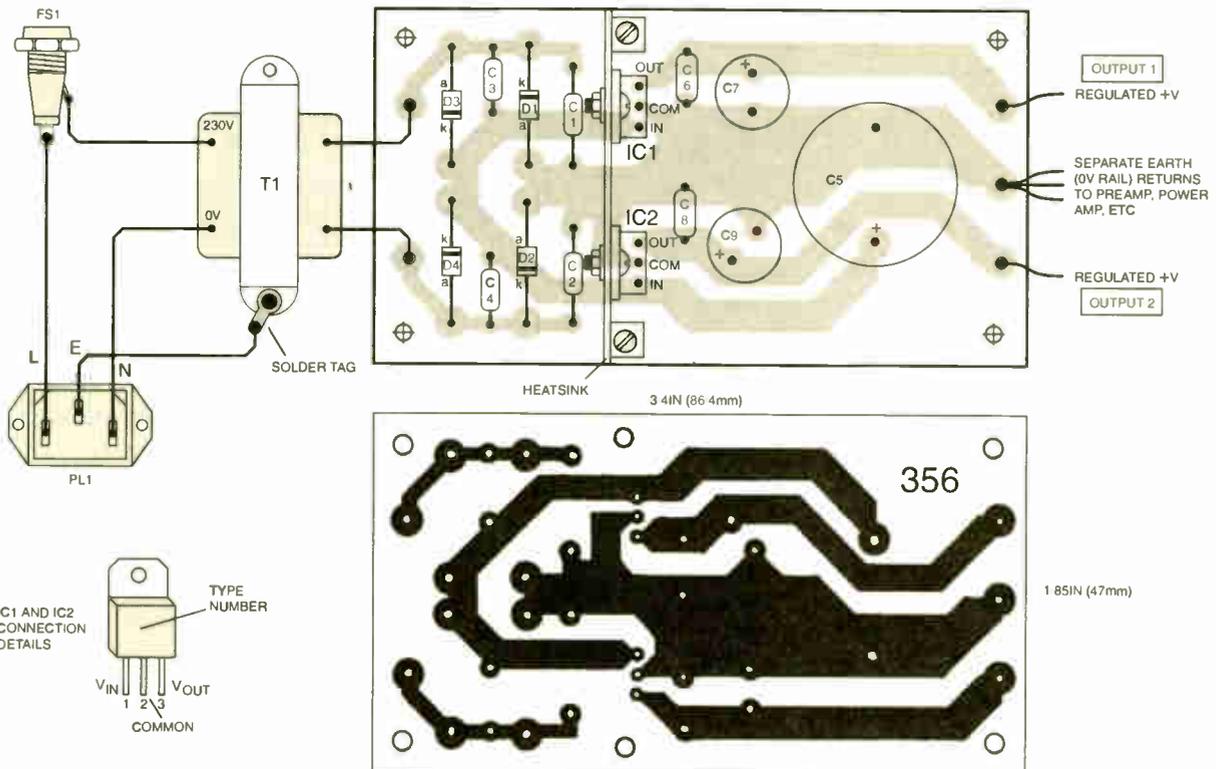
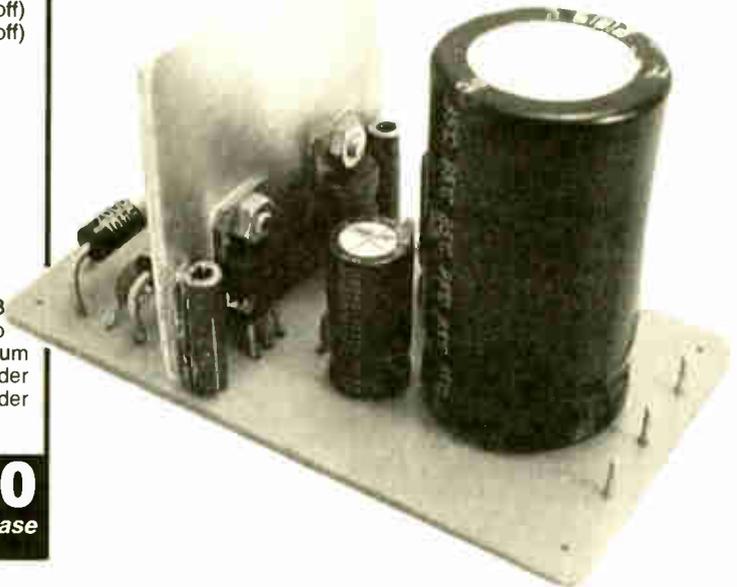


Fig.2. Power Supply printed circuit board, full-size copper master and suggested mains transformer and separate panel fuseholder interwiring. The 16 s.w.g. aluminium heatsink measures 45mm x 45mm.

LOUDSPEAKERS

followed by the larger electrolytic types and the voltage regulators IC1 and IC2. Finally, you will need to bolt a heatsink to the regulators and details of choosing a suitable heatsink will be given shortly. Solder pins, inserted at the lead-out points, simplify the task of off-board wiring.

Diodes D1 to D4, the reservoir capacitor, C5, and the regulators, IC1 and IC2, have to be chosen to suit the voltage and current to be delivered by the power supply. The requirements are summarised in Table 1 and the associated notes. Details of the modest current needs of the various preamplifiers were given in Part 2 of the series, and the current demands of the power amplifiers are scheduled in Table 2.

Dimensions and fixing arrangements for mains transformers vary and this heavy component should be mounted directly into or on the metal equipment case bottom or chassis panel. A Euro-style mains inlet plug, with a built-in fuseholder for FS1, is strongly recommended. You can, of course, use a separate panel-mounting fuseholder if you wish, see Fig.2.

Mains Earth should be connected to any metal case and to the core and cladding of the transformer. (A solder tag bolted under one of the mains transformer mounting lugs makes a good earthing point for the mains Earth lead.)

Interwiring details to off-board components are also shown in Fig.2. Leads connecting the mains transformer to the inlet plug and the p.c.b., and any mains switch wiring, should be tightly twisted to minimise external fields. Keep the transformer at least 150mm (6in.) away from signal input wiring.

Toroidal transformers have a smaller external field than units with conventional cores. They are the component of choice when the equipment is particularly compact and/or high gain preamplifiers are used.

HEATSINKING

Unless the current drain is to be very low (say 20mA or less), the regulator i.c.s must be bolted to a heatsink. The 45mm x 45mm sheet of 16s.w.g. aluminium shown on the drawing (Fig.2) is sufficient for current drains up to 1A when the voltage drop across the regulators is not too extreme.

For larger current loads it is suggested that the heatsink be extended and bolted to the metal case or chassis of the unit to ensure adequate heat transfer. Failure to properly dissipate heat from the regulators will result in the devices shutting down.

COMMISSIONING

Once construction has been completed, check the p.c.b. for poor soldered joints and bridged tracks. Check the orientation of electrolytic capacitors, diodes and regulators.

Make sure that the primary windings of the mains transformer are connected to suit the local supply voltage, and that the secondary windings are connected, in phase, to deliver the correct voltage to the power supply p.c.b. It is a good idea to connect the transformer to the mains and check the secondary voltage with a test meter before linking it to the p.c.b. **Extra care must be taken when carrying out this last task.**

Check the voltage across the reservoir capacitor C5, and that the voltages delivered by regulators (IC1 and IC2) are correct before using the supply to power any equipment.

Loudspeaker (speaker) designers have to make compromises. Sensitivity, good transient and good high frequency response call for a lightweight cone and speech coil assembly. Power handling and an extended low frequency response require a large, strong (and heavy) cone and coil.

For good sensitivity, the magnetic field cutting the voice coil must be intense. Unfortunately, this increases the impedance at the cone's resonant frequency. However, this impedance rise can be controlled by the speaker enclosure, and a powerful magnet is always preferable.

The reproduction of low frequencies involves large cone excursions and the suspension must be highly compliant. High compliance also lowers the cone's resonant frequency, and this extends the speaker's low frequency response. However, the need to maintain control of the position of the voice coil in the magnet gap imposes limits on how free the suspension can be.

Cone movement for a given sound output reduces with increasing speaker size but, as we have seen, greater diaphragm mass impairs transient and high-frequency response.

HORSES FOR COURSES

To avoid performance being excessively degraded by these conflicting requirements, domestic "hi-fi" systems usually combine two or more speakers, each being designed to reproduce part of the audio frequency spectrum.

The low frequency unit, or *bass* speaker, has a comparatively heavy cone and voice coil with a highly compliant suspension. Clever designers have managed to obtain reasonable results with small speakers, but an extended low frequency response and good power handling are more easy to achieve with speakers of 200mm (8in.) or more in diameter.

Mid-range units are sometimes provided when the low frequency speaker is large (300mm to 450mm or 12in. to 18in. diameter). As one would expect, cones are lighter, the compliance is often stiffer, and the chassis can form a sealed enclosure.

High-frequency units, or "*tweeters*", have a very small diaphragm, which is commonly dome shaped to improve sound dispersal. Units of this kind always have sealed backs.

Whilst moving coil tweeters are the preferred option for hi-fi applications, horn-loaded piezoelectric units are often fitted in the high power speaker systems used by musicians. The impedance of these devices rises, and their power consumption falls almost to zero, as the applied frequency is lowered. They do not, therefore, require a "crossover unit", and are easy to connect into multiple speaker systems.

COMMUNICATIONS

Loudspeakers intended primarily for speech reproduction in communications equipment have to perform well over a restricted frequency range, usually around 300Hz to 3000Hz.

Inexpensive speakers of the type manufactured for portable receivers are better suited for this purpose, and, if space is available, a 102mm (4in.) diameter unit is

to be preferred. Clarity will be impaired if low frequencies are allowed to excite the cone of a speaker of this kind, and measures to prevent this were discussed in Part 1 (May '02).

IMPEDANCE


Speech coil impedance is usually measured at around 400Hz. At this frequency, the inductance of the coil has a minimal effect, and its impedance is only one or two ohms more than its d.c. resistance. As frequency rises, the inductance of the speech coil has a growing impact and impedance mounts steadily.

The movement of the speech coil in the magnetic field induces in it a voltage which opposes the signal voltage. At the cone's resonant frequency, very little energy is needed to sustain it in motion, and it vibrates readily, over larger distances, for a comparatively small power input.

These larger cone excursions generate a greater opposing voltage, or back-e.m.f., and speech coil impedance, at resonance, increases by as much as a factor of ten over its nominal value. The more powerful the magnetic field, the more dramatic the rise in impedance.

Impedance peaking at cone resonance (between 30Hz and 100Hz for low frequency speakers), and the gradual rise in impedance with increasing frequency, makes the response of the speaker non-linear. (The power which can be fed to a speaker system falls as its impedance rises). Fortunately, the former can be tamed by good enclosure design, and the latter can be overcome by the use of filter networks and the addition of a tweeter.

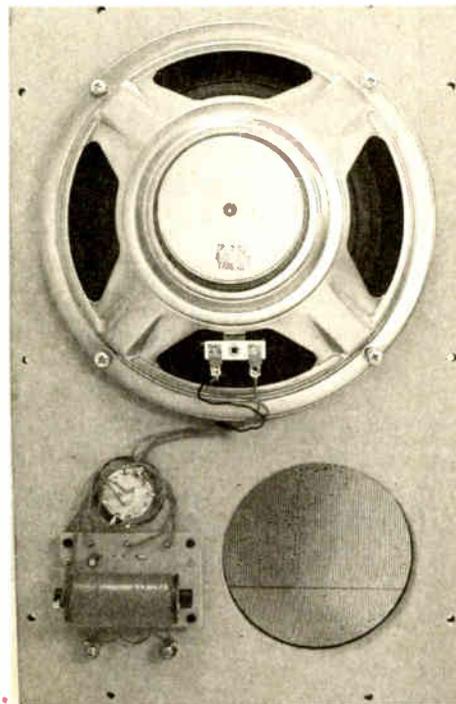Care must always be taken to ensure that the rated impedance of a speaker system is not too low for the power amplifier. Too low an impedance will cause excessive dissipation in the output transistors and, if there is no overload protection circuitry, the power amplifier will be ruined.



Safe supply voltage and speaker impedance combinations for the various i.c. power amplifiers were given in Part 1. They are summarised here in Table 2.

CROSSOVERS

When two or more speakers are used to improve performance, arrangements must be made to allocate the audio spectrum between them.

The resistance presented by capacitors to the flow of alternating current decreases as frequency rises. With inductors, resistance increases with rising frequency. This frequency-dependant opposition to current flow is known as *reactance*.

Capacitors and inductors can be combined in simple networks which utilise this phenomenon to allocate frequency bands to different speakers. Circuits and design data are given in Fig.3 and inductor and capacitor values for common speaker impedances, and a range of crossover frequencies, are set out in Table 3. The reactances of standard value capacitors, at

Table 3: Crossover Network Inductor and Capacitor Values

Crossover frequency Hertz		500	1000	1500	2000	2500	3000	3500	4000	4500
4 ohm Speaker 1st Order Filter	L	1.3	0.63	0.42	0.32	0.25	0.21	0.18	0.16	0.14
	C	80	40	26	20	16	13	11	10	8
4 ohm Speaker 2nd Order Filter	L	1.8	0.9	0.6	0.5	0.35	0.3	0.25	0.22	0.2
	C	56	28	18	14	11	9	8	7	6
8 ohm Speaker 1st Order Filter	L	2.6	1.26	0.84	0.64	0.5	0.42	0.36	0.32	0.28
	C	40	20	13	10	8	6.5	5.5	5	4
8 ohm Speaker 2nd Order Filter	L	3.6	1.8	1.2	1	0.7	0.6	0.5	0.44	0.4
	C	28	14	9	7	6	4.5	4	3.5	3

Inductance values, L, are given in mH (millihenries).

Capacitor values, C, are given in μF (microfarads).


See text for guidance on rounding figures up or down to nearest standard value.

various audio frequencies, were tabulated in Part Two.

FILTER ORDERS

The simple "first order" filters shown in Fig.3a and Fig.3d are perfectly suitable for domestic systems rated at up to 15W.

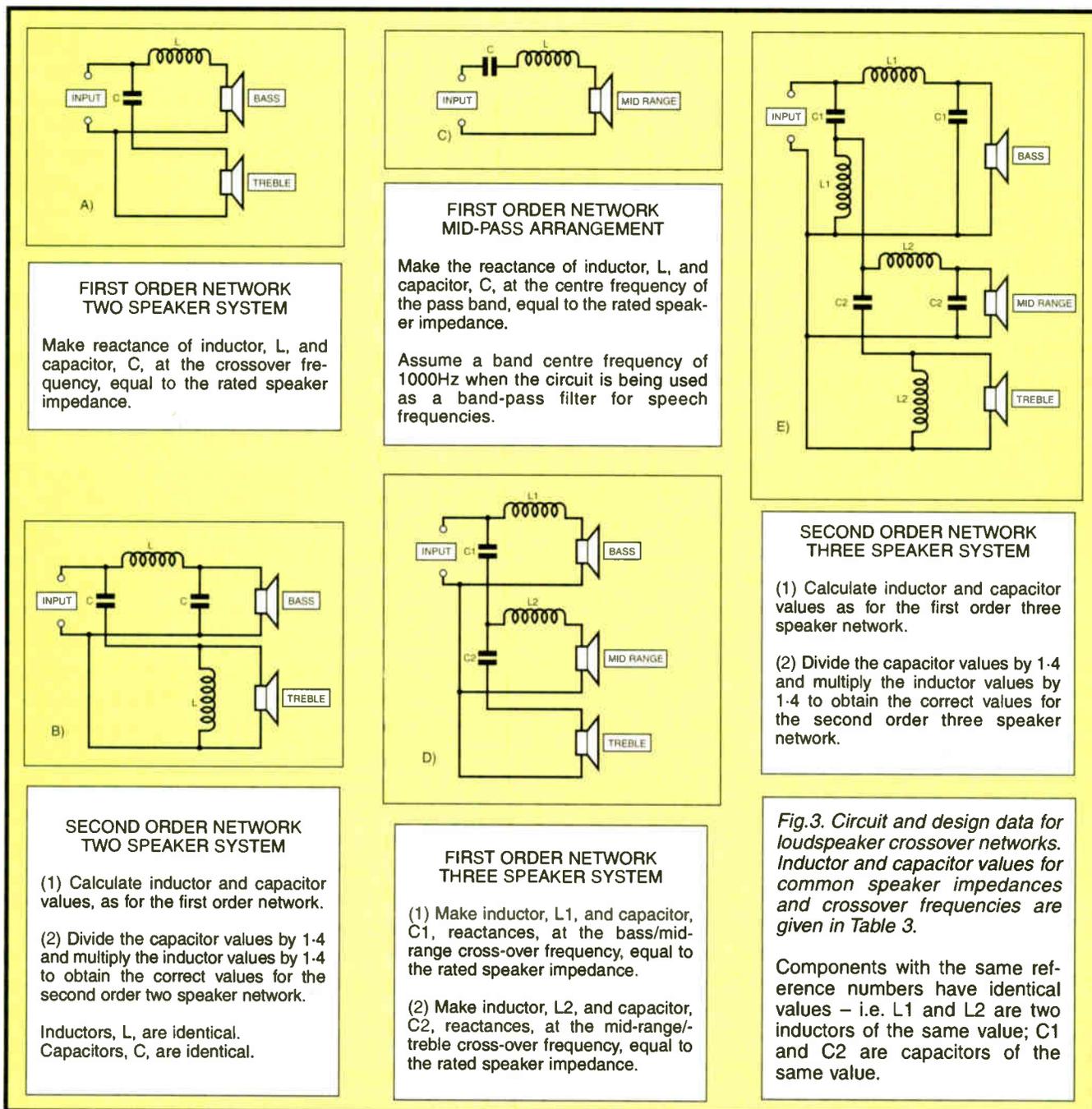Low frequency roll-off above the crossover frequency is 6dB per octave and this may not be sufficient to protect some tweeters when higher powered amplifiers are used. In these cases, the second order filters, shown in Fig.3b and Fig.3e, which produce a 12dB roll-off, are safer options.



CROSSOVER FREQUENCY

With two-speaker systems the crossover frequency is usually between 1kHz and 4.5kHz, and the tweeter manufacturer's recommendations should be followed. If the unit is of uncertain origin, adopt a crossover frequency of around 2.5kHz: this will normally be satisfactory.

When the bass speaker is large (12 inches diameter or more), a crossover at 1kHz or even lower can produce a more even frequency response. Suitable tweeters tend to be rather costly, but an inexpensive alternative will be described later.

THREE SPEAKERS

Another way of ensuring a more even response when a large bass speaker is used is to install a third, mid-range unit. Suitable circuits are given in Fig.3d and Fig.3e.

The bass/mid-range crossover point is usually around 500Hz with open chassis mid-range speakers, and 1000Hz with sealed back units. The mid-range/treble crossover is generally between 4.5kHz and 6kHz. Again, the recommendations of the speaker manufacturer should be followed.

PHASING

Parallel connected bass speakers must be wired in phase to avoid cancellation of the lower audio frequencies. Use a 1.5V dry cell to test for phasing on unmarked speakers by noting the battery positive connection for the outward movement of the cone.

Crossover networks introduce phase shift, but, as frequency increases, phasing becomes less important. Readers can try reversing the connections to mid-range units. However, unless they have a very refined ear, they are not likely to detect any difference.

CROSSOVER COMPONENTS

Inductors

Inductors for home-made crossovers have to be hand wound. The amount of wire, and the resistive losses, can be greatly reduced by winding the coils on short lengths of ferrite aerial rod. Core saturation problems should not arise at the power levels encountered in domestic installations.

Bobbin construction is illustrated in Fig.4. Winding details for the inductor values likely to be encountered are given in Table 4.

The wire should be wound on evenly, and masking tape, applied over each layer, will make the task a little easier. Constructors who have difficulty producing neat windings should increase the diameter of the bobbin ends for the larger inductance coils.

Capacitors

The bipolar electrolytic capacitors used in crossover networks are available in a limited range of values. Capacitors of this kind can be formed by connecting two ordinary electrolytics back-to-back, and this makes possible the production of non-standard values. The details are given in Fig.5. Capacitors rated at 50V working

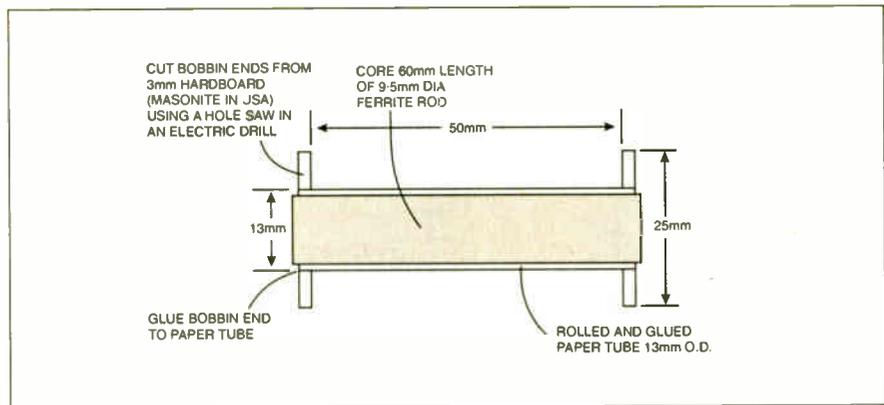


Fig.4. Inductor bobbin construction details.

Table 4: Inductance of Ferrite-cored Coils

Induct mH	0.1	0.2	0.3	0.4	0.5	0.75	1	1.5	2	2.5	3	3.5
No. of turns	45	60	75	90	100	125	150	175	200	225	250	275

Use 20 s.w.g. (19 a.w.g.) enamelled copper wire for coils up to 2mH.

Use 22 s.w.g. (21 a.w.g.) enamelled copper wire for 2.5mH to 3.5mH coils. See illustration for details of bobbin and core.

will be suitable for all of the power amplifiers described in Part 1.

The performance of electrolytic capacitors can become uncertain at high audio frequencies, and the best crossover networks use components with a paper, polyester or polypropylene dielectric.

Tolerances

Variations in the composition of ferrite rod will affect the tabulated inductor values shown in Table 4 by plus or minus 10 per cent or so. Bipolar electrolytics, whether purchased or homemade, have a tolerance, at best, of plus or minus 20 per cent.

Fortunately, loudspeaker crossover networks are very forgiving, and component spreads even greater than this produce no audible difference. When calculated values are being rounded up or down, it is prudent to err on the high side with inductors and on the low side with capacitors.

BANDPASS FILTERS

Mention has already been made of the desirability of restricting the audio bandwidth of speakers used primarily for speech communication. An inductor and capacitor can be combined to produce a bandpass effect, and a typical circuit is given in Fig.3c.

As a starting point, select the inductor and capacitor values for a centre frequency of 1000Hz (1kHz). If a more severe attenuation of frequencies below 300Hz and above 3000Hz (3kHz) is required, reduce the capacitor and increase the inductor value. When using this network with earphones, connect both earpieces in parallel to produce an impedance of 16 ohms, and perform the calculations on this basis.

Although extremely simple, this measure will greatly improve the clarity of speech, especially when signals are overlaid by received or generated noise within the amplifiers.

CROSSOVER UNIT

The circuit diagram for an inexpensive 8ohm Crossover/Filter unit suitable for a multi-purpose workshop speaker is shown

FORMULAE FOR THE REACTANCE OF INDUCTORS AND CAPACITORS

$$X_L = 0.00628 f L \text{ ohms}$$

$$X_C = \frac{159000 \text{ ohms}}{f c}$$

where

f is in Hertz
L is in millihenries (mH)
and C is in microfarads (μF)

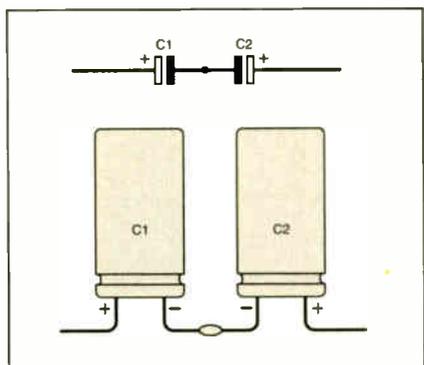


Fig.5. Creating a bipolar electrolytic from two capacitors.

FORMULAE FOR COMBINING CAPACITORS

Two capacitors in series:

$$C_x = \frac{C_1 \times C_2}{C_1 + C_2}$$

Capacitors in parallel:

$$C_x = C_1 + C_2 + C_3 \dots$$

The working voltage of each capacitor should be at least 1.5 times the peak-to-peak signal voltage developed across the loudspeaker at maximum input.

CROSSOVER/AUDIO FILTER

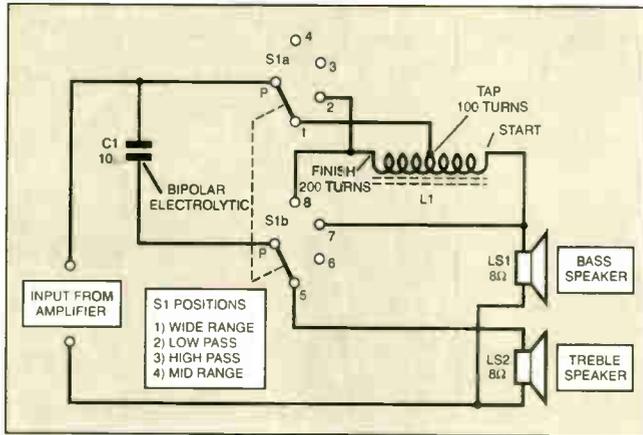


Fig.6. Circuit diagram for the Loudspeaker Crossover/Audio Filter.

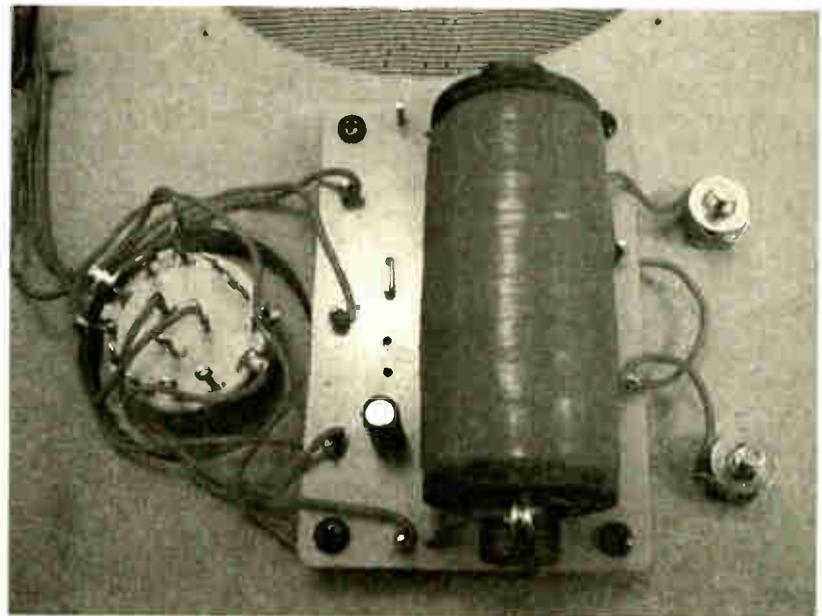
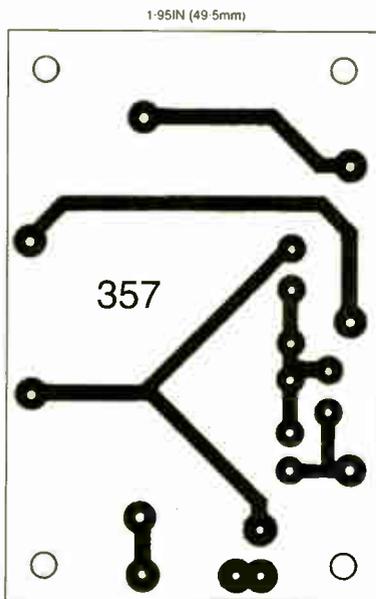
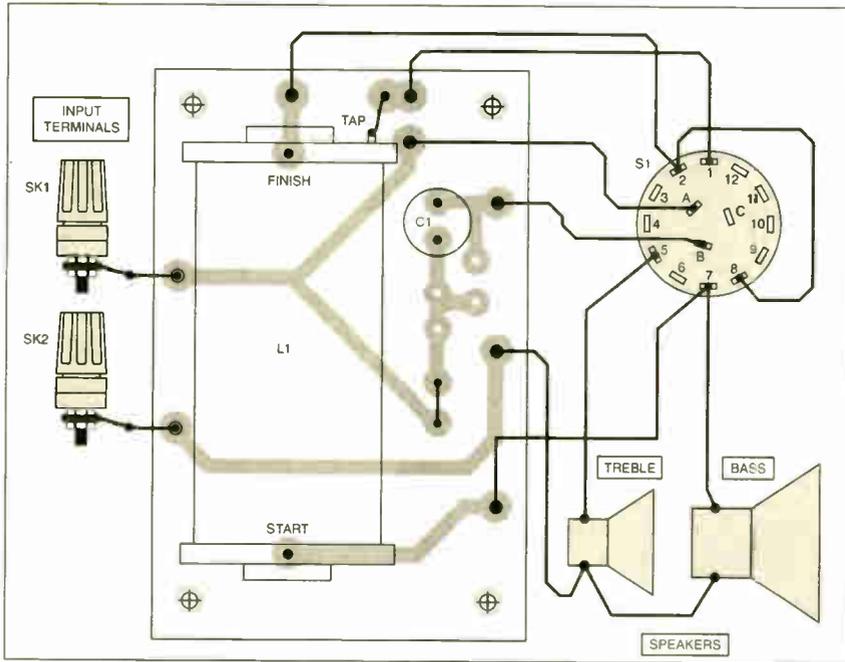


Fig.7. Crossover/Audio Filter printed circuit board component layout, interwiring to off-board components and full-size copper foil master. The completed crossover is shown in the above photograph.

COMPONENTS

CROSSOVER/AUDIO FILTER

Capacitors

- C1 10µ bipolar radial elect. 50V (Alternatively, two 22µ standard elect. connected back-to-back – see text and Fig.5)

Inductor

- L1 9.5mm (3/8in.) dia. ferrite rod, length 63mm (2½in.); card, hardboard and glue for bobbin. Enamelled copper wire: Crossover only – 100 turns 20 s.w.g. (19 a.w.g.), Crossover and Filter – 200 turns 22 s.w.g. (21 a.w.g.). See Fig.4 and text

Miscellaneous

- S1 3-pole 4-way rotary switch (only two poles used)
SK1, SK2 4mm screw terminal post/socket (2 off)

Printed circuit board available from the *EPE PCB Service*, code 357 (Crossover/Filter); multistrand and connecting wire; plastic control knob; speaker terminals; solder pins; solder etc.

Approx. Cost
Guidance Only

£9
excluding speakers

in Fig.6. The first order filter serves as a basic crossover when the speaker is being used for testing or listening to "hi-fi" equipment.

Switching out the Treble speaker and connecting the inductor in series with the Bass speaker gives a low-pass (top cut) effect. Connecting the capacitor in series with the speaker provides a high-pass (bass cut) arrangement. With the inductor and capacitor in series with the speaker, response to speech frequencies is emphasised, making the unit suitable for use with a communications receiver or for surveillance work.

Rotary switch S1 selects the required function, and the inductor is tapped to provide appropriate values for the crossover and speech filter.

CONSTRUCTION


Construction of the Crossover/Filter Unit is based on a small single-sided printed circuit board (p.c.b.). This board is available from the *EPE PCB Service*, code 357.

The topside component layout, full-size copper foil master and off-board wiring details are illustrated in Fig.7. Again, solder pins at the lead-out points will simplify off-board wiring. The p.c.b. makes provision for series and parallel combinations of capacitors, and a wire link must be inserted

if capacitor C1 is a single, bipolar electrolytic.

Constructors interested only in "hi-fi" applications can ignore the switching arrangements and simply connect a 100-turn (0.5mH) inductor and the capacitor as shown in Fig.3a.

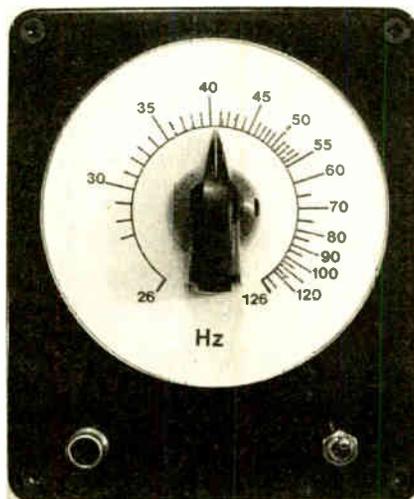
Next Month: The final part will deal with speaker enclosures and include a low-cost, high-performance design



Low Frequency Oscillator for loud-speaker resonance checking.

which incorporates this month's Crossover/Filter unit.

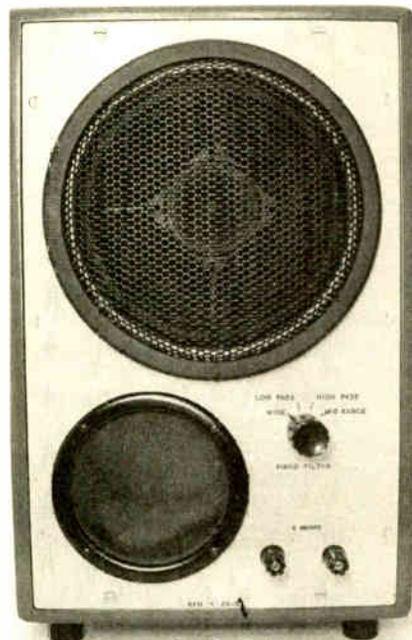The construction of a simple and inexpensive oscillator and resonance detector, which can be used to match any speaker to an enclosure and optimise performance, will also be described.



SHOP TALK

with David Barrington

Infra-Red Autoswitch

As the *Infra-Red Autoswitch* project is mains powered, all the components have been specially selected to fit directly on the small printed circuit board (p.c.b.). If alternative, non-board mounting components, such as the mains transformer and relay, are used you *must* take extra care when building and testing this unit. In this case, it is very important that the p.c.b. and any off-board parts be mounted in its case *before* testing and that a separate *battery* supply is used for checking its operation, prior to mains connection.

The special Sharp IS471F infra-red sensor/detector came from **RS Components** and carries the order code 564-396. They also supplied the p.c.b. mounting, short-circuit proof, mains transformer with twin 9V 0.027A (0.5VA total) secondaries, code 310-1263. These components can be ordered from any *bona-fide* RS stockists, including some of our advertisers. You can order direct (*credit card only*) on ☎ 01536 444079 or on the web at rswww.com. A post and handling charge will be made.

The 12V d.c. low-profile relay, with 12A 250V a.c. rated single-pole changeover contacts, used in the model was purchased from **Rapid Electronics** (☎ 01206 751166 or www.rapid-electronics.co.uk), code 60-4630. We understand that RS (see above) also stock a similar relay, code 198-6933.

The specified low-profile case came from **CPC** (*credit card only*), ☎ 08701 202530, code EN55028. A post and packing charge is made on all orders under £30. The Autoswitch printed circuit board is available from the *EPE PCB Service*, code 358 (see page 539).

Teach-In 2002 - Lab 9

Once again, it's only the sensor and semiconductor devices called for in this month's *Teach-In 2002 Lab Work* that will give some readers sourcing grief. Starting with the Nemoto NAP-7AU gas sensor/compensator pair, these were obtained from **Maplin** (☎ 0870 264 6000 or www.maplin.co.uk), code FM87U and are sold as a pair.

We have found two listings for the precision low off-set op.amp type OP177 and it can be ordered from **Rapid Electronics** (☎ 01206 751166 or www.rapidelectronics.co.uk), code 82-0092, or **RS Components** (☎ 01536 444079 or on the web at rswww.com), code 127-2868. Expect to pay a handling and postage charge.

If readers experience any difficulty in finding a local source for the 4093 quad 2-input NAND Schmitt trigger (Rapid 83-0420) and the ADC0804 8-bit analogue-to-digital chip (Maplin QQ0CA or RS 411-674) they should contact the above mentioned companies. The relevant code numbers are shown in brackets.

The Linear Technology LTC1062CN8 5th order switched capacitor low-pass filter i.c., used in the *Anti-aliasing Filter* (Lab 9.5), appears to be listed only by RS (see above), code 633-880.

EPE Stylopic

A couple of items proved hard to find when tracking down parts for the *EPE StyloPIC* project. The National Semiconductor LM13600 transconductance amplifier i.c. and the SGS-Thompson L272 dual power op.amp i.c. only appear to be listed by RS, codes 304-453 and 635-167 respectively. You can order

them direct from RS (*credit card only*) on ☎ 01536 444079 or on the web at rswww.com. A post and handling charge will be levied.

The above company supplied the Texas TLC7524CN 8-bit digital-to-analogue converter chip, code 650-087. It is also currently listed by **Rapid** (☎ 01206 751166 or www.rapidelectronics.co.uk), code 82-0764, but double check it is the 16-pin device being supplied.

For those readers unable to program their own PICs, a ready-programmed PIC16F877-20 microcontroller can be purchased from **Magenta Electronics** (☎ 01283 565435 or www.magenta2000.co.uk) for the inclusive price of £10 each (overseas add £1 p&p). It is the 20MHz version you require. The software is available on a 3.5-in. PC-compatible disk (*EPE* Disk 5) from the *EPE* Editorial Office for the sum of £3 each (UK), to cover admin costs (for overseas charges see page 539). It is also available *Free* from the *EPE* web site: [ftp://ftp.epemag.wimborne.co.uk/pub/PIC/StyloPIC](http://ftp.epemag.wimborne.co.uk/pub/PIC/StyloPIC).

The printed circuit board/keyboard is available from the *EPE PCB Service*, code 359 (see page 539).

Simple Audio Circuits - 3

Most of our components advertisers should be able to supply all the parts needed to construct the circuits in this month's instalment of the *Simple Audio Circuits*. A suitable Bulgin fused Euro-style mains inlet, chassis mounting, plug (code MK18U or FT37S) together with an insulation, rear tag, protective cover (code JK67X) and line socket (UL16S) is listed by **Maplin** (☎ 0870 264 6000 or www.maplin.co.uk). They also list the 6A 200V P600D rectifier diode for one version of the Power Supply Unit, code UK60Q.

If problems are experienced in obtaining a ferrite rod for the Crossover unit, we understand, from the author, that one is obtainable from **JAB, PO Box 5774, Birmingham, B44 8PJ** (*mail order only*), and **J. Birkett** (☎ 01522 520767). You will need to cut the rod down to size (take care, it is brittle!). These two firms can also supply 50g (2oz) reels of enamelled copper wire for the Crossover.

The two printed circuit boards are available from the *EPE PCB Service*, codes 356 (PSU) and 357 (Crossover) - see page 539.

Rotary Combination Lock

Probably the most expensive item when purchasing components for the *Rotary Combination Lock* project is likely to be the heavy-duty power solenoid. The one in the model cost about £15 and came from **RS** (☎ 01536 444079 or rswww.com) and is their 12V d.c. standard pull action, spring return type, code 250-1303. They also supplied the Omron 12V d.c. ultra-min., p.c.b. mounting relay, code 369-359.

The two printed circuit boards are available from the *EPE PCB Service*, code 260 (Lock) and 361 (Interface).

PLEASE TAKE NOTE

L.E.D. Sequencer (Ingenuity Unlimited) June '02
Page 406. To prevent the i.c. outputs (IC2, IC3) from adversely affecting each other, 1N4148 signal diodes should be inserted between each i.c. pin and the respective i.e.d. The anode on the pin and cathode on the i.e.d.

World Lamp June '02
Where it is said that VR1 should be turned clockwise, this should read anti-clockwise, and where anti-clockwise, clockwise.

Toolkit TK3
Updated files for V1.2 are now on our FTP site. Only files Disk 1 and Disk 3 are affected.



A COMPLETE RANGE OF INVERTERS

150W TO 2500W - 12V & 24V

A Complete range of regulated inverters to power 220V and 240V AC equipment via a car, lorry or boat battery. Due to their high performance (>90%) the inverters generate very little heat. The high stability of the output frequency (+/-1%) makes them equally suitable to power sensitive devices.

These inverters generate a modified sine wave, which are considerably superior to the square waves which are produced by most other inverters. Due to this superior feature they are capable of powering electrical equipment such as TV's, videos, desktop & notepad computers, microwave ovens, electrical lamps, pumps, battery chargers, etc.

Low Battery Alarm

The inverters give an audible warning signal when the battery voltage is lower than 10.5V (21V for the 24V version). The inverter automatically shuts off when the battery voltage drops below 10V (20V for the 24V version). Fuse protected input circuitry.

Order Code	Power	Voltage	Price
651.581	150W Continuous	12V	£36.39
651.578	150W Continuous	24V	£36.39
651.582	300W Continuous	12V	£50.64
651.585	300W Continuous	24V	£50.64
651.583	600W Continuous	12V	£101.59
651.593	600W Continuous	24V	£101.59
651.587	1000W Continuous	12V	£177.18
651.597	1000W Continuous	24V	£177.18
651.602	1500W Continuous	12V	£314.52
651.605	1500W Continuous	24V	£314.52
651.589	2500W Continuous	12V	£490.54
651.599	2500W Continuous	24V	£490.54



ILLUSTRATION SHOWN IS 651.583 600W VERSION.

All prices are inclusive of V.A.T. Carriage (B.D) Per Order

Many uses include:- . Fetes . Fairgrounds . Airshows . Picnics . Camping . Caravans . Boats . Carnivals . Field Research and . Amateur Radio field days * Powering Desktop & Notepad Computers.

DELIVERY CHARGES ARE £6.00 PER ORDER. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLC.S ETC. PRICES ARE INCLUSIVE OF V.A.T. SALES COUNTER. VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX, OR EMAIL US AT SALES@BKELEC.COM ALTERNATIVELY SEND CHEQUE OR POSTAL ORDERS MADE PAYABLE TO BK ELECTRONICS.



B.K. ELECTRONICS



UNIT 1, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR
TEL.: +44(0)1702-527572 FAX.: +44(0)1702-420243

For Full Specifications View our web site at:-
WWW.BKELEC.COM/INVERTERS.HTM



20% discount for EPE readers

digimess® power supplies from £99.00 inc vat & del



Vann Draper Electronics Ltd
The test & measurement specialists
www.vanndraper.co.uk
Test equipment from Grundig, digimess, Kenwood, Hameg, Tektronix, Avo and more.

Vann Draper is offering over 20% discount to readers of *Everyday Practical Electronics* on their new range of low cost digimess® power supplies.

The range includes single, dual, triple and high current output types. All feature LED displays of voltage and current and can be operated in constant voltage or constant current modes. Dual and triple types have switching for independent, series, parallel and tracking modes. All models are supplied complete with mains lead, operating manual and a 1 year guarantee.

Model number	HY3003	HY3003-2	HY3003-3	HY3010	HY3020
Price (inc vat & del)	£99.00	£169.00	£199.00	£275.00	£375.00
No of outputs	Single	Dual	Triple	Single	Single
Output voltage	0-30V	2 x 0-30V	2 x 0-30V, 5V	0-30V	0-30V
Output current	0-3A	2 x 0-3A	2 x 0-3A, 3A	0-10A	0-20A
Load regulation	<0.01%	<0.01%	<0.01%	<0.02%	<0.02%
Ripple & noise	<1mV rms	<1mV rms	<1mV rms	<3mV rms	<3mV rms
Dimensions (mm)	291x158x136	365x265x164	365x265x164	365x265x164	365x265x164

To order, simply post the coupon to:
Vann Draper Electronics Ltd, Stenson House, Stenson, Derby DE73 1HL.
Or Tel 01283 704706 Fax 01283 704707 Email sales@vanndraper.co.uk

Use this coupon for your order

Please supply me:

(Qty) (Model) (Price)

(Qty) (Model) (Price)

Name: _____

Address: _____

Tel No: _____

Total £ _____

Cheques payable to Vann Draper Electronics Ltd or debit my visa, mastercard or switch card:

Card type: _____

Card No: _____

Expiry date: _____ Switch Issue No: _____

Signature: _____

Overseas readers can still obtain this discount but carriage charges vary according to country. Please telephone, fax, email or write to Vann Draper.

USING THE PIC'S PCLATH COMMAND

JOHN WALLER

How to use PCLATH to access a PIC's higher program addresses and place tables where you want them.

JOHN Becker described extended data memory bank use in *EPE* June 2001, with particular reference to the PIC16F87x devices which contain up to 512 bytes of data memory. The data memory is divided into "banks" of 128 bytes, and John explained how to cope with the complexity of up to four banks.

In a similar way, the program memory scope varies from 2K to 8K bytes, depending on the device, and is partitioned into 2048 (2K) byte-wide pages. Normally, the use of the term *page* would apply to sections of data memory and program memory; Microchip has chosen *bank* to apply to data memory (special function and general purpose registers), and has reserved the term *page* for program memory. It is convenient here to divide pages into *sub-pages* of 256 bytes each, with eight sub-pages to a page.

The extension of program memory across page boundaries is somewhat transparent (of no concern) to the programmer, but there are constraints on setting the program counter which must be complied with for correct operation of the program.

PAGE ALLOCATION

Most readers are probably very familiar with the PIC16x84, which has 1K of program memory in a single page. All the tables used in the *PIC Tutorial* series (Mar to May '98), for example, are placed in the first 256 bytes of program memory in the 'x84, a constraint imposed for a reason that may not immediately be apparent.

In fact, tables may be put anywhere in program memory space, once the operation of the PCLATH function is understood, and the table is wholly contained within a sub-page. The number of bits

required to access different spans of program memory is shown in Table 1.

The program counter (PC) value is held in a 13-bit special function register, which can be regarded as having two parts – PCH (Program Counter High) and PCL (Program Counter Low), for the high and low bytes, respectively. PCH resides in the upper five bits of the PC, whereas PCL resides in the lower eight bits.

PCL can be written to directly, as is done when normally accessing tables, for example, and the response to amending PCL takes immediate effect. PCH, though, can only be written to via the lower five bits of special function register PCLATH. Writing to PCLATH, however, only takes effect when the CALL, GOTO or arithmetic operation involving PCL is performed.

It is worth noting that PCLATH is a write-only buffer. It is not safe to read PCLATH in order to (perhaps) do PC arithmetic (although Microchip's MPSIM simulator lets you do this).

Table 2 shows starting addresses for pages and sub-pages which are accessed under PCLATH control.

Table 2. Starting Addresses for Pages and Sub-Pages (Addresses are in hexadecimal.)

Sub-page	Page 0	Page 1	Page 2	Page 3
0	0000	0800	1000	1800
1	0100	0900	1100	1900
2	0200	0A00	1200	1A00
3	0300	0B00	1300	1B00
4	0400	0C00	1400	1C00
5	0500	0D00	1500	1D00
6	0600	0E00	1600	1E00
7	0700	0F00	1700	1F00

Table 1. Number of Program Counter Bits Required in Relation to PCLATH

Number of bytes in program memory	Number of bits required in program counter	Number of bits required in PCLATH
2048 (2K)	11	0
4096 (4K)	12	1
8192 (8K)	13	2

SETTING PROGRAM COUNTER VALUE

There are three ways in which the programmer can set a value into the program counter (PC):

- An instruction which carries out an arithmetic operation on the PC. The most commonly used such instruction is adding a value to the PC from the working register when accessing a table, such as `ADDWF PCL,F` as used in the example program listings.
- A `CALL` or `GOTO` instruction which places the address of a label into the PC.
- A `RETURN` instruction which places the contents of the stack top into the PC.

ARITHMETIC OPERATIONS

Arithmetic operations on the PC involve the working register and other 8-bit wide registers. It therefore follows that only PCL can be set with an arithmetic instruction. PCH remains at whatever value it holds at the time of the instruction.

It is possible to place a table anywhere in program space by setting PCLATH before the call to the table is made. As explained presently, the purpose of PCLATH is to set PCH for the call itself. Then, at the arithmetic instruction, it is used again to set PCH, but with an important distinction:

The call itself only requires bits 3 and 4 of PCH to be set, whereas the arithmetic instruction requires bits 0 to 4 to be set, for 8K program memory devices. For 4K program memory devices, bit 4 of PCH is ignored.

The program example shows how this is done. Fortunately, the value may be set into PCLATH for all 5 (4) bits and need not be changed again until after the table has returned its value. Fig.1 illustrates this process.

CALL AND GOTO

The operation code for `CALL` and `GOTO` instructions sets 11 bits of the destination address, which is all that is needed in 2K program memory devices. The additional bits are set from PCLATH bit 3 for 4K program memory devices, and bits 3 and 4K for 8K devices. This is shown in Fig.2.

LISTING 1

```
MOVLW %00001000 ; Set up for page 1
MOVWF PCLATH    ; sub-page 0
MOVLW 2         ; Get third line from
CALL TABLE1    ; first table
MOVWF PORTB     ; Display it on Port B
CLRF PCLATH     ; Set for page 0 and sub-page 0
LOOP1: BTFSS PORTA,0 ; Loop until button 0
       GOTO LOOP1   ; pressed
```

LISTING 2

```
.ORG %0000100001111111 ; 087Fh (hex), page 1
                          sub-page 0
TABLE1: ADDWF PCL,F
        RETLW %00100100
        RETLW %01011100
        RETLW %10000110
        RETLW %00011001
```

LISTING 3

```
MOVLW %00001011 ; Set up for page 1
MOVWF PCLATH    ; sub-page 3
MOVLW 1         ; Get second line from
CALL TABLE2    ; second table
MOVWF PORTB     ; Display it on port B
CLRF PCLATH     ; Set up for page and sub-page 0
LOOP2: BTFSS PORTA,1 ; Loop until button 1
       GOTO LOOP2   ; pressed
```

LISTING 4

```
.ORG %0000101101011001 ; 0B59h, page 1
                          sub-page 3
TABLE2: ADDWF PCL,F
        RETLW %11010001
        RETLW %01110101
        RETLW %10100000
        RETLW %11000010
```

RETURN INSTRUCTION

A **CALL** instruction pushes PCL and PCH values onto the stack. A **RETURN** instruction pops those PCL and PCH values and puts them into the PC, and no manipulation of PCLATH is required. It might be necessary, however, to set PCLATH after the return, as shown in the following example.

PROGRAM EXAMPLE

This program example (the software for which is available as stated later) is designed for a PIC16F877 device plugged into the *Toolkit Mk3* board (Oct '01) with Port B connected to the l.e.d.s and Port A bits 0 to 3 connected to the four push-button switches. It can equally well be simulated through other equivalent hardware assemblies (as a breadboard assembly for instance). Throughout the example, program memory span is artificially extended by the use of **ORG** (origin) statements.

The uncommitted switch inputs are connected to Port A bits 0 to 3 in active high mode. Button "X" will be used to refer to the switch connected to Port A bit X. The

uncommitted l.e.d. outputs are connected to Port B. Ports A and B are initialised accordingly. The program comprises a series of table calls and jumps, with pauses waiting on a button press to allow the value returned from a table to be viewed on the l.e.d.s.

The first operation from the example program, after initialisation, is shown in Listings 1 and 2 (the grammar used is TASM).

The first two lines in Listing 1 set all bits in PCLATH to zero, except bit 3. The table in Listing 2 starts at address 087Fh. Table 2 shows this address is in page 1, sub-page 0, meaning only bit 3 in PCLATH should be set, to make it equal to 08h. The third line in Listing 1 sets the table line access parameter. The fourth line calls the table, whereby bits 3 and 4 of PCLATH are prepended to (placed in front of) the opcode to give the full table address, as in Fig.2.

Execution now passes to the first line in Listing 2. There the first five bits in PCLATH are prepended to the ALU result of the arithmetic operation, as in Fig.1.

Since the value in the working register (W) is 2, the program counter jumps to the third data line in the table and returns a value of %10000110, which is then shown on the l.e.d. display at the fifth line of Listing 1.

The sixth line returns PCLATH back to its original value, an essential step if the following **GOTO** is to work correctly. The program now loops indefinitely until button 0 is pressed, whereby execution passes to Listings 3 and 4.

The operation of the second pair of Listings (3 and 4) is almost the same as the first pair. The table address is still in page 1, but is in sub-page 3, since 0B59h - 0800h = 0359h, and 0359h / 256 = 3.35, or 3 rounded down to the nearest integer; this may also be determined from Table 2. In Listing 4 the second line from the table, %01110101 is returned and displayed, and the program loops until button 1 is pressed, whereby execution passes to Listing 5.

TABLES BEYOND SUB-PAGE 0

Listing 5 shows how a table could be placed in the 16F84, for example, outside of the first 256 bytes of program memory within a page. Here the table is at address 0564h, or page 0, sub-page 5, as set by the first two lines. The next two lines call for the fourth line from the third table, which returns %01100110 for display on Port B, similarly to before.

Since the **GOTO** destination address is in the same page as the third table address, there is no need to reset PCLATH before entering the loop, which may be subsequently exited by pressing button 2. On exit, the following three lines set up and execute a jump to page 3, as shown in Listing 6.

Note that in Listing 6 it was sufficient to set bits 3 and 4 (in Listing 5) only of PCLATH for the jump to occur correctly; in other words, the sub-page is immaterial for this particular operation, as in Fig.2. But for the second and third lines of Listing 6, where preparations are made to access the table at TABLE4, setting sub-page 2 is material, and this is done simply by setting bit 1 of PCLATH.

The first line in the table is then accessed, and a value of %10010111 is returned for display on Port B. Pressing button 3 exits from the loop to the final,

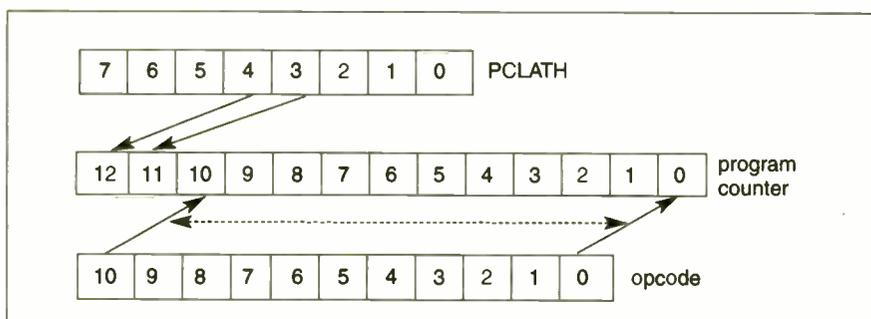


Fig.1. Setting the Program Counter for an Arithmetic Instruction

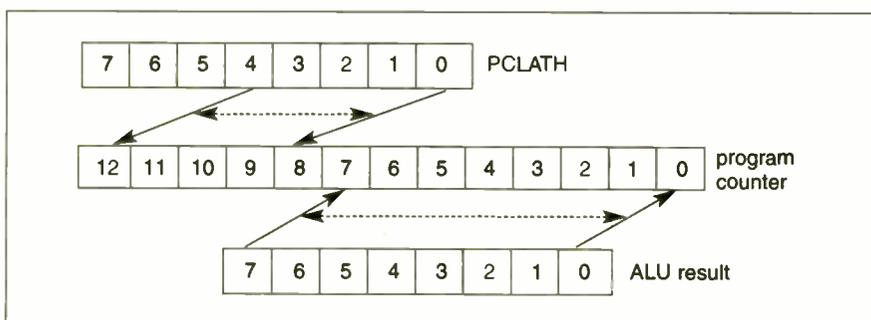


Fig.2. Setting the Program Counter for a CALL or GOTO Instruction

LISTING 5

```
MOVLW %00000101 ; Set up for page 0
MOVWF PCLATH ; sub-page 5
MOVLW 3 ; Get fourth line from
CALL TABLE3 ; third table
MOVWF PORTB ; Display it on port B
LOOP3: BTFSS PORTA,2 ; Loop until button 2
GOTO LOOP3 ; pressed
MOVLW %00011000 ; Set up for page 3
MOVWF PCLATH ; sub-page 0
GOTO JUMP1 ; Go there

.ORG %0000010101100100 ; 0564h, page 0
; sub-page 5.

TABLE3: ADDWF PCL,F
RETLW %00110111
RETLW %11001101
RETLW %11100001
RETLW %01100110
```

and infinite, loop whereby %11111111 is shown on Port B.

PROGRAMMER'S TASK

Every **CALL** and **GOTO**, and every arithmetic operation affecting the PC, requires that **PCLATH** contains the correct value for the operation concerned. Sometimes, for example, **GOTO** is used in a timing loop, which might have to allow for two additional **PCLATH**-setting instructions, and this loop might lie across a page boundary.

Somehow these matters must be catered for in PIC programs, whether they are written in "normal" PIC code, or in a high level language, such as BASIC or C. As with so much in programming, there are diverse opinions on which is the best technique. A useful strategy, for instance, could be:

1. Assign a functionality to each of the pages which minimizes **CALL** and **GOTO** instructions across page boundaries.
2. If possible, provide buffer zones, with no instructions, near page boundaries.
3. Write a first pass for the code ignoring the need to set **PCLATH**; have it assembled and examine the listing.
4. Determine where **CALL** and **GOTO** instructions cross page boundaries, and where table calls (or other arithmetic operations on **PCL**) cross sub-page boundaries.
5. Readjust tables so they are completely contained in a sub-page.
6. Include **PCLATH** setting instructions where required.
7. Repeat steps 4, 5, and 6 until no further corrections are required.

In an automatic program to do the above, steps 1, 2, and 3 would mostly be done by the programmer, and the automatic program would do the rest. The programmer might have to try again if the process does not converge.

PRACTICALITIES

In practical terms, though, manual inspection and iteration during program development is at the very least tedious and time consuming. At worst, it can be highly error prone. Each time a program is modified, you need to repeat the fix-up process, and on subsequent occasions the chances are that you have mostly forgotten how large chunks of the program work in detail.

LISTING 6

```
.ORG %0001101010011100 ; 1A9Ch, page 3
; sub-page 2
JUMP1: MOVLW 0 ; For first line of table
BSF PCLATH,1 ; Set up for sub-page 2
CALL TABLE4 ; fourth table
MOVWF PORTB ; Display it on Port B
LOOP4: BTFSS PORTA,3 ; Loop until button 3
GOTO LOOP4 ; pressed
FINAL: MOVLW $FF
MOVWF PORTB
GOTO FINAL
TABLE4: ADDWF PCL,F
RETLW %10010111
RETLW %00111111
RETLW %01101011
RETLW %10101010
```

Alternatively, every relevant instruction that might involve page boundaries could be preceded by **PCLATH**-setting instructions, whether they are needed or not, a brute-force approach. Whilst it can be argued that it would be cumbersome and consume valuable program memory space to set **PCLATH** for every such instruction, there is a lot to be said for the "brute force" approach if programming space permits it and there are doubts about where page boundaries might lie.

The use of **PCLATH** is essential in many larger PIC programs, and it is a command that you should familiarise yourself with through experiment. Perhaps the best advice is to use it in a fashion you feel comfortable with, and which you have proved through experimentation to be reliable. While evolving that technique, remember that you have to keep your wits about you – but then, don't you always in programming!

STRUCTURED PROGRAMMING

Program structure, whether in the PIC language, or a high-level language, is the province of the program author(s), although there are guide lines. For example, this author's policy is:

- a. Where something seems to be overwhelmingly complex, break it down into chunks of manageable size.
- b. Try and write separate routines (terminated in a **RETURN**) for each of the chunks, and aim to keep routine size to a page or less; avoid what is called "spaghetti code" which goes on and on without a break.
- c. Make a routine self-contained with as few links to other routines as possible. Do not use **GOTO** instructions between routines (but remember the PIC's stack only allows a limited number of "nested" calls).
- d. All variables (general purpose registers) in the PIC language are "global", that is, visible to all routines. Be careful to reduce the number of routines which alter variable values to as small a number as possible, preferably one only, perhaps by defining more variables than is strictly necessary. Be especially cautious where variable values are altered in interrupt routines. Read Malcolm Wiles articles on *Using PIC Interrupts* (Mar/Apr '02) carefully.
- e. Insert comments at the head of each routine which describe what the routine

does, what routine(s) it calls, and where it is called from.

f. Nearly every line, or group of lines, in the code deserves its own comment, even if trivial. Define what each variable does. When mystified by some lines of code, or things seem to be ambiguous, a seemingly trivial comment can help. Use capitalisation or punctuation to make it clear how many lines comments apply to. In the listings shown in this article, comments start with a capital letter, and continue over more than one line where appropriate, to the line before another headed by a capital letter. For example, in Listing 1, the first comment applies to the first two lines. Check your spelling!

g. Remember: comments are written once but read many times. Test your comment writing quality by reviewing what you wrote six months ago to determine if it still makes sense!

h. Where appropriate, put things in alphabetical order.

RESOURCE

The full illustrative software listing for this article is available from the *EPE* Editorial office on 3.5in disk (*EPE* Disk 5 – for which a nominal handling charge applies, see *PCB Service* page), and is also available for free download from our ftp site, accessible via the top of the main page at www.epemag.wimborne.co.uk and held in folder **PUB/PICS/PCLATH**.

Note that only the software for *Toolkit TK3* V1.2 and higher version numbers can handle addresses above 2K and the **PCLATH** command. □

COMING SOON!

We have a number of short PIC programming features in the pipeline. These are just two to look out for:

Using PICs and Square Roots Algorithm. Peter Hemsley again shows us a programming routine that is extremely well thought-out, is neat and compact, and works beautifully – it is a superior maths function that the PIC family lack, yet which is often needed in a variety of applications (next month).

TK3, Win2000 and WinXP. Mark Jones has unravelled the secrets of getting our *Toolkit TK3* programming software running under the Windows 2000 and XP platforms.

ROTARY COMBINATION LOCK

THOMAS SCARBOROUGH

Pure logic and a "stack of cards" function help to maintain the security of your cherished possessions.

THE purpose of this design is to emulate as closely and as simply as possible the traditional rotary combination lock. Full emulation would be possible with a complex design – close emulation is possible with a remarkably simple circuit – in this case using just two CMOS i.c.s and three transistors.

Pseudo-rotary combination locks are well known. These usually use a combined dial and pushbutton, with limited rotation of the dial. The dial is usually turned to a number in the sequence, then a pushbutton is pressed to register the number. Both this and the characteristics of the standard wafer rotary switch (its rotation-limit-stop and snap-action) make such locks seem poor substitutes for the real thing.

This design has smooth 360° rotation, does not use a pushbutton switch, and offers roughly twice the security of a 4-digit keypad lock. It also prevents aimless turning of the dial, and is able to send a secret panic (*duress*) signal to another location.

The last two features are optional, and may be built onto an additional printed circuit board, which may also be interfaced to a standard intruder alarm system.

SYNC LOCKING

The Rotary Combination Lock has one significant difference to the old mechanical lock – it needs to be turned "in sync" with a pulsed l.e.d. That is, the lock's dial must point to each number in sequence at the moment that an l.e.d. pulses.

Once opened, the lock is closed again by turning the dial to a Reset digit. Assuming that the rotary dial has twelve positions, there is one chance in 20,736 (that is 12^4) that a prospective thief would randomly hit the right combination.

In practice, however, due to the construction of the wafer rotary switch, the chances of randomly hitting the right combination are much less than this. On the


other hand, there is better than one chance in two that the would-be thief's *first* move will trigger an alarm.

A particular advantage of the Rotary Combination Lock is that its fascia may be artistically altered to suit every taste. In fact the lock need not even be rotary – the circuit would also work with a standard keypad, or with various arrangements of momentary-action, normally-open switches. These switches need not even be mounted together in the same place.

CIRCUIT DESCRIPTION

The Rotary Combination Lock is based on a standard cascaded latch using four AND gates, IC2a to IC2d, as shown in Fig.1.

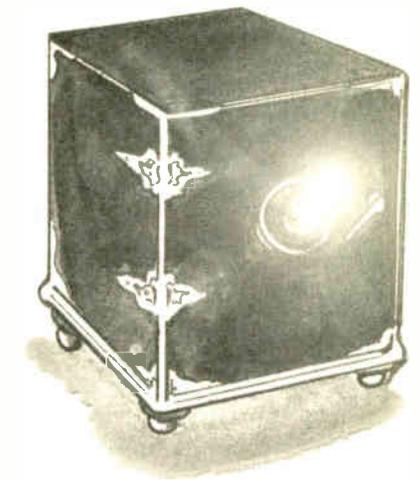Let us consider the action of just one of these gates. According to AND logic, output terminal pin 3 will remain low (logic 0)




for all combinations of inputs at pins 1 and 2, except when *both* inputs go high (logic 1) together. In this case, output terminal pin 3 also goes high.

Normally, pin 2 is held low through resistor R8 and pin 1 is held high through R14, consequently IC2a's output pin 3 is held low. When IC2a pin 2 is taken high through the 12-way rotary switch S1 (see later) both inputs are now high, so pin 3 also goes high. As pin 3 is fed back to pin 2, the gate becomes "latched" with its output high.

As a result, IC2b's input pin 6 is also held high. This gate's input pin 5 is normally held low through R9 and the same logic applies as with IC2a, so it too can be triggered when a pulse is received from switch S1, which enables IC2c to be triggered via S1, and so on through IC2d.

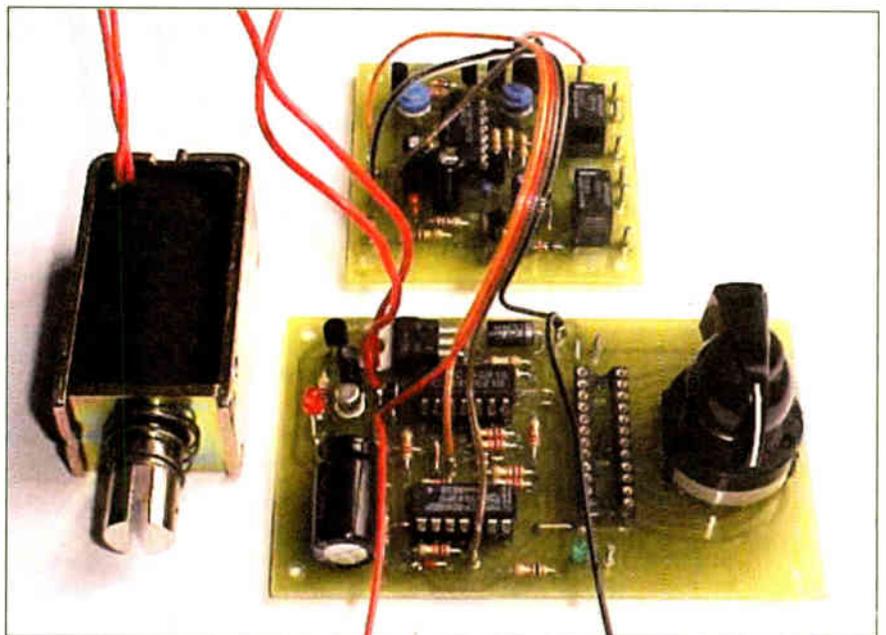Next, consider what happens when a negative-going (logic 0) pulse is applied to IC2a pin 1. This causes output pin 3 to go low and each of the four latches IC2a to IC2d now resets – collapsing, as it were, like a stack of cards, in accordance with AND logic.



This reset action is triggered if switch S1 is set to any position other than the four which connect to the IC2 gate chain. The pulses from these other positions control the opening and closing of electronic switches IC1a and IC1b. Their control inputs are normally held low via resistors R4 and R6 and their "gate paths" remain open (very high impedance). When either of them receives a pulse from switch S1, the respective gate path closes, causing IC2a pin 1 to be pulled low via diode D3 or D4, so resetting the IC2 gate chain.

If it is IC1b that is triggered, the negative-going pulse generated at the junction of R7 and IC1b pin 3 is used to activate the Interface alarm discussed later. However, IC1a is not connected to the alarm controller, and this allows one switch position to be used as a Reset digit, to close the lock after it has been opened, as well as six digits to trigger an alarm in the case of aimless turning of the dial.

Diode D5 in IC2d's feedback path prevents the possibility of a brief positive-going pulse from S1 reaching the gate (g) of transistor TR3.

When the third digit of the 4-digit code has been set by switch S1, IC2c pin 9 goes high, as does pin 12 of IC1d, causing this bilateral switch to close. This means that

switch IC1c is now potentially able to conduct. When IC1c's control pin 6 goes high, this causes a high pulse at IC1d pin 11. This pulse may also be sent to the Interface unit as a Duress signal.

The Duress switch position may either replace the 4th digit in the 4-digit sequence, or add a 5th digit to the 4th. Thus someone who knows that this is a 4-digit system would not notice anything out of the ordinary when the Duress position is selected. The Duress signal may also be sent after the 4th digit has been selected, e.g. on closing the lock again.

UNIUNCTION OSCILLATOR

The positive-going pulses which are routed through the 12-way rotary switch S1 are produced by a unijunction transistor (u.j.t.) oscillator based on TR2. The u.j.t. oscillator is chosen for its simplicity – it uses just four components to flash I.e.d. D2 and provide a positive pulse at its base 1 (b1).

A u.j.t. has a low "off" resistance (called its "inter-base" resistance, or R_{BB}), and this would cause this I.e.d. to glow continuously if it were wired to base 1 or base 2. For this reason, it is wired to the emitter (e), which has a high emitter-to-base "off"

resistance. Current through the I.e.d. is modest, so a high brightness I.e.d. would serve best in this position. Do not change the value of resistor R3.

A u.j.t. is similar in its design to an n-channel field effect transistor (f.e.t.), but with some important differences. Perhaps most importantly, its n-type material is only slightly doped, which creates an "avalanche" effect when the emitter potential reaches the transistor's "peak point" (in this case just over 8V), causing the u.j.t. to conduct simultaneously between its emitter and both bases.

When the u.j.t. conducts, the potential at base 1 rises sharply, and a positive pulse is sent to transistor TR1, which now conducts. TR1 ensures that the u.j.t. oscillator

Fig.2. Minor circuit change for "releasing" the lock

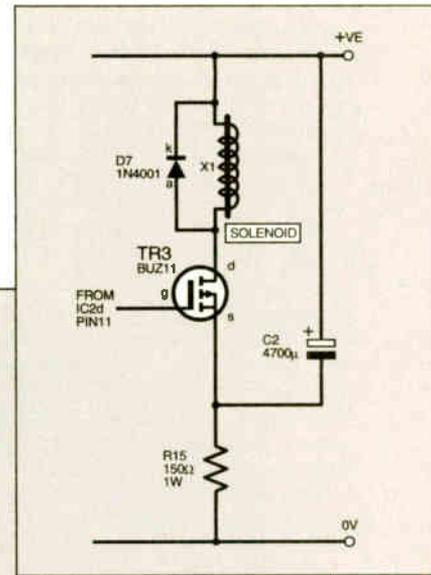
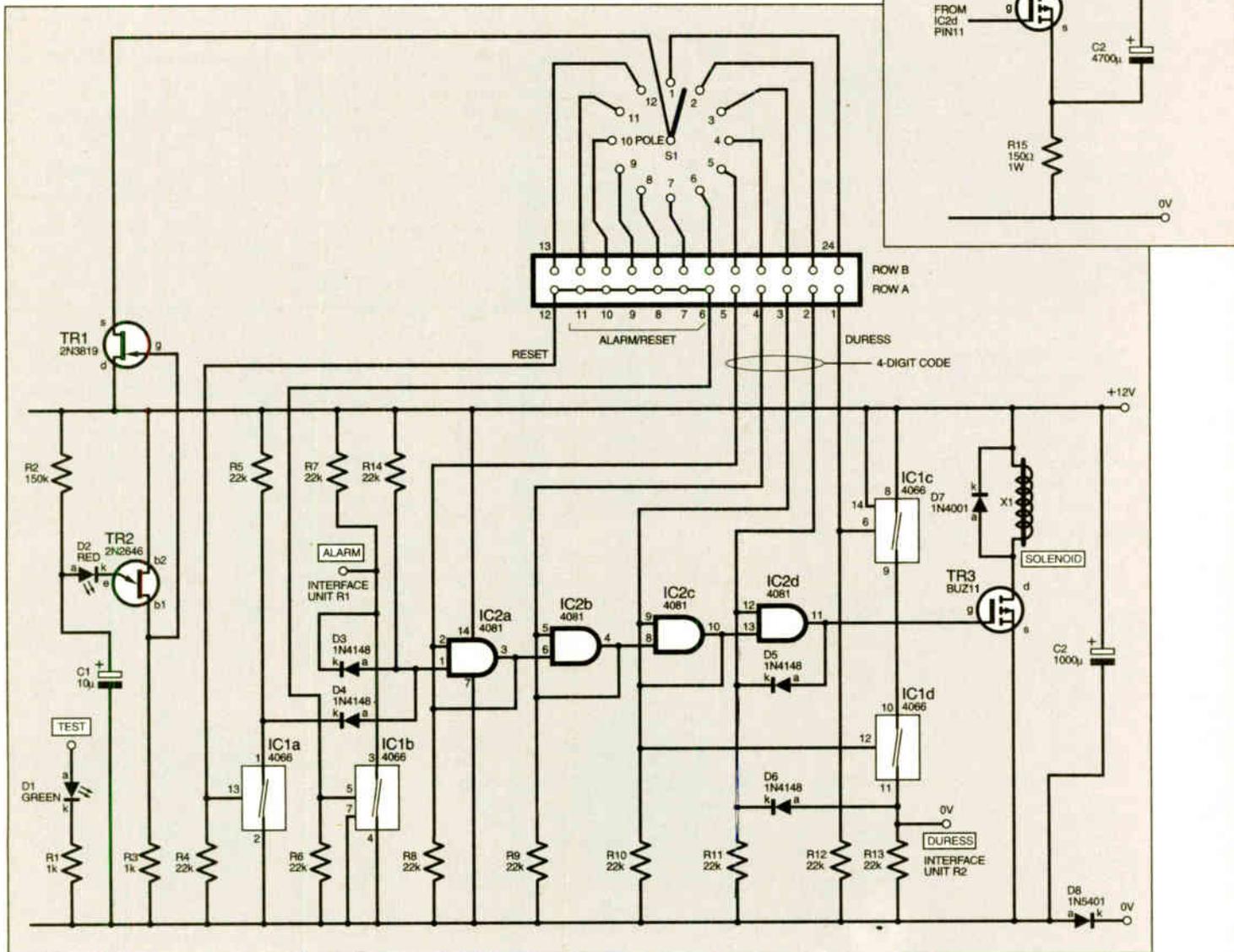


Fig.1. Circuit diagram for the Rotary Combination Lock. Note how positive pulses are routed through the 12-way rotary switch S1, via the 24-pin "combination" d.i.i. socket.

is not unduly loaded, and also that no negative-going pulses will reach the circuit and so unbalance it.


SOLENOID

The solenoid is powered by power MOSFET TR3, which conducts when the potential at its gate rises above about 4V, as provided by the output of IC2d. When IC2d latches, TR3 conducts, and the solenoid retracts with a convincing whack. The solenoid's integral spring enables the lock to close again when the circuit receives a Reset pulse from switch S1.

The specified MOSFET has an extremely low "on" resistance (0.04Ω), and this ensures that there is minimal power dissipation in the device, and therefore minimal generation of heat. In fact TR3 remains cool without any heatsinking.

Note that TR3 should not be substituted with "any old" power MOSFET, since a power MOSFET with a higher "on" resistance will dissipate more power, thus generating more heat, which would then need the use of a suitable heatsink.

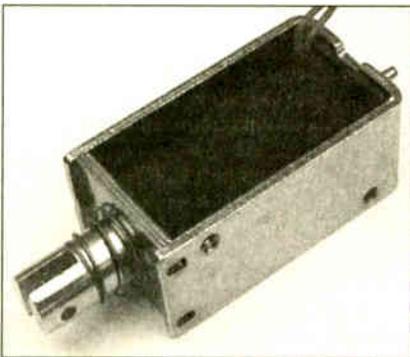A momentary action pushswitch may be wired between IC1a pin 13 and the +12V line if desired, so that the lock may be closed again with a button-press. Thus this lock could be used, for example, to open a door, and the pushbutton switch used to reset the lock after entering.



The specified solenoid consumes nearly 10W, and this means that a 12V 1A power supply is required. The solenoid could also be replaced with a relay if this would better suit the requirements of the application. Although the solenoid is rated for a continuous 12V, with the prototype it was found that after 15 minutes or so it generated an uncomfortable amount of heat (it is supposedly permitted to warm to 105°C)!

If the lock is likely to remain opened (solenoid active) for long periods, a simple modification to the circuit can be made as shown in Fig.2. This changes the lock from one that simply opens to one that briefly "releases". A tapered plunger may then be used to click the lock shut. This arrangement may be used also where only a smaller 12V power supply (100mA upwards) is to hand.

Note that diode D8 in the 0V line, which prevents reverse polarity power supply connection, warms as well when the lock is opened, and this is normal.

If desired, a number of solenoids may be wired in parallel. In this case, separate MOSFETs must be used in place of the single one used as TR3, and their gates are commoned. The power supply's rating *must* be suitably increased, as well as the rating of diode D8.

COMPONENTS

Approx. Cost
Guidance Only

£40
excluding batts

ROTARY COMBINATION LOCK

Resistors

R1, R3	1k (2 off)
R2	150k
R4 to R14	22k (11 off)
R15	150Ω 1W

All 0.25W 5% carbon film, except R15.

Capacitors

C1	10μ sub-min radial elect. 16V
C2	1000μ sub-min radial elect. 16V (see text)

Semiconductors

D1	green l.e.d., 3mm
D2	ultrabright red l.e.d. (3mm)
D3 to D6	1N4148 signal diode (4 off)
D7	1N4001 50V 1A rect. diode
D8	1N5401 100V 3A rect. diode
TR1	2N3819 f.e.t. transistor
TR2	2N2646 u.j.t. transistor
TR3	BUZ11 power MOSFET
IC1	4066 or 4016 quad bilateral switch
IC2	4081 quad AND gate

Miscellaneous

S1	1-pole 12-way rotary switch, p.c.b. mounting
X1	Solenoid, standard pull action, spring return, 12V d.c.

Printed circuit board, available from the *EPE PCB Service*, code 360; knob and dial for switch S1; 24-pin d.i.l. socket; 14-pin d.i.l. socket (2 off); connecting wire; solder pins; solder, etc.

See
**SHOP
TALK**
page

INTERFACE MODULE

Resistors

R1 to R3	100k (3 off)
R4, R7	4k7 (2 off)
R5	470Ω
R6	220k
R8, R10	1k (2 off)
R9, R11	22k (2 off)

All 0.25W 5% carbon film

Potentiometers

VR1, VR2	1M cermet preset (2 off)
----------	--------------------------

Capacitors

C1	100n min. polyester
C2, C4, C5	220μ sub-min. radial elect. 16V (3 off)
C3	1μ sub-min. radial elect. 16V
C6	100μ sub-min. radial elect. 16V

Semiconductors

D1, D4, D5	1N4148 signal diode (3 off)
D2	red l.e.d., 3mm
D3	green l.e.d., 3mm
D6	1N4001 50V 1A rect. diode
TR1	BC337 npn transistor
TR2	2N3819 f.e.t. transistor
TR3, TR4	BC547 npn transistor (2 off)
IC1	7556 dual CMOS timer

Miscellaneous

RLA, RLB	ultra-min, s.p.c.o. relay, 12V, low-power, p.c.b. mounting (2 off)
S1	min. s.p.s.t. pushswitch, p.c.b. mounting

Printed circuit board, available from the *EPE PCB Service*, code 361; 14-pin d.i.l. socket, connecting wire, solder pins, solder, etc.


Finally, l.e.d. D1 is provided to test rotary switch S1. A test lead can be connected between the anode (a) of the l.e.d. and any position of S1 (row B). The switch is then turned until D1 pulses. This is very helpful in setting up the circuit (more later).

CONSTRUCTION

Begin construction by making modifications to the rotary switch, S1, to provide full and smooth 360° rotation. Without this, the switch would fail to give the "feel" of a genuine rotary combination lock, although the circuit would still work perfectly well.

Remove the switch's rotation-limit washer and clip off its tab. Carefully prise open the switch, observing where each part fits. To cancel the snap-action of the switch, so that it will rotate smoothly, take out the spring and the two ball-bearings – if they have not shot out already! The author opens up such items inside a glass jar – the pieces can be awfully hard to find if they shoot into the air!

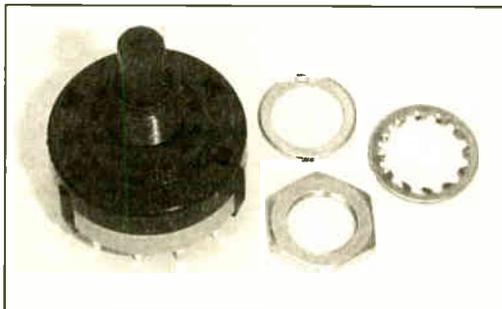Internally, there is a rotation-limit stop which is an integral part of the plastic moulding, which is to be found at the bottom of the switch's well. Cut or chisel this out, then test to see that there is a smooth



The rotary switch, before modification, showing the external limit washer and fixing nut and washer. Part of the switch body showing the internal rotation limit stop "pip" – which has to be removed to allow 360 degrees rotation.

360° rotation. Now snap the switch shut again, *carefully*, so as not to jog the small metal contacts out of place.

MAIN BOARD

Details of the main printed circuit board (p.c.b.) for the Rotary Combination Lock are shown in Fig.3. This board is available from the *EPE PCB Service*, code 360.

Solder the link wires, solder pins, and the three dual-in-line (d.i.l.) sockets. Note that some of the link wires are soldered beneath the d.i.l. sockets, and that the two link wires beneath MOSFET TR3 should be sheathed to prevent contact with its body when it is mounted flat with the board.

Next solder in position the resistors, diodes, and l.e.d.s, continuing with the capacitors and transistors. Transistor TR3 is static sensitive, and anti-static precautions should be observed, the most important being to ground your body immediately before handling (via a metal water tap for example). In the author's experience, f.e.t. TR1 is also a fragile device, and should be handled with care.

Be careful to observe the correct orientation of the electrolytic capacitors, transistors, diodes and i.c.s.

Attach the solenoid and l.e.d. D2 to the allocated solder pins. Finally, solder rotary wafer switch S1 into place on the p.c.b.

Thoroughly check the accuracy of your assembly and soldering and then insert the CMOS i.c.s IC1 and IC2, again observing anti-static precautions.

No case is specified, since the Rotary Combination Lock could be used in any number of applications, and thus mounted in various places. Ensure that the p.c.b. and switch are well protected from the elements.

The solenoid may be used as is, so that its plunger normally resides in a corresponding hole in a door frame. Alternatively, a mechanical arrangement may be used as shown in Fig.4. A suitable cover may then be used to enclose the mechanics.

Firmly fix a dial with a pointer to the shaft of rotary switch S1 – if the pointer slips out of place, your combination could be lost!

SETTING UP

Having ensured that there are no solder bridges or short-circuits on the board, connect it to a 12V 1A power supply. Check first that power MOSFET TR3 remains cool. If it does not, turn off the power immediately, and re-check the circuit.

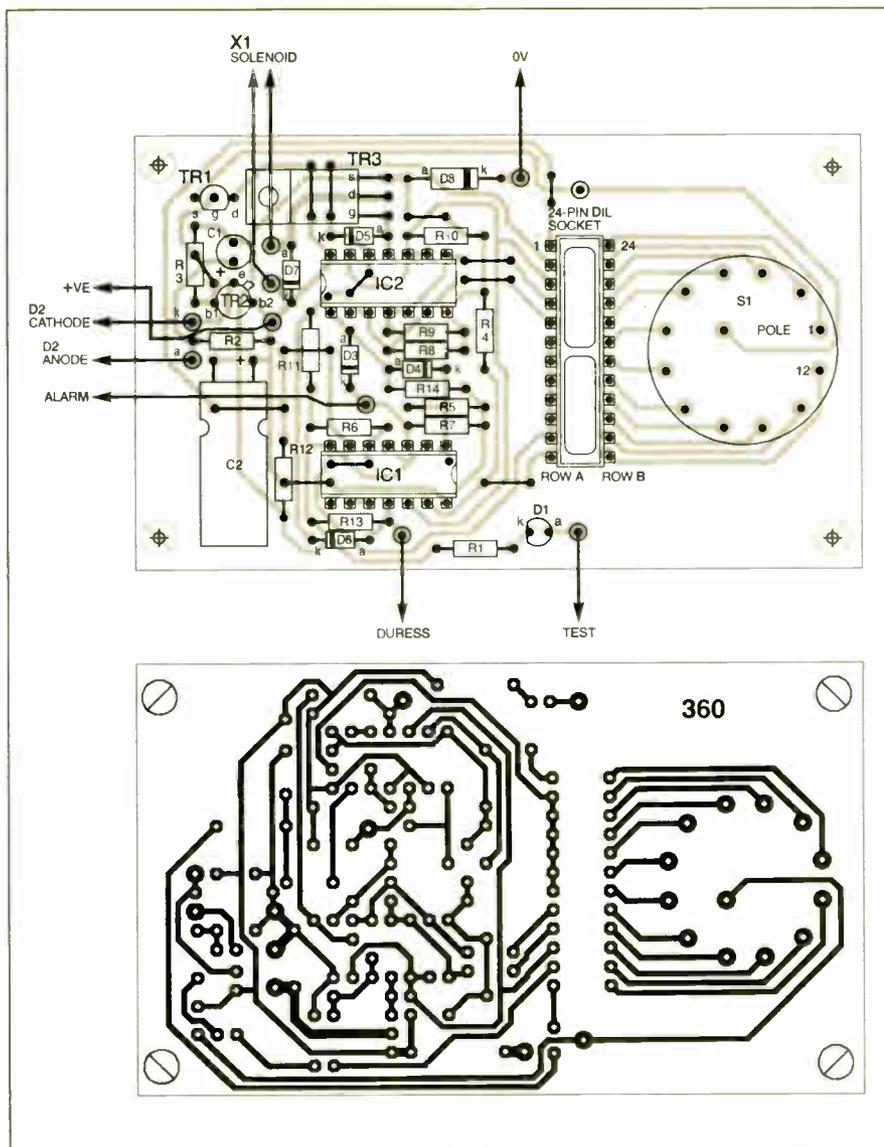


Fig.3. Rotary Combination Lock printed circuit board component layout, full-size copper foil master and lead-off wires.

Check that l.e.d. D2 is flashing. The solenoid should at this point not have closed yet.

One of the most important aspects of setting up is to configure rotary switch S1. A 24-pin d.i.l. socket (two rows of 12 holes) is used for this purpose, with sheathed link wires being used to set the combination. This is relatively simple to do, and permits easy changing of the combination at a later stage.


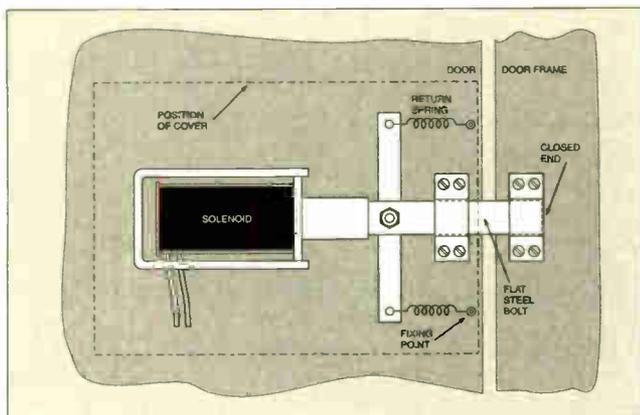
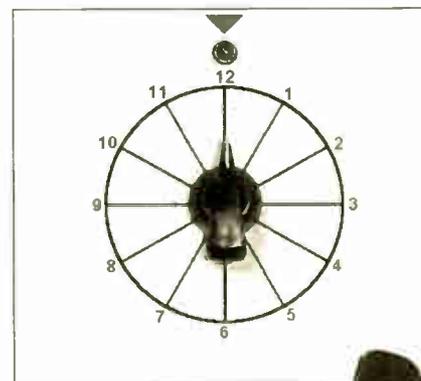


Fig.4. Mechanical "bolt" arrangement using a solenoid.

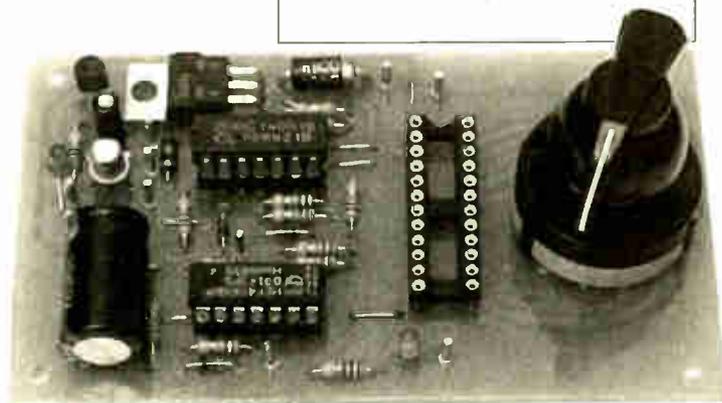


Completed prototype lock p.c.b. and suggested "combination" display scaling (above).

Alternatively, 24-pin plug-in sockets could be used to swap combinations in and out. Twelve sheathed link wires are used, with bared, untinned ends, each between 2cm and 4cm in length, as required. These are "jumped across" from Row A to Row B to set the combination.

For example, suppose we want to set the first digit of the 4-digit code, which is pin 5 of the 24-pin d.i.l. socket (pins 5, 4, 3 and 2 are used for the 4-digit code – see Fig.1). Plug in a sheathed link wire at pin 5 (Row A). Next, turn the rotary dial more or less to the position you would prefer for this first digit. Temporarily connect the solder pin adjacent to D1 to each hole in Row B (pins 13 to 24), until you find which of these lights i.e.d. D1. You might need to give the dial a little "play" to find the exact position. Now plug in the spare end of this first digit's wire into this hole.

The same procedure is now followed for the remaining eleven wires (refer to Fig.1). When all twelve wires have been plugged in at both sides of the socket (Row A to Row B), test the lock by turning the dial to the correct 4-digit sequence in synchronisation with the flashing of i.e.d. D2 (that is, the dial must be pointing to each number at the moment that D2 flashes).

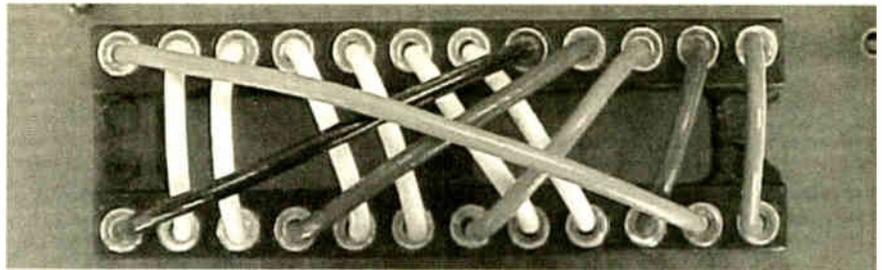The solenoid should operate decisively when the correct code has been selected. Turn to the Reset digit position that you have chosen to release the solenoid again. If it does not release, turn off the power and carefully re-check the circuit. Check again for warming in TR3 when the solenoid operates – there should be virtually no perceptible warming.



Using plastic-covered wires to set up the lock's combination in the board-mounted 24-pin d.i.l. socket.

Note that a fairly precise turning of the switch dial is required. This is not difficult, but if you are a few degrees out of true when turning to a position on the dial, this could reset the lock, or send Alarm or Duress pulses to the Interface board.

WORKED EXAMPLES

Suppose you are using a dial marked with 12 positions (as on a clock face), and have selected 1-2-3-4 on the dial as your 4-digit code (not recommended!), with 5 as the Reset digit, and 6 as the Duress digit. Digits 7, 8, 9, 10, 11, and 12 now remain, and these are therefore used as Alarm digits. The options include the following:

- The 4-digit code (1-2-3-4) opens the lock.
- Reset (5) closes the lock.
- 1-2-3 (the first three digits of the 4-digit code) followed by Duress (6) opens the lock and simultaneously sends a secret Duress signal to the Interface p.c.b.

- The 4-digit code (1-2-3-4) followed by Duress (6) opens the lock, then sends a secret Duress signal.

- Duress (6) followed by Reset (5) sends the secret Duress signal just before closing the lock.

Note that Duress *only* works as a substitute 4th digit, *or* as an additional 5th digit at the end of the 4-digit code. This feature remains disabled until the third digit of the 4-digit code has been selected.

- Positions 7, 8, 9, 10, 11 and 12 (Alarm) all trigger the alarm.

- Selecting 1-2-2-3 would have no effect, since four separate digits are required for the 4-digit code, each one different from the other.

- Finally, 2-1-5-3 (as an example) would represent a very lucky would-be thief! Each one of these digits misses both the Alarm and Duress digits. The chance of such a 4-digit lucky miss is about 1 in 33 (that is $1 / (5 / 12)^4$).

ALARM INTERFACE

THIS Interface circuit may be used not only to interface the Rotary Combination Lock just described to a standard intruder alarm system, but will also serve as a simple stand-alone, two-zone alarm system. It is also capable of switching powerful alarm sounders and beacons directly.

Besides this, the Interface is capable of a variety of standard switching options, of which four are described. These include:

- A "single-action" pushbutton
- A "dead man's handle" (strictly speaking, this term has been superseded by more politically correct terminology!)
- A "conditional" switch
- A timer

INTERFACE CIRCUIT

The circuit for the Interface is relatively straightforward and its schematic diagram is shown in Fig.5. It uses a 7556 CMOS dual monostable timer (IC1) which is used to close relays RLA and RLB for specific periods when pulses are received from the lock's main circuit board.

Presets VR1 and VR2 are used to set the duration of triggering of each of the monostable timers between about 0.7 seconds and two-and-a-half minutes with the component values shown. The values of capacitors C2 and C5 may be increased for longer timing periods.

IC1 requires a negative pulse at each of its trigger inputs, pin 6 and pin 8. A negative-going Alarm pulse is applied to IC1's trigger pin 6 from the main lock circuit.

However, the lock's Duress pulse is positive-going, so this needs to be inverted before it is presented to IC1b's trigger pin 8. This is accomplished with the help of transistor TR1, which is wired as a standard inverter.

The purpose of capacitor C1 at TR1's base is to damp any possible mains transients, since these may even pass through a regulated power supply. One would not want to rouse a rapid-reaction squad with a small mains transient (from a hairdryer, say!)


The specified relays are rated at 60V d.c. 1A, with a maximum switched power of 30W, or 125V a.c. 1A, and a

maximum switched power of 62.5VA. This means that they may be used to switch powerful alarm sounders and beacons directly – so long as their ratings are not exceeded.

Alternatively, they could be used to switch power relays, which in turn could switch even bigger loads.

OBLIGATORY INHIBITION

The Interface circuit includes a significant inhibition, in the form of field effect transistor (f.e.t.) TR2. Assuming that a would-be thief would abandon the Rotary Combination Lock at the moment

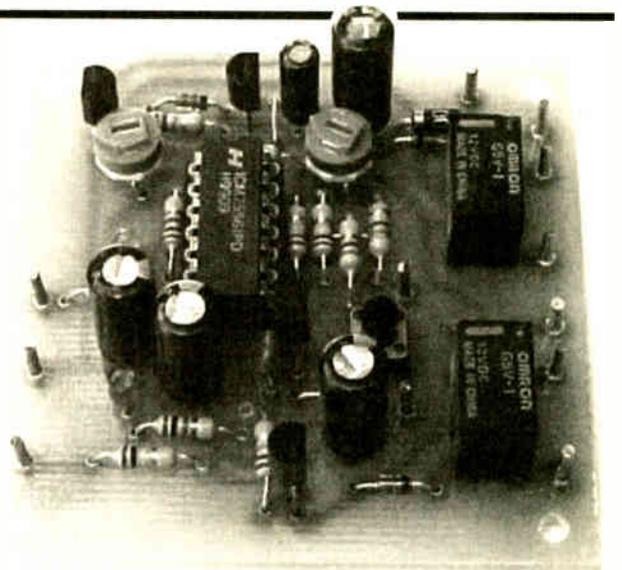

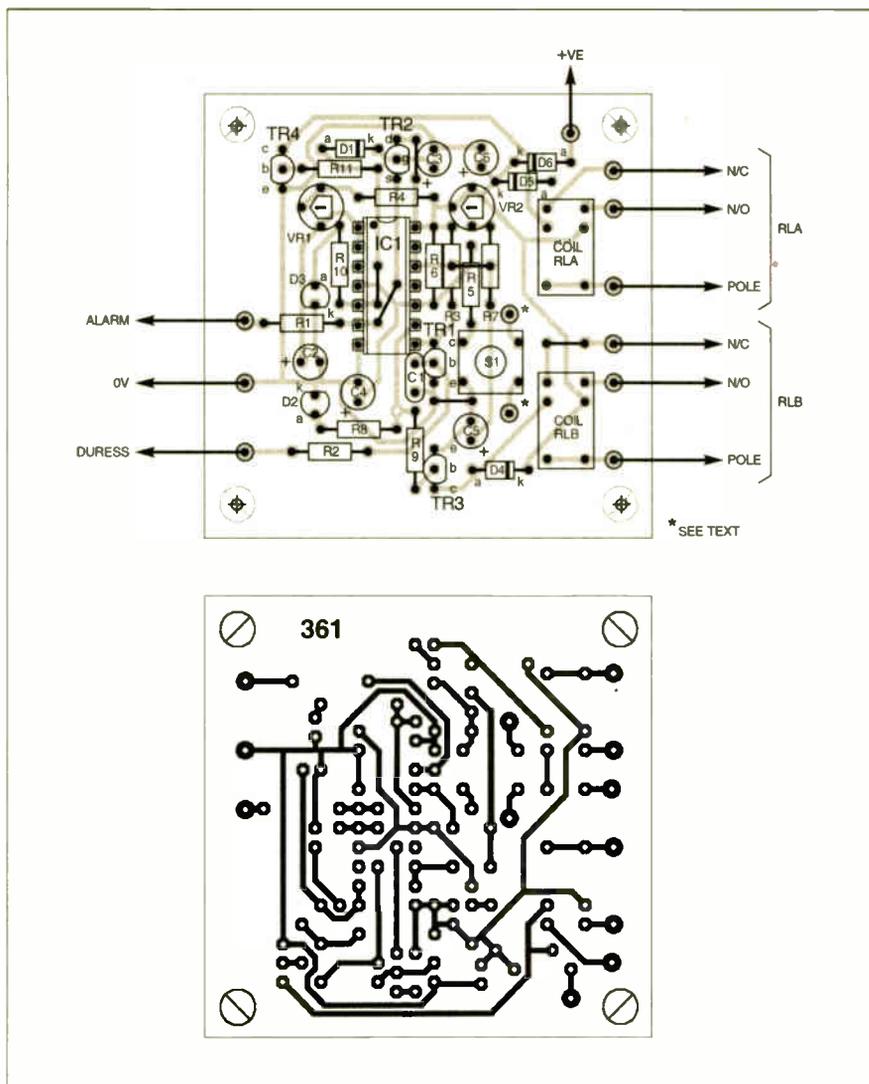


Fig. 6. Interface topside component layout, lead-off wiring details and full-size underside copper foil master pattern.

on the Interface p.c.b. are taken to these inputs of the intruder alarm system – or the POLE and N/O outputs are taken to normally-open inputs of the intruder alarm system.

STAND-ALONE ALARM

The Interface p.c.b. may also be used as a simple stand-alone, two-zone alarm system. In this case, normally-closed switches may be wired in series (these would protect, for instance, doors and windows) and connected between the Alarm input and the positive power line, with a “pull-down” resistor of 22kΩ taken from the input to 0V (see Fig. 7a).

Note that “normally-closed” refers to switches that are closed when the door, for example, is closed, but open when the door opens.

The Duress input may serve the same purpose, only the switches are now wired between the Duress input and 0V, while a “pull-up” resistor of 22kΩ is taken from this input to the positive power line (see Fig. 7b).

Bear in mind that the Alarm input has the Inhibit function, while the Duress input reacts immediately to every positive pulse it receives. The Inhibit function may be removed simply by taking out diode D1 from the p.c.b.

Normally-open switches may also be used. These are wired in parallel, and in

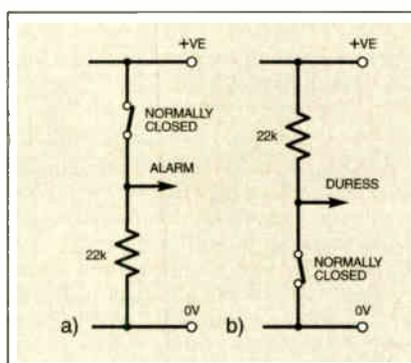


Fig. 7. Circuit details for a stand-alone alarm system.

this case, the positions of the 22kΩ resistors and the switches are swapped around.

OTHER USES

The “single-action” switch was described earlier. A “dead man’s handle” can perform a vitally important function in certain situations.

In a recent highly publicised case near the author, a pump attendant left his pump (apparently for lunch), and a team in some water-filled caves below nearly lost their lives. A “dead man’s handle” could prevent such incidents by sounding an alarm if, for instance, a pump is abandoned for too long

– or if, as the term suggests, the pump attendant should drop dead!

This is accomplished as follows: the alarm sounder is connected to relay RLA’s POLE and N/O connections. The Interface’s Alarm input is then tied low with a 22kΩ “pull-down” resistor, which is wired between the Alarm input and 0V.

This means that monostable IC1a would continually be triggering, and the alarm would always be sounding – if TR2 were not there to inhibit incoming negative-going pulses. Then the anode of D1 should be disconnected from its existing position and connected to IC1 pin 9 instead. A hole is provided for this purpose on the p.c.b., at the junction of R8 and R9 (see Fig. 6).

Now, every time a Duress pulse is received, the Alarm trigger is disabled. If, however, no Duress pulse is received, TR2’s Inhibit feature times out, monostable IC1a triggers, and RLA pole contact switches over to the normal open contact – sounding the alarm. The Duress input may be tied low with a 22kΩ resistor, and a normally-open switch (perhaps a lever switch) wired between the input and the positive line to operate the “dead man’s handle”.

All that now remains is for you to decide how soon you would like the alarm to sound after the unit has been abandoned (this is determined by capacitor C3 – see earlier), and how long you would like the alarm to sound (which is set by VR1). Adjust preset VR2 to its minimum value, since IC1b merely serves as a trigger in this application. Switch S1 serves to instantly cancel the alarm.

CONDITIONAL SWITCH

A “conditional” switch is one which switches on condition that another switch has (or has not) been activated during a predetermined period beforehand. This would have a wide variety of possible uses. For instance, it could be used to “authorise” the use of another switch for a predetermined period. It could also be used to disable another switch for a predetermined period, or be used as a form of double-handed switch.

The logic required to do this is simple, and the author leaves the details to the ingenuity of the constructor. In short, one set of relay contacts is wired in series with the opposite monostable timer’s input, so making one input dependent on the state of the opposite relay. Remember to use 22kΩ “pull-up” or “pull-down” resistors where necessary, so that no inputs are left “floating”.


TIME OUT

Finally, the Alarm input may be used as a timer. This begins to time the instant that a pushbutton is pressed, and will receive no further trigger inputs until the timing period has ended. It may be instantly reset at any time by means of switch S1.

For this purpose, the value of capacitor C3 may be reduced to nF, so that the pushbutton is disabled only for two or three seconds after the timing period has ended. A 22kΩ “pull-up” resistor is wired between the input and the positive rail, and a momentary-action pushbutton is wired between the Alarm input and 0V.

The instant the pushbutton is pressed, the timing period begins. The output is taken from relay RLA. □

CIRCUIT SURGERY

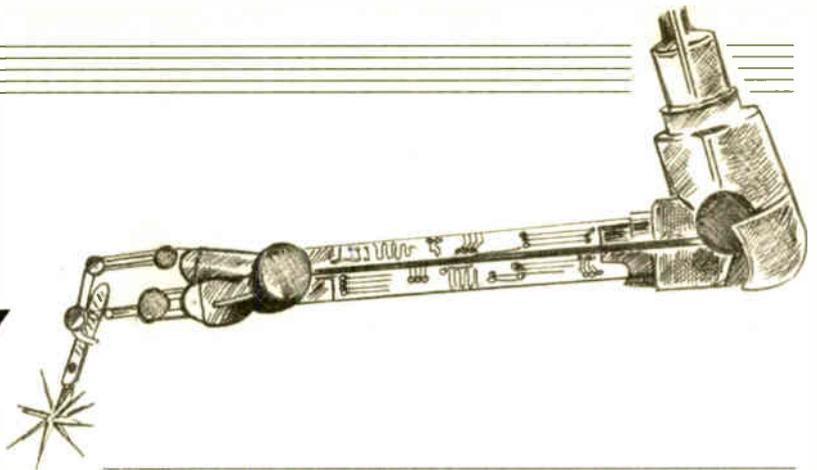

**ALAN WINSTANLEY
and IAN BELL**

Our monthly surgeons examine the fundamentals of bandgap references, revisit Y-class capacitors and a supply surprise.

Mind the Bandgap

Regular EPE reader *Gerard Galvin* asks by email: *What does the term 'bandgap voltage' mean? I've seen the term in data sheets and I think it relates to reference voltages.*

First of all, **bandgap** is a term relating to the physics of semiconductors and electrical conduction in general. In order for a material to be an electrical conductor the electrons must detach themselves from their atoms so that they can move around and form an electric current.

"Attached" electrons near the "outside" of the atom possess a certain range of energy values known as the **valence band**. "Unattached" electrons, which are free to move around and hence take part in conduction, also have a range of possible energy values, known as the **conduction band**.

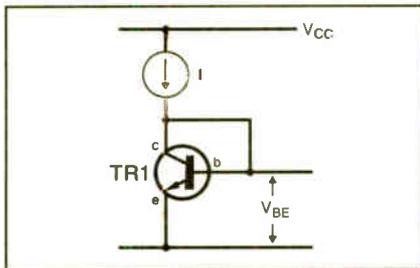


Fig.1. Basic V_{BE} voltage reference using a diode-connected transistor supplied with a constant current. V_{BE} has a negative temperature coefficient.

It is not possible for an electron to have an energy value between the valence and conduction ranges. The separation between these allowed energy ranges, that is from the top of the valence range to the bottom of the conduction range, is the **bandgap**.

For insulators the bandgap is very large so conduction does not take place. For conductors such as metals the valence and conduction bands overlap so electrons can easily move between them and conduction readily takes place. For semiconductors the bandgap is small so things get interesting: we can significantly change the electrical properties by adding "impurity" atoms as we do with diodes and transistors.

Effects such as light-dependent conduction are related to the bandgap too – e.g. if a photon provides the correct amount of energy to an electron in a semiconductor valence band, it can jump into the conduction band.

A full understanding of bandgaps and related issues requires some advanced physics and is therefore beyond the scope of this column. We will therefore move on to look at bandgap reference circuits.

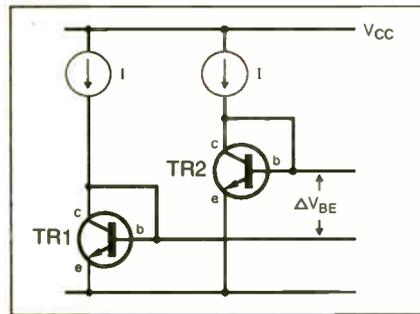


Fig.2. Two diode-connected transistors of different physical sizes provide a voltage, ΔV_{BE} , with a positive temperature coefficient.

Band of Circuits

In circuits such as analogue-to-digital converters it is essential to have an accurate and stable reference voltage if an accurate and stable conversion is required. We touch on this in *Teach-In 2002 Part 9*, but we did not have space to go into reference circuits in detail.

A number of possibilities spring to mind when considering how we might design a voltage reference, with the most obvious perhaps being to use the diode voltage drop (or transistor base-emitter voltage of a diode-connected transistor – see Fig. 1) or a Zener diode. These approaches are used in circuits that do not have to be particularly stable, but they are not suitable for high precision applications because of the high sensitivity of these voltages to changes in temperature. The Zener diode is more stable than the V_{BE} voltage by about a factor of three, but Zener diodes are noisy and the stability is simply not good enough for many critical applications.

Note that the "arrow in a circle" symbol in Fig. 1 is a constant current source, which we have discussed before in *Circuit Surgery*. In this case we could simply use a resistor, on the assumption that the supply voltage and V_{BE} voltages do not change much.

The V_{BE} voltage of the circuit in Fig. 1 would typically be about 0.6V at room temperature but it has a *negative* temperature coefficient – in fact V_{BE} decreases by about 2mV per degree Celsius increase. Some temperature sensor circuits actually make use of this very characteristic.

We can use the diode-connected transistor as long as we compensate for the temperature change. One way of doing this is to add V_{BE} to another voltage which has the *opposite* temperature coefficient. If we take two transistors of *different physical sizes* supplied with the same current, as shown in Fig. 2, it turns out that the temperature coefficient of the *difference* between the two V_{BE} voltages (labelled (ΔV_{BE} or "delta V_{BE} ") is positive. So if we build a circuit with an output V_{ref} given by

$$V_{ref} = V_{BE} + k \Delta V_{BE}$$

and we choose the right value for the constant k , then we get a temperature-stable voltage reference.

We can obtain a current that is proportional to the difference in V_{BE} using the

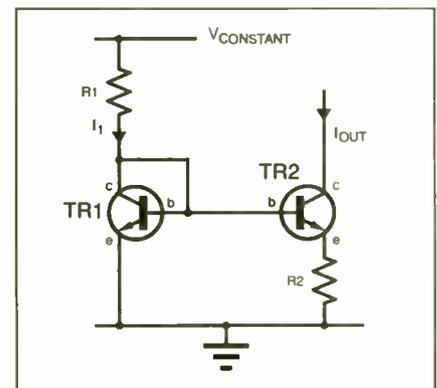


Fig.3. Here, I_{OUT} is proportional to the difference between the transistors' V_{BE} voltages and it has a positive temperature coefficient.

circuit in Fig.3. Here resistor R1 acts as a current source as both V_{CONSTANT} and V_{BE} of TR1 are fixed. The value of I_{OUT} is equal to the current in resistor R2 (ignoring TR2's base current).

The current in R2 is set by the voltage across it, which is the difference in the V_{BE} values (ΔV_{BE}) of the two transistors. Thus I_{OUT} is proportional to ΔV_{BE} . To get a voltage proportional to ΔV_{BE} we just pass I_{OUT} through a resistor.

The collector (c) of TR2 is the output of a current source and can therefore be set to any voltage within the operating range of the source. If we connect it to a voltage equal to V_{BE} (supplied from the base of a conducting transistor with its emitter connected to ground – see Fig.4) then the voltage at the other end of a resistor, R3, carrying I_{OUT} will be at $V_{\text{BE}} + R3 \cdot I_{\text{OUT}}$. As I_{OUT} is proportional to ΔV_{BE} this gives us a reference voltage in the form we were looking for.

After choosing component values which give the correct value for k the voltage obtained is around 1.2V and is related to the band gap for silicon. The voltage stability is about ten times better than a Zener and can be further enhanced by more sophisticated circuits.

To get a practical reference circuit we note that the V_{CONSTANT} we require for the current source input can be V_{ref} – our reference output voltage (clever isn't it!). The same voltage can also be used for V_{BIAS} for the transistor supplying the V_{BE} voltage. Current to the whole circuit can be supplied via a resistor (R4) from the power supply which gives us a basic temperature-compensated voltage reference (see Fig.5).

This circuit was published in 1971 by Robert Widlar (a highly respected engineer whose name often headed up many National Semiconductor application notes), and is one of the many implementations of the bandgap reference that are now available. The output from Fig.5. would usually be buffered by an op.amp to prevent loading effects. Other bandgap circuits put the op.amp and reference in a feedback loop to further stabilise the circuit. Bandgap references are available as integrated circuits such as the LM113 and LM10 from National Semiconductor. *IMB.*

Capacitors: Class of Y2

Roger Warrington writes:

With respect to Circuit Surgery in the June issue and the discussion about X-Class and Y-Class capacitors, the statements you made are essentially correct. However, I feel that the effect of the difference between Y1 and Y2 caps ought to have been pointed out since getting it wrong could be lethal. I speak as a retired safety test engineer for the British Standards Institute.

There are various different standards for complete equipment but they all require TWO levels of insulation between dangerous voltage and the operator. The two levels can be "basic" and earth, or "double" or "reinforced".

Note for the purposes of all standards, both Live and Neutral sides of the mains are considered as dangerous for two reasons: (a) the spikes referred to in the article which are with respect to earth and (b) there is the possibility of reversing the Live and Neutral as occurs with some continental wall plugs etc.

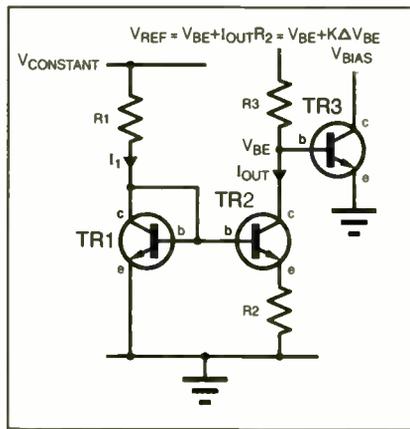


Fig.4. Concept circuit for bandgap reference.

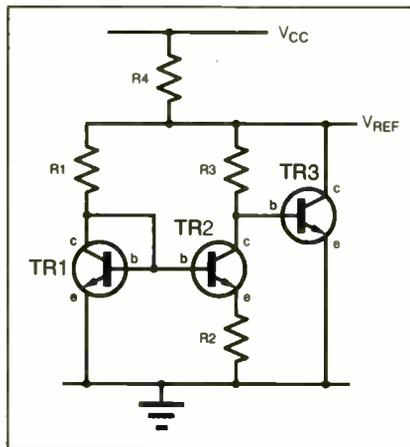


Fig.5. Practical circuit of Fig.4 – The Widlar Bandgap Reference.

or the two-pin "figure eight" type of mains power cord used on some appliances.

Now to the crux of the matter: a Y2 capacitor is only considered to be the equivalent of "basic" insulation. Thus it is suitable for use between mains and a safety earth because the safety earth provides the second level of protection in the event of failure. It is NOT suitable for use between mains and an unearthed ground or secondary circuit that may be touchable by the user.

Generally speaking it is safer to consider that any secondary circuitry or conductive parts will be touchable by the operator (though there are plenty of exceptions in these days of plastics), but in order to confirm it one has to have a detailed knowledge of the spacing requirements for the particular voltage. In any case it's safe to assume that your readers will have their fingers in the secondary circuit workings with the power on. After all that's why they read the magazine.

A number of switch-mode power supplies use Y capacitors between floating secondary circuits and the mains as an aid to suppressing interference or even to detect the presence of the mains. Since there is no safety earth, the requirement is for "double" or "reinforced" insulation. This requires the use of two equal Y2 capacitors in series, or one Y1 type.

Note that there is an earth leakage current flowing through these caps and in the case of using two Y2 caps, the current through a single one should not exceed the limit. The limit varies with the standard, medical standards being much more critical for instance.

However, for non-medical use in Class II equipment (Class II means no safety earth) the limit is normally 0.25mA. Thus one can do the sums of E / X_c and deduce a maximum value of Y capacitance for 250V 50Hz of about 3nF. Of course, putting two in series will halve the effective capacitance so a single Y1 cap may be preferable.

Roger Warrington C.Eng MIEE by email.

Thank you for filling us in with this technical information. As we mentioned previously, Y-Class capacitors are rated for direct connection to earth although they effectively bypass the mains insulation of the apparatus. X-Class capacitors are not permissible in that mode.

Clearly, it is difficult to cover this in any depth without reference to the lengthy technical standards, something that I feel goes beyond the remit of *Circuit Surgery*. Nevertheless, even though *EPE* is a hobbyist magazine, where relevant we do try to set a good example by applying standards used by experts. *ARW.*

More Supply Surprises

Back in April 2002 *Circuit Surgery* we recounted the tale, with hopefully a happy ending, of a reader who had purchased a Yaesu transceiver but couldn't locate a suitable Battery Charger for it. After talking to the manufacturers we suggested the RS 250-1397 basic charging unit. I then heard back from *George Jacobs* who writes:

I was ever so relieved to hear that my battery problem had been solved – thank you ever so much! I went along with your opinion and decided to buy the suggested power unit. However, when I rang RS Components they said they could not help me because they do not supply individual customers, only companies and business etc. That really flattened me. I have written twice to Yaesu but they have not replied. I may have to sell the Transceiver and buy another model instead.

I was dismayed to hear that you had been turned away when you tried to buy the recharger. Firstly for the benefit of readers in the USA and elsewhere, RS Components has nothing to do with the vendor you may know as Radio Shack (or Tandy). You will see RS Components part numbers quoted frequently in our constructional articles as well as in *Shoptalk*. RS Components (<http://rswww.com>) is a vast UK-based component supplier that over the years has built up an excellent reputation for delivering a high quality service to industry.




Even so, the information you received from RS Components was incorrect. A very apologetic RS advisor confirmed that although they are strictly speaking a "trade only" organisation they are still happy to deal with individuals on a credit card basis (only). They were keen to phone you to sort out your order.

Readers should note that the only other way to buy from RS is via their web site, which is what I do if I need an RS part in a hurry. I suggested you give RS another try, this time asking for the New Customer Reception department if you have any further problems. *ARW.*

Video Surveillance



- C-MOS B/W Camera 15mm/15mm £29.00
- C-MOS Colour Camera 15mm/15mm £65.00
- PCB B/W Camera 32mm/32mm £24.00
- PCB Colour Camera w/Audio 32mm/32mm £65.00
- 23cm (1.3GHz) Video/Audio Transmitter £35.00
- 13cm (2.4GHz) Video/Audio Transmitter £35.00
- 1.2 Watt 2.4GHz Video/Audio Transmitter £120.00
- 4" TFT Boxed Colour Monitor w/Audio £110.00
- Video to VGA Converter £65.00
- VGA to Video Converter £90.00
- External USB Video Capture Box £55.00

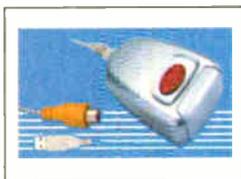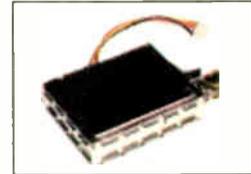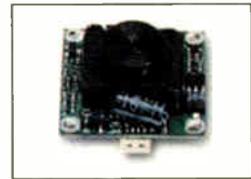

All prices exclude VAT.

Many more products on our website:

WWW.BITZTECHNOLOGY.COM

Tel: 01753 522 902 Fax: 01753 571 657

Wireless Remote Controls



RC-11
3 channels RC-11 Key fob
Control Transmitter with
Rolling Code technology.

RC-11 Price: £14.99



UC-216
3 channels receiver with 2 relays
output working from 9V to 12vdc
UC-216 with learning mode and
rolling code technology.

UC-216 9-12Vdc £29.00
UC-222 240 Vac £29.00

Also

- Wireless pager alarm PG-4W £125.00
- Wireless PIR alarm JA-60S £49.00
- Wireless door magnet alarm £39.00
- Wireless smoke alarm £49.00
- Wireless glass break alarm £49.00
- Wireless alarm control panel £99.00
- Wireless alarm control panel with digital /voice dialler £149.00

Distributors Welcome.

All prices exclude VAT and carriage. All transmitters are licence exempt working on 433.92Mhz. All transmitters work with rolling code technology.

Bitz Technology Ltd
sales@bitztechnology.com
+44 (0) 1753 522 902

PRACTICALLY SPEAKING

Robert Penfold looks at the Techniques of Actually Doing It!

It is generally conceived that it is the colour-coded components that should give the most identification problems to beginners at electronic project construction. However, once you have learnt the basic resistor colour code and one or two variations on it, there should be little difficulty in determining the value of any colour-coded component. Components that are marked with values or type numbers using letters and numbers should leave even less room for error, and each one should be exactly what it says on the casing.

Clear as Mud

It is clear from readers' letters that things are not as straightforward as this in practice. Readers having problems with a project often include descriptions of some of the components that they suspect of being the wrong thing. Semiconductors in general, and integrated circuits in particular, are probably the worst offenders when it comes to spurious markings. Even experienced project builders can sometimes take a while to sort out the "wheat from the chaff". Matters are certainly easier if you understand the fundamentals of semiconductor type numbers.

Understandably, most semiconductor manufacturers like their name or logo to be prominently displayed on their products. Virtually all integrated circuits carry a manufacturer's name such as "MAXIM" or (more usually) a logo - see Fig.1. One or other of these is often squeezed onto small semiconductors such as low-power transistors. These are usually easy to spot and should not give any major problems.

In addition to the name or logo of the manufacturer and the type number, most semiconductors usually have some additional letters and numbers.

Over the years there has been a tendency for the logos and additional markings to become more prominent at the expense of type numbers, etc. This can be very confusing for beginners, but the secret of success is to look for meaningful markings and ignore everything else.

The extraneous markings are usually just things like batch numbers, the date of manufacture in some obscure form, a code number indicating the particular factory where the component was made, and things of this general type. They are, of course, of no relevance to the project builder.

The secret of success with component markings is to avoid panicking if you are faced with a jumble of digits,

and look for something that could be a type number or value. Things like batch numbers are usually in a form that avoids them being easily confused with type numbers or values.

It helps to bear in mind that the convention with integrated circuits is for the type number to be given first, followed by any batch number, etc. Hence the eight-pin device shown in Fig.1 is an NE602AN and not an FSH4930 or 9501nA. Similarly, the 16-pin device is a MAX232CPE and not a 9450N. Unfortunately, the same convention is not used with capacitors and most other components.

Numbers Up

Even if you manage to ignore the spurious markings, there can still be problems with the type number or value. Integrated circuits are undoubtedly the worst offenders, since the same chip can be sold under different

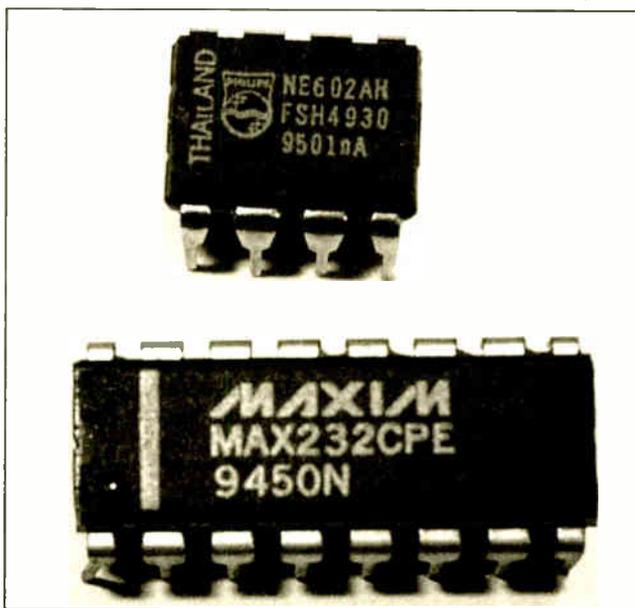


Fig.1. The markings on integrated circuits usually include a lot of "excess baggage".

type numbers. In general, the basic type number is the same, but it is preceded by the manufacturer's code letters and followed by a suffix that denotes the case style.

Having several manufacturers producing the same chip might seem a little odd, but equipment producers do not like being tied to a single source for components. Having a second source of supply, or even several sources, makes a component more marketable.

Unfortunately, it also results in the same component being marketed under several slightly different type numbers. Provided you obtain the correct chip, it should not matter which particular manufacturer it was produced by.

Not all integrated circuits are available with multiple prefixes. Some devices are only produced by one manufacturer, and this is particularly common with the more specialised types. Others are produced under the same type number regardless of which company actually made the device. The "NE" suffix for the eight-pin chip in Fig.1 suggests it was made by Signetics, but the logo clearly indicates that it was made by Philips.

Logic

The devices that are most likely to have a variety of prefixes are the popular operational amplifiers and logic devices, both of which are commonly used in projects for the home constructor. In components lists it is normal for only the basic type number to be specified, or perhaps the basic type number plus a suffix.

With the 4000 series CMOS logic devices for example, a type number such as 4066BE might be specified. Here "4066" is the basic type number, and "BE" is the suffix. The same method of identification is often used in component catalogues, with no particular manufacturer being mentioned.

Some of the very large suppliers do offer devices from a specific manufacturer, and may even offer a choice of manufacturers in some cases. Where there is a choice, simply opt for whichever one is the cheaper.

There is a further complication with the 74** series TTL logic devices, because various families of improved chips have been introduced over the years. The original devices had basic type numbers that started with "74" and then had a two or three digit number (e.g. 74245).

The original TTL logic integrated circuits are now largely obsolete. Later logic families are identified by adding two or three letters after the "74" part of the type number. These are the identification letters for some common TTL logic families:

HC	high-speed CMOS (e.g. 74HC02)
HCT	high-speed CMOS using normal TTL logic levels (e.g. 74HCT02)
LS	low-power Schottky (e.g. 74LS02)
LCX	low-voltage and high speed (e.g. 74LCX02)
LVX	low-noise, low current and high-speed (e.g. 74LVX02)

There have been many other TTL logic families, but these have not stood the test of time and you are unlikely to encounter them. It is the first three in the list that are most commonly used in EPE projects.

In general, compatibility between various TTL logic groups is not very good. They have different supply voltage ranges, logic voltage requirements, drive currents, and input currents. Some are more tolerant of supply noise than others.

Unless you are sure you know what you are doing it is definitely not a good idea to use a device from the wrong logic family. A substitute of this type will sometimes work, but it is more likely to fail. There is also a risk of the supply voltage being inappropriate for the substitute device, which could result in it being damaged.

Tail Piece

On the face of it, the suffix is more crucial than the prefix. These days most integrated circuits are available in a variety of case styles, but only the dual in-line (d.i.l.) variety is normally used in do-it-yourself projects. In practice there is less than total uniformity in the suffixes, so what appears to be the wrong suffix can appear on a perfectly suitable device. On the other hand, an increasing range of surface-mount devices is listed in most component catalogues, so you have to be careful to order the right type.

The original 4000 CMOS devices had an "AE" suffix, but the improved "B" series devices that are still in use today and have a "BE" suffix superseded these. The "E" simply means that the device is in a plastic d.i.l. encapsulation.

A few devices are available with a "UBE" suffix, and the "U" stands for unbuffered. The "UBE" version should always be used if it is specified in a components list, but the standard "BE" variety should otherwise be used.

An "E" in a suffix is not the only letter used to indicate a plastic d.i.l. encapsulation. Both "P" and "N" are commonly used to indicate this type of encapsulation, and there are further variants such as "G" or "H". There are often two or three letters in the suffix, and some manufacturers seem to use one letter to denote the case material (plastic or ceramic) and another to indicate the pinout configuration. More commonly an additional letter is used to indicate whether the device is a commercial grade component or a higher-grade type such as an industrial or military type.

Most EPE projects normally require the "bog standard" commercial variety and these normally have "C" in the suffix. Higher-grade devices should work perfectly well if used instead of a standard commercial grade component, since they are all basically the same chip. The superior versions have wider operating temperature ranges, and may be superior in other respects.

Euro ICs

Some integrated circuits have European type numbers, and these start with a "T" followed by two letters, a serial

number, and a suffix letter (e.g. TBA820M). Devices of this type have the same type number regardless of the manufacturer concerned, so it is important to obtain a component that has precisely the right type number. It is otherwise virtually certain that you will obtain completely the wrong device, or the right chip but in the wrong encapsulation.

Transistors and Diodes

Transistors and diodes do not have the same type number variations as integrated circuits. The prefix does not usually indicate the manufacturer, although there are some exceptions such as the "TI" and "TIL" prefix used by Texas Instruments.

Devices having European codes start with two letters that indicate the semiconductor material used and the type of component, as detailed below:

First Letter	Meaning
A	Germanium
B	Silicon
C	Gallium Arsenide
R	Compound materials
Second Letter	Meaning
A	Small signal diode
B	Rectifier or variable capacitance diode
C	Small signal audio transistor
D	Power transistor
E	Point contact diode
F	Low power high frequency transistor
K	Hall-effect device
L	High frequency power transistor
N	Opto-isolator
P	Photo diode
Q	LED
T	Thyristor or triac
U	High-voltage transistor
X	Rectifier
Y	High-power rectifier
Z	Zener diode

A BC109 for example, is therefore a small silicon transistor for audio use. The number is simply a serial type, starting from 100.

American semiconductors have a "1N", "2N", or "3N" prefix. The number is one less than the number of leads the device has, so diodes and rectifiers have 1N*** type numbers, and transistors mostly have 2N*** type numbers. A few transistors have four leads and a 3N*** type number. Again, the number following the suffix is a serial type.

Devices having Japanese Industry Standard (JIS) type numbers are occasionally used in EPE projects. These start with a number that indicates the number of leads in the same way as the American system. The next digit is always an "S", and the third digit indicates the type of component using a code letter ("D" for a low-frequency npn transistor for example). This is followed by the usual serial number.

One slightly confusing aspect of Japanese type numbers is that the first two digits are often absent from the actual components. A "2SC646" for example, would probably just be

marked "C646". Fig.2 shows two more examples. Since the first two digits are of little practical value, their absence is of no real importance.

Transistor Suffixes

Clearly, small semiconductors have rigidly standardised type numbers and there is not the "free-for-all" associated with integrated circuits. The only variations are in the suffixes applied to some transistors.

With the American devices there is sometimes an "A" on the end of the type number, and this is used to indicate that the device concerned is an improved version of the basic device. The original and improved versions are effectively two different devices and it is not a good idea to use one in place of the other.

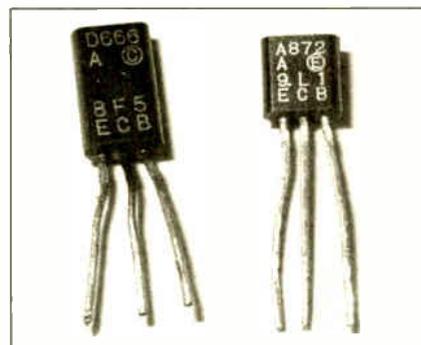


Fig.2. The device on the left is a 2SD666A and the one on the right is a 2SA872A

A more common variation is where a suffix letter is added to a European transistor type number. This letter indicates that the device is in a particular gain group, as follows:

Letter	Gain Range
A	110 to 220
B	220 to 450
C	420 to 800


If no suffix is given in a components list it does not matter which gain group you use, and it is also all right to use a device that lacks the suffix. Where a particular gain group is specified it will usually be the highest ("C" suffix) group. It is quite likely that the project will not work properly if you use a transistor from the wrong gain group or one that is not graded.

A few American devices, and the 2N2926 in particular, use coloured spots on the device to indicate its gain group. This method is based on the resistor colour code, with brown representing the lowest gain group, and red, orange, yellow, etc., representing progressively higher gain ranges. Again, if a particular colour is specified it is important to use a device from the correct gain group.

Colour coding is little used with semiconductors, but there are some American diodes that use a variation on the resistor colour code to indicate the serial number. For example, a 1N914 diode would have white, brown, and yellow bands to respectively indicate the 9, 1, and 4 part of the type number. No multiplier band is used with this system. There should be no difficulty with this type of coding provided you know the resistor colour code.

EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS


ELECTRONICS PROJECTS

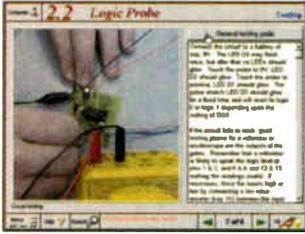

Logic Probe testing

Electronic Projects is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included. The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.


ELECTRONICS CAD PACK

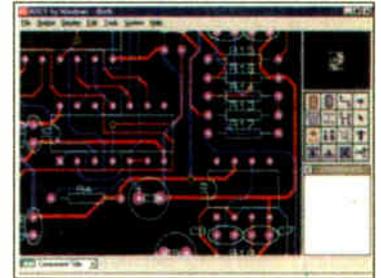

PCB Layout

Electronics CADPACK allows users to design complex circuit schematics, to view circuit animations using a unique SPICE-based simulation tool, and to design printed circuit boards. CADPACK is made up of three separate software modules. (These are restricted versions of the full Labcenter software.) **ISIS Lite** which provides full schematic drawing features including full control of drawing appearance, automatic wire routing, and over 6,000 parts. **PROSPICE Lite** (integrated into ISIS Lite) which uses unique animation to show the operation of any circuit with mouse-operated switches, pots, etc. The animation is compiled using a full mixed mode SPICE simulator. **ARES Lite** PCB layout software allows professional quality PCBs to be designed and includes advanced features such as 16-layer boards, SMT components, and an autorouter operating on user generated Net Lists.


ELECTRONIC CIRCUITS & COMPONENTS V2.0

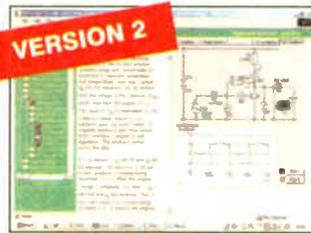

Circuit simulation screen

Provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals:** units & multiples, electricity, electric circuits, alternating circuits. **Passive Components:** resistors, capacitors, inductors, transformers. **Semiconductors:** diodes, transistors, op.amps, logic gates. **Passive Circuits. Active Circuits. The Parts Gallery** will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.

ANALOGUE ELECTRONICS

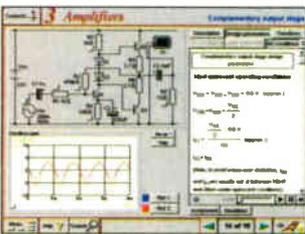

Complimentary output stage

Analogue Electronics is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits. Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections), **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections). **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections). **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

NEW ROBOTICS & MECHATRONICS




Case study of the Milford Instruments Spider

Robotics and Mechatronics is designed to enable hobbyists/students with little previous experience of electronics to design and build electromechanical systems. The CD-ROM deals with all aspects of robotics from the control systems used, the transducers available, motors/actuators and the circuits to drive them. Full case study material (including the NASA Mars Rover, the Milford Spider and the Furby) is used to show how practical robotic systems are designed. The result is a highly stimulating resource that will make learning, and building robotics and mechatronic systems easier. The Institutional versions have additional worksheets and multiple choice questions.

- Interactive Virtual Laboratories
- Little previous knowledge required
- Mathematics is kept to a minimum and all calculations are explained
- Clear circuit simulations


DIGITAL ELECTRONICS V2.0

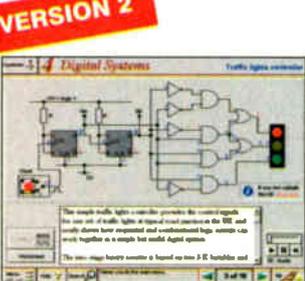

Virtual laboratory – Traffic Lights

Digital Electronics builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (opposite), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen. Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units. Sections on Boolean Logic and Venn diagrams, displays and chip types have been expanded in Version 2 and new sections include shift registers, digital fault finding, programmable logic controllers, and microcontrollers and microprocessors. The Institutional versions now also include several types of assessment for supervisors, including worksheets, multiple choice tests, fault finding exercises and examination questions.

FILTERS

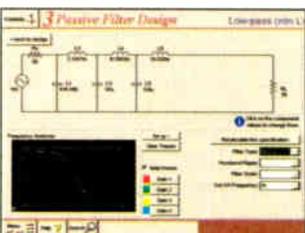

Filter synthesis

Filters is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev op.amp filters.

PRICES

Prices for each of the CD-ROMs above are:

(Order form on third page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student£45 inc VAT
 Institutional (Schools/HE/FE/Industry).....£99 plus VAT
 Institutional 10 user (Network Licence)£199 plus VAT
 Site Licence.....£499 plus VAT

PICmicro TUTORIALS AND PROGRAMMING


HARDWARE

VERSION 2 PICmicro MCU DEVELOPMENT BOARD

Suitable for use with the three software packages listed below.

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 13 individual I.e.d.s, quad 7-segment display and alphanumeric I.c.d. display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- All inputs and outputs available on screw terminal connectors for easy connection

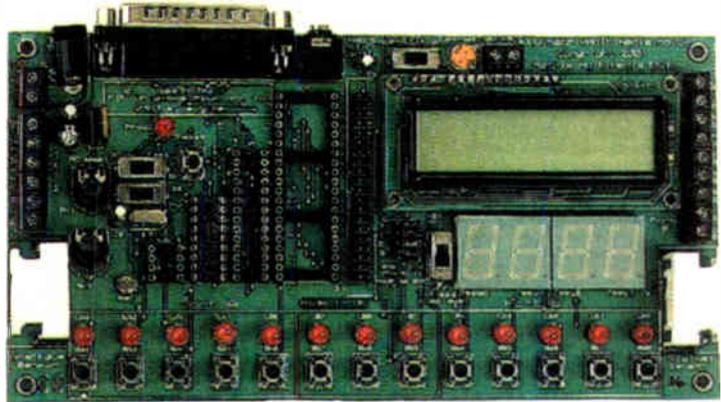

£145 including VAT and postage
12V 500mA plug-top PSU (UK plug) £7
25-way 'D' type connecting cable £5




SOFTWARE

Suitable for use with the Development Board shown above.

ASSEMBLY FOR PICmicro V2 (Formerly PICTutor)

Assembly for PICmicro microcontrollers V2.0 (previously known as PICTutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes. The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller. This is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed which enhances understanding.

- Comprehensive instruction through 39 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.

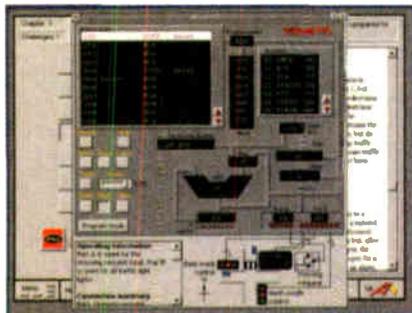


Virtual PICmicro

'C' FOR PICmicro VERSION 2

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

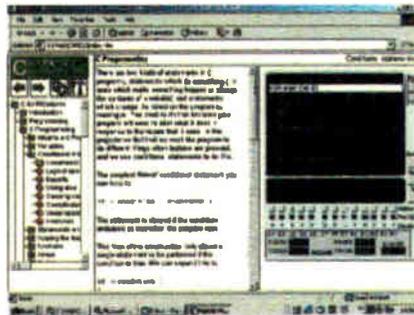- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running Windows 95, 98, NT, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.


FLOWCODE FOR PICmicro

Flowcode is a very high level language programming system for PICmicro microcontrollers based on flowcharts. Flowcode allows you to design and simulate complex robotics and control systems in a matter of minutes.

Flowcode is a powerful language that uses macros to facilitate the control of complex devices like 7-segment displays, motor controllers and I.c.d. displays. The use of macros allows you to control these electronic devices without getting bogged down in understanding the programming involved.

Flowcode produces MPASM code which is compatible with virtually all PICmicro programmers. When used in conjunction with the Version 2 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols (ISO5807)
- Full on-screen simulation allows debugging and speeds up the development process
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 8, 18, 28 and 40-pin devices
- Institutional versions include virtual systems (burglar alarms, car parks etc.).

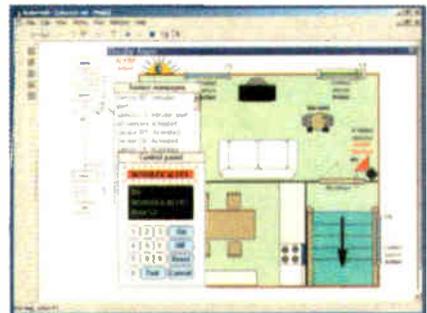

Burglar Alarm Simulation

PRICES

Prices for each of the CD-ROMs above are:

(Order form on next page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student
 Institutional (Schools/HE/FE/Industry)
 Flowcode Institutional
 Institutional 10 user (Network Licence)
 Site Licence

£45 inc VAT
 £99 plus VAT
 £70 plus VAT
 £249 plus VAT
 £599 plus VAT


TEACH-IN 2000 – LEARN ELECTRONICS WITH EPE

EPE's own *Teach-In* CD-ROM, contains the full 12-part *Teach-In* series by John Becker in PDF form plus the *Teach-In* interactive software covering all aspects of the series. We have also added Alan Winstanley's highly acclaimed *Basic Soldering Guide* which is fully illustrated and which also includes *Desoldering*. The *Teach-In* series covers: Colour Codes and Resistors, Capacitors, Potentiometers, Sensor Resistors, Ohm's Law, Diodes and L.E.D.s, Waveforms, Frequency and Time, Logic Gates, Binary and Hex Logic, Op.amps, Comparators, Mixers, Audio and Sensor Amplifiers, Transistors, Transformers and Rectifiers, Voltage Regulation, Integration, Differentiation, 7-segment Displays, L.C.D.s, Digital-to-Analogue.

Each part has an associated practical section and the series includes a simple PC interface so you can use your PC as a basic oscilloscope with the various circuits. **A hands-on approach to electronics with numerous breadboard circuits to try out.**

£12.45 including VAT and postage. Requires Adobe Acrobat (available free from the Internet – www.adobe.com/acrobat).

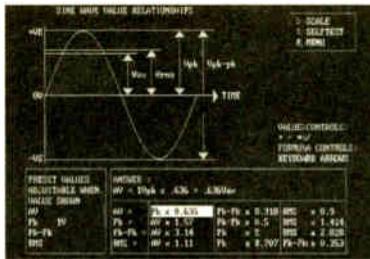
FREE WITH EACH TEACH-IN CD-ROM – *Electronics Hobbyist Compendium* 80-page book by Robert Penfold. Covers Tools For The Job; Component Testing; Oscilloscope Basics.



SURFING THE INTERNET

NET WORK

ALAN WINSTANLEY

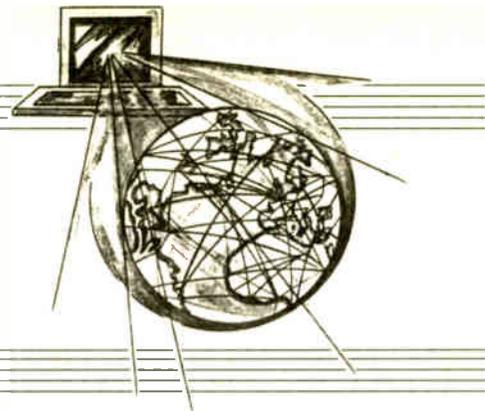

A Fistful of Dollars

WELCOME to *Net Work*, our column written for Internet users. As regular readers will know, ever since its beta days Google (www.google.com) has been my preferred search engine for hunting down elusive information on the Internet. It is a "pure" search engine that runs on a whole farm of computers and it returns results almost instantaneously.

Compare this with Yahoo! (www.yahoo.com), one of the world's most popular directories: while Google searches the Internet, Yahoo! searches its own database of web sites instead, which it has organised in a highly structured manner. The same is true of the popular Open Directory Project, the largest human-edited directory on the web at www.dmoz.org. Web sites are included in the Yahoo! directory only with the permission of Yahoo! editors, and it's an expensive affair: new business entries pay \$299 per year to have their web site listed in Yahoo! Entry into the ODP is free.

If you search Yahoo! but fail to find a result in its directory, Yahoo! will politely offer you more results gleaned from the rest of the Internet courtesy of... Google. This is typical of the way in which major search engine databases are used to feed results into other web sites such as AOL. Click the Directory tab on Google and you will see the similarity to the ODP.

For a Few Dollars More

This month I highlight some other useful search tools that Google has to offer. Not only can Google search web pages but it can also hunt down *images*: simply click the Images tab on the Google main page then enter a search phrase. Google Images will return thumbnails of all the relevant images it finds on the web. (It is not quite clear why a microscopic close-up of a creepy crawly should appear under a listing of CMOS chip, but there you are.)

Stuck for an answer to something? Google Answers is a new beta development whereby you can actually commission a little research to help you answer a thorny problem. Presently, Google Answers is hosted at <https://answers.google.com/answers/main>. For a small fee (you decide how much) Google researchers promise to supply a paragraph or more of information that answers your question as well as links to websites that can provide more material.

The more you bid, the quicker the reply is likely to be, and the more research that is needed, the more you should offer to pay. You could even apply online to be a Google researcher yourself, though you shouldn't book an exotic holiday on the prospect of any rich rewards.

Some interesting new developments from Google are presently on show at <http://labs.google.com>. The most interesting one for *EPE* readers will be the new Google Glossary: just type in an obscure acronym or phrase and Google will seek out a definition on the web.

A test for typical electronics terms including *TTL*, *mcu*, *vlsi* and *CMOS* rapidly returned definitions together with a corresponding lists of web sites. Google Glossary is not America-centric either: it immediately defined HMCE (Her Majesty's Customs and Excise) and DVLA (the UK's Driver and Vehicle Licencing Authority) with

its usual speed. Voice-controlled searches by phone are also on the cards.

Other tools under development include Google Sets, an interesting attempt to return "sets" of terms that relate to a number of words or phrases that you enter. This can be great fun to play with.

In the News

One of the most important search functions provided is Google News (<http://news.google.com>). This searches their entire archive of Usenet, including those it inherited from Deja News. This is a priceless information resource that all readers should become familiar with. It works extremely well and runs directly in your web browser as an online newsreader.

Still on the subject of Usenet archives, there is a fascinating archive of the last twenty years of Usenet posts at http://www.google.com/googlegroups/archive_announce_20.html. Read about the first mention of Microsoft (May 1981), the first fax machine in February 1983, and the first mention of Tim Berners-Lee's "world wide web" project (August 1991). On the 30 March 1998 we see the first mention of Google itself, which has since evolved from the Stanford University mathematical model into today's indispensable research tool.

Lastly, if you are at all keen on using the Internet for research you

should download the extremely handy web browser toolbar from Google, which runs in Windows and needs Microsoft Internet Explorer version 5 or later.


Tiscali 10.0

Despairing of spiralling phone bills and resigned to the fact that broadband access will not arrive in the neighbourhood any day now, I finally ditched a LineOne (now Tiscali) Surftime tariff which was paid for with the quarterly phone account. I signed up for a FRIACO account (flat rate internet access call origination – i.e. an unmetered connection) with Tiscali instead. This offers a £14.99 fixed price service with no minimum call charge and unlimited access with a two-hour cut-off.

Tiscali's heavily advertised "10.0" package – the "great new service that gives you instant access to our key products" – is just a consolidation of some ISP portal offerings of dial up access, web space, mail, text messaging and more. Bundle ten services together, add some lifestyle-type TV advertising marketing and you get a trendy new account that, in my case, took a whole afternoon to set up, and suffered from incomprehensible error messages on the web site that needed several support calls at 50p/minute to resolve. This in turn cancelled out any likely savings for the first month.

In practice, access is not always proving that reliable, especially after dark, but overall it is quite workable. Remember that whichever ISP you dial up through, you will usually be using their SMTP servers for your outgoing mail. I was quite shocked to suffer lengthy delays (several days) due to a broken mail server, which made communications very garbled at times and made it more efficient to actually write a letter.

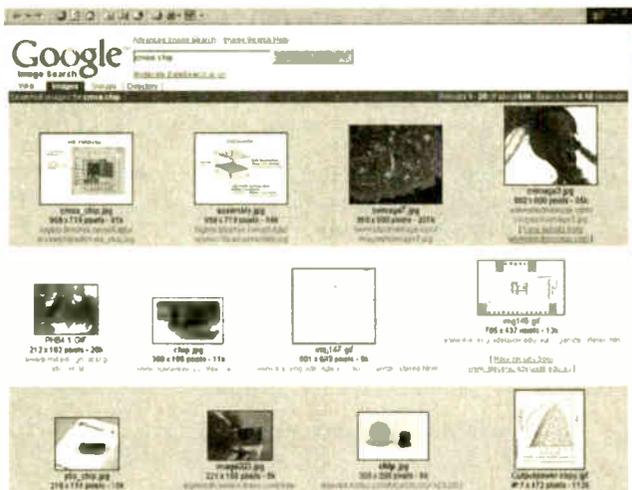See you next month for more *Net Work*. You can reach the author by email at alan@epemag.co.uk.




Google's Image Search will find and display a gallery of images that are published on the world wide web.

TEACH-IN 2002

Part Nine – Analogue-to-Digital Conversion, Sampling and Nuclear Radiation Sensing

IAN BELL AND DAVE CHESMORE

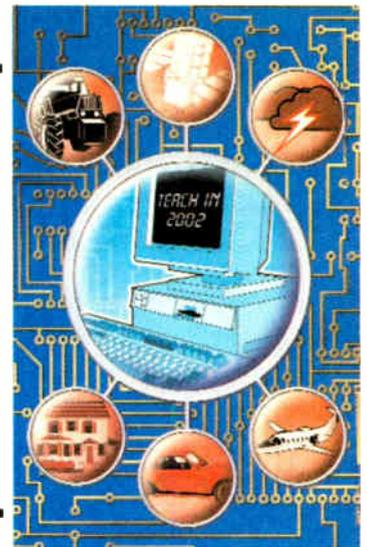

Making Sense of the Real World: Electronics to Measure the Environment

GOING DIGITAL

THE main aim of this series has been to look in depth at sensors and the circuitry connected directly to them. However, apart from their use in very basic measurement instruments, sensors are usually part of larger systems where their signals are interpreted or processed in some form of computer or other complex digital circuit.

For *EPE* readers, the PIC microcontroller is likely to form the heart of many sensor-based systems, but in general, a large range of microcontrollers, PCs, DSPs (digital signal processors) and custom designed integrated circuits are used to process sensor data.

We will not be covering PIC programming or PIC interfacing in this series, but this month we look at the fundamental issues involved in converting sensor data from analogue to digital (A-to-D) form. As usual we will be looking at some sensors and this month it is the turn of nuclear radiation sensing. Since it is difficult to design labs for nuclear radiation sensing, we will be looking at analogue-to-digital conversion, problems and solutions.

WHY GO DIGITAL?

Up to now, nearly all of our circuits have been analogue in nature, so why change to digital? There are several reasons why digital signals are better than analogue:

- Digital signals are better for transmitting down long cables since an analogue signal is degraded due to the wire's resistance and the addition of noise. So, at the end of the wire, the analogue signal's SNR (signal-to-noise ratio) is lower. A digital signal also has a lower SNR but as long as it can still be detected as a logic 1 (high voltage), it can be reconstructed – a method known as **regeneration**. This becomes important when very long cables are used, such as undersea telephone cables for example.
- Digital signals can be processed many ways in microcontrollers and specialized **digital signal processors (DSPs)** when the equivalent analogue circuits would be extremely complex. Just think how

many op.amps would be needed for a low-pass filter with a roll-off of 240dB per octave – at one op.amp per 24dB, we would need 10 op.amps plus 40 resistors and 20 capacitors! It is possible to implement such a filter in digital form using arithmetic on a DSP.

- Digital signals can be stored in memory whereas analogue signals cannot easily be stored unless on tape.
- Digital signals can be **encrypted** against interception and in theory can be made totally secure. Analogue signals can only be **scrambled**, i.e. the spectrum and/or the time domain waveform is mixed up and reconstructed when received. Scrambling is not secure since many of the signal's characteristics (e.g. speech) are preserved and it is relatively easy to unscramble.

Digital signals are not always good, though, especially if we are going to transmit them over, for example, radio because they need a much wider bandwidth than the original analogue signal. This so-called **bandwidth expansion** can be such that it is not always possible to use digital transmission. We will illustrate this later when we have introduced the concepts needed.

SMART AND INTELLIGENT SENSORS

Up to now, we have been looking at sensors separately from associated circuitry such as linearising and amplifying circuits. Advances in technology, particularly in integrated circuit fabrication, provide us with the ability to include most if not all signal conditioning circuitry on the same piece of silicon as the sensor. Such devices are called **integrated sensors** and we have already used some of these – TSL250 photodiode and integrated amplifier and LM35 temperature sensor are two examples.

We can go further and add a microcontroller creating a so-called **smart sensor**. This allows much more functionality including:

- data logging – storing values in memory at intervals

- digital signal processing such as filtering, calculating averages, maximum and minimum values, transforming data into meaningful units, e.g. voltage from a temperature sensor into degrees Celsius; transmitting data, e.g. RS-232 or formatting data for a printer, display, etc.

All this requires us to convert voltages, currents, etc. into a digital form, i.e. using an A-to-D converter. We can go one stage further and add "intelligence" to create **intelligent sensors**. By *intelligence* we mean artificial intelligence such as expert systems or artificial neural networks.

These allow the intelligent sensor to perform tasks that normal microcontrollers cannot. Examples include detecting and sometimes "repairing" (or ignoring) faults in sensors, performing difficult signal analysis and actually recognizing different signals. We will be discussing intelligent sensors next month.

ANY NUMBER YOU LIKE?

A numerical value held in a digital circuit consists of a binary number with a fixed number of digits (bits). For example, if we have eight bits we can have binary numbers ranging from 00000000 to 11111111 (0 to 255) in decimal.

We have a specific maximum and minimum value (0 and 255 in this case), and we also have a finite number of possible different values (256 in this case). This limits the step size in moving from one possible value to the next, for example, starting at two the next possible value is three.

Compare this with an analogue signal. We would also usually have a fixed maximum and minimum, possibly set by the supply voltage or the characteristics of a sensor, but the number of possible values is effectively infinite.

For example, starting at 2.0V we could step to 2.1V, 2.01V, 2.001V, 2.0001V and so on. There are practical limits, of course, due to how small a step we could either control or detect, but from the perspective of an ideal circuit the number of possible analogue values is infinite, whereas even for an ideal digital circuit it is specifically limited.

The mapping of an infinite range of analogue values onto the limited number of digital values is called **quantisation**. A circuit called an **Analogue-to-Digital Converter (ADC)** is used to obtain the digital representation of an analogue signal.

ADCs come in many types and forms; they are available as individual i.c.s but are also built into some microcontrollers. To convert a digital signal to analogue we use a **Digital-to-Analogue Converter (DAC)**. Similarly, these have a variety of forms and may be built into microcontrollers.

We stated earlier that an 8-bit binary number gives us a range of 0 to 255. Does this mean that it would only be useful for a signal of 0V to 255V? The answer is *no* because we can **scale** the range of values represented by the binary number in any way we like. A range of 0 to 255 could represent 0V to 255mV in 1mV steps, 0V to 1V in 3.91mV steps, 0 to 1.02V in 4mV steps, 10V to 25V in 0.0588V steps, -3.55V to -1V in 0.01V steps, and so on. Note that the **span** of the signal represented by the binary number does not have to start at 0V.

We can also represent both negative and positive numbers using our binary digits. The simplest way is to designate one of the bits as the sign (e.g. 0 for positive, 1 for negative) and use the remaining bits for the numerical value. For eight bits this would give a range of -127 to +127, which again could be scaled to represent any actual range of voltages or currents.

Other ways of representing negative numbers in digital circuits and computers are in use (such as two's complement), but a discussion of these is outside the scope of this series.

As this series is mainly concerned with getting data from sensors we will look at the ADC in detail, however similar concepts (such as resolution) apply to DACs.

ADC CHARACTERISTICS

In Fig.9.1 are shown a schematic symbol of an ADC and the signals typically associated with it. There is the analogue input, the *n*-bit digital output, a reference voltage (which may be fixed for some ADCs), and a clock or "start conversion" control (which may not always be present).

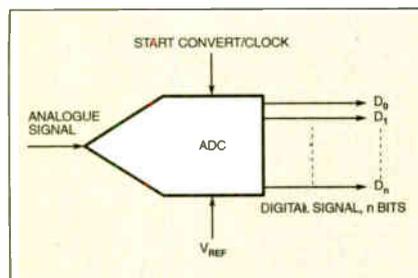


Fig.9.1. Signals associated with an ADC.

The example shows parallel digital output, but some converters output the digital data in serial form. The ADC converts the range of voltages between 0V and the reference voltage, V_{REF} , known as the **full scale range (FSR)** into a binary number 0 to $2^n - 1$.

Obtaining an accurate, stable (with time and temperature), and low noise voltage reference is quite difficult, but fortunately

such references are often built in to ADC chips. If not, separate voltage reference i.c.s are available for this purpose.

Output codes other than binary (e.g. Gray code) are used by some ADCs, but we will only consider binary converters. To change the scaling of input voltage to output code, V_{REF} can be changed within limits specified for the ADC.

To change the span of voltages converted, shifting the converted range away from starting at 0, or to change the scaling beyond that controllable via V_{REF} , requires external level shifting, gain or attenuation circuitry (e.g. using the shift and amplify circuits described in *Teach-In 2002* Parts 2 and 3).

The binary output has *n* bits labelled D_0 through to D_n . D_0 represents the units column of the binary number and is called the **Least Significant Bit (LSB)**. D_n represents the two-to-the-power-*n* column of the binary number (e.g. for eight bits this would be the 2^7 s or 128s column).

D_n is called the **Most Significant Bit (MSB)**. The binary number output by the ADC changes by one (that is, by an LSB) for an input voltage change of $V_{REF}/2^n$. This voltage is also referred to as an LSB.

The dynamic range of the ADC indicates the difference between the largest and smallest output code and is given by the ratio of FSR to LSB and is equal to 2^n . Expressed in decibels it is approximately $6n$ dB. Example dynamic range figures are given in Table 9.1.

Table 9.1 – ADC resolution

Number of bits (n)	Number of Levels (2^n)	Dynamic Range/dB	Resolution/%
3	8	18	12.5
4	16	24	6.3
8	255	48	0.4
10	1024	60	0.98
12	4096	72	0.0224
16	65536	96	0.0015
20	1048576	120	0.00010

In some applications, such as sound processing (voice, music, etc.), dynamic range is particularly important. The perceived (by humans) dynamic range can be improved by using a non-linear conversion characteristic.

The **resolution** of an ADC, which determines the smallest analogue change which it can distinguish with respect to its range, is specified by the number of bits, or by the percentage of full scale that the LSB represents. Resolutions as a percentage of full scale for various numbers of bits are also given in Table 9.1.

It is instructive to compare these resolutions with the accuracy available from sensors and their associated analogue circuits. For example, there would be little point in using a 16-bit converter with a sensor and measurement circuit which had an inherent (and acceptable) accuracy of two percent.

In Fig.9.2 is shown the output of an ideal 3-bit ADC plotted against the input voltage.

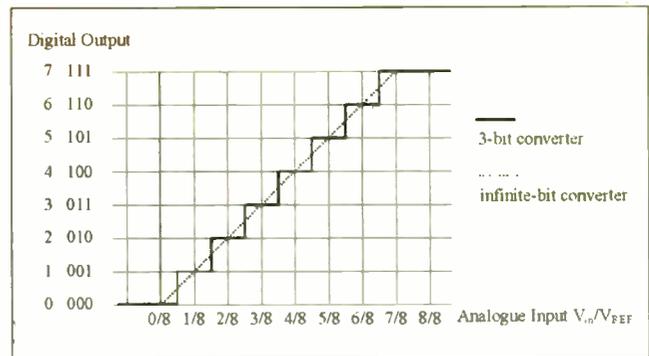


Fig.9.2. Input-Output characteristics of a 3-bit DAC.

The graph also shows the output characteristic of a converter with infinite resolution (dotted line). The difference between the actual characteristic and the infinite resolution characteristic is known as the **quantization error**, and results in **quantization noise** in the digital representation of the signal.

SAMPLING

So far we have only considered the voltage response of the ADC, but we also need to look at the time and frequency aspects of converters. ADCs take a finite time to convert an analogue voltage to digital form, this means that there is a finite number of conversions per second – this is the **sampling frequency**.

There is a very important rule that states that we **must sample a waveform at a rate of at least twice the highest frequency in the waveform**. If we fail to do this, the sampled waveform will be a distorted and inaccurate representation of the original – in the worse cases the sampled waveform may end up completely different from the original.

The rule is known as the **Nyquist criterion** (or **sampling theorem**) and the process by which distortion occurs due to inadequate sampling is called **aliasing**. The minimum sampling frequency of twice the signal frequency is known as the **Nyquist rate**. Later we do a

Lab experiment to illustrate this.

The illustration in Fig.9.3 shows an analogue waveform and three sampled versions of the waveform at different sampling rates. Waveforms (b) to (d) are obtained using a **sample and hold circuit**, which would form part of an ADC. In an ADC it is the **stable** value from the sample and hold output that is converted to digital form.

The signals in Fig.9.3 are all analogue in nature, they are not digital codes. The flat (held) parts of waveforms (b) to (d) can still take an infinite number of possible levels. Signals like this – which are analogue in terms of levels, but which only change value at specific points in time – are called **discrete time analogue signals**, the usual analogue signal (as in Fig.9.3a) is referred to as a **continuous time analogue signal**.

There are some types of circuit that directly process discrete time analogue

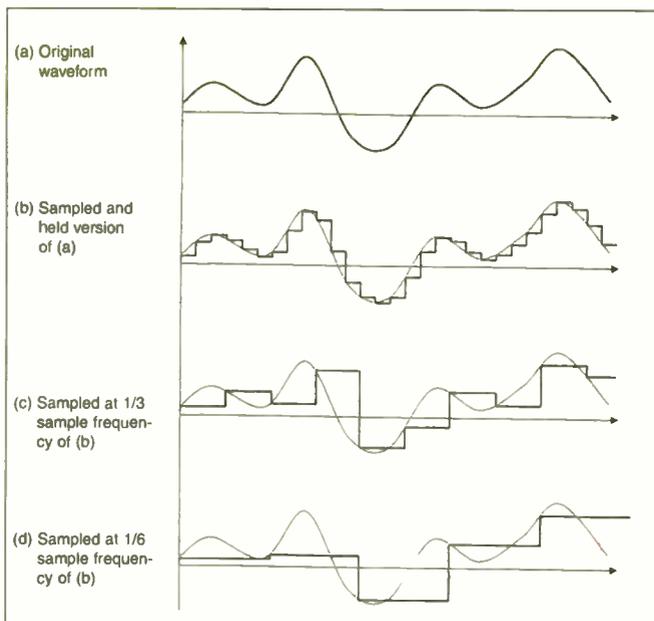


Fig.9.3. Example of the effect of sampling frequency.

signals. Perhaps the most well-known of these are **switched capacitor** circuits, which have several important uses, including filters.

Returning to the Nyquist sampling theorem, and looking at Fig.9.3, we conclude that waveform (b) is at a reasonable sampling rate – you can see that it resembles the original. Waveform (c) is either two slow or very close to the minimum sample rate. Waveform (d) is definitely too slow – the sampled waveform bears little resemblance to the original.

If we only dealt with sinewaves it would be easy to ensure that we were sampling at the Nyquist rate, but real signals are complex and have a spectrum of frequencies present in them – and we may not always be sure exactly what to expect.

In order to make sure that aliasing cannot lead to distortion of a converted waveform when using an ADC, we often need to filter the signal to remove all frequencies above half the ADC conversion rate. A low pass filter, preferably with a nice sharp cut-off and minimal pass-band distortion, is typically required (see last month for information on filters).

Although we are concentrating on ADCs it is worth noting that the analogue signal obtained directly from a DAC would look something like Fig.9.3b. In order to obtain a smooth continuous time analogue signal the DAC output is filtered using a low pass filter with a cutoff at half the sample frequency. This would restore (b) to the form shown in (a).


NYQUIST FORMULA

The Nyquist sampling criterion is written mathematically as:

$$f_S \geq 2f_{MAX}$$

where f_{MAX} is the maximum frequency in the signal. As we mentioned earlier, this is an extremely important concept and needs more explanation. Fig.9.4 shows three identical sinewaves sampled at exactly $2f_{MAX}$, $1.5f_{MAX}$ and f_{MAX} . The sampling points are denoted by the vertical lines and the dots.

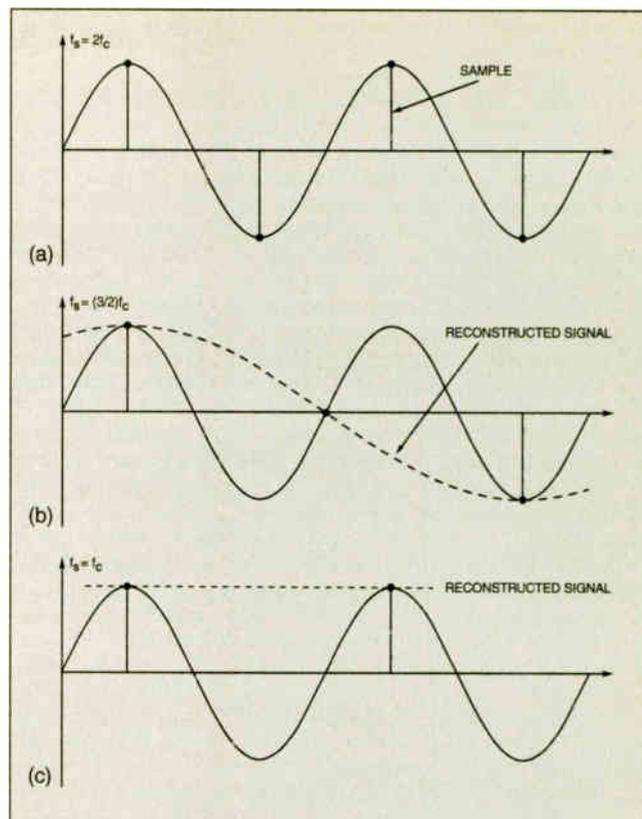If we try to reconstruct the signal by putting the sampled signals through a low



Right: Fig.9.4. Illustration of aliasing.

pass filter then we can see that in (a), the signal can be reconstructed successfully but in (b) we get a lower frequency. In the worst case, when $f_S = f_{MAX}$ we get a d.c. signal!

We can look at this another way by examining what happens in the frequency domain. Fig.9.5a shows an amplitude-versus-frequency graph for a signal with energy present up to f_{MAX} . Note that we have *negative* frequencies to $-f_{MAX}$ – don't worry about this, it is a consequence of the mathematics!

When we sample this signal, we get a graph like that in Fig.9.5b which is a repeated (to infinity) series of spectra centred at $\pm f_S, \pm 2f_S, \pm 3f_S, \pm 4f_S$, etc. Now, if f_S is greater than $2f_{MAX}$ the spectra are separated, but if f_S is smaller, the spectra overlap (Fig.9.5c). This is aliasing and it means that the original signal cannot be reconstructed.

If the signal is a single frequency sine-wave then, as its frequency is increased up to $f_S/2$, it will be correctly sampled. Between $f_S/2$ and f_S the signal will appear to have a frequency of $f_S - f$ until $f = f_S$ when the output will be d.c. If the frequency is increased further then it will appear to start again at d.c. and increase. We will be looking at this in the Lab experiments.

In practice, the sampling frequency is usually quite a bit larger than $2f_{MAX}$ to

guarantee a good representation of the signal. Obviously, the higher the sampling rate, the better the representation (see Fig.9.3) but this has an immediate consequence – more samples per second equates to more memory storage!

So, there is a compromise between quality and memory storage. Audio CDs are a good example of this. The maximum input frequency is typically 16kHz which means that the theoretical minimum sampling frequency is 32kHz but the actual frequency is 44.1kHz. There are some very clever ways of reducing the sampling rate – **compression** (e.g. MP3) but these rely on a knowledge of the way in which sounds are produced and only work on the correct types of signal. MP3 only works for speech

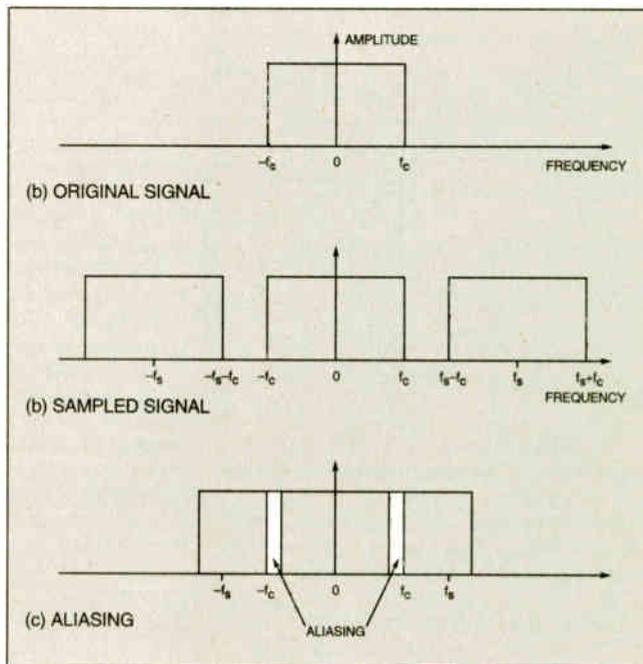


Fig.9.5. Aliasing in the frequency domain.

and music and would not work for compressing video.

ANTI-ALIASING FILTERS

As we see from the experiments, the Picoscope ADC-40 exhibits this behaviour which means that we can get incorrect results for high frequencies. How do we stop this? We use a low pass filter called an **anti-aliasing filter** which is placed between the input signal and the ADC as shown in Fig.9.6.

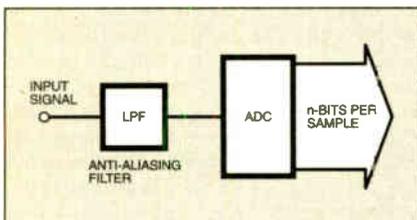


Fig.9.6. Preceding an ADC by an anti-aliasing filter.

The filter must have a sharp roll-off and have a cut-off frequency at less than $f_s/2$. One of the most common filters used nowadays is the switched capacitor filter, similar to that used last month. One of the Lab experiments this month uses a filter to stop aliasing on the Picoscope.

BANDWIDTH EXPANSION

Now we have all the requisite concepts, let us return to the idea that digital signal transmission needs a much wider bandwidth than transmitting the analogue signal directly. We will use the transmission of speech as an example. Human speech has frequency components up to 10kHz but we can reduce the bandwidth to around 3.4kHz without reducing the overall intelligibility. This 3.4kHz is the bandwidth of common analogue telephones.

In order to turn the signal into a digital form, we need to sample it. According to the Nyquist sampling criterion, the minimum rate is 6.8kHz. However, a higher value of 8kHz is used since the anti-aliasing filter will not have an infinite roll-off. Once sampled the signal is then converted into digital form using an ADC. The smallest number of levels needed to give good quality is around 200 and an 8-bit ADC has 256 levels.

We now have a signal sampled 8,000 times per second and converted into 8-bit samples. This gives $8 \times 8,000$ bits per second = 64,000 bits per second. A transmission path needs to have a bandwidth at least 64kHz to accommodate this. Compare this with the original of 3.4kHz – we need nearly 19 times the bandwidth!

RADIATION SENSING

Our main sensing topic this month is nuclear radiation. Obviously we won't be able to carry out any experiments but we can look at the principles of nuclear radiation and how it can be measured. Before discussing sensors, we need to examine the causes of nuclear radiation.

All elements are made up of a nucleus surrounded by a cloud of negatively charged electrons. The nucleus of any atom contains positively charged protons and neutrons (no charge), with the exception of hydrogen which consists of a proton.


The chemical properties of an atom are determined by its **atomic number**, which is the number of protons in its nucleus. The **atomic mass** is the number of protons plus the number of neutrons. An **isotope** of an element has the same number of protons but a different number of neutrons. Some isotopes are stable and do not decay, but many are unstable and undergo spontaneous disintegration forming another element and releasing electromagnetic radiation (gamma rays or X-rays) or elementary particles such as beta or alpha particles:

Alpha particle. An alpha particle is a helium nucleus (positively charged) which is relatively heavy compared with other particles and is easily absorbed by the air or materials such as paper. The alpha particle is changed into a helium atom by capturing two electrons from other atoms, such as nitrogen and oxygen atoms in the atmosphere.

Beta particle. Beta decay is characterized by a nuclear reaction in which the atomic number changes but not the atomic mass. Beta particles can be negatrons (electrons) or positrons which have the mass of an electron but with a positive charge.

Gamma ray emission. Many alpha and beta emission processes leave the nucleus in an excited state which then returns to its non-excited state accompanied by the release of a gamma ray. Gamma rays are electromagnetic in nature.

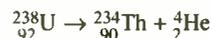We can write nuclear decay as an equation. For example, the decay of uranium-238 into thorium-234 is written as:



The top number is the atomic mass and the bottom the atomic number. This decay produces an *alpha particle* which, as just said, is a helium nucleus. As another example, the conversion of carbon-14 to nitrogen-14 produces a negatron and a neutrino (ν) and is written as:



ENVIRONMENTAL NUCLEAR RADIATION

Nuclear radiation always makes the news because of an inherent fear of radiation-induced diseases such as leukaemia and cancers. Radiation is always present in very small quantities and it is calculated that 87 percent of the radiation to which we are exposed each year comes from natural sources such as rocks, soil, space (cosmic rays) and food (source *This Common Inheritance – Britain's Environmental Strategy*, Government White Paper, 1990). Most of the remainder is from medical uses.

Our exposure to radiation also depends on where we live – granite-bearing rocks produce radon (Rd), an inert but radioactive gas. In fact, it is estimated that 50 percent of radiation in the UK is from radon. If you are interested in radon, browse

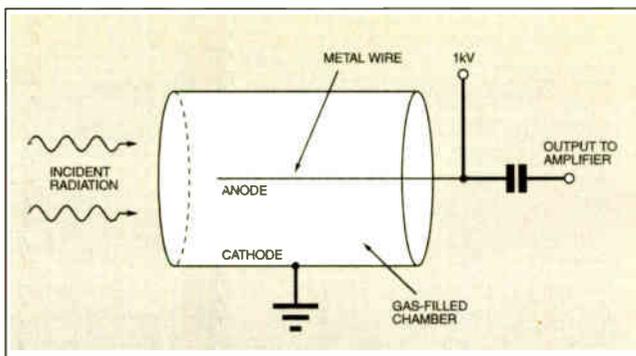


Fig.9.7. Geiger-Muller tube construction.

www.bre.co.uk/radon/links.html. This is the Building Research Establishment and the page referred to has links to bodies such as the DETR (Department of Transport and the Regions).

Astronauts receive large doses of radiation ranging from solar X-rays and solar particles to cosmic rays. Electronic equipment in space is very susceptible to radiation and only **radiation-hardened** electronics can be used.

The *Galileo* spacecraft orbiting Jupiter has encountered high levels of radiation during its tour of Jupiter's moons and as the spacecraft has become older, increasing numbers of faults have been occurring due to radiation damage. It has apparently endured more than twice its designed amount of radiation and is still operational.

The two major areas where we are likely to hear of or encounter radiation are nuclear power stations and in medicine. Nuclear power stations are widespread in the world and in some countries such as Belgium and France they produce as much as 69 percent of the country's electricity. In Britain, this is around 20 percent.


Power stations can be highly dangerous and most of us will remember Chernobyl, where caesium released by the explosion settled on grazing land in the UK and entered the human food chain, mainly via sheep.

The other worry is the disposal of waste which may remain radioactive for thousands of years. It is ironic that nuclear power would appear to be the most environmentally friendly if we think about global warming as it does not produce carbon dioxide, but the waste products are certainly not environmentally friendly!

In medicine, X-rays are well known but radioactive isotopes are used for many purposes, such as labelling, where the radioactive material is used to **label** a chemical (e.g. iodine) and its movement through the body can be traced.

NUCLEAR RADIATION DETECTORS


Perhaps the most well known radiation detector is the Geiger-Muller (GM) tube. A schematic diagram of a typical GM tube is shown in Fig.9.7 consisting of a tube filled with argon through which passes a wire. The outside of the tube is grounded and the wire has about 1kV on it. Any radioactive particles (this includes X-rays and gamma rays) entering the tube ionize the gas, creating ions and electrons. The electrons are attracted to the wire whilst the ions are attracted to the grounded tube. The resulting drop in voltage at the wire is detected

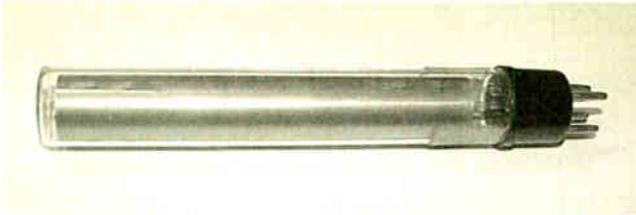

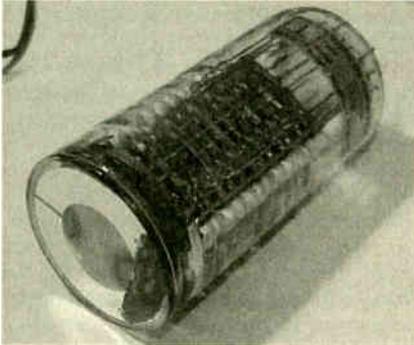Example of a Geiger-Muller tube.

and amplified to produce a digital pulse which can be counted.

One problem with GM counters is that it takes time for the charge built up to dissipate, meaning that it exhibits a **dead time**, producing an upper limit to the number of counts per second. The dead time is of the order of 50ms to 200ms.



Example of a photomultiplier.

A second method is known as **scintillation** where X-rays and nuclear particles striking a special screen produce flashes of light. These flashes are extremely faint but can be amplified using a **photomultiplier** tube. One of the most common scintillation materials is sodium iodide; others include zinc sulphide, anthracene and terphenyl.

The photomultiplier is a device in which an incoming photon causes an electron to be emitted from a surface, this is accelerated towards a cathode at, say, 100V potential. When the electron hits the cathode it releases many more electrons which are then accelerated to another cathode at, say, 200V, and so on. A typical photomultiplier may have 10 cathodes.

The resulting current at the final electrode is many times more than one electron and can be detected. Fig.9.8 shows a schematic diagram of a scintillation detector.

A third method is to use semiconductors, sometimes known as **lithium-drifted silicon detectors**. Germanium is sometimes used. Fig.9.9 shows a diagram of such a device. It consists of three layers of doped silicon – a *p*-type layer facing the radiation to be sensed, an **intrinsic** zone and an

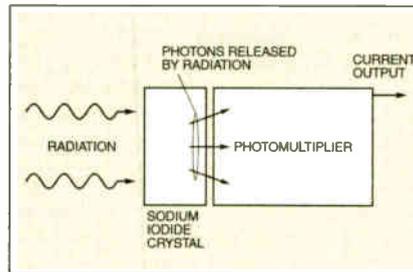


Fig.9.8. Scintillation detector.

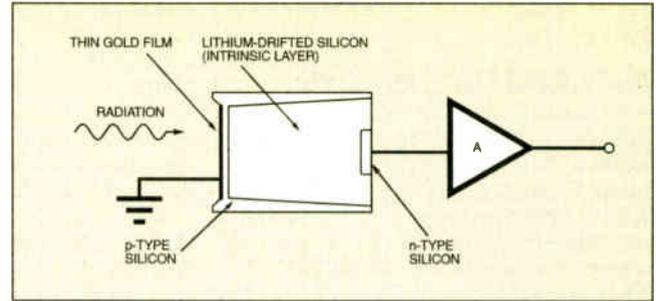


Fig.9.9. Lithium-drifted sensor.

n-type layer. The outer surface of the *p*-type layer is coated with a thin gold layer to act as an electrical contact. The output is taken from the *n*-type layer and amplified.

The intrinsic layer, which is *p*-type silicon, is doped with lithium in an unusual way. A lithium layer is deposited onto the *p*-type layer and the whole device heated to around 400°C, at which point the lithium diffuses into the silicon and converts the *p*-type into *n*-type silicon.

While it is still at 400°C, a d.c. potential is applied, which causes the lithium ions to drift into the *p*-type layer and replace holes. The overall effect is for the intrinsic layer to act in a similar manner to the gas in a GM tube and when a particle impinges on the sensor, a current spike is produced.

One other thing – the sensor is cooled by liquid nitrogen to –196°C to reduce electrical noise. In fact, if the sensor is allowed to reach room temperature, its performance is degraded because the lithium will diffuse rapidly in the silicon.

If you have any queries directly related to this series, you can write to the authors c/o the Editorial address, or you can email them at teach-in@epemag.demon.co.uk (no file attachments or general electronic queries please).

TEACH-IN 2002 – Lab Work 9

DAVE CHESMORE

GAS SENSING, DIGITAL SAMPLING AND EXPERIMENTS WITH AN ADC

Lab 9.1 Gas Sensor Circuit

LAST month we discussed the principles of gas sensing. Here, we present a circuit capable of sensing butane, ethanol, hydrogen and methane. It is based on the Nemoto NAP-7AU sensor.

The sensor consists of two separate devices – the sensor itself and a compensator which has the same characteristics as the sensor but its resistance doesn't change with the presence of gases. The sensor and compensator are resistive and placed in two arms of a bridge circuit. When a gas is present, the sensor's

resistance changes and the bridge becomes unbalanced.

The complete circuit diagram of the Gas Sensor is shown in Fig.9.10. The bridge is powered from a 2.2V power supply derived from an LM317 variable voltage regulator (IC1). The output voltage is set by preset potentiometer VR1. The sensor and compensator are notated as X1 and X2 respectively. The other arms of the bridge are formed by 30Ω resistors (in our case 2 × 15Ω) and balanced by potentiometer VR2.

Since the output of the bridge is a difference voltage, we need to use a difference

amplifier, which is formed by IC2. The gain is set to 21 but can be changed if the ratio between resistors R6, R7 and R8, R9 is changed. You can also use an instrumentation amplifier instead of IC2 to give a better CMRR.

It is advisable to construct and set the 2.2V supply before attaching it to the bridge as the sensor X1 may be damaged by higher voltages. Once constructed, monitor the voltage at point A and vary VR1 until it reads 2.2V.

Build the rest of the circuit and connect the 2.2V supply. Monitor the output and

COMPONENTS



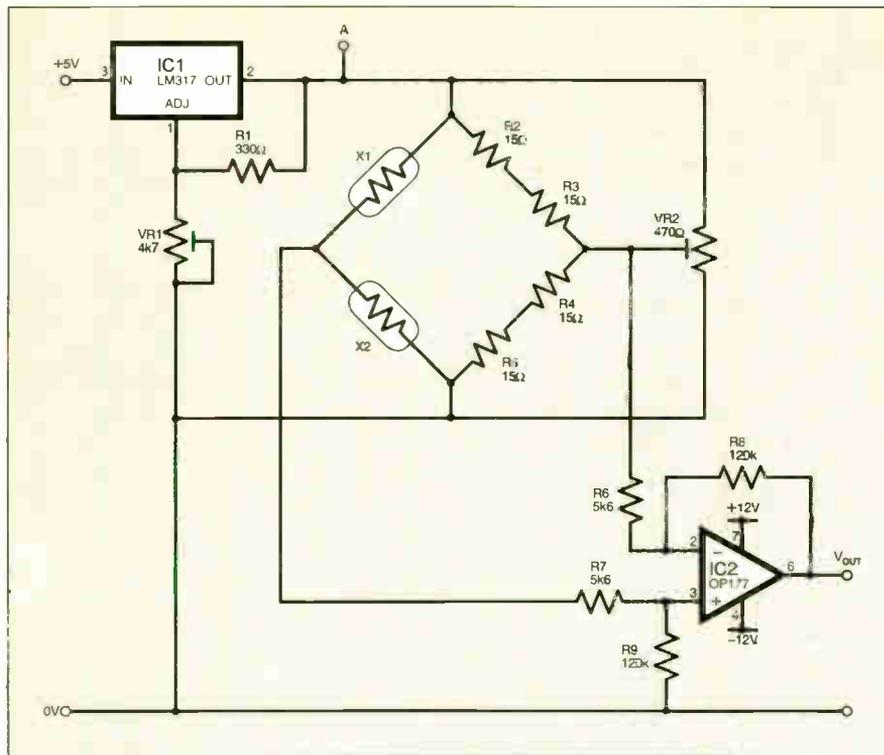


Fig.9.10. Gas Sensor: circuit diagram.

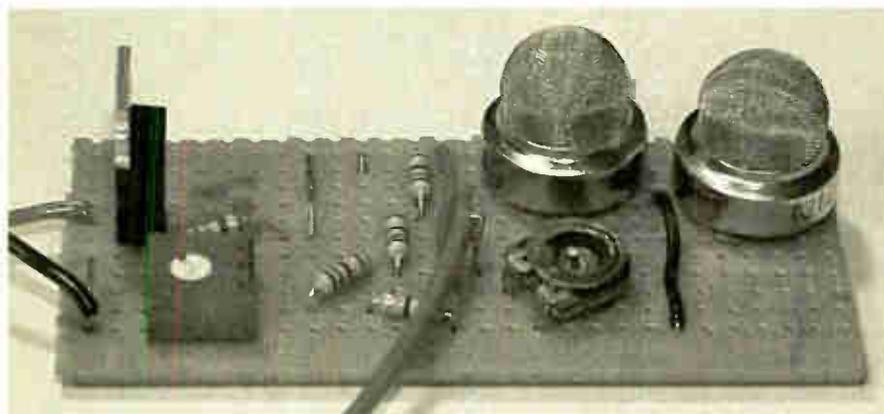

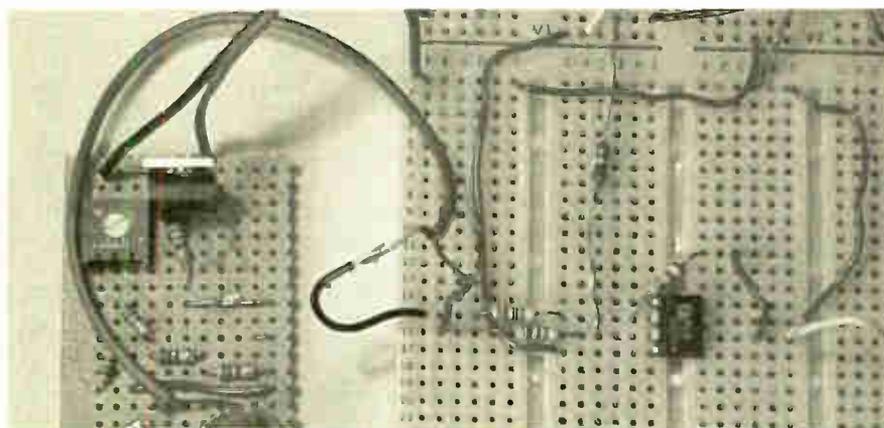The sensor circuit in Fig.9.10 is assembled on stripboard.



The stripboard is then connected to the op.amp on the breadboard.

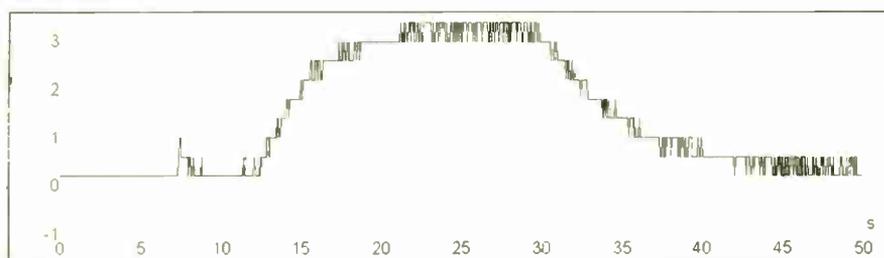


Fig.9.11. Response of Gas Sensor to alcohol.

Lab 9.1

Resistors

R1	330Ω
R2 to R5	15Ω (4 off)
R6, R7	5k6 (2 off)
R8, R9	120k (2 off)

All 0.25W 5% carbon film.

Potentiometers

VR1	4k7 sub.min preset
VR2	470Ω sub.min preset

Semiconductors

IC1	LM317 variable voltage regulator, 1.5A
IC2	OP177 op.amp
X1/X2	NAP-7AU gas sensor/compensator pair

Miscellaneous

Stripboard section (see photo).

See
SHOP
TALK
page

Lab 9.2

Resistors

R1	120k
R2, R3	2k2 (2 off)
R4	12k
R5 to R12	470Ω (8 off)

All 0.25W 5% carbon film.

Potentiometer

VR1	10k rotary carbon, lin
-----	------------------------

Capacitors

C1	10μ tantalum, 16V
C2	100n polyester
C3	150p ceramic/ polystyrene

Semiconductors

D1 to D8	red l.e.d. (8 off) (see text)
IC1	4093 quad 2-input NAND Schmitt trigger
IC2	ADC0804 8-bit ADC

Lab 9.5

Resistors

R1	6k8
R2	15k
R3, R4	27k (2 off)
R5	470k

All 0.25W 5% carbon film.

Capacitors

C1	82p ceramic/ polystyrene
C2	100p ceramic/ polystyrene
C3, C5	10n polyester (2 off)
C4	10μ tantalum, 16V

Semiconductors

IC1	4093 quad 2-input NAND Schmitt trigger
IC2	LTC1062 5th order switched capacitor low-pass filter

N.B. Some components are repeated between Lab Works.

Approx. Cost
Guidance Only

£26
excl. hardware

vary VR2 until the output is 0V. The circuit is then ready to be tested with gases.

Testing is straightforward as long as you are careful. Ethanol (alcohol) is probably the best to use as it is readily available! Soak a piece of cotton wool in some alcohol (e.g. vodka) and place it close to the sensor. The output of the circuit should change as indicated in Fig.9.11. The output for our test circuit reached about 3.5V. The reaction time is about 10 seconds.

You can repeat the tests with other gases such as butane. Note that this circuit is not calibrated. Also note that the output will be negative if you have the sensor and compensator the wrong way round!

Lab 9.2 A-D Converter Demonstration Circuit

It is beyond the scope of these articles to provide complete circuits for ADCs, partly because there are so many available! Here, we will show how to control a common ADC at low speed so that the binary output can be observed for different input voltages.

The complete circuit is shown in Fig.9.12 and it uses a readily available National Semiconductor ADC0804 8-bit ADC (IC2). The ADC has three control inputs, chip select (CS), write (WR) and read (RD), together with two analogue inputs, $V_{in(+)}$ and $V_{in(-)}$. The final input is for a reference voltage and is denoted as $V_{ref/2}$.

The binary output goes from 00000000 at $V_{in(-)}$ to 11111111 at V_{ref} . For example, if $V_{in(-)}$ is 0V and the voltage at $V_{ref/2}$ is 2.0V then the 00000000 is equivalent to 0.0V and 11111111 equivalent to 4.0V.

In our demonstration circuit, the reference voltage is set at half the supply by potential divider R2 and R3; this makes 11111111 equal to 5V. Chip select (CS) is set low to permanently enable the device and Read (RD) set low to enable the outputs (D0 to D7). Control of the ADC is via the Write input (WR) which is active low and is derived from a low frequency squarewave oscillator (IC1) operating at about 200Hz.

The internal operation of the ADC is controlled by an internal high speed oscillator operating at a frequency set by resistor R4 and capacitor C3. This means that each conversion takes place over about 100ms but at 200 samples per second.

The input voltage to be converted to digital output is provided by VR1 and the binary output is displayed on l.e.d.s D1 to D8, which are buffered by resistors R5 to R12. (An l.e.d. array was used in the test model, but individual l.e.d.s. can be used instead.)

Construct the circuit in Fig.9.12 and vary potentiometer VR1. You should see the l.e.d.s changing in a binary manner. The accompanying photograph shows a binary value of 01011111 which is equal to 95 in decimal (least significant bit is at the top of the array).

Using the signal generator from Part 8, you could input a low frequency sinewave and watch the binary values changing. You can also vary the value of $V_{ref/2}$ and show that the range can be changed.

A full datasheet for the ADC0804 can be found at the National Semiconductor web site (www.natsemi.com).

Lab 9.3 Illustration of Aliasing – Time Domain

We can illustrate aliasing very easily using the Picoscope and the sinewave


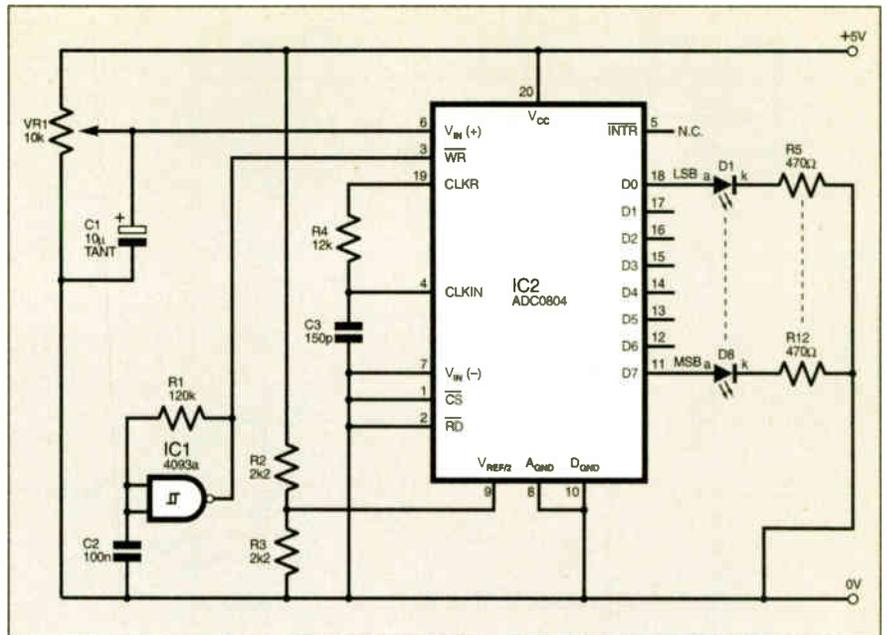


Fig.9.12. A-to-D converter demonstration circuit.

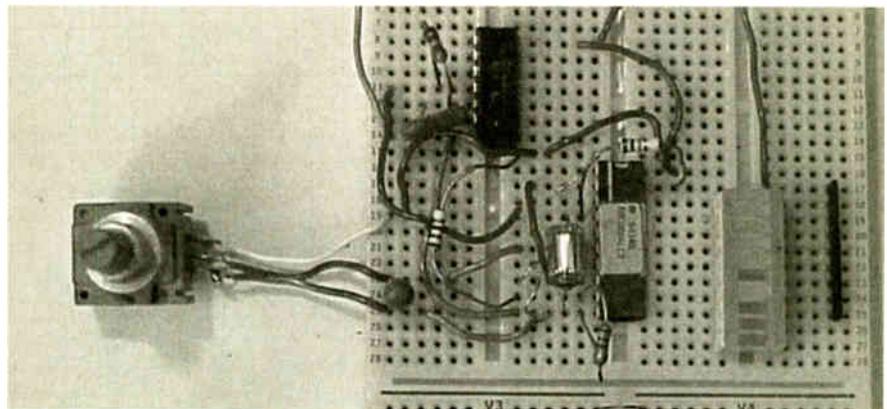

Breadboard assembly for the circuit in Fig.9.12.

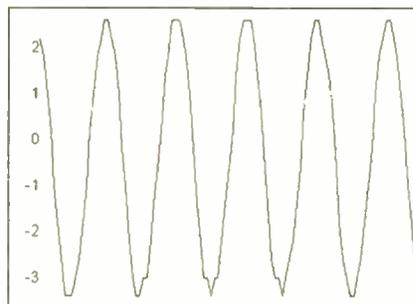


Fig.9.13. Picoscope display of a sinewave at 1kHz.

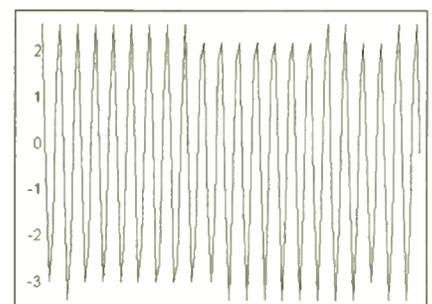


Fig.9.14. Picoscope display at 4kHz, beginning to show a small amount of aliasing.

generator from Part 8 (Fig.8.11). Connect the generator to the Picoscope input and set the frequency to about 1kHz. The Picoscope display should be similar to that in Fig.9.13, showing that the signal is almost correctly displayed.

Now increase the signal to 4kHz; again the almost correct waveform should be displayed, but with a small amount of aliasing just beginning to appear (Fig.9.14). Increase the input frequency further until it is about 10kHz – you

should see something like that in Fig.9.15. It does not look much like a pure 10kHz sinewave! It is the sampling rate fixed inside the Picoscope software that causes this.

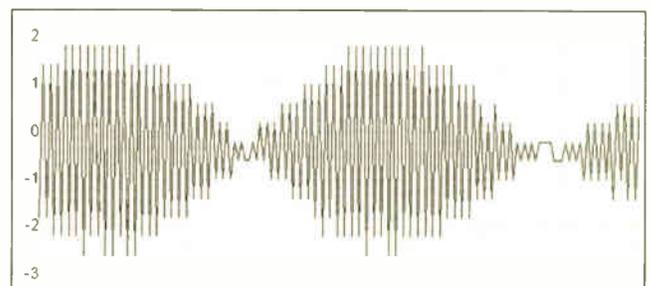


Fig.9.15. Picoscope display at 10kHz, dramatically showing how aliasing has disrupted the signal quality.

Lab 9.4 Illustration of Aliasing - Frequency Domain

Aliasing can also be seen by using the Picoscope Spectrum Analyser. See Panel 9.1 for details of how to operate the analyser. Select the Spectrum Analyser, set the sampling rate to 10kHz and FFT size to 1024. Input a 1kHz sinewave and observe the display - you should see a peak in the spectrum at about 1kHz.

Increase the frequency to 4kHz; the peak in the display should correspond (Fig.9.16). Now increase it to 5kHz and then 6kHz. The peak will go from the far right hand side of the display (5kHz) and move to the left, reading 4kHz as shown in Fig.9.17!

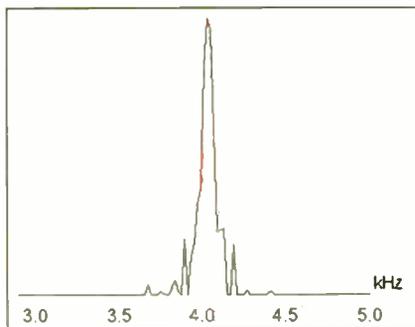


Fig.9.16. Spectrum analysing a 4kHz sinewave at 10kHz.

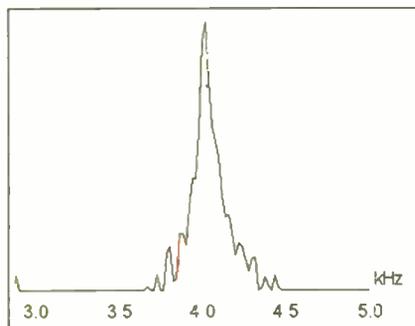


Fig.9.17. When spectrum analysing a 6kHz sinewave at 10kHz, aliasing causes the waveform to be shown as representing a 4kHz signal.

Carry on increasing the frequency and see what happens. When the frequency is 10kHz, the peak should read 0Hz (Fig.9.18). Further increasing the input frequency continues to increase the displayed spectrum, which goes up again.

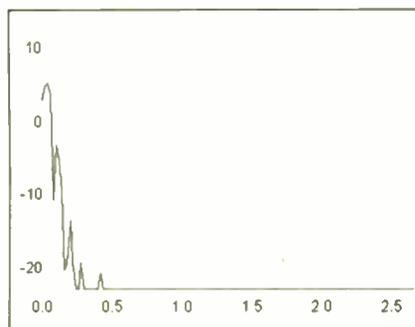


Fig.9.18. When spectrum analysing a 10kHz sinewave at 10kHz, the display indicates that the signal is occurring at around 0Hz!

PANEL 9.1. Picoscope Spectrum Analyzer

The Picoscope Spectrum Analyzer can be started from within the oscilloscope display either by clicking the button on the panel (second button from the left) or via the View drop-down menu - select *new spectrum*. The spectrum is shown with frequency on the x-axis and signal power in dB on the y-axis. The default set-up is for a maximum frequency of 10kHz and an FFT (Fast Fourier Transform) size of 256 points.

The number of points in the FFT determines the frequency resolution of the display - the higher the number of points (always a power of 2) the better the resolution, *but* the slower the update of the display because it takes longer to calculate the spectrum.



The Spectrum Analyzer operates on *blocks* of data and calculates the FFT for each block. One problem with this is that the division of the signal into blocks introduces distortion in the form of side-lobes in the spectrum because the end of a block is abrupt, giving rise to additional false frequency components.

This is overcome by multiplying the data by a *window* which reduces the data at the beginning and end of the block progressively to zero to remove the abrupt ends. There are many windows available which can be selected via the *settings*:

options menu (F5). The default set-up is *Blackman*, which is best for reducing sidelobes.

FFT size can be changed to between 128 and 4096 using the same menu option. In addition, you can change the display from dB to volts and display current spectrum, average spectrum or capture the spectrum peaks.

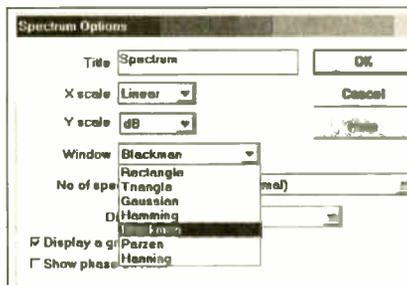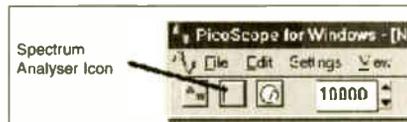Finally, the sampling frequency can be changed on the main display from a maximum of 10kHz to 100Hz. The default is 10kHz. The timebase option (*settings: timebase*, F2) also allows you to change the frequency.



This behaviour can be explained by Nyquist: the sampling frequency is 10kHz and the maximum input frequency is therefore 5kHz. For an input frequency f , below $f_s/2$ the output is f ; between $f_s/2$ and f_s , the output is $f_s - f$.

Lab 9.5 Anti-aliasing Filter

Build the circuit of Fig.9.19, which is nearly identical to Fig.8.16 in last month's Lab Work. The filter has a cut-off frequency of 4kHz, determined by the oscillator formed around IC1a, which has an output at approximately 400kHz.

Placing this filter between the input signal and the Picoscope should stop all

aliasing problems. Try repeating Labs 9.3 and 9.4 with the filter in place.

Note that the filter has a cut-off frequency of 4kHz and not 5kHz; this is because the filter is not perfect and some energy is passed above the cut-off frequency which would be aliased if it were set to half of the sampling frequency. Also note that the cut-off frequency should be changed if the sampling frequency is changed.

NEXT MONTH

In Part 10 next month we conclude the *Teach-In 2002* series by discussing smart and intelligent sensors, telemetry systems and sensor networks.

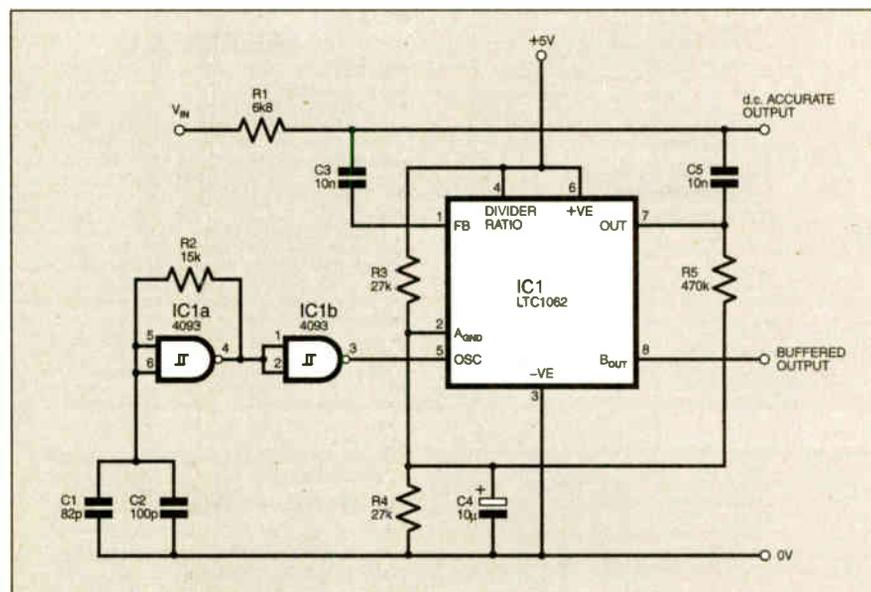


Fig.9.19. Anti-aliasing filter, having a cut-off frequency of 4kHz.



EPE TEACH-IN 2000 CD-ROM

The whole of the 12-part *Teach-In 2000* series by John Becker (published in *EPE* Nov '99 to Oct 2000) is now available on CD-ROM. Plus the *Teach-In 2000* interactive software covering all aspects of the series and Alan Winstanley's *Basic Soldering Guide* (including illustrations and Desoldering).

Teach-In 2000 covers all the basic principles of electronics from Ohm's Law to Displays, including Op.Amps, Logic Gates etc. Each part has its own section on the interactive software where you can also change component values in the various on-screen demonstration circuits.

The series gives a hands-on approach to electronics with numerous breadboard circuits to try out, plus a simple computer interface which allows a PC to be used as a basic oscilloscope.

ONLY **£12.45** including VAT and p&p

Order code Teach-in CD-ROM

Robotics

INTRODUCING ROBOTICS WITH LEGO MINDSTORMS

Robert Penfold
Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various "click-together" components supplied in the basic RIS kit. Then explains in simple terms how the "brain" of the robot may be programmed on screen using a PC and "zapped" to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Details building and programming instructions provided, including numerous step-by-step photographs.

288 pages - large format Order code BP901 £14.99

MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS - Robert Penfold

Covers the Vision Command System

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using Lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with 'waiter service' when you clap your hands, perform tricks, 'see' and avoid objects by using 'bats radar', or accurately follow a line marked on the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit.OCX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an 'intelligent' sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

298 pages Order code BP902 £14.99

ANDROIDS, ROBOTS AND ANIMATRONS

John Lovine
Build your own working robot or android using both off-the-shelf and workshop constructed materials and devices. Computer control gives these robots and androids two types of artificial intelligence (an expert system and a neural network). A lifelike android hand can be built and programmed to function doing repetitive tasks. A fully animated robot or android can also be built and programmed to perform a wide variety of functions.

The contents include an Overview of State-of-the-Art Robots; Robotic Locomotion; Motors and Power Controllers; All Types of Sensors; Tilt; Bump; Road and Wall Detection; Light; Speech and Sound Recognition; Robotic Intelligence (Expert Type) Using a Single-Board Computer Programmed in BASIC; Robotic Intelligence (Neural Type) Using Simple Neural Networks (Insect Intelligence); Making a Lifelike Android Hand; A Computer-Controlled Robotic Insect Programmed in BASIC; Telepresence Robots With Actual Arcade and Virtual Reality Applications; A Computer-Controlled Robotic Arm; Animated Robots and Androids; Real-World Robotic Applications.

224 pages Order code MGH1 £19.99

DIRECT BOOK SERVICE

NOTE: ALL PRICES INCLUDE UK POSTAGE

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order to your door. Full ordering details are given on the last book page.

For a further selection of books see the next two issues of *EPE*.

Radio

BASIC RADIO PRINCIPLES AND TECHNOLOGY

Ian Poole
Radio technology is becoming increasingly important in today's high technology society. There are the traditional uses of radio which include broadcasting and point to point radio as well as the new technologies of satellites and cellular phones. All of these developments mean there is a growing need for radio engineers at all levels.

Assuming a basic knowledge of electronics, this book provides an easy to understand grounding in the topic.

Chapters in the book: Radio Today, Yesterday, and Tomorrow; Radio Waves and Propagation; Capacitors, Inductors, and Filters; Modulation; Receivers; Transmitters; Antenna Systems; Broadcasting; Satellites; Personal Communications; Appendix - Basic Calculations.

263 pages Order code NE30 £15.99

PROJECTS FOR RADIO AMATEURS AND S.W.L.S.

R. A. Penfold
This book describes a number of electronic circuits, most of which are quite simple, which can be used to enhance the performance of most short wave radio systems.

The circuits covered include: An aerial tuning unit; A simple active aerial; An add-on b.f.o. for portable sets; A wavetramp to combat signals on spurious responses; An audio notch filter; A parametric equaliser; C.W. and S.S.B. audio filters; Simple noise limiters; A speech processor; A volume expander.

Other useful circuits include a crystal oscillator, and RTTY/C.W. tone decoder, and a RTTY serial to parallel converter. A full range of interesting and useful circuits for short wave enthusiasts.

92 pages Order code BP304 £4.45

AN INTRODUCTION TO AMATEUR RADIO

I. D. Poole
Amateur radio is a unique and fascinating hobby which has attracted thousands of people since it began at the turn of the century. This book gives the newcomer a comprehensive and easy to understand guide through the subject so that the reader can gain the most from the hobby. It then remains an essential reference volume to be used time and again. Topics covered include the basic aspects of the hobby, such as operating procedures, jargon and setting up a station. Technical topics covered include propagation, receivers, transmitters and aerials etc.

150 pages Order code BP257 £5.49

VALVE RADIO AND AUDIO REPAIR HANDBOOK

Chas Miller
This book is not only an essential read for every professional working with antique radio and gramophone equipment, but also dealers, collectors and valve technology enthusiasts the world over. The emphasis is firmly on the practicalities of repairing and restoring, so technical content is kept to a minimum, and always explained in a way that can be followed by readers with no background in electronics. Those who have a good grounding in electronics, but wish to learn more about the practical aspects, will benefit from the emphasis given to hands-on repair work, covering mechanical as well as electrical aspects of servicing. Repair techniques are also illustrated throughout.

A large reference section provides a range of information compiled from many contemporary sources, and includes specialist dealers for valves, components and complete receivers.

288 pages Order code NE34 £20.50

Computers and Computing

MULTIMEDIA ON THE PC

Ian R. Sinclair
In this book, you'll find out what a CD ROM is, how it works, and why it is such a perfect add-on for a PC, allowing you to buy programmes, text, graphics and sound on a CD. It also describes the installation of a CD ROM drive and a sound card, pointing out the common problems that arise, and then shows how to use them to create a complete multimedia presentation that contains text, photos, a soundtrack with your own voice recorded as a commentary, even animation and edited video footage.

184 pages Order code PC112 £12.95

HOW TO BUILD YOUR OWN PC

Morris Rosenthal
More and more people are building their own PCs. They get more value for their money, they create exactly the machine they want, and the work is highly satisfying and actually fun. That is, if they have a unique beginner's guide like this one, which visually demonstrates how to construct a state-of-the-art computer from start to finish.

Through 150 crisp photographs and clear but minimal text, readers will confidently absorb the concepts of computer building. The extra-big format makes it easy to see what's going on in the pictures. For non-specialists, there's even a graphical glossary that clearly illustrates technical terms. The author goes "under the hood" and shows step-by-step how to create a socket 7 (Pentium and non-intel chipsets) and a Slot 1 (Pentium II) computer, covering: What first-time builders need to know; How to select and purchase parts; How to assemble the PC; How to install Windows 98. The few existing books on this subject, although badly outdated, are in steady demand. This one delivers the expertise and new technology that fledgling computer builders are eagerly looking for.

224 pages - large format Order code MGH2 £21.99

PIC YOUR PERSONAL INTRODUCTORY COURSE

SECOND EDITION John Morton
Discover the potential of the PIC microcontroller through graded projects - this book could revolutionise your electronics construction work!

A uniquely concise and practical guide to getting up and running with the PIC Microcontroller. The PIC is one of the most popular of the microcontrollers that are transforming electronic project work and product design.

Assuming no prior knowledge of microcontrollers and introducing the PIC's capabilities through simple projects, this book is ideal for use in schools and colleges. It is the ideal introduction for students, teachers, technicians and electronics enthusiasts. The step-by-step explanations make it ideal for self-study too: this is not a reference book - you start work with the PIC straight away.

The revised second edition covers the popular reprogrammable EEPROM PICs: P16C84/16F84 as well as the P54 and P71 families.

270 pages Order code NE36 £13.99

UNDERSTANDING PC SPECIFICATIONS

R. A. Penfold (Revised Edition)
If you require a microcomputer for business applications, or a high quality home computer, an IBM PC or compatible is often the obvious choice. They are competitively priced, and are backed up by an enormous range of applications programs, hardware add-ons, etc. The main difficulty for the uninitiated is deciding on the specification that will best suit his or her needs. PCs range from simple systems of limited capabilities up to complex systems that can happily run applications that would have been considered beyond the abilities of a microcomputer not so long ago. It would be very easy to choose a PC system that is inadequate to run your applications efficiently, or one which goes beyond your needs and consequently represents poor value for money.

This book explains PC specifications in detail, and the subjects covered include the following: Differences between types of PC (XT, AT, 80386, etc); Maths co-processors; Input devices (keyboards, mice, and digitisers); Memory, including both expanded (EMS) and extended RAM; RAM disks and disk caches; Floppy disk drive formats and compatibility; Hard disk drives (including interleaved factors and access times); Display adaptors, including all standard PC types (CGA, Hercules, Super VGA, etc); Contains everything you need to know if you can't tell your EMS from your EGA!

128 pages Order code BP282 £5.45

Theory and Reference


Bebop To The Boolean Boogie

By Clive (call me Max) Maxfield
Specially imported by EPE - Excellent value

An Unconventional Guide to Electronics Fundamentals, Components and Processes

This book gives the "big picture" of digital electronics. This indepth, highly readable, up-to-the-minute guide shows you how electronic devices work and how they're made. You'll discover how transistors operate, how printed circuit boards are fabricated, and what the innards of memory ICs look like. You'll also gain a working knowledge of Boolean Algebra and Karnaugh Maps, and understand what Reed-Muller logic is and how it's used. And there's much, MUCH more (including a recipe for a truly great seafood gumbol). Hundreds of carefully drawn illustrations clearly show the important points of each topic. The author's tongue-in-cheek British humor makes it a delight to read, but this is a REAL technical book, extremely detailed and accurate. A great reference for your own shelf, and also an ideal gift for a friend or family member who wants to understand what it is you do all day...

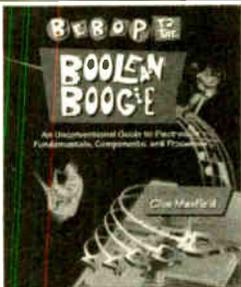470 pgs - large format **Order code BEB1** £26.95



BEBOP BYTES BACK (and the Boboputer Computer Simulator) CD-ROM

Clive (Max) Maxfield and Alvin Brown

This follow-on to *Bebop to the Boolean Boogie* is a multimedia extravaganza of information about how computers work. It picks up where "Bebop I" left off, guiding you through the fascinating world of computer design...



and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the CD-ROM contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the CD-ROM contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this!

Over 800 pages in Adobe Acrobat format
£21.95 including VAT and p&p

Order code BEB2 CD-ROM

ELECTRONICS MADE SIMPLE

Ian Sinclair

Assuming no prior knowledge, *Electronics Made Simple* presents an outline of modern electronics with an emphasis on understanding how systems work rather than on details of circuit diagrams and calculations. It is ideal for students on a range of courses in electronics, including GCSE, C&G and GNVQ, and for students of other subjects who will be using electronic instruments and methods.

Contents: waves and pulses, passive components, active components and ICs, linear circuits, block and circuit diagrams, how radio works, disc and tape recording, elements of TV and radar, digital signals, gating and logic circuits, counting and correcting, microprocessors, calculators and computers, miscellaneous systems.

199 pages **Order code NE23** £13.99

SCROGGIE'S FOUNDATIONS OF WIRELESS AND ELECTRONICS - ELEVENTH EDITION

S. W. Amos and Roger Amos

Scroggie's Foundations is a classic text for anyone working with electronics, who needs to know the art and craft of the subject. It covers both the theory and practical aspects of a huge range of topics from valve and tube technology, and the application of cathode ray tubes to radar, to digital tape systems and optical recording techniques.

Since *Foundations of Wireless* was first published over 60

years ago, it has helped many thousands of readers to become familiar with the principles of radio and electronics. The original author Sowerby was succeeded by Scroggie in the 1940s, whose name became synonymous with this classic primer for practitioners and students alike. Stan Amos, one of the fathers of modern electronics and the author of many well-known books in the area, took over the revision of this book in the 1980s and it is he, with his son, who have produced this latest version.

400 pages **Order code NE27** £21.99

GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

96 pages **Order code BP239** £4.49

DIGITAL GATES AND FLIP-FLOPS

Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of microprocessor techniques as applied to digital logic.

200 pages **Order code PC106** £9.95

Music, Audio and Video

QUICK GUIDE TO ANALOGUE SYNTHESIS

Ian Waugh

Even though music production has moved into the digital domain, modern synthesizers invariably use analogue synthesis techniques. The reason is simple - analogue synthesis is flexible and versatile, and it's relatively easy for us to understand. The basics are the same for all analogue synths, and you'll quickly be able to adapt the principles to any instrument, to edit existing sounds and create exciting new ones. This book describes: How analogue synthesis works; The essential modules every synthesizer has; The three steps to synthesis; How to create that bass sound; How to generate filter sweeps; Advanced synth modules; How to create simple and complex synth patches; Where to find soft synths on the Web.

If you want to take your synthesizer - of the hardware or software variety - past the presets, and program your own sounds and effects, this practical and well-illustrated book tells you what you need to know.

60 pages **Order code PC118** £7.45

QUICK GUIDE TO MP3 AND DIGITAL MUSIC

Ian Waugh

MP3 files, the latest digital music format, have taken the music industry by storm. What are they? Where do you get them? How do you use them? Why have they thrown record companies into a panic? Will they make music easier to buy? And cheaper? Is this the future of music?

All these questions and more are answered in this concise and practical book which explains everything you need to know about MP3s in a simple and easy-to-understand manner. It explains:

How to play MP3s on your computer; How to use MP3s with handheld MP3 players; Where to find MP3s on the Web; How MP3s work; How to tune into Internet radio stations; How to create your own MP3s; How to record your own CDs from MP3 files; Other digital audio music formats.

Whether you want to stay bang up to date with the latest music or create your own MP3s and join the on-line digital music revolution, this book will show you how.

60 pages **Order code PC119** £7.45

ELECTRONIC MUSIC AND MIDI PROJECTS

R. A. Penfold

Whether you wish to save money, boldly go where no musician has gone before, rekindle the pioneering spirit, or simply have fun building some electronic music gadgets, the designs featured in this book should suit your needs. The projects are all easy to build, and some are so simple that even complete beginners at electronic project construction can tackle them with ease. Stripboard layouts are provided for every project, together with a wiring diagram. The mechanical side of construction has largely been left to individual constructors to sort out, simply because the vast majority of project builders prefer to do their own thing in this respect.

None of the designs requires the use of any test equipment in order to get them set up properly. Where any setting up is required, the procedures are very straightforward, and they are described in detail.

Projects covered: Simple MIDI tester, Message grabber Byte grabber, THRU box, MIDI auto switcher, Auto/manual switcher, Manual switcher, MIDI patchbay, MIDI controlled switcher, MIDI lead tester, Program change pedal, Improved program change pedal, Basic mixer, Stereo mixer, Electronic swell pedal, Metronome, Analogue echo unit.

124 pages **Order code PC116** £10.95

THE INVENTOR OF STEREO - THE LIFE AND WORKS OF ALAN DOWER BLUMLEIN

Robert Charles Alexander

This book is the definitive study of the life and works of one of Britain's most important inventors who, due to a cruel set of circumstances, has all but been overlooked by history.

Alan Dower Blumlein led an extraordinary life in which his inventive output rate easily surpassed that of Edison, but whose early death during the darkest days of World War Two led to a shroud of secrecy which has covered his life and achievements ever since.

His 1931 Patent for a B.natural Recording System was so revolutionary that most of his contemporaries regarded it as more than 20 years ahead of its time. Even years after his death, the full magnitude of its detail had not been fully utilized. Among his 128 patents are the principal electronic circuits critical to the development of the world's first electronic television system. During his short working life, Blumlein produced patent after patent breaking entirely new ground in electronic and audio engineering.

During the Second World War, Alan Blumlein was deeply engaged in the very secret work of radar development and contributed enormously to the system eventually to become 'H2S' - blind-bombing radar. Tragically, during an experimental H2S flight in June 1942, the Halifax bomber in which Blumlein and several colleagues were flying, crashed and all aboard were killed. He was just days short of his thirtieth birthday.

420 pages **Order code NE32** £15.99

VIDEO PROJECTS FOR THE ELECTRONICS CONSTRUCTOR

R. A. Penfold

Written by highly respected author R. A. Penfold, this book contains a collection of electronic projects specially designed for video enthusiasts. All the projects can be simply constructed, and most are suitable for the newcomer to project construction, as they are assembled on stripboard.

There are faders, wipers and effects units which will add sparkle and originality to your video recordings, an audio mixer and noise reducer to enhance your soundtracks and a basic computer control interface. Also, there's a useful selection on basic video production techniques to get you started.

Complete with explanations of how the circuit works, shopping lists of components, advice on construction, and guidance on setting up and using the projects, this invaluable book will save you a small fortune.

Circuits include: video enhancer, improved video enhancer, video fader, horizontal wiper, improved video wiper, negative video unit, fade to grey unit, black and white keyer, vertical wiper, audio mixer, stereo headphone amplifier, dynamic noise reducer, automatic fader, pushbutton fader, computer control interface, 12 volt mains power supply.

124 pages **Order code PC115** £10.95

PC MUSIC - THE EASY GUIDE

Robin Vincent

How do I make music on my PC? Can I record music onto my PC? What's a sequencer? How can I get my PC to print a music score? What sort of a soundcard do I need? What hardware and software do I need? How do I connect a keyboard to my PC?

Just a few of the questions you've probably asked. Well, you'll find the answers to all these questions, and many more, in this book. It will show you what can be done, what it all means, and what you will need to start creating your own music on your PC. It's an easy read, it's fully illustrated and it will help you understand how a computer can be used as a creative music tool.

It covers soundcards, sequencers, hard disk digital audio recording and editing, plug-ins, printing scores with notation software, using your PC as a synthesizer, getting music onto and off the Internet, using Windows, sample PC music setups, FAQs, a glossary, advice on hardware and software, and a list of industry contacts.

116 pages **Order code PC117** £11.95

HIGH POWER AUDIO AMPLIFIER CONSTRUCTION

R. A. Penfold

Practical construction details of how to build a number of audio power amplifiers ranging from about 50 to 300/400 watts r.m.s. includes MOSFET and bipolar transistor designs.

96 pages **Order code BP277** £4.49

ALL PRICES INCLUDE UK POST AND PACKING
CD-ROM prices include VAT and/or postage to anywhere in the world

Circuits, Data and Design

PRACTICAL ELECTRONIC FILTERS

Owen Bishop

This book deals with the subject in a non-mathematical way. It reviews the main types of filter, explaining in simple terms how each type works and how it is used.

The book also presents a dozen filter-based projects with applications in and around the home or in the constructor's workshop. These include a number of audio projects such as a rhythm sequencer and a multi-voiced electronic organ.

Concluding the book is a practical step-by-step guide to designing simple filters for a wide range of purposes, with circuit diagrams and worked examples.

88 pages

Order code BP299

£5.49

DIGITAL ELECTRONICS -

A PRACTICAL APPROACH

With FREE Software: Number One

Systems - EASY-PC

Professional XM and Pulsar (Limited Functionality)

Richard Monk

Covers binary arithmetic, Boolean algebra and logic gates, combination logic, sequential logic including the design and construction of asynchronous and synchronous circuits and register circuits. Together with a considerable practical content plus the additional attraction of its close association with computer aided design including the FREE software.

There is a 'blow-by-blow' guide to the use of EASY-PC Professional XM (a schematic drawing and printed circuit board design computer package). The guide also conducts the reader through logic circuit simulation using Pulsar software. Chapters on p.c.b. physics and p.c.b. production techniques make the book unique, and with its host of project ideas make it an ideal companion for the integrative assignment and common skills components required by BTEC and the key skills demanded by GNVQ. The principal aim of the book is to provide a straightforward approach to the understanding of digital electronics.

Those who prefer the 'Teach-In' approach or would rather experiment with some simple circuits should find the book's final chapters on printed circuit board production and project ideas especially useful.

250 pages (large format)

Order code NE28

£17.99

A BEGINNER'S GUIDE TO TTL DIGITAL ICs

R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip/flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in the "real world".

142 pages

Order code BP332

£5.45

HOW TO USE OP.AMPS

E. A. Parr

This book has been written as a designer's guide covering many operational amplifiers, serving both as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible.

160 pages

Order code BP88

£4.49

CIRCUIT SOURCE BOOK 2

R. A. Penfold

This book will help you to create and experiment with your own electronic designs by combining and using the various standard "building blocks" circuits provided. Where applicable, advice on how to alter the circuit parameters is provided.

The circuits covered are mainly concerned with signal generation, power supplies, and digital electronics.

The topics covered in this book include: 555 oscillators; sine-wave oscillators; function generators; CMOS oscillators; voltage controlled oscillators; radio frequency oscillators; 555 monostables; CMOS monostables; TTL monostables; precision long timers; power supply and regulator circuits; negative supply generators and voltage boosters; digital dividers; decoders, etc; counters and display drivers; D/A and A/D converters; opto-isolators, flip/flops, noise generators, tone decoders, etc.

Over 170 circuits are provided, which it is hoped will be useful to all those involved in circuit design and application, be they professionals, students or hobbyists.

192 pages

Order code BP322

£5.45

For a further selection of books see the next two issues of EPE

Project Building & Testing

ELECTRONIC PROJECTS FOR EXPERIMENTERS

R. A. Penfold

Many electronic hobbyists who have been pursuing their hobby for a number of years seem to suffer from the dreaded "seen it all before" syndrome. This book is fairly and squarely aimed at sufferers of this complaint, plus any other electronics enthusiasts who yearn to try something a bit different. No doubt many of the projects featured here have practical applications, but they are all worth a try for their interest value alone.

The subjects covered include:- Magnetic field detector, Basic Hall effect compass, Hall effect audio isolator, Voice scrambler/descrambler, Bat detector, Bat style echo location, Noise cancelling, LED stroboscope, Infra-red "torch", Electronic breeze detector, Class D power amplifier, Strain gauge amplifier, Super hearing aid.

138 pages

Order code BP371

£5.45

ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including the following topics:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering; making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby.

135 pages

Order code BP392

£5.49

PRACTICAL FIBRE-OPTIC PROJECTS

R. A. Penfold

While fibre-optic cables may have potential advantages over ordinary electric cables, for the electronics enthusiast it is probably their novelty value that makes them worthy of exploration. Fibre-optic cables provide an innovative interesting alternative to electric cables, but in

most cases they also represent a practical approach to the problem. This book provides a number of tried and tested circuits for projects that utilize fibre-optic cables.

The projects include:- Simple audio links, F.M. audio link, P.W.M. audio links, Simple d.c. links, P.W.M. d.c. link, P.W.M. motor speed control, RS232C data links, MIDI link, Loop alarms, R.P.M. meter.

All the components used in these designs are readily available, none of them require the constructor to take out a second mortgage.

132 pages

Order code BP374

£5.45

RADIO BYGONES

We also carry a selection of books aimed at readers of EPE's sister magazine on vintage radio *Radio Bygones*. These books include the *Comprehensive Radio Valve Guides* (five books with a free copy of the Master Index) for just £15. Also Jonathan Hill's excellent *Radio Radio*, a comprehensive book with hundreds of photos depicting the development of the British wireless set up to the late 1960s.

The three volumes of our own *Wireless For the Warrior* by Louis Meulstee are also available. These are a technical history of radio communication equipment in the British Army from pre-war through to the 1960s.

For details see the shop on our UK web site at www.epemag.wimborne.co.uk or contact us for a list of *Radio Bygones* books.

BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £1 per book. For the rest of the world airmail add £2 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard, Amex, Diners Club or Switch - minimum card order is £5 - to:

**DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LTD.,
408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery - more for overseas orders. *Please check price and availability (see latest issue of Everyday Practical Electronics) before ordering from old lists.*

For a further selection of books see the next two issues of EPE.

Tel 01202 873872 Fax 01202 874562. Email: dbs@epemag.wimborne.co.uk

Order from our online shop at: www.epemag.wimborne.co.uk/shopdoor.htm

BOOK ORDER FORM

Full name:

Address:

.....

.....

..... Post code: Telephone No:

Signature:

I enclose cheque/PO payable to DIRECT BOOK SERVICE for £

Please charge my card £ Card expiry date.....

Card Number Switch Issue No.....

Please send book order codes:

.....

Please continue on separate sheet of paper if necessary
If you do not wish to cut your magazine, send a letter or copy of this form

PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to The PCB Service, *Everyday Practical Electronics*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872; Fax 01202 874562; E-mail: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm. Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).
NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail.
Back numbers or photostats of articles are available if required – see the *Back Issues* page for details.

Please check price and availability in the latest issue.

Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
★ <i>EPE</i> Icebreaker – PCB257, programmed PIC16F877 and floppy disc	MAR '00	Set only £22.99
★ Micro-PICscope	APR '00	259 £4.99
Garage Link – Transmitter Receiver		261 } Set £5.87 262 }
Versatile Mic/Audio Pre-amplifier	MAY '00	260 £3.33
PIR Light Checker		263 £3.17
★ Multi-Channel Transmission System – Transmitter Receiver Interface		264 } Set £6.34 265 } 266 }
★ Canute Tide Predictor	JUNE '00	267 £3.05
★ PIC-Gen Frequency Generator/Counter	JULY '00	268 £5.07
G-Meter		269 £4.36
★ <i>EPE</i> Moodloop	AUG '00	271 £5.47
Quiz Game Indicator		272 £4.52
Handy-Amp		273 £4.52
Active Ferrite Loop Aerial	SEPT '00	274 £4.67
★ Remote Control IR Decoder	Software only	–
★ PIC Dual-Channel Virtual Scope	OCT '00	275 £5.15
Handclap Switch	NOV '00	270 £3.96
★ PIC Pulsometer	Software only	–
Twinkling Star	DEC '00	276 £4.28
Festive Fader		277 £5.71
Motorists' Buzz-Box		278 £5.39
★ PICtogram		279 £4.91
★ PIC-Monitored Dual PSU-1 PSU Monitor Unit		280 £4.75
		281 £5.23
Static Field Detector (Multi-project PCB)		932 £3.00
Two-Way Intercom	JAN '01	282 £4.76
UFO Detector and Event Recorder		283 } Set £6.19
Magnetic Anomaly Detector		284 }
Event Recorder		285 }
Audio Alarm		–
★ Using PICs and Keypads	Software only	–
Ice Alarm	FEB '01	287 £4.60
★ Graphics L.C.D. Display with PICs (Supp)		288 £5.23
Using the LM3914-6 L.E.D. Bargraph Drivers		289 } Set £7.14
Multi-purpose Main p.c.b.		290 }
Relay Control		291 }
L.E.D. Display		–
★ PC Audio Power Meter	Software only	–
Doorbell Extender: Transmitter	MAR '01	292 £4.20
Receiver		293 £4.60
Trans/Remote		294 £4.28
Rec./Relay		295 £4.92
<i>EPE</i> Snug-bug Heat Control for Pets	APR '01	296 £6.50
Intruder Alarm Control Panel		297 £6.97
Main Board		298 £4.76
External Bell Unit		–
Camcorder Mixer	MAY '01	299 £6.34
★ PIC Graphics L.C.D. Scope		300 £5.07
Hosepipe Controller	JUNE '01	301 £5.14
Magfield Monitor (Sensor Board)		302 £4.91
Dummy PIR Detector		303 £4.36
★ PIC16F87x Extended Memory	Software only	–
Stereo/Surround Sound Amplifier	JULY '01	304 £4.75
Perpetual Projects Uniboard-1		305 £3.00
Solar-Powered Power Supply & Voltage Reg.		306 £4.75
MSF Signal Repeater and Indicator		307 £4.44
Repeater Board		308 £5.39
Meter Board		–
★ PIC to Printer Interface		309 £4.99
Lead/Acid Battery Charger	AUG '01	310 £5.07
Shortwave Loop Aerial		311 £6.50
★ Digitimer – Main Board		312 £4.36
– R.F. Board		–
Perpetual Projects Uniboard-2		305 £3.00
L.E.D. Flasher – Double Door-Buzzer		305 £3.00
Perpetual Projects Uniboard-3	SEPT '01	305 £3.00
Loop Burglar Alarm, Touch-Switch Door-Light and Solar-Powered Rain Alarm		313 } Set £6.10
L.E.D. Super Torches – Red Main		314 }
– Display Red		315 £4.28
– White L.E.D.		316 £5.94
★ Sync Clock Driver		317 £4.91
★ Water Monitor		–

PROJECT TITLE	Order Code	Cost
Camcorder Power Supply	OCT '01	318 £5.94
PIC Toolkit Mk3		319 £8.24
Perpetual Projects Uniboard-4. Gate Sentinel, Solar-powered Bird Scarer and Solar-Powered Register		305 £3.00
Teach-In 2002 Power Supply	NOV '01	320 £4.28
Lights Needed Alert		321 £5.39
Pitch Switch		322 £5.87
Capacitance Meter – Main Board (double-sided)		323 } Set £12.00
– Display Board (double-sided)		324 }
★ ★ PIC Toolkit TK3 – Software only		–
4-Channel Twinkling Lights	DEC '01	325 £6.82
Ghost Buster – Mic		326 } Set £5.78
– Main		327 }
★ PIC Polywhatsit – Digital		328 } Set £7.61
– Analogue		329 }
Forever Flasher	JAN '02	330 £4.44
Time Delay Touch Switch		331 £4.60
★ PIC Magick Musick		332 £5.87
Versatile Bench Power Supply		333 £5.71
★ PIC Spectrum Analyser	FEB '02	334 £7.13
Versatile Current Monitor		335 £4.75
Guitar Practice Amp		336 £5.39
★ PIC Virus Zapper	MAR '02	337 £4.75
RH Meter		338 £4.28
★ PIC Mini-Enigma – Software only		–
★ Programming PIC Interrupts – Software only		–
★ PIC Controlled Intruder Alarm	APR '02	339 £6.50
★ PIC Big Digit Display	MAY '02	341 £6.02
Washing Ready Indicator		342 £4.75
Audio Circuits-1 – LM386N-1		343 £4.28
– TDA7052		344 £4.12
– TBA820M		345 £4.44
– LM380N		346 £4.44
– TDA2003		347 £4.60
– Twin TDA2003		348 £4.75
World Lamp	JUNE '02	340 £5.71
Simple Audio Circuits-2 – Low, Med and High Input Impedance Pre-amplifiers (Single Trans.)		349 £4.60
Low-Noise Pre-amplifier (Dual Trans.)		350 £4.75
Tone Control		351 £4.60
Bandpass Filter		352 £4.75
Frequency Standard Generator – Receiver		353 £4.12
– Digital		354 £6.82
355 £5.71		
★ Biopic Heartbeat Monitor		–
Simple Audio Circuits – 3	JULY '02	356 £4.60
– Dual Output Power Supply		357 £4.44
– Crossover/Audio Filter		358 £4.91
Infra-Red Autoswitch		359 £6.50
★ <i>EPE</i> StyloPIC		360 £5.39
Rotary Combination Lock – Main Board		361 £4.91
– Interface Board		–
★ Using the PIC's PCLATH Command – Software only		–

EPE SOFTWARE

Software programs for *EPE* projects marked with a single asterisk ★ are available on 3.5 inch PC-compatible disks or free from our Internet site. The following disks are available: *PIC Tutorial* (Mar-May '98); *PIC Toolkit Mk2 V2.4d* (May-Jun '99); *EPE Disk 1* (Apr '95-Dec '98); *EPE Disk 2* (1999); *EPE Disk 3* (2000); *EPE Disk 4* (2001); *EPE Disk 5* (Jan 2002 issue to current cover date); *EPE Teach-In 2000*; *EPE Spectrum*; *EPE Interface Disk 1* (October '00 issue to current cover date). ★ ★ PIC Toolkit TK3 software (Nov '01) is on CD-ROM. The 3.5 inch disks are £3.00 each (UK), the CD-ROM is £6.95 (UK). Add 50p each for overseas surface mail, and £1 each for airmail. All are available from the *EPE PCB Service*. All files can be downloaded free from our Internet FTP site: <ftp://ftp.epemag.wimborne.co.uk>.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code Project Quantity Price

Name

Address

Tel. No.

I enclose payment of £..... (cheque/PO in £ sterling only) to:



**Everyday
Practical Electronics**
MasterCard, Amex, Diners
Club, Visa or Switch



Card No.

Card Exp. Date..... Switch Issue No.....


Signature.....

NOTE: You can also order p.c.b.s by phone, Fax, Email or via our Internet site on a secure server:

<http://www.epemag.wimborne.co.uk/shopdoor.htm>

**WHETHER ELECTRONICS IS YOUR HOBBY
OR YOUR LIVELIHOOD . . .
YOU NEED THE MODERN ELECTRONICS MANUAL
and the ELECTRONICS SERVICE MANUAL**

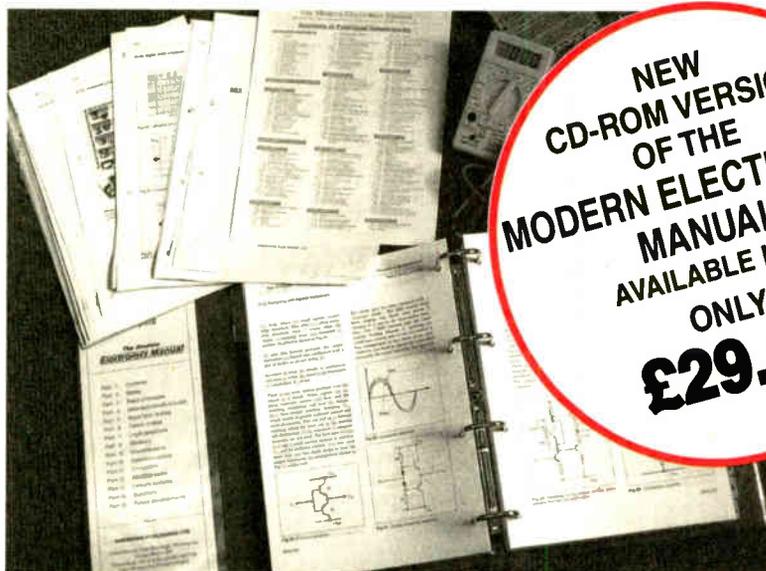THE MODERN ELECTRONICS MANUAL (CD-ROM VERSION ONLY)



**NEW
CD-ROM VERSION
OF THE
MODERN ELECTRONICS
MANUAL
AVAILABLE NOW
ONLY
£29.95**

*The essential reference
work for everyone
studying electronics*

- Over 800 pages
- In-depth theory
- Projects to build
- Detailed assembly instructions
- Full components checklists
- Extensive data tables
- Manufacturers' web links
- Easy-to-use Adobe Acrobat format
- Clear and simple layout
- Comprehensive subject range
- Professionally written
- Regular Supplements

EVERYTHING YOU NEED TO GET STARTED AND GO FURTHER IN ELECTRONICS!

The revised CD-ROM edition of the Modern Electronics Base Manual (MEM) contains practical, easy-to-follow information on the following subjects:

BASIC PRINCIPLES: Electronic Components and their Characteristics (16 sections from Resistors and Potentiometers to Crystals, Crystal Modules and Resonators); Circuits Using Passive Components (10 sections); Power Supplies; The Amateur Electronics Workshop; The Uses of Semiconductors; Digital Electronics (6 sections); Operational Amplifiers; Introduction to Physics, including practical experiments; Semiconductors (5 sections) and Digital Instruments (3 sections).

CIRCUITS TO BUILD: There's nothing to beat the satisfaction of creating your own projects. From basic principles, like soldering and making printed circuit boards, to the tools needed for circuit-building, the Modern Electronics Manual and its Supplements describe clearly, with appropriate diagrams, how to assemble a radio, loudspeaker circuits, amplifiers, car projects,

a computer interface, measuring instruments, workshop equipment, security systems, medical and musical circuits, etc. The Base Manual describes 12 projects including a Theremin and a Simple TENS Unit.

ESSENTIAL DATA: Extensive tables on diodes, transistors, thyristors and triacs, digital and linear i.c.s.

EXTENSIVE GLOSSARY: Should you come across a technical word, phrase or abbreviation you're not familiar with, simply look up the glossary included in the Manual and you'll find a comprehensive definition in plain English.

The Manual also covers **Safety** and provides web links to component and equipment **Manufacturers and Suppliers**. The most comprehensive reference work ever produced at a price you can afford, the CD-ROM edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the **essential** information you need.

THE MODERN ELECTRONICS MANUAL (MEM - CD-ROM version only)

Revised CD-ROM Edition of Basic Work: Contains over 800 pages of information in Adobe Acrobat format. Edited by John Becker.

Regular Supplements: Additional CD-ROMs each containing approximately 500 pages of additional information on specific areas of electronics will be available for £19.95 each. Information on the availability and content of each Supplement CD-ROM will be sent to you as they become available.

Presentation: CD-ROM suitable for any modern PC. Requires Adobe Acrobat Reader which is included on the MEM CD-ROM.

Price of the Basic Work: £29.95 POST FREE.

ORDER BOTH MANUALS TOGETHER AND SAVE £10

A mass of well-organised and clearly explained information is brought to you by expert editorial teams whose combined experience ensures the widest coverage

Regular Supplements to these unique publications, keep you abreast of the latest technology and techniques if required

ELECTRONICS SERVICE MANUAL

(PRINTED VERSION ONLY)

EVERYTHING YOU NEED TO KNOW TO GET STARTED IN REPAIRING AND SERVICING ELECTRONIC EQUIPMENT

SAFETY: Be knowledgeable about Safety Regulations, Electrical Safety and First Aid.

UNDERPINNING KNOWLEDGE: Specific sections enable you to Understand Electrical and Electronic Principles, Active and Passive Components, Circuit Diagrams, Circuit Measurements, Radio, Computers, Valves and Manufacturers' Data, etc.

PRACTICAL SKILLS: Learn how to identify Electronic Components, Avoid Static Hazards, Carry Out Soldering and Wiring, Remove and Replace Components.

TEST EQUIPMENT: How to Choose and Use Test Equipment, Assemble a Toolkit, Set Up a Workshop, and Get the Most from Your Multimeter and Oscilloscope, etc.

SERVICING TECHNIQUES: The regular Supplements include vital guidelines on how to Service Audio Amplifiers, Radio Receivers, TV Receivers, Cassette Recorders, Video Recorders, Personal Computers, etc.

TECHNICAL NOTES: Commencing with the IBM PC, this section and the regular Supplements deal with a very wide range of specific types of equipment – radios, TVs, cassette recorders, amplifiers, video recorders etc..

REFERENCE DATA: Detailing vital parameters for Diodes, Small-Signal Transistors, Power Transistors, Thyristors, Triacs and Field Effect Transistors. Supplements include Operational Amplifiers, Logic Circuits, Optoelectronic Devices, etc.

The essential work for servicing and repairing electronic equipment

- Around 900 pages
- Fundamental principles
- Troubleshooting techniques
- Servicing techniques
- Choosing and using test equipment
- Reference data
- Easy-to-use format
- Clear and simple layout
- Vital safety precautions
- Professionally written
- Regular Supplements
- Sturdy gold blocked ring-binder

ELECTRONICS SERVICE MANUAL (ESM - Printed version only)

Basic Work: Contains around 900 pages of information. Edited by Mike Tooley BA
Regular Supplements: Unlike a book or encyclopedia, this Manual is a living work – continuously extended with new material. If requested, Supplements are sent to you on approval approximately every three months. Each Supplement contains around 160 pages – all for only £23.50+£2.50 p&p. You can, of course, return any Supplement (within ten days) which you feel is superfluous to your needs. You can also purchase a range of past Supplements to extend your Base Manual on subjects of particular interest to you.

Presentation: Durable looseleaf system in large A4 format

Price of the Basic Work: £29.95
 (to include a recent Supplement FREE).



Guarantee

Our 30 day money back guarantee gives you complete peace of mind. If you are not entirely happy with the *Electronics Service Manual*, for whatever reason, simply return it to us in good condition within 30 days and we will make a full refund of your payment – no small print and no questions asked. All we ask is that you pay the return postage. (Overseas buyers also have to pay our overseas postage charge). Sorry, but we can only make exchanges on the *Modern Electronics Manual* (CD-ROM version) if the CD-ROM is faulty, we cannot offer a money back guarantee on this product as the content can be printed out.

Wimborne Publishing Ltd., Dept Y7, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562.
 Online shop: www.epemag.wimborne.co.uk/shopdoor.htm

PLEASE send me



- THE MODERN ELECTRONICS MANUAL (CD-ROM version only)
- ELECTRONICS SERVICE MANUAL plus a FREE SUPPLEMENT (Printed version only)
- I enclose payment of £29.95 (for one Manual) or £49.90 for both Manuals (saving £10 by ordering both together) plus postage if applicable.
- I also require the appropriate ESM Supplements four times a year. These are billed separately and can be discontinued at any time. (Please delete if not required.)

FULL NAME
 (PLEASE PRINT)

ADDRESS

.....POSTCODE

SIGNATURE

- I enclose cheque/PO in UK pounds payable to Wimborne Publishing Ltd.
- Please charge my Visa/Mastercard/Amex/Diners Club/Switch Switch Issue No.....

Card No. Card Exp. Date

ORDER FORM

Simply complete and return the order form with your payment to the following address:

Wimborne Publishing Ltd, Dept. Y7, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND

We offer a 30 day MONEY BACK GUARANTEE on ESM – see the panel above for details.

POSTAGE CHARGES FOR ESM

MEM CD-ROM POST FREE TO ALL COUNTRIES
 (Note we use the VAT portion of the MEM CD-ROM payment to pay for overseas postage)

Postal Region	Price PER ESM PRINTED MANUAL	
	Surface	Air
Mainland UK	FREE	–
Scottish Highlands, UK Islands & Eire	£7 each	–
Europe (EU)	–	£23 each
Europe (Non-EU)	£23 each	£30 each
USA & Canada	£28 each	£39 each
Far East & Australasia	£35 each	£43 each
Rest of World	£28 each	£52 each

Please allow four working days for UK delivery.
 NOTE: Surface mail can take over 10 weeks to some parts of the world. Each ESM weighs about 4kg when packed.

Everyday Practical Electronics reaches twice as many UK readers as any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last seventeen years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. VAT must be added. Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, Mill Lodge, Mill Lane, Thorpe-le-Soken, Essex CO16 0ED. Phone/Fax (01255) 861161.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

TOTALROBOTS

ROBOTICS, CONTROL & ELECTRONICS TECHNOLOGY

High quality robot kits and components
UK distributor of the OOPic microcontroller

Secure on-line ordering
Rapid delivery
Highly competitive prices

Visit www.totalrobots.com

Tel: 01372 741954

New PCB Product

MAGTRIX CONNECTORS™

Division of Victor Ignition Ltd

21st Century Battery Connection
+ Advanced Design Flexibility
in a Minimum of Space

Send for leaflet

Email: sales@victorignition.co.uk

Tel: 01254 830761

Fax: 01254 830408

Valve Output Transformers: Single ended 50mA, £4.50, push/pull 50W, £38; 100W, £53. Mains Transformers: Sac 220V 30mA 6V 1A, £3; 250V 60mA 6V 2A, £5; 250V 80mA 6V 2A, £6. High Voltage Caps: 50µF 350V, 68µF 500V, 150µF 385V, 220µF 400V, 330µF 400V, 470µF 385V, all £3 ea., 32-32µF 450V £5, 4µF 800V oil filled paper block £10, 10H 200mA choke £14. Postage extra. Record Decks and Spares: BSR, Garrard, Goldring, motors, arms, wheels, headshells, spindles, etc. Send or phone your want list for quote.

RADIO COMPONENT SPECIALISTS



337 WHITEHORSE ROAD, CROYDON
SURREY, CR0 2HS. Tel: (020) 8684 1666

Lots of transformers, high volt caps, valves, output transformers, speakers, in stock. Phone or send your wants list for quote.

ELECTRONICS SURPLUS SALE

Send now for a 5kg assorted parcel of electronic components containing resistors, capacitors, semiconductors, connectors, switches and other miscellaneous items, only £10 (plus p&p £1.25). Payment can be made by any major credit/debit card (Visa, Mastercard, Switch, Delta, Electron, Solo), cheque or postal order or send see for a bargain list to:

FML ELECTRONICS

FREEPOST NEA 3627 BEDALE, NORTH YORKSHIRE DL8 2BR
SPECIALIST SUPPLIERS OF SEMICONDUCTORS, RESISTORS, CAPACITORS
AND OTHER ELECTRONIC COMPONENTS AT COMPETITIVE PRICES
TEL: 01677 425840

Z88

NOW AVAILABLE WITH
128K AND 512K - OZ4

ALSO SPECTRUM AND QL PARTS

W. N. RICHARDSON & CO.
PHONE/FAX 01494 871319

E-mail: wnr@compuserve.com
RAVENSMEAD, CHALFONT ST PETER, BUCKS, SL9 0NB

BOWOOD ELECTRONICS LTD

Contact Will Outram for your
Electronic Components

Email: sales@bowood-electronics.co.uk

Web: www.bowood-electronics.co.uk

7 Bakewell Road, Baslow, Derbyshire DE45 1RE

Tel/Fax: 01246 583777

Send 41p stamp for catalogue

X-10® Home Automation We put you in control™

Why tolerate when you can automate?

An extensive range of 230V X-10 products and starter kits available. Uses proven Power Line Carrier technology, no wires required.

Products Catalogue available Online.

Worldwide delivery.

Laser Business Systems Ltd.

E-Mail: info@laser.com

<http://www.laser.com>

Tel: (020) 8441 9788

Fax: (020) 8449 0430



OLIMEX

<http://www.olimex.com/pcb>

PCB prototypes for \$26

FR-4, 1.5 mm, 35/35 um copper,
160x100 mm, double side, PTH,
soldermask, component silkscreen
production in 3-5 working days
made in Bulgaria
no import tax to Europe, UK and US

BTEC ELECTRONICS TECHNICIAN TRAINING

VCE ADVANCED ENGINEERING
ELECTRONICS AND ICT
HNC AND HND ELECTRONICS
NVQ ENGINEERING AND IT

Next course commences

16th SEPTEMBER 2002

FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE
(Dept EPE) 20 PENYVERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: (020) 7373 8721

VVT TRANSFORMERS

Transformers and Chokes for all types
of circuits including specialist valve units
Custom design or standard range
High and low voltage

Variable Voltage Technology Ltd

Unit 24 Samuels Whites Estate

Cowes, Isle of Wight PO31 7LP

Tel: 01983 280592 Fax: 01983 280593

email: sales@vvt-cowes.freemove.co.uk

www.vvttransformers.co.uk

PARTY/DISCO LIGHTS

All mains 240 Volt. New, boxed and ready to use.
FREE DELIVERY, MAIL ORDER ONLY

MAINS MINI STROBE. Adjustable flash rate 1-10 flashes/second.
Quality grey steel case with bracket. £24.95.

4-BULB DISCO PARTY LIGHT. Takes 4 R080 coloured bulbs.
Sequences without music, speeds up with music beat. Quality
metal case and stand. £44.50

MIRROR BALL KIT. 8 inch (20cm) mirror ball, 240V rotator, 240V
pin spotlight and bulb. 5 coloured filters. Bargain £44.50

ROPE LIGHT. 3 coloured channels, 6 metres long. Speed con-
troller. Crushed ice effect flexible tube. Versatile effect. £39.95.

Send Cheque or Postal Order PAYABLE TO B. SIMMONDS to:

SIMMONDS SURPLUS CO.

12 Marina Drive, Wolverton, Bucks MK12 5DW

Tel: 01908 225254

www.luv-it-electronics.co.uk

Quality Components at lowest ever price

Mail order only - we do not deal in credit cards

If we have not got it we send you a cheque back

We only deal in Cheques or Postal Orders

www.luv-it-electronics.co.uk

Phone 01843 570905

Miscellaneous

FREE PROTOTYPE PRINTED CIRCUIT
BOARDS! Free prototype p.c.b. with quantity
orders. Call Patrick on 028 9073 8897 for
details. Agar Circuits, Unit 5, East Belfast
Enterprise Park, 308 Alberbridge Road, Belfast
BT5 4GX.

EDUCATIONAL ELECTRONIC KITS,
GCSE, Physics, Hobbyist. 2 x 1st class stamps
for catalogue. Electroteach, PO Box 2594,
Cannock, WS12 4YH.

www.electroteach.com.

PRINTED CIRCUIT BOARDS - QUICK
SERVICE. Prototype and production artwork
raised from magazines or draft designs at low
cost. PCBs designed from schematics.

Production assembly, wiring and software pro-
gramming. For details contact Patrick at Agar
Circuits, Unit 5, East Belfast Enterprise Park,
308 Alberbridge Road, Belfast, BT5 4GX.
Phone 028 9073 8897, Fax 028 9073 1802,
Email agar@argonet.co.uk.

G.C.S.E. ELECTRONICS KITS, at pocket
money prices. S.A.E. for FREE catalogue. SIR-
KIT Electronics, 52 Severn Road, Clacton,
CO15 3RB. www.geocities.com/sirkituk.

VALVES AND ALLIED COMPONENTS IN
STOCK - please ring for free list. Valve equip-
ment repaired. Geoff Davies (Radio). Phone
01788 574774.

ANNOUNCING A NEW VENTURE! -
metaStable Electronics. Self-assembly kits
for the electronics enthusiast. Visit www.metastable.electronics.btinternet.co.uk.
ELECTRONICS ENGINEER available to
develop your prototype project from schematic
drawing to assembled p.c.b. Phone 01633
895580. Mobile 07748 658567.

STRIPBOARD PROTOTYPE DESIGNER.
Design on your computer for only £20. Try
before you buy. Email: sbpd@foxware.f9.co.uk.

SELLING UP, 1,000s of components, resis-
tors, capacitors, semiconductors, hardware etc.
Also Signal Generator, PSU and part completed
projects. Offers? Tel: 01869 249039.

220 PRACTICAL ELECTRONICS, £20,
collect or carriage extra. (30kg). Leicester
(0116) 2871522.

TRAIN TODAY FOR A BETTER FUTURE

Now you can get the skills and qualifications you need for career success with an ICS Home Study Course. Learn in the comfort of your own home at the pace and times that suit you. ICS is the world's largest, most experienced home study school. Over the past 100 years ICS have helped nearly 10 million people to improve their job prospects. Find out how we can help YOU. Post or phone today for FREE INFORMATION on the course of your choice

Electrical Contracting & Installation
Electrical Engineering
C&G/ICS Basic Electronic Engineering
C&G/ICS Basic Mechanical Engineering
TV and Video Servicing
Radio and Hi-Fi Servicing
Refrigeration Heating & Air Conditioning
Motorcycle Maintenance

FREEPHONE 0500 581 557

Or write to: International Correspondence Schools, FREEPOST 882, 8 Elliot Place, Cldyway Skypark, Glasgow, G3 8BR. Tel: 0500 581 557 or Tel/Fax: Dublin 285 2533

Please send me my Free Information on your Electronics Courses.

Mr/Mrs/Ms/Miss
(BLOCK CAPITALS PLEASE) _____ Date of Birth / /

Address _____

Postcode _____

Occupation _____ Tel. No. _____

From time to time, we permit other carefully screened organisations to write to you about products and services. If you would prefer not to hear from such organisations please tick box Dept. ZEEVC1F2

ELECTRONICS SURPLUS CLEARANCE SALE

FLUKE HANDHELD DIGITAL MULTIMETER MODEL 8024B. Cancelled export order. Brand new and boxed but with original purchasing organisation's small identifying mark on case. With test leads and handbook. List price £150. Our price £47.50. P&P £6.50.

A DIGITAL HANDHELD LCR METER. Measuring inductance, capacitance, resistance. LCD display. Range 2mH to 20H inductance. 2000pF to 200µF capacitance. 200 ohm to 20 megohm resistance. Brand new with test leads and manual. £44.00. P&P £3.50.

12V D.C. TO 240V A.C. 300 WATT POWER INVERTER. Ideal for use in your caravan, car, boat, to run TV, lighting, fridges, recharge your mobile phone, etc. Compact size, brand new and boxed, fully guaranteed. £49.50, p&p £6.50.

250 ¼ watt metal/carbon film resistors	£1	VALVE ASSOCIATED ITEMS	
30 5mm red I.e.d.s	£1	5 High voltage capacitors, 0.1µF 1000V axial	£3
30 BCY71	£1	5 0.05µF 600V axial	£3
30 BCY72	£1	50 Vintage carbon one watt resistors. Useful values	£3
30 BFX30	£1	15 100 ohm wirewound resistors, 3W	£1
30 BC640	£1	5 Valveholders, Octal, B7G, B9A (state which)	£2.50
30 BC558	£1	3 68µF 450V wkg electrolytics, 1¼in. x ¼in. dia.	£2.50
10 OC42 Military spec	£2.50	3 47µF 400V wkg electrolytic, ¼in. x ¼in. dia.	£2.50
30 2N4393	£1	4 22µF 250V wkg electrolytic, 1in. x ¼in. dia. axial	£1
10 555 Timer chips	£1	4 47µF mixed dielectric axial capacitors, 250V wkg	£1
4 IEC 3-pin mains input chassis socket	£1	5 10µF 400V electrolytic, 1in. x ¼in. dia. axial	£2
		5 Terminal block 4 screw terminals, 2¼in. length with fixing holes	£1

BOOKS:

ELECTRIC UFOs by Albert Budden. The effects of electromagnetic pollution, UFOs, fire-balls, abnormal states. 286 pages, photos. £10.

MULLARD HIGH QUALITY SOUND REPRODUCTION. A constructional manual for building valve amplifiers, pre-amps, tuners, circa 1958. 48 large format pages, facsimile copy. £12.50.

MULLARD VALVE DATA AND EQUIVALENTS HANDBOOK. Over 300 pages of valve data, base connections, characteristics and operating conditions for Mullard valves and their equivalent makes. Facsimile reprint. £16.50, p&p £2.25.

Send 2 first class stamps for the *Electronic Surplus Trader* - our latest catalogue full of component bargains, valves, high voltage capacitors, obsolete semiconductors etc.

P&P £1.60 under £10. Over Free unless otherwise stated.

(Dept E) CHEVET SUPPLIES LTD

157 Dickson Road, BLACKPOOL FY1 2EU

Tel: (01253) 751858. Fax: (01253) 302979

E-mail: chevet@globalnet.co.uk Telephone Orders Accepted



SQUIRES

MODEL & CRAFT TOOLS

A COMPREHENSIVE RANGE OF MINIATURE HAND AND POWER TOOLS AND AN EXTENSIVE RANGE OF

ELECTRONIC COMPONENTS

FEATURED IN A FULLY ILLUSTRATED
528 PAGE MAIL ORDER CATALOGUE

2002 ISSUE

**SAME DAY DESPATCH
FREE POST AND PACKAGING**

Catalogues: FREE OF CHARGE to addresses in the UK.
Overseas: CATALOGUE FREE, postage at cost charged to credit card

SHOP EXTENSION NOW OPEN

Squires, 100 London Road,
Bognor Regis, West Sussex, PO21 1DD



TEL: 01243 842424

FAX: 01243 842525




Metal Enclosures

Kit Builder or Project Developer

Off the shelf singles or multiples from our standard range
Specials by arrangement. Please Email your requirements



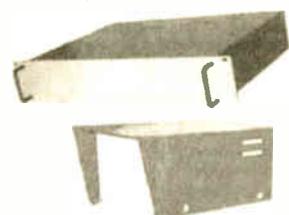Wellberry Cases
(Manufacturers to the trade since 1971)
Ion Farm
Lower Gravenhurst
Beds MK45 4HH
Fax/Phone 01525 860081



Now Available Mail Order
Direct From Manufacturer
Online order form & Catalogue
www.wellberry.co.uk
Email sales@wellberry.co.uk

N. R. BARDWELL LTD (Est. 1948)

100 Signal Diodes 1N4148	£1.00	200 Ass'd. disc ceramic capacitors	£1.00
75 Rectifier Diodes 1N4001	£1.00	50 Ass'd. SMD Presets (sm, stand, cermet)	£1.00
50 Rectifier Diodes 1N4007	£1.00	50 Ass'd. RF chokes (inductors)	£1.00
10 W01 Bridge Rectifiers	£1.00	50 Ass'd. grommets	£1.00
10 555 Timer I.C.s	£1.00	80 Ass'd. solder lugs, piconns, terminals	£1.00
4 741 Op Amps	£1.00	10 Ass'd. crystals - plug in	£1.00
50 Assorted Zener Diodes 400mW	£1.00	8 Ass'd. oil switches	£1.00
12 Assorted 7-segment Displays	£1.00	20 Miniature slide switches sp/oo	£1.00
25 5mm I.e.d.s, red, green or yellow	£1.00	100 Ass'd. beads (ceramic, teflon, fish spine)	£1.00
25 3mm I.e.d.s, red, green or yellow	£1.00	30 Ass'd. di sockets up to 40 way	£1.00
75 5mm I.e.d.s, green, 6-5mm legs	£1.00	10 TV coax plugs, plastic	£1.00
50 Axial I.e.d.s, 2mcd red Diode Package	£1.00	40 metres very thin connecting wire, red	£1.00
25 Ass'd. High Brightness I.e.d.s, var cots	£1.00	10 1in. glass reed switches	£1.00
20 BC182 Transistors	£1.00	100 Any one value ¼W 5% cf resistors range 1R to 10M	£0.45
25 BC212 Transistors	£1.00	10 7812 Voltage Regulators	£1.00
30 BC237 Transistors	£1.00	300 Ass'd. resistors, W/W/S/W, mostly on tapes	£1.00
20 BC327 Transistors	£1.00	8 Ass'd. push-button switches, multi-bank, multi-pole	£1.00
30 BC328 Transistor	£1.00	40 Ass'd. Radial Electrolytics, 4-7-220µF	£1.00
30 BC547 Transistor	£1.00		
20 BC548 Transistor	£1.00		
30 BC546 Transistors	£1.00		
30 BC549 Transistors	£1.00		
25 BC557 Transistors	£1.00		
30 BC558 Transistors	£1.00		
30 BC559 Transistors	£1.00		
20 2N3904 Transistors	£1.00		
100 1nF 50V wkg Axial Capacitors	£1.00		
100 4N7 50V wkg Axial Capacitors	£1.00		
80 Ass'd capacitors electrolytic	£1.00		
80 Ass'd capacitors 1nF to 1µF	£1.00		

288 Abbeydale Road, Sheffield S7 1FL


Phone: 0114 255 2886 ★ Fax: 0114 255 5039

e-mail: sales@bardwells.co.uk ★ Web: www.bardwells.co.uk

Prices include VAT. Postage £1.65

44p stamp for lists or disk

POs, Cheques and Credit Cards accepted

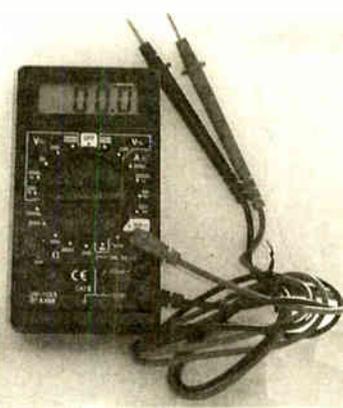

DIGITAL TEST METER

Built-in transistor test socket and diode test position.
DC volts 200mV to 1000V.
AC volts 200V to 750V.
DC current 200mA to 10A.
Resistance 200 ohms to 2000K ohms.

£5.99 incl. VAT

SEE OUR WEB PAGES FOR MORE COMPONENTS AND SPECIAL OFFERS
www.bardwells.co.uk

**FREE 304-page
colour catalogue**

Great value for Speakers, Microphones, Headphones, Aerials, Transmitters, TV Amps, Plugs, Sockets, Leads, CD Storage Cases, CCTV, Security, Connectors, Adaptors, Switch Boxes, Gadgets, Pic-a-Matching & Effects, Mixers, Amplifiers, Turntables, Multi-taps, Leads, Car Audio, Test Equipment, Hobby Kits, Computer Leads & Accessories, Power Supplies, Inverters, Transformers, Battery Chargers, Tools, Soldering, Switches, Fuses, Indicators, Cable & Wire, Crossovers, Speaker Hardware, PA Amps, and a great deal more... all for the price of a stamp.

Sky Electronics
40-42 Cricklewood Broadway,
London, NW2 3ET
Tel: 020 8450 0995
Fax: 020 8208 1441
Email: sales@cricklewoodelectronics.com
www.skyelectronics.co.uk

The Catalogue is FREE to shop callers or send stamps to the value of £1.85 to cover postage.

ELECTRONICS 2002

Watch Slides on TV.

Make videos of your slides. Digitise your slides (using a video capture card) "Liesgang diatv" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. More details see www.diatv.co.uk.
£91.91 + VAT = £108.00



Board cameras all with 512 x 582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10V and 12V DC 150mA.
47MIR size 60 x 36 x 27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye) £37.00 + VAT = £43.48
30MP size 32 x 32 x 14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole £35.00 + VAT = £41.13
40MC size 39 x 38 x 27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses £32.00 + VAT = £37.60
Economy C mount lenses all fixed focus & fixed iris
VSL1220F 12mm F1.6 12 x 15 degrees viewing angle £15.97 + VAT £18.76
VSL4022F 4mm F1.22 63 x 47 degrees viewing angle £17.65 + VAT £20.74
VSL6022F 6mm F1.22 42 x 32 degrees viewing angle £19.05 + VAT £22.38
VSL8020F 8mm F1.22 32 x 24 degrees viewing angle £19.90 + VAT £23.38

Better quality C Mount lenses

VSL1614F 16mm F1.6 30 x 24 degrees viewing angle £26.43 + VAT £31.06
VWL813M 8mm F1.3 with iris 56 x 42 degrees viewing angle £77.45 + VAT = £91.00
1206 surface mount resistors E12 values 10 ohm to 1M ohm
100 of 1 value £1.00 + VAT 1000 of 1 value £5.00 + VAT

866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily
£7.46 + VAT = £8.77



Please add £1.66 + vat = £1.95 postage & packing per order

JPG Electronics
Shaws Row, Old Road, Chesterfield, S40 2RB.
Tel 01246 211202 Fax 01246 550959
Mastercard/Visa/Switch
Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

SHERWOOD ELECTRONICS

FREE COMPONENTS

Buy 10 x £1 Special Packs and choose another one FREE

SP1 15 x 5mm Red LEDs	SP135 6 x Miniature slide switches
SP2 12 x 5mm Green LEDs	SP136 3 x BFY50 transistors
SP3 12 x 5mm Yellow LEDs	SP137 4 x W005 1-5A bridge rectifiers
SP6 15 x 3mm Red LEDs	SP138 20 x 2/63V radial elect. caps.
SP7 12 x 3mm Green LEDs	SP140 3 x W04 1-5A bridge rectifiers
SP8 10 x 3mm Yellow LEDs	SP142 2 x CMOS 4017
SP10 100 x 1N4148 diodes	SP143 5 Pairs min. crocodile clips (Red & Black)
SP11 30 x 1N4001 diodes	SP145 6 x ZTX300 transistors
SP12 30 x 1N4002 diodes	SP146 10 x 2N3704 transistors
SP20 20 x BC184 transistors	SP147 5 x Stripboard 9 strips x 25 holes
SP21 20 x BC212 transistors	SP151 4 x 8mm Red LEDs
SP23 20 x BC549 transistors	SP152 4 x 8mm Green LEDs
SP24 4 x CMOS 4001	SP153 4 x 8mm Yellow LEDs
SP25 4 x 555 timers	SP154 15 x BC548 transistors
SP26 4 x 741 Op.Amps	SP156 3 x Stripboard, 14 strips x 27 holes
SP28 4 x CMOS 4011	SP160 10 x 2N3904 transistors
SP29 3 x CMOS 4013	SP161 10 x 2N3906 transistors
SP34 20 x 1N914 diodes	SP165 2 x LF351 Op.Amps
SP36 25 x 10/25V radial elect. caps.	SP166 20 x 1N4003 diodes
SP37 12 x 100/35V radial elect. caps.	SP167 6 x BC107 transistors
SP39 10 x 470/16V radial elect. caps.	SP168 6 x BC108 transistors
SP40 15 x BC237 transistors	SP172 4 x Standard slide switches
SP41 20 x Mixed transistors	SP175 20 x 1/63V radial elect. caps.
SP42 200 x Mixed 0.25W C.F. resistors	SP177 10 x 1A 20mm quick blow fuses
SP47 5 x Min. PB switches	SP182 20 x 4-7/63V radial elect. caps.
SP49 4 x 5 metres stranded core wire	SP183 20 x BC547 transistors
SP102 20 x 8-pin DIL sockets	SP187 15 x BC239 transistors
SP103 15 x 14-pin DIL sockets	SP189 4 x 5 metres solid core wire
SP104 15 x 16-pin DIL sockets	SP192 3 x CMOS 4066
SP109 15 x BC557 transistors	SP193 20 x BC213 transistors
SP112 4 x CMOS 4093	SP195 3 x 10mm Yellow LEDs
SP115 3 x 10mm Red LEDs	SP197 6 x 20 pin DIL sockets
SP116 3 x 10mm Green LEDs	SP198 5 x 24 pin DIL sockets
SP124 20 x Assorted ceramic disc caps	SP199 5 x 2.5mm mono jack plugs
SP126 8 x Battery clips - 4 ea. PP3 + PP9	SP200 5 x 2.5mm mono jack sockets
SP130 100 x Mixed 0.5W C.F. resistors	
SP131 2 x TL071 Op.Amps	
SP133 20 x 1N4004 diodes	
SP134 15 x 1N4007 diodes	

RESISTOR PACKS - C.Film

RP3 5 each value - total 365 0.25W	£3.00
RP7 10 each value - total 730 0.25W	£4.25
RP10 1000 popular values 0.25W	£6.15
RP4 5 each value-total 365 0.5W	£4.00
RP8 10 each value-total 730 0.5W	£6.65
RP11 1000 popular values 0.5W	£8.40

2002 Catalogue now available £1 Inc. P&P or FREE with first order.

P&P £1.25 per order. NO VAT

Orders to:

Sherwood Electronics,
7 Williamson St., Mansfield,
Notts. NG19 6TD

ADVERTISERS INDEX

AUDON ELECTRONICS	470
N. R. BARDWELL	543
BITZ TECHNOLOGY	521
B.K. ELECTRONICS	Cover (iv)/508
BULL ELECTRICAL	Cover (ii)
CHEVET SUPPLIES	543
CRICKLEWOOD ELECTRONICS	470
CROWNHILL ASSOCIATES	Cover (iii)
DISPLAY ELECTRONICS	466
ESR ELECTRONIC COMPONENTS	474
FOREST ELECTRONIC DEVELOPMENTS	471
ICS	543
JPG ELECTRONICS	544
LABCENTER	481
MAGENTA ELECTRONICS	472/473
MILFORD INSTRUMENTS	485
PICO TECHNOLOGY	497
QUASAR ELECTRONICS	468/469
SHERWOOD ELECTRONICS	544
SKY ELECTRONICS	544
SQUIRES	543
STEWART OF READING	470
VANN DRAPER ELECTRONICS	508
WCN SUPPLIES	487
WELLBURY CASES	543

ADVERTISEMENT MANAGER: PETER J. MEW

ADVERTISEMENT OFFICES:

EVERYDAY PRACTICAL ELECTRONICS, ADVERTISEMENTS,
MILL LODGE, MILL LANE, THORPE-LE-SOKEN,
ESSEX CO16 0ED.

Phone/Fax: (01255) 861161

For Editorial address and phone numbers see page 475

PIC BASIC COMPILERS

Crownhill Associates
smart electronic solutions

PIC Basic Plus & PIC Basic Pro Compilers

PIC BASIC Plus, supports the popular 14 bit Microchip PIC-Microcontrollers, allowing the user to write professional programs in BASIC. The compilers produce fast, tight machine code to load directly into the PIC-Microcontroller. The Compiler produces code that is guaranteed 100% compatible with Microchips MPASM assembler. The compiler allows direct comparison between the BASIC program and the assembly listing. Two compilers are available, the PIC Basic Pro, entry level compiler and PIC BASIC Plus, professional compiler. Both produce fast assembly code from BASIC. The Compilers run under Windows 95,98,NT,ME and XP and are supplied with a comprehensive, Windows based editor with Syntax highlighting and just two key clicks to compile and program and detailed manuals with worked examples. The Compilers support a range of programmers including the Microchip PICStart-plus and our own development programmers. For a free demo of the Pro compiler visit our web site www.letbasic.com, or join our web based forum to hear what other users think of our compilers and supporting products... (PIC BASIC Pro is supplied with the book "Experimenting with the LET Basic Pro compiler" by Les Johnson, an invaluable guide for the beginner. See the web site for an example chapter).


Technical support is provided online via our web based forum, www.picbasic.org, or to tutors via telephone direct from the Author. Additional support can be provided to tutors using our development system for educational purposes.



Development system



Prototype PCB system

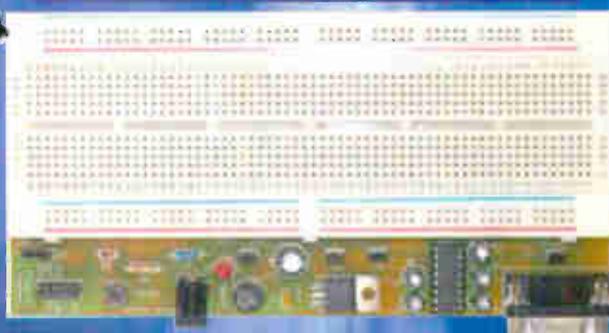

Supplied with source code and documentation for 20 Educational projects. Supports LCD displays from 2x16 Chrs to 128x64 dot matrix Graphics panel

Programmers



All supporting components stocked at competitive prices
e.g PIC 16F84 04 /P - £1.80 each, PIC 16F877 04 /P £3.95 each
LCD 2x16 Chrs, £7.50 each LCD 128x64 dot matrix £15.95 each
Many more items stocked, email sales@crowhill.co.uk for prices

WorldRadioHistory

£49.95 - PRO
£99.95 - PLUS

Visit our web sites: www.picbasic.org

www.letbasic.com

32, Broad Street, Ely
Cambridge, CB7 4AH

Tel: +44 (0) 1353 666709
Fax: +44 (0) 1353 666710
sales@crowhill.co.uk

All prices exclude:
VAT, postage and packing



POWER AMPLIFIER MODULES-LOUDSPEAKERS-MIXERS 19 INCH STEREO AMPLIFIERS-ACTIVE CROSS/OVERS.

* PRICES INCLUDE V.A.T.
* PROMPT DELIVERY

OMP MOS-FET POWER AMPLIFIERS HIGH POWER, TWO CHANNEL 19 INCH RACK

10,000's
SOLD
TO PRO
USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)
MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS ARE R.M.S. INTO 4 OHMS, WITH BOTH CHANNELS DRIVEN
FEATURES:- * Independent power supplies with two toroidal transformers
* Twin L.E.D. Vu Meters * Level controls * Illuminated on/off switch * Jack / XLR inputs
* Speakon Outputs * Standard 775mv inputs * Open and Short circuit proof * Latest Mos-Fets
for stress free delivery into virtually any load * High slew rate * Very low distortion * Aluminium
cases * MXF600 & MXF900 fan cooled with D.C. Loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC

SIZES:-
MXF200 W19" D11" H3 1/2" (2U)
MXF400 W19" D12" H5 1/4" (3U)
MXF600 W19" D13" H5 1/4" (3U)
MXF900 W19" D14" H5 1/4" (3U)

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL £12.50 Each



FLIGHTCASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of latest loudspeaker technology and enclosure designs. All models utilise high quality studio cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands. The FC15-300 incorporates a large 16 X 6 inch horn. All cabinets are fitted with the latest Speakon connectors for your convenience and safety. Five models to choose from.

WOMEN
SOFT-TOE



PLEASE NOTE:- POWER RATINGS
QUOTED ARE IN WATTS R.M.S. FOR
EACH INDIVIDUAL CABINET ALL
ENCLOSURES ARE 8 OHMS

15=15 Inch speaker
12=12 Inch speaker

- ibl FC15-300 WATTS Freq Range 35Hz-20kHz, Sens 101dB, Size H695 W502 D415mm
Price:- £299.00 per pair
 - ibl FC12-300 WATTS Freq Range 45Hz-20kHz, Sens 96dB, Size H600 W405 D300mm
Price:- £249.00 per pair
 - ibl FC12-200 WATTS Freq Range 40Hz-20kHz, Sens 97dB, Size H600 W405 D300mm
Price:- £199.00 per pair
 - ibl FC12-100 WATTS Freq Range 45Hz-20kHz, Sens 100dB, Size H546 W380 D300mm
Price:- £179.00 per pair
 - ibl WM12-200 WATTS Freq Range 40Hz-20kHz, Sens 97dB, Size H418 W600 D385mm
Price:- £125.00 Each
- SPECIALIST CARRIER DEL:- £12.50 per pair, wedge monitor £7.00 each
Optional Metal Stands PRICE:- £49.00 per pair Delivery:- £6.00

CATALOGUE 2001 2002

Robots

Test & Tools

Electronic Kits

The Sky's
The Limit
Catalogue

Communication

Security

B.K. Electronics

Unit 1, Comet Way, Southend-on-Sea, Essex, SS2 6TR
Tel: 01702-527572 Fax: 01702-420243

FREE Our Sky's The Limit Catalogue with
over 3000 items covering all your interests.
The catalogue is free with any item ordered from this advert
and to personal callers or £4.00 to cover P&P if ordered separately.
This is fully refundable with your first order.

100 WATT ACTIVE SUB BASS AMPLIFIER PANEL



AN ACTIVE SUB BASS AMPLIFIER WITH A TRUE 100W
RMS OUTPUT SUPERB CONSTRUCTION WITH THE
FACILITIES TO INTEGRATE SEEMLESSLY INTO MOST
HI-FI OR HOME CINEMA SETUPS. USE THIS PANEL
PLUS ONE OF OUR LOUDSPEAKERS TO MAKE YOUR
OWN SUB WOOFER THAT WILL MATCH OR BEAT MOST
COMMERCIALLY AVAILABLE SUB WOOFERS.

FEATURES:- * 100W RMS INTO 8 OHMS * HIGH AND
LOW LEVEL INPUTS * TOROIDAL TRANSFORMER
* SHORT CIRCUIT PROTECTION * D.C. SPEAKER
PROTECTION * FREQUENCY ROLL OFF, LOWER
10Hz, UPPER 60Hz TO 240Hz (FULLY ADJUSTABLE)
* AC3 COMPATIBLE FILTER CAN BE BYPASSED
FOR 5-1 FORMATS * AIRTIGHT CONSTRUCTION
* TENS OF THOUSANDS OF OUR PANELS ALREADY
IN USE. * COMPLETE WITH LEADS

SPECIFICATIONS:- * POWER 100W RMS @ 8 OHMS * FREQ RESP. 10Hz 15kHz
-3dB * DAMPING FACTOR >200 * DISTORTION 0.05% * S/N A WEIGHTED
>100dB * SUPPLY 230V A.C. * WEIGHT 2.7Kg * SIZE H254 X W254 X D94mm
THERE ARE 2 VERSIONS OF THE ABOVE PANEL AVAILABLE :-BSB100/8
8 OHM VERSION BSB100/4 4 OHM VERSION BOTH PANELS ARE PRICED AT
£117.44 + £5.00 P&P INCL. V.A.T. CHECK WEBSITE FOR PANELS UP TO 500W

OMP X03-S STEREO 3 WAY ACTIVE CROSSOVER SWITCHABLE 2-WAY



BASS MID TOP BASS/MID TOP BASS MID/TOP
CONFIGURED 3 WAY 2 WAY BASS/MID COMBINED 2 WAY MID/TOP COMBINED

FEATURES:-

Advanced 3-Way Stereo Active Cross-Over (Switchable two way), housed in a 19" x 1U case. Each channel has three level controls: Bass, Mid & Top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency. There are two versions available:- X03-S Bass-Mid 125/250/500Hz, Mid-Top 1.8/3/5kHz, all at 24 dB per octave. X03 Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5kHz, all at 24 dB per Octave. Please make sure you ask for the correct model when ordering. The 2/3 way selector switches are also accessed by removing the front fascia. Each stereo channel can be configured separately. Bass Invert Switches are incorporated on each channel. Nominal 775mV input/output. Fully compatible with the OMP Rack Amplifier and Modules.

BOTH MODELS PRICED AT :- £117.44 + £5.00 P&P

OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY
BUILT AND TESTED

These modules now enjoy a world-wide reputation for quality, reliability, and performance at a realistic price. Four models are available to suit the needs of the professional and home market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heatsink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS

OMP/MF 100 Mos-Fet Output Power 110 watts
R.M.S. into 4 ohms, frequency response 1Hz -
100kHz -3dB, Damping Factor >300, Slew Rate
45V/uS, T.H.D. typical 0.002%, Input Sensitivity
500mV, S.N.R. 110dB, Size 300 x 123 x 60mm.
Price:- £42.85 + £4.00 P&P

OMP/MF 200 Mos-Fet Output Power 200 watts
R.M.S. into 4 ohms, frequency response 1Hz -
100kHz -3dB, Damping Factor >300, Slew Rate
50V/uS, T.H.D. typical 0.001%, Input Sensitivity
500mV, S.N.R. 110dB, Size 300 x 155 x 100mm.
Price:- £66.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output Power 300 watts
R.M.S. into 4 ohms, frequency response 1Hz -
100kHz -3dB, Damping Factor >300, Slew Rate
60V/uS, T.H.D. typical 0.001%, Input Sensitivity
500mV, S.N.R. 110dB, Size 330 x 175 x 100mm.
Price:- £89.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output Power 450 watts
R.M.S. into 4 ohms, frequency response 1Hz -
100kHz -3dB, Damping Factor >300, Slew Rate
75V/uS, T.H.D. typical 0.001%, Input Sensitivity
500mV, S.N.R. 110dB, Fan Cooled, D.C.
Loudspeaker Protection, 2 Second Anti Thump
Delay, Size 385 x 210 x 105mm.
Price:- £135.85 + £6.00 P&P

OMP/MF 1000 Mos-Fet Output Power 1000 watts
R.M.S. into 2 ohms, frequency response 1Hz -
100kHz -3dB, Damping Factor >300, Slew Rate
75V/uS, T.H.D. typical 0.001%, Input Sensitivity
500mV, S.N.R. 110dB, Fan Cooled, D.C.
Loudspeaker Protection, 2 Second Anti Thump
Delay, Size 422 x 300 x 125mm.
Price:- £261.00 + £12.00 P&P

NOTE MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS:
STANDARD - INPUT SENS 500mV/BANDWIDTH 100kHz OR PEC
(PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS
775mV, BANDWIDTH 50kHz ORDER STANDARD OR PEC



DELIVERY CHARGES:- PLEASE INCLUDE AS ABOVE,
TO A MAXIMUM AMOUNT £30.00. OFFICIAL ORDERS
FROM SCHOOL, COLLEGES, GOVT. PLCs ETC. PRICES
INCLUDE OF V.A.T. SALES COUNTER, CREDIT CARD
ORDERS ACCEPTED BY POST PHONE OR FAX.



B.K. ELECTRONICS

REF D5

UNIT 1 COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR.
TEL.: 01702-527572 FAX.: 01702-420243
Web:- <http://www.bkelec.com> E-Mail sales@bkelec.com