

**FREE
SUPPLEMENT**

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EVERYDAY

MAY 2003

PRACTICAL

ELECTRONICS

£2.95

**FREE
SUPPLEMENT**

PIC TUTORIAL V2

Part 2 - The best
introduction to
using PIC
microcontrollers

SUPER MOTION SENSOR

Highly sensitive
auto-adjusting design




DOOR CHIME
Electronic Ding Dong

PLUS

BACK TO BASICS 4
LIVE WIRE DETECTOR • MW RADIO
Two easy to build projects

<http://www.epemag.wimborne.co.uk>

World Radio History

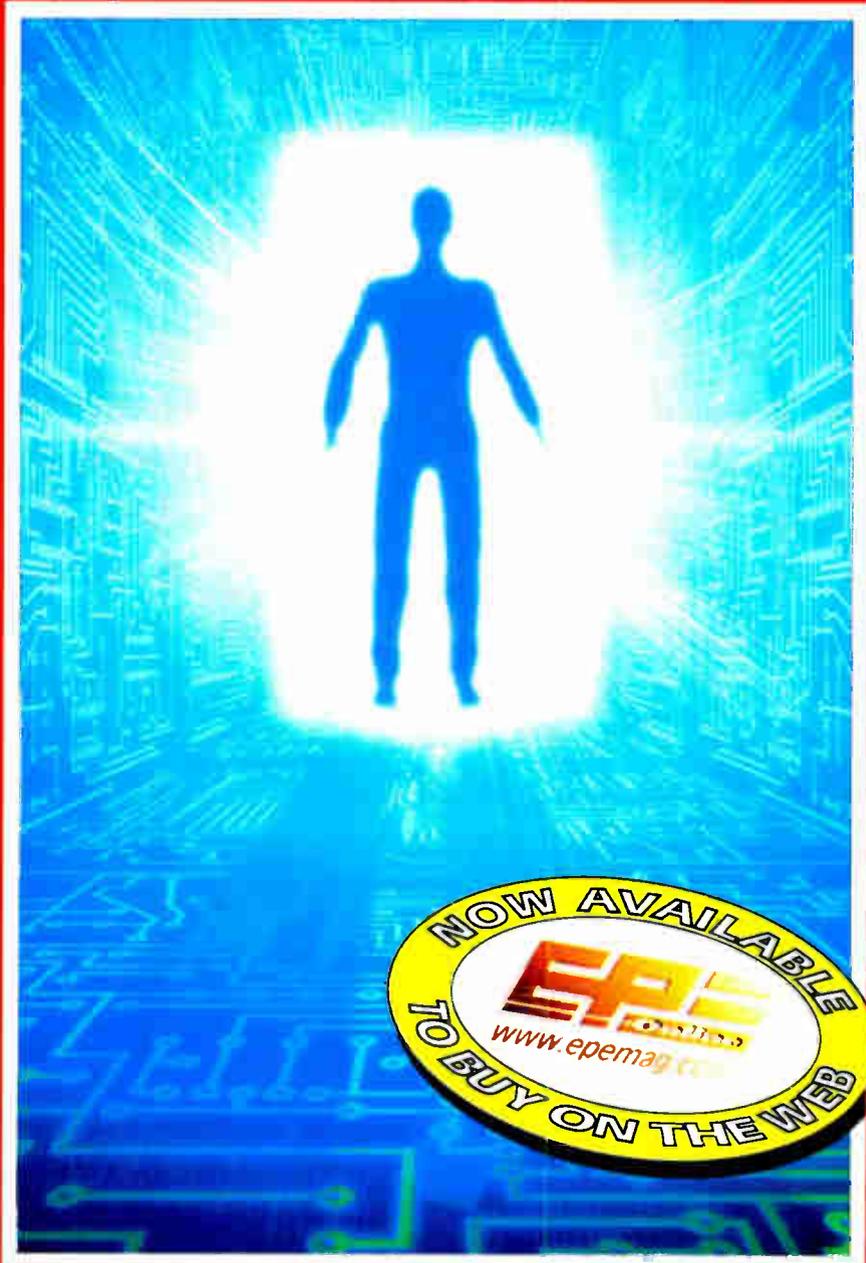

05



Colour CCTV camera. 8mm lens, 12V d.c. 200mA 582x628 Resolution 380 lines Automatic aperture lens Mirror function PAL Back Light Compensation MLR. 100x40x40mm. Ref EE2 £69



Built-in Audio 15lux CCD camera 12V d.c. 200mA 480 lines s/n ratio >48db 1v P-P output 110x60x50mm. Ref EE1 £99



Metal CCTV camera housings for internal or external use. Made from aluminium and plastic they are suitable for mounting body cameras in. Available in two sizes 1 - 100x10x170mm and 2 - 100x70x280mm. Ref EE6 £22 EE7 £26 multi-position brackets. Ref EE8 £8



Excellent quality multi-purpose TV/TFT screen, works as just a LCD colour monitor with any of our CCTV cameras or as a conventional TV. Ideal for use in boats and caravans 49.7MHz-91.75MHz VHF channels 1-5, 168.25MHz-222.75MHz VHF channels 6-12. 471.25MHz-869.75MHz Cable channels 112.325MHz-166.75MHz Z1-Z7. Cable channels 224.25MHz-446.75MHz Z8-Z35 5" colour screen. Audio output 150mW. Connections, external aerial, earphone jack, audio/video input, 12V d.c. or mains. Accessories supplied Power supply, Remote control, Cigar lead power supply, Headphone Stand/bracket. 5" model £139 Ref EE9. 6" model £149. Ref EE10



Fully cased IR light source suitable for CCTV applications. The unit measures 10x10x150mm, is mains operated and contains 54 infra-red LEDs. Designed to mount on a standard CCTV camera bracket. The unit also contains a daylight sensor that will only activate the infra red lamp when the light level drops below a preset level. The infrared lamp is suitable for indoor or exterior use, typical usage would be to provide additional IR illumination for CCTV cameras. £49. Ref EE11



This device is mains operated and designed to be used with a standard CCTV camera causing it to scan. The black clips can be moved to adjust the scan angle, the motor reversing when it detects a clip. With the clips removed the scanner will rotate constantly at approx 2.3rpm. 75x75x80mm £23. Ref EE12



Colour CCTV Camera measures 60x45mm and has a built in light level detector and 12 IR LEDs. 2 lux 12 IR LEDs 12V d.c. Bracket Easy connect leads £69. Ref EE15



A high quality external colour CCTV camera with built in Infra-red LEDs measuring 60x60x60mm Easy connect leads colour Waterproof PAL 1/4" CCD 542x588 pixels 420 lines .05 lux 3.6mm F2 78 deg lens 12V d.c. 400mA Built in light level sensor. £99. Ref EE13



A small compact colour CCTV camera measuring just 35x28x30mm (camera body) Camera is supplied complete with mounting bracket, built in IR, microphone and easy connect leads. Built in audio Built in IR LEDs Colour 380 line resolution PAL 0.2 us +18db sensitivity. Effective pixels 628x582 Power source 6-12V d.c. Power consumption 200mW £36. Ref EE16



Complete wireless CCTV system with video. Kit comprises pinhole colour camera with simple battery connection and a receiver with video output. 380 lines colour 2.4GHz 3 lux 6-12V d.c. manual tuning Available in two versions, pinhole and standard. £79 (pinhole) Ref EE17, £79 (standard). Ref EE18



Small transmitter designed to transmit audio and video signals on 2.4GHz. Unit measures 45x35x10mm. Ideal for assembly into covert CCTV systems Easy connect leads Audio and video input 12V d.c. Complete with aerial Selectable channel switch £30. Ref EE19



2.4GHz wireless receiver Fully cased audio and video 2.4GHz wireless receiver 190x140x30mm, metal case, 4 channel, 12V d.c. Adjustable time delay, 4s, 8s, 12s, 16s. £45. Ref EE20



Colour pinhole CCTV camera module with audio Compact colour pinhole camera measuring just 20x20x20mm, built-in audio and easy connect leads PAL CMOS sensor 6-9V d.c. Effective Pixels 628x582 Illumination 2 lux Definition >240 Signal/noise ratio >40db Power consumption 200mW £35. Ref £35



Self-cocking pistol pliers with metal body. Self-cocking for precise string alignment Aluminium alloy construction High tech fibre glass limbs Automatic safety catch Supplied with three bolts Track style for greater accuracy. Adjustable rearsight 50lb drawweight 150ft sec velocity Break action 17" string 30m range £21.65 Ref PLCR002 **INFRA-RED FILM** 6" square piece of flexible infra-red film that will only allow IR light through. Perfect for converting ordinary torches, lights, headlights etc to infra-red output only using standard light bulbs Easily cut to shape. 6" square £15. Ref IRF2 or a 12" sq for £29 **IRF2A NEW 12" SQUARE SOLAR PANEL** Kevlar backed, 3watt output. Copper strips for easy solder connections £14.99. Ref 15P42 **PACK OF 4 JUST £39.95. REF 15P42SP**



Dummy CCTV cameras These motorised cameras will work either on 2AA batteries or with a standard DC adapter (not supplied) They have a built in movement detector that will activate the camera if movement is detected causing the camera to 'pan' Good deterrent. Camera measures 20cm high, supplied with rawl plugs and fixing screws. Camera also has a flashing red LED built in. £9.95. Ref CAMERAE

BULL ELECTRICAL
 UNIT D, HENFIELD BUSINESS PARK,
 HENFIELD, SUSSEX BN5 9SL
**TERMS: CASH, PO OR CHEQUE WITH ORDER
 PLUS £5.50 P&P (UK) PLUS VAT.
 24 HOUR SERVICE £7.50 (UK) PLUS VAT.
 OVERSEAS ORDERS AT COST PLUS £3.50
 (ACCESS/VISA/SWITCH ACCEPTED)**
'phone: 01273 491490 Fax 491813
Sales@bullnet.co.uk

POWERSAFE DEEP CYCLE BATTERIES



6V 100AH NOW ONLY £19 EACH



12V 51AH NOW ONLY £29.95 EACH



We also have some used 2.3AH 12V (same as above) these are tested and in good condition and available at an extremely good price for bulk buyers, box of 30 just £49.99. Ref SLB23C



Aiptek Pocket DV Up to 2000 still pics before requiring download!! The all new Pocket DV, it's amazing... such advanced technology, such a tiny size - you will be the envy of your friends!! This camera will take up to 3.5 minutes of Video and Audio, up to 2000 digital still pictures or 30 minutes of voice recording! Then just connect it to your PC via the USB cable (Supplied) and after transferring the data you can start all over again!! £69. Ref POCKETDV



The smallest PMR446 radios currently available (54x87x37mm). These tiny handheld PMR radios not only look great, but they are user friendly & packed with features including VOX, Scan & Dual Watch. Priced at £59.99 PER PAIR they are excellent value for money. Our new favourite PMR radios!! Standby: - 35 hours Includes: - 2 x Radios, 2 x Belt Clips & 2 x Carry Strap £59.95 Ref ALAN1 Or supplied with 2 sets of rechargeable batteries and two mains chargers £84.99. Ref Alan2






Beltronics BEL550 Euroradarand GATSO detector Claimed Detection Range: GATSO up 400m, Radar & Laser guns up to 3 miles. Detects GATSO speed cameras at least 200 metres away, plenty of time to adjust your speed £319. Ref BEL550



Fully Portable - Use anywhere Six automatic programmer for full body pain relief, shoulder pain, back/neck pain, aching joints, rheumatic pain, sports injuries **EFFECTIVE DRUG FREE PAIN RELIEF TENS** (Transcutaneous Electrical Nerve Stimulation) units are widely used in hospitals, clinics throughout the United Kingdom for effective drug free pain relief. This compact unit is now approved for home use. TENS works by stimulating nerves close to the skin releasing endorphins (nature's anaesthetics) and helping to block the pain signals sent to the brain. Relief can begin within minutes, and a 30 minute treatment, can give up 12 hours relief or more. The TENS mini Microprocessors offer six types of automatic programme for shoulder pain, back/neck pain, aching joints, Rheumatic pain, migraines headaches, sports injuries, period pain. In fact all over body treatment! Will not interfere with existing medication. Not suitable for anyone with a heart pacemaker. Batteries supplied. £19.95 Ref TEN327 Spare pack of electrodes £5.99. Ref TEN327X

**SHOP ONLINE
 AT
 WWW.BULLNET.CO.UK**

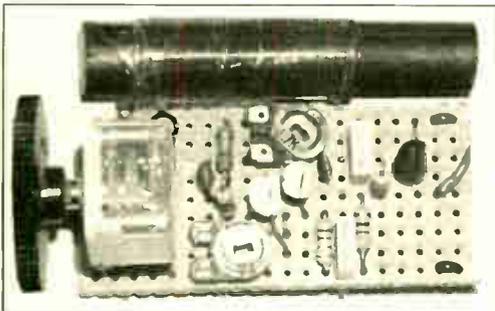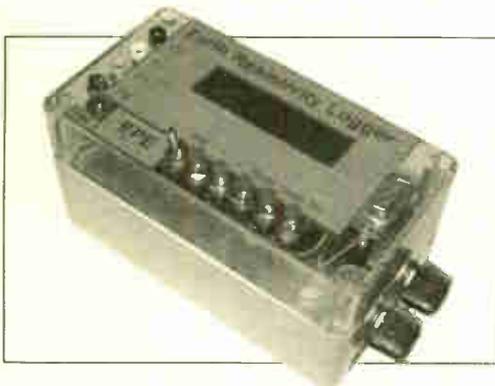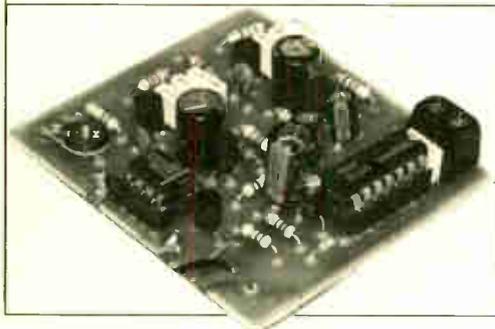

Projects and Circuits

- SUPER MOTION SENSOR** by Thomas Scarborough **316**
A highly responsive design that even detects a single finger moving at five metres!
- INGENUITY UNLIMITED** hosted by Alan Winstanley **326**
Fully Automatic Egg Timer; Heart Rate Monitor; Microwatt L.E.D. Flasher
- DOOR CHIME** by Bart Trepak **328**
Give your front door that "ding-dong" appeal of yesteryear!
- BACK TO BASICS - Part 4. Live Wire Detector; Medium Wave Radio** **346**
by Bart Trepak. Illustrating how transistors can create useful designs
- EARTH RESISTIVITY LOGGER - Part 2** by John Becker **360**
Describing the software that helps locate the hidden mysteries of our ancestors

Series and Features

- TECHNO TALK** by Andy Emmerson **322**
Barcodes are set to disappear!
- NEW TECHNOLOGY UPDATE** by Ian Poole **332**
Improved antennae materials enhance mobile phone comms
- CIRCUIT SURGERY** by Alan Winstanley and Ian Bell **334**
Digital timing without glitches; More on circuit diagram symbols
- NET WORK - THE INTERNET PAGE** surfed by Alan Winstanley **352**
Sniping a deal on eBay; Paying by Paypal
- PRACTICALLY SPEAKING** by Robert Penfold **354**
Constructor's guide to building circuits on plain matrix board

Regulars and Services

- EDITORIAL** **315**
- NEWS** - Barry Fox highlights technology's leading edge **323**
Plus everyday news from the world of electronics
- BACK ISSUES** Did you miss these? Many now on CD-ROM! **338**
- READOUT** John Becker addresses general points arising **343**
- SHOPTALK** with David Barrington **350**
The *essential* guide to component buying for *EPE* projects
- PLEASE TAKE NOTE** Earth Resistivity Logger Part 1 (Apr '03) **350**
- CD-ROMS FOR ELECTRONICS** **356**
A wide range of CD-ROMs for hobbyists, students and engineers
- PRINTED CIRCUIT BOARD AND SOFTWARE SERVICE** **359**
PCBs for *EPE* projects. Plus *EPE* project software
- DIRECT BOOK SERVICE** **369**
A wide range of technical books available by mail order, plus more CD-ROMs
- ELECTRONICS MANUALS** **372**
Essential reference works for hobbyists, students and service engineers
- ADVERTISERS INDEX** **376**

FREE SUPPLEMENT

- EPE PIC TUTORIAL V2 - Part 2** **between pages 340 and 341**
Quite simply the best low-cost way to learn about using PICs! An enhanced revision of our highly acclaimed series of 1998. Part 3 published next month.

© Wimborne Publishing Ltd 2003. Copyright in all drawings, photographs and articles published in **EVERYDAY PRACTICAL ELECTRONICS** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our June 2003 issue will be published on Thursday, 8 May 2003. See page 307 for details

Readers Services • Editorial and Advertisement Departments 315

Visit our website
www.distel.co.uk

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

GIANT 10" 7-SEGMENT DISPLAYS

A bulk purchase enables us to bring to you these GIANT 7-segment digital displays at a now affordable price! The 10" character size gives exceptional readability at long distances and enables a host of applications including, score boards, digital clocks, counters, event timers etc. As the units are a simple electro-mechanical device and operate from 12V DC, simple switching via switches, relays, PIC or PC may be used to control single or multiple digits. Units feature integral 'Zero Power' memory which greatly simplifies design. For an excellent DIY practical article, see the May issue of 'Everyday Practical Electronics' magazine. Ideal School / College construction project. Supplied in good RFE condition, complete with data sheet.



Less than 30% of makers price **Only £29.95(B) or 4 / £99.00(D)**
Order RW44 Order PH26

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!! The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors **£36.95**
TELEBOX ST as ST but fitted with integral speaker **£39.50**
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner **£69.95**
For overseas PAL versions state 5.5 or 6 mHz sound specification.
*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Telebox's, code (B)

TELEBOX ST for composite video input type monitors **£36.95**
TELEBOX ST as ST but fitted with integral speaker **£39.50**
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner **£69.95**
For overseas PAL versions state 5.5 or 6 mHz sound specification.
*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Telebox's, code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite 1V pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £39.95 code (B)**
See www.distel.co.uk/data_my00.htm for picture + full details

HARD DISK DRIVES 2 1/2" 14"

2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H) **New £59.95**
2 1/2" TOSHIBA MK4313MAT 4.3Gb laptop (8.2 mm H) **New £105.00**
2 1/2" TOSHIBA MK6409MAV 6.1Gb laptop (12.7 mm H) **New £98.00**
2 1/2" TOSHIBA MK1614GAV 18 Gb laptop (12 mm H) **New £149.95**
2 1/2" to 3 1/2" conversion kit for PCs, complete with connectors **£15.95**
3 1/2" COMPAQ 313706-B21 (IBM) 9 gb ULT/SCSI3 **New £199.00**
3 1/2" FUJI FK-309-26 20mb MFM I/F RFE **£59.95**
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE **£59.95**
3 1/2" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE **£69.00**
3 1/2" QUANTUM 405 Prodriv ve 42mb SCSI I/F, New RFE **£49.00**
5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE **£49.95**
5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb **£69.95**
5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested **£69.95**
5 1/4" HP 97548 850 Mb SCSI RFE tested **£99.00**
5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested **£195.00**
8" NEC D2246 85 Mb SMD interface. **£99.00**
8" FUJITSU M2322K 160Mb SMD I/F RFE tested **£195.00**
8" FUJITSU M2392K 2 Gb SMD I/F RFE tested **£345.00**
Many other floppy & H drives, IDE, SCSI, ESDI etc from stock, see website for full stock list. Shipping on all drives is code

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

MITSUBISHI FA3445ETKL 14" Ind. spec SVGA monitors **£245**
FARNELL 0.60V DC @ 50 Amps, bench Power Supplies **£995**
FARNELL AP3080 0.30V DC @ 80 Amps, bench Supply **£1850**
KINGHOLD CZ403/1 0.50V @ DC 200 Amps - NEW **£3950**
1kW to 400 kW - 400 Hz 3 phase power sources - ex stock **£760**
IBM 8230 Type 1, Token ring base unit driver **£2500**
Wayne Kerr RA200 Audio frequency response analyser **£49**
INFODEC IU - 24 port RJ45 network patchpanels, #TH93 **£69**
3COM 16670 12 Port Ethernet hub - RJ45 connectors #LD97 **£89**
3COM 16671 24 Port Ethernet hub - RJ45 connectors **£69**
3COM 16700 8 Port Ethernet hub - RJ45 connectors NEW **£39**
IBM 53F5501 Token Ring ICS 20 port lobe modules **£POA**
IBM MAU Token ring distribution panel 8228-23-5050N **£45**
AIM 50 Low distortion Oscillator 9Hz to 330KHz, IEEE I/O **£550**
ALLGON 8360.11805-1880 MHz hybrid power combiners **£250**
Trend DSA 274 Data Analyser with G703(2M) 64 i/o **£POA**
Marconi 6310 Programmable 2 to 22 GHz sweep generator **£4500**
Marconi 2022C 10KHz-1GHz RF signal generator **£1550**
HP1650B Logic Analyser **£3750**
HP3781A Pattern generator & HP3782A Error Detector **£POA**
HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts **£1800**
HP6264 Rack mount variable 0-20V @ 20A metered PSU **£475**
HP54121A DC to 22 GHz four channel test set **£POA**
HP81300 opt 020 300 MHz pulse generator, GPIB etc **£7900**
HP A1, A0 8 pen HPGL high speed drum plotters - from **£550**
HP DRAFTMASTER 18 pen high speed plotter **£750**
Keithley 590 CV capacitor / voltage analyser **£1800**
Racal ICR40 dual 40 channel voice recorder system **£3750**
Fiskers 45KVA 3 ph On Line UPS - New batteries **£4500**
Emerson AP130 2.5KVA industrial spec UPS **£1499**
Mann Tally MT645 High speed line printer **£2200**
Intel SBC 486/133SE Multibus 486 system, 8Mb Ram **£945**

IC's - TRANSISTORS - DIODES

OBSELETE SHORT SUPPLY BULK
10,000,000 items EX STOCK
For MAJOR SAVINGS
CALL or see web site www.distel.co.uk

COMPUTER MONITOR SPECIALS

Legacy products
High spec genuine multisync
CGA, EGA, VGA, SVGA

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, in EXCELLENT little used condition. Tilt & Swivel Base **£4.75**
VGA cable for IBM PC included. **Only £129 (E)** Order as CG73

External cables for other types of computers available - CALL

Generic LOW COST SVGA Monitors

We choose the make, which includes Compaq, Mitsubishi, IBM, etc. Supplied ready to run with all cables, Standard RTB 90 day guarantee.

14" **£59.00**
15" **£69.00**
17" **£79.00**
Supplied in good used condition. Shipping code (D)

VIDEO MONITORS

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both 15.625 and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed. Dimensions: W14" x H12 1/4" x 1 1/2" D. **Only £99.00 (E)**

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 1 1/2" D. 240 V AC mains powered. **Only £79.00 (D)**

INDUSTRIAL COMPUTERS

Tiny shoebox sized industrial 40 Mhz 386 PC system measuring only (mm) 266 x X 88 x H 272 D. Ideal for dedicated control applications running DOS, Linux or even Windows! Steel case contains 85 to 265 V AC 50 / 60 Hz 70 Watt PSU, a 3 slot ISA passive backplane and a Rocky 318 (PC104) standard, single board computer with 8 MByte NON VOLATILE solid state 'Disk On Chip' RAMDISK. System comprises: Rocky 318 (PC104) SBC ISA card with 40MHz ALI 386SX CPU, 72 pin SIMM slot with 16 Mbyte SIMM, AMI BIOS, battery backed up real time clock. 2 x 9 pin D 16550 serial ports. EPP/ECP printer port, mini DIN keyboard connector, floppy port, IDE port for hard drives up to 528 MByte capacity, watchdog timer and PC/104 bus socket. The 8 MByte solid state 'disk on a chip' has its own BIOS, and can be fdisked, formatted & booted. Supplied BRAND NEW fully tested and guaranteed. For full data see featured item on website. Order as CG36. **Only £99.00 (D)**

100's of applications inc: firewall routers, robotics etc

19" RACK CABINETS

Europe's Largest Stocks of quality rack cabinets, enclosures and accessories. Over 1000 Racks from stock

This month's special
33 / 42 / 47 U - High Quality All steel Rack Cabinets

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvred back door and double skinned top section with top and side louvres. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, pre-punched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue, some grey available - CALL - Can be supplied in many other configurations.

Order as BC44 **£245**
Order as DT20 **£345**
Order as RV36 **£410**

Call for shipping quotation

COLOUR CCD CAMERAS

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full autolight sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available. Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cams etc, etc.

Order as LK33 **ONLY £79.00 or 2 for £149.00 (B)**

SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. **ONLY £89.00 (B)**
ENCARTA 95 - CDROM, Not the latest - but at this price! **£7.95**
DOS 5.0 on 3 1/2" disks with concise books c/w QBasic **£14.95**
Windows for Workgroups 3.11 + Dos 6.22 on 3.5" disks **£55.00**
Windows 95 CDROM Only - No Licence - **£19.95**

Wordperfect 6 for DOS supplied on 3 1/2" disks with manual **£24.95**

SOLID STATE LASERS

Visible red, 670nm laser diode assembly. Unit runs from 5 V DC at approx 50 mA. Originally made for continuous use in industrial barcode scanners, the laser is mounted in a removable solid aluminium block, which functions as a heatsink and rigid optical mount. Dims of block are 50 w x 50 d x 15 mm. Integral features include over temperature shutdown, current control, laser OK output, and gated TTL ON / OFF. Many uses for experimental optics, comms & lightshows etc. Supplied complete with data sheet. Order as TD91 **ONLY £24.95 (A)**

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies. Ex Stock - Call or see our web site.

RELAYS 200,000 FROM STOCK

Save £££'s by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting etc. CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save £££'s

display
-ELECTRONICS-

ALL MAIL TO
Dept PE, 29 / 35 Osborne Rd
Thornton Heath
Surrey CR7 8PD
Open Mon - Fri 9.00 - 5.30

18 Million Items On Line Now!
Secure ordering, Pictures, information
www.distel.co.uk
email = admin@distel.co.uk

ALL ENQUIRIES
0208 653 3333
FAX 0208 653 8888

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 7 working days clearance. Cancellation charges (A)=£3.50, (B)=£6.50, (C)=£15.00, (D)=£18.00, (E)=£18.00, (F)=CALL. Allow approx 3 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale which can be viewed at our website and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Display Electronics 2002. E & O.E.


NEXT MONTH

FREE
SUPPLEMENT
PIC TUTORIAL V2
Part 3

PICRONOS L.E.D. WALL CLOCK

Inspired by a reader whose giant l.e.d. wall clock had ticked its last tock and could not be revived, this design uses a mixture of ancient and modern techniques, old in the form of l.e.d.s for the display rather than an l.c.d., and modern in the form of a PIC microcontroller (inevitably!). It has the following characteristics:

- Crystal controlled
- Circular display having diameter of 250mm (9.3in.)
- Inner ring of 60 l.e.d.s displaying both seconds and minutes
- Outer ring of 12 l.e.d.s displaying hours in conventional (analogue) 12-hour format
- Inner zone of 100 l.e.d.s in 4-digit 7-segment numerical format, cyclically displaying hours (24-hour format) and minutes, months and days of month, and temperature in degrees Celsius
- Powered at 9V to 12V d.c. via a mains supply adaptor, with battery back-up
- Adjustable brilliance of the l.e.d. numerals to suit personal taste

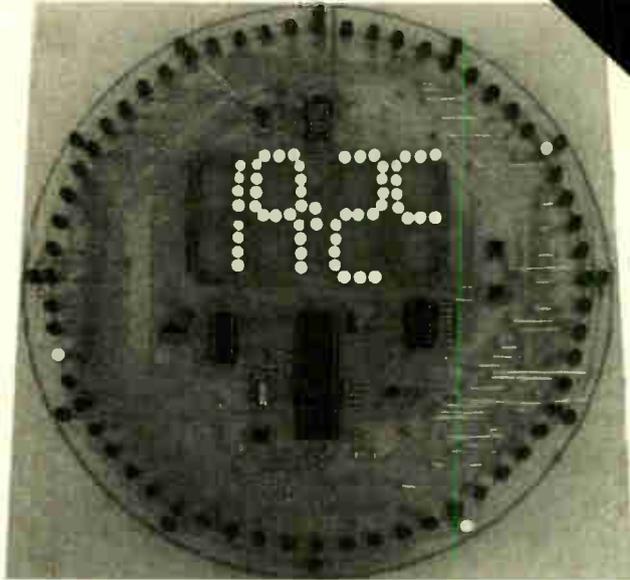

RADIO CIRCUITS

Intended to dispel the mysteries of radio, this short series of articles by Raymond Haigh features a variety of circuits for the set builder and experimenter.

Towards the end of the 19th century, sending a radio signal a few hundred yards was considered a major achievement. At the close of the 20th, man was communicating with space probes at the outermost edge of the solar system. No other area of science and technology has affected the lives of people more completely.

This series will view the technology in a historical perspective and try to dispel its mysteries. The main purpose, however, is to

present a variety of practical circuits for set builders and experimenters. You will be able to build a wide range of receivers, everything from a crystal set to a superhet.

FIDO PEDOMETER

Fido's designer enjoys trekking in remote regions where estimating the distance walked can be difficult and retracing steps frustrating! He developed Fido to help solve this problem without the expense of buying a GPS navigational aid. Fido can record the distance traversed by a walker or runner and calculates average speed – a useful addition when planning how long it will take to get back to comfort!

A PIC16F84A microcontroller is employed and the unit can be set to work in miles or kilometres. Clever software allows Fido to be taught to stay at heel – to recognise the length of your stride and keep track of your progress.

NO ONE DOES IT BETTER

EVERYDAY
PRACTICAL
ELECTRONICS

**DON'T MISS AN
ISSUE – PLACE YOUR
ORDER NOW!**
Demand is bound to be high

JUNE 2003 ISSUE ON SALE THURSDAY, MAY 8

QUASAR ELECTRONICS LIMITED

PO Box 6935, BISHOPS STORTFORD, Herts CM23 4WP

TEL: 0871 717 7168 FAX: 0871 277 2728

ADD £2.00 P&P to all orders for 1st Class. UK £1.00. Next day (Inured £2.00) £7, Europe £5.00, Rest of World £10.00. We accept all major credit cards. Make cheques/PO's payable to Quasar Electronics. Prices include 17.5% VAT, MAIL ORDER ONLY. FREE CATALOGUE with order or send 2 x 1st class stamps (refundable) for details of over 150 kits & publications.



PROJECT KITS


Our electronic kits are supplied complete with all components, high quality PCBs (NOT cheap Tripad strip board!) and detailed assembly/operating instructions

- **2 x 25W CAR BOOSTER AMPLIFIER** Connects to the output of an existing car stereo cassette player, CD player or radio. Heatsinks provided. PCB 76x75mm. **1046KT £24.95**
- **3-CHANNEL WIRELESS LIGHT MODULATOR** No electrical connection with amplifier. Light modulation achieved via a sensitive electret microphone. Separate sensitivity control per channel. Power handling 400W/channel. PCB 54x112mm. Mains powered. Box provided. **5014KT £24.95**
- **12 RUNNING LIGHT EFFECT** Exciting 12 LED light effect ideal for parties, discos, shop-windows & eye-catching signs. PCB design allows replacement of LEDs with 220V bulbs by inserting 3 TRIACS. Adjustable rotation speed & direction. PCB 54x112mm. **1026KT £15.95; BOX (for mains operation) 2026BX £9.00**
- **DISCO STROBE LIGHT** Probably the most exciting of all light effects. Very bright strobe tube. Adjustable strobe frequency. 1-60Hz. Mains powered. PCB: 60x68mm. Box provided. **6037KT £28.95**
- **ANIMAL SOUNDS** Cat, dog, chicken & cow. Ideal for kids farmyard toys & schools. **SG10M £5.95**
- **3 1/2 DIGIT LED PANEL METER** Use for basic voltage/current displays or customise to measure temperature, light, weight, movement, sound levels, etc. with appropriate sensors (not supplied). Various input circuit designs provided. **3061KT £13.95**
- **IR REMOTE TOGGLE SWITCH** Use any TV/VCR remote control unit to switch onboard 12V/1A relay on/off. **3058KT £10.95**
- **SPEED CONTROLLER** for any common DC motor up to 100V/5A. Pulse width modulation gives maximum torque at all speeds. 5-15VDC. Box provided. **3067KT £12.95**
- **3 x 8 CHANNEL IR RELAY BOARD** Control eight 12V/1A relays by Infra Red (IR) remote control over a 20m range in sunlight. 6 relays turn on only, the other 2 toggle on/off 3 operation ranges determined by jumpers. Transmitter case & all components provided. Receiver PCB 76x89mm. **3072KT £52.95**

PRODUCT FEATURE

COMPUTER TEMPERATURE DATA LOGGER

PC serial port controlled 4-channel temperature meter (either deg C or F). Requires no external power. Allows continuous temperature data logging of up to four temperature sensors located 200m+ from motherboard/PC. Ideal use for old 386/486 computers. Users can tailor input data stream to suit their purpose (dump it to a spreadsheet or write your own BASIC programs using the INPUT command to grab the readings). PCB just 38mm x 38mm. Sensors connect via four 3-pin headers. 4 header cables supplied but only one DS18S20 sensor. Kit software available free from our website. **ORDERING: 3145KT £23.95 (kit form); AS3145 £29.95 (assembled); Additional DS18S20 sensors £4.95 each**

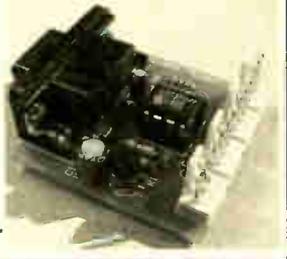

- **SOUND EFFECTS GENERATOR** Easy to build. Create an almost infinite variety of interesting/unusual sound effects from birds chirping to sirens. 9VDC. PCB 54x85mm. **1045KT £8.95**
- **ROBOT VOICE EFFECT** Make your voice sound similar to a robot or Darlek. Great fun for discos, school plays, theatre productions, radio stations & playing jokes on your friends. When answering the phone! PCB 42x71mm. **1131KT £8.95**
- **AUDIO TO LIGHT MODULATOR** Controls intensity of one or more lights in response to an audio input. Safe, modern opto-coupler design. Mains voltage experience required. **3012KT £8.95**
- **MUSIC BOX** Activated by light. Plays 8 Christmas songs and 5 other tunes. **3104KT £7.95**
- **20 SECOND VOICE RECORDER** Uses non-volatile memory - no battery backup needed. Record/play messages over & over. Playback as required to greet customers etc. Volume control & built-in mic. 6VDC. PCB 50x73mm. **3131KT £12.95**
- **TRAIN SOUNDS** 4 selectable sounds: whistle blowing, level crossing bell, 'clackety-clack' & 4 in sequence. **SG01M £6.95**
- **PC CONTROLLED RELAY BOARD** Convert any 286 upward PC into a dedicated automatic controller to independently turn on/off up to eight lights, motors & other devices around the home, office, laboratory or factory. Each relay output is capable of switching 250VAC/4A. A suite of DOS and Windows control programs are provided together with all components (except box and PC cable). 12VDC. PCB 70x200mm. **3074KT £31.95**
- **2 CHANNEL UHF RELAY SWITCH** Contains the same transmitter/receiver pair as 30A15 below plus the components and PCB to control two 240VAC/10A relays (also supplied). Ultra bright LEDs used to indicate relay status. **3082KT £27.95**
- **TRANSMITTER RECEIVER PAIR** 2-button keyfob style 300-375MHz Tx with 30m range. Receiver encoder module with matched decoder IC. Components must be built into a circuit like kit 3082 above. **30A15 £14.95**
- **PIC 16C71 FOUR SERVO MOTOR DRIVER** Simultaneously control up to 4 servo motors. Software & all components (except sensors/control pots) supplied. 5VDC. PCB 50x70mm. **3102KT £15.95**
- **UNIPOLAR STEPPER MOTOR DRIVER** for any 5/6/8 lead motor. Fast/slow & single step rates. Direction control & on/off switch. Wave, 2-phase & half-wave step modes. 4 LED indicators. PCB 50x65mm. **3109KT £14.95**
- **PC CONTROLLED STEPPER MOTOR DRIVER** Control two unipolar stepper motors (3A max. each) via PC printer port. Wave, 2-phase & half-wave step modes. Software accepts 4 digital inputs from external switches & will single step motors. PCB fits in O-shell case provided. **3113KT £17.95**
- **12-BIT PC DATA ACQUISITION/CONTROL UNIT** Similar to kit 3093 above but uses a 12 bit Analogue-to-Digital Converter (ADC) with internal analogue multiplexer. Reads 8 single ended channels or 4 differential inputs or a mixture of both. Analogue inputs read 0-4V. Four TTL/CMOS compatible digital input/outputs. ADC conversion time <10µs. Software (C, QB & Win), extended D shell case & all components (except sensors & cable) provided. **3118KT £52.95**
- **LIQUID LEVEL SENSOR/RAIN ALARM** Will indicate fluid levels or simply the presence of fluid. Relay output to control a pump to add/remove water when it reaches a certain level. **1080KT £5.95**
- **AM RADIO KIT 1** Tuned Radio Frequency front-end, single chip AM radio IC & 2 stages of audio amplification. All components inc. speaker provided. PCB 32x102mm. **3063KT £10.95**
- **DRILL SPEED CONTROLLER** Adjust the speed of your electric drill according to the job at hand. Suitable for 240V AC mains powered drills up to

X FACTOR PUBLICATIONS

THE EXPERTS IN RARE & UNUSUAL INFORMATION!

Full details of all X-FACTOR PUBLICATIONS can be found in our catalogue. N.B. Minimum order charge for reports and plans is £5.00 PLUS normal P&P.

- **SUPER-EAR LISTENING DEVICE** Complete plans to build your own parabolic dish microphone. Listen to distant voices and sounds through open windows and even walls! Made from readily available parts. **R002 £3.50**
- **LOCKS** - How they work and how to pick them. This fact filled report will teach you more about locks and the art of lock picking than many books we have seen at 4 times the price. Packed with information and illustrations. **R008 £3.50**
- **RADIO & TV JOKER PLANS** We show you how to build three different circuits for disrupting TV picture and sound plus FM radio! May upset your neighbours & the authorities! DISCRETION REQUIRED. **R017 £3.50**
- **INFINITY TRANSMITTER PLANS** Complete plans for building the famous Infinity Transmitter. Once installed on the target phone, device acts like a room bug. Just call the target phone & activate the unit to hear all room sounds. Great for home/office security! **R019 £3.50**
- **THE ETHER BOX CALL INTERCEPTOR PLANS** Grabs telephone calls out of thin air! No need to wire-in a phone bug. Simply place this device near the phone lines to hear the conversations taking place! **R025 £3.00**
- **CASH CREATOR BUSINESS REPORTS** Need ideas for making some cash? Well this could be just what you need! You get 40 reports (approx 800 pages) on floppy disk that give you information on setting up different businesses. You also get valuable reproduction and duplication rights so that you can sell the manuals as you like. **R030 £7.50**

SURVEILLANCE

High performance surveillance bugs. Room transmitters supplied with sensitive electret microphone & battery holder/clip. All transmitters can be received on an ordinary VHF-FM radio between 88-108MHz. Available in Kit Form (KT) or Assembled & Tested (AS).

ROOM SURVEILLANCE

- **MTX - MINIATURE 3V TRANSMITTER** Easy to build & guaranteed to transmit 300m @ 3V Long battery life, 3-5V operation. Only 45x18mm. B. **3007KT £6.95 AS3007 £11.95**
- **MTX - MINIATURE 9V TRANSMITTER** Our best selling bug Super sensitive, high power - 500m range @ 9V (over 1km with 18V supply and better aerial). 45x19mm. **3018KT £7.95 AS3018 £12.95**
- **HPTX - HIGH POWER TRANSMITTER** High performance, 2 stage transmitter gives greater stability & higher quality reception. 1000m range 6-12V DC operation. Size 70x15mm. **3032KT £9.95 AS3032 £18.95**
- **MMTX - MICRO-MINIATURE 9V TRANSMITTER** The ultimate bug for its size, performance and price. Just 15x25mm. 500m range @ 9V. Good stability 6-18V operation. **3051KT £8.95 AS3051 £14.95**
- **VTX - VOICE ACTIVATED TRANSMITTER** Operates only when sounds detected. Low standby current. Variable trigger sensitivity 500m range. Peaking circuit supplied for maximum RF output. On/off switch 6V operation. Only 63x38mm. **3028KT £12.95 AS3028 £24.95**
- **HARD-WIRED BUG/TWO STATION INTERCOM** Each station has its own amplifier, speaker and mic. Can be set up as either a hard-wired bug or two-station intercom. 10m x 2-core cable supplied. 9V operation. **3021KT £15.95 (kit form only)**
- **TRYS - TAPE RECORDER VOX SWITCH** Used to automatically operate a tape recorder (not supplied) via its REMOTE socket when sounds are detected. All conversations recorded. Adjustable sensitivity & turn-off delay. 115x19mm. **3013KT £9.95 AS3013 £21.95**



TELEPHONE SURVEILLANCE

- **MTX - MINIATURE TELEPHONE TRANSMITTER** Attaches anywhere to phone line. Transmits only when phone is used! Tune-in your radio and hear both parties. 300m range. Uses line as aerial & power source. 20x45mm. **3016KT £8.95 AS3016 £14.95**
- **TRH - TELEPHONE RECORDING INTERFACE** Automatically record all conversations. Connects between phone line & tape recorder (not supplied). Operates recorders with 1.5-12V battery systems. Powered from line. 50x33mm. **3033KT £9.95 AS3033 £18.95**
- **TPA - TELEPHONE PICK-UP AMPLIFIER/WIRELESS PHONE BUG** Places pick-up coil on the phone line or near phone earpiece and hear both sides of the conversation. **3055KT £11.95 AS3055 £20.95**

HIGH POWER TRANSMITTERS

- **1 WATT FM TRANSMITTER** Easy to construct. Delivers a crisp, clear signal. Two-stage circuit. Kit includes microphone and requires a simple open dipole aerial. 8-30VDC. PCB 42x45mm. **1009KT £12.95**
- **4 WATT FM TRANSMITTER** Comprises three RF stages and an audio preamplifier stage. Piezoelectric microphone supplied or you can use a separate preamplifier circuit. Antenna can be an open dipole or Ground Plane. Ideal project for those who wish to get started in the fascinating world of FM broadcasting and want a good basic circuit to experiment with. 12-18VDC. PCB 44x146mm. **1028KT £22.95 AS1028 £34.95**
- **15 WATT FM TRANSMITTER (PRE-ASSEMBLED & TESTED)** Four transistor based stages with Philips BL 88 in final stage. 15 Watts RF power on the air. 88-108MHz. Accepts open dipole, Ground Plane, 5/8, J, or YAGI antennas. 12-18VDC. PCB 70x220mm. Mains meter needed for alignment. **1021KT £99.95**
- **SIMILAR TO ABOVE BUT 25W OUTPUT.** **1031KT £195.95**

700W power. PCB: 48mm x 65mm. Box provided. **6074KT £17.95**

- **3 INPUT MONO MIXER** Independent level control for each input and separate bass/treble controls. Input sensitivity: 240mV. 18V DC. PCB: 60mm x 185mm. **1052KT £16.95**
- **NEGATIVE/POSITIVE ION GENERATOR** Standard Cockcroft-Walton multiplier circuit. Mains voltage experience required. **3057KT £10.95**
- **LED DICE** Classic intro to electronics & circuit analysis. 7 LEDs simulate dice roll, slow down & land on a number at random. 555 IC circuit. **3003KT £9.95**
- **STAIRWAY TO HEAVEN** Tests hand-eye co-ordination. Press switch when green segment of LED lights to climb the stairway - miss & start again! Good intro to several basic circuits. **3005KT £9.95**
- **ROULETTE LED 'Ball'** spins round the wheel, slows down & drops into a slot. 10 LEDs. Good intro to CMOS decade counters & Op-Amps. **3006KT £10.95**
- **12V XENON TUBE FLASHER TRANSFORMER** steps up a12V supply to flash a 25mm Xenon tube. Adjustable flash rate. **3163KT £13.95**
- **LED FLASHER 1.5** ultra bright red LED's flash in 7 selectable patterns. **3037MKT £5.95**
- **LED FLASHER 2** Similar to above but flash in sequence or randomly. Ideal for model railways. **3052MKT £5.95**
- **INTRODUCTION TO PIC PROGRAMMING.** Learn programming from scratch. Programming hardware, a PIC16F4 chip and a two-part, practical, hands-on tutorial series are provided. **3081KT £21.95**
- **SERIAL PIC PROGRAMMER** for all 818/28/40 pin DIP serial programmed PICs. Shareware software supplied limited to programming 256 bytes (registration costs £14.95). **3096KT £10.95**
- **ATMEL 89C051 PROGRAMMER** Simple-to-use yet powerful programmer for the Atmel 89C1051, 89C2051 & 89C4051 uC's. Programmer does NOT require special software other than a terminal emulator program (built into Windows). Can be used with ANY computer/operating system. **3121KT £24.95**
- **3V/1.5V TO 9V BATTERY CONVERTER** Replace expensive 9V batteries with economic 1.5V batteries. IC based circuit steps up 1 or 2 'AA' batteries to give 9V/18mA. **3035KT £5.95**
- **STABILISED POWER SUPPLY 3-30V/2.5A** Ideal for hobbyist & professional laboratory. Very reliable & versatile design at an extremely reasonable price. Short circuit protection. Variable DC voltages (3-30V). Rated output 2.5 Amps. Large heatsink supplied. You just supply a 24VAC/3A transformer. PCB 55x112mm. Mains operation. **1007KT £16.95**
- **STABILISED POWER SUPPLY 2-30V/5A** As kit 1007 above but rated at 5Amp. Requires a 24VAC/5A transformer. **1096KT £27.95**
- **MOTORBIKE ALARM** Uses a reliable vibration sensor (adjustable sensitivity) to detect movement of the bike to trigger the alarm & switch the output relay to which a siren, bikes horn, indicators or other warning device can be attached. Auto-reset. 6-12VDC. PCB 57x64mm. **1011KT £11.95 Box 2011BX £7.00**
- **CAR ALARM SYSTEM** Protect your car from theft. Features vibration sensor, courtesy/boot light voltage drop sensor and bonnet/boot earth switch sensor. Entry/exist delays, auto-reset and adjustable alarm duration. 6-12VDC. PCB: 47mm x 55mm. **1019KT £11.95 Box 2019BX £8.00**
- **PIEZO SCREAMER** 110dB of ear piercing noise. Fits in box with 2 x 35mm piezo elements built into their own resonant cavity. Use as an alarm siren or just for fun! 6-9VDC. **3015KT £10.95**
- **COMBINATION LOCK** Versatile electronic lock comprising main circuit & separate keypad for remote opening of lock. Relay supplied. **3029KT £10.95**
- **ULTRASONIC MOVEMENT DETECTOR** Crystal locked detector frequency for stability & reliability. PCB 75x40mm houses all components. 4-7m range. Adjustable sensitivity. Output will drive external relay/circuits. 9VDC. **3049KT £13.95**
- **PIR DETECTOR MODULE 3-lead** assembled unit just 25x35mm as used in commercial burglar alarm systems. **3076KT £8.95**
- **INFRARED SECURITY BEAM** When the invisible IR beam is broken a relay is tripped that can be used to sound a bell or alarm. 25 metre range. Mains rated relays provided. 12VDC operation. **3130KT £12.95**
- **SQUARE WAVE OSCILLATOR** Generates square waves at 6 preset frequencies in factors of 10 from 1Hz-100KHz. Visual output Indicator. 5-18VDC. Box provided. **3111KT £8.95**
- **PC DRIVEN POCKET SAMPLER/DATA LOGGER** Analogue voltage sampler records voltages up to 2V or 20V over periods from milli-seconds to months. Can also be used as a simple digital scope to examine audio & other signals up to about 5KHz. Software & D-shell case provided. **3112KT £18.95**
- **20 MHz FUNCTION GENERATOR** Square, triangular and sine waveform up to 20MHz over 3 ranges using 'coarse' and 'fine' frequency adjustment controls. Adjustable output from 0-2V p-p. A TTL output is also provided for connection to a frequency meter. Uses MAX038 IC. Plastic case with printed front/rear panels & all components provided. 7-12VAC. **3101KT £69.95**

BARGAIN BUY!

Great introduction to electronics. Ideal for the budding electronics expert! Build a radio, burglar alarm, water detector, Morse code practice circuit, simple computer circuits, and much more! NO soldering, tools or previous electronics knowledge required. Circuits can be built and unassembled repeatedly. Comprehensive 68-page manual with explanations, schematics and assembly diagrams. Suitable for age 10+. Excellent for schools. Requires 2 x AA batteries. Order Code EPL030 ONLY £14.95 (phone for bulk discounts). 130, 300 and 500-in-ONE also available.

30-IN-ONE Electronic Projects Lab



WEB: <http://www.QuasarElectronics.com>
email: epesales@QuasarElectronics.com

Secure Online Ordering Facilities
Full Kit Listing, Descriptions & Photos
Kit Documentation & Software Downloads

www.QuasarElectronics.com

Credit Card Sales: 0871 717 7168


Enhanced 'PICALL' ISP PIC Programmer

Kit will program virtually ALL 8 to 40 pin* serial and parallel programmed PIC microcontrollers. Connects to PC parallel port. Supplied with fully functional pre-registered PICALL DOS and WINDOWS AVR software packages, all components and high quality DSPTH board. Also programs certain ATMEL AVR, SCENIX SX and EEPROM 24C devices. New devices can be added to the software as they are released. Blank chip auto detect feature for super-fast bulk programming. Hardware now supports ISP programming. *A 40 pin wide ZIF socket is required to program 0-3in. devices (Order Code AZIF40 @ £15.00).



3144KT	Enhanced 'PICALL' ISP PIC Programmer	£59.95
AS3144	Assembled Enhanced 'PICALL' ISP PIC Programmer	£64.95
AS3144ZIF	Assembled Enhanced 'PICALL' ISP PIC Programmer c/w ZIF socket	£79.95

ATMEL AVR Programmer

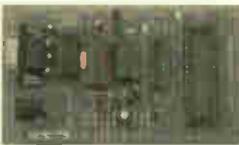

Powerful programmer for Atmel AT90Sxxxx (AVR) micro controller family. All fuse and lock bits are programmable. Connects to serial port. Can be used with ANY computer and operating system. Two LEDs to indicate programming status. Supports 20-pin DIP AT90S1200 & AT90S2313 and 40-pin DIP AT90S4414 & AT90S8515 devices. NO special software required - uses any terminal emulator program (built into Windows). The programmer is supported by BASCOM-AVR Basic Compiler software (see website for details).

3122KT	ATMEL AVR Programmer	£24.95
AS3122	Assembled 3122	£34.95

Atmel 89Cx051 and 89xxx programmers also available.

PC Data Acquisition & Control Unit

With this kit you can use a PC parallel port as a real world interface. Unit can be connected to a mixture of analogue and digital inputs from pressure, temperature, movement, sound, light intensity, weight sensors, etc. (not supplied) to sensing switch and relay states. It can then process the input data and use the information to control up to 11 physical devices such as motors, sirens, other relays, servo motors & two-stepper motors.



FEATURES:

- 8 Digital Outputs: Open collector, 500mA, 33V max.
 - 16 Digital Inputs: 20V max. Protection 1K in series, 5-1V Zener to ground.
 - 11 Analogue Inputs: 0-5V, 10 bit (5mV/step.)
 - 1 Analogue Output: 0-2.5V or 0-10V. 8 bit (20mV/step.)
- All components provided including a plastic case (140mm x 110mm x 35mm) with pre-punched and silk screened front/rear panels to give a professional and attractive finish (see photo) with screen printed front & rear panels supplied. Software utilities & programming examples supplied.

3093KT	PC Data Acquisition & Control Unit	£99.95
AS3093	Assembled 3093	£124.95

See opposite page for ordering information on these kits

ABC Mini 'Hotchip' Board




Currently learning about microcontrollers? Need to do something more than flash a LED or sound a buzzer? The ABC Mini 'Hotchip' Board is based on Atmel's AVR 8535 RISC technology and will interest both the beginner and expert alike. Beginners will find that they can write and test a simple program, using the BASIC programming language, within an hour or two of connecting it up.

Experts will like the power and flexibility of the ATMEL microcontroller, as well as the ease with which the little Hot Chip board can be "designed-in" to a project. The ABC Mini Board 'Starter Pack' includes just about everything you need to get up and experimenting right away. On the hardware side, there's a pre-assembled micro controller PC board with both parallel and serial cables for connection to your PC. Windows software included on CD-ROM features an Assembler, BASIC compiler and in-system programmer. The pre-assembled boards only are also available separately.

ABCMINISP	ABC MINI Starter Pack	£64.95
ABCMINIB	ABC MINI Board Only	£39.95

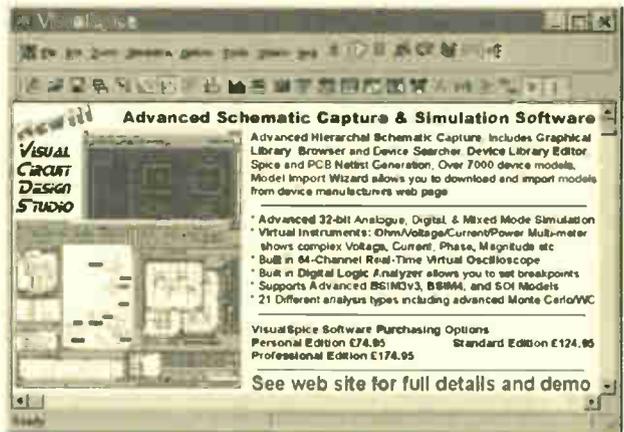Advanced 32-bit Schematic Capture and Simulation Visual Design Studio



Serial Port Isolated I/O Controller

Kit provides eight relay outputs capable of switching 4 amps at mains voltages and four optically isolated digital inputs. Can be used in a variety of control and sensing applications including load switching, external switch input sensing, contact closure and external voltage sensing. Programmed via a computer serial port, it is compatible with ANY computer & operating system. After programming, PC can be disconnected. Serial cable can be up to 35m long, allowing 'remote' control. User can easily write batch file programs to control the kit using simple text commands. NO special software required - uses any terminal emulator program (built into Windows). All components provided including a plastic case with pre-punched and silk screened front/rear panels to give a professional and attractive finish (see photo).



3108KT	Serial Port Isolated I/O Controller Kit	£54.95
AS3108	Assembled Serial Port Isolated I/O Controller	£64.95

SPECIAL OFFERS

TEKTRONIX 2445A
4 x 150MHz delay cursors etc. Supplied with 2 Tektronix probes.
ONLY **£425**

- TEKTRONIX 2232 Digital Storage Scope. Dual Trace, 100MHz, 100MW/s with probes... £525
- H.P. 54501A Dig. Oscilloscope, 100MHz 4-Ch... £425
- H.P. 3312A Function Gen., 0-1Hz-13MHz, AM/FM Sweep/Tri/Gate/Burst etc... £300
- FARNELL Dual PSU XA35-2T, 0-35V, 0-2A, Twice QMD, I.c.d. Display... £180
- CIRRUS CRL254 Sound Level Meter with Calibrator 80-120dB, LEO... £150
- FARNELL AMM255 Automatic Mo Meter, 1.5MHz-2GHz, unused... £300
- FARNELL DSG1 Low Frequency Syn Sig. Gen., 0-001Hz-99.99kHz, low distortion, TTL/Square/Pulse Outputs etc... £95
- FLUKE 8060A Handheld True RMS, DMM, 4 1/2 digit... As new £150, used £95
- BECKMAN HD110 Handheld 3 1/2 digit DMM, 28 ranges, with battery, leads and carrying case... £40

- H.P. 3310A Function Gen., 0-005Hz-5MHz, Sine/Sq/Tri/Ramp/Pulse... £125
- FARNELL LFM4 Sine/Sq Oscillator, 10Hz-1MHz, low distortion, TTL output, Amplitude Meter... £125
- H.P. 545A Logic Probe with 546A Logic Pulser and 547A Current Tracer... £90
- FLUKE 77 Multimeter, 3 1/2-digit, handheld... £60
- FLUKE 77 Series 11... £70
- HEME 1000 L.C.O. Clamp Meter, 00-1000A, in carrying case... £60

- BLACK STAR ORION PAL/TV Colour Pattern Generator... from £75-£125
- THURBYHANDER TG210 Function Generator, 0-002Hz-2MHz, TTL etc... £80-£95
- THURBYHANDER P.S.U. PL320QMO, 0V-32V, 0A-2A Twice (flame colours)... £200

Datron 1061 ONLY **£150**
High Quality 5.5 Digit Bench Multimeter
True RMS/4 wire Res/Current Converter/IEEE

Datron 1061A ONLY **£225**
High Quality 6 1/2 digit Bench Multimeter
True RMS/4 wire/Current Converter

Racal Receiver RA1772 ONLY **£250**
50kHz-30MHz
L.E.D. Display, Basically working.

MARCONI 2019A



AM/FM SYNTHESISED SIGNAL GENERATOR
80 kHz - 1040MHz
NOW ONLY **£400**

- MARCONI 893C AF Power Meter, Sinad Measurement... Unused £100, Used £80
- MARCONI 2610 True RMS Voltmeter, Autoranging, 5Hz-25MHz... £195
- GOULD J3B Sine/Sq Osc., 10Hz-100kHz, low distortion... £75-£125
- AVO 8 Mk. 6 in Every Ready case, with leads etc... £80
- Other AVOs from... £25
- GOODWILL GVT427 Dual Ch AC Millivoltmeter, 10mV-300V in 12 ranges, Freq. 10Hz-1MHz... £100-£120
- SOLARTRON 7150 DMM 6 1/2-digit Tri RMS-IEEE... £95-£150
- SOLARTRON 7150 Plus... £200

- HIGH QUALITY RACAL COUNTERS**
- 9904 Universal Timer Counter, 50MHz... £50
 - 9916 Counter, 10Hz-520MHz... £75
 - 9918 Counter, 10Hz-560MHz, 9-digit... £50
 - WAYNE KERR B424 Component Bridge... £125
 - RACAL/AIM 9343M LCR Databridge, Digital Automeasurement of R, C, L, Q, O... £200
 - HUNTRON TRACKER Model 1000... £125
 - FLUKE 8050A 4-5 Digit, 2A, True RMS... £75
 - FLUKE 8010A 3-5 Digit, 10A... £50
 - FLUKE 8012A 3-5 Digit, 2A... £40

Racal 9008 ONLY **£95**
Automatic Modulation Meter, AM/FM 1-5MHz-2GHz

Portable Appliance Tester ONLY **£180**
Megger Pat 2

- H.P. 6012B DC PSU 0-60V, 0-50A, 1000W... £1000
 - FARNELL AP60/50 1KW Autoranging... £1000
 - FARNELL H60/50 0-50V, 0-50A... £750
 - FARNELL H60/25 0-60V, 0-25A... £400
 - Power Supply HPS3010, 0-30V, 0-10A... £140
 - FARNELL L30-2 0-30V, 0-2A... £80
 - FARNELL L30-1 0-30V, 0-1A... £60
- Many other Power Supplies available

FARNELL DTV12-14 OSCILLOSCOPE ONLY **£75**
Dual trace, 12MHz TV, coupling. ONLY

FARNELL LF1 SINE/SQ OSCILLATOR ONLY **£75**
10Hz-1MHz.

- OSCILLOSCOPES**
- TEKTRONIX TDS350 dual trace, 200MHz, 1GS, Unused £1500
 - TEKTRONIX TDS320 dual trace, 100MHz, 500MW/s... £1200
 - TEKTRONIX TDS310 dual trace, 50MHz, 200MW/s... £950
 - LECROY 9400A dual trace, 175MHz, 5GS... £750
 - HITACHI VC653, d'trace, 200MHz, 20MW/s, delay etc. Unused £500
 - PHILIPS PM3092 2+2-ch, 200MHz, delay etc., £800 as new £950
 - PHILIPS PM3082 2+2-ch, 100MHz, delay etc., £700 as new £800
 - TEKTRONIX TA5465 dual trace, 100MHz, delay etc... £750
 - TEKTRONIX 2465B 4-ch, 400MHz, delay cursors etc... £1500
 - TEKTRONIX 2465 4-ch, 300MHz, delay cursors etc... £900
 - TEKTRONIX 468 Dig Storage, dual trace, 100MHz, delay... £450
 - TEKTRONIX 466 Analog Storage, dual trace, 100MHz... £250
 - TEKTRONIX 485 dual trace, 350MHz, delay sweep... £550
 - TEKTRONIX 475 dual trace, 200MHz, delay sweep... £350
 - TEKTRONIX 465B dual trace, 100MHz, delay sweep... £325
 - TEKTRONIX 2215 dual trace, 60MHz, delay sweep... £250
 - PHILIPS PM3217 dual trace, 50MHz, delay... £200-£250
 - GOULD OS1100 dual trace, 30MHz, delay... £125
 - HAMEG HM303.6 dual trace, 35MHz component tester as new... £240
 - HAMEG HM303 dual trace, 30MHz component tester... £200
- Many other Oscilloscopes available

- MARCONI 2022E Synth AM/FM Sig Gen 10kHz-1.01GHz I.c.d. display etc... £525-£750
- H.P. 8657A Synth sig gen, 100kHz-1040MHz... £2000
- H.P. 8656B Synth sig gen, 100kHz-990MHz... £1350
- H.P. 8656A Synth sig gen, 100kHz-990MHz... £995
- RAS APN62 Synth, 1Hz-260kHz sig. gen, balanced/unbalanced output, I.c.d. display... £425
- PHILIPS PM5328 sig gen, 100kHz-180MHz with 200MHz, freq. counter, IEEE... £550
- RACAL 9081 Synth AM/FM sig gen, 5kHz-1024MHz... £250
- H.P. 3325A Synth function gen, 21MHz... £600
- MARCONI 6500 Amplitude Analyser... £1500
- H.P. 4192A Impedance Analyser... £5000
- H.P. 4275A LCR Meter, 10kHz-10MHz... £2750
- H.P. 8903A Distortion Analyser... £1000
- WAYNE KERR 3245 Inductance Analyser... £2000
- H.P. 8112A Pulse Generator, 50MHz... £1250
- MARCONI 2440 Frequency Counter, 20GHz... £1000
- H.P. 5350B Frequency Counter, 20GHz... £2000
- H.P. 5342A 10Hz-19GHz Frequency Counter... £800
- H.P. 1650B Logic Analyser, 80-channel... £1000
- MARCONI 2035 Mod Meter, 500kHz-2GHz... £750

- RADIO COMMUNICATIONS TEST SETS**
- MARCONI 2955/2995A... From £1500
 - ROHDE & SCHWARZ CMT 61-1000MHz... £2000
 - SCHLUMBERGER 4040... £900

JUST IN

- H.P. 6063B DC Electronic Load, 3-240V/0-10A, 250W... POA
- H.P. 66312A PSU, 0-20V/0-2A... £400
- H.P. 66311B PSU, 0-15V/0-3A... £400
- H.P. 66309D PSU Dual, 0-15, 0-3A/0-12, 0-1-5A... £750
- H.P. 6632B PSU, 0-20V/0-5A... £500
- H.P. 6632A PSU, triple output ranging from 0-7V 0-5A to 0-20V 3-4A... £850
- H.P./AGILENT 34401A DMM 6 1/2 digit... £400/£450
- H.P. 3478A DMM 5 1/2 digit... £275
- FLUKE 45 DMM dual display... £400
- KEITHLEY 2010 DMM 7 1/2 digit... £950
- KEITHLEY 617 Programmable Electrometer... £1250
- TEKTRONIX 2010 DMM 7 1/2 digit... £1500
- H.P. 4338B Milliohmmeter... £500
- RACAL Counter type 1999 2.6GHz... £500
- H.P. Counter type 53131A 3GHz... £850
- H.P./AGILENT 33120A Func. Gen./ARB, 100kHz-15MHz... £900/£1000
- SONY/TEKTRONIX AFC320 Arbitrary Func. Gen... £1250
- H.P. 8904A Syn Function Gen, DC-800kHz... £1000/£1250
- BLACK STAR JUPTTOR 2010 Func. Gen, 0-2Hz-2MHz with frequency counter... £140
- H.P. 8115A Pulse Generator, 1mV-50MHz... £1950
- H.P. 8657B Syn Sig. Gen, 0-1-2080MHz... £2500
- CO-AXIAL SWITCH, 1.5GHz... £40
- IEEE CABLES... £10

SPECTRUM ANALYSERS

- H.P. 8651B 50Hz-6.5GHz... \$9K
- H.P. 8560A 50kHz-3GHz synthesised... \$9K
- H.P. 8554E 9kHz-2.9GHz... £4500
- H.P. 8551E 1MHz-1.8GHz, 75 Ohm... £2750
- H.P. 853A with 8555A 100kHz-21GHz... £1750
- H.P. 8558B with Main Frame, 100kHz-1500MHz... £750
- H.P. 3580A 20Hz-40MHz... £2500
- H.P. 3580A 5Hz-50MHz... £600
- ADVANTEST RA131B 10kHz-3.5GHz... £2750
- EATON/AILTECH 757 0-001-22GHz... £750
- MARCONI 2382 100Hz-400MHz, high resolution... £2000
- MARCONI 2370 30Hz-110MHz... from £500
- H.P. 182 with 8557 10kHz-350MHz... £500
- H.P. 141T SYSTEMS 8553 1kHz-110MHz... £500
- 8554 50kHz-18GHz... £750
- H.P. 8443 Tracking Gen/Counter, 110MHz... £1000
- H.P. 8444 OPT 059... £750
- B&K 2033R Signal Analyser... £850
- H.P. 8754A Network Analyser, 4MHz-1300MHz... £1250
- H.P. 3557A Network Analyser, 5Hz-200MHz... £3000
- H.P. 53310A Mod Domain Analyser Opt 001/003... £5000
- ONO SOKKI CF300 Portable FFT Analyser... £1500
- H.P. 8720C Microwave Network Analyser, 50MHz-20GHz... £12500

STEWART of READING

110 WYKEHAM ROAD, READING, BERKS. RG6 1PL
Telephone: (0118) 9268041. Fax: (0118) 9351696
www.stewart-of-reading.co.uk
Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

Used Equipment - GUARANTEED. Manuals supplied
This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists.
Please check availability before ordering.
CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage

FRUSTRATED!

Looking for ICs TRANSISTORS?
A phone call to us could get a result. We offer an extensive range and with a world-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



- 2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD ADC AN AM AY BA BC BD BDT BDV BDW BDX BF BFR BFS BFJ BFX BFY BLY BLX BS BR BRX BRY BS BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUV BUW BUX BUZ CA CD CX CXA DAC DG DM DS DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA KIA L LA LB LC LD LF LM M MSM MA MAB MAX MB MC MDAJ MJE MJF MM MN MPS MPSA MPSH MPSU MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD STRM STRS SVI T TA TAA TAG TBA TC TCA TDA TDB TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN ZTX + many others

PLEASE ASK FOR OUR FREE CD-ROM (in Excel) STOCK LIST
We Stock a Massive Range of Components

Mail, phone, Fax Credit Card orders and callers welcome



Cricklewood Electronics Ltd
40-42 Cricklewood Broadway London NW2 3ET
Tel: 020 8452 0161 Fax: 020 8208 1441

SQUIRES

MODEL & CRAFT TOOLS

A COMPREHENSIVE RANGE OF MINIATURE HAND AND POWER TOOLS AND AN EXTENSIVE RANGE OF

ELECTRONIC COMPONENTS

FEATURED IN A FULLY ILLUSTRATED

624 PAGE MAIL ORDER CATALOGUE

2003 ISSUE

SAME DAY DESPATCH

FREE POST AND PACKAGING

Catalogues: FREE OF CHARGE to addresses in the UK.
Overseas: CATALOGUE FREE, postage at cost charged to credit card

SHOP EXTENSION NOW OPEN

Squires, 100 London Road, Bognor Regis, West Sussex, PO21 1DD


TEL: 01243 842424

FAX: 01243 842525



Learn to Program in C with FED !

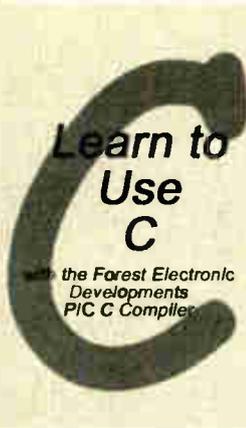Free book provides complete introduction to C programming for the PIC



Our free book will take you through the process of learning C from variables through constants to pointers and then structures and unions. Most of the examples are standalone and are as small as possible to enable the purpose and effect to be easily understood. Nearly all can be run on our PIC C Compiler simulator so you can experiment quickly - but code can also be run on practically any C Compiler.

- Start to use C for the PIC – standard portable code with a standard syntax designed to be “close” to the processor for efficiency in size and speed
- Suitable for beginners or BASIC programmers
- Covers Comments and Statements, Variables and Constants, Expressions, Functions, Program Control, Pointers, Structures & Unions, and the Pre-processor.
- The final example is a comprehensive real time programming application showing the simultaneous use of LCD, keypads, timers, clocks and ports
- Examples will run on our development board
- Soft copy of examples provided - ready to run on the PIC C Compiler
- Examples will run on other C Compilers


Download Free of Charge – www.fored.co.uk/ccomp.htm (follow the link “Learn C with FED”)

FED – PIC C Compiler products

WIZ – C Visual Development for the FED PIC C Compiler

- An application designer for the FED PIC C Compiler FULLY including the PIC C Compiler
- Drag a software component on to your design & set up the parameters using check boxes, drop down boxes and edit boxes (see shot below)
- Connect the component to the PIC pins using the mouse
- Select your own C functions to be triggered when events occur (e.g. Byte received, timer overflow etc.)
- Simulate, Trace at up to 10x the speed of MPLAB
- Generate the base application automatically and then add your own functional code in C or assembler
- Supports over 80 PICS - 16F87x, 16F627/8, 16C55x, 16C6x, 16F8x, 16C7xx 18Cxx, 18Fxxx, 12F629/675 etc.
- Demonstration download available :

www.fored.co.uk/CDemo.htm

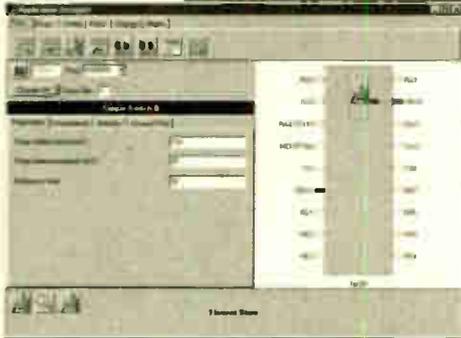

Screen shot (left) shows push button element connected to the PIC, Parameters may be set to control debounce and repeat. C function may be specified to call when the button is pressed

FED PIC C Compiler


- C Compiler designed to ANSI standards
- Supplied with library routines for C standard functions and many interface applications including I2C, LCD, LED's, timers, EEPROM, IRDA, Dallas 1 Wire, Hex Keypad, Maths, asynchronous serial interfacing, clocked data etc.
- With complete development/simulation environment including LCD/Keypad/LED/RS232 terminal
- View your simulation on a logic analyser application showing waveforms, timing or analogue results
- Profiler shows execution count, execution time and average time for functions and code blocks
- Smart linker – efficiently tiles routines throughout memory to minimise long jumps and page setting bits
- Supports the FED In Circuit Debugger for 16F87x and 18Fxx devices

WIZ-C and C Compiler Pricing :

PIC C Compiler	£60.00
PIC C Compiler Professional	£90.00
WIZ-C	£70.00
WIZ-C Professional	£100.00

WIZ-C products are provided with introductory tutorial, full extensive manuals provided on CD. All prices may be reduced by £20.00 if the product is purchased at the same times as WIZ-ASM, or serial programmer, or our Development board.

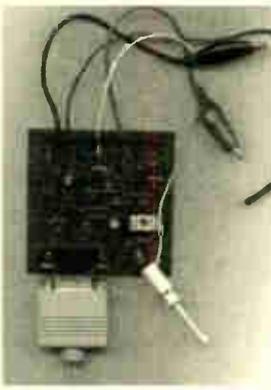In Circuit Debugger Supports 16F87x and 18Fxxx



- Allows real hardware to be examined & programs to be debugged and to be run in real time on your application
- The FED ICD requires only one data I/O pin on the PIC which can be chosen from any of ports B, C or D.
- Can program and re-program applications in circuit
- Up to 13 breakpoints (18F version)
- Run, Animate, single step and step over, run to cursor line, set PC to any value in the program
- Trace execution in the original C or Assembler source files
- View and change values of PIC special function registers, W and the ports.
- Standard serial interface to PC

Programmiers and Development Board (See web pages)

PIC Programmer - Handles serially programmed PIC devices in a 40 pin multi-width ZIF socket. 16C55X, 16C6X, 16C7X, 16C8x, 16F62x, 16F8X, 12C508, 12C508, 12C509, 16C72XPIC 14000, 16F87X, 18Cxxx, 18Fxxx, 12F6xx etc.

Also In-Circuit programming.

Operates on PC serial port

Price : £45/kit, £50/built & tested

Development Board – For ALL 40 pin PICS from 16cxxx, 16Fxxx and 18C/Fxxx. Includes In-Circuit Programmer – NO separate programmer required. LCD interface, hex keypad, LED's and Driver, 32 I/O pins on header, I2C EEPROM, 2 Serial Interfaces, Will run FED PIC BASIC (supplied free on CD ROM), 1A 5V regulator etc.

The CD-ROM is supplied with FED PIC BASIC and Compiler

Price : £45/kit, £50/built & tested, CD - £5.00. Manual on CD-ROM or download free from our web site

Forest Electronic Developments
12 Belcowne Walk, Sway,
LYMINGTON, Hampshire, SO41 6DU
Email – info@fored.co.uk
Web Site – <http://www.fored.co.uk>
01590-681511 (Voice/Fax)



Prices : Please add £3.00 for P&P and handling to each order, and then EU residents add VAT at 17.5%. Cheques/POs payable to Forest Electronic Developments, phone with credit card details, or order from our secure web site

MAIL ORDER ONLY • CALLERS BY APPOINTMENT

EPE PROJECT PICS

Programmed PICs for *EPE Projects

12C508/9 - £3.90; 16F627/8 - £4.90

16C84/16F84/16C71 - £5.90

16F876/877 - £10.00

All inc. VAT and Postage

(*Some projects are copyright)

EPE MICROCONTROLLER P.I. TREASURE HUNTER

The latest MAGENTA DESIGN - highly stable & sensitive - with I.C. control of all timing functions and advanced pulse separation techniques.

- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

KIT 847 £63.95

68000 DEVELOPMENT TRAINING KIT

- NEW PCB DESIGN
- 8MHz 68000 16-BIT BUS
- MANUAL AND SOFTWARE
- 2 SERIAL PORTS
- PIT AND I/O PORT OPTIONS
- 12C PORT OPTIONS

KIT 621

£99.95

- ON BOARD 5V REGULATOR
- PSU £6.99
- SERIAL LEAD £3.99

Stepping Motors

MD100...Std 100 step...£9.99

MD200...200 step...£12.99

MD24...Large 200 step...£22.95



PIC PIPE DESCALER

- SIMPLE TO BUILD
- HIGH POWER OUTPUT
- AUDIO & VISUAL MONITORING
- SWEPT FREQUENCY

An affordable circuit which sweeps the incoming water supply with variable frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve lathering ability by altering the way salts in the water behave.

Kit includes case, P.C.B., coupling coil and all components. High coil current ensures maximum effect. L.E.D. monitor.

KIT 868 £22.95 POWER UNIT.....£3.99



MICRO PEST SCARER

Our latest design - The ultimate scarer for the garden. Uses special microchip to give random delay and pulse time. Easy to build reliable circuit. Keeps pets/pests away from newly sown areas, play areas, etc. uses power source from 9 to 24 volts.

- RANDOM PULSES
- HIGH POWER
- DUAL OPTION

KIT 867..... £19.99

KIT + SLAVE UNIT.....£32.50



Plug-in power supply £4.99

WINDICATOR

A novel wind speed indicator with LED readout. Kit comes complete with sensor cups, and weatherproof sensing head. Mains power unit £5.99 extra.

KIT 856..... £28.00

★ TENS UNIT ★

DUAL OUTPUT TENS UNIT

As featured in March '97 issue.

Magenta have prepared a FULL KIT for this excellent new project. All components, PCB, hardware and electrodes are included.

Designed for simple assembly and testing and providing high level dual output drive.

KIT 866. . Full kit including four electrodes £32.90

Set of 4 spare electrodes £6.50

1000V & 500V INSULATION TESTER

Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms.

Kit includes wound coil, cut-out case, meter scale. PCB & ALL components.

KIT 848. £32.95



EPE TEACH-IN 2000

Full set of top quality NEW components for this educational series. All parts as specified by EPE. Kit includes breadboard, wire, croc clips, pins and all components for experiments, as listed in introduction to Part 1.

*Batteries and tools not included.

TEACH-IN 2000 -

KIT 879 £44.95

MULTIMETER £14.45

SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube plus instructions for message loading.

KIT 849 £16.99

12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMs at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

KIT 790 £29.90

SUPER BAT DETECTOR

1 WATT O/P, BUILT IN SPEAKER, COMPACT CASE 20kHz-140kHz

NEW DESIGN WITH 40kHz MIC.

A new circuit using a 'full-bridge' audio amplifier i.c., internal speaker, and headphone/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.

KIT 861 £24.99

ALSO AVAILABLE Built & Tested. . . £39.99



MOSFET MKII VARIABLE BENCH POWER SUPPLY 0-25V 2.5A

Based on our Mk1 design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.



Kit No. 845 £64.95

ULTRASONIC PEST SCARER

Keep pets/pests away from newly sown areas, fruit vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS



- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

KIT 812..... £15.00

SIMPLE PIC PROGRAMMER

KIT 857... £12.99


Includes PIC16F84 chip disk, lead, plug, p.c.b., all components and instructions

Extra 16F84 chips £3.84 Power Supply £3.99

MAGENTA BRAINIBOT I & II

- Full kit with ALL hardware and electronics
- As featured in *EPE* Feb '03 – KIT 910
- Seeks light, beeps, avoids obstacles
- Spins and reverses when 'cornered'
- Uses 8-pin PIC
- ALSO KIT 911 – As 910 PLUS programmable from PC serial port – leads and software CD provided

NEW

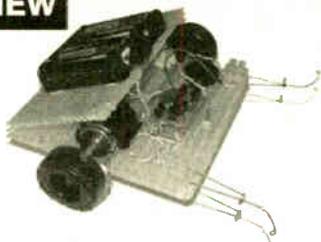

KIT 910 £16.99 KIT 911 £24.99

PIC 16F84 MAINS POWER 4-CHANNEL CONTROLLER & LIGHT CHASER

- ZERO VOLT SWITCHING
- OPTO ISOLATED 5 Amp
- 12 KEYPAD CONTROL
- HARD-FIRED TRIACS
- WITH SOURCE CODE
- SPEED & DIMMING POT.
- EASILY PROGRAMMED

Kit 855 £39.95

PIC 16F84 LCD DISPLAY DRIVER

INCLUDES 1-PIC16F84 WITH DEMO PROGRAM SOFTWARE DISK, PCB, INSTRUCTIONS AND 16-CHARACTER 2-LINE

LCD DISPLAY

Kit 860 £19.99

Power Supply £3.99

FULL PROGRAM SOURCE CODE SUPPLIED – DEVELOP YOUR OWN APPLICATION!


Another super PIC project from Magenta. Supplied with PCB, industry standard 2-LINE x 16-character display, data, all components, and software to include in your own programs. Ideal development base for meters, terminals, calculators, counters, timers – Just waiting for your application!

8-CHANNEL DATA LOGGER

As featured in Aug./Sept. '99 *EPE*. Full kit with Magenta redesigned PCB – LCD fits directly on board. Use as Data Logger or as a test bed for many other 16F877 projects. Kit includes programmed chip, 8 EEPROMs, PCB, case and all components.

KIT 877 £49.95 inc. 8 x 256K EEPROMS

ICEBREAKER

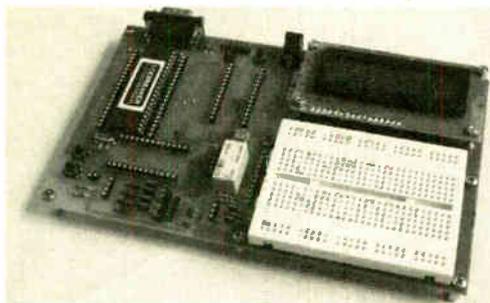PIC Real Time In-Circuit Emulator

- Icebreaker uses PIC16F877 in circuit debugger
- Links to Standard PC Serial Port (lead supplied)
- Windows™ (95+) Software included
- Works with MPASM and MPLAB Microchip software
- 16 x 2 L.C.D., Breadboard, Relay, I/O devices and patch leads: supplied

As featured in March '00 *EPE*. Ideal for beginners AND advanced users. Programs can be written, assembled, downloaded into the microcontroller and run at full speed (up to 20MHz), or one step at a time.

Full emulation means that all I/O ports respond exactly and immediately, reading and driving external hardware.

Features include: Reset; Halt on external pulse; Set Breakpoint; Examine and Change registers, EEPROM and program memory; Load program. Single Step with display of Status, W register, Program counter, and user selected 'Watch Window' registers.

KIT 900 . . . £34.99

POWER SUPPLY £3.99 STEPPING MOTOR 100 STEP £9.99

EPE PIC TOOLKIT 3

NEW

- THE LATEST TOOLKIT BOARD – 8, 18, 28 AND 40-PIN CHIPS
- MAGENTA DESIGNED P.C.B. WITH COMPONENT LAYOUT AND EXTRAS
- L.C.D., BREADBOARD AND PIC CHIP INCLUDED
- ALL TOP QUALITY COMPONENTS AND SOFTWARE SUPPLIED

KIT 880 . . . £34.99 with 16F84 . . . £39.99 with 16F877

PIC TOOLKIT V2

- SUPER UPGRADE FROM V1 • 18, 28 AND 40-PIN CHIPS
- READ, WRITE, ASSEMBLE & DISASSEMBLE PICS
- SIMPLE POWER SUPPLY OPTIONS 5V-20V
- ALL SWITCHING UNDER SOFTWARE CONTROL
- MAGENTA DESIGNED PCB HAS TERMINAL PINS AND OSCILLATOR CONNECTIONS FOR ALL CHIPS
- INCLUDES SOFTWARE AND PIC CHIP

KIT 878 . . . £22.99 with 16F84 . . . £29.99 with 16F877

EPE PIC Tutorial

At last! A Real, Practical, Hands-On Series

- Learn Programming from scratch using PIC16F84
- Start by lighting l.e.d.s and do 30 tutorials to Sound Generation, Data Display, and a Security System.
- PIC TUTOR Board with Switches, l.e.d.s, and on board programmer

PIC TUTOR BOARD KIT

Includes: PIC16F84 Chip, TOP Quality PCB printed with Component Layout and all components* (*not ZIF Socket or Displays). Included with the Magenta Kit is a disk with Test and Demonstration routines.

KIT 870 £27.95, Built & Tested £42.95

Optional: Power Supply – £3.99, ZIF Socket – £9.99

LCD Display £7.99 LED Display £6.99

Reprints Mar/Apr/May 98 – £3.00 set 3

SUPER PIC PROGRAMMER

- READS, PROGRAMS, AND VERIFIES
- WINDOWS® SOFTWARE
- PIC16C AND 16F – 6X, 7X, AND 8X
- USES ANY PC PARALLEL PORT
- USES STANDARD MICROCHIP • HEX FILES
- OPTIONAL DISASSEMBLER SOFTWARE (EXTRA)
- PCB, LEAD, ALL COMPONENTS, TURNED-PIN SOCKETS FOR 18, 28, AND 40 PIN ICs

- SEND FOR DETAILED INFORMATION – A SUPERB PRODUCT AT AN UNBEATABLE LOW PRICE.

Kit 862 £29.99

Power Supply £3.99

DISASSEMBLER SOFTWARE £11.75

PIC STEPPING MOTOR DRIVER

INCLUDES PCB, PIC16F84 WITH DEMO PROGRAM, SOFTWARE DISC, INSTRUCTIONS AND MOTOR.

Kit 863 £18.99

FULL SOURCE CODE SUPPLIED ALSO USE FOR DRIVING OTHER POWER DEVICES e.g. SOLENOIDS

Another Magenta PIC project. Drives any 4-phase unipolar motor – up to 24V and 1A. Kit includes all components and 48 step motor. Chip is pre-programmed with demo software, then write your own, and re-program the same chip! Circuit accepts inputs from switches etc and drives motor in response. Also runs standard demo sequence from memory.

MAGENTA

All prices include VAT. Add £3.00 p&p. Next day £6.99

Tel: 01283 565435 Fax: 01283 546932 E-mail: sales@magenta2000.co.uk

052003



Station Road, Cullercoats, Tyne & Wear, NE30 4PQ

Prices Exclude Vat @17.5%, UK Carriage £1.50 (less than 1kg) £3.50 greater than 1kg



See Next / Last Months Ad. for COMPONENT ACCESSORIES

Table of electronic components including 4000 Series, 74HC Series, and 74LS Series with part numbers and prices.

Table of electronic components including RAM, A/D Converters, Voltage Regulators, Diodes, and Transistors with part numbers and prices.

Table of electronic components including Bridge Rectifiers, Thyristors, Diodes, and Transistors with part numbers and prices.

Table of electronic components including various diodes, transistors, and other parts with part numbers and prices.

Tel: 0191 2514363 Fax: 0191 2522296 Email: sales@esr.co.uk http://www.esr.co.uk

EVERYDAY PRACTICAL ELECTRONICS

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

VOL. 32 No. 5 MAY 2003

Editorial Offices:

EVERYDAY PRACTICAL ELECTRONICS EDITORIAL
WIMBORNE PUBLISHING LTD., 408 WIMBORNE ROAD EAST,
FERNDOWN, DORSET BH22 9ND

Phone: (01202) 873872. Fax: (01202) 874562.

Email: enquiries@epemag.wimbome.co.uk

Web Site: www.epemag.wimbome.co.uk

EPE Online (downloadable version of EPE): www.epemag.com

EPE Online Shop: www.epemag.wimbome.co.uk/shopdoor.htm

See notes on Readers' Technical Enquiries below – we regret lengthy technical enquiries cannot be answered over the telephone.

Advertisement Offices:

EVERYDAY PRACTICAL ELECTRONICS ADVERTISEMENTS
MILL LODGE, MILL LANE,
THORPE-LE-SOKEN, ESSEX CO16 0ED

Phone/Fax: (01255) 861161 Email: epeads@aol.com

TIME OUT

Electronics can do all manner of things, quite often some it should not. During a recent overnight stay in a Travel Inn I experienced an unusual fault with the electronics. The TV set in the room had a built-in i.e.d. digital clock with an alarm facility. I set the alarm for 7.30a.m. and went to bed. As is often the case when sleeping in hotels, I woke up during the night at 4.45a.m. as shown by the clock. On waking again, later, I noted the clock still said 4.45, since it was getting light outside I checked my watch to discover it was actually 6.30. Oh well, the clock had somehow "frozen" at 4.45. However, I was surprised when the alarm sounded at 7.30, even though the display still said 4.45 and, to add to my amazement, when I cancelled the alarm the display returned to the correct time.

Now maybe I'm not being too bright – I certainly was not at 4.45a.m. – but then many readers will have experienced unusual phenomena when working with various circuits.

Cost Engineering

I remember many years ago when working in the RGD/KB development labs in Kent that one engineer was employed to cut the cost of various TV designs before they went into production. I was fascinated to see how many components he could strip out of a new TV circuit design and still get the set to work. Of course, some of the mods resulted in a degradation in performance that was unacceptable, but many seemed to make no difference.

The company also spent a great deal of time testing all sorts of components to see which ones would be the most cost effective in their products. For instance, would it be worth paying for a more expensive potentiometer if a cheaper one would last for a few years – say 10,000 operations – without getting "noisy" or breaking down. Remote control had not made much impact in those days so the on/off volume control would be used quite a bit. Cheaper pots would obviously suffice for lesser used controls like brightness and contrast.

With the massive increase in component reliability and reduction in cost over the years, I guess this type of cost saving engineering is not quite so important today. After all, it costs the same to make a chip containing 10,000 components as it does one with only 1,000 components, once the initial design has been finalised.



AVAILABILITY

Copies of EPE are available on subscription anywhere in the world (see opposite), from all UK newsagents (distributed by COMAG) and from the following electronic component retailers: Omni Electronics and Yebo Electronics (S. Africa). EPE can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased and downloaded for just \$10.99US (approx £7) per year available from www.epemag.com

SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £15.50, 12 months £29.50, two years £54; Overseas: 6 months £18.50 standard air service or £27.50 express airmail, 12 months £35.50 standard air service or £53 express airmail, 24 months £66 standard air service or £101 express airmail.

Online subscriptions, for downloading the magazine via the Internet, \$10.99US (approx £7) for one year available from www.epemag.com.

Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subs. Dept., Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimbome.co.uk. Also via the Web at: <http://www.epemag.wimbome.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Switch or Visa. (For past issues see the Back Issues page.)

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £6.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Amex, Diners Club, Switch and MasterCard accepted. Send, fax or phone your card number, card expiry date and card security code (the last 3 digits on or just under the signature strip), with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.



Editor: MIKE KENWARD

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Administration: FAY KENWARD

Editorial/Admin: (01202) 873872

Advertisement Manager:

PETER J. MEW, Frinton (01255) 861161

Advertisement Copy Controller:

PETER SHERIDAN, (01202) 873872

On-Line Editor: ALAN WINSTANLEY

EPE Online (Internet version) Editors:

CLIVE (MAX) MAXFIELD and ALVIN BROWN

READERS' TECHNICAL ENQUIRIES

E-mail: techdept@epemag.wimbome.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons.

PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in EPE employ voltages than can be lethal. **You should not build, test, modify or renovate any item of mains powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.**

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers (see *Shoptalk*). We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.

SUPER MOTION SENSOR

THOMAS SCARBOROUGH

Responds to minute fluctuations in light level. Will detect a single finger moving at 5 metres or a person crossing a path at 20 metres distance.

THE most basic problem with regard to standard light sensors is that these frequently trigger at a specific light level, while what happens in real life is that ambient light levels fluctuate all the time. Therefore a standard light sensor will function correctly only in a controlled environment, or under highly predictable conditions.

The Super Motion Sensor described here, on the other hand, auto-adjusts over the range of about 50 lux to 60,000 lux (that is, a 40W incandescent light-bulb in a 10m² room to direct sunlight). It really “shines”, dare we say, in the mid-range of about 100 lux to 10,000 lux (that is, a modestly lit room to bright shade).

It is what is called a “passive” system, in that it does not generate the light which it detects, nor does it use any additional circuitry for this purpose. At the same time, it may be used in the same way as both “active” and “passive” systems.

BRIGHT IDEAS

In daylight, the Super Motion Sensor will typically detect a single finger moving at a distance of 5 metres – *without* the use of any lenses. It will detect a person crossing a path at 20 metres’ distance – without lenses.

Under a.c. lighting, it will typically detect a person walking in front of an ordinary light source (e.g. a 60W incandescent light-bulb) at 20 metres – also without the use of any lenses. Note, however, that in this case the sensor is pointed *directly* at the light source, and its range as a “passive” system under a.c. lighting will typically be only eight metres or so.

Generally speaking, a single lens will double these distances, while the use of two lenses, if an “active” system is used, will multiply the basic range by six or seven. With an inexpensive laser diode, a

range of hundreds of metres may be achieved.

Since the circuit responds to *fluctuations* in light level, rather than the crossing of a specific light threshold, it is much more flexible than a typical active system. Also, it is not limited to crossing a light threshold in one direction only, e.g. from brighter to dimmer, but may be used in situations of decreasing *and* increasing light.

ENLIGHTENING IDEAS


The Super Motion Sensor has several possible applications and no doubt readers will have their own unique ideas, including possibly some of the following:



It may be used as a “light fence” (or broken beam alarm). However, in contrast to the standard light fence, it requires virtually no set-up. It may simply be placed within the line-of-sight of almost any light source, including vague ambient light, and switched on. It may also be used where a beam is “un-broken” – for example, where a computer monitor is blocking a beam, and the monitor is removed.

Since it is not limited to the crossing of a specific light threshold, it will respond to a wide range of variations in light and shadow – for instance, a car entering a driveway, a person moving in a room, or wind rustling the leaves of a tree.

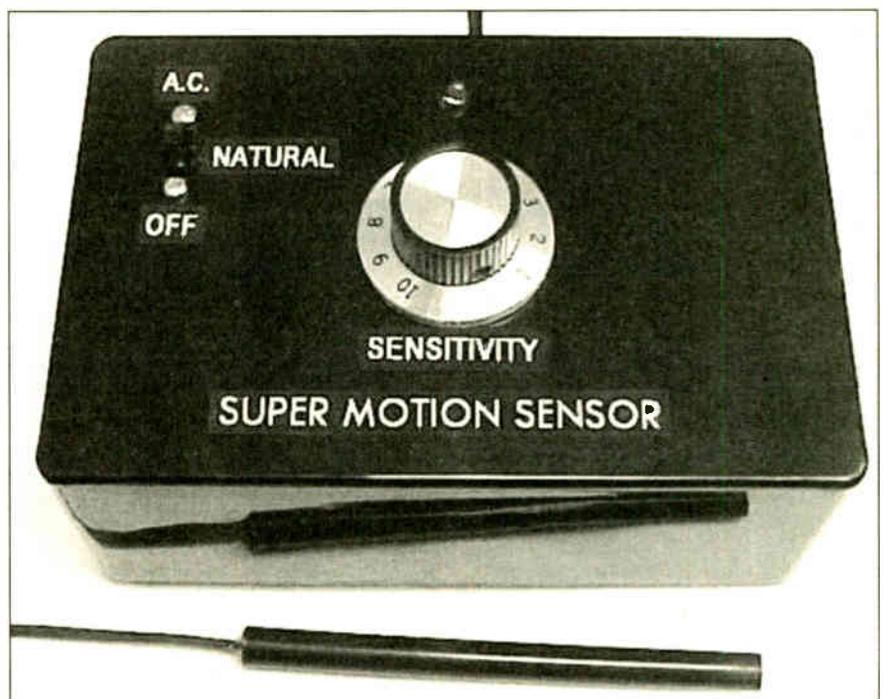The author’s original interest came from a three-wheel vehicle which he drove. This vehicle had an open cab, which seemed to invite all-comers to climb into it and play with the controls. In one case, a young boy let off the hand-brake and went careering into a tree! How could the vehicle sense, from a good distance, whether anyone was approaching?



With two light sensors mounted in the roof framework of the cab, one at each side of the vehicle, and "looking" down onto the pavement through plastic tubes, these detected feet moving over a wide range of lighting conditions. The circuit in turn triggered a spoken message – which, alas, seemed to attract yet more curiosity!

In a similar way, the Motion Sensor may be placed in luggage that needs to be protected in a public place, with a light sensor "looking" upwards over a suitable angle. If anyone should reach for the luggage, or stoop over it, or move it, an alarm would be triggered. Moreover, it would continue to trigger as long as the luggage was in motion.

Lastly, it may be used to detect *direction* of movement. If one refers to the author's *Big-Ears Buggy* project (*EPE*, Aug. '02), the two front-end preamplifier stages in that circuit may be replaced with two Super Motion Sensors, with the outputs of the "Sensors" being taken, in each case, from IC3 pin 6 to resistors R15 and R16 of the *Big-Ears Buggy*. In this case – as an example – a person entering a building would be detected, but not a person exiting.

the values of the capacitors were increased, this would further extend the time periods involved. A fire alarm system typically triggers when it detects a rise of 22°C per minute, while the Super Motion Sensor will potentially detect a change of just a fraction of 1°C. (A terrific Temperature Tracker, perhaps?).

When the charge on the capacitor (the potential) at the comparator's inverting (–) input rises higher than that at the non-inverting (+) input, or when the potential at the non-inverting input falls below that of the inverting input, the comparator's output goes "low", thereby triggering a monostable timer and a relay.

As with any detection circuit, there are certain physical variations which the circuit should detect, and others which it should exclude. Perhaps the most important exclusion in this case is natural variations in ambient light – such as sunrise, sunset, or the shadows cast by clouds. This the Motion Sensor achieves by comparing variations in light level at a speed that is *almost* too fast for it to detect slower, natural variations. Unless the circuit is set very sensitively, these are excluded.

moment a more sophisticated alternative (this was *not* incorporated in the present design, since it would have made it an "experienced constructors only" project). **The following should under no circumstances be tried unless the constructor is experienced with circuits that are connected to the mains. Mains electricity can kill you.**

Consider that the two bilateral switches receive their timing from the a.c. mains rather than the astable oscillator incorporated in the circuit. This would cause the circuit to switch in sympathy with fluctuations in a.c. lighting, thus making it virtually completely immune to 50Hz flicker (60Hz in the USA). Sensitivity under a.c. lighting would be significantly increased, and the need for any readjustment when moving the circuit from natural lighting to a.c. would be obviated.

The author tested this successfully by connecting a low voltage pulse derived from the a.c. mains supply to the control pins of the bilateral switches. In this case, the link wire adjacent to pin A (Fig.4) is removed from the printed circuit board (p.c.b.), and the peak voltage pulse is adjusted to just below 12V.

This last concept opens the possibility of a Defective Lighting Detector. If a.c. lighting should waver or become defective, the Super Motion Sensor would immediately pick this up. The author's prototype picked up several "brownouts" (voltage/lighting drops) during testing.

ANALOGUE vs DIGITAL

Originally, the author took a *digital* approach, translating light level to binary numbers, then making a binary comparison over time. This was done by converting the resistance of the l.d.r. to frequency, and the frequency to binary numbers. If a series of binary comparisons showed themselves to be unequal, then a motion was detected.

This approach, however, ran into an unthought-of hitch. In order to obtain two binary numbers which were sufficiently accurate to compare reliably, at high sensitivity (thus obtaining an equal result if the light level remained constant), a high degree of timing accuracy was required. While this would not have been too difficult to achieve, it would have considerably complicated the circuit.

Another problem presented itself with this approach, in that if a relatively constant light level caused the least significant binary digit to switch between a 0 and a 1, or to vacillate between the two, this gave the illusion of detection having taken place. A solution which was tried successfully was to make a *series* of binary comparisons instead of only one.

The present analogue approach, besides avoiding these difficulties, obviates the need for three or four digital i.c.s. or a microcontroller at the core of the circuit.

CIRCUIT DETAILS

We are now in a position, we might say, to "shed more light" on the full Super Motion Sensor circuit – see Fig.2.

One half of a 7556 CMOS timer i.c. (IC1a) is wired as an astable oscillator, and, with the help of IC2c, configured as an inverter, this is used to switch bilateral switches IC2a and IC2b alternately. This circuit configuration is seldom seen, due

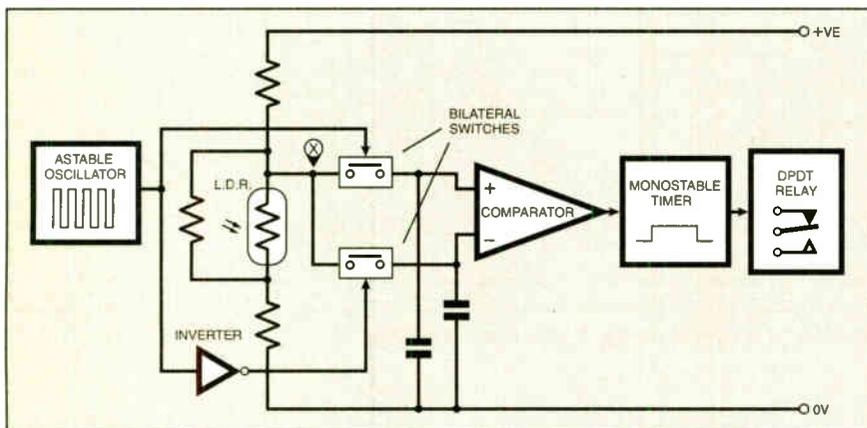


Fig.1. Simplified block schematic diagram of the Super Motion Sensor.


HOW IT WORKS

Block diagram Fig.1 is a simplified representation of the circuit, and gives a good overview as to how the Super Motion Sensor works.

A light dependent resistor (l.d.r.) is so wired in conjunction with the three resistors shown that, between darkness and full sunlight, it offers a potential at point X of between roughly one-quarter and three-quarters of the supply voltage. This potential is presented simultaneously to the inputs of two bilateral switches.

An astable oscillator, together with an inverter, switches the two bilateral switches alternately, typically at a few Hertz, so that the two capacitors are alternately charged. Since the resistance of the bilateral switches in the "off" state is very high, and the input impedances of the op.amp comparator very high, the charge on the capacitors is "trapped" in the spaces between the bilateral switches and the comparator. This will ordinarily vary very little during switching. These are referred to as sample-and-hold circuits.

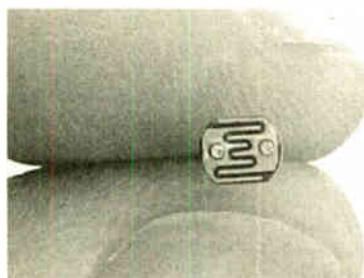So little, in fact, does the charge on the two capacitors vary over time that the astable oscillator could easily be slowed, and the l.d.r. replaced with a thermistor. If



Miniature light dependent resistor (l.d.r.), about twice size, clasped between thumb and finger.

While still on the *concept* of the Super Motion Sensor, a difficulty arises when a.c. lighting is used, as it does with most light sensor circuits. This is because a.c. lighting fluctuates at a rate of 50 cycles per second (60 in the USA), and while the eye does not normally see this, due to persistence of vision, the fluctuation or flicker of a.c. lighting can be sufficient to trigger the circuit. The more the light flickers (e.g. fluorescent lighting), the greater the difficulty this presents.

DANGER LEVEL

A simple solution is given later with the circuit shown in Fig.2 – but consider for a

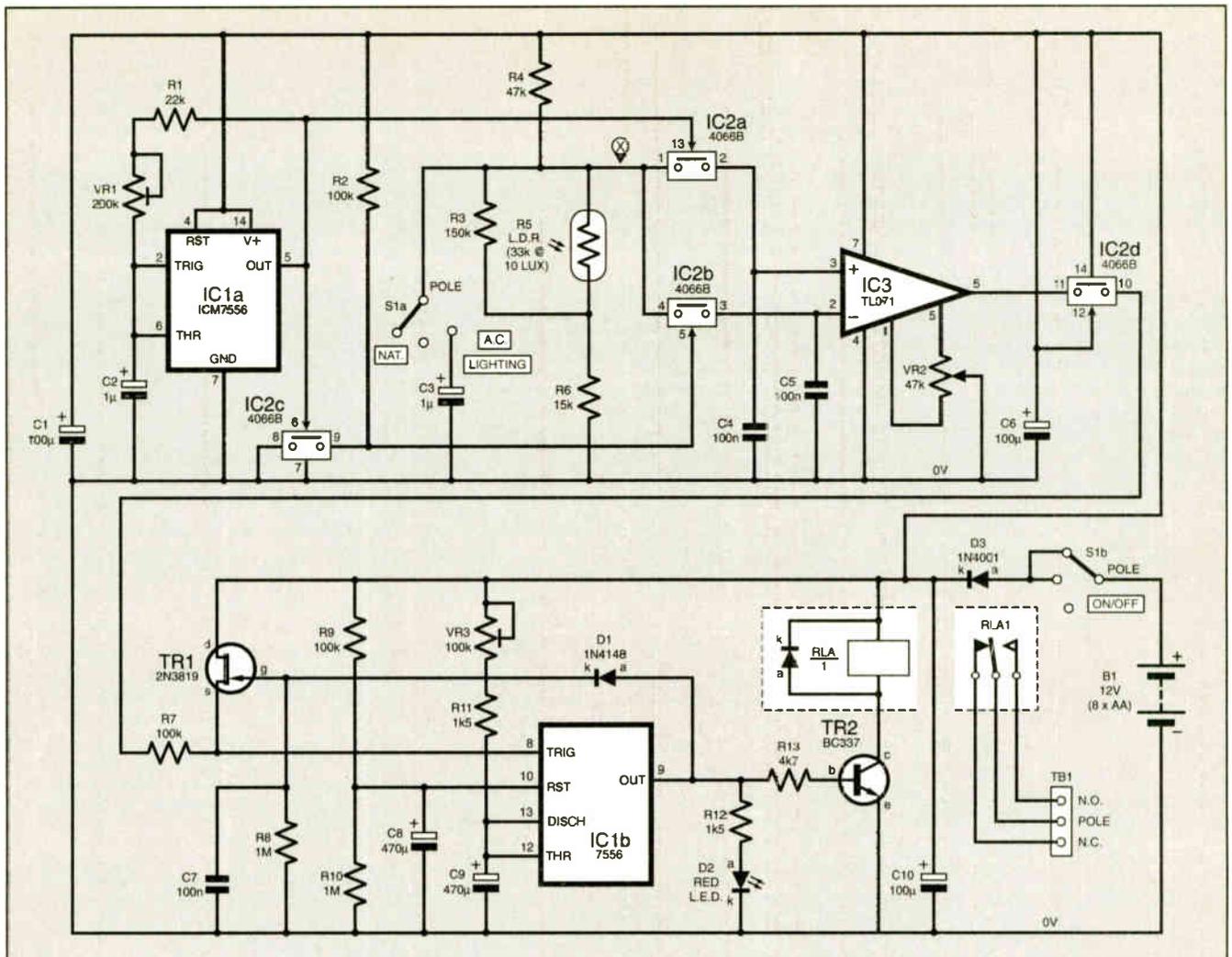


Fig.2. Complete circuit diagram for the Super Motion Sensor.

probably to its inability to be more than lightly loaded without disturbing the timing. However, in this case IC2's control pins have a very high input resistance, and this configuration represents an easy means of obtaining the required 1:1 mark-space ratio which the "orthodox" configuration does not so simply provide.

Potential divider network R3 to R6, including the l.d.r., provides the required potential at point X to charge capacitors C4 and C5 through the bilateral switches. The values of R3, R4 and R6 are chosen so that, regardless of the light sensor used, the potential at point X stays between 24% and 78% of supply voltage. This means that a wide variety of sensors may be used in place of the specified l.d.r., including phototransistors, photodiodes, and infra-red and ultra-violet devices.

INTERCHANGE

Although l.d.r.s have slower response times than other devices, an l.d.r. was chosen here because it may easily be interchanged with similar devices of the same family. This is not always the case with phototransistors and photodiodes, which have some awkward relatives. Note that if a photodiode is used, the cathode (k) would normally be wired to the junction of R3 and R4. An l.d.r. is completely non-polar.

Consider now that if the light level remains constant over time, there will be a similar charge on capacitors C4 and C5.

However, if the light level *changes* over time, one of the two capacitors will retain a higher or lower charge than the other. This triggers op.amp comparator IC3 (that is, it goes "low" at its output).

Strictly speaking, the comparator triggers only if the voltage at the inverting input rises above that at the non-inverting input – i.e. if the voltage at the inverting input rises, or if the voltage at the non-inverting input falls. However, bear in mind that every increase in light level is followed by an attendant decrease and vice versa, so has little consequence in practice.

The two bilateral switches, IC2a and IC2b, are switched between about 3Hz and 30Hz, depending on the setting of preset VR1. Faster switching will mean smaller differences in charge between C4 and C5 (thus lesser sensitivity), but will react more readily to faster fluctuations in light level. Slower switching will mean the opposite, and would make the circuit a little more sensitive to natural variations such as moving clouds. Preset VR1's mid-position should suit in most cases.

ROUGH AND READY

With regard to a.c. lighting, the present circuit offers a rough and ready solution in the form of smoothing capacitor C3 at point X, which smooths out the worst of a.c. flicker. A necessary result of this, unfortunately, is some loss of sensitivity, although it does present a reasonably

good solution. For particularly bad lighting situations, the value of C3 may be increased.

Op.amp comparator IC3 was chosen particularly for its high input impedance, which is necessary so that capacitors C4 and C5 should retain their charge. It was also chosen specifically for its provision of an offset-null, which is used to balance the differential input stage so that the inverting input is normally "higher" than the non-inverting input.

Failing this, the potentials at the two inputs would be "too close for comfort", and might or might not trigger IC3. A method that is frequently used to "balance" such circuits is a potential divider at the inverting input, but for a number of reasons, this is less satisfactory.

SENSE OF AMBIENCE

Bilateral switch IC2d represents another circuit option. As it stands, IC2d has its control pin (12) wired to the positive rail, so that the corresponding bilateral switch will always conduct.

However, if IC2d pin 12 were taken to a potential divider incorporating a second l.d.r., as shown in Fig.3, IC2d could be used to disable the Motion Sensor as ambient light levels either increased or decreased.

As shown, the circuit is disabled with increasing light level. If R1 and VR1 were swapped around with the l.d.r., the circuit


would be disabled with decreasing light level.

EXTREMELY SENSITIVE

The present circuit is one of extreme sensitivity, and the first stages especially require "quietness" to function properly. Therefore, no l.e.d. is used to display the switching action of IC1a (although this might be helpful). Also, no l.e.d. is used to show the state of the output of IC3. A relatively small value is chosen for timing capacitor C2, and supply decoupling is employed throughout (C1, C6, and C10).

A special problem presents itself, however, in the form of relay RLA. This carries a relatively heavy current when switched by monostable IC1b, and would ordinarily upset the circuit and reduce its sensitivity.

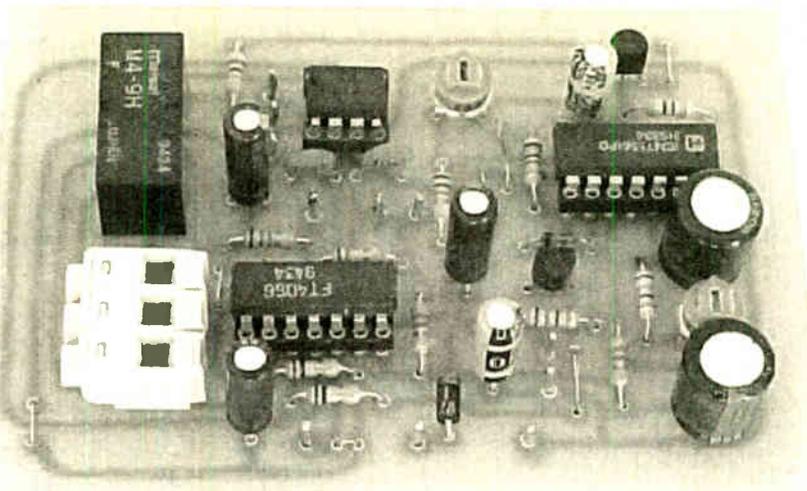This problem is overcome by "blanking" the relay's action through transistor TR1, which disables the trigger input (pin 8) of timer IC1b, allowing a short period (a fraction of a second) for the circuit to settle



Layout of components on the completed circuit board. The relay can be seen top left.

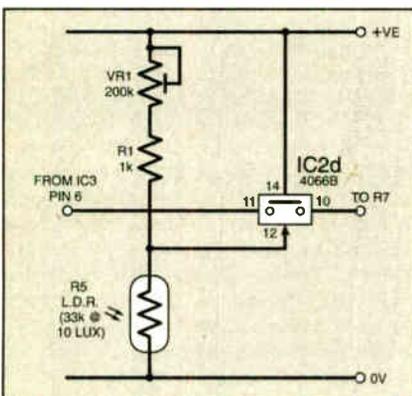


Fig.3. Circuit addition, using a second l.d.r., to achieve daytime/night-time switching.

after relay RLA has disengaged. At the same time, l.e.d. D2 is included in this blanking, so that it, too, may not upset the normal operation of the circuit.

The blanking action works as follows: When the output of IC1b goes "high", capacitor C7 is charged, and TR1's gate is held "high". This means that it conducts, and the potential at the junction of TR1 source and R7 is also high.

Therefore, with trigger pin 8 being held "high", this is disabled for a moment, giving the circuit time to settle after relay RLA has disengaged. Capacitor C7 discharges mainly through resistor R8.

Current consumption of the circuit is less than 10mA on standby, so that battery operation (e.g. 8 x AA batteries) is feasible.

CONSTRUCTION

The Super Motion Sensor is built on a printed circuit board (p.c.b.), measuring 65mm x 95mm. The topside component layout and full-size underside copper foil master are shown in Fig.4. This board is available from the EPE PCB Service, code 391.

Begin construction by soldering in position the three dual-in-line (d.i.l.) sockets and the board lead-off solder pins. This should be followed by the resistors, capacitors and the preset potentiometers VR1 and VR3. Next, the diodes D1, D3 and the two transistors should be inserted on the p.c.b., paying particular care to their polarity.

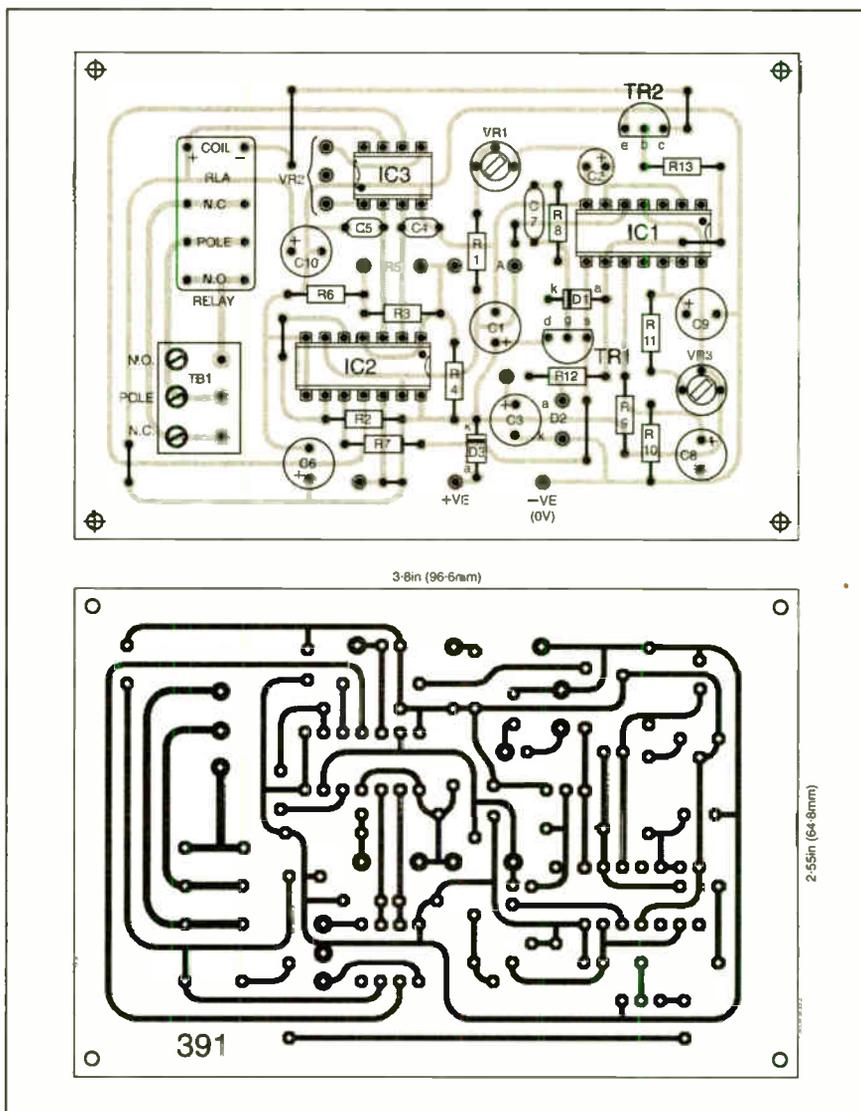


Fig.4. Printed circuit board topside component layout and full-size underside copper foil master pattern for the Super Motion Sensor.

Finally, the relay and the three-way terminal block should be installed on the board.

Use suitable lengths of connecting wire to wire up the off-board components VR2, l.e.d. D2, slide switch S1 and the battery clip. The author used a length of 8-way ribbon cable to provide a neat result.

LIGHT SENSOR

When an l.d.r. is in its "naked" state, it has a very wide viewing angle, and its sensitivity is low. The sensitivity may be greatly enhanced by making it "look" down the length of a narrow, black tube (see Fig.5 and photograph). In this way

the distances described earlier were achieved.

The tube may be cut from the shaft of a felt pen. The leads of the l.d.r. are then stuck through a small, firm piece of foam rubber (not conductive foam rubber!), soldered to a suitable length of "twin-flex" wire, and pushed into the tube.

Epoxy glue is used to set the whole in place, and a rubber grommet may be added

to the case for neatness. The sensor is then soldered to the p.c.b. as shown in the interwiring diagram Fig.5.

CASING-UP

Once soldering is complete, insert the i.c.s in the d.i.l. sockets, observing the correct orientation (note: these are orientated differently). Note that IC1 and IC2 are CMOS devices, and require care when handling (first discharge your body to ground). In the author's experience, j.f.e.t. TR1 is also more fragile, and it, too, requires some care.

Mount the Sensitivity control VR2, l.e.d. D2 and slide switch S1 on the case base; now the top. The constructor might also wish to replace presets VR1 and VR3 with shafted potentiometers, and mount these on the case for easy adjustment. The p.c.b. was mounted on the lid (bottom) of the case, and a partition was slotted into the case to hold the batteries.

While the circuit diagram Fig.2 shows a 12V power supply, the circuit may also be powered off 9V if desired. Note that the relay's voltage rating will need to match the supply voltage. Alternatively, a lower voltage rating may be used for the relay (e.g. 5V), if the link wire at TR2's collector is replaced with a suitable resistor.

If in doubt, use a one kilohm (1k) preset potentiometer here wired as a variable resistor, beginning at 1k and turning it back until the relay triggers in sync with l.e.d. D2. The preset may then be replaced with a fixed resistor.

Generally speaking, a Telecom relay (for which the p.c.b. is designed) will carry about 60W across its switching contacts – but check specifications first.

The author used an ultrabright red l.e.d. for D2, so that the circuit could be tested at a distance. In some cases, the range of the

circuit is such that an ordinary l.e.d. may not be seen without binoculars!

A p.c.b.-mounting terminal block is used to connect the unit to external circuits (e.g. a siren). The provision of "blinking", as described earlier, enables one to run such circuits off the Super Motion Sensor's own power supply.

CALIBRATION AND USE

Commence the setting up of the Sensor by turning preset VR1 and potentiometer VR2 to their mid positions, and turn preset VR3 back (anticlockwise) completely, then switch on – selecting natural or a.c. lighting with switch S1.

The circuit will take a few seconds to settle and come to life, as capacitor C8 charges and IC1b's reset pin goes "high". L.E.D. When VR2 is suitably adjusted, D2 should illuminate and the relay click as a hand is moved over the l.d.r.

If l.e.d. D2 illuminates repeatedly, turn back VR2 (anticlockwise). If it does not illuminate at all, turn it up (clockwise).

If the circuit does not work as described, immediately switch off and disconnect the power, and carefully re-check. Ensure that there are no solder bridges on the p.c.b., that all components are inserted correctly, and that all interwiring is correct.

Once it has been established that the circuit is working, presets VR1 and VR3 may be further adjusted. The function of VR1 has been described above. Preset VR3 adjusts the trigger period of monostable IC1b and thus the "on" time of the relay between about half a second and 30 seconds.

The Super Motion Sensor will work best in situations of good contrast (e.g. shadows on a white wall). It would be best to adjust it to a little less than its maximum sensitivity.

What ultimately matters is that it should exclude any variations in light level that might cause unwanted triggering – e.g.

COMPONENTS

Resistors

R1	22k	See SHOP TALK page
R2, R7, R9	100k (3 off)	
R3	150k	
R4	47k	
R5	min. light dependent resistor (l.d.r.), 33k @ 10 lux (or similar – see text)	
R6	15k	
R8, R10	1M (2 off)	
R11, R12	1k5 (2 off)	
R13	4k7	

All 0-25W 5% carbon film, except R5

Potentiometers

VR1	200k cermet preset
VR2	47k rotary carbon, linear
VR3	100k cermet preset

Capacitors

C1, C6, C10	100µ radial elect. 16V (3 off)
C2, C3	1µ radial elect. 16V (2 off)
C4, C5, C7	100n ceramic disc (3 off)
C8, C9	470µ radial elect. 16V (2 off)

Semiconductors

D1	1N4148 signal diode
D2	5mm ultrabright red l.e.d.
D3	1N4001 50V 1A diode
TR1	2N3819 n-channel field effect transistor
TR2	BC337 npn medium power transistor
IC1	7556 CMOS dual timer
IC2	4066B quad bilateral switch (or equivalent)
IC3	TL071CN j.f.e.t. op.amp

Miscellaneous

S1	2-pole 3-position slide switch
RLA	12V coil, p.c.b. mounting relay, Telecom type with built-in protection diode (see text)
TB1	3-way, p.c.b. mounting, terminal block, 5mm pitch

Printed circuit board available from the EPE PCB Service, code 391; ABS plastic case, size to suit; 8-pin dual-in-line (d.i.l.) socket; 14-pin d.i.l. socket (2 off); calibrated knob; black plastic tube for l.d.r. housing (see text); 8 x AA battery holder; battery clip; 8-way ribbon cable (optional); "twin-flex" wire; link wire; solder pins; solder, etc.

Approx. Cost
Guidance Only

£15
excl. batts & case

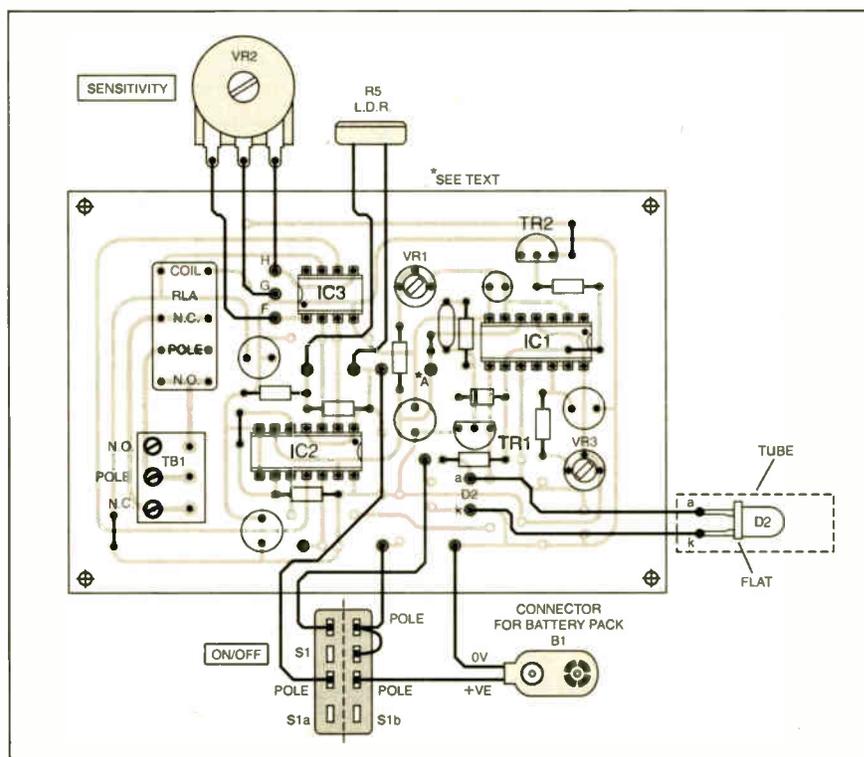


Fig.5. Details of the interwiring from the circuit board to off-board components. Note that the On/Off slider switch contact line-up may differ to that shown.



Completed Sensor showing front panel Sensitivity control and the lighting conditions slide switch.


birds flying past, leaves fluttering, or cloud movements. Even if sensitivity is reduced by, say, one-quarter, the circuit remains unusually responsive.

With some experimentation, it may be set to transition seamlessly from Natural to A.C. lighting – but this, unfortunately, will not occur at maximum sensitivity for both.

If maximum sensitivity under natural lighting triggers the circuit under a.c., then adjust for maximum sensitivity under a.c. – and vice versa.

Radio Bygones

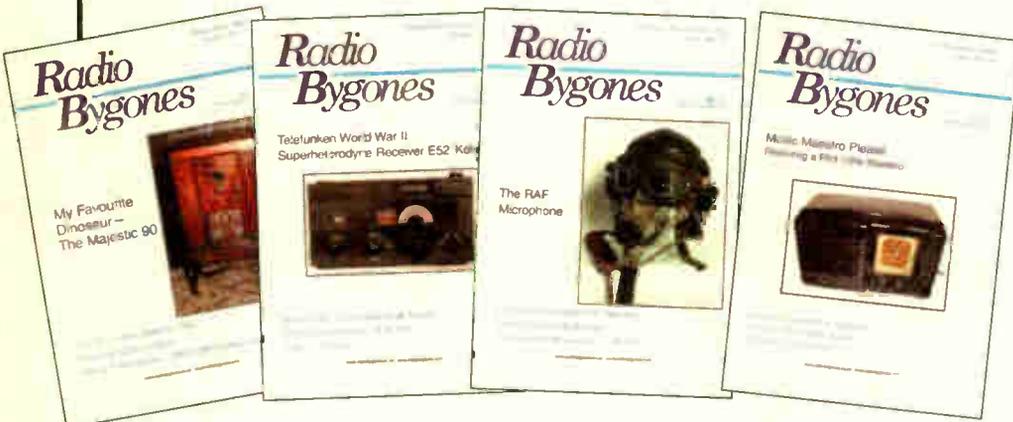The leading magazine for vintage radio enthusiasts



Now Also Available To **BUY ONLINE**
www.radiobygones.com
 Log on, pay by credit card and download the magazine to your PC
ONLY \$9.99 (US dollars)
FOR 6 ISSUES
 A free issue is available

WHETHER your interest is in restoring domestic radio and TV or in amateur radio, in military, aeronautical or marine communications, in radar and radio navigation, in instruments, in broadcasting, in audio and recording, or in professional radio systems fixed or mobile. RADIO BYGONES is the magazine for you.

ARTICLES on restoration and repair, history, circuit techniques, personalities, reminiscences and just plain nostalgia – you'll find them all. Plus features on museums and private collections and a full-colour photo-feature in every issue.

IT'S MOSTLY about valves, of course, but 'solid-state' – whether of the coherer and spark-gap variety or early transistors – also has a place.

FROM THE DAYS of Maxwell, Hertz, Lodge and Marconi to what was the state-of-the-art just a few short years ago . . .

There is also a selection of free readers' For Sale and Wanted advertisements in every issue.

Radio Bygones covers it all!

THE MAGAZINE is published six times a year, and is available by postal subscription. It is not available at newsagents.

TO TAKE OUT a subscription, or to request a sample copy, please contact:

RADIO BYGONES, Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.

Tel: 01202 873872. Fax 01202 874562. Web sites: www.radiobygones.co.uk www.radiobygones.com

Tiny Tags Talk Volumes

Barcodes are set to disappear! Andy Emmerson explains.

FOR many people (including the author!) "retail therapy" is an ideal means of lifting the spirit but even then the pleasure can easily vanish when faced with a long checkout queue and a barcode scanner that refuses to recognise product codes. At this stage cashiers tend to panic and call for assistance leaving shoppers to seethe while the queue that they haplessly chose is log-jammed.

Barcode scanning may soon be a thing of the past, however, if the current plans for r.f. tagging keep to schedule. And time is at the heart of this story simply because time is money to retailers.

Barcodes take time to scan, simply because they have to be passed manually in front of a scanning device. The more goods you are buying, the longer the process is and the slower the transaction. Obvious that may be but it's also highly relevant to supermarket customers in a hurry to get home at 6pm on a Friday evening.

TOUCHLESS TECHNIQUE

A far better solution would be one in which each product you have bought "told" the till its details without prompting or handling. The same applies to luggage transiting airports, and commuters boarding buses or trains in the rush hour. For all of these a touchless solution would be far preferable.

Commuters are lucky. In several major cities season ticket holders now have a radio-activated pass that needs only to be waved near a sensor (no more shoving tickets into slots). The same technique is used to protect high-value goods in retail stores; try walking out of a clothing store with an unpaid-for garment, then stand by for action as the alarm goes off.

All of these systems rely on tuned radio circuits embedded in tags or tickets detuning a low-power radio frequency field. The same principle underpins the new RFID (radio frequency identification) tags proposed to replace barcodes on retail goods and travellers' baggage.

Applying an RFID tag to every product out on the shelves is the retailer's ultimate dream, a concept endorsed at the annual Retail Automation Conference in London last autumn. At this stage the cost of the tags and the new equipment to interrogate them is still prohibitive but this is set to plummet as the idea catches on. Unified standards need to be drawn up too before the practice becomes commonplace or even universal, but the idea is to create a single, globally recognised numbering scheme similar to the universal product code employed on barcodes now. There are also data privacy issues to be resolved if retailers associate RFID tag data with customers' loyalty card details.

One firm that has committed to RFID tagging is personal hygiene manufacturer Gillette, which has purchased 50 million tags for use in the UK and USA. Tesco is its first retail partner and will trial tagged Gillette products in Cambridge. Other early adopters, such as Woolworths in the UK and the GAP fashion stores in the USA, have already conducted trials and seen the merits of the system. Data accuracy is stated as 99.7 per cent, far better than previous systems, and the feeling is that companies should concentrate on the benefits rather than the cost.

FOOD CHAIN

Even if you do not spot RFID tags immediately in your local supermarket, that does not mean the idea has failed. They will still be used for coding products by the crate or tray load further back in the food chain, for instance at Marks & Spencer. The upmarket retailer recently announced the world's largest rollout of RFID tagging, with a scheme to tag 3.5 million food trays passing through its warehouse and distribution system.

As pallets or cases of goods leave one location for another, they will pass readers that will pinpoint the progress of each and every consignment. As well as helping pinpoint slow-moving inventory, the system will also provide automatic proof-of-delivery at each point along the line of route, assisting both Marks and their suppliers. "Stock shrinkage" (*theft* to the rest of us) will be reduced too, as it will be possible to spot the exact stage where items go missing. The same technique is already in use in parts of the automotive industry.

The savings suppliers make can be passed on to consumers and there are other end-user benefits too. Greater information capture means better stock control; wastage will be reduced and shelves should never go empty under normal conditions. It will also be easier to identify, in real time, batches of products that need to be recalled or replaced for any reason.

TECHY STUFF

So much for the benefits, how exactly do RFID tags work? Tags can be active (with an integrated battery) or else passive (deriving energy from the r.f. field generated by

the reader). Active tags have longer range and can transmit more information but carry a heavy cost penalty. Passive tags are much lighter, less expensive and should last more or less forever.

A company in the USA, Allen Technology, produces a read-only tag with 64-bit memory weighing 25 grams. It operates on 915MHz, a licence-free band for industrial, scientific and medical purposes in North America (used for cellular radio here in Europe). Another US firm, Matrics, also uses this band; its products have a read range of three metres and the product is totally tamperproof.

In Europe Philips has joined forces with Tagsys to develop a low-cost smart label system operating at 13.56MHz. These tags, which are similar in size to the sticky label security tags already used to prevent theft, incorporate tiny i.c.s made by Philips, used with r.f. equipment made by Tagsys, and can be read at a rate of 150 items per second.

The actual data that can be contained in RFID tags is awesome and far greater than the humble barcode can carry. Tags applied to some EMI CD albums already state a global product identification code that embraces their origin and final retail destination. This is only the tip of the proverbial iceberg and the data has the potential to document a complete product history, including date and place of manufacture, ownership and far more.

READY FOR TAKE OFF

There is a general agreement that RFID tagging will take off when the cost of the tag drops to one per cent of the cost of the product it is applied to, and that date is still some way off. Semiconductors made of organic materials are cited as one way of reaching this price break but the jury is still out on the feasibility of the manufacturing process. It is, nonetheless, a matter of when rather than whether, simply because the benefits are so attractive.

A report by analysts AMR Research indicates that early adopters have reaped cost savings equalling five per cent of sales turnover, an advantage not to be sniffed at. 2005 is the date that the research firm says when r.f. tagging becomes viable and until then we must wait and see.

Ancient Optical Comms

Mechanics' Magazine 7 January 1826 describes an ingenious "Gas-Light Night Telegraph" which, despite thoughts to the contrary, was not an April Fool project.

Six gas lanterns were arranged in a triangle and could be illuminated or extinguished rapidly by opening and closing gas taps to the main supply, concealed pilot flames doing the actual lighting. Combinations of lamps lit would indicate letters of the alphabet, rather as pointing needles did in the electric telegraphs of Cooke and Wheatstone that followed soon afterwards – and rendered this form of optical communication still-born.

ATRAC-TIVE MUSIC SNACKING

Barry Fox highlights Sony's system that can rip 30 music CDs onto one.

SONY has announced a major modification of the CD system which lets home copiers rip at least 30 music CDs onto a single blank CD, and play the music back on a £100 portable stereo.

Sony's system, to go on sale in May, uses Atrac3Plus, a much improved version of the ATRAC compression system which Sony developed ten years ago for Mini Disc. Now that the patents on CD have run out, Sony is free to adapt ATRAC for use with CD. Sony has coined the phrase "music snacking" because one disc can hold enough different music to satisfy every taste or mood.

By analysing the music in 52 separate frequency bands before converting it into digits, and then tweaking the digits, ATRAC records stereo onto a blank CD at 48Kbps, which is around a third the amount of data needed for MP3 and one thirtieth the amount used for CD. So one blank CD, costing a few pence, can now hold 30 hours of music.

Sony's new ATRAC CD Walkman will start at under £100 and play either the new home-recorded 30 hour discs, or conventional CDs, or MP3 discs. The price includes free ATRAC compression software, called Sonic Stage "Simple Burner", that lets a home computer do the recording.

The player comes with rechargeable batteries which allows up to 150 hours playing time. This, reminds Sony, is "enough to fly to Australia and back three times".

Sound quality will be acceptable for people who are used to listening to MP3.

Jack Rabbit

Philips, the company which jointly owned the patents on CD, is doing things differently. Philips' new DVD PC burner

works at four times normal speed to record music in MP3 format onto blank DVDs – which hold at least seven times as much music as a blank CD. The MP3 DVDs then play back on a portable DVD player called Jack Rabbit, costing around £200.

News of both developments came as a surprise to the music industry's trade bodies, the International Federation for the Phonographic Industry and Recording Industries Association of America. But both bodies were surprisingly sanguine. The RIAA did not feel the need to make any comment and the IFPI says its faith is in "the availability of legitimate on-line music services". These, the IFPI hopes, will encourage people to buy music instead of copying it for free from CDs or unauthorised Internet sites.

Less surprising, Sony Music also refused to comment.

SAVE WITH FLUKE

FLUKE is offering a 24% saving when purchasing their Combo Kit. This includes the top of the range 179 DMM, which is a true r.m.s. meter, an integrated temperature probe, set of silicon test leads and hook clips, and alternative leads with special electronic test probes.

The meter offers 0.09% basic d.c. accuracy, has a large easy to read 6000 count backlit display and features an analogue bargraph. Frequency, capacitance and resistance ranges are up to 100kHz, 10,000 μ F and 50M Ω respectively. Temperatures up to +260°C can be read with the plug-in Fluke 80BK thermocouple probe.

In addition the meter offers enhanced troubleshooting features, which include Min/Max/Avg recording, with an audible warning, AutoHold and Display Hold. A set of the latest 1.5m long SureGrip silicone test leads are included, plus a meter and accessory case, a pair of test probes offering 1mm replaceable steel and spring loaded gold tips, and a hook set with a 6.4mm opening.

The suggested retail price for the kit is £188, representing a 24% saving over the purchase of the individual items. It is available from authorised Fluke distributors. Browse www.fluke.co.uk.



ALLIGATOR CLIPS



POMONA Electronics have introduced a complete family of flexible boot alligator test clip products. They have a CAT III 1000V 10A rating and are adaptable to meet a variety of test needs, attaching to terminals up to 7.6mm o.d.

Pomona's offering includes two probe tip adapters, two patch cords and one alligator clip for test lead attachment. The probe adapters interface to standard 2mm and 4mm lantern tip DMM probes. The patch cords include alligator-to-alligator, and alligator-to-rightangle sheathed banana plug and are offered with flexible heat resistant silicone wire.

For more information browse:

www.pomona.cc and www.pomonaelectronics.com.

OUT THE WINDOWS

By Barry Fox

NOT everyone wants Windows. In October '02, Microsoft and Orange staged a mega event in London to announce the world's first Windows-powered Smartphone service. SPV will offer Sound, Pictures and Video on the move for 40 million Orange subscribers in 21 countries, using GPRS cell-phones with the Windows operating system and Internet Explorer. The Orange phones are made under contract in Taiwan by HTC.

At the launch Microsoft and Orange proudly announced outside support from Sendo, the go-getting cell-phone company started by ex-Philips management and now selling high spec, low cost phones in over twenty countries in Europe and Asia. Sendo was at the Microsoft event to show off the Windows-powered Z100 "world's smartest phone". But now Sendo has dumped Microsoft Windows and switched to the rival Nokia/Symbian operating system.

Sendo says that "for legal reasons" it cannot say why it canned the deal with Microsoft, just weeks before launch of the Z100. But a spokeswoman confirms that Sendo now wants to work with a company which lets its partners work with the source code. Microsoft won't, Nokia will.



A COMPLETE RANGE OF INVERTERS

150W TO 2500W - 12V & 24V

A Complete range of regulated inverters to power 220V and 240V AC equipment via a car, lorry or boat battery. Due to their high performance (>90%) the inverters generate very little heat. The high stability of the output frequency (+/-1%) makes them equally suitable to power sensitive devices.

These inverters generate a modified sine wave, which are considerably superior to the square waves which are produced by most other inverters. Due to this superior feature they are capable of powering electrical equipment such as TV's, videos, desktop & notepad computers, microwave ovens, electrical lamps, pumps, battery chargers, etc.

Low Battery Alarm

The inverters give an audible warning signal when the battery voltage is lower than 10.5V (21V for the 24V version). The inverter automatically shuts off when the battery voltage drops below 10V (20V for the 24V version). Fuse protected input circuitry.

Order Code	Power	Voltage	Price
651.581	150W Continuous	12V	£36.39
651.578	150W Continuous	24V	£36.39
651.582	300W Continuous	12V	£50.64
651.585	300W Continuous	24V	£50.64
651.583	600W Continuous	12V	£101.59
651.593	600W Continuous	24V	£101.59
651.587	1000W Continuous	12V	£177.18
651.597	1000W Continuous	24V	£177.18
651.602	1500W Continuous	12V	£314.52
651.605	1500W Continuous	24V	£314.52
651.589	2500W Continuous	12V	£490.54
651.599	2500W Continuous	24V	£490.54

All prices are inclusive of V.A.T. Carriage £6.00 Per Order

Many uses include:- Fetes . Fairgrounds . Airshows . Picnics . Camping . Caravans . Boats . Carnivals . Field Research and . Amateur Radio field days * Powering Desktop & Notepad Computers.



B.K. ELECTRONICS



UNIT 1, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR
TEL.: +44(0)1702-527572 FAX.: +44(0)1702-420243



DELIVERY CHARGES ARE £6.00 PER ORDER. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLC,S ETC. PRICES ARE INCLUSIVE OF V.A.T. SALES COUNTER. VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX, OR EMAIL US AT SALES@BKELEC.COM ALTERNATIVELY SEND CHEQUE OR POSTAL ORDERS MADE PAYABLE TO BK ELECTRONICS.

For Full Specifications View our web site at:-
WWW.BKELEC.COM/INVERTERS.HTM

PROTEUS

The Complete Electronics Design System

Schematic Capture

PCB Layout

SPICE Simulation

Auto Placement

CPU Models

Auto Routing

Virtual System Modelling

Schematic & PCB Layout

- Powerful & flexible schematic capture.
- Auto-component placement and rip-up/retry PCB routing.
- Polygonal gridless ground planes.
- Libraries of over 8000 schematic and 1000 PCB parts.
- Bill of materials, DRC reports and much more.

Mixed Mode SPICE Circuit Simulation

- Berkeley SPICE3F5 simulator with custom extensions for true mixed mode and interactive simulation.
- 6 virtual instruments and 14 graph based analysis types.
- 6000 models including TTL, CMOS and PLD digital parts.
- Fully compatible with manufacturers' SPICE models.

Proteus VSM - Co-simulation and debugging for popular Micro-controllers

- Supports PIC, AVR, 8051, HC11 and ARM micro-controllers.
- Co-simulate target firmware with your hardware design.
- Includes interactive peripheral models for LED and LCD displays, switches, keypads, virtual terminal and much, much more.
- Provides source level debugging for popular compilers and assemblers from Crownhill, IAR, Keil, and others.

New Features in Version 6

- Drag and drop toolbars.
- Visual PCB packaging tool.
- Improved route editing.
- Point and click DRC report.
- Multiple design rules (per net).
- Multiple undo/redo.

Call Now for Upgrade Pricing

**Works with
PIC Basic Plus
from Crownhill
Associates**

labcenter

Electronics


53-55 Main Street, Grassington. BD23 5AA

Tel: 01756 753440
Fax: 01756 752857

Contact us for
Free Demo CD

www.labcenter.co.uk
info@labcenter.co.uk

INGENUITY UNLIMITED

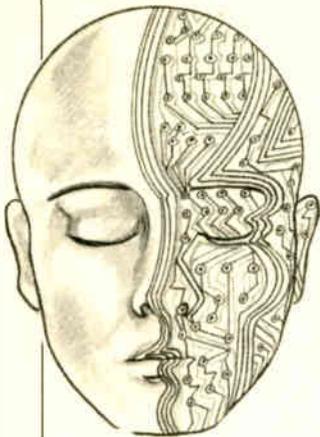

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas *must be the reader's own work* and **must not have been submitted for publication elsewhere**. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and full circuit diagram showing all relevant component values. **Please draw all circuit schematics as clearly as possible.** Send your circuit ideas to: *Ingenuity Unlimited*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown Dorset BH22 9ND. (We do not accept submissions for *IU* via E-mail.) Your ideas could earn you some cash and a prize!



WIN A PICO PC BASED OSCILLOSCOPE WORTH £586

- 100MS/s Dual Channel Storage Oscilloscope
- 50MHz Spectrum Analyser
- Multimeter • Frequency Meter
- Signal Generator

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC based oscilloscope could be yours. Every 12 months, Pico Technology will be awarding an ADC200-100 digital storage oscilloscope for the best *IU* submission. In addition, a DrDAQ Data Logger/Scope worth £69 will be presented to the runner up.

Fully Automatic Egg Timer – Just White

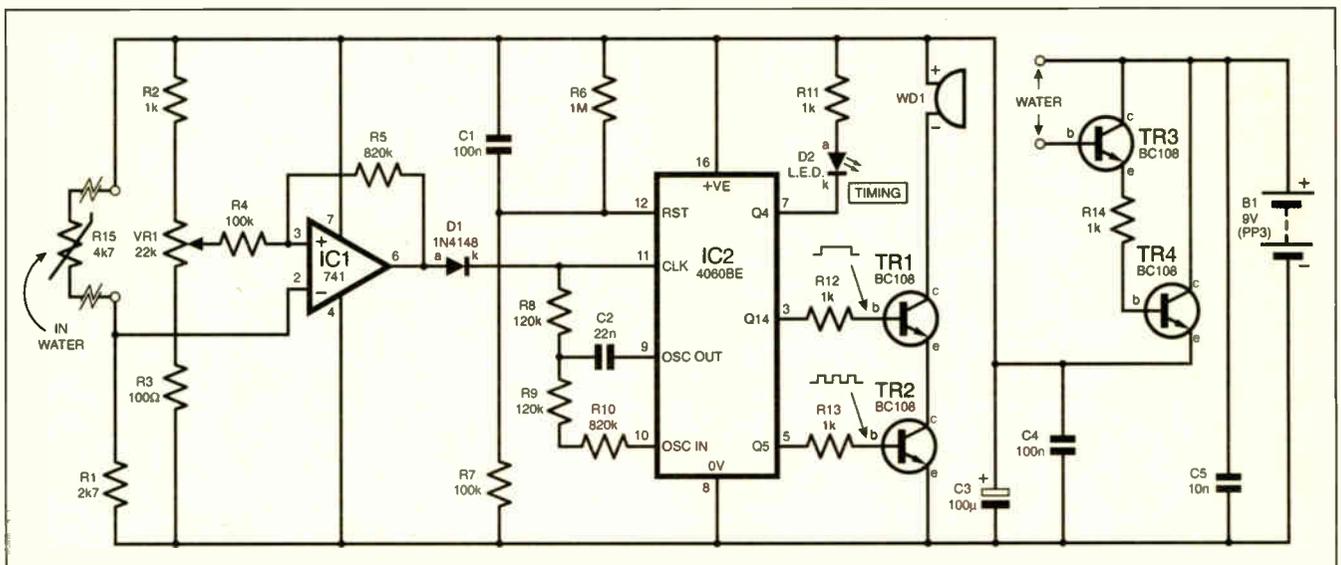


Fig. 1. Complete circuit diagram for the Fully Automatic Egg Timer.

ONE of the most tasty and natural sources of protein is without doubt the humble boiled egg, however desirable results can often be difficult to attain (i.e. solid egg white and liquid yolk) without prior experimentation. Egg connoisseurs everywhere will appreciate the inexpensive circuit of Fig.1, which produces almost perfect results with a wide variety of pan sizes, water volumes and heat rates.

Egg Thermidor

Thermistor R15 is placed in the pan of water and forms a bridge arrangement with resistors R1, R2 and R3 and potentiometer VR1. A low value of 4k7 has deliberately been chosen for R15, so that in the event of water breaching the seal around its leads, the resistance of the water (approx. 50k) in parallel with it will have minimal overall effect.

Op.amp IC1 operates in comparator mode, with resistors R4 and R5 providing hysteresis in order to ensure a clean switching action. Potentiometer VR1 is set so that when the

water reaches 70°C, the point at which the eggs actually begin to cook, IC1 is triggered and a logic 1 appears at its output.

Consequently, pin 11 of a 4060 ripple counter IC2 is now at logic 1 and a count-down of four minutes, forty seconds (\pm about 7 seconds) commences, a period determined by resistors R8, R9, R10 and polystyrene close tolerance capacitor C2. Substituted components cannot be used in place of C2, as this would significantly affect accuracy.

Capacitor C1 in series with resistor R7 applies a power-on reset to IC2, so that it begins operation in a predictable state when timing commences. Resistor R6 discharges C1 when the device is switched off.

Light Work

The l.e.d. D2 is illuminated upon power-up via current limiting resistor R11, as pin 7 of IC2 at this point is at logic 0. Once the timer has been activated, pin 7 begins to oscillate between logic 0 and 1 at a low frequency of 1Hz to 2Hz, resulting in D2 flashing instead.

After four minutes and forty seconds, pin 3 of IC2 switches from logic 0 to 1 and turns on transistor TR1 via current limiting resistor R12, which activates the buzzer WD1. As TR2 is constantly pulsed by pin 5 at approximately 2Hz, the buzzer is given a more noticeable "beep, beep..." sound, rather than a constant tone. Capacitors C3 to C5 are noise decoupling components that help stabilize the power supply.

Transistors TR3 and TR4 and resistor R14 form a water-activated switch that automatically applies power to the circuit when the sensor prods are immersed in the water; these are located on a probe containing the thermistor. The circuit should be housed in a metal box and clipped onto the end of the pan handle so that heat and steam cannot come into contact with the components.

It should be noted that once the alarm has sounded, the eggs must be cut open immediately, so that they cannot continue to cook from the heat retained in them.

M. A. Jones, Harrogate, N. Yorkshire

Heart Rate Monitor – See The Beat

THE simple but very reliable monitor shown in Fig.2 will be an asset to those who have difficulty finding their pulse in their wrist. It is also useful for checking the pulse rate immediately after exercise, which should be well above the normal rate of 60-80 beats per minute if any benefit from the exercise is to be derived.

Light Finger

The device depends for its operation on variations in light intensity. When a finger is placed on a light dependent resistor R2, the l.d.r. detects the minute changes in light level caused by variations in blood flow as the heart pumps. These light changes are translated into minute voltage fluctuations that are subsequently amplified through a two-stage amplifier, a non-inverting op.amp (IC1a) and an inverting op.amp (IC1b), by a gain of approximately 800 as determined by resistors R5, R7 and R10.

At the output (pin 7 of IC1b), each heart-beat is reflected in the rhythmical swing of a meter needle across the dial of a milliammeter (ME1) or other suitable panel meter. No special lighting is needed as the l.d.r. is able to "see" through a finger tip in normal daylight.

The gain of the first op.amp is fed into the second and the overall gain is sufficient to obtain a healthy swing of the meter needle. Almost any moving coil meter can be pressed into service because we are not concerned with voltage or current measurement, only the needle deflections across the dial.

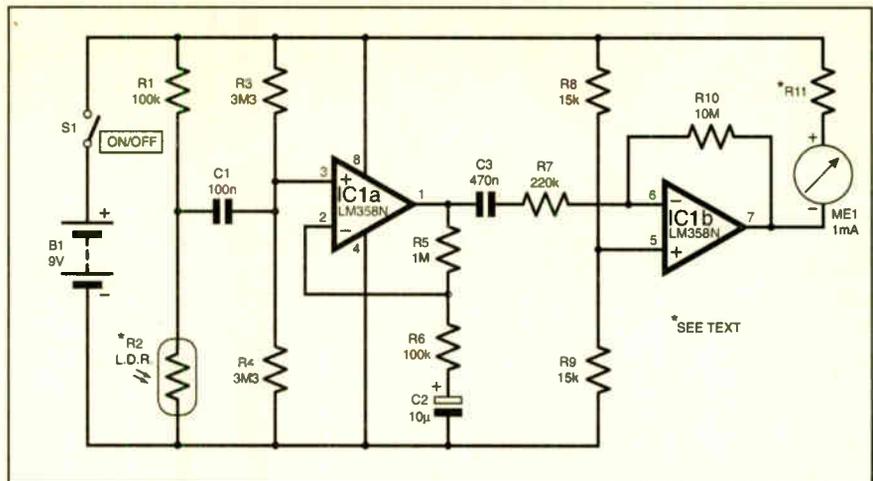


Fig.2. Heart Rate Monitor circuit diagram.

However, be sure to fit a series limiting resistor R11 to suit the meter and prevent damage.

A miniature button-type l.d.r. is preferred to the bulkier ORP12 so that the finger can completely cover the sensor surface and prevent stray lighting from reaching it. Two discrete 741 op.amps could be used in place of the LM358N if more readily available.

Although not shown here, the prototype also housed a 30-second timer, using a 555 with an l.e.d. indicator. When the timer is initiated, the needle movements are counted during the 30 second period, then doubled to obtain pulses per minute. The circuit could

also be adapted as a front-end to more advanced monitoring systems.

In use, after the unit is switched on, allow several seconds for the meter needle to stabilise somewhere about mid-scale. Place the fleshy part of the middle finger tip on the l.d.r. and rest the hand comfortably while keeping it still, then monitor the meter needle movement. If the meter needle responds by only a small amount, it is probably because your hand is excessively cold and the circulation is sluggish.

Tony Lee,
Old Reynella, Australia

Microwatt L.E.D. Flasher – Relaxing Light

THE circuit of Fig.3 is a complementary relaxation oscillator that has been utilised to form a low power l.e.d. flasher. The heart of the circuit is the 5.1V 0.5W Zener diode D2, the absence of which reduces the operating efficiency of the circuit. Current from the anode of the Zener diode provides base bias for transistor TR2.

In order to reduce the current requirement of TR2 to a minimum, a high gain npn transistor (BC549C) has been selected. The resistor R1 is the energy saver which acts in conjunction with capacitor C1, a reservoir for the whole circuit. Transistor TR1 (BC559) is a pnp type that provides current for the flash.

To get a flash of fairly good intensity C1 has to be kept fully charged and the action is obtained by keeping the time constant of R1/C1 smaller than the time constant of the timing circuit around TR2, which consists of components R3 to R5 and C2. The capacitors should ideally be low leakage tantalum types.

Using component values as per the circuit diagram, the flash rate obtained was approximately 40 per minute with fairly good intensity using a 9V battery. The actual current consumption at the precise time of flash is well below 0.4mA. The circuit is tolerant of voltages ranging from 6V to 12V though a frequency variation is noticeable when supply voltage varies.

Unlike many other flasher circuits, this one has a very short flash duration. The instantaneous release of energy from the 100µF capacitor (C1) has to be fully utilised to illuminate the l.e.d., and a 3mm clear red l.e.d. was chosen as a satisfactory compromise.

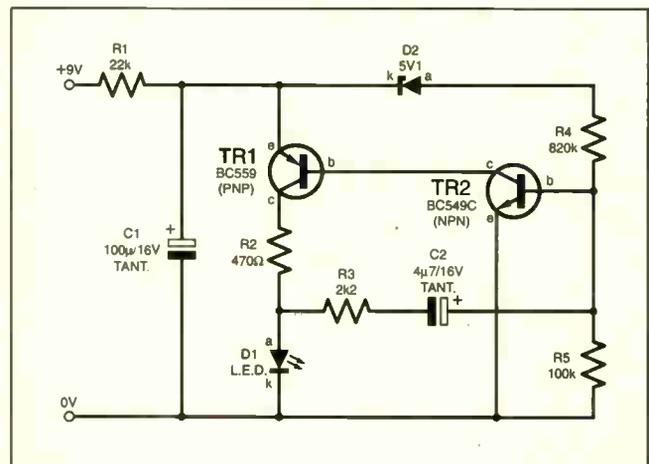


Fig.3. Circuit diagram for a Microwatt L.E.D. Flasher.

Experimenters might find various other applications due to the very economical power consumption, e.g. by replacing R1 with a 2k2 resistor and addition of a small piezo buzzer in place of the l.e.d. or in parallel with it, thus converting it into a low current bleeper.

K.N.S. Nair,
Selangor, Malaysia.

Signing Off . . .

Sadly this is the last *Ingenuity Unlimited* column that I will be hosting, but don't worry, IU will continue. It has been my pleasure to help bring you almost 300 readers' circuits since the original *Practical Electronics* column was relaunched in *EPE* nearly ten years ago. Unfortunately, pressure of work has gained the upper hand, and so I will be handing over to the Editorial staff at *EPE* HQ who will continue to publish a selection of your circuit ideas

with valuable prizes donated by Pico Technology for the best.

I'll still be working hard as usual over at *Circuit Surgery* and *Net Work* – the Internet column, and working on a number of other projects as well. I would like to express my gratitude to all those readers, correspondents and friends around the world who have sent their good wishes and offered me their encouragement over the years. It is much appreciated, and it has been great fun. Alan Winstanley.

**WHY NOT SEND
US YOUR
CIRCUIT IDEA?**


**Earn some extra
cash and possibly
a prize!**



Constructional Project

DOOR CHIME

BART TREPAK

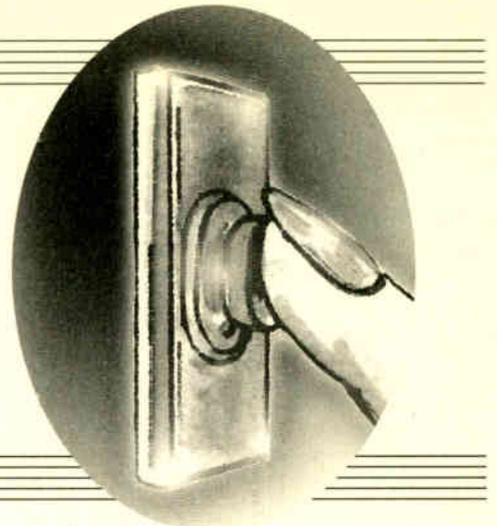

Add a touch of nostalgia to your front door and have a real "ding-a-ling" with this low-cost unit.

In the good old days, when computers were huge monsters that lived on the air conditioned top floors of banks and insurance company headquarters and PICs were used with shovels on building sites to dig holes, life was so much simpler.

Nobody in their right mind would want to use either of these to announce the arrival of a visitor to their door and instead a far simpler solution was found – the door chime, which had the added advantage of not playing the Wedding March for twenty minutes each time a double glazing salesman came to call.

Luckily, these did not exist either and only the familiar "ding-dong" sound of the lady selling cosmetics disturbed the peace and tranquillity of the family as they huddled around their warm valve wireless set listening to the Home Service instead of arguing about which of the hundred and fifty odd channels to watch or record on their top of the range digital satellite TV/DVD recorder . . . Ah, those were the days . . . now even nostalgia isn't what it used to be!

To try to return to those simpler times, the author decided to build a door chime that would recreate the sound of the original with electronics (well some things have to move on) but without recourse to microcontrollers, ROMs or hard to obtain special i.c.s.

Mechanical door chimes produced their characteristic sound by alternately striking two steel rods or plates, once as the door switch is pushed to provide the "Ding" and the other as it is released to sound the "Dong". The main characteristics of these sounds are that they are pure tones and, in common with all instruments which are struck, the sound is loud at first and then decays. In other words two decaying sine waves of different frequencies must be generated, one when the switch is pressed and one when it is released.

SINE WAVE OSCILLATORS

At first glance this seems simple enough to do and there are many circuits for producing sine waves. Basically, an inverting amplifier with its output connected to a feedback network which at a certain frequency produces a phase change of 180 degrees is all that is required.

When this is coupled to the input of the amplifier which itself exhibits a 180 degree phase change between its input and output, the total phase change becomes 360 degrees (i.e. in phase). This means that the circuit will oscillate but only if the gain is high enough to replace the inevitable losses in the feedback circuit.

If the gain is too high, the amplitude of the output waveform will grow until it limits or clips on the supply rails producing distortion or a square wave (which does not sound so pleasing). If it is too low the circuit may not start to oscillate at

all. Many sine wave oscillators therefore employ some form of circuit to control the gain of the amplifier and keep it stable.

PHASE SHIFT

The circuit chosen was a phase shift oscillator where the feedback is provided by a three-stage high-pass network with each stage providing a phase shift of 60 degrees. Here oscillation occurs at the frequency at which the phase shift through the network is 180 degrees and this depends on the values of the capacitors and resistors used.

Normally they will have the same value, although making one of the resistors variable allows the frequency to be adjusted within limits. The frequency of oscillation is given by the formula: $f = 1/2\sqrt{6RC}$. The gain required to sustain oscillation is easily supplied by a simple transistor amplifier.


DELAYED RESPONSE

To produce a decaying output rather than one which persists for as long as the battery is connected appeared much more difficult. Some form of voltage controlled amplifier or attenuator was considered but this was rejected as being too complicated – we are after all only trying to replace two metal rods.

Various other schemes were tried including varying the base drive to the transistor but these not only varied the amplitude of the signal but also its frequency (producing all sorts of sounds none of which were even vaguely reminiscent of a door chime).

Also, the amplitude varied in the wrong way hardly changing at first and then changing rapidly rather than smoothly as required. In the end, the simple expedient of powering the oscillator through a (large) capacitor proved to be the most successful.

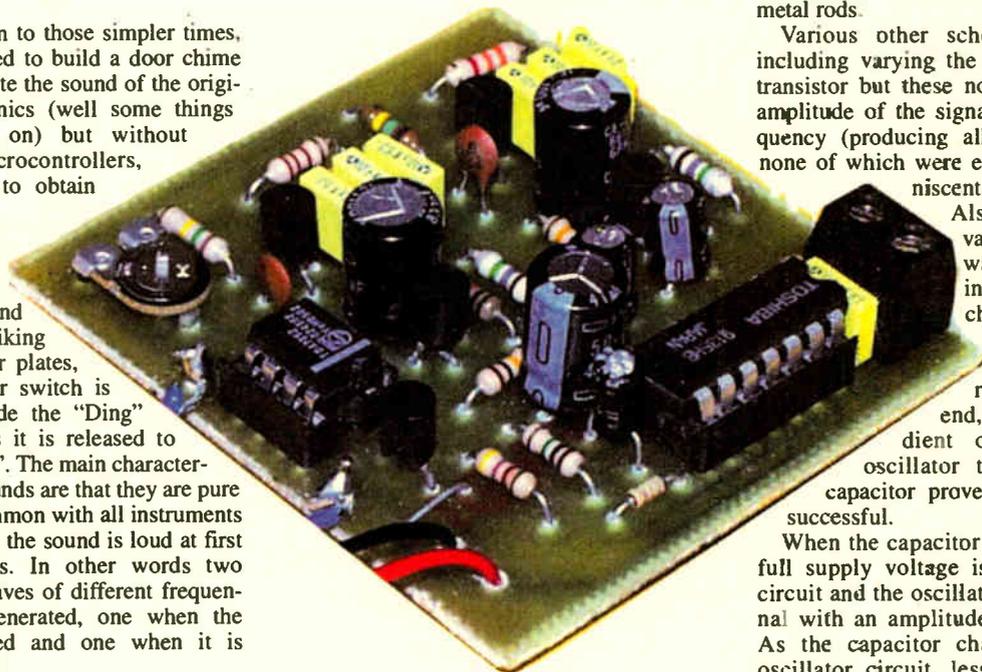When the capacitor is discharged, the full supply voltage is available to the circuit and the oscillator produces a signal with an amplitude of several volts. As the capacitor charges up via the oscillator circuit, less and less of the



supply voltage is available across the oscillator itself and so its amplitude falls until eventually the signal becomes inaudible.

The circuit continues to oscillate without clipping or suddenly cutting out at a certain minimum voltage level thus producing a smoothly reducing signal. It also has the great advantage in a door chime circuit, which spends most of its time in the stand-by state, in reducing the current drain to zero once the capacitor is fully charged. In this state it draws no current and is ready for the next caller requiring only the capacitor to be discharged to initiate another cycle.

A SWITCH IN TIME

Since two tones must be generated, two oscillators are required together with their associated capacitors. In theory, the capacitor could be discharged by the door switch but since the two tones do not sound simultaneously, the capacitors need to be discharged sequentially – the first when the switch is closed and the second when it opens. As well as this, both contacts would have to remain open during the stand-by condition so that neither capacitor was shorted out and this would require some pretty fancy switching.

Nowadays, of course, you can have any type of doorbell switch you like on your door – as long as it is a simple push-to-make type. Double-pole or changeover types suitable for mounting on your front door are not readily available (if at all) and

you would probably not want to change your existing one anyway so that a further circuit must be added to switch on the oscillators in the correct sequence under the control of a single contact.

CIRCUIT DETAILS

The full circuit diagram of the Door Chime is shown in Fig.1 and consists of two oscillators built around TR1 and TR3, the circuitry for switching them on and an audio amplifier, IC2, to drive the speaker.

The switching stage is centred on IC1, a quad CMOS NAND gate and all of the gates are connected as logic inverters. When the doorbell switch S1 is pressed, the input of the first inverter, IC1a, goes high causing its output to go low and the output of the second inverter, IC1b, to go high.

Both of these inverters drive *pnp* transistors, TR2 and TR4, via capacitors C5 and C10, so that when the output of an inverter goes low, the associated transistor is switched on, briefly discharging its output capacitor (C6/C11 as appropriate) and switching on its oscillator. When the output of the inverter goes high however, it has no effect on the transistor which remains off.

Thus when the door switch is pressed, TR2 turns on briefly and when it is released, TR4 is turned on so that the two oscillators are switched on sequentially. Note that if the switch is held depressed, then only the first (Ding) oscillator TR1 is switched on and the second (or Dong) oscillator TR3 will only sound when the switch is released.

SWITCH-OFF

The two oscillators switch off automatically by themselves (when the voltage on the negative plates of capacitors C6 and C11 falls) but the audio amplifier, IC2, must also be switched off in order to reduce the current drain of the circuit. This is done by wiring the remaining two gates, IC1c and IC1d, as a monostable.

When the input of IC1c goes low (which happens when the switch is pressed) its output will go high and capacitor C14 will charge quickly via diode D1. This will cause the output of IC1d to go low switching on transistor TR5 and the supply to the audio amplifier IC2. Note that the transistor will remain on for as long as the door switch is held pressed.

When the switch is released, C14 discharges via resistor R15 until eventually the gate output goes low, switching off the transistor and the supply to the amplifier. The values of C14 and R15 are chosen to ensure that this will happen only after the second oscillator has ceased to function.

AUDIO AMPLIFIER

The audio amplifier (IC2) chosen is the TDA7052 power amp i.c. which, in fact, contains two amplifiers which drive loudspeaker LS1 in a bridge configuration. This gives an output which is typically four times greater than that which could be achieved with a single-ended output and ensures a loud signal even with a relatively low supply voltage.

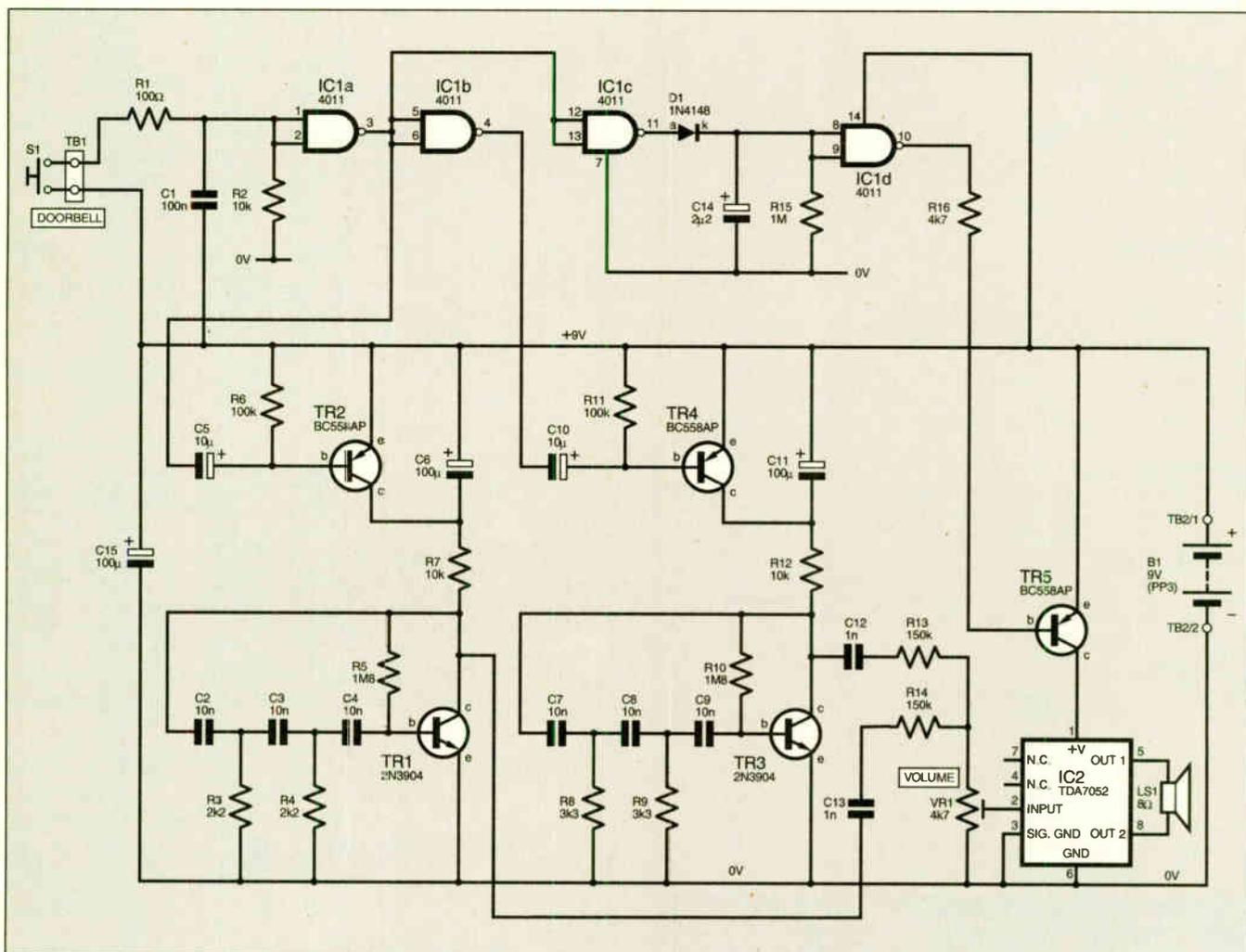


Fig.1. Complete circuit diagram for the Door Chime. S1 is the doorbell pushswitch.

As there is no d.c. voltage across the loudspeaker in amplifiers using this configuration, the usual large value coupling capacitor is not required. Apart from a supply decoupling capacitor (C15), the only other component needed is a Volume control which in this case is preset type (VR1).

The outputs of the oscillators are fed to the amplifier input (IC2 pin 2) via capacitors C12 and C13 and resistors R13 and R14 which attenuate and mix the two oscillator outputs across level-setting preset VR1.

As mentioned, to reduce the current drain, the supply to the amplifier is also switched off when the chimes stop. The absence of a speaker coupling capacitor is therefore an advantage as there are no audible clicks when the supply is switched on and off.

The circuit is powered by a 9 volt battery and the current drain in stand-by, which with this sort of application is most of the time, is virtually zero so that battery life will be close to the shelf life.

CONSTRUCTION

Initially it was intended to build the circuit on stripboard but as the number of

components grew it was decided to design a printed circuit board. This will simplify construction quite considerably.

The final component layout, full-size copper foil master and wiring details are shown in Fig.2. This board is available from the *EPE PCB Service*, code 390.

All of the components except for the loudspeaker and battery (and, of course, the doorbell switch) are mounted on the board and these are connected to the p.c.b. via flying leads, either soldered directly to the board or through terminal blocks. The components are all pretty standard and no special precautions need be taken other than to make sure all electrolytic capacitors, transistors and other polarity sensitive components are mounted the correct way around.

Note also that transistors TR1 and TR3 are *nnp* types while TR2, TR4 and TR5 are *pnp*. The pinouts of the *nnp* types specified are slightly unusual and so if you intend to use substitute devices, such as BC548 or BC182, you will need to check their pinouts first. Being a CMOS device, IC2 should be handled with care and mounted in a 14-pin socket. Although IC1 is not sensitive to static, a socket was also used for this device.

The circuit is powered by a 9V PP3 battery and

although the layout shows a terminal block, TB2, to connect this, a simple PP3 battery connector and its leads may be used and soldered directly in its place. Note that there is also a wire link adjacent to this terminal block which can be made from a discarded component lead.

The loudspeaker LS1 can be a miniature one and this should be soldered to the board at the position shown using flying leads. It is a good idea to use solder pins here (and for the battery connector if a terminal block is not used) to avoid damaging the p.c.b. tracks as wires soldered directly to the board often break at this point leading to repeated soldering operations.

TESTING

Provided the circuit layout has been carefully followed, the unit should work as soon as a speaker and battery are connected. The Volume control preset VR1 should be adjusted to give a pleasing sound without distortion which can occur at high volumes if the output of the amplifier clips on the supply rails.

Although the component values given should produce an acceptable door chime sound, this can be modified according to personal taste. As mentioned, the basic oscillator frequencies can be altered by varying one of the resistors in the ladder network.

COMPONENTS

Resistors

R1	100Ω
R2, R7, R12	10k (3 off)
R3, R4	2k2 (2 off)
R5, R10	1M8 (2 off)
R6, R11	100k (2 off)
R8, R9	3k3 (2 off)
R13, R14	150k (2 off)
R15	1M
R16	4k7

All 0.25W 5% carbon film

Potentiometer

VR1	4k7 carbon preset, horizontal
-----	-------------------------------

Capacitors

C1	100n polyester
C2 to C4, C7 to C9	10n polyester (6 off)
C5, C10	10μ radial elect. 16V (2 off)
C6, C11, C15	100μ radial elect. 16V (3 off)
C12, C13	1n disc ceramic (2 off)
C14	2μ2 radial elect. 16V

Semiconductors

D1	1N4148 signal diode
TR1, TR3	2N3904 <i>nnp</i> low power transistor (2 off)
TR2, TR4, TR5	BC558 <i>pnp</i> low power transistor (3 off)
IC1	4011 CMOS quad 2-input NAND gate
IC2	TDA7052 power amp.

Miscellaneous

LS1	8 ohm miniature loudspeaker
B1	9V battery (PP3), with clips and leads
TB1, TB2	2-way, p.c.b. mounting, screw terminal block (2 off)

Printed circuit board available from the *EPE PCB Service*, code 390; plastic case, size and type to choice; doorbell switch, push-to-make (see text); 8-pin d.i.l. socket; 14-pin d.i.l. socket; connecting wire; solder pins; solder etc.

Approx. Cost
Guidance Only

£12

excl. batts & speaker

See
**SHOP
TALK**
page

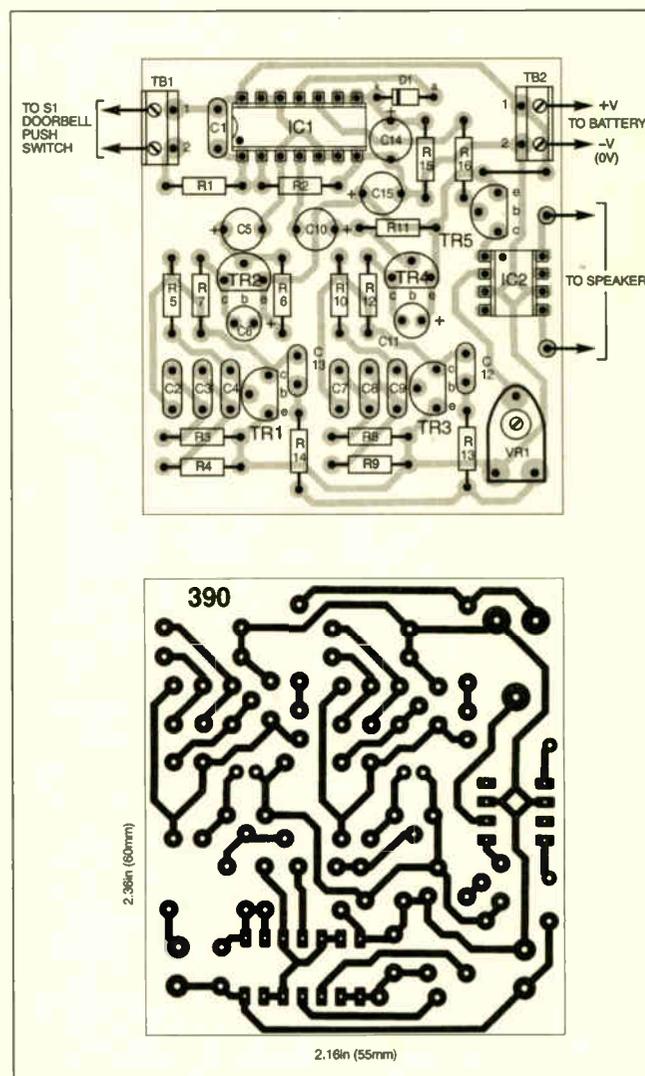


Fig.2. Printed circuit board component layout, wiring details and full-size copper foil master for the Door Chime.

This is perhaps done most easily by substituting a preset potentiometer in place of the resistors R4 and/or R9 and adjusting it to get the desired effect. Note that as well as altering the frequency, it will also change the amplitude of the note which can cause distortion of the wave shape by over driving the output amplifier but this can usually be corrected by adjusting the volume control preset.


It can also produce less than pleasing results especially when mixed with the output of the other oscillator. If a radically different frequency is required, it is probably better to change the values of the capacitors.

DECAY TIME

The other characteristic which can be altered is the decay time and this is controlled by the current drain of the oscillator transistors (which is probably best left as it is) and the values of the series capacitors C6 and C11. These may be increased to 470µF or beyond or indeed decreased depending on taste, although both should have the same value to preserve the "ding-dong" effect.

In this case, the value of C14 would also need to be increased to ensure that the amplifier remains powered until the tone has died away. The values of C5 and C10 may also need to be increased to ensure that the capacitors are fully discharged at the start of each tone.

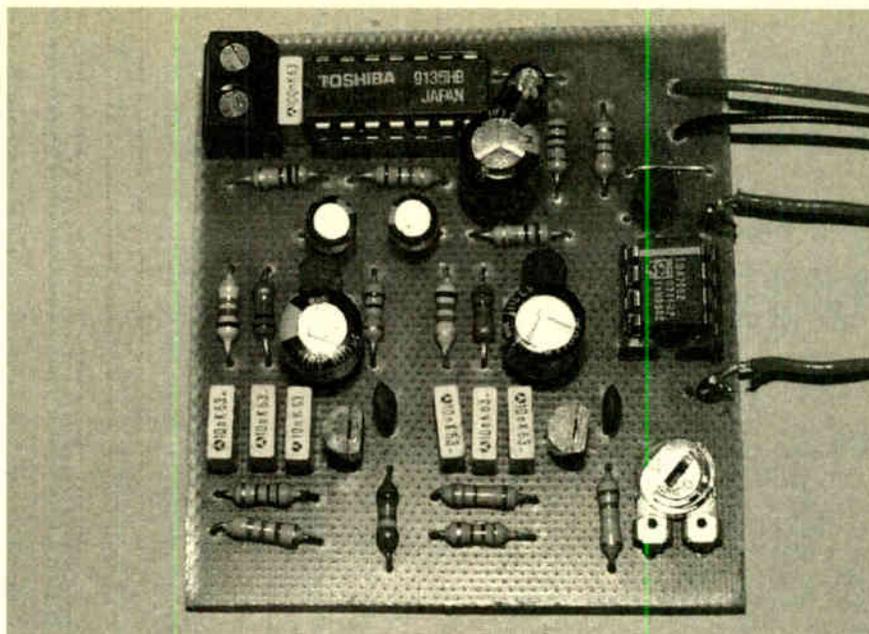If the first tone is still sounding loudly when the second one commences, the two frequencies will beat together resulting in harmonics being generated and this can



lead to the production of some more or less pleasant (or interesting) sounds.

Unlike custom i.c.s where the timing and the frequencies generated are all derived from one master clock oscillator, here each note can be adjusted to produce any sound of any duration required. By swapping the values of R4 and R9 for example, a "dong-ding" effect can be produced.

There is also no reason why a further oscillator could not be added to provide a

3-note chime or indeed a larger number to recreate the Westminster chimes. Although, in these cases the oscillator switching signals would need to be derived from a counter such as the CMOS 4017 with the pushswitch providing only the start signal.

While these modifications may be suitable as a door chime to produce just the sound you were looking for, they will do little to recreate those "good old days"! □

ELECTRICAL ENGINEER

Battery Powered Consumer Products • Attractive Package • Hull

**RECKITT
BENCKISER**

www.reckittbenckiser.com

Reckitt Benckiser is the force behind many of the world's favourite healthcare brands. Names like Vanish, Finish and Air Wick – each number 1 or 2 in its sector. Central to everything we do is a uniquely confident, entrepreneurial, "can-do" culture. A passionate commitment to competing hard and ultimately, to winning.

The organisation:

We have operations in 60 countries, sales in 180 and sales revenues in excess of £3 billion. Due to the introduction of new and exciting product ranges, we are now looking for a highly passionate and talented Electrical Engineer with extensive experience of the battery powered consumer products industries.

The role:

- Provide vital electronics design input to NPD projects, producing simple household consumer products which utilise mains and battery power.
- Serve as a technical expert on important product development programmes.
- Conduct benchmarking exercises, identifying sourcing opportunities, cost reduction possibilities and product enhancements.
- Support the full scale production plans which will include training operations staff and ensuring legislative requirements are also met.

The requirements:

- Electrical or Electronics Engineer qualified to Degree level.
- Strong design experience within consumer products industries with battery powered technology.
- Passionate about electrical design and challenges in the consumer products industry.
- Able to identify and manage relationships with third party sources.
- Ability to work within challenging schedules and to launch plans in a fast paced environment.

Interested candidates should apply to our retained consultant, Nimo Saeed at Astbury Jones, enclosing a full CV with covering letter. Please quote NS/EE1 on all correspondence. All direct applications will be forwarded to Astbury Jones.



Astbury Jones Executive Search, 26 Dover Street, Mayfair, London W1S 4LY.
Tel: +44 (0) 20 7629 6116. Fax: +44 (0) 20 7763 7101. E-mail: nimos@astburyjones.com

New Technology Update

*Antennae with a high dielectric constant are less prone to proximity effects in mobile phones.
Ian Poole reports.*

MENTION an antenna to anyone and it conjures up an image of either a television Yagi antenna array on the chimneystack of a house, or a view of an amateur radio wire antenna.

In recent years it has been possible to implement far better antenna designs as a result of a vast array of simulation software that is available. It is possible to predict performance in terms of gain, direction pattern and many other parameters before any metal is put together.

These simulations can also take account of nearby objects that may affect the performance. As a result, major improvements have been made in the way antennas are designed, enabling far more efficient designs to be made more quickly. The need to perform many long tests on an antenna test site has been vastly reduced as the designs can be made almost perfectly first time.

A considerable amount of work has been put into the development methods for conventional conducting antennas. However, there has been plenty of development directed towards new ideas for antennas. With the increasing requirements for wireless links, antennas need to be made smaller, and to be incorporated into equipment more easily.

Proximity Effects

One of the major restrictions with antennas that use existing techniques is that nearby objects have a considerable effect on the performance. This means that for antennas such as those used in mobile phones, the proximity of other parts of the phone need to be taken into consideration. Naturally hand and body capacitance from the user has a major effect on the antenna and this will vary quite considerably dependent upon a number of factors, including the way the user is holding the phone, the electrical characteristics of his or her body and so forth.

Antennas on mobile phones themselves may only be 45% efficient under ideal conditions. However when the phone is held close to the head this can drop to as low as just a few percent. This means that the transmitter section of the phone needs to generate more power to enable reliable communication to be maintained with the base station, and this results in a much greater level of drain on the battery.

High Dielectric Antennae

To address these problems a Cambridge (UK) based company named Antenova has developed a new type of antenna called a high dielectric antenna (HDA). This type of antenna uses material with a high

dielectric constant as the basis of the radiating element rather than a conducting element as used in a conventional antenna.

The idea has been known about for many years. The first ideas were postulated in the 1930s. However, it has not been possible to develop them until recently. The electric and magnetic fields are contained within the dielectric and as a result it was not possible to measure them. Some early experimental models were built to demonstrate the principal in the laboratory, but their bandwidth was small, and they were not repeatable because of a lack of understanding of the electric and magnetic modes being excited within the dielectric.

During the 1990s development of simulation software took place and as a result it was possible to gain a much clearer picture of what was happening within the dielectric. It became possible to plot the electric and magnetic fields and from this an understanding of the modes in which the dielectric was being excited could be gained.

Physical Aspects

The antennas may be constructed using a small cylinder of dielectric material with a disc attached. A small metal or conducting probe is inserted into the material to act as a launcher and this is fed with the RF signal. If the relationship between the radio frequency signal and the dimensions of the dielectric are correct then a displacement current standing wave pattern will be set up. Using Maxwell's equations it has been predicted that this will radiate, and this indeed is what actually happens.

These dielectric antennas are physically smaller than their conducting counterparts. Under some circumstances they may be only a tenth the size and this can be a distinct advantage. Many of today's wireless devices are small, requiring low profile antennas and the new HDAs are ideal candidates for these applications because they can be accommodated more easily within the electronics.

A further advantage is that they are less affected by nearby objects and this too enables them to be incorporated more easily onto a circuit card or other item. The fields are almost totally contained within the dielectric of the antenna itself, whereas the fields from a conventional antenna extend out by a wavelength and more, with the result that any objects within this range have a major effect on performance.

As a result of the relative immunity to nearby objects it is possible to have an HDA design where two separate antennas are placed very close to one another without any noticeable effect on performance.

Bluetooth

The new technology is ideal for many of the emerging wireless communications systems. Bluetooth, WiFi, and the like, all need small antennas that can be incorporated into a small electronics card. They also lend themselves well to many cellular telecomm applications, although the technology is better suited to frequencies above around 900MHz.

Whilst they can be used for bands within the 850MHz to 900MHz region, the higher frequency bands around 1800MHz and 1900MHz are far more applicable, along with many of the new 3G allocations that are slightly higher in frequency.

Antenova have built relationships with cellphone manufacturers and it is expected the new technology will be used extensively in this arena before long.

Currently much of the development work that is under way is focussed on frequencies around 5-8GHz. This is one of the so-called "unlicensed" bands that are starting to be used by some of the wireless LAN cards.

At the moment the 2-4GHz band is the most popular, but with the rapidly growing requirement for even faster data rates, people are migrating to 5-8GHz where the levels of interference are less and the bandwidth is greater, both elements enabling higher data rates to be achieved.

Diversity Reception

The fact that two antennas can operate close to one another provides the opportunity to provide what is called diversity reception. This form of reception is required because signals often reach a receiver via several paths. When they combine at the receiving antenna they may combine constructively to provide a better signal or they may tend to cancel one another out.

The interference patterns set up by the signals arriving via several paths mean that even a relatively short change in distance can make a large difference to the signal. As a result, the problem can be overcome by having two separate receiver front ends and two antennas relatively close to one another. The best signal is then used by the overall receiver system. As the HDAs can be operated close to one another they are ideal for using for diversity reception systems.

Further information can be gained from the Antenova website at www.antenova.com and more information about new technology can be found at www.radio-electronics.com.

New Product

Atlas LCR Passive Component Analyser (Model LCR40)

"No other LCR is as easy as this!"

Just clip on the test leads and press test. The Atlas LCR will automatically identify the type of component, apply the appropriate test level and frequency, display the component's value and more!

Probes are detachable too, so you can use the optional SMT tweezers for your tiny unmarked passives - fantastic.

Inductance range: 1µH to 10H
 Capacitance range: 1pF to 10,000µF
 Resistance range: 1Ω to 2MΩ
 Basic accuracy: 1%
 Test signals: 1V, 3mA max

£79

fully inclusive UK price



Lots of accessories available soon!

atlas

semiconductor analyser

Check and identify your semi's

- Automatic component identification
- Pinout identification
- Transistor gain measurement
- MOSFET gate threshold measurement
- PN junction characteristics measurement
- Shorted Junction identification
- Transistor leakage measurement
- Just connect the part anyway round and press the button!
- Auto power on/off

£60

fully inclusive UK price



NOW MEASURES TRANSISTOR LEAKAGE!

enclosure colours may vary

Supports:

- Bipolar transistors,
- Darlington transistors,
- Diode protected transistors,
- Resistor shunted transistors,
- Enhancement mode MOSFETs,
- Depletion mode MOSFETs,
- Junction FETs,
- Low power triacs and thyristors,
- Diodes and diode networks,
- LEDs (+bicolours)

NPN bipolar Darlington
 Diode protection between C-E
 Resistor shunt between B-E
 Current gain Hfe=125
 Enhancement mode N-Ch MOSFET
 Gate Threshold Vgs=3.7
 RED COL BLUE COL
 Volt 8.77V
 c=8



Visit www.peakelec.co.uk to download the data sheets, user guides and copies of independent reviews. You can pay using a cheque, postal order, credit or debit card and even pay securely online. Please contact us for your volume requirements.

Also available from: (prices vary)



PEAK
 electronic design ltd

Atlas House, Kiln Lane
 Harpur Ind. Est., Buxton
 Derbyshire, SK17 9JL, UK


Tel. 01298 70012

www.peakelec.co.uk
sales@peakelec.co.uk

Fax. 01298 70046



CIRCUIT SURGERY

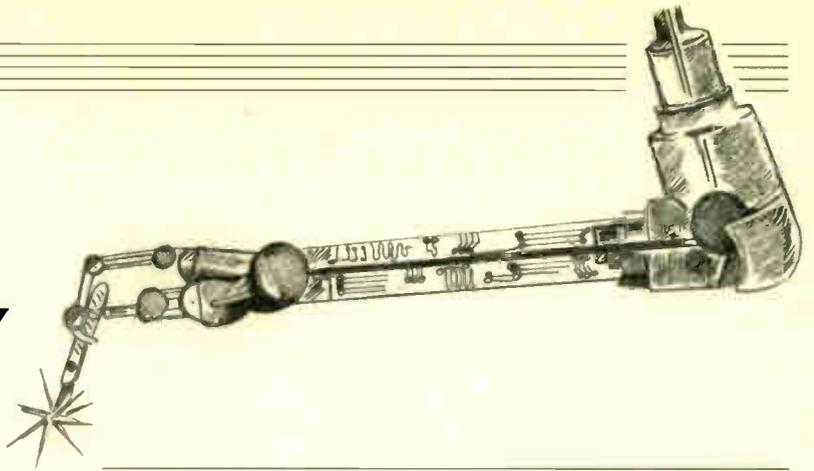

**ALAN WINSTANLEY
and IAN BELL**

This month, we unravel a subtle timing problem on a reader's digital circuit. We also offer more circuit diagram tips for beginners, illustrated with a selection of schematic symbols of common components.

Perfect Timing

Dr. G. L. Manning of Edgware wrote to describe his interesting experiences of timing problems with digital counters, about which we can make some enlightening observations. Some excerpts of his letter follow:

In the circuit shown in Fig.1 (which is part of a larger circuit), the required count length is from 0 through to 5 (0101 binary). The various binary values are decoded to an active low 1-of-n code by IC4. The NAND gate detects the 6 condition and resets the counter by a low signal applied to CLR.

The small time the counter spends in the 6 state is not a problem in this application, however, it is this resetting that goes wrong. It worked as required on a bread-board with its stray capacitance but only worked on a p.c.b. once an extra delaying capacitance was added in the form of C14.

On my unmodified p.c.b. version the count sequence was 0 1 2 3 0... (binary 0000 0001 0010 0011 0000). I suspect that the synchronous flip-flops in IC2 take slightly different times to settle, so after 0011 the next output could be 0111 for just long enough to trigger a reset, prior to settling at the steady state of 0100. Hence, the capacitor C14 slows down the transition of the bit C so that the intermediate combination does not occur.

Further investigation involved replacing IC2 with a ripple (asynchronous) counter which has the advantage that bit C is not clocked (low-to-high transition) until preceding bit B settles to zero (its high-to-low transition). Perfect function is observed without the need for C14.

Finally Dr. Manning adds a couple of questions:

Directly clearing the synchronous counter directly from output Y6 (omitting IC3A and C14) also works correctly. Is there some subtle timing/propagation delay in IC4 which means that it does not respond to the intermediate output value?

A final observation is that all chips tested behaved the same, but all were from the

same manufacturer. Are such critical timing errors manufacturer-dependent? Thanks from Godfrey Manning, G4GLM

Let's deal with the questions first. The response of digital circuits to (relatively) short duration pulses (glitches) is rather like the inertia of objects when they are pushed. Objects may or may not move when given a (relatively) gentle push (due to friction), and logic circuits may or may not respond when a glitch is applied to one of their inputs.

The "inertia" is different for different circuits, so it is quite natural to find that the NAND gate responds to the short duration intermediate state from the counter, whereas the decoder does not. This behaviour can be described as a subtle timing issue, but it is not an error. There is, however, another possible explanation for this behaviour, which we discuss later.

The response to glitches does not just vary between different circuit "designs" (e.g. NAND gate and decoder); it also varies between individual instances of circuits or gates (e.g. two individual decoder chips). Manufacturer's datasheets usually specify the typical delay and longest delay for the response of the logic chip. If a chip is slower than the longest delay specified, then it has not met the specification and you may have a right to replacement; however, there is usually no *minimum* delay specified so a particularly fast device is not usually regarded as being out of specification.

Therefore, two manufacturers could produce nominally the same i.c. type

(74LS161 or whatever) and one manufacturer's devices could well be on average much faster than another. Thus it is possible to find circuits that will work (at least most of the time) with one manufacturer's chips and fail (at least most of the time) with another's. In practice this is pretty rare, but it does happen.

The Chips Are Down

We know of cases where production lines have been halted due to almost 100 per cent failures of a circuit board after a change of chip manufacturer for a basic logic device, or after the chip manufacturer changed their production process and suddenly an i.c. was (for example) much faster than before. If the "new" chip is in specification then the board manufacturer has no claim against the chip manufacturer.

Such problems occur in circuit designs that are too sensitive to possible variations in circuit parameters (such as gate delay). Asynchronously resetting counters as shown in Fig.1 is an example of this – it is quite common practice, but it does not always work.


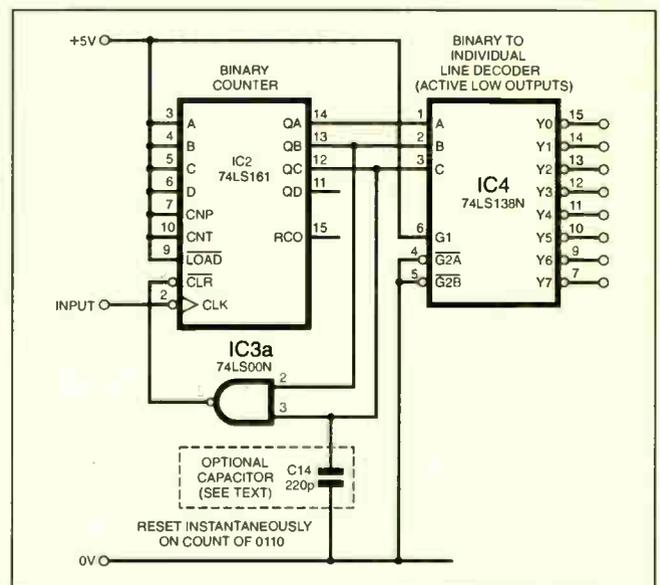


Fig. 1. Circuit example for asynchronously resetting counters.

SYMBOL FILE-2

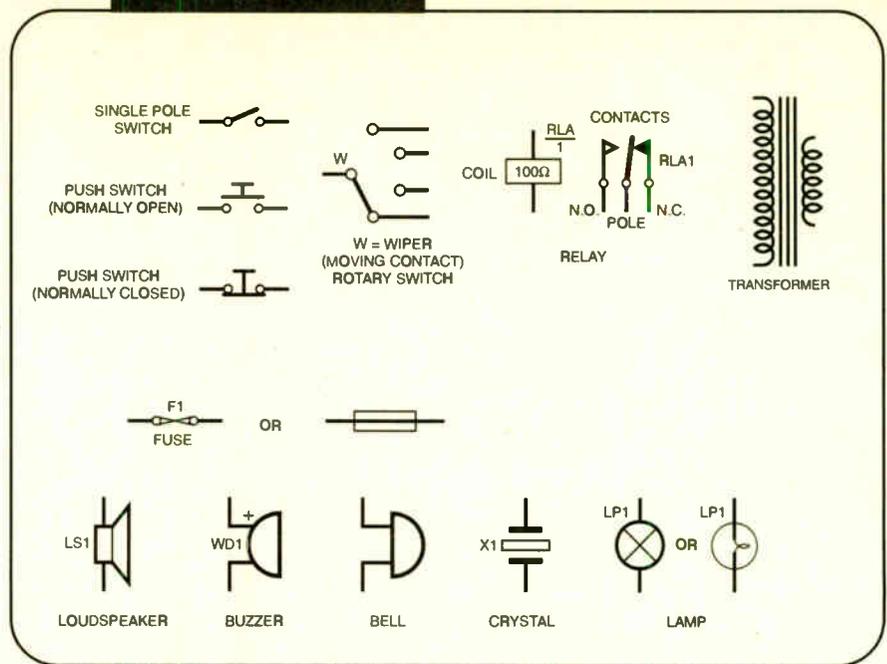

A selection of common circuit symbols.

For mass-produced commercial electronic designs it is usually better to avoid such sensitivities, but for hobbyist designs, where typically only one copy of the circuit is made the fact that tweaks such as adding a capacitor can make the circuit work means that it is not so critical. Having said that, it is good practice for the amateur designer to try to avoid having to use tweaks, by designing a more robust circuit in the first place.

There are a few variations on Fig.1 that could help in this respect: one approach is to use a counter that is guaranteed not to produce a reset glitch on the wrong count. The reader's use of the asynchronous counter would appear to be a solution here, but it is a bit ironic as asynchronous counters are often avoided in circuits like this because of their tendency to produce glitches due to intermediate output states. Although it worked in this case it is not a general solution!

Bit of a Problem

One potential problem with the circuit shown in Fig.1 is that the reset is produced by detecting bits B and C being equal to 1, irrespective of bit A. This allows the circuit to reset on a 0111 intermediate output as hypothesized by Dr. Manning.

If a three-input NAND gate were used to detect 0110, then the 0111 intermediate state would be unlikely to trigger the reset. Of course, the A bit would have to be inverted before connection to the NAND gate.

This may also be why using the Y6 output to reset the counter worked – the Y6 output from IC4 is decoded using all the counter's outputs so fewer intermediate states will decode as Y6. This may account for the variation in the circuit's behaviours using the IC3a and Y6 to drive the reset, rather than their different "inertias" as discussed earlier.

A more robust design is obtained by using a synchronous reset rather than the asynchronous one employed in Fig.1. The 74LS163 has such a reset, but is otherwise like the 74LS161. The circuit of Fig.1 could be modified to use a 74LS163 by changing the NAND gate (and inverter) to

detect binary 5 (0101). A three input gate is needed, but the capacitor is not required.

When the counter is outputting 5, the CLR line will go low causing the counter to reset to 0000 on the next clock. Even better would be to connect Y5 to the 74LS163's CLR. This would avoid the need for a NAND gate and inverter. In this circuit the counter would never go into the unused 6 state, even for a short time. *I.M.B.*


Simple Symbols

In last month's *Circuit Surgery* we described the basic technique of reading a circuit diagram. A circuit schematic is nothing more than a road map, with the towns and cities (electronic components) being interconnected by roads (conductors). We also said that a circuit diagram rarely contains the practical information that may be needed during assembly. Usually we cannot tell from the diagram what type of wire to use nor how to install it: is it handling a


sensitive microphone signal or a 3kW heating element?

We must "read" the drawing to find out what is going on, and we must then refer to the constructional information provided. A roadway intersection (electrical junction) is represented by a blob on a circuit diagram – see Fig.1 on page 263 of the April 2003 issue for details. The constructional details will offer essential information that relates to cable specification, insulation and pinout information etc., so that you can ensure that parts are connected together properly and components are inserted the right way round.

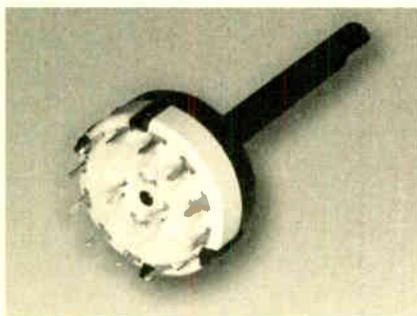In Symbol File-1 last month we showed the symbols for resistors and capacitors, including variations of those used in EPE. This month, more basic schematic information is given Symbol File-2 which shows the symbols that depict basic components including switches, fuses, transformers, buzzers, loudspeakers and more




Rotary Switch, 2-pole 6-way

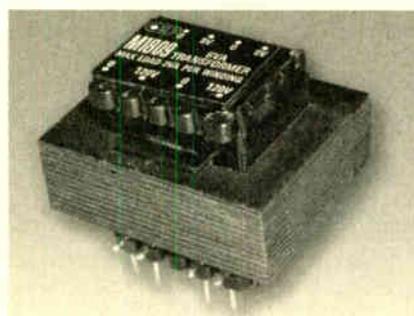


Mains Transformer, p.c.b. mounting




Relay

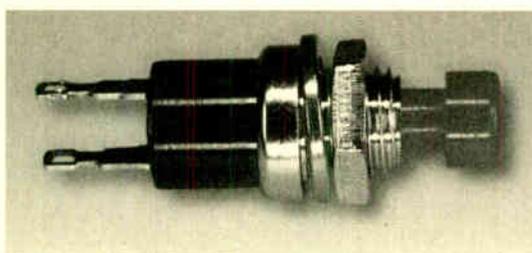

Pushswitch

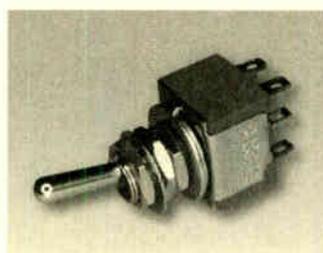

Toggle Switch

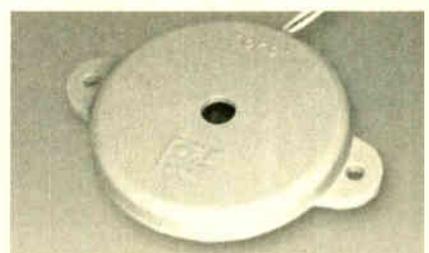

Piezo sounder disc

SYMBOL FILE-3

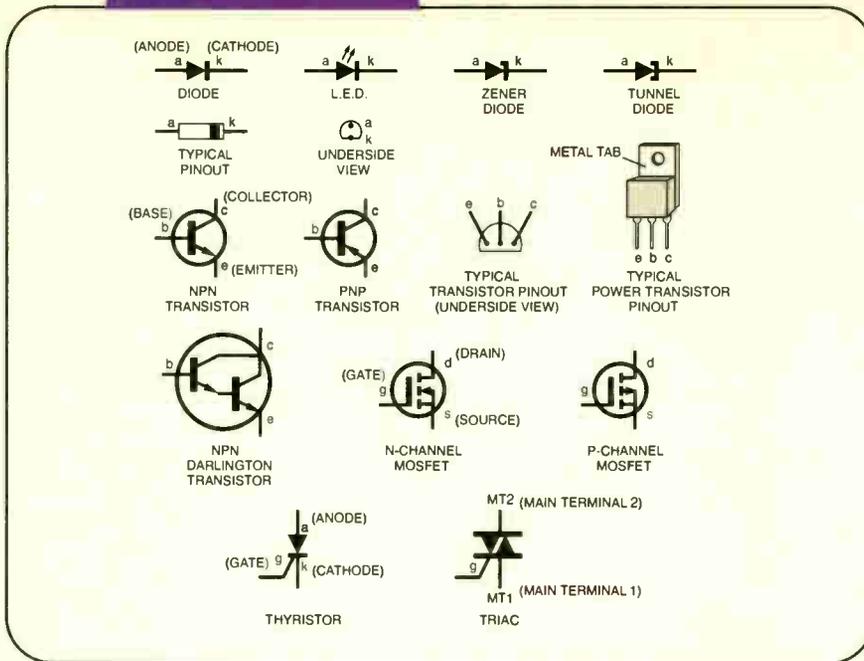


Fig.2. A selection of popular circuit symbols for semiconductors.

besides. With a little practice, you will soon be able to find your way around a circuit diagram and recognise all the major components used by the designer.

A Helping Hand

Devices such as resistors, inductors and capacitors are classed as “passive” components as they have no “electronic intelligence”. However, almost every circuit uses “active” semiconductor components including diodes, transistors and integrated circuit chips.

Our experience tells us that the incorrect fitting of semiconductor devices causes a large proportion of circuit construction problems. Almost every semiconductor device requires connecting in a unique way if the circuit is to work successfully, and so in Symbol File-3 we show common semiconductor symbols, which can be compared against their physical pinouts and styles (see photos).

By adding extra information in circuit schematics, *EPE* helps constructors to understand diagrams. Starting with a diode,

these have two terminals (anode and cathode), hence the *a* and *k* designations that are shown in our drawings. It is not uncommon to connect these the wrong way round – which may sometimes destroy the device!

Almost always, a stripe on the diode body indicates the cathode (*k*). (For an example, see the Atmospherics Monitor project last month, and compare the circuit diagram with the stripboard layout). This rule applies to most types of diode, including the Zener voltage reference device also shown.

Light-emitting diodes (l.e.d.s) find their way into many projects and again their terminal arrangement is described in a pinout drawing. Note that in this case the pinout is a worm’s eye view of this device, i.e. *as seen looking from underneath the component*. A flat side on the body helps to determine the orientation of the l.e.d. (usually it marks the cathode).

Status Symbols

The symbols for *npn* and *pnp* (hence, “bipolar”) transistors, along with a typical

specialist “Darlington” transistor (which merely combines two transistors into one package to produce a much higher gain), are also given in Symbol File-3. The use of transistors is often a stumbling block for beginners in electronics, and again *EPE* helps you by labelling the pins *e*, *b*, or *c* for emitter, base or collector respectively in circuit diagrams.

The incorrect connection of transistors is a very common error made by novices, but mistakes can be avoided by comparing the pinout diagrams with the circuit diagram. Smaller low-power bipolar transistors are usually produced in a plastic package whilst power transistors are packaged in TO-3 steel cans or TO-220 plastic tab styles.

In the case of small transistors, pinouts are almost always seen as an **underside** view, but power devices may have a frontal view instead. Either way, identifying the correct polarity of a transistor is essential for successful construction. Fortunately the advent of the Internet means that data sheets can now be downloaded directly from manufacturer’s web sites.

On then to MOSFET transistors, and the symbol for the common *n*-channel and *p*-channel devices are given in Symbol File-3. Note how the arrowhead points the other way, when compared with *npn* and *pnp* transistors! As usual, *EPE* designates the terminals (*drain*, *source* and *gate*) of MOSFETs in circuit diagrams. We described MOSFETs in more detail in the Jan. and Feb. ’03 issues of *Circuit Surgery*, and a follow-up is in the pipeline.

Finally, to round off semiconductor circuit symbols, those for a thyristor and triac are shown, along with their terminal designations. It is worth pointing out that triacs are often associated with mains voltage control circuits, and therefore all constructional details must be followed closely, especially concerning the insulation aspects, in order to avoid any possibility of receiving accidental mains electric shock from the triac’s metal mounting tab.

In the third part of our circuit diagram mini-series next month, we look at integrated circuits, followed by power rails and ground (earth) symbols and other considerations. *ARW*.



Diode, glass or plastic package




Power Triac, stud mounted




Red L.E.D.



Power Transistors

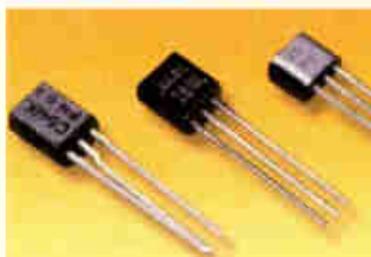

Transistors, plastic package

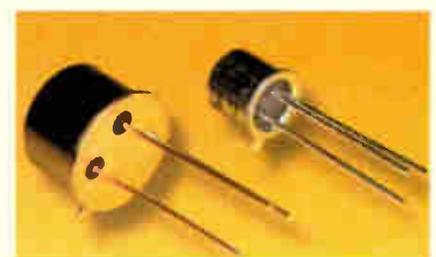


Transistors, metal can


AutotraxTM

Electronic Design Automation

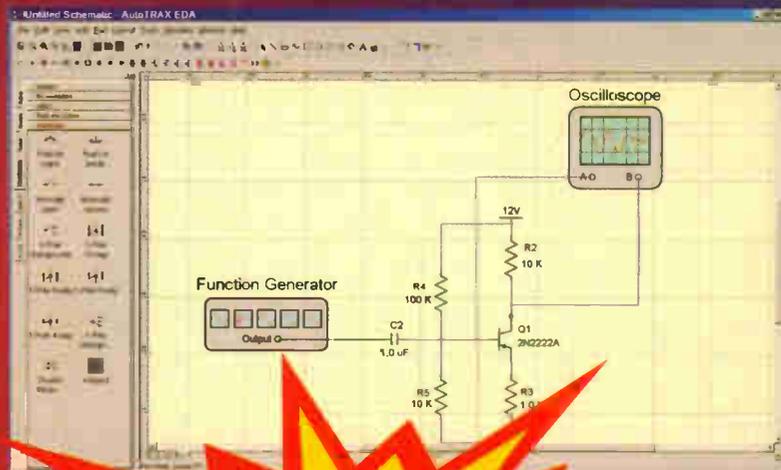Schematic Capture
SPICE Simulation
PCB Layout
Auto-Layout/Router
3D PCB Visualization
Database Support



**Totally
FREE!
No limits**

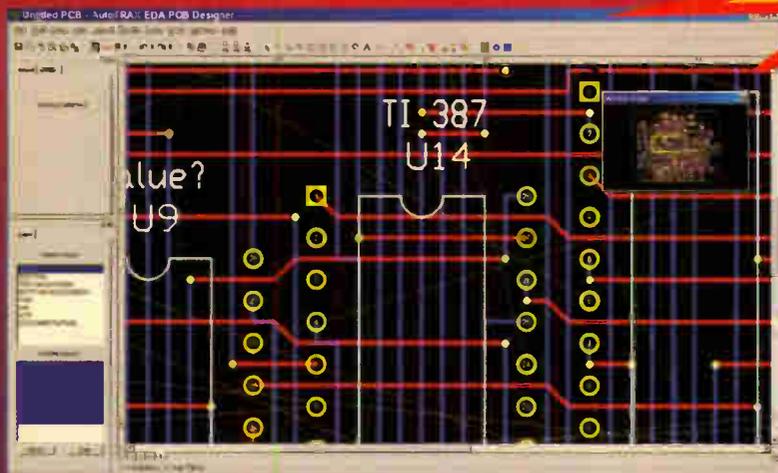

- Drag and drop parts onto your schematic.
- Connect them together.
- Add virtual instruments such as scopes and function generators.
- Use the PCB design wizard to create your PCB.
- Autolayout and autoroute the board.
- View the board in 3D.
- Output to Gerber and AutoCAD/Solidworks.

To find out more go to www.autotraxEDA.com

First, I want to congratulate you on an excellent EDA concept. Great graphics, nice storage concept, nice integration. And you have got the tool use JUST RIGHT. It might seem minor, but sensible ways of doing things like building parts, adding pins to parts, using wires, etc make a massive difference to the basic useability of an EDA tool. I've been using EDA tools for 20 years now ... and the system you have here is as good as anything I've ever used ... Phillip Dimond

Why wait? Download the unlimited FREE software NOW!

www.autotraxEDA.com



See us on booth #824 at the PCB West conference/exhibition
in San Jose, California, March 12-13 2003

We can supply back issues of *EPE* by post, most issues from the past three years are available. An *EPE* index for the last five years is also available at www.epemag.wimborne.co.uk or see order form below. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photocopy of any *one article* (or *one part* of a series) can be purchased for the same price. Issues from Nov. 98 are available on CD-ROM – see next page – and issues from the last six months are also available to download from www.epemag.com.

DID YOU MISS THESE?

JAN '02

PROJECTS • PIC Magick Musick • Time Delay Touch Switch • Versatile Bench Power Supply • Forever Flasher.

FEATURES • Teach-In 2002 – Part 3 • Practically Speaking • Ingenuity Unlimited • New Technology Update • Circuit Surgery • Net Work – The Internet Page.

FEB '02

PROJECTS • PIC Spectrum Analyser • Guitar Practice Amp • HT Power Supply • Versatile Current Monitor.

FEATURES • Teach-In 2002 – Part 4 • Ingenuity Unlimited • Russian Space Shuttle Revisited • Circuit Surgery • Interface • New Technology Update • Net Work – The Internet Page.

MAR '02

PROJECTS • MK484 Shortwave Radio • PIC Virus Zapper • RH Meter • PIC Mini-Enigma.

FEATURES • Teach-In 2002 – Part 5 • Ingenuity Unlimited • Programming PIC Interrupts-1 • Circuit Surgery • Practically Speaking • New Technology Update • Net Work – The Internet Page.



APR '02

PROJECTS • Electric Guitar Tuner • PIC Controlled Intruder Alarm • Solar Charge and Go • Manual Stepper Motor Controller.

FEATURES • Teach-In 2002 – Part 6 • Interface • Programming PIC Interrupts-2 • Circuit Surgery • Ingenuity Unlimited • New Technology Update • Net Work – The Internet Page • *FREE* Giant Op.Amp Data Chart.

MAY '02

PROJECTS • PIC Big-Digit Display • Simple Audio Circuits – 1 • Freezer Alarm • Washing Ready Indicator.

FEATURES • Teach-In 2002 – Part 7 • Ingenuity Unlimited • Practically Speaking • New Technology Update • Circuit Surgery • Net Work – The Internet Page.

JUNE '02

PROJECTS • Biopic Heartbeat Monitor • Frequency Standard Generator • Simple Audio Circuits – 2 • World Lamp.

FEATURES • Teach-In 2002 – Part 8 • Interface • New Technology Update • Circuit Surgery • Ingenuity Unlimited • Net Work – The Internet Page.

JULY '02

PROJECTS • EPE StyloPIC • Infra-Red Autoswitch • Simple Audio Circuits – 3 • Rotary Combination Lock.

FEATURES • Teach-In 2002 – Part 9 • Practically Speaking • Using The PIC's PCLATH Command • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Net Work – The Internet Page.

AUG '02

PROJECTS • PIC World Clock • Pickpocket Alarm • Big-Ears Buggy • Simple Audio Circuits – 4.

FEATURES • Teach-In 2002 – Part 10 • Using Square Roots with PICs • Ingenuity Unlimited • Evolutionary Electronics • Interface • Circuit Surgery • Net Work – The Internet Page.

SEPT '02

PROJECTS • Freebird Glider Control • Portable Telephone Tester • *EPE* Morse Code Reader • Vinyl to CD Preampifier.

FEATURES • Circuit Surgery • New Technology Update • Practically Speaking • Net Work • Flowcode for PICmicro • Logic Gate Inverter Oscillators • Net Work – The Internet Page.



OCT '02 Photocopies only

PROJECTS • *EPE* Bounty Treasure Hunter • IC Tester • Headset Communicator • PIC-Pocket Battleships.

FEATURES • Circuit Surgery • New Technology Update • Logic Gate Inverter Oscillators – 2 • Interface • Network – The Internet Page • Using TK3 With Windows XP and 2000.

NOV '02 Photocopies only

PROJECTS • *EPE* Hybrid Computer – 1 • Tuning Fork and Metronome • Transient Tracker • PICAXE Projects-1 (Egg Timer – Dice Machine – Quiz Game Monitor).

FEATURES • Practically Speaking • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Net Work – The Internet Page.

DEC '02

PROJECTS • Versatile PIC Flasher • *EPE* Hybrid Computer – 2 • Door Defender • PICAXE Projects – 2 (Temperature Sensor – Voltage Sensor – VU Indicator).

FEATURES • Electronic Paper • Alternative Uses for Transistors • Interface • Circuit Surgery • New Technology Update • Ingenuity Unlimited • Net Work – The Internet Page • 2002 Annual Index.

JAN '03

PROJECTS • *EPE* Minder • F.M. Frequency Surfer • Wind Speed Meter • PICAXE Projects-3 (Chaser Lights).

FEATURES • Who Really Invented The Transistor • TechnoTalk • Circuit Surgery • Practically Speaking • New Technology Update • Computer GOTOs • Ingenuity Unlimited • Net Work – The Internet Page.

FEB '03

PROJECTS • Wind Tunnel • Brainbot Buggy • Back To Basics-1 (Hearing Aid, Audio Power Amplifier) • Tesla High Voltage Transformer.

FEATURES • In The Bag • Techno Talk • Circuit Surgery • New Technology Update • Interface • Ingenuity Unlimited • Net Work – The Internet Page.



MAR '03

PROJECTS • Wind-Up Torch Mk II • 200kHz Function Generator • Driver Alert • Back-To-Basics-2 (Metal Detector, Simple Timer).

FEATURES • Ingenuity Unlimited • Practically Speaking • Techno Talk • New Technology Update • Circuit Surgery • Peak LCR Component Analyser Review • Net Work – The Internet Page.

APR '03

PROJECTS • Atmospheric Monitor • Intelligent Garden Lights Controller • Back-To-Basics-3 (Touch Light, Plant Watering Reminder) • Earth Resistivity Logger-Part 1.

FEATURES • Ingenuity Unlimited • Techno Talk • New Technology Update • Circuit Surgery • Interface • Network – The Internet Page • *SPECIAL SUPPLEMENT* – *EPE* PIC Tutorial V2-Part 1.

BACK ISSUES ONLY £3.50 each inc. UK p&p.

Overseas prices £4 each surface mail, £5.50 each airmail.

We can also supply issues from earlier years: 1998 (except Jan. to May, July, Sept., Nov., Dec.), 1999 (except Aug., Dec.), 2000 (except Feb.), 2001 (except May, Sept., Oct.), 2002 (except Oct., Nov.) Where we do not have an issue a photocopy of any *one article* or *one part* of a series can be provided at the same price.

ORDER FORM – BACK ISSUES – PHOTOCOPIES– INDEXES

- Send back issues dated
- Send photocopies of (article title and issue date)
- Send copies of last five years indexes (£3.50 for five inc. p&p – Overseas £4 surface, £5.50 airmail)

Name

Address

.....Tel:

I enclose cheque/P.O./bank draft to the value of £

Please charge my Visa/Mastercard/Amex/Diners Club/Switch £ Switch Issue No.

Card No.

Card Expiry Date Card Security Code (The last 3 digits on or just under the signature strip)

SEND TO: **Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.**

Tel: 01202 873872. Fax: 01202 874562.


E-mail: orders@epemag.wimborne.co.uk On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm

Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.


M05/03

STORE YOUR BACK ISSUES ON MINI CD-ROMS

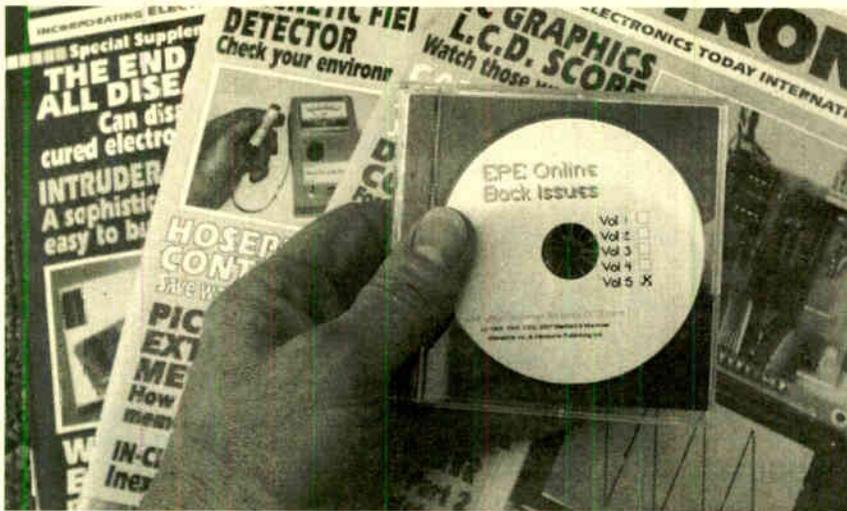

**VOL 7
NOW AVAILABLE**

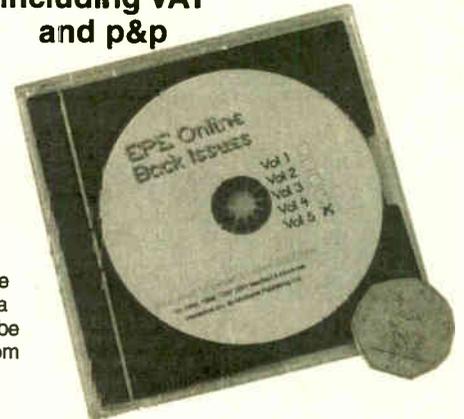**ONLY
£14.45** each
including VAT
and p&p



A great way to buy **EPE Back Issues** – our mini CD-ROMs contain back issues from our **EPE Online** website plus bonus articles, all the relevant PIC software and web links. Note: no free gifts are included. All this for just £14.45 each including postage and packing.

VOL 1 CONTENTS

BACK ISSUES – November 1998 to June 1999 (all the projects, features, news, IUs etc. from all eight issues). Note: No advertisements are included. **PIC PROJECT CODES** – All the available codes for the PIC based projects published in these issues.

VOL 2 CONTENTS

BACK ISSUES – July 1999 to December 1999 (all the projects, features, news, IUs, etc. from all six issues). Note: No advertisements are included. **PIC PROJECT CODES** – All the available codes for the PIC-based projects published in these issues.

VOL 3 CONTENTS

BACK ISSUES – January 2000 to June 2000 (all the projects, features, news, IUs, etc. from all six issues). **PIC PROJECT CODES** – All the available codes for the PIC-based projects published in these issues.

VOL 4 CONTENTS

BACK ISSUES – July 2000 to Dec. 2000 (all the projects, features, news, IUs etc. from all six issues). **PROJECT CODES** – All the available codes for the programmable projects in these issues.

VOL 5 CONTENTS

BACK ISSUES – January 2001 to June 2001 (all the projects, features, news, IUs etc. from all six issues). **PROJECT CODES** – All the available codes for the programmable projects in these issues, including those for *Interface*.

VOL 6 CONTENTS

BACK ISSUES – July 2001 to December 2001 (all the projects, features, news, IUs etc. from all six issues). **PROJECT CODES** – All the available codes for the programmable projects in these issues, including those for *Interface*.

VOL 7 CONTENTS

BACK ISSUES – Jan 2002 to June 2002 (all the projects, features, news, IUs etc. from all six issues). **PROJECT CODES** – All the available codes for the programmable projects in these issues, including those for *Interface*.

EXTRA ARTICLES – ON ALL VOLUMES

BASIC SOLDERING GUIDE – Alan Winstanley's internationally acclaimed fully illustrated guide. **UNDERSTANDING PASSIVE COMPONENTS** – Introduction to the basic principles of passive components. **HOW TO USE INTELLIGENT L.C.D.s**, By Julian Ilett – An utterly practical guide to interfacing and programming intelligent liquid crystal display modules. **PhyzyB COMPUTERS BONUS ARTICLE 1** – Signed and Unsigned Binary Numbers. By Clive "Max" Maxfield and Alvin Brown. **PhyzyB COMPUTERS BONUS ARTICLE 2** – Creating an Event Counter. By Clive "Max" Maxfield and Alvin Brown. **INTERGRAPH COMPUTER SYSTEMS 3D GRAPHICS** – A chapter from Intergraph's book that explains computer graphics technology in an interesting and understandable way with full colour graphics.

EXTRA ARTICLE ON VOL 1 & 2. THE LIFE & WORKS OF KONRAD ZUSE – a brilliant pioneer in the evolution of computers. A bonus article on his life and work written by his eldest son, including many previously unpublished photographs.

NOTE: These mini CD-ROMs are suitable for use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader (available free from the Internet – www.adobe.com/acrobat)

Order on-line from
www.epemag.wimborne.co.uk/shopdoor.htm
or www.epemag.com (USA \$ prices)
or by phone, Fax, E-mail or Post

BACK ISSUES MINI CD-ROM ORDER FORM

Please send me (quantity) BACK ISSUES CD-ROM VOL 1
Please send me (quantity) BACK ISSUES CD-ROM VOL 2
Please send me (quantity) BACK ISSUES CD-ROM VOL 3
Please send me (quantity) BACK ISSUES CD-ROM VOL 4
Please send me (quantity) BACK ISSUES CD-ROM VOL 5
Please send me (quantity) BACK ISSUES CD-ROM VOL 6
Please send me (quantity) BACK ISSUES CD-ROM VOL 7
Price £14.45 each – includes postage to anywhere in the world.

Name

Address

.....

..... Post Code

I enclose cheque/P.O./bank draft to the value of £

Please charge my Visa/Mastercard/Amex/Diners Club/Switch

£

Card No.

Card Security Code (The last 3 digits on or just under the signature strip)

Expiry Date Switch Issue No.

SEND TO: **Everyday Practical Electronics,
Wimborne Publishing Ltd.,**

408 Wimborne Road East, Ferndown, Dorset BH22 9ND.

Tel: 01202 873872. Fax: 01202 874562.

E-mail: orders@epemag.wimborne.co.uk

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.




BS2-IC




BS2-SX



BS2E-IC


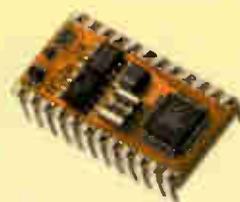


BS2P/24

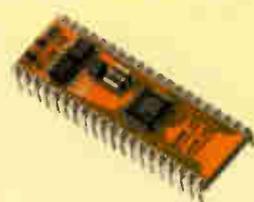

BS2P/40

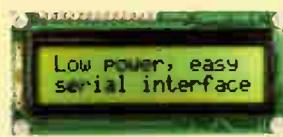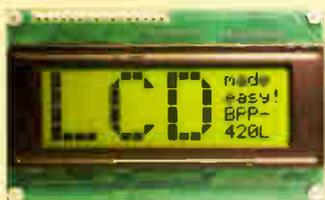Parallax BASIC Stamps - still the easy way to get your project up and running!



Serial Alphanumeric and Graphic Displays, Mini-Terminals and Bezel kits

www.milinst.com



Animated Head



3-Axis Machine



Six-Legged Walkers



Robotic Arms




Bipeds

Robotic models for both the beginner and the advanced hobbyist



Servo Drivers

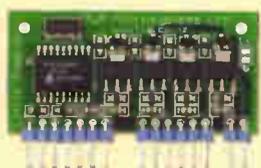


Motor Drivers



On-Screen Displays



DMX Protocol

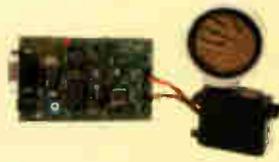

U/Sound Ranging


Animatronics and Specialist Interface-Control Modules



Quadravox MP3 & Speech Systems



SensoryInc Voice Recognition

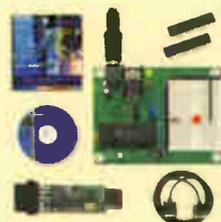

Parallax Ubicom Tool Kits



Tech-Tools PIC & Rom Emulators



BASICMicro PIC BASIC Compilers

Development Tools

Milford Instruments Limited Tel 01977 683665, Fax 01977 681465, sales@milinst.com

EPE PIC TUTORIAL V2


JOHN BECKER

PART TWO

FREE SUPPLEMENT

Quite simply the easiest low-cost way to learn about using PIC Microcontrollers!

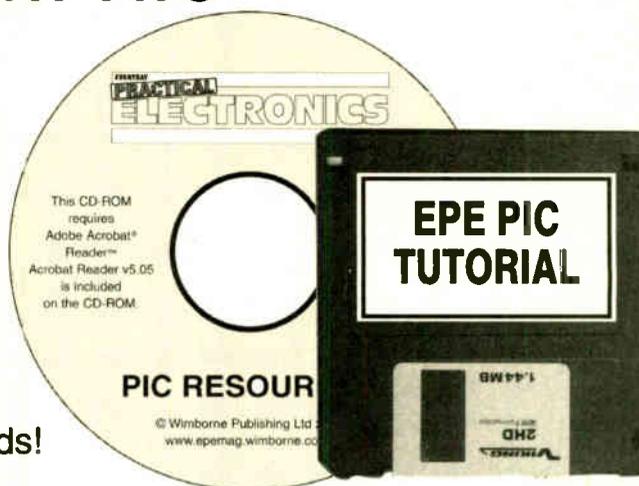In this part we play with switches, make noises, count times, and generally have fun with some more PIC16F84 commands!



TUTORIAL 7 CONCEPTS EXAMINED

Switch monitoring
Command ANDLW
Command ANDWF
Command ADDWF
Command ADDLW
Nibbles
STATUS bit 1
Digit Carry flag
Bit code DC

CONNECTIONS NEEDED

All Port B to all l.e.d.s.
Port A RA0-RA3 to switches SW0-SW3 (via CP19-CP16)
CP21 to +5V OUT
CP20 to 0V OUT
Capacitor C7 as 1 μ F
Preset VR1 set to minimum resistance (fully clockwise)

From hereon we shall usually omit the program initialisation commands that have up to now been shown at the top of each listing. Some will be included where they help to clarify the program. Otherwise, assume that any name used in the listing extracts shown will have been defined or equated in the headings. The commands are included in full on the disk file program listings (source code).

We now turn to looking at how data is input via switches and shall continue to show the results on individual l.e.d.s. In Tutorials 21 and 22 we shall look at 7-segment l.e.d.s and alphanumeric l.c.d.s as the output displays.

First connect TK3's pushbutton switches SW0, SW1, SW2, SW3 (via CP19, CP18, CP17, CP16) to PORTA pins RA0, RA1, RA2, RA3 respectively. Connect the switch power pin CP21 to the +5V OUT pin, and switch power pin CP20 to the 0V OUT pin. Port pins RA0 to RA3 are now

LISTING 8 - PROGRAM TK3TUT8

```
BEGIN    CLRF COUNT
LOOP     MOVF PORTA,W
         ANDLW B'00000001'
         ADDWF COUNT,F
         MOVF COUNT,W
         MOVWF PORTB
         GOTO LOOP
```

connected so that they are normally biased low (to 0V) but will go high (+5V) when their respective switches are pressed.

Run TK3TUT8.HEX. Pushing switch SW0 on and off, PORTB's l.e.d.s will be seen to go on and off in a binary sequence when the switch is on (pressed), but will remain in the last condition when the switch is off (released). In this example, the program tests whether the status of switch SW0, which is connected to PORTA RA0 (bit 0), is on or off. If the switch is on then the counter variable, COUNT, is repeatedly added to (by 1 in this example). A value of zero is added to the count if the switch is off. The count value is output to PORTB.

First let's look at two of the commands introduced here. ANDLW and ADDWF. Their counterparts ANDWF and ADDLW will also be examined.

COMMANDS ANDLW AND ANDWF

As no doubt most of you are aware, if one binary number is ANDed with another, then only if the same bits of both numbers are set (1) will the answer also have a 1 in that position. Any zeros on either or both sides for any bit will automatically produce a result of 0, e.g.:

```
First number: 01110010
Second number: 01011001
ANDed answer: 01010000
```

This technique is widely used in electronics and computing, the final answer determining the subsequent action to be taken by a circuit or software routine.

There are two ANDING commands available with PICs, ANDLW (AND Literal to W), and ANDWF (AND W with File value). Suppose that the first number in the foregoing examples (01110010) is already contained within W, we then wish to AND it with a fixed number as stated in a program command. Assuming that the fixed number is the second number quoted, the command is:

```
ANDLW B'01011001'
```

The PIC ANDs the second (literal) number with that already held in W. The answer (01010000) is retained by W and is available to be further manipulated or copied into any file as specified by the command which follows ANDLW. You could, for example, use the command MOVWF PORTB which will turn on l.e.d.s LD6 and LD4 (01010000).

Any of the three numerical formats may be used with ANDLW, e.g. B'00011111' (binary), H'1F' (hexadecimal). 31 (decimal), are all legitimate and equal. It is also legitimate to use a name that has been equated with a value, e.g. ANDLW PORTB (which would AND 6 with W since we have previously specified that the name PORTB represents the value 6).

The command ANDWF is used to AND an existing value within W to a value within a named file, either retaining the answer in W (ANDWF FILENAME,W) or putting back in the named file (ANDWF FILENAME,F).

It is not possible to directly AND the contents of two files together, the value of one or other file must have already been moved into W before the ANDing can take place. With both commands ANDLW and ANDWF, if the answer is zero, the Zero

flag of STATUS is set. If the answer is greater than zero, the Zero flag is cleared. Zero is the only flag affected by an AND command.

COMMANDS ADDLW AND ADDWF

There are two ADDing commands available with PICs, ADDLW (ADD Literal to W), and ADDWF (ADD W to a File value). Command ADDLW is used where a fixed number (literal) within a program is to be added to an existing value within W and which has been obtained by a previous operation. Suppose that W holds the answer produced in the previous ANDing example, 01010000 (decimal 80), and you wish to add a fixed value to it, 53 decimal (00110101), for instance. The command would be:

```
ADDLW 53 (or ADDLW H'35' hexadecimal, or ADDLW B'00110101' binary).
```

The answer in this instance is 10000101 (decimal 133) and is retained in W for further use or copying into a file, e.g. MOVWF PORTB.

Command ADDWF adds the contents of W to the value within a stated file. The answer can be held in W (ADDWF PORTB,W) or put back into the named file (ADDWF PORTB,F).

Three flags within STATUS are affected by any ADD command, Carry, Zero and Digit Carry. If the answer to an addition is greater than 255, the Carry flag is set, otherwise it is cleared. If the answer equals zero, the Zero flag is set, otherwise it is cleared. The third flag, Digit Carry, you have not encountered yet. Although the concept is not illustrated until later (Tutorial 19), it is appropriate to describe it now.

If you imagine that an 8-bit binary number (e.g. 10110110) is split into two halves (known as "nibbles"), 1011 and 0110, the righthand nibble is monitored by the PIC as a separate digit and it is served by its own flag, the Digit Carry flag. If an addition takes place which produces a result greater than 15 (binary 1111) for that nibble, the Digit Carry flag is set, otherwise it is cleared.

LISTING 8 FLOW

Having described the new terms, we shall now detail what happens in Listing 8. As said at the start of Tutorial 7, switches SW0 to SW3 are biased so that their respective PORTA pins are normally at 0V (low) but go high when pressed. In this example program, at the label LOOP the contents of PORTA are copied into W (MOVF PORTA,W), which then holds the status of all five usable bits of that port. We are only interested, though, in the status of the switch on PORTA bit 0, switch SW0. Therefore, in the next command (ANDLW B'00000001') bit 0 is ANDed with 1 to isolate its value, the other seven bits in W being cleared by the respective zeros of the ANDed value.

The answer in W is then added to the contents of the counter (ADDWF COUNT,F). Next, the contents of the counter are brought back into W (MOVF COUNT,W) and then copied into PORTB (MOVWF PORTB), whose l.e.d.s are turned on or off depending on the binary

count value. With the command GOTO LOOP, the sequence is repeated.

It will be seen that there is only an increase in the count value if PORTA bit 0 holds a 1, therefore the count will only change if the switch is on (pressed). Pressing any other switch connected to PORTA has no effect. When the counter passes 255, its value rolls over to zero and starts counting upwards again.

EXERCISE 7

7.1. Can you see another way of writing the first two lines using MOVLW and ANDWF?

7.2. Can you see how the BTFSS or BTFSC commands might be used to achieve the same output result; the use of MOVLW 1 or ADDLW 1 could be useful here.

7.3. There is also the opportunity to use INCF in this type of situation. Try rewriting to include this command.

TUTORIAL 8

CONCEPTS EXAMINED

Increasing speed of TK3TUT8
Bit testing for switch status

CONNECTIONS NEEDED

All Port B to all l.e.d.s.
Port A RA0-RA3 to switches SW0-SW3 (via CP19-CP16)
CP21 to +5V OUT
CP20 to 0V OUT
Capacitor C7 as 1μF
Preset VR1 set to minimum resistance (fully clockwise)

LISTING 9 - PROGRAM TK3TUT9

```
LOOP BTFSS PORTA,0
      GOTO LOOP
      INCF COUNT,F
      MOVF COUNT,W
      MOVWF PORTB
      GOTO LOOP
```

In TK3TUT8 we saw that the count adding commands etc. were performed even if the count value was zero. This is a waste of processing speed, why bother to add zero to a count? The program in Listing 9 shows a faster alternative. Run TK3TUT9.HEX.

By using the command BTFSS to check the status of a switch (in this case still SW0 on PORTA bit 0), if the switch is not pressed we can avoid the count incrementing procedure, jumping immediately to a further switch status test. Alternatively, in another program, by substituting another destination instead of LOOP, we could jump to a totally different routine and perform some other procedure.

Another choice is to use the command RETURN instead of GOTO LOOP to return to another routine which had called this one. Commands CALL and RETURN will be covered in Tutorial 13.

It is expected that you will recognise from Listing 9 what the program does and how it does it. If you don't, re-read Tutorial 4 and the section on BTFSS.

EXERCISE 8

8.1. What happens if you use BTFSC instead of BTFSS?

8.2. Could one of the Zero flag testing commands be used instead of BTFSS? If so, how, and would an AND command be useful? (Remember that PORTA has more bits than just bit 0).

TUTORIAL 9

CONCEPT EXAMINED

Responding to a switch press only at the moment of pressing

CONNECTIONS NEEDED

All Port B to all l.e.d.s.
Port A RA0-RA3 to switches SW0-SW3 (via CP19-CP16)
CP21 to +5V OUT
CP20 to 0V OUT
Capacitor C7 as 1μF
Preset VR1 set to minimum resistance (fully clockwise)

LISTING 10 - PROGRAM TK3TUT10

```
BEGIN CLRf COUNT
      CLRf SWITCH
TESTIT BTFSC PORTA,0
      GOTO TSTPRV
      BCF SWITCH,0
      GOTO TESTIT
TSTPRV BTFSC SWITCH,0
      GOTO TESTIT
      INCF COUNT,F
      MOVF COUNT,W
      MOVWF PORTB
      BSF SWITCH,0
      GOTO TESTIT
```

In the switch press examples of Listings 8 and 9, we saw that the counter was incremented for the entire duration of the switch being on. Often, only a single response to a change of switch status might be required. This entails testing the switch status and comparing it with a previous test. Only if the switch is on and if that on condition has not yet been responded to will the next action be performed.

Load TK3TUT10.HEX. You are still monitoring PORTA bit 0 for the switch press (SW0), responding to it via the l.e.d.s on PORTB. Observe the l.e.d.s while pressing SW0 on and off. For each pressing, only one change of the l.e.d. count will occur (but note that low-cost switches may cause switch-bounce, resulting in the count increasing for each bounce – a matter covered later).

Study Listing 10: the entry to the routine is at BEGIN where two variables, COUNT and SWITCH are cleared. At the label TESTIT, the command is BTFSC PORTA,0, testing the status of PORTA bit 0 (is it clear?). Remember that we are only interested in the bit being set. If it is false that bit 0 is clear (i.e. that it is set – the switch is pressed) the command GOTO TSTPRV is performed and then the status of SWITCH bit 0 is tested, BTFSC SWITCH,0. This bit serves as the flag to keep track of the previous status of the switch. At this moment, the bit will be clear because the whole byte was cleared on entry to the routine. Consequently, the GOTO TESTIT command is skipped, the count is incremented and its value output to PORTB.

Now SWITCH bit 0 is set (BSF SWITCH,0) to indicate that the count has been incremented for this switch press (i.e. the flag is set), and the program jumps back to TESTIT. If the switch is still pressed, then at TSTPRV the BTFSC SWITCH,0 command will produce a false answer and the command GOTO TESTIT will be performed, thus preventing the counter from being further incremented at this time.

What is now needed is for the switch to be released so that the two commands BCF SWITCH,0 (clear the flag) and GOTO TESTIT can occur. The stage is then once again set for the next switch press to be responded to by the counter.

EXERCISE 9

9.1. In Listing 10, AND and MOV commands could have been used instead of BTFSC and BCF. How, and with what other command?

9.2. Would using BTFSS instead of BTFSC involve more commands and labels having to be used as well?

9.3. Because low cost switches have probably been used, there is the danger that mechanical switch bounce might occur, causing the count to be incremented undesirably. Another counter could be used to cause a delay in the rate of switch testing to eliminate the effects of switch bounce. How would you implement the delay, and where would you put the commands required. Hint, another label will be needed as well.

TUTORIAL 10

CONCEPTS EXAMINED

Performing different functions depending upon which of two switches is pressed

The use of a common sub-routine serving two other routines

CONNECTIONS NEEDED

All Port B to all I.e.d.s.
Port A RA0-RA3 to switches SW0-SW3 (via CP19-CP16)
CP21 to +5V OUT
CP20 to 0V OUT
Capacitor C7 as 1 μ F
Preset VR1 set to minimum resistance (fully clockwise)

Run TK3TUT11.HEX and experiment with the switches on PORTA bits 0 and 2 (SW0 and SW2). You will discover that switch SW0 causes the count displayed on the I.e.d.s to be increased, and that switch SW2 decreases the count. The basic logic flow is the same as that in Listing 10, except that two switches are used and each switch is responsible for a different routine.

Note that whilst each switch could have had its own routine to output to PORTB, the two routines would be the same. Consequently, each switch routine is routed into a common output sub-routine (OUTPUT). At the end of SW0's routine, the command GOTO OUTPUT needs to be given, but at the end of SW2's routine, no GOTO OUTPUT command is needed because OUTPUT follows immediately after it. It is said to reach OUTPUT by *default* because it does not need to be told to go there.

LISTING 11 – PROGRAM TK3TUT11

```
BEGIN      CLRf COUNT
           CLRf SWITCH
TEST1      BTFSC PORTA,0
           GOTO TSTPR1
           BCF SWITCH,0
           GOTO TEST2
TSTPR1     BTFSC SWITCH,0
           GOTO TEST2
           BSF SWITCH,0
           INCF COUNT,F
           GOTO OUTPUT
TEST2      BTFSC PORTA,2
           GOTO TSTPR2
           BCF SWITCH,2
           GOTO TEST1
TSTPR2     BTFSC SWITCH,2
           GOTO TEST1
           BSF SWITCH,2
           DECF COUNT,F
OUTPUT     MOVF COUNT,W
           MOVWF PORTB
           GOTO TEST1
```

EXERCISE 10

10.1. How do you think a single test for *neither* of the switches being pressed could be introduced, shortening the testing time? Could an AND be used with a STATUS check, or can a STATUS check be used on its own without an AND? (Think carefully about the latter.)

10.2. How would you increase the count by more than one, say two, at each press of switch SW0? With the knowledge you've gained so far, three ways should come to mind, one of them including the use of a new named variable.

10.3. If you want to add 255 each time a switch SW0 press occurs, do you need an ADD command, or is there another command which will do the same job? (Think *rollover*.)

TUTORIAL 11

CONCEPTS EXAMINED

The ease of reflecting PORTA's switches on PORTB's I.e.d.s!
Command COMF
Command SWAPF
Inverting a byte's bit logic
Swapping a byte's nibbles

CONNECTIONS NEEDED

All Port B to all I.e.d.s.
Port A RA0-RA3 to switches SW0-SW3 (via CP19-CP16)
CP21 to +5V OUT
CP20 to 0V OUT
Capacitor C7 as 1 μ F
Preset VR1 set to minimum resistance (fully clockwise)

Load TUT12.HEX. Experiment with pressing any combination of the four

LISTING 12 – PROGRAM TK3TUT12

```
LOOP      MOVF PORTA,W
           ANDLW B'00001111'
           MOVWF PORTB
           GOTO LOOP
```

switches on PORTA (SW0 to SW3) while observing the I.e.d.s on PORTB. This routine should need no further comment. Another way of expressing the first two commands is:

```
LOOP      MOVLW B'00001111'
           ANDWF PORTA,W
```

Now load TUT13.HEX and run it, again experimenting with pressing any combination of the switches on PORTA (SW0 to SW3) and observing the I.e.d.s on PORTB.

LISTING 13 – PROGRAM TK3TUT13

```
LOOP      SWAPF PORTA,W
           ANDLW B'11110000'
           MOVWF PORTB
```

You will see while you press PORTA's four switches, that they are having their status displayed on PORTB's four lefthand I.e.d.s (LD7 to LD4), even though you have not changed the wiring to PORTB and the I.e.d.s. Had there been a fifth switch, on PORTA RA4, it would be affecting the first I.e.d. on the right (LD0) – if a different AND value were used (what value?).

What is happening is that the software has been told to swap and move into W (SWAPF PORTA,W) the left and righthand four bits of PORTA (its nibbles, as introduced in Tutorial 7). The answer is then ANDed with bits that reflect the swapped status in order to remove any possibility of influence by the unused bits of PORTA's register.

The SWAPF command is especially useful if the values of the two nibbles are required separately as values of up to 15 (00001111). A good example of its use will be seen in Tutorial 21. It is illustrated now because of its programming similarity to TK3TUT12 and TK3TUT14.

The F suffix can be used with SWAPF instead of W, as with other files discussed. There is no command which allows nibbles to be swapped once the byte is in W. If a byte within W needs swapping, it must be put out to a file, and then the SWAPF (FILENAME),W command given to bring it back into W.

Let's look now at another command which uses a similar demonstration routine to TK3TUT12 and TK3TUT13. Run TK3TUT14.HEX. Once more, experiment with pressing any combination of switches SW0 to SW3 while watching PORTB's I.e.d.s.

LISTING 14 – PROGRAM TK3TUT14

```
LOOP      COMF PORTA,W
           ANDLW B'00001111'
           MOVWF PORTB
           GOTO LOOP
```

You will now discover that instead of I.e.d.s being turned on when a switch is pressed, they are turned off, and vice versa. This is due to the command COMF, which automatically inverts each bit of a byte, 1s becoming 0s, 0s becoming 1s, i.e. it performs a task known as *complementing*, hence COMF, which means *Complement File*.

There are several uses for this command, one of which is the situation when all the switches are biased to the +5V line instead of 0V. In that instance, and using the switch testing techniques shown earlier, pressing the switches would produce the wrong bit levels for the commands shown: switches would need to be held pressed for off, releasing them for on. Not an easy thing to do with push-switches!

Swap over the 0V and +5V connections to pins CP21 and CP20 so that PORTA pins RA0 to RA3 are biased to +VE, going low when switches SW0 to SW3 are pressed. Run the program again. You will find that the l.e.d.s respond as they did for TK3TUT12. Now run TK3TUT12 again and confirm that the l.e.d. results are the inverse of that previously seen with it.

Another use for COMF is in subtraction. This is a concept for experienced programmers and will not be demonstrated here. In a nutshell, the use of COMF allows addition to be used instead of subtraction while still achieving the desired objective. This technique can be easier in some instances than using the available subtraction commands.

The F suffix can be used with COMF instead of W, as with other files discussed. There is no command which allows the inversion of a byte once it is in W. If a byte within W needs inversion, it must be put out to a file, and then the COMF (FILE-NAME),W command given to bring it back into W.

EXERCISE 11

With these exercises, reconnect the +5V connection to CP21 and 0V to CP20.

11.1 If SWAPF was not available as a command, how would you write a routine which produced the same result (would RLF or RRF be suitable commands)?

11.2 Rewrite TK3TUT13 and TK3TUT14, putting the contents of W out to a file of any name (which you must equate at the beginning of the program), performing another COMF or SWAPF action, and then bringing it back into W for output to PORTB. Can PORTB be used as the temporary file store in these rewrites?

11.3. Write a routine that allows the nibbles of a byte to be put into separate files and each having a value no greater than H'0F' (decimal 15); there are several ways of doing it.

TUTORIAL 12 CONCEPTS EXAMINED

Generating an output frequency in response to a switch press

The use of two port bits set to different input/output modes

Command NOP

CONNECTIONS NEEDED

All Port B to all l.e.d.s.

Port A RA0-RA3 to switches SW0-SW3 (via CP19-CP16)

Port A RA4 connected as in Fig.3 (audio connection)

CP21 to +5V OUT

CP20 to 0V OUT

1μF capacitor C7 omitted (from hereon)

Preset VR1 set to minimum resistance (fully clockwise)

LISTING 15 - PROGRAM TK3TUT15

```
SOUND      MOVLW 80
            MOVWF NOTE
            MOVWF FREQ
GETKEY     BTSS PORTA,0
            GOTO GETKEY
            DECFSZ NOTE,F
            GOTO GETKEY
            MOVF FREQ,W
            MOVWF NOTE
            MOVLW B'00010000'
            ADDWF PORTA,F
            GOTO GETKEY
```

So far we have been outputting data to l.e.d.s, and at a comparatively slow rate. We have also been using one port as a switch input and the other port as the output. Here we examine how the same port can be used simultaneously for input and output via different bits. In doing so, we use sound as the medium by which we indicate the status of a switch, generating an audible frequency when it is pressed.

The 1μF capacitor used up till now for C7 should be omitted from hereon.

Connect a 330Ω resistor between RA4 and the +5V connection at CP21. Pin RA4 is an open-collector pin and this resistor biases it so that an output can be generated on it. Connect a 1μF capacitor with its positive lead on the junction of RA4 and the resistor. Connect the negative lead of the capacitor to the signal terminal of a jack socket that suits your personal (high-impedance) headphones (see Fig.3).

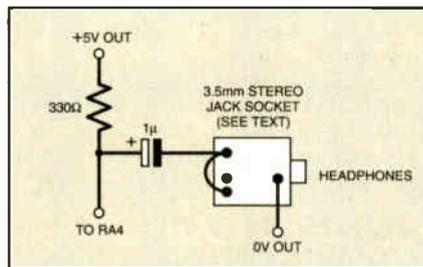


Fig.3. Audio output connections.

Do not connect a loudspeaker directly to this circuit as there is insufficient power to drive it.

Load TK3TUT15.HEX and press switch SW0 on and off. A frequency tone will be heard when the switch is pressed.

In the initialising statements at the head of the full TK3TUT15.ASM program, PORTA has been set with bits 0 to 3 as inputs and bit 4 as an output (MOVLW B'00001111', MOVWF TRISA). You should now recognise all the commands given in the heart of the program shown. Only a general commentary on what happens is now given.

On entry into the routine headed SOUND, a value of 80 is loaded into the files named NOTE and FREQ. The value is arbitrary as far as this demonstration is concerned. You may choose any other from 1 up to 255; the lower the value, the higher the frequency generated.

PORTA's status is monitored at GETKEY and the setting (logic 1) of PORTA bit 0 by switch SW0 is being looked for. Switch testing is repeated until SW0 is pressed, setting RA0 high.

When that occurs, file NOTE is decremented and its zero status tested. If it is not yet zero, the routine jumps back to the switch test.

When the switch has been pressed for long enough (mere thousandths of a second), NOTE will eventually reach zero, at which point the command MOVF FREQ,W is reached, followed by the fixed value of FREQ being reset into NOTE. Next, the value in PORTA has 16 (binary 00010000) added to it to increment the count at bit 4 (so alternating the bit between 0 and 1), and then there is a jump back to further switch testing.

For as long as switch SW0 is pressed, PORTA bit 4 will be periodically incremented. The speed at which the routine runs causes this bit to change at the audio frequency rate to which you are listening. If you adjust the rate setting preset, VR1, you will hear the change in the resulting frequency.

In a real-life situation, of course, the operating frequency of the system would normally be fixed. One frequency correction choice then is to change the value of FREQ.

There is, though, another factor that will affect the resulting audio frequency: the number of commands within the controlling loops. To illustrate the point, let's change the number of commands involved.

You may think that to add more commands would be difficult, what would they do which would not interfere in the completion of the loop? Well, there are several options, such as repeating some of the existing commands, MOVF FREQ,W for example, or MOVWF NOTE. Neither of these commands would actually change anything, except for the rate of operation. However, a tailor-made command is already available in the PIC's command codes which is intended for use where minor delay tactics are needed, command NOP.

COMMAND NOP

Command NOP simply stands for NO Operation. Responding to this command takes the PIC just as long as responding to any other single-cycle command but its response is to just do nothing!

This command, then, can be used here to slow down the resulting note frequency. Insert it immediately before DECFSZ NOTE,F. When running the amended program you will notice that a change in the output frequency has occurred.

EXERCISE 12

12.1. Experiment with different values for FREQ. What happens if you set FREQ to zero - does it stop a note being generated? Explain the result.

12.2. Experiment with more than one NOP command in the loop.

12.3. At which other places can you alternatively insert NOP, and is the frequency change still noticeable?

12.4. Are there any places where you cannot use NOP?

12.5. When the audio frequency is not being generated there is the likelihood that RA4 will be set low, so sinking current through the 330Ω resistor. Can the program be modified so that this cannot occur.

TUTORIAL 13

CONCEPTS EXAMINED

Command CALL
Command RETURN
Command RETLW

CONNECTIONS NEEDED

All Port B to all l.e.d.s.
Port A RA0-RA3 to switches SW0-SW3
(via CP19-CP16)
CP21 to +5V OUT
CP20 to 0V OUT
Preset VR1 set to minimum resistance
(fully clockwise)

LISTING 16 – PROGRAM TK3TUT16

```
LOOP CALL PROG1
      MOVWF PORTB
      GOTO LOOP
PROG1 MOVF PORTA,W
      RETURN
```

Before looking further into sound generation, there are several commands that we should examine. Three of those are associated with calling sub-routines: CALL, RETURN and RETLW.

Load TK3TUT16.HEX and experiment with pressing different combinations of switches SW0 to SW3 while observing PORTB's l.e.d.s.

COMMANDS CALL, RETURN AND RETLW

Programs can be written as a series of sub-routines which can be reached in one of three ways, directly by default (without being told to go there), via a GOTO command, or by a CALL command. (Routing following automatic detection of an interrupt event is another matter and is discussed later.)

We have shown several examples of the first two. Program TK3TUT4 (Tutorial 4) uses them both: the sub-routine LOOP1 is entered directly following the initialisation routine. LOOP2 is also entered directly from the end of LOOP1. Both LOOP1 and LOOP2 are then further accessed by GOTO commands.

However, a CALL command can be used if one routine needs to make use of another and then once that has been completed, for the program to jump back to continue from the command that follows the call. The use of sub-routines allows the same routine to be accessed from many other areas within the overall program, so saving on program space.

A second command always has to be used before the program returns to the calling origin. That command takes one of two forms, RETURN (which is an obvious command – return to where you came from) or RETLW (RETurn to where you came from with a Literal value held in W). There is a third return command, RETFIE, which we shall meet later in connection with interrupts.

A GOTO command can never be used to end a sub-routine call – the PIC will continue to expect a return command and, if repeated calls to a sub-routine are made without a RETURN or RETLW command, it will become confused and unpredictable

results could occur. For example, the following is “illegal”:

```
PROG1 CALL PROG2
      GOTO PROG1
PROG2 GOTO PROG1
```

This is “legal”, though:

```
PROG1 CALL PROG2
      GOTO PROG1
PROG2 RETURN
```

When the program returns from a CALL following a RETURN command, the contents of W are those which were put there by the last command which used W. Consequently, you can perform a complex sub-routine, end up with an answer in W and, using the RETURN command, return to the main program with that result still retained in W.

Command RETLW, though, returns to the main program with W holding the value which RETLW has acquired as part of that command. A literal value is always specified as part of the RETLW command, e.g. RETLW 127 or RETLW 0. That value replaces any other value within W and is the one which is held in W on the return to the calling point. The value may be expressed in decimal, hexadecimal, binary or as a “named” value equated during program initialisation.

To explain Listing 16 then, at LOOP the sub-routine at PROG1 is CALLED from where the value held in PORTA is moved into W. A return is made to the loop where the next command to be performed is MOVWF PORTB, after which the GOTO LOOP command again takes us back to CALL PROG1 again.

It is important to be aware that PICs have a limit to the number of calls that can be nested (calls being made from within calls). This is due to the PIC's Stack (the

area that monitors the return addresses when calls are completed) being limited to only eight address values. If the Stack receives more than eight addresses it will over-write the earlier ones, causing a program crash.

There is no way to read or write to the Stack or to determine how full it is. It is therefore imperative that if you are using nested calls then you must keep very careful track of how many you are using. In such cases consider whether you could achieve the same result by using GOTO commands for some of the calls, or by returning to the previous calling routine before making the next call.

Run program TK3TUT16 and confirm that l.e.d.s LD0 to LD3 respond as expected to the pressing of the four switches.

EXERCISE 13

13.1. Rearrange TK3TUT16 so that reading PORTA is in the main loop and outputting data to PORTB is in the called routine.

13.2. Try adding other commands in the subroutine, such as AND or ADD.

13.3. Use RETLW as the final statement in the subroutine, using any literal value of your choice, verifying its operation!

TUTORIAL 14

CONCEPTS EXAMINED

Tables
Register PCL (again)
Register PCLATH

CONNECTIONS NEEDED

All Port B to all l.e.d.s.
Port A RA0-RA3 to switches SW0-SW3
(via CP19-CP16)
CP21 to +5V OUT
CP20 to 0V OUT
Preset VR1 set to minimum resistance
(fully clockwise)

LISTING 17 – PROGRAM TK3TUT17

```
BANK0
GOTO LOOP
TABLE ANDLW B'00001111' ; AND W with 15
      ADDWF PCL,F ; ADD to PCL
      RETLW 255 ; 0 11111111
      RETLW 1 ; 1 00000001
      RETLW '5' ; 2 00110101
      RETLW 0 ; 3 00000000
      RETLW 31 ; 4 00011111
      RETLW 193 ; 5 11000001
      GOTO OTHER ; 6 00100000
      RETURN ; 7 00000111
      RETLW B'10101010' ; 8 10101010
      RETLW H'C7' ; 9 11000111
      RETLW 'A' ; 10 01000001
      RETLW 65 ; 11 01000001
      RETLW 'B' ; 12 01000010
      RETLW 'x' ; 13 01111000
      GOTO OTHER1 ; 14 10001110
                        ; or 10011110
                        ; 15 00000000
LOOP MOVF STORE,W
      RETURN
      MOVF PORTA,W
      CALL TABLE
      MOVWF PORTB
      GOTO LOOP
OTHER RETLW STORE
OTHER1 MOVLW 128
      ADDWF PORTA,W
      RETURN
```

The use of look-up tables, whose tabulated commands or values are determined by a value set elsewhere in a program, is of enormous benefit. Tables depend on the use of the Program Counter (PCL – discussed in Tutorial 4) and the commands CALL, RETLW, RETURN and GOTO. They can be used with other calls within them, but this usually requires making additional commands prior to accessing the table. When a table is accessed, the value already held in W is added to PCL and causes the program to jump forward by the same number of program commands as are in W. The command at the jump address is then performed.

Load TK3TUT17.HEX, run it and experiment by pushing switches SW0 to SW3 in any combination while observing the l.e.d.s. on PORTB. The l.e.d.s should come on according to the binary value shown in the comments column of Listing 17, i.e. all l.e.d.s will be on if no switch is pressed.

In TK3TUT17, the instruction BANK0, although individually stated in the extract shown here, follows the initialisation in the normal way. After initialisation, and before any tables are encountered, the command GOTO LOOP bypasses the table commands. Failure to bypass them would cause confusion to the PIC.

At the first command of LOOP, switch data from PORTA is brought into W. The CALL TABLE command then routes the program to the first command within the table, ANDLW B'00001111' (decimal 15).

The AND command is essential here to limit the possible value which can be added to the Program Counter (PCL). Although only the four switches SW0 to SW3 are in use, in another situation another switch might be connected to pin RA4, and so the binary value at PORTA could be greater than 15 (all five switches on = 11111 binary = 31 decimal) and we also know that the number of "routing" commands within the table is 16 (0 to 15). If the table were to be given a value greater than 15, the additive PCL address jump would cause the program to jump beyond the boundary permitted, with unpredictable results. The ANDing could, alternatively, have been done immediately prior to CALL TABLE.

OMITTING THE AND COMMAND

There are circumstances when the AND statement is not needed. For example, if it is known that the value present in W on the call can never be greater than five, AND would not be needed and the table could be limited to six jump options only (remember that 0 counts as a jump value). However, if in doubt about the maximum value that could be in W, always use a value limiter of some sort (techniques other than AND can be used).

This limiting is especially necessary when a program is being developed since errors in other regions of the program could result in an excessive W value, resulting in a system "crash". When consequential crashes of this type occur, it can be difficult sometimes to establish the primary cause of the problem which is elsewhere.

At the command ADDWF PCL,F the ANDed value remaining in W is added to the Program Counter and the command

within the table which corresponds to the new address is performed. For clarity, W's entry value is shown alongside each of the 16 table jumps.

If the W value is 0, then the command performed within the table is the first one (0), RETLW 255. As instructed, the program now returns to the calling point with 255 in W. If the value added to PCL is 5, the command performed is RETLW 193. In all instances of the RETLW command within the table, the stated literal value is copied into W and the return is made. You will see that, as with other xxxLW commands, the literal value can be expressed in decimal, hexadecimal, binary or equated name values.

What you have not encountered yet is the use of characters in single quotes. Any standard ASCII character from the full 0 to 255 set can be entered in this way, numbers, upper or lower case letters, symbols, etc.

During assembly, any character within the quotes is translated into its ASCII value and it is that value which is returned in W. (In reality, a lot of the ASCII codes will not be available on your keyboard.) Note that only the "apostrophe" type of quote is permitted ('), that normally residing on your keyboard between the semicolon (;) and the hash symbol (#). The double-quote symbol (") is not permitted, nor is the "left-hand" single quote (') found on many keyboards (to the left of numeral 1 and the exclamation mark).

Four examples of "quoted" characters are shown in the table. Quoted '5' will be translated as ASCII 53 (not as the value 5); 'A' and 'B' will become ASCII 65 and 66 respectively; lower case 'x' will be returned as ASCII 120. You will find this conversion technique invaluable when compiling tables of messages for output to an alphanumeric l.c.d. (Tutorial 22).

The simple command RETURN at jump 7 will cause the current value already within W to be returned; i.e. the value on the switches after it has been ANDed with 15. It may not be immediately clear what this action would achieve, but an example is given in Tutorial 15.

TABLED GOTO

There are two examples of a tabled GOTO command in Listing 17, at jumps 6 and 14. These cause the program to jump to the sub-routines named, OTHER and OTHER1. At OTHER, the command MOVLW STORE is executed, after which the program returns to the calling program (not back into the table) with the equated address value of STORE (see full ASM listing).

The routine at OTHER1 shows how a table jump can go to a routine in which more than one action can be performed, in this case adding 128 to the value at PORTA, then returning as usual. Any action can be performed here, on any file, for any purpose, and there is no limit to the number of commands performed before the final RETURN (within the program space available, of course).

The command at table jump 15 is interesting. It looks as though a command other than GOTO, RETURN or RETLW is being performed. However, this jump is the last in the table and so it is perfectly legitimate to perform any other action(s) here since

the program will automatically follow them through without interfering with the normal table action.

Here the simple action of getting the value held in STORE is performed, immediately followed by a RETURN. Note that the value returned from jump 15 may not necessarily be zero as shown, since STORE has not been given any value when the program is initialised and so could take any random value between 0 and 255.

What would cause table difficulties is if the command at a mid-table jump did not allow an immediate exit from the table. For example, consider the following mid-table jump commands:

```
RETLW 0           ; 3
MOVWF STORE,W    ; 4
RETLW 193        ; 5
```

Jump 3 would be OK, so would jump 5. Jump 4, though, would perform MOVWF STORE,W (bringing the value within STORE into W), but the exit route for that command is via the address of jump 5, which is RETLW 193, immediately replacing the value acquired in jump 4 with the value 193. Not very helpful!

Mind you, the commands GOTO or RETURN could be at jump 5, which would be fine for jump 4, but what of the result of actually jumping to jump 5, would you necessarily want to just RETURN or GOTO?

One could, perhaps, envisage a table consisting only of INCF STORE,F commands, for example, in which the number of increments generated would be the equivalent of the entry point value of W. But the use of a loop or an addition would, though, probably be more appropriate to that requirement.

It is legitimate to GOTO a table, or arrive at it from the end of another routine, but in this case it may be necessary to only exit the table by GOTO commands. Unless you are already in the middle of a call, "return" commands will cause a program crash.

Advanced use of Tabled GOTOs is discussed by Malcolm Wiles in his feature *PIC Macros and Computed GOTOs of EPE* Jan '03 – this is on the PIC Resources CD-ROM.

TABLE SPAN

There is a significant restriction on tables which must not be overlooked. Because of the way in which the Program Counter handles the calls to and from tables, all of the tabulated data must be contained within the first 256 addresses of the program (0 to 255). Not a single jump address must fall outside this block (except as discussed in a moment).

When writing software, it can sometimes be difficult, depending on program structure, to ascertain from the code editing program (word-processing software) whether or not the tables overlap beyond the block. If this is the case, come out of the WP package and assemble the code. Don't send it to the PIC, but come back into the WP and examine the .LST file that has been generated for the program as it now stands. Look at the address numbers (in the third column as you saw earlier in Listing 3A) and see if any part of the table(s) occurs beyond the H'00FF' hex address (decimal 255). Any overlap beyond (even H'0100' – 256 decimal) is unacceptable.

PCLATH

Advanced programmers do have a way round the table block limit should they need to find one. It is through the use of the PCLATH register which allows additional 256 byte blocks to be used elsewhere in the program. This command will, of course, be useful if the total number of tabulated items is greater than 256. Being an advanced programmer's command, we shall not illustrate PCLATH here. Interested readers are referred to John Waller's *Using the PIC's PCLATH Command* in *EPE* July '02 – again it is on the PIC Resources CD-ROM.

With both the "normal" and PCLATH modified table areas there is no limit to the number of tables within them, and the calling routines can be anywhere within the program, start, middle or end. It is perfectly legitimate to have sub-routines placed between different tables, but remember that their length also consumes part of the 256 byte block.

EXERCISE 14

14.1. Write a routine that calls a table which multiplies a binary number by seven. Use the switches as the source of that number (pressing more than one switch as necessary) and restrict it to

between 0 and 7, showing the results on PORTB's l.e.d.s.

14.2. Create a table to convert the binary numbers generated by the switches (multiple pressing again) to a BCD (binary coded decimal) format; tens of units in the left four l.e.d.s, units in right four l.e.d.s. (If you are not familiar with BCD, think about what it might mean and how it might be shown on l.e.d.s. The use of BCD formats is discussed in Tutorial 19.)

TUTORIAL 15 CONCEPTS EXAMINED

Using four switches to create four different notes

Use of a table to selectively route program flow

CONNECTIONS NEEDED

All Port B to all l.e.d.s.

Port A RA0-RA3 to switches SW0-SW3 (via CP19-CP16)

Port A RA4 connected as in Fig.3 (audio connection)

CP21 to +5V OUT

CP20 to 0V OUT

Preset VR1 set to minimum resistance (fully clockwise)

The program in Listing 18 allows any one of four notes to be played by the switches on PORTA RA0 to RA3 (SW0 to SW3). As with Tutorial 12, the audio output is on RA4. Reconnect your audio monitor, load TK3TUT18.HEX and press some switches. You will immediately notice that the "note" frequencies belong to no musical scale known to man. There is nothing we propose to do about that, we are interested in more mundane matters!

The object of this program is to show the use of a table and several sub-routines which allow four notes to be played (singly) depending on the switch presses. Multiple pressing of switches is ignored.

To conserve page space only one note routine is shown. The others are identical except that they process different notes and PLAY4 omits the GOTO OUTPUT command since OUTPUT immediately follows its final command. You will see the now-familiar commands in the GETKEY and PLAY1 routines. The table should seem recognisable as well.

As in Listing 17, when the program first starts, the table is bypassed and the first main command is at PRESET. Here the frequency values for the four notes are set up as NOTE and FREQ variables.

Switches are monitored as before and calls made to the table. There, routing to different notes occurs only if individual switches are pressed (jumps 1, 2, 4, 8). Any other switch setting, including none, results in a return to the calling point.

When the selected note routine has been processed, a jump to OUTPUT occurs from where the output pin RA4 is toggled, causing a note to be heard. A RETURN command follows, returning the program to the calling point.

Even from this cut-down version of the program, it is apparent that a lot of commands are involved and that many of them are similar (PRESET) or even identical (PLAY by four).

You will also see that only five calls to the table achieve useful results. The others

are wasted but have to be included because four switches can generate 16 permutations of settings. You can't just say to the musician "never press more than one key at once", you have to allow for human fallibility. If an error can be made by the program user, it will at some time *be* made – Murphy's Law. Programmers must always think about what *might* happen and write the software accordingly (making it "user-friendly" is another way of putting it!).

The programmer must usually also think about program speed and program compactness. Sometimes they can both achieve the same result, but not always. However, for the sake of discussing program options available, in a moment we'll look at how TK3TUT18.ASM could be written in another way. First an exercise for you:

EXERCISE 15

15.1. Try to change the frequency values in TK3TUT18.ASM to produce notes that are somewhat more harmonically related! What problems do you come up against?

TUTORIAL 16 CONCEPTS EXAMINED

Indirect addressing

Using unnamed file locations

Register FSR

Register INDF

LISTING 18 – PROGRAM TK3TUT18

```
TABLE    ANDLW B'00001111'
         ADDWF PCL,F
         RETURN          ; 0
         GOTO PLAY1     ; 1
         GOTO PLAY2     ; 2
         RETURN          ; 3
         GOTO PLAY3     ; 4
         RETURN          ; 5
         RETURN          ; 6
         RETURN          ; 7
         GOTO PLAY4     ; 8
         RETURN          ; 9
         RETURN          ;10
         RETURN          ;11
         RETURN          ;12
         RETURN          ;13
         RETURN          ;14
         RETURN          ;15

PRESET   MOVLW 80
         MOVWF NOTE1
         MOVWF FREQ1
         MOVLW 110
         MOVWF NOTE2
         MOVWF FREQ2
         MOVLW 140
         MOVWF NOTE3
         MOVWF FREQ3
         MOVLW 160
         MOVWF NOTE4
         MOVWF FREQ4
GETKEY   MOVF PORTA,W
         CALL TABLE
         GOTO GETKEY
PLAY1    DECFSZ NOTE1,F
         RETURN
         MOVF FREQ1,W
         MOVWF NOTE1
         GOTO OUTPUT
(PPLAY2 to PLAY4 are similar to PLAY1)
OUTPUT  MOVLW B'00010000'
         ADDWF PORTA,F
         RETURN
```

LISTING 19 – PROGRAM TK3TUT19

```
TABLE    ANDLW B'00000011'
         ADDWF PCL,F
         RETLW 10
         RETLW 20
         RETLW 40
         RETLW 80

SETUP    MOVLW 4
         MOVWF LOOPA
         CLRF COUNT
         MOVLW NOTE1
         MOVWF FSR
SETUP1   MOVF COUNT,W
         CALL TABLE
         MOVWF INDF
         INCF FSR,F
         INCF COUNT,F
         DECFSZ LOOPA,F
         GOTO SETUP1
GETKEY   MOVF PORTA,W
         ANDLW B'00001111'
         MOVWF STORE
         MOVLW 4
         MOVWF LOOPA
ROTATE   BTFSZ STORE,3
         GOTO PLAY
         BCF STATUS,C
         RLF STORE,F
         DECFSZ LOOPA,F
         GOTO ROTATE
         GOTO GETKEY
PLAY     DECF LOOPA,W
         ADDLW NOTE1
         MOVWF FSR
         DECFSZ INDF,F
         GOTO GETKEY
         DECF LOOPA,W
         CALL TABLE
         MOVWF INDF
OUTPUT  MOVLW B'00010000'
         ADDWF PORTA,F
         GOTO GETKEY
```

CONNECTIONS NEEDED

All Port B to all l.e.d.s.
Port A RA0-RA3 to switches SW0-SW3 (via CP19-CP16)
Port A RA4 connected as in Fig.3 (audio connection)
CP21 to +5V OUT
CP20 to 0V OUT
Preset VR1 set to minimum resistance (fully clockwise)

Time now to examine a concept that allows us to access generalised routines which can manipulate file values without actually specifying the file names within them. This concept is called "Indirect Addressing". It also has profound implications for the ability to minimise the number of sub-routines required by a program. Program TK3TUT19, which uses the technique, will then be discussed and demonstrated.

Indirect Addressing allows the use of generalised routines which do not apply to any specific files. The file which the routine accesses is specified prior to entry into the routine and can be changed at will to suit different aspects of the program.

COMMANDS FSR AND INDF

The two key commands (or, rather, "file registers") in Indirect Addressing are FSR (File Special Register) and INDF (INDirect File). The idea of Indirect Addressing is that you place the address of the file that you wish to access in file FSR. Commands to access the specified file address are then made via file INDF.

Not only does this facility allow the same routine to be applied to different calling routines, it also allows a loop to access a sequence of files without having to specify their individual addresses other than that for one of them in the sequence.

In the following example, assume that we have a sequence of files between addresses H'20' and H'2F' (16 files). Let's call the first file FILE0. Its address will have been equated at the head of the program in the usual way. However, provided we assume the next three addresses to be reserved for 15 files which are consecutive to FILE0, we do not have to give them names unless we actually need to use the names in the body of the program. Even then the names could be anything we like; they do not have to be called FILE1, FILE2 etc., unless we wish to.

Suppose, for example, we wished to clear all 16 of these files prior to another routine and that we shall do it in ascending order using a loop. Prior to entering the loop we get the address of the first file, in this case FILE0, copy it into FSR and reset the loop counter, let's call it LOOPA:

```
MOVLW FILE0
MOVWF FSR
CLRWF LOOPA
```

Now all we need to do is use the following simple routine:

```
RESET CLRWF INDF,F
        INCF FSR,F
        INCF LOOPA,F
        BTFSS LOOPA,4
        GOTO RESET
```

Command CLRWF INDF,F clears the file whose address is held in FSR. Next, INCF FSR,F increments the value held by FSR, in other words FSR is incremented to point to the next file we wish to clear (FILE0 in the first instance of the loop, FILE1 in the next). Next, we increment the loop counter, INCF LOOPA,F, and test its bit 4 (BTFSS LOOPA,4) to see if a count value of 16 (00010000) has been reached (remember we started at 0). If the count is not yet 16, the loop is repeated, GOTO RESET. If the count equals 16, the next command after GOTO RESET is performed, whatever that might be in a full program. Another way of doing it (and there are several ways) is:

```
MOVWF FILE0
MOVWF FSR
MOVLW 16
MOVWF LOOPA
RESET CLRWF INDF,F
        INCF FSR,F
        DECFSZ LOOPA,F
        GOTO RESET
```

You can also use similar constructions to access a sequence of table values (from anywhere within that table) and add them to the values within a sequence of indirectly addressed files, keeping the maximum resulting addition to less than the maximum number of temporary registers that the PIC provides.

In the following example (nothing directly to do with TK3TUT19), the first address required in the table is at jump 3. This value is first placed into COUNT (MOVLW 3, MOVWF COUNT). We want to start adding the acquired table value to the file starting six bytes beyond FILE0 so the value of 6 is then added to the address of FILE0 and the result placed into FSR (MOVLW 6, ADDLW FILE0, MOVWF FSR). We also want to perform the action five times, once for each note, so a loop (LOOPA) is set up with the initial value of 5 (MOVLW 5, MOVWF LOOPA).

The real action then starts at label GETVAL. The current value held in COUNT is copied into W (MOVWF COUNT,W). The table is called (CALL TABLE) and value held in the table at the location indicated by the value in W is retrieved from the table, being automatically placed into W. The value from the table now in W is then added to the value in the file held via INDF and pointed to by FSR, and the result is stored back into the same file (ADDWF INDF,F). File FSR is now incremented (INCF FSR,W), so incrementing the address of the file held via INDF. Count is incremented (INCF COUNT,F), and LOOPA is decremented. If LOOPA is not yet zero the process repeats.

```
MOVLW 3
MOVWF COUNT
MOVLW 6
ADDLW FILE0
MOVWF FSR
MOVLW 5
MOVWF LOOPA
MOVWF COUNT,W
CALL TABLE
ADDWF INDF,F
INCF FSR,F
INCF COUNT,F
DECFSZ LOOPA,F
GOTO GETVAL
```

INDIRECT ADDRESSING DEMONSTRATED

In the following worked example, part of whose program is shown in Listing 19, we demonstrate how Indirect Addressing allows generalised file accessing routines to be used, how a table can help in that process, and how it helps code to be compacted to achieve more actions within the space available. Because only four switches are available, the program is limited to four notes, but if more switches were to be added somehow, the process could readily be extended to suit.

With your audio monitor still connected, load TK3TUT19.HEX and play with the four push-switches on PORTA (SW0 to SW3). You will find that all four switches produce "notes", but not musically tuned, though! The technique used is, in effect, the same as that demonstrated in TK3TUT18. There are, though, some notable (no pun!) differences:

First, if you look at the full listing on your disk, you will see that in the initialisation, we have only equated NOTE1 and there is no mention of FREQ1 etc. Yet, we are actually using four files to behave as NOTE1 to NOTE4 and we use a table instead of FREQ1 to FREQ4.

What we have done (as discussed a moment ago) is to consider a block of consecutive file addresses to be allocated to NOTE1/NOTE4, starting at H'20'. To remind us at some future time, there is a comment alongside NOTE1 to this effect in the full disk listing. The next address which we specify cannot, therefore, occur until the fifth byte later, at H'24', where LOOPA is equated. Any consecutive block of four bytes could have been used.

As seen in the full program and the extract in Listing 19, a table has four values in it and an AND command limits the jump span from zero to three. The values shown are the tuning values which will be accessed periodically throughout the program while it is running.

INDIRECTION

Routines SETUP and SETUP1 make use of the indirect addressing facility to set the initial (FREQ) values into the four notes. Next comes routine GETKEY in which the status of the four switches is obtained in the usual way. There are 16 possible combinations of the switches and we only want four of them, those for any single switches being pressed.

We could, of course, not use a table but simply test each bit of PORTA in turn and use GOTO statements to obtain data about which note should be played and which note reset value is needed. Instead, though, for the sake of demonstration, a different technique is used, converting the 4-bit PORTA value to a 2-bit value, covering four possible combinations rather than 16.

PORTA's value is ANDed with B'00001111' and copied into STORE, and a loop set for a maximum of four operations. Up to four rotate left (RLF) actions can then be called in routine ROTATE, and the value of STORE bit 3 tested. Each bit of STORE corresponds to a separate switch, so the rotation allows all four switches to be tested. If a 1 is found during the rotation, the value of the loop

corresponds to the switch in question and a jump is made to the play routine. If a zero is found, then no switches are pressed and no note play action occurs.

In the PLAY routine, the loop value (LOOPA) is decremented while being moved into W (the loop value will be between 4 and 1 but for program ease we need a value between 3 and 0). The value of W is added to the address of NOTE1 and the answer is put into the indirect address register FSR. The note now pointed to by FSR is decremented via INDF and if the result is not zero, a return to GETKEY is made.

A zero result causes the value of LOOPA to again be decremented into W and then the table is called, returning with the reset value for the note in use, which is put into it via INDF. As we have seen before, the output value at PORTA RA4 is then incremented and a jump back to GETKEY occurs.

Had this whole operation been programmed as separate routines for each note, its length would have been considerably greater, as in the previous example of TK3TUT18; indirect addressing, bit rotation and a table have changed that. (Consider the length that would have been required if we were using eight switches for eight notes – a situation that would have also brought up the problem of a table that was greater than 256 commands!) We shall use indirect addressing again later.

EXERCISE 16

16.1. In Program TK3TUT19, priority has been given to switches in descending order (test bit 3). How would you rewrite to give priority in ascending order?

16.2. If you wanted one of the switches to be ignored, what extra command(s) would be needed, and where? When considering where, think of the number of times the situation has to be checked for between each input of PORTA's value, remembering that each command processed wastes valuable time.

16.3. Is the AND command at the head of the table actually necessary?

16.4. As the program stands, there is one extra file name used than needs to be; which file could be used in two situations?

16.5. Also, with careful thought, parts of the program could be slightly rewritten to save at least seven commands. Can you spot how this could be done? Question all aspects, from initialisation downwards (see also the full listing).

(Whilst the SETUP routine could be heavily rewritten to save four of these commands, in a real programming situation, unless you are short of program space, it is better to concentrate on saving commands in routines that are being called frequently, so significantly increasing the speed of operation. SETUP is only used once, and so has no affect on the loop speed.)

TUTORIAL 17 CONCEPTS EXAMINED

Command XORLW
Command XORWF
Command IORLW
Command IORWF
Tone modulation

LISTING 20 – PROGRAM TK3TUT20

```
GETKEY   MOVF PORTA,W
          ANDLW B'00001111'
          XORLW B'11111010'
          MOVWF PORTB
          GOTO GETKEY
```

CONNECTIONS NEEDED

All Port B to all l.e.d.s.
Port A RA0-RA3 to switches SW0-SW3 (via CP19-CP16)
Port A RA4 connected as in Fig.3 (audio connection)
CP21 to +5V OUT
CP20 to 0V OUT
Preset VR1 set to minimum resistance (fully clockwise)

In a moment, we shall come down to a somewhat simpler audio program, in which we illustrate how two tones can be created, one modulated, the other fixed. Both tones could find use in, for example, a simple intruder alarm. Also to be illustrated is how the combined status of two or more switches on a port can be tested using the XOR (Exclusive-OR) command. This allows us to take one action only if all the specified switches are on simultaneously, otherwise taking another action. First, let's examine the XOR command on its own.

COMMAND XOR

The command XOR checks for "equality" between two numbers. There are two commands, XORLW (XOR Literal with W) and XORWF (XOR W with value in specified File). The latter is followed by the file name, a comma, and the destination (W or F), e.g. XORWF STORE,W and XORWF STORE,F.

Probably you know that in electronics there are XOR gates included in the digital logic chip families, and you will no doubt have read descriptions of truth tables relating to just two inputs of an XOR gate (two bits):

```
0 XOR 0 = 0
0 XOR 1 = 1
1 XOR 0 = 1
1 XOR 1 = 0
```

As far as a PIC's XOR function is concerned, the result of XORing two bytes of eight bits is the condition being checked. It is easier here to show the principle by means of switches and l.e.d.s rather than by truth tables. To do this we should really use eight switches on one port and eight l.e.d.s on the other. However, since PORTA has only four switches connected to it, we shall just use a 4-bit number to illustrate the principle, via four l.e.d.s on PORTB.

The basic program we shall use is shown in Listing 20. Run program TK3TUT20.HEX and play with PORTA's switches. You will find that when no switches are pressed, PORTB l.e.d.s LD0 and LD2 are off, and LD1 and LD3 are on, as are LD4 to LD7. When switch SW1 and SW3 are pressed, they turn off their respective l.e.d.s (LD1 and LD3). Switches SW0 and SW2 turn on their l.e.d.s (LD0 and LD2) when pressed.

In this listing, the value on PORTA is input as usual. The next command

(ANDLW B'00001111') is necessary to this demonstration since we only want to use the first four bits of PORTA. If PORTA had eight bits that could be used, the AND command would be omitted. The status of each switch is being XORed with the respective bit in the statement XORLW B'11111010'; switch 0 with bit 0, switch 1 with bit 1, etc.

If any bit of PORTA is equal to that of the same bit in the XOR command, the same bit in the W register will be cleared. Thus two zeros will produce a 0, and two 1s will produce a 0. If the bits are dissimilar (1 and 0) the W bit is set (1). The reason that the four lefthand l.e.d.s are on is that bits 4 to 7 from the AND command and bits 4 to 7 from the XOR command have resulted in four non-equalities.

Suppose that the switches produce binary number 0111, the ANDed result in W is 00000111, the sequence of events is:

```
MOVF PORTA,W   answer = xxxx0111
ANDLW B'00001111' answer = 00000111
XORLW          11111010
                answer = 11111101
```

Bits that are equal to their counterparts have their corresponding l.e.d.s turned off, those that are *not* equal have their l.e.d.s turned on. Take another example:

```
MOVF PORTA,W   answer = xxxx0010
ANDLW B'00001111' answer = 00000010
XORLW          00000010
                answer = 00000000
```

Here each bit is equal to its counterpart, therefore all l.e.d.s are turned off, i.e. a zero result has occurred and, importantly, the Zero flag will have been set accordingly. Therefore, we can check for equality by checking the Zero flag following an XOR command. Non-equality clears the flag, equality sets it. Consequently, following an XOR command you simply check STATUS,Z and route accordingly.

LISTING 21 – PROGRAM TK3TUT21

```
GETKEY   MOVF PORTA,W
          ANDLW B'00001111'
          XORLW B'00001010'
          MOVWF PORTB
          BTFSC STATUS,Z
          BSF PORTB,7
          GOTO GETKEY
```

Let's use l.e.d. LD7 to illustrate this, turning it on if equality exists, turning it off if it doesn't. Any bit between 0 and 3 which is equal to the same XOR bit will have its corresponding l.e.d. turned off, otherwise its l.e.d. will be on. Load TK3TUT21.HEX and press PORTA switches SW0 to SW3 to observe this in action. Pressing SW3 and SW1 together causes LB7 to come on. The commands are shown in Listing 21.

COMMAND IOR

Although we shall not meet it until later (Tutorial 21), it is opportune to mention now that there is an "ordinary" OR command available. It is more correctly termed "Inclusive-OR" (as opposed to Exclusive-OR). It has two versions, IORLW

LISTING 22 – PROGRAM TK3TUT22

```

ENTRY      MOVLW 80
           MOVWF NOTE
           MOVWF FREQ
           MOVLW 128
           MOVWF MODLAT
           MOVLW 64
           MOVWF DELAY
GETKEY     MOVF PORTA,W
           ANDLW B'00000011'
           XORLW B'00000011'
           BTFSC STATUS,Z
           GOTO GETKEY
           DECFSZ NOTE,F
           GOTO GETKEY
           MOVF FREQ,W
           BTFSC PORTA,1
           GOTO OUTPUT
           DECFSZ DELAY,F
           GOTO GK2
           BSF DELAY,6
           DECFSZ MODLAT,F
           GOTO GK2
           BSF MODLAT,7
           ADDWF MODLAT,W
           MOVWF NOTE
           MOVLW B'00010000'
           ADDWF PORTA,F
           GOTO GETKEY

GK2
OUTPUT

```

(Inclusive OR Literal with W) and IORWF (IOR W with value in specified File). The latter is followed by the file name, a comma, and the destination (W or F), e.g. IORWF STORE,W and IORWF STORE,F.

MODULATION

The use of XOR in a practical situation is illustrated in Listing 22. Temporarily swap over the connections to CP20 and CP21 so that RA0 to RA3 are biased normally high, going low when pressed. Reconnect the audio output.

Load TK3TUT22.HEX, press any switches SW0 to SW3, but principally use switches SW0 and SW1 since these are the ones coded to be active.

Listening to the output from PORTA, you will find that switch SW0 controls a static tone and SW1 controls a modulated (ramped) tone. As you will have heard, the tone starts at a low pitch, ascends and then jumps back low again, repeatedly. Adjust VR1 until this fact is more obvious. All other switches are ignored. Look at the program's listing.

As with earlier tone generation examples, a starting value is loaded into NOTE and FREQ, then a modulation starting value is loaded into MODLAT, and a delay value into DELAY, after which the GETKEY loop is entered. Here the switch settings on PORTA are read and ANDed with 00000011 to extract the status of switches SW0 and SW1. The answer is XORed with the same value to check for equality. If neither switch is pressed, no further action is required and the routine jumps back to GETKEY.

We are looking for the situation in which either of the two switches is pressed. We could do it simply by bit testing (indeed, it would be easier!), but part of the aim of this demo is to show a use of XOR. When either switch is pressed, NOTE is

decremented and checked for zero and reset as appropriate, as before.

When zero is encountered, if switch SW1 is pressed, the DELAY counter is decremented, if it is zero, DELAY is then reset to 64 (BSF DELAY,6), the value of MODLAT is added to the NOTE reset value and the value of MODLAT itself is then decremented. When MODLAT reaches zero, it is reset to 128 (BSF MODLAT,7). The OUTPUT routine is common to both switch routings.

Note how bit values of MODLAT and DELAY are set to reset these counters to their original values. This works because both values are known to have reached zero.

EXERCISE 17

17.1. Experiment with different settings for FREQ, DELAY and MODLAT

17.2. How would you change the coding to respond to two other switches instead, e.g. SW2 and SW3?

17.3. How would you reverse the ramp to create a rising tone rather than a falling one?

17.4. The addition of a third switch would allow tones to be switched for rising, falling or fixed. Can you write the program for it?

17.5. Can you add another routine which would create a triangular modulation pattern (rising tone, followed by falling, followed by rising, and so on)?

TUTORIAL 18 CONCEPTS EXAMINED

OPTION register
INTCON register
TMR0 register
Command OPTION_REG
Command INTCON

LISTING 23 – PROGRAM TK3TUT23

```

MAIN     CLRf PORTA
           CLRf PORTB
           BANK1
           CLRf TRISA
           CLRf TRISB
           MOVLW B'10000000'
           MOVWF OPTION_REG
           BANK0
           CLRf RATE
           MOVLW 8
           MOVWF COUNT
           BCF INTCON,2
           BTFSS INTCON,2
           GOTO MAIN
           BCF INTCON,2
           MOVLW B'00010000'
           ADDWF PORTB,F
           BTFSS STATUS,C
           GOTO MAIN
           DECFSZ COUNT,F
           GOTO MAIN
           BSF COUNT,3
           INCF RATE,W
           ANDLW 7
           MOVWF RATE
           MOVWF PORTB
           BANK1
           IORLW B'10000000'
           MOVWF OPTION_REG
           BANK0
           GOTO MAIN

```

Command TMR0
Use of internal timer

CONNECTIONS NEEDED

All Port B to all l.e.d.s.
Port A RA0-RA3 to switches SW0-SW3 (via CP19-CP16)
CP20 to +5V OUT
CP21 to 0V OUT
Preset VR1 set to maximum resistance (fully anti-clockwise)

The PIC16F84 has one special register reserved for use as an 8-bit timer, TMR0 (Timer 0). It divides its input frequency by 256 and can be both written to and read from. In most situations, though, it is unlikely that you will need to use the read/write facility, but note that if TMR0 is written to, the timer is inhibited from counting for two clock cycles.

Probably more useful than writing to TMR0 is to use its output as it occurs naturally at the 1:256 division rate, and then to use the prescaler to subdivide that rate as required. The prescaler divides its input pulses by presettable powers of two. There are eight possible division ratios which are set via bits 0, 1 and 2 of the OPTION register. When used with TMR0, the prescaler division ratios are 1:2, 1:4, 1:8, 1:16, 1:32, 1:64, 1:128 and 1:256.

The prescaler can alternatively be allocated for use with the Watchdog Timer (WDT), in which mode each of these ratios is halved (minimum is thus 1:1 and maximum is 1:128) – more on this later.

OPTION NAMING

Note that the OPTION register should not be equated as such since Microchip previously had a command actually named OPTION and use of this term in an ASM file assembled by MPASM causes an error condition. Consequently it is preferable that the register should be equated as OPTION_REG (Microchip's equated term in their INC files). You may still sometimes come across the equated name OPTION, or even OPHUN instead.

(It should also be noted that bit 7 of the OPTION register controls the PIC's Light-pullups facility and should be set high to turn it off, as in Listing 23 – this facility is discussed separately later.)

We commented earlier that the PIC effectively runs at one quarter of the input clock frequency at pin 16 (OSC1/CLKIN). When TMR0 is used as an internal timer, the pulses it counts also occur at one quarter of the clock frequency. So, if the clock frequency (set by a crystal oscillator, perhaps) is running at 3.2768MHz, TMR0 will count at 819200Hz and its 1:256 roll-over rate will be 3200Hz. This rate is then divided by the ratio set into the prescaler. If we divide by 32, for example, we obtain the convenient rate of 100Hz.

In TMR0 mode, when the prescaler rolls-over to zero, a flag is set in the INTCON register, at bit 2. The setting of this bit can be used as an interrupt (see Part 3) which automatically routes the program to another specified routine, irrespective of which routine is currently being processed, returning to the same point after the interrupt procedure has been finished. The interrupt can also be turned off and INTCON bit 2 read by the

program to establish its status, taking action accordingly.

TIMER SUB-DIVISION

Using the timer and the prescaler, you can specify that some actions will only be performed at specified sub-divided values of the clock frequency. Amongst other things, this allows the PIC to be used as a real-time clock, a function towards which we now progress.

First, let's illustrate the effect of setting different prescaler ratios and, using the l.e.d.s on PORTB, show what happens. Load TK3TUT23.HEX and run it. Set VR1 to full anti-clockwise rotation (slowest rate). In this program we read the status of INTCON bit 2 rather than using the interrupt facility (discussed in Tutorial 27).

Initially, you will see a fairly fast binary count occurring on PORTB's l.e.d.s LD3 to LD7. It is created with the timer "in-circuit" with the prescaler set for a minimum division ratio of 1:2. This is because OPTION_REG bits 0 to 2 are set to 000, a value which is shown on LD0, LD1 and LD2 – all off initially.

This rate of counting continues for eight cycles of 32 increments (incrementing PORTB's count in steps of eight). The ratio is then set at 1:4 (prescaler value 001), and again another eight cycles occur. Similarly, the other ratios are set. The difference in the resulting l.e.d. count rates will be obvious.

Adjust the setting of preset VR1 if the slowness becomes tedious in later ratios. After the eight ratios, the whole cycle restarts from 1:2.

Looking at Listing 23, you will see that the TMRO rate is set into the OPTION_REG register while in BANK1 mode, along with the port direction registers.

EXERCISE 18

18.1. Study TK3TUT23.ASM, note the comments and see if you understand what is happening at each stage. Note the detection and resetting of the INTCON,2 flag and the need to go via BANK1 when changing the prescaler rate.

TUTORIAL 19 CONCEPT EXAMINED

BCD (Binary Coded Decimal) counting

CONNECTIONS NEEDED

All Port B to all l.e.d.s.
Port A RA0-RA3 to switches SW0-SW3 (via CP19-CP16)
CP20 to +5V OUT
CP21 to 0V OUT
Preset VR1 set to maximum resistance (fully anti-clockwise)

Having established the use of the timer, we now work towards its use as the pulse source for a real-time clock. There are a few bridges to be crossed yet, though. The first is counting in decimal rather than binary, facilitating the eventual output to a 7-segment l.e.d. or a liquid crystal display. We could keep the counted units in one byte, tens in another, hundreds in another, and so on, but, to conserve precious byte space, it is equally possible to use each byte as two 4-bit nibbles, keeping units in bits 0 to 3, and tens

LISTING 24 – PROGRAM TK3TUT24

```

MAIN      BTFSS INTCON,2
          GOTO MAIN
          BCF INTCON,2
          INCF COUNT,F
          MOVF COUNT,W
          ADDLW 6
          BTFSS STATUS,DC
          GOTO OUTPUT
          MOVWF COUNT
          ADDLW 96
          BTFSC STATUS,C
          CLRF COUNT
OUTPUT    MOVF COUNT,W
          MOVWF PORTB
          GOTO MAIN

```

in bits 4 to 7. Hundreds units and tens would be treated similarly in a second byte.

For simplicity now, we concentrate on counting up to 99, first considering the use of two bytes. In 8-bit binary, a value of decimal 9 is expressed as 00001001, decimal 10 is 00001010, decimal 16 is 00010000. It is obvious that with decimal values we have no single symbol for a number greater than nine. When a value one greater than nine occurs, what we do is reset the units digit to 0 and add one to the next digit, i.e. ten is written as 10.

While counting in binary coded decimal (BCD), we can do a similar thing. When the byte holding the units reaches ten, we reset that byte to zero and add one to the next byte. In 8-bit BCD and at a count of nine, the two bytes would read 00000000 (tens) and 00001001 (units). At the count of ten, the bytes become 00000001 (tens) and 00000000 (units).

When using two nibbles of an 8-bit byte (instead of the above two bytes), a BCD value of nine reads as 00001001, but a BCD value of ten reads as 00010000. And, for example, a BCD value of 37 reads as 00110111, i.e. the lefthand nibble (MSN – Most Significant Nibble) holds a value of 3 and the righthand nibble (LSN – Least Significant Nibble) holds 7. A value of 99 is expressed as 10011001. For a value of 100, both nibbles are reset to zero (00000000) and if there is a byte for hundreds and tens of hundreds, its righthand nibble (LSN) would be incremented, and so on.

Thus, when counting in BCD, we have to check the four bits of the LSN on their own and see if their value is greater than nine. If it is, that nibble is reset and the MSN incremented. The MSN is then taken on its own as a 4-bit value and checked if it is greater than nine. If so, this nibble is reset and the LSN of the next byte incremented accordingly.

CHECKING FOR EXCESS VALUES

There are (as in many programming matters) several ways of checking the nibbles for excess values, of which we shall describe one: an additive checking routine. We said earlier (Tutorial 7) that there is a Digit Carry (DC) flag which signals if the binary value of the LSN has become greater than 15 following an addition. We can use this fact by adding a number to the LSN which will make the answer greater

than 15 if the basic value of the LSN is greater than 9.

The number to be added is 6, e.g. $10 + 6 = 16$ with DC flag set; $9 + 6 = 15$ with DC flag clear. Therefore, to check if an LSN value is greater than 9, we temporarily add 6 to it and check the DC flag. If the flag is clear, the LSN is left as it is. If the flag is set, we increment the MSN and clear the LSN.

There is a short cut to doing this, taking advantage of the fact that $10 + 6 = 16$, being 00010000 in binary. If you look at this answer, the LSN is now zero, while the MSN has been incremented automatically, thus representing decimal 10 in BCD. Thus, when we add 6 to the byte as a whole, if the DC flag is clear, no further action on that byte is needed (or on any subsequent bytes for that matter). If, though, the DC flag is set, we simply replace the existing value in the byte with the value now stored temporarily. These commands do the job:

```

INCF COUNT,F      ; increment file
                  ; value
MOVLW 6           ; move 6 into W
ADDWF COUNT,W    ; add it to new file
                  ; value but keep
                  ; answer in W
BTFSC STATUS,DC  ; is the Digit
                  ; Carry flag clear?
MOVWF COUNT      ; no, it's set so
                  ; move W into file,
                  ; replacing previ-
                  ; ous value

```

(next command)

The above check is done in respect of LSN, but when the DC flag is set, the resulting action changes the value of the MSN, which then has to be checked to see if it (as a 4-bit nibble) is greater than 9, i.e. is the BCD value of the whole byte now equal to or greater than decimal 100?

Again there is an easy additive technique. If we translate the binary value of BCD 100 (10100000) the decimal answer is 160. If we temporarily add 96 ($256 - 160$) to the whole byte, we can then check the Carry flag (C) to see if it has been set, which it will be if the binary answer has rolled over beyond 255. As before, if the flag is clear, the byte can remain as is; if the flag is set, we replace the value with the temporary one.

(Note that the DC and Carry flags are unaffected by an INCF or INCFSZ command.)

Here's the extended routine. Note the inverted logic for checking Digit Carry and Carry flags, BTFSS STATUS,DC in the first instance, BTFSC STATUS,C in the second.

```

INCF COUNT,F
MOVLW 6
ADDWF COUNT,W
BTFSS STATUS,DC
GOTO ENDADD
MOVWF COUNT
MOVLW 96
ADDWF COUNT,W
BTFSC STATUS,C
MOVWF COUNT
ENDADD (program continues)

```

Let's look at the BCD additive technique in practice, triggering it from the timer

routine. In Listing 24, note the use of CLRF COUNT before OUTPUT at the end. This can be used here since we know that adding 1 to the count is occurring, rather than adding values of 2 or greater. In the latter instance, the resulting temporary answer must be MOVED into COUNT, as in the above examples.

Load TK3TUT24.HEX and observe the count incrementing on the l.e.d.s. The prescaler is now run at a fixed ratio of 1:128. Try adjusting VR1 so that an l.e.d. count rate of one per second (1Hz) occurs. (The tolerance of VR1 and the in-circuit capacitance may not allow you to set the rate quite this slow without also amending the OPTION_REG timing value.)

EXERCISE 19

19.1. Suppose our counting system was not decimal but quinary, i.e. no digit greater than 5, rather than no digit greater than 9. How would you change the additive values in the above examples (you can use decimal, binary or hexadecimal for those!).

19.2. Checking for excess BCD values can be done using an XOR technique which is valid if the count is being incremented rather than added to. Adding to the BCD value cannot be used with XOR since the answer could be to either side of the equality being checked for. Can you write an XORed BCD incrementing program?

TUTORIAL 20 CONCEPTS EXAMINED

Real-time timing at 1/25th second
Counting seconds 0 to 60

LISTING 25 - PROGRAM TK3TUT25

```

CLRF PORTA
CLRF PORTB
BANK1
CLRF TRISA
CLRF TRISB
MOVLW B'10000110'
MOVWF OPTION_REG
BANK0
MOVLW 25
MOVWF CLKCNT
CLRF CLKSEC
BCF INTCON,2

MAIN      BTFSS INTCON,2
          GOTO MAIN
          BCF INTCON,2
          DECFSZ CLKCNT,F
          GOTO MAIN
          MOVLW 25
          MOVWF CLKCNT
          INCF CLKSEC,F
          MOVF CLKSEC,W
          ADDLW 6
          BTFSS STATUS,DC
          GOTO OUTPUT
          MOVWF CLKSEC
          MOVLW B'01100000'
          XORWF CLKSEC,W
          BTFSS STATUS,Z
          CLRF CLKSEC

OUTPUT    MOVF CLKSEC,W
          MOVWF PORTB
          GOTO MAIN

```

CONNECTIONS NEEDED

All Port B to all l.e.d.s.
Port A RA0-RA3 to switches SW0-SW3 (via CP19-CP16)
CP20 to +5V OUT
CP21 to 0V OUT
Crystal oscillator

Moving on from decade counting between 0 and 99, it is an easy step to count in BCD from 0 to 59, accurately simulating the seconds count of a real-time clock. In doing so, though, it can be useful to actually increase the count rate available via the prescaler from 1Hz to 25Hz, 50Hz or even 100Hz. Indeed, if a crystal oscillator running at the convenient rate of 3.2768MHz is used, it is actually easier to work with one of these three rates. This is due to the sub-division values available from a crystal of this frequency which can be used in conjunction with the TMR0. Prescaler division ratios of 1:128, 1:64 or 1:32 respectively produce these rates.

So now go over to crystal control on TK3's p.c.b. Go into TK3's PIC Configuration option and select crystal XT instead of the previous RC mode. Leave all other settings as they are. Send the configuration to the PIC. Set TK3's switch S2 to crystal mode. It is assumed that the crystal on your p.c.b. is 3.2768MHz. Crystals having a different frequency may be used but the clock timings shown on your l.c.d. will differ accordingly.

All of the programs you have used so far, with the exception of TK3TUT2, can be run under crystal control. Consequently, if you want to go back and look at some of them again, you do not need to reset the PIC for RC mode.

Load TK3TUT25.HEX and observe PORTB's l.e.d.s. You will see them incrementing at a rate of one per second, and the twin-nibble BCD count will be seen to progressively step from zero to BCD 59 (01011001), then restart again at zero, just as would an ordinary seconds clock and, indeed, it should take one minute for the full cycle to occur.

In this program the prescaler rate has been set for 1:128, providing an INTCON,2 pulse rate of 1/25th of second. A counter, CLKCNT, counts down from 25 in response to the pulses. When it reaches zero, it is reset to 25 and a seconds counter, CLKSEC is incremented in BCD.

Checking for the BCD count becoming ten is performed by the additive (+6) technique we have already shown. However, checking for the count being at BCD 60 is done using the XOR equality testing method (XOR 01100000 = BCD 60). If equality exists, the CLKSEC counter is reset to zero.

EXERCISE 20

20.1 There are three commands associated with the XOR check. What XOR coding would be needed to lose one of them?

TUTORIAL 21 CONCEPTS EXAMINED

Using 7-segment l.e.d. displays
Showing hours, minutes and seconds
Command IORLW (usage)

CONNECTIONS NEEDED

7-segment display as in Fig.6
CP20 to +5V OUT

LISTING 26 - PROGRAM TK3TUT26

```

COMCATHODE
ADDWF PCL,F
RETLW B'00111111' ;0
RETLW B'00000110' ;1
RETLW B'01011011' ;2
RETLW B'01001111' ;3
RETLW B'01100110' ;4
RETLW B'01101101' ;5
RETLW B'01111100' ;6
RETLW B'00000111' ;7
RETLW B'01111111' ;8
RETLW B'01100111' ;9
; common cathode codes

```

```

COMANODE
ADDWF PCL,F
RETLW B'11000000' ;0
RETLW B'11111001' ;1
RETLW B'10100100' ;2
RETLW B'10110000' ;3
RETLW B'10011001' ;4
RETLW B'10010010' ;5
RETLW B'10000011' ;6
RETLW B'11111000' ;7
RETLW B'10000000' ;8
RETLW B'10011000' ;9
; common anode codes

```

```

MAIN      BTFSS INTCON,2
          GOTO MAIN
          BCF INTCON,2
          DECFSZ CLKCNT,F
          GOTO MAIN
          MOVLW 25
          MOVWF CLKCNT
          INCF CLKSEC,F
          MOVF CLKSEC,W
          ADDLW 6
          BTFSS STATUS,DC
          CLRF CLKSEC

```

```

OUTPUT    MOVF CLKSEC,W
          ANDLW B'00001111'
          CALL COMCATHODE
          MOVWF PORTB
          GOTO MAIN

```

CP21 to 0V OUT
Crystal oscillator

Obviously it is not feasible to show hours, minutes and seconds by just using BCD formatted values on individual l.e.d.s. We need a display which is more suited to being understood. Such a display could be via alphanumeric liquid crystal displays (l.c.d.s) and a typical routine using them will be shown later on.

Another choice is the use of 7-segment l.e.d. displays, and that is the route we now take. First, though, we must examine how the output from PORTB needs to be coded to drive a single 7-segment common cathode l.e.d. display. We shall then extend the principle to multiplexing four such displays to show a full 24-hour clock.

As Tutorial 21 is the only section to use 7-segment displays, you may prefer not to purchase one at this time, and to just read about using them, for future reference. Don't skip reading this section, though, as other concepts are examined.

Each segment of a 7-segment l.e.d. display has to be controlled by individual PIC

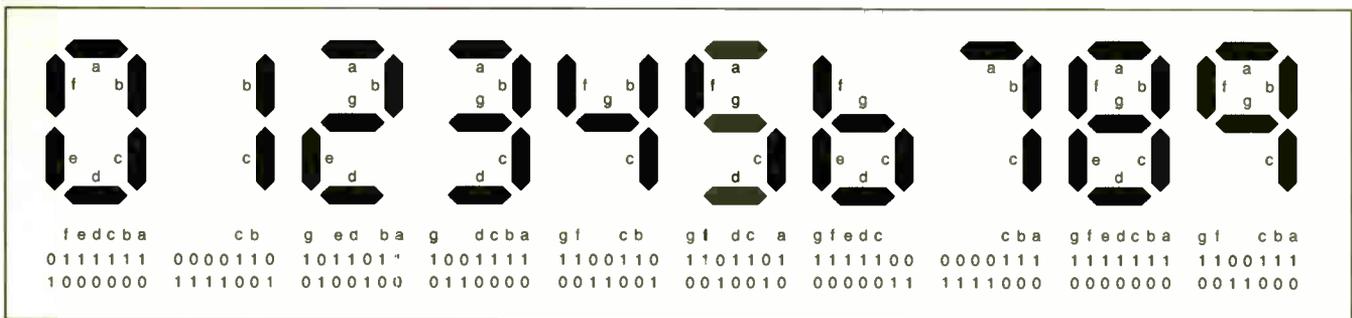


Fig. 4. Numerals 0 to 9 on a 7-segment I.e.d. display, plus controlling binary codes for common cathode (middle line) and common anode (bottom line).

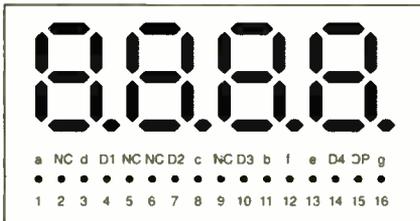


Fig. 5. Pinouts for a typical 4-digit multiplexed 7-segment I.e.d. display.

data lines. It does not matter in which order the data lines are connected to the display since the way that they are activated can be set from within the PIC's controlling program. For convenience, here we use PORTB lines RB0 to RB6 connected in their natural order to segments A to G.

In Fig. 4 are shown the segments and code letters required to form the ten numerals 0 to 9. Also shown are two lines of binary code. The first one shows the bits which need to be taken high if a common cathode display is used. The second is for a common anode display, each line being taken low to turn on the segment. It is a common cathode display that we use here; its pinouts are shown in Fig. 5. Connect it to the p.c.b. as shown in Fig. 6, ensuring that the 330Ω resistors do not short between each other. Also connect RA0-RA3 to TR2-TR5 via CP8-CP11. The program keeps transistor TR2 turned on constantly.

Load TK3TUT26.HEX. You will see the individual numerals being shown on the left-hand digit on a cyclic basis from 0 to 9. Using the crystal oscillator selected for the

LISTING 27 - PROGRAM TK3TUT27

```

MAIN      CALL DIGSEL
          BTFSS INTCON,2
          GOTO MAIN
          BCF INTCON,2
          DECFSZ CLKCNT,F
          GOTO MAIN
          MOVLW 25
          MOVWF CLKCNT
          NCF CLKSEC,F
          MOVF CLKSEC,W
          ADDLW 6
          BTFSS STATUS,DC
          GOTO ENDTIM
          MOVWF CLKSEC
          MOVLW B'01100000'
          XORWF CLKSEC,W
          BTFSC STATUS,Z
          CLRF CLKSEC
          GOTO MAIN
ENDTIM
SECTEN   SWAPF CLKSEC,W
          GOTO OUTPUT
SECONE   MOVF CLKSEC,W
          ANDLW B'00001111'
          CALL COMCATHODE
          MOVWF PORTB
          INCF DIGIT,W
          MOVWF PORTA
          RETURN
DIGSEL   INCF DIGIT,W
          ANDLW 1
          MOVWF DIGIT
          ADDWF PCL,F
          GOTO SECTEN
          GOTO SECONE
  
```

previous Tutorial, the rate of display will be at one unit per second. In other words, it can be regarded as being a seconds counter.

Referring to Listing 26, you will see that the counting routine is very similar to that in Listing 25, but only dealing with units of seconds. Now, though, instead of the count being sent to individual I.e.d.s it is converted in the COMCATHODE table to that numeral when used with a common cathode display. Since we know that the value held in W when the table is called can never be greater than nine, an AND command is not needed with this table.

MULTIPLEXING

Obviously, to show the tens of seconds as well we need a second 7-segment display. However, it is not possible, of course, to use the same PORTB data lines to control both displays simultaneously. Nor can we use PORTA for the second display, it hasn't enough lines. What we can do, though, is to connect PORTB to the segments of both display digits and then alternate the data being output between units and tens values, turning on each digit (via their common cathode pins) only when the relevant data is being sent to them. If this is done at a fast enough rate, the eye is fooled into thinking that both displays are on simultaneously - persistence of vision.

This technique is known as multiplexing, and what we do in this instance is to put the common cathode of each display under control of two separate data lines on PORTA, RA0 and RA1. However, the pins cannot supply sufficient current to adequately drive 7-segment displays (PIC pins can handle around 20mA to 25mA - see PIC datasheets). To provide enough current to drive them, the port lines are buffered by transistors TR2 and TR3 configured as current sinks. The emitters are connected to the 0V line and the collectors are connected to the common cathodes of the displays. The displays are turned on when PORTA lines go high.

Note that for this example the active digits are the righthand two (controlled by TR4 and TR5) in Fig. 6. The other two digits are ignored.

The program which is now required to drive the two displays is shown in Listing 27. Load TK3TUT27.HEX.

Studying Listing 27, first note that (for the sake of demo) an XOR command is used to check for a count value equal to 60 (BCD). Next, and significantly for two displays, digit-alternating commands have been introduced. At label MAIN the command CALL DIGSEL is given. In DIGSEL, a digit counter (DIGIT) is incremented, ANDed with 1, and the result of this increment is carried by W into the

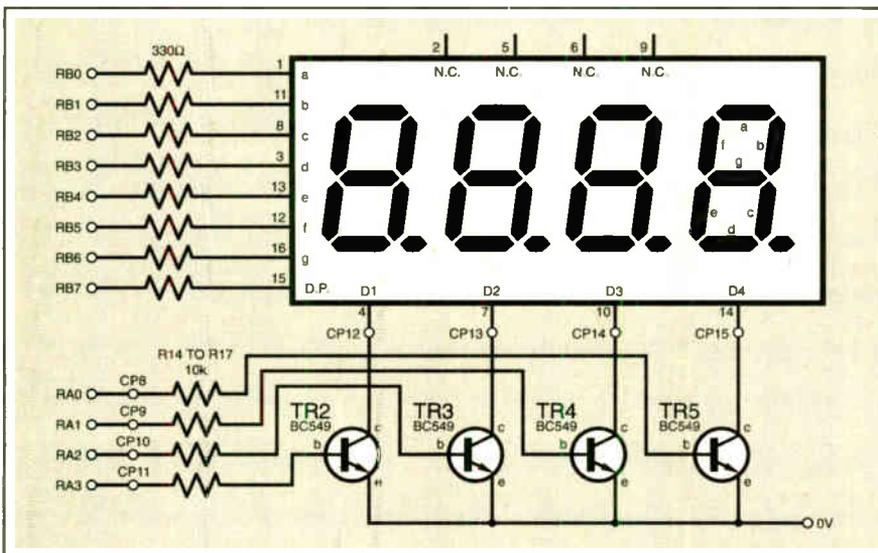


Fig. 6. Connections required to drive a 4-digit 7-segment common cathode I.e.d. module.

LISTING 28 - PROGRAM TK3TUT28

```

DIGSEL   INCF DIGIT,W
         ANDLW B'00000011'
         MOVWF DIGIT
         BTFSS PORTA,4
         ADDLW 2
         ADDWF PCL,F
         GOTO HRSTEN
         GOTO HRSONE
         GOTO MINTEN
         GOTO MINONE
         GOTO SECTEN
         GOTO SECONE
DIGSHW   MOVF DIGIT,W
         ADDWF PCL,F
         RETLW 1
         RETLW 2
         RETLW 4
         RETLW 8
MAIN     CALL DIGSEL
         BTFSS INTCON,2
         GOTO MAIN
         BCF INTCON,2
         CALL CLKADD
         GOTO MAIN
CLKADD   DECFSZ CLKCNT,F
         RETURN
         MOVLW 25
         MOVWF CLKCNT
SECCLK   INCF CLKSEC,F
         MOVLW 6
         ADDWF CLKSEC,W
         BTFSS STATUS,DC
         RETURN
         MOVWF CLKSEC
         XORLW B'01100000'
         BTFSS STATUS,Z
         RETURN
         CLRf CLKSEC

```

table that immediately follows. There are only two jumps in this table, GOTO SECTEN and GOTO SECONE.

Note that the table is still within the 256 block permitted for tables. If this were not the case, the table would need to be placed separately within that block.

Routine SECTEN extracts the tens of units value. Command SWAPF CLKSEC,W swaps the nibbles of the seconds and holds the result in W, putting the tens of seconds into the LSN position. The routine then jumps to OUTPUT, where command ANDLW B'00001111' isolates that nibble, zeroing the MSN bits now in W.

Next, the COMCATHODE table (as in Listing 26) is called to obtain the 7-segment code for that number, which is output to PORTB. Now the digit counter value is obtained (INCF DIGIT,W) and output to PORTA to turn on that digit of the display. The INCF command is used because DIGIT only alternates between 0 and 1, whereas PORTA needs to be alternated between 1 and 2 (binary 01 and 10).

Routine SECONE is similar, dealing with the units of seconds. Here we can simply get the LSN by using MOVF CLKSEC,W, ANDing it with B'00001111' at OUTPUT. The rate of alternation between the two digits is several kilohertz, slowing down briefly each time a time-out is detected.

24 HOURS

Whilst one would like to use six digits in order to display a full 24-hour clock

showing hours, minutes and seconds simultaneously, this is not convenient since we only have five lines on PORTA which can control individual digits. Therefore, we must compromise and continue to use a 4-digit display but which can now have its data sources changed when a switch is pressed. In this way, we can show either hours and minutes together, or minutes and seconds. The program which does this is TK3TUT28, part of which is shown in Listing 28. Load TK3TUT28.HEX then look at listing 28.

Each time the seconds roll over to zero from 59, the minutes need incrementing; each time they roll over to zero from 59, the hours need incrementing. The hours, though, need to roll over to zero from 23. As far as incrementing each of the three counters is concerned, the easiest thing to do (but not the shortest) is to use three separate BCD routines - as we do in TK3TUT28 (see full listing). The minutes routine is the same as the seconds one, both requiring a count from 0 to 59, with routines to check for 10 and 60. The hours routine, though, requires slight alteration.

With the hours, we need to check when counts of 10 and 20 occur (+6 check), and also when 24 occurs (BCD = 00100100). This check cannot be done in the same way as for the BCD 60 check. With the latter, the check is made at the same time as the tens are incremented. For 24 hours, the simplest test is to check on each hourly digit increment:

```

HRSCLK  INCF CLKHRS,F
         MOVLW 6
         ADDWF CLKHRS,W
         BTFSC STATUS,DC
         MOVWF CLKHRS
         XORLW B'00100100'
         BTFSC STATUS,Z
         CLRf CLKHRS

```

The activating of the decimal point, when required, is done by setting the correct bit in the code once the table has been called (BSF PORTB,7), as seen in the OUTPUT routine:

```

OUTPUT  ANDLW B'00001111'
         CALL COMCATHODE
         CLRf PORTA
         MOVWF PORTB
         CALL DIGSHW
         MOVWF PORTA
         MOVF DIGIT,W
         XORLW 1
         BTFSC STATUS,Z
         BSF PORTB,7
         RETURN

```

Minutes and seconds values are dealt with in the same manner. Minutes units, though, are accompanied by the decimal point bit. Seconds are processed similarly, but without any additional bit setting for colons or points. In Tutorial 24 we shall show how a similar result can be achieved by using fewer commands. A loop plays an active role and a table is used when checking the roll-over values for the time.

In Listing 28, when switch SW4 is not pressed (checked by BTFSS PORTA,4), a value of 2 is added to effective value of DIGIT, to cause the table jumps within DIGSEL to be to the minutes and seconds

LISTING 29 - PROGRAM TK3TUT29

```

TABLCD  ADDWF PCL,F
         RETLW B'00110011'
         RETLW B'00110011'
         RETLW B'00110010'
         RETLW B'0010101100'
         RETLW B'00000110'
         RETLW B'00001100'
         RETLW B'00000001'
         RETLW B'00000010'
MESSAG  ADDWF PCL,F
         RETLW 'R'
         RETLW 'E'
         RETLW 'A'
         RETLW 'D'
         RETLW ' '
         RETLW 'E'
         RETLW 'P'
         RETLW 'E'
SETUP   CALL PAUSIT
LCDSET  CLRf LOOP
        CLRf RSLINE
LCDST2  MOVf LOOP,W
        CALL TABLCD
        CALL LCDOUT
        INCF LOOP,F
        BTFSS LOOP,3
        GOTO LCDST2
        CALL PAUSIT
        CLRf LOOP
LCDMSG  BSF RSLINE,4
LCDMS2  MOVf LOOP,W
        CALL MESSAG
        CALL LCDOUT
        INCF LOOP,F
        BTFSS LOOP,3
        GOTO LCDMS2
        GOTO NOMORE
NOMORE  GOTO NOMORE
LCDOUT  MOVWF STORE
        MOVLW 50
        MOVWF LOOPA
        DECFSZ LOOPA,F
        GOTO DELAY
        CALL SENDIT
        CALL SENDIT
        RETURN
SENDIT  SWAPF STORE,F
        MOVf STORE,W
        ANDLW 15
        IORWF RSLINE,W
        MOVWF PORTB
        BSF PORTA,5
        BCF PORTA,5
        RETURN
PAUSIT  MOVLW 5
        MOVWF CLKCNT
        CLRf INTCON
PAUSE   BTFSS INTCON,2
        GOTO PAUSE
        BCF INTCON,2
        DECFSZ CLKCNT,F
        GOTO PAUSE
        RETURN

```

display routines. Pressing SW3 results in hours and minutes being shown.

You will observe that the brilliance of the display is less than that previously seen, due to the multiplexing. In a real clock situation, the use of a high brightness display would probably be preferable.

Note that ANDing with B'00001111' (as we have done several times in this section)

is a common requirement and it is actually easier to type in using its decimal equivalent of 15, so the ANDLW 15 command could be used instead.

You will see in Listing 26 that a COMANODE table is provided as well. In other applications using common anode displays this table would be called from the OUTPUT routine rather than COMCATHODE. In this instance the transistors would have their collectors connected to the +5V line and their emitters to the anode control pins of the display. Common cathode displays cannot be used with TK3's p.c.b. as the transistor emitters are connected to the 0V line.

EXERCISE 21

21.1. You may have noticed "ghost" images on the "off" segments for the active digits in TK3TUT27, but not in TK3TUT28. Study TK3TUT28's full listing and amend TK3TUT27 similarly to eliminate the "ghosts".

21.2. Create a table that holds all 16 conversions for a hexadecimal count (i.e. 0 to 9 and A to F) to be shown on a 4-digit common anode display. Write a simple counting routine which makes use of it. What compromise might you have to accept?

21.3. Extend the routine from 21.2 so that it blanks the display of any leading zeros (i.e. don't show 0007, but just show 7 on its own).

TUTORIAL 22

CONCEPTS EXAMINED

- Using intelligent l.c.d.s
- Setting l.c.d. contrast
- Initialising the l.c.d.s
- Sending a message to the l.c.d.

CONNECTIONS NEEDED

- L.C.D. as in Fig.7
- CP20 to +5V OUT
- CP21 to 0V OUT
- Crystal oscillator

Having established how 7-segment displays can be driven by the PIC, we now show how an alphanumeric l.c.d. can be used to achieve not only the same result, but one that has additional facilities as well. The coding required is not especially complex, although minimum timing factors for some aspects of sending data to an l.c.d. have to be observed.

The first requirement is to show the basics of how data is output to an l.c.d. from the PIC. We shall not cover the l.c.d. itself in any great detail – you are referred to manufacturer's datasheets for more information.

Here, we first show how the l.c.d. is initialised for 4-bit data transfer from the PIC, using two control lines, RS and E. Line RS sets the l.c.d. for inputting either character data or control data. Line E tells the l.c.d. to act on the data output to it.

Disconnect the l.c.d. module and connect the l.c.d. to the p.c.b. as in Fig.7. Typical l.c.d. pinouts are shown in Fig.8. Load TK3TUT29.HEX and run it. While reading these next paragraphs, refer to Listing 29 as appropriate.

The first time the l.c.d. is used, the Contrast control VR2 should be adjusted until the display is clearly visible.

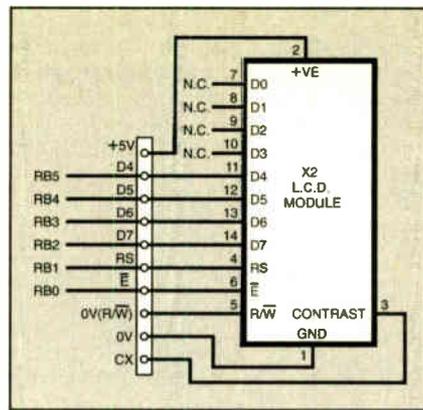


Fig.7. Connection between l.c.d. and TK3 p.c.b.

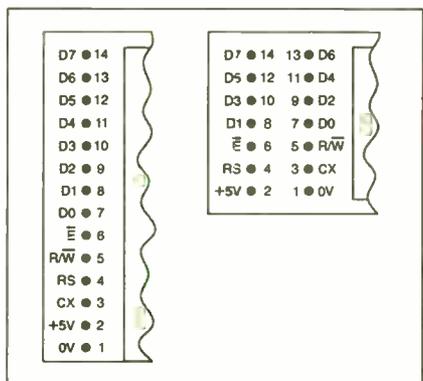


Fig.8. The two "standard" l.c.d. module pinout arrangements.

DELAYED START

When the l.c.d. is under high speed control from a device such as the PIC, it is necessary to allow a minimum of 1/5th of a second between the circuit being switched on and any data being sent to the l.c.d. So, after the PIC's initialisation, the program jumps to the routine at SETUP which, via sub-routine PAUSIT, creates this delay by making use of the prescaler.

The prescaler has been set for an INTCON,2 pulse every 1/25th of a second, so a loop beginning at PAUSE is used to wait for five of these pulses to be completed, i.e. 1/5th of a second. Then a series of commands is sent to set the l.c.d. into the required 4-bit mode. (There are other command routines possible which achieve a similar result.) The commands are held in the table TABLCD, which is accessed from the routine at label LCDSET. The first command here clears the loop counter and the byte (RSLINE) which holds the RS-controlling bit.

Bit 4 of RSLINE is used to inform the l.c.d. what type of data is being sent to it. The bit is cleared for control data, and set for character data. Now, in the manner of table use which was demonstrated earlier, the control commands from TABLCD are sent to the l.c.d. via the LCDST2 routine.

The loop counter is then cleared, RSLINE bit 4 is set and used to inform the l.c.d. that the next commands being sent to it are character data.

Then the message held in the table MESSAG is sent via the routine headed LCDMSG. The l.c.d. displays this message on its first line, starting at the left. Now, for

the sake this demo, the perpetual loop at NOMORE is entered and no more actions occur. To replay the routine, use the Reset switch.

In both data sending routines, the l.c.d. output routine is called by the command CALL LCDOUT. The entire block between the start of LCDOUT and the final RETURN at the end of SENDIT is responsible for sending each byte of 8-bit data to the LCD as two 4-bit nibbles, to which control data is then ORed to expand them to a full 8-bit byte. Nibble data is held in the LSN of this byte, control data (in this instance just that for lines RSLINE and E) is held in its MSN.

On entry into LCDOUT, the data brought in on W is copied into a temporary file, STORE. Now a delay loop is entered. The l.c.d. can only handle bytes of data coming to it at a rate which allows previous data received to be processed fully. Details of the delay required are stated in manufacturer's datasheets. In theory, the delay depends on the type of data and command being sent, but on a practical level, a fixed delay of so many PIC commands can be used. In this example, LOOPA is set for 50 and then decremented until zero, as performed by the instructions:

```
MOVLW 50
MOVWF LOOPA
DELAY DECFSZ LOOPA,F
GOTO DELAY
```

In the author's experience with many programs, this delay is satisfactory for a PIC running at up to about 5MHz. Too short a delay will result in erratic behaviour of the l.c.d., probably accompanied by erroneous display results. The most likely result of this is that the display will not enter 2-line mode, characterised by a line of dark pixels on the upper line, but none on the lower, which will remain blank. If this occurs, the delay loop value should be increased.

Following the delay, there is a call to SENDIT. In SENDIT, the MS nibble of data is retrieved from STORE with the commands:

```
SWAPF STORE,F
MOVWF STORE,W
ANDLW 15
```

The first command swaps the two nibbles within STORE, the second copies STORE into W, and then W is ANDed with 15 to isolate bits 0 to 3. The result is ORed with the RSLINE bit and the byte is then output to the l.c.d. via PORTB. The E line is taken high and immediately low again, telling the l.c.d. to process the data on its data inputs. A return to the calling point occurs and then SENDIT is again called. This time, the LSN is extracted from STORE and sent to the l.c.d. in the same way. After two returns, the program returns to the original calling point.

It is important to note that the port bits which are used in these routines to control the Data, RSLINE and E lines reflect the physical connections between the PIC and the l.c.d. as shown in Fig.7. It is permissible to use other PIC port lines for this purpose, but the controlling bits of the software must be changed accordingly.

EXERCISE 22

22.1. There are two commands in the LCDOUT to SENDIT routine which, while being perfectly legitimate, are actually unnecessary. What are they and why are they not needed? (Think "default".)

22.2. When the l.c.d. is first initialised, it is possible (though not definite) that all its character positions (cells) will show as black squares. Sending the message will correct that situation for the first eight cells. How could you ensure that the remaining eight cells on the top line are set to "clear" blanks? There are two methods; try both.

22.3. How would you now set the lower line to all blanks?

TUTORIAL 23 CONCEPTS EXAMINED

Coding hours, minutes and seconds for an alphanumeric l.c.d.
Shortened clock monitoring code
Command SUBLW
Command SUBWF

CONNECTIONS NEEDED

L.C.D. as in Fig.7
CP20 to +5V OUT
CP21 to 0V OUT
Crystal oscillator

Having shown how the l.c.d. can have data written to it, we now show how the method can be extended in order to display 24-hour clock data.

Load TK3TUT30.HEX then glance at the display from time to time while you read on here.

COMMANDS SUBLW AND SUBWF

Rather late on perhaps, in the program we are about to display we illustrate the first use of subtraction. PICs have two subtraction commands, SUBLW (Subtract W from Literal) and SUBWF (Subtract W from File). The latter command is used with either the F or the W suffix, e.g. SUBWF (FILE),F and SUBWF (FILE),W.

One might reasonably have expected that SUBLW would actually mean Subtract Literal from W. This is not the case, the subtraction is that of W from the Literal. Consequently, unless you keep your wits about you, this is a command that you could quite easily use incorrectly.

In the following code, the value in the file named DEMO is subtracted from 30 and the result put back into DEMO (the first two lines are just to put an initial value into DEMO):

```
MOVLW 20
MOVWF DEMO
MOVF DEMO,W
SUBLW 30
MOVWF DEMO
```

In this case, the answer is 10 (30 - 20), even though instinctively we might have expected 30 to be subtracted from 20. In this next example, to illustrate SUBWF, again it is the value already in W which is subtracted from the value in file DEMO, the result being returned to DEMO. This is more logical. (Once more the first two commands are just to put an initial value into DEMO.)

LISTING 30 - PROGRAM TK3TUT30

```
MAIN      BTFSS INTCON,2
          GOTO MAIN
          BCF INTCON,2
          CALL CLKADD
          GOTO MAIN
CLKADD    DECFSZ CLKCNT,F
          RETURN
          MOVLW 25
          MOVWF CLKCNT
          MOVLW CLKSEC
          MOVWF FSR
          MOVLW 3
          MOVWF LOOP
          CLRF STORE1
          ADDCLK
          INCF INDF,F
          MOVLW 6
          ADDWF INDF,W
          BTFSC STATUS,C
          MOVWF INDF
          ADDCL2
          MOVF STORE1,W
          CALL CHKVAL
          MOVWF STORE2
          MOVF INDF,W
          SUBWF STORE2,F
          BTFSC STATUS,C
          GOTO CLKSHW
          CLRF INDF
          INCF STORE1,F
          INCF FSR,F
          DECFSZ LOOP,F
          GOTO ADDCLK
          CLKSHW
          MOVLW B'11000000'
          CALL LCDLIN
          MOVF CLKHRS,W
          CALL LCDFRM
          MOVLW ':'
          CALL LCDOUT
          MOVF CLKMIN,W
          CALL LCDFRM
          MOVLW ':'
          CALL LCDOUT
          MOVF CLKSEC,W
          CALL LCDFRM RETURN
          LCDFRM
          MOVWF STORE2
          SWAPF STORE2,W
          ANDLW 15
          IORLW 48
          CALL LCDOUT
          MOVF STORE2,W
          ANDLW 15
          IORLW 48
          CALL LCDOUT
          RETURN
          LCDLIN
          BCF RSLINE,4
          CALL LCDOUT
          BSF RSLINE,4
          RETURN
```

```
MOVLW 20
MOVWF DEMO
MOVLW 5
SUBWF DEMO,F
```

The answer put back into DEMO is, of course, 15 (20 - 5).

In these two examples, the value subtracted is less than the value from which it is being subtracted. What happens if the opposite is true?

For a start, if the value subtracted is greater than the value from which it is being subtracted, the byte simply "rolls-over". We have already shown that decrementing a value of zero results in an

answer of 255. Decrementing, of course, is simply a subtraction of 1 from a number and we could, therefore, consider the 0 - 1 situation as being expressed (256 + 0) - 1 = 255.

What we have done by using the addition of 256, is to "borrow" the 256 in order to achieve the correct 8-bit result. The same roll-over situation applies to subtraction of numbers greater than 1. Thus subtracting 20 from 10 produces an answer of 246 (256 + 10 - 20 = 246).

We are quite used to "borrowing" in normal arithmetic, so the concept should be familiar to you, although we express the result of subtracting 20 from 10 as equalling -10.

The difference with PICs (and other digital devices) is that we cannot produce a negative answer as such. What we can do, however, is to use a flag to indicate that a borrow or negative answer situation has occurred. With the PIC, the Carry bit is used for this purpose. In a subtraction operation we simply test the Carry bit to establish whether or not there has been a borrow.

This, though, is where another "invert-ed" concept has to be applied to SUB commands. Whereas with the ADD commands the Carry bit is Set if a carry result occurs, with the SUB commands the Carry bit is Cleared if a borrow occurs, and it is Set if a borrow does *not* occur.

You could, perhaps, regard the Carry bit as being the bit which is available to be "borrowed" for the subtraction, hence it remaining set if a borrow is not needed, and cleared if it is.

The following are examples of routines which test the Carry bit in a subtraction operation:

```
MOVLW 30
MOVWF DEMO
MOVF DEMO,W
SUBLW 20
MOVWF DEMO
BTFSS STATUS,C
INCF STORE,F
RETURN
```

The above example will cause STORE to be incremented since a borrow will occur when 30 is subtracted from 20. The next example, 30 - 20, does not result in a borrow, so STORE remains at its previous value:

```
MOVLW 20
MOVWF DEMO
MOVF DEMO,W
SUBLW 30
MOVWF DEMO
BTFSS STATUS,C
INCF STORE,F
RETURN
```

You will see the use of SUBWF and the subsequent testing of the Carry bit for the occurrence of a borrow in TK3TUT30.

NEXT MONTH


In the final part of this series we move on to some of a PIC's "sophisticated" operations. You might also care to obtain a PIC16F877 (although this is optional) as we also illustrate some advanced programming techniques that can be used with this device family, as listed on page 3 of Part 1.

FLOWLOG

datalogging • control • electrical measurement

A NEW, LOW COST OSCILLOSCOPE, DATALOGGER AND CONTROL UNIT

£99
+VAT

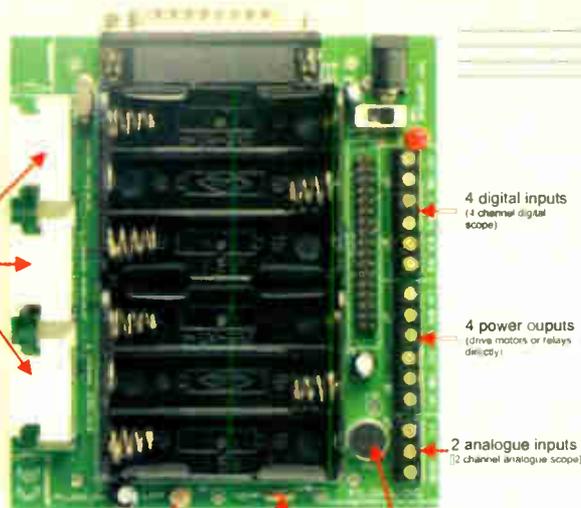

external sockets for a range of over 30 sensors including pH, current, ECG, temperature, magnetic field, humidity etc.

4 digital inputs (4 channel digital scope)

4 power outputs (drives motors or relays directly)

2 analogue inputs (2 channel analogue scope)


on-board light sensor

on-board temperature sensor


on-board mike for sound and sound level

FREE SOFTWARE APPLICATIONS INCLUDE:


2 channel analogue scope

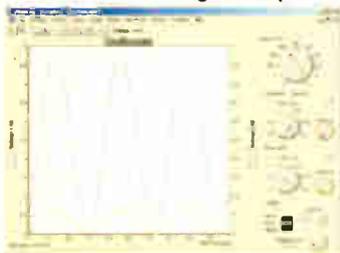


4 channel digital scope

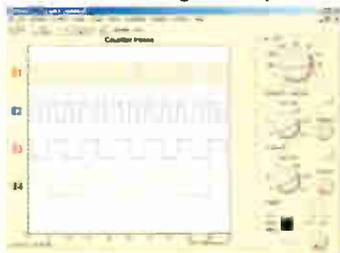

advanced datalogging software

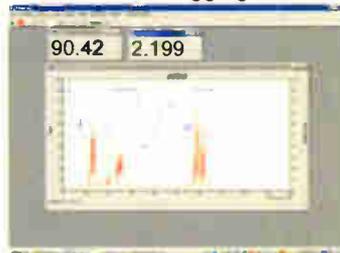

flexible control software

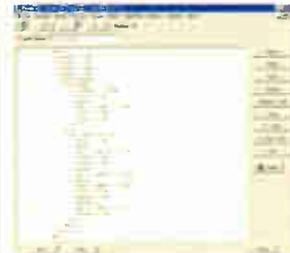

Flowlog is a new computer interface that provides datalogging, control and electrical measurement functions for use in science and electronics. Flowlog provides unrivalled value for money and performance. Please log onto our web site for full specification and description.

www.matrixmultimedia.co.uk
sales@matrixmultimedia.co.uk
 t. 0870 700 1831 f. 0870 700 1832

TRcontrol Solutions

Innovative Products Imaginative Solutions



I²C and Serial LCD Modules

Embedded Internet Solutions



Rapid Development Micro-Controllers



Visit our site www.trcontrolsolutions.com
 or Phone us on 020 8823 9230

TOTALROBOTS

Robotics, Control & Electronics Technology

BEAM Robots



Programmable Mobile Robots



Robot Arms



Visit our site www.totalrobots.com
 or Phone us on 020 8823 9220

EPE PIC RESOURCES CD-ROM



A companion to the EPE PIC Tutorial V2 series of Supplements (EPE April, May, June 2003)

ONLY £14.45 INCLUDING VAT and P&P

Contains the following Tutorial-related software and texts:

- EPE PIC Tutorial V2 complete demonstration software, John Becker, April, May, June '03
- PIC Toolkit Mk3 (TK3 hardware construction details), John Becker, Oct '01
- PIC Toolkit TK3 for Windows (software details), John Becker, Nov '01

Plus these useful texts to help you get the most out of your PIC programming:

- How to Use Intelligent L.C.D.s, Julyan Ilett, Feb/Mar '97
- PIC16F87x Microcontrollers (Review), John Becker, April '99
- PIC16F87x Mini Tutorial, John Becker, Oct '99
- Using PICs and Keypads, John Becker, Jan '01
- How to Use Graphics L.C.D.s with PICs, John Becker, Feb '01
- PIC16F87x Extended Memory (how to use it), John Becker, June '01
- PIC to Printer Interfacing (dot-matrix), John Becker, July '01
- PIC Magick Musick (use of 40kHz transducers), John Becker, Jan '02
- Programming PIC Interrupts, Malcolm Wiles, Mar/Apr '02
- Using the PIC's PCLATH Command, John Waller, July '02
- EPE StyloPIC (precision tuning musical notes), John Becker, July '02
- Using Square Roots with PICs, Peter Hemsley, Aug '02
- Using TK3 with Windows XP and 2000, Mark Jones, Oct '02
- PIC Macros and Computed GOTOs, Malcolm Wiles, Jan '03
- Asynchronous Serial Communications (RS-232), John Waller, unpublished
- Using I²C Facilities in the PIC16F877, John Waller, unpublished
- Using Serial EEPROMs, Gary Moulton, unpublished
- Additional text for EPE PIC Tutorial V2, John Becker, unpublished

NOTE: The PDF files on this CD-ROM are suitable to use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader – included on the CD-ROM

Order on-line from
www.epemag.wimborne.co.uk/shopdoor.htm
 or www.epemag.com (USA \$ prices)
 or by Phone, Fax, Email or Post.

EPE PIC RESOURCES CD-ROM ORDER FORM

Please send me (quantity) EPE PIC RESOURCES CD-ROM
 Price £14.45 each – includes postage to anywhere in the world.

Name

Address

..... Post Code

I enclose cheque/P.O./bank draft to the value of £

Please charge my Visa/Mastercard/Amex/Diners Club/Switch

£

Card No.

Card Security Code (The last 3 digits on or just under the signature strip)

Expiry Date Switch Issue No.

**SEND TO: Everyday Practical Electronics,
 Wimborne Publishing Ltd.,
 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.
 Tel: 01202 873872 Fax: 01202 874562.
 Email: orders@epemag.wimborne.co.uk**

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

BECOME A PIC WIZARD WITH THE HELP OF EPE!

READOUT

Email: john.becker@epemag.wimborne.co.uk

John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

All letters quoted here have previously been replied to directly.

WIN A DIGITAL MULTIMETER

A 3½ digit pocket-sized I.c.d. multimeter which measures a.c. and d.c. voltage, d.c. current and resistance. It can also test diodes and bipolar transistors.

Every month we will give a Digital Multimeter to the author of the best *Readout* letter.



★ LETTER OF THE MONTH ★

P.C.B. CAD AND XP

Dear EPE,

Having read Malcolm Wiles' letter (*Readout* April '03) of concern about using his present p.c.b. CAD package on new PC equipment has forced me to write to you. Reading his comments about using Windows XP, I assume that, like thousands of other PC users, he has been given misguided information about the operating system.

I, too, have tried many types of p.c.b. CAD program (shareware and commercial), some that were written for DOS, Win95, Win98 and XP. I have not found one yet that will not run on Windows XP. The same applies for most other software too. Over the last 12 months I have converted dozens of Win 98 and Win ME users to XP. The operating system is years ahead of its predecessors, being, in my opinion, the most stable system ever. My system has never crashed nor had blue screens since loading it 14 months ago. XP does not allow the use of badly written programs – the type that attempt to write over critical Windows memory locations.

I have some good advice for those who have been misguided. Don't knock it until you've tried it!

On a change of subject I think your mag is great. Its continuing popularity must be due to

the constant variety that is covered in it. My favourite at present is PIC programming.

I am interested to know if you have any plans in the future to build an X, Y, Z plotter that will read Gerber or Drill files produced by p.c.b. CAD programs.

Charles Fenton,
via email

You are very reassuring about XP, Charles. I've not tried it for myself yet, still variously using 95, 98 and ME.

Years ago I tried to build a plotter but my limited mechanics skills and equipment defeated me. No-one has ever offered us one that I know of. These days I'm sure that it would actually not be appropriate for us to publish one anyway, with the quality of the printers now available, most readers would probably not find any benefit. Admittedly the size of image that could be handled by a decent plotter would find appeal in some quarters, but few readers are likely to need large p.c.b. images.

Even I do not usually require an image larger than A4, although my PICronos L.E.D. Wall Clock being published next month is wider than A4, but I adequately coped by combining two printout sections.

RAIN MAN

Dear EPE,

With regard to Ferren MacIntyre's letter and your comments to him about rain gauges in *Readout* April '03 – for a long time I worked on the telemetry for a river authority and the classic tipping bucket was about the only accurate method of measuring rain fall and also give a close approximation as to the time the rain started/stopped.

The idea of a gauge with no moving parts is very interesting. We actually had a tipping bucket failure due to ants building their nest under it! However, I feel the method outlined by Ferren of using a V notch weir may present a few problems with regard to calibration. From what I can remember of weirs there are a host of calibration curves depending on the amount of flow over the weir.

The manual type of rain gauge uses a funnel to drain the rain into a long small diameter but calibrated glass jar. I wonder if it would be feasible to bring this device up to date by placing a pressure transducer in the jar? The gauge could be interrogated at 15 minute intervals, as is the norm. There is the small problem, though, of when did the rain start? This would have to be done in software which could sense a change in level/stable-level as being the start or stop time respectively.

May I also draw your attention to April's *Plant Watering Reminder*. If the probe is to be left in the soil, which will obviously be moist, then polarisation will occur around the probes with a build up of gas around them and the device will slowly cease to function thereby giving a false indication.

Peter Mitchell, via email

Years ago, Peter, when I designed my first weather centre, I did consider tipping buckets and the like, but decided the mechanics were probably beyond the tools that I have. These days, on behalf of readers who could be in a similar predicament, I still would not wish to go down the mechanical route (one reason I investigated, and have implemented, solid-state wind speed/direction sensing). An ants problem I'd not even considered, but as a programmer I suppose I should have been prepared to eliminate bugs, though!

Certainly I can see a way in which I could design a pressure sensitive rain gauge, but I think the cost could outweigh its usefulness. First the water level sensor would need to be waterproofed. Secondly, I think it would be necessary to also sense atmospheric pressure with another sensor, to remove that influence from the readings of the first sensor. Using ultrasonics, as I commented in my reply to Ferren, is a technique I've used in the past and am again in the design being worked on.

Yes, perhaps a note on polarisation should have been added to the *Plant Watering Reminder*. It's worth remembering, though, that it is only a simple circuit and by its nature not equipped with the features that would be expected from a more sophisticated design.

I discussed the problems of polarisation in brief in Part One of my *Earth Resistivity Logger* (April '03). The *ER's* PC program also has a click button that lets you read about experiments that can be carried out into measuring soil conditions and the associated problems.

GETTING ORG-ANISED

Dear EPE,

I have recently purchased a *PIC Toolkit MK3* board from Magenta and am working through your *PIC Tutorial*. I have typed the first example listing into my WordPerfect program and saved as an ASCII text file. When I try to assemble from ASM to HEX all I can get is a message telling me that an ORG statement has not been found and that the assembly has been aborted. But I have typed in the ORG statements as needed. What am I doing wrong?

Graham Payne, via email

I first pointed out to Graham that he need not type it from the published listing as all the software is available for free download from our ftp site, access through the top of our home page at www.epemag.wimborne.co.uk (and of course it's also available for purchase on disk as described in the article).

It would also be a mistake to type in all the example programs since as we progress into the Tutorial, it is only extracts of the listings that are shown. They are on their own and without all the "fixtures and fittings" that must accompany any PIC program, and so cannot stand alone. However, I told Graham I would be interested to see the file that he had created as I could not understand why it would not assemble even though the required ORGs were there.

Having received Graham's file the answer was simple! Every typed in statement had been placed hard left of the text page. Consequently TK3 was not finding statements in their correct columns, and overlooking the ORGs in column 1 when it was expecting them in column 2. TK3 and other PIC programming assemblers all expect to find commands starting in column 2.

Column 1 is reserved for labels. Just putting a space in front of each line was all that was necessary, making TK3 think the commands were in column 2.

The concept of columns is in a sense somewhat arbitrary. TK3 and many other programmers first examine each line of text and split it into sections. The section splits are initially determined by the position at which blank spaces or tab commands (the "separators") are found, with consecutive occurrences of either being ignored. Any text to the left of the first separator is regarded as being in column 1. Any text between separators one and two is in column 2, etc.

Columns are also created by the presence of commas in some commands, as in the case of MOVF PORTB,W for instance. In this statement MOVF is regarded as in column 2, PORTB in col 3, and W in col 4

When you are keying in PIC commands, ideally make column 2 start so there's room for labels in column 1 and to keep things neat and tabulated. Study my listings.

AMPLIFIERS

Dear EPE,

Have you done any projects about amplifier construction, including the tone controls?

Engr. Daniel A. Offiong,
Calabar, Nigeria., via email

We have not done much on amplifiers in recent years, but Raymond Haigh's series of four articles, Simple Audio Circuits, might interest you, published in May-Aug '02.

Back issues can be bought from HQ, see the Back Issues page, or from our Online shop, accessible via the top of our UK home page at <http://www.epemag.wimborne.co.uk>.

WIND TUNNEL

Dear EPE,

Regarding John Becker's *Wind Tunnel* (Feb '03), and the subject of "smoke", model railway enthusiasts use a 12V device, made in Germany under the Seute brand name, which takes a few drops of light oil "down the funnel" to give a modest stream of smoke for several minutes. Another, less messy, source is the humble mozzie-coil (they go for ages) or its perfumed relative, incense/joss-sticks available from "new-age" shops. Used with a perforated tube across the air-path, several streamers may be made from one source of smoke.

**Brian Conner,
Newtown, N.S.W., via email**

Thanks, Brian. In fact I tried to get joss-sticks, living in a multi-cultural area, I had expected to find them, but failed. Nor could I get model train smoke from my local model shop.

BIG DIGIT DISPLAY

Dear EPE,

Thanks for the *Big Digit Display* project featured in your May '02 issue. A couple of years ago I "procured" four of these 7-segment displays when Shell service stations in Australia refurbished their outlets. There must have been thousands of these devices that were just trashed. However, no-one was able to supply any control devices or info, apart from your Fig.1 and Fig.2 details. So they've sat in the groundsman's hut at my rugby club gathering dust, spiders and wasps. Yes, I know your article was last year, but it was mid-season over here and too late to start on the project, but now that rugby time is here again I needed to get myself into gear.

Have you had any feedback relating to remote control either by infra-red or r.f.? Could you please advise how I go about finding out that info? It's just that it's a long way to dig a trench to run the cables to the other side of the paddock (and needs much amber nectar to encourage us!).

Peter Finch, Australia, via email

I suggest that you consider using r.f., Peter. It's highly unlikely that infra-red will reach far enough. Browse www.rfsolutions.co.uk for r.f. modules.

And nectar's even more enjoyable if you don't have to work for it!

PIC PATIENCE

Dear EPE,

I have experienced problems with a PIC16F84 when the power is removed and then quickly turned back on. Nearly all of your circuits use a 100nF capacitor between the power pin and ground which I always include.

The problem is most obvious when an l.c.d. is connected to the chip. I can regularly get the chip to start up with the display showing garbage and nothing else seems to function. Am I doing something wrong? Can you offer an alternative.

Simon Smyth, via email

You should always allow time for a circuit's capacitors to discharge fully following switch off and before re-applying power. Intelligent devices like PICs and l.c.d.s require an initialisation procedure when powering up. By switching off and then on again immediately, the device's internals could be caught in mid-stroke, so to speak, through the disruption of partly losing power, but not enough to be triggered into their initialisation procedure when power resumes. They will certainly get confused if you don't allow time for the power supply voltage to drop sufficiently. So yes, Simon, you are doing something wrong, not being patient!

If what you are trying to do is restart the program from the beginning to observe a particular action, there is an alternative to switching off the power. With all of my PIC designs, there is a diode and resistor between the PIC's MCLR pin (pin 4 on a PIC16F84 and the +5V line). There is then a connection point on the board that joins to pin 4, and usually marked as MCLR. Connect

a push-to-make switch between that point and the 0V line. Pressing the switch automatically resets the PIC so that it is forced to restart the program from the beginning when the switch is released.

Do not use this technique with any PIC circuit that has its MCLR pin connected directly to the +5V power rail, i.e. without a buffering resistor such as my circuits have (but other people's designs may not). Doing so would short out the power supply.

SOURCING VB

Dear EPE,

I wish to try my hand at programming in Visual Basic. Is this very hard to master? I am ok with Z80, ST6 and PIC but would like get at the PC. What exactly would I need to purchase to get something up and running? If you can point me in the right direction it would be most helpful.

John Ramsey-Brown, via email

Well, John, I found VB6 much easier to learn than I expected, partly helped by some aspects of it being similar to QBasic which I already knew. Problem now though is that VB6 does not seem to be so obviously available – my local PC World for instance no longer has VB6 on its shelves and has not replaced it with the later and more expensive version, VB Net.

However, talking to their manager recently, I was told that although not on the display shelves, VB6 is shown in their latest catalogue. I found it in the books section on page 557, under Visual Basic. It shows the same version that I learned on and continue to use, Visual Basic 6.0 Deluxe Learning Edition Book/CD package, £75.18. Well worth it.

It is a superb tool and I love using it, as much as I do PICs!

TELE-FEEDING (1)

Dear EPE,

After reading Norman Blair's letter about Tele-Feeding in *Readout* March '03, it occurred to me that I had controlled some equipment via the phone using the Velleman K6501 remote control by telephone. This uses DTFM codes which are fairly secure and up to three outputs are possible from memory. I believe Maplin stock this kit, which might help Norman.

David Lerner, via email

Thanks David

TELE-FEEDING (2)

Dear EPE,

There is a way that Norman Blair can use the telephone legally to signal his animal feeder – and with the bonus of having the telephone being usable with an answerphone at the same time. If he purchases/has an answerphone that will either ignore an invalid DTMF code for remote retrieval (or simply doesn't have remote access to begin with), then an acoustically coupled microphone (mic plonked near the answerphone speaker) fed into a cheap DTMF decoder i.c. could do the job well.

He would need to dial in, wait for the outgoing message to finish and then press the required key(s) to activate the gadget. So long as the answering machine had call screening – most do – this would work well, offer a degree of immunity from false activation and be completely legal.

If security was not an issue, then he wouldn't even need a PIC, just a DTMF decoder, crystal, a few discretes, an op.amp and a microphone, an output via a general-purpose transistor and a relay with back-EMF diode across its coil. I'm not sure if Maplin still stock DTMF decoders, but Farnell do and they do supply to private users at trade price. Come to think of it, up to 12 different devices could be controlled in this way – 16 in fact if Norman has access to a keypad with ABCD as well as the usual set of buttons.

Incidentally, if anyone has a spare i-button hybrid module for sale (sold by Maplin's before they discontinued it), I'd appreciate an email, I

cannot find another self-contained device that can recognise up to six i-buttons anywhere.

**Mark Tibbert, via email
Mark@lineisp.com**

Thank you Mark. So, Norman, you are spoilt for choice thanks to David and Mark. And, readers, can you help Mark?

PICTUR V2 PLUS MSCOMM

Dear EPE,

The April issue is a nice edition – I've been awaiting your *PIC Tutorial V2* with some anticipation as I'm hoping to plug most of the significant gaps in my limited PIC knowledge. From the contents page, it looks like it's going to be great.

Secondly, I read Robert Penfold's April *Interface* article and in the State Monitoring section, he states that there is no way to monitor the RI (Ring Indicator) signal. This isn't entirely correct. The OnComm event is raised with ComEvent set to comEvRing. However, not all chip-sets support this signal. More information can be found in the MSCOMM on-line help.

Joe Farr, via email

Thank you, Joe, we look forward to publishing your sophisticated serial interface that we are discussing with you separately.

STACK ENHANCEMENT

Dear EPE,

In the March issue *Readout*, John Waller writes about the 8-level-deep limit on the stack of PICs such as the F877. Microchip have a software solution for the smaller PICs with only a 2-level stack (application note 527), which could be modified to give a bigger stack on the larger PICs.

**David Tilch,
Johannesburg, South Africa, via email**

Thanks David. In fact a fair bit of correspondence was generated on this subject, but too lengthy and in-depth to publish. Some of the solutions offered though had such an overhead cost in terms of code involved, I became determined that I would find ways round ever needing to use a stack quantity greater than that allowed by the PICs I currently use.

BROWSE THESE

Dear EPE,

Readers could find the following free software on the web to be interesting:

SIMatrix: www.newburytech.co.uk.

Quickfield: www.tera-analysis.com or www.quickfield.com.

The first is SIMatrix' simulation demo. I have the full copy at work, but the free version (which is sort of node limited) has proved quite useful at home. It allows you to save circuits but there is a limit to how many components can be used in the simulation. I've also used it for producing circuit diagrams (bigger than it will allow you to simulate) which is also useful.



The other one is Quickfield's Student edition. It's a finite element analysis package. I've used it for calculating the resistance of odd shapes of polysilicon on ASICs. You can define a geometry and having defined the resistivity, you can see the current distribution – in living colour. You can then get it to calculate resistance. It also does electrostatic and magnetic stuff. That's probably not what most of your readers do, but it can be really educational.

Just got into your *Toolkit TK3*. Very nice. (Is John on the Microchip payroll? I think they owe him!)

Graham Johnston, via email

Thanks for the info and kind comments Graham – I'm waiting for a huge cheque from Microchip (even a little one would do), but it's still not come even after these many years of supporting them! Ah well, I suppose some things one does for love, not money!

DrDAQ Data Logger

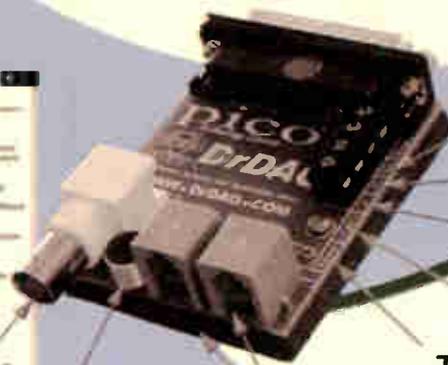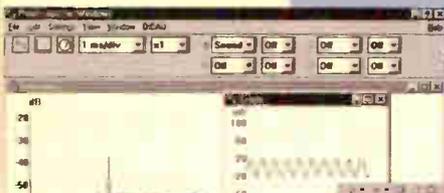

Output

Resistance

Voltage

Light level

Temperature

pH

Microphone

External sensors: Humidity

Temperature

O2 In Air


Reed Switch

- Low cost - under £60
- Built in sensors for light, temperature and sound (level and waveforms)
- Use DrDAQ to capture fast signals
- Outputs for control experiments
- Supplied with both PicoScope (oscilloscope) and PicoLog (data logging) software

For more information on DrDAQ, please visit:

www.picotech.com/ds/drdaq54

PC Oscilloscopes

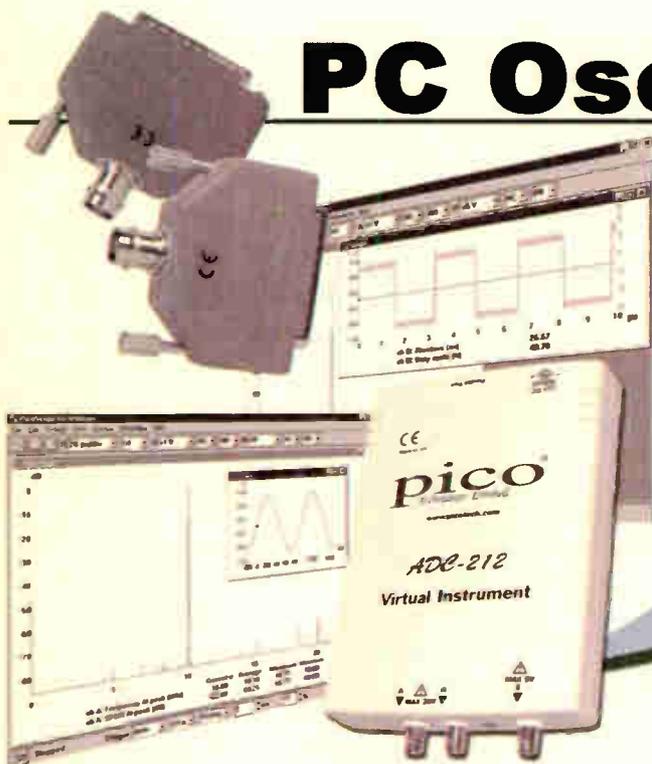

- Scope and spectrum analyser functions
- A fraction of the cost of benchtop scope
- Save multiple setups, for ease of use
- Save, print and e-mail your traces
- FREE technical support for life
- FREE software and upgrades
- Automated measurements

For more information on our scopes, please visit:

www.picotech.com/ds/scope71

Tel: 01480 396395 Fax: 01480 396296 E-mail: sales@picotech.com

PICO
Technology Limited

Constructional Project

BACK TO BASICS



BART TREPAK

Part Four

Illustrating how useful circuits can be designed simply using transistors.

LIVE WIRE DETECTOR

WHEN it comes to useful circuits using very few components, this one takes some beating, as a quick look at the component list will show. Using only three transistors, together with one resistor and a light emitting diode (l.e.d.), it performs a whole series of functions that make it useful for professional electricians and DIY enthusiasts alike.

Despite its extreme simplicity, it can be used to detect if a cable is live, identify the live conductor itself, and to test the fuse in a plug without even dismantling it. It can even be used to locate breaks in a circuit, which makes it ideal, for instance, for finding which lamp in the Christmas decorations has blown or become disconnected, causing the whole chain not to light.

As if this were not enough, it can even be used to test light bulbs, fuses and relay coils for continuity.

CIRCUIT DIAGRAM

The circuit diagram for the Live Wire Detector is shown in Fig.22. It is basically a very high gain amplifier, although no attempt has been made to minimise signal distortion. Indeed, it is not even biased, so it amplifies only the positive part of the sinusoidal mains frequency signal.

The fact that no base bias current is used is an advantage here. It means that when the circuit is not actively being used it draws no significant current, and so an on/off switch is not required.

The electric field, which exists around any conductor connected to an a.c. source, is remotely picked up by a short aerial wire or a small plate (such as a drawing pin)

that is connected to the base of transistor TR1. This field, which will exist even if the conductor is not actually carrying a current, will induce a voltage at the transistor base (b) causing it to turn on.

The alternating base current will, of course, be minute as the effective impedance in the base circuit (which consists of the stray capacitance between the conductor and the detector probe) is very high and the collector current is therefore very small.

The collector current, however, provides the base current for transistor TR2. The currents at the emitter (e) of TR1 and the collector (c) of TR2, jointly provide the base current for TR3. In effect, the three transistors form a super transistor, which has a gain equal to the product of their individual gains.

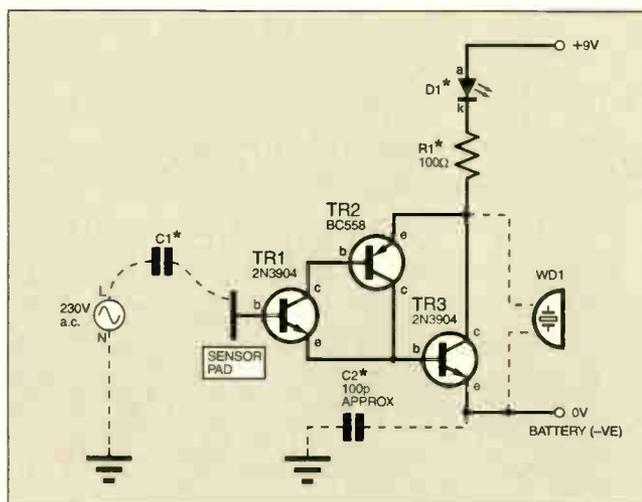


Fig.22. Circuit diagram for the Live Wire Detector.

The resulting current passing through TR3 via resistor R1 and l.e.d. D1, is large enough to light the l.e.d. Resistor R1 is included to limit the current. In fact, the l.e.d. flickers at the frequency of the electrical field source, at 50Hz for the UK

mains supply (60Hz for USA). This is because TR1 is only turned on when the voltage on its base goes positive, but this is too fast to be noticeable visually.

The effect can be used to advantage. By connecting a piezo sounder or high-impedance earpiece between the collector and emitter of transistor TR3, an audio indication of the presence of mains fields can be provided, in the form of a 50Hz buzz (60Hz in USA). If this is preferred to a visual indication, then the l.e.d. can be replaced by a link wire and the value of resistor R1 increased to 10k. A louder sound output will also result.

The l.e.d. will only be turned on when the sensor is brought close to the live conductor in a mains cable, enabling it to be easily identified. When the sensor is removed from near the cable, the l.e.d. will be turned off. The circuit's earth is effectively provided by the capacitance of the mains circuit supply to the user's hand, and the user's body capacitance to earth, which is around 100pF (depending on body size!).

Gluing aluminium foil to the inside of the plastic case and connecting it to the battery negative can increase the hand capacitance effect, although this is not usually necessary. These stray capacitances

COMPONENTS

Resistor		See
R1	100Ω	SHOP
Semiconductors		TALK
D1	red l.e.d., 5mm	page
TR1, TR3	2N3904 npn transistor (2 off)	
TR2	BC558 pnp transistor	
Miscellaneous		
WD1	piezo sounder or high impedance earpiece	

Stripboard, 8 holes x 8 strips; drawing pin (see text); PP3 9V battery; PP3 battery clip; plastic case to suit; connecting wire; solder, etc.

Approx. Cost
Guidance Only

£3
excl. case and battery

are shown in Fig.22 as capacitor C1 and C2, illustrating how stray capacitance, which can be a problem in many high gain and high frequency circuits, can sometimes be used to advantage.

Note that the mains Neutral is approximately at Earth potential, although it is not connected to it.

CONSTRUCTION

The circuit is built on a piece of stripboard, as shown in Fig.23. There are no track cuts required. Ensure that the transistors and l.e.d. are correctly orientated.

The piezo sounder, or earpiece, can be connected directly to the stripboard. or a suitable jack plug and socket arrangement can be used, as has been shown in previous designs in this series.

Mount the circuit inside a small plastic box, size and shape of your choosing, but which should be large enough to house the battery.

USING THE UNIT

The unit will perform many useful functions and can even replace a multimeter in some instances, especially if only a go/no go display is required. Bringing the sensor close to a live conductor will be indicated by the l.e.d. lighting. This can be used to identify the live conductor in a cable without the need for an electrical contact, as is generally the case with a neon type mains tester. **Do not use it close to an uninsulated live mains carrying conductor.**

The live terminal of a mains outlet socket can also be checked to ensure that it has been wired correctly. If the socket is fitted with an on/off switch, this should be switched on. Bringing the unit close to the N or E terminals should not cause the l.e.d. to turn on, but bringing it close to the terminal should.

FUSE CHECKER

The unit is also very useful in checking if the fuse in a mains plug is serviceable, without the bother of dismantling the plug or unplugging the appliance. This should be the first thing that should be checked when confronted by an apparently faulty appliance. It can be done simply by using this Live Wire Detector to check if the cable between the plug and appliance is live when the appliance is plugged in.

A blown fuse will be indicated by the l.e.d. not lighting, as will a disconnected live wire in the plug. Unfortunately, a disconnected neutral wire will not be revealed by this unit so that a visual inspection may be required, although disconnected wires in modern factory fitted moulded plugs are most unlikely.

LIGHTS CHECK

Older style Christmas Tree lights consist of a number of series-connected low voltage lamps (normally 20 x 12V or 40 x 6V) connected across the 230V mains supply. Any one of these failing open circuit or becoming disconnected will cause the whole chain to fail. Discovering the offending bulb can mean disconnecting, checking and reconnecting each bulb in turn. Murphy's Law ensures that it is usually one of the last bulbs checked which will be found to be the cause!

The chain is usually connected (starting at the plug) with a wire from the L terminal to the first bulb, the other end of which

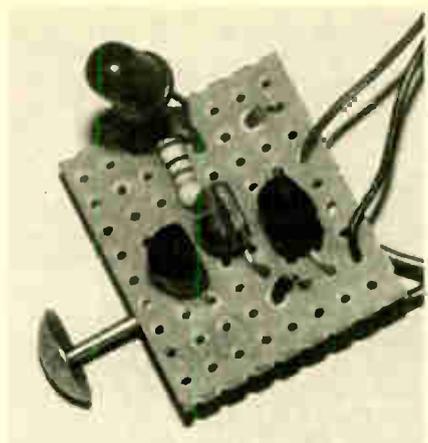
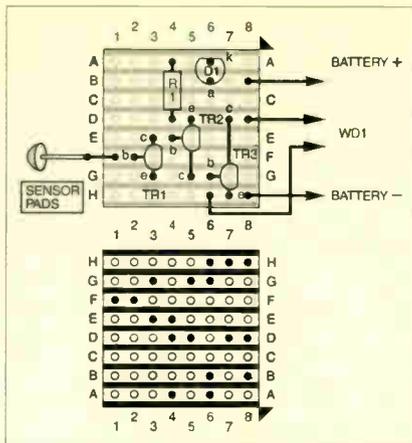


Fig.23. Live Wire Detector stripboard component layout and completed prototype circuit board. Note there are no breaks in the underside copper strips.

is connected by a short wire to the next bulb and so on down the chain with a long wire (twisted around the other wires) from the last bulb back to the N terminal in the plug.

If, say, the fourth bulb is faulty or has become disconnected, bringing the sensor close to the first, second, third and fourth bulbs in turn will cause the l.e.d. to light. But the l.e.d. will not light after the fourth bulb, indicating a fault there.


Where the conductors are twisted, it may be found that the circuit only responds along certain sections of the cable. This is because at various places the Live wire will be shielded from the sensor by the other conductor. It is important, therefore, to check along a good length of cable in case this effect gives the impression that a cable is not live when it is.

Bringing the sensor close to an earthed appliance should also not light the l.e.d. unless the earth cable is disconnected or broken so that this unit can also be used to check this.

TAKE CARE

It is clear that a non-lighting l.e.d. does not mean that a cable is safe as this could be due to the above shielding effect, or a poor sensor circuit Earth (if the user is on a ladder for instance). It could even be due to detector's battery being disconnected or exhausted! It is therefore most important that the unit is checked on a known live cable, or by touching the sensor, to ensure that the l.e.d. is operating, before testing an unknown conductor.

It will be noticed that touching the sensor normally only lights the l.e.d. briefly if the unit is held in the hand. If it is placed on an insulating surface, especially in a region with a high mains field (anywhere near a live conductor), it will glow brightly. This behaviour can be used to test light bulbs, fuses etc., by touching the sensor plate with one terminal of the component while holding the other in your hand. A blown fuse or bulb will not light the l.e.d., allowing continuity to be checked.

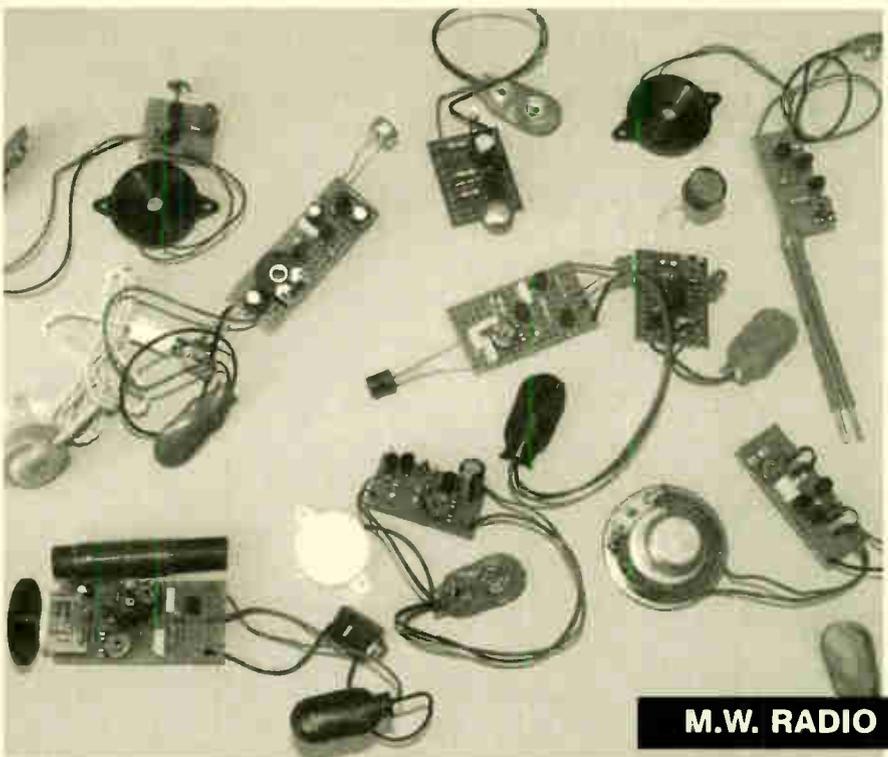

M.W. RADIO

Some of the simple transistor-based circuit assemblies described in this series.

MEDIUM WAVE RADIO

NO series about transistor circuits would be complete without a simple radio circuit and, although better performance is obtainable using integrated circuits, simple radios are still fun to build and use and have been popular since the first transistors were introduced, well over 50 years ago.

RADIO RULES

Before describing the operation of this circuit, it may be useful to review a few basic principles which govern radio transmission. Aerials (both transmitting and receiving) are much more efficient when their length is comparable to the wavelength of the signal to be used.

Since wavelength is inversely proportional to frequency, it is clear that lower frequencies require longer aerials. It is, therefore, impractical to try to transmit audio signals directly as this would require aerials several hundred kilometres long, so most radio transmissions are restricted to higher frequencies, above a few hundred kilohertz.

CARRY ON

To transmit any useful information (e.g. speech or music) this high frequency, which is called the *carrier frequency* must be modulated and various schemes exist for doing so. Frequency modulation (f.m.), where the frequency of the carrier is varied by the audio signal, is the most widely used for hi-fi transmissions, although amplitude modulation (a.m.) is still popular where lower quality is acceptable.

This is probably due to the ease with which an a.m. radio signal can be *demodulated* and the audio signal recovered. The use of a carrier also has the great advantage of permitting simultaneous transmission by a large number of radio stations, each on a different frequency, while still allowing the listener to tune into one particular station.

In Fig. 24 is shown a high frequency carrier which is amplitude modulated by a low frequency signal. In this case it is a sine wave, although it would more likely be a complex speech or music waveform. To receive this, a circuit that responds only to the carrier frequency (or a small range of frequencies around it) is required and here the tuned circuit, which we illustrated in the *Metal Detector* project (Part 2, March '03), can be used.

TUNED CIRCUIT

A tuned circuit has a low impedance at all frequencies except its resonant frequency (which is determined by the value of the inductor and capacitor used) so that all signals appearing at the aerial will be short circuited to earth, except the frequency to which the circuit is tuned.

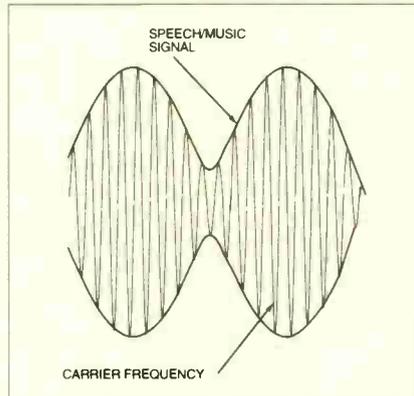
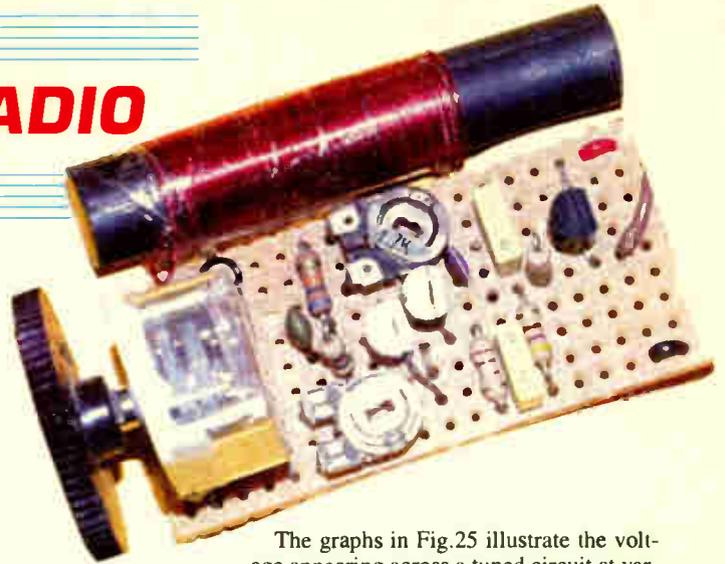


Fig. 24. The make-up of an amplitude modulated (a.m.) radio signal.

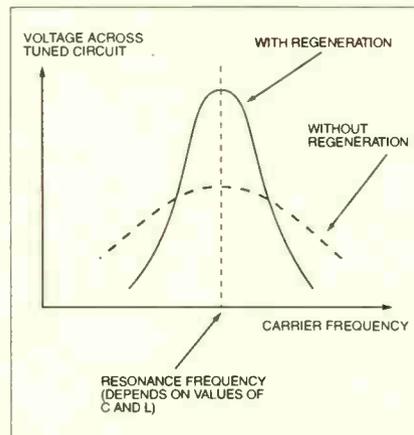


Fig. 25. Frequency response of a tuned circuit.

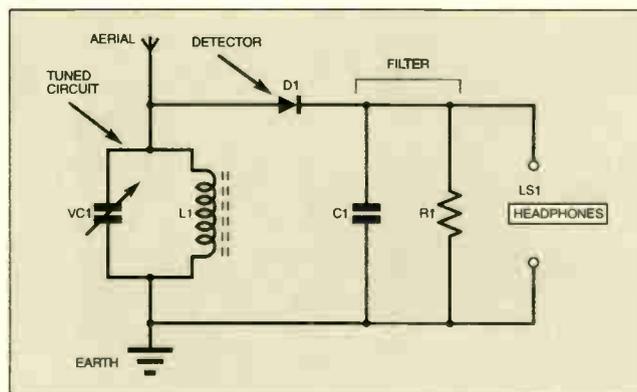


Fig. 26. Basic radio receiver circuit.

The graphs in Fig. 25 illustrate the voltage appearing across a tuned circuit at various frequencies. It will be seen that the voltage falls away gradually as the applied carrier frequency differs from the resonant frequency of the tuned circuit. Thus if all transmissions on all frequencies had an equal amplitude, the one coinciding with the resonant frequency would produce the largest output.

This is, of course, not the case as some transmitters radiate at lower power or are further away, resulting in a lower voltage at the receiver. For the best results it is clear that the peak response should be as "sharp" as possible to achieve maximum suppression of unwanted signals. This is governed by losses inherent in the tuned circuit and the smaller these are, the sharper will be the response.

BASIC CIRCUIT

A simple radio receiver circuit diagram is shown in Fig. 26. The tuned circuit is formed by an inductor, L1, and a variable capacitor, VC1. The latter enables a range of frequencies to be tuned in.

Assuming the transmitted signal is that in Fig. 24, the signal appearing across the tuned circuit will be identical. To recover the audio signal, the received signal must be demodulated. This can be done with a single diode, D1, which allows only the positive portion of the signal to pass. It is followed by a simple filter, consisting of capacitor C1 and resistor R1, which removes the high frequency carrier signal, leaving only the audio signal, which can be listened to via suitable headphones.

Given a long aerial and a good earth connection, together with very sensitive headphones, you may just about be able to receive a strong local a.m. station using this circuit. For a portable radio, however, it is useless, but it gives an idea of what is required to make a radio.

IMPROVEMENTS

Aerial signals smaller than the forward voltage of the diode (about 0.6V for a silicon diode) will not be passed to the headphones so the sensitivity of the circuit must be improved to allow weaker stations to be received.

The problem with using only one tuned circuit is that its response is too "flat" and with today's crowded wavebands, it is

difficult to select only one station and stronger stations transmitting on an adjacent frequencies to that required can interfere with reception. To improve the selectivity, commercial receivers use many more tuned circuits, but this leads to other problems that need much more complex circuits to resolve.

SENSITIVITY

The sensitivity of the radio can be improved simply by amplifying the aerial signal before it is fed to the detector, while to improve the selectivity, the losses inherent in the tuned circuit must be minimised to sharpen its response. As a first step, any impedance connected across the tuned circuit must be made high to load the tuned circuit as little as possible. Consequently the input impedance of the amplifier must be high.

The tuned circuit is coupled to the base of transistor TR1 by capacitor C1. The latter prevents the d.c. conditions from being upset by the low resistance of L1. The input impedance of this stage is high due to the large value bias resistor R2 and the resistance in the emitter circuit, provided by preset potentiometer VR1, so that the tuned circuit is only lightly loaded.

The circuit around transistor TR1 is very reminiscent of that used in the Metal Detector referred to earlier, in which the first transistor operated as an oscillator. Potentiometer VR1 is adjusted so that there is just insufficient positive feedback to sustain oscillation.

As the frequency to which the circuit is tuned increases, this feedback also increases but since the input impedance falls, the losses in the tuned circuit increase so that the circuit remains stable and VR1 should not need to be constantly re-adjusted.

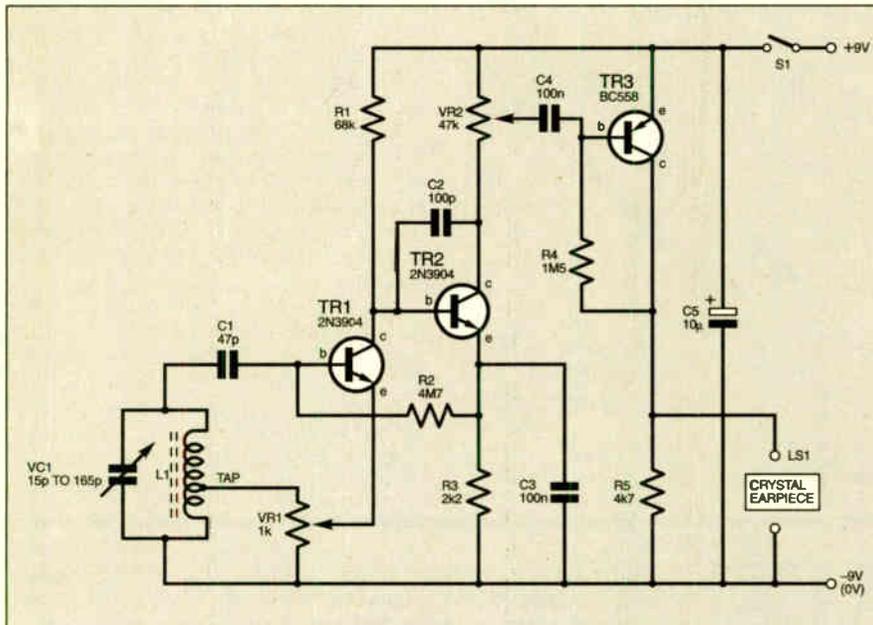


Fig.27. Practical circuit diagram for the Medium Wave Radio.

Another thing that can be done is to try to replace some of the tuned circuit losses by using positive feedback. However, this can lead to oscillation, and so the feedback level must be closely controlled. It is found that the selectivity is greatly improved if the circuit is just on the verge of oscillation.

Most circuits using this technique (which was called *regeneration* in old valve receivers) have a separate control to do this, but which is tricky to use, having to be adjusted for each station and is the reason why no modern commercial radios use it. With careful adjustment, though, it is possible to do away with this control and ensure that once set up, no further adjustment is required.

PRACTICAL CIRCUIT

The circuit diagram for a suitable receiver is shown in Fig.27. As in Fig.26, the tuned circuit is formed by inductor L1 and variable capacitor VC1. The coil acts not only as an inductor but also an aerial and the directional properties of the ferrite rod on which it is wound can also be useful to help eliminate unwanted stations from interfering with reception.

Transistor TR1 amplifies the signal appearing across the tuned circuit, boosting the sensitivity of the circuit and eliminating the need for an earth connection. No separate detector diode is used in this design as this function is carried out by the collector (c) of TR1.

Transistor TR2 further amplifies the signal but the gain at high frequency is very low due to the presence of capacitor C2, so that only the audio signal is amplified while the residual radio frequency carrier signal is suppressed. Using d.c. negative feedback via R2 stabilises the operating point of the two transistors, while capacitor C3 bypasses TR2's emitter resistor, R3, so increasing the gain of this stage at audio frequencies.

The collector load consists of poten-

COMPONENTS

Resistors		See SHOP TALK page
R1	68k	
R2	4M7	
R3	2k2	
R4	1M5	
R5	4k7	
Potentiometers		
VR1	1k skeleton preset	
VR2	47k skeleton preset	
Capacitors		
C1	47p ceramic	
C2	100p ceramic	
C3, C4	100n polyester (2 off)	
C5	10µ radial elect. 25V	
VC1	15p to 185p variable capacitor	
Semiconductors		
TR1, TR2	2N3904 npn transistor (2 off)	
TR3	BC558 pnp transistor	
Miscellaneous		
L1	Ferrite rod, 50mm x 10mm, with coil (see text)	
LS1	high impedance earpiece	

Stripboard, 19 holes x 9 strips; PP3 9V battery; PP3 battery clip; plastic case to suit; 28swg enamelled copper wire; solder, etc.

Approx. Cost
Guidance Only **£5**
excl. case, earpiece and battery

tiometer VR2, which forms a volume control enabling the signal level to TR3, the earpiece driver, to be varied.

CONSTRUCTION

The circuit is constructed on stripboard, as shown in Fig.28. Care must be taken to ensure that stray capacitance is minimised by keeping component leads as short as possible.

Aerial coil L1 is made by winding 10 turns of 28s.w.g. enamelled wire onto a


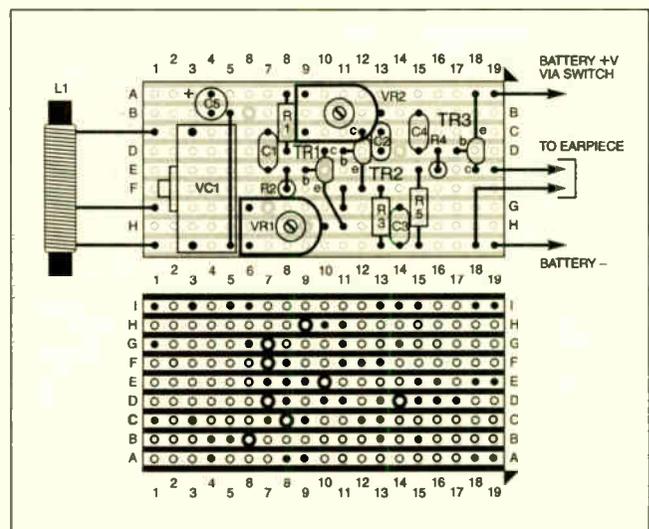


Fig.28. Radio stripboard component layout, wiring and details of breaks required in the underside copper tracks.

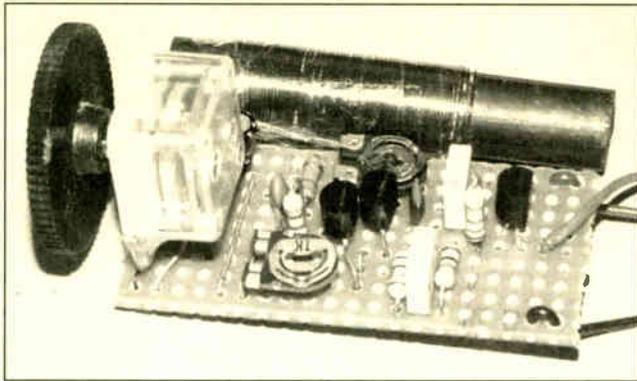

Completed radio showing the ferrite rod aerial.

piece of ferrite rod, 50mm long and 10mm in diameter. This forms the feedback winding and should be followed by a further 60 turns to form the main coil.

Each turn should be made adjacent to the previous one and the whole winding should be secured to the ferrite rod with insulation tape. The final number of turns may need to be adjusted (up or down) depending on the actual capacitance range of variable capacitor VC1, which is used to obtain the required medium waveband coverage.

Since it is easier to remove turns than to add them once the wire has been cut to length, it is preferable to initially wind slightly more turns than required.

A miniature tuning capacitor was used in the prototype for VC1, with a value range of 15pF to 165pF. The actual range is not too critical as most values can be accommodated by varying the number of turns on the coil, as just said, and/or connecting fixed capacitors across VC1 to adjust the range span.

TUNING CHECKS

Once construction is finished, VR1 and VR2 should be turned fully clockwise and a battery connected. Adjust VC1 until a station is heard and then adjust the signal amplitude using VR1. If the circuit oscillates

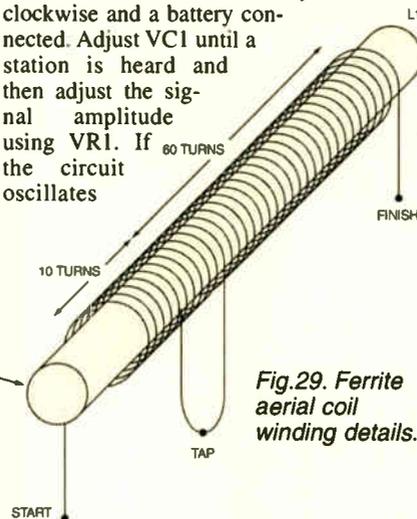


Fig.29. Ferrite aerial coil winding details.

(which is heard as a high pitched whistle in the earpiece) turn VR1 back slightly.

Turn VC1 fully clockwise and check that no oscillation occurs on other stations, re-adjusting VR1 if required. The circuit should now not oscillate, irrespective of which station is tuned in.

The circuit will draw about 2mA, so an on/off switch is required. Alternatively, a 3.5mm stereo jack socket can be fitted for the earpiece with the tip terminal connected to TR3's collector, the centre terminal connected to the circuit's 0V line (marked as Battery -V). The battery negative itself is then connected to the outer terminal.

Inserting the earpiece plug will short out these last two terminals, switching on the power to the circuit. The principle is similar to that in Fig.7 of Part 1, Feb. '03.

In the concluding part of this series, next month, we describe a Twilight Switch, and a simple circuit for that most fascinating of all musical instruments – the Theremin.

SHOP TALK

with David Barrington

Super Motion Sensor

Nearly all of the "miniature" light-dependent resistors we looked up in various components catalogues seem to be within the specification required for the *Super Motion Sensor* project. A suitable l.d.r. should certainly be stocked by many of our components advertisers.

The 12V relay used for this project **must** have switching contacts rated for the appliance it is going to be controlling. This may mean that it will not sit directly on the circuit board so you will have to mount it separately and "hard wire" the relay to the p.c.b.'s appropriate copper pads. The Telecom type, mentioned by the author, should be widely available, but do not forget to check the contact ratings before purchase.

The TL071 low noise, low distortion op.amp is a popular device and should not present any buying problems. It was selected particularly for its high input impedances, which are necessary for this circuit. The 4066 quad bilateral switch i.c. is another popular widely-stocked device.

The Sensor printed circuit board is available from the *EPE PCB Service*, code 391 (see page 359).

Back-To-Basics 4 – Live Wire Detector/M.W. Radio

Some readers may experience problems with a couple of parts for the *Medium Wave Radio*, one of this month's *Back-To-Basics* projects.

Most components suppliers carry a 100mm length by 10mm diameter ferrite rod, which means readers will have to cut it to size. One problem, ferrite is very brittle and great care will be needed when cutting this material. One suggestion is to score around the rod diameter, at the required length, and then give it

a "gentle" tap to snap it apart. We see that **WCN Supplies** (☎ 023 8066 0700) are currently "advertising" a 140mm x 10mm ferrite rod, with an unwanted tuning coil, at a reasonable price.

The specified tuning capacitor is normally found listed as a miniature "transistor radio" type. However, the favourite value is 20pF to 126pF, which should be OK for this simple radio. One was found listed by **ESR Components** (☎ 0191 251 4363 or www.esr.co.uk), code 896-110.

No component problems should be met with the *Live Wire Detector*, the second simple project this month.

Door Chime

The audio amplifier i.c. chosen for the *Door Chime* project is the TDA7052 power amp chip which, in fact, contains two amplifiers in a single 8-pin d.i.l. package. This device is widely held and should not present any buying difficulties. You should certainly give **Cricklewood Electronics** (☎ 020 8452 0161) a call as we understand they have stocks.

The rest of the components are standard "off-the-shelf" items. Your local DIY superstore should have a suitable front doorbell pushswitch, if you do not already have one, of course. The small printed circuit board is available from the *EPE PCB Service*, code 390 (see page 359).

PLEASE TAKE NOTE


Earth Resistivity Logger (April '03)

Page 292. The wrong operating frequency for the crystal X1 is listed in the Components box. This should be 3.6864MHz. The circuit diagram Fig.5 and text are correct.

Shoptalk (April '03)

We regret that we gave an incorrect telephone number for Farnell and that it should be 0113 263 6311. You can also use 0870 1200 200.

PIC Training & Development System

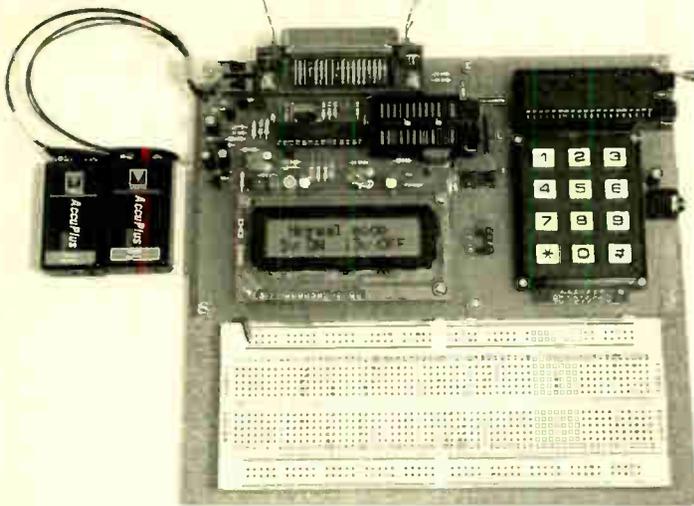

Programming PICs the Easy Way

Programming PICs the Easy Way is the title of a new 208 page book by Peter Brunning which is now included in our PIC Training & Development System. This new book provides a very fast start for any newcomer to PIC programming who needs to rapidly get to the situation where he or she can write their own programmes. This book starts with four very simple experiments where the programmes are written out in full detail so that the basic programming concepts are understood. In the rest of the book each chapter sets a specific task which creates a real life PIC controlled circuit. The complexity of the programming for these projects is hidden away in ready made subroutines. So although the reader is working in PIC assembly language it is used as if it were a high level language. This has the great advantage of allowing a newcomer to create their own complex programmes in the shortest time with the minimum amount of typing, while retaining all the advantages of working in PIC assembly language.

Projects:- Traffic Lights Controller, Simple Text Messages, Using the Keypad, Creating a Siren Sound, Realistic Dice Machine, Freezer Thaw Warning Device, Voltage Measurement and Temperature Measurement.

For readers with very little electronics experience appendix E introduces resistors, capacitors, diodes, transistors, MOSFETs and logic circuits.

The software suite has been updated to include the library routines and a system which allows break points to be placed in the programme in the actual PIC so that hardware problems can be more easily located.

Our PIC training and development system now consists of our universal mid range PIC programmer, a 208 page easy programming book, a 306 page book covering the PIC16F84, a 262 page book introducing the PIC16F877 family, and a suite of programmes to run on a PC. Two ZIF sockets and an 8 pin socket allow most mid range 8, 18, 28 and 40 pin PICs to be programmed. The plugboard is wired with a 5 volt supply. The software is an integrated system comprising a text editor, assembler disassembler, simulator and programming software. The programming is performed at normal 5 volts and then verified with plus and minus 10% applied to ensure that the device is programmed with a good margin and not poised on the edge of failure. The DC version requires a 15 to 20 volt supply with a 2.1mm plug which is not included (UK plugtop supply £8.95). The battery version requires two PP3 batteries which are not included.

Order Code P404:-

- Universal mid range PIC programmer module
- + Book Programming PICs the Easy Way
- + Book Experimenting with PIC Microcontrollers
- + Book Experimenting with the PIC16F877 (2nd edition)
- + Universal mid range PIC software suite
- + PIC16F84, 16F628 and 16F872 test PICs £179.91
- UK Postage (2 day) and insurance £ 9.00
- (Europe postage & Insurance ... £16.50. Rest of world . £32.50)

Order Code P405:-

- Universal mid range PIC programmer module
- + Book Programming PICs the Easy Way
- + Universal mid range PIC software suite
- + PIC16F628 and PIC16F872 test PICs £129.91
- UK Postage and insurance £ 7.50

Experimenting with PIC Micros

This book introduces the PIC16F84 and PIC16C711. We begin with four simple experiments, which are the same as in the easy programming book but this time using the PIC16F84. Then we study the basic principles of PIC programming, learn about the 8 bit timer, how to drive the liquid crystal display, create a real time clock, experiment with the watchdog timer, sleep mode, beeps and music, including a rendition of Beethoven's *Für Elise*. Finally there are two projects to work through, using the PIC16F84 to create a sinewave generator and investigating the power taken by domestic appliances. In the space of 24 experiments, two projects and 56 exercises the book works through from absolute beginner to experienced engineer level.

The best way to get the PIC programming language into your memory is to laboriously type every programme out in full so there are no short cuts in this book. However, we do understand that problems crop up where a typing error causes too much heart ache. If you do get stuck visit our web site, follow the instructions and we will email you the correct text.

Ordering Information


Telephone with Visa, Mastercard or Switch, or send cheque/PO to have your order immediately processed. Despatch is usually within 2 days of order being received unless we are out of stock. All prices include VAT if applicable. Postage must be added to all orders. Please state DC or battery version. If not stated battery version will be assumed.

Hardware required

Our PIC Training and Development System uses DOS based software which will run on any modern PC with a 386 processor or better. It is optimised for use with Windows 98. For other Windows systems the software should be run directly from DOS. Our website contains full information about Windows XP which also applies in general terms to Windows 2000 and Windows NT.

Please visit our website for full information:-

www.brunningsoftware.co.uk

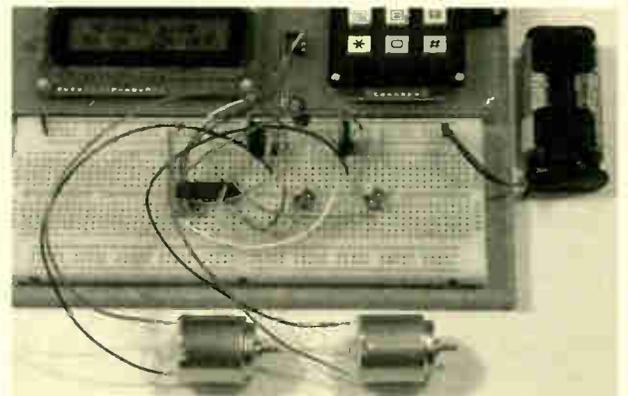

Experimenting with the PIC16F877

This book starts with the simplest of experiments to give us a basic understanding of the PIC16F877 family. Then we look at the 16 bit timer, efficient storage and display of text messages, simple frequency counter, use a keypad for numbers, letters and security codes, and examine the 10 bit A/D converter.

The 2nd edition has two new chapters. The PIC16F627 is introduced as a low cost PIC16F84. We use the PIC16F627 as a step up switching regulator, and to control the speed of a DC motor with maximum torque still available. Then we study how to use a PIC to switch mains power using an optoisolated triac driving a high current triac.


Mail order address:

Brunning Software 138 The Street, Little Clacton, Clacton-on-sea, Essex, CO16 9LS. Tel 01255 862308

SURFING THE INTERNET

NET WORK

ALAN WINSTANLEY

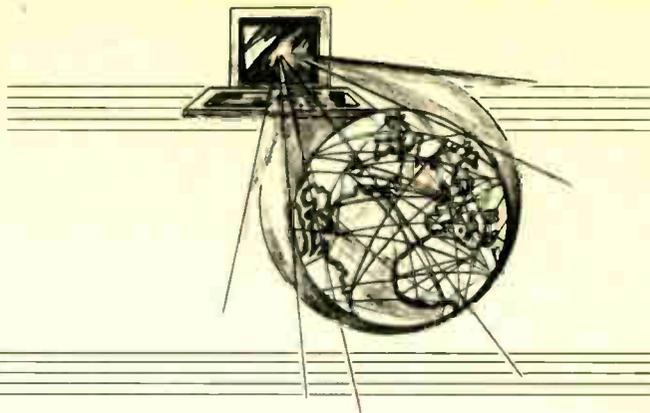

It's a Steal

IN last month's column the auction web site eBay (www.ebay.co.uk – or select your own country's web site) was described in further detail. eBay enables its members to sell a huge variety of products in its auctions, which run for a preset period that is timed accurately to the second.

When bidding for an item, it can be infuriating to lose the auction when a competing higher bid is entered just a few seconds before the auction closes. This is especially the case when struggling with dial-up access, as it is impossible to refresh the screen more than once or twice within the closing minute of the auction.

One way of clinching a deal is to place an earlier bid that is sufficiently high enough that no-one else will want to beat it; provided that a realistic grip is kept on the likely value of the item and you don't get too carried away with bidding, you can hopefully frustrate any competing bids if you pitch yours sensibly. (As an example of getting carried along with the bidding, the author recently noticed a copy of Adobe Photoshop 7.0 that sold for £460.00, which is fast approaching the maximum full retail price on the High Street, and nearly 40% above a typical eBay price.)

There is no substitute, though, for trumping the deal with your own bid placed only a few seconds before bidding is due to close. This last-moment winning bid is known as "sniping" and to the uninitiated eBay, losing an auction to a "sniper" can be infuriating! To the sniper though, such a victory can be immensely satisfying!

On the Line

The trick to successful sniping is to use an online bidding service. A search on Google for *auction stealing* or *auction sniping* will highlight a number of web sites that provide this service such as that offered by Auctionstealer (www.auctionstealer.com or www.auctionstealer.co.uk).

The service places a bid automatically on your behalf during the final few moments of an auction (note that some sniping services appear to use software running on your computer instead). This also relieves you of the onerous task of having to be present at your computer in order to place your bid just before closing time.

The Auctionstealer system is easy to use and works like magic: simply create a username and password, and then enter the number of the eBay item you are interested in, together with your maximum bid. As a free service, Auctionstealer will then enter your own bid ten seconds before the auction closes.

For low value items, this is a great way of having your bids entered automatically, without any need to watch the bidding for yourself. The process is seamless with the eBay auction site, so it appears to eBay that you have placed a bid just as you usually do. However the ten-second period does still offer scope for being outbid by others.

Premium Service

If you are keen to win what might be described as a

particularly "juicy-looking" item, then Auctionstealer offers a paid-for premium service starting with a \$1 fee per item, that will enter your bid just *three seconds* before closure. This leaves no time for anyone else to respond to your bid (unless another sniper has bid a higher price) and it has resulted in some wonderful deals being struck! The paid-for service also extends to monthly subscriptions for frequent bidders if desired.

Payment is made by Paypal; in fact in the author's case, buying a series of \$1 bids by Paypal resulted in the writer's credit card being locked by Visa, who viewed the series of small Internet transactions with suspicion. This became apparent when a major Internet purchase of a new TV was made the next day, because the credit card transaction was declined.

Overall, a combination of eBay's web site and Auctionstealer has produced a number of valuable "finds" and it's worth bookmarking both sites for future use.

Paying the Paypal Way


The problem mentioned above regarding credit card processing, which resulted in the writer's credit card being frozen, highlights the fact that trading on the Internet is becoming ever more difficult, mainly due to the increased security measures that the credit card companies and banks have put into place. In the UK it is not easy for new businesses to open an Internet merchant account anyway, so they may not be able to accept CC payments during their start-up phase.

Buyers and consumers should also be aware of the conditions now imposed by the credit card companies concerning the use of their credit card via the Internet. In particular, many CC providers, who demand that only a secure server be used for payments, expressly prohibit customers from sending a credit card number by open email (something that is very unwise to do anyway).

The writer recorded three \$1 payments to Paypal, then to make doubly sure that the subsequent Internet purchase of a TV was indeed genuine, the writer had to confirm this to Visa by phone, and they still sent a letter seeking further confirmation that the transaction was indeed genuine. The security of financial systems is being tightened up everywhere, to stamp out fraud and money-laundering.

Paypal (www.paypal.com) is the ubiquitous online credit card processing service now owned by eBay, which boasts of having 20 million registered users. The system sounds easy enough but is full of pitfalls for the unwary user or business owner. For example, their web site states "You can pay anyone with an email address . . . even if they don't have a Paypal account" ". . . The money will be sent directly to your recipient . . ."

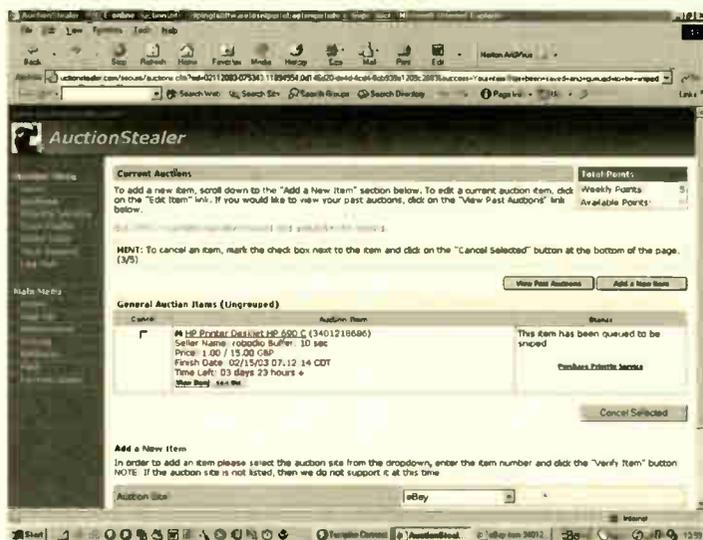Sounds easy enough, but is it? Next month we look more closely at Paypal and highlight some of the potential problems that exist when doing business the Paypal way. If you have your own Paypal story to tell or would like to comment, you can email me at alan@epemag.demon.co.uk. See you next month.



Auctionstealer allows last-second bids to be made.

Technobots Ltd

THE ONE STOP SHOP FOR THE ROBOT
BUILDER, RADIO CONTROL AND
ENGINEERING ENTHUSIAST



www.m2robot.com

Below is just a small selection of the thousands of products we supply, details of these and many more are available on-line at www.technobots.co.uk or contact us for a free catalogue

Secure on-line ordering at www.technobots.co.uk

Tel: 023 8077 4000 Fax: 023 8087 3776

YUASA SLA BATTERIES NP SERIES	
Ah - Voltage	Price
NP1-6	£12.31
NP1.2-6	£6.89
NP2.8-6	£8.58
NP4-6	£8.22
NP7-6	£20.68
NP10-6	£12.34
NP12-6	£12.45
NP0.8-12	£16.25
NP1.2-12	£9.03
NP2-12	£18.99
NP2.1-12	£10.26
NP2.3-12	£12.34
NP2.8-12	£11.49
NP3.2-12	£13.53
NP4-12	£14.68
NP7-12	£12.63
NP12-12	£27.43
NP17-12	£37.15
NP24-12	£47.25
NP38-12	£72.05
NP65-12	£111.81

YUASA SLA BATTERIES NPC SERIES	
Ah - Voltage	Price
NPC17-12	£38.78
NPC24-12	£49.90
NPC30-12	£59.10
NPC38-12	£78.44
NPC65-12	£114.04

Also available, the Hawker Odyssey range of batteries

NI-CADS	
Sanyo N-3000CR Fast charge / discharge	
1.2V 3000mAh	£3.35
Also available, Ni-Cad Ni-MH packs from 4.8V to 14.4V from 600 to 3000mAh	

BATTERY CHARGERS	
We have a range of chargers for SLA / Ni-CAD / Ni-MH batteries from 600mA to 20A	
LED VOLTMETERS	
Type	Price
12V 3LED	£4.50
24V 5 LED	£6.00
36V 5 LED	£6.00
36V 7LED	£8.50
4.8V Micro	£8.49
6.0V Micro	£8.49

MOTORS	
Voltage, A / W	Price
1.5 - 3V, 1.2A	£0.80
3-6V, 0.76A	£1.20
12-24V, 1A	£3.00
6-12V, 4.6A	£4.40
24V, 150W	£24.95
12V, 400W	£113.74
12V, 630W	£98.23
24V, 750W	£88.23
12V, 500W*	£74.97
12V, 800W*	£74.97
24V, 500W*	£74.97
24V, 800W*	£74.97
24V, 1200W*	£90.48

* Motor not continuously rated



150W 24V dc Motor-Just £24.95

ELECTRONIZE MOTOR SPEED CONTROLLERS	
These controllers plug direct into a standard RC radio receiver 2-24V (7-24V for controllers with BEC)	
Rating	Price
10A - Kit	£18.67
10A + BEC - Kit	£20.85
15A - Kit	£20.66
15A + BEC - Kit	£23.04
10A	£26.08
10A + BEC	£28.26
15A	£28.07
15A + BEC	£30.35
15A - CPU Based	£33.20
15A + BEC - CPU	£35.48
30A - CPU Based	£37.95



From £18.67

4QD MOTOR SPEED CONTROLLERS	
These controllers use a potentiometer or voltage input to set speed. For RC input, interfaces available	
Voltage / Current	Price
12V / 35A	£57.00
24V / 35A	£57.00
36V / 35A	£59.38
12V / 70A	£83.13
24V / 70A	£83.13
36V / 70A	£85.50
12V / 120A	£123.50
24V / 120A	£123.50
36V / 120A	£128.25
24/36V / 150A	£180.50
24.36V / 200A	£190.00
24/36V / 300A	£232.75



Just £107.99

Futaba radio control gear available at discount prices

Model	Price
Skysports 4	£107.99
Skysports 4	£107.99
Skysports 6	£120.79
Fieldforce 6	£215.94

These prices also include Ni-Cad batteries, charger, receiver, servo's and crystals. Upgrade options available.

- ALSO ON OUR WEB SITE**
- Cable 0.5mm to 16mm2
 - Cable ties
 - 2 pole connectors to 175A
 - 2 pole 300A terminal blocks
 - Extensive range of crimps
 - Radio control
 - Servo's
 - RC Crystals
 - RC Receivers
 - Gyro's
 - Pneumatic rams
 - Nylon tubing / hoses
 - Solenoid valves
 - Pressure regulators
 - CO2 extinguishers
 - Spur gears
 - Chain and sprockets
 - Polycarbonate
 - Mild steels
 - Aluminium to order
 - Titanium to order
 - Nuts & Bolts
 - Bearings
 - Wheels
 - Automotive relays
 - High pressure valves
 - Safety relief valves
 - Quick exhaust valves
 - Pressure gauges
 - High performance batteries + access to hundreds of thousands of other products

SUPPORT
Whether you are an experienced constructor or have never constructed a robot before, our technical people are always willing to offer advice. Email them on support@technobots.co.uk

LIVE EVENTS
There are many live events held around the country featuring many of the fighting robots you will recognise from the popular BBC TV show. Visit the events section on the Technobots web site and see if there is an event near you or even participate!

Technobots Ltd, Unit 17, Solent Business Centre, Millbrook Road west, Southampton, Hampshire SO15 0HW

Technobots is a mail order company but customers are welcome to visit our sales counter by appointment only due to our some times irregular opening hours. We accept payment by most major credit / debit cards, cheque, postal order and Technobots gift vouchers. Note carriage is extra and is charged by weight (details on our web site) and we deliver to worldwide destinations. All prices include VAT (not applicable for non EEC customers) currently at 17.5%. Minimum mail order charge £5.00. Please allow 5 days for dispatch of your goods subject to availability. Full terms and conditions available on our web site. Many prices discounted for quantity orders. Prices subject to change, latest prices as displayed on our web site.

PRACTICALLY SPEAKING

Robert Penfold looks at the Techniques of Actually Doing It!

ONE of the most common requests for help comes from readers who have gained some experience at building projects, and wish to move on to designing their own circuit boards. As to be expected there is a natural need for a progression from cloning published projects to a more "do your own thing" approach. Some wish to substantially modify existing designs or merge them, but the primary aim of most is to build from published circuits.

There are plenty of circuits published in books, on the Internet, and in *EPE's Ingenuity Unlimited* pages. In order to turn one of these into a working project it is necessary to work out your own circuit layout using stripboard, a custom printed circuit board, or whatever.

A custom printed circuit board certainly gives the neatest results. Designing and building their own printed circuit boards is something that many electronic project builders undertake routinely, but it is not the best place to start. Initially, it is better to use a simpler and more direct method that involves fewer skills and processes.

Stripboard is by far the most popular choice, but it would be a mistake to overlook plain matrix board. This was once a popular construction method, but these days it is mainly used for testing prototype circuits rather than for final construction.

Hole Truth

Plain matrix board is essentially stripboard minus the underside copper strips. There are expensive wiring systems available that utilize this type of board, but again, these are really aimed at the production of commercial prototypes.

Some solder, a plain matrix board and some single strand wire is all that is needed for project building. The general scheme of things is to fit the components onto the board in much the same way as for a custom board or stripboard.

However, instead of the leads being cut short and soldered to copper tracks on the underside of the board, they are bent over at right angles and used to carry the interconnections (see Fig.1). In other words, the leadout wires are used to replace the copper tracks of a normal printed circuit board.

Some modern components, such as integrated circuits and many capacitors, have pins instead of leadout wires. In other cases the component leads may simply be too short. In either case some 22s.w.g. or 24s.w.g. tinned copper wire can be used to bridge any gaps in the wiring.

If necessary, interconnections can be carried on the top side of the board by threading the wire up through one hole

in the board and then back down through another. This is the equivalent of a double-side printed circuit board or link-wires used on a stripboard, and it enables wires to cross without touching.

Plainly Speaking

Although no one is ever going to accuse plain matrix construction of looking particularly neat, this method of construction can have definite advantages. When designing any form of board layout it is important to bear in mind that there are stray couplings from one part of a circuit to another.

There can be inductive couplings, but it is coupling through stray capacitance that is the major problem in most cases. For instance, a capacitor is simply two pieces of metal separated by a layer of insulation, so two pieces of wire with air in between constitute a capacitor. Two copper tracks running side by side on a printed circuit board or a stripboard can also act as a capacitor.

The values involved are tiny, but a very small amount of capacitance in the wrong place can be sufficient to produce instability or other problems. The problem is most acute with circuits that involve large amounts of amplification and (or) operate at high frequencies.

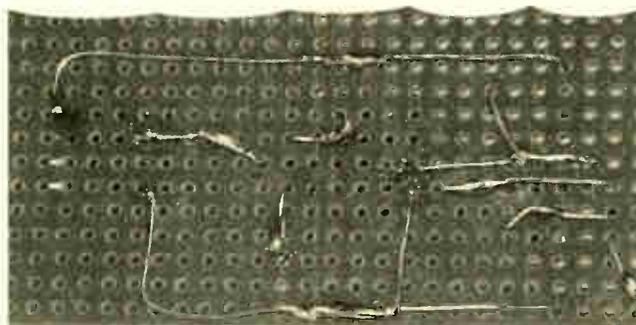


Fig.1. Plain matrix construction is not particularly neat but it is simple and efficient.

Going Astray

The stray capacitance problem is worst with stripboard because it has numerous copper tracks running the full length of the board, which produces a large number of built-in capacitors that are relatively high in value. There are ways of minimising the problem, such as making cuts in the strips to isolate unused pieces, or even peeling away unused bits of copper strip. An earthed strip can act as a screen between parts of a circuit where stray feedback could be a problem.

It can be a struggle to get some H.F. circuits to work on stripboard, and there is no guarantee of success. Plain matrix board does not eliminate these problems, but it keeps them to an absolute minimum. It is the equal of a custom printed circuit board in this respect.

Practically any type of project can be constructed on plain boards, but it can be awkward to use with some types of circuit. The main problem area is digital circuits that use numerous digital chips with huge numbers of interconnections.

This type of thing can be accommodated by plain matrix construction, but it can be very time consuming and difficult to produce neat and reasonably compact layouts. Construction times can also be very long.

The popularity of microcontrollers means that traditional digital circuits of this type are now something of a rarity, so the plain matrix approach is applicable to most modern circuits.

Initial Placements

Probably the most difficult part of designing board layouts is knowing where to start. This is almost certain to be a major sticking point for someone trying their first few board designs.

Initially, try a couple of board layouts for very simple projects. They can be done as pure exercises if there are no simple projects that you wish to build.

The circuit diagram shown in Fig.2 was featured in an *Interface* article, and it is designed to produce a low current +5V output from a PC printer port. This type of single chip circuit is ideal for initial attempts at board design.

A CAD program and a PC are ideal for drawing up this type of thing. All these programs can produce a grid of dots on the screen to aid the placement of lines and shapes, and the dots can be used to represent the holes in the board. Many people use graph paper when drawing up designs on paper, but drawing up your own chunkier version on plain paper using something like a 4H pencil is a better alternative.

Plain matrix board has the holes drilled on the usual 0.1 inch (2.54mm) matrix, but it is easier to see everything clearly if the designs are drawn at double life size. Initially anyway, draw the design as a top view only. Connecting wires can be represented as dashed lines, or drawn using a different colour to the one used for the top layer.

Getting Started

Start with a board outline that is definitely a lot wider than is required so that there is no risk of the design running out of space at one end. The height must have (say) five rows of holes to accommodate mounting holes, two for the supply rails, and sufficient rows between the supply rails for the circuit.

In the case of Fig.2, the 8-pin integrated circuit requires four rows, and

three or four rows should be included above and below to allow some room to manoeuvre. Making the board as small as possible is not a consideration, so four holes were used above and below the integrated circuit. This could be reduced to three or even two holes if space was limited.

Next the integrated circuit is drawn into place on its allotted rows of holes, somewhere near the middle of the board. The normal orientation for integrated circuits is with pin one at the top, but in this case the layout is likely to be easier with the chip the other way around (as indicated by the pin numbers).

With a custom printed circuit board it is possible to design a neat component layout and then join everything together with a complex track pattern. With plain matrix and stripboard construction it is better to "go with the flow", and use a component layout that gives simple and reasonably direct interconnections.

First Steps

The obvious first step is to draw the connections from IC1 to the supply rails, and in this case there are two pins that connect to the positive rail (pins 4 and 8). The simplest way of handling this is to add the supply connection for pin 4 and then add a connection between pins 4 and 8. The next step is to start adding the components to the design.

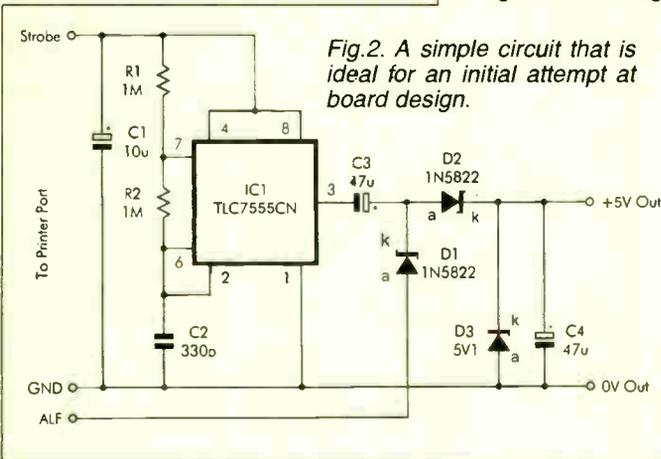


Fig. 2. A simple circuit that is ideal for an initial attempt at board design.

they are readily accessible. In the real thing these connections are made via solder pins on the board. The double-sided variety of pin is better for this method of construction, as these provide more for the wires on the underside of the board to be connected to.

You should end up with a design similar to that shown in Fig. 4; without the deliberate mistakes. The unused areas at each end of the board have been erased and the two mounting holes have been added. Two are sufficient for small boards, but for larger boards it is advisable to use one near each corner.

Final Analysis

Even with a simple design it is advisable to put it to one side for half

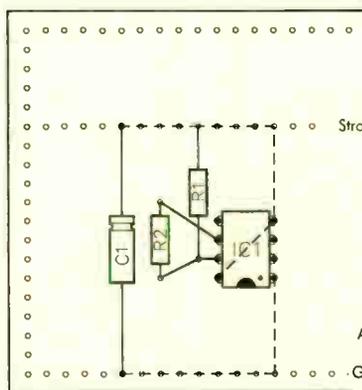


Fig. 3. Initial design stages.

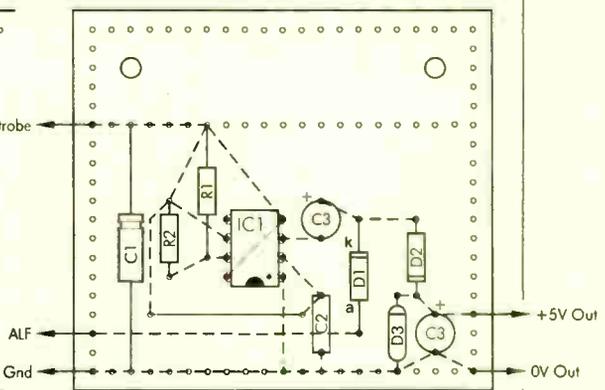


Fig. 4. Finished but unchecked design - spot the "deliberate" mistakes.

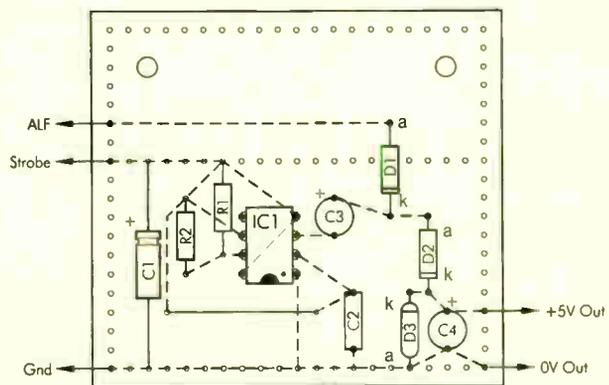


Fig. 5. Corrected and, hopefully, working design.

It is best to start by adding the components that connect to the integrated circuit and gradually work outwards. Resistors R1 and R2 can be added to the left of IC1, and capacitor C1 can be added between the supply rails. This gives a layout something like that shown in Fig. 3, but there is no single design that is right. There are usually numerous layouts that will give the desired set of interconnections.

The process continues with the components being added one by one, and linked to the rest of the design. The circuit diagram will usually act as a general guide to the physical layout, but it should not be slavishly followed. Have the components and a board handy when designing layouts on "paper". It is then easy to check that sufficient space is being left for each component.

Finally, the off-board connections are added, and they should preferably be at or near an edge of the board where

an hour or so and then give the design a thorough check. An advantage of this method of construction, and stripboard construction, is that any errors that make it through to the finished board can usually be corrected without too much trouble. A major blunder with a custom printed circuit board usually means building the whole thing again.

Even though errors are easily corrected it is better to get it right first time. Incorrect connections can cause expensive damage to the components, and there could be safety issues as well.

In the case of Fig. 4, there are a couple of obvious errors. The capacitor labelled C3 near the bottom right-hand corner of the board is actually C4. More importantly, the wire from the anode (a) of diode D1 to the solder pin crosses the 0V supply connection to IC1, and would short-circuit to it.

There are several possible solutions to this, and one of them is simply to leave the design unchanged, but with insulating plastic sleeving added to one of the wires. The solder pin could be moved to just below D1, but this would move it away from the other input connections. Another option is to weave one of the wires onto the top side of the board, over the other wire, and then back down again.

Yet another option is to do some juggling with the basic design. This is quite easy if a CAD program is being used, and a modified design of Fig. 4 is shown in Fig. 5.

Avoid making numerous changes simply because it is easy to do so. It is easy to end up in a situation where

two errors are added for each one that is corrected. In a similar vein, too much tidying up in an attempt to make the design "pretty" can add errors into what was previously a working layout.

Grand Designs

Producing layouts for larger circuits uses the same basic methods. Larger circuits break down into a number of circuit blocks, and with modern designs there is usually an integrated circuit at the heart of each block. Take things stage-by-stage, gradually building up the design.

Plain matrix board is not well suited to really large projects, but with small and medium sized circuits it represents an easy way of getting started with your own layouts. Unlike stripboard construction, it should work first time with temperamental circuits where stray capacitance can be a problem.

EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS


ELECTRONICS PROJECTS



Logic Probe testing

Electronic Projects is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included. The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.

ELECTRONICS CAD PACK

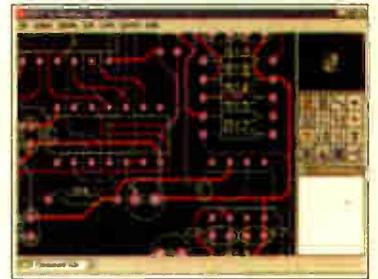

PCB Layout

Electronics CADPACK allows users to design complex circuit schematics, to view circuit animations using a unique SPICE-based simulation tool, and to design printed circuit boards. CADPACK is made up of three separate software modules. (These are restricted versions of the full Labcenter software.) **ISIS Lite** which provides full schematic drawing features including full control of drawing appearance, automatic wire routing, and over 6,000 parts. **PROSPICE Lite** (integrated into ISIS Lite) which uses unique animation to show the operation of any circuit with mouse-operated switches, pots, etc. The animation is compiled using a full mixed mode SPICE simulator. **ARES Lite** PCB layout software allows professional quality PCBs to be designed and includes advanced features such as 16-layer boards, SMT components, and an autorouter operating on user generated Net Lists.


ELECTRONIC CIRCUITS & COMPONENTS V2.0



Circuit simulation screen

Provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals:** units & multiples, electricity, electric circuits, alternating circuits. **Passive Components:** resistors, capacitors, inductors, transformers. **Semiconductors:** diodes, transistors, op.amps, logic gates. **Passive Circuits. Active Circuits. The Parts Gallery** will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.

ANALOGUE ELECTRONICS

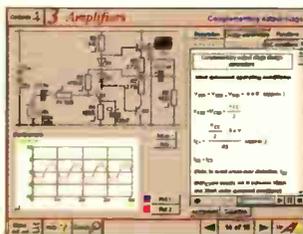


Complimentary output stage

Analogue Electronics is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits.

Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections), **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections). **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections). **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

ROBOTICS & MECHATRONICS

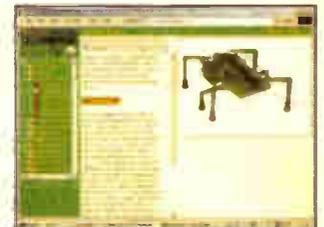


Case study of the Milford Instruments Spider

Robotics and Mechatronics is designed to enable hobbyists/students with little previous experience of electronics to design and build electromechanical systems. The CD-ROM deals with all aspects of robotics from the control systems used, the transducers available, motors/actuators and the circuits to drive them. Case study material (including the NASA Mars Rover, the Milford Spider and the Furby) is used to show how practical robotic systems are designed. The result is a highly stimulating resource that will make learning, and building robotics and mechatronic systems easier. The Institutional versions have additional worksheets and multiple choice questions.

- Interactive Virtual Laboratories
- Little previous knowledge required
- Mathematics is kept to a minimum and all calculations are explained
- Clear circuit simulations


DIGITAL ELECTRONICS V2.0

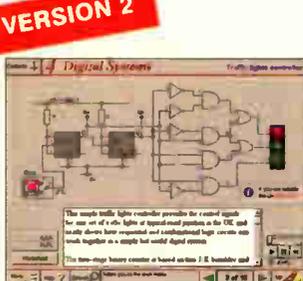

Virtual laboratory – Traffic Lights

Digital Electronics builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (opposite), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen. Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units. Sections on Boolean Logic and Venn diagrams, displays and chip types have been expanded in Version 2 and new sections include shift registers, digital fault finding, programmable logic controllers, and microcontrollers and microprocessors. The Institutional versions now also include several types of assessment for supervisors, including worksheets, multiple choice tests, fault finding exercises and examination questions.

FILTERS

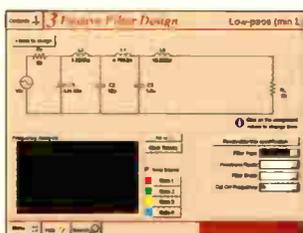

Filter synthesis

Filters is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev op.amp filters.

PRICES

Prices for each of the CD-ROMs above are:

(Order form on third page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student£45 inc VAT
 Institutional (Schools/HE/FE/Industry).....£99 plus VAT
 Institutional 10 user (Network Licence)£199 plus VAT
 Site Licence.....£499 plus VAT

PICmicro TUTORIALS AND PROGRAMMING

HARDWARE

VERSION 2 PICmicro MCU DEVELOPMENT BOARD

Suitable for use with the three software packages listed below.

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 13 individual I.e.d.s, quad 7-segment display and alphanumeric I.c.d. display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- All inputs and outputs available on screw terminal connectors for easy connection



£145 including VAT and postage

12V 500mA plug-top PSU (UK plug) £7

25-way 'D' type connecting cable £5

SOFTWARE

Suitable for use with the Development Board shown above.

ASSEMBLY FOR PICmicro V2 (Formerly PICtutor)

Assembly for PICmicro microcontrollers V2.0 (previously known as PICtutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes. The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller. This is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed which enhances understanding.

- Comprehensive instruction through 39 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.




Virtual PICmicro

'C' FOR PICmicro VERSION 2

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

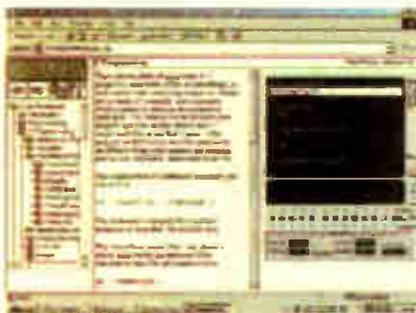- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running Windows 98, NT, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.

FLOWCODE FOR PICmicro

Flowcode is a very high level language programming system for PICmicro microcontrollers based on flowcharts. Flowcode allows you to design and simulate complex robotics and control systems in a matter of minutes.

Flowcode is a powerful language that uses macros to facilitate the control of complex devices like 7-segment displays, motor controllers and I.c.d. displays. The use of macros allows you to control these electronic devices without getting bogged down in understanding the programming involved.

Flowcode produces MPASM code which is compatible with virtually all PICmicro programmers. When used in conjunction with the Version 2 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols (ISO5807)
- Full on-screen simulation allows debugging and speeds up the development process
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 8, 18, 28 and 40-pin devices
- Institutional versions include virtual systems (burglar alarms, car parks etc.).



Burglar Alarm Simulation

PRICES

Prices for each of the CD-ROMs above are:

(Order form on next page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student
Institutional (Schools/HE/FE/Industry)
Flowcode Institutional
Institutional 10 user (Network Licence)
Site Licence

£45 inc VAT
£99 plus VAT
£70 plus VAT
£249 plus VAT
£599 plus VAT

TEACH-IN 2000 – LEARN ELECTRONICS WITH EPE

EPE's own *Teach-In* CD-ROM, contains the full 12-part *Teach-In* series by John Becker in PDF form plus the *Teach-In* interactive software covering all aspects of the series. We have also added Alan Winstanley's highly acclaimed *Basic Soldering Guide* which is fully illustrated and which also includes *Desoldering*. The *Teach-In* series covers: Colour Codes and Resistors, Capacitors, Potentiometers, Sensor Resistors, Ohm's Law, Diodes and L.E.D.s, Waveforms, Frequency and Time, Logic Gates, Binary and Hex Logic, Op.amps, Comparators, Mixers, Audio and Sensor Amplifiers, Transistors, Transformers and Rectifiers, Voltage Regulation, Integration, Differentiation, 7-segment Displays, L.C.D.s, Digital-to-Analogue.



Sine wave relationship values


Each part has an associated practical section and the series includes a simple PC interface so you can use your PC as a basic oscilloscope with the various circuits.

A hands-on approach to electronics with numerous breadboard circuits to try out.


£12.45 including VAT and postage. Requires Adobe Acrobat (available free from the Internet – www.adobe.com/acrobat).

FREE WITH EACH TEACH-IN CD-ROM – *Electronics Hobbyist Compendium* 80-page book by Robert Penfold. Covers Tools For The Job; Component Testing; Oscilloscope Basics.

FREE BOOK WITH TEACH-IN 2000 CD-ROM

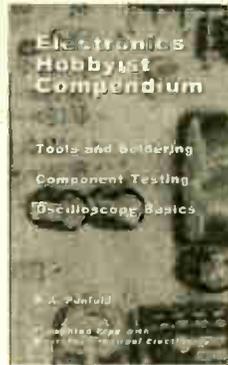

DIGITAL WORKS 3.0

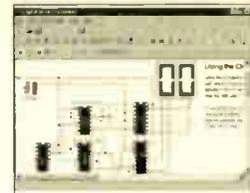

Counter project

Digital Works Version 3.0 is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability • Software for simulating digital logic circuits • Create your own macros – highly scalable • Create your own circuits, components, and i.c.s • Easy-to-use digital interface • Animation brings circuits to life • Vast library of logic macros and 74 series i.c.s with data sheets • Powerful tool for designing and learning. **Hobbyist/Student £45 inc. VAT. Institutional £99 plus VAT. Institutional 10 user £199 plus VAT. Site Licence £499 plus VAT.**

ELECTRONICS IN CONTROL


Two colourful animated courses for students on one CD-ROM. These cover Key Stage 3 and GCSE syllabuses. **Key Stage 3:** A pictorial look at the Electronics section featuring animations and video clips. Provides an ideal introduction or revision guide, including multi-choice questions with feedback. **GCSE:** Aimed at the Electronics in many Design & Technology courses, it covers many sections of GCSE Electronics. Provides an ideal revision guide with Homework Questions on each chapter. Worked answers with an access code are provided on a special website.

Single User £29 inc. VAT. Multiple User £39 plus VAT
Student copies (available only with a multiple user copy) **£6 plus VAT**
(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

MODULAR CIRCUIT DESIGN

Contains a range of tried and tested analogue and digital circuit modules, together with the knowledge to use and interface them. Thus allowing anyone with a basic understanding of circuit symbols to design and build their own projects. Version 3 includes data and circuit modules for a range of popular PICs; includes PICAXE circuits, the system which enables a PIC to be programmed without a programmer, and without removing it from the circuit. Shows where to obtain free software downloads to enable BASIC programming. Essential information for anyone undertaking GCSE or "A" level electronics or technology and for hobbyists who want to get to grips with project design. Over seventy different Input, Processor and Output modules are illustrated and fully described, together with detailed information on construction, fault finding and components, including circuit symbols, pinouts, power supplies, decoupling etc.

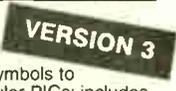Single User £19.95 inc. VAT. Multiple User £34 plus VAT
(UK and EU customers add VAT at 17.5% to "plus VAT" prices)



ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 JPG images of electronic components. This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details).



Also contains a **FREE** 30-day evaluation of Paint Shop Pro 6 – Paint Shop Pro image editing tips and on-line help included!

Price £19.95 inc. VAT

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 95/98/NT/2000/ME/XP, mouse, sound card, web browser.

Please send me:

CD-ROM ORDER FORM

- Electronic Projects
- Electronic Circuits & Components V2.0
- Analogue Electronics
- Digital Electronics V2.0
- Filters
- Electronics CAD Pack
- Robotics & Mechatronics
- Assembler for PICmicro
- 'C' for PICmicro
- Flowcode for PICmicro
- Digital Works 3.0

Version required:

- Hobbyist/Student
- Institutional
- Institutional 10 user
- Site licence



- PICmicro Development Board (hardware)
- Development Board UK plugtop power supply
- Development Board 25-way connecting lead

- Teach-In 2000 + FREE BOOK
- Electronic Components Photos
- Electronics In Control – Single User
- Electronics In Control – Multiple User
- Modular Circuit Design – Single User
- Modular Circuit Design – Multiple User

Note: The software on each version is the same, only the licence for use varies.

Full name:

Address:

Post code: Tel. No:

Signature:

I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

Please charge my Visa/Mastercard/Amex/Diners Club/Switch: £ Card expiry date:

Card No: Switch Issue No.

Card Security Code (The last 3 digits on or just under the signature strip)

ORDERING

ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world
EU residents outside the UK add £5 for airmail postage per order

Institutional, Multiple User and Deluxe Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU (European Union) country, then add 17½% VAT or provide your official VAT registration number).

Send your order to:

Direct Book Service
Wimborne Publishing Ltd
408 Wimborne Road East
Ferndown, Dorset BH22 9ND

To order by phone ring

01202 873872. Fax: 01202 874562

Goods are normally sent within seven days

E-mail: orders@wimborne.co.uk

Online shop:

www.epemag.wimborne.co.uk/shopdoor.htm

PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872; Fax 01202 874562; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm.** Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).
NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail.
Back numbers or photostats of articles are available if required – see the Back Issues page for details. We do not supply kits or components for our projects.
Please check price and availability in the latest issue.
A number of older boards are listed on our website.
 Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
Doorbell Extender: Transmitter	MAR '01 292	£4.20
Receiver	293	£4.60
Trans/Remote	294	£4.28
Rec./Relay	295	£4.92
EPE Snug-bug Heat Control for Pets	APR '01 296	£6.50
Camcorder Mixer	MAY '01 299	£6.34
★PIC Graphics L.C.D. Scope	300	£5.07
Hosepipe Controller	JUNE '01 301	£5.14
Magfield Monitor (Sensor Board)	302	£4.91
Dummy PIR Detector	303	£4.36
★PIC16F87X Extended Memory Software only	-	-
Stereo/Surround Sound Amplifier	JULY '01 304	£4.75
Perpetual Projects Uniboard-1 Solar-Powered Power Supply & Voltage Reg. MSF Signal Repeater and Indicator	305	£3.00
Repeater Board	306	£4.75
Meter Board	307	£4.44
★PIC to Printer Interface	308	£5.39
Lead/Acid Battery Charger	AUG '01 309	£4.99
Shortwave Loop Aerial	310	£5.07
★Digitimer – Main Board	311	£6.50
– R.F. Board	312	£4.36
Perpetual Projects Uniboard-2 L.E.D. Flasher – Double Door-Buzzer	305	£3.00
Perpetual Projects Uniboard-3 Loop Burglar Alarm, Touch-Switch Door-Light and Solar-Powered Rain Alarm	SEPT '01 305	£3.00
L.E.D. Super Torches – Red Main	313	} Set £6.10
– Display Red	314	
– White L.E.D.	315	
★Sync Clock Driver	316	£5.94
★Water Monitor	317	£4.91
Camcorder Power Supply	OCT '01 318	£5.94
PIC Toolkit Mk3	319	£8.24
Perpetual Projects Uniboard-4. Gate Sentinel, Solar-powered Bird Scarer and Solar-Powered Register	305	£3.00
Teach-In 2002 Power Supply	NOV '01 320	£4.28
Lights Needed Alert	321	£5.39
Pitch Switch	322	£5.87
Capacitance Meter – Main Board (double-sided) – Display Board (double-sided)	323	} Set £12.00
324		
★ ★PIC Toolkit TK3 – Software only	-	-
4-Channel Twinkling Lights	DEC '01 325	£6.82
Ghost Buster – Mic	326	} Set £5.78
– Main	327	
★PIC Polywhatsit – Digital	328	} Set £7.61
– Analogue	329	
Forever Flasher	JAN '02 330	£4.44
Time Delay Touch Switch	331	£4.60
★PIC Magick Musick	332	£5.87
Versatile Bench Power Supply	333	£5.71
★PIC Spectrum Analyser	FEB '02 334	£7.13
Versatile Current Monitor	335	£4.75
Guitar Practice Amp	336	£5.39
★PIC Virus Zapper	MAR '02 337	£4.75
RH Meter	338	£4.28
★PIC Mini-Enigma – Software only	-	-
★Programming PIC Interrupts – Software only	-	-
★PIC Controlled Intruder Alarm	APR '02 339	£6.50
★PIC Big Digit Display	MAY '02 341	£6.02
Washing Ready Indicator	342	£4.75
Audio Circuits-1 – LM386N-1	343	£4.28
– TDA7052	344	£4.12
– TBA820M	345	£4.44
– LM380N	346	£4.44
– TDA2003	347	£4.60
– Twin TDA2003	348	£4.75
World Lamp	JUNE '02 340	£5.71
Simple Audio Circuits-2 – Low, Med and High Input Impedance Preamplifiers (Single Trans.)	349	£4.60
Low-Noise Preamplifier (Dual Trans.)	350	£4.75
Tone Control	351	£4.60
Bandpass Filter	352	£4.75
Frequency Standard Generator – Receiver	353	£4.12
– Digital	354	£6.82
★Biopic Heartbeat Monitor	355	£5.71

PROJECT TITLE	Order Code	Cost
Simple Audio Circuits – 3	JULY '02	
– Dual Output Power Supply	356	£4.60
– Crossover/Audio Filter	357	£4.44
Infra-Red Autoswitch	358	£4.91
★EPE StyloPIC	359	£6.50
Rotary Combination Lock – Main Board	360	£5.39
– Interface Board	361	£4.91
★Using the PIC's PCLATH Command – Software only	-	-
Big-Ears Buggy	AUG '02 362	£5.71
★PIC World Clock	363	£5.39
Simple Audio Circuits-4 – Low Freq. Oscillator	364	£4.44
– Resonance Detector	365	£4.28
Vinyl-To-CD Preamplifier	SEPT '02 366	£5.71
★Freebird Glider Control	367	£4.91
★Morse Code Reader	368	£5.23
Headset Communicator	OCT '02 369	£4.75
EPE Bounty Treasure Hunter	370	£4.77
★Digital I.C. Tester	371	£7.14
★PIC-Pocket Battleships – Software only	-	-
Transient Tracker	NOV '02 372	£4.75
★PICAXE Projects-1: Egg Timer; Dice Machine; Quiz Game Monitor (Multiboard)	373	£3.00
★Tuning Fork & Metronome	374	£5.39
★ ★EPE Hybrid Computer – Main Board	375	£18.87
– Atom Board	376	£11.57
★PICAXE Projects-2: Temperature Sensor; Voltage Sensor; VU Indicator (Multiboard)	DEC '02 373	£3.00
★Versatile PIC Flasher	377	£5.07
★PICAXE Projects-3: Chaser Lights 6-Channel Mains Interface	JAN '03 373	£3.00
EPE Minder – Transmitter	381	£5.08
– Receiver	378	£4.75
★Wind Speed Monitor	379	£5.39
Tesla Transformer	380	£5.08
★Brainbot Buggy	FEB '03 382	£5.07
★Wind Tunnel	383	£3.00
200kHz Function Generator	384	£6.02
Wind-Up Torch Mk II	MAR '03 385	£6.34
★Driver Alert	386	£4.75
★Earth Resistivity Logger	387	£6.35
★Intelligent Garden Lights Controller	APR '03 388	£6.02
★PIC Tutorial V2 – Software only	389	£3.96
Door Chime	-	-
Super Motion Sensor	MAY '03 390	£5.07
	391	£5.55

EPE SOFTWARE

Software programs for *EPE* projects marked with a single asterisk ★ are available on 3.5 inch PC-compatible disks or free from our internet site. The following disks are available: **PIC Tutorial** (Mar-May '98); **PIC Tutorial V2** (Apr-June '03); **EPE Disk 1** (Apr '95-Dec '98); **EPE Disk 2** (1999); **EPE Disk 3** (2000); **EPE Disk 4** (2001); **EPE Disk 5** (2002); **EPE Disk 6** (Jan 2003 issue to current cover date – excl. Earth Resistivity); **EPE Earth Resistivity Logger** (Apr-May '03); **EPE Teach-In 2000**; **EPE Spectrum**; **EPE Interface Disk 1** (October '00 issue to current cover date). ★★ The software for these projects is on CD-ROM. The 3.5 inch disks are £3.00 each (UK), the CD-ROMs are £6.95 (UK). Add 50p each for overseas surface mail, and £1 each for airmail. All are available from the *EPE PCB Service*. All files can be downloaded free from our internet FTP site: <ftp://ftp.epemag.wimborne.co.uk>.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code	Project	Quantity	Price
Name			
Address			
Tel. No.			
I enclose payment of £..... (cheque/PO in £ sterling only) to:			
			
Everyday Practical Electronics			
MasterCard, Amex, Diners Club, Visa or Switch			
Card No.			
Card Exp. Date		Switch Issue No	
Card Security Code			
(The last 3 digits on or just under the signature strip)			
Signature			
NOTE: You can also order p.c.b.s by phone, Fax, Email or via our internet site on a secure server: http://www.epemag.wimborne.co.uk/shopdoor.htm			

Constructional Project

EARTH RESISTIVITY LOGGER

JOHN BECKER



Part Two

Help your local archaeological society to locate and reveal the hidden mysteries of our ancestors.

IN Part One last month we discussed the principles of earth resistivity monitoring and described the construction of a circuit through which this could readily be accomplished and the data stored for computer analysis. This month we detail the software that can help in this analysis, and then examine some of the soil probing techniques. The latest updates to the software are then discussed, followed by briefly considering the ethics of surveying and some practical advice and a list of further reading.

PC SOFTWARE

The Earth Resistivity Logger's PC software is written in Visual Basic 6 (VB6). It has been proved under Windows 95, 98 and ME. It has not been tested with Windows NT, XP or 2000 as the author does not have these systems.

Readers who wish to try running the software under the last three systems may find benefit from reading Mark Jones' article *Running TK3 under Windows XP and 2000*, published in Oct '02.

There are six screens associated with the Logger's VB6 program:

- Main screen as shown below, through which sectional analysis of the survey data is performed
- Full graph screen on which all 128 × 128 download amplitude values are displayed graphically, in oscilloscope fashion (bottom photo on next page)
- Full grid screen on which all 128 × 128 download values are displayed as grid squares having amplitude-related hues or greys (top photo on next page)
- Download screen through which data retrieval from the Logger is initiated
- Directory screen through which previously recorded survey logging files can be loaded for on-screen analysis
- Error Message screen – which hopefully you will never see! This comes into action if the VB6 software detects various types of error (such as trying to load a named file which does not exist). It does not intercept errors which occur outside VB6's specified

error interception repertoire as programmed by the author – the PC itself will report any such unlikely events.

MAIN PC SCREEN

The main screen offers several options to enable you to analyse the data received from the Logger. It must be said, though, that the facilities offered through the Windows Excel software supported by most PCs probably exceed what this screen can offer – more on Excel later.

There are two main areas on this screen, as seen in its screen-dump photograph.

To the right is a 20 × 20 grid block of squares, arranged so that the vertical axis represents the survey site columns, and the horizontal axis the site rows. The site data values determine the colour or grey-scale appearance of each of these squares. Two scroll bars are provided which allow the grid data coordinates to be panned vertically and horizontally so that all 16384 values of a 128 × 128 survey grid can be viewed in 400-sample blocks, seamlessly joined.

The range of coordinates from the grid matrix displayed is stated below it. To know the precise coordinate of any square, add the values (numbered 0 to 19) indicated alongside the edges of the matrix.

GRID COLOURING

There is a choice of four options regarding the colour shade range, as shown at the left of the screen. The lefthand bargraph display shows the grey-scale range available, from white to black, 36 shades in all, representing values from 0 (white) to full black (35).


The second bargraph shows a 36-value range of "rainbow" colour shades arranged in the order that VB6 offers them in the system's own (peculiar!) numerical order. They are allocated by the program to represent 0 (top) to 35 (bottom).

Bargraph 3 is a monochrome scale of colours essentially in the green range but with varying intensities of red added. The 36 shades are again numbered from top to bottom as 0 to 35.

The 8-colour bargraph shows the "primary" colours offered by VB6, numbered 0 to 7, top to bottom.

The quality and definition of the scale shades may vary depending on the quality of your VDU.

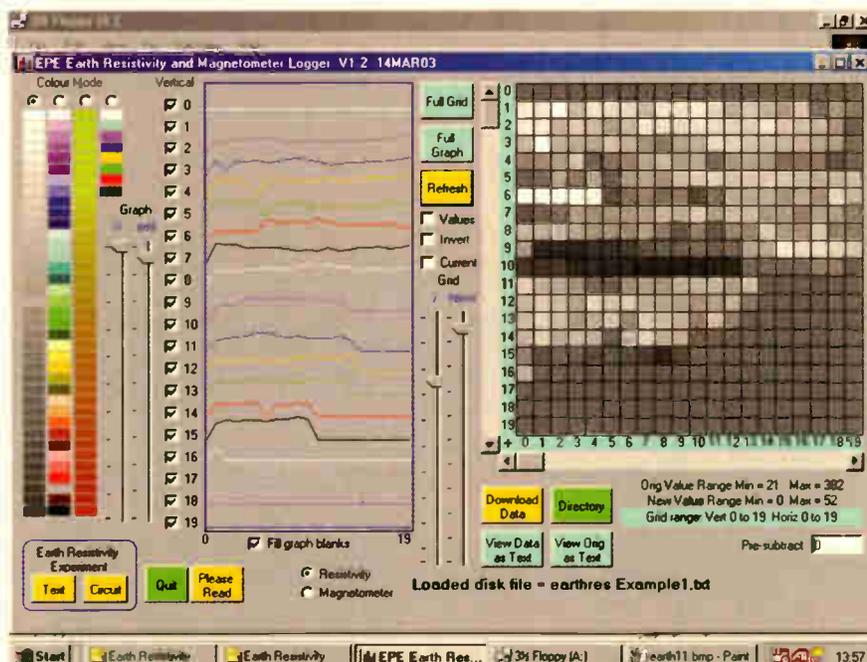The scales are selected by clicking on the "radio" buttons above them. In



Example of the prototype's revised main screen displays and facilities.



Example of the full screen grid display, using a zoom value of x9. With zoom at x1 all 16,384 grid squares are shown. The contrast will show more clearly on screen than it may on this printed page.

practice, the greyscale and monochrome bargraph provide the clearest indication of sample value relationships.

The values which are actually obtained from the survey site could, as said previously, fall into the range 0 to 1023. Two slider controls are provided so that the values logged can be suitably displayed as comparative values within the grid squares. They are to the left of the grid squares, jointly captioned Graph, with sub-captions of / (forward slash symbol) and *minus*. Clicking the sub-captions with the mouse cursor toggles them to show X (multiply) and *add*, and back again on the next click.

With the lefthand control, moving the slider causes the basic sample values to be either multiplied or divided by the slider's value, according to its sub-caption mode. Similarly with the second slider, adding or subtracting the slider's value. Multiplication/division take place first in the software routine, followed by add/minus.

These two controls allow the optimum shades or colour to be shown that best illustrate the sample value relationships. Even seemingly similar readings can have their values manipulated to increase the contrast.

Above the two sliders is a Show Values tick box. When unticked, just the colour shades are shown. When ticked, the equivalent numerical value of the scale shade, from 0 to 35, or 0 to 7 as appropriate, is displayed within the squares as well. Clicking the box alternates the two modes.

If a particular shade is too dark to read the value, move the mouse cursor over it and a "Tool Tip Text" box will appear, stating the value. Tool Tip Text box messages appear for various functions on screen if you move the cursor over them.

To the bottom of the screen below the grid are two text lines. The first shows the actual range of the sample values, the second shows the range after correction.

Note that if an original sample value of 0 is found, a dash line (-) is shown in place of a numerical value. This allows recognition of any survey site squares for which a sample has not been taken.

WAVEFORM DISPLAY

The large vertical display area towards the left of the screen shows the sample values plotted as graph waveforms. There are 20 lines (each numbered) representing the numbered grid rows to their right. Horizontally, the lefthand end of each line corresponds with the lefthand side of the grid row.

The two sliders to the left of the graph area allow the plot values to be varied in the same way as with the grid, with the same multiply/divide and add/minus options. Thus the display can again be manipulated to show the survey site features to best degree, in this case as differing amplitude waveforms.

The range of sample graph values is changed at the same time as the grid's coordinate range is set via its scroll and pan sliders.

Below the graph area is another tick box, Fill Graph Blanks. When the box is unticked, any zero values in the original (unmodified) samples are not plotted on screen, indicating any survey site squares that have not been sampled. With the box ticked, the zero values are plotted so that a continuous graph line is shown. Clicking the box alternates the modes.

To the left of the graph display are 20 numbered tick boxes. These allow selected graph lines to be hidden (no tick) to make the viewing of the data in the other lines clearer. As with all tick boxes, clicking them again alternates between on and off.

INVERSION

Below the Show Values tick box is another tick box, Invert Values. When surveying, less-dense soil produces higher values than dense soil. High values produce darker shades on the grid squares and lower troughs on the graph lines.

The Invert Values tick box allows the value relationships to be swapped, high becoming low, low becoming high. This allows denser soil conditions to be displayed more darkly on the grid than for less-dense soil, and the graph lines to show peaks rather than troughs (valleys). Clicking the box alternates between the two modes. The default is for inversion (tick on).

REFRESH BUTTON

The VB6 program allows the main screen to be minimised and shifted in the usual Windows-type fashion. Because VB6 does not regard the graph lines as being "permanent", these can be fully or partially erased by the act of minimising or shifting. To restore the graph lines on-screen, click the Refresh button.

It is also necessary to use the Refresh on the Full Grid and Full Graph screens to action various value selection changes.

FULL DISPLAY SCREENS

There are two buttons, marked Full Grid and Full Graph. They respectively cause the selected full screen mode to be displayed. On both, value manipulation and



Example of the full screen graph display. The zoom is at x9 to emphasise the contour lines. The samples cover a maximum area of 16 rows x 26 columns, each sample representing one square metre. The data is the same as in the full grid display and is in eight colours on the screen.

inversion are available as on the main screen. So too is colour mode selection.

Above and to the left of the grid and graph areas are two sliders. When clicked, these display the survey site grid coordinates to which their arrows point. Their position is also used by the zoom slider facility at the top left.

There are 10 values of zoom selectable according to the ratio $Zoom / 2 + 0.5$, with a range of $\times 1$ to $\times 5.5$. The slider arrow positions determine the origin point on which the enlargement is made. Intercepts are included in the program to keep the display within the bounds of its frame.

DOWNLOADING DATA


You require a standard serial cable, of the type used with normal modems (D-range 9-way male to female, straight through), for data transfer from the Logger. It should have a connector suited to your PC at one end, and a 9-pin male plug at the other. Adaptors (25-pin to 9-pin) are available if an existing modem lead has a 25-pin male plug.




Download option screen.

To download data serially from the Logger, first click on the Download Data button at the bottom of the main screen. This causes a message screen to be displayed, asking if you want to continue with the download, or cancel the call and re-show the full main screen.

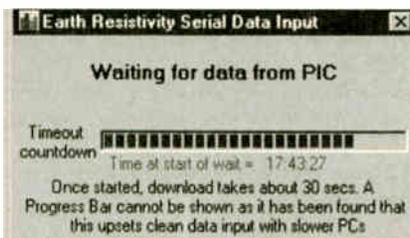If the OK button is clicked the small Download screen is displayed. As advised on the previous message you now have about 30 seconds in which to press the Logger's Download switch S7. During this 30 seconds or so, a bargraph shows the



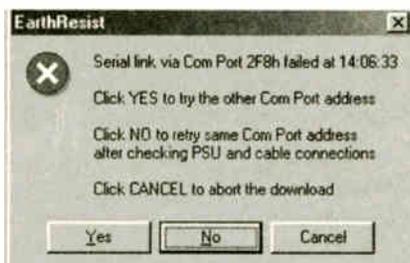Countdown bargraph while waiting for data to start coming from PIC.



Screen displayed in the event of data not received due to COM port failure.


elapsing time before a time-out error occurs.

If the time-out occurs before data is received, you are offered the options to cancel the download, for the PC to try downloading via its other COM port address (there are two allowed for, COM1 and COM2, at addresses 2F8h and 3F8h), or to retry downloading from the same COM port address.

If you choose that the other COM port address should be tried, this address is stored to the EarthResSettings.txt file, which resides in the same folder as the rest of the Earth Resistivity software. It is then recalled next time you run the program.

It is permissible to change the COM port address within this file if you wish (via Windows Notepad for instance) – it is the first entry in the file. Take care not to upset the positions of the other lines in the file. These lines set various parameters for the program each time it is loaded and run.

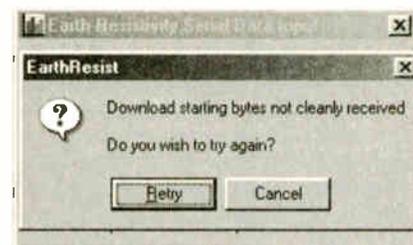When the Logger starts to send data before the time-out ends, and the PC begins to receive it, the countdown



Screen displayed if synchronisation is not correct.

bargraph halts and a confirmation that data is being received is displayed. The full 32K block of Logger data (16384 samples) is downloaded at 9600 baud, and initially stored into temporary memory locations.

During this process, another time-out countdown of about one second per data byte is monitored. If this period is exceeded the program assumes that the download is complete (the PIC has stopped sending data), or that the serial link has been broken.

Because the download is asynchronous (i.e. no handshaking), an error checking routine has been included. When the PIC starts transmitting, it first sends several zeros followed by the message RESISTY.

When the PC program finds that the one-second serial time-out has occurred, it checks through the first 20 downloaded bytes to see if these values contain the ASCII coded RESISTY message. It also assesses whether the download quantity is correct.

If neither fact is correct, the screen displays a message box stating so,

offering the option to try again or cancel the download.

Occasionally, the PC software thinks that data is arriving immediately following the click of OK in the Download message box, even before the Logger's Download switch S7 has been pressed. The reason has not been found. It is a rare situation, though, and in this event the PC software almost immediately experiences a time-out as data does not continue to arrive, and then offers you the option to try again.

It is worth waiting a couple of seconds after OK has been clicked before pressing switch S7, in case this situation is about to occur. Once the Logger has started to send data the process must run its full course and cannot be halted. The same applies to the PC routine, it too cannot be interrupted, and will continue until a time-out has been experienced.


It had been hoped to provide a bargraph to graphically show the progress of the download. Regrettably, it was found that on slower PCs the software is incapable of simultaneously updating the bargraph (or other visual forms of timing) and reliably inputting the serial data. Consequently, this option has not been provided. It takes about 30 seconds to download the full 32768 bytes. A starting time is displayed on screen below the primary time-out bargraph.

When the download has been successfully finished, a routine combines all the double-byte values into single 16-bit binary values. These are converted to decimal and combined into lines of text data, each value separated by a comma. Each line holds the data for one survey site row (128 values). There are 128 lines, representing the number of survey columns.

This data is then output to disk, to a file whose unique name is in the form of the following example:

EarthRes 12JAN03 10-27-35.TXT

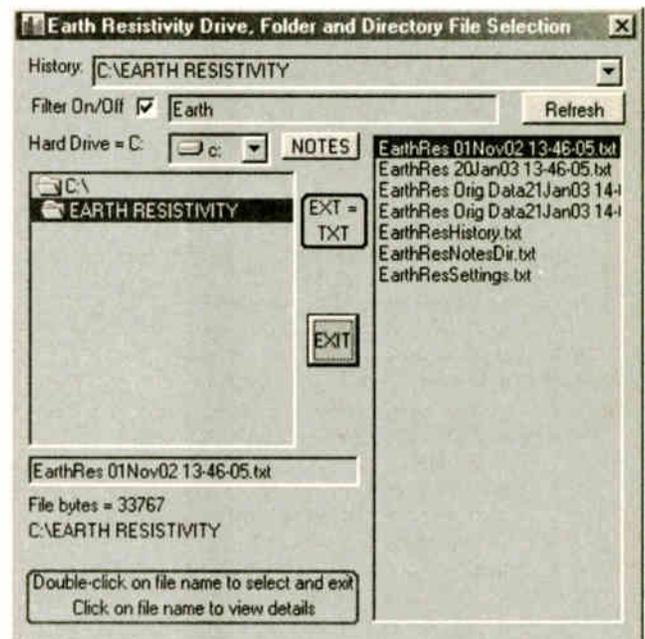in which the date and time (hh-mm-ss) is that applying at the moment that the file is



Example of the folder directory screen through which files from any folder path can be selected according to a filtered prefix option.

created. (The Logger itself has not been provided with date or location recording options – it is up to you to record this information in some other way.) The file is held in the same folder that holds the rest of the Earth Resistivity software.

Having saved the file, the software splits the recombined values into a matrix of registers whose coordinates correspond with those used during the site sampling.

It is these values that are used for display via the main screen's graph and grid areas. They are plotted there immediately the Download screen closes. Simultaneously, the grid matrix location coordinate sliders are reset to zero. The value correction sliders are left as previously set, allowing various sets of file data to be recalled from disk for viewing under the same corrective conditions.

On return to the main screen after the Download, the name of the current file loaded (in this instance that just saved) is displayed in bold towards the screen's bottom right.

LOADING SAVED FILES

To load the program with data from a previously saved file, click on the Directory button. This displays a multi-function screen through which files in any folder on any installed disk can be selected. It is a modified version of the Directory screen originally designed for use with the author's *PIC Toolkit TK3* software (Nov '01), and since used in modified form with other VB6 programs as well.

It will not be discussed in detail here as the screen has a NOTES button which calls up a Windows Notepad text window through which you can read the detail of the Directory screen's use.


In brief, you can change drives and folder paths, set a "filter" option to only show files having a specified prefix in their name, and recall previously selected paths through a History box. To select a file, double click on its name in the righthand display area. This causes it to be loaded and split for grid matrix allocation in the same way that the downloaded file just discussed was split and displayed.

One of the author's files is included with the software (but with fewer than 400 samples), plus a much longer one produced by Nick during his survey work. Experiment with them and the screen's manipulative controls.

USING WINDOWS EXCEL

When the downloaded survey data is output to disk, it is formatted to suit its analysis and display via Windows Excel, a facility that should be on any PC running Windows 95 and later (search your Windows CD-ROM for it if it is not already on your system).

As well as offering graphing facilities, Excel provides for mathematical expressions to be computed, making it capable of being set-up to calculate true earth resistivity in relation to known resistance and current factors. Study Excel's Help facility, and read Anthony Clark's book. (As said last month, though, Nick's surveys were done in relation to signal amplitude values and not the actual resistance, but see later.)

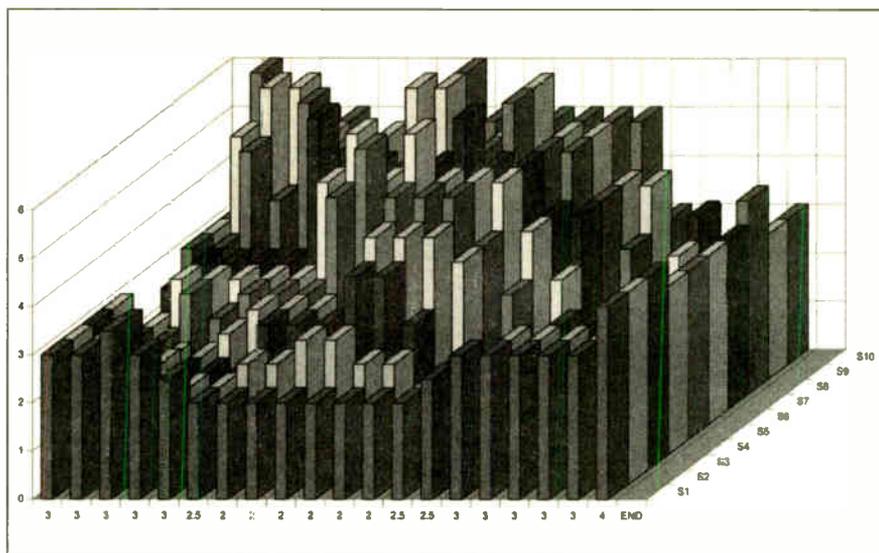

Example of using Windows Excel to display data graphically.

The formatting simply entails using commas to separate the sample values, which are expressed as normal text characters (e.g. 1234).

Inevitably, there are many versions of Excel and specific use details that apply to all of them cannot be given. The chances are, though, that the use will be similar to that on the author's main PCs. The following is the procedure he uses for Excel 97:

Load Excel, using Windows' Find button to locate it if necessary – on the author's PCs it is at

C:\MSOffice\Excel\EXCEL.EXE

Now follow the path File (in top toolbar), Open, Select folder, set File Type to Text Files, then double click on the required EarthRes file name to load it. A Text Import Wizard – Step 1 of 3 window is now shown, with the first several imported values on display. Select the Delimited option as the active "radio" button.

Click Next to show the Text Import Wizard – Step 2 of 3 window. Click the "Delimited Comma" box to reveal a tick. Click other ticks to become unticked (if necessary). Ignore the "Text Qualifier" box.

Click Next to show the Text Import Wizard – Step 3 of 3 window. Ignore the options offered, but click Finish.

The main Excel screen will now be shown, with the survey values allocated to column and row boxes.

Left click on one of these boxes, say the first one at top left, to select the starting coordinate of the matrix area you wish to show graphically. With the left mouse button still held down, move the mouse downwards and to the right, causing the selected boxes to show white text on a black background as the area is increased. The first box, though, remains as black on white.

EXCEL GRAPHING

Release the mouse button when you've selected the required area. Now click on the Chart Wizard icon on the top tool bar (it looks like several vertical rectangles, with an elongated diagonal shape above them – a chimney falling onto a factory?). The mouse cursor becomes a similar (but not identical) symbol plus a cross, representing that graphing mode has been selected.

Move this cursor anywhere over the darkened area and left click to reveal the Chart Wizard – Step 1 of 5 window. The darkened area reverts to normal black on white, surrounded by a dotted box, possibly "shimmering".

Ignore the options offered and just click Next, to show the Chart Wizard – Step 2 of 5 window. Select (left click) one of the graph type options offered, the "3-D Column" option is suggested.

Click Next to show the Chart Wizard – Step 3 of 5 window. Select one of the chart type variants on offer, the one numbered 6, perhaps.

Click Next to show the Chart Wizard – Step 4 of 5 window, and an illustration of the Sample Chart selected will be seen. Ignore the right hand option boxes and click Next, to show the Chart Wizard – Step 5 of 5 window. Now just click on Finish.

The graph type selected will now be displayed on the main Excel screen, with the value boxes still visible behind it. It can be moved around the screen and sized in the usual Windows style. A small (mobile) Chart selection window will also be displayed, allowing different options of display to be selected and manipulated.

Save the file and its graphical displays (more than one can be generated on the screen at any time and placed at different positions) as an Excel-type file with any name of your choosing. Alternatively, simply Exit unsaved if you prefer.

It is now up to you to experiment with Excel's numerous options, calling up its Help files for more information. It is an amazing package with many uses, and seemingly ideal for the sort of analysis that archaeological survey data calls for. In a word – experiment!

PROBING METHODS

The construction of the probe assemblies will be discussed once some of the probing techniques have been examined.

There are several probing methods available through which to obtain grid data about a survey site. The author makes no attempt to recommend any one in particular. You must do your own research into that, through the references given later, and by chatting to those in archaeological societies who know about such things.

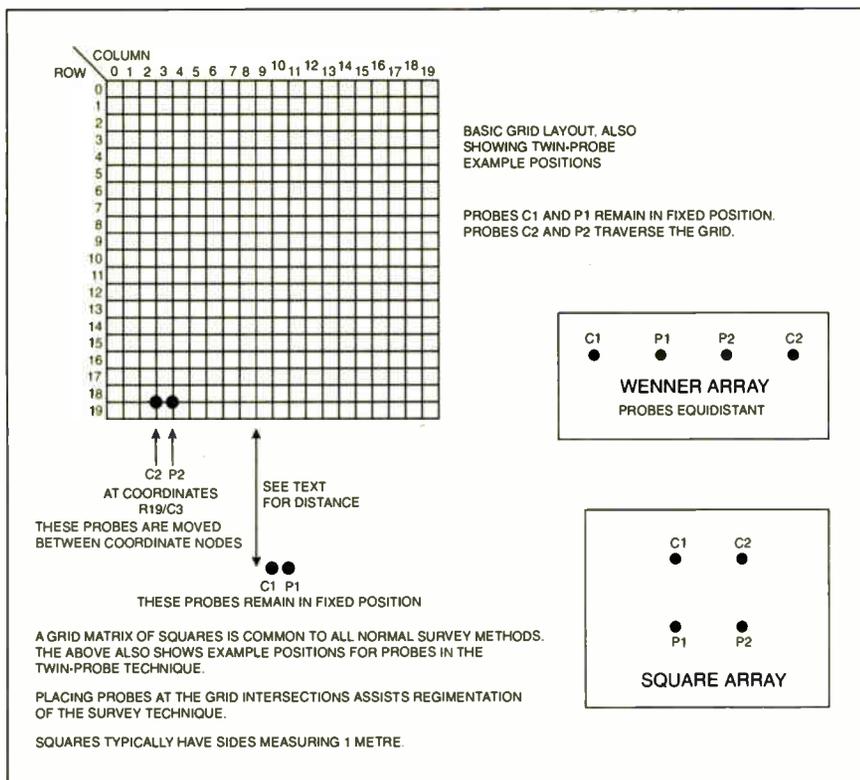


Fig.8. A 20 x 20 grid layout with Twin-Probe example positions, and the positioning of the probes in Wenner and Square arrays.

There are numerous archaeological web sites with bulletin boards and "chat-zones" on-line if you search through the excellent www.google.com, or other quality internet search engines. It is worth noting, though, that Anthony Clark considers the Twin-Probe technique to be that most suitable to archaeological work, and is the one used by Nick with his surveys.

With all techniques, the area to be surveyed is first marked out as a grid with tapes or similar, to form squares having sides of, say, one metre in length (this is a commonly quoted distance in this context), and probably forming a 20 x 20 matrixed area, see Fig.8.

Anthony Clark comments that plastic covered clothes line is also useful for setting out a grid matrix. He cautions, though, that it can be difficult to untangle and on one site he knows of, it had to be "guarded in the presence of sheep, by whom it was regarded as a rare delicacy"!

TWIN-PROBE

The Twin-Probe technique is apparently more suited to initial surveying of a site, establishing whether or not it is worth carrying out a more detailed survey.

With this method, the two probes C1 and P1 are inserted into the ground, sufficient to make electrical contact with it (see earlier), centrally to and somewhat outside the area to be surveyed. Anthony Clark discusses the best distance in his book.

Probe C1 is the transmitting probe connected to the comparator IC3, via switch S2. Probe P1 is one of the receiving probes, connected to the input of op.amp IC4a.

Probes C2 and P2 are inserted into the ground, to a similar depth, at the far corners of the first square to be monitored, say top left, coordinate R0/C0 (row 0, column 0). Probe C2 is the 0V reference probe, and P2 is connected to the input of op.amp IC4b. The respective leads from the Logger

are then connected to the probes, using heavy duty crocodile clips seems the easiest method.

The Logger's storage coordinates are set to suit the square number, i.e. to R0/C0 in this case, and a reading saved to the Logger's serial EEPROM by pressing switch S8.

The C2/P2 probes are then moved to the top corners of the next square, to the right for example, to be monitored and its coordinates set into the Logger, in this case R0/C1. Again a reading is stored to the EEPROM.

The process continues fully across horizontally for the width of the marked survey area, e.g. R0/C19 (the final column of this row in a 20 x 20 grid). The probes are then moved down by one row, and the process repeated, to the left this time, back to R1/C0. And then down by another row, and so on for all 400 squares.

WELL ORDERED

Note that the relative order of all probe connections must be maintained during the survey. Differences in reading can result if the order is changed, hence the earlier recommendation that the plugs and crocodile clips should be colour-coded.

In practice, it does not matter in which direction you move the probes, or whether you start the survey from the top of the grid or the bottom. Note that the PC screen regards location 0,0 as being at top left of the screen.

"Be methodical and consistent" seems to be the key phrase, though – this helps you to establish a routine that becomes second nature, which the author soon found when starting his own mini surveys!

It was also soon found that it is not necessary to move both probes on each occasion. Since one is already at the corner of the next square, it is only necessary to move the probe from the corner now

finished with, putting it in the next square's opposite top corner, and swap the probe leads to retain the correct order.

The author surveyed his garden several times in different ways during design development, and on each occasion became faster at doing so. On the final survey, on an 11 x 7 grid (77 samples) it took about an hour and half.

Of course, during the process of doing the test surveys, several methods for speeding it were imagined. For a solitary surveyor, perhaps the most efficient in terms of speed would be to insert separate probes at each corner of the matrix prior to taking readings. It would then only be required to repeatedly change the lead connections – a seemingly much faster "conveyor belt" system. No doubt, though, having an assistant would probably make the moving of just two probes a speedy alternative.

A perhaps less practical method was (bizarrely?) thought up too – using a motorised vehicle like a golf buggy with probes attached to the wheels in Boadicea fashion. This would then be driven back and forth across the grid, the probes automatically inserting themselves, and triggering the storing of each reading at the correct coordinates! (Well – a chap can dream, can't he?!)

WENNER PROBING

Another seemingly useful technique is known as the Wenner configuration. In this method the four probes are arranged in a straight line, equally spaced apart, say a metre between them. Fig.8b shows the order of arrangement.

This method is apparently better suited to doing a more detailed survey of the matrixed grid site. The principle is that the TX probes are the outer two. The RX probes are in line between them. The current flows across the TX pair and is picked up across the RX pair, the received signal value varying with the resistance in series with the probes in a more direct fashion than with the twin-probe technique.

A variant of this technique, the Schlumberger, in which the probes are not equally spaced, is discussed in Anthony Clark's book. But he regards it as not ideally suited to archaeological surveying.

SQUARE ARRAY

Another method is known as the Square Array in Anthony Clark's book. With this method, the TX and RX pairs are placed at the corners of the one metre squares, as shown in Fig.8c. The four probes are moved as a set from square to square.

The transmission signal flows between the TX pair as before. This time the RX pair pick up the radiated signal at the same distance from the TX probes. If the soil resistance between the TX and RX pairs is uniform, so too will be the amplitude of the signal received by both RX probes.

Tests showed that because the probes are connected to a differential amplifier, if the two input amplitudes are the same, they will cancel each other out at the final combining stage (IC4c).

If, on the other hand, the amplitudes are not the same, the difference between them is that which will be finally output from IC4c. In this case, what would be looked for is any difference values, indicating the edge of a subterranean feature.

It is evident, however, that balanced (zero) readings, when the two input values are equal, would only indicate the uniformity of the terrain in that grid. It would not indicate whether that uniformity was due to a highly resistive feature or a highly conductive one. Nonetheless, the detection of only outlines might in itself be a desirable situation.

A variant of this technique would be to place the two TX probes at one end of a column, and the RX pair at the other, taking a reading and moving both pairs to the next column, still at the top and bottom points. This could perhaps yield initial information about whether or not a site is worth examining more closely. Not being an archaeologist, though, the author cannot comment on the validity of this.

Anthony Clark discusses the above named probing techniques in more detail, and describes others.

PROBE CONSTRUCTION

During garden tests with the prototype Logger, individual metal rods measuring about one metre long by 5mm diameter, and with a right-angled bend at the top were used as the probes. These were purchased inexpensively from a garden centre, their intended use being to support plants.

A recently observed, but not tried, possibility was in the form of long inexpensive barbecue skewers – seen in a local supermarket.

If you wish to construct purpose-built probe structures of more durability, and perhaps greater ease of use, the probe

assemblies described by Robert Beck should be considered. Schematics of the original figures illustrating these probes have been redrawn and are repeated here. Other than the following details, no additional information can be offered.

Robert's rigid frame assembly for two probes is shown in Fig.9. Details of his single probe are given in Fig.10.

His original text states that the Twin-Probe assembly was specially developed and that its top member is a wooden batten, 30mm x 50mm x 1050mm, the ends of which are bound with self-amalgamating tape to form hand grips.

An aluminium platform is attached to the centre of this batten to carry the case that holds the electronics, secured by rubber bands. The bottom member is a similar wooden batten, but this piece must have good insulating properties (to prevent current leakage between the probes). He suggests that you

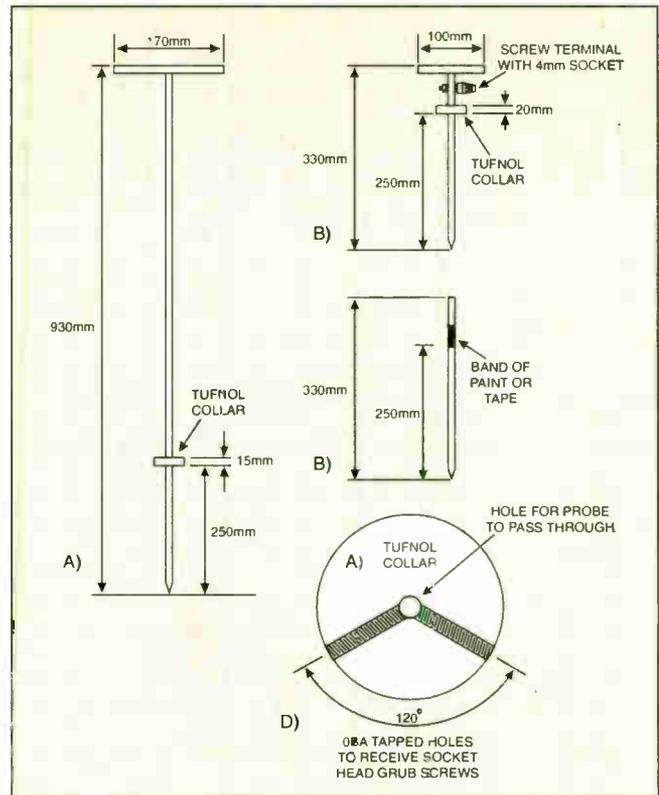


Fig. 10. Construction details of Robert Beck's probes.

either dry and coat the batten with varnish, or devise insulating collars of Tuffnol or similar material, and fit them where the probes go through the batten.

The top and bottom battens are held together by metal conduit pipes, threaded at each end and secured by lock-nuts.

In describing the construction of the other probes, he says that none of their dimensions are critical and may be dictated by what is to hand. In Fig. 10a is shown a substantial probe made out of stainless steel tubing with a brazed on T-handle and tip which assist soil penetration. This probe is designed to be used by the operator in the standing position.

A smaller version of Fig. 10a is shown in Fig. 10b. This has a 4mm screw terminal added, an alternative method of wire connection.

Probes may be constructed of material other than stainless steel, which is expensive and a little difficult to obtain, he says (provided it is corrosion resistant of course).

An extremely simple probe is shown in Fig. 10c and which may be constructed from 6mm diameter metal rod, i.e. brazing or uncoated welding rod, mild steel, silver steel, etc. A depth guide consisting of a band of paint or insulating tape is added and connections are made to the top using a crocodile clip.

The depth stop in Fig. 10d is adjustable by means of an Allen key. The material need not be insulating, and could be of metal if desired.

SERIAL OCX

Since finalising the *Earth Resistivity Logger* Part One for publication last month, reader Joe Farr has provided *EPE* with a specially written SerialIO.OCX program that allows legal access to Visual Basic's own serial control I/O facilities.

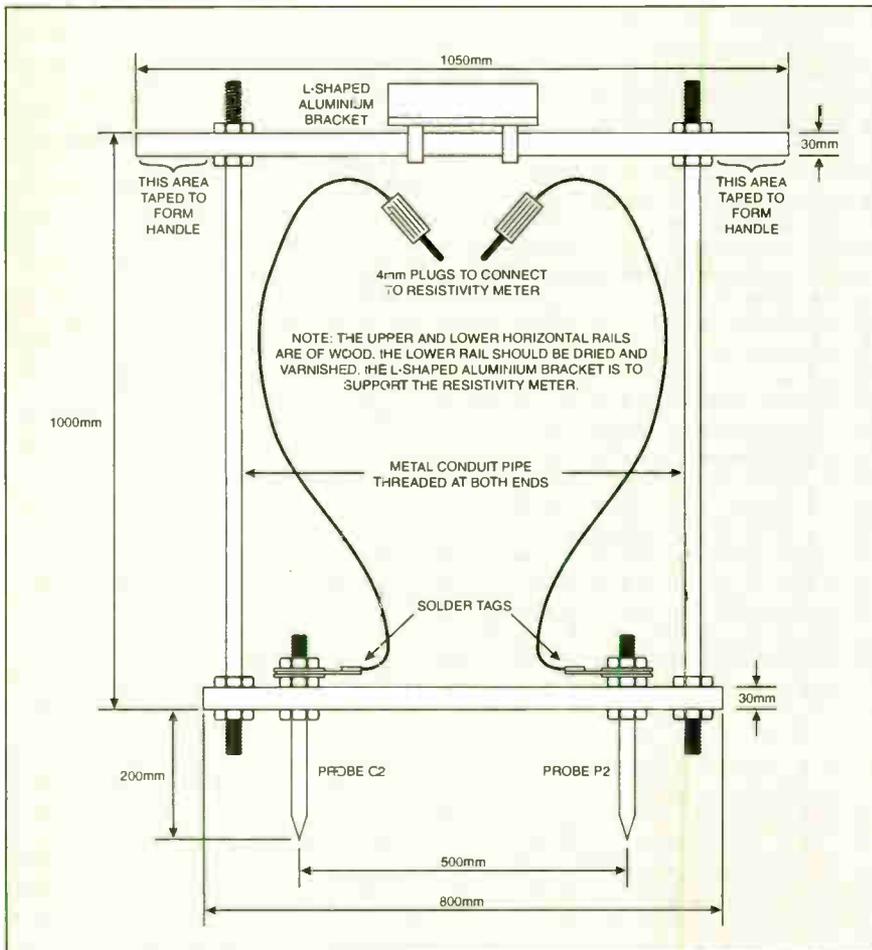


Fig. 9. Support frame for the Twin Probe configuration used by Robert Beck.

This option has previously only been available to readers who have a registered version of MSCOMM (as Robert Penfold has discussed many times through his *Interface* series).

Joe's serial OCX facility will be published in full at a later date – probably the September issue. However, a section of Joe's program has been built into this Earth Resistivity (ER) program and is available to readers who are using the EarthResist.EXE standalone version.

To use Joe's option, though, several changes need to be made to ER's p.c.b., without which the facility cannot function. They are:

1. Cut the track (0V) connecting to IC7 (MAX232) pin 13.
2. Connect IC7 (MAX232) pin 13 to 9-pin serial socket SK3 pin 3.
3. Connect IC7 (MAX232) pin 12 to IC5 (PIC) pin 18 (RC7).

This action allows the PIC to receive handshake data from the PC.

To set the PIC program to respond to the correct serial data transmission routine, initiate the following procedure:

1. Before switching on power, press and hold down the Mode switch, S6.
2. The screen will go into serial path change mode, alternating at about one-second intervals between a display saying "SERIAL PORT NORM" (original version) and "SERIAL PORT OCX" (Joe's OCX).
3. Release switch S6 when the mode you require is shown. This mode becomes the active path mode and is also stored into the PIC's data EEPROM, to be recalled next time the program is run.
4. On release of switch S6, normal running of the PIC program resumes. The serial path mode may be changed whenever you choose.

PC OCX SETTING

Ensure that the PC is also set for the chosen mode, as follows:

Click the on-screen button labelled Please Read. Accept the option that then follows to read the text. Having read it, exit the text reading screen to reveal another options screen. This allows you to choose between the new OCX option and the original (normal) serial mode. Click YES for Joe's OCX, NO if you want to use the normal serial download as originally written into the ER program, or CANCEL to exit without making a change to the serial path used.

Your choice is recorded to disk and recalled next time the program is run. You may change your mind at another time if you wish, re-entering via the Special Note button to do so.

Note that the same mode must be selected for the PIC and the PC.

The advantage of Joe's program is that it allows a bargraph to display the progress of the data input procedure. It is also likely to be better at detecting input data problems as it uses a handshake procedure to communicate with the PIC, inputting the 32768 bytes of data in blocks of 256 bytes.

Whilst the original program inputs data that is usually 100% accurate, there is the occasional loss of synchronisation, which

is reported on screen, allowing you to re-download if you prefer, although minor "first aid" is provided by the program to regain sync after that point. It is rare, though, for more than one loss of sync to occur. Such loss should not occur with Joe's OCX program.

It should be noted that readers who wish to make their own changes to the ER source code cannot make use of Joe's OCX input option. For that to be used, the installation of Joe's full OCX facility is required. For copyright reasons this will not become available to readers until its publication. Attempting to examine the ER source code will generate an error condition because of the presence of Joe's program. Until Joe's full serial program becomes available, the ER program can only be recompiled if Joe's sub-program (EarthResOCX) and all references to it in the main program are removed.

Also be aware that this version of ER with Joe's OCX has not yet been proved on a wide variety machines. If it will not work on your PC, revert to using the normal serial download option on PIC and PC. Please advise us at HQ if this is necessary, telling us the PC and its operating system type.

SURVEY CURRENT MONITORING

Another feature added to this version is the ability to monitor the current flowing between the transmission (TX) probes. It too requires a small change to the PCB:

1. Cut the track between resistor R16 and pin 7 of IC4.
2. Connect the now-open end of R16 to the pole of switch S2.

With switch S2 in the R5 (1k resistor) position, current flows from the switch pole through the 1k resistor and to 0V via the resistance of the soil. These two resistances form a potential divider. The square wave voltage at their junction is buffered by R16 and half-wave rectified by diode D2. The resulting peak positive voltage is monitored via PIC pin RA0 operating in analogue (ADC mode). The peak voltage depends on the resistance of the soil, and from this voltage value the equivalent relative current through the resistance path can be calculated.

To establish an initial reference value prior to any survey, switch on the unit. Then set switch S2 to the setting that directly connects the pole to IC3 output pin 6. Do not connect transmission probe C1 to socket SK2 at this time. Press switch S6 (Mode) and hold it pressed, then press switch S8 (Save) and hold it pressed until the message REF SAVED appears, preceded by a value. Release S8, then release S6. The value shown is now stored to the PIC's EEPROM for present and future use. Then switch S2 to the 1k resistor (R5) path.

During active surveying, the voltage at the pole of S2 is subtracted from the reference value and stored as a 6-bit number into bits 1 to 6 of the MSB of the survey value recorded to the external serial EEPROM IC6. The range of current values acceptable is from 0 to 63, and the actual value is displayed as the second value on l.c.d. line 1 when in Test Mode (S9 on). It is followed by the letter

A. The first value shown (followed by B) is that monitored from IC4b pin 8, as described in Part One. The output from IC4a is no longer monitored via the l.c.d.

If current values greater than 62 are encountered, they are limited to 63, and the word MAX is displayed on the l.c.d. Switch S2 may be used to select one of the other resistors (R3 to R6) in the event that the site being surveyed has greater or lesser resistance than appropriate to a 1k fixed resistor value. Do not change the resistor value during a survey.

The PC program stores the full 2-byte survey value to disk. On re-input the current value is extracted from the MSB, and the MSB is then limited to one active bit (bit 0). The range of survey values is then from 0 to 511. During surveying, the gain setting via switch S3 should be chosen to keep the values below 511, favouring a middle range centred on 256. If a value greater than 511 is encountered by the PIC, it is limited to 511 and the word MAX is shown on the l.c.d.

CURRENT ON/OFF OPTION

All three display screens of the PC program now have an extra tick box marked Current. When it is ticked, each survey value is multiplied by its associated current value divided by 10. The theory is that slight differences in the transmission current value at each survey grid square affect the actual value of the received voltage signal from the receiving probes. By relating these voltages to their prevailing transmission current, compensation is made for variations in the latter. The current values are not actual milliamp values, but simply numbers representing the relative current flowing.

It is suspected, however, that in practice the variations make little difference to the interpretation of the displayed results. To repeat the statement made in Part One, the aim of this Logger is to show relative differences in signal amplitude across a site being surveyed. It is the differences that then indicate different sub-soil features.

If there are significant differences they are worth physical investigation. If there are no significant differences, then the site is probably not worth examining further, unless such techniques as magnetometry or ground-penetrating radar reveal differently. A magnetometer design is currently being worked on and will be published in *EPE* at some time in the future, but not yet scheduled.

We shall be interested to learn if you find that the current-monitoring feature enhances the results of your survey. Let us know via *EPE* HQ.

DOT MATRIX

A further option added to the PC program since Part One is the dot-matrix display facility, operative when the Matrix tick-box on the Full Grid screen is ticked. This draws small squares on the display whose dimensions are relative to the signal amplitude.

The principle is a bit like the dots that make up a B&W photograph in a newspaper (known as half-tone). It will be more useful with a large amount of survey data on screen than with a small quantity.

MISCELLANY

A few other "tweaks" have also been added since Part One.

The text and demo circuit for some experiments referred to on Part One page 1 are now accessible via buttons at the bottom left of the screen.

Two other buttons allow you to examine the survey data as text files, one showing the twin-byte values separately, the other as the full combined value. These values include the current values as well.

All three display screens have also been given a "pre-subtract" box, allowing you to subtract, say, the minimum value received from all other values, enabling relevant data to be extracted from any overall bias levels.

Because this PC software will be used with the Magnetometer currently under development, two "radio" buttons allow selection of whether Earth Resistivity or Magnetometer data will be processed. Ensure that the Resistivity button is the one selected.

ETHICS

It was said in the opening paragraph in Part One that the original *Earth Resistivity Meter* published in *EPE* was an electronic tool to assist amateur archaeological societies. So too is this Logger design.

Whilst there is nothing to stop anyone from carrying out surveys on their own property, there are considerable ethical issues regarding the surveying of other land.

First, other land is not *your* land, and so any surveying of it requires the permission of those who own it. Remember that **all land in the British Isles is owned by someone**. Find out who it is and gain their permission before you proceed.

Secondly, **do not dig without an archaeologist's involvement**. If you have located through your earth resistivity survey something that proves to be a site of any importance, your unsupervised digging will certainly destroy information that is necessary to fully interpret the site.

Earth resistivity surveying is essentially non-invasive except for the slight intrusion made by the probes just into the surface. Many landowners could well be as interested as an archaeological society in knowing what history might lie beneath their land, especially if they are approached in a polite manner and it is explained to them that the resistivity surveying is just a matter of sticking some shallow probes in the soil.

Remember that some locations are designated as Scheduled Ancient Monuments and that permission to carry out any form of research on them requires official approval. Experienced local archaeological societies will know where these sites are and whether or not surveying permission is likely to be granted, and if so, by whom. If such information is not already known to a society, enquiries at the local town hall should provide answers.

JOIN A SOCIETY

It really is in your interests to join an archaeological society if you are not already a member. It is also in the society's interests if you join them and they then have the use of your Logger!



Nick's survey was done not far from where John Constable painted this Boat Building Near Flatford Mill scene. The contours in the full graph screen shown earlier clearly indicate a trench comparable to that in this painting. Illustration courtesy of

www.excelsiordirect.com/constable.htm.

To find a local society, look in the telephone directory, or ask at the library. The author's local library building even has a display of the artefacts found by the society in his area. It is a region once heavily populated by the Romans, with many artifacts that have been found on display, and even the ruins of two Roman villas (but left where they were found!).

Only a few hundred yards from the author's house a Roman corn drier was recently found by his local society. 400 yards further on are the ruins of a Roman bath house. It is quite probable that his garden is on a site where Roman's once trod.

Although his survey graphics did not show anything other than known modern features, and probably including builder's rubble of recent decades, perhaps he'll one day do a more detailed survey and then call in the archaeologists to uncover an amazing find – one way to get the garden dug for him!

NICK'S SURVEY

Nick was fortunate enough to be permitted to survey a site made famous by English artist Constable (before he was promoted to Sergeant says reader and friend John Waller – quoting an old Goon Show line!).

Constable painted several pictures of sites at and around Flatford Mill in Essex. One of them is his *Boat Building Near Flatford Mill*, which is reproduced here. It is near that site that Nick surveyed and his results are those illustrated earlier in the full graph and full screen illustrations. They reveal very clearly the sub-surface features that could have been bays cut into the ground where boats might well have been tied up. Much of the site, though, is now overgrown with trees, preventing adequate survey.

The primary area covered in the survey is approximately 16m x 26m at maximum dimensions. Most of it was covered in one day, but then rain "stopped play" for several weeks.

PRACTICAL ADVICE

From his experience with the prototype of this Logger, and from his general surveying activity, Nick offers the following advice:

- For extensive survey work the battery needs to be bigger than PP3 size
- The case should be larger than in the prototype and a better shape to carry about
- Do not use small plugs and sockets
- The sockets need to be solidly mounted, possibly on a metal base of some description, and include strain relief, it's surprising how hard you have to pull 50m of cable laying on wet grass!
- Lay the survey out accurately, based on a 3, 4, 5 triangle to get the lines perpendicular. Bamboo canes make good markers for the 1-metre grid intersections. If using clothes line with metre marks, beware that rope stretches. Survey tapes (typically 30m) need to be carefully cleaned after use, or they get full of dirt and can jam
- Keep perfect track of what you have surveyed, it is horribly easy to lose track of the grid section that you have just recorded
- Probe around the site at random before you start to make sure that you are set up to keep the Logger's values roughly around 250
- Try and get it all done in a day – a shower overnight throws in a step function because you are then working in the area that the rain will have penetrated
- Coil everything neatly – controlling 50 metres of cable across a plot is tricky

- Buy high visibility cable in case someone tries to trip over it!
- Colour code the probes – you need to be consistent
- Ask permission, most people will be chuffed to bits that you want to do the survey – but not everybody, and make sure that you are not somewhere where you should not be
- Make contact with your local archeology group, they will be very helpful and interested, and may well bite your arm off to get you helping them
- Be prepared to talk to people, you will cause interest if you are somewhere public, and they will be surprisingly knowledgeable – and probably have all been watching *Time Team*
- Keep your ears open for local stories of old ruins, you might be the one that rediscovers something lost to history because you happened to take the time to listen to the ramblings of the old guy in the pub
- You can do a survey on your own, but it is much easier with two of you
- Keep a note book that notes the time, place, date, etc of the survey and things like weather conditions which could explain odd results, for example if it started to rain half way through the work
- Any survey must have a repeatable base point, or base line so that if you do find something interesting, you can be sure where it was without having to repeat the survey!

- Use compass bearings, fixed physical features, corners of buildings, drain covers etc, or triangulate from fixed points if the survey is in an open area. Most archaeologists work north to south.

ACKNOWLEDGEMENTS

The author offers very grateful and appreciative thanks to Nick Tile for carrying out extensive field tests with the prototype, for discussing at length many aspects of its use, for lending *Seeing Beneath the Soil* and vetting the script.

The author also thanks those *EPE* readers who provided him with information during the development of this design (in alphabetical order!):

Dave Allen for sending an ancient issue of *ETI* containing a rudimentary ER circuit using d.c. probing (and yes Dave, this design could be used for monitoring relative impurity content levels in water).

Peter Barnes, for vetting the script and for several useful email exchanges of thoughts and circuits, plus comments from his archaeologist acquaintance Derek about using Robert Beck's design.

Robert Beck, for the original inspiration. Aubrey Scoon, for comments about stray electrical currents in the soil.

ODAS, the Orpington and District Archaeological Society, and Alan Hart in particular.

FURTHER READING

Applied Geophysics, W.M. Telford, L.P. Geldart, K.E. Sheriff, D.A. Keys. Cambridge University Press. ISBN 0521-20670-7.

Applied Geophysics, Griffiths and King, Pergamon Press. 1965. (ISBN unknown).

Seeing Beneath the Soil, Prospecting Methods in Archaeology. Anthony Clark. Routledge. 2000. ISBN 0-415-21440-8. This is a revised edition of the title referenced in *EPE* Feb '97, and having a different ISBN and publisher. It is the most informative source used by the author during the design of this Logger.

It additionally covers other earth surveying techniques, including magnetometry, and provides several further reference sources. It is known to be available for online ordering from www.Amazon.com and www.BOL.com, current price around £25.

USEFUL WEB SITES

www.archaeology.co.uk. Various aspects of the subject, including further links, access to the magazine *Current Archaeology*, and to the Council for Independent Archaeology.

www.geop.ubc.ca. Source of semi-mathematical tutorial on earth resistivity and a link to a site called Introduction to Exploration Geophysics.

www.google.com. Excellent search engine.

LOGGING OFF

The ER software placed on the *EPE* ftp site on 17 March '03, was version V1.2. Look in on the site occasionally to see if any further updates have been introduced. □

CORRECTION

Crystal X1 should be 3-6864MHz (as in Fig.5), *not* 3-2768MHz as in the components list.

EPE BINDERS

KEEP YOUR MAGAZINES SAFE – RING US NOW!

This ring binder uses a special system to allow the issues to be easily removed and re-inserted without any damage. A nylon strip slips over each issue and this passes over the four rings in the binder, thus holding the magazine in place.

The binders are finished in hard-wearing royal blue p.v.c. with the magazine logo in gold on the spine. They will keep your issues neat and tidy but allow you to remove them for use easily.

The price is £6.95 plus £3.50 post and packing. If you order more than one binder add £1 postage for each binder after the *initial* £3.50 postage charge (overseas readers the postage is £6.00 each to everywhere except Australia and Papua New Guinea which costs £10.50 each).

Send your payment in £'s sterling cheque or PO (Overseas readers send £ sterling bank draft, or cheque drawn on a UK bank or pay by card), to **Everyday Practical Electronics, Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562.**


E-mail: editorial@epemag.wimborne.co.uk.

Web site: <http://www.epemag.wimborne.co.uk>

Order on-line from:

www.epemag.wimborne.co.uk/shopdoor.htm

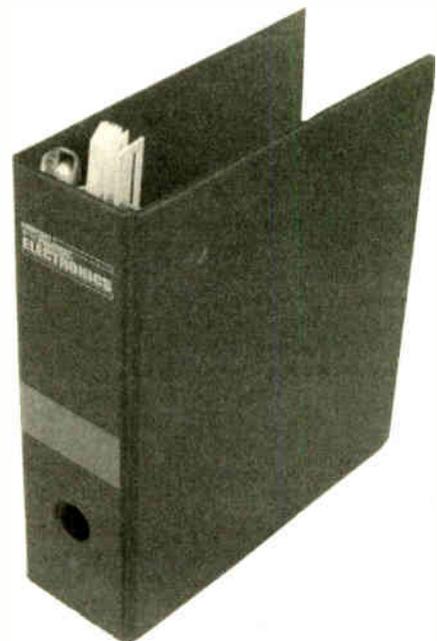We also accept card payments. Mastercard, Visa, Amex, Diners Club or Switch. Send your card number and card expiry date plus Switch Issue No. with your order.



FREE *Electronics Hobbyist Compendium* book with Teach-In 2000 CD-ROM



EPE TEACH-IN 2000 CD-ROM

The whole of the 12-part *Teach-In 2000* series by John Becker (published in *EPE* Nov '99 to Oct 2000) is now available on CD-ROM in PDF form. Plus the *Teach-In 2000* interactive software covering all aspects of the series and Alan Winstanley's *Basic Soldering Guide* (including illustrations and Desoldering).

Teach-In 2000 covers all the basic principles of electronics from Ohm's Law to Displays, including Op.Amps, Logic Gates etc. Each part has its own section on the interactive software where you can also change component values in the various on-screen demonstration circuits.

The series gives a hands-on approach to electronics with numerous breadboard circuits to try out, plus a simple computer interface which allows a PC to be used as a basic oscilloscope.

ONLY **£12.45** including VAT and p&p

Order code Teach-In CD-ROM

PROJECT CONSTRUCTION

PRACTICAL REMOTE CONTROL PROJECTS

Owen Bishop

Provides a wealth of circuits and circuit modules for use in remote control systems of all kinds; ultrasonic, infrared, optical fibre, cable and radio. There are instructions for building fourteen novel and practical remote control projects. But this is not all, as each of these projects provides a model for building dozens of other related circuits by simply modifying parts of the design slightly to suit your own requirements. This book tells you how.

Also included are techniques for connecting a PC to a remote control system, the use of a microcontroller in remote control, as exemplified by the BASIC Stamp, and the application of ready-made type-approved 418MHz radio transmitter and receiver modules to remote control systems.

160 pages

Order code BP413

£6.49

ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including the following topics:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering; making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby.

135 pages

Temporarily out of print

A PRACTICAL INTRODUCTION TO SURFACE MOUNT DEVICES

Bill Mooney

This book takes you from the simplest possible starting point to a high level of competence in handworking with surface mount devices (SMD's). The wider subject of SM technology is also introduced, so giving a feeling for its depth and fascination.

Subjects such as p.c.b. design, chip control, soldering techniques and specialist tools for SM are fully explained and developed as the book progresses. Some useful constructional projects are also included.

Whilst the book is mainly intended as an introduction it is also an invaluable reference book, and the browser should find it engaging.

120 pages

Order code BP411

£5.49

FAULT-FINDING ELECTRONIC PROJECTS

R. A. Penfold

Starting with mechanical faults such as dry joints, short-circuits etc, coverage includes linear circuits, using a meter to make voltage checks, signal tracing techniques and fault finding on

DIRECT BOOK SERVICE

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

FOR A FURTHER SELECTION OF BOOKS
SEE THE NEXT TWO ISSUES OF EPE.

All prices include UK postage

logic circuits. The final chapter covers ways of testing a wide range of electronic components, such as resistors, capacitors, operational amplifiers, diodes, transistors, SCRs and triacs, with the aid of only a limited amount of test equipment.

The construction and use of a Tristate Continuity Tester, a Signal Tracer, a Logic Probe and a CMOS Tester are also included.

136 pages

Order code BP391

£5.49

TEST EQUIPMENT CONSTRUCTION

R. A. Penfold

This book describes in detail how to construct some simple and inexpensive but extremely useful, pieces of test equipment. Stripboard layouts are provided for all designs, together with wiring diagrams where appropriate, plus notes on construction and use.

The following designs are included:-

AF Generator, Capacitance Meter, Test Bench Amplifier, AF Frequency Meter, Audio Multivoltmeter, Analogue Probe, High Resistance Voltmeter, CMOS Probe, Transistor Tester, TTL Probe. The designs are suitable for both newcomers and more experienced hobbyists.

104 pages

Order code BP248

£4.49

ROBOTICS

INTRODUCING ROBOTICS WITH LEGO MINDSTORMS

Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various "click-together" components supplied in the basic RIS kit. Explains in simple terms how the "brain" of the robot may be programmed on screen using a PC and "zapped" to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robot.

Detailed building and programming instructions provided, including numerous step-by-step photographs.

288 pages

Order code BP901

£14.99

MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS - Robert Penfold

Covers the Vision Command System

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using Lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with 'waiter service' when you clap your hands perform tricks, 'see' and avoid objects by using 'bats radar', or accurately follow a line marked on the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit.OCX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an 'intelligent' sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

298 pages

Order code BP902

£14.99

RADIO / TV VIDEO

ELECTRONIC PROJECTS FOR VIDEO ENTHUSIASTS

R. A. Penfold

This book provides a number of practical designs for video accessories that will help you get the best results from your camcorder and VCR. All the projects use inexpensive components that are readily available, and they are easy to construct. Full construction details are provided, including stripboard layouts and wiring diagrams. Where appropriate, simple setting up procedures are described in detail; no test equipment is needed.

The projects covered in this book include: Four channel audio mixer, Four channel stereo mixer, Dynamic noise limiter (DNL), Automatic audio fader, Video faders, Video wipers, Video crispener, Mains power supply unit.

109 pages

Order code BP356

£5.45

SETTING UP AN AMATEUR RADIO STATION

I. D. Poole

The aim of this book is to give guidance on the decisions which have to be made when setting up any amateur radio or short wave listening station. Often the experience which is needed is learned by one's mistakes, however, this can be expensive. To help overcome this, guidance is given on many aspects of setting up and running an efficient station. It then proceeds to the steps that need to be taken in gaining a full transmitting licence.

Topics covered include: The equipment that is needed; Setting up the shack; Which aerials to use; Methods of construction; Preparing for the licence.

An essential addition to the library of all those taking their first steps in amateur radio.

86 pages

Order code BP300

£4.45

EXPERIMENTAL ANTENNA TOPICS

H. C. Wright

Although nearly a century has passed since Marconi's first demonstration or radio communication, there is still research and experiment to be carried out in the field of antenna design and behaviour.

The aim of the experimenter will be to make a measurement or confirm a principle, and this can be done with relatively fragile, short-life apparatus. Because of this, devices described in this book make liberal use of cardboard, cooking foil, plastic bottles, cat food tins, etc. These materials are, in general, cheap to obtain and easily worked with simple tools, encouraging the trial-and-error philosophy which leads to innovation and discovery.

Although primarily a practical book with text closely supported by diagrams, some formulae which can be used by straightforward substitution and some simple graphs have also been included.

72 pages

Order code BP278

£4.00

25 SIMPLE INDOOR AND WINDOW AERIALS

E. M. Noll

Many people live in flats and apartments or other types of accommodation where outdoor aerials are prohibited, or a lack of garden space etc. prevents aerials from being erected. This does not mean you have to forgo shortwave-listening, for even a 20-foot length of wire stretched out along the skirting board of a room can produce acceptable results. However, with some additional effort and experimentation one may well be able to improve performance further.

This concise book tells the story, and shows the reader how to construct and use 25 indoor and window aerials that the author has proven to be sure performers. Much information is also given on shortwave bands, aerial directivity, time zones, dimensions etc.

50 pages

Order code BP136

£2.25

THEORY AND REFERENCE

Bebop To The Boolean Boogie

By Clive (call me Max) Maxfield
Specially imported by EPE - Excellent value

An Unconventional Guide to Electronics Fundamentals, Components and Processes

This book gives the "big picture" of digital electronics. This indepth, highly readable, up-to-the-minute guide shows you how electronic devices work and how they're made. You'll discover how transistors operate, how printed circuit boards are fabricated, and what the innards of memory ICs look like. You'll also gain a working knowledge of Boolean Algebra and Karnaugh Maps, and understand what Reed-Muller logic is and how it's used. And there's much, MUCH more (including a recipe for a truly great seafood gumbol). Hundreds of carefully drawn illustrations clearly show the important points of each topic. The author's tongue-in-cheek British humor makes it a delight to read, but this is a REAL technical book, extremely detailed and accurate. A great reference for your own shelf, and also an ideal gift for a friend or family member who wants to understand what it is you do all day...

476 pgs - large format Order code BEB1 £26.95

BEBOP BYTES BACK (and the Boboputer Computer Simulator) CD-ROM

Clive (Max) Maxfield and Alvin Brown

This follow-on to *Bebop to the Boolean Boogie* is a multimedia extravaganza of information about how computers work. It picks up where "Bebop I" left off, guiding you through the fascinating world of computer design...



and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the CD-ROM contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the CD-ROM contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this!

Over 800 pages in Adobe Acrobat format
£21.95 including VAT and p&p

Order code BEB2 CD-ROM

ELECTRONICS MADE SIMPLE

Ian Sinclair

Assuming no prior knowledge, *Electronics Made Simple* presents an outline of modern electronics with an emphasis on understanding how systems work rather than on details of circuit diagrams and calculations. It is ideal for students on a range of courses in electronics, including GCSE, C&G and GNVQ, and for students of other subjects who will be using electronic instruments and methods.

Contents: waves and pulses, passive components, active components and ICs, linear circuits, block and circuit diagrams, how radio works, disc and tape recording, elements of TV and radar, digital signals, gating and logic circuits, counting and correcting, microprocessors, calculators and computers, miscellaneous systems.

199 pages Order code NE23 £13.99

SCROGGIE'S FOUNDATIONS OF WIRELESS AND ELECTRONICS - ELEVENTH EDITION

S. W. Amos and Roger Amos

Scroggie's Foundations is a classic text for anyone working with electronics, who needs to know the art and craft of the subject. It covers both the theory and practical aspects of a huge range of topics from valve and tube technology, and the application of cathode ray tubes to radar, to digital tape systems and optical recording techniques.

Since *Foundations of Wireless* was first published over 60

years ago, it has helped many thousands of readers to become familiar with the principles of radio and electronics. The original author Sowerby was succeeded by Scroggie in the 1940s, whose name became synonymous with this classic primer for practitioners and students alike. Stan Amos, one of the fathers of modern electronics and the author of many well-known books in the area, took over the revision of this book in the 1980s and it is he, with his son, who have produced this latest version.

400 pages Order code NE27 £21.99

GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

96 pages Order code BP239 £4.49

DIGITAL GATES AND FLIP-FLOPS

Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of microprocessor techniques as applied to digital logic.

200 pages Order code PC106 £9.95

MUSIC, AUDIO AND VIDEO

QUICK GUIDE TO ANALOGUE SYNTHESIS

Ian Waugh

Even though music production has moved into the digital domain, modern synthesisers invariably use analogue synthesis techniques. The reason is simple - analogue synthesis is flexible and versatile, and it's relatively easy for us to understand. The basics are the same for all analogue synths, and you'll quickly be able to adapt the principles to any instrument, to edit existing sounds and create exciting new ones. This book describes: How analogue synthesis works; The essential modules every synthesiser has; The three steps to synthesis; How to create phat bass sounds; How to generate filter sweeps; Advanced synth modules; How to create simple and complex synth patches; Where to find soft synths on the Web.

If you want to take your synthesiser - of the hardware or software variety - past the presets, and program your own sounds and effects, this practical and well-illustrated book tells you what you need to know

60 pages Order code PC118 £7.45

QUICK GUIDE TO MP3 AND DIGITAL MUSIC

Ian Waugh

MP3 files, the latest digital music format, have taken the music industry by storm. What are they? Where do you get them? How do you use them? Why have they thrown record companies into a panic? Will they make music easier to buy? And cheaper? Is this the future of music?

All these questions and more are answered in this concise and practical book which explains everything you need to know about MP3s in a simple and easy-to-understand manner. It explains:

How to play MP3s on your computer; How to use MP3s with handheld MP3 players; Where to find MP3s on the Web; How MP3s work; How to tune into Internet radio stations; How to create your own MP3s; How to record your own CDs from MP3 files; Other digital audio music formats.

Whether you want to stay bang up to date with the latest music or create your own MP3s and join the on-line digital music revolution, this book will show you how.

60 pages Order code PC119 £7.45

ALL PRICES INCLUDE UK POST AND PACKING CD-ROM prices include VAT and/or postage to anywhere in the world

ELECTRONIC MUSIC AND MIDI PROJECTS

R. A. Penfold

Whether you wish to save money, boldly go where no musician has gone before, rekindle the pioneering spirit, or simply have fun building some electronic music gadgets, the designs featured in this book should suit your needs. The projects are all easy to build, and some are so simple that even complete beginners at electronic project construction can tackle them with ease. Stripboard layouts are provided for every project, together with a wiring diagram. The mechanical side of construction has largely been left to individual constructors to sort out, simply because the vast majority of project builders prefer to do their own thing in this respect.

None of the designs requires the use of any test equipment in order to get them set up properly. Where any setting up is required, the procedures are very straightforward, and they are described in detail.

Projects covered: Simple MIDI tester, Message grabber, Byte grabber, THRU box, MIDI auto switcher, Auto/manual switcher, Manual switcher, MIDI patchbay, MIDI controlled switcher, MIDI lead tester, Program change pedal, Improved program change pedal, Basic mixer, Stereo mixer, Electronic swell pedal, Metronome, Analogue echo unit.

124 pages Order code PC116 £10.95

THE INVENTOR OF STEREO - THE LIFE AND WORKS OF ALAN DOWER BLUMLEIN

Robert Charles Alexander

This book is the definitive study of the life and works of one of Britain's most important inventors who, due to a cruel set of circumstances, has all but been overlooked by history.

Alan Dower Blumlein led an extraordinary life in which his inventive output rate easily surpassed that of Edison, but whose early death during the darkest days of World War Two led to a shroud of secrecy which has covered his life and achievements ever since.

His 1931 Patent for a Binaural Recording System was so revolutionary that most of his contemporaries regarded it as more than 20 years ahead of its time. Even years after his death, the full magnitude of its detail had not been fully utilized. Among his 128 patents are the principal electronic circuits critical to the development of the world's first electronic television system. During his short working life, Blumlein produced patent after patent breaking entirely new ground in electronic and audio engineering.

During the Second World War, Alan Blumlein was deeply engaged in the very secret work of radar development and contributed enormously to the system eventually to become 'H2S' - blind-bombing radar. Tragically, during an experimental H2S flight in June 1942, the Halifax bomber in which Blumlein and several colleagues were flying, crashed and all aboard were killed. He was just days short of his thirty-ninth birthday.

420 pages Order code NE32 £17.99

VIDEO PROJECTS FOR THE ELECTRONICS CONSTRUCTOR

R. A. Penfold

Written by highly respected author R. A. Penfold, this book contains a collection of electronic projects specially designed for video enthusiasts. All the projects can be simply constructed, and most are suitable for the newcomer to project construction, as they are assembled on stripboard.

There are faders, wipers and effects units which will add sparkle and originality to your video recordings, an audio mixer and noise reducer to enhance your soundtracks and a basic computer control interface. Also, there's a useful selection on basic video production techniques to get you started.

Complete with explanations of how the circuit works, shopping lists of components, advice on construction, and guidance on setting up and using the projects, this invaluable book will save you a small fortune.

Circuits include: video enhancer, improved video enhancer, video fader, horizontal wiper, improved video wiper, negative video unit, fade to grey unit, black and white keyer, vertical wiper, audio mixer, stereo headphone amplifier, dynamic noise reducer, automatic fader, pushbutton fader, computer control interface, 12 volt mains power supply.

124 pages Order code PC115 £10.95

PC MUSIC - THE EASY GUIDE

Robin Vincent

How do I make music on my PC? Can I record music onto my PC? What's a sequencer? How can I get my PC to print a music score? What sort of a soundcard do I need? What hardware and software do I need? How do I connect a keyboard to my PC?

Just a few of the questions you've probably asked. Well, you'll find the answers to all these questions, and many more, in this book. It will show you what can be done, what it all means, and what you will need to start creating your own music on your PC. It's an easy read, it's fully illustrated and it will help you understand how a computer can be used as a creative music tool.

It covers soundcards, sequencers, hard disk digital audio recording and editing, plug-ins, printing scores with notation software, using your PC as a synthesiser, getting music onto and off the Internet, using Windows, sample PC music set-ups, FAQs, a glossary, advice on hardware and software, and a list of industry contacts.

116 pages Order code PC117 £11.95

HIGH POWER AUDIO AMPLIFIER CONSTRUCTION

R. A. Penfold

Practical construction details of how to build a number of audio power amplifiers ranging from about 50 to 300/400 watts r.m.s. includes MOSFET and bipolar transistor designs.

96 pages Order code BP277 £4.49

CIRCUITS AND DESIGN

AN INTRODUCTION TO PIC MICROCONTROLLERS

Robert Penfold
Designing your own PIC based projects may seem a daunting task, but it is really not too difficult providing you have some previous experience of electronics.

The PIC processors have plenty of useful features, but they are still reasonably simple and straightforward to use. This book should contain everything you need to know.

Topics covered include: the PIC register set; numbering systems; bitwise operations and rotation; the PIC instruction set; using interrupts; using the analogue to digital converter; clock circuits; using the real time clock counter (RTCC); using subroutines; driving seven segment displays.

166 pages **Temporarily out of print**

PRACTICAL OSCILLATOR CIRCUITS

A. Filnd
Extensive coverage is given to circuits using capacitors and resistors to control frequency. Designs using CMOS, timer i.c.s and op.amps are all described in detail, with a special chapter on "waveform generator" i.c.s. Reliable "white" and "pink" noise generator circuits are also included.

Various circuits using inductors and capacitors are covered, with emphasis on stable low frequency generation. Some of these are amazingly simple, but are still very useful signal sources.

Crystal oscillators have their own chapter. Many of the circuits shown are readily available special i.c.s for simplicity and reliability, and offer several output frequencies. Finally, complete constructional details are given for an audio sinewave generator.

133 pages **Order code BP393** £5.49

PRACTICAL ELECTRONICS HANDBOOK -

Fifth Edition, Ian Sinclair
Contains all of the everyday information that anyone working in electronics will need.

It provides a practical and comprehensive collection of circuits, rules of thumb and design data for professional engineers, students and enthusiasts, and therefore enough background to allow the understanding and development of a range of basic circuits.

Contents: Passive components, Active discrete components, Circuits, Linear i.c.s., Energy conversion components, Digital i.c.s., Microprocessors and microprocessor systems, Transferring digital data, Digital-analogue conversions, Computer aids in electronics, Hardware components and practical work, Micro-controllers and PLCs, Digital broadcasting, Electronic security.

440 pages **Order code NE21** £16.99

COIL DESIGN AND CONSTRUCTIONAL MANUAL

B. B. Babani
A complete book for the home constructor on "how to make" RF, IF, audio and power coils, chokes and transformers. Practically every possible type is discussed and calculations necessary are given and explained in detail. Although this book is now twenty years old, with the exception of toroids and pulse transformers little has changed in coil design since it was written.

96 pages **Order code 160** £4.49

OPTOELECTRONICS CIRCUITS MANUAL

R. M. Marston
A useful single-volume guide to the optoelectronics device user, specifically aimed at the practical design engineer, technician, and the experimenter, as well as the electronics student and amateur. It deals with the subject in an easy-to-read, down-to-earth, and non-mathematical yet comprehensive manner, explaining the basic principles and characteristics of the best known devices, and presenting the reader with many practical applications and over 200 circuits. Most of the i.c.s and other devices used are inexpensive and readily available types, with universally recognised type numbers.

182 pages **Order code NE14** £20.99

OPERATIONAL AMPLIFIER USER'S HANDBOOK

R. A. Penfold
The first part of this book covers standard operational amplifier based "building blocks" (integrator, precision

rectifier, function generator, amplifiers, etc), and considers the ways in which modern devices can be used to give superior performance in each one. The second part describes a number of practical circuits that exploit modern operational amplifiers, such as high slew-rate, ultra low noise, and low input offset devices. The projects include: Low noise tape preamplifier, low noise RIAA pre-amplifier, audio power amplifiers, d.c. power controllers, opto-isolator audio link, audio millivolt meter, temperature monitor, low distortion audio signal generator, simple video fader, and many more.

120 pages **Order code BP335** £5.45

A BEGINNERS GUIDE TO CMOS DIGITAL ICs

R. A. Penfold
Getting started with logic circuits can be difficult, since many of the fundamental concepts of digital design tend to seem rather abstract, and remote from obviously useful applications. This book covers the basic theory of digital electronics and the use of CMOS integrated circuits, but does not lose sight of the fact that digital electronics has numerous "real world" applications.

The topics covered in this book include: the basic concepts of logic circuits; the functions of gates, inverters and other logic "building blocks"; CMOS logic i.c. characteristics, and their advantages in practical circuit design; oscillators and monostables (timers); flip/flops, binary dividers and binary counters; decade counters and display drivers.

119 pages **Order code BP333** £5.45

AUDIO AND MUSIC

INTRODUCTION TO DIGITAL AUDIO

(Second Edition) Ian Sinclair
The compact disc (CD) was the first device to bring digital audio methods into the home.

This development has involved methods and circuits that are totally alien to the technician or keen amateur who has previously worked with audio circuits. The principles and practices of digital audio owe little or nothing to the traditional linear circuits of the past, and are much more comprehensible to today's computer engineer than the older generation of audio engineers.

This book is intended to bridge the gap of understanding for the technician and enthusiast. The principles and methods are explained, but the mathematical background and theory is avoided, other than to state the end product.

128 pages **Order code PC102** £8.95

VALVE & TRANSISTOR AUDIO AMPLIFIERS

John Linsley Hood
This is John Linsley Hood's greatest work yet, describing the milestones that have marked the development of audio amplifiers since the earliest days to the latest

systems. Including classic amps with valves at their heart and exciting new designs using the latest components, this book is the complete world guide to audio amp design.

Contents: Active components; Valves or vacuum tubes; Solid-state devices; Passive components; Inductors and transformers; Capacitors, Resistors, Switches and electrical contacts; Voltage amplifier stages using valves; Valve audio amplifier layouts; Negative feedback; Valve operated power amplifiers; Solid state voltage amplifiers; Early solid-state audio amplifiers; Contemporary power amplifier designs; Preamplifiers; Power supplies (PSUs); Index.

250 pages **Order code NE24** £21.99

AUDIO AMPLIFIER PROJECTS

R. A. Penfold
A wide range of useful audio amplifier projects, each project features a circuit diagram, an explanation of the circuit operation and a stripboard layout diagram. All constructional details are provided along with a shopping list of components, and none of the designs requires the use of any test equipment in order to set up properly. All the projects are designed for straightforward assembly on simple circuit boards.

Circuits include: High impedance mic preamp, Low impedance mic preamp, Crystal mic preamp, Guitar and GP preamplifier, Scratch and rumble filter, RIAA preamplifier, Tape preamplifier, Audio limiter, Bass and treble tone controls, Loudness filter, Loudness control, Simple graphic equaliser, Basic audio mixer, Small (300mW) audio power amp, 6 watt audio power amp, 20/32 watt power amp and power supply, Dynamic noise limiter.

A must for audio enthusiasts with more sense than money!

116 pages **Order code PC113** £10.95

VALVE AMPLIFIERS

Second Edition, Morgan Jones
This book allows those with a limited knowledge of the field to understand both the theory and practice of valve audio amplifier design, such that they can analyse and modify circuits, and build or restore an amplifier. Design principles and construction techniques are provided so readers can devise and build from scratch, designs that actually work.

The second edition of this popular book builds on its main strength - exploring and illustrating theory with practical applications. Numerous new sections include: output transformer problems; heater regulators; phase splitter analysis; and component technology. In addition to the numerous amplifier and preamplifier circuits, three major new designs are included: a low-noise single-ended LP stage, and a pair of high voltage amplifiers for driving electrostatic transducers directly - one for headphones, one for loudspeakers.

288 pages **Order code NE33** £29.95

LOUDSPEAKERS FOR MUSICIANS

Vivan Capel
This book contains all that a working musician needs to know about loudspeakers; the different types, how they work, the most suitable for different instruments, for cabaret work, and for vocals. It gives tips on constructing cabinets, wiring up, when and where to use wadding, and when not to, what fittings are available, finishing, how to ensure they travel well, how to connect multi-speaker arrays and much more.

Ten practical enclosure designs with plans and comments are given in the last chapter, but by the time you've read that far you should be able to design your own!

164 pages **Order code BP297** £5.49

BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £2 per book. For the rest of the world airmail add £3 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **DIRECT BOOK SERVICE** or card details, Visa, Mastercard, Amex, Diners Club or Switch to: **DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LIMITED, 408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery - more for overseas orders. Please check price and availability (see latest issue of *Everyday Practical Electronics*) before ordering from old lists.

For a further selection of books see the next two issues of *EPE*.

Tel 01202 873872 Fax 01202 874562. E-mail: dbs@epemag.wimborne.co.uk
Order from our online shop at: www.epemag.wimborne.co.uk/shopdoor.htm

BOOK ORDER FORM

Full name:

Address:

.....

..... Post code: Telephone No:

Signature:

I enclose cheque/PO payable to DIRECT BOOK SERVICE for £

Please charge my card £ Card expiry date

Card Number Switch Issue No.

Card Security Code (the last three digits on or just below the signature strip)

Please send book order codes:


.....

Please continue on separate sheet of paper if necessary

**WHETHER ELECTRONICS IS YOUR HOBBY
OR YOUR LIVELIHOOD . . .**

**YOU NEED THE MODERN ELECTRONICS MANUAL
and the ELECTRONICS SERVICE MANUAL**

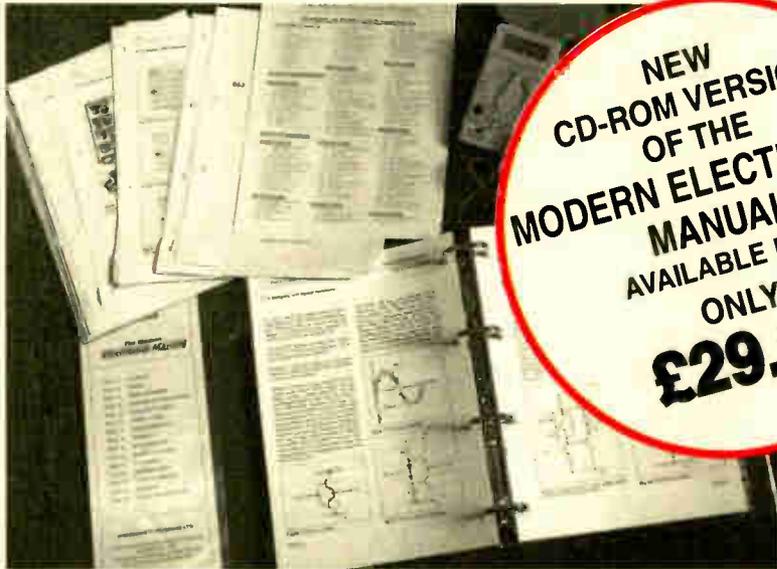THE MODERN ELECTRONICS MANUAL (CD-ROM VERSION ONLY)



**NEW
CD-ROM VERSION
OF THE
MODERN ELECTRONICS
MANUAL
AVAILABLE NOW
ONLY
£29.95**

**The essential reference
work for everyone
studying electronics**

- Over 800 pages
- In-depth theory
- Projects to build
- Detailed assembly instructions
- Full components checklists
- Extensive data tables
- Manufacturers' web links
- Easy-to-use Adobe Acrobat format
- Clear and simple layout
- Comprehensive subject range
- Professionally written
- Regular Supplements

EVERYTHING YOU NEED TO GET STARTED AND GO FURTHER IN ELECTRONICS!

The revised CD-ROM edition of the Modern Electronics Base Manual (MEM) contains practical, easy-to-follow information on the following subjects:

BASIC PRINCIPLES: Electronic Components and their Characteristics (16 sections from Resistors and Potentiometers to Crystals, Crystal Modules and Resonators); Circuits Using Passive Components (10 sections); Power Supplies; The Amateur Electronics Workshop; The Uses of Semiconductors; Digital Electronics (6 sections); Operational Amplifiers; Introduction to Physics, including practical experiments; Semiconductors (5 sections) and Digital Instruments (3 sections).

CIRCUITS TO BUILD: There's nothing to beat the satisfaction of creating your own projects. From basic principles, like soldering and making printed circuit boards, to the tools needed for circuit-building, the Modern Electronics Manual and its Supplements describe clearly, with appropriate diagrams, how to assemble a radio, loudspeaker circuits, amplifiers, car projects,

a computer interface, measuring instruments, workshop equipment, security systems, medical and musical circuits, etc. The Base Manual describes 12 projects including a Theremin and a Simple TENS Unit.

ESSENTIAL DATA: Extensive tables on diodes, transistors, thyristors and triacs, digital and linear i.c.s.

EXTENSIVE GLOSSARY: Should you come across a technical word, phrase or abbreviation you're not familiar with, simply look up the glossary included in the Manual and you'll find a comprehensive definition in plain English.

The Manual also covers **Safety** and provides web links to component and equipment **Manufacturers and Suppliers**. The most comprehensive reference work ever produced at a price you can afford, the CD-ROM edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the **essential** information you need.

THE MODERN ELECTRONICS MANUAL (MEM - CD-ROM version only)

Revised CD-ROM Edition of Basic Work: Contains over 800 pages of information in Adobe Acrobat format. Edited by John Becker.

Regular Supplements: Additional CD-ROMs each containing approximately 500 pages of additional information on specific areas of electronics are available for £19.95 each. Information on the availability and content of each Supplement CD-ROM will be sent to you.

Presentation: CD-ROM suitable for any modern PC. Requires Adobe Acrobat Reader which is included on the MEM CD-ROM.

Price of the Basic Work: £29.95 POST FREE.

ORDER BOTH MANUALS TOGETHER AND SAVE £20

A mass of well-organised and clearly explained information is brought to you by expert editorial teams whose combined experience ensures the widest coverage. Regular Supplements to these unique publications, keep you abreast of the latest technology and techniques if required.

ELECTRONICS SERVICE MANUAL

(PRINTED VERSION ONLY)

EVERYTHING YOU NEED TO KNOW TO GET STARTED IN REPAIRING AND SERVICING ELECTRONIC EQUIPMENT

SAFETY: Be knowledgeable about Safety Regulations, Electrical Safety and First Aid.

UNDERPINNING KNOWLEDGE: Specific sections enable you to Understand Electrical and Electronic Principles, Active and Passive Components, Circuit Diagrams, Circuit Measurements, Radio, Computers, Valves and Manufacturers' Data, etc.

PRACTICAL SKILLS: Learn how to identify Electronic Components, Avoid Static Hazards, Carry Out Soldering and Wiring, Remove and Replace Components.

TEST EQUIPMENT: How to Choose and Use Test Equipment, Assemble a Toolkit, Set Up a Workshop, and Get the Most from Your Multimeter and Oscilloscope, etc.

SERVICING TECHNIQUES: The regular Supplements include vital guidelines on how to Service Audio Amplifiers, Radio Receivers, TV Receivers, Cassette Recorders, Video Recorders, Personal Computers, etc.

TECHNICAL NOTES: Commencing with the IBM PC, this section and the regular Supplements deal with a very wide range of specific types of equipment – radios, TVs, cassette recorders, amplifiers, video recorders etc..

REFERENCE DATA: Detailing vital parameters for Diodes, Small-Signal Transistors, Power Transistors, Thyristors, Triacs and Field Effect Transistors. Supplements include Operational Amplifiers, Logic Circuits, Optoelectronic Devices, etc.

The essential work for servicing and repairing electronic equipment

- Around 900 pages
- Fundamental principles
- Troubleshooting techniques
- Servicing techniques
- Choosing and using test equipment
- Reference data
- Easy-to-use format
- Clear and simple layout
- Vital safety precautions
- Professionally written
- Regular Supplements
- Sturdy gold blocked ring-binder

ELECTRONICS SERVICE MANUAL

(ESM – Printed version only)

Basic Work: Contains around 900 pages of information. Edited by Mike Tooley BA
Regular Supplements: Unlike a book or encyclopedia, this Manual is a living work – continuously extended with new material. If requested, Supplements are sent to you on approval approximately every three months. Each Supplement contains around 160 pages – all for only £23.50+£2.50 p&p. You can, of course, return any Supplement (within ten days) which you feel is superfluous to your needs. You can also purchase a range of past Supplements to extend your Base Manual on subjects of particular interest to you.

Presentation: Durable looseleaf system in large A4 format

Price of the Basic Work: £29.95
 (to include a recent Supplement FREE).



Guarantee

Our 30 day money back guarantee gives you **complete peace of mind**. If you are not entirely happy with the *Electronics Service Manual*, for whatever reason, simply return it to us in good condition within 30 days and we will make a **full refund of your payment** – no small print and no questions asked. All we ask is that you pay the return postage. (Overseas buyers also have to pay our overseas postage charge). Sorry, but we can only make **exchanges on the Modern Electronics Manual (CD-ROM version) if the CD-ROM is faulty**, we cannot offer a money back guarantee on this product as the content can be printed out.

Wimborne Publishing Ltd., Dept Y5, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562.
 Online shop: www.epemag.wimborne.co.uk/shopdoor.htm

PLEASE send me



- THE MODERN ELECTRONICS MANUAL (CD-ROM version only)
- ELECTRONICS SERVICE MANUAL plus a FREE SUPPLEMENT (Printed version only)
- I enclose payment of £29.95 (for one Manual) or £39.90 for both Manuals (saving £20 by ordering both together) plus postage if applicable.
- I also require the appropriate ESM Supplements four times a year. These are billed separately and can be discontinued at any time. (Please delete if not required.)

FULL NAME (PLEASE PRINT)

ADDRESS

.....

.....POSTCODE

SIGNATURE

- I enclose cheque/PO in UK pounds payable to Wimborne Publishing Ltd.
- Please charge my Visa/Mastercard/Amex/Diners Club/Switch Switch Issue No

Card No

Card Exp. Date Card Security Code

(The last 3 digits on or just under the signature strip)

ORDER FORM

Simply complete and return the order form with your payment to the following address:

Wimborne Publishing Ltd, Dept. Y5, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND

We offer a 30 day MONEY BACK GUARANTEE on ESM – see the panel above for details.

POSTAGE CHARGES FOR ESM

MEM CD-ROM POST FREE TO ALL COUNTRIES
 (Note we use the VAT portion of the MEM CD-ROM payment to pay for overseas postage)

Postal Region	Price PER ESM PRINTED MANUAL	
	Surface	Air
Mainland UK	FREE	–
Scottish Highlands, UK Islands & Eire	£7 each	–
Europe (EU)	–	£23 each
Europe (Non-EU)	£23 each	£30 each
USA & Canada	£28 each	£39 each
Far East & Australasia	£35 each	£43 each
Rest of World	£28 each	£52 each

Please allow four working days for UK delivery.

NOTE: Surface mail can take over 10 weeks to some parts of the world. Each ESM weighs about 4kg when packed.

mem-cd

PRACTICAL ELECTRONICS

Everyday Practical Electronics reaches twice as many UK readers as any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last eighteen years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, Mill Lodge, Mill Lane, Thorpe-le-Soken, Essex CO16 0ED. Phone/Fax (01255) 861161.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

TOTALROBOTS

ROBOTICS, CONTROL & ELECTRONICS TECHNOLOGY

High quality robot kits and components
UK distributor of the OOPic microcontroller

Secure on-line ordering
Rapid delivery
Highly competitive prices

Visit www.totalrobots.com

Tel: 0208 823 9220

X-10® Home Automation We put you in control™

Why tolerate when you can automate?

An extensive range of 230V X-10 products and starter kits available. Uses proven Power Line Carrier technology, no wires required.

Products Catalogue available Online.
Worldwide delivery.

Laser Business Systems Ltd.

E-Mail: info@laser.com

<http://www.laser.com>

Tel: (020) 8441 9788

Fax: (020) 8449 0430



GREENWELD Mail Order Specialists

ELECTRICAL & ELECTRONIC COMPONENTS & KITS, TOOLS, MATERIALS & HARDWARE

Ask now for our FREE catalogue with the latest special offers

Greenweld Limited
Unit 14 Hornum Industrial Park
West Hornum • Brentwood • Essex • CM13 3XD
Tel: 01277 811042 • Fax: 01277 812419
Email: bargains@greenweld.co.uk
Visit our website www.greenweld.co.uk

PC Oscilloscope & Signal Generator



Affordable Digital PC Oscilloscope and Signal Generator. Plugs into printer port. Samples at up to 20MHz or 30MHz. Generates sine, triangular, saw, square and sweep wave. Custom wave downloaded and output at 20MHz or 30MHz step rates.

Prices from £139.00

Visit www.clsystem.co.uk or call 07986 860815

VV TRANSFORMERS


Transformers and Chokes for all types of circuits including specialist valve units
Custom design or standard range
High and low voltage

Variable Voltage Technology Ltd

Unit 3, Sheat Manor Farm, Chillerton,
Newport, Isle of Wight, PO30 3HP
Tel: 0870 243 0414 Fax: 01983 280593
email: sales@vvt-cowes.freemove.co.uk

www.vvttransformers.co.uk

Cooke International

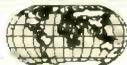

www.cooke-int.com

Electronic Test & Measuring Equipment

Tel: (+44) 0 1243 55 55 90

Operating & Service Manuals

BTEC ELECTRONICS TECHNICIAN TRAINING

VCE ADVANCED ENGINEERING
ELECTRONICS AND ICT
HNC AND HND ELECTRONICS
NVQ ENGINEERING AND IT
**PLEASE APPLY TO COLLEGE FOR
NEXT COURSE DATE**
FULL PROSPECTUS FROM

**LONDON ELECTRONICS COLLEGE
(Dept EPE) 20 PENYWERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: (020) 7373 8721**

BOWOOD ELECTRONICS LTD

Contact Will Outram for your
Electronic Components

Email: sales@bowood-electronics.co.uk

Web: www.bowood-electronics.co.uk

7 Bakewell Road, Baslow, Derbyshire DE45 1RE

Tel/Fax: 01246 583777

Send 41p stamp for catalogue

EPE NET ADDRESSES

EPE FTP site: <ftp://ftp.epemag.wimborne.co.uk>

Access the FTP site by typing the above into your web browser, or by setting up an FTP session using appropriate FTP software, then go into quoted sub-directories:

PIC-project source code files: [/pub/PICS](#)

PIC projects each have their own folder; navigate to the correct folder and open it, then fetch all the files contained within. *Do not try to download the folder itself!*

EPE text files: [/pub/docs](#)

Basic Soldering Guide: [solder.txt](#)

Ingenuity Unlimited submission guidance: [ing_unit.txt](#)

New readers and subscribers info: [epe_info.txt](#)

Newsgroups or Usenet users advice: [usenet.txt](#)

Ni-Cad discussion: [nicadfaq.zip](#) and [nicad2.zip](#)

Writing for EPE advice: [write4us.txt](#)

You can also enter the FTP site via the link at the top of the main page of our home site at:

<http://www.epemag.wimborne.co.uk>

Shop now on-line: www.epemag.wimborne.co.uk/shopdoor.htm

Miscellaneous

FREE PROTOTYPE PRINTED CIRCUIT BOARDS! Free prototype p.c.b. with quantity orders. Call Patrick on 028 9073 8897 for details. Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast BT5 4GX.

PRINTED CIRCUIT BOARDS - QUICK SERVICE. Prototype and production artwork raised from magazines or draft designs at low cost. PCBs designed from schematics. Production assembly, wiring and software programming. For details contact Patrick at Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast, BT5 4GX. Phone 028 9073 8897, Fax 028 9073 1802, Email agar@argonet.co.uk.

G.C.S.E. ELECTRONICS KITS, TOOLS, pocket money prices. S.A.E. for free catalogue. SIR-KIT Electronics, 52 Severn Road, Clacton, CO15 3RB. www.geocities.com/sirkituk.

VALVES AND ALLIED COMPONENTS IN STOCK - please ring for free list. Valve equipment repaired. Geoff Davies (Radio). Phone 01788 574774.

REQUIRE "EXPERT" CONSULTATIONS by correspondence etc. to plug-the-gaps re: repairing of older computer equipment (286/386 etc)? Interested? Ancient of Days to: fredeaves@yahoo.co.uk. 10 Station Close, Swansthorpe, Norfolk NR14 8PW.

END HARDWARE HEADACHES! You've assembled your circuit and written your software but you cannot find that enclosure or other mechanical component? Why not contact Chaffinch Engineering? Telephone 020 8898 0933 or write: Unit 4, 37 Hamilton Road, Twickenham, Middlesex TW2 6SN. Website: www.chaffinch-engineering.co.uk. Work in: metal, plastic and wood. Reasonable rates. No job too small.

BUILD A COMMUNICATIONS RECEIVER! Fascinating projects from £10.50. Free catalogue, 33p sae. QRP, 27 Amberley Street, Bradford, W. Yorkshire, BD3 8QZ.

B.S.R. TAPE DECK, 240V, 3-speed plus heads, £9.95. Parcel: amplifiers, tuners, £16. K.I.A., 1 Regent Road, Ilkley LS29.

FREE Catalogue Available On Request



WCN Supplies • Dept EPE • The Old Grain Store • Rear Of 62 Rumbridge Street • Totton • Southampton • SO40 9DS
Telephone or Fax On Southampton 023 8066 0700 • Email: info@wcn-supplies.fsnet.co.uk

Telephone, Fax Or Email For Your Free Catalogue

Autonomous Programmable Robot Kits
Accessories - Sensors - Controller Boards

competition-robotics.com

Secure on-line ordering. Fast, friendly service.



Tel: 01793 636119 Fax: 01793 705772
e-Mail: sales@competition-robotics.com

Web: www.competition-robotics.com

YOUR FUTURE LOOKS BRIGHT WITH ICS

Make a real success of yourself by gaining the vital skills and qualifications you need with an ICS home study course. You learn in your own time, at your own pace and from the comfort of your home. And with over 13 million successful students, you'll be joining the most experienced home study school in the world. You can do it with ICS! So why not improve your job prospects today by calling us now or returning the coupon below.

Electrical Contracting & Installation
Electrical Engineering
C&G Basic Electronic Engineering
C&G Basic Mechanical Engineering
TV & Video Servicing
Radio & Hi-Fi Servicing
Refrigeration, Heating & Air Conditioning
Motorcycle & ATV Repair

FREEPHONE 0500 581 557 www.icslern.co.uk

Or write to: International Correspondence Schools, FREEPOST 882, 8 Elliot Place, Clydeside Skypark, Glasgow, G3 8BR. Tel: 0500 581 557 or from Eire call 1846 620 490

Please send me my Free Information on your Technical Courses.


Mr/Ms/Ms/Ms (BLOCK CAPITALS PLEASE) _____ Date of Birth: / /
Address: _____
Postcode: _____
E-mail: _____ Tel No: _____

From time to time, we permit other carefully screened organisations to write to you about products and services. If you prefer not to hear from such organisations please tick box Dept ZEEVC1C3

N. R. BARDWELL LTD (Est. 1948)

100	Signal Diodes 1N4148	£1.00	80	Ass'd capacitors electrolytic	£1.00
25	Rectifier Diodes 1N4001	£1.00	80	Ass'd capacitors 1nF to 1µF	£1.00
50	Rectifier Diodes 1N4007	£1.00	200	Ass'd disc ceramic capacitors	£1.00
10	W01 Bridge Rectifiers	£1.00	50	Ass'd. Sial Presets (sn, stand, varmet)	£1.00
10	5/5 Timer IC's	£1.00	50	Ass'd. RF inductors (inductors)	£1.00
4	741 Op Amps	£1.00	50	Ass'd. grommets	£1.00
50	Assorted Zener Diodes 400mW	£1.00	10	Ass'd. crystals - plug in	£1.00
12	Assorted 7-segment Displays	£1.00	8	Ass'd. switches	£1.00
35	Assorted I.e.d.s, various shapes, colours & sizes	£1.00	20	Miniature slide switches spst	£1.00
25	5mm I.e.d.s, red, green or yellow	£1.00	8	Ass'd. push-button switches multi-bank, multi-pole	£1.00
25	3mm I.e.d.s, red, green or yellow	£1.00	30	Ass'd. di! sockets up to 40 way	£1.00
75	5mm I.e.d.s, green, 6-5mm legs	£1.00	10	TV coax plugs, plastic	£1.00
40	Axial I.e.d.s, 2mcd red Diode Package	£1.00	40	metres very thin connecting wire, red	£1.00
25	Ass'd. High Brightness I.e.d.s, var cols	£1.00	20	1in. glass reed switches	£1.00
30	BC182L Transistors	£1.00	100	Any one value 1/4W 5% of resistors range 1R to 10M	£0.45
35	BC212L Transistors	£1.00	10	7812 Voltage Regulators	£1.00
40	BC237 Transistors	£1.00	300	Ass'd resistors, 1/4W/1/2W, mostly on tapes	£1.00
20	BC327 Transistors	£1.00			
30	BC328 Transistors	£1.00			
30	EC547 Transistors	£1.00			
20	BC547B Transistor	£1.00			
30	BC548 Transistors	£1.00			
30	BC549 Transistors	£1.00			
25	BC567 Transistors	£1.00			
30	BC558 Transistors	£1.00			
30	BC559 Transistors	£1.00			
20	2N3904 Transistors	£1.00			
100	1nF 50V wkg Axial Capacitors	£1.00			
100	4N7 50V wkg Axial Capacitors	£1.00			

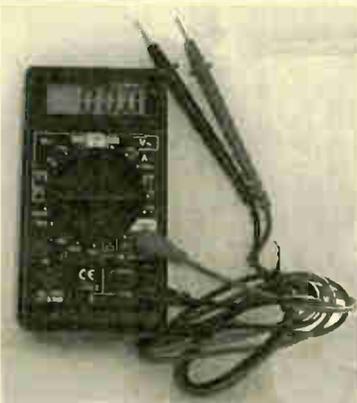268 Abbeydale Road, Sheffield S7 1FL
Phone (local rate): 0845 166 2329
Fax: 0114 255 5039
e-mail: sales@bardwells.co.uk Web: www.bardwells.co.uk
Prices include VAT. Postage £1.55
44p stamp for lists or disk
POs, Cheques and Credit Cards accepted



DIGITAL TEST METER

Built-in transistor test socket and diode test position.
DC volts 200mV to 1000V.
AC volts 200V to 750V.
DC current 200mA to 10A.
Resistance 200 ohms to 2000K ohms.

£5.99 incl. VAT

SEE OUR WEB PAGES FOR MORE COMPONENTS AND SPECIAL OFFERS
www.bardwells.co.uk

SHERWOOD ELECTRONICS

FREE COMPONENTS

Buy 10 x £1 Special Packs and choose another one FREE

SP1	15 x 5mm Red LEDs	SP134	15 x 1N4007 diodes
SP2	12 x 5mm Green LEDs	SP135	6 x Miniature slide switches
SP3	12 x 5mm Yellow LEDs	SP136	3 x BFY50 transistors
SP6	15 x 3mm Red LEDs	SP137	4 x W005 1.5A bridge rectifiers
SP7	12 x 3mm Green LEDs	SP138	20 x 2.2/63V radial elect. caps.
SP8	10 x 3mm Yellow LEDs	SP140	3 x W04 1.5A bridge rectifiers
SP10	100 x 1N4148 diodes	SP142	2 x CMOS 4017
SP11	30 x 1N4001 diodes	SP143	5 Pairs min. crocodile clips (Red & Black)
SP12	30 x 1N4002 diodes	SP145	6 x ZTX300 transistors
SP18	20 x BC182 transistors	SP146	10 x 2N3704 transistors
SP20	20 x BC184 transistors	SP147	5 x Stripboard 9 strips x 25 holes
SP21	20 x BC212 transistors	SP151	4 x 8mm Red LEDs
SP23	20 x BC549 transistors	SP152	4 x 8mm Green LEDs
SP24	4 x CMOS 4001	SP153	4 x 8mm Yellow LEDs
SP25	4 x 555 timers	SP154	15 x BC548 transistors
SP26	4 x 741 Op.Amps	SP156	3 x Stripboard, 14 strips x 27 holes
SP28	4 x CMOS 4011	SP160	10 x 2N3904 transistors
SP29	3 x CMOS 4013	SP161	10 x 2N3906 transistors
SP34	20 x 1N914 diodes	SP165	2 x LF351 Op.Amps
SP36	25 x 10/25V radial elect. caps.	SP166	20 x 1N4003 diodes
SP37	12 x 100/35V radial elect. caps.	SP167	5 x BC107 transistors
SP39	10 x 470/16V radial elect. caps.	SP168	5 x BC108 transistors
SP40	15 x BC237 transistors	SP172	4 x Standard slide switches
SP41	20 x Mixed transistors	SP174	20 x 22/25V radial elect. caps.
SP42	200 x Mixed 0.25W C.F. resistors	SP175	20 x 1/63V radial elect. caps.
SP47	5 x Min. PB switches	SP177	10 x 1A 20mm quick blow fuses
SP49	4 x 5 metres stranded core wire	SP182	20 x 4-7/63V radial elect. caps.
SP102	20 x 8-pin DIL sockets	SP183	20 x BC547 transistors
SP103	15 x 14-pin DIL sockets	SP187	15 x BC239 transistors
SP104	15 x 16-pin DIL sockets	SP189	4 x 5 metres solid core wire
SP105	4 x 74LS00	SP192	3 x CMOS 4066
SP109	15 x BC557 transistors	SP195	3 x 10mm Yellow LEDs
SP112	4 x CMOS 4093	SP197	6 x 20 pin DIL sockets
SP115	3 x 10mm Red LEDs	SP198	5 x 24 pin DIL sockets
SP116	3 x 10mm Green LEDs	SP199	5 x 2.5mm mono jack plugs
SP124	20 x Assorted ceramic disc caps	SP200	5 x 2.5mm mono jack sockets
SP126	6 x Battery clips - 3 ea. PP3 + PP9		
SP130	100 x Mixed 0.5W C.F. resistors		
SP131	2 x TL071 Op.Amps		
SP133	20 x 1N4004 diodes		

RESISTOR PACKS - C.Film

RP3	5 each value - total 365 0.25W	£3.10
RP7	10 each value - total 730 0.25W	£4.35
RP10	1000 popular values 0.25W	£6.25
RP4	5 each value-total 345 0.5W	£4.00
RP8	10 each value-total 690 0.5W	£6.65
RP11	1000 popular values 0.5W	£8.50

2003 Catalogue now available £1 inc. P&P or FREE with first order. P&P £1.50 per order. NO VAT

Orders to:
Sherwood Electronics,
7 Williamson St., Mansfield,
Notts. NG19 6TD.

Watch Slides on TV.

Make videos of your slides. Digitise your slides (using a video capture card)

"Liesgang diatv" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. More details see www.diatv.co.uk.

£91.91 + VAT = £108.00



Board cameras all with 512 x 582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10V and 12V DC 150mA.

47MIR size 60 x 36 x 27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye) £37.00 + VAT = £43.48

30MP size 32 x 32 x 14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole £35.00 + VAT = £41.13

40MC size 39 x 38 x 27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses £32.00 + VAT = £37.60

Economy C mount lenses all fixed focus & fixed iris

VSL1220F 12mm F1.6 12 x 15 degrees viewing angle £15.97 + VAT £18.76

VSL4022F 4mm F1.22 63 x 47 degrees viewing angle £17.65 + VAT £20.74

VSL6022F 6mm F1.22 42 x 32 degrees viewing angle £19.05 + VAT £22.38

VSL8020F 8mm F1.22 32 x 24 degrees viewing angle £19.90 + VAT £23.38

Better quality C Mount lenses

VSL1614F 16mm F1.6 30 x 24 degrees viewing angle £26.43 + VAT £31.06

VWL813M 8mm F1.3 with iris 56 x 42 degrees viewing angle £77.45 + VAT = £91.00

1206 surface mount resistors E12 values 10 ohm to 1M ohm

100 of 1 value £1.00 + VAT 1000 of 1 value £5.00 + VAT

866 battery pack originally intended to be used with an orbitel mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily

£7.46 + VAT = £8.77



Please add £1.66 + vat = £1.95 postage & packing per order

JPG Electronics

Shaws Row, Old Road, Chesterfield, S40 2RB.

Tel 01246 211202 Fax 01246 550959

Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

STILL IN BUSINESS

Most items advertised or listed previously are probably still in stock, including the **BT INSULATION TESTER** with multimeter which internally generates voltage which enables you to read insulation directly in megohms. The multimeter has 4 ranges AC/DC volts, 3 ranges DC milliamps, 3 ranges resistance and 5 amp range. These instruments are tested and guaranteed OK, probably cost at least £50 each, yours for only **£7.50** with leads, carrying case **£2** extra. Order Ref: 7.5P4.

J & N FACTORS

Stairbridge Lane, Bolney, RH17 5PA

Telephone (01444) 881965

ADVERTISERS INDEX

ASTBURY JONES	331
AUTOTRAX	337
N. R. BARDWELL	375
B.K. ELECTRONICS	Cover (iv)/324
BRUNNING SOFTWARE	351
BULL ELECTRICAL	Cover (ii)
CRICKLEWOOD ELECTRONICS	310
CROWNHILL ASSOCIATES	Cover (iii)
DISPLAY ELECTRONICS	306
ENERGISE TECHNOLOGY	375
ESR ELECTRONIC COMPONENTS	314
FOREST ELECTRONIC DEVELOPMENTS	311
ICS	375
J & N FACTORS	376
JPG ELECTRONICS	376
LABCENTER	325
MAGENTA ELECTRONICS	312/313
MATRIX MULTIMEDIA	341
MILFORD INSTRUMENTS	340
PEAK ELECTRONIC DESIGN	333
PICO TECHNOLOGY	345
QUASAR ELECTRONICS	308/309
SHERWOOD ELECTRONICS	376
SQUIRES	310
STEWART OF READING	310
TECHNOBOTS	353
TOTAL ROBOTS	341
WCN SUPPLIES	375

ADVERTISEMENT MANAGER: PETER J. MEW

ADVERTISEMENT OFFICES:

EVERYDAY PRACTICAL ELECTRONICS, ADVERTISEMENTS, MILL LODGE, MILL LANE, THORPE-LE-SOKEN, ESSEX CO16 0ED.

Phone/Fax: (01255) 861161

For Editorial address and phone numbers see page 315

PIC BASIC

Crownhill Associates

smart electronic solutions

The most cost effective solution to PIC programming and development - Ever!!

Proton ^{New Improved} LET PIC BASIC

- ReWritten from the ground up
- Best Value For Money
- Most powerful entry level compiler
- 100% MPASM™ compatibility
- Windows™ 98,ME,2000,NT & XP compliant
- Real-Time Syntax checking
- Integrated PIC Programmer driver
- Program with one keystroke
- View BASIC and the resulting Assembly
- Supplied with book "LET PIC BASIC Unleashed" by Les Johnson

Free Evaluation copy from:
www.picbasic.org

LET PIC BASIC £65.00


Proton ^{ACCESS THE WORLD OF} SMART SMART CARDS

PIC BASIC Smart Card Development system

Another First from Crownhill, access the world of SMART CARDS using PIC BASIC. This versatile development system provides a platform for the development of applications using SMART memory cards and SECURE memory cards. Detailed documentation describes all aspects of development using the sample cards supplied, source code and circuit diagrams are included.

- Includes card Reader Writer hardware and circuit
- Integrated Boot Loader - No programmer required
- Sample cards, Documentation
- Fully commented LICENSE FREE Source code

Proton Smart from £59.95

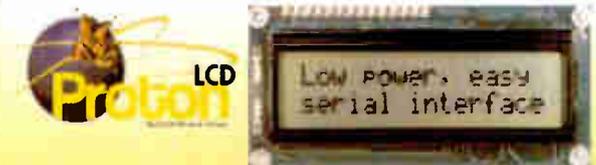

2x16 serial LCD display, supplied as a kit or ready assembled. PCB, PICmicro, LCD display, Circuit, LICENSE FREE commented source code

Proton LCD £16.95

Proton ^{PIC BASIC Plus} v2

- Windows™ Integrated Development Environment
- Integrated serial bootloader software "program without a programmer!"
- Support for 12/14/18bit series devices
- Handles 32bit signed and unsigned variables (numbers up to ± 2147483647)
- Specific commands for on-chip peripherals
- Comprehensive command set
 - Tighter code generation than MBASIC
 - More functionality than MELABS PICBASIC Pro
 - More flexible than all BASIC Stamps
- Integrates directly into Proteus VSM - allows you to build a virtual circuit and see your BASIC code run in real-time - see www.labcenter.co.uk
- Easy macro Integration (includes Floating pointmath example)
- Aimed at graduates, and professionals, all code produced is LICENCE FREE

Free Evaluation copy from:
www.picbasic.org

Crownhill PIC BASICv2 £125.00

Proton ^{PIC BASIC / InterNet} Development System

The worlds First PIC BASIC InterNet development system allowing PIC BASIC projects to communicate across the WORLD via the InterNet. Development board includes RS232, Ethernet Interface and dedicated controller, LCD, Prototype area, Power supply and full documentation.

Proton Net £169.95

Visit www.picbasic.org for comprehensive details of these and other PIC BASIC products, including:



Full range of DEVELOPMENT boards, incl Graphics LCD's and Audio



www.labcenter.co.uk
Proteus VSM Fully supported by PICBASIC Plus



Infra RED TX and Rx development system, with experiments and source code

All prices subject to Postage Packing and VAT
All major credit cards accepted, telephone, web or mail order.

www.picbasic.org

32 Broad Street, Ely, Cambs, CB7 4AF United Kingdom Tel: +44 (0) 1353 666709 Fax: +44 (0) 1353 666707



**POWER AMPLIFIER MODULES-LOUDSPEAKERS-MIXERS
19 INCH STEREO AMPLIFIERS-ACTIVE CROSS/OVERS.**

- * PRICES INCLUDE V.A.T.
- * PROMPT DELIVERY

**OMP MOS-FET POWER AMPLIFIERS
HIGH POWER, TWO CHANNEL 19 INCH RACK**

10,000's
SOLD
TO PRO
USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)
MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS ARE R.M.S. INTO 4 OHMS, WITH BOTH CHANNELS DRIVEN
FEATURES:- * Independent power supplies with two toroidal transformers
* Twin L.E.D. Vu Meters * Level controls * Illuminated on/off switch * Jack / XLR inputs
* Speakon Outputs * Standard 775mv inputs * Open and Short circuit proof * Latest Mos-Fets
for stress free delivery into virtually any load * High slew rate * Very low distortion * Aluminium
cases * MXF600 & MXF900 fan cooled with D.C. Loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC

SIZES:-
MXF200 W19" D11" H3 1/2" (2U)
MXF400 W19" D12" H5 1/4" (3U)
MXF600 W19" D13" H5 1/4" (3U)
MXF900 W19" D14" H5 1/4" (3U)

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL £12.50 Each



FLIGHTCASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of latest loudspeaker technology and enclosure designs. All models utilise high quality studio cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands. The FC15-300 incorporates a large 16 X 6 inch horn. All cabinets are fitted with the latest Speakon connectors for your convenience and safety. Five models to choose from.

WEDGE MONITOR



PLEASE NOTE:- POWER RATINGS QUOTED ARE IN WATTS R.M.S. FOR EACH INDIVIDUAL CABINET ALL ENCLOSURES ARE 8 OHMS

15=15 Inch speaker
12=12 Inch speaker

- ibi FC15-300 WATTS Freq Range 35Hz-20kHz, Sens 101dB, Size H695 W502 D415mm Price:- £299.00 per pair
- ibi FC12-300 WATTS Freq Range 45Hz-20kHz, Sens 96dB, Size H600 W405 D300mm Price:- £249.00 per pair
- ibi FC12-200 WATTS Freq Range 40Hz-20kHz, Sens 97dB, Size H600 W405 D300mm Price:- £199.00 per pair
- ibi FC12-100 WATTS Freq Range 45Hz-20kHz, Sens 100dB, Size H546 W380 D300mm Price:- £179.00 per pair
- ibi WM12-200 WATTS Freq Range 40Hz-20kHz, Sens 97dB, Size H418 W600 D385mm Price:- £125.00 Each

SPECIALIST CARRIER DEL £12.50 per pair wedge monitor £7.00 each
Optional Metal Stands PRICE £49.00 per pair Delivery:- £6.00

CATALOGUE 2001-2002

The Sky's The Limit Catalogue

Robots, Test & Tools, Electronic Kits, Communication, Security, Order Accessories

B.K. Electronics

Unit 1, Comet Way, Southend-on-Sea, Essex, SS2 6TR
Tel: 01702-527572 Fax: 01702-420243
E-mail: sales@bkelec.com Web: www.bkelec.com

FREE Our Sky's over 3000 items... The catalogue is free with any item ordered from this advert and to personal callers of £4.00 to cover P&P if ordered by mail. This is fully refundable with your first order.

OMP X03-S STEREO 3 WAY ACTIVE CROSSOVER

SWITCHABLE 2-WAY



BASS MID TOP CONFIGURED 3 WAY
BASS/MID TOP 2 WAY BASS/MID COMBINED
BASS MID/TOP 2 WAY MID/TOP COMBINED

FEATURES:-
Advanced 3-Way Stereo Active Cross-Over (Switchable two way), housed in a 19" x 1U case. Each channel has three level controls: Bass, Mid & Top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency; There are two versions available:- X03-S Bass-Mid 125/250/500Hz, Mid-Top 1.8/3/5kHz, all at 24 dB per octave. X03-B Bass-Mid 250/500/600Hz, Mid-Top 1.8/3/5kHz, all at 24 dB per Octave. Please make sure you ask for the correct model when ordering. The 2/3 way selector switches are also made by removing the front fascia. Each stereo channel can be configured separately. Bass Invert Switches are incorporated on each channel. Nominal 775mv input/output. Fully compatible with the OMP Rack Amplifier and Modules.

BOTH MODELS PRICED AT :- £117.44 + £5.00 P&P

OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heatsink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS

OMP/MF 100 Mos-Fet Output Power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. 110dB, Size 300 x 123 x 60mm. Price:- £42.85 + £4.00 P&P

OMP/MF 200 Mos-Fet Output Power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Size 300 x 155 x 100mm. Price:- £66.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output Power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Size 330 x 175 x 100mm. Price:- £83.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output Power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti Thump Delay. Size 385 x 210 x 105mm. Price:- £135.85 + £6.00 P&P

OMP/MF 1000 Mos-Fet Output Power 1000 watts R.M.S. into 2 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti Thump Delay. Size 422 x 300 x 125mm. Price:- £261.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV/BANDWIDTH 100kHz OR PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BANDWIDTH 50kHz. ORDER STANDARD OR PEC

100 WATT ACTIVE SUB BASS AMPLIFIER PANEL



AN ACTIVE SUB BASS AMPLIFIER WITH A TRUE 100W RMS OUTPUT. SUPERB CONSTRUCTION WITH THE FACILITIES TO INTEGRATE SEAMLESSLY INTO MOST HI-FI OR HOME CINEMA SETUPS. USE THIS PANEL PLUS ONE OF OUR LOUDSPEAKERS TO MAKE YOUR OWN SUB WOOFER THAT WILL MATCH OR BEAT MOST COMMERCIALLY AVAILABLE SUB WOOFERS.

FEATURES:- * 100W RMS INTO 8 OHMS * HIGH AND LOW LEVEL INPUTS * TOROIDAL TRANSFORMER * SHORT CIRCUIT PROTECTION * D.C. SPEAKER PROTECTION * FREQUENCY ROLL OFF, LOWER 10Hz, UPPER 60Hz TO 240Hz (FULLY ADJUSTABLE) * AC3 COMPATIBLE FILTER CAN BE BYPASSED FOR 5-1 FORMATS. * AIRTIGHT CONSTRUCTION * TENS OF THOUSANDS OF OUR PANELS ALREADY IN USE. * COMPLETE WITH LEADS

SPECIFICATIONS:- POWER 100W RMS @ 8 OHMS * FREQ RESP. 10Hz 15kHz -3dB * DAMPING FACTOR >200 * DISTORTION 0.05% * S/N A WEIGHTED >100dB * SUPPLY 230V A.C. * WEIGHT 2.7Kg * SIZE H254 X W254 X D94mm

THERE ARE 2 VERSIONS OF THE ABOVE PANEL AVAILABLE :- BSB100/8 8 OHM VERSION BSB100/4 4 OHM VERSION BOTH PANELS ARE PRICED AT £117.44 + £5.00 P&P INCL. V.A.T. CHECK WEBSITE FOR PANELS UP TO 500W



DELIVERY CHARGES:- PLEASE INCLUDE AS ABOVE. TO A MAXIMUM AMOUNT £30.00. OFFICIAL ORDERS FROM SCHOOL, COLLEGES, GOVT. PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER. CREDIT CARD ORDERS ACCEPTED BY POST PHONE OR FAX.



B.K. ELECTRONICS REF D5
UNIT 1 COMET WAY, SOUTHEAST-ON-SEA, ESSEX. SS2 6TR.
TEL.: 01702-527572 FAX.: 01702-420243
Web:- <http://www.bkelec.com> E-Mail sales@bkelec.com