

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EVERYDAY

OCTOBER 2005

# PRACTICAL ELECTRONICS

£3.30

**USB THE EASY WAY**  
PIC-Based USB Interface

**PHOTIC PHONE**  
A digital optical 'phone link

**HALLOWEEN HOWLER**  
Uses digital WAV files  
in EEPROM

■■■■ PLUS

**BACK TO BASICS - 7**

Parking Radar  
Telephone Switch

[www.epemag.co.uk](http://www.epemag.co.uk)





Colour CCTV camera, 8mm lens, 12vdc200ma a 582x628 Res 380 lines Automatic aperture lens Mirror function PAL Back Light Comp MLR, 100x40x40mm ref EE2 £75.90

Built in Audio 15lux CCD camera 12vdc 200ma 480 lines s/n ratio >48 db 1v P-P output 110x60x50mm ref EE1 £108.90



Metal CCTV camera housings for internal or external use. Made from aluminium and plastic they are suitable for mounting body cameras in. Available in two sizes 1-100x70x170mm and 2-100x70x280mm Ref EE6 £22 EE7 £26 Multi position brackets Ref EE8 £8.80



Excellent quality multi purpose TV/TFT screen, works as just a LCD colour monitor with any of our CCTV cameras or as a conventional TV ideal for use in boats and caravans 49.75mhz-91.75mhz VHF channels 1-5, 168.25mhz-222.75mhz VHF channels 6-12, 471.25mhz-869.75mhz. Cable channels 112.325mhz-166.75mhz Z1-Z7, Cable channels 224.25mhz-446.75mhz Z8-Z35 5" colour screen, Audio output 150mW, Connections, external aerial, earphone jack, audio/video input, 12vdc or mains, Accessories supplied Power supply Remote control Cigar lead power supply Headphone Stand/bracket. 5" model £139 Ref EE9.



Self cocking pistol plcr002 crossbow with metal body. Selfcocking for precise string alignment Aluminium alloy construction High tec fibre glass limbs Automatic safety catch Supplied with three bolts Track style for greater accuracy Adjustable rear sight 50lb draw weight 150ft sec velocity Break action 17" string 30m range £23.84 Ref PLCR002



Fully cased IR light source suitable for CCTV applications. The unit measures 10x10x150mm, is mains operated and contains 54 infra red LEDs. Designed to mount on a standard CCTV camera bracket. The unit also contains a daylight sensor that will only activate the infra red lamp when the light level drops below a preset level. The infrared lamp is suitable for indoor or exterior use, typical useage would be to provide additional IR illumination for CCTV cameras. £53.90 ref FF11



Colour CCTV Camera measures 60x45mm and has a built in light level detector and 12 IR leds 2 lux 12 IR leds 12vdc Bracket Easy connect leads £75.90 Ref EE15



A high quality external colour CCTV camera with built in Infra red LEDs measuring 60x60x60mm Easy connect leads colour Waterproof PAL 1/4" CCD542x588 pixels 420 lines .05lux 3.6mm F2 78 deg lens 12vdc 400ma Built in light level sensor. £108.90 Ref EE13



A small colour CCTV camera just 35x28x30mm Supplied with bracket, easy connect leads. Built in audio. Colour 380 line res, PAL 0.2lux+18db sensitivity Effective pixels 628x582 6-12vdc Power 200mw £39.60 Ref EE16



Peltier module. Each module is supplied with a comprehensive 18 page Peltier design manual featuring circuit designs, design information etc etc. The Peltier manual is also available separately Maximum watts 56.2 40x40mm Imax 5.5A Vmax 16.7Tmax (c-dry N2) 72 £32.95 (inc manual) REF PELT1, just manual £4.40 ref PELT2



GASTON SEALED LEAD ACID BATTERIES 1.3AH 12V @ £5.50 GT1213 3.4AH 12V @ £8.80 GT1234 7AH 12V @ £8.80 GT127 17AH 12V @ £19.80 GT1217

3km Long range video and audio link complete with transmitter, receiver, 12.5m cables with pre fitted connectors and aerials. Achieve up to 3km. Cameras not included Ideal for stables, remote buildings etc. Mains power required £299



Complete wireless CCTV system with video. Kit comprises pinhole colour camera with simple battery connection and a receiver with video output. 380 lines colour 2.4ghz 3lux6-12vdc manual tuning. Available in two versions, pinhole and standard. £79 (pinhole) Ref EE17, £86.90 (standard) Ref EE18



All new and boxed, bargain prices. Good quality sealed lead acid batteries



1.2ghz wireless receiver Full cased audio and video 1.2ghz wireless receiver 190x140x30mm, metal case, 4 channel, 12vdc Adjustable time delay, 4s, 8s, 12s. 16s. £49.50 Ref EE20

The smallest PMR446 radios currently available (54x87x37mm). These tiny handheld PMR radios look great, user friendly & packed with features including VOX, Scan & Dual Watch. Priced at £59.99 PER PAIR they are excellent value for money. Our new favourite PMR radios! Standby: - 35 hours Includes: - 2 x Radios, 2 x Belt Clips & 2 x Carry Strap £59.95 Ref ALAN1 Or supplied with 2 sets of rechargeable batteries and two mains chargers £93.49 Ref Alan2

The TENS mini Microprocessors offer six types of automatic programme for shoulder pain, back/neck pain, aching joints, Rheumatic pain, migraines headaches, sports injuries, period pain. In fact all over body treatment. Will not interfere with existing medication. Not suitable for anyone with a heart pacemaker. Batteries supplied. £21.95 Ref TEN327 Spare pack of electrodes £6.59 Ref TEN327X

Dummy CCTV cameras These motorised cameras will work either on 2 AA batteries or with a standard DC adapter (not supplied) They have a built in movement detector that will activate the camera if movement is detected causing the camera to 'pan' Good deterrent. Camera measures 20cm high, supplied with fixing screws. Camera also has a flashing red led. £10.95 Ref CAMERAB

INFRA RED FILM 6" square piece of flexible infra red film that will only allow IR light through Perfect for converting ordinary torches, lights, headlights etc to infrared output using standard light bulbs Easily cut to shape. 6" square £16.50 ref IRF2 or a 12" sq for £34.07 IRF2A

THE TIDE CLOCK These clocks indicate the state of the tide, Most areas in the world have two high tides and two low tides a day, so the tide clock has been specially designed to rotate twice each lunar day (every 12 hours and 25 minutes) giving you a quick and easy indication of high and low water. The Quartz tide clock will always stay calibrated to the moon. £23.10 REF TIDECL

LINEAR ACTUATORS 12-36VDC BUILT IN ADJUSTABLE LIMIT SWITCHES POWDER COATED 18" THROW UP TO 1,000 LB THRUST (400LB RECOMMENDED LOAD) SUPPLIED WITH MOUNTING BRACKETS DESIGNED FOR OUTDOOR USE These brackets originally made for moving very large satellite dishes are possibly more suitable for closing gates, mechanical machinery, robot wars etc. Our first sale was to a company building solar panels that track the sun! Two sizes available, 12" and 18" throw. £32.95 REF ACT12.

Samarium magnets are 57mm x 20mm and have a hole (5/16th UNF) in the centre and a magnetic strength of 2.2 gauss. We have tested these on a steel beam running through the offices and found that they will take more than 170lbs (77kgs) in weight before being pulled off. With keeper. £21.95 REF MAG77

New transmitter, receiver and camera kit. £69.00 Kit contains four channel switchable camera with built in audio, six IR leds and transmitter, four channel switchable receiver, 2 power supplies, cables, connectors and mounting bracket. £69.00 Wireless Transmitter Black and white camera (75x50x55mm) Built in 4 channel transmitter (switchable) Audio built in 6 IR Leds Bracket/stand Power supply 30 m range Wireless Receiver 4 channel (switchable) Audio/video leads and scart adapter Power supply and Manual £69.00 ref COP24

This miniature Stirling Cycle Engine measures 7" x 4-1/4" and comes complete with built-in alcohol burner. Red flywheel and chassis mounted on a green base, these all-metal beauties silently running at speeds in excess of 1,000 RPM attract attention and create awe wherever displayed. This model comes completely assembled and ready to run. £106.70 REF SOL1

High-power modules using 125mm square multi-crystal silicon solar cells with bypass diode Anti reflection coating and BSF structure to improve cell conversion efficiency: 14%. Using white tempered glass, EVA resin, and a weatherproof film along with an aluminum frame for extended outdoor use. system Lead wire with waterproof connector. 80 watt 12v 500x1200 £315.17, 123w 12vdc 1499x662x46 £482.90 165 w 24v 1575x826x46mm £652.30

**BULL GROUP LTD**  
UNIT D HENFIELD BUSINESS PARK  
HENFIELD SUSSEX BN5 9SL  
TERMS: CASH, PO, CHEQUE PRICES+VAT  
WITH ORDER PLUS £5.50 P&P (UK) PLUS VAT.  
24 HOUR SERVICE £7.50 (UK) PLUS VAT.  
OVERSEAS ORDERS AT COST PLUS £3.50  
Tel: 0870 7707520 Fax 01273491813  
Sales@bullnet.co.uk  
www.bullnet.co.uk



Ultra-compact, lightweight, easy to use and comfortable to hold, the new NVMT is unique for a night scope in offering a tactile, suregrip plastic body shell and, for extra protection/grip, partial rubber armouring. Currently the top of the range model, the NVMT G2+ features a 'commercial grade' Gen 2+ Image Intensifier Tube (IIT). The NVMT has a built-in, powerful Infrared (IR) illuminator for use in very low light/total darkness. Power for the scope and IR is provided by 1 x 3V Lithium CR123A battery (not supplied). A green LED next to the viewfinder indicates when the Image Intensifier Tube is switched on while a red LED indicates when the IR illuminator is switched on. Type Gen Weight Size Lens Mag 2x, Weight 400g, 125x82x35mm angle of view 30 deg, built in infra red, rang 3 - 400m, supplied with batteries £849 ref COB24023.

55 - 200 WATT INFRA RED TORCHES Search guard 1 infrared torch Plastic bodied waterproof infrared rechargeable lamp. 100mm diameter lens, 200mm body length, 55 watt bulb, 1,000,000 candle power (used as an indication of relative power) Supplied complete with a 12v car lighter socket lead/charger and a 240v mains plug in charger. £49 REF square 1. Also available, 70watt @ £59, 100watt @ £79, 200watt @ £99.



B2 AIR RIFLE Available in .177 and .22" 19" Tapered Rifled Barrel Adjustable Rear Sight Full Length Wooden Stock Overall Length 43" approx Barrel Locking Lever • Also available in CARBINE Grooved for Telescopic Sight model with 14" barrel - no front sight for use with scope. Weight approximately 6lbs Extremely Powerful 22 £28.90, .177 £24.70, pellets (500) £2.55, sights 4x20 £6.80, 4x28 £15.32 Other models available up to £250 www.airpistol.co.uk

12V SOLAR PANELS AND REGULATORS 9WATT £58.75 15WATT £84.25 22WATT £126.70 Regulator up to 60 watt £21.25 Regulators up to 135 watt £38.25

The combination of multi-crystal cells and a high-reliability module structure make this series of solar panels the ideal solar module. For large-scale power generation hundreds or even thousands of modules can be connected in series to meet the desired electric power requirements. They have a high output, and highly efficient, extremely reliable and designed for ease of maintenance. Separate positive negative junction boxes and dual-by-pass diodes are a few examples of some of its outstanding features. Supplied with an 8 metre cable. Perfect for caravans, boats, etc. Toughened glass.






This set is deluxe in every way! It includes a nice assortment of balls, rakes, hooks, diamonds, two double ended picks, a broken key extractor, and three tension wrenches. And just how do you top off a set like this? Package it in a top grain leather zippered case. Part: LP005 - Price £45.00 This 32 piece set includes a variety of hooks, rakes, diamonds, balls, extractors, tension tools ... and comes housed in a zippered top grain leather case. If you like choices, go for this one! Part: LP006 - Price £65.00 If you want run toward the biggest pick set you can find, here it is. This sixty piece set includes an array of hooks, rakes, diamonds, balls, broken key extractors, tension wrenches, and even includes a warded pick set! And the zippered case is made, of course, of the finest top grain leather. First Class! Part: LP007 - Price £99.00

Mamod steam roller, supplied with fuel and everything you need (apart from water and a match!) £85 REF 1312 more models at www.mamodspares.co.uk

Mamod steam roller, supplied with fuel and everything you need (apart from water and a match!) £130 REF 1318 more models at www.mamodspares.co.uk

PEANUT RIDER STIRLING ENGINE This all metal, black and brass engine with red flywheel is mounted on a solid hardwood platform. comes complete with an alcohol fuel cell, extra wick, allen wrenches, and Owner's Manual. Specifications: Base is 5-1/4" x 5-1/4", 4" width x 9" height, 3/4" stroke, 3-1/2" flywheel £141.90

SHOP ONLINE  
WWW.BULLNET.CO.UK

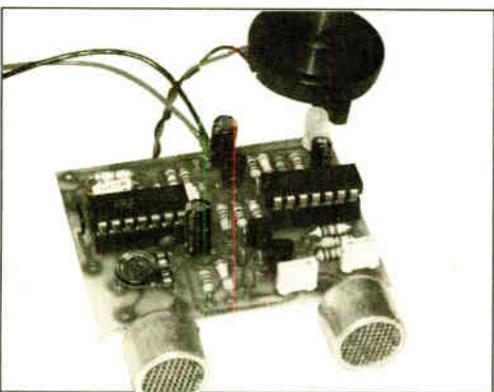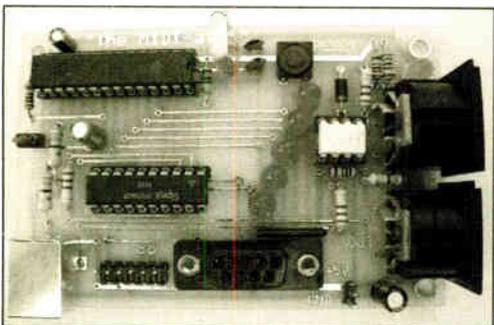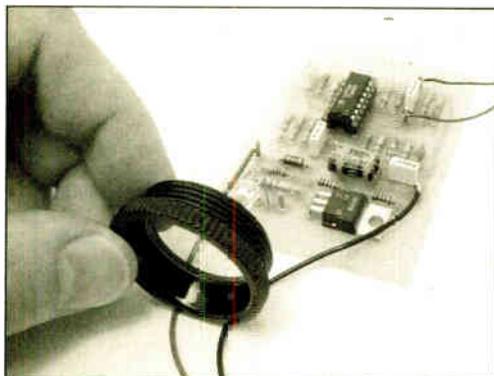

© Wimborne Publishing Ltd 2005. Copyright in all drawings, photographs and articles published in **EVERYDAY PRACTICAL ELECTRONICS** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our November 2005 issue will be published on Thursday, 13 October 2005. See page 667 for details

## Projects and Circuits

- HALLOWEEN HOWLER** by Mike Hibbett **676**  
Fun project; the sound comes from WAV files stored in EEPROM
- PIC-BASED USB INTERFACE** by Robert Lang **686**  
USB the easy way with a PIC18F2455 microcontroller
- INGENUITY UNLIMITED - Sharing your Ideas with others** **698**  
Cybervox Light Interface; Theremin Volume Control; Voltage Splitter; Pulsed Motor Speed Controller
- PHOTIC PHONE** by Thomas Scarborough **708**  
Communicate digitally over a light beam
- BACK TO BASICS - 7 Parking Radar and Telephone Switcher** **720**  
by Bart Trepak  
Simple, easy-to-build circuits based on one or two CMOS logic chips

## Series and Features


- TECHNO TALK** by Mark Nelson **684**  
The foggy history of electronic development
- INTRODUCING THE VIRTUAL DIY CALCULATOR** **694**  
by Clive "Max" Maxfield & Alvin Brown  
Learn how computers do maths without making your brain ache!
- NET WORK - THE INTERNET PAGE** surfed by Alan Winstanley **702**  
Dealing with spyware
- PIC N' MIX** by John Becker **703**  
More on getting a DS1267 dual digital potentiometer working with a PIC
- INTERFACE** by Robert Penfold **714**  
Using a D/A converter in a transistor tester
- CIRCUIT SURGERY** by Ian Bell **726**  
Chopper op.amp i.c.s

## Regulars and Services

- PIC PROJECTS CD-ROM** **670**  
20 "hand PICKed" PIC projects
- EDITORIAL** **675**
- SHOPTALK** with David Barrington **680**  
The *essential* guide to component buying for *EPE* projects
- NEWS** - Barry Fox highlights technology's leading edge **682**  
Plus everyday news from the world of electronics
- BACK ISSUES** Did you miss these? **706**
- SUBSCRIBE TO *EPE*** And save money **716**
- CD-ROMS FOR ELECTRONICS** **717**  
A wide range of CD-ROMs for hobbyists, students and engineers
- DIRECT BOOK SERVICE** **728**  
A wide range of technical books available by mail order, plus more CD-ROMs
- READOUT** John Becker addresses general points arising **731**
- PRINTED CIRCUIT BOARD SERVICE** **733**  
PCBs for *EPE* projects
- ELECTRONICS MANUALS** **734**  
CD-ROM reference works for hobbyists, student and service engineers
- ADVERTISERS INDEX** **736**

**Readers Services • Editorial and Advertisement Departments 675**

# Learn About Microcontrollers

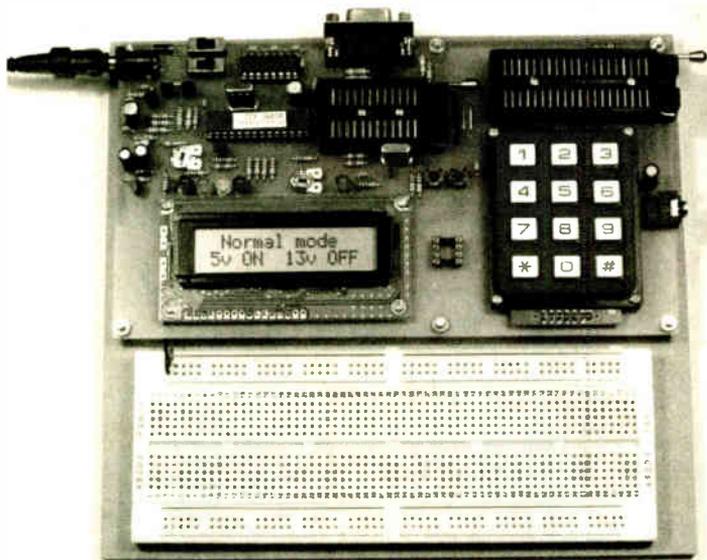

## PIC Training & Development System

The best place to start learning about microcontrollers is the PIC16F84 with its simple easy to understand internal structure. Then continue on using the more sophisticated PIC16F877 family.

At the heart of our system are two real books which lie open on your desk while you use your computer to type in the programme and control the hardware. Start with four simple programmes. Run the simulator to see how they work. Test them with real hardware. Follow on with a little theory....

Our PIC training course consists of our mid range PIC programmer, a 298 page book teaching the fundamentals of PIC programming in assembly language, a 274 page book introducing the C programming language for PICs, and a suite of programmes to run on a PC. The module is an advanced design using a 28 pin PIC16F870 to handle the timing, programming and voltage switching requirements. Two ZIF sockets and an 8 pin socket allow most mid range 8, 18, 28 and 40 pin PICs to be programmed. The plugboard is wired with a 5 volt supply. The programming is performed at 5 volts, verified with 2 volts or 3 volts applied and verified again with 5.5 volts applied to ensure that the PIC is programmed correctly over its full operating voltage. UK orders include a plugtop power supply.

- Universal mid range PIC programmer module
  - + Book *Experimenting with PIC Microcontrollers*
  - + Book *Experimenting with PIC C*
  - + PIC assembler and C compiler software suite
  - + PIC16F84 and PIC16F870 test PICs. . . . . £159.00
- (Postage & insurance UK £10, Europe £15, Rest of world £25)

## Which Language to Learn

Everyone should start programming PICs using assembly language. That is the only way to fully understand what happens. Then there are good arguments in some applications to change over to using a high level language, but, BASIC or C? At the beginning BASIC is easy to learn while C can seem very strange, but the weakness of BASIC comes from its ease of use, while the power of C lurks in its strangeness. Once the early stages are past programmes are easier to write in C than in BASIC.

## Experimenting with PIC Microcontrollers

This book introduces PIC assembly language programming using the PIC16F84, and is the best way to get started for anyone who is new to PIC programming. We begin with four easy experiments, the first of which is explained over ten and a half pages assuming no starting knowledge of PICs. Then having gained some practical experience we study the basic principles of PIC programming, learn about the 8 bit timer, how to drive the liquid crystal display, create a real time clock, experiment with the watchdog timer, sleep mode, beeps and music, including a rendition of Beethoven's *Fur Elise*. Finally there are two projects to work through, using the PIC16F84 as a sinewave generator and investigating using the PIC16F88 (from the PIC16F877 family) to monitor the power taken by domestic appliances. In the space of 24 experiments, two projects and 56 exercises the book works through from absolute beginner to experienced engineer level.

Web site:- [www.brunningsoftware.co.uk](http://www.brunningsoftware.co.uk)

Mail order address:

**Brunning Software** 138 The Street, Little Clacton, Clacton-on-sea, Essex, CO16 9LS. Tel 01255 862308

## PIC C Language

The second book *Experimenting with PIC C* starts with an easy to understand explanation of how to write simple PIC programmes in C. The first few programmes are written for a PIC16F84 to keep continuity with the first book *Experimenting with PIC Microcontrollers*. Then we see how to use the same C programmes with the PIC16F627 and the PIC16F877 family.

We study how to create programme loops using C, we experiment with the IF statement, use the 8 bit and 16 bit timers, write text, integer and floating point variables to the liquid crystal display, and use the keypad to enter numbers.

Then its time for 25 pages of pure study, which takes us much deeper into C than is directly useful with PICs as we know them - we are studying for the future as well as the present. We are not expected to understand everything that is presented in these 25 pages, the idea is to begin the learning curve for a deep understanding of C.

In chapter 9 we use C to programme the PIC to produce a siren sound and in the following chapter we create the circuit and software for a freezer thaw warning device. Through the last four chapters we experiment with using the PIC to measure temperature, create a torch light with white LEDs, control the speed of one then two motors, study how to use a PIC to switch mains voltages, and finally experiment with serial communication using the PIC's USART.


Some of the programmes towards the end of *Experimenting with PIC C* are shown in assembler and C to enable the process to be fully explained, and in the torch light experiments, due to the fast switching speed, the programmes are written only in assembler.

As you work through this book you will be pleasantly surprised how C makes light work of calculations and how easy it is to display the answers.
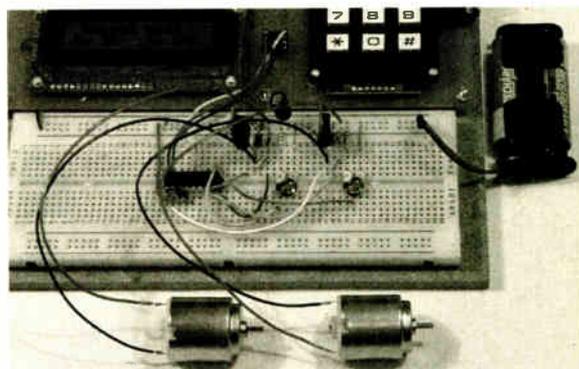
## Ordering Information

The programmer module connects to the serial port of your PC (COM1 or COM2). All our software referred to in this advertisement will operate within Windows 98, XP, NT, 2000 etc.

Telephone with Visa, Mastercard or Switch, or send cheque/PO. All prices include VAT if applicable.



## White LED and Motors

Our PIC training system uses a very practical approach. Towards the end of the second book circuits need to be built on the plugboard. The 5 volt supply which is already wired to the plugboard has a current limit setting which ensures that even the most severe wiring errors will not be a fire hazard and are very unlikely to damage PICs or other ICs.

We use a PIC16F627 as a freezer thaw monitor, as a step up switching regulator to drive 3 ultra bright white LEDs, and to control the speed of a DC motor with maximum torque still available. A kit of parts can be purchased (£30) to build the circuits using the white LEDs and the two motors. See our web site for details.

# NEXT MONTH

## TEACH-IN 2006

Are you starting electronics for the first time? Or perhaps you are a little more experienced but have missed out on some aspects of electronics? Do you wonder about how circuits work and what really goes on inside them? Do you want to be able to design and build your own circuits and get them to work first time? Are you a student or thinking about gaining a formal qualification in electronics? If the answer to any one or more of these questions is "yes" then our Teach-In 2006 series is going to be just right for you!

We won't assume that you have any previous knowledge, and while we will include the relevant theory, we won't bore you with a lot of mathematics. Each part includes a number of Practical Investigations providing you with an opportunity to prove why real circuits work. And with each part there will be a short multiple choice Quiz on-line for you to enter.

A Final Test will also be available on-line, successful completion of which will lead to the award of a personalised EPE Teach-In Certificate, something that will provide you with lasting formal recognition of your success.

### List of Topics

- Units, Multiples and Sub-multiples. Atoms, Electrons and Electric Current. Periodic Table. Introducing Resistors, Batteries, Switches. Current, Voltage and Resistance. Potential Difference. Ohm's Law.
- Circuit Diagrams. Series and Parallel Circuits. Circuit Construction Techniques. Basic Measurements – The Multimeter. More Circuit Theory. Power and Energy. Voltage Divider. Current Divider.
- Charge and Capacitance. Introducing Capacitors and Inductors. Magnetism and Inductance.
- Introducing Transformers and Semiconductors. Diodes. Rectifiers. Power Supplies.
- Introducing Transistors. Basic Concepts of Amplifiers. Gain and Frequency Response. Single and Multi-stage Amplifiers. Coupling.
- Test and Measurement. Waveforms. The Oscilloscope. Signal Sources and Signal Generators. Optoelectronics. Introducing Light Emitting Diodes.
- Digital Electronics. Introducing Logic Circuits.
- Introducing Microprocessors and PICs. Programming. Interfacing. Typical Applications.
- Analogue Electronics. Introducing Operational Amplifiers. Inverting, Non-inverting and Differential Amplifiers. Filters. Comparators. Typical Applications.
- Radio and Communications. Tuned Circuits. Modulation and Demodulation. Transmitters and Receivers. Aerials. Introducing Quartz Crystals. Typical Applications. Radio Constructional Project.



## CAMERA WATCH MK2

The publication of the first EPE Speed Camera Watch project in Jan '05 generated a lot of interest and many suggestions for enhancements. Camera Watch Mk2 addresses those suggestions.

It uses GPS signals to locate speed cameras. It can store up to 10,000 camera positions and can scan them all within one second. An I.C.D. provides the visual feedback and enables the display of additional GPS related information.

As requested, an RS232 PC interface has been added. The unit's database can now be extracted, uploaded to the internet and shared with other users.

You can also download other user's databases and merge them with your own. A special web site has been set up for this option.

Significantly, too, the ability to set an acoustic warning for exceeding preset speeds (30, 40, 50, 60 and 70 mph) has also been added.

## PIC CHROMATONE

You've all experienced Sound-to-Light displays – haven't you – discos, parties, raves, etc? But what about Light-to-Sound? Bet that's probably a new one to you – but not any longer if you read next month's light-controlled musical novelty!

Light-to-sound? Well it's just a matter of turning thoughts on their head a bit. Given the infinite variety of colour tones around us, all we do is to electronically sense what colours they are and produce frequency tones specific to them.

It must be said, though, the resulting design is a gimmick. But it's a fun gimmick, and should provide much musical entertainment!

**DON'T MISS AN  
ISSUE – PLACE YOUR  
ORDER NOW!**

see page 727

Or take out a subscription and save money.

see page 716

**EVERYDAY  
PRACTICAL  
ELECTRONICS**

**NOVEMBER 2005 ISSUE ON SALE THURSDAY, OCTOBER 13**



**Quasar Electronics Limited**  
 PO Box 6935, Bishops Stortford,  
 CM23 4WP  
 Tel: 0870 246 1826  
 Fax: 0870 460 1045  
 E-mail: sales@quasarelectronics.com

**Postage & Packing Options** (Up to 2kg gross weight): UK standard 3-7 Day Delivery – £3.95; UK Mainland Next Day Delivery – £8.95; Europe (EU) – £6.95; Rest of World – £9.95 | Order online for reduced price UK Postage!  
 We accept all major credit/debit cards. Make cheques/POs payable to Quasar Electronics Limited.  
 Prices include 17.5% VAT. MAIL ORDER ONLY.  
 Call now for our FREE CATALOGUE with details of over 300 high quality kits, projects, modules and publications.



# QUASAR **0871** CREDIT CARD **717 7168** electronics SALES

Helping you make the right connections!

## PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

### Programmer Accessories:

- 40-pin Wide ZIF socket (ZIF40W) £15.00
- 18VDC Power supply (PSU010) £19.95
- Leads: Parallel (LDC136) £4.95 / Serial (LDC441) £4.95 / USB (LDC644) £2.95

### NEW! USB 'Flash' PIC Programmer


USB PIC programmer for most 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows Software. ZIF Socket and USB Plug A-B lead not incl.



Kit Order Code: 3128KT – £34.95  
 Assembled Order Code: AS3128 – £39.95
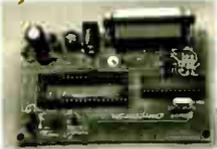
### "PICALL" ISP PIC Programmer

"PICALL" will program virtually all 8 to 40 pin serial-mode AND parallel-mode (PIC16C5x family)\* Programmed PIC micro controllers. Free fully functional software. Blank chip auto detect for super fast bulk programming. Parallel port connection. Supply: 16-18V dc.  
 Assembled Order Code: AS3117 – £24.95



### ATMEL 89xxx Programmer

Uses serial port and any standard terminal comms program. 4 LEDs display the status. ZIF sockets not included. Supply: 16VDC.



Kit Order Code: 3123KT – £29.95


### NEW! USB & Serial Port PIC Programmer

USB/Serial connection. Header cable for ICSP. Free Windows software. See website for PICs supported. ZIF Socket and USB Plug A-B lead extra. 18VDC.

Kit Order Code: 3149KT – £34.95  
 Assembled Order Code: AS3149 – £49.95
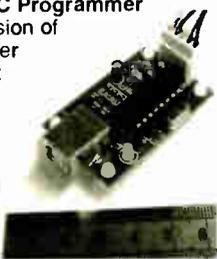
### USB Flash ICSP PIC Programmer

Fully assembled version of our 3128 USB Flasher PIC Programmer but WITHOUT the pre-programming socket. It just has 5-pin ICSP header (GND, VCC, CLK, DAT, VPP) and cable. No external PSU required. Free Windows software.



Order Code: AS3182 – £37.95

### ABC Maxi AVR Development Board

The ABC Maxi board has an open architecture design based on Atmel's AVR AT90S8535 RISC microcontroller and is ideal for developing new designs.



#### Features:

- 8Kb of In-System Programmable Flash (1000 write/erase cycles)
- 512 bytes internal SRAM
- 512 bytes EEPROM
- 8 analogue inputs (range 0-5V)
- 4 Opto-isolated Inputs (I/Os are bi-directional with internal pull-up resistors)
- Output buffers can sink 20mA current (direct i.e.d. drive)
- 4 x 12A open drain MOSFET outputs
- RS485 network connector
- 2-16 LCD Connector
- 3-5mm Speaker Phone Jack
- Supply: 9-12VDC.

The ABC Maxi STARTER PACK includes one assembled Maxi Board, parallel and serial cables, and Windows software CD-ROM featuring an Assembler, BASIC compiler and in-system programmer.

Order Code ABCMAXISP – £89.95  
 The ABC Maxi boards only can also be purchased separately at £69.95 each.

## Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU for all units: Order Code PSU445 – £8.95

### Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security.

4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 TXs can be learned by one Rx (kit includes one Tx but more available separately). 4 indicator LEDs.  
 Rx: PCB 77x85mm, 12VDC/6mA (standby).  
 Two & Ten Channel versions also available.  
 Kit Order Code: 3180KIT – £39.95  
 Assembled Order Code: AS3180 – £47.95



### Computer Temperature Data Logger

Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 38x38mm. Powered by PC. Includes one DS1820 sensor and four header cables.

Kit Order Code: 3145KT – £16.95  
 Assembled Order Code: AS3145 – £23.95  
 Additional DS1820 Sensors – £3.95 each




### NEW! DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12VDC.



Kit Order Code: 3140KT – £39.95  
 Assembled Order Code: AS3140 – £59.95

### Serial Port Isolated I/O Module

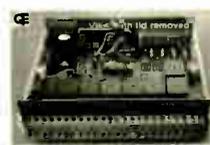

Computer controlled 8-channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch

states, etc). Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Includes plastic case 130 x 100 x 30mm. Power: 12VDC/500mA.

Kit Order Code: 3108KT – £49.95  
 Assembled Order Code: AS3108 – £59.95

### Infra-red RC 12-Channel Relay Board



Control 12 on-board relays with included infra-red remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm.

Supply: 12VDC/0.5A.  
 Kit Order Code: 3142KT – £39.95  
 Assembled Order Code: AS3142 – £49.95

### PC Data Acquisition & Control Unit

Monitor and log a mixture of analogue and digital inputs and control external devices via the analogue and digital outputs. Monitor pressure, temperature, light intensity, weight, switch state, movement, relays, etc. with the appropriate sensors (not supplied). Data can be processed, stored and the results used to control devices such as motors, sirens, relays, servo motors (up to 11) and two stepper motors.



#### Features


- 11 Analogue Inputs – 0-5V, 10 bit (5mV/step)
- 16 Digital Inputs – 20V max. Protection 1K in series, 5-1V Zener
- 1 Analogue Output – 0-2.5V or 0-10V. 8 bit (20mV/step)
- 8 Digital Outputs – Open collector, 500mA, 33V max
- Custom box (140 x 110 x 35mm) with printed front & rear panels
- Windows software utilities (3-1 to XP) and programming examples
- Supply: 12V DC (Order Code PSU203)

Kit Order Code: 3093KT – £64.95  
 Assembled Order Code: AS3093 – £94.95

Most items are available in kit form (KT suffix) or pre-assembled and ready for use (AS prefix).

**Hot New Kits This Summer!**  
Here are a few of the most recent kits added to our range. See website or join our email Newsletter for all the latest news.

**NEW! EPE Ultrasonic Wind Speed Meter**

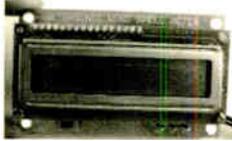


Solid-state design wind speed meter (anemometer) that uses ultrasonic techniques and has no moving parts and does not need calibrating. It is intended for sports-type activities, such as track events, sailing, hang-gliding, kites and model aircraft flying, to name but a few. It can even be used to monitor conditions in your garden. The probe is pointed in the direction from which the wind is blowing and the speed is displayed on an LCD display.

**Specifications**

- Units of display: metres per second, feet per second, kilometres per hour and miles per hour
- Resolution: Nearest tenth of a metre
- Range: Zero to 50mph approx.

Based on the project published in Everyday Practical Electronics, Jan 2003. We have made a few minor design changes (see web site for full details). Power: 9VDC (PP3 battery or Order Code PSU345). Main PCB: 50 x 83mm. Kit Order Code: 3168KT – £34.95

**NEW! Audio DTMF Decoder and Display**

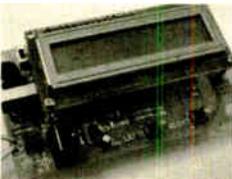

Detects DTMF tones via an on-board electret microphone or direct from the phone lines through the onboard audio transformer. The numbers are displayed on a 16-character, single line display as they are received. Up to 32 numbers can be displayed by scrolling the display left and right. There is also a serial output for sending the detected tones to a PC via the serial port. The unit will not detect numbers dialled using pulse dialling. Circuit is microcontroller based.

Supply: 9-12V DC (Order Code PSU345). Main PCB: 55 x 95mm. Kit Order Code: 3153KT – £17.95  
Assembled Order Code: AS3153 – £29.95

**NEW! EPE PIC Controlled LED Flasher**



This versatile PIC-based LED or filament bulb flasher can be used to flash from 1 to 160 LEDs. The user arranges the LEDs in any pattern they wish. The kit comes with 8 superbright red LEDs and 8 green LEDs.

Based on the Versatile PIC Flasher by Steve Challinor, EPE Magazine Dec '02. See website for full details. Board Supply: 9-12V DC. LED supply: 9-45V DC (depending on number of LED used). PCB: 43 x 54mm. Kit Order Code: 3169KT – £11.95

Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix)

**FM Bugs & Transmitters**  
Our extensive range goes from discreet surveillance bugs to powerful FM broadcast transmitters. Here are a few examples. All can be received on a standard FM radio and have adjustable transmitting frequency.

**MMTX' Micro-Miniature 9V FM Room Bug**



Our best selling bug! Good performance. Just 25 x 15mm. Sold to detective agencies worldwide. Small enough to hide just about anywhere. Operates at the 'less busy' top

end of the commercial FM waveband and also up into the more private Air band. Range: 500m. Supply: PP3 battery. Kit Order Code: 3051KT – £8.95  
Assembled Order Code: AS3051 – £14.95

**HPTX' High Power FM Room Bug**

Our most powerful room bug. Very Impressive



performance. Clear and stable output signal thanks to the extra circuitry employed. Range: 1000m @ 9V. Supply: 6-12V DC (9V PP3 battery clip supplied). 70 x 15mm. Kit Order Code: 3032KT – £9.95  
Assembled Order Code: AS3032 – £17.95

**MTTX' Miniature Telephone Transmitter**



Attach anywhere along phone line. Tune a radio into the signal and hear

exactly what both parties are saying. Transmits only when phone is used. Clear, stable signal. Powered from phone line so completely maintenance free once installed. Requires no aerial wire – uses phone line as antenna. Suitable for any phone system worldwide. Range: 300m. 20 x 45mm. Kit Order Code: 3016KT – £7.95  
Assembled Order Code: AS3016 – £13.95

**3 Watt FM Transmitter**



Small, powerful FM transmitter. Audio preamp stage and three RF stages deliver 3 watts of RF power. Can be used with the electret

microphone supplied or any line level audio source (e.g. CD or tape OUT, mixer, sound card, etc). Aerial can be an open dipole or Ground Plane. Ideal project for the novice wishing to get started in the fascinating world of FM broadcasting. 45 x 145mm. Kit Order Code: 1028KT – £23.95  
Assembled Order Code: AS1028 – £31.95

**25 Watt FM Transmitter**

Four transistor based stages with a Philips BLY89 (or equivalent) in the final stage. Delivers a mighty 25 Watts of RF power. Accepts any line level audio source (input sensitivity is adjustable). Antenna can be an open dipole, ground plane, 5/8, J, or YAGI configuration. Supply 12-14V DC, 5A. Supplied fully assembled and aligned – just connect the aerial, power and audio input. 70 x 220mm. Order Code: AS1031 – £134.95



**CREDIT CARD SALES**  
0871 717 7168

Helping you make the right connections!

**Electronic Project Labs**  
Great introduction to the world of electronics. Ideal gift for budding electronics expert!

**500-In-1 Electronic Project Lab**

This is the top of the range and is a complete electronics course taking you from beginner to 'A' level standard and beyond! It contains all the parts and instructions to assemble 500 projects. You get three comprehensive course books (total 368 pages) – *Hardware Entry Course*, *Hardware Advanced Course* and a micro-computer based *Software Programming Course*. Each book has individual circuit explanations, schematic and assembly diagrams. Suitable for age 12 and above. Order Code EPL500 – £149.95  
**30, 130, 200 and 300-in-1 project labs also available – see website for details.**



**Number 1 for Kits!**  
With over 300 projects in our range we are the UK's number 1 electronic kit specialist. Here are a few other kits from our range.

- 1046KT – 25W Stereo Car Booster £29.95
- 3087KT – 1W Stereo Amplifier £6.95
- 3105KT – 18W BTL mono Amplifier £9.95
- 3106KT – 50W Mono Hi-fi Amplifier £23.95
- 3143KT – 10W Stereo Amplifier £10.95
- 1011-12KT – Motorbike Alarm £12.95
- 1019KT – Car Alarm System £12.95
- 1048KT – Electronic Thermostat £9.95
- 1080KT – Liquid Level Sensor £6.95
- 3003KT – LED Dice £7.95
- 3006KT – LED Roulette Wheel £9.95
- 3074KT – 8-Ch PC Relay Board £24.95
- 3082KT – 2-Ch UHF Relay £30.95
- 3126KT – Sound-Activated Relay £8.95
- 3063KT – One Chip AM Radio £11.95
- 3102KT – 4-Ch Servo Motor Driver £15.95
- 3155KT – Stereo Tone Controls £11.95
- 1096KT – 3-30V, 5A Stabilised PSU £32.95
- 3029KT – Combination Lock £7.95
- 3049KT – Ultrasonic Detector £14.95
- 3130KT – Infra-red Security Beam £13.95
- SG01MKT – Train Sounds £6.95
- SG10 MKT – Animal Sounds £5.95
- 1131KT – Robot Voice Effect £9.95
- 3007KT – 3V FM Room Bug £6.95
- 3028KT – Voice-Activated FM Bug £11.95
- 3033KT – Telephone Recording Adpt £8.95
- 3112KT – PC Data Logger/Sampler £18.95
- 3118KT – 12-bit Data Acquisition Unit £49.95
- 3101KT – 20MHz Function Generator £69.95



**www.quasarelectronics.com**

Secure Online Ordering Facilities ● Full Product Listing, Descriptions & Photos ● Kit Documentation & Software Downloads

# EPE PIC PROJECTS VOLUME 1 MINI CD-ROM



**A plethora of 20 "hand-PICked" PIC Projects from selected past issues of EPE**  
Together with the PIC programming software for each project plus bonus articles

The projects are:

**PIC-Based Ultrasonic Tape Measure**

You've got it taped if you PIC this ultrasonic distance measuring calculator

**EPE Mind PICKler**

Want seven ways to relax? Try our PIC-controlled mind machine!

**PIC MIDI Sustain Pedal**

Add sustain and glissando to your MIDI line-up with this inexpensive PIC-controlled effects unit

**PIC-based MIDI Handbells**

Ring out thy bells with merry tolling – plus a MIDI PIC-up, of course!

**EPE Mood PICKer**

Oh for a good night's sleep! Insomniacs rejoice – your wakeful nights could soon be over with this mini-micro under the pillow!

**PIC Micro-Probe**

A hardware tool to help debug your PIC software

**PIC Video Cleaner**

Improving video viewing on poorly maintained TVs and VCRs

**PIC Graphics LCD Scope**

A PIC and graphics LCD signal monitor for your workshop

**PIC to Printer Interface**

How to use dot-matrix printers as data loggers with PIC microcontrollers

**PIC Polywhatsit**

A novel compendium of musical effects to delight the creative musician

**PIC Magick Musick**

Conjure music from thin air at the mere untouching gesture of a fingertip

**PIC Mini-Enigma**

Share encrypted messages with your friends — true spymaster entertainment

**PIC Virus Zapper**

Can disease be cured electronically? Investigate this controversial subject for yourself

**PIC Controlled Intruder Alarm**

A sophisticated multi-zone intruder detection system that offers a variety of monitoring facilities

**PIC Big-Digit Display**

Control the giant ex-British Rail platform clock 7-segment digits that are now available on the surplus market

**PIC Freezer Alarm**

How to prevent your food from defrosting unexpectedly

**PIC World Clock**

Graphically displays world map, calendar, clock and global time-zone data

**PICAXE Projects**

A 3-part series using PICAXE devices – PIC microcontrollers that do not need specialist knowledge or programming equipment

**PIC-based Tuning Fork and Metronome**

Thrill everyone by at long last getting your instrument properly tuned!

**Versatile PIC Flasher**

An attractive display to enhance your Christmas decorations or your child's ceiling

**ONLY  
£14.45**  
INCLUDING  
VAT and P&P

**Order on-line from**  
[www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)  
or [www.epemag.com](http://www.epemag.com) (USA \$ prices)  
or by Phone, Fax, Email or Post.

NOTE: The PDF files on this CD-ROM are suitable to use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader.

## EPE PIC PROJECTS CD-ROM ORDER FORM

Please send me ..... (quantity) EPE PIC PROJECTS VOL 1 CD-ROM

Price £14.45 each – includes postage to anywhere in the world.

Name .....

Address .....

..... Post Code .....

I enclose cheque/P.O./bank draft to the value of £ .....

Please charge my Visa/Mastercard/Amex/Diners Club/Switch

£ .....

Card No. ....

Card Security Code ..... (The last 3 digits on or just under the signature strip)

Start Date ..... Expiry Date ..... Switch Issue No. ....

**SEND TO: Everyday Practical Electronics,  
Wimborne Publishing Ltd.,**

**408 Wimborne Road East, Ferndown, Dorset BH22 9ND.**

Tel: 01202 873872. Fax: 01202 874562.

Email: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

**BECOME A PIC PROJECT BUILDER WITH THE HELP OF EPE!**

# Europe's Largest Surplus Store

20,000,000 Items on line NOW!  
New items added daily

Established for over 25 years UK company Display Electronics prides itself on offering a massive range of electronic and associated electro-mechanical equipment and parts to the Hobbyist, Educational and Industrial user. Many current and obsolete hard to get parts are available from our vast stocks, which include:

- ◆ 6,000,000 Semiconductors
- ◆ 5,000 Power Supplies
- ◆ 25,000 Electric Motors
- ◆ 10,000 Connectors
- ◆ 100,000 Relays & Contactors
- ◆ 2000 Rack Cabinets & Accessories
- ◆ 4000 Items of Test Equipment
- ◆ 5000 Hard Disk Drives

**We Ship Worldwide**

**Surplus Wanted**

**www.distel.co.uk**

Display Electronics  
29 / 35 Osborne Road  
Thornton Heath  
Surrey UK CR7 8PD

Telephone  
**[44] 020 8653 3333**  
Fax **[44] 020 8653 8888**

# Easy Components

**10% OFF**



£9.99



£4.99

Our components sets are so useful you'll wonder how you coped without! Buying a component set is simply the easiest way to keep stock of those project building essentials!

**1/2W Precision Metal Film Resistors** evenly distributed over 73 E12/E24 values from **10Ω to 10MΩ**. Pure convenience! Just **£9.99** for a set of 1040 resistors.

**Electrolytic Capacitor set? CAP-001** has 105 Grade A electrolytics, in 14 values from **0.47µF to 2200µF** (16v - 63v). Perfect for power supply / filter experiments and only **£4.99**.

But wait, there's more! **Veroboard** from **£2.99**. **100 63v Polyester Capacitors** for **£4.99**, and **SMD-001** boasts 1130 **Surface Mount Resistors** in 1206 & 0805 packages for **£12.99**.



*It's time to get smart about buying components. Visit our website or write to us and ask for a free catalogue!*

10% off for EPE readers. Codeword: **FARADAY**  
Mail order P&P: **£2.50** (Free P&P orders over **£20**)

**www.fastcomponents.co.uk**

Tel: **0870 750 4468** Fax: **0870 137 6005**  
Winchester House, Winchester Road, Walton-on-Thames, Surrey. KT12 2RH

## PLEASE ENSURE YOU TELEPHONE TO CHECK AVAILABILITY OF EQUIPMENT BEFORE ORDERING OR CALLING.

### SPECIAL OFFERS

#### OSCILLOSCOPES

|  |      |
|--|------|
| TEKTRONIX 2247A 4 Channel 100MHz Counter/Timer Voltmeter     | £275 |
| TEKTRONIX 2335 Dual Trace 100MHz Delay Sweep                 | £125 |
| TEKTRONIX 485 Dual Trace 350MHz Delay Sweep                  | £300 |
| IWATSU SS3711 4 Channel 100MHz Delay Sweep                   | £150 |
| PHILIPS 3065 2+1 Channel 100MHz Dual TB Delay - Autoset £200 | £150 |
| PHILIPS 3065 2+1 Channel 60MHz Dual TB Delay - Autoset       | £150 |
| PHILIPS PM3217 Dual Trace 50MHz Delay Sweep                  | £125 |
| KIKUSUI COS6100 5 Trace 100MHz Delay                         | £150 |
| TEKTRONIX 475A Dual Trace 250MHz Delay Sweep                 | £175 |
| TEKTRONIX 475 Dual Trace 200MHz Delay Sweep                  | £150 |
| TEKTRONIX 465B Dual Trace 100MHz Delay Sweep                 | £125 |
| TEKTRONIX 465 Dual Trace 100MHz Delay Sweep                  | £95  |
| PHILIPS PM3209 Dual Trace 40MHz Delay                        | £125 |
| PHILIPS PM3215 Dual Trace 50MHz                              | £75  |
| KENWOOD CS4035 Dual Trace 40MHz                              | £50  |
| PANASONIC VP5564A Dual Trace 40MHz                           | £50  |
| HITACHI V525 Dual Trace 50MHz Cursors                        | £95  |
| HITACHI V523 Dual Trace 50MHz Delay                          | £80  |
| HITACHI V425 Dual Trace 40MHz Cursors                        | £75  |
| HITACHI V422 Dual Trace 40MHz                                | £50  |
| HITACHI V223 Dual Trace 20MHz Delay                          | £50  |
| HITACHI V222 Dual Trace 20MHz                                | £50  |
| HITACHI V212 Dual Trace 20MHz                                | £50  |
| FARNELL DTV12-14 Dual Trace 12MHz                            | £40  |

#### STORAGE

|   |      |
|---|------|
| PHILIPS PM3320 Dual Trace 200MHz 250Ms/S                    | £300 |
| LECRYO 9400 Dual Trace 125MHz                               | £325 |
| TEKTRONIX 468 Dual Trace 100MHz Delay Sweep Digital Storage | £200 |
| VELLEMAN HP55 1MHz 5MHz Sampling Handheld Unused £60        |      |

#### ANALYSERS

|  |       |
|--|-------|
| ADVANTEST R3265A 100Hz-8GHz              | £4500 |
| TEKTRONIX 482P 50MHz-21GHz               | £2250 |
| HP8560A 50Hz-2.9GHz Beam in Tracking Gen | £2950 |
| HP 8560A 50Hz-2.9GHz                     | £2950 |
| HP 8569A 10MHz-22GHz                     | £950  |
| HP 8565A 10MHz-22GHz                     | £750  |
| HP 853A with 8559A 100kHz-21GHz          | £1100 |
| HP 182T with 8559A 100kHz-21GHz          | £750  |
| HP182T with 8558B 100kHz-1500MHz         | £600  |

|  |           |
|--|-----------|
| HP 182T with 8557A 10kHz-350MHz            | £300-£400 |
| HP 140T with 8555A 13MHz-18GHz             | £500      |
| ADVANTEST TR4131 10kHz-3.5GHz              | £350      |
| WAYNE KERR SSA1000A 150kHz-1GHz            | £950      |
| MARCONI 2382 200Hz-400MHz High Resolution  | £1250     |
| MARCONI 2370 30Hz-110MHz                   | £500      |
| HP 8754A Network Analyser 4-1300MHz        | £500      |
| MARCONI 6500A Amplitude Analyser with head | £750      |
| HP 334A Distortion Analyser 5Hz-600kHz     | £100      |

#### SIGNAL GENERATORS

|   |           |
|---|-----------|
| HP 8360B Sweeper with 83-82B 10MHz-20GHz                  | £1-400    |
| HP 8360A Sweeper with 83-82A 10MHz-20GHz                  | £1-250    |
| HP 8360B Main Frame Only                                  | £125      |
| HP 83525B RF Plug-in for 8350 0.01-8.4GHz                 | £300      |
| HP 83500A RF Plug-in for 8350 0.01-2.20GHz                | £300      |
| HP 8660C Sig Gen 1-3GHz                                   | £150      |
| HP 8660C Sig Gen 2-8GHz                                   | £150      |
| HP 8660A RF Plug-in for 8660C 1-2600MHz                   | £         |
| HP86631B Auxiliary Section for 8660C                      | £         |
| HP86632B Modulation Section for 8660C                     | £         |
| MARCONI 2017 0.01-124MHz Low Phase Noise                  | £100      |
| MARCONI 2019 Synthesised AM/FM 80kHz-1040MHz              | £325      |
| FLUKE 6060B AM/FM Syn Sig Gen 10kHz-10500MHz              | £200      |
| LEAD-5R LS2221B Sig Gen 25-950MHz                         | £400      |
| HP 8656B Synthesised 0.1-900MHz                           | £400      |
| HP 8656A Synthesised 0.1-900MHz                           | £400      |
| HP 8640A AM/FM 500kHz-512MHz                              | £150      |
| HP 8620C Sweep Osc with 86290B 2-18.6GHz                  | £200      |
| HP8620C Sweep Osc with 86222B 0.01-2.4GHz                 | £200      |
| HP8620C/B/A with any of the following plug-ins            | £150-£200 |
| HP 86220A Plug in 10-1300MHz                              |           |
| HP 86230B Plug in 1.5-4GHz                                |           |
| HP 86235A Plug in 1.7-4.3GHz                              |           |
| HP 86240A Plug in 2-8.5GHz                                |           |
| HP 86240C Plug in 3-6-8.4GHz                              |           |
| HP 86245A Plug in 5.9-12.4GHz                             |           |
| HP86250B Plug in 8-12.4GHz                                |           |
| HP 86250D Plug in 8-12.4GHz                               |           |
| HP 86260A Plug in 12.4-14GHz                              |           |
| MARCONI TF2015 AM/FM 10-520MHz                            | £95       |
| MARCONI TF2016 AM/FM 12kHz-120MHz                         | £95       |
| PHILIPS PM5328 100kHz-180MHz with 200MHz Freq Counter IEE | £225      |
| PANASONIC VP8117A AM/FM 100kHz-110MHz                     |           |
| FM 0-100kHz Digital Display etc. Unused                   | £225      |

|   |         |
|---|---------|
| HP 8165A Programmable Sigma Source 1MHz-50MHz (Pulse Function)                | £325    |
| HP 3325A Synthesised Function Gen 21MHz                                       | £350    |
| HP 3312A Function Gen 0.1Hz-13MHz AM/FM Sleep/Trip/Burst etc.                 | £200    |
| WAVETEK 21 Stabilised Function Gen 11MHz                                      | £225    |
| WAVETEK 23 Synthesised Function Gen 12MHz                                     | £275    |
| EXACT 529 AM/FM Function Gen in 20MHz   | £150    |
| ANALOGUE 2030 Synthesised Multi Function Waveform                             | £250    |
| THANDER T6563 Pulse/Function Gen 5MHz   | £195    |
| THANDER T6502 Sweep/Function Gen 5MHz   | £195    |
| KRON-HITE 5200A Sweep Func Gen 0.0003Hz-3MHz                                  | £150    |
| HP 3310B Info as 3310A + etc.   | £120    |
| HP 3310A Func. Gen 0.005Hz-5MHz Sine/Sq/Tri/Ramp/Pulse                        | £80     |
| PHILIPS PM5132 Function Gen 0.1Hz-2MHz  | £95     |
| PHILIPS PM5131 Function Gen 0.1Hz-2MHz  | £75     |
| FEEDBACK FG601 Func. Gen 0.01Hz-1MHz  | £60     |
| HP B112A Pulse Gen 50MHz  | £750    |
| HP B111A Pulse Generator 20MHz  | £400    |
| LYONS PG73N Pulse Gen 20MHz   | £50     |
| LEADER LAG120B Sine/Sq/Aux Generator 10Hz-1MHz                                | £60     |
| FARNELL LFM4 Sine/Sq Osc. 10Hz-15Hz Low Distortion TTL Output Amplitude Meter | £50     |
| GOULD J3B Sine/Sq Osc 10Hz-100kHz Low Distortion                              | £50-£75 |
| FARNELL LFI Sine/Sq Oscillator 10Hz-1MHz                                      | £50     |
| MARCONI SANDERS 4056C Signal Source 850-2000MHz                               | £125    |
| MARCONI SANDERS 4056B Signal Source 850-2150MHz                               | £125    |
| MARCONI SANDERS 4056A Signal Source 2-4GHz                                    | £125    |
| MARCONI SANDERS 4057B Signal Source 4.5-8.5GHz                                | £125    |
| MARCONI SANDERS 4059A Signal Source 12-18GHz                                  | £125    |
| MARCONI SANDERS 4070A Signal Source 400-1200MHz                               | £125    |
| FLUKE 6011A Synthesised 11MHz   | £125    |
| PHILIPS 5514A Colour Bar Generator Video                                      | £195    |
| BLACK STAR ORION Colour Bar Gen   | £50     |
| BLACK STAR ORION Later Version Metal Case                                     | £75     |

|  |      |
|--|------|
| HP 5316A Universal Counter 0-100MHz HPB            | £36  |
| THANDAR TFB10 Frequency Counter 5Hz-200MHz Battery | £60  |
| THANDAR TF200 Frequency Meter 10Hz-200MHz 8 digit  | £40  |
| BLACK STAR Meteor 100 Counter 5Hz-100MHz           | £55  |
| BLACK STAR 1325 Counter Timer 1300MHz              | £160 |
| BECKMAN UC10A Universal Counter 120MHz             | £150 |
| LEADER LDC3043 Digital Counter 100MHz              | £125 |

#### DIGITAL MULTIMETERS ETC

|  |      |
|--|------|
| SOLARTRON 7150 6 1/2 digit True RMS IEE  | £75  |
| SOLARTRON 7150 Plus As Above + Temp Measurement                                | £100 |
| DATRON 1055 5 1/2 digit Autocal AC/DC Resistance IEE                           | £95  |
| FLUKE 77 3 1/2 digit Handheld  | £35  |
| FLUKE 77 Series 2 3 1/2 digit Handheld   | £45  |
| FLUKE 8600A 4 1/2 digit True RMS Handheld                                      | £75  |
| BECKMAN HD110 3 1/2 digit Handheld in Carry Case                               | £30  |
| TTI 995A 3 1/2 digit Bench   | £80  |
| SOLARTRON 7045 4 1/2 digit Bench   | £30  |
| AVO D4116 3 1/2 digit with Batteries & Leads                                   | £20  |
| AVO 8 M6 in Ever Ready Case with Leads etc                                     | £75  |
| AVO 8 M15 with Leads etc   | £50  |
| RACAL 9300 True RMS RF Millivoltmeter  | £125 |
| RACAL 9300 True RMS Millivoltmeter 5Hz-20MHz usable to 20MHz                   | £30  |
| RACAL 9100B as 9300  | £45  |
| GOODWILL GV7427 Dual Chan AC Millivoltmeter 10mV in 12 ranges 10Hz-1MHz Unused | £75  |
| KENWOOD VT176 Dual Chan Millivoltmeter   | £40  |

#### POWER SUPPLIES

|  |      |
|--|------|
| FARNELL XA35T 0-0.35V 0-2A Two Digit                     | £95  |
| FARNELL LT30-2 0-30V 0-2A Twice                          | £110 |
| FARNELL B3020 30V 20A Variable No Meters                 | £110 |
| FARNELL B3010 30V 10A Variable No Meters                 | £55  |
| FARNELL LT30-1 0-30V 0-1A Twice                          | £75  |
| FARNELL L30-2 0-30V 0-2A                                 | £55  |
| FARNELL L30-1 0-30V 0-1A                                 | £40  |
| FARNELL L30-0 0-350V 0-200mA                             | £125 |
| FARNELL D30-2T 0-30V 0-2A Twice Digital                  | £95  |
| THURLEY PL330 0-30V 0-3A Digital (Kenwood badged)        | £75  |
| THURLEY TS30215 0-30V 0-2A LCD                           | £65  |
| THURLEY PL320 0-30V 0-2A Digital                         | £55  |
| TAKASAGO GMO35-3 0-35V 0-3A 2 Meters                     | £45  |
| TAKASAGO TMO35-3 0-35V 0-2A 2 Meters                     | £35  |
| ISOLATING TRANSFORMER - Yellow - 500VA with 13Amp Socket | £35  |

#### FREQUENCY COUNTERS/TIMERS

|   |      |
|---|------|
| EIP 371 Source Locking Microwave Counter 10Hz-18GHz | £325 |
| GIP 331 Autoneg Microwave Counter 825MHz-18GHz      | £195 |
| HP 5386A Counter 10Hz-3GHz                          | £350 |
| FEEDBACK SC2230 Counter 1.3GHz                      | £75  |
| RACAL 9915 Counter 13Hz-520MHz                      | £85  |
| RACAL 9906 Universal Counter 200MHz                 | £85  |
| RACAL 9904 Counter/Timer 50MHz                      | £50  |
| RACAL 1991 Counter/Timer 160MHz 9 digit             | £195 |
| MARCONI 2431A Frequency Meter 2GHz                  | £50  |
| MARCONI 2437 Counter/Timer 10MHz                    | £75  |
| HP 3340A Autoneg Microwave Counter 10Hz-18GHz       | £250 |

## STEWART OF READING

17A King Street, Mortimer, Near Reading RG7 3RS  
Telephone: (0118) 933 1111. Fax: (0118) 933 2375  
www.stewart-of-reading.co.uk  
Open 9am-5.00pm Monday to Friday (other times by arrangement)

Used Equipment - GUARANTEED. Manuals supplied  
This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists.  
Please check availability before ordering.  
CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage

## MAIL ORDER ONLY • CALLERS BY APPOINTMENT

### EPE PROJECT PICS

#### Programmed PICs for \*EPE Projects

12C508/9 - £3.90; 16F627/8 - £4.90

16C84/16F84/16C71 - £5.90

16F876/877 - £10.00

All inc. VAT and Postage

(\*Some projects are copyright)

### EPE MICROCONTROLLER P.I. TREASURE HUNTER

The latest MAGENTA DESIGN - highly stable & sensitive - with I.C. control of all timing functions and advanced pulse separation techniques.

- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

**KIT 847** ..... £63.95

### PIC PIPE DESCALER

- SIMPLE TO BUILD
- HIGH POWER OUTPUT
- AUDIO & VISUAL MONITORING
- SWEPT FREQUENCY

An affordable circuit which sweeps the incoming water supply with variable frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve lathering ability by altering the way salts in the water behave.

Kit includes case, P.C.B., coupling coil and all components. High coil current ensures maximum effect. L.E.D. monitor.



**KIT 868** ..... £22.95      **POWER UNIT**.....£3.99

### MICRO PEST SCARER

Our latest design - The ultimate scarer for the garden. Uses special microchip to give random delay and pulse time. Easy to build reliable circuit. Keeps pets/pests away from newly sown areas, play areas, etc. uses power source from 9 to 24 volts.

- RANDOM PULSES
- HIGH POWER
- DUAL OPTION



Plug-in power supply £4.99

**KIT 867**..... £19.99

**KIT + SLAVE UNIT**..... £32.50

### WINDICATOR

A novel wind speed indicator with LED readout. Kit comes complete with sensor cups, and weatherproof sensing head. Mains power unit £5.99 extra.

**KIT 856**..... £28.00

## ★ TENS UNIT ★

### DUAL OUTPUT TENS UNIT

As featured in March '97 issue.

Magenta have prepared a FULL KIT for this excellent new project. All components, PCB, hardware and electrodes are included. Designed for simple assembly and testing and providing high level dual output drive.

**KIT 866**.. Full kit including four electrodes £32.90

Set of 4 spare electrodes £6.50

### 1000V & 500V INSULATION TESTER



Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms.

Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

**KIT 848**..... £32.95

## EPE TEACH-IN 2000

Full set of top quality NEW components for this educational series. All parts as specified by EPE. Kit includes breadboard, wire, croc clips, pins and all components for experiments, as listed in introduction to Part 1.

\*Batteries and tools not included.

**TEACH-IN 2000** -

**KIT 879** £44.95

**MULTIMETER** £14.45

### SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube plus instructions for message loading.

**KIT 849** ..... £16.99

### 12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMs at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

**KIT 790** ..... £29.90

### SUPER BAT DETECTOR

1 WATT O/P, BUILT IN SPEAKER, COMPACT CASE 20kHz-140kHz NEW DESIGN WITH 40kHz MIC.

A new circuit using a 'full-bridge' audio amplifier i.c., internal speaker, and headphones/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.

**KIT 861** ..... £34.99

ALSO AVAILABLE Built & Tested... £48.99




### 68000 DEVELOPMENT TRAINING KIT

- NEW PCB DESIGN
- 8MHz 68000 16-BIT BUS
- MANUAL AND SOFTWARE
- 2 SERIAL PORTS
- PIT AND I/O PORT OPTIONS
- 12C PORT OPTIONS
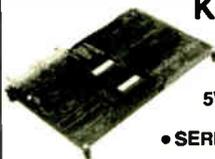
#### KIT 621

£99.95

- ON BOARD 5V REGULATOR
- PSU £6.99
- SERIAL LEAD £3.99



### Stepping Motors

MD100...Std 100 step...£9.99

MD200...200 step...£12.99

MD24...Large 200 step...£22.95



### MOSFET MkII VARIABLE BENCH POWER SUPPLY 0-25V 2.5A

Based on our Mk1 design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.



Kit No. 845 ..... £64.95

### ULTRASONIC PEST SCARER

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS



- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

**KIT 812**..... £15.00

### SIMPLE PIC PROGRAMMER

**KIT 857**... £12.99

Includes PIC16F84 chip disk, lead, plug, p.c.b., all components and instructions

Extra 16F84 chips £3.84 Power Supply £3.99

## PIC LCD DISPLAY DRIVER

16 Character x 2 Line display, pcb, programmed PIC16F84, software disk and all components to experiment with standard intelligent alphanumeric displays. Includes full PIC source code which can be changed to match your application.

**KIT 860.....£19.99**

- Learn how to drive the display and write your own code.
- Ideal development base for meters, calculators, counters, timers — just waiting for your application!
- Top quality display with industry standard driver, data and instructions

## PIC STEPPING MOTOR DRIVER

PCB with components and PIC16F84 programmed with demonstration software to drive any 4 phase unipolar motor up to 24 Volts at 1 Amp. **Kit includes 100 Step Hybrid Stepping Motor** Full software source code supplied on disc.

Use this project to develop your own applications. PCB allows 'simple PIC programmer' 'SEND' software to be used to reprogram chip.

**KIT 863.....£18.99**

## 8 CHANNEL DATA LOGGER

From Aug/Sept '99 EPE. Featuring 8 analogue inputs and serial data transfer to PC. Magenta redesigned PCB - LCD plugs directly onto board. Use as Data Logger or as a test bed for developing other PIC16F877 projects. Kit includes lcd, prog. chip, PCB, Case, all parts and 8 x 256k EEPROMs

**KIT 877.....£49.95**

## PIC16F84 MAINS POWER CONTROLLER & 4 CHANNEL LIGHT CHASER / DIMMER

- Zero Volt Switching
- Opto-Isolated 5 Amp HARD FIRED TRIACS
- 12 Way keypad Control

- With program source code disk.
- Chase Speed and dimming potentiometer controls.
- Reprogram for other applications

**KIT 855.....£39.95**

## PIC TUTOR 1 EPE MARCH APRIL MAY '98 PIC16F84 STARTER SERIES

The original PIC16F84 series by John Becker. Magenta's Tutor board has individual switches and leds on all portA and PortB lines, plus connectors for optional 4 digit seven segment led display, and 16 x 2 intelligent lcd. Written for newcomers to PICs this series. Disk has over 20 tutorial programs. Connect to a PC parallel port, send, run, and experiment by modifying test programs - *Then Write and Program your Own*

**KIT 870... £27.95, Built...£42.95**


16x2 LCD..£7.99. LED display..£6.99. 12VPSU..£3.99

## SUPER PIC PROGRAMMER

Magenta's original parallel port programmer. Runs with downloaded WINDOWS 95 - XP software. Use standard Microchip .HEX files. Read/Prog/Verify wide range of 18,28, and 40 pin PICs. Including 16F84/876/877, 627/8, (Inc. 'A' versions) + 16xx OTPs.

**KIT 862... £29.99** Power Supply £3.99

## ICEBREAKER

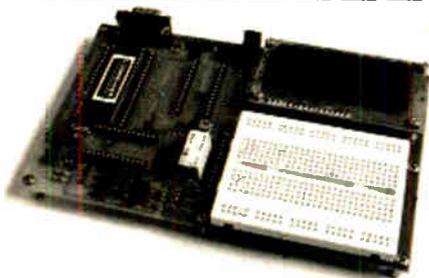

### PIC Real Time In-Circuit Emulator

- ICEbreaker uses PIC16F877 in-circuit debugger.
- Links to standard PC Serial port (lead supplied).
- Windows (95 to XP) Software included
- Works with MPASM assembler
- 16 x 2 LCD display, Breadboard, Relay, I/O devices and patch leads.

Featured in EPE Mar'00 Ideal for beginners & experienced users.

**KIT 900...£34.99** With serial lead & software disk, PCB, Breadboard, PIC16F877, LCD, all components and patch leads.  
POWER SUPPLY - £3.99 STEPPING MOTOR 100 Step £9.99

Programs can be written, downloaded, and then tested by single-stepping, running to breakpoints, or free run at up to 20Mhz.

**Full emulation means that all ports respond immediately - reading and driving external hardware.**

Features include: Run; set Breakpoint; View & change registers, EEPROM, and program memory; load program; watch window registers.

## 20W Amp. Module


EPE May '05 -- Superb Magenta Stereo/Mono Module

Wide bandwidth Low distortion 11W /channel Stereo 20W Mono True (rms) Real Power

Short Circuit & Overheat Protected. Needs 8 to 18V supply.

Stable Reliable design

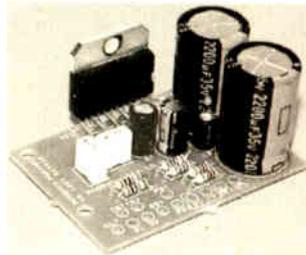
Latest Technology IC with local feedback gives very high performance.



**KIT 914** (all parts & heatsink for stereo or mono) **£11.90**
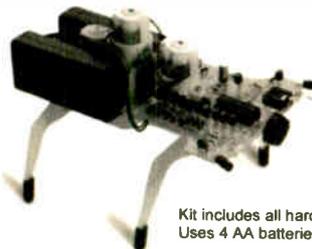
## Magenta BrainiBorg

A super walking programmable robot with eyes that sense obstacles and daylight: BrainiBorg comes with superb PC software CD (WIN95+ & XP) and can be programmed to walk and respond to light and obstacles on any smooth surface.



CD contains illustrated constructional details, operating principles, circuits and a superb Educational Programming Tutorial.

Test routines give real-time 'scope traces of sensor and motor signals. Connects to PC via SERIAL port with the lead supplied.

Kit includes all hardware, components, 3 motor/gearboxes. Uses 4 AA batteries (not supplied). An Ideal Present!

**KIT 912** Complete Kit with CD rom & serial lead **£49.99**

**KIT 913** As 912 but built & tested circuit board **£58.95**

## EPE PIC Tutorial

EPE April/May/June '03 and PIC Resources CD

- Follow John Becker's excellent PIC toolkit 3 series.
- Magenta Designed Toolkit 3 board with printed component layout, green solder mask, places for 8, 18, 28 (wide and slim), and 40 pin PICs. and Magenta extras.
- 16 x 2 LCD, PIC chip all components and sockets included.

**KIT 880** (with 16F84) **£34.99**, built & tested **£49.99**

**KIT 880** (with 16F877) **£39.99**, built & tested **£55.99**

## EPE TEACH-IN 2004

THE LATEST NOV 03 SERIES All parts to follow this new Educational Electronics Course. Inc. Breadboard, and wire, as listed on p752 Nov. Issue.

Additional Parts as listed in 'misc.' Section (less RF modules, Lock, and Motor/g.box)

Reprints: £1.00 per part.

**KIT 920.....£29.99** **KIT921.....£12.99**

## MAGENTA BRAINIBOT I & II

- Full kit with ALL hardware and electronics.
- As featured in EPE Feb '03 (KIT 910)
- Seeks light, beeps, and avoids obstacles
- Spins and reverses when "cornered"
- Uses 8 pin PIC chip
- ALSO KIT 911 - As 910 PLUS programmable from PC serial port leads and software CD included.



**KIT 910....£16.99** **KIT 911....£24.99**

# MAGENTA

All prices include VAT. Add £3.00 p&p. Next day £6.99

Tel: 01283 565435 Fax: 01283 546932 email: sales@magenta2000.co.uk

**102005**



**ESR ELECTRONIC COMPONENTS**

Station Road, Cullercoats, Tynes & Wear, NE30 4PQ

Prices Exclude Vat @17.5%. UK Carriage £2.50 (less than 1kg) £5.50 greater than 1kg. Cheques / Postal orders payable to ESR Electronic Components. PLEASE ADD CARRIAGE & VAT TO ALL ORDERS

**See Next / Last Months Ad. for COMPONENT ACCESSORIES**

|             |          |       |         |       |
|-------------|----------|-------|---------|-------|
| 4000 Series | 74HC74   | £0.19 | 74LS122 | £0.31 |
| 4000B       | 74HC75   | £0.21 | 74LS123 | £0.31 |
| 4001B       | 74HC76   | £0.20 | 74LS125 | £0.28 |
| 4002B       | 74HC85   | £0.23 | 74LS126 | £0.25 |
| 4008B       | 74HC86   | £0.22 | 74LS132 | £0.26 |
| 4009UB      | 74HC107  | £0.40 | 74LS133 | £0.36 |
| 4010B       | 74HC123  | £0.33 | 74LS136 | £0.23 |
| 4011B       | 74HC126  | £0.46 | 74LS138 | £0.26 |
| 4012B       | 74HC126  | £0.46 | 74LS145 | £0.56 |
| 4013B       | 74HC122  | £0.24 | 74LS148 | £0.44 |
| 4014B       | 74HC133  | £0.30 | 74LS151 | £0.38 |
| 4015B       | 74HC137  | £0.30 | 74LS152 | £0.36 |
| 4017B       | 74HC138  | £0.26 | 74LS153 | £0.22 |
| 4018B       | 74HC139  | £0.31 | 74LS156 | £0.27 |
| 4019B       | 74HC151  | £0.33 | 74LS157 | £0.21 |
| 4020B       | 74HC153  | £0.30 | 74LS158 | £0.21 |
| 4021B       | 74HC154  | £0.94 | 74LS160 | £0.48 |
| 4021B       | 74HC157  | £0.40 | 74LS161 | £0.44 |
| 4022B       | 74HC158  | £0.23 | 74LS163 | £0.44 |
| 4023B       | 74HC160  | £0.64 | 74LS164 | £0.48 |
| 4024B       | 74HC162  | £0.28 | 74LS165 | £0.48 |
| 4025B       | 74HC162  | £0.28 | 74LS173 | £0.24 |
| 4026B       | 74HC164  | £0.23 | 74LS174 | £0.24 |
| 4027B       | 74HC164  | £0.23 | 74LS175 | £0.30 |
| 4028B       | 74HC165  | £0.35 | 74LS190 | £0.60 |
| 4029B       | 74HC173  | £0.38 | 74LS191 | £0.27 |
| 4030B       | 74HC174  | £0.27 | 74LS192 | £0.40 |
| 4035B       | 74HC175  | £0.35 | 74LS193 | £0.43 |
| 4040B       | 74HC193  | £0.40 | 74LS195 | £0.24 |
| 4041B       | 74HC195  | £0.32 | 74LS221 | £0.41 |
| 4042B       | 74HC240  | £0.32 | 74LS240 | £0.32 |
| 4043B       | 74HC241  | £0.37 | 74LS241 | £0.32 |
| 4044B       | 74HC244  | £0.40 | 74LS243 | £0.30 |
| 4046B       | 74HC245  | £0.34 | 74LS244 | £0.38 |
| 4047B       | 74HC251  | £0.30 | 74LS245 | £0.45 |
| 4048B       | 74HC253  | £0.25 | 74LS247 | £0.97 |
| 4049B       | 74HC257  | £0.25 | 74LS251 | £0.24 |
| 4049UB      | 74HC259  | £0.29 | 74LS252 | £0.24 |
| 4050B       | 74HC273  | £0.32 | 74LS258 | £0.24 |
| 4051B       | 74HC299  | £0.61 | 74LS266 | £0.14 |
| 4052B       | 74HC365  | £0.28 | 74LS273 | £0.32 |
| 4054B       | 74HC367  | £0.38 | 74LS279 | £0.24 |
| 4055B       | 74HC368  | £0.29 | 74LS283 | £0.47 |
| 4060B       | 74HC373  | £0.35 | 74LS365 | £0.21 |
| 4063B       | 74HC374  | £0.34 | 74LS367 | £0.21 |
| 4066B       | 74HC393  | £0.52 | 74LS368 | £0.39 |
| 4067B       | 74HC393  | £0.52 | 74LS374 | £0.38 |
| 4068B       | 74HC541  | £0.25 | 74LS374 | £0.38 |
| 4069UB      | 74HC563  | £0.56 | 74LS378 | £0.62 |
| 4070B       | 74HC573  | £0.27 | 74LS390 | £0.34 |
| 4071B       | 74HC574  | £0.30 | 74LS393 | £0.33 |
| 4072B       | 74HC595  | £0.27 | 74LS395 | £0.26 |
| 4073B       | 74HC597  | £0.22 |         |       |
| 4075B       | 74HC688  | £0.46 |         |       |
| 4076B       | 74HC4002 | £0.31 |         |       |
| 4077B       | 74HC4017 | £0.36 |         |       |
| 4078B       | 74HC4020 | £0.36 |         |       |
| 4081B       | 74HC4040 | £0.36 |         |       |
| 4082B       | 74HC4049 | £0.28 |         |       |
| 4085B       | 74HC4051 | £0.30 |         |       |
| 4086B       | 74HC4052 | £0.34 |         |       |
| 4093B       | 74HC4053 | £0.34 |         |       |
| 4094B       | 74HC4060 | £0.22 |         |       |
| 4098B       | 74HC4075 | £0.22 |         |       |
| 4099B       | 74HC4078 | £0.32 |         |       |
| 4502B       | 74HC4511 | £0.64 |         |       |
| 4503B       | 74HC4514 | £0.84 |         |       |
| 4508B       | 74HC4514 | £0.84 |         |       |
| 4510B       | 74HC4538 | £0.41 |         |       |
| 4511B       | 74HC4543 | £0.90 |         |       |
| 4512B       |          |       |         |       |
| 4515B       |          |       |         |       |
| 4516B       |          |       |         |       |
| 4518B       |          |       |         |       |
| 4520B       |          |       |         |       |
| 4521B       |          |       |         |       |
| 4526B       |          |       |         |       |
| 4527B       |          |       |         |       |
| 4528B       |          |       |         |       |
| 4529B       |          |       |         |       |
| 4532B       |          |       |         |       |
| 4536B       |          |       |         |       |
| 4538B       |          |       |         |       |
| 4541B       |          |       |         |       |
| 4543B       |          |       |         |       |
| 4555B       |          |       |         |       |
| 4556B       |          |       |         |       |
| 4584B       |          |       |         |       |
| 4585B       |          |       |         |       |
| 4724B       |          |       |         |       |
| 40106B      |          |       |         |       |
| 40109B      |          |       |         |       |
| 40174B      |          |       |         |       |
| 40175B      |          |       |         |       |

|      |           |       |
|------|-----------|-------|
| 4031 | LM13700   | £0.44 |
| 4032 | LMC660CN  | £0.40 |
| 4033 | LMC6032IN | £0.28 |
| 4034 | LP311N    | £0.25 |
| 4035 | LP312N    | £0.12 |
| 4036 | LP339N    | £0.26 |
| 4037 | LT1013CN8 | £0.36 |
| 4038 | M34-1     | £0.23 |
| 4039 | M34-2     | £0.26 |
| 4040 | MAX202CPE | £0.56 |
| 4041 | MAX208CN  | £0.64 |
| 4042 | MAX220CPE | £0.29 |
| 4043 | MAX222CPE | £0.38 |
| 4044 | MAX232CPE | £0.36 |
| 4045 | MAX485CP  | £0.22 |
| 4046 | MAX485CP  | £0.28 |
| 4047 | MAX485CP  | £0.28 |
| 4048 | MAX485CP  | £0.28 |
| 4200 | MAX485CP  | £0.28 |

|      |        |       |
|------|--------|-------|
| 4201 | LM335Z | £0.19 |
| 4202 | LM339N | £0.36 |
| 4203 | LM348N | £0.36 |
| 4204 | LM352D | £1.46 |
| 4205 | LM358Z | £0.13 |
| 4206 | LM380N |       |

# EVERYDAY PRACTICAL ELECTRONICS

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

## VOL. 34 No. 10 OCTOBER 2005

### Starting Out

Teaching electronics or design and technology? A student studying electronics or design and technology? A newcomer to electronics? Generally interested in electronics and want to learn more? Like to brush up on your electronics theory? Then our new ten part *Teach-In* series is sure to be of interest to you – or someone you might know. It starts next month and you will find more details about it on page 667.

We think the on-line monthly test and end of series on-line test and certificate are a first for *EPE*. Our *Teach-In* courses are always popular and, as this one has been written by Mike Tooley, who is well known for his many books and articles and who edited our *Electronics Service Manual*, it will no doubt be very well received. Mike has over 30 years experience in teaching electronics at all levels and has an easy-going writing style that helps to get the subject across in a readily understandable form.

Don't miss the start of the series next month. With cut backs by high street newsagents you may find issues are sold out quickly. We suggest you place an order with your newsagent or take out a subscription and save money – see page 716.

### Cameras Again!

Next month also sees the publication of a Mk2 *Speed Camera Watch*. The original version, published in the January issue, aroused a great deal of interest and the Mk2 version has been greatly enhanced. One of the major changes – suggested by readers – has been to add an audible speed warning. This makes it easy to keep to the speed limit without constantly checking the speedo. So when you come off the motorway into a 30mph area it will help to make sure you adjust your speed accordingly. The memory has also been enlarged to hold up to 10,000 camera or black spot coordinates so, hopefully, it will cover everywhere you want to go, and keep you within the law.



#### AVAILABILITY

Copies of *EPE* are available on subscription anywhere in the world (see opposite), from all UK newsagents (distributed by COMAG) and from the following electronic component retailers: Omni Electronics and Yebo Electronics (S. Africa). *EPE* can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased and downloaded for just \$14.99US (approx £8) per year available from [www.epemag.com](http://www.epemag.com)

#### SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £16.50, 12 months £31, two years £57; Overseas: 6 months £19.50 standard air service or £28.50 express airmail, 12 months £37 standard air service or £55 express airmail, 24 months £69 standard air service or £105 express airmail. To subscribe from the USA or Canada see the last magazine page. Online subscriptions, for downloading the magazine via the Internet, \$14.99US (approx £8) for one year available from [www.epemag.com](http://www.epemag.com). Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to *EPE* Subs. Dept., Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: [subs@epemag.wimborne.co.uk](mailto:subs@epemag.wimborne.co.uk). Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Maestro or Visa. (For past issues see the *Back Issues* page.)

#### BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £7.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Amex, Diners Club, Maestro and MasterCard accepted. Send, fax or phone your card number, card expiry date and card security code (the last 3 digits on or just under the signature strip), with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

**Editorial Offices:**  
EVERYDAY PRACTICAL ELECTRONICS EDITORIAL  
Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown,  
Dorset BH22 9ND  
Phone: (01202) 873872. Fax: (01202) 874562.

**Email:** [enquiries@epemag.wimborne.co.uk](mailto:enquiries@epemag.wimborne.co.uk)  
**Web Site:** [www.epemag.co.uk](http://www.epemag.co.uk)  
**EPE Online** (downloadable version of *EPE*): [www.epemag.com](http://www.epemag.com)  
**EPE Online Shop:** [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)  
See notes on **Readers' Technical Enquiries** below – we regret lengthy technical enquiries cannot be answered over the telephone.

**Advertisement Offices:**  
EVERYDAY PRACTICAL ELECTRONICS ADVERTISEMENTS  
408 Wimborne Road East, Ferndown, Dorset BH22 9ND  
Phone: 01202 873872 Fax: 01202 874562  
**Email:** [stewart.keam@wimborne.co.uk](mailto:stewart.keam@wimborne.co.uk)

**Editor:** MIKE KENWARD  
**Deputy Editor:** DAVID BARRINGTON  
**Technical Editor:** JOHN BECKER  
**Business Manager:** DAVID J. LEAVER  
**Subscriptions:** MARILYN GOLDBERG  
**General Manager:** FAY KEARN  
**Editorial/Admin:** (01202) 873872  
**Advertising Manager:**  
STEWART KEARN (01202) 873872  
**On-Line Editor:** ALAN WINSTANLEY  
**EPE Online** (Internet version) **Editors:**  
CLIVE (MAX) MAXFIELD and ALVIN BROWN

#### READERS' TECHNICAL ENQUIRIES

**E-mail:** [techdept@epemag.wimborne.co.uk](mailto:techdept@epemag.wimborne.co.uk)  
We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**.

#### PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. A number of projects and circuits published in *EPE* employ voltages that can be lethal. You should not build, test, modify or renovate any item of mains powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.

#### COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers (see *Shoptalk*). We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

#### ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.


#### TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.



# Halloween Howler

Mike Hibbett

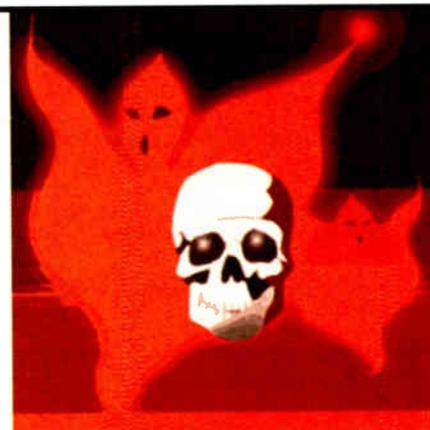

Halloween's coming – why not give your "trick or treat" visitors a scare?!

**P**ICTURE a pumpkin head, eyes lighting up red and emitting an eerie howl when someone walks past it!

Although intended to help generate a bit of fun over Halloween, this project also serves to demonstrate just how easy (and cheap) it can be to output audio in an electronics project. The sound comes from a pre-recorded computer "WAV" file stored in a small non-volatile memory. WAV files can be downloaded from the internet, extracted from music CDs and even recorded by yourself on a PC using software supplied with most operating systems.

The circuit can be configured into one of two modes of operation: Halloween Howler, which includes a light sensor to detect moving objects, and a generic three-input design that allows one of three stored sound samples to be played when an input is asserted. This second setup provides a more general purpose sound generator that can have a number of uses. Only minor component changes are required for the different setups, which are described later.

## WAV File Format

WAV files are one of the simplest formats used for storing sounds on a PC and are typically used for short sound clips. They are not a very efficient format. For example, a CD quality four minute music track requires about 42MB. An MP3 format file would require a tenth of that, but also requires complex encoding and decoding algorithms to record and play back.

A WAV file consists of a small header section which defines how the content has been recorded followed by the data itself. When a sound source is recorded, for example from the microphone on your PC, there are two factors that will determine the quality and size of the file: the number of data bits used per sample, and the rate at which samples are taken.

Values of four, eight and 16 are typical for the number bits per sample, while the sample rate varies typically from 8000 to 44000 samples per second. The sample rate determines the maximum frequency that you can record and must be at least twice that of the highest frequency to be sampled.

For reasons that will become clear later, the WAV files used in this design are encoded at 11025 samples per second, with an 8-bit resolution per sample. This provides an acceptable quality sound output without requiring enormous and expensive memory storage. WAV files are easy to create in this format on a PC, and existing higher quality sound files can be easily re-encoded to this format.

## Digital-to-Analogue Conversion

The heart of this project is the circuit which converts the digital representation of the sound, stored in the WAV file, into an analogue signal. In other words, it is a

digital-to-analogue converter (DAC). DACs are not just used for creating audio, they are used in PC video cards to create the analogue video signals, and they find many other uses in embedded control systems.

There are a number of ways to implement a DAC. Some of the more common methods that can be used in a hobby project are:

**Pulse Width Modulation:** Many microcontrollers provide an option to control a pulse-width modulated (p.w.m.) peripheral, such as a motor for example. The p.w.m. control is generally run at least three times the sample rate, and the output signal is connected to an RC (resistor/capacitor) filter to produce an averaged analogue signal. The nice feature is that it requires just a single output pin, and is a good option if you have a spare p.w.m. on your micro.

**On chip DAC:** Some high performance microcontrollers have a DAC peripheral built in, with a resolution of eight to 16 bits. These are the easiest to use.

**Dedicated DAC:** These implement all the electronics into a single chip, such as the Analog Devices DAC08 for example.

**Discrete R2R DAC:** This technique uses an array of resistors connected to a parallel port on the microcontroller. This is cheap, easy to route on a p.c.b. and very effective. It is also very easy to drive in software.

**Single bit DAC:** Uses a single output port pin to drive an RC circuit, at high speed. However, the sound file needs to be encoded in a special way and the encoder must "model" the characteristics of the RC circuit. It's quite complex and hard to understand but very easy to implement if you have a fast enough microcontroller.

**Digital Potentiometer:** These devices can readily be used as 8-bit (or greater) DACs, the "wiper" output providing an analogue voltage in respect of an input digital value.



## Chosen R2R DAC

For this project the simplest and cheapest method is used, the discrete R2R DAC. By carefully examining the I/O (input/output) port requirements (memory interface, DAC output pins, trigger input pins) a search of the Microchip database showed that the PIC16F628 was ideal for the purpose. It is small, cheap and every available pin can be used, so nothing is wasted! In the Howler there is plenty of free code space for adding extra features later on should you wish to.

The trick behind making an R2R DAC work lies in being able to drive all the output pins simultaneously. Delays in setting some outputs will result in unacceptable distortion in the audio signal. That limits the number of bits (and therefore the DAC resolution) – we can drive at most eight bits simultaneously, so eight bits it is then!

The next issue to deal with is the sample rate. CD quality audio is sampled at 44kHz: there are two problems with that rate. First we would not be able to read data from memory fast enough, and secondly we would quickly run out of storage space. The industry-standard rate of 11025Hz was chosen as a fair compromise.

As it is a standard encoding rate, so we can use existing PC tools to create our sound sources, it allows us to store almost six seconds of sound, and we can read data from a serial EEPROM (electrically erasable programmable read-only memory) at this rate. The sound's quality isn't bad either. In theory it would be possible to run at a sample rate of 22050Hz, but with just three seconds of recorded sound. Feel free to tinker!

## Circuit Description

There are two configurations that can be used for the Halloween Howler. They both use the same circuit, which is shown in Fig.1, with a few minor changes. We first describe the Halloween setup and explain the changes required for the second setup later.

The circuit is based around a PIC16F628 microcontroller, IC5, that reads a standard Windows WAV file stored in a serial EEPROM, IC2. The eight bits of data that represent each sound sample are output on PIC PORTB, to which the R2R DAC is connected.

Capacitor C4 provides some initial filtering, and as this signal is quite high impedance it is buffered by an op.amp, IC3a. Op.amp IC3b acts as both a low pass filter (C5 and R25) and attenuator to provide the correct drive to a small audio power amplifier, IC4. The low pass filter removes the high frequency artifacts caused by the signal switching at the sample rate.

The audio amplifier based around IC4 uses the device's application sheet design and produces about 350mW, more than enough to drive a small 4Ω or 8Ω loudspeaker connected to jumper connector TB8. Potentiometer VR1 provides a volume control.

Light emitting diodes D1 and D2 are standard 5mm red l.e.d.s that illuminate when the sound is triggered, simulating glowing red eyes. Any l.e.d.s will do, so

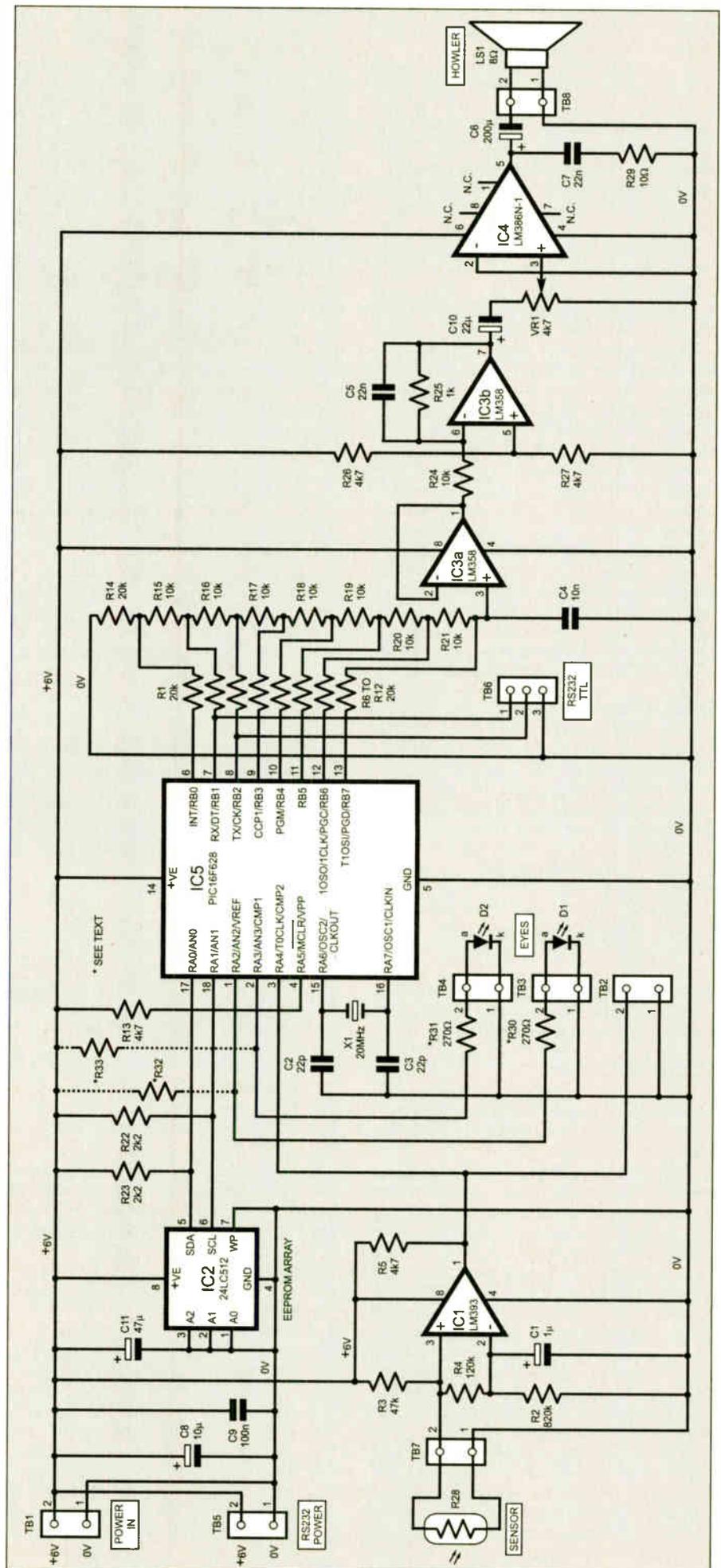


Fig.1. Complete circuit diagram for the Halloween Howler

long as the PIC's drive capability of 25mA per pin is not exceeded.

The sound output is triggered by a sudden rise in light level on a light dependent resistor (l.d.r.), R28, connected to TB7. Op.amp IC1 is configured as a comparator into which the l.d.r. is fed. Capacitor C1 and resistor R2 provide a bias to the comparator's reference input so that gradual changes in light level, such as sunrise or clouds passing over the moon, do not trigger the sound output. The sensitivity of the circuit is largely determined by resistor R4; reduce this to increase the sensitivity.

The circuit is triggered by a sudden rise in light level – the idea being that as someone approaches the pumpkin the light level falls, then as they go past, the circuit triggers. So the pumpkin wakes up behind them, adding to the scary effect!

Serial EEPROM IC2 holds the WAV file sound data, of up to 64KB, about six seconds. A PC can be connected via RS232 interface on TB5 and TB6 using a suitable level shifter circuit as shown later in Fig.3.

The serial EEPROM also holds data which defines how the p.c.b. is configured. The sound file and the configuration information are downloaded using a simple PC program, *dlwav.exe*.

The board is powered at 6V, supplied by four 1.5V batteries connected via TB1.

## Alternative Setup

The PIC software supports a second mode of operation, using three input signals to trigger one of three stored WAV files. In this configuration the light detection circuitry and l.e.d.s D1 and D2 are removed (but not their jumper headers, TB7, TB3 and TB4, respectively).

Other circuit changes are:

R30, R31 replaced by wire links  
R32, R33 values changed to 4k7  
IC1, R2, R3, R4, C1 not fitted

The three new trigger inputs are connected to TB2, TB3 and TB4. A low level input will trigger the sound.

## Construction


Printed circuit board component and track layout details are shown in Fig.2. This board is available from the *EPE PCB Service*, code 535.

Solder the two wire links first, then i.c. sockets and jumper header pins (terminal pins may be used instead of the latter), followed by the remaining components. Before fitting the i.c.s, apply power and check that the (nominally) 6V supply voltage is reaching the correct i.c. socket pins. Remove power and fit the i.c.s, observing normal static precautions when handling them.

Wire up l.e.d.s D1 and D2 via TB3 and TB4, connect a speaker via TB8 and connect the light sensor l.d.r. to TB7. The l.d.r. is not polarity sensitive and can be fitted either way round.

If you are programming your own PIC it must be programmed with the Osc HS, power-up timer and watchdog options enabled in the Config bits.

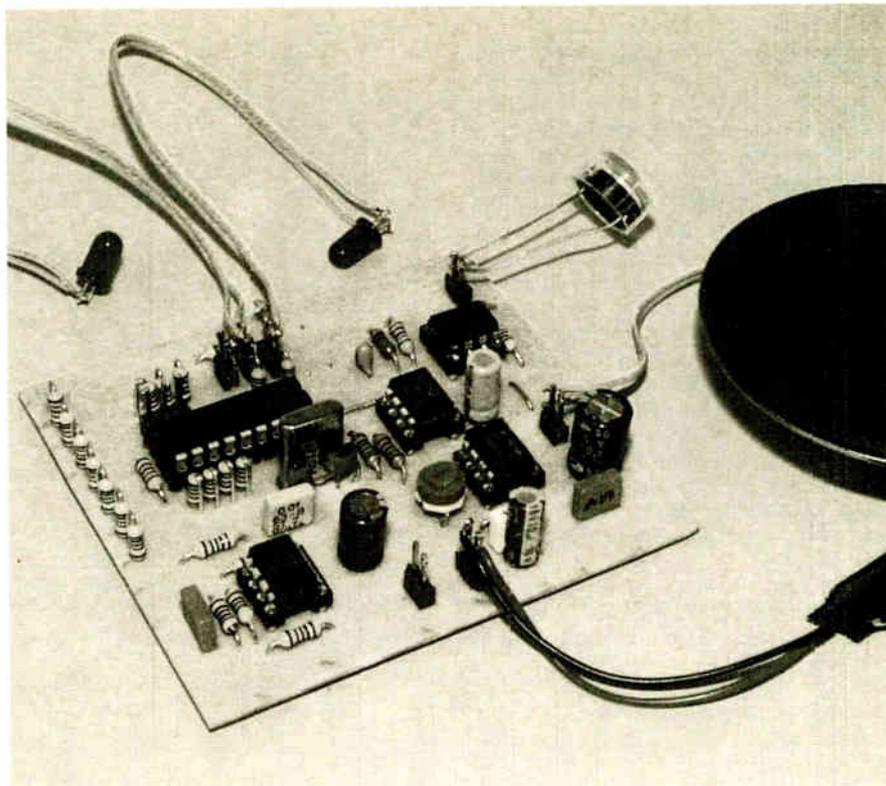Download your WAV file to the board, then power the board up again. Quickly move your hand over the l.d.r.; The "eyes" l.e.d.s will illuminate while the sound is



Finished prototype with the off-board components attached ready for the pumpkin

## COMPONENTS

Approx. Cost  
Guidance Only

£20

excl speaker, batts & interface

### Resistors

|                    |                                      |                      |
|--------------------|--------------------------------------|----------------------|
| R1, R6 to R12, R14 | 20k 1% (11 off)                      |                      |
| R2                 | 820k                                 | <b>See SHOP TALK</b> |
| R3                 | 47k                                  |                      |
| R4                 | 120k                                 |                      |
| R5, R13, R26, R27  | 4k7 (4 off)                          |                      |
| R15 to R21, R24    | 10k 1% (8 off)                       |                      |
| R22, R23           | 2k2 (2 off)                          |                      |
| R25                | 1k                                   |                      |
| R28                | ORP12 l.d.r.                         |                      |
| R29                | 10Ω                                  |                      |
| R30, R31           | 270Ω see text (2 off)                |                      |
| R32, R33           | 4k7 or not fitted (see text) (2 off) |                      |

All 0.25W 5% carbon film unless stated

### Potentiometer

|     |                 |
|-----|-----------------|
| VR1 | 4k7 min. preset |
|-----|-----------------|

### Capacitors

|        |                                       |
|--------|---------------------------------------|
| C1     | 1μ radial elect. 25V                  |
| C2, C3 | 22p ceramic disc, 2.5mm pitch (2 off) |
| C4     | 10n ceramic disc, 5mm pitch           |
| C5, C7 | 22n ceramic disc, 5mm pitch (2 off)   |
| C6     | 220μ radial elect. 16V                |
| C8     | 10μ radial elect. 16V                 |
| C9     | 100n ceramic disc, 5mm pitch          |
| C10    | 22μ radial elect. 63V                 |

|            |  |
|------------|--|
| C11        | 47μ radial elect. 10V                              |
| C12 to C16 | 1μ radial elect. 25V (optional – see text) (5 off) |

### Semiconductors

|        |   |
|--------|---|
| D1, D2 | 5mm red l.e.d., (2 off)                                 |
| IC1    | LM393 dual op.amp                                       |
| IC2    | 24LC512 serial EEPROM                                   |
| IC3    | LM358 dual op.amp                                       |
| IC4    | LM386N-1 audio power amp                                |
| IC5    | PIC16F628-20 microcontroller, pre-programmed (see text) |
| IC6    | MAX232 RS232 converter (optional – see text)            |

### Miscellaneous

|             |  |
|-------------|--|
| TB1 to TB10 | jumper header or 1mm terminal pins (see text)        |
| SK1         | 9-pin D-type connector, female (optional - see text) |
| LS1         | 8Ω min. speaker                                      |
| X1          | 20MHz Crystal  |

Printed circuit board, available from the *EPE PCB Service*, code 535; 8-pin d.i.l. socket (4 off); 16-pin d.i.l. socket (see text); 18-pin d.i.l. socket; strip-board (optional – see text); pumpkin!; connecting, solder, etc.

being played. Adjust volume potentiometer VR1 for an appropriate sound level.



You can download WAV files to the board any number of times; The EEPROM can be written to over 100,000 times so you are unlikely to wear it out!

## Pumpkin Head

Once you are happy with the setup you can install it into a pumpkin. It's best to place the p.c.b. and speaker inside a sealed plastic bag since the inside of a pumpkin remains damp for many weeks.

Position the light sensing l.d.r. in the "mouth" and the l.e.d.s close to the holes cut for the "eyes". Covering the eye holes with red crepe paper helps to diffuse the light and adds to the scary effect.

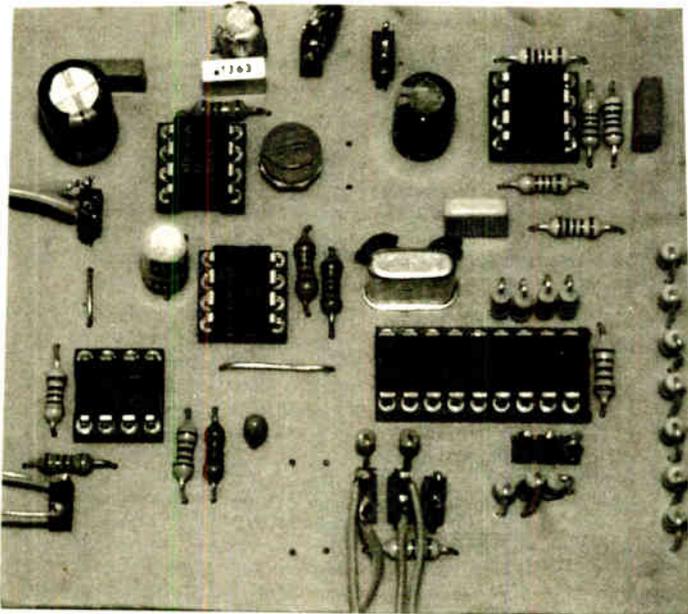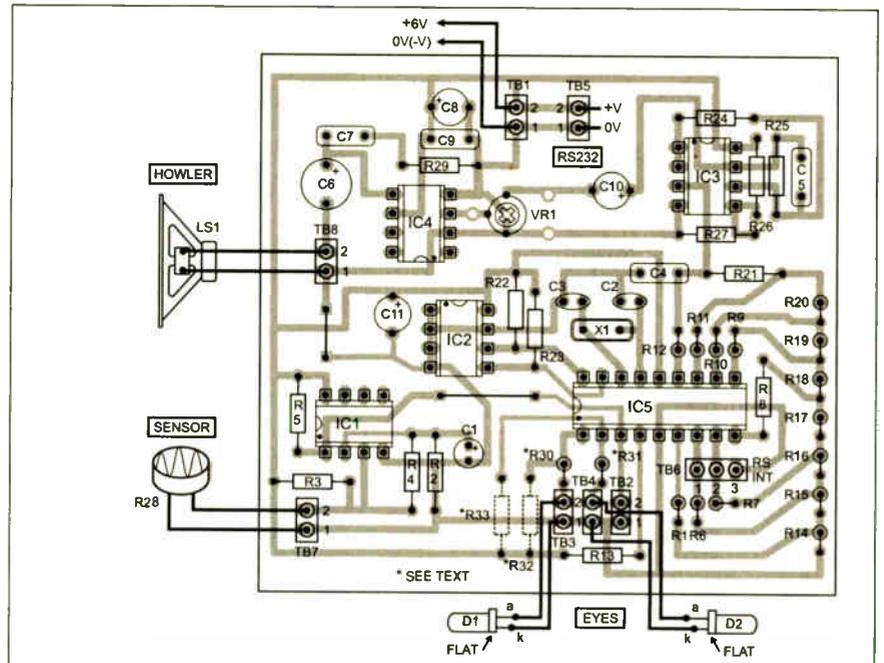Positioning the pumpkin requires a little thought, since it must be pointing to a light source (such as a porch lamp). It must be positioned so that the light is interrupted when someone approaches. A little experimentation may be required, and the value of resistor R4 adjusted if necessary.



Completed Howler prototype circuit board. Note resistors R33 and R32 do not appear on this board and the author has used header pins for the wiring take-off terminals

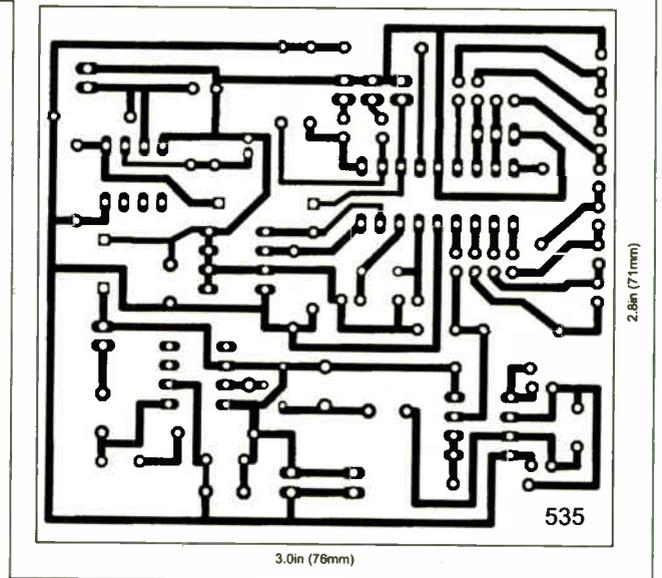


Fig.2. Printed circuit board topside component layout, off-board wiring details and full-size underside copper foil master pattern for the Halloween Howler

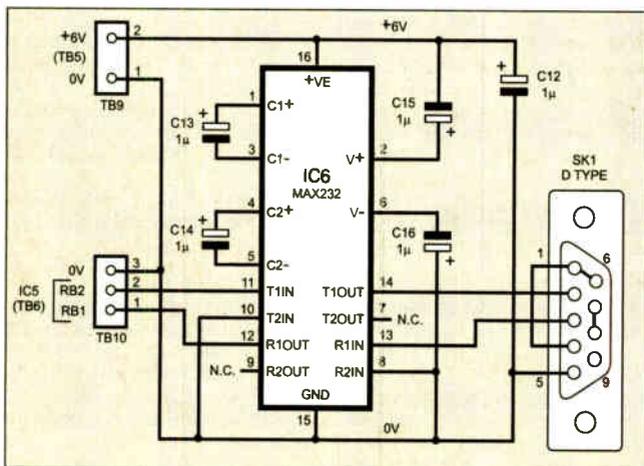


Fig.3. Suggested circuit diagram for a suitable RS232 Interface using the Maxim MAX232 chip. This circuit and accompanying board has not been tested with the Howler

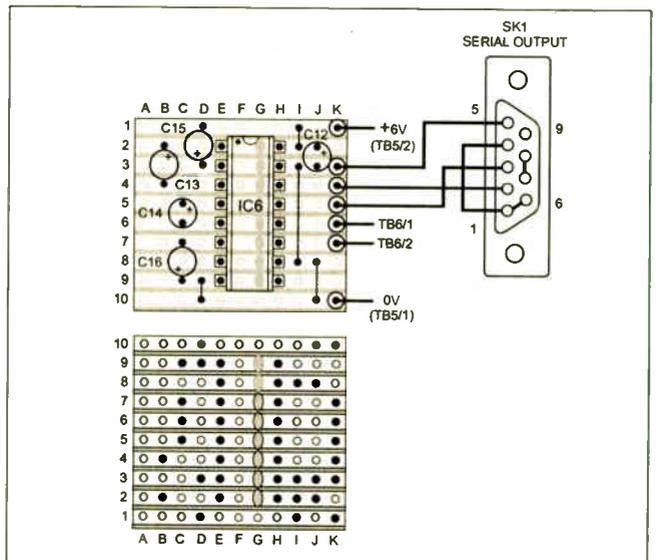


Fig.4. Stripboard component layout and wiring details for the suggested RS232 Interface circuit

The final effect on visitors is priceless, and worth the effort!

## Sound Downloading

The WAV file files can be downloaded from the *EPE* website (see later). The program consists of *dlwav.exe* and *cp30fwm.dll*. Copy these files to a directory on your PC (any name you want) and then run the *dlwav.exe* program.

An example of the program window is shown in Fig.5. First select the appropriate COM port, then click on the p.c.b. configuration that you will be using. If you choose the second option then two further input boxes will appear for additional sound files. Type in the names of the sound files you want to use, or click on the browse button to find them using Explorer.

## Download Interface

When you are ready to download the files to the board, connect an RS232 interface circuit to the PC and p.c.b. If you do not have such an interface, the circuit shown in Fig.3 can be assembled on stripboard. A suggested layout is shown in Fig.4, but has not been tested with the prototype.

Click the Download button in (as in Fig.5). After a few seconds the program should indicate it is waiting for the p.c.b. to respond. Apply power to the p.c.b. After a few seconds the *dlwav* screen should indicate the download progress. Downloading takes approximately 90 seconds. When it has finished, remove power from the p.c.b.

and disconnect the cables.

The program will check that the sound files are of the correct format. They must be stored in 11025Hz, 8-bit Mono mode format. Microsoft's Sound Recorder application can re-sample audio files to the correct format. If you open a WAV file in Sound Recorder and select the **File->Save As** option you can click on the Change button in the dialog and select the correct format. If the sound sample is too long it will be truncated by the *dlwav* program, although you can also use the Sound Recorder application to trim the file to the length you want.

Suitable sounds can be easily found on the Internet and resampled to the correct format if necessary. A search via [www.google.com](http://www.google.com) for "Halloween sounds" resulted in plenty of interesting options! If you choose to record your own sounds make sure that you record at a high level using a decent microphone. Low volume sound samples will not playback well. The

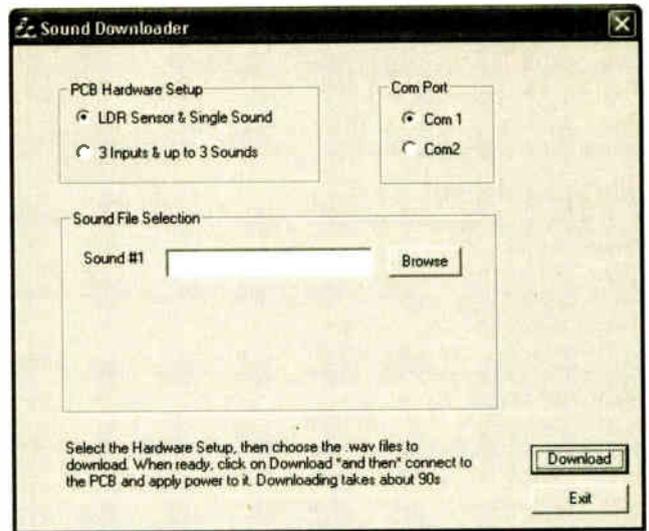


Fig.5. Screenshot of the download application window

author found a cheap "Studio Microphone" quite acceptable.

## Resources

Software, including source code files, for this design can be downloaded *free* from the *EPE* Downloads site, accessible via the home page at [www.epemag.co.uk](http://www.epemag.co.uk). It is held in the PICs folder, under Halloween.

This month's *Shop Talk* provides information about obtaining pre-programmed PICs and component buying advice. □

# SHOP TALK

with David Barrington

## Halloween Howler

No real "howlers" appeared when casting an eye down the components list for the *Halloween Howler* project. The LM op.amps and audio power amp i.c.s. should be widely available from our components advertisers.

For those readers who intend to program their own PICs, it should be pointed out that it's the 20MHz version of the PIC16F628-20 that is required. This is usually identified by the -20 after the main type number.

The MAX232 RS232 serial interface i.c. is one of the most favoured devices and readers should have no trouble in obtaining one from most of our components advertisers. For more technical details you could log-on to [www.maxim-l.c.com](http://www.maxim-l.c.com).

Some readers may experience difficulty in locating the 24LC512 serial EEPROM. This is currently listed by **Maplin** (☎ 0870 429 6000 or [www.maplin.co.uk](http://www.maplin.co.uk)), code N31BH. The serial EEPROM holds the WAV file sound data, up to 64KB, about six seconds.

Standard 5mm red i.e.d.s are used to simulate the "glowing eyes". Almost any i.e.d. will do here, so long as the PIC's drive capability of 25mA per pin is *not* exceeded.

For those readers unable to program their own PICs, ready programmed PIC16F628-20 microcontrollers can be purchased from **Magenta Electronics** (☎ 02083 565435 or [www.magenta2000.co.uk](http://www.magenta2000.co.uk)) for the inclusive price of £4.90 each (overseas add £1 for p&p). The sound file and the configuration information can be downloaded *free* from the *EPE* Downloads site, accessible via the home page at [www.epemag.co.uk](http://www.epemag.co.uk). It is held in the PICs folder under Halloween.

The Howler printed circuit board is available from the *EPE PCB Service*, code 535 (see page 733). Don't forget to seal the completed p.c.b. and miniature speaker inside a plastic bag; the inside of a pumpkin remains very moist for many weeks.

## PIC-Based USB Interface

The most surprising aspect when checking through the availability of components for the *PIC-Based USB Interface* was the s.i.l. resistor array. Component suppliers carried plenty of stocks of these resistor arrays but none at the 680 ohms specified in the article. However, a 680 ohms 5-way commoned s.i.l. resistor module was found listed by **Farnell** (☎ 0870 1200 100 or [www.farnellinone.co.uk](http://www.farnellinone.co.uk)), code 476-330.

The Darlington output opto-isolator type 6N139 is currently stocked

by **Rapid Electronics** (☎ 01206 751166 or [www.rapidelectronics.co.uk](http://www.rapidelectronics.co.uk)), code 58-0602. Readers should have no difficulty purchasing the MAX232 RS232 serial interface chip, this is one of the more popular devices.

For the USB type-B socket you could approach **ESR Components** (☎ 0191 251 4363 or [www.esr.co.uk](http://www.esr.co.uk)), who carry a large range of PCB connectors. Also try **Jaycar** (see back cover), code PS-092 or **Jameco** ([www.jameco.com](http://www.jameco.com)), code 230957.

The PIC18F2455 is one of the new USB-enabled flash memory micro-controllers and for those readers unable to program their own PICs, pre-programmed PIC18F2455s can be purchased from **Magenta Electronics** (☎ 02083 565435 or [www.magenta2000.co.uk](http://www.magenta2000.co.uk)) for the inclusive price of £10 each (overseas add £1 for p&p). The software, including source code files, is available for *free* download via the Downloads link on our UK website at [www.epemag.co.uk](http://www.epemag.co.uk).

The printed circuit board is available from the *EPE PCB Service*, code 536, (see page 733).

## Photic Phone

The IRF610 *n*-channel power MOSFET called for in the *Photic Phone* project does not appear to be in favour with our components advertisers. However, it is listed by **Farnell** (☎ 0870 1200 100 or [www.farnellinone.co.uk](http://www.farnellinone.co.uk)), code 354-430 and **RS Components** (☎ 01536 44079 or [rswww.com](http://rswww.com)) code 139-833.

The author specified a 500 ohm resistor for the ultrabright i.e.d., but as 510 ohms is the preferred value and it is shown as this in the circuit diagram. The Siemens SFH203 photodiode was purchased (*credit card only*) from **RS** (see above), code 195-681.

The Phone printed circuit boards are available as a pair from the *EPE PCB Service*, codes 531 and 532. As to the lens option, we leave that to readers own ingenuity. A toy telescope or binoculars perhaps.

## Back to Basics – Parking Radar/Telephone Switch

We do not expect readers to encounter any buying problems when shopping for parts for the *Parking Radar* or *Telephone Switch*, this month's *Back To Basics* projects. The relay used with the *Telephone Switch* board will, of course, need to be selected to suit the ratings of the appliance being controlled.

The 40kHz ultrasonic transmitter and receiver transducers, used in the *Parking Radar*, are normally sold in pairs. As an idea it might be worth investigating a combined single transmitter/receiver transducer from **Jaycar** (see back cover), code AU-5550. We have no idea as to the pinout arrangement for this device.

The two printed circuit boards are available from the *EPE PCB Service*, codes 533 (Radar) and 534 (Tele) – see page 733.

# buy.Microchip - source the parts you need - quickly and easily



<http://buy.microchip.com>

*When developing or manufacturing products, time to market is essential and this may mean you need to get hold of parts quickly. To complement our distributors' inventory of Microchip product, buy.Microchip gives you the ability to order direct from our factory.*

## buy.Microchip - The easy way to source parts 24 hours a day, 7 days a week

Buy online, pay by credit card

Complements existing distribution channels

Currently available in 28 European countries

Buy any Microchip product - devices, tools and development kits

Special fast-turnaround, flexible factory test cell

Items in stock ship within 48 hours of ordering

Speed is important. You need to bring products to market fast to beat your competitors, and can't afford to wait around for long-leadtime components or development tools. Microchip has created buy.Microchip, an extension of the Microchip website that allows you to place orders directly with Microchip to ensure the fastest possible delivery of the parts you need.

Microchip's distributors carry an extensive range of our vast product range. However, sudden increases in demand mean your requirements change and your particular, unique, product requirements may not be immediately available from a distributor. Conventional semiconductor production approaches can make it difficult to respond quickly.

Microchip have built an innovative "Flex Cell" in our testing facility that is used to provide the parts sold through buy.Microchip.

Basically it's a flexible test cell, which is separate from our high volume test line. While the flex cell shares the same test platform, test software, testing method and quality standards, it has one difference. In the flex cell, Microchip breaks set-ups all day to reconfigure to the immediate need of our customers. As a result, flex cell delivers short lead-times, but it costs more to manufacture so this is reflected in the pricing. If you have an urgent requirement, buy.Microchip can get you parts fast!

**buy.MICROCHIP**  
ONLINE CATALOG  
One-stop shopping for MCUs, digital signal controllers, analog and serial EEPROMs.  
<http://buy.microchip.com>



## ALL SYSTEMS ARE GO!

From movies to betting, the sky's the limit reports Barry Fox

**L**OVE it or hate it, Rupert Murdoch's satellite station *BSkyB* just keeps going from strength to strength. Murdoch's son James is now CEO and running the show.

At a recent meeting held to update city analysts, Chief Financial Officer Jeremy Darroch described the company as being in "robust health" and reported 12% subscriber growth over the last year, with 11% revenue growth.

Churn, subscribers who stop paying, averages 10.3% per year. Despite this, Sky now has 7.78 million paying subscribers with home dishes. Average revenue from each subscriber is now £384. "We expect 8m subscribers by the end of this year and 10m by end of the decade" says Murdoch. "We have 0.89m Sky+ PVR users with 1m expected in the next few weeks." Asked whether Sky's 10 million target is dependent on the UK government's analogue switch off plans, Murdoch admitted: "Of course there is some connection – the (government) switch off plan does not have a lot of clarity."

Revenue from Sky's interactive TV betting is rising by 40% a year with more growth expected following liberalisation of the UK laws. People can now lose even more money they cannot afford from the privacy of their homes. To protect children the electronic programme guide is being redesigned, with the option to remove all adult material from the menu and control the replay of Sky+ recordings.

An intriguing new service will be launched before the end of year that will let five million top-tier subscribers who also have a broadband connection use it to download movies and sports to a PC, or laptop "to watch on a train".

"We shall start by offering a few hundred movies on demand" says Murdoch. No details of the cost or technology are yet available. But Sky confirms that the PC will need to download a software application and very small print on a slide shown by Murdoch showed *Spiderman 2* using a file of 500MB – almost certainly with MPEG-4 compression instead of MPEG-2, as currently used by Sky and Freeview. Sky has already confirmed that its HDTV service, due for launch early next year, will use MPEG-4.

"The move from MPEG-2 to MPEG-4 will have to happen" says Murdoch. He also confirms that Sky and Microsoft are partners in DRM, the Digital Rights Management that controls how and when downloads can be viewed.

### Question Time

But many key questions on the new broadband service remain unanswered, most important how long the download will remain playable on a PC and what happens if a customer churns out. Murdoch's reply on this was very vague. "The DRM rights will depend on the window. They will vary with the title. There are no details yet. We will have details as we move forward".

The vagueness may be due to the fact that Sky is currently re-negotiating its movie contracts with three Hollywood studios.

Details also remain sketchy on the HDTV service now promised for 2006. There will be an additional charge for the receiver which will have one Ethernet and two USB ports and "greatly expanded hard drive" for the connection of peripherals and "a variety of new features"

"By 2007 CRT production will be discontinued – there will be 10 million HD Ready sets sold by end of the decade" says Murdoch. "By Christmas you will be able to buy a very good quality HD Ready screen for under £1000. It's going to be great. It's going to be a big story over the next five or six years".

### Down To Earth

More immediate and down to earth Sky will soon launch a battery radio that works anywhere in the house or garden to receive the sound of satellite stations that can normally only be heard from a mains-powered receiver with fixed dish antenna. The Gnome comes in two halves, a transceiver that plugs into the back of an ordinary satellite receiver, and a pint-sized portable.

A wireless telemetry link at 433MHz lets the portable switch channels on the satellite receiver; an FM signal at 864MHz carries hi-fi stereo to the portable. Working range is around 30 metres; the likely cost around £100. The Gnome is being made for Sky by Global Communications of Essex.

Murdoch confirms the Gnome will also work with *Freesat*, Sky's free-to-air satellite radio and TV service.

When Murdoch was asked about recent concern over the life cycle of existing receivers and how long receiver boxes can be expected to last, and a comment by Sky's suppliers that they are not allowed to talk about planned life, he tried to reassure:

"Life cycle is not an issue – at this point. We don't see any deterioration. There is a lot of life in them yet... I looked again before this conference. If we did see something I would tell you".

## ToothPIC Unveiled

At a recent London gathering FlexiPanel Ltd unveiled ToothPIC, a PIC microcontroller module with in-built Bluetooth and radio communications software libraries. The class-1 radio is FCC/CE certified and has 100m range with its integral antenna.

"ToothPIC offers you radio communications straight out of the box." said Richard Hoptroff, managing director of FlexiPanel. "No specialist knowledge of radio frequency design is required. Indeed, many remote control and data acquisition applications can use our off-the-shelf firmware, so the PIC doesn't even need to be programmed."

Based on the high-end PIC18LF6720 microcontroller, ToothPIC is supported by a large range of free software, from on-chip firmware solutions such as OpenTooth, which provides access control from a cellphone, to the user interface server, which allows it to create user interfaces on PCs, pocket PCs and high-end cellphones. Using Wireless Field Programming it can be reprogrammed from any Windows PC via Bluetooth, allowing OEMs to distribute product upgrades to their customers by email.

"We are really enthusiastic about the ToothPIC modules." says beta customer Marcel Jacomet, Lecturer at Bemer Fachhochschule, Switzerland, who uses them for teaching. "They are so simple to use and to download our own applications."

Utility functions are provided to take easy advantage of the ToothPIC peripherals, including real time clock, UART, 10-bit 12 channel A/D inputs and five p.w.m. outputs. The on-board power regulator accepts anything from 3V to 10V.

For more information on FlexiPanel's ToothPIC browse: [www.flexipanel.com](http://www.flexipanel.com).


# Conrad's One-Stop Shopping

**F**OLLOWING our welcome to Conrad Electronics last month, the company have filled us in with a bit more information about themselves:

Conrad has more than 80 years at the cutting edge of technology and says it leads the world in the supply of components. The Company began with providing components for kits for making radios in the 1920s, and then progressed in the 1930s to kits for making TVs. Components are now supplied for computers, multimedia, telephone, radio, and a multitude of home systems and electrical needs.

Conrad offers its products and services by catalogue, through retail branches and also via the Internet. Over 110 million products are shipped each year and products are supplied directly to customers in more than 150 countries worldwide. There are over 15,000 components on the website!

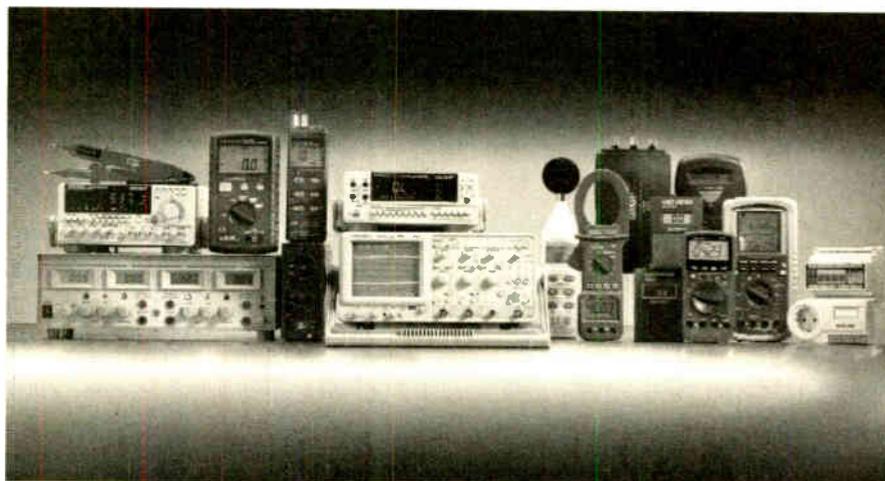You can also subscribe online to the free regular Newsletter and stay informed about all the latest offers and exciting products.




In Conrad's advert with us (see elsewhere in this issue), you can obtain a discount of 10% off orders valued at £30 or more. You'll also get the chance to win a Voltcraft Multimeter worth £139 in Conrad's Prize Draw!

For more information on Conrad browse: [www.conrad-direct.co.uk](http://www.conrad-direct.co.uk).

Email: [customerservice@conrad-direct.co.uk](mailto:customerservice@conrad-direct.co.uk) or Tel 0870 732 3223.

## Brunning Update Training

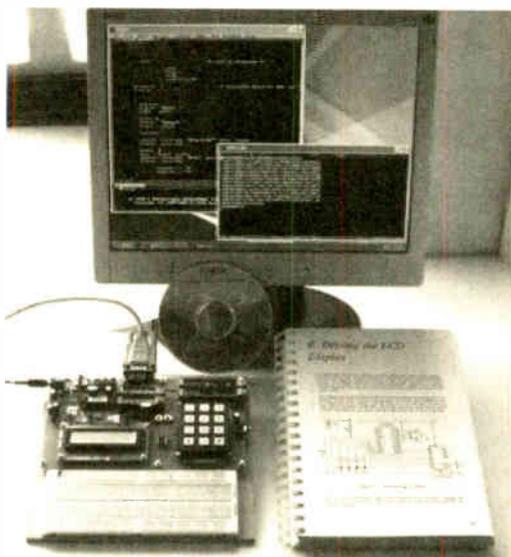

Brunning Software have just released a revised and updated version of their PIC Training and Development System. Peter Brunning believes that the practical approach is the natural way of learning so the theory is kept to a minimum. But he also believes that a newcomer can never become a proficient PIC programmer unless he or she has a grounding in the language of the processor.

The first of the two books included with the course gives a gentle start to PIC assembly language, while the second book teaches how to program

PICs using the C language. The P801 PIC Training System works through from absolute beginner to experienced engineer level.

For £159 plus postage you get a programmer module which is also your experimental test bed, two books, CD with PIC assembler and C compiler, plugtop PSU (UK only) and PC serial COM lead.

For more information contact Brunning Software, 138 The Street, Little Clacton, Clacton-on-Sea, Essex C016 9LS.

Tel: 01255 862308. Web: [www.brunningsoftware.co.uk](http://www.brunningsoftware.co.uk).

## PCB-POOL

The team at PCB-POOL have launched a number of new services. In their recent press release they say that they are Europe's largest on-line p.c.b. prototype supplier and are broadening their offering, promising a range which will suit every level of p.c.b. designer. The improvements will provide for reduced lead-times, and electrical testing as standard. The aim of the service is to pass on the cost saving benefits of prototype p.c.b. manufacture to the designer. Expensive tooling and photoplot charges have been eliminated.

The company has recognized the importance of receiving high quality p.c.b. prototypes, and all files are fully design-rule checked and validated by experienced CAM engineers. As an extra assurance for p.c.b. designers full electrical test is being offered on all four to six layer prototypes free of charge.

You can order pre-production quantities, working from a standard lead-time of eight working days. A fast turnaround service with a reduced lead-time of five working days is also available.

For further information visit: [www.pcb-pool.com](http://www.pcb-pool.com), or free phone: 0800 3898560.

## Quote...Unquote

Dixons, one of the UK's leading retailers of consumer technology on the high street, has announced the launch of a Dixons-exclusive, Hitachi-branded Hi-Fi that the retailer believes will redefine the shape of future home entertainment systems.

**OUT** are tape decks, CD-only players, AM radios and other legacy technologies.

**IN** are a 40GB hard drive that stores 10,000 songs, a DAB radio, a DVD player that plays all CD formats, and high specification speakers. Other enhancements include front and rear USB ports to enable owners of MP3 players to plug and play or plug and go.

## USELESS AT THEIR JOB

**Why cannot historians agree on even the key elements of recent electronic history? Mark Nelson investigates**

**Y**OU'D think that historians could at least do the job they're paid to do. As professionals, they of all people should be able to sort out who invented what and when.

"History is bunk," famously said the industrialist Henry Ford and from this you might infer he had a low opinion of historians. I could easily take offence at this remark, having a degree in economic and social history, but I feel bound to agree – up to a point. "Historians" manage to present multiple versions of what they present as facts, so it's not hard to criticise historians for failing to come up with a single, incontrovertible version of past events.

If only life were that simple! History exists to justify people's beliefs, as the conflicting versions of how any industrial or territorial dispute began will readily illustrate. And who invented radio – Marconi, Popov, Tesla or Nathan Stubblefield? It all depends whose side you are on!

### Perception of Kilby

And in that vein I had to smile when I read Jack Kilby's obituary in the September issue of this magazine, where it stated that he was the inventor of the monolithic integrated circuit (i.c.). It may be received wisdom but it's a "fact" that's widely contested by alternative historians and it all boils down to what you call an integrated circuit.

By common consent an integrated circuit contains both active and passive electronic components, all "integrated" in a single package. Who first invented it, patented it or turned it into a practical device is a matter of debate:

Jack Kilby of Texas Instruments invented the i.c. in 1958, yet the patent was awarded the following year to Robert Noyce, co-founder of Fairchild Semiconductor Corporation. In the event, both pioneers shared the honours when the U.S. Academy of Engineering bestowed on them both the academy's Draper Award in 1978; in 1989 President George Bush (senior) awarded each \$175,000.

So how come they both invented the i.c.? It depends on your definition. Kilby had the notion that all parts of an electronic circuit, not merely the transistor, could be made out of silicon on a single substrate. Creating the entire circuit in monolith i.c. form would make it smaller and much easier to produce. The idea appealed to his employers and in just over a month Kilby had built a working model.

This was in September 1958 and in February of the following year Texas

Instruments filed a patent for their "Solid Circuit", which was shown publicly for the first time in March.

### Rough Justice?

Ingenuous as this Solid Circuit was, it could not in itself set the world alight with just one transistor on-board. Someone who realized this was Robert Noyce, who had independently thought along similar lines. Although he did not start until January 1959, his debut design was the first i.c. with more than one transistor.

Aware, too, of Kilby's work he delivered a patent application that stressed the unique characteristics of his own design along with details of its potential applications, something missing from Kilby's presentation. This paid off for him and it was he who was awarded the patent for the first integrated circuit while Kilby's submission was still being analysed. Was this rough justice? It's hard to tell.

Of course you cannot do much with such basic circuit elements and it fell to others to develop i.c.-type devices with practical applications. The microprocessor is one and in 1968 Los Angeles computer expert Gilbert Hyatt took the integrated circuit a step further by including in one place all the pieces necessary to operate a computer (except memory and interface).

His patent application for this microprocessor was submitted in 1970 and although three engineers from Intel Corporation created the first commercially viable microprocessor the following year, while Hyatt's paperwork was still being scrutinised, it was nevertheless Hyatt who was eventually credited with its invention by the U.S. Patent Office.

### Ancient History

But this is by no means the end of the bickering and there are several other valid claimants for the credit of being father of the i.c. Radar scientist Geoffrey (G.W.) Dummer of Britain's Royal Aircraft Establishment had already outlined his ideas for integrated circuits in May 1952 and attempted to build a prototype in 1956.

His 1952 revelation was made at a conference in Washington D.C. when he explained how a solid block of material such as silicon could comprise separate layers that would act as the key components needed by electronic systems. He was thus the first person to publicise the concepts that Kilby and Noyce later brought to fruition.

Unfortunately for Dummer, his rudimentary integrated circuit of 1956 failed to persuade

British investors willing to fund further research, losing an opportunity to create a multi-million pound industry.

If you broaden the definition of the i.c. to include thermionic technology, then the honours must fall to the Germans. For in 1926 the Loewe company's OE 333 radio receiver employed a valve that incorporated two audio amplifier stages plus a final amplifier, all in a single standard-size glass tube.

You can see photos of this 3NF valve on the Web at [www.jogis-roehrenbude.de/Roehren-Geschichtliches/Loewe-Roehren/Loewe.htm](http://www.jogis-roehrenbude.de/Roehren-Geschichtliches/Loewe-Roehren/Loewe.htm) and if you read German, you may care to download the period literature offered on this page.

### Final Example

For my final example of disputed history, let's take a truly fundamental innovation of modern times, the printed circuit board or p.c.b. It's modern history after all, so determining the inventor must be a total no-brainer, but surprisingly not. A clue to the fact that it's perhaps not such a modern invention is its alternative and older name, the printed wiring board or PWB.

Because it was first exploited in earnest on the other side of the Atlantic, a notion grew up that the Americans invented the process to speed production of rugged military radios during World War II (p.c.b.s did not become commonplace in consumer electronics for another decade or more).

Then more diligent researchers named the inventor as Paul Eisler (1907-1995), an Austrian-born engineer who like many of his comrades came to Britain in the 1930s.

According to Eisler's own testimony, he first conceived the technique at his home around 1936, using small strips of copper foil fixed with varnish onto Bakelised paper (paper impregnated with phenolic resin to form a rigid but easily shattered board). In his book *My Life with the Printed Circuit*, he states that he employed his "first printed circuit invention in the form of a complete radio set that worked perfectly", as a credential when applying for a job with Plessey.

We can certainly credit Eisler with creating the first true printed circuit board but the idea was by no means new in 1936. A fascinating piece of research in the *Articles* section of [www.circuitree.com](http://www.circuitree.com) reveals a patent of 1903 by Albert Parker Hanson, living in Berlin, for circuit boards using stamped copper tracks bonded adhesively to paraffined paper. The patent even illustrates double-sided and multilayer p.c.b.s – such modernity over 100 years ago!



# Switch on to Conrad and get **10% OFF**

From power supplies and components to circuits and accessories, if you need the latest technology, there's only one place to look.

Europe's favourite electronics and technology retailer, Conrad offers a huge selection of over 15,000 of the most popular products at the best prices.

Place any first order over £30 and we'll reward you with a 10% saving. That's right, 10% OFF! And you'll also get the chance to win a Voltcraft Multimeter worth £139 in our exclusive Prize Draw.

So why go anywhere else?

## Plus WIN A Voltcraft Multimeter worth **£139**

- Large display
- Backlight
- Optical interface
- Professional performance
- 40,000 counts LCD




Switch on to Conrad today and visit  
[www.conrad-direct.co.uk/multimeter](http://www.conrad-direct.co.uk/multimeter)

**CONRAD**  
www.conrad-direct.co.uk  
Electronics. Technology. Tradition.

# PIC-Based USB Interface

Robert Lang

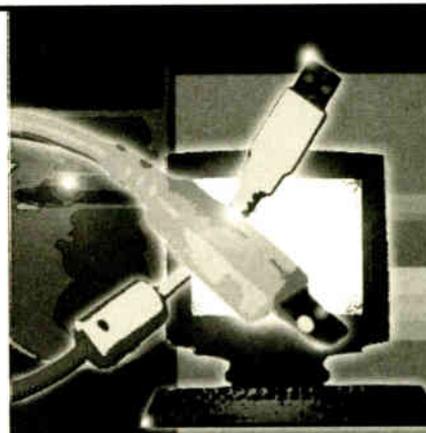

## How to easily use USB to communicate with the new PIC18F2455 microcontroller

**A**RE you ready to jump on the Universal Serial Bus (USB) bandwagon? Maybe you have an existing embedded application you would like to update to use USB. Maybe you have a new PIC application you would like to develop to use USB. In this article we explore the basics of an easy way of getting data into and out of a PIC18F2455 microcontroller using its USB interface.

The design allows existing RS232 devices to be controlled by a Windows 2000/XP USB connection. In addition, I.e.d.s can be controlled over the USB. Although the design is simple, it illustrates the process of getting data into and out of the PIC over a USB connection. The "easy way" approach to USB makes maximum use of existing free software and Windows drivers.

### Introduction to USB

The goals of the USB 2.0 development team were very lofty. They wanted to simplify, from the user's point of view, personal computer peripherals. They wanted a system that supported real time video, voice and audio data. They wanted a protocol that could handle isochronous data transfers and asynchronous messaging.

They wanted a standard interface that could quickly be used in products. They wanted new classes of devices that would expand the personal computer's capability, and they wanted backward compatibility with previous versions of USB.

The result is *Universal Serial Bus Specification, Revision 2*, a 650 page behemoth, that is available as a free download (see References, Ref.1, later). The USB specification contains almost anything you would want to know about USB, it is suggested that you start by reading Chapter 9 which discusses the USB device framework.

Chapter 9 includes device requests, descriptors and class definitions. USB allows peripherals to be plugged and unplugged without down-powering the computer. This process, called "enumeration", involves communicating with the peripheral to discover its identity and characteristics.

Information about the device is contained in descriptors that are transmitted to the host during enumeration. A unique address is assigned to each peripheral to be used for run-time transfers. The device is also assigned a configuration during the enumeration process.

### Slave Protocol


All USB peripherals are slaves that obey a defined protocol. They must react to request transactions sent from the host PC. For example, the peripheral must respond to control transactions that request detailed information about the device and its configuration. All USB devices support the requests and descriptor definitions described in Chapter 9.

In addition, devices may provide extended services that are characteristic of a group of devices. A class of devices, for example the Audio Device Class, is defined by a specific set of descriptors, requests and interface/endpoint usage. So you might find descriptors, request and interface usage relating to a volume control in the Audio Device Class but not in the Imaging Device Class.

Each USB device has two or more endpoints. An endpoint is a uniquely addressable portion of the USB device that is a sink or source of information that flows between the host and the device. One can think of an endpoint as a device buffer where data is placed to be transferred by the USB engine to or from the host. USB is a host-centric protocol so "IN" endpoints transfer data to the host from the USB device and "OUT" endpoints transfer data from the host to the USB device.

USB 2.0 supports four types of data transfer: Control, Interrupt, Isochronous and Bulk. Control transfers are typically used for command and status operations. They are essential and all enumeration functions are performed using control transfers. Interrupt transfers are typically non-periodic, small device "initiated" communication requiring bounded latency. An Interrupt request is queued by the device until the host polls the USB device.

Isochronous transfers occur continuously and periodically. They typically contain time sensitive information, such as an audio or video stream where a delay or retry would be unacceptable. However, if a

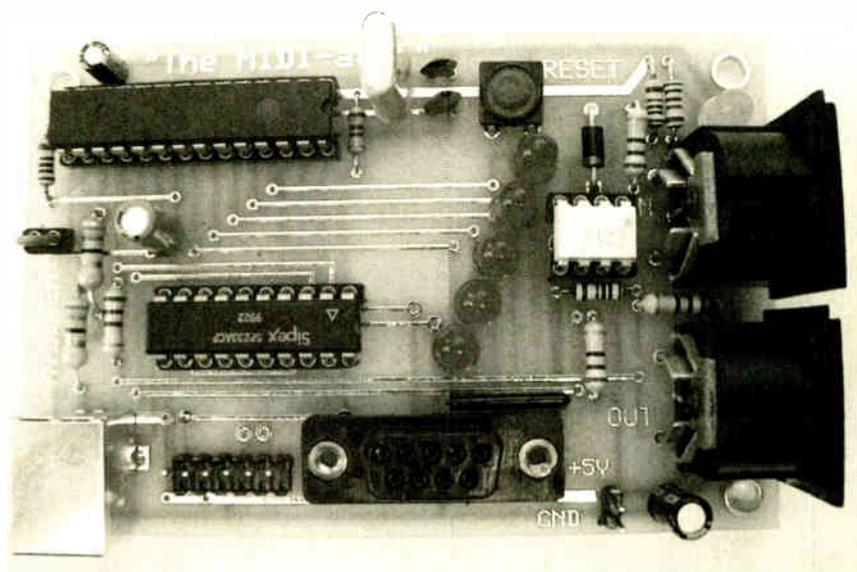

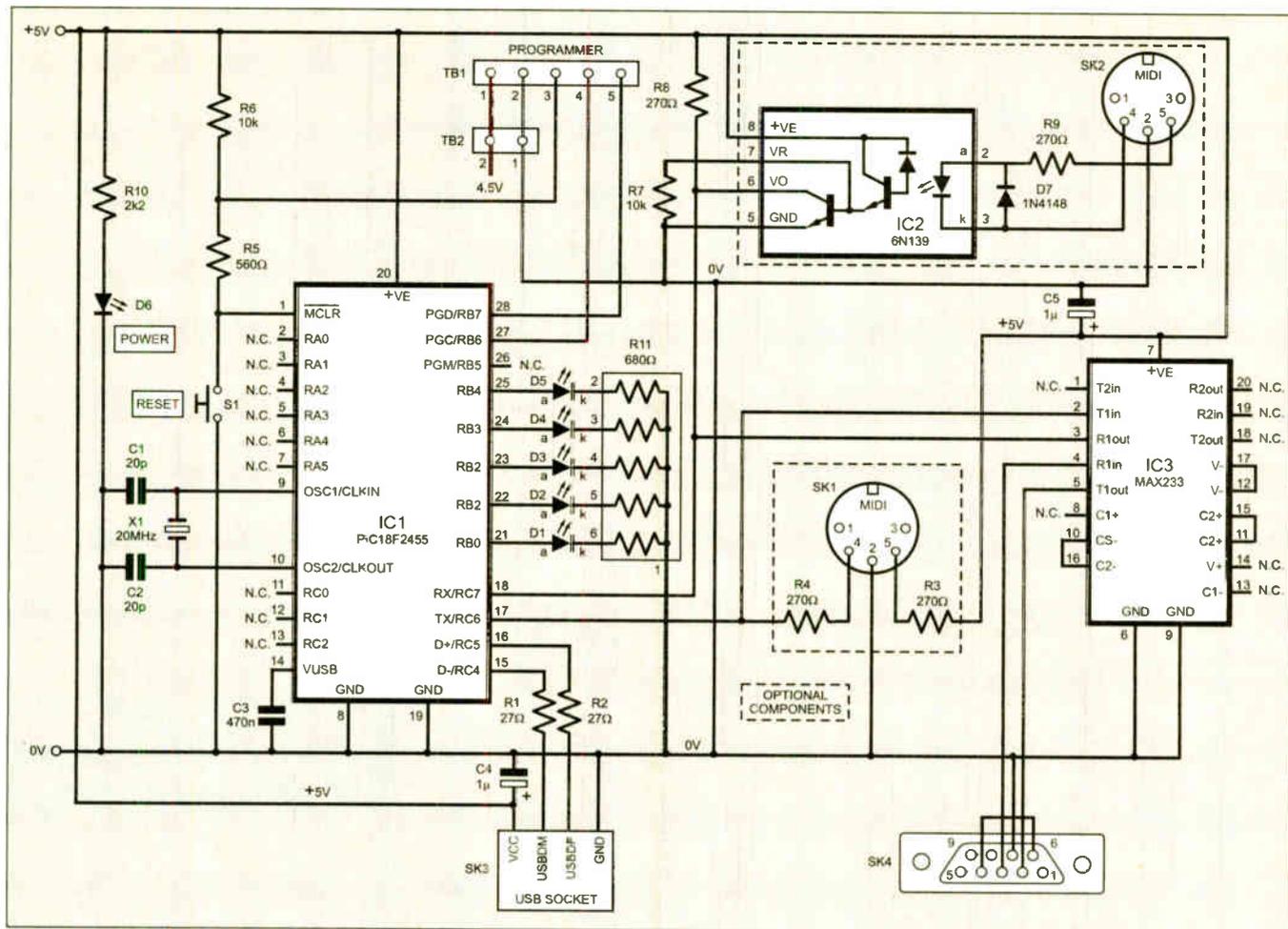


Fig.1. Complete circuit diagram for the PIC-Based USB Interface

packet or frame were to be dropped every now and again, it is less likely to be noticed by the listener/viewer.

Bulk transfers provide error correction on the data payload and error detection/re-transmission mechanisms, ensuring data is transmitted and received without error. Bulk transfers are the lowest priority and use spare un-allocated bandwidth on the bus after all other transactions have been allocated.

## Class Definitions

A USB device class is a group of devices that has a common set of descriptors, requests and interface/endpoint usage. Some of the USB device classes that have been defined in the specifications include Audio Device Class, Imaging Device Class, Communication Device Class (CDC), Human Interface Device (HID) Class, Mass Storage Device Class, Printer Device Class and others. Some of the classes have subclasses such as the MIDI devices under the Audio Class.

If you can fit your device into a standard USB device class then you can leverage your software development efforts by using the standard device drivers written by the operating system developers.

With our "easy" approach to USB we make the device a Communication Device. A complete description of the communication device class is contained in *Universal Serial Bus Class Definitions for Communication Devices* (Ref.2). It is only 121 pages.

Putting the USB device into the Communication Device class has two advantages:

1. Microchip has written and freely distributes PIC software for the Communication Device class to emulate RS232 over a USB connection.

2. From the PC side, the USB device just looks like a COM port to the Windows software. This allows us to use existing Windows software like Hyperterminal to communicate with the device over the USB port.

## PIC18F2455

The PIC18F2455 is one of the new USB-enabled flash memory microcontrollers from Microchip. It has 24K bytes of flash program memory that allow the user to store about 12 thousand 16-bit instructions which can be erased and reprogrammed electrically. The flash program memory supports 100,000 write/erase cycles and has a greater than 40-year data retention period.

This PIC has 2048 bytes of RAM data memory, and has many of the features users have come to expect from Microchip: a universal synchronous-asynchronous receiver/transmitter (USART), four timers, ten 10-bit ADC channels, and a master synchronous serial port (MSSP). The MSSP is useful for communicating with peripheral devices such as serial EEPROMS, and supports SPI and I<sup>2</sup>C protocols. The PIC18F2455 operates at clock speeds up to 48MHz.

The USB engine is V2.0 compliant and operates at low (1.5 million bits per sec) and full (12Mb/sec) speeds. The USB engine supports all types of data transfer and up to 32 endpoints. It has one kilobyte of RAM starting at 400h that is shared between the CPU and the USB engine. This shared memory can be configured for optimum use by the user. The first few locations are defined in `usbmap.c` and `usbmap.h` and are used for an endpoint (buffer) descriptor table consisting of: STAT, CNT and ADR.

There is one buffer descriptor table for each endpoint. STAT is the status register for the endpoint. Bit 7 determines who owns the buffer (CPU or USB engine) and who can write to it. CNT is the number of bytes in the buffer. ADR is the pointer to where the endpoint buffer starts in the 400h to 7FFh range.

## Circuit Description

The circuit diagram for the PIC-Based USB Interface described here is fairly simple and is shown in Fig.1. We begin with the power supply. There is none – the device is powered by the USB bus!

There are a couple of critical components. One is C3, a 470nF capacitor connected to V<sub>USB</sub> on the PIC18F2455. This is a filter capacitor and without it the PIC may not run at USB full speed. Since we are using power from the USB bus, we also need the 1μF capacitors, C4 and C5, to reduce the inrush current when the device is plugged into the USB bus.

When designing the circuit board, there were grand plans to make it also function as a USB MIDI interface. For that reason some additional components were added as outlined in Fig.1. The additional hardware needed for MIDI is very minimal – an optical isolator, IC2, on the input, some resistors and a couple of MIDI sockets. To get Windows to recognize the device as a MIDI interface, the PIC must be reprogrammed. The MIDI components are not needed for this project, but may be helpful to experienced readers who wish to add their own PIC code to make use of them.

The PIC18F2455 is the heart of the system. Use is made of its internal USB voltage regulator, USB transceiver and USB pull-up resistors. A 20MHz crystal (X1), in conjunction with capacitors C1 and C2, provides the clock signal. The 20MHz clock is increased to 48MHz inside the PIC.

The PIC handles all communications with the host over the USB bus and handles the two-way serial communication at 115,200 bits per second to the MAX233 RS232 driver/receiver, IC3. This device converts the 0V to 5V signals from the PIC to  $\pm 12V$  RS232 signals. The MAX233 generates the  $\pm 12V$  levels internally from the +5V supply line with no external components.

The output from IC3 is routed to socket SK4 where the RS232 cable is connected.

The five I.e.d.s (D1 to D5) are tied to the PIC's RB0 to RB4 pins and are used for status indicators as explained later. Pins RB6 and RB7 were used for in-circuit programming of the PIC during development of the software. The Reset switch, S1, connects the PIC's MCLR pin to the 0V line, causing the PIC to restart the program.

## Construction

Component and track layout details for the printed circuit board are shown in Fig.2. This board is available from the *EPE PCB Service*, code 536. Start assembly by soldering in the link wires, using 22-gauge single-core wire. Next, solder the small components: diodes, resistors and capacitors. Add sockets for the PIC18F2455, MAX233 and the 20MHz crystal.

Now place a mounting screw under the USB socket position if you plan to use that hole to secure the board in a box. The screw cannot be accessed once the USB socket is installed. Alternatively, you may prefer to use the board without a box, in which case you could fix four stick-on rubber feet to it later.

Next mount the reset switch, and sockets SK3 and SK4.

Omit those components which are for the MIDI interface, unless you intend to write your own PIC software for it.

If you intend to program the PIC yourself using a programmer suited to the PIC18F2455, mount the programming connector, TB1, and test points TB2. Pre-programmed PICs and source code files are available as stated later.

## Software Writing

Because Microchip wrote the CDC software in C, it was decided to write the remainder of the software in C as well. The C18 compiler is available for

# COMPONENTS

## Resistors

|                   |   |
|-------------------|---|
| R1, R2            | 27 $\Omega$ (2 off)                               |
| R3, R4,<br>R8, R9 | 270 $\Omega$ (4 off)<br>(see text)                |
| R5                | 560 $\Omega$                                      |
| R6                | 10k   |
| R7                | 10k (see text)                                    |
| R10               | 2k2   |
| R11               | 680 $\Omega$ 5-way<br>commoned<br>resistor module |

All 0.25W 5% carbon film unless stated

## Capacitors

|        |  |
|--------|--|
| C1, C2 | 20p ceramic disc,<br>5mm pitch (2 off) |
| C3     | 470n ceramic disc<br>5mm pitch         |
| C4, C5 | 1 $\mu$ radial elect.<br>10V (2 off)   |

## Semiconductors

|          |                                   |
|----------|-----------------------------------|
| D1 to D6 | red I.e.d. (6 off)                |
| D7       | 1N4148 signal<br>diode (see text) |

See  
SHOP  
TALK  
page

|     |  |
|-----|--|
| IC1 | PIC18F2455<br>microcontroller,<br>pre-programmed<br>(see text) |
| IC2 | 6N139 opto-isolator<br>(see text)                              |
| IC3 | MAX233 RS232<br>interface                                      |

## Miscellaneous

|          |  |
|----------|--|
| S1       | min. s.p. push-to-<br>make switch      |
| SK1, SK2 | 5-pin DIN socket<br>(2 off) (see text) |
| SK3      | USB B connector,<br>p.c.b. mounting    |
| SK4      | 9-pin D-type connector<br>(female)     |
| X1       | 20MHz crystal                          |
| TB1      | 5-way terminal<br>pin block            |
| TB2      | 2-way terminal<br>pin block            |

Printed circuit board, available from the *EPE PCB Service*, code 536; 20-pin d.i.l. socket; 28-pin d.i.l. socket; connecting wire; solder, etc.

Approx. Cost  
Guidance Only

**£25**

excluding case

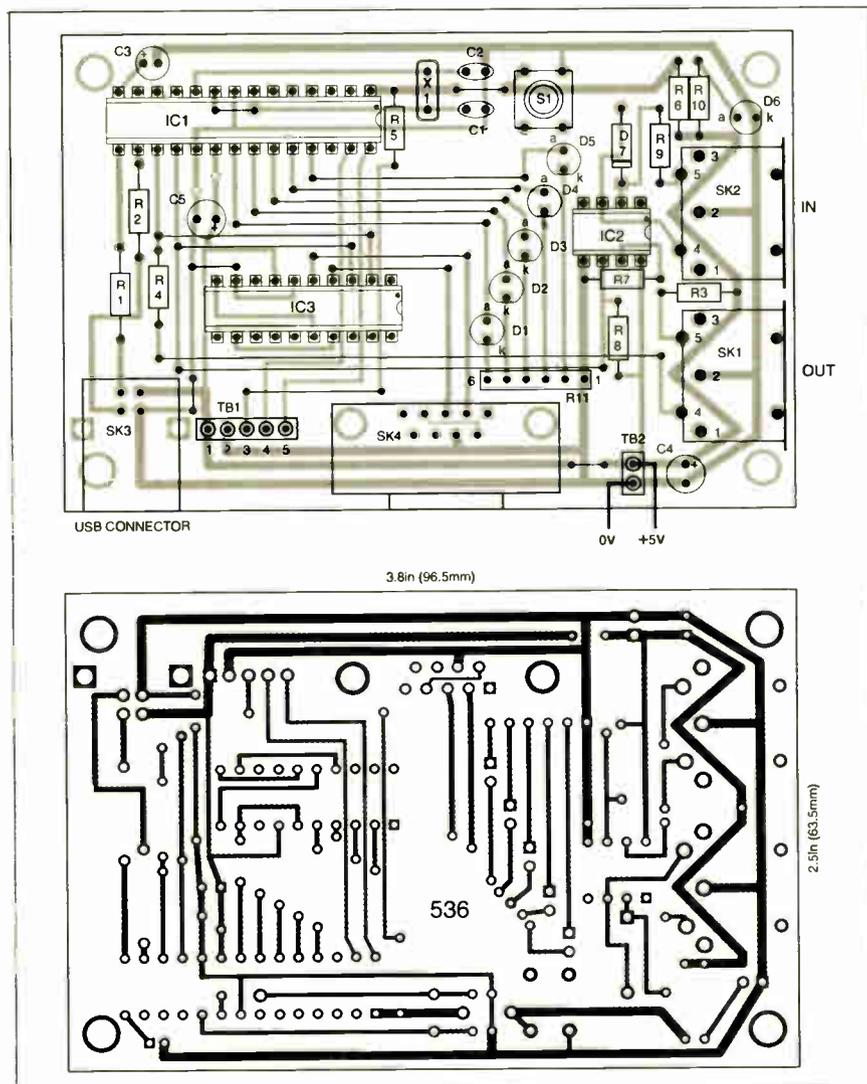


Fig.2. Component and track layout details for the PIC-Based USB Interface p.c.b.

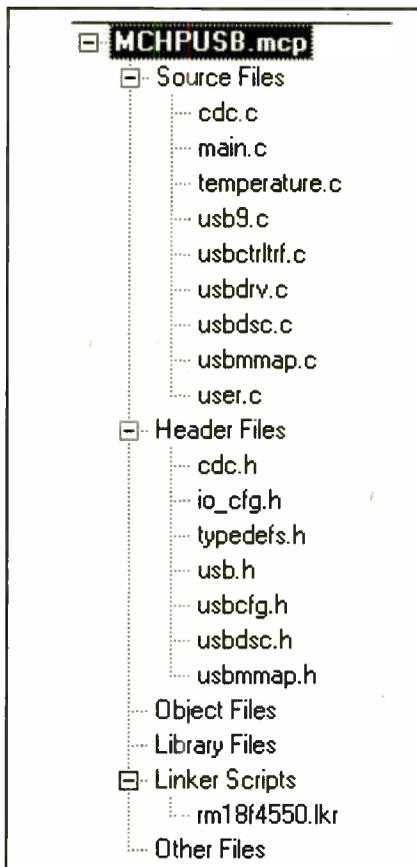


Fig.3. Files for the communication device class firmware

download from Microchip (see later) and is free for the first 60 days. After that time the compiler reverts to an un-optimized version. For that reason, the PIC software for this project was compiled with all optimization turned off.

Part of this design's software uses the CDC framework provided by Microchip, from whom it can be downloaded free. Additional information on the CDC framework can be found in Ref.3. When the MCHPUSB code is loaded into the C18 compiler the project files are as shown in Fig.3.

To compile the source code for this USB device, first delete the `temperature.c`, `user.c`, `usbcfg.h` and `main.c` files from the display. Then replace the `main.c` and `usbcfg.h` files with the ones supplied for this USB interface. Listing 1 shows the modified files installed in the project. If you are using a bootloader you can use the linker file supplied with the project, otherwise you should use the standard `18F2455.lkr` file.

The basic information about the device is contained in the device descriptor `device_dsc`, and configuration descriptor `cfg01` contained in file `usbdsc.c`. For example, the device descriptor, shown in Listing 2, tells the host that this is a CDC type device, and that the packet size for endpoint EP0 is eight bytes.

The vendor ID and product IDs are defined here. A vendor ID of `0x04D8` identifies this as a Microchip device. Normally the vendor ID and product ID are used to identify the operating system driver to be loaded when the device is plugged into the USB port.

## Listing 1 Files For USB Device

```
[FILE_INFO]
file_000=system\usb\usbmmap.c
file_001=system\usb\usbdrv\usbdrv.c *
file_002=system\usb\usb9\usb9.c
file_003=autofiles\usbdsc.c
file_004=system\usb\usbctrlrnf\usbctrlrnf.c
file_005=system\usb\class\cdc\cdc.c
file_006=main.c *
file_007=system\usb\usbmmap.h
file_008=autofiles\usbcfg.h
file_009=system\usb\usb.h
file_010=system\typedefs.h
file_011=autofiles\usbdsc.h
file_012=system\usb\class\cdc\cdc.h
file_013=C:\mcc18\lkr\18f2455.lkr          * files modified
```

## Listing 2 USB Device Descriptor

```
rom USB_DEV_DSC device_dsc=
{
    sizeof(USB_DEV_DSC), // Size of this descriptor in bytes
    0x01, // DEVICE descriptor type=1
    0x0200, // USB Spec Release Number in BCD format=2.00
    0x02, // Class Code, 2=CDC device
    0x00, // Subclass code
    0x00, // Protocol code
    0x08, // Max packet size for EP0 =8, see usbcfg.h
    0x04D8, // Vendor ID
    0x000A, // Product ID: CDC RS-232 Emulation Demo
    0x0000, // Device release number in BCD format
    0x01, // Pointer to Manufacturer string descriptor
    0x02, // Pointer to Product string descriptor
    0x00, // Pointer to Device serial number string (none)
    0x01 // Number of possible configurations
};
```

## Descriptor Pointers

In addition, the device descriptor points to some string descriptors for the manufacturer and product. The `rom` in the `device_dsc` type statement means that this constant information will be stored in program memory, thus freeing up valuable RAM memory on the PIC18F2455 device.

The configuration descriptor, `cfg01`, defines the amount of power that the device can draw, 100mA. Two interfaces are defined in the configuration descriptor. The first interface (#0) has one endpoint (EP02\_IN) which does 8-byte interrupt transfers. EP02\_IN is polled by the host every 2ms. The second interface (#1) has two endpoints (EP03\_OUT and EP03\_IN) which do bulk data transfers. The data packet size is 64 bytes.

The string descriptors consist of a byte containing the size of the string descriptor, a byte containing the value "3" that identifies it as a string descriptor and a string containing the text in Unicode format. Microchip has cleverly performed the conversion to Unicode by declaring each character as a word type.

## Variable Locations

The Microchip CDC framework software is general-purpose and automatically allocates the USB (400h-7FFh) region of memory. Because the framework does this automatically, it is not as clear where variables are located in memory, as is the case when using assembly language or allocating the variables manually.

The PIC18F2455 has rules as to how the memory must be allocated, which are defined in Ref.4. Table 1 shows the USB portion of the PIC18F2455 memory as allocated by the Microchip USB framework and the `main.c` program.

The framework provides several functions which are used to communicate over the USB:

- `mUSBUSARTIsTxTrfReady` determines if the USB engine is ready to accept a new string to transmit via USB

- `mUSBUSARTTxRam` writes a string of known length from data memory to USB

- `GetsUSBUSART` reads a string from the USB

- `mCDCGetRxLength` reports the length of the last string read from USB

Microchip advises that these functions should not be used in a blocking manner such as:

```
while (!mUSBUSARTIsTxTrfReady());
```

Since the CDC framework is written to poll the USB data, there must be nothing in the software that will cause a significant delay in the polling.

## Interrupts

Although the USB portion of the program does not use any interrupts, it became necessary to use interrupts to handle the RS232 serial interface. Interrupts are triggered when a character is received or a character can be transmitted.

It may be useful to follow along with the author's source code available from *EPE*. Received characters are loaded into 128-byte circular buffers (`serial_input_buffer` and `serial_output_buffer`) by the `usart_handler` interrupt routine. The routines `serial_receive` and `serial_send` are used to access the data in the buffers.

## Indicators

A series of indicators has been implemented using the l.e.d.s. When the device is first powered up, all five l.e.d.s D1 to

Table 1 USB RAM Memory Allocation

| RAM Address (hex) | Value (hex) | Variable Name             | Description   | Function   | MEMORY NAME |
|-------------------|-------------|---------------------------|---|--|-------------|
| 400               | variable    | ep0bo.Stat                | Buffer Descriptor Status Register (See page 171-174 of Reference 3)                           | Buffer Descriptor Table (BDT) for Endpoint 0 Out | USB RAM4    |
| 401               | 08          | ep0bo.Cnt                 | # of Bytes to be transmitted (before transmission) or bytes transmitted (after transmission). |  |             |
| 402               | 18          | ep0bo.ADRL                | Buffer Address Low Byte   |  |             |
| 403               | 04          | ep0bo.ADRH                | Buffer Address High Byte  |  |             |
| 404               | variable    | ep0bi.Stat                | Buffer Descriptor Status Register (See page 171-174 of Reference 3)                           | Buffer Descriptor Table (BDT) for Endpoint 0 In  |             |
| 405               | 08          | ep0bi.Cnt                 | Buffer size in bytes (before receive) or # of bytes received (after receive).                 |  |             |
| 406               | 20          | ep0bi.ADRL                | Buffer Address Low Byte   |  |             |
| 407               | 04          | ep0bi.ADRH                | Buffer Address High Byte  |  |             |
| 408-413           |             |                           | unused for CDC application  |  |             |
| 414               | variable    | ep2bi.Stat                | Buffer Descriptor Status Register (See page 171-174 of Reference 3)                           | Buffer Descriptor Table (BDT) for Endpoint 2 In  |             |
| 415               | 08          | ep2bi.Cnt                 | # of Bytes to be transmitted (before transmission) or bytes transmitted (after transmission). |  |             |
| 416               | 00          | ep2bi.ADRL                | Buffer Address Low Byte   |  |             |
| 417               | 05          | ep2bi.ADRH                | Buffer Address High Byte  |  |             |
| 418               | variable    | ep3bo.Stat                | Buffer Descriptor Status Register (See page 171-174 of Reference 3)                           | Buffer Descriptor Table (BDT) for Endpoint 3 Out |             |
| 419               | 40          | ep3bo.Cnt                 | # of Bytes to be transmitted (before transmission) or bytes transmitted (after transmission). |  |             |
| 41A               | 08          | ep3bo.ADRL                | Buffer Address Low Byte   |  |             |
| 41B               | 05          | ep3bo.ADRH                | Buffer Address High Byte  |  |             |
| 41C               | variable    | ep3bi.Stat                | Buffer Descriptor Status Register (See page 171-174 of Reference 3)                           | Buffer Descriptor Table (BDT) for Endpoint 3 In  |             |
| 41D               | 40          | ep3bi.Cnt                 | Buffer size in bytes (before receive) or # of bytes received (after receive).                 |  |             |
| 41E               | 48          | ep3bi.ADRL                | Buffer Address Low Byte   |  |             |
| 41F               | 05          | ep3bi.ADRH                | Buffer Address High Byte  |  |             |
| 420-427           | ...         | SetupPkt[8]               | 8 bytes   | Endpoint 0 Out Buffer                            |             |
| 428-42F           | ...         | CtrlTrfData[8]            | 8 bytes   | Endpoint 0 In Buffer                             |             |
| 500-507           | ...         | cdc_notice[8]             | 8 bytes   | Endpoint 2 In Buffer                             |             |
| 508-547           | ...         | cdc_data_rx[64]           | 64 bytes  | Endpoint 3 Out Buffer                            | USB RAM5    |
| 548-587           | ...         | cdc_data_tx[64]           | 64 bytes  | Endpoint 3 In Buffer                             |             |
| 700-77F           | ...         | serial_input_buffer(128)  | 128 bytes   |  |             |
| 780-7FF           | ...         | serial_output_buffer(128) | 128 bytes   |  | USB RAM7A   |

D5 are flashed sequentially. This indicates that the device is programmed and that the clock is running. Next, the l.e.d.s are flashed as shown in Table 2 while the USB enumeration is done.

When the enumeration is successfully completed l.e.d.s D1 and D2 will flash alternately. During the first enumeration the operating system will ask for a device driver.

The user must point to the directory that contains the `mchpcdc.inf` file as shown in Fig.4. This file contains information that matches the product ID and vendor ID to the `usbser.sys` driver. The communication device class driver for Windows is called

`usbser.sys` and is part of the Windows 2000/XP operating system.

The system will complain that the driver has not passed the Windows Logo testing, which is surprising since Microsoft wrote the driver, but continue the installation anyway. When the software installation is complete you will see Fig.5 on screen.

The flow of the main program is as follows. The `InitializeSystem` routine flashes the l.e.d.s to verify that the program is working, initialises the USB and initialises the USART to a transmission rate of 115,200 bits per second. The bit rate can be changed in the `IntializeUSART` routine.

Next the serial interrupts are enabled by the `EnableInterrupts` routine. All of the USB transmissions are handled by the `USBTasks` routine which is part of the CDC framework provided by Microchip. The `DataTransfer` routine displays the USB status on the l.e.d.s by calling the `BlinkUSBStatus` routine.

The `USB_to_USART_handler` handles the processing of received USB data and its transmission out via the RS232 connection. The `USART_to_USB_handler` does the receipt of incoming RS232 data and the queuing of the data for USB transmission. The `display_leds` routine is called by these

last two routines to control the l.e.d.s based on the data received by the device.

Just to make it interesting, the receipt of certain characters toggle the l.e.d.s on and off. If a "0" is received, the logic showing the USB status in the l.e.d.s is turned off. Of course your imagination is the only limit to what can be done on the PIC once the USB data link is working.

There was some difficulty with getting the RS232 input to work. The first problem had to do with some variables, like `istart`, that were used in both the interrupt routine and the main routines. These variables needed to be declared as `volatile` to make sure both routines used the latest values.

A second problem had to do with the way the number of received bytes was calculated in the `serial_rxbytes` routine. This routine had to be modified to work with the C18 compiler. The C18 compiler was used to compile and link the C source into the `MCHPUSB.hex` file.

If you are programming your own PIC, make sure that your system works with the PIC18F2455 since the programming algorithm is different to that for many other PICs.

## Hardware Testing

Before plugging the device into your computer's USB port, check its operation by

**Table 2 LED Blink Codes**

| USB STATE                           | LED 1  | LED2      | LED 3     | LED 4     | LED 5     |
|-------------------------------------|--|-----------|-----------|-----------|-----------|
| Detached State                      | off  | off       | off       | off       | off       |
| Attached State                      | on   | on        | off       | off       | off       |
| Powered State                       | on   | off       | off       | off       | off       |
| Default State                       | off  | on        | off       | off       | off       |
| Addressed State                     | blinking   | off       | off       | off       | off       |
| Configured State                    | blinking   | blinking  | off       | off       | off       |
| ASCII '0' received via USB or USART | LEDs toggled between Configured State and all off. |           |           |           |           |
| ASCII '1' received via USB or USART | toggled  | unchanged | unchanged | unchanged | unchanged |
| ASCII '2' received via USB or USART | unchanged  | toggled   | unchanged | unchanged | unchanged |
| ASCII '3' received via USB or USART | unchanged  | unchanged | toggled   | unchanged | unchanged |
| ASCII '4' received via USB or USART | unchanged  | unchanged | unchanged | toggled   | unchanged |
| ASCII '5' received via USB or USART | unchanged  | unchanged | unchanged | unchanged | toggled   |

applying a 5V power source to connector TB2. The first thing that should happen is that the l.e.d.s should flash sequentially. This means that the device is powered and programmed. The device should draw less than 55mA. If it does not, stop and check the circuit.

Do not plug the device into your USB port until you are sure your wiring is correct or you may damage the port. Some, but not all USB ports, have overload protection, so do not rely on it.

The next thing to do is to plug the device into the USB port and check that the device is properly enumerated (see earlier). This can be done using the `USBVIEW` program (see later). Fig.6 shows the output of the `USBVIEW` program with the hardware and software of this article connected.

`USBVIEW` shows that the device has one configuration and a maximum control packet size of eight bytes. It operates at full speed and has three open pipes. The first

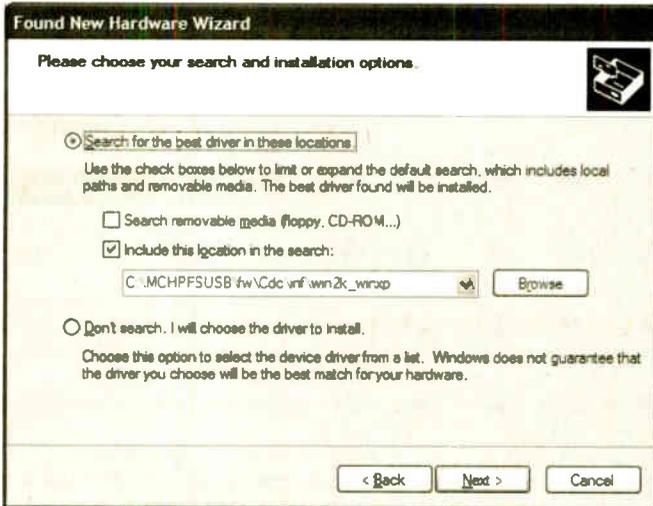


Fig.4. First device enumeration

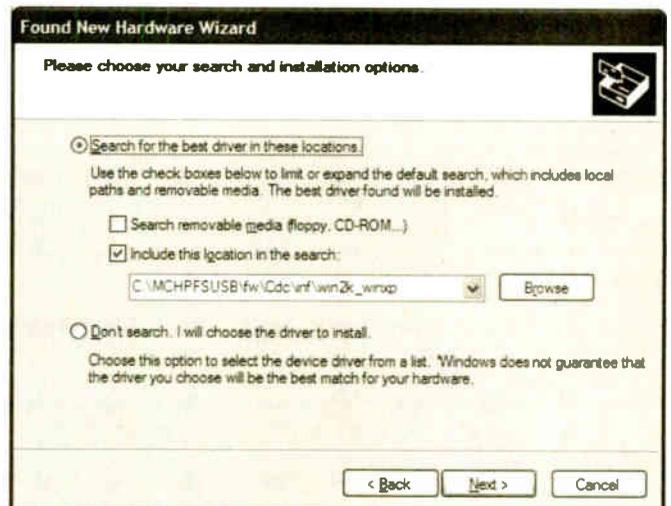


Fig.5. USBVIEW of installed device



Fig.5. Successful completion of Windows driver installation

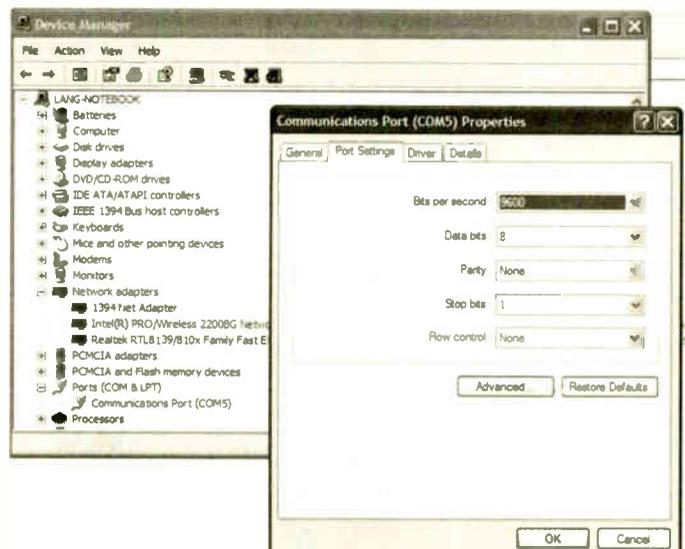


Fig.7. Device Manager view of installed device

pipe uses interrupt data transfers and is for device-to-host data transfers (82) every 2ms and has a maximum packet size of eight bytes.

The second pipe uses bulk data transfers and is for host-to-device data transfers (03) and has a maximum packet size of 64 bytes. The third pipe uses bulk data transfers and is for device-to-host data transfers (83) and has a maximum packet size of 64 bytes. We can also look at the USB device using the XP device manager as shown in Fig. 7.

It will be seen that the USB device looks like a standard Windows COM port (COM5). To Windows application programs, like Hyperterminal or a program you might write in Visual Basic or C, the device will look like a standard COM port and can be accessed as one.

## Hyperterminal Test

The final test involves using the Hyperterminal (or other) terminal emulation program. Plug the USB device into a Windows 2000/XP PC running Hyperterminal, connect a loopback plug to the RS232 socket on the USB as shown in Fig. 8. With this configuration the transfer of data into and out of the device can be observed.

RS232 data routed out of the device is sent back to it via the loopback plug. The data typed into Hyperterminal will also appear on the Hyperterminal screen after being sent to the USB device, sent out the RS232 connector, read back in the RS232 connector and transmitted via USB back to the host.

Although there are no data flow controls on the USART data, blocks of 15,000 characters have been sent and received successfully at 115,200 bits per second using this device.

One additional piece of information about using Windows programs like Hyperterminal with the USB device: if you unplug the USB device from the host computer with Hyperterminal running, when you plug the USB device back into the host, Hyperterminal will not be able to communicate with it.

The proper sequence, if you want to unplug the device and reconnect it, is to shutdown Hyperterminal before unplugging. This applies whether the USB is disconnected by unplugging or using its Reset switch (S1).

For the final test, remove the loopback plug. Now if you type a "0" in the Hyperterminal the flashing l.e.d.s should stop. Typing consecutive "1"s should turn on and off l.e.d. D1. Likewise "2, 3, 4, 5" should turn on and off l.e.d.s D2, D3, D4

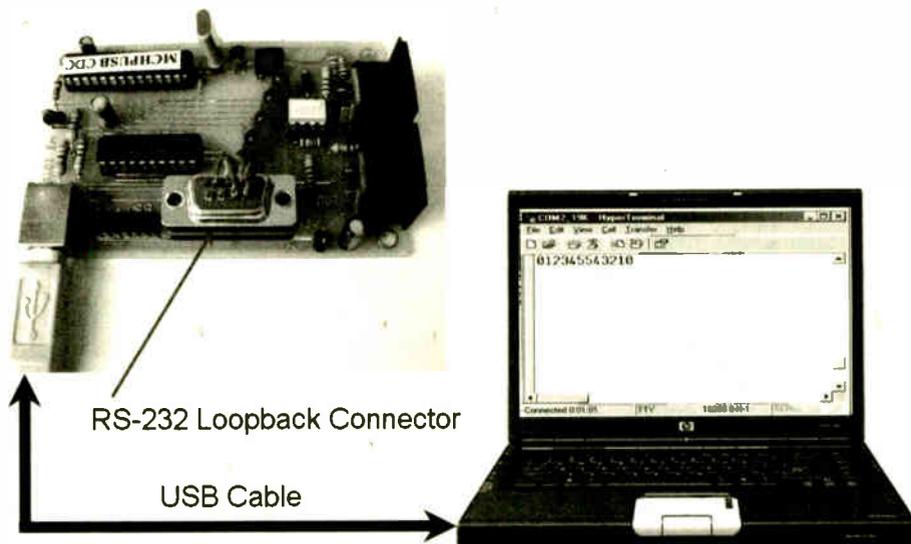


Fig. 8. USB-RS232 Testing Configuration

and D5. Another "0" should set the l.e.d.s back to the USB status reporting mode.

Note that this logic is seen to work when the loopback is plugged in, but it will not be seen when the USB "0" takes the device out of USB status reporting mode – the "0" being echoed from the loopback plug puts it back into USB status reporting mode.

## Conclusion

This is an interesting project which allows computers using the Windows 2000/XP operating system to communicate with a PIC microcontroller over the USB port. The device allows computers that do not have a COM serial port to use legacy devices.

This project also provides a practical introduction to USB, to CDC devices, to one of the new USB flash PICs and to the C18 compiler. As well as showing how l.e.d.s can be controlled via USB, it also provides the basics of getting data into and out of a PIC using USB, becoming the foundation of more complicated USB PIC projects.

## Resources

Sourcecode is available for free download from our Downloads site, access via [www.epemag.co.uk](http://www.epemag.co.uk).

## References

1. Universal Serial Bus Revision 2.0 Specification:  
[www.usb.org/developers/docs/](http://www.usb.org/developers/docs/)
2. Universal Serial Bus Class Definitions for Communication Devices:

[www.usb.org/developers/devclass\\_docs#approved](http://www.usb.org/developers/devclass_docs#approved)

3. Migrating Applications to USB from RS-232 UART with Minimal Impact on PC Software, Microchip Application Note AN956.

4. Microchip datasheet PIC18F2455/2550/4455/4550 for High Performance Enhanced Flash USB Microcontrollers with nanoWatt Technology:

[ww1.microchip.com/downloads/en/DeviceDoc/39632b.pdf](http://ww1.microchip.com/downloads/en/DeviceDoc/39632b.pdf)

5. PIC18F2XX0/2XX5/4XX0/4XX5 Flash Microcontroller Programming Specification from [www.microchip.com](http://www.microchip.com)

6. Microchip MPLAB C18 Student Edition Compiler:

[www.microchip.com/stellent/idcplg?IdcService=SS\\_GET\\_PAGE&nodeId=1406&dDocName=en010014&part=SW006011](http://www.microchip.com/stellent/idcplg?IdcService=SS_GET_PAGE&nodeId=1406&dDocName=en010014&part=SW006011)

7. Communication Device Class (CDC) Firmware:

[www.microchip.com/stellent/idcplg?IdcService=SS\\_GET\\_PAGE&nodeId=2124&param=en022625](http://www.microchip.com/stellent/idcplg?IdcService=SS_GET_PAGE&nodeId=2124&param=en022625)

8. USBVIEW Computer Program:  
[www.ftdichip.com/Resources/Utilities.htm](http://www.ftdichip.com/Resources/Utilities.htm)

Robert Lang is a professional electrical engineer interested in embedded microprocessors, mechanical musical instruments and MIDI. He is a freelance writer for electronic hobbyist, computer and synthesizer magazines. He can be reached at [rlang@netdoor.com](mailto:rlang@netdoor.com) or by a Google search for HARPSITRON. □

**EP**  
Online  
[www.epemag.com](http://www.epemag.com)


Get your magazine "instantly" anywhere in the world – buy and download from the web. TAKE A LOOK, A FREE ISSUE IS AVAILABLE A one year subscription (12 issues) costs just \$14.99 (US) [www.epemag.com](http://www.epemag.com)

# MikroElektronika

MICROCONTROLLER DEVELOPMENT TOOLS
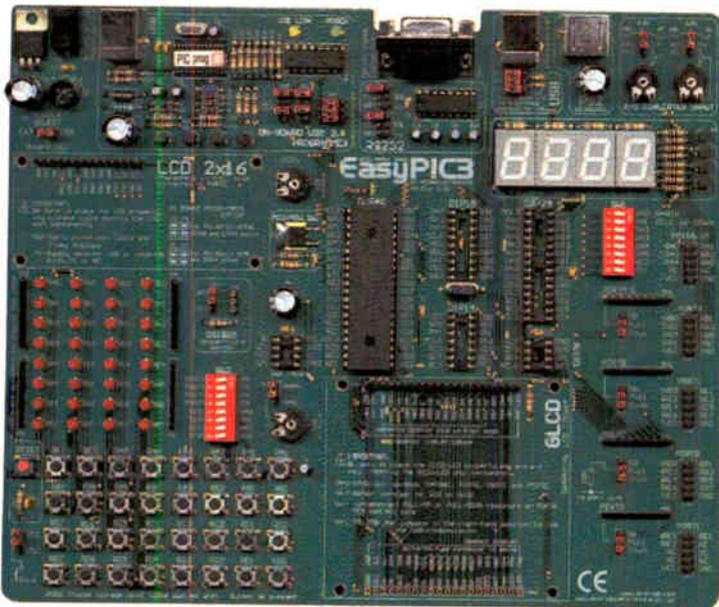
## from Breadboarding Systems

Make PICmicro<sup>®</sup> development easy with the EasyPIC3 - only £99!



The new EasyPIC3 Development Board combines a versatile development/experiment board with a built-in USB programmer. With its wealth of on-board I/O devices and support for virtually all 8, 14, 18, 28 and 40-pin PICmicro<sup>®</sup> microcontrollers in the 10F, 12F, 16F and 18F families, we're certain you won't find a more versatile high quality board at such a low price. The EasyPIC3 Development Board is supplied with USB programming/power cable, programming software and useful example programs.

Also available are similar boards for the 8051, AVR and dsPIC, each at the same great price of £99 including UK delivery and VAT—please telephone or see our website for further details.

### EasyPIC3 Development Board features:

- High quality development/experiment board with built-in USB 2.0 high-speed programmer.
- Programming software compatible with Windows operating systems including 2000 and XP.
- Comes with a PIC16F877A microcontroller but compatible with virtually all 8, 14, 18, 28 and 40-pin PICmicro<sup>®</sup> devices in the 10F, 12F, 16F and 18F families.
- On-board I/O devices including switches, LEDs, seven-segment displays, potentiometers and RS-232 interface. Now also features USB and PS/2 keyboard interface connectors.
- Provision for easy fitting of optional DS18S20 temperature sensor, and LCD and GLCD displays.
- All I/O lines available for off-board expansion.
- Wide range of optional add-on boards available including ADC, DAC, EEPROM, Compact Flash, MMC/SD, Keypad, RTC, RS-485, CAN and IrDA. Additional add-ons available soon.
- Powered from your PC's USB port or optional mains adapter.
- Supplied with example programs written in assembly language, BASIC, C and Pascal.
- Supplied with Microchip Technology's MPLAB development software and demonstration versions of MikroElektronika's mikroBASIC, mikroC and mikroPascal compilers.

### Learn about microcontrollers with our EasyPIC3 Starter Pack - just £149!

We've taken the EasyPIC3 Development Board and added a 16x2 character LCD display, 128x64 graphical LCD, DS18S20 temperature sensor, RS-232 serial communications cable and our own easy-to-follow microcontroller tutorial to form a complete and self-contained Starter Pack—everything you need to learn about and experiment with microcontrollers! With this pack you will quickly become proficient in microcontroller programming and interfacing. Please see our website for full list of covered topics.

### Make programming easy too with mikroBASIC, mikroC and mikroPascal

Three incredibly easy-to-use yet powerful compilers for PICmicro<sup>®</sup> microcontrollers, each featuring a user-friendly code editor, built-in tools and routines and source-level debugger. Supplied libraries facilitate rapid development and include ADC, CAN, Compact Flash, EEPROM, Ethernet, Graphic LCD, I<sup>2</sup>C, LCD, 1-wire, PWM, RS-485, sound, SPI, USART, USB routines and many more. mikroBASIC and mikroPascal—£99 each, mikroC—£149.


Call 0845 226 9451 or order online at [www.breadboarding.co.uk](http://www.breadboarding.co.uk)

All prices include UK delivery and VAT. Major credit and debit cards accepted. Secure online ordering.
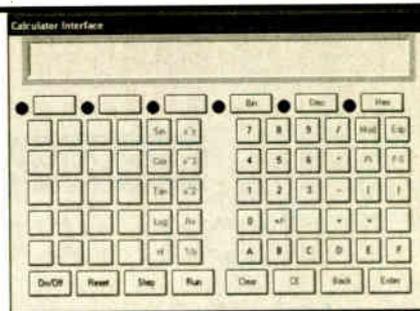
# Introducing the Virtual DIY Calculator

Clive "Max" Maxfield & Alvin Brown

Learn how computers do maths without making your brain ache!



**W**HEN you come to think about it, there are lots of "application-type" computer books along the lines of *Learn Prof. Cuthbert Dribble's Visual Programming V6.0 In 21 Days* (you often have only 21 days, because that's when version 7.0 of the software is going to come out). Sad to relate, however, there really aren't many tomes – outside of mega-complex University courses – that teach how computers actually work.

In order to address this sad state of affairs, the authors decided to pen their own humble offering. One point we considered is that it's a lot easier to learn how to do something if you actually have a specific project in mind.

For example, if someone simply hands you a plank of wood, a saw, a hammer and some nails, you might hang around for a while pondering just what to do. But if you are also presented with the plans for a simple bird table, then you can immediately leap into the fray with gusto and abandon.

Thus, we decided to base a book (details are given later) on the concept of a simple calculator called the DIY Calculator. The cunning part of all of this is that we created the DIY Calculator as a virtual machine that runs on your home computer. This article is a spin-off from the book and is designed to give a brief introduction as to how the DIY Calculator functions. In order to facilitate this, you can download a fully-functional copy of the DIY Calculator software from our website at [www.DIYCalculator](http://www.DIYCalculator) for free (you'll find instructions on how to download and install the calculator on the website).

## Computers and Calculators

In its broadest sense, a computer is a device that can accept information from the outside world, process that information using logical and/or mathematical operations, make decisions based on the results of this processing, and – ultimately – return the processed information to the outside world in its new form.

The main elements forming a computer system are its central processing unit (CPU), its memory devices (ROM and RAM) that are used to store programs (sequences of instructions) and data, and its input/output (I/O) ports that are used to communicate with the outside world. The

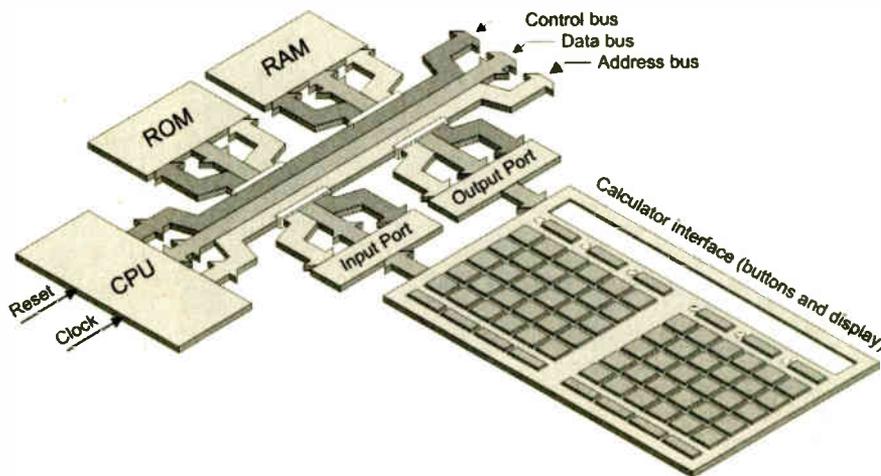


Fig. 1. The main elements forming a computer-calculator. Reproduced from *How Computers Do Math* with the kind permission of the publisher

CPU is the "brain" of the computer, because this is where all of the number-crunching and decision-making is performed. Read-only memory (ROM) has its contents hard-coded as part of its construction; by comparison, in the case of random access memory (RAM), you can load new values into it and read these values back out again later.

The term "bus" is used to refer to a group of signals that carry similar information and perform a common function. A computer actually makes use of three buses called the control bus, address bus, and data bus. The CPU uses its address bus to "point" to other components in the system; it uses the control bus to indicate whether it wishes to "talk" (output/write/transmit data) or "listen" (input/read/ receive data); and it uses the data bus to convey information back and forth between itself and the other components. Our virtual computer is equipped with a data bus that is eight bits wide and an address bus that is 16

bits wide. This allows the address bus to point to  $2^{16} = 65,536$  different memory locations, which are numbered from 0 to 65,535 in decimal; %0000000000000000 to %1111111111111111 in binary; or \$0000 to \$FFFF in hexadecimal, where the concepts of binary and hexadecimal are briefly introduced a little later in this article.

Once we've conceived the idea of a general-purpose computer, the next step is to think of something to do with it. In fact

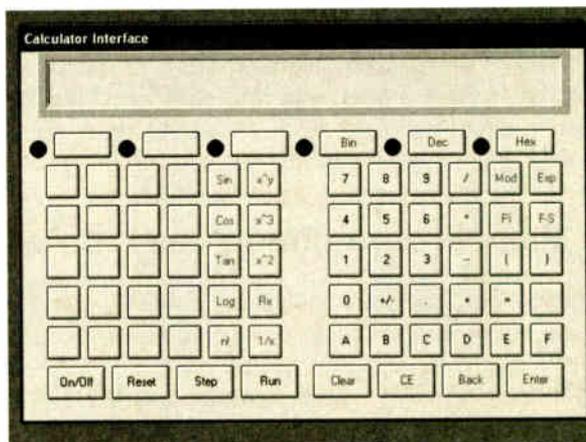


Fig. 2. Screenshot of the DIY Calculator's interface

there are millions of tasks to which computers can be assigned, but the application we're interested in here is that of a simple calculator. So what does it take to coerce a computer to adopt the role of a calculator? Well, one thing we require is some form of user interface, which will allow us to present data to – and view results from – the computer (Fig.1).

The calculator's user interface primarily consists of buttons and some type of display. Each button has a unique binary code associated with it, and this code will be presented to the computer's input port whenever that button is pressed. Meanwhile, one of the computer's output ports can be used to drive the display portion of the interface.

## A Simple Test Case

In order to provide a simple demonstration as to how the DIY Calculator works, download your free copy and install it as described on our website. Now use the **Start > Programs > DIY Calculator > DIY Calculator** command (or double-click the **DIY Calculator** icon on your desktop) to launch this little rascalion, which should look something like the screenshot shown in Fig.2.

Click the **On/Off** button on the calculator interface to power it up and then click on some of the "0" through "9" buttons. Nothing happens, because we haven't loaded a program yet. In a moment we are going to create our own program, but just to provide a simple example, we've already provided a test case for you to play with as part of the download.

Use the **Tools > Assembler** command (or click the appropriate icon in the main window's tool bar) to launch an application called the assembler. Now use the assembler's **File > Open** command to open the file called **hello.asm** that you'll find in the **C:\DIY Calculator\Work** folder on your system.

This program is in a low-level computer programming language known as *assembly language*. Each computer has its own assembly language, but once you've learned one (especially one as simple as ours), this makes it much easier to learn others if you need to do so.

Now use the assembler's **File > Assemble** command. This takes our source program and assembles (translates) it into a new file called **hello.ram** that contains

| Value    | Decimal | Binary | Hexadecimal |
|----------|---------|--------|-------------|
| zero     | 0       | %0000  | \$0         |
| one      | 1       | %0001  | \$1         |
| two      | 2       | %0010  | \$2         |
| three    | 3       | %0011  | \$3         |
| four     | 4       | %0100  | \$4         |
| five     | 5       | %0101  | \$5         |
| six      | 6       | %0110  | \$6         |
| seven    | 7       | %0111  | \$7         |
| eight    | 8       | %1000  | \$8         |
| nine     | 9       | %1001  | \$9         |
| ten      | 10      | %1010  | \$A         |
| eleven   | 11      | %1011  | \$B         |
| twelve   | 12      | %1100  | \$C         |
| thirteen | 13      | %1101  | \$D         |
| fourteen | 14      | %1110  | \$E         |
| fifteen  | 15      | %1111  | \$F         |

Fig.3. Binary and hexadecimal

Listing 1: Program to read button codes and write to the main display

```

CLRCODE: .EQU $10      # Code to clear main display
MAINDISP: .EQU $F031   # Output port to main display
KEYPAD: .EQU $F011    # Input port from keypad

                .ORG $4000      # Set origin to address $4000
                LDA CLRCODE     # Load ACC with clear code
                STA [MAINDISP]  # Store ACC to main display

LOOP:          LDA [KEYPAD]     # Load ACC from the keypad
                CMPA $0F        # Compare accumulator to $0F
                JC [LOOP]       # Jump if C flag is set
                STA [MAINDISP]  # ... else copy ACC to display
                JMP [LOOP]      # Jump to LOOP

                .END           # End of the program

```

the raw instruction and data values that will be processed by our virtual CPU. The contents of this file are in a form called *machine code*, because this is the form that is actually executed by the computer (machine).

Use the assembler's **File > Exit** command to dismiss this application. Next, use the **Memory > Load RAM** command to load the **hello.ram** file that you'll find in the **C:\DIY Calculator\Work** folder into the DIY Calculator's memory. Finally, click the **Run** button to execute this program and see the message "Hello World" appear on the calculator's main display.

## Binary and Hexadecimal

In a moment we're going to create our own program, but before we start, we need to understand that computers store and manipulate data using the binary number system, which comprises just two digits: 0 and 1. One wire (or register bit/memory element) can be used to represent two distinct binary values: 0 or 1; two wires can represent four binary values: 00, 01, 10, and 11; three wires can represent eight binary values: 000, 001, 010, 011, 100, 101, 110, and 111; and so on. As our virtual computer has an 8-bit data bus, this can be used to represent 256 different binary values numbered from 0 to 255 in decimal or %00000000 to %11111111 in binary (where the "%" symbol is used to indicate a binary value).

The problem is that humans tend to find it difficult to think in terms of long strings of 0s or 1s. Thus, when working with computers, we tend to prefer the hexadecimal number system, which comprises 16 digits: 0 through 9 and A through F as shown in Fig.3.

In this case, we use "\$" characters to indicate hexadecimal values. Each hexadecimal digit directly maps onto four binary digits (and vice versa of course). This explains why we noted earlier that our 16-bit address bus could be used to point to  $2^{16} = 65,536$  different memory locations, which are numbered from \$0000 to \$FFFF in hexadecimal.

## The Accumulator (ACC) and Status Register (SR)

There are just a couple more things we need to know before we plunge headfirst into the fray. As illustrated in Fig.4, amongst other things, our CPU contains two 8-bit registers called the *accumulator* (ACC) and the *status register* (SR). (In this context, the term "register" refers to a

group of memory elements, each of which can store a single binary digit.)

As its name implies, the accumulator is where the CPU gathers, or "accumulates", intermediate results. In the case of the status register, each of its bits is called a *status bit*, but they are also commonly referred to as *status flags* or *condition codes*, because they serve to signal (flag) that certain conditions have occurred. We will only concern ourselves with the carry (C) flag for the purposes of our example program.

Since we may sometimes wish to load the status register from (or store it to) the memory, it is usual to regard this register as being the same width as the data bus (eight bits in the case of our virtual system). However, our CPU employs only five status flags, which occupy the five least-significant bits of the status register. This means that the three most-significant bits of the register exist only in our imaginations, so their non-existent contents are, by definition, undefined.

## The Program Itself

For the purposes of this article, we're going to create a simple program that first clears the calculator's main display, and then loops around waiting for us to click one or buttons on the keypad. If any of these buttons are part of the "0" through "9" or "A" through "F" set, we're going to display these value on the main display. In a moment we're going to enter our program as shown in Listing 1. But before we do that, let's walk through this code step-by-step.

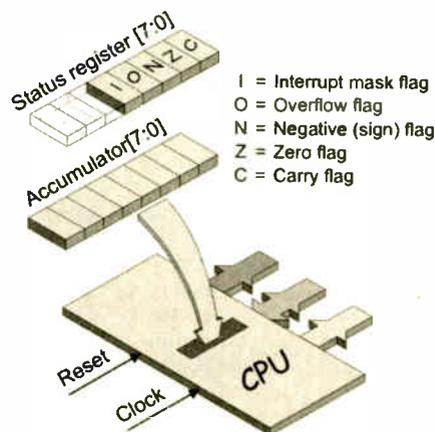


Fig.4. The accumulator (ACC) and status register (SR)

The first thing we do is to declare some constant labels and associated them with certain values using **EQU** ("equate") commands. In the case of this program, the **CLRCODE** label is associated with a hexadecimal value of \$10, which is a special code that will clear the calculator's main display. By comparison, the **MAINDISP** label is associated with the hexadecimal value \$F031, which happens to be the address of the output port that drives the calculator's main display. Similarly, the **KEYPAD** label is associated with the hexadecimal value \$F011, which is the address of the input port that is connected to the calculator's keypad. (Note that everything to the right of a "#" character is treated as a comment and is therefore ignored by the assembler.)

Following the **.EQU** commands we see a **.ORG** ("origin") statement, which we use to specify \$4000 as being the start address in our program. (The reason we use \$4000 is that this is the first address in the DIY Calculator's virtual RAM. When we come to run the program, the DIY Calculator will automatically start at this address.)

Next, we use a **LDA** ("load accumulator") instruction to load our special clear code into the accumulator, and then we use a **STA** ("store accumulator") instruction to copy this value to the main display, thereby clearing it.

Now we find ourselves at the **LOOP** address label, which is where we are going to wait for the user to click on a key. There are a couple of things we need to understand here. First, our virtual calculator's front panel contains an 8-bit register. By default, this register is loaded with a dummy value of \$FF. When we click a button on the keypad, a code associated with that button is loaded into this register. When the CPU reads from the input port connected to the calculator's keypad, it actually reads the value out of this register. Furthermore, the act of performing this read automatically reloads the register with its default \$FF value. Last but not least, the hexadecimal codes associated with the "0" through "9" and "A" through "F" keys are \$00 through \$09 and \$0A through \$0F, respectively (we'd have been extremely silly to make this work any other way).

When we arrive at the **LOOP** label, we use a **LDA** ("load accumulator") instruction to load the accumulator from the memory location pointed to by the **KEYPAD** label. As we previously noted, this is the address of the input port connected to the calculator's keypad. Next, we use a **CPMA** ("compare accumulator") instruction to compare the contents of the accumulator with a value of \$0F.

If the value in the accumulator is larger, the carry (C) status flag will be loaded with 1; this means that the user clicked a button whose code is higher than \$0F, which we don't wish to happen. Thus, if the user did click a button other than "0" through "9" or "A" through "F", the **JC** ("jump if carry") instruction will return the program to the **LOOP** label to await another key. Otherwise, we use a **STA** ("store accumulator") instruction to copy this key code to the main display, and then we use a **JMP** ("unconditional jump") instruction to return us to the **LOOP** label to await another key.

The final statement in the program is a **.END** that, not surprisingly, informs the assembler that its task here is completed.

## Entering and Running the Program

Now we're really ready to rock and roll. If you haven't already done so, launch the DIY Calculator and invoke the assembler. (If you still have the assembler open from running the test case earlier, then use its **File > New** command to create a new source code file.)

Enter the program shown in Listing 1, use the assembler's **File > Save As** command to save this program with the name **mykeytest.asm**, and then use the assembler's **File > Assemble** command to translate your source program into a machine code equivalent called **mykeytest.ram** (if any errors are reported in the status bar at the bottom of the assembler window, debug them and re-assemble the program). Finally, use the assembler's **File > Exit** command to dismiss this application.

Click the **On/Off** button on the calculator interface to power it up. (Alternatively, if the calculator is still powered up from running the test case earlier, then use the main window's **Memory > Purge RAM** command to delete the old program from the calculator's memory.) Next, use the **Memory > Load RAM** command to load the **mykeytest.ram** file that you just created into the DIY Calculator's memory.

Now, click the **Run** button to execute this program and observe that the main display is cleared. The program is now looping around waiting for you to press a key. Try clicking several of the "0" to "9" and "A" to "F" keys and observe the corresponding characters appearing on the main display. Also try clicking some of the other keys (such as "=" and "+") and observe that – due to the way in which we created our program – these are discarded and do not appear on the display.

## But Wait, There's More!

We've really only scratched the surface of what is possible with the DIY Calculator. For example, click the **Reset** button on the calculator's front panel. Make sure the main window fills your screen, and then use the **Display > CPU Registers**, **Display > Memory Walker**, and **Display > I/O Ports** commands to invoke these utilities. As each tool appears, drag it to a clear area on your screen (if you have enough room on your screen, you might also try launching the **Display > Message System** utility).

Now click the **Step** button on the calculator's front panel a few times and watch what happens in the various displays for each click. Next, click one of the number buttons – say the "6" key – and then click the **Step** button a couple more times, again watching the various displays for each click.

Note that you can use the main window's **Help > Contents** command to learn more about what these diagnostic tools do. And if you want to experiment a little further, a slightly more testing example program that uses the DIY Calculator to implement a simple pseudo-random number generator is described on the website. □

## Further Projects

The book, *How Computers Do Math*, is organized in an interesting way. First there are a series of chapters introducing fundamental concepts such as *Subroutines* and *Recursion*. Each chapter is then backed up by a suite of interactive laboratories, each of which details what the reader will learn and how long it will take (typically 20 to 40 minutes each), followed by step-by-step instructions that walk the reader through that lab.

For educators, the CD ROM accompanying the book includes all of the labs as Adobe Acrobat files that can be printed out and used as handouts. Also, all of the illustrations in the book are provided as PowerPoint slides that can be used as the basis for presentations.

The chapters and labs build on each other until, at the end, we have a four function calculator that can input numbers in decimal, convert them into 16-bit binary integers, perform addition, subtraction, multiplication, and division on these binary values, and then present the results from these calculations in decimal on the main display. But this is only a starting point. On the DIY Calculator's website, it is intended to develop this much further by introducing the concept of floating-point values, describing our own simple floating-point format, and then implementing binary floating-point versions of our input, output, and math subroutines. (We are also going to do the same for Binary Coded Decimal (BCD) – check the website for more details.)

And this is still just the beginning, because (in conjunction with schools, colleges, universities, and individual readers), we plan on creating subroutines (with associated documentation) to implement many more math functions. These will be provided on the website for folks to download and experiment with and – hopefully – to say "I can do better than that" and send in their own versions.

As yet another example of something that may interest educators, as a final year project at the beginning of 2005, a team of students at the University of Newcastle upon Tyne, created VHDL models of the DIY calculator and then implemented a physical version of the little scamp using a field-programmable gate array (FPGA) development board. (Details of this project, including the VHDL source files and the project notes, are available on our website.)

So there you have it. Now there is a way to learn about how computers work – and how they do math – that's actually fun and doesn't make your brain ache or your eyes water. We'd love to hear what you think about all of this, so please feel free to email us at [info@DIYCalculator.com](mailto:info@DIYCalculator.com) to share your thoughts and ideas.

The book, *How Computers Do Math* – John Wiley & Sons, ISBN 0471732788 – is scheduled to roll off the printing presses September 2005. Throughout *How Computers Do Math*, we introduce the way in which computers work and walk readers through the process of creating a simple four-function calculator program (add, subtract, multiply and divide) from the ground up. □

# WIRELESS *for the* WARRIOR

## Volume 4 CLANDESTINE RADIO

**A technical history of Radio Communication Equipment in clandestine and special forces operations**

**Volume 4 'Clandestine Radio'** – not only 'spy' equipment but sets used by Special Forces, Partisans, Resistance, 'Stay Behind' organisations, Diplomatic Service, Australian Coast Watchers, RDF and intercept receivers, bugs and radar beacons. The information has been compiled through the collaboration of a vast number of collectors and enthusiasts around the world. Volume 4 includes information on more than 230 sets and ancillaries. It contains 692 pages in hardback format, and features over 850 photographs, 360 line drawings and 440 data tables.

**Volume 1 'Wireless Sets No.1 to 88'** – covers the early radios, prior to the outbreak of World War II, and wartime sets which were never released in large quantities or were abandoned after trials.

**Volume 2 'Standard Sets for World War II'** – provides information in detail of mass-produced Wireless Sets such as No.18, 19, 22 and 38. Additionally included are a number of post-war sets on which development had been started during World War II.



**Volume 3 'Reception Sets'** – the receivers described span the era 1932 to the 1960s, and coverage includes not only reception sets specifically designed or adapted for the British Army, but also sets adopted from other arms (RN and RAF), special receivers, direction finding receivers, army broadcast reception sets, Canadian and Australian army sets, commercial receivers adopted by the army, and army welfare reception sets.

### PRICES INCLUDING POSTAGE

|       | UK     | Europe airmail.<br>Rest of World<br>surface mail | Rest Of World<br>airmail |
|-------|--------|--|--------------------------|
| Vol 1 | £33.00 | £34  | £44                      |
| Vol 2 | £43.50 | £47*   | £55.95*                  |
| Vol 3 | £42.50 | £47  | £55.95                   |
| Vol 4 | £45    | £49*   | £57.95*                  |

\*For delivery to Canada Vol.2 and Vol 4 can only be sent by surface post.

Cheques made payable to Direct Book Service.  
**Direct Book Service, Wimborne Publishing Ltd,**  
 408 Wimborne Road East, Ferndown, Dorset BH22 9ND  
 Tel: 0202 873872 Fax: 0202 874562  
[www.radiobygones.co.uk](http://www.radiobygones.co.uk)

Please send me: **Wireless For The Warrior**

.....(quantity) Vol 1; .....(quantity) Vol 2; .....(quantity) Vol 3; .....(quantity) Vol 4

Name ..... Address .....

Post Code .....  I enclose cheque/postal order/bank draft to the value of £.....

Please charge my Visa/Mastercard/Amex/Diners Club/Maestro

£..... Card No: .....

Card security No: ..... (last 3 digits on the signature strip)

Valid From ..... Expiry Date ..... Maestro Issue No .....

# WIRELESS *for the* WARRIOR

# Ingenuity Unlimited




**WIN A PICO PC BASED OSCILLOSCOPE WORTH £586**

- 5GS/s Dual Channel Storage Oscilloscope
- 50MHz Spectrum Analyser
- Multimeter
- Frequency Meter
- USB Interface.

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC-based oscilloscope could be yours. Every 12 months, Pico Technology will be awarding a PicoScope 3205 digital storage oscilloscope for the best IU submission. In addition a DrDAQ Data Logger/Scope worth £59 will be presented to the runner up.

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas *must be the reader's own work and must not have been published or submitted for publication elsewhere*. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and include a full circuit diagram showing all component values. **Please draw all circuit schematics as clearly as possible.** Send your circuit ideas to: *Ingenuity Unlimited*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. (We do not accept submissions for IU via email). Your ideas could earn you some cash and a prize!
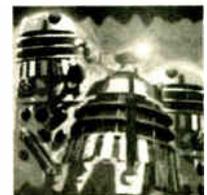
## Cybervox Light Interface – *Enlightened Extermination*



**D**ALEK aficionados will know that when these diabolical creatures speak, a set of head mounted lights flash in sympathy with each spine-chilling word spoken. The circuit shown in Fig.1 is designed to be attached to the *EPE Cybervox* (July '05) and will flash filament lights whenever a word is spoken.

The voice signal is picked from the *Cybervox* board at connection point 19 (junction of C16 and the signal side of

VR5). The signal is passed via capacitor C1 to an amplifier formed around an LM351 op.amp. The voltage gain of this amplifier is adjustable from about  $\times 10$  to  $\times 1000$ . The gain level set by VR1 forces the output of the amplifier to swing between the supply rails (referred to as clipping) – a situation which is normally to be avoided.

In this application, however, these large voltage swings are usefully rectified by

D1 and D2 and used to charge capacitor C4. As soon as the voltage across C4 reaches 0.6V, transistor TR1 conducts, turning on l.e.d. D3. Power transistor TR2 is used to switch more demanding loads such as filament lights and will only require a heatsink if more than two bulbs are wired in parallel.

**Mike Boyden,  
Binfield, Bracknell**

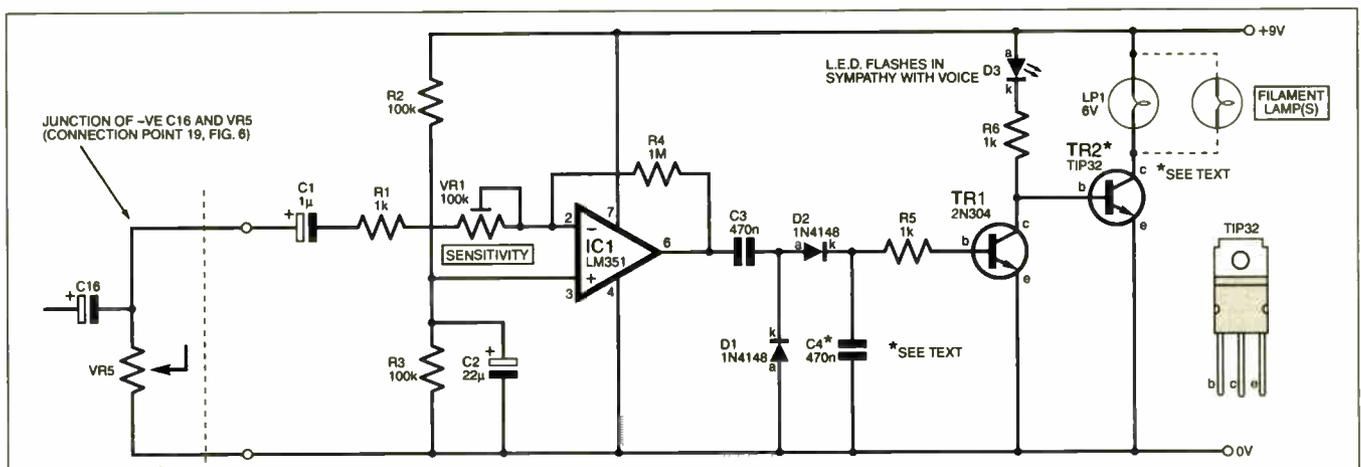


Fig.1. Circuit for the add-on Cybervox Light Interface for the EPE Cybervox Dalek voice emulator project – July '05 issue

# Theremin Volume Control – *Waving Soundly*

**I**N the *EPE Theremin* (Oct '04), Robert Penfold commented that his method for volume control gave a somewhat abrupt variation. Fig.2 shows an alternative, which still adheres to the concept of using hand capacitance to change the volume, but has the advantage of a nice gradual action whilst still allowing a tremolo effect to be obtained by fluttering the hand or fingers.

The circuit is simple, easy to set up and has a low component count. As it was designed to be a direct replacement for Robert's volume control, it only requires a single supply of 9V, and it could well be useful in other applications.

The design is based on an ICM7556 dual timer, with one half functioning as an astable oscillator and driving the other, which is connected as a monostable pulse generator. The hand capacitance sensor is an aluminium plate, 18cm x 10cm as a rough match to hand size. This is mounted in the vertical plane and with the 10cm side vertical, and is situated at one side of the instrument case behind a 6mm thick sheet of MDF, which gives a convenient lower limit for hand proximity.

The plate is connected directly to the 7556, no isolating capacitor being needed. No specific timing capacitor is used either, and the inherent stray circuit capacitance gave a suitable frequency of about 25kHz with the 1.2MΩ timing resistor, R1. This arrangement maximises the hand capacitance effect, for greatest sensitivity.

In use, the monostable is adjusted by preset VR1 to have a period slightly shorter than that of the oscillator when a hand is not near the sensor plate, whereupon the output voltage is as shown in Fig.3a, changing to that in Fig.3b and then Fig.3c as the oscillator period progressively lengthens when a hand nears the plate.

This waveform is then inverted by a CA3140 op.amp, whereupon the time-averaged output voltage is low for the Fig.2a waveform and increases as a hand nears the sensor. Output averaging is performed by the R6, C4 filter, thus providing the steady voltage needed to supply control current to pin 5 of the original CA3080 gain-control amplifier (IC4).

The CA3140 was chosen not for its high

input impedance but for its good slewrate characteristic and because its output bottoms at only a few millivolts above the negative rail, which is necessary to enable the CA3080 gain to be reduced to zero for total sound cut-off.

For optimum operation, it is important that VR1 is adjusted until zero sound is only just achieved and it is convenient therefore to have it as a front panel control. The Theremin note then becomes audible when a hand approaches within some 12cm to 15cm from the sensor plate.

If VR1 is turned much below the setting for zero sound output then the

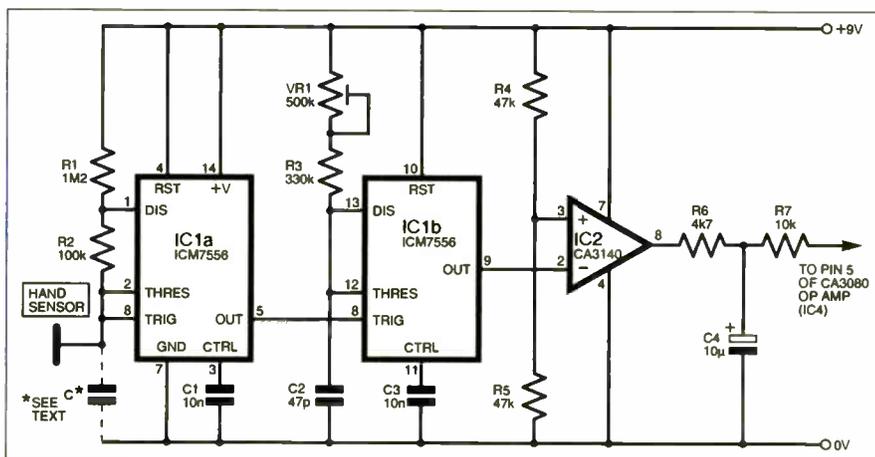


Fig.2. Theremin Volume Control circuit diagram

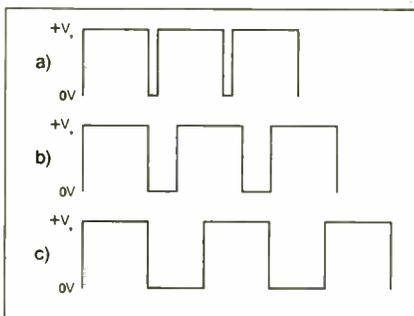


Fig.3. Monostable output waveform

monostable period will exceed that of the astable oscillator. This means that it will only trigger on alternate cycles of the oscillator, resulting in an output waveform having about a 50:50 mark-space ratio and hence giving a considerable sound output in the absence of a hand near the sensor.

This is a useful characteristic, simplifying any setting-up work on the Theremin tone production circuitry and also obviating the need for i.e.d. indication of control circuit functioning.

Tony Read, Rugby

## Voltage Splitter – *Single Bias*

**T**HE commonly used method to split a single supply is to use an op.amp and two resistors, as shown in Fig.4. Using an LM386 audio i.c. instead of the op.amp, the resistors are not required, see Fig.5. This saves on board space. Of 20 LM386s tried, 15 of them split the voltage to within 5%. The worst was 8.4%. This was sufficient for my application and would probably be so for most applications.

If more accurate splitting is required this

can be done by connecting one or the other input to the negative rail via a 47kΩ pot (Fig.6). With most examples the split could be set precisely. With a 12V supply and loading only the one side with a 200Ω resistor (30mA) caused less than 0.5% change in the split (regulation). This is better performance than the op.amp solution can provide.

Op.amps are normally limited to 20mA

of imbalance current. It is quite possible that other more robust audio amp i.c.s, such as the TDA2003, can be used if a more rigid split and a higher imbalance current is required. The LM386N-4 will handle 18V. The LM386N-1 has a quiescent current of 8mA at 12V. This should not be too onerous even for a battery application.

Neville Frewin,  
Fontainebleu, South Africa

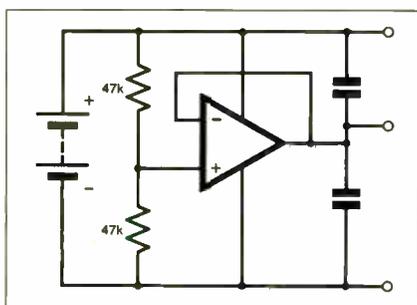


Fig.4. Splitter using an op.amp

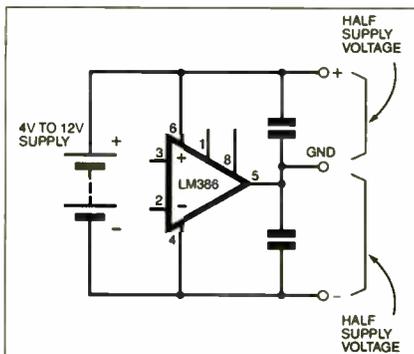


Fig.5. Splitter using an LM386

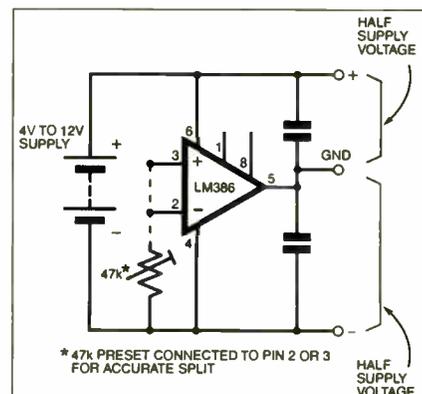


Fig.6. An LM386 splitter with trimmer

# Pulsed Motor Speed Controller – Over and Out

**T**HE circuit diagram shown in Fig. 7 was built to keep the speed of a motor constant with varying load conditions. It works by driving the motor with a train of 12V pulses, and varying the mark/space ratio of these pulses to control its speed. This method is reckoned to be more efficient than using a linear regulator because the series pass transistor dissipates much less power.

The speed of the motor is determined by measuring the voltage developed across it when no power pulse is being applied (this is effectively using the motor as a generator) and comparing its output voltage to a reference.

The 555 timer, IC1, is configured in its astable mode with capacitor C3 and resistor R8 determining the “output low” pulse width. This is of constant duration (about 7ms) and drives transistor TR1, via resistor R2, to feed a 12V power pulse to the motor M1.

The “output high” duration (“the dead time”) is determined by the value of the timing capacitor charge current. This charge current is itself determined by the voltage developed across the motor when no power is being applied to it. This motor voltage is compared by comparator TR2 to a 4.7V reference voltage provided by Zener diode D2.

So, if the voltage across the motor is less than about 3.5V transistor TR2 conducts and turns on TR3, its collector current charging timing capacitor C3. Resistor R7 limits the maximum collector current of TR3 and so limits the minimum “dead time” of the power pulses.

## Switch-On

At switch-on, the voltage developed across the motor between the power pulses is zero so transistors TR2 and TR3 both conduct heavily and timing capacitor C3's charge time is very short. As the motor accelerates to its target speed and its “generated” voltage increases, TR2 and TR3 both reduce their conduction, increasing the time it takes to charge C3 and so the “dead time” increases.

Eventually, an equilibrium is reached when the voltage generated across the motor is about the same as the reference voltage minus the voltages dropped across TR2's emitter-base junction and diode D1 junction. Diode D1 protects TR2's emitter-base junction from reverse bias during the 12V power pulse to the motor. During the power pulse both TR2 and TR3 are switched off so they have no effect on C3's discharge current.

Capacitor C1 reduces the voltage “spike” developed across the motor produced by its internal inductance when the 12V pulse ends, and is most important to protect transistor TR1. Capacitor C2 provides a “soft start” for the motor by making the reference voltage build up slowly on switch-on; it can be omitted or increased in value as desired.

If the circuit is unstable, for instance, the motor is continually starting and stopping, increase the value of resistor R4 to reduce the system gain until stability is achieved.


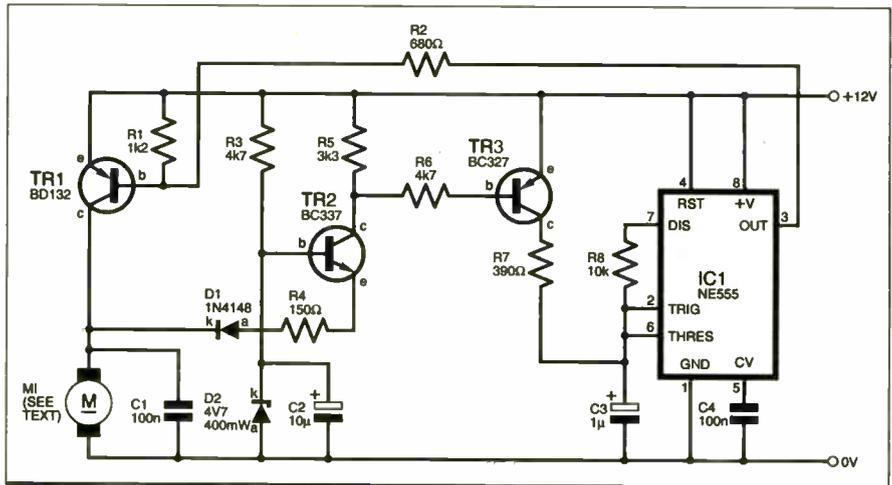


Fig.7. Circuit diagram for the Pulsed Motor Speed Controller

Fig.8. General set up of garage door lock from inside of garage

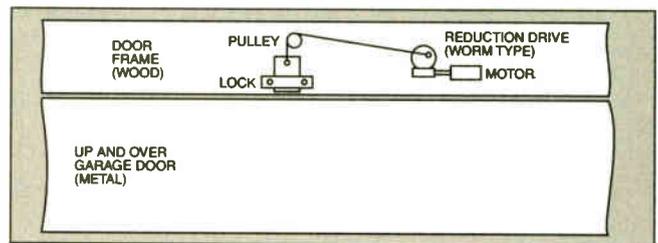

## Up-and-Over Lock Out

I use the circuit with a motor and worm-type reduction drive salvaged from an old VCR (the cassette loading mechanism) to form part of a lock mechanism for an up-and-over garage door, see Fig.8. All I had to do was add a small bolt through the output gear so that I could fasten the drive cord to it.

The drive cord is “shock leader” for fishing lines – I do not know what that is used for but I know that it has a 45lb breaking strain rating, and its waterproof (the garage gets damp in the winter).

The lock plates are both 1/4in. aluminium and so rustproof and strong enough for the job. As can be seen from Fig.8, the motor lifts and lowers the lock plate thereby opening and closing the door lock.

In practice, it works fine from no load to stall, though it is a bit juddery at low load. If the judder is too great, reduce the value of capacitor C3. The motor has a stall current of about 600mA, and it should be ensured that the series pass transistor TR1 is still saturated under such conditions – reduce the value of resistor R2 if necessary to ensure that this is the case.

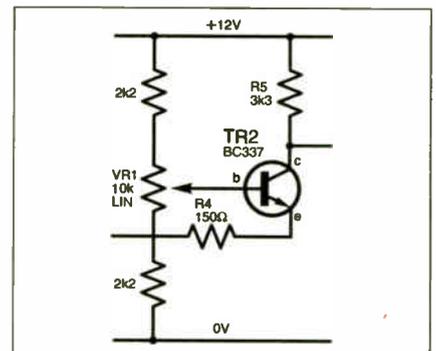


Fig.9. Alternative base bias arrangement for transistor TR2 to give variable speed

The circuit should work fine as a variable speed controller by varying the reference voltage on TR2's base (b), though judder may be encountered at low speeds and with low loads unless the timing capacitor C3 is reduced in value. Suitable circuit alterations for this are shown in Fig.9. It must be stressed that this circuit modification is untested.

Peter A. Tomlinson,  
Hull, East Yorkshire.

## INGENUITY UNLIMITED BE INTERACTIVE

IU is your forum where you can offer other readers the benefit of your Ingenuity. Share those ideas, earn some cash and possibly a prize.






**the Atlas DCA55**

- Automatically analyse most 2 and 3 leaded semiconductors.
- Automatically identify all leads, just connect any way round!
- Measures lots of parameters too such as gain,  $V_{BE}$ ,  $V_{GS}$ , etc...

DCA55  
**£49**

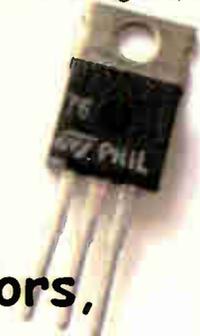

LCR40  
£69.00

DCA55  
£49.00

SCR100  
£99.00


Passive components, semiconductors,  
power devices, network cabling  
**Choose your perfect analyser**

**New Low Prices!**

limited time only

**the Atlas LCR40**

- Automatically identify Inductors, Capacitors and Resistors.
- Inductors from 1 $\mu$ H to 10H.
- Capacitors from 1pF to 10,000 $\mu$ F.
- Resistors from 1 $\Omega$  to 2M $\Omega$
- 1% Basic accuracy.
- Automatic frequency selection.

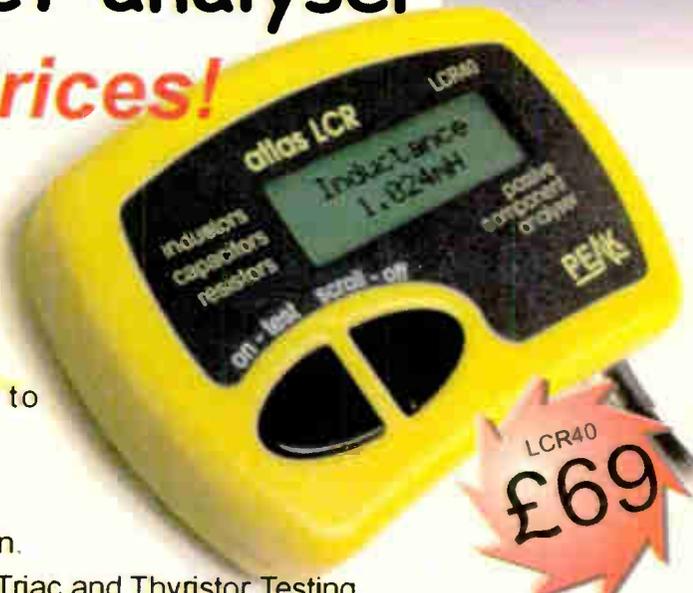

LCR40  
**£69**

**Triac and Thyristor Testing**

**ESR Measurement**



model ESR60

**£79**

**£99**



model SCR100

**Cat5 Cable Testing**



model UTP05

**£79**

"Star Pack"  
LCR and DGA  
in carry case  
£118.00

Carry cases  
£15.00

SMD Tweezer  
Probes for LCR  
£19.00

Spare Battery  
£1.75

accessories & carry cases



[www.peakelec.co.uk](http://www.peakelec.co.uk)

all prices include UK Delivery and VAT

Don't just test it...  
**...Analyse it!**

# Net Work

Alan Winstanley



**L**AST month's *Net Work* column highlighted AuthSMTP (see [www.authsmtp.net](http://www.authsmtp.net)), a third party mail service that promises to solve most outgoing email problems. This can be a perfect solution for users having domain mail relaying problems, or other issues such as a regular ISP's mail server being blacklisted due to spam campaigns.

In use, AuthSMTP's service is holding up extremely well and has been entirely trouble free for the past three months, offering superior performance to the writer's broadband service provider, although the writer's Eudora E-mail software was problematic initially. A 14-day trial of AuthSMTP can be ordered online.


## They're Spying On Us

This month we revisit the thorny topic of dealing with spyware and we take a look at some of the latest and most popular anti-spyware programs. Spyware is said to affect 90% of Windows PCs and can be dropped onto a computer in a number of ways. It may be included in some trial software, or it could originate from certain web pages or other computer files or downloads. Spyware programs reside on a host computer such as a PC and may be used to transmit credit card numbers or login details to a third party, or may have marketing-related purposes instead. They may hijack your web browser home page as well.

Some of the worst examples of spyware involve elements of "social engineering" which play mind-games by raising uncertainties in the minds of users and tricking them into clicking through to another web site. For example, a pop-up might appear that warns you that your PC has an infection (which it has: it's the pop-up itself); clicking through might take you to a cheap utility software.

In a recent example, the author became increasingly irked to find a pop-up advert appearing every time he visited eBay's web site. By using the free spyware removal tool Ad.Aware (highlighted in May 2005 *Net Work*, see [www.lavasoft.de](http://www.lavasoft.de)), some spyware was detected, but every time it was deleted by Ad.Aware, the pop-up advertisement re-appeared. Only by using a whole armory of anti spyware tools was the problem eventually cured.

The pop-up was also deceptive, as it resembles an authentic dialogue box that encourages neophyte computer users to click a "Next" button. The only redeeming grace was the unobtrusive warning link along the bottom of the pop-up. A similar pop-up also appeared, this time with a logo for "Casale Media". This Internet marketing company claims to operate one of the world's largest online media marketing networks, with 140 million "unique users" per month.

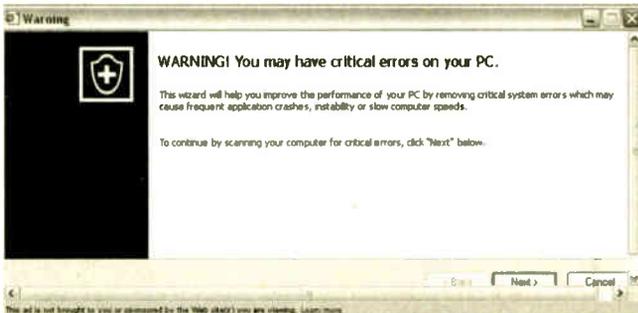

Example of a spyware-generated pop-up

## Not Us, Guv'nor

The eBay problem was eventually tracked down to "People On Page" spyware advertising. I asked Casale Media to comment on this form of persistent pop-up advertising. Casale assured me that they do not have the ability to target anyone's computer or put any software onto their machine.


They added that they do not support pop-up advertisements and they specify that any site hosting adverts must only place pop-uppers, and the amount of advertisements displayed to individual users is restricted to one per day. Casala blamed the persistent appearance of pop-ups on the presence of third party adware, as the Casale network only placed pop-uppers – which appear after a short duration, underneath the main target web site.

The source of the People on Page spyware could not be pinpointed, and it proved troublesome to remove (it appeared to defeat AdAware SE), demonstrating the wisdom of using a range of spyware removal tools to hopefully cure any problems.

Large portal sites such as [www.download.com](http://www.download.com), [www.shareware.com](http://www.shareware.com), [www.snapfiles.com](http://www.snapfiles.com) and TUCOWS (The Ultimate Collection of Windows Software at [www.tucows.com](http://www.tucows.com)) are good places to start searching for utilities. Current anti-spyware contenders worth considering include: Paretologic's Xoftspy ([www.xoftspy.co.uk](http://www.xoftspy.co.uk), free download, \$39.95 one-time fee for the full version), the excellent Spyware Doctor ([www.pctools.com](http://www.pctools.com) £19.95) and the ubiquitous Spybot Search and Destroy (donationware) from [www.safer-networking.org/en/download/](http://www.safer-networking.org/en/download/).

Webroot offers the acclaimed Spysweeper for \$29.95 per year (free trial available from [www.webroot.com](http://www.webroot.com)). Other spyware tools to consider are Sunbelt Software's CounterSpy which has a 15 day trial and costs \$19.95 per year. See [www.sunbelt-software.com/CounterSpy.cfm](http://www.sunbelt-software.com/CounterSpy.cfm) for their take on Microsoft's own Anti Spyware tools, which is available in beta from Microsoft via <http://tinyurl.com/47cus>.

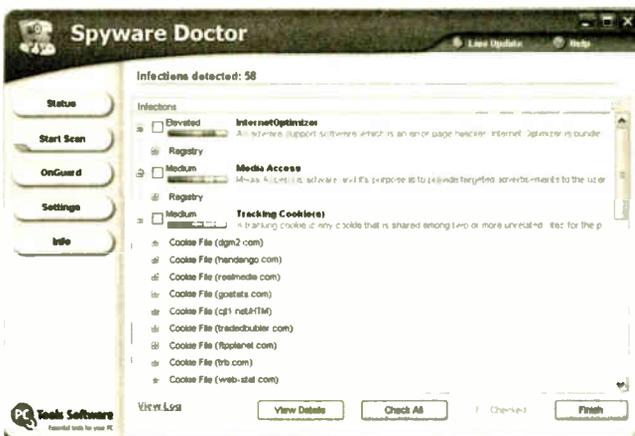Next month, I'll be looking at ways of handling web site passwords and logins, without having to resort to memory or some dog-eared notebook (that you lost anyway). If you have any comments, suggestions or feedback please email them to the writer at [alan@epemag.demon.co.uk](mailto:alan@epemag.demon.co.uk)



Just one of many anti spyware programs

# PIC N' MIX

JOHN BECKER

Our periodic column for your PIC programming enlightenment

## More on using a DS1267 dual digital potentiometer with a PIC

**L**AST month we examined the basics of using the DS1267 dual digital potentiometer chip. We now look at some further aspects of its use.

### Stacked Configuration

The potentiometers can be connected in series as in Fig.5. This stacked configuration allows the user to double the end-to-end resistance and the number of steps from 256 to 512 (9-bit resolution).

The wiper output for the stacked pots is taken from the Sout pin, which is the multiplexed output of the wiper of pot 0 (W0) or pot 1 (W1), as governed by the stack select bit (bit 0). If bit 0 = 0, the output to Sout will be that of W0. If bit 0 = 1, the Sout output will be from W1.

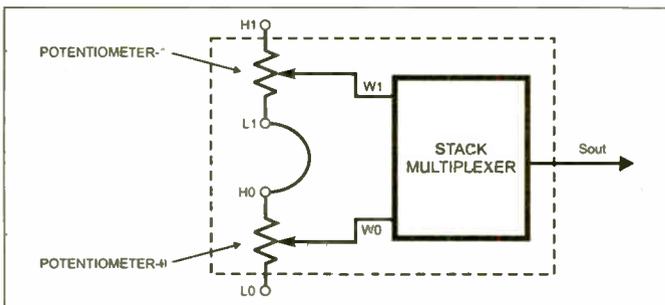


Fig.5. Stacking the pots

### Cascade Operation

Multiple DS1267s can be daisy-chained as in Fig.6. As a data bit is entered into the shift register, a bit will appear at the Cout output. The stack select bit will always be the first out at the beginning of a transmission. The Cout pin is always active regardless of the state of RST. This allows the shift register to be read without changing its value.

The Cout output can be used to drive the DQ input of another DS1267. When connecting multiple devices together, the total

number of bits transmitted must always be 17 times the number of DS1267s in the daisy-chain.

An optional feedback resistor of between 2k and 10k can be placed between the Cout terminal of the last device and the first DQ input. This allows the PIC to be read as well as written to, or to circulate data through the daisy-chain.

When reading data via the Cout pin and feedback resistor, the PIC must set its pin that controls the DQ line into a high-impedance (input) state. When RST is taken high, bit 17 is present on the final Cout pin, which is fed back to the first DQ input through the resistor. The first DQ pin's status can then be read by the PIC. By successive clocking of the CLK line, the register contents can be read and stored into PIC registers allocated by the user for the purpose.

When the CLK input is then taken from low to high, bit 17 is loaded into the first position of the DS1267 register, and bit 16 becomes present on final Cout and first DQ pins. After 17 bits (of 17 times the number of DS1267s in the daisy-chain), the data will have been shifted completely around and back to its original position. When RST is taken low to end data transfer, the same value as before the read occurred is loaded into the W0, W1 and stack select bit registers.

### Cascading Demo

The demo code discussed last month simply illustrates the writing of data to a single DS1267. It can also be used with two or more DS1267s cascaded, as in Fig.7. The control code now requires pot values

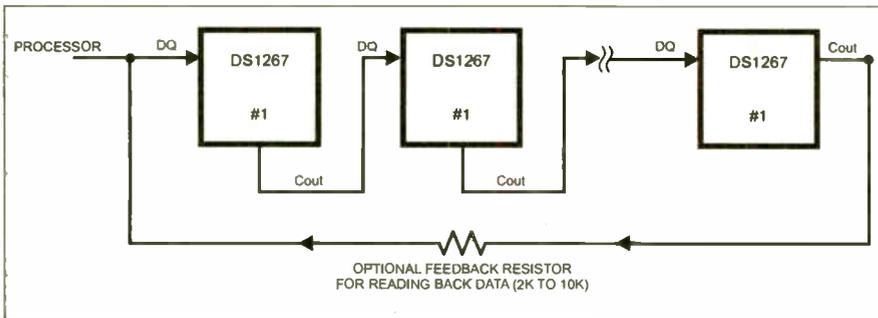


Fig.6. Daisy-chaining several DS1267 devices

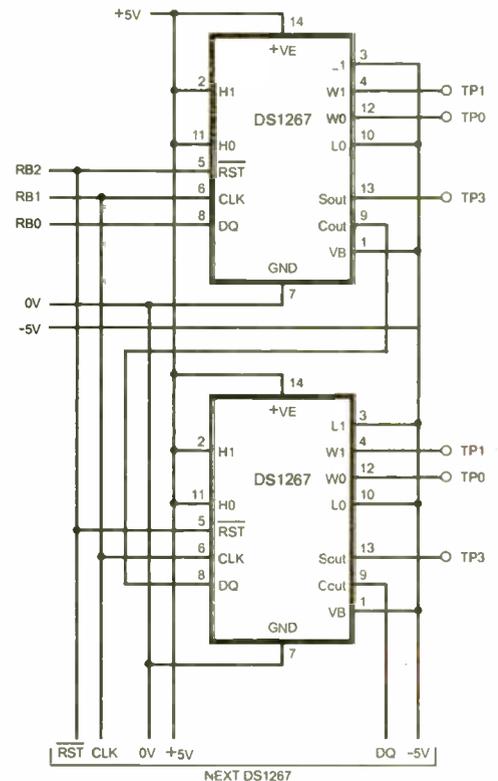


Fig.7. Cascading demo circuit

appropriate to each pot in the chain. These codes are sent in the same way as with one DS1267, but as a serial stream of  $17 \times$  the number of DS1267s (two in this case).

By deleting the goto ENDPOT command the demo sends data to both chips. Note though that as written the code sends the first data group to the second chip, and the second group to the first chip. The ramping rate for the second pot group is higher than for the first.

### Practically Speaking

In reality, it will be unlikely that repetitive looped control of one or more DS1267s would be required, unless ramped waveforms at various frequencies and slope angles were required.

Instead, it is more likely the pot wiper values may only need to be changed periodically. For this the PIC would only set particular values into the POTVALx registers immediately prior to the sending routine being called (call SETPOTS). Then at the end of that routine, the goto SETPOTS command would be replaced by a single return command.

## Applications

The diagrams in Fig.8a and Fig.8b show two ways in which the DS1267 can be used in a circuit. In Fig.8b, the required pot is connected between the +5V and -5V lines. The wiper is then connected to the non-inverting input of a unity-gain (buffering) op.amp. The op.amp output can then be used to control some other aspect of the circuit.

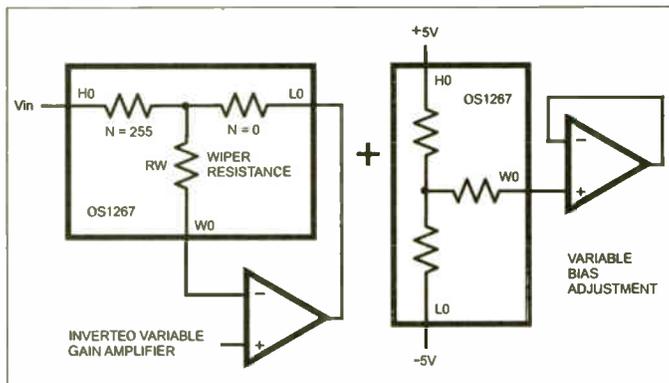


Fig.8. Using a DS1267 with an op.amp

Secondly, Fig.8a shows how the gain of an op.amp circuit can be amended by a DS1267 pot. The gain of the circuit is set by the relative resistance values at either side of the pot's wiper. A further implementation of this idea is shown in the full datasheet.

In a forthcoming *EPE* project, a DS1267 is used with a single op.amp to control not

only the gain, but also the offset bias of the stage. In that application, the setting of the pots is performed via a PC coupled to the controlling PIC.

It should be noted that any op.amp used as above should be defined as a rail-to-rail device.

## Data Readback

A use for reading back data from a DS1267 has so far not been imagined. But should you wish to do so, a loop similar to that in SETPOTS should be written, in which the PIC's data pin is set as an input. Three registers are then needed, one each for the pot data and one for the stack bit. The feedback resistor referred to earlier must be added. The process would then be along the lines of the logic in Table 2.

## Meter Monitoring

If an oscilloscope is not available, the W0, W1 and Sour waveforms can be monitored via a multimeter. This requires that a delay loop is put into the code, so that the analogue voltages at the three pins can be followed on the meter. As it stands, the

Table 2. Data Readback Logic

```

set RST high
read data (DQ) bit and store it as the
  stack bit
send clock high then low
read data bit
store it into bit 0 of PIC's first pot
  register
rotate that register left by one place
send clock high then low
repeat process eight times
repeat the last eight reads for the
  second pot register
set RST low
use the readback values as required
  
```

Listing 2

```

DELAY: decfsz COUNTER0,F
goto DELAY
decfsz COUNTER1,F
goto DELAY
return
  
```

demo code is clocked at too fast a rate for a meter.

Such a loop could consist of a routine such as that in Listing 2. This could be called by the command `call DELAY` immediately prior to the final command `goto SETPOTS`. This delay code would slow the wiper code changing routine by a factor of  $256 \times 256 = 65536$ . Other more sophisticated delay routines could be used instead, for example by using the PIC's timer to set the delay length.

ANDRE LAMOTHE'S  
**XGAMESTATION**  
LEARN STEP-BY-STEP HOW TO DESIGN  
AND BUILD YOUR OWN VIDEO GAME CONSOLE!

Design inspired by the Atari 800/2600,  
Sinclair ZX Spectrum, Apple II & Commodore 64!

Complete Package eBook Integrated IDE

SX52 CPU  
80 MIPS!

OPEN SOURCE!

**FEATURES:**

- Great for Hobbyists AND Students!
- Complete Software Development Kit!
- eBook on Designing the XGS Console!
- Parallax SX-Key Compatible!
- Fully Assembled XGS Micro Edition Unit!
- The Fun Way to Learn Embedded Systems!

PAL & NTSC  
COMPATIBLE!

WWW.XGAMESTATION.COM  
SUPPORT@NURVE.NET | PH 925.736.2098 (USA)

**Lichfield Electronics**  
For electronic kits, components and tools

**Aoyue 909 All in one**  
The 909 repair system contains a high quality closed circuit 0 to 15V 1.5A power supply, 35W temp controlled 24V soldering iron (200-480C) and a 450W 100-500C Hot air gun for SMD work  
**£99.99**

**Aoyue 936 Soldering Iron**  
This temperature controlled 35W soldering iron Has a range of between 200C-480C and comes complete with spare heating element and iron holder. Very simple to use and only **£24.99**

**WWW.LICHFIELDELECTRONICS.CO.UK**

**Work station & 0-15V PSU**  
The Aoyue 398 Power Source Platform is a combined 0-15V closed circuit power supply & work table with stepless PCB clamps.  
**£34.99**

**Autoranging RS232 multimeter**  
The UT60 is an autoranging multimeter with RS232 interface enabling readings to be displayed on a PC. Features include fused 10A range, frequency, capacitance, data hold, selectable auto/manual ranging, continuity buzzer and full icon display. **£64.99**

Open Mon-Sat: 9.00-5.00 Sun: 10.00-4.00  
Lichfield Electronics, The Corn Exchange, Conduit Street,  
Lichfield, Staffordshire, WS13 6JU

**AVIT Research**

www.avitresearch.co.uk

USB has never been so simple...



Special Price  
**£29.99**

**USB to TTL Serial Cable**

- Simple and Easy way to give USB support to your designs
- Connects directly to microcontroller UART or I/O pins
- PC communicates as a standard serial device
- All circuitry integrated into sleek moulded USB plug
- 4-way connector (Gnd, RX, TX and +5v)
- Supplied with PC drivers, example code and tutorial
- Special Price of only £29.99 including VAT

AVIT Research also supply:

**I<sup>2</sup>C Bus Tool** - Allows your PC to monitor and control the I<sup>2</sup>C Bus

- Invaluable tool for developers using the I<sup>2</sup>C Bus
- See website for full details



www.avitresearch.co.uk

info@avitresearch.co.uk

0870 741 3636

**Build Your Own Weather Station**



- ▶ Measure Wind Speed
- ▶ Measure Wind Direction
- ▶ Measure Temperature
- ▶ Easy Build Kit
- ▶ FREE Software
- ▶ USB or RS232
- ▶ Optional Humidity Module
- ▶ Optional Pressure Module
- ▶ Optional Rainfall Gauge
- ▶ Simple 1-wire® connection
- ▶ Build and add your own devices

|                     |     |
|---------------------|-----|
| Weather Starter Kit | £59 |
| RS232 Interface     | £25 |
| USB Interface       | £29 |
| Humidity Module     | £39 |
| Pressure Module     | £49 |
| Rainfall Gauge      | £59 |

Prices exclude VAT and delivery

For more information, manuals and downloads on this and other interesting products see [www.audon.co.uk](http://www.audon.co.uk)

**audon Electronics**

www.audon.co.uk | +44 (0)115 925 8412 | Fax +44 (0)115 925 9757

**PCB-POOL**

SERVICING YOUR COMPLETE PROTOTYPE NEEDS

- Prototypes at a fraction of the cost
- Industry standard quality
- Tooling and setup included
- Follow up series runs
- Any contour
- CAM / CAD consulting
- Fr4 1.6mm, 35µm Cu

PRICE CHECK!  
**1 EUROCARD** 35µm  
+ Tooling  
+ Photoplots  
+ VAT

= £ 29.89\*

\*Shipping rates may vary. Price = 0.49

**€ 49**

**FREE**



Freephone

**0800-389 9560**

Simply send your files and order ONLINE

**WWW.PCB-POOL.COM**



**Test and Measurement Solutions**

**£128**

**DS10000** "Signal" Oscilloscope "Storage"

2 x 1MS/s Input Channels + waveform generator output

**£149**

**PicoScope** "Storage" Oscilloscope "Storage"

40MS/s sample rate  
Removable probe tip with BNC adapter

**£199**

**MSO-100** "Storage" Oscilloscope "Storage"

16 Channels  
500MS/s max sample rate

**USB Instruments**  
PC Oscilloscopes & Logic Analyzers

Our range of PC Instruments may be budget priced, but have a wealth of features normally only found in more expensive instrumentation. Our DS10000 and PicoScope oscilloscopes have high-speed digital triggering including related functions and come with the EasyScope oscilloscope application analyzer software and the EasyLogic digital application software. Our EasyLogger data logging software, the new Windows UI based easyconnect for 3rd party software interfacing to our boards. Our ART16 and ART16 Logic Analyzers feature 16th capture channels of data at a blazing 300MS/s sample rate in a compact enclosure. Detailed specifications and software downloads for these products can be found at [www.usb-instruments.com](http://www.usb-instruments.com)

**EasySync Ltd**

373 Scotland Street  
Glasgow G5 3US  
United Kingdom

Tel: 0141 418 0181  
Fax: 0141 419 0110

Web: <http://www.easysync.co.uk>  
E-Mail: [sales@easysync.co.uk](mailto:sales@easysync.co.uk)

\* Prices shown exclude PP and VAT where applicable

We can supply back issues of *EPE* by post, most issues from the past three years are available. An *EPE* index for the last five years is also available at [www.epemag.co.uk](http://www.epemag.co.uk) or see order form below. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photocopy of any *one article* (or *one part* of a series) can be purchased for the same price. Issues from Nov. 98 are available on CD-ROM – see next page – and issues from the last six months are also available to download from [www.epemag.com](http://www.epemag.com).

Please make sure all components are still available before commencing any project from a back-dated issue.

## DID YOU MISS THESE?

### JUNE '04 Photocopies only

**PROJECTS** • PIC Quickstep • Crafty Cooling • MIDI Synchronome • Body Detector Mk2.  
**FEATURES** • Clinical Electrotherapy • Ingenuity Unlimited • Teach-In 2004 – Part 8 • Interface • Circuit Surgery • Techno Talk • PIC-N'-Mix • Net Work – The Internet Page.

### JULY '04 Photocopies only

**PROJECTS** • Portable Mini Alarm • Bongo Box • Hard Drive Warbler • EPE PIC Magnetometry Logger-1.  
**FEATURES** • Making Front Panel Overlays • Practically Speaking • Teach-In 2004 – Part 9 • Ingenuity Unlimited • Circuit Surgery • Techno Talk • PIC-N'-Mix • Net Work – The Internet Page.

### AUG '04

**PROJECTS** • EPE Scorer • Keyring L.E.D. Torch • Simple F.M. Radio • EPE PIC Magnetometry Logger – 2.  
**FEATURES** • PIC To PS/2 Mouse and Keyboard Interfacing • Techno Talk • Circuit Surgery • Teach-In 2004 – Part 10 • Interface • Ingenuity Unlimited • PIC-N'-Mix • Net Work – The Internet Page.



### SEPT '04

**PROJECTS** • EPE Wart Zapper • Radio Control Failsafe • Rainbow Lighting Control • Alphamouse Game.  
**FEATURES** • Light Emitting Diodes – Part 1 • High Speed Binary-To-Decimal For PICs • Practically Speaking • Ingenuity Unlimited • Techno-Talk • Circuit Surgery • PIC-N'-Mix • Network – The Internet Page

### OCT '04 Photocopies only

**PROJECTS** • EPE Theremin • Smart Karts – Part 1 • Volts Checker • Moon and Tide Clock Calendar.  
**FEATURES** • Light Emitting Diodes – 2 • Circuit Surgery • Interface • Ingenuity Unlimited • Techno Talk • PIC-N'-Mix • Network – The Internet Page • ROBOTS – Special Supplement

### NOV '04

**PROJECTS** • Thunderstorm Monitor • M.W. Amplitude Modulator • Logic Probe • Smart Karts - 2.  
**FEATURES** • Light Emitting Diodes-3 • Floating Point Maths for PICs • Ingenuity Unlimited • PE 40th Anniversary • Circuit Surgery • Techno Talk • PIC-N'-Mix • Net Work – The Internet Page.

### DEC '04 Photocopies only

**PROJECTS** • Super Vibration Switch • Versatile PIC Flasher • Wind Direction Indicator • Smart Karts - 3.  
**FEATURES** • Light Emitting Diodes-4 • Ingenuity Unlimited • Circuit Surgery • Interface • PIC 'N' Mix • Techno Talk • Net Work – The Internet Page • INDEX Vol. 33.

### JAN '05

**PROJECTS** • Speed Camera Watch • Gate Alarm • Light Detector • Smart Karts - 4.  
**FEATURES** • Practically Speaking • 32-Bit Signed Integer Maths for PICs • Ingenuity Unlimited • Circuit Surgery • Techno Talk • PIC 'N' Mix • Picoscope 3205 Review • Net Work – The Internet Page



### FEB '05

**PROJECTS** • PIC Electric Mk2 Pt1 • Sneaky • Sound Card Mixer • Smart Karts - 5.  
**FEATURES** • Interface • Circuit Surgery • Ingenuity Unlimited • Techno Talk • PIC 'N' Mix • E-Blocks and Flowcode V2.0 Reviews • Net Work – The Internet Page

### MAR '05

**PROJECTS** • Cat Flap • Stereo Headphone Monitor • PIC Electric Mk2 Pt2 • Smart Karts - 6 • Bongo Box.  
**FEATURES** • TK3 Simulator and PIC18F Upgrade • Circuit Surgery • Ingenuity Unlimited • Techno Talk • PIC 'N' Mix • Practically Speaking • Net Work – The Internet Page

### APR '05

**PROJECTS** • Spontaflex Radio Receiver • Safety Interface • Fridge/Freezer Door Alarm • Smart Karts - 7.  
**FEATURES** • Back To Logic Basics - 1 • Circuit Surgery • Ingenuity Unlimited • Interface • PIC18F Microcontroller Family Introduction • Techno Talk • Net Work – The Internet Page

### MAY '05


**PROJECTS** • Crossword Solver • DAB Radio Aerial • 20W Amplifier Module • Smart Karts - 8 • Water Level Detector • Burglar Alarm  
**FEATURES** • Back To Logic Basics - 2 • Circuit Surgery • Ingenuity Unlimited • Passive Component: Testing • Practically Speaking • Techno Talk • Net Work – The Internet Page

### JUNE '05

**PROJECTS** • PIC Ultrasonic Radar • Radio Control Model Switcher • Super-Ear Audio Telescope • Electronic Scarecrow • Digital Lock  
**FEATURES** • Catch the Wave (Tsunami) • Back To Basics – 3 • Digital TV Switchover • Programming PIC 18F Interrupts • Circuit Surgery • Interface • Ingenuity Unlimited • Net Work – The Internet Page
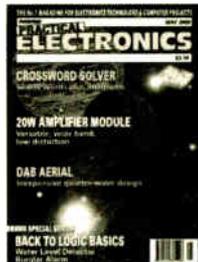
### JULY '05

**PROJECTS** • Cybervox • LF and VLF Converter • Multi-Clap Switch • Doorchime • Electronic Dice  
**FEATURES** • Discovering PICs Reviewed • Back To Basics – 4 • Digital TV Switchover • Practically Speaking • Circuit Surgery • Interface • Net Work – The Internet Page



### AUG '05

**PROJECTS** • Motor Amplifier • Pain Monitor • Audio System-Communications • Kitchen Timer • Room Thermometer  
**FEATURES** • Back To Basics – 5 • Circuit Surgery • Interface • Ingenuity Unlimited • Techno Talk • PIC 'N' Mix • NetWork – The Internet Page

### SEPT '05

**PROJECTS** • All Band Radio • Snooker and Darts Scoreboard • Multicore Cable Tester • Controlling Model Railway Signals • Daily Reminder • Whistle Switch  
**FEATURES** • Back To Logic Basics – 6 • Circuit Surgery • Practically Speaking • Ingenuity Unlimited • Techno Talk • PIC 'N' PIC • Net Work – The Internet Page

## BACK ISSUES ONLY £3.80 each inc. UK p&p.

Overseas prices £4.50 each surface mail, £5.50 each airmail.

We can also supply issues from earlier years: 2000 (except Feb., Mar., July, Oct.), 2001 (except Feb., May, Aug., to Nov.), 2002 (except Feb., June, Aug. to Nov.), 2003 (except June), 2004 (except June, July, Oct. and Dec). Where we do not have an issue a photocopy of any *one article* or *one part* of a series can be provided at the same price.

### ORDER FORM – BACK ISSUES – PHOTOCOPIES– INDEXES

- Send back issues dated .....
- Send photocopies of (article title and issue date) .....
- Send copies of last five years indexes (£3.80 for five inc. p&p – Overseas £4.50 surface, £5.50 airmail)

Name .....

Address .....

.....Tel: .....

I enclose cheque/P.O./bank draft to the value of £ .....

Please charge my Visa/Mastercard/Amex/Diners Club/Switch £ .....

Card No. .... Switch Issue No .....

Valid From ..... Card Expiry Date ..... Card Security Code .....

(The last 3 digits on or just under the signature strip)

SEND TO: Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.

Tel: 01202 873872. Fax: 01202 874562.


E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk) On-line Shop: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.


M10/05

# STORE YOUR BACK ISSUES ON MINI CD-ROMS

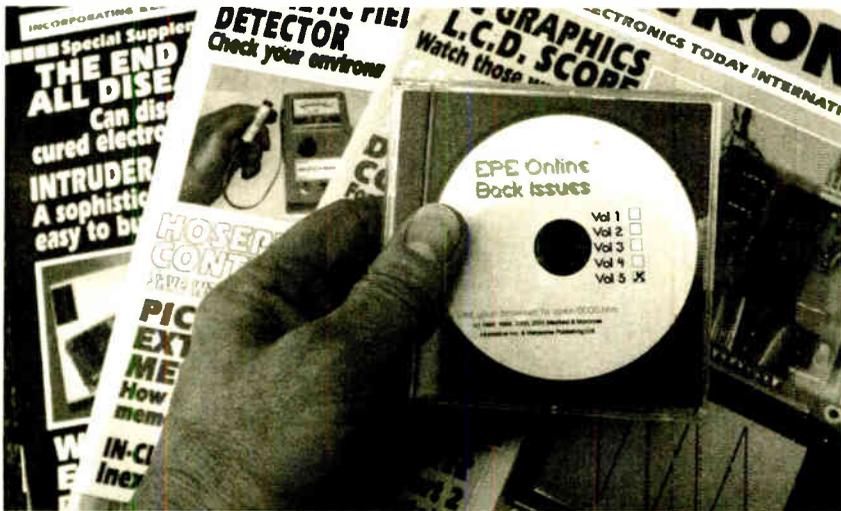

**VOL 12  
NOW AVAILABLE**

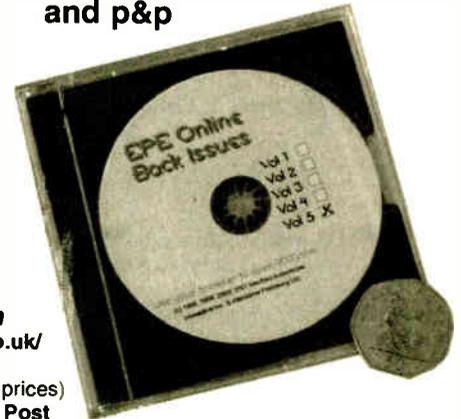**ONLY  
£14.45 each**  
including VAT  
and p&p



A great way to buy *EPE* Back Issues – our mini CD-ROMs contain back issues from our *EPE Online* website plus bonus articles, all the relevant PIC software and web links. Note: no free gifts are included. All this for just £14.45 each including postage and packing.

- VOL 1: BACK ISSUES** – January 1999 to June 1999  
Plus some bonus material from Nov and Dec 1998
- VOL 2: BACK ISSUES** – July 1999 to December 1999
- VOL 3: BACK ISSUES** – January 2000 to June 2000
- VOL 4: BACK ISSUES** – July 2000 to December 2000
- VOL 5: BACK ISSUES** – January 2001 to June 2001
- VOL 6: BACK ISSUES** – July 2001 to December 2001
- VOL 7: BACK ISSUES** – January 2002 to June 2002
- VOL 8: BACK ISSUES** – July 2002 to December 2002
- VOL 9: BACK ISSUES** – January 2003 to June 2003
- VOL 10: BACK ISSUES** – July 2003 to December 2003
- VOL 11: BACK ISSUES** – January 2004 to June 2004
- VOL 12: BACK ISSUES** – July 2004 to December 2004

Order on-line from  
[www.epemag.wimborne.co.uk/  
shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)  
or [www.epemag.com](http://www.epemag.com) (USA \$ prices)  
or by phone, Fax, E-mail or Post

NOTE: These mini CD-ROMs are suitable for use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader (available free from the Internet – [www.adobe.com/acrobat](http://www.adobe.com/acrobat))

## WHAT IS INCLUDED

All volumes include the *EPE Online* editorial content of every listed issue, plus all the available PIC Project Codes for the PIC projects published in those issues.

Note: Some supplements etc. can be downloaded free from the Library on the *EPE Online* website at [www.epemag.com](http://www.epemag.com). No advertisements are included in Volumes 1 and 2; from Volume 5 onwards the available relevant software for *Interface* articles is also included.

## EXTRA ARTICLES – ON ALL VOLUMES

**BASIC SOLDERING GUIDE** – Alan Winstanley's internationally acclaimed fully illustrated guide. **UNDERSTANDING PASSIVE COMPONENTS** – Introduction to the basic principles of passive components. **HOW TO USE INTELLIGENT L.C.D.s**, by Julyan Ilett – An utterly practical guide to interfacing and programming intelligent liquid crystal display modules. **Phyzyb COMPUTERS BONUS ARTICLE 1** – Signed and Unsigned Binary Numbers. By Clive "Max" Maxfield and Alvin Brown. **Phyzyb COMPUTERS BONUS ARTICLE 2** – Creating an Event Counter. By Clive "Max" Maxfield and Alvin Brown. **INTERGRAPH COMPUTER SYSTEMS 3D GRAPHICS** – A chapter from Intergraph's book that explains computer graphics technology. **FROM RUSSIA WITH LOVE**, by Barry Fox – Russian rockets launching American Satellites. **PC ENGINES**, by Ernest Flint – The evolution of Intel's microprocessors. **THE END TO ALL DISEASE**, by Aubrey Scoon – The original work of Rife. **COLLECTING AND RESTORING VINTAGE RADIOS**, by Paul Stenning. **THE LIFE & WORKS OF KONRAD ZUSE** – a brilliant pioneer in the evolution of computers. A bonus article on his life and work written by his eldest son, including many previously unpublished photographs.

Note: Some of the **EXTRA ARTICLES** require WinZip to unzip them.

## BACK ISSUES MINI CD-ROM ORDER FORM

- Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 1
  - Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 2
  - Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 3
  - Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 4
  - Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 5
  - Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 6
  - Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 7
  - Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 8
  - Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 9
  - Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 10
  - Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 11
  - Please send me ..... (quantity) BACK ISSUES CD-ROM VOL 12
- Price £14.45 each – includes postage to anywhere in the world.

Name .....

Address .....

..... Post Code .....

I enclose cheque/P.O./bank draft to the value of £ .....

Please charge my Visa/Mastercard/Amex/Diners

Club/Maestro

£ .....

Card No. ....

Card Security Code ..... (The last 3 digits on or just under the signature strip)

Valid From ..... Expiry Date .....

Maestro Issue No. ....


SEND TO: **Everyday Practical Electronics,  
Wimborne Publishing Ltd.,  
408 Wimborne Road East, Ferndown, Dorset BH22 9ND.**  
Tel: 01202 873872. Fax: 01202 874562.  
E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

# Photic Phone

Thomas Scarborough

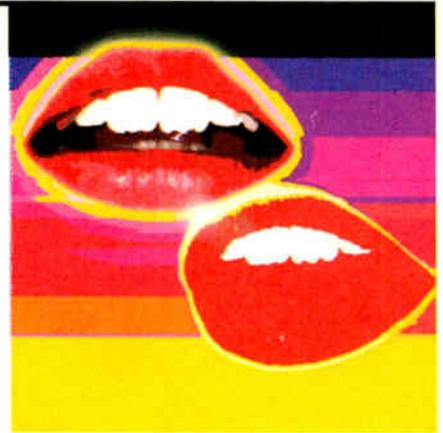

Using a single ultrabright l.e.d., this simple low-cost, high security, optical voice link achieved a range of four metres, and 15 metres with a single lens

**T**HIS project slices up the human voice into forty-thousand binary segments a second, transmits it over a light-beam, then re-integrates it at the other side. That is, it applies pulse width modulation (p.w.m.) to the voice, to create a binary transmission. This is far more advantageous than similar analogue circuits, which typically achieve a range of no more than a few metres.

The circuit presented here has a range approximately five times greater than similar analogue circuits. Without the use of lenses, the prototype Photic Phone achieved a range of four metres. With a single lens at the Transmitter, it achieved a range of 15 metres. In theory, therefore, with the use of two lenses, it should achieve a range of fifty metres using a single cheap, ultrabright l.e.d.

The problem with similar analogue circuits is that these depend on a light beam of continuously variable intensity. What happens in this case is that, over distance, the subtler nuances of the light beam are lost – and with them the intelligibility of the voice.

Transmitting a voice in binary form has the advantage of always transmitting at full intensity. This means that even the weakest nuances of a voice will reach the Receiver as strongly as the rest.

## Lighting The Way

Besides being good fun, communicating via a light-beam may have certain advantages over other methods of transmission. It requires no wires, it needs no radio license, it is very cheap to implement, and it is all but impossible for anyone to eavesdrop on a transmission. Not only this, but the Photic Phone may also be used with fibre optic cable or a laser (at a price)!

It has at least one further, less obvious use. This is to detect pulsed, reflected light. In this case the circuit would require a few small modifications, in particular the addition of an oscillator to the Transmitter circuit, and a diode charge pump to the Receiver. Such a circuit should have a potential range of a few metres with lenses, and would detect, for example, persons walking past a window or approaching a door.

## In Concept

While the Photic Phone has an unusually good “line-of-sight” range, it does have two limitations in particular which the constructor might wish to be aware of. First, it has a “tinny” sound which does not match the quality of the humble telephone. However, its sound quality is more than adequate for clear voice communication. Second, although it incorporates fairly effective filtering, there is likely to be an audible hum when it is used under a.c. lighting.

The seed for this project was sown with the original *Wind-Up Torch* (*EPE*, October 2000). In order to conserve power, the author pulsed the torch’s light on the one hand, and gathered it with a lens on the other. It was then noted that a pulsed, focused ultrabright l.e.d. would easily light up objects 15 metres away.

The next impetus came as the author was developing the *Bat Detector* (*EPE*, March 2004). While contemplating the circuit diagram, it seemed obvious that it should be possible to transmit a modulated voice over a light-beam. This proved to be true, and a simple experiment achieved a short range.

The author also wondered just how simple such a circuit might potentially be. At first a direct analogue-to-binary conversion of the voice at the voice’s natural frequency – around 300Hz – was tried.

Although this had the advantage of great simplicity, the clarity of transmission (or lack of it) was such that one could barely, if at all, make out what was being said. Female voices were more easy to discern than male – perhaps due to their higher frequency.

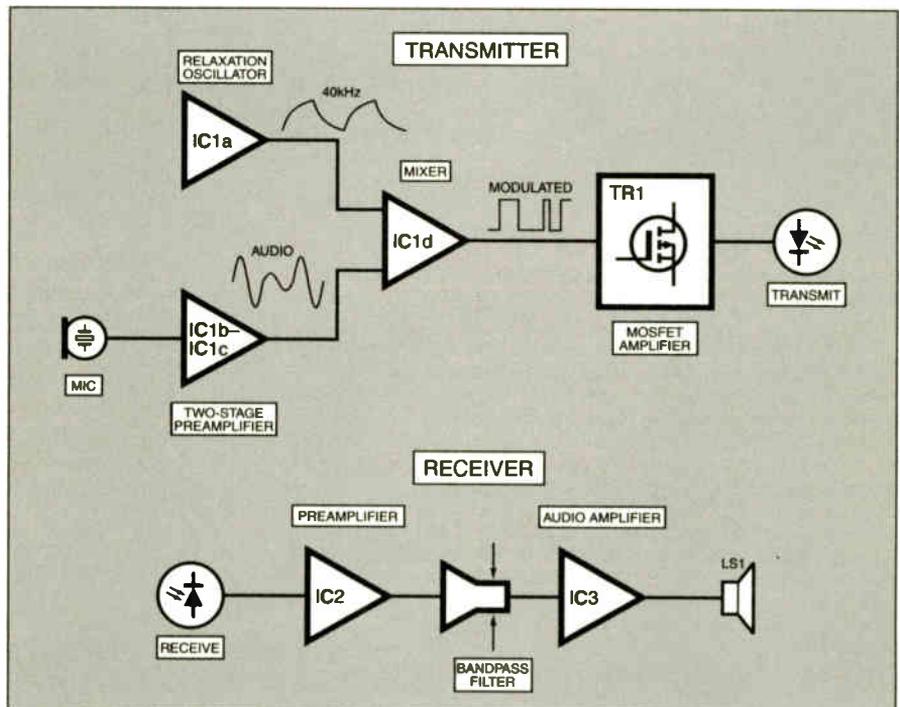


Fig.1. Block schematic diagram showing the general Transmitter and Receiver line-up that makes up the Photic Phone

Clarity further improved if compression was applied at the transmitter. However, this approach was obviously not destined for practical success.

The obvious way to go, it seemed, was p.w.m. (pulse width modulation). This is not the same as digital transmission, since the latter converts the voice into equally spaced 0s and 1s, usually in a mathematically encoded form. Nor is it the same as amplitude modulation (a.m.), which modulates the amplitude of a signal. Instead, p.w.m. chops up the voice into binary segments with varying mark-space ratios, which correlate directly to the voice.


## Fast Response

A breakdown of the Photic Phone system into the Transmitter and Receiver sections is shown in the block diagram Fig.1.

The next key question was how fast an ultrabright l.e.d. would be able to switch. The author found that many ultrabright l.e.d.s (although not white l.e.d.s) could switch at 100kHz. Therefore, to be on the safe side, a modulating frequency a little above 40kHz was chosen for the circuit.

Again, it was considered whether compression would be required at the transmitter. However, in practice this proved not to be necessary, on condition that one knows approximately how loudly to speak into the microphone. As shown, the piezo microphone needs to be held about 10cm from the mouth when speaking normally.

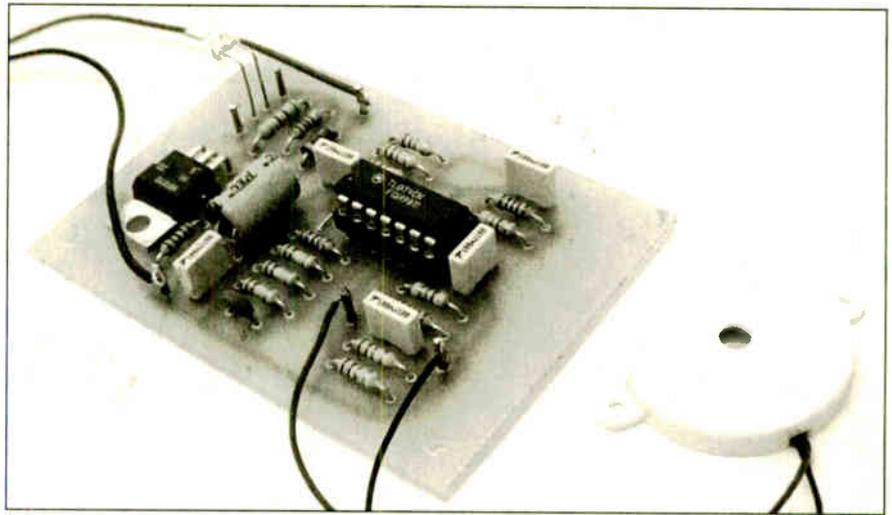As it turned out, one of the most important requirements of the circuit was filtering. Firstly, a low-pass filter (482Hz) was required to reduce acoustic feedback. An early prototype produced acoustic feedback at 15 metres distance. This low-pass filter also doubles as demodulation or



Completed prototype Transmitter circuit board. The passive piezoelectric sounder acts as the circuit's microphone

“decoding” for the modulated voice. Secondly, it was necessary to include a high-pass filter (175Hz) at the receiver end, to suppress the hum of a.c. lighting.

Note that since a power MOSFET (TR1) is used to switch the ultrabright l.e.d. D1, the light output of the Transmitter could easily be increased. A few ultrabright l.e.d.s could be used at once, or even the exceptionally bright Lumileds that are now available on the hobbyist market.

## Transmitter Circuit

The full circuit diagram for the Transmitter stage of the Photic Phone is shown in Fig.2. Op.amp IC1a is configured as a relaxation oscillator, running at just over 40kHz. Notice that its output is taken

from inverting input pin 2, instead of output pin 1. This is to obtain a rough approximation of a triangle wave for the modulating signal, which is presented to IC1d pin 13.

Next, a simple preamplifier, IC1b and IC1c, is employed to amplify the signal from a piezo microphone, MIC1. This is a cheap, disc type, piezo sounder, without an integral drive circuit.

The potential at IC1b non-inverting input pin 5 is lightly biased through resistors R1 and R2, and gain is set through resistors R7 and R10. The values of these two resistors may be increased for greater sensitivity, and vice versa. However, bear in mind that greater sensitivity means increased acoustic feedback, which is more problematic at shorter distances.

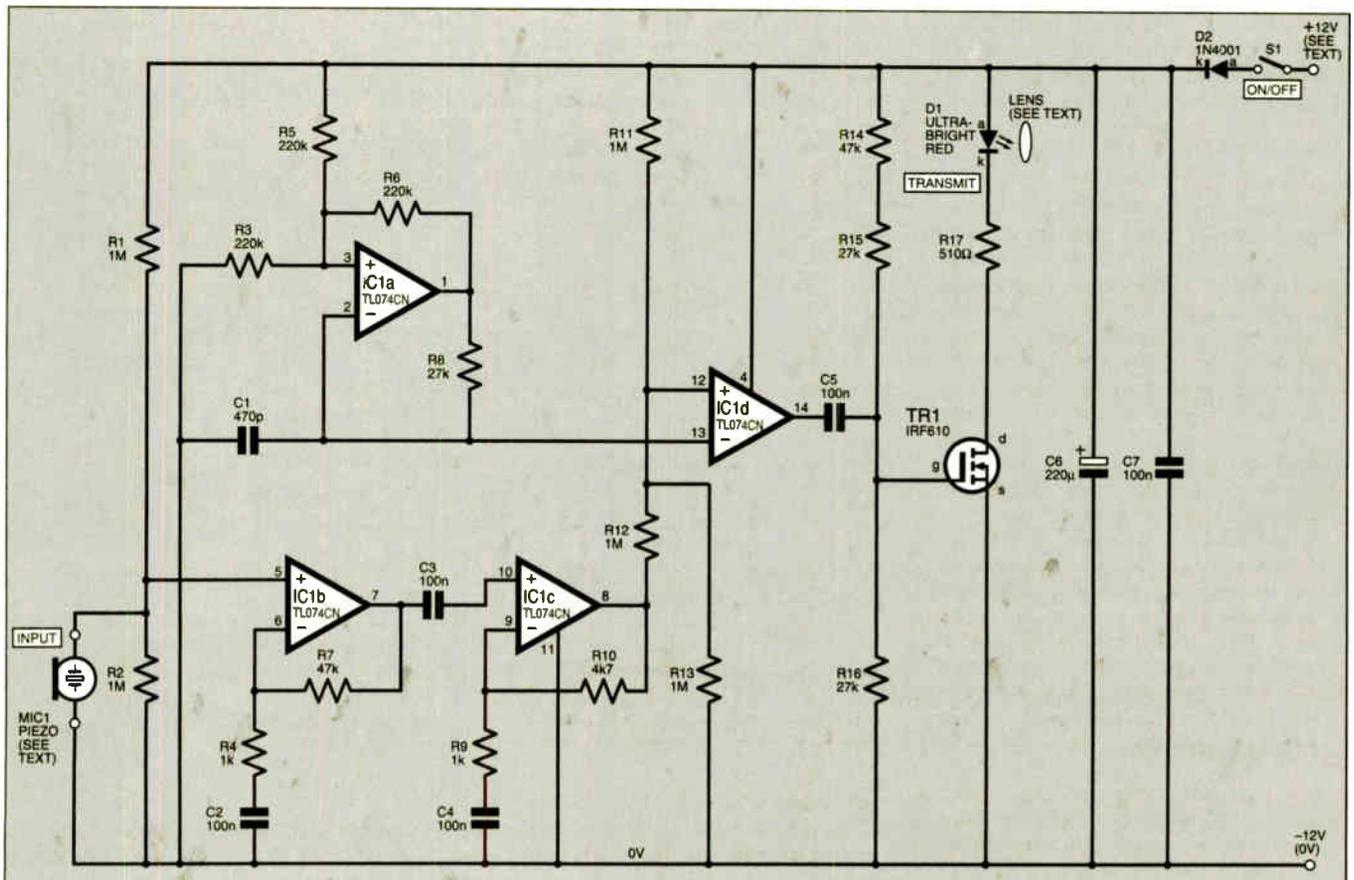


Fig.2. Complete circuit diagram, less power source, for the Photic Phone Transmitter

Resistors R11 to R13 are particularly important to the circuit, since these “contain” the signal at IC1d input pin 12 within one-third and two-thirds of the supply voltage. That is, the maximum amplitude of the preamplifier signal at IC1d input pin 12 matches the maximum amplitude of the modulating signal at IC1d input pin 13.

Lastly, the gate (g) of MOSFET TR1 is biased at its switching voltage through resistors R14 to R16, so that a modulated signal at IC1d output pin 14 causes the ultrabright “transmit” i.e.d. D1 to switch. If a different MOSFET is used, R14 to R16 may need to be adjusted so that the potential at TR1’s gate (g) approximates the switching voltage. Bearing this in mind, most power MOSFETs may be used.


## Receiver Circuit

The complete circuit diagram for the Receiver section is shown in Fig.3. This comprises a preamplifier, IC2, followed by a simple passive bandpass filter, and a 500mW r.m.s. audio amplifier i.c. IC3.

The “receive” photodiode D3 was taken from the author’s spares box, but any sensitive photodiode or phototransistor may be used here, e.g. the Siemens SFH203. As a rough guide, the resistance of the author’s photodiode fell below 10kΩ when situated 10cm from the “transmit” i.e.d. D1.

Resistor R18 may be modified to suit D3, and ideally the potential at the D3/R18 junction would be about half supply voltage when receiving. A light dependent resistor (l.d.r.) also worked here, but with much reduced sensitivity.

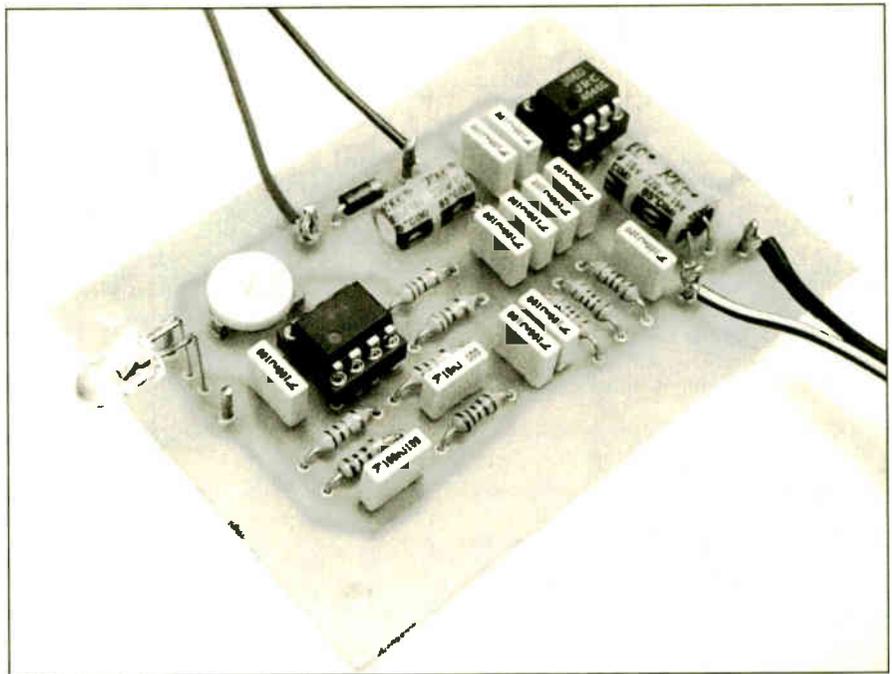Of course, an infra-red diode could be used for D1, with a matching photodiode or phototransistor for D3. In this case, the Photic Phone would communicate invisibly. However, considering the difficulty of working with an invisible beam, the author would not wish to attempt this himself!



Component layout on the finished Receiver board

## Light Signals

The potential at the junction between photodiode D3 and resistor R18 fluctuates rapidly as a light signal is received. This is fed to the non-inverting input (pin 3) of preamplifier IC2 by means of coupling capacitor C8. The preamplifier’s non-inverting input (pin 2) is biased by means of resistors R19 and R20.

After this follow five passive filters, which make up a second-order low-pass filter (cut-off 482Hz), and a third-order high-pass filter (cut-off 173Hz), which form a bandpass filter when combined. This filter essentially permits the voice to pass, while filtering out both low frequency ripples caused by a.c. lighting, and the

high frequency modulating signal. While active filters could have been used in this circuit, this would not have contributed to a simpler circuit, nor would it strictly have been necessary.

The fact that the high-pass filter is third-order, and its cut-off frequency relatively high, reveals that ripple from a.c. lighting was problematic during development of the circuit. While this filter does not completely eliminate hum, it greatly reduces it, particularly if photodiode D3 is placed in a black tube (see Fig.6). One could insert another high-pass filter if desired.

The author was unable to find the required 9.2 kilohm resistors for the filter,

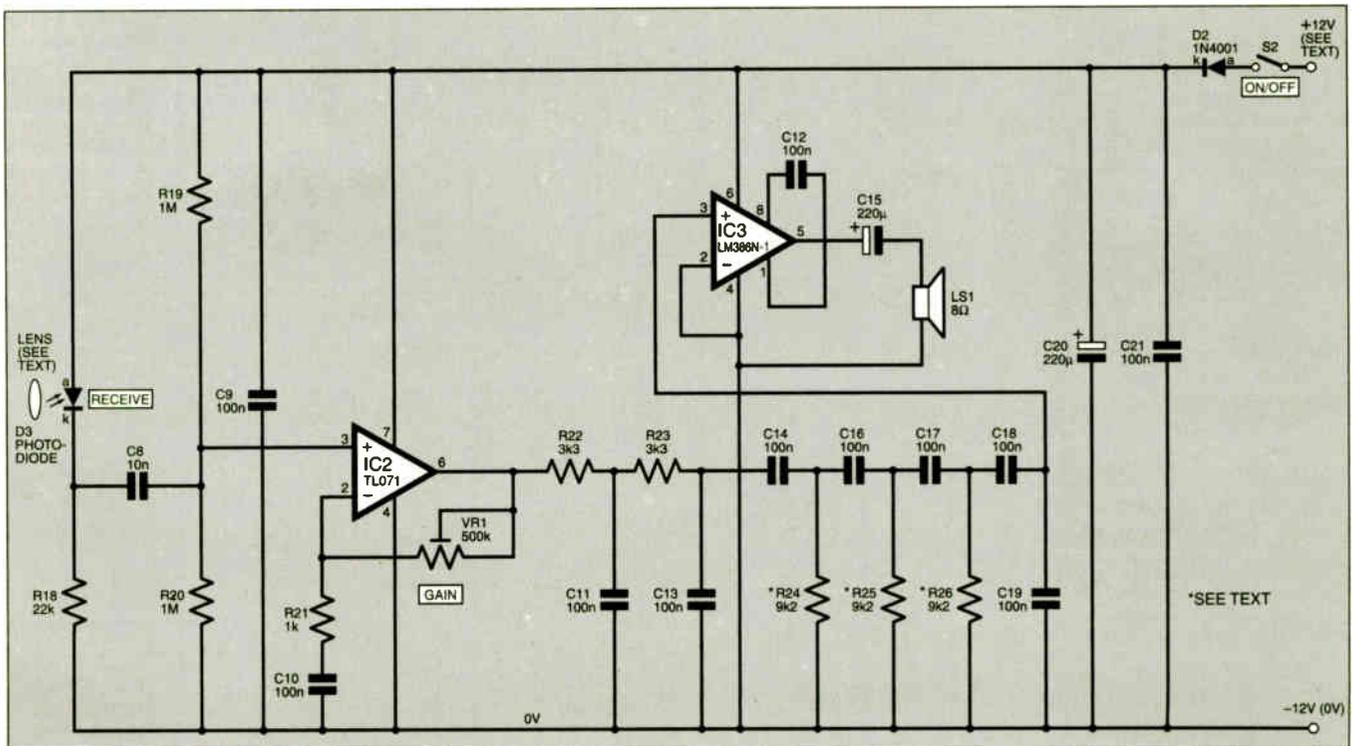


Fig.3. Full circuit diagram for the Receiver section of the Photic Phone. Note the lens is optional – see text

## Resistors

|                    |  |
|--------------------|--|
| R1,R2, R11 to R13, |  |
| R19,R20            | 1M (7 off)                             |
| R3, R5, R6         | 220k (3 off)                           |
| R4, R9, R21        | 1k (3 off)                             |
| R7, R14            | 47k (2 off)                            |
| R8, R15, R16       | 27k (3 off)                            |
| R10                | 4k7                                    |
| R17                | 510Ω                                   |
| R18                | 22k                                    |
| R22,R23            | 3k3 (2 off)                            |
| R24 to R26         | 9k2 (10k and 100k in parallel) (3 off) |

All 0.25W 5% carbon film

## Potentiometers

|     |                            |
|-----|----------------------------|
| VR1 | 500k enclosed round preset |
|-----|----------------------------|

## Capacitors

|                 |                                    |
|-----------------|------------------------------------|
| C1              | 470p ceramic or polyester          |
| C2 to C5, C7,   |                                    |
| C9 to C14,      |                                    |
| C16 to C19, C21 | 100n ceramic or polyester (16 off) |
| C6, C15, C20    | 220μ radial elect. 16V (3 off)     |
| C8              | 10n ceramic or polyester           |

See  
SHOP  
TALK  
page

## Semiconductors

|        |  |
|--------|--|
| D1     | ultrabright red l.e.d. (see text)                                |
| D2, D4 | 1N4001 50V 1A rect. diode (2 off)                                |
| D3     | sensitive photodiode or phototransistor (e.g. SFH203 – see text) |
| TR1    | IRF610 n-channel power MOSFET                                    |
| IC1    | TL074CN quad j.f.e.t. op.amp                                     |
| IC2    | TL071 j.f.e.t. op.amp  |
| IC3    | LM386N-1 audio amplifier   |

## Miscellaneous

|        |   |
|--------|---|
| MIC1   | 3V to 30V piezo sounder, without integral driver                              |
| S1, S2 | s.p.s.t. toggle or slider switch (2 off)                                      |
| LS1    | 0.5W 8 ohm miniature loudspeaker  |
| B1, B2 | 12V sealed lead-acid battery or 12V regulated power supply – see text (2 off) |

Printed circuit boards available from the *EPE PCB Service*, codes 531(Trans.) and 532(Rec.); 8-pin d.i.l. socket (2 off); 14-pin d.i.l. socket; ABS plastic case, size and style to choice (see text); lenses (optional – see text); screened microphone cable (optional); cable ties; battery clip (2 off); solder pins (12 off); solder, etc.

however, an easy solution is to use 10 kilohm resistors and to wire 100kΩ resistors in parallel, which equals about 9.1 kilohms.

The cut-off frequency of the filters is calculated with the formula  $f=2\pi CR$ . The two low-pass filters comprise R22/C11 and R23/C13, while the three high-pass filters comprise resistors R24 to R26 and capacitors C14, C16 and C17.

## Audio Amplifier

The audio signal amplifier, IC3, uses the popular LM386N-1 i.c., which puts out a respectable 0.5W r.m.s. into 8 ohms. Capacitor C19 is used as a final low-pass filter, recommended in data sheets (usually its value lies around 10nF), and C15 is a coupling capacitor for loudspeaker LS1.

To simplify design, the usual Zobel network at the output of IC3 was omitted. Capacitor C12 is used to boost the amplifier's gain, and this may be increased up to 10μF for increased gain, its positive terminal wired to pin 1 of IC3).

The current consumption of both Transmitter and Receiver is fairly high (about 15mA each), therefore two 12V sealed lead-acid batteries would be recommended, or two 12V regulated power supplies.

## Construction

The printed circuit boards (p.c.b.s) for the Transmitter and Receiver both measure just 80mm (3.15in.) × 55mm (2.17in.). Instructions are given here for soldering both boards simultaneously.

The component layouts, off-board wiring and underside copper foil master patterns for the Transmitter and Receiver p.c.b.s for the Photoc Phone are given in Fig.4 and Fig.5. These boards are available as a pair from the *EPE PCB Service*, codes 531(Trans.) and 532(Rec.)

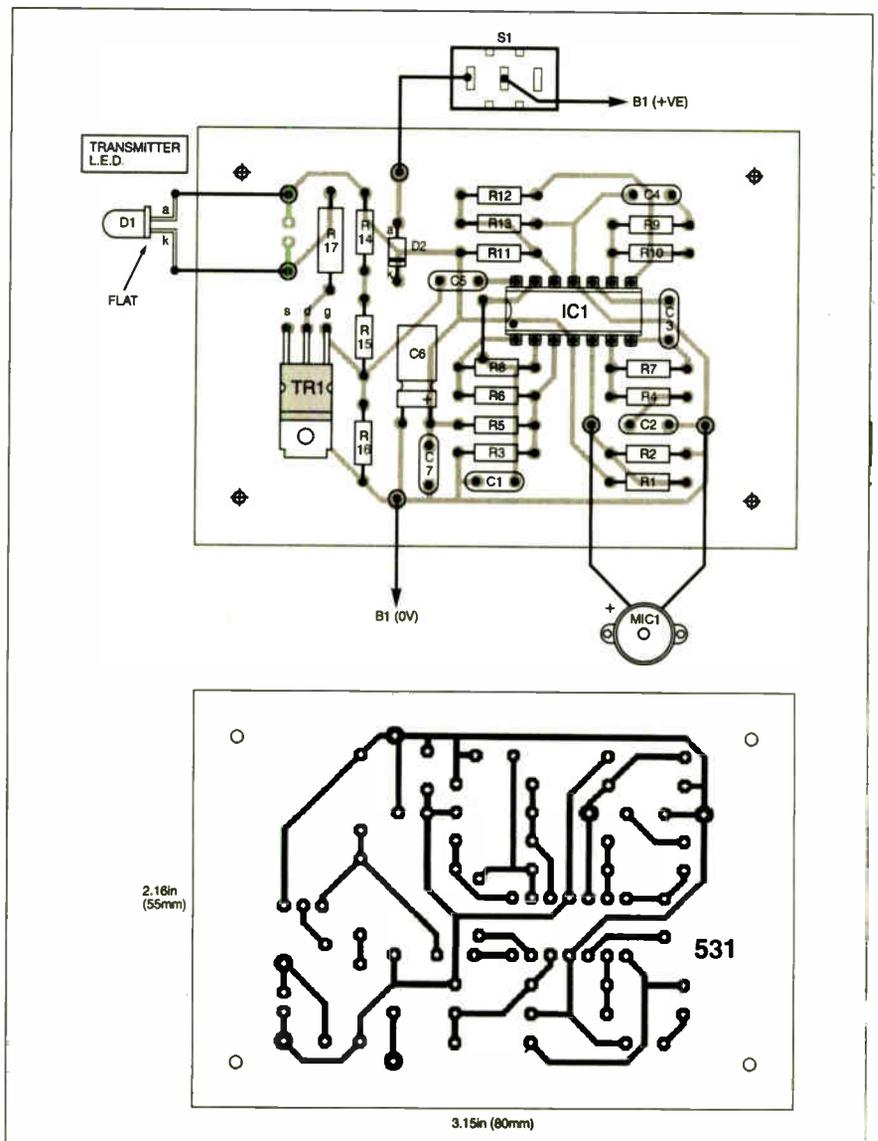


Fig.4. Transmitter printed circuit board component layout and wiring details

Since the two circuits amplify audio signals, and operate at a relatively high frequency, good solder joints need to be made throughout. All the components are fairly robust, and should not suffer from a good (though not excessive) application of solder. The integrated circuits should not be inserted in their dual-in-line (d.i.l.) sockets until circuit board construction has been completed and double checked for any component placement errors or bad soldering connections, including "bridged" copper tracks.


Working on each board in turn, begin construction by soldering the twelve solder pins, the three d.i.l. sockets, the twenty-six resistors and twenty-one capacitors (note the polarity of C6, C15 and C20). Solder preset potentiometer VR1, diodes D1 to D4 (D1 and D3 may be situated off-board for convenience), and transistor TR1.

Follow this by attaching the piezo microphone MIC1, loudspeaker LS1 and the two battery clips, observing the correct polarity, to the circuit boards as shown in Fig.4 and Fig.5. Finally, insert IC1 to IC3 in the d.i.l. sockets, observing their correct orientation.
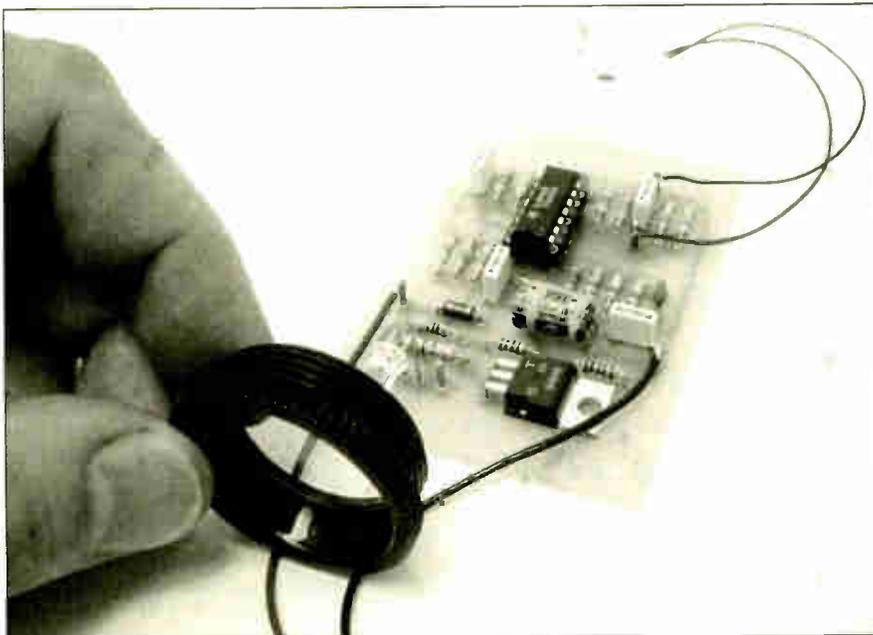
### Final Assembly

Suitable ABS plastic cases may be used for the Transmitter and Receiver, with the Transmitter being mounted on a tripod if desired. The piezo sounder/microphone MIC1 may be mounted in a separate, small ABS case, and wired to the p.c.b. by means of screened microphone cable to make a "CB-style" handheld microphone.

Lenses may be used with the Transmitter and Receiver as shown in Fig.6. and each should increase the range of the Photic Phone a few times over. Either add a single lens at the Transmitter (see photograph), or lenses at both the Transmitter and Receiver. The lenses are positioned so that the semiconductor chips within D1 and D3 are located precisely at the focal points of the lenses. A method for determining the approximate focal length of a lens is shown in Fig.6.



Experimenting with a lens in front of the Transmitter's ultrabright light emitting diode (l.e.d.) to check its operating range. With no lens it reached four metres and with it achieved a range of around 15 metres. The completed Receiver board is shown below left.


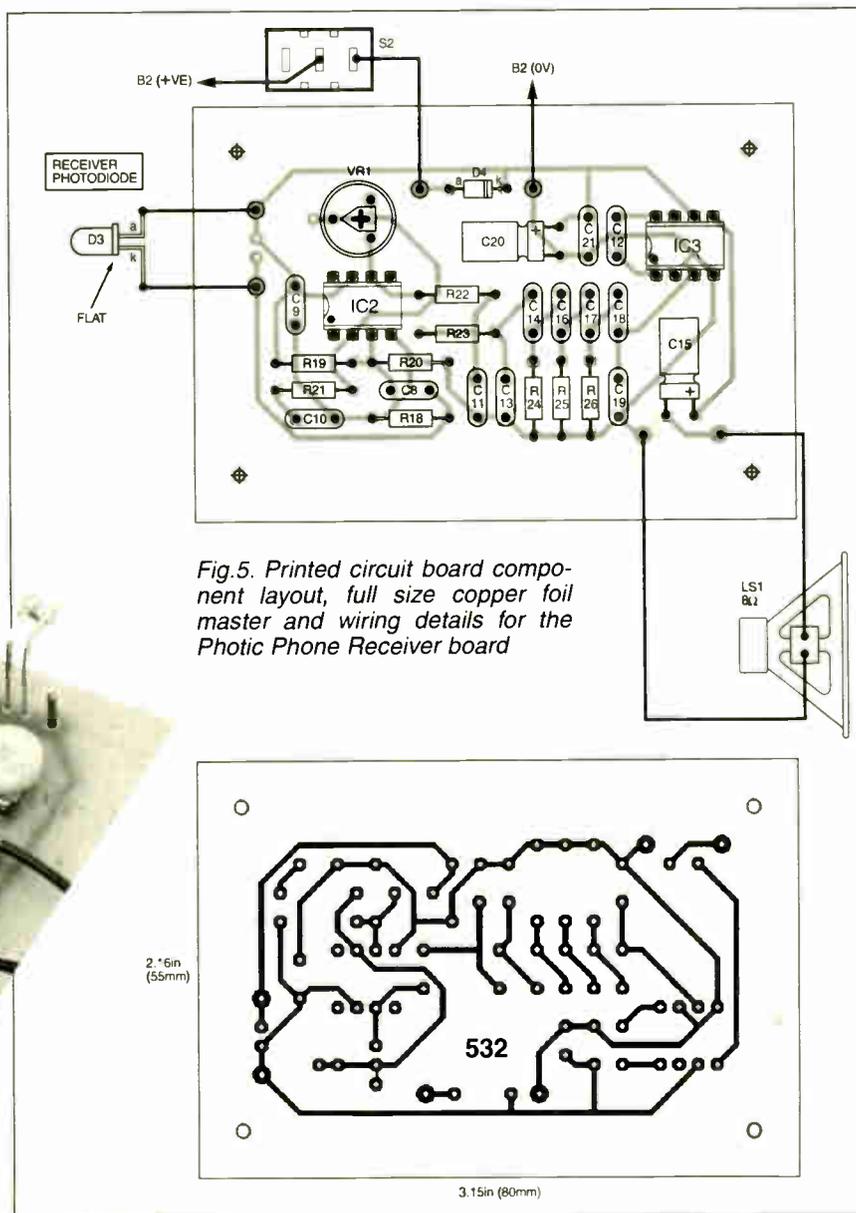


Fig.5. Printed circuit board component layout, full size copper foil master and wiring details for the Photic Phone Receiver board

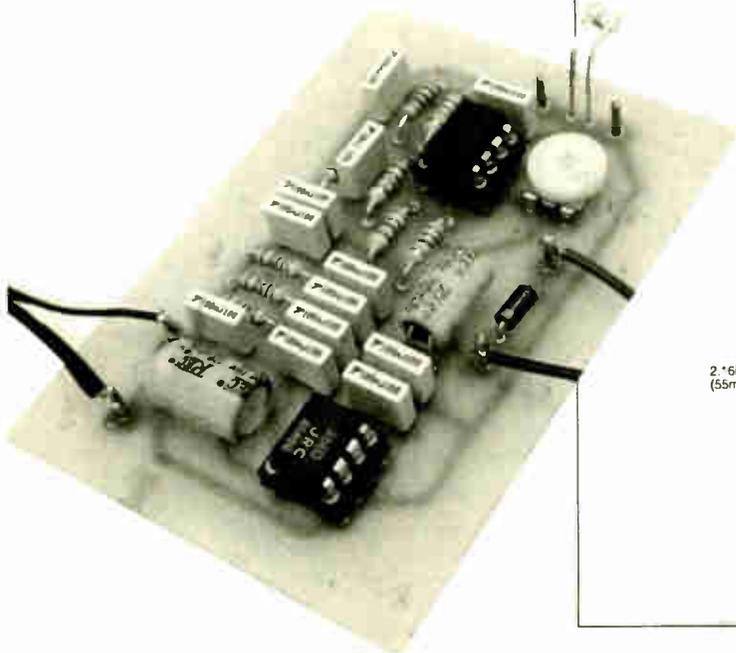

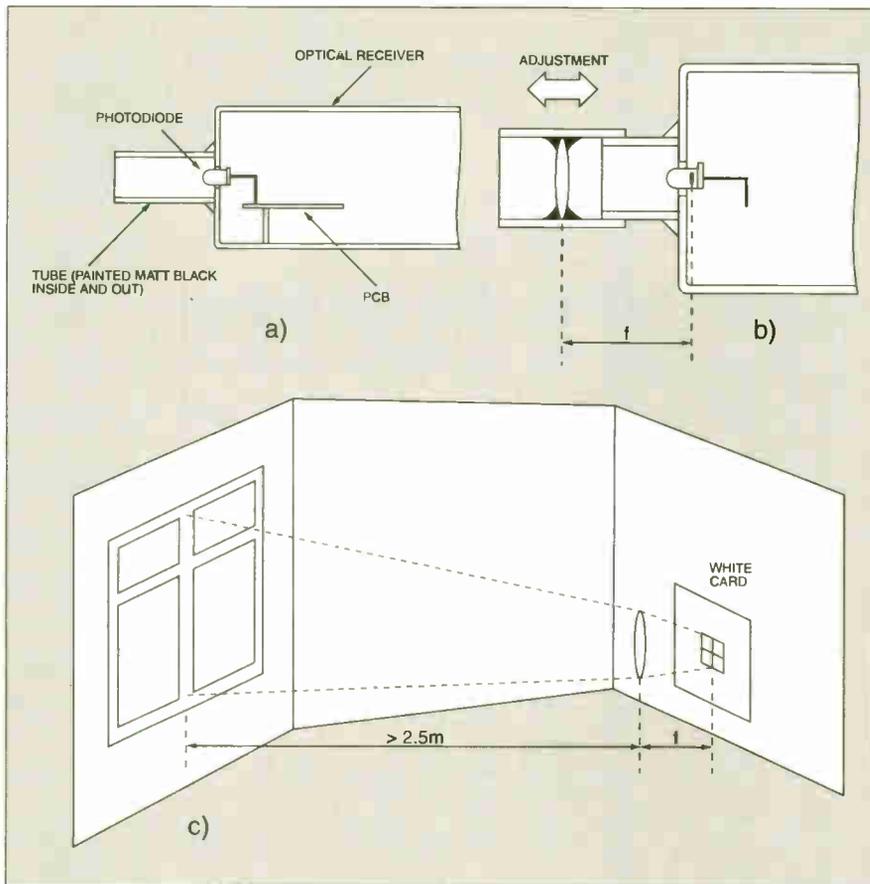


Fig.6. (a) Method of reducing mains lighting hum, (b) suggested adjustable lens mounting arrangement and (c) determining the approximate focal length of a lens

## Setting Up and Use

Begin the setting up procedure by turning the Receiver's preset Gain control VR1 up (clockwise) about one-third. If the circuit is powered up under a.c. lighting, a soft hum should be heard. If the volume of the hum varies as you move your hand across photodiode D3, this is a likely indication that all is well with the Receiver.

Now place the Transmitter about one metre from the Receiver, with the ultrabright i.e.d. D1 pointing directly at photodiode D3. When you power up the Transmitter, D1 should immediately illuminate, and there may be a squeal in loudspeaker LS1 due to acoustic feedback.

If there is no acoustic feedback, tap microphone MIC1. The tap should be heard in the loudspeaker. In the case of acoustic feedback, back-off (turn anti-clockwise) preset VR1 slightly until the Receiver is silenced, then tap microphone MIC1. Again, the tap should be heard in the loudspeaker.


From here on, it is now merely a matter of "pushing the boundaries" by increasing the range, experimenting with the gain of the Receiver with preset VR1 (note that higher gain does not always translate to better performance), and by experimenting with lenses. It should be found that, with a single lens at the Transmitter, the Photic Phone should operate over 10 metres' distance with ease, and likely a good deal further.

Note that for two-way, "line-of-sight" communication you will require two sets of Photic Phones.
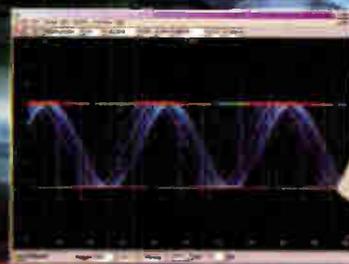
# PicoScope 3000 Series PC Oscilloscopes

The PicoScope 3000 series oscilloscopes are the latest offerings from the market leader in PC oscilloscopes combining high bandwidths with large buffer memories. Using the latest advances in electronics, the oscilloscopes connect to the USB port of any modern PC, making full use of the PC's processing capabilities, large screens and familiar graphical user interfaces.

- High performance: 10GS/s sampling rate & 200MHz bandwidth
- 1MB buffer memory
- High speed USB 2.0 interface
- Advanced display & trigger modes
- Compact & portable
- Supplied with PicoScope & PicoLog software



| PicoScope                  | 3204                        | 3205                  | 3206                  |
|----------------------------|-----------------------------|-----------------------|-----------------------|
| Bandwidth                  | 50MHz                       | 100MHz                | 200MHz                |
| Sampling rate (effective)  | 2.5GS/s                     | 5GS/s                 | 10GS/s                |
| Sampling rate (binic shot) | 50MS/s                      | 100MS/s               | 200MS/s               |
| Channels                   | 2-Ext trigger               | 2+Ext trigger/Sig gen | 2-Ext trigger/Sig gen |
| Oscilloscope timebase      | 5ns/div to 50s/div          | 2ns/div to 50s/div    | 1ns/div to 50s/div    |
| Timebase accuracy          | 50ppm                       | 500ps                 | 50ppm                 |
| Spectrum range             | 0 to 25MHz                  | 0 to 50MHz            | 0 to 100MHz           |
| Buffer memory size         | 256KB                       | 512KB                 | 1MB                   |
| Resolution - accuracy      | 8 bits, 3 $\frac{1}{2}$     |                       |                       |
| Range                      | ±100mV to ±20V              |                       |                       |
| PC Connection              | USB 2.0, USB 1.1 compatible |                       |                       |


Tel: 01480 396395

[www.picotech.com/scope296](http://www.picotech.com/scope296)

**pico**  
Technology Limited

# INTERFACE

Robert Penfold

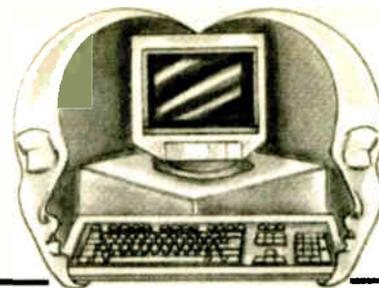

## USING A D/A CONVERTER IN A TRANSISTOR TESTER

In the previous *Interface* article we considered the basics of using a digital to analogue converter to provide analogue to digital conversion. In particular, the use of this method in an "improved" transistor tester was considered. Most transistor testers use a fixed base current which produces a collector current that varies widely depending on the gain of the device.

The method outlined previously uses a "suck it and see" approach that steps-up the base current until a certain collector current is achieved. In other words, it uses a fixed collector current and a variable base current. This ensures that the gain reading is always taken at a reasonably high collector current where the test device will operate quite efficiently. This avoids having low gain but serviceable transistors being erroneously indicated as duds.

### Transistor Tester Circuit

The circuit diagram for the transistor tester appears in Fig.1. The digital to analogue converter is based on an AD557JN chip (IC1), and this has been covered in recent *Interface* articles. It is an 8-bit converter that has an output voltage range of 0 to 2.55 volts, which equates to a resolution of 10 millivolts. In this application a voltage swing of 2.55 volts is adequate and it is not necessary to use any amplification. Some signal conditioning is required though, since it is actually a variable output current that is needed and not a variable voltage.

Of course, using a series resistor gives a simple but often effective form of voltage-to-current conversion, but in this case about 0.6 volts is needed before a significant current will start to flow. This is simply due to the fact that a silicon transistor has a

forward threshold potential of about 0.6 volts. Once that threshold has been reached, large increases in the base current produce little increase in the base voltage.

One way around this problem is to simply adjust the mathematics of the software to take the forward threshold voltage into account. A slight drawback of this method is that it reduces the effective resolution of the system, with output values from 0 to 60 being left unused. The alternative used here is to process the output voltage of IC1 using a simple non-inverting buffer amplifier based on IC2. However, the inclusion of D1 in the negative feedback network adds about 0.6 volts to the output potential from IC1, nullifying the forward threshold voltage of test components.

### NPN Testing

The base of a *npn* test device is driven from the output of IC2 via resistor R2. The collector load resistor for an *npn* test transistor is R3, and IC3 is used as the voltage comparator.

The Select In handshake input is used to monitor the output of IC3. R4 and R5 set the comparator's threshold voltage at half the supply potential, or 2.5 volts in other words. The base current is incremented until the collector voltage falls below this level, which occurs with a collector current of just over 20 milliamps.

This is high enough to ensure that any test device will operate efficiently, and realistic readings should even be obtained when testing power transistors. On the other hand, the test current is not so high that small signal transistors are in danger of being zapped.

The base current is a little over eight microamps per LSB, so multiplying the

final value output to the converter by eight gives the base current in microamps. The current gain of a transistor is equal to its collector current divided by the base current, and with this design the collector current is 20 milliamps (20000 microamps).

Dividing 20000 by the final base current therefore gives the current gain of the test component. The mathematics can be simplified slightly, and dividing 2500 (20000/8 = 2500) by the final value sent to the converter gives the current gain of the test device.

### PNP Testing

Some additional circuitry is needed in order to accommodate *pnnp* test devices. The base current for a *pnnp* test transistor is fed via R6 to a simple current mirror based on TR1 and TR2. The collector of TR2 drives the base of a *pnnp* test device, and sinks a current that is approximately equal to the input current via R6. Resistor R7 acts as the collector load for *pnnp* test components, and IC4 acts as the voltage comparator that detects the collector voltage going through the half-supply level. Its output is monitored by the printer port's Paper Out handshake line.

The connections to the two voltage comparators are such that their outputs go high when the 20 milliamp threshold current is exceeded. The software therefore has to increment the base current until a high logic level is detected from the relevant comparator. Rather than having *npn/pnp* switching, the interface has separate *npn* and *pnp* test sockets.

The circuit requires an accurate and stable +5V supply that can handle currents of up to 50 milliamps. The connections to the printer port are made using a piece of

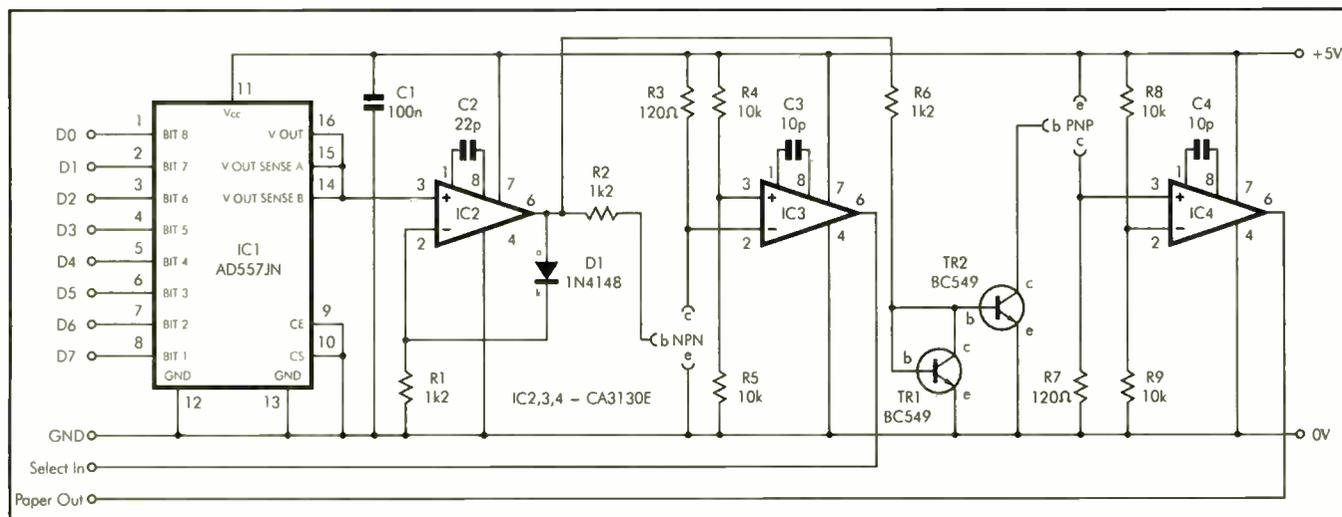


Fig.1. The circuit diagram for the Transistor Tester. Separate test sockets are used for npn and pnp test transistors.

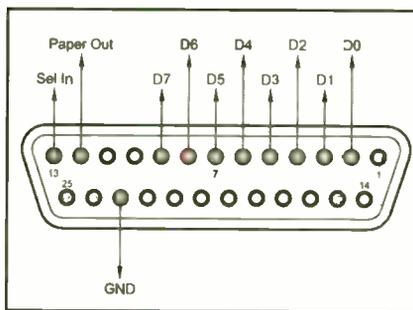


Fig.2. The 11 connections to the printer port are made via a 25-way D-type connector.

11-way ribbon cable that will probably have to be peeled from a 20-way cable. It is advisable to use a connecting cable that is no more than about two or three metres long. A 25-way male D connector is fitted at the PC end of the cable, and the correct method of connection is shown in Fig.2.

All four integrated circuits are MOS devices that require the usual anti-static handling precautions. Diode D1 can be any small signal silicon diode such as a 1N914 or 1N4148. For optimum accuracy with *pnp* test components the current gains of TR1 and TR2 should be reasonably well matched, so there is an advantage in using two components from the same gain group (e.g. BC549Cs).

Miniature 3-way DIN sockets are suitable for making the connections to most small transistors. It is necessary to make up a set of test leads to accommodate awkward transistors such as power types. The connections to power devices can be made by way of miniature crocodile clips or small spring-loaded test prods.

## Software

The sample program for the transistor tester is an extension of the analogue to digital converter program described in the previous *Interface* article. The form has two labels (see Fig.3), one of which acts as the digital readout, while the other just provides a "Transistor Tester" heading. There are two command buttons, and operating the appropriate one takes a reading from an *npn* (Command1) or *pnp* (Command2) test transistor. The subroutine for the *npn* button is in Listing 1.

The routine is a For Next loop that outputs values from 1 to a maximum of 255 to the data lines of the printer port. The count is started at 1 rather than 0 in order to avoid errors later in the routine due to a division by zero.

Each time the value in variable "loopcount" is incremented, the corresponding current gain is calculated and displayed on the digital readout. However, the value is incremented so fast that only the final gain figure is actually displayed.

When bit 4 of the handshake input port (&H379) goes high, loopcount is set at 255 and the loop is brought to a halt. This line is placed at the end of the loop so that the display is left showing a valid reading.

If the measured current gain is less than 10, an If...Then instruction displays "OPEN" on the readout. This indicates that the test device is not exhibiting a significant amount of current gain and it has probably gone open circuit.

It is important that each test device is checked initially without the base terminal connected. This should result in "OPEN" being displayed, because only minute leakage currents will flow through a serviceable device with no base current applied. Obtaining any gain reading when no base current is applied indicates that the test component has an excessively high leakage current and is faulty.

A current gain reading of 2500 is intercepted by another If...Then instruction that displays "CLOSED" on the digital readout. Real-world transistors have current gains of no more than about 1000, and a gain of 2500 indicates that the test component has gone closed circuit. A faulty device in this state will provide a "CLOSED" reading with or without the base terminal connected.

The routine for testing *pnp* transistors is essentially the same as the one for checking *npn* devices. The only difference is that a masking value or 32 rather than 16 is used when testing the state of the handshake input line, so that the Paper Out line at bit 5 of the handshake input register is monitored.

## Listing 1

```
Private Sub Command1_Click()
```

```
For loopcount = 1 To 255
Out &H378, loopcount
Currentgain = 2500 \ loopcount
Label1.Caption = Currentgain
If Currentgain = 9 Then
Label1.Caption = "OPEN"
If Currentgain = 2500 Then
Label1.Caption = "CLOSED"
If (Inp(&H379) And 16) = 16 Then
loopcount = 255
Next loopcount
```

```
End Sub
```

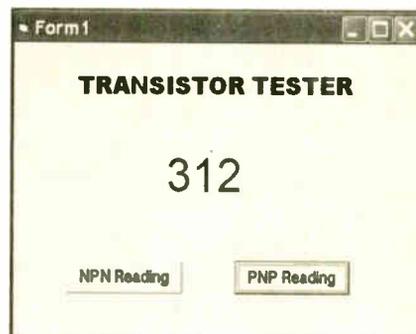


Fig.3. The sample transistor tester program in action. Operating a button takes a reading for the appropriate type (*npn* or *pnp*) of transistor.

## Modes

A common display is used for *npn* and *pnp* devices, but it would obviously be a simple matter to add another label component and use that for *pnp* readings. With separate displays it would be possible to use the two loops with a timer component so that readings were updated (say) 20 or 30 times per second. The system functions properly with *npn* and *pnp* devices connected simultaneously, so it would then effectively provide separate *npn* and *pnp* testers.

It is possible to alter the collector current at which measurements are made, and it is just a matter of altering the values of resistors R2, R3, R6, and R7. Resistors R2 and R6 must have the same value, which has to be ten times higher than the value used for R3 and R7. The correct value for R3 and R7 is equal to 2.5 divided by the required test current (in amps). The circuit is unlikely to work well using test currents of more than about 30 milliamps, or much less than about one milliamp.

This system of gain measurement gives better resolution at low gains than at the other end of the range. This was deemed acceptable as it was primarily designed for checking low gain devices that tend to be problematic when tested using simple transistor testers.

Making R2 and R6 20 times higher in value than R3 and R7 would accommodate gains down to 20, and would give better resolution at high gains. Of course, the mathematics in the software would have to be adjusted to suit this change. The current gain would be equal to 5000 divided by the final value fed to the digital-to-analogue converter.

## EPE BINDERS

The EPE ring binder uses a special system to allow the issues to be easily removed and re-inserted without any damage. A nylon strip slips over each issue and this passes over four rings in the binder, thus holding the magazine in place.

The binders are finished in hard-wearing royal blue p.v.c. with the magazine logo in gold on the spine. They will keep your issues neat and tidy but allow you to remove them for use easily.

The price is £7.95 plus £3.50 post and packing. If you order more than one binder add £1 postage for each binder after the initial £3.50 postage charge (overseas readers the postage is £6.00 each to everywhere except Australia and Papua New Guinea which costs £10.50 each).

Send your payment in £'s sterling cheque or PO (Overseas readers send £ sterling bank draft, or cheque drawn on a UK bank or pay by card), to **Everyday Practical Electronics, Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562.**

E-mail: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk). Web site: <http://www.epemag.co.uk>  
Order on-line from [www.epemag.co.uk/shopdoor.htm](http://www.epemag.co.uk/shopdoor.htm)

We also accept card payments. Mastercard, Visa, Amex, Diners Club or Maestro. Send, fax or phone your card number, card expiry date and card security code (the last 3 digits on or just under the signature strip), plus Maestro Issue No. with your order.

## SQUIRES MODEL & CRAFT TOOLS

100 London Road, Bognor Regis,  
West Sussex, PO21 1DD.

Tel 01243 842424, Fax 01243 842525.  
email: [sales@squirestools.com](mailto:sales@squirestools.com)

The Squires 2006 Mail Order Catalogue has just been published. It features over 10,000 tools, materials and components all available by POST FREE mail order. If you would like to receive a copy of our catalogue, please contact us at the above address.

**Our Shop is open 9.00 - 5.30 Monday to Saturday.**



**EVERYDAY PRACTICAL ELECTRONICS**  
INCORPORATING ELECTRONICS TODAY INTERNATIONAL



UK readers you can  
**SAVE 71p**  
 on every issue of *EPE*

How would you like to pay £2.58 instead of £3.30 for your copy of *EPE*?  
 Well you can – just take out a one year subscription and save over 71p an issue,  
 or £8.60 over the year

You can even save over 92p an issue if you subscribe for two years  
 – a total saving of £22.20

Overseas rates also represent exceptional value

You also:

- Avoid any cover price increase for the duration of your subscription
- Get your magazine delivered to your door each month
- Ensure your copy, even if the newsagents sell out

**STARTING  
 NEXT MONTH  
 TEACH-IN  
 2006  
 ENROL  
 NOW!**

Order by phone or fax with a credit card or by post with a cheque or postal order, or  
 buy on-line from [www.epemag.co.uk](http://www.epemag.co.uk) (click on "Subscribe Now")

**EPE SUBSCRIPTION PRICES**

Subscriptions for delivery direct to any address in the UK:  
 6 months £16.50, 12 months £31, two years £57; Overseas:  
 6 months £19.50 standard air service or £28.50 express airmail,  
 12 months £37 standard air service or £55 express airmail,  
 24 months £69 standard air service or £105 express airmail.  
 Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to *EPE* Subs. Dept., Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: [subs@epemag.co.uk](mailto:subs@epemag.co.uk). Also via the Web at <http://www.epemag.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Maestro or Visa. (For past issues see the *Back Issues* page.)

**ONLINE SUBSCRIPTIONS**

Online subscriptions, for downloading the magazine via the Internet, \$14.99US (approx. £8) for one year available from [www.epemag.com](http://www.epemag.com).

**USA/CANADA SUBSCRIPTIONS**

To subscribe to *EPE* from the USA or Canada please telephone Express Mag toll free on 1877 363-1310 and have your credit card details ready. Or fax (514) 355 3332 or write to Express Mag, PO Box 2769, Plattsburgh, NY 12901-0239 or Express Mag, 8155 Larrey Street, Anjou, Quebec, H1J 2L5.  
 Email address: [expsmag@expressmag.com](mailto:expsmag@expressmag.com).  
 Web site: [www.expressmag.com](http://www.expressmag.com).  
 USA price \$60(US) per annum, Canada price \$97(Can) per annum – 12 issues per year.  
*Everyday Practical Electronics*, periodicals pending, ISSN 0262 3617 is published twelve times a year by Wimborne Publishing Ltd., USA agent USACAN at 1320 Route 9, Champlain, NY 12919. Subscription price in US \$60(US) per annum. Periodicals postage paid at Champlain NY and at additional mailing offices. POSTMASTER: Send USA and Canada address changes to *Everyday Practical Electronics*, c/o Express Mag., PO Box 2769, Plattsburgh, NY, USA 12901-0239.

**SUBSCRIPTION ORDER FORM**



- 6 Months: UK £16.50, Overseas £19.50 (standard air service), £28.50 (express airmail)
  - 1 Year: UK £31.00, Overseas £37.00 (standard air service) £55 (express airmail)
  - 2 Years: UK £57.00, Overseas £69.00 (standard air service) £105 (express airmail)
- To: *Everyday Practical Electronics*,  
 Wimborne Publishing Ltd., 408 Wimborne Road East,  
 Ferndown, Dorset BH22 9ND  
 Tel: 01202 873872 Fax: 01202 874562  
 E-mail: [subs@epemag.co.uk](mailto:subs@epemag.co.uk)

I enclose payment of £ ..... (cheque/PO in £ sterling only), payable to *Everyday Practical Electronics*

My card number is: .....  
 Please print clearly, and check that you have the number correct

Signature .....

Card Security Code ..... (The last 3 digits on or just under the signature strip)

Card Ex. Date ..... Maestro Issue No. ....

Name .....


Address .....

Post code ..... Tel. ....

Subscriptions can only start with the next available issue.

# EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS


## ELECTRONICS PROJECTS

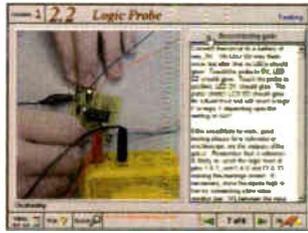

Logic Probe testing

*Electronic Projects* is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included. The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.


## ELECTRONICS CAD PACK

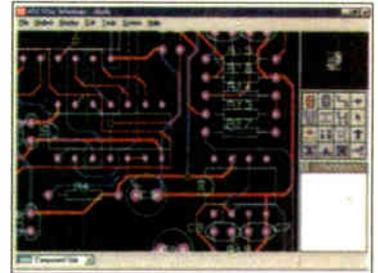

PCB Layout

Electronics CADPACK allows users to design complex circuit schematics, to view circuit animations using a unique SPICE-based simulation tool, and to design printed circuit boards. CADPACK is made up of three separate software modules. (These are restricted versions of the full Labcenter software.) **ISIS Lite** which provides full schematic drawing features including full control of drawing appearance, automatic wire routing, and over 6,000 parts. **PROSPICE Lite** (integrated into ISIS Lite) which uses unique animation to show the operation of any circuit with mouse-operated switches, pots, etc. The animation is compiled using a full mixed mode SPICE simulator. **ARES Lite** PCB layout software allows professional quality PCBs to be designed and includes advanced features such as 16-layer boards, SMT components, and an autorouter operating on user generated Net Lists.


## ELECTRONIC CIRCUITS & COMPONENTS V2.0

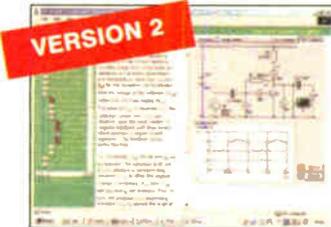

Circuit simulation screen

Provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals:** units & multiples, electricity, electric circuits, alternating circuits. **Passive Components:** resistors, capacitors, inductors, transformers. **Semiconductors:** diodes, transistors, op.amps, logic gates. **Passive Circuits.** **Active Circuits.** **The Parts Gallery** will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.

## ANALOGUE ELECTRONICS

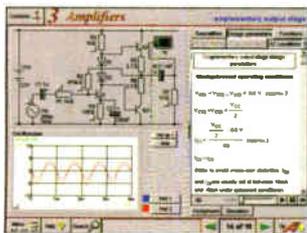

Complimentary output stage

*Analogue Electronics* is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits. Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections), **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections). **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections). **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

## ROBOTICS & MECHATRONICS



Case study of the Milford Instruments Spider

Robotics and Mechatronics is designed to enable hobbyists/students with little previous experience of electronics to design and build electromechanical systems. The CD-ROM deals with all aspects of robotics from the control systems used, the transducers available, motors/actuators and the circuits to drive them. Case study material (including the NASA Mars Rover, the Milford Spider and the Furby) is used to show how practical robotic systems are designed. The result is a highly stimulating resource that will make learning, and building robotics and mechatronic systems easier. The Institutional versions have additional worksheets and multiple choice questions.

- Interactive Virtual Laboratories
- Little previous knowledge required
- Mathematics is kept to a minimum and all calculations are explained
- Clear circuit simulations


## DIGITAL ELECTRONICS V2.0



Virtual laboratory – Traffic Lights

*Digital Electronics* builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (opposite), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen. Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units. Sections on Boolean Logic and Venn diagrams, displays and chip types have been expanded in Version 2 and new sections include shift registers, digital fault finding, programmable logic controllers, and microcontrollers and microprocessors. The Institutional versions now also include several types of assessment for supervisors, including worksheets, multiple choice tests, fault finding exercises and examination questions.

## ANALOGUE FILTERS

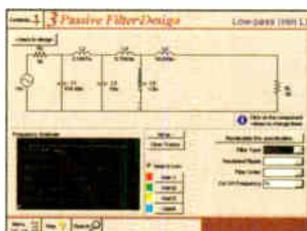

Filter synthesis

*Analogue Filters* is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev

## PRICES

Prices for each of the CD-ROMs above are:

(Order form on third page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student .....£45 inc VAT  
 Institutional (Schools/HE/FE/Industry).....£99 plus VAT  
 Institutional 10 user (Network Licence).....£249 plus VAT  
 Site Licence.....£499 plus VAT

# PICmicro TUTORIALS AND PROGRAMMING


## HARDWARE

### VERSION 3 PICmicro MCU DEVELOPMENT BOARD

*Suitable for use with the three software packages listed below.*

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices from the 12, 16 and 18 series PICmicro ranges. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

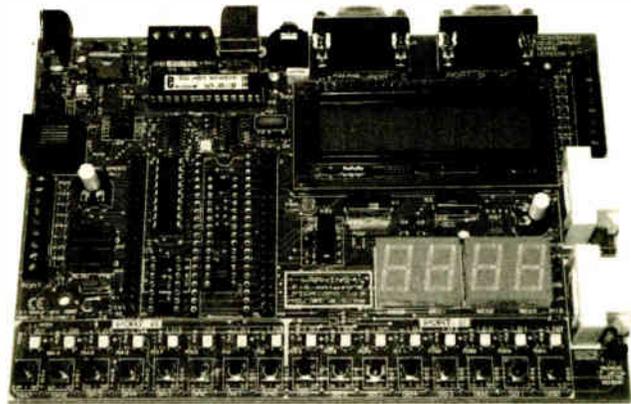- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 16 individual i.e.d.s, quad 7-segment display and alphanumeric l.c.d. display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- USB programmable
- Can be powered by USB (no power supply required)



**£158 including VAT and postage**

**supplied with USB cable and programming software**

## SOFTWARE


*Suitable for use with the Development Board shown above.*

### NEW V3
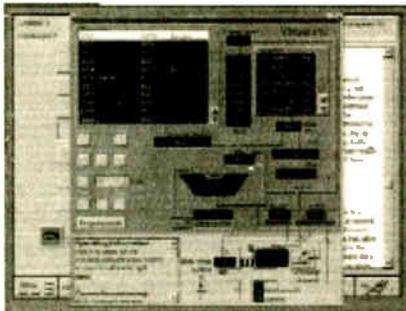
#### ASSEMBLY FOR PICmicro V3 (Formerly PICtutor)

Assembly for PICmicro microcontrollers V3.0 (previously known as PICtutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes. The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller. This is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.




Virtual PICmicro

#### 'C' FOR PICmicro VERSION 2

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

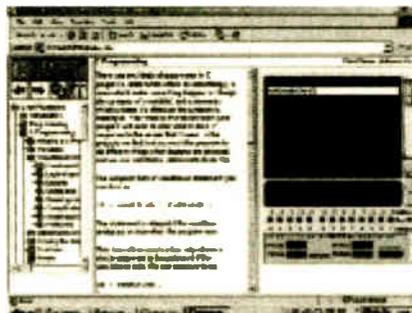- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running Windows 98, NT, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.


#### FLOWCODE FOR PICmicro V2

Flowcode is a very high level language programming system for PICmicro microcontrollers based on flowcharts. Flowcode allows you to design and simulate complex robotics and control systems in a matter of minutes.

Flowcode is a powerful language that uses macros to facilitate the control of complex devices like 7-segment displays, motor controllers and l.c.d. displays. The use of macros allows you to control these electronic devices without getting bogged down in understanding the programming involved.

Flowcode produces MPASM code which is compatible with virtually all PICmicro programmers. When used in conjunction with the Version 2 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols (ISO5807)
- Full on-screen simulation allows debugging and speeds up the development process
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- Professional versions include virtual systems (burglar alarm, buggy and maze, plus RS232, IrDa etc.).

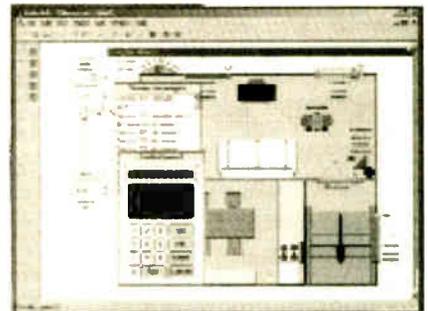

Burglar Alarm Simulation

## PRICES

Prices for each of the CD-ROMs above are:

*(Order form on next page)*


*(UK and EU customers add VAT at 17.5% to "plus VAT" prices)*

Hobbyist/Student  
Flowcode V2 Hobbyist/Student  
Institutional (Schools/HE/FE/Industry)  
Flowcode Professional  
Institutional/Professional 10 user (Network Licence)  
Site Licence

£45 inc VAT  
£57 inc VAT  
£99 plus VAT  
£99 plus VAT  
£300 plus VAT  
£599 plus VAT
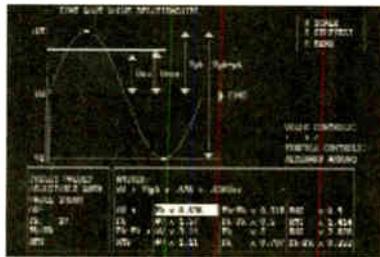
# TEACH-IN 2000 – LEARN ELECTRONICS WITH EPE

EPE's own Teach-In CD-ROM, contains the full 12-part Teach-In series by John Becker in PDF form plus the Teach-In interactive software (Win 95, 98, ME and above) covering all aspects of the series. We have also added Alan Winstanley's highly acclaimed *Basic Soldering Guide* which is fully illustrated and which also includes *Desoldering*. The Teach-In series covers: Colour Codes and Resistors, Capacitors, Potentiometers, Sensor Resistors, Ohm's Law, Diodes and L.E.D.s, Waveforms, Frequency and Time, Logic Gates, Binary and Hex Logic, Op.amps, Comparators, Mixers, Audio and Sensor Amplifiers, Transistors, Transformers and Rectifiers, Voltage Regulation, Integration, Differentiation, 7-segment Displays, L.C.D.s, Digital-to-Analogue. Each part has an associated practical section and the series includes a simple PC interface (Win 95, 98, ME ONLY) so you can use your PC as a basic oscilloscope with the various circuits.




Sine wave relationship values

A hands-on approach to electronics with numerous breadboard circuits to try out.


**£12.45 including VAT and postage.** Requires Adobe Acrobat (available free from the Internet – [www.adobe.com/acrobat](http://www.adobe.com/acrobat)).

**FREE WITH EACH TEACH-IN CD-ROM** – *Electronics Hobbyist Compendium* 80-page book by Robert Penfold. Covers Tools For The Job: Component Testing; Oscilloscope Basics.

**FREE BOOK WITH TEACH-IN 2000 CD-ROM**

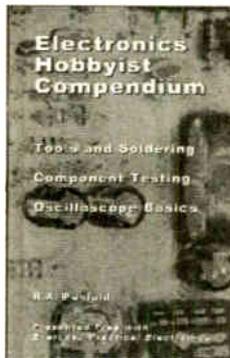

# DIGITAL WORKS 3.0

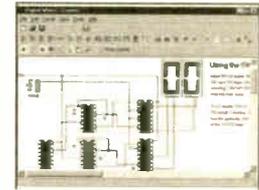

Counter project

*Digital Works Version 3.0* is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability ● Software for simulating digital logic circuits ● Create your own macros – highly scalable ● Create your own circuits, components, and i.c.s ● Easy-to-use digital interface ● Animation brings circuits to life ● Vast library of logic macros and 74 series i.c.s with data sheets ● Powerful tool for designing and learning. **Hobbyist/Student £45 inc. VAT. Institutional £99 plus VAT. Institutional 10 user £249 plus VAT. Site Licence £599 plus VAT.**

## ELECTRONICS IN CONTROL

Two colourful animated courses for students on one CD-ROM. These cover Key Stage 3 and GCSE syllabuses. **Key Stage 3:** A pictorial look at the Electronics section featuring animations and video clips. Provides an ideal introduction or revision guide, including multi-choice questions with feedback. **GCSE:** Aimed at the Electronics in many Design & Technology courses, it covers many sections of GCSE Electronics. Provides an ideal revision guide with Homework Questions on each chapter. Worked answers with an access code are provided on a special website.

**Single User £29 inc. VAT. Multiple User £39 plus VAT**  
Student copies (available only with a multiple user copy) £6 plus VAT  
(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

## MODULAR CIRCUIT DESIGN

**VERSION 3**

Contains a range of tried and tested analogue and digital circuit modules, together with the knowledge to use and interface them. Thus allowing anyone with a basic understanding of circuit symbols to design and build their own projects. Version 3 includes data and circuit modules for a range of popular PICs; includes PICAXE circuits, the system which enables a PIC to be programmed without a programmer, and without removing it from the circuit. Shows where to obtain free software downloads to enable BASIC programming. Essential information for anyone undertaking GCSE or "A" level electronics or technology and for hobbyists who want to get to grips with project design. Over seventy different Input, Processor and Output modules are illustrated and fully described, together with detailed information on construction, fault finding and components, including circuit symbols, pinouts, power supplies, decoupling etc.


**Single User £19.95 inc. VAT. Multiple User £34 plus VAT**  
(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 95/98/NT/2000/ME/XP, mouse, sound card, web browser.
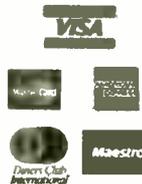
## Please send me: CD-ROM ORDER FORM

- Electronic Projects
- Electronic Circuits & Components V2.0
- Analogue Electronics
- Digital Electronics V2.0
- Filters
- Electronics CAD Pack
- Robotics & Mechatronics
- Assembly for PICmicro V2
- 'C' for PICmicro V2
- Flowcode V2 for PICmicro
- Digital Works 3.0

- Version required:
- Hobbyist/Student
  - Institutional
  - Institutional/Professional 10 user
  - Site licence



- PICmicro Development Board V2 (hardware)
- Development Board UK plugtop power supply
- Development Board 25-way connecting lead

- Teach-In 2000 + FREE BOOK
- Electronic Components Photos
- Electronics In Control – Single User
- Electronics In Control – Multiple User
- Modular Circuit Design – Single User
- Modular Circuit Design – Multiple User

Note: The software on each version is the same, only the licence for use varies.

Full name: .....

Address: .....

..... Post code: ..... Tel. No: .....

Signature: .....

I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

Please charge my Visa/Mastercard/Amex/Diners Club/Switch: £

Valid From: ..... Card expiry date: .....

Card No: ..... Switch Issue No. ....

Card Security Code ..... (The last 3 digits on or just under the signature strip)

## ORDERING ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world  
EU residents outside the UK add £5 for airmail postage per order

**Institutional, Multiple User and Deluxe Versions** – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU (European Union) country, then add 17½% VAT or provide your official VAT registration number).

Send your order to:  
Direct Book Service  
Wimborne Publishing Ltd  
408 Wimborne Road East  
Ferndown, Dorset BH22 9ND

To order by phone ring  
01202 873872. Fax: 01202 874562


Goods are normally sent within seven days

E-mail: [orders@wimborne.co.uk](mailto:orders@wimborne.co.uk)

Online shop:  
[www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

# Back to Basics – CMOS Logic Devices

Bart Trepak

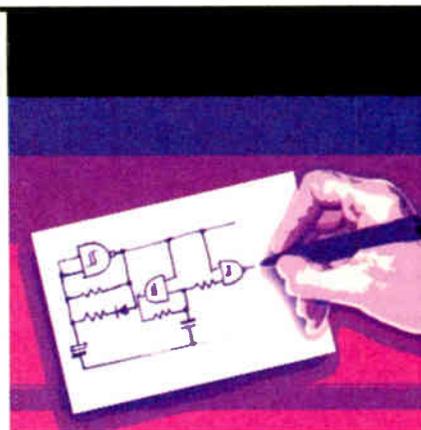

## Part 7 – Parking Radar and Telephone Switch

Illustrates how useful circuits can be designed simply using CMOS logic devices as the active components

**A**MONG the many gimmicks fitted to modern top-of-the-range cars, a parking radar would rank as one of the more useful. Presented now is a little unit that is both inexpensive and easily fitted to any car (even an “old banger”) and should help to prevent expensive mishaps!

The unit uses ultrasonics to determine the distance to an obstruction, the presence of which is indicated initially by an l.e.d. As the distance is reduced, a sounder emits a tone that rises in pitch to give a rough indication of the distance before impact!

As well as its intended use, this unit could also be suitable for a blind or partially sighted person to indicate the presence of obstacles in their path.

### Basic Operation

All radars operate on more or less the same principle – a signal is transmitted which bounces back from the target to a receiver, which measures the time taken for the echo to return.

For long distance radar, radio frequency signals are used, but for short range applications (up to a few tens of metres) ultrasonics offer a simpler method. Despite the frequency being beyond the range of human hearing, the speed of the sound is still roughly 300m/sec, or 1m every 3ms.

This sort of time is easily resolved using ordinary components. Ultrasonic beams are also moderately directional (typically

having a beam width of about 30°) so that only the object roughly in front of the transmitter should be detected.

The Parking Radar block diagram is shown in Fig.7.1. The master oscillator controls a 40kHz oscillator which drives an ultrasonic transmitter producing an ultrasonic beam directed at the target. The beam is reflected back, picked up by the ultrasonic receiver whose output signal is amplified. The resulting signal is used to set a bistable which has been previously reset at the start of the transmission.

The result is a pulsed output from the bistable. The duration of the pulses depends on the time between the transmission and its reception. Fig.7.2 illustrates the waveforms at various points in

the circuit when the distance is large, medium and small. At very large distances (not shown) the reflected signal is too small to set the bistable and so the output remains low, while at decreasing distances, the output spends more and more time in the logic high state.

This p.w.m. (pulse width modulated) waveform is fed to a simple integrator which produces a d.c. voltage proportional to the distance from the target. This could be read on a suitably calibrated meter but here it is used to control a voltage controlled oscillator (VCO) which produces an audio tone increasing in pitch as the distance to the target is reduced.

The range obtainable from such a system is limited by four factors: the power

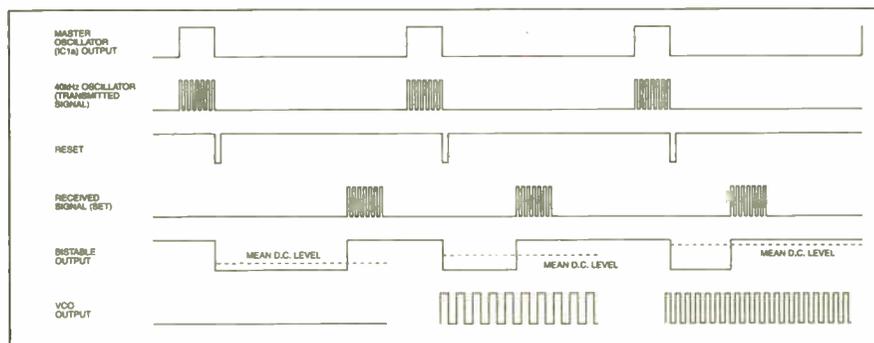


Fig.7.2. Waveforms at various points in the circuit when the “object” distance is large, medium and small


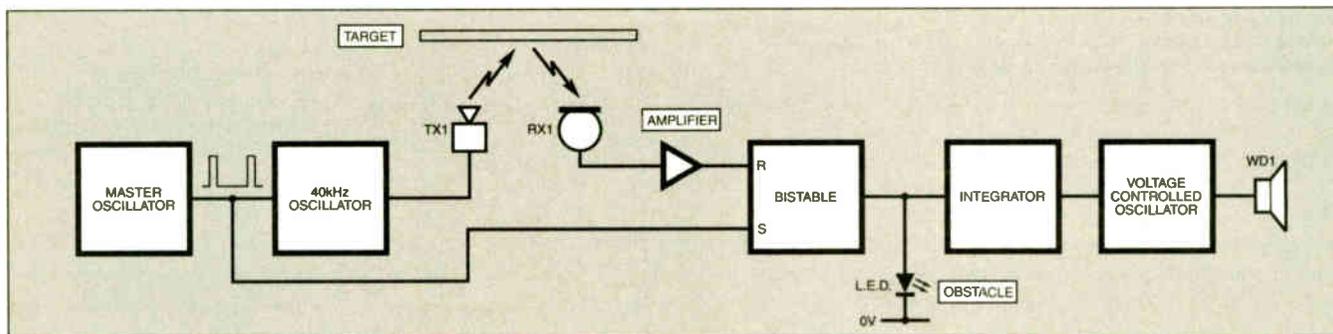


Fig. 7.1. Block schematic diagram for the Parking Radar. The Ultrasonic Transmitter and Receiver transducers are labelled TX1 and RX1 respectively

transmitted; the gain of the echo amplifier; target reflection efficiency; the direction in which the echo is reflected. This will obviously be different for large flat surfaces perpendicular to the beam than for irregular or angled surfaces which will tend to absorb or disperse the signal rather than reflect it towards the receiver.

Sophisticated ranging systems include a variable gain amplifier to amplify weak received signals more than strong ones to provide a constant amplitude return signal to get around these problems. Fortunately in this application, where a miss is as good as a mile, we are only interested in short ranges (normally less than one metre) which make such measures largely unnecessary, even with poorly reflecting surfaces.

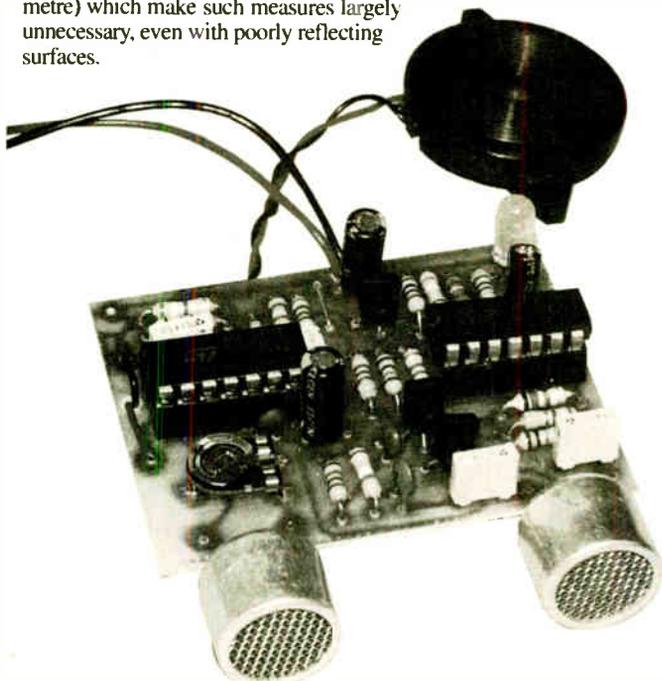

### Circuit Diagram

The complete circuit diagram for the Parking Radar is shown in Fig.7.3.

The master oscillator formed around Schmitt NAND gate IC1a produces short positive-going pulses of about 0.4ms duration every 4ms, as defined by components C1, R1, R2 and D1. When IC1a output pin 10 goes high, the oscillator built around IC1b is enabled and oscillates at a frequency of 40kHz, adjustable by preset VR1. IC1c inverts the output of IC1b, and transducer TX1 is driven in anti-phase by both gates for maximum power output.

When the output of IC1a goes low, it switches off the transmission. It also generates a pulse across capacitor C7, which triggers the bistable formed around IC2a and IC2b.

The echo signal reflected from the target is picked up by transducer RX1 and amplified by the circuit around transistors TR1 and TR2. The reset input of the bistable is held just above the logic threshold of the gate by the potential divider formed by resistors R8 and R9. Transistor TR2's collector (c) is coupled to this input via capacitor C8. The output of IC2a (and thus IC2c) is therefore a rectangular waveform which goes low when the transmitted signal ends and high when it is received after being reflected.

The distance range at which the amplified echo signal is large enough to reset the bistable is about one metre with the components shown, although this can be varied somewhat by altering the value of R9. At this range i.e.d. D2, which is controlled by the output from IC1c, begins to turn on giving an indication of the presence of an obstacle.

The output from IC2c also feeds into the integrator formed around R12 and C9. The voltage across C9 rises according to the time for which the output of IC2c is high. It increases as the range decreases.

A simple voltage controlled oscillator (VCO) is formed by IC1d and its associated components. As the voltage across C9 rises, transistor TR3 is turned on harder and passes a greater current, causing capacitor C10 to charge faster. When the voltage at the input of IC1d falls below the lower logic threshold, the output goes high, discharging C10 via D3 and R16.

Although the discharge time remains constant, the charge time falls and consequently the oscillation frequency rises with increased current flowing into the base (b) of TR3. This is reproduced by the piezo buzzer WD1 as a tone with a rising pitch. The frequency varies from low frequency clicks at a range of around 1m, to about 300Hz when the range has fallen to 5cm. Resistor

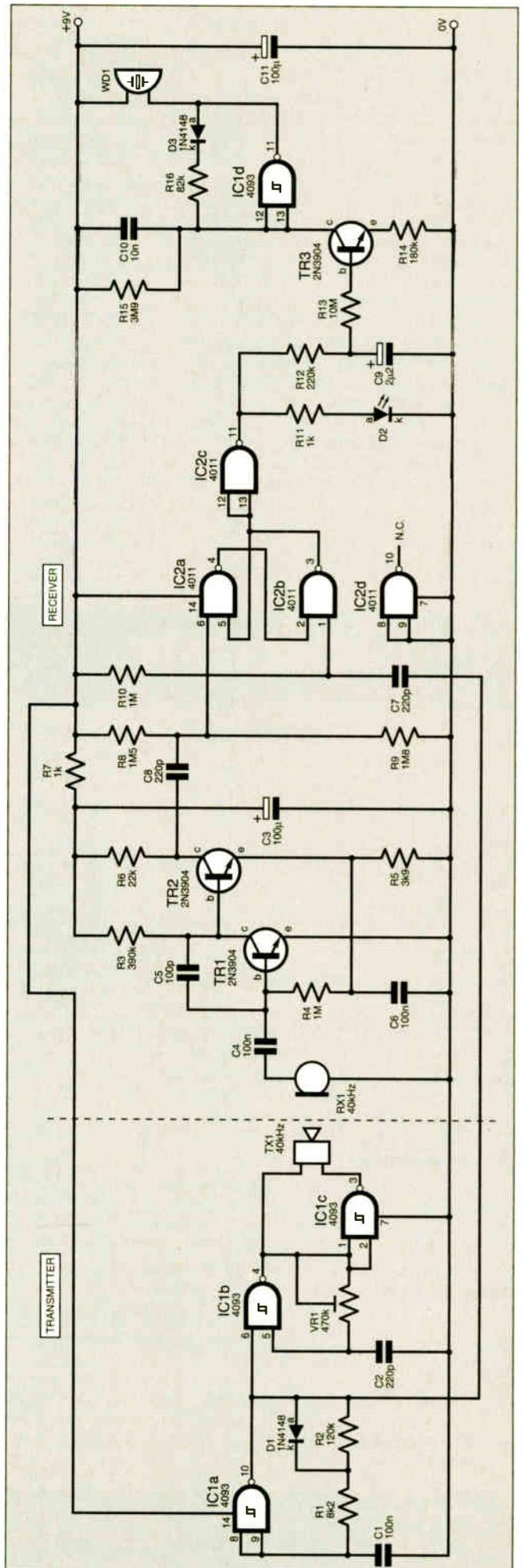


Fig.7.3. Full circuit diagram for the Parking Radar

R15 is included to suppress oscillation due to leakage when TR3 is off.

## Construction

Printed circuit board component and track layout details are shown in Fig.7.4. This board is available from the *EPE PCB Service*, code 533.

The board should be assembled in order of ascending component size. Normal precautions should be observed regarding component orientation for diodes, transistors etc. and when handling the CMOS i.c.s. Use sockets for i.c.s, but do not insert the i.c.s. until the board has been fully checked.

Pads for the battery connector are provided although some form of d.c. plug and socket may be more appropriate in this application. Care should be taken to ensure the correct polarity of the supply.

Transducers TX1 and RX1 are not interchangeable in this application. Their function should be marked on their case. The pin connected to the case is the 0V terminal. The transducers should be mounted on the p.c.b. pads provided, not on extension leads. Although the prototype used ordinary transducers, waterproof ones are preferable.

The only setting up required is the adjustment of VR1 to obtain a 40kHz signal across TX1. This is best done using an oscilloscope but in the absence of one, the voltage across RX1 or at TR2 collector (c) can be monitored and VR1 adjusted for maximum echo signal strength.

The circuit is fairly uncritical in component values but the values of R8 or R9 may need to be altered to ensure that the quiescent voltage (when no signal is present) at their junction is above the logic high threshold of IC2a. Typically, this means greater than about 5V with a 9V supply.

## Enclosures

The p.c.b. should be housed in a suitable enclosure mounted somewhere on the back of the car. The type will depend on individual circumstances. It needs to protect the components from moisture and dampness. Added protection can be given by coating the p.c.b. with a "conformal" spray.


The l.e.d. and buzzer are mounted in a separate case connected back to the p.c.b. If preferred, the buzzer may be connected to the 0V line rather than to +9V, which will enable a 3-core cable to be used for the overall assembly interconnections.

Since the unit has a minimum range indication of about 5cms, note that the warning tone will not increase in frequency once this

distance is reached. The circuit therefore does not give an indication of distance down to zero as this will normally be indicated by a crunching sound!

The maximum range is around one metre (depending on the target). This unit is not suited to modifying for greater distance detection.

The circuit should be powered by a 9V battery, although operation at 12V is also possible. The total current drawn at 9V is around 1.5mA, rising to some 10mA when sounding, so that an on/off switch is recommended. This can be a panel mounted type which can be switched on manually or by a relay activated by the reversing light when the reverse gear is selected if automatic switching is preferred. For the other applications mentioned, different arrangements for this will no doubt need to be devised.

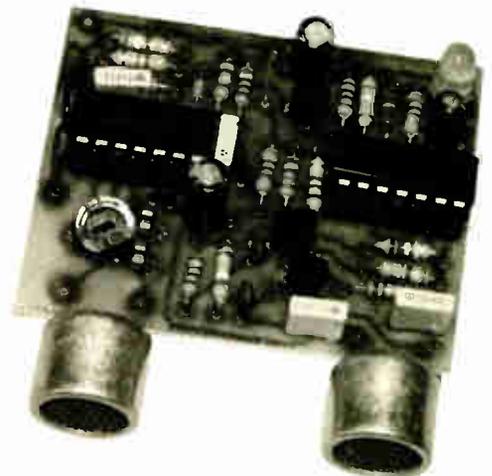

# COMPONENTS

## PARKING RADAR

### Resistors

|        |            |     |      |
|--------|------------|-----|------|
| R1     | 8k2k       | R8  | 1M5  |
| R2     | 120k       | R9  | 1M8  |
| R3     | 390k       | R12 | 220k |
| R4,R10 | 1M (2 off) | R13 | 10M  |
| R5     | 3k9        | R14 | 180k |
| R6     | 22k        | R15 | 3M9  |
| R7,R11 | 1k (2 off) | R16 | 82k  |

### Potentiometer

|     |                      |
|-----|----------------------|
| VR1 | 470k skeleton preset |
|-----|----------------------|

### Capacitors

|          |                                   |
|----------|-----------------------------------|
| C1,C4,C6 | 100n polyester or ceramic (3 off) |
| C2,C7,C8 | 220p disc ceramic (3 off)         |
| C3,C11   | 100µ radial elect. 16V (2 off)    |
| C5       | 100p disc ceramic                 |
| C9       | 2µ2 radial elect. 16V             |
| C10      | 10n polyester or ceramic          |

### Semiconductors

|            |                             |
|------------|-----------------------------|
| D1,D3      | 1N4148 signal diode (2 off) |
| D2         | 5mm red l.e.d.              |
| TR1 to TR3 | 2N3904 npn transistor       |
| IC1        | 4093 quad Schmitt NAND gate |
| IC2        | 4011 quad NAND gate         |

### Miscellaneous

|     |   |
|-----|---|
| TX1 | 40kHz ultrasonic transmitter (see text) |
| RX1 | 40kHz ultrasonic receiver (see text)    |
| WD1 | piezo sounder                           |

Printed circuit board, available from the *EPE PCB Service*, code 533; 14-pin d.i.l. socket (2 off); cases to suit; 9V battery and clip (see text); connecting wire; solder etc.

Approx. Cost  
Guidance Only

**£15**

excl case and batts

See  
SHOP  
TALK  
page

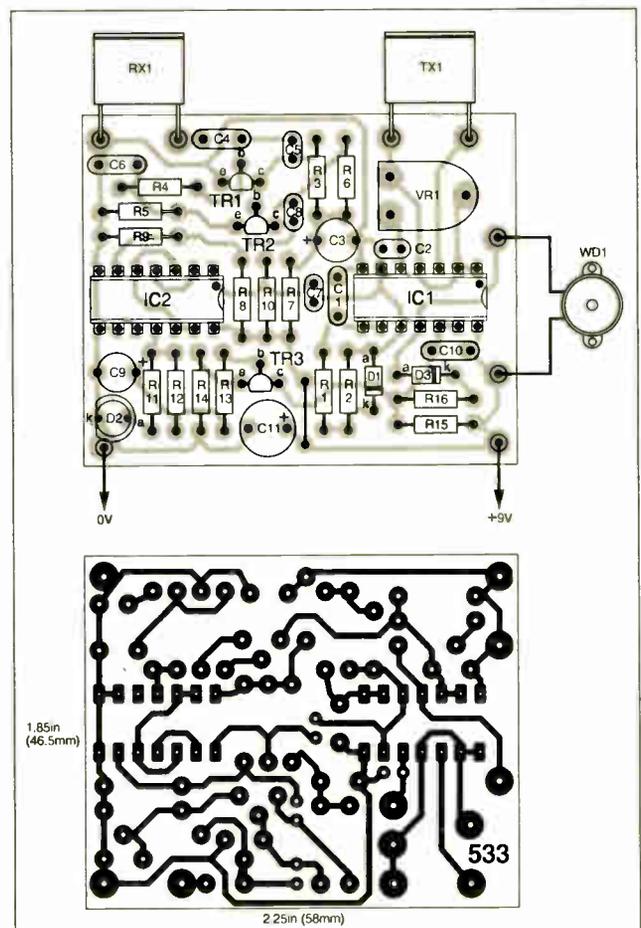


Fig.7.4. Printed circuit board component layout, full underside copper foil master and off-board wiring for the Parking Radar module



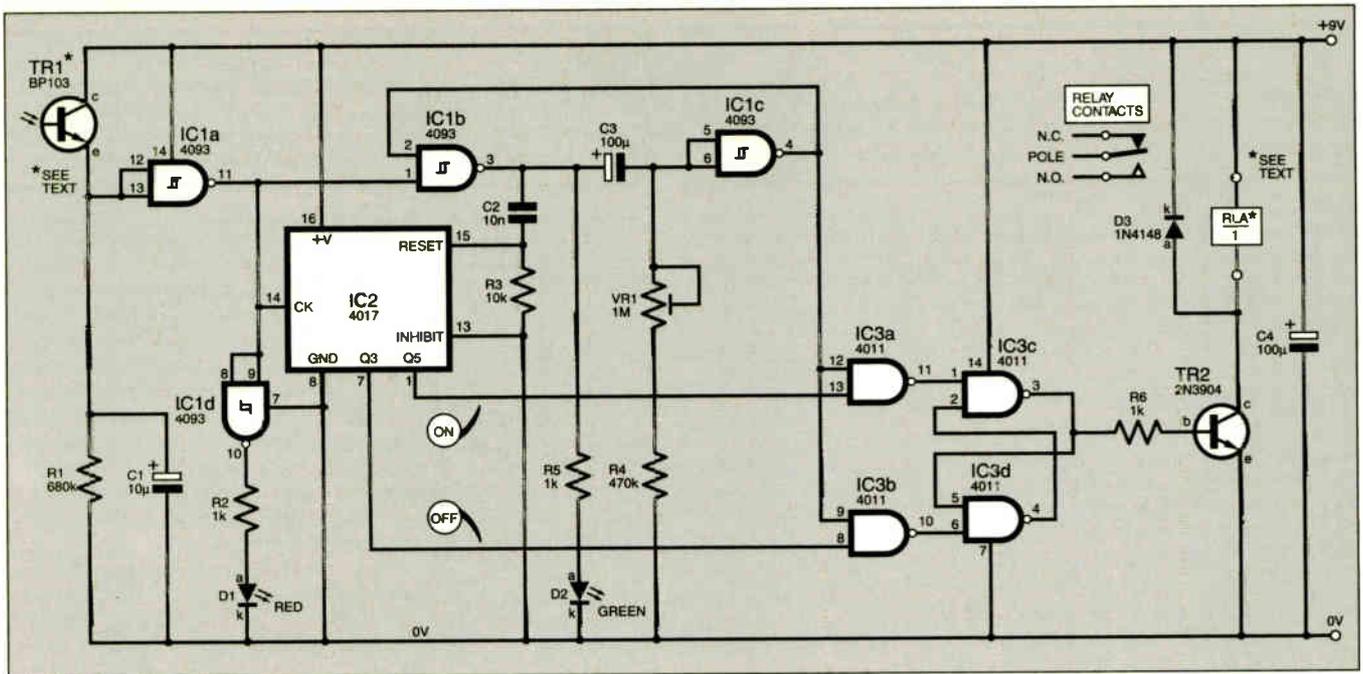


Fig. 7.6. Complete circuit diagram for the Telephone Switch. No direct connection to the phone line is required. Two options of phone interfacing can be made, one optical, the other audio


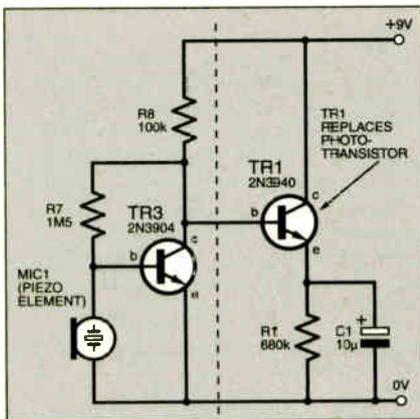


Fig. 7.7. Alternative audio input circuit

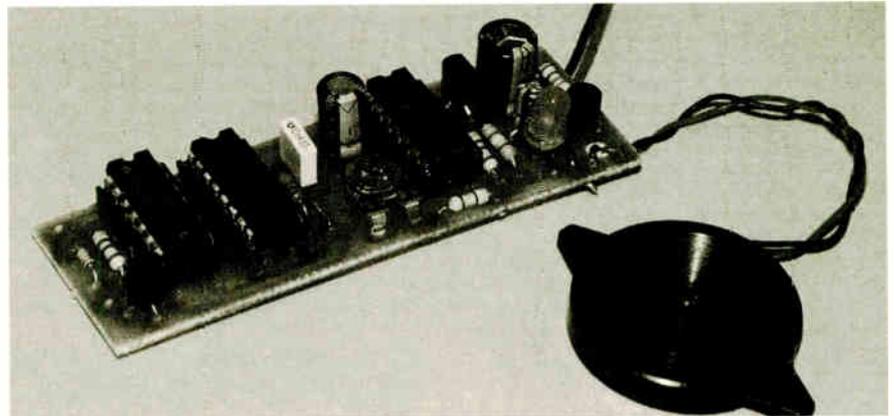

Completed Telephone Switch incorporating the audio input circuit

## Circuit Diagram

The complete circuit diagram for the Telephone Switch is shown in Fig. 7.6. The circuit has been designed so that no direct connection to the phone line is required. Two choices of interface can be made, one optical, the other audio.

The optical interface can be via a commercial plug-in extension ringer unit. As well as an audio output, these normally have an l.e.d. which flashes in time with each ring. In Fig. 7.5, a phototransistor, TR1, detects the flashing l.e.d. and its output is fed to the inputs of Schmitt NAND gate IC1a.

If an extension ringer is not available, the audio input circuit of Fig. 7.7 may be used instead. The phone rings, detected by microphone MIC1, are amplified by transistor TR3 and fed to an npn transistor used as TR1 in place of the phototransistor.

Whichever method is used, when the telephone rings, TR1 will switch on causing capacitor C1 to charge and the inputs of IC1a to go high. This gate is connected as an inverter so that its output will go low, triggering the monostable built around IC1b and IC1c.

The values of resistor R1 and capacitor C1 are chosen so that the circuit will not respond to the ending of individual rings, and so the output of IC1a will therefore remain low throughout the overall time that the telephone rings.

The output from IC1a also feeds to IC1d, which drives l.e.d. D1 via buffer resistor R2. The l.e.d. indicates when the circuit responds to a call and it should remain on (and not flash) until the call is terminated.

When the monostable is triggered, the output of IC1b goes high (indicated by l.e.d. D2). This causes counter IC2 to be reset via C2, and the output of IC1c to go low, triggering via C3. With IC1c output low, gates IC3a and IC3b are disabled, preventing the output bistable formed by gates IC3c and IC3d, from changing state.

## Time Out

Each time the call is terminated the output of IC1a will go high, switching off l.e.d. D1 and causing the counter to advance but not affect the monostable, which remains in its triggered state with l.e.d. D2 turned on.

Eventually, when the monostable times out after a period determined by the value of C3 and R4/VR1, the output of IC1c will go high, enabling gates IC3a and IC3b. If three or five calls have been received by this time, then counter outputs Q3 or Q5 will be high, causing the output of either gate IC3b or IC3a to go low.

If gate IC3a goes low, the bistable will be set with the output of IC3c going high. This switches on TR2 via R6 and turns on relay RLA, switching on the supply to the load to be controlled.

If IC3b's output goes low, however, the bistable will be cleared and the output of IC3c will go low, switching off TR2 and the relay. Diode D3 inhibits back-e.m.f. generation when the relay switches off.

If any other number of calls, except three or five, are received by the time that the monostable times out, counter outputs Q3 and Q5 will be low and the outputs of IC3b and IC3c will remain in their previous state, as will the relay. The circuit stays in this state until another call is received, which will again reset the counter and the operation will begin again. The output circuit will, however, only respond to three or five rings.

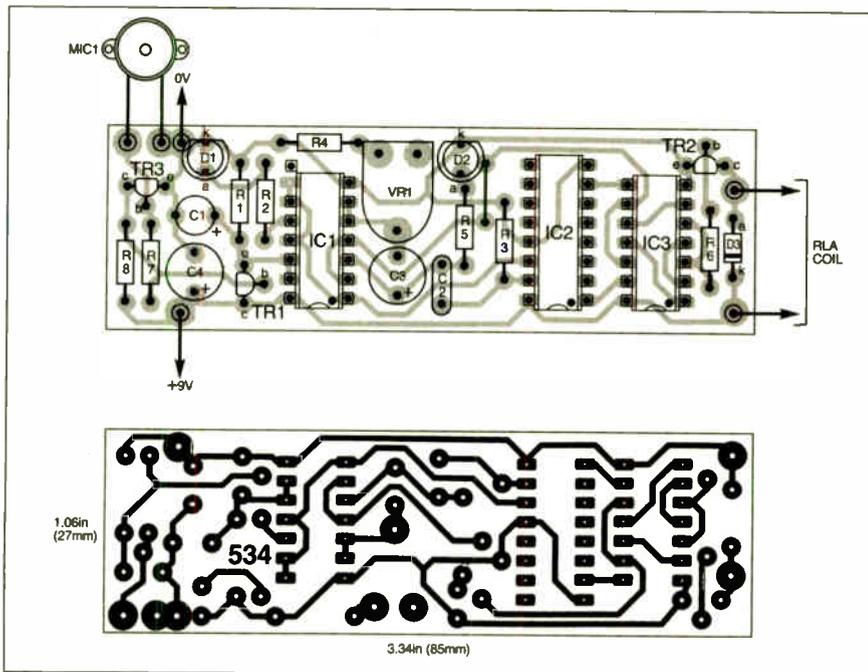


Fig. 7.8. Printed circuit board component layout, full-size copper foil master and off-board wiring details for the "audio" version of the Telephone Switch

## Power Supply

The unit can operate from a range of d.c. supply voltages, but 9V is suggested. It draws virtually no current (especially if the phototransistor input version is built) when no calls are being received. Current consumption will rise slightly when a call is received due mainly to the l.e.d.s, but will rise dramatically when the relay is energised.

A 9V battery supply can be used when testing the circuit, but for serious use a 9V d.c. mains adaptor is recommended, especially if the relay is to be left energised for long periods. A low voltage mains adaptor of the type used for powering small appliances such as radios and calculators would be ideal. *Do not exceed a supply of 15V d.c.*

## Construction

Printed circuit board component and track layout details are shown in Fig. 7.8. This board is available from the *EPE PCB Service*, code 534.

The p.c.b. will accommodate either version of the input circuit. If the phototransistor version is built, the microphone, TR3 and resistors R7 and R8 should be left out and the phototransistor fitted in place of TR1.

The phototransistor specified is housed in an l.e.d.-type package with only the collector and emitter terminals connected. There is no base lead and so the centre pad (b) on the p.c.b. for TR1 should be left unconnected. Note that the collector (c) terminal is adjacent to the flat area on the rim of the package so that this lead should go to the pad connected to the positive battery supply.

It will probably be necessary to mount the phototransistor on flying leads and these should be kept as short as possible. One possible method of coupling the phototransistor to the l.e.d. on the extension ringer is to use a clear epoxy resin to ensure a good light path between the two components. Once this has set, it should

be painted black or covered with an opaque material to ensure that ambient light does not upset the operation of the circuit.

## Flying Leads

The board should be assembled and checked as stated previously. Note that the relay and microphone (if used) should be connected to the allocated pads by means of flying leads. The microphone is a piezo type more often encountered in designs as a sounder (it can work in either mode). Although the type used in the prototype had red and black leads, it may be connected either way around.

If possible, these leads should not be extended as this could make the circuit sensitive to stray electrical fields. The microphone should be placed close to a telephone or glued to an extension ringer to ensure that the circuit responds. In noisy environments it is possible that the circuit could be triggered by other random sounds and care should be taken to ensure that this cannot happen by shielding the microphone. If these efforts prove unsuccessful, the phototransistor option should be used.

## Relay

The relay should be chosen to suit the supply voltage, although in practice most relays will operate from a range of voltages. Most 12V relays for example will operate quite satisfactorily from a supply of 9V to 15V. A higher voltage rating is to be preferred as these will generally have a higher coil resistance and therefore draw a lower current when operating.

The relay contacts must be rated for the appliance to be switched. Do not connect the relay to an a.c. mains powered appliance unless you are suitably qualified or supervised.

Depending on the application, it may be desirable to mount the circuit in a box. The choice of case is yours. In may then be more convenient to mount the

l.e.d.s on the panel, in which case the leads may simply be extended as required (although in use they are not really required as, hopefully, there will not be anyone at home to observe them!). Holes will also be required for the microphone or photo transistor as well as sockets for a d.c. supply.

## Testing

The circuit may be tested and set up by connecting a 9V battery and a temporary l.e.d. (in series with a suitable ballast resistor of say 1k) across the relay coil terminals. When the microphone is tapped (or the phototransistor illuminated), both l.e.d.s D1 and D2 should light. D1 should switch off shortly afterwards while D2 should remain on.

The circuit should be activated a number of times by tapping the microphone or switching on the phototransistor, making sure each time that D1 switches off again. If five such "inputs" are made within the time D2 is on, the temporary l.e.d. should light (or the relay switch on) when D2 switches off. Repeating the procedure with only three "inputs" should cause the output to switch off, while any other number of "inputs" made within the time that D2 is on should be ignored by the circuit.

Once this has been done, it would be best to "phone a friend" or at least get him to phone you. When your phone rings, make sure that l.e.d. D1 only lights once and remains on for the duration of the ringing call. If it follows the individual rings by switching off each time, the value of R1 or C1 should be increased.

Do not make the values of R1 or C1 much larger than necessary to achieve this because the l.e.d. may then remain on for too long after the call has terminated and the circuit could fail to recognise the next call. The components specified should not need to be altered in the majority of cases.

It then only remains to set preset VR1 for a monostable time (D2 on) sufficiently long to enable five separate calls to be made to the number. This will obviously depend on how many digits must be dialled and if a re-dial facility is used, but the time should be made as short as possible to minimise the possibility of false switching.

Remember that extra digits such as area codes may need to be dialled, especially if the device is to be used from abroad. Of course, this unit has been designed to switch the output on after five calls and off after three but this could be easily changed by utilising the other outputs of the 4017 counter.

**Next Month:** Weather Vane Repeater and a Noughts & Crosses Emigma (see below).



# Circuit Surgery

Ian Bell



Following on from last month, our "consultant surgeon" looks into some chopper op.amp i.c.s and offers some circuit advice on how to use them

**L**AST month, in response to one of the threads on the *EPE Chat Zone*, we looked at the theory of chopper stabilised amplifiers (also known as auto-zeroing amplifiers). These circuits have very low drift and are therefore suitable for use with very low frequency signals, where slow changes in the amplifier's offsets with time due to factors such as temperature and power supply fluctuations cannot be easily blocked or filtered out.

We discussed how these circuits achieved high precision by continuously nulling their own offsets. This month we will look at a couple of real chopper amplifier chips, with which you might like to experiment.

## For the Chop

The TLC2654 is a high-precision chopper-stabilized operational amplifier from Texas Instruments. It has very good d.c. precision, featuring an extremely low change in offset voltage with temperature of around  $0.003\mu\text{V}/^\circ\text{C}$ , and a very low offset of around  $1\mu\text{V}$  maximum.

These figures are much better than can be achieved with ordinary operational amplifiers. In addition, as we explained last month, low-frequency noise is significantly reduced compared with ordinary operational amplifiers by the chopper stabilization due to the reduction of  $1/f$  noise.

The TLC2652, another chopper-amp from Texas Instruments, has even better noise performance than the TLC2654, but less precision. You have to choose the best chip for the job you want it to do. Of course other manufacturers make chopper stabilised amplifiers too, such as the National Semiconductor LMV2011, the Linear Technology LTC1050, the Analog Devices AD8551 and the Microchip TC7650. All have different combinations of capabilities and features. Both the TLC2652 and TLC2654 are available from Farnell in 8-pin d.i.l. packages for around £4. They also stock the LTC1050 and one or two other choppers.

The TLC2652 has a very high input impedance CMOS input stage and is particularly suitable for low-level signal processing applications such as strain gauges, thermocouples, and other transducer amplifiers. It has a default chopping frequency of 450Hz.

The higher chopping frequency of the TLC2654, compared with the TLC2652, accounts for the better noise performance and bandwidth, which covers a frequency spectrum from near d.c. to 10kHz, with best performance up to 5kHz. Like the TLC2652, it is suitable for wide-bandwidth low frequency and subsonic applications and is also appropriate for use with strain gauges and thermocouples.

## A Packaged Deal

Both the TLC2652 and TLC2654 are available in 8-pin and 14-pin d.i.l. versions and have the pinouts shown in Fig.1. On the 8-pin version you get the dual power supply ( $V_{DD+}$  and  $V_{DD-}$ ), differential inputs (IN- and IN+), and output (OUT) that you would expect with any operational amplifier, plus three other less familiar pins:  $C_{XA}$ ,  $C_{XB}$  and CLAMP.

These are for the nulling capacitors and clamping feature, which we will look at in more detail later. The 14-pin version includes provision for an external clock (INT/EXT, CLK IN, CLK OUT) and a special connection point for the nulling capacitors (C RETURN).

A number of other chopper stabilized op.amps have the same or similar pin connections, for example the TC7650. The LTC1050 is different: it does not need external capacitors so pin 1 and pin 8 are no-connections and has a clock input on pin 5.

The  $C_{XA}$  and  $C_{XB}$  pins are used to connect two capacitors which are required for operation of these amplifiers. The capacitors are used for holding the nulling trim voltage, as explained last month.

However, the user does not have to control the chopping process in any way and these devices can simply be used as operational amplifiers. The chopping frequency is fixed by the internal oscillator and is invisible to the user. The 14-pin versions do provide the user with more control – the chopping can be driven from an external clock.

The capacitors connected to  $C_{XA}$  and  $C_{XB}$  should be in the range of  $0.1\mu\text{F}$  to  $1\mu\text{F}$  and located as close as possible to the pins. On the 8-pin versions of the chips the other end of each capacitor is connected to either  $V_{DD-}$  or  $V_{DD+}$  (see Fig. 2). On the 14-pin version there is a special C RETURN pin to which the capacitors can be connected. In applications needing a fast response use high-quality film capacitors such as mylar, polystyrene, or polypropylene. In other applications, ceramic or other low-grade capacitor are satisfactory.

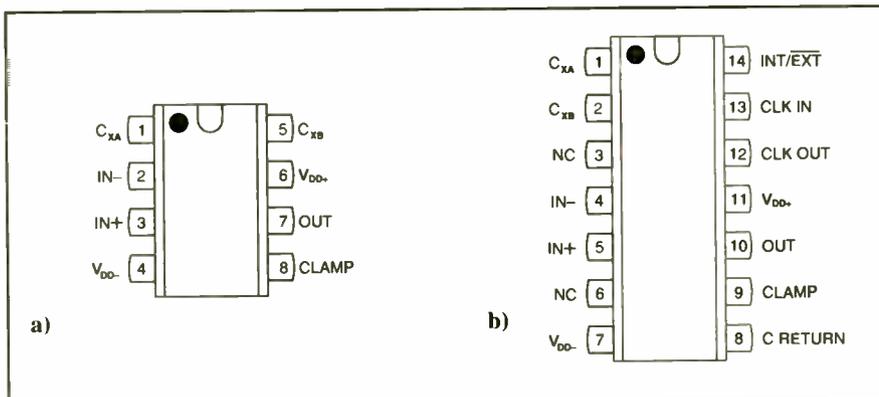


Fig.1. (a) Pinout connections for the TLC2652 and TLC 2654 8-pin version and (b) the pinout details for the 14-pin version

## In Response

One problem with chopper amplifiers that we did not discuss last month is their response to overload conditions, which occur when very large input signals push the output into saturation at one of the supply rails. Under these conditions the circuit is no longer a linear amplifier and is therefore unable to find the correct nulling voltage to compensate for offsets.

Thus, after an overload, a chopper amp may take some time to recover to full performance. The CLAMP pin provides a means by which the internal circuitry can detect overload conditions and hence prevent the amplifier from becoming heavily saturated. This in turn speeds up recovery once the overload condition is removed.

If clamping is required the CLAMP pin is connected to the inverting input IN- (in parallel with the closed-loop feedback resistor) (see Fig.3). If connected the clamp is automatically activated when the output is approximately 1V from either supply rail.

When activated the clamp reduces the gain of the amplifier and the output is prevented from going into saturation. Since the output must source or sink current through the clamp circuitry the maximum output voltage swing is slightly reduced when the clamp is used.

## On Guard

In order to get the full benefit of high precision capabilities of chopper stabilised amplifiers, good circuit board layout is required. Problems are caused by leakage across the p.c.b. (printed circuit board), so thorough cleaning and drying after construction is important.

Also, a useful technique is to include an input guard in the p.c.b. layout. A guard is a p.c.b. copper track in a ring surrounding the input terminals, which absorbs leakage currents. The ring connects to a low impedance point ideally at the same common mode voltage as the inputs. The concept of the p.c.b. guard ring layout is shown in Fig.4; the actual layout for a given application will depend on the i.c. package used.

Chopper stabilised operational amplifiers can be used in the same circuit configurations as ordinary op. amps, including

those for inverting and non-inverting amplifiers. These are shown in Fig.5. These schematics include the guard ring (the circles near the inputs). Two circles are drawn on the schematic as both inputs are guarded, but only one ring is created on the p.c.b., as shown in Fig. 4.

Of course, with the TLC2652 and TLC2654, and other choppers with external nulling capacitors, these are present whereas they may not be in a normal op. amp circuit. You may also use the clamp facility, but this is not included in Fig.5. If required, connect the clamp (pin 5) to the inverting input (pin 2) as shown in Fig.3.

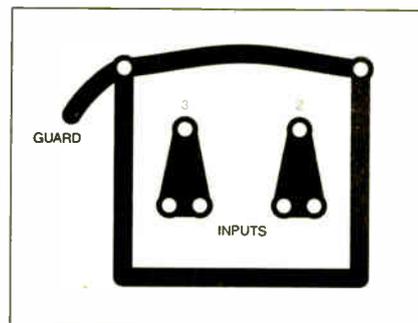


Fig.4. Input "guard ring" on a printed circuit board tracking

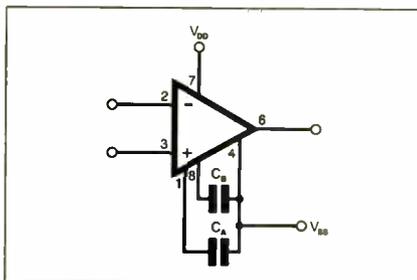


Fig.2. Connection details for the nulling capacitors

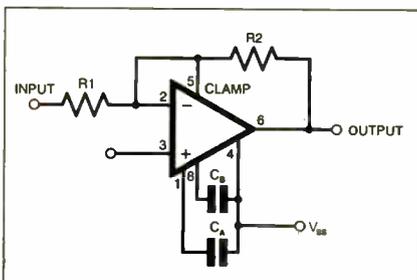


Fig.3. If clamping (overload protection) is required, the CLAMP pin is connected to the inverting input IN- pin

The gains of the circuits in Fig.5 are set by the values of resistors R1 and R2 in the usual way. The gain is  $R2/R1$  for the inverting amplifier and  $1+(R2/R1)$  for the non-inverting amplifier. Resistor R3 does not contribute to the gain setting, but is present to help minimise offsets. The value

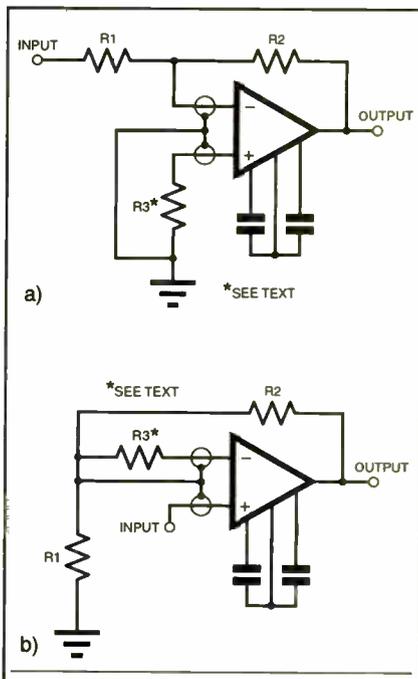


Fig.5. Circuit arrangement for (a) an inverting amplifier and (b) a non-inverting amplifier. Note the input guard ring connections and nulling capacitors

of R3 should be equal to the parallel combination of R1 and R2, that is  $(R1 \times R2)/(R1 + R2)$ . This value ensures that the impedance of the external circuit viewed from each input is equal, to minimise the difference in voltage drops due to input bias currents. □

## Obtaining EPE

An initiative in the UK is designed to help you obtain your favourite magazines from newsagents. Called *Just Ask!* its aim is to raise awareness that newsagents can stock, order and often home deliver magazines.

Don't Miss Out  
**Just ask!**  
Your local newsagent to order this magazine

**EVERYDAY PRACTICAL ELECTRONICS**  
THE ONLY MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PRODUCTS

## NEWSAGENTS ORDER FORM

Please reserve/deliver a copy of *Everyday Practical Electronics* for me each month

Signed .....

Name and Address .....

Post Code ..... Tel .....

*Everyday Practical Electronics* is published on the second Thursday of each month and distributed S.O.R. by COMAG  
Make sure of your copy of *EPE* each month – cut out or photostat this form, fill it in and hand it to your newsagent.

FREE *Electronics Hobbyist Compendium* book with Teach-In 2000 CD-ROM



## EPE TEACH-IN 2000 CD-ROM

The whole of the 12-part *Teach-In 2000* series by John Becker (published in *EPE* Nov '99 to Oct 2000) is now available on CD-ROM. Plus the *Teach-In 2000* interactive software (Win 95, 98, ME and above) covering all aspects of the series and Alan Winstanley's *Basic Soldering Guide* (including illustrations and Desoldering).

*Teach-In 2000* covers all the basic principles of electronics from Ohm's Law to Displays, including Op.Amps, Logic Gates etc. Each part has its own section on the interactive software where you can also change component values in the various on-screen demonstration circuits.

The series gives a hands-on approach to electronics with numerous breadboard circuits to try out, plus a simple computer interface (Win 95, 98, ME only) which allows a PC to be used as a basic oscilloscope.

ONLY **£12.45** including VAT and p&p

Order code Teach-In CD-ROM

## Robotics

### INTRODUCING ROBOTICS WITH LEGO MINDSTORMS

Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various "click-together" components supplied in the basic RIS kit. Then explains in simple terms how the "brain" of the robot may be programmed on screen using a PC and "zapped" to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Details building and programming instructions provided, including numerous step-by-step photographs.

288 pages - large format Order code BP901 £14.99

### MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS - Robert Penfold

Covers the Vision Command System

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using Lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with 'waiter service' when you clap your hands, perform tricks, 'see' and avoid objects by using 'bats radar', or accurately follow a line marked on the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit.OCX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an 'intelligent' sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

298 pages Order code BP902 £14.99

### ANDROIDS, ROBOTS AND ANIMATRONS - Second Edition - John Iovine

Build your own working robot or android using both off-the-shelf and workshop constructed materials and devices. Computer control gives these robots and androids two types of artificial intelligence (an expert system and a neural network). A lifelike android hand can be built and programmed to function doing repetitive tasks. A fully animated robot or android can also be built and programmed to perform a wide variety of functions.

The contents include an Overview of State-of-the-Art Robots; Robotic Locomotion; Motors and Power Controllers; All Types of Sensors; Tilt; Bump; Road and Wall Detection; Light; Speech and Sound Recognition; Robotic Intelligence (Expert Type) Using a Single-Board Computer Programmed in BASIC; Robotic Intelligence (Neutral Type) Using Simple Neural Networks (Insect Intelligence); Making a Lifelike Android Hand; A Computer-Controlled Robotic Insect Programmed in BASIC; Telepresence Robots With Actual Arcade and Virtual Reality Applications; A Computer-Controlled Robotic Arm; Animated Robots and Androids; Real-World Robotic Applications.

224 pages Order code MGH1 £16.99

# DIRECT BOOK SERVICE

NOTE: ALL PRICES INCLUDE UK POSTAGE

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order to your door. Full ordering details are given on the last book

For a further selection of books see the next two issues of *EPE*.

## Radio

### BASIC RADIO PRINCIPLES AND TECHNOLOGY

Ian Poole

Radio technology is becoming increasingly important in today's high technology society. There are the traditional uses of radio which include broadcasting and point to point radio as well as the new technologies of satellites and cellular phones. All of these developments mean there is a growing need for radio engineers at all levels.

Assuming a basic knowledge of electronics, this book provides an easy to understand grounding in the topic.

Chapters in the book: Radio Today, Yesterday, and Tomorrow; Radio Waves and Propagation; Capacitors, Inductors, and Filters; Modulation; Receivers; Transmitters; Antenna Systems; Broadcasting; Satellites; Personal Communications; Appendix - Basic Calculations.

263 pages Order code NE30 £18.99

### PROJECTS FOR RADIO AMATEURS AND S.W.L.S.

R. A. Penfold

This book describes a number of electronic circuits, most of which are quite simple, which can be used to enhance the performance of most short wave radio systems.

The circuits covered include: An aerial tuning unit; A simple active aerial; An add-on b.f.o. for portable sets;

A wavetrap to combat signals on spurious responses; An audio notch filter; A parametric equaliser; C.W. and S.S.B. audio filters; Simple noise limiters; A speech processor; A volume expander.

Other useful circuits include a crystal oscillator, and RTTY/C.W. tone decoder, and a RTTY serial to parallel converter. A full range of interesting and useful circuits for short wave enthusiasts.

92 pages Order code BP304 £4.45

### AN INTRODUCTION TO AMATEUR RADIO

I. D. Poole

Amateur radio is a unique and fascinating hobby which has attracted thousands of people since it began at the turn of the century. This book gives the newcomer a comprehensive and easy to understand guide through the subject so that the reader can gain the most from the hobby. It then remains an essential reference volume to be used time and again. Topics covered include the basic aspects of the hobby, such as operating procedures, jargon and setting up a station. Technical topics covered include propagation, receivers, transmitters and aerials etc.

150 pages Order code BP257 £5.49

## Computers and Computing

### THE INTERNET FOR THE OLDER GENERATION

Jim Gatenby

Especially written for the over 50s. Uses only clear and easy-to-understand language. Larger type size for easy reading. Provides basic knowledge to give you confidence to join the local computer class.

This book explains how to use your PC on the Internet and covers amongst other things: Choosing and setting up your computer for the Internet. Getting connected to the Internet. Sending and receiving emails, photographs, etc., so that you can keep in touch with family and friends all over the world. Searching for and saving information on any subject. On-line shopping and home banking. Setting up your own simple web site.

228 pages Order code BP600 £8.99

### HOW TO BUILD YOUR OWN PC -

Third Edition

Morris Rosenthal

More and more people are building their own PCs. They get more value for their money, they create exactly the machine they want, and the work is highly satisfying and actually fun. That is, if they have a unique beginner's guide like this one, which visually demonstrates how to construct a state-of-the-art computer from start to finish.

Through 150 crisp photographs and clear but minimal text, readers will confidently absorb the concepts of computer building. The extra-big format makes it easy to see what's going on in the pictures. For non-specialists, there's even a graphical glossary that clearly illustrates technical terms. The author goes "under the hood" and shows step-by-step how to create a socket 7 (Pentium and non-intel chipsets) and a Slot 1 (Pentium II) computer, covering: What first-time builders need to know; How to select and purchase parts; How to assemble the PC; How to install Windows 98. The few existing books on this subject, although badly outdated, are in steady demand. This one delivers the expertise and new technology that fledgling computer builders are eagerly looking for.

224 pages - large format Order code MGH2 £20.99

### PIC YOUR PERSONAL INTRODUCTORY COURSE

SECOND EDITION John Morton

Discover the potential of the PIC microcontroller through graded projects - this book could revolutionise your electronics construction work!

A uniquely concise and practical guide to getting up and running with the PIC Microcontroller. The PIC is one of the most popular of the microcontrollers that are transforming electronic project work and product design.

Assuming no prior knowledge of microcontrollers and introducing the PIC's capabilities through simple projects, this book is ideal for use in schools and colleges. It is the ideal introduction for students, teachers, technicians and electronics enthusiasts. The step-by-step explanations make it ideal for self-study too: this is not a reference book - you start work with the PIC straight away.

The revised second edition covers the popular reprogrammable EEPROM PICs: P16C84/16F84 as well as the P54 and P71 families.

270 pages Order code NE36 £15.99

### eBAY FOR BEGINNERS

Cherry Nixon

There are two kinds of people, those who are trading on eBay and the rest who are missing out. Though eBay has been embraced by entrepreneurs all over the world, it remains the peoples' site and offers the largest market for the smallest fee.

eBay presents an opportunity for everyone, the trick is to master it. This book shows you how to start trading on eBay UK. It also offers advice on getting organised and tips to put you ahead.

The book has been developed from Cherry's popular hands-on course "Buying and Selling on eBay for Technological Simpletons". In addition to fully explaining eBay and how to trade on it there are sections on Paypal, producing pictures of your sale items, fees and accounts, safety and security including what to do when things go wrong and what protection is provided.

178 pages Order code BP551 £8.99

### NEWNES PC TROUBLESHOOTING

POCKET BOOK - THIRD EDITION

Howard Anderson, Mike Tooley

All the essential data for PC fault-finding and upgrading. This book provides a concise and compact reference that describes, in a clear and straightforward manner, the principles and practice of fault-finding and upgrading PCs and peripherals. The book is aimed at anyone who is involved with the installation, configuration, maintenance, upgrading, repair or support of PC systems. It also provides non-technical users with sufficient background information, charts and checklists to enable the diagnosis of faults and help to carry out simple modifications and repairs. In order to reflect rapid changes in computer technology (both hardware and software) this new edition has been completely revised and rewritten.

256 pages Order code NE41 £19.99

# Theory and Reference

## BEBOP TO THE BOOLEAN BOOGIE

Second Edition  
Clive (Max) Maxfield

BOOK PLUS  
CD-ROM

This book gives the "big picture" of digital electronics. This in-depth, highly readable, up-to-the-minute guide shows you how electronic devices work and how they're made. You'll discover how transistors operate, how printed circuit boards are fabricated, and what the innards of memory ICs look like. You'll also gain a working knowledge of Boolean Algebra and Karnaugh Maps, and understand what Reed-Muller logic is and how it's used. And there's much, MUCH more. The author's tongue-in-cheek humour makes it a delight to read, but this is a REAL technical book, extremely detailed and accurate. Comes with a free CD-ROM which contains an eBook version with full text search plus bonus chapter - An Illustrated History of Electronics and Computing.

**Contents:** Fundamental concepts; Analog versus digital; Conductors and insulators; Voltage, current, resistance, capacitance and inductance; Semiconductors; Primitive logic functions; Binary arithmetic; Boolean algebra; Karnaugh maps; State diagrams, tables and machines; Analog-to-digital and digital-to-analog; Integrated circuits (ICs); Memory ICs; Programmable ICs; Application-specific integrated circuits (ASICs); Circuit boards (PWBs and DWBs); Hybrids; Multichip modules (MCMs); Alternative and future technologies.

500 pages **Order code BEB1** £27.50

## BEBOP BYTES BACK (and the Beboputer Computer Simulator)

CD-ROM  
Clive (Max) Maxfield and Alvin Brown

CD-ROM

This follow-on to *Bebo to the Boolean Boogie* is a multimedia extravaganza of information about how computers work. It picks up where "Bebo!" left off, guiding you through the fascinating world of computer design... and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the CD-ROM contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the CD-ROM contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the



slightest bit interested in the inner workings of computers, then don't dare to miss this!

Over 800 pages in Adobe Acrobat format

CD-ROM **Order code BEB2 CD-ROM** £21.95

## SCROGGIE'S FOUNDATIONS OF WIRELESS AND ELECTRONICS - ELEVENTH EDITION

S. W. Amos and Roger Amos

Scroggie's Foundations is a classic text for anyone working with electronics, who needs to know the art and craft of the subject. It covers both the theory and practical aspects of a huge range of topics from valve and tube technology, and the application of cathode ray tubes to radar, to digital tape systems and optical recording techniques.

Since *Foundations of Wireless* was first published over 60 years ago, it has helped many thousands of readers to become familiar with the principles of radio and electronics. The original author Sowerby was succeeded by Scroggie in the 1940s, whose name became synonymous with this classic primer for practitioners and students alike. Stan Amos, one of the fathers of modern electronics and the author of many well-known books in the area, took over the revision of this book in the 1980s and it is he, with his son, who have produced this latest version.

400 pages **Temporarily out of print**

## GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

96 pages **Order code BP239** £5.49

## STARTING ELECTRONICS, THIRD EDITION

KEITH BRINDLEY

NEW

A punchy practical introduction to self-build electronics. The ideal starting point for home experimenters, technicians and students who want to develop the real hands-on skills of electronics construction.

A highly practical introduction for hobbyists, students, and technicians. Keith Brindley introduces readers to the functions of the main component types, their uses, and the basic principles of building and designing electronic circuits.

Breadboard layouts make this very much a ready-to-run book for the experimenter, and the use of multimeter, but not oscilloscope, and readily available, inexpensive components makes the practical work achievable in a home or school setting as well as a fully equipped lab.

288 pages **Order code NE42** £10.99

## THE AMATEUR SCIENTIST

CD-ROM

CD-ROM

The complete collection of The Amateur Scientist articles from *Scientific American* magazine. Over 1,000 classic science projects from a renowned source of winning projects. All projects are rated for cost, difficulty and possible hazards.

Plus over 1,000 pages of helpful science techniques that never appeared in *Scientific American*.

Exciting science projects in: Astronomy; Earth Science; Biology; Physics; Chemistry; Weather... and much more! The most complete resource ever assembled for hobbyists, and professionals looking for novel solutions to research problems.

Includes extensive Science Software Library with even more science tools.

Suitable for Mac, Windows, Linux or UNIX. 32MB RAM minimum, Netscape 4.0 or higher or Internet Explorer 4.0 or higher.

Over 1,000 projects



CD-ROM **Order code AS1 CD-ROM** £19.95

# Music, Audio and Video

## MAKING MUSIC WITH YOUR COMPUTER

NEW

Stephen Bennett

Nearly everyone with musical aspirations also has a computer. This same computer can double as a high quality recording studio capable of producing professional recordings. This book tells you what software and hardware you will need to get the best results.

You'll learn about recording techniques, software and effects, mixing, mastering and CD production.

Suitable for PC and Mac users, the book is full of tips, "how to do" topics and illustrations. It's the perfect answer to the question "How do I use my computer to produce my own CD?"

92 pages **Order code PC120** £10.95

## QUICK GUIDE TO ANALOGUE SYNTHESIS

Ian Waugh

Even though music production has moved into the digital domain, modern synthesisers invariably use analogue synthesis techniques. The reason is simple - analogue synthesis is flexible and versatile, and it's relatively easy for us to understand. The basics are the same for all analogue synths, and you'll quickly be able to adapt the principles to any instrument, to edit existing sounds and create exciting new ones. This book describes: How analogue synthesis works; The essential modules every synthesiser has; The three steps to synthesis; How to create phat bass sounds. How to generate filter sweeps; Advanced synth modules; How to create simple and complex synth patches; Where to find soft synths on the Web.

If you want to take your synthesiser - of the hardware or software variety - past the presets, and program your own sounds and effects, this practical and well-illustrated book tells you what you need to know.

60 pages **Order code PC118** £7.45

## QUICK GUIDE TO MP3 AND DIGITAL MUSIC

Ian Waugh

MP3 files, the latest digital music format, have taken the music industry by storm. What are they? Where do you get them? How do you use them? Why have they thrown record companies into a panic? Will they make music easier to buy? And cheaper? Is this the future of music?

All these questions and more are answered in this concise and practical book which explains everything you need to know about MP3s in a simple and easy-to-understand manner. It explains:

How to play MP3s on your computer; How to use MP3s with handheld MP3 players; Where to find MP3s on the Web; How MP3s work; How to tune into Internet radio stations; How to create your own MP3s; How to record your own CDs from MP3 files; Other digital audio music formats.

Whether you want to stay bang up to date with the latest music or create your own MP3s and join the on-line digital music revolution, this book will show you how.

60 pages **Order code PC119** £7.45

## ELECTRONIC MUSIC AND MIDI PROJECTS

R. A. Penfold

Whether you wish to save money, boldly go where no musician has gone before, rekindle the pioneering spirit, or simply have fun building some electronic music gadgets, the designs featured in this book should suit your needs. The projects are all easy to build, and some are so simple that even complete beginners at electronic project construction can tackle them with ease. Stripboard layouts are provided for every project, together with a wiring diagram. The mechanical side of construction has largely been left to individual constructors to sort out, simply because the vast majority of project builders prefer to do their own thing in this respect.

None of the designs requires the use of any test equipment in order to get them set up properly. Where any setting up is required, the procedures are very straightforward, and they are described in detail.

Projects covered: Simple MIDI tester, Message grabber, Byte grabber, THRU box, MIDI auto switcher, Auto/manual switcher, Manual switcher, MIDI patchbay, MIDI controlled switcher, MIDI lead tester, Program change pedal, Improved program change pedal, Basic mixer, Stereo mixer, Electronic swell pedal, Metronome, Analogue echo unit.

124 pages **Order code PC116** ~~£10.95~~ £5.45

## THE INVENTOR OF STEREO - THE LIFE AND WORKS OF ALAN DOWER BLUMLEIN

Robert Charles Alexander

This book is the definitive study of the life and works of one of Britain's most important inventors who, due to a cruel set of circumstances, has all but been overlooked by history.

Alan Dower Blumlein led an extraordinary life in which his inventive output rate easily surpassed that of Edison, but whose early death during the darkest days of World War Two led to a shroud of secrecy which has covered his life and achievements ever since.

His 1931 Patent for a Binaural Recording System was so revolutionary that most of his contemporaries regarded it as more than 20 years ahead of its time. Even years after his death, the full magnitude of its detail had not been fully utilized. Among his 128 patents are the principal electronic circuits critical to the development of the world's first electronic television

system. During his short working life, Blumlein produced patent after patent breaking entirely new ground in electronic and audio engineering.

During the Second World War, Alan Blumlein was deeply engaged in the very secret work of radar development and contributed enormously to the system eventually to become 'H2S' - blind-bombing radar. Tragically, during an experimental H2S flight in June 1942, the Halifax bomber in which Blumlein and several colleagues were flying, crashed and all aboard were killed. He was just days short of his thirty-ninth birthday.

420 pages **Order code NE32** £17.99

## VIDEO PROJECTS FOR THE ELECTRONICS CONSTRUCTOR

R. A. Penfold

Written by highly respected author R. A. Penfold, this book contains a collection of electronic projects specially designed for video enthusiasts. All the projects can be simply constructed, and most are suitable for the newcomer to project construction, as they are assembled on stripboard.

There are faders, wipers and effects units which will add sparkle and originality to your video recordings, an audio mixer and noise reducer to enhance your soundtracks and a basic computer control interface. Also, there's a useful selection on basic video production techniques to get you started.

Complete with explanations of how the circuit works, shopping lists of components, advice on construction, and guidance on setting up and using the projects, this invaluable book will save you a small fortune.

Circuits include: video enhancer, improved video enhancer, video fader, horizontal wiper, improved video wiper, negative video unit, fade to grey unit, black and white keyer, vertical wiper, audio mixer, stereo headphone amplifier, dynamic noise reducer, automatic fader, pushbutton fader, computer control interface, 12 volt mains power supply.

124 pages **Order code PC115** ~~£10.95~~ £5.45

## HIGH POWER AUDIO AMPLIFIER CONSTRUCTION

R. A. Penfold

Practical construction details of how to build a number of audio power amplifiers ranging from about 50 to 300/400 watts r.m.s. includes MOSFET and bipolar transistor designs.

96 pages **Temporarily out of print**

# Circuits, Data and Design

## PRACTICAL ELECTRONIC FILTERS

Owen Bishop

This book deals with the subject in a non-mathematical way. It reviews the main types of filter, explaining in simple terms how each type works and how it is used.

The book also presents a dozen filter-based projects with applications in and around the home or in the constructor's workshop. These include a number of audio projects such as a rhythm sequencer and a multi-voiced electronic organ.

Concluding the book is a practical step-by-step guide to designing simple filters for a wide range of purposes, with circuit diagrams and worked examples.

88 pages

Order code BP299

£5.49

## DIGITAL ELECTRONICS -

### A PRACTICAL APPROACH

With FREE Software: Number One Systems - EASY-PC

FREE SOFTWARE

Professional XM and Pulsar (Limited Functionality)

Richard Monk

Covers binary arithmetic, Boolean algebra and logic gates, combination logic, sequential logic including the design and construction of asynchronous and synchronous circuits and register circuits. Together with a considerable practical content plus the additional attraction of its close association with computer aided design including the FREE software.

There is a 'blow-by-blow' guide to the use of EASY-PC Professional XM (a schematic drawing and printed circuit board design computer package). The guide also conducts the reader through logic circuit simulation using Pulsar software. Chapters on p.c.b. physics and p.c.b. production techniques make the book unique, and with its host of project ideas make it an ideal companion for the integrative assignment and common skills components required by BTEC and the key skills demanded by GNVQ. The principal aim of the book is to provide a straightforward approach to the understanding of digital electronics.

Those who prefer the 'Teach-In' approach or would rather experiment with some simple circuits should find the book's final chapters on printed circuit board production and project ideas especially useful.

250 pages (large format)

Temporarily out of print

## A BEGINNER'S GUIDE TO TTL DIGITAL ICs

R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip/flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in the 'real world'.

142 pages

Order code BP332

£5.45

## MICROCONTROLLER COOKBOOK

Mike James

The practical solutions to real problems shown in this cookbook provide the basis to make PIC and 8051 devices really work. Capabilities of the variants are examined, and ways to enhance these are shown. A survey of common interface devices, and a description of programming models, lead on to a section on development techniques. The cookbook offers an introduction that will allow any user, novice or experienced, to make the most of micro-controllers.

240 pages

Order code NE26

£23.99

## RADIO BYGONES

We also carry a selection of books aimed at readers of *EPE's* sister magazine on vintage radio *Radio Bygones*. These books include the *Comprehensive Radio Valve Guides* (five books with a Free copy of the Master Index) for just £15. Also Jonathan Hill's excellent *Radio Radio*, a comprehensive book with hundreds of photos depicting the development of the British wireless set up to the late 1960s.

The four volumes of our own *Wireless For the Warrior* by Louis Meulstee are also available. These are a technical history of radio communication equipment in the British Army and clandestine equipment from pre-war through to the 1960s.

For details see the shop on our UK web site at [www.epemag.co.uk](http://www.epemag.co.uk) or contact us for a list of *Radio Bygones* books.

# Project Building & Testing

## ELECTRONIC PROJECTS FOR EXPERIMENTERS

R. A. Penfold

Many electronic hobbyists who have been pursuing their hobby for a number of years seem to suffer from the dreaded "seen it all before" syndrome. This book is fairly and squarely aimed at sufferers of this complaint, plus any other electronics enthusiasts who yearn to try something a bit different. No doubt many of the projects featured here have practical applications, but they are all worth a try for their interest value alone.

The subjects covered include:- Magnetic field detector, Basic Hall effect compass, Hall effect audio isolator, Voice scrambler/descrambler, Bat detector, Bat style echo location, Noise cancelling, LED stroboscope, Infra-red "torch", Electronic breeze detector, Class D power amplifier, Strain gauge amplifier, Super hearing aid.

138 pages

Order code BP371

£5.45

## FAULT-FINDING ELECTRONIC PROJECTS

R. A. Penfold

Starting with mechanical faults such as dry joints, short-circuits etc, coverage includes linear circuits, using a meter to make voltage checks, signal tracing techniques and fault finding on logic circuits. The final chapter covers ways of testing a wide range of electronic components, such as resistors, capacitors, operational amplifiers, diodes, transistors, SCRs and triacs, with the aid of only a limited amount of test equipment.

The construction and use of a Tristate Continuity Tester, a Signal Tracer, a Logic Probe and a CMOS Tester are also included.

136 pages

Temporarily out of print

## PRACTICAL FIBRE-OPTIC PROJECTS

R. A. Penfold

While fibre-optic cables may have potential advantages over ordinary electric cables, for the electronics enthusiast it is probably their novelty value that makes them worthy of exploration. Fibre-optic cables provide an innovative interesting alternative to electric cables, but in most cases they also represent a practical approach to the problem. This book provides a number of tried and tested circuits for projects that utilize fibre-optic cables.

The projects include:- Simple audio links, F.M. audio

link, P.W.M. audio links, Simple d.c. links, P.W.M. d.c. link, P.W.M. motor speed control, RS232C data links, MIDI link, Loop alarms, R.P.M. meter.

All the components used in these designs are readily available, none of them require the constructor to take out a second mortgage.

132 pages

Order code BP374

£5.45

## DISCOVERING PICS

W.D. Phillips

A good introduction to PIC programming, covering everything you need to know to get you started. No previous knowledge of microcontrollers is required, but some previous experience with electronic circuits is assumed. Covers the basic concept of a micro-controller, fundamentals of a PIC-based circuit and using the MPLAB program. Further chapters introduce binary, PIC architecture, the instruction set, the PIC memory map and special registers plus real world programming. Four simple projects are also fully described; a Wavy Wand, an Electronic Dice, a Games Timer and a Pulse Monitor.

The associated CDROM contains the book in PDF format, MPLAB (plus instruction manuals in PDF format) and all the programs covered in the book as assembler (ASM) files.

In addition a p.c.b. based hardware kit is also available that makes up into the Wavy Wand which will spell out a short message via a line of l.e.d.s when waved through the air.

190 pages, A4 spiral bound

Book + CDROM Order code DOC1 £22.00

Book + CDROM + Hardware Order code DOC2 £28.50

For a further selection of books see the next two issues of *EPE*

## BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £2 per book. For the rest of the world airmail add £3 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard, Amex, Diners Club or Maestro to:

**DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LTD.,  
408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND.**

Orders are normally sent out within seven days of receipt, but please allow 28 days for delivery - more for overseas orders. *Please check price and availability (see latest issue of Everyday Practical Electronics) before ordering from old lists.*

For a further selection of books and CD-ROMs see the next two issues of *EPE*.

Tel 01202 873872 Fax 01202 874562. Email: [dbs@epemag.wimbome.co.uk](mailto:dbs@epemag.wimbome.co.uk)

Order from our online shop at: [www.epemag.co.uk/shopdoor.htm](http://www.epemag.co.uk/shopdoor.htm)

## BOOK/CD-ROM ORDER FORM

Full name: .....

Address: .....

.....

.....

..... Post code: ..... Telephone No: .....

Signature: .....

I enclose cheque/PO payable to DIRECT BOOK SERVICE for £ .....

Please charge my card £ ..... Card expiry date.....

Card Number ..... Maestro Issue No.....

Card Security Code ..... (The last 3 digits on or just below the signature strip)

Please send book/CD-ROM order codes: .....

.....

Please continue on separate sheet of paper if necessary  
If you do not wish to cut your magazine, send a letter or copy of this form

# READOUT

## WIN AN ATLAS LCR ANALYSER WORTH £69

Email: john.becker@wimborne.co.uk

**John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!**

All letters quoted here have previously been replied to directly.

An Atlas LCR Passive Component Analyser, kindly donated by Peak Electronic Design Ltd., will be awarded to the author of the *Letter Of The Month* each month.

The Atlas LCR automatically measures inductance from 1 $\mu$ H to 10H, capacitance from 1pF to 10,000 $\mu$ F and resistance from 1 $\Omega$  to 2M $\Omega$  with a basic accuracy of 1%.



## ★ LETTER OF THE MONTH ★

### Dalek Gigs!

*I've recently been chatting with Mike Boyden, who has built several of my Cybervox Dalek voice emulators (July '05) and which are being used by various Dalek "clubs". The concept of such "clubs" greatly amused my wife and I told Mike so. He replied:*

Tell your wife that Dalek stuff is far too serious a matter to be left in the hands of children! (I only found out about it when approached by a local guy who bought a Dalek from a (BBC licensed would you believe) workshop.

He earns a very tidy sum doing "gigs" with his Dalek which have included (and I am not making this up):

- Weddings
- A funeral (to press the button to move the casket into the next world – I kid you not)
- Shopping Mall promotions (he once

stopped a running thief by shouting: "STOP OR I WILL EXTERMINATE YOU ..." at which point the thief stopped frozen to the spot, whereupon he was carted off by security people)

- Appearances at Strip Clubs (I didn't ask ...)
- POP Festivals

Oh yes, not to mention ... he has been set on fire, had water poured onto him (disabling the Dalek and all the electronics) and fallen off the stage and into a crowd of 50,000 drunken head bangers at some sort of rave event.

So tell her some Daleks have found a very eventful life on earth – he he he ...

**Mike Boyden, via email**

*That's hilarious Mike, thanks for sharing it. And thanks too for your IU offering in this issue – the Dalek lighting interface for Cybervox. I should've thought of doing that myself originally!*

### PIC Spanish Translator

Dear EPE,

After recently building your wonderful TK3 PIC programmer, and going through the *PIC Tutorial*, I have been considering trying to develop a Spanish translator/study aid and was wondering whether you have anything similar planned for a future project?

Ideally I would like voice playback and recognition but maybe this would be stretching a PIC too far! Playback seems possible though by using a PWM output as the D to A converter but it would require an awfully large memory to store the samples.

Maybe something similar to the *Crossword Solver* (May '05) would suffice if it had the added feature of a couple of games, hangman etc, to help you learn new vocabulary. Again though I'm coming across problems in getting a dictionary file that I could use to base the design on and that comes in a compressed format so it will fit into a PIC's program memory along with the program code.

My final point is whether to code in assembly language, C or even BASIC? It seems that the device doesn't need to run extremely quickly so I'm thinking that C or BASIC may be the best way to go if I can get my hands on a freeware compiler.

I'd like to actually get this design off the ground one day and so I was hoping that you or one of your readers could possibly point me in the right direction or have any advice.

Thank you for listening and supplying such a thought provoking magazine. Hoping that now I have TK3 up and running and with the help of your magazine I may at last be able to build my own PIC controlled device.

**Lee Archer, via email**

*Thanks for the kind words Lee! A translator is not something that should be undertaken lightly by anyone. Whilst in principle the technique needed is simple, its implementation would be complex because of the vast vocab such a device would need, and that needs lots of memory. And voice recognition is way beyond what hobbyists can realistically achieve.*

*Also, there are commercial devices available, I have a German/English unit for instance – key in a word in either language and the equivalent in the other is shown on screen.*

*I'm not a great user of C and would suggest that the compactness of code written in PIC assembler might be better.*

*So best of luck if you attempt it, but it's not something I would feel comfortable trying, although I recognise the challenge!*

### Crossword Update

Dear EPE,

As a result of chatting with several readers I have made some updates to the *Crossword Solver* code (May '05). These changes address the following issues:

1. The L.c.d. access routines would not always start properly on power up.
2. Words greater than 16 characters in length had a character missing when displayed.
3. The unit did not reject a request for a word longer than its biggest entry, resulting in rubbish being displayed.

That was quite handy feedback from readers since I am using the 4-bit display method in my forthcoming *Camera Watch Mk2* project!

A quick question – do you have any PIC assembly code, or an algorithm, for taking a 16-bit unsigned binary number and displaying it in decimal ASCII? All the algorithms I have come across use the "divide by 10" technique which is quite "expensive", even on a PIC18F. I'll use them if necessary but I was wondering if there was a better algorithm?

**Mike Hibbett, via email**

*Thanks for the updated code Mike, which is now on our Downloads site (via [www.epemag.co.uk](http://www.epemag.co.uk)).*

*Regarding your query, I use Peter Hemsley's BIN2DEC (binary to deci-*

*mal) routine, then OR (or ADD) 48 to all decimal digit values (each 0 to 9) so that an l.c.d. shows them as ASCII characters. You'll find many examples of my use of this in my published software. Peter's excellent 32-maths routines are on our Downloads site.*

### Rally Components

Dear EPE,

Your July '05 Letter of the Month cast doubts about buying cheap bargain components at rallies. I agree it is most frustrating to spend time and effort constructing a project, only to find it doesn't work because of cheap faulty components.

This is self-inflicted punishment. If one goes to the time and trouble to remove components from disregarded p.c.b.s and expect them to work – well, I wonder! My time is more valuable than this wasted exercise.

I consider it good practice to test all the components before I solder them into a project to verify they are within the correct tolerance. This saves time trying to trace a defective component after the circuit is built.

I buy my spares from a reputable small firm which attends all the major rallies, and is very reasonable pricewise.

**Ken Barry, Blackpool, via email**

*Thanks for that Ken.*

## As One Door Opens ...

Dear EPE,

I feel that the increased availability of the Internet and "black box" technology has been the final "nail in the coffin" for hobbies like amateur radio, weather satellite receiving and data communications by the airwaves. Increased competition in the consumer electronics manufacturing industry has also made the hobbyist construction of audio equipment largely unfeasible. But I'm pleased that *EPE* continues to contain many inventive designs.

We must, however, remember that current projects using the PIC processors may seem impressive today but years ago a designer would only have had a limited armoury of components including passive devices, semiconductors and a range of discrete analogue and digital i.c.s. Here the hardware design would have to be finalised and could not be "tweaked" later in the software.

What of the future for amateur electronics? The promised invasion of surface mounted devices failed to lead to the demise of dual-in-line integrated circuits, as the EU safety and EMC directive failed to stem the interest in amateur electronics and I don't suppose the introduction of lead-free solder in the future will do so either.

As long as there are people willing to design and publish high quality electronic projects and manufacturers produce suitable devices there seems no need to worry about the popularity of the hobby.

**Chris Lewis, via email**

*To take your first point first, Chris, I think many will disagree with you about the demise of amateur radio. There is considerable evidence of thriving HAM activity, even though it may no longer be publicised so heavily as it used to be.*

*Furthermore, despite the availability of low cost (and not so low cost) audio equipment, there is still an interest in building one's own amplifier, and indeed there is considerable satisfaction to be gained by doing so. Reader response to Raymond Haigh's articles in this area prove the point.*

*But you are right about PICs in a sense - technology does move on, and techniques change because of that. Sooner or later something more advanced than a microcontroller may indeed come along and ultimately replace it.*

*But it's a case of "as one door opens another one shuts - partly". The microcontroller is not going to disappear until something better appears, even then it is likely to continue to exist alongside the new technology. Look at how valves were once dominant, but when transistors came along, valves were not totally ousted, and continue to be used even now in several forms. Nor have i.c.s replaced transistors. There is a role for both.*

*And as long as technology exists, there will always be those who wish to explore it in a variety of ways, including the construction of designs based upon it, and so will magazines like *EPE* cater for such interests, in both practical and tutorial roles.*

## Pain Monitor

Dear EPE,

I read with interest your article on how to build a pain monitor (Aug '05). We have developed a number of advanced units similar to yours (8051 based) over the last six years and have presented many studies, using the devices, to consultant anaesthetists at national meetings. Our professor is head of the pain management service at the University Hospitals of Leicester and director of UHL research and development, he specialises in pain management.

We have conducted considerable research in the area of portable pain measurement devices and have worked with large companies like GSK to evaluate our devices. We are looking into commercial opportunities, but unfortunately the market is very small and the free pain gauge that you show is widely used, even though it is not the correct format compared to paper VAS scores.

There was a commercial unit sold called the Clinitrac, this is no longer available due to poor sales and the advent of PDA questionnaire systems with VAS. PDA systems have been validated and are widely used by drug companies and researchers of chronic and acute pain, although we feel that they are not entirely suitable.

I think that your unit would be useful for a doctor/patient that wishes to gain a rough estimate of pain scores but would not be suitable for controlled research data.

Of course, if we could really measure pain electronically, instead of the subjective measures currently used, the unit would be on every doctors wish list. The problem is as elusive as measurement of depth of anaesthesia, although some progress has been made in this area.

I like your wildlife monitor idea, given folks increased interest in the environment, this has great potential and would provide very useful data for researchers in this area.

**Ed Pallett,**

**University Division of Anaesthesia,  
Leicester Royal Infirmary,  
via email**

*Thanks for your interesting letter Ed, which I sent on to Mark Piper, the anaesthetist who inspired my design. One of the first questions I asked him was about electrically monitoring pain, and he confirmed it's not possible, although I had expected that there might be brain waves which could be monitored in this respect.*

## Laser ranges with PICs

Dear EPE,

Reading the August '05 *Readout*, I thought you might like to ponder the way radio altimetry worked. The frequency of transmission is linearly swept so that the return is at a slightly different frequency to the transmission, and the difference gives the range. If the difference frequency is small enough it could be handled by a PIC? But I don't know if the frequency of a laser can be swept.

**John Waller, Plainfield, USA,  
via email**

*That's intriguing John! I'll think on it, thank you.*

## GPS Validity

Dear EPE,

I refer to my letter about GPS validity in Aug '05 (thanks for printing it by the way).

It seems to me the Standard is not so standard after all! Perhaps I should explain a bit more. The values I refer to come directly from the NMEA GGA Standard and the validity flag can actually have any value from 0 to 8 (although many values are not used). This standard is used by all professional GPS equipment, Trimble Navigation is probably the industry standard.

The following was copied from [www.gpsinformation.org/dale/nmea.htm](http://www.gpsinformation.org/dale/nmea.htm)

GGA - essential fix data which provide 3D location and accuracy data, e.g.:

\$GPGGA,123519,4807.038,N,01131.000,E,1,08,0.9,545.4,M,46.9,M,,\*47

|               |  |
|---------------|--|
| GGA           | Global Positioning System Fix Data                             |
| 123519        | Fix taken at 12:35:19 UTC                                      |
| 4807.038,N    | Latitude 48 deg 07.038' N                                      |
| 01131.000,E   | Longitude 11 deg 31.000' E                                     |
| 1             | Fix quality:   |
|               | 0 = invalid  |
|               | 1 = GPS fix (SPS)  |
|               | 2 = DGPS fix   |
|               | 3 = PPS fix  |
|               | 4 = Real Time Kinematic  |
|               | 5 = Float RTK  |
|               | 6 = estimated (dead reckoning) (2.3 feature)                   |
|               | 7 = Manual input mode  |
|               | 8 = Simulation mode  |
| 08            | Number of satellites being tracked                             |
| 0.9           | Horizontal dilution of position                                |
| 545.4,M       | Altitude, Meters, above mean sea level                         |
| 46.9,M        | Height of geoid (mean sea level) above WGS84 ellipsoid         |
| (empty field) | Time in seconds since last DGPS update                         |
| (empty field) | DGPS station ID number the checksum data, always begins with * |
| *47           |  |

**Colin Gill, via email**

*Now the fog clears - thanks for the info Colin! So I'll keep my decoding as is for GPRMC (I don't use GGA).*

## FR4 Laminate

Dear EPE,

I have been buying your mag for years now and this is the first time I have needed to ask a question.

I need to get hold of some unclad, i.e. plain with no copper, FR4 laminate, or equivalent, to make a circuit board that I will put turret tags or equivalent onto.

Can you point me in a direction where I can get some?

**Paul, via email**

*Sorry Paul, I regret that I don't know of any supplier - ask readers directly through our Chat Zone (via [www.epemag.co.uk](http://www.epemag.co.uk)). By quoting you now in *Readout*, let's see if this also gets you any reader response via the editorial office.*

# PCB SERVICE

Printed circuit boards for most recent EPE constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872; Fax 01202 874562; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm.** Cheques should be crossed and made payable to **Everyday Practical Electronics (Payment in £ sterling only).**

**NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail. Back numbers or photostats of articles are available if required – see the Back Issues page for details. We do not supply kits or components for our projects.**

**Please check price and availability in the latest issue. A large number of older boards are listed on our website. Boards can only be supplied on a payment with order basis.**

| PROJECT TITLE  | Order Code | Cost         |
|--|------------|--------------|
| Infra-Guard  | 439        | £5.07        |
| ★ Moon Clock   | 442        | £5.71        |
| ★ Teach-In '04 Part 6 – Software only                | –          | –            |
| ★ EPE Seismograph Logger                             | –          | –            |
| Control Board  | 440        | } pair £6.50 |
| Sensor Amp. Board                                    | 441        |              |
| In-Car Lap-Top PSU                                   | 443        | £4.60        |
| Beat Balance Metal Detector                          | 444        | £4.60        |
| Teach-In '04 Part 7 – Transmitter                    | 445        | £4.91        |
| Receiver   | 446        | £4.75        |
| Moisture   | 447        | £4.44        |
| ★ PIC Quickstep                                      | 448        | £5.71        |
| Body Detector MkII                                   | 449        | £4.91        |
| ★ Teach-In '04 Part 8 – Software only                | –          | –            |
| ★ MIDI Synchronome – Software only                   | –          | –            |
| Hard Drive Warbler                                   | 450        | £4.60        |
| ★ Bongo Box  | 451        | £6.02        |
| Portable Mini Alarm – Sensor                         | 452        | £5.23        |
| – Counter  | 453        | £5.07        |
| ★ Teach-In '04 Part 9                                | –          | –            |
| PIC Combination Lock Alarm Monitor                   | 454        | £5.07        |
| ★ EPE Magnetometry Logger                            | 455        | £5.71        |
| Keyring L.E.D. Torch                                 | 456        | £4.12        |
| ★ Teach-In '04 Part 10 – PIC Curtain or Blind Winder | 457        | £5.39        |
| Simple F.M. Radio – F.M. Tuner                       | 458        | £5.07        |
| – Tone Control                                       | 459        | £4.75        |
| – Audio Power Amp (TDA2003)                          | 347        | £4.60        |
| – Power Supply                                       | 460        | £5.39        |
| ★ EPE Scorer   | 461        | £6.66        |
| – Control Board                                      | 462        | £7.93        |
| – Display Board                                      | 463        | £5.55        |
| – Slave Board  | 463        | £5.55        |
| ★ PIC to Mouse/Keyboard – Software only              | –          | –            |
| EPE Wart Zapper                                      | 464        | £4.60        |
| ★ Radio Control Fallsafe                             | 465        | £4.76        |
| ★ AlphaMouse Game                                    | 466        | £4.60        |
| ★ Rainbow Lighting Controller – Software only        | –          | –            |
| ★ Moon and Tide Clock Calendar                       | 467        | £5.55        |
| Volts Checker  | 468        | £4.20        |
| ★ Smart Karts – Software only                        | –          | –            |
| Logic Probe  | 469        | £4.76        |
| Thunderstorm Monitor                                 | 470        | £5.39        |
| MW Amplitude Modulator                               | –          | –            |
| – V.F.O./Buffer                                      | 471        | £4.76        |
| – Modulator/PA                                       | 472        | £5.07        |
| – Power Supply                                       | 473        | £4.76        |
| Super Vibration Switch                               | 474        | £4.75        |
| Wind Direction Indicator                             | 475        | £6.18        |
| ★ PIC Flasher Mk2 – Control Board                    | 476        | £4.75        |
| – Transmitter  | 477        | £4.44        |
| – Multipurpose Board                                 | 478        | £4.75        |
| – Simple Cyclor                                      | 479        | £4.44        |
| – Luxeon V Controller                                | 480        | £4.44        |
| – Power Supply                                       | 473        | £4.76        |
| Light Detector                                       | 481        | £4.44        |
| ★ Camera Watch                                       | 482        | £6.03        |
| Gate Alarm – Oscillator                              | 483        | £4.92        |
| – Delay/Timer  | 484        | £4.92        |
| ★ Sneaky – Transmitter                               | 485        | £4.60        |
| – Receiver   | 486        | £4.91        |
| ★ PIC Electric Mk2 – Control                         | 487        | £5.87        |
| – Sensor   | 488        | £5.71        |
| Sound Card Mixer                                     | 489        | £7.29        |
| Headphone Monitor                                    | 490        | £5.71        |
| EPE Cat Flap   | 491        | £6.02        |
| ★ Bingo Box – Main                                   | 492        | £9.04        |
| – Big Digit Display                                  | 493        | £10.31       |
| Spontaflex Radio– Tuner                              | 494        | £5.55        |
| – Coil Pack  | 495        | £5.71        |
| – Audio Amplifier                                    | 496        | £5.55        |
| – Tuning Capacitor Board                             | 406        | £4.28        |
| ★ Safety Interface                                   | 497        | £6.18        |
| Back-To-Basics 1– Fridge/Freezer Door Alarm          | 498        | £5.39        |

| PROJECT TITLE                        | Order Code | Cost         |
|--------------------------------------|------------|--------------|
| ★ Crossword Solver                   | 499        | £6.66        |
| 20W Amplifier Module                 | 500        | £5.14        |
| Back-To-Basics 2 – Water Level Alarm | 501        | £5.39        |
| – Burglar Alarm                      | 502        | £5.87        |
| ★ PIC Ultrasonic Scanner             | 503        | £6.66        |
| ★ Radio Control Model Switcher       | 504        | £5.87        |
| Back-To-Basics 3 – Scarecrow         | 505        | £5.55        |
| – Digital Lock                       | 506        | £6.66        |
| CompactFlash Interface Board         | 507        | £6.66        |
| LF/VLF Converter                     | 508        | £5.71        |
| – Fixed Capacitor Board              | 509        | £5.86        |
| – Mixer/Oscillator Board             | 510        | £5.23        |
| – Buffer Amplifier                   | 511        | £5.23        |
| – Q-Multiplier                       | 406        | £4.28        |
| – Tuning Capacitor Board             | 512        | £6.34        |
| Back-To-Basics 4 – Doorchime         | 513        | £6.02        |
| – Electronic Dice                    | 514        | £6.82        |
| ★ Cybervox                           | 515        | £6.66        |
| Multi-Clap Switch                    | –          | –            |
| Audio System                         | 516        | £6.02        |
| – Preampifier                        | 517        | £5.23        |
| – Mic. Supply Board                  | 518        | £6.02        |
| – Power Amp                          | 519        | £7.14        |
| ★ Pain Monitor                       | 520        | £7.45        |
| MotorAmp                             | –          | –            |
| Back-To-Basics 5                     | 521        | £5.87        |
| – Kitchen Timer                      | 522        | £6.02        |
| – Room Thermometer                   | –          | –            |
| All-Band Radio – Full Version        | 523        | £5.71        |
| – Mini Version                       | 524        | £5.23        |
| ★ Multicore Cable Tester – Main      | 525        | £6.19        |
| – Active                             | 526        | £5.55        |
| Back-To-Basics 6 – Daily Reminder    | 527        | £6.19        |
| – Whistle Switch                     | 528        | £5.87        |
| ★ Model Railway Signal Control       | 529        | £6.19        |
| ★ Snooker/Darts Scoreboard           | 530        | £8.72        |
| Photic Phone – Transmitter           | 531        | } pair £6.98 |
| – Receiver                           | 532        |              |
| Back-To-Basics 7 – Parking Radar     | 533        | £5.71        |
| – Telephone Switch                   | 534        | £5.55        |
| ★ Halloween Howler                   | 535        | £6.02        |
| ★ PIC-Based USB Interface            | 536        | £6.19        |

## EPE SOFTWARE

★ All software programs for EPE Projects marked with an asterisk, and others previously published, can be downloaded free from our Downloads site, accessible via our home page at: [www.epemag.co.uk](http://www.epemag.co.uk).




## EPE PRINTED CIRCUIT BOARD SERVICE

| Order Code  | Project | Quantity  | Price |
|---|---------|---|-------|
| Name .....  |         |   |       |
| Address .....   |         |   |       |
| Tel. No. ....   |         |   |       |
| I enclose payment of £..... (cheque/PO in £ sterling only) to:  |         |   |       |
|                        |         |  |       |
| <b>Everyday Practical Electronics</b>   |         |   |       |
| <b>MasterCard, Amex, Diners Club, Visa or Switch/Maestro</b>  |         |   |       |
| Card No. ....   |         |   |       |
| Valid From .....  |         | Expiry Date .....   |       |
| Card Security Code ..... Switch/Maestro Issue No .....  |         |   |       |
| (The last 3 digits on or just under the signature strip)  |         |   |       |
| Signature .....   |         |   |       |
| <b>NOTE: You can also order p.c.b.s by phone, Fax, Email or via our Internet site on a secure server:</b> |         |   |       |
| <a href="http://www.epemag.wimborne.co.uk/shopdoor.htm">http://www.epemag.wimborne.co.uk/shopdoor.htm</a> |         |   |       |

# ELECTRONICS MANUALS ON CD-ROM £29.95 EACH

## ELECTRONICS SERVICE MANUAL

## THE MODERN ELECTRONICS MANUAL

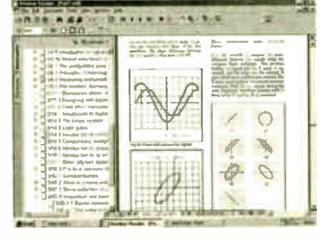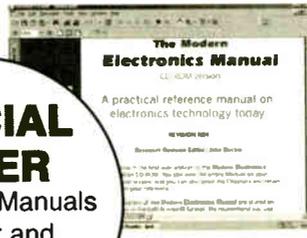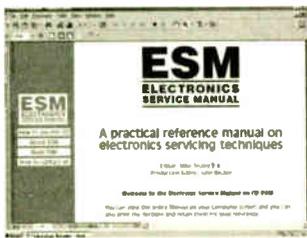

**SPECIAL OFFER**  
Order both Manuals together and **SAVE £10**

**Everything you need to know to get started in repairing electronic equipment**

- Around 900 pages • Fundamental principles • Troubleshooting techniques • Servicing techniques • Choosing and using test equipment • Reference data • Manufacturers' web links
- Easy-to-use Adobe Acrobat format • Clear and simple layout
- Vital safety precautions • Professionally written • Supplements

**SAFETY:** Safety Regulations, Electrical Safety and First Aid.  
**UNDERPINNING KNOWLEDGE:** Electrical and Electronic Principles, Active and Passive Components, Circuit Diagrams, Circuit Measurements, Radio, Computers, Valves and Manufacturers' Data, etc. **PRACTICAL SKILLS:** Learn how to identify Electronic Components, Avoid Static Hazards, Carry Out Soldering and Wiring, Remove and Replace Components. **TEST EQUIPMENT:** How to Choose and Use Test Equipment, Assemble a Toolkit, Set Up a Workshop, and Get the Most from Your Multimeter and Oscilloscope, etc. **SERVICING TECHNIQUES:** The Manual includes vital guidelines on how to Service Audio Amplifiers. The Supplements include similar guidelines for Radio Receivers, TV Receivers, Cassette Recorders, Video Recorders, Personal Computers, etc. **TECHNICAL NOTES:** Commencing with the IBM PC, this section and the Supplements deal with a very wide range of specific types of equipment – radios, TVs, cassette recorders, amplifiers, video recorders etc. **REFERENCE DATA:** Diodes, Small-Signal Transistors, Power Transistors, Thyristors, Triacs and Field Effect Transistors. Supplements include Operational Amplifiers, Logic Circuits, Optoelectronic Devices, etc.

**The essential reference work for everyone studying electronics**

- Over 800 pages • In-depth theory • Projects to build • Detailed assembly instructions • Full components checklists • Extensive data tables • Manufacturers' web links • Easy-to-use Adobe Acrobat format • Clear and simple layout • Comprehensive subject range • Professionally written • Supplements

**BASIC PRINCIPLES:** Electronic Components and their Characteristics; Circuits Using Passive Components; Power Supplies; The Amateur Electronics Workshop; The Uses of Semiconductors; Digital Electronics; Operational Amplifiers; Introduction to Physics, including practical experiments; Semiconductors and Digital Instruments.

**CIRCUITS TO BUILD:** The Base Manual describes 12 projects including a Theremin and a Simple TENS Unit.

**ESSENTIAL DATA:** Extensive tables on diodes, transistors, thyristors and triacs, digital and linear i.c.s.

**EXTENSIVE GLOSSARY:** Should you come across a technical word, phrase or abbreviation you're not familiar with, simply look up the glossary and you'll find a comprehensive definition in plain English.

The Manual also covers **Safety** and provides web links to component and equipment **Manufacturers and Suppliers**.

Full contents list available online at: [www.epemag.wimborne.co.uk](http://www.epemag.wimborne.co.uk)

**SUPPLEMENTS:** Additional CD-ROMs each containing approximately 500 pages of additional information on specific areas of electronics are available for £19.95 each. Information on the availability and content of each Supplement CD-ROM will be sent to you.

**Presentation:** CD-ROM suitable for any modern PC. Requires Adobe Acrobat Reader which is included on the CD-ROM.  
 Wimborne Publishing Ltd., Dept Y10, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562.

**PLEASE** send me



THE MODERN ELECTRONICS MANUAL CD-ROM

ELECTRONICS SERVICE MANUAL CD-ROM

I enclose payment of £29.95 (for one Manual) or £49.90 for both Manuals (saving £10 by ordering both together).

FULL NAME .....  
 (PLEASE PRINT)

ADDRESS .....

.....

.....

..... POSTCODE .....

SIGNATURE .....

I enclose cheque/PO in UK pounds payable to Wimborne Publishing Ltd.

Please charge my Visa/Mastercard/Amex/Diners Club/Switch/Maestro

Card No ..... Switch/Maestro Issue No .....

Valid From ..... Expiry Date .....

Card Security Code ..... (The last 3 digits on or just under the signature strip)

### ORDER FORM

Simply complete and return the order form with your payment to the following address:

Wimborne Publishing Ltd,  
 Dept. Y10,  
 408 Wimborne Road East, Ferndown,  
 Dorset BH22 9ND

Price includes postage to anywhere in the World

We will happily exchange any faulty CD-ROMs but since the content can be printed out we do not offer a refund on these items.

**Your CD-ROM(s) will be posted to you by first class mail or airmail, normally within four working days of receipt of your order**

Everyday Practical Electronics reaches twice as many UK readers as any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last twenty years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £10 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. VAT must be added. Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Phone: 01202 873872. Fax: 01202 874562. Email: epeads@wimborne.co.uk

For rates and information on display and classified advertising please contact our Advertisement Manager, Stewart Kearn as above.

## TOTALROBOTS

### ROBOTICS, CONTROL & ELECTRONICS TECHNOLOGY

High quality robot kits and components  
UK distributor of the OOPic microcontroller


Secure on-line ordering  
Rapid delivery  
Highly competitive prices

Visit [www.totalrobots.com](http://www.totalrobots.com)

**Tel: 01737 371688**
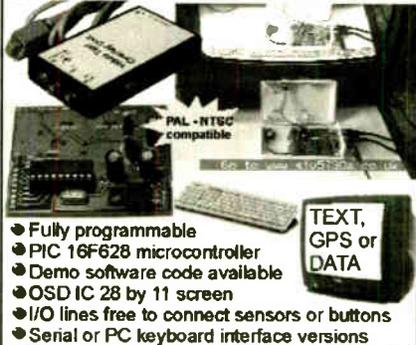
## The Versatile, Programmable On Screen Display System

[www.STV5730A.co.uk](http://www.STV5730A.co.uk)



- Fully programmable
- PIC 16F628 microcontroller
- Demo software code available
- OSD IC 28 by 11 screen
- I/O lines free to connect sensors or buttons
- Serial or PC keyboard interface versions

## VVT TRANSFORMERS

Transformers and Chokes for all types of circuits including specialist valve units  
Custom design or standard range  
High and low voltage

### Variable Voltage Technology Ltd

Unit 3, Sheat Manor Farm, Chillerton,  
Newport, Isle of Wight, PO30 3HP  
Tel: 0870 243 0414 Fax: 01983 721572

email: [sales@vvt-cowes.freemove.co.uk](mailto:sales@vvt-cowes.freemove.co.uk)  
[www.vvttransformers.co.uk](http://www.vvttransformers.co.uk)

## Miscellaneous

**MAKE YOUR HOBBY A BUSINESS.**  
Earn money making a unit for the partially sighted. Exclusive areas. Outlets provided. Full assembly Instruction manual and suppliers. DETAILS 02392 830158

**VALVES AND ALLIED COMPONENTS IN STOCK.** Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

**FREE! PROTOTYPE PRINTED CIRCUIT BOARDS!** Free prototype p.c.b. with quantity orders. Call Patrick on 028 9073 8897 for details. Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast BT5 4GX.

**PRINTED CIRCUIT BOARDS - QUICK SERVICE.** Prototype and production artwork raised from magazines or draft designs at low cost. PCBs designed from schematics. Production assembly, wiring and software programming. For details contact Patrick at Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast BT5 4GX. Phone 028 9073 8897, Fax 028 9073 1802, Email [agar@argonet.co.uk](mailto:agar@argonet.co.uk)

**½ PRICE VALVES AND RADIO & ELECTRONIC COMPONENTS**  
Catalogues available for £1 refundable on 1st order. Over 1480 different valves and over 500 radio/electronic components. W. Burcher, 676 Foxhall Road, Ipswich, Suffolk, IP3 8NQ. TEL: 01473 272218

**WANTED GRUNDIG YACHT BOY RADIO.** Must be model 210 from between 1970-1974. Must be in mint condition. Will pay very good money for a set in mint condition. Contact Peter Tankard on Tel 0114 2316321

## X-10® Home Automation

We put you in control™

**Why tolerate when you can automate?**

An extensive range of 230V X-10 products and starter kits available. Uses proven Power Line Carrier technology, no wires required.

Products Catalogue available Online.

Worldwide delivery.

### Laser Business Systems Ltd.

E-Mail: [info@laser.com](mailto:info@laser.com)

<http://www.laser.com>

Tel: (020) 8441 9788

Fax: (020) 8449 0430

**N.R. BARDWELL LTD**  
ELECTRONIC COMPONENT SUPPLIES  
Stock of I.e.d.s, Semiconductors, Resistors, Capacitors and many more items.  
Send 44p for lists or visit our secure online ordering of [www.bardwells.co.uk](http://www.bardwells.co.uk)  
288, Abbeydale Road, Sheffield. S7 1FL  
Email - [sales@bardwells.co.uk](mailto:sales@bardwells.co.uk)

## [www.pawbooks.co.uk](http://www.pawbooks.co.uk)

Using ICs. Pinout diagrams.  
Numeric control.

Interactive Demonstrations.

Write, save, load your own programs.  
See ICs working on screen.

## BOWOOD ELECTRONICS LTD

Suppliers of Electronic Components

Place a secure order on our website or call our sales line  
All major credit cards accepted

Web: [www.bowood-electronics.co.uk](http://www.bowood-electronics.co.uk)

Unit 1, McGregor's Way, Turnoaks Business Park,  
Chesterfield, S40 2WB. Sales: 01246 200222

Send 60p stamp for catalogue

Please  
mention EPE  
when replying to  
advertisements

To advertise your  
company

Contact:

Stewart Kearn

Tel: 01202 873872

Email:

[stewart.kearn@wimborne.co.uk](mailto:stewart.kearn@wimborne.co.uk)

## BTEC ELECTRONICS TECHNICIAN TRAINING

NATIONAL ELECTRONICS  
VCE ADVANCED ICT  
HNC AND HND ELECTRONICS  
FOUNDATION DEGREES  
NVQ ENGINEERING AND IT  
DESIGN AND TECHNOLOGY

LONDON ELECTRONICS COLLEGE  
20 PENYVERN ROAD  
EARLS COURT, LONDON SW5 9SU  
TEL: (020) 7373 8721  
[www.lec.org.uk](http://www.lec.org.uk)

## Rechargeable Batteries With Solder Tags

### NIMH

|            |       |
|------------|-------|
| AA 2000mAh | £2.82 |
| C 4Ah      | £4.70 |
| D 9Ah      | £7.60 |
| PP3 150mAh | £4.95 |



### NICAD

|           |       |
|-----------|-------|
| AA 650mAh | £1.41 |
| C 2.5Ah   | £3.60 |
| D 4Ah     | £4.95 |
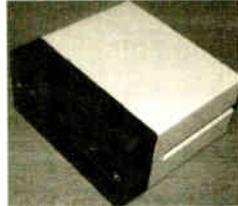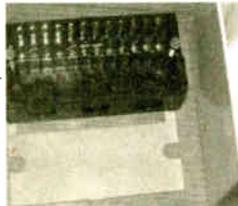
### Instrument case with edge connector and screw terminals

Size 112mm x 52mm x 105mm tall

This box consists of a cream base with a PCB slot, a cover plate to protect your circuit, a black lid with a 12 way edge connector and 12 screw terminals built in (8mm pitch) and 2 screws to hold the lid on. The cream bases have minor marks from dust and handling price £2.00 + VAT(=£2.35) for a sample or £44.00+VAT (=£51.70) for a box of 44.



866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily £7.46 + VAT = £8.77



Please add £1.66 + VAT = £1.95 postage & packing per order

## JPG Electronics

Shaws Row, Old Road, Chesterfield, S40 2RB.

Tel 01246 211202 Fax 01246 550959

www.JPGElectronics.com

Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

# ADVERTISERS INDEX

|                           |             |
|---------------------------|-------------|
| AUDON ELECTRONICS         | 705         |
| AVIT RESEARCH             | 705         |
| BETA-LAYOUT               | 705         |
| BREADBOARDING SYSTEMS     | 693         |
| BRUNNING SOFTWARE         | 666         |
| BULL GROUP                | Cover (ii)  |
| CONRAD ELECTRONICS        | 685         |
| DISPLAY ELECTRONICS       | 671         |
| EASYSYNC                  | 705         |
| ESR ELECTRONIC COMPONENTS | 674         |
| FAST COMPONENTS           | 671         |
| JAYCAR ELECTRONICS        | Cover (iv)  |
| JPG ELECTRONICS           | 736         |
| LABCENTER                 | Cover (iii) |
| LICHFIELD ELECTRONICS     | 704         |
| MAGENTA ELECTRONICS       | 672/673     |
| MICROCHIP TECHNOLOGY INC. | 681         |
| NURVE NETWORKS LLC        | 704         |
| PEAK ELECTRONIC DESIGN    | 701         |
| PICO TECHNOLOGY           | 713         |
| QUASAR ELECTRONICS        | 668/669     |
| SHERWOOD ELECTRONICS      | 736         |
| SQUIRES                   | 715         |
| STEWART OF READING        | 671         |

### ADVERTISEMENT OFFICES:

408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND

PHONE: 01202 873872

FAX: 01202 874562

EMAIL: epeads@wimborne.co.uk

For Editorial address and phone numbers see page 675

## SHERWOOD ELECTRONICS

### FREE COMPONENTS

Buy 10 x £1 Special Packs and choose another one FREE

|   |   |
|---|---|
| SP1 15 x 5mm Red LEDs                     | SP135 5 x Miniature slide switches                    |
| SP2 12 x 5mm Green LEDs                   | SP136 3 x BFY50 transistors                           |
| SP3 12 x 5mm Yellow LEDs                  | SP137 4 x W005 1-5A bridge rectifiers                 |
| SP5 25 x 5mm 1 part LED clips             | SP138 20 x 2-2/63V radial elect. caps.                |
| SP6 15 x 3mm Red LEDs                     | SP140 3 x W04 1-5A bridge rectifiers                  |
| SP7 12 x 3mm Green LEDs                   | SP142 2 x CMOS 4017                                   |
| SP8 10 x 3mm Yellow LEDs                  | SP143 5 Pairs min. crocodile clips (Red & Black)      |
| SP9 25 x 3mm 1 part LED clips             | SP144 5 Pairs min. crocodile clips (assorted colours) |
| SP10 100 x 1N4148 diodes                  | SP146 10 x 2N3704 transistors                         |
| SP11 30 x 1N4001 diodes                   | SP147 5 x Stripboard 9 strips x 25 holes              |
| SP12 30 x 1N4002 diodes                   | SP151 4 x 8mm Red LEDs                                |
| SP18 20 x BC182 transistors               | SP152 4 x 8mm Green LEDs                              |
| SP20 20 x BC184 transistors               | SP153 4 x 8mm Yellow LEDs                             |
| SP23 20 x BC549 transistors               | SP154 15 x BC548 transistors                          |
| SP24 4 x CMOS 4001                        | SP156 3 x Stripboard, 14 strips x 27 holes            |
| SP25 4 x 555 timers                       | SP160 10 x 2N3904 transistors                         |
| SP26 4 x 741 Op.Amps                      | SP161 10 x 2N3906 transistors                         |
| SP28 4 x CMOS 4011                        | SP164 2 x C106D thyristors                            |
| SP29 3 x CMOS 4013                        | SP165 2 x LF351 Op.Amps                               |
| SP33 4 x CMOS 4081                        | SP166 20 x 1N4003 diodes                              |
| SP34 20 x 1N914 diodes                    | SP167 5 x BC107 transistors                           |
| SP36 25 x 10/25V radial elect. caps.      | SP168 5 x BC108 transistors                           |
| SP37 12 x 100/35V radial elect. caps.     | SP171 8 Metres 18SWG solder                           |
| SP38 15 x 47/25V radial elect. caps.      | SP172 4 x Standard slide switches                     |
| SP39 10 x 470/16V radial elect. caps.     | SP173 10 x 220/25V radial elect. caps                 |
| SP40 15 x BC237 transistors               | SP174 20 x 22/25V radial elect. caps                  |
| SP41 20 x Mixed transistors               | SP175 20 x 1/63V radial elect. caps.                  |
| SP42 200 x Mixed 0-25W C.F. resistors     | SP177 10 x 1A 20mm quick blow fuses                   |
| SP47 5 x Min. PB switches                 | SP178 10 x 2A 20mm quick blow fuses                   |
| SP49 4 x 5 metres stranded core wire      | SP181 5 x Phono plugs - assid colours                 |
| SP101 8 Metres 22SWG solder               | SP182 20 x 4-7/63V radial elect. caps.                |
| SP102 20 x 8-pin DIL sockets              | SP183 20 x BC547 transistors                          |
| SP103 15 x 14-pin DIL sockets             | SP187 15 x BC239 transistors                          |
| SP104 15 x 16-pin DIL sockets             | SP189 4 x 5 metres solid core wire                    |
| SP105 4 x 74LS00                          | SP192 3 x CMOS 4066                                   |
| SP109 15 x BC557 transistors              | SP195 3 x 10mm Yellow LEDs                            |
| SP112 4 x CMOS 4093                       | SP197 6 x 20 pin DIL sockets                          |
| SP115 3 x 10mm Red LEDs                   | SP198 5 x 24 pin DIL sockets                          |
| SP116 3 x 10mm Green LEDs                 | SP199 5 x 2-5mm mono jack plugs                       |
| SP118 2 x CMOS 4047                       | SP200 5 x 2-5mm mono jack sockets                     |
| SP124 20 x Assorted ceramic disc caps     |   |
| SP126 6 x Battery clips - 3 ea. PP3 + PP9 |   |
| SP130 100 x Mixed 0-5W C.F. resistors     |   |
| SP131 2 x TL071 Op.Amps                   |   |
| SP133 20 x 1N4004 diodes                  |   |
| SP134 15 x 1N4007 diodes                  |   |

### RESISTOR PACKS - C.Film

|                                     |       |
|-------------------------------------|-------|
| RP3 5 each value - total 365 0-25W  | £3.30 |
| RP7 10 each value - total 730 0-25W | £4.55 |
| RP10 1000 popular values 0-25W      | £6.45 |
| RP4 5 each value-total 345 0-5W     | £4.20 |
| RP8 10 each value-total 690 0-5W    | £6.85 |
| RP11 1000 popular values 0-5W       | £8.70 |

2005 Catalogue available £1 inc. P&P or FREE with first order. P&P £1.50 per order. NO VAT Cheques and Postal Orders to: Sherwood Electronics, 7 Williamson St., Mansfield, Notts. NG19 6TD.

## EPE SUBSCRIPTIONS

SAVE 71p AN ISSUE OVER UK NEWSTAND PRICES ON A UK ONE YEAR SUBSCRIPTION

Subscriptions for delivery direct to any address in the UK: 6 months £16.50, 12 months £31, two years £57; Overseas: 6 months £19.50 standard air service or £28.50 express airmail, 12 months £37 standard air service or £55 express airmail, 24 months £69 standard air service or £105 express airmail. Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to *EPE Subs. Dept.*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Switch or Visa. (For past issues see the Back Issues page.)

## ONLINE SUBSCRIPTIONS

Online subscriptions, for downloading the magazine via the Internet, \$14.99US (approx. £8) for one year available from [www.epemag.com](http://www.epemag.com).


## USA/CANADA SUBSCRIPTIONS

To subscribe to *EPE* from the USA or Canada please telephone Express Mag toll free on 1877 363-1310 and have your credit card details ready. Or fax (514) 355 3332 or write to Express Mag, PO Box 2769, Plattsburgh, NY 12901-0239 or Express Mag, 8155 Larrey Street, Anjou, Quebec, H1J 2L5. Email address: [expmag@expressmag.com](mailto:expmag@expressmag.com). Web site: [www.expressmag.com](http://www.expressmag.com). USA price \$60(US) per annum, Canada price \$97(Can) per annum - 12 issues per year.

*Everyday Practical Electronics*, periodicals pending, ISSN 0262 3617 is published twelve times a year by Wimborne Publishing Ltd., USA agent USACAN at 1320 Route 9, Champlain, NY 12919. Subscription price in US \$60(US) per annum. Periodicals postage paid at Champlain NY and at additional mailing offices. POSTMASTER: Send USA and Canada address changes to *Everyday Practical Electronics*, c/o Express Mag., PO Box 2769, Plattsburgh, NY, USA 12901-0239.

# PROTEUS

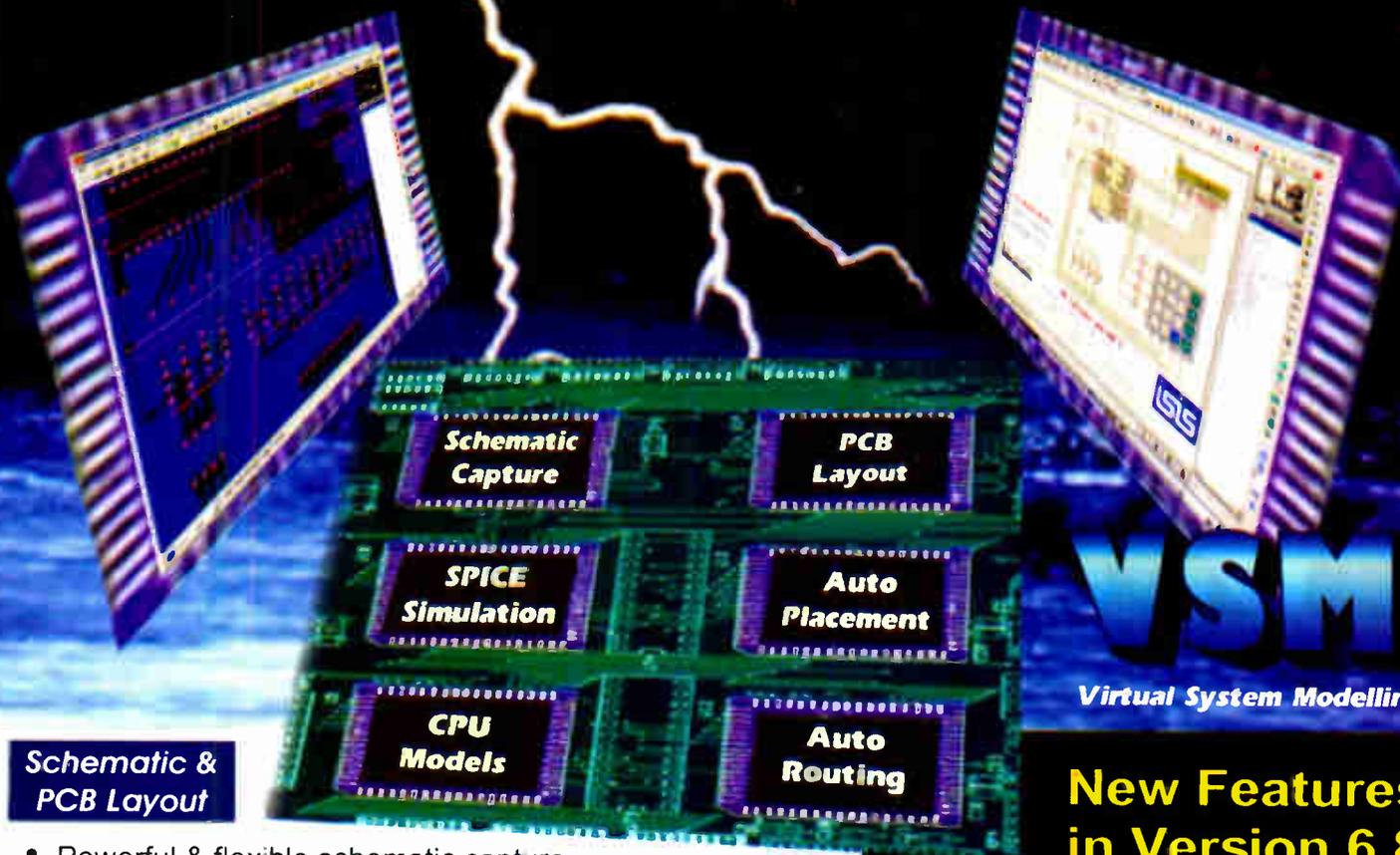**The Complete Electronics Design System**



## Schematic & PCB Layout

- Powerful & flexible schematic capture.
- Auto-component placement and rip-up/retry PCB routing.
- Polygonal gridless ground planes.
- Libraries of over 8000 schematic and 1000 PCB parts.
- Bill of materials, DRC reports and much more.

## Mixed Mode SPICE Circuit Simulation

- Berkeley SP CE3F5 simulator with custom extensions for true mixed mode and interactive simulation.
- 6 virtual instruments and 14 graph based analysis types.
- 6000 models including TTL, CMOS and PLD digital parts.
- Fully compatible with manufacturers' SPICE models.

## Proteus VSM - Co-simulation and debugging for popular Micro-controllers

- Supports PIC, AVR, 8051, ARM7 and BASIC STAMP micro-controllers.
- Co-simulate target firmware with your hardware design.
- Includes interactive peripheral models for LED and LCD displays, switches, keypads, virtual terminal and much, much more.
- Compatible with popular compilers and assemblers from Microchip, Crownhill, IAR, Keil, and others.

## New Features in Version 6.8

- Interactive Design Rule Check.
- Mitring / Unmitring.
- Enhanced track editing.
- Struct/Array expansion.
- ELF/DWARF file loader.
- Expanded model libraries.

**Call Now for Upgrade Pricing**

**NEW**

**ARM/LPC2000**

**MODELS FOR  
PROTEUS VSM  
NOW AVAILABLE**

**labcenter**  
*Electronics*  
53-55 Main Street, Grassington. BD23 5AA

Tel: 01756 753440  
Fax: 01756 752857

Contact us for  
**Free Demo CD**

**www.labcenter.co.uk**  
**info@labcenter.co.uk**

# This is where we live!

## Jaycar Electronics

Yes that's right, down town, down under in Sydney Australia. We are a bunch of electronics enthusiasts who sell a great range of goodies through our FREE 400 page catalogue! (see below) Don't be frightened! You can purchase on the Net from us 24/7/365 through our secure encrypted system. Post and packing charges are modest and you can have any of 8000 + unique products delivered to your door within 7 - 10 days of your order. Some specific products are shown below.

### Theremin Synthesiser Kit

KC-5295 £17.50 + post & packing

The Theremin is a weird musical instrument that was invented early last century but is still used today. The Beach Boys' classic hit "Good Vibrations" featured a Theremin. By moving your hand between the antenna and metal plate, you create weird sound effects like in those scary movies!

Kit includes a machined, silk-screened, and pre drilled case, circuit board, all electronic components, and clear English instructions.



9VDC power supply required (Maplin #G674R £9.99).

### 50MHz Frequency Meter Kit with LCD Display

KC-5369 £20.30 + post & packing

If you want a great value frequency meter, then this project is for you. It features autoranging operation for ease of use, switching between its three ranges. High resolution of 0.1Hz up to 150Hz, 1Hz between 150Hz and 16MHz, and 10Hz above 16MHz. It can be powered by a 9V battery or wall adaptor (not included) and the case measures just 5 1/8" x 2 5/8" x 1". Kit includes laser cut & silk screened case, circuit board, electronic components, & clear English instructions.



### Lead Acid Battery Zapper Kit

KC-5414 £11.75 + post and packing

This simple circuit is designed to produce bursts of high-energy pulses to help reverse the effects of sulfation in "wet" lead acid batteries. This is particularly useful when the battery has been sitting for a period of time without use. Kit includes circuit board, case, leads, electronic components, and clear English instructions.



NEW KIT




Caution! Battery should be disconnected from the vehicle when using this project


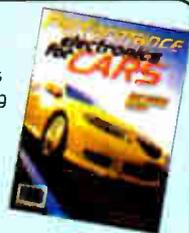
### Performance Electronics for Cars Book

BS-5080 £6.35 + post & packing

Australia's leading electronics magazine, Silicon Chip, has developed a range of projects for performance cars. There are 16 projects in total, ranging from devices for remapping fuel curves, to nitrous controllers, and more! The book includes all instructions, components lists, colour pictures, and circuit layouts. There are also chapters on engine management, advanced systems, DIY modifications, and more. Over 150 pages! All of the projects described are available in kit form, exclusively from Jaycar. Check out our website for all the details.



Here are just two...

### Universal Voltage Switch Kit

KC-5377 £8.70 + post and packing

This is a universal module which can be adapted to suit a range of different applications. It will trip a relay when a preset voltage is reached. It can be configured to trip with a rising or falling voltage, so it is suitable for a wide variety of voltage outputting devices eg., throttle position sensor, air flow sensor, EGO sensor. It also features adjustable hysteresis (the difference between trigger on/off voltage), making it extremely versatile. You could use it to trigger an extra fuel pump under high boost, anti-lag wastegate shutoff, and much more. Kit supplied with PCB, and all electronic components.



Recommended box UB2 £0.97 each



### Smart Fuel Mixture Display


KC-5374 £8.15 + post & packing

This new 'smart' version has a few additional touches such as, auto dimming for night driving, emergency lean-out alarm, and better circuit protection. Another great feature, is the 'dancing' display which operates when the ECU is operating in closed loop. Closed loop means that the air/fuel ratio is optimum for fuel economy and emission performance. Kit supplied with PCB and all electronic components.

\* Car must be fitted with air flow and EGO sensors (standard on all EFI systems) for full functionality.



Recommended box UB3 £0.97 each

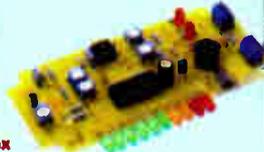

### Digital Fuel Mixture Display

KC-5300 £18.30 + post and packaging

Monitor your car's air fuel ratio in real time on a three-digit display as well as on the programmable 10-LED bargraph. The kit will indicate ratios between 11.8 & 20.6 for petrol and 12.7 & 21.5 for propane/LPG. Features include: lean and rich indication, fast 220ms update time for bargraph, 440ms update time for 3-digit display, 0-1V display for setting up adjustments, dot or bar option for bargraph and automatic display dimming for night driving. All this in a case measuring just 3.25 x 2.12 x 1.22 in. Kit includes case with silk-screened panel, PCBs, pre-programmed PIC micro, 7-segment displays, red acrylic, hook-up wire and all electronic components.

## We Stock...

Electronic Components, Sub-Assemblies & Electronic Kits

Power Products & Accessories

Audio & Visual Equipment & Accessories

Computer & Telecoms Accessories

Burglar Alarms & Surveillance Equipment

Lighting Products & Accessories

Gadgets & Unique Gifts

### Post and Packing Charges:

| Order Value    | Cost |
|----------------|------|
| £20 - £49.99   | £5   |
| £50 - £99.99   | £10  |
| £100 - £199.99 | £20  |
| £200 - £499.99 | £30  |
| £500+          | £40  |

Max weight 12lb (5kg) - heavier parcels POA. Minimum order £20.

Log on to [www.jaycarelectronics.co.uk/catalogue](http://www.jaycarelectronics.co.uk/catalogue) for your FREE catalogue!

0800 032 7241

(Monday - Friday 09.00 to 17.30 GMT + 10 hours only).

For those who want to write:  
100 Silverwater Rd Silverwater NSW 2128  
Sydney AUSTRALIA



400+ page Catalogue