

THE No 1 UK MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EPE EVERYDAY PRACTICAL ELECTRONICS

www.epemag.co.uk

www.epemag.com

STUDENTS' AMP

- * 14Hz to 100kHz frequency response
- * <0.04% total harmonic distortion
- * 105dB signal-to-noise ratio
- * 20W RMS output



STAR POWER

High efficiency supply for
Luxeon Star LEDs
Ideal for use in cars,
caravans and boats



FREE ENTRY COMPETITION

Win a Microchip PICkit 2 Debug Express Kit

APRIL 2007 £3.50



Plus * PIC Polyphonium Pt2 * SMS Controller Pt2



HB7 Stirling Engine


Base measurements: 128 mm x 108 mm x 170 mm, 1 kg
 Base plate: beech - Working rpm: 2000 rpm/min. (the engine has a aluminium good cooling Cylinder)
 Bearing application: 10 high-class ball-bearings
 Material: screw, side parts all stainless steel
 Cylinder brass, Rest aluminium and stainless steel.
 Available as a kit £80.75 or built £84.99
www.mamodspares.co.uk



STEAM ENGINE KIT

Everything in the kit enables you to build a fully functional model steam engine. The main material is brass and the finished machine demonstrates the principle of oscillation. The boiler, uses solid fuel tablets, and is quite safe. All critical parts (boiler, end caps, safety vent etc.) are ready finished to ensure success. The very detailed instruction booklet (25 pages) makes completion of this project possible in a step by step manner. Among the techniques experienced are silver soldering, folding, drilling, fitting and testing. £29.70 ref STEAMKIT Silver solder/flux pack £3.50 ref SSK

www.mamodspares.co.uk

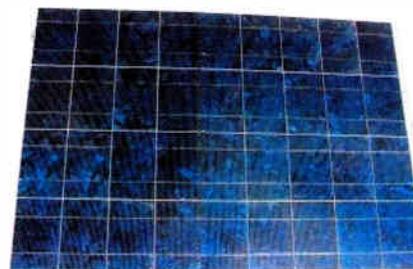

Solar Panels

We stock a range of solar photovoltaic panels. These are polycrystalline panels made from wafers of silicon laminated between an impact-resistant transparent cover and an EVA rear mounting plate. They are constructed with a lightweight anodised aluminium frame which is predrilled for linking to other frames/roof mounting structure, and contain waterproof electrical terminal box on the rear. 5 watt panel £29 ref 5wnav 20 watt panel £99 ref 20wnav 60 watt panel £249 ref 60wnav. Suitable regulator for up to 60 watt panel £20 ref REGNAV



HB9 Stirling engine

Base measurements: 156 mm x 108 mm x 130 mm, 0,6 Kg
 Base plate: beech Working rpm: approx. 2,000 min
 Bearing application: 6 high-class ball-bearings
 Material of the engine: brass, aluminium, stainless steel
 running time: 30-45 min.
 Available as a kit £97.75 or built £101.99
www.mamodspares.co.uk



HB14 Stirling Engine

Base measurements: 156 mm x 108 mm x 150 mm, 1 kg
 Base plate: beech Working rpm: 2000 - 2500 rpm/min. .
 Incl. drive-pulley for external drives Bearing application: 10 high-class ball-bearings Material: screw, side parts total stainless steel Cylinder brass Rest aluminium, stainless steel Available as a kit £140.25 or built £144.50
www.mamodspares.co.uk



Solar evacuated tube panels

(20 tube shown) These top-of-the-range solar panel heat collectors are suitable for heating domestic hot water, swimming pools etc - even in the winter! One unit is adequate for an average household (3-4 people), and it is modular, so you can add more if required. A single panel is sufficient for a 200 litre cylinder, but you can fit 2 or more for high water usage, or for heating swimming pools or underfloor heating. Some types of renewable energy are only available in certain locations, however free solar heating is potentially available to almost every house in the UK! Every house should have one - really! And with an overall efficiency of almost 80%, they are much more efficient than electric photovoltaic solar panels (efficiency of 7-15%). Available in 10, 20 and 30 tube versions. 10 tube £199, 20 tube £369, 30 tube £549. Roof mounting kits (10/20 tubes) £12.50, 30 tube mounting kit £15



HB10 Stirling Engine

Base measurements: 156 mm x 108 mm x 130 mm, 0,6 Kg
 Base plate: beech Working rpm: approx. 2,000 rpm
 Bearing application: 6 high-class ball-bearings
 Material of the engine: brass, aluminium, stainless steel
 running time: 30-45 min
 Available as a kit £97.75 or built £101.99
www.mamodspares.co.uk



HB15 Stirling Engine

Base measurements: 128 mm x 108 mm x 170 mm, 0,75 kg
 Base plate: beech Working rpm: 2000 rpm/min. (the engine has a aluminium good cooling Cylinder)
 Bearing application: 6 high-class ball-bearings
 Material: screw, side parts total stainless steel
 Cylinder brass Rest aluminium, stainless steel
 Available as a kit £97.75 or built £102
www.mamodspares.co.uk



HB11 Stirling Engine

Base measurements: 156 mm x 108 mm x 130 mm, 0,7 Kg
 Base plate: beech
 Working rpm: 2000 - 2500 rpm/min, run Bearing application: 4 high-class ball-bearings Material: screw, side parts total stainless steel Cylinder brass Rest aluminium, stainless steel.
 Available as a kit £97.75 or built £101.99
www.mamodspares.co.uk



HB16 Stirling Engine

Base measurements: 128 mm x 108 mm x 170 mm, 1 kg
 Base plate: beech Working rpm: 2000 rpm/min. (the engine has a aluminium good cooling Cylinder)
 Bearing application: 10 high-class ball-bearings
 Material: screw, side parts total stainless steel
 Cylinder brass Rest aluminium, stainless steel.
 Available as a kit £140.25 or built £144.50



HB12 Stirling Engine

Base measurements: 156 mm x 108 mm x 130 mm, 1 Kg
 Base plate: beech Working rpm: 2000 - 2500 rpm/min, Bearing application: 6 high-class ball-bearings
 Material: screw, side parts total stainless steel
 Cylinder brass Rest aluminium, stainless steel.
 Available as a kit £136 or built £140.25
www.mamodspares.co.uk



2kW WIND TURBINE KIT

The 2kW wind turbine is supplied as the following kit: turbine generator 48v three taper/ twisted fibreglass blades & hub 8m tower (four x 2m sections) guylines / anchors / tensioners / clamps foundation steel rectifier 2kW inverter heavy-duty pivot tower. £1,499



HB13 Stirling Engine

Base measurements: 156 mm x 108 mm x 150 mm, 0,75 kg
 Base plate: beech Working rpm: 2000 - 2500 rpm/min,
 Bearing application: 6 high-class ball-bearings Material: screw, side parts total stainless steel Cylinder brass
 Available as a kit £97.75 or built £101.99



BENCH PSU 0-15V 0-2a Output and voltage are both smooth and can be regulated according to work, Input 230V, 2 1/2-number LCD display for voltage and current, Robust PC-grey housing Size 13x15x21cm, Weight 3,2kg £48 REF trans2



NEW ELECTRONIC CONSTRUCTION KITS

This 30 in 1 electronic kit includes an introduction to electrical and electronic technology. It provides components that can be used to make a variety of experiments including Timers and Burglar Alarms. Requires: 3 x AA batteries. £15.00 ref BET1803

AM/FM Radio This kit enables you to learn about electronics and also put this knowledge into practice so you can see and hear the effects. Includes manual with explanations about the components and the electronic principles. Req's: 3 x AA batts. £13 ref BET1801

This 40 in 1 electronic kit includes an introduction to electrical and electronic technology. It provides components that can be used in making basic digital logic circuits, then progresses to using Integrated circuits to make and test a variety of digital circuits, including Flip Flops and Counters. Req's: 4 x AA batteries. £17 ref BET1804

The 75 in 1 electronic kit includes an introduction to electrical and electronic technology. It provides components that can be used to make and test a wide variety of experiments including Water Sensors, Logic Circuits and Oscillators. The kit then progresses to the use of an integrated circuit to produce digital voice and sound recording experiments such as Morning Call and Burglar Alarm. Requires: 3 x AA batteries. £20 ref BET1806

www.slips.co.uk

BULL GROUP LTD
 UNIT D HENFIELD BUSINESS PARK
 HENFIELD SUSSEX BN9 9SL
 TERMS: C/ CARDS, CASH, PO, CHEQUE OR
 ONLINE ORDERING. PRICES PLUS VAT
 UK DELIVERY £5.50
 TEL 0870 7707520 FAX 01273 491813
 sales@bullnet.co.uk

ISSN 0262 3617





PROJECTS ... THEORY ...
NEWS ... COMMENT ...
POPULAR FEATURES ...

VOL. 36. No. 4 APRIL 2007

EPE EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

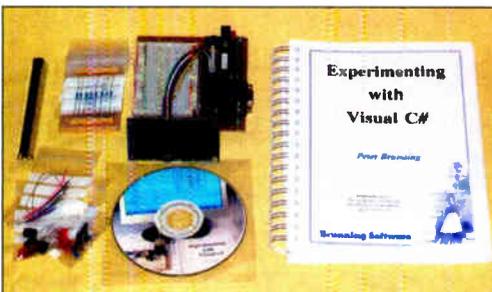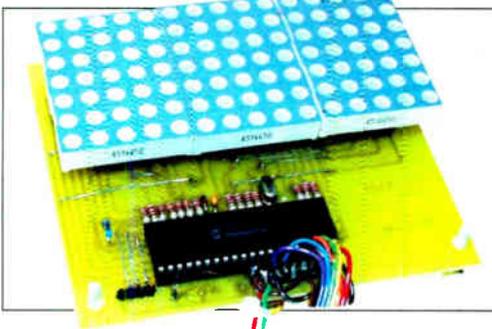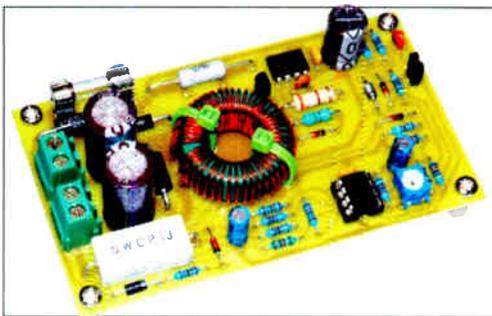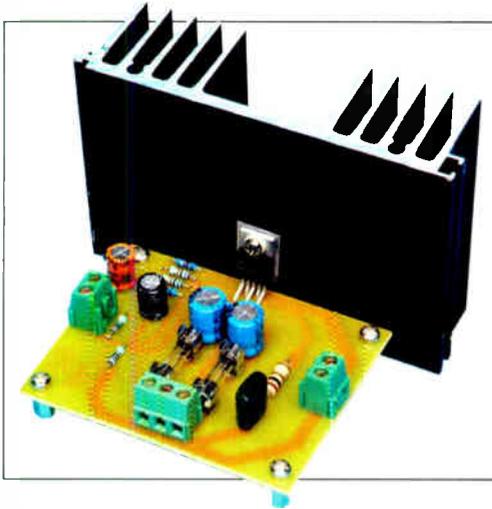www.epemag.co.uk
EPE Online: www.epemag.com



© Wimborne Publishing Ltd 2007. Copyright in all drawings, photographs and articles published in *EVERYDAY PRACTICAL ELECTRONICS* is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our May 2007 issue will be published on Thursday, 12 April 2007, see page 72 for details.

Projects and Circuits

- STUDENTS' AMP** by Peter Smith 10
Great sound, inexpensive, easy to build 20W module
- STAR POWER** by Peter Smith 22
Luxeon Star LED supply that runs off 12V DC, ideal for cars, caravans and boats
- PIC POLYPHONIUM – PART 2** by John Becker 38
LED display interface
- SMS CONTROLLER – PART 2** by Peter Smith 50
Control equipment from anywhere using SMS and an old Nokia mobile phone
- INGENUITY UNLIMITED – Sharing your Ideas with others** 58
Wind Speed Monitor

Series and Features

- TECHNO TALK** by Mark Nelson 16
Automotive electronics looks set to change
- PIC N' MIX** by Mike Hibbett 18
PICs and USARTs
- INTERFACE** by Robert Penfold 30
Are your software programs Vista compatible?
- VISUAL C TRAINING COURSE** by Robert Penfold 46
Review of a new product
- CIRCUIT SURGERY** By Ian Bell 55
Active current measurement
- NET WORK – THE INTERNET PAGE** surfed by Alan Winstanley 64
A failing memory; Biometric memory gets a thumbs up

Regulars and Services

- EDITORIAL** 7
- NEWS** – Barry Fox highlights technology's leading edge 8
Plus everyday news from the world of electronics
- FREE ENTRY COMPETITION** 29
Win a Microchip PICkit 2 Debug Express Kit!
- CD-ROMS FOR ELECTRONICS** 34
A wide range of CD-ROMs for hobbyists, students and engineers
- READOUT** John Becker addresses general points arising 61
- DIRECT BOOK SERVICE** 66
A wide range of technical books available by mail order, plus more CD-ROMs
- EPE PCB SERVICE** 70
PCBs for *EPE* projects
- ADVERTISERS' INDEX** 72

Readers' Services • Editorial and Advertisement Departments 7



08717 Credit Card Sales 177 168

PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £15.00
18Vdc Power supply (PSU010) £19.95
Leads: Parallel (LDC136) £4.95 / Serial (LDC441) £4.95 / USB (LDC644) £2.95

NEW! USB & Serial Port PIC Programmer



USB/Serial connection. Header cable for ICSP. Free Windows XP software. See website for PICs supported. ZIF Socket and USB lead extra. 18Vdc.

Kit Order Code: 3149KT - £37.95
Assembled Order Code: AS3149 - £49.95

NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows XP Software. ZIF Socket and USB lead not incl. Assembled Order Code: AS3128 - £44.95
Assembled with ZIF socket Order Code: AS3128ZIF - £59.95



'PICALL' ISP PIC Programmer



Will program virtually all 8 to 40 pin serial-mode AND parallel-mode (PIC15C family) PIC microcontrollers. Free Windows software. Blank chip auto detect for super fast bulk programming. Optional ZIF socket.

Assembled Order Code: AS3117 - £24.95
Assembled with ZIF socket Order Code: AS3117ZIF - £39.95

ATMEL 89xxx Programmer



Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16Vdc.

Kit Order Code: 3123KT - £24.95
Assembled Order Code: AS3123 - £34.95

Introduction to PIC Programming

Go from complete beginner to burning a PIC and writing code in no time! Includes 49 page step-by-step PDF Tutorial Manual, Programming Hardware (with LED test section), Win 3.11—XP Programming Software (Program, Read, Verify & Erase), and 1rewritable PIC16F84A that you can use with different code (4 detailed examples provided for you to learn from). PC parallel port. Kit Order Code: 3081KT - £16.95
Assembled Order Code: AS3081 - £24.95



ABC Maxi AVR Development Board

The ABC Maxi is ideal for developing new designs. Open architecture built around an ATMEL AVR AT90S8535 microcontroller. All circuits are embedded within the package and additional add-on expansion modules are available to assist you with project development.



Features

8 Kb of In-System Programmable Flash (1000 write/erase cycles) • 512 bytes internal SRAM • 512 bytes EEPROM • 8 analogue inputs (range 0-5V) • 4 Opto-isolated Inputs (I/Os are bi-directional with internal pull-up resistors) • Output buffers can sink 20mA current (direct LED drive) • 4 x 12A open drain MOSFET outputs • RS485 network connector • 2-16 LCD Connector • 3.5mm Speaker Phone Jack • Supply: 9 12Vdc

The ABC Maxi STARTER PACK includes one assembled Maxi Board, parallel and serial cables, and Windows software CD-ROM featuring an Assembler, BASIC compiler and in-system programmer. Order Code ABCMAXISP - £89.95
The ABC Maxi boards only can also be purchased separately at £69.95 each.

Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU for all units: Order Code PSU445 £8.95

Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two & Ten Channel versions also available. Kit Order Code: 3180KT - £44.95
Assembled Order Code: AS3180 - £51.95



Computer Temperature Data Logger



Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 38x38mm. Powered by PC. Includes one DS1820 sensor and four header cables. Kit Order Code: 3145KT - £18.95
Assembled Order Code: AS3145 - £25.95
Additional DS1820 Sensors - £3.95 each

Most items are available in kit form (KT suffix) or pre-assembled and ready for use (AS prefix).

DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12Vdc. Kit Order Code: 3140KT - £46.95
Assembled Order Code: AS3140 - £59.95



Serial Port Isolated I/O Relay Module



Computer controlled 8 channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch states, etc).

Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Once programmed, unit can operate without PC. Includes plastic case 130x100x30mm. Power: 12Vdc/500mA. Kit Order Code: 3108KT - £54.95
Assembled Order Code: AS3108 - £64.95

Infrared RC 12-Channel Relay Board



Control 12 onboard relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm. Supply: 12Vdc/0.5A

Kit Order Code: 3142KT - £47.95
Assembled Order Code: AS3142 - £59.95

PC / Standalone Unipolar Stepper Motor Driver

Drives any 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps max. Provides speed and direction control. Operates in stand-alone or PC-controlled mode. Up to six 3179 driver boards can be connected to a single parallel port. Supply: 9Vdc. PCB: 80x50mm. Kit Order Code: 3179KT - £11.95
Assembled Order Code: AS3179 - £18.95



Bi-Polar Stepper Motor Driver also available (Order Code 3158 - details on website)

DC Motor Speed Controller (100V/7.5A)



Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 9-18Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - £13.95
Assembled Order Code: AS3067 - £19.95

Bidirectional DC Motor Driver also available (Order Code 3166 - details on website)

Hot New Kits This Summer!

Here are a few of the most recent kits added to our range. See website or join our email Newsletter for all the latest news.

EPE Ultrasonic Wind Speed Meter



Solid-state design wind speed meter (anemometer) that uses ultrasonic techniques and has no moving parts and

does not need calibrating. It is intended for sports-type activities, such as track events, sailing, hang-gliding, kites and model aircraft flying, to name but a few. It can even be used to monitor conditions in your garden. The probe is pointed in the direction from which the wind is blowing and the speed is displayed on an LCD display.

Specifications

- Units of display: metres per second, feet per second, kilometres per hour and miles per hour
- Resolution: Nearest tenth of a metre
- Range: Zero to 50mph approx.

Based on the project published in *Everyday Practical Electronics*, Jan 2003. We have made a few minor design changes (see website for full details). Power: 9Vdc (PP3 battery). Main PCB: 50x83mm. Kit Order Code: 3168KT - £36.95

Audio DTMF Decoder and Display




Detects DTMF tones via an onboard electret microphone or direct from the phone lines through an audio transformer. The numbers are displayed on a 16

character, single line display as they are received. Up to 32 numbers can be displayed by scrolling the display left and right. There is also a serial output for sending the detected tones to a PC via the serial port. The unit will not detect numbers dialled using pulse dialling. Circuit is microcontroller based. Supply: 9-12V DC (Order Code **PSU445**). Main PCB: 55x95mm.

Kit Order Code: 3153KT - £20.95

Assembled Order Code: AS3153 - £29.95

EPE PIC Controlled LED Flasher

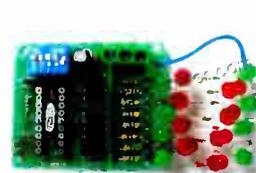

This versatile PIC based LED or filament bulb flasher can be used to flash from 1 to 176 LEDs. The user

arranges the LEDs in any pattern they wish. The kit comes with 8 super bright red LEDs and 8 green LEDs. Based on the Versatile PIC Flasher, *EPE Magazine* Dec 02. See website for full details. Board Supply: 9-12Vdc. LED supply: 9-45Vdc (depending on number of LED used). PCB: 43x54mm. Kit Order Code: 3169KT - £11.95

Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

FM Bugs & Transmitters

Our extensive range goes from discreet surveillance bugs to powerful FM broadcast transmitters. Here are a few examples. All can be received on a standard FM radio and have adjustable transmitting frequency.

MMTX' Micro-Miniature 9V FM Room Bug



Our best selling bug! Good performance. Just 25x15mm. Sold to detective agencies worldwide. Small enough to hide just about anywhere.

Operates at the 'less busy' top end of the commercial FM waveband and also up into the more private Air band. Range: 500m. Supply: PP3 battery. Kit Order Code: 3051KT - £8.95
Assembled Order Code: AS3051 - £14.95

HPTX' High Power FM Room Bug

Our most powerful room bug.

Very impressive performance. Clear and stable output signal thanks to the extra circuitry employed. Range: 1000m @ 9V. Supply: 6-12V DC (9V PP3 battery clip supplied). 70x15mm. Kit Order Code: 3032KT - £9.95
Assembled Order Code: AS3032 - £17.95



MTTX' Miniature Telephone Transmitter



Attach anywhere along phone line. Tune a radio into the signal and hear exactly what both parties are saying. Transmits only

when phone is used. Clear, stable signal. Powered from phone line so completely maintenance free once installed. Requires no aerial wire - uses phone line as antenna. Suitable for any phone system worldwide. Range: 300m. 20x45mm. Kit Order Code: 3016KT - £7.95
Assembled Order Code: AS3016 - £13.95

Wide Band Synthesised FM Transmitter



PLL based crystal-locked wide band FM transmitter delivering a high quality, stable 10mW output.

Accepts both MIC audio signal (10mV) and LINE input (1V p-p) for example hi-fi, CD, audio mixer (like our kit 1052) or computer sound card. Supply: 9-15Vdc. Kit Order Code: 3172KT - £19.95
Assembled Order Code: AS3172 - £32.95

3 Watt FM Transmitter



Small, powerful FM transmitter. Audio pre-amp stage and three RF stages deliver 3 watts of RF power. Use with the

electret microphone supplied or any line level audio source (e.g. CD or tape OUT, mixer, sound card, etc). Aerial can be an open dipole or Ground Plane. Ideal project for the novice wishing to get started in the fascinating world of FM broadcasting. 45x145mm. Kit Order Code: 1028KT - £23.95
Assembled Order Code: AS1028 - £31.95



QUASAR
electronics
Get Plugged In!

**Credit
Card
Sales
0871
717
7168**

Electronic Project Labs

Great introduction to the world of electronics. Ideal gift for budding electronics expert!

500-in-1 Electronic Project Lab

Top of the range. Complete self-contained electronics course. Takes you from beginner to 'A' Level standard and beyond! Contains all the hardware and manuals to assemble 500 projects. You get 3 comprehensive course books (total 368 pages) - *Hardware Entry Course*, *Hardware Advanced Course* and a microprocessor based *Software Programming Course*. Each book has individual circuit explanations, schematic and connection diagrams. Suitable for age 12+. Order Code EPL500 - £149.95
Also available - 30-in-1 £15.95, 130-in-1 £37.95 & 300-in-1 £59.95 (details on website)



Tools & Test Equipment

We stock an extensive range of soldering tools, test equipment, power supplies, inverters & much more - please visit website to see our full range of products.

Precision Digital Multimeter (4.5 Digit)



A highly featured, high-precision digital multimeter with a large 4.5 digit LCD display. High accuracy (0.05%). Auto-zeroing, polarity selection and over-range indication. Supplied complete with shrouded test leads, shock-proof rubber holster, built-in probe holder and stand. Supplied fully assembled with holster,

battery and presentation box. Features include:

Capacitance • Audio Frequency • Data Hold • hFE / Diode Test • Auto Power Off

Technical Specifications

DC voltage: 200mV-1000V • AC voltage: 2V-700V • DC current: 2mA-20A • AC current: 20mA-20A • Resistance: 200Ω-200MΩ • Capacitance: 2nF-20μF • Frequency: 20kHz • Max display: 19999


Order Code: MM463 - Was £44.95 **Now on sale at just £29.95!**

See our website for more special offers!



www.QuasarElectronics.com

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads

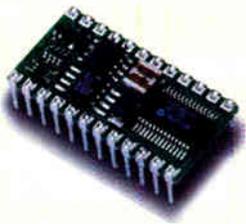

BS2-IC




BS2-SX



BS2E-IC





BS2P/24

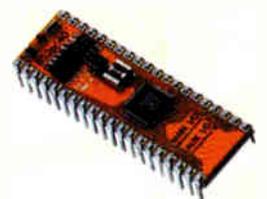

BS2P/40

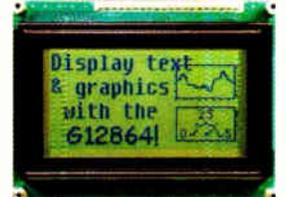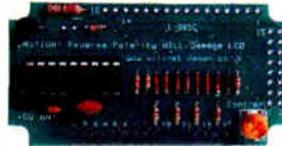Parallax BASIC Stamps - still the easy way to get your project up and running!



**Serial Alphanumeric and Graphic Displays,
Mini-Terminals and Bezel kits**


www.milinst.com




Animated Head



3-Axis Machine

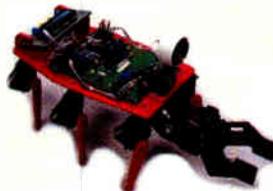

Six-Legged Walkers

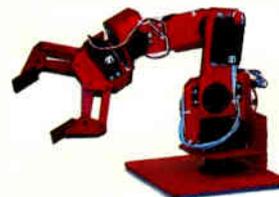


Robotic Arms




Bipeds

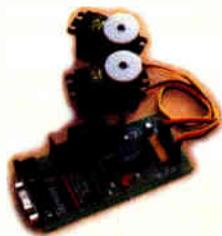Robotic models for both the beginner and the advanced hobbyist



Servo Drivers

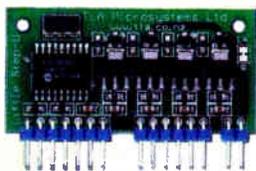

Motor Drivers



On-Screen Displays



DMX Protocol



U/Sound Ranging


Animatronics and Specialist Interface-Control Modules



Quadravox
MP3 & Speech Systems



SensoryInc
Voice Recognition

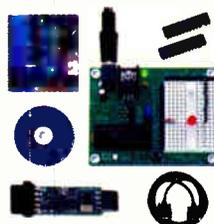

Parallax
Ubicom Tool Kits



Tech-Tools
PIC & Rom Emulators



BASICMicro
PIC BASIC Compilers

Development Tools

Milford Instruments Limited Tel 01977 683665, Fax 01977 681465, sales@milinst.com

EPE PROJECT PICs

Programmed PICs for EPE Projects
 12C508/9-£3.90; 16F627/8 - £4.90
 16F84/71/ - £5.90
 16F876/877/ 18Fxxxx - £10.00
 All inc. VAT and Postage

1kV/500V Insulation Tester



Super design. Regulated output and efficient circuit. Dual scale meter, compact case. Reads up to 200 Megohms. Kit includes wound ferrite transformer, drilled and punched case, meter scale, PCB & ALL components. (Needs PP3 battery).

KIT 848...£32.95

DUAL OUTPUT TENS UNIT

An excellent kit for this project based on the EPE March'97 Design. Our Full Kit includes all components, hardware and an improved Magenta pcb. All hardware and electrodes are included. Designed for simple assembly and testing, providing a high level controlled dual output drive.

KIT 866 .. £32.90
 Inc. 4 electrodes

Set of 4 Spare
 Electrodes £6.50

EPE MICROCHIP P.I. Treasure Hunter

Stable Sensitive Pulse Induction detector. Easy to build and use. No ground effect - works in sea water. Detects Gold Silver, ferrous and non ferrous metals.

KIT 847 ... £63.95

Kit Includes Head-phones, coil and all Hardware

Ultrasonic PEST Scarers

Two Ultrasonic PEST Scarers. Kit 812 produces regular high level pulses of 32kHz. Kit 867 produces Random pulses and can work with an optional slave unit to give two separate ultrasound sources. Both kits need 9V supply.

Kit 812 ... £14.81 psu . 3.99

Kit 867 ... £19.99 867Slave £12.51

MOSFET MKII Bench PSU 0-25V 2.5A

Based on Mk1 design, with switching pre-regulator for high efficiency. Panel meters for A and V. Toroidal transformer. Variable Volts 0 - 25 AND Variable Current limit from 0 - 2.5A

Kit includes punched and labelled case. A classic and essential piece of test gear

Kit 845 ... £64.95



68000 Trainer Kit 621.. 99.95

Stepping & DC Motors

A range of motors for many applications. Visit our website for more details

MD100 100 step Unipolar..... £9.99

MD200 200 step Unipolar..... £12.99

MD24 Type '23' size 200 step...£22.95

MAGENTA BRAINIBOT I & II

- Full kit with ALL hardware and electronics.
- As featured in EPE Feb '03 (KIT 910)
- Seeks light, beeps, and avoids obstacles
- Spins and reverses when 'cornered'
- Uses 8 pin PIC chip
- ALSO KIT 911 - As 910 PLUS programmable from PC serial port leads and software CD included.

BRAINIBOT




KIT910..£16.99

KIT911..£24.99

PIC PIPE DESCALER

- SIMPLE TO BUILD
 - SWEPT FREQUENCY OUTPUT
 - HIGH POWER
 - AUDIO & VISUAL MONITORING
- An affordable circuit which sweeps the incoming water supply with varying frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve the way salts in the water behave.

Kit includes case PCB coupling coil and all components. High coil current ensures maximum effect. LED and piezo monitor.

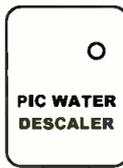

KIT 868 .. £22.95 PSU £3.99

12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMs or other UV erasable windowed devices at a time in 20 minutes. Operates from a 12 Volt supply (400mA). Ideal for mobile work - and in educational applications where mains voltages are to be avoided. Safety interlock prevents contact with UV.

KIT 790 £29.90

PIC LCD DISPLAY DRIVER

- 16 Character x 2 Line display, pcb, programmed PIC16F84, software disk and all components to experiment with standard intelligent alphanumeric displays. Includes full PIC source code which can be changed to match your application.
- Learn how to drive the display and write your own code.
- Ideal development base for meters, calculators, counters, timers --- just waiting for your application
- Top quality display with industry standard driver, data and instructions

KIT 860.£19.99

PIC STEPPING MOTOR DRIVER

PCB with components and PIC16F84 programmed with demonstration software to drive any 4 phase unipolar motor up to 24 Volts at 1 Amp. **Kit includes 100 Step Hybrid Stepping Motor** Full software source code supplied on disc. Use this project to develop your own applications. PCB allows 'simple PIC programmer' 'SEND' software to be used to reprogram chip.

KIT 863.....£18.99

8 CHANNEL DATA LOGGER

From Aug/Sept.'99 EPE. Featuring 8 analogue inputs and serial data transfer to PC. Magenta redesigned PCB - LCD plugs directly onto board. Use as Data Logger or as a test bed for developing other PIC16F877 projects. Kit includes lcd, programmed chip, PCB, Case, all parts and 8 x 256k EEPROMs


KIT 877.....£49.95

SUPER PIC PROGRAMMER

Magenta's original parallel port programmer. Runs with downloaded WINDOWS 95 - XP software. Use standard Microchip .HEX files. Read/Prog/Verify wide range of 18,28, and 40 pin PICs. Including 16F84/876/877, 627/8. (Inc. 'A' versions) + 16xx OTPs.

KIT 862. £29.99 Power Supply £3.99

ICEBREAKER

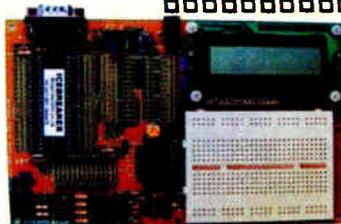

PIC Real Time In-Circuit Emulator

With serial lead & software disk, PCB, Breadboard, PIC16F877, LCD, all components and patch leads.

KIT 900...£34.99
 PSU £3.99

ICEbreaker uses PIC16F877 in-circuit debugger functions.

• Featured in EPE Mar'00
 Ideal for beginners & experienced users. Windows (95 to XP) Software included

20W Stereo Amp.

EPE May '05 -- Magenta Stereo/Mono Module

Wide band Low distortion 11W / channel Stereo
 20W Mono. True (rms) Real Power

Short Circuit & Overheat Protected. Needs 8 to 18V supply.

Latest Technology - Stable, Reliable, high performance IC with local feedback.

KIT 914 £11.90

(includes all parts & heatsink for stereo or mono)



Magenta BrainiBorg



A super walking programmable robot with eyes that sense obstacles and daylight.

BrainiBorg comes with PC software CD (WIN95+ & XP) with illustrated construction details, and can be programmed to walk and respond to light and obstacles on any smooth surface.

Kit includes all hardware, components, & 3 motor/gearboxes. Uses 4 AA batteries (not supplied).

KIT 912 ... £29.99

(Kit with CD Rom & Serial Lead)

KIT 913 ... £38.95

(As 912 but Built & Tested Circuit board)

EPE PIC Toolkit 3

As in EPE Apr/May/Jun '03 and on PIC Resources CD

- Magenta Designed Toolkit 3 board with printed component layout, green solder mask, places for 8,18, 28 (wide and slim), and 40 pin PICs, and many Magenta extras. Also runs with WinPic800 prog. Software.
- 16 x 2 LCD, PIC chip all parts and sockets included.
- Follow John Becker's excellent 'PIC tutorial 2' series.

KIT 880 ... £34.99 (With 16F84 Chip)

KIT 880 ... £39.99 (With 16F877 Chip)

OR - Built & Tested £49.99 & £55.99

EPE TEACH-IN 2004

COMPLETE 12 PART SERIES FROM NOV03 All parts to follow this Educational Electronics Course. Inc. Breadboard, and wire, as listed on p752 Nov 03'
KIT920..£29.99

Additional Parts as listed in 'misc.' Section (less RF modules, Lock, and Motor/g.box)

KIT921.£12.99

Reprints £1.00 per part.

BAT DETECTORS

Magenta's Super Heterodyne Bat detectors. Our best selling kit 861 now includes a drilled case and front panel label. The MkIib and digital MkIII are supplied built & ready to go

KIT 861 .. £37.99

MkIib .. £49.95

Soft Zip Up Pouch for all 3...£5.99

MkIII .. £89.95

All Prices include VAT, Add £3.00 P&P per order, or £7.99 for next day. Chqs. P.O. & Most major cards accepted. See our Website for many more kits, products, & Secure On Line ordering. Mail Order Only.

MAGENTA
 ELECTRONICS LTD
 135 Hunter Street Burton on Trent
 Staffs DE14 2ST UK
 email: sales@magenta2000.co.uk

www.magenta2000.co.uk

Tel: 01283 565435

Fax: 01283 546932

4000 Series	74HC157	£0.22	74LS251	£0.24	OP27CN	£2.33	LM317K	£2.28	Thyristors	BC182B	£0.09	BF337	£0.40	ZTX690B	£0.37
4000B	£0.27	74HC158	£0.23	74LS257	£0.24	OP90GP	£2.91	LM332K	£2.40	2N5600	£0.19	BF422	£0.15	ZTX705	£0.39
4001B	£0.16	74HC161	£0.27	74LS258	£0.24	OP97FP	£1.84	LM334Z	£0.96	2N5611	£0.65	BF423	£0.15	ZTX750	£0.25
4002B	£0.19	74HC162	£0.27	74LS266	£0.24	P113GP	£3.44	LM337T	£5.44	BT151-500R	£0.65	BF459	£0.33	ZTX751	£0.34
4008B	£0.23	74HC163	£0.26	74LS273	£0.32	OP176GP	£2.09	LM338K	£5.31	10A01D	£0.36	BF499	£0.40	ZTX753	£0.40
4009UB	£0.23	74HC164	£0.23	74LS279	£0.24	OP177GP	£2.18	LM338T	£1.10	PO102AA	£0.30	BF529	£0.29	ZTX789A	£0.41
4101B	£0.23	74HC165	£0.21	74LS283	£0.47	OP200GP	£5.60	LM723	£0.40	TIC106E	£0.49	BF824	£0.31	ZTX790A	£0.41
4101B	£0.16	74HC173	£0.38	74LS365	£0.21	OP213FP	£5.20	LP2950CZ5.0	£0.72	TIC116E	£0.66	BF825	£0.33	ZTX851	£0.50
4102B	£0.16	74HC174	£0.27	74LS367	£0.21	OP275GP	£2.57	REF01CP	£2.31	TIC126D	£0.77	BF828	£0.27	ZTX853	£0.50
4103B	£0.18	74HC175	£0.35	74LS368	£0.21	OP282GP	£2.27	REF195CP	£3.04	TL431CP	£1.14	BF850	£0.30	ZTX951	£0.54
4104B	£0.30	74HC193	£0.39	74LS373	£0.39	OP283GP	£5.20	SC3524N	£0.82	BT136-500	£0.58	BFV51	£0.22	ZX1048A	£0.48
4105B	£0.27	74HC195	£0.32	74LS374	£0.38	OP290GP	£4.28	SC3524N	£0.82	BT136-600	£0.50	BFV52	£0.20	ZTX1051A	£0.46
4106B	£0.20	74HC240	£0.32	74LS378	£0.62	OP297GP	£4.64	SC3543	£0.88	BT137-600	£0.58	BS107	£0.15	ZTX1053A	£0.45
4107B	£0.21	74HC241	£0.37	74LS390	£0.34	OP400GP	£11.81	SS12141P	£6.88	IN914	£0.05	BS170	£0.15		
4108B	£0.29	74HC244	£0.40	74LS393	£0.33	OP495GP	£8.69	SSM12142P	£6.16	IN916	£0.04	BS208A	£1.40		
4109B	£0.25	74HC245	£0.34	74LS395	£0.26	RC4136	£1.00	SSM12143P	£3.78	IN4001	£0.20	BS225A	£1.54		
4202B	£0.25	74HC251	£0.25	74 Series				SSM12144P	£3.78	IN4002	£0.20	BU500A	£1.40		
4202B	£0.32	74HC252	£0.25	7407	£0.40			SSM12145P	£3.78	IN4003	£0.20	BU500B	£1.54		
4203B	£0.23	74HC259	£0.29	Linear ICs				SSM12146P	£3.78	IN4004	£0.20	BU500C	£1.40		
4204B	£0.22	74HC273	£0.32	AD524AD	£23.04			SSM12147P	£3.78	IN4005	£0.20	BU500D	£0.98		
4205B	£0.20	74HC299	£0.61	AD548JN	£2.48			SSM12148P	£3.78	IN4006	£0.20	BU500E	£1.06		
4206B	£0.67	74HC365	£0.28	AD590JH	£5.28			TBA120S	£1.04	IN4007	£0.20	BU500F	£1.14		
4207B	£0.21	74HC367	£0.38	AD595AQ	£13.92			TBA120S	£1.04	IN4008	£0.20	BU500G	£0.78		
4208B	£0.21	74HC368	£0.38	AD595AQ	£13.92			TBA810S	£0.75	IN4009	£0.20	BU500H	£0.68		
4209B	£0.38	74HC373	£0.35	AD6205JN	£16.20			TBA820A	£0.53	IN4010	£0.20	BU500I	£0.68		
4303B	£0.17	74HC374	£0.34	AD633JN	£5.92			TDA1170S	£4.80	IN4011	£0.20	BU500J	£0.68		
4303B	£0.31	74HC390	£0.37	AD648JN	£2.57			TDA2004	£2.24	IN4012	£0.20	BU500K	£0.68		
4404B	£0.19	74HC393	£0.36	AD654JN	£5.51			TDA2030AV	£1.24	IN4013	£0.20	BU500L	£0.68		
4404B	£0.31	74HC363	£0.56	AD711JN	£1.97			TDA2050V	£2.51	IN4014	£0.20	BU500M	£0.68		
4404B	£0.19	74HC373	£0.27	AD712JN	£2.51			TDA2611A	£1.88	IN4015	£0.20	BU500N	£0.68		
4404B	£0.35	74HC374	£0.30	AD736JN	£5.80			TDA2824A	£0.79	IN4016	£0.20	BU500P	£0.68		
4407B	£0.25	74HC395	£0.27	AD797AN	£7.25			TDA2653A	£2.99	IN4017	£0.20	BU500Q	£0.68		
4408B	£0.34	74HC597	£0.22	AD811JN	£6.00			TDA2004	£2.24	IN4018	£0.20	BU500R	£0.68		
4409B	£0.29	74HC688	£0.46	AD812AN	£6.32			TDA2004	£2.24	IN4019	£0.20	BU500S	£0.68		
4409UB	£0.17	74HC4002	£0.31	AD820AN	£3.41			TDA2004	£2.24	IN4020	£0.20	BU500T	£0.68		
4500B	£0.20	74HC4017	£0.36	AD822AN	£5.20			TDA2004	£2.24	IN4021	£0.20	BU500U	£0.68		
4501B	£0.23	74HC4020	£0.36	AD829JN	£6.41			TDA2004	£2.24	IN4022	£0.20	BU500V	£0.68		
4502B	£0.32	74HC4040	£0.29	AD830AN	£5.44			TDA2004	£2.24	IN4023	£0.20	BU500W	£0.68		
4503B	£0.22	74HC4049	£0.31	AD847JN	£5.95			TDA2004	£2.24	IN4024	£0.20	BU500X	£0.68		
4504B	£0.56	74HC4051	£0.50	AD9696KN	£7.73			TDA2004	£2.24	IN4025	£0.20	BU500Y	£0.68		
4505B	£0.34	74HC4052	£0.34	ADEL2020A	£5.06			TDA2004	£2.24	IN4026	£0.20	BU500Z	£0.68		
4606B	£0.16	74HC4053	£0.22	ADM222A	£3.55			TDA2004	£2.24	IN4027	£0.20	BU500A	£0.68		
4606B	£0.18	74HC4060	£0.23	ADM222A	£3.55			TDA2004	£2.24	IN4028	£0.20	BU500B	£0.68		
4606B	£0.18	74HC4075	£0.23	ADM485JN	£2.97			TDA2004	£2.24	IN4029	£0.20	BU500C	£0.68		
4606B	£0.20	74HC4076	£0.32	ADM666AN	£2.72			TDA2004	£2.24	IN4030	£0.20	BU500D	£0.68		
4606B	£0.19	74HC4511	£0.64	ADM690AN	£5.13			TDA2004	£2.24	IN4031	£0.20	BU500E	£0.68		
4609UB	£0.18	74HC4514	£0.84	ADM691AN	£6.48			TDA2004	£2.24	IN4032	£0.20	BU500F	£0.68		
4707B	£0.15	74HC4538	£0.41	ADM695AN	£6.48			TDA2004	£2.24	IN4033	£0.20	BU500G	£0.68		
4707B	£0.20	74HC4543	£0.90	ADM699AN	£3.58			TDA2004	£2.24	IN4034	£0.20	BU500H	£0.68		
4707B	£0.18	74LS Series		CA3046	£0.65			TDA2004	£2.24	IN4035	£0.20	BU500I	£0.68		
4707B	£0.17	74LS00	£0.38	CA3130E	£0.87			TDA2004	£2.24	IN4036	£0.20	BU500J	£0.68		
4707B	£0.30	74LS01	£0.14	CA3140E	£0.63			TDA2004	£2.24	IN4037	£0.20	BU500K	£0.68		
4707B	£0.28	74LS02	£0.22	CA3240E	£0.91			TDA2004	£2.24	IN4038	£0.20	BU500L	£0.68		
4707B	£0.30	74LS03	£0.29	DG211CJ	£1.25			TDA2004	£2.24	IN4039	£0.20	BU500M	£0.68		
4707B	£0.30	74LS04	£0.30	DG411DJ	£2.00			TDA2004	£2.24	IN4040	£0.20	BU500N	£0.68		
4801B	£0.21	74LS05	£0.19	ICL7106CPL	£2.06			TDA2004	£2.24	IN4041	£0.20	BU500P	£0.68		
4802B	£0.28	74LS08	£0.14	ICL7107CPL	£2.06			TDA2004	£2.24	IN4042	£0.20	BU500Q	£0.68		
4805B	£0.28	74LS08	£0.19	ICL7109CPL	£5.76			TDA2004	£2.24	IN4043	£0.20	BU500R	£0.68		
4806B	£0.33	74LS09	£0.15	ICL761DCP	£1.00			TDA2004	£2.24	IN4044	£0.20	BU500S	£0.68		
4903B	£0.16	74LS10	£0.27	ICL7621	£0.84			TDA2004	£2.24	IN4045	£0.20	BU500T	£0.68		
4904B	£0.29	74LS11	£0.27	ICL7660SP	£0.80			TDA2004	£2.24	IN4046	£0.20	BU500U	£0.68		
4908B	£0.22	74LS12	£0.33	ICM7555	£0.41			TDA2004	£2.24	IN4047	£0.20	BU500V	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			TDA2004	£2.24	IN4048	£0.20	BU500W	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			TDA2004	£2.24	IN4049	£0.20	BU500X	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			TDA2004	£2.24	IN4050	£0.20	BU500Y	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			TDA2004	£2.24	IN4051	£0.20	BU500Z	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			TDA2004	£2.24	IN4052	£0.20	BU500A	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			TDA2004	£2.24	IN4053	£0.20	BU500B	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			TDA2004	£2.24	IN4054	£0.20	BU500C	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			TDA2004	£2.24	IN4055	£0.20	BU500D	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			TDA2004	£2.24	IN4056	£0.20	BU500E	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			TDA2004	£2.24	IN4057	£0.20	BU500F	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			TDA2004	£2.24	IN4058	£0.20	BU500G	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			TDA2004	£2.24	IN4059	£0.20	BU500H	£0.68		
4909B	£0.35	74LS15	£0.24	ICM7555	£0.41			T							

EPE EVERYDAY PRACTICAL ELECTRONICS

THE UK's No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

VOL. 36 No. 4 APRIL 2007

Editorial Offices:
EVERYDAY PRACTICAL ELECTRONICS EDITORIAL
Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown,
Dorset BH22 9ND
Phone: (01202) 873872. Fax: (01202) 874562.
Email: enquiries@epemag.wimborne.co.uk
Web Site: www.epemag.co.uk
EPE Online (downloadable version of EPE): www.epemag.com
EPE Online Shop: www.epemag.wimborne.co.uk/shopdoor.htm
See notes on **Readers' Technical Enquiries** below – we regret
technical enquiries cannot be answered over the telephone.
Advertisement Offices:
EVERYDAY PRACTICAL ELECTRONICS ADVERTISEMENTS
408 Wimborne Road East, Ferndown, Dorset BH22 9ND
Phone: 01202 873872 Fax: 01202 874562
Email: stewart.kearn@wimborne.co.uk


The Future

Over the last couple of months Barry Fox has reported in *News* on the giant Consumer Electronics Show in Las Vegas. As always, the show is the place where innovative new products are placed in front of consumers. We thought it would be interesting to see where the major companies think we will be in, say five years from now, given that developments in electronics seem to go at an ever increasing pace. Jeffrey Belk, one of the Show's panelists, commented "If we would have predicted five years ago what's available today, they probably would have locked us up in a rubber room." So you can see prediction is not an easy task.

The general view seems to be more connectivity – in other words our TV, DVD, audio, laptop, phone, MP3, camera, GPS etc., will all talk to each other. One wonders how this will sit when bugs and viruses invade the system, or whether the major companies will ever agree on a standard for communication? Maybe all your equipment will have to come from one manufacturer, in which case we don't see that catching on in five years!

In addition to more connectivity, they also predict more availability, where practically every type of information is available, not just when we want it but where we want it. "Someday, (content transfer) may be embedded in the wallpaper" commented Rudy Provoost of Philips Electronics.

When asked what they feel the buying public wants, the consensus was for more reliability, i.e. cellphones that never drop a call and computers that never crash, plus value for money – more performance for fewer pounds – and greater compatibility. "Affordability and ease of use are two of the biggest issues we have" said Rudy Provoost. I'll second that, having spent hours trying to initialise a wireless router only later to be told by the helpline that the set-up instructions were inadequate. And yes I had (eventually) read them all. Let's hope the "affordability and ease of use" issues are soon improved, and that we will get a standard for communication between equipment without a massive 'standards' battle that helps nobody, least of all the consumer.

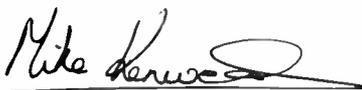

AVAILABILITY

Copies of *EPE* are available on subscription anywhere in the world (see opposite) and from all UK newsagents (distributed by SEYMOUR). *EPE* can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased and downloaded for just \$15.99US (approx £9.00) per year available from www.epemag.com

SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £18.75, 12 months £35.50, two years £66. Overseas: 6 months £21.75 standard air service or £30.75 express airmail, 12 months £41.50 standard air service or £59.50 express airmail, 24 months £78 standard air service or £114 express airmail. To subscribe from the USA or Canada call Express Mag toll free on 1877-363-1310

Online subscriptions, for downloading the magazine via the Internet, \$15.99US (approx £9.00) for one year available from www.epemag.com.

Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subs, Dept., Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Maestro or Visa. (For past issues see the *Back Issues* page.)

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue PVC, printed with the magazine logo in gold on the spine. Price £7.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days, but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Amex, Diners Club, Maestro and MasterCard accepted. Send, fax or phone your card number, card expiry date and card security code (the last 3 digits on or just under the signature strip), with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

Editor: MIKE KENWARD
Consulting Editors: DAVID BARRINGTON
JOHN BECKER
Business Manager: DAVID J. LEAVER
Subscriptions: MARILYN GOLDBERG
General Manager: FAY KEARN
Editorial/Admin: (01202) 873872
Advertising Manager:
STEWART KEARN (01202) 873872
On-line Editor: ALAN WINSTANLEY
EPE Online (Internet version) **Editors:**
CLIVE (MAX) MAXFIELD and ALVIN BROWN

READERS' TECHNICAL ENQUIRIES

E-mail: techdept@epemag.wimborne.co.uk
We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years' old. Letters requiring a personal reply *must* be accompanied by a **stamped self-addressed envelope or a self-addressed envelope and international reply coupons. We are not able to answer technical queries on the phone.**

PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. A number of projects and circuits published in *EPE* employ voltages that can be lethal. **You should not build, test, modify or renovate any item of mains-powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.**

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers. We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

Although the proprietors and staff of *EVERYDAY PRACTICAL ELECTRONICS* take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment, as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.



More at CES 2007

Barry Fox reports on a couple more items he found at this year's
CES Show at Las Vegas

Dolby Volume

The most common complaint made to broadcasters by listeners and viewers is that the commercials are too loud, or some stations are too quiet to hear, or movies create impact by suddenly blasting high volume sound effects and annoy neighbours, especially late at night. Dolby Labs has already tried to help the industry help itself, by offering graduated sound level meters and advice on how to use them. But largely to no avail, so Dolby has developed a new consumer system called Dolby Volume.

After measuring countless broadcasts, Dolby found that sound levels can vary by as much as 30dB when the viewer switches channels or is hit by an advert. Psycho-acoustically, 10dB is a doubling of perceived volume, so a 30dB difference is an ear-bending eightfold change. Moreover, because the ear is non-linear, as the sound level drops, the bass and treble drop by a disproportionate amount.

Dolby Volume is a psychoacoustic algorithm that will work inside a TV receiver to even out the overall volume level, and compensate for the non-linear effects. The trick, says Brett Crockett, of Dolby's Research Lab in San Francisco, is to make the system track the audio in real time, and apply intelligent compensation so quickly that the listener does not notice. A conventional 'dumb' compressor or automatic gain control makes background noise pump and breathe as the level of speech or music fluctuates.

Dolby Volume works in the digital domain, and can handle any input, up to 24-bit, 96kHz and even beyond. After a one-time calibration set up, when the listener enters personal listening preferences, the system continually buffers and 'listens' to around 200 PCM samples of the sound, while adjusting the output level to suit the listener and compensating for perceptual loss of high and low frequencies at low listening levels. This process adds a delay of only 16ms, which set-makers can trade off against the much longer video processing delays in digital TVs.

The system can be used to balance the different sound levels that an AV amplifier gets from all its many sources, such as radio, TV, DVD, BD, HD-DVD and iPod. Dolby Volume can also be adapted for use in cars, with a microphone measuring background noise and adjusting the Dolby Volume to match.

If Dolby's offer to the electronics industry is taken up, future TV sets and amplifiers will have a Dolby Volume control. The computer code, on which the system relies, will be released to the industry during the next few months. Using the same business model as for other Dolby processing systems, chip-makers will be able to develop and sell chips without paying a royalty. Set makers will then pay a royalty to Dolby when they enable the Volume system. Dolby expects to see the first working sets at CES next year.

"This follows on from all the work we did on analogue noise reduction" says Crockett. "We don't spend time looking for

music and speech that makes a system sound good, we spend time looking for material that makes it sound bad. We try to break the system before announcing it".

But if anyone does not like the results, they can disable Dolby Volume and make their volume control work just like it always did. Judging by the press reaction to very impressive demonstrations given in Las Vegas, it is very unlikely many will use the Off switch.

Will broadcasters object? "Currently some of them are annoying listeners to the point of completely skipping or muting adverts" says Crockett. "With Dolby Volume people continue to listen".

5.1 Video

Is 5.1 video the next step after 5.1 surround sound? Panasonic's booth at CES sported a small room with one of the most adventurous demonstrations of the show – the 5.1 Vision Jazz Club.

The room had five plasma panels, a 103-inch (261.6cm) display at the front and two 65-inch (165cm) panels at each side of the room, positioned vertically like information panels at an airport. But instead of displaying information, all five panels picture one member of a five-piece jazz group recorded by respected music producer Elliot Sheiner. The front panel shows the pianist, the left side panels show the bass player and guitarist, and the two right side panels show the sax player and drummer.

The 5.1 sound matches the video location so the viewer is quite literally in the middle of the band.

Radio-Electronics.Com Tutorials

The website Radio-Electronics.Com (www.radio-electronics.com) that provides free radio and electronics related information, tutorials and articles, now has more than 400 pages of tutorial content. The site, which is aimed at electronics engineers and students, is run and edited by Ian Poole of Adrio Communications Ltd, and aims to provide concise, useful overviews and tutorials in an easy to read form.

The website covers a wide range of radio and electronics topics, ranging from receiver technology, through antennas, radio propagation, circuits, components, test and measurement to the other technologies including cellular

telecommunications, Wi-Fi, Bluetooth, UWB and more. This makes the site a one-stop-shop for information for the electronics engineer and electronics enthusiast. All of the articles and tutorials aim to be written in an easy to read style, making them approachable for most people.

The site prides itself on keeping up with the latest technology and to prove this there are summaries of Wibree (the new low power wireless standard from Nokia) along with summaries of HSDPA and HSUPA being introduced on many cellular networks. With new pages being added all the time, many more new technologies will shortly be covered.

In passing the 400 landmark, the Editor, Ian Poole commented, "Having more than 400 tutorial pages on the site makes Radio-Electronics.Com one of the largest electronics information resources on the Internet. However, we are not going to stop there. Not only will we be putting more tutorial and reference information on the site, but we have more plans to broaden its appeal, and we will be adding some new areas – so keep an eye out on what is happening."


The site has been in existence for over six years and, since its inception, it has grown steadily in size and the number of visitors. It also regularly receives very positive comments from readers who have found it useful in providing the information they need.

EasyDAQ USB Card

EasyDAQ has announced the launch of a new low cost USB card, adding to its existing range of USB-powered data acquisition and automation/control products. The new USB8VI4DIOR card is available as a general purpose, 8-channel voltage input, 4-channel DIO and 4-channel relay card. Voltage input and DIO/Relay channels are opto-isolated.

Available with a choice of two relay types (10A power or 1A gold contact signal), and either fixed or two-part (male/female) screw terminal connectors. The card is suitable for a wide range of voltage measurement, contact closure applications, signal switching or control, mains voltage power switching purposes etc. It is USB powered and hot swappable, with voltage input, relay channel and USB power status indication LEDs. It is also available with LabView, Visual Basic, Visual C, Agilent VEE and Delphi example programs, or it can be commanded via programs such as Windows HyperTerminal.

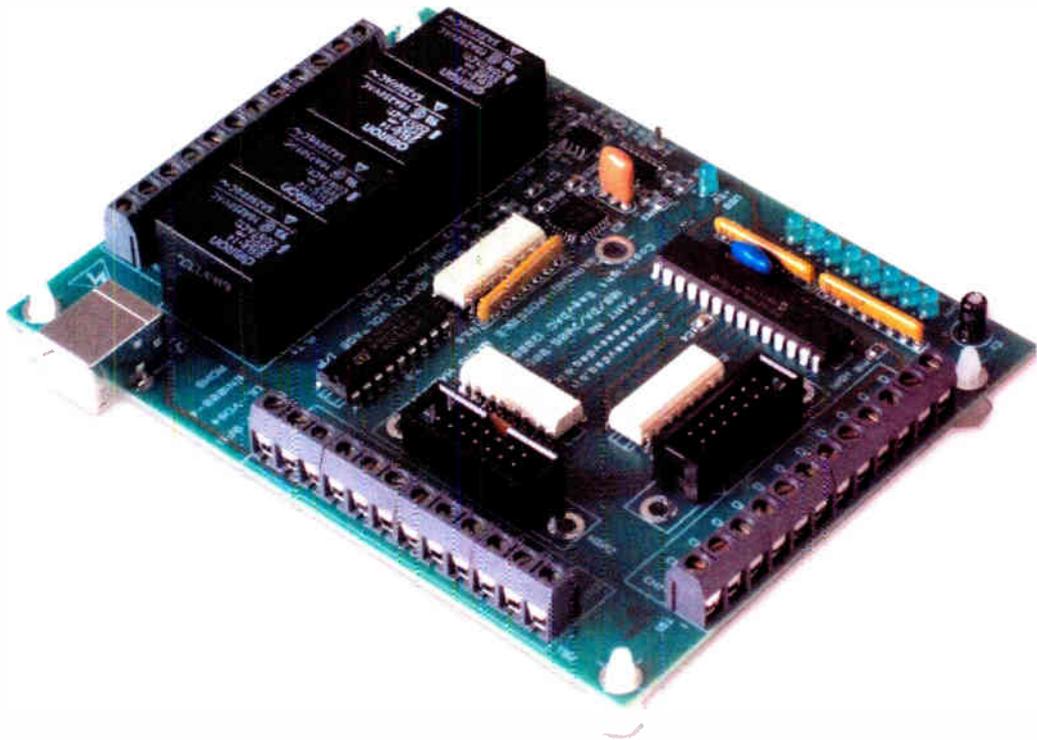For more details and full datasheet, contact EasyDAQ, 14 Brook Lane, Corfe Mullen, Wimborne, Dorset, BH21 3RD. Tel: 01202 600747. Email: info@easydaq.biz. Web: www.easydaq.biz.



Microchip Real ICE Emulator

Microchip have announced the MPLAB REAL ICE Emulation system. This offers low-cost and faster memory interfacing.

The new emulation system is fully integrated into the free MPLAB Integrated Development Environment (IDE) used for writing code, building projects, testing, verification and programming. With MPLAB, the new system supports a wide range of debugging facilities, such as complex breakpoints, application code tracing and data logging, code execution stop-watch and real-time variable monitoring.

For further information browse www.microchip.com.

BLETCHLEY £10 SEASON TICKET

Bletchley Park, the historic site of secret British code breaking activities during World War II and the birthplace of the modern computer, is launching a brand new Season Ticket initiative that will be of particular benefit to people visiting the area on an overnight break, as well as those who live up to at least two hour's drive from the Park.

Since January 2007, all visitors have the opportunity to convert their one-day £10 adult entry ticket into a 12-month season ticket, which will then allow them to have unlimited and free visits to the Park following their first visit. Visitors will also be given the chance to sign a Gift Aid declaration form enabling Bletchley Park, as a charitable organisation, to recoup around 28 per cent of the ticket value. This will then be ploughed back into the much needed restoration and upkeep of the Park and its facilities.

"Figures show that a large percentage of our visitors have travelled from a wide range of locations throughout the UK, up to at least two hour's drive," says Simon Greenish, director, Bletchley Park. "Once

they get here, most admit that there is too much to see in just one day, from our popular guided tours and the Mansion, to Colossus, the Bombe and, of course, Enigma and our various other wartime codebreaking machines.

But with our new 12-month season ticket, visitors will be able to make the journey to Bletchley Park as often as they like and not pay a penny more for the rest of the year, whether they are coming back to see our permanent collections, or for one of our special events, such as the Churchill weekend."

Once again, Bletchley Park has an exciting new programme of special events in 2007, commencing on 9 April with an Easter Eggstravaganza for the kids and a Forties Family Festival on 28 May. Other major events this year include the inauguration of Alan Turing's Hut 8, the launch of Colossus and the Eombe, a Polish Day, Classic Car and Motorbike Picnic, Alice in Wonderland event, Churchill Weekend and Enigma Festival, as well as the annual Blitz Night in November.

Season ticket holders will be eligible to attend most special events for no extra charge. Around Easter the Park will also be launching a brand new restaurant, which will be returning to Hut 4, home of the Naval Enigma.

For further information call 01908 640404 or email info@bletchleypark.org.uk. To purchase tickets in advance through their secure website, go to www.bletchleypark.org.uk/shop/.

The standard cost of admission is adults £10, concessions £8 (OAPs and students with valid ID card) and £6 (children aged 12 to 16), children under 12 admitted free of charge. Family Ticket: £25 (two adults and two children aged 12 to 16). Tickets include a guided tour and/or the use of a wand. Car parking is £3.

Bletchley Park is open during 2007 every day except Christmas Day and New Years

Day. Weekdays: 10.30am – 4.00pm, last admissions 2.30pm. From 26th March: 9.30am – 5.00pm, last admissions 3.30pm. Weekends/public holidays: 10.30am – 4.00pm, last admissions 2.30pm.

EDUCATIONAL WEATHER KITS

Quasar Electronics have introduced a new range of educational weather station kits.


The Weather Observatory Starter Kit encourages young children (8+ years) to learn and understand the science behind different weather conditions. It provides a good range of meteorological measurements and is ideal for use in Primary Schools and at home.

Through it, children can perform measurement of temperature, wind direction and rainfall, learn about pH, humidity, air pressure and many more meteorological subjects. It is supplied with an informative activity handbook and costs £9.95 including VAT. For full details see www.quasarelectronics.com/met128.htm.

The Digital Weather Station Kit is a unique kit that will provide hours of enjoyment while learning and understanding the science behind diverse weather conditions. Quasar say it is a must for Primary Schools and for children at home from the age of 10+.

It provides a high precision digital wind speed meter with temperature, relative humidity, wind direction and rainfall measurement. It also helps with understanding pH, pollution, the greenhouse effect, clouds and lightning. Supplied with a colour, easy-to-follow, informative activities handbook, it costs £32.95 including VAT. Full details are at www.quasarelectronics.com/met131.htm.

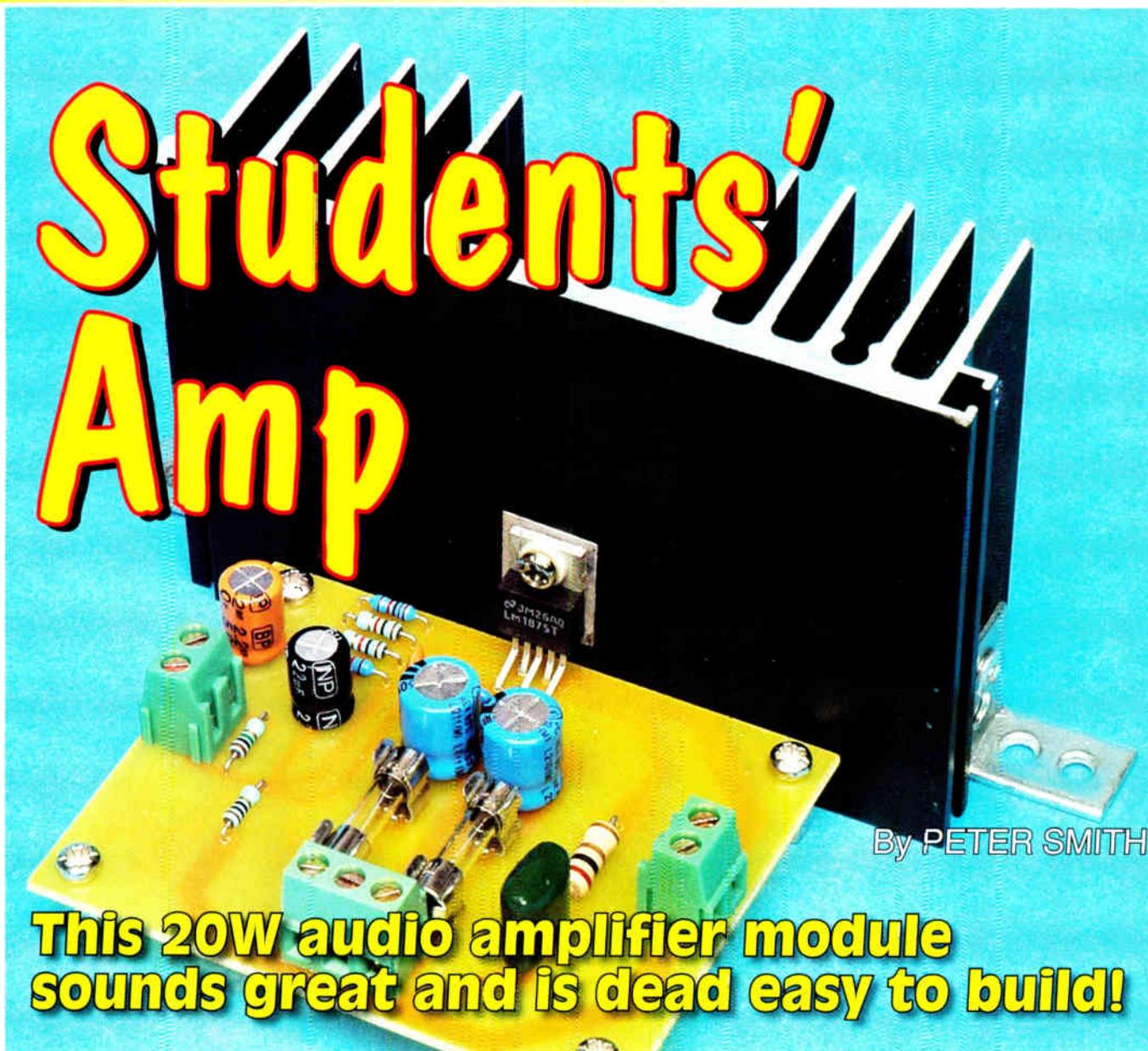Quasar's full range of science kits can be found at www.quasarelectronics.com/science_kits.htm.



BUILDING AN AUDIO amplifier is a popular choice when it comes to the hands-on part of electronics courses. We can well imagine the classroom question “Well, does it work?” answered in a flash with “Listen to this, disbeliever!”

That’s the best part of building an audio amp; you and your peers actually get to hear the final work punch out a favourite tune or two hundred!

However, amplifiers that produce more than a few watts of power can be difficult to construct and expensive. This is where our Students’ Amp comes in. It features a simple board layout for easy construction, is relatively inexpensive and even includes over-temperature and short-circuit protection.

As power amplifier modules go, this unit may not rank at the top for

raw power but you’ll be hard pressed to find a simpler circuit. The design is based on a single IC, the LM1875T 20W audio amplifier from National Semiconductor. This IC comes in a TO-220 package and, combined with a handful of other parts and a suitable power supply, delivers over 20W RMS into either a 4Ω or 8Ω loudspeaker.

What’s more, the specifications are quite impressive for such a bare-bones circuit. With a signal-to-noise (S/N) ratio of 105dB and a distortion figure of less than 0.04% for 1kHz at 20W (see graphs – Figs.7 to 11), it could well be used as the basis for a hifi stereo amplifier. The frequency response extends from 14Hz to beyond 100kHz when measured at 1W RMS.

The LM1875 includes an internal 4A current limit, preventing damage

should the output be accidentally shorted to ground. It also includes ‘safe operating area’ (SOA) protection, meaning that the current limit is dynamically reduced according to the voltage present at the output.

Because so much power has to be dissipated by such a small package, the LM1875 also has in-built thermal protection. This effectively shuts the device down if there is excess heat build up in the chip itself (at about 170°C).

Circuit description

The circuit diagram (see Fig.1) for the amplifier module reveals just the LM1875 power amplifier (IC1) and a handful of support components.

The closed loop gain of the amplifier is set to 23 by the 22kΩ and 1kΩ resistors on the inverting input (pin 2),

following the standard non-inverting amplifier feedback rules (ie, voltage gain = $22k/1k + 1 = 23$).


The $22\mu\text{F}$ capacitor in series with the $1k\Omega$ resistor sets the lower end of the amplifier's frequency response. Another factor in the low-end response is the high-pass filter in the input signal path, formed by the $2.2\mu\text{F}$ coupling capacitor and $22k\Omega$ resistor.

Overall, the result is a rapid frequency response roll-off below about 10Hz (see Fig.11). Following this, a $1k\Omega$ series resistor and a 330pF capacitor form a low-pass filter, eliminating problems with high-frequency noise pickup on the input leads.

Non-polarised electrolytic capacitors (marked NP) are used in these positions because the voltages present are too small to polarise conventional electrolytics.

Keen-eyed readers will have detected that the input circuitry is not connected directly to power supply ground but instead goes via a 10Ω resistor. This has little effect in a single (mono) amplifier setup but in a stereo setup, it helps to reduce currents circulating in the ground wiring which can degrade separation between channels.

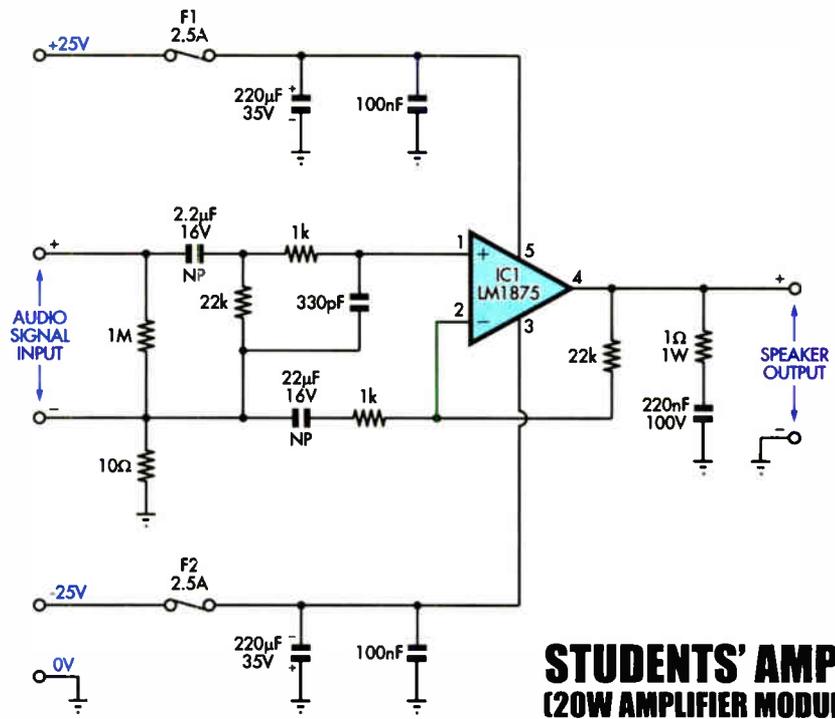Finally, a 1Ω 1W resistor in series with a 220nF capacitor at the output of IC1 forms a Zobel network, designed to neutralise the effects of the speaker's voice coil inductance at the higher end of the frequency spectrum.



STUDENTS' AMP (20W AMPLIFIER MODULE)


Fig.1: the circuit consists of little more than the LM1875, which contains a complete low-distortion 20W amplifier, with overload protection, in a 5-pin TO-220 package.

Amplifier construction

Construction of the amplifier module is quite straightforward, with all parts mounting on a small PC board. Fig.2 shows the parts layout.

The resistors should be installed first, followed by the capacitors. Use

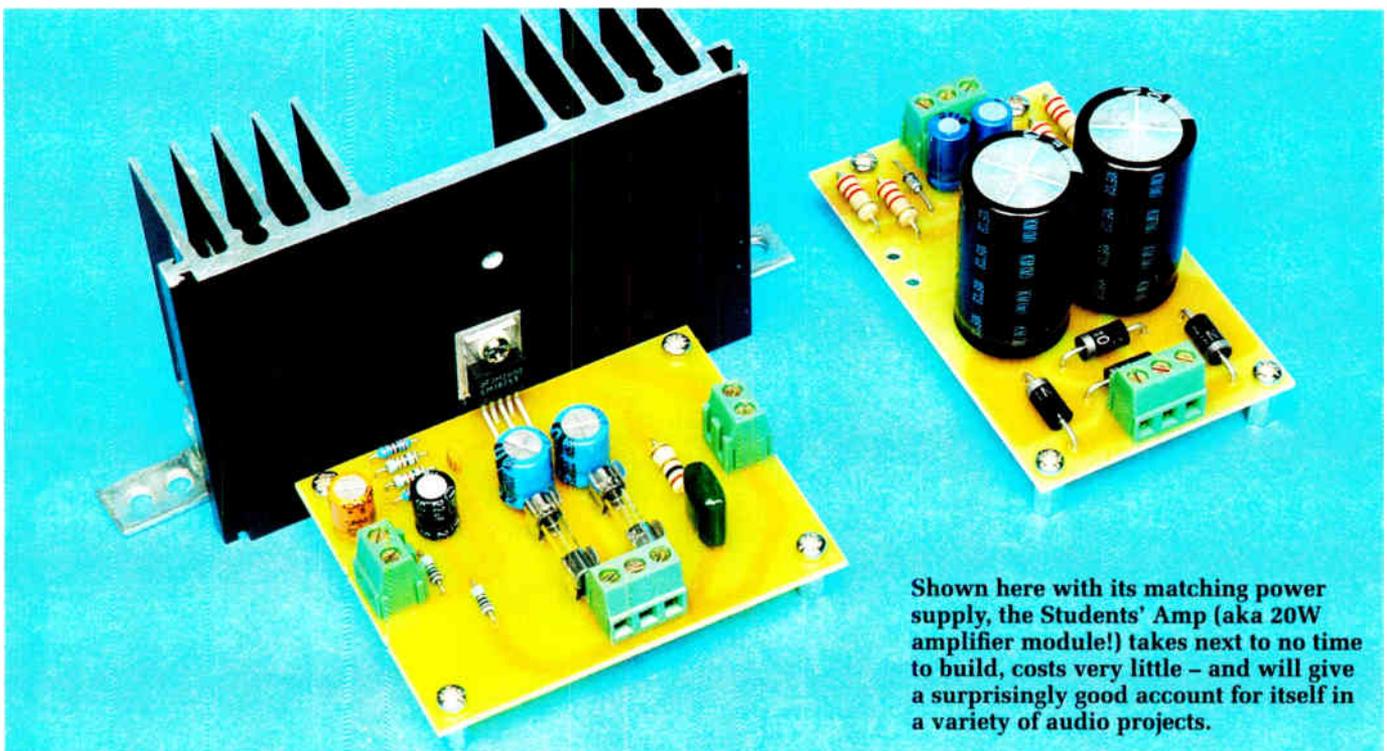your meter to verify the value of resistors where necessary. Note that the two $220\mu\text{F}$ capacitors are polarised and must go in with their positive leads oriented as indicated on the component overlay. The remaining two electrolytic capacitors are



Shown here with its matching power supply, the Students' Amp (aka 20W amplifier module!) takes next to no time to build, costs very little – and will give a surprisingly good account for itself in a variety of audio projects.

Constructional Project

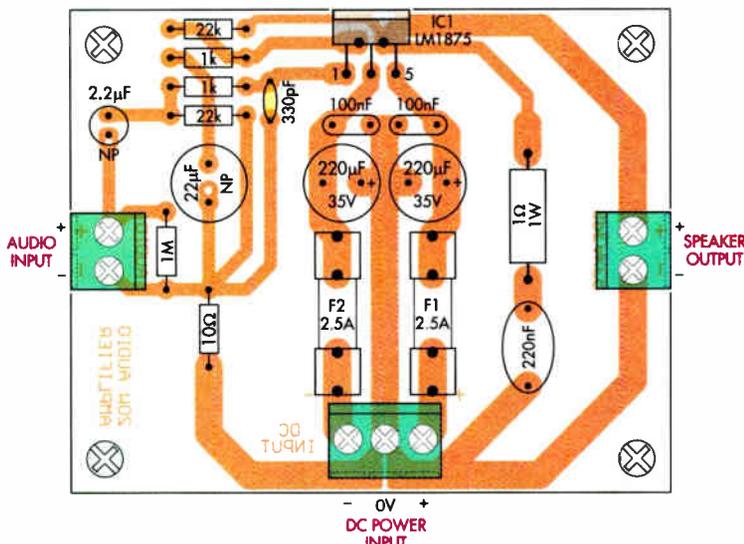


Fig.2: use this diagram when assembling the amp module. Double-check that you have the two 220µF capacitors in the right way around, as indicated by the '+' markings.

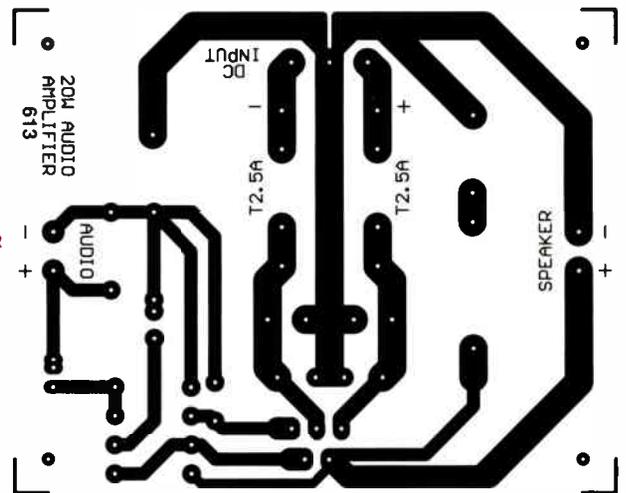


Fig.3: full size PC board pattern for the amplifier. If you're wondering why this looks different to the overlay pattern at left, this view is from the copper side while the overlay is 'through the board' as if an x-ray.

non-polarised and can be installed either way around.

Install the fuse clips and terminal blocks next, pushing them all the way down onto the board surface before soldering. Note the retaining tabs on the fuse clips; be sure to orient these towards the outer (fuse end) side, otherwise you won't be able to plug in the fuses later.

The LM1875 is installed last of all. First, fit 10mm tapped spacers to the corner mounting positions of the board, then slip the LM1875 into position. As its leads are preformed at the factory, they shouldn't require more than minor tweaking for a comfortable fit in the PC board holes.

Make sure that the LM1875 is sitting 'square' (ie, perpendicular to the board surface) and then carefully turn the assembly over and solder only the centre pin of the package. The remaining four pins should only be soldered after attachment to the heatsink, so let's do that next.

Heatsink mounting

Place the board and heatsink on a flat surface and bring them together, centring the LM1875 in the available heatsink width. Dependent on the particular type of heatsink, it may also be necessary to line up the hole in the tab with a gap between

fins. Now gently mark around the inside of the tab hole with a sharp pencil.

Centre-punch the pencilled circle and first drill a 1mm pilot hole, then step up to a 3mm (or 1/8-inch) bit for the final size.


Once drilled, the edges of the hole must be deburred to obtain a perfectly smooth surface. This can be achieved by gently rotating the tip of a much larger drill in the hole opening by hand, held between the thumb and forefinger.

The LM1875 can now be bolted to the heatsink using a TO-220 insulating kit (ie, a mica washer and insulating bush). Fig.12 shows the assembly details. Smear all mating surfaces with a thin film of heatsink compound before bolting the assembly together. Take care not to 'skew' the LM1875 as the screw is tightened.

To complete your work, you must now solder the remaining leads of the LM1875. Gingerly turn the whole assembly over, being careful not to disturb the relationship between the PC board and heatsink.

Place something under the board to support its weight and keep it at right angles to the heatsink while you solder the remaining leads. It's also a good idea to reheat and resolder the centre pin of the IC to relieve any stresses imposed during assembly.

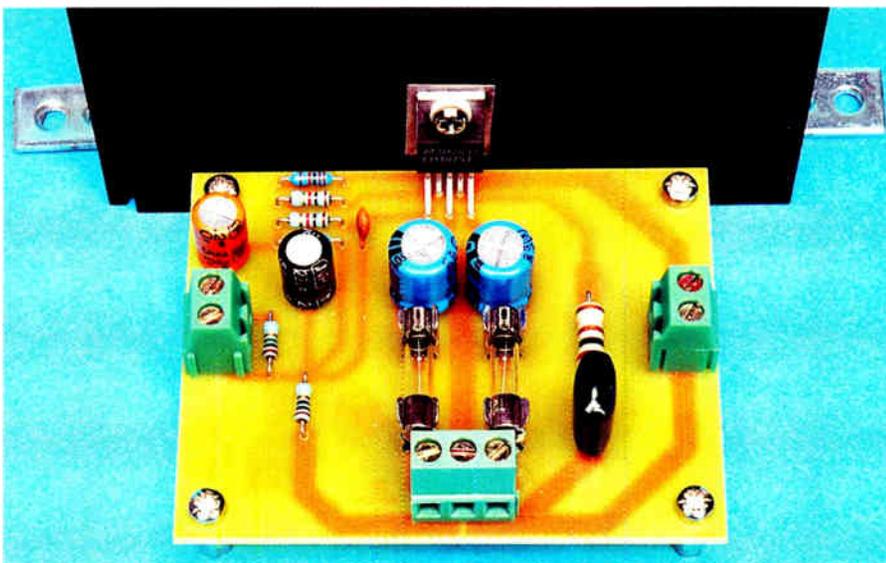Once done, use your multimeter to confirm that the metal tab of the LM1875 is indeed electrically isolated from the heatsink.



The completed amplifier module is bolted to its heatsink via the LM1875. Take particular care once the amplifier is in this state – it's quite easy to break the legs of the IC if you allow the board to flex with reference to the heatsink.

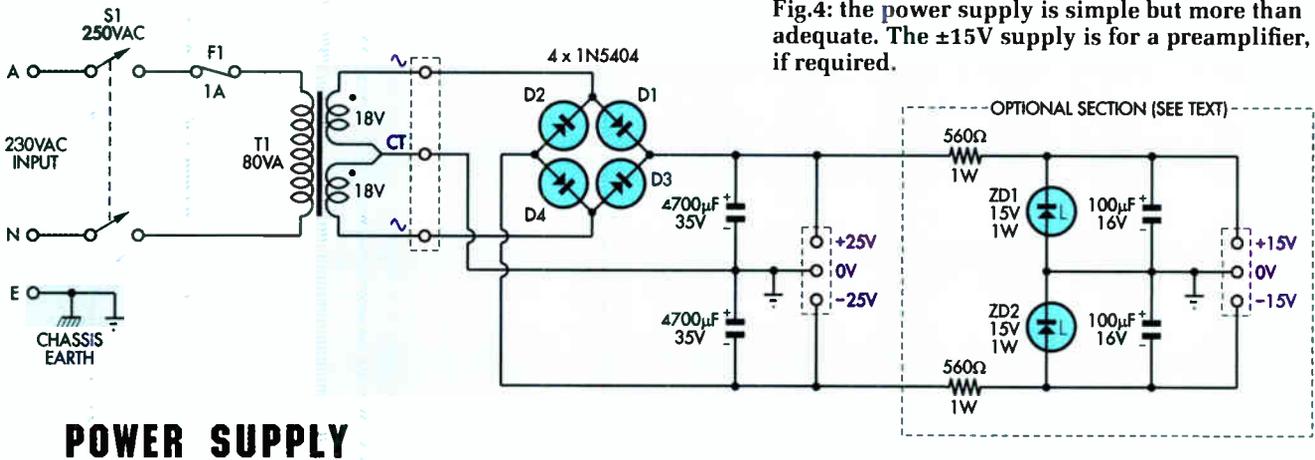


Fig.4: the power supply is simple but more than adequate. The $\pm 15\text{V}$ supply is for a preamplifier, if required.

POWER SUPPLY

Power supply

The power supply circuit for the amplifier module appears in Fig.4. An 80VA mains transformer with two 18V secondary windings or a single 36V centre-tapped winding is used. The secondary feeds a bridge rectifier and filter, formed by diodes D1-D4 and two 4700 μF 35V capacitors. The output is about $\pm 25\text{V}$ unloaded and is suitable for powering one or two amplifier modules.

If designing your own power supply, note that the rails to the LM1875 **must not** exceed $\pm 30\text{V}$. Voltages lower than the recommended $\pm 25\text{V}$ can be used, but the output power will be less than shown in the performance graphs. Refer to the LM1875 datasheet for more information (from www.national.com).

The circuit also shows a $\pm 15\text{V}$ preamplifier supply, based on two simple Zener diode regulators. This supply is optional and can be left out if not required.

Power supply assembly

Fig.5 shows how to assemble the power supply PC board to suit the Students' Amp. Note that the 4700 μF capacitors are 35V rated but higher voltage types are fine too.

Install diodes D1 to D4 first, aligning the banded (cathode) ends as shown. Follow these with the two 3-way terminal blocks and then the two 4700 μF capacitors. Make certain that you have the positive leads of the capacitors the right way around.

You can leave out all the remaining components unless you

specifically require the $\pm 15\text{V}$ supply for a preamplifier.

Wiring

Use heavy-duty (7.5A) multistrand cable for all DC power and speaker connections. The +25V, -25V and 0V wires to the amplifier module should also be twisted together to minimise radiated noise.

Now on the mains (230V AC) side, be sure to use only mains-rated (250V AC) cable and insulate all exposed connections. This includes the use

of rubber boots or heatshrink tubing on the rear of IEC sockets, switches and fuseholders. The idea is to ensure that even with the covers off and power on, it is impossible to accidentally make contact with live mains voltages.

The mains earth must be connected to a metal chassis using the arrangement shown in Fig.13. Return all earth wires to this point to eliminate potential earth loops.

When in any doubt, refer your work to an experienced person for checkout

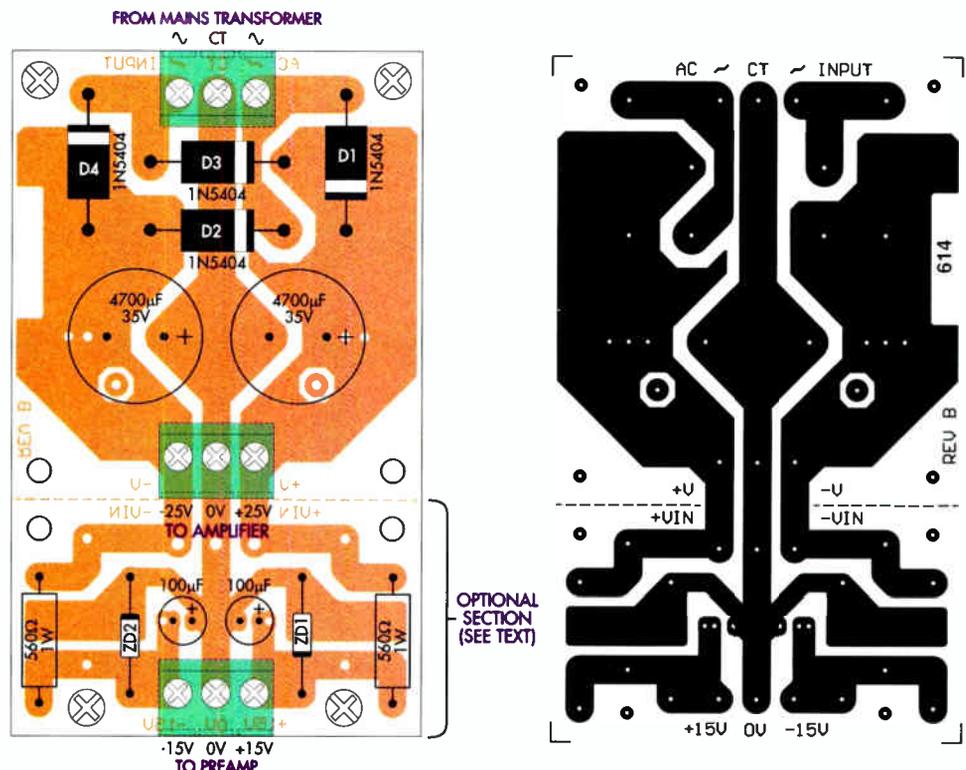


Fig.5: here's how to assemble the power supply board. One of these can power two modules for a stereo set-up. The full size pattern is shown at right (Fig.6).

Constructional Project

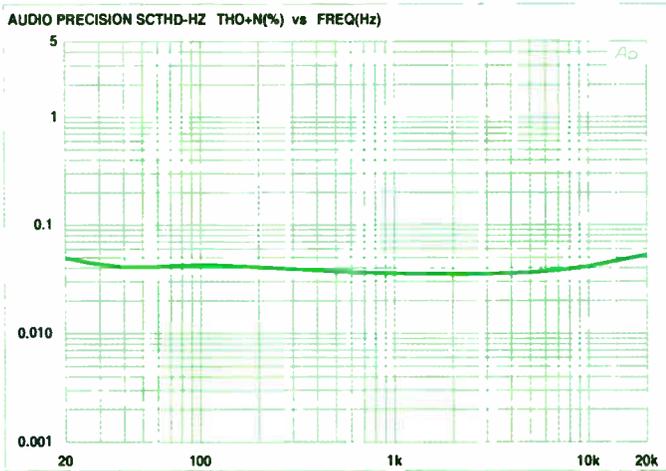


Fig.7: THD versus frequency at 1W into an 8Ω load.

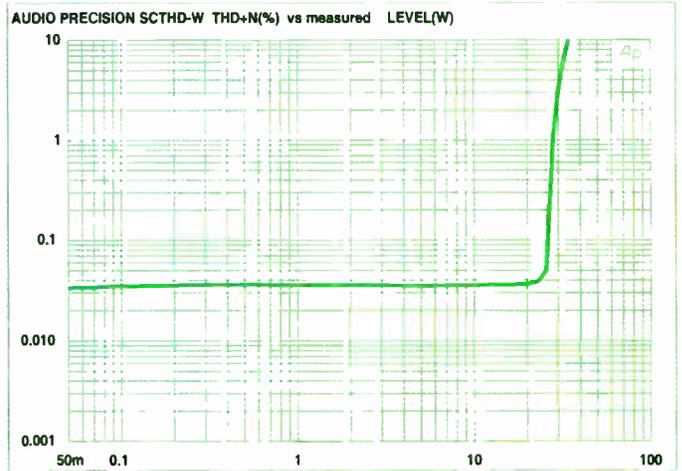


Fig.10: THD versus power at 1kHz into an 8Ω load.

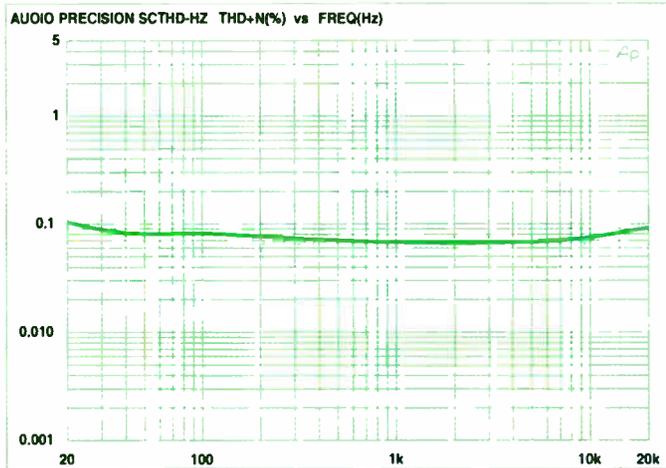


Fig.8: THD versus frequency at 1W into a 4Ω load.

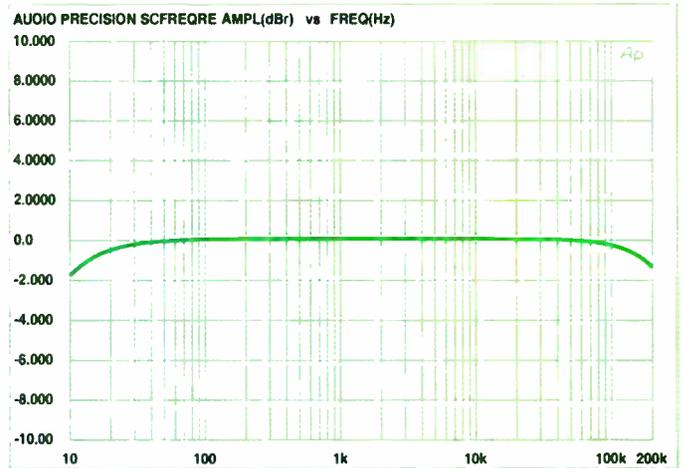


Fig.11: frequency response at 1W into an 8Ω load.

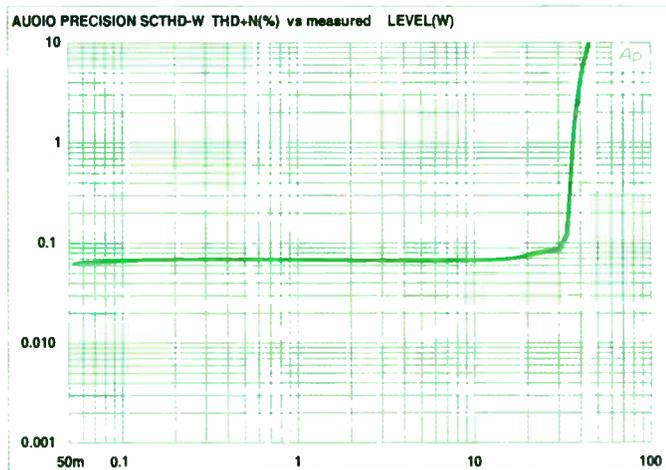


Fig.9: THD versus power at 1kHz into a 4Ω load

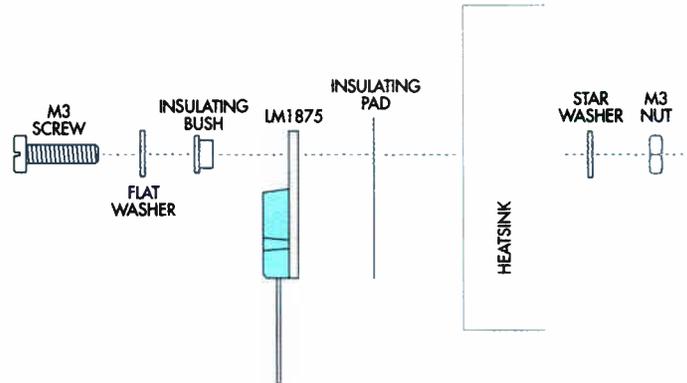



Fig.12: this diagram shows how the LM1875 is attached to its heatsink.

before connecting to the 230V AC mains outlet for the first time. **Never take shortcuts with mains wiring – it could be fatal!**

Testing

Before applying power, go back over the board and carefully check

Fig.13: the mains earth must be securely attached to a metal chassis as shown here. Tighten the first nut very firmly before winding on the second 'lock-nut'. The power supply ground (0V) must also be connected to this point.

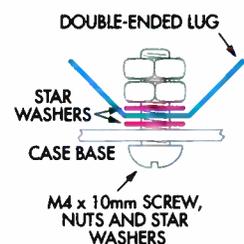

Parts List – Students' 20W Amplifier Module

Amp Module

- 1 PC board, coded 613, available from the *EPE PCB Service*, size 80mm x 63.5mm
- 2 2-way 5mm/5.08mm terminal blocks
- 1 3-way 5mm/5.08mm terminal block
- 4 M205 PC-mount fuse clips
- 2 M205 2.5A slow-blow fuses
- 1 1.4°C/W heatsink
- 1 TO-220 insulation kit (bush, insulating washer) & heatsink compound
- 4 M3 x 10mm tapped spacers
- 4 M3 x 6mm pan head screws
- 1 M3 x 10mm pan head screw
- 5 M3 nuts
- 1 M3 flat washer

Semiconductors

- 1 LM1875T 20W audio amplifier (IC1)

Capacitors

- 2 220µF 35V PC electrolytic
- 1 22µF 16V non-polarised (bipolar) PC electrolytic
- 1 2.2µF 16V non-polarised (bipolar) PC electrolytic
- 1 220nF 100V metallised polyester

- 2 100nF 50V monolithic ceramic
- 1 330pF 50V ceramic disc

Resistors (0.25W 1%)

- 1 1MΩ 2 22kΩ 2 1kΩ
- 1 10Ω 1 1Ω 1W 5%


Power Supply

- 1 PC board, coded 614, available from the *EPE PCB Service*, size 90mm x 54.5mm
- 4 1N5404 3A power diodes (D1-D4)
- 2 4700µF 35V (or 50V) PC electrolytic capacitors
- 1 18V+18V 80VA mains transformer
- 2 3-way 5mm/5.08mm terminal blocks
- 4 M3 x 10mm tapped spacers
- 4 M3 x 6mm pan head screws

M4 x 10mm screw, two nuts and star washers, and a double-ended solder lug for securing the metal chassis earthing point

Parts for optional preamp supply section

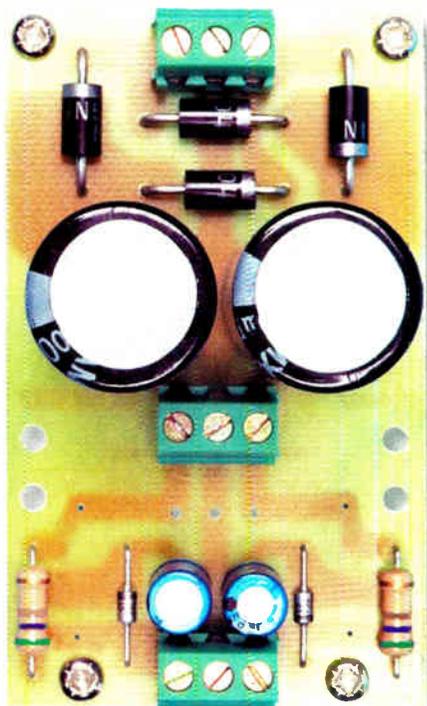- 2 15V 1W Zener diodes (ZD1,ZD2)
- 2 100µF 16V PC electrolytic capacitors
- 2 560Ω 1W 5% resistors
- 1 3-way 5mm/5.08mm terminal block



This view shows the completed power supply for the amplifier. The components at the bottom are for the optional $\pm 15V$ preamp power supply and may be left out if not required.

that all parts are correctly located and oriented. That done, install the fuses and connect the power supply leads, taking particular care that you have the positive and negative leads around the right way!

Do not connect the loudspeaker or an audio input signal at this stage.

Note that you must have the heat-sink fitted, as the LM1875 has to dissipate substantial power even without an audio signal present.

Check the supply rail voltages first – these must be within 10% of the nominal value. Finally, check the DC voltage across the loudspeaker terminals. It should be less than $\pm 50mV$.

If this checks out, the loudspeaker can be connected (switch off first) and an audio input signal applied for final testing.

EPE

Reproduced by arrangement with SILICON CHIP magazine 2007.
www.siliconchip.com.au

ANDRE LAMOTHE'S

XGAMESTATION

LEARN STEP-BY-STEP HOW TO DESIGN AND BUILD YOUR OWN VIDEO GAME CONSOLE!

Design inspired by the Atari 800/2600, Sinclair ZX Spectrum, Apple II & Commodore 64!



Complete Package



eBook



Integrated IDE



FEATURES:

- Great for Hobbyists AND Students!
- Complete Software Development Kit!
- eBook on Designing the XGS Console!
- Parallax SX-Key Compatible!
- Fully Assembled XGS Micro Edition Unit!
- The Fun Way to Learn Embedded Systems!

PAL & NTSC COMPATIBLE!



WWW.XGAMESTATION.COM

SUPPORT@NURVE.NET PH: 925.736.2098(USA)



Get your magazine 'instantly' anywhere in the world – buy and download from the web. A one year subscription (12 issues) costs just \$15.99 (US) www.epemag.com

TAKE A LOOK, A FREE ISSUE IS AVAILABLE

All Change

Automotive electronics looks set to change gear, as Mark Nelson reports

FEW of the technologies in daily use change dramatically, although you might say the transition to digital photography from analogue film was pretty fundamental. More often it's evolution rather than revolution, as with cars. But automotive electronics looks shortly set to change gear quite significantly.

Ask most car enthusiasts what's going on in their world from a technology perspective and they'll probably mention the dash for diesel or perhaps a move to bio-fuels. We certainly need to make our cars more economical; currently only some 40 percent of British cars run on diesel although across the Channel in France the figure is closer to 70 percent. We also need to make our cars more economically; more than 90 percent of the energy consumed by a car goes up in smoke during the manufacturing process itself, which is why scrapping still viable cars to buy less thirsty new ones doesn't make a huge lot of sense.

ADAS unveiled

Crucial as fuel systems and energy efficiency are, let's leave them for a moment and consider how we can make drivers more efficient and effective. They have an equal role to play.

The buzzword today is Advanced Driver Assistance Systems – ADAS for short – electronic systems designed to help the driver in his or her process of driving. The German multinational company Siemens explains the need and advantages of ADAS like this. Complex traffic situations with increasing numbers of traffic participants always demand full attention. Intelligently linked comfort and safety systems support the driver and convey a more confident driving experience.

This is a diplomatic and very positive description of the benefits of ADAS but others put it more bluntly, that ADAS may be the only way to reduce the carnage on the roads. Road accidents are a frighteningly prolific cause of death according to the World Health Organization, racing from ninth most common reason worldwide in 1990 to third place in 2010.

Automobile manufacturers, equipment suppliers, governments and academics are in broad agreement that ADAS technologies represent our best hope of automotive accident avoidance (the positive spin) or reducing the severity and lethality of car crashes (the negative presentation).

Sleeping at the wheel

So what kind of electronics can we expect to find in ADAS? The key thing to grasp is that ADAS do not reduce driver

responsibility. They are neither a control mechanism nor even an automatic pilot or failsafe system. So no sleeping at the wheel. Instead, ADAS alert drivers to facts they may be unaware of, providing drivers with all the information they need to know. Active intervention systems may come later but it's unlikely that the first generation of ADAS will dare go this far.

Cunningly, they avoid 'information overload' by prioritising the information you need to know. As the Siemens literature explains, all the information collected is evaluated continually and imperceptibly for the driver, presenting only what he or she needs to know. A clearly defined prioritisation process decides how relevant each kind of information is in each respective situation and which system should be used to alert the driver. Depending on the requirement, it can be a head-up-display appearing 'inlaid in light' on the windscreen, an LED in the door frame out of direct vision or perhaps a discreet steering correction.

Elementary stuff

So what are the main elements of ADAS? Chief among these are:

- Adaptive cruise control
- Drowsiness detection, with audible alarms and a blast of icy air
- Blind spot detection
- Parking assistance
- Night vision
- Pedestrian and cyclist detection
- Lane-change warning
- Traffic sign (speed limit) recognition
- Minimum distance maintenance in slow-moving traffic to avoid low-speed crashes.

This is by no means an exhaustive list, but it gives you a good flavour of what's feasible. Ignoring the information processing techniques, the data gathering devices are quite fascinating. Traffic sign recognition and lane-change warning will rely on miniature CMOS cameras, whilst enhanced night vision will use infrared sensors. Adaptive cruise control will most likely employ radar, whilst parking assistance will make use of ultrasound.

Digital signal processing will underpin all of these processes, which is where companies such as Siemens and Texas Instruments are in the lead with dedicated data acquisition devices, signal processors and the digital media processors necessary for handling and presenting the output of all this processed information.

All of which sounds very good, especially if ADAS live up to their promise and manufacturers can agree on standard

interfaces and electrical interchangeability. We can all look forward to safer and calmer motoring, as well as fascinating new articles in this magazine once low-cost video, radar and ultrasound modules filter down into our domain.

Boon or gimmick?

What we don't know yet is how the public will react to ADAS. Will they pay the extra for what will presumably be an optional extra? Will they scorn devices that call into question their driving skills or disable anything they think might reduce their control? Or might ADAS lull drivers into a false sense of security or reduce individual responsibility, leaving all that to the magic box?

Research undertaken into public attitudes by P.T. Blythe and A. Curtis of Newcastle upon Tyne University indicates that ADAS should find ready acceptance. Most people have little awareness of ADAS applications but perceive them to offer both safety plus ease and comfort benefits. The academics say attitudes are favourable towards such systems providing they can be switched off by the driver and negative when they cannot. Nonetheless, people are only willing to pay for those applications that they can easily and readily identify as having a clear and direct benefit for them, and even then they are reluctant to fork out much for these advantages.

Blyth and Curtis suggest that if ADAS applications are to find commercial success, good public education is vital, possibly with tax advantages for those prepared to take them up. Possibly the greatest barrier to the introduction of ADAS will lie not in public attitudes but determining where legal responsibility would lie should the systems fail. Watch this space!

Great balls of, er, silicon?

New research has been published on ball lightning, which you may remember we discussed last year. Brazilian scientists are the latest team to have created ball lightning artificially and according to physicist Antonio Pavão and doctoral student Gerson Paiva of the Federal University of Pernambuco, the physical manifestation that others and I have seen is silicon vapour. They postulate the silicon vapour is created when forked lightning hits soil in the ground and effectively burns it in the air.

According to *National Geographic* magazine, Pavão and Paiva simulated the process using electrodes to shock silicon wafers with enough electricity to create a silicon vapour. Most of the artificial orbs lasted two to five seconds.

Rapid

Cables & connectors

Connectors:
audio/video
mains/power
multipole
RF/coaxial
single pole

Electrical & power

Electrical products
& lighting
Fans & motors
Fuses & circuit breakers
Security & warning
devices
Batteries

Electronic components

Capacitors
Inductors & chokes
Filters & suppression
Resistors &
potentiometers
Transformers
Relays & solenoids
Sensors
Switches
Optoelectronics
Discrete
semiconductors
Integrated Circuits
Micros & crystals
Semiconductor
hardware

Tools, fasteners & production equipment

Cases
Fasteners & fixings
Storage/packing
equipment
Health & safety
Service aids
Soldering equipment
Test equipment
Electronic/electrical
tools
Mechanical tools
Power tools

 <p>NE555 Timer ICs From £0.08 Order code: 82-0336</p>	 <p>Only £3.60 Hobby & craft scissors Order code: 52-0940</p>	 <p>Only £25.99 Hobby magnifier (White) Order code: 86-3352</p>
 <p>Economy Plus tool kit Order code: 85-0052 Only £8.95</p>	 <p>Velleman audio power meter Order code: 70-4122 Only £11.99</p>	 <p>Miniature toggle switches From £0.30 Order code: 75-0082</p>
 <p>Low power NPN transistors From £0.015 Order code: 81-0466</p>	 <p>E12 Lamp holder Order code: 41-0776 From £0.03</p>	 <p>0.5kg Reel 22swg solder Order code: 85-0595 Only £6.95</p>
 <p>318 Digital LCD multimeter Order code: 85-0719 Only £9.90</p>		 <p>0402 Multilayer ceramic chip capacitor Order code: 71-1883 From £0.30</p>
		 <p>20x5mm Time lag glass fuses Order code: 26-0570 From £6.00</p>

FREE DELIVERY

On all orders over £25
(excluding VAT)
UK mainland only

SAME DAY DESPATCH

NO MINIMUM ORDER

UK mainland only

TECHNICAL ADVICE

DATASHEETS

CALL & COLLECT

TRADE COUNTER



Request your free catalogue by sending your full contact details
and quote reference EPE to marketing@rapidelec.co.uk

www.rapidonline.com

Tel: **01206 751166**
Fax: **01206 751188**
sales@rapidelec.co.uk

Rapid, Severalls Lane, Colchester,
Essex CO4 5JS

World Radio History

defining the standard

PICs and USARTs – A PICs USART is another valuable internal peripheral facility

LAST month we discussed Timers, a frequently used internal peripheral. This month we look at another popular peripheral, the USART. Unlike a timer, the USART provides an external interface for the microcontroller and finds uses in many projects that require connection to a PC or another complex electronic device.

Before we dive in, however, we should discuss what the acronym USART stands for, and describe the operating modes. The details appear complex but like many aspects of microcontroller design, its application to a project can be quite straightforward, as we will see later.

The USART

USART stands for Universal Synchronous/Asynchronous Receiver Transmitter. A bit of a mouthful and somewhat misleading, since many of us associate receivers and transmitters with radios. Here, it refers to data – sending and receiving information over port pins using some kind of protocol. (Protocol means ‘an agreed method of exchanging information’, a term stolen from diplomacy circles.)

As you might guess from the name, a USART supports two modes of communication: Synchronous and Asynchronous. Both use a single pin to transfer data in a serial fashion, bit by bit. Both the transmitter and the receiver need to agree on the rate at which the data bits are transferred, and this is where the two modes differ.

Fig.1 shows data communication in synchronous mode. Only one pin is used for transferring data, but another is used to send a ‘clock’ signal to the receiver so it knows when to sample the data line. This way the two devices do not need to share knowledge of the data rate; the clock, generated by the master, synchronises the receiver to the incoming data.

In synchronous mode the USART peripheral uses only two port pins for communication, so transmission and reception cannot occur simultaneously. One must transmit, then change to receive mode to get any returned data. This is called ‘half-duplex’ communication.

The additional benefit of synchronous communication is that the speed at which communication occurs can be varied dynamically, since data is only latched into the receiver on a clock edge.

Asynchronous communication on the other hand does not have a separate clock signal to indicate each data bit. The port pin previously used to provide the clock signal can now be used as another data signal, allowing simultaneous, bi-directional

communication (referred to as ‘full-duplex’.)

Fig.2 demonstrates the reception of an asynchronous signal. The eight data bits are ‘framed’ by a start bit and a stop bit. The start and stop bits are the same size as a data bit. As there is no clock signal the receiver uses the initial negative transition of the start bit as a ‘marker’ for the incoming data. The receiver then delays

by 1.5 times the length of a data bit, and takes a sample of the signal, by now hopefully in the middle of the first data bit.

This all relies heavily on the receiver and transmitter agreeing on the exact data rate, and having accurate internal timing (from a crystal oscillator for example) to ensure that one device does not drift relative to the other. The absence of a dedicated clock signal forces a requirement on the design to use precision oscillators. As most microcontroller designs do use precision oscillators anyway, this is not normally an issue.

Synchronous mode

Where synchronous operation scores over asynchronous is that the rate at which the data bits are transferred from one chip to another is controlled by the master device. The receiver neither knows nor cares what the speed of the transfer will be; it will shift in a data bit only when the transmitter’s clock signal toggles. This greatly simplifies the design of the interface (especially in smaller devices such as EEPROM memory) since the receiver does not need to generate an accurate clock signal that is precisely aligned to the other communicating device.

This benefit does come at the cost of an extra I/O pin needed for the clock signal, but that is a small price to pay in some circumstances. That is why you don’t see asynchronous interfaces on small low cost devices like EEPROM memory – providing an accurate oscillator would cost more than the actual memory!

Examples of synchronous communication protocols include SPI and I²C. These are such common interfaces that Microchip provides a dedicated peripheral for those, so the USART is not often used in this mode. With speeds of up to 10M bits/second, however,

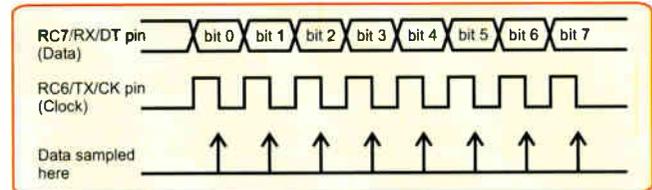


Fig.1. Synchronous communication

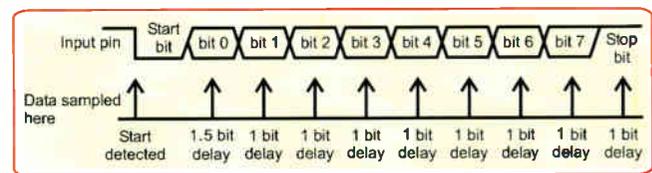


Fig.2. Asynchronous communication

synchronous mode is ideal for transferring data at high speed. Perfect for processor-to-processor communication in a PIC-based parallel computer for example (very definitely a subject for another article!).

USART variants

The PIC range of microcontrollers implement a number of variants of the USART, including none at all on the smaller parts. (This is not necessarily a problem; there are ways to implement a software USART, as we will see later.) The differences are minor and once you have understood how to use one USART, you will have no trouble adapting to a different type on another processor.

The Addressable USART, or AUSART, provides a mechanism for adding a ‘message address’ byte into a transmission. Rather than generate interrupts on every byte detected over the serial interface, only bytes marked as address bytes will generate an interrupt. This is particularly useful in a multi-drop serial link where several devices are connected to the same serial bus. The microcontroller can ignore all data bytes except address bytes; when one of these is received, the processor can check to see if the address is for itself, and if so, enable normal data reception. It reduces the amount of time a processor spends processing data bytes that are not intended for itself, thereby freeing up time to do other important tasks, or remain in a low power mode.

The Enhanced USART, or EUSART, extends the AUSART features by adding automatic Baud rate detection into the hardware of the USART peripheral. Combined with a little software, it is possible for a slave device to align its Baud rate to that of a transmitter. It’s a niche feature and in the author’s opinion, best ignored.

Stick with a known Baud rate and crystal oscillators!

By far the most common use for the USART is as an asynchronous RS232 link to a PC. Despite seeming to be coming to the end of its life as a result of the USB standard, the ancient RS232 interface is still with us and likely to remain so for supporting legacy devices. An RS232 interface to a PC can be a valuable debugging aid during software development, enabling you to display memory, status messages or even the content of SFR registers. Although this sounds rather primitive, it's a technique that is frequently used in professional embedded software development.

The RS232 standard was created in the early 1960's and typically used to talk to modems, video terminals and their predecessors, teletype printers. The standard is now formally called EIA232 but most of us still refer to it by its original name. Linking to a PC is not the only use for a USART, however, as it is also a popular interface to GPS receivers and RF modems and so will continue to be an important interface for years to come.

RS232 interface

A complete RS232 interface consists of several signals, not just receive and transmit data. Some of these signals are used for 'flow control' so that a receiver can instruct the transmitter to pause data transfer while it processes the data. These signals, called 'request to send' (RTS) and 'clear to send' (CTS) are not part of the USART peripheral and must be implemented using standard port I/O pins, should you wish to use them.

For most applications, however, hardware flow control is unnecessary as the handshaking can be done by the 'protocol' used to transfer data. Send some data, wait for an acknowledgement and then continue. It reduces the maximum data transfer rate, but simplifies the hardware and software design.

There is a surprising problem that should be taken into consideration when transferring data from a PIC-based design to a PC – if you transmit data from the PIC without delays between bytes the PC can lose data, since it is unable to respond fast enough to the data appearing on its serial port. This is a rather bizarre problem when one thinks about it; a PC running at 1GHz can be out-gunned by a humble 4MHz PIC. This is because the PC has many other things to do (such as managing a TCP/IP stack, or running a virus scan in the background.) This can be avoided by adding a delay between bytes being sent out, or requiring an acknowledgement before continuing.

USART use

So that's an overview of the USART and the different communication modes it can work in. Now, how do we use it?

The first place to start at is the block diagram in the datasheet, as we did with Timers last month. We are going to look at the Enhanced addressable USART in the PIC18F2420, a favourite of the author. The receiver and transmitter sections operate independently, and are shown as two separate block diagrams in Fig.3 and Fig.4. The block diagrams follow a similar style to the timer block diagram; the words in capitals

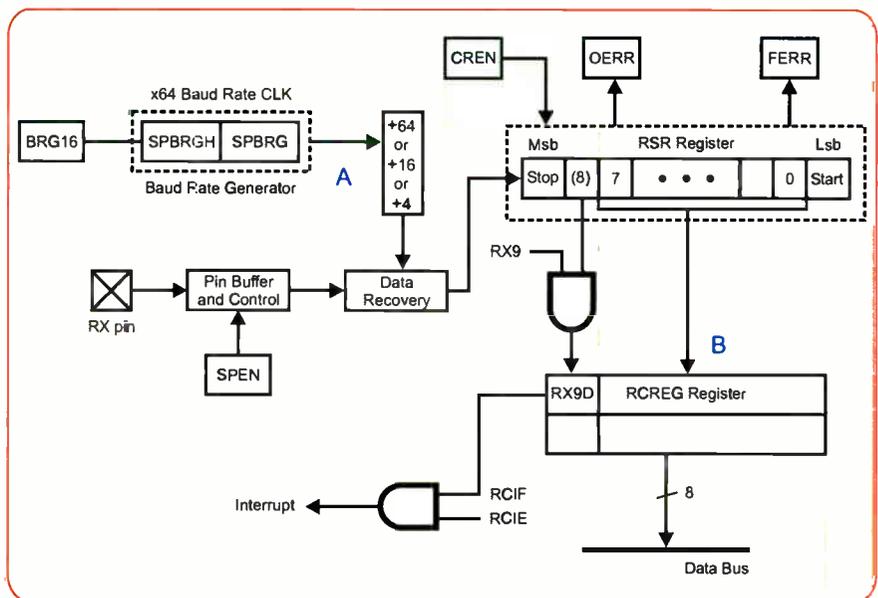


Fig.3. USART receiver

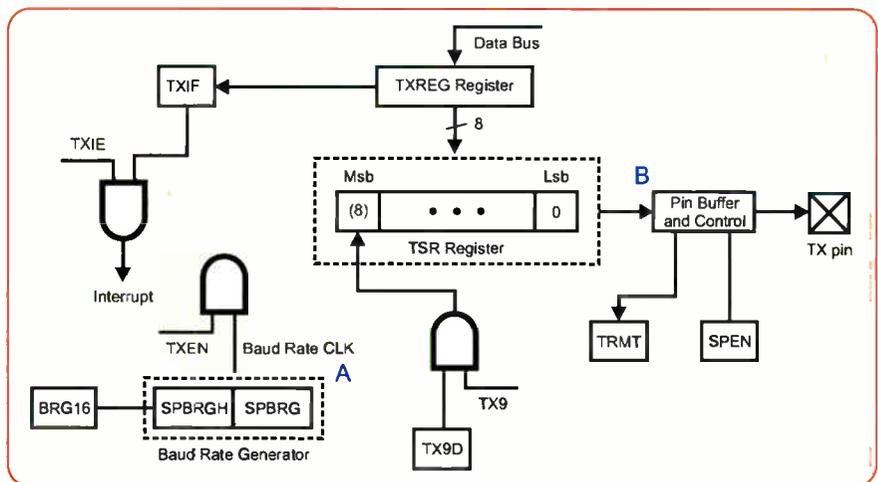


Fig.4. USART transmitter

are either special function register names or bits in registers.

The USART itself is really just a shift register, 'clocking' bits out onto a pin in the case of the transmitter, and clocking them in, in the case of a receiver. The rate at which this clocking occurs is determined by the Baud Rate Generator shown at position A in the diagrams. This is a register (or pair of registers, in the case of the PIC18F2420) that controls a divider circuit that reduces the main oscillator frequency down to the data rate required. There is a single Baud rate generator shared between the receiver and transmitter, but otherwise the receiver and transmitter are independent.

There are two pins associated with the USART, normally PORTC6 and PORTC7. These are multi-function pins that can be used for I/O if the USART functionality is not required.

In synchronous mode, port pin PORTC6 becomes the clock signal, and PORTC7 is either the receiver input or the transmitter output depending on the mode selected.

With asynchronous communication, reception is more complicated than transmission. The edge of the start bit marks the beginning of a data byte, and the CPU then samples the input pin at 16 different points

within each data bit time period and the average used to decide if the signal is high or low at that point. As you might guess, the transmitter and receiver must have very similar Baud rates, otherwise the receiver will 'drift' and over the eight data bits being received will start to record incorrect data.

Problems like these can be very difficult to find, so it is best to make sure that both transmitter and receiver use good clock sources, such as a crystal or ceramic oscillator. A rule of thumb is that the clocks of the two communicating devices should be within 2% of each other, which rules out resistor-capacitor (RC) or inductor-capacitor (LC) circuits. Although an RC oscillator can be calibrated it will exhibit too large a variation across temperature and voltage extremes.

Physical linking

Before setting up a USART, you need to make some decisions about how the physical link will operate. There are many options, and sometimes several ways to achieve the same result. Let's assume that the link will be asynchronous and not require any hardware flow control (the common setup), and that we are using a PIC18F2420 running at 20MHz. We need to consider the following:

Baud Rate: How fast do you want your link to run? Will you use a standard speed? If your interface is going to connect to a PC then you should ideally use one of the standard Baud rates such as 4800, 9600 or 115200. If the interface is going to display a simple text based menu on a PC then 9600 will be fine, although 115200 would be better, and easily achievable if you are running your processor off a fast enough clock.

Baud Rate Settings: There are three options for selecting the Baud rate, to give you the greatest flexibility in selecting a Baud rate for a given oscillator frequency. These are determined by the BRG16 and BRGH bits in the TXSTA and BAUDCON registers.

Data Width: Eight data bits is the standard, but you may want to add a 9th bit and use it for parity indication. A parity bit can help you identify a corrupted byte, but it isn't very effective and requires additional software written by yourself. You may have to use it if you are connecting to a third-party device that insists in transmitting parity (some magnetic card readers require this.)

Address Recognition: Are you connecting several devices to the same serial bus (like in RS485) and want to have hardware support for recognising address bytes? This is a useful feature in that case, but is not normally used in point-to-point links.

Interrupts: Are you going to have a simple system for sending and receiving data that just 'polls' the USART for status changes, or will you use interrupts? Interrupts complicate the coding effort but simplify the design, and allows for a more efficient use of the processor.

Example

To start off with, let's decide on 115200 Baud, eight data bits, no parity, no address recognition and no interrupts. There are several special function registers that we need to set up before we can start using the USART.

The order in which we do them is like this:

- Set PORTC6 to input
- Set PORTC7 to input
- Load SPBRG register
- Load SPBRGH register
- Set options in BAUDCON
- Set options in TXSTA
- Set options in RXSTA
- Set CREN bit in RXSTA

The difficult part is in deciding what values to use for SPBRG and SPBRGH. There are three register bits that determine how these values are calculated and fortunately the datasheet gives a series of tables with example values for different clock sources (Table 18-3 in the PIC18F2420 datasheet.) These tables offer different SPBRG values for different settings of the SYNC, BRGH and BRG16 bits.

Taking our 20MHz clock source as an example, we can look at the various tables to find a match with our desired Baud rate of 115200. The first table gives an SPBRG value of 2 for that Baud rate, but with an

error of 9.58%. That's not going to be good enough, so looking on two tables down, a value of 10 for SPBRG gives a 1.38% error (an actual Baud rate of 113636), close enough for our needs. To use this value the BRGH bit must be set, and BRG16 cleared (meaning that the BRG register is only 8 bits wide, not 16).

This is what the initialisation code would look like:

```
movlw 0xC0
movwf TRISC
clrf SPBRGH
movlw 0x0A
movwf SPBRG
bsf BAUDCON, BRG16
bsf TXSTA, BRGH
bcf TXSTA, SYNC
bsf RCSTA, SPEN
bsf RCSTA, CREN
```

To receive a byte, poll the RCIF bit in the PIR1 register, which will be set when a byte has been received. Before reading the byte it is important to check for any errors that may have occurred. To do this, read the RCSTA register and check the FERR and OERR bits. If either of these are set you must clear the error, otherwise the receiver will go 'mute' and ignore any further data. To clear an error issue the following instructions:

```
bcf RCSTA, CREN
bcf RCSTA, OERR
bcf RCSTA, FERR
bsf RCSTA, CREN
```

Transmitting a byte is somewhat easier; simply write the byte to be sent into the transmit register TXREG. Before writing a byte, however, one should check that the transmit shift register is not still busy sending a previous byte. This is done by polling the TXIF bit in the PIR1 register:

```
wait:
btfss PIR1, TXIF
goto wait
```

While using polling during transmission is quite reasonable, it is often impractical for reception. To enable interrupt processing, simply set the interrupt enable flags for PEIE, RCIE and the global interrupt enable flag GIE:

```
bsf PIE1, RCIE
bsf INTCON, PEIE
bsf INTCON, GIE
```

Then within your interrupt routine, simply test the receiver flag:

```
int:
btfss PIR1, RCIF
bra otherCode
```

```
; check for error
; read byte
```

Bit-bashing

It is possible to enable interrupts on other actions, such as the transmitter becoming empty, which would make a fully interrupt driven serial transmit and receive system possible. While the

peripheral provides the interrupt events, you must write the software to support them yourself. Fortunately, as previously mentioned, there are many examples of code available.

Of course, it is possible to implement a USART in software without any special peripheral hardware support, by 'bit-bashing' the signal. This technique is used on smaller devices with no hardware support, or on larger parts when two or more USARTs are required. The *EPE CameraWatch2* project did this; it used the hardware USART for communicating with an embedded GPS module, and a 'bit-bashed' interface for providing an interface to a PC.

Bit-bashed transmission is straight forward. The algorithm would look like this:

INITIALISATION

```
set pin to output
set pin high
```

TRANSMIT

```
set pin low
delay 1 bit time
for each bit
  set pin to bit value
  delay 1 bit time
end for
set pin high
delay 1 bit time
```

You just need to ensure that the 1-bit delay is accurate, and that interrupts are not enabled during the transmission of a byte.

The receiver section of a bit-bashed USART is similar:

INITIALISATION

```
set pin to input
```

RECEIVE

```
wait for pin going low
delay 1.5 bit time
for each bit
  test input pin
  store bit level
  delay 1 bit time
end for
test input pin
if low, ignore data
```

Although this technique works, it has a few flaws. The error detection is not very good – a spurious glitch on the receive line would be detected as a data byte, and also the sampling of each data bit occurs only once in the middle of each bit. A real USART will take several samples in each data bit time, and average the samples.

Bit-bashing is also very time consuming since the CPU cannot do any other work while bytes are being transmitted. Since you have to perform very accurate delays in software, you cannot have interrupts enabled during transmission or reception. However, these limitations can often be acceptable.

Application notes

The Microchip website www.microchip.com has a number of application notes on serial communications.

Batteries



Zinc Chloride, Alkaline, NiMH, NiCD & Sealed Lead Acid batteries. We carry battery packs for racing & radio control. We also manufacture the NiCD Bot-Pack+, a high performance custom made pack with forced cooling options for the most demanding applications.

Sample pricing:

- GP AA Greencell £0.79 / pk4
- GP AA Greencell £0.13 / cell in trade boxes of 320 (ideal for schools)
- GP AA Ultra Alkaline £1.20 / pk4
- GP AA NiMH 1300mAh £3.95 / pk4
- Racing packs from £11.95
- 12V 2.2Ah to 44Ah SLA from £6.99

Power Supplies / Chargers



13.8V 20A power supply with Amps display £43.87

Power supplies fixed and variable voltage to 15V 40A. Chargers for NiCD, NiMH, LiPo & SLA batteries to 12V 20A.



Sample pricing:

- GP AA charger with 2 off 1300mAh cells £5.45
- 13.8V 20A Power Supply from £34.12

Motors



Probably the best range of DC model motors in the UK. From under 0.5W to 1000W, 1.5 to 36V. Geared motors from 0.3W to 800W. Ideal for most model engineering applications especially robotics. Planetary geared motors from just 1.2g to our top of the range 750W (that's 1HP) weighing in at 6.35kg.



As well as motors, we have wheels, axles & bearings to help complete your project.



Sample pricing:

- Visit our website to see over 140 models of motor
- 12V 150W Motor £17.95
 - Geared motors from £4.70
 - 750W 36V geared motors from £90.95

Visit our website to see over 2,000 products to order on-line. Need advice?, we offer full technical support via our FAQ forum.

Technobots Ltd
The Old Grain Store
Rear of 62 Rumbridge Street
Totton, Hampshire, SO40 9DS
Tel: 023 8086 3120 Fax 023 8086 1534
Lines open Mon - Thur 0900 to 1330

Technobots.co.uk

Robotics, Models and Technology Supplies

Established in 2001, Technobots Ltd supply a wide range of electronics and engineering products to the hobby market, schools, Colleges & Universities.

Motor Speed Controllers



DC motor speed controllers from 1A to 300A. Various interfacing options including RC, I2C, serial &

analogue voltage. Relay reversing and fully solid state H-bridge, single and dual channel variants.



Sample pricing:

- Dual 1A motor controller £17.09
- 10A motor controller kits from £19.87
- 75A controllers from £87.50

Radio Control



A wide range of radio control products including transmitters, receivers, servos, gyros, crystals, interfaces, leads etc.

Sample pricing:

- 4-Channel 40MHz FM transmitter / receiver / crystals from £34.95

Microcontrollers



The 'PICAXE' range of programmable microcontrollers. Write in BASIC or Flowchart and download straight into the microcontroller, so no expensive programmers are required. The 8 pin version provides 5 i/o pins (1 analogue input). The 18 pin version provides 8 outputs and 5 inputs (3 of the inputs have analogue capabilities). The 28-pin version provides 9-17 outputs, 0-12 inputs and 0-4 separate analogue inputs.

Sample pricing:

- 8 pin starter kit including software, lead, battery holder, PCB & components for £9.94
- 28 pin version pictured above £21.74

Robot Kits

We carry a wide range of robot kits from BEAM to full combat and includes the very popular Robonova biped walker. Kits range in price from £16.95 to £689.05 built by enthusiasts & school pupils from all over the UK. Many are programmable via a PC, RC or autonomous. Full details of these and lots more can be found on our website.




Mechanical & Hardware



We carry a wide range of mechanical products many of which are hard to find elsewhere. Bearings from 1mm to 30mm bore. Plastic and steel pulleys, plastic and

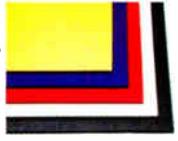steel gears from MOD 0.5 to MOD 2.0. Steel chain sprockets in 6 & 8mm, 3/8" & 1/2" pitch. Silver steel, EN24T steel, collets & shaft couplings. Nuts and



bolts from M2 to M12, springs, clips & Pins. Wide range of engineering materials including aluminium (6082 T6 to 12mm thick), brass tube, rod, sheet etc..

Polycarbonate sheet from 1mm to 12mm thick, PVC sheet, polymorph etc.. Wheels from 9mm to 250mm diameter.

Featured Product




We believe this to be the lowest retail priced 4-channel 40MHz FM radio control set in the UK. The set includes the transmitter, receiver and crystal pair from just £34.95. Upgrade options available.



Sample pricing:

- Transmitter, receiver and xtals £34.95
- As above but with a set of 8 AA batteries £35.95
- As above but with a set of 8 AA rechargeable batteries £41.49
- Add a fast charger for an additional £11.46

Electrical

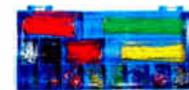

Glass, automotive and maxi fuses from 1A to 100A, fuse holders, cable from 0.5mm² to 16mm².

Pre-stripped wire kits for breadboards. Connectors from 5A to 300A, wide range of crimp connectors bagged in 100's or in kits. Circuit breakers from 3A to 30A. Cable ties, tie bases, spiral wrap and heatshrink (1.2 to 101.6mm diameter).

All prices include VAT



Whilst we are an internet based company, we do have a shop where visitors are very welcome to browse.

Please check our website for opening hours and if making a long journey, we suggest phoning first to ensure stock availability. If ordering on-line, 90% of orders dispatched within 2 working days.

PayPal





The photo at left shows the completed power supply module. Position the inductor (L1) so that it's well clear of surrounding components and secure it to the PC board using small cable ties. At right is a 5W Luxeon star LED, shown about 50% larger than actual size.



STARPOWER

High-efficiency supply for Luxeon Star LEDs

Based on a switching regulator IC, this simple project is just the job for powering 1W to 5W ultrabright Luxeon Star LEDs. It's easy to build, runs off 12V DC and can be easily tailored to suit your requirements.

By PETER SMITH

BACK IN THE October 2006 issue, we presented a simple linear power supply for powering 1W Luxeon Star LEDs from a 12V supply. Predictably, we've already received requests for a version that will drive the, brighter 3W and 5W Stars.

In addition, many constructors want a higher efficiency supply for use in boats, caravans and cars. This new design fits the bill and includes low battery cutout as well.

Unlike the original design, which is based on a linear regulator, this new supply employs a step-down switching regulator. The advantages of this method include much improved efficiency and significantly reduced heat generation.

In fact, when driving a single 3W Star, this supply is at least twice as

efficient as a linear supply or simple current-limiting resistor. Obviously, this means longer battery life. Lower heat generation also means that you can build the supply into a case without the need for additional heatsinking.

The project can be powered from any 12V DC (nominal) supply and can be set up to source 350mA, 700mA or 1000mA of regulated current to suit the Luxeon Star LED range.

Block diagram

The circuit is based around a Motorola MC34063 DC to DC converter IC. This chip contains all of the functions necessary to construct a complete low-power step-down switchmode regulator – see Fig.1.

A simplified block diagram of the step-down regulator appears in Fig.2.

Essentially, when transistor Q1 switches on, current through the series inductor (L1) increases with time, storing energy in its magnetic field. When Q1 is switched off, the magnetic field collapses and the energy is discharged into the output filter capacitor and load via diode D3.

A free-running sawtooth oscillator in the MC34063 determines the maximum switch 'on' time. The 'on' time of the switch (Q1) versus its 'off' time determines the fraction of the input voltage that appears at the output.

IC1 controls the 'on' time by monitoring the voltage on its feedback pin. As this voltage falls below 1.25V, Q1's 'on' time increases. Conversely, as the feedback voltage increases, the 'on' time decreases. Complete 'on' cycles are skipped if the feedback voltage remains above the 1.25V set point for the duration of the 'on' period.

In a typical implementation, the feedback pin would be connected to the output via a voltage divider to regulate the output voltage. However, our design regulates output current instead.

Current through the LED(s) is sensed via resistor R1 and then amplified by op amp IC2. The result is applied to the feedback pin of IC1 via a trimpot, VR1,

Main Features

- Powers one or two 1W or 3W Stars, or a single 5W Star
- High efficiency for minimum battery drain
- Low battery cutout (11.5V)
- Input polarity and transient protected
- Output short-circuit protected
- Ideal for use in boats, caravans and cars

allowing accurate current adjustment's to be made.

Simply put, the output current is regulated by maintaining the voltage across the sense resistor at about 100mV. In practice, the actual sense voltage depends on the value of R1 and the position of the trimpot VR1.

Circuit details

The complete circuit diagram appears in Fig.3. Following the circuit from the input voltage side, diode D1 provides reverse-polarity protection. A Schottky type is used here to reduce voltage losses.

Next, a 24V Zener diode (ZD1) clamps input transients to less than the maximum voltage rating of downstream components. A 470µF capacitor then filters the input and provides a low-impedance source for the high-frequency switching circuitry.

As described earlier, transistor Q1 acts as a switch in series with the inductor (L1). A Zetex low V_{CESAT} (collector-emitter saturation voltage) type was chosen for Q1 to improve efficiency and reduce heat dissipation.

The performance of the switching circuit is further enhanced by a turn-off speed-up circuit, which operates as follows:

During an 'on' cycle, transistors internal to the MC34063 switch on, bringing pins 1 and 8 towards ground. This forward-biases the base-emitter junction of Q1 via D4 and L2, switching the transistor on.

When the 'on' cycle ends, pins 1 and 8 go open circuit and the current through L2 ceases abruptly. The magnetic field around L2 collapses, generating a voltage of opposite polarity to the charge voltage. This forward-biases the base-emitter junction of Q2, momentarily switching it on and con-

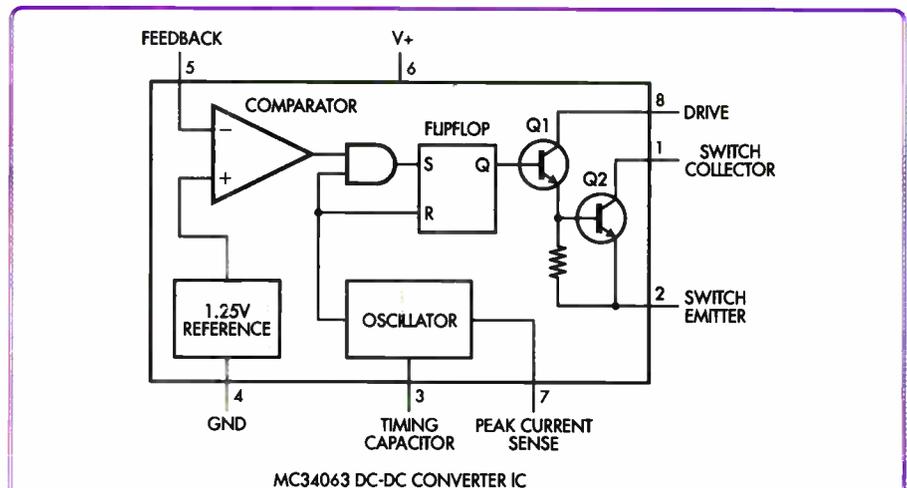


Fig.1: inside the MC34063 DC-DC Converter IC. It contains the circuitry to build a step-up, step-down or inverting switching regulator.

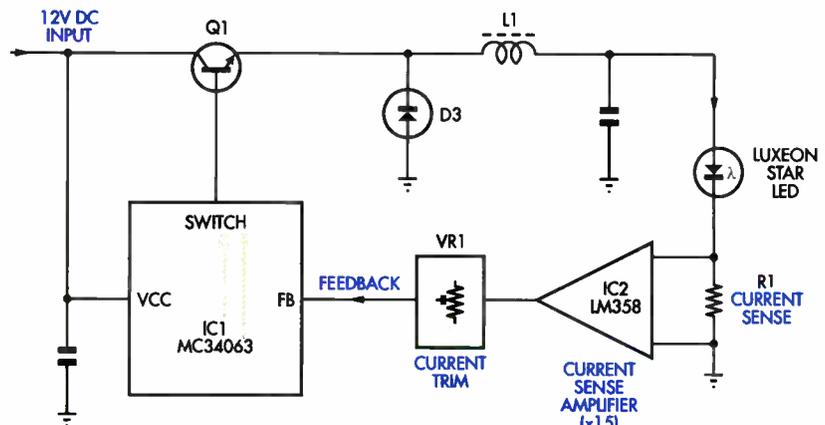


Fig.2: the basic block diagram of the step-down switching regulator section. A fraction of the input voltage is transferred to the output under control of an MC34063 switching regulator IC. The LED current is regulated by sensing the voltage drop across a small series resistance (R1).

necting the base of Q1 to its emitter.

This results in significantly faster turn-off of Q1 than is possible with a resistive pull-up alone. By minimising the transition time between saturation and turn-off, collector power dissipation, and therefore switching losses, are effectively reduced.

When Q1 switches off, diode D3 provides a discharge path for the inductor (L1) to the output filter capacitor and load. Again, a Schottky diode is used for its fast switching and low forward voltage characteristics. Note that we've specified high current (3A) devices in order to withstand a continuous short-circuit condition at the output.

In normal operation, the peak current that flows in the transistor and inductor during each switching cycle is well within the limits of the component ratings. However, with an

overloaded or short-circuited output, or with excessively high input voltages, the peak current could increase to destructive levels.

To counteract this problem, IC1 senses peak current via a 0.15Ω 5W resistor in series with the input. When the peak voltage across this resistor nears 330mV, the MC34063 progressively reduces the maximum 'on' time of the switch by shortening the positive ramp of the oscillator.

Current sensing

A resistor in series with the LED provides a means of sensing output current. The voltage developed across R1 is amplified by one half of a dual op amp (IC2b), which is configured as a differential amplifier. With the resistor values shown, the sense voltage is amplified by a factor of 15 and applied to one end of VR1.

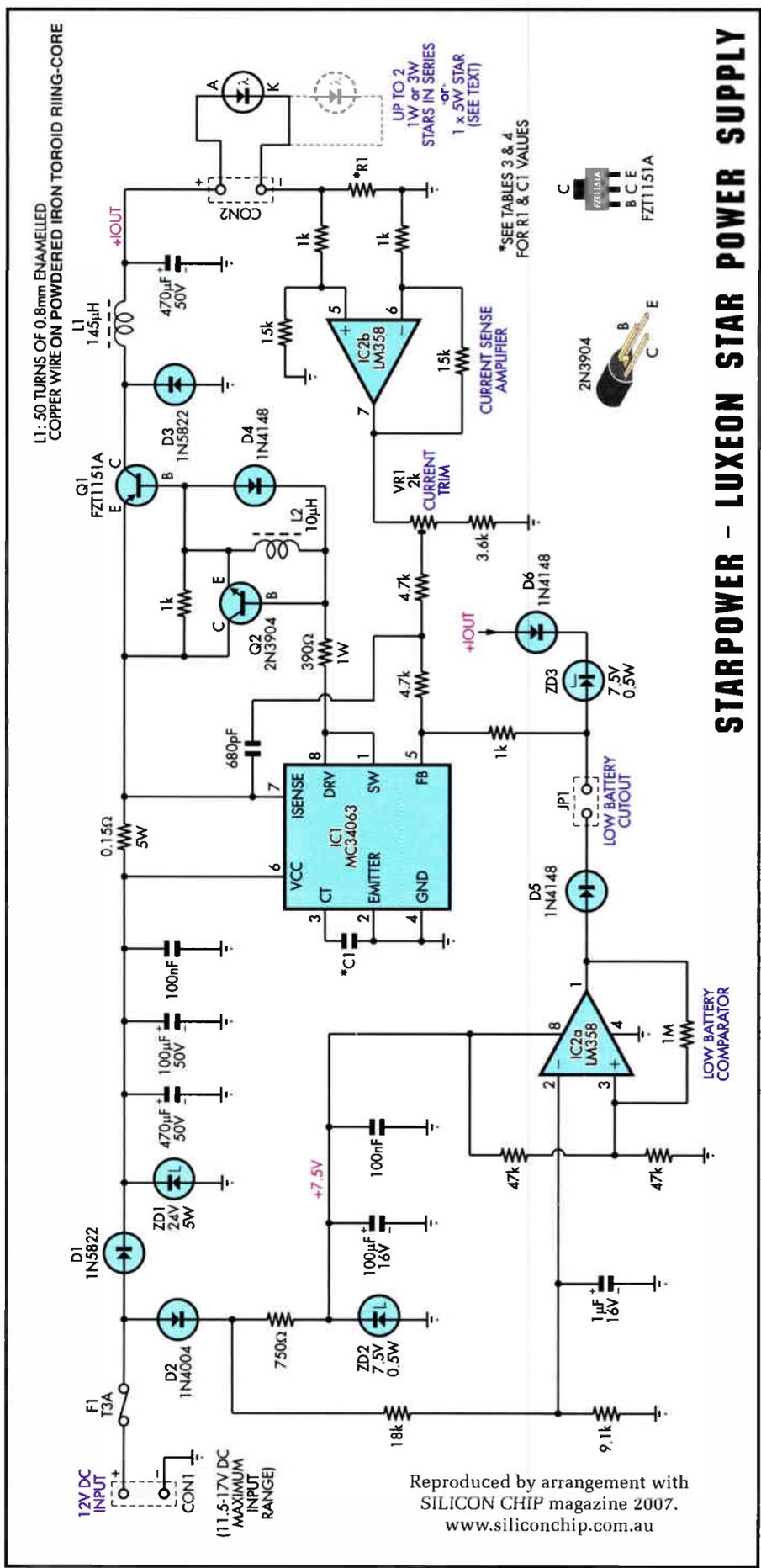


Fig.3: the complete circuit diagram for the power supply module. A low VCEsat transistor (Q1) is used for the switching circuit to minimise heat dissipation and improve efficiency. Output current is selectable in three ranges by choosing an appropriate value for R1.

Effectively, trimpot VR1 provides a means of adjusting the voltage drop across R1. As the wiper is moved towards the top (clockwise), less voltage is required across R1 to satisfy the feedback loop, so the output current decreases. The opposite occurs when the wiper is moved downwards, attenuating the op amp's output and thus increasing the output current.

During construction, R1 is selected from Table 3 to suit the desired LED current. These values were chosen such that close to 100mV will be present across the resistor at the listed LED current level. It's then just a matter of adjusting VR1 to get the precise current level.

To reduce harmonics in the switching circuit, a novel scheme is used to 'feed forward' a small portion of the switching signal into the feedback circuit. This is achieved with a 680pF capacitor between the ISENSE and FB pins of IC1.

Low battery cutout

IC2a is used as a simple voltage comparator for the low battery cutout circuit. It works as follows.

Zener diode ZD2 provides a clean +7.5V supply for this op amp. This 7.5V rail is also divided in half by two 47kΩ resistors to provide a reference voltage for the comparator on (non-inverting) pin 3. Similarly, the power supply input voltage is divided down by 18kΩ and 9.1kΩ resistors and applied to the negative (inverting) input (pin 2).

When the voltage on pin 2 falls below that on pin 3 (corresponding to less than 11.5V at the supply input), the output swings towards the positive rail, forcing IC1's feedback input above the 1.25V set point. This stops IC1 from switching and reduces the input current drain to quiescent levels (less than 10mA).

A 1MΩ resistor between the op amp output (pin 1) and its positive input ensures fast switching and provides a few hundred millivolts of hysteresis. In addition, a 1μF capacitor at the inverting input (pin 2) filters out any

Parts List: Star Power – Luxeon LED Power Supply

- 1 PC board, code 615, available from the *EPE PCB Service*, size 105mm x 60mm
- 1 powdered-iron toroid ring-core, 28 x 14 x 11mm (L1 – see text)
- 170cm (approx) 0.8mm enamelled copper wire
- 1 10 μ H RF choke (L2)
- 2 2-way 5mm (or 5.08mm) terminal blocks (CON1, CON2)
- 1 2-way 2.54mm SIL header (JP1)
- 1 jumper shunt (JP1)
- 1 8-pin IC socket
- 2 M205 PC mount fuse clips
- 1 M205 3A slow blow fuse
- 4 M3 x 10mm tapped spacers
- 4 M3 x 6mm pan head screws
- 2 small cable ties
- 1 heatsink for 3W or 5W LEDs (see text)
- 1 2k Ω miniature horizontal trimpot (VR1)

Heavy-duty (7.5A) cable for power input and LED output wiring. (Cable length between output and LEDs should be no more than (25cm).)

Semiconductors

- 1 MC34063 DC-DC converter (IC1)
- 1 LM358 dual op amp (IC2)
- 1 FZT1151A PNP transistor (Q1)
- 1 2N3904 NPN transistor (Q2)
- 2 1N5822 3W Schottky diodes (D1, D3)

- 1 1N4004 diode (D2)
- 3 1N4148 signal diodes (D4 - D6)
- 1 24V 5W Zener diode (ZD1)
- 2 7.5V 0.5W (or 1W) Zener diodes (ZD2, ZD3)
- 1 or 2 1W or 3W Luxeon Star LEDs; or 1 5W Luxeon Star LED (see text)

Capacitors

- 2 470 μ F 50V low-ESR PC electrolytic
- 1 100 μ F 50V low-ESR PC electrolytic
- 1 100 μ F 16V PC electrolytic
- 1 1 μ F 16V PC electrolytic
- 2 100nF 50V monolithic ceramic
- 1 1.2nF 50V ceramic disc (or polyester)
- 2 680pF 50V ceramic disc
- 1 560pF 50V ceramic disc
- 1 330pF 50V ceramic disc

see text

Resistors (0.25W 1%)

- 1 1M Ω
- 2 47k Ω
- 1 18k Ω
- 2 15k Ω
- 1 9.1k Ω
- 2 0.15 Ω 5W (or 3W) 5%
- 1 0.1 Ω 5W (or 3W) 5%
- 1 0.27 Ω 5W (or 3W) 5%
- 2 4.7k Ω
- 1 3.6k Ω
- 4 1k Ω
- 1 750 Ω
- 1 390 Ω 1W 5%

see text

Additional resistors for testing

- 1 10 Ω 5W 5% (350mA test)
- 1 4.7 Ω 5W 5% (700mA test)
- 1 3.3 Ω 5W 5% (1000mA test)

momentary transients and ensures that the negative input remains below the positive input during power up.

Note that despite this filtering, the LED will flash momentarily at power on and power off. This is because unlike the LM358 op amp, the MC34063 operates right down to 3V.


Finally, a series diode (D6) and 7.5V Zener diode (ZD3) connected between the output and the feedback circuits prevents the output voltage rising much above 9V if the LED is inadvertently disconnected. This helps to reduce the peak current flow that occurs if the output is reconnected with power applied.

Construction

The assembly is straightforward, with all the parts mounted on a PC

board coded 615 and measuring 105 x 60mm. The parts are all installed on the board in the conventional manner, except for switching transistor Q1, a surface-mount (SMT) device, which is installed on the copper side (Fig.6).

Fig.4: this scope shot shows the switching waveform present on the cathode of D3 (top trace) versus the MC34063's on-board oscillator on pin 3 (bottom trace). Note that the switching frequency will vary significantly according to LED type and number and will not necessarily equal the oscillator frequency.

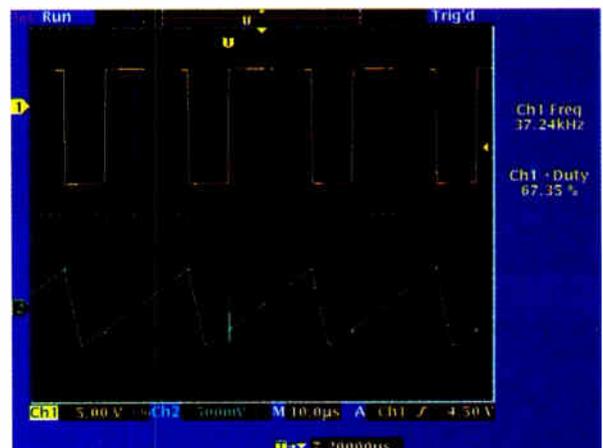

The first job is to mount Q1. Although this is an SMT device, it has relatively large pins with ample spacing that are easy to solder.

To install it, place the copper side of the board up and position Q1 precisely as shown on the overlay diagram (Fig.6) before soldering the leads.

With Q1 in place, turn the board over and install the two wire links using 0.7mm tinned copper wire or similar. One of the links (shown dotted) goes underneath IC2, so it's important that it goes in first!

Next, install all the low-profile components, starting with the 0.25W resistors and diodes. All the diodes, including the Zeners, are polarised devices and are installed with their banded ends oriented as shown.


An IC socket can be installed for IC2. However, IC1 should be soldered directly to the board (no socket!) to eliminate the effects of contact resistance. Be sure to align the notched (pin 1) ends as indicated.

All remaining components can now be installed except for the electrolytic capacitors. It's easier to leave these until after the inductor (L1) is in place.

Select appropriate values for C1 and R1 from Tables 3 and 4. It's very important that these match your intended application (type of LED and one or two LEDs in series). The parts list includes all of these parts, so you will have an extra three ceramic capacitors and two 5W (or 3W) resistors left over once assembly is complete.


Winding the inductor

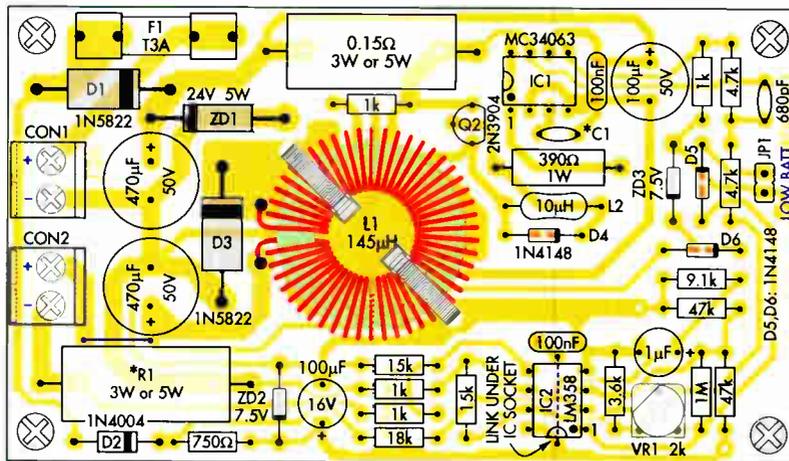The inductor (L1) must be hand-wound using the specified toroidal core and about 170cm of 0.8mm enamelled copper wire. Play out the wire into a straight length, removing any kinks before you begin.



*SEE TABLES 3 & 4 FOR R1 & C1 VALUES

Fig.5: follow this layout diagram when installing the parts on the PC board and don't forget the link under IC2.

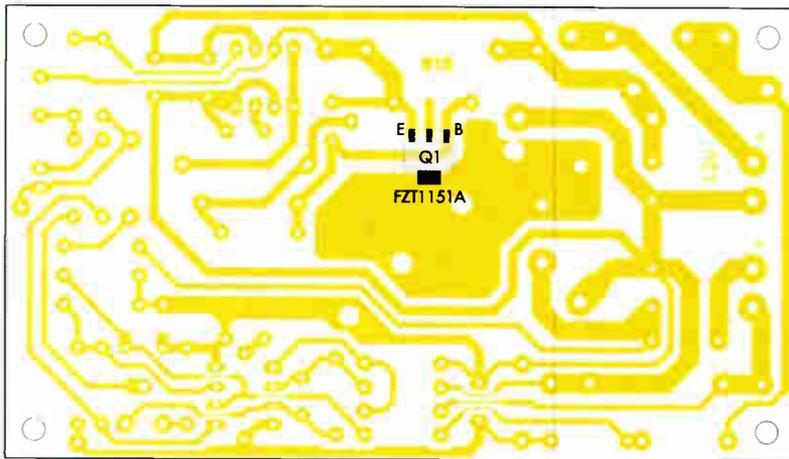

BOTTOM (COPPER) SIDE

Fig.6: the mounting details for transistor Q1. It's soldered on the copper side of the board using a fine-tipped soldering iron.

It's easier to wind one half at a time, so start by feeding about half of the wire through the centre of the core. Wind on the first half using firm even tension and keep the

turns as close as possible without overlapping.

Now repeat this procedure with the second half of the wire. In total, the core will accommodate 50 turns

Table 2: Capacitor Codes

Value	μF Code	EIA Code	IEC Code
100nF	0.1 μF	104	100n
1.2nF	0.0012 μF	122	1n2
680pF	-	681	680p
560pF	-	561	560p
330pF	-	331	330p

if there are no gaps between adjacent turns on the inside of the core.

Now count the total number of turns. With a bit of luck, you should have 49 or 50 (one less is OK!). Trim and fashion the ends of the wire so that the assembly slips home easily into the holes in the PC board with a few millimetres protruding out the opposite side.

Next, scrape the enamel off the ends of the wire, tin them and reposition the inductor on the PC board. Don't solder the wires just yet though. It's important to first attach the inductor to the board using small cable ties. Position the inductor so that it is well clear of surrounding components before tightening up the ties. That done, solder and trim the wire ends.

Finally, install all the electrolytic capacitors to complete the job. Take particular care with orientation – their positive leads must go in as indicated by the '+' markings on the overlay diagram.

Setup and testing

Before connecting an LED to the output for the first time, the supply should be checked for correct operation. During the test, we'll also set the output current to an initial value to suit the type of LEDs being used.

The test involves inserting a 5W test resistor in the LED output terminals.

Table 1: Resistor Colour Codes

No.	Value	4-Band Code (1%)	5-Band Code (1%)
□	1M Ω	brown black green brown	brown black black yellow brown
□	47k Ω	yellow violet orange brown	yellow violet black red brown
□	18k Ω	brown grey orange brown	brown grey black red brown
□	15k Ω	brown green orange brown	brown green black red brown
□	9.1k Ω	white brown red brown	white brown black brown brown
□	4.7k Ω	yellow violet red brown	yellow violet black brown brown
□	3.6k Ω	orange blue red brown	orange blue black brown brown
□	1k Ω	brown black red brown	brown black black brown brown
□	750 Ω	violet green brown brown	violet green black black brown
□	390 Ω 5%	orange white brown gold	not applicable

The resistor value to use depends on the output current level selected during assembly. For 350mA of current, use a 10Ω test resistor, for 700mA a 4.7Ω value and 1000mA a 3.3Ω value.

Don't cut the resistor leads short. It should be screwed into the LED output terminal block and suspended in mid-air, such that it's not in contact with anything; **it will get very hot!** *With this in mind, the circuit should not be powered up for more than a few minutes with the test resistor in place.*

Remove the jumper shunt on JP1 if you installed it earlier and rotate VR1 fully clockwise. Connect a 12V DC (1A or higher) power source to the input terminals and power up. Monitor the voltage across R1 (not the test resistor) with your multimeter and adjust VR1 to get the desired current level. The correct sense voltage for each current level is listed in Table 3.

For example, if you want 700mA for a 3W LED, you will have installed a 0.15Ω resistor for R1, so adjust VR1 to get a 105mV reading on your meter.

If all checks out, you're almost ready to go. Remove the test resistor and replace it with the Star LED leads. Power up again and check that the voltage across R1 is as previously set. If necessary, readjust VR1 to get the listed reading.

Note: the light output from these LEDs could damage your eyesight. Do not stare directly into the LED beam at close range!

If you have a variable DC bench supply, you can also test the low battery cutout circuit by slowly reducing the input voltage. At about 11.5V, the LED should switch off. Remember to install the jumper shunt on JP1 to enable this function.

Note: in a quiet environment, you may be able to hear a low level 'squeal' coming from the inductor (L1). This is completely normal and is due to the harmonics caused by the gated oscillator architecture of the MC34063 switching regulator IC.

Fault-finding

If your meter reads way off the mark and/or adjusting VR1 has no effect, then there is a fault on the board. Switch off immediately and remove the test resistor, then power up again with nothing connected to the output.

With your meter set to read volts, first measure between pins 1 and 8 of

IC2. These are the op amp supply pins, so you should get close to 7.5V. If not, look for problems around ZD2 and its associated circuitry.

Next, measure between pins 6 and 4 of IC1. Again, these are the supply pins of the IC, but this time, expect about 0.3V less than the input voltage.

If you have an oscilloscope, you can check that the oscillator in the MC34063 is working by examining the waveform on pin 3. You should see a clean sawtooth waveform like that shown in Fig.4.

Assuming the above measurements are OK, then it's back to basics. Examine the board closely for correct component placement and soldering defects, especially around IC1, IC2 and the 100μF 16V capacitor. It's easy to get solder bridges between the closely spaced tracks in these areas.

Mounting and wiring


The completed power supply module can be mounted without an enclosure if a protected location is available. Alternatively, it can be housed in a UB3-sized box for ruggedness.

For marine applications, the entire assembly will need to be conformally coated or installed in a sealed enclosure to keep corrosion at bay.

The power input and LED output wiring must be run using heavy-duty (7.5A) cable. We recommend no more than



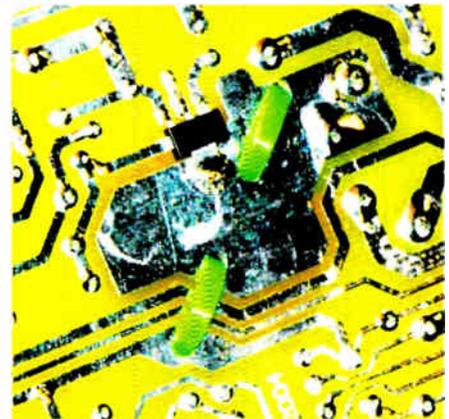Bend and shape the ends of the winding so that the assembly slips easily into the holes in the PC board. This shot of the underside of L1 shows the general idea, although this core doesn't have the full 50 turns!



This larger-than-life size view shows how transistor Q1 is mounted on the underside of the PC board.

Table 3: Selecting Resistor R1

LED Type	LED Current	R1	Sense Voltage
1W Star	350mA	0.27Ω	94.5mV
3W Star	700mA	0.15Ω	105mV
3W Star	1000mA	0.1Ω	100mV
5W Star	700mA	0.15Ω	105mV

Table 4: Selecting Capacitor C1

LED Type	No. of LEDs in Series	Colour	C1
1W Star	1	Red, Red-Orange, Amber	330pF
1W Star	2	Red, Red-Orange, Amber	680pF
1W Star	1	White, Green, Cyan, Blue, Royal Blue	560pF
1W Star	2	White, Green, Cyan, Blue, Royal Blue	1.2nF
3W Star	1	All	560pF
3W Star	2	All	1.2nF
5W Star	1	All	1.2nF

Constructional Project

about 25cm of cable length between the power supply output and the LEDs.

Keeping your LEDs cool

This project can be used to power any of the 1W, 3W or 5W Luxeon Star range. Out of these, the 1W version is by far the easiest to use because of its relaxed heatsinking requirements.

In fact, when operated in low ambient temperatures, no additional heatsinking is necessary for versions with board mounted optics (Star/O).

However, in most real-world applications, a small heatsink will help to keep the LED junction temperature within spec, as well as prevent heat damage to the acrylic lens. This can often be as simple as a flat metal panel or the lid of a metal case, for example.


Unlike the 1W types, the 3W and 5W Stars require careful attention to heatsinking, particularly when reliability and long service life are important. Despite this requirement, the excellent 'lumens per pound' rating of the 3W Stars definitely makes them worth a look. So how is the heatsink size determined? Let's find out!

Heatsink basics

We can calculate the required heatsink thermal resistance once we know the maximum junction temperature, ambient temperature and power dissipated.

As only about 10% of the input power to the LED is emitted as light, it is disregarded in the following calculations. Assuming a nominal LED forward voltage of 3.6V, power dissipation can be found using Ohms law:
 $P_D = V/I = 3.6V/1A = 3.6W$

We mounted our 3W Star on a 48mm square heatsink pinched from an old 486 motherboard. Drill two 3mm mounting holes in line with the slot between the fins and then deburr the holes to obtain a smooth mounting surface. A thin smear of heatsink compound between surfaces will aid heat transfer. You'll need to use nylon washers under the heads of the screws to prevent short circuits to the solder pads on the Star PC board. Don't be tempted to run the 3W or 5W Stars without a heatsink – they'll quickly self-destruct! Wide, narrow and elliptical beam lenses can be fitted to suit most applications.

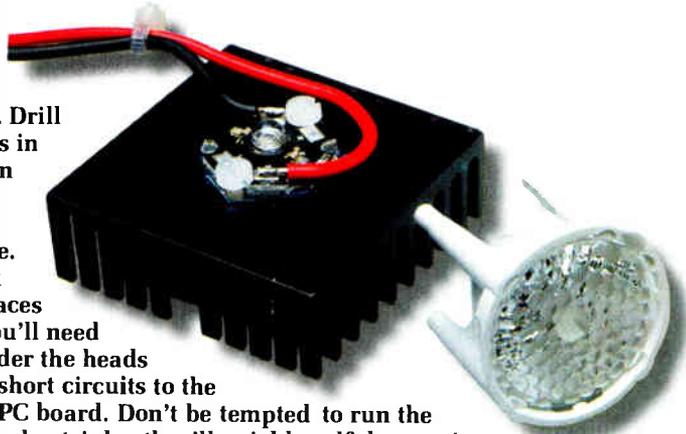

Using the absolute maximum LED junction temperature of 135°C and an ambient temperature of 25°C, the junction to ambient thermal resistance is:

$$\begin{aligned}R_{TH_{J-A}} &= T_J - T_A / P_D \\ &= 135^\circ\text{C} - 25^\circ\text{C} / 3.6\text{W} \\ &= 30.5^\circ\text{C/W}\end{aligned}$$

Next, subtract the junction to board resistance ($R_{TH_{J-B}}$) listed in the datasheet to find the board to ambient thermal resistance. For most board-mounted Stars, this is 17°C/W:

$$\begin{aligned}R_{TH_{B-A}} &= R_{TH_{J-A}} - R_{TH_{J-B}} \\ &= 30.5^\circ\text{C/W} - 17^\circ\text{C/W} \\ &= 13.5^\circ\text{C/W}\end{aligned}$$

The result is the maximum allowable heatsink resistance needed to keep the LED junction temperature at or below the maximum rating at 25°C ambient.

The 48 × 48mm finned heatsink shown in the adjacent photo was originally designed for cooling Intel 486 and Motorola 68000 series microprocessors but works equally well here. According to our rough calculations, it has a thermal resistance of

about 8°C/W when operated in free air in the vertical position.

So far, we've assumed operation up to the maximum LED junction temperature of 135°C. However, when operated continuously at this maximum, LED light output decreases quite markedly over time. To achieve the 20,000 hours at 50% lumen maintenance figure shown in the datasheets, Lumileds specifies a lower maximum junction temperature of 90°C.

Reworking the figures for this lower temperature, you can see that a heatsink resistance of 1°C/W would be required. This would be difficult to implement in practice, necessitating a bulky heatsink, perhaps even with forced-air cooling.

For maximum life with a realistic heatsink size, the answer is to drive the LEDs at reduced current. For this reason, Lumileds also characterises the 3W Star for operation at 700mA, stating lumen maintenance of 70% after 50,000 hours at the lower temperature figure.

The maximum heatsink resistance needed in this case is 8.8°C/W at 25°C ambient, meaning our chosen heatsink barely makes the grade. If operation in the horizontal position is required or higher ambient temperatures are likely, then a lower resistance heatsink is needed.

The above information is also applicable to the 5W Star, although its life versus junction temperature figures are radically different to the 3W version. Note also that it's rated for a maximum of 700mA forward current and has a higher forward voltage than the 3W device. Refer to the individual device datasheets for more information.

To learn all about heatsinking, check out the 'Thermal Design using Luxeon Power Light Sources' application brief, available from the Lumileds website at www.lumileds.com.

EPE

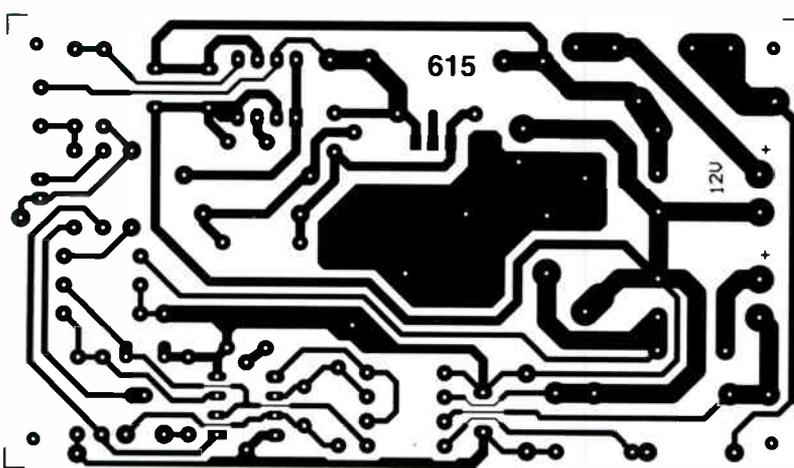


Fig.7: this is the full-size etching pattern for the PC board.

FREE ENTRY COMPETITION



In-Circuit Debugging

Win a Microchip PICkit 2 Debug Express Kit!

Everyday Practical Electronics is offering its readers the chance to win one of three Microchip PICkit 2 Debug Express Kits! The kit supports Microchip's popular PICkit™2 development programmer by allowing in-circuit debugging of selected PIC microcontrollers. This enables engineers to begin development with PIC microcontrollers for a very low initial investment. The kit connects to any personal computer via USB, and its in-circuit debugging features include halt, single step and setting a breakpoint.

The Kit includes Microchip's 44-pin PIC16F917 Flash microcontroller demo board, the PICkit 2 programmer, USB cable and software CDs, including Microchip's free MPLAB® IDE, integrated development environment, and a host of other software - enabling new users to easily get started with an embedded control design.

For the chance to win a PICkit 2 Debug Express Kit, log onto www.microchip-comp.com/epe-pickit2debug and enter your details in the online entry form.

INTERFACE

Robert Penfold



ARE YOUR SOFTWARE PROGRAMS VISTA COMPATIBLE?

AT the time of writing this piece, the new Windows Vista operating system had just been launched by Microsoft. From the point of view of writing software for use with PC add-ons, the launch of Windows XP, a little over five years ago, was not particularly helpful.

In fact, it was quite troublesome, and produced problems with many existing programs that had worked well with Windows 98 and ME. New programs written using tried and tested methods often failed to operate with Windows XP. On the plus side, existing programming languages such as Visual BASIC 5 and 6 worked well under this operating system.

Losing Touch

The main problem with the new Windows XP was that it did not permit direct control of the addresses in the input/output map. This meant that writing directly to hardware at its output address did not work. Reading direct from an input address was equally ineffective. In order to ensure that conflicts were avoided, the operating system required read and write operations to the ports to be handled via its official and well controlled routes.

This was not actually new, and was a requirement when using Windows NT or 2000. Windows XP was the upgrade path for these operating systems, and for Windows 98 and ME. Upgrading from Windows NT or 2000 was relatively straightforward, but there were big differences between Windows 98/ME and Windows XP.

Programs that handled the ports directly worked well under Windows 98/ME, but at best with Windows XP they failed to control or read from the add-on gadget. Some programs ground to a halt with error messages while others crashed the computer.

Ways around this problem were found, and on the face of it these should work as well with Windows Vista as they did with XP. With some methods this is probably the case, but it would be naïve to expect all programs for PC add-ons that worked perfectly well with Windows XP will perform equally flawlessly under Vista. Apart from this specific issue, there are other potential problems due to general compatibility matters.

Runtime Modules

An important point to keep in mind here is that some programming languages do not produce fully-compiled programs, and Visual BASIC 6 is certainly in this category. Some programs written in Visual BASIC 6, and other versions of this programming language, seem remarkably small when they are compiled. The usual reason for this is that the program is relying on one or more runtime modules, which are mostly in the form of dynamic link library

(DLL) files, but there are a few other types, such as ActiveX (OCX) files.

Many of these runtime modules are supplied with a modern version of Windows and are included as part of a standard installation. Consequently, there is normally no need to distribute them with Visual BASIC programs.

Unfortunately, only a subset of tried and tested runtime modules are supplied with Windows Vista. This leaves a substantial number of modules that are also tried and tested with Vista, but are not supplied as part of the Vista operating system.

A full list of the modules supplied as part of Vista, plus a list of those that have been tested but are not included, can be found at this web page:

<http://msdn2.microsoft.com/en-us/vbrun/ms788708.aspx>

One notable omission from the runtime modules supplied with Vista is the **mscomm32.ocx** ActiveX component that enables Visual BASIC 6 to access the serial (COM) ports. However, this module is in the list of tried and tested modules not included with Vista, so programs that use this as a means of reading and writing to the serial ports should work properly in this respect when used with Windows Vista. This includes some software featured in past issues of *EPE*.

As far as I am aware, this module was not included with earlier versions of Windows either, so the situation has not really changed. It used to be necessary to distribute this component with any programs that utilised it, and it still is necessary to do so. This component was only supplied with the more upmarket versions of Visual BASIC, which also included a license to distribute it with any software that required its facilities.

It Just Works

The web page mentioned previously also includes some general information about the Vista compatibility of Visual BASIC 6 itself and programs written using this programming language. Microsoft is committed to 'it just works' compatibility, which is presumably meant to be taken literally. This apparently

applies to the Visual BASIC 6 program itself, as well as any programs written using this language.

Third-Party

Of course, there are numerous third-party runtime modules for use with Visual BASIC and other PC programming languages. Understandably, Microsoft takes no responsibility for how well (or otherwise) these operate under Windows Vista. It is up to the producers of these modules to check their compatibility and, where necessary, modify them to suit the new operating system.

Many of the programs featured in the *Interface* series rely on **Inpout32.dll** to enable Visual BASIC 6 programs to perform direct read and write operations with devices in the input/output map. The supporting software for some *EPE* projects also requires the services of this module. It provides programming languages such as Visual BASIC 6 with the **Inp** and **Out** commands that were at one time a standard part of most programming languages, but are hardly ever included these days. Unfortunately, **Inpout32.dll** does not seem to work at all with Windows Vista. This is perhaps a bit surprising, since it contacts the hardware via approved routes and works perfectly with Windows XP.

The Visual BASIC 6 programs that I have tried all worked perfectly in the sense that everything appeared to be operating correctly on the screen. Fig.1 shows the result when using a Vista based system to run the power supply program featured in the previous *Interface* article. It all seems to be working properly and there are no error messages, but it has no

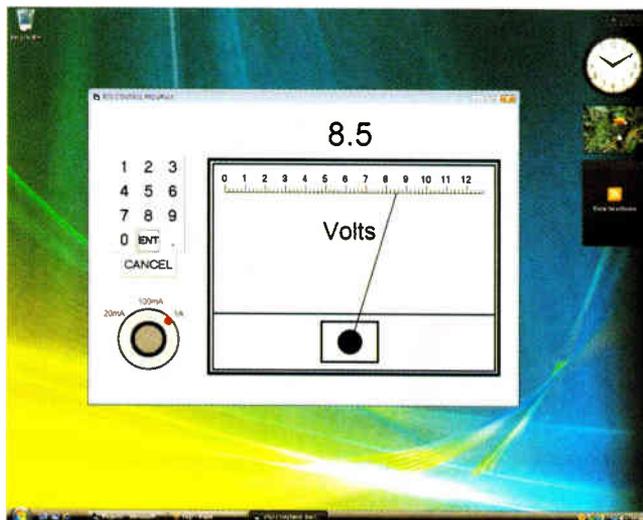


Fig.1: The power supply program runs perfectly under Windows Vista, apart from the fact that it does not write any data to the printer port.

effect on the power supply unit driven from the printer port. Everything worked fine when using the same hardware and program with Windows XP as the operating system.

As yet, there is little information on the Internet regarding Windows Vista and **Inpout32.dll**, but it would appear that it does not work with 32-bit or 64-bit versions of Vista. Possibly, in due course, someone will produce a new version of **Inpout32.dll** that is fully Vista compatible. In the meantime though, programs that rely on this component are unusable with systems running Windows Vista.

The inevitable conclusion from this is that Visual BASIC 6 programs have good compatibility with Windows Vista, but there can be problems with any that are reliant on some form of third-party add-on. It is unlikely that there will be any problems with a Visual BASIC 6 program that uses Microsoft's **mscomm32.ocx** ActiveX control to provide communication with the serial ports. With non-Microsoft it is a different matter, and it could be necessary to obtain an updated module.

Of course, there should be no problems with incompatible programs when using a

BASIC 6 installed, but an error message is produced each time it is launched.

However, once the program is 'up and running' it does seem to run all right when producing simple applications (Fig.3). Apart from any contentious add-ons, it produces compiled programs that seem to run well under Windows XP or Vista. Of course, things might not operate quite as smoothly when producing more advanced pieces of software.

Progress?

It is noticeable that the more PC hardware and software progresses, the harder it

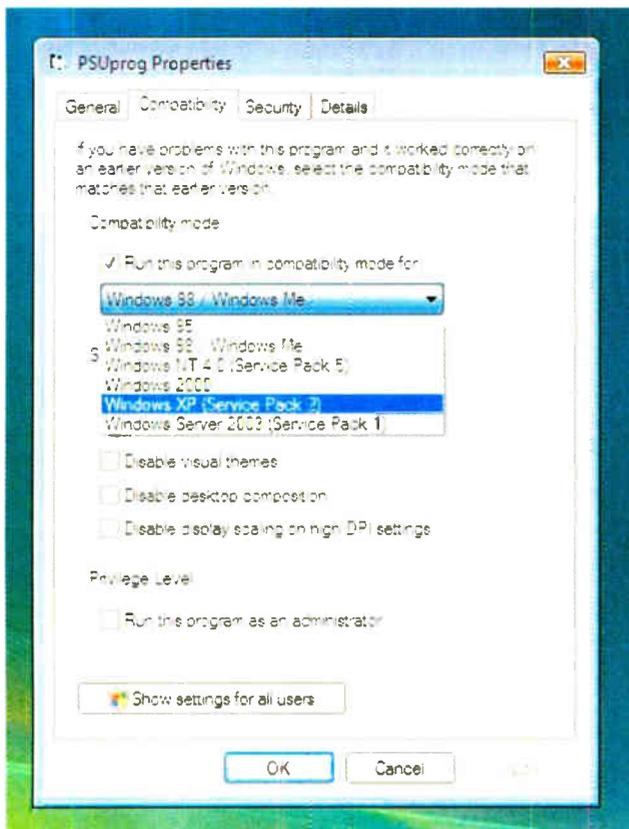


Fig.2: Windows Vista provides compatibility modes for programs written to operate with previous versions of Windows. In practice, the degree of compatibility provided is sometimes inadequate

Setting Compatibility

There is a facility in Windows Vista that enables programs written for earlier versions of Windows to be run in a so-called compatibility mode. The idea is for Vista to run the program in the same way that it would be run in some previous version of Windows. This is essentially the same feature that was introduced in Windows XP, and like its predecessor, it is not always effective.

The compatibility level of a program can be altered by locating the program (EXE) file using Windows Explorer and right-clicking its entry. Then select Properties from the pop-up menu, followed by the Compatibility tab in the new window that appears.

If there is no compatibility tab, run the program, close it, and then try again. The required operating system is then selected from the drop-down menu (Fig.2). Unfortunately, this does not give sufficient compatibility to make **Inpout32.dll** usable with Windows Vista, but it might give better results with other compatibility problems.

problems due to bugs that have yet to be corrected, the compiled programs are guaranteed to be fully compatible with Windows Vista. Using the built-in facilities to communicate via the serial port should produce programs that run equally well under Windows XP and Vista.

Once again though, compatibility is not guaranteed if a third-party add-on is used. Using an old add-on with a modern programming language will not remove any incompatibility problems. Using **Inpout32.dll** with modern programming languages tends to be a bit awkward anyway, but even if you do manage to do so, this ploy will certainly not produce programs that are Vista compatible.

VB6 Under Vista

Trying to install Visual BASIC 6 on a PC running Windows Vista produces warning messages, some of which indicate that the operating system 'thinks' that it is actually Visual C++ that is being installed. With persistence it is possible to get Visual

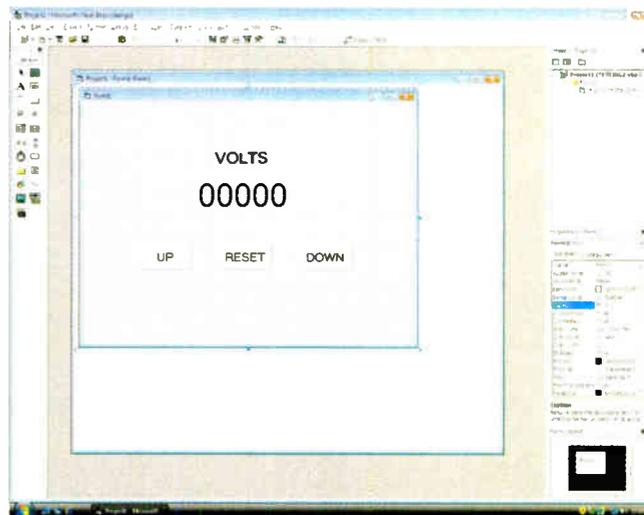


Fig.3: Visual BASIC 6 can be installed and run under Windows Vista, but only just. This is in line with Microsoft's 'it just works' compatibility for this software

more recent programming language, such as Visual C# or Visual BASIC 2005 Express. These programming languages were designed to provide compatibility with Windows Vista. Apart from any

becomes to use a PC with simple add-on projects. In most respects Visual BASIC is well suited to producing programs for user add-ons, but it requires some supporting software in order to access the input/output ports.

Recent versions of Visual BASIC have been aimed at those producing complex applications, which makes them less accommodating when producing simple control software for a PC hardware project. On the hardware side of things, the gradual demise of the ISA bus plus the phasing out of the standard serial and parallel ports has made things even more difficult.

While it is probably a bit early to proclaim simple interfacing to the serial and parallel ports as a thing of the past, it seems unlikely that this method will be a practical proposition for very much longer. In the not too distant future it will probably be a matter of using USB or not bothering at all. Unfortunately, using a USB port is never likely to be as straightforward as directly accessing a port in the input/output map.



Our Full Colour



Be the first one on the block to get hold of our brand new, expanded and fully updated colour catalogue. It's just bursting with new products across many ranges. Check it out at www.jaycarelectronics.co.uk/catalogue



POST AND PACKING CHARGES:

Order Value	Cost	Order Value	Cost
£20 - £49.99	£5	£200 - £499.99	£30
£50 - £99.99	£10	£500+	£40
£100 - £199.99	£20		

Max weight 12lb (5kg). Heavier parcels POA. Minimum order £20.
Note: Products are dispatched from Australia, so local customs duty and taxes may apply.

Magnetic Cartridge Pre-amp

KC-5433 £11.75 + post & packing

This kit is used to amplify the 3-4mV signals from a phono cartridge to line level, so you can use your turntable with the CD or tuner inputs on your Hi-Fi amplifier - most modern amps don't include a phono input any more. Dust off the old LP collection or use it to record your LPs on to CD. The design is suitable for 12" LPs, and also allows for RIAA equalisation of all the really old 78s. Please note that the input sensitivity of this design means it's only suitable for moving-magnet, not moving-coil cartridges. Kit includes PCB with overlay and all electronic components.

- Requires 12VAC power



DC Relay Switch

KC-5434 £4.50 + post & packing

An extremely useful and versatile kit that enables you to use a tiny trigger current - as low as 400µA at 12V to switch up to 30A at 50VDC. It has an isolated input, and is suitable for a variety of triggering options. The kit includes PCB with overlay and all electronic components with clear English instructions.



Car Air Conditioner Controller Kit

KC-5437 £11.75 + post & packing

This kit stops the air conditioner in your car from taking engine power under acceleration. It will allow the compressor to run with low throttle even when the cabin temperature setting has been reached and will automatically switch the compressor off at idle. It also features an override switch, an LED function indicator. Kit supplied with PCB with overlay and all electronic components with clear English instructions.

Radar Speed Gun

KC-5429 £29.00 + post & packing

This Doppler radar gun reads speed in km/h or mph up to 250 km/h or 155 mph. It has a resolution of 1 km/h or 1 mph with an accuracy of 1%, and also has a hold switch so you can freeze the reading. There's a jiffy box to mount the electronics in, and the enclosure for the radar gun assembly is made from 2 x coffee tins or similar. Details included. Kit includes PCB and all specified components with clear English instructions.

- Requires 12VDC power.



Programmable High Energy Ignition System

KC-5442 £26.25 + post & packing


This advanced and versatile ignition system can be used on both two & four stroke engines. The system can be used to modify the factory ignition timing or as the basis for a stand-alone ignition system with variable ignition timing, electronic coil control and anti-knock sensing.

Features:

- Timing retard & advance over a wide range
- Suitable for single coil systems
- Dwell adjustment
- Single or dual mapping ranges
- Max & min RPM adjustment
- Optional knock sensing
- Optional coil driver
- Kit supplied with PCB, and all electronic components.



Recommended box UB3
HB-6013 £1.05

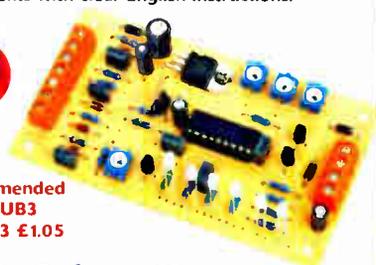


Short Circuits 1 Learning System

KJ-8502 £11.95 + post & packing

Short Circuits 1 uses a learning system designed around a baseboard and template where all components are mounted and connected using our exclusive spring system. The templates show exactly where each component goes and almost guarantees success. The 20+ projects are fun & simple to build and all components are included.

- 96 pages in full colour
- 275 x 205mm

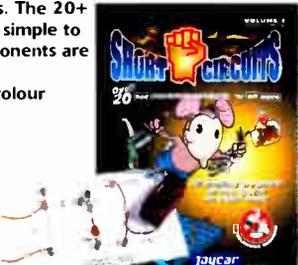Projects include:
Short circuit tester
Magic eye alarm
Police siren
Electronic organ
and many more.



Ignition Coil Driver

KC-5443 £13.00 + post & packing

Add this ignition coil driver to the KC-5442 Programmable Ignition System and you have a complete stand-alone ignition system that will trigger from a range of sources including points, Hall Effect sensors, optical sensors, or the 5 volt signal from the car's ECU. Kit includes PCB with overlay and all specified components.

- Kit supplied with PCB, and all electronic components.

Knock Sensor

KC-5444 £5.00 + post & packing

Add this option to your KC-5442 Programmable High Energy Ignition system and the unit will automatically retard the ignition timing if knocking is detected. Ideal for high performance cars running high octane fuel. Requires a knock sensor which is cheaply available from most auto recyclers.

- Kit supplied with PCB, and all electronic components.

Due in June


Fuel Cut Defeater Kit

KC-5439 £6.00 + post & packing

This simple kit enables you to defeat the factory fuel cut signal from your car's ECU and allows your turbo charger to go beyond the typical 15-17psi factory boost limit. Note: Care should be taken to ensure the boost levels and fuel mixture don't reach an unsafe level.

- Kit supplied with PCB, and all electronic components.

Recommended box UB5
HB-6016

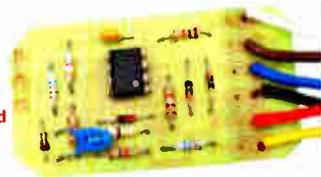

High Range Adjustable Temperature Switch for Cars

KC-5376 £22.75 + post & packing

This temperature switch can be set anywhere up to 1200°C, so it is extremely versatile. The relay can be used to trigger an extra thermo fan on an intercooler, a sensor near your turbo manifold to trigger water spray cooling, or a simple buzzer to indicate high temperature. The LCD displays the temperature constantly and can easily be dash mounted. Kit included PCB with overlay and all electronic components with clear English instructions.



www.jaycarelectronics.co.uk

Catalogue for 2007 has arrived!

Everyday Practical Electronics Feature Kits

Everyday Practical Electronics Magazine has been publishing a series of popular kits by the acclaimed Silicon Chip Magazine Australia. These projects are brilliantly designed 'bullet proof' and already tested down under.

All Jaycar kits are supplied with specified board components, quality fibreglass tinned PCBs and have clear English instructions. Watch this space for future featured kits.

Luxeon Star LED Driver Kit

KC-5389 £9.75 + post & packing

Luxeon high power LEDs are some of the brightest LEDs available in the world. They offer up to 120 lumens per unit, and will last up to 100,000 hours! This kit allows you to power the fantastic 1W, 3W, and 5W Luxeon Star LEDs from 12VDC. Now you can take advantage of these fantastic LEDs in your car, boat, or caravan.

- Kit supplied with PCB, and all electronic components.




As published in this month's Everyday Practical Electronics Magazine!

SMS Controller Module Kit

KC-5400 £15.95 + post & packing

Control appliances or receive alert notification from anywhere. By sending plain text messages this kit will allow you to control up to eight devices. It can also monitor four digital inputs. It works with old Nokia handsets such as the 5110, 6110, 3210, and 3310, which can be bought inexpensively if you do not already own one. Kit supplied with PCB, pre-programmed microcontroller and all electronics components with clear English instructions.

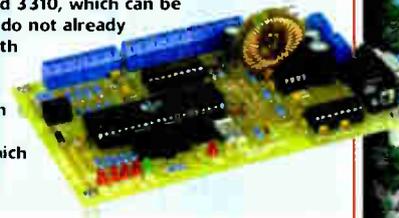- Requires a Nokia data cable which can be readily found in mobile phone accessory stores.



Three Stage FM Transmitter

KJ-8750 £6.50 + post & packing

This is a Three-Stage radio transmitter that is so stable you could use it as your personal radio station and broadcast all over your house. Great for experiments in audio transmission. It includes a microphone but you can transmit other material as well. Includes a mic, PCB with overlay and all other parts.

- Requires 9V battery (not included)
- Instructions included in kit




Delta Throttle Timer Kit

KC-5373 £7.95 + post & packing

It will trigger a relay when the throttle is depressed or lifted quickly. There is a long list of uses for this kit, such as automatic transmission switching of economy to power modes, triggering electronic blow-off valves on quick throttle lifts and much more. It is completely adjustable, and uses the output of a standard throttle position sensor. Kit supplied with PCB and all electronic components.

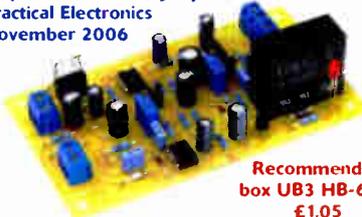- As published in Everyday Practical Electronics November 2006



Recommended box UB3 HB-6013 £1.05

Automotive Courtesy Light Delay

KC-5392 £5.95 + post & packing

This kit provides a time delay in your vehicle's interior light, for you to buckle-up your seat belt and get organised before the light dims and fades out. It has a 'soft' fade-out after a set time has elapsed, and has universal wiring. Kit supplied with PCB with overlay, all electronics components and clear English instructions.

- As published in Everyday Practical Electronics February 2007

Recommended box UB5 HB-6015 £0.83




Studio 350 High Power Amplifier Kit

KC-5372 £55.95 + post & packing

It delivers a whopping 350WRMS into 4 ohms, or 200WRMS into 8 ohms. Using eight 250V 200W plastic power transistors, it is super quiet, with a signal to noise ratio of -125dB(A) at full 8 ohm power. Harmonic distortion is just 0.002%, and frequency response is almost flat (less than -1dB) between 15Hz and 60kHz. Kit supplied in short form with PCB and electronic components. Kit requires heatsink and +/- 70V power supply (a suitable supply is described in the instructions).

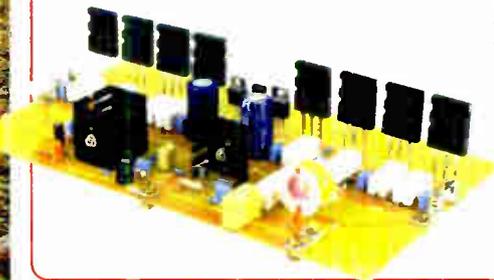- As published in Everyday Practical Electronics October & November 2006




Smart Card Reader and Programmer Kit

KC-5361 £15.95 + post & packing

Program both the microcontroller and EEPROM in the popular gold, silver and emerald wafer cards. Card used needs to conform to ISO-7816 standards, which includes ones sold by Jaycar. Powered by 9-12 VDC wall adaptor or a 9V battery. Instructions outline software requirements that are freely available on the internet. Kit supplied with PCB, wafer card socket and all electronic components. PCB measures: 141 x 101mm.

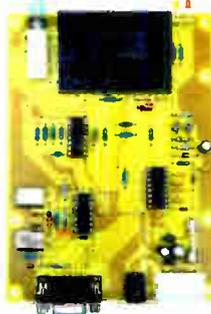- As published in Everyday Practical Electronics May 2006
- Requires 9-12VDC wall adaptor (Maplin #UG01B £13.99)



Jaycar cannot accept responsibility for the operation of this device, its related software, or its potential to be used in relation to illegal copying of smart cards in cable TV set top boxes.

Audio Video Booster Kit

KC-5350 £31.95 + post & packing

This kit will boost your video and audio signals preserving them for the highest quality transmission to your projector or large screen TV. It boosts composite, S-Video, and stereo audio signals. Kit includes case with silkscreened and punched panels, PCB and all electronic components.

- As published in Everyday Practical Electronics March 2006



Requires 9VAC wall adaptor (Maplin #GU09K £9.99).

Log on to www.jaycarelectronics.co.uk/catalogue for your FREE catalogue!

0800 032 7241

(Monday - Friday 09.30 to 17.30 GMT + 10 hours only). For those who want to write: 100 Silverwater Rd Silverwater NSW 2128 Sydney AUSTRALIA

All prices in £ Stg



Jaycar Electronics

www.jaycarelectronics.co.uk

EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS

ELECTRONICS PROJECTS




Logic Probe testing

Electronic Projects is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included.

The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.


ELECTRONICS CAD PACK

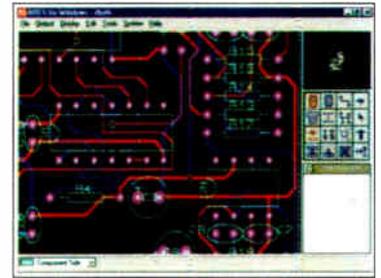

PCB Layout

Electronics CADPACK allows users to design complex circuit schematics, to view circuit animations using a unique SPICE-based simulation tool, and to design printed circuit boards. CADPACK is made up of three separate software modules. (These are restricted versions of the full Labcenter software.) **ISIS Lite** which provides full schematic drawing features including full control of drawing appearance, automatic wire routing, and over 6,000 parts. **PROSPICE Lite** (integrated into ISIS Lite) which uses unique animation to show the operation of any circuit with mouse-operated switches, pots, etc. The animation is compiled using a full mixed mode SPICE simulator. **ARES Lite** PCB layout software allows professional quality PCBs to be designed and includes advanced features such as 16-layer boards, SMT components, and an autorouter operating on user generated Net Lists.


ELECTRONIC CIRCUITS & COMPONENTS V2.0

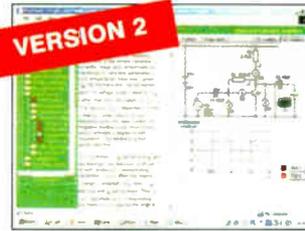

Circuit simulation screen

Provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals**: units & multiples, electricity, electric circuits, alternating circuits. **Passive Components**: resistors, capacitors, inductors, transformers. **Semiconductors**: diodes, transistors, op.amps, logic gates. **Passive Circuits**. **Active Circuits**. The **Parts Gallery** will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.

ANALOGUE ELECTRONICS V2

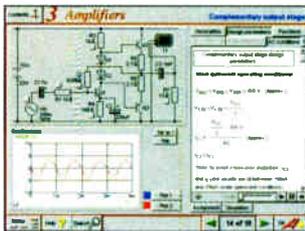

Complimentary output stage

Analogue Electronics is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits.

Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections), **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections). **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections). **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

ROBOTICS & MECHATRONICS




Case study of the Milford Instruments Spider

Robotics and Mechatronics is designed to enable hobbyists/students with little previous experience of electronics to design and build electromechanical systems. The CD-ROM deals with all aspects of robotics from the control systems used, the transducers available, motors/actuators and the circuits to drive them. Case study material (including the NASA Mars Rover, the Milford Spider and the Furby) is used to show how practical robotic systems are designed. The result is a highly stimulating resource that will make learning, and building robotics and mechatronic systems easier. The Institutional versions have additional worksheets and multiple choice questions.

- Interactive Virtual Laboratories
- Little previous knowledge required
- Mathematics is kept to a minimum and all calculations are explained
- Clear circuit simulations

DIGITAL ELECTRONICS V2.0

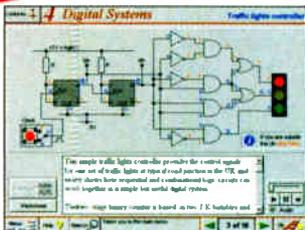


Virtual laboratory – Traffic Lights

Digital Electronics builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (opposite), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen.

Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units. Sections on Boolean Logic and Venn diagrams, displays and chip types have been expanded in Version 2 and new sections include shift registers, digital fault finding, programmable logic controllers, and microcontrollers and microprocessors. The Institutional versions now also include several types of assessment for supervisors, including worksheets, multiple choice tests, fault finding exercises and examination questions.

ANALOGUE FILTERS

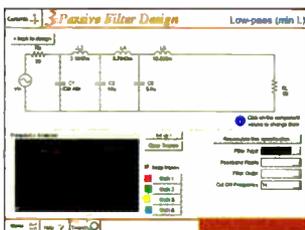

Filter synthesis

Analogue Filters is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev

PRICES

Prices for each of the CD-ROMs above are:

(Order form on third page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)


Hobbyist/Student.....	£45 inc VAT
Institutional (Schools/HE/FE/Industry).....	£99 plus VAT
Institutional 10 user (Network Licence)	£249 plus VAT
Site Licence.....	£499 plus VAT

VERSION 3 PICmicro MCU DEVELOPMENT BOARD

Suitable for use with the three software packages listed below.

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices from the 12, 16 and 18 series PICmicro ranges. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

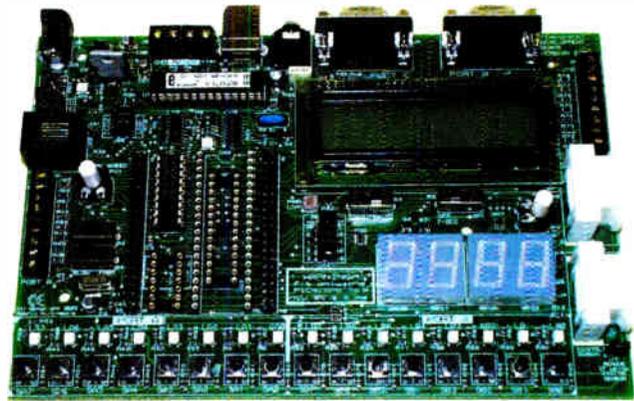- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 16 individual I.e.d.s, quad 7-segment display and alphanumeric I.c.d. display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- USB programmable
- Can be powered by USB (no power supply required)



£158 including VAT and postage

supplied with USB cable and programming software

SOFTWARE


Suitable for use with the Development Board shown above.



ASSEMBLY FOR PICmicro V3 (Formerly PICtutor)

Assembly for PICmicro microcontrollers V3.0 (previously known as PICtutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes. The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller. This is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.

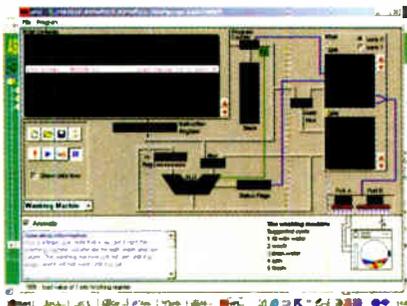


'C' FOR PICmicro VERSION 3

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

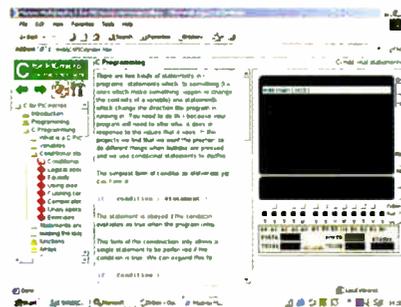- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running Windows 98, NT, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.

FLOWCODE FOR PICmicro V3

Flowcode is a very high level language programming system for PICmicro microcontrollers based on flowcharts. Flowcode allows you to design and simulate complex robotics and control systems in a matter of minutes.

Flowcode is a powerful language that uses macros to facilitate the control of complex devices like 7-segment displays, motor controllers and I.c.d. displays. The use of macros allows you to control these electronic devices without getting bogged down in understanding the programming.

Flowcode produces MPASM code which is compatible with virtually all PICmicro programmers. When used in conjunction with the Version 3 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols (ISO5807)
- Full on-screen simulation allows debugging and speeds up the development process
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- New features in Version 3 include 16-bit arithmetic, strings and string manipulation, improved graphical user interface and printing, support for 18 series devices, pulse width modulation, I2C, new ADC component and many more.



PRICES

Prices for each of the CD-ROMs above are:

(Order form on next page)


(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student
 Institutional (Schools/HE/FE/Industry)
 Institutional/Professional 10 user (Network Licence)
 Site Licence
 Flowcode 10 user (Network Licence)
 Flowcode 50 user (Network Licence)

£45 inc VAT
 £99 plus VAT
 £300 plus VAT
 £599 plus VAT
 £350 plus VAT
 £699 plus VAT

TEACH-IN 2000 – LEARN ELECTRONICS WITH EPE

EPE's own Teach-In CD-ROM, contains the full 12-part Teach-In 2000 series by John Becker in PDF form plus the Teach-In interactive software (Win 95, 98, ME and above) covering all aspects of the series. We have also added Alan Winstanley's highly acclaimed Basic Soldering Guide which is fully illustrated and which also includes Desoldering. The Teach-In series covers: Colour Codes and Resistors, Capacitors, Potentiometers, Sensor Resistors, Ohm's Law, Diodes and L.E.D.s, Waveforms, Frequency and Time, Logic Gates, Binary and Hex Logic, Op.amps, Comparators, Mixers, Audio and Sensor Amplifiers, Transistors, Transformers and Rectifiers, Voltage Regulation, Integration, Differentiation, 7-segment Displays, L.C.D.s, Digital-to-Analogue. Each part has an associated practical section and the series includes a simple PC interface (Win 95, 98, ME ONLY) so you can use your PC as a basic oscilloscope with the various circuits.

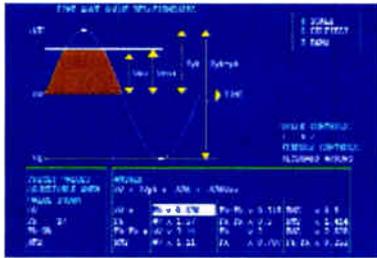

Sine wave relationship values

FREE TWO BOOKLETS PLUS CD-ROM WITH TEACH-IN 2000




A hands-on approach to electronics with numerous breadboard circuits to try out.

£12.45 including VAT and postage. Requires Adobe Acrobat (available free from the Internet – www.adobe.com/acrobat).

FREE WITH EACH TEACH-IN CD-ROM – Understanding Active Components booklet, Identifying Electronic Components booklet and The Best Of Circuit Surgery CDROM.

DIGITAL WORKS 3.0

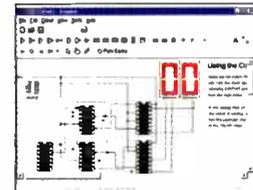

Counter project

Digital Works Version 3.0 is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability ● Software for simulating digital logic circuits ● Create your own macros – highly scalable ● Create your own circuits, components, and i.c.s ● Easy-to-use digital interface ● Animation brings circuits to life ● Vast library of logic macros and 74 series i.c.s with data sheets ● Powerful tool for designing and learning. **Hobbyist/Student £45 inc. VAT. Institutional £99 plus VAT. Institutional 10 user £249 plus VAT. Site Licence £599 plus VAT.**

NEW PROJECT DESIGN WITH CROCODILE TECHNOLOGY

An Interactive Guide to Circuit Design

An interactive CD-ROM to guide you through the process of circuit design. Choose from an extensive range of input, process and output modules, including CMOS Logic, Op-Amps, PIC/PICAXE, Remote Control Modules (IR and Radio), Transistors, Thyristors, Relays and much more. Click Data for a complete guide to the pin layouts of i.c.s, transistors etc. Click More Information for detailed background information with many animated diagrams. Nearly all the circuits can be instantly simulated in Crocodile Technology* (not included on the CD-ROM) and you can customise the designs as required.

WHAT'S INCLUDED

Light Modules, Temperature Modules, Sound Modules, Moisture Modules, Switch Modules, Astables including 555, Remote Control (IR & Radio), Transistor Amplifiers, Thyristor, Relay, Op-Amp Modules, Logic Modules, 555 Timer, PIC/PICAXE, Output Devices, Transistor Drivers, Relay Motor Direction & Speed Control, 7 Segment Displays. Data sections with pinouts etc., Example Projects, Full Search Facility, Further Background Information and Animated Diagrams.

Runs in Microsoft Internet Explorer

*All circuits can be viewed, but can only be simulated if your computer has Crocodile Technology version 410 or later. A free trial version of Crocodile Technology can be downloaded from: www.crocodile-clips.com. Animated diagrams run without Crocodile Technology.

Single User **£39.00 inc. VAT.**

Multiple Educational Users (under 500 students) **£59.00 plus VAT.** Over 500 students **£79.00 plus VAT.**

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)



ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 JPG images of electronic components. This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details). Also contains a FREE 30-day evaluation of Paint Shop Pro 6 – Paint Shop Pro image editing tips and on-line help included!

Price **£19.95 inc. VAT**



Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 95/98/NT/2000/ME/XP, mouse, sound card, web browser.

Please send me: CD-ROM ORDER FORM

- Electronic Projects
- Electronic Circuits & Components V2.0
- Analogue Electronics
- Digital Electronics V2.0
- Analogue Filters
- Electronics CAD Pack
- Robotics & Mechatronics
- Assembly for PICmicro V3
- 'C' for PICmicro V2
- Flowcode V3 for PICmicro
- Digital Works 3.0

Version required:

- Hobbyist/Student
- Institutional
- Institutional/Professional 10 user
- Site licence



- PICmicro Development Board V3 (hardware)

- Teach-In 2000 + FREE BOOK
- Electronic Components Photos
- Project Design – Single User
- Project Design – Multiple User (under 500 students)
- Project Design – Multiple User (over 500 students)

Note: The software on each version is the same, only the licence for use varies.

Full name:

Address:

Post code: Tel. No:

Signature:

I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

Please charge my Visa/Mastercard/Amex/Diners Club/Maestro: £

Valid From: Card expiry date:

Card No: Maestro Issue No.

Card Security Code (The last 3 digits on or just under the signature strip)

ORDERING

ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world
EU residents outside the UK add £5 for airmail postage per order

Institutional, Multiple User and Deluxe Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU (European Union) country, then add 17½% VAT or provide your official VAT registration number).

Send your order to:

Direct Book Service
Wimborne Publishing Ltd
408 Wimborne Road East
Ferndown, Dorset BH22 9ND

To order by phone ring

01202 873872. Fax: 01202 874562

Goods are normally sent within seven days

E-mail: orders@wimborne.co.uk

Online shop:

www.epemag.wimborne.co.uk/shopdoor.htm

Helping You Succeed



Does your business need more support and resources?

Successful organizations recognize the value of a strategic supplier relationship to help them deliver innovative products to their markets in a timely and cost-effective manner. Microchip Technology supports more than 45,000 customers worldwide, and we're

committed to helping you succeed. In addition to our high-performance silicon solutions, Microchip provides a long list of support functions that reduce time to market and lower your total system cost. And we have significantly expanded our local technical resources.

Use microchipDIRECT to:

Register today!



- Order directly from Microchip, 24 hours a day, 7 days a week with a credit card or credit line
- Receive competitive, direct volume pricing on all devices
- Check our product inventory
- Order broken reels at steep discounts
- Use fast and inexpensive production programming (now available)
- Place and maintain your order securely from any network connection
- Assign a PO number to your order
- Create a unique part number for any item ordered
- Receive e-mail notification of orders, deliveries, quote status and more

microchip
DIRECT
www.microchipdirect.com

Now
Pb-free!
RoHS Compliant

 **MICROCHIP**
www.microchip.com

The Microchip name and logo, PIC, and dsPIC are registered trademarks of Microchip Technology Incorporated in the USA and other countries. All other trademarks and registered trademarks are the property of their respective owners.
© Microchip Technology 2007. All rights reserved. ME156Eng/01.07

PIC POLYPHONIUM



- ✳ Polyphonic musical design
- ✳ PC-linked with on-screen musical score
- ✳ Create your own music
- ✳ LED display interface

By JOHN BECKER

Part 2: LED Display Control Interface

LAST MONTH in Part One we told how when visiting various steam fairs, the author has been fascinated by the grandeur of the sights and sounds of the superb showman's fairground organs there in abundance. We then described a PIC-controlled unit that commemorated them, generating polyphonic music in response to data keyed in as music scores on a PC and sent to the PIC's onboard memory devices.

Inside-out

This month we describe two means whereby the same data can be output to the outside world to control additional software or hardware, emulating perhaps some of the moving artifacts seen on such grand organs,

and which the user can design for themselves. We shall not describe the construction of such hardware, but shall now illustrate how the data can be used to control two different multi-bank arrays of LEDs.

Giant message display unit

First we describe how the Polyphonium's master control unit can be interfaced to the *EPE Giant LED Message Display* of November 2006, with just the addition of one chip – another PIC microcontroller, used in semi-slave mode. The circuit for this PIC is shown in Fig.4.

The circuit is purely for those who love to experiment. It and its software simply prove the basis for what some may wish to take further

in some way. No guidance is given on this point.

This PIC takes the 8-bit data output by IC1 pins RB0-RB7 in Fig.1 – last month. It ignores any note length bytes. Bytes containing notes and their octaves are converted to a serial data stream which is output at 9600 Baud to the first Slave PIC on the *Giant LED Message Display*. As

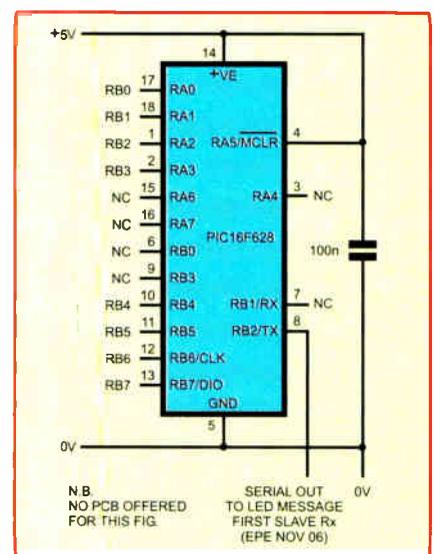


Fig.4: circuit diagram for a simple RS232 serial interface for the LED Display

Dedicated LED display

A separate dedicated LED display unit is now described, along with its constructional guidance. This uses a bank of LEDs which show the note, octave and relative on-time, as dictated by the type of note being played: crotchet, minim, quaver, etc. Pre-programmed PICs are available from Magenta Electronics. See their advert in this issue for contact details. The circuit diagram is shown in Fig.5.

Data is input to IC1's port pins RC0 to RC7 from the Polyphonium's control PIC IC2. The data has been split by that device so that it is output as pairs of separate data bytes. The first byte of the pair holds the note (A, B, C etc) in its LSN (least significant nibble, bits 3-0) and its octave in its MSN (most significant nibble, bits 7-4). The second byte of the pair holds the data value for the note's type.

There are twelve possible notes, including sharps, for each octave. A range of seven octaves is possible. There are 14 note types, seven principle ones, plus their dotted versions. In music, the principle types have a 'play duration' that doubles for each type


with the published unit, data is then rippled though all the slave displays used, in Moving Message mode, visually displaying the note and octave values.

The bytes coming in from the right, progressively become history along the chain of LEDs as the music and display progresses. Bytes which are a repeat of the previous one are ignored.

The PIC used is a PIC16F628, operating under its own internal clock oscillator running at 4MHz. Selected pins on PORTA and PORTB are used to input the data from IC1 in Fig.1, last month. Serial data is output at pin RB2. It is powered from the Polyphonium controller's 5V supply.

Software for this PIC (**PolyLEDMSGxx.asm**), is available from the *EPE* Downloads site (access via www.epemag.co.uk). The PIC is not available preprogrammed. No constructional details are offered for Fig.4, it could be assembled on stripboard.

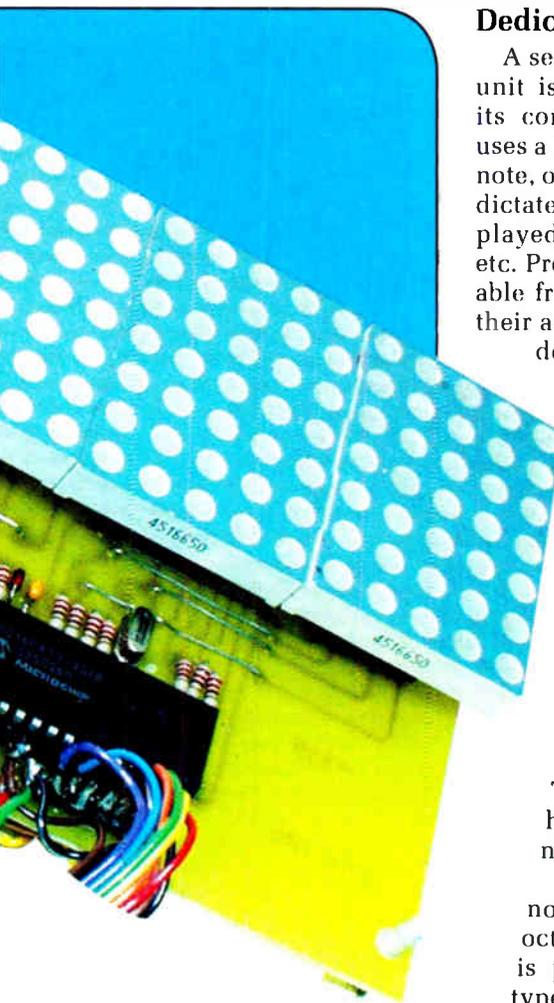To use the interface, remove the master control PIC in the unit, and connect the serial output from Fig.4 to the serial line previously served by that PIC, connecting to the first Slave circuit.



Last month's Master Control and Note Generator Unit

LED control circuit

The circuit for the LED control is shown in Fig.5 to the right of the control PIC, IC1. The columns are turned on via transistors TR1-TR12, which provide them with +5V when active. The LEDs in any row are turned on when their controlling voltage is at 0V and the corresponding column is at +5V. Resistors R1-R14 limit the current flowing through the LEDs when turned on, limited to the maximum total current that can be sunk by each of the PIC's Ports B and D (typically 200mA, as quoted in the PIC's datasheet).

The values of the resistors should not be decreased in order to attempt to increase the brilliance of the LEDs. The use of high-brightness LED modules is recommended. The multiplexing technique inherently

Parts List – PIC Polyphonium

LED Display Interface

- | | |
|---|---|
| 1 PC board, code 612, available from the <i>EPE PCB Service</i> , size 116.8 x 96.5mm | 1 PIC16F877-20 preprogrammed microcontroller – see text (IC1) |
| 1 plastic case, size and type to individual choice | |
| 3 2-inch, high brightness, 35-LED matrix modules (X1 to X3) | |
| 1 10MHz crystal (X4) | |
| 2 s.p.d.t. toggle switches (S1, S2) | |
| 6 14-pin DIL sockets – see text | |
| 1 40-pin DIL socket (IC1) | |
| Semiconductors | |
| 1 1N4148 signal diode (D1) | |
| 12 2N3904 <i>n</i> p <i>n</i> transistors (TR1 to TR12) | |
| | Capacitors |
| | 1 100n ceramic disc (C1) |
| | 2 10p ceramic disc (C2, C3) |
| | Resistors (0.25W 5%) |
| | 14 100Ω (R1 to R14) |
| | 1 1k (R15) |
| | 1 10k (R16) |
| | Multicoloured ribbon cable and connectors (see text); 1mm terminal solder pins; solder etc. |

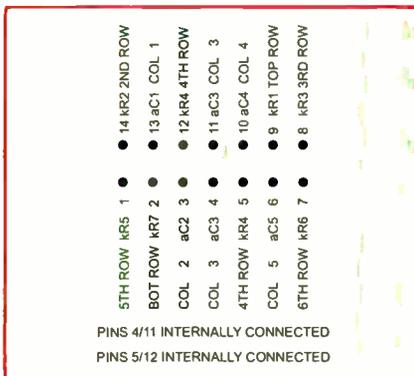


Fig.8: connections and their notations for the LED modules

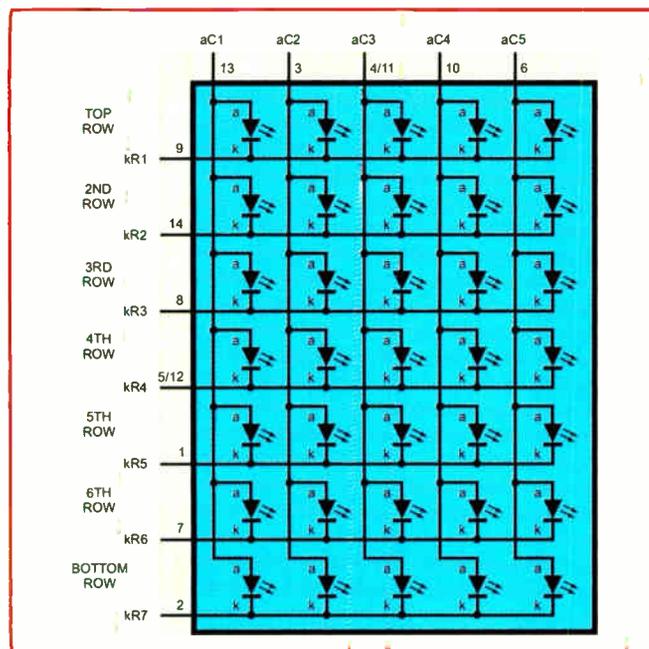


Fig.7: how the LEDs are connected within the modules

reduces the average brightness seen compared to that which would be expected from LEDs under constant power with the same voltage and ballast resistor values.


Switches S1 and S2 change the overall LED note length periods, in multiples of two, in binary order 2, 4, 8, 16.

As usual, provision has been made for the PIC to be programmed in situ if preferred, via the pins marked as TB1, in the author's standard order. Diode D1 and resistor R16 prevent distress to the +5V power line from the programming voltages, typically +14V and 0V are variously applied to PIC pin 1 (MCLR).

Construction

Component positioning and track layout details for the Display printed circuit board (PCB) are shown in Fig.9. This board is available from the *EPE PCB Service*, code 612.

As with Part One, assemble in order of ascending component size, starting off with the on-board link wires, noting that some go under the IC1 position. Use a DIL (dual-in-line) socket for this IC, also solder in two strips of 7-way DIL sockets cut in half lengthwise for the displays, then use another set of identical sockets plugged into the first. It is in these that the displays are ultimately inserted, raising their height to allow

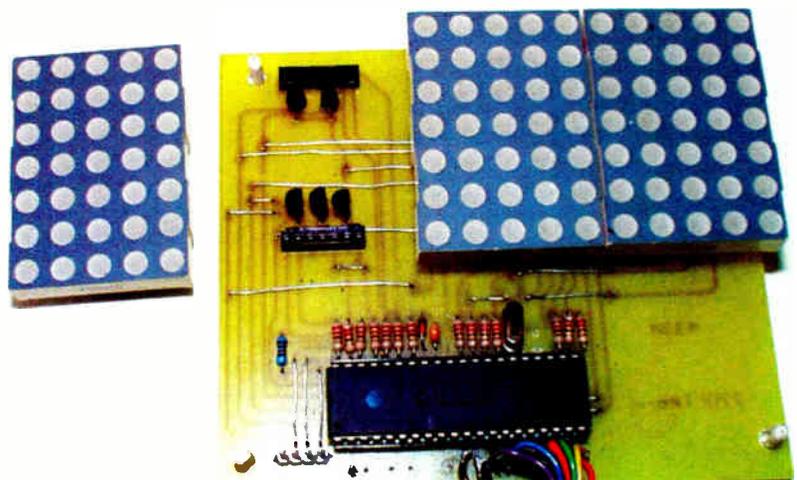

One of the LED matrix modules removed from the circuit board to reveal the driver transistors

Constructional Project

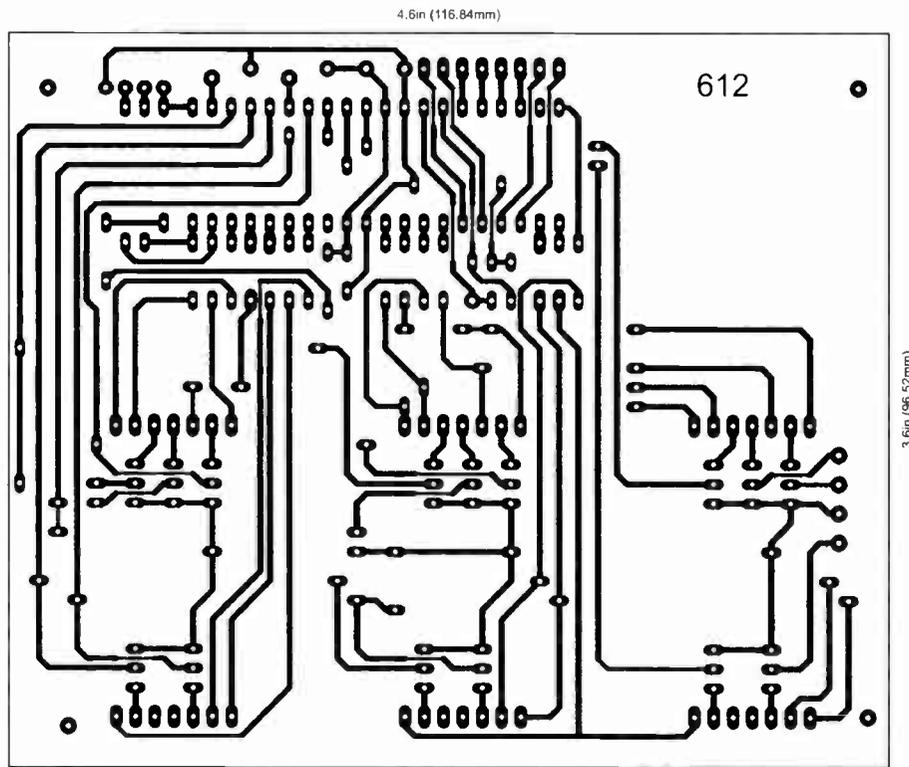
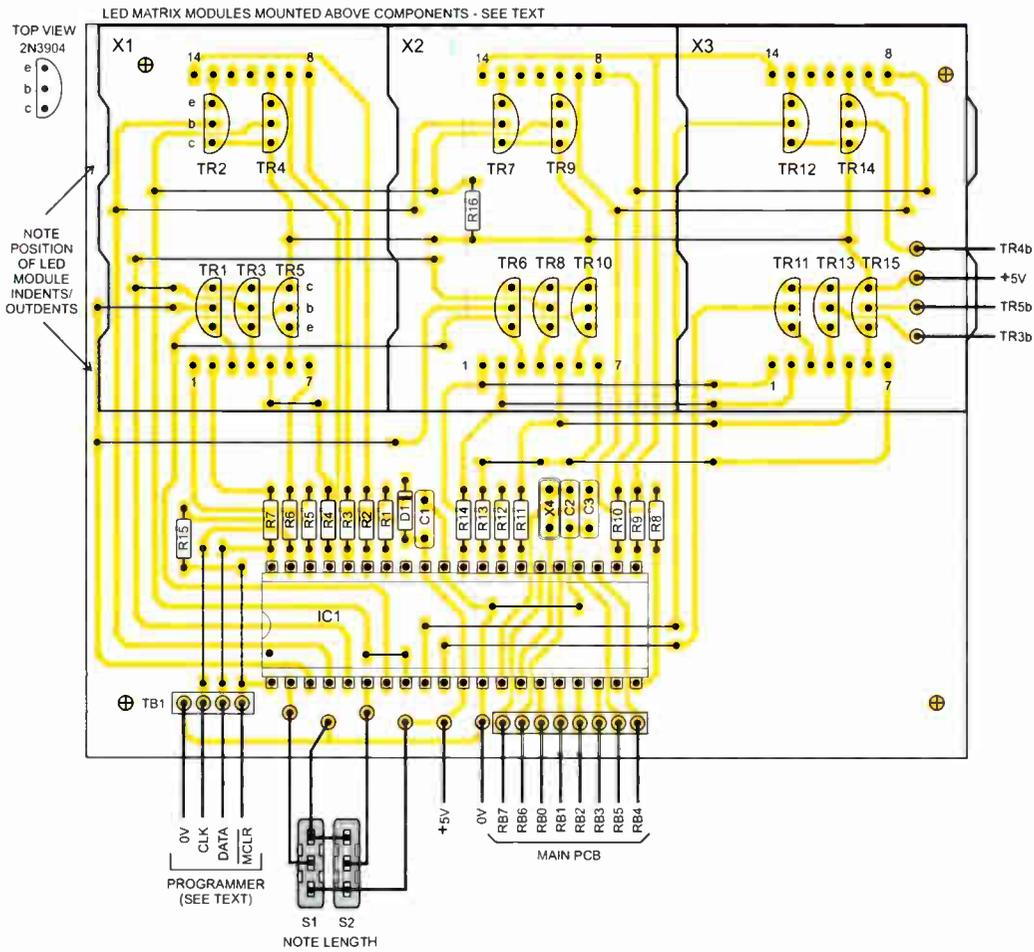


Fig.9: printed circuit board component layout, full-size copper foil master and off-board wiring details for the LED Display Interface

for the transistors which go beneath them. Make sure that the transistor orientation is according to the notations shown. Diode D1's orientation should also be correctly observed.


Thoroughly check the soldering accuracy and component positioning before inserting the pre-programmed PIC and the LED modules. Then apply power supplied by the main board of the Polyphonium, and check that it is still at +5V.

Case notes

The prototype board was not mounted in a case. Choose one to suit you and it, drilling holes for the switches and data input socket (a 24-pin D-type with the prototype, allowing for the eight data lines plus the power leads, and using alternate pins). A suitable equivalent connector and connections are required at the main control board. The use of ribbon cable is suggested.

Program operation

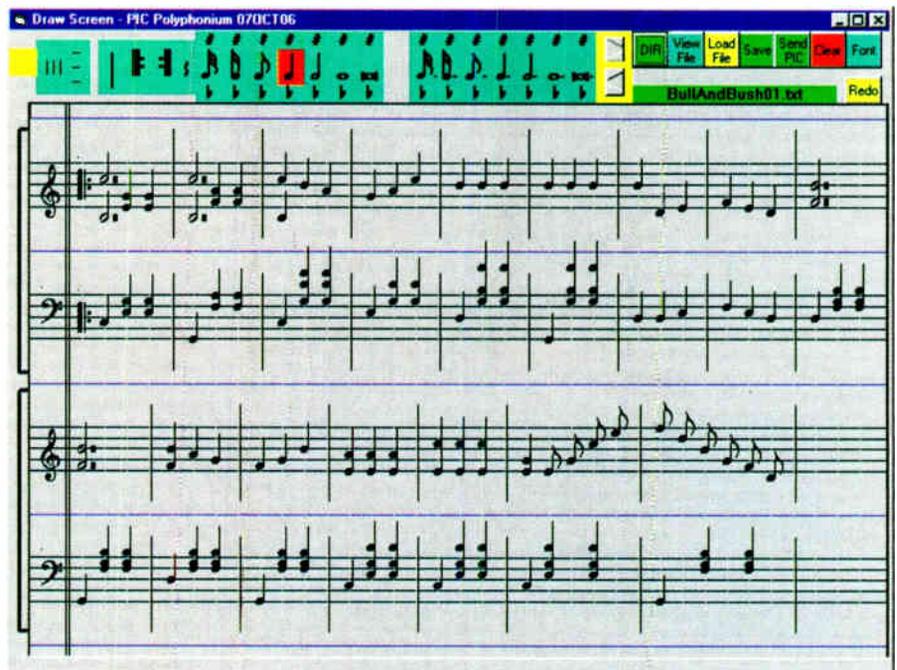There are several key routines to the operation of what is essentially a simple program. Only extracts are shown here since several parts within the main sections are basically repeats.



Screen dump showing an example of a section of a music score keyed in, and the majority of the control buttons

Refer to the full ASM program listing for the detail.

On power up, and following a load of initialisation procedures, the program enters the repeating loop routine at LOOPA (Listing 1).

The transistor controlling pins of Ports A and E are cleared, ensuring that all LEDs are initially off.

Then, at LOOPIT, a 16-stage loop, controlled by register LOOPB, is entered which calls another loop, DOLOOPA (Listing 1A). The route here depends on the count value, routing selectively to control the multiplexed columns, as indicated by the example for OUTCOLB1 in Listing 2.


This takes the note value data for the first column controlled by PORTB, held in COLUMNB1, and outputs it to PORTB. It also takes the note value data for the first column controlled by PORTD, held in COLUMND1, and outputs it to PORTD. In both instances, `comf` is used to load W with an inverted value of the bits as the equivalent LED row bits need to be low to allow the LED to conduct when its power supply line is selected.

Note that in other control instances it may not be necessary to invert the bits.

The controlling transistor is then turned on, so passing current into the chosen LED path, in this case by PORTA, bit 4 (other bits of PORTA, and of PORTE, are used for other columns). A return to the calling routine is then made.

PORT C bit 7

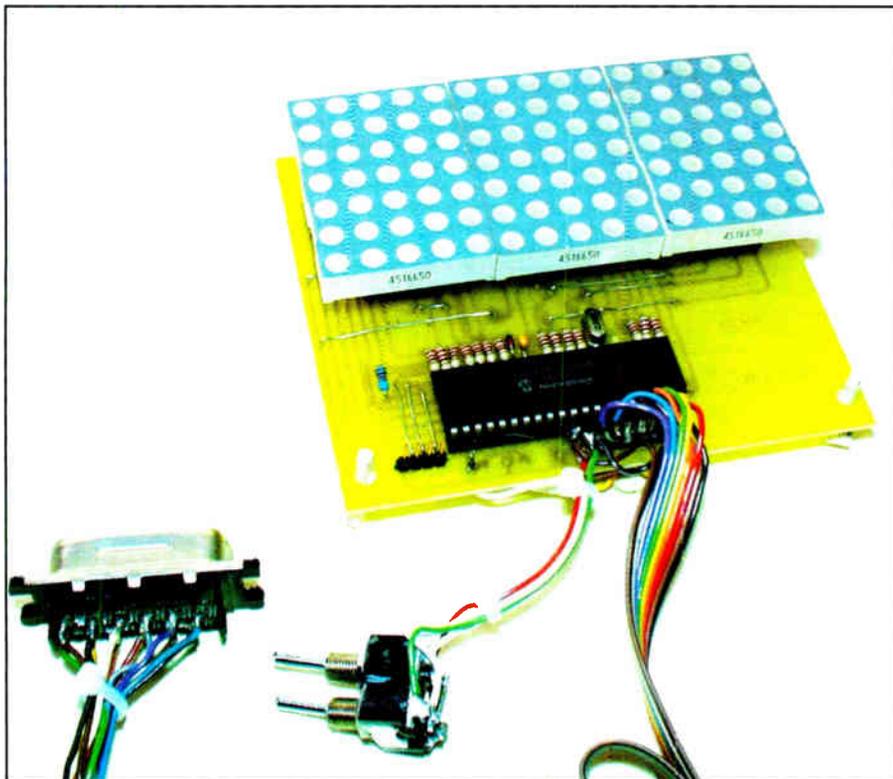Now bit 7 of the incoming data from PORTC is tested. If it is high, the



Prototype LED Display board showing the two 'note length' switches and the author's data input connector (see text). An equivalent arrangement is required at the Main Control PCB (last month)

***** SOFTWARE LISTINGS *****

Listing 1

```
LOOPIT:
  clrf PORTA
  clrf PORTE
  clrf LOOPA
  movlw 16
  movwf LOOPB

LOOPIT3:
  clrf SWITCH          ; get additional note length
                      ; rate from switches

  btfsc PORTA,0
  bsf SWITCH,0
  btfsc PORTA,4
  bsf SWITCH,1
  call SWITCHVAL
  BANK1
  movwf OPTION_REG    ; set TMR0 accordingly
  BANK0
  call DOLOOPA
  btfsc PORTC,7       ; is bit 7 set (note length
                      ; value byte)?
  goto NOTELENGTH    ; yes. Immediate
                      ; response for
                      ; NOTELENGTH data

  movf PORTC,W        ; get note value
  movwf NOTEVAL
  bcf NOTELENFLAG,0  ; clear note length flag

LOOPIT4:
  decfsz LOOPB,F
  goto LOOPIT3
  movlw 16
  movwf LOOPB
  incf LOOPA,F
  movf LOOPA,W
  xorlw 7
  btfss STATUS,Z
  goto LOOPIT3
  clrf LOOPA
  call DODELAYS
  goto LOOPIT3
```

Listing 1A

```
DOLOOPA:
  movf LOOPA,W
  andlw 7
  addwf PCL,F
  goto OUTCOLB1
  goto OUTCOLB2
  goto OUTCOLB3
  goto OUTCOLB4
  goto OUTCOLB5
  goto OUTCOLE1
  goto OUTCOLE2
```

Listing 2

```
OUTCOLB1:
  comf COLUMNB1,W
  movwf PORTB
  comf COLUMNB1,W
  movwf PORTD
  movlw 4
  movwf PORTA
  return
```

Listing 3

```
NOTELENGTH:
  movf NOTELENFLAG,W
  andlw 1
  btfss STATUS,Z      ; has note length flag been set?
  goto LOOPIT4        ; yes, continue LOOPA
  movf PORTC,W        ; no, so update all
  call SETLEN         ; get note length
  movwf LENGTHNOTE
  call OCTAVE         ; get note val & oct data
  movwf RATE
  call CHOSENROUTE
  bsf NOTELENFLAG,0  ; set note length flag
  goto ROUTEIT        ; do update
```

Listing 3A

```
ROUTEIT:
  movf CHOSEN0,W      ; which note path to use
  addwf PCL,F
  return              ; 0 no path
  goto VAL1           ; 1 Path 1
  goto VAL2           ; 2 Path 2
```

Listing 4

```
VAL1:
  movf NOTEVAL,W
  andlw 15            ; note val in LSB
  movwf STORE
  movlw COLUMNB0     ; add note to address
                      ; of COLUMNB0

  addwf STORE,W
  movwf FSR
  movwf SELECTCOL1
  movf RATE,W        ; octave held in rate
  movwf INDF         ; put into correct column
  movf LENGTHNOTE,W
  movwf DELAY1
  clrf LENGTHNOTE
  bsf CHOSEN1,0      ; flag to show path is chosen
  goto LOOPIT
```

Listing 5

```
DODELAYS:
  btfss INTCON,2     ; has a timer time-out
                      ; been detected?
  return             ; no

DEC1:
  decfsz DELAY1,F    ; no, dec DELAY, is it zero?
  goto DEC2          ; no
  bcf CHOSEN1,0      ; clear flag to show path
                      ; now free

  movf SELECTCOL1,W ; clear column
  movwf FSR
  clrf INDF

DEC2: (similar routine)
```

byte represents note length data and a call is made to the routine (NOTELENGTH – Listing 3) which extracts it. If the bit is low, a note data byte is present, so the full value of PORTC is copied into NOTEVAL.

To prevent the NOTELEN routine from being fully actioned in the likely event that the same data remains present on PORTC for several passes of the loop, a flag (NOTELENFLAG, bit 0) is used to indicate if the routine is to be run (bit 0 = 0) or a return immediately made (bit 0 = 1).

If the bit is low, the table routine at SETLEN is called in which the relative timing length of the note is chosen according to its type. This value is set into LENGTHNOTE and a call made to the routine at OCTAVE. Here the octave value for the received note is placed into RATE, and then CHOSENROUTE is called.

The path in which the RATE Value is placed depends on which is not currently in use. Had the PIC allowed for 84 such registers (12 notes x 7 octaves) to be used, a different technique would have been employed. Regrettably, there is insufficient user-memory space to do so, and with the PIC running at only 4MHz, there is insufficient speed to cope with the subsequent timing delays in such a long procedure.

After the return from CHOSENROUTE is made, the NOTELENFLAG flag is set to indicate that this received note length value has been processed. There is then a direct jump to ROUTEIT. The first few lines of this routine are given in Listing 3A. It causes the value now held in CHOSEN0 to route to the available path routine, as held in VAL1 to VAL9. All are similar, and the VAL1 routine is shown in Listing 4.

Here the value of the note itself (A, B, C etc) is extracted and, via the INDF register, the column allocated to that note is selected, and its appropriate octave bit is set. A jump back to LOOPIT is then made, whereupon the loop repeats as before.

Should no path currently be available (all in use) the value is processed by a dummy routine at VAL9. This simply processes matters in the same way as the other eight VALs, but places the results into dummy equivalent registers. So a constant

loop timing is maintained. Such a situation can develop if the received note rate is too fast for the note turn off delays to keep paths clear.

If PORTC bit 7 is not set, the incoming value is stored into NOTEVAL and the NOTELENFLAG, 0 is cleared so that the next incoming note length byte can then be immediately processed.

LOOPB is then decremented, and if it is not zero, the process repeats. If it is zero, LOOPB is reloaded with a value of 16 and LOOPA is incremented. If LOOPA's value is not equal to seven, the process again repeats.

If LOOPA is equal to seven, then LOOPA is cleared and a call made to the note turn off timing delays at DODELAYS, after which the process is again repeated.

LED turn-off delays

At DODELAYS, the delays are only processed if the PIC's TMR0 timer has rolled over (btfss INTCON, 2), being exited if it has not.

If it has rolled over, nine delay counters are decremented (the ninth being a dummy, as discussed earlier). One such counter is shown in Listing 5.

If a particular counter is not yet zero, the next one is immediately processed. If it is now zero, the chosen path flag is cleared, to indicate that this path is free again. The column to which it relates is then cleared via the INDF register, turning off the active LED column.

The next delay is then similarly actioned, and so on until the end of the ninth delay when the TMR0 overflow is cleared and a return made to the calling routine, which continues as before.

Flow concept

These routines may appear more complicated than they actually are. The logic behind them is really very simple – receive data from the PC and turn on an appropriate LED for a given length of time, then turn it off again. But there are many conditional requirements which need to be taken into account during the process.

The process is somewhat similar to that used to control the tone generation in last month's main unit. But there are differences. If you are thinking of controlling other equipment

by the main unit, you now have two examples of how you might process the basic data.

Whichever method you choose, you must extract the note itself, its octave and its duration. However, if you are thinking about controlling 84 items of external equipment, one for each note, the examples here can only be a guide. 84 paths will need a lot of multiplexing with additional chips, possibly PICs. The author showed one way in which several PICs can be chained in the *Giant LED Message Display* of Nov '06.

External equipment

In many cases of external equipment, just a single PIC bit can control it, interfaced with a current boosting buffer such as a transistor. Solenoids used to open and close organ pipes, for instance, could be controlled in this way (with suitable back-EMF diodes across the solenoids, of course).

So could the single arm movements of a manikin seemingly conducting the performance, or hitting a triangle at selected points. It would be easy enough to write your own software so that the beats were related to note play rate subdivisions, depending on whether the beat were 3-4 or 2-4 time, for instance.

The hitting of drums could also be controlled by this timing, or they could be triggered by given notes.


For drum rolls, the author might think of activating the type of electro-mechanics as used to trigger the clappers for alarm bells. Turn on a controlling motor at the start of a note or beat, then turn it off again. The mechanical action of the clapper physically causing the drum roll.

Remember that all the glorious showman's organs were invented before the era of electronics. Basically, very simple means had to be used to control their mechanics by opening and closing an air or steam valve when the punched controlling roll required it. It would no doubt have delighted the author to have invented such items had he been around then.

He is sure that some of you will be inspired to invent your own modern equivalents, using the Polyphonium's controller as your 'rolling punched card'. **EPE**

Visual C Training Course

By Robert Penfold

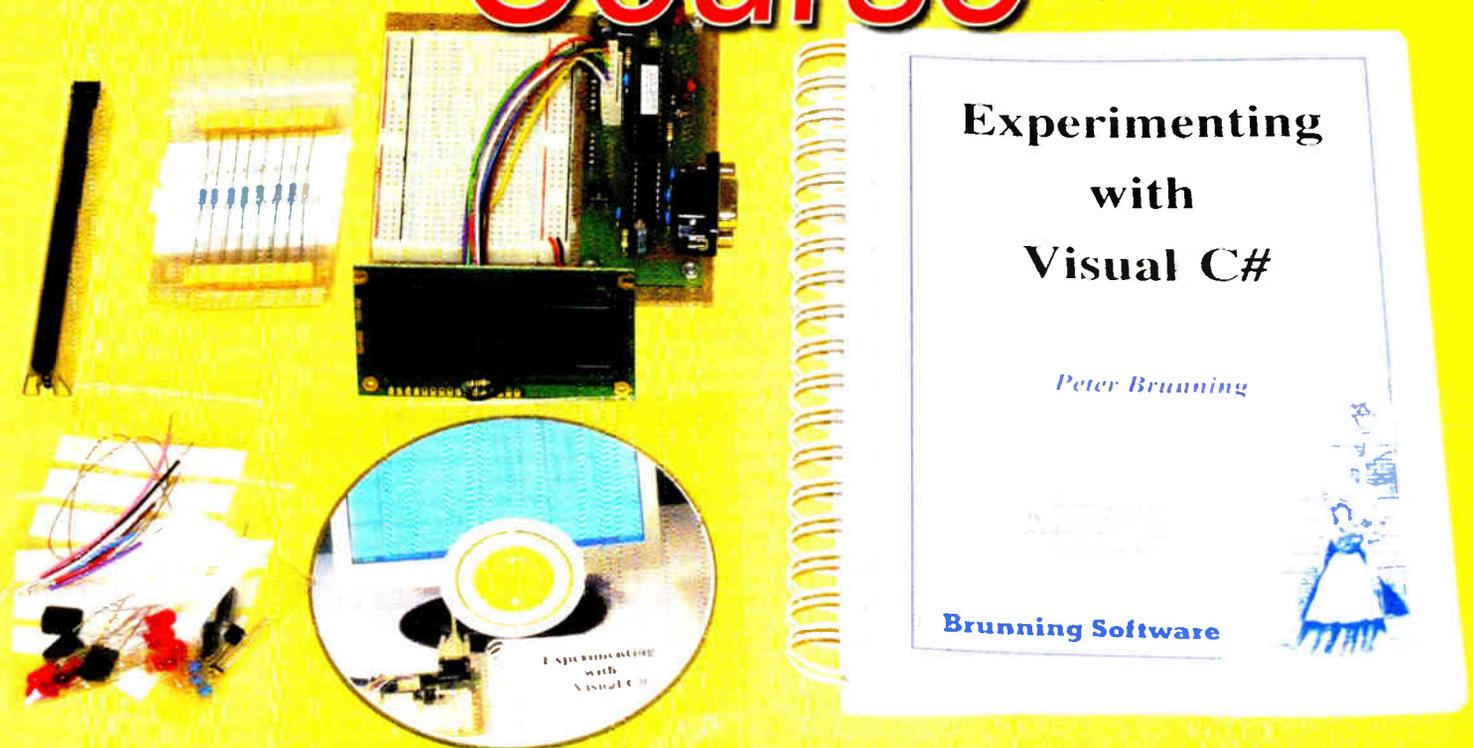

The C programming language became popular in the early days of PCs, when it was noted for its ability to hack into the hardware at a low level as well as operating as a high level language for complex tasks. Modern versions of C have, like most other programming languages, tended to become more and more complex. In the case of C, it was usurped by the more object oriented C++, and visual versions of C++. There is now Visual C# as well, which is intended to give the power of C++, but with improved user friendliness.

Compared to earlier versions, modern high level programming languages are usually less well suited to writing software for add-on computer projects. They are primarily designed for those producing word processors, sophisticated web applications, and so on.

They are in many respects 'over the top' for relatively simple applications such as the software for a piece of computer-based test equipment.

Writing this type of program is usually possible, but you have to find and exploit the aspects of the programming language that are of use, while ignoring the other 95 percent or so.

Express results

The Visual C Training Course from Brunning Software is not a full course in C programming. It is intended to provide an introduction to using Visual C to produce the control software for your own PC add-ons. It provides details of the aspects of C programming that are of use in this context, while leaving out those that are likely to be of little practical value. By 'cutting to the chase' it is possible to get started with your own programs relatively quickly, since there is little time wasted on learning aspects of C programming that will never be needed for this type of programming.

Although the title of the course refers to 'Visual C', the course is actually based on Microsoft's Visual C# Express

Edition. This is a cut-down version of Visual C#, but it is perfectly adequate for producing programs for use with PC add-ons. It has the advantage of being available as a free download from the Microsoft website.

At about 30 megabytes for the basic program, it is not essential to have some form of broadband connection in order to download it. However, a full installation, which includes the MSDN Express library, requires a few hundred megabytes to be downloaded and might not be a practical proposition unless some form of broadband access is available. The basic program is sufficient to run the example programs featured in this course.

The Express version of Visual C# lacks the more upmarket features of the full program, but it is otherwise fully operational. There are no restrictions on saving or compiling your programs for example.

Although the Express versions of Microsoft's programming languages

were originally to be made available for one year, this time limit has now been removed. Being able to experiment with programs and ultimately write your own without the need to buy an expensive programming language is clearly a big advantage.

In the kit

The course consists of a book and various pieces of hardware. The book is called *Experimenting with Visual C#*, is ring-bound, and has 272 pages that are approximately 240 by 175mm. It is nicely produced using good quality paper and clear printing with plenty of excellent diagrams.

The main piece of hardware is a serial interface unit that includes a solderless prototyping board (Fig.1). The interface provides eight latching digital outputs and five analogue/digital inputs, and is based on a PIC18F2525 microcontroller. It is a pity that the interface does not provide a full 8-bit digital input port, but this limitation is to some extent mitigated by the ability of the five inputs to operate as analogue types.

Physically, the interface is quite basic, but it is also quite tough and should be capable of standing up to a fair amount of use. A 9-pin PC serial lead is needed to connect the interface to a PC. A suitable lead is not included as standard, but it can be supplied as a low-cost extra, as can a mains power unit.

There is a potential problem in using a serial port to link the interface to the computer, and this is simply that it is increasingly common for new PCs to lack a serial port. The suggested solution to the problem is to buy a USB/serial converter. This method should work well since the interface is accessed via a standard Windows route that does not involve any programming trickery. There should be no problem in using the interface, provided the converter is installed properly as a standard Windows serial port.

The other items of included hardware are the resistors, LEDs, and integrated circuits needed in order to complete the various demonstration circuits featured in the book. There is also a 16 x 2 LCD module that is needed for some of the more advanced demonstration circuits.

Finally, there is a CD-ROM that contains the demonstration programs

in the form of simple text files that can be used via the Copy and Paste method. Using these should save a great deal of time and avoid problems with typing errors. There are no program files that can be loaded directly into Visual C#.

No serial lead or power supply unit were provided with the review system. However, I had no difficulty getting the test unit connected and powered-up using a serial lead from a PIC programmer and a suitable mains adaptor selected from a collection of a dozen or so of these units.

With anything of this type I would still recommend paying the small additional cost of the optional lead and power supply. These should guarantee that there will be no hassle or delays involved in getting the system 'up and running'.

If it has powered up correctly the unit flashes an LED and briefly displays a message on the LCD module. It is then a matter of trying a test program to determine whether it is communicating correctly with the computer. The review system operated first time and without any problems (see Fig.2).

By the book

A system of this type is clearly of little real value unless the documentation provides a good understanding of programming and interfacing techniques. The supplied book does a good

job of things, and does not assume that the user has any previous knowledge of programming or electronics. It is assumed that the user knows how to use a PC. A basic knowledge of electronic components and programming would certainly be helpful, but neither are required in order to follow the examples in the book and utilise the system.

The book starts with some basic information about using Visual C#, such as adding components to a form, changing their properties, and running a program. It then gives some information about building a serial interface for use with the provided interfacing examples. Since the book is available separately, it is possible to build your own interface unit and then try out the examples. Doing things this way would require a fair amount of expertise though, and would probably not save a huge amount of money.

Subsequent chapters deal with simple programs that provide an easy introduction to using the interface and also serve as simple checks to ensure that it is working correctly. The review unit was tried with several example programs and always worked first time. Further chapters deal with slightly more advanced circuits and programs. The projects include such things as a simple electronic dice and a more realistic version, a digital IC tester, and a digital-to-analogue converter.

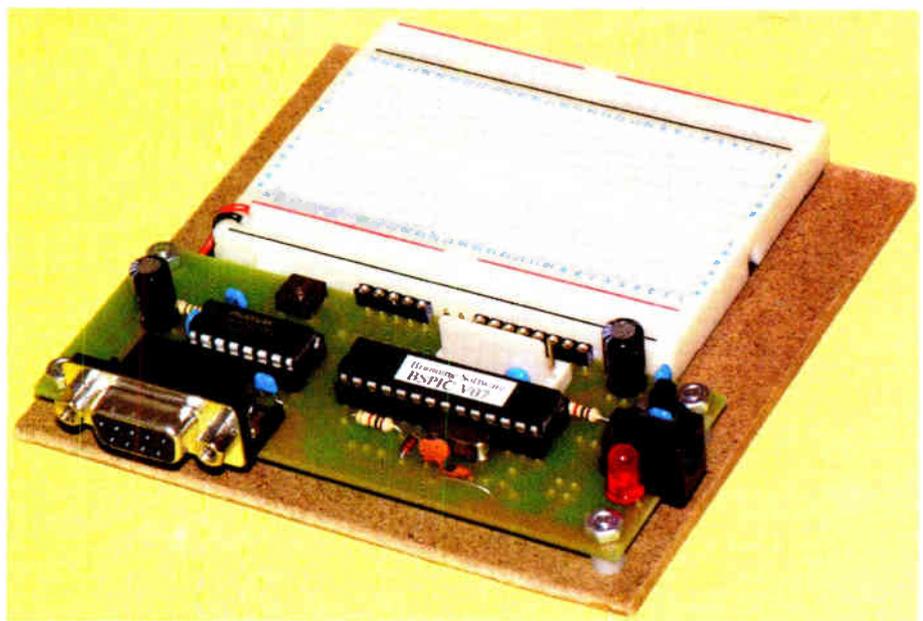


Fig.1: the AUX200 interface includes a solderless breadboard that is used when building and testing the projects featured in the course. The LED flashes to indicate that the unit has powered up correctly.

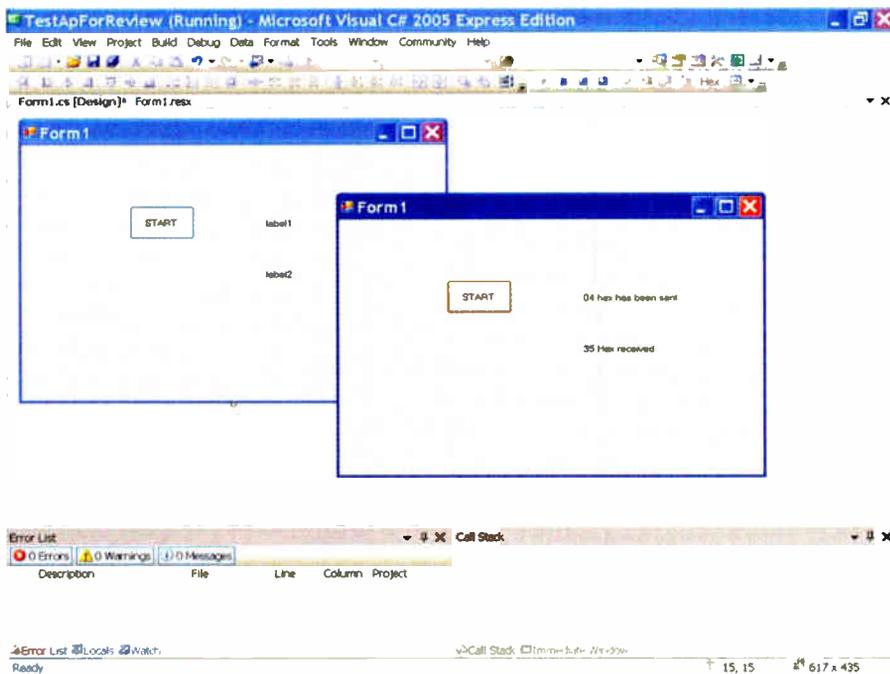


Fig.2: the simple test program has successfully written data to and read data back from the AU200X interface unit. Visual C# Express is available as a free download from the Microsoft website

These chapters also introduce important aspects of programming, such as variables, loops, and functions. The visual approach to programming greatly reduces the amount of program code that has to be written by the programmer. However, it is still necessary to write some simple routines in order to make a program do something useful. These routines use conventional programming techniques, complete with loops, variables, and so on.

Later chapters show how these conventional programming techniques can be used in practice. These chapters also cover more advanced topics such as temperature measurement, writing data to the LCD display, using graphics, a low frequency oscilloscope, and Fourier analysis.

No soldering is required in order to build the example circuits. They are easily assembled on the interface's solderless breadboard, and all the components needed are included. There are even some pre-cut and prepared connecting leads. Circuit diagrams and practical layout diagrams are included in the book, and building the circuits is therefore quick and straightforward.

Conclusion

This course certainly provides an easy introduction to using Visual C# with PC add-ons, but I suppose that some might

question the choice of any form of C for applications of this type. However, Visual C# is much easier to use than other modern versions of this language.

The *Experimenting with Visual C#* book succeeds in stripping things down to the basics so that real-world programs can be produced quite easily, and without becoming an expert C programmer. You are not swamped with pages of program code that does little more than flash an LED a few times! Although Visual C# might not be everyone's first choice for this type of programming, it represents a practical way of writing software for PC add-ons.

The *Experimenting with Visual C#* book is well written and reasonably easy to follow. The number of example projects is not very large, but those that are featured are covered in detail. For a training course, this is much better than having numerous examples that are given inadequate coverage. As the inner working of the PIC-based interface are described in some detail, it should be possible for users to use the lessons learned from the course to produce their own PC projects.

However, it would be necessary to gain a fair amount of expertise with PIC processors in order to do this. In fact, the use of the PIC method of serial interfacing to the PC means that the user has to learn a certain amount about PIC programming and hardware

System Requirements

There is no minimum system requirement as such, but in order to use the course properly it is obviously necessary to have a PC that is up to the task of running Visual C# Express. This is the minimum system recommended by Microsoft:

- Windows 2000 with SP4, or a later version of Windows such as XP or Vista
- A processor running at 600MHz or more (1GHz or more recommended)
- 192 megabytes of RAM (256 megabytes or more recommended)
- 500 megabytes of hard drive space (1.3 gigabytes for a full installation including the MSDN Express library)

in order to follow the course properly. Another point to bear in mind is that although the serial approach to PC interfacing has its advantages, especially when used with an 'intelligent' PIC-based project, there are also a few drawbacks. In particular, potential users of this method should bear in mind that some applications are precluded by the relatively slow data transfer rates.

Cost

The Visual C Training Course should appeal to hobbyists and professionals looking for a simple introduction to basic PC interfacing. I found the course interesting and easy to use, and it can certainly be recommended. It is competitively priced, and the fact that it is based on a free programming language helps to keep costs to a minimum.

The cost of the Brunning Software Visual C Training Course is £88-00 plus £8-00 for postage and insurance. A serial lead costs an extra £3-00, and a mains adaptor is £4-00 plus an additional £2-00 for postage and insurance. Further details are available from:

Brunning Software, 138 The Street, Little Clacton, Clacton-on-sea, Essex, CO16 9LS, UK.


Telephone – 01255 862308

Email – pic@brunningsoftware.co.uk

Web – <http://brunningsoftware.co.uk>

EPE

Learn About Microcontrollers

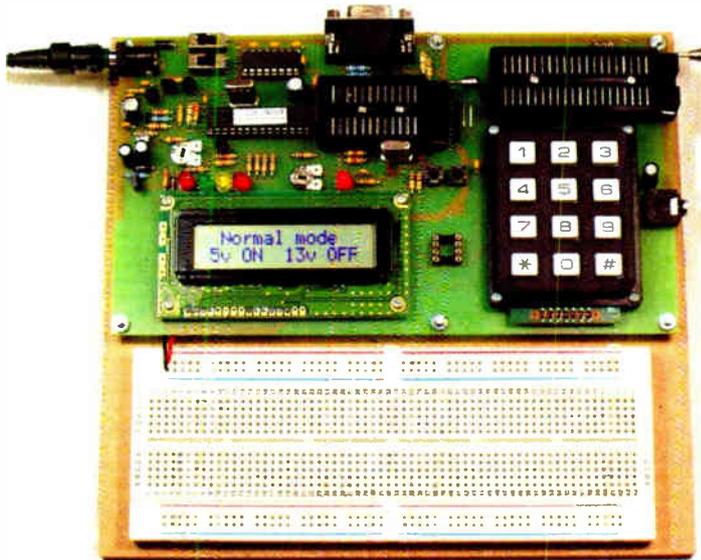

Updated PIC Training Course

Our microcontroller training course has been completely updated. PICs are still without any doubt the right place to start, but we must accept that it is time for the PIC16F84 to gracefully fade away. The PIC16F627A is now the best place to begin our learning process. This is a low cost PIC offering many internal facilities but we start by using it in the very simplest way.

At the heart of our system are two real books which lie open on your desk while you use your computer to type in the programme and control the hardware. Start with four simple programmes. Run the simulator to see how they work. Test them with real hardware. Follow on with a little theory.....

Our PIC training course consists of our 16F/18F PIC programmer, a 300 page book teaching the fundamentals of PIC programming in assembly language, a 274 page book introducing the C programming language for PICs, and a suite of programmes to run on a PC. The module is an advanced design using a 28 pin PIC16F873A to handle the timing, programming and voltage switching requirements. Two ZIF sockets allow most 8, 18, 28 and 40 pin PICs to be programmed. The plugboard is wired with a 5 volt supply. The programming is performed at 5 volts, verified with 2 volts or 3 volts applied and verified again with 5.5 volts applied to ensure that the PIC is programmed correctly over its full operating voltage. UK orders include a plugtop power supply.

P927 PIC Training & Development Course comprising.....

- Universal 16C, 16F and 18F PIC programmer module
- + Book *Experimenting with PIC Microcontrollers* (2007 edition)
- + Book *Experimenting with PIC C* (2007 edition)
- + PIC assembler and C compiler software on CD
- + PIC16F627A, PIC16F88, PIC16F870

and PIC18F2420 test PICs. £159.00

(Postage & insurance UK £10, Europe £18, Rest of world £25)

Experimenting with PIC Microcontrollers

Everyone should start programming PICs using assembly language because this is the only way to fully understand what happens, but there is a general misconception that PIC assembly language is difficult. Imagine trying to teach English grammar to a child before allowing him or her to speak yet that is how most books approach a technical subject. Our first book introduces PIC assembly language programming by jumping straight in with four easy experiments. The first is explained over ten and a half pages assuming no starting knowledge of PICs. Then having gained some practical experience we study the basic principles of PIC programming, learn about the 8 bit timer, how to drive the liquid crystal display, create a real time clock, experiment with the watchdog timer, sleep mode, beeps and music, including a rendition of Beethoven's *Fur Elise*. Then there are two projects to work through, using a PIC16F627A as a sine wave generator and investigating using a PIC16F88 to monitor the power taken by domestic appliances. Then we learn how to adapt the experiments so the software runs in the PIC16F877 family, PIC16F84 and PIC18F2420. In the space of 24 experiments, two projects and 56 exercises the book works through from absolute beginner to experienced engineer level, covering a comprehensive selection of the most up to date PICs.

Web site:- www.brunningsoftware.co.uk

PIC C Language

The second book *Experimenting with PIC C* starts with an easy to understand explanation of how to write simple PIC programmes in C. We start our experiments using the PIC16F627A then we see how easy it is to use the same C programmes with the PIC16F877 family, the PIC16F88 and the PIC16F84.

We study how to create programme loops using C, we experiment with the IF statement, use the 8 bit and 16 bit timers, write text, integer and floating point variables to the liquid crystal display, and use the keypad to enter numbers.

Then its time for 25 pages of pure study, which takes us much deeper into C than is directly useful with PICs as we know them – we are studying for the future as well as the present. We are not expected to understand everything that is presented in these 25 pages, the idea is to begin the learning curve for a deep understanding of C.

In chapter 9 we use C to programme the PIC to produce a siren sound and in the following chapter we create the circuit and software for a freezer thaw warning device. Through the last four chapters we experiment with using the PIC to measure temperature, create a torch light with white LEDs, control the speed of one then two motors, study how to use a PIC to switch mains voltages, and finally experiment with serial communication using the PIC's USART.


Some of the programmes towards the end of *Experimenting with PIC C* are shown in assembler and C to enable the process to be fully explained, and in the torch light experiments, due to the fast switching speed, the programmes are written only in assembler.

As you work through this book you will be pleasantly surprised how C makes light work of calculations and how easy it is to display the answers.

Ordering Information

The programmer module connects to the serial port of your PC (COM1 or COM2) or through a USB to COM adapter (COM3 or COM4). All our software referred to in this advertisement will operate within Windows 98, XP, NT, 2000 etc.

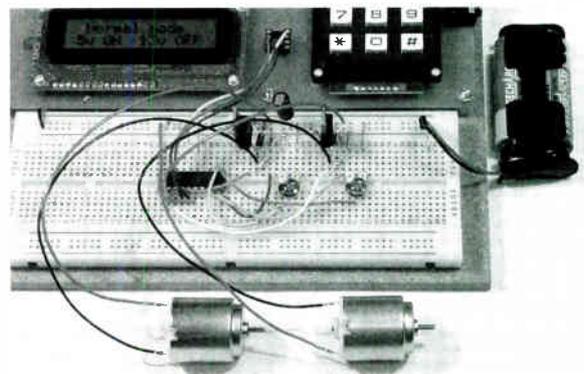Telephone with Visa, Mastercard or Switch, or send cheque/PO. All prices include VAT if applicable.



White LED and Motors

Our PIC training system uses a very practical approach. Towards the end of the second book circuits need to be built on the plugboard. The 5 volt supply which is already wired to the plugboard has a current limit setting which ensures that even the most severe wiring errors will not be a fire hazard and are very unlikely to damage PICs or other ICs.


We use a PIC16F627A as a freezer thaw monitor, as a step up switching regulator to drive 3 ultra bright white LEDs, and to control the speed of a DC motor with maximum torque still available. A kit of parts can be purchased (£30) to build the circuits using the white LEDs and the two motors. See our web site for details.

Mail order address:

Brunning Software

138 The Street, Little Clacton, Clacton-on-sea,
Essex, CO16 9LS. Tel 01255 862308

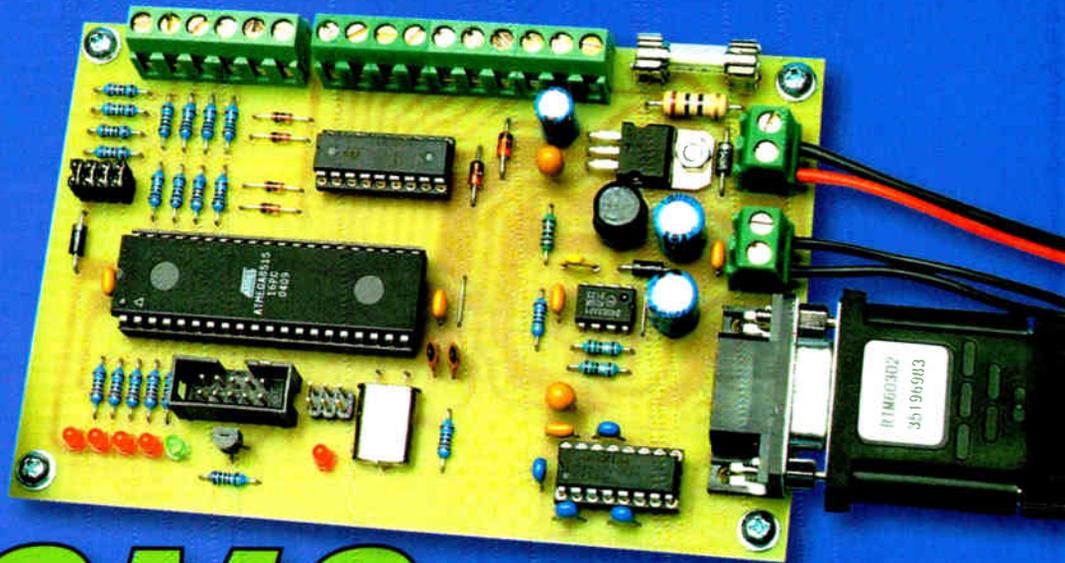Control equipment from anywhere, anytime, using SMS and an old Nokia mobile phone! – By Peter Smith



SMS Controller Pt.2

Last month, we described the circuit for the SMS Controller and gave the assembly details. This month, we tell you how to complete the circuit checking and describe how the unit is used.

Having carried out the power supply checks described last month in Part 1, the next step is to check out the serial interface and the microcontroller.

First, disconnect the power and insert IC1 and IC3 into their sockets. If the microcontroller needs to be programmed, then you should do that next. Refer to the Microcontroller Programming panel for more details on this.

Next, install jumper shunts on JP4 to JP7. These should always be in place when the inputs (IN1 - IN4) are not connected, otherwise the micro's

port pins will be 'floating' in an indeterminate logic state.

Conversely, remove all jumper shunts from JP1-JP3 if installed earlier and apply power. The 'Comms Error' LED (LED1) should illuminate, while all other LEDs (except the 'Power' LED) should be off. This indicates that the micro cannot communicate with the phone, which of course isn't connected yet. However, it does tell us that the micro is doing what it should.

Note: the very first time you apply power, all red LEDs may come on for one second and then go out, with just

the 'Comms Error' LED remaining on. This sequence indicates that the micro has automatically erased its on-board EEPROM, ready for programming.

If you get a different result, the problem is most likely due to one or more pins of the micro having missed their sockets and bent underneath the chip.

If bent pins aren't the problem, then check out the oscillator circuit, consisting of crystal X1 and the two 22pF capacitors. If you have access to an oscilloscope, you can observe the operation of the oscillator on pin 18. In addition, check the voltage on the micro's RESET input (pin 9). This pin should measure close to +5V during normal operation, going low only during power up and power down.

The final step involves a quick checkout of the RS232 interface circuit. Measure the voltage between pin 2 of IC4 and ground and pin 6 of IC4 and

ground. You should get around +9.5V and -9.3V, respectively. These voltages are generated by the MAX232's internal charge pumps, in conjunction with the four 1 μ F capacitors.

If your board passes all the tests, you can now connect the data cable between your board and phone. Note that it's a good idea to power off both devices when connecting and disconnecting this cable.

Suitable case

If desired, the completed module can be housed in a 'UB1' size plastic box or similar, with a slot cut in the side of the box to accommodate the terminal block wiring.

The mobile phone must be positioned at least 50cm from the controller and associated wiring so that RF energy from its antenna doesn't interfere with the circuit operation. **This is very important!** If this separation cannot be attained in your application, then the controller must be housed in a metal case or shielded from the phone with a large metal plate.

Alternatively, both the 5110 and 6110 models support connection of an external antenna, which would allow good separation and improve signal strength in some areas.

Operational basics

System operation is quite straightforward – when any of the digital inputs change state, the controller sends a pre-programmed SMS message to the nominated mobile number. Conversely, when you want to turn any of the outputs on or off, you send a message to the controller.

The messages used in both directions are programmed during the setup procedure. This allows the use of messages related to the task at hand. For example, you might want to assign the message 'pump' to turn on the first output and 'nopump' to turn it off. This means that you don't need to remember which output the pump is connected to or which state (high or low) is on or off.

The controller also recognises a number of unique messages, called 'in-built commands', that can be sent from another mobile to program the system during setup, as well as modify system behaviour during normal operation. A summary of all these commands appears in Table 2. Before we look at how to set up the controller, let's look at each command in detail.



On the 3310 model, the serial interface is accessible through a hole in the rear of the case, underneath the battery. The data cable is terminated with a plastic head assembly that includes a set of spring-loaded contacts as well as tabs to retain the battery that it partly displaces.

In-built commands

ACKON – this command forces the controller to respond to every message that it receives. If a received message is deemed valid, the controller responds with 'OK'. If a message is unknown, the response is 'bad cmd'.

ACKOFF – the opposite of **ACKON**. All further acknowledgments are disabled.

CHARGE{number} – this command allows you to modify the battery charging parameters, dependent on the model of phone in use.

For the 5110 and 6110, the {number} value defines the battery level at which the on-board charger is switched on. Only values between 0 and 4 are valid. A value of 4 instructs the controller to continually charge the phone and is therefore not recommended. The default level is 1.

For the 3210 and 3110, a timed charge/discharge scheme is used instead, as battery level information is not available to the controller. The {number} value defines the charge time in minutes, with the discharge time being fixed at 8 hours. Only

values between 10 and 240 are valid. The default charge time is 40 minutes.

COUNT – Use this command to get the total number of messages sent and received by the controller, as well as the firmware version number. The returned message is in the format 'r=nnnnn s=nnnnn v=nn.nn', where 'r' and 's' are the total number of received and sent messages, respectively.

DIS{string} – in some situations, you may not want to be informed when a particular input changes state but still want to receive notification on the remaining inputs. An example of this might be when one sector of an alarm system is faulty and has been isolated. Using this command, you can disable notification on either or both states of any input.

For example, suppose a message of 'SECTOR1ALARM' is programmed to be sent when an input goes low and a complementary message of 'SECTOR1IDLE' is programmed to be sent when it returns high. To stop receiving these messages each time the input toggles, you could send the commands

Microcontroller Programming

You can purchase a ready programmed microcontroller (IC1) from Magenta Electronics – see page 5. Alternatively, you'll need to program the microcontroller yourself.

A 10-way header (CON5) has been included on the PC board for connection to an 'in-system' type programmer.

Once you have a suitable programmer, together with the necessary cables and Windows software to drive it, all you need to complete the job is a copy of the microcontroller program for the SMS Controller. This can be downloaded from our web site – go to the 'Downloads' section.

This contains the file 'SMS.HEX', which needs to be programmed into the micro's program (FLASH) memory. Just follow the instructions provided

with the programmer and software to complete the task.

Fuse bits

We've specified either AT90S8515-8 or ATmega8515-16 microcontrollers for this project. Although it has many improvements over its predecessor, the ATmega8515 is a pin-for-pin replacement for the AT90S8515. In fact, we've tested this project with both of these devices to ensure compatibility.

The only additional requirement when using the ATmega8515 is to ensure that the fuse bits are correctly programmed. The default fuse settings in the AT90S8515 are OK and should not be altered.

Reproduced by arrangement with SILICON CHIP magazine 2007.
www.siliconchip.com.au

If a password had been set, it must immediately follow the **LOGIN** command. An exception to this is in programming mode (JP3 in), where password checking is not performed.

LOGOUT – this command disables all outgoing messages. It's wise to send this command to the controller before you switch off your phone. If your phone's battery goes flat, or it's stolen or misplaced, use a friend's phone to first **LOGIN** and then **LOGOUT**. If you don't, a malfunctioning system could see you rack up a phone bill of astronomical proportions – a compelling reason to use only a prepaid plan for the phone connected to the controller (see panel in Part 1)!

PASS{string} – sets a new password of 1 to 8 characters long. Passwords longer than 8 characters elicit a 'bad pass' response. The initial password is programmed during the setup procedure. Once set, it can be changed at any time but only from the currently logged-in phone (see **LOGIN** command).

STAT – returns the current state of the digital input and open-collector output ports. The displayed format is 'XXXX YYYYYYYY', where 'X' and 'Y' are 'H' for logic high or 'L' for logic

'**DISSECTOR1ALARM**' followed by '**DISSECTOR1IDLE**'.

EN{string} – the opposite of **DIS{string}**, this command reinstates notification on the input and state designated by {string}.

LOGIN{pass} – essentially, this command tells the controller your cur-

rent mobile phone number. You don't actually need to enter the number, as it's automatically gleaned from the incoming message. All messages are forwarded to the mobile phone that sent the last **LOGIN** command, which remains valid until another **LOGIN** or **LOGOUT** command is received.

Table 2: Command Summary

Command	Function
ACKON	Enable acknowledge messages
ACKOFF	Disable acknowledge messages
CHARGE{number}	Modify battery charge level (5110 & 6110) or charge time (3210 & 3310)
COUNT	Get SMS sent & received counters & firmware version number
DIS{string}	Disable state change messages on input defined by {string}
EN{string}	Enable state change messages on input defined by {string}
LOGIN	Enable message transmissions to your current mobile number
LOGOUT	Disable further message transmissions to your mobile
PASS{string}	Set new password to {string} (8 characters max.)
STAT	Get snapshot of digital inputs & open-collector outputs
The following commands are valid only in programming mode (JP3 in):	
IN{n}{L}{message}	Define the message the controller sends when input {n} goes low
IN{n}{H}{message}	Define the message the controller sends when input {n} goes high
OUT{n}{L}{message}	Define the message you send to drive output {n} low
OUT{n}{H}{message}	Define the message you send to drive output {n} high
OUT{n}{P}{message}	Define the message you send to pulse output {n} low

Here's a summary of the commands recognised by the controller. The curly braces are used here for clarity and should not be included in your messages. Note: do not use spaces after command words.



A complete lineup of the supported models, from left to right: 5110, 6110, 3210 and 3310.

low. The input port is displayed first, followed by the output port, with the most-significant bits (IN4 and OUT8) displayed first.

For the output port, an 'H' (high) indicates the driver is switched off, whereas an 'L' (low) indicates it is on. Note that external circuits may invert this logic.

A response from the **STAT** command looks like this: 'HHLH HLHHHHH'. In this case, IN2 is low and IN1, IN3 and IN4 are high. On the output side, OUT7 is on (low) and all other drivers are off (high).

The following commands operate only in programming mode (JP3 in):

IN{n}{L}{message} – defines the message that will be sent by the controller when input {n} goes low. For example, suppose you've connected a switch to the first input (IN1), as shown in Fig.7(b) – last month. When the switch is closed, the input changes state from a logic high (+5V) to a logic low (0V). To receive the message 'SWITCH CLOSED', the required command would be **IN1LSWITCH CLOSED**.

Of course, you can use any message you like, as long as it's no more than 16 characters long.

IN{n}{H}{message} – defines the message that will be sent by the controller when input {n} goes high. Using the previous example, to receive

the message 'SWITCH OPEN' when the first input (IN1) changes from a logic low to a logic high, the required command would be: **IN1HSWITCH OPEN**.

OUT{n}{L}{message} – defines the message that you send to the controller to drive output {n} low. For example, suppose you've connected a relay to OUT1, as shown in Fig.6(a) – last month. A low on this output grounds one end of the relay coil, switching it on. Assuming you want to use the message 'RELAY ON', the required command would be **OUT1LRELAY ON**.

OUT{n}{H}{message} – defines the message that you send to the controller to drive output {n} high. From the previous example, to switch the relay off with the message 'RELAY OFF', the required command would be **OUT1HRELAY OFF**.

OUT{n}{P}{message} – defines the message that you send to the controller to pulse output {n}. When the controller receives this message, the specified output will be driven low for one second, after which it returns high. Again from the previous examples, to pulse a relay on OUT1 using the message 'PULSE RELAY', the required command would be **OUT1PPULSE RELAY**. It's important to note that when any output is defined as a 'pulsed' output, you cannot

also define it with the **OUT{n}{L}** or **OUT{n}{H}** commands.

Message syntax

Messages used in the 'IN' and 'OUT' commands can be composed from any characters in the available repertoire but the total length must be limited to 16 characters. Longer messages are automatically truncated. Spaces can be used in the body of messages **but not adjacent to the command or password strings (ie, DO NOT use spaces after command words)**.

In addition, all user-defined messages, including the password, are *case sensitive*. This is a trap for the unwary: 'PUMP ON' and 'pump on' are not the same message! Inbuilt commands, on the other hand, are not case sensitive.

Finally, your messages must not start with the in-built command words **ACKON, ACKOFF, CHARGE, COUNT, DIS, EN, LOGIN, LOGOUT, PASS** or **STAT**.

Example setup

Let's look at a fictitious system setup to see how it all works. The specifications for this system are as follows:

- All commands to the controller must be acknowledged.
- The system is to be password protected. The initial password will be 'REDDWARF'.

LED Indicators

Five LEDs are provided to indicate system status; four red (LED1 – LED4) and one green (LED5). The red LEDs indicate error conditions, so during normal operation none of them should be on.

LED1 – Comms Error: when illuminated, this LED indicates a controller to phone communications problem. Normally, it comes on for 6 seconds after power on and then goes out. If it doesn't go out, check for problems with the controller to phone cable connection. In addition, check that phone security (PIN) has been disabled and that the phone comes up ready for use at power on.

LED2 – No Service: indicates that the phone is not registered within the mobile network (check signal strength) or that an outgoing message has been disallowed. The latter is typically due to an empty pre-paid account.

Note that although your service provider will block outgoing messages when an account expires, most still allow inbound messages for a certain length of time.

LED3 – Send Error: when illuminated, the controller has failed to send one or more messages. This can be caused by a variety of problems, including mobile network overload, momentary signal dropout, an empty pre-paid account, phone malfunction or an intermittent controller to phone connection.

LED4 – Delete Error: indicates that the controller cannot delete a message from SIM memory. Cycle the phone power to correct this problem. If the error persists, then there may be a problem with the SIM card or phone.

LED5 – In Use: this LED comes on when you login to the system and goes out when you logout.

- A relay is connected to OUT1, as shown in Fig.6(a) – last month. The relay controls a pump motor.
- The relay is to be switched on by sending 'PUMP ON' to the controller.
- The relay is to be switched off by sending 'PUMP OFF' to the controller.
- A switch is connected to IN1, as shown in Fig.7(b) – last month. The switch detects water level in a tank.
- When the switch closes, we want to receive the message 'TANK OVERFLOW'.
- When the switch opens, we want to receive the message 'LEVEL NORMAL'.

We start in programming mode by installing a jumper on JP3 and powering up. After the 'Comms Error' LED goes out (about 6 seconds), we can send our programming commands from a second mobile phone, as follows:

```
LOGIN (the green LED illuminates)
ACKON
PASSREDDWARF
OUT1LPUMP ON
OUT1HPUMP OFF
IN1LTANK OVERFLOW
IN1HLEVEL NORMAL
```

This completes the programming, so

JP3 must now be removed, returning the system to operating mode. We can now control the pump by 'SMSing' the following messages to the controller:
PUMP ON (switch the pump on)
PUMP OFF (switch the pump off)

If our imaginary tank overflows and the switch closes, we'll receive the message:

TANK OVERFLOW

When the level subsides and the switch opens, we will receive the message:

LEVEL NORMAL

Now suppose we don't want to receive the 'LEVEL NORMAL' message again. Instead, we only want to be informed when there is an overflow. We can disable the 'LEVEL NORMAL' notification by sending:

DISLEVEL NORMAL

To later reinstate notification, we'd send:

ENLEVEL NORMAL

To change the password to 'STARGATE' and disable acknowledgments, we could send:

PASSSTARGATE
ACKOFF

To log out of the system and prevent further messages being sent by the controller:

LOGOUT (the green LED goes out)

Finally, note that all future logins will require the current password, as follows:

LOGINSTARGATE

Each command is sent as a separate message. After the **ACKON** command, the controller will acknowledge all subsequent commands; you should wait until you receive these before sending the next command. Although you don't need acknowledgments turned on, it's the only way to be certain that the controller has received and processed your commands. This is much more important during normal operation, when you're far from the controller and can't see what's happening.

The password and all user-programmed messages are stored in the micro's EEPROM, so you only need to program the system once. The same goes for the output port state. If a power failure occurs, the last state will be automatically reinstated when power is restored.

You can reprogram the system at any time simply by repeating the steps outlined above. When you redefine a message for any input or output, the old message is automatically overwritten.

If you'd like to start from scratch, then all of the previously programmed messages can be deleted in one operation by erasing the microcontroller's EEPROM. This is achieved by powering off and installing a jumper on JP1. When you power up again, all four red LEDs come on to indicate that erasure is complete.

Note that this operation also wipes the password and all other parameters, including the 'SMS sent' and 'SMS received' counters.

Finally, you can erase just the password by powering off and installing a jumper on JP2. At the next power on, the password will be erased. Be sure to remove JP2 when done, otherwise the **PASS** command will have no effect!

Security

While it's not strictly necessary to program a password during setup and testing, we recommend that you do so before 'going live'. A password is an effective way of preventing someone else taking control of the module without your knowledge.

Once you've successfully logged in, the SMS controller will only accept messages from your mobile phone number. Messages from all other



The 3210 interface is also accessible under the rear cover but unlike the 3310, there's no need to remove the battery. Once in place, the connector and cable extend at right angles from the rear of the phone, which may make mounting awkward in some cases.

numbers are simply ignored. An exception to this is the **LOGIN** command itself, which can be issued from any mobile number at any time, regardless of whether you're already logged in or not. This allows you to regain control of the system using a second phone should your current phone be lost or stolen.

EPE

Credits

Thanks go to the gnokii team, who kindly published details of their work with the Nokia serial bus protocols. You'll find their web site at: www.gnokii.org.

Regular Clinic

Circuit Surgery

Ian Bell



Active Current Measurement

RECENTLY there has been some discussion on the *EPE Chat Zone* (via www.epemag.co.uk) about the measurement of current by amplifying the voltage drop across a small resistor. CZ User *Chuckieboy* started the discussion by posting a question about the lack of stability of the reading obtained from such a circuit. Here are some extracts from his post:

I measure the voltage drop across a 0.1Ω resistor and use an op amp to boost the voltage. The voltage coming out of the op amp seems smooth enough, but my reading is up and down. I feed the op amp with 2 × 1kΩ resistors which go either side of the 0.1Ω resistor. The voltage comes out 0V to 5V with 0V to 400mV across the resistor. I've done some Google searching but got confused as there seem to be so many ways of doing it.

At the time of writing, there is insufficient information on the details of Chuckieboy's circuit and the nature of the instability to provide a specific diagnosis, but we can look at some of the ways of approaching this problem and hopefully reduce the confusion.

Key application

A key application of resistive current sensing is the measurement of the supply current being used by a circuit. This may typically be used for power monitoring consumption and providing smart battery management, or to detect fault or misuse conditions causing excessive current, and hence provide a safe shutdown.

The approach is fundamentally very simple – a sensing resistor is inserted in the supply or ground line between the power supply and the circuit. The sense voltage (V_S) dropped across the sensing resistor (R_S) is used to measure the supply current, I :

$$I = V_S / R_S$$

Despite this basic simplicity, there are some potential difficulties with the design of the measurement of supply current measurement circuits, and the possibility of detrimental side effects on the system for which the supply current is being measured.

In consideration

A number of factors may need to be considered when designing supply current measurement circuits. These

include heating and power dissipation in the sense resistor, the effect of ground voltage offset or supply voltage drop on the measured circuit, accuracy of the current measurement required, voltage output of power supply (high voltage circuits may need different approaches) and the physical nature of the ground/chassis in the system.

The value of R_S is typically a fraction of an ohm, possibly only a few milliohms for systems consuming several amps. V_S typically has a value of tens of millivolts. The sense resistor dissipates power, P :

$$P = I^2 R_S$$

Making R_S smaller reduces dissipation, but also makes measuring the consequently smaller V_S less accurate. On the other hand, smaller dissipation will reduce self-heating in R_S which may help accuracy.

If the value of R_S is temperature dependent (which it usually will be), the value of R_S will be different for high and low supply currents and the reading will not be so accurate unless this is taken into account. R_S does not have to be a resistor; it could be a piece of wire or a PCB track (trace).

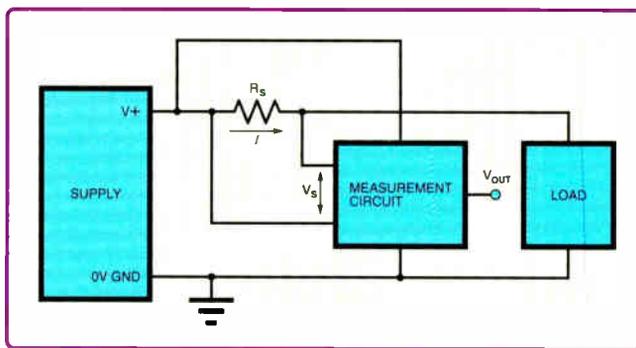


Fig.1: high-side supply current measurement

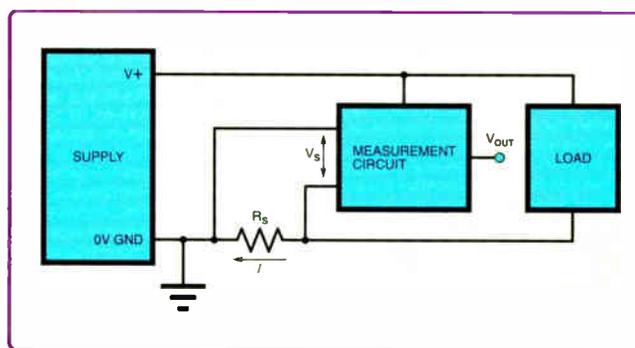


Fig.2: low-side supply current measurement

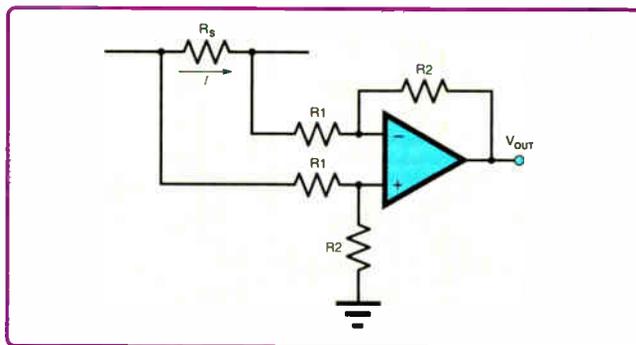


Fig.3: high-side current measurement using a differential amplifier

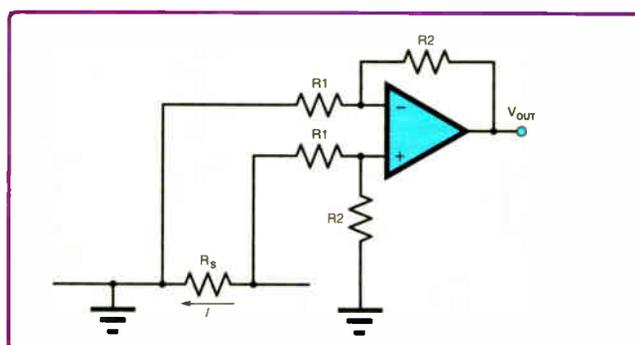


Fig.4: low-side current measurement using a differential amplifier

If the current being sensed has a large high-frequency component, the sense resistor must have low inductance. For example, this would be the case with a fast digital circuit which switched a large number of outputs (such as a bus) simultaneously at speed. Wirewound resistors have the highest inductance and low-inductance metal-film resistors are probably the best choice in many cases.

Implementation approaches

As Chuckieboy indicates, there are a variety of different approaches to circuit implementation. These have different advantages and disadvantages and are suited to different situations. We can build measurement circuits using op amps, but there are also special ICs available for supply current measurement.

One of the key decisions when designing a supply monitor is whether to use high-side or low-side current monitoring. High-side monitoring uses a sense resistor in the supply line, whereas low-side monitoring places it in the ground line. The basic configurations of these two types of supply measurement circuits are shown in Fig.1 and Fig.2.

In general, low-side circuits are easier to design. The sensing circuit sees V_S as a small positive voltage relative to the PSU's ground. This can be easily amplified ready for display on a meter or input to a microcontroller's analogue-to-digital converter (ADC).

However, there is serious problem with low-side monitoring in that the circuit being measured will not have a true ground voltage. Any signal passed between this circuit and other circuitry connected to ground will be subject to

an offset voltage equal to V_S . This will usually be intolerable in any system processing precision analogue signals.

In situations, such as automotive systems where components are grounded by their mechanical connection to the chassis, use of low side monitoring may be impossible. For these reasons high-side monitoring is often preferred.

A differential amplifier using an op amp may be used for both high-side and low-side measurement. Typical circuits are shown in Fig.3 and Fig.4.

CMRR Problem

One problem with the differential amplifier circuit used in Figs. 3 and 4 is that its common mode rejection ratio (CMRR) is very poor or, more specifically, is highly dependent on the accuracy of the resistors used. The differential amplifier's output should depend only on the voltage drop across the sense resistor, but the voltage at the sense resistor appears as a common mode input to the amplifier. If the CMRR is poor, this voltage will influence the amplifier's output, distorting the current measurement.

Use of ordinary 5% or 10% resistors in the differential amplifier circuit will lead to very poor common mode rejection. You need 0.01% resistor accuracy to get just 86dB of CMRR with a perfect op amp!

In an experimental situation you could adjust the resistor values to maximise the CMRR, but you would have to take care that values did not drift. A better solution is to use a differential amplifier IC with built-in accurate resistors, such as the MAX4198 and MAX4199 from Maxim. See Fig.5.

These ICs are described as micropower, single-supply, rail-to-rail, precision

differential amplifiers. The MAX4198 is factory trimmed to a fixed gain of +1V/V, and the MAX4199 is trimmed to a fixed gain of +10V/V. These gains are set with an error of 0.01%.

With these devices the standard differential amplifier configurations provide common-mode rejection of 90dB for the MAX4198 and 110dB for the MAX4199. For further information consult Maxim's datasheet at <http://datasheets.maxim-ic.com/en/ds/MAX4198-MAX4199.pdf>.

CM input range

One important thing you have to watch for when designing supply current monitoring circuits using op amps, is the common mode input range of the op amp. For example, consider Fig.3. The high side sense resistor has one terminal connected to the power supply rail, and by virtue of the small voltage drop essential to prevent this resistor interfering with the measurement, the other side of R_S will be at almost the same voltage. This means that the op amp's common mode input voltage is about equal to the supply voltage.

Not all op amps work happily under such conditions, so this is something you must check when selecting an op amp for this task. The manufacturer's datasheet will detail the acceptable common mode input range. Special high side current monitoring ICs are, of course, designed to cope with large common mode input voltages.

One of the op amps Chuckieboy mentioned trying was the LM324. Unfortunately, the common mode input range specified on the LM324's datasheet (from National Semiconductor, available on line at www.national.com) only goes to 1.5V below the positive supply.

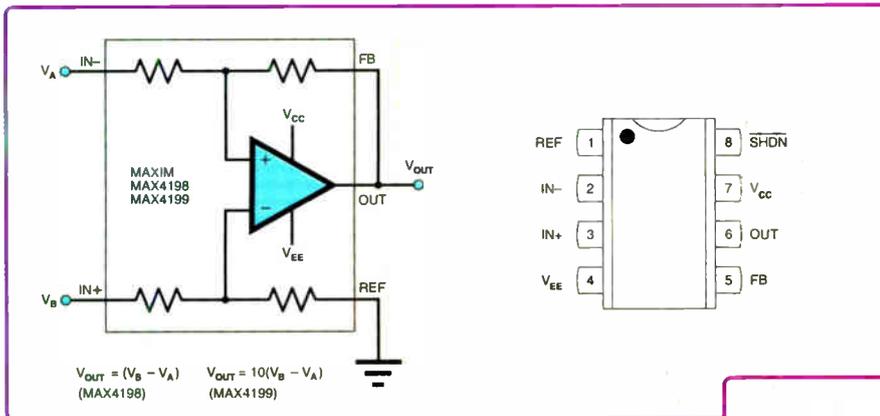


Fig.5: differential amplifier configuration and chip pinout for the MAX4198 and MAX4199 (from Maxim's datasheet)

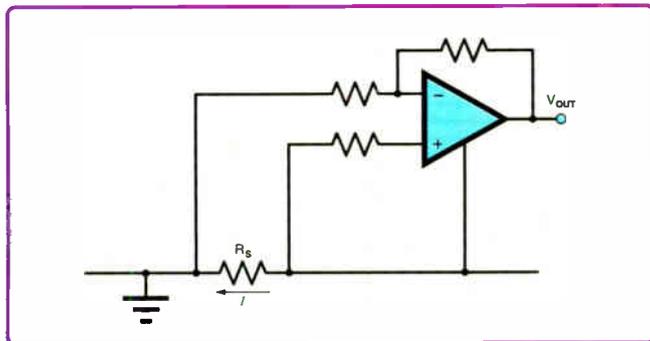


Fig.6: in this configuration the op amp must have an input voltage range that extends below its negative supply voltage

A high-side monitor would exceed that requirement and therefore the LM324 is very unlikely to function correctly (although no damage should occur).

He also mentioned the LT1491 from Linear Technology (www.linear.com), which is a much better choice as it is a micropower rail-to-rail input and output op amp. This op amp is able to cope with common mode signals equal to its supply voltage.

The situation with common mode input range becomes even more difficult if the

op amp's supply pins are the 'wrong' side of the sense resistor. This is illustrated in Fig.6 in which the op amp's common-mode input range must extend below zero by V_S . This capability is rarer than rail-to-rail common mode range, but is a further advantage of the MAX4198 which has an input voltage range which extends 100mV beyond the supply rails.

Special high-side current measurement ICs are also available, for example the range of devices from Maxim, which

includes devices such as MAX4071, MAX4172, MAX 4173 and MAX4372. Fig.7 shows an example of a circuit using one of the specialist current measurement ICs, the MAX4070, which is a bidirectional, high-side, current-sense amplifier with reference. Maxim expects this device to be used for monitoring battery charge and discharge currents in notebooks, cellphones, and other portable equipment.

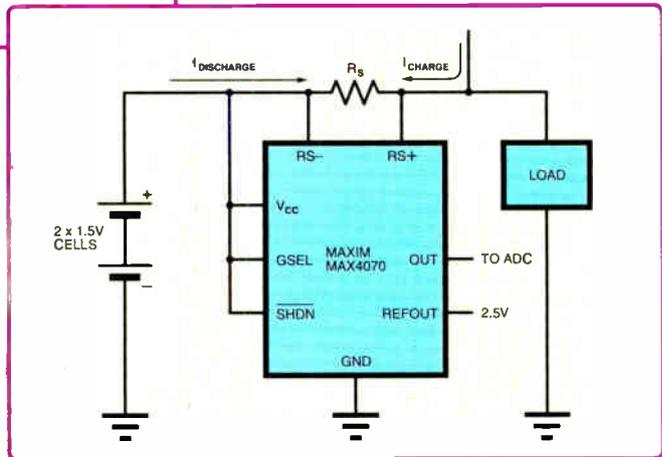


Fig.7: bidirectional current sensing to monitor battery charge and discharge using the MAX4070 (Maxim datasheet)

The output voltage of the circuit in Fig.7 is greater than the reference voltage (2.5V) if the battery is charging and less than the reference if the battery is discharging. The difference between the output and reference is proportional to the current flowing in the sense resistor R_S (charge or discharge) and may be connected to an ADC input of a microcontroller or similar device. For further information consult the datasheet at <http://datasheets.maxim-ic.com/en/ds/MAX4069-MAX4072.pdf>.



agar Circuits

PCB DESIGN & MANUFACTURE
for both the Hobbyist and Professional

PCBs designed and produced from :

- Notes
- Schematics
- Specifications
- Descriptions
- Print - outs
- Gerbers

Available With or without component assembly

* FREE * PCB PROTOTYPE With Quantity Orders

Email: adinfo@agarcircuits.com
Tel: 028 (90) 738 897



Laser Business Systems Ltd
<http://www.laser.com>
<http://www.cbus-shop.com>
 Tel: +44 (0) 20 8441 9788
 Fax: +44 (0) 20 8449 0430
 Email: info@laser.com



C-Bus Shop
CLIPSAL C-Bus
New C-Bus Wireless
 coming soon






We are an authorised distributor of C-Bus intelligent lighting and control system from Clipsal Integrated Systems with an extensive range of home automation related products. We also stock Barix Ethernet based MP3, communications and control products and CAT5e based KAT5 AV transmission and IR control system.

Why tolerate when you can automate?

Ingenuity Unlimited

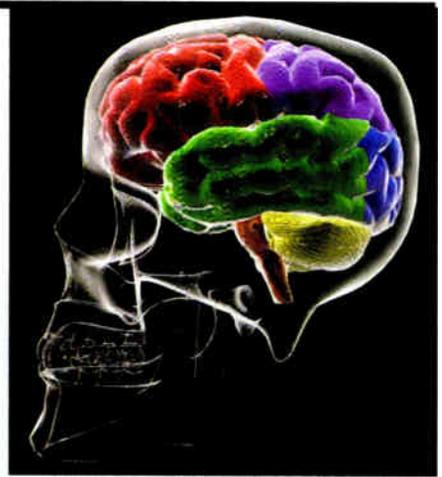

WIN A PICO PC-BASED OSCILLOSCOPE WORTH £586

- 5GS/s Dual Channel Storage Oscilloscope
- 50MHz Spectrum Analyser
- Multimeter
- Frequency Meter
- USB Interface.

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC-based oscilloscope could be yours. Every 12 months, Pico Technology will be awarding a PicoScope 3205 digital storage oscilloscope for the best IU submission. In addition a DrDAQ Data Logger/Scope worth £59 will be presented to the runner up.

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas *must be the reader's own work and must not have been published or submitted for publication elsewhere*. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and include a full circuit diagram showing all component values. **Please draw all circuit schematics as clearly as possible.** Send your circuit ideas to: *Ingenuity Unlimited*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. (We do not accept submissions for IU via email.) Your ideas could earn you some cash and a prize!

Wind Speed Monitor – *How Discretely Bloweth the Wind?*

INSPIRED by John Becker's ingenious original design for measuring wind speed using ultrasonic transducers (*EPE* Jan '03), but lacking his PIC programming skills, the author wondered if a similar method could be used but without a PIC. The design described here works quite well, although it does have some significant performance shortcomings compared to John's elegant PIC-based version and it uses many more ICs.

Fundamentals

The equations associated with the discrete version are as follows, where:

- d = the distance between two pairs of ultrasonic receivers and transmitters, A and B
- v_w = velocity of wind, blowing from B towards A
- v_s = velocity of sound in air
- t_r = response time of receivers (assumed to be the same for both)

The total apparent time for a pulse to travel from A to B against the wind is:

$$t_1 = d/(v_s - v_w) + t_r \quad (1)$$

The total apparent time for the pulse to travel from B to A with the wind is:

$$t_2 = d/(v_s + v_w) + t_r \quad (2)$$

An up/down counter, driven by a clock frequency of f Hz, is enabled to count up during t₁ and down during t₂:

$$\begin{aligned} \text{count up} &= f \times t_1 \\ \text{count down} &= f \times t_2 \end{aligned}$$

If C is the remaining count, then:

$$C = f \times (t_1 - t_2) \quad (C \text{ is positive as } t_1 > t_2)$$

Substituting for t₁ and t₂ from (1) and (2) gives:

$$\begin{aligned} C &= f \times \left(\frac{d}{v_s - v_w} + t_r - \frac{d}{v_s + v_w} - t_r \right) \\ &= f \times \left(\frac{d(v_s + v_w) - d(v_s - v_w)}{(v_s + v_w)(v_s - v_w)} \right) \end{aligned}$$

$$= f \times \left(\frac{2 \times d \times v_w}{(v_s^2 - v_w^2)} \right)$$

But v_s² is much greater than v_w² so C is approx equal to f × 2d × v_w/v_s² (3)

As f, d and v_s are constant, the number held in the counter will be directly proportional to the wind speed.

Calc-Free

To remove the need for any calculations, make:

$$\begin{aligned} f \times 2d/v_s^2 &= 1 \quad (4) \\ \text{then } C &= v_w \end{aligned}$$

Hence the number remaining in the counter will be the actual wind speed in whatever units have been chosen for d, f and v_s. In practice, any convenient clock frequency can be chosen, say 500kHz, and d is then calculated.

Practical Example

For the display in MPH:

$$\begin{aligned} v_s &= 741 \text{ miles/hour} \\ f &= 500\text{kHz} = 500 \times 10^3 \\ \text{count} &= f \times 60 \times 60 \text{ cycles} \\ &\quad \text{per hour} = 1.8 \times 10^9 \end{aligned}$$

$$\begin{aligned} d &= v_s^2/2f \quad \text{from (4)} \\ &= 741^2/(2 \times 1.8 \times 10^9) \text{ miles} \\ &= 1.53 \times 10^{-4} \text{ miles} \\ &= 1.53 \times 10^{-4} \times 3 \times 1760 \text{ feet} \\ &= 0.81 \text{ feet} \\ &= 9.68 \text{ inches (246mm)} \end{aligned}$$

The Circuit

The sequence of operation is controlled by the outputs of a decimal divider, IC7, driven by a 10Hz clock, IC14d (Fig.4). During the period of count 0 to 1, OR gate IC6b closes analogue switch IC2a and connects the first receiver, RX1 and TR1, through IC1a and IC1b (Fig.2), to the reset of one half of D-type flip-flop, IC3 (Fig.3). Resistor R4 and capacitor C3, on pin 5 of IC6b (Fig.2) ensure that its output remains high during the IC's transition from 0 to 1.

At the same time, referring to Fig.1, transmitter TX1 is selected by switch IC2c and the synchronous up/down counter formed by IC10 and IC11 (Fig.5) is set to count up. At the start of count 1 from IC7 (Fig.4) in Fig.1, pin 3 of IC6a triggers a 1ms monostable, IC4, which enables the

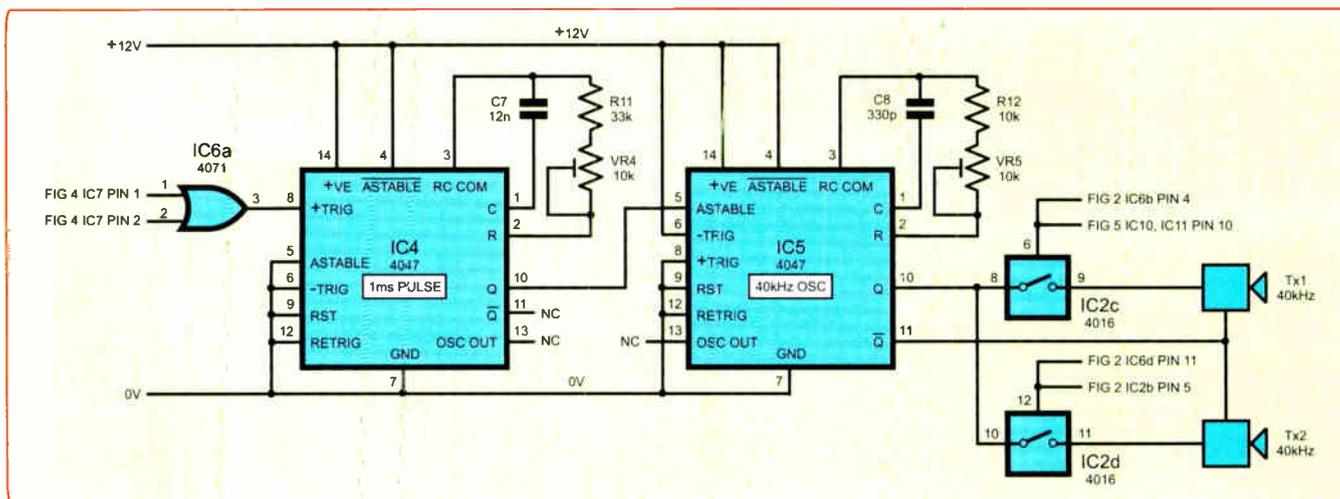


Fig.1 Transmitter driver circuits

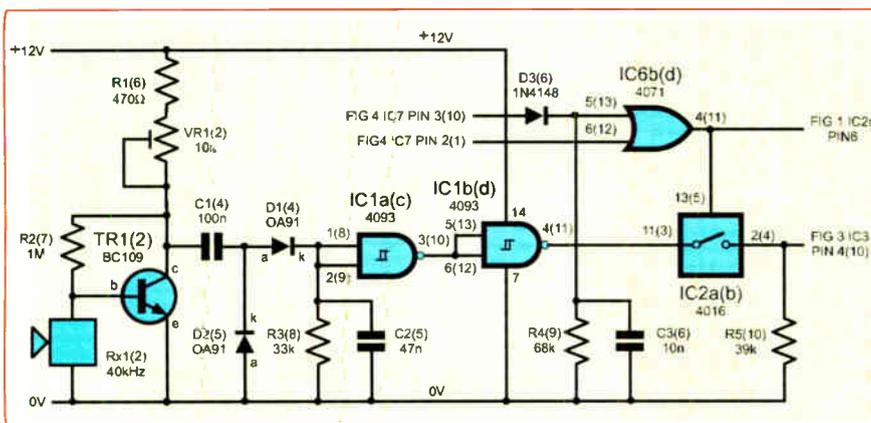


Fig.2. Receiver Circuit

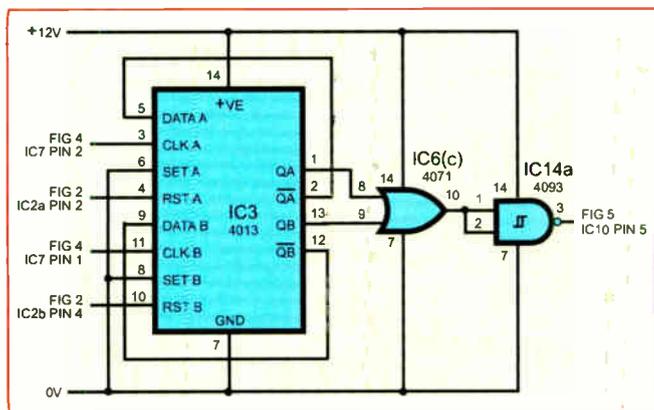


Fig.3. Dual D-type flip-flop stage

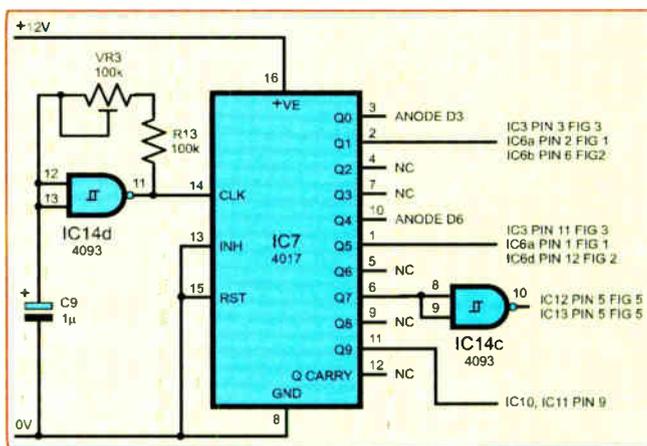


Fig.4. Sequence controller

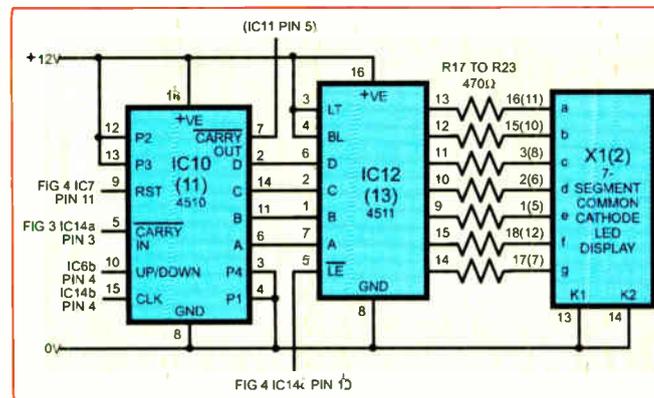


Fig.5. Up/Down counter and display driver

INGENUITY UNLIMITED

BE INTERACTIVE

IU is your forum where you can offer other readers the benefit of your Ingenuity. Share those ideas, earn some cash and possibly a prize.

40kHz oscillator IC5 which drives TX1, sending a pulse to receiver RX1 (Fig.2). Count 1 also clocks one half of flip-flop IC3 (Fig.3), TR1 in Fig.2 goes high and starts the up/down counter (Fig.5) via IC6c and IC14a (Fig.3).

While the pulse is travelling against the wind from TX1 to RX1, the counter is counting up. The counter is driven by a stable clock provided by the 10MHz oscillator module, IC8 (Fig.6). IC9 divides its output by 20 to give 500kHz. As IC8 and IC9 use a 5V stabilised supply (IC16), and the rest of the circuit employs 12V, an LF351 op amp, IC15, is used to restore the logic level to 12V. As the slew rate of the LF351 is inadequate for 500kHz, IC14b squares up the output for the counter. (This is a bit unconventional, but the author had a spares box of op amps!)

When the pulse arrives at RX1 (Fig.2), it is amplified by TR1 and demodulated by germanium diodes D1 and D2. The receiver has a finite response time and as the demodulated pulse rises, it triggers IC1a and is inverted by IC1b, which resets flip-flop IC3 (Fig.3). (The response time is added to the true transit time of the pulse and would appear to cause an error. However, as shown previously, the response times of the two receivers cancel out, provided they are both the same.)

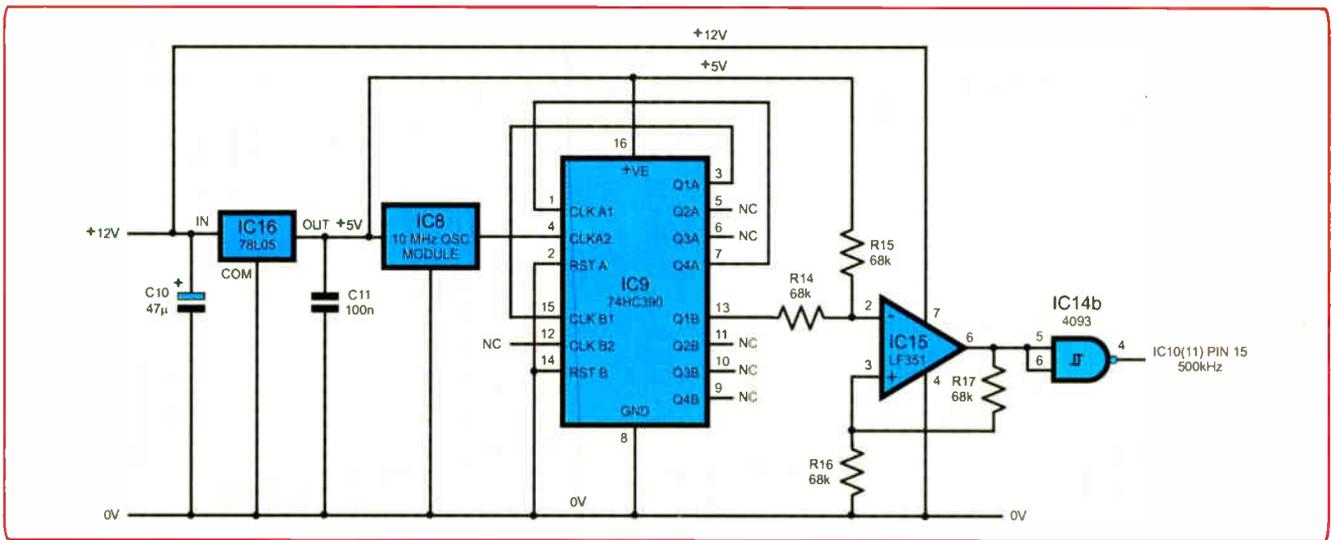


Fig.6. The 500kHz clock and restore logic level section

In Fig.3, as flip-flop IC3 resets, its QA output goes low and the counter is stopped, via IC6c and IC14a. There is then a short delay until count 4. During the period of counts 4 and 5, the output of IC6d goes high and the other receiver, RX2, is selected through the switch IC2b, and the second transmitter, TX2, through IC2d.

The counter (Fig.5) was previously set to count down by IC6b (Fig.2) at the end of count 1. At the start of count 5, IC6a (Fig.1) triggers IC4, enabling IC5 which drives TX2. The counter then counts down until the pulse is received by RX2, which resets the

flip-flop and stops the counter. The outputs of the counters are sent to the two 7-segment LED display drivers IC12 and IC13 (Fig.5).

At count 7 the drivers send the stored number to the LED displays (Fig.5), which show the wind speed. Only two displays are needed as the remaining count is unlikely to exceed 99 (MPH!). At count 9, the counter is reset and the cycle repeats.

Setting Up

Referring to Fig.1, adjust preset potentiometer VR5 to give a frequency of 40kHz from IC5 and maximum output

from the receivers at the collectors of TR1 and TR2 (Fig.2). Set the pulse length from IC4 (Fig.1) to about 1ms with VR4. The sequence controller IC7 (Fig.4) is set by VR3 to run at 10Hz. The display should read zero with no wind. If it does not, adjust VR1 together with VR2 so that each receiver has the same response time.

Stephen Stopford,
London

(John Becker reckons that programming PICs is easier than what Stephen must have gone through to achieve his design!)

PLEASE ENSURE YOU TELEPHONE TO CHECK AVAILABILITY OF EQUIPMENT BEFORE ORDERING OR CALLING.

SPECIAL OFFERS

OSCILLOSCOPES

TEKTRONIX 22474 4 Channel 100MHz Counter/Timer/ Voltmeter	£275
TEKTRONIX 2335 Dual Trace 100MHz Delay Sweep	£125
TEKTRONIX 485 Dual Trace 350MHz Delay Sweep	£300
IWATSU SS5711 4 Channel 100MHz Delay Sweep	£150
PHILIPS 3065 2+1 Channel 100MHz Dual TB/Delay - Autoset	£200
PHILIPS 3065 2+1 Channel 60MHz Dual TB/Delay - Autoset	£150
PHILIPS PM3217 4 Trace 50MHz Delay Sweep	£125
KIKUSUI CS56100 5 Trace 100MHz Delay	£150
TEKTRONIX 475A Dual Trace 250MHz Delay Sweep	£175
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep	£150
TEKTRONIX 465B Dual Trace 100MHz Delay Sweep	£125
TEKTRONIX 465 Dual Trace 100MHz Delay Sweep	£95
PHILIPS PM3209 Dual Trace 40MHz Delay	£125
PHILIPS PM3215 Dual Trace 50MHz	£75
KEWOOD CS4035 Dual Trace 40MHz	£50
PANASONIC VP5564A Dual Trace 40MHz	£50
HITACHI V525 Dual Trace 50MHz Cursors	£95
HITACHI V523 Dual Trace 50MHz Delay	£80
HITACHI V425 Dual Trace 40MHz Cursors	£75
HITACHI V422 Dual Trace 40MHz	£60
HITACHI V223 Dual Trace 20MHz Delay	£60
HITACHI V222 Dual Trace 20MHz	£50
HITACHI V212 Dual Trace 20MHz	£50
FARNELL DTV12-14 Dual Trace 12MHz	£40

STORAGE

PHILIPS PM3320 Dual Trace 200MHz 250Ms/S	£300
LECROY 9400 Dual Trace 125MHz	£325
TEKTRONIX 468 Dual Trace 100MHz Delay Sweep Digital Storage	£200
VELLEMAN HP55 1MHz 5MHz Sampling Handheld Unused	£60

ANALYSERS

ADVANTEST R3265A 100Hz-80Hz	£4500
TEKTRONIX 482P 50kHz-21GHz	£2250
HP8560A 50Hz-2.9GHz Built In Tracking Gen	£3250
HP 8560A 50Hz-2.9GHz	£2950
HP 8569A 10MHz-22GHz	£3950
HP 8565A 10MHz-22GHz	£750
HP 853A with 8559A 100kHz-21GHz	£1100
HP 182T with 8559A 100kHz-21GHz	£750
HP 182T with 8558B 100kHz-1500MHz	£600

HP 182T with 8557A 10kHz-350MHz	£300-£400
HP 140T with 8555A 10MHz-180Hz	£500
ADVANTEST TR4131 10kHz-3.5GHz	£350
WAYNE KERR SS41000A 150kHz-1GHz	£350
MARCONI 2382 200Hz-400MHz High Resolution	£1250
MARCONI 2370 30Hz-110MHz	£500
HP 8754A Network Analyser 4-1300MHz	£500
MARCONI 6500A Amplitude Analyser with head	£750
HP 334A Distortion Analyser 5Hz-600kHz	£100

SIGNAL GENERATORS

HP 8350B Sweeper with 83592B 10MHz-200Hz	£1500
HP 8350A Sweeper with 83592A 10MHz-200Hz	£1250
HP 8350B Main Frame Only	£125
HP 83525B RF Plug-in for 8350 0.01-8.4GHz	£500
HP 83590A RF Plug-in for 8350 2-20GHz	£800
HP 8660C Sig Gen 1.3GHz	£450
HP 8660C Sig Gen 2.6GHz	£750
HP 8660A RF Plug-in for 8660C 1-2500MHz	£
HP8631B Auxiliary Section for 8660C	£
HP8632B Modulation Section for 8660C	£
MARCONI 2017 0.01-124MHz Low Phase Noise	£900
MARCONI 2019 Synthesised AM/FM 80kHz-1040MHz	£325
FLUKE 6060B AM/FM Syn Sig Gen 10kHz-1050MHz	£300
LEADER LSG221B Sig Gen 25-950MHz	£200
HP 8656B Synthesised 0.1-990MHz	£500
HP 8656A Synthesised 0.1-990MHz	£400
HP 8640A AM/FM 500kHz-512MHz	£150
HP 8620C Sweep Osc with 86200B 2-18.6GHz	£500
HP8620C Sweep Osc with 86222B 0.01-2.4GHz	£400
HP8620C/BA with any of the following plug-ins	£150-£200
HP 86220A Plug in 10-1300MHz	£
HP 86230B Plug in 1.5-4GHz	£
HP 86235A Plug in 1.7-4.3GHz	£
HP 86240A Plug in 2-8.5GHz	£
HP 86240C Plug in 3-8-8.6GHz	£
HP 86154A Plug in 5.9-12.4GHz	£
HP86250B Plug in 8-12.4GHz	£
HP 86250D Plug in 8-12.4GHz	£
HP 86260A Plug in 12.4-18GHz	£
MARCONI TF2015 AM/FM 10-520MHz	£95
MARCONI TF2016 AM/FM 10kHz-120MHz	£95
PHILIPS PMS328 100kHz-180MHz with 200MHz Freq Counter IEEE	£225
PANASONIC VP8117A AM/FM 100kHz-110MHz FM 0-100kHz Digital Display etc. Unused	£225

HP 8165A Programmable Signal Source 1MHz-50MHz (Pulse Function)	£325
HP 3325A Synthesised Function Gen 21MHz	£350
HP 3312A Function Gen 0.1Hz-13MHz AM/FM Sleep/Tri/Burst etc.	£290
WAVETEK 21 Stabilised Function Gen 11MHz	£225
WAVETEK 23 Synthesised Function Gen 12MHz	£275
EXACT 529 AM/FM Function Gen 20MHz	£150
ANALOGUE 2030 Synthesised Multi Function Waveform	£250
THANDER TG503 Pulse/Function Gen 5MHz	£195
THANDER TG502 Sweep/Function Gen 5MHz	£195
KRON-HITE 5200A Sweep Func Gen 0.0003Hz-3MHz	£150
HP 3310B Info as 3310A + etc	£120
HP 3310A Func Gen 0.004Hz-5MHz Sine/Sq/Tri/Ramp/Pulse	£80
PHILIPS PMS132 Function Gen 0.1Hz-2MHz	£95
PHILIPS PMS131 Function Gen 0.1Hz-2MHz	£75
FEEDBACK FG601 Func Gen 0.001Hz-1MHz	£60
HP 8112A Pulse Gen 50MHz	£750
HP 8111A Pulse Generator 20MHz	£400
LYONS PG73N Pulse Gen 20MHz	£50
LEADER LAG120B Sine/Sq Audio Generator 10Hz-1MHz	£60
FARNELL LFM4 Sine/Sq Osc 10Hz-1MHz Low Distortion	£60
TTI Output Amplitude Meter	£60
GOULD J3B Sine/Sq Osc 10Hz-100kHz Low Distortion	£50-£75
FARNELL LFI Sine/Sq Oscillator 10Hz-1MHz	£50
MARCONI SANDERS 6055C Signal Source 850-2000MHz	£125
MARCONI SANDERS 6055B Signal Source 850-2150MHz	£125
MARCONI SANDERS 6055A Signal Source 2-4GHz	£125
MARCONI SANDERS 6057B Signal Source 4.5-8.5GHz	£125
MARCONI SANDERS 6059A Signal Source 12-18GHz	£125
MARCONI SANDERS 6070A Signal Source 400-1200MHz	£125
FLUKE 6011A Synthesised 11MHz	£125
PHILIPS S514V Colour Bar Generator Video	£95
BLACK STAR ORION Colour Bar Gen	£150
BLACK STAR ORION Later Version Metal Case	£75

HP 5316A Universal Counter 0-100MHz HP/IB	£395
THANDER TF810 Frequency Counter 5Hz-200MHz Battery	£60
THANDER TF200 Frequency Counter 10Hz-200MHz 8 digit	£40
BLACK STAR Meteor 100 Counter 5Hz-100MHz	£50
BLACK STAR 1225 Counter Timer 1300MHz	£150
BECKMAN LC101A Universal Counter 120MHz	£160
LEADER LDC903A Digital Counter 100MHz	£125

DIGITAL MULTIMETERS etc

SOLARTRON 7150 6 1/2 digit True RMS IEEE	£70
SOLARTRON 7150P/Plus As Above + Temp Measurement	£100
DATRON 1065 5 1/2 digit Autocal AC/DC Resistance IEEE	£75
FLUKE 77 3 1/2 digit Handheld	£35
FLUKE 77 Series 2 3/4 digit Handheld	£45
FLUKE 8060A 1 1/2 digit True RMS Handheld	£75
BECKMAN HD110 3 1/2 digit Handheld in Carry Case	£30
TTI 1905A 5 1/2 digit Bench	£60
SOLARTRON 7045 4 1/2 digit Bench	£30
AVO DA116 3 1/2 digit with Batteries & Leads	£20
AVO 8 MM5 in Ever Ready Case with Leads etc	£75
AVO 8 MM5 with Leads etc	£60
RACAL 9301A True RMS R/F Millivoltmeter	£125
RACAL 9300 True RMS Millivoltmeter 5Hz-20MHz usable to 60MHz	£30
RACAL 9300B 9300	£45
GOODWILL GVT427 Dual Chan AC Millivoltmeter 10mV in 12 ranges 10Hz-1MHz Unused	£75
KENWOOD VT176 Dual Chan Millivoltmeter	£40

POWER SUPPLIES

FARNELL XA35.2T 0-35V 0-2A Twice Digital	£95
FARNELL L7302 0-30V 0-2A Twice	£110
FARNELL B3020 30V 20A Variable No Meters	£110
FARNELL B3010 30V 10A Variable No Meters	£75
FARNELL L7301 0-30V 0-1A Twice	£75
FARNELL L302 0-30V 0-2A	£75
FARNELL L301 0-30V 0-1A	£40
FARNELL E350 0-350V 0-200mA	£125
FARNELL D30-2T 0-30V 0-2A Twice Digital	£75
THURLBY PL330 0-32V 0-3A Digital (Kenwood badged)	£75
THURLBY TS30215 0-30V 0-2A LCD	£65
THURLBY PL320 0-30V 0-2A Digital	£55
TAKASAGO GMO35-3 0-35V 0-3A 2 Meters	£45
TAKASAGO TMO35-2 0-35V 0-2A 2 Meters	£35
ISOLATING TRANSFORMER - Yellow - 500VA with 13Amp Socket	£35

STEWART of READING

17A King Street, Mortimer, Near Reading RG7 3RS

Telephone: (0118) 933 1111. Fax: (0118) 933 2375

www.stewart-of-reading.co.uk

Open 9am-5.00pm Monday to Friday (other times by arrangement)

Used Equipment - GUARANTEED. Manuals supplied

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists.

Please check availability before ordering.

CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage

READOUT

Email: john.becker@wimborne.co.uk

John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

All letters quoted here have previously been replied to directly.

WIN AN ATLAS LCR ANALYSER WORTH £79

An Atlas LCR Passive Component Analyser, kindly donated by Peak Electronic Design Ltd., will be awarded to the author of the *Letter Of The Month* each month.

The Atlas LCR automatically measures inductance from 1 μ H to 10H, capacitance from 1pF to 10,000 μ F and resistance from 1 Ω to 2M Ω with a basic accuracy of 1%.
www.peakelec.co.uk



★ LETTER OF THE MONTH ★

Congrats and Suggestions

Dear EPE,

I just want to say 'Thank you!' for Mike Hibbett's wonderful *C or PICs* series in *EPE* recently. The series has prompted me (a middle-aged molecular biologist without formal electronics and programming training, who's been reading *EPE* and other mags for many years, but hardly finds the time to build and program anything outside his head) to buy a PIC programmer and a few PIC18Fs, and learn to program them in C as a summer project (I'm in New Zealand).

Being a novice to C, I wouldn't have succeeded without Mike's articles, despite having some programming experience (Perl, VB). It's always those first few steps to get over the initial hurdle – we call it 'activation energy'. Biological enzymes and chemical catalysts work by lowering that hurdle, and these articles have been exactly that – a great catalyst!

Given the large code space and low price of the 18F PICs, and C18/MPLAB, I find it hard to justify learning to program them in assembler. So I would like to encourage you to continue writing about the topic – personally, I feel a few more examples incorporating standard tasks would be most helpful.

How about re-coding some of the assembler examples Microchip provides for their demo boards? Using those, your readers won't have to build hardware as it is (more) economical to buy the demo boards – (those wanting to can do so as both circuit and PCB layout are on the Microchip website); you could just refer to the circuitry 'as per Microchip' without sacrificing page space; and the *EPE* community will gain a nice collection of code 'snippets' covering most routine jobs.

Furthermore, I think we need more help using the USB facility on these chips, as Microchip's documentation is not very comprehensive, and a little too abstract even for 'initiated' novices. Mike's latest articles cover sending data via USB to a PIC very well. How about describing how to send data from a PIC via USB to a PC. Again, writing code for some of the circuits previously published in *EPE* would be useful and *EPE* won't have to re-publish the circuits.

For example, using one of the Dallas sensors to measure temperature, using a PIC to keep it constant and log the data while offline from the PC, sending stored data to the PC and checking for new settings when connected would be fantastic.

The bootloader itself is also worth more coverage, as I have seen statements that Microchip's C code won't fit in lower registers of the 2550 when compiled with the student edition of the compiler (once the optimisations are disabled). And describing how to connect to the PIC on the USB port using one or more of the visual languages (C#, VB, Delphi, all of which are now available free to hobbyists) would be a very welcome one-off article.

Finally, the Microchip website has a reference to add Ethernet connectivity to PICs – that would be cool to learn with C, as would be hooking PICs up to some of the now very cheap USB devices – Bluetooth, WiFi, etc.

Regarding a constructional project involving hardware, maybe a relationship with Microchip could be of interest – something like an extended demo board that is used to test all the functions accessed via the C code described in the future series. Microchip should welcome this, as it will expose more users to their chips, and you will help train

their future customers, which can only be good for them.

Klaus Lehnert, Auckland, New Zealand, via email

We do have a tie-up with Microchip and will be running some articles from them in the future – there will also be a free Microchip CDROM with the June issue.

Mike Hibbett replied to Klaus:

Thank you for your comments, the feedback is always welcome!

Regarding 'code snippets', I think it's an excellent idea – I'll try to set up something, like a library of useful functions for the PIC. It's unlikely that I would re-write existing assembly code though, since this can just be linked into a C project if needed. I'll probably be covering how to link in assembly language routines in a later article.

Your point about the USB project is well noted; as much as we hobbyists love RS232 it is a 'dying' interface and we are all going to have to embrace USB or Ethernet at some point. I will probably cover more on USB in the months to come.

I see you have noticed that Microchip have moved into providing Ethernet solutions – I noticed too! I have some samples of their Ethernet to SPI interface IC, and I have already planned to include an article on it in Pic'N'Mix at some point this year. It's a great little IC, one I have been waiting some time for, and I'm looking forward to playing with it.

Thank you very much for the comments. I am a great fan of the C language, and was very pleased when EPE agreed to let me share my enthusiasm with readers by writing the articles. Programming is great fun and I hope you continue to enjoy it.

Mike Hibbett, via email

Wind Power

Following on from the Editorial in the Feb '07 issue, there have been a number of letters on the subject of alternative power sources. It has also come up on the EPE Chat Zone recently (access via www.epemag.co.uk). Here are a few of the letters we've received by email.

Mike Mee:

I believe that *EPE* can provide some very useful construction articles on alternative power generation, but not in the way suggested. As you point out, Bull Group offer wind turbines, as do B&Q, so why

attempt mechanical construction in an electronics magazine?

The way forward has to be with the electronics required to provide 240V AC from any of the generation methods, i.e. wind, photovoltaic or water wheel.

There are two possible routes here, depending on whether power is to be stored or not. If storage batteries are required the first item is a charger of some sophistication that can take in virtually any DC voltage up to about 150V and *correctly* charge the battery connected to it.

Commercial units seem to be able to be set for batteries up to 60V in 12V

increments, some are even able to auto-sense and select the required voltage. Currents in the region of 30A to 60A.

Inverters – with the battery as above, the inverter can be set for a certain input voltage, which might make for a slightly easier design. Inverters designed for direct input, no batteries, must take whatever is thrown at them, i.e. 75V to 150V, even 250V to 500V in some cases, and provide 240V AC with a true sinusoidal waveform suitable for grid connection.

The next interesting bit is that the inverter should be able to synchronise with the National Grid and auto connect itself when

it has something to give, and to give all it can in preference to the mains supply. Power of 3kW+ would be useful, so that many people could at least run the immersion heater in summer and shut off the gas boiler for six months, or supplement the AC mains requirements for the full year. There are many options here, and one heck of a challenge!

While the Grid supply people don't seem to mind me connecting home made projects requiring power via a transformer to the mains, I think they may be a bit more fussy about power producing systems being paral- lled to them as the consequences of 'out of phase' connection are interesting to put it mildly! I have some experience of this as a marine engineer paralleling generator sets – **don't get it wrong!**

Modern electronics is up to it, you just need the designers. What about it?

www.windsave.com – this site, I think is the supplier to B&Q and provides about 1kW to a 13A socket i.e. erect windmill and plug into the household ring main.

www.unlimited-power.co.uk – this site is worth looking at for the data sheets of chargers, inverters, photovoltaic cells and wind turbines, and general information and inspiration.

David Houghton:

The Feb '07 Editorial was a welcome confirmation of the conclusion I had nearly reached on domestic wind turbines. I have been researching alternative energy for some time and it is very difficult to be realistic as opposed to being self-deceived into believing there is a bargain of free energy just waiting to be collected. I for one would welcome guidance on other DIY alternative options. The comparison of light outputs from various sources in the same issue was useful too.

Solar cells produce little current at low voltage. Solar collectors might be worth- while from the energy angle but they look unsightly on the roof and if one's plumbing is working fine it seems a pity to disturb it.

Would collecting rain water give better rewards than alternatives for those with water meters? An additional higher roof tank might be employed so that its head of water is used in preference to the mains. That tank could be topped up by water from butts pumped by electricity from solar cells solely when it's available. No need to store the electricity in batteries, just store a head

of water. Precautions would need to be taken, for example to avoid damage to ceil- ings due to the extra weight in the roof.

How about having a small area solar col- lector with large area parabolic mirrors reflecting the sun onto it? Has a communi- ty group geothermal energy source been investigated to overcome the objection of it being too big a project for one household?

These are just a few of the options and objections that *EPE* could investigate for readers with the initial emphasis on point- ing our efforts to potentially fruitful alter- native projects. I won't carry out my plan to replace some of our kitchen concealed flu- orescents with LEDs now that I've learned they are less efficient!

How about it *EPE*, can you do the research and tell us the best options with detailed projects to follow?

Peter Woffinden:

After reading in Feb'07 about wind tur- bines, I think you should publish something, even if it's only a small whirlygig type that produces up to 12V at around 100mA. I have been playing around for about a year and built one out of a car alternator with neomydium magnets in the rotor. The blades are made from 8-inch diameter pipe that I hope to use to charge the battery on an electric fence unit/bird scarer. I haven't sorted the controller to stop it overcharging the battery yet.

Well readers, are there any among you who have the necessary expertise to take up the challenges for EPE? Drop us an email or letter.

Network Servers and PICs

Dear *EPE*,

I've been subscribing to *EPE Online* for a few years now. Recently there's been a net server developed, the PICAXE Net Server, which is fine but could one of your authors start the development of a Net Server using one of the 18F series of PICs, particularly with one of the newer 18F PICs of the species, 4550, 4620 or better. I'm sure there would be masses of interest, especially as it would enable security control from anywhere on the planet plus many other uses of remote control too numerous to mention.

The code could also be written in C which would further boost popularity. I know that now there's interest in developing code for Microchip PICs in C++, I use the FED C compiler, FED advertise with you and I know

that Robin Abbott is at this moment develop- ing his version of the FED C++ compiler, we're waiting with eager anticipation. As they say, the future's bright.

Glynne Hewlett, via email

I sent Glynne's comments on to Mike Hibbett, who replied to him:

Small network servers (a microcontroller with a TCP/IP 'internet stack') have been around for a few years now. One of the first really useful designs was the PicoWeb, for which the design is still available at www.picoweb.net.

One of the main obstructions to building such a unit, however, has been the difficulty in purchasing a suitable ethernet interface IC. These ICs tend to be very fine pitch too. Things are improving however; Microchip are soon to release PIC microcontrollers with an internal ethernet interface, and in an easy to use package. You may rest assured that when these parts become readily available, your wishes will be addressed!

Mike Hibbett, via email

Project Index

Dear *EPE*,


I thought you might like to know that I have a database containing details of all con- structional projects published in *EPE* since 1992 (when I first bought the magazine). The database is available either as an MS Access file or with a stand-alone application included to view and search for projects by description or year.

I update the details at the end of each year from the published index, so the database cur- rently has projects to the end of 2006. Both versions can be downloaded from **www.elec- tronics2000.co.uk**. I originally made the database for my own use, never being able to find old projects I wanted to refer to, and find it invaluable from time to time.

Incidentally, I'm sure you used to publish indexes on your website but I can't find them anymore. If you did it would save a lot of typ- ing next year! Keep up the good work with the magazine.

Simon Carter MEng MIET, via email

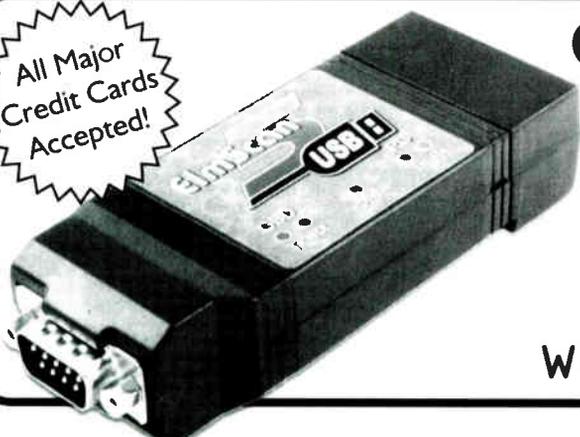Thanks Simon. In fact there is a Project Index for 1998 to 2006 on our UK website, via www.epemag.co.uk. Click on 'Project Index' on the top left corner of the home page.



ElmScan 5 USB Scan Tool

All Major Credit Cards Accepted!

- Diagnose any car with EOBD
- Based on the ELM327 IC
- Supports all EOBD and OBD-II protocols
 - ✓ ISO15765-4 (CAN)
 - ✓ ISO14230-4 (Keyword 2000)
 - ✓ ISO9141-2
 - ✓ J1850 VPW
 - ✓ J1850 PWM
- 9600 or 38400 baud
- Supported by more software than any other OBD interface
- Inexpensive
- Full Speed USB 1.1
- Automatic protocol detection
- Package includes cables, software CD, and Quick Start Guide
- Buy from your local UK distributors!

www.ElmScan5.com/epe



CAN-1 Board - Interface CAN via MCP2551
\$18.00 USD

CAN-2 Board - Make CAN network with SPI interface
\$21.00 USD

RS485 Board - Connect devices into RS-485 network
\$17.00 USD

Serial Ethernet - Make ethernet network with SPI Interface (ENC28J60)
\$28.00 USD

CF Board - Easy way to use Compact flash in your design
\$18.00 USD

MMC/SD Board - Easy way to use MMC and SD cards in your design
\$18.00 USD

EEPROM Board - Serial EEPROM board via I2C interface
\$9.00 USD

RTC Board - PCF8583 RTC with battery backup
\$16.00 USD

ADC Board - 12-bit analog-to-digital converter(ADC) with 4 inputs
\$22.00 USD

DAC Board - 12-bit digital-to-analog converter(DAC) with SPI
\$18.00 USD

Keypad 4x4 Board - Add keypad to your application
\$9.00 USD

Accel. Board - Accel. is an electronic device that will measure acceleration forces
\$16.00 USD

PICFlash
with mikroICD support


PICFlash programmer - an ultra fast USB 2.0 programmer for PIC microcontrollers. Continuing its tradition as one of the fastest PIC programmer on the market, the new PICFlash with mikroICD now supports more PIC MCUs giving the developer a wider choice of PIC MCU for further prototype development. mikroICD debugger enables you to execute mikroC / mikroPascal / mikroBasic programs on a host PIC microcontroller and view variable values. Special Function Registers (SFR), memory and EEPROM as the program is running.....**\$89.00 USD**

- All of our products are shipped in special protective boxes.
- On-line secure ordering provides a fast and safe way to buy our products.

Find your distributor: UK, USA, Germany, Japan, France, Spain, Greece, Turkey, Italy, Slovenia, Croatia, Macedonia, Pakistan, Malaysia, Austria, Taiwan, Switzerland, Lebanon, Syria, Egypt, Portugal

EasyPIC4 Development Board

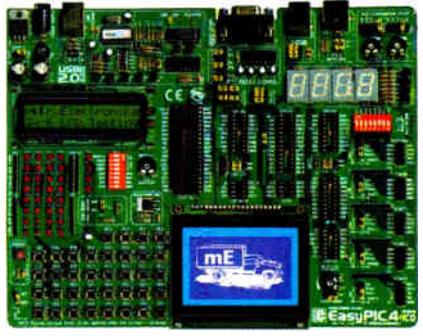with on-board USB 2.0 programmer and mikroICD



3 in 1 DEVELOPMENT SYSTEM

HARDWARE
LCD ON-BOARD
USB 2.0
ON-BOARD PROGRAMMER
PERFORMANCE
DEVELOPMENT BOARD

EasyPIC4 development board: Following in the tradition of the EasyPIC3 as one of the best PIC development systems on the market, the EasyPIC4 has more new features for the same price. The system supports 8, 14, 18, 20, 28 and 40 pin PIC microcontrollers (it comes with a PIC16F877A).



mikroICD is a highly effective tool for Real-Time debugging on a hardware level. The ICD debugger enables you to execute a mikroC/mikroPascal/mikroBasic program on a host PIC microcontroller and view variable values. Special Function Registers (SFR), memory and EEPROM as the program is running.

On-board USB 2.0 PICFlash programmer - an ultra fast USB 2.0 programmer for fast MCU programming. Continuing its tradition as the fastest PIC programmer on the market, the new PICFlash with mikroICD now supports more PIC MCUs giving the developer a wider choice of PIC MCU for further prototype development.



Package contains: EasyPIC4 development system, USB cable, Serial cable, User's manual, mikroICD, mikroC/mikroPascal/mikroBasic drivers and examples; in C, BASIC and Pascal language. Note: LCD, DS1220 temp., sensor and GLCD are optional.

EasyPIC4 Development System **\$119.00 USD**
Optional:
2x16 LCD and DS1820 temperature sensor **\$15.00 USD**
Graphic LCD 128x64 dots **\$17.00 USD**

mikroElektronika Compilers

Pascal, Basic and C Compilers for various microcontrollers



Supporting an impressive range of microcontrollers, an easy-to-use IDE, hundreds of ready-to-use functions and many integrated tools makes MikroElektronika compilers one of the best choices on the market today. Besides mikroICD, mikroElektronika compilers offer a statistical module, simulator, bitmap generator for graphic displays, 7-segment display conversion tool, ASCII table, HTML code export, communications tools for SD/MMC, UDP (Ethernet) and USB, EEPROM editor, programming mode management, etc.

Each compiler has many routines and examples such as EEPROM, FLASH and I2C, SD card reading/writing, writing to character and graphic LCDs, manipulation of push-buttons, 4x4 keyboard and PS/2 keyboard input, generation of signals and sounds, character string manipulation, mathematical calculations, I2C, SPI, RS232, CAN, USB, RS485 and Cwireless communications, Manchester coding management, logical and numerical conversion, PWM signals, interrupts, etc. The CD-ROM contains many ready-written and tested programs for use with our development boards.

Regular price:	Price with discount:
mikroBasic(PIC) \$49.00 USD	mikroBasic(PIC) (-30%) \$34.30 USD
mikroPascal(PIC) \$49.00 USD	mikroPascal(PIC) (-30%) \$34.30 USD
mikroC(PIC) \$249.00 USD	mikroC(PIC) (-30%) \$174.30 USD

mikroBasic(AVR) \$149.00 USD	mikroBasic(AVR) (-30%) \$104.30 USD
mikroPascal(AVR) \$149.00 USD	mikroPascal(AVR) (-30%) \$104.30 USD

mikroBasic(dsPIC) \$149.00 USD	mikroBasic(dsPIC) (-30%) \$104.30 USD
mikroPascal(dsPIC) \$249.00 USD	mikroPascal(dsPIC) (-30%) \$174.30 USD
mikroC(dsPIC) \$249.00 USD	mikroC(dsPIC) (-30%) \$174.30 USD

LV24-33 Development Board

The Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroICD

System supports 64, 80 and 100 pin PIC24F/24H/dsPIC33F microcontrollers (it comes with PIC24FJ96GA010 - PIC24 16-bit Microcontroller, 96 KB Flash Memory, 8 KB RAM in 100 Pin Package). Examples in BASIC, PASCAL and C are included with the system. You can choose between USB or External Power supply. LV 24-33 has many features that makes your development easy. Explore new PIC24F/24H/dsPIC33F PIC MCUs with LV 24-33 and experience all advantages of this microcontrollers.

LV24-33 Development System **\$149.00 USD**

Uni-DS 3 Development Board

with on-board USB 2.0 programmer

System supports PIC, AVR, 8051, ARM and PSoC microcontrollers with a large number of peripherals. It is enough to switch a card and continue working in the same development environment but with a different chip. Uni-DS3 has many features that makes your development easy. You can choose between USB or External Power supply. Each MCU card has own USB 2.0 programmer on it!

Uni-DS3 Development System [with one MCU card]..... **\$199.00 USD**

dsPICPRO2 Development Board

with on-board USB 2.0 programmer

System supports dsPIC microcontrollers in 64 and 80 pin packages. It is delivered with dsPIC30F6014A microcontroller. The dsPICPRO2 development system is a full-featured development board for Microchip dsPIC MCU. dsPICPRO2 board allows microcontroller to be interfaced with external circuits and a broad range of peripheral devices. This development board has an on-board USB 2.0 programmer and integrated connectors for SD/CF memory cards, 2 x RS232 port, RS485, CAN, DAC etc..

dsPICPRO2 Development System **\$239.00 USD**

EasyARM Development Board

with on-board USB 2.0 programmer

EasyARM board comes with Philips LPC2214 microcontroller. Each jumper, element and pin is clearly marked on the board. It is possible to test most of the industrial needs on the system: temperature controllers, counters, timers etc. EasyARM has many feature to make your development easy. One of them - on-board USB 2.0 programmer with automatic switch between 'run' and 'programming' mode. Examples in C language are provided with the board.

EasyARM Development System **\$149.00 USD**

Easy8051A Development Board

with on-board USB 2.0 programmer

System is compatible with 14, 16, 20 and 40 pin microcontrollers (it comes with AT89S8252). USB 2.0 programmer is built in and programming can be done without removing the microcontroller. Many industrial applications can be tested on the system: temperature controllers, counters, Easy8051A development system is a full-featured development board for 8051 microcontrollers. It was designed to allow students or engineers to easily exercise and explore the capabilities of the 8051 microcontrollers.

Easy8051A Development System **\$114.00 USD**

BIGPIC4 Development Board

with on-board USB 2.0 programmer and mikroICD

Following in the tradition of its predecessor, the BIGPIC3 as one of the best 80-pin PIC development systems on the market, BIGPIC4 continues tradition with more new features for same price. System supports the latest 64 and 80-pin PIC microcontrollers (it is delivered with PIC18F8520). Many ready made examples guarantee successful use of the system. Ultra fast on-board programmer and mikroICD (In-circuit Debugger) enables very efficient debugging and faster prototype developing. Examples in C, BASIC and Pascal language are provided with the board.

BIGPIC4 Development System **\$132.00 USD**

EasyAVR4 Development Board

with on-board USB 2.0 programmer

System supports 8, 20, 28 and 40 pin microcontrollers (it comes with ATMEGA16). Each jumper, element and pin is clearly marked on the board. It is possible to test most of the industrial needs on the system: temperature controllers, counters, timers etc. EasyAVR4 is an easy to use Atmel AVR development system. On-board USB 2.0 programmer makes your development easy. Examples in BASIC and Pascal language are provided with the board.

EasyAVR4 Development System **\$114.00 USD**

EasyPSoC3 Development Board

with on-board USB 2.0 programmer

System supports 8, 20, 28 and 48 pin microcontrollers (it comes with CY8C27843). Each jumper, element and pin is clearly marked on the board. EasyPSoC3 is an easy to use PSoC development system. On-board USB 2.0 programmer provides fast and easy in system programming. EasyPSoC3 has many features that makes your development easy. You can choose between USB or External Power supply. EasyPSoC3 also supports Character LCD as well as Graphic LCD.



EasyPSoC3 Development System **\$169.00 USD**

EasypsPIC3 Development Board

with on-board USB 2.0 programmer

System supports 18, 28 and 40 pin microcontrollers (it comes with dsPIC30F4013 general purpose microcontroller with internal 12 bit ADC). EasypsPIC3 has many features that makes your development easy. Many ready made examples in C, BASIC and PASCAL language guarantee successful use of the system. On-board USB 2.0 programmer allows for faster prototype development.

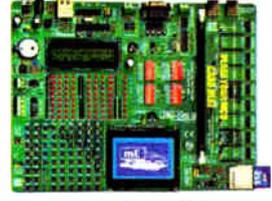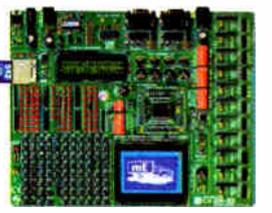EasypsPIC3 Development System **\$119.00 USD**



Net Work



Alan Winstanley

A failing memory

A staple ingredient of many users' Internet diets is eBay, the online emporium that sells new and used merchandise in every classification imaginable. Most transactions are completed successfully and there are millions of satisfied buyers and sellers.


Sometimes, though, a deal seems too good to be true. The photo shows a new 2GB USB memory branded as Kingston, one of the top names in memory components. A buyer sourced this via eBay for a price that is much less than branded sellers; the eBay seller played the common trick of charging excess for postage, which doubled the cost to about £16 (\$32), totalling a few pounds cheaper than other web sites. The only problem is that it turned out to be a counterfeit. It is a remarkable copy of a reputable product, with extremely convincing packaging, accessories, barcodes and multi-lingual instructions. Even a seasoned buyer would be fooled.

The story unfolded when the product failed in use, and close-up photographs were emailed to Kingston, who soon confirmed that the item was not genuine. Memory chips are graded after manufacture and the rejects are not reliable enough for the number of read/write cycles that a USB thumb drive will experience. So the drive suddenly packed up on the job, without giving its owner any written notice beforehand.



This Kingston USB memory drive was purchased via eBay – a convincing counterfeit.

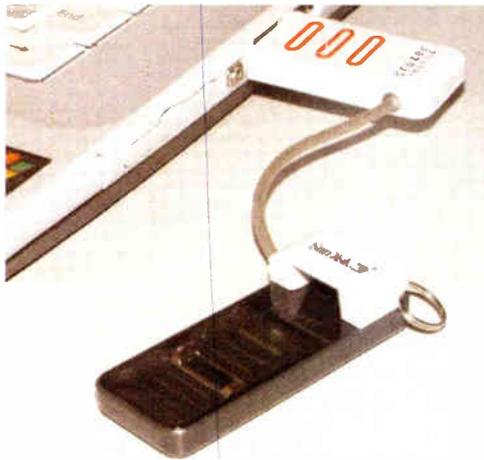(below) Sandisk Cruzer Profile memory contains an effective fingerprint scanner



(having a feedback score of several thousand) related to herbal remedies, aromatherapeutic goods and, erm, physique enhancement products. So ask yourself the question, where would such a seller get a box of 48 cheap 2GB Kingston DataTraveler memory drives from? One could be generous and assume that he bought them in good faith, but from whom? Unfortunately eBay is one method used to fence stolen or counterfeit goods, though eBay clearly acted very swiftly when a verified report of counterfeit sales was submitted.

Biometric memory gets a thumbs-up

Continuing on the subject of USB memory drives and data security, the author has been using an interesting biometric device made by Sandisk. The Sandisk Cruzer Profile is a 512k or 1GB drive that contains a fingerprint scanner. It uncouples to form a USB plug with a 7cm flexible wire connected to a combined memory drive and fingerprint scanner that works surprisingly well. It requires a USB port and will not work on an unpowered hub.

One of the great benefits of the Cruzer Profile is its ability to capture network or website logins that are accessible only by swiping a registered fingerprint. You could log into your eBay account, PayPal or even the EPE Chat Zone forum, simply by tapping the Cruzer icon in the system tray, point to the website you wish to log into, and then swipe a finger across the scanner. The system is pleasingly accurate and once a print has been scanned – usually successful first time – the owner of the dexterous digit is automatically logged in to the appropriate web page. A border around the web page briefly flashes to register the secure login.

And if your favourite forefinger is smothered in a Band-Aid, no problem: the Sandisk Cruzer profile software will register (or 'enrol') all ten prints, if preferred. The device is completely portable as the software and logins are contained within the fingerprint-protected USB drive. Simply plug it into a port, and then open up by scanning a print. It is an ideal accessory for a laptop, but you may need a USB extension lead (see eBay) to run the device on your desk. You can buy the Sandisk Cruzer Profile from Misco (www.misco.co.uk) or via Amazon.co.uk from about £16.00.


You can E-mail me at:

alan@epemag.demon.co.uk

Where does this leave the buyer? It seems they have bought a hard-luck story. The item was 'pulled' from eBay within the hour after Kingston notified eBay of the forgeries. Kingston, however, was not interested in compensating those who had reported the illicit copies to them, and consequently they missed a low-cost opportunity to reciprocate with some goodwill, e.g. by replacing the item for a genuine product.

Individuals have to follow the complaints procedures of eBay and PayPal and some users can be forgiven for giving up. For some buyers, the feeling of being ripped off would be a very corrosive one and, incensed at losing £15 on a transaction, they would spend their valuable time trying to claw back their money, complaining to Trading Standards, eBay, PayPal, magazines and more beside, while others will just shrug and write it off to experience.

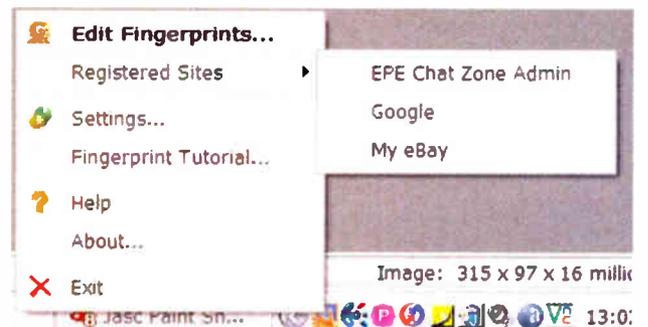Looking at the seller's credentials, alarm bells should really have sounded before the eBay deal was struck: the seller's other items



Simply select your website, scan your fingerprint and the device will open the webpage and log you in automatically

YOU WON'T GET YOUR FINGERS BURNT

It may surprise you but buying an Antex soldering iron costs less than you think in the long run. British made to exacting standards, they last significantly longer than imported brands. And with a wide range of thermally balanced soldering irons, you can pick up a "fixed temperature" or "in-handle" temperature model that will suit your needs perfectly.

None of which will burn a hole in your pocket.

If your hobby demands the best iron for the job but you don't want to get your fingers burnt by the cost, visit our website or your electronics retailer for the coolest models around.

Pick up an

ANTEX


Not just any old iron.



www.antex.co.uk

2 Westbridge Industrial Estate Tavistock,
Devon PL19 8DE Tel 01822 613565

Build Your Own Weather Station

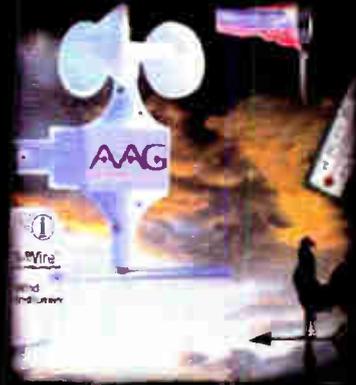

- ▶ Measure Wind Speed
- ▶ Measure Wind Direction
- ▶ Measure Temperature
- ▶ Easy Build Kit
- ▶ FREE Software
- ▶ USB or RS232
- ▶ Optional Humidity Module
- ▶ Optional Pressure Module
- ▶ Optional Rainfall Gauge
- ▶ Simple 1-wire® connection
- ▶ Build and add your own devices

Weather Starter Kit	£59
RS232 Interface	£25
USB Interface	£29
Humidity Module	£39
Pressure Module	£49
Rainfall Gauge	£59

Prices exclude VAT and delivery

For more information, manuals and downloads on this and other interesting products see www.audon.co.uk

AUDON Electronics

www.audon.co.uk | +44 (0)115 925 8412 | Fax +44 (0)115 925 9757

SHERWOOD ELECTRONICS

FREE COMPONENTS

Buy 10 x £1 Special Packs and choose another one FREE

SP1 15 x 5mm Red LEDs	SP135 5 x Miniature slide switches
SP2 12 x 5mm Green LEDs	SP136 3 x BFY50 transistors
SP3 12 x 5mm Yellow LEDs	SP137 4 x W005 1.5A bridge rectifiers
SP4 25 x 3mm 1 part LED clips	SP138 20 x 2.2/63V radial elect. caps
SP5 16 x 3mm Red LEDs	SP140 3 x W04 1.5A bridge rectifiers
SP6 12 x 3mm Green LEDs	SP142 2 x CMOS 4017
SP7 10 x 3mm Yellow LEDs	SP143 5 Pairs min. crocodile clips (Red & Black)
SP8 25 x 3mm 1 part LED clips	SP144 5 Pairs min. crocodile clips (assorted colours)
SP9 100 x 1N4146 diodes	SP146 10 x 2N3704 transistors
SP10 50 x 1N4001 diodes	SP147 5 x Stripboard 9 strips x 25 holes
SP11 50 x 1N4002 diodes	SP151 4 x 8mm Red LEDs
SP12 20 x BC182 transistors	SP152 4 x 8mm Green LEDs
SP13 20 x BC184 transistors	SP153 4 x 8mm Yellow LEDs
SP14 20 x BC549 transistors	SP154 15 x BC549 transistors
SP15 4 x CMOS 4001	SP156 3 x Stripboard, 14 strips x 27 holes
SP16 4 x 555 timers	SP160 10 x 2N3904 transistors
SP17 4 x 741 Op.Amps	SP161 10 x 2N3906 transistors
SP18 4 x CMOS 4011	SP164 2 x C106D thyristors
SP19 3 x CMOS 4013	SP165 2 x LF351 Op.Amps
SP20 4 x CMOS 4081	SP166 20 x 1N4003 diodes
SP21 20 x 1N914 diodes	SP167 5 x BC107 transistors
SP22 25 x 10/25V radial elect. caps.	SP168 5 x BC108 transistors
SP23 12 x 100/35V radial elect. caps.	SP171 8 Metres 18SWG solder
SP24 15 x 47/25V radial elect. caps.	SP172 4 x Standard slide switches
SP25 10 x 470/16V radial elect. caps.	SP173 10 x 220/25V radial elect. caps
SP26 15 x BC237 transistors	SP174 20 x 22.25V radial elect. caps
SP27 20 x Mixed transistors	SP175 20 x 1/63V radial elect. caps
SP28 5 x Min. PB switches	SP177 10 x 1A 20mm quick blow fuses
SP29 4 x 5 metres stranded core wire	SP178 10 x 2A 20mm quick blow fuses
SP30 8 Metres 22SWG solder	SP181 5 x Phono plugs - assorted colours
SP31 20 x 8-pin DIL sockets	SP182 20 x 4.7/63V radial elect. caps
SP32 15 x 14-pin DIL sockets	SP183 20 x BC547 transistors
SP33 15 x 16-pin DIL sockets	SP187 15 x BC239 transistors
SP34 4 x 74LS00	SP189 4 x 5 metres solid core wire
SP35 109 x BC557 transistors	SP192 3 x CMOS 4066
SP36 4 x CMOS 4093	SP195 3 x 10mm Yellow LEDs
SP37 3 x 10mm Red LEDs	SP197 6 x 20 pin DIL sockets
SP38 3 x 10mm Green LEDs	SP198 5 x 24 pin DIL sockets
SP39 2 x CMCS 4047	SP199 5 x 2.5mm mono jack plugs
SP40 20 x Assorted ceramic disc caps	SP200 5 x 2.5mm mono jack sockets
SP41 6 x Battery clips - 3 ea. PP3 + PP9	
SP42 100 x Mixed 0.5W C.F. resistors	
SP43 2 x TL071 Op.Amps	
SP44 20 x 1N4304 diodes	
SP45 15 x 1N4007 diodes	

RESISTOR PACKS - C.Film

RP3 5 each value - total 365 0.25W	£3.40
RP7 10 each value - total 730 0.25W	£4.65
RP10 1000 popular values 0.25W	£6.60
RP4 5 each value-total 345 0.5W	£4.30
RP8 10 each value-total 690 0.5W	£6.95
RP11 1000 popular values 0.5W	£8.95

2007 Catalogue available £1 inc. P&P or FREE with first order. P&P £1.75 per order. NO VAT Cheques and Postal Orders to: **Sherwood Electronics, 7 Williamson St., Mansfield, Notts. NG19 6TD.**

DIRECT BOOK SERVICE

NOTE: ALL PRICES INCLUDE UK POSTAGE

FREE Two booklets and a Circuit Surgery CD-ROM with Teach-In 2000 CD-ROM



EPE TEACH-IN 2000 CD-ROM

The whole of the 12-part *Teach-In 2000* series by John Becker (published in *EPE* Nov '99 to Oct 2000) is now available on CD-ROM. Plus the *Teach-In 2000* interactive software (Win 95, 98, ME and above) covering all aspects of the series and Alan Winstanley's *Basic Soldering Guide* (including illustrations and Desoldering).

Teach-In 2000 covers all the basic principles of electronics from Ohm's Law to Displays, including Op.Amps, Logic Gates etc. Each part has its own section on the interactive software where you can also change component values in the various on-screen demonstration circuits.

The series gives a hands-on approach to electronics with numerous breadboard circuits to try out, plus a simple computer interface (Win 95, 98, ME only) which allows a PC to be used as a basic oscilloscope.

ONLY £12.45 including VAT and p&p

Order code Teach-In CD-ROM

Circuits and Design

A BEGINNER'S GUIDE TO TTL DIGITAL ICs

R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip/flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in the "real world".

142 pages

Order code BP332

£5.45

PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Bridges the gap between complicated technical theory, and "cut-and-try" methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias - tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-Current Circuits, Passive Components, Alternating-Current Circuits, Networks and Theorems, Measurements.

256 pages

Order code BP53

£5.49

MICROCONTROLLER COOKBOOK

Mike James

The practical solutions to real problems shown in this cookbook provide the basis to make PIC and 8051 devices really work. Capabilities of the variants are examined, and ways to enhance these are shown. A survey of common interface devices, and a description of programming models, lead on to a section on development techniques. The cookbook offers an introduction that will allow any user, novice or experienced, to make the most of microcontrollers.

240 pages

Order code NE26

£23.50

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

FOR A FURTHER SELECTION OF BOOKS SEE THE NEXT TWO ISSUES OF EPE

All prices include UK postage

EASY PC CASE MODDING

R.A Penfold

Why not turn that anonymous grey tower, that is the heart of your computer system, into a source of visual wonderment and fascination. To start, you need to change the case or some case panels for ones that are transparent. This will then allow the inside of your computer and it's working parts to be clearly visible.

There are now numerous accessories that are relatively inexpensive and freely available, for those wishing to customise their PC with added colour and light. Cables and fans can be made to glow, interior lights can be added, and it can all be seen to good effect through the transparent case. Exterior lighting and many other attractive accessories may also be fitted.

This, in essence, is case modding or PC Customising as it is sometimes called and this book provides all the practical details you need for using the main types of case modding components including:- Electro luminescent (EL) 'go-faster' stripes; Internal lighting units; Fancy EL panels; Data cables with built-in lighting; Data cables that glow with the aid of 'black' light from an ultraviolet (UV) tube; Digital display panels; LED case and heatsink fans; Coloured power supply covers.

192 pages

Order code BP542

£8.99

NEWNES PC TROUBLESHOOTING POCKET BOOK - SECOND EDITION

Howard Anderson, Mike Tooley

All the essential data for PC fault-finding and upgrading. This book provides a concise and compact reference that describes, in a clear and straightforward manner, the principles and practice of fault-finding and upgrading PCs and peripherals. The book is aimed at anyone who is involved with the installation, configuration, maintenance, upgrading, repair or support of PC systems. It also provides non-technical users with sufficient background information, charts and checklists to enable the diagnosis of faults and help to carry out simple modifications and repairs. In order to reflect rapid changes in computer technology (both hardware and software) this new edition has been completely revised and rewritten.

256 pages

Order code NE41

£20.50

NEWNES INTERFACING COMPANION

Tony Fischer-Cripps

A uniquely concise and practical guide to the hardware, applications and design issues involved in computer interfacing and the use of transducers and instrumentation.

Newnes Interfacing Companion presents the essential information needed to design a PC-based interfacing system from the selection of suitable transducers, to collection of data, and the appropriate signal processing and conditioning.

Contents: Part 1 - Transducers; Measurement systems; Temperature; Light; Position and motion; Force, pressure and flow. Part 2 - Interfacing; Number systems; Computer architecture; Assembly language; Interfacing; A to D and D to A conversions; Data communications; Programmable logic controllers; Data acquisition project. Part 3 - Signal processing; Transfer function; Active filters; Instrumentation amplifier; Noise; Digital signal processing.

295 pages

Order code NE38

£31.00

Computing & Robotics

WINDOWS XP EXPLAINED

N. Kantaris and P. R. M. Oliver

If you want to know what to do next when confronted with Microsoft's Windows XP screen, then this book is for you. It applies to both the Professional and Home editions.

The book was written with the non-expert, busy person in mind. It explains what hardware requirements you need in order to run Windows XP successfully, and gives an overview of the Windows XP environment.

The book explains: How to manipulate Windows, and how to use the Control Panel to add or change your printer, and control your display; How to control information using WordPad, Notepad and Paint, and how to use the Clipboard facility to transfer information between Windows applications; How to be in control of your filing system using Windows Explorer and My Computer; How to control printers, fonts, characters, multimedia and images, and how to add hardware and software to your system; How to configure your system to communicate with the outside world, and use Outlook Express for all your email requirements; How to use the Windows Media Player 8 to play your CDs, burn CDs with your favourite tracks, use the Radio Tuner, transfer your videos to your PC, and how to use the Sound Recorder and Movie Maker; How to use the System Tools to restore your system to a previously working state, using Microsoft's Website to update your Windows set-up, how to clean up, defragment and scan your hard disk, and how to backup and restore your data; How to successfully transfer text from those old but cherished MS-DOS programs.

268 pages

Order code BP514

£7.99

INTRODUCING ROBOTICS WITH LEGO MINDSTORMS

Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various "click-together" components supplied in the basic RIS kit. Explains in simple terms how the "brain" of the robot may be programmed on screen using a PC and "zapped" to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Detailed building and programming instructions provided, including numerous step-by-step photographs.

288 pages - large format

Order code BP901

£14.99

MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS - Robert Penfold

Covers the Vision Command System

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using Lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with 'waiter service' when you clap your hands, perform tricks, 'see' and avoid objects by using 'bats radar', or accurately follow a line marked on

the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit.OCX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an 'intelligent' sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

298 pages

Order code BP902

£14.99

THE PIC MICROCONTROLLER YOUR PERSONAL INTRODUCTORY COURSE - THIRD EDITION John Morton

Discover the potential of the PIC microcontroller through graded projects - this book could revolutionise your electronics construction work!

A uniquely concise and practical guide to getting up and running with the PIC Microcontroller. The PIC is one of the most popular of the microcontrollers that are transforming electronic project work and product design.

Assuming no prior knowledge of microcontrollers and introducing the PICs capabilities through simple projects, this book is ideal for use in schools and colleges. It is the ideal introduction for students, teachers, technicians and electronics enthusiasts. The step-by-step explanations make it ideal for self-study too: this is not a reference book - you start work with the PIC straight away.

The revised third edition covers the popular reprogrammable Flash PICs: 16F54/16F84 as well as the 12F508 and 12F675.

270 pages

Order code NE36

£18.50

INTRODUCTION TO MICROPROCESSORS AND MICROCONTROLLERS - SECOND EDITION

John Crisp

If you are, or soon will be, involved in the use of microprocessors and microcontrollers, this practical introduction is essential reading. This book provides a thoroughly readable introduction to microprocessors and microcontrollers. Assuming no previous knowledge of the subject, nor a technical or mathematical background. It is suitable for students, technicians, engineers and hobbyists, and covers the full range of modern micros.

After a thorough introduction to the subject, ideas are developed progressively in a well-structured format. All technical terms are carefully introduced and subjects which have proved difficult, for example 2's complement, are clearly explained. John Crisp covers the complete range of microprocessors from the popular 4-bit and 8-bit designs to today's super-fast 32-bit and 64-bit versions that power PCs and engine management systems etc.

222 pages

Order code NE31

£22.00

Testing, Theory and Reference

THE AMATEUR SCIENTIST CD-ROM

The complete collection of The Amateur Scientist articles from *Scientific American* magazine. Over 1,000 classic science projects from a renowned source of winning projects. All projects are rated for cost, difficulty and possible hazards.


Plus over 1,000 pages of helpful science techniques that never appeared in *Scientific American*.

Exciting science projects in: Astronomy; Earth Science; Biology; Physics; Chemistry; Weather . . . and much more! The most complete resource ever assembled for hobbyists, and professionals looking for novel solutions to research problems. Includes extensive Science Software Library with even more science tools.

Suitable for Mac, Windows, Linux or UNIX. 32MB RAM minimum, Netscape 4.0 or higher or Internet Explorer 4.0 or higher. Over 1,000 projects

Order code AS1 CD-ROM

£19.95

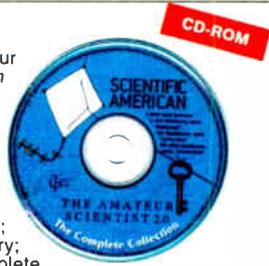

BEBOP BYTES BACK (and the Bebop Computer Simulator) CD-ROM

Clive (Max) Maxfield and Alvin Brown

This follow-on to *Bebop to the Boolean Boogie* is a multimedia extravaganza of information about how computers work. It picks up where "Bebop I" left off, guiding you through the fascinating world of computer design . . . and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the CD-ROM contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the CD-ROM contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this!

Over 800 pages in Adobe Acrobat format

Order code BEB2 CD-ROM

£21.95



GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

96 pages

Order code BP239

£5.49

OSCILLOSCOPES – FIFTH EDITION

Ian Hickman

Oscilloscopes are essential tools for checking circuit operation and diagnosing faults, and an enormous range of models are available.

This handy guide to oscilloscopes is essential reading for anyone who has to use a 'scope for their work or hobby; electronics designers, technicians, anyone in industry involved in test and measurement, electronics enthusiasts . . . Ian Hickman's review of all the latest types of 'scope currently available will prove especially useful for anyone planning to buy – or even build – an oscilloscope.

The contents include a description of the basic oscilloscope; Advanced real-time oscilloscope; Accessories; Using oscilloscopes; Sampling oscilloscopes; Digital storage oscilloscopes; Oscilloscopes for special purposes; How oscilloscopes work (1): the CRT; How oscilloscopes work (2): circuitry; How oscilloscopes work (3): storage CRTs; plus a listing of Oscilloscope manufacturers and suppliers.

288 pages



Order code NE37

£24.00

PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING

Robin Pain

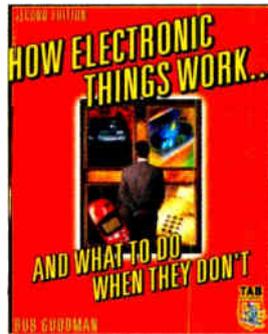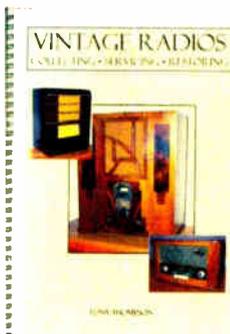To be a real fault finder, you must be able to get a feel for what is going on in the circuit you are examining. In this book Robin Pain explains the basic techniques needed to be a fault finder.



Simple circuit examples are used to illustrate principles and concepts fundamental to the process of fault finding. This is not a book of theory, it is a book of practical tips, hints and rules of thumb, all of which will equip the reader to tackle any job. You may be an engineer or technician in search of information and guidance, a college student, a hobbyist building a project from a magazine, or simply a keen self-taught amateur who is interested in electronic fault finding but finds books on the subject too mathematical or specialised.

The fundamental principles of analogue and digital fault finding are described (although, of course, there is no such thing as a "digital fault" – all faults are by nature analogue). This book is written entirely for a fault finder using only the basic fault-finding equipment: a digital multimeter and an oscilloscope. The treatment is non-mathematical (apart from Ohm's law) and all jargon is strictly avoided.

274 pages

Order code NE22

£28.99

ELECTRONIC TEST EQUIPMENT HANDBOOK

Steve Money

In most applications of electronics, test instruments are essential for checking the performance of a system or for diagnosing faults in operation, and so it is important for engineers, technicians, students and hobbyists to understand how the basic test instruments work and how they can be used.

The principles of operation of the various types of test instrument are explained in simple terms with a minimum of mathematical analysis. The book covers analogue and digital meters, bridges, oscilloscopes, signal generators, counters, timers and frequency measurement. The practical uses of these instruments are also examined.

206 pages

Order code PC109

£9.95

DIGITAL GATES AND FLIP-FLOPS

Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of micro-processor techniques as applied to digital logic.

200 pages

Order code PC106

£9.95

UNDERSTANDING ELECTRONIC CONTROL SYSTEMS

Owen Bishop

Owen Bishop has produced a concise, readable text to introduce a wide range of students, technicians and professionals to an important area of electronics. Control is a highly mathematical subject, but here maths is kept to a minimum, with flow charts to illustrate principles and techniques instead of equations.

Cutting edge topics such as microcontrollers, neural networks and fuzzy control are all here, making this an ideal refresher course for those working in industry. Basic principles, control algorithms and hardwired control systems are also fully covered so the resulting book is a comprehensive text and well suited to college courses or background reading for university students.

The text is supported by questions under the headings Keeping Up and Test Your Knowledge so that the reader can develop a sound understanding and the ability to apply the techniques they are learning.

228 pages

Order code NE35

£22.50

HOW ELECTRONIC THINGS WORK – AND WHAT TO DO WHEN THEY DON'T

Robert Goodman

You never again have to be flummoxed, flustered or taken for a ride by a piece of electronics equipment. With this fully illustrated, simple-to-use guide, you will get a grasp on the workings of the electronic world that surrounds you – and even learn to make your own repairs.

You don't need any technical experience. This book gives you: Clear explanations of how things work, written in everyday language. Easy-to-follow, illustrated instructions on using test equipment to diagnose problems. Guidelines to help you decide for or against professional repair. Tips on protecting your expensive equipment from lightning and other electrical damage. Lubrication and maintenance suggestions.

Covers: colour TVs, VCRs, radios, PCs, CD players, printers, telephones, monitors, camcorders, satellite dishes, and much more!

394 pages

Order code MGH3

£21.99

VINTAGE RADIOS – COLLECTING ● SERVICING ● RESTORING

Tony Thompson

The essential guide to collecting, repairing and restoring vintage valve radios. These receivers are becoming ever more popular as collectibles, this is a good thing because it means that a very large piece of technological history is being reclaimed when at one time many thought it lost forever. If you look around, you will find plenty of valve radio sets just waiting for a loving restoration. They may not yet be the most highly prized, and they are unlikely to be in top condition, but they can be yours and, if you develop the skills outlined in this book, you will possess radio receivers to be proud of.

The book covers radio history, styling, faultfinding, chassis and cabinet restoration, types of set.

124 pages spiral bound

Order code TT1

£13.50

All prices include UK P&P

Project Building

ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including the following topics:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering; making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby.

135 pages **Order code BP392** £5.49

BUILDING VALVE AMPLIFIERS

Morgan Jones

The practical guide to building, modifying, fault-finding and repairing valve amplifiers. A hands-on approach to valve electronics – classic and modern – with a minimum of theory. Planning, fault-finding, and testing are each illustrated by step-by-step examples.

A unique hands-on guide for anyone working with valve (tube in USA) audio equipment – as an electronics experimenter, audiophile or audio engineer.

Particular attention has been paid to answering questions commonly asked by newcomers to the world of the vacuum tube, whether audio enthusiasts tackling their first build, or more experienced amplifier designers seeking to learn the ropes of working with valves. The practical side of this book is reinforced by numerous clear illustrations throughout.

368 pages **Order code NE40** £22.50

Theory and Reference

THE EMERGENCE OF BROADCASTING IN BRITAIN

Brian Hennessy

The beginning of any great enterprise should be recorded for posterity. Few knew that the *Children's Hour* "Uncles", Arthur, Jeff and Caractacus, were also the engineers who struggled by day to develop technical equipment – and would soon become Assistant Controller, Station Director and Organiser of Programmes for the BBC.

This is a very human account, from the dawn of radio to the attainment of a Royal Charter in the late 1920s. It tells of the struggles and frustrations of engineers in developing innovative equipment and of the great John Reith who battled with everyone to bring the BBC from a staff of four up to a Corporation of several hundred.

Brian Hennessy's book also describes the development of broadcasting equipment, the search for premises and looming bankruptcy before ending with the emergence of a firmly established Chartered Corporation – the BBC.

Meticulous research over many years, over a hundred photographs, plans and diagrams as well as interviews with many of those who were there at the time, make this a valuable and original work for those involved in media studies, for radio enthusiasts or simply for those interested in radio and the fascinating story of the emergence of broadcasting.

436 pages **Order code EBB** £26.00

COIL DESIGN AND CONSTRUCTIONAL MANUAL

B. B. Babani

A complete book for the home constructor on "how to make" RF, IF, audio and power coils, chokes and transformers. Practically every possible type is discussed and calculations necessary are given and explained in detail. Although this book is now twenty years old, with the exception of toroids and pulse transformers little has changed in coil design since it was written.

96 pages **Order code BP160** £4.49

PRACTICAL ELECTRONIC FILTERS

Owen Bishop

This book deals with the subject in a non-mathematical way. It reviews the main types of filter, explaining in simple terms how each type works and how it is used.

The book also presents a dozen filter-based projects with applications in and around the home or in the constructor's workshop. These include a number of audio projects such as a rhythm sequencer and a multi-voiced electronic organ.

Concluding the book is a practical step-by-step guide to designing simple filters for a wide range of purposes, with circuit diagrams and worked examples.

188 pages **Order code BP299** £5.49

ELECTRONIC PROJECTS FOR EXPERIMENTERS

R. A. Penfold

Many electronic hobbyists who have been pursuing their hobby for a number of years seem to suffer from the dreaded "seen it all before" syndrome. This book is fairly and squarely aimed at sufferers of this complaint, plus any other electronics enthusiasts who yearn to try something a bit different.

The subjects covered include:- Magnetic field detector, Basic Hall effect compass, Hall effect audio isolator, Voice scrambler/descrambler, Bat detector, Bat style echo location, Noise cancelling, LED stroboscope, Infra-red "torch", Electronic breeze detector, Class D power amplifier, Strain gauge amplifier, Super hearing aid.

138 pages **Order code BP371** £5.45

PRACTICAL FIBRE-OPTIC PROJECTS

R. A. Penfold

While fibre-optic cables may have potential advantages over ordinary electric cables, for the electronics enthusiast it is probably their novelty value that makes them worthy of exploration. Fibre-optic cables provide an innovative interesting alternative to electric cables, but in most cases they also represent a practical approach to the problem. This book provides a number of tried and tested circuits for projects that utilize fibre-optic cables.

The projects include:- Simple audio links, F.M. audio link, P.W.M. audio links, Simple d.c. links, P.W.M. d.c. link, P.W.M. motor speed control, RS232C data links, MIDI link, Loop alarms, R.P.M. meter.

All the components used in these designs are readily available, none of them require the constructor to take out a second mortgage.

132 pages **Order code BP374** £5.45

STARTING ELECTRONICS, THIRD EDITION

KEITH BRINDLEY

A punchy practical introduction to self-build electronics. The ideal starting point for home experimenters, technicians and students who want to develop the real hands-on skills of electronics construction.

A highly practical introduction for hobbyists, students, and technicians. Keith Brindley introduces readers to the functions of the main component types, their uses, and the basic principles of building and designing electronic circuits.

Breadboarding layouts make this very much a ready-to-run book for the experimenter, and the use of multimeter, but not oscilloscopes, and readily available, inexpensive components makes the practical work achievable in a home or school setting as well as a fully equipped lab.

288 pages **Order code NE42** £11.50

VIDEO PROJECTS FOR THE ELECTRONICS CONSTRUCTOR

R. A. Penfold

Written by highly respected author R. A. Penfold, this book contains a collection of electronic projects specially designed for video enthusiasts. All the projects can be simply constructed, and most are suitable for the newcomer to project construction, as they are assembled on stripboard.

There are faders, wipers and effects units which will add sparkle and originality to your video recordings, an audio mixer and noise reducer to enhance your soundtracks and a basic computer control interface. Also, there's a useful selection on basic video production techniques to get you started.

Circuits include: video enhancer, improved video enhancer, video fader, horizontal wiper, improved video wiper, negative video unit, fade to grey unit, black and white keyer, vertical wiper, audio mixer, stereo headphone amplifier, dynamic noise reducer, automatic fader, pushbutton fader, computer control interface, 12 volt mains power supply.

124 pages **Order code PC115** £5.45

BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £2 per book. For the rest of the world airmail add £3 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard, Amex, Diners Club or Maestro to:

**DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LTD.,
408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery – more for overseas orders. Please check price and availability (see latest issue of *Everyday Practical Electronics*) before ordering from old lists.

For a further selection of books see the next two issues of *EPE*.

Tel 01202 873872 Fax 01202 874562. Email: dbs@wimborne.co.uk

Order from our online shop at: www.epemag.co.uk

BOOK ORDER FORM

Full name:

Address:

.....

.....

..... Post code: Telephone No:

Signature:

I enclose cheque/PO payable to DIRECT BOOK SERVICE for £

Please charge my card £ Card expiry date

Card Number Maestro Issue No.....

Card Security Code (the last three digits on or just under the signature strip)

Please send book order codes:

.....

Please continue on separate sheet of paper if necessary
If you do not wish to cut your magazine, send a letter or copy of this form

PCB-POOL®

SERVICING YOUR COMPLETE PROTOTYPE NEEDS

1 EUROCARD
(160 x 100 mm)
+ Tooling
+ Photoplots
+ VAT

€49

Price example
Any size and contour possible

Optional:

- Soldermask
- Fast-turnaround
- Silkscreen
- 4-Layer Multilayer
- 6-Layer Multilayer

DOWNLOAD OUR FREE LAYOUT SOFTWARE!

Over 18,000 Customers

Freephone 0800-3898560

tel.: +353 (0)61 701170
fax: +353 (0)61 701165
pcb-pool@businesspool.com

Simply send your files and order ONLINE: **PCB-POOL.COM**

PEAK

tel. 01298 70012
fax. 01298 70046
www.peakelec.co.uk
sales@peakelec.co.uk

electronic design ltd

Handheld Test Gear - Cool, Smart

Atlas DCA
Semiconductor Analyser £35

Atlas LCR
Passive Component Analyser £79

Atlas ESR
Capacitance and ESR Meter £39

Atlas SCR
Triac/Thyristor Analyser £109

Prices include UK delivery and VAT

No Compromise Oscilloscope

Other oscilloscopes in this price range force you to compromise on one of the key specifications: sampling rate, memory depth or bandwidth.

The PicoScope 5000 series is a no compromise PC oscilloscope at a price every engineer can afford.

www.picotech.com/scope401 01480 396395

pico Technology

- 1GS/s sampling rate
- 250MHz bandwidth
- 128M sample buffer memory
- 125MS/s 12 bit AWG built in

PicoScope 5203
32M buffer £1195

PicoScope 5204
128M buffer £1795

PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. Double-sided boards are NOT plated through hole and will require 'vias' and some components soldering both sides. All prices include VAT and postage and packing. Add £1 per board for *airmail* outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872; Fax 01202 874562; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm.** Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only). **NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail.** Back numbers or photocopies of articles are available if required – see the *Back Issues* page for details. We do not supply kits or components for our projects.

Please check price and availability in the latest issue. A large number of older boards are listed on, and can be ordered from, our website.

Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
Photic Phone – Transmitter – Receiver	OCT '05 531 } pair	£6.98
Back-To-Basics 7 – Parking Radar – Telephone Switch	533 } 534 } pair	£5.71 £5.55
★ Halloween Howler	535	£6.02
★ PIC-Based USB Interface	536	£6.19
★ PIC Chromatone	NOV '05 537	£6.82
Back-To-Basics 8 – Noughts and Crosses Enigma – Weather Vane Repeater	538 } 539 } pair	£6.66 £6.18
★ Multi-Function F/C Switch	540	£5.87
★ Speed Camera Watch Mk2	541	£6.35
Solid-State Valve Power Supply	DEC '05 542	£6.35
★ Vehicle Frost Box Mk2	543	£5.71
★ Propeller Monitor	544	£6.02
Solid-State Hammond	545	£6.18
★ PIC Ambilux Sunset Switch	JAN '06 546 } 547 } pair	£5.71 £6.98
Current Clamp Adaptor for Multimeters	548	£5.39
★ Tiptronic-Style Gear Indicator – Micro Board – Display Board – Hall Speed Board	549 } 550 } 551 } set	£7.61
★ Keypad Alarm	FEB '06 552	£6.02
3-Way Active Crossover	553	£9.20
Jazzy Heart	554	£6.02
Status Monitor– Transmitter – Receiver	555 } 556 } pair	£7.61
Power Up Video/Audio Booster (double-sided)	MAR '06 557 } 558 } pair	£6.82 £12.00
★ Telescope Interface	559	£6.50
'Smart' Slave Flash	APR '06 560	£6.18
Programmable Continuity Tester PortaPAL	561	£5.87
– Microphone Board	562	£6.18
– Auxiliary Board	563	£5.87
– Main Board	564	£8.56
– Charger Board	565	£6.66
Omni Pendulum	566	£6.34
Smart Card Reader/Programmer	MAY '06 567	£7.61
LED Lighting For Your Car (set of 15 boards)	568	£14.75
Digital Reaction Timer	569	£7.13
Poor Man's Metal Locator	JUN '06 570	£5.71
★ Digital Instrument Display for Cars – Micro Board – Display Board	571 } 572 } pair	£7.77
Widgy Box	573	£7.29
Phone Ring & Test	574	£6.82
★ Sudoku Unit	JUL '06 575	£6.66
PC Power Monitor	576	£6.50
Home Theatre Sound Level Checker	AUG '06 577	£6.66
Adjustable DC-DC Converter For Cars	578	£6.50
★ Telephone Dialler For Buglar Alarms	579	£6.97
★ High Intensity Torch	580	£5.39
★ Low Cost 50MHz Frequency Meter Version 1 Version 2 Version 3	SEP '06 581 } 582 } 583 } pair	£6.66 £6.66 £6.66
Smart Mixture Display for your Car	584	£6.50
Water Level Gauge – Sensor – Display	585 } 586 } pair	£6.98

PROJECT TITLE	Order Code	Cost
Fridge Door-Open Alarm	OCT '06 587	£5.71
Linear Supply For 1W Star LEDs (Pair)	588a & b	£6.50
Through-Glass Alarm	589	£7.61
Quick Brake	NOV '06 590	£6.50
Studio 350 Power Amplifier	591	£9.51
Micropower Battery Protector	592	£5.71
★ Giant LED Message Display – Master – Slave	594 } 595 } pair	£5.55 £6.50
Lapel Microphone Adaptor	DEC '06 593	£6.18
RGB To Component Video Converter (double sided)	596	£12.69
USB Power Injector	597	£5.87
★ Mind Trainer	598	£6.50
Balanced Microphone Preamp	JAN '07 599	£6.82
High-Efficiency Power Supply for 1W Star LEDs	600	£6.19
Jumping Spider	601	£5.71
★ Programmable Robot	FEB '07 602	£6.50
Courtesy Light Delay	603	£5.87
★ Deep Cycle Battery Charger Power Board Control Board Display Board	604 } 605 } 606 } set	£11.10
★ PIC Digital Geiger Counter (double sided)	607	£12.53
IR Remote Checker	MAR '07 608	£6.35
★ SMS Controller	609	£7.93
★ Lap Counter For Swimming Pools	610	£7.14
★ PIC Polyphonium – Main Board	611	£8.25
PIC Polyphonium – LED Display Interface	APR '07 612	£7.13
Students' Amp – Amplifier – PSU	613 } 614 } pair	£6.02 £6.02
Star Power	615	£6.50

EPE SOFTWARE

★ All software programs for *EPE* Projects marked with an asterisk, and others previously published, can be downloaded *free* from our Downloads site, accessible via our home page at: www.epemag.co.uk.

PCB MASTERS

PCB masters for boards published from the March '06 issue onwards can also be downloaded from our UK website (www.epemag.co.uk); go to the "Downloads" section.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code Project Quantity Price

.....

Name

Address

.....

Tel. No.

I enclose payment of £..... (cheque/PO in £ sterling only) to:



**Everyday
Practical Electronics**



**MasterCard, Amex, Diners
Club, Visa or Switch/Maestro**



Card No

Valid From Expiry Date

Card Security Code Maestro Issue No
(The last 3 digits on or just under the signature strip)

Signature

NOTE: You can also order p.c.b.s by phone, Fax, Email or via the shop on our website on a secure server:

<http://www.epemag.co.uk>

Everyday Practical Electronics reaches more UK readers than any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last twenty-two years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £10 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Phone: 01202 873872. Fax: 01202 874562. Email: epeads@wimborne.co.uk. For rates and information on display and classified advertising please contact our Advertisement Manager, Stewart Kearn as above.

**www.
CONTROLBITZ
.com**

**BTEC ELECTRONICS
TECHNICIAN TRAINING**

NATIONAL ELECTRONICS
VCE ADVANCED ICT
HNC AND HND ELECTRONICS
FOUNDATION DEGREES
NVQ ENGINEERING AND IT
DESIGN AND TECHNOLOGY

LONDON ELECTRONICS COLLEGE
20 PENYWERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: (020) 7373 8721
www.lec.org.uk

BOWOOD ELECTRONICS LTD

Suppliers of Electronic Components
Place a secure order on our website or call our sales line
All major credit cards accepted
Web: www.bowood-electronics.co.uk
Unit 1, McGregor's Way, Turnoaks Business Park,
Chesterfield, S40 2WB. Sales: 01246 200222
Send 60p stamp for catalogue

**VISIT OUR ONLINE
SHOP TO ORDER
SUBSCRIPTIONS (AND
RENEWALS), BACK
ISSUES, CDROMS,
BOOKS, PCBs, AND
MANUALS**

www.epemag.co.uk



**Versatile Programmable PIC
On Screen Display System**

Free demo code
PAL - NTSC compatible
● PIC 16F628 microcontroller
● 28 by 11 character screen
● Fully programmable
● Text over composite video
● Demo software available
● Free I/O for sensors or buttons
www.STV5730A.co.uk

**N.R. BARDWELL Ltd – est 1948
Electronic Component Supplies**

LED's, Semis, IC's Resistors, Caps, etc
send 44p for lists. 1000's bargains at our
secure site: www.bardwells.co.uk
288, Abbeydale Rd. Sheffield. S7 1FL
0845 166 2329 (local rate)

HEROS TECHNOLOGY LTD

<http://www.herostechtechnology.co.uk>
● Electronic Components and Services.
● RF Components.
● PIC microcontrollers practical applications never been
so simple with our Modules Boards and Software.
● Peripheral modules for all microcontrollers
● Solution for Developers, Pre-production, Educational
and Hobby applications

RSH ELECTRONICS

ELECTRONIC COMPONENTS & KITS
P&P £2.50 (orders over £25 Free P&P)
A wide range of popular components.
No Minimum Order. No Sign-up. No VAT.
Visit our easy to use website
www.rshelectronics.co.uk

SAFFRON ELECTRONICS LTD

Suppliers of High Quality Electronic Components
since 1991
Resistors, Caps, Batteries, Chargers, Semiconductors,
LED's, IC's, PCB's, Switches, Solder, Cable, Wire, Etc.
Online Catalogue and Shop available at
www.SaffronElectronics.co.uk
Saffron House, 16 Field Street, Cannock, Staffs. WS11
5QPTelephone: 0845 166 2314 (local rate)

Your own complete
eCommerce 24/7 site
for only £10 per week!
Domain, secure hosting, emails,
shopping basket, etc, included.
details: www.eConcept.co.uk

Miscellaneous

VALVES AND ALLIED COMPONENTS IN STOCK. Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

WANTED OLD HALF INCH FERRITE RODS. Must be half inch (12.7mm) in diameter and be six inches long or more. will pay very good money for the ferrite rods. Contact Peter Tankard on Sheffield 0114 2316321 between 9am and 10pm.

FOR ½ PRICE VALVE CLEARANCE catalogue send £1.00 in 1st or 2nd class stamps **FOR COMBINED VALVE & COMPONENT CLEARANCE list** send £1.50 in 1st or 2nd class stamps. W. Burcher, 676 Foxhall Road, Ipswich, Suffolk, IP3 8NQ. Tel: 01473 272218.

BUILD A 'STAR' TYPE TESTER for EECIV and Teves II/IV ABS. Full details at www.graynada.co.uk and follow the FCR link. or email info@graynada.co.uk



www.epemag.com

**Get your magazine
'instantly' anywhere
in the world – buy
and download from
the web.**

**TAKE A LOOK, A
FREE ISSUE IS
AVAILABLE**

**A one year subscription
(12 issues) costs just
\$15.99 (US)**

**Back issues are also
available**



www.epemag.com

Europe's Largest Surplus Store

20,000,000 Items on line NOW !
New items added daily

Established for over 25 years, UK company Display Electronics prides itself on offering a massive range of electronic and associated electro-mechanical equipment and parts to the Hobbyist, Educational and Industrial user. Many current and obsolete hard to get parts are available from our vast stocks, which include:

- ◆ 6,000,000 Semiconductors
- ◆ 5,000 Power Supplies
- ◆ 25,000 Electric Motors
- ◆ 10,000 Connectors
- ◆ 100,000 Relays & Contactors
- ◆ 2000 Rack Cabinets & Accessories
- ◆ 4000 Items of Test Equipment
- ◆ 5000 Hard Disk Drives

We Ship Worldwide

Surplus Wanted

www.distel.co.uk

Display Electronics
29 / 35 Osborne Road
Thornton Heath
Surrey UK CR7 8PD

Telephone
[44] 020 8653 3333
Fax [44] 020 8653 8888


Rechargeable Batteries With Solder Tags

NIMH		NICAD	
AA 2000mAh	£2.82	AA 650mAh	£1.41
C 4Ah	£4.70	C 2.5Ah	£3.60
D 9Ah	£7.60	D 4Ah	£4.95
PP3 150mAh	£4.95		

Instrument case with edge connector and screw terminals

Size 112mm x 52mm x 105mm tall

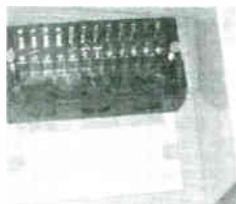This box consists of a cream base with a PCB slot, a cover plate to protect your circuit, a black lid with a 12 way edge connector and 12 screw terminals built in (8mm pitch) and 2 screws to hold the lid on. The cream bases have minor marks from dust and handling price £2.00 + VAT(=£2.35) for a sample or £44.00+VAT (=£51.70) for a box of 44.



866 battery pack originally intended to be used with an orbitel mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily £7.46 + VAT = £8.77



Please add £1.66 + VAT = £1.95 postage & packing per order

JPG Electronics
Shaws Row, Old Road, Chesterfield, S40 2RB.
Tel 01246 211202 Fax 01246 550959
www.JPGElectronics.com
Mastercard/Visa/Switch
Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

EPE EVERYDAY PRACTICAL ELECTRONICS

NEXT MONTH

CONTROL YOUR COSTS WITH THIS ENERGY METER

Have you recovered from the shock of receiving your latest electricity bill? Have you resolved to reduce your electricity usage? This Energy Meter lets you accurately monitor energy usage for individual appliances and even figures out what it costs to run them.

BASS EXTENDER

This Bass Extender circuit can give you as much as an extra octave of bass response from your existing hifi speakers, as long as you are not running them near full power.

SMS CONTROLLER ADD-ONS

The universal nature of the SMS Controller means that it can be used in a huge variety of applications. As a result, external interface circuits will sometimes be required. Here are three handy add-ons: (1) a test jig; (2) a PIR sensor interface; and (3) a low-battery alarm.

MAY '07 ISSUE ON SALE APRIL 12

ADVERTISERS INDEX

AGAR	57
ANTEX	65
AUDON ELECTRONICS	65
BETA-LAYOUT	69
BRUNNING	49
BULL GROUP	Cover (ii)
DISPLAY ELECTRONICS	72
EASYSYNC	Cover (iii)
ESR ELECTRONIC COMPONENTS	6
JAYCAR ELECTRONICS	32/33
JPG ELECTRONICS	72
LABCENTER	Cover (iv)
LASER BUSINESS SYSTEMS	57
MAGENTA ELECTRONICS	5
MICROCHIP	37
MIKROELEKTRONIKA	63
MILFORD INSTRUMENTS	4
NURVE NETWORKS LLC	15
PEAK ELECTRONIC DESIGN	69
PICO TECHNOLOGY	69
QUASAR ELECTRONICS	2/3
RAPID ELECTRONICS	17
SCANTOOL	62
SHERWOOD ELECTRONICS	65
STEWART OF READING	60
TECHNOBOTS	21

ADVERTISEMENT OFFICES:

408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND
PHONE: 01202 873872 FAX: 01202 874562
EMAIL: epeads@wimborne.co.uk

For Editorial address and phone numbers see page 7

Everyday Practical Electronics, ISSN 0262 3617 is published monthly (12 times per year) by Wimborne Publishing Ltd., USA agent USACAN Media Dist. Srv. Corp. at 26 Power Dam Way Suite S1-S3, Plattsburgh, NY 12901. Periodicals postage paid at Plattsburgh, NY and at additional mailing Offices. POSTMASTER: Send address changes to Everyday Practical Electronics, c/o Express Mag., PO Box 2769, Plattsburgh, NY, USA 12901-0239.

featured products

CAN-USB

USB - CAN Bus adapter
 £81.50



CAN-232

RS232 - CAN Bus Adapter
 £61.00

Affordable CAN Bus Solutions from £61 (CAN-232)

CANUSB and CAN-232 are small adapters that plug into any PC USB / RS232 Port respectively to give instant CAN connectivity. These can be treated by software as a standard Windows COM Port. Sending and receiving can be done in standard ASCII format. These are high performance products for much less than competitive solutions.

Bronze Prize Winner
 NASA Tech Briefs 2004
 Products of the Year

£125.00



DS1M12 2 channel 1MS/s PC scope,
 signal generator & data logger

USB Instruments - PC Oscilloscopes & Logic Analyzers

Our PC Instruments may be budget priced but have a wealth of features normally only found in more expensive instrumentation. Our oscilloscopes have sophisticated digital triggering including delayed timebase and come with application software and DLL interface to 3rd Party apps. Our ANT8 and ANT16 Logic Analyzers feature 8/16 capture channels of data at a blazing 500MS/S sample rate in a compact enclosure.

ANT16

16 channel logic analyzer
 - probe set extra
 £195.00



USB-2COM-M £36.00

2 Port Industrial USB RS232 Serial with wall mount bracket and 5V DC auxiliary output



USB-COM-PL
 £12.50

Quality USB to RS232 converter cable with detachable 10cm extender cable. FTDI Chipset and Drivers for superior compatibility and O.S. support.

1 to 16 port USB to Serial Adapters from £12.50

With over 20 different models available, we probably stock the widest range of USB Serial Adapters available anywhere. We offer converter cables, multi-port enclosure style models in metal and plastic, also rack mount units with integral PSU such as the USB-16COM-RM. Serial interfaces supported include RS232, RS422 and RS485. We also supply opto-isolated RS422 and RS485 versions for reliable long distance communications. All our USB Serial products are based on the premium chipsets and drivers from FTDI Chip for superior compatibility, performance and technical support across Windows, MAC-OS, CE and Linux platforms.

NETCOM-813
 £350.00



8 Port Industrial Ethernet RS232 / RS422 / RS485 Serial Server with wall mount bracket and PSU.

ES-W-3001-M
 £125.00



Single Port high performance Industrial Wireless Ethernet RS232 / RS422 / RS485 Serial Server with PSU and wall mount bracket. Connects wired also.

Ethernet & Wi-Fi 802-11b/g RS232/422/485 Serial Servers

One to eight port Industrial strength Ethernet and Wireless ethernet serial RS232/RS422/RS485 Servers. Connect to your serial device remotely over your Wireless network, Ethernet or via the Internet. Based on the 32-bit ARM CPU these systems offer powerful serial connectivity and a wealth of features. WLAN models comply with IEEE 802.11b/g, max. 54 Mb/s and also offer a 10/100Mbps secondary ethernet connection. All models come complete with PSU. Prices start at only £85.00 (NetCOM 111).



uPCI-400HS

4 Port UPCI RS232 Serial Card
 Splder Cable or COMBOX IO
 (extra)
 £65.00

£10.00

UPCI Serial Cards from £15 (uPCI-100L)

Discover our great value for money range of multi-port uPCI serial cards. Supporting from one to eight ports, the range includes RS232, RS422, RS485 and opto-isolated versions. Our 4 port and 8 port models can connect through external cables or the Innovative wall mounting COMBOX.

EasySync Ltd

373 Scotland Street
 Glasgow G5 8QB U.K.

Tel: +44 (141) 418-0181 Fax: +44 (141) 418-0110

Web : <http://www.easysync.co.uk>

E-Mail: sales@easysync.co.uk

* Prices shown exclude carriage and VAT where applicable

PROTEUS

ELECTRONIC DESIGN



FROM CONCEPT

TO COMPLETION

SCHEMATIC CAPTURE PROSPICE EMBEDDED SIMULATION PCB DESIGN

ISIS SCHEMATIC CAPTURE

A powerful capture package tailored for today's engineer and designed to allow rapid entry of complex schematics for simulation and PCB Layout.

PROSPICE MIXED MODE SIMULATOR

A customised implementation of the industry standard Berkeley SPICE 3F5 engine with extensive optimisations and enhancements for true mixed mode simulation and circuit animation.

VSM VIRTUAL SYSTEM MODELLING

The world's first and best schematic based microcontroller co-simulation software. Proteus VSM allows you to simulate the interaction between software running on a microcontroller and any analog or digital electronics connected to it. This streamlines the project lifecycle and obviates the need for expensive hardware analysis tools.

ARES PCB DESIGN

A modern and professional layout package which seamlessly integrates with the ISIS capture software. Features such as autoplacement and autorouting, interactive DRC and an intuitive interface all serve to maximise productivity and reduce time to market.

LABCENTER ELECTRONICS LTD.

A technology pioneer in the EDA industry since 1988.
Technical support direct from the program authors.
Flexible packages and pricing tailored to customer requirements.

CONTACT US NOW
to discuss requirements or
request a **FREE** evaluation copy.

Tel: 01756 753440
Fax: 01756 752857
Email: info@labcenter.co.uk

labcenter  www.labcenter.co.uk
Electronics

Labcenter Electronics Ltd., 53-55 Main Street, Grassington,
North Yorks, BD23 5AA. Registered in England 4692454
World Radio History