

THE No 1 UK MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EPE EVERYDAY PRACTICAL **ELECTRONICS**

www.epemag.co.uk

www.epemag.com

STANDBY POWER SAVER

Save power – remotely turns
off TVs/DVDs/Amplifiers etc.

V8 DOORBELL



INDUCTANCE & Q-FACTOR METER – 1

- ★ Inductance from 200nH to 10mH
- ★ Q-Factor 1-120 (approx)
- ★ Autoranging measurement frequency

PLUS BUILD YOUR OWN SEISMOGRAPH

OCT 2007 £3.50





HB7 Stirling Engine

Base measurements: 128 mm x 108 mm x 170 mm, 1 kg
 Base plate: beech - Working rpm: 2000 rpm/min. (the engine has a aluminium good cooling Cylinder)
 Bearing application: 10 high-class ball-bearings
 Material: screw, side parts all stainless steel
 Cylinder brass, Rest aluminium and stainless steel.
 Available as a kit £80.75 or built £84.99
www.mamodspares.co.uk



STEAM ENGINE KIT

Everything in the kit enables you to build a fully functional model steam engine. The main material is brass and the finished machine demonstrates the principle of oscillation. The boiler, uses solid fuel tablets, and is quite safe. All critical parts (boiler, end caps, safety vent etc.) are ready finished to ensure success. The very detailed instruction booklet (25 pages) makes completion of this project possible in a step by step manner. Among the techniques experienced are silver soldering, folding, drilling, fitting and testing. £29.70 ref STEAMKIT Silver solder/flux pack £3.50 ref SSK

www.mamodspares.co.uk



Solar Panels

We stock a range of solar photovoltaic panels. These are polycrystalline panels made from wafers of silicon laminated between an impact-resistant transparent cover and an EVA rear mounting plate. They are constructed with a lightweight anodised aluminium frame which is predrilled for linking to other frames/roof mounting structure, and contain waterproof electrical terminal box on the rear. 5 watt panel £29 ref 5wnav 20 watt panel £99 ref 20wnav 60 watt panel £249 ref 60wnav. Suitable regulator for up to 60 watt panel £20 ref REGNAV



HB9-Kit

HB9 Stirling engine
 Base measurements: 156 mm x 108 mm x 130 mm, 0,6 Kg
 Base plate: beech Working rpm: approx. 2,000 min
 Bearing application: 6 high-class ball-bearings
 Material of the engine: brass, aluminium, stainless steel
 running time: 30-45 min.
 Available as a kit £97.75 or built £101.99
www.mamodspares.co.uk




HB14 Stirling Engine

Base measurements: 156 mm x 108 mm x 150 mm, 1 kg
 Base plate: beech Working rpm: 2000 - 2500 rpm/min, .
 Incl. drive-pulley for external drives Bearing application:
 10 high-class ball-bearings Material: screw, side parts total
 stainless steel Cylinder brass Rest aluminium, stainless
 steel Available as a kit £140.25 or built £144.50
www.mamodspares.co.uk




Solar evacuated tube panels

(20 tube shown) These top-of-the-range solar panel heat collectors are suitable for heating domestic hot water, swimming pools etc - even in the winter! One unit is adequate for an average household (3-4 people), and it is modular, so you can add more if required. A single panel is sufficient for a 200 litre cylinder, but you can fit 2 or more for high water usage, or for heating swimming pools or underfloor heating. Some types of renewable energy are only available in certain locations, however free solar heating is potentially available to almost every house in the UK! Every house should have one - really! And with an overall efficiency of almost 80%, they are much more efficient than electric photovoltaic solar panels (efficiency of 7-15%). Available in 10, 20 and 30 tube versions. 10 tube £199, 20 tube £369, 30 tube £549. Roof mounting kits (10/20 tubes) £12.50, 30 tube mounting kit £15

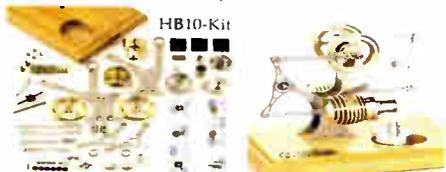

HB10-Kit

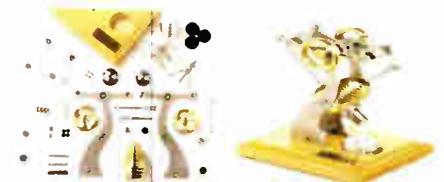HB10 Stirling Engine
 Base measurements: 156 mm x 108 mm x 130 mm, 0,6 Kg
 Base plate: beech Working rpm: approx. 2,000 rpm
 Bearing application: 6 high-class ball-bearings
 Material of the engine: brass, aluminium, stainless steel
 running time: 30-45 min
 Available as a kit £97.75 or built £101.99
www.mamodspares.co.uk



HB15 Stirling Engine

Base measurements: 128 mm x 108 mm x 170 mm, 0,75 Kg
 Base plate: beech Working rpm: 2000 rpm/min. (the engine has a aluminium good cooling Cylinder)
 Bearing application: 6 high-class ball-bearings
 Material: screw, side parts total stainless steel
 Cylinder brass Rest aluminium, stainless steel
 Available as a kit £97.75 or built £102
www.mamodspares.co.uk



HB11 Stirling Engine

Base measurements: 156 mm x 108 mm x 130 mm, 0,7 Kg
 Base plate: beech
 Working rpm: 2000 - 2500 rpm/min, run Bearing application:
 4 high-class ball-bearings Material: screw, side parts
 total stainless steel Cylinder brass Rest aluminium, stain-
 less steel.
 Available as a kit £97.75 or built £101.99
www.mamodspares.co.uk



HB16 Stirling Engine

Base measurements: 128 mm x 108 mm x 170 mm, 1 kg
 Base plate: beech Working rpm: 2000 rpm/min. (the engine has a aluminium good cooling Cylinder)
 Bearing application: 10 high-class ball-bearings
 Material: screw, side parts total stainless steel
 Cylinder brass Rest aluminium, stainless steel.
 Available as a kit £140.25 or built £144.50



HB12 Stirling Engine

Base measurements: 156 mm x 108 mm x 130 mm, 1 Kg
 Base plate: beech Working rpm: 2000 - 2500 rpm/min,
 Bearing application: 6 high-class ball-bearings
 Material: screw, side parts total stainless steel
 Cylinder brass Rest aluminium, stainless steel.
 Available as a kit £136 or built £140.25
www.mamodspares.co.uk



2kw WIND TURBINE KIT

The 2kW wind turbine is supplied as the following kit: turbine generator 48v three taper/ twisted fibreglass blades & hub 8m tower (four x 2m sections) guylines / anchors / tensioners / clamps foundation steel rectifier 2kW inverter heavy-duty pivot tower. £1,499




HB13 Stirling Engine

Base measurements: 156 mm x 108 mm x 150 mm, 0,75 kg
 Base plate: beech Working rpm: 2000 - 2500 rpm/min,
 Bearing application: 6 high-class ball-bearings Material:
 screw, side parts total stainless steel Cylinder brass
 Available as a kit £97.75 or built £101.99

BULL GROUP LTD
 UNIT D HENFIELD BUSINESS PARK
 HENFIELD SUSSEX BN5 9SL
 TERMS: C/ CARDS, CASH, PO, CHEQUE OR
 ONLINE ORDERING. PRICES PLUS VAT
 UK DELIVERY £5.50
 TEL 0870 7707520 FAX 01273 491813
 sales@bullnet.co.uk

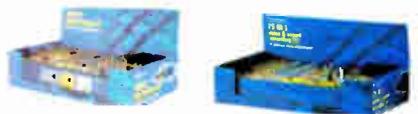BENCH PSU 0-15V 0-2a Output and voltage are both smooth and can be regulated according to work. Input 230V, 21/2-number LCD display for voltage and current, Robust PC-grey housing Size 13x15x21cm, Weight 3,2kg £48 REF trans2



NEW ELECTRONIC CONSTRUCTION KITS

This 30 in 1 electronic kit includes an introduction to electrical and electronic technology. It provides components that can be used to make a variety of experiments including Timers and Burglar Alarms. Requires: 3 x AA batteries. £15.00 ref BET1803

AM/FM Radio This kit enables you to learn about electronics and also put this knowledge into practice so you can see and hear the effects. Includes manual with explanations about the components and the electronic principles. Req's: 3 x AA batts. £13 ref BET1801

This 40 in 1 electronic kit includes an introduction to electrical and electronic technology. It provides components that can be used in making basic digital logic circuits, then progresses to using Integrated circuits to make and test a variety of digital circuits, including Flip Flops and Counters. Req's: 4 x AA batteries. £17 ref BET1804

The 75 in 1 electronic kit includes an introduction to electrical and electronic technology. It provides components that can be used to make and test a wide variety of experiments including Water Sensors, Logic Circuits and Oscillators. The kit then progresses to the use of an integrated circuit to produce digital voice and sound recording experiments such as Morning Call and Burglar Alarm. Requires: 3 x AA batteries. £20 ref BET1806
www.slips.co.uk

ISSN 0262 3617



PROJECTS... THEORY...
NEWS... COMMENT...
PCULAR FEATURES...

VOL. 36, No. 10 OCTOBER 2007

EPE EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

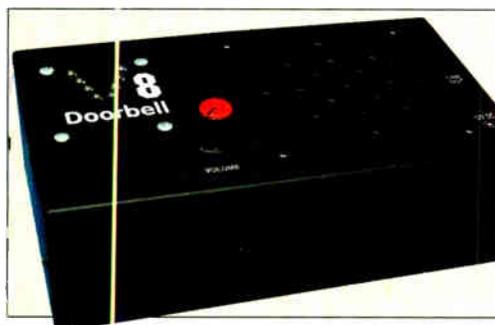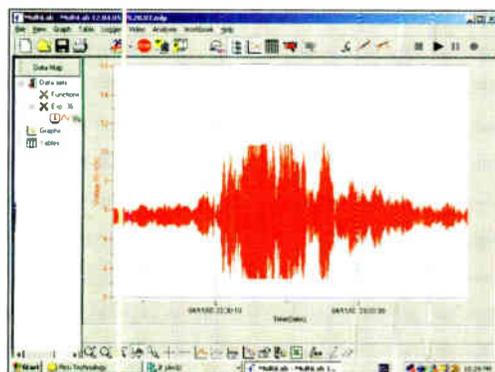www.epemag.co.uk
EPE Online: www.epemag.com



© Wimborne Publishing Ltd 2007. Copyright in all drawings, photographs and articles published in *EVERYDAY PRACTICAL ELECTRONICS* is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our November 2007 issue will be published on Thursday, 11 October 2007, see page 80 for details.

Projects and Circuits

- V8 DOORBELL** by John Clarke 12
Sounds like a real V8 engine
- INGENUITY UNLIMITED – sharing your ideas with others** 27
Monitoring PSU output current and voltage
- INDUCTANCE & Q-FACTOR METER** by Leonid Lerner 28
A wide range multi-frequency inductance and Q-factor meter
- STANDBY POWER SAVER** by John Becker 52
Remotely turns off appliances in standby mode
- BUILD YOUR OWN SEISMOGRAPH** by Dave Dobeson 62
Display 'tremors' on a PC

Series and Features

- TECHNO TALK** by Mark Nelson 10
Keeping The Lights On
- PIC N' MIX** by Mike Hibbett 24
More on 1-wire protocol
- THE POWER OF MECHATRONICS – PART 5** by Ian Pearson 36
A New Dimension
- BANNING THE BULB** by Dave Geary 40
An analysis of low energy bulbs
- CIRCUIT SURGERY** by Ian Bell 46
Regulator stability and switch bounce
- INTERFACE** by Robert Penfold 60
Setting Parallel Port Outputs to Inputs
- NET WORK** by Alan Winstanley 76
First steps in broadband

Regulars and Services

- EDITORIAL** 7
- NEWS** – Barry Fox highlights technology's leading edge 8
Plus everyday news from the world of electronics
- PLEASE TAKE NOTE** 26
V2 PC Scope
- SUBSCRIBE TO EPE** and save money 48
- CD-ROMS FOR ELECTRONICS** 49
A wide range of CD-ROMs for hobbyists, students and engineers
- READOUT** John Becker addresses general points arising 73
- EPE PCB SERVICE** 78
PCBs for EPE projects
- ADVERTISERS INDEX** 80

Readers' Services • Editorial and Advertisement Departments 7


PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £14.95
18Vdc Power supply (PSU010) £18.95
Leads: Parallel (LDC136) £3.95 / Serial (LDC441) £3.95 / USB (LDC644) £2.95

NEW! USB & Serial Port PIC Programmer

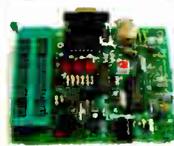

USB/Serial connection. Header cable for ICSP. Free Windows XP software. See website for PICs supported. ZIF Socket and USB lead extra. 18Vdc.

Kit Order Code: 3149KT - £39.95

Assembled Order Code: AS3149 - £49.95

NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows XP Software. ZIF Socket and USB lead not incl.



Assembled Order Code: AS3128 - £44.95

Assembled with ZIF socket Order Code: AS3128ZIF - £59.95

'PICALL' ISP PIC Programmer



Will program virtually all 8 to 40 pin serial-mode AND parallel-mode (PIC15C family) PIC microcontrollers. Free Windows software.

Blank chip auto detect for super fast bulk programming. Optional ZIF socket.

Assembled Order Code: AS3117 - £24.95

Assembled with ZIF socket Order Code: AS3117ZIF - £39.95

ATMEL 89xxxx Programmer



Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16Vdc.

Kit Order Code: 3123KT - £24.95

Assembled Order Code: AS3123 - £34.95

Introduction to PIC Programming

Go from complete beginner to burning a PIC and writing code in no time! Includes 49 page step-by-step PDF Tutorial Manual, Programming Hardware (with LED test section), Win 3.11—XP Programming Software (Program, Read, Verify & Erase), and 1rewritable PIC16F84A that you can use with different code (4 detailed examples provided for you to learn from). PC parallel port.



Kit Order Code: 3081KT - £16.95

Assembled Order Code: AS3081 - £24.95

ABC Maxi AVR Development Board

The ABC Maxi is ideal for developing new designs. Open architecture built around an ATMEL AVR AT90S8535 microcontroller. All circuits are embedded within the package and additional add-on expansion modules are available to assist you with project development.



Features

8 Kb of In-System Programmable Flash (1000 write/erase cycles) • 512 bytes internal SRAM • 512 bytes EEPROM • 8 analogue inputs (range 0-5V) • 4 Opto-isolated inputs (I/Os are bi-directional with internal pull-up resistors) • Output buffers can sink 20mA current (direct LED drive) • 4 x 12A open drain MOSFET outputs • RS485 network connector • 2-16 LCD Connector • 3.5mm Speaker Phone Jack • Supply: 9-12Vdc

The ABC Maxi STARTER PACK includes one assembled Maxi Board, parallel and serial cables, and Windows software CD-ROM featuring an Assembler, BASIC compiler and in-system programmer.

Order Code ABCMAXISP - £89.95

The ABC Maxi boards only can also be purchased separately at £69.95 each.

Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. 12Vdc PSU for all units: Order Code PSU445 £8.95

Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output.

Range up to 40m. Up to 15 Tx's can be learnt by one Rx

(kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two & Ten Channel versions also available.

Kit Order Code: 3180KT - £44.95

Assembled Order Code: AS3180 - £54.95



Computer Temperature Data Logger

Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 45x45mm. Powered by PC. Includes one DS1820 sensor.

Kit Order Code: 3145KT - £17.95

Assembled Order Code: AS3145 - £24.95

Additional DS1820 Sensors - £3.95 each



4-Ch DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12Vdc.



Kit Order Code: 3140KT - £54.95

Assembled Order Code: AS3140 - £69.95

8-Ch Serial Port Isolated I/O Relay Module

Computer controlled 8 channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch states, etc). Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Includes plastic case 130x100x30mm. Power: 12Vdc/500mA.



Kit Order Code: 3108KT - £54.95


Assembled Order Code: AS3108 - £64.95

Infrared RC 12-Channel Relay Board

Control 12 onboard relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm. Supply: 12Vdc/0.5A

Kit Order Code: 3142KT - £47.95

Assembled Order Code: AS3142 - £59.95

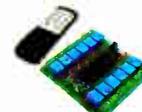

Audio DTMF Decoder and Display

Detect DTMF tones from tape recorders, receivers, two-way radios, etc using the built-in mic or direct from the phone line. Characters are displayed on a 16 character display as they are received and up to 32 numbers can be displayed by scrolling the display. All data written to the LCD is also sent to a serial output for connection to a computer. Supply: 9-12V DC (Order Code PSU445). Main PCB: 55x95mm.

Kit Order Code: 3153KT - £24.95

Assembled Order Code: AS3153 - £34.95



Telephone Call Logger

Stores over 2,500 x 11 digit DTMF numbers with time and date. Records all buttons pressed during a call. No need for any connection to computer during operation but logged data can be downloaded into a PC via a serial port and saved to disk. Includes a plastic case 130x100x30mm. Supply: 9-12V DC (Order Code PSU445).

Kit Order Code: 3164KT - £54.95

Assembled Order Code: AS3164 - £69.95



Most items are available in kit form (KT suffix) or pre-assembled and ready for use (AS prefix).

Hot New Products!

Here are a few of the most recent products added to our range. See website or join our email Newsletter for all the latest news.

Embedded Engineer's Development Tool (Atmel 89S & AVR)

At last the development tool kit for Atmel 89S & AVR devices that engineers have dreamed of has arrived. The kit includes a Built-in ISP Programmer, Target Section, Interfacing Board, Cables, eBook with codes, e-Learning Software with explanation and CD all in one neat package. Devices covered include 89S51, 89S52, 89S8253, mega8515, mega8535, mega8, mega16 & mega32.

Features

Designed for working professionals, students and product development companies. You can connect any device like LCD, 7-Segment, Sensors, Switches to any desired port of the microcontroller. No dedicated connections between microcontroller and the interfacing sections. You can connect anything, anywhere. e-Learning Tutorial and Book are included. Once you start using the kit, you should never feel the need to attend any trainings because it is simple to use and all concepts are explained in simple language using the tutorial and book. Includes 89S51, 89S52, ATmega8, ATmega16, ATmega32 In-circuit Programmer - no need to buy a separate programmer! No ZIF Sockets. No hassle inserting and removing microcontroller to program. In-circuit programming reduces development time as you do not need to move microcontroller.

Contents

- In circuit programmer for 89S and AVR series (supports up to Atmega128)
- 89S51/52 target section
- ATmega8 Target section
- ATmega16/32 Target section
- Switches
- Relays
- LEDs
- 7 Segment Displays
- 16 X 2 LCD
- ADC
- Motor Driver
- RS232
- EEPROM
- Cables
- Connectors
- Serial Port Lead
- e-Learning Software
- e-Datasheets
- HandyProg Programming software
- IDEs for code writing
- Application source code

Assembled Order Code: EEDT - **£89.95**

Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

Motor Speed Controllers

Here are just a few of our controller and driver modules for AC, DC, Unipolar/Bipolar stepper motors and servo motors. See website for full details.

DC Motor Speed Controller (100V/7.5A)



Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - **£13.95** Assembled Order Code: AS3067 - **£21.95**

PC / Standalone Unipolar Stepper Motor Driver

Drives any 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps max. Provides speed and direction control. Operates in stand-alone or PC-controlled mode. Up to six 3179 driver boards can be connected to a single parallel port. Supply: 9Vdc. PCB: 80x50mm. Kit Order Code: 3179KT - **£12.95** Assembled Order Code: AS3179 - **£19.95**



Bi-Polar Stepper Motor Driver

Drive any bi-polar stepper motor using externally supplied 5V levels for stepping and direction control. These usually come from software running on a computer. Supply: 8-30Vdc. PCB: 75x85mm. Kit Order Code: 3158KT - **£17.95** Assembled Order Code: AS3158 - **£27.95**



Bidirectional DC Motor Controller

Controls the speed of most common DC motors (rated up to 32Vdc/10A) in both the forward and reverse direction. The range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections. Kit Order Code: 3166v2KT - **£17.95** Assembled Order Code: AS3166v2 - **£27.95**



AC Motor Speed Controller (700W)

Reliable and simple to install project that allows you to adjust the speed of an electric drill or single phase 230V AC motor rated up to 700 Watts. Simply turn the potentiometer to adjust the motors RPM. PCB: 48x65mm. Not suitable for use with brushless AC motors. Kit Order Code: 1074KT - **£12.95** Assembled Order Code: AS1074 - **£18.95** Box Order Code 2074BX - **£5.95**



QUASAR
electronics
Get Plugged In!

Credit Card Sales
0871 717 7168

Electronic Project Labs

Great introduction to the world of electronics. Ideal gift for budding electronics expert!

500-in-1 Electronic Project Lab

Top of the range. Complete self-contained electronics course. Takes you from beginner to 'A' Level standard and beyond! Contains all the hardware and manuals to assemble 500 projects. You get 3 comprehensive course books (total 368 pages) - *Hardware Entry Course*, *Hardware Advanced Course* and a microprocessor based *Software Programming Course*. Each book has individual circuit explanations, schematic and connection diagrams. Suitable for age 12+. Order Code EPL500 - **£149.95**



Also available - 30-in-1 **£16.95**, 130-in-1 **£39.95** & 300-in-1 **£59.95** (details on website)

Tools & Test Equipment

We stock an extensive range of soldering tools, test equipment, power supplies, inverters & much more - please visit website to see our full range of products.

Professional Digital Multimeter (9 Function inc Temperature)

High quality DMM offering 31 ranges and 9 functions (see table below for full details) and adjustable LCD screen for easy viewing. Supplied with shrouded test leads, K type temperature probe, shock-proof rubber holster, built-in probe holder & stand.



Large 36mm digit adjustable LCD display • Auto power OFF • Data hold • Automatic polarity indication • Low battery indication • Audible continuity test • Transistor hFE and diode test

Technical Specifications

DC voltage: 200mV-1000V • AC voltage: 2V-750V • DC current: 20mA-10A • AC current: 20mA-10A • Resistance: 200Ω-200MΩ • Capacitance: 2nF-20μF • Temperature: 0 - 1000°C • Max display: 1999

Order Code: DMM225 - Was **£31.95**

Now on sale at just **£21.95!**


See website for more super deals!



www.QuasarElectronics.com

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads


Compact Control Design

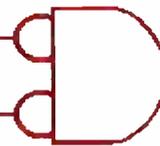

Compact Control Design has a range of off the shelf products designed to meet your control, monitoring and acquisition needs. All products use the latest technology to provide top performance in a small size and at a low cost. We also provide a full hardware and software design service.

P0701 USB PIC

USB 2.0 interface. Can be bus powered or self powered.
Powerful PIC18F4580 Microcontroller running at 40MHz. Up to 10MIPS performance.
All microcontroller I/O pins available except RA6, RA7 (oscillator) and RC6, RC7 (serial port).
Bootloader pre-programmed and download software included, enabling quick and easy programming of applications.
No need for a separate programming device.
Many example applications and firmware available, see Compact Control Design download page.
Connector has standard 40 pin 0.1" pitch 0.6" wide footprint.
High quality tuned pin connectors suitable for most IC sockets and prototyping boards.

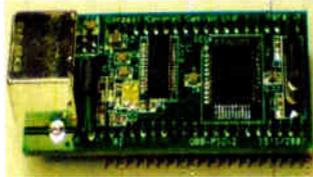


Compatible with Microchip's MPLab 'free of charge' programming environment. Libraries and linker scripts included to support assembler programs (MPLab) and popular compilers.

PRICE:£26.00
+ VAT

P0704 Developer Board

The P0704 developer board is an ideal way to get started with our USB-PIC module and motor driver modules. All of the USB-PIC module I/O signals are available through screw terminals making connections to sensors, switches, lamps, relays etc. easy. Ports B & E (11 I/O signals) can also be configured with pull-ups and input filtering suitable for connection to limit switches, home position sensors etc. The board supports up to 4 motor driver modules, each module position accepts either a Stepper motor module or a DC motor module. The board allows bus-powered or self powered operation of the USB-PIC module & includes a P0615 mini regulator so only a single power supply is required for the motor driver modules.

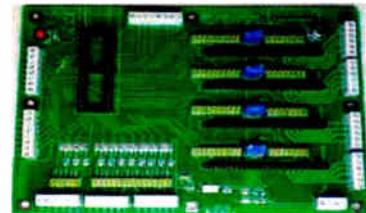


All options are configured using jumpers, and stepper motor drive current can be easily adjusted for each module by variable resistors. All connections are made by high quality screw terminals. The board has been designed to accommodate other driver modules as they become available.

PRICE:£55.00
+ VAT

P0613 DC Motor


Pulse width modulation control for DC motors, electro-magnets etc.
It has a motor supply voltage of 8 to 36V. The maximum drive current is 2.5 Amp. There are pulse and direction inputs. The PWM control is up to 100KHz. Mode input for controlling motor braking and sleep input for power saving. There is built in short circuit and over temperature protection, a fault output pin activates if either of these is detected. No heat sink is required. The board has dimensions of 66x30mm and is 12mm high. There is an adapter available providing easy to use screw terminals for all connections. All the control inputs are opto-isolated.

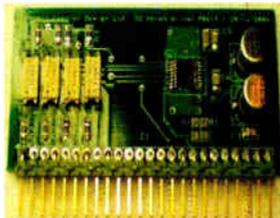

PRICE:£14.00
+ VAT

P0612 Stepper Motor Driver

The unit has a motor supply voltage of 5 to 30V. The maximum drive current per phase is 750mA. It has current mode control. The drive current is controlled with a resistor. It has a selectable step size of full, half, 1/4 + 1/8. There is a step frequency of 0 to 200KHz and reset and sleep inputs for initialization and power saving. It is a compact size with dimensions of 66x32mm by 12mm high. The P0612 does not require a heat sink. There is an adapter available which provides easy to use screw terminals for all connections. All the control inputs are opto-isolated.

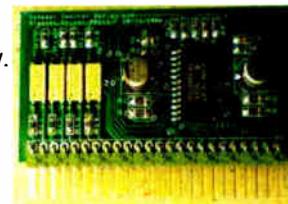

PRICE:£15.00
+ VAT

MonCon


MonCon is a product range intended to form the intelligence at the heart of any equipment from bench-top scientific instruments, production equipment, ATE etc. up to large process control systems. The MonCon range takes a new approach to monitoring and control by using modules that encapsulate a complete task, such as the stepper motor controller module that includes all inputs and outputs necessary to form a complete stepper motor controller/driver including encoder feedback. The general purpose modules, such as the Analogue input board are designed to be customized at minimum cost. We can supply such modules to your requirements at little or no additional cost. The MonCon range is based on a collection of modules, each performing specific and well defined tasks. All modules plug into a back plane which provides power distribution, intercommunication and incorporates the necessary connectors linking the MonCon system to the rest of the equipment. The modules and backplane connectors have been designed to simplify the interconnection requirements within your equipment.

Most devices, such as stepper motors, sensors etc. are wired to the MonCon backplane directly with no splices or links so the wiring loom is simplified, cheaper to manufacture and more reliable.


We understand that many manufacturers would want to have full control over critical parts of their products, so we are happy to allow our customers to manufacture under license. The product range currently consists of the following - standard back planes with 4, 6 or 8 slots, controller modules for stepper and DC motors, controller modules for valves and solenoids, pressure control, flow control etc.

a USB interface to allow connection to a PC etc. various I/O modules, Parallel I/O, relay output and Analogue I/O modules.

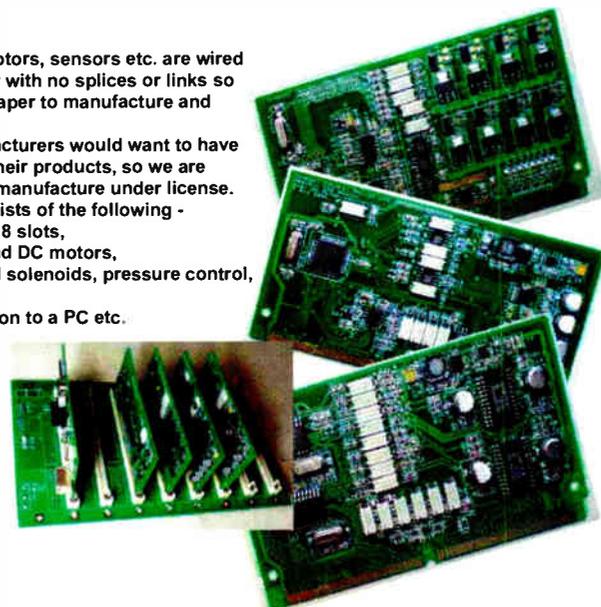The MonCon range has been designed with flexibility in mind. Backplanes and modules to meet your requirements can generally be designed & supplied within 6 weeks of receiving a full specification.



Embedded Ethernet Solutions

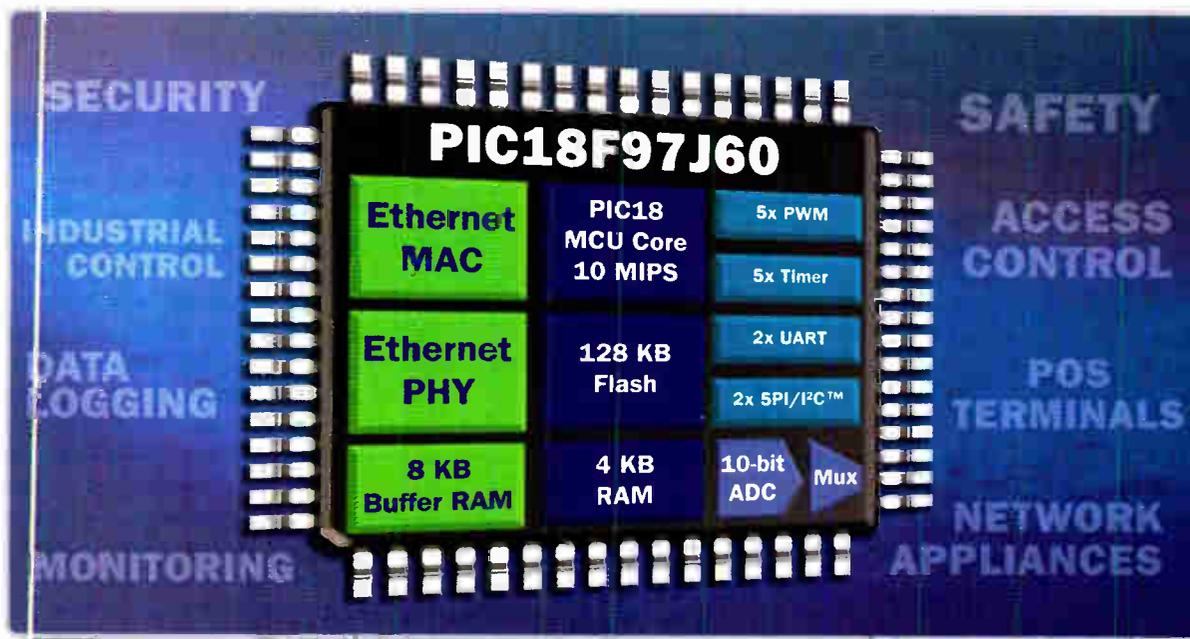


Monitor, control or re-program your application remotely using the integrated Ethernet PIC18F97J60 Microcontroller family and **FREE** TCP/IP software.

3 EASY STEPS TO GET STARTED...

1. Learn about our Ethernet devices in 20 minutes
Take advantage of our Ethernet web seminars.
2. Download our **FREE** TCP/IP software
Our TCP/IP stack is available in source code for flexible and optimized code size.
3. Check out our low-cost Ethernet tools
Evaluate the PIC18F97J60 family with the **PICDEM.net™ 2 Demonstration Board** (DM163024) at www.microchipDIRECT.com.

Device	Price	Flash (KB)	Features
PIC18F97J60	100	128	10-BaseT Ethernet
PIC18F87J60	80	128	12 KB RAM
PIC18F67J60	64	128	(8 KB dedicated Ethernet)
PIC18F96J65	100	96	5x 16-bit timers
PIC18F86J65	80	96	10-bit ADC, 16 channels
PIC18F66J65	64	96	analog comparators
PIC18F96J60	100	64	2 UART with LIN protocol
PIC18F86J60	80	64	2 SPI, 2 I2C™
PIC18F66J60	64	64	Industrial Temperature -40° to +85°C
ENC28J60	28	8K RAM	MAC, PHY, SPI Interface

Or you may consider...

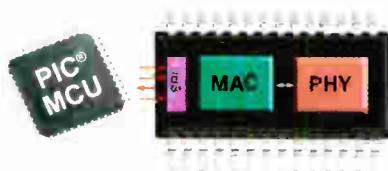

...adding Ethernet to any application with Microchip's ENC28J60 stand-alone Ethernet controller with full software support for PIC18, PIC24 and dsPIC® DSCs.

Visit www.microchip.com/ethernet today!

microchip
DIRECT
www.microchipdirect.com

Now
Pb-free!
RoHS Compliant

MICROCHIP
www.microchip.com/ethernet

PCB Production - Development
0.1" Copper Stripboard

Size	Tracks/Holes	
23 x 64mm	9T / 25H	£0.24
62 x 95mm	24T / 37H	£0.87
95 x 127mm	36T / 50H	£1.41
95 x 432mm	36T / 170H	£4.39
100 x 100mm	39T / 38H	£1.40
100 x 500mm	39T / 199H	£6.20
119 x 455mm	46T / 179H	£5.40

Stripboard track cutter £1.99

Solderless Breadboard
Tie Points & Size Power Rails

390	81 x 60mm	2	£2.75
840	175 x 67mm	2	£4.86
740	175 x 55mm	1	£4.03
640	175 x 42mm	0	£3.08

Many other sizes available, also jump wires & matrix board.

PCB Production - Drafting Materials
A4 Artwork Film (per 10 sheets)

Clear Manual Film	£1.20
Clear Loser Film	£1.75
White HQ Loser Film	£4.62

Etch Resist Pens
"Dolo" Pen £3.36
"Squadster" Fine Pen £0.96

Etch Resist Transfers
Seno mixed DIL pods £2.24
Seno mixed Rnd pods £2.24
Alfoc mixed pods £1.84
Transfer Spatular £1.25

We carry the full range of Seno & Alfoc PCB transfers, see our catalogue for full details.

Soldering Irons
We carry in stock a wide range of soldering iron and soldering accessories. Irons from 12 to 100 Watts.

20W 240V Basic	£3.74
25W 240V Ceramic	£7.14
30W 240V Basic	£4.68

Desolder Pumps
Basic 165 x 18mm £2.85
Anistotic 195mm £3.92
Antex Mini 198mm £6.02
Antex Pro 210mm £10.26

Soldering Station
A 48W adjustable temperature soldering station with a rotary dial, LED Temperature metering, on-off switch, iron holder and tip cleaning sponge. This station features accurate heat sensing for instant compensation & stable temperatures. Adjustable temperature range of 150 - 420°C, Low voltage iron with Silicone cable. Supply 240V, Iron: 24V 48W

Model 167-540 £41.66

Soldering Station
A 48W adjustable temperature soldering station with a rotary dial, Digital Temperature indication, on-off switch, iron holder and tip cleaning sponge. This station features accurate heat sensing for instant compensation & stable temperatures. Adjustable temperature range of 150 - 480°C, Low voltage iron with Silicone cable. Supply: 240V, Iron: 24V 48W

Model 167-570 £55.61

Digital Multimeter
Model: 121-120
Price: £11.47

A highly featured digital multimeter for professional use. Offers 30 ranges and 8 functions including temperature, capacitance, diode, continuity and hFE measurement. Large 3.5 digit LCD display with automatic polarity indicator. Supplied with shrouded test leads, K type temperature probe and stock proof rubber holster.

Technical Specifications
DC voltage 200mV - 1000V (±0.5%)
AC volts 2V - 700V (±0.8%)
DC current 2mA - 20A (±1.2%)
AC current 200mA - 20A (±1.8%)
Resistance 200 Ohms - 20M Ohms (±0.8%)
Capacitance 2000pF - 20µF (±2.5%)
Temperature 0°C - 1000°C (±1.5%)
Frequency 20kHz (±1%)
Max display 1999
Power supply 9V (PP3 battery)
Dimensions 88 x 173 x 40 mm

PCB Production - Processing Equipment
We carry a large range of the photographic & chemical processing equipment for PCB production, a full list with full technical specifications is available in our catalogue or visit our web site.

UV Exposure units
2 x 8W Tubes, 6 min timer
229 x 159mm working oreo Model 332-002 £98.75
4 x 15W Tubes, 7½ min timer
330 x 260mm working oreo Model 332-004 £209.48

Chemical Processing
Low cost plastic tray £2.30
Process tanks feature electrically operated pumps and/or heaters with thermostat control, suitable for boards upto 320 x 260mm. Universal Tank with heater Model 333-007 £169.58
Bubble etch Tank with heater & bubble pump. Model 333-004 £208.48

Any of these items, carriage £5.50

PCB Production - Tools
Drill Bits
HSS parallel shank bits available in sizes from 0.3mm to 2.0mm.

0.3-0.95mm in 0.05mm steps	£0.60ea	£4.00/10
1.0-2.0mm in 0.1mm steps	£0.40ea	£3.60/10

HSS Reduced shank (2.35mm) bit available in sizes from 0.6mm to 1.7mm in 0.1mm steps £0.84ea £7.60/10

Reground Tungsten carbide reduced shank available in sizes from 0.6 to 1.6mm in 0.1mm steps £1.90

Drilling Machines
Expo Reliant 12V drill, 3.8mm capacity, 8400rpm £12.78
Expo Zircon 12V drill, 3.8mm capacity, 11900rpm £14.20

Minicroft MX1 230V, 8000 - 21000rpm with chuck & collet. Model EPE270-390 Normol price £48.51

SPECIAL PRICE £31.02

Servisol Products
Aerosols

200ml Switch Cleaner	£2.30
200ml Freezer	£4.39
400ml Foam Cleanser	£2.13
400ml Cleaner / lubricant	£2.79
75ml Vide Head Cleaner	£1.94
200ml Aero Klene	£3.33
200ml Aer Duster	£5.13
250ml Cold Clean	£3.14
200ml Label remover	£3.52
400ml Isopropyl alcohol	£3.42

Tubes

10g Heatsink Compound	£1.66
25g Heatsink Compound	£2.60
50g Silicone grease	£3.16

Bench Power Supplies
A range of single output regulated bench power supplies with variable voltage & current limiting. Features: Short circuit and "Foldback" overload protection, Metal case with on/off switch, outputs via Red, Black & Green (Earth) 4mm shrouded sockets

Model: 461-550	0-30V0-3A	£70.88
Model: 461-552	0-50V 0-3A	£81.00
Model: 461-554	0-30V 0-10A	£135.00

Panel Meters
High quality analogue panel meters, class 2, zero point correction, mirror scale and wired for panel illumination. Meter size 46 x 60mm, Cutout size: 39mmØ.

Range	Int Ω	
0-500µA	6k5	
0-1000µA	1k0	
0-5000µA	430Ω	
0-1mA	200Ω	
0-10mA	20Ω	
0-50mA	1Ω	
0-100mA	0.2Ω	
0-1A	60mΩ	
0-3A	20mΩ	
0-5A	12mΩ	
0-15A	4mΩ	
C-10V	10k	
0-15V	15k	
0-30V	30k	
±500µA	1k9	

All meters £5.89 each
6V Lamps £1.23 / pair

Magnifying Desk Lamp
A high quality scratch resistant magnifying glass fitted to a ball-jointed swivel arm and desk mount. An integral fluorescent tube provides illumination. Magnification 3x Lens: 120mmØ - Use: 22W Daylight simulation.

Model: 028-205 £28.80

New The Electronic Shop.co.uk
Sound & Lighting equipment for the Entertainment Industry

PCB Production - Laminates
Copper clad low cost paper composite board

100 x 160mm Board	£0.54
100 x 220mm Board	£0.62
160 x 233mm Board	£1.02
220 x 233mm Board	£1.40
8" x 12" Board	£1.96

Copper clad - glass fibre
Single & Double 1.6mm 305g/m²

100 x 160mm Single	£1.06
100 x 220mm Single	£1.49
160 x 233mm Single	£2.29
220 x 233mm Single	£2.88
8" x 12" Single	£3.98
100 x 160mm Double	£1.09
100 x 220mm Double	£1.25
160 x 233mm Double	£2.30
220 x 233mm Double	£2.90
8" x 12" Double	£4.05

Photoresist Coated
1.6mm 35 micron Pre-coated with a high quality photoresist layer. Available in low cost paper composite or Glass fibre, Single & Double sided. Other sizes also available.

Size	Paper Single	Double	Glass Fibre Single	Double
4 x 6"	£1.47	£1.82	£1.89	£2.17
6 x 12"	£4.20	£5.04	£5.60	£6.23
9 x 12"	£6.30	£7.70	£8.40	£9.38
10 x 12"	£8.19	£10.01	£10.78	£11.83
12 x 12"	£8.26	£10.08	£10.99	£12.25

100 x 160mm	£2.38	£2.66
203 x 114mm	£3.01	£3.43
220 x 100mm	£3.08	£3.71
233 x 160mm	£4.83	£5.32
233 x 220mm	£6.83	£7.70

PCB Production - Chemicals

100ml Aerosol Photoresist spray, covers 2m²	£4.62
50g Powder developer, makes 10l	£1.09
500g Powder developer, makes 10l	£7.08
250g Ferric Chloride Pellets, makes 500ml	£1.68
500g Ferric Chloride Pellets, makes 1l	£3.04
2.5kg Ferric Chloride Pellets, makes 5l	£9.84
1.1kg Clear Fine etch crystals, makes 5l	£17.58
90g Tin Plating Powder, makes 1l	£11.58
200ml Aerosol Flux spray	£3.41
110ml Aerosol PCB Laquer spray	£3.54

Tools - Cutters & Strippers
We carry a wide range of specialist tools for the electronics industry including:

Side Cutters

130mm Low cost	£1.99
115mm Dropper	£2.38
115mm Box Jointed	£4.26
145mm Long reach	£3.40

Wire Strippers

130mm Low cost	£2.30
150mm Dropper 5mmØ	£5.86

Tools - Ratchet Crimping Pliers
High quality ratchet crimping pliers for various terminals including Automotive, Data, Power and Data connections.

Red / Blue / Yellow	£15.80
3NC / 4NC RF series	£15.08
R111/12 Data Series	£22.32
R145 Data Series	£20.43
R111/12 & 45 Series	£11.83

CKE Tools Crimp Pliers

Green/Red/Blue	£24.38
Red/Blue/Yellow	£22.88
0.24-2.5mm² crimps	£26.01
0.5-6.0mm² crimps	£26.01
Non insulated crimps	£24.38

Cable - Ribbon
7/0.127mm Grey ribbon cable on a 0.05" 1.27mm pitch with a red identifying stripe. Supplied by 305mm (1ft) or on full 30.5m (100ft) reels.

Size	per 305mm	per Reel
10 Woy	£0.10	£5.80
14 Woy	£0.14	£7.50
16 Woy	£0.16	£8.58
20 Woy	£0.20	£10.72
24 Woy	£0.24	£13.94
34 Woy	£0.34	£18.22
40 Woy	£0.40	£21.44
50 Woy	£0.50	£26.80
60 Woy	£0.64	£33.92

IDC Crimp tool £10.60

CAT5e Networking
UTP Cable
Conforms to CAT5E
100MHz standard,
EIA verified TIA/EIA 568-B.2

305m Box	£45.31
100m Reel	£22.28

exc carriage.

R145 Outlet Kit
Backing Box
2 Gong Plate
R145 Module
Blank Module
Coloured id inserts.
£2.99eo £2.42 (10+)

Tools
Plastic punch down tool
& cable stripper £1.40
Professional punch down
IDC & trim tool £7.38

Outlets
CAT5e Outlet Module £1.70
1 Gong Plate (2 Mods) £0.50
2 Gong Plate (4 Mods) £0.75
½ Module Blank £0.25
1 Module Blank £0.35
2 Module Blank £0.45

Other keystone outlets, switches & accessories available. Patch & Cross-over leads from £0.50

Now available online
Outlets, switches & accessories
A friend for life

DRAPER
JOKARI

ESR Electronic Components
www.esr.co.uk

Tel: 0191 2514363
Fax: 0191 2522296
sales@esr.co.uk

Station Road
Cullercoats
Tyne & Wear
NE30 4PQ

Prices Exclude Vat @17%
UK Carriage £2.50 (less than 1kg)
£5.50 greater than 1kg or >£30
Cheques / Postal orders payable to
ESR Electronic Components.

PLEASE ADD CARRIAGE & VAT TO ALL ORDERS

EPE EVERYDAY PRACTICAL ELECTRONICS

THE UK'S No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

VOL. 36 No. 10 OCTOBER 2007

Editorial Offices:

EVERYDAY PRACTICAL ELECTRONICS EDITORIAL
Wimborne Publishing Ltd., Sequoia House, 398a Ringwood
Road, Ferndown, Dorset BH22 9AU
Phone: (01202) 873872. Fax: (01202) 874562.

Email: enquiries@epemag.wimborne.co.uk

Web Site: www.epemag.co.uk

EPE Online (downloadable version of EPE): www.epemag.com

EPE Online Shop: www.epemag.wimborne.co.uk/shopdoor.htm

See notes on **Readers' Technical Enquiries** below – we regret technical enquiries cannot be answered over the telephone.

Advertisement Offices:

EVERYDAY PRACTICAL ELECTRONICS ADVERTISEMENTS
Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU
Phone: 01202 873872 Fax: 01202 874562

Email: stewart.kearn@wimborne.co.uk

Saving the planet...

This month we present the *Standby Power Saver*. With much noise (hot air!) being generated about the cost to the environment of carbon emissions this is a topical subject. If we all turned off all of our appliances, instead of leaving them on standby, the power saved would be around 1TWh (one terrawatt hour – that is 1 with 12 zeros or 10^{12}) annually. With our fossil fuels running out it is a very significant saving. Of course, the Power Saver uses energy and its construction also uses energy, so we could never save the whole 1TWh, but every little helps!

The other area raising interesting arguments on power saving is the use of compact fluorescent lamps (CFLs) and various views on this have been aired in *EPE* over the last few months; the subject is addressed again this month in our *Banning The Bulb* article.

...or not!

I personally do not believe that the carbon emissions we generate are having any effect on the environment. A number of scientific studies do not support the global warming bandwagon – it may be getting warmer, but not because we take plane flights or run our cars, or turn on our TVs etc.

As John Becker shows in the *Standby Power Saver* article, the 'standby' electricity consumption in a year is equivalent to 1.4 million long haul flights, so maybe we should be protesting the equipment manufacturers and the government to legislate against 'standby' in its present form, rather than protesting airport expansion. Global travel is never going to go away, but we can easily do something to save electrical energy, as our project demonstrates.

As a matter of fact, the emissions from the cattle we breed for milk and beef do far more 'harm' than travel. Livestock are responsible for around 18 percent of 'greenhouse gasses' – more than all forms of travel put together, so maybe we should all become vegans!



AVAILABILITY

Copies of *EPE* are available on subscription anywhere in the world (see opposite) and from all UK newsagents (distributed by SEYMOUR). *EPE* can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased and downloaded for just \$18.99US (approx £9.50) per year, available from www.w.epemag.com

SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £18.75, 12 months £35.50, two years £66; Overseas: 6 months £21.75 standard air service or £30.75 express airmail, 12 months £41.50 standard air service or £59.50 express airmail, 24 months £78 standard air service or £114 express airmail. To subscribe from the USA or Canada call Express Mag toll free on 1877-363-1310

Online subscriptions, for downloading the magazine via the Internet, \$18.99US (approx £9.50) for one year available from www.epemag.com.

Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subs. Dept., Wimborne Publishing Ltd, Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Maestro or Visa. (For past issues see the *Back Issues* page.)

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue PVC, printed with the magazine logo in gold on the spine. Price £7.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days, but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Amex, Diners Club, Maestro and MasterCard accepted. Send, fax or phone your card number, card expiry date and card security code (the last 3 digits on or just under the signature strip), with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.



Editor: MIKE KENWARD

Consulting Editors: DAVID BARRINGTON

JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

General Manager: FAY KEARN

Editorial/Admin: (01202) 873872

Advertising Manager:

STEWART KEARN (01202) 873872

On-line Editor: ALAN WINSTANLEY

EPE Online (Internet version) Editors:

CLIVE (MAX) MAXFIELD and ALVIN BROWN

READERS' TECHNICAL ENQUIRIES

E-mail: techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years' old. Letters requiring a personal reply *must* be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons. We are not able to answer technical queries on the phone.

PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in *EPE* employ voltages that can be lethal. You should not build, test, modify or renovate any item of mains-powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

Although the proprietors and staff of *EVERYDAY PRACTICAL ELECTRONICS* take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment, as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.

Printing Without Wires

Has the security problem been cracked? Barry Fox examines the question.

Printing without wires is not as easy as it sounds. The system must ensure privacy for document printing and no risk of someone in the street or next door eavesdropping data or hijacking the printer, accidentally or maliciously, to waste paper and ink by printing hundreds of pages.

Bluetooth is reasonably secure because the signal is weak and does not leak through walls. But this makes it well nigh useless for home or office wireless networking.

WiFi to the IEEE 802.11 family of standards uses much stronger signals which reach several hundred metres, and through some walls. But WiFi is notoriously insecure unless the owner sets WEP or WPA password

keys on all networked equipment. Firewalls, antivirus and anti-spyware protection can then block communication unless correctly set up. So many people still use WiFi without security.

Lexmark claims to have cracked the problem of security with simplicity in a new range of seven printers, all with built-in WiFi. Set-up is by a Lexmark software CD which is run on the PC while connected to the printer by USB cable. The PC sends password instructions down the cable to the printer, which stores the instructions in non-volatile memory. The USB cable can then be disconnected and the PC and printer thereafter communicate securely by WiFi.

So the long-reach signals cannot be intercepted by a third party. Surprisingly, the new printers cannot be connected by WiFi to one of the new generation of WiFi cameras. Nor do they have built-in Bluetooth for wireless connection to a camera phone.

To print pictures from a camera, the owner must resort to the traditional techniques of connecting the printer to a PC by USB cables, or using the PictBridge standard for connecting the printer direct to a camera by USB cable, or taking the memory card from a camera and slotting it into the printer's card reader.

Lexmark was unable to say whether a future firmware upgrade will be available to let the new printers connect wirelessly to a WiFi camera.

Pico Trigger Power

Pico Technology have just added a set of advanced trigger types to the PicoScope 5000 series of scopes to make it easier to trigger on complex waveforms.

The PicoScope 5000 series PC Oscilloscopes are Pico's top-performing scopes, with the world's fastest real-time sampling rate, for a USB PC scope,


of 1GS/s. This, together with a probe-tip bandwidth of 250MHz, makes them ideal for use with high-speed analogue and digital signals. The scope's huge memory buffer – either 32M or 128M samples depending on the version – ensures that the high sampling rate can be used on a wide range of timebases without losing detail.

The new advanced trigger types are part of a continuing programme of upgrades for the PicoScope 5000 series scopes, which has recently seen the addition of an auto-setup command and a new spectrum view. The new trigger types are dual-edge, window, pulse-width, drop-out, interval and logic triggering. Window triggering detects when signals go into or out of a given range, so is useful for finding overvoltages. Pulse-width triggering can recognise short or long pulses, so it helps you find glitches and timing violations.

The drop-out trigger finds the moment when a repetitive signal, such as a clock, goes dead. Interval triggering detects when two successive clock edges fail to meet a timing condition. Finally, logic triggering lets you trigger on practically any combination of up to four input levels or voltage windows.

If you're troubleshooting digital signals, you will be able to use these new trigger types to obtain a stable display of complex digital waveforms, such as serial data streams and control signals. The PicoScope 5000 series scopes are ideal instruments for digital troubleshooting because of their high sampling rate and large buffer size, which when used together allow you to capture long-duration snapshots with high time resolution.

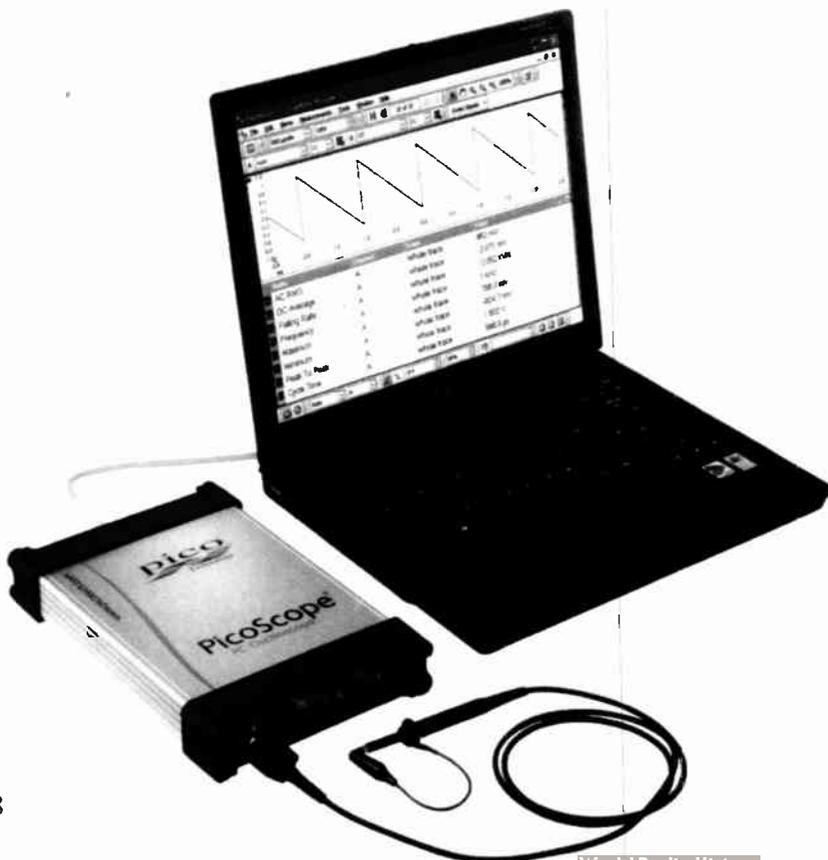The latest PicoScope 6 upgrade with advanced triggering is available now for download, free of charge, from the Pico Technology website at www.picotech.com. Call Pico on +44 (0) 1480 396 395 for more details.



Microchip Launches Semiconductor Wiki

Microchip has announced ICwiki – a website that enables engineers to collaborate and share information related to semiconductor products, applications and best practices. Using Wiki technology, participants can change content on the site and participate in web logging ('blogging'), voting and messaging. ICWiki is available in several different languages, including English, Chinese, Japanese, French, German, Italian, Portuguese, Russian and Spanish.

Following recent trends toward online social networking, ICwiki was designed to help engineers share knowledge about designs and applications, as well as helping university students gain access to knowledge that can help bridge their transition from academia to industry.

Participants can work together in either public or private blogs via the site's Group Decision Support Systems (GDSS) feature. Subject areas on the new Wiki include particular market areas such as automotive, home appliances and robotics; functional topics such as algorithms, oscillators, PCB layout best practices and signal conditioning; and product topics such as microcontrollers, Digital Signal Controllers (DSCs), analogue and memory products.



The new ICwiki, while promoting links between academia and industry, also forms an important part of the 'University of Microchip'. This is Microchip's education and training program, not only supporting universities all around the world, but also encom-

passing training provision in Regional Training Centres (RTCs) worldwide, at Microchip's MASTERS conferences and in online Design Centers.

For further information, visit Microchip's Web site at (www.microchip.com/ICwiki).

Robotics Research Fosters Wales and French Connection

Robots that are programmed to explore underwater and send images to the surface were among the research projects tackled by students from France who have spent four months working closely with lecturers at the University of Wales, Newport.

The four students, from Ecole Nationales Supérieure de Mécanique et des Microtechniques (L'ENSMM) in Besançon in Eastern France, came to Wales to work on a series of ongoing projects at the Mechatronics Research Centre in the University's Departments of Computing and Engineering.

"It was a pleasure to welcome these overseas students, whose work on a number of diverse robotics-based projects will enable us to continue our research by providing us with the hardware and software to try new control systems and artificial intelligence algorithms," said computing lecturer Dr Christopher Tubb.

"The students came here on the SOCRATES programme which supports European cooperation in key areas, including new technologies. They have been working with the Department of Computing on projects that make up the final year module element of the university's degree programme and also meet the requirements of their programme of study, which involves an internship with an industrial partner.

"One of the students, Antoine Faucher, carried out work on a new project we are looking at, possibly in conjunction with the local authority, which involves

Human Power Vehicles (HPVs). The local authority is interested both from a recycling and an in town without the car perspective, as we will probably be using old bikes and other recycled material. This project is linked to the idea that within an urban environment the use of human powered vehicles can provide personal transport in a clean, quiet and safe manner".

For further information browse www3.newport.ac.uk/news/displayStory.aspx?story_id=163.

MERG's 40th Anniversary

The Model Electronic Railway Group (MERG) is celebrating its 40th anniversary. Its Summer Journal just received reflects this.

As usual, the Journal reports the activities of the various groups around the southern UK. Features focus on model railways in general, including a PIC-based design for reading track occupancy into a PC, complete with the ASM code. Other electronic add-ons are discussed as well. It's good to see that matters relating to DCC controllers are coming more to the fore in the UK.

The Group also report that they have over 900 members and new ones are joining at the rate of 15 per month. They believe that this is due to the huge interest in DCC and the large reservoir of resources the Group is able to offer modellers.

To find out more about MERG, contact the Membership Secretary, Brian Martin, 40 Compton Avenue, Poole, Dorset BH14 8PY. Tel: 01202 701930. Email: memsec@merg.info.

TV SURGERY BOOKINGS

The Science Photo Library tell us that it is now possible to book a doctor's appointment in the UK through your digital TV. More than 1100 doctor's surgeries across the UK are offering booking and cancellation services through a TV, after a two-year pilot study showed that the method reduced the number of missed appointments, saving time for GPs and support staff.

The system is planned to expand in the near future, with the ability to order repeat prescriptions being added. The service is available through an interactive button on a digital TV remote control.

The Science Photo Library is at 327-329 Harrow Road, London W9 2RB. Tel: 020 7422 1100. Web: www.sciencephoto.com.

EOCS Magazine

We have been sent the latest quarterly issue of the magazine of the Electronic Organ Constructors Society (EOCS). Just one item that it's interesting to highlight here is an article on copying and restoring recording tapes. This news writer recently tried to buy some more quarter inch recording tape, and failed. Few shops knew what was wanted. None had product. This article relates to copying tapes to CD.

If you are interested in constructing electronic organs and related items, browse www.eocs.org.uk, or contact Ron Coates, Treasurer/Secretary EOCS, 2 Boxhill Way, Seaford, Sussex BN25 3QB. Tel: 01323 894909.

Keeping The Lights On

The chaos predicted by doomsayers for when fossil fuel resources run out is not inevitable. The radically new approach to power generation that we'll need may exist already. Mark Nelson examines an idea that defies received wisdom.

Today's prodigious consumption of electricity is unsustainable. But owners of tellys, washing machines and dishwashers are not minded to trade these for board games, tubs with hand mangles and washing-up brushes. Big problem? Yes. Inevitable? Not necessarily.

Right now everyone is contemplating the incredibly high cost of replacing traditional power stations with nuclear, windpower or wavepower systems. All of these have practical and environmental drawbacks ranging from minor to severe.

Radical rethink

Frequently received wisdom is wrong. So-called 'eco bulbs' (CFLs or compact fluorescent lamps) are totally un-ecological, as I explained last month. And there's a growing number of radical scientists who consider today's method of electrical power generation and distribution totally out-of-date.

Today, we generate electricity centrally and distribute it to consumers down long cables. It made perfect sense 50 years ago, but does the method still stack up? Does it make sense in a world starved of fossil fuel resources for generating that power?

Not according to energy analyst Walt Paterson, whose new book, *Keeping The Lights On: Towards Sustainable Electricity*, discusses how to deliver a genuinely sustainable electricity system for the future.

The self-professed troublemaker trained as a nuclear physicist and has spent the rest of his life teaching, writing and acting as a consultant. Now he proposes an entirely different way to think about energy, what we want from it and how we get it.

In his view, we can still enjoy the benefits of having electricity on tap; the only thing is that we'll produce it locally instead of centrally. This will require major investment but if this is the cheapest way of 'keeping the lights on', then it certainly deserves consideration. At the same time it opens the door to vast opportunities for designers and manufacturers to supply the electronic systems for supporting the new paradigm.

Paterson's patter

According to Walt Paterson, "Traditional electricity is a century old, obsolete and overdue for improvement. But we keep getting it wrong. The decisions that governments and companies are taking now are making matters worse, missing opportunities all over the world."

But although innovative technologies, novel finance models and greener business ethics all simplify the route towards sustainable electricity services, the evolution is much too slow. Too many governments, too many companies, too many people cling

stubbornly to out-of-date assumptions and mindsets, argues Paterson.

So what does he advocate? In a nutshell, the decentralisation of power generation. A very substantial amount of the electricity used in homes and offices worldwide is used to keep the ambient temperature more agreeable. Better thermal insulation and ventilation would eliminate much of the energy currently used in poorly designed buildings. Installing this in existing buildings is expensive but would cost far less if designed into all new buildings.

We also waste a lot of power on lights left on unnecessarily; simple time switches linked to motion detectors can switch off unneeded lights in factories and offices. These switches are available now but the cost of buying and retro-fitting them in existing buildings is a serious disincentive. Making them compulsory in new structures would open new mass markets, bringing down unit prices and guaranteeing reduced electricity bills.

Wrong model

The measures just described would reduce the amount of power used, as would greater use of more efficient (LED-based) light sources. Nevertheless, they are only palliatives and do not address the root cause of our waste of electricity – producing more than we need.

Unlike other public utilities such as water or gas, mains electricity cannot be stored. It has to be generated at the time it is used. The system, explains Paterson, therefore needs to have enough generation capacity available to meet the maximum load on the system. For most of the day, however, this generation operates below its maximum output or else stands idle.

To match the quantity of power generated to people's needs we can do this far more accurately on a small-scale decentralised basis, either locally for small groups of consumers or on-site per building or group of properties. Gas engines are feasible as are microturbines and solid-state inverters supplied by banks of batteries charged by solar cells and wind turbines. Stirling engines and fuel cells will be commercially more attractive too. "But such local generation still faces stubborn opposition in some quarters", remarks Paterson with obvious regret.

Dreams into reality

Early moves in this direction are already looking promising. A textbook scheme of this kind is working in Woking (Surrey), where the local authority installed the first sustainable community energy system of its type in the world. The technical description is combined heat and power (CHP)

co-generation, in which the heat produced in generating electricity is captured to produce hot water and central heating, unlike conventional power stations, which lose heat from electricity generation to the atmosphere.

Phase 1 of Woking's sustainable community energy network serves the Civic Offices, the Victoria Way Car Park (where the CHP station is located), two hotels, a conference and events centre and other premises. Surplus power is exported to other local buildings and sheltered housing. Woking is also the location of the UK's first combined residential photovoltaic/CHP project, where the integrated photovoltaics (solar cell) roof and CHP system have the potential to achieve 100% sustainability in electricity.

Woking is undoubtedly a world leader in sustainable energy use. The town has the UK's most energy-efficient public sector building stock, while the council offers private householders a condensing boiler for the same price as a conventional boiler. Nearly 10 per cent of Britain's solar photovoltaics are installed in Woking.

Further small-scale CHP plants, in which electronics have a vital control function, are being rolled out without fuss or commotion all over the country now. These so-called 'micro CHP' systems are being installed in a growing number of new residential developments by local authorities and housing associations, supplying affordable and constant, low-cost hot water, heating and electricity, and reduces emissions of carbon dioxide.

A typical system is the one supplied by specialist supplier EC Power Ltd at the Abbeyfields sheltered housing scheme in Faversham, Kent, which the company estimates will reduce Swale Housing Association's carbon dioxide output by 12,000kg per year.

Fantastic prospect?

Is this fantastic news for those worried about the planet – or simply fantasy? It's far too soon to determine but supporters of this approach are putting up powerful arguments. Walt Paterson is under no illusions and the last word goes to him.

"Sustainability can only emerge gradually, in electricity as in every other aspect. Minds, however, can change rapidly. If people stop taking the existing structure of electricity for granted, begin to examine and question it, and come to feel that an alternative structure would be preferable, this change of mind will have a fundamental effect on decisions taken from then on. If decisions are made not by some central authority but by a wide range of participants with varied interests, who see electricity differently, the effect may be untidy but dramatic."

Batteries



Zinc Chloride, Alkaline, NiMH, NiCD & Sealed Lead Acid batteries. We carry battery packs for racing & radio control. We also manufacture the NiCD Bot-Pack+, a high performance custom made pack with forced cooling options for the most demanding applications.

Sample pricing:

- GP AA Greencell £0.79 / pk4
- GP AA Greencell £0.13 / cell in trade boxes of 320 (ideal for schools)
- GP AA Ultra Alkaline £1.20 / pk4
- GP AA NiMH 1300mAh £3.95 / pk4
- Racing packs from £11.95
- 12V 2.2Ah to 44Ah SLA from £6.99

Power Supplies / Chargers



13.8V 20A power supply with Amps display £43.87

Power supplies fixed and variable voltage to 15V 40A. Chargers for NiCD, NiMH, LiPo & SLA batteries to 12V 20A.



Sample pricing:

- GP AA charger with 2 off 1300mAh cells £5.45
- 13.8V 20A Power Supply from £34.12

Motors



Probably the best range of DC model motors in the UK. From under 0.5W to 1000W, 1.5 to 36V. Geared motors from 0.3W to 800W. Ideal for most model engineering applications especially robotics. Planetary geared motors from just 1.2g to our top of the range 750W (that's 1HP) weighing in at 6.35kg.



As well as motors, we have wheels, axles & bearings to help complete your project.



Sample pricing:

- Visit our website to see over 140 models of motor
- 12V 150W Motor £17.95
- Geared motors from £4.70
- 750W 36V geared motors from £90.95

Visit our website to see over 2,000 products to order on-line. Need advice?, we offer full technical support via our FAQ forum.

Technobots Ltd
The Old Grain Store
Rear of 62 Rumbidge Street
Totton, Hampshire, SO40 9DS
Tel: 023 8086 3120 Fax 023 8086 1534
Lines open Mon - Thur 0900 to 1330

Technobots.co.uk

Robotics, Models and Technology Supplies

Established in 2001, Technobots Ltd supply a wide range of electronics and engineering products to the hobby market, schools, Colleges & Universities.

Motor Speed Controllers



DC motor speed controllers from 1A to 300A. Various interfacing options including RC, I2C, serial &

analogue voltage. Relay reversing and fully solid state H-bridge, single and dual channel variants.



Sample pricing:

- Dual 1A motor controller £17.09
- 10A motor controller kits from £19.87
- 75A controllers from £87.50

Radio Control



A wide range of radio control products including transmitters, receivers, servos, gyros, crystals, interfaces, leads etc.

Sample pricing:

- 4-Channel 40MHz FM transmitter / receiver / crystals from £34.95

Microcontrollers



The 'PICAXE' range of programmable microcontrollers. Write in BASIC or Flowchart and download straight into the microcontroller, so no expensive programmers are required. The 8 pin version provides 5 i/o pins (1 analogue input). The 18 pin version provides 8 outputs and 5 inputs (3 of the inputs have analogue capabilities). The 28-pin version provides 9-17 outputs, 0-12 inputs and 0-4 separate analogue inputs

Sample pricing:

- 8 pin starter kit including software, lead, battery holder, PCB & components for £9.94
- 28 pin version pictured above £21.74

Robot Kits

We carry a wide range of robot kits from BEAM to full combat and includes the very popular Robonova biped walker. Kits range in price from £16.95 to £689.05 built by enthusiasts & school pupils from all over the UK. Many are programmable via a PC, RC or autonomous. Full details of these and lots more can be found on our website.



Mechanical & Hardware



We carry a wide range of mechanical products many of which are hard to find elsewhere. Bearings from 1mm to 30mm bore. Plastic and steel pulleys, plastic and steel gears from MOD 0.5 to MOD 2.0. Steel chain sprockets in 6 & 8mm, 3/8" & 1/2" pitch. Silver steel, EN24T steel, collets & shaft couplings. Nuts and



bolts from M2 to M12, springs, clips & Pins. Wide range of engineering materials including aluminium (6082 T6 to 12mm thick), brass tube, rod, sheet etc..

Polycarbonate sheet from 1mm to 12mm thick, PVC sheet, polymorph etc.. Wheels from 9mm to 250mm diameter.

Featured Product




We believe this to be the lowest retail priced 4-channel 40MHz FM radio control set in the UK. The set includes the transmitter, receiver and crystal pair from just £34.95. Upgrade options available.

Sample pricing:


- Transmitter, receiver and xtals £34.95
- As above but with a set of 8 AA batteries £35.95
- or with a set of 8 AA rechargeable batteries £41.49
- Add a fast charger for an additional £11.46

Electrical

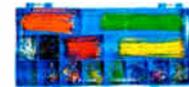

Glass, automotive and maxi fuses from 1A to 100A, fuse holders, cable from 0.5mm² to 16mm².

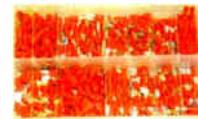Pre-stripped wire kits for breadboards. Connectors from 5A to 300A, wide range of crimp connectors bagged in 100's or in kits. Circuit breakers from 3A to 30A. Cable ties, tie bases, spiral wrap and heatshrink (1.2 to 101.6mm diameter).



All prices include VAT



Whilst we are an internet based company, we do have a shop where visitors are very welcome to browse.

Please check our website for opening hours and if making a long journey, we suggest phoning first to ensure stock availability. If ordering on-line, 90% of orders dispatched within 2 working days.

PayPal



By JOHN CLARKE

V8

DOORBELL



Is the sound of a V8 music to your ears? Does the roar and deep rumble of a V8 engine raise your pulse rate? With this V8 doorbell you can impress your friends and neighbours. You can have the sound of a V8 without even starting your car. In fact, you don't even need a car.

Does the sound of a powerful V8 instead of a boring 2-tone doorbell appeal to you? This V8 doorbell really does sound like a V8 and it is loud as well, with an inbuilt 5-watt amplifier.

Not only does it sound like a proper V8, it also lights up an 8-LED 'V' display, each time you press the doorbell pushbutton. In fact, you can have a V8-LED display at your front door and another on the doorbell case.

The V8 Doorbell is housed in a plastic case and is powered by a plugpack. For normal use, the internal 100mm diameter loudspeaker can be used and this provides a good simulation

of the V8 sound, particularly if the loudspeaker is 'tuned' using a length of PVC pipe – more on this later. For more volume, you can use a larger loudspeaker or if you want to go the whole hog, connect a bigger power amplifier and loudspeaker.

If the V8 Doorbell does not sound quite how you like it, you can easily tailor the circuit to make small changes to the way the V8 sounds. Altering the software can make even greater changes. That way, you may be able to reproduce the sound of your favorite V8.

We even allow for simulation of V6 engines. Well, grudgingly, and there are some restrictions on

the settings that can be used. But enough of puny engines; let's get back to V8s.

That 'lurveverly' V8 burble

V8s have a characteristic sound that makes them stand out from smaller engines. Each marque has its own 'sound' that distinguishes it from the others and much effort is made by the manufacturers to ensure that their V8 has the most appealing 'signature'.

The characteristic V8 sound is mainly determined by the way the exhaust system is configured. In a typical V8, each cylinder of the engine is connected to an exhaust outlet pipe with four pipes merging into one, on each side of the engine.

Some V8s have completely separate left and right exhaust systems (twin exhausts). The lengths of pipe between the engine and silencer affect the way the sound is mixed from the two sides of the engine. In a single exhaust system, one exhaust pipe must be longer than the other, to reach to the one side of the car body. In a twin exhaust, the mixing happens in the air and at our ears.

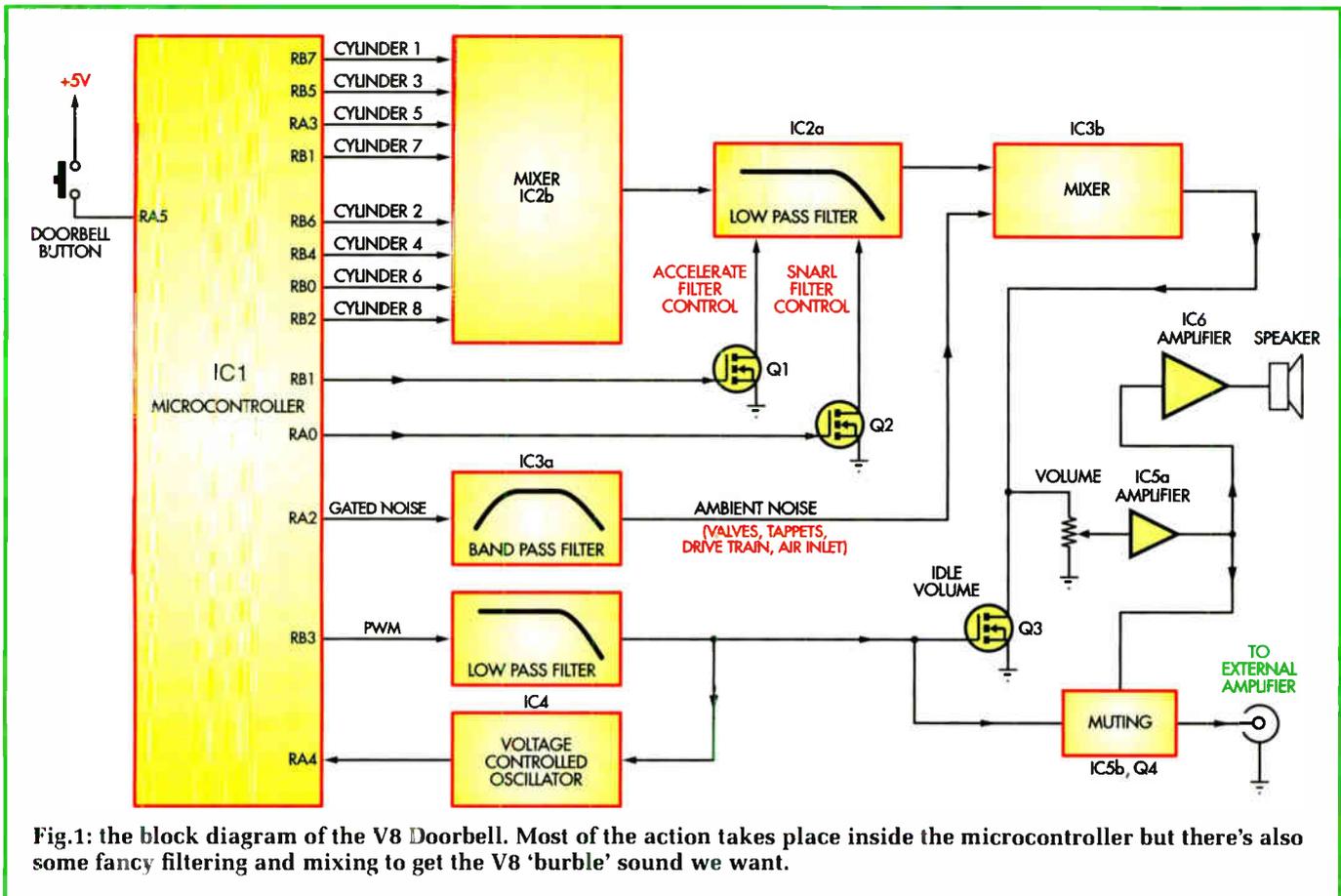


Fig.1: the block diagram of the V8 Doorbell. Most of the action takes place inside the microcontroller but there's also some fancy filtering and mixing to get the V8 'burble' sound we want.

Block diagram

We have simulated the sound of a V8 with the above principles in mind. The block diagram of Fig.1 shows how it is done. When the doorbell is pressed, the microcontroller begins to produce signals from eight ports to simulate the firing of the eight cylinders. They produce tones in a sequence similar to the firing in a real engine. Typically, there can be an overlap between when one cylinder fires and the next, so in effect there can be two sources of signal at any one time.

In this design, you can select several overlap options and the degree of overlap between the cylinders will affect the sound of the simulated engine. The overlaps that can be selected are a 60° overlap, a 30° overlap, zero overlap or a 30° gap between cylinder firing.

Cylinder outputs 1-4 produce their tones with different phasing to that of cylinder outputs 5-8. This is to simulate mixing of the left and right side exhausts of the engine. You can alter the phase from its initial 180° setting to any other value in steps of about 20°.

Cylinder outputs are mixed together in IC2b and then fed through a low-pass filter. This filter acts like a silencer in that it attenuates high frequency noise but allows through some low frequency noise. The Accelerate Filter Control (Q1) and the Snarl Filter Control (Q2) alter the way the filter works. These make changes to the filter characteristics to allow more high frequency signals to pass during acceleration and at high RPM simulation.

The microcontroller's RA2 port functions as a gated noise source, generating random noise only during part of each cylinder's firing cycle. This simulates valve, tappet, drive train and air inlet sounds. This is fed to bandpass filter IC3a and then mixed with the cylinder signal by IC3b.

Transistor Q3 provides for an increase in volume level at higher RPM, under control of a pulse width modulated (PWM) signal from port RB3 of the micro. After filtering, the PWM signal becomes a DC voltage to drive Q3. This DC voltage also controls a voltage controlled

oscillator (VCO) which alters its frequency depending on the input voltage. The VCO's output is fed to port RA4 of IC1 and it therefore determines the effective engine RPM.

The final signal is fed to the volume control pot and amplifier IC5a. This is muted so that there is no signal until the doorbell is pressed. Power amplifier IC6 drives the loudspeaker.

Circuit details

Fig.2 shows the complete circuit. IC1 is a PIC16F628 microcontroller that produces the simulated V8 engine signals. IC1 operates at 20MHz, as set by crystal X1.

The doorbell input at RA5 is normally low (0V) when switch S1 is open, since the 1kΩ resistor pulls it to ground. When the switch is closed, the input is pulled to +5V. A 100nF capacitor across the resistor removes noise picked up by the doorbell wiring, while the 2.2kΩ resistor acts to restrict current to the RA5 input if there is a transient voltage spike. The closed switch is detected by IC1 and so it begins to produce the engine sound sequence.

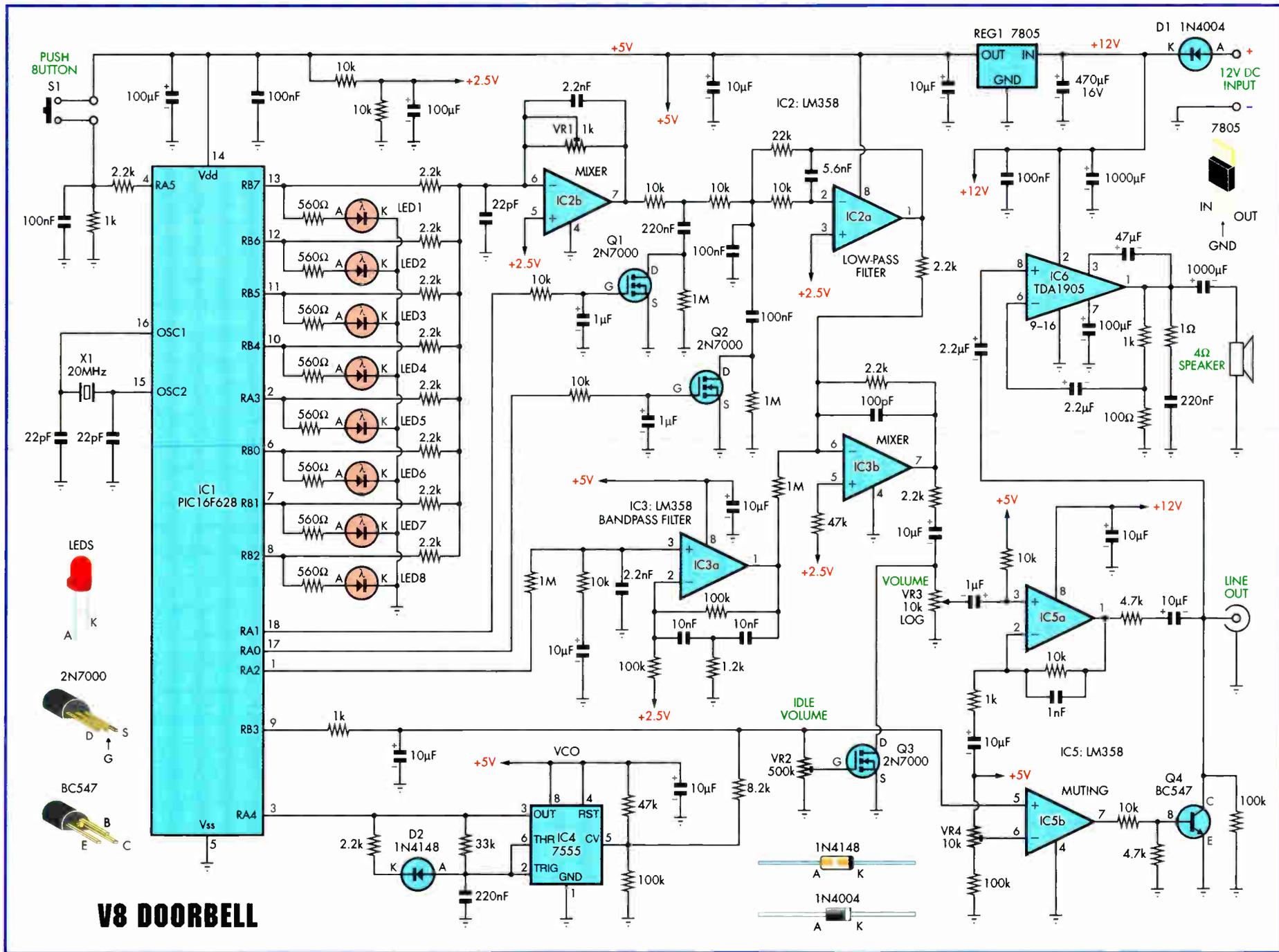


Fig.2 (left): the complete circuit of the V8 Doorbell. A PIC16F628 microcontroller (IC1) produces the simulated V8 engine signals. These signals are then processed and fed to audio amplifier stage IC6.

The port outputs at RB0 to RB2, RA3 and RB4 to RB7 are applied via 2.2kΩ resistors to op amp IC2b, connected as a mixer with its gain set by trimpot VR1. These ports also drive LEDs 1 to 8 via 560Ω resistors to give the V8 display. Op amp IC2a is the low-pass filter stage. In its normal state, this filter acts to sharply roll off the signal above 600Hz when MOSFETS Q1 and Q2 are both switched on.

When Q1 is switched off, its associated 220nF capacitor is effectively switched out of circuit and this reduces the filter's effectiveness at rolling off signal levels above 185Hz. Similarly, when Q2 is switched off, the 100nF capacitor is out of circuit and the filter action is further reduced.

The 1MΩ resistors tying the capacitors to ground are included to maintain the DC voltage across these capacitors so that there is no DC shift in signal when they are switched in or out. Q1 and Q2 are controlled by the RA1 and RA0 outputs of IC1 respectively. The 10kΩ resistor and 1μF capacitor on the gate (G) of each MOSFET slow down the switch-on and switch-off rates of the MOSFETS to eliminate switching noise.

In practice, both MOSFETS are switched on during idle to provide the full effect of the filter. When the 'engine' speed is increased, Q1 is switched off to produce the noise of acceleration and as RPM rises further, Q2 is switched off for the 'snarl' effect at high RPM. The low-pass filter output at pin 1 of IC2a is fed to op amp IC3b, another mixer, via a 2.2kΩ resistor.

Gated noise

Gated noise from the RA2 output of IC1 is attenuated via a voltage divider comprising a 1MΩ resistor and a 10kΩ resistor in series with a 10μF capacitor. The 10nF capacitors and 1.2kΩ resistor form a half-T filter that allows a relatively narrow band of frequencies, centred on about 6.6kHz, to pass through. The 100kΩ resistor between pin 2 and pin 1 broadens the bandwidth of the filter to allow a wider range of frequencies to pass than if the

Parts List – V8 Doorbell

- 1 main PC board, code 637, available from the *EPE PCB Service*, size 171mm x 105mm
- 1 display PC board, code 638, size 56 x 48mm
- 1 plastic utility box, 197 x 113 x 63mm
- 1 12V DC 1A plugpack
- 1 4Ω 100mm diameter loudspeaker
- 1 130mm length of 100mm diameter PVC tubing
- 1 doorbell switch (S1)
- 1 20MHz crystal (X1)
- 1 8-way right-angle pin header
- 1 8-way pin header
- 2 8-way pin header sockets
- 1 2-way PC-mount screw terminal block
- 1 2.5mm DC socket
- 1 panel-mount RCA phono socket
- 1 knob to suit potentiometer
- 1 80mm length of 8-way rainbow cable
- 1 150mm length of 3-way rainbow cable
- 1 80mm length of hookup wire
- 1 80mm length of single-core shielded cable
- 1 80mm length of figure-8 light duty wire
- 1 suitable length of figure-8 doorbell wire
- 1 150mm length of 0.8mm tinned copper wire
- 4 12mm M3 tapped spacers
- 13 M3 x 10mm screws
- 5 M3 nuts
- 9 PC stakes

Semiconductors

- 1 PIC16F628 microcontroller programmed with engine3.hex (IC1). Ready-programmed PICs are available from Magenta Electronics – see their advert
- 3 LM358 dual op amps (IC2, IC3, IC5)

- 1 7555 CMOS timer (IC4)
- 1 TDA1905 5W amplifier (IC6)
- 3 2N7000 MOSFETS (Q1-Q3)
- 1 BC547 NPN transistor (Q4)
- 1 7805 5V regulator (REG1)
- 1 1N4004 1A diode (D1)
- 1 1N4148 switching diode (D2)
- 8 5mm red high intensity LEDs (LED1-LED8)

Capacitors

- 2 1000μF 16V PC electrolytic
- 1 470μF 16V PC electrolytic
- 3 100μF 16V PC electrolytic
- 1 47μF 16V PC electrolytic
- 10 10μF 16V PC electrolytic
- 2 2.2μF 16V PC electrolytic
- 3 1μF 16V PC electrolytic
- 3 220nF MKT polyester
- 5 100nF MKT polyester
- 2 10nF MKT polyester
- 1 5.6nF MKT polyester
- 2 2.2nF MKT polyester
- 1 1nF MKT polyester
- 1 100pF ceramic
- 3 22pF ceramic

Resistors (0.25W 1%)

- | | |
|---------|----------|
| 4 1MΩ | 2 4.7kΩ |
| 5 100kΩ | 13 2.2kΩ |
| 2 47kΩ | 1 1.2kΩ |
| 1 33kΩ | 5 1kΩ |
| 1 22kΩ | 8 560Ω |
| 11 10kΩ | 1 100Ω |
| 1 8.2kΩ | 1 1Ω |

Potentiometers

- 1 1kΩ multi-turn side adjust screw trimpot (code 102) (VR1)
- 1 500kΩ horizontal trimpot (code 504) (VR2)
- 1 10kΩ log 16mm potentiometer (VR3)
- 1 10kΩ horizontal trimpot (code 103) (VR4)

resistor was not present. The output of IC3a is fed to mixer IC3b via a 1MΩ resistor.

The output from IC3b is passed through a 2.2kΩ resistor and a 10μF DC blocking capacitor. MOSFET Q3 shunts this signal to ground when conducting but has no effect on the signal throughput when it is switched off.

Q3 is controlled via the filtered PWM signal from pin 9 of IC1. The

1kΩ resistor and 10μF capacitor filter this 19kHz signal and the filtered DC voltage is applied via trimpot VR2 to the gate of Q3.

Op amp IC5a is a non-inverting amplifier with a gain of 11. It amplifies the signal taken from the wiper of VR3 so that the level is suitable for the following power amplifier. IC5a is biased at +5V so that when there is no signal, its pin 1 output sits at 5V. This allows a large voltage swing before the output clips. High

Table 1: Capacitor Codes

Value	μF Code	IEC Code	EIA Code
220nF	0.22 μF	220n	224
100nF	0.1 μF	100n	104
10nF	0.01 μF	10n	103
5.6nF	0.0056 μF	5n6	563
2.2nF	0.0022 μF	2n2	222
1nF	0.001 μF	1n0	102
100pF	NA	100p	100
22pF	NA	22p	22

frequency roll-off for the amplifier is set at around 16kHz to prevent high-frequency instability. Its output is coupled to power amplifier IC6 via a 4.7k Ω resistor and a 10 μF DC blocking capacitor.

Transistor Q4 provides muting of the output signal and is controlled by comparator IC5b and the filtered PWM signal from pin 9 of IC1. IC5b operates in the following way. When the circuit is quiescent (ie, not producing any V8 sounds), the filtered PWM signal is at 5V. This is monitored at pin 5 of IC5b and is compared with the voltage set by trimpot VR4, fed to pin 6. VR4 is set so that pin 6 is at about 4.7V and so pin 7 of IC5b will be high at around 11V. This high signal drives the base of Q4 which therefore shunts any noise signals to ground.

When the doorbell is pressed, the microcontroller begins to produce the V8 sounds and the PWM signal immediately drops to 4.5V and so pin 7 of IC5b goes low and Q4 is switched off. The signal at IC5a's output now passes to the Line output socket and to IC6, the power amplifier.

Power amplifier

IC6 is a TDA1905 power amplifier rated to produce 5W into 4 Ω with a 14V supply. It includes thermal shutdown if it overheats and a very low noise output. For the intermittent use it gets in this circuit, it is ideal. Gain of the amplifier is set at 11 by the 100 Ω and 1k Ω resistors connected between pin 1 and ground, with the feedback signal AC-coupled to pin 6 via a 2.2 μF capacitor.

The 100 μF capacitor at pin 7 provides supply ripple rejection, while the 47 μF capacitor between pin 1 and pin 3 provides classic bootstrapping between the amplifier's output and driver stages. A 1000 μF capacitor across the 12V supply provides a reserve for transient power output while a 100nF bypass capacitor provides high-frequency filtering.

IC4 is a CMOS 555 timer set up as a voltage controlled oscillator (VCO). Its output is fed to port RA4 (pin 3) of the microcontroller to determine the audible engine RPM.

Pin 5 (threshold control) is used to set the output frequency. When pin 3 of IC4 is low, diode D2 discharges the 220nF capacitor at pins 2 and 6 relatively quickly, via the series connected 2.2k Ω resistor. When pin 3 goes high, the 220nF capacitor only charges via the 33k Ω resistor since D2 is now reversed-biased.

The resulting pulse waveform at pin 3 has a relatively short low period and a longer high-level period; ie, a high duty cycle. We then vary the voltage at pin 5 to control the output frequency. When pin 5 is up around 5V, the frequency is low and if pin 5 is low the frequency is higher.

Power for the circuit is provided by a 12V DC plugpack. Diode D1 prevents damage if the supply is connected the wrong way round, while the 470 μF capacitor provides extra filtering. The 12V supply feeds IC5 and IC6 while REG1, an LM7805 5V regulator, supplies the rest of the circuit.

Construction

The V8 Doorbell is built onto two PC boards: a main board coded 637 (171 x 105mm) and an LED display board coded 638 (56 x 48mm). The two PC boards and the 100mm diameter loudspeaker are housed inside a plastic utility box measuring 197 x 113 x 63mm.

Before installing any of the parts, check the two PC boards for any shorts between the copper tracks or for any breaks in the connections. Also check the hole sizes. You will need 3mm holes for the mounting positions in the four corners of the display PC board and for the regulator screw on the main PC board.


That done, begin the assembly by installing the links and resistors on the main PC board – see Fig.3. Use the resistor colour table as a guide to selecting each resistor, then check each value using a digital multimeter.

Once the resistors are in, the diodes can be installed, taking care with their orientation. Follow these with IC2 to IC6, make sure that each IC goes in the correct position and is mounted the right way around.

An IC socket must be used for IC1, the PIC. Install it now, then solder in the three MOSFETS (Q1 to Q3) and transistor Q4.

Table 2: Resistor Colour Codes

No.	Value	4-Band Code (1%)	5-Band Code (1%)
4	1M Ω	brown black green brown	brown black black yellow brown
5	100k Ω	brown black yellow brown	brown black black orange brown
2	47k Ω	yellow violet orange brown	yellow violet black red brown
1	33k Ω	orange orange orange brown	orange orange black red brown
1	22k Ω	red red orange brown	red red black red brown
11	10k Ω	brown black orange brown	brown black black red brown
1	8.2k Ω	grey red red brown	grey red black brown brown
2	4.7k Ω	yellow violet red brown	yellow violet black brown brown
13	2.2k Ω	red red red brown	red red black brown brown
1	1.2k Ω	brown red red brown	brown red black brown brown
5	1k Ω	brown black red brown	brown black black brown brown
8	560 Ω	green blue brown brown	green blue black black brown
1	100 Ω	brown black brown brown	brown black black black brown
1	1 Ω	brown black gold gold	brown black black silver brown

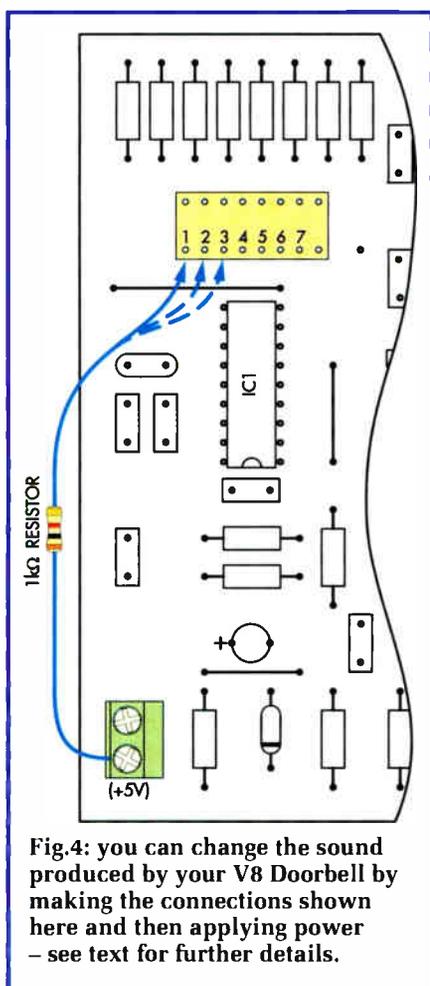

right-angle header plug and a PC stake. Don't install the LEDs just yet – that step comes later.

Putting aside the display board for the moment, our next task is to prepare the case. This involves drilling eight holes in a 'V' pattern for the eight LEDs, plus four mounting holes each for the display board and the loudspeaker. In addition, you will also have to drill holes in the lid in front of the loudspeaker cone area, to allow sound to escape.

Another hole is required in the front panel for the volume control pot. And finally, two holes are required in one end of the base for the RCA (phono) output socket and the DC power plug, plus another hole in the opposite end for the doorbell switch wire entry.

The four 12mm tapped Nylon spacers can now be fastened to the lid at the display board mounting points. These are secured using four M3 × 6mm screws.

That done, slip the eight LEDs into their mounting holes on the PC board (make sure you get them the right way around), then secure the board

to its spacers. It's then simply a matter of pushing the LEDs through their respective holes in the front panel and then soldering their leads to their copper pads.

Finally, the loudspeaker and pot can be secured to the lid and the wiring completed as shown in Fig.3. Don't forget to run the wire lead from the PC stake near the 8-way header on the main board to the PC stake on the display board.

Test and adjustment

Now for the smoke test. First, apply power to the circuit and check for 5V between pins 4 and 8 of both IC2 and IC3, between pins 1 and 4 of IC4 and between pins 5 and 14 of IC1. That done, check for about 12V between pins 4 and 8 of IC5 and pins 2 and 9 of IC6.

If these voltages are correct, switch off and install IC1 in its socket. However, if there are no voltages, check the polarity of the DC plug on the plugpack. The centre pin should be positive.

OK, now let's see if it actually works. To do this, connect the doorbell switch to the terminal block (using figure-8 wire) and adjust the various trim pots as follows:

- (1) set VR1 fully anticlockwise;
- (2) set VR2 and VR3 fully clockwise;
- (3) set VR4 so that its wiper voltage is at +4.7V with respect to ground.

Now press the doorbell and slowly adjust multi-turn trimpot VR1 clockwise. The engine sound should start to increase in volume. The final setting for VR1 depends on personal preference

– set it too far clockwise and the sound will become very harsh. A lower setting will produce a cleaner engine sound.

Trimpot VR2 is set so that you obtain the required idle volume, compared to the 'rev up' volume. It's just a matter of slowly adjusting this pot until the idle volume is suitably lower than the 'revved-up' volume.


If required (ie, if you want more 'oomph'), a 100mm PVC pipe joiner (or 120mm length of pipe) can be secured to the lid in front of the loudspeaker using silicone sealant. This 'tuned' pipe makes the sound more resonant and penetrating. If you like, you can try different lengths of pipe to vary the effect.

Note that you may need to file some slots in the pipe so that it clears the loudspeaker mounting screws.

Individual preferences


There are seven setting changes that can be made to IC1's software to produce different sounds. This involves connecting a wire and a series 1kΩ resistor between the +5V terminal (for the doorbell switch) and one of seven terminals on the 8-way header pin, as shown in Fig.4.

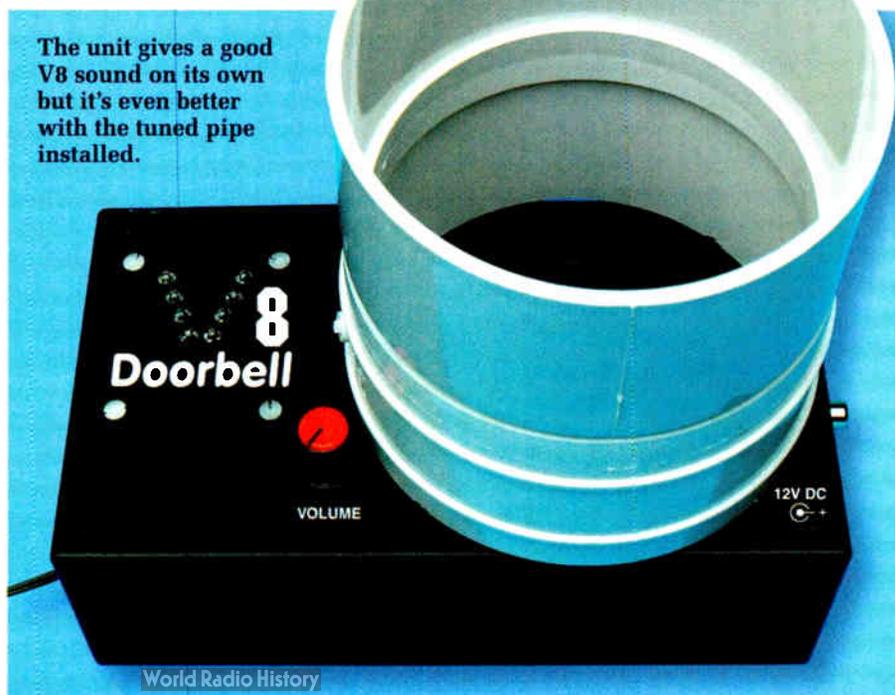When a connection is made to one of these pins during power up, the required software change is made automatically. Note, however, that it's important that the +5V supply rail is fully discharged to 0V before powering up if the change is to take effect.



Constructional Project

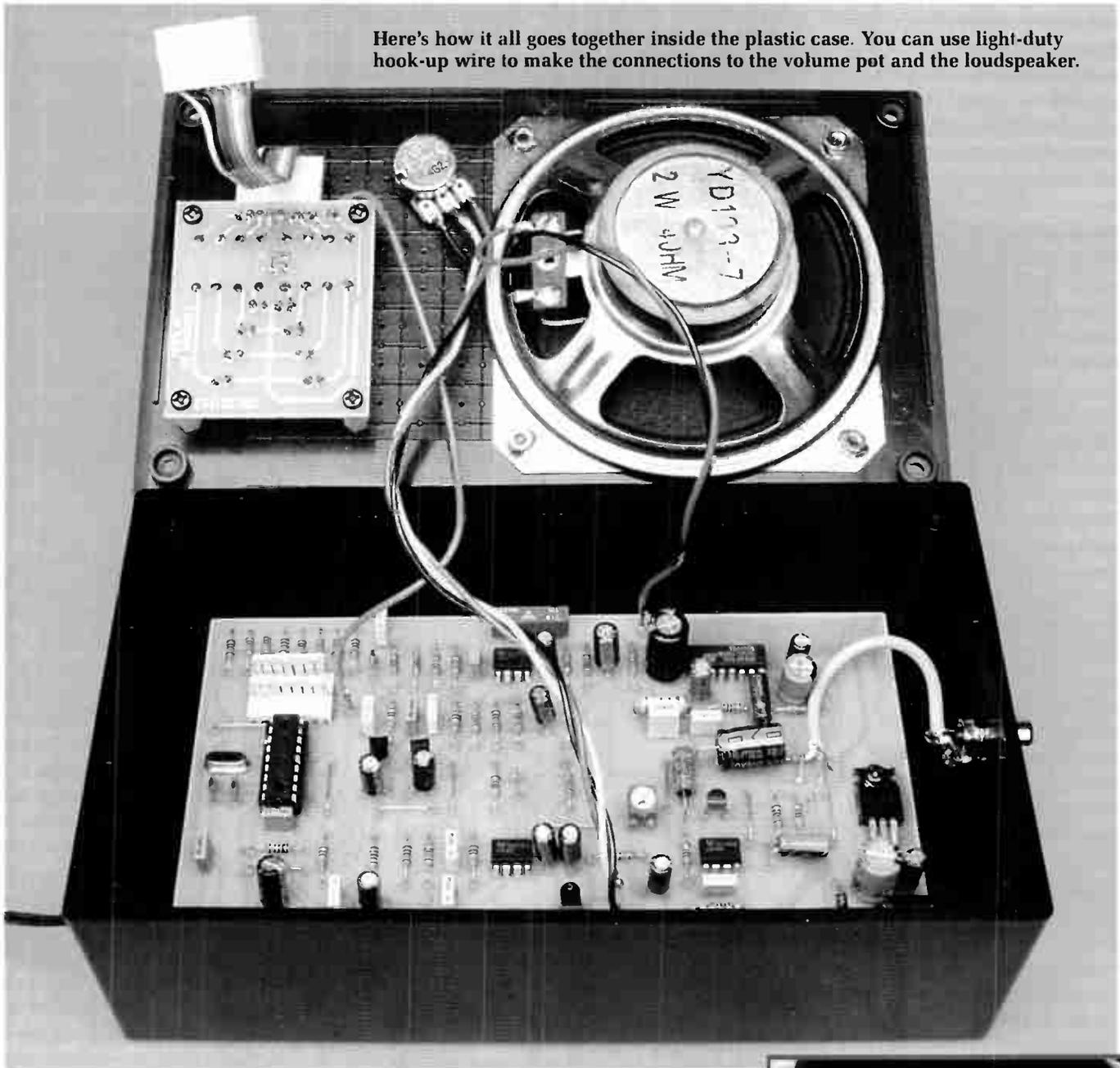Here's how it all goes together inside the plastic case. You can use light-duty hook-up wire to make the connections to the volume pot and the loudspeaker.



In fact, it's a good idea to measure the voltage between the +5V terminal of REG1 and ground after the power is switched off, to ensure the power has been completely removed.

Note also that the resistor only has to be connected at power up. It can then be disconnected when you are satisfied with the new sound. The options available are summarised below:


Terminal 1: you can adjust the V8 sound to simulate different lengths of exhaust pipe between the lefthand and righthand sides of the engine. This is the phasing adjustment. Phasing can

be altered in steps of about 20°, from its original default of 180°.


Terminal 2: the 180° default setting of the phase and the exhaust note frequency can be reset using this input (see Terminals 5 and 6 below).

Terminal 3: this terminal alters the amount of overlap for the sound generated by each cylinder firing. It can be altered in sequence from 60° to 30° to 0° and finally to a 30° gap.

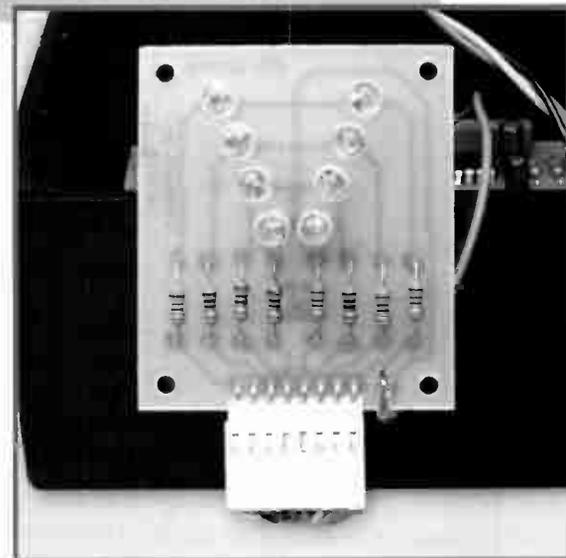Terminal 4: the 6 or 8-cylinder selection is made using this input. This alternatively selects either setting, with the LED display showing which cylinders are firing.



Constructional Project

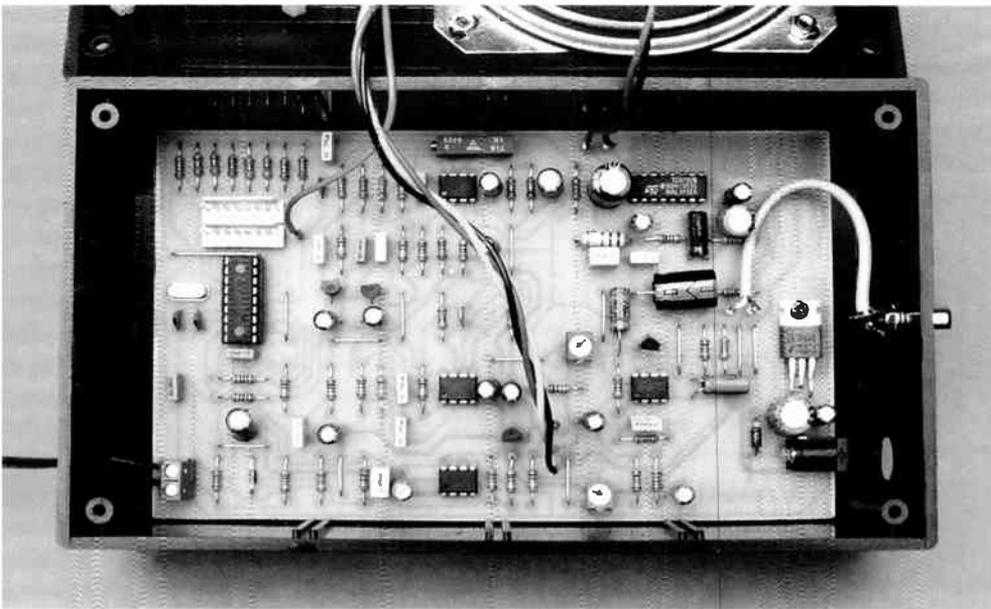

The PC board is secured by clipping it into the integral slots in the side of the case. Power comes from a 12V DC 1A plugpack.

Note that only the 0° and 30° gap settings should be used in 6-cylinder mode. Do not use the 60° and 30° overlap settings, as this will simulate a 6-cylinder engine with an erratic seventh cylinder. The correct setting will be seen on the 'V' display when only six LEDs light. If seven LEDs light, change the overlap setting using Terminal 3.

Terminals 5 and 6: these inputs allow the exhaust frequency to be

altered slightly. Terminal 5 increases the frequency, while Terminal 6 lowers it.

If the frequency is increased too far from the original value, the sound will have a 'raspy' quality at the top of the rev range. However, it takes many applications of power to make large changes to the frequency.

The frequency can be reset to its default value using Terminal 2.

Terminal 7: this selects whether the

doorbell includes an idling period before the two revving sequences.

Other changes

The idle RPM can be set by changing the 33kΩ resistor at pin 3 of IC4 – a larger resistance will lower the RPM or you can use a 50kΩ trimpot to adjust this to your liking.

The ambient noise can be increased in frequency by decreasing the 1.2kΩ resistor in the 'twin-T' filter of IC3a and vice versa. In addition, the 10kΩ resistor at pin 3 of IC3a sets the degree of mixing with the cylinder firing sound. A lower value will reduce the ambience and vice versa, or you can use a 22kΩ trimpot to adjust this.

You can also make major changes to the doorbell sound characteristics by altering the software. To do this, you will need to be able to modify the software, reassemble the code and re-program IC1. Some PIC programming experience will be necessary.

A much fuller sound is available if you use a large loudspeaker housed in a suitable box. For more volume, you may want to use a more powerful amplifier and this can be connected using the RCA phono line output socket.

If you do this, you can either disconnect the internal loudspeaker or you can leave it connected so that it operates as an extension. **EPE**



OUT NOW £6.99

FROM WHSMITH, OR £8.50 INCLUDING P&P FROM OUR *DIRECT BOOK SERVICE*

ELECTRONICS TEACH-IN


BY MIKE TOOLEY

plus FREE CD-ROM

A broad-based introduction to electronics – find out how circuits work and what goes on inside them. Plus 15 easy-to-build projects. The 152 page A4 book comes with a free CD-ROM containing the whole *Teach-In 2006* series (originally published in *EPE*) in PDF form, interactive quizzes to test your knowledge, TINA circuit simulation software (a limited version – plus a specially written TINA Tutorial), together with simulations of the circuits in the *Teach-In* series, plus Flowcode (a limited version) a high level programming system for PIC microcontrollers based on flowcharts.

Available from larger branches of WHSmith or see our *Direct Book Service*

Learn About Microcontrollers

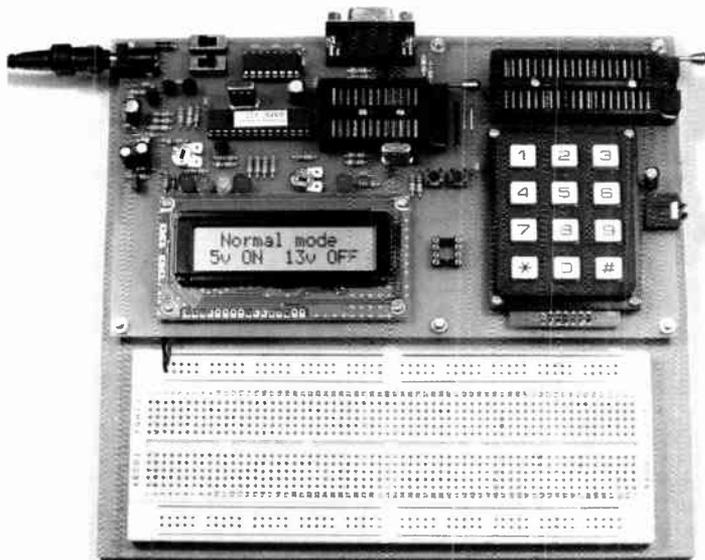

PIC Training Course £159

The best place to begin learning about microcontrollers is the PIC16F627A. This is very simple to use, costs just £1.30, yet is packed full of features including 16 input/output lines, internal oscillator, comparator, serial port, and with two software changes is a drop in replacement for the PIC16F84.

Our PIC training course starts in the very simplest way. At the heart of our system are two real books which lie open on your desk while you use your computer to type in the programme and control the hardware. Start with four simple programmes. Run the simulator to see how they work. Test them with real hardware. Follow on with a little theory.....

Our PIC training course consists of our PIC programmer, a 300 page book teaching the fundamentals of PIC programming, a 274 page book introducing the C language, and a suite of programmes to run on a PC. The module uses a PIC to handle the timing, programming and voltage switching. Two ZIF sockets allow most 8, 18, 28 and 40 pin PICs to be programmed. The programming is performed at 5 volts, verified with 2 volts or 3 volts and verified again with 5.5 volts to ensure that the PIC works over its full operating voltage. UK orders include a plugtop power supply.

P927 PIC Training & Development Course comprising.....

Universal 16C, 16F and 18F PIC programmer module

+ Book Experimenting with PIC Microcontrollers

+ Book Experimenting with PIC C

+ PIC assembler and C compiler software on CD

+ PIC16F627A, PIC16F88, PIC16F870

and PIC18F2321 test PICs. £159.00

(Postage & insurance UK £10, Europe £18, Rest of world £25)

Experimenting with PIC Microcontrollers

This book introduces PIC programming by jumping straight in with four easy experiments. The first is explained over ten and a half pages assuming no starting knowledge of PICs. Then having gained some experience we study the basic principles of PIC programming, learn about the 8 bit timer, how to drive the liquid crystal display, create a real time clock, experiment with the watchdog timer, sleep mode, beeps and music, including a rendition of Beethoven's *Fur Elise*. Then there are two projects to work through, using a PIC as a sinewave generator, and monitoring the power taken by domestic appliances. Then we adapt the experiments to use the PIC16F877 family, PIC16F84 and PIC18F2321. In the space of 24 experiments, two projects and 56 exercises we work through from absolute beginner to experienced engineer level using the most up to date PICs.

Experimenting with PIC C

The second book starts with an easy to understand explanation of how to write simple PIC programmes in C. Then we begin with four easy experiments to learn about loops. We use the 8/16 bit timers, write text and variables to the LCD, use the keypad, produce a siren sound, a freezer thaw warning device, measure temperatures, drive white LEDs, control motors, switch mains voltages, and experiment with serial communication.

Web site:- www.brunningsoftware.co.uk

Visual C# Course £88

Visual C# Training Course comprising.....

Book Experimenting with Visual C#

+ AUX200 latching serial port

+ liquid crystal display assembly

+ programme text on CD

+ pack of components. £88.00

(Postage UK £8, Europe £14, Rest of world £22)

You will need to download Visual C# Express which is free. Full instructions are in the book.

In October 2003 Martin Crane purchased our original PIC training course and in September 2005 he updated to the latest version. Three weeks before Christmas 2006 we had a telephone call from Mrs Crane to order our Visual C# training course as a Christmas present for her husband. On 21st March 2007 we received an email from Martin Crane which includes his personal review of the course. Here are a few lines from his text.....

For years I've wished to write my own applications that control external equipment from my PC.

Eureka! Peter Brunning has shown just how simple it really is. I am up and running at last. Most people seem to start with Visual BASIC, I found it truly frustrating. C# has combined everything you could wish for and more besides. The visual interface will be instantly familiar to Visual BASIC users but with far more options. The code side is dealt with by Peter in such a way that with no knowledge what so ever you can within a very short time be using the serial port. Brunning Software's serial port interface (included with the course) comes pre-programmed but the code is listed in the book together with the available features. Congratulations Peter for producing a truly hands on training package.

Martin Crane


(a very satisfied customer)

See:- www.brunningsoftware.co.uk/vcreview.htm

Ordering Information

Both training courses need either a free serial port on your PC or a USB to COM adapter (full details on website). All software referred to in this advertisement will operate within Windows XP, NT, 2000 or later.

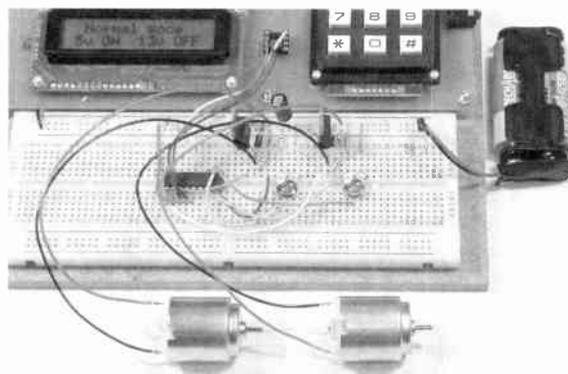Telephone with Visa, Mastercard or Switch, or send cheque/PO. All prices include VAT if applicable.



White LED and Motors

Our PIC training system uses a very practical approach. Towards the end of the second book circuits need to be built on the plugboard. The 5 volt supply which is already wired to the plugboard has a current limit setting which ensures that even the most severe wiring errors will not be a fire hazard and are very unlikely to damage PICs or other ICs.

We use a PIC16F627A as a freezer thaw monitor, as a step up switching regulator to drive 3 ultra bright white LEDs, and to control the speed of a DC motor with maximum torque still available. A kit of parts can be purchased (£30) to build the circuits using the white LEDs and the two motors. See our web site for details.

Mail order address:

Brunning Software

138 The Street, Little Clacton, Clacton-on-sea,
Essex, CO16 9LS. Tel 01255 862308

JAYCAR ELECTRONICS

Minimum Order



430+ Pages
Full Colour

675+ New
Products

Minimum
order now
only £10


Visit
www.jaycarelectronics.co.uk
and obtain your free copy
of our 430+ page full
colour catalogue.



2 Channel USB Oscilloscope

QC-1930 £83.75 + post & packing

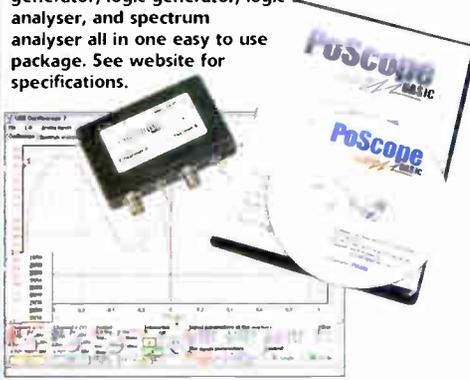Using Plug 'n Play USB technology and providing full optical isolation from the computer, this oscilloscope is easy to setup and use, as well as providing protection for the computer. The software is a fully featured chart recorder, function generator, logic generator, logic analyser, and spectrum analyser all in one easy to use package. See website for specifications.



Digital Megohmmeter

QM-1492 £28.00 + post & packing

Megohmmeters generate high voltage, low current signals for testing the breakdown strength of electrical insulation. Includes a rubber holster, test leads with alligator clips, 200M and 2000M Ohm ranges and simple, one button 'push to test' operation.



We stock an
extensive range of
Digital Multimeters!

Autoranging DMM

QM-1535 £8.50 + post & packing

An excellent, accurate meter that is Cat II rated. It features diode, frequency and capacitance test, duty cycle, continuity, relative measurement and includes battery, probes and holster.



Precision Japanese Made Carbon Steel Tools

125mm Precision Long Nose Pliers

TH-1885 £7.00 + post & packing

The pliers feature serrated jaws and a box joint to provide a precise action and strong grip. The coil spring ensures smooth, fatigue-free use. Insulated soft touch handles.



These quality tools are made in Japan from the same High Carbon Steel that is used to make professional chef's knives

150mm Precision Side Cutters

TH-1891 £8.00 + post & packing


These cutters are designed for sharp cutting in precision wiring. They have insulated soft-touch handles and a coil return spring for fatigue-free use.



Universal Speaker Protection and Muting Module Kit

KC-5450 £8.75 + post & packing

Protects your expensive speakers against damage in the event of catastrophic amplifier failure such as a shorted output transistor. In addition, the circuit also banishes those annoying thumps that occur when many amplifiers are switched on or off, especially when the volume is set to a high level. The design also incorporates an optional over temperature heat-sensor that will disconnect the speakers if the output stage gets too hot. Configurable for supply voltages between 22VDC-70VDC. Supplied with a silk screened PCB, relay and all electronic components.

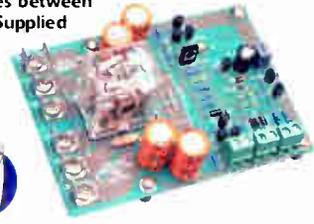

50MHz Frequency Meter MKII Kit

KC-5440 £20.50 + post & packing

This compact, low cost 50MHz Frequency Meter is invaluable for servicing and diagnostics. This upgraded version features an automatic indication of units (Hz, kHz, MHz or GHz) and prescaler. Kit includes PCB with overlay, enclosure, LCD and all electronic components.

- 8 digit reading (LCD)
- Prescaler switch
- 3 resolution modes
- Powered by 5 x AAA batteries or DC plugpack

Improved
model for
2007




Requires 5VDC wall adaptor (Maplin L66BQ £7.79)

Speedo Corrector MkII Kit

KC-5435 £10.25 + post & packing

When you modify your gearbox, diff ratio or change to a large circumference tyre, it may result in an inaccurate speedometer. This kit alters the speedometer signal up or down from 0% to 99% of the original signal. With this improved model, the input setup selection can be automatically selected and it also features an LED indicator to show when the input signal is being received. Kit supplied with PCB with overlay and all electronic components.

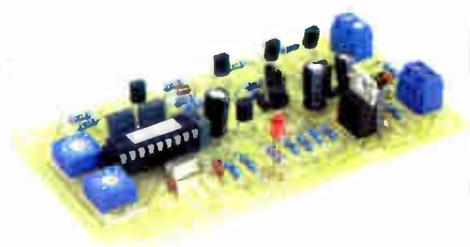

Recommended box UB5 use HB-6015 £0.83

POST AND PACKING CHARGES:

Order Value	Cost	Order Value	Cost
£20 - £49.99	£5	£200 - £499.99	£30
£50 - £99.99	£10	£500+	£40
£100 - £199.99	£20		

Max weight 12lb (5kg). Heavier parcels POA. Minimum order £10.

Note: Products are despatched from Australia, so local customs duty and taxes may apply.

How to order:

Phone: Call Australian Eastern Standard Time Mon-Fri on 0800 032 7241

Email: techstore@jaycarelectronics.co.uk

Post: PO BOX 6424, Silverwater NSW 1811. Australia Expect 10-14 days for air parcel delivery

Adaptive Turbo Timer Kit

KC-5451 £13.25 + post & packing

Ordinary turbo timers with a fixed time setting don't adapt to engine use and can turn off too early if the car has been driven hard, or run your engine overtime if the car has only been pottering about. This excellent kit overcomes the problem by constantly monitoring engine load and adjusting the timer run-time to suit the turbo's cooling need. Maximum cool down can be adjusted from a few seconds to 15 minutes and the timer will automatically work within this range. Indicators show when the timer is in operation, cooling period, and sensor level. Kit supplied with silk screened PCB and all electronic parts.



Value Now Only £10

Everyday Practical Electronics Feature Kits

Everyday Practical Electronics Magazine has been publishing a series of popular kits by the acclaimed Silicon Chip Magazine Australia. These projects are 'bullet proof' and already tested down under. All Jaycar kits are supplied with specified board components, quality fibreglass tinned PCBs and have clear English instructions. Watch this space for future featured kits.

V8 Sounding Doorbell

KC-5405 £25.95 + post & packing

Hear the rumble of a big V8 engine when visitors press the button on your doorbell. The kit also features a background noise that sounds like tappets and valves working away, for an even more realistic effect. There is a 'V' made from LEDs that light up in sync with the rumble, and the large 100mm speaker ensures that it sounds genuine. Supplied with silk screened and solder masked PCBs, silk screened and machined case, push button bell switch, speaker, wire, and all electronic components.




As published in this month's Everyday Practical Electronics Magazine!

RFID Security Module Receiver Kit

KC-S393 £28.95 + post & packing

Radio Frequency Identity (RFID) is a contact free method of controlling an event such as a door strike or alarm etc. An "RFID Tag" transmits a unique code when energised by the receiver's magnetic field. As long as a pre-programmed tag is recognised by the receiver, access is granted. This module provides normally open and normally closed relay contacts for flexibility. It works with all EM-4001 compliant RFID tags. Kit supplied with PCB, tag, and all electronic components.

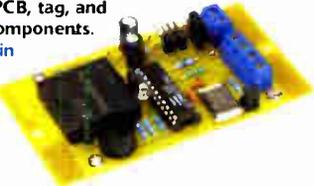As published in Everyday Practical Electronics Magazine August 2007



Automotive Courtesy Light Delay

KC-S392 £5.95 + post & packing

This kit provides a time delay in your vehicle's interior light, for you to buckle-up your seat belt and get organised before the light dims and fades out. It has a 'soft' fade-out after a set time has elapsed, and has universal wiring. Kit supplied with PCB with overlay, all electronic components and clear English instructions.

As published in Everyday Practical Electronics Magazine February 2007



Recommended box UBS HB-6015 £0.83

3V - 9V DC-to-DC Converter Kit

KC-S391 £4.95 + post & packing

This little converter allows you to use regular Ni-Cd or Ni-MH 1.2V cells, or alkaline 1.5V cells for 9V applications. Using low cost, high capacity rechargeable cells, this kit will pay for itself in no time. You can use any 1.2-1.5V cells you desire. Imagine the extra capacity you would have using two 9000mAh D cells in replacement of a low capacity 9V cell. Kit supplied with PCB, and all electronic components.

As published in Everyday Practical Electronics Magazine June 2007



Lead Acid Battery Zapper Kit

KC-5414 £11.75 + post & packing

This simple circuit is designed to produce bursts of high-energy pulses to help reverse the damaging effects of sulphation in wet lead acid cells. This is particularly useful when a battery has been sitting for a period of time without use. The effects are dependant of the battery's condition and type, but the results can be quite good indeed. Kit supplied with case, silkscreened lid, leads, inductors, and all electronic components, with clear English instructions.

As published in Everyday Practical Electronics Magazine July 2007



Luxeon Star LED Driver Kit

KC-S389 £9.75 + post & packing

Luxeon high power LEDs are some of the brightest LEDs available in the world. They offer up to 120 lumens per unit, and will last up to 100,000 hours! This kit allows you to power the fantastic 1W, 3W, and 5W Luxeon Star LEDs from 12VDC. Now you can take advantage of these fantastic LEDs in your car, boat, or caravan.

Kit supplied with PCB, and all electronic components.

As published in Everyday Practical Electronics Magazine April 2007




Jacob's Ladder High Voltage Display Kit

KC-5445 £11.75 + post & packing

With this kit and the purchase of a 12V ignition coil (available from auto stores and parts recyclers), create an awesome rising ladder of noisy sparks that emits the distinct smell of ozone. This improved circuit is suited to modern high power ignition coils and will deliver a spectacular visual display. Kit includes PCB, pre-cut wire/ladder and all electronic components.

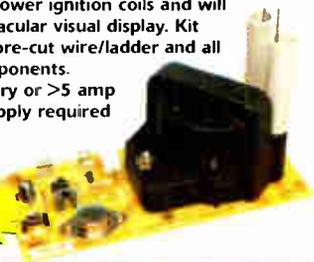12V car battery or >5 amp DC power supply required



Improved model for 2007

Three Stage FM Transmitter

KJ-8750 £6.50 + post & packing

This is a Three-Stage radio transmitter that is so stable you could use it as your personal radio station and broadcast all over your house. Great for experiments in audio transmission. Includes a mic, PCB with overlay and all other parts.

Requires 9V battery (not included)
Instructions included in kit



10A 12VDC Motor Speed Controller

KC-S225 £7.75 + post & packing

Use this kit for controlling 12V DC motors in cars such as fuel injection pumps, water/air intercoolers and water injection on performance cars. You can also use it for headlight dimming and for running 12VDC motors in 24V vehicles. The kit will control loads up to 10 amps, although the addition of an extra MOSFET transistor will double that capacity to an amazing 20 amps.

Kit includes PCB plus all electronic components to build the 10A version.



Log on to www.jaycarelectronics.co.uk/catalogue for your FREE catalogue!

0800 032 7241

(Monday - Friday 09.00 to 17.30 GMT + 10 hours only)
For those who want to write: 100 Silverwater Rd
Silverwater NSW 2128 Sydney AUSTRALIA

Minimum order now only £10

430+ page Catalogue

All prices in £

Jaycar Electronics

www.jaycarelectronics.co.uk

World Radio History

PIC N' MIX

MIKE HIBBETT

Our periodic column for your PIC programming enlightenment

More on 1-wire protocol – and a response to the Brain Teaser challenge!

WE continue on from last month's article on the 1-wire protocol by developing some software routines that can be used to communicate with 1-wire devices. These routines will be written in assembler since this is the language that most *EPE* readers seem to be familiar with, and can be used with applications written either in assembler or a high level language like 'C'.

We will be using MPLAB as the development environment and prototyping the code on the PicKit2 hardware platform, since this ties in nicely with recent tutorial articles. Although the code is targeted to a PIC16 family part (the PIC16F917) it can be easily 'ported' to other devices in the Microchip range.

Portable code

Presenting general purpose re-useable assembly language routines is always a difficult task. The author's favorite PIC devices are in the PIC18F range which have additional instructions that can make the code more efficient, but consequently much harder to translate back to a simpler processor family, such as the PIC10F or PIC16F. By choosing a mid-range device, like the PIC16F917, and keeping the code as non-processor specific as possible makes (hopefully!) the porting exercise to other devices as simple as possible.

Do bear in mind that incorporating assembly routines into your code is not the only way to build a 1-wire application; as we mentioned last month, some software vendors provide routines implemented as part of a BASIC language programming environment. You would have to pay for those of course, but if you want to understand how to write the routines yourself (or understand how they were written), there is no real substitute for going right back to basics and walking through the development of the routines. Hopefully, you will gather some understanding of the low level software this month, and will gain the confidence to incorporate the routines in to your own future programs, or even better, modify them for your own special needs.

Protocol detail

Before we start writing any code, let's take a look at the protocol in more detail. The application note 132 from Dallas/Maxim (available on their website, see reference 1) details this, but in a quite complex manner. We have simplified the timing diagrams to the bare essentials, as shown in Fig.1. It's still complicated, so let's go through them in detail.

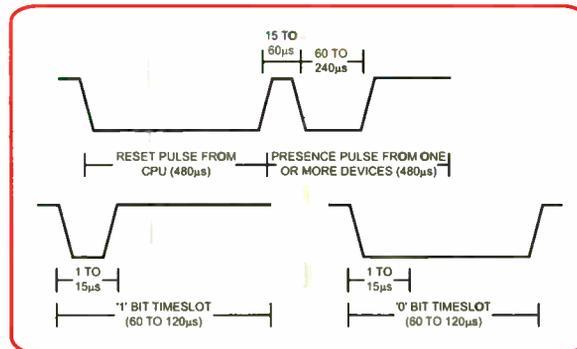


Fig.1. Basics timings

The three diagrams in Fig.1 show how the three main activities on the 1-wire data wire are performed. Each diagram shows how the voltage on the data wire varies over time, starting from the left and moving to the right. When the line on the diagram is 'high', it indicates the data wire is at the high voltage: 5V for example. When the line is 'low', it indicates the wire is being driven to zero volts.

The sloping line indicates when the signal is transitioning from one level to another. This transition is normally shown with an exaggerated slope, and in most 1-wire systems the transition can take a few microseconds. Note that the default, idle state of the line is floating, driven 'high' by the bus pull-up resistor.

The first activity used when one wishes to send messages on the bus is the Reset/Presence cycle, shown at the top of Fig.1. This is used at the beginning of any communication with a 1-wire device, as it causes all devices on the bus to reset themselves back to a known default condition.

The procedure is as follows:

1. The CPU drives the wire low for 480µs (this is the 'reset' signal)
2. The CPU then turns its I/O pin to an input, allowing the signal to be pulled high
3. After 15µs, the CPU monitors its input I/O pin to look for a device on the bus driving the wire low (this is the 'presence' signal)
4. 15µs after detecting the reset signal, any device connected to the bus will drive the wire low for at least 60µs to indicate its presence

All devices connected to the bus will drive the signal low, so detecting that the wire has gone low only indicates that there is at least one device on the bus – there could, of course, be hundreds. How you communicate with a specific device is determined by the high level commands mentioned last month.

Once the CPU has finished waiting for the devices to indicate their presence (after a period of about 480µs), the CPU can send out one of the 1-wire

messages on the bus. As with any serial communication protocol, messages are sent by 'wagging' a data line up and down, with a 'high' level on the data wire indicating a '1' bit, and a 'low' level on the wire indicating a '0' bit.

With only a single wire available to send the data, some method is required to allow the receiver to 'know' when to look at the data wire for each data bit sent by the transmitter. This is done by sending a short 'low' pulse on the data line prior to sending the actual data bit.

The bottom two diagrams in Fig.1 show how a '1' and a '0' data bit will be sent. By using a short 'trigger' pulse at the start of each data bit, the two devices – the main CPU and the remote 1-wire device – do not need to run tightly aligned clocks to keep in sync.

For the CPU to receive data from a 1-wire device, it simply leaves the I/O pin connected to the data wire as an input and 'listens' for the voltage level to drop to zero volts. The 1-wire protocol describes when a device should transmit and when it should listen, and as all devices connected to the bus will obey the protocol, communication is possible even though there may be hundreds of devices on a single wire.

Bottom up approach

Writing software for interfaces such as this typically follows a 'bottom up' approach – you start off by thinking about how you will control the voltages on the wire, write and test those, then think about how you will use those routines to generate the correct timing (to correspond with the timing diagrams such as in Fig.1) to give data transfer between devices. Once those routines are written, you can then forget about the hardware issues, put your multi-meter away and concentrate on writing

software to use the 1-wire protocol commands and messages.

In engineering circles, the low level routines used to provide the transfer of messages over the hardware are called *drivers*. These typically consist of subroutines to initialise the interface, read messages and write messages, and tend to have names like `initHw`, `readByte` and `writeByte`. We will present some suitable driver code in this article, with an example of how to use it.

Developing code to talk to external devices requires the use of a hardware emulator or real hardware – you cannot use a PC simulator such as the one available in the MPLAB IDE. Emulators (complex pieces of hardware that are essentially versions of the PIC processor, with access to some of the internal signals) are expensive, but for an interface like this we can build a very simple circuit on which to test our code.

Of course, if you have a hardware debugger such as the PicKit2 or ICD then testing is even easier. The test circuit shown in Fig.2 uses the PIC16F917, to match the processor on the PicKit2, but you should be able to use any PIC processor with no or minimal changes.

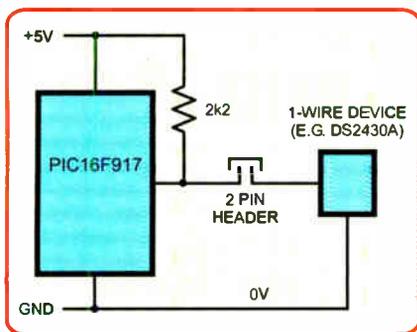


Fig.2. Debugging test circuit

The circuit does not show an oscillator – this is because in our example code we will use the internal, calibrated RC oscillator that runs at 8MHz. It makes for a really simple, compact circuit! You can, of course, use an external oscillator if you wish, just change the CONFIG register settings for the clock source appropriately.

With such a simple interface – it can't get any simpler – the choice of which I/O pin to use is easy. Any. We wired a Dallas DS2430A 256-bit EEPROM to the prototyping area on the PicKit2 demo board and used the debugger to assist with the code development, but as this article is about 1-wire interfaces we will ignore the debugging activities.

Software

Once again, before even thinking about writing your code, think about how you are going to organise it into various source files. Obviously, you will want a file to hold the actual 1-wire 'driver' routines, which we will call `1wire.asm`. Then there will be a different file that will hold the high level program, which calls the driver

and does some useful work. We will call that `main.asm`.

Thinking about the design a little further, there will obviously be a need for some routine or routines to provide very precise delays. These could go in `1wire.asm`, but they are going to be very general purpose, and quite likely to be useful in another project. We will place any delay routines in a file `delays.asm`.

At this stage, there is one further improvement we could make: write higher level routines for accessing particular devices (such as `readeprom` and `writeeprom` in the case of the DS2430A) and store these in a file named after that particular device (`ds2430a.asm` for example). It's a good idea, but for clarity we will skip that step. So we will create three files:

`main.asm`
`delays.asm`
`1wire.asm`

Delay timing

Referring back to Fig.1, it's clear that we need several delay times: 15 μ s, 60 μ s, 240 μ s and 480 μ s. While we could create routines to implement exactly those timing delays, it's much more flexible to produce a general purpose routine that can satisfy all the options. We do that by passing in the time delay required in the W register.

Performing accurate delays in assembly is quite easy, if you know how fast your processor clock is running, and you don't mind not being able to do other things (like service interrupts) while the delay is executing. We have created a simple `delay5us` routine that will delay for the number of multiples of 5 μ s specified in the W register. The routine is a little inaccurate at low delay times (it adds about 2.5 μ s additional time during the call) but will be perfectly suited to our needs.

The routine, along with all the other code, can be found on the EPE website download page (access via www.epemag.co.uk) in the *Pic N' Mix* folder.

Sending data

Now we can time the delays for toggling the I/O pin up and down, it's time to look at the meat of the problem – sending data bits on the wire, as defined in `1-wire.asm`. We start with the initialisation of the hardware.

The natural state of the 1-wire data signal is floating, pulled high by the pullup resistor that also serves to power the remote device(s). To achieve this, we set our chosen I/O pin, RB1, to an input. Nothing else is required.

As we mentioned before, there are four main activities required in our low level software: sending a reset signal, writing a '1' bit, writing a '0' bit, and reading the state of the bus. We will deal with these one at a time.

Sending a reset signal to the remote devices is really a three-staged procedure – the CPU drives the wire low for 480 μ s, waits for 15 μ s and then looks for a 'low' level on the wire for up to 240 μ s, indicating the presence of a device. The entire detection time takes 480 μ s, presumably to

allow the remote devices time to finish their own startup activities. The code for this can be found in the routine `reset1wire`.

Writing '1' and '0' data bits to the bus is very straight forward; pull the line low for 5 μ s, then either keep the line low for a '0' bit or return the port pin to an input to allow the wire to rise high, signaling a '1' bit. After a delay of 55 μ s, the data line must be returned to the high level by setting the port pin to an input. These routines are called `writelbit` and `write0bit`.

Reading data from the bus (or, more correctly, from a device on the bus) is always initiated by the host microcontroller. To read a data bit you drive the bus low and then immediately release it. Then 15 μ s later, read the level on the wire to determine the bit value. Repeat for however many data bits need to be read. This routine has been called `read1wire`, and returns the value of the data bit in the W register.

These three routines, along with `reset1wire` and `init1wireHw`, completely define the code required to connect the software we write to the physical hardware. From now on, you can forget about what pin your devices are connected to; all higher level software will rely on these five routines alone. This is what software engineers call *abstraction*, hiding the complexity of the lower levels of software. It's an essential technique when you are working on large, complex programs.

Finally

That about wraps it up for 1-wire interfacing; performing the actual read and write functionality is a simple case of calling the write and read functions in an order that matches the commands mentioned last month. The remaining routines in `1-wire.asm` implement the high level commands, such as reading and writing memory. The file `main.asm` contains some example calls to show how they all fit together.

Last, but by no means least, we must specify the value of the CONFIG register. Specifically for our example circuit, we must select the INTOSC option to enable the 8MHz internal oscillator. We do that in the main application file `main.asm`.

The example source code available on the EPE website's download page contains all the routines necessary to experiment with this interesting and low cost network interface.

Brain teaser

There were some interesting responses to August's 'brain teaser' on alternative methods for generating random numbers. One in particular caught our eye, from **Godfrey Manning** in the UK:

Here's a theoretical suggestion for hardware random-number generation, although I haven't tried it out in practice. An electro-mechanical buzzer generates electrical noise and a relay can be wired as a buzzer. The noise is then tapped off by inductive coupling and capacitively coupled to the next stage. Next come two possible means of signal processing to produce digital pulses, then two ideas as to what to do with them.

First possibility: suitable Zener diodes limit the peaks, but it's no good having one to each rail as one will be like a normal forward-biased diode, depending on the polarity of the pulse. So the appropriate Zener diode comes into effect by having a Schottky diode (fast, but low-voltage-drop) in series with it, only allowing unidirectional conduction.

The signal, thus limited, is applied to the mid-point of a high-impedance potential divider (giving half-supply when quiescent), also one input of an op amp comparator. The other op amp input is fixed at half-supply. The op amp output therefore bounces from one rail to the other, depending on the polarity of the incoming voltage spike.

Passed through a Schmitt-triggered gate this produces a random pulse train.

Alternative processing: a Zener diode limits positive peaks and a Schottky diode limits negative ones, which is then passed straight into a Schmitt-triggered gate.

First, a means of using this train of random bits: read the digital value n times, at each of n 'ticks' of a regular clock pulse. These n readings then become the consecutive bits of an n -wide random number (this technique is like a UART serial-to-parallel conversion). So n would be eight for a byte value, sixteen for a word.

Alternative application: a regular clock pulse is applied to the D (Data) input of a D-type flip-flop. Then the random bit stream clocks the flip-flop. At any

given instant, the probability of a 0 or 1 entering the flip-flop is equal, but the random effect is that the moment of clocking is chosen according to the noise pulse train. Presumably, the flip-flop state is determined on the rising edge of the random clock. On the descending edge of the random clock, the Q output of the flip-flop must be captured and becomes the next bit to contribute to the n -wide final number.

The buzzer is an electromagnetic compatibility nightmare and must be in a screened enclosure! Power is taken into the screened box by feed-through capacitors with series inductors hard up against the outside terminal.

Certainly an unusual suggestion, although potentially limited due to mechanical wear and tear over time if the random data is being accessed continuously. Commercial random number generator designs typically use the noise generated by electrons moving through a resistor or diode, amplified and then fed through a circuit not dissimilar to that which Godfrey describes above.

Thanks to everyone for their random number suggestions.

New brain teaser

This month's teaser is an exercise in studying the Microchip website:

One of the features that the PIC10, 12, 16 and 18 families of processors share in com-

mon is that the rate at which instructions are executed (the instruction cycle time) is fixed at one instruction every four clock cycles. This is why it is so easy to produce accurate delay time routines in assembly languages.

Assuming your design had to operate at 5V, if you wanted to choose a processor in any of the above families that had the fastest rate of instruction execution, which one (or ones) would you choose? Would the voltage at which you ran the processor have an effect on your answer?

An honorary mention in a later article for the first correct answer. Submissions by email to mike.hibbett@gmail.com or in writing or by email to *EPE*.

If there is a subject that you would like to see covered in a future *Pic 'N Mix* article feel free to contact the author, either directly or via *EPE*.

References

1. Application Note 132. <http://pdf-serv.maxim-ic.com/en/an/app132.pdf>

PLEASE TAKE NOTE

V2 PC Scope (August '07)

Page 15, Parts List. The type number for IC7 and IC9 should read **LMC6482**. The circuit diagram Fig.2 is correct.

Electronics Engineers - Join A Winning Team! UK and Czech Republic

We are looking for Engineers for the United Kingdom & Czech Republic.

The Lektronix Group of Companies are the worlds leading provider of Industrial Automation repairs with an enviable reputation for the best in technical excellence and customer service.

Due to the huge demand for our services we need to employ additional engineers at our three UK workshops (West Midlands, South Wales and Northern Ireland) to keep pace with the work we are receiving.

Also, due to future expansion throughout Europe we are looking for English speaking engineers to train and work in the UK with eventual relocation to our workshop in Brno, Czech Republic.

We are looking for Electronic Repair Engineers, Electronic Repair Technicians and Electronic Component Level Repair Engineers.

Do you have an interest in electronics?
Have you any experience in the field of practical electronics?
Have you experience in Radio/Television/Home Electronics?
Does your hobby/interest include electronics?
Are you willing to learn new tricks - electronic engineering?
Do you want work in an exciting and challenging environment?
Do you have any experience with Machine Tool Systems - PLC's - Servo Drives - Servo Motors - Monitors-VDU's - AC Drives - DC Drives - Temperature Control - Digital Electronics - Analogue Electronics?

We offer a competitive salary and all the other benefits normal with a go ahead company.

Lektronix




Please Contact: Mr Brian Stewart
Lektronix Ltd, Unit C1, Anchor Brook Ind Park,
Wharf Approach, Aldridge, West Midlands,
WS9 8EQ, United Kingdom.

Telephone +44 (0)1922 455555 for an application form or apply on line at www.lektronix.net



Ingenuity Unlimited

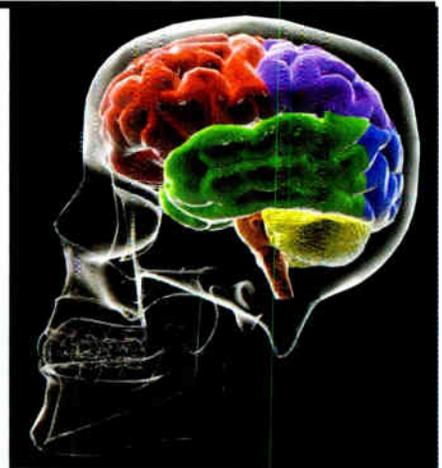

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas *must be the reader's own work* and **must not have been published or submitted for publication elsewhere**. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and include a full circuit diagram showing all component values. **Please draw all circuit schematics as clearly as possible**. Send your circuit ideas to: *Ingenuity Unlimited*, Wimborne Publishing Ltd., Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU. (We do not accept submissions for IU via email.) Your ideas could earn you some cash and a prize!

WIN A PICO PC-BASED OSCILLOSCOPE WORTH £799

- 200MHz Analogue Bandwidth Dual Channel Storage Oscilloscope
- Spectrum Analyser
- Multimeter
- Frequency Meter
- USB Interface.

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC-based oscilloscope could be yours.

Every 12 months, Pico Technology will be awarding a PicoScope 3206 digital storage oscilloscope for the best IU submission. In addition a PicoScope 2105 Handheld 'Scope worth £199 will be presented to the runner up.

Monitoring PSU output current and voltage – *Minimising switch resistance*

When monitoring the output of a bench PSU it is convenient to use a single panel meter switched to read voltage or current. I used the simple circuit at Fig.1. Switch S1 selects the shunt R1 for current measurement and S2 selects the series resistance R2 for voltage.

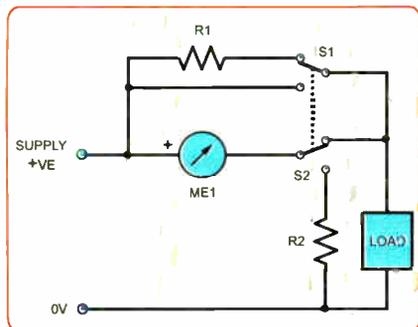


Fig.1. Basic circuit for a power supply output current and voltage monitor

But it was found that the current readings were inconsistent. The penny finally dropped when I realised that as resistor R1 has a low value, the 'on' resistance of switch S1 could be significant as they are in series. Measurement using a low ohms meter showed that the 'on' resistance of S1 varied between 10mΩ and 30mΩ, depending on how frequently it was operated.

A typical 100 microamp moving coil meter, scaled to read 1A, requires a shunt of

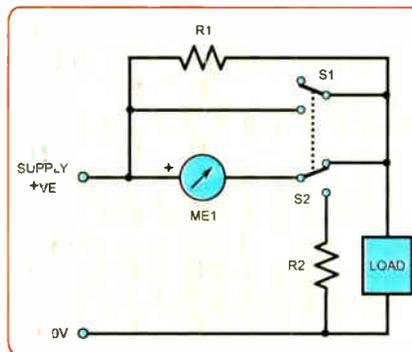


Fig.2. Final simple add-on circuit for monitoring the output current and voltage of a bench power supply. Note switch S1 is no longer in series with shunt resistor R1

about 150mΩ. If S1 adds 30mΩ or so to the shunt, this causes a positive reading error of about 20%. The effect is linear, so if S1 adds only 15mΩ the error will be 10%.

Modifying the circuit to Fig.2 solved the problem as S1 is no longer in series with the shunt R1. Switch S2's 'on' resistance has no significant effect as it is much less than either the meter coil or R2.

Incidentally, to find the shunt and series resistances R1 and R2 quickly, I use the formulas:

$$\begin{matrix} \text{Voltmeter} & \text{Ammeter} \\ R2 = Rm(n - 1) & R1 = Rm/(n - 1) \end{matrix}$$

Where: Rm = meter coil resistance in ohms; n = voltage and current multiplication factors.

Stephen Stopford,
London

INGENUITY UNLIMITED BE INTERACTIVE

IU is your forum where you can offer other readers the benefit of your Ingenuity. Share those ideas, earn some cash and possibly a prize.





This unique project demonstrates what can be achieved with a relatively simple circuit and some clever programming. With only a microcontroller and a handful of components, it functions as a wide-ranging, multi-frequency inductance and Q-factor meter.

Inductance & Q-Factor Meter

Pt.1: By LEONID LERNER

INDUCTORS ARE UBIQUITOUS, being indispensable in circuits such as loudspeaker crossover networks, switchmode power supplies and RF amplifiers. Unlike other components, inductors are often hand-made, particularly when prototyping or assembling a do-it-yourself project. At a minimum, this suggests the need for a meter to check inductance values prior to use in circuit.

But that is not the end of the story. Of all the passive components, inductors typically show the greatest deviation from ideal behaviour. This is due primarily to coil resistance and the hysteresis of the core material.

The picture is further complicated by the fact that the losses are frequency dependent. The skin effect in copper wire and the complicated frequency characteristics of magnetic materials both come into play and are apparent even at audio frequencies.

To provide a more informative picture of inductor performance then, this meter allows you to measure the Q factor of a prospective resonant circuit at the operating frequency. If you've never heard of Q factor, then read on . . .

Measuring L and Q

There are several basic methods of measuring the inductance (L) and

the Q-factor of a tuned circuit, the most common being 'temporal' (time domain) and 'spectral' (frequency domain). The spectral method was described in the *Poor Man's Q-Meter* article in the June 2007 issue of *EPE*. It consists of applying a sinusoidal voltage of varying frequency to a resonant circuit and measuring the circuit response as a function of applied frequency.

The response of such a circuit will generally follow that shown in Fig.1, with a peak at a given frequency, dropping away on both sides in a bell-shaped curve. Circuit theory demonstrates that the peak angular frequency squared is just the inverse

Specifications

Range

Inductance: 200nH - 10mH
Q-Factor: 1-120 (approx.)

Power Supply

9V DC 300mA plugpack

Features

(1) Internal or external tank capacitance facility for accurate Q measurements

(2) Measurement frequency autoranging up to 20MHz

of the inductance (L) times the capacitance (C). So if we know C, then the inductance can be found.

On the other hand, the Q factor is the ratio of the peak frequency to the width of the bell-shaped curve at half-power. This is how the Q is manifested experimentally. Theoretically, it is defined as the ratio of the circuit reactance to its resistance at resonance.

It should be emphasised that the preceding definitions are only approximations but give excellent results provided Q is greater than 2 or so. For heavily damped resonant circuits, the relationships between waveform and circuit parameters are more complicated. However, we are not interested in such circuits here.

Temporal method

The temporal method of inductance measurement is adopted in this design. It is based on the fact that when a rectangular pulse is applied to a resonant LCR circuit, such as that shown in Fig.2, decaying oscillations give rise to a ringing waveform. These oscillations continue until all energy is dissipated in the circuit resistance, with their frequency the same as that at which the peak occurred in the spectral response. The Q factor in the temporal response manifests itself as the ratio of the oscillation coefficient (the angular frequency) to twice the decay coefficient.

We can use this information to measure the L and Q of a parallel-resonant circuit with a squarewave generator and a scope. The generator is connected to the tuned circuit via a large resistor, so as not to appreciably load the circuit and thereby alter the Q. This resistance should be larger than the series resistance multiplied by Q².

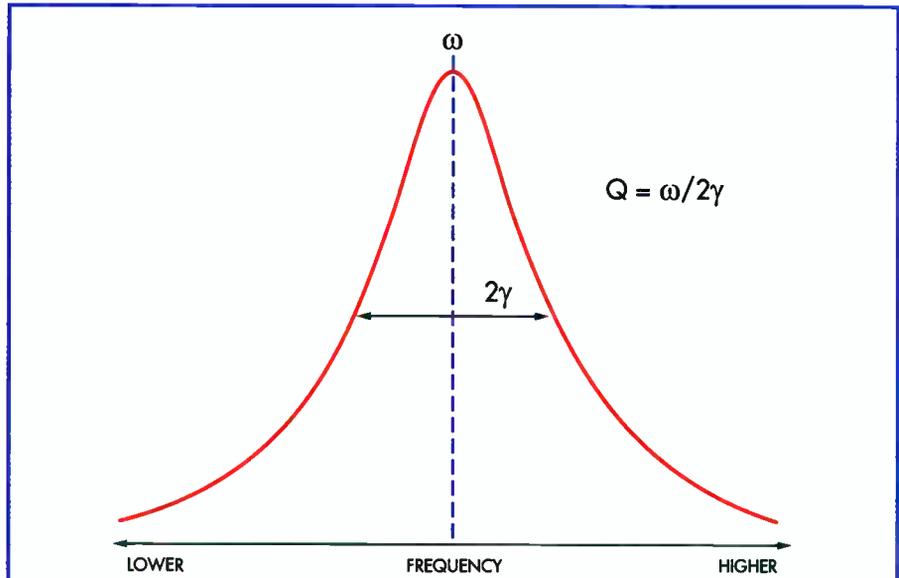


Fig.1: the spectral response of a resonant circuit reveals a peak at a given frequency, dropping away on both sides in a bell-shaped curve. The Q factor is manifest as the ratio of the peak frequency to the width of the bell-shaped curve at half-power.

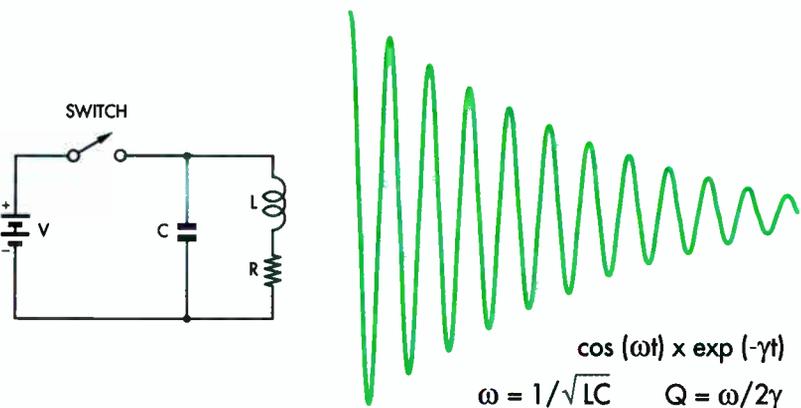


Fig.2: the temporal method used in this design relies on decaying oscillations after a rectangular pulse is applied to the resonant circuit. The Q factor manifests as the ratio of the oscillation coefficient (the angular frequency) to twice the decay coefficient.

A typical oscilloscope trace of a ringing waveform set up in a resonant circuit by such a generator is shown in Fig.3. The period is the time required for the signal to undergo N oscillations, divided by N. The Q factor is the number of oscillations required for the peak amplitude (starting at some convenient peak) to drop to about 0.043 of its initial value. In practice, one can get better accuracy by counting the number of oscillations for the amplitude to drop to one fifth, and multiplying this number by two.

The above procedure is the basis for this project, with an AT90S2313

microcontroller performing the multiple functions of generator, scope and calculator. A liquid crystal display (LCD) and keypad are also included to provide a convenient means of setting basic parameters and observing the measurement results.

Fourier transformed

It is interesting that one can get from the ringing waveform of the temporal response to the bell-shaped curve of the spectral response by a technique called the 'Fourier Transform', or its numerically useful form, the Fast Fourier Transform (FFT). This means one

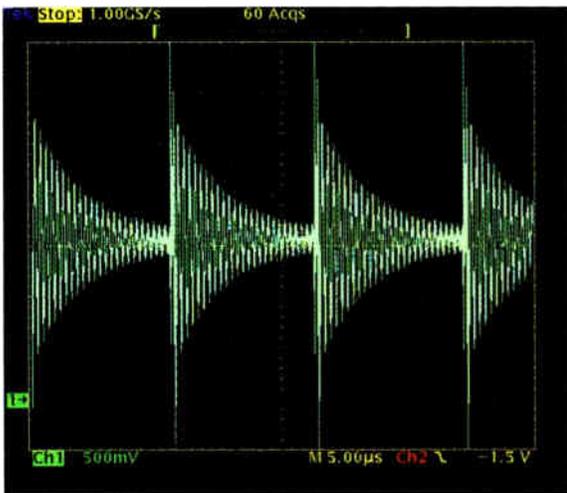


Fig.3: this scope shot shows the response of an LCR circuit to an applied pulse. Decaying oscillations give rise to a ringing waveform, which continues until all energy supplied by the pulse is dissipated in the circuit resistance. The frequency of oscillation is the same as would occur at the peak in the spectral response.

does not actually have to make spectral measurements in order to obtain the spectral response.

This is useful because it is much easier to extract the parameters of interest from the spectral plot than from the temporal plot. The former involves just finding a peak in the data, while the latter requires establishing and then counting the zero-crossings. Another advantage in using FFTs is that the effects of the inevitable analogue noise, as well as digitising distortions, are minimised, as they are separated from the signal in the Fourier analysis.

Depending on circuit Q, our meter can measure inductances as low as 200nH and as high as 10mH. The range

of Q measured varies from about 1 to 120. In addition, the meter indicates when both L and Q values are out of bounds (indicated by the letter 'E' on the display).

Circuit basics

Before looking at the circuit operation in some detail, it is instructive to consider the block diagram in Fig.4. The central component of the system is an Atmel AT90S2313 microcontroller. This particular micro was chosen because it is relatively cheap yet includes all of the features needed to minimise the total component count.

The micro controls a 'pulsar', which is used to excite a tank circuit. The


tank circuit consists of the inductor under test and a paralleled capacitor. The capacitor can be selected by the user and connected externally. Alternatively, one of three internal capacitor values can be chosen from the keypad.

To minimise loading and compensate for circuit losses, the waveform from the tank circuit is buffered and amplified by an op amp. Following this, it is fed into a sample-and-hold (S/H) circuit and then into an analogue-to-digital converter (ADC).


The ADC functions are contained mostly within the micro so they do not appear on the block diagram. A ramp converter was chosen for its simplicity and low cost. For readers not already familiar with this type of converter, its operation can be summarised as follows:

A conversion cycle begins with the charging of a capacitor from a constant-current source. As the capacitor begins to charge, a binary counter starts counting from zero. The increas-

Fig.5 (right): complete circuit diagram (minus power supply) for the meter. A high-speed sample and hold circuit made up of a simple counter (IC2), analogue switch (IC3) and some clever programming allows the meter to measure resonant circuits at frequencies up to 20MHz.

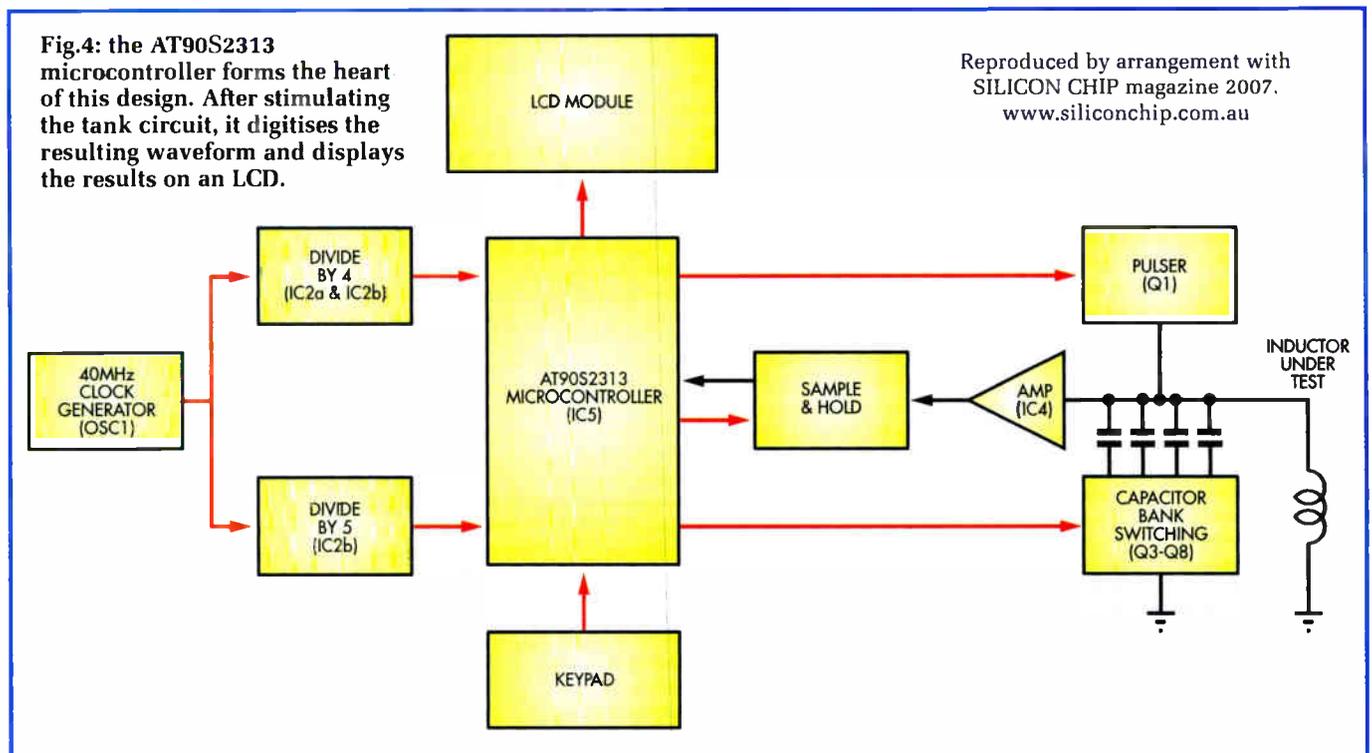

Constructional Project

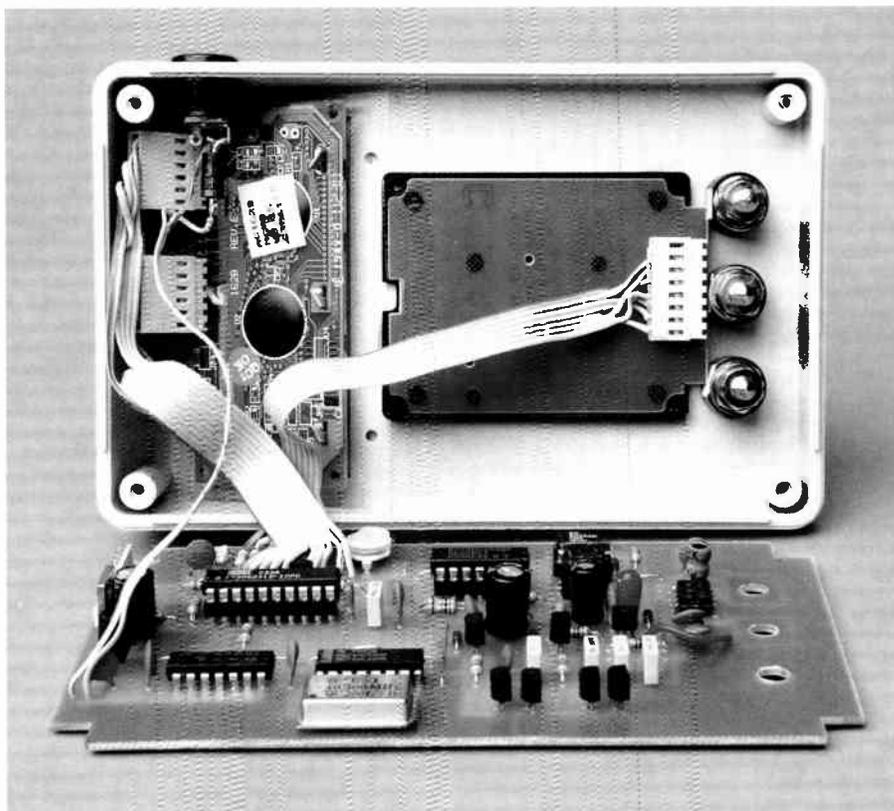

This is the view inside the completed prototype. The full construction details will be published in Pt.2, next month.

ing capacitor voltage (the 'ramp') is continually compared with the input voltage. When the two voltages are equal, the comparator stops the counter, whose count is then proportional to the input voltage.

Although simple, ramp converters have a comparatively long conversion time and a somewhat reduced precision. In this application, precision is not of particular concern since it is the time characteristics of the signal that are of paramount importance.

However, conversion time *is* important. Inductors in the order of a few hundred nanohenries require measurement frequencies of tens of megahertz to achieve a sufficiently large Q and so an accurate measurement. This is clearly well beyond the capabilities of our simple ramp converter. Even if the design was to use a dedicated high-speed (20MHz or better) ADC, the micro would not be fast enough to store the results of each conversion.

All this overlooks the fact that the ringing waveform is repetitive. It can, therefore, be digitised at low speed by repeatedly stimulating the tank circuit and measuring each waveform at progressively larger offsets from time zero.

To achieve the desired 20MHz sampling rate, measurements must be made at 25ns intervals. This is achieved with the aid of a programmable sample-and-hold block which holds each measurement long enough for the low-speed ramp converter to complete its task.

Detailed operation

The circuit diagram for the majority of the L/Q Meter appears in Fig.5. Let's start at the test terminals, where the inductor under test and capacitor(s) are connected to form the tank circuit.

Transistor Q1 is used to pulse the tank circuit. It is driven via a 100 Ω current limiting resistor from output port bit PD5 (IC5, pin 9). A second 100 Ω resistor in the emitter (E) circuit limits peak pulse current to about 50mA. Diode D2 provides isolation between the tank circuit and the driver so as not to dampen the oscillations.

Installing a shorting link between the 'A' and 'B' terminals links the inductor under test with an internal set of capacitors. A 1nF capacitor across the terminals fixes the minimum capacitance. Two other capacitor values (10nF and 100nF) can be switched into the circuit under program control

using port bits PD3 and PD4 (IC5, pins 7 and 8).

Signals from these pins are fed through isolating diodes D6 and D7 to current amplifiers Q3 and Q6 and from there to switching transistors Q4/Q5 and Q7/Q8. Two medium-current transistors are used in parallel to reduce the dynamic collector-emitter resistance and hence its influence on the circuit Q . Even so, the transistors contribute about 0.5 Ω series resistance and the influence of this on the Q should be borne in mind.

Relays could have been used to reduce the series resistance further. However, these are slow, prone to failure and not really in accord with our solid-state approach. In addition, the use of high-current audio transistors is precluded by their high output capacitance. If there is some concern about the contribution of the internal circuitry to the Q factor then you can leave out the link and use an external tank capacitor.

Fast op amp needed


So as not to load the tank circuit, the output signal is buffered by an op amp (IC4), which is connected in a non-inverting configuration for high input impedance. An AD8055 op amp was chosen for the task as it has a high gain-bandwidth product and high slew rate and is stable when driving capacitive loads at low gains. Lower spec op amps are not suitable here, as they would severely limit the frequency range of the meter.

Ideally, the output from the op amp should swing between about 0 to 4V maximum, which is the maximum input range of the comparator. To this end, op amp gain is set to about 1.8 by the 1.2k Ω and 1k Ω resistors, counteracting losses in the circuit.

To maximise dynamic range and minimise the influence of noise and digitisation errors, the AD8055 and analogue switch (IC3) are powered from $\pm 5V$ supplies. Furthermore, the inverting input of the op amp is biased at $-1.8V$, meaning that the output (pin 6) will swing either side of $+1.8V$. This scheme makes the most of available headroom, which is limited to about 3.7V. Note that the micro is programmed to reject the initial part of the ringing should saturation occur.

Hold it a moment

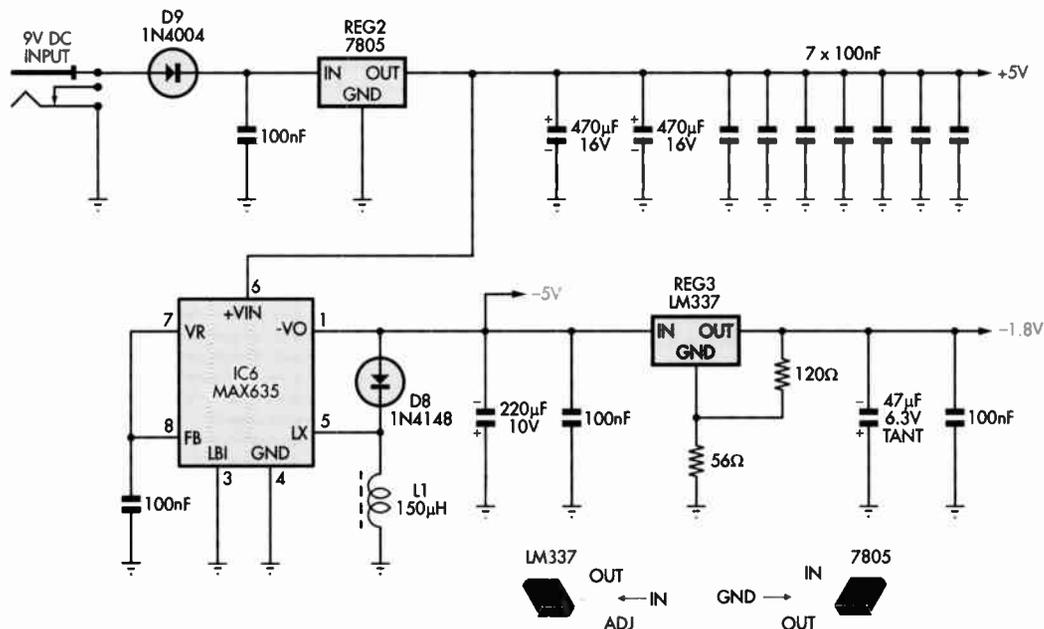The output of the op amp drives a high-speed sample-and-hold circuit



DIGITAL L/Q METER POWER SUPPLY

Fig.6: the power supply section. A conventional +5V regulator (REG2) powers the entire circuit, while a switchmode inverter (IC6) generates -5V for some of the analogue circuitry. An LM337 negative regulator (REG3) is used only to generate a bias voltage for op amp IC4.

ahead of the comparator (ADC) input on pin 12 of the microcontroller. The S/H circuit consists primarily of an analogue switch (IC3c) and a 680pF storage capacitor.

As mentioned earlier, the micro digitises a measurement by repetitively sampling successive waveforms. Samples are taken at incremental offsets from time zero to build a complete and accurate digitisation of the ringing waveform.

Sampling begins by closing the analogue switch (IC3c) at time zero. After the programmed delay, the switch is opened, leaving the 680pF storage capacitor charged to the waveform voltage at that instant. Our slow ADC then has sufficient time to digitise the voltage, after which it is stored and the cycle repeats. This is represented graphically in the scope shots of Figs.7a and 7d.

Unfortunately, the 100ns cycle time of the micro means that it is too slow to directly control the analogue switch (IC3c). With a maximum 20MHz sampling rate, we need 25ns resolution. This is provided by external logic, consisting of a 40MHz oscillator module (OSC1), timing circuits (IC1 and IC2) and a level converter (Q2, D1, IC3d, etc), all under control of the Atmel microcontroller (IC5).

Level conversion

Let's look at the level converter circuit first. It consists mainly of transistor Q2, diode D1 and analogue switch IC3d. The sole purpose of this circuit is to convert the 0 to 5V levels from the NAND gate output (IC1a) to $\pm 5V$ levels to control the S/H switch (IC3c).

Since the minimum sample time is only 25ns, Q2 is required to switch in nanoseconds and have a slew rate in the order of 1000V/ μ s. This is achieved with the use of a high beta transistor and 100 Ω resistors in the base-emitter circuits, as well as the germanium diode (D1) between the collector and base. The results can be seen in the oscilloscope trace of Fig.7a.

Q2 inverts the control signal from IC1a, so a spare analogue switch (IC3d) is used to invert it again before it is fed to the control pin of the S/H switch.

Timing secrets

The two divide-by-2 sections of a dual decade counter (IC2) are cascaded to divide the 40MHz clock down to 10MHz for the micro's clock input on pin 5. The divide-by-5 section of the second half of the decade counter (IC2b) is used to derive two out-of-phase 8MHz timing signals.

Output 3 (bit 2) of the counter (pin 9) is used by the micro as an 8MHz synchronisation signal. It is high during only one state of the five states of the counter, allowing precise determination of the instantaneous state of the 8MHz clock with respect to the 10MHz clock.

Output 2 (bit 1) of the counter is Nanded with port bit PD0 (pin 2) of the micro via IC1a to generate the 'hold' signal for the S/H circuit. As the micro's port outputs are synchronised to its 10MHz clock, the difference between the rising edges of the two signals on IC1a's inputs allows generation of 0ns, 25ns, 50ns and 75ns delays under program control. This can be seen in the simplified timing diagram of Fig.8.

Output 2 is also Nanded with port bit PD1 via IC1d so that the micro can freeze the counter. Note that Output 2 is used here instead of Output 1 as it goes high earlier in the counting cycle, thus allowing for the propagation delay through gates IC1c-IC1d and IC2b.

Digitising

The micro program performs analogue-to-digital conversions by using the AT90S2313's internal comparator

How The Ringing Waveform Is Digitised

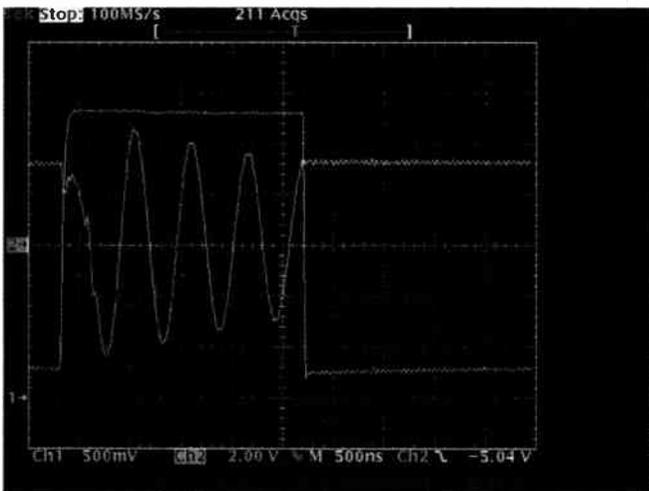


Fig.7a: the following series of scope shots were captured at progressively longer timebase settings and provide an insight into how the ringing waveform is digitised. Here, the green trace shows the waveform at the S/H output (pin 9 of IC3c), while the red trace shows the control signal on pin 6. Note the very fast transitions of the latter, which for the all-important trailing edge (hold) constitutes 7ns, or 1400V/ μ s. The waveform is oscillating at a 1.8MHz rate and its instantaneous value is captured when the control signal goes low. Also, note that the voltage at the S/H output doesn't decay noticeably during the hold period (red trace low), when the analogue-to-digital conversion takes place.

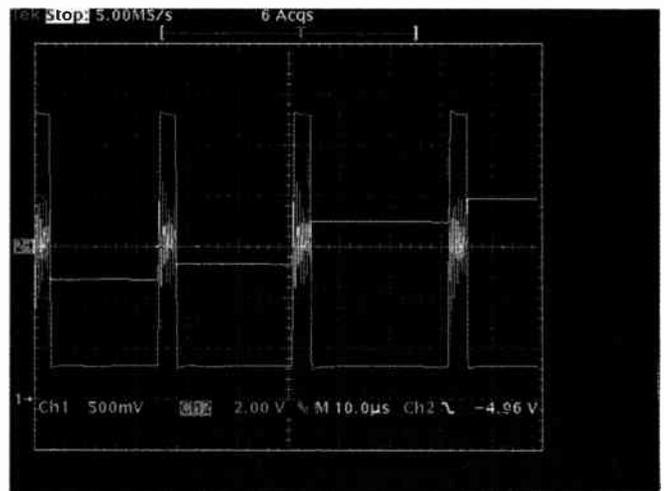


Fig.7b: a waveform is acquired by continuously stepping the delay between the pulse applied to the tank circuit and the hold signal. The rising plateaus generated by successively greater delays capture the rising edge of a particular sinusoidal cycle and show how a repetitive 1.8MHz signal is effectively frozen and reproduced on a much larger time scale. Note that the hold period or the time interval between successive pulses, reflected in the length of the plateaus, increases with increasing voltage. This is because the conversion time of the ramp converter is proportional to the sampled voltage.

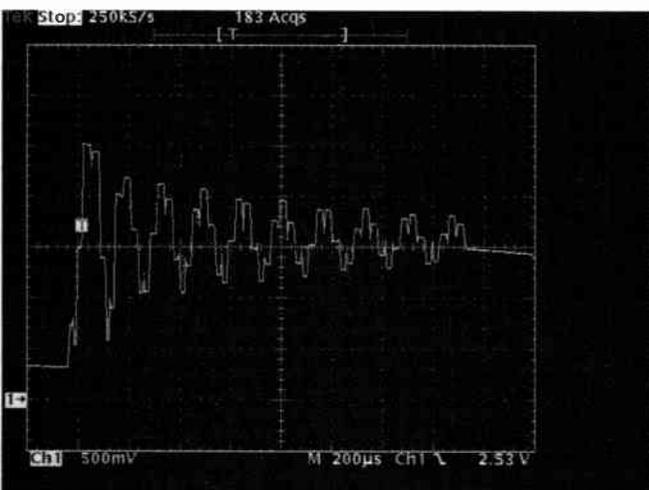


Fig.7c: with a timebase of 200 μ s/div, the sample-and-hold control signal is now just a succession of spikes and is not shown. At this time scale, the sequence of flat plateaus reproduces a digitised version of the original ringing waveform of Fig.7a, occurring at a rate almost 1000 times faster.

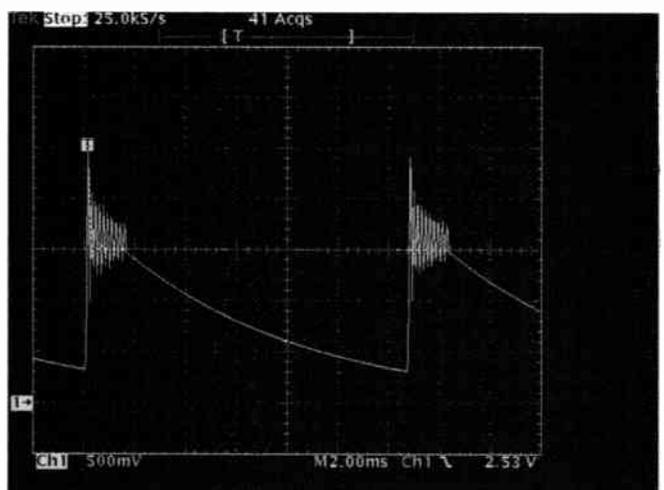


Fig.7d: this final shot is at the longest timebase setting (2ms/div). Each bunch of oscillations is the digitised ringing waveform in the previous figure. Between acquisitions the micro performs calculations, so the S/H circuit is idle and the charge on the 680pF capacitor decays.

in a ramp converter. This requires a voltage rising at a constant rate to be produced at the inverting input of comparator IC5 (pin 13). This is produced by an LM334 constant current

source (REG1) which is used to charge a 4.7nF capacitor.

The LM334 provides temperature compensation in this time-critical part of the circuit.

The input signal (via the S/H circuit) is applied to the non-inverting input of the comparator (pin 12). The output of the comparator is programmed to trigger a counter interrupt inside the

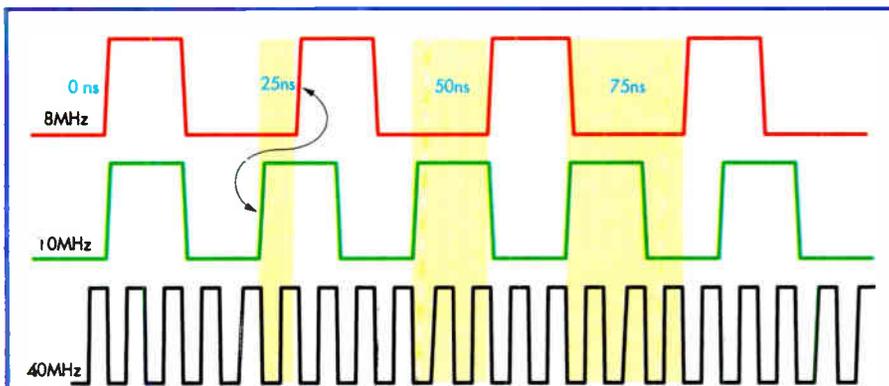


Fig.8: the time difference between the rising edges of 8MHz and 10MHz clock signals are exploited to enable high-speed sampling. The micro latches a high on PD1 (pin 3) on the rising edge of its 10MHz clock and after a 0, 25, 50 or 75ns delay, the rising edge of the 8MHz clock freezes the input voltage at that instant.

AT90S2313 when the ramp voltage exceeds the input voltage.

Note that the LM334 is rather slow compared to the speed of the rest of the circuit, so current is not switched at its input terminal. Instead, switching is performed at pin 13 of the micro, which is connected to an internal pull-down transistor. This shunts current from the LM334 until the conversion commences.

Once enough of the waveform is acquired, the microcontroller performs an FFT of the sample and finds the spectral peak. The FFT is a complicated mathematical procedure and is quite computationally intensive. It is therefore usually performed on high-speed floating-point processors, such as Intel's Pentium class and above.

However, speed is not of paramount importance in this application. More importantly, the results must be accurate and this was confirmed by comparing the results of two FFTs, one performed on a Pentium and the other on an AT90S2313.

Display and keypad

A 2-line × 16-character LCD module, keypad and ISP (in-system programming) interface to the micro via port B (PB2 to PB7) and one bit of port D (PD6). A number of port B lines are shared between devices. The LCD module is interfaced in 4-bit rather than 8-bit mode, so only its upper data lines (DB4 - DB7) are connected.

The keypad has 12 keys, organised in a matrix of 4 rows × 3 columns. The micro pulses each row in turn and polls the columns to determine which key is being pressed. Note that 4.7kΩ resistors are included in series with all the keypad lines to protect the port pins. This means that if a key is pressed while the micro is updating the LCD, no harm is done.

Power supply

The power supply section of the L/Q Meter appears in Fig.6. Starting at the DC input socket, diode D9 provides reverse polarity protection ahead of a 7805 positive voltage regulator (REG2). This regulator provides +5V for the entire board.

As explained earlier, -5V is also needed for op amp IC4 and the analogue switch (IC3), and this is generated from the +5V rail by a MAX635 switchmode voltage inverter (IC6). As shown, this device requires only a diode (D8), inductor (L1) and filter capacitor to function as complete switchmode inverter.

The -5V rail is reduced to -1.8V by an LM337 negative voltage regulator (REG3). The 120Ω and 56Ω resistors between the GND and OUT terminals set the output voltage to -1.8V, to be used as a bias voltage in the op amp circuit.

Next month

That's all we have room for this month. Next month, we will give the full construction details and describe how the Inductance & Q-Factor Meter is used.

EPE

Out Of Bounds Detection & Display

The meter measures frequency and decay constant, so L and Q are derived quantities. This means that a Q value will be out of bounds when the meter cannot acquire sufficient periods of oscillatory decay to reliably calculate a decay constant.

This can occur for one of three reasons: (1) the Q is too low; (2) the Q is too high, so that negligible decay is observed on the scale of several hundred oscillations; or (3) the decay occurs on a very large time scale outside the range of the meter (this can occur when the measured frequency drops to several tens of kilohertz).

Note that an out-of-bounds Q does not automatically indicate that L and f are also unobtainable. These parameters will continue to be displayed, although their precision generally drops to around 10-20% of nominal. If no stable value for f can be had, then the L and f displays will blank out and a sole 'E' will show in the Q position.

Constructors should also be aware that LC circuits can have parasitic oscillations. If these are large, they can register as an incorrect value for L. This occurs because some inductors cannot be well approximated by a simple theoretical L, so there is no unique answer to 'what is the value of this inductor?'.

Nevertheless, the value derived from the frequency of oscillation with a given capacitor is a perfectly legitimate result, though if one were to make measurements at other frequencies, or use $V = L \times dl/dt$ to get L, a different answer could be obtained.

In other words, some thought must be given to the details of the measurement, rather than relying solely on the instrument to produce the magic number!

The Power of Mechatronics

Part Five – A New Dimension by Ian Pearson

In the last issue we introduced the concept of the Virtual Demonstration Board (VDB) in the context of adding speech interaction to a system. This was achieved using the Proteus VSM development tool from Labcenter Electronics (see back cover).

This month we will continue in a similar vein, but we will look at some of the

other capabilities the Proteus VSM tool can offer. Our theme is Mechatronics, which involves interaction with sensors and mechanical components. Traditionally, this is difficult to achieve without physical hardware. We will, therefore, look at the implementation of the PICDEM Mechatronics Development Board in a virtual development environment.

Virtual development

A virtual development board provides a means to perform system development without needing hardware. However, the aim is not to exclude hardware completely, that is after all the end goal of any design cycle, but to help reduce the total design cycle time. If we can reduce the number of

hardware iterations required to reach a final design then we should be able to save time and crucially cost.

While we are trying out new ideas, or want to understand how a particular function works before we invest the time building a prototype, we can make use of the mixed mode simulation provided by the combination of MPLAB IDE and Proteus VSM. This will often prove more productive than creating a breadboard, soldering wires and checking connections, only to find you need to change a component during your first test, moments after building the board.

The use of the system simulator helps to reduce this cycle as the component change becomes a simple replacement, or a change of value in the schematic capture interface. An example simulation on a PC screen is shown in Fig. 1.

Once we have a design and are learning how the design functions we can make use of the virtual instruments, voltage and current probes and graph functions provided by the system simulator. These are all functions which can be provided

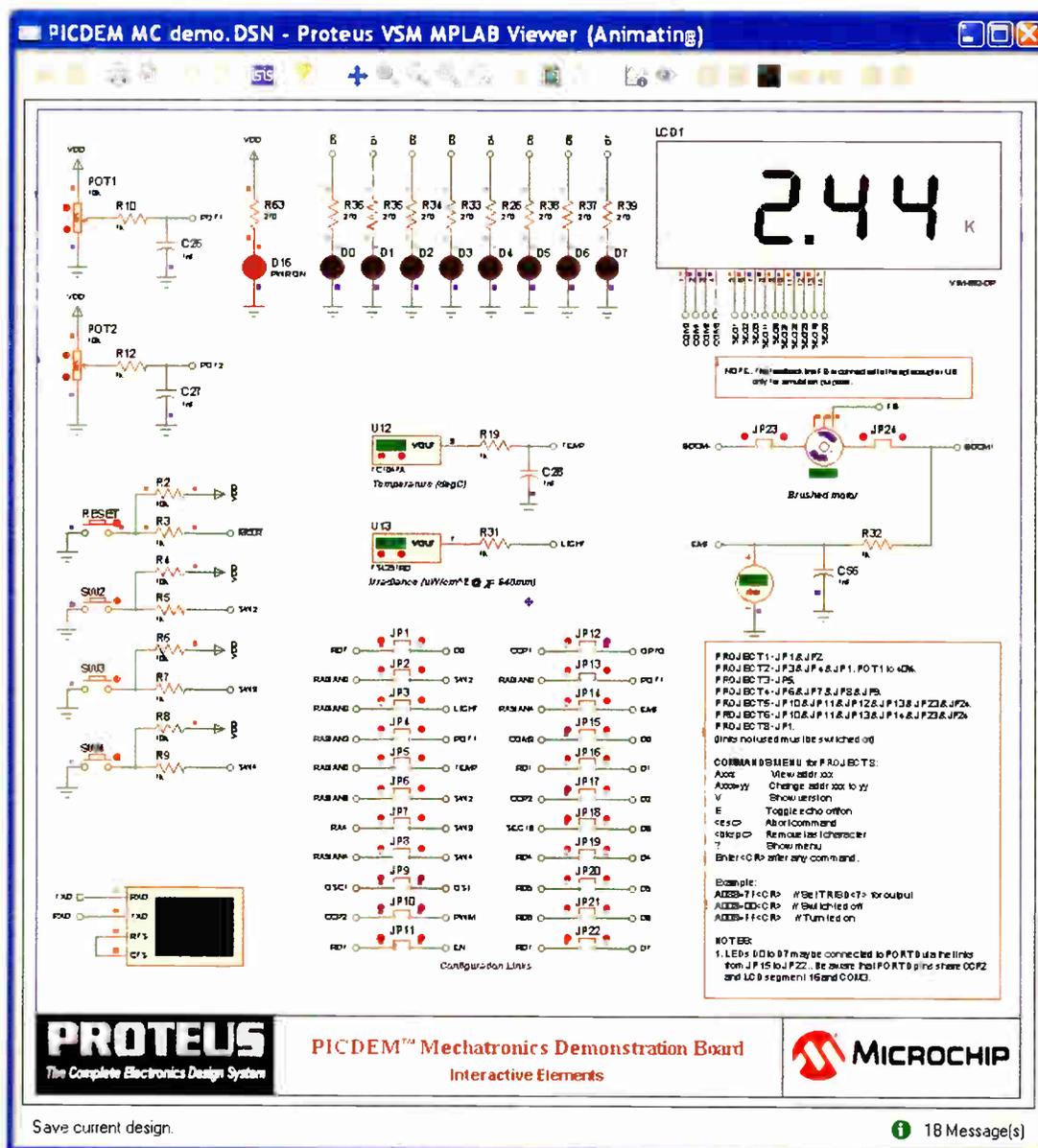


Fig. 1. PICDEM Mechatronics demo board running a DC motor and back-EMF measurement and control (Project 6).

by hardware, but often at significant expense. In a mixed mode system we may wish to add an oscilloscope, maybe a logic analyser, log a voltage against time, add a protocol analyser for I²C or SPI. All of these are added quickly and easily to the design and help us to refine our system saving time and effort.

This is all very well, but these are all electronic components and we are creating a mechatronic system. We want to add a display, maybe a motor, surely we can't simulate these, can we? The benefit of the Proteus VSM simulator is that it allows you to add a number of electromechanical components, sounders, displays and models of sensors. This allows us to perform a full system simulation.

A major benefit from a software development perspective is the ability to perform operations such as range testing of a sensor. If, for instance, we wanted to test the full operating range of a temperature sensor, how difficult is it to create an environment in which we can re-create a -40°C to +125°C operating range.

In the case of the mechatronics board we have a light sensor, this again would be difficult in a real world environment to create and test a specific set point. We can, of course, bypass the sensor and use a voltage source, but this requires us to manually convert the voltage source to temperature so we can cross refer the test. Using the system simulation method makes this much easier. Examples are given in Fig.2 and Fig.3.

The virtual instrument and ground terminal can be added from within the MPLAB viewer by right clicking and choosing **Place -> Instrument -> DC Voltmeter**.

The examples allow us to easily cross compare an expected reading with the output

voltage reading from the ADC. The up and down buttons on the sensor are used to adjust the displayed value and hence the output voltage. Once the values have been set up, the instrument can be wired up, all without leaving MPLAB.

So, at this point, the virtues of system simulation should be apparent. Let's take a look at what we can do with the PICDEM Mechatronics VDB.

Using the VDB

Before we start using the demo board we need to make sure we have both MPLAB and the relevant version of Proteus VSM installed. You will need to use MPLAB V7.60 or greater and the demo version of Proteus at V7.1 SP4 or above. You may, therefore, need to download the latest version from the MPLAB page on the Microchip website at www.microchip.com/mplab, from where both MPLAB and the demo version of Proteus VSM are available.

Alternatively, if you have already installed Proteus from the CD provided with your May edition of *EPE*, then you can use the update manager to obtain the latest release of the demo version. This update process is necessary to ensure you have the latest library and part models, plus the demo code design

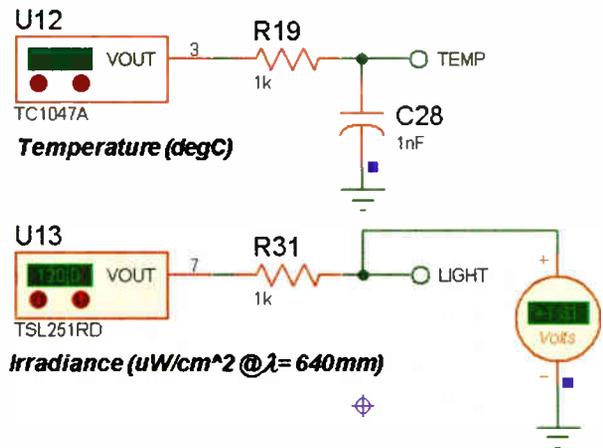


Fig.2. The virtual sensors with additional virtual instrument to compare output voltage with stated value.

for the PICDEM Mechatronics board. (The Mechatronics Demo Board and model of the PIC16F917 were released in the period between printing of the CD and release of this article).

So what can we do with a virtual demo board? This board offers a representation of a physical system. It differs in that some of the components we would normally expect to see on a design, such as power components and connectors, may be omitted. This can be for purposes of clarity or, if no annotation to PCB is to be performed, we can omit components as we need only include those devices required to perform our simulation.

If we subsequently decide to improve the capability of our system and create a PCB we can add the necessary components. The act of omitting components also helps to improve simulation time as there is less computation to perform. If we do decide to add all necessary components to create a physical PCB, then we can set the properties on a component to exclude it from simulation. This has the same effect as omission from a simulation perspective, but provides all of the necessary data for system creation.

In the same vein as exclusion from simulation, we can also exclude items from the PCB. This is useful where we have added components or instruments to aid simulation which would not be required on a final system. The examples that follow are all based around the standard demo package released with the PICDEM Mechatronics Demo Board hardware. To this we add the schematic design file for the Proteus VSM simulator which, combined with MPLAB IDE, allows us to perform our system level simulation and debug. This approach allows us to perform a comparison between the functionality that can be achieved with a virtual system and physical hardware.

We can debug in much the same way as we would with hardware tools using breakpoints. The physical hardware state is frozen at the breakpoint, unlike in hardware. This allows us to confirm hardware operation and step through actions to confirm code without losing the hardware status. See Fig.4.

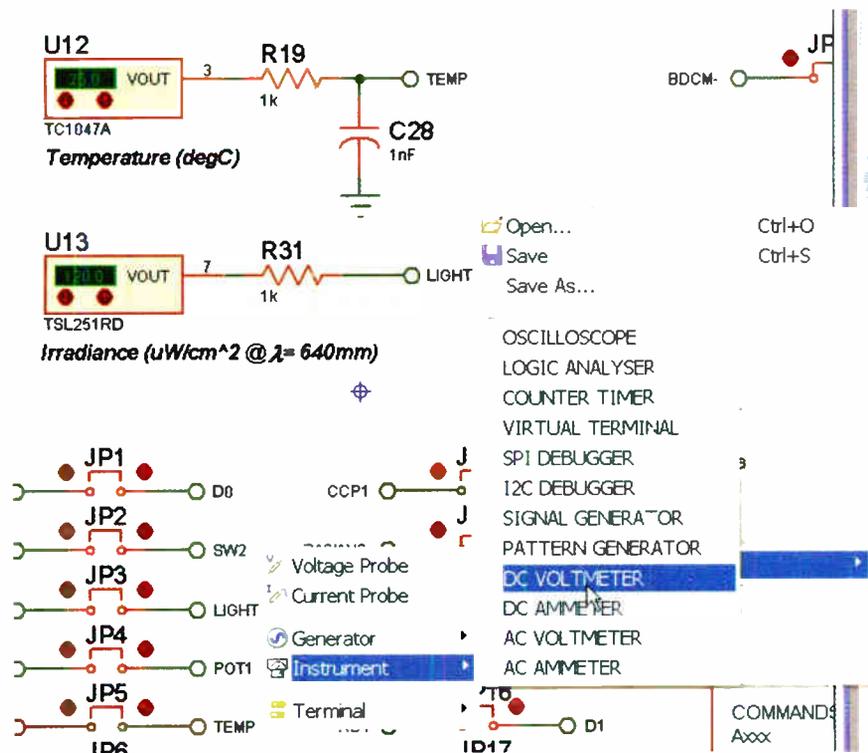


Fig.3. The virtual instrument and ground terminal can be added from within the MPLAB viewer.

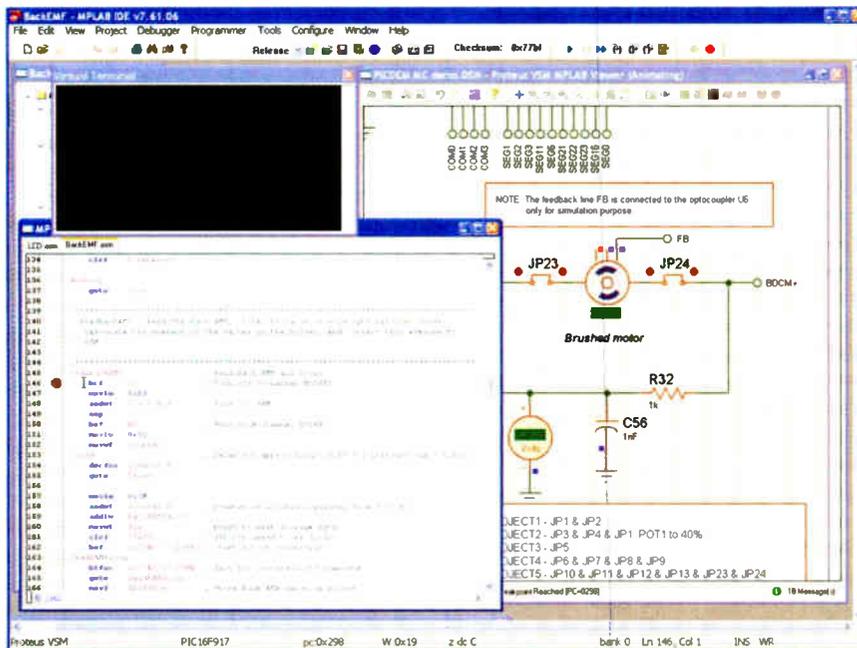


Fig.4. Example of a debugging screen.

All of the software examples are written in MPASM. It is possible to write your own applications using the C language because the Hitech PICC Lite compiler is now bundled in the installation of MPLAB V7.62 and later. At the time of writing, however, the examples have yet to be ported to the PICC Lite compiler.

Device options

The device provided on the VDB is the PIC16F917. This device is a member of the mid-range architecture family and is one of the more peripheral-rich devices in this product group. The benefit that this provides is that we can use the high functionality, large pin count devices to develop our system. Once we have achieved the functionality we require, it is then possible to assess if we can use an alternative device in the family, which may be more suitable from a cost, size or other requirement.

As devices in the family groups share the same architecture and instruction set, and largely the same peripheral set, then migration to a different device is made significantly less difficult. Certainly, the physical Mechatronics Demo Board is laid out to accept 40-pin and 20-pin devices from the mid-range family of devices. The PIC16F917 allows us to complete all of the projects, except Project 9, which uses the more advanced ECCP module of the 20-pin PIC16F690.

The tasks we can perform in our virtual simulation take us from basic interaction, using digital I/O to reading a switch position and subsequently illuminating an LED; through using the ADC to read sensors; output of data to a direct drive segment-based LCD using the on-board LCD controller module and the ability to drive a virtual DC motor with the on-board capture, compare and PWM (CCP).

When approached from the perspective of using a more functional device in a

virtual environment, we can very quickly achieve success and determine if our system is feasible. Once the initial design concepts are achieved we can quickly determine if we need to add functionality and move to a better, more functional device or, alternatively, if we need to, move to a more cost-optimised device.

The move to a cost-optimised design may require us to create the equivalent of a hardware module using software and I/O. Using the virtual approach, we can quickly make these changes and perform comparisons using the built-in analysis tools. Once we feel we have narrowed down the design we can perform our first hardware build. This method should then save us a significant amount of time and effort and hopefully allow us to get our product to market much earlier.

The limitations enforced with the demo version of the simulation system are that we cannot alter the schematic. It is node locked, so components cannot be added or removed. We can add instruments to help us perform our debug but we are limited to the equivalent of a non-alterable piece of hardware.

This restriction aside, we do obtain a fully functional virtual equivalent of the PICDEM Mechatronics board. We can use this to perform all of the standard labs provided and we can make use of the virtual instruments and graphs to help us observe and learn about what is happening on the circuit, without the immediate need to invest in hardware tools.

A further limitation is that the exact part we require may not be modelled. If this is the case, then requests for new models can be made to Labcenter or we can make use of the approach outlined above using a more functional superset level device and choosing the functionality we need on that device to create our design.

Using the VDB

Once we have both MPLAB IDE and Proteus VSM installed we need to open our project. Within MPLAB IDE choose **Project > Open** and then navigate to the PICDEM MC Demo folder in `C:\Program Files\Labcenter Electronics\Proteus 7 Demo\Samples\VSM MPLAB Viewer\Eval Boards\`.

Here you will find the PICDEM MC demo and a number of other VDBs which can also be tried. Alternatively, you can download the support package from the *EPE* website (access via www.epemag.co.uk).

To help you perform the exercises and use the mechatronics VDB you should download the user guide for the PICDEM Mechatronics board, also available from the *EPE* website. There is also a quick link to the mechatronics demonstration kit via www.microchip.com/mechatronics.

The PICDEM Mechatronics PCB is a very functional development board and as

PROJECT1 - JP1 & JP2.
 PROJECT2 - JP3 & JP4 & JP1. POT1 to 40%.
 PROJECT3 - JP5.
 PROJECT4 - JP6 & JP7 & JP8 & JP9.
 PROJECT5 - JP10 & JP11 & JP12 & JP13 & JP23 & JP24.
 PROJECT6 - JP10 & JP11 & JP13 & JP14 & JP23 & JP24
 PROJECT8 - JP1.
 (links not used must be switched off)

COMMANDS MENU for PROJECT 8:

Axxx View addr xxx
 Axxx=yy Change addr xxx to yy
 V Show version
 E Toggle echo off/on
 <esc> Abort command
 <bkspc> Remove last character
 ? Show menu
 Enter <CR> after any command.

Example:

A088=7F<CR> // Set TRISD<7> for output
 A008=00<CR> // Switch led off
 A008=FF<CR> // Turn led on

NOTES:

1. LEDs D0 to D7 may be connected to PORTD via the links from JP15 to JP22.. Be aware that PORTD pins share CCP2 and LCD segment 16 and COM3.

Fig.5. Jumper settings aide memoire

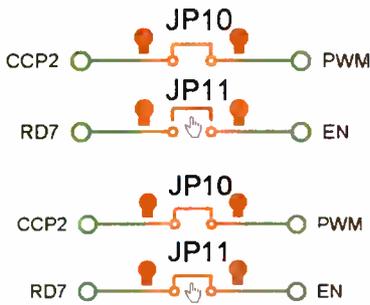


Fig.6. Jumpers are default open as the demo board is generic to all projects, to engage a jumper, simply click on it.

such does require a number of jumper changes to be made to route functions between a device pin and board function. To keep the number of design files to a minimum, this approach has been repeated on the VDB using an active link. To help understand which links need to be used for each project an *aide memoire* is provided on the schematic sheet, as shown in Fig.5 and Fig.6.

The *PICDEM Mechatronics Demo Board User Guide* provides a good reference to work your way through each of the labs provided, discussing what is being performed and the board setup to achieve the function required.

Development tools

MPLAB V7.62 includes bundled compilers from CCS and HiTech. Of particular interest is the HiTech PICC Compiler for

Exclusive board offer

The Microchip PICDEM Mechatronics Development Board not only supports all of the projects featured in this series of articles but also includes nine example projects, each complete with source code.

To claim your exclusive *EPE* 20% discount on the Microchip PICDEM Mechatronics Development Board contact ACAL Semiconductors on Telephone: +44 (0)118 902 9702. Fax: +44 (0)118 902 9614. Email: sales@acalsemis.co.uk. Website: www.acalsemis.co.uk

the Mid-Range Family of PICs and it specifically supports the PIC16F917. The compiler is a *lite* version and is therefore limited to a range of supported devices and also some of the device capabilities are restricted. All of the base line PICs and a number of Mid-Range PICs are supported.

For the 16F917 this limitation is to one page of program memory and two banks of RAM, thus providing a code space of 2K words and 176 bytes of RAM. Given the scope of the demonstrations this quantity of memory is however more than adequate. Full details of the PICC Lite C Compiler can be found on the HI-TECH website at www.htsoft.com/products/compilers/PI_CCLite.php.

Links

- www.microchip.com/mechatronics
- www.labcenter.com
- www.htsoft.com
- www.epemag.co.uk

ANDRE LAMOTHE'S
XGAMESTATION
 LEARN STEP-BY-STEP HOW TO DESIGN
 AND BUILD YOUR OWN VIDEO GAME CONSOLE!
 Design Inspired by the Atari 800/2600,
 Sinclair ZX Spectrum, Apollo II & Commodore 64!

Complete Package eBook Integrated IDE

SX52 CPU 80 MIPS! OPEN SOURCE!

FEATURES:

- Great for Hobbyists AND Students!
- Complete Software Development Kit!
- eBook on Designing the XGS Console!
- Parallax SX-Key Compatible!
- Fully Assembled XGS Micro Edition Unit!
- The Fun Way to Learn Embedded Systems!

PAL & NTSC COMPATIBLE!

WWW.XGAMESTATION.COM
 SUPPORT@NURVE.NET | PH 925.736.2098(USA)

RADIO MODULES FOR WIRELESS DATALINKS

Radiometrix continues to be recognised as the leading manufacturer of wireless datalinks for a wide variety of applications: it brings to market high-quality yet cost effective VHF & UHF low power radio modules that cater for the needs of OEMs manufacturing for international wireless data transmission industries.

Products available include:

- Narrow Band and Wide Band FM Transmitters, Receivers and Transceivers
- Single Channel and Multi-channel operation
- UHF and VHF ISM bands
- Custom design service
- Encoders and Decoders for RF remote control
- Radio Packet Modems
- Radio Packet Controllers
- Evaluation Kits

Applications include:

- Security & Alarm
- Telecommand or Remote Control
- Telemetry
- Industrial and Commercial
- Data Logging
- Automatic Meter Reading (AMR)
- Tracking




Radiometrix Ltd
 Hartcran House
 231 Kerton Lane
 Harrow, Middlesex
 HA3 8RP UK

Tel: +44 20 8909 9595
 Fax: +44 20 8909 2233
 sales@radiometrix.com

www.radiometrix.com

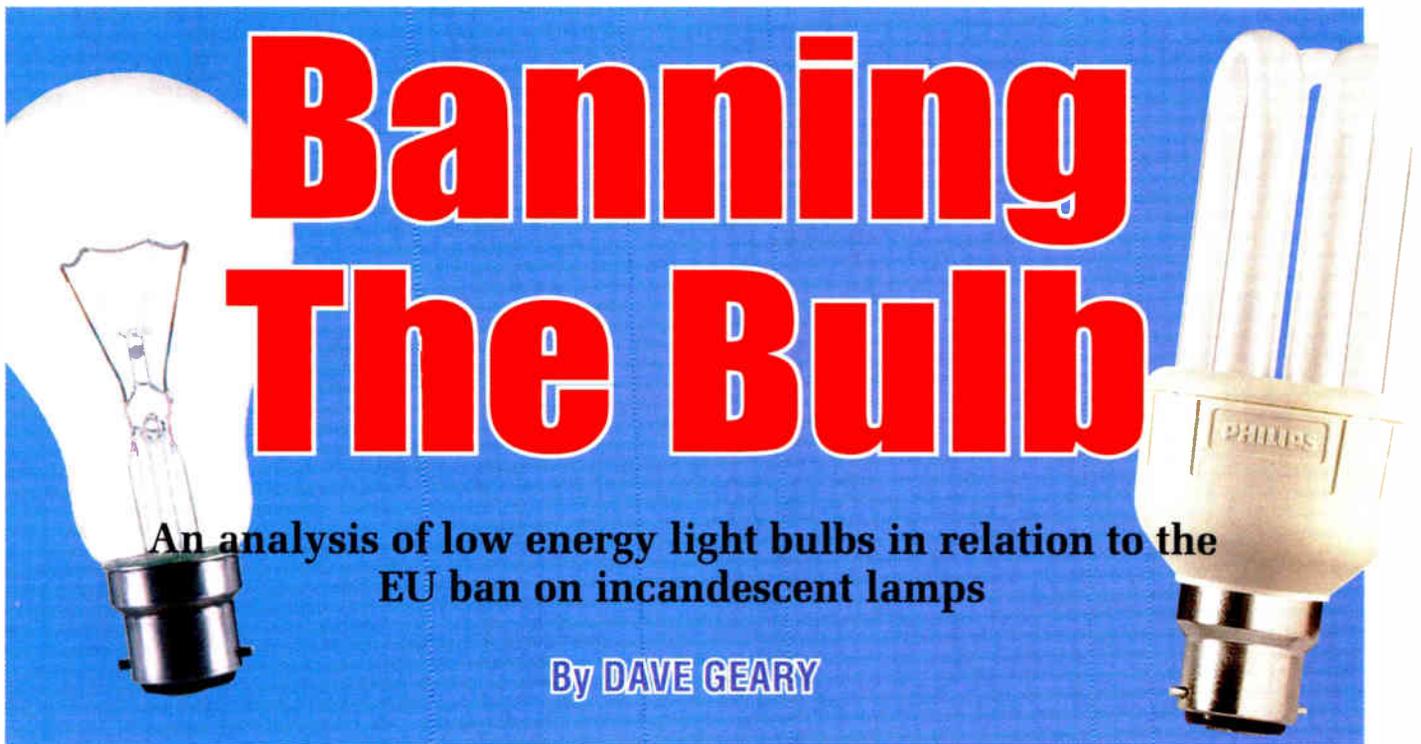RADIOMETRIX 20 YEARS OF INNOVATION FROM THE PIONEERS IN WIRELESS



THE *EPE Chat Zone* recently highlighted a potential move by the EU to ban incandescent lamps, including the humble domestic 'bulb'. In this article the author hopes to confirm what is true and dispel some myths, look at the potential impacts of this move and look at some of the solutions, including Compact Fluorescent Lamp (CFL), Tungsten Halogen (TH), and Light Emitting Diode (LED) technologies.

The author's background is over 20 years in the electrical wholesale distribution industry and he hopes you will forgive his use of the word 'lamp'. The 'trade' considers bulbs to be things that you plant! Lamps are sources of light, and they are installed in luminaires (or possibly, light fittings). The word 'bulb' is hereby banned!

History of electric lamps

Firstly, some background. The General Lighting Service (GLS) lamp (Fig.1) was invented in the late nineteenth century, but right from the beginning was the subject of some controversy. There are two claims to be the original inventor and the lighting industry is still divided on just who is responsible for the massive effect artificial lighting has had on social and industrial development.

In the American corner, Thomas Edison (1847-1931) was an American inventor who achieved over 1000 patents. Although not the first to produce

light from electricity, he designed a practical implementation which would become commercially viable.

Joseph Swan (1828-1914) was an Englishman who beat Edison to a practical design (1860) but was limited by the resources available to him at the time. Despite the now perceived rivalry, both inventors were eventually united in the Edison-Swan United

Electric Light Company, and the brand of Ediswan lamps was born.

The operation of the GLS lamp has changed little but improvements have been made to extend the life and efficacy (light output for energy input) until the limit of the technology has been reached. Improvements have been made in the gas that replaces air inside the lamp and also the material used for filaments, from the bamboo supports used by Edison to tungsten steel used today.

Today, we see the same technology not just in the humble GLS lamp, but also in decorative versions of different colours, shapes and sizes. The candle lamp is the same technology but with a nicer shape, and all colours are produced by acid etched glass



Fig.1. Philips GLS lamp



Fig.2. Philips Brilliantline low voltage dichroic



Fig.3. Philips SON Sodium High Pressure Sodium Discharge



Fig.5. Philips HPLN Mercury Discharge



Fig.4. Philips SOX Sodium street lamp

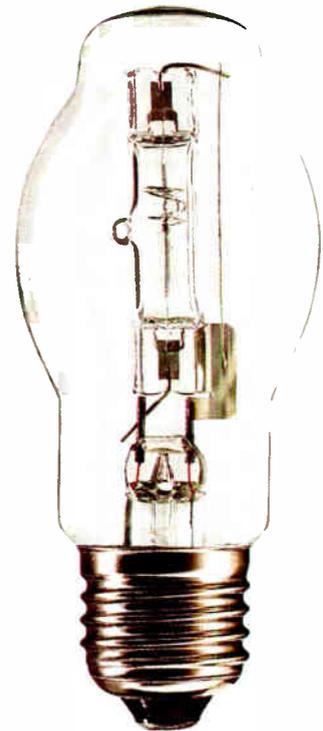


Fig.6. Philips HalogenA Discharge

or even just a painted coating. The tungsten halogen lamp, most easily recognised as low voltage spotlamps (Fig.2) in shops and kitchens, is one of the later developments which utilises clever chemistry to maximise life and light output, with some of the newest lamps using infrared filter/mirror technology to further enhance efficiency. Some of this technology will continue to be used for many years to come.

Legislation and rumour

Commercial users have, of course, long since abandoned the old technology wherever possible to obtain the energy savings associated with discharge technology. This term includes all fluorescent lamps/tubes, compact fluorescent, sodium (Fig.3 and Fig.4), mercury (Fig.5) and metal halide lamps as used, for example, in streetlighting and shops. In addition, discharge lamps last longer and the cost of labour, including replacement access, which in some cases far outweighs the additional cost of these lamps and the necessary fittings.

Domestically, of course, there is no labour cost and generally it's easy to assume that the energy cost associated with lighting is small. However, with energy costs spiralling this is no longer the case, and with the costs of more energy efficient replacements coming down, the payback period is realistic.

The precise details of the proposed EU ban on incandescent lamps have yet to be disclosed. Even the Australian ban, which was announced some

time ago, refers to 'less energy efficient incandescent lamps' and is not specific to type or wattage. However, various sources indicate that it is the higher wattage (40W to 100W) types used for general lighting which are targeted, and not those used for special applications (oven lamps, refrigerators, etc).

Many have assumed that the only allowable replacement will be compact fluorescent, but, in fact, other technologies, such as tungsten halogen (filament), are likely to be permissible as they are more efficient than GLS. They also maintain compatibility with dimmers and can be switched to full brightness immediately, so making

Table 1: Generalised Comparison

Type	CFL	TH
Runs	warm	hot
Hours	longest	better than GLS
Colour	to specification	2700K (as GLS)
Starts	slowly-mod fast	instant
Appearance	OK-awful	'bulb' (different shape)
Energy	best	med
Dimmable	no*	yes
Env Impact Mfr	higher	lower
Cost	med-high	med

*some CFLs now have dimming capability, but not with traditional dimmers.

them suitable for security lighting. The key here is the measurement of efficiency/efficacy – lumens per watt (lm/W). The current Part L of the UK Building Regulations requires 40 lm/W.

Tungsten halogen lamps also have another key advantage – they are outside the scope of the WEEE directive (explained later) which will require yet more recycling segregation of rubbish in future years.

Retrofit replacements

For most of us, there are two options; Compact Fluorescent (CFL) and Tungsten Halogen (TH). A quick and very generalised comparison is shown in Table 1.

Tungsten halogen

Examples of the tungsten halogen option include the Philips HalogenA GLS replacement (Fig.6) and the Osram BT, which have been around for many years. Recently, there has been a dramatic expansion of the range to include other shapes and types of lamp. For example, the traditional reflector (or spot) lamp used in many kitchens and task lamps is now available in a lower energy TH version. Philips boast between 10% and 40% more light output, twice the life of the traditional lamp, and a 'whiter' light than the older technology. There are even replacements for decorative 'candle' lamps.

The difference between tungsten halogen and traditional GLS lamps is in the gas which fills the glass envelope, the filament, and the running temperature of the lamp. A GLS lamp uses the gas to delay the filament burning itself out, whereas tungsten halogen uses the gas to redeposit vapourised fragments of tungsten back onto the filament. This recycling extends the life of the lamp and provides additional stability to allow the filament to have a higher designed running temperature, which in turn increases light output in the visible spectrum.

As can be seen from the comparison table, tungsten halogen goes some way towards reducing energy consumption, and offers advantages of appearance, compatibility with dimmers, and lower environmental impact in manufacture. However, they do not achieve the extremely long life and low energy usage of CFLs. The author's understanding is that tungsten



Fig.7. Philips SL lamp in latest guise

halogen lamps will not be the subject of the proposed ban since their efficiency is enhanced over GLS.

Compact fluorescent

In general, lamps across the industry are specified on the following criteria:

- Type or range, possibly manufacturer e.g. Philips HalogenA
- Power, in watts
- Cap, e.g. BC for Bayonet Cap
- Colour, e.g. Clear/Pearl, or Cool White (fluorescent), sometimes by number such as 840 (explained later)

CFL retrofit lamps add two additional factors – life and light output per watt. These lamps first started life as the Philips SL range, which older readers might recall as a very heavy glass jar containing a folded fluorescent tube, a starter, and a wirewound choke.

They were excellent in many respects, but were relatively expensive for most of their product life. As a result, domestic use was limited but in the world of commercial buildings, the SL offered significant savings when

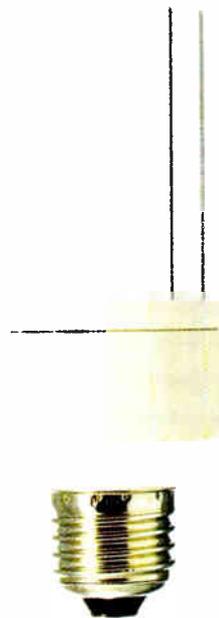


Fig.8. Philips Master PL-E

the energy reduction was added to the long life and consequent labour saving due to not having to change lamps so often.

Their weight was also an issue, and the author has visited many clients over the years where SL lamps were installed hanging downwards, in downlighters, and towards the end of their life it was easy to pick out bits of brown resin that had fallen out of the choke and were laying on the inside of the glass jar! Of course, put them in a standard lamp, facing upwards ('base down' as the industry calls it), and the bayonet cap SL lamp would



Fig.9. Two new lamps from Megaman



Fig.10. Philips PL-E – note the loops against ‘sticks’ on this version

swing from side to side, pivoting on the pins on its base under its own weight! However, it would be wrong to underestimate the importance of this lamp, especially as it has only recently disappeared from sale, albeit with lighter, electronic gear installed (Fig.7).

Current lamps are much smaller, lighter, and more efficient (Fig.8 and Fig.9). Cost pressures, particularly with consumer demand, have forced the development of domestic and commercial grades. The consumer

is making a decision on a handful of lamps around the home, and the energy saving effect is far lower. In addition, there are no labour costs to changing a lamp, just the nuisance factor. For these reasons, the lamp needs to have a lower price tag to make it an attractive proposition.

Manufacturers have responded to this by offering lower priced lamps with lower output and shorter life than the commercial ranges (Fig.10). It is not unusual to find a domestic lamp in the Superstore with a rated life of, say, 5000 hours, and a commercial grade lamp with between 15,000 and 20,000 hours. The cost difference is significant, with some supermarkets selling domestic lamps at under £1, with commercial lamps being typically between £5 and £10. This difference is insignificant if you have to pay someone to change a lamp three times instead of once.

Light output

The lower light output may not be critical domestically but commercially it is very important, with standards for lighting in buildings requiring a given light output. If lower output lamps are installed, more fittings will be required and this negates any saving. Of course, the context of this article is retrofit lamps and it is unlikely that any commercial landlord would wish to add fittings to an existing installation, even if matching ones are available.

For the domestic market, while all of the major lamp manufacturers are producing an ever expanding product

range, the most diverse is probably from Megaman. They are a fairly new entrant to the UK market and specialise in just retrofit lamps.

Commercial products tend to have a higher price tag but also higher output and longer life, which makes them an excellent prospect. In truth, these lamps are a better choice for the domestic market as well, but only to those who recognise the longer term benefits.

Cost comparison

Philips have developed a clever Excel-based tool called ‘Cost Of Ownership’, which compares an existing lamp against a potential replacement, taking into account the price of the lamp, anticipated life, energy costs, and the labour cost each time a lamp is replaced. The latter is often a massive contributor to cost commercially, but since the scope of this text is typically domestic, it should be considered nil.

Other manufacturers operate similar methods of comparison, but of course the mathematics is fairly simple. To illustrate, let’s take the example of a 60W GLS lamp used for four hours per day, seven days per week, replaced with an 11W compact fluorescent. Table 2 makes some assumptions about energy cost and the cost of a new lamp. It also shows a typical domestic CFL available from the supermarket and a typically more expensive commercial grade CFL. Pessimistic prices and lamp life have been assumed for the CFLs, so this is a worst case scenario.

Table 2: Cost Comparisons

	60w GLS	11W CFL Domestic	11W CFL Commercial
Hours per day	4	4	4
Hours per year (based on 365 days)	1460	1460	1460
<i>Cost of Buying Lamps</i>			
Lamp life	1500	5000	15000
No of lamp changes per year	0.97	0.29	0.10
Cost of new lamp	0.20	3.00	7.00
Cost of buying lamps per year	0.19	0.88	0.68
<i>Cost of Running Lamps</i>			
Lamp power (W)	60	11	11
Electricity cost £/kWh	0.09	0.09	0.09
Cost of running lamps per year	7.88	1.45	1.45
<i>Cost of Buying and Running</i>	8.08	2.32	2.13

It is evident from the table that the commercial grade CFL is actually far better value than the GLS lamp it replaces, even though it costs 35 times as much.

Carbon footprint

Notwithstanding the obvious financial benefits of CFL, there are impacts on the environment associated with lighting. Philips state that 19% of all energy consumption worldwide is lighting related (a figure attributed to the International Energy Agency). The energy saving aspects of CFLs are, therefore, unarguable.

If recycled, the environmental impact of moving CFLs from factory to eventual user and then to recycling facility is mitigated by the number of new lamps being reduced (i.e. fewer changes means less movement of goods).

Any use of energy has an environmental impact. Osram have provided a technical data sheet which uses a comparison between the overall impact of 15 GLS lamps against one of their commercial grade replacements.

The 15 incandescent lamps will use some 12.9kWh in their manufacture, and 1125kWh in energy during operation. This totals 1137.9kWh. The CFL replacement uses only 3.4kWh in manufacture, 225kWh during operation, totalling 228.4kWh. This represents, according to the datasheet, a saving of 909.5kg of carbon dioxide emissions.

The mercury within the lamp is mitigated by the mercury which is not emitted during the burning of fossil fuels to produce the extra energy. An Osram CFL uses mercury (as all must to operate), but this has been reduced through design to 3mg per lamp.

Disposal – WEEE Directive

However, these lamps also use a cocktail of artificial substances in their construction, including mercury and phosphorous, and as a result are included in the WEEE Directive (Waste Electrical and Electronic Equipment) requiring the recycling of these lamps for commercial users. Domestic users will be advised and requested to recycle, possibly via the retailer from which they were purchased.

Later in 2007, it is highly likely that prices of CFLs will have to rise to cover

their eventual recycling/disposal, although this will not be sufficient to remove the huge running cost advantage over GLS.

The WEEE Directive covers, within lighting:

- Luminaires for fluorescent lamps with the exception of luminaires in households
- Straight fluorescent lamps
- Compact fluorescent lamps
- High intensity discharge lamps, including pressure sodium lamps and metal halide lamps
- Low pressure sodium lamps
- Other lighting or equipment for the purpose of spreading or controlling light with the exception of filament bulbs

Source: www.weeedirectory.com

All items within the scope of the WEEE Directive must be recycled, including such items as refrigerators and televisions. Since these items are fairly expensive, the added surcharge for recycling is insignificant and is generally being absorbed by the manufacturer. In the case of lamps, the unit price is far lower and recycling costs are more significant. At the time of writing, there is still some debate within the industry as to whether prices will simply rise to cover it or, commercially at least, there will be a separate environmental disposal charge on CFLs and some other lamps, as is currently the case with tyres.

GLS lamps are not affected since their construction is of inert materials. There is an expectation of a 'WEEE charge' of around 30p per lamp or an increase in the price of the lamp of similar proportions.

A new organisation, Recolight, is responsible for collecting these charges and administering payments to recycling companies, see www.recolight.co.uk.

Households are under no obligation to recycle under the WEEE Directive, although it is encouraged, and could be required under local bylaws.

To quote www.weeedirectory.com:

Consumers and the WEEE Directive – Household:

As a private household you are under no obligations to recycle WEEE, but, you will receive information encouraging you to recycle WEEE.

The precise link is www.weeedirectory.com/Default.aspx?tabid=95

Control gear – lamp electronics

One potential concern with retrofit CFLs is that the fittings may not have adequate ventilation or other methods of cooling. The fitting is not likely to suffer any ill effects, since the running temperature of any incandescent lamp is far greater than the fluorescent replacement.

Osram point out that all electronic ballasts are sensitive to ambient temperature, although so long as this is below around 70°C, then the normal life of the gear will be achieved, i.e. life of the overall lamp will be unaffected. Over 70°C, and life reduces exponentially, so this may be an issue in certain installations.

Philips do not believe that life will be adversely affected, provided that the CFL used is of an equivalent to the GLS replaced.

Another issue which touches on control gear is the warm-up time. Modern replacement lamps from the leading manufacturers reach full output within less than 30 seconds, and this depends again on ambient temperature; the colder the room, the dimmer the lamp will be initially. However, Osram state that their electrodeless technology, as used on the Dulux EL Longlife Classic A 20W, comes on instantly at around 90% output, then rising to 100%.

The Lighting Association requires that, in normal operation, all CFLs should reach at least 60% brightness in 60 seconds, and the major brands discussed here would appear to easily meet that criterion. They go on to recommend that consumers should only purchase lamps which bear the logo 'Energy Saving Recommended' and avoid cheap, poor quality lamps.

Most older designs of CFL retrofit lamps use an electronic version of the conventional inductive starter circuit. However, the electrodeless Osram lamps, and other newer designs, use a high frequency (30kHz to 50kHz) control gear which further enhances efficiency and eliminates visible flicker, together with stroboscopic effects.

Over recent years, the overall lamp (including control gear) size for any given wattage has significantly reduced, together with control gear losses, and the mercury content of the lamps. Conversely, average lifetimes have increased.

The author sought clarity on the question of power factor from Philips: 'The stated wattage on the lamp includes the effect of the inherent power factor and does not further influence energy savings.' They go on to make another valid point: 'The marked reduction of current with CFL lamps also reduces the distribution losses in the supply system'.

Special uses and alternative approaches

Retrofit lamps have traditionally been viewed as uncontrollable, other than 'on' and 'off'. However, the Osram range now incorporates extra facilities, such as photocell control (to allow for automatic simulation of 'at home' lighting, Dulux EL-SENSOR), dimming via conventional dimmers (Osram EL-DIM), or dimming with a switch on the case of the EL-VARIO.

So far, this text has concentrated on retrofit solutions, where the luminaire (fitting) is already installed and there is no desire to change it. The best solution, of course, is a fitting which is designed to use a more energy efficient light source and, if fluorescent, incorporates the required control gear in the fitting.

This also has the advantage of offering high frequency gear, which operates the lamp at around 32kHz, eliminating all traces of flicker, all stroboscopic effects and reducing energy consumption by, typically, a further 5% to 10%. Thorn Lighting are one of many manufacturers offering such luminaires, and while much of their range is commercially focussed, a trawl on *Google* will find many companies offering excellent energy saving fittings which are also attractive.

LED technology is still in its relative infancy and is yet to offer a viable alternative for key reasons: first, the light output is not yet sufficiently high, and second, the light output of an LED degrades over time too much to allow the meeting of minimum light level requirements to be guaranteed for enough of the product life. Osram and Philips both contend these issues will be solved in the near future.

By way of comparison, efficiencies, irrespective of colour appearance of the lamp and the aesthetics of the lamp, are shown in Table 3 for typical Philips versions.

The author has made a contribution to an industry charity – The Electrical and Electronic Industries Benevolent Association (www.eeiba.org) – in recognition of the support received from lamp manufacturers in the preparation of this article.

The key factors are always energy efficiency and acceptability of aesthetics. Hopefully, this article has provided some thought-provoking information – hard fact – to counter the rumours that CFLs are either 'all good' or 'all bad'. The author has used them very successfully, but only where appropriate. Have a look on the manufacturers' websites, there are lots of new products arriving to meet the challenges – these are exciting times!
EPE

Acknowledgements and References

Megaman (UK) Limited – www.megamanuk.com

Philips Lighting Limited – www.lighting.philips.com

Osram Limited – www.osram.co.uk

Ban The Bulb – www.banthebulb.org

Energy Saving Trust – www.energysavingtrust.org.uk

Recolight – www.recolight.co.uk

WEEE Directory – www.weedirectory.com

Thorn Lighting – www.thornlight.com

The Lighting Association – www.lightingassociation.com

Table 3: Typical Lamp Efficiencies

Lamp	lm/W	Life
GLS	10-15	1000 hrs
TH (Philips BTT HalogenA)	14-17	2000 hrs
CFL (Philips Master PL electronic)	46-68	15000 hrs (70% output)
LED	<45	35000 hrs (70% output)

www.epemag.co.uk



agar Circuits

PCB DESIGN & MANUFACTURE
for both the Hobbyist and Professional

PCBs designed and produced from:

- Notes
- Schematics
- Specifications
- Descriptions
- Print-outs
- Gerbers

Available With or without component assembly

* FREE * PCB PROTOTYPE With Quantity Orders

Email: adinfo@agarcircuits.com
Tel: 028 (90) 738 897

Laser  Why tolerate when you can automate?

 Home Automation

 KATS AV transmission and IR control system

 Brix Ethernet based MP3, communications and control systems



C-Bus Shop
C-Bus and C-Bus Wireless

www.cbus-shop.com


www.laser.com

Integrators, Installers, Trade and Retail customers welcome

Laser Business Systems Ltd
Tel: +44 (0) 20 8441 9788
Fax: +44 (0) 20 8449 0430
Email: info@laser.com
16 Garthland Drive, EN5 3BB

Circuit Surgery

Ian Bell

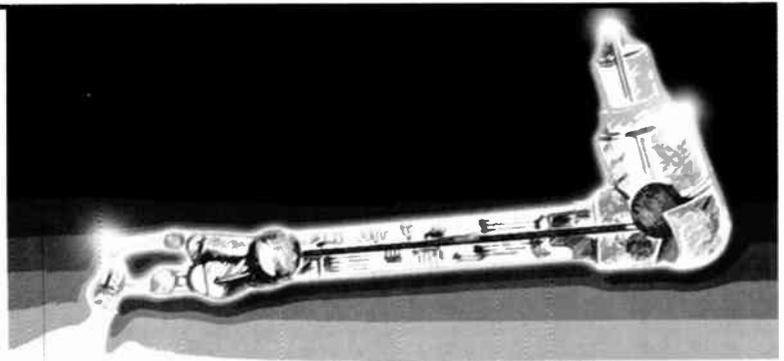

Regulator stability and switch bounce

User **Gerry** posted a question on the *EPE Chat Zone* (via www.epemag.co.uk) concerning the recent *Circuit Surgery* articles on regulator stability.

I've been following the recent Circuit Surgery articles. Although I understood them, I was wondering what are the symptoms of an 'unstable' regulator?

I appreciate that it'll oscillate, but if it's at such a high frequency surely this wouldn't show up on a multimeter? Or do regulators simply not work when they oscillate? I've been using regulators for years and, to my knowledge, have never had this problem, but these articles have me curious now!

Gerry is correct that the key symptom of instability is (by definition) oscillation, but unfortunately it is not possible to give a simple general description of the impact this will have because there is a wide range of possibilities. The oscillation will vary in both frequency and amplitude depending on the type of regulator and the impedance of the supply. It is also likely to be temperature sensitive.

As was noted in the previous articles, it is LDO (low dropout) regulators that are particularly susceptible to instability, not standard regulators. Also, if the instructions on the datasheet are followed and the correct types and values of capacitors are used, there should not be any problems. If this applies to Gerry then it is not surprising that he has never experienced problems.

Non-functional?

It is possible that the regulator's output will be so far from what it should be that the circuit would be considered non-functional. Although this might be annoying, at its least, it is easy to detect and diagnose. However, an unstable regulator may also oscillate at a low amplitude while maintaining more or less the correct DC level. You may need to look at the supply with an oscilloscope to see this.

An application note from Analog Devices/Analog Integrations Corporation (AIC) titled *Analysis of LDO oscillation issues* (ANO25) (see www.analog.com.tw/DB/doc/app_note/an025.pdf) gives an example waveform for an AIC1730-33 3.3V low-noise 150mA LDO regulator suffering instability. The amplitude of the oscillation is around 400mV and the

frequency is about 170kHz, but remember this is just an example and other unstable regulators will behave differently. For those interested in the mathematical analysis of stability (which we only skimmed over in the *Circuit Surgery* articles) the same application note also provides a pole-zero analysis of an LDO regulator equivalent circuit.

The impact of an LDO oscillating in this way will depend on the nature of the circuit being powered by it. In effect, the oscillations create a high level of power supply noise. As LDO regulators are typically used instead of switching circuits in low noise applications this is quite likely to be a serious problem.

If the oscillation frequency of the regulator is within the range of frequencies processed by the circuit then it is likely that it will be manifested as a strong noise signal in the circuit's output. However, if the oscillation is well outside the circuit's range, it may not be so obvious. This does not mean all is well of course, as there may be other undesirable effects such as increased electromagnetic emissions from the circuit board causing interference elsewhere.

Zeitghost, responding to Gerry's post on the forum, provides an interesting example of a circuit that was apparently OK, but, in fact, was not functioning exactly as it should be due to regulator instability.

I remember a regulator based on the 7663 that oscillated gently at about 20kHz. This didn't matter until the power control for a UHF transmitter changed from being ground referenced to being +5V referenced. It went totally unnoticed until one day I increased the span on a spectrum analyzer and found two sidebands at +/- 20kHz re the carrier.

Bouncing switches

The problem of switch bounce has also been discussed on the *EPE Chat Zone* recently. This is an issue which has frequently confused beginners over the years.

Typically, someone connects a mechanical switch as an input to a logic circuit, presses the switch once and finds the circuit behaving as if the switch has been pressed two or three times. If you don't know that switch contacts bounce, causing the switch to go on and off a few

times before it settles, then this can be quite a perplexing problem.

At first, people suffered from this problem with discrete logic circuits built from 4000 or 74 series or similar devices, but now PIC and other microcontroller-based projects also need to take account of switch bounce. For discrete logic, the problem is often particularly acute if the switch is connected to a clock or other 'edge-triggered' logic input.

Capacitor cure?

Chat Zone user **Turbo46** is aware of the need to debounce switches in his PIC application, but was asking for advice on getting it just right.

I'm currently having a little problem with debouncing a switch. When the switch is pressed, the non-polarised capacitor debounces the switch ok, and the I/O pin goes high. But my problem is the stored voltage in the capacitor holding the I/O pin high for ages. I'm currently using a 100nF capacitor. Should I make the value of my capacitor smaller, or should I use a polarised capacitor or discharge the capacitor?

Fig.1 shows a simple switch and pull-up resistor arrangement, which could be used as the input to a logic circuit, or connected to a microcontroller digital I/O pin configured for an input. A possible waveform for the circuit's output is also shown in Fig.1. Here we see the switch bouncing

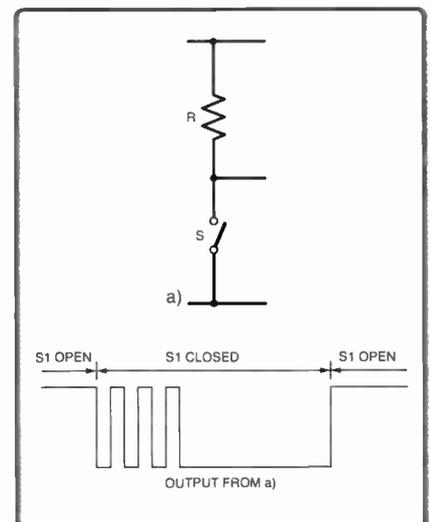


Fig.1. Bouncing switch

three times as the contact is closed, but not as it is opened.

This is not the only possible behaviour – different switches bounce different amounts and at different switch positions. The number of bounces often varies each time an individual switch is used. The duration of bouncing also varies with switch type, but is typically in the range of hundreds of microseconds up to 10ms to 20ms (although even longer bounce times do occur).

The way in which the user actuates the switch – hard/soft fast/slow movement – will also affect bouncing behaviour. A further complication is that during bouncing, the voltage transitions may not cover the full supply range and may therefore take logic inputs into their undefined region (between 0 and 1).

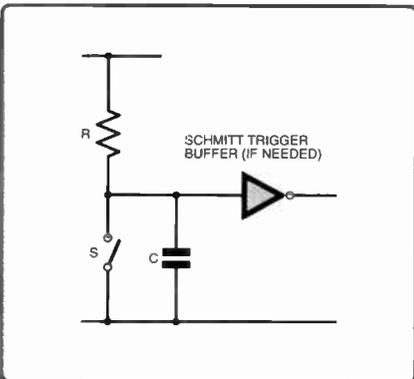


Fig.2. Using a capacitor to debounce a switch

One of the simplest approaches to debouncing is to use a capacitor as shown in Fig.2. This is the arrangement Turbo46 is referring to. The RC time constant should be a little more than the switch bounce time. If it is much greater, then the response of the debouncing switch may be too slow, and the system may be perceived as sluggish by the user.

The slowly rising input signal produced by the circuit in Fig.2 may be a problem for some logic families, and particularly noisy environments may even cause a similar problem to bouncing as noise pushes the input over the logic threshold and back again. This may produce even more unwanted transitions than the original switch bounce. If it is a problem, a Schmitt trigger device can be inserted between the switch and the logic input to produce clean logic switching (as shown in Fig.2).

Another potential problem with the circuit in Fig.2 is when high currents flow in the switch when it is closed. If a relatively large value of capacitor is used, this may degrade the switch over time.

Furthermore, when S is closed, R is connected across the supply and will consume power, so R should be as large as possible to minimise this. So it is best to use a relative large resistor value and a relatively small capacitor value for the RC value required, taking into account the maximum resistor value that will provide a reliable pull-up with the logic technology used.

Additional resistor

A resistor can be placed in series with the capacitor to limit the current as shown in Fig.3, in which case a diode may also

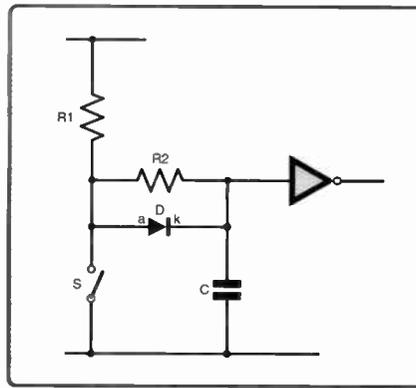


Fig.3. Improved debounce circuit

be required (as shown). If the diode is not present then both R1 and R2 set the RC time constant when the switch is open.

This results in a slower circuit than if just R1 is used. Resistor R1 could be made smaller but this increases the current taken when the switch is closed. A potential problem with this circuit is that logic input leakage current dropped across the resistor may degrade the logic levels.

All this means that the choice of component values for this circuit may be tricky at times, although it should always be possible to get it to work.

An RS flip-flop can also be used to debounce a switch as shown in Fig.4. This requires a changeover switch and two pull-up resistors, but does not require any setting of time constants, and does not suffer from problems with slowly changing inputs.

When the switch changes, any bouncing will simply set or reset the flip-flop multiple times, but this does not matter as only the first set or reset changes the state of the flip-flop. Note that individual switch contacts bounce open and closed, but the switch does not bounce all the way between the two contacts, otherwise this circuit would not work.

Other techniques

When using a microcontroller, switches can be debounced using software. Typically, the code detects a change on the switch and then waits for a bounce delay before checking the switch's state again and acting on the switch press if the state has actually changed.

The code is simple and examples are readily available, but it can be more difficult to do software debounce if a large number of switches are required. In such cases, hardware debouncing using a debounce IC may be preferable.

There are special switch debouncing ICs available, for example from Maxim (www.maxim-ic.com). The MAX 6816, MAX6817 and MAX6818 are single, dual, and octal switch debouncers,

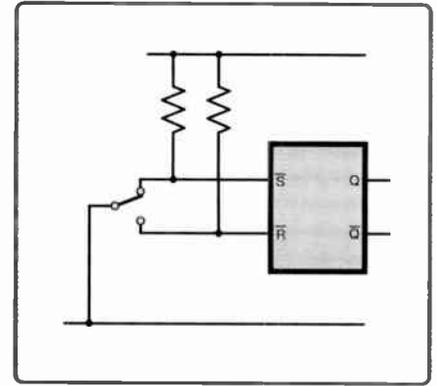


Fig.4. Switch debounce using an RS flip-flop

respectively. The switch inputs on these devices have overvoltage clamping diodes to protect against damaging fault conditions and switch input voltages can safely swing to $\pm 25V$ with respect to ground. A typical circuit using the MAX6816 single switch debouncer is shown in Fig.5.

The MAX6818 monitors eight switches and provides a switch change-of-state output, which indicates if any of the switches have changed state. This simplifies interfacing to a microcontroller, which does not have to do the work of checking to see if each of the individual switches have changed. A typical circuit using the MAX6818 is shown in Fig.6.

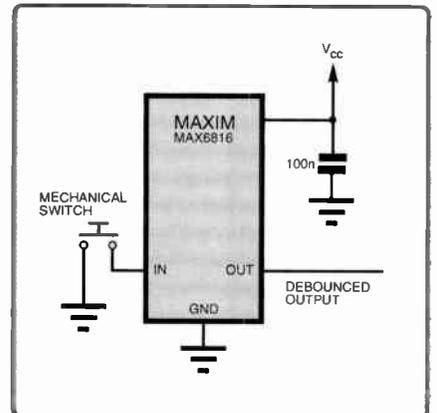


Fig.5. Switch debounce using a MAX 6816 (Maxim datasheet)

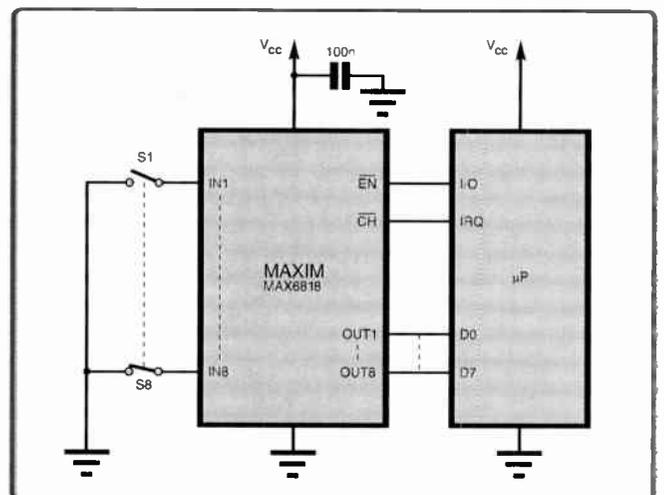


Fig.6. Multiple switch debounce using a MAX6818 (Maxim datasheet)



EPE EVERYDAY PRACTICAL ELECTRONICS



UK readers you can
SAVE 54p
on every issue of *EPE*

How would you like to pay £2.96 instead of £3.50 for your copy of *EPE*?
Well you can – just take out a one year subscription and save 54p an issue,
or £6.50 over the year

You can even save 75p an issue if you subscribe for two years
– a total saving of £18.00

Overseas rates also represent exceptional value

You also

Avoid any cover price increase for the duration of
your subscription

Get your magazine delivered to your door each month

Ensure your copy, even if the newsagents sell out

Order by phone or fax with a credit card or by post with a cheque or postal order, or
buy online from www.epemag.co.uk (click on "Subscribe Now")



EPE SUBSCRIPTION PRICES

Subscriptions for delivery direct to any address in the UK:
6 months £18.75, 12 months £35.50, two years £66; Overseas:
6 months £21.75 standard air service or £30.75 express airmail,
12 months £41.50 standard air service or £59.50 express airmail,
24 months £78 standard air service or £114 express airmail.
Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to *EPE Subs. Dept.*, Wimborne Publishing Ltd., Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at <http://www.epemag.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Maestro or Visa. (For past issues see the *Back Issues* page.)

ONLINE SUBSCRIPTIONS

Online subscriptions, for downloading the magazine via the Internet, \$18.99US (approx. £9.50) for one year available from www.epemag.com.

USA/CANADA SUBSCRIPTIONS

To subscribe to *EPE* from the USA or Canada please telephone Express Mag toll free on 1877 363-1310 and have your credit card details ready. Or fax (514) 355 3332 or write to Express Mag, PO Box 2769, Plattsburgh, NY 12901-0239 or Express Mag, 8155 Larrey Street, Anjou, Quebec, H1J 2L5. Email address: expsmag@expressmag.com. Web site: www.expressmag.com. USA price \$60(US) per annum, Canada price \$97(Can) per annum – 12 issues per year. *Everyday Practical Electronics*, periodicals pending, ISSN 0262 3617 is published twelve times a year by Wimborne Publishing Ltd., USA agent USACAN at 1320 Route 9, Champlain, NY 12919. Subscription price in US \$60(US) per annum. Periodicals postage paid at Champlain NY and at additional mailing offices. POSTMASTER: Send USA and Canada address changes to *Everyday Practical Electronics*, c/o Express Mag., PO Box 2769, Plattsburgh, NY, USA 12901-0239.

SUBSCRIPTION ORDER FORM



- 6 Months: UK £18.75, Overseas £21.75 (standard air service), £30.75 (express airmail)
 - 1 Year: UK £35.50, Overseas £41.50 (standard air service) £59.50 (express airmail)
 - 2 Years: UK £66.00, Overseas £78.00 (standard air service) £114 (express airmail)
- To: *Everyday Practical Electronics*,
Wimborne Publishing Ltd., Sequoia House,
398a Ringwood Road, Ferndown, Dorset BH22 9AU
Tel: 01202 873872 Fax: 01202 874562
E-mail: subs@epemag.wimborne.co.uk

I enclose payment of £ (cheque/PO in £ sterling only), payable to *Everyday Practical Electronics*

My card number is:
Please print clearly, and check that you have the number correct

Signature

Card Security Code (The last 3 digits on or just under the signature strip)

Card Ex. Date Maestro Issue No.

Name


Address

Post code Tel.

Subscriptions can only start with the next available issue.

EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS


ELECTRONICS PROJECTS

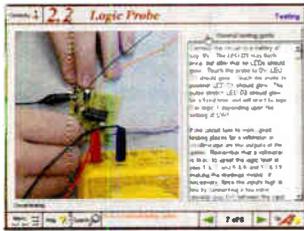

Logic Probe testing

Electronic Projects is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included. The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.

DIGITAL WORKS 3.0

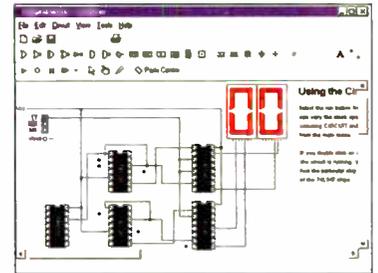

Counter project

Digital Works Version 3.0 is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability

- Software for simulating digital logic circuits
- Create your own macros – highly scalable
- Create your own circuits, components, and i.c.s
- Easy-to-use digital interface
- Animation brings circuits to life
- Vast library of logic macros and 74 series i.c.s with data sheets
- Powerful tool for designing and learning.


ELECTRONIC CIRCUITS & COMPONENTS V2.0



Circuit simulation screen

Provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals**: units & multiples, electricity, electric circuits, alternating circuits. **Passive Components**: resistors, capacitors, inductors, transformers. **Semiconductors**: diodes, transistors, op.amps, logic gates. **Passive Circuits**. **Active Circuits**. **The Parts Gallery** will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.


ANALOGUE ELECTRONICS

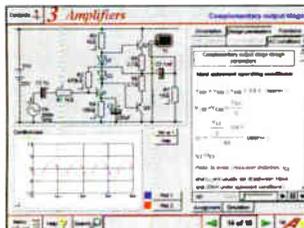

Complimentary output stage

Analogue Electronics is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits. Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections). **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections). **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections). **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.


DIGITAL ELECTRONICS V2.0

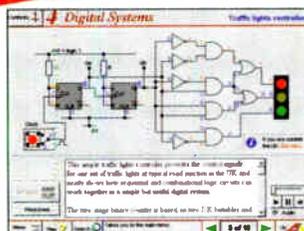

Virtual laboratory – Traffic Lights

Digital Electronics builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (opposite), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen. Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units. Sections on Boolean Logic and Venn diagrams, displays and chip types have been expanded in Version 2 and new sections include shift registers, digital fault finding, programmable logic controllers, and microcontrollers and microprocessors. The Institutional versions now also include several types of assessment for supervisors, including worksheets, multiple choice tests, fault finding exercises and examination questions.

ANALOGUE FILTERS

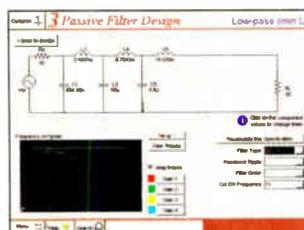

Filter synthesis

Analogue Filters is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev op.amp filters.

ROBOTICS & MECHATRONICS



Case study of the Milford Instruments Spider

Robotics and Mechatronics is designed to enable hobbyists/students with little previous experience of electronics to design and build electromechanical systems. The CD-ROM deals with all aspects of robotics from the control systems used, the transducers available, motors/actuators and the circuits to drive them. Case study material (including the NASA Mars Rover, the Milford Spider and the Furby) is used to show how practical robotic systems are designed. The result is a highly stimulating resource that will make learning, and building robotics and mechatronic systems easier. The Institutional versions have additional worksheets and multiple choice questions.

- Interactive Virtual Laboratories
- Little previous knowledge required
- Mathematics is kept to a minimum and all calculations are explained
- Clear circuit simulations

PRICES

Prices for each of the CD-ROMs above are:

(Order form on third page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student	£45 inc VAT
Institutional (Schools/HE/FE/Industry)	£99 plus VAT
Institutional 10 user (Network Licence)	£249 plus VAT
Site Licence	£499 plus VAT

PICmicro TUTORIALS AND PROGRAMMING


HARDWARE

VERSION 3 PICmicro MCU DEVELOPMENT BOARD

Suitable for use with the three software packages listed below.

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices from the 12, 16 and 18 series PICmicro ranges. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

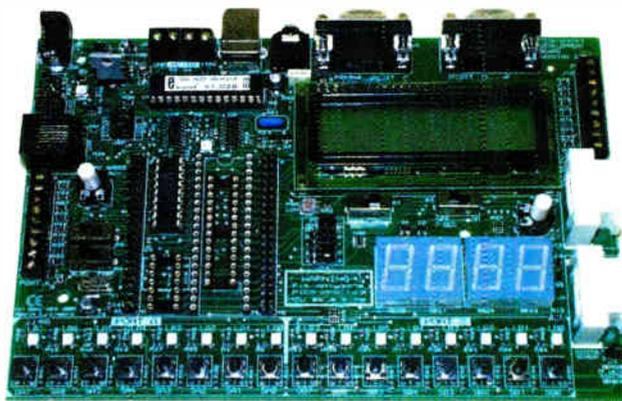- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 16 individual I.e.d.s, quad 7-segment display and alphanumeric I.c.d. display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- USB programmable
- Can be powered by USB (no power supply required)



£158 including VAT and postage, supplied with USB cable and programming software

SPECIAL OFFER


£40 OFF Buy the Development Board together with any Hobbyist/Student or Institutional versions of the software CD-ROMs listed below and take £40 off the total (including VAT) price.

SOFTWARE

ASSEMBLY FOR PICmicro V3 (Formerly PICtutor)

Assembly for PICmicro microcontrollers V3.0 (previously known as PICtutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes. The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller. This is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.

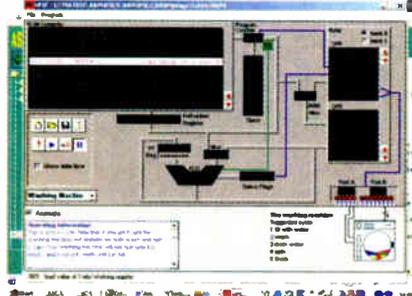

'C' FOR 16 Series PICmicro VERSION 4

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running Windows 98, NT, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.

FLOWCODE FOR PICmicro V3

Flowcode is a very high level language programming system for PICmicro microcontrollers based on flowcharts. Flowcode allows you to design and simulate complex systems in a matter of minutes. A powerful language that uses macros to facilitate the control of devices like 7-segment displays, motor controllers and I.c.d.s. The use of macros allows you to control these devices without getting bogged down in understanding the programming.

Flowcode produces MPASM code which is compatible with virtually all PICmicro programmers. When used in conjunction with the Version 3 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols
- Full on-screen simulation allows debugging and speeds up the development process.

- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- New features in Version 3 include 16-bit arithmetic, strings and string manipulation, improved graphical user interface and printing, support for 18 series devices, pulse width modulation, I2C, new ADC component etc. The Hobbyist/Student version is limited to 4K of code (8K on 18F devices).



PRICES

Prices for each of the CD-ROMs above are:

(Order form on next page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student
Institutional (Schools/HE/FE/Industry)
Institutional/Professional 10 user (Network Licence)
Site Licence
Flowcode 10 user (Network Licence)
Flowcode 50 user (Network Licence)

£45 inc VAT
£99 plus VAT
£300 plus VAT
£599 plus VAT
£350 plus VAT
£699 plus VAT

SPECIAL PACKAGE OFFER

TINA Pro V7 (Basic) + Flowcode V3 (Hobbyist/Student)

TINA Analogue, Digital, Symbolic, RF, MCU and Mixed-Mode Circuit Simulation, Testing and PCB Design

£50.00

including VAT and p&p

TINA Design Suite is a powerful yet affordable software package for analysing, designing and real time testing analogue, digital, MCU, and mixed electronic circuits and their PCB layouts. You can also analyse RF, communication, optoelectronic circuits, test and debug microcontroller applications.

Enter any circuit (up to 100 nodes) within minutes with TINA's easy-to-use schematic editor. Enhance your schematics by adding text and graphics. Choose components from the large library containing more than 10,000 manufacturer models. Analyse your circuit through more than 20 different analysis modes or with 10 high tech virtual instruments. Present your results in TINA's sophisticated diagram windows, on virtual instruments, or in the live interactive mode where you can even edit your circuit during operation.

Customise presentations using TINA's advanced drawing tools to control text, fonts, axes, line width, colour and layout. You can create, and print documents directly inside TINA or cut and paste your results into your favourite word-processing or DTP package.

TINA includes the following Virtual Instruments: Oscilloscope, Function Generator, Multimeter, Signal Analyser/Bode Plotter, Network Analyser, Spectrum Analyser, Logic Analyser, Digital Signal Generator, XY Recorder.

Flowcode V3 (Hobbyist/Student) – For details on Flowcode, see the previous page.

This offer gives you two separate CD-ROMs in DVD style cases – the software will need registering (FREE) with Designsoft (TINA) and Matrix Multimedia (Flowcode), details are given within the packages.

Get TINA + Flowcode for a total of just £50, including VAT and postage.

PROJECT DESIGN WITH CROCODILE TECHNOLOGY

An Interactive Guide to Circuit Design

An interactive CD-ROM to guide you through the process of circuit design. Choose from an extensive range of input, process and output modules, including CMOS Logic, Op-Amps, PIC/PICAXE, Remote Control Modules (IR and Radio), Transistors, Thyristors, Relays and much more. Click Data for a complete guide to the pin layouts of i.c.s, transistors etc. Click More Information for detailed background information with many animated diagrams.

Nearly all the circuits can be instantly simulated in Crocodile Technology* (not included on the CD-ROM) and you can customise the designs as required.

WHAT'S INCLUDED

Light Modules, Temperature Modules, Sound Modules, Moisture Modules, Switch Modules, Astables including 555, Remote Control (IR & Radio), Transistor Amplifiers, Thyristor, Relay, Op-Amp Modules, Logic Modules, 555 Timer, PIC/PICAXE, Output Devices, Transistor Drivers, Relay Motor Direction & Speed Control, 7 Segment Displays. Data sections with pinouts etc., Example Projects, Full Search Facility, Further Background Information and Animated Diagrams.

Runs in Microsoft Internet Explorer

*All circuits can be viewed, but can only be simulated if your computer has Crocodile Technology version 410 or later. A free trial version of Crocodile Technology can be downloaded from: www.crocodile-clips.com. Animated diagrams run without Crocodile Technology.

Single User £39.00 inc. VAT.

Multiple Educational Users (under 500 students) £59.00 plus VAT. Over 500 students £79.00 plus VAT.

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)



THE AMATEUR SCIENTIST

3.0

The complete collection of The Amateur Scientist articles from *Scientific American* magazine. Over 1,000 classic science projects from a renowned source of winning projects. All projects are rated for cost, difficulty and possible hazards. Plus over 1,000 pages of helpful science techniques that never appeared in *Scientific American*.



Exciting science projects in: Astronomy; Earth Science; Biology; Physics; Chemistry; Weather . . . and much more! The most complete resource ever assembled for hobbyists, and professionals looking for novel solutions to research problems. Includes extensive Science Software Library with even more science tools. Suitable for Mac, Windows, Linux or UNIX. 32MB RAM minimum, Netscape 4.0 or higher or Internet Explorer 4.0 or higher. Over 1,000 projects.

Price £19.95 inc. VAT

ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 JPG images of electronic components. This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details).



Also contains a FREE 30-day evaluation of Paint Shop Pro 6 – Paint Shop Pro image editing tips and on-line help included!

Price £19.95 inc. VAT

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space, Windows 95/98/NT/2000/ME/XP, mouse, sound card, web browser.

Please send me:

CD-ROM ORDER FORM

- Electronic Projects
- Electronic Circuits & Components V2.0
- Analogue Electronics
- Digital Electronics V2.0
- Analogue Filters
- Digital Works 3.0
- Robotics & Mechatronics
- Assembly for PICmicro V3
- 'C' for 16 Series PICmicro V4
- Flowcode V3 for PICmicro
- The Amateur Scientist 3.0

Version required:

- Hobbyist/Student
- Institutional
- Institutional/Professional 10 user
- Site licence



- PICmicro Development Board V3 (hardware)

- TINA Pro V7 Basic + Flowcode V3 Hobbyist/Student
- Electronic Components Photos
- Project Design – Single User
- Project Design – Multiple User (under 500 students)
- Project Design – Multiple User (over 500 students)

Note: The software on each version is the same, only the licence for use varies.

Full name:

Address:

.....Post code:Tel. No:

Signature:

I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

Please charge my Visa/Mastercard/Amex/Diners Club/Switch: £

Valid From:Card expiry date:

Card No:Maestro Issue No.

Card Security Code (The last 3 digits on or just under the signature strip)

ORDERING

ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world. EU residents outside the UK add £5 for airmail postage per order.

Institutional, Multiple User and Deluxe Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU (European Union) country, then add 17.5% VAT or provide your official VAT registration number)

Send your order to:

Direct Book Service

Wimborne Publishing Ltd

Sequoia House, 398a Ringwood Road

Ferndown, Dorset BH22 9AU

To order by phone ring

01202 873872. Fax: 01202 874562

Goods are normally sent within seven days

E-mail: orders@wimborne.co.uk

Online shop:

www.epemag.wimborne.co.uk/shopdoor.htm

Play your part in reducing energy use at home

Standby Power Saver

By JOHN BECKER



Readers will be aware that internationally active measures are being taken to conserve energy. One such source of energy consumption is from TVs and other domestic items being left in Standby mode. It is perhaps human nature that most of us use this option, preferring the more instantaneous revitalising of the TV rather than turning it off when not needed, and then having to wait while it warms up again. It also saves getting up out of the chair to physically switch it off!

PCs are other culprits that are left in standby rather than being turned off. The reason here is more fundamental. A procedure has to be entered each time we wish to turn off a PC, and there is the fairly lengthy time that it takes to reboot back into working mode.

There are other household appliances that have a standby option as well.

The unit presented here offers an answer to the standby problem of TVs and other devices, but not to that associated with PCs.

Handset options

Basically the design consists of two units, one handheld, the other mains powered and connected to the TV or other appliance between its normal plug and the mains socket. Communication between the units is by radio frequency (RF) at the UK legal frequency of 433MHz, using ready-made and readily available transmitter/receiver modules. This means that a radio transmitting license is not required in the UK.

At its basic level, the system comprises one transmitting module controlling a single receiving unit. It is possible, though, to use a single controller to control up to 64 receiving modules, jointly or independently.

This possibility allows households with more than one TV etc (but not PCs, as mentioned) to be all controlled by the same transmitter. The range is up to about 70 metres, so will penetrate through the rooms and ceilings of most houses. The main unit can thus be

kept in one room and appliances in other rooms controlled from the same place.

Each controlled unit is allocated an independent ID code, between 0 and 63, set by the user with link wires on the PCB (printed circuit board), or using switches. The controller then, by means of switches, selects the ID code of the unit it wishes to control.

Receiver units also have an independent push-switch allowing the transmitted setting to be over-ridden and the unit turned on and off directly.

Appliances have their mains power switched on and off by means of a relay in the receiving unit. The receiving unit is plugged into the mains supply, and the appliance then plugged into the receiver. The relay is basically designed to switch up to 5A AC, but it may be changed to another capable of switching greater currents.

It is stressed that the assembly of the mains aspect of the receivers must only be done by someone suitably competent at doing so. Mains electricity is potentially hazardous and can kill.


Transmitter

The complete circuit diagram for the transmitting (Tx) unit is shown in Fig.1. It is under control of PIC microcontroller IC1. At any time the mode under which it operates is set by S2 to S4. The individual ID code that it transmits is set by the bank of six DIL switches jointly labelled S5.

To control a single receiving unit, Apparatus On or Off switch S4 is switched appropriately, and S2, the Named Unit switch, is pressed.

The PIC sends a basic general ID code first. This minimises the risk that other transmitters in the neighbourhood operating on the same 433MHz frequency will interfere. This ID code may be selected by the user to be any value between 64 and 127 (more on this later).

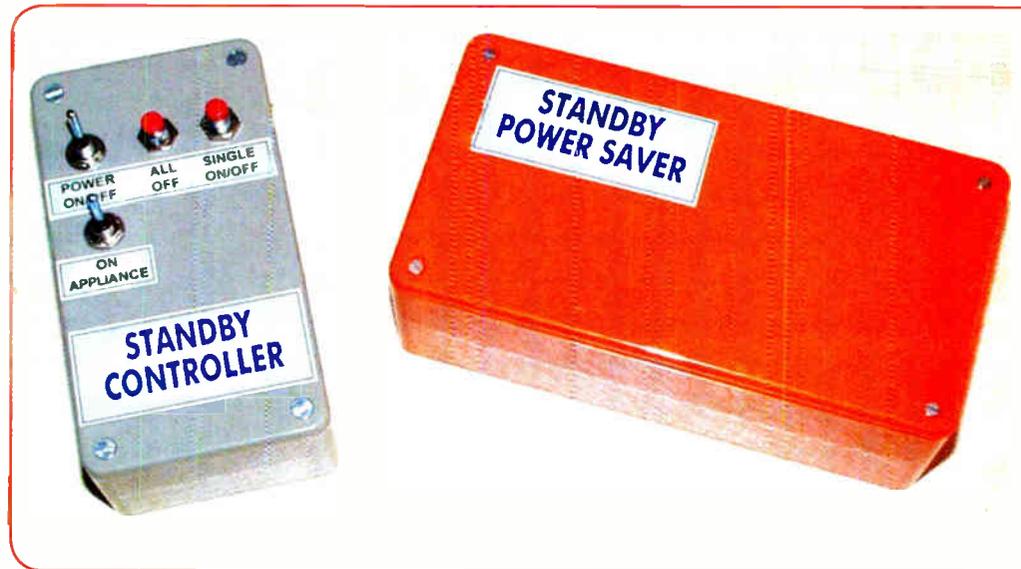The PIC then sends the ID of the unit to be controlled, a user selected value



The completed prototype transmitter (left) and receiver (right) modules that make up the Standby Power System. Not shown on the receiver unit are the Main ID and Unit On/Off pushbutton switches (S6 and S7)

between 0 and 63. To this value is added the status of switch S4, zero for Turn Power Off, or 128 for Turn Power On.

The PIC's signals are sent to the transmitter module, IC2, an RF Solutions type AM-TX1-433 (also available from RS Components Ltd as stock

number 310-9891). Data transfer rate is at 4800 Baud.

On receipt of both ID codes, the desired receiver unit then performs the task required.

To control all possible 64 units simultaneously, switch S3 is pressed

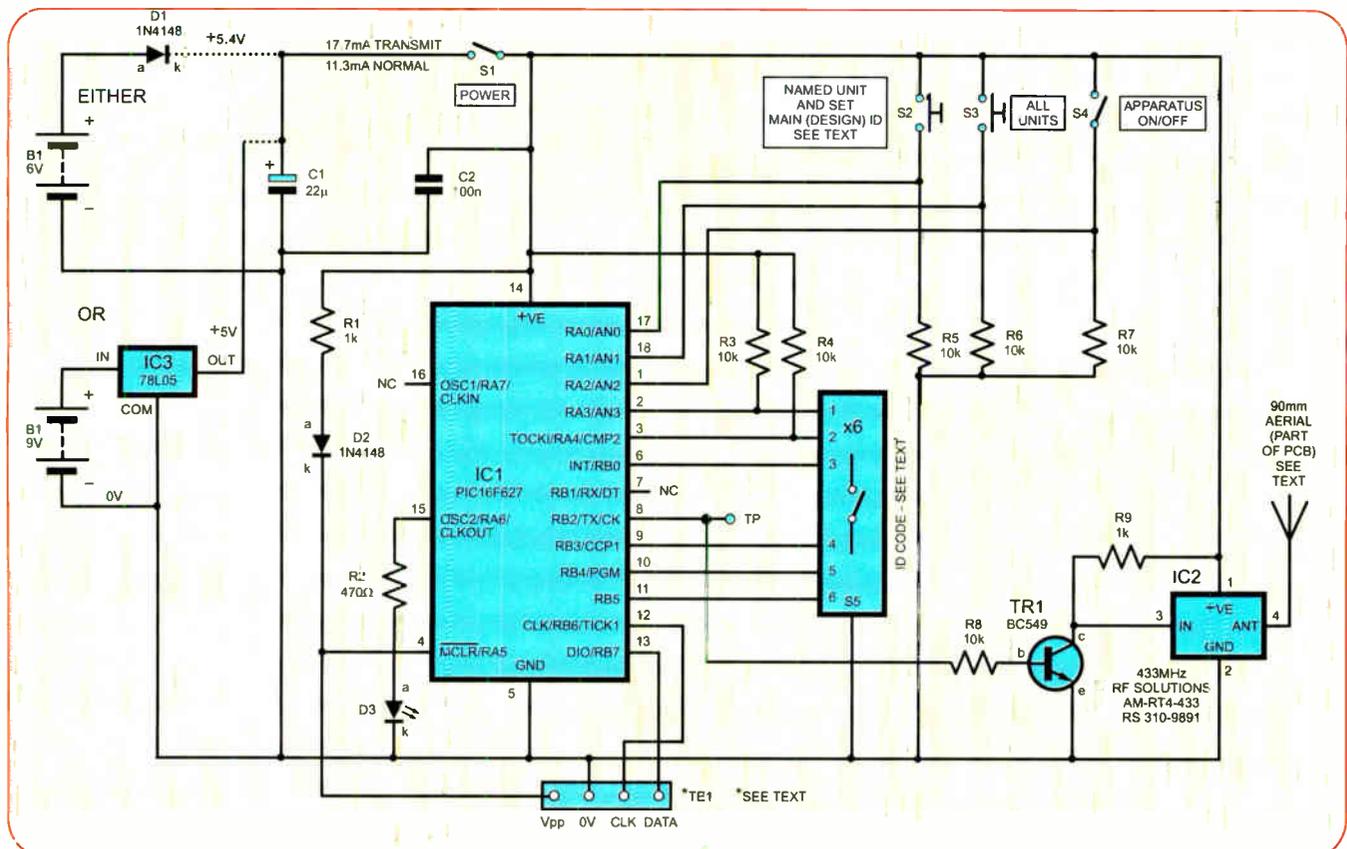


Fig.1. Circuit diagram for the Standby Power Saver transmitter. There are two power supply options – see text

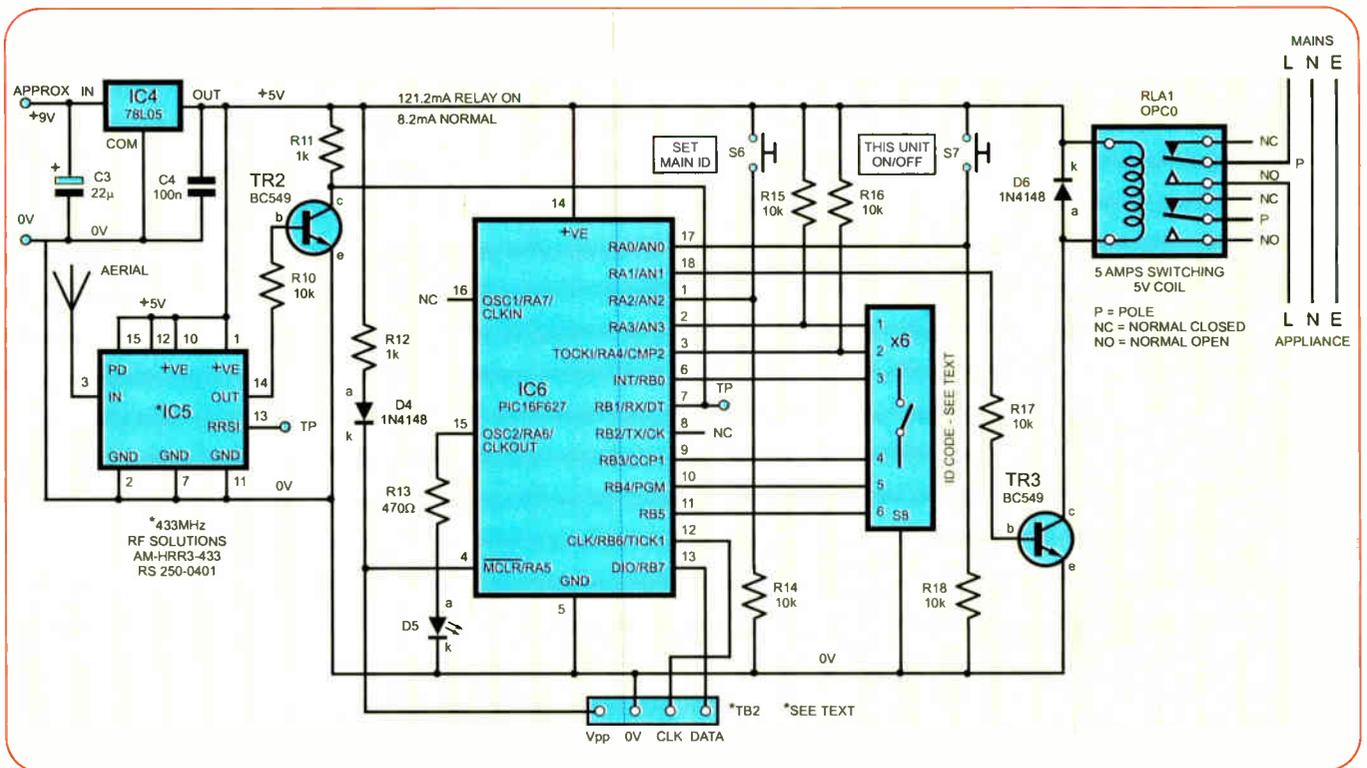


Fig.2. Circuit diagram for the remote receiver section of the Standby Power Saver

and again the PIC sends a main ID code and a unit ID which commences at 0 and increments up to 63. Any unit which receives the main ID and its individual ID code, again performs the task required.

LED D3 is turned on during transmission, and turned off again at the end, so the user knows when the process is complete. Even when sending all 64 codes, the cycle time is only about one second.

Receiver

The circuit diagram for the receiving (Rx) unit is shown in Fig.2. The circuit comprises receiver module IC5, an RF Solutions type AM-HRR3-433 (also available from RS Components Ltd as stock number 250-401), PIC microcontroller IC6, and a few peripheral components, including the 5A AC relay, RLA1.

The receiver sends any received codes to the PIC, which assesses whether or not they have the appropriate main and individual unit IDs. Both of these are determined by the bank of six switches, or link wires, S8 (more on this later). If the codes are valid, the PIC then switches transistor TR3, and thus the relay, on or off as

required. Diode D6 inhibits any back-EMF pulse generated at the moment the relay is switched off.


The relay is a PCB-mounted two-pole changeover type rated for switching up to 5A. Both Live and Neutral appliance lines may be jointly switched as required. LED D5 is turned on when the relay is switched on.

Switch S7 allows the relay to be manually switched on or off as required.

Switch bank S8 is used when the receiver's ID is to be set by S6.

Both units

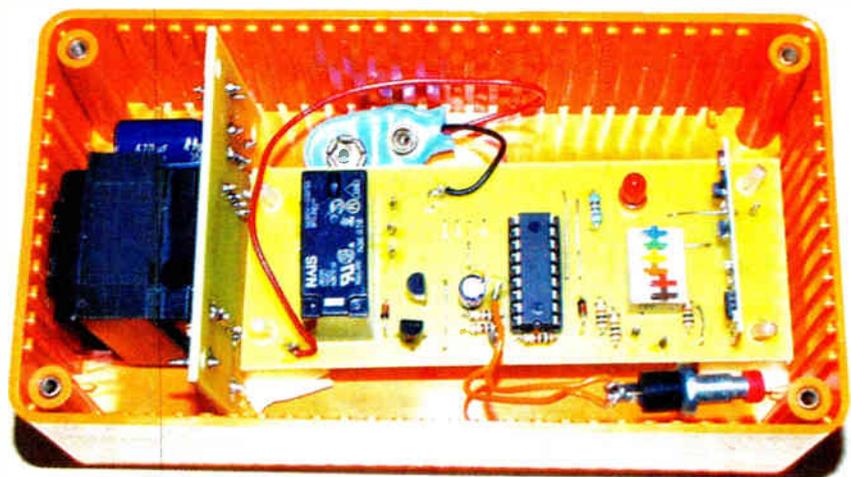The PICs operate at 4MHz, as set by their own internal oscillator. Communication between transmitter and receiver is at 4800 Baud. Both PIC units are powered at +5V, derived from a basic 9V supply, which is regulated down to +5V by regulators IC3 (Tx) and IC4 (Rx).



Layout of components, including optional mains power supply, inside a partially completed receiver unit

Parts List – Standby Power Saver

TRANSMITTER

- 1 PC board, code 639 (Trans) available from the *EPE PCB Service*, size 96mm x 38mm
- 1 plastic case, size and type to individual choice
- 1 433MHz AM radio transmitter module, type AM-RT4-433 (RF Solutions) (IC2)
- 2 miniature SPST toggle switches (S1, S4)
- 2 miniature push-to-make SP pushbutton switches (S2, S3)
- 1 6-way DIL switch or six SPST toggle switches – see text (S5)
- 1 12-pin DIL socket – see text
- 1 18-pin DIL socket
- Multistrand connecting wire; battery to suit – see text; solder etc.

Semiconductors

- 2 1N4148 signal diodes (D1, D2)
- 1 3mm red LED (D3)
- 1 BC549 NPN transistor, or similar small-signal type (TR1)
- 1 PIC16F627-4 preprogrammed microcontroller (IC1). (Ready-programmed PICs are available from Magenta Electronics – see their advert)
- 1 78L05 +5V 100mA voltage regulator (IC3)

Capacitors

- 1 22 μ F radial elect., 16V (C1)
- 1 100nF ceramic disc, 5mm pitch (C2)

Resistors (0.25W 5% carbon)

- 6 10k (R3 to R8)
- 2 1k (R1, R9)
- 1 470 Ω (R2)

RECEIVER

- 1 PC board, code 640 (Rec), available from the *EPE PCB Service*, size 104mm x 38mm
- 1 plastic case, size and type to individual choice
- 1 433MHz AM radio receiver module, type AM-HRR3-433 (RF Solutions) (IC5)
- 1 DPCO PC-mounting DIL relay; 5A AC switching, 5V coil (RLA1)
- 2 miniature push-to-make SP pushbutton switches (S6, S7)
- 1 6-way DIL switch or link wires – see text (S8)
- 1 12-pin DIL socket – see text
- 1 18-pin DIL socket
- Multistrand connecting wire; 9V power source – see text; solder etc.

Semiconductors

- 2 1N4148 signal diodes (D4, D6)
- 1 3mm red LED (D5)
- 1 BC549 NPN transistor, or similar small-signal type (TR2, TR3)
- 1 78L05 +5V 100mA voltage regulator (IC4)
- 1 PIC16F627-4 preprogrammed microcontroller (IC6). (Ready-programmed PICs are available from Magenta Electronics – see their advert)

Capacitors

- 1 22 μ F radial elect., 16V (C3)
- 1 100nF ceramic disc, 5mm pitch (C4)

Resistors (0.25W 5% carbon)

- 6 10k (R10, R14 to R18)
- 2 1k (R11, R12)
- 1 470 Ω (R13)

9V PSU (Optional)

- 1 PC board, code 641 (PSU), available from the *EPE PCB Service*, size 76mm x 38mm
- 1 230V AC mains transformer, with 6.3V AC 100mA minimum secondary (T1)
- 1 50V 1A bridge rectifier (REC1)
- 1 1A fuse and chassis fuseholder (FS1)
- Mains cable, plug and socket to suit; solder pins; solder etc.

With the Tx unit, it is intended that a PP9 9V battery is used, although a 6V battery could be used instead. In this latter case diode D1 reduces that voltage to below the maximum allowed for the PIC (5.5V) and regulator IC3 is then omitted.

For the Rx unit, the power may be supplied by a PP3 9V battery, or via the simple PSU shown in Fig.3.

Connector blocks TB1 and TB2 allow the PICs to be programmed when installed on the PCBs if preferred. The pins are in the author's usual configuration. The software is available from the 'Downloads' section of the *EPE* website.

Rx PSU

The circuit diagram for the simple 9V DC power supply (PSU) is shown in Fig.3. It is intended that the same mains supply as is controlled for the appliance should be used.

Transformer T1 steps down the mains voltage (230V AC in the UK) to 6.3V AC. This is rectified by REC1, smoothed by capacitors C1 and C2, from which approximately 9V DC is available for the Rx unit.

Assembly

There are three printed circuit boards (PCBs) for this design. They are available from the *EPE PCB Service*, codes 639 (Tx), 640 (Rx), 641 (PSU). Only one Tx PCB is needed. For the Rx units, an Rx PCB is needed for each controlled appliance, plus a PSU PCB if required.

The circuit board assemblies and full-size copper tracking details are shown in Fig.4, Fig.5 and Fig.6. As said earlier, the mains aspects of this design must only be assembled by those who are competent to do so.

Assemble the PCBs in order of component assembly size, starting with the on-board wire links. Use sockets for the dual-in-line (DIL) ICs, and observe the correct polarity for all electrolytic capacitors and semiconductors. Do not

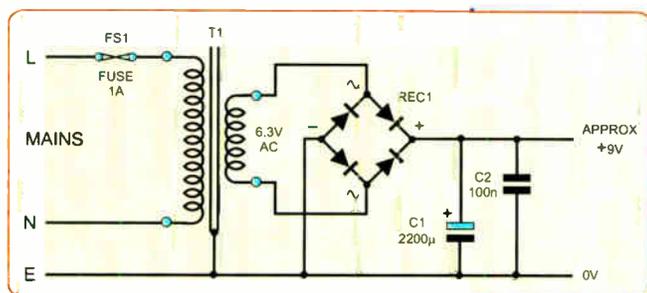


Fig.3. Suggested mains power supply circuit

TRANSMITTER BOARD


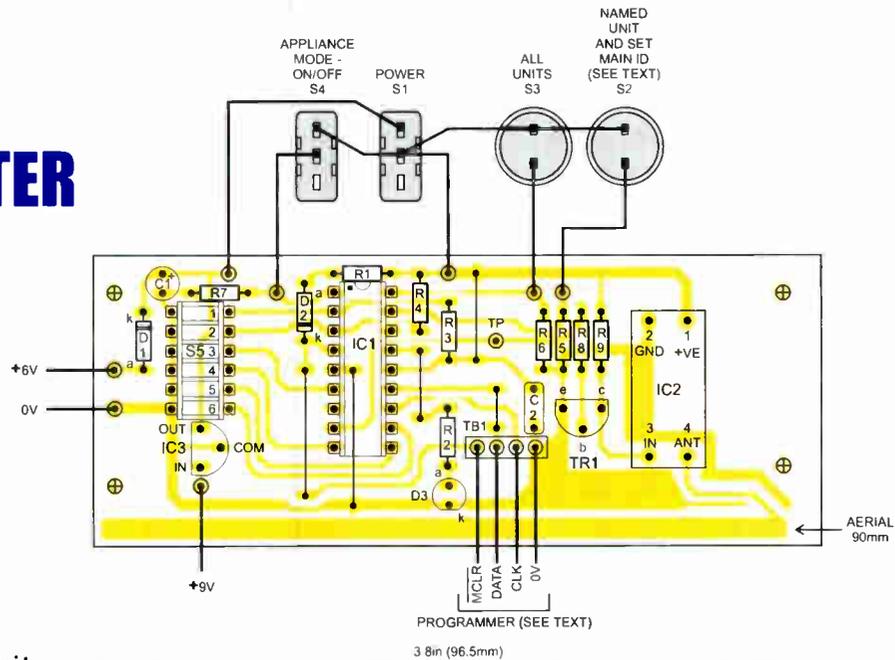


Fig.4: Printed circuit board topside component layout, interwiring details and full-size underside copper foil master for the transmitter unit

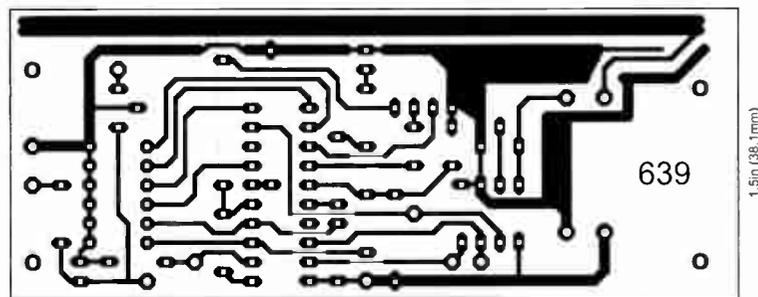

RECEIVER BOARD



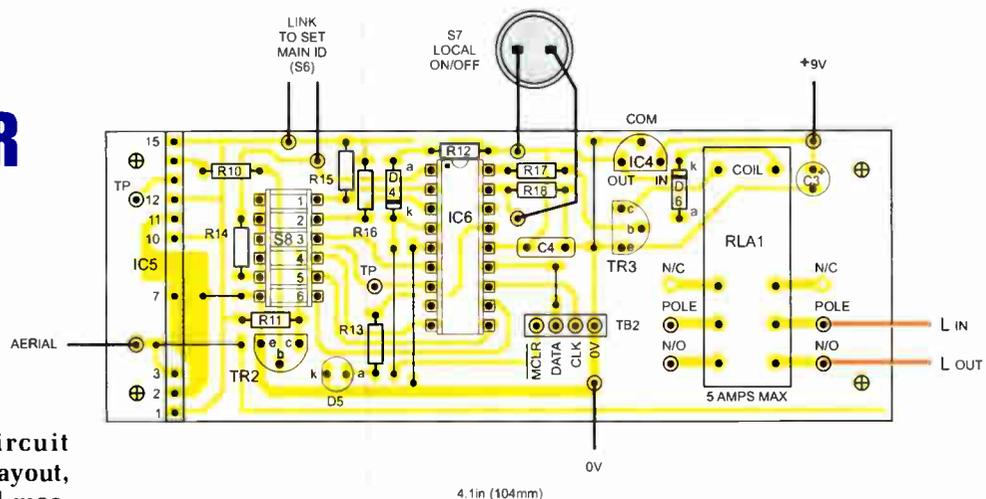


Fig.5: Printed circuit board component layout, full-size copper foil master and wiring details for a single receiver unit. You will, of course, require a receiver for each additional appliance. Note the relay contacts must be rated according to the appliance being controlled

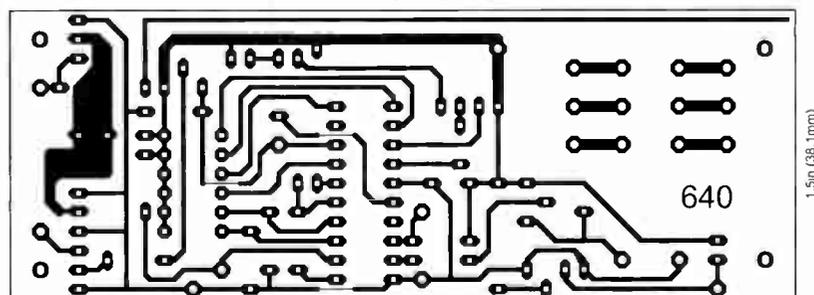

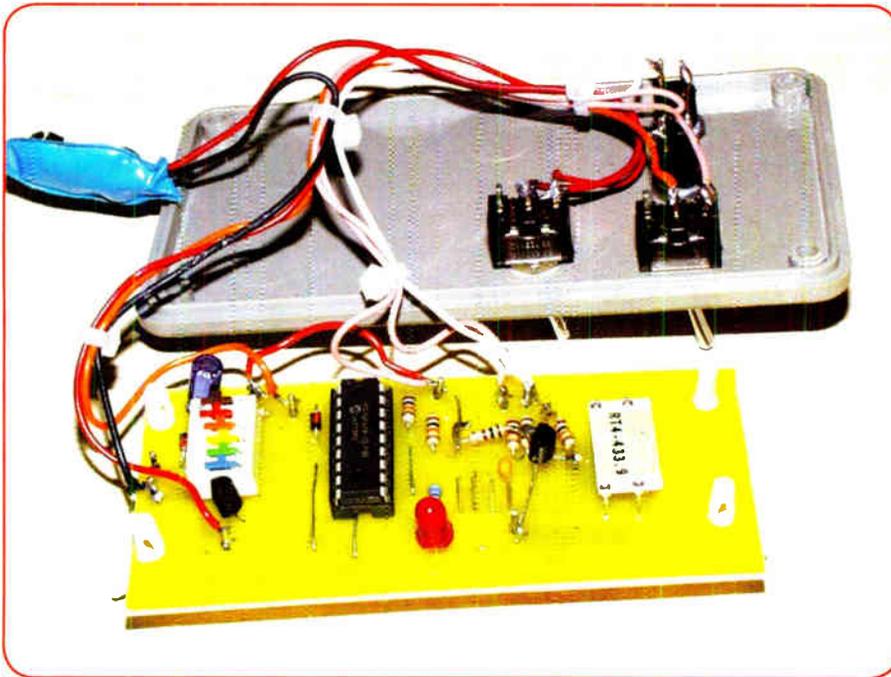

Prototype transmitter circuit board and function switches mounted on the lid of the case

insert the DIL ICs until the correctness of the assembly and the power lines has been fully checked.

It is up to the user to decide whether Tx switch S5 is a DIL type mounted on the PCB, or separate SP toggle switches mounted on the top of the case. All Rx units may use link wires to set the required ID codes if desired.

The aeriels are part of the PCB tracks. The aerial for the transmitter

must not have its length changed in order to comply with regulations associated with the licence-free transmitter module. The receiver aerial can be extended if preferred.

Just an ordinary plastic case was used for the prototype Tx unit. If preferred, a more sophisticated handheld case appropriate to TV control units may be used.

A plastic case must also be used for the Rx unit, ensuring that mains

voltages cannot appear on external surfaces or switches etc. If the PSU PCB is used, keep a reasonable distance between it and the Rx PCB. Mains cable must enter and leave the case by suitable locking grommets, and be terminated by suitable mains plugs and sockets.

If a different relay to the PCB mounting one suggested for the Rx unit is used, it must be adequately secured to the case side if it is not suitable for the DIL PCB mounting holes provided.

Setting ID codes

If just a single Tx/Rx units pair is used, it is not necessary to set an individual ID code. Just ensure that switches S5 and S8 are set so that their PIC-connected pins are at 5V. This sets the ID code to a fixed value of 0 for the Main ID and 127 for the individual IDs. If you think that no-one in your neighbourhood might have a transmitter whose frequency may interfere with your receiver, then the Main ID code does not need setting.

However, if you discover that there is another transmitter upsetting the system. The Main ID code can be altered as follows:

Switch off power to the units and allow a few seconds for the smoothing capacitors to discharge.

For the Tx module, set the switches in S5 to the binary code of the Main ID you want between 0 and 63. The PIC automatically adds 64 to that value.

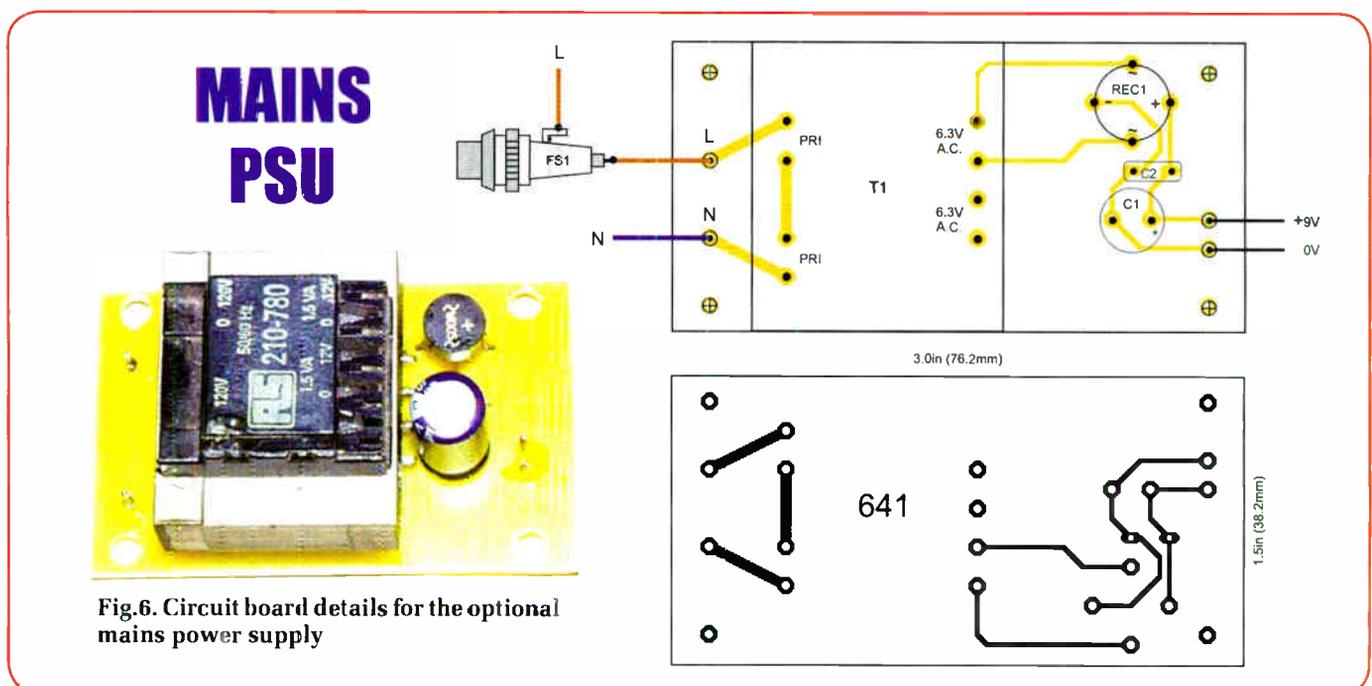


Fig.6. Circuit board details for the optional mains power supply

Constructional Project

Press S2 and hold it pressed while power is switched on. Wait a couple of seconds and switch it off again. The Main ID code is now stored in the PIC's Data EEPROM for future recall.

For each Rx module, with the power off again, set the switches in S8 to the same binary code as set into the Tx module. Then press S6 and hold it pressed while power is reapplied for a couple of seconds or so. Then switch it off. The Main ID code is again stored in the PIC's Data EEPROM for future recall. Should you wish to change the Main ID at a later time, follow the same procedure.

For individual Rx modules, their specific ID codes can be changed at any time without any procedure, simply setting the binary switch or linking wires to the code required. When receiving data, the Rx modules only respond to that arriving and having the same specific ID.

Similarly with the Tx module, simply set the binary switches to the value for any particular Rx module. That code is then automatically sent when the Tx switch S2 is used.

Standby cost to the environment

Searching via www.google.com shows many sites relating to the costs

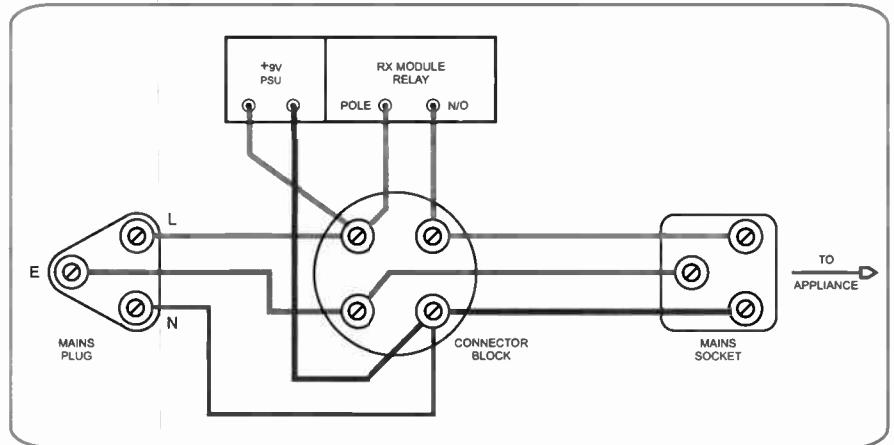


Fig.7. Suggested wiring arrangement linking the receiver unit between the mains supply and the appliance to be controlled

to the environment of leaving TVs and other equipment in Standby mode.

The actual figures quoted vary slightly but are typically in the region of 24% of total TV and 50% of total VCR energy use. The average TV on standby consumes about 5W, drawing about 90% of normal energy.

Figures include the fact that 1TWh (terawatt/hour) of energy is lost annually and 800,000 tonnes of carbon are emitted to generate it. CO₂ emis-

sions amount to the equivalent of 1.4 million long-haul flights. The average household has up to 12 gadgets left on standby or charging at any one time.

It is acknowledged that this design also uses energy, but that use is far less than that required by an appliance in standby mode. Even when batteries are used, there is still a cost to the environment by manufacturing them.

But it still makes sense to minimise the use of Standby mode. **EPE**

PCB-POOL®

SERVICING YOUR COMPLETE PROTOTYPE NEEDS

1 EUROCARD
(160 x 100 mm)
+ Tooling
+ Photoplots
+ VAT

€49

Price example
Any size and contour possible!

Optional:

- Soldermask
- Fast-turnaround
- Silkscreen
- 4-Layer Multilayer
- 6-Layer Multilayer

DOWNLOAD OUR FREE LAYOUT SOFTWARE!

Over **18,000** Customers

LEAD FREE

Freephone **0800-3898560**

Tel: +353 (0)61 701170
Fax: +353 (0)61 701165
pcb-pool@bt.com

Simply send your files and order ONLINE: **PCB-POOL.COM**

www.rkeducation.co.uk
solutions for teaching and learning

New Products

RKP18HighPower


A PCB suitable for a wide range of applications including DC motor control. The board has 5 inputs and 8 outputs, each output is a high power TO220 FET with a protection diode and 2 way terminal block
Unpopulated PCB £2.50 - Populated System £6.50

RKP18Relay

A PCB that is perfect when relays are being used. The PCB has 2 relays, the user can select either internal or external power. The PCB also has 5 inputs, 2 digital outputs and 4 high power outputs making this a very flexible product
Unpopulated PCB £2.50 - Populated System £6.50
These have been designed to use 18 pin PIC® and PICAXE® chips and they have a PICAXE® boatloader socket and circuit included

Other PCBs for 8 + 18pin PIC®/PICAXE® chips from 75p
We also stock a range of training/development systems for PIC® and PICAXE® chips starting from £5.00 fully populated

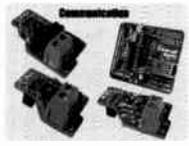*Please check for details Prices exclude VAT
rkeducation@hotmail.com Fax: 01262 410154
www.rkeducation.co.uk



- CAN-1 Board** - Interface CAN via MCP2551
- CANSPI Board** - Make CAN network with SPI interface
- RS485 Board** - Connect devices into RS-485 network
- Serial Ethernet** - Make ethernet network with SPI interface (ENC28J60)
- IrDA2 Board** - IrDA2 serve as wireless RS232 communication between two MCUs.



- CF Board** - Easy way to use Compact flash in your design.
- MMC/SD Board** - Easy way to use MMC and SD cards in your design.
- EEPROM Board** - Serial EEPROM board via I2C interface.
- RTC Board** - PCF8593 RTC with battery backup.



- ADC Board** - 12-bit analog-to-digital converter (ADC) with 4 inputs.
- DAC Board** - 12-bit digital-to-analog converter (DAC) with SPI.
- Keypad 4x4 Board** - Add keypad to your application.
- Accel. Board** - Accel. is an electronic device that measures acceleration forces.

PICFlash with mikroCD support



PICFlash programmer - an ultra fast USB 2.0 programmer for the PIC microcontrollers. Continuing its tradition as one of the fastest PIC programmer on the market, it now PICFlash with mikroCD now supports more PIC MCUs giving developer a wider choice of PIC MCU for further prototype development. mikroCD debugger enables you to execute mikroC / mikroBasic / mikroPascal programs on the host PIC microcontroller and view variable values, Special Function Registers (SFR), memory and EEPROM while the program is running.

- All of our products are shipped in special protective boxes.
- On-line secure ordering provides fast and safe way of buying our products.

EasyPIC4 Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroCD



Following tradition of its predecessor EasyPIC3 as one of the best PIC development systems on the market, EasyPIC4 has more new features for the same price. The system supports 8-, 14, 18, 20, 28 and 40 pin PIC microcontrollers (it comes with PIC16F877A). USB 2.0 on-board programmer with mikroCD (In-Circuit Debugger) enables very efficient debugging and faster prototype development. Examples in C, BASIC and Pascal language are provided with the board.

LV24-33 Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroCD



System supports 64, 80 and 100 pins PIC24F/24H/dsPIC33F microcontrollers (it comes with PIC24FJ64GA010 - PIC24 16-bit Microcontroller, 96 KB Flash Memory, 8 KB RAM in 100 Pin Package). Examples in BASIC, PASCAL and C are included with(in) the system. You can choose between USB and External Power supply. LV 24-33 has many features that make your development easy. USB 2.0 on-board programmer with mikroCD (In-Circuit Debugger) enables very efficient debugging and faster prototype development.

PICPLC16B Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroCD



PICPLC16B is a system designed for controlling industrial systems and machines. 16 inputs with optocouplers and 16 relays (up to 10A) can satisfy many industrial needs. The ultra fast mikroCD (In-Circuit Debugger) enables very efficient debugging and faster prototype development. Features : RS485, RS232, Serial Ethernet, USB 2.0 on-board programmer and mikroCD (In-Circuit Debugger) on-board.

mikroElektronika Compilers

Pascal, Basic and C Compilers for various microcontrollers



Supporting an impressive range of microcontrollers, an easy-to-use IDE, hundreds of ready-to-use functions and many integrated tools makes MikroElektronika compilers one of the best choices on the market today. Besides mikroCD, mikroElektronika compilers offer a statistical module, simulator, bitmap generator for graphic displays, 7-segment display conversion tool, ASCII table, HTML code export, communication tools for SD/MMC, UDP (Ethernet) and USB, EEPROM editor, programming mode management, etc.

Each compiler has many routines and examples such as EEPROM, FLASH and MMC, reading/writing SD and CF cards, writing character and graphics on LCDs, manipulation of push-buttons, 4x4 keyboard and PS/2 keyboard input, generation of signals and sounds, character string manipulation, mathematical calculations, I2C, SPI, RS232, CAN, USB, RS485 and OneWire communications, Manchester coding management, logical and numerical conversion, PWM signals, interrupts, etc. The CD-ROM contains many already-written and tested programs to use with our development boards.


mikroElektronika manufactures competitive development systems. We deliver our products across the globe and our satisfied customers are the best guarantee of our first-rate service. The company is an official consultant on the PIC microcontrollers and the third party partner of Microchip company. We are also an official consultant and third party partner of Cypress Semiconductors since 2002 and official consultant of Philips Electronics company as well. All our products are RoHS compliant.

<http://www.mikroe.com/en/distributors/>

Find your distributor: UK, USA, Germany, Japan, France, Greece, Turkey, Italy, Slovenia, Croatia, Macedonia, Pakistan, Malaysia, Austria, Taiwan, Lebanon, Syria, Egypt, Portugal, India.

Uni-DS 3 Development Board

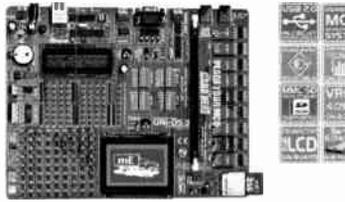Complete Hardware and Software solution with on-board USB 2.0 programmer



The system supports PIC, AVR, 8051, ARM and PSoC microcontrollers with a large number of peripherals. In order to continue working with different chip in the same development environment, you just need to switch a card. UNI-DS3 has many features that make your development easy. You can choose between USB or External Power supply. Each MCU card has its own USB 2.0 programmer!

EasysdsPIC4 Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroCD



The system supports 18, 28 and 40 pin microcontrollers (it comes with dsPIC30F4013 general purpose microcontroller with internal 12-bit ADC). EasysdsPIC4 has many features that make your development easy. Many of these already made examples in C, BASIC and PASCAL language guarantee successful use of the system. Ultra fast USB 2.0 on-board programmer and mikroCD (In-Circuit Debugger) enables very efficient debugging and faster prototype developing.

EasyARM Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer



EasyARM board comes with Philips LPC2214 microcontroller. Each jumper, element and pin is clearly marked on the board. It is possible to test most of industrial needs on the system: temperature controllers, counters, timers etc. EasyARM has many features making your development easy. One of them is on-board USB 2.0 programmer with automatic switch between 'run' and 'programming' mode. Examples in C language are provided with the board.

EasyAVR4 Development Board

with on-board USB 2.0 programmer



The system supports 8, 20, 28 and 40 pin microcontrollers (it comes with ATMEGA16). Each jumper, element and pin is clearly marked on the board. It is possible to test most of industrial needs on the system. temperature controllers, counters, timers etc. EasyAVR4 is an easy-to-use Atmel AVR development system. Ultra fast USB 2.0 on-board programmer enables very efficient and faster prototype developing. Examples in BASIC and Pascal language are provided with the board.

Easy8051B Development Board

with on-board USB 2.0 programmer



System is compatible with 14, 16, 20, 28 and 40 pin microcontrollers (it comes with AT89S8253). Also there are PLCC44 and PLCC32 sockets for 32 and 44 pin microcontrollers. USB 2.0 Programmer is supplied from the system and the programming can be done without taking the microcontroller out.

LV 18FJ Development Board


Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroCD



System supports 64, 80 and 100 pin PIC18FxxJxx microcontrollers (it comes with PIC18F87J60 - PIC18 Microcontroller with an integrated 10Mbps Ethernet communications peripheral, 80 Pin Package). LV 18FJ is easy to use Microchip PIC18FxxJxx development system. USB 2.0 on-board programmer with mikroCD (In-Circuit Debugger) enables very efficient debugging and faster prototype development. Examples in C, BASIC and Pascal language are provided with the board.

dsPICPRO 3 Development Board

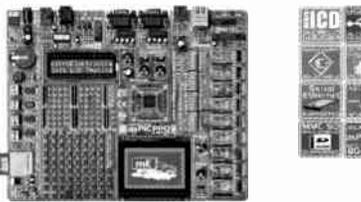
Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroCD



The system supports dsPIC microcontrollers in 64 and 80 pins packages. It is delivered with dsPIC30F6014A microcontroller. dsPICPRO3 development system is a full-featured development board for the Microchip dsPIC MCU. dsPICPRO3 board allows microcontroller to be interfaced with external circuits and a broad range of peripheral devices. This development board has an on-board USB 2.0 programmer and integrated connectors for MMC/SD memory cards, 2 x RS32 port, RS485, CAN, on-board ENC28J60 Ethernet Controller, DAC etc.

BIGPIC4 Development Board

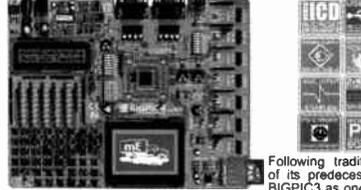Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroCD



Following tradition of its predecessor BIGPIC3 as one of the best 80-pin PIC development systems on the market, BIGPIC4 continues the tradition with more new features for the same price. System supports the latest (64) and 80-pin PIC microcontrollers (it is delivered with PIC18F8520). Many of these already made examples in C, BASIC and Pascal language guarantee successful use of the system. Ultra fast on-board programmer and mikroCD (In-Circuit Debugger) enables very efficient debugging and faster prototype developing.

BIGAVR Development Board

with on-board USB 2.0 programmer



The system supports 64-pin and 100-pin AVR microcontrollers (it is delivered with ATMEGA128 working at 10MHz). Many already made examples guarantee successful use of the system. BIGAVR is easy to use Atmel AVR development system. BIGAVR has many features that makes your development easy. You can choose between USB or External Power supply. BIGAVR also supports Character LCD as well as Graphic LCD.

EasyPSoC3 Development Board

with on-board USB 2.0 programmer



The system supports 8, 20, 28 and 48 pin microcontrollers (it comes with CY8C27643). Each jumper, element and pin is clearly marked on the board. EasyPSoC3 is an easy-to-use PSoC development system. On-board USB 2.0 programmer provides fast and easy in-system programming.

Please visit our website for more info <http://www.mikroe.com>

SOFTWARE AND HARDWARE SOLUTIONS FOR EMBEDDED WORLD

INTERFACE

Robert Penfold



SETTING PARALLEL PORT OUTPUTS TO INPUTS

THE previous *Interface* article covered the use of an eight-bit digital output plus one or two digital inputs to monitor up to 16 switches using a conventional diode gating and scanning technique. It is a technique that is commonly used as a means of reading keyboard switches, and it works well in most cases.

There can be problems when it is used with some types of digital input, such as those that have built-in pull-up resistors. The inputs of a PC's printer port usually have these resistors as a means of making their MOS-based circuits act more like the TTL types used in the original PCs. A 'floating' TTL input goes to logic 1 (high) due to the type of input circuit used, and pull-up resistors on MOS inputs give something that roughly approximates to the genuine article.

Virtue out of a necessity

There can be problems if the pull-up resistors are quite low in value, as they can then interfere with a passive driver circuit, such as a simple keyboard scanning type

based on diodes and resistors. One way around the problem is to make a virtue out of a necessity, and make the pull-up resistors part of the input circuit. This is the method used in the circuit of Fig.1, which functions in essentially the same manner as the basic scanning circuit described in the previous *Interface* article.

The basic scheme of things is to set each bit of the digital output high, in sequence, and to read the state of the digital input on each occasion. With this circuit, the pull-up resistor on the digital input normally takes it to logic 1.

However, when the switch for the active (high) output is closed, transistor TR1 will be biased into conduction and the input will be taken to logic 0. The scanning process therefore tests the state of each switch, with logic 1 being returned for an open switch, and logic 0 being returned for a switch that is closed.

Strictly speaking, the circuit is not a passive type, because it uses a switching transistor. No power supply is needed though, because the transistor is effectively powered from the PC's +5V supply via the

pull-up resistors. The circuit is, therefore, as convenient as a conventional passive one that uses diodes, but no form of active switching device.

Active extension

Like the passive version, the active circuit is easily extended to accommodate more switches. It is just a matter of using an additional circuit that is identical to the original, and can be driven from the same eight outputs. It feeds a different input though, and this input is used to read the eight additional switches.

In the circuit of Fig.2 switches S1 to S8 are read via the Select In handshake input, which is at bit 4 of the printer port's status register. Switches S9 to S16 are read using the Paper Empty (PE) handshake input at bit 5 of the status register.

There are five handshake inputs available at the printer port of a PC, which means that it should be possible to accommodate up to 40 switches in five banks of eight. It does not necessarily represent the best way of reading dozens of switches, but it is certainly

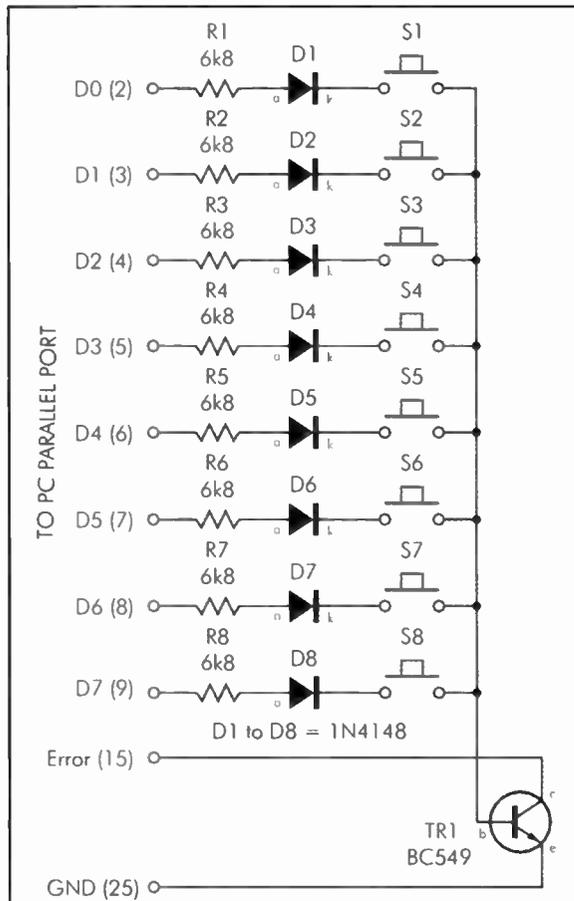


Fig.1. Simple 'active' circuit for monitoring eight switches

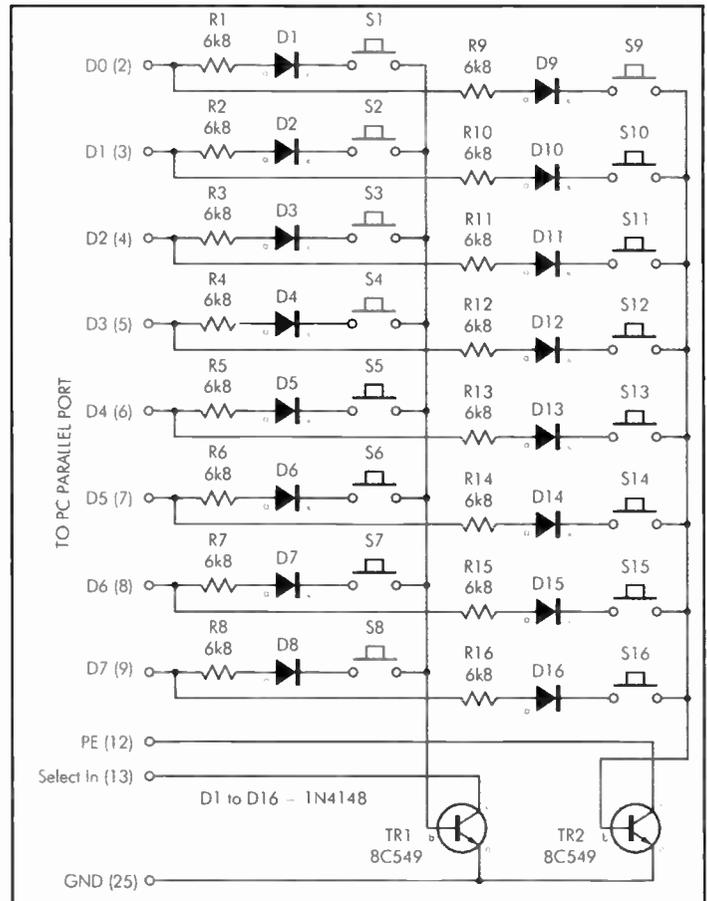


Fig.2. Extending the 'active' circuit to accommodate 16 switches

Listing 1

```

Private Sub Form_Load()
Out &H378, 0
End Sub

Private Sub Timer1_Timer()
Out &H378, 1
If (Inp(&H379) And 16) = 16 Then Shape1.FillColor = &HFF&
If (Inp(&H379) And 16) = 0 Then Shape1.FillColor = &HFF00&
If (Inp(&H379) And 32) = 32 Then Shape9.FillColor = &HFF&
If (Inp(&H379) And 32) = 0 Then Shape9.FillColor = &HFF00&

Out &H378, 2
If (Inp(&H379) And 16) = 16 Then Shape2.FillColor = &HFF&
If (Inp(&H379) And 16) = 0 Then Shape2.FillColor = &HFF00&
If (Inp(&H379) And 32) = 32 Then Shape10.FillColor = &HFF&
If (Inp(&H379) And 32) = 0 Then Shape10.FillColor = &HFF00&

Out &H378, 4
If (Inp(&H379) And 16) = 16 Then Shape3.FillColor = &HFF&
If (Inp(&H379) And 16) = 0 Then Shape3.FillColor = &HFF00&
If (Inp(&H379) And 32) = 32 Then Shape11.FillColor = &HFF&
If (Inp(&H379) And 32) = 0 Then Shape11.FillColor = &HFF00&

Out &H378, 8
If (Inp(&H379) And 16) = 16 Then Shape4.FillColor = &HFF&
If (Inp(&H379) And 16) = 0 Then Shape4.FillColor = &HFF00&
If (Inp(&H379) And 32) = 32 Then Shape12.FillColor = &HFF&
If (Inp(&H379) And 32) = 0 Then Shape12.FillColor = &HFF00&

Out &H378, 16
If (Inp(&H379) And 16) = 16 Then Shape5.FillColor = &HFF&
If (Inp(&H379) And 16) = 0 Then Shape5.FillColor = &HFF00&
If (Inp(&H379) And 32) = 32 Then Shape13.FillColor = &HFF&
If (Inp(&H379) And 32) = 0 Then Shape13.FillColor = &HFF00&

Out &H378, 32
If (Inp(&H379) And 16) = 16 Then Shape6.FillColor = &HFF&
If (Inp(&H379) And 16) = 0 Then Shape6.FillColor = &HFF00&
If (Inp(&H379) And 32) = 32 Then Shape14.FillColor = &HFF&
If (Inp(&H379) And 32) = 0 Then Shape14.FillColor = &HFF00&

Out &H378, 64
If (Inp(&H379) And 16) = 16 Then Shape7.FillColor = &HFF&
If (Inp(&H379) And 16) = 0 Then Shape7.FillColor = &HFF00&
If (Inp(&H379) And 32) = 32 Then Shape15.FillColor = &HFF&
If (Inp(&H379) And 32) = 0 Then Shape15.FillColor = &HFF00&

Out &H378, 128
If (Inp(&H379) And 16) = 16 Then Shape8.FillColor = &HFF&
If (Inp(&H379) And 16) = 0 Then Shape8.FillColor = &HFF00&
If (Inp(&H379) And 32) = 32 Then Shape16.FillColor = &HFF&
If (Inp(&H379) And 32) = 0 Then Shape16.FillColor = &HFF00&

```

possible to do so. A scanning system is unlikely to represent the fastest method of reading switches, but the highest possible operating speed is unlikely to be crucial when monitoring mechanical switches.

Software

The Visual BASIC listing consists of eight main sections, with each one providing essentially the same action. It requires a form that has 16 shape components, which act as indicator 'lights' (Fig.3) on a one per switch basis. The colour of the 'light' is red when the corresponding switch is open, and green when it is closed.

A timer component is also required, and this should have a low Interval value of about 20 so that the program scans at a reasonably high rate. The program utilizes **input32.dll**, which must be available to the system in order to make the Inp and Out instructions function properly.

The first section of the program simply sets the output port with all the outputs initially low, which is not really necessary with this simple demonstration program since it starts the scanning process

immediately. However, it could be important in applications that use the scanning process intermittently.

The next section is used to read switches S1 and S9, which are the switches that are read when output D0 is high. The first line writes a value of 1 to the output port, and it is assumed here that the port is at addresses from &H370 to &H37a. The addresses used in the Inp and Out instructions must be changed to suit in cases where an alternative address range is used.

Each switch is read by a pair of If...Then statements, which operate in the same basic manner. The first pair set the colour of Shape1 to red (&HFF&) or green (&HFF00&), depending on whether bit 4 of the status register is low or high. Bits of the register other than bit 4 are masked by using a bitwise And operation with a masking value of 16.

The second pair of If...Then statements are much the same, but they control the colour of Shape9, and a masking value of 32 is used in the And operations so that bit 5 of the status register is read and the other bits are masked.

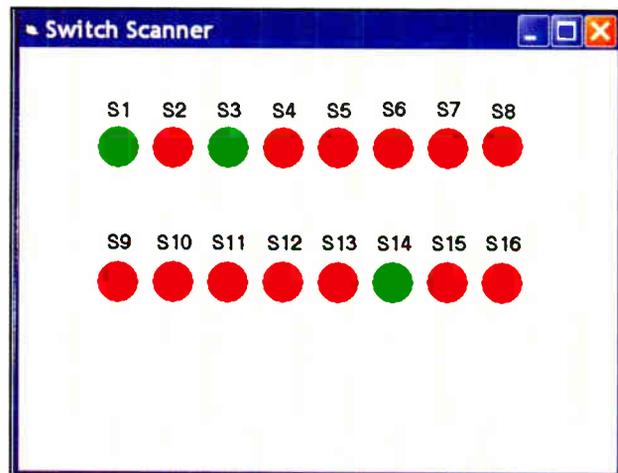


Fig.3. Typical screen layout for scanning 16 switches. Red – switch open, and green –switch closed

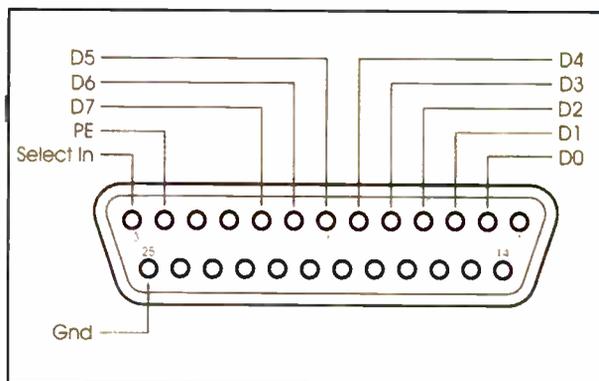


Fig.4. Connections to the PC printer port are made via a 25-way male D-type connector

The other seven sections of the program operate in the same fashion, but they control the colour of Shape 2 and Shape 10, Shape 3 and Shape 11, and so on through to Shape 8 and Shape 16. In a real-world application, it will usually be necessary to have the program do something more than control the colour of a shape component, but it is simply a matter of using the appropriate actions in the If... Then statements.

It would probably be possible to reduce the size of the program using a loop, but it is reasonably compact in its present form. Also, with the program in this form it is easy to make any switch provide practically any action. If necessary, each switch could have a totally different function.

The simple hardware of this interface is not particularly fast by the standards of modern logic, but it is still very fast when compared to a Visual BASIC program when running on even the best of current PCs. Consequently, there is no need to include any delay loops to give the interface time to respond to changes at the output port. Very short delays might be necessary if a fast programming language is used.

Connections


The connections to a PC printer port are made via a male 25-way D connector, and Fig.4 shows the eleven connections that are needed in this case. As when using any circuit that interfaces to the PC via a simple parallel port, the connecting lead should be no more than about two or three metres long. Otherwise there is a risk of stray coupling between the leads causing erratic results.

Build Your Own

Seismograph

Ever wondered how a seismograph works? Here's one that you can build yourself. It uses a horizontal swinging pendulum to detect earthquake waves and you can even display the results on a PC.

By **DAVE DOBESON***

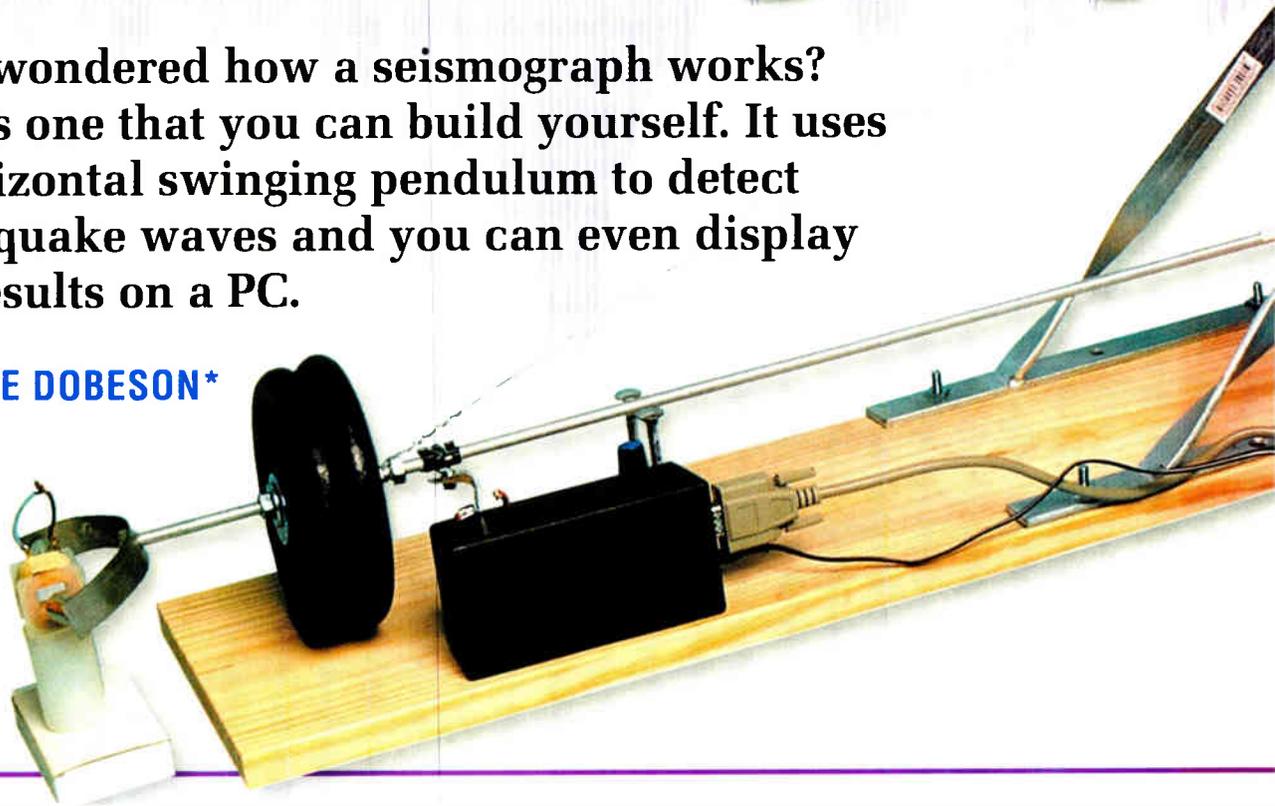

MOST Britains are thankful that we are not seriously affected by the large earthquakes and volcanoes that regularly devastate so many other parts of the world. However, few realise how easy it is to make your own amateur seismograph.

Plate tectonics

Before we take a look at the design of our seismograph, let's first find out why major earthquakes occur. In particular, we need to have some understanding of 'plate tectonics'.

The basics are very simple – the crust of the earth is made up of about 20 major 'plates' that 'float' on semi-liquid layers underneath. Earthquakes commonly occur at the boundaries of the plates, where they collide and

produce stresses in the Earth's crust. For example, deep ocean faults off the coast of Sumatra produced the magnitude 9.0 'Boxing Day Tsunami' earthquake in 2004 and the related Niass 8.7 earthquake in April, 2005.

Of course, many large earthquakes go unreported because they occur under the ocean or in sparsely populated areas and have no impact on humans.

If you look at the United States Geological Survey (USGS) home page and click on 'Latest Earthquakes' (to show the last seven days' earthquakes for the US and the world), you will see where many of the larger earthquakes occur – see www.usgs.gov.

The site also has detailed information on the tectonic forces causing

earthquakes, the design and operation of professional seismographs, records of historically significant quakes and links to records in other countries.

If your home-made seismograph detects a real earthquake, the event should also be reported within minutes by the above site.


Designed for schools

This do-it-yourself seismograph was originally described in *Scientific American* in 1979 and has been adapted for science teachers to build and use in the school laboratory.

Movements of the seismograph, which is basically a horizontal pendulum, are detected using a simple light sensor circuit. In operation, a metal vane attached to one end of the pendulum



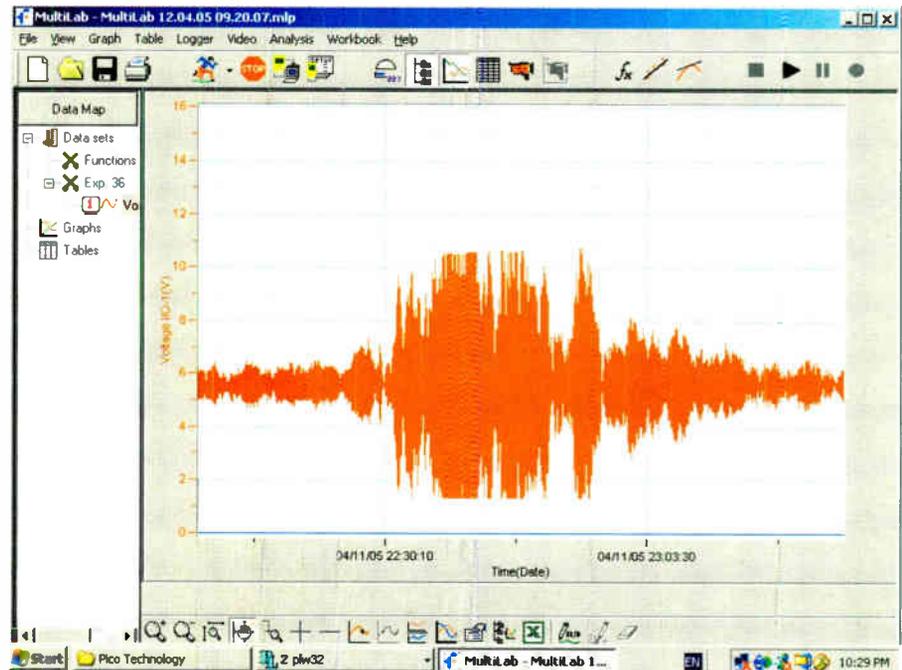The mechanical section of the seismograph uses parts that are readily available from a hardware store. It's based on a swinging horizontal pendulum and movement is detected using a vane and light sensor circuit mounted at one end.



This seismograph plot shows a magnitude 6.5 quake that occurred in Papua New Guinea on April 11, 2005. A 6.8 quake near Noumea was detected only five hours later. The detector circuit used was the same as described here.

The seismograph described here is known as a 'Lehman' or 'Horizontal Pendulum' seismograph. It's also called a 'Swinging Gate Seismograph', because the bar and its supporting wire look like an old-fashioned farm gate. The 'hinges' (actually the pivot points) of the 'gate' are not quite vertically aligned, with the top hinge just forward of the bottom hinge so that the 'gate' will swing shut. In practice, this means that the horizontal pendulum (or bar) swings slowly back to its original resting position.

The accompanying photos show the basic set-up. As can be seen, it includes an 800mm long 16mm threaded steel rod that's fitted with a 2 to 3kg mass at one end. The other end of the rod is ground to an edge and pivots on the end of a 13mm bolt – this forms the lower pivot point.

The supporting wire is attached to the rod at one end, just before the weights, and to a turnbuckle at the other end. This then pivots about 25-35cm above the lower pivot.

If we align the seismograph pivots so that the top pivot is less than 1mm forward of the bottom pivot, then the seismograph bar will always swing back to its central position and will have a natural period of about 5-10 seconds. However, if the pivots are exactly vertically aligned, there will

be no restoring force and it will never swing back. We cannot move the top pivot too far forward though, otherwise the seismograph will be very insensitive.

This unit is very sensitive to the mostly horizontal motion of earthquake 'L-waves' but is insensitive to 'P-waves', which are mostly vertical.

By the way, it's important to remember that although we often talk about the bar (or pendulum) of the seismograph 'swinging', it's really the room that moves during an earthquake. The bar, because of the inertia of a heavy mass attached to one end, initially stays still. In effect, the unit and its associated logger act as a low-pass filter which renders the unit insensitive to everyday events (footsteps, doors closing, passing traffic, etc).

The accompanying photos show most of the construction details. The only critical dimension is that the top pivot must be less than 1mm in front of the lower pivot. As well as the wooden

(or bar) partially blocks the light between a LED and an LDR (light-dependant resistor). However, when the bar moves (ie. during an earthquake), the amount of light falling on the LDR is modulated by the metal vane.

This signal is then fed to a low-cost op amp circuit which, in turn, feeds into a data logger. Finally, the output of the data logger is fed to a computer to store, display and print the results. A PICAXE-based A/D converter and a freeware graphing program called 'StampPlot Lite' can do the same job.


Building the seismograph

OK, let's first take a look at the mechanical details of our seismograph and find out how it's built.

About The Author*

Dave Dobeson is a science teacher at Turramurra High School, Australia and the University of Sydney Science Teacher Fellowship holder for 2005.

Constructional Project

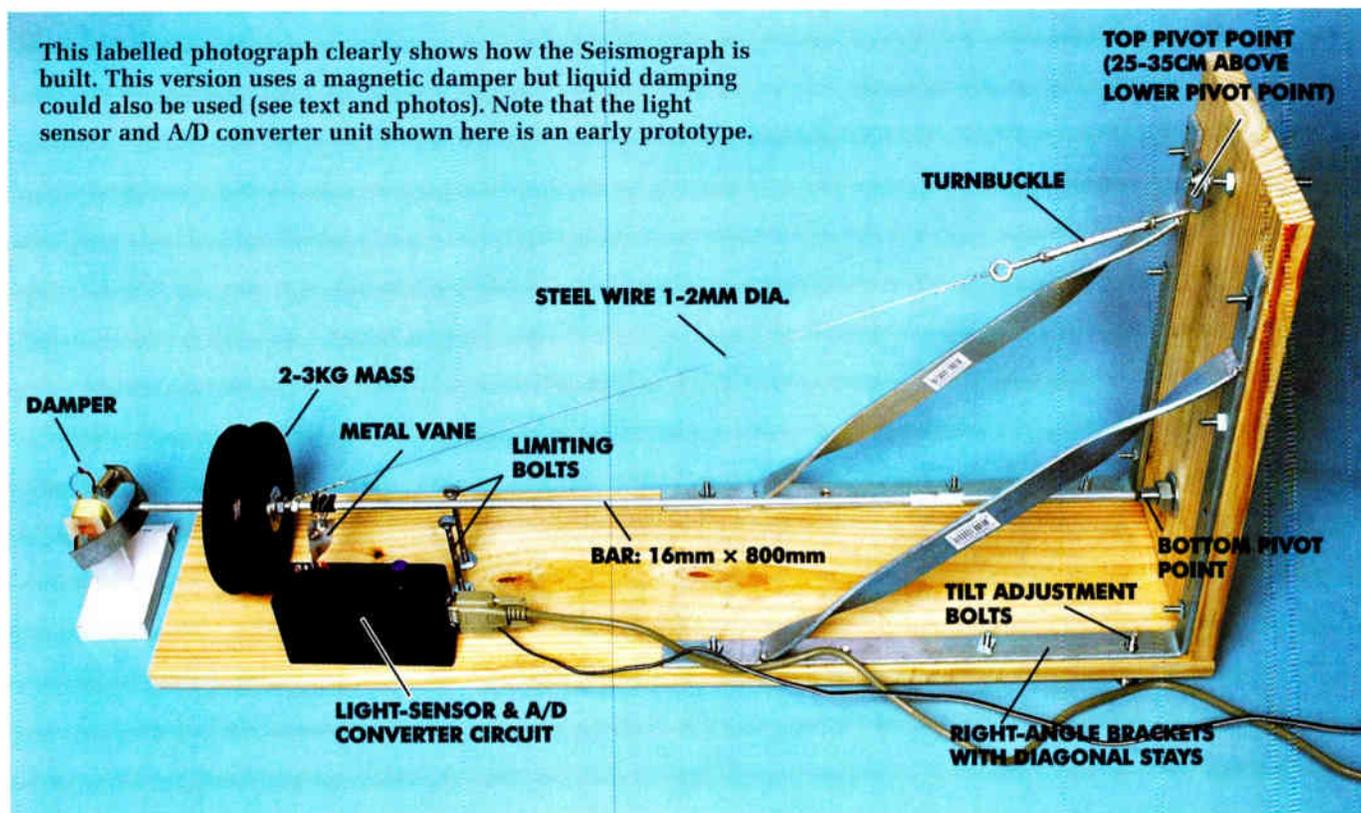

frame shown, the unit could be built into any strong cupboard, bookcase, shelf or even a strong, metal frame. In that case, the brackets and wooden frame would not be needed. Any type of metal rod could be used (as long as it's strong enough) and the same goes for the mass at one end.

Note that you will have to 're-zero' the seismograph for the first few weeks after building it, as the wire, brackets and wood flex under the strain. After that, it will be a matter of making routine adjustments every few months.

Top pivot point

The top 'hinge' (or pivot point) is made by drilling a 5mm diameter hole about half-way through the outer section of a large, thick washer – ie, to make a 'dimple'. Smaller washers and a nut are used to hold the large washer in position, while a nut and lockwasher behind the wooden upright panel lock the bolt in place.

As shown in the photos, the hook at the end of the turnbuckle sits in this dimple, so that it can pivot freely. In operation, the turnbuckle adjusts the tilt of the bar and is set so that the bar is horizontal. The securing bolt can be screwed in or out to move the top pivot point relative to the bottom pivot. This is important for the overall functioning

of the seismograph because it affects the natural period of the bar (ie, the time for one complete swing from the centre to one side, then back through the centre to the other side and finally back to the centre again).

A period of about five seconds seems to work best.

The pivot end of the 16mm threaded rod is ground to a knife-edge and this sits vertically against the end of a 13mm bolt. Wind a nut onto the rod before you cut and grind it, so that the thread is restored when the nut is removed. Be sure to use safety goggles when drilling, cutting or grinding metals – you only have one pair of eyes.

Note that the lower mounting point must be directly below the upper mounting point. The best way to ensure this is to use a plumb-bob made from fine fishing line and a lead sinker.

The two rear-most vertical bolts that go through the support brackets are used for tilt adjustment – see photo. These both screw into threads that are tapped through the wooden base and the brackets (nuts under the wooden base will do) and each has a screwdriver slot cut into its end. This allows you to use a screwdriver to tilt the seismograph sideways and forwards or backwards, to alter the

position of the bar and thus its period and sensitivity.

The far end of the seismograph wooden frame has a single central support. A sheet of plywood underneath will stop the three supports from sinking into the carpet when the unit is positioned on the floor.

Swinging the weight

Just about any mass of 2 to 3kg will provide sufficient inertia to initially keep the bar still during an earthquake, provided it doesn't hang too far below the bar. A pair of 1.25kg barbell weights are ideal for the job. They cost less than £3 each from a sports store and come with a ready-made hole through the middle. This means they can be simply slipped over the end of the bar and clamped in position using nuts and washers on either side.

Damping

Once earthquake waves set the bar swinging, it will keep swinging for hours unless it is damped. Perfect damping would stop the bar with a few swings but in practice, under two to three minutes is OK.

You can use either liquid or magnetic damping. For liquid damping, a 40 x 50mm plastic paddle dipped into a rectangular container of water

will do the job. You can use a small bulldog clip to attach the paddle to the bar (see bottom right). The water will need topping up each week or so.

Magnetic damping involves attaching one or two super magnets to the end of the bar using a U-shaped bracket. A thick sheet of aluminium or a coil of wire with the ends joined is then placed in the magnetic field.

When the bar moves (ie, during an earthquake), current is induced into the aluminium or wire coil. This in turn produces a magnetic field that counters the magnets and so damps the motion of the bar.

Discarded computer hard disks are a good source for super magnets but be careful – supermagnets are dangerous and the author has been badly cut when a pair decided to play 'north attracts south, with his hand in between'. They can also be a disaster if they get too close to your credit cards or a computer monitor!

On the other hand, the good thing about magnetic damping is that once you get it right, it stays right.

Old aquarium air pumps have coils of fine wire, which can be used for magnetic damping if the ends of the wires are joined together. A 400g coil of 0.7mm enamelled wire with the ends joined together and a super magnet that moves inside the coil gives almost perfect damping.

Use your multimeter to check that the winding hasn't burnt out before using the coil.

The perfect location for your seismograph is on a concrete block that's set into bedrock at the bottom of a sealed mine shaft! If you don't have access to a mine shaft(!), the seismograph

should be installed in a closed room or cupboard, or in a strong bookcase surrounded by a Perspex cover (to prevent air movement over the unit).

Circuit details


Many different seismograph detector and A/D (analogue-to-digital) converter circuits are available on the net. The best-known site is called the Public Seismic Network at www.psn.quake.net (in California). It has designs that go from pens writing on rolls of paper to very complex circuits with low-noise op amps, 16-bit A/D converters and damping using negative feedback.

By contrast, the circuit used here is quite simple – see Fig.1. As previously stated, it's based on a light sensor circuit that's interrupted by a metal vane attached to the end of the bar. In practice, the unit is set up so that the vane normally blocks about half the light from the LED to its LDR.

The light detector and its associated op amp circuit is exactly the same as the one designed for use with some school data loggers. The logger output is simply taken from the output of IC1, as shown. Alternatively, you can add your own data logger, based on A/D converter stage IC2 (a PICAXE-08M).

In greater detail, power for the circuit comes from a 9V DC plugpack supply. Diode D1 provides reverse polarity protection, while the associated 100Ω resistor and 470μF capacitor provide decoupling and ripple filtering.

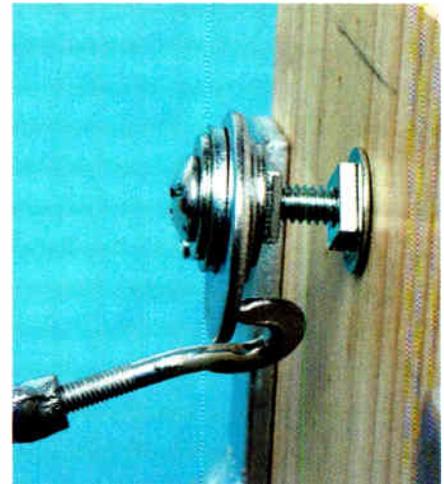The filtered DC rail is used to power LED1 via a 1kΩ current limiting resistor. The LDR and its associated 10kΩ resistor effectively form a voltage divider across this supply rail, the voltage at their junction varying according



The hook at the end of the turnbuckle sits in a 5mm dimple that's drilled into a large washer to form the top pivot point.



The lower pivot point is formed by first grinding the end of the bar to a sharp edge. This sharp edge then rests vertically against the end of a 13mm x 40mm-long bolt.

to the resistance of the LDR. This in turn depends on the amount of light reaching it from the LED.


The output from the LDR is fed to the inverting (pin 2) input of op amp



Above and right: these two views show the alternative damping methods for the swinging bar. Magnetic damping (above) uses a couple of super magnets and a coil of wire, while liquid damping (right) uses a 40 x 50mm plastic paddle dipped into a rectangular container of water.



Constructional Project

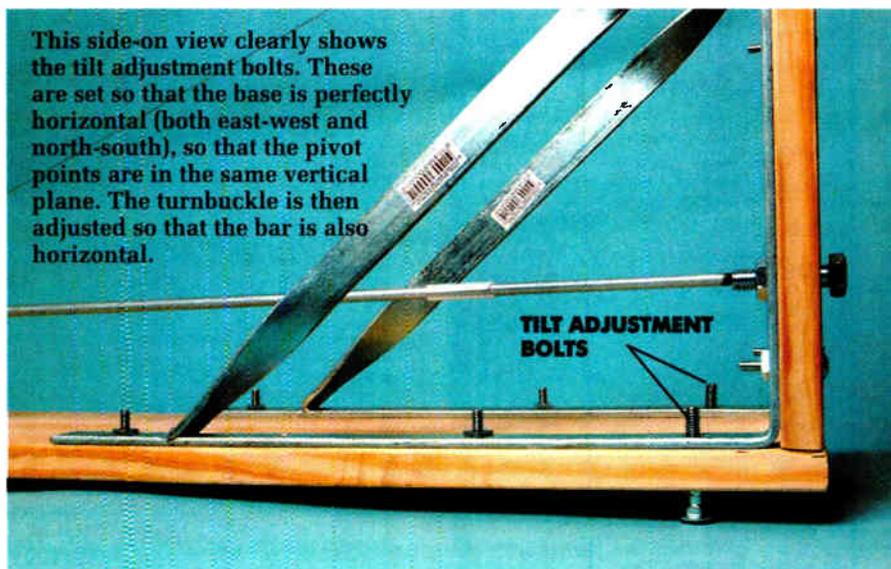

IC1 (741) via two back-to-back 470 μ F capacitors. These capacitors block the DC component at the output of the LDR, while allowing signal fluctuations to be fed to the op amp. They also block any slow variations in the LDR signal due to thermal variations in the room.

IC1 functions as an inverting amplifier stage. Its non-inverting input (pin 3) is biased to half the supply voltage using two 10k Ω resistors, while its gain can be varied from 0 to 10 using potentiometer VR1, which is in the feedback loop.

Note that although the circuit shows a 741 op amp, you could also use an OP27 device for improved accuracy.

IC1's output appears at pin 6 and is fed to a voltage divider consisting

of two 3.3k Ω resistors. The top of this divider (ie, at pin 6) can be used to directly drive an external data logger. Alternatively, the divider output (at the junction of the resistors) can be used to provide a nominal 0-5V signal, which may be required by some loggers.

Pin 6 of IC1 also drives trimpot VR2 and this is used to set the maximum signal level into pin 3 of IC2 (to about 4V). IC2 is programmed to function as an A/D converter, using the simple program, Listing 1, in the accompanying panel (more on this later). Its output is taken from pin 7 (P0) and fed to pin 2 of DB9 socket CON2.

This socket is in turn connected to the serial port of a PC, to provide the alternative data logger.

The PICAXE-08M is programmed via pin 3 of CON2 socket. The incoming data signal is fed to pin 2 (SER IN) of IC2 via a voltage divider consisting of 22k Ω and 10k Ω resistors.

Power for IC2 is supplied via a 3-terminal voltage regulator REG1. This provides a regulated +5V rail to pin 1.

Building the circuit


Building the circuit is easy since all the parts are mounted on a small PC board, coded 636. Fig.2 shows the assembly details.

Note that REG1 and the PICAXE (IC2) are required only if you don't already have a data logger. If you do have a logger, these parts can simply be left out, along with the DB9F socket, trimpot VR2, the 100nF capacitor and the 22k Ω and 10k Ω voltage divider resistors from pin 2 of IC2.


Begin by installing the resistors and capacitors. Table 1 shows the resistor colour codes but it's also a good idea to check each resistor using a digital multimeter before soldering them into circuit, just to make sure.

Follow these parts with diode D1, the two IC sockets (don't install the ICs yet) and trimpot VR2. Take care to ensure that D1 and the electrolytic capacitors go in the right way around.

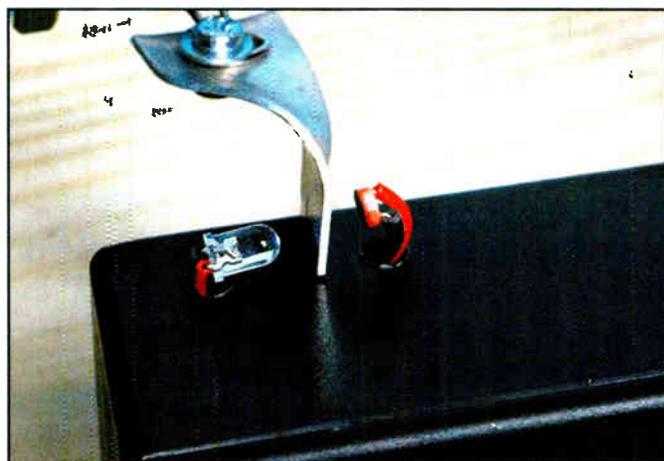LED1 can go in next. Bend its leads down through 90° close to its body before installing it at full lead length on the PC board – ie, the centre of the LED should be about 22mm above the PC board (see photo). Again, take care to ensure that it's oriented correctly.



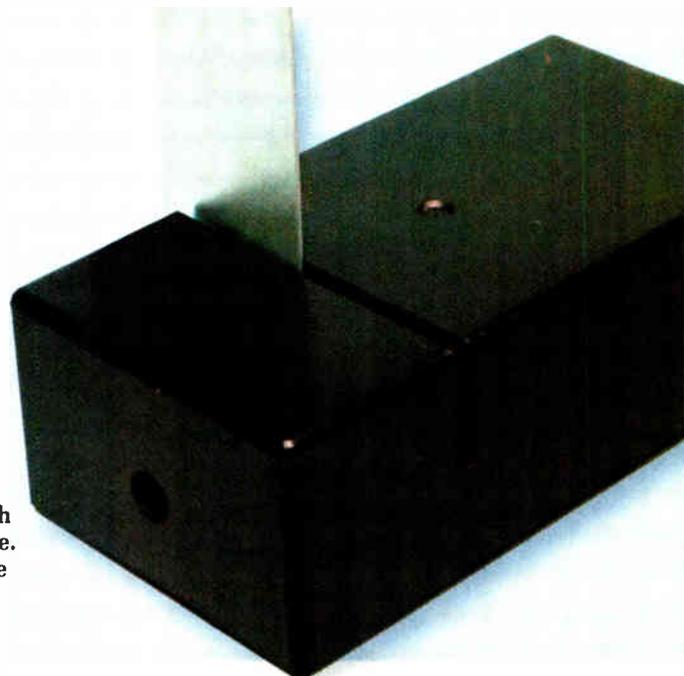In the prototype, the LED and the LDR were brought out through holes in the case, with the vane sitting between them – see above. By contrast, in the final version, the LED and LDR are inside the case and the vane rides in a slot. The vane is positioned so that it normally 'shadows' about half the LED body.



Parts List – Simple Seismograph

That done, you can install the LDR but there's just one wrinkle here. The 10kΩ resistor shown in series with the LDR on Fig.1 is correct for most LDRs. However, some LDRs have a lower resistance than others in the presence of light and you may have to adjust the value of the series resistor accordingly.

That's easy to do – just measure the resistance of the LDR in a brightly lit room and use a series resistor that's about the same value. The value isn't all that critical. In practice, you can buy 1kΩ, 3.3kΩ and 10kΩ resistors and use the one that's closest to the measured LDR value.

The LDR is mounted in similar fashion to the LED – ie, bend its leads down through 90° before installing it. It should be mounted so that its face is directly aligned with the LED.

Regulator REG1 is mounted with its metal tab flat against the PC board. To do this, bend its leads downwards by 90° about 5mm from its body, then secure it to the board using a M3 x 6mm machine screw and nut before soldering its leads. There's no need for a heatsink, as it supplies just a few milliamps to IC2.

The board assembly can now be completed by fitting CON1, CON2, potentiometer VR1 and a 3-pin header for the external logger interface.

Serial cable options

A standard serial cable is used to connect the PC board to the computer (if you're using a PC as the data logger). There are several options here.

First, you could go out and buy a serial cable but that's the expensive way of doing things. It's far better to scrounge a cable instead. For example, if you have an old modem (left over from your dial-up days), you can use its serial cable (you did keep it, didn't you?) to connect to the PC.

Another possibility is to use a serial cable from a discarded

1 PC board, code 636, available from the <i>EPE PCB Service</i> , size 123 x 57mm	4 10kΩ	1 100Ω
1 9V DC plugpack	2 3.3kΩ	
1 2.1mm DC power socket, to suit plugpack (CON1)	Plus 1 x 10kΩ or 1 x 3.3kΩ or 1 x 1kΩ to match LDR resistance – see text	
1 DB9F connector, PC mount	Mechanical Parts	
1 plastic utility box, 130 x 67 x 44mm	1 800mm long x 16mm threaded steel rod	
4 9mm-long untapped spacers	5 16mm nuts and washers to suit rod	
4 M3 x 15mm machine screws	1 50mm long x 6.5mm bolt	
4 M3 nuts	3 6.5mm nuts and washers	
3 PC stakes	1 40mm long x 13mm bolt	
1 serial computer cable (see text)	1 13mm nut and washers	
2 8-pin IC sockets	1 9.75mm washer	
1 100kΩ rotary potentiometer, linear (VR1)	1 1-metre length 1-2mm diameter steel wire	
1 5kΩ horizontal trimpot (VR2)	2 bulldog clips to suit	
1 Light Dependent Resistor (LDR1)	1 2-2.5kg mass (eg, 2 x 1.25kg barbell weights)	
1 3-way pin header	1 piece of thin aluminium sheet (to interrupt light beam)	
Semiconductors	1 50 x 50mm piece of aluminium or rigid plastic for paddle (see text)	
1 741 or OP27 op amp (IC1)	2 small bolts and nuts to fasten paddle to bulldog clips	
1 PICAXE-08M microcontroller (IC2) www.picaxe.co.uk	2 braced right-angle brackets, 250 x 250mm	
1 7805 3-terminal + 5V voltage regulator (REG1)	8 6.5mm x 40mm bolts, nuts and washers	
1 1N4004 diode (D1)	3 16mm x 100mm round-head bolts, nuts and washers	
1 red or white high-brightness LED (LED1)	1 wooden base, 900 x 250 x 20mm	
Capacitors	1 wooden back, 400 x 250 x 20mm	
3 470µF 25V electrolytic		
1 100nF MKT (code 104 or 100n)		
Resistors (0.25W, 1%)		
1 22kΩ	1 1kΩ	

mouse. Just cut the cable off close to the mouse, then strip the wires back and use a multimeter to identify which lead goes to which pin on the socket – you need to use the leads that go to pins 2, 3 and 5 (the rest can be trimmed off).

These leads can then be soldered directly to three PC stakes mounted at the appropriate points on the PC board. As a bonus, you don't need the

on-board DBF9 socket, which means you can save even more money.


Checks and adjustments

Before fitting the two ICs, it's necessary to make several voltage checks. First, connect a 9V DC plugpack supply and switch on. The LED should immediately come on. If necessary, adjust it so that it shines directly on the LDR.

Table 1: Resistor Colour Codes

No.	Value	4-Band Code (1%)	5-Band Code (1%)
1	22kΩ	red red orange brown	red red black red brown
4	10kΩ	brown black orange brown	brown black black red brown
2	1kΩ	brown black red brown	brown black black brown brown
1	100Ω	brown black brown brown	brown black black black brown

Constructional Project

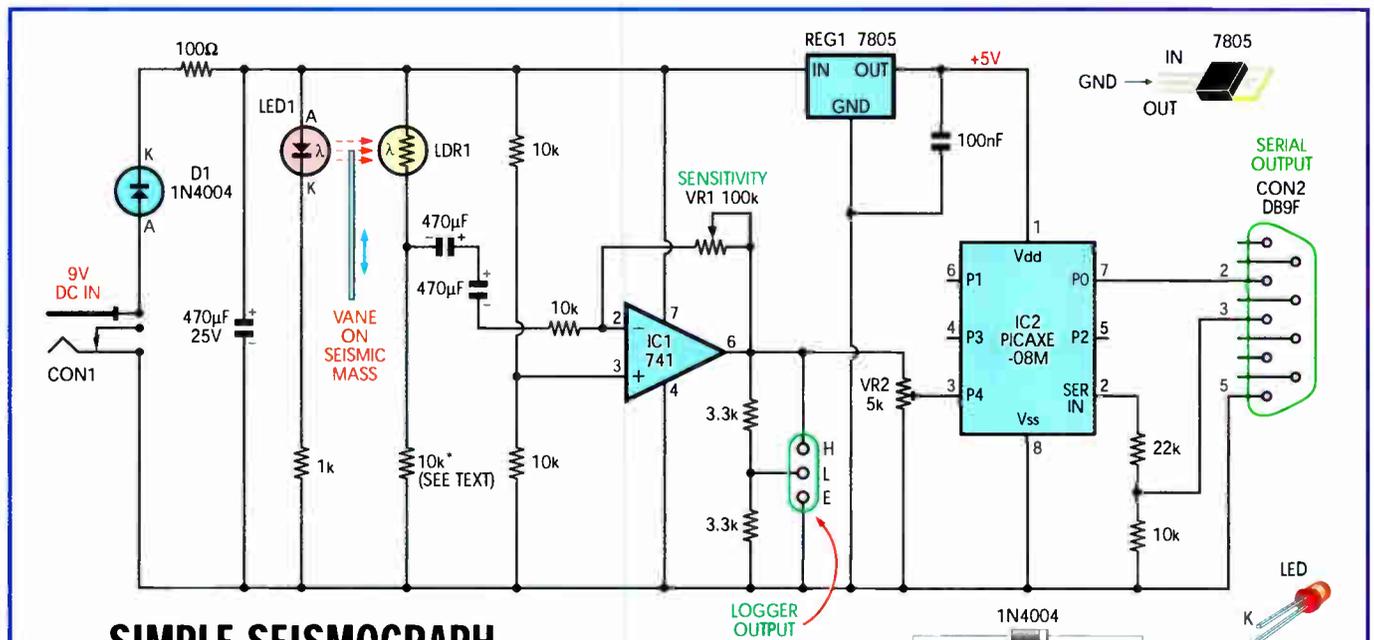

SIMPLE SEISMOGRAPH

Fig.1: the circuit uses a light detector based on LED1 and LDR1 to detect movement of an interrupter vane placed between them. The resulting signal is then amplified by IC1 and fed to the logger output. IC1 also drives IC2, a PICAXE-08M chip programmed to function as an A/D converter. Its output can then be fed to the serial input of a PC, to provide an alternative data logger.

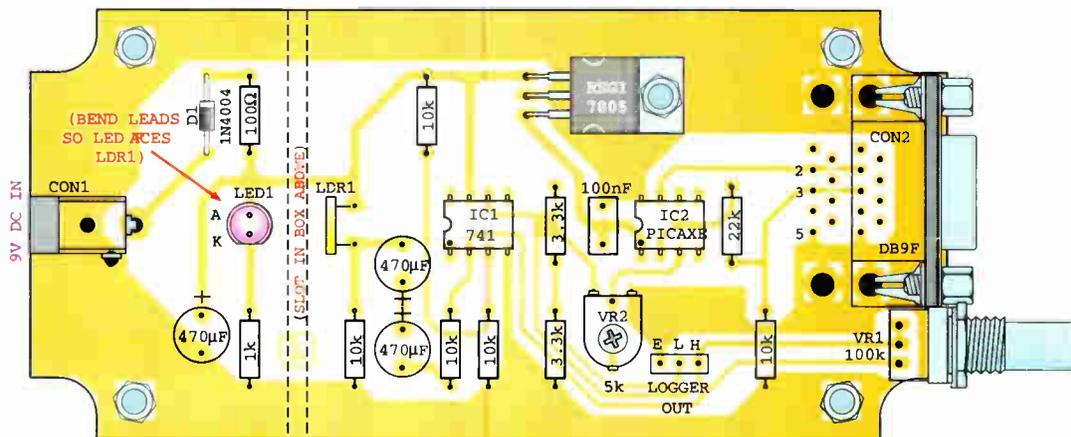


Fig.2: install the parts on the PC board as shown here, making sure that all polarised parts are correctly oriented. IC2, REG1, VR2 and CON2 can be left out if you already have an external data logger.


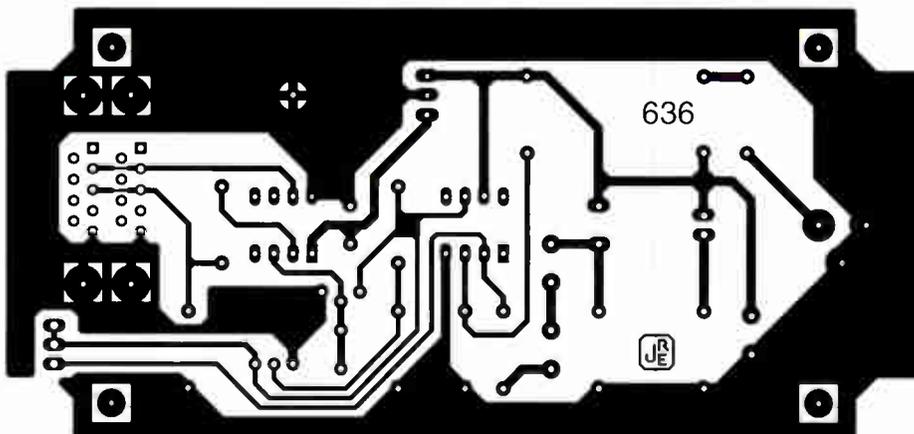



Fig.3: this is the full-size etching pattern for the Seismograph PC board.

Next, use a digital multimeter to check the voltages on IC1's socket pins. Pin 7 should be at the supply voltage (about 9V, depending on the plugpack), pin 2 should change when the light to the LDR is suddenly interrupted and pin 3 should be at half the supply voltage. That done, check for +5V on pin 1 of IC2's socket and for 0V on pins 2, 3, 7 and 8.

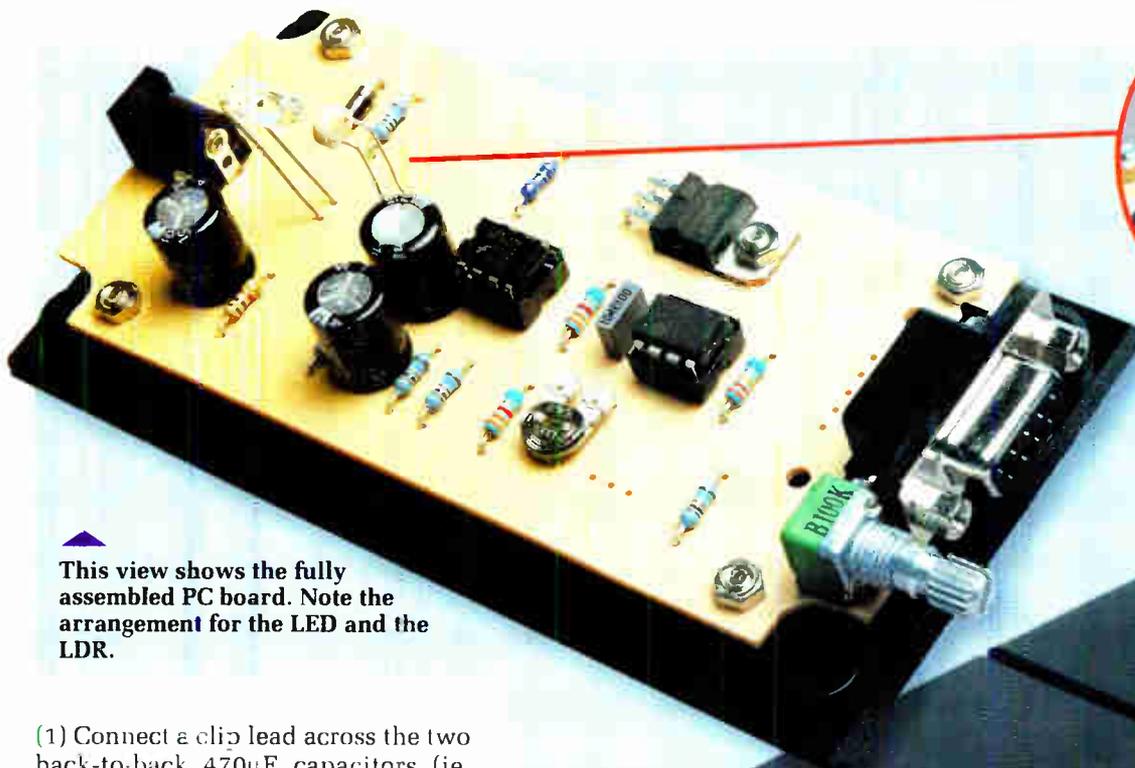If it all checks out so far, disconnect the plugpack and install IC1 (but not IC2). You now have to adjust trimpot VR2 so that the voltage on pin 3 of IC2 can never exceed 5V. This is done as follows:



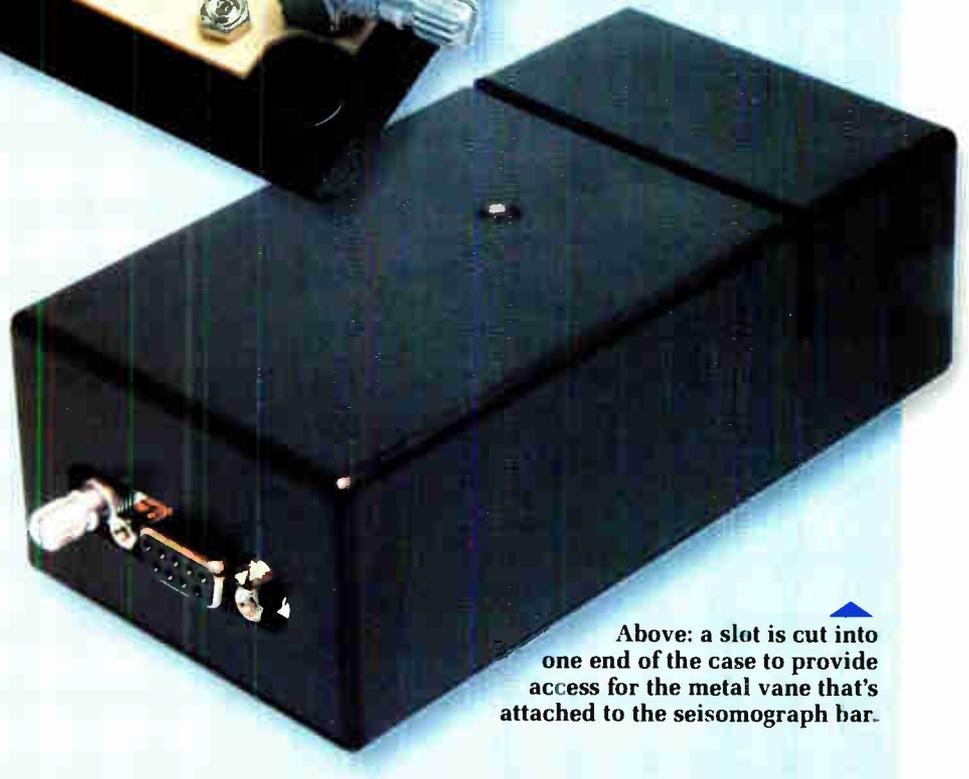▲ This view shows the fully assembled PC board. Note the arrangement for the LED and the LDR.



▲ Above: a slot is cut into one end of the case to provide access for the metal vane that's attached to the seismograph bar.

- (1) Connect a clip lead across the two back-to-back 470 μ F capacitors (ie, short them out)
- (2) Set both VR1 and VR2 to their mid-range positions
- (3) Place a piece of thick cardboard (or other opaque object) between the LED and the LDR (to block the light)
- (4) Reapply power and check the voltage at pin 6 of IC1. It should be about 1V less than the supply rail
- (5) Monitor the voltage at pin 3 of IC2's socket and adjust VR2 for a reading of 4V (or slightly less).

Once that's done, disconnect the plug-pack and install the PICAXE-08M, with its notch facing to the left – see Fig.2.

Final assembly

The PC board is designed to fit inside a standard (130 × 67 × 44mm) plastic case. It's mounted on the lid on four 9mm untapped spacers and secured using M3 × 15mm long screws and nuts.

That done, you have to make a cut-out in one end of the case to provide clearance for the DBF9 socket (CON2) and the pot shaft. This cutout measures 45mm long × 12mm high and is about 12mm from the lip of the base.

Alternatively, if you're not using CON2, the serial cable can be run through a small hole in the case and secured using a small cable tie. The same applies if you are connecting an external logger to the 3-pin header.

You also need a hole directly in-line with the DC power socket (CON1). This is horizontally centred 17mm

from the lip of the case and should be drilled and reamed to 8mm.

Finally, a slot must be cut in the case, in line with the light sensor, to provide access for the vane that's attached to the bar. This slot should be positioned 37mm from the end of the case and can be about 4mm wide. The unit can then be assembled into the case and attached to the base of the seismograph.

Position the vane so that it normally blocks about half the light between the LED and the LDR.

Programming the PICAXE

To program the PICAXE, you first have to download the free

'Programming Editor' from www.rev-ed.co.uk/picaxe.

That done, connect the board to your computer via the serial cable (this should be done with the computer off) and download the simple program shown in Listing 1 into the PICAXE chip.

If you increase the logging interval to 10 seconds by changing line 5 to 'wait 10', you can keep a continuous seismograph record for up to a week. You could also hang a piezo transducer off the PICAXE and add an 'Alarm' loop to the program to warn you if b1 exceeds a certain value.

Once the program is loaded and running in the PICAXE-08M (check

Tectonic Plates, Earthquake Waves & The Richter Scale

"An earthquake is the way the Earth relieves its stress by transferring it to the people who live on it." – Dr Lucy Jones, USGS.

EARTHQUAKES occur when adjacent blocks of the Earth's crust slide past each other along a fracture we call a fault line.

Most active faults are located near the boundaries of the Earth's tectonic plates. These plates move in several ways: (1) they can slide past each other; (2) they can move away from each other (diverge); or (3) they can move towards each other (converge).

For example, the west coast of New Zealand's South Island – which is at the eastern edge of the Australian-Indian plate – moves north along the Alpine Fault. This movement is relative to the eastern side of the island, which is part of the Pacific plate. This area experiences several magnitude five quakes every year, as well as much larger but less frequent earthquakes.

Plate divergence generally occurs at mid-ocean ridges, such as the Atlantic's, which rises above sea-level to form Iceland's central rift valley. Convergence occurs at 'subduction zones' like the one that caused Aceh's Boxing Day earthquake. Here, the northern edge of the Australian-Indian plate is descending under Indonesia, which is part of the Eurasian Plate.

While most active faults are located near plate margins, about 10% of active faults occur well away from the plate margins. The earthquakes generated in these locations are known as intra-plate earthquakes and are mostly thought to occur either as a response to stress transmitted through the plate from its interaction with adjacent plates or from thermal equilibration, which can cause

contraction as the plate cools down or expansion as the plate warms up. The Australian Northern Territory's Tennant Creek fault is a world-famous example of one of these intra-plate structures and generates a number of generally small earthquakes each year.

Several types of vibrations are generated as blocks of rock grind past each other during an earthquake and these propagate around and through the planet as different types of earthquake waves. The fastest (and the first to arrive) are 'Primary' or P-waves, which are longitudinal compressional waves that propagate at speeds of 1.5-8km/s (depending on rock density). The next fastest are the 'Secondary' or S-waves which are shear waves (or transverse waves) and these propagate at speeds of about 3.2-4.8km/s.

Both P and S-waves move through the body of the planet and are refracted and reflected as they encounter rock density and composition changes. However, S-waves cannot propagate through the liquid part of the Earth's core. In fact, it was by examining the geographic pattern of P-waves and S-waves that led to the formulation of the core-mantle-crust model of the Earth.

The slowest waves are surface waves, which propagate at speeds of about 2-5km/s. There are two types of surface waves: Rayleigh and Love (L) waves. It's the shear and surface waves that generally cause the damage associated with earthquakes.

By measuring the time gap between the arrival of the P and S waves, it's possible to calculate how far away the earthquake was from the seismograph. This is roughly 500km for every minute between their arrival. The location of the epicentre is determined by a form of 'triangulation'.

To do this, a circle corresponding to the calculated distance is drawn

around at least three different seismograph locations on a map of the region. Where the circles intersect is the likely epicentre. Most earthquakes occur at depths of less than 100km.

P-waves have higher frequencies and are best detected with a 'Short Period (one second or less) Vertical Seismograph', while S, L and Rayleigh waves have lower frequencies and are best detected by a 'Long Period (10 seconds or longer) Seismograph', such as the design described here. Professional seismic stations have short, long and wide-band seismographs mounted north-south, east-west and also vertically, with both low and high-sensitivity detectors.

Analysis and filtering of the seismic patterns allows the arrival of each type of wave to be determined from the mixture of P, S, L and Rayleigh waves, reflections (PP and SS waves), refracted waves and alternative path surface waves. Our seismograph, with a one-second (or 10 second) sample rate, will probably only detect S-waves and the much larger displacement L-waves and Rayleigh waves. If you live very close to the action, such as in New Zealand or Papua New Guinea, you might also detect P-waves.

The Richter value, devised by Charles Richter in 1935, is basically a logarithmic measuring scale. It's calculated according to the largest ground motion waves that are detected 100km from the epicentre of the earthquake. Because the scale is logarithmic, a magnitude 7 earthquake has 10 times the ground motion (and more than 30 times the energy) of a magnitude 6 quake.

The Aceh Earthquake measured 9.0 on the Richter scale and released many thousands of times more energy than the 5.6 Newcastle earthquake of 1989.

by looking at the 'debug' screen), you must close down the PICAXE Programming Editor to free the COM Port, so that the StampPlot Lite program can use it. StampPlot Lite is available free from www.selmaware.com

Using StampPlot Lite

StampPlot Lite is the logging program. Once it's installed, you need to carry out the following steps:

(1) Set the COM port so that it's the same as the port that connects to the PICAXE.

(2) Change the Baud rate to 4800.

(3) Click on 'Connect' and 'Plot Data' – the program should immediately begin to graph the values sent by the PICAXE-08M. You can test this by blowing on the bar from a distance of about one metre. Adjust the Sensitivity control (VR1) for

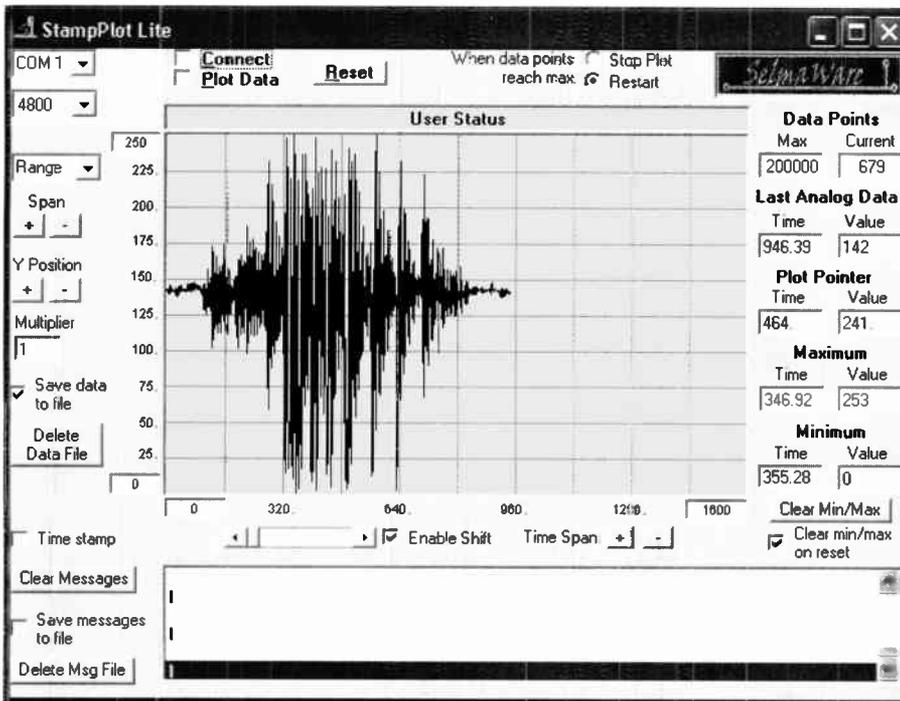


Fig.3: this simulated plot of an earthquake was produced during final sensitivity tests of the seismograph. A gentle puff of air aimed towards the seismograph masses from two metres away produced the first 'earthquake' waves, while similar puffs from one metre gave the full scale deflection.

Program Listing 1

```
main:
readadc10 4, b1      'makes an A-D conversion of the value at input 4 and sends to b1
debug b1            'allows you to see the value at b1 on the Picaxe debug screen
sertxd (#b1,cr,lf)  'sends the value of b1 out to the StampPlot Lite program
wait 1              'sets the time gap in seconds between readings
goto main           'makes the program loop back to the start
```

full-scale deflection. The 'action' near the bottom of the screen indicates that data is being collected.

(4) Set the maximum number of points to 200,000 or higher.

(5) A 'Time Span' of 400 seconds will show each swing of the bar during testing but increasing this to 25,600 will let you see most of a night's recording. The UK is normally a long way from the action and different types of earthquake waves will continue to arrive for more than an hour after a distant quake.

(6) Click on 'Save data to file' so the program saves the data as a .txt file.

(7) Click on 'Clear min/max on reset' and you will be able to see if any values have been detected that are significantly above the background line (ie, an earthquake) and when this occurred (approximately). If you deselect 'Connect' and 'Plot Data' to stop the recording, you can look back at stored parts of the graph by moving the bar next to 'Enable Shift'. The running graph can be seen on the screen and '.txt' values can be exported to Excel and graphed.

(8) Click on 'Time Stamp' so that Excel will show 'Time' on the graphs.

Good luck and I hope that the Earth moves for you. **EPE**

Acknowledgement: thanks to Dr Tom Hubble of the University of Sydney for his geological knowledge and neighbours Jo and Manfred for computing and design assistance.



www.epemag.com

Get your magazine 'instantly' anywhere in the world – buy and download from the web.

TAKE A LOOK, A FREE ISSUE IS AVAILABLE

A one year subscription (12 issues) costs just \$18.99 (US)

Back issues are also available

componentbin.com

Online Store!

Our online store contains an ever expanding variety of products designed for engineers, hobbyists and students. These include:

- ARM Development Systems
- Ethernet Modules
- RF Modules
- Graphic LCD Displays (With example software!)
- Home Automation
- Power Conversion
- Components & Connectors
- And Much More!
- Educational Discounts Available

Full product support with reference software and secure online ordering to kickstart your development.

www.componentbin.com
+44 (0) 1354 778224

SHERWOOD ELECTRONICS

PLEASE NOTE NEW MAIL ORDER ADDRESS

Buy 10 x £1 Special Packs and choose another one FREE

SP1 15 x 5mm Red LEDs	SP134 15 x 1N4007 diodes
SP2 12 x 5mm Green LEDs	SP135 5 x Miniature slide switches
SP3 12 x 5mm Yellow LEDs	SP136 3 x BFY50 transistors
SP5 25 x 5mm 1 part LEDs clips	SP137 4 x W005 1.5A bridge rectifiers
SP6 15 x 3mm Red LEDs	SP138 20 x 2/2/63V radial elect. caps.
SP7 12 x 3mm Green LEDs	SP142 2 x CMOS 4017
SP8 10 x 3mm Yellow LEDs	SP143 5 Pairs min. crocodile clips (Red & Black)
SP9 25 x 3mm 1 part LED clips	SP144 5 Pairs min. crocodile clips (assorted colours)
SP10 100 x 1N4148 diodes	SP146 10 x 2N3704 transistors
SP11 30 x 1N4001 diodes	SP147 5 x Stripboard 9 strips x 25 holes
SP12 30 x 1N4002 diodes	SP151 4 x 8mm Red LEDs
SP18 20 x BC182B transistors	SP152 4 x 8mm Green LEDs
SP20 20 x BC184B transistors	SP153 4 x 8mm Yellow LEDs
SP23 20 x BC549B transistors	SP154 15 x BC548B transistors
SP24 4 x CMOS 4001	SP155 3 x Stripboard, 14 strips x 27 holes
SP25 4 x 555 timers	SP160 10 x 2N3904 transistors
SP26 4 x 741 Op.Amps	SP161 10 x 2N3906 transistors
SP28 4 x CMOS 4011	SP164 2 x C106D thyristors
SP29 3 x CMOS 4013	SP165 2 x LF351 Op.Amps
SP33 4 x CMOS 4081	SP166 20 x 1N4003 diodes
SP34 20 x 1N914 diodes	SP167 5 x BC107 transistors
SP36 25 x 10/25V radial elect. caps.	SP168 5 x BC108 transistors
SP37 12 x 100/35V radial elect. caps.	SP171 8 Metres 18SWG solder
SP38 15 x 47/25V radial elect. caps.	SP172 4 x Standard slide switches
SP39 10 x 470/16V radial elect. caps.	SP173 10 x 220/25V radial elect. caps
SP40 15 x BC237 transistors	SP174 20 x 22/25V radial elect. caps
SP41 20 x Mixed transistors	SP175 20 x 1/63V radial elect. caps.
SP42 200 x Mixed 0.25W C.F. resistors	SP177 10 x 1A 20mm quick blow fuses
SP47 5 x Min. PB switches	SP178 10 x 2A 20mm quick blow fuses
SP49 4 x 5 metres stranded core wire	SP181 5 x Phono plugs - asstd colours
SP101 8 Metres 22SWG solder	SP182 20 x 4.7/63V radial elect. caps.
SP102 20 x 8-pin DIL sockets	SP183 20 x BC547B transistors
SP103 15 x 14-pin DIL sockets	SP189 4 x 5 metres solid core wire
SP104 15 x 16-pin DIL sockets	SP192 3 x CMOS 4066
SP109 15 x BC557B transistors	SP195 3 x 10mm Yellow LEDs
SP112 4 x CMOS 4093	SP197 6 x 20 pin DIL sockets
SP115 3 x 10mm Red LEDs	SP198 5 x 24 pin DIL sockets
SP116 3 x 10mm Green LEDs	SP199 5 x 2.5mm mono jack plugs
SP118 2 x CMOS 4047	SP200 5 x 2.5mm mono jack sockets
SP124 20 x Assorted ceramic disc caps	
SP126 6 x Battery clips - 3 ea. PP3 + PP9	
SP130 100 x Mixed 0.5W C.F. resistors	
SP131 2 x TL071 Op.Amps	
SP133 20 x 1N4004 diodes	

RESISTOR PACKS - C.Film

RP3 5 each value - total 365 0.25W	£3.40
RP7 10 each value - total 730 0.25W	£4.65
RP10 1000 popular values 0.25W	£6.60
RP4 5 each value-total 345 0.5W	£4.30
RP8 10 each value-total 690 0.5W	£6.95
RP11 1000 popular values 0.5W	£8.95

2007 Catalogue available £1 inc. P&P or FREE with first order. P&P £1.75 per order. NO VAT
Cheques and Postal Orders to:
**Sherwood Electronics,
10 NEWSTEAD STREET,
MANSFIELD, NOTTS. NG19 6JJ**

No Compromise Oscilloscope

Other oscilloscopes in this price range force you to compromise on one of the key specifications: sampling rate, memory depth or bandwidth.

The PicoScope 5000 series is a no compromise PC oscilloscope at a price every engineer can afford.

www.picotech.com/scope431 01480 396395

pico
Technology



1GS/s sampling rate
250MHz bandwidth
128M sample buffer memory
125MS/s 12 bit AWG built in

PicoScope 5203
32M buffer £1195

PicoScope 5204
128M buffer £1795

READOUT

Email: editorial@wimborne.co.uk

John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

All letters quoted here have previously been replied to directly.

WIN AN ATLAS LCR ANALYSER WORTH £79

An Atlas LCR Passive Component Analyser, kindly donated by Peak Electronic Design Ltd., will be awarded to the author of the *Letter Of The Month* each month.

The Atlas LCR automatically measures inductance from 1 μ H to 10H, capacitance from 1pF to 10,000 μ F and resistance from 1 Ω to 2M Ω with a basic accuracy of 1%.
www.peakelec.co.uk



★ LETTER OF THE MONTH ★

SMT Rework

Dear EPE,

The email from Edward Chase (*Readout*, Aug '07) brings to mind my adventures on a naval base in the early 90s. Some training simulator equipment was under development, based on a VME-bus computer rack, and there were problems with an interface for which I was expensively scrambled to have a look and see what was going on.

VME has an unfortunate feature, in that one of the bus address signals is immediately adjacent to a -12V supply rail. Working with one of the processor cards on an extender (an adapter, which lets you have a card running while accessible outside the rack), I was quickly probing the signals with a scope and accidentally shorted the address signal to the -12V pin, which promptly blew every card plugged into the rack at the time (which included, fortunately, only the ones needed for my particular debugging, having taken the precaution of removing the others). Two out of three processor cards had address buffers fried, but I needed two cards minimum to make any further progress, and it was a weekend so there was no access to spares or any tools I didn't have with me, and neither were the cards of my own company's manufacture.

I managed to trace the address signal from the edge connector to the relevant address buffer chip, which (woe-of-woes) was a 20-pin SOIC (i.e. surface mount, 0.05in lead pitch), but there were also lots more of these particular buffers used on the card. If I could do it with the tools to hand, I realised I could steal a good buffer from one of the dead cards to repair the other dead card, and along with the remaining live card be able to carry on the investigation - except that the tools to hand were no

more than normal pliers, cutters, screwdrivers, and a 15W soldering iron.

It has to be said that SOIC is probably the least difficult SMT package to deal with. I took a trip out to a local shop and bought a pack of wedding-dress pins (very fine, still in my tool kit to this day and also useful for probing a wire through its insulation), sacrificed a plastic biro as a handle and melted a pin into it, forming a tiny hook on the end of the pin. With the hook and soldering iron and a little extra solder to wet the joints, I worked my way around a dead chip lifting each lead in turn (practice) to get the chip off, then I did the same with a presumed good chip on the other dead board. The pins on the good chip, and the solder pads where it was to go, had to be levelled off by removing as much solder as possible with desoldering braid, and finally I was able to tack the chip into place and solder all round.

I'm proud to say it worked (though less proud of why I had to do it). I completed my debugging, and the maintenance people had a load of kit to send off for repair on the following Monday.

Bear in mind that was SOIC - 0.05in lead pitch. Edward Chase is asking about 0.5mm (0.02in)! No, that's not a mistake, they do exist (and even smaller). Normal workshop methods for hand assembly of SMT use hot air, and solder paste rather than wire. On the production line, the bare PCB has solder paste screen-printed onto it through a mask corresponding to the solder pads only, the components are placed onto the pads (and held by the stickiness of the solder paste), then the whole lot goes through an infra-red reflow oven (which melts the solder and completes the joints).

The biggest problem with hand assembly is stopping excess solder

bridging the incredibly narrow gaps between leads, or getting rid of it if it does. The really fine-pitched devices rely on the solder mask (a coating on the PCB that repels solder) to 'discourage' the melted solder going where it shouldn't, and only the minimum required amount of solder.

Lead-free solder is another issue. The higher temperatures required (for less time to avoid component and PCB damage) is tricky for hand assembly of conventional components, let alone SMT.

I'm not saying it can't be done, but Edward has to make a judgement whether there is anything to lose in a failed attempt (that might become irreparable in the process). Unless he has access to a professional SMT rework workstation, I would take on 0.05in, and maybe even 1mm, as long as the pins are easily accessible, but I would draw the line there and anticipate a long job. Of course, a lot of SMT chips these days have connections obscured under the device itself, and you might as well give up and go home.

Complete disassembly of an SMT board is simplicity itself: shine a hot-air paint stripper at it for a few moments, turn upside down and give it a sharp tap!

PS: If selected as Letter of the Month, donate to charity (yes, it's me again!)

**Ken Wood,
via email**

Thanks for those observations Ken. I trust Edward and others will find them useful.

Yes, you are LOM again - so thank you too for that generous offer. I leave it to HQ to decide which charity benefits.

Techno Talk and CFLs

Dear EPE,

I would disagree in part with *Techno Talk* Sept '07:

'Standard CFL bulbs do not work with existing dimmer switches', true, but no longer true. Versions are available.

'30 seconds and four minutes to reach full brightness', generally not true, although I could accept two minutes. Newer designs are faster and getting better all the time.

'Lamp life is reduced when CFLs are switched on and off frequently.' True of all lamps with the possible exception of LEDs. In this case there are other components within the 'driver', as the trade calls it, which may be affected - I've no data on this, however.

'Rapid death if they are allowed to overheat', true of all lamps, including LEDs.

'CFLs produce light in a narrow frequency range'. No, CFLs are triphosphor lamps with a colour rendering index of around 85%. The ordinary house lamp is indeed 100%, but I challenge anyone to notice a practical difference. However, the colour appearance is different, which is not the same as showing up colours.

'The future is SSL - solid-state lighting' - agreed!

Otherwise, I generally agree with this article. Philips are (privately) very confident about their LED technology, which should see real products early 2008.

Osram are already there, but not yet with practical replacements.

**Dave Geary,
via email.**

Dave thanks for that. We welcome your article on Banning the Bulb, elsewhere in this issue. Mark Nelson responds -

Thanks John for allowing me to comment. Dave Geary and I are not in major disagreement.

'Standard CFLs ... dimmer switches' - that's precisely why I used the word 'standard'. Versions are indeed 'becoming available ... that will', but that still does not apply to the standard ones you buy in the shops now.

Regarding brightness, Dave refers to newer ones and getting better. I accept this but I am referring to ones that I bought ten years ago and will happily send him as proof! I am happy to accept the delayed warm-up in return for longer life.

'Rapid death for all lamps' – OK, but I find them even less tolerant of confined shades.

'CFL frequency range' – I should have expressed myself more carefully but as Dave admits the colour appearance is different, he supports the point I made quite nicely. See also the top two graphs at www.darksky.org/images/light_spec, which illustrate clearly that the light quality is different.

**Mark Nelson,
via email**

CFLs

Dear EPE,

I received my June issue of *EPE* only recently. Nevertheless, I would like to comment on your editorial in that issue on compact fluorescent lamps.

First, it isn't exactly correct to describe the announcement in Australia as a 'ruling'. It was an announcement by one cabinet minister at one press conference of a plan to introduce this as a government policy. Since then, our government has been spectacularly quiet about the idea.

Probably because...

Second, it seems that the relevant cabinet minister didn't only forget to do his technical homework, he also forgot to do his legal homework. Our political system here is more like that in America than that in Britain. Our federal government has a lot of power, but its power is not unlimited and for some issues, the power is with the State governments, not with the Federal government. I expect this initiative to progress here at the speed of a thousand snails.

You and/or your readers might be interested in my experience with CFLs. When these first became available, in the early 1990s, partly just because I like to be modern, I embraced them enthusiastically and ruthlessly converted almost every light to use a CFL, even to the extent of replacing some quite expensive 'pride and joy' light fittings when I discovered that they couldn't support the weight or the size of the CFLs.

While some CFLs worked well, I encountered many problems. The first generation lamps were not anywhere near as reliable as the advertising claimed. It is significant that some were withdrawn promptly from the market and became unavailable.

For a while, the market was split. It became possible to buy reasonably reliable lamps for a reasonable price, but price was a poor indicator of reliability and about the only simple purchasing strategy was: 'cheap lamps are almost certain to be rubbish; expensive lamps are not certain to be worth the price; it is important to buy only one, test it, and if it is still working next year, and still available next year, it might be safe to buy some more of them'.

Clearly, this is a cumbersome strategy for buying something as simple and commonplace as a light bulb. Other problems include:

Your advice that normal CFLs are not dimmable is honest and accurate. I notice that some pro-CFL lobbyists claim that dimmable CFLs are available. This is true-ish, but only true-ish. The CFLs that work with dimmers must be special lamps, need special dimmers, and importantly, need an electrician to visit to install special wiring

and special light fittings. Once the wiring has been converted to use a dimmable CFL, it can't be used with anything other than a dimmable CFL. Dimmable CFLs are so different from what most people expect them to be that we probably need to invent a different word or phrase, perhaps 'dimmable' for the familiar and 'variable intensity' for CFLs.

A couple of friends have installed normal CFLs in circuits with normal dimmers. They promise that they always leave the dimmer set to full brightness, but their CFLs are spectacularly unreliable, and sometimes fail within a couple of months. I haven't investigated thoroughly, but I suspect that even at full brightness, the dimmer needs a few volts itself and delivers a voltage to the CFL that is sufficiently different from what it expects that some internal component is overstressed. A peek inside the base of a CFL reveals that the electronics are very definitely designed to 'domestic' standards, and even under ideal conditions totter on the brink of their stress limits.

Maybe I'm just fussy, but most styles look industrial and ugly. The current fashion for 'olde worlde' light fittings compounds this problem.

In some circuits, some modern lamps glow in the dark. It probably isn't a hazard, but it is certainly eerie and annoying. Probably, the next generation will include an extra component to fix this.

The colour temperature is not well explained, even less well understood, and poorly standardized. In most shops, these things are sold by shop assistants, not by physicists or photographers, and even simple questions can provide minutes of amusement and entertainment as shop assistants struggle to pretend that they know all about these volty and ampy things, usually revealing that they'd be much happier in the gardening section of the store.

The market has not improved and if anything, is worse now than a few years ago. While some prices have tumbled, rubbish is commonplace and buying a lamp worth its price is very much a 'lucky dip'. Even the longish life becomes part of the problem; if I believed in mysticism, I'd believe that the lamps know when I throw the receipt into the rubbish; pine for it, and fail within a few days so that they can join it.

Currently, I regard CFLs as 'too temperamental to be worth the trouble', and I am gradually converting most of my lights back to a variety of simple incandescent lamps. Although some of these are also rubbish, at least they are inexpensive rubbish.

**Keith Anderson,
Kingston, Tasmania,
via email**

Keith, we're sorry to hear of your problematic experience with these lamps. Perhaps the newer products Dave Geary speaks of in his article on the subject elsewhere in this issue may prove more reliable to you.

Disappointed programmer

Dear EPE,

Having received *EPE* and *PE* since the early 70's I am now beginning to regret my renewal for the next two years. The reason is simple, PICs! I've followed John's excellent *PIC Tutorials V1* and *V2* of which I understood every word, and that includes all his various projects published since. From this experience I even managed to program some of my own projects.

However, since the time some readers versed in C cajoled *EPE* to take it up, I rarely understand any of the writers who followed with their discussions. Not only has no one bothered to tackle C for beginners, but the present PIC writers sometimes bandy the buzz words without providing a glossary. What is I²C, SPI, bit banging or a bit-bashed USART, older directives, Boren bits, the LPTIOSC config bit, Bit PBADEN, capture mode. I could go on but it seems like one particular author (obviously an expert and very enthusiastic about his subject) is in a hurry to cover a lot of ground in minimum time but his erudition lost me a year ago because he deals with PIC subjects outside the bounds of my own experience.

Now I am aware from *EPE Chat Zone* that many readers are in the 'trade' and no doubt understand it all, or exactly where it fits any gaps in their own knowledge, or alternatively have means of reference. However, I am sure there must be many more readers like myself who are 'lone workers' with no one to refer to other than the Microchip website (run by experts for other experts). Incidentally, while having a moan, the only thing I learned about *Mechatronics* was how to spell it!

**Pat Alley,
via email**

I sent Pat's comments on to Mike Hibbett, who is the author providing EPE readers with more information on using C with PICs, and other aspects of PIC programming and use. Mike is a professional software writer, well versed in different methods for writing PIC software code. Personally, I have great respect for his knowledge, and have been learning much from what he has written for EPE. He replies:

I appreciate the comments, which are probably as a result of the attempt I am making to satisfy a wide range of reader's skills. So for example, one month I might cover 'how to read datasheets', and choose the terminology accordingly, and then another month discuss a very advanced topic (such as the I-wire bus system this month).

I'll do my best to give a more reasonable split in subject complexity in the future, but if there are any particular subjects that readers would like explained from a beginner's view point I would be very interested to hear – I'm always interested in new ideas for subjects!

**Mike Hibbett,
via email**

Pat, there is also the additional fact that it is not necessary to know C in order to program PICs, as you have already discovered through my PIC Tutorials. But I understand the desire of readers to know about C for PICs when they may already be partly familiar with C, but not necessarily in the PIC context.

Personally, I have a vague familiarity with using C, but wish to go on programming PICs through the assembly language route and am unlikely to change to C. I acknowledge that there will be many who disagree with my decision.

Regarding the terms you mention, most are covered in the datasheets for the PICs concerned. The intention of PIC 'n Mix and many other PIC-related articles is not to give an in depth view of a particular PIC, and it is expected that readers who are interested in that PIC will have already obtained a free datasheet for it from the Microchip website at: www.microchip.com.

Build Your Own Weather Station



- ▶ Measure Wind Speed
- ▶ Measure Wind Direction
- ▶ Measure Temperature
- ▶ Easy Build Kit
- ▶ FREE Software
- ▶ USB or RS232
- ▶ Optional Humidity Module
- ▶ Optional Pressure Module
- ▶ Optional Rainfall Gauge
- ▶ Simple 1-wire® connection
- ▶ Build and add your own devices

Weather Starter Kit	£59
RS232 Interface	£25
USB Interface	£29
Humidity Module	£39
Pressure Module	£49
Rainfall Gauge	£59

Prices exclude VAT and delivery

For more information, manuals and downloads on this and other interesting products see www.audon.co.uk

audon Electronics

www.audon.co.uk | +44 (0)115 925 8412 | Fax +44 (0)115 925 9757

MAGENTA ELECTRONICS LTD

135 Hunter Street Burton on Trent Staffs DE14 2ST
Tel: 44 (0)1283 565435 Fax: 44 (0)1283 546932

Chips, Parts & Kits for EPE Projects

Programmed PICs and chips for most EPE projects. Check our website or 'phone for prices. We have supplied kits for EPE* projects for almost 30 years!! (& Everyday Electronics)

20W Stereo Amp.

Wide band Low distortion 11W /channel Stereo 20W Mono. True (rms) Real Power

Short Circuit & Overheat Protected. Needs 8 to 18V supply.

(Kit inc. all parts & heatsink for stereo or mono)

KIT 914- £11.90



Latest Technology - Stable, Reliable, high performance

Top Kits.

ICEbreaker PIC16F877 in - circuit emulator - Kit 900... £34.99

1kV/500V Insulation Tester Inc. drilled case -Kit 848.. £32.95

Pipe Descaler - High Power with led monitor - Kit 868..£22.95

Ultrasonic PeST Scarer random 32k pulses Kit867..£19.99

P-I Metal Detector Micro based design - sensitive Kit847..£63.95

MAGENTA Bat Detectors

Our original famous KIT detector KIT 861...£37.99 & See the new built MKIIb and MKIII on the web.

All Prices Include VAT, Add £3.00 P&P per order, or £7.99 for next day. Chqs. P.O. & most major cards accepted. Mail Order Only.

MAGENTA www.magenta2000.co.uk
sales@magenta2000.co.uk

PEAK

electronic design

tel. 01298 70012
fax. 01298 70046
www.peakelec.co.uk
sales@peakelec.co.uk

Handheld Test Gear - Cool, Smart.



Atlas DCA **£55**

Atlas DCA Model DCA55 Semiconductor Analyser



Atlas ESR **£89**

Atlas ESR Model ESR60 ESR and Capacitance Meter



Atlas LCR **£79**

Atlas LCR Model LCR40 Inductor, Capacitor, Resistor Analyser



Atlas SCR **£99**

Atlas SCR Model SCR100 Triac and Thyristor Analyser

UK. Please add £1.00 p&p to your order. Prices include UK VAT. Please see website for overseas pricing.

NEW! High Capacity Alkalines! At Silly Prices!



2 x C Ultra Alkaline



8 x AAA Ultra Alkaline



2 x D Ultra Alkaline



9v PP3 Ultra Alkaline



GP23A/MN2 12V Ultra Alkaline



12 x AA Ultra Alkaline

Net Work



Alan Winstanley

First steps in broadband

A friend who works from home asked for recommendations for a broadband supplier, as they wanted to adopt Internet access for their new business. The bewildering array of choices made it a difficult question to answer. First, the availability of ADSL (asymmetric digital subscriber line) broadband depends on whether the local phone exchange is equipped to provide it, and performance then depends on the distance the signal travels in terms of copper wire miles, poor connections and the quality of the wiring.

Much has been highlighted recently about the unfair marketing practices of broadband suppliers, especially about adverts with headline-grabbing speeds of 'up to' 8Mbps (megabits per second), when in reality such speeds are often impossible to achieve due to the limiting factors of distance, congestion and line quality.

Whether buying broadband as a new customer, or upgrading an existing service, the first thing to be aware of is the disclaimer that performance is subject to practical line tests after you place an order, and second, no ISP is likely to guarantee the transmission rate that you will actually experience. Websites such as Virgin Media's broadband checker <http://broadbandchecker.co.uk/> indicate the likely availability in your postcode area, and comparison websites, including www.broadbandchoices.co.uk and www.uswitch.com, offer alternatives for you to choose from.

Broadband suppliers have their own merits – including cost, locally-based services, free or premium technical support or free hardware. Sometimes, an introductory discount is available for the first few months. Some areas have cable access, so the choice of supplier is restricted, but for most of us broadband means ADSL, delivered by your choice of ISP through your BT phone line. In rural areas, perhaps consider satellite or find out if a local specialist service is available. One example is the wireless mesh service offered by the award-winning company South Witham Broadband (www.wireless.southwitham.net/), which was built by local people to deliver broadband to their villages.

There was a time when AOL (www.aol.co.uk/) compact disks were found on every computer magazine (and in every letterbox – see www.nomoreoldcds.com). AOL is firmly a family-orientated service that uses proprietary software for mail and browsing: I know of some AOL users who were aghast at the prospect of firing up Internet Explorer or Outlook Express on their AOL connection!

AOL encapsulates its customers in a safe environment away from the wild west of the Internet. Most other ISPs just provide raw broadband connections and associated services, such as anti-spam and antivirus, and they just leave you, your wits and your computer to fend for themselves out on the Internet.

The need for speed

Casual users will be happy with 2Mbps speeds but most will probably opt for a rate of (up to) 8Mbps. The cheapest packages may have a monthly ceiling of data transfer but

many tariff packages have no capped usage restrictions, subject to their interpretation of 'fair use' – your connection may be throttled back or even suspended altogether, if you regularly overdo your downloads.

ISPs may tempt new customers with a **free modem or router**: however, as mentioned before in *Net Work*, only a router properly set up for security should be considered good enough. A single-port straight-through modem is insecure and is best discarded. Wireless networks should also be set up robustly for security, to prevent unauthorised use of your broadband by your neighbours or 'drive-by' users. Setting up a secure wireless network may require specialist help, and an hour's expert labour might be money well spent. PC World's The Tech Guys charge from £69.99 (www.thetechguys.com/) for this.

Another consideration might be the sending of **own domain-name mail**: some ISPs (notably BT) suffer a major malfunction when their customers send mail as 'From: *user@myowndomain.co.uk*.' BT has been known to block legitimate mail because they disputed the domain name details.

Outbound mail servers can be slow or busy especially if networks are overloaded with spam. Rather than rely on the broadband supplier's SMTP server, the classic workaround for sending outbound (SMTP) mail is to use an authenticated third party mailservice, notably Authsmtp (www.authsmtp.net), which is a robust low-cost service that removes the dependence on your ISP's SMTP servers. This is also relevant if you intend to send out bulk Email campaigns regularly. In June 2007 Tiscali users found to their cost that relying on an ISP's own SMTP service was not always wise, as there was an outage lasting for about a week.

The foregoing factors are some key points to consider when shopping around for an ISP. It should not be forgotten that some Internet users have very low usage requirements and are happy with 56k dial-up access for checking email or for occasional web surfing, paying say 5p per call added to their BT phone bill. It may well pay to examine the benefits of always-on high speed broadband though: even if it costs more. For some users the time saved over waiting for dial-up can make broadband worthwhile.

Both dial-up and broadband users could gain a useful increase in speed by using the download accelerator service from Onspeed (www.on-speed.com). For a flat rate of £24.99 or €39.99 a year, Onspeed promises a tenfold increase for dial-up and five times increase for broadband users. Web pages, emails and some file types are compressed 'on the fly' using Onspeed's patented server-based technologies, and then uncompressed on the client's PC using Onspeed's software. It is claimed to work in most countries apart from certain African or Middle Eastern areas.

Next month some of the current anti-virus software packages are outlined. You can email Alan at: alan@epemag.demon.co.uk

ONSPEED
WHILE OFFICIAL INTERNET

"Speed up all your Internet connections
**Dial-up, Broadband
and Mobile Phones**"

ONSPEED for **Dial Up** ONSPEED for **Broadband** ONSPEED for **Mobile**

£24.99 a year £24.99 a year £24.99 a year

Onspeed offers to accelerate Internet speeds for dial-up, broadband and mobile users, using a patented file-type compression technology

Check out our website, 1,000s of items in stock.



PM3082 - £195



HP 34401A - £500 to £550



HP33120A - £575 to £700



HP 8563A - £6,000

DIGITISING/STORAGE OSCILLOSCOPES

HP 54616B Digitising 500MHz 2GS/S 2 Channel	£1,100
TEKTRONIX TDS520 Digitising 500MHz 500MS/S 2 Channel	£800
TEKTRONIX TDS360 Digitising 200MHz 1GS/S 2 Channel	£650
TEKTRONIX 2232 Dual Trace 100MHz 100MS/S	£325
HP 54600B Dual Trace 100MHz 20MS/S with RS232, 2HP Probes, Ops Manual, Pouch & Front Cover	£325
TEKTRONIX TDS224 Digitising 100MHz 4 Channel 1GS/S	£750

SCOPEMETERS

FLUKE 97 Dual Trace 50MHz 25 MS/S	£295
-----------------------------------	------

OSCILLOSCOPES

TEKTRONIX 2465B 4 Channel 400MHz Delay Cursors etc inc Tek Probes	£750
PHILIPS PM3082 2+2 Channels 100MHz Delay TB etc Autoset	£195
TEKTRONIX 2445A 4 Channel 150MHz Delay Sweep Cursor etc	£375
GRUULD OS300 Dual Trace 20MHz	£75
PHILIPS PM3217 Dual Trace 50MHz Delay Sweep	£125
FARNELL DTV12-14 Dual Trace 12MHz	£40
TEKTRONIX P6139A 100MHz Probes - Unused	£140

STEWART of READING

17A King Street, Mortimer, Near Reading RG7 3RS
 Telephone: (0118) 933 1111
 Fax: (0118) 933 2375
 www.stewart-of-reading.co.uk
 9am-5.00pm Monday to Friday



MARCONI 2024 - £1,250 to £1,500

SPECTRUM ANALYSERS

HP 8563A 9KHz-22GHz Synthesised	£6,000
HP 8560A 50Hz-2.9GHz Synthesised Various opts.	£1,900-£3,250
HP 8530A 10KHz-1.5GHz	£1,400
HP 3580A 5Hz-50KHz	£295
ADVANTEST TR4132 100KHz-1000MHz	£750

SIGNAL GENERATORS

HP 83731A Synthesised 1-20GHz	£5,000
Marconi 2032 Sig Gen 10KHz-5.4GHz Opt 01/02/06	£3,250
Avionics	£750
HP 8648A Sig Gen 0.1-1000MHz	£750
Cigatronix 7100 Synth 10MHz-20GHz (internal sweep/mod -130 to +15-IBM)	£3,000
Marconi 2024 9KHz-2.4GHz - HPIB used/unused	£1,250-£1,500
Marconi 2022E Synthesised AM/FM 10KHz-1.01GHz	£500
Marconi 2019A Synthesised AM/FM 80KHz-1040MHz used/unused	£150-£195
HP 33120A Function Gen. 100 microHz-15MHz	£575-£700
T T I TG211 Function Gen 0.002Hz-2MHz TTL etc	£70
R&S APN62 Synth Function Gen 1Hz-260KHz Bal/Unbal Output LCD	£195
Metrix CX5000 Pulse Gen 50MHz Programmable	£150
HP 3325A Synthesised Function Gen 21MHz	£295

HF 3312A Funct on Gen 0.1Hz-13MHz AM/FM Sweep/Tn/Burst etc	£175
HF 8112A Pulse Gen 50MHz	£350
HF 8116 Pulse/Function Gen 50MHz	£750
Geuld J38 Sine/Sq-Osc 10Hz-100KHz Low Distortion	£50-£75

FREQUENCY COUNTER/TIMERS

HP 5350B Counter 20 GHz	£750
Marconi 2440 Counter 20 GHz	£500
Riscal 1998 Counter 10Hz-1.3GHz	£225
Riscal 1991 Counter/Timer 160MHz 9 Digit	£150
HP 53131A Univer. al Counter 3GHz Opt. 001 oven unused/used	£995/£750
HP 53131A Universal Counter 225MHz Oven-in original boxes - unused/used	£700/£600

DIGITAL MULTIMETERS

HP/Agilent 34401A 6 1/2 Digit	£500/£550
Sclartron 7150Plus 6 1/2 Digit True RMS IEEE with temp measurement	£75
F Jke 77 series 2 1/2 Digit Handheld	£45
A/O 8 Mk6 In Ever Ready Case with Leads etc.	£75
A/O 8 Mk5 with Leads etc	£50
Goodwill GVT427 Dual Ch AC Millivoltmeter 10mV in 12 ranges 10Hz-1MHz Unused	£60

MISCELLANEOUS

MARCONI 2955A Radio Communications Test Set	£1,000
MARCONI 2955 Radio Communications Test Set	£625
MARCONI 6960B RF Power Meter with head	£500
MARCONI 893C AF Power Meter S nad Measurement Unused	£50
HP 4192A Impedance Analyser with 16047A Text Fixture etc	£3,500
HP 8902A Measuring Receiver 150KHz-1300MHz	£4,500
HP 85032A Calibration Kits	£400
SEAWARD Nova Pat Tester	£195
BIRD 43 Wattmeter - Many Elements Available	£75
HUNTRON 1K00 Tracker	£75
RACAL DANIA 9343M LCR Database Digital Auto Measurements of RCL QD	£95
RACAL 900B Automatic Modulator Meter 1.5MHz-2GHz	£60
MEGGER PAT2 Tester	£95

POWER SUPPLIES

FARNELL AP60/50 0-60V 0-50A 1kW Switch Mode	£400
FARNELL HEB250-60V 0-25A	£400
THURLBY PL320QMD 0-30V 0-2A Twice Digital	£160
H P 6626A Precision High Resolution 4 Outputs C-7V 0-15mA or 0-50V 0-0.5A Twice 0-16V 0-0.2A or 0-50V 0-0.2A Twice	£500
FARNELL XA35 2T 0-35V 0-2A Twice Digital	£95
FARNELL B30/1030V 10A Variable No Meters	£55
FARNELL L730-10-30 0-1A Twice	£60
FARNELL L30 2 0-30v 0-2A	£50
THURLBY PL3300-32V 0-3A Digital (Kenwood badged)	£75
THURLBY PL320-30V 0-2A Digital	£55
TAKASAGO GM035-2 0-35V 0-2A2 Meters	£35

Used Equipment - GUARANTEED.

Most Manuals supplied

Please check availability before ordering or calling.

Prices plus carriage and VAT



All Major Credit Cards Accepted!

ElmScan 5 USB Scan Tool

- Diagnose any car with EOBD
- Based on the ELM327 IC
- Supports all EOBD and OBD-II protocols
 - ✓ ISO15765-4 (CAN)
 - ✓ ISO14230-4 (Keyword 2000)
 - ✓ ISO9141-2
 - ✓ J1850 VPW
 - ✓ J1850 PWM
- 9600 or 38400 baud
- Supported by more software than any other OBD interface
- Inexpensive
- Full Speed USB 1.1
- Automatic protocol detection
- Package includes cables, software CD, and Quick Start Guide
- Buy from your local UK distributors!

www.ElmScan5.com/epe

EP EVERYDAY PRACTICAL ELECTRONICS

NEWSAGENTS ORDER FORM

Please reserve/deliver a copy of *Everyday Practical Electronics* for me each month

Name and Address

Postcode Tel

Everyday Practical Electronics is published on the second Thursday of each month and distributed S.O.R. by SEYMOUR
 Make sure of your copy each month - cut out or photocopy this form, fill it in and hand it to your newsagent

PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. Double-sided boards are NOT plated through hole and will require 'vias' and some components soldering both sides. All prices include VAT and postage and packing. Add £1 per board for *airmail* outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU. Tel: 01202 873872; Fax 01202 874562; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm.** Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only). **NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail.** Back numbers or photocopies of articles are available if required – see the *Back Issues* page for details. We do not supply kits or components for our projects.

Please check price and availability in the latest issue. A large number of older boards are listed on, and can be ordered from, our website. Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
★ Keypad Alarm	FEB '06 552	£6.02
3-Way Active Crossover	553	£9.20
Jazzy Heart	554	£6.02
Status Monitor – Transmitter	555	} pair £7.61
– Receiver	556	
Power Up	MAR '06 557	£6.82
Video/Audio Booster (double-sided)	558	£12.00
★ Telescope Interface	559	£6.50
'Smart' Slave Flash	APR '06 560	£6.18
Programmable Continuity Tester	561	£5.87
PortaPAL		
– Microphone Board	562	£6.18
– Auxiliary Board	563	£5.87
– Main Board	564	£8.56
– Charger Board	565	£6.66
Omni Pendulum	566	£6.34
Smart Card Reader/Programmer	MAY '06 567	£7.61
LED Lighting For Your Car (set of 15 boards)	568	£14.75
Digital Reaction Timer	569	£7.13
Poor Man's Metal Locator	JUN '06 570	£5.71
★ Digital Instrument Display for Cars		
– Micro Board	571	} pair £7.77
– Display Board	572	
Widgy Box	573	£7.29
Phone Ring & Test	574	£6.82
★ Sudoku Unit	JUL '06 575	£6.66
PC Power Monitor	576	£6.50
Home Theatre Sound Level Checker	AUG '06 577	£6.66
Adjustable DC-DC Converter For Cars	578	£6.50
★ Telephone Dialler For Buglar Alarms	579	£6.97
★ High Intensity Torch	580	£5.39
★ Low Cost 50MHz Frequency Meter	SEP '06	
Version 1	581	£6.66
Version 2	582	£6.66
Version 3	583	£6.66
Smart Mixture Display for your Car	584	£6.50
Water Level Gauge – Sensor	585	} pair £6.98
– Display	586	
Fridge Door-Open Alarm	OCT '06 587	£5.71
Linear Supply For 1W Star LEDs (Pair)	588a & b	£6.50
Through-Glass Alarm	589	£7.61
Quick Brake	NOV '06 590	£6.50
Studio 350 Power Amplifier	591	£9.51
Micropower Battery Protector	592	£5.71
★ Giant LED Message Display – Master	594	£5.55
– Slave	595	£6.50
Lapel Microphone Adaptor	DEC '06 593	£6.18
RGB To Component Video Converter (double sided)	596	£12.69
USB Power Injector	597	£5.87
★ Mind Trainer	598	£6.50
Balanced Microphone Preamp	JAN '07 599	£6.82
High-Efficiency Power Supply for 1W Star LEDs	600	£6.19
Jumping Spider	601	£5.71
★ Programmable Robot	FEB '07 602	£6.50
Courtesy Light Delay	603	£5.87
★ Deep Cycle Battery Charger		
Power Board	604	} set £11.10
Control Board	605	
Display Board	606	
★ PIC Digital Geiger Counter (double sided)	607	£12.53

PROJECT TITLE	Order Code	Cost
IR Remote Checker	MAR '07 608	£6.35
★ SMS Controller	609	£7.93
★ Lap Counter For Swimming Pools	610	£7.14
★ PIC Polyphonium – Main Board	611	£8.25
PIC Polyphonium – LED Display Interface	APR '07 612	£7.13
Students' Amp – Amplifier	613	£6.02
– PSU	614	£6.02
Star Power	615	£6.50
Bass Extender	MAY '07 618	£5.87
Caravan Lights Check	619	£6.18
★ Energy Meter – Main Board	JUN '07 616	} pair £9.83
– Display Board	617	
3V to 9V Converter (PCB plus TL499A IC)	620 + chip	£7.53
Bat Sonar	621	£6.03
MiniCal 5V Meter Calibration Standard	JUL '07 622	£6.82
Lead-Acid Battery Zapper	623	£6.50
Video Reading Aid	624	£6.50
Digi-Flash Slave	625	£5.55
TwinTen Stereo Amplifier	AUG '07 626	£9.83
Printer Port Hardware Simulator	627	£6.66
★ RFID Security Module	628	£6.02
★ V2 PC Scope – Control Board	629	£7.13
Analogue Board	630	£6.50
★ Flexitimer – Main Board	SEPT '07 631	£7.29
– Display Board 1	632	£7.29
– Display Board 2	633	£7.29
– Display Board 3	634	£7.29
Pocket Tens Unit	635	£6.35
★ Simple Seismograph	OCT '07 636	£6.66
★ V8 Doorbell		
– Main Board	637	} pair £11.42
– Display Board	638	
★ Standby Power Saver		
– Transmitter	639	£6.34
– Receiver	640	} pair £6.97
– PSU	641	

EPE SOFTWARE

★ All software programs for *EPE* Projects marked with an asterisk, and others previously published, can be downloaded free from our Downloads site, accessible via our home page at: www.epemag.co.uk.

PCB MASTERS

PCB masters for boards published from the March '06 issue onwards can also be downloaded from our UK website (www.epemag.co.uk); go to the "Downloads" section.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code	Project	Quantity	Price
Name			
Address			
Tel. No.			
I enclose payment of £..... (cheque/PO in £ sterling only) to:			
			
Everyday Practical Electronics			
			
MasterCard, Amex, Diners Club, Visa or Switch/Maestro			
Card No			
Valid From		Expiry Date	
Card Security Code		Maestro Issue No	
(The last 3 digits on or just under the signature strip)			
Signature			
NOTE: You can also order p.c.b.s by phone, Fax, Email or via the shop on our website on a secure server: http://www.epemag.co.uk			

CLASSIFIED ADVERTISEMENTS

EPE EVERYDAY PRACTICAL ELECTRONICS

Everyday Practical Electronics reaches more UK readers than any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last twenty-two years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £10 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU. Phone: 01202 873872. Fax: 01202 874562. Email: epeads@wimborne.co.uk. For rates and information on display and classified advertising please contact our Advertisement Manager, Stewart Kearn as above.

RSH ELECTRONICS
 UK & International Suppliers of Electronic Components & Kits
New Look Website - Extended Ranges - Lower Prices
 Capacitors Resistors Transistors Optoelectronics PCBs Breadboard
 Solder Switches Cable Batteries Tools CMOS ICs Potentiometers
 P&P £2.50 (orders over £25 free P&P) No Min Order. No VAT
ORDER ONLINE AT OUR ALL NEW WEBSITE:
www.rshelectronics.co.uk

**BTEC ELECTRONICS
 TECHNICIAN TRAINING**
**NATIONAL ELECTRONICS
 VCE ADVANCED ICT
 HNC AND HND ELECTRONICS
 FOUNDATION DEGREES
 NVQ ENGINEERING AND IT
 DESIGN AND TECHNOLOGY**
LONDON ELECTRONICS COLLEGE
 20 PENYVERN ROAD
 EARLS COURT, LONDON SW5 9SU
 TEL: (020) 7373 8721
www.lec.org.uk

BOWOOD ELECTRONICS LTD
Suppliers of Electronic Components
 Place a secure order on our website or call our sales line
 All major credit cards accepted
 Web: www.bowood-electronics.co.uk
 Unit 1, McGregor's Way, Turnoaks Business Park,
 Chesterfield, S49 2WB. Sales: 01246 200222
 Send 69p stamp for catalogue

GPS video overlay unit

 Display GPS data as text over the signal from any composite video camera.
WWW.STV5730A.CO.UK

**THIS SPACE
 COULD BE YOURS
 FOR JUST £50**
Contact Stewart on 01202 873872
stewart.kearn@wimborne.co.uk

VALVES AND ALLIED COMPONENTS IN STOCK. Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.
FOR ½ PRICE VALVE CLEARANCE catalogue send £1.00 in 1st or 2nd class stamps **FOR COMBINED VALVE & COMPONENT CLEARANCE** list send £1.50 in 1st or 2nd class stamps. W. Burcher, 676 Foxhall Road, Ipswich, Suffolk. IP3 8NQ. Tel: 01473 272218.

ELECTRONICS TEACH-IN

On Sale Now at WHS £6.99

N.R. BARDWELL Ltd – est 1948
Electronic Component Supplies
 LED's, Semis, IC's Resistors, Caps, etc send 44p for lists. 1000's bargains at our secure site: www.bardwells.co.uk
 288, Abbeydale Rd. Sheffield. S7 1FL
0845 166 2329 (local rate)

EPE Online
www.epemag.com
Get your magazine 'instantly' anywhere in the world – buy and download from the web.
TAKE A LOOK, A FREE ISSUE IS AVAILABLE
A one year subscription (12 issues) costs just \$18.99 (US)
Back issues are also available



Europe's Largest Surplus Store

20,000,000 Items on line NOW!
New items added daily

Established for over 25 years, UK company Display Electronics prides itself on offering a massive range of electronic and associated electro-mechanical equipment and parts to the Hobbyist, Educational and Industrial user. Many current and obsolete hard to get parts are available from our vast stocks, which include:

- ◆ 6,000,000 Semiconductors
- ◆ 5,000 Power Supplies
- ◆ 25,000 Electric Motors
- ◆ 10,000 Connectors
- ◆ 100,000 Relays & Contactors
- ◆ 2000 Rack Cabinets & Accessories
- ◆ 4000 Items of Test Equipment
- ◆ 5000 Hard Disk Drives

We Ship Worldwide

Surplus Wanted

www.distel.co.uk

Display Electronics
29 / 35 Osborne Road
Thornton Heath
Surrey UK CR7 8PD

Telephone
[44] 020 8653 3333
Fax [44] 020 8653 8888



Rechargeable Batteries With Solder Tags

NIMH		NICAD	
AA 2000mAh	£2.82	AA 650mAh	£1.41
C 4Ah	£4.70	C 2.5Ah	£3.60
D 9Ah	£7.60	D 4Ah	£4.95
PP3 150mAh	£4.95		

Instrument case with edge connector and screw terminals

Size 112mm x 52mm x 105mm tall

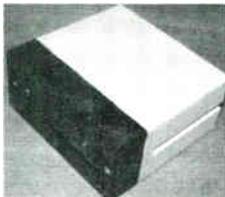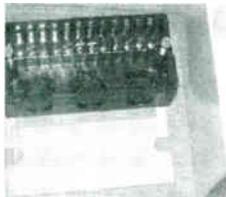This box consists of a cream base with a PCB slot, a cover plate to protect your circuit, a black lid with a 12 way edge connector and 12 screw terminals built in (8mm pitch) and 2 screws to hold the lid on. The cream bases have minor marks from dust and handling price £2.00 + VAT(=£2.35) for a sample or £44.00+VAT (=£51.70) for a box of 44.



866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily £7.46 + VAT = £8.77



Please add £1.66 + VAT = £1.95 postage & packing per order

JPG Electronics
Shaws Row, Old Road, Chesterfield, S40 2RB.
Tel 01246 211202 Fax 01246 550959
www.JPGElectronics.com
Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

EP EVERYDAY PRACTICAL ELECTRONICS

NEXT MONTH

TEACH-IN 2008 – Using PIC Microcontrollers

TEACH-IN 2008 takes a slightly different format to previous Teach-Ins. Whereas the earlier ones have concentrated on telling you about components and how to use them in general, Teach-In 2008 takes a specific component, a PIC microcontroller, and examines it in detail, providing information on how to use PICs in your own projects.

Constructional examples will be given in each part and a simple PIC programmer is described in Part 1.

ELECTROCARDIOGRAPH

An easy-to-build project which will let you take your own electrocardiogram (ECG) and display it on a PC. You can read, display, save to disk and print the electrical waveform generated by your heart – or anyone else's.

VEHICLE MULTI-VOLTAGE MONITOR

Want to monitor the battery voltage, the airflow meter or oxygen sensor signals in your car? This versatile voltage monitor can do it all and includes display dimming so the LEDs are not too bright at night.

NOVEMBER '07 ISSUE ON SALE OCTOBER 11

ADVERTISERS INDEX

AGAR CIRCUITS	.45
AUDON ELECTRONICS	.75
BETA-LAYOUT	.58
BRUNNING SOFTWARE	.21
BULL GROUP	Cover (ii)
COMPACT CONTROL DESIGN	.4
DISPLAY ELECTRONICS	.80
ESR ELECTRONIC COMPONENTS	.6
JAYCAR ELECTRONICS	.22/23
JPG ELECTRONICS	.80
LABCENTER	Cover (iv)
LASER BUSINESS SYSTEMS	.45
LEKTRONIX LTD	.26
MAGENTA ELECTRONICS	.75
MICROCHIP	.5
MIKROELEKTRONIKA	.59
NURVE NETWORKS LLC	.39
PEAK ELECTRONIC DESIGN	.75
PICO TECHNOLOGY	.72
RAPID	Cover (iii)
RADIOMETRIX	.39
R.K. EDUCATION	.58
QUASAR ELECTRONICS	.2/3
SCANTOOL	.77
SHERWOOD ELECTRONICS	.72
STEWART OF READING	.77
TECHNOBOTS	.11
TSIEN	.72

ADVERTISEMENT OFFICES:

SEQUOIA HOUSE, 398A RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AU
PHONE: 01202 873872 FAX: 01202 874562

EMAIL: epheads@wimborne.co.uk

For Editorial address and phone numbers see page 7

Everyday Practical Electronics, ISSN 0262 3617 is published monthly (12 times per year) by Wimborne Publishing Ltd., USA agent USACAN Media Dist. Srv. Corp. at 26 Power Dam Way Suite S1-S3, Plattsburgh, NY 12901. Periodicals postage paid at Plattsburgh, NY and at additional mailing Offices. POSTMASTER: Send address changes to Everyday Practical Electronics, c/o Express Mag., PO Box 2769, Plattsburgh, NY, USA 12901-0239.

Cables & connectors

Connectors:
audio/video
mains/power
multipole
RF/coaxial
single pole

Electrical & power

Electrical products
& lighting
Fans & motors
Fuses & circuit breakers
Security & warning
devices
Batteries

Electronic components

Capacitors
Inductors & chokes
Filters & suppression
Resistors &
potentiometers
Transformers
Relays & solenoids
Sensors
Switches
Cptoelectronics
Discrete
semiconductors
Integrated Circuits
Micros & crystals
Semiconductor
hardware

Tools, fasteners & production equipment

Cases
Fasteners & fixings
Storage/packing
equipment
Health & safety
Service aids
Soldering equipment
Test equipment
Electronic/electrical
tools
Mechanical tools
Power tools



Velleman 5 in 1 Emergency tool mini-kit
Order code: 70-4060
Only **£8.95**



Velleman FM Radio kit
Order code: 70-4024
Only **£10.55**



224 Piece Ceramic capacitor kit
Order code: 13-0206
Only **£6.50**



510 Piece Carbon film resistor kit
Order code: 13-0201
Only **£5.50**



Pliers set 4 piece
Order code: 86-0662
Only **£8.95**



123 Robotic projects for Evil Genius
Order code: 97-6034
Only **£14.99**



200mm Red cable ties pack 100
Order code: 04-0647
Only **£1.40**



Screwdriver set 75 piece
Order code: 86-0654
Only **£14.95**



4.0MHz HC-49/U Crystal
Order code: 90-0145
From **15p**



16 x 1 Alphanumeric LCD display
Order code: 57-0906
Only **£5.80**



L297 Stepper motor driver
Order code: 82-0198
Only **£6.95**



L293 4 Channel driver
Order code: 82-0192
Only **£3.19**



4 Phase Unipolar stepper motor
Order code: 37-0507
Only **£7.00**



IQ2 Programmable controller
Order code: 13-0910
Only **£9.20**

All prices exclude VAT

Request your free catalogue by sending your full contact details and quote reference EPE to marketing@rapidelec.co.uk

FREE DELIVERY

On all orders over £25
(excluding VAT)
UK mainland only

SAME DAY DESPATCH

NO MINIMUM ORDER

UK mainland only

TECHNICAL ADVICE

DATASHEETS

CALL & COLLECT

TRADE COUNTER



www.rapidonline.com

Tel: **01206 751166**
Fax: **01206 751188**
sales@rapidelec.co.uk

Rapid, Severalls Lane, Colchester,
Essex CO4 5JS

World Radio History

defining the standard

PROTEUS DESIGN SUITE

TIME FOR A CHANGE ?



NEW IN DESIGN SUITE 7:

NEW: Redesigned User Interface includes modeless selection, modeless wiring and intuitive operation to maximise speed and ease of use.

NEW: Design Explorer provides easy navigation, design inspection tools and cross-probing support to improve quality assurance and assist with fault finding.

NEW: 3D Visualisation Engine provides the means to preview boards in the context of a mechanical design prior to physical prototyping.

NEW: Simulation Advisor includes reporting on simulation problems with links to detailed troubleshooting information where appropriate.

NEW: Trace capability within both MCU and peripheral models provides detailed information on system operation which allows for faster debugging of both hardware and software problems.

NEW: Hundreds of new device models including PIC24, LPC2000, network controllers and general purpose electronic components.

Electronic Design From Concept To Completion

Labcenter  www.labcenter.com
Electronics

Labcenter Electronics Limited
Registered in England 4692454

E-mail: info@labcenter.com

Tel: +44 (0) 1756 753440

Fax: +44 (0) 1756 752857

Registered Address: 53-55 Main Street, Grassington, North Yorks, UK, BD23 5AA