

# PRACTICAL ELECTRONICS


NOVEMBER 1968

THREE SHILLINGS

*This Month...*

**RHYTHM  
GENERATOR**

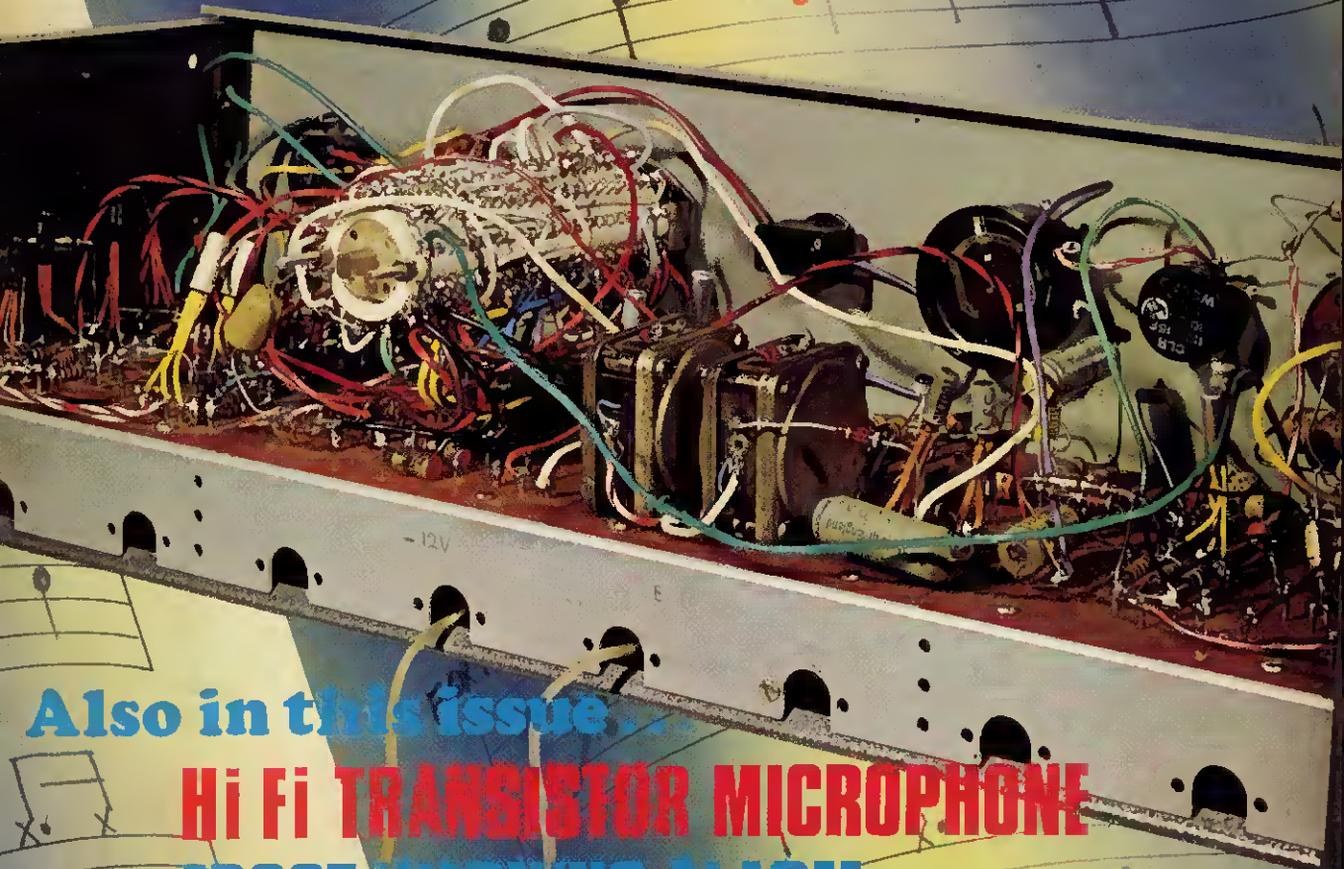*Samba...*  
*Waltz...*  
*Gha Gha Gha...*  
*Quick-Stop...*



**Also in this issue...**

**Hi Fi TRANSISTOR MICROPHONE  
FROST WARNING ALARM**

**AND**

NEW EXPERIMENTAL SERIES

**BIONICS**

**ADCOLA**  
PRODUCTS LIMITED  
(Regd. Trade Mark)

**SOLDERING  
EQUIPMENT**

## **LEADERS IN PRECISION SOLDERING!**

THE RANGE OF ADCOLA  
SOLDERING INSTRUMENTS  
INCLUDE MODELS FROM  
19 WATTS WITH A WIDE  
SELECTION OF BITS, COPPER  
OR LONG LIFE  
PENTACOATED. FOR EACH  
MODEL PRICES START AT 33/6.



COURTESY OF THORN ELECTRONICS LTD.

**FOR A QUALITY SOLDERING INSTRUMENT  
AT THE RIGHT PRICE, CHOOSE ADCOLA.  
AVAILABLE AT SHOPS AND DEALERS  
THROUGHOUT THE COUNTRY.**

**ADCOLA PRODUCTS LTD.  
ADCOLA HOUSE  
GAUDEN ROAD  
LONDON, S.W.4**

**TELEPHONE  
01-622 0291/3**


**SEND COUPON FOR LATEST  
LEAFLET**

NAME

ADDRESS

# Lasky's Radio
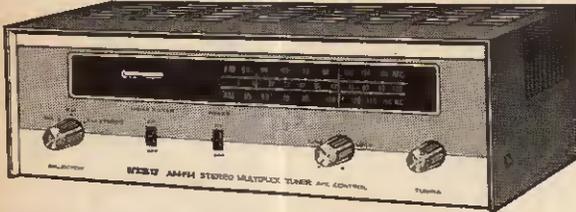
## SPECIAL INTEREST ITEMS! OUTSTANDING HI-FI BARGAIN



### AF3-U AM/FM STEREO TUNER

Superbly engineered by world famous manufacturer, the Model AF3-U is an ultra sensitive AM/FM stereo multiplex tuner using 14 valves and 9 diodes. The extra wide bandwidth of the tuner and unique multiplex circuitry ensures the finest possible FM reception with optimum stereo separation of over 38dB. Stereo signal beacon with special circuitry unaffected by external noise, simplifies FM stereo broadcast selection. 3 gang variable condenser provides highly sensitive reception on both bands. The multiplex circuit is completely free from subcarrier leakage and permits direct tape recording without any beat noise interference. An MPX noise filter is also fitted. Brief specification: 14 valves, 2 Germanium diodes and 2 Silicon diodes. Frequency range: FM—50-108Mc/s, AM—585-1,605kc/s. Sensitivity: FM—1.0µV/98Mc/s, AM—2µV/100kc/s. Output FM/FM Stereo 2V, AM—3V. Frequency response: FM—20-20,000c/s. Distortion less than 1%. Special Circuits: FM Stereo indicator, AFC, Noise filter. Output for direct tape recording. Hammer enamel and brushed alloy finish. Cabinet size 14½ x 6 x 9½ in. For 220/240V a.c. Mains (50 or 60c/s) operation. Complete with operating manual. List Price 55 Gns.

Lasky's Price 26 Gns. Carriage and Packing 7/6

## COMMUNICATION RECEIVERS

### TRIO

#### MODEL 9R-59DE

Brief spec.: 4 band receiver covering 550kc/s to 30Mc/s continuous and electrical band spread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4½ ohm output and phone jack. Special features: SSB-CW • ANL • Variable BFO • 8 meter • Sep. band spread dial • IF frequency 455kc/s • Audio output 1.5W • Variable RF and AF gain controls. For use on 115/250V a.c. Mains. Beautifully designed control layout finished in light grey with dark grey case, size 7 x 15 x 10½ in. Weight 19½ lb. Fully guaranteed, complete with instruction manual and service data.

Lasky's Price £39.15.0 Carriage and Packing 12/6

#### MODEL JR-500SE

Brief spec.: Covers all the amateur bands in 7 separate ranges between 3.5 and 29.7Mc/s. Circuit uses 7 valves, 2 transistors and 5 diodes plus 8 crystals; output 8 and 500 ohm and 500 ohm phone jack. Special features: Crystal controlled oscillator • Variable BFO • VFO • AVC • ANL • 8 meter • SSB-CW • Stand-by switch • Special double gear dial drive with direct reading down to 1MHz • Remote control socket for connection to a transmitter. Audio output 1 watt. For use on 115/240V a.c. Mains. Superb modern styling and control layout—finished in dark grey. Cabinet size 7 x 13 x 10½ in. Weight 18½ lb. Fully guaranteed, complete with instruction manual and service data.

Lasky's Price £68.0.0 Carriage and Packing 12/6

### FOSTER HF-204 COMBINED MICROPHONE/HEADSET

High quality moving coil headphones and sensitive dynamic microphone combined in one lightweight unit. For use with tape recorders (provides constant monitoring), communications equipment, PA (crowd or traffic control), stage direction, language labs, etc. Extremely comfortable to wear for long periods—adjustable foam padded cushions, vinyl covered headband. Headphone imp. 8Ω, max. input 100mW. Microphone imp. 26Ω. Weight 8.5oz. Single cable contains both headphone and microphone leads. List Price 7 Gns.

Lasky's Price 59/6 Post 2/6


## GET YOUR LASKY'S CATALOGUE

FREE Second Great Reprint Issue Now Ready. Twelve 16 x 11½ in pages—over 1,500 items! Just send your name, address and 1/- for post only

## CONSTRUCTORS BARGAINS
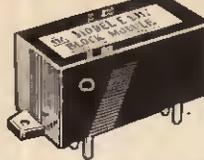
### LASKY'S ENCAPSULATED SOLID STATE MODULES

8 completely new special function circuit modules. Size of each module only 2½ x 1½ x ¾ in. Ready for immediate use—just connect to power source (usually 9V batt.), input and output. Encapsulated modules are shockproof and almost indestructible. Comp. with full ins. Post 1/6 each.



- E-1311 Phono Pre-amp Module—max. output 3V. RMS, input 50mV, input imp. 100kΩ, gain 28dB, RIAA compensation. 29/6
- E-1312 Tape Head Pre-amp Module—max. output 3V, RMS, input 50mV, input imp. 100kΩ, gain 26dB, NARTB compensation. 29/6
- E-1313 Microphones Pre-amp Module—max. output 4V, RMS, input 50mV, input imp. 100kΩ, gain 25dB, response 18-50kc/s. 29/6
- E-1314 Power Amplifier Module—max. output 300mW, input imp. 1kΩ, gain 20dB, response 50-10kc/s, distortion 3% at 20mW. 29/6
- E-1315 Electronic Organ (tone oscillator) Module—frequency 200-1,000c/s, output 80mW. For use with keyboard, variable resistors and 8Ω speaker. 25/-
- E-1316 Morse Code Practice Oscillator Module—frequency 400c/s, output 80mW. For use with Morse key and speaker. 25/-
- E-1317 Modulated Wireless Signal Transmitter for use in test bench fault finding—frequency 400c/s-30Mc/s, tone freq. 400c/s. For use with any AM receiver. 25/-
- E-1318 Lamp Flasher Module—flashes two miniature lamps alternately. For use with 6V, 100/200mA bulbs and 6V power supply. 25/-

## TEST EQUIPMENT

### NEW LASKY'S EXCLUSIVE MIDLAND Model 10-502 VHF AIRCRAFT BAND CONVERTER

An entirely new item for the radio enthusiast bringing instant reception of the ground-to-air, air-to-ground waveband. For use with any standard AM or FM radio covering 535 to 1,605kc/s, 88 to 103Mc/s respectively—with no electrical conversion or connection required. The Model 10-502 (self powered by one 9V (FP3 type) battery) is merely placed close to the receiving set and then tuned over 110 to 135Mc/s which covers the whole aircraft communications band. Volume and reception effectiveness is adjusted by moving both sets to the most favourable position and balancing the volume controls of each accordingly. The Model 10-502 has a smartly designed black plastic cabinet with brushed metal front panel and 15in chrome telescopic antenna, size only 4 x 2½ x 2½ in (inc. knobs). Complete with battery and full instructions.



Lasky's Price 79/6 Post 3/6

### TTC Model C-1051

A completely new design 20,000 O.P.V. pocket multimeter with mirror scale circuit and built-in thermal protection. Exceptionally large easy to read meter with D'Arsonval movement. Colour coded scales. Single positive click-in, recessed selection switch for all ranges. Ohm zero adjustment. Range spec. a.c. volts: 0-6-30-300-1,200V at 10k/ohms/V. D.c. volts: 0-3-15-150-300-1,2KV at 20k/ohms/V. Resistance: 0-60K-6megs. D.c. current: 0-60µA-300mA. Decibels: -20dB to +17dB. Hand calibration gives extremely high standard of accuracy on all ranges. Uses one 1½V penlight battery. Strong impact resistant plastic cabinet—size only 4½ x 3½ x 1½ in. Two colour buff/green finish. Complete with test leads and battery. Orig. list price \$5.50.



LASKY'S PRICE 75/- Post 2/6

### CLEAR PLASTIC PANEL METERS

Precision made in Japan by TTC. Each meter boxed and fully guaranteed with all fixing nuts and washers. Sizes are of front panel. Add 1/6 P. on each. (Quotes for quantities.)

Type KR-52 3 x 2½ in (Illustrated)	1mA	5mA	100mA	300V	50µA	1mA 5 meter	100µA	500µA
	38/6	38/6	38/6	35/-	58/6	58/6	52/6	48/-
Type MK-38A 1½ in square	29/6	27/6	27/6	27/6	37/6	29/6	27/6	29/6
Type MK-45A 2½ in square	29/6	29/6	29/6	29/6	49/6	49/6	42/6	35/-
Type KR-65 3½ x 3½ in	38/6	37/6	35/6	38/-	58/6	48/-	58/-	48/-
Type MK-65A 3½ in square	38/6	38/6	38/6	38/6	58/6	58/6	52/6	48/-



#### Branches

207 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 3271  
Open all day Saturday, early closing 1 p.m. Thursday

33 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-636 2605  
Open all day, 9 a.m.—6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel.: FLEet St. 2833  
Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

#### High Fidelity Audio Centres

42 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2573  
Open all day Thursday, early closing 1 p.m. Saturday

118 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 9789  
Open all day Saturday, early closing 1 p.m. Thursday

# SEW PANEL METERS

Send S.A.E. for full lists. Other ranges available. Please include postage. Special quotations for quantities.



## CLEAR PLASTIC METERS

Type MR. 52P. 2 1/2 in square fronts			
50μA	59/6	100mA	37/6
500μA	48/6	500mA	37/6
100μA	49/6	1 amp.	37/6
100-0-100μA	45/-	5 amp.	37/6
500μA	42/6	10V d.c.	37/6
1mA	37/6	20V d.c.	37/6
5mA	37/6	50V d.c.	37/6
10mA	37/6	300V d.c.	37/6
50mA	37/6	15V a.c.	37/6
500μA	59/6	100mA	37/6
500-0-500μA	48/6	500mA	37/6
100μA	49/6	1 amp.	37/6
100-0-100μA	45/-	5 amp.	37/6
500μA	42/6	10V d.c.	37/6
1mA	37/6	20V d.c.	37/6
5mA	37/6	50V d.c.	37/6
10mA	37/6	300V d.c.	37/6
50mA	37/6	15V a.c.	37/6


## Type MR. 38P. 1 21/32 in square fronts

50μA	37/6	750mA	25/-
50-0-50μA	35/-	1 amp.	25/-
100μA	35/-	2 amp.	25/-
100-0-100μA	32/6	5 amp.	25/-
200μA	32/6	3V d.c.	25/-
500μA	37/6	10V d.c.	25/-
500-0-500μA	35/-	20V d.c.	25/-
1mA	25/-	50V d.c.	25/-
1-0-1mA	25/-	100V d.c.	25/-
2mA	25/-	150V d.c.	25/-
5mA	25/-	300V d.c.	25/-
10mA	25/-	500V d.c.	25/-
20mA	25/-	750V d.c.	25/-
50mA	25/-	15V a.c.	25/-
100mA	25/-	50V a.c.	25/-
150mA	25/-	150V a.c.	25/-
200mA	25/-	300V a.c.	25/-
300mA	25/-	500V a.c.	25/-
500mA	25/-	8 meter 1mA	20/6
		VU meter	39/6

## Type MR. 45P. 2 1/4 in square fronts

50μA	42/6	10V d.c.	27/6
50-0-50μA	39/6	20V d.c.	27/6
100μA	39/6	50V d.c.	27/6
100-0-100μA	35/-	300V d.c.	27/6
500μA	28/6	15V a.c.	27/6
1mA	27/6	300V a.c.	27/6
5mA	27/6	8 meter 1mA	35/-
10mA	27/6	VU meter	42/6
50mA	27/6	1 amp a.c.*	27/6
100mA	27/6	5 amp a.c.*	27/6
500μA	27/6	10 amp a.c.*	27/6
1 amp.	27/6	20 amp a.c.*	27/6
5 amp.	27/6	30 amp a.c.*	27/6

## BAKELITE PANEL METERS

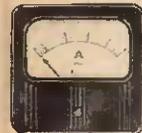

\*Moving iron, all others moving coil.

Type MR. 65. 3 1/4 in square fronts			
25μA	37/6	500mA	32/6
50μA	45/-	1 amp.	32/6
50-0-50μA	42/6	5 amp.	32/6
100μA	42/6	15 amp.	32/6
100-0-100μA	42/6	30 amp.	32/6
300μA	32/6	80 amp.	32/6
1mA	32/6	5V d.c.	32/6
1-0-1mA	32/6	10V d.c.	32/6
5mA	32/6	20V d.c.	32/6
10mA	32/6	50V d.c.	32/6
50mA	32/6	180V d.c.	32/6
100mA	32/6	300V d.c.	32/6
30V a.c.*	32/6		
60V a.c.*	32/6		
150V a.c.*	32/6		
300V a.c.*	32/6		
1 amp. a.c.*	32/6		
5 amp. a.c.*	32/6		
10 amp. a.c.*	32/6		
20 amp. a.c.*	32/6		
30 amp. a.c.*	32/6		
50 amp. a.c.*	32/6		
10V d.c.	32/6		
20V d.c.	32/6		
50V d.c.	32/6		
180V d.c.	32/6		
300V d.c.	32/6		

## NEW RANGE OF "SEW" EDGEWISE METERS

MODEL PE70. Dimensions 3 17/32 x 1 11/32 x 2 1/4 deep overall. Available as follows:

50 microamp	57/6	500 microamp	48/6
50-0-50 microamp	55/-	1 milliamp	48/6
100 microamp	53/-	300V a.c.	45/-
100-0-100 microamp	52/6	VU meter	62/6
200 microamp	52/6		Post extra



## TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120kc/s to 500Mc/s on 6 bands. Directly calibrated. Variable RF attenuator, audio output. Xtal socket for calibration. 220/240V a.c. Size 140 x 215 x 170mm. Brand new with instructions. £15.

Carr. 7/6.

## TY 75 AUDIO SIGNAL GENERATOR

Sine Wave 20c/s to 20Kc/s. Square Wave 20c/s to 30Kc/s. High and low impedance output. Output variable up to 8 volts. 220/240 volts a.c. Size 210 x 100 x 120mm. Brand new with instructions. £18. Carr. 7/6.



## T.M.C. 1000 SERIES KEY SWITCHES

Brand New with knobs as follows.

1 way, 2 c/o 7/6; 1 way, 2 c/o 2b, 7/6; 1 way, 4 c/o 8/6; 2 way, 3m, 8/6; 2 way, 2 c/o, 2 c/o 8/6; 2 way, 2 c/o, 4 c/o, 10/-.

Post extra. Quantities available.


## NOMBEX TRANSISTORISED TEST EQUIPMENT

All Post Paid with Battery



Model 22. Power Supply 0-15V d.c.	£14.10.0
Model 30. Audio Generator.	£10.10.0
Model 31. R.F. Signal Generator.	£12.10.0
Model 32. C.R.R. Bridge.	£20.0.0
Model 33. Inductance Bridge.	£20.0.0
Model 66. Inductance Bridge.	£18.0.0
Model 61. Power Supply.	£20.10.0

## AVO CT.38 ELECTRONIC MULTIMETERS

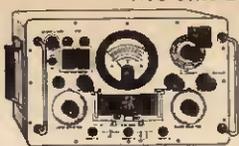

High quality 97 range instrument which measures a.c. and d.c. Voltage, Current, Resistance and Power output. Ranges d.c. volts 250mV-10,000V. (10megΩ-110megΩ input). D.c. current 10μA-25 amps. Ohms: 0-1,500Ω. A.c. volt 100mV-250V (with RF measuring head up to 250Mc/s). A.c. current 10μA-25 amps. Power output 50 micro-watts-5 watts. Operation 97/10/200/250V. C. Supplied in perfect condition complete with circuit lead and RF probe £25. Carr. 15/-.

## TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose D/B oscilloscope. T.B. 2c/s-750 kc/s. Bandwidth 0.6 Mc/s. Sensitivity 33mV/CM. Operating voltage 0/110/200/250V a.c. Supplied in excellent working condition. £22.10.0. Or complete with all accessories, probe, leads, lid, etc. £25. Carrage 30/-.

## AM/FM SIGNAL GENERATORS



Oscillator Test No. 2. A high quality precision instrument made for the Ministry by Airmec. Frequency coverage 20-80Mc/s. AM/ C.W./F.M. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12V d.c. or 0/110/200/250V a.c. Size 12 x 8 1/2 x 9 1/2. Supplied in brand new condition complete with all connectors fully tested. £45. Carr. 20/-.

## ADMIRALTY B.40 RECEIVERS



Just released by the Ministry. High quality 10 valve receiver manufactured by Murphy. Coverage in 6 bands 50kc/s - 30Mc/s, I/F 500 kc/s. Incorporates 2 R.F. and 3 I.F. stages, band-pass filter, noise limiter, crystal controlled B.F.O., callibrator I/F, output, etc. Built-in speaker, output for phones. Operation 150/230V a.c. Size 19 1/2 x 18 1/2 x 16 1/2. Weight 114lb. Offered in good working condition. £22.10.0. Carr. 30/-.



## CLASS D WAVEMETERS

A crystal controlled heterodyne frequency meter covering 17-8Mc/s. Operation on 6 volts d.c. Ideal for amateur use. Available in good used condition £5.12.6. Carr. 7/6. Or brand new with accessories £7.18.6. Carr. 7/6.

## MARCONI CT44/TF956 AF ABSORPTION WATTMETER



1 μwatt to 6 watts £20. Carr. 20/-.

## AVOMETERS



Supplied in excellent condition, fully tested and checked. Complete with probe, leads and instructions. Model 47A £29.10.6. P. & P. 7/6 each.


## AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded. 150 W. £12.6. P. & P. 3/- 300 W. £22.7.6. P. & P. 3/6 500 W. £31.0.0. P. & P. 6/6 1,000 W. £5.10.0. P. & P. 7/6 1,500 W. £6.10.0. P. & P. 9/6 3,000 W. £7.10.0. P. & P. 12/6 7,000 W. £15.10.0. P. & P. 20/-

## MARCONI TEST EQUIPMENT
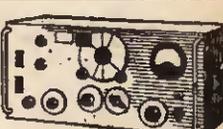
### EX-MILITARY RECONDITIONED.

TF 144G STANDARD SIGNAL GENERATORS. 85kc/s-25 Mc/s, £25. Carr. 30/- TF 285. VIDEO OSCILLATOR. 0-5Mc/s, £45. Carr. 30/- TF 193M. BEAT FREQUENCY OSCILLATOR. 0-40kc/s, 900/250V a.c. £20. Carr. 30/- TF 142E. Distortion Factor Meter, £20. Carr. 20/-. All above offered in excellent condition fully tested and checked. TF 1100 VALVE VOLT-METER, Brand New, £50. T.P. 1267 TRANSMISSION TEST SET, Brand New, £75. TF 1371. Wide Band Millivolt Meter, £50.



## Variable Voltage Transformers

Brand new, guaranteed and carriage paid. High quality construction. Input 230V 50-60 cycles. Output full variable from 0-250V. Bulk quantities available. 1 amp.-£5.10.0; 2.5amp.-£8.15.0; 5 amp.-£9.15.0; 8 amp.-£14.10.0; 15 amp.-£18.10.0; 22 amp.-£21; 20 amp.-£27.

## ROSSOR DOUBLE BEAM OSCILLOSCOPES

Type 1035 general purpose, a.c. coupled. Type 1049 L.F. d.c. coupled £35 each. Carr. 30/-.

## AMERICAN TAPE

First grade quality American tapes. Brand new. Discount on quantities. 3/6 5in. 250ft. L.F. acetate ..... 10/- 3 1/2in. 500ft. T.P. mylar ..... 10/- 5in. 600ft. std. plastic ..... 8/6 5in. 900ft. L.F. acetate ..... 10/- 5in. 1,200ft. D.P. mylar ..... 15/- 5in. 1,800ft. T.P. mylar ..... 22/6 5in. 1,200ft. L.F. acetate ..... 12/6 6 1/2in. 1,900ft. L.F. mylar ..... 16/- 5 1/2in. 1,800ft. D.P. mylar ..... 22/6 3 1/2in. 2,400ft. T.P. mylar ..... 39/6 7in. 1,200ft. std. acetate ..... 12/6 7in. 1,800ft. L.F. acetate ..... 15/- 7in. 1,800ft. L.F. mylar ..... 20/- 7in. 2,400ft. D.P. mylar ..... 25/- 7in. 3,600ft. T.P. mylar ..... 45/- Postage 2/-, Over £3 post paid.

## NO.76 TRANSMITTER

2-12 Mc/s. Crystal Controlled (not supplied). 807PA. Operation 12V. D.C. (Rotary transformer), 9 watts output. C.W. only. New condition. 72/6. Carr. 12/6.

## LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

0-20kc/s. Output 5kΩ or 500 ohms. 200/250V a.c. offered in excellent condition. £12.10.0. Carrage 10/-.

## OMRON MK. 2 RELAYS

Brand New and Boxed. 24 volt d.c. coils. 3 Pole changeover. 5 amp contacts. 7/6 each. P. & P. 1/6.

**G. W. SMITH & Co. (Radio) Ltd.**  
3-34 Lisle St., W.C.2  
ALSO SEE OPPOSITE PAGE

# MULTIMETERS for EVERY purpose!

**LAFAYETTE DE-LUXE 100 KΩ/VOLT "LAB TESTER"**  
Giant 6 1/2 in. scale.  
Built-in meter protection. 0/5/2.5/10/50/250/600/1,000V d.c. 0/3/10/50/250/500/1,000V a.c. 0/10/100μA/10/100/500 MA/2.5/10A. 0/1K/10K/100K/10M/100MΩ. —10 to 49.4dB. £18.18.0. P. & P. 3/6.



**TE-500 20,000 VOLT GIANT MULTIMETER**  
6 1/2 in. full view meter. 2 colour scale, overload protection. 0/2.5/10/250/1,000/5,000V d.c. 0/25/12.5/10/50/200/1,000/5,000V d.c. 0/50μA/110/100/500μA/10A/200K/200K/20MΩ. £15. P. & P. 3/6.



**LAFAYETTE 57 Range Super 50,000 O.P.V. Multimeter.** D.c. Volts 125V-1000V. A.c. Volts 1.5V-1000V. D.c. Current 25μA-10 Amp. Ohms. 0-15 MegΩ. dB. —20 to +81dB. Overload Protection. £12.10.0. Carr. 3/6.



**MODEL AS-100D. 100KΩ/VOLT 6 1/2 in. mirror scale.** Built-in meter protection. 0/3/12/60/120/360/600/1,200V. d.c. 0/6/30/120/300/600V. a.c. 0/30μA/6/60/300mA/12 Amp. 0/2K/200K/2M/200MΩ. —20 to +17dB. £12.10.0. P. & P. 3/6.



**NEW MODEL 600. 20,000 O.P.V. with overload protection.** Mirror scale. 0/0.5/2.5/10/25/100/250/500/1,000V. d.c. 0/2.5/10/25/100/250/500/1,000V. a.c. 0/50μA/5/50/500mA. 12 amp. d.c. 0/60K/6 Meg. 0/2megohm. £8.17.6. Post paid.



**MODEL AF-105. 50KΩ/Volt.** Mirror scale, built-in meter protection. 0/3/3/12/50/120/300/600/1,200V. d.c. 0/6/30/120/300/600/1,200V. a.c. 0/30μA/6/60/300mA/12 Amp. 0/10K/1M/10M/100 MΩ. —20 to +17 dB. £8.10.0. P. & P. 3/6.



**PROFESSIONAL 20,000 O.P.V. LAB. TESTER**  
Automatic overload protection, mirror scale. Ranges: 1/10/50/250/500/1,000V. d.c. and a.c. 0-500μA. 10mA, 250μA. Current: 0/20K, 200K, 2 megohm. Decibels: —20 to +22dB. £5.19.6. P. & P. 2/6.



**MODEL TE-12. 20,000 O.P.V.** 0/0.1/0.30/120/600/1,200/3,000/6,000V. d.c. 1/6/30/120/600/1,200V. a.c. 0/60μA/6/60/600MA. 0/8K/600K/6Meg./100. Megohm. Buzer. 2 MF. £5.19.6. P. & P. 3/6.



**MODEL TE-70. 30,000 O.P.V.** 0/3/15/60/300/600/1,200V. d.c. 0/6/30/120/600/1,200V. a.c. 0/30μA/6/30/300μA/6/16K/160K/1.6M/1.6megohm. £5.10.0. P. & P. 3/6.




**MODEL TE 80. 20,000 O.P.V.** 0/1/10/50/100/500/1,000V. a.c. 0/5/25/50/250/500/1,000V. d.c. 0-50μA. 5/50/500mA. 0/6K/60K/600K/6 Meg. £4.17.6. P. & P. 3/6.



**MODEL 250T. 2,000 O.P.V.** 0/10/50/100/2,500V. d.c. 0/10/50/500/2,000V. a.c. 0/2megohm. 0/250 mA. —20 to +36dB. 49/6. P. & P. 2/6.



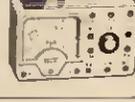**MODEL PT-34. 1,000 O.P.V.** 0/10/50/100/500/1,000V. a.c. and d.c. 0/1/100/500 mA. d.c. 0/100 KΩ 38/6. P. & P. 1/6.



**UNR-30. 4-BAND COMMUNICATION RECEIVER**  
Covering 550Kc/s—30Mc/s. Incorporates variable BFO for CW/SSB reception. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. a.c. Supplied brand new guaranteed with instructions. Carr. 7/6. **13 GNS.**




**LAFAYETTE MODEL HA700 AM/CWSSB AMATEUR COMMUNICATION RECEIVER**  
8 valves, 5 bands incorporating 2 MECHANICAL FILTERS for exceptional selectivity and sensitivity. Frequency coverage on 5 bands 150-400Kc/s, 550-1,600Kc/s, 1.6-4.0Mc/s, 4.8-14.5Mc/s, 10-30Mc/s. Circuit incorporates 3-B.F. stage, aerial trimmer, noise limiter, B.F.O. product detector, electrical bandspread, 4 meter, slide rule dial. Output for phones, low to 2KΩ or speaker 4 or 8ohms. Operation 220/240V. a.c. 8/2. S.A.E. for leaflet.



**NEW LAFAYETTE SOLID STATE HA600 RECEIVER**  
5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE. 150Kc/s TO 400Kc/s AND 550Kc/s TO 30Mc/s. F.E.T. front end • 2 mechanical filters • Huge dial • Product detector • Variable BFO • Noise limiter • 8 Meter • 24in. Bandspread • 230V a.c./12V d.c. gen. earth operation • RF gain control. Size 15in x 9in x 2 1/2in. Wt. 18 lb. **EXCEPTIONAL VALUE £45.** Carr. 10/- S.A.E. for full details.



**TRIO COMMUNICATION RECEIVER MODEL 9R-50DE**  
4 band receiver covering 550Kc/s to 30Mc/s continuous and electrical band spread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack SSB-CW • AXL • Variable BFO • 8 meter • Sep. band spread dial • IF 44Kc/s • Amplitude output 1.5W. • Variable RF and AF gain control. 115/230V. a.c. Mains. Beautifully designed. Size 7 x 15 x 10in. With instruction manual and service data. £27.10.0. Carriage 12/6.

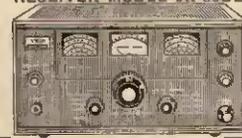

**LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER**  
A completely new transistorised receiver covering 150-174Mc/s. Fully tunable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75Ω aerial input. Headphone jack. Operation 230V a.c./12V d.c. Neg. earth. £27.10.0. Carr. 10/-




**LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER**  
19 transistors, 3 diodes, 1HF music power, 30W at 8Ω. Response 30-20,000 ±2dB at 1W Distortion 1% or less. Inputs 3mV and 250mV. Output 3-25Ω. Separate L and R volume controls. Treble and bass control. Stereo phone jack. Brushed aluminium, gold anodised extruded front panel with complimentary metal case. Size 10 1/2 x 3 1/2 x 7 1/2 in. Operation 115/230V. A.V. £28. Carr. 7/6.



**GARRARD DECKS**  
Brand new and guaranteed.  
1025 mono £7.10.0  
1025 stereo £7.19.6  
2025 TC less cart. £7.19.6  
2025 TC stereo £8.19.6  
3705 Mk.II less cart. £12.10.0  
A70 Mk.II less cart. £12.10.0  
LA B80 Mk.II less cart., with base £27.10.0 Carr. 7/6 each

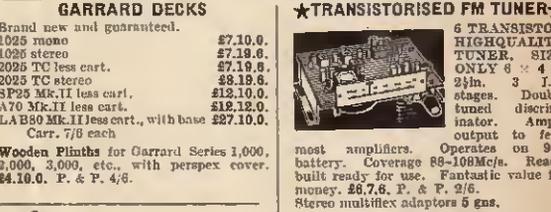**Wooden Plinths for Garrard Series 1,000, 2,000, 3,000, etc., with perspex cover. £4.10.0. P. & P. 4/6.**

**\*TRANSISTORISED FM TUNER\***  
6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6 x 4 x 2 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V. battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £6.7.6. P. & P. 2/6. Stereo multiflex adaptors 5 gns.



**GARRARD TAPE MOTORS**  
Brand new stock as used by famous manufacturer. 200/250V a.c. Capstan motor 15/-, Fast Forward 10/6, Post Rewind 10/6. P. & P. 3/6. Set of three motors 32/6. P. & P. 5/-.


**HOSIDEN DH04S 2-WAY STEREO HEADSETS**  
Each headphone contains a 2 1/2 in woofer and a 1/2 in tweeter. Built in individual level controls. 25-18,000c/s. 6Ω Imp. with cable and stereo plug. £5.19.6. P. & P. 2/6.



**DUBILIER NITROGEN CONDENSERS.**  
Brand new. 8mF 800V, 8/8. P. & P. 2/6; 2mF, 5,000V, 42/6. P. & P. 5/-.

**RECORDING HEADS**  
Reuter 1-track. As fitted to Callaro Mk. 1V and Studio Decks. High Imp. record play back, low Imp. erase. Brand new. 19/6 pair. MINIFLUX 1-track record 12/6. GORMOCORD 4-track with mounting plate. TRI-100/F/W record/playback 65/-; TRI-120/F/W record/playback 65/-; EEL 1-6 F/W Erase 20/-; MARRIOTT 4-track heads. Record/playback. High Imp. 65/-; Erase low Imp. 20/-; Post extra.

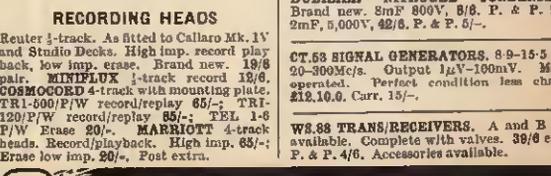**MODEL ZQM TRANSISTOR CHECKER**  
It has the fullest capacity for checking of A, B and Ico. Equally adaptable for checking diodes, etc. Spec: A: 0-7-0-9987. B: 2-500. Ico: 0-50 microamps 0-50A. Resistance for diode: 200Ω-1MΩ. Supplied complete with instructions, battery and leads. £5.19.6. P. & P. 2/6.



**ADVANCE TEST EQUIPMENT**  
Brand new and boxed in original sealed cartons

**VM76. VALVE VOLTMETER**  
R.F. measurements in excess of 100Mc/s and d.c. measurements up to 1,000V with accuracy of ±2%. D.c. range 300mV to 1kV. A.c. range 300mV to 300V RMS. Resistance 0.02-500MΩ. Price £72.

**VM78. A.C. MILLIVOLT METER**  
Transistorised. 1mV to 300V. Frequency 1c/s to 1Mc/s. Price £35.

**VM79. UHF MILLIVOLT METER**  
Transistorised. A.c. range 10mV to 3V. D.c. current range 0.01 4/A to 0.3mA. Resistance 1 ohm to 10 megohms. £125.

**H1B. AUDIO SIGNAL GENERATOR**  
15c/s to 50kc/s, sine or square wave. Price £30.

**J1B. AUDIO SIGNAL GENERATOR**  
15c/s to 50kc/s. Price £30.

**J2B. AUDIO SIGNAL GENERATOR**  
As per J1B except fitted with output meter. £35.

**TT15. TRANSISTOR TESTER**  
£37.10.0. Carriage 10/- per item.

**GW SMITH & CO (RADIO) LIMITED**  
Phone GERRARD 8204/9155  
Cables SMITHEX LESQUARE  
3-34 LISLE STREET, LONDON, W.C2

**OPEN**  
9 a.m. to 6 p.m. every day Mon. to Sat. Trade supplied.



<b>DULCIHI-FI AMP.</b> STEREO 7w X 7w MODEL 207 Usual price £19.19.0 Our big discount price 15½ guineas plus 10/- p/p.	<b>RECORD PLAYER AMP.</b> As fitted to most popular record players. Our Bargain Price 59/6 only. Fully built and tested. EL84 output. 230-240V mains operated. 2 controls —vol.,—tone on flying lead. P/p. 3/6.	<b>"SOLENT"</b> Scandinavian style speaker system (teak). Full maker's guarantee. 12 watt output. Imp. 8-15 ohms. Woofer 6½" 10,000 gauss. Tweeter 3½" Frequency response 40c/s. 20Kc/s. LIST PRICE 18 Gns. <b>OUR PRICE 11 GNS.</b> +10/- p/p.	<b>SONOTONE</b> 9TA-HC diamond 50/- plus 2/6 p/p.	● <b>BARGAIN</b> — Speakers, Hi-Fi — The Baker Selhurst Sealwart, 12in round, 15 watt rating, 12,000 lines gauss, 3 or 15 ohms, response 45-13,000c/s. Bass resonance 40-50c/s, solid aluminium chassis. Our price £4.19.6. Brand new, 12 months' unconditional guarantee. P/P 6/6. ● <b>BARGAIN</b> — Speakers, Hi-Fi — The Baker Selhurst Guitar Group 25, 12in round 25 watt rating, 12,000 gauss, 15 ohms, response 30-10,000c/s, solid aluminium chassis, heavy duty cone. Our price £4.19.6. Brand new, 12 months' unconditional guarantee. P/P 6/6.
------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	---------------------------------------------------------------	------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

<b>BARGAIN—CHANGER DECKS AT          LOWEST PRICES EVER</b> Plinth WB1 £2.15.0 Cover SPC1 £2.15.0 GARRARD 1025 p/p. 7/6 £8.0.0 GARRARD 2025 p/p. 7/6 £8.10.0 AT60 Mk. II p/p. 8/6 £13.10.0 SP25 Mk. II p/p. 8/6 £12.10.0 BSR UA25 p/p. 7/6 £6.15.0	<b>BUDGET HI-FI SYSTEM</b> <b>YOU WON'T FIND A BETTER BARGAIN—ANYWHERE!</b> TELETON F2000 STEREO (MULTIPLEX) C AM-FM TUNER AMP. £35.8.11 O TELETON S1003 SPEAKER M ENCLOSURES (PAIR) £9.13.6 P GARRARD SP25, SONOTONE 9TA. DIAM. L PLINTH TO MATCH £22.1.4 E <b>59</b> GNS. FREE DELIVERY TOTAL £67.3.9
-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

<b>EMI HI-FI SPEAKERS</b> 13×8in. 47/6, p/p. 5/-, 13×8in. plus 2 twr. 57/6, p/p. 7/6, 8×5in., 7×4in. 22/6, p/p. 3/6. Catalogue, full spec. on request. Distributors for EMI Sound.	Beautiful oiled teak enclosure to suit EMI 13×8in. speakers. Retail value £8.15.0. Our low- price ONLY 99/6 plus 8/- p/p.	<b>FULL EAGLE RANGE TUNER UNITS,          AMPLIFIERS, MICROPHONES, SPEAKERS,          ACCESSORIES, etc.</b> All less 15%.
------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------------

INTERNATIONAL MAGNETIC TAPE				BASF TAPE 33½ OFF			
	Standard	Long Play	Double Play		Standard	Long Play	Double Play
5"	600ft. 10/-	900ft. 13/6	1200ft. 17/-	5"	600ft. 12/6	900ft. 17/-	1200ft. 27/6
5½"	900ft. 13/6	1200ft. 16/6	1800ft. 21/-	5½"	900ft. 17/-	1200ft. 21/6	1800ft. 36/-
7"	1200ft. 15/-	1800ft. 17/6	2400ft. 26/-	7"	1200ft. 21/6	1800ft. 33/-	2400ft. 52/6

POST & PACKING 2/-. OVER £5 FREE


Thank you for reading our advertisement.

**S.B.E. Atlas House, Chorley Old Rd., Bolton**


**BOLTON  
25881**
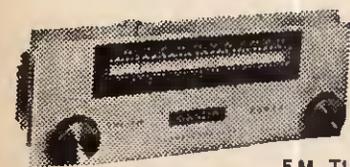
# MARTIN IS HIGH-FIDELITY

*The first and still the most  
satisfactory unit assembly system*



F.M. TUNER

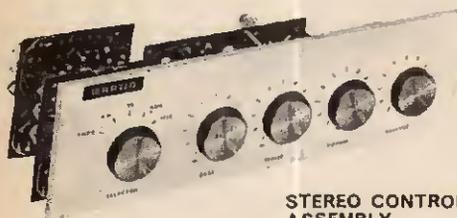

STEREO CONTROL  
ASSEMBLY

For many years now Martin Electronics have been producing highly efficient and dependable prefabricated module-type units for simple assembly into reasonably priced high fidelity systems. Many purchased at the time of the introduction of the Martin Audiokit system are in regular use to this day, completely justifying our claims for years of trouble-free service. No system gives you wider flexibility in the choice of units available than Martin and all equipment conforms precisely to stated specification.

When new units are introduced, they are designed for adding to those produced so far, making it easy and economical to extend and improve your existing Martin Audiokit set-up. Anyone can assemble Martin equipment with ease and the fore-knowledge that when finished, he will be possessed of a true hi-fi assembly of the very best kind which looks and sounds completely professional in every way—and MARTIN AUDIO-KITS remain as ever, the units that have true add-on-ability.

## AMPLIFIER SYSTEMS • TUNERS • RECORDERS

ONLY FROM MARTIN

Cover the widest possible range of requirements. They are available for Mono, and can be doubled up for conversion to stereo, or as complete stereo units, 3 ohm and 15 ohm systems. Special pre-amp for low output pick-ups. Escutcheon panels to suit the arrangement you choose. Tuner is styled to match.

UNITS INCLUDE:

- 5-stage input selector
- Pre-amp tone controls
- 10 watt amp. (3 ohms)
- 10 watt amp. (15 ohms)
- Mains power supply
- F.M. Tuner

Start by sending for leaflets at once

Trade enquiries invited

**MARTIN ELECTRONICS LTD.**

154/5 HIGH STREET, BRENTFORD  
MIDDLESEX. 15Leworth 1161/2


### MARTIN ELECTRONICS

154 High Street, Brentford, Middlesex  
Please send Recordakit/F.M. Tuner/Audiokit  
Hi-Fi Leaflets. (Strike out items not wanted)

Name .....

Address .....

P.E.10/68

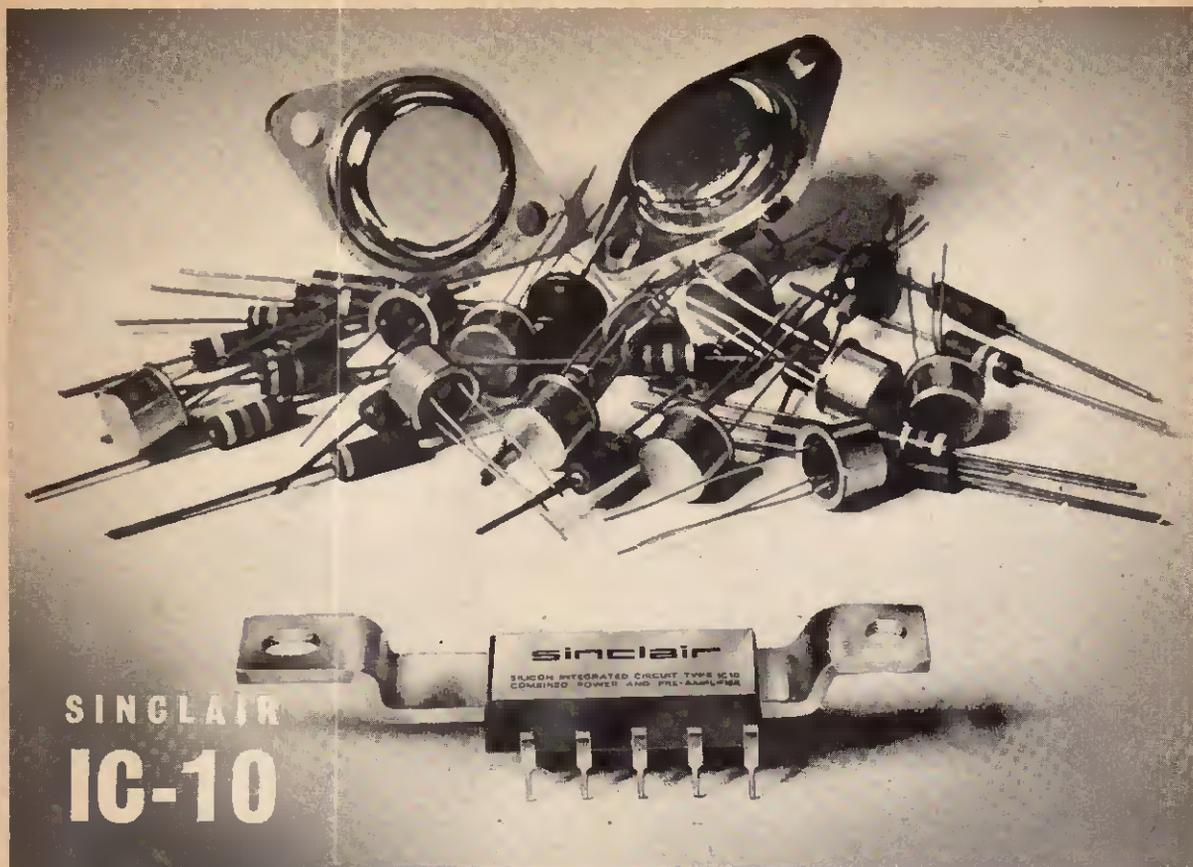

## the world's most advanced high-fidelity amplifier

The Sinclair IC-10 is the World's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, which has an output power of 10 Watts, is a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick. This tiny chip contains 13 transistors (including two power types), 2 diodes, 1 zenor diode and 18 resistors, all of which are formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins.

Monolithic I.C.'s. were originally developed for use in computer and space applications where their extraordinary toughness and reliability were even more important than their minute size. These same advantages make them ideal for linear applications such as audio amplifiers, but hitherto they have been confined to low power applications. The IC-10 thus represents a very exciting advance. Not only is it far more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most

important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of the usual tone and volume controls and a battery or mains power supply. However, the IC-10 is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout) etc.

The photographic masks required for producing monolithic I.C.'s. are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. So we are able to sell the IC-10 at a price far below that of the components for a conventional amplifier of comparable power. At the same time, we give a 5 year unconditional guarantee on each IC-10 knowing that every unit will work as perfectly as the original and do so for a lifetime.

**sinclair**

**SINCLAIR RADIONICS LTD, 22 Newmarket Rd. Cambridge. Tel: 0643-52731**

# 10 WATT MONOLITHIC INTEGRATED CIRCUIT AMPLIFIER

## ■ Specifications


Power Output	10 Watts peak, 5 Watts R.M.S. continuous.
Frequency response	5 Hz to 100 KHz $\pm 1$ dB.
Total harmonic distortion	Less than 1% at full output.
Load impedance	3 to 15 ohms.
Power gain	110dB (100,000,000,000 times) total.
Supply voltage	8 to 18 volts.
Size	1 x 0.4 x 0.2 inches.
Sensitivity	5 mV.
Input impedance	Adjustable externally up to 2.5 M ohms for above sensitivity.

## ■ Circuit Description


The circuit diagram of the IC-10 is shown on the right. The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. The output stage operates in class AB with closely controlled quiescent current which is independent of temperature. A high level of overall negative feedback is used round both sections and the amplifier is completely free from cross-over distortion at all supply voltages. Thus battery operation is eminently satisfactory.
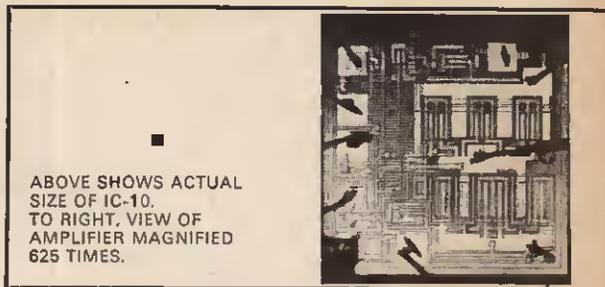
## ■ Construction

The monolithic I.C. chip is bonded onto a gold plated area on the heat sink bar which runs through the package. Wires are then welded between the I.C. and the tops of the pins which are also gold-plated in this region. Finally the complete assembly is encapsulated in solid plastic which completely protects the circuit. The final device is so rugged that it can be dropped thirty feet on to concrete without any effect on performance. The circuit will also work perfectly at all temperatures from well below zero to above the boiling point of water.



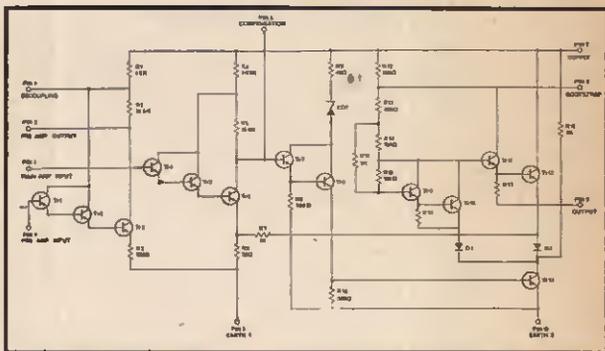ABOVE SHOWS ACTUAL SIZE OF IC-10. TO RIGHT, VIEW OF AMPLIFIER MAGNIFIED 625 TIMES.



## ■ Applications

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity uses. These include public address, loud-hailers, use in cars, inter-com., stabilised power supplies, electronic organs, oscillators, volt meters, tape recorders, solar cell amplifier, radio receivers.

The transistors in the IC-10 have cut off frequencies greater than 500 MHz so the pre-amp section can be used as an R.F. or I.F. amplifier making it possible to build complete radio receivers without any additional transistors.



**SINCLAIR  
IC-10**


*The complete IC-10 with the manual and 5 year guarantee costs just*

**59'6**

*Post free*

**SINCLAIR RADIONICS LIMITED,**  
22 NEWMARKET ROAD, CAMBRIDGE  
Telephone OCA3-52731

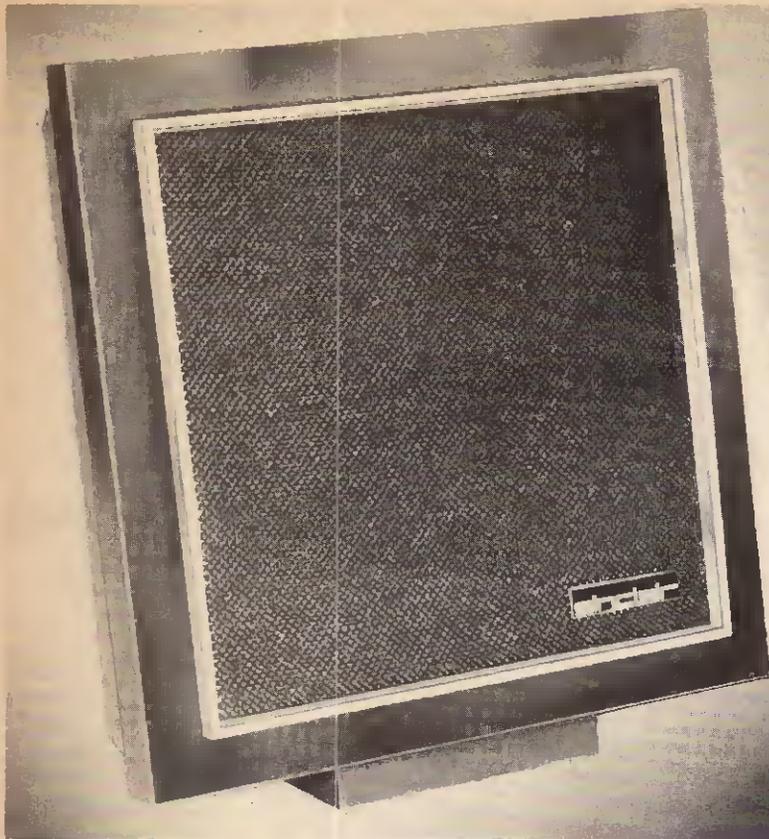**ORDER FORM AND MORE SINCLAIR  
DESIGNS OVERLEAF**



## SINCLAIR Q.14

# The most challenging loudspeaker development in years

It costs about a quarter of what you would expect to pay for a good stereo speaker system when you choose Q.14s. This is because of the considerable amount of research and experimentation into the acoustic properties of special materials that went into the design of this excellent speaker. It resulted in an instrument so outstandingly good that experts, reviewers and the public alike were unanimous in their praise for the Q.14 at this year's Audio Fair. The Q.14 is very compact, measuring only 9 $\frac{1}{2}$ in square on its face by 4 $\frac{1}{2}$ in deep. Its unusual contours permit it to be positioned where no ordinary speaker could be used to advantage. The neat black matt finish

with aluminium bar trim keep this speaker pleasantly in conformity with modern design trends. The Q.14 has acoustically contoured and sealed sound chamber. Smooth response from 60-16,000Hz. Loading up to 14 watts. 8 ohms impedance. Brilliant transient response. Size 9 $\frac{1}{2}$ in square on face. Finished black matt with aluminium bar trim. Detachable pedestal base. *Hear the Q.14 in your own home. If you are not delighted with it, send it back, and your money, including cost of return postage to this office, will be refunded in full.*

**£7-19-6**

**sinclair**

**SINCLAIR RADIONICS LTD., CAMBRIDGE**

**Sinclair IC-10 a revolutionary new amplifier-See previous pages-**

# SINCLAIR MICROMATIC

## The smallest radio set in the world

The Sinclair Micromatic is available ready built or in kit form. This latter now comes in a convenient new presentation pack complete down to a generous free supply of solder. The moulded polystyrene interior enables you to check the contents in an instant, and helps to make building even easier and surer. Now, the Micromatic is better than ever—more powerful and better sounding to assure superb listening. Selectivity is better than many larger sets. Whether you build it, or buy your Micromatic ready built, it is the best and the smallest personal radio in the world—and it's British. In elegant aluminium fronted black case with slow motion tuning.



- $1\frac{1}{4} \times 1\frac{1}{8} \times \frac{1}{2}$  in
- Tunes over medium waves
- Plays anywhere
- Magnetic earpiece
- In kit form or complete

Complete kit inc. magnetic ear-piece and instructions.

49/6

59/6

Ready built and tested

Mallory Mercury Cell RM.675 (2 needed) each 2/9.



## IN THE NEW KIT PACK

This attractive new presentation pack enables you to check the contents of your kit instantly. Everything is there down to the last nut and includes easy to follow instructions and generous supply of free solder.



**SINCLAIR PZ.4**  
STABILISED POWER SUPPLY UNIT

A heavy duty a.c. mains power supply unit delivering 18V d.c. at 1.5A. Designed for Sinclair IC-10 or for assemblies using two Z.12s and stereo 25 unit.

99/6

Ready built and tested.

# SINCLAIR Z.12

## 12 WATT AMPLIFIER AND PRE-AMP

The Sinclair Z.12 has fantastic power-to-size ratio, and great adaptability. It will operate from batteries or PZ.4 mains power supply unit, and gives superb stereo reproduction for modest outlay. Thousands are in use throughout the world—in hi-fi, electronic music instruments, P.A., intercom systems, etc. This true 12 watt amplifier is supplied ready built, tested and guaranteed together with the Z.12 manual which details control circuits enabling you to match the Z.12 to your precise requirements. For complete listening satisfaction use your Z.12 system with Q.14 loudspeakers. It assures superb quality with substantial saving in outlay.



### ★ IDEAL FOR BATTERY OPERATION

$3 \times 1\frac{1}{2} \times 1\frac{1}{2}$  in ● Class B Ultralinear output ● 15-50,000Hz  $\pm 1$ dB ● Suitable for 3, 5, 8 or 15 $\Omega$  input—2mV into 2k $\Omega$  ● Output—12 watts R.M.S.

continuous sine wave (24W peak) 15V music power (30V peak) ● Ready built, tested and guaranteed.

89/6

## SINCLAIR GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full at once and without question. Full service facilities available to all purchasers.



**SINCLAIR RADIONICS LTD**  
22 NEWMARKET ROAD  
CAMBRIDGE. OCA3-52731

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Please send POST FREE

NAME .....

ADDRESS .....

For which I enclose cash/cheque/money order

PE1068

# RADIONIC

**LEARN AS YOU BUILD  
AT HOME  
THE EXCITING WAY**

Clear, simple, versatile, this rugged system can build almost any electronic circuit. Ideal for the experimenter; the teacher; and the complete beginner. Already used by well over 1,500 schools in the U.K.

Selected by the Council of Industrial Design for all British Design Centres. Featured in Sound and Television broadcasts.

Beautifully engineered; battery operated; no soldering; no prior knowledge needed. Results guaranteed by our technical department. People say:

- "I can only describe the results as brilliant, absolutely brilliant."
- "You have opened up a new world."
- "Nothing could paint the picture clearer than building these sets."
- "The kit has been used by my son (aged 10) with complete success."
- "Most impressive—a stroke of genius whoever devised it."

**UNIQUE!** Our "No soldering" printed circuit board for superhet portable. Simply insert components and tighten nuts.

No. 1 Set £7.10.0. 14 Circuits (Earphone)

No. 2 Set £9.0.0. 20 Circuits (Earphone)

No. 3 Set £13.10.0. 22 Circuits (7" x 4" Loudspeaker Output)


No. 4 Set £18.10.0. 26 Circuits (incl. 6-transistor and reflex superhets)

**ELECTRONICS KIT:** 80 plus circuits £19.7.0. (Prices Post Free)


Full details from:

**RADIONIC PRODUCTS LIMITED**  
STEPHENSON WAY, THREE BRIDGES  
CRAWLEY, SUSSEX  
Tel.: CRAWLEY 27028

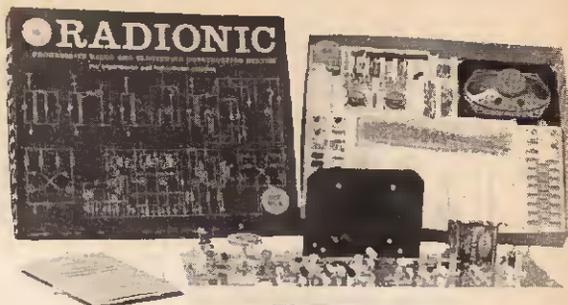
## RADIO & ELECTRONIC INSTRUCTIONAL SYSTEM



A No. 4 SET and 6-TRANSISTOR SUPERHET

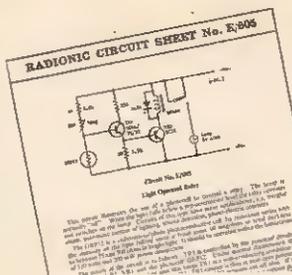

Theoretical Circuit

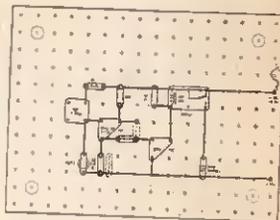

Practical Layout

E1605 Light Operated Relay.

Our 'E' Series of basic electronic circuits is available separately.

**4-STATION INTERCOM**

£7/15/0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 60ft. and other accessories. P. & P. 7/6.

**WIRE-LESS INTERCOM**  
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price 12 gns. P. & P. 7/6 extra.

**INTERCOM/BABY ALARM**

Originally 6 gns. OUR PRICE ONLY 59/6

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 60ft. connecting wire. Battery 2/6. P. & P. 4/6.

**Transistor TELEPHONE AMPLIFIER**

Useful 6 gns. 59/6

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 2/6 extra. P. & P. 2/6. Full price refunded if not satisfied in 7 days.

**WEST LONDON DIRECT SUPPLIES (PE/10)**  
169 KENSINGTON HIGH STREET, LONDON. W.8

**IT'S A MUST  
OUR  
CATALOGUE  
JOIN THE  
THOUSANDS  
OF SATISFIED CUSTOMERS  
SEND NOW FOR**

**OUR NEW 1968/69  
illustrated catalogue  
NOW AVAILABLE  
(send 2/- in stamps for your copy)**

Catalogue contains prices and details of Amplifiers — Hi-Fi Tuners — Loudspeakers — Pick-ups — Playing Decks — Microphones — Test Meters — Hand Tools — Valves — Soldering Irons — Tape Recording Accessories, etc.

**OFFICIAL SUPPLIERS TO MANY  
EDUCATION AUTHORITIES AND  
RESEARCH ESTABLISHMENTS**

Usual Educational Discounts

**ALPHA RADIO SUPPLY CO**  
103 Leeds Terrace, Leeds 7. Tel. 25187

**CRESCENT RADIO LTD.**  
(electronic component specialists)

For all regular components try  
40 Mayes Road, Wood Green, N.22  
For surplus components and equipment try  
11 Mayes Road, Wood Green, N.22

**THREE TRANSISTOR RADIO KIT**  
For you to make on a ready made printed circuit board. Gives good loudspeaker reception on the medium wave. Price includes postage and full set of instructions. Complete Kit 39/6 each.

**SPECIAL LINES**

45 m/h Ferroxcube Choke L.A.3 size	4/6 each
Midget Relays 500 ohm at 9 volt	5/- each
OC81 Driver Transformer (Transformer-Transistor Type)	2/- each
Mullard Polystyrene Capacitors 0.47mF	2/- per doz.
Brass B.A. Terminals	6d each
On/Off Rocker Switches	1/3 each
D/P Mains Rotary Switches	2/- each
3.5m/in Insulated Jack Socket	1/- each
Twin Transistor Heat Clips (OC81 size)	6d each
8 ohm Transistor Earpieces	1/6 each

**REED SWITCHES**

Hivac X54	4/6 each
Hivac X59	4/6 each
Hivac UD 563	4/6 each

**BARGAIN CHASSIS**  
All usable components

1 Electrolytic capacitor 100 plus 100mF	
1 Electrolytic capacitor 100mF at 150V	
1 Electrolytic capacitor 8mF w/ 450V	
1 0.12mF @ 600V	
2 Silicon Diodes	
2 Pre set Pots (1) 500kΩ, (1) 2MΩ.	
1 2mF 350V	
5 mixed resistors	
1 Transformer	6/6 each


With our new premises in Mayes Road we can now offer an even wider selection of components for the home constructor and enthusiast.

**POSTAGE WITH ORDER PLEASE**


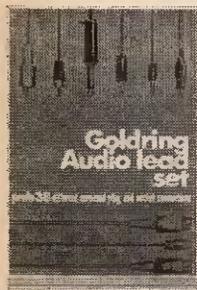
## Short of a lead?

With a 3-pin DIN plug on one end and 3.5mm jack on the other? With the Goldring Screened Audio Lead Set, you've got it—instantly—at your finger tips. And 37 other different equipment-to-equipment connections as well. With cable lengths of 20', 40', or 60' according to the combinations you use. All tidily and instantly to hand in a small neat storage box. There's no longer any need to have an unwieldy collection of dozens of different leads... and still be short of the right one! This new Goldring set will give you most of the connections you're ever likely to want—without searching for cables and plugs, without soldering, without waiting, without further expense. The Goldring Audio Lead Set, from your Hi-Fi dealer, **£3.6.0** is a real investment at



\*Goldring are now marketing an extremely useful range of individually packed leads, plugs, sockets and connections for audio enthusiasts.

**GOLDRING MANUFACTURING CO. (G.B.) LTD.,**  
486-488 High Road, Leytonstone, London, E.11.  
Tel: Leytonstone 8343.

## SOLDERING INSTRUMENTS



With the introduction of the latest moulded Nylon handle, the change-over to this type throughout the range is now complete. The LITESOLD range includes seven models (10, 18, 20, 25, 30, 35 and 60 watts), and many accessories.

The newest handle is fitted to the 30, 35 and 60 watt models, the latter being an improved version of the 55 watt model which it supersedes.

Other improvements featured on the 60 watt model are the simplification of the bit mounting and element fixing arrangements, which bring it into line with the other LITESOLD models. There is also an increase in performance.

All LITESOLD models are now available, to special order, with neon indicator lamps. This feature is valuable in reducing the risk of burns, and of fires caused by instruments left on.

The indicators are mounted inside the handles, which are made from translucent Nylon for this application. An orange glow is clearly seen through the handles whenever the supply is switched on.

Please ask for colour catalogue L/37

## LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, GR9 2LL  
Tel. 01-688 8589 & 4559



### STEREOGRAM CABINET \$19

An elegant Stereogram Cabinet in modern Veneered Mahogany and cloth covered Front Panel

BLACK LEATHERETTE SIDE PANELS  
Dimensions: 52" x 17½" x 12". Speaker positions for Twin 10" x 5" Speakers




OTHER MODELS—SEND FOR LIST

17in.—£11.10.0 Carr. 30/-

19in. SLIM-LINE  
FERGUSON 24 gns.


TWO-YEAR GUARANTEE  
EX-RENTAL TELEVISIONS

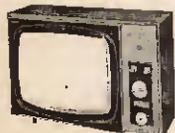FREE ILLUSTRATED  
LIST OF TELEVISIONS  
17"—19"—21"—23"



WIDE RANGE OF MODELS  
SIZES AND PRICES  
DEMONSTRATIONS DAILY

### COCKTAIL/STEREOGRAM CABINET £25

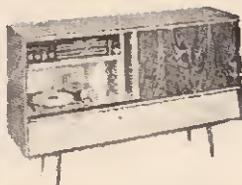

Polished walnut veneer with elegant glass fronted cocktail compartment, padded. Position for two 10" elliptical speakers. Record storage space. Height 35½", width 52½", depth 14½". Legs 1 gn. extra.

### TRANSISTOR CHASSIS DI 59/6

6 Transistors, LW/MV. Brand New. Famous British Manufacturer (LESS SPEAKERS). Size 7½" x 3½" P. & P. 4/6.

### TRANSISTOR RECORD PLAYER CABINETS 19/6 P. & P. 7/6.

### SINGLE PLAYER CABINETS 15/6. P. & P. 7/6.

TRANSISTOR CASES 19/6. Cloth covered, many colours. Size 9½" x 6½" x 3½". P. & P. 3/6. Similar cases in plastic 7/6.

### AUTOCHANGERS £8.19.6

Garrard 3000 with Sonotone 9T HC. D/S Stereo Cartridge.

**DUKE & CO. (LONDON) LTD.**  
621/3 Romford Road, Manor Park, E.12  
Phone 01-478 6001-2-3 Stamp for Free List.

# Look What's New from HEATHKIT



## Low-cost FM Stereo Receiver, AR-17


Kit K/AR-17

**£39.0.0**

P.P. 10/6

Cabinet walnut or teak finish **£3.10.0** extra

28 transistor, 7 diode circuit, 14 watts music power, 10 watts r.m.s. from 25-35,000Hz @  $\pm 1$ dB. Automatic stereo indicator light. Adjustable phase control. Complete front panel controls. Flywheel tuning. Factory assembled and aligned FM front-end. Circuit board assembly. Compact 10 $\frac{3}{8}$ " deep  $\times$  3" high  $\times$  12" wide. Use free standing with Heathkit cabinet optional extra.

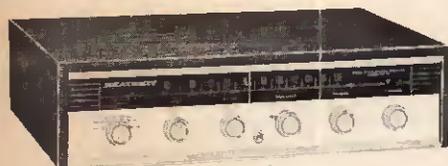

## Quality FM Stereo Receiver, AR-14

Kit K/AR-14

**£54.0.0**

P.P. 13/6

Cabinet walnut or teak finish **£4.10.0** extra

31 transistor, 10 diode circuit can deliver  $\pm 1$ dB, 15 to 50,000Hz at 10 watts per channel (20 watts total) 15 watts per channel 1HF music power (30 watts total). Wide-band FM/FM stereo tuner plus two preamps, two power amplifiers. Compact only 3 $\frac{3}{8}$ " high  $\times$  15 $\frac{1}{4}$ " wide  $\times$  12" deep. Install in a wall, free standing or in Heathkit cabinet optional extra. 210-240V 50Hz a.c.



## Low-cost FM Mono Receiver, AR-27

Kit K/AR-27

**£22.10.0**

P.P. 10/6

Cabinet walnut veneered **£3.10.0**

13 transistor, 6 diode circuit. 7 watts music power.  $\pm 1$ db, 25 to 60,000Hz at 6 watts. Input connectors for phono and aux. Complete front panel controls. Flywheel tuning, factory pre-aligned FM tuner. Circuit board assembly. Compact bookshelf size. Install in a wall, free standing or in cabinet optional extra. 210-240V 50Hz a.c. operation.




Kit K/IM-25

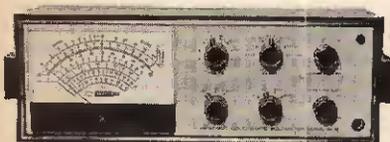**£48.10.0**

P.P. 10/6

9 a.c. and 9 d.c. ranges 150mV up to 1,500V f.s. 7 resistance ranges, 10 ohms centre scale with multipliers  $\times 1$ ,  $\times 10$ ,  $\times 100$ ,  $\times 1k$ ,  $\times 10k$ ,  $\times 100k$  and  $\times 1Meg$ . . . measures from 1 ohm to 1,000Mohms. 11 current ranges from 15 $\mu A$  full scale to 1.5A full scale. 11Mohm input impedance d.c. 10Mohm input impedance a.c. 6" 200 $\mu A$  meter. Internal battery power or 120/240V a.c. 50Hz supply. PCB construction.




Kit K/IM-16

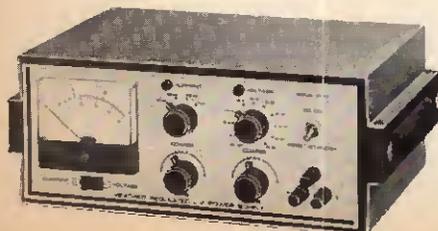**£28.8.0**

P.P. 10/6

8 a.c. and 8 d.c. ranges 0-5V to 1,500V f.s. 7 ohm-meter ranges with 10 ohms centre scale with multipliers  $\times 1$ ,  $\times 10$ ,  $\times 100$ ,  $\times 1k$ ,  $\times 10k$ ,  $\times 100k$  and  $\times 1Meg$ . . . 11Mohm input on d.c., 1Mohm on a.c. Internal battery power or 120/240V a.c. 50Hz supply.



## Solid-State Low Voltage Power Supply, IP-27

Kit K/IP-27

**£46.12.0**

P.P. 10/6

0.5 to 50V d.c. with better than  $\pm 15$  Millivolts regulation. Four current ranges 50mA; 150mA, 500mA, and 1.5 amperes. Adjustable current limiter: 30 to 100% all ranges. Panel meter for output voltage or current.

# HEATHKIT for Top Value in Electronics

A kit for every interest — Home Workshop — Hi-Fi — Radio — Test — Amateur

## Latest STEREO TAPE RECORDER, STR-1



Fully portable—own speakers

Kit £58. 0. 0 incl. P.T. P.P. 10/6  
Ready-to-use £72. 0. 0 incl. P.T.  
P.P. 10/6

### FOR THIS SPECIFICATION

½ track stereo or mono record and playback at 7½, 3½ and 1½ lps. Sound-on-sound and sound-with-sound capabilities. Stereo record, stereo playback, mono record and playback

on either channel. 18 transistor circuit for cool, instant and dependable operation. Moving coil record level indicator. Digital counter with thumb-wheel zero reset. Stereo microphone and auxiliary inputs and controls, speaker/headphone and external amplifier outputs... front panel mounted for easy access. Push-button controls for operational modes. Built-in stereo power amplifier giving 4W rms per channel. Two high efficiency 8" x 5" speakers. Operates on 230V a.c. supply.

Versatile recording facilities. So easy to build—so easy to use.

## Latest STEREO AMPLIFIER, TSA-12

12 x 12 watts output

Kit £32. 16. 0 less cabinet P.P.10/6  
Cabinet £2. 5. 0 extra



Ready-to-use £39. 10. 0 (less cab.) P.P. 10/6

### FOR THIS SPECIFICATION

17 transistors, 6 diode circuit. ±1dB, 16 to 50,000Hz at 12W per channel into 8 ohms. Output suitable for 8 or 15 ohm loudspeakers. 3 stereo inputs for Gram, Radio and Aux. Modern low silhouette styling. Attractive aluminium, golden anodised front panel. Handsome assembled and finished walnut veneered cabinet available. Matches Heathkit models TFM-1 and AFM-2 transistor tuners.

Full range power... over extremely wide frequency range. Special transformerless output circuitry. Adequately heat-sinked power transistors for cool operation—long life, 6 position source switch.

## High-performance CAR RADIO, CR-1



Superb long and medium wave entertainment wherever you drive. Complete your motoring pleasure with this compact outstanding unit.

8 Latest semiconductors (6 transistors, 2 diodes). For 12V positive or 12V negative earth systems. Powerful output (4W). Preassembled and aligned tuning unit. Push-button tone and wave change controls. Positive manual tuning. Easy circuit board assembly. Instant operation, no warm-up time. Tastefully styled to harmonise with any car colour scheme. High quality output stage will operate two loudspeakers if desired. Can be built for a total price.

KIT (incl. speaker) £14.12.0 incl. P.T.  
P.P. 4/6

Ready-to-use £19.12.0  
(incl. speaker) P.P. 4/6

## Latest Portable Stereo Record Player, SRP-1

Automatic playing of 16, 33, 45 and 78 rpm records. All transistor—cool instant operation. Dual LP/78 stylus. Plays mono or stereo records. Suitcase portability. Detachable speaker enclosure for best stereo effect. Two 8in x 5in special loudspeakers. For 220-250V a.c. mains operation. Overall cabinet size 15½ x 3½ x 10½in.



Compact, economical stereo and mono record playing for the whole family—plays anything from the Beatles to Bartok. All solid-state circuitry gives room filling volume.

KIT £28.6.0 incl. P.T. P.P. 10/6

Ready-to-use £35.4.0  
P.P. 10/6

## A wide range of SPEAKER SYSTEMS



SSU-1

**HI-FI SPEAKER SYSTEM. Model SSU-1.** Ducted-port bass reflex cabinet "in the white". Two speakers. Vertical/horizontal models with legs. Kit £14. 0. 0. P.P. 12/- Without legs, Kit £13. 4. 0 incl. P.T. P.P. 7/6



Berkeley

**The BERKELEY SLIM-LINE SPEAKER SYSTEM,** fully finished walnut or teak veneered cabinet for faster construction. Special 12" bass unit and 4" mid/high frequency unit. Range 30-17,000Hz. Size 26" x 17" only 7½" deep. Modern attractive styling. Excellent value.

Kit £21. 4. 0. P.P. 13/6

Ready-to-use £24. 0. 0. P.P. 13/6

## Transistor Portables

**UXR-1,** now available in Modern coloured cases or leather.

6 transistor, 1 diode circuit. 7 x 4in. speaker. LW and MW coverage. Case: brown leather; or colours navy blue, coral pink, lime green. Please state 2nd choice.

Kit £12. 8. 0. incl. P.T. Colour

Kit £13. 8. 0. incl. P.T. Leather

Ready-to-use £15.10.0. P.P. 4/6



UXR-1

**UXR-2,** choice of black or brown real leather cases.

7 transistor, 3 diode circuit. Battery saving circuitry. LW and MW coverage. Pushbutton wave change. Slide rule tuning.

Kit £15. 10. 0. incl. P.T. Leather

Ready-to-use £17.10.0. P.P. 6/-




UXR-2

SEE HEATHKIT MODELS at

**GLOUCESTER**  
Factory and Showroom  
Bristol Road

**LONDON**  
233 Tottenham  
Court Road

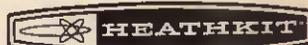**BIRMINGHAM**  
17-18 St. Martins House  
Bull Ring



## FREE CATALOGUE

Describes these and over 250 other Heath Kits. Save up to 50% by building them yourself. Use coupon and send for your FREE copy, today!

**DAYSTROM LTD. Dept. PE-11**  
Gloucester Tel. 29451

Enclosed is £..... plus Packing and Post.

Please send model(s).....

Please send FREE Heathkit Catalogue.  Details.....

Name.....  
(Please Print)

Address.....

City.....

Prices and Specifications subject to change without prior notice.

# Ordering Components is FUN



with **THIS**  
Catalogue  
in your hands!

**A bargain  
at 7/6  
plus 3/- p&p.**

Ever had trouble locating a particular piece for your project? Ever wasted time thumbing through confusing price lists? Ever been foot-weary and frustrated tramping round the shops?

Sigh no more. Just sink into an armchair and enjoy life with a Home Radio Catalogue! Pick your parts. Grab your pen. Make for a letter-box. Your chosen items will be with you almost before you can get back to that armchair!

This Catalogue really is a *must* if you're interested in Radio and Electronics. It has 256 pages, over 7,000 items listed, over 1,300 illustrations. With each catalogue we supply a Bargain List, a Book Mark giving Electronic Abbreviations, an Order Form and an Addressed Envelope. All this for only 7/6 plus 3/- post and packing. By the way, every catalogue contains 5 vouchers, each worth 1/- when used as directed. Send the coupon today with your cheque or P.O. for 10/6.

Please write your Name and Address in block capitals

Name .....

Address .....

Home Radio (Mitcham) Ltd., Dept. PE, 187 London Rd., Mitcham, CR4 2YQ

## ELECTRONS AND NEURONS

DOWN the ages mathematicians, philosophers, scientists, and other great minds have expended thought and effort in attempts to devise machines with some kind of artificial intelligence. Numerous artifacts, automata, or robots (name them what you will) that imitate, albeit in a crude way, some of the characteristic attributes of man have been built at various times. The techniques employed have been equally varied in character.

Since the advent of electronics, the crude efforts of earlier days have been put in the shade. Much more is possible now. The intelligent machine is now a reality. But it is well to separate fact from fancy.

The affinity between electronic circuit systems and living systems is generally well known. The creation of an electronic system analogous in many ways to the human nerve system can be achieved. But even so, the electronic automata will fall short of its human counterpart in many important respects. Present techniques do not permit the assembling of anything like the electronic equivalent of the 10,000 million cells or neurons contained in the human brain. Despite this limitation, some truly amazing results have already been achieved in simulating certain human faculties. Assuredly great advances will continue to be made.

Scientists have explored electronic circuit techniques for biological and other research purposes. Their technological interests overlap those of industrial engineers who specialise in the field of control systems and automation. Apart from this, however, the philosophical approach of the scientist intent upon building working models that closely resemble a living cell or whole animal will be in contrast with the more materialistic approach of the engineer engaged in designing systems for strictly utilitarian purposes.

Now, can the amateur do anything purposeful and creative in this rather exotic field? We think he can, and for this reason have launched this month a fascinating series entitled "Bionics". In one sense, the experimenter will be on familiar ground, working with the normal electronics stock-in-trade; but he will need to reorientate his thinking to a considerable extent.

Experimenting in this field of "electrons and neurons" will lead to a wider appreciation of other branches of science, particularly biology. It could be a stimulating change from more mundane applications of electronics.

F. E. Bennett—*Editor*

## THIS MONTH

### CONSTRUCTIONAL PROJECTS

SENSITIVE D.C. VOLTMETER	773
HI FI TRANSISTOR	
MICROPHONE	781
RHYTHM GENERATOR	792
FROST ALARM	802

### SPECIAL SERIES

BIONICS—I	768
EXPERIMENTS WITH SOUND, LIGHT, AND COLOUR—4	804


### GENERAL FEATURES

INGENUITY UNLIMITED	784
INFRA-RED COMMUNICATIONS	788
LSA DEVICE	813

### NEWS AND COMMENT

EDITORIAL	767
MARKET PLACE	787
NEWS BRIEFS	801
MEETINGS	801
RADIO TRADE SHOWS 1968	808

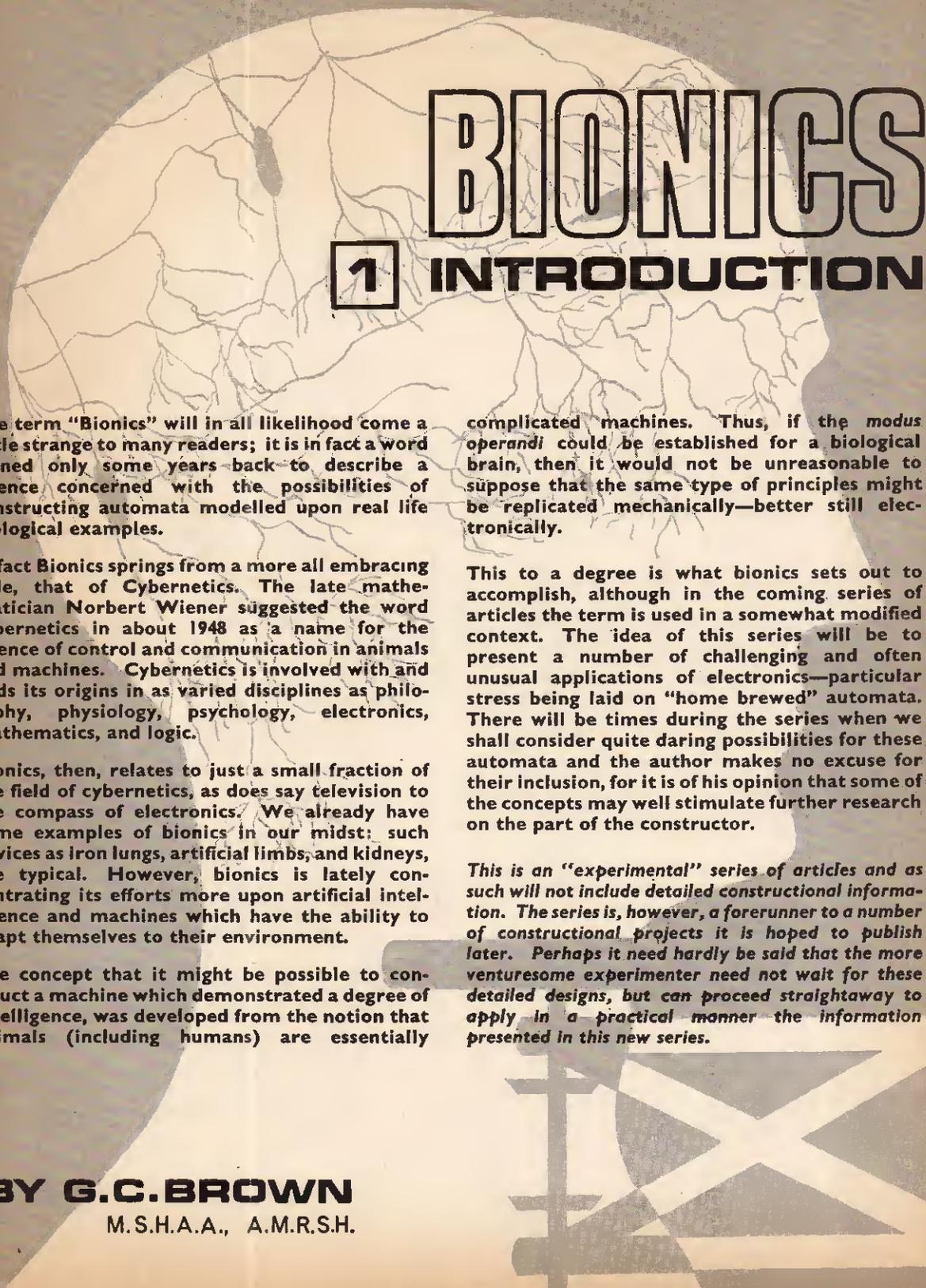*Our December issue will be published on  
Friday, November 15*



# BIONICS

## 1 INTRODUCTION

The term "Bionics" will in all likelihood come a little strange to many readers; it is in fact a word coined only some years back to describe a science concerned with the possibilities of constructing automata modelled upon real life biological examples.

In fact Bionics springs from a more all embracing title, that of Cybernetics. The late mathematician Norbert Wiener suggested the word cybernetics in about 1948 as a name for the science of control and communication in animals and machines. Cybernetics is involved with and finds its origins in as varied disciplines as philosophy, physiology, psychology, electronics, mathematics, and logic.

Bionics, then, relates to just a small fraction of the field of cybernetics, as does say television to the compass of electronics. We already have some examples of bionics in our midst: such devices as iron lungs, artificial limbs, and kidneys, are typical. However, bionics is lately concentrating its efforts more upon artificial intelligence and machines which have the ability to adapt themselves to their environment.

The concept that it might be possible to construct a machine which demonstrated a degree of intelligence, was developed from the notion that animals (including humans) are essentially

complicated machines. Thus, if the *modus operandi* could be established for a biological brain, then it would not be unreasonable to suppose that the same type of principles might be replicated mechanically—better still electronically.

This to a degree is what bionics sets out to accomplish, although in the coming series of articles the term is used in a somewhat modified context. The idea of this series will be to present a number of challenging and often unusual applications of electronics—particular stress being laid on "home brewed" automata. There will be times during the series when we shall consider quite daring possibilities for these automata and the author makes no excuse for their inclusion, for it is of his opinion that some of the concepts may well stimulate further research on the part of the constructor.

*This is an "experimental" series of articles and as such will not include detailed constructional information. The series is, however, a forerunner to a number of constructional projects it is hoped to publish later. Perhaps it need hardly be said that the more venturesome experimenter need not wait for these detailed designs, but can proceed straightaway to apply in a practical manner the information presented in this new series.*

**BY G.C. BROWN**  
M.S.H.A.A., A.M.R.S.H.

## The design and construction of electronic "animals" or machines with artificial intelligence

In nearly every one of us there is a latent desire to create. Not only to create, but to create something unique. It is therefore not surprising that since time immemorial man has made numerous (relatively unsuccessful) attempts to devise machines that might imitate himself.

Probably one of the first examples we can find is the lever; not in fact an actual imitation of man, but a device that could aid his physical strength. As time continued, so he produced more and more powerful "muscle amplifiers" (this is, after all what they are), and so if we stop to consider say a huge jib crane capable of lifting some tons, the amplification factor involved may well be in the order of several million. No mean feat, for a man!

### AMPLIFICATION OF MENTAL ENERGY

The foregoing examples serve to indicate the "stepping stones" from which man began his attempts to synthesise certain characteristics of himself and other animals. It was not long, however, before it occurred to him that if *muscular* energy could be amplified, so indeed the same should apply to *mental* energy, and so we have the abacus or bead board which certain Asiatic countries are still using with great success.

With the advent of electronics it was at once realised that more rapid and yet more powerful machines could be built; and so we see the giant abaci of today: we call them computers. When electronic computers came into existence the popular press of course tended to over glamourise the machines' capabilities using such anthropomorphic terminology as "brains", "thought", etc. What the press lost sight of was that a basic digital computer however powerful or rapid, is still none-the-less a rather more sophisticated version of a mechanical desk calculator.


### THOUGHT AND LEARNING PROCESSES

Unfortunately, although thought is a very intimate part of us we remain, ironically enough, unable to specify exactly what it is. However, we can say what it is not, and in no wise does any characteristic of a computer (save perhaps memory) qualify the right to be called a thought process. Before a computer can operate at all on the complex mathematics that it must handle, a programme often taking months to prepare and containing very precise orders, must accompany any calculation. If this were not enough, the computer must have all its instructions written in machine language.

It was not until about two decades ago, that man even began to "scratch the surface" of what appear to be the underlying principles of "thought" and learning processes. Although little is still understood, it is now possible to synthesise certain characteristics of the biological brain, albeit crudely, by applying the wealth of electronic principles we now have at our elbow. It is with this in mind, and with the almost limitless possibilities that it suggests that we shall discuss, and even construct, artefacts which will have "memory" and the ability to "learn".
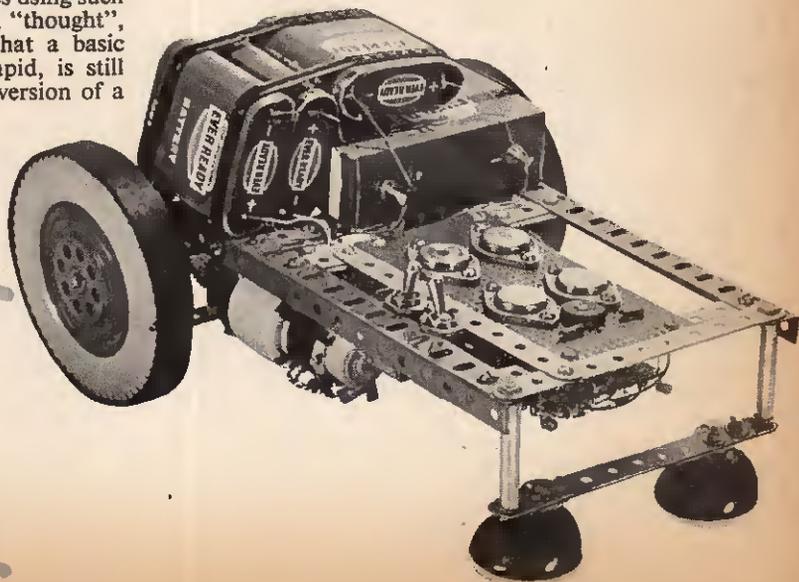
### MOBILE BREADBOARD

However, prior to considering rather more exotic devices, from a practical point of view it is a pre-requisite that we design and build some type of mobile breadboard



upon which we can perform modifications and "surgery". This then will be our first consideration, and at this stage an initial glance at Fig. 1.1 will reveal the main structure and "muscles" of the electronic animal.

Generally speaking, those of us whose interests lie in electronics rarely claim a similar zeal for the field of mechanics. In bionics this state of affairs can be a real handicap, because there are all too often times when a particular item just does not exist and one has no alternative but to fabricate. However, most of the mechanical problems can be largely solved by the use of Meccano, which readily lends itself to adaptation and "grafting". In addition, Meccano produce "ready-made" drive gearboxes which can either be used in conjunction with one of their motors, or a motor of the constructor's choice.

As will be seen from Fig. 1.1, the breadboard is basically of rigid box construction, cross members being incorporated to reduce possible twist along the length and increase its strength. The choice of chassis size was very much an arbitrary one; but in fact, providing readers maintain the general format it may be constructed to personal preference.

### GEARBOX AND WHEELS

The original model was shod with plastic tracks, but as these are frequently difficult to come by we have chosen separately driven wheels for the device given here. The motor gearbox units are mounted at the rear end of the chassis, and drive power is transmitted via final bevel gears to the road wheels. The forward end of the chassis is supported by a pair of castors; one at each corner. This was found necessary, since a single castor introduced excessive chassis twist.

The "muscles" selected to power our model are a pair of Meccano E15R motor gearbox units, but in fact any reliable equivalent would do just as well provided that the overall gear ratio is kept lower than 160 : 1. Any higher ratio would tend to make the "animal" rather intractable, and apart from anything else accurate observation would become impossible.


There are, of course, two fundamental methods for controlling the motors: relays and power transistors. As variable (analogue) control of the motors was often required, relays were rejected at an early stage in favour of power transistors. The use of transistors involves somewhat more complex circuit arrangements, but in view of their inexpensiveness and ability to provide more sophisticated control, extra time taken in building the equipment is adequately rewarded.

### "MUSCLE" CONTROL CIRCUITS


The "muscle control" circuits are shown in Fig. 1.2. At the risk of causing some slight confusion the right and left hand side motors have been referred to respectively as Port and Starboard—the reason becomes obvious upon reflection because the right hand motor will cause the "animal" to move to port, and vice-versa. Motor Mo1 is therefore Port and Mo2 Starboard: together they drive the animal in forward or reverse directions.

Alternative steering and drive arrangements of course are possible, but owing to various problems that will be apparent as we progress, the present scheme will be retained. In any case there are unlikely to be any actual biological examples which utilise separate steering and motive systems; indeed, steering is usually a function of motivation. In our model steering is achieved as an integral part of the drive functions.

Fig. 1.1. Mobile breadboard for experiments in the building of an intelligent machine or electronic "animal"

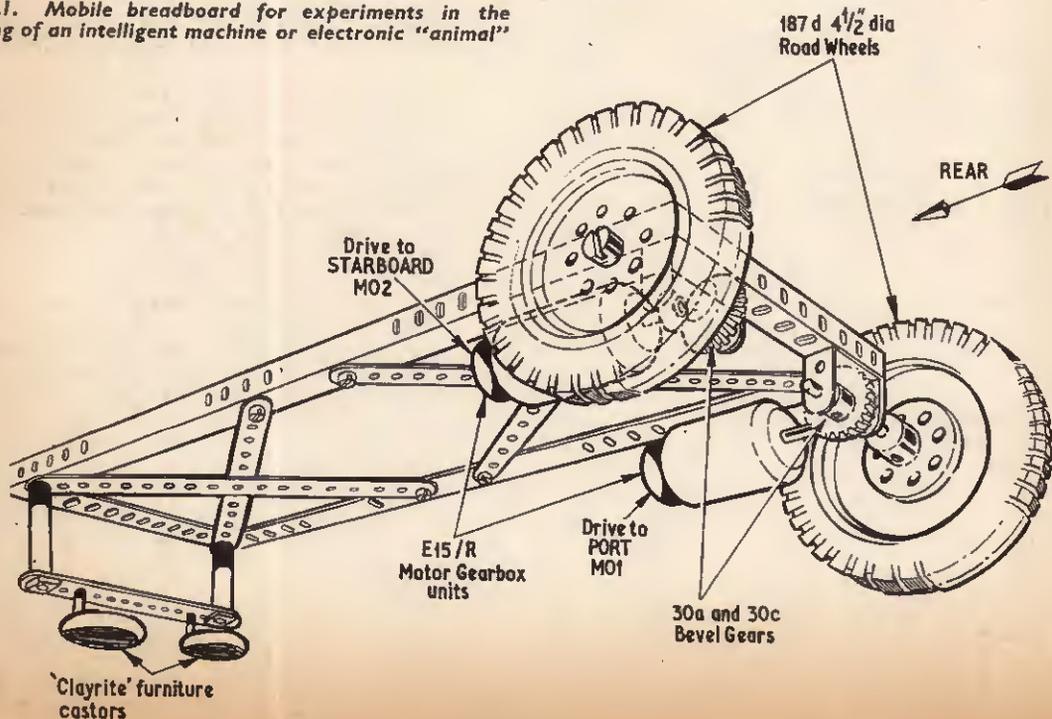



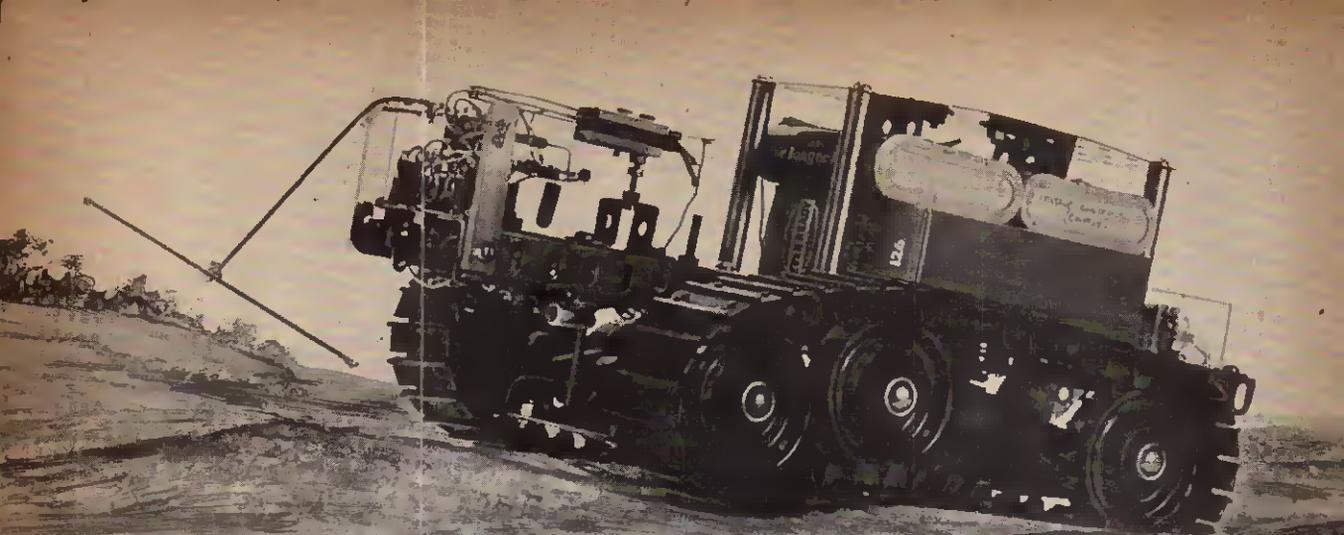

Another problem arises from the fact that animals often produce responses from what seem to be a whole repertoire of possible actions; it is therefore sometimes impossible to be specific about outputs.

At present then, for our purposes at least, we must be content to base our reasoning along the lines of well tested and easily reproducible features of behaviour. Even then, actual design work must needs be largely based on experiment.

### CONDITIONED REFLEX

One aspect of animal behaviour which should show us some rewards upon synthesis, is the conditioned reflex.

Reflexes, or more correctly reflex responses, are due to stimuli exciting certain sensory organs: they may for example be the result of light shone into the eyes, or a touch applied to some area upon the skin. These stimuli having excited a receptor cause nerve impulses to pass along the various neural pathways to the reasoning part of the brain, or cortex. Here they may interact with other types of sensory information either produced simultaneously or stored at some time in the past.

Now the reflex that concerns us is a special condition occurring as a result of the former variety, the conditioned reflex—let us call it  $R_c$ . To understand what it is and how it may be evoked, we must hearken back to Pavlov's early experiments.

Pavlov, who performed the conditioning experiments with hungry dogs, used food as a basic drive—this we shall call the "specific" stimulus  $S_s$ . The amount of saliva produced upon application of  $S_s$  was then measured. When the animals became hungry again, a further stimulus was included which would not normally cause salivation; this was a "neutral" stimulus in the form of sound, i.e. a bell. This we shall designate  $S_n$ .

Pavlov found that if  $S_n$  was applied shortly before  $S_s$ , and the combination repeated a few times,  $S_n$  would eventually produce salivation in the same way that  $S_s$  did. Hence the animals had *learnt* that the sound of the bell meant food. The neutral stimulus  $S_n$  had thus been conditioned to the specific stimulus  $S_s$  and so the result of applying  $S_n$  at future times was to elicit a conditioned reflex.

There are two important factors to remember if we require the stimulus combination to be successful in producing a conditioned reflex. Firstly  $S_n$  should occur *before*  $S_s$  *not after*; the reader will appreciate that there is little point in sounding the dinner gong after the meal has been eaten! The second fact is that assuming  $S_n$  occurs before  $S_s$ , it must be *just* before, or else it will

be of no significance. Otherwise it would be rather like announcing lunch, two hours before it was served!

### INHIBITION

So far, so good! But we have only considered the excitation mode of conditioning. What if we continue the application of  $S_n$  without the reinforcement of  $S_s$ ? That is, ring the bell without feeding the animal.

The effect of course can be virtually predicted; the bell no longer signifies the coming of food, and so the conditioned reflex is inhibited. The animal therefore no longer responds to  $S_n$ . This state of affairs is generally referred to as extinction.

However, an interesting fact emerges from inhibition of this kind, in that it too can be inhibited. One easy way to bring  $R_c$  back is to re-establish the reinforcement ( $S_s$ ).

There are more unexpected ways too: assume we take the case of a dog which, say yesterday, had its conditioned response extinguished. If today we re-apply  $S_n$ , back comes the conditioned response as strong as before; even more surprising is the fact that no matter how many times  $R_c$  is extinguished it will always re-appear. This "recovery" or disinhibition as it is called, seems to be the result of the inhibition placed upon  $R_c$  dissipating with time.

### DISTRACTING STIMULI


Disinhibition can occur in an even more striking way, a way which in fact caused Pavlov no end of problems from quite a different point of view. During his experiments there were times when he found it difficult, often impossible, to condition the animals—and it was not long before he realised the cause.

Most of the experiments were conducted in an environment where the ambient noise level was relatively high, resulting in distracting stimuli which either inhibited the conditioning, or caused irrelevant conditioned responses. These strong "external" stimuli whilst inhibiting excitation, will also remove inhibition. Hence, if  $R_c$  has been extinguished it can be recalled by the simple expedient of introducing a powerful external stimulus.

With the conditioned reflex mentioned earlier, we considered only two kinds of stimuli. Of course, virtually any stimulus combination could be used, and as we proceed with the design of our electronic "animal" so its need to deal with more and more combinations (some of them quite unusual) will increase.

Next month: "Muscle" control and reflex response.

# SENSITIVE D.C. VOLTMETER

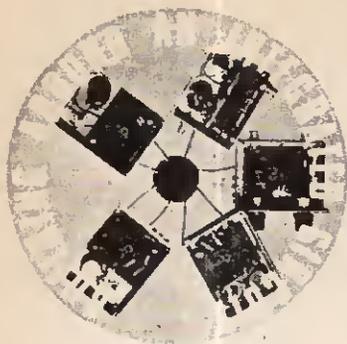

This is the third project in our five-part series

featuring the integrated circuit linear amplifier Type SL701C

Now that the inexpensive high gain silicon transistors are readily available, very small collector currents in the order of tens of microamps are often encountered in equipment, and a conventional multirange voltmeter may consume sufficient current to make voltage readings inaccurate. This article describes a d.c. amplifier which may be used to increase the sensitivity of a meter by ten or one hundred times.

## VALUE OF INTEGRATED CIRCUIT

We could design and build a high gain d.c. amplifier using conventional components, but we might have a problem with drift in d.c. levels with temperature. The best solution would be to use an integrated circuit operational amplifier, where the manufacturer has already done the best he can to minimise offset voltage and drift, and where the very method of construction ensures that components are *inherently* excellently matched.

Until this point in our series on the use of the operational amplifier, we have only considered a.c. circuits, and have suggested that the d.c. level at the output of the amplifier will be almost zero. While this is true, since we now require a d.c. amplifier, we must investigate in more detail the reasons for this offset.

## THE OFFSET VOLTAGE

The d.c. offset at the output of the amplifier is due to the following causes.

(a) Mismatch of the electrical characteristics of the amplifier; mainly the difference between base to emitter voltages and current gains of the two transistors which comprise the differential input pair, and also the mismatch between their associated collector resistors.

(b) The finite input current flowing through the series resistor in each input lead.

Since the magnitude of the offset will depend on the closed loop gain of the complete amplifier circuit, the parameters of the integrated circuit itself are always referred back to the input of the integrated circuit. If the amplifier were perfect each input would draw the same current and require the same base to emitter voltage, but in practice this is not so. The difference between the input currents is defined as the input offset current, while the input offset voltage is that voltage which has to be applied between the input terminals to obtain zero output voltage.

For a d.c. amplifier it is obviously important to know what output offset we must expect, and how to trim this out if required, but even for an a.c. amplifier the undistorted peak to peak swing of the output may be restricted if the d.c. steady state level of the output is appreciably unbalanced.


For the Plessey SL701C the parameters we require are:

Input base current (either side)	= $3\mu\text{A}$ maximum
Input offset base current	= $1.8\mu\text{A}$ maximum
Input offset voltage	= $25\text{mV}$ maximum

These are maximum figures, and typical figures are less. By inserting the appropriate figures in the formulae to be considered next we can obtain typical or maximum values, but we have only used the maximum values for our examples. For completeness we first consider the offset of an a.c. amplifier.
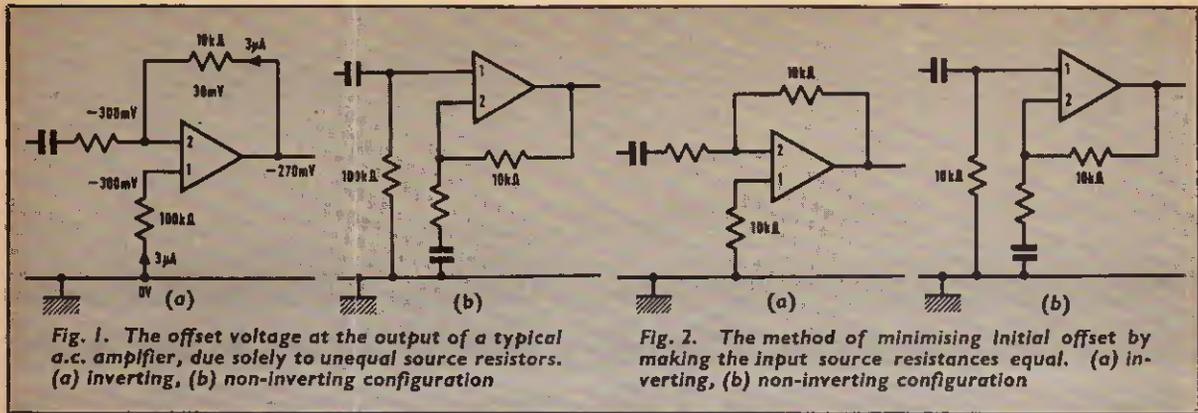
## OFFSET VOLTAGE OF AN A.C. AMPLIFIER

For the amplifier it does not matter if we use the inverting or non-inverting configuration, the d.c. conditions are identical. In the example of Fig. 1 we have a 100 kilohm resistor from the non-inverting input to earth and a 10 kilohm resistor from the inverting



input to the output. The output is assumed to be a low impedance point so that the effective source resistance for this input is 10 kilohm.

If we assume for the moment that there is no offset voltage and no offset current from the integrated circuit, we can work out the possible offset voltage. Input 1 draws up to  $3\mu\text{A}$  through 100 kilohms and so can be up to 300mV below earth potential. If there is no offset voltage between the two inputs (in any case the maximum value of 25mV we might have is small compared with 300mV) then input 2 must also be at  $-300\text{mV}$ .

Since input 2 also draws  $3\mu\text{A}$ , the 10 kilohm resistor will have 30mV across it and the d.c. level of the output will have to be at  $-270\text{mV}$  to maintain these d.c. conditions. We thus have an output offset voltage of 270mV solely due to the different source resistors for the two input. If we now take offset voltage and current into account this could increase or decrease this value depending on the relative polarities.

Unless we specifically need the high input impedance of 100 kilohms for the non-inverting configuration we can minimise this offset due to unequal source resistors by making the resistors equal, as in Fig. 2.

In the inverting configuration it might be advisable to decouple the non-inverting input to earth, both to prevent capacitive pickup which might cause positive feedback and also to help maintain closed loop h.f. stability. This is especially important if a high value of source resistance is used, as in Fig. 3.

### INITIAL OFFSET

If the source resistors are made equal so that the effects of input base currents through the input resistors

are approximately self cancelling, then the initial offset (it depends now on the offset current and offset voltage) may be calculated. The offset due to current is given by the input offset current multiplied by the source resistance, for our example of Fig. 2, this becomes: Offset due to current =  $1.8 \cdot 10^{-6} \cdot 10 \cdot 10^3 = 18\text{mV}$

We are better off with low values for the source resistors rather than high ones.

From the d.c. point of view any offset voltage at the input is amplified unity times, so that the possible total offset is:


$$\begin{aligned} \text{Total offset} &= \text{offset due to current} + \text{offset due to voltage} \\ &= 18 + 25\text{mV} = 43\text{mV} \end{aligned}$$


We can place these results into a general formula for future reference, and need the Fig. 4. The offset voltage has been shown as an addition to the non-inverting input while the current offset has been shown as a current which in effect flows out or into the inverting input and through the feedback resistor. We have equal source resistors for both inputs, and  $I_d$  is the current offset and  $E_d$  the voltage offset. Total offset = current offset  $\times R$  + voltage offset.

$$E_o = I_d R + E_d \quad \text{A.C. amplifier}$$
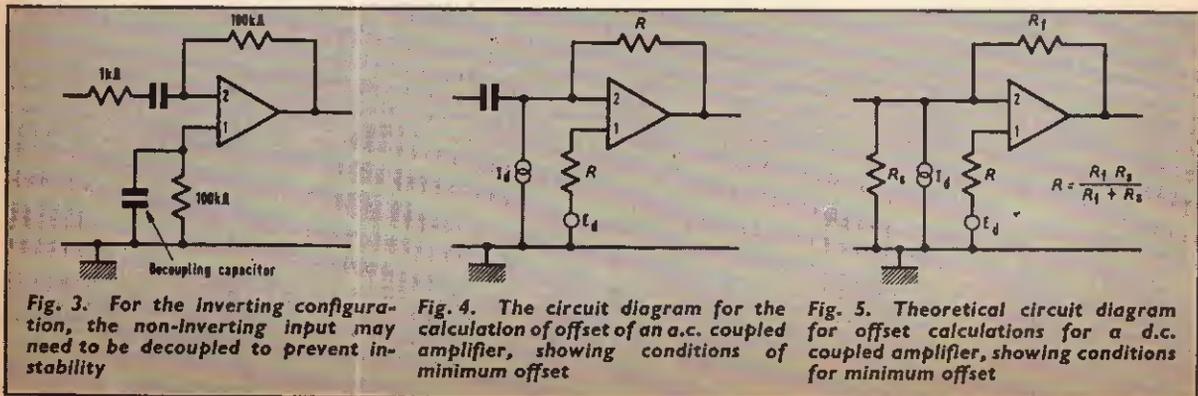
### OFFSET VOLTAGE OF A D.C. AMPLIFIER

For a d.c. amplifier we have a similar situation, but the offset voltage of the integrated circuit is amplified by the overall gain of the complete circuit (Fig. 5).



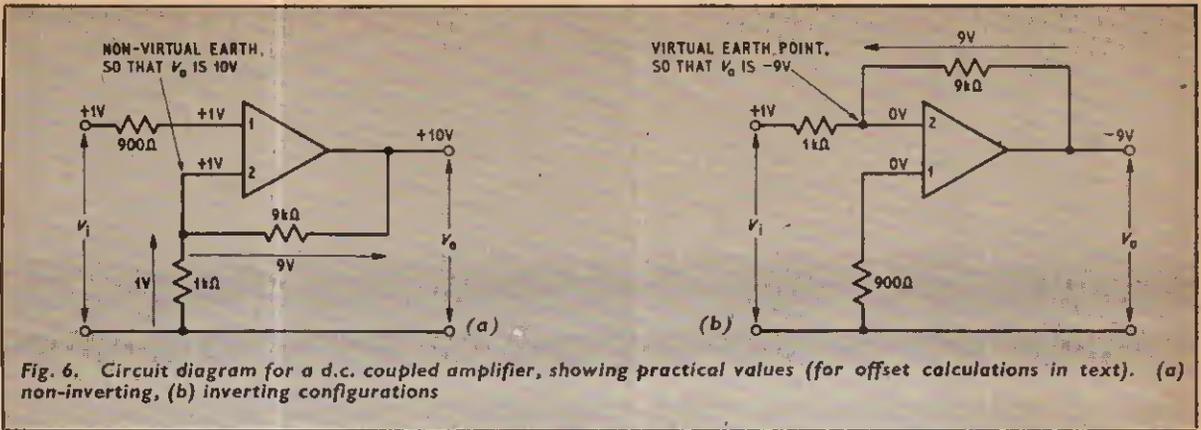

In this case to maintain the same source resistance for each input, the resistor  $R$  has to be made equal to the resistance of  $R_s$  and  $R_f$  in parallel.

$$R = \frac{R_f R_s}{R_f + R_s}$$

If we consider the practical d.c. amplifier of Fig. 6, we can arrive at our d.c. offset. From the point of view of the feedback both circuits are identical, but from the signal point of view we obtain different gains because of the slight difference in how the signal is applied. For the non-inverting configuration the input adds to the voltage developed across the feedback resistor, while for the inverting configuration this does not happen.

For Fig. 5 or Fig. 6 the total offset voltage is given by:

$$E_o = E_d \left( 1 + \frac{R_f}{R_s} \right) + I_d R_f \quad \text{D.C. amplifier}$$

In the case of Fig. 6 this becomes:

$$E_o = 25(1 + 9) + 1.8 \cdot 10^{-6} \cdot 9 \cdot 10^3 \\ = 250 + 16.2 \text{mV} = 266.2 \text{mV}$$

For a.c. amplifiers where the d.c. offset might reduce the available swing or for d.c. amplifiers where we require 0V out for 0V input, we will wish to balance out any offset.


## AMPLIFIERS WITH OFFSET BALANCING

The best type of circuit chosen to balance offset depends on the impedance of the signal source. For low impedance sources (say up to 5 kilohm) the circuits of Fig. 7a or b are suitable.

In Fig. 7a since we have a control to balance offset, the low value resistor from the non-inverting input to earth may be omitted.  $R_3$  is chosen to be much greater than  $R_1$  and the range on the potentiometer is chosen so that the gain from point X (of  $R_f$  over  $R_3$ ) to the output is sufficient to balance out the expected offset. For Fig. 7b  $V_{R1}$  is chosen to be much greater than  $R_1$ , while the high value resistor to the h.t. line is chosen to give a suitable range.

For a high impedance source acting as a current generator, it would be better to use the circuit of Fig. 8. To give sufficient range on the potentiometer the values are chosen so that the potentiometer value is 1.5 times  $R_2$  while the series resistor is 0.5 of  $R_2$ . This gives (for  $R_2$  of 47 kilohms) a potentiometer value of 70 kilohms and a series resistor of 22 kilohms, so that using 100 kilohms with a series resistor of 22 kilohms should give more than enough range.

Now that we have dealt, in general, with d.c. amplifiers and balancing, we can go on to consider our current amplifier.

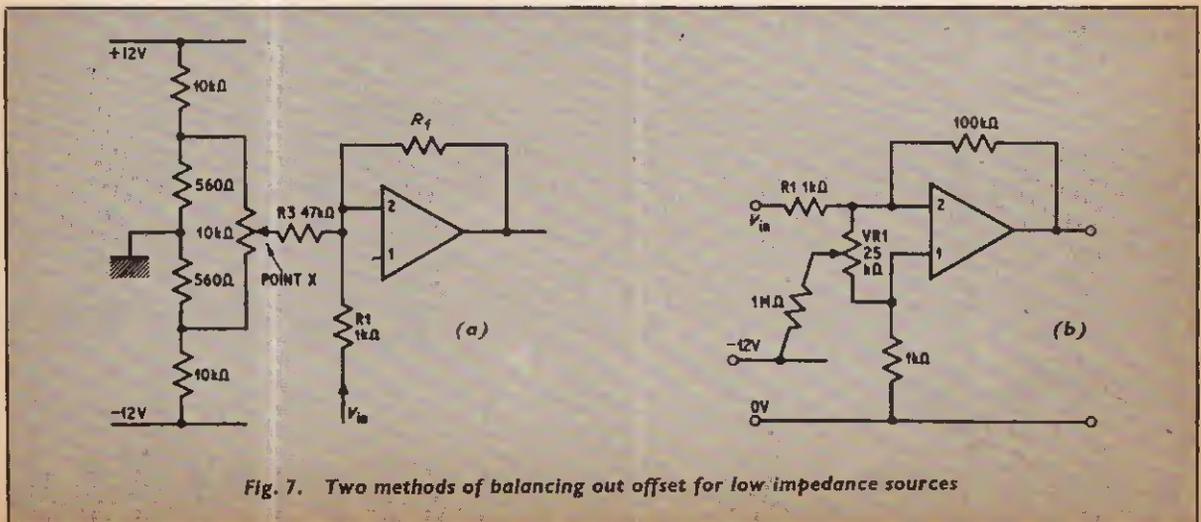

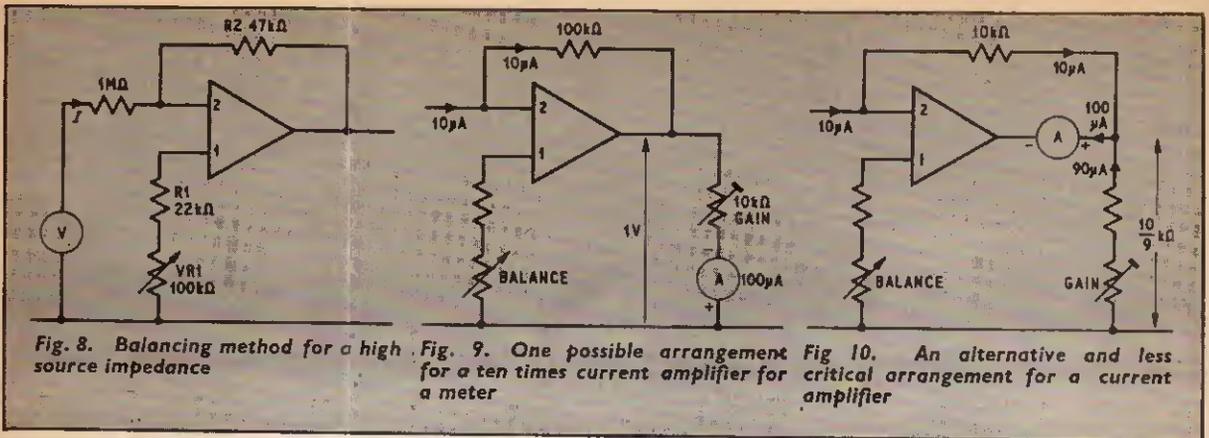


Fig. 8. Balancing method for a high source impedance

Fig. 9. One possible arrangement for a ten times current amplifier for a meter

Fig. 10. An alternative and less critical arrangement for a current amplifier

### THE CURRENT AMPLIFIER

We would use a circuit like Fig. 8 to give us the gain we require, and a suitable circuit for a  $100\mu\text{A}$  meter and times ten gain is given in Fig. 9.

An alternative approach is Fig. 10, and this was adopted because it has the advantage that the meter resistance does not enter into the calculations for current gain, and once the circuit is set up we could replace the  $100\mu\text{A}$  meter by another meter of known sensitivity and still expect its sensitivity to be multiplied by ten times.

The complete finalised amplifier circuit is shown in Fig. 11. R7 is included in series with the meter to limit the maximum current, while R8 is shunted across the meter to complete the d.c. path for the amplifier if the meter is removed. R8 need not be added for a permanently wired in unit. C1 rolls off the amplifier response at a low frequency and prevents any possible difficulties due to h.f. instability.

### CONSTRUCTION

The form of construction given in this article follows the pattern set by the previous projects in this series. The integrated circuit IC1 and most of the discrete components are mounted on a piece of perforated s.r.b.p. This board is secured to the die-cast box, using extra nuts or spacers to provide clearance between the metal and live points on the circuit board. The

box should have already been drilled to accommodate the sockets, feed-through terminals and the potentiometer VR1. All essential details can be obtained from the diagram Fig. 12 and the accompanying photograph.

Individual constructors may wish to use a larger box so that the meter can be built-in with the electronics. The battery could also be accommodated within such a larger box, thus achieving a single, self-contained piece of test gear.

### SETTING UP

For this circuit using a  $100\mu\text{A}$  meter and a times 10 gain (to give 100 kilohms volt sensitivity) the input offset for the amplifier will be up to  $1.8\mu\text{A}$ . When this is multiplied by our gain of 10 times it becomes  $\pm 18\mu\text{A}$  as a maximum value, which is still small in comparison with our f.s.d. of  $100\mu\text{A}$ .

In our instrument we used a balance control of 10 kilohm and suitable series resistor to give a control range of  $\pm 6\mu\text{A}$ . While this was adequate, it is quite small, and it would be preferable to use a 25 kilohm potentiometer to give more range. The series resistor R4 can then be chosen so that the potentiometer gives a control centred about zero.

Since the 10V range is probably the most useful one, the instrument was set up by applying a known voltage

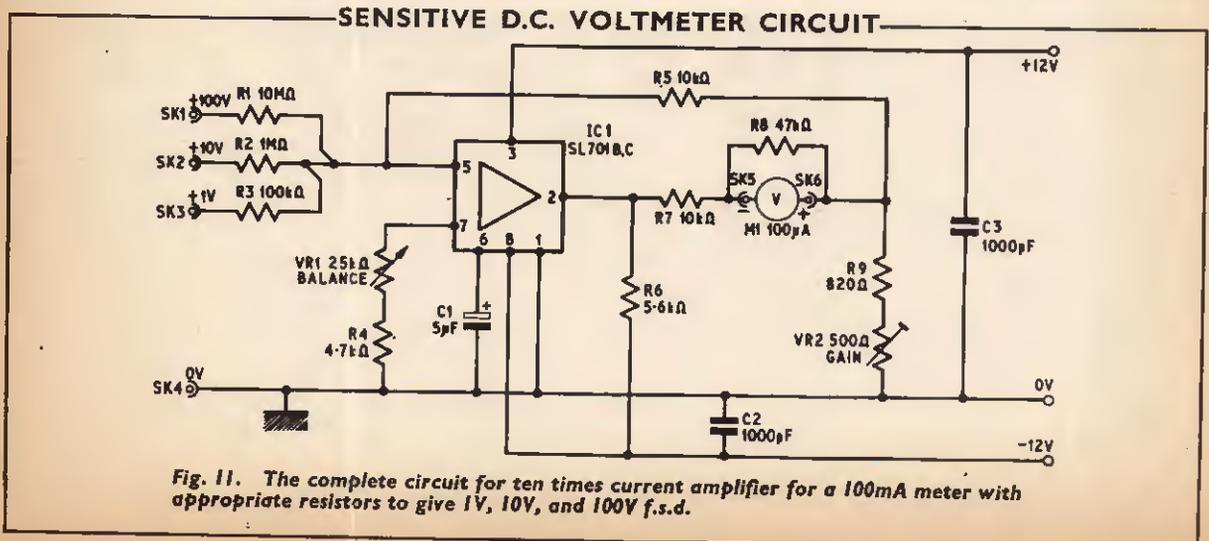


Fig. 11. The complete circuit for ten times current amplifier for a  $100\mu\text{A}$  meter with appropriate resistors to give 1V, 10V, and 100V f.s.d.

**Build yourself a quality  
transistor radio  
guaranteed results  
backed by our  
after sales service!**

## roamer seven mk iv

SEVEN WAVEBAND PORTABLE AND CAR RADIO WITH A SUPER SPECIFICATION GIVING OUTSTANDING PERFORMANCE!  
7 FULLY TUNABLE WAVEBANDS—  
MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND.



Extra M.W. band for easier tuning of Luxembourg, etc.  
Built-in ferrite rod aerial for Medium and Long Waves.  
5 Section 22in. chrome-plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push-pull output.  
7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker for rich-tone volume. Air spaced gauged tuning condenser. Separate on/off switch, volume control, wave change switches and tuning control. Attractive case with hand and shoulder straps. Size 9 x 7 x 4in. approx. First-grade components. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build with guaranteed results.

**Total building costs**  
**£5.19.6** P. & P. Personal Earpiece with switched socket for private listening 5/- extra.  
7/6

Parts price list and easy build plans 3/- (Free with parts).

## pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND (to 50 metres approx.) PORTABLE WITH SPEAKER AND EARPIECE

Attractive black and gold case. Size 8½ x 1½ x 3½in. Fully tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. All first grade components—7 stages—5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list, 2/8 (FREE with parts).



**Total building costs**  
**44/6** P. & P.  
3/6

## transona five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND (to 50 metres approx.) PORTABLE WITH 3" SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. Fully tunable. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. All first grade components. Easy build plans and parts price list 1/6 (FREE with parts).



**Total building costs**  
**47/6** P. & P.  
3/9

## super seven

THREE WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case size 7½ x 5½ x 1½in. with gill fittings. The ideal radio for home, car or outdoors. Covers Medium and Long Waves and Trawler Band. Special circuit incorporating 2 R.F. Stages, push pull output, ferrite rod aerial, 7 transistors and 2 diodes, 3in. speaker (will drive larger speaker) and all first grade components. Easy build plans and parts. Price list 2/- (FREE with parts). (Personal Earpiece with switched socket for private listening 5/- extra.)



**Total building costs**  
**69/6** P. & P.  
4/6

## roamer six

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case with gill fittings, size 7½ x 5½ x 1½in. World wide reception. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. All top grade components. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. (Carrying strap 1/6 extra.) Easy build plans and parts price list 2/- (FREE with parts). Personal Earpiece with switch socket for private listening 5/- extra.)



**Total building costs**  
**79/6** P. & P.  
4/6

## NEW LOOK melody six



8 stages—6 transistors and 2 diodes. Covers Medium and Long Waves. Top quality 3in. Loudspeaker for quality output and also with Personal Earpiece with switched socket for private listening. Two R.F. Stages for extra boost. High "Q". Ferrite Rod Aerial. Push-pull output. Handsome pocket size case with gill fittings. Size 6½ x 4 x 2in. Easy build plans and parts price list 2/- (FREE with parts).

**Total building costs**  
**69/6** P. & P.  
4/3

## RADIO EXCHANGE LTD

61 HIGH STREET, BEDFORD. Tel.: Bedford 52367

I enclose £..... please send items marked

ROAMER SEVEN  ROAMER SIX   
TRANSONA FIVE  SUPER SEVEN   
POCKET FIVE  MELODY SIX

Parts price list and plans for.....

Name.....

Address.....

- Callers side entrance Stylo Shoe Shop.
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12.30 Sat.

**MOTOR BARGAINS**

Ideal for model makers, record players, tape decks, etc.




**6.3 D.C. Motor.** 10,900 r.p.m. at 230mA. 1 1/2in. x 1in. diameter. Shaft 1/16in. long x 3/64in. dia. diameter. 9/8. P. & P. 2/6



**9v. D.C. Gram Deck replacement motor.** 2 1/2in. x 1 1/2in. diameter. Shaft 1/16in. long x 3/32in. dia. 17/8. P. & P. 2/-.


**TWO 30/- FOR P. & P. 2/6**

**ELECTRIC MOTOR**

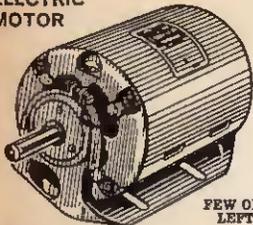

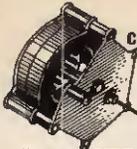
**FEW ONLY LEFT!**

Made by Crompton Parkinson. Single phase 1/4h.p. Motor 230/250V, 50 cycles. 1.3 amps. 1,425 r.p.m. Continuous rating. Spindle 1 1/4 x 1/16in. dia. Overall size less spindle approx. 8 x 6in. Perfect condition. A bargain for the work bench. 89/8. Carr. 12/6.



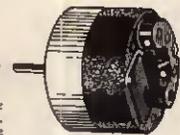**SYNCHRONOUS CLOCK TYPE MOTORS**

Gear for 40 revolutions per minute. 230V, 50 cycle, with mounting flange. Size approximately 1 1/2in. deep x 2 1/2in. diameter. **ONLY 22/6. P. & P. 2/6.**



**DELAY ACTION TIME SWITCH**

Made by Smiths. A.C. operation. 200/250V. Double pole. Will give time delays from 0-10 minutes. Size 2 1/2in. dia. x 2 1/2in. long (inc. 1/16in. x 3/16in. dia. spindle). **BARGAIN PRICE 17/8. P. & P. 2/6.**

**GARRARD DECKS**

3080 with Sonotone 9TARC Stereo Cartridge ..	29.19.8
3080 with Sonotone 9TARC Diamond Stereo Cartridge ..	210.19.6
AT60 MKII less cartridge ..	218.19.6
AT60 MKII with Decca Deram Stereo Cartridge ..	218.14.6
SP. 25 MKII less cartridge ..	211.19.6
SP. 25 MKII with Decca Deram Stereo Cartridge ..	216.14.0
AP.75 less cartridge ..	224.3.11
L.A.S.80 MKII less cartridge ..	224.19.0


All plus P. & P. 12/6

Mono Cartridge 17/6 extra. Stereo Cartridge 22/6 extra.

**LONDON'S LOWEST COMPONENT PRICES**



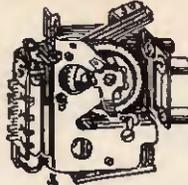**SEND 4d POSTAGE FOR OUR NEW FULLY COMPREHENSIVE 24 PAGE CATALOGUE OF VALVES, TRANSISTORS, DIODES, SEMI-CONDUCTORS, TRANSFORMERS, ETC. THOUSANDS OF ITEMS LISTED AND PRICED. SEND NOW AND SAVE MONEY WITH LIND-AIR COMPONENTS.**



**SELECTOR DRIVE**

Numerous applications. Electro magnet and brass tooth wheel. A switch wafer and contacts are coupled to this and arranged to be on for 10 pulses and off for 15. An Auxiliary contact is normally on but off 1 in every 25. Complete with suppressor, resistors, plus series contact for continuous operation. Ideal window displays, switching lamps, models, etc. 12V or 24V d.c. Brand new and boxed, 12/8. P. & P. 2/6.

**LIND-AIR OPTRONICS LTD**

*London's Leading Component Shops*


**25 & 53 TOTTENHAM COURT ROAD, LONDON, W.1. Tel. 01-580 1116/1117/4534/7679**

Open 9-6 p.m. Monday to Saturday Inclusive. Open Thursday until 7 p.m.

**ALL POST ORDERS TO Dept. PE 1168 25 Tottenham Court Road London, W.1**

**YOURS FREE FOR 7 DAYS**

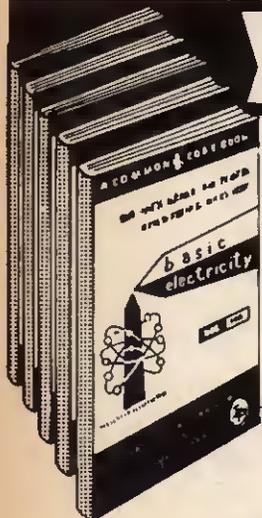**The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)**



You'll find it easy to learn with this outstandingly successful **NEW PICTORIAL METHOD**—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The latest research into simplified learning techniques. This has proved that the **PICTORIAL APPROACH** to learning is the quickest and soundest way of gaining mastery over these subjects. **TO TRY IT, IS TO PROVE IT**

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

**WHAT READERS SAY**

"May I take this opportunity to thank you for such enlightening works and may I add, in terms, easily understood by the novice." L. W. M., Birmingham.

"I find that the new pictorial method is so easy to understand and I will undoubtedly enjoy reading the following five volumes: thank you for a wonderful set of books." C. B., London.

"Please accept my admiration for producing a long felt want in the field of understanding Electronics." S. B. J., London.

"The easiest set of manuals it has been my pleasure to study." J. P. P., Taunton.

A TECH-PRESS PUBLICATION

**POST NOW FOR THIS OFFER!!**

To The SELRAY BOOK CO., 60 HAYES HILL, BROMLEY BR2 7HP

Please send me **WITHOUT OBLIGATION TO PURCHASE**, one of the above sets on **7 DAYS FREE TRIAL**, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. **BASIC ELECTRICITY 72/-**. Cash Price or Down Payment of 15/- followed by 4 fortnightly payments of 15/- each. **BASIC ELECTRONICS 84/-**. Cash Price or Down Payment of 15/- followed by 5 fortnightly payments of 15/- each. This offer applies to **UNITED KINGDOM ONLY**. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

**BASIC ELECTRICITY**  **BASIC ELECTRONICS**

Prices include Postage and Packing.

Signature ..... (If under 21 signature required of parent or guardian)

NAME ..... BLOCK LETTERS

FULL POSTAL ADDRESS.....


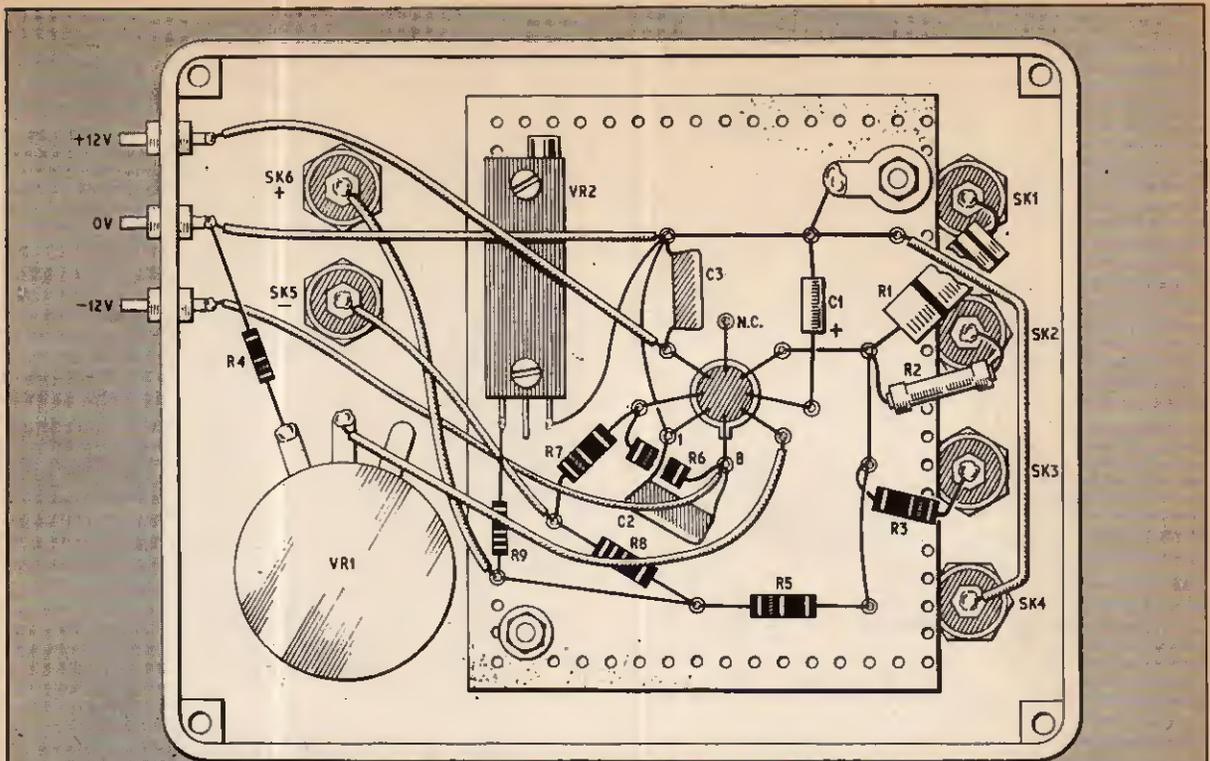
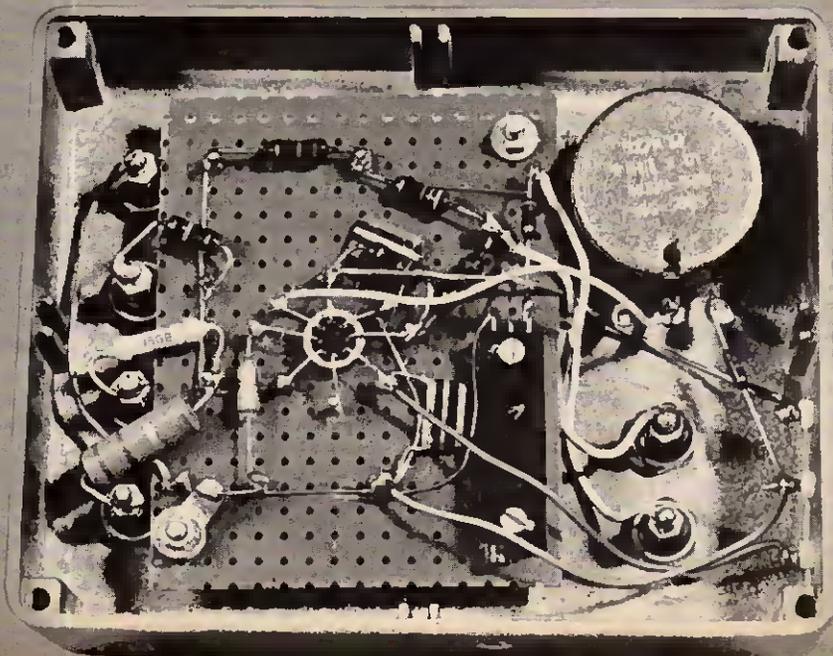


Fig. 12. Layout and wiring of the d.c. voltmeter amplifier

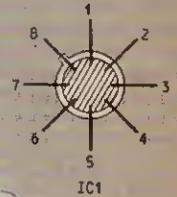

## COMPONENTS . . .

### Resistors

R1	10M $\Omega$	5%	H.S.
R2	1M $\Omega$	5%	H.S.
R3	100k $\Omega$	5%	H.S.
R4	4.7k $\Omega$	10%	carbon
R5	10k $\Omega$	5%	H.S.
R6	5.6k $\Omega$	10%	carbon
R7	10k $\Omega$	10%	carbon
R8	47k $\Omega$	10%	H.S.
R9	820 $\Omega$	10%	H.S.

### Potentiometers

VR1	25k $\Omega$ carbon
VR2	500 $\Omega$ preset (Radiospares)

### Capacitors

C1	5 $\mu$ F elect. 12V
C2	1,000pF ceramic
C3	1,000pF ceramic

### Miscellaneous

IC1	Linear integrated circuit (d.c. coupled amplifier —SL701C). (Available direct from the makers: The Plessey Co. Ltd., Components Group, Cheney Manor, Swindon, Wiltshire. Price: 18s)
M1	Moving coil meter, 100 $\mu$ A f.s.d.
SKI-6	4mm sockets, and matching plugs (Radiospares) 6 off
Die-cast box	4 $\frac{1}{2}$ in $\times$ 3 $\frac{1}{2}$ in $\times$ 1in (Electroniques 46R.043A, but see text)
Perforated s.r.b.p.	3in $\times$ 2 $\frac{1}{2}$ in
Three insulated feed-through terminals	
Control knob	
6B.A. screws and nuts	

on this range and adjusting VR2 until the meter read correctly. On the 10V or 100V ranges the instrument can be zeroed with the input open or short circuited since the input resistance (1 megohm or 10 megohm) is high enough in comparison with the 10 kilohm feedback resistance to not affect balance conditions. On the 1V range this is not quite so, and there is a shift of 2 per cent of f.s.d. between open and short circuit conditions. For the most accurate results this range should be zeroed with the leads short circuited.

Once the zero is set, drift is negligible, and only very occasional adjustment is required.

### SOME POSSIBLE MODIFICATIONS

#### (a) Range Extensions

Although the amplifier is intended as an addition to increase the sensitivity of a single or multirange meter, it could be constructed as a complete d.c. voltmeter (see also under "Construction"), and a meter scaled 0-1 and 0-3 could be employed with advantage to give ranges of 1, 3, 10, 30, 100V f.s.d. (making the 300 kilohm resistor up out of 120 kilohm and 180 kilohm in series, and making the 3 megohm resistor up out of 1.2 megohm and 1.8 megohm in series).

#### (b) 1mA Meter Increased to 100 $\mu$ A f.s.d.

The meter series resistor should be decreased to 1 kilohm and the input resistors chosen at 10 kilohms/volt.

#### (c) 1mA Meter Increased to 10 $\mu$ A f.s.d.

Again the series resistor should be decreased to 1 kilohm, the input resistors need to be chosen at 100 kilohms/volt. To obtain this current gain of 100 times VR2 has to be reduced to 100 ohms and R9 reduced to about 47 ohms. The maximum offset is 180 $\mu$ A which is  $\frac{1}{2}$  f.s.d. and the existing balance control values should still be suitable.

#### (d) 100 $\mu$ A Meter Increased to 1 $\mu$ A f.s.d.

The meter series resistor should be left at 10 kilohm, while the input resistors have to be chosen at 1 megohm/volt. VR2 has to be reduced to 100 ohms with R9 at 47 ohms. The maximum offset is now 180 $\mu$ A, which is well over f.s.d., and there will be some difficulty in zero setting. One solution would be to retain the 25 kilohm potentiometer and series resistor but add an extra 1 kilohm potentiometer in series as well, the former becomes the coarse zero with the latter the fine zero. A more elegant solution would be to use a helical potentiometer of 10 kilohms with a suitable series resistor chosen to give a balance about zero.

Once set, the balance is reasonably stable with temperature, and would only need to be adjusted every (say) ten minutes, the difficulty is that a single turn potentiometer does not have sufficient resolution, rather than that the circuit drifts with temperature!

**Next month: A fixed frequency sine wave test oscillator, based on the same type IC.**

**LASTS THE WHOLE YEAR THROUGH!**

**1969** JANUARY FEBRUARY MARCH APRIL MAY JUNE JULY AUGUST SEPTEMBER OCTOBER NOVEMBER DECEMBER

## Practical Gift for a practical man!

A full-year series of PRACTICAL ELECTRONICS issues delivered by post each month would be an ideal Christmas present. Why not give a subscription to a friend? He would certainly find the magazine just as interesting as you do and each issue would remind him of your good wishes.

But don't think too long—Christmas is very close. Act now and send your friend's name and address, together with your own and a remittance to cover each subscription to: Subscription Manager, Practical Electronics (Z), Tower House, Southampton Street, London, W.C.2. We will despatch first copies to arrive in time for Christmas, and send an attractive Christmas greetings card in your name to announce each gift.

RATES (including postage) for one year (12 issues), United Kingdom and Overseas, £2 2s 0d.

To avoid disappointment, make sure of your own copy by placing a regular order NOW with your newsagent.

# Hi Fi

# TRANSISTOR MICROPHONE

By H.E. OWENS



A Hi Fi Microphone that can be used with 100ft of cable without electrostatic or magnetic interference

CRYSTAL microphones are generally viewed with scorn in the hi-fi fraternity, an image well deserved by the majority. For while some of the more carefully designed examples are capable of natural, wide range reproduction and, price for price, can be superior to dynamic types, there remains one serious disadvantage: the capacitive nature of the crystal element limits the length of the output lead to a maximum of about 10ft. More than this will progressively attenuate the signal.

Also, a very high input impedance is required of the associated amplifier to achieve full bass response, and because of this the circuit becomes sensitive to electrostatic hum pick-up and cable-handling noises. To add to our difficulties, the better the acoustic quality of the microphone, the lower will be its output!

## F.E.T. PRE-AMPLIFIER

This article describes the construction of a low-noise f.e.t. pre-amplifier designed to do justice to the wide response of a specified crystal microphone insert, and physically small enough to be mounted as an integral unit with the insert and battery in a convenient metal tube.

Used in this way, it completely overcomes hum pick-up and permits the use of a long output cable, but it can alternatively be housed in a larger case and equipped with an input socket for use as a general purpose audio booster having a voltage gain of at least 25 (28dB), suitable for feeding valve or transistor equipment. It will handle inputs of up to 50mV and the frequency response is flat from 10Hz to 100kHz.

## CIRCUIT DESCRIPTION

The circuit (Fig. 1) consists of a common-source f.e.t. stage, TR1, having an input impedance of around 5 megohms (recommended value for the insert used), direct coupled to an emitter follower, TR2. This has a voltage "gain" of slightly less than unity but, because of 100 per cent negative feedback, reduces the signal impedance to less than 2 kilohms.

The input series resistor R1, in conjunction with the gate-to-source capacitance of the f.e.t., forms an r.f.

stopper. This was found to be necessary when using the prototype next door to a radio taxi base station, when broadcasts persisted in breaking through despite the excellent linearity of the f.e.t. and the screening properties of the tube.

With this potential source of trouble overcome, the microphone is immune to all forms of interference—both electrostatic and magnetic. To prove the point, the prototype has been tested alongside a high-power radio transmitter, sitting on top of a transformer carrying 500W, and feeding a tape recorder through 100ft of unshielded flex.

## BATTERY SUPPLY

Current drain is less than 0.5mA and the circuit will operate consistently to a supply end-point of 15V, thus obtaining good service life from the 22½V battery. Resistor R5 provides a charging path for C2.

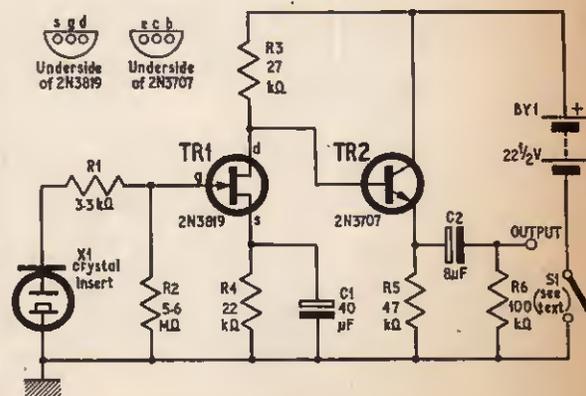


Fig. 1. Circuit diagram of the transistor-amplified microphone. The source, gate and drain of the f.e.t. (TR1) correspond functionally to the emitter, base and collector, respectively, of conventional bipolar transistors

# COMPONENTS . . .

## Resistors

R1 3-3k $\Omega$	R4 22k $\Omega$
R2 5-6M $\Omega$	*R5 47k $\Omega$
*R3 27k $\Omega$	R6 100k $\Omega$
All 10%, $\frac{1}{4}$ W carbon. *R3 and R5 should be low noise types	

## Capacitors

C1 40 $\mu$ F 6V elect.
C2 8 $\mu$ F 12V elect.

## Transistors

2N3819 n-channel field effect transistor	} Texas Instruments.
2N3707 npn silicon	

## Insert

X1 Acos 39/1 crystal (Henry's Radio)

## Miscellaneous

Tube: brass, copper or brass-clad steel,  $\frac{7}{8}$ in bore  $\times$  approx.  $4\frac{1}{2}$ in long. Steel strip, approx. 8in long  $\times$   $\frac{1}{4}$ in wide. Cartridge-type connector. Polyshrink tube No. 50 if required (black or white, sold in multiples of 1ft), Home Radio. Piece of Veroboard,  $1\frac{1}{2}$ in  $\times$   $\frac{3}{4}$ in. 4B.A. solder tag. Thin p.v.c. flex.

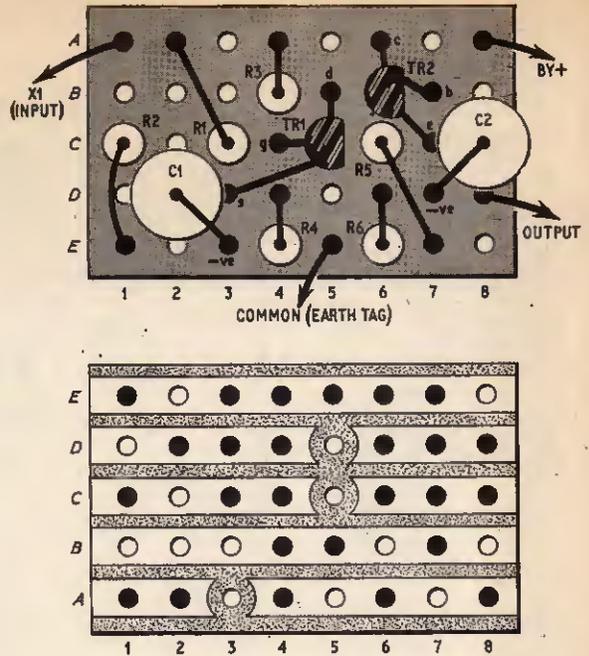


Fig. 2. Component layout and underside of the board with connection details to other components.

From the stability point of view, no capacitor is required across BY1. But as a safeguard against the occasional battery that causes frying noises as it nears the end of its life, a 10 $\mu$ F 25V electrolytic could be connected between holes A7 and E8 on the circuit board (see Fig. 2), with the positive end taken to A7. This measure was found to be necessary with only one of the large number of batteries that died prematurely while voltage and current adjustments were being made to the prototype, and was therefore omitted.

## AMPLIFIER CONSTRUCTION

The amplifier occupies exactly half the length of the Veroboard presented with last month's issue of PRACTICAL ELECTRONICS—so there's sufficient material for a (spaced) stereo pair of microphones if desired!

Cut off a portion measuring five strips wide by eight holes long. After making the appropriate breaks in the copper (refer to Fig. 2), the components can be soldered in, starting with R1 and ending with the transistors.

To ensure the finished assembly will go into the tube, all component leads must be cut to the absolute minimum and solder blobs, rough ends, etc. should be filed away from the underside of the board.

It is important that the amplifier board be insulated from the S-shaped sub-frame, this prevents the copper strip on the underside of the board from being shorted out. This is best accomplished by cutting out a piece of cardboard, or any plastics material, the same size as the wiring board and glueing it between the underside of the wiring board and sub-assembly chassis.

If the amplifier is to be tested before making up the rest of the microphone, use an earthed tobacco tin or something similar to screen the input.



View of the completed transistor microphone prior to insertion in the metal tube. It is important to insulate the amplifier board from the metal sub-assembly.

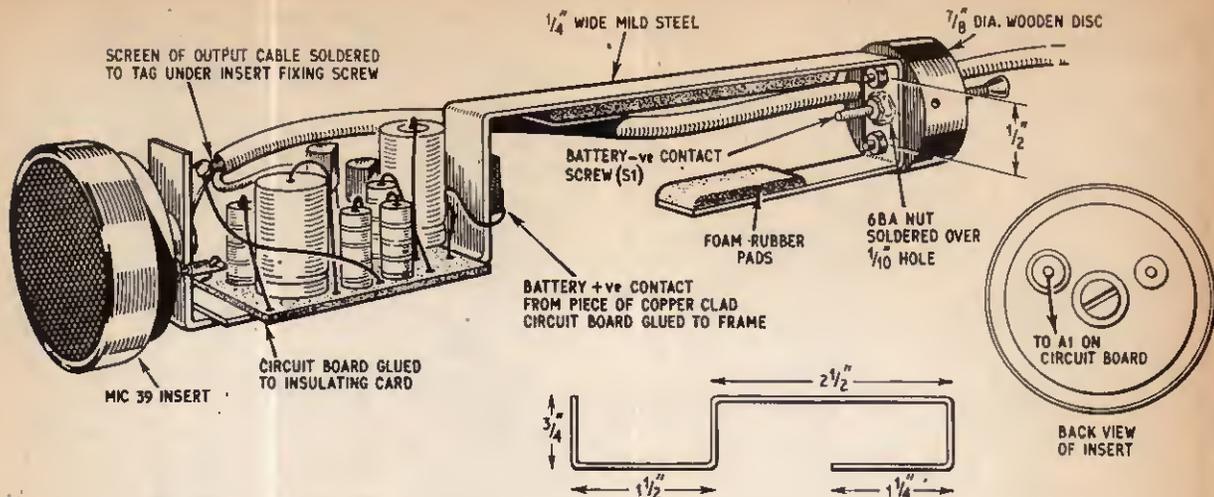


Fig. 3. Construction of the transistor microphone, with battery and metal cover removed

### MECHANICAL CONSTRUCTION

The drawings (Figs. 2 and 3) and photographs give most of the constructional information necessary. The amplifier and battery are mounted on an S-shaped sub-frame of mild steel, carrying the microphone insert at one end and a circular block of wood plus a made-up on/off "switch" at the other (Fig. 3). The case is a  $\frac{7}{8}$  in. i.d. thin-walled steel or copper tube (it must of course be metallic) secured by two screws into the wood block. The tube is grounded by contact with the rim of the insert.

The length of the sub-frame, and the quantity of strip needed to make it, is a little unpredictable because the radius of the bends will vary from one constructor to the next. Start with slightly more strip than necessary and cut off the excess after making the final bend. After drilling the appropriate holes and attaching the insert and wood disc, the assembly can be measured and the tubular case trimmed to size.

The wood disc in the prototype was cut with a hack-saw from a piece of whitewood  $\frac{3}{8}$  in thick and filed to shape, but constructors who take pride in their carpentry or who own a lathe will no doubt use their own methods.

### FITTING THE INSERT


When connecting the amplifier to the insert on no account make a direct soldered connection, because the heat will immediately dissolve the crystal. Use a gramophone cartridge type connector, or trap the lead under a piece of plastic sleeve pushed over the "live" post. Note that the "earth" pole is integral with the case and need not be used, as continuity is achieved via the central fixing screw and 4B.A. tag.

### FINAL FINISH

Various finishes are possible. The tube can be given a "satin" finish by twisting it in a wad of wire wool and protecting with a couple of coats of clear lacquer, or it can be painted.

For the sake of trying a new material, the prototype was sheathed in black "Polyshrink" (available from Home Radio), which is a soft plastics tubing that shrinks dramatically when heated. The correct size is No. 50, suitable for covering objects of 0.8 in to 1.25 in diameter. A particular advantage of the material is its ability to damp handling noises.

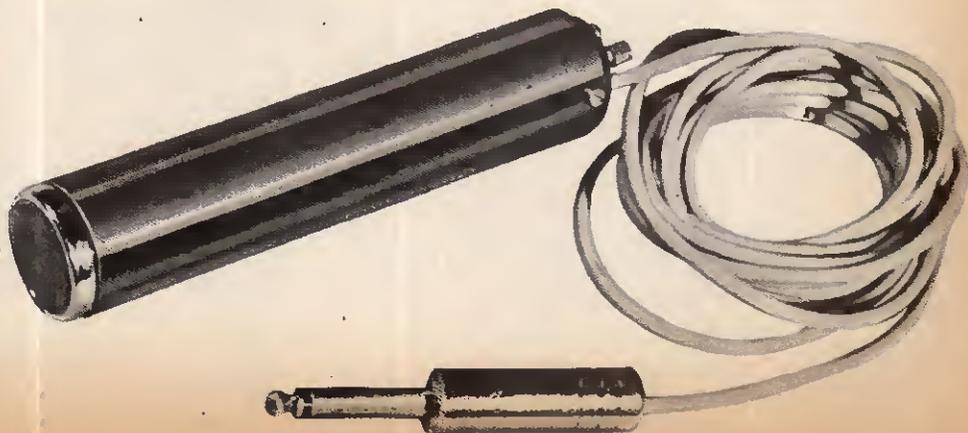View of the completed transistor microphone



## USING THE MICROPHONE

Before setting up the completed unit for trial one most important point must be noted. The amplifier will not function until the contact adhesive used to attach it to the sub-frame is completely dry. The prototype produced a terrifying rumbling noise caused by leakage through the damp glue from the supply line to the high impedance input, and had to be left overnight for the noise to subside.

The specified insert is "pressure operated" and therefore non-directional over most of the frequency range. At higher frequencies however, it has a greater sensitivity to sounds arriving directly on axis, which can be useful in balancing the "presence" of individual voices or instruments.

Average male speech at a distance of 12in from the microphone produces a peak level of about 70mV at the amplifier output, and at 3ft an upright piano (played forté) produces 400mV, so that normally the microphone will be used in the line, or radio, socket of a recorder or amplifier.

Fig. 4 shows a simple attenuator to prevent overloading the first stage of tape recorders having only a microphone socket. Without the attenuator, the output is sufficient to feed a simple passive mixer.

Although the output impedance of the microphone is effectively 2 kilohms so far as immunity to electrostatic hum pick-up on the line is concerned, it should not be operated into a load of much less than 5 kilohms. Doing so will cause distortion on peaks and bass loss through C2.


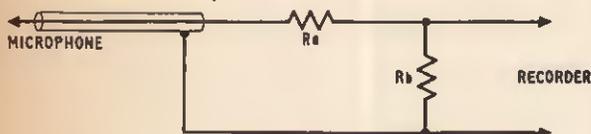


Fig. 4. An attenuator to prevent overloading of recorders that have only a low-level microphone socket. With  $R_b = 2.7k\Omega$ ,  $R_a$  should be around  $22k\Omega$  for valve recorders and  $220k\Omega$  for transistor models. Components should be at the recorder end of the microphone output cable, and can probably be mounted inside the plug
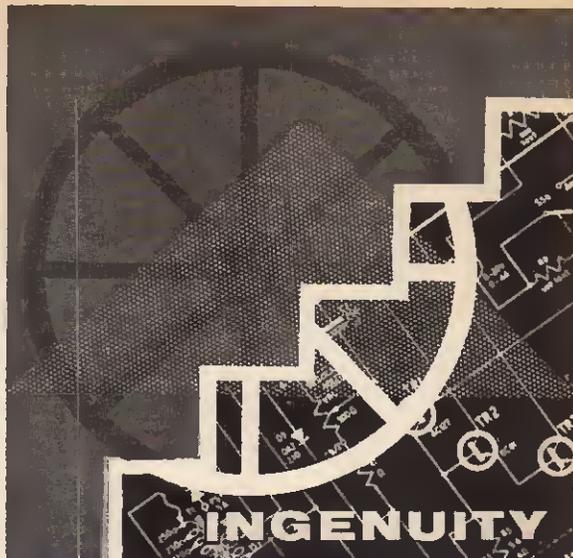
## PERFORMANCE DETAILS

Judged subjectively the microphone has a most satisfactory performance, with a noise level far lower than could be achieved with the same insert feeding a typical valve pre-amplifier. The maker's literature for the 39/1 insert quotes a frequency response flat from 40Hz to 15,000Hz, with a broad peak of 5dB at about 8.5kHz. Played through wide-range equipment, the peak is noticeable as a slightly metallic quality on orchestral instruments, but this is the only clue to the "economy" nature of the device.

The battery should last at least six months, used for an hour every day or for eight hours each weekend. Expressed another way, 3s worth of energy will allow recording of 120 7in reels of l.p. tape at 7½in/sec. The complete transistor microphone with battery and flex costs less than £2 10s.



# UNLIMITED!

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

This is YOUR page and any idea published will be awarded payment according to its merit.

## PHASE SPEAKER


**A**FTER reading the article in PRACTICAL ELECTRONICS on Musical Phase, September issue, I thought my method of making phased recordings may be of interest.

The signal to be phased is amplified in the normal way, but the output is fed into an extension speaker with the microphone of a tape recorder mounted as shown in the diagram below.

With the selected programme playing and the tape recorder on record the speaker and microphone are moved towards a sound reflecting surface and away from a sound reflecting surface.

When the speaker and microphone are one foot away from a wall the microphone picks up sound from the speaker only. But when the two are moved closer to the wall, sound reflected off the wall, which is out of phase, is also picked up.

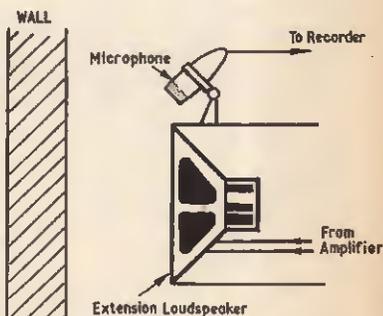The only problem with this system is that the recording level on the tape recorder has to be decreased as the gap between the wall and speaker/microphone diminishes.



- G. Stratton,  
Dawlish, Devon.

## DE LUXE PLAYERS

PORTABLE CABINET As Illustrated. To fit standard player or autochanger. **69/6**  
**ROB AMPLIFIER 3 WATT.** Ready made and tested with UCL82 triode pentode valve and loud- **59/6**  
**SUPERIOR AMPLIFIER.** Built and tested. Better sound!  
 Isolated AD Mains Transformer. 3 watt ECL82 triode pentode valve. Volume and tone controls with knobs. Quality Loudspeakers.  
**SINGLE PLAYERS MONO STEREO (9v. 45 rpm only)**  
 EMI Junior 22.19.6  
 Garrard SP225 22.19.6  
 Garrard SP25 21.19.6  
 Philips AG1018 21.0.19.6  
 Garrard 401 22.9.19.6  
 All fitted LF78 stylus and pickup crystal complete.



Post 5/6 each item

**AUTOCHANGERS MONO**  
 BSR Superlimb 22.19.6  
 Garrard 1000 22.19.6  
 BSR Transcription U470 21.0.19.6  
 Stereo/Mono 21.2.19.6  
 Garrard Stereo/Mono Model 3009 21.0.19.6  
 Garrard AT60 21.2.19.6


**GARRARD TEAKWOOD BASE W.B.L.** Ready cut out for mounting 1000, 2000, 3000, SP25, AT60. **65/-**  
**GARRARD PERSEF COVER SPEC. 1 FOR W.B.1 EACH**

**PICK UP ARM** Complete with AGOS LF-78 Turnover GP87 and Stylus 25/-; GP87 15/-; Stereo 35/-.

**CRYSTAL MIKE INSERTS**  
 1 1/2 x 2in. 8/6; AGOS 1 1/2 x 2in. 8/6. BMS. 1" dia. 9/6  
**MOVING COIL MIKE** with Remote Control Switch 12/6
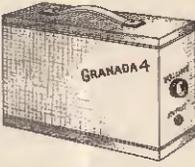
## PORTABLE TRANSISTOR AMPLIFIER

Many uses, Intercoms, Baby Alarms, Guitar Practice, Telephones or Record Player Amplifier. **ONE WATT OUTPUT** Wooden cabinet 1 1/2 x 3 x 4 1/2 in. Resins covered two tone grey. Four transistors, 7 x 4 in. speaker. Volume control. Jack socket. Uses PP3 battery.



OUR PRICE **79/6** Post 5/6. Worth double

**COLLARO BATTERY RECORD DECKS** 4 speed model 5v. operated. Complete with pick-up fitted crystal cartridge. Plays 7, 10, 12in. records. Elected auto stop and start. Ideal for use with above transistor amplifiers. **OUR PRICE 69/6** POST 3/6

**THE ABOVE GRANADA AMPLIFIER AND PLAYER DECK STOP FREE IF PURCHASED TOGETHER**

**WEYRAD P50—TRANSISTOR COILS**  
 RA2W 6 in. Ferrite Aerial Spare Cores ..... 6d  
 with car aerial coil 12/6  
 Diver Trans. LFDM4 ..... 9d  
 One P50/1AC ..... 5/4  
 Printed Circuit, PCAL ..... 9/6  
 L.F. P50/200 470 kcs ..... 5/7  
 J.B. Tuning Gasm ..... 10/6  
 3rd I.F. P50/300 ..... 3/-  
 Telescopic Chrome Aerials 6in. extends to 23in. 5/-

**VOLUME CONTROLS**  
 Long spindles, Midget Size 5 K. Ohms to 2 Meg. LOG or LIN. 1/8 3/-. D.P. 5/-  
 STEREO 1/8 10/6, D.P. 14/6  
 5K. S.P. Edge type, 5/-

**80ohm Coax 8d. yd.**

**SEMI-AIR SPACED** 40 yd. 20/-; 60 yd. 30/-  
**FRINGE LOW LOSS** Ideal 685 lines yd. **1/6**

**VEROBOARD 0.15 MATRIX**  
 2 1/2 x 5in. 3/6. 2 1/2 x 3 1/2in. 5/6. 3 1/2 x 3 1/2in. 2/6.  
**EDGE CONNECTORS** 16 way 5/-; 24 way 7/6.  
**PINS 30 per packet 3/4. FACE CUTTERS 7/6.**  
 S.R.P.F. Board 0.15 MATRIX 2 1/2in. wide 6d. per lin., 3 1/2in. wide 9d. per lin., 4in. wide 1/- per lin. (up to 12in.).  
**BLACK ALUMINIUM CHASSIS.** 18 s.w.g. 2 1/2in. sides. 7 x 4in., 5/6; 8 x 7in., 4/6; 11 x 3in., 6/6; 11 x 7in., 7/6; 13 x 9in., 9/6; 14 x 11in., 12/6; 15 x 14in., 15/-.  
**ALUMINIUM PANELS** 18 s.w.g. 12 x 12in. 6/6; 14 x 9in. 5/6; 12 x 8in., 4/6; 10 x 7in., 3/6; 8 x 6in., 2/6; 6 x 4in., 1/6.

## Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key  
 1in. 18/- 1in. 17/8 1 1/2in. 16/8 1 3/4in. 24/- 2 1/2in. 44/8  
 1in. 18/- 1in. 19/8 1 1/2in. 20/8 1 3/4in. 22/- 2 1/2in. 57/8  
 4in. 13/8 1 1/2in. 19/6 1 3/4in. 21/8 2in. 39/- 1in. sq. 38/6

**'SONOCOLOR' CINE RECORDING TAPE**  
 5" reel, 900' with LP strobe markings, also cine light deflector-mirror for synchronization. **14/- each.**

**Tape Spools 2/8. Tape Splicer 5/-. Leader Tape 4/8. Reuter Tape Heads for Collaro models 2 track 2 1/2" pair. UNIVERSAL TAPE CASSETTES Type C80. OUR PRICE 14/-.**

## "THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER



200/250 v. A.C. Leaflet S.A.E. **35/-** Post 2/6

**RETURN OF POST DESPATCH** Minimum Post and Packing charge 2/6.

## BARGAIN STEREO PARCEL

E.A.N. STEREO PLAYER CABINET suitable for B.S.E. Player Decks with 4 + 4 STEREO AMPLIFIER and TWO INTO TUNER/RECORDERS BUILT **£13.19.6.**

**NEW TUBULAR ELECTROLYTICS**  
 2/850V ..... 2/3 100/25V ..... 2/ 3/800V ..... 9/6  
 4/450V ..... 2/3 250/25V ..... 2/6 16/800V ..... 12/6  
 8/450V ..... 2/3 800/25V ..... 4/- 16+16/800V ..... 7/6  
 16/450V ..... 3/- 3+8/450V ..... 3/6 32+32/800V ..... 3/6  
 32/450V ..... 3/9 9+16/450V ..... 3/6 50+50/800V ..... 7/-  
 25/25V ..... 1/9 16+16/450V ..... 4/8 68+100/800V ..... 11/6  
 50/50V ..... 2/- 22+22/800V ..... 4/6 500/800V ..... 2/6  
**SUB-MIN. ELECTROLYTICS** 2, 4, 8, 16, 25, 50, 100, 250mF 15V 2/-; 500, 1000mF 12V 3/6; 2000mF 25V 7/-  
**CERAMIC** 500V 1pF to 0.01mF, 9d. Discs 1/-.

**PAPER TUBULARS**  
 350V-0.1 9d. 0.5 2/6; 1mF 3/-; 5mF 150V 3/-  
 500V-0.001 to 0.05 9d.; 0.1 1/-; 0.25 1/6; 0.5 2/-  
 1.00V-0.001, 0.002, 0.0047, 0.01, 0.05, 1/8; 0.047, 0.1, 2/6  
**SILVER MICA** Close tolerance 1%, 5-500pF 1/-; 500-2,200pF 2/-  
 2,700-5,600pF 3/6; 6,800pF-0.01, 1mF 6/- each  
**TWIN GANG** "0-0" 200pF+170pF, 10/8; 305pF, miniatur 10/-; 500pF standard with trimmers, 9/8; 500pF smallest less trimmers, 7/6; 500pF full modern, standard 9/-; **mini 5-range 600pF 12/8.** Single 100pF 7/6; Twin 12/6  
**SHORE WAY** Single 100pF 25pF, 50pF, 75pF, 100pF, 100pF, 5/6 each. Can be ganged. Coupler 8d each.  
**TUNING** Solid dielectric, 100pF, 300pF, 500pF, 5/- each.  
**TRIMMERS** Compression 30, 50, 70pF, 1/-; 100pF, 150pF, 1/8; 250pF, 1/8; 300pF, 760pF, 1/8; 1000pF, 2/6.

**250V RECTIFIERS** Selenium 1 watt 100mA 5/-; BY100 10/-  
**CONTACT COOLED** 1 watt 60mA 7/6; 85mA 9/6.  
 Full wave Bridge 75mA 10/-; 150mA 19/6; TV rect. 10/-  
**RESISTORS** Preferred values, 10 ohms to 10 meg.  
 1/2 w. 1/2 w. 20% 3d.; 1 1/2 w. 3d.; 1 w. 10% 6d.  
**HIGH STABILITY** 1 w. 10% 10 ohms to 10 meg., 2/-  
 Ditto 5%. Preferred values 10 ohms to 22 meg., 9d.  
 5 watt 0.5 to 0.8 ohm 3 w. 2/-  
 10 watt 10 ohms to 0.8 ohm ohms 2/-  
 15 watt 10 ohms to 0.8 ohm ohms 2/-  
**10K, 15K, 20K, 25K, 30K, 10W, 3/-**  
**FULL WAVE BRIDGE CHARGER RECTIFIERS:**  
 6 or 12v. output. 1 1/2 amp. 9/6; 1 1/8; 4a. 17/6.  
**CHARGER TRANSFORMERS** P. & P. 5/- Input 200/250v. for 6 or 12v., 1 amp.; 17/8; 3 amps., 21/-; 4 amps., 30/-

**WIRE-WOUND 3-WATT** Values STANDARD SIZE POTS. 10 ohms to 20 K. **4/6** LONG SPINDLE **7/6**  
 Carbon 20 K to 2 meg. 50 OHMS to 100 K.  
**VALVE HOLDERS, MOULDED 9d.; CERAMIC 1/- EACH.**

**NEW MULLARD TRANSISTORS 6/- each**  
 OC71, OC72, OC81, OC44, OC46, OC171, OC170, AF117.  
**REFRANGO TRANSISTOR TRANSFORMERS.**  
 TT45, Push Pull Drive, 9 CT. 6/-; TT48 Output, OTS 1 1/2-  
 TT49, Interstage, 20:1, 6/-; TT52 Output 3 ohms, 4+5:1, 8/-

**TRANSISTOR MAINS POWER PACK, FAMOUS MAKE, FULLY SMOOTHED. FULL WAVE CIRCUIT 49/6**  
 9 Volt 500mA Size 5 x 3 1/2 x 2 1/2  
**TRANSFORMER ONLY, Size 2 1/2 x 1 1/2 x 1 1/2 in 9 volt 10/6**

## MAINS TRANSFORMERS

Post 5/- each

250-0-250 50 mA. 6.3 v. 2 amps. center tapped 19/8  
 250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 30/-  
 350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 3 a. or 5 v. 2 a. 35/-  
 300-0-300 120 mA. 6.3 v. 4 a. C.T. 6.3 v. 2 a. 45/-  
**MINIATURE 200 v. 20 mA. 6.3 v. 1 a. .... 12/6**  
**MIDGET 220 v. 45 mA., 6.3 v. 2 a. .... 17/8**  
**HEATER TRANS. 6.3 v. 1 a. 8/6; 6.3 v. 4 a. .... 12/6**  
 Ditto tapped sec. 1.4 v. 2, 3, 4, 5, 6.3 v. 1 1/2 amp. .... 12/6  
**GENERAL PURPOSE LOW VOLTAGE.** Outputs 2, 4, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 a. .... 30/-  
 1 amp. 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 45, 60, 35/-  
 3 amp. 0-12 v. and 0-18 v. .... 19/8  
**AUTO TRANSFORMERS** 0-115-300 v. Input/Output, 60w. 13/6; 150w. 30/-; 500w. 92/6; 1000w. 175/-

**COAXIAL PLUG 1/3. PANEL SOCKETS 1/3. LINE SOCKETS 2/-**  
**OUTLET BOXES. SURFACE OR FLUSH 4/6.**  
**BALANCED TWIN FEEDERS 1/4. yd. 80 or 300 ohms.**  
**CAR AERIAL PLUGS 1/6; SOCKETS 1/6; LINE SOCKETS 2/-**  
**JACK SOCKET 5/4. open-circuit 2/8. closed circuit 4/6;**  
 Chrome Lead Socket 7/6. DIN 3-pin 1/6; 5-pin 2/-; Lead 3/6  
 Phone Plug 1/-; Phone Socket 1/-; 3 ohm; 3 ohm 1/9  
**JACK PLUGS 5/4. Chrome 3/-; 2.5mm 1/9; 3.5mm 2/6; DIN 3-pin 3/6; 4-pin 5/-**


**WAVE-CHANGE SWITCHES WITH LOW SPINDLES.**  
 2 p. 2-way, or 2 p. 6-way, or 8 p. 4-way 4/8 each.  
 1 p. 12-way, or 4 p. 2-way, or 3 p. 3-way, 4/8 each.  
 Wavechange "MAKERS" 1 p. 12-way, 2 p. 8-way, 3 p. 4-way, 4 p. 2-way, 5 p. 2-way, 6 p. 2-way 17/-; 3 water 22/-

**TOGGLE SWITCHES, sp. 3/6; sp. dt. 3/6; dp. 3/6; dp. dt. 4/6**



1968 GRAM CHASSIS  
 Post 6/-  
 Three Wavebands: Five Valves: ECH81, EP89, Long. Med., Short, Gram. ECH81, EL84, E294, 12-month guarantee. A.C. 200-250V. Ferrite Aerial 5 watts 3 ohm. Chassis 13 1/2in. 7in. x 5in. dial size 13in. x 4in. Two pilot Lamps. Four Knobs. **£10.19**  
 Aligned calibrated. Chassis isolated from mains  
**DE LUXE STEREO GRAM CHASSIS V.H.F., MW, SW 19-50m. SW 60-180m. Magic eye, push buttons. £19.19**  
 6 valve plus recit. Size 15 x 7 1/2 x 6in. high.

## BAKER MAJOR £8

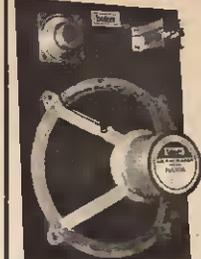

30-14,500 c.p.s., latest double cone, woofer and tweeter cone together with a special BAKER magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. Rated 90 watts. Voice coils available 3 or 8 or 15 ohms. Price £8, or Module Kit, SW17,000 c.p.s. with tweeter, crossover, baffle and instructions. £10.19.6

**LOUDSPEAKER CABINET WADING 18in wide, 26 1/2in high**  
**BAKER "GROUP SOUND" SPEAKERS—POST FREE**  
 'Group 25' 'Group 35' 'Group 50'  
 12 watt 6gns. 15 watt 8 1/2 gns. 15 watt 18gns.  
 26 watt 30 gns. 30 watt 60 gns.  
**ALL MODELS "BAKER SPEAKERS" IN STOCK**

**E.M.I. Cone Tweeter** 2 1/2in square, 8-20kcs, 10W 17/6.  
**Quality Horn Tweeter** 2-12kcs, 10W 29/6. **Crossover** 12/6.  
**LOUDSPEAKERS P.M. 3 OHMS.** 2 1/2in. 3in. 4in. 5in. 7 x 4in. 15/6 each; 8in 22/6; 6in 12/6; 10in 30/-; 12in. Double cone 8 or 15 ohm 35/-; 10 x 6in. 30/-; 8 x 6in. 21/-  
**E.M.I. Double Cone** 181 x 8in. 3 or 15 ohm models. 45/-  
**SPECIAL OFFER:** 8 ohm, 2 1/2; 8 ohm, 3 1/2in. 21/6; 15/6 EACH 25 ohm, 6 x 4in; 35 ohm, 3in; 15 ohm, 10 x 8 1/2in. 7 x 4in.  
**SPEAKER FRET** Tysan various colours. 5 1/2in. wide, from 10/- ft.; 26in. wide from 5/- ft. **SAMPLES S.A.K.**  
**EXPANDED METAL** Gold or Silver 12 x 12 in., 8/-

**ALL PURPOSE HEADPHONES**  
 H.E. HEADPHONES 2000 ohms General Purpose 19/8  
 H.E. HEADPHONES 2000 ohms Super Sensitive 35/-  
 LOW RESISTANCE HEADPHONES 3-5 ohms 38/-  
 DE LUXE PADDED STEREO PHONES 8 ohms 79/6

## MINETTE AMPLIFIER



For ALL Record Players.  
 A.C. Mains Transformer.  
 Chassis size 7 x 3 1/2 x 4in high. Valves ECL82, EZ80.  
 12 month guarantee. Quality output 5 ohm matching.  
 Bassinet offer complete with engraved control panel, valves, knobs, volume and tone controls, wired and tested. **Post 5/6 79/6**

## ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES

**BARGAIN AM TUNER, Medium Wave. 79/6**  
 Transistor Superhet. Ferrite aerial, etc.

**BARGAIN DE LUKE TAPE SPLICER, etc. 17/6**  
 Trims, joins for editing and repairs. With 3 blades.

**BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with 59/6**  
 separate controls into single output.

**BARGAIN TRANSISTOR FM-LW-MW TUNER: 10 semi conductors Calibrated tuning dial. 9 v. operation. FM289-108 Mc/s; MW 190-600 meters. LW 600-1419/6**  
 2000 metres. Size 2 1/2 x 8 x 5 1/2in.

**BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control 69/6**  
**40-PAGE EAGLE CATALOGUE 5/- Post Free**

★ RADIO BOOKS ★ (Postage 9d.)

Practical Transistor Receivers ..... 5/-  
 Practical Stereo Handbook ..... 3/6  
 Super-sensitive Transistor Pocket Radio ..... 2/8  
 High Fidelity Speaker Enclosures and Plans ..... 5/-  
 Radio Valve Guide, Books 1, 2, 3, or 4 ea. 5/- 50 ea. 5/-  
 Practical Radio Inside Out ..... 4/6  
 Shortwave Transistor Receivers ..... 4/8  
 Transistor Communication Sets ..... 7/6  
 Modern Transistor Circuits for Beginners ..... 5/-  
 Miniature Transistor Receivers ..... 5/-  
 Wireless World Radio Valve Data ..... 9/6  
 At a glance valve equivalents ..... 9/-  
 Valves, Transistors, Diodes equivalents manual ..... 10/8  
 How to receive Foreign T.V. programmes on your set by simple modifications ..... 5/-

**SANGAMO 3 inch SCALE METERS 45/-**  
 Various calibrations/movements, 500 M.C. range;  
 1 Milliamm; 0-50-50 Microamp, etc. S.A.E. for list.

**POCKET MOVING COIL MULTIMETER. 49/6**  
 0-1.000 A.C./D.C. ohms 0 to 100k, etc.  
**SUPERIOR MOVING COIL MULTIMETER 99/6**  
 0-2-500V. D.C. 20,000 ohms per volt. 0-1.000V. A.C. Ohms 0 to 5 meg. 50 Microamps (Full list Meters S.A.E.)

**BRAND NEW QUALITY EXTENSION LOUDSPEAKER**  
 Black plastic cabinet, 200w. lead and adaptor. For any radio, intercom, tape recorder, etc. 2 to 15 ohm. **PRICE 30/-**  
 Size: 7 1/2 x 5 1/2 x 8". Post 2/6

**CALLERS WELCOME**  
**337 WHITEHORSE ROAD, WEST CROYDON**

Written guarantee with every purchase. (Export: Send remittance and extra postage, no C.O.D.) Buses 133, 68 pass door, S.R. Stn. Selhurst. Tel. 01-884 1665

# EXCEL

in

# ELECTRONICS

## Through this ICS 3-way Training Method:

### MASTER THE THEORETICAL SIDE

**1** From basic principles to advanced applications, you'll learn the theory of electronic engineering, quickly and easily through ICS. That's because each course is set out in easy-to-understand terms.

### MASTER THE PRACTICAL SIDE

**2** ICS show you how to develop your practical abilities in electronic engineering—*alongside* your theoretical studies. It's the only sure way to success. All training manuals are packed with easy-to-follow illustrations.

### MASTER THE MATHEMATICAL SIDE

**3** To many this aspect is a bitter problem. Even more so because no electronic engineer is complete without a sound working knowledge of maths. But new ICS teaching makes mathematics easier to learn.

#### Wide range of courses available include:

Radio/TV Engineering and Servicing, Closed Circuit TV, Electronics, Electronic Maintenance, Servomechanisms, Computer Engineering, Numerical Control Electronics, etc.

#### EXPERT COACHING FOR:

INSTITUTION OF ELECTRONIC AND RADIO ENGINEERS  
CITY AND GUILDS TELECOMMUNICATION TECHNICIANS  
CITY AND GUILDS ELECTRONIC SERVICING  
R.T.E.B. RADIO/TV SERVICING CERTIFICATE  
RADIO AMATEURS' EXAMINATION  
P.M.G. CERTIFICATES IN RADIOTELEGRAPHY

Build your own radio, transistor portable, and professional-type test instruments with an ICS Practical Radio and Electronics Course. Everything simply explained and easy to handle. All components and tools supplied. For details post coupon below.

Member of the Association of British Correspondence Colleges

FOR **FREE** HANDBOOK POST THIS COUPON TODAY  
I.C.S., Dept. 151, INTERTEXT HOUSE,  
PARKGATE ROAD, LONDON, S.W.11

NAME .....

ADDRESS .....

OCCUPATION..... AGE..... 5/68

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

## S-DeC BREADBOARDING

- Fast, reliable, solderless circuit assembly
- Contacts last indefinitely
- Use ordinary components again and again
- Test *all* the circuits in the magazines

This breadboard is used professionally by development engineers throughout the world. Over 80% of current production is exported.

A booklet of projects is included with each kit giving construction details for a variety of circuits such as amplifiers, oscillators, VHF transmitter, radio, etc.

**S-DeC Kit:** One S-DeC with Control Panel, Jigs and Accessories for solderless connections to controls, etc., with booklet "S-DeC Projects" giving construction details for a variety of circuits. **29/6d** retail.

**4-DeC Kit:** Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "S-DeC Projects" all contained in a strong, attractive, plastic case. Ideal for the professional user. **£5.17.8** retail.

AVAILABLE FROM LEADING SUPPLIERS

or in case of difficulty from

**S.D.C. PRODUCTS (Electronics) LTD**

THE CORN EXCHANGE, CHELMSFORD, Essex

Telephone: Chelmsford (OCH 5) 56215

The most accurate  
pocket size  
**CALCULATOR**  
in the world

The 66 inch OTIS KING scales give you *extra* accuracy. Write today for free booklet, or send 82/6 for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.

**CARBIC LTD.** (Dept. PE19)  
54 Dundonald Road, London, S.W.19



## SILICON RADIATION DETECTOR

The NUTRONICS semiconductor radiation detector ND7 is a compact, low cost, versatile radiation detector with a window area of 7mm<sup>2</sup> and Alpha energy resolution of 50-100 Kev. FWHM, which has been expressly designed for use in educational establishments and by amateur experimenters.

The NUTRONICS semiconductor radiation detector ND7 detects Alphas, Beta, Gamma Radiation, Fission Fragments, X-rays and Protons.

Send for technical data sheet.

**SOLID STATE NUTRONICS LTD.**  
5A Voltaire Road, London, S.W.4

Tel.  
01-874 8608



## NEW HI FI CENTRE

A high quality mains powered integrated transistor stereo amplifier and pre-amplifier has just been introduced by **Audio Components and Services**, Sound Studios, Bell Hill, off Crown Hill, Croydon, Surrey.

A printed circuit board complete with heatsinks and control mounting together with a circuit diagram is available at 50s. Components as required, or the whole project in kit form, are available at £12.

There are six transistors in each channel and an output of 6½ volts into 8 or 15 ohm loads is achieved from 250mV input. Input impedance is 800 kilohm and will accept up to 4 volts without overloading. All measurements are r.m.s.

A selector switch provides for gram., radio and tape positions and there is a tape take-off socket. The tone control circuits are similar to that shown in the P.E. data booklet *Transistor Circuits* (see April issue).

It is claimed that the amplifier can be constructed in six hours using a d.c. voltmeter and the usual constructional tools.

Readers in the Croydon area may also be interested to learn that **Audio Components and Services** intend to develop the second floor as a large service department specialising in audio service and applications. Also, if there is sufficient interest, space and facilities could be made available for enthusiasts for increasing the scope of their hobby.

## NON-WALK FEET!

The term self-adhesive, high friction, and odourless is given by **West Hyde Developments Ltd.**, 30 High Street, Northwood, Middlesex, to their range of small feet for instrument cases. They are made in a non-plasticised, resilient, high hysteresis material, having a high friction coefficient—their description, not ours.

Suitable for instrument cases, domestic equipment, radios, drawer bumpers, etc., these feet are self-adhesive or screw fixing or both and will not mark or discolour the surface they are placed on. The feet measure ⅜in diameter by ⅜in high, with a recessed countersunk hole for a 6BA screw in the centre.

It is claimed that if the feet are fixed to a case which is temporarily placed on a sloping surface it will not slip or walk.

## EMERGENCY LIGHT

A portable lamp with bright all-round illumination has a multitude of uses around the home, is indispensable when camping and is a useful accessory for the "shack" in case of power failure.


The Tildawn hurricane lantern, powered by standard dry batteries, provides just such a light from a 5in high virtually unbreakable polypropylene dome. Very stable when standing on its wide base, it will also

# MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.



*Belling Lee miniature terminal*

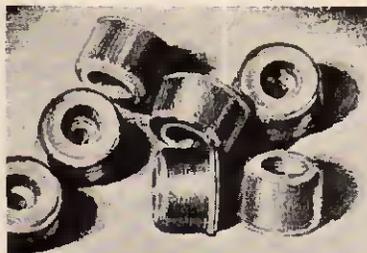

*Instrument case feet by West Hyde Developments*

*Hurricane lantern marketed by Harris Marketing*



hang by the handle, body inverted with the globe downwards, or horizontal with the base flat against a wall. Designed to withstand rough treatment, this robust lamp can be dropped or even thrown across the floor without apparent damage. Takes one or two AD28 or similar batteries, giving up to 50 hours illumination.

The Tildawn Lantern retails at 32s 6d plus batteries and is available from electrical stores. In case of difficulty contact the sole distributors, **Harris Marketing**, 16 Hillcroome Road, Sutton.

## MINIATURE COMPONENT

A series of miniature terminals, no thicker than a pencil, with a current rating of 10 amperes and a breakdown voltage greater than 4kV d.c., is announced by **Belling and Lee Ltd.**, Great Cambridge Road, Enfield, Middlesex.

Known as type L1726, these new terminals are only a quarter the size of standard terminals but have all the same features. These include a captive head available with a choice of six standard colours, a socket in the top for plugging in connections to extra equipment, and a cross-hole in the clamping gap which will accept wires up to 15 s.w.g.

The moulded panel bush is keyed to prevent rotation. The stem terminates in an integral solder pin for rear panel wiring.

## LITERATURE

A new Catalogue No. 137 describes the complete range of products manufactured by **Arcoelectric Switches Ltd.**

Divided into seven sections, covering transformer signal lamps, switches, neon indicators, and signal lampholders, etc., the catalogue lists numerous new styles and the section on car switches and indicators has been expanded.

Copies of the new 76 page catalogue can be obtained from **Arcoelectric Switches Ltd.**, Central Avenue, West Molesey, Surrey.


## NOTICES

**LST Components** inform us that due to an enormous response to their advertisement all stocks of Texas reject transistors were exhausted with the publication of the September issue.

Unfortunately, due to an error the advertisement in the October issue was not corrected and the same item was repeated.

The manufacturers of Timac automatic timer switches, **Kangol Ltd.**, have appointed **Electroniques**, Edinburgh Way, Harlow, Essex, as distributors of their timing controls.

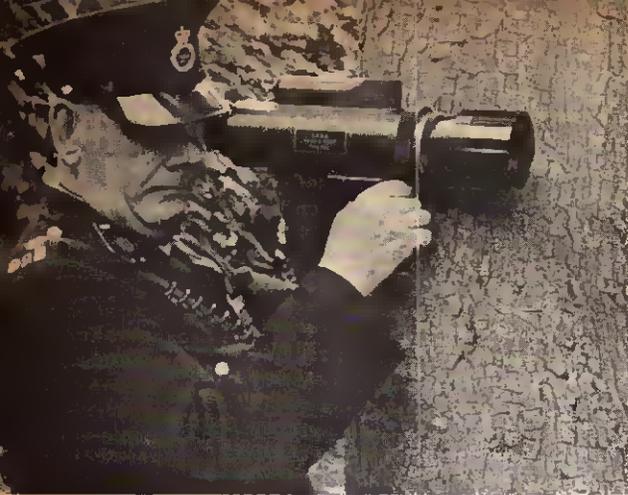Both the 3-pin plug-in types and the permanent wired-in versions are now stocked for immediate dispatch from **Electroniques**.



A police observer using a hand-portable passive sight infra-red viewer

# INFRA-RED COMMUNICATIONS

By M. A. COLWELL

INFRA-RED radiation occurs in similar form as visible radiation, but occurs in that part of the electromagnetic frequency spectrum below visible light (see Fig. 1). Therefore it has the properties of wavelength and frequency just as visible light has, but because its wavelength is longer, it is not visible to the naked eye.

However, light from tungsten filament lamps contains a very high proportion of infra-red (about 90 per cent) and is useful for experimental and industrial work whereby, with the use of filters, the visible light can be made invisible (Fig. 2).

When the wavelength of any kind of electromagnetic radiation becomes very short, i.e. for frequencies above about 3,000 megahertz, it is more convenient to refer to wavelength in microns, micrometers or Ångströms. The infra-red region lies in the 0.75 to  $10^3$  microns range, one micron being equal to one  $10^{-6}$  metre, although the division between infra-red and microwave frequencies is not clearly defined.

This region is further sub-divided into "near" (0.75 to 1.5 microns), "intermediate" (1.5 to 10 microns) and "far" (beyond 10 microns) regions, while above 300 microns it is often referred to as the "submillimetre" region.

## PROPERTIES OF INFRA-RED

Electromagnetic radiation in the infra-red region is sometimes able to penetrate objects which would otherwise stop visible light. Here it is important to

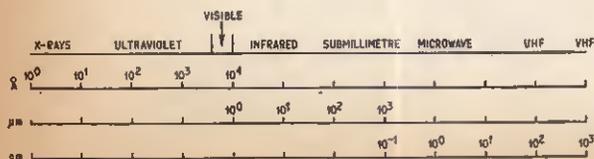


Fig. 1. Electromagnetic spectrum

think of it as radio waves which pass through physical obstructions, whereas visible light requires line of site communication.

This property is extremely useful, as we shall see later, in that an infra-red beam can be directed to a given point without being seen. High power lamps can be used here with a black opaque screen to cut off visible light rays. Clear glass will pass all visible light but will only pass near infra-red rays up to about 2.5 microns.

If transmission in the intermediate and far infra-red regions is required certain semiconductor materials can be used. Up to recent times germanium and silicon have been used, but now gallium arsenide is proving very valuable.

It is possible to detect infra-red by absorption and conversion of heat. However, this can be a cumbersome process, as was shown by early experiments where a blackened thermometer was used.

More lately, thermocouple detectors or photoconductive cells were made to respond over a wide frequency range, then perhaps filtered as required. This method is disadvantageous because the response to temperature changes in the transmitting object were too slow.

Current developments illustrated in this article show examples of detection of pure infra-red radiation from natural sources ("passive") and reflected radiation dependent on an infra-red beam being bounced off an object ("active").

## CARRIER WAVE

There is now a new line of thinking based on the active system whereby the transmitted infra-red can be used as the carrier wave for pulse code frequency

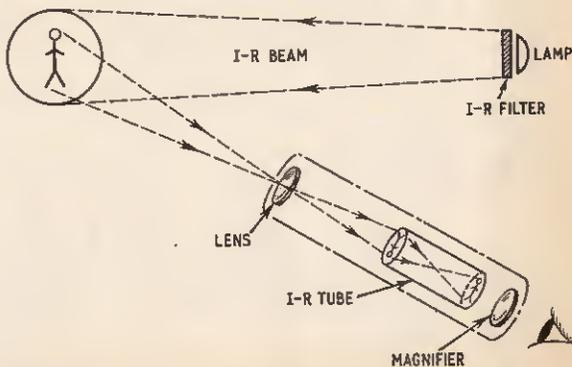


Fig. 2. An active infra-red system consisting of an infra-red source, which is a normal lamp with a filter to remove the visible part of the spectrum, and an optical viewing system incorporating an image converter tube

modulated audio signals. Propagation is by waveguide or line of sight, the waveguide being in the form of 2 micron diameter glass fibre.

This technique (known as "fibre optics") is becoming a commercially viable proposition, although certain difficulties still remain to be ironed out. Much work has been carried at the Ministry of Technology Signals Research and Development Establishment near Christchurch in close collaboration with industry to develop a system of communication in which telephone land lines transmitting at pure audio can be replaced by glass fibre.

### GLASS FIBRE OPTICS

The engineering aspect of producing suitable glass fibre is critical, chiefly in the elimination of impurities, particularly traces of iron, which gives ordinary glass the typical green appearance on its cut surface. Glass required for fibre optic communication must be "white" to avoid filtering and unnecessary attenuation, and must be of the correct dimensions.

In this, the single-mode or waveguide fibre, there are only a few possible modes of transmission and maximum bandwidth is obtained, typically 10,000MHz over 1km. This type of fibre is most suitable where very wide band, single channel systems are required, such as data or telephone trunk links.

If several fibres are contained in one "cable" no insulation is necessary between each provided the physical conditions of each fibre have been satisfied. This is because the refractive index of the glass ensures that the infra-red or light beam is kept within the bounds of each fibre. Consequently, common experiences such as stray capacitance and i.f. radiation and crosstalk are virtually non-existent in fibre optic communication. On the other hand, attenuation is at present still a problem which can be overcome by using line repeaters.

To minimise attenuation the beam must not be allowed to touch the walls. Early experiments involved the insertion of expensive servo-operated lenses at intervals along the length of fibre. More recently, it has been found that if the core is sheathed with a suitable glass cladding of lower refractive index the light will be adequately contained within the core.

Strange as it may seem, the glass fibre although only about as thick as human hair, has a high tensile strength

*An infra-red optical two-way telephone using YIG (yttrium iron garnet) modulator. Frequencies up to 100kHz and a range up to 2km is obtainable* (M.E.L. LTD.)



*The scene through a passive sight looking at an intruder under overcast, starlight conditions*

and is inherently flexible. If suitably protected from crushing and given a protective plastics coating, it can be inserted into cable ducts with the ease of conventional copper wire. So here we now have a 200-core cable with an overall diameter about the same as the conventional plastics covered single-core bell wire. Consequently more channels can be fed through underground ducts than with the present copper cable.

### LASER TRANSMISSION

Having looked at the link between two stations, what about the stations themselves; how does one get the signal into the fibre at one end and out at the other? The answer quite briefly is the laser and a silicon photodiode. The laser must emit a beam which can be injected into such a small diameter, must have high speed and efficiency and operate in the near infra-red region. Gallium arsenide electroluminescent sources are used in the laser which transmits at room temperature, a pulse code modulated signal. The laser beam is injected accurately near the source into the fibre end, which is sheathed in polished Perspex for laboratory convenience, and to reduce scattering on entry. The received signal is picked up by a silicon photodiode, decoded and amplified in the usual way.

By using glass fibre the laser beam is not dependent on straight line-of-sight transmission paths; indeed, there is no reason why the fibre should not be layed haphazardly or even in coil form, provided that bends and kinks are not unnecessarily severe.

### TUNING THE LIGHT BEAM

Optical communications systems rely on the usual signal generation as applied to any other form of radio communication. Harmonic generation, frequency mixing and frequency tuning take place at optical frequencies. Tuning is an interesting subject on its own and when applied to laser technology the results can be in the form of pure colour generation.

Experiments at S.R.D.E. have demonstrated the ability to "fire" a pre-tuned colour beam for a fraction of a second on a white screen. Development here is still at the purely experimental stage, but apart from being used in signal transmission, there is the possibility of applying the technique to coloured light displays.

A narrow band source of radiation can be tuned over most of the visible and near infra-red regions of the spectrum. The tunable source results from the selective addition of a laser frequency to a frequency

from a continuum of frequencies generated by the laser in a liquid placed immediately in front of a non-linear electro-optical crystal.

### NEODYMIUM-GLASS LASER

A high power Q-switched neodymium/glass laser (Fig. 3) is used to generate an intense continuum of frequencies in a 20cm cell of carbon disulphide. As soon as the laser beam enters the liquid, it causes a non-linear increase in the refractive index of the liquid. The laser beam is forced into propagating in a region of relatively high refractive index, and is reflected in on itself at the interface between these two regions.

After a further non-linear increase in the refractive index, the laser is self-trapped and rapidly collapses into a filament, the smallest so far identified having diameters of about 2 to 5 microns. The power density in the filament is very high—about  $10^9$  watts per square centimetre—leading to efficient stimulated scattering.

On leaving the carbon disulphide cell the intense continuum and unchanged laser radiation are directed



*A modified pair of binoculars used as an optical transceiver. The range is about half a mile, but the required power is minimal in comparison to conventional systems*

into a lithium niobate crystal where frequency addition takes place. Tuning of the sum frequency is achieved by altering the temperature of the lithium niobate. A tunable difference frequency has also been generated so that tunable narrow band frequencies can be generated in practically the whole 0.3 to 13.0 micron spectral range.

### ACTIVE LINE-OF-SIGHT

Other methods of active infra-red communication are generally based on line-of-sight transmission paths, although the modulation process is here applied to the transmitting crystal attached to a modified pair of binoculars. This method is limited in range to about half a mile, but the required power is minimal in comparison to conventional systems.

This makes the system particularly useful in environments where reflections from nearby structures would interfere with conventional systems. Examples would be in the building industry, ship's intercom and ship-to-ship radio telephone.

The added attraction is that the two stations, once lined up could be used for viewing as well as speech, forming a visual radio-optical telephone. The speech

modulated signal is transmitted by a gallium arsenide lamp through the right-hand lens of the binoculars to the left-hand lens of the receiving binoculars. Inside this the optical picture is passed through to the eye piece in the normal way; while the speech signal is picked up by a silicon photodiode after being deflected by a specially coated prism.


### INTERFERENCE FREE

The link uses a pulse frequency modulation system at 20kHz, eliminating the critical factors of heat haze causing signal fluctuations, hand shake or changes in daylight level. A voice operated switch is incorporated to change from receive to transmit; the system is interference free and is completely secure from eavesdroppers.

The gallium arsenide *pn* junction in the lamp is forward biased to emit infra-red light at 0.9 micron wavelength. The range of the instrument is dependent on visibility and increases to about half a mile at a visibility of about 10,000 metres, although it is expected that improvements will be made in due course.

The foregoing principles have now been released for commercial exploitation, having been developed originally for military purpose, and are born out of the concept of using separate infra-red light beams to flood a particular scene or object for viewing with infra-red sensitive viewers.

The current state of the art in infra-red detection is expected to be put to use in industrial or civil espionage control and crime detection.

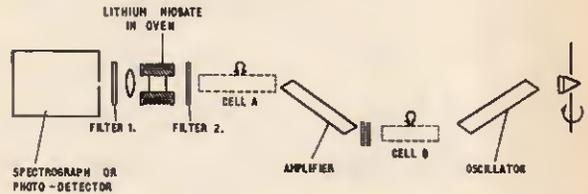

*Fig. 3. Block diagram of the neodymium glass tunable laser*

A typical example has been cited whereby the Thames river police are finding it increasingly difficult to make an arrest of dockside warehouse prowlers without arousing the attention of the prowler. The "telescopic" infra-red viewer can be used in pitch dark to watch the activities of an intruder. Of course, a lighted match or torch will apparently flood the infra-red scene immediately giving the security patrol an even better picture.

### PASSIVE LINE-OF-SIGHT

The passive system relies on the detection of objects by their emission of temperature variance with atmospheric temperature. The photograph of the potential intruder shows up clearly with the building. It is now possible to make devices which can discriminate a 1 degree difference between an object and its background. As a result such a device will detect the presence of an animal, a vehicle or human being.

A more advanced method is the thermal imager, incorporating several detectors and a scanning system. The signal is applied to a cathode ray tube to give a visual picture from heat contrasts rather than colour and brightness contrasts.

## IMAGE INTENSIFIER

Although not strictly relevant to infra-red, it is worth looking at recent development of image intensifiers because their applications are similar to those of passive infra-red detectors.

The image intensifier is a passive night vision device which can amplify light directly by 50,000 times. It is a small cylindrical encapsulation with three light intensifying modules each supplied by an e.h.t. of 15kV (Fig. 4).

Each module is a vacuum envelope with fibre optic input and output windows. A photocathode on the inner surface of the input window emits electrons according to the intensity of incidental light. These electrons are electrostatically focused and accelerated on to a phosphor screen on the output window to give a visible image.

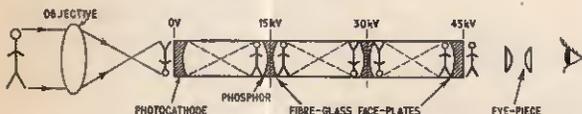


Fig. 4. A three-stage cascade intensifier tube.

A single module is not sensitive enough for poor light conditions; this is why three are usually banked together in a single envelope.

This intensifier needs no special lighting conditions, so true reproduction of natural light can be achieved, even in starlight conditions. The performance is dependent on atmospheric visibility, ambient brightness and contrast.

Applications lay in intensifying x-ray images, night navigation, and microscopy.

## FUTURE POSSIBILITIES

Infra-red detection has numerous applications in industry and public life. The Ministry of Technology has released details of the work described in this article and it is expected that the following lines will be followed up on the basis of infra-red experiments already, and still being, carried out.

Tremendous possibilities in the study of wild life and nature conservation seem apparent when one is told that Vampire bats have been successfully bred in this country for the first time under close observation by infra-red.

Automatic fire alarm systems become a much more simple and reliable proposition and can double up as intruder alarms at the same time.

Infra-red radio and television links can be coupled with trunk telephone lines in the laser powered fibre optic system.

Closed circuit broadcasting in a room equipped with a centrally placed gallium arsenide transmitter and infra-red detection equipment overcomes problems of multi-image reflection and absorption experienced from conventional radio devices; no wires are needed.

Telephone tapping is avoided by using the infra-red modulated binocular and fibre optic systems.

Development work is still going on at S.R.D.E. and co-operation from manufacturers including Barr and Stroud, English Electric, E.M.I., Elliott Bros., Hilger and Watts, Marconi Instruments, Mullard, Plessey and 20th Century Electronics, has brought to light some advances that could well place infra-red techniques in its rightly deserved place in civil communications.

Acknowledgement is made to the Ministry of Technology, S.R.D.E. Christchurch, for illustrations used in this article. ★

# NEXT MONTH!

## ELECTRONIC GAMES

### TO BUILD FOR

# CHRISTMAS

Keep the party going with these fascinating games. Can be constructed from full instructions in next month's issue.



## ELECTRONIC STOCKMARKET

Easy to build and absorbing to play, bringing four or more people all the thrills and hazards of stock and share investment. Monetary gains and losses are represented by charges stored in "Cash" and "Bank" capacitors, the taxman takes his toll, and the winner is the first to make a million.

## FLIP-FLOP

The new electronic version of "heads or tails"; can be made on the P.E. Printed Wiring Board. A pocket size novelty you can carry around to play at any time, wherever you are.

ALSO

## DOOR CHIME

Another Printed Wiring Board project, producing a pleasing vibrating tone when the doorbell button is pressed.

## PRACTICAL

# ELECTRONICS

DECEMBER ISSUE On Sale Nov. 15

MAKE SURE OF YOUR COPY

**T**HE article describes a variable-tempo rhythm generator which can be used to accompany a piano, organ or other musical instrument.

The percussive effects reproduced electronically are high and low bongoes, short and long brushes, and bass drum.

The rhythm selector switches provide instantaneous choice of any one of 12 popular dance rhythms each one being both variable in its tempo and instrumental colour to suit the needs of the music or moods of the instrumentalist.

### OPERATION

The principle of operation of the rhythm generator is most easily described by reference to the block schematic diagram shown in Fig. 1. The heart of the system is a twisted-ring counter driven by a variable frequency clock-pulse generator. The counter has eight outputs and is so arranged that positive-going pulses appear on the output leads in sequence and in time with the clock pulse generator. A start switch S1, ensures that, on switching on, the first pulse occurs on output 1, the next pulse on output 2 and so on up to pulse number 8. The ninth pulse appears on output 1 again and the whole sequence is repeated indefinitely.

The positive-going pulses are fed to two sets of eight differentiator circuits which allow short positive pulses to pass via the rhythm selector switch to the various

sound generating circuits. The two sets of differentiators, set 1 and set 2, are controlled by a bistable circuit (bistable 5) which changes state for every complete cycle of the ring counter. Thus the first eight pulses are derived from differentiators in set 1 whilst the second eight pulses are derived from set 2.

A sequence switch, S2, is connected to the bistable and may be used to over-ride the alternating set 1/set 2 sequence to give either set 1 sequence only or set 2 sequence. It will be seen later that this facility gives a possible total number of rhythms which is greater than the number of positions on the rhythm selector switch.

For certain rhythms involving 3/4 or 6/8 time the basic counter is required to have only 6 pulses for each complete cycle and this is accomplished, when required, by part of the rhythm selector switch, which modifies the counter interconnections.

The arrangement given is that used by the author but the system is easily modified to suit individual constructor's requirements.

### CLOCK GENERATOR AND RING COUNTER

The tempo of the selected rhythm is governed by the frequency of the clock-pulse generator shown in Fig. 2. The circuit is a conventional astable multivibrator and control of frequency is obtained by varying the voltage supplied to the base resistors by means of VR1. To

Cha Cha Cha!


Samba!

Foxtrot!

Quickstep!



# Rhythm

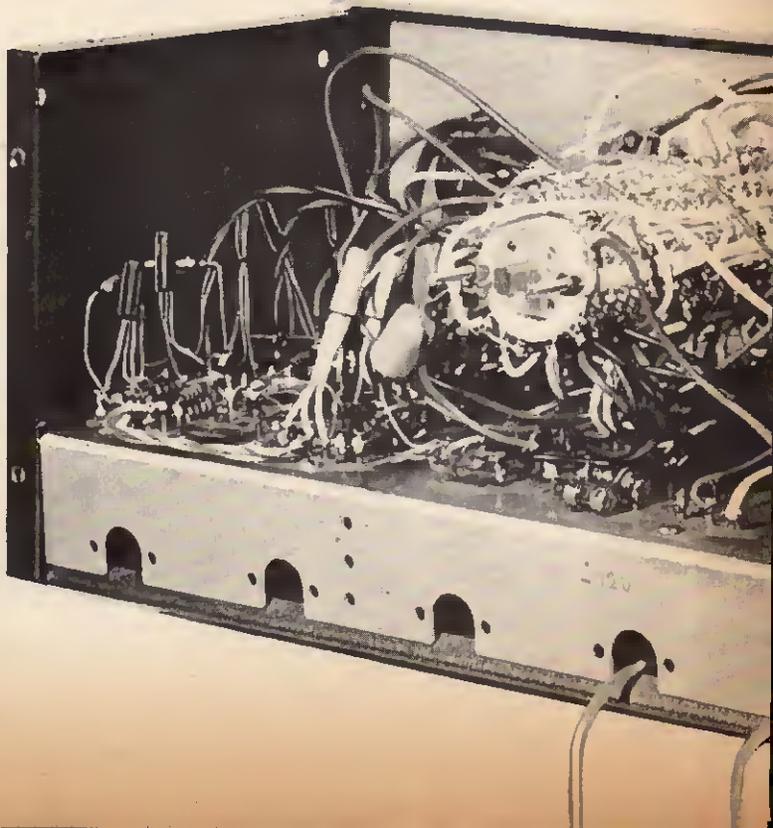


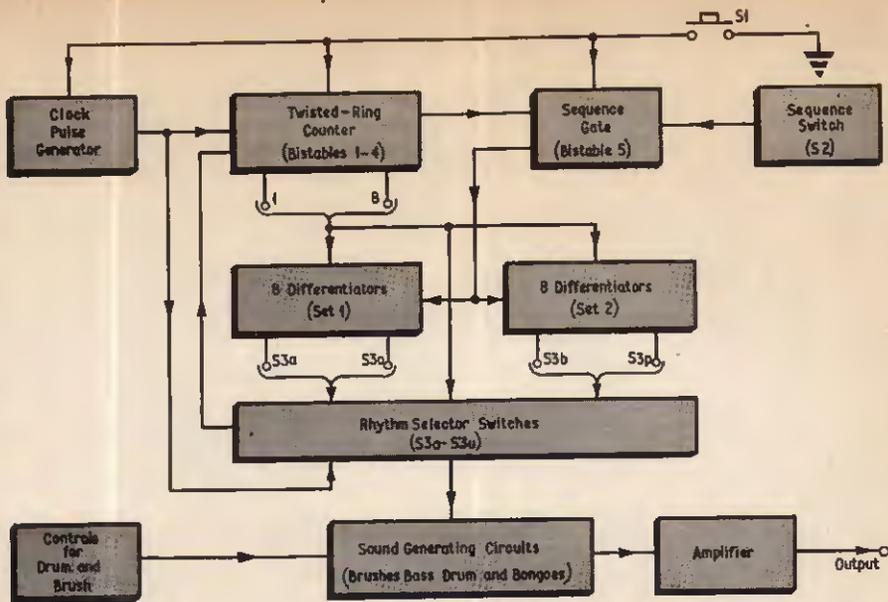


Fig. 1. Block diagram of rhythm generator

# Generator

By P. R. Allcock

Beguine!  
Tango!  
Waltz!

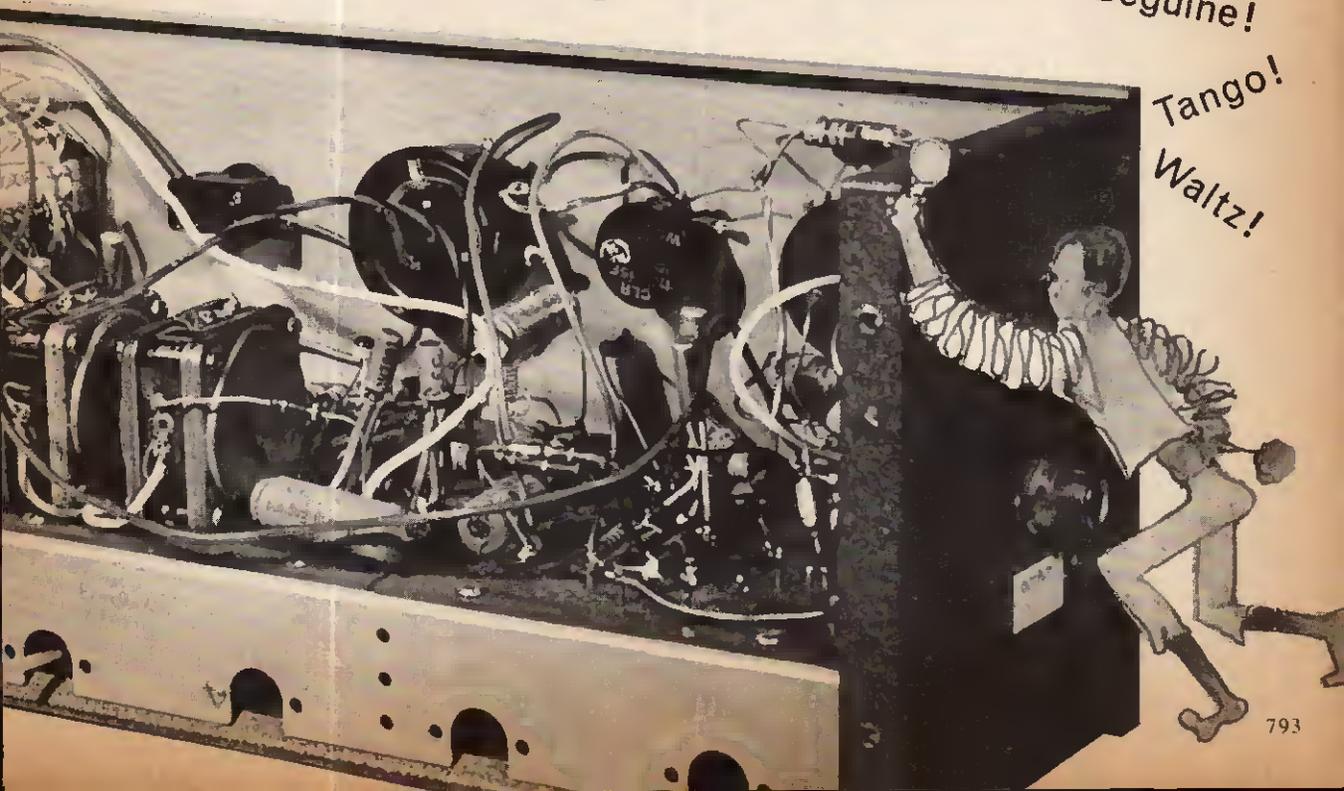

# BOARD A CIRCUIT

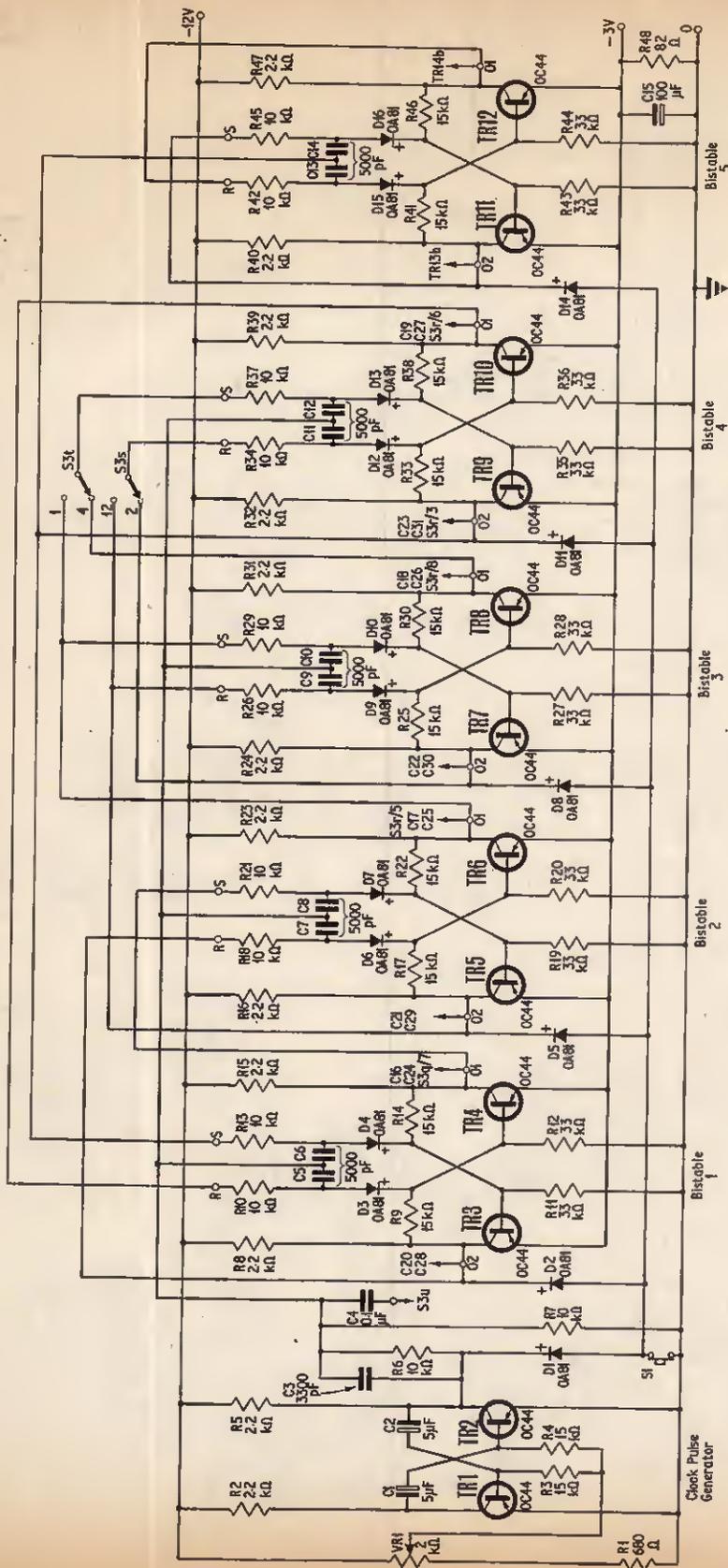


Fig. 2. Circuit diagram of clock pulse generator, twisted ring counter and sequence going bistable

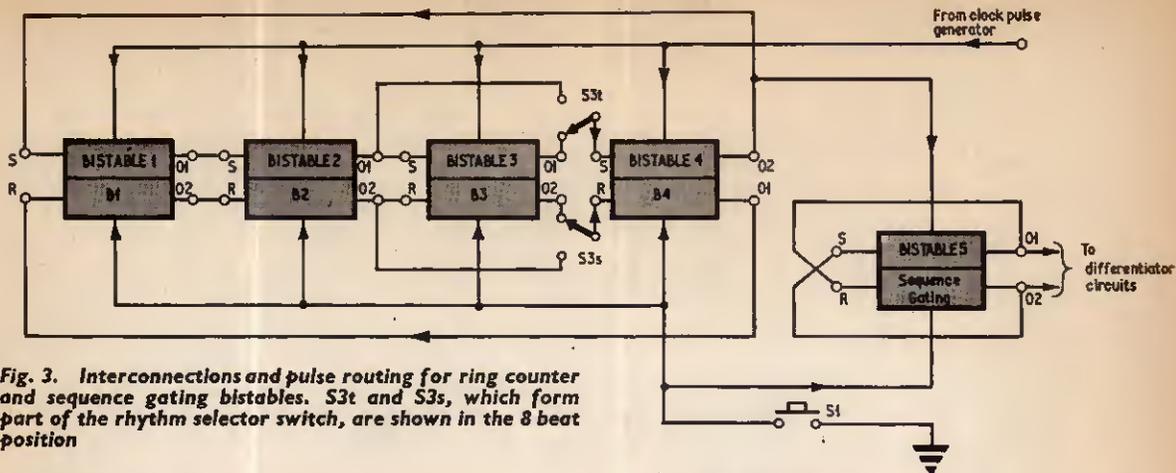


Fig. 3. Interconnections and pulse routing for ring counter and sequence gating bistables. S3t and S3s, which form part of the rhythm selector switch, are shown in the 8 beat position

simplify the design of the counter circuit the pulse amplitude was reduced by R6 and R7.

Coupling to the ring counter (bistables 1-4) is by way of capacitor C3 which ensures adequate rise time for the clock pulse generator's output when loaded by the cascaded bistables.

Since bistables 1 to 4 are identical in mode of operation the action of bistable 1 will only be considered before examining beat generation in the whole counter.

The circuit has two stable states TR3 on and TR4 off which is the reset state, and TR3 off and TR4 on which is the set state. Before operation of the start switch S1 the circuit is held in its reset condition by diode D2 which clamps the collector of TR3 to earth.

### START SWITCH

Operation of the start switch allows clock pulses to pass to the base of TR3 or TR4, the routing being dependent on the voltage existing at the points R and S. These two points are connected in the complete circuit to the collector output O1 and O2 of bistable 4. Reference to Fig. 3 clarifies these bistable interconnections.

Since at any instant one transistor of each bistable will be on and the other off the potentials fed to S and R will be different and it may be seen from the circuit that the two possible potentials are -12V and -3V approximately (corresponding to off and on conditions respectively).

### STEERING CIRCUITS

If we assume that the potential at S is -3V and that at R is -12V, the clock pulses arriving at C5 and C6 are differentiated by C6R13 and C5R10 but due to the potential difference between S and R only D4 allows pulses to pass. For D3 or D4 to conduct, the clock pulse amplitude must exceed the potential difference between S and TR3 base, or R and TR4 base, respectively. The first pulse steered via D4 to TR3 base turns TR3 off and TR4 on, that is the bistable is

set. Subsequent pulses have no effect as long as the voltages at S and R are maintained. In normal operation the voltages at S and R will eventually change over due to a change of state of the bistable to which they are connected and the next clock pulse arriving at C5 and C6 will be steered via D3 and reset the bistable to its original state.

The pattern of operation for the first four bistable circuits obviously depends on the instants at which the voltages on S and R are changed over for each bistable element and this in turn depends on the way the elements are interconnected. To cater for a wide variety of rhythms it is necessary to have counter operation corresponding to both 3/4 and 4/4 time at least. Certain rhythms may need other counting sequences and this is considered later.

### BASIC 8-BEAT COUNTER

The eight-beat counter can be used to generate a wide variety of rhythms involving 2, 4, 8 or 16 beats to the bar and the required form of interconnection is shown in Fig. 3. The sequence of operation for this arrangement, assuming that the start switch has just been opened, is as follows:

With all bistables initially reset.

- |                      |               |
|----------------------|---------------|
| Clock Pulse 1—Set B1 | 6—Reset B2    |
| 2—Set B2             | 7—Reset B3    |
| 3—Set B3             | 8—Reset B4    |
| 4—Set B4             | 9—Set 1, etc. |
| 5—Reset B1           |               |

The O1 collector outputs of the first four bistables generate positive-going pulses for the first four beats in the sequence and the O2 outputs generate similar pulses for the last four beats of the sequence. The 16 beat cycle is produced by diverting these eight pulses alternately via two sets of pulse differentiators.

For rhythms involving 3/4 or 6/8 time only three bistable circuits are required in the counter and this is easily arranged by switching S and R of bistable 4 to O1 and O2 of bistable 2 instead of bistable 3. This

TABLE I.

Pulse	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
Set 1	D	—	Sb	—	Sb	—	Sb	—	D	—	Sb	—	Sb	—	Sb	—
Set 2	D	—	—	—	Hb	—	Hb	—	D	—	—	—	Hb	—	Hb	—
Alternate	D	—	Sb	—	Sb	—	Sb	—	D	—	—	—	Hb	—	Hb	—

D=Drum

Sb=Short brush

Hb=High bongo

## BOARD B CIRCUIT

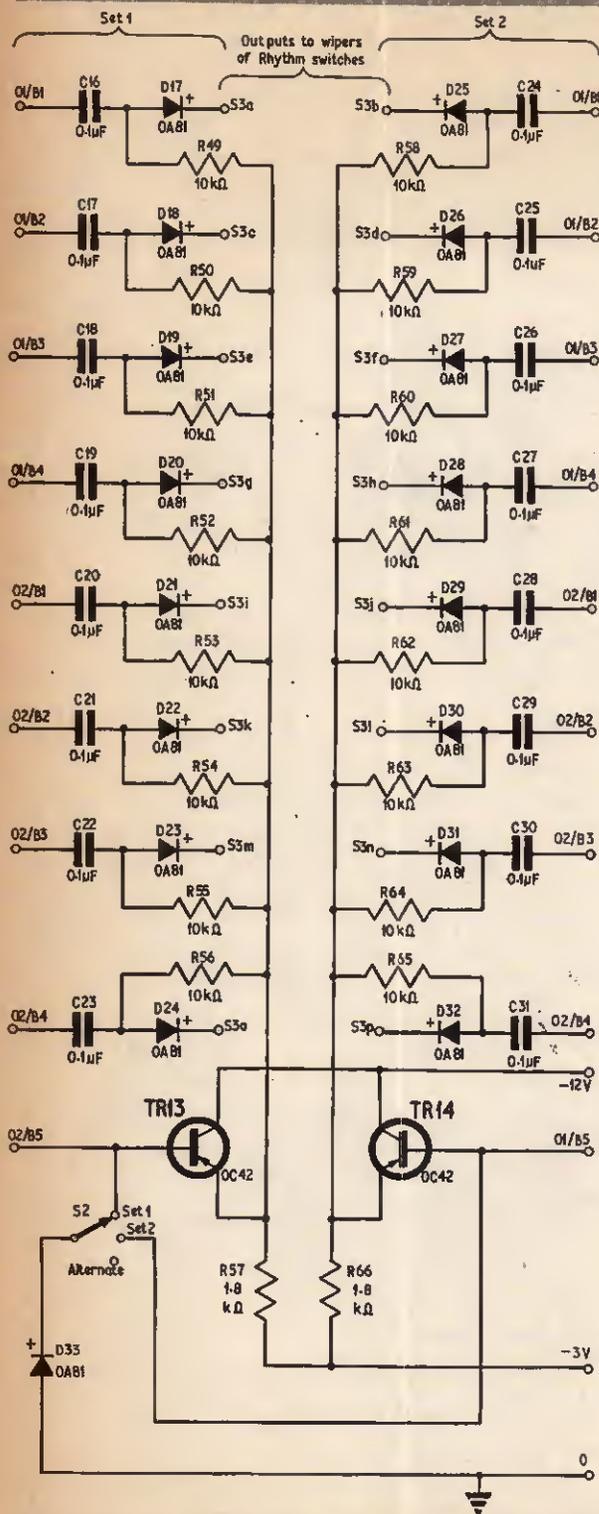


Fig. 4. The two sets of eight differentiators which shape and route the output pulses from the ring counter to the rhythm selector switch wafers S3a to S3p. Pulse sequences are governed by the switch position of S2

particular change of interconnections is accomplished by two wafers on the main rhythm selector switch. The resulting cycle now generates the first three beats at the O1 outputs of bistables 1, 2 and 4 and the last three beats at the O2 outputs of the same three bistables.


It should be noted that bistable 3 still operates simultaneously with bistable 4 due to its connection with bistable 2, but it does not affect the counting sequence and its outputs are not used when operating in this condition. The start switch is necessary to ensure that the counter does not run in an unwanted sequence involving the unused combinations of states of the four bistables and ensures that the first beat of each rhythm pattern appears at O1 on bistable 1. The counter output pulses are differentiated and only the positive-going spikes are used to operate the sound generating circuits.

### DIFFERENTIATORS

The circuit for differentiating the output pulses is shown in Fig. 4. It will be seen that there are two sets of differentiator networks each receiving eight (or six) consecutive pulses from the main counter. However, only one set is operative at any one time depending on the state of bistable 5. This bistable is fed from the O2 output of bistable 4 and thus changes state for every complete cycle of 8 (or 6) pulses, and by controlling the emitter followers TR13 and TR14 the differentiated pulses are gated in groups (in a similar manner to the bistable steering) via the first or second set of diodes when the sequence switch is in the "alternate" position. The other two positions of the sequence switch override bistable 5 and allow pulses to pass via the first or second set of diodes. The diode outputs are connected to the wipers of S3a to S3p wafers on the rhythm switch which routes the pulses to the various sound generating circuits. Thus for each position of the rhythm switch it is possible to generate two different rhythm patterns of six or eight beats each, or one pattern of 12 or 16 beats using alternate sets of pulses. Fig. 5 gives the sequential routing of pulses for 16 beats at the rhythm switch assembly.

A simple example will make the operation of this section easier to follow. Let us assume that the differentiator circuit's output pulses are routed by way of the rhythm selector switches to the sound producing circuits in the following sequence. S3a and S3b to the bass drum circuit; S3e, S3j and S3m to the short brush; S3j and S3n to the high bongo. The counter is set for eight beat operation and for each position of the sequence switch S2 the following rhythms result (see Fig. 1):

"Set 1" position of S2 produces a repeated rhythm involving drum, and three short brush sounds, whilst

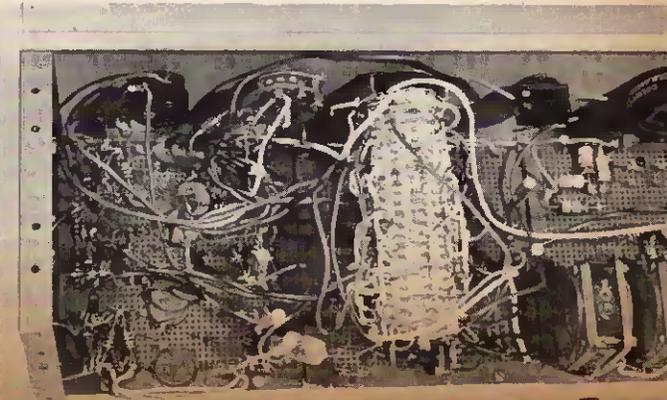

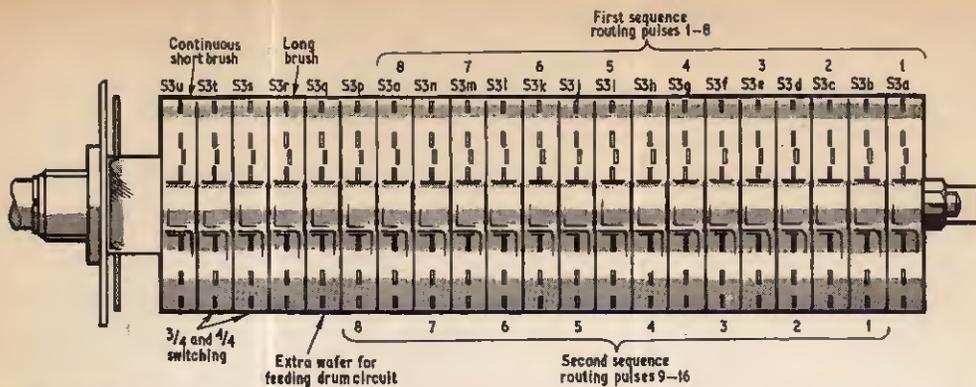


Fig. 5. 'Makaswitch' assembly, showing disposition of wafers and functions

## COMPONENTS . . .

### TWISTED RING COUNTER BOARD "A"

#### Resistors

R1 680Ω	R13 10kΩ	R25 15kΩ	R37 10kΩ
R2 2.2kΩ	R14 15kΩ	R26 10kΩ	R38 15kΩ
R3 15kΩ	R15 2.2kΩ	R27 33kΩ	R39 2.2kΩ
R4 15kΩ	R16 2.2kΩ	R28 33kΩ	R40 2.2kΩ
R5 2.2kΩ	R17 15kΩ	R29 10kΩ	R41 15kΩ
R6 10kΩ	R18 10kΩ	R30 15kΩ	R42 10kΩ
R7 10kΩ	R19 33kΩ	R31 2.2kΩ	R43 33kΩ
R8 2.2kΩ	R20 33kΩ	R32 2.2kΩ	R44 33kΩ
R9 15kΩ	R21 10kΩ	R33 15kΩ	R45 10kΩ
R10 10kΩ	R22 15kΩ	R34 10kΩ	R46 15kΩ
R11 33kΩ	R23 2.2kΩ	R35 33kΩ	R47 2.2kΩ
R12 33kΩ	R24 2.2kΩ	R36 33kΩ	R48 82Ω

All 10%, ½ watt carbon

#### Potentiometer

VR1 2kΩ wire wound

#### Capacitors

C1 5μF 15V	} elect.	C4 0.1μF ceramic
C2 5μF 15V		C5-C14 5,000pF mica (10 off)
C3 3,300pF polystyrene		C15 100μF 15V, elect.

#### Diodes

D1-D16 OA81 (16 off)

#### Transistors

TR1-TR12 OC44 (12 off)

#### Switch

- S1 Press to make/press to break (1A Castelco)  
S2 Single-pole, 3-way

### DIFFERENTIATORS BOARD "B"

#### Resistors

R49-R56 10kΩ	R58-R65 10kΩ
R57 1.8kΩ	R66 1.8kΩ

#### Capacitors

C16-C32 0.1μF

#### Diodes

D17-D33 OA81

#### Transistors

TR13-TR14 OC42

### BONGOES, MONOSTABLE AND NOISE GENERATOR BOARD "C"

#### Resistors

R67-R68 22kΩ	R74 1.8kΩ	R80 1.8kΩ
R69 82kΩ	R75 390kΩ	R81* See text
R70 10kΩ	R76 15kΩ	R82 3.9kΩ
R71 47kΩ	R77 33kΩ	R83 330Ω
R72 10kΩ	R78 39kΩ	R84 330Ω
R73 47kΩ	R79 3.3kΩ	

#### Capacitors

C33*	} See text	C36 0.068μF	C38 25μF elect. 25V
C34*		C37 1.0μF	C39 250μF elect. 50V
C35 0.01μF			

#### Transistors

TR15 ME4103 TR16 OC71 TR17 OC44 TR18 OC71

#### Diodes

D34-D36 OA81

#### Inductors

L1-L2 700 turns of 36 s.w.g. enamelled wire wound on Mullard ferrite pot core (Henry's Radio)

### LONG BRUSH, SHORT BRUSH, BASS DRUM AND PREAMP BOARD "D"

#### Resistors

R85 8.2kΩ	R91 39kΩ	R97 10kΩ	R103 120kΩ
R86 1.5MΩ	R92 10kΩ	R98 18kΩ	R104 47kΩ
R87 33kΩ	R93 10kΩ	R99 22kΩ	R105 4.7kΩ
R88 8.2kΩ	R94 10kΩ	R100 4.7kΩ	R106 4.7kΩ
R89 1.5MΩ	R95 120kΩ	R101 1.8kΩ	R107 330Ω
R90 10kΩ	R96 120kΩ	R102 120kΩ	R108 4.7kΩ

All 10%, ½ watt carbon

#### Potentiometers

VR2 50kΩ VR3 10kΩ VR4 100Ω

#### Capacitors

C40 0.01μF	C46 1.0μF	C52 1,000pF
C41 0.002μF	C47 0.5μF	C53 0.068μF
C42 0.68μF	C48 0.05μF	C54 25μF 25V elect.
C43 0.5μF	C49 0.05μF	C55 2,200pF
C44 5.0μF 15V	C50 25μF 25V	C56 6,800pF
	elect.	elect.
C45 0.1μF	C51 1,500pF	C57 6,800pF

#### Diodes

D37-D38 OA81

#### Transistors

TR19 OC42 TR20 OC42 TR21 OC42 TR22 OC71

#### Rhythm Switch Assembly

S3 Single-pole, 12-way "Break before make" wafers (Radiospares) (21 off)  
Standard "Maka-Switch" shafting assembly with 6in spindle to suit switch wafers

#### Socket

SK1 coaxial socket

#### Inductor

L3 560 turns of 34 s.w.g. enamelled wire wound on Mullard LA1 ferrite pot core (Henry's Radio)

#### Chassis Assembly (Lektrokit)

S.r.b.p. chassis plate No. 4 (4 off)  
Front panel No. 1 LK-401 (1 off)  
Chassis rail LK-201 (2 off) Side plates LK-301 (2 off)  
Covers LK-501 (3 off) Soldering pins LK-3011  
6B.A. ¼in screws and nuts  
(Parts for chassis assembly from Home Radio Ltd. Catalogue number shown should be included when ordering)

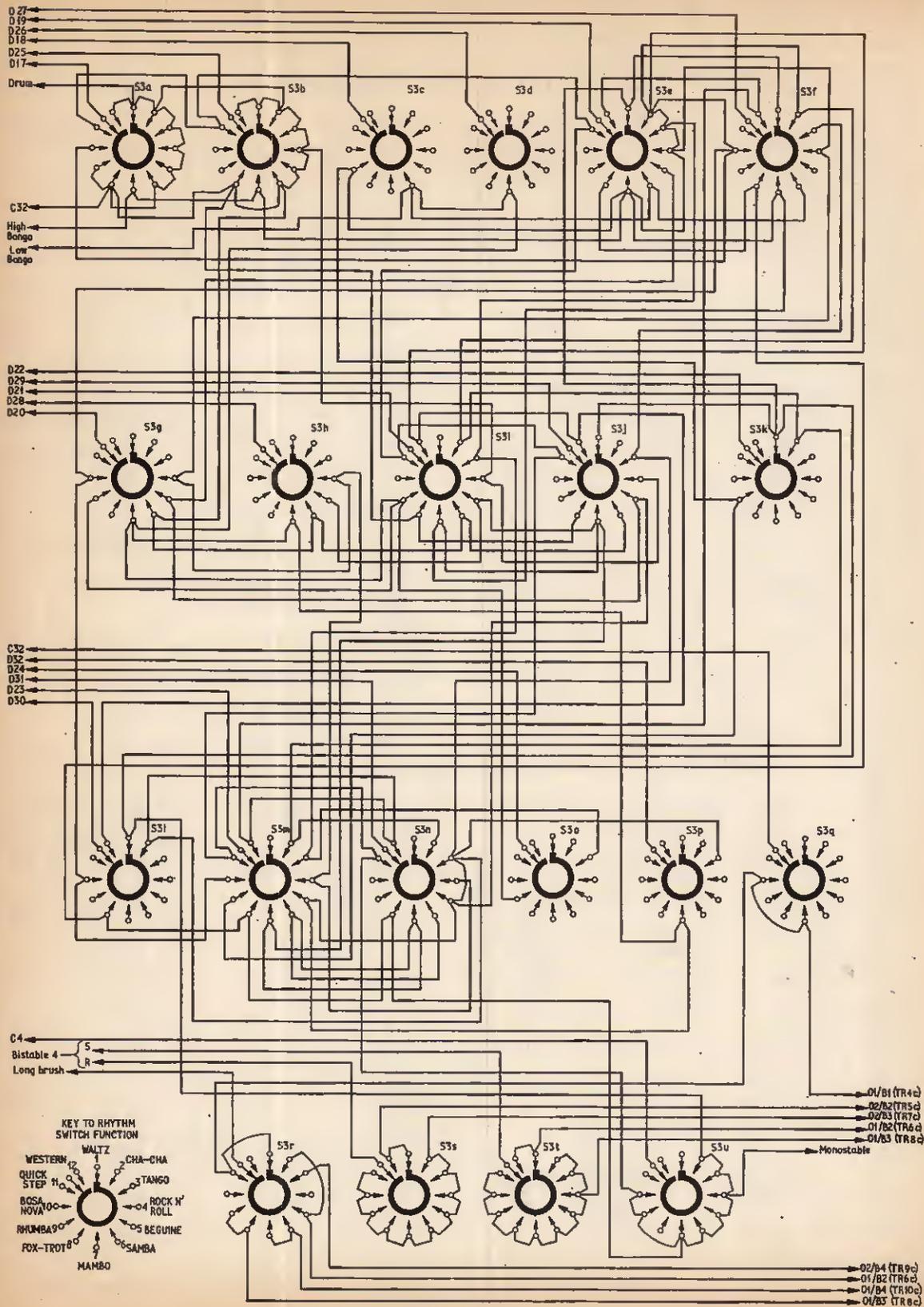


Fig. 6. Rhythm selector switch (S3) wiring diagram

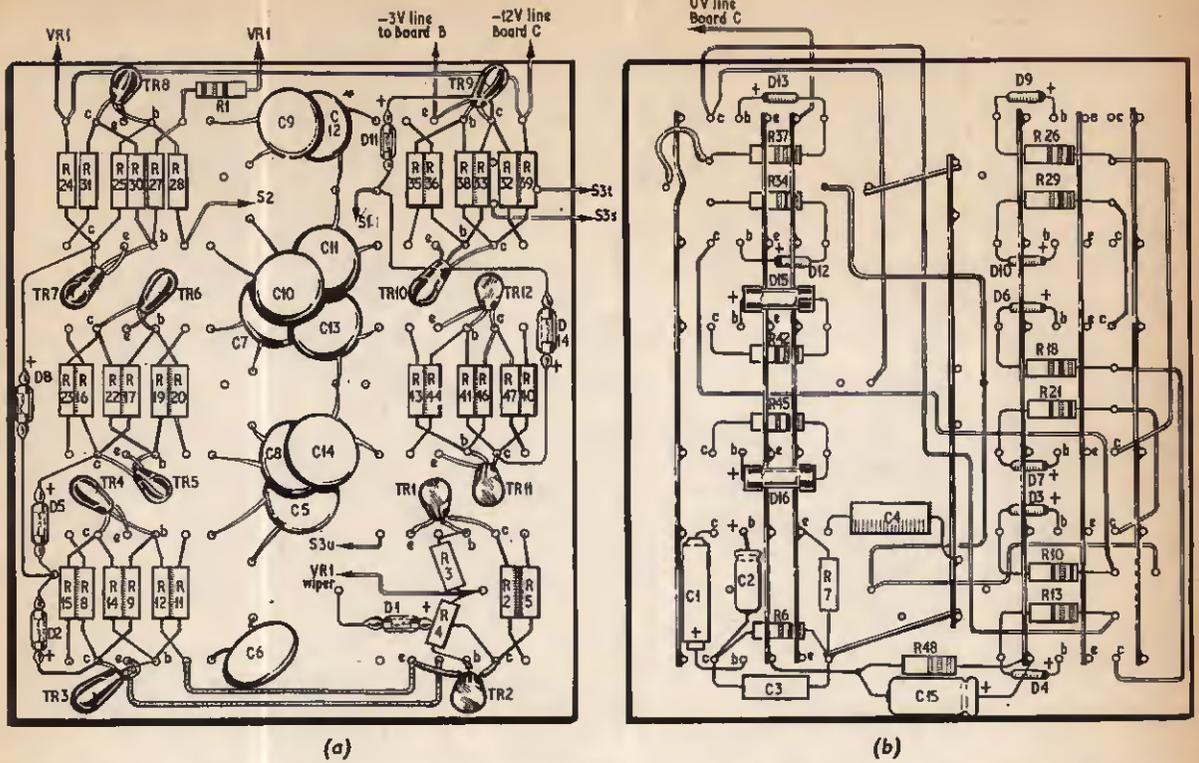


Fig. 7. Component layout and wiring for clock pulse generator and bistable board "A". (a) topside view; (b) underside view

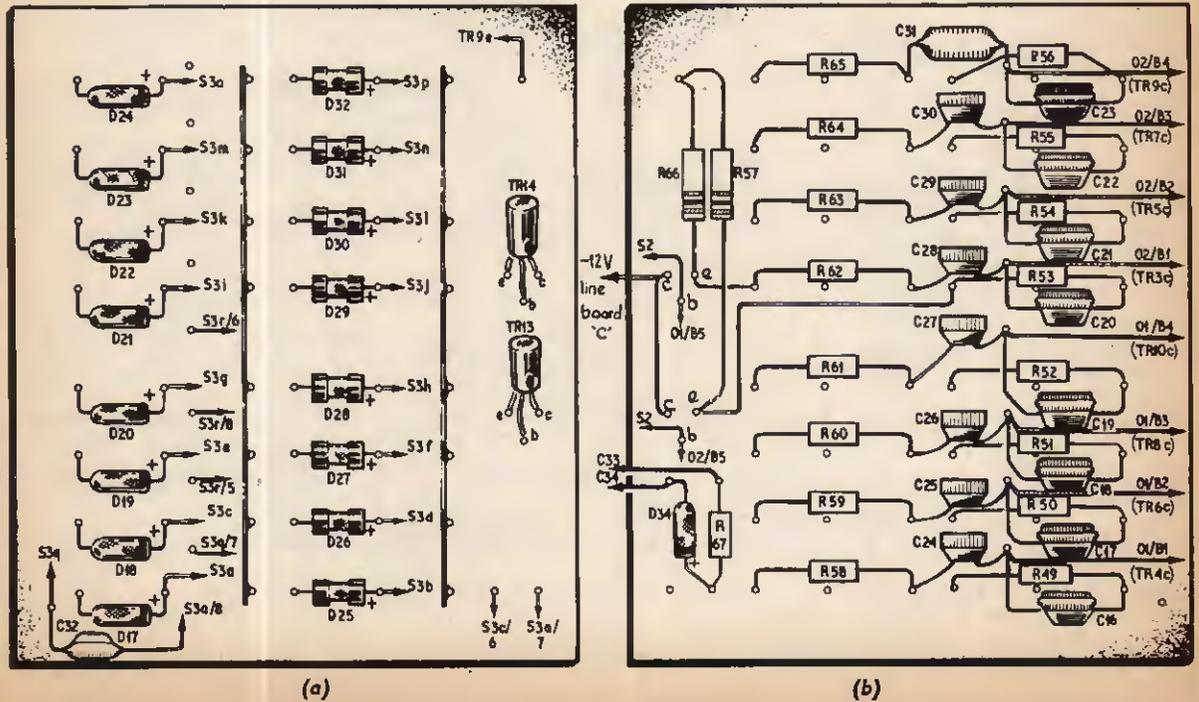


Fig. 8 Component layout and wiring for differentiator board "B". (a) topside view; (b) underside view

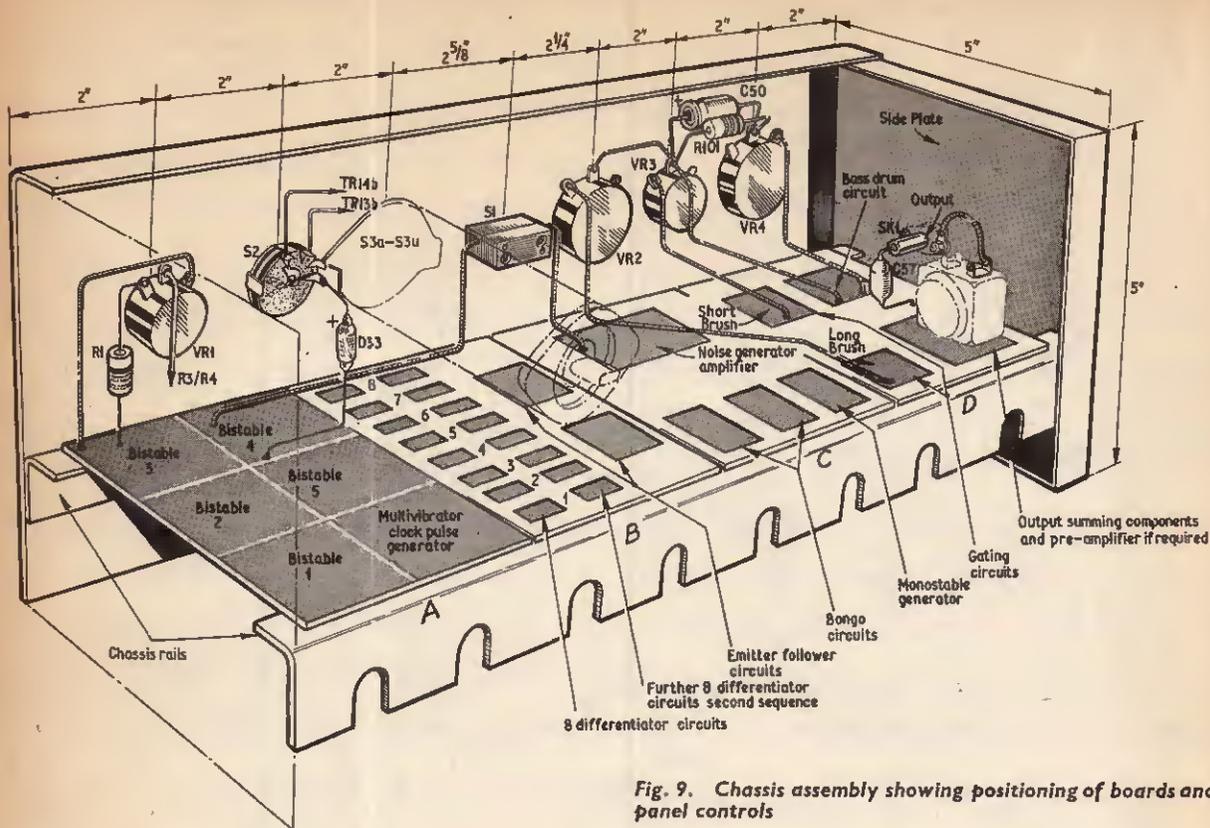


Fig. 9. Chassis assembly showing positioning of boards and panel controls

"Set 2" produces a repeated rhythm involving drum and two high bongo sounds. "Alternate" generates both the previous rhythms alternately.

### RHYTHM SWITCH ASSEMBLY

The 12 position rotary switch used in the selection and routing of the various pulse patterns is made up from a "Maka switch" kit. This must be of the long type with 6in spindle.

Twenty-one single pole, 12-way wafers are individually threaded on to the spindle, each one being firmly butted against the other making sure that all the wiper tags are in common alignment.

Before inter wafer wiring is commenced reference should be made to Fig. 5 which shows the order of the switch wafers relative to the front panel. Using this in conjunction with the wiring diagram of Fig. 6 inter-connection should be commenced.

Starting at switch wafer S3a, wiring to tags which are electrically common should first be made and then flying connections to other wafer tags as indicated. The inter wafer wiring should proceed systematically from switch wafer S3a through to S3u with no board flying lead connections being made at this stage. With wiring completed the switch bank should be placed to one side.

### BOARD ASSEMBLY

Referring to Fig. 7a showing the topside of board A, solder pins should be located at the positions indicated. The tapered design of these makes for easy push fitting, and also allows the pins to be easily moved to other holes if some congestion is encountered if using larger size capacitors or resistors.

Components should now be mounted, each pin connection being a good mechanical bond by wrapping round a turn of component lead before soldering.

With topside assembly completed, the board should now be reversed and the underside wiring carried out as shown in Fig. 7b.

Board B assembly, Figs. 8a and 8b, should be completed and both boards laid temporarily aside.

### CHASSIS ASSEMBLY

The prototype unit was built using a Lektrokit chassis system, see Fig. 9. Both the panel controls and the disposition of the circuits employed are shown on the annotated s.r.b.p. chassis plates. Since this first article is concerned with boards A and B component assembly on these alone will be dealt with.

It is convenient to commence the Lektrokit assembly shown in Fig. 9 by bolting the two chassis rails to one side plate using standard 6B.A. by 1/4in cheesehead screws and nuts. The other side is then attached to the free end of the chassis rails in similar manner. Chassis boards A and B should then be mounted to the chassis rails by means of 6B.A. x 1/4in screws and nuts.

Before attaching the front panel this should be drilled as indicated for the fixing of panel controls. Hole diameters have not been given, but the switch and control retaining nuts can function as templates for this.

Panel controls should then be attached and the front panel connected to the flanges of the side plates by 6B.A. x 1/4in screws, the lower two of which pass also through the chassis rail.

Next month we will present the final part of this article which will deal with the sound forming circuits and final wiring of the unit.

# NEWS BRIEFS

## Big Deal!

ELECTRONIC data handling techniques are spreading through the London Stock Exchange. Several leading broking and jobbing firms are using facsimile systems installed by the Muirhead Group to speed communications between their small offices or "boxes" near the Stock Exchange and their main offices in other parts of the City.

One leading firm of stockbrokers find that, by sending facsimile copies of dealing slips via their Mufax communication system from their box to their office, they can provide an even flow of work for their contract department staff.

## Colour Series for Trainee Engineers

A BBC TV COLOUR SERIES, intended to implement the Engineering Industry Training Board's integrated first year course for engineering craft trainees, started on BBC-2 Thursday, October 3, at 7.10 p.m.

While the series does not itself aim to provide a complete or continuous course, but a number of self-contained groups of programmes on selected topics, the groups are arranged, as far as possible, to fit the order of subjects as treated in most college time-tables, and also to provide a logical progression. All programmes reflect aspects of the trainees' work—theory, works practice and industrial application.

## High Speed Gas

INSTRUMENTATION and mass-flow computers supplied by Honeywell's Industrial Products Group have a key automotive role in the new East Midlands Gas Board supergrid system, now being changed from manual operation, directed centrally, to remote control from the Board's control room at Leicester.

Essential feature for control purposes is to know the quantity of gas passing into each grid offtake. Grid Control at East Midlands Gas Board requires this information in terms of standard cubic feet. Because of this and the fact that the gas density can vary at different points in the system, it was considered essential to compensate for these variations at the point of measurement and present all flow information to Central Control in standard form. This unifies the read-outs from all the various stations and enables the information to be processed into printed data.

This flow information, together with data such as backbone main and grid pressures, is displayed on digital indicators on an extensive control desk, with mimic diagram, at Central Control.

## College Computers

A TOTAL of 22 analogue/hybrid computer systems from the Solartron range have been purchased this year by educational establishments both at home and overseas.

Latest two orders were signed on the stand during the recent IFIP Exhibition in Edinburgh, and both the systems will be installed in Scotland.

Robert Gordon's Institute of Technology, Aberdeen, followed-up their purchase of an HS7-1 earlier this year with an order for a double HS7-3A system valued at £30,000.

On the same day a £17,000 HS7-3A was also ordered by Paisley College of Technology.

Orders have also been placed recently by colleges in Ireland, Sweden and Italy.

## The Unknown Mass

A £42,000 CONTRACT has been awarded to the English Electric Industrial Control and Automation Group at Kidsgrove by Imperial Chemical Industries, Pharmaceuticals Division, for an on-line M2140 computer system, see photograph.

The M2140 will be used to process data from a high resolution mass spectrometer. This mass spectrometer is used by the Pharmaceuticals Division's research department to determine the chemical structures of unknown chemical compounds.



## Meetings . . .

### SOCIETY OF ELECTRONIC AND RADIO TECHNICIANS

#### BIRMINGHAM

October 25, 7.30 p.m. *Colour Television—The Decoder*, by W. J. Anderson, at Room G.11, Bynck Kenrick Suite, University of Gosta Green, Birmingham 4.

#### GLASGOW

October 18, 7.30 p.m. *Airport Telecommunications*, by W. A. S. Aitken, at Y.M.C.A., 100 Bothwell Street, Glasgow, C.2.

#### MANCHESTER

October 31, 8.00 p.m. *Colour Television Servicing*, by T. M. Robinson, at John Dalton College, Manchester.

#### MIDDLESBROUGH

October 29, 7.30 p.m. *Microelectronics*, by T. M. Ball, at Cleveland Scientific Institute, Corporation Road, Middlesbrough, Yorkshire.

### INSTITUTION OF ELECTRICAL ENGINEERS


#### LONDON

October 16, 5.30 p.m. *Thin Film Transistors*, by Prof. J. C. Anderson, at I.E.E., Savoy Place, London, W.C.2.

October 17, 10.00 a.m. *Colloquium System Structures of Modern Computers*, at Middlesex Hospital Medical School. Tickets for this meeting must be obtained from the Secretary, I.E.E., Savoy Place, London, W.C.2.

October 23, 5.30 p.m. *Electro-optics*, by Dr J. Bass and Dr K. F. Hulme, at I.E.E., Savoy Place, London, W.C.2.

# FROST ALARM

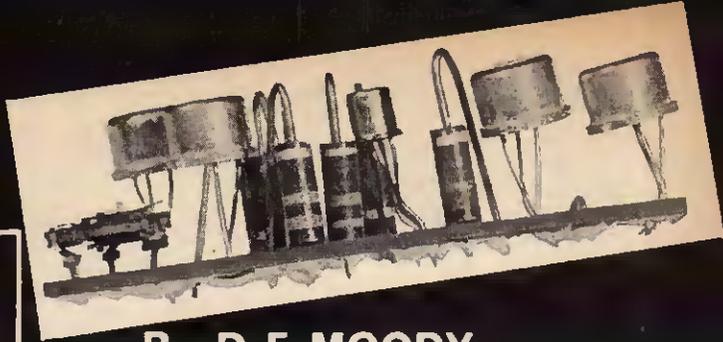

By D. F. MOODY

**T**HIS unit, although primarily designed for the motorist as a road ice indicator, can also be used as an early warning device for the protection of domestic water pipes and greenhouse or outdoor plants when frost is imminent.

In preparing this design the requirements were for long term stability, ease of initial calibration, immunity from small supply variations and operation of the indicator from off to full on over a narrow temperature range.

The circuit employed is essentially a solid state bridge arrangement with a thermistor, or temperature sensing element, included in one of the bridge arms. Indication of bridge unbalance, caused when frost is imminent, can be either visual or audible.

Since ice formation on dimly lit roads at night is much less apparent than in the day, a lamp on the car dashboard which is illuminated with a cautionary red glow, when external temperature is at 0 degree Centigrade will prove an excellent indicator of prevailing road conditions.

For the householder, who is usually asleep when frost is abroad, the strident tones of an electric bell will provide the spur for some protective action.

In describing the unit, both systems will be presented.

## HOW IT WORKS

In Fig. 1 it will be seen that TR1 and TR2 are complementary *pnp* and *npn* transistors forming two arms of a bridge circuit with the base bias resistors R1, R4, which span the supply, making up the other arms.

When balance is achieved by adjustment of VR1, the potential at the junction of the bias chain resistors R2 and R3 will be equal to the potential at the collector junction of TR1 and TR2 which is half the supply voltage. TR3 and TR4, which form part of the detector circuit, are non-conducting as the base/emitter potential drops of both transistors are negligible ensuring that both are cut off.

If the emitter resistance of TR2 increases the bridge circuit will become unbalanced. The resistance of thermistor X1, which exhibits a negative coefficient of resistance, will increase with a reduction of temperature with a subsequent increase of potential drop across the collector load of TR1 comprising TR2, VR1 and the thermistor.

Since this collector voltage rise is positive, both TR3 and TR4 will conduct so switching on TR5 which bottoms to illuminate the lamp LP1 or energise a relay, whichever load is employed.

## CONSTRUCTION

Construction of the unit is fairly simple. Cut the copper strips according to Fig. 2. Then assemble the components, starting at one end of the board and working through to the other end.

When complete check the wiring and make sure the cases of the ASY26 and ASY28 transistors are not

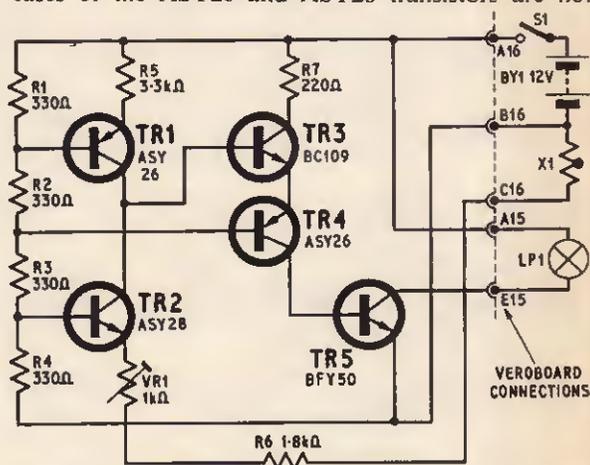


Fig. 1. Circuit diagram of frost alarm. Connections at A15/E15 can be either lamp or relay depending on application

touching each other or any part of the circuit as the cases are connected to the base. If the lead lengths of the transistors are kept short this will prevent any subsequent movement and possible damage.

## CALIBRATION

The most convenient way to calibrate the unit is to connect the 12-volt supply, lamp, thermistor, and switch to the Veroboard as shown in Fig. 2, using long lengths of miniature p.v.c. 7/40 wire for the thermistor connection.

The module and supply should then be arranged on top of a refrigerator.

If a Centigrade thermometer is placed at a spot close to the ice-box, it is possible by adjustment of the thermostat controller to set the temperature at freezing point or 0 degree Centigrade. If the indicating unit is intended for domestic use, the refrigerator temperature adjustment should be for a couple of degrees above zero.

# COMPONENTS . . .

With these reference-temperatures established the thermistor should be placed at the position occupied by the thermometer. The thin, flexible, 7/40 wires will permit closure of the refrigerator doors, whilst calibration is in progress. Since the thermistor is wire ended precautions should be taken to prevent any chance of accidental short circuit, by laying it on a piece of cloth.

The supply should now be switched on and VR1 gradually advanced till the lamp just switches on. Reducing the resistance value of this potentiometer slightly will just turn off the lamp. No more adjustment of the unit is necessary as calibration is now complete and the module is ready for installation.

If a bell indicator is required a lightweight relay with suitable contact rating for a volt bell should be substituted for the lamp. The calibration procedure for this should proceed on the lines as before.

## HOUSING THE UNIT

The unit, including batteries, can be housed in a suitably sized wooden box if intended for domestic use.

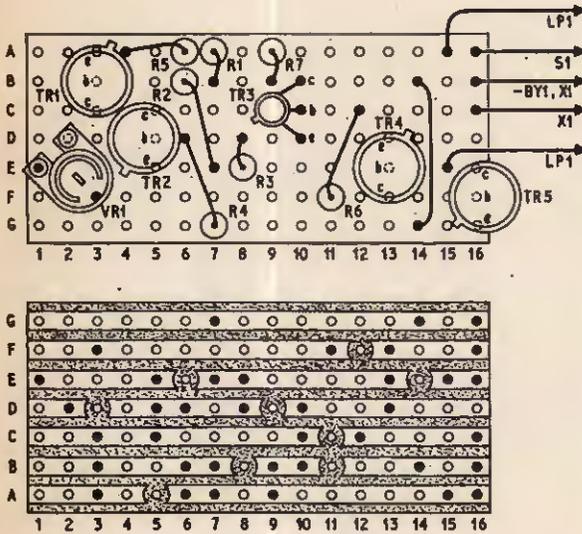


Fig. 2. Veroboard assembly showing top view arrangement of components and breaks in conductor strips

For motorists, since the supply is taken from the car battery, the box dimensions can be considerably reduced. In the author's prototype a small plastic case was used and then fitted to the dashboard. A convenient form of attachment is sticky tape.

Holes should be cut to the diameter of the lamp shank and the diameter of the calibration pre-set potentiometer VR1. This will make for easy screwdriver access even though calibration will only be rarely necessary, say once every two years.

If the unit is to be used in a car, S1 may be omitted. One of the two supply leads should be connected to some convenient anchorage point on the car chassis and the other connected to the ignition switch, so that power to the unit will be turned off when the ignition key is removed. Before embarking on these wiring instructions, it is important that the car chassis polarity should first be determined, that is whether positive or negative. When this is done, the relevant supply connections can be made without risk of damage.

Resistors	
R1	330Ω 5%
R2	330Ω 5%
R3	330Ω 5%
R4	330Ω 5%
R5	3-3kΩ 5%
R6	1-8kΩ 10%
R7	220Ω 10%
All ½W carbon	

### Potentiometer

VR1 1kΩ miniature carbon preset

### Transistors

TR1	ASY26	} (Henry's Radio Ltd.)
TR2	ASY28	
TR3	BC109	
TR4	ASY26	
TR5	BFY50	

### Thermistor

X1 CZ9A

### Switch

S1 Single pole on/off toggle

### Battery

BY1 Two Ever Ready PPI, 6V batteries (see text)

### Lamp

LP1 12V, 0.75W L.E.S. (Radiospares)  
Relay (if required) 670Ω lightweight B and R type  
(Home Radio—Cat. No. Z70B)

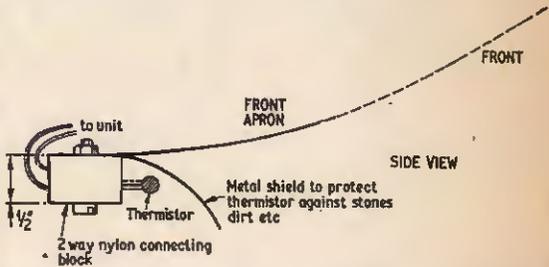


Fig. 3. Method of thermistor mounting to front apron of car

## THERMISTOR MOUNTING

The thermistor was mounted on a section of nylon terminal block. In domestic applications the junction between thermistor and its unit connecting leads can be made mechanically with the terminal screws of the nylon block. For car use, these leads should be soldered and connected as before to preclude any chance of the retaining screws loosening and producing an open circuit.

Final fixing of the block should be by screw to either wall or shelf.

To detect road ice hazards, the block should be mounted at the front of the car, under the front bumper. To prevent damage to the thermistor by stones and dirt thrown up from the road, a small deflecting shield was formed by bending a length of sheet aluminium or tin to the width of the nylon block, see Fig. 3. If a ½in hole is drilled in the car's front apron, both shield and block can be affixed with a nut and bolt.





# EXPERIMENTS WITH SOUND LIGHT & COLOUR

PART 4 By F.C. JUDD, A. Inst. E

Without the amplitude modulation and grid pulses the display would simply be a circle. With modulation at around 10Hz the circle will be displayed successively as in Fig. 4.4. With pulses applied to the c.r.t. grid parts of the expanding circle will be blanked out. The relationship between the fundamental frequency of the signal forming the circle and the grid pulses will decide exactly the number of blanked out segments.

The waveforms in Fig. 4.3 may serve to illustrate the pattern frequency to pulse frequency relationship more clearly, and (as Fig. 4.4 shows) would produce a pattern divided by two since each grid pulse occurs twice during one cycle of the pattern frequency. Therefore if the pattern frequency were 250Hz then the grid pulse frequency would be 500Hz.

The determination of given patterns is therefore a matter of relating the frequencies of deflector coil signals to those of the grid pulses. The frequency of the grid pulses can of course remain constant and the fundamental patterns or deflection signal frequencies varied accordingly.

**T**HE cathode ray tube colour pattern display described in the second and third parts of this series lends itself most admirably for sound programming, i.e. for producing preconceived or random patterns and sequences of patterns in synchronisation with music. The system also offers exciting possibilities for filming, using all the various film techniques such as superimposing, zooming and panning. The writer has in fact produced a 15 minute colour film from the display, complete with electronic music sound tracks, but more of this later.

## FORMATION OF PATTERNS

It may be realised that patterns can be preconceived by knowing precisely the frequencies and waveform of signals applied to the deflector coils and the frequencies of the grid pulses.

The photograph shown in Fig. 4.1 was taken from the c.r.t. display and although reproduced here in black and white it does show the basic formation of the pattern as circular. On the actual display the pattern appeared in multi-colour and moving, i.e. slowly spinning.

The pattern was formed from an amplitude modulated sine wave fed via the phase shift network to both deflector coils as described in Part 3. This produced the expanding rings effect shown in Fig. 4.2 and which is divided into four segments by grid blanking pulses. The one in the photograph (Fig. 4.1) is divided into five segments, but this division can be any number from two up to seven or eight or more.

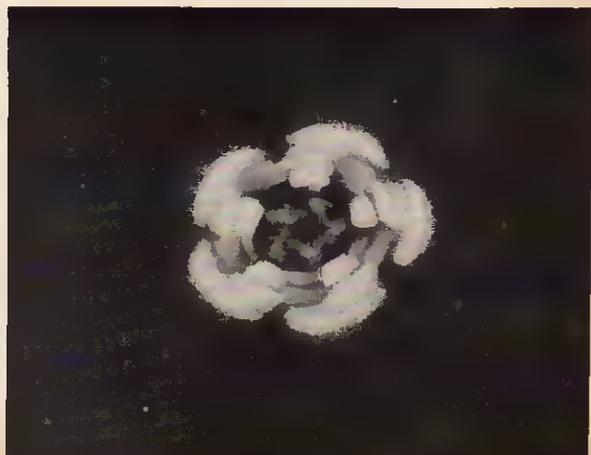


Fig. 4.1. A circular segmented pattern derived from the c.r.t. display

## SIGNAL SOURCES

In order to produce complex patterns of this nature, at least two audio frequency sine square wave generators and a signal mixer are necessary—although interesting patterns can be produced from music only. The combinations of signal sources and ways in which these can be fed to the deflector coil amplifiers are as follows:

1. Audio generator to input 1 and audio generator to input 2.
2. Audio generator to input 1 and music signals to input 2 or vice versa.
3. Audio generator to both inputs with phase shift network in circuit.
4. Music to both inputs with phase shift network in circuit.
5. Audio generator and music signals mixed to both inputs via phase shift network.
6. Two or more audio generators with signals mixed to input 1 and music to input 2.

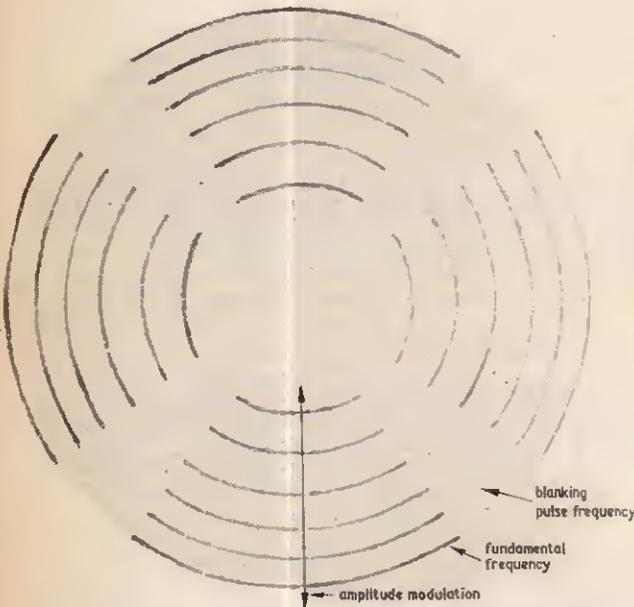


Fig. 4.2. How a circular "expanding rings" pattern similar to that shown in Fig. 4.1 is formed

## CO-ORDINATING SOUND WITH PATTERNS

Since patterns can be partly or wholly formed from music signals, they can be made to appear to form and move in synchronisation, i.e. rhythmically with music. Moreover the signals for the patterns, whether derived from music or audio signal generators, can be recorded on magnetic tape with a conventional domestic tape recorder. A programme of patterns and music can therefore be tape recorded and replayed at any time.

## ELECTRONIC MUSIC

The choice of music to which the patterns can be made to form and change and move must be left to aesthetic and musical tastes of the experimenter. Electronic music is of course a natural for a display of this kind and it was this type of music that originally prompted the writer to investigate the possibilities of sound, light and colour co-ordination as described in these articles.

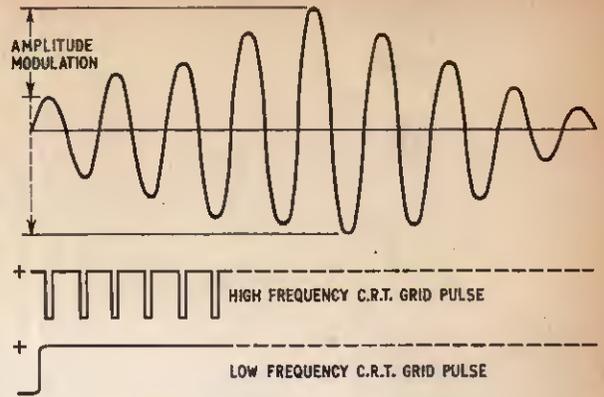


Fig. 4.3. Relationship of pattern signal frequency to grid pulse frequencies

There are a number of records of electronic music available and the fact that pure tone is frequently used in this kind of music makes it very suitable for producing patterns. Those who have the necessary audio signal generators and a tape recorder might well be able to produce both music sound tracks and patterns specifically composed one for the other.

## CIRCULAR PATTERNS

Programming in its simplest form would be to feed music signals directly to both inputs of the display with the phase shift network in circuit. With this arrangement predominantly circular patterns would be formed and in exact time with the music.

As a variation a small 50Hz signal could be injected into one amplifier, just sufficient to produce a horizontal line to the maximum width of the screen. This forms a simple time base for music signals injected into the other deflector amplifier. The display will be rather like that of music on a conventional oscilloscope with a slow time base in a multiplicity of colours.

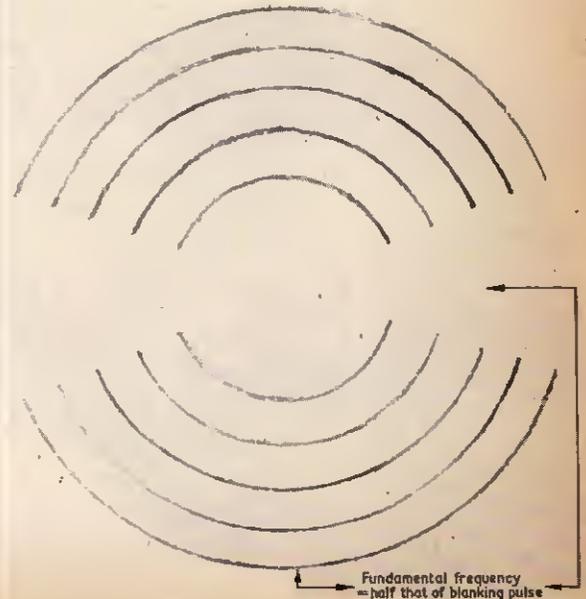


Fig. 4.4. How a pattern would be formed with the signals shown in Fig. 4.3

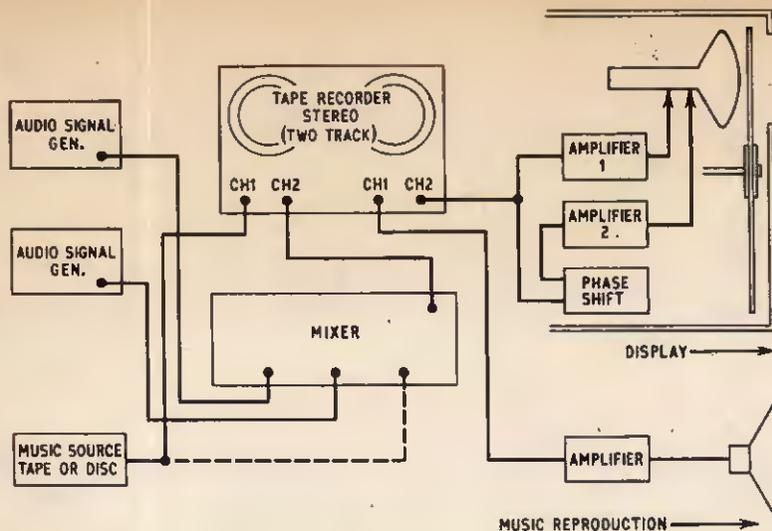


Fig. 4.5. System and equipment used by the author for programming pattern signals and music on magnetic tape

## USING TWO DIFFERENT INPUTS

With the aid of one or more audio generators given patterns can be produced and made to come and go as well as move in time with music, but this requires very rapid manipulation of the generator controls.

A similar arrangement but one not so difficult to manipulate is to feed music to one amplifier and an audio generator to the other. The music signals will provide the rhythmic movement whilst formation or shape is produced with the generator controls, i.e. frequency variation, amplitude variation and switching from sine to square-waves.

## TAPE RECORDER

Programming with a tape recorder and an audio generator, as well as music signals, provides the ultimate and most dynamic effects. With this equipment the signals for a programme can be recorded and the tape edited if necessary by the usual technique of cutting and splicing.

For example the pattern signals can be recorded first in chosen sequences by stopping and starting the tape. This allows ample time in which to carry out this part of the programming, i.e. the generator frequencies can be pre-set before actually recording. The ideal tape recorder for this is a half- or quarter-track stereo record/playback machine preferably with "off tape" outputs or at least through signal outputs. Such a recorder allows for feeding the pattern signals through to the display before and/or during actual recording.

The block diagram in Fig. 4.5 shows the arrangement employed by the writer for recording patterns and music tracks for the c.r.t. display described in the two previous articles.

## LISSAJOUS PATTERNS AND MUSIC

Although comparatively simple in shape, the most striking patterns are 2 to 1 and 3 to 1 Lissajous patterns from sine or square waves. Over-complex patterns produced from music have no definite shape and after a while become uninteresting.

Superimposing music signals upon slowly moving Lissajous patterns is quite effective and gives the illusion of movement in time with the music. Low frequency signals produce the most contrasting colour effects, i.e. frequencies which are equal to, or multiples of the scanner speed and low frequency grid pulses (10, 15, 25 and 30Hz).

## FILMING FROM THE DISPLAY


The brilliance intensity of the c.r.t. patterns is high enough for filming with ordinary 8mm artificial light colour film such as Kodachrome 25 ASA film, providing the patterns are reproduced within an area of approximately 2in x 2in. This means operating with a close-up lens, but most dynamic sequences can be filmed this way. The writer has made a 15 minute film with electronic music sound tracks. (Readers who are not equipped for filming might well find a local cinefilm enthusiast or cineclub interested in filming such unusual but nevertheless creative material from their own version of this c.r. colour display.)

The photograph, Fig. 4.6, shows the arrangement used by the writer with an 8mm reflex camera equipped for zooming and with a close-up lens so that patterns could be made to fill the cine screen. Here is a description of the way in which the film was produced.

First it was decided that a coloured background would enhance the overlays of colour patterns filmed directly from the display. The whole film was exposed at 12 frames per second with the aperture at f2.8 to a white surface illuminated in colour by means of a 60 watt lamp behind coloured cinemoid. Deep blues, green and dark red provided the best colour background.

## SUPERIMPOSED PATTERNS

Then the film was run through no less than three more times in order to superimpose patterns one upon the other and employing all the filming techniques the camera would allow: zooming, panning, fading and de-focussing, etc. This, together with electronic

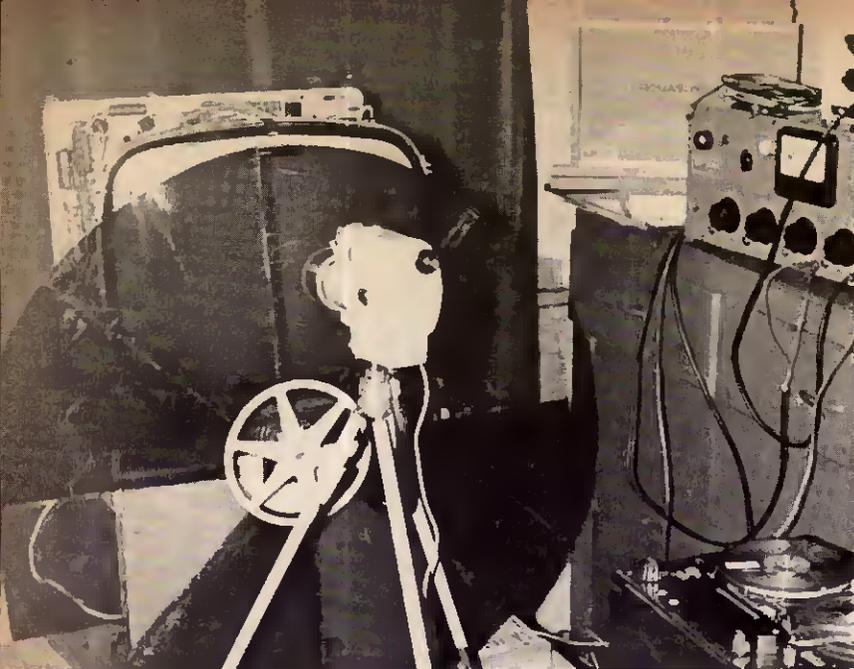

**Fig. 4.6.** Set-up for filming the c.r.t. colour pattern display. Note close-up lens on cine camera

control over the pattern signals, produced some excellent shots which were then edited for showing with sound tracks of electronic music.

A short sequence of film is shown in Fig. 4.7. Unfortunately this is not reproduced here in colour but in the original the background is deep red with the patterns appearing in yellow and mauve. The film speed was 12 to 16 frames per second at F2.8.

### PROGRAMMING THE SIMPLE COLOUR LIGHT DISPLAY


The method of feeding music signals directly to the input of the simple colour light block display was dealt with in Part 1, which also gave constructional details of the display itself.

Audio sine tones from a signal generator and a tape recorder could also be employed to obtain repeating sequences of colour change and movement with this light display. The method of programming is similar to that described in the previous paragraphs, i.e. music is recorded on one track and control signals on the other. By using audio sine wave signals much more defined changes can be obtained since tones can be selected with frequencies midway between those covered by the filter circuits.

In conclusion the writer would like to mention that one PRACTICAL ELECTRONICS reader suggested the use of thyristor control for larger lamps in a display similar to the one described in our opening article. The method proposed could of course be used. In fact there is virtually no limit to the possible arrangements for controlling light from filtered music, or by means of impulse or tones recorded on magnetic tape themselves in synchronisation with music. The writer has attempted only to outline the subject and provide sufficient basic circuit information and other details to encourage others to experiment with two possible methods. A great field is open for those prepared to explore. ★



**Fig. 4.7.** An 8mm film strip showing patterns from the c.r.t. display. The original film was in brilliant colour (see text)

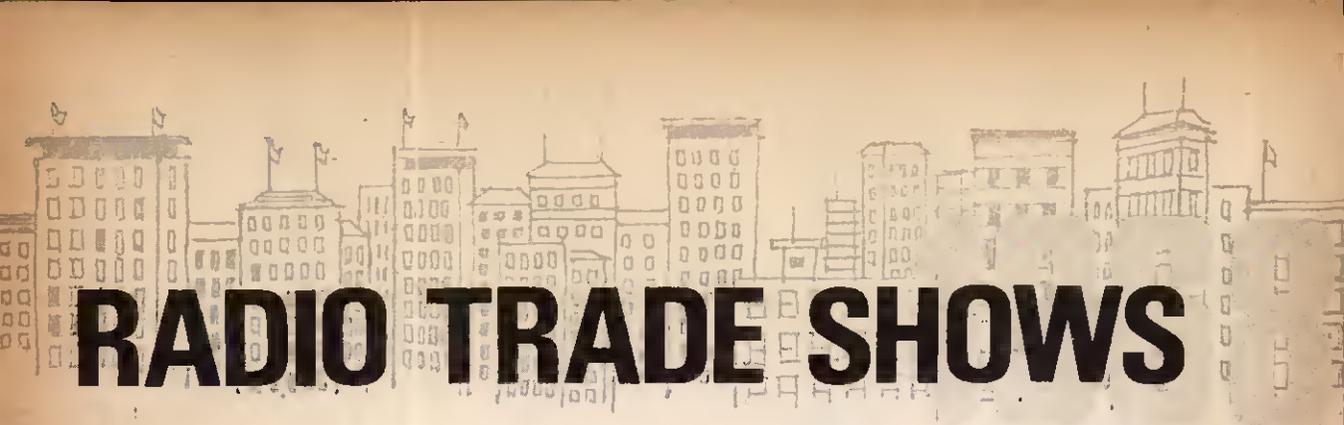

# RADIO TRADE SHOWS

## Jottings from jaunts around the London trade shows

A VISIT to the Earls Court Radio Show used to be an outing for all the family. Dad went to nod knowledgeably over specifications, Mum to see her idols on the BBC stand—and make the final buying decisions—and the kiddies to collect colourful leaflets.

Declining commercial support finally closed the “public” show in 1964, and the handful of separate trade shows held during the run of the show, particularly by foreign manufacturers excluded from the main event, has grown ever since.

### TWENTY-TWO DIFFERENT SHOWS

This year, a record 57 manufacturers and distributors, more than half of whom were traceable to continental origins, displayed their wares in 22 centres in London over a period of five days. The majority occupied hotel bedrooms, the more illustrious took over complete ballrooms, and some used their own premises.

All the exhibitors we spoke to were in favour of this fragmented showing and had no regrets over the exclusion of Mum, Dad and offspring—there were fewer distractions and those who came to view came also to buy. A retailer said he found the staff on the stands better informed than the professional demonstrators of Earls Court days, and the environment more

suitable for viewing and listening. But he was concerned for the less well-known exhibitors, whose success depended on how energetically they advertised before the show. It takes a dealer with stout walking boots and a heart of gold to traverse five miles of London's West End to see the efforts of a newcomer!

This short report will concentrate mainly on new audio equipment—development in other fields will be covered by the companion journals *Practical Television* and *Practical Wireless*.

### UNITS v. RADIOGRAMS

Although there is undoubtedly a trend to integrated amplifier/tuners with separate record playing decks and loudspeakers, this is not quite so definite as a tour around this caravan of shows might initially suggest.


Most of the unit audio was due to continental exhibitors who, as has been stated, were present in force. A large British manufacturer said that radiograms were still very popular in this country and would never be outstripped by strings of “bits and pieces”—even though he was well aware which approach gave better performance per pound. Another, who earned a comfortable living from “bits and pieces” said the opposite.

Sinclair System 2000 f.m. tuner



Perpetuum-Ebner PE2020 automatic/manual turntable with base and transparent cover

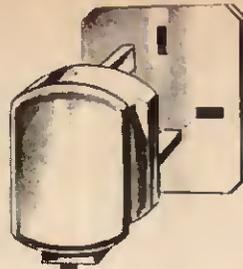plug in  
the smallest  
soldering iron  
available



**Complete precision soldering kit**



This kit—in a rigid plastic "tool-box" — contains everything you need for precision soldering.

- Model CN 15 watts miniature iron, fitted  $\frac{3}{16}$ " bit.
- Interchangeable spare bit,  $\frac{3}{32}$ ".
- Interchangeable spare bit,  $\frac{3}{32}$ ".
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron
- Space for stowage of lead and plug

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

From Electrical and Radio Shops or send cash to Antex. **49/6**

... pin-point precision soldering ... fingertip control ... bits that do not stick to shafts ... bits that slide over elements ... sharp heat at the tip ... reliable elements ... spares always available ...

in Europe, Africa, Asia, America ... ANTEX soldering irons are used by experts and amateurs alike; they have found out the advantages of Antex ...

you can too ... buy one in a shop or direct from us ... or ask for our catalogue first.

CN 15 watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from  $\frac{.040$ " (1mm) up to  $\frac{3}{16}$ ". For 240, 220, 110, 50 or 24 volts.

**32/6**

From Electrical and Radio Shops or send cash to Antex.

ACTUAL SIZE



G 18 watts. Ideal for miniature work on production lines. Interchangeable spare bits,  $\frac{3}{32}$ ",  $\frac{1}{8}$ ",  $\frac{3}{16}$ ", and  $\frac{1}{4}$ ". For 240, 220 or 110 volts. 32/6.



E 20 watts. Fitted with  $\frac{1}{4}$ " bit. Interchangeable spare bits  $\frac{3}{32}$ ",  $\frac{1}{8}$ ",  $\frac{3}{16}$ ". For 240, 220, 110 or 24 volts. 35/-.



ES 25 watts. Fitted with  $\frac{1}{8}$ " bit. Interchangeable bits  $\frac{3}{32}$ ",  $\frac{3}{16}$ " and  $\frac{1}{4}$ ". Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. 35/-.



F 40 watts. Fitted  $\frac{5}{16}$ " bit. Interchangeable bits  $\frac{1}{4}$ ",  $\frac{3}{16}$ ",  $\frac{1}{8}$ ",  $\frac{3}{32}$ ". Very high temperature iron. Available for 240, 220, 110, 24 or 20 volts. 42/6.

Spare bits and elements for all models and voltages immediately available from stock.



Model CN240/2  
15 watts - 240 volts

Fitted with nickel plated bit ( $\frac{3}{32}$ ") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex.

**31/-**



**PRECISION MINIATURE SOLDERING IRONS**  
made in England

Antex, Mayflower House, Plymouth, Devon  
Telephone: Plymouth 67377/8. Telex 45296. Giro No. 345007.

To: Antex, Mayflower House, Plymouth, Devon

- Please send me the Antex colour catalogue
- Please send me the following irons


Quantity	Model	Bit Size	Volts	Price
.....	.....	.....	.....	.....
.....	.....	.....	.....	.....
.....	.....	.....	.....	.....

I enclose cheque/P.O./cash value.....

NAME.....

ADDRESS.....

PE 11..... Telephone.....

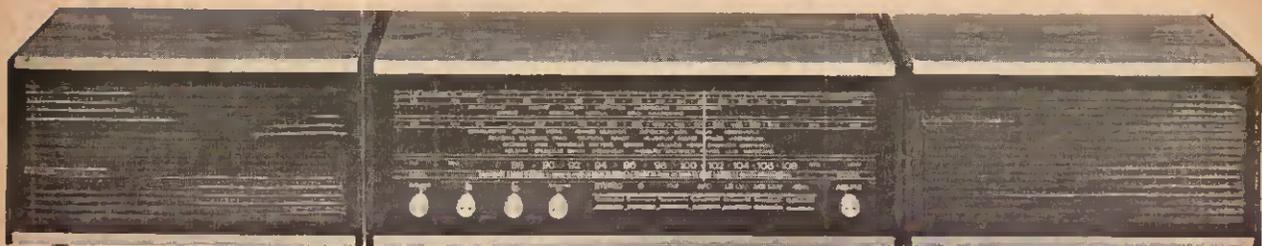

*Arena stereo tuner amplifier type T1500F with two HT21 speaker units*

### IMPRESSIVE ADVANCES

Approaching from central London, our first port of call was the Arena display in the Piccadilly Hotel, where we were greeted by news of "the most advanced tuner-amplifier on the market". It uses silicon diodes for tuning both v.h.f. and medium wavebands, uses an improved version of the company's plug-in modular construction, has a sensitivity of 0.5 microvolts on f.m. and has an audio output of 90W r.m.s. per channel. The exhibits also provided a second opportunity to hear the smaller-scale T1500F tuner-amplifier which was briefly reviewed in the May issue of PRACTICAL ELECTRONICS.

Second audio exhibit to highlight the advance in electronics was the now well-known Sinclair 10W integrated circuit amplifier, a pair of which had been made up as a stereo amplifier specially for the show and demonstrated through the new Q14 mini speaker. Another exhibit was the System 2000 pulse counting f.m. tuner, which uses varactors to permit continuous tuning by remote control. A new tuner, to complement the Neoteric amplifier, is to appear shortly.

### PERCUSSION GENERATOR

The Eagle products stand provided a welcome opportunity for creative knob-twiddling in the shape of the Rhythm Master percussion generator, which gives seven percussion sounds and nine rhythms. (Do-it-yourselfers will be interested in the rhythm generator design that appears elsewhere in this issue.) The display included some of the variety of plugs, sockets, microphones, and effects generators handled by the company.



**Eagle Products**  
*Rhythm Master percussion generator*

### RECORD PLAYING EQUIPMENT

On the Perpetuum-Ebner stand we saw Germany's attempt to overcome the audiophile's inbred mistrust of automatic record changing. The PE2020 has a 7lb turntable, adjustable vertical tracking angle, stylus pressure and antiskating force, a rotating centre spindle and an ingenious stepped turntable for detecting record-size.

Record playing equipment for different needs, but equally ingenious, was shown by Discatron. The RHR9001 was a combined portable radio and 45 r.p.m. record player, similar in styling to a conventional radio. Other combinations included a record and tape player, and a radio, record and tape player.

### RADIO FOR CASSETTE RECORDER

An interesting accessory on the Aiwa stand was a small radio tuner which slips into their 736 Compact cassette recorder. The TPR101, a combined recorder and multi-band radio, gained its first public showing.

A last minute addition to the Alba range was a deluxe radiogram, Model 4007.

With a 30W amplifier and two tuner units, Crown made their first attack on the British hi-fi market.

### WELL CONTENTED TRADE VISITORS

As a percentage of the whole, there was little innovation in this collection of displays. Colour TV, f.e.t.s., integrated circuits, micro-speakers have ceased to amaze—but no trade visitor was likely to feel bored. He could enter a competition for £1,000, a holiday in Hamburg or a night on the town. He could relax and watch cabaret, or politely refuse 57 complimentary Martinis on the trot. ★



CATALOGUE 1968

# KJ ENTERPRISES

Britain's premier mail-order recording tape and audio specialists

17 THE BRIDGE · WEALDSTONE · HARROW MIDDLESEX. TELEPHONE 01-427 7758

DISCOUNTS UP TO 40%

**FREE CATALOGUE**


Please send your latest catalogue to:

NAME .....

ADDRESS .....

K. J. ENTERPRISES, (Dept. P.E.)  
17 THE BRIDGE, WEALDSTONE, MIDDLESEX.

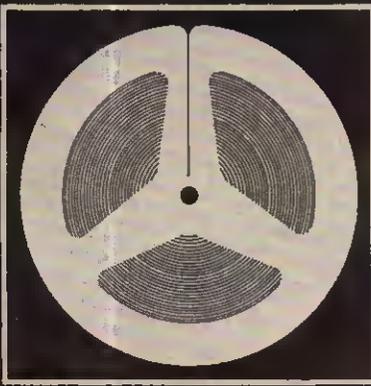Suppliers to Schools, Universities and Government Departments



# STEP UP YOUR EARNINGS...

IT TELLS YOU ALL ABOUT—Installing domestic wiring, regulations, equipment, testing, cables and faults, meters and switch-gear, lighting, water heating, space heating, cookers, refrigeration, public address equipment . . . in fact everything you need to add to your income, to really advance in your work.


## with this complete library of electrical know-how and practice

You can have this handsomely-bound library of facts, figures, vital theory and day-to-day practice sent to your home to examine free of charge. It will help you understand the many branches of the vast electrical industry from installation work of all kinds, Equipment Instruments, Motors and Machines, Repair work, Maintenance and Operation right through to the Generation and Distribution of electricity. And, to make the 2,350 pages of absorbing text crystal clear there are over 2,000 'action' photos and explanatory drawings. In addition you receive a slip-case of 36 large Blueprint charts and sheets of handy data. Plus fascinating colour booklet of transparent pages which peel away to reveal how a Nuclear Power Station is operated.

Leading experts explain in detail. Written by 87 experts, this PRACTICAL library is planned to give you the knowledge which would normally take a lifetime to acquire. Send for your free trial set now—no obligation to purchase.



# PRACTICAL ELECTRICAL ENGINEERING

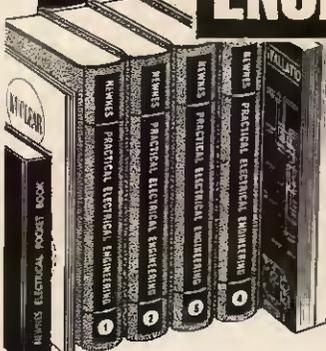

**Here is what you receive**

4 Volumes strongly bound in Grey Moroquette, 9 1/2 in. x 6 1/2 in. containing 2,352 Pages of instructive information on latest practice; 2,100 Photographs, Diagrams, Working Drawings, many showing actual operations in works and plants.

24 Data Sheets in colour.

12 Quick-reference Blueprint Charts, each in the large size of 16 1/2 in. x 11 1/2 in.

**NUCLEAR POWER STATIONS BOOKLET**

Newnes Electrical Pocket Book Nearly 400 pages with 258 illustrations, diagrams, tables. (Value 10/6d.)

# Use it FREE for 7 days

To: Buckingham Press Ltd., 18-19 Warren Street, London, W.1  
Please send PRACTICAL ELECTRICAL ENGINEERING without obligation to buy if you accept my application. I will return the books in 8 days or post—

Tick (✓) here  Full cash price of £16, or  16/- dep. & 16 monthly payments of 20/-.

If you are under 21 your father must fill up the coupon

Full Name (Block letters) .....

Address .....

County .....

Occupation .....

Signature ..... Mr. Mrs. Miss

PEE/3835

(Credit price £16.16s.) For Eire & N.I. send £16 with coupon. Elsewhere Overseas add 26/- p. & p.

Please tick (✓) here  
The address on left is my/our property   
Rented   
unfurnished   
Furnished   
Temporary address   
If none of the above please answer here

## GOODMANS HIGH FIDELITY MANUAL

A Guide to full listening enjoyment



The Manual is much more than a catalogue of Goodmans High Fidelity Loudspeakers—it contains informative articles, including advice on stereo, special beginners page, and full cabinet drawings. You'll find it interesting as well as informative.

The Perfect Combination  
**MAXAMP 30**

**TRANSISTORISED STEREOPHONIC HIGH FIDELITY AMPLIFIER 15 + 15 watts** · Silicon solid state Integrated pre-amplifier · Negligible distortion · **£54.0.0.**

**STEREOMAX**

**MATCHING AM/FM STEREOPHONIC FM TUNER**  
Transistorised · Outstanding specification · Stereo decoder (optional) · **£65.5.0 + £15.14.0 P.T.**

Both **MAXAMP 30** and **STEREOMAX** have polished wood cases (10 1/2" x 5 1/2" x 7 1/2" deep) in Teak or Walnut to order.

Full specifications of the Maxamp 30 and Stereomax are given in the High Fidelity Manual—send the coupon for your FREE copy—or pay an early visit to your Goodmans dealer.

**FREE** Please send Hi-Fi Manual together with name and address of my nearest Goodmans dealer.

Name .....

Address .....

PE11

## GOODMANS LOUDSPEAKERS LTD

AXIOM WORKS · WEMBLEY · MIDDLESEX. Tel: 01-902 1200

IT'S BARGAIN TIME AT



MORE TO CHOOSE FROM—LESS TO PAY

**IMPORTANT NEW AMPLIFIER  
T.R.S. STEREO 4-4**



5 transistor transformerless stereo amplifier with integrated pre-amp. A T.R.S. design based on newly developed Mullard 4 watt modules with EC108 pre-amp. Suitable also for speakers from 3 to 15 ohms. With bass and treble cut/boost. Response—60 to 14kHz  $\pm$ 3dB. This excellently engineered layout requires only wiring between controls and modules. Complete with metal chassis and simplex teak-ended cabinet for instant assembly. Stereo/Mono and Radio/PU switches. Amplifier Kit with Knobs, etc., £7.19.8 (p/p 3/6)  
**T.R.S. Power Unit £25.0** (p/p 2/6)  
**T.R.S. Simplex Cabinet, £117.8** (p/p 2/6)  
 4 pre-DIN plugs and sockets if purchased separately, 15/0. Complete kit inc. cabinet/power pack/DIN plugs and sockets  
**£12.10** (post free)

**T.R.S. STEREO FM TUNER**  
 Available shortly, this comes in prefabricated module form ready for instant and simple assembly. Excellent sensitivity, switchable APC, automatic stereo function, rugged construction and matching appearance with T.R.S. stereo 4-4. S.A.E. brings details.

**SINGLAIR IC-10**  
 This fantastically minute amplifier includes pre-amp in a 13 transistor circuit a twentieth of an inch square. Delivers 5 watts (10W peak). As advertised. With manual  
**59/6**  
**ALL SINGLAIR PRODUCTS IN STOCK AS ADVERTISED**

**GARRARD UNITS AND PLINTHS**  
**LM3000 Record Player with 9T.A. Stereo Cartridge.** £105.0

**AT.60 Mk. II De-luxe Auto-changer, die-cast turntable. Less cartridge.** £135.0  
**SP.25 De-luxe single record player, die-cast turntable. Less cartridge.** £119.8

Brand new in makers' cartons. Packing and carriage on any one of above 7/6.

**GARRARD PLINTH WB.1** In the Teak for any of above units. (Packing and carriage 5/-). 65/-  
**Garrard clear-view rigid perspex cover** (carriage 4/6), 82/8.

**CARTRIDGE OFFER TO PURCHASERS OF PLAYER UNITS—STEREO** Sonolone 9TA/MC Ceramic with diamond 45/6; Decca Deram with diamond 92/8; MONO Acos GP91-1 21/-; Goldring Mx2M 28/6.

**EMI 4 speed single player, 16in T/able with separate arm and T/O cartridge 69/6** (p. & p. 5/-).

**TAPE AND FREE WALLET OFFER**  
 With each reel of this fine tape by an internationally famous manufacturer we give a beautiful strongly made wallet in simulated leather with space for a reel each side. This is professional quality full frequency tape with metallised leader/stop foils. These library wallets solve once and for all the problems of efficient, tidy storage.  
 5 1/2in. reel, 1200ft. 17/6 5 1/2in. reel, 900ft. 12/6 with wallet.  
 7in. reel 1800ft. 22/6 TAPE REELS—7in., 2/8; with wallet, 5 1/2in.—2/-; 5in.—2/-; p. & p. 1/6 per reel 3in.—1/3 (p. & p. 6d.).

**LARGE STOCKS OF TRANSISTORS AND MIDGET RESISTORS AND CONDENSERS**  
**"DIP-KIT"** Adhesive copper strip, 5in reel, 1/2 in 2/-  
**VERBOBOARD** in all sizes.

**MONEY SAVING LISTS**  
 Eight large printed pages, packed with bargain offers including difficult to find lines. Send 6d. for latest copy.

**WHEN ORDERING**  
 Send cash with order. Post and packing where not stated add 1/- per 1lb; 1/9; 1lb; 3/6; 2lb; 5/-; 6d; 6/6; 10lb; 8/-; 14lb; over 10/-.

**TRS RADIO COMPONENT SPECIALISTS**

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY  
 Telephone: 01-684 2188  
 9 a.m.—6 p.m. daily  
 1 p.m. Weds.  
 A few minutes from Thornton Heath Stn. (S.R. Victoria Section)

**new  
VARI-STAT  
thermostatic  
soldering iron**

High Production Model D  
 Miniature Iron 50 watt  
 Voltage 12-250 volt  
 Weight 1 3/4oz.  
 "Screw on" Bit sizes 1/16in., 3/32in., 1/8in., 3/16in., 1/4in.  
 Our range also includes:  
 Standard Miniature Model 50W  
 Standard Instrument Model 70W  
 High Production Instrument Model 125W  
 Industrial Model 500W

PRICE  
**60/6**

All these irons give excellent bit and element life since the thermostat completely eliminates overheating and controls reserve heating capacity which makes possible continuous soldering without chilling of the bit. The consistent temperature makes these irons ideal for printed circuit work.

**CARDROSS ENGINEERING CO. LTD.,**  
 Woodyard Road, Dumbarton.  
 Phone: Dumbarton 2655

**NEW RANGE BBC 2 AERIALS**

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

**Loft Mounting Arrays, 7 element, 37/6; 11 element, 45/-; 14 element, 52/8; 18 element, 60/-; Wall Mounting with Cranked Arm, 7 element, 40/-; 11 element, 47/-; 14 element, 55/-; 18 element, 62/8; Mast Mounting with 2in. clamp, 7 element, 42/8; 11 element, 55/-; 14 element, 62/-; 18 element, 70/-; Chimney Mounting Arrays, Complete, 7 element, 72/8; 11 element, 80/-; 14 element, 87/6; 18 element, 95/-; Complete assembly instructions with every unit. Low Loss Cable, 1/6 yd. U.H.F. Pre-amps from 75/-. State clearly channel number required on all orders.**

**BBC · ITV AERIALS**

**BBC (Band 1). Telescopic loft, 25/-; External S/D, 36/-; "H", £2.15.0.**  
**ITV (Band 2). 3 element loft array, 30/-; 5 element, 40/-; 7 element, 50/-; Wall mounting, 3 element, 47/6; 5 element, 52/8.**  
**Combined BBC/ITV. Loft 1+3, 49/-; 1+5, 59/-; 1+7, 69/-; Wall mounting 1+3, 57/8; 1+5, 67/6; Chimney 1+3, 67/6; 1+5, 75/-.**  
**VHF transistor pre-amps, 75/-.**

**COMBINED BBC1-ITV-BBC2 AERIALS**  
 1+3+9, 70/-; 1+5+9, 80/-; 1+5+14, 90/-; 1+7+14, 100/-; Loft mounting only. Special leaflet available.

**F.M. (Band 2). Loft S/D, 15/-; "H", 32/8; 3 element, 55/-; External units available. Co-ax. cable, 8d. yd. Co-ax. plugs, 1/4. Outlet boxes, 5/-; Diplexer Crossover Boxes, 15/6. C.V.O. or C.O.D. P. & P. 5/-; Send 6d. stamps for illustrated lists.**

CALLERS WELCOME  
 OPEN ALL DAY SATURDAY

**K.V.A. ELECTRONICS (Dept. P.E.)**  
 27 Central Parade, New Addington  
 Surrey—CRO-01B  
 LODGE HILL 2266

**NEW BOOKS**

**SEPTEMBER**

- AM-FM-TV ALIGNMENT** by R. G. Middleton 30/-
- HANDBOOK OF ELECTRONIC CIRCUITS** by R.G.A. Service Co. 20/-
- PRACTICAL POWER-SUPPLY CIRCUITS** by John Potter Shields 24/-
- SYMFAC (R) GUIDE TO TV SERVICING** by the PF Reporter Editorial Staff 26/-
- TELEVISION TAPE FUNDAMENTALS** by Harold E. Ennes 40/-

**OCTOBER**

- ABC'S OF ELECTRICAL SOLDERING** by Louis M. Dezettel 18/-
- BENCH SERVICING MADE EASY 2nd Edition** by R. G. Middleton 26/-
- ELECTRICAL AND ELECTRONIC SIGNS AND SYMBOLS** by R. G. Middleton 35/-
- ELIMINATING ENGINE INTERFERENCE** by John D. Lenk 16/-
- TRANSISTOR SUBSTITUTION HANDBOOK 8th Edition** by the Howard W. Sams Engineering Staff 16/-

**NOVEMBER**

- TRANSISTOR FUNDAMENTALS VOL. 1 BASIC SEMICONDUCTOR AND CIRCUIT PRINCIPLES** by Robert J. Britte 35/-
- VOL 2 BASIC TRANSISTOR CIRCUITS** by Charles A. Pike 35/-
- VOL 3 ELECTRONIC EQUIPMENT CIRCUITS** by Martin Gersten 35/-
- VOL 4 DIGITAL AND SPECIAL CIRCUITS** by Reginald Peniston and Louis Schweitzer 35/-

**FOULSHAM-SAMS TECHNICAL BOOKS**

(W. FOULSHAM & CO. LTD.)  
 YEovil RD SLOUGH, BUCKS, ENGLAND

# LIMITED SPACECHARGE ACCUMULATION MODE

**LSA DEVICE**  
By B.T.G. Tan

A major breakthrough in electronics rivalling in importance that brought about by the transistor has been achieved by recent research on semiconductors. A whole new family of semiconductor devices is being developed, which will in time do for microwave electronics what the transistor has already done for the present-day application of electronics in the domestic and industrial fields. This important development depends on the ability of a semiconducting material, gallium arsenide, to emit microwaves when a voltage is applied to a slice of the material. This concluding article deals with negative resistance and the L.S.A. device used to overcome the problem of high frequency limitations.

LAST month we considered the properties of semiconductor materials and the theory behind the transistor. The high frequency limitation of the latter device was pointed out.

This month we introduce some comparatively new semiconductor devices which overcome these high frequency limitations and thus offer promise of further great advances in semiconductor technology.

## A NEGATIVE RESISTANCE DEVICE

The next semiconductor active device of major importance that came on the scene utilised the property of negative resistance.

Ordinary positive resistance is given by the voltage/current ratio for the current flow due to the voltage applied across a resistance. This would be given by the slope of a current-voltage graph as shown in Fig. 21a.

The characteristic of negative resistance on the graph shows a negative (downward) slope as in Fig. 21b, i.e. an increase in voltage resulting in a decrease in current.

Current is determined by the rate of flow of electric charge, so it depends both on the numbers and the velocities of the charge carriers as well as their charge. In normal positive resistance, the number  $n$  of charge carriers flowing in a circuit usually stays constant while their velocity increases regularly with increasing applied voltage, so that  $I$  increases with  $V$ .

If we could somehow decrease  $n$  with increasing  $V$  sharply enough, there will be a decrease in  $I$  and thus negative resistance will occur.

## THE TUNNEL DIODE


The tunnel diode, a negative resistance device working in this way, was invented in 1958 by a Japanese physicist, L. Esaki. It consists of a single  $pn$  junction in which the  $p$ - and  $n$ -type regions are very heavily doped. Thus the difference in levels on both sides is so great that the bottom of the conduction band in the  $n$ -type region is below the top of the valence band in the  $p$ -type region. This is illustrated in Fig. 22a.

Practically no electrons and holes can flow across the junction and the current is virtually zero. If the junction is biased forward very slightly, reducing the potential difference, the electrons still cannot run uphill into the  $p$ -type region as the potential difference is still very great. However, they are now brought into levels corresponding with those of the holes opposite them in the  $p$ -type region. These holes are nothing but absences of electrons.

By the laws of quantum physics, an electron in the  $n$ -type region is able to "tunnel" through the junction barrier into an empty electron level at the same height in the  $p$ -type region, i.e. a hole. This surprising effect is allowed a certain small probability by quantum physical laws.

As the number of electrons is so large, some of them do tunnel through and are able to constitute a current across the junction (see Fig. 22b). As the bias is increased, more electron and hole levels are brought opposite one another and the tunnel current increases, see Fig. 23.

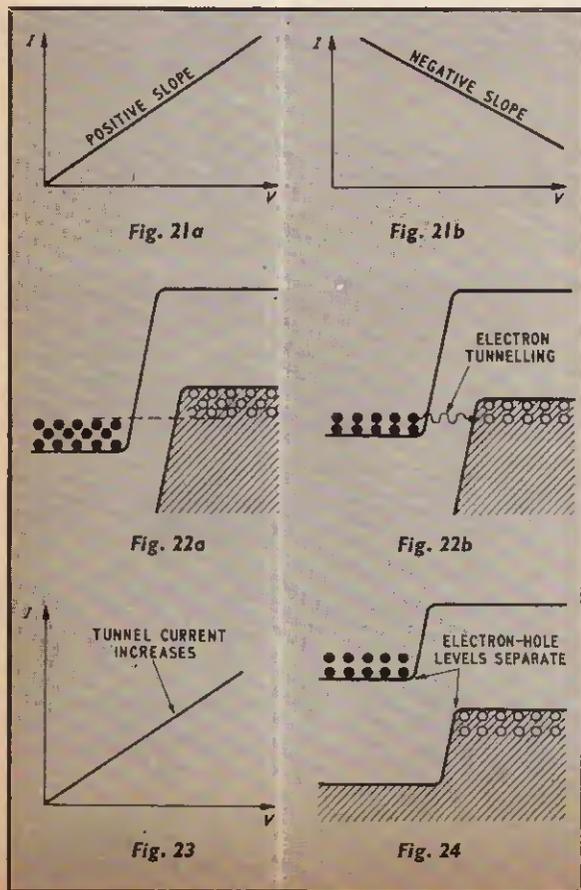As the bias is increased further, the electron and hole levels separate again, and the number of electrons able to tunnel across decreases (Fig. 24). The tunnel current thus decreases with increasing voltage.



The current-voltage graph thus has a negative slope and the junction exhibits negative resistance (Fig. 25). On increasing the bias still further, the junction begins to conduct an appreciable normal forward bias current.

Thus a tunnel diode with an appropriate bias applied to it will behave as a negative resistance. It can be used in an LC circuit to generate electrical oscillations (Fig. 26).

### SHORT TRANSIT TIME

The theoretical high frequency response of the tunnel diode should only be limited by the time taken for the electrons to tunnel through the junction. As the tunnelling is an extremely fast phenomenon, this transit time limitation is much less restrictive than that on the transistor, and thus it can work at much higher frequencies. Tunnel diodes can be operated in the lower frequency section of the microwave spectrum. However, the tunnel diode also has its own high frequency limitations.

Like all diodes, it has exposed net charges on either side of the junction. These charges are slightly affected by an external bias, and so the junction has a very small capacitance  $C_j$ , which must be added to the  $C$  in the LC circuit. The frequency of oscillation is now

$$1/[2\pi\sqrt{L(C + C_j)}]$$

Thus no matter how small we make  $L$  or  $C$ , the junction capacitance will always impose an upper limit on the frequency of oscillation of the resonant circuit.

However, the tunnel diode is a significant advance on the transistor as a high frequency active device. It has two layers and one junction compared with three layers and two junctions of the transistor, which is a reduction in complexity. Gallium arsenide (GaAs) devices do not depend at all on junction effects for their functioning. Their negative resistance is purely a property of their bulk material, and depends only on the behaviour of the charge carriers in the bulk material.

### THE NEGATIVE RESISTANCE PROPERTY OF GaAs

The negative resistance of gallium arsenide depends not on a decrease in  $n$  with an increase of voltage, but a decrease in velocity, with  $n$  remaining constant. When an  $n$ -type GaAs slice is biased to a certain voltage, a further increase in voltage will result in a decrease in the velocity of the electrons. Since it is the electric field (voltage per unit length) across the slice that matters rather than the voltage, a graph of the velocity of the electrons against the applied electric field must be plotted and is shown in Fig. 27.

When the field across the GaAs slice is above about 3,000 volts per centimetre, it starts to exhibit negative resistance, as the current across the slice will decrease due to the decreasing velocity with increasing electric field, i.e. voltage across the slice. A decrease in the velocity of the electrons means that less charge will flow across the slice in a given time, i.e. less current will flow.

### THE FIRST GaAs OSCILLATOR

The first GaAs active device functioning as a negative resistance oscillator was discovered by J. B. Gunn in 1964 while he was doing research on the high field properties of semiconductors. A rod of GaAs when biased above 3kV/cm began oscillating electrically and also emitted microwaves, the oscillations being at microwave frequencies.

H. Kroemer then put forward the explanation that the GaAs rod was acting as an oscillator because of its negative resistance property. Kroemer drew attention

to the fact that three British physicists, B. K. Ridley, T. B. Watkins and C. Hilsum, had hitherto predicted that GaAs would show the property of negative resistance under these conditions.

### FUNDAMENTAL THEORY

To understand why GaAs exhibits negative resistance, it is necessary to refer to fundamental semiconductor physics. Our previous energy level diagrams (see Part 1) only show the energy values of the electrons in a semiconductor, the horizontal axis simply standing for the physical dimensions of the semiconductor bulk.

An energy level diagram can be drawn to show both the energy and momentum of the electrons in the conduction band (Fig. 28a). In this diagram, the horizontal axis stands for the momentum of the electrons. An electron in the conduction band must lie on the curved line, i.e. it can only have the simultaneous values of energy and momentum that the points on the line have. This is because the energy and momentum of a moving object are closely related. This relation involves the mass of the object.

Now, as the electron moves in the semiconductor, its movement is affected by the positive charges of the atomic nuclei in the semiconductor. Thus it does not move in quite the same way as a free electron in space. The effect of these nuclei on the electron can be taken into account by considering the electron as having an effective mass quite different from its actual mass. The

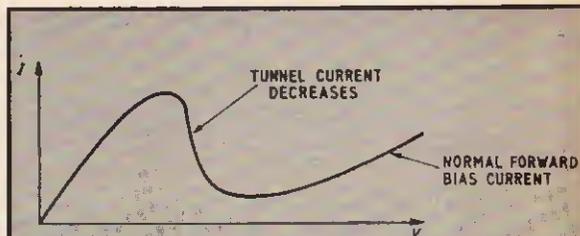


Fig. 25

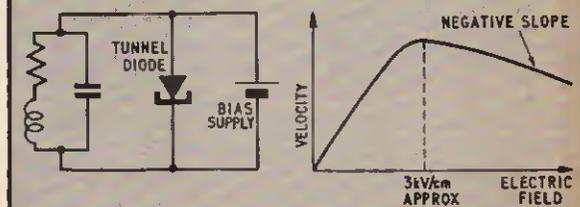


Fig. 26

Fig. 27

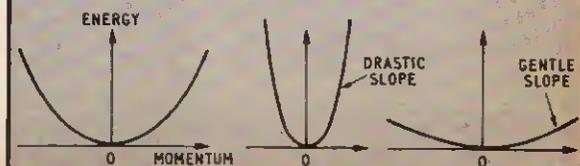


Fig. 28a

Fig. 28b

Fig. 28c

## DRY JOINT TESTER

The most reliable way of testing for a dry joint is to measure the resistance between the component lead and the printed circuit board. Our kit for doing this comprises a large scale (3in.) moving coil meter, a variable resistance for adjusting zero setting, and a wiring diagram with instructions. The only additional items you will need are a battery, some wire, a pair of test rods. Price 19/8. Postage and insurance 2/6.

## FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Galux" tubes for fish tanks and indoor plants. Chokes are super-bright, mostly brass filled. Kit A—10-20W, 19/8. Kit B—30-40W, 19/6. Kit C—50W, 19/8. Kit D—125W, 22/- . Kit E—65W, 19/6. Kit MF1 is for 6in., 9in. and 12in. miniature tubes 19/6. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kit MF1 3/6 on first kit then 3/6 on each two kits ordered.

## REED-SWITCH

Suitable for dozens of different applications, such as burglar alarms, conveyor belt switching. These are simply glass in cased switches which can be operated by a passing permanent magnet coil. A special buy enables us to offer these at 2/6 each, or 24/- a dozen. Suitable magnets are 1/- each.

## MINIATURE WAFER SWITCHES

4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—2 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 3/6 each, 36/- dozen, your assortment.

## WATERPROOF HEATING ELEMENT

25 yards length 70W. Self-regulating temperature control. 10/- post free.

## BLANKET SWITCH

Double Pole with neon let into side so it is luminous in dark. Ideal for dark room light, or use with waterproof element—blue plastic case. 5/6 each.

## BLANKET SIMMERSTAT

Although looking like, and fitted as an ordinary blanket switch, this is in fact a device for switching the blanket on for varying time periods, thus giving a complete control from off to full heat. Also, suitable for controlling the temperature of any other appliances using up to 1 amp. Listed at 27/6 each, we offer these while our stock lasts at only 12/6 each.

## PHOTO-ELECTRIC KIT

All parts to make light operated switch/burglar alarm/counter, etc. Kit comprises printed circuit, Laminated Boards and chemicals, Latching relay, Infra-red sensitive Photocell and Hood, 2 Transistors, cond., Terminal Block, Plastic case, Essential data, circuits and P.C. chassis plans of 10 photo-electric device including auto. car parking light, modulated light alarm. Simple invisible ray switch—counter—stray light alarm—warming tone electronic alarm—projector lamp stabiliser, etc. Only 39/6, plus 2/- post and insur.

PP3 Eliminator. Play your pocket radio from the mains! Save 2s. Complete component kit comprises 4 rectifiers—mains dropper—resistor—smoothing condenser and instructions. Only 6/6 plus 1/- post.

## THERMOSTATS

Type "A" 15A for controlling room heaters, greenhouse, air conditioning. Has spindle for pointer knob. Quicker adjustable from 50-80°/6, plus 1/- post. Suitable box for wall mounting, 5/- F. & P. 1/-.

Type "B" 15A. This is a 17in long rod type made by the famous Suavio Co. Spindle adjustable from 50-550°F. Internal screw alters the setting so this could be adjustable over 30° to 1,000°F. Suitable for controlling furnace,

oven kiln, immersion heater or to make flame-start, or fire alarm, 8/6, plus 2/6 post and insurance.

Type "D". We call this the Ice-stat as it cuts in and out at around freezing point, 2/3 amps. Has many uses one of which would be to keep the 10ft. pipes from freezing. If a length of our blanket wire (16 yds. 10/-) is wound round the pipes, 7/6, F. & P. 1/1.

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature, 7/6, plus 1/- post.

Type "F". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks—thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developers an chemical baths of all types. Adjustable over range 50° to 150°F. Price 18/-, plus 2/- post and insurance.

## HI-FI BARGAIN


**FULL FI 12 INCH LOUDSPEAKER.** This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of this country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S.—Cone Moulded fibre—Freq. response 30-10,000c/s—Main resistance 80c/s—Chassis Diam. 12in.—12in. over mounting holes—Baffle hole 11in. Diam.—Mounting holes 4, holes—1in. diam. on pitch circle 1 1/2in. diam.—Overall height 8 1/2in. A 28 speaker offered for only 28/8 plus, plus 7/6 P. & P. Specify three or fifteen ohms. Don't miss this offer.



## BARGAIN OF THE YEAR
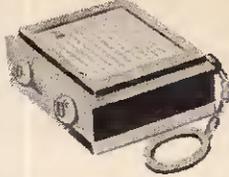
### MICRO-SONIC

7 transistor Key chain loudspeaker Radio in very pretty case, size 2 1/2 x 2 1/2 x 1 1/2in—complete with soft leather zipped bag. Specification: Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1800kc/s. Sensitivity: 50mV/meter. Intermediate frequency: 455kc/s, or 450kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. 19/6 plus 2/6 post and ins., less batteries. A pair of rechargeable everlasting batteries 7/- pair.




## YOU NEVER NEED BUY ANOTHER BATTERY

For your transistor radio. Stupendous offer this month—a Nickel Cadmium battery stock together with a mains operated charger which you mount on the back of your set. The mains flex unplugs so the set remains completely portable. Offered for less than the cost of the batteries alone. ONLY 29/6, plus 3/8 post.
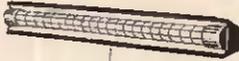
## INFRA-RED HEATERS

Make up one of these latest type heaters. Ideal for bathroom, etc. They are simple to make from our easy-to-follow instructions—uses silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watt element, all parts, metal casing as illustrated, 19/6, plus 4/8 post and insurance. Full switch 3/- extra.



## THIS MONTH'S SNIP

### BREAKDOWN PARCEL

This unit is really an army telephone less hand-set. It contains the following useful items:

1. Hand operated magneto generator which will light lamps, generate shocks, etc.
2. Magneto bell, which will work with above generator or from the mains through a step down transformer.
3. Morse Tapper.
4. A very sensitive change-over relay which will operate from 1 1/2V upwards.
5. A useful assortment of components comprising switches, jack-sockets, matching transformers, chokes, tag-strips, etc. Price 14/6 plus postage and insurance 6/6.

## PROTECT VALUABLE DEVICES

### FROM THERMAL RUNAWAY OR OVERHEATING:

Thyristors, rectifiers, transistors etc. which use heat-sinks can easily be protected; simply make the contact thermostat part of the heat-sink. Motors and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90-100°F or with the dial removed range setting is between 80 and 300°F. Price 10/-.



## DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions, 19/8 plus 2/6 post and insurance. Or available made up 25/-, plus 2/6 post.




## 16 R.P.M. GEARED MOTOR

Made by Smiths Electric, these are almost silent running, but are very powerful. They operate from normal to 240V mains and the final shaft speed is 16 r.p.m. 15/- . Post and ins. 2/6.
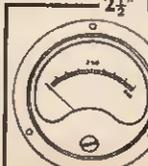
## 2 1/2" MOVING COIL METER

Meters are always being needed and they are jolly costly when you have to buy them in a hurry. So it's sensible to take advantage of this offer: 2 1/2in. (3in. o.d.) flush mounting moving coil meter, only 8/6 each. These are scaled 0-300mA but once the internal shunt is removed the f.s.d. is usually about 10mA so you can make it into almost anything by adding shunts or series resistors. These are Ex. W.D. of course but are all new and unused. Price only 8/6 each plus 2/6 post. 12 or more post free.



## MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6V, 8V, 12V for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 19/6, plus 3/8 postage.

## CASSETTE LOADED DICTATING MACHINE

Battery operated and with all accessories. Really fantastic offer a British made 231 outfit for only 28/19/6, brilliantly designed for speed and efficiency—cassette takes normal spools drops in and out for easy loading—all normal functions—accessories include: stethoscopic earpiece—crystal microphone has on/off switch—telephone pick-up—tape reference pad—DON'T MISS THIS UN-REPEATABLE OFFER—SEND TODAY, 28/19/6 plus 7/6 post and insurance. Footswitch 18/6 extra. Spare Cassettes at 7/6 each, three for 21. See in the Dark **INFRA-RED BINOCULARS**



These infra-red binoculars when fed from a high voltage source will enable objects to be seen in the dark, provided the objects are in the rays of an infra-red beam. Each eye tube contains a complete optical lens system as well as the infra-red cell. These optical systems can be used as lenses for TV cameras—light cells, etc. (details applied). The binoculars form part of the Army night driving (Tabby) equipment. They are unused and believed to be in good working order but sold without a guarantee. Price 23.17.6, plus 10/- carr. and ins. Handbook 2/6.

## Be first this year

### SEE AND PLANT RAISING


Soil heating wire and transformer. Suitable for standard size garden frame. 19/6, plus 3/6 post and ins.

### GANGED POTS

Standard type and size with good length of spindle—made by Morganite. List price is 10/- each but if you act quickly you can have them at 12/- doz. (or 1/6 each if less than doz.). Following valves in stock all "in"—10K—10K—100K—100K—500K—500K all new and unused. Post 2/6 on 1st doz. then 1/- per doz. 6 doz. or more post free.
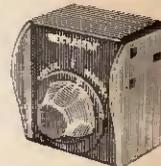
## BECKASTAT

This is an instant thermostat, simply plug your appliance into it and its lens into wall plug. Adjustable setting for normal air temperatures. 13 A loading. Will save its cost in a season. 19/6, Postage and ins. 2/9.



## TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 7/6 each.

## MAINS RELAYS

Type A 210/250V AC coil, 2 types, one for single whole chassis mounting, has 3 pairs heavy duty changeover contacts. 8/6 each.  
Type B in clear plastic case on tin base, plugs into oval valve holder. 2 pairs changeover contacts. 12/6 each.

Where postage is not definitely stated as an extra then orders over £3 are post free. Below £3 add 2/6. Semi-conductors add 1/- post. Over 21 post free. S.A.E. with enquiries please.

# ELECTRONICS (CROYDON) LIMITED

(Dept. P.E.) 266 LONDON ROAD, WEST CROYDON, CRO 2TH  
also at 102/3 TAMWORTH ROAD, CROYDON, SURREY

# DUXFORD ELECTRONICS (PE)

## 97/97A MILL ROAD, CAMBRIDGE

(Visit us—at our new Mail Order, Wholesale & Retail Premises)

**MINIMUM ORDER VALUE 5/-**

C.W.O. Post and Packing 1/-

**DISCOUNT 10% over £2  
15% over £5**

**CERAMIC DISC CAPACITORS (Hunts).** 500V  $\pm 20\%$ ; 100, 220, 330pF. -20%, +80%; 470, 680, 1,000pF. 5d each.

**ELECTROLYTIC CAPACITORS (Mullard).** -10% to +50%.

Subminiature (all values in $\mu$ F)						
4V	3	32	64	125	250	400
6.4V	6.4	25	50	100	200	320
10V	4	16	32	64	125	200
16V	2.5	10	20	40	80	125
25V	1.6	6.4	12.5	25	50	80
40V	1	4	8	16	32	50
64V	0.64	2.5	5	10	20	32
Price	1/6	1/3	1/2	1/-	1/1	1/2

Small (all values in $\mu$ F)					
4V	800	1,250	2,000	3,200	
6.4V	640	1,000	1,600	2,500	
10V	400	640	1,000	1,600	
16V	250	400	640	1,000	
25V	160	250	400	640	
40V	100	160	250	400	
64V	64	100	160	250	
Price	1/6	2/-	2/6	3/-	

**POLYESTER CAPACITORS (Mullard)**  
 Tubular, 10%, 160V: 0-01, 0-015, 0-022 $\mu$ F, 7d. 0-033, 0-047 $\mu$ F, 8d. 0-068, 0-1 $\mu$ F, 9d. 0-15 $\mu$ F, 11d. 0-22 $\mu$ F, 1/- 0-33 $\mu$ F, 1/3. 0-47 $\mu$ F, 1/6. 0-68 $\mu$ F, 2/3. 1 $\mu$ F, 2/8.  
 400V: 1,000, 1,500, 2,200, 3,300, 4,700pF, 6d. 6,800pF, 0-01, 0-015, 0-022 $\mu$ F, 7d. 0-033 $\mu$ F, 8d. 0-047 $\mu$ F, 9d. 0-068, 0-1 $\mu$ F, 11d. 0-15 $\mu$ F, 1/2. 0-22 $\mu$ F, 1/6. 0-33 $\mu$ F, 2/3. 0-47 $\mu$ F, 2/8.  
 Modular, metallised, P.C. mounting, 20%, 250V: 0-01, 0-015, 0-022 $\mu$ F, 7d. 0-033, 0-047 $\mu$ F, 8d. 0-068, 0-1 $\mu$ F, 9d. 0-15 $\mu$ F, 11d. 0-22 $\mu$ F, 1/- 0-33 $\mu$ F, 1/3. 0-47 $\mu$ F, 1/8. 0-68 $\mu$ F, 2/3. 1 $\mu$ F, 2/9.

**POLYSTYRENE CAPACITORS:** 5%, 160V (unencapsulated): 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820pF, 5d. 1,000, 1,500, 2,200pF, 6d. 3,300, 4,700, 5,600pF, 7d. 6,800, 8,200, 10,000pF, 8d. 15,000, 22,000pF, 9d. 1%, 100V (encapsulated): 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820pF, 1/- 1,000, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900pF, 1/3. 4,700, 5,000, 5,600, 6,800, 8,200, 10,000, 12,000, 15,000pF, 1/6. 18,000, 22,000, 27,000, 33,000, 39,000pF, 1/9. 0-047, 5,000, 0-056 $\mu$ F, 2/- 0-068, 0-082, 0-1 $\mu$ F, 2/3. 0-12 $\mu$ F, 2/9. 0-15, 0-18 $\mu$ F, 3/- 0-22 $\mu$ F, 4/- 0-27, 0-33 $\mu$ F, 5/- 0-39 $\mu$ F, 5/9. 0-47, 0-5 $\mu$ F, 6/3.

**JACK PLUGS (Screened):** Heavily chromed,  $\frac{1}{2}$ in Standard: 2/9 each. Side-entry: 3/3 each. Standard (Unscreened): With L, K, grey, white, red, blue, green or yellow covers, 2/3 each.

**JACK SOCKETS ( $\frac{1}{2}$ in Plug):** With black or white bezel and chrome nut, 2/9 each. Available with: Break/Break, Make/Break, Break/Make, Make/Make contacts.

**POTENTIOMETERS (Carbon):** Long life, low noise,  $\frac{1}{2}$ W at 70°C.  $\pm 20\% \leq \pm M$ ,  $\pm 30\% > \pm M$ . Body dia.,  $\frac{1}{2}$ in. Spindle, 1in  $\times$   $\frac{1}{2}$ in. 2/- each. Linear: 100, 250, 500 ohms, etc., per decade to 10M. Logarithmic: 5k, 10k, 25k, etc., per decade to 5M.

**SKELTON PRE-SET POTENTIOMETERS (Carbon):** Linear: 100, 250, 500 ohms, etc., per decade to 5M. Miniature: 0-3V,  $\pm 20\% \leq \pm M$ ,  $\pm 30\% > \pm M$ . Horizontal (0-7in  $\times$  0-4in P.C.M.) or Vertical (0-4in  $\times$  0-2in P.C.M.) mounting, 1/- each. Submin. 0-1W at 70°C.  $\pm 20\% \leq \pm M$ ,  $\pm 30\% > \pm M$ . Horizontal (0-4in  $\times$  0-2in P.C.M.) or Vertical (0-2in  $\times$  0-1in P.C.M.) mounting, 10d each.

**RESISTORS (Carbon film), very low noise. Range: 5%, 4-7% to 1M $\Omega$  (E24 Series); 10%, 10 $\Omega$  to 10M $\Omega$  (E12 Series).  $\frac{1}{2}$ W (10%), 1 $\frac{1}{2}$ d (over 99, 1 $\frac{1}{2}$ d), 100 off per value 12/-  $\frac{1}{2}$ W (5%), 2d (over 99, 1 $\frac{1}{2}$ d), 100 off per value 13/9.  $\frac{1}{4}$ W (10%), 2d (over 99, 1 $\frac{1}{2}$ d), 100 off per value 13/9.  $\frac{1}{4}$ W (5%), 2 $\frac{1}{2}$ d (over 99, 2d), 100 off per value 15/6.**

**SEMICONDUCTORS:** OA5, OA81, 1/9. OC44, OC45, OC71, OC81, OC81D, OC82D, 2/- OC72, 2/3. OC170, OC171, 2/6. AF115, AF116, AF117, 3/- OC73, 3/3. OC140, 4/3.

**SILICON RECTIFIERS (0-5A):** 170 P.I.V., 2/9. 400 P.I.V., 3/- 800 P.I.V., 3/3. 1,250 P.I.V., 3/9. 1,500 P.I.V., 4/-

**SWITCHES (Chrome finish, Silver contacts):** 3A 250V, 6A 125V. Push Buttons: Push-on or Push-off (with white, black, green or red buttons) 5/- Toggle Switches: SP/ST, 3/3. SP/DT, 3/6. SP/DT (with centre position) 3/9. DP/ST, 4/3. DP/DT, 5/-

**PRINTED CIRCUIT BOARD (Verob).**  
 0-15in Matrix: 3 $\frac{1}{2}$ in  $\times$  2 $\frac{1}{2}$ in, 3/3. 5 $\frac{1}{2}$ in  $\times$  2 $\frac{1}{2}$ in, 3/11. 3 $\frac{1}{2}$ in  $\times$  3 $\frac{1}{2}$ in, 3/11. 5in  $\times$  3 $\frac{1}{2}$ in, 5/6.  
 0-1 Matrix: 3 $\frac{1}{2}$ in  $\times$  2 $\frac{1}{2}$ in, 4/- 5in  $\times$  2 $\frac{1}{2}$ in, 4/6. 3 $\frac{1}{2}$ in  $\times$  3 $\frac{1}{2}$ in, 4/6. 5in  $\times$  3 $\frac{1}{2}$ in, 5/3.

**RECORDING TAPE (Finest quality MYLAR—almost unbreakable).**  
 Standard Play: 5in, 600ft, 7/6. 5 $\frac{1}{2}$ in, 850ft, 10/6. 7in, 1,200ft, 12/6. Long Play: 3in, 225ft, 4/- 5in, 900ft, 10/6. 5 $\frac{1}{2}$ in, 1,200ft, 13/- 7in, 1,800ft, 18/-

Send S.A.E. for May, 1968 Catalogue

ERSIN



for quick,  
easy, reliable  
soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required. Ersin Multicore Savbit Alloy also reduces wear of copper soldering iron bits.



**SIZE 5  
HANDY  
SOLDER  
DISPENSER**

Contains 10 ft. coil of 18 s.w.g. Ersin Multicore Savbit Alloy, 2/6 each.



**SIZE 15  
SOLDER  
DISPENSER**

Contains 21 ft. coil of 60/40 Alloy, 22 s.w.g. Ideal for small components, transistors, diodes, etc. 3/- each.



**SIZE 12**

Ideal for home constructors. Contains 90 ft. of 18 s.w.g. Ersin Multicore Savbit Alloy on a plastic reel. 15/- each.



**BIB MODEL 8  
WIRE STRIPPER  
AND CUTTER**

Strips insulation cleanly and quickly, fitted with unique 8 gauge wire selector. Plastic handles. 9/6 each.



From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

**NEW PREMISES  
INCREASED RANGE OF  
COMPONENTS**

**LARGER AND MORE CONCISE  
HANDBOOK**

**EITHER WRITE,**

**TELEPHONE or CALL to . . .**

**STUDENT ELECTRONIC SERVICES**

**196 Regent Road, Salford 5, Lancs.**

**Tel. 061-872 5187**

difference between the effective mass and the actual mass varies with different semiconductors and also with the energy levels of the electron.

Considering the movement of an electron in a semiconductor, using its effective mass instead of its actual mass, the effect of the atomic nuclei on the electron can be taken into account automatically. The effective mass of an electron at any point on the energy-momentum diagram is related to the slope of the curve at that point.

Thus in a semiconductor, whose energy-momentum diagram looks like that in Fig. 28b, the effective masses of the electrons at the bottom of the conduction band is less than those at the bottom of the conduction band of a semiconductor with an energy-momentum diagram of gentler slope like that in Fig. 28c.

### ENERGY-MOMENTUM CURVE

Gallium arsenide has an energy-momentum curve with a drastic slope (Fig. 28b). The electrons at the bottom of the conduction band have a small effective mass.

Now, GaAs also has secondary curves of gentler slope higher up in its energy-momentum diagram (Fig. 29a). If we apply a voltage to a GaAs slice, the electrons having a small effective mass are easily moved and the current across the slice increases. As they are accelerated by the voltage, they gain energy and they rise up the curve on the diagram. We show the rise only on one side of the momentum axis as they are accelerated and gain momentum only in one direction—that due to the applied voltage.

As they approach the levels of the secondary curve, they begin to get transferred to the energy levels there. This is because the energy levels there are much more numerous than the energy levels on the main curve at the same height (Fig. 29b).

Once they are on the bottom of the secondary curve, their effective masses are much larger as the slope of the secondary curve is much gentler. As a result, their velocity decreases, since an object with a large mass is harder to move than an object with a small mass. As we further increase the voltage, more and more electrons get transferred to the secondary curve and the overall velocity of the electrons decreases. The velocity-electric field curve thus has a negative slope (Fig. 30).

The electron current will thus decrease with increasing applied voltage, and the GaAs slice exhibits negative resistance.

### THE GUNN EFFECT

A slice of gallium arsenide when biased into the negative resistance region should be able to generate electrical oscillations when put into an LC circuit.

When Gunn observed the oscillations in the GaAs rod, what was actually happening was that the rod itself and its mounting made up its own LC circuit and thus oscillated at a frequency determined by its own physical dimensions. As the oscillations were at microwave frequencies, the rod radiated the oscillating electrical energy in the form of electromagnetic waves. This is because a circuit element carrying an oscillation will radiate more and more electromagnetic energy as the wavelength of the oscillation decreases and becomes comparable to the physical dimensions of the element. This is a fundamental of aerial theory.

This microwave emission phenomenon from GaAs was called the Gunn Effect after its discoverer.

### ELECTRON BUNCHING


In the Gunn Effect, it was later found that when the GaAs rod is biased into the negative resistance region, and begins to emit microwaves, a bunch of electrons collects at one end of the rod near the contact and travels to the other end. As soon as it reaches the other end, another bunch forms at the first end and the process repeats itself. This occurred in step with the oscillations; in fact, it seemed to determine the frequency of the oscillations.

The electrons in the rod when it is in the negative resistance region do not behave like normal electrons in a normal positive resistance material. In a positive resistance material a bunch of electrons will be dispersed in a short time. In a negative resistance material, as the electrons travel along in the material due to the voltage applied to the material, any slight bunching up leads to a greater accumulation of electrons. This is because the bunching up creates a higher field in the area of the bunch due to the electrons' own charges.

This higher field affects the electrons in and near the bunch, which then slow down because of the negative velocity-field slope. Thus instead of dispersing, a further accumulation of electrons takes place and what is known as a domain forms and travels across the rod.
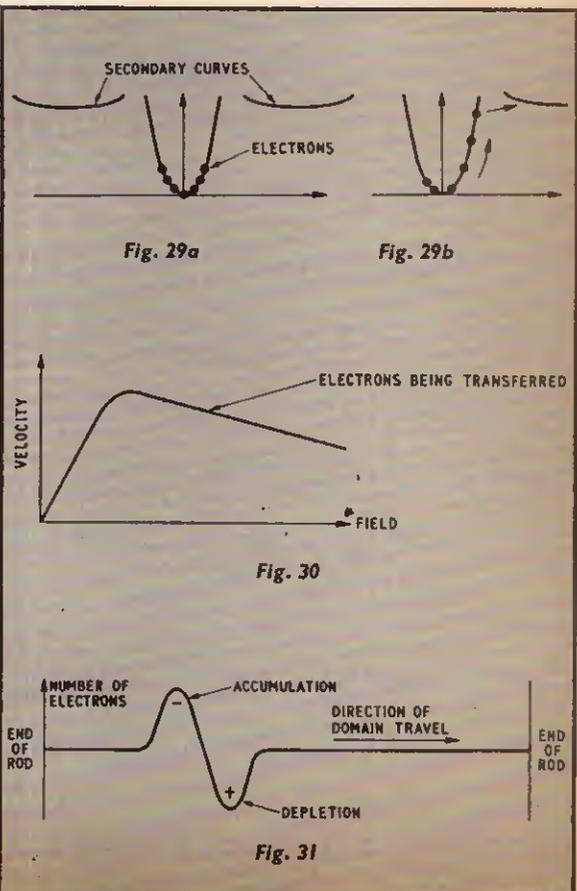
### DOMAIN FORMATION

The actual nature of the domain is an accumulation of electrons preceded by a layer depleted of electrons. The overall number of electrons in the rod remains the same (Fig. 31).



The result of this domain formation and travel is to limit the high frequency response of the device. The frequency of the oscillations is tied to the transit-time of the domain across the rod. The domains will always form since natural inhomogeneities in the GaAs will always result in unevenness in the electron distribution in the rod. This unevenness is most pronounced at the end of the rod where the electrical contacts are made, so that the domains form at the ends. Only one domain is sustained at a time; as the domain consists of electrons, it travels under the influence of the applied field to the other end of the rod. Another domain then forms at the first end and repeats the process.

### EFFECTIVE CAPACITANCE

We may look at the high frequency limitation of the Gunn Effect device from another angle. The domain consists of a layer of accumulated electrons having a negative charge relative to the rest of the rod, and a depleted layer having a net positive charge. This is like a charged capacitor because the accumulated charge depends on the external applied field.

Thus like the tunnel diode, the Gunn Effect device is frequency-limited by this effective capacitance. However, it is able to oscillate in the microwave region of the electromagnetic spectrum.

### THIN SLICES BY EPITAXIAL GROWTH

Clearly then, the high frequency microwave response is limited by the formation of the domains. In practice, the frequency limit is pushed up by making the domain transit-time as short as possible. This is done by making the distance between the contacts as short as possible, and thin slices of gallium arsenide and not rods are used as microwave oscillators.

These slices are formed by a process known as epitaxial growth, which also gives layers of the very high purity required for this purpose. Thin films of GaAs are deposited onto a heavily doped GaAs substrate which serves as one contact. A further thin film of heavily doped GaAs is deposited on the working layer to serve as the other contact (Fig. 32).

Microwaves of up to about 30GHz have been emitted from such devices. However, the restriction on the thickness of the slice limits the power capability of the device. As higher frequencies are reached by using thinner layers, the power output drops sharply.

### THE LSA MODE

Since the frequency limitation is imposed by the moving domains, could we not get rid of them? If we could, such a GaAs slice would be able to function as a pure negative resistance device in an oscillator circuit.

J. E. Carroll, in early 1966, found that by putting a Gunn Effect device in a suitable circuit, the domain could be extinguished before it reached the other end. In the middle of 1966, M. W. Kennedy discovered that he could make a Gunn Effect device oscillate at a frequency far in excess of its usual one determined by the domain transit-time. J. A. Copeland then demonstrated theoretically and experimentally that in this case, the domains were being prevented from forming at all.

Here at last was the major breakthrough. The GaAs was now being used as a pure negative resistance oscillator, Fig. 33a, and the frequency of oscillations was determined by the external LC circuit (actually a cavity at microwave frequencies).

How were the domains prevented from forming? They form only when the GaAs is in the negative resistance region of the velocity-field curve. The GaAs slice was put in a resonating circuit and biased into the negative resistance region. A load impedance in the circuit was of such a value that the oscillating voltage across the load was large enough to bring the voltage bias across the GaAs slice at one end of each oscillatory swing into the positive resistance section of the velocity-field diagram (Fig. 33b).

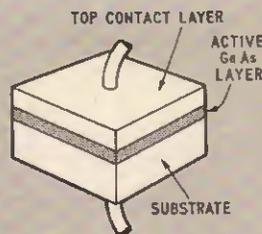


Fig. 32

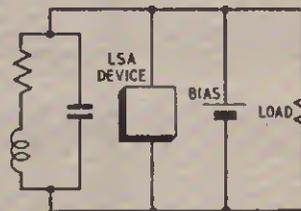


Fig. 33a


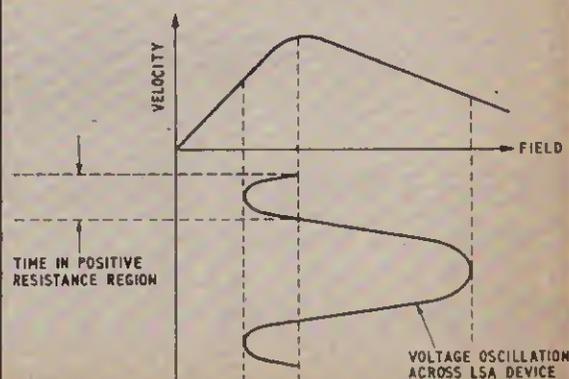


Fig. 33b
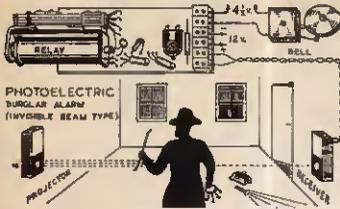
# PHOTOELECTRIC KIT

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Phototransistor, Latching Relay, 2 Transistors, Condenser, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



## PHOTOELECTRIC KIT 39/6

Postage & Pack. 2/6 (UK)  
Commonwealth:  
SURFACE MAIL 3/6  
AIR MAIL £1.00  
Australia, New Zealand,  
S. Africa, Canada & U.S.A.  
Also Essential Data Circuits  
and Plans for Building

12 PHOTOELECTRIC PROJECTS. (1) Steady-Light Photo-Switch/Alarm, (2) Modulated-Light Alarm, (3) Long-Range Stray-Light Alarm, (4) Relay-Less Alarm, (5) Warbling-Tone Alarm, (6) Closed-Loop Alarm, (7) Projector Lamp Stabiliser, (8) Electronic Projector Modulator, (9) Mains Power Supply, (10) Car Parking Lamp Switch, (11) Automatic Headlamp Dipper, (12) Super-Sensitive Alarm.

## INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1, Invisibile-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.  
CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack. 1/6 (UK). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

## JUNIOR PHOTOELECTRIC KIT

Versatile Invisibile-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.  
CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc., Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs".  
Price 19/6. Postage and Pack. 1/6 (UK). Commonwealth 2/-; Air Mail 4/-.

## JUNIOR OPTICAL KIT


CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build a miniature invisibile beam projector and photocell receiver. Price 10/6. Postage and Pack. 1/6 (UK). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

# PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS ON A PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4 1/2" x 2 1/2". (2) 1 Board for Matchbox Radio, (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet Printed Circuits for Amateurs. (9) 2 Miniature Radio Diets SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS.

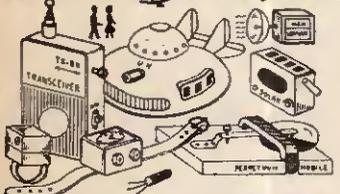A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.



## EXPERIMENTER'S PRINTED CIRCUIT KIT 8/6

Postage & Pack. 1/6 (UK)  
Commonwealth:  
SURFACE MAIL 2/-  
AIR MAIL 8/-  
Australia, New Zealand,  
South Africa, Canada

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRIFLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1-62" x 9-5" x 2-5". (11) Wristwatch Radio 1-15" x 8-0" x 5-5". (12) Ring Radio 7-0" x 7-0" x 5-5". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P.P. Amplifier. (16) Intercom. (17) I-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Alarm, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Wire-less Door Bell. (33) Ultrasonic Switch/Alarm. (34) Stereo Preamplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.

## YORK ELECTRICS

333 YORK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

# R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, WELLFIELD RD., S.W.16  
Special 24 Hour Mail Order Service

AZ11	9/6	KT67	46/-	UCH42	10/6	12Q7GT	4/6	2N2904A	12/6	GEX841	15/-
BY100	5/6	KT81(7CS)	10/6	UCH91	8/6	20L1	17/-	2N2996	5/6	GEX841	15/-
CU	20/6	KT81(7CS)	10/6	UCH92	10/6	20P4	19/-	2N2996	5/6	GEX841	15/-
DAF91	4/6	KT61(GEC)	3/6	UCH93	10/6	20P4	19/-	2N2996	5/6	GEX841	15/-
DAF91	4/6	KT61(GEC)	3/6	UCH94	10/6	25Z4	8/3	28008	12/-	GJRM	3/6
DAF96	6/9	KT88	27/6	UF89	7/6	26Z5GT	7/6	28004	11/-	GJM	3/6
DC90	7/6	KTW61	10/6	UL41	9/6	25Z6GT	8/6	28006	4/6	HD2987	4/-
DF91	3/6	KTW62	10/6	UL84	7/6	30C16	13/6	28006	2/6	HG6002	4/-
DF96	6/9	KT64	17/6	UX41	7/6	30C17	14/-	28012	5/6	JKDA	22/6
DE91	5/6	PC86	11/6	VF48	25/6	30C18	13/6	28018	5/6	JKDA	15/-
DE91	5/6	PC86	11/6	VF48	25/6	30F11	16/-	28018	6/6	JK10B	15/-
DE92	8/6	PC88	11/6	VR100/30	5/6	30FL12	16/-	28018	6/6	JK19A	22/6
DE96	7/9	PC87	8/9	VR100/30	5/6	30FL12	16/-	28018	6/6	JK12A	12/6
DL66	18/-	PC900	9/6	W31	6/6	30PL14	13/6	28301	12/6	K835A	5/-
DL92	6/9	PC94	9/3	W65	15/-	30L15	15/3	28320	9/3	MAT10	8/6
DL96	6/9	PC99	11/-	Z319	25/6	30L17	14/-	28702	13/6	MAT10	7/9
DL96	7/6	PC189	11/6	Z709	23/6	30L19	12/-	45L	4/6	NKT128	6/-
DL910	12/6	PCF80	7/6	Z800U	23/6	30P19	13/6	AC107	10/6	NKT142	8/-
DL916	30/-	PCF86	9/6	OA2	6/3	30PL11	15/6	AC126	8/6	NKT211	6/-
DL919	30/-	PCF91	10/6	OB2	6/3	30PL13	15/6	AC127	7/6	NKT214	6/-
DV4360	7/6	PCF602	10/6	OC3	5/6	30PL14	15/6	AC128	6/6	NKT216	7/6
DY86	6/6	PCF808	12/6	OZ4	4/6	35L06GT	8/6	AC176	4/6	NKT317	6/-
DY87	6/6	PCL82	7/9	13GT	8/6	35V4	4/6	AC177	7/6	NKT318	6/-
EB90C	12/6	PCL83	9/3	1R5	5/6	35Z4GT	5/6	AC138	5/6	NKT221	6/-
E180F	17/6	PCL84	7/9	2D23	5/6	50C6	6/3	ACY19	6/3	NKT223	6/-
E180C	22/6	PCL85	9/3	2E26	20/6	50D6GD	31/6	ACY20	5/6	NKT224	4/6
EABC90	7/6	PCL86	9/3	3A5	7/6	80	8/6	ACY21	6/6	NKT225	4/6
EAF34	10/6	PCN84	20/6	3B29	40/6	85A1	25/6	ACY23	6/6	NKT227	5/6
EAF31	3/6	PCN85DD	3C45	65/-	88A2	4/6	ACY28	4/6	NKT228	6/-	
EB033	7/6	12/-	AX150A	9/6	90A6	4/6	AD140	10/6	NKT251	5/-	
EB041	9/9	PFL200	14/6	BR40Y	8/9	90A6	4/6	AD161	11/6	NKT252	5/6
EB090	4/6	PL36	10/6	8U4G	4/6	90C1	12/6	AD114	6/6	NKT274	6/-
EBF90	7/6	PL81	8/6	8V4G	8/6	90C2	25/6	AF115	8/6	NKT304	6/-
EBF93	6/6	PL82	7/9	8V4G	4/6	86Z2	25/6	AF116	6/6	NKT305	6/-
EBF99	6/6	PL84	6/9	8ZAG	6/9	150B3	9/6	11/6	8/6	NKT404	12/6
EBL21	11/6	PL500	15/6	630L2	13/6	150B3	8/6	AF118	10/6	NKT450	12/6
EBL91	27/6	PK4	14/6	6AK6	4/6	801	6/6	AP125	6/3	NKT675	6/-
EC033	16/-	PK28	12/6	6AK6	6/6	803	35/6	AF178	12/6	NKT676	6/-
EC040	16/-	PK28	12/6	6AK6	6/6	803	35/6	AF178	12/6	NKT677	6/-
EC041	3/6	PK33	9/6	6A4	3/6	811	25/6	G111	22/6	NKT678	6/-
EC082	4/6	PK81	6/6	6AN8	10/6	813	7/6	AS221	7/6	NKT713	7/6
EC083	6/3	PK82	6/6	6A4	4/6	866A	13/6	AS221	12/6	NKT777	6/-
EC085	5/6	PK83	6/6	6A4	6/6	872A	5/6	AS223	30/6	OA5	3/6
EC088	7/6	PK80	10/6	6AS6	6/6	8651	7/6	ATZ10	30/6	OA7	4/6
ECF90	6/6	PK81	10/6	6AS7	15/6	866A	8/6	AU120	39/6	OA10	3/6
ECF92	7/6	PK82	10/6	6A7G	4/6	8672	7/6	BC107	7/6	OA17	5/6
ECF95	12/6	QQV02/6	45/6	6A7G	6/6	8707	10/6	BCY47	10/6	OA7	5/6
ECF96	12/6	QQV03/10	6/4G	16/6	6691	25/6	BC109	7/6	OA79	2/6	
ECH81	5/9	30/6	6BA6	5/6	6749	40/6	BCY31	13/6	OA81	2/6	
ECH83	8/6	QQV03/20	6/6E	5/6	6783	10/6	BCY33	7/6	OA85	2/6	
ECL80	7/6	105/6	6BH6	7/6	6843	65/6	BCY34	6/6	OA86	4/6	
ECL82	7/6	QQV04/15	6/3E	3/6	6963	10/6	BCY39	24/6	OA21	3/6	
ECL84	10/3	105/6	6BK4	27/6	6987	7/6	BCY40	12/6	OA200	3/6	
ECL86	9/6	QQV06/40	6/6N6	7/6	6958	10/6	BCZ11	5/6	OA202	4/3	
ECL800/30	90/6	6BQ7A	7/6	6059	18/6	BDY11	27/6	OA210	7/8		
EP9	20/6	QQV6/10	6BR7	8/6	6960	6/6	BDY12	32/6	OA290	11/6	
EP37A	7/6	70/6	6BR8	9/6	6961	12/6	BFY81	3/6	OA291	10/6	
EPF9	6/6	QS70/20	5/6	6B57	16/3	6052	14/6	BFY52	4/6	OA292	8/6
EP41	10/6	QS75/20	3/6	6B60	14/6	6053	21/6	GA204	12/6	OA293	8/6
EP80	5/6	QS75/80	20/6	6B7	14/6	6064	7/6	BSY27	0/6	OA290	8/6
EP86	6/9	QS83/3	7/3	6C4	2/6	6065	9/6	BSY28	5/6	OA2908	8/6
EP89	5/6	QS92/10	4/6	6C8E	5/6	6067	10/6	BSY51	7/6	OA2224	9/6
EP91	3/6	QS95/10	5/6	6C8D	22/6	6080	25/6	BSY53	7/6	OA2224	10/6
EP92	2/6	QS105/45	10/6	6C10	6/6	6096	8/6	BSY50A	5/6	OA2225	10/6
EP93	10/6	QS105/15	8/6	6C10	8/6	6145	8/6	BTY10	12/6	OA294	8/6
EP183	6/6	QS150/30	5/6	6CW4	12/6	9003	9/6	BTY58	10/6	OA2246	4/6
EP184	6/6	QS150/36	6/4	15/6	9003	9/6	BTY59	10/6	OA2246	4/6	
EPF804	21/6	20/6	6DK6	9/6	TRANSISTORS	140/6	OA2290	9/6			
EPF60	10/6	QS150/45	6F23	13/6	IN21	3/6	BY100	5/6	OC19	20/6	
EB90	7/6	20/6	6F84	12/6	IN22	5/6	BY114	5/6	OC19	7/6	
EL33	12/6	QS150/80	6F85	12/6	IN29	12/6	BY111	9/6	OC29	16/6	
EL84	10/6	20/6	6F88	11/6	IN192	17/6	BY112	12/6	OC22	10/6	
EL41	10/6	QS1209	7/3	6G5	2/6	IN3065	13/6	BY13	7/6	OC23	11/6
EL42	10/6	QQV13	10/6	6J6	3/6	IS113	4/6	BY218	15/6	OC24	16/6
EL41	7/9	QV04-7	12/6	6J7G	4/9	IS131	4/6	CDT1313	12/6	OC25	9/6
EL84	4/9	QV05-25	7/6	6K7G	2/-	IS420R	12/6	GA4	2/6	OC26	7/6
EL86	7/6	QV06-20	6/6	6L6	7/6	IS12	6/6	BY127	2/6	OC28	7/6
EL85	7/6	R10	16/6	6L6G	7/6	IG210	12/6	CRS105	7/6	OC29	12/6
EL90	6/6	R17	8/6	6Q7G	6/6	2G399	5/6	CV102	3/6	OC36	12/6
EL95	5/6	R18	7/6	6Q8T	5/6	2G381	5/6	CV103	3/6	OC38	12/6
EL360	22/6	R19	7/9	6S7M	7/6	2G382	6/6	CV425	3/6	OC41	3/6
EL600	20/6	R45/500	8/6	6SL7CT	4/9	2G401	5/6	CV228	20/6	OC42	5/6
EL821	6/6	R130P	35/6	6Y60	4/6	2C403	6/6	CV225	25/6	OC43	9/6
EL822	16/6	3P41	3/6	6X4	3/6	2G414	6/6	CV290	8/6	OC44	4/6
EL820	20/6	3P41	3/6	6X5G	4/6	2G415	6/6	CV188	20/6	OC45	3/6
EM34	25/6	3P61	3/6	6X5G	4/6	2G416	6/6	CV178	30/6	OC46	5/6
EM60	7/6	STV280/40	8/6	6Y6T	6/6	2G416	6/6	CV188	30/6	OC47	7/6
EM81	7/9	25/6	7B8	11/6	2G417	6/6	CV189	30/6	OC48	5/6	
EM84	7/6	STV280/80	8/6	6Z47	9/6	2G417	6/6	BY11	9/6	OC49	7/6
EB32	24/6	85/6	7C5	15/6	2G424	9/6	DD190	9/6	OC57	16/6	
EY81	7/6	SU2150	12/6	7E6	15/6	2N410					

**GET THIS SPECIAL PACK NOW AND  
WITH THE *FREE* VEROBOARD  
ENCLOSED IN THE LAST ISSUE  
COMPLETE THE SERIES OF  
CIRCUITS IN THE OCT., NOV.  
and DEC. NUMBERS OF  
"Practical Electronics"**



Pack consists of Spot Face Cutter and 5 pieces of Veroboard cut to size.

**Available now at your usual retailer**

TRADE ENQUIRIES TO


**NORMAN ROSE (Electrical) LTD.,** 8 St. Chad's Place, Gray's Inn Road,

TECHNICAL ENQUIRIES TO

**VERO ELECTRONICS LTD.,** Industrial Estate, Chandler's Ford, Hants SO5 3ZR

London, W.C.1

## RADIO CONSTRUCTOR

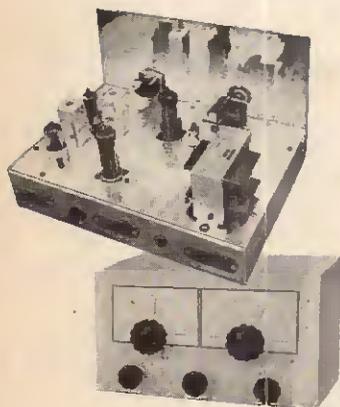

## OCTOBER ISSUE

NOW ON SALE

### FEATURES

#### A BAND SPREAD H.F. BANDS SUPERHET

An outstanding constructional project for the beginner to short wave listening

By F. G. Rayer

**PLUS** 2 DETACHABLE DATA SHEETS

*other constructional articles include:*

- **CRYSTAL MICROPHONE MATCHING UNIT**
- **INFINITE RESISTANCE VOLTMETER**
- **ULTRA-SENSITIVE LIGHT OPERATED SWITCH**

From your newsagent price 3/-, or 3/6 inclusive of postage, from Data Publications Ltd.  
57 Maida Vale, London, W.9

While the GaAs is in this section it has a normal positive resistance; thus the electrons do not accumulate to form a domain but will disperse in the normal way. The formation and existence of the domain can only take place between each swing into the positive resistance region, when the GaAs is back in the negative resistance region.

### PURE NEGATIVE RESISTANCE

In the quenched domain mode observed by Carroll, the time between swings was long enough to permit domain formation, but short enough to quench the domain before it reached the other end of the slice. Now, if this time, which is determined by the frequency of the oscillation, were even shorter, the domains which take a finite time to form will not even have any chance to do so. Thus the GaAs slice can operate as a pure negative resistance device. This was achieved by Kennedy and Copeland.

The frequency of oscillation which is now determined by the resonant LC network must be high enough to prevent domain formation. This is a good thing, since it is the higher frequencies that we are interested in anyway.

### HIGHER POWER POSSIBLE

Because there is no transit-time limitation on the devices, they do not have to be made very thin. They can be fairly long so that they can handle much greater powers than Gunn Effect devices at higher frequencies. Copeland has recommended that they be made long in the direction parallel to the current flow and thin in a perpendicular direction to the flow, so that heat can be easily removed from the sides of the devices (Fig. 34).

This mode of operation of gallium arsenide as a negative resistance material is known as the Limited Space-charge Accumulation (LSA) mode, since the electrons are prevented (limited) from accumulating to form space-charge (bunched charges).

LSA devices are the first true negative resistance devices which depend only on the properties of a bulk material and not on layers or junctions. It is interesting to note this further step in the decrease of the number of layers necessary in a semiconductor active device, compared to the three layers of the transistor and the two layers of the tunnel diode. Furthermore, each progressive step has pushed the frequency limit of oscillation higher.

### THE FUTURE OF LSA DEVICES

LSA devices hold exciting promise for the future wider applications of microwave electronics. In the not too distant future one can envisage the commercial production of small portable radar sets.

Using Gunn Effect devices, prototype portable radar sets have been constructed and demonstrated by the Royal Radar Establishment.

The availability of tiny, simple and efficient microwave generators and oscillators at millimetre wavelengths brings nearer the day when the personal portable sound and colour television transceiver for communication with anybody else in the world is a working reality.

At the time of writing, Copeland has obtained 20mW output of c.w. microwaves at 88GHz with GaAs slices operating in the LSA mode. The GaAs slices were thin and originally intended for operation in the Gunn

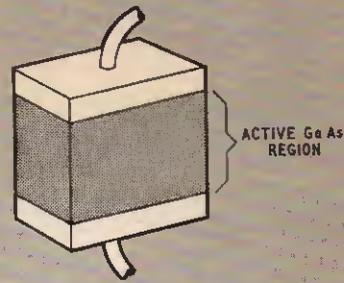


Fig. 34

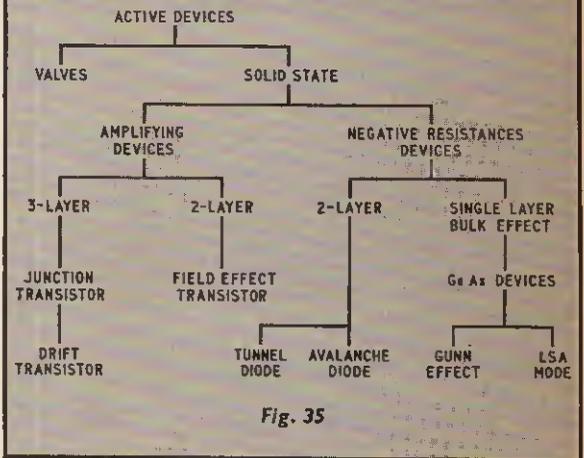


Fig. 35

Effect mode. When proper LSA devices to Copeland's design have been constructed, they will undoubtedly be able to generate much higher powers.

Even then, the powers already obtained are much higher than those ever generated by previous semiconductor active devices at such high frequencies.

### INTENSE RESEARCH

Research on LSA devices is now proceeding intensely in many laboratories and gaining momentum with each week. The writer is certain that by the time this article appears, significant progress will have been made in the practical construction, operation and application of these devices.

As a matter of interest, a chart (Fig. 35) showing the progress of the development, and the relationships of active devices is included. ★

### MUSICAL PHASE

In the article *Musical Phase* (September) the name of the co-author M. G. Lewis B.Sc., was inadvertently omitted. Mr. Lewis was in fact responsible for the invention of the Pradge phase generating equipment described in this article.

# LOOK!

**PRACTICAL!**

**VISUAL!**


**EXCITING!**



a new 4-way method of mastering  
**ELECTRONICS**  
by *doing* — *and* — *seeing* . . .

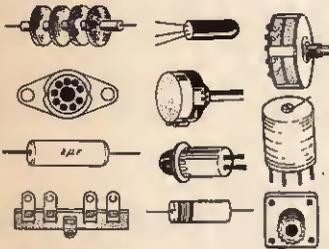**1** ▶ **OWN and HANDLE a**

complete range of present-day **ELECTRONIC PARTS and COMPONENTS**




**2** ▶ **BUILD and USE**

a modern and professional **CATHODE RAY OSCILLOSCOPE**



**3** ▶ **READ and DRAW and**

**UNDERSTAND CIRCUIT DIAGRAMS**

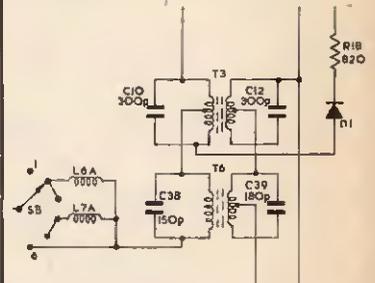

**4** ▶ **CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- VALVE EXPERIMENTS
- PHOTO ELECTRIC CIRCUIT
- A.C. EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- COMPUTER CIRCUIT
- D.C. EXPERIMENTS
- AMPLIFIERS
- BASIC RADIO RECEIVER
- SIMPLE COUNTER
- OSCILLATORS
- ELECTRONIC SWITCH
- TIME DELAY CIRCUIT
- SIGNAL TRACER
- SIMPLE TRANSMITTER
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW  
for  
**BROCHURE**

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: we do not employ representatives

NAME..... BLOCK CAPS

ADDRESS..... PLEASE PE II

## TRANSISTOR STEREO 8 + 8 MK II



Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work. Cir-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response  $\pm 3dB$ , 20-20,000cps. Bass boost approx. to +12dB. Treble cut approx. to -10dB. Negative feedback 18dB over main amp. Power requirements 25V at 0.6 amp.

**PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £3.0.0.** All Post Free. Circuit diagram, construction details and parts list (free with kit) 1/6. (S.A.E.).



**SPECIAL PURCHASE!**  
**E.M.L. 4-SPEED PLAYER**  
Heavy 8 1/2 in. metal turntable. Low flutter performance 200/260 V shaded motor (90 V tap). Complete with latest type lightweight pick-up arm and mono cartridge with 1/2 stylus for LP/78. LIMITED NUMBER ONLY 63/-. P. & P. 6/6.

### 4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing.

**E.M.L. MODEL 999 Single Player** with unit mounted pick-up arm and mono cartridge ..... £5.5.0  
**B.S.R. UA25** with latest mono compatible cart. . . . . £6.19.6  
All plus Carriage and Packing 6/6.

**LATEST GARRARD MODELS.** All types available 1000 SP25, 3000, AT80 etc. Send S.A.E. for latest Bargain Prices!

**LATEST B.S.R. K1X MONO COMPATIBLE CARTRIDGE** With turnover sapphire stylus suitable for playing 78, EP, LP and Stereo records with mono equipment. ONLY £2/6. P. & P. 2/-.

**SONOTONE STARC compatible Stereo Cartridge** with diamond stylus 50/-. P. & P. 2/-.

**MONO T/0 CARTRIDGE.** Complete with LP & 78 sapphire stylus. Brand new 12/6. P. & P. 2/-.

**NEW ONLY! ACOS GP68/1.** For EP and LP 10/-. P. & P. 2/-.

### QUALITY RECORD PLAYER AMPLIFIER

A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL24, E280 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7 1/2 in. x 3 d. x 6 h. Ready built and tested. PRICE 75/-. P. & P. 6/-.

**ALSO AVAILABLE** mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.

**DE LUXE QUALITY PORTABLE R/P CABINET**  
Uncut motor board size 14 1/2 x 12 in., clearance 2 in. below, 5 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD autochanger or Single Player Unit (except AT70 and SP25). Size 18 x 15 x 8 in. PRICE £39.0.0. P. & P. 9/6.

## HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer, E280 rectifier and ECL82 triode pentode valve as auto amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7 in. wide x 3 in. deep x 6 in. high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with valves and good quality output transformer. LIMITED NUMBER ONLY.

**OUR BEST BOTTOM BARGAIN PRICE 49/6**

P. & P. 6/-

**8 WATT AMPLIFIER.** Push Pull using ECC83, E280 and two EL84 valves. Suitable for use with tuner or gram. Separate bass, treble and volume controls. Absolutely complete with attractive fascia panel. Size 12 x 3 1/2 x 3 in. high. Brand new and tested £7.17.6. P. & P. 3/6.

**BRAND NEW 8 OHM LOUSPEAKERS**  
6 in. 14/-; 6 1/2 in. 18/8; 8 in. 27/-; 7 x 4 in. 18/8; 10 x 6 in. 27/8. E.M.L. 8 x 5 in. with high flux magnet 21/-. E.M.L. 13 1/2 x 6 in. with high flux ceramic magnet 48/- (15 ohm 48/-). E.M.L. 13 x 6 in. with two inbuilt tweeters and crossover network. 3 or 15 ohms 4 gu. P. & P. 6 in. 2/-, 6 1/2 x 8 in. 2/6, 10 x 12 in. 3/6 per speaker.

**BRAND NEW, 12 in. 15W H/D Speakers**, 3 or 15 ohms. By well-known British maker. Now with Hi Flux ceramic ferobar magnet assembly. £5.10.0. P. & P. 6/- Guitars Models: 55/-, 44/-, 55/-, 48/-

**E.M.L. 8 in. HEAVY DUTY TWEETERS.** Powerful ceramic magnet. Available in 3 or 8 ohms 15/- each; 15 ohms 18/6 each. P. & P. 2/6.

**12 in. "RA" TWIN CONE LOUSPEAKER.** 10 watts peak handling. 3 or 15 ohm, 25/-, P. & P. 3/6.

**35 OHM SPEAKERS**  
3 1/2 in. 12/6; 7 x 4 in. 21/-, P. & P. 2/- per speaker.

**VYNAL AND BEXINE SPEAKERS AND CABINET FABRICS** approx. 54 in. wide, Usually 35/- yd., our price 13/6 yd. length. P. & P. 2/6 (min. 1 yd.). S.A.E. for samples.

**LATEST COLLARO MAGNAVOX 368 STEREO TAPE DECK.** Three speeds 4 track, takes up to 7 1/2. spools. Send S.A.E. for latest prices.

**B.S.R. TDE, 4-TRACK STEREO TAPE DECK.** Send S.A.E. for latest price.

**QUALITY PORTABLE TAPE RECORDER CASE.** Brand new. Beautifully made. Only 48/6. P. & P. 8/6.

**Dual Purpose Bulk Tape Eraser and Tape Head Demagnetiser** 55/-. P. & P. 2/6.

**ACOS CRYSTAL MIKES.** High imp. for desk or hand use. High sensitivity, 18/6. P. & P. 1/6.

**ACOS HIGH IMPEDANCE CRYSTAL STICK MIKES.** Listed at 42/-. OUR PRICE 21/-. P. & P. 1/6.

**SPECIAL OFFER! MOVING COIL STICK MIKE.** Fitted on 002 switch remote control. High quality. High or low impedance. (State imp. required). BARGAIN PRICE 30/-. P. & P. 2/6.

**NEW S.T.O. TYPE 95 MINIATURE RELAYS—** 12 volt. 4 a/p. c/o contacts. 1 sup rating. Coil resistance 185 ohms. Size approx. {x 1 1/2} x 1 1/2 in. high. 10/- each. P. & P. 1/6.

Also some similar to above but coil resistance 5,800 ohms 48 volt operation. 8/- each. P. & P. 1/6.

**SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG.** 400pF + 146pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 kc/s I.F. Size approx. 2 1/2 x 1 1/2 in. Only 8/6. P. & P. 2/6.

**TRANSFORMER.** For transistor power supplies. Send S.A.E. for latest prices.

**Pri. 200/240V. Sec. 0-0-9 at 500mA. 11/-. P. & P. 2/6.**  
**Pri. 200/240V. Sec. 12-0-12 at 1 amp. 14/6. P. & P. 2/6.**  
**Pri. 200/240V. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 3/6.**

**MATCHED PAIR OF 21 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS.** Stack size 1 1/2 x 1 1/2 in. Output trans. tapped for 3 ohm and 15 ohm output. 10/- pair plus 2/- P. & P.

**PARMEKO 7-10 WATT OUTPUT TRANSFORMERS** to match pair of ECL82's in push-pull. Sec. tapped 3-75, 7-6 and 15 ohm. Stack size 2 1/2 x 2 1/2 in. approx. ONLY 12/-. P. & P. 3/6.

**7-10 WATT OUTPUT TRANSFORMERS** to match pair of ECL82's in push-pull to 3 ohm output. ONLY 11/-. P. & P. 2/6.

**BRAND NEW MAINS TRANSFORMERS** for Bridge Rectifier, Pri. 240V AC. Sec. 240V at 50mA and 6-3V at 1.5 amp. Stack size 2 1/2 x 1 1/2 in. 10/6. P. & P. 3/6. (Special quotations for quantities).

**NEON A.C. MAINS INDICATOR.** For panel mounting, cut out size 1 1/2 x 1 1/2 in. deep inc. terminal. White case with lens giving bright red light. For mains 200/250V. 2/6 each. P. & P. 6d. (6 or more post free).

**HIGH GRADE COPPER LAMINATE BOARDS** 6 x 6 x 1/4 in. PIVE for 10/-. P. & P. 2/6.

**BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched Pair) 15/-; V19/10p, 10/-; OC11 5/-; OC75 6/-; AF117 7/6.**

Set of Mullard 8 transistors OC44, 2—OC45, AC123D, matched pair AC128 25/-; Mullard LFH3 Audio Transistor Pack AC128D and matched pair AC128 12/6; ORP12 Cadmium Sulphide Cell 10/6. All post free.



**3-VALVE AUDIO AMPLIFIER MODEL HA34**  
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates ECC83, EL24, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and lends extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.5.0. P. & P. 6/-.

**HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-.

## SPECIAL OFFER!




A great opportunity to purchase a first class GENERAL PURPOSE, HIGH SENSITIVITY PORTABLE AMPLIFIER. Completely self contained and can be used for a variety of purposes, i.e. Intercom, Baby Alarm, Booster unit for transistor radios etc., also ideal for classroom unit etc. Works perfectly with our special offer High Impedance Dynamic Microphone (80/-). Output 1000mV. Uses standard 9 volt battery. Smart two tone carrying case 12 x 4 x 9 in. fitted standard input jack socket, volume controls, 7 x 4 in. speaker. Completely built and tested, brand new with full maker's guarantee.

Only 79/6 P. & P. 5/6
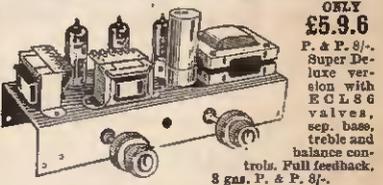
## STEREO AMPLIFIER

Incorporating 2 ECL82's and 1 E280, heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



ONLY £59.6 P. & P. 9/6. Super Deluxe version with ECL82 valves, sep. base, treble and balance controls. Full feedback. 8 gu. P. & P. 3/-.

## HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT


**Type TAI**  
Peak output in excess of 1 1/2 watts.  
● All standard British components.  
● Built on printed circuit panel size 8 x 3 in.  
● Generous size Driver and Output Transformers.  
● Output transformer tapped for 3 ohm and 15 ohm speakers.  
● Transistors (GET114 or S1 Mullard OC81D and matched pair of OC81 o/p). ● 9 volt operation.  
● Everything supplied, wire, battery clips, solder, etc.  
● Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. SPECIAL PRICE 45/-. P. & P. 3/-. Also ready built and tested, 52/6. P. & P. 3/-.

## FM/AM TUNER HEAD

Beautifully designed and precision engineered by Dornier & Wadsworth Ltd. Supplied ready fitted with twin .0005 tuning condenser for AM connection. Prealigned FM section covers 88-102Mc/s. I.F. output 10-7 Mc/s. Complete with ECC86 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at £7/6 each. P. & P. 3/-. **GOBLE F.M. TUNER HEAD.** 88-100 Mc/s. 10-7 Mc/s. I.F. 15/- plus 2/6 P. & P. (ECC85 valves, 3/6 extra).
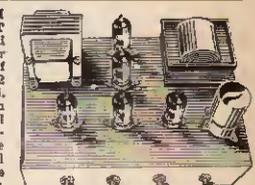
## 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for music and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 ohm speaker and 3 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY £7.9.6. P. & P. 8/6. Also available ready built and tested complete with sid. input sockets, £8.5.0. P. & P. 8/6.



Open all day Saturday  
Early closing Wed. 1 p.m.  
A few minutes from South Wimbledon  
Tuba Station

## HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19

Tel. 01-540 3985

SEND STAMPED ADDRESS ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.



### THE DORSET (600mW Output)

7-transistor fully tunable M.W.-L.W. superhet portable— with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Size: 12" x 8" x 3".

MAINS POWER PACK KIT: 9/6 extra.

Price £5.5.0 plus 7/6 p. & p. Circuit 2/6 FREE WITH PARTS.

### THE ELEGANT SEVEN MK. III (350mW output)

7-transistor fully tunable M.W.-L.W. portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 9/6 extra.

Price £4.9.6 plus 7/6 p. & p.

Circuit 2/6 FREE WITH PARTS.



### 50 WATT AMPLIFIER A.C. MAINS 200-250V

An extremely reliable general purpose valve amplifier—with six electronically mixed inputs. Suitable for use with: mics, guitars, gram, tuner, organs, etc. Separate bass and treble controls.

Price 27 gns. plus 20/- p. & p.

### X101 10W SOLID-STATE HI-FI AMP WITH INTEGRAL PRE-AMP

Specifications: RMS Power Output (into 8 ohms speaker): 10 watts continuous (sine wave), 13 watts music power. Sensitivity (for rated output): 1mV into 3K ohms (0-33 micro-amp). Total Distortion (@ 1kHz): at 5 watts 0-35%, at rated output 1-5%. Frequency Response: Minus 3dB points 20Hz and 40kHz. Speaker: 8-ohm (3-15 ohms may be used). Supply voltage: 24V d.c. @ 800mA (6-24V may be used).



Control assembly: including resistors and capacitors.

1. Volume: PRICE 5/-.

2. Treble: PRICE 6/-.

3. Comprehensive bass and treble: PRICE 10/-.

The above 3 items can be purchased for use with the X101.

Power Supplies for the X101:


F101 M (for mono) 35/- plus 4/6 p. & p. F101 S (for stereo) 42/6 plus 4/6 p. & p.

Price 49/6

plus 2/6 p. & p.
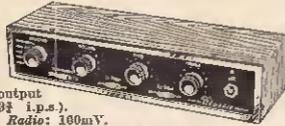
### THE CLASSIC

Controls: Selector switch. Tape speed equalisation switch (3½ and 7½ i.p.s.). Volume, Treble, Bass, 2 position scratch filter and 2 position rumble filter.



Specification: Sensitivities for 10 watt output at 1kHz. Tape head: 3mV at 3½ i.p.s. Mag. P.U.: 2mV. Cer. P.U.: 80mV. Radio: 180mV. Aux.: 100mV. Tape/Rec. output: 100mV. Equalisation for each input is correct to within ±2dB (R.I.A.A.) from 20Hz to 20kHz. Tone control range: Bass ±13dB at 160Hz. Treble ±14dB at 16kHz. Total distortion: (for 10 watt output) <1.5%. Signal noise: <-60dB. A.C. mains 200-250V. Size: 12½" long, 4½" deep, 2½" high. Teak finished case. Price 8 gns. p. & p. free.

### THE RELIANT 10W SOLID-STATE HIGH QUALITY AMPLIFIER

Specifications: Output: 10 watts R.M.S. Sine-wave; 13 watts R.M.S. Music-power. Output impedance: 8 to 4 ohms. Inputs: 1. Xtal mic 10mV; 2. Gram/radio 250mV. Tone controls: Treble control range ±12dB at 10kHz; Bass control range ±13dB at 100Hz. Frequency response (with tone controls central): Minus 3dB points are 20Hz and 40kHz. Signal to noise ratio: better than -60dB. Transistors: 4 silicon Planar type and 3 Germanium type. Mains input: 230-250V a.c. Size of chassis: 10" x 3½" x 3". A.C. Mains 200-250V. For use with 8Ω, or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble Hz control Two inputs with control for gram, and mike. Built and tested. 8" x 5" speaker to suit: Price 14/6 plus 1/6 p. & p. Crystal mike to suit: 12/6 plus 1/6 p. & p. PRICE £5.5.0 plus 5/- p. & p.

### RECORD PLAYER SNIP


The "Princess" 4 speed automatic record changer and player engineered with the utmost precision for beauty, long life and trouble free service. Will take up to ten records which may be mixed 7in to 10in or 12in. Patent stylus brush cleans stylus after each playing and at shut off, the pick-up locks itself into its recess, a most useful feature with portable equipment—other features include pick-up height adjustment and stylus pressure adjustment. This truly is a fine instrument which you can purchase this month at only £5.19.6 complete with cartridge and ready to play. Post and Insurance 7/6 extra. A.C. Mains 240V.



Price £5.19.6
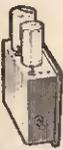
### CYLDON U.H.F. TUNER

Complete with FC88 and FC88 Valves. Full variable tuning. New and unused. Size 4½" x 5½" x 3½". Complete with circuit diagram. 35/- plus 3/6 p. & p.



### THREE-IN-ONE HI-FI 10 WATT SPEAKER

A complete Loud Speaker system on one frame, combining three matched ceramic magnet speakers with a low loss cross-over network. Peak handling power 10 watts. Impedance 16 ohms. Flux density 11,000 gauss. Resonance 40-60c/s. Frequency range 50c/s to 20kc/s. Size 13½" x 8½" x 4½". By famous manufacturer. List price £7. Our price 69/6 plus 5/- p. & p. Similar speaker to the above without tweeters in 3 and 16 ohms 39/6 plus 5/- p. & p.

Goods not despatched outside U.K. Terms C.W.O. All enquiries S.A.E.

## RADIO & TV COMPONENTS (ACTON) LTD.

21d High Street · Acton · London W.3

323 Edgware Road · London W.2

Orders by post to our Acton address please

ORGAN BUILDERS! SILICON N.P.N. TRANSISTORS, ALL INDIVIDUALLY TESTED IN PUBLISHED DIVIDER CIRCUIT! GOLD-PLATED LEADS FOR EASY SOLDERING! Unbeatable value at 1/6 each or £5/- per 100.

TRANSISTORISED FLUORESCENT LIGHT. 8 WATT 12in TUBE. Current drain only 700mA! Complete and tested £2/19/6 only! Or in kit form:

Case	..	..	7/6
Transistor	..	..	10/-
Lamp holders	..	..	4/-
Condensers, etc.	..	..	3/-
Transformer (on printed circuit)	..	..	13/6
Tube	..	..	8/-

### TRANSISTORS

OC200, OC203, OC204, all at 2/- each. ASY22, 2N753, BSY28, BSY65, 2G344A, 2G345A, 2G345B, 2G371A, 2G378A, all at 1/6 each.

Transistors similar to OC44, OC71 and OC72, all 1/- each.

Unmarked, untested transistors, 7/6 for 50.

LIGHT SENSITIVE TRANSISTORS (similar OCP 71), 2/- each.

30 watt transistors (ASZ17), 10/- each.

DIODES. Very low leakage. Make excellent detectors, also suitable for keying electronic organs, 1/- each, 20 for 10/-.

### RECTIFIERS

BY100, 800 p.i.v., 2/6 each, 24/- per doz., £7/10/- per 100, £50 per 1,000.

BYZ13, 6-amp, 400 p.i.v., available on same terms.

### MULLARD POLYESTER CAPACITORS FAR BELOW COST PRICE!

0-001µF	400 volts	..	3d	0-02µF	200 volts	..	3d
0-0015µF	400 volts	..	3d	0-15µF	160 volts	..	6d
0-0018µF	400 volts	..	3d	0-22µF	160 volts	..	6d
0-0022µF	400 volts	..	3d	0-27µF	160 volts	..	6d
0-01µF	400 volts	..	3d	1µF	125 volts	..	1/-

VERY SPECIAL VALUE! Small Silver-mica, Ceramic, Polystyrene Condensers. Well assorted. Mixed types and values. 10/- per 100. PAPER CONDENSERS, MIXED BAGS, 0-0001 to 0-5µF, 12/6 per 100.

RESISTORS! Give-away offer! Mixed types and values, ½ to ½ watt, 6/6 per 100, 55/- per 1,000. Individual resistors 3d each. Also ½ to 3 watt close tolerance. Mixed values. 7/6 100, 55/- 1,000. WIRE-WOUND RESISTORS. 1 watt to 10 watts. Mixed bags only. 16 for 10/-.

### RECORD PLAYER CARTRIDGES

#### ACOS

GP 67/2	Mono.	15/-	complete with needles.
GP 91/3	Stereo Compatible	£1/-	..
GP 93/1	Stereo Ceramic	£1/5/-	..
GP 94/1	Stereo Ceramic	£1/5/-	..

Small pick-up arms complete with cartridge and needle, 10/- only.

TRANSISTORISED SIGNAL INJECTOR KIT R.F./I.F./A.F. 10/- only

TRANSISTORISED SIGNAL TRACER KIT 10/- only

### VEROBOARD

2¼in x 1in	0-15in matrix	1/1	17in x 2¼in	0-15in matrix	11/-
3¼in x 2¼in	0-15in matrix	3/3	17in x 3¼in	0-15in matrix	14/8
3¼in x 3¼in	0-15in matrix	3/11	3¼in x 2¼in	0-1in matrix	3/9
5in x 2¼in	0-15in matrix	3/11	3¼in x 3¼in	0-1in matrix	3/11
5in x 3¼in	0-15in matrix	5/6	5in x 2¼in	0-1in matrix	3/11
			5in x 3¼in	0-1in matrix	5/6

Spot Face Cutter 7/6. Pin Insert Tool 9/6. Terminal Pins 3/6-36.

### MULTIMETERS. 20,000 ohms per volt.

Ranges: a.c. 1,000V, 500V, 100V, 50V, 10V.

d.c. 250mA, 2-5mA, 50µA.

d.c. 2,500V, 500V, 250V, 50V, 25V, 5V.

Resistance: 0/60kΩ and 0/6MΩ.

Special price £4/- only.

### ELECTROLYTIC CONDENSERS

0-25µF	3 volt	4µF	4 volt	25µF	12 volt	100µF	16 volt
1µF	6 volt	4µF	12 volt	25µF	25 volt	125µF	25 volt
1µF	20 volt	4µF	25 volt	30µF	6 volt	320µF	4 volt
1-25µF	16 volt	6µF	6 volt	30µF	10 volt	320µF	10 volt
2µF	3 volt	8µF	3 volt	50µF	6 volt	400µF	6-4 volt
2µF	350 volt	8µF	12 volt	64µF	2-5 volt		
2-5µF	16 volt	10µF	6 volt	64µF	9-9 volt		
3µF	25 volt	10µF	25 volt	100µF	9 volt		
3-2µF	64 volt	25µF	6 volt	100µF	16 volt		

All at 1/- each. 20 assorted (our selection) 10/-.

Orders by post to:

G. F. MILWARD, DRAYTON BASSETT, NEAR TAMWORTH, STAFFS.

Please include suitable amount to cover post and packing. Minimum 2/-.

Stamped addressed envelope must accompany any enquiries. For customers in Birmingham area goods may be obtained from Rock Exchanges, 231 Alum Rock Road, Birmingham 8.

# BI-PRE-PAK LIMITED

## TRANSISTORS PRICE

AC107	3/-	OC170	3/-
AC126	2/4	OC171	4/-
AC127	2/4	OC200	3/6
AC128	2/4	OC201	7/-
ACY17	3/-	2G301	2/6
AF114	4/-	2G303	2/6
AF115	3/6	2N711	10/-
AF116	3/6	2N1302-3	4/-
AF117	4/6	2N1304-5	5/-
AF118	3/6	2N1306-7	6/-
AF119	3/6	2N1308-9	8/-
AF186	10/-	2S303	5/-
AF139	10/-	Power	
BFY50	4/-	Transistors	
BSY25	7/6	OC20	10/-
BSY26	3/-	OC23	10/-
BSY27	3/-	OC25	8/-
BSY28	3/-	OC26	5/-
BSY29	3/-	OC28	10/-
BSY95A	3/-	OC35	5/-
OC41	2/6	OC36	7/6
OC44	1/11	AD149	10/-
OC45	1/9	2N2287	20/-
OC71	2/6	Diodes	
OC72	2/6	AA42	2/-
OC73	3/6	OA10	2/-
OC81	2/6	OA70	1/9
OC81D	2/6	OA79	1/9
AF102	12/6	OAB1	1/9
OC139	2/6	OA182	2/-
OC140	3/6	IN914	1/6

## EXCITING NEW PAKS

FOR AMATEURS, PROFESSIONALS, FACTORIES, ORGAN BUILDERS, AND THOSE PEOPLE THAT JUST USE LARGE QUANTITIES OF TRANSISTORS.

### XA PAK

Germanium PNP type transistors, equivalents to a large part of the OC range, i.e. 44, 45, 71, 72, 81, etc.

PRICE £5 PER 1000

### XB PAK

Silicon TO-18 CAN type transistors NPN/PNP mixed lots, with equivalents to OC200-1, 2N706a, BSY27/29, BSY95A.

PRICE £5.50 PER 500  
PRICE £10 PER 1000

### XC PAK

Silicon diodes miniature glass types, finished block with polarity marked, equivalents to OA200, OA202, BAY31-39 and DK10, etc.

PRICE £5 PER 1000

ALL THE ABOVE UNTESTED PACKS HAVE AN AVERAGE OF 75% OR MORE GOOD SEMICONDUCTORS. FREE PACKS SUSPENDED WITH THESE ORDERS. ORDERS MUST NOT BE LESS THAN THE MINIMUM AMOUNTS QUOTED PER PACK.

P/P 2/6 PER PACK (U.K.)

## PRE-PAKS

Selection from our lists

No.		Price
B1	50 Unmarked Trans. Untested	- 10/-
B2	4 Solar Cells Inc. Book of Instructions	- 10/-
B6	17 Red Spot AF Transistors	- 10/-
B6A	17 White Spot RF Transistors	- 10/-
B9	1 ORP 12 Light Sensitive Cell	- 9/-
B53	25 Sil. Trans. 400 Mc/s	Brand New - 10/-
B54	40 " " NPN To5	Trans Voltage - 10/-
B55	40 " " NPN To18	& Gain Fallouts 10/-
B56	40 " " NPN/PNP	All Tested - 10/-
B68	10 Top Hat Recs. 750 M/A	100-800 PIV - 10/-
B69	20 Diodes. Gld-Bnd. Germ Sil. Planer	- 10/-
B74	5 Gld-Bnd. Diodes, 2-QA9, 3-QA5	- 10/-
B75	3 Comp. Set. 2G371, 2G381, 2G339A	- 10/-
C2	1 Unijunction Transistor 2N2160	- 15/-
C26	3 TEXAS Power Transistors 2S012A	- 15/-
C32	6 Top Hat Recs. IS100 Type	- 15/-
A1	7 Silicon Rectifiers BY100 Type	- 20/-
A3	25 Mixed Marked and Tested Transistors	- 20/-
A21	5 Power Transistors IAD149/IOC26 and 3 others	- 20/-

AND MANY MORE

# FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 10/- WITH ORDERS OVER £4

## TRANSISTORS ONLY 1/- EACH

SILICON • PLANAR • N.P.N. • P.N.P.

All these types available

2N929	2N706	2S131	2S103	2N696	2N1613	2S733	BFY10
2S501	2N706A	2S512	2S104	2N697	2N1711	2N726	2S731
2N2411	2N3011	2S102	2N2220	2N1507	2N1893	2N2484	2S732

All tested and guaranteed transistors—unmarked. Manufacturers over runs for the new PRE-PAK range.

## NEW UNMARKED UNTESTED PAKS

25	BSY95A NPN Silicon	TRANSISTORS	10/-
10	1000 PIV 1 amp. Min. Silicon	DIODES	10/-
25	BSY26-27 NPN Silicon	TRANSISTORS	10/-
10	10 Watt Silicon All Voltages	ZENERS	10/-
25	BFY50-1-2 NPN Silicon	TRANSISTORS	10/-
10	4 amp. Stud. Silicon	RECTIFIERS	10/-
25	BC107-8-9 NPN Silicon	TRANSISTORS	10/-
40	1N914-6 OA200/202 Sub. Min. Silicon	DIODES	10/-
150	Min. Germ. High Quality	DIODES	10/-
25	2N706 A NPN Silicon	TRANSISTORS	10/-

PRE-PAK, N.605 POWER TRANSISTOR EQUIVALENT TO NKT301-4 **5/- each**

TANTALUM CAPACITORS **4/- each**

## BRAND NEW PAK • JUST RELEASED

REPLACES OUR VERY POPULAR B.39 PAK. BRAND NEW SHORT LEAD COMPONENTS ALL FACTORY MARKED AND MOUNTED ON PRINTED CIRCUIT PANELS.

80 TRANSISTORS & DIODES ALL 10/-  
50 HIGH TOLERANCE RESISTORS  
20 VARIOUS CAPACITORS FOR

PLEASE STATE WHEN ORDERING PAK P.I. 2/- P. & P. WITH THIS PAK.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a perfectly linear and accurate rev. counter for any car. **20/- each**  
State 4 or 6 cylinder.

FREE CATALOGUE AND LISTS for:—

ZENER DIODES  
TRANSISTORS, RECTIFIERS  
FULL PRE-PAK LISTS  
& SUBSTITUTION CHART

MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

THERE IS ONLY ONE  
BI-PRE-PAK LTD  
BEWARE OF IMITATIONS

**FIRST EVER LOGIC KITS**

Learn for yourself how computers work, even make one for yourself. Full instructions for a noughts and crosses machine, binary counters, timers, etc. L1. 5gns. L2. 10gns. Introducing the Norkit range. Norkit Junior £2. Norkit Senior £16.

**Details Free**  
Free Paks suspended with Logic Kit Orders.

FREE! A WRITTEN GUARANTEE WITH ALL OUR SEMICONDUCTORS

# BI-PRE-PAK LTD

DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344

# Practical Electronics Classified Advertisements

The pre-paid rate for classified advertisements is 1/3 per word (minimum order 15/-), box number 1/6 extra. Semi-displayed setting £4. 2. 6 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL ELECTRONICS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL ELECTRONICS, George Newnes Ltd., 15/17 Long Acre, London, WC2, for insertion in the next available issue.

## MISCELLANEOUS

**BUILD IT** in a DEWBOX quality cabinet 2in x 2½in x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

## BIG BARGAIN PARCEL

Containing transistors, diodes, capacitors, fuses, connecting wire, sleeving, valve holders, tag strips, potentiometers, etc.

**10/-** POST PAID

**SALOP ELECTRONICS**  
7a Greyfriars Road, Coleham  
Shrewsbury, Shropshire

S.A.E. for latest lists

## ARTIFICIAL LIFE

Well almost, because the NEW range of projects include: an electronic 'animal' which LEARNS, and a device capable of REPRODUCING itself! Other projects SURE TO INTRIGUE YOU are an audio transmitter/receiver which has quite an amazing range and requires NO LICENCE; also a machine which recognizes itself, and an electronic dog whistle, etc., etc. HOSTS OF EASY-TO-CONSTRUCT projects. SEND 2/6 for your list—NOW!

To: 'BOFFIN PROJECTS'

incorporating  
BIONIC DESIGNS  
4 CUNLIFFE RD.

STONELEIGH, EWELL, SURREY

**NEW! ADD STEREO EFFECTS**



**TO YOUR LISTENING...**

"NEW DIMENSIONS" gives fabulous Big Hall 3-dimension effect to all music. PLUS adjustable echo, vibrato and tone. Battery 9v. model for radio, tape or player. Speaker 25/- extra. **8 gns.**

**CAR VERSION** for 6v. or 12v. + or - earth. 10 gns. including rear speaker. 5/- post and ins. either model.

Send S.A.E. for full details direct from manufacturers—NOW!

**D.E.W. LTD.**  
P.E., 251 Ringwood Road, Ferndown, Dorset

## MISCELLANEOUS (continued)

**CALL OR SEND** for list from the most interesting shop in Lancashire. Electrical Mechanical and Electronic Goods. ROGERS, 31 Nelson Street, Southport.

## TAPE RECORDERS, TAPES, ETC.

**TAPES TO DISC**—using finest professional equipment—45 r.p.m. 12/-. S.A.E. leaflet. DERBY, High Bank, Hawk Street, Carnforth, Lancs.

## EDUCATIONAL

**GET INTO ELECTRONICS**—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. A.M.I.E.R.E., R.T.E.B., City & Guilds, Radio, T/V, Telecoms., etc. For FREE 100-page book, write Dept. 856K, CHAMBERS COLLEGE, 148 Holborn, London, E.C.1.

## EDUCATIONAL (continued)

**STUDY RADIO, TELEVISION AND ELECTRONICS** with the world's largest home study organisation. City & Guilds; R.T.E.B., etc. Also practical courses with equipment. No books to buy. Write for FREE Prospectus to ICS (Dept. 577), Intertext House, London, SW11.

**ENGINEERS.** A technical certificate or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B. and G.C.E. exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto, Electronics, Radio, Computers, Draughts., Building, etc. For full details write for FREE 132-page guide. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 125K), Aldermaston Court, Aldermaston, Berks.

# CITY AND COUNTY OF BRISTOL BRISTOL TECHNICAL COLLEGE

Principal: E. Poole, B.Sc.(Eng.), C.Eng., M.I.Mech.E., M.I.Prod.E.

## CAREERS IN RADIO AND RADAR

### Marine Radio Officers

2 year full-time course leading to the Second and First Class P.M.G. Certificates and the B.O.T Radar Maintenance Certificate.

Conversion Course (Second Class to First Class).

R.T. Licences (Full or Restricted)

### Courses for Qualified Marine Radio Officers

Single Sideband Techniques (2 weeks)  
Marine Electronics Course (Phase I—duration 3 months)

Advanced Marine Electronics Course (Phase II—duration 3 months)

### Licensed Aircraft Radio Engineers

2 year full-time course covering the Aircraft Radio Engineers Licences categories A and B, issued by the Board of Trade (Civil Aviation) followed by a six-months' course for Radar Rating (A and B) in association with the above.

Training given on the latest types of Marine and Aircraft equipment in modern, approved laboratories at

## THE SCHOOL OF RADIO AND RADAR

Senior Lecturer-in-Charge: F. E. Bartrop

For further information apply to:—

**The Registrar, BRISTOL TECHNICAL COLLEGE  
ASHLEY DOWN, BRISTOL 7**

**BOOKS AND PUBLICATIONS**

**SURPLUS HANDBOOKS**

- 19 set Circuit and Notes ..... 6/6 P.P. 6d
- 1155 set Circuit and Notes .... 6/6 P.P. 6d
- H.R.O. Technical Instructions ... 5/6 P.P. 6d
- 38 set Technical Instructions... 5/6 P.P. 6d
- 46 set Working Instructions... 5/6 P.P. 6d
- 88 set Technical Instructions... 7/- P.P. 6d
- BC. 221 Circuit and Notes ..... 5/6 P.P. 6d
- Wavemeter Class D Tech. Instr 5/6 P.P. 6d
- 18 set Circuit and Notes ..... 5/6 P.P. 6d
- BC.1000 (31 set) Circuit & Notes 5/6 P.P. 6d
- CR.100/B.28 Circuits and Notes 10/- P.P. 9d
- R.107 Circuit and Notes ..... 7/- P.P. 6d
- A.R.88D. Instruction Manual... 18/- P.P. 6d
- 62 set Circuit and Notes ..... 6/6 P.P. 6d
- 52 set Sender & Receiver Circuits 7/6. post free
- Circuit Diagrams 5/- each post free.
- R.1116/A, R.1224/A, R.1355, R.F. 24, 25, & 26.
- A.1134, T.1154, CR.300, BC.342, BC.312.
- BC.348, J.E.M.P. BC.624, 22 set.
- Resistor Colour Code Indicator... 2/6 P.P. 6d

S.A.E. with all enquiries please.  
Postage rates apply to U.K. only.  
Mail order only to:  
**Instructional Handbook Supplies**  
Dept. P.E., Talbot House, 28 Talbot Gardens  
Leeds 8

**FOR SALE**

**ILLUSTRATED CATALOGUE** No. 17 Manufacturers' Surplus and New Electronic Components including Semiconductors. 3/- post free. **ARTHUR SALLIS LTD.**, 28 Gardner Street, Brighton.

**HIGH GLOSS METALLIC  
HAMMERED ENAMEL**  
"MAKES FANTASTIC  
DIFFERENCE TO PANELS"  
say hundreds of enthusiastic users  
'Crackle' pattern appears like mags  
on wood and metal. No under-  
coat. Air dries 15 min.  
to hard glossy finish.  
Heat, liquid and  
scratchproof. Lt. **Hammerite**  
BRUSH OR SPRAY-ON  
and Dk. Blue; Bronze; Silver; Green; Black.  
Send for Free list, or 8/- (+ 1/9 post) for trial  
1pt. TIN, colour samples and instructions.  
Send NOW.  
**FINNIGAN'S SPECIALTY PAINTS** Dept. P.E.  
STOCKFIELD. Tel. 2280 Northumberland.

**BRASS, STEEL, LIGHT ALLOY, STAINLESS  
STEEL TUBE.** Bar Material, Tools, Mechanical, Electrical, plus Assorted Lots. Send S.A.E. for latest Cat. of 1,000 items. K. R. WHISTON, Dept. BPE, New Mills, Stockport.

**MORSE MADE !!  
EASY**

**FACT NOT FICTION.** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.  
For details and course C.O.D. ring B.T.D. 01-889 2896 or send 8d. stamp for explanatory booklet to:  
**GGGS/R, 46 GREEN LANE, FURLEY, SURREY**

**WANTED**

**VALVES WANTED,** brand new popular types boxed. **DURHAM SUPPLIES (E)**, 367F, Kensington Street, Bradford 8, Yorkshire.

**WANTED.** Retail outlets for New/Surplus Radio-Electronic Spares. Excellent profits. Details from Box 13.

**SURPLUS RELAYS.** Post Office 3000 type. Any condition. Send particulars to D. SMITH, 330 Bath Road, Kettering, Northants, or ring 053-6 2681 evenings.

**SERVICE SHEETS**

**RADIO TELEVISION,** over 8,000 Models. **JOHN GILBERT TELEVISION**, 1b Shepherds Bush Rd., London, W.8. SHE 8441.

**SERVICE SHEETS**

(continued)

**SERVICE SHEETS. RADIO, TELEVISION, TAPE RECORDERS,** 1925-1968, by return post, from 1/- with free fault-finding guide. Catalogue 6,000 models, 2/8. Please send stamped addressed envelope with all orders/enquiries. **HAMILTON RADIO**, 54e London Road, Bexhill, Sussex.

**SITUATIONS VACANT**

A.M.I.E.R.E., A.M.S.E. (Elec.), City & Guilds, G.C.E., etc., on "Satisfaction or Refund of Fee" terms. Wide range of Home Study Courses in Electronics, Computers, Radio, T.V., etc. 182-page Guide—FREE. Please state subject of interest. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept. 124K), Aldermaston Court, Aldermaston, Berks.

**CAREER EMPLOYMENT OPPORTUNITIES FOR TELECOMMUNICATIONS TECHNICIANS**

**LONDON AND THE HOME COUNTIES**  
A number of vacancies still remain to be filled by experienced men who have obtained the City and Guilds Intermediate Certificate in Telecommunications Engineering or an equivalent or higher technical qualifications.  
Salary: £1,255 (at age 25) to £1,429 per annum in London. £1,130 to £1,304 per annum in Home Counties. Plus additional allowances when shift working.  
Candidates and both their parents must have been British subjects at all times since birth. Previous applicants should not re-apply.  
Further details and Application Forms from:  
**The Personnel Officer (PE),  
Diplomatic Wireless Service  
Hanslope Park  
Wolverton, Bucks.**  
Please quote reference.

**SITUATIONS VACANT (continued)**

**SINCLAIR RADIONICS LIMITED**

Require Service Engineers for varied and rewarding work in their service department. Experience of transistor circuitry is necessary. Write, giving full details, age, etc., to Richard Torrens, Sinclair Radionics Limited, 22 Newmarket Road, Cambridge.

**ARE YOU PRACTICAL AND FED UP WITH YOUR PRESENT JOB?**

We require a number of junior and senior engineers with drive and initiative for:—  
Circuit design—development and prototype construction, etc.:  
Electro-mechanical drafting—printed circuit/chassis layouts, etc.:  
Production line test and inspection engineers: Production line fault finders.  
Excellent prospects and full training given, day release considered. Salary up to £1,400 depending on experience and qualifications.  
Send full details in writing of experience to date and present salary to:—  
**Mr. B. C. Johnson,  
Solid State Controls Limited,  
Brunel Road,  
Acton, W.3,  
London.**

**TECHNICAL TRAINING by ICS IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING**

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.  
ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Electronics, Computers, etc. Expert coaching for:  
• C. & G. TELECOMMUNICATION TECHNICIANS' CERTS.  
• C. & G. ELECTRONIC SERVICING.  
• R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.  
• RADIO AMATEURS' EXAMINATION.  
• P.M.G. CERTIFICATES IN RADIOTELEGRAPHY.

Examination Students Coached until Successful.  
**NEW SELF-BUILD RADIO AND ELECTRONIC COURSES**  
Build your own 5-valve receiver, transistor portable, signal generator, multi-meter and valve volt meter—all under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

**A WHOLE WORLD OF KNOWLEDGE AWAITS YOU!**

International Correspondence Schools  
(Dept. 152), Intertext House, Parkgate Road,  
London, S.W.11.

NAME .....  
Block Capitals Please

ADDRESS .....

..... 11.68

RECEIVERS AND COMPONENTS

R & R RADIO

51 Burnley Road, Rawtenstall  
Rossendale, Lancs  
Tel.: Rossendale 3152

VALUES BOXED, TESTED & GUARANTEED

EBF80	3/-	PCC84	3/-	PY82	3/-
EBF89	3/6	PCF80	3/6	UI91	4/6
ECC82	3/6	PCF82	3/6	U301	4/6
ECL80	3/6	PCL82	4/6	6F23	5/-
EF80	1/6	PCL83	4/6	10P14	3/6
EF85	3/6	PCL84	5/6	20P5	3/6
EF183	3/6	PL36	5/6	30P5	2/6
EF184	3/6	PL81	4/6	30L15	5/6
EY86	4/6	PL83	4/6	30P12	4/6
EL41	5/6	PY33	5/6	30C15	5/6
EZ40	4/6	PY81	3/6	30PL13	5/6
EBC41	4/6	PY800	3/6	30PL14	5/6

POST, ONE VALVE 9d. TWO TO SIX 6d.  
OVER SIX POST PAID.

MICROSWITCHES

all new, wide variety for many jobs from 2/-. Waterproof and metalclad from 9/-.

SYNCHRONOUS MOTORS

with gear boxes 300 rpm to 1 rev 24 hrs. All new, wide variety 3 to 20 watts mostly 230v A.C. 2500 rpm for fans, tape decks, etc. from 7/6d.

S.A.E. list.

HOLFORD & CO.  
6 Imperial Square, Cheltenham

FULL SPEC SEMICONDUCTORS  
DATA SUPPLIED ALL TYPES

TRANSISTORS	RECTIFIERS
2N697 4/-	IN914 1/3
2N706 1/9	200mA 200V 1/-
2N706A 2/3	3A 600V 3/6
2N708 4/-	3A 800V 3/6
2N914 4/6	10A 600V 5/6
2N2369 3/3	10A 800V 6/6
BSY26 2/6	
BSY27 2/6	
BSY28 2/6	

INTEGRATED CIRCUITS  
Pack of 6 Logic Elements 30/-  
Linear Amps 5/-

MAIL ORDER ONLY P & P 1/-

ROB-ELEC

84 Foster Hill Road, Bedford

BI-PAK SEMICONDUCTORS

500 Chesham House  
150 Regent Street  
London W1

QUALITY OF THE PAKS SATISFACTION GUARANTEED

SUPER PAKS—BRAND NEW  
Untested Semiconductors

QUALITY-TESTED VALUE PAKS ★ BARGAINS

2 Drift Trans. 2N1225 Germ. PNP 100Mc/s ...	10/-
6 Matched Trans. OC44/45/81/81/D Red Spot AF Trans. PNP ...	10/-
20 White Spot RF Trans. PNP ...	10/-
16 Silicon Rects. 3A 100-400 PIV ...	10/-
5 Silicon Rects. 100 PIV ...	10/-
2 OC140 Trans. NPN Switching ...	10/-
1 2A SCR 100 PIV ...	10/-
3 Sil. Trans. 25303 PNP ...	10/-
4 Zener Diodes 250mW 3-12V ...	10/-
3 200Mc/s Sil. Trans. NPN BSY26/27 ...	10/-
3 Zener Diodes 400mW 33V 5% Tol. ...	10/-
4 High Current Trans. OC242 Eqt. ...	10/-
2 Power Transistors 1 OC261 OC35 5 Silicon Rects. 400 PIV 250mA ...	10/-
4 OC75 Transistors Mullard Type ...	10/-
1 Power Trans. OC20 100V ...	10/-
10 OC202 Sil. Diodes Sub-min. ...	10/-
2 Low Noise Trans. NPN 2N929/30 1 Sil. Trans. NPN VCB 100 ZT86 ...	10/-
8 OA81 Diodes ...	10/-
4 OC72 Transistors Mullard Type ...	10/-
4 OC77 Transistors Mullard Type ...	10/-
5 Metal Alloy Transistors Mat. Type ...	10/-
5 GET884 Trans. Eqt. OC44 ...	10/-
2 GET883 Trans. Eqt. OC45 ...	10/-
2 N2708 Sil. Trans. 300Mc/s NPN ...	10/-
5 GT41/45 Germ. Trans. PNP Eqt. OC71 ...	10/-
3 GT31 LF Low Noise Germ. Trans. PNP ...	10/-
6 IN914 Sil. Diodes 75 PIV 75mA ...	10/-
8 OA95 Germ. Diodes Sub-min. ...	10/-
3 NPN Germ. Trans. NKT773 ...	10/-
2 OC22 Power Trans. Germ. ...	10/-
2 OC25 Power Trans. Germ. ...	10/-
2 OC73 Mullard Trans. ...	10/-
4 AC128 Trans. NPN High Gain ...	10/-
2 AC127/129 Comp. pair PNP/NPN ...	10/-
3 2N1307 PNP Switching Trans. ...	10/-
10 CG62H Germ. Diodes Eqt. OA71 ...	10/-
3 AF116 Mullard Type Trans. ...	10/-
12 Assorted Germ. Diodes Marked ...	10/-
4 AC126 Germ. PNP Trans. ...	10/-
1 ORP61 Photo-conductive cell ...	10/-
2 GET880 Low Noise Germ. Trans. ...	10/-

4 Silicon Rects. 100 PIV 750mA ...	10/-
3 AF117 Trans. Mullard Type ...	10/-
7 OC81 Type Trans. ...	10/-
3 OC171 Trans. Mullard Type ...	10/-
5 2N2926 Sil. Epoxy Trans. ...	10/-
7 OC71 Type Trans. ...	10/-
25 Trans. Heatsinks fit TO-18, TO-18 ...	10/-
2 25701 Sil. Trans. Texas ...	10/-
3 12V Zeners 400mW ...	10/-
2 10A 600 PIV Sil. Rects. IS425R ...	15/-
3 BC108 Sil. NPN High Gain Trans. ...	15/-
1 2N910 NPN Sil. Trans. VCB100 80Mc/s ...	15/-
2 1.800 PIV Sil. Rect. 1-5A RS310 AF ...	15/-
3 BSY95A Sil. Trans. NPN 200Mc/s ...	15/-
3 OC200 Sil. Trans. Mullard ...	15/-
2 Sil. Power Rects. BYZ13 ...	15/-
1 Sil. Power Trans. NPN 100Mc/s TK201A ...	15/-
6 Zener Diodes 3-15V Sub-min. ...	15/-
2 2N1132 PNP Epitaxial Planar Sil. Trans. ...	15/-
3 2N697 Epitaxial Planar Trans. Sil. ...	15/-
4 Germ. Power Trans. Eqt. OC16 ...	15/-
1 Unijunction Trans. 2N2646 ...	15/-
2 Sil. Trans. 200Mc/s 60Veb ZT83/84 ...	15/-
1 Unijunction Trans. 2N2160 TO-S can G.E. ...	15/-
2 Sil. Rects. 5A 400 PIV Stud Type ...	15/-
2 Germ. Power Trans. OC28/29 ...	15/-
1 10A Sil. Stud. Rect. 800 PIV ...	15/-
1 Tunnel Diode AEY11, 1,050Mc/s ...	15/-
2 2N2712 Sil. Epoxy Planar HFE225 ...	15/-
8 BY 100 Type Sil. Rects. ...	20/-
25 Sil. and Germ. Trans. Mixed, all marked New ...	30/-
4 OC44 Germ. Trans. ...	10/-

FREE One 10/- Pack of your own choice free with orders valued £4 or over.

★ TESTED DEVICES ★

AC125 ...	2/3	MAT101 ...	3/6
AC176 ...	5/6	MAT120 ...	3/6
AC177 ...	4/6	MAT121 ...	3/6
ACY18 ...	3/6	NKT773 ...	4/6
AF114 ...	3/6	NKT781 ...	3/6
AF139 ...	10/-	OC44 ...	1/9
AF181 ...	10/-	OC45 ...	1/9
AF186 ...	10/-	OC701 ...	4/6
AD140 ...	7/6	OC309 ...	4/6
AD149 ...	7/6	ST140 ...	3/6
AD161 ...	7/6	ST141 ...	4/6
AD162 ...	7/6	2N696 ...	4/6
AFZ12 ...	10/-	2N697 ...	3/6
BC107 ...	5/6	2N320 ...	4/9
BC108 ...	5/6	2N1306 ...	4/6
BC109 ...	5/6	2N1613 ...	4/6
BCY33 ...	5/6	2N2147 ...	15/-
BCY34 ...	6/6	2N2894 ...	8/6
BCZ110 ...	5/6	2N3819 ...	15/-
BCZ11 ...	6/6	2N3920 ...	25/-
BFY50 ...	7/6	2N3906 ...	9/6
BFY51 ...	7/6	2S302 ...	5/6
BFY52 ...	7/6	2S303 ...	4/6
MAT100 ...	3/6	2S304 ...	6/6

TRANSISTOR MANUAL BY G.E. INC. CIRCUITS, APPLICATIONS, CHARACTERISTICS, THEORY. 30/- EACH. 647 PAGES. P.P. 2/6. S.C.R. MANUAL BY G.E. INC. L.A. S.C.R.'s. G.T. SWITCHES, THEORY, RATINGS, APPLICATIONS.

SL70IC Plessey Amplifier INTEGRATED CIRCUIT As mentioned in P.E. articles using I.C.'s. 21/- EACH Also full Plessey range of I.C.'s in stock.

OCP71 8/6 each IMPORTANT NOTICE OWING TO EXPANSION AND REORGANIZATION OUR NEW MAILING ADDRESS IS: BI-PAK SEMICONDUCTORS, 500 CHESHAM HOUSE, 150 REGENT STREET, LONDON, W.1. ALL OUR ADVERTISED STOCKS STILL AVAILABLE. PLEASE SEND C.W.O. Add 1/- Post and Packing. Minimum Order 10/-.

UNIUNCTION

UT46, Eqt. 2N2646, Eqt. TIS43, BEN3000 7/6 EACH

SIL. RECTS. TESTED

PIV 750mA 3A 10A 30A	3/6	4/6	9/6
50 2/6	3/6	6/6	15/-
100 2/3	3/6	6/6	15/-
200 2/6	4/6	6/6	20/-
300 3/6	4/9	8/6	22/-
400 3/6	6/6	9/6	25/-
500 4/6	6/6	9/6	30/-
600 4/3	7/6	10/6	37/-
800 4/9	8/6	15/6	40/-
1000 6/6	10/6	17/6	50/-

SCR's

PIV IAMP 7A 16A 30A	25	7/6	30/6
50 7/6	8/6	10/6	35/6
100 8/6	10/6	15/6	45/6
200 12/6	15/6	20/6	55/6
300 15/6	20/6	25/6	65/6
400 17/6	25/6	35/6	80/6
500 30/6	40/6	45/6	95/6
600	40/6	50/6	—

CADMIUM CELLS

ORP12, ORP60 8/6 each

PRINTED CIRCUITS

EX-COMPUTER Packed with semiconductors and components, 10 boards give a guaranteed 35 trans and 35 diodes. Our price 10 boards 10/- Plus 2/- P. & P.

INTEGRATED CIRCUITS

Epoxy TO5 8 lead µL 900 Buffer @ 11/- µL 914 Dual Gate @ 11/- µL 923 J-K Flip Flop @ 14/- IC circuits data, 1/6 etc.

PLASTIC PLANARS

2N3708A 8 FOR 10/- 20 FOR 20/- 100 FOR 64. FULLY TESTED TRANSISTORS

PAK NO.

U1 120 Glass Sub-min. General Purpose Germanium. Diodes ...	10/-
U2 60 Mixed Germanium Transistors AF/RF ...	10/-
U3 75 Germanium Gold Bonded Diodes Sub-min. Sim. OAS, OA-47 ...	10/-
U4 40 Germanium Transistors like OC81, AC128 ...	10/-
U5 60 200mA Sub-min. Sil. Diodes ...	10/-
U6 40 Silicon Planar Transistors NPN Sim. BSY95A, 2N706 ...	10/-
U7 16 Silicon Rectifiers Top-Hat 750mA Vltg. Range 0-1,000 ...	10/-
U8 50 Silicon Planar Diodes DO-7 Glass 250mA Sim. OA200/202 ...	10/-
U9 20 Mixed Volts 1 watt Zener Diodes ...	10/-
U10 20 BAY50 charge storage Diodes DO-7 Glass ...	10/-
U11 30 PNP Silicon Planar Transistors TO-5 Sim. 2N1132 ...	10/-
U12 12 Silicon Rectifiers Epoxy 500mA up to 800 PIV ...	10/-
U13 30 PNP-NPN Sil. Transistors OC200 and 25104 ...	10/-
U14 150 Mixed Silicon and Germanium Diodes ...	10/-
U15 30 NPN Silicon Planar Transistors TO-5 Sim. BSY50, 2N697 ...	10/-
U16 10 3A Silicon Rectifiers Stud Type up to 1,000 PIV ...	10/-
U17 30 Germanium PNP AF Transistors TO-5 like ACY17-22 ...	10/-
U18 B, 6A Silicon Rectifiers BYZ13 Type up to 600 PIV ...	10/-
U19 30 Silicon NPN Transistors like BC108 ...	10/-
U20 12 1-5A Silicon Rectifiers Top Hat up to 1,000 PIV ...	10/-
U21 30 AF. Germanium Alloy Transistors 2G300 Series and OC71 ...	10/-
U22 10 IA Glass Min. Silicon Rectifiers High Volts ...	10/-
U23 30 MATT's like MAT series PNP Transistors ...	10/-
U24 20 Germanium IA Rectifiers GJM Series up to 300 PIV ...	10/-
U25 25 300Mc/s NPN Silicon Transistors 2N708, BSY27 ...	10/-
U26 30 Fast Switching Silicon Diodes like IN914 Micro-Min. ...	10/-
U27 12 NPN Germanium AF Transistors TO-1 like AC127 ...	10/-
U28 Experimenters Assortment of Integrated Circuits, Untested. Consisting of Gates, Flip-Flops, Buffers, Registers, etc., Dual-In-Line, 8 Assorted Pieces ...	20/-
U29 10 SCR/2 1 Amp 0-500 PIV ...	20/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

TRANSISTOR EQUIVALENT BOOK 52 pages of Cross References for transistors and diodes, types include British, European, American and Japanese. Specially imported by BI-PAK 10/- each.

BI-PAK GUARANTEE SATISFACTION OR MONEY BACK

# BARGAIN PACKS!

- 4 FST3/8 STC Sil. Rectifiers New and Marked 800 piv 1/2 amp. Good substitute for BY100, etc... 13/-
- 4 RAS310AF STC Avalanche Rectifiers New and Marked 1,200 piv 1/2 amp 5A surge rated... 20/-
- 6 GJ4M New and Marked AEI Germanium Rectifiers 50 piv 1 amp... 10/-
- 4 GP297/1 Sub-miniature power transistors Texas New and Marked... 10/-
- 2 ZF16 STC New and Marked 16V 300mW Zener Diodes... 10/-
- 1 Pair of AD161/AD162 NPN/PNP Power Complementary Pair... 15/-
- 1 Pair of AC128/AC176 NPN/PNP Driver Complementary Pair... 10/-
- 1 Set OC82D +2 x OC82 Matched Pair New Mullard Marked... 10/-
- 4 BS195A STC New and Marked Planar Transistors... 10/-
- 4 BC108 Mullard Latest type Low noise planars New and Marked... 10/-
- 6 NKT276 New and Marked Newmarket Audio General purpose transistor... 10/-
- 36 Square inches of 0-15 in Matrix Veroboard—the most popular pack of all—only from LST... 10/-
- 4 NKT162 New and Marked Newmarket Switching Transistor... 10/-
- 2 OC19 New and Marked Mullard Power Transistors... 10/-
- 5 BA115 New and Marked Mullard Colour Television Diodes... 10/-
- 4 2G371B New and Marked Texas Audio Transistors... 10/-
- 4 BYX38/600 Mullard New and Marked Power Studs 600 piv 2 1/2 amp... 16/-
- 1 "Designers Guide to British Transistors" New data book with over 1,000 types listed—Computer selected substitution chart. Just out from Publishers (add 2/6 this item post)... 25/-

POSTAGE AND PACKING BY FIRST CLASS MAIL NOW 1/- MINIMUM PER ORDER

**TIS43A**  
Resistors  
2N2446, 2N2448, 2N2449  
**UNIUNION 6/9d**  
Including data

**2N3819**  
Texas Field Effect Transistor  
10/-

**FAIRCHILD uLogic**  
uL900 Buffer 1-6 7-12 12.5  
uL914 Dual Gate 11/- 9/6 8/4  
uL923 JK Flip Flop 14/- 12/6 11/9  
2 Page data sheets 2/6d

**SL701C** Plessey Integrated Circuits 24/6

**SCR1+2pc1S113**  
For P8 Drill Controller (Entry Issue) 10/- 8/-

**BC107/8/9 2/9d**

**T0716 Tunnel Diode 12/-**

**SILICON RECT'S**

FULLY TESTED GUARANTEED

PIV	200mA	750mA	2A	10A
50	6d	2/3	—	—
100	9d	1/6	2/3	4/6
200	1/3	2/9	5/6	—
400	2/-	2/9	4/-	8/-
600	3/-	—	4/6	9/6
800	—	3/9	5/-	11/6
1,000	—	—	6/4	14/-

**LOOKING FOR QUALITY, VALUE & SERVICE? Write**

**STOP**

2N2926	2/6	AF116	4/4	GET115	9/-	OC83	3/-
2N2972	5/-	AF117	4/4	HAT100	7/9	OC81D	3/-
2N2974	5/-	AF124	4/4	HAT101	6/9	OC82	3/-
2N2975	4/6	AF127	4/4	MAT120	7/9	OC82D	3/-
2N2976	4/6	AF139	15/-	HAT121	8/6	OC83	4/-
2N2977	4/6	AF235	12/-	OAS	3/8	OC123	7/6
2N2978	4/9	AF186	12/-	O47	1/6	OC139	8/-
2N2979	4/9	AF211	3/8	O470	1/6	OC140	12/-
2N2979	4/9	AF211	3/8	O479	1/6	OC149	4/-
2N2979	4/9	AF211	3/8	2xOAPM	4/6	OC170	4/-
2N2979	4/9	AF211	3/8	O481	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O482	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O483	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O484	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O485	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O486	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O487	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O488	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O489	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O490	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O491	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O492	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O493	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O494	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O495	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O496	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O497	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O498	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O499	1/6	OC171	4/-
2N2979	4/9	AF211	3/8	O500	1/6	OC171	4/-

Post and Packing 9d  
Free Export Catalogue

**LST COMPONENTS**  
7 COPPOLD ROAD  
BRENTWOOD ESSEX  
BRENTWOOD 7904  
24 HOUR POSTAL SERVICE

PLEASE SEND 1968 CATALOGUE TO:  
(Black Capitals)  
I ENCLOSE 1/6 STAMPS

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

(PEA)

**BRAND NEW MINIATURE ELECTROLYTICS**, 15 volt, 2, 6, 8, 10, 15, 20, 30, 40, 50, 100 mfd, 8/6 dozen, 30 for £1. The G. R. SUPPLY CO., 127 Chesterfield Rd., Sheffield, S8 0RN.

**TRANSISTOR PANELS**  
New boxed, size 9in x 6in x 1 1/2in with "Valvo" transistors type OC45 or similar, with full length leads, also an equal number of OA85 diodes, H/S resistors, etc. Built on perforated board in a metal frame.

Panel of 20 transistors, diodes, etc. 20/-  
30 — 25/-  
40 — 30/-  
60 — 45/-  
80 — 50/-  
100 — 60/-  
120 — 75/-  
150 — 90/-  
200 — 120/-  
250 — 150/-  
300 — 180/-  
400 — 240/-  
500 — 300/-  
600 — 360/-  
800 — 480/-  
1,000 — 600/-

1/- each, 9/- per doz. Min. order 10/-

**COMPUTER PANELS** with 40 sil. pnp or npn transistors, Diodes and res., 23/6 Post Paid.

**COMPUTER PANELS (Flip-Flop)** with 8-2G371 with diodes, 7/6; without diodes, 5/-, Panel with 16-OC84, etc. 10/-  
" " 8-OC43 or GET875 & OAB1 7/-  
50-OA81 6/-

Postage 6d per panel

**TEST CARDS**, 6 transistors 20 for 20/-  
**ELECTROLYTICS** 25,000 @ 12V, 16,000 @ 12V, 15,000 @ 10V, 10,000 @ 30V, 4,000 @ 60V, 3,000 @ 80V, 2,000 @ 50V, 1,200 @ 180V, 8/6 Post Paid.

**ZENER DIODES** 2-4, 2-7, 3-6, 4-7.5, 5-25, 5-75, 6-2, 6-8, 7-5, 13, 15, 16, 18, 20, 27, 30, 33 volts, 3/6 each, mostly 1 watt

**POLYSTYRENE CAPACITORS 350V**: 180, 270, 330, 390, 470, 560, 680, 820pF, 1,800, 2,200, 2,700, 3,300, 5,600, 6,800, 8,200

**125V**: 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 4,700, 5,600, 6,800, 8,200, 0-015, 80pF ceramic 200pF 5M, any selection 2/- doz. 4-40pF trimmers 4/- doz.

**BRAND NEW BOXED CHASSIS** containing 2-OC25, 2-OC29 12 VVV resistors 30/-, Postage 1/6.

**NEW CROSS RADIO**  
6 OLDHAM ROAD, MANCHESTER 4

**COMPONENTS AT GIVE-AWAY-PRICES!**  
Comprising: Transistors; 1% Resistors; Condensers; Diodes; Valve Holders; plus very useful 9-way plug/sockets. Over 100 components from ex-Brand New Equipment 10/-, or 250 assorted as above 20/- post paid. Order now and avoid disappointment.  
**DIAMOND MAIL ORDER PRODUCTS**, Prospect House, Canal Head, Pocklington, York.


**U.J.T.'s** equiv. 2N2846, TIS43 6/- each. Tested. P. & P. 6d per order. Data supplied, L.F.H. ELECTRONICS, 65 Flanders Mansions, Flanders Road, London, W.4.

**SEMICONDUCTORS**. For sale, 300,000 fully tested, but unboxed silicon transistors and diodes. Standard types, 2N706, 2N706A, 2N2860, 2N708, BSY types, 1N914, etc. Send offers, or for details to Box 15.

<b>RECORDING TAPES</b>	<b>A. MARSHALL &amp; SON (LONDON) LTD</b> 28 Cricklewood Broadway, London, N.W.2 P.E. 20 Tel. 01-452 0161/2				<b>COMPONENTS</b>
<p>Fully Guaranteed</p> <p>7" STD 1,200' 7/3 7" L/P 1,800' 12/3 7" D/P 2,400' 19/- 5 1/2" STD 900' 6/6 5 1/2" L/P 1,200' 9/6 5 1/2" D/P 1,800' 14/9 5" STD 600' 5/3 5" L/P 900' 7/3 5" D/P 1,200' 10/9 3" L/P 185' 2/3 3" D/P 225' 3/- 4" D/P 300' 4/- 7" D/P Concorde 3,000' 33/6 Spools: 8 1/2" 6/3, 7" 2/6, 5 1/2" 2/3, 5" 2/3, 4" 2/-, 3 1/2" 1/9, 3" 1/9, 2 1/2" 1/10.</p> <p><b>CASSETTE TAPES</b> C-60 15/6, C-90 11/6</p> <p>Post and Packing up to 3 reels 2/9, otherwise 4/6.</p> <p><b>SPEAKERS (3 ohm)</b> 8" x 5" 19/6, 7" x 4" 15/6, 3" 9/6, 5" 14/6, 8" 25/6, 12" 39/6.</p> <p>Post and Packing 1/6d</p>	<p>IN914 2/- 2N3707 4/- BF115 4/6 NKT262 4/6 IN916 1/6 2N3708 4/- BFX12 6/6 NKT264 4/6 IS120 2/6 2N3709 4/- BFX13 6/6 NKT271 4/6 IS130 2/6 2N3710 4/- BFX29 15/- NKT403 15/- IS132 2/6 2N3711 4/- BFX84 8/- NKT405 15/- 2N696 5/- 2N3819 10/- BFX85 10/- NKT603 6/6 2N697 5/- OC106 6/- BFX86 8/- NKT613 6/6 2N706 3/- AC127 4/- BFX87 10/- NKT674 6/6 2N708 3/- AC127 3/- BFX88 8/- NKT677 5/- 2N929 6/6 ACY17 5/- BFX50 5/6 NKT713 5/6 2N930 6/6 ACY18 5/- BFX51 4/6 NKT781 6/- 2N1302 4/6 ACY19 5/- BFX52 5/6 OC23 8/- 2N1303 4/6 ACY20 5/- BSX19 5/6 OC26 7/6 2N1304 5/6 ACY21 5/- BSX20 5/6 OC28 7/6 2N1305 5/6 ACY22 4/- BSX21 8/- OC35 7/6 2N1306 6/6 AD140 8/- BSX76 4/6 OC36 7/6 2N1307 6/6 AD149 8/- BSX76 4/6 OC44 3/- 2N1308 8/- AD161 7/6 BSX27 4/- OC45 2/6 2N1309 8/- AD162 7/6 BSX28 4/- OC71 2/6 2N1310 6/6 AF114 5/- BSX29 4/6 OC72 3/6 2N1711 6/6 AF117 5/- BSX38 4/6 OC74 4/6 2N2220 5/- ASY26 4/6 BSX39 4/6 OC75 3/- 2N2369A 8/- ASY27 8/6 BSY40 4/6 OC81 4/- 2N2904 8/- ASY28 6/6 BSY95A 4/- OC83 5/- 2N2905 8/- ASY21 4/6 BFX10 4/6 OC170 6/- 2N2906 8/- BC107 3/6 BZ10 9/- OC171 6/- 2N2906 8/- BC108 3/6 BZ11 7/6 OC200 5/6 2N2926 3/6 BC109 3/6 BZ12 6/- OC201 5/6 2N3053 7/6 BCY33 5/6 BZ13 5/- OC202 8/6 2N3055 19/6 BCY34 4/6 MAT100 6/6 OCPT1 8/6 2N3702 4/- BCY38 6/6 MAT101 6/6 OA91 1/6 2N3703 4/6 BCY39 6/6 MAT120 6/6 OA95 1/6 2N3704 4/6 BCY71 10/6 MAT121 6/6 OA200 2/- 2N3705 4/6 BCY72 6/6 NKT261 4/6 OA202 2/-</p>	<p>Veroboard 3 1/2" x 2 1/2" 3/6; 3 1/2" x 3 1/2" 4/3; 3 1/2" x 5" 5/6; 1 7/8" x 3 1/2" 1/6-1/2; 5" x 2 1/2" 4/3.</p> <p>Cutter 9/- 4 wats 5d; 1 watt 6d; 2 watt 1/-; 3 watt 1/6; 5 watt 2/0.</p> <p><b>Electrolytics:</b> 15V 1MFD up to 100MFD 1/6, 25V 25MFD or 50MFD 1/6, 100MFD 2/9, 250MFD 2/9, 500MFD 3/9.</p> <p><b>Presets:</b> STD Horizontal or Vertical 1/6.</p> <p><b>Fairchild ICs.</b> L900 11/- L914 1/- L923 14/-</p> <p>Silvered Mic-20 up to 820pF 1/6.</p> <p>Post and Packing for Transistors and Components 1/- per order. Send 6d stamp for complete list.</p>			

## RECEIVERS AND COMPONENTS (continued)

### WE ARE BREAKING UP COMPUTERS

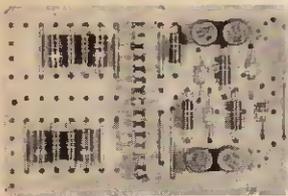

**COMPUTER PANELS** (assorted) 2 x 4in. 8 for 10/-, POST FREE, with min. 30 transistors.  
**100 for 65/- + p. & p. 6/6**, 1,000 for **£30 + carr.**  
**GIANT PANELS** 5 1/2 x 4in. with 20 Transistors, 30 Min. Diodes, 56 Min. Resistors and 9 560H Inductors on each board, 3 for **£1**. Post Free.  
**PANELS** with 2 Power Transistors slt. to OC28 on each board + components, 3 Boards (4 x OC28) 10/-  
**POWER TRANSISTORS** stan. 2N174 Bx. Eqpt. 4 for 10/-, p. & p. 1/-  
**OVERLOAD CUT OUTS** Panel Mounting in the following values at 5/- each. 11, 2, 3, 4, 5, 7, 8 amp.  
**TOS TRANSISTOR COOLERS**, 7/6 doz.  
**MINIATURE GLASS NEONS**, 12/6 doz.  
**LONG ARM TOGGLE SWITCHES**, ex. eqpt. 16/- doz., p. & p. 2/6.  
**NEW MIXED DISC CERAMICS**, 150 for 10/-, p. & p. 1/-  
**LARGE CAPACITY ELECTROLYTICS**, 4 1/2in. 2in. diam. Screw Terminals. All at 6/- each. 4/18 each, p. & p.  
 4,900 Mfd. 75v. D.C. wkg. 10,000 Mfd. 30v. D.C. wkg. 6,300 Mfd. 75v. D.C. wkg. 25,000 Mfd. 15v. D.C. wkg. 10,000 Mfd. 35v. D.C. wkg. 1,500 Mfd. 180v. D.C. wkg.  
**KEYTRONICS**, 52 Earls Court Road, London, W.8  
*Mail order only. Send 1/- stamps for list.*

## TAPE HEADS

**BSE BRAD. 39/6** pair  
2 TRACK  
**BSE MAIL 39/6** pair  
4 TRACK  
**REUTER - COLLARO ERASE 2/6**  
4-TRACK  
**F.M. WIRELESS MICROPHONE**  
 94-104Mc/s. Transistorised. Operates from 9V battery. Complete with additional secret tin clip microphone. List **£12/10/- ONLY**. These cannot be exported in U.K. **£6.15.0**

**TRANSISTORISED FM TUNER**  
 6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in x 4in x 2 1/2in 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 85-105Mc/s. Ready built ready for use. Fantastic value for money **£6.17.6**

**FM MULTIPLEX STEREO ADAPTOR**  
 Printed circuit biscuit, 4 trans. 6 diodes 9V with full instructions **£5.19.6**

**LOUDSPEAKERS 12"**  
 20 watt, 15 ohm. SUPER **£5.10.0**  
**12" 25 watt, 16 ohm, GUITAR SPEAKER** **£5.15.0**

**FULL RANGE HIGH COMPLIANCE. 8" 16 ohm, 15 watt** **£6.2.6**  
**30-20K**

**6 1/2" 16 ohm, 10 watt, 30-15K** **£5.5.0**  
**4" 16 ohm, 5 watt, 40-16K** **£3.6.0**

**MULTIMETERS** from **32/-**  
**SWITCH ROTARY. RECIPROCATING 4 POSITION, 15A.** **5/-**

**LOUDSPEAKERS. 2" 3/8**  
 40 ohm, 2 1/2" 80 ohm. **12" TWIN COILS 10** **35/-**  
 12" 15 or 30 ohm. **TWEETER 16 ohm** **29/6**  
 10 watt, 18K-CPS. **CROSSOVER NET- WORK 16 ohm** **15/6**

**REFLEX CONE TYPE WATERPROOF SPEK.**  
 5 watt, 8 ohm, 900. 16,000c/s PA & Music Relay **£4.5.0**

**SUPER SILICON RECT. T.V., etc.**, 1,200 PIV 800mA, 6/- or complete with inst. resistor, condenser, 7/8; 400 PIV HW 6A, 6/-; 200 PIV HW 6A, 6/-.

Stamped envelope for full selection and bargain offers in Multimeters, Radios, Baby Alarms, Intercoms, Walkie-Talkies, Rectifiers and Eagle Lists. UNDER £1-P. & P. 6d. OVER £1 post free, C.O.D. 3/6. MAIL ORDER ONLY.

## DURHAM SUPPLIES

367F, KENSINGTON STREET  
 BRADFORD 8, YORKSHIRE

## RECEIVERS AND COMPONENTS (continued)

**BARGAIN PARCELS** of new surplus Electronic Components, 3/-, 5/-, 10/-, post free. DOLPHIN ELECTRONICS, 5 Pooles Way, Brixia Close, Burntwood, nr. Lichfield.

**REPANGO** Transistor Coils and Transformer, for the Constructor. Send stamp for lists RADIO EXPERIMENTAL PRODUCTS LTD., 33 Much Park Street, Coventry.

## ELECTRICAL

**240 VOLT ELECTRICITY ANYWHERE**



most brilliant performance ever from 12-volt Car Battery. BRILLIANT HEAVY DUTY 240 volt AMERICAN DYNAMOTOR with BIG 220 WATT OUTPUT. Marvellous for TELEVISION, ELECTRIC DRILLS, MAINS LIGHTING and ALL UNIVERSAL AC/DC MAINS EQUIPMENT. Marvellous for Fluorescent lighting. Thousands of uses. Tremendous purchase of this de luxe model makes fantastically low price possible.

ONLY £6 each plus 10/- delivery. C.O.D. with pleasure. MONEY BACK if not DELIGHTED. Please send S.A.E. for full illustrated details.

Dept. PE, STANFORD ELECTRONICS  
 Rear Derby Road, North Frammade  
 BLACKPOOL, Lancashire

## MODERN DICTIONARY OF ELECTRONICS 70/-

AUTHORITATIVE, COMPREHENSIVE, COMPLETELY UP TO DATE, BY GRAF. 3rd ED. POSTAGE 4/6.

**DESIGNERS GUIDE TO BRITISH TRANSISTORS** by Kampel. 25/-, P. & P. 1/6.

**ELECTRONIC MUSICAL INSTRUMENT MANUAL**, new 5th ed. by Douglas. 55/-, P. & P. 3/-.

**PAL COLOUR T.V.** by Mullard. 12/6. P. & P. 1/-.

**SILICON CONTROLLED RECTIFIERS** by Lytel. 21/-, P. & P. 1/3.

**COMPUTERS FOR THE AMATEUR CONSTRUCTOR** by Warring. 20/-, P. & P. 1/-.

**ABC'S OF TRANSISTORS** by Mann. 20/-, P. & P. 1/-.

**ELECTRONIC GAMES AND TOYS YOU CAN BUILD** by Buckwalter. 24/-, P. & P. 1/-.

**SOLID STATE POWER SUPPLIES AND CONVERTERS** by Lytel. 20/-, P. & P. 1/-.

**F.E.T. CIRCUITS** by Turner. 25/-, P. & P. 1/3.

**ELECTRONIC MOTOR CONTROL** by Lytel. 30/-, P. & P. 1/3.

## UNIVERSAL BOOK CO.

12 LITTLE NEWPORT ST., LONDON, W.C.2  
 (Leicester Square Tube Station)


## BATTERY ELIMINATORS

The battery of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 9v; 7 1/2v; 6v; 4 1/2v (single output) 39/6 each. P. & P. 2/9. 9v + 9v; 6v + 6v; or 4 1/2v + 4 1/2v (two separate outputs) 42/6 each. P. & P. 2/9. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.  
 (Dept. P.E.), 31 Oliver Road, London. E.17

## ELECTRICAL

**HEAT LIGHT SPEED CONTROL Unit**

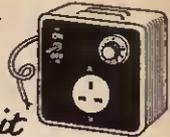

An Electronic unit capable of controlling electrical equipment up to 3,000 watts capacity. Fingertip control of all a.c./d.c. electrical equipment. Suitable for all types of lighting arrangements. Incandescent lamps. Spot lamps. Arc lamps. Floodlights. Makes an ideal dimming unit. Ideal for controlling all types of electric drills and up to 2 h.p. electric motors for all applications. Ideal for all types of electric heaters. Suitable for lathes and power tools. Contains the latest electronic switching devices and associated thyristor circuitry. Size 6 x 5 x 2 1/2in. Louvred metal case in pleasing hammer finish. Attractive front panel with matching socket and controls. Recommended price 25 gu. Huge purchase enables us to offer them at **£8.19.6**, carriage and insurance 10/-, C.O.D. if required.

## AIRCRAFT - POLICE BAND BROADCAST REC.

A small transistorised receiver that will receive civil aircraft and police/fire/ambulance broadcasts. Operates from a 9 volt battery that fits internally. 6 transistors. Robust metal cabinet size approx. 7 x 4 x 4in. Attractive front panel. Speaker or headphone output. Improved type de luxe model price **£8.10.0**, carriage 10/-. Few only. Brand new and unused.

## TRANS/RECEIVERS AIR/SEA/RESCUE TYPE

Must be dismantled or exported. Complete with mike/speaker aerial. Work up to 100 miles. Cost Govt. over £40 each. **£2.10.0** per set, 10/- P. & P. 2 sets **£5**, post free.

## TRAWLER TOP BAND RECEIVER KIT

This wonderful little set will provide hours of listening pleasure. Listen to the thrilling sound of an SOS at sea. Super for listening to the Hams at work. A printed circuit layout makes it simple to build in a short time. Fully comprehensive instructions. Employ the latest components and transistors. Complete down to the last detail. An ideal project for beginners. Price **£6.10/-**, Post 6/-. Matching speaker and cabinet 30/- extra.

## 40 METRE BAND RECEIVER

These excellent receivers were made for the Government by a famous manufacturer. They will cover the complete amateur band. Aircraft, Marine and other Government Stations. It is a 5 valve superhet and works from standard dry batteries. Built in a robust metal case size 10 x 6 x 4in. Half moon calibration tuning dial. Phone or speaker output. Not new but in excellent condition. **£3.10.0**, carriage 10/-. Few only. Also complete with associated transmitter covering same band (for export, or licenced use). Price **£5.15.0**, carriage 15/-.

**MINIATURE TRANSISTORISED BFO UNITS.** This small fully transistorised tunable BFO unit will enable any set to receive CW or SSB reception. Compact single hole fixing. Full fitting details. Only 49/6, P. & P. 3/6.

**MOVING COIL HEADPHONES AND MICROPHONES.** Brand new in makers' cartons, 25/-, P. & P. 5/-.

New Component Centre open at this address.

**GLOBE SCIENTIFIC LTD.**  
 DEPT. P.E. 15, 24 CAWOODS YARD,  
 MILL STREET, LEEDS 9

**PARKERS SHEET  
METAL FOLDING  
MACHINES  
HEAVY VICE  
MODELS**



With Bevelled Former Bars

Carr. free

- No. 1. Capacity 18 gauge mild steel x 36in. wide ... £12.10.0  
 No. 2. Capacity 18 gauge mild steel x 24in. wide ... £7.5.0  
 No. 3. Capacity 16 gauge mild steel x 18in. wide ... £7.5.0  
 Also new bench models. Capacities 48in. x 18 gauge £40. 36in. x 18 gauge £25. 24in. x 16 gauge £24. Carriage free.

End folding attachments for radio chassis. Tray and Box making for 36in. model, 5/6 per ft. Other models 3/6. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 3997

**HI-FI AUDIO PRINTED CIRCUITS**

READY DRILLED WITH CIRCUIT DIAGRAMS

**ACS.1** Pre-Amplifier for magnetic p.u., etc. plus high impedance circuit or high impedance circuit with tone control complement. Two Boards make complete Hi-Fi Pre-Amplifier. 17/- per Board.

**ACS.6** Complete circuit board for 5 watt + 5 watt rms transistor amplifier and high impedance Pre-Amplifier. Mains Powered. Heat sinks mounted on circuit board. 50/- per Board.

All components supplied separately or in kit form. **ADVICE IS FREE. AFTER SALES SERVICE GUARANTEED.** Styling and results more than satisfy. Chassis, Facias, Cabinets made to order. Callers welcome. S.A.E. for lists.

**AUDIO COMPONENTS AND SERVICES**

SOUND STUDIOS, BELL HILL (OFF CROWN HILL), CROYDON, SURREY. PHONE 688 3706

**TWO SCOOPS FROM "KING'S"  
CONTINUOUS LOOP**

(NEVER ENDING - NO REWINDING)

**TAPE CASSETTE**

**BULK PURCHASE  
RIDICULOUS PRICE**

IDEAL BACKGROUND MUSIC - LANGUAGE COURSES, ETC. 200ft. HIGH QUALITY AMPEX TAPE. WILL FIT ALL TAPE RECORDERS.

CANNOT BE REPEATED

NEARLY ALL GONE  
HURRY! NOW ONLY **18/-** EACH P&P 6d.

ALSO

**BARGAIN PRICED-PHILIPS TYPE CASSETTES  
TO FIT ALL CASSETTE RECORDERS**

TYPE C.90 LASTS 1½ Hrs. 18/11d

TYPE C.60 LASTS 1 Hr. 12/11d

SEND NOW. (post & pack 6d each)

**KING'S TELE-SERVICE CO.**  
105/107 DAWES ROAD, FULHAM, S.W.6  
FULHAM 1668-2998

**ELECTROVALUE**

**Rapid Mail Order Service  
UNBEATABLE VALUE IN NEW SEMICONDUCTORS**

30 watt BAILEY AMPLIFIER complement

40861 12/8; 40862 16/8; BC125 12/-;  
 40863 12/8; 40864 16/8; BC107 2/8; BC109 3/8;  
 40865 12/8; 40866 16/8; BC125 12/-;  
 40867 12/8; 40868 16/8; BC107 2/8; BC109 3/8;  
 40869 12/8; 40870 16/8; BC125 12/-;  
 40871 12/8; 40872 16/8; BC107 2/8; BC109 3/8;  
 40873 12/8; 40874 16/8; BC125 12/-;  
 41359 12/8; 41360 16/8; BC107 2/8; BC109 3/8;  
 41361 12/8; 41362 16/8; BC125 12/-;  
 41



## RADIO TECHNICIAN TRAINING



IN THE

# RAAF

Vacancies exist in the Royal Australian Air Force for men who are interested in being trained in the Technical Radio fields. Applicants should be United Kingdom citizens resident in the U.K. aged between 18 and 33 years. Qualified personnel up to the age of 43 years are also invited to apply.

*Free passage to Australia is provided for families and pay commences from date of enlistment in London.*

Further information can be provided by writing or phoning:—

**RAAF CAREERS OFFICER (Dept. P.E.) AUSTRALIA HOUSE  
STRAND, LONDON W.C.2 Telephone No: 01-836 2435**

### EXCLUSIVE OFFER

KITS for Transformerless Amplifiers, ZENER DIODES, ASSORTMENTS of Capacitors, Potentiometers, Carbon Film Resistors and branded new. ORIGINAL TRANSISTORS

(Except from our SPECIAL OFFER B/1968)

**KIT No. 7 for high quality, high power A.F. transformerless amplifier**

6 transistors 20W only 59/-  
Supply voltage 30V  
Working current 40-1, 300mA  
Loud-speaker connection 4 ohm  
Input voltage at max. vol. 20mV  
Input resistance 2Kohm  
Frequency range 20Hz-20KHz

Printed circuit panel for KIT No. 7

The circuit diagram and the parts list are enclosed with every KIT  
**ZENER DIODES 1W 4.3, 5.6, 6.2, 6.6, 7.5, 8.2, 9.1, 10, 11, 12V 2/4 each**

**ASSORTMENTS of ELECTRONIC COMPONENTS**

**ORDER No.:**

<b>DIO 3</b>	100 p. germanium diodes sub-miniature	13/4
<b>TRA 1</b>	50 p. different transistors	13/4
<b>ZE 101</b>	10 p. zener diodes different values 250mW-1W	22/6
<b>ELKO 1</b>	30 p. 1.f. Electrolytic capac. sub-min. good sel.	16/-
<b>KER 1</b>	100 p. disk-, tubular-and pearl capac. 20 val. x 5	12/6
<b>KON 1</b>	100 p. plastic foil condens. 20 val. x 5 good sel.	12/6
<b>EIN 1</b>	10 p. adjust. potentiom. ohm values good select.	8/6
<b>WID 1-1/8</b>	100 p. carbon film resist., axial, 1/2W 20 val. x 5	12/-
<b>WID 1-1/2</b>	100 p. carbon film resist., axial, 1/2W 20 val. x 5	12/-

**BRAND NEW ORIGINAL TRANSISTORS**

AC 153	AC 128 1/4	AF 27 = AC 127 1/6	AF 144 = AF 116 1/9
AC 188K	AC 178 2/-	AF 149 = AF 117 1/4	
AD 136	2/3	AF 142 = AF 114 2/-	RF 107 = BC 107 1/6
AD 150	3/6	AF 143 = AF 115 1/9	2N 706 = BSY 62 1/6

All goods BRAND NEW of HIGH QUALITY, fully guaranteed. NET Prices Subject to prior sale.

Our deliveries are ex stock Zurich/Switzerland by air-mail C.O.D. Postage and packing will be charged at self-costs.

Please request our complete free SPECIAL OFFER B/1968.  
We shall be very pleased to receive your trial order:



**EUGEN QUECK**

**CH-8810 HORGEN  
Switzerland**

**Ingenieur-Büro  
Import-Export  
Bahnhofstr. 5**

### PHONE

## WENTWORTH RADIO

BAR 3087

104 SALISBURY ROAD, HIGH BARNET

BC109	4/-
BCY70	5/-
BFY51	4/9
BY127	4/6
OAB1	1/6
OA95	1/6
2G301	4/3
2G302	6/-
2G303	4/7
2G308	7/3
OC71	2/3
OC72	2/6
OC81D	2/3
OC170	2/3
OC171	2/3

**CASH WITH ORDER**

### THIS MONTH'S BARGAINS

"Special Offer"

BC107	Genuine	3/-
BC108	Genuine	2/11

Send S.A.E. for latest Price List  
All Components Now Supplied

QUOTATIONS SUPPLIED  
FOR LARGE QUANTITIES

NKT713	5/3
NKT717	8/3
NKT773	4/9
NKT271	4/-
NKT272	4/-
NKT274	4/-
NKT275	4/-
NKT304	14/6
NKT403	16/-
NKT404	14/-
2N3702	4/6
2N3706	4/6
2N3707	5/3
2N3708	3/-
2N3709	3/4

P. & P. 1/-

### EAGLE MULTIMETERS

EP30K, 120/-, p.p. 4/6; EP10KN, 100/-, p.p. 4/6;  
EP20KN, 90/-, p.p. 3/6; EP30KN, 150/-, p.p. 4/6;  
EP50LN, 210/-, p.p. 4/6, details on request.

High Stability Resistors 1% 1W, 2W. Full standard range plus many multimeter values. 5% 1/2W, 4d. Full stock list on request.

0-50 microamp level meters, 15/-, post 1/-

High Res. Phones, 3,000 Ohm, 15/-, p.p. 1/-

Multimeter ITI-2, 20,000 o.p.v. d.c., 0-5, 25, 50, 250, 2,500V d.c., 10, 50, 100, 500, 1,000V a.c.; 0-50µA, 0-2.5mA, 250mA; 0-50K Ohm. 0-63M Ohm. capacity and dB ranges, 70/-, post 3/-

Postage extra, cash with order.

**PLANET INSTRUMENT CO.**  
25(E) DOMINION AVENUE, LEEDS 7

### 12in. DE-LUXE MKII £9

The exceptional quality and performance of the "De-luxe MKII" brings truly breathtakingly rich sound from a single loudspeaker, recreating the musical spectrum virtually flat from 25 to 16,000 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special Baker "FERROBA" magnet assembly having a flux density of 14,000 gauss and a total flux of 150,000 Maxwells. Bass resonance 32-38 c.p.s. Rated 15 watts. Voice coils available 3 or 8 or 15 ohms. Suitable for any High Fidelity System. Design capability concept has programmed third generation hardware giving fantastically delightful sound at this amazing bargain price.



48 page Enclosure Manual 5/9 post paid.

**Baker Reproducers Ltd**

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684 1665

**YUKAN SELF-SPRAY** SO PROFESSIONAL THE YUKAN AEROSOL WAY-  
Get these air drying GREY HAMMER NOW! OR BLACK WRINKLE (CRACKLE) finishes

Yukan Aerosol spraykit contains 16 oz. fine quality, durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 14/11 at our counter or 15/11 carriage paid, per push-button self-spray can. Also Durable, best and water resistant Black Matt finish (12 oz. self-spray cans only) 13/11 carriage paid.

SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/6) for 18/11, carriage paid. Choice of 13 self-spray plain colours and primer (floor car quality) also available.

Please enclose cheque or crossed P.O. for total amount to:

**YUKAN, DEPT. PE/1 307A, EDGWARE ROAD, LONDON, W.2**

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too.

Closed All December for Annual Holiday

Other Yukan Air Drying Aerosols, 16 oz. or 13 1/2 oz. can, include:  
Zinc Chromate  
Clear Lacquer  
Metallics: Grey, Blue, Bronze and Gold.



# VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had your copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

## On 'SATISFACTION OR REFUND OF FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

### WHICH OF THESE IS YOUR PET SUBJECT?

**ELECTRONIC ENG.**  
Advanced Electronic Eng.—  
Gen. Electronic Eng.—  
Applied Electronics—  
Practical Electronics—  
Radar Tech.—  
Frequency Modulation—  
Transistors.

**ELECTRICAL ENG.**  
Advanced Electrical Eng.—  
General Electrical Eng.—  
Installations—  
Draughtsmanship—  
Illuminating Eng.—  
Refrigeration—  
Elem. Elec. Science—  
Elec. Supply—  
Mining Elec. Eng.

**CIVIL ENG.**  
Advanced Civil Eng.—  
General Civil Eng.—  
Municipal Eng.—  
Structural Eng.—  
Sanitary Eng.—  
Road Eng.—  
Hydraulics—  
Mining—  
Water Supply—  
Petrol Tech.

**RADIO & T.V. ENG.**  
Advanced Radio—  
General Radio—  
Radio & TV Servicing—  
TV Engineering—  
Telecommunications—  
Sound Recording—  
Automation—  
Practical Radio—  
Radio Amateurs' Examination.

**MECHANICAL ENG.**  
Advanced Mechanical Eng.—  
Gen. Mech. Eng.—  
Maintenance Eng.—  
Diesel Eng.—  
Press Tool Design—  
Sheet Metal Work—  
Welding—  
Eng. Pattern Making—  
Inspection—  
Draughtsmanship—  
Metallurgy—  
Production Eng.

**AUTOMOBILE ENG.**  
Advanced Automobile Eng.—  
General Auto. Eng.—  
Auto. Maintenance—  
Repair—  
Auto. Diesel Maintenance—  
Auto. Electrical Equipment—  
Garage Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power? A.M.I.E.R.E., B.Sc.(Eng.), A.M.S.E., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., A.M.I.Ex., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., C.ENG., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY  
316A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

### THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointments Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

132 PAGES OF EXPERT CAREER - GUIDANCE

#### PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Electronics, Radio, T.V., Etc., A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Electronics Electronics Engineering Practical Radio Radio & Television Servicing Automation

#### INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

## B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES"—send for your copy NOW—FREE and without obligation.



### POST COUPON NOW!

TO B.I.E.T., 316A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME .....

ADDRESS .....

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

## THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

Published about the 15th of the month by GEORGE NEWNES LIMITED, Tower House, Southampton Street, London, W.C.2, at the recommended maximum price shown on the cover. Printed in England by THE CHAPEL RIVER PRESS, Andover, Hants. Sole Agents—Australia and New Zealand: GORDON & GOTCH (A/sia) Ltd.; South Africa and Rhodesia: CENTRAL NEWS AGENCY LTD.; East Africa: STATIONERY & OFFICE SUPPLIES LTD. Subscription rate including postage for one year: To any part of the World £2 2s. 0d.

Nearly 1,700 Circuits & Diagrams plus full repair data for

# 800 POPULAR MODELS

**GREAT  
NEW  
EDITION**

## RADIO & TV SERVICING

### Big time-saving repair library steps up your earnings

Here is a great new edition of RADIO & TV SERVICING, to save your time, to boost your earning-power. Packed with CIRCUITS, REPAIR DATA and vital information it covers all the popular 1965-1968 TVs, Radios, Grams, Record Players and Tape Recorders—including latest data on COLOUR TV. Thousands of sets of previous editions sold. Now you can examine this big NEW edition free for a week. 3 handsome volumes—over 1,500 pages written by a team of research engineers—there's no other publication like it. Hurry—send no money—simply post this leaflet . . . There can be no reprint once stocks are sold and there's absolutely no obligation to buy under this free trial offer.


FULL DATA & CIRCUITS FOR REPAIR OF

● TELEVISIONS INCLUDING
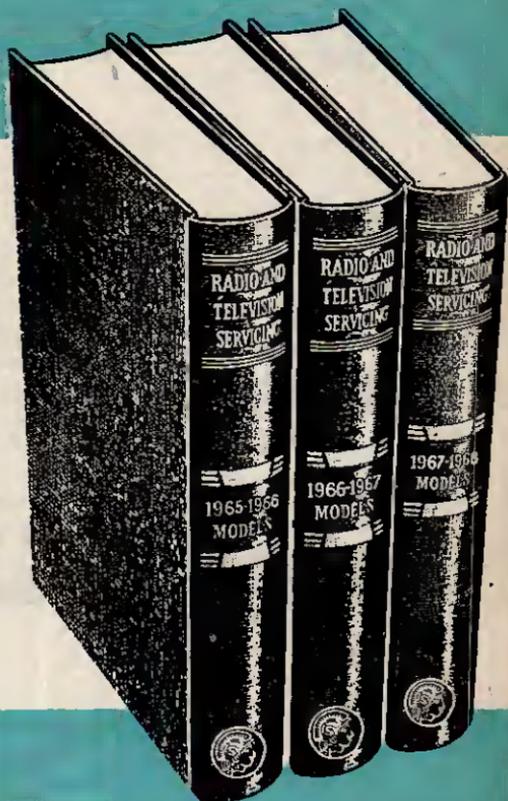
## COLOUR TV

- RADIOS, RADIOGRAMS
- CAR RADIOS
- RECORD PLAYERS
- TAPE RECORDERS

Nearly 60 leading makes covered  
from *Alba* to *Decca*, from *Ferguson*  
to *Sanyo*—full list shown overleaf.



It's yours — by post on a week's


# FREE TRIAL

SEND NO MONEY—SIMPLY POST  
THIS REPLY-PAID LEAFLET TODAY

SEE ON BACK FOR YOUR FREE TRIAL FORM

# RADIO & TV SERVICING
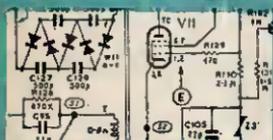
## POPULAR MODELS—1968 RIGHT BACK TO 1965




Circuit diagrams




Printed panel diagrams



Component layout diagrams

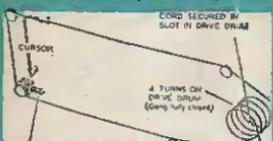

Drive-cord diagrams

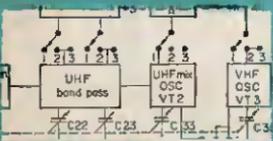

Block diagrams

### SERVICING DATA FOR ALL THESE MAKES

Aiwa, Alba, Baird (including colour TV), Beogram, Beolit, Bush, Carousel, Corsor, Dansette, Decca, Defiant, Dynaport, Dynatron, Eddystone, Ekco, Elizabethan, Ever Ready, Ferguson, Ferranti, Fidelity, G.E.C. (including colour TV), Grundig, H.M.V., Kolster-Brandes, Hitachi, Invicta, McMichael, Marconiphona, Masteradio, Motorola, Murphy, National, Newmatic, Pam, Perdio, Peto-Scott, Philips (including colour TV), Portadyne, Pye, Radiomobile, R.G.D., Regentone, Roberts' Radio, Sanyo, Sharp, Smith's Radiomobile, Sobell (including colour TV), S.T.C., Sony, Standard, Stella, Stereo-sound, Teletron, Thorn, Trans Arena, Ultra, Van Der Molen, World Radio.

### PLUS LATEST DEVELOPMENTS IN RADIO & TELEVISION

Including—Integrated Tuners, Stereo Multiplex Broadcasting—The Zenith-G.E. System: Receiver, Decoder and adjustments, Aerial, etc. Colour TV Receivers, Colour TV Test Card F, Servicing Transistor Equipment, Chemical Aids to Servicing, Batteries and Rechargeable Cells, Sound-on-Sync., Double Line Sync., Silicon Transistors, etc.

**OVER 1,500 PAGES, 1,644 CIRCUITS, COMPONENT LAYOUT DIAGRAMS, PRINTED PANEL DIAGRAMS, TABLES AND WAVEFORM GRAPHS.**

*Handsomely bound in rich maroon and gold.*

**SEND FOR YOUR FREE TRIAL SET TODAY**

**ABSOLUTELY NO OBLIGATION TO BUY**

**See it FREE**

Complete section below, fold along A to A turning this section under. Then fold across at B and C and tuck B into C so reply-paid section shows. Post today.

Please tick (✓) here

This address is for a

new property

flat

furnished flat

furnished apartment

temporary

holiday

if one of the above, please show here

If you are under 21 your father must fill in this section.

Name:.....

(BLOCK LETTERS)

Address:.....

County:.....

Occupation:.....

Signature:.....

Mr. Mrs. Miss

Please send RADIO & TV SERVICING—1965/68 Models in 3 volumes without obligation to buy if you Full accept my application. I will return the book(s) in 8 days or post—

Tick (✓) here

Full cash price of £12, or

15/- deposit and 16 monthly payments of 15/-


Also send me on 7 days trial PRACTICAL ELECTRICAL ENGINEERING.

For Eire and N.I. send cash price with coupon. Elsewhere overseas send cash price plus 20/- post, packing and insurance.

RV3/PEE/3688

Postage will be paid by Buckingham Press Ltd.

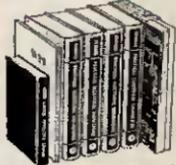No postage stamp necessary if posted in Gt. Britain or Northern Ireland



Tick coupon above to examine PRACTICAL ELECTRICAL ENGINEERING 4 Handsome Volumes Plus case of 36 charts and pocket book

Over 2,000 explanatory drawings and photos, 2,350 pages, it includes—Installation Work of all Kinds—Wiring regulations, testing, etc. Instruments, Machines, Equipment—Motors and Control Gear, Transformers, Rectifiers, Instruments. Operation, Maintenance, Repair—Generation, Transmission, Distribution, etc.

If kept after free trial, 16/- deposit then 16 monthly payments of 20/- paying £16.16s in all. Cash in 8 days £16.

BUSINESS REPLY SERVICE  
Licence No. OF. 381/1

BUCKINGHAM PRESS LTD.,  
18-19 WARREN STREET,  
LONDON, W.1

# ENGLANDS LEADING COMPONENT & EQUIPMENT CENTRES

## SOLID STATE-HIGH FIDELITY AUDIO EQUIPMENT

Audio Equipment developed from Dinsdale Mk.II—each unit or system will compare favourably with other professional equipment selling at much higher prices.

COMPLETE SYSTEMS FROM **£15.5.0**

THE FINEST VALUE IN HIGH FIDELITY—CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS

All units available separately.

SEND FOR 16 PAGE BROCHURE (No. 21) TODAY! DEMONSTRATIONS DAILY AT '303' EDGWARE ROAD



## Acclaimed by everyone THE MAYFAIR ELECTRONIC ORGAN



A completely new development in portable electronic musical instruments and a new field for the home constructor. The 'MAYFAIR' produces a multitude of the most pleasing sounds with a wide range of tone colours suitable for classic or popular music. The organ is fully polyphonic, that is full chords can be played over the entire keyboard. Supplied as a kit of parts which includes 185 transistors, printed circuit panels, special fully sprung and depth of touch adjusted keyboard, attractive vinyl covered cabinet with carry handle. A complete detailed and illustrated construction manual is provided with circuits and full parts lists. Cost can be spread by purchasing the components packet by packet. All parts supplied are fully guaranteed. Full after sales service.

A new source of construction for the keen electronics fan either amateur or professional. Once built the 'MAYFAIR' will then provide years of enjoyable entertainment. **TOTAL COST 99 Gns.**

ORGAN COMPONENTS - We carry a comprehensive stock of organ components for TRANSISTOR AND VALVE FREE PHASE designs. Defensed terms available. COMPLETE KIT Deposit £29.19.0. 12 monthly payments of £7. TOTAL £113.19.0. BUILT AND TESTED Deposit £38.8.0 and 12 monthly payments of £9. Total £144.8.0. EXPORT ENQUIRIES INVITED

## BRITISH MADE CAR RADIOS

A fine precision engineered car radio that's perfect company for long hours on the road. So easy to install and operate—and the price is exactly right. Has quick push-button operation for immediate station selection and choice of Medium or Long wave frequency. Manual tuning facilities. Push-button controls. Output of 3½ watts ensures clear, top quality sound even at high motoring speeds. Price includes 7" x 4" speaker, full accessories and instructions.

POSITIVE OR NEGATIVE EARTH EASI-TUNE £12.12.0. pp. 4/6 £10.10.0. pp. 4/8  
AUTOBAHN MANUAL as the EASI-TUNE, but with a single MW/LW Push Button.  
CAR AERIALS \* 3-Section Single Hole Wing or Boot Mounting 19/6 Brochure 15 Multi Section fully disappearing type with locking device, single hole mounting 35/- Post free with Car Radio or pp. 2/8 separately.

## TRANSISTOR AMPLIFIER

INTEGRATED 7 WATT AMPLIFIER & PREAMPLIFIER—MAY With Full Bass Treble and Volume Controls  
A brilliant new design suitable for home or portable installations. For use with magnetic and crystal/ceramic cartridges, radio tuners, microphones, tape head replay and auxiliary inputs. Output is for 3 to 16 ohm speakers. It favours the user in so many ways—with fantastic power, with far greater adaptability, with freedom to operate it from batteries or mains power supply unit (the new PS 20 is ideal for this), hi-fi installations, electronic guitars and organs, P.A. installations, intercom systems, etc. This 7-watt amplifier is supplied ready built, tested and guaranteed.

For complete listening satisfaction. FOR ONLY £8/10/0 P.P. 4/- (OPTIONAL MAINS UNIT PS.20 62/2, P.P. 3/-) Illustrated Brochure No. 12.

## BUILD THESE PRACTICAL DESIGNS

LIST		
I.C.F.M. TUNER	£5.2.6.	39B
Switched F.M. Tuner	£3.17.6.	308
Fluorescent Camping Light	£3.2.6.	43

Let us have your enquiries for parts for current PW and PE designs. S.A.E. PLEASE.



## NEW MODELS NOMBREX

TRANSISTORISED Test Equipment  
PRICE Leaflet  
MODEL £ s. d. No.  
22 Power Supply 14 0 0 22  
30 Audio Generator 19 10 0 24  
31 R.F. Generator 12 10 0 25  
32 C.R. Bridge 19 10 0 26  
33 Inductance Bridge 20 0 0 29  
Send for descriptive illustrated Brochure.



## DO IT YOURSELF MW/LW PORTABLE

New printed circuit design with full power output. Fully tunable on both MW/LW bands. 7 transistors plus diode, push-pull circuit. Fitted 5 inch speaker, large ferrite aerial and Mullard transistors. Easy to build with terrific results. All local and Continental stations.  
**TOTAL COST £6.19.6.** P.P. 4/6  
TO BUILD (Send for Brochure)

## MULLARD 1 WATT AMPLIFIER

WITH VOLUME CONTROL Suitable 7 x 4 inch 3 ohm speaker 17/6 Ideal for Portable Record Players, Inter-Comms, Baby Alarms etc. pp. 4/6 For 9 Volts operation. **45/-** 3/6d.

## ITS SO EASY TO BUILD TO PROFESSIONAL STANDARDS

To get the best out of your MAGNADOX STEREOGRAPHIC DECK Type 363, you need a MARTIN RECORDKIT. This comprises a special high quality 8 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board, together with necessary transformers, switches, control knobs—in fact everything needed down to the last screw FOR MAKING A SUPERB TAPE RECORDER, which, when built, will compare favourably with instruments costing twice as much, yet you need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY AND SUCCESS ASSURED.



TWO TRACK Deck Amplifier, Cabinet and Speaker. Complete kits with MICROPHONE 7 in 1200 ft. tape, spare spool. Today's value £55. OUR PRICE 36 gns.  
FOUR-TRACK Deck Amplifier, Cabinet and speaker. Complete kits with MICROPHONE 7 in 1200 ft. tape, spare spool. Today's Value £80. OUR PRICE 39 gns.  
P.P. 22/6  
ALL UNITS AVAILABLE SEPARATELY. Both models. ASK FOR BROCHURE B.

VHF FM SUPERHET TUNER MKII \*3-MULLARD TRANSISTORS & 4 DIODES \* 300 KHz BANDWIDTH \* PRINTED CIRCUIT CONSTRUCTION \* HIGH FIDELITY REPRODUCTION MONO AND STEREO \* MATCHES AUDIO MK II EQUIPMENT  
A popular VHF FM Tuner now used throughout the country for quality reception of monophonic and, with the decoder stereophonic broadcast. There is no doubt about it—VHF FM gives the truest sound. Exceptionally stable economically—best. **TOTAL COST £6.19.6.** DECEMBER £5.19.6 (CABINET 20/- EXTRA) ASK FOR LEAFLET 3.



TRANSISTORS, RECTIFIERS, ZENERS, SCR'S TUNNEL DIODES, FIELD EFFECT TYPES, VALVES, CRYSTALS  
**New 1968 32-page Booklet**  
Price 1/- Post Paid  
Circuits with Data, Details and Prices of over 2000 different types. This booklet is a must for every enthusiast. MANUFACTURERS—DISTRIBUTORS. We also publish a QUANTITY, SEMI-CONDUCTOR BULLETIN. Please write to us for your copy.

## NEW—MALLORY LONG LIFE MERCURY BATTERIES

50% OFF LIST PRICES  
\* RM12 1.35 volts 3600 mAh OUR PRICE 5/- each size 2 3/8 dia.  
RM25 10.35 volts 350 mAh Pack of 8. Size 2 3/8 x 8 dia. OUR PRICE 10/- each  
Easily replaces the right size cells. These cells are ideal for any application where SMALL SIZE HIGH CAPACITY and LONG LIFE are required. QUANTITY QUOTATIONS WRITE OR PHONE EXTN. 2.



## GARRARD DECKS

BRAND NEW All below list price  
2025 Mono/Stereo .. .. . 8 19 6  
300 LM with ST4HC .. .. . 8 19 6  
SP25 MK II .. .. . 12 12 0  
LAB80 MK II .. .. . 26 0 0  
AT60 .. .. . 10 12 6  
AT50 MK II .. .. . 13 19 6  
40 MK II .. .. . 11 10 0  
3500 Mono/Stereo .. .. . 14 10 0  
401 .. .. . 27 10 0  
AP75 .. .. . 21 10 0  
S155 .. .. . 13 10 0  
S165 .. .. . 16 19 6  
S175 .. .. . 32 10 0  
S195 .. .. . 33 10 0  
A70 MK II .. .. . 13 12 0  
Send for illustrated brochures 16, 17  
Complete range of accessories available



## TRANSISTORS—SEMI-CONDUCTORS

COMPLETELY NEW 1968 LIST OF 1000 types available from stock. Send for your FREE COPY TODAY. (List No. 36)  
S.C.R.'s from 5/-  
Field Effect Transistors from 9/6  
Power Transistors from 5/-  
Diodes and Rectifiers from 1/6

## Hi-Fi equipment to suit EVERY POCKET

Ask for Hi-Fi—Stock List Leaflet 16.17 VISIT OUR NEW HI-FI CENTRE at 309 EDGWARE RD.

for all leading makes  
AMPLIFIERS  
TUNERS  
DECKS  
SPEAKERS  
MICROPHONES  
SYSTEMS  
ALL WITH DISCOUNTS  
IT WILL PAY YOU TO PAY US A VISIT!

## Fully Illustrated CATALOGUE

COMPLETELY NEW 9th EDITION (1968)  
The most COMPREHENSIVE—CONCISE—CLEAR—COMPONENTS CATALOGUE  
Complete with 10/- worth discount vouchers FREE WITH EVERY COPY.  
\* 32 pages of transistors and semi-conductor devices, valves and crystals.  
\* 200 pages of components and equipment.  
\* 65 pages of microphones, decks and Hi-Fi equipment.

6,500 ITEMS  
300 BIG PAGES  
**Send today 8/6** Post Paid

# HENRY'S RADIO LTD

303 Edgware Road, London, W.2. Mail Order Dept. all types of Components, Organ Dept. (01) 723-1008/9  
309 Edgware Road, London, W.2. High Fidelity Sales, P.A. and Test Equipment, Record Decks (01) 723-6963

OPEN MON.—SAT. 9 a.m.—6 p.m. THURS. 9 a.m.—1 p.m.