

PRACTICAL

ELECTRONICS

JUNE 1969

THREE SHILLINGS



STROBOSCOPE

ALSO INSIDE:

ENLARGER EXPOSURE METER

ADCOLA

PRODUCTS LIMITED
(Registered Trade Mark)

THE RELIABLE SOLDERING INSTRUMENT!



SEND COUPON FOR LATEST LEAFLET

ADCOLA PRODUCTS LTD
ADCOLA HOUSE
GAUDEN ROAD
LONDON SW4

NAME

ADDRESS


.....

.....

.....

PE170

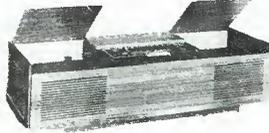STEREOGRAM CABINET £19
An elegant Stereogram Cabinet in modern Veneered Mahogany and cloth covered Front Panel
BLACK LEATHERETTE SIDE PANELS
Dimensions: 52" x 17½" x 12". Speaker positions for Twin 10" x 5" Speakers



SPEAKERS 6/6
2" - 75Ω. 2½" - 35Ω. P. & P. 2/6.
ACOS MICS. 35/- STANDARD
STICK MIC. 2gns. P. & P. 3/6.
ASSORTED CONDENSERS
10/- for 50. P. & P. 7/6.
ASSORTED RESISTORS
10/- for 50. P. & P. 4/6.
ASSORTED CONTROLS
10/- for 25. P. & P. 7/6.
TRANSISTORS
MULLARD MATCHED
OUTPUT KIT
9/- OC81D—2 OC81's.
P. & P. FREE.
FERRITE RODS 3/6
6", 8" x ⅜" complete with
LW/MW COILS. P. & P. FREE.

DUKE & CO. (LONDON) LTD.
621/3 Romford Road, Manor Park, E.12
Phone 01-478 6001-2-3 Stamp for Free List.

17in.—£11.10.0 Carr. 30/-
19in. SLIM-LINE
FERGUSON 24 gns.
TWO-YEAR GUARANTEE
EX-RENTAL TELEVISIONS

FREE ILLUSTRATED
LIST OF TELEVISIONS
17"—19"—21"—23"



WIDE RANGE OF MODELS
SIZES AND PRICES
DEMONSTRATIONS DAILY

RECORD PLAYER CABINET
49/6.

Cloth covered. Size 16½" x 14½" x 8"
Takes any modern autochanger.
P. & P. 7/6.

SINGLE PLAYER CABINETS
15/6. P. & P. 7/6.

TRANSISTOR CASES 19/6.
Cloth covered, many colours.
Size 9½" x 6½" x 3". P. & P. 3/6.
Similar cases in plastic 7/6.


**TWO-YEAR GUARANTEED
REGUNNED TUBES**

70° & 90° 14in.—69/6, 17in.—
89/6, 21in.—99/6, 110° 17in.,
19in. & 21in.—99/6, 23° (not
bonded)—119/6. Exchanged
Bowls. Carr. 10/6.

PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4½" x 2½". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.

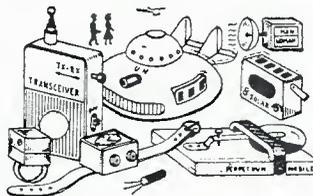

**EXPERIMENTER'S
PRINTED CIRCUIT KIT**
8/6

Postage & Pack. 1/6 (UK)

Commonwealth:
SURFACE MAIL 2/-
AIR MAIL 8/-
Australia, New Zealand
South Africa, Canada.

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photo-cell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Miniature Radio Receivers based on the "Triplexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1-62" x .93" x .25". (11) Wristwatch Radio 1-15" x .80" x .55". (12) Ring Radio .70" x .70" x .35". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wireless Microphone. (32) Wire-less Door Bell. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.


YORK ELECTRICS
333 YORK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

Lasky's Radio

LASKY'S RADIO ESTABLISHED OVER
36
YEARS

SPECIALIST RELAYS

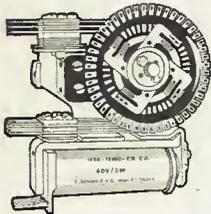

SCHRACK 4 POLE 12 WAY

This stepping relay inches one step per pulse of the coil, contacts are provided for continuous stepping and 2 pole changeover at position "6". Uses include programming Christmas tree lights, selection of stations on multiway intercom systems (using standard 2 way intercoms), Servo steering of radio control models. Automatic operation of model railways, etc.

Type RT 319600 OR Type RT 319120
60V - 2W coil 12V - 2W coil

LASKY'S PRICE **59/6** each

Post 2/6



THORN PYGMY PLUG-IN RELAY

A miniature 8 pin plug-in relay with 10A double changeover configuration. Mains operated coil switched for internal powered remote mains switching, using one contact as a latch to hold the relay in until the external circuit is broken. Coil resistance 82K/ohms, 200-240V AC/DC operation.

LASKY'S PRICE **12/6** Post 12/6


AEI MINIATURE RELAY



A miniature shrouded 3 pole "make" relay of the chassis mounting type. DC coil resistance 900 Ω 24V operation. Useful for remote audio switching circuits, control systems, using low voltage and current, controlling small DC motors and pilot lights, etc., and any application switching three circuits from one switch.

LASKY'S PRICE **8/6** Post 10/6

TTC Model A-1005 FM TUNER CHASSIS

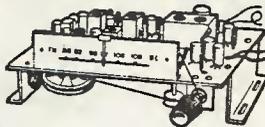

1,000's sold of this highly sensitive FM tuner—fully tunable—range 88 to 108 Mc/s. Completely wired on printed circuit 10.3 Mc/s IF, 6 transistors and 3 diodes. Slow motion tuning drive. Size 6 1/2 x 4 x 2 1/2 in. Operates from any 9v d.c. source. Full data and circuit supplied.

LASKY'S PRICE **£6.19.6**

Post 3/6

ADD MULTIPLEX TO THE MODEL A-1005

You can enjoy stereo sound with the Model A-1005 FM Tuner above by adding the TTC Model A-1005M Multiplex Adaptor. Brief Specification: MPX input sensitivity 100mv. Output 150mV. Self powered by a 9V battery. 4 transistor and 6 diode circuit. Size 5 1/2 x 2 x 1 1/2 in. Also suitable for use with other FM tuners with MPX input.

LASKY'S PRICE **99/6** Post 3/6

TTC Model A-1007 AM TUNER CHASSIS

Fully tunable over 530-1,600 Kc/s, 3 transistor and one diode high output circuit, fully assembled and tested on printed circuit board. Uses variable condenser and oscillator converter. Power is taken from any suitable amplifier using a 9V d.c. supply. Ferrite rod aerial. Size 4 x 2 1/2 x 1 1/2 in (ex. tuning control). Complete with full data and circuit.

LASKY'S PRICE **69/6** Post 3/6

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 3271
Open all day, 9 a.m.—6 p.m. Monday to Saturday
33 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-636 2605
Open all day, 9 a.m.—6 p.m. Monday to Saturday
152/3 FLEET STREET, LONDON, E.C.4 Tel.: 01-353 2833
Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

SKYROVER Mk II

COMMUNICATIONS RECEIVER



A completely new short wave receiver exclusive to Lasky's, at a real economy price. Four valve line up using one each 6BE6, 6BA6, 6AV6 and 6AR5 valves, gives highly sensitive reception and power-

ful gain. Switch selected SW frequency range cover: 1.5 to 30 Mc/s in three separate bands spread ranges and full

AM medium waveband cover in one range 550-1,600 kc/s. Vernier reduction drive tuning with fine hair line cursor. Controls include volume on/off, BFO, Band selector. Power on indicator lamp. External antenna connections and mains lead at rear, 8 ohms internal speaker plus standard 5mm jack socket for phones on front. For 220/240V a.c. mains operation. Strong metal cabinet finished in grey crackle with anodised silver front panel. Size 9 1/2 x 5 1/2 x 5 1/2 in. Complete with mains lead and full instructions. Previously listed at £17.15.0. (A credit note for the difference in price will be given to customers who purchased this unit at the original price after Jan. 1st '69, on presentation of receipt).

LASKY'S PRICE **£13.13.0**

Post 5/-

TCC G-1120

HEADPHONE/BOOM MICROPHONE SET



This lightweight headphone and boom microphone assembly is especially suitable for TV camera crews, communications equipment, language labs., recording studios, etc. The fully adjustable headset is extremely comfortable to wear for long periods. Low impedance microphone allows long cables to be used without any signal loss. Used with a Tape Recorder this assembly will provide constant monitoring. High quality specification and superb finish at a price you can afford.

Headset spec.: Dynamic, impedance 16 ohms. Frequency res. 20-14,000Hz. Input 200mW. Cord length 16in with jack plug fitted. Mic. spec.: Dynamic, impedance 200 ohms. Frequency res. 200-8000Hz, sensitivity 75dB. Cord length 69in complete with jack plug.

LASKY'S PRICE **£6.5.0**

Post 2/6

BUDGET PRICED CASSETTES

"OVERTURE" High quality cassettes from the U.S.A. C.60—10/6 C.90—15/- C.120—20/-

Post 1/- each. 4 and over Post Free. Special quotes for quantities.

GET YOUR LASKY'S AUDIO-TRONICS PICTORIAL

FREE

16 colour pages in large 16 x 11in. format packed with 1,000's of items from our vast stocks. Hi-Fi, Radio, Electronics, Test equipment.

Send 1/6 for post only and inclusion on our regular mailing list

High Fidelity Audio Centres

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2573
Open all day, 9 a.m.—6 p.m. Monday to Saturday

118 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 9789
Open all day Saturday, early closing 1 p.m. Thursday

prepare now for tomorrow's world

Today there is a huge demand for technologists such as electronics, nuclear and computer systems engineers, radio and television engineers, etc. In the future, there will be even more such important positions requiring just the up-to-date, advanced technical education which CREI, the Home Study Division of McGraw-Hill Book Co., can provide.

CREI Study Programmes are directly related to the problems of industry including the latest technological developments and advanced ideas. The individual tuition given by the CREI panel of experts in each specialised field is comparable in technical content with that of technical colleges.

Take the first step to a better job now — enrol with CREI, the specialists in Technical Home Study Education.

CREI Programmes are available in:

Electronic Engineering Technology * Industrial Electronics for Automation * Computer Systems Technology * Nuclear Engineering * Mathematics for Electronics Engineers * Television Engineering * Radar and Servo Engineering * City and Guilds of London Institute: Subject No. 49 and Advanced Studies No. 300.

**CREI (London), Walpole House,
173-176 Sloane Street, London S.W.1.**
A Subsidiary of McGraw-Hill Inc.

Post this coupon today for a better future

To C.R.E.I. (London), Walpole House, 173-176 Sloane Street, London S.W.1.
Please send me (without obligation) details of your Educational Programmes

please tick

My interest is City and Guilds General

Name

Address

Electronics experience

PE14

SEMICONDUCTORS

BRAND NEW AND FULLY GUARANTEED

IN914	1/6	2N2904	8/-	ACY18	5/-	BF181	8/6	GET103	5/-
IN916	1/6	2N2904A	8/-	ACY19	5/-	BF184	7/6	GET113	4/-
IS010	3/6	2N2905	8/-	ACY20	4/-	BF194	6/6	MFI102	8/6
IS020	3/6	2N2905A	8/-	ACY21	5/-	BFY12	3/6	MFI103	7/6
IS021	4/-	2N2906	8/-	ACY22	4/-	BFX3	5/6	MFI104	7/6
IS025	5/-	2N2906A	8/-	ACY28	4/-	BFX29	12/6	MFI105	8/-
IS113	3/-	2N2907	8/-	AD140	8/-	BFX30	8/6	NKT0013	8/6
IS120	2/6	2N2907A	8/-	AD149	8/-	BFX35	19/6	NKT216	10/6
IS121	2/6	2N2923	5/-	AD161	7/6	BFX43	8/6	NKT217	8/6
IS130	2/6	2N2924	5/-	AF114	5/-	BFX44	8/6	NKT261	4/6
IS131	2/6	2N2925	5/6	AF116	5/-	BFX68	13/6	NKT262	4/6
IS132	2/6	2N2926	5/6	AF117	5/-	BFX68A	14/6	NKT264	4/6
IS44	2/-	.. Green	3/6	AF118	5/-	BFX85	10/-	NKT271	4/6
2G301	4/-	.. Yellow	3/3	AF124	5/-	BFX86	8/-	NKT272	4/6
2G302	4/-	.. Orange	3/-	AF127	5/-	BFX87	10/-	NKT275	4/6
2G303	4/-	.. Red	2/9	AF181	6/6	BFX88	5/-	NKT281	5/6
2G371	3/-	.. Brown	2/6	AF186	11/-	BFX92A	12/6	NKT403	15/6
2N696	5/-	2N3005	15/-	AF212	5/6	BFY10	4/6	NKT404	12/6
2N697	5/-	2N3005	6/6	AF213	5/6	BFY11	4/6	NKT405	15/-
2N698	4/6	2N3053	6/6	ASZ12	4/6	BFY17	4/6	NKT673	6/6
2N706	3/-	2N3054	15/-	ASZ27	8/6	BFY18	4/6	NKT674	5/-
2N706A	3/-	2N3055	19/6	ASZ28	6/6	BFY19	4/6	NKT677	5/6
2N708	4/-	2N3070	4/-	ASZ29	4/6	BFY19	4/6	NKT713	5/6
2N929	5/6	2N3702	4/-	ASZ21	4/6	BFY41	10/-	NKT781	6/-
2N930	6/6	2N3703	4/6	BAX13	2/6	BFY50	4/6	NKT20329	8/6
2N1090	6/6	2N3705	4/6	BAX16	2/9	BFY51	4/6	NKT8011	15/6
2N1091	6/6	2N3706	4/6	BAY38	3/6	BFY52	4/6	NKT8012	19/6
2N1131	9/6	2N3707	4/-	BC107	3/6	BFY77	9/6	NKT8013	22/6
2N1132	9/6	2N3708	4/-	BC108	3/6	BFY90	12/6	OA5	2/6
2N1302	4/6	2N3709	4/6	BC109	3/6	BFY10	5/6	OA9	2/-
2N1303	4/6	2N3710	4/6	BC113	3/6	BSX19	5/6	OA70	1/6
2N1304	5/6	2N3711	4/6	BC118	6/6	BSX20	5/6	OA73	2/-
2N1305	3/6	2N3712	4/6	BC125	13/6	BSX21	8/6	OA79	1/9
2N1306	6/6	2N3820	23/6	BC128	13/6	BSX26	10/6	OA81	1/6
2N1307	6/6	2N3821	17/6	BC147	3/6	BSX27	10/6	OA79	1/9
2N1309	8/-	2N4058	6/6	BC149	5/-	BSX28	6/6	OA85	1/6
2N1507	5/6	2N4059	5/-	BC182	4/6	BSX29	10/6	OA85	1/6
2N1613	6/6	2N4060	5/-	BC183	4/6	BSX60	19/6	OA90	1/6
2N1711	6/6	2N4062	6/6	BC184	4/6	BSX76	8/6	OA91	1/6
2N1712	6/6	2N4063	6/6	BCY30	7/6	BSX77	8/6	OA95	1/6
2N1893	8/-	2N4254	9/6	BCY32	5/6	BSX78	8/-	OA200	2/-
2N2102	13/6	2N4255	8/6	BCY33	5/6	BSY26	4/6	OC26	6/6
2N2147	17/6	2N4284	3/6	BCY34	4/6	BSY27	4/6	OC28	6/6
2N2148	17/6	2N4285	3/6	BCY38	5/6	BSY28	4/6	OC35	6/6
2N2160	14/6	2N4286	3/6	BCY39	6/6	BSY29	4/6	OC36	6/6
2N2193	6/6	2N4287	3/6	BCY40	7/6	BSY38	4/6	OC34	6/6
2N2193A	5/6	2N4287	3/6	BCZ11	5/-	BSY39	4/6	OC44	2/6
2N2194A	5/6	2N4289	3/6	BCY43	6/6	BSY40	5/6	OC45	2/6
2N2217	9/6	2N4290	3/6	BCY54	7/6	BSY51	10/6	OC71	2/6
2N2218	10/6	2N4291	3/6	BCY70	5/6	BSY52	10/6	OC72	2/6
2N2219	10/6	2N4292	3/6	BCY71	9/6	BSY53	9/6	OC75	4/6
2N2220	5/-	AA213	2/6	BCY72	5/-	BSY54	6/-	OC81	4/6
2N2221	5/-	AA217	2/6	BCY73	4/6	BSY95A	3/6	OC82	4/6
2N2222	5/-	AC107	8/6	BCZ11	6/6	BY10	9/6	OC8D	7/6
2N2368	6/6	AC126	4/-	BD124	12/-	BYX10	5/6	OC139	6/6
2N2369	7/6	AC127	3/-	BF115	4/6	BYZ10	9/6	OC140	6/6
2N2369A	5/-	AC128	4/-	BF167	6/6	BYZ11	7/6	OC200	5/6
2N2539	4/6	AC176	6/-	BF173	7/6	BYZ12	6/-	OC201	5/6
2N2540	4/6	AC187	12/-	BF180	9/-	BYZ13	5/-	OC202	8/6
2N2646	11/6	AC188	12/-						
2N2696	6/6	ACY17	5/-						

RECORDING TAPES

Fully Guaranteed

7"	STD	1,200'	7/3
7"	L/P	1,800'	12/3
7"	D/P	2,400'	19/-
5 1/2"	STD	900'	6/6
5 1/2"	L/P	1,200'	9/6
5 1/2"	D/P	1,800'	14/9
5"	STD	600'	5/3
5"	L/P	900'	7/3
5"	D/P	1,200'	10/9
3"	D/P	185'	2/3
3"	L/P	225'	3/-
3"	D/P	300'	4/-
7"	D/P Concorde	1 15 1/6	16 450 3/3
		1 40 1/9	25 64 1/6
		2 15 1/6	25 10 1/6
		2 350 2/0	25 25 1/6
		2 5 16 1/9	25 50 1/6
		4 15 1/6	32 15 1/6
		4 40 4/9	32 40 1/6
		4 350 2/3	32 450 1/6
		5 15 1/6	40 64 1/6
		6-4 64 1/9	40 16 1/6
		8 18 1/6	50 16 1/6
		8 40 1/6	50 15 1/6
		8 450 3/-	50 25 1/6
		10 15 1/6	50 50 2/-
		10 25 1/6	64 25 1/6
		12-5 25 1/9	80 64 1/6
		16 10 1/9	80 16 1/6
		16 18 1/6	100 12 1/6

CASSETTE TAPES

C-60 13/6, C-90 18/6

Post and Packing up to 3 reels 2/9, otherwise 4/6.

SPEAKERS (3 ohm)

10"	6"	37/6
9"	4"	23/6
8"	5"	19/6
7"	4"	15/6
5"	3"	12/6
3"	9/6	5" 14/6
8"	27/6	12" 39/6

Post and Packing 1/6

TRIYSTORS

1 AMP: 50V 5/-, 100V 5/6, 200V 7/-, 400V 9/6.
3 AMP: 50V 6/-, 100V 7/6, 200V 8/-, 400V 10/-.
Equivalent BYT 91/100R 15/- each
ZENERS: 1 1/2 WATT 2.7-33V 4/6
400m/w 3.0-330 5/-

INTEGRATED CIRCUITS

R.C.A.
CA3005, 3013, 3014, 3018 30/-
CA3019, 3020 27/6 CA3011, 3036 20/-
CA3023 32/6 CA3012 25/-
FAIRCHILD L923 14/-
DATA SHEETS FOR RCA DEVICES 2/- per type

Presets std., horiz. or vert.
Potentiometers, Log/Lin

MFD	V	Price	MFD	V	Price	MFD	V	Price
1	15	1/6	16	450	3/3	100	15	1/6
1	40	1/9	25	64	1/6	100	25	1/6
2	15	1/6	25	10	1/6	100	50	2/6
2	350	2/0	25	25	1/6	125	4	1/6
2.5	16	1/9	25	50	1/6	200	16	2/-
4	15	1/6	32	15	1/6	250	25	2/9
4	40	4/9	32	40	1/6	250	50	3/9
4	350	2/3	32	450	1/6	320	10	1/6
5	15	1/6	40	64	1/6	400	16	2/9
6-4	64	1/9	40	16	1/6	500	6	2/6
8	18	1/6	50	16	1/6	500	25	3/9
8	40	1/6	50	15	1/6	500	50	4/9
8	450	3/-	50	25	1/6	640	16	3/6
10	15	1/6	50	50	2/-	1000	12	3/9
10	25	1/6	64	25	1/6	1000	16	4/-
12-5	25	1/9	80	64	1/6	1000	25	5/-
16	10	1/9	80	16	1/6	1000	50	9/-
16	18	1/6	100	12	1/6			

VEROBOARD

3 1/2" x 2 1/2" 3/6
CA x 3 1/2" 4/3
Cutter 9/-
3 1/2" x 5" 5/6
17" x 3 1/2" 16/-
5" x 2 1/2" 4/3

RESISTORS

1/2 watt 10%, 4d.
1/2 watt 5%, 5d.
3 watt, 1/6
5 watt 2/-

SEND 6d. STAMP FOR CATALOGUE
P.P. for Components 1/6 per order

A. MARSHALL & SON
28 CRICKLEWOOD BROADWAY, LONDON, N.W.2
01-452 0161/2/3 CALLERS WELCOME

PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451

OXFORD ST.



COMPLETE STEREO SYSTEM

FOR ONLY

39 GNS

CARRIAGE 35/-



The Premier Stereo System consists of an all transistor stereo amplifier, Garrard Model 2025 auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor Amplifier has an output of 5 watts per channel with inputs for pick up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends: Size 12" x 5 1/2" x 3 1/2" high (Amplifier available separately if required £14.19.6. Carr. 7/6).

GARRARD RECORD UNITS

1025 Stereo/Mono cart.	£7.19.6	
2025 Stereo/Mono cart.	£8.19.6	Teak Plinth with perspex cover as above £5.10.0. Carr. 5/6 extra.
3000 with 9TAHCD Carriage 7/6 extra	£9.19.6	
AT60 MKII less cart.	£13.19.8	
SP25 MKII less cart.	£11.19.8	
AP75 less cart.	£19.0.0	Teak Plinth with perspex cover Carr. 7/6 ex.
SL75 less cart.	£29.0.0	
SL95 less cost	£38.10.0.	Carrriage 10/- extra.

GOLDRING RECORD UNITS

GL68 less cart. £22.7.0. GL75 less cart. £35.15.5. Carriage 10/- extra.

PICK-UP CARTRIDGES

SHURE M3D (Stereo)	£7.10.0
B.S.O. SP1 (Stereo)	£5. 5.0
PICKERING V15/AC2 (Stereo)	£8.10.0
SONOTONE 9TAHC/Diamond (Stereo)	£2.15.0
ACOS GP91/ISC (Mono compatible)	£1.13.5
ACOS GP93-1 (Stereo)	£2. 8.7
ACOS GP94-1 (Stereo)	£2.14.8
B.S.R. X3M (Mono compatible)	£1.16.5
B.S.R. X3H (Mono compatible)	£1.16.5
RONETTE 105 (Stereo)	£1.15.0
RONETTE 106 (Stereo)	£1.15.0

All complete with mounting brackets and instructions. Post and Packing 1/6 each.

WELLER SOLDERING TOOLS



"Expert" Solder Gun. Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 watt. 240 volt A.C. 67/8 P. & P. 2/- "Marksman" Soldering Iron. Lightweight, conventional 1/16" pencil bit. Ideal for regular bench use and all those jobs around the home. 25 watts. 240 volt. A.C. 31/8 P & P 2/-.

"PREMIER" TAPE CASSETTES

C60 Type	10/6
60 min.	
C90 Type	15/-
90 min.	
CI20 Type	20/-
120 min.	
P. & P. 1/-.	



CASSETTE HEAD CLEANER
Removes unwanted deposits from delicate tape heads. Fits all cassette recorders. 15/- P. & P. 1/-.




HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted Fitted 2 1/2" speaker units with soft padded ear muffs. Adjustable headband. 8ohm impedance. Complete with 6ft. lead and stereo jack plug. 59/6 P. & P. 5/-.

MONO HEADPHONES 2000 ohm 14/6 P. & P. 2/6.
STEREO STETHOSCOPE SET Low imp. 25/- P. & P. 2/-.
MONO STETHOSCOPE SET Low imp. 10/6 P. & P. 2/-.

"PREMIER" SPEAKER SYSTEM

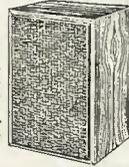Specially designed oiled teak cabinet with vynair front. Size 12 1/2" high, 7 1/2" wide, 6 1/2" deep. Fitted 6 1/2" EMI 8ohm Bass speaker with rolled surround and matching 3" E.M.I. tweeter. Fully lagged. £7.19.6. Carr. 7/6.



MULTI TESTERS



MODEL D14. A really versatile instrument that makes a handy pocket size tool. Measures AC or DC voltage in three ranges of 0-15-150-1000 volts. Resistance 0-100,000 ohms. Current 0-150 mA D.C. Size only: 3 1/2 x 2 1/2 x 1 1/2 in. Complete with battery, test leads and instructions 49/6. P. & P. 2/6.



POCKET SIZE MODEL. With wide-angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt A.C. 10 C.D. 10,000 ohms/volt A.C. 19 Ranges: 0-5-25-50-250-500-2500 volts D.C. 0-10-50-100-500-1000 volts A.C. 0-50 uA-2-5 mA-250 mA D.C. 0-5000 ohms-5 megohms. 10u ui-0-001 mfd-1 mfd. -20 to +22dB. Complete battery, test lead and instructions. £4.19.6. P. & P. 3/6.

WIDE RANGE OF HI-FI STEREO EQUIPMENT ON DEMONSTRATION

All leading makes available including Rogers, Armstrong, Dulci, Wharfedale, Goodmans, Goldring, Shure, etc. etc.

SPECIAL OFFER

BALFOUR "PRINCESS"

4 Speed Autochanger fitted ACOS Mono Compatible t/o cartridge. Complete with TEAK BASE. ONLY £5.19.6. Carr. 7/6.



MONO GRAM AMPLIFIER

2 1/2 watts output. Uses EL34 valve, double wound mains transformer. Ideal for use with any record deck. Volume/ on/off and tone controls on flying leads. Output impedance 3 ohms. Size overall 5 1/2" w. x 5 1/2" d x 3" h. A.C. 200/240V. ONLY 49/6. P. & P. 5/-.


JULIETTE NA.5018 5 BAND 18 TRANSISTOR MAINS/BATTERY RADIO

Covers AM 540-1600Kc/s. Marine 1-6-4-6Mc/s. FM 88-108Mc/s. VHF 108-134Mc/s. PB 145-174Mc/s. Ferrite bar aerial for AM/FM. Telescopic aerial for FM/VHF/PB. 4" P.M. Speaker. Operates on AC 250v. or D.C. by four 1.5v. batteries. Size: 9 1/2" x 5 1/2" x 3 1/2". PREMIER PRICE 38 gns. P. & P. 10/-.



TWO STATION TRANSISTOR INTERCOMS.

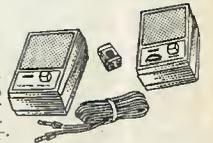Complete with battery and 50ft. connecting wire. Compact size, two way call system. Ideal for home, office, factory, etc. ONLY 49/6 P. & P. 4/-.



FOUR STATION INTERCOM. Master unit and 3 slaves. Ideal for office and home. Complete with battery and connecting wire £7.19.6 P. & P. 5/6.

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP3 3" 250' P.V.C.	5/6	DT6 5 1/2" 1800' POLYESTER	22/6
TT3 3" 450' POLYESTER	7/6	TT6 5 1/2" 2400' POLYESTER	37/6
DT3 3 1/2" 600' POLYESTER	11/6	SP7 7" 1200' POLYESTER	12/6
SP5 5" 600' P.V.C.	8/6	LP7 7" 1800' P.V.C.	15/-
LP5 5" 900' P.V.C.	10/-	DT7 7" 2400' POLYESTER	25/-
DT5 5" 1200' POLYESTER	15/-	TT7 7" 3600' POLYESTER	50/-
LP6 5 1/2" 1200' P.V.C.	12/6		

TAPE SPOOLS 3" 1/-, 5", 5 1/2", 7" 1/6. TAPE CASES 5", 5 1/2", 7" 2/6. Post and Packing 3" 1/-, 5", 5 1/2" 1/6, 7" 2/- (3 reels and over Post Free).




Sinclair

Z.12 - for all you want from any amplifier

The Z.12 is a most versatile integrated amplifier and pre-amp in which power, compactness and true high-fidelity standards are combined within a unit of very modest price. The most widely used unit of its kind in the world, the Z.12 has an output of 12W R.M.S. continuous sine wave (24W peak) or 15W music power (30W speak). It has Class B ultralinear output which can be fed into any loud-speaker from 3 to 15 ohms. (Two 3 ohm speakers can be used in parallel.) Frequency response—15 to 50,000Hz \pm 1dB; input sensitivity—2mV into 2 K/ohms. The Z.12 will operate from any power source between 6 and 20V d.c. As such,

a car battery or the P.Z.4 are eminently suitable, giving much wider than usual scope in the applications to which the Z.12 may be put. As well as hi-fi, these include systems for P.A., electronic guitars, organs, intercom systems, laboratory, education or industry. You will find the Z.12 in use in such instances again and again. The Sinclair Z.12 is supplied ready built, tested and guaranteed, complete with manual of circuits and instructions for matching it to your precise requirements. Two may be used in stereo when, with the Stereo 25 and P.Z.4 together with two Q.14s, you will have an ideal high fidelity assembly.


89/6

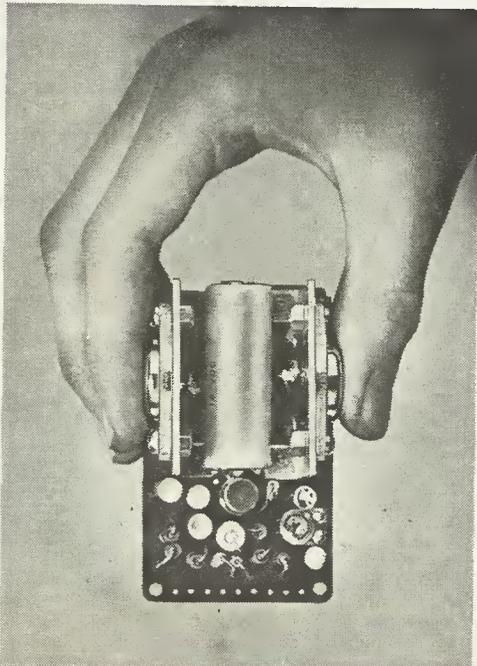

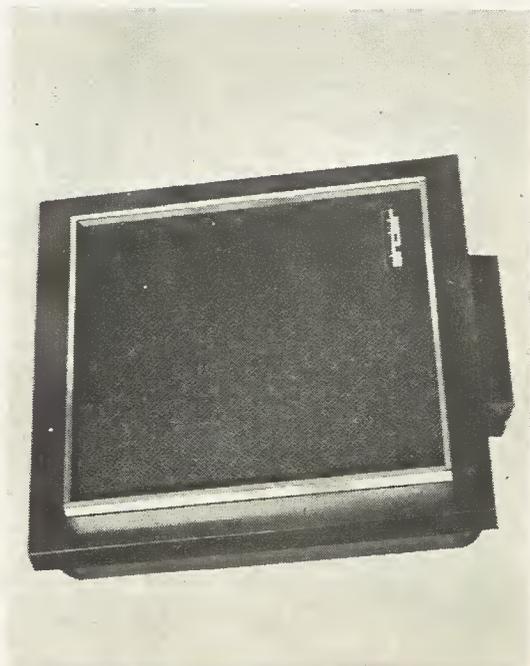Q.14 - the unique loudspeaker

New materials and original design techniques have been used to produce speaker of fantastic quality at a most attractive price. Experts and reviewers have enthusiastically endorsed its performance. The shape and size of the Q.14 make it far more adaptable to its environment than is the case with conventionally styled speakers so that it is much easier to position this speaker in the room in which it is to be heard. The Sinclair Q.14 has a substantially flat frequency

response from 60 to 16,000Hz and outstandingly good transient response. It will comfortably handle up to 14W loading and is positively brilliant in stereo. Measuring 9 $\frac{1}{2}$ in square by 4 $\frac{1}{2}$ in deep, this loudspeaker is finished in matt black with solid aluminium bar trim. Try the Q.14 in your own home without delay. If you are not delighted with it, your money including cost of return postage to Sinclair will be refunded immediately.



£7.19.6

+ 2/11 P/T Surcharge

Stereo 25 de-luxe pre-amp/control unit

This is a very elegantly styled unit, which, although designed basically for use with the Z.12, is readily adaptable for use with any high quality power amplifier system. The switched input selector allows for Pick-up, Radio and Auxiliary and there are controls for bass cut and lift, treble cut and lift, volume and stereo balance. P.U. input is equalised to R.I.A.A. curve from 50 to 20,000Hz \pm 1dB and

instructions manual provided gives matching details for pick-ups, shows how to connect up, etc. The front panel of the Stereo 25 is finished in brushed and polished aluminium embellished in black. The control knobs are in solid aluminium to match. Size $6\frac{1}{2}$ x $2\frac{1}{4}$ x $2\frac{1}{2}$ plus knobs. Supplied built, tested and guaranteed.

£9.19.6

PZ.4 - stabilised power supply unit

Designed specially to meet the power requirements for an assembly of two Z.12s and the Stereo 25, this heavy duty transistorized power supply unit has stabilised output of 18V d.c. at up to 1.5A. It is for a.c. mains operation 200/250V.

Supplied built, tested and guaranteed.

99/6

SINCLAIR MICROMATIC

Whether you buy your Micromatic in kit form or built ready for use, you must not deny yourself the thrill of owning this fantastically small British receiver. Smaller than a matchbox, it has power, range and selectivity that must be experienced to be believed. The high quality magnetic earpiece supplied with the set ensures excellent reproduction indoors and out. The Micromatic tunes over the medium waveband and has A.G.C. to counteract fading from distant stations. Bandpass tuning makes reception of Radio 1 easier, in fact you will find this set performing in some cases where other sets cannot be heard at all. The Micromatic is housed in a neat black case given an elegantly modern appearance by the attractive aluminium front panel and matching tuning control.

YOUR SINCLAIR GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full at once and without question.

FULL SERVICE FACILITIES AVAILABLE TO ALL PURCHASERS.

Goods sent post free in U.K. and overseas by airmail. Air mail extra at cost.

Kit in fitted pack with magnetic earpiece, instructions and free solder

49/6

+11d P/T
Surcharge

Built, tested and guaranteed, inc. magnetic earpiece

59/6

+11d P/T
Surcharge

Mallor Mercury Cell type RM.675 (2 required) 2/9 each

Please send POST FREE

NAME.....




ADDRESS.....

For which I enclose cash [cheque/ money order

PE.669

OCA3-52731

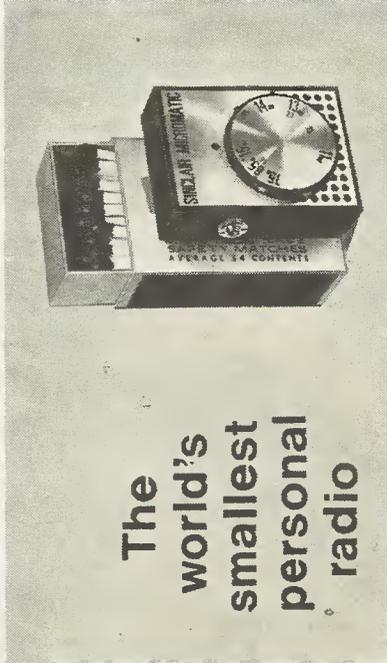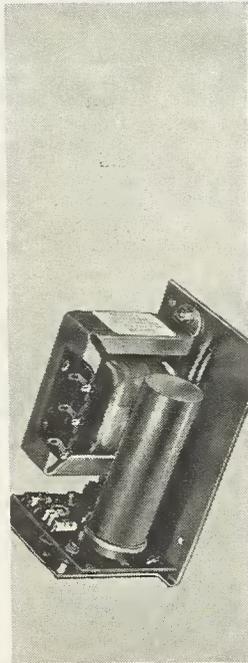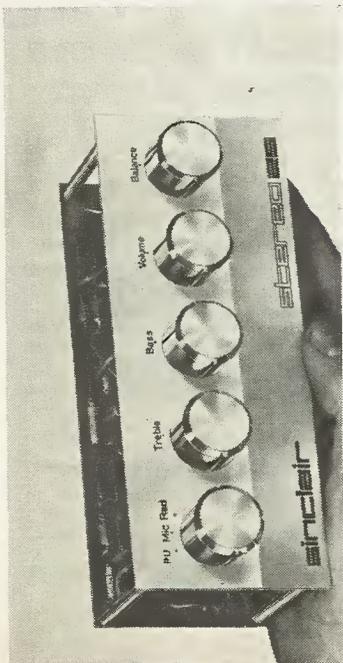SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE



The world's smallest personal radio




GEATRONIX LIMITED

EDUCATIONAL ELECTRONIC EQUIPMENT

MANUFACTURERS OF NORKIT

A new HOBBY for the automation age

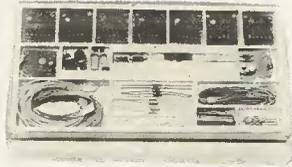- ★ Simple building bricks to build your own ELECTRONIC BRAINS.
- ★ Easy to understand handbooks to guide you.
- ★ Learn about LOGIC, BINARY arithmetic and BOOLEAN algebra.
- ★ Modules are rapidly assembled and dismantled to use again.
- ★ Make machines that play games, control model railways, etc. and control automatic machines of any description.




NORKIT JUNIOR £8.16.0
(as shown)

NORKIT SENIOR £17.12.0
Handbooks supplied for each kit
or available separately 6/- each

LOGIC DEMONSTRATION UNIT TYPE LDU.1

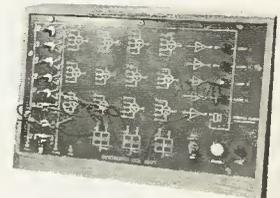A new teaching aid for rapidly setting up and demonstrating logic circuits. Stackable patching leads are used to interconnect logic symbols on a mimic diagram. The symbols are connected to appropriate components inside the unit. Switches and pushbuttons are provided to simulate input conditions and outputs are indicated by lamps and an audible alarm.



£68.0.0

Telephone: SOUTHEND 62521

GEATRONIX LTD., 28 REDSTOCK RD., SOUTHEND-ON-SEA, ESSEX



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

"I am highly delighted with the books; I didn't know a complicated subject could be so easily presented."

J. K., Earlsfield.

"I am pleased to say how understandable your books are. I have now quite a sound knowledge of Electronics."

P. S., Southgate.

"I know your Manuals will prove invaluable for my training and career as a technician."

J. L., S. Shields.

A TECH-PRESS PUBLICATION

POST NOW FOR THIS OFFER!!

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/-, Cash Price or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/-, Cash Price or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY

BASIC ELECTRONICS

Prices include Postage and Packing.

Signature

(If under 21 signature required of parent or guardian)

NAME

BLOCK LETTERS

FULL POSTAL


ADDRESS.....

Build yourself a quality transistor radio

backed by our after sales service!

roamer seven mk iv

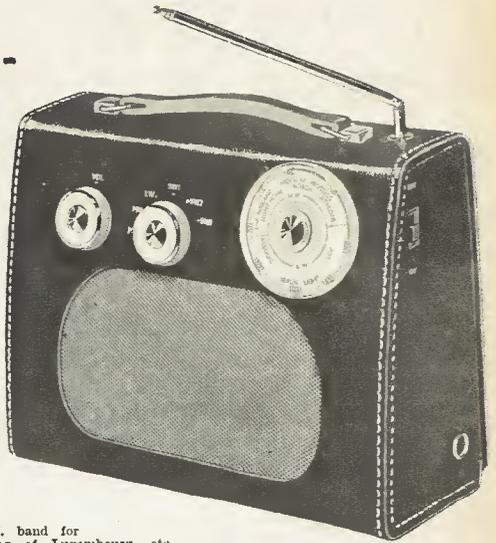SEVEN WAVEBAND PORTABLE
SEVEN TUNABLE WAVEBANDS—
MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND.




Extra M.W. band for easier tuning of Luxembourg, etc. Built-in ferrite rod aerial for Medium and Long Waves. 5 Section 22in. chrome-plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push-pull output. 7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker for rich-tone volume. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. First-grade components. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build.

Total building costs
£5.19.6 P. & P. 7/6 Personal Earpiece with switched socket for private listening 5/- extra.

Parts price list and easy build plans 3/- (Free with parts).

NEW LOOK

melody six

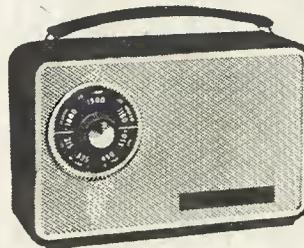

8 stages—6 transistors and 2 diodes. Covers Medium and Long Waves. Top quality 3in. Loudspeaker for quality output and also with Personal Earpiece with switched socket for private listening. Two R.F. Stages for extra boost. High "Q". Ferrite Rod Aerial. Push-pull output. Handsome pocket size case with gilt fittings. Size 6½ x 4 x 2in. Easy build plans and parts price list 2/- (FREE with parts).

Total building costs
69/6 P. & P. 4/3

RADIO EXCHANGE LTD

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER SEVEN ROAMER SIX

TRANSONA FIVE SUPER SEVEN

POCKET FIVE MELODY SIX

Parts price list and plans for.....

Name.....


Address.....

P.E.6-69

pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND (to 50 metres approx.) PORTABLE WITH SPEAKER AND EARPIECE

Attractive black and gold case. Size 6½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. All first grade components—7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list, 1/8 (FREE with parts).

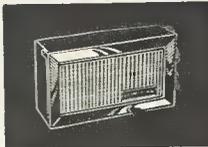

Total building costs
44/6 P. & P. 3/6

transona five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND (to 50 metres approx.) PORTABLE WITH SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. All first grade components. Easy build plans and parts price list 1/8 (FREE with parts).



Total building costs
47/6 P. & P. 3/9

super seven

THREE WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case size 7½ x 5½ x 1½in. with gilt fittings. The ideal radio for home, or outdoors. Covers Medium and Long Waves and Trawler Band. Special circuit incorporating 2 R.F. Stages, push pull output, ferrite rod aerial, 7 transistors and 2 diodes, 3in. speaker (will drive larger speaker) and all first grade components. Easy build plans and parts. Price list 2/- (FREE with parts). (Personal Earpiece with switched socket for private listening 5/- extra.)



Total building costs
69/6 P. & P. 4/6

roamer six

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case with gilt fittings, size 7½ x 5½ x 1½in. Tunable on Medium and Long waves, two short waves, Trawler band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. All top grade components. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. (Carrying strap 1/8 extra.) Easy build plans and parts price list 2/- (FREE with parts).



Total building costs
79/6 P. & P. 4/6

- Callers side entrance Stylo Shoe Shop.
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12.30 Sat.

NEW CATALOGUE

Nearly 200 pages giving full details of a comprehensive range of **COMPONENTS, TEST EQUIPMENT, COMMUNICATION EQUIPMENT AND HI-FI EQUIPMENT.** Each section greatly enlarged and fully illustrated. Thousands of items many at bargain prices. **FREE DISCOUNT COUPONS VALUE 10/-.**

SEND NOW—ONLY 7/6 PEP!

TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose D/B oscilloscope. B.E. 2 c/s-750 kc/s. Bandwidth 5.5 Mc/s. Sensitivity 33 mV/CM. Operating voltage 0/110/200/250 V. a.c. Supplied in excellent working condition. £22.10.0. Or complete with all accessories, probe, leads, lid, etc. £25. Carriage 30/-.

ADMIRALTY B.40 RECEIVERS

Released by the Ministry. High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 650 kc/s-30 Mc/s. I.F. 500 kc/s. Incorporates 2 R.F. and 3 I.F. stages, band-pass filter, noise limiter, crystal controlled B.F.O., calibrator. O/P output, etc. Built-in speaker-output for phones. Operation 150/230 V a.c. Size 19 1/2 x 13 1/2 x 1 1/2 in. Weight 114 lb.



Offered in good working condition. £22.10.0. Carr. 30/- With circuit diagrams. Also available B.41 I.F. version of above. 15 kc/s-700 kc/s. £17.10.0. Carr. 30/-.

R209 MK II COMMUNICATION RECEIVER

11 valve high grade communication receiver suitable for tropical use. 1-20 Mc/s on 4 bands. AM/CW/FM operation. Incorporates speaker, vernier driver, BFO. Aerial trimmer, internal speaker and 12 V d.c. internal power supply. Supplied in excellent condition, fully tested and checked.

£12.10.0

Carr. 20/-



ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons.

VM.76 VALVE VOLTMETER
R.F. measurements in excess of 100 Mc/s and d.c. measurements up to 100V with accuracy of ±2% d.c. range 300 MV to 1kV a.c. range 300 MV to 300V RMS. Resistance 0.2-500Ω. Price £72.

VM.78 A.C. MILLIVOLT METER
Transistorised 1 MV-300V. Frequency 1 c/s to 1 Mc/s. Price £55.

VM.79 UHF MILLIVOLT METER
Transistorised. A.c. range 10 MV-2V. D.c. current range 0.01μA-0.3mA. Resistance 1 ohm-10 megohms. Price £125.

H1B AUDIO SIGNAL GENERATOR
15 c/s-50 kc/s. sine or square wave. Price £30.

J1B AUDIO SIGNAL GENERATOR
15 c/s-50 kc/s. Price £20.

J2B AUDIO SIGNAL GENERATOR
As per J1B except fitted with output meter. Price £35.

TT1S TRANSISTOR TESTER
£37.10.0

Carriage 10/- per item.





AVOMETERS

Supplied in excellent condition, fully tested and checked. Complete with prods, leads and instructions. Model 47A £9.19.8 P. & P. 7/6.

UNR-30 4-BAND COMMUNICATION RECEIVER

Covering 550 kc/s-30 Mc/s. Incorporates BFO. Built-in speaker and phone jack. Metal cabinet. Operation 220/240V. a.c. Supplied brand new, guaranteed with instructions. Carr. 7/6

13 gns.

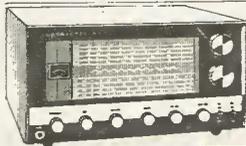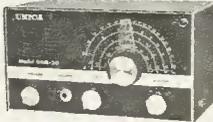

LAFAYETTE SOLID STATE HAGOOD RECEIVER

5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE 150 kc/s-400 kc/s and 550 kc/s-30 Mc/s. F E T front end • 2 mechanical filters • Huge dial • Product detector • Crystal calibrator • Variable BFO • Noise Limiter • 8 meter • 24in Bandspread • 230 V a.c./19 V d.c. reg. operation • RF ratio control. Size 15in x 9in x 8in. Weight 18 lb. EXCEPTIONAL VALUE. £45. Carr. 10/- S.A.E. for full details.

Variable Voltage TRANSFORMERS

Brand new, guaranteed and carriage paid. High quality construction. Input 230 V 50-60 cycles. Output fully variable from 0-250 V. Bulk quantities available. 1 amp.—£5.10.0; 2.5 amp.—£6.15.0; 5 amp.—£9.15.0; 8 amp.—£14.10.0; 10 amp.—£18.10.0; 12 amp.—£21.0.0; 20 amp.—£37.0.0.




CLEAR PLASTIC PANEL METERS

First grade quality Moving Coil panel meters available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Type MR 38P. 1 1/2 in square faces.

500-0-500μA	25/-	50mA	25/-	150V D.C.	25/-
1mA	25/-	100mA	25/-	300V D.C.	25/-
1-0-1mA	25/-	150mA	25/-	500V D.C.	25/-
2mA	25/-	200mA	25/-	750V D.C.	25/-
5mA	25/-	300mA	25/-	15V A.C.	25/-
10mA	25/-	500mA	25/-	50V A.C.	25/-
750mA	25/-	3V D.C.	25/-	150V A.C.	25/-
50-0-50μA	35/-	1 amp	25/-	300V A.C.	25/-
100μA	35/-	2 amp	25/-	500V A.C.	25/-
1000-0-100μA	32/6	5 amp	25/-	8 meter 1mA 29/6	
200μA	31/6	20mA	25/-	100V D.C.	25/-
500μA	37/6			VU meter	38/6

Postage Extra. Larger sizes available—send for lists.

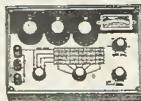TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 megΩ. 6 Ranges ±1%. L.L. 1μH-11.1 HENRYS. 6 Ranges -2%. C. 10pF-11110 mF.d. 6 Ranges ±2%. TURNS RATIO 1:1/1000-1:11100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 2 1/2 in. £20. P. & P. 5/-.

CLASS D WAVEMETERS



A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6V d.c. Ideal for amateur use. Available in good used condition. £5.19.8. Carr. 7/6. Or brand new with accessories. £7.19.8. Carr. 7/6.

TE-20RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s-260 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V a.c. Brand new with instruction. £15.0.0. P. & P. 7/6. S.A.E. for details.

ARF-100 COMBINED AF-RD SIGNAL GENERATOR

A.F. SINE WAVE 20-200,000 c/s. Square wave 20-30,000 c/s. O.P. HIGH IMP. 21V. P/P600Ω 3.8 V-30P. TF 100 kc/s-300 Mc/s. Variable R.F. attenuation int/ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240 V a.c. £30.0.0. Carr. 7/6.

GARRARD

FULL CURRENT RANGE OFFERED, BRAND NEW AND GUARANTEED AT FANTASTIC SAVINGS

SRP22 Mono	£6.10.0	*SP25 MKII	£11.19.8
SRP22 Stereo	£8.19.8	*SL5	£11.19.8
*1025 Mono	£7.10.0	*A70 MKII	£11.19.8
*1025 Stereo	£7.15.0	*AT60MKII	£13.10.0
*2025 Stereo	£7.19.8	*SL65	£14.14.0
*2025T/C		AP75	£17.17.0
Mono/Stereo	£8.17.8	401	£28.7.6
*3000 Stereo	£9.19.8	SL75	£29.0.0
		SL95	£35.0.0



Carriage/insurance 7/6 extra any model. WB4 Bases £3.19.8. Perspex covers £3.10.0. *Special offer base and cover available for these models at £4.15.0. Carr. 5/- Full range of Garrard accessories available.

* TRANSISTORISED FM TUNER *

HIGH TRANSISTOR QUALITY TUNER. SIZE ONLY 6 1/2 x 4 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money. £6.7.6. P. & P. 2/6. Stereo multiplex adaptors 99/6.

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.19.8. P. & P. 3/6.

NEW MODEL 500. 30,000 O.P.V. with overload protection. mirror scale 250/500/1,000 V d.c. 0/2.5/10/25/100/250/500/1,000 V. a.c. 0/50 μA/5/50/500 μA. 12 amp. d.c. 0/0.6/6 Meg/60 Meg/£8.17.6. Post paid.

MODEL TE-10A. 20 kΩV 5/25/50/250/500/500 V d.c. 10/50/100/500/1,000 V a.c. 0/50μA/2.5 mA/250 mA d.c. 0/6K/6 meg. ohm. -20 to +22dB. 10-0, 100mFd. 0-100-0-1mFd. 68/6. P. & P. 2/6.

TE-16A Transistorised Signal Generator. 5 ranges 400 kHz-30 MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide, easy to read scale. 800 kHz modulation. 5 1/2 x 3 1/2 in. Complete with instructions and leads. £7.19.8. P. & P. 4/-.

MODEL ZQM TRANSISTOR CHECKER

It has the fullest capacity for checking on A, B and Ico. Equally adaptable for checking diodes, etc. Spec.: A: 0.7-0.9967. B: 5-200. Ico: 0-50 microamps 0-5 mA. Resistance for diode 200Ω-1 MΩ. Supplied complete with instructions, battery and lead. £5.19.8. P. & P. 2/6.



LAFAYETTE LA-22AT TRANSISTOR STEREO AMPLIFIER

19 transistors, 8 diodes. 1HF music power 30 W at 8 ohms. Res. 30-20,000 ±2 dB at 1 W. Distortion 1% or less. Inputs: 3 MV and 250 MV. Output: 3-16 ohms. Separate L. and R. volume controls. Treble and bass control. Stereo phone jack. Brushed aluminium gold-anodised extruded front panel with metal case. 10 1/2 x 3 1/2 x 7 1/2 in. 115/230V. A.C. £28. Carr. 7/6.

G.W. SMITH & CO (RADIO) LIMITED

3 and 34, LISLE STREET, O1-437 8204
LEICESTER SQ., LONDON, W.C.2 O1-437 9155
311, EDGWARE RD., LONDON, W.2 O1-262 0387
(ALL MAIL ORDERS TO - 3, LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2)

9 a.m. to 6 p.m. Mon. to Sat. (Edgware Road) 1/2 day (Thurs.) Trade supplied.

4-STATION INTERCOM



£7/15/0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price 12 gns. P. & P. 9/8 extra.

INTERCOM/BABY ALARM



65/-

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.

Transistor TELEPHONE AMPLIFIER



59/6

Why not boost your business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/3)
169 KENSINGTON HIGH STREET, LONDON, W.8

RADIO COMMUNICATIONS HANDBOOK

by R.S.G.B. 63/- P. & P. 4/6

USING SCOPES IN TRANSISTOR CIRCUITS by Middleton. 32/- P. & P. 1/9.

TRANSISTOR T.V. TRAINING COURSE by Middleton. 35/- P. & P. 1/9.

AM-FM-TV ALIGNMENT by Middleton. 30/- P. & P. 1/6.

49 EASY TRANSISTOR PROJECTS by Brown. 16/- P. & P. 1/3.

PRACTICAL OSCILLOSCOPE HANDBOOK by Turner. 25/- P. & P. 1/6.

PRINCIPLES OF TRANSISTOR CIRCUITS new 4th ed. by Amos. 25/- P. & P. 1/6.

COMPUTERS SELF TAUGHT BY EXPERIMENTS by Brayton. 30/- P. & P. 1/6.

ELECTRONIC MUSICAL INSTRUMENT MANUAL by Douglas. 55/- P. & P. 2/-.

AMATEUR RADIO ANTENNAS by Hooton. 35/- P. & P. 1/6.

ELECTRONIC NOVELTY DESIGNS by Kampel. 8/6 P. & P. 1/-.

HI-FI YEAR BOOK 1969 ED. 15/- P. & P. 1/9.

UNIVERSAL BOOK CO.

12 LITTLE NEWPORT ST., LONDON, W.C.2
(Leicester Square Tube Station)

NEW RANGE BBC 2 AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays, 7 element, 37/6. 11 element, 45/-. 14 element, 52/6. 18 element, 60/-. Wall Mounting with Cranked Arm, 7 element, 60/-. 11 element, 67/-. 14 element, 75/-. 18 element, 82/6. Mast Mounting with 2in. clamp, 7 element, 42/6; 11 element, 55/-. 14 element, 62/-. 18 element, 70/-. Chimney Mounting Arrays, Complete, 7 element, 72/6; 11 element, 80/-. 14 element, 87/6; 18 element, 95/-. Complete assembly instructions with every unit. Low Loss Cable, 1/6 yd. U.H.F. Pre-amps from 75/-. State clearly channel number required on all orders.

BBC - ITV AERIALS



BBC (Band 1). Telescopic loft, 25/-. External S/D, 80/- "H", £2.15.0.

ITV (Band 3). 3 element loft array, 30/-. 5 element, 40/-. 7 element, 50/-. Wall mounting, 3 element, 47/6. 5 element, 52/6.

Combined BBC/ITV. Loft 1+3, 40/-; 1+5, 50/-; 1+7, 60/-; Wall mounting 1+3, 37/6; 1+5, 47/6; Chimney 1+3, 37/6; 1+5, 75/-.

VHF transistor pre-amps, 75/-.

COMBINED BBC1-ITV-BBC2 AERIALS 1+3+9, 70/-; 1+5+9, 80/-; 1+5+14, 90/-; 1+7+14, 100/-. Loft mounting only. Special leaflet available.

F.M. (Band 2). Loft S/D, 15/-, "H", 32/6, 3 element, 55/-. External units available. Co-ax. cable, 8d. yd. Co-ax. plugs, 1/4. Outlet boxes, 5/-. Pinger Crossover Boxes, 13/6. C.W.O. or C.O.D. 2, 3, 4, 5, 6, 7. Send Oil Stamps for illustrated lists.

CALLERS WELCOME

OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS (Dept. P.E.)
40-41 Monarch Parade
London Road, Mitcham, Surrey
01-648 4884

DIOTRAN SALES

P.O. BOX 5
WARE, HERTS
TEL.: WARE 3442

EX-COMPUTER PANELS I.B.M. Size 2in. x 4in. with TRANSISTORS, DIODES, RESISTORS, CAPACITORS, etc. Over 1 million already Sold out to the Trade. 70,000 only left at our Ridiculous Price of £3 per 100 panels or £28 per 1,000 panels. Plus carriage, charged extra at cost.

Post and Packing costs are continually rising. Please add 1/- towards same. CASH WITH ORDER PLEASE

OVERSEAS QUOTATIONS BY RETURN SHIPMENTS TO ANYWHERE IN THE WORLD

OVER 3 MILLION SILICON ALLOY & GERM. TRANSISTORS AVAILABLE FOR IMMEDIATE DELIVERY

MANUFACTURERS' TYPE	SURPLUS		END OF PRODUCTION	
	Qty.	Qty.	Qty.	Qty.
TRANSISTORS				
Type and Construction	Price	Price	Price	Price
A1. Germ. Audio.	100	500	1,000	10,000
N.P.N. T-O-1	£3.10	£15	£25	£200
A2. Germ. A.F. T-O-5	£1	£3	£5	£40
A3. Germ. A.F. T-O-1	£1	£3	£5	£40
A4. Germ. R.F. T-O-1	£1.10	£4.10	£7.10	£60
A5. Germ. R.F. T-O-5	£1.10	£4.10	£7.10	£60
A6. Germ. V.H.F. T-O-1	£3.10	£15	£25	£200
A7. Mixed Germ. A.F.-R.F. 15-	£2.10	£4	£12	£100
A8. Germ. A.F. 2G300	£2	£7.10	£12.10	£100
A9. Sil. Alloy P.N.P. T-O-5	£2	£7.10	£12.10	£100

NO OPEN OR SHORTS—ALL GOOD TRANS.

TEXAS SILICON ALLOY TRANSISTORS
25302 Eqvt. OC200 VcB40 Hfe 15-50 1-49 off 3/6 each
25303 " OC201 VcB15 Hfe 25-75 50-99 off 3/- each
25304 " OC202 VcB15 Hfe 45-120 100 off 2/6 each
ALL BRAND NEW, FULLY GUARANTEED & MARKED.

HIGH QUALITY SILICON PLANAR DIODES.
SUB-MINIATURE DO-7 Glass Type, suitable replacements for OA200, OA202, BAY38, 1S130, 1S940, 200,000 to clear at £4 per 1,000 pieces. GUARANTEED 80% GOOD.

SILICON PLANAR PLASTIC TRANSISTORS.
2N3708A VcB30 Hfe 20-60. All marked, fully tested and guaranteed 1 off 1/6 each; 100 off 10d. each; 500 off 9d. each; 1,000 off 7 1/2d. each.

TO-18 METAL CAN SILICON PLANAR TRANSISTORS. VERY HIGH QUALITY 99% good. Type 2N706 B5Y27 £7.10 per 500 pieces; £12.10 per 1,000 pieces.

THYRISTORS (S.C.R.'s), FULLY TESTED, BRAND NEW AND CODED: TO-5 CASE

Type No.	PIV	Amp	Each
2N1595	50	1	7/6
2N1596	100	1	8/-
2N1597	200	1	10/-
2N1598	300	1	14/-
2N1599	400	1	15/-
BTX30-500	500	1	22/-
BTX30-600	600	1	25/6

TO-46 CASE (STUD)

Type No.	PIV	Amp	Each
2N1771	50	4-7	9/-
2N1772	100	4-7	9/6
2N1773	200	4-7	12/6
2N1774	300	4-7	16/6
2N1777	400	4-7	19/-
2N1778	500	4-7	25/6
2N2619	600	4-7	30/-
BTY79-150	150	4-7	12/-
BTY79-250	250	4-7	14/-
BTY79-400	400	4-7	20/-

TO-48 CASE (STUD)

Type No.	PIV	Amp	Each
2N682	50	16	12/-
2N683	100	16	15/-
2N685	200	16	19/6
2N687	300	16	25/6
2N688	400	16	32/6
2N689	500	16	47/6
2N690	600	16	50/6
2N691	700	16	56/-
2N692	800	16	62/-

1/- each TESTED TRANSISTORS 1/- each

ONE PRICE ONLY P.N.P. N.P.N.	SILICON PLANAR 1/- EACH
BC108 2N696 2N1132 2N2220 25733	
BC109 2N697 2N1613 2N3707 2N3391	
BFY50 2N706 2N1711 2N3111 2N1544	
BFY51 2N708 2N2904 25102 2N2906	
BFX84 2N929 2N2905 25103 2N2907	
BFX86 2N930 2N2924 25104 2N2696	
BFX88 2N1131 2N2926 25732 2N3702	
	2N3703
	2N3704

From Manufacturers' Over-runs—Unmarked Plastic and Metal cases.

GERM. P.N.P AND N.P.N TRANSISTORS FULLY TESTED, UNMARKED 1/6 EACH

OC125	ACY22	ACY36	NKT677	OC81	2G381
OC126 <td>ACY27 <td>NKT41 <td>NKT713 <td>OC82 <td>2G382</td> </td></td></td></td>	ACY27 <td>NKT41 <td>NKT713 <td>OC82 <td>2G382</td> </td></td></td>	NKT41 <td>NKT713 <td>OC82 <td>2G382</td> </td></td>	NKT713 <td>OC82 <td>2G382</td> </td>	OC82 <td>2G382</td>	2G382
OC127 <td>ACY28 <td>NKT42 <td>NKT773</td> <td>2G301</td> <td>2G399A</td> </td></td>	ACY28 <td>NKT42 <td>NKT773</td> <td>2G301</td> <td>2G399A</td> </td>	NKT42 <td>NKT773</td> <td>2G301</td> <td>2G399A</td>	NKT773	2G301	2G399A
OC128 <td>ACY29 <td>NKT212 <td>OC44</td> <td>2G302</td> <td></td> </td></td>	ACY29 <td>NKT212 <td>OC44</td> <td>2G302</td> <td></td> </td>	NKT212 <td>OC44</td> <td>2G302</td> <td></td>	OC44	2G302	
OC130 <td>ACY30 <td>NKT213 <td>OC45</td> <td>2G303</td> <td></td> </td></td>	ACY30 <td>NKT213 <td>OC45</td> <td>2G303</td> <td></td> </td>	NKT213 <td>OC45</td> <td>2G303</td> <td></td>	OC45	2G303	
OC19 <td>ACY31 <td>NKT214 <td>OC71</td> <td>2G308</td> <td>1/6</td> </td></td>	ACY31 <td>NKT214 <td>OC71</td> <td>2G308</td> <td>1/6</td> </td>	NKT214 <td>OC71</td> <td>2G308</td> <td>1/6</td>	OC71	2G308	1/6
OCY20 <td>ACY34 <td>NKT215 <td>OC72</td> <td>2G371</td> <td>each</td> </td></td>	ACY34 <td>NKT215 <td>OC72</td> <td>2G371</td> <td>each</td> </td>	NKT215 <td>OC72</td> <td>2G371</td> <td>each</td>	OC72	2G371	each
OCY21 <td>ACY35 <td>NKT271 <td>OC75</td> <td>2G374</td> <td></td> </td></td>	ACY35 <td>NKT271 <td>OC75</td> <td>2G374</td> <td></td> </td>	NKT271 <td>OC75</td> <td>2G374</td> <td></td>	OC75	2G374	

POWER TRANSISTORS

OC25	OC35	NKT403	ASZ17
OC26 <td>AD130</td> <td>NKT404</td> <td>T13027</td>	AD130	NKT404	T13027
OC28 <td>AD140</td> <td>NKT405</td> <td>T13028</td>	AD140	NKT405	T13028
OC29 <td>AD149</td> <td>NKT452</td> <td>T13029</td>	AD149	NKT452	T13029

Manufacturers' Surplus Germ. A.F.

TRANSISTOR EQVT. BOOK

2,500 cross references of transistors—British, European, American and Japanese. A must for every transistor user. Exclusively distributed by DIOTRAN SALES. 15/- EACH.

FULLY TESTED DEVICES AND QUALITY GUARANTEED—SURPLUS TO REQUIREMENTS

OA203 Silicon Diode, Fully Coded.
OC201 PIV 250mA. Price £20 per 1,000 pieces.
ORP12 Cadmium Sulphide Cell.
1-24 9/- each; 25-99 7/- each; 100-999 6/- each; 1,000 up 5/6 each. Made in Holland.
BY100 SIL. RECT'S 800 PIV 550mA.
1-49 2/6 each; 50-99 2/3 each; 100-999 2/- each; 1,000 up 1/10 each. Fully Coded. 1st Qty.

BAND NEW FULLY TESTED EPOXY CASE UNIJUNCTION TRANSISTORS. Type T1543 and BEN 3000 and replacement for 2N2646.

Full data available. LOWEST PRICE AVAILABLE ANYWHERE. 100 off 4/- each = £20; 500 off 3/6 each = £87.10; 1,000 off 3/- each = £150. Sample devices 7/- each on request.

Sub-Min. Plastic 1 Amp Sil. Rect.

Type No.	PIV	Each
IN4001	50	1/3
IN4002	100	1/6
IN4003	200	2/-
IN4004	400	2/9
IN4005	600	3/3
IN4006	800	3/9
IN4007	1,000	4/9

Vast mixed lot of subminiature glass diodes. Comprising of Silicon, Germ., Point Contact and Gold Bonded types plus some Zeners. 500,000 available at Lowest of Low Price. 1,000 pieces £3.0.0. 5,000 pieces £13.10.0. 10,000 pieces £23.

You won't believe this



IT-18

but you can own a circuit tester for under £13

THE HEATHKIT TEST TWINS are now available at just a fraction of the price of comparable models. How come? Because we have eliminated our assembly costs by giving YOU the satisfaction of building your own equipment.

HEATHKIT IT-18 PORTABLE IN-CIRCUIT TRANSISTOR TESTER

Heath engineers have brought about a breakthrough in transistor servicing. They have taken the high cost of transistor testers and brought them down to earth. The IT-18 has all the facilities you need for fast, in-circuit transistor testing.

HEATHKIT IM-17 PORTABLE SOLID STATE VOLT-OHM METER

Transistorised 'valve-voltmeter' with an 11 meg-ohm input impedance. Battery powered to work anywhere. Features zero-adjust controls, a DC polarity reversing switch to eliminate switching leads, plus continuous rotation 12 position function switch.

Full specifications of these and many other units will be found in our 1969 catalogue — it's yours for the asking.

- I don't believe it — please send me your catalogue immediately.
- Include me on your mailing list.

NAME

ADDRESS

PE 6



DAYSTROM LIMITED,
Gloucester GL2 6EE England.
Tel.Glos.29451. Telex 43216

S.E.S. YOUR COMPLETE SUPPLIER

196 Regent Road, SALFORD 5, Lancashire

TELEPHONE 061-872 5187

(Member of the Harrop Industrial Group)

C.W.O. please 1/- p. & p. for orders of components under £1
 Orders of Lektrokitt: 2/- handling charge on orders under £1
 5/- handling charge on orders under £5

RESISTORS: All brand new, Hi-Stab, low noise, 5% tol. carbon film. $\frac{1}{2}$ W E12 series 4.7 ohm to 10M, 2d. each or 15/- per 100 of one value. $\frac{1}{2}$ W E24 series 4.7 ohm to 10M, 2d. each or 15/- per 100 of one value. $\frac{1}{2}$ W E12 series 2.2 ohm to 3.9 ohm, 8d. each. $\frac{1}{2}$ W E12 series 10 ohm to 10M. (10% tol.), 3d. each. $\frac{3}{4}$ W—wirewound—0.5 ohm to 12 ohm, 1/6 each. 5W—wirewound—15 ohm to 82kohm, 1/9 each. S.E.S. Pre-Pack gives you 5 off each, 5% resistors from 4.7 ohm to 1M either $\frac{1}{4}$ or $\frac{1}{2}$ watt. 65 different values (E12)—ONLY £2 12s. 6d. ***NOW— $\frac{1}{2}$ W carbon film 5%, E12 series 10 ohm to 100kohm, 2d. each.

PRE-SETS: Min. skeleton carbon track, low noise with good stability; Values—Lin: 1k, 2.5k, 5k, etc., to 5M; Log: 5k, 10k, 25k, etc., to 1Mohm, only 10d. each. Sub-Min skeleton Lin. track: 1k, 2.5k, 5k, etc., to 5M, only 9d. each. Slider pre-sets wirewound $\frac{1}{2}$ W rating Lin: 10 ohm to 5k, 2/3 each. $\frac{3}{4}$ W wirewound fully enclosed Lin. tracks. 10 ohm to 30k, 3/9.

POTENTIOMETERS: Min. enclosed, carbon track and wiper contact only 2/6; Values—Lin: 1k, 2.5k, 5k, etc., to 10M; Log: 5k, 10k, 25k, etc., to 5Mohm. Min. with double-pole switch, insulated spindles only 5/6. Values—Lin: 25k, 50, 100k; Log: 3k, 5k, 10k, 25k, 500k, 1M, 2M. $\frac{3}{4}$ W wirewound Lin. tracks 50 ohm to 100kohm, 7/4 each.

CAPACITORS: New genuine Mullard Electrolytics

(Min.)	(Small)	(Multi ples)
6.4V 6.4 25 50 100 200 320 640 1,000 1,600 2,500	8-8 μ F	6/6
10V 4 16 32 64 125 200 400 640 1,000 1,600	8-8 μ F	6/6
16V 2.5 10 20 40 80 125 250 400 640 1,000	8-8 μ F	6/6
25V 1.6 6.4 12.5 24 50 80 160 250 400 640	8-8 μ F	6/6
40V 1 4 8 16 32 50 100 160 250 400	8-8 μ F	6/6
64V 0.64 2.5 5 10 20 32 64 100 160 250	8-8 μ F	6/6

Prices: 1/- 10d. each 1/3 1/6 1/9 2/6

(Large)	(Multi ples)
25V 800 1,250 2,000 4,000 6,400 500V 8-8 μ F 6/6	6/6
40V 500 800 1,250 2,500 4,000 500V 16-16 μ F 7/6	7/6
64V 320 500 800 1,600 2,500 350V 32-32 μ F 7/3	7/3
Prices: 5/- 6/6 8/- 12/6 15/- 350V 50-50 μ F 9/-	9/-

(all values in Microfarads)

Mullard Miniature Metallised Polyester 250V. 0.01, 0.015, 0.022, 0.033, 0.047, 0.068 μ F, 6d. each. 0.1, 0.15, 0.22 μ F, 7d. each.
 Mullard Polyester Film and Foil 400V. 0.001, 0.0015, 0.0022, 0.0033, 0.0047, 0.0068, etc., to 0.33 μ F, 6d. each. 0.047 to 0.1 μ F, 8d. each. 0.15 μ F, 10d. 0.22 μ F, 1/-, 0.33 μ F, 1/6, 0.47 μ F, 1/9.
 Disc Ceramics (Erie) 500V, 1,000, 4,700pF, 5d. each. Silver Micas 1% tol. 500V, 2.2pF to 820pF, 1/- each. Polystyrene 160V, 100-1,000pF, 5d. each. ***NOW—Bead anteniums (polarised) 35V, 0.47, 0.68, 1 μ F, 2/6 each. 2.2, 3.3, 4.7, 6.8 μ F, 3/4 each. 20V 10 μ F, 15V 22 μ F, 10V 33 μ F, 6V 47 μ F, 3/9 each. Low Voltage Disc Ceramics 20V—0.01, 0.022, 0.047 μ F, 10d. each. 0.1, 0.22, 1/3 each. Midget Tubular Ceramics—0.002, 0.003 μ F, 10d. each.

SEMICONDUCTORS: All New and Unused
 Mullard: OA5, 4/6; OA81 3/4; OA202 2/3; OC71 4/-; OC72 4/6; OC44 7/9; OC45 6/-; BC107, 109 3/9 each; BC108 3/6; BFY51 4/6; MPF 105 9/6.
 Silicon Rectifiers—(0.5A) 400piv 2/9; 800piv 3/-; 1,500 piv 3/6; (1.2A) 400piv 6/-; 800piv 7/-; 1,500piv 7/6; (2.5A) 400piv 6/6; 800piv 7/6; 1,500piv 10/6. (1.2A and 2.5A types are stud mounted—Anode). ***NOW—2N2924 3/6; 2N2926 (Brown or Red) 2/6. (Orange) 2/9. (Yellow) 3/-, (Green) 3/3; 2N3643 8/6; 2N3794, 2N4289 4/- each; 1N4148 1/6.

SWITCHES: 100 series—SPST 3/8; SPDT 3/11; DPST 4/6; DPDT 4/8. 400 series SPST 3/2; SPDT 3/6; SPDT (with centre position) 3/8. Series 500—push-to-make or push-to-break 3/11 each (push buttons available in white, red, black, green). Slide Switch 3/4; Wave Change switches 5/9 each. Miniature "Maka-Switch" also available—Shafts 5/-; Wafers 5/4 each.

PLUGS AND SOCKETS: Min. Plugs (black or red) 6d. Min. Sockets to fit 7d. Banana Plugs (black or red) 9d. 4mm Sockets to fit (black, red, green) 9d. Co-Ax Plugs 1/2. Co-Ax Sockets 11d. Sub-Min Jack Plugs and Sockets 1/- each. Min. Jack Plugs and Sockets 3/- each. Recorder Plugs 3-way 2/7 5-way 3/-; Recorder Sockets 3-way 1/2, 5-way 1/4.

WIRE: Min. Stranded (available in 10 colours) 3d. yd. Solid Core 3d. yd. 14/00075in. Stranded 4d. yd. Min. Mains Lead 1/3 yd. Min. Microphone cable 1/6 yd. Co-Ax cable 1/3 yd.

LAMPS: Min. Wire Ended Neons 2/-; Panel Neon Indicator 6/4; Pilot Light +12V bulb 8/-; Min. Flange Light +12V bulb 11/-.

SOLDERING IRONS: A.N.T.E.X. CN240 15W mains operated, small, 32/6. E240 20W mains operated, specially shaped handle, 35/-; Spare bits and elements available. Also stands for above irons, 11/6 each. ***NOW—SOLDER by Multicore—at Reduced Prices to Everyone! Size A—Approx. 20ft coil 60/40 Alloy 22 s.w.g. in dispenser. Recommended retail price 3/-, OUR PRICE 2/9. Size B—Approx. 200ft reel 60/40 Alloy 22 s.w.g.; individually packed. Recommended retail price 15/-, OUR PRICE 12/6. BIB Wire Strippers: strips insulation without nicking wire. Recommended retail price 4/6, OUR PRICE 4/-.

LEKTROKIT: Chassis construction system—the professional look to a home construction. Parts to build a chassis 8 $\frac{1}{2}$ x 4 $\frac{1}{2}$ in.—2 chassis rails 1/10 each. 2 side plates 4/4 each. Front panel (covered in crack-proof paint) 8/3. Perforated cover 3/5. 2 plain covers 4/5 each. 4 rubber feet 9d. 7 boards available each 4 $\frac{1}{2}$ x 4in.—Aluminium board drilled for 6 valveholders 8/6, B8A, B9A, 2/6. Aluminium board drilled for 2 valveholders international octal, UX4, etc., 2/4. 0.1in. perforated grid SRBP board, 2/9. Veroboard 0.1in. and 0.2in. 6/6 each. Cloverleaf aluminium board 6/- (Cloverleaf lead throughs 6d. each. Pins for SRBP board 4/6 100).

For full details of all our stocks send 3/6 for our bright explanatory 120 page catalogue, or 6d. stamp for Data Sheets.

ELECTROVALUE

EVERYTHING BRAND NEW AND TO SPEC. NO SURPLUS

SPECIALIST SUPPLIERS OF TRANSISTORS

IN TYPES TO SUIT ALMOST ALL APPLICATIONS

- COMPETITIVE PRICES
- HIGH QUALITY COMPONENTS FOR TRANSISTOR CIRCUITS
- PEAK SOUND AS ADVERTISED
- CATALOGUE Our latest 1969 catalogue is packed with up-to-the-minute items and invaluable information. Send 1/6 for your copy now.
- DISCOUNTS 10% on orders for components for £3 or more. 15% on orders for components for £10 or more.
- POSTAGE on orders for £1, add 1/-. FREE on orders for £1 or over. Overseas orders welcome—Carriage charged at cost.

ELECTROVALUE

(DEPT. PE), 32a ST. JUDES RD., ENGLEFIELD GREEN, EGHAM, SURREY
 Telephone: Egham 5533 (STD 0784-3)

AMAZING MINI-DRILL

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 $\frac{1}{2}$ volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) 79/6 p.p. 2/6. De Luxe Professional Kit with 17 tools 130/- p.p. 4/6. Money Ref. Guarantee.

FOR PRECISION MODEL WORK

+ 6 TOOLS

ONLY 39/6 R&P 2/

MERLIN SUPPLY CO.
 Dept. PE6D, Nailsea, Bristol BS19 2LP

The most accurate pocket size CALCULATOR in the world


The 66 inch OTIS KING scales give you extra accuracy. Write today for free booklet, or send 82/6 for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.

CARBIC LTD. (Dept. PE23)
 54 Dundonald Road, London, S.W.19

FREE BOOKLET ON REQUEST

NEW! HSL.700 MONO TRANSISTOR AMPLIFIER

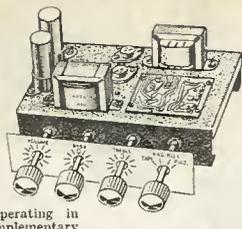A really high fidelity mono amplifier with performance characteristics to suit the most discriminating listener. 6 transistor circuit with integrated pre amplifier assembled on special printed sub panel.



AD161-AD162 operating in symmetrical complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier power supply for a.c. mains 200-240v. Controls: bass, treble, volume/on/off. Function selector for PU1, PU2, tape, radio. The HSL.700 is strongly constructed on rigid steel chassis bronze hammer anodized finish, size 9 1/2 x 5 x 4 1/2 in. high.

Performance figures—
Sensitivity—PU1—50mV, 56K input impedance.
PU2—110mV, 1 meg input impedance.
Tape—110mV, 1 meg input impedance.
Radio—110mV, 1 meg input impedance.
Output power measured at 1Kc—6.2 watts RMS into 3 ohms, 5.8 watts RMS into 15 ohm. Overall frequency response 30c/a-18Kc/s. Continuously variable tone controls: Bass, +8db to -12db at 100c/s. Treble, +10db to -10db at 10Kc/s.

The HSL.700 has been designed for true high fidelity reproduction from radio tuner, gramophone deck and tape recorder pre amp but is also capable of being used in conjunction with a guitar by connecting to PU1 socket and the peak output power will then be in the region of 15 watts.

Supplied complete with knobs, attractive anodized aluminium front escutcheon panel, four spindles (can be cut to suit your housing requirements) full circuit diagram and operating instructions. Limited number.

OUR SPECIAL PRICE £7.19.6. P. & P. 7/6.

BRAND NEW 3 OHM LOUDSPEAKERS

5in.14/-, 6in.15/6, 8in.27/-, 7 x 4in.18/6, 10 x 6in.27/6, E.M.I. 8 x 5in. with high flux magnet 21/-. E.M.I. 13 x 8in. with high flux ceramic magnet 42/- (15 ohm 45/-), E.M.I. 13 x 8in. with two inbuilt tweeters and crossover network. 3 or 15 ohms 4 gns. P. & P. 5in. 2/-, 6 1/2 x 8in. 2/6, 10 x 12in. 3/6 per speaker.

BRAND NEW 12in. 15W H/D Speakers, 3 or 15 ohms. By well-known British maker. Now with Hi Flux ceramic ferrobar magnet assembly. **£5.40.0.** P. & P. 5/-. Guitar Models: 25w. 46; 35w. 48.

E.M.I. 3in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 ohms 15/- each; 15 ohms 18/- each. P. & P. 2/6.

12in. "RAC" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3 or 15 ohm, 35/-, P. & P. 3/6.

35 OHM SPEAKERS
3 1/2in. 12/6; 7 x 4in. 21/-. P. & P. 2/- per speaker.

LATEST COLLARO MAGNAVOX 363 STEREO TAPE DECK. Three speeds 4 track, takes up to 7in. spools. **£16.0.0.** Carr. 10/-

QUALITY PORTABLE TAPE RECORDER CASE. Brand new. Beautifully made. Only 49/6. P. & P. 8/6. Dual Purpose Bulk Tape Eraser and Tape Head Magnetizer 35/-. P. & P. 3/-.

CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity, 18/6. P. & P. 1/6.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE 21/-. P. & P. 1/6.

CARBON MIKE INSERTS. Brand New. 2 1/2in. dia. 5/-, P. & P. 1/6.

NEW S.T.C. TYPE 25 MINIATURE RELAYS— 48 volt. 4 g/s, c/o contacts. 1 amp rating. Coil resistance 5,800 ohms. Size approx. 1 1/4 x 1 1/4 in. high. 8/6 each. P. & P. 1/6.

SPECIAL OFFER: PLESSEY TYPE 29 TWIN TUNING GANG. 400pF + 149pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 kc/s i.F. Size approx. 2 x 1 1/4 in. Only 8/6. P. & P. 2/6.

MAINS TRANSFORMER. Primary 200-240V two separate 1/2 wave secondaries giving approx. 18V at 1 amp and 20V at 1.2 amp; secs. can be connected in series for 36V at 1.5 amp. Ideal for transistor power supplies. Drop through mounting. Stack size 2 1/2 x 3 1/2 in. 15/-. P. & P. 6/-.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 9-0-9 at 500mA. 11/-, P. & P. 2/6. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 14/6. P. & P. 2/6. Pri. 200/240V. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 3/6.

MATCHED PAIR OF 2 1/2 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS. Stack size 1 1/2 x 1 1/2 in. Output trans. tapped for 3 ohm and 15 ohm output. 10/- plus 2/- P. & P.

HIGH GRADE COPPER LAMINATE BOARDS
8 x 6 x 1/4 in. FIVE for 10/-. P. & P. 2/-.

Open all day Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station

TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work. Cir-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to the proud of. Brief specification: Freq. response ±3dB. 20-20,000c/s. Bass boost approx. to +12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 25V at 0.6 amp.

PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £3.0.0. All Post Free. Circuit diagram, construction details and parts list (free with kit) 1/6. (S.A.E.).

Official stockists of all
PEAK SOUND HI-FI EQUIPMENT
including the
P.W. DOUBLE 12 STEREO AMPLIFIER
as featured in Practical Wireless,
April, May and June issues.

- | | |
|--|----------------|
| Component pack as specified. | 4.0 |
| 2 Spools of "Cir-Kit" | 4.13.0 |
| Pre-amp and tone control kits | 7.0 |
| 4 3 1/2in. x 2in. "Cir-Kit" matrix | 8.0 |
| 2 Boards 5in. x 3 1/2in. | 7.19.0 |
| 2 P.A.12-15 Power Amp Kits | 12.0 |
| 2 Heat Sink assemblies | 4.10.0 |
| 1 P.S.45V power supply kit | 2.12.6 |
| 1 Pack-fair atomospheric leak finished Cabinet kit | 2.0.0 |
| 5 Controls as specified | |
| Total cost | £28.5.6 |

(Excluding metal work, knobs, plugs and sockets and fuses)



SPECIAL PURCHASE!

E.M.I. 4-SPEED PLAYER

Heavy 8 1/2in. metal turntable. Low flutter performance 200/250 V above motor (90 V tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. ONLY 63/-. P. & P. 6/6.

QUALITY RECORD PLAYER AMPLIFIER MK II



A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, EZ80 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3 d. x 6 h. Ready built and tested. **PRICE 75/-.** P. & P. 6/-.

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. **PRICE 87/6.** P. & P. 7/6.

DE LUXE QUALITY PORTABLE R/P CABINET MK II Unsent motor board size 14 1/2 x 12in. clearance 2in. below, 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. **PRICE 79/6.** P. & P. 9/6.

FM/AM TUNER HEAD

Beautifully designed and precision engineered by Dornier & Wadsworth Ltd. Supplied ready fitted with twin -0005 tuning condenser for AM connection. Prealigned FM section covers 86-102Mc/s. I.F. output 10.7Mc/s. Complete with ECC85 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-. **GORLER F.M. TUNER HEAD.** 88-109 Mc/s. 10.7 Mc/s. I.F. 15/- plus 2/6 P. & P. (ECC85 valves, 8/6 extra).

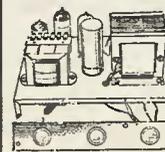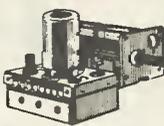


3-VALVE AUDIO AMPLIFIER MODEL HA34

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 1/2 in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate bass, treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£4.5.0.** P. & P. 6/-.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. **79/6.** P. & P. 6/-.

BRAND NEW TRANSISTOR BARGAINS. GET 15/- (Matched Pair) 15/-, V15/10p, 10/-; OC71 5/-; OC76 6/-; AF117 3/6; 2G339 (NFN) 3/-. Set of Mullard 6 transistors OC44, 2-OC45, AC128D, matched pair AC128 25/-; ORP12 Cadmium Sulphide Cell 10/6. All post free.

DE LUXE STEREO AMPLIFIER

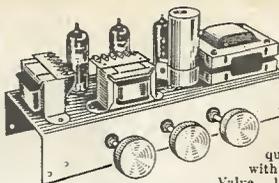

A.c. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum.

Valve line up—2 x ECL86 Triode Pentodes. 1 x EZ80 as full wave rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 1 1/2 in. w. x 4 in. x. Overall height including valves 5in. Ready built and tested to a high standard. **Price 8 gns.** P. & P. 8/-.


4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. **E.M.I. MODEL 999 Single Player with unit mounted pick-up arm and mono cartridge..... £5.5.0**
B.S.R. UA25 with latest mono compatible cart..... £8.19.6
All plus Carriage and Packing 6/6.
LATEST GARRARD MODELS. All types available 1025, 2025, SP25, 3000, AT60 etc. Send S.A.E. for Latest Prices!
PLINTH UNITS cut out for Garrard Models 1025, 2025, 2000, 3000, AT60, SP25. With rigid perspex cover. OUR PRICE 5 gns. complete. P. & P. 8/6.

SONOTONE STAGH compatible Stereo Cartridge with diamond stylus 50/-, P. & P. 2/-.
LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP (Stereo) 78. 32/6. P. & P. 2/-.
LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP (mono or stereo records on mono equipment. 30/-, P. & P. 2/-.
FEW ONLY! ACOS HIGH-G Mono Cartridge for EP and LP. Only 10/-, P. & P. 2/-.

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TAI
● Peak output in excess of 1 1/2 watts.
● All standard British components.
● Built on printed circuit panel size 6 x 3in.
● Generous size Driver and Output Transformers.
● Output transformer tapped for 3 ohm and 15 ohm speakers.
● Transistors (GET114 or S1 Mullard AC128D and matched pair of AC128 o/p). ● 9 volt operation.
● Everything supplied, wire, battery clips, solder, etc.
● Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. **SPECIAL PRICE 45/-.** P. & P. 3/-. Also ready built and tested, 52/6. P. & P. 3/-.

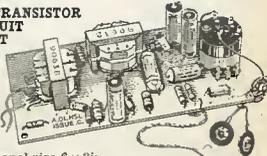


HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer, EZ80 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with valves and good quality output transformer. **FEW ONLY.**

OUR ROCK BOTTOM BARGAIN PRICE 49/6 P. & P. 6/-

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 15 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY **£7.8.6.** P. & P. 8/6. Also available ready built and tested complete with std. input sockets, **£9.5.0.** P. & P. 8/6.

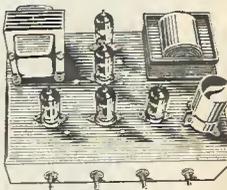

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19

Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

If it's
components
you're after...

... you need the

HOME RADIO CATALOGUE

Its the finest, most comprehensive Catalogue we have ever produced—this latest edition. It has 330 pages, over 8,000 items listed, over 1,500 of them illustrated. Everything for the keen constructor—including tools and test gear. With each Catalogue we supply a 30-page Price Supplement, a bookmark giving electronic abbreviations, and an order form. All for only 8/6d plus 3/6d post, packing and insurance. Moreover, every catalogue contains 6 vouchers, each worth 1/- when used as directed.

Please write your Name and Address in block capitals

Name _____

Address _____



Home Radio (Components) Ltd., Dept. P.E.,
234-240 London Road, Mitcham, CR4 3HD, Surrey

POST THIS COUPON NOW
with cheque or P.O. for 12/-

The Price of 12/- applies only to catalogues
purchased by customers residing in U.K.



MAIL ORDER

A VERY large number of constructors, possibly the majority, depend upon mail order for their components. Outside London and a few other large centres, facilities for personal shopping rarely exist. It must be acknowledged that the present day amateur constructional activity is sustained in the main by the suppliers who provide this service through the post. Electronics enthusiasts in the more remote parts of the United Kingdom in particular have cause to be grateful for this development in retail distribution methods. The reader in Wick or St. Davids, for example, has access to precisely the same great range of components as the reader in the suburbs of London. This is only just and fair, for the individual living in a sparsely populated area is likely to be even closer wedded to his hobby than the person who suffers from a surfeit of counter attractions in town or city.

The mail order system has its own inherent weaknesses and because of certain shortcomings, this service is often a mixed blessing to those who are entirely dependent upon it for their component needs. From readers' correspondence, a number of points of criticism emerge. A frequent complaint is the impossibility of obtaining all requirements for one particular project from a single supplier. The need to write to several firms is time consuming and the project may remain uncompleted for a long while—maybe all for the want of a single item. This is exasperating to say the least; more seriously, it may cool the reader's enthusiasm for the hobby. Often a complaint of this nature is coupled with the suggestion that mail order suppliers should be encouraged to make up complete kits of parts for constructional projects published in this magazine.

We have every sympathy for readers who suffer this kind of frustration but we are also aware of the problems of the retail trade. The huge variety of electronic components on the market today is quite staggering. The average retailer can only stock a limited range of items and generally some form of specialisation is adopted which has economic advantages to both seller and purchaser. Regarding complete kits, even where an extensive range of components is stocked, it would not be a viable business proposition to make up kits for every design published. True, the more popular projects certainly seem to offer a lucrative business but the retailer would, by and large, have to back his own hunches for it is impossible to forecast the demand any particular design will arouse.

F. E. Bennett—*Editor*

THIS MONTH

CONSTRUCTIONAL PROJECTS

STROBOSCOPE	416
LINEAR SCALE OHMMETER	427
P.E. ORGAN—2	440
PHOTOGRAPHIC ENLARGER EXPOSURE METER	450

SPECIAL SERIES

OPERATIONAL AMPLIFIERS—I	421
COLD CATHODE TUBES—2	435

GENERAL FEATURES

OPTICAL CHARACTER RECOGNITION	454
AN INTERNATIONAL TECHNICAL LANGUAGE	461
INGENUITY UNLIMITED	465

NEWS AND COMMENT

EDITORIAL	415
SPACEWATCH	424
MARKET PLACE	439
ELECTRONORAMA	448
A.P.A.E. EXHIBITION	453
NEWS BRIEFS	458
POINTS ARISING	458
LABEX EXHIBITION	462
PHYSICS EXHIBITION	469
READOUT	470

*Our July issue will be published on
Friday, June 13*

All correspondence intended for the Editor should be addressed to: The Editor, PRACTICAL ELECTRONICS, IPC Magazines Ltd., Tower House, Southampton Street, London, W.C.2. Advertisement Offices: PRACTICAL ELECTRONICS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Phone: 01-236 8080.
Subscription Rates including postage for one year, to any part of the world, 42s. © IPC Magazines Ltd., 1969. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is specially reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

STROBOSCOPE

By B. HUNTER

THE stroboscope is basically a flashing light, the frequency of which may be varied from a few flashes per second to several hundred per second. If a rotating or vibrating object is viewed by this flashing light, and the flash frequency is adjusted until it coincides with the speed of rotation or vibration, then the object will appear stationary (the object will also appear stationary if the frequency of the flashes is a sub-multiple of the speed of rotation).

The complete unit consists of the four basic sections described below.


FLASH TUBE AND ASSOCIATED CIRCUITRY

The flash tube (V1) is an NSP2 type which is capable of flashing at a maximum frequency of 250Hz. The tube is gas filled and has four electrodes; the anode, the cathode and two grids or trigger electrodes.

If a voltage of between 220 and 380 volts is applied between cathode and anode, and a suitable voltage pulse is applied across the trigger electrodes, some of the gas in the tube is ionised and conducts. This conduction triggers off a discharge between the cathode and the anode, and the tube emits a flash of light.

In the circuit described here, trigger 2 (Pin 4) is held about 50V positive with respect to earth by the potential divider formed by R7 and R8; trigger 1 (Pin 5) is at earth potential. When it is required to fire the tube, trigger 1 is made negative with respect to earth, and when it is more than .50V negative, the tube will fire.

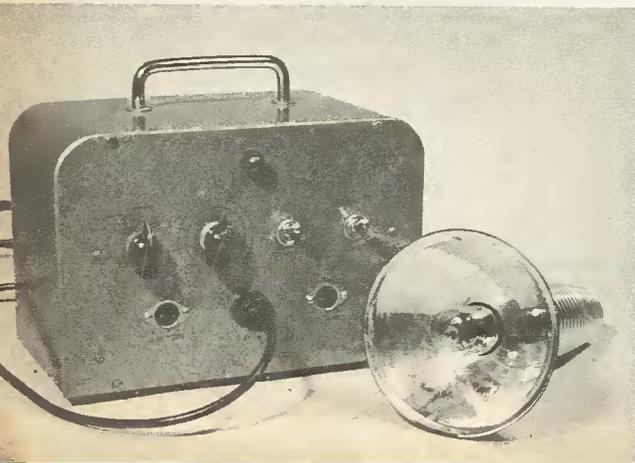Complete stroboscope showing flash head and front panel layout



To supply the large amount of energy required for the flash, it is necessary to connect a capacitor (C10 to C15) across the tube between cathode and anode. Between flashes this capacitor charges up to supply potential, and during the flash it is rapidly discharged through the tube releasing all the stored energy in a very short period.

Although paper capacitors are recommended for the discharge capacitors, the author has successfully used polyester types. However, it is not known if polyester capacitors will last as long as paper ones but they have the advantage of smaller size for the same capacitance; the final choice of type is left to the constructor.

TRIGGER CIRCUIT

The trigger circuit consists of the capacitor C9, two resistors (R5 and R6) and the thyristor SCR1. The capacitor charges to supply potential through R5 and R6 between flashes. This means that, when C9 is fully charged, point "x" in Fig. 1 is positive with respect to point "y" which is at earth potential, since there is virtually no current flow through R6. When the thyristor is triggered it becomes a short circuit and earths point "x". At this instant, point "y" is negative with respect to earth, C9 then discharges through R6. This fulfils the trigger requirements for the tube, as stated earlier, and hence the tube fires.

Once the thyristor has been turned on, it will not turn off until the current flowing through it falls below a value known as the holding current. As soon as C9 has discharged the only current which will flow through the thyristor is from the h.t. line through R5, therefore R5 must have a high enough resistance to limit the current to below the thyristor's holding current.

DESIGN POINTS

When the holding current is known, R5 may be easily calculated from Ohm's law. If the holding current for the thyristor used is not known, R5 can be calculated by the following method.

Connect a voltmeter across SCR1 as shown in Fig. 2 (making R5, 6 kilohms). With the h.t. on, the full supply volts should appear across the thyristor. The gate of the thyristor should now be made about 4V positive with respect to the cathode. This may be conveniently arranged by connecting a battery between the gate and the cathode (Fig. 2).

When the gate is made positive, the voltage across the thyristor should fall, almost to zero, showing that the thyristor has turned on. Removing the voltage on the

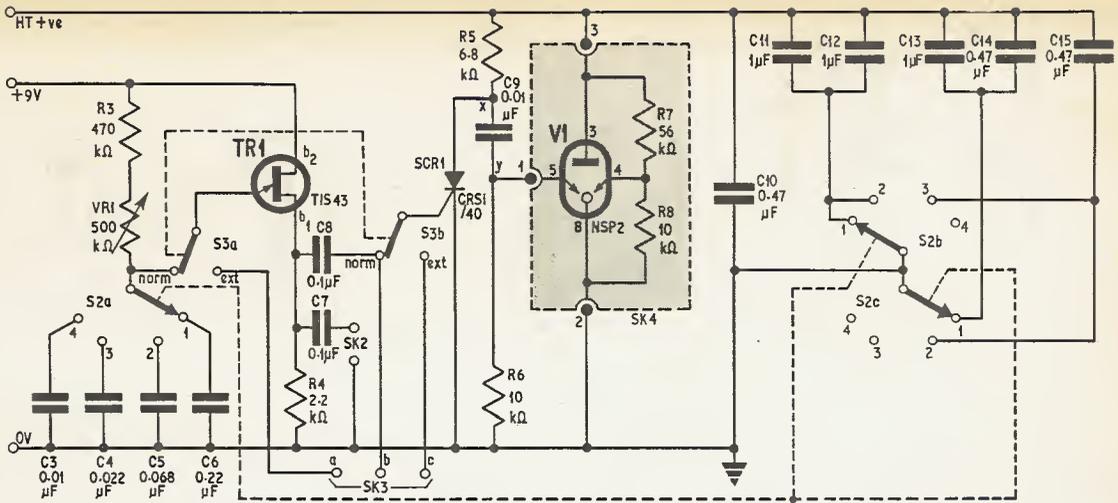


Fig. 1. Circuit diagram of the stroboscope not showing the power supply

gate, should cause the voltage across the thyristor to return to the supply voltage, showing that it has turned off.

If the voltage does not reappear, the current through the thyristor is above the holding current, and R5 should be increased to the next preferred value. The above procedure is then repeated until the thyristor turns off as soon as the gate voltage is removed.

The thyristor specified requires about 50mA holding current, therefore R5 is made 6.8 kilohms, limiting the current to 44mA. The dissipation in R5 at 44mA is about 13 watts, therefore R5 must be at least a 10W resistor (maximum current is only passed for part of each cycle).

Because C9 is charged through R5 and R6, the sum of these resistors must not be too great, or C9 will not charge fully at higher flashing rates. The maximum flashing rate is 250Hz (limited by the tube), therefore the shortest period of time in which C9 must charge will be four milliseconds, hence the maximum value of R5 + R6 is 40 kilohms (R6 is 10 kilohms, so that R5 + R6 will be 16.8 kilohms—well within the limit).

PULSE GENERATOR


In order to turn the thyristor on, some form of pulse generator is required. There are certain conditions which the pulse generator must meet. These are:

- (1) A pulse greater than 3V is required, as this is the minimum gate turn-on voltage for the thyristor specified.
- (2) The pulse should be a positive spike with a very short rise-time, in order to trigger the thyristor reliably.
- (3) The pulse generator must be stable at any frequency.
- (4) The generator must supply pulses over a range of frequencies from 10Hz to 250Hz.

One form of pulse generator which meets all of these conditions is the unijunction transistor oscillator (Fig. 1); it also has the advantage of simplicity.

When a voltage is applied to the oscillator, one of the capacitors C3 to C6 (depending upon the position of switch S2), begins to charge through R3 and VR1 causing the voltage on the emitter of the unijunction to rise until, at a certain voltage, the unijunction fires.

Fig. 2. Set up for finding the value of R5

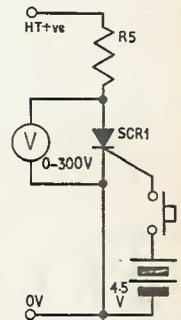

The capacitor then discharges through R4, producing a very fast pulse at the gate of the thyristor which turns it on.

The pulse generator gives the necessary frequency coverage in four ranges, 10Hz to 25Hz, 20Hz to 55Hz, 50Hz to 110Hz, and 100Hz to 250Hz. The ranges are selected by switching the charging capacitor; frequency adjustment over each range is achieved by VR1. The range switch (S2) is a three pole switch; one pole switches the frequency range capacitors C3 to C6 and the other two poles switch the discharge capacitors C11 to C15.

EXTERNAL TRIGGERING

The unit may be triggered externally thus enabling it to be synchronised with a rotating or vibrating object. This is particularly useful for observation of rotating machinery not having a constant speed. External triggering also enables the unit to be used for timing car ignition systems.

Socket SK3 is provided for trigger inputs and switch S3 selects internal or external triggering. With the switch in the external position, two triggering circuits are obtainable.

By shorting connections "b" and "c" on SK3 a low voltage pulse applied between "a" and earth will turn on the unijunction and trigger the thyristor in the normal manner. The second triggering method is to apply a pulse directly to the gate of the thyristor via connection "c" on SK3. In this case the pulse must be greater than the minimum triggering voltage of the

thyristor (3V for the thyristor specified) and should have a fast rise time in order to trigger the thyristor reliably.

POWER SUPPLY

The h.t. supply (Fig. 3) is obtained by half-wave rectification of the 250V a.c. from the transformer by the rectifier D1—C1 provides some smoothing.

The low voltage required for the pulse generator is obtained by bridge rectification of the 6.3 volt heater supply from the transformer (T1) and, with smoothing provided by C2, this gives 9V d.c. Very little current is

COMPONENTS . . .

Resistors

- R1 3.3k Ω 10W wirewound
- R2 27 Ω
- R3 470k Ω
- R4 2.2k Ω
- R5 6.8k Ω 10W wirewound
- R6 10k Ω
- R7 56k Ω $\frac{1}{2}$ W
- R8 10k Ω $\frac{1}{2}$ W
- All 10%, $\frac{1}{4}$ W carbon except where stated

Potentiometer

- VRI 500k Ω linear

Capacitors

- C1 8 μ F elect. 450V
 - C2 100 μ F elect. 15V
 - C3 0.01 μ F 12V
 - C4 0.022 μ F 12V
 - C5 0.068 μ F 12V
 - C6 0.22 μ F 12V
 - C7 0.1 μ F 12V
 - C8 0.1 μ F 12V
 - C9 0.01 μ F 400V
 - C10 0.47 μ F
 - C11 1 μ F
 - C12 1 μ F
 - C13 1 μ F
 - C14 0.47 μ F
 - C15 0.47 μ F
- } 400V paper or polyester (see text)

Semiconductors

- TRI TIS43 unijunction transistor
- SCR1 CRS1/40 400 p.i.v. 1A thyristor
- D1 BY100
- D2-D5 OA200 or OA202 (4 off)

Switches

- S1 2 pole on/off toggle
- S2 Maka Switch shaft unit and 3 pole, 4 way wafer
- S3 2 pole change-over toggle

Transformer

- T1 Mains primary; secondary 250V at 25mA and 6.3V, 1.2A (Radiospares)

Flash Tube

- V1 NSP2 flash tube (Ferranti)

Sockets

- SK1 Mains plug and socket (Bulgin type P429)
- SK2 3 pin DIN socket
- SK3 3 pin DIN socket
- SK4 Mains plug and socket (Bulgin type P429)

Miscellaneous

- 6.3V panel lamp and holder
- 250mA fuse and holder
- Veroboard—0.15in pitch, 4 $\frac{1}{2}$ in \times 8in (see Figs. 4 and 5)
- Case (see text)
- Four mounting pillars (1 $\frac{1}{4}$ in \times $\frac{1}{4}$ in diameter)

required by the pulse generator (of the order of 2mA), so almost any diodes will suffice for the bridge rectifier (D2 to D5).

CONSTRUCTION

The unit is built on two pieces of veroboard; the low voltage supply components, pulse generator and trigger circuit on one board, and the h.t. supply components and the discharge capacitors (C10 to C15) on the other board. Layout of each board is shown in Figs. 4 and 5, the connections to the boards being made as shown.


The unit is housed in a case measuring 9in \times 6in \times 5in, the boards are mounted upright beside the mains transformer as shown in the photograph and Fig. 6.

Board "A" is fixed to the chassis by the two mounting brackets; board "B" is then attached to board "A" by four pillars. Both boards must be mounted well clear of all other components and the chassis.

The flash tube can be housed in a torch case or a special holder can be made up. The international octal base used for the NSP2 tube is mounted behind the reflector which must be cut away to clear the tube. If a special holder is made, an old car headlamp reflector can be used (it must be the old type—not a modern sealed beam unit).

Resistors R7 and R8 are mounted on the base and a three core mains lead and Bulgin plug connect the flash unit to SK4. Care must be taken to prevent any of the base connections from shorting to each other or the case.

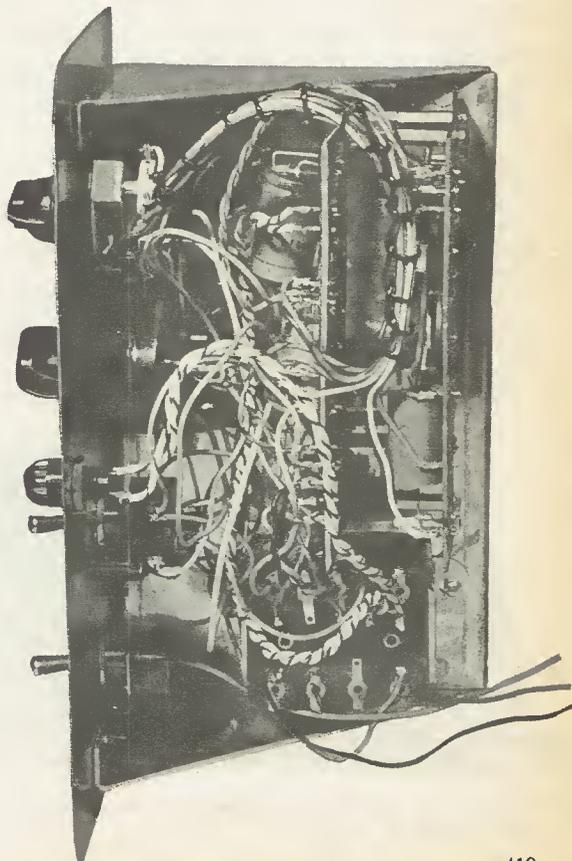Interior view of unit showing component layout. See Fig.6



EXPERIMENTS WITH THE OPERATIONAL AMPLIFIER

By G. K. FAIRFIELD

The first of three articles dealing with this versatile type of amplifier and the many uses to which it may be put in measurement, test and general experimental work.

DURING experimental work, it is often required to make many different measurements of component values and circuit performance. The acquisition of individual bridges and meters to measure all of these can be a very expensive process. An alternative approach, suggested in this article, is to construct a circuit to do each job as it arises and take the circuit to pieces when it is no longer required.

This does not sound a very practical proposition and in the past this would have involved careful design and construction, together with the necessary calibration procedures probably not available to the experimenter. With the advent of the operational amplifier this situation has changed and it is now quite feasible to construct, for example, an accurate inductance meter in less than half an hour, provided an a.c. meter, a source of alternating current (for example, 50Hz mains voltage) and an operational amplifier are available.

Before beginning to describe the many uses to which this interesting device can be put, it will probably be necessary to explain to many readers what is meant by an operational amplifier.

WHAT IS AN OPERATIONAL AMPLIFIER?

The operational amplifier was originally developed during the 1940's for use in high accuracy analogue computers. It is basically a d.c. amplifier having a very large gain and it is always used with components added to give a large amount of negative feedback around the circuit. To understand the basic function of an operational amplifier, consider the block schematic diagram in Fig. 1.1 and carry out a few simple calculations on it.

The d.c. amplifier shown in the diagram always consists of an odd number of amplifying stages so as to provide an inverted signal at its output terminals. We can therefore state that its gain is $-A = -V_o/V_i$.

The two elements Z_i and Z_f are added to provide negative feedback. The input element has an impedance Z_i and the feedback element has an impedance Z_f . We can see from the diagram that the input signal current to the amplifier, i_i , is the sum of the current through the feedback network, i_{fb} , and that through the input element, i_s .

$$i_i = i_{fb} + i_s$$

Now if the voltages at the input and output of the whole network are v_s and v_o , as shown, and the actual voltage at the amplifier input as v_i , then using Ohm's Law:

$$i_i = i_{fb} + i_s = \frac{v_o - v_i}{Z_f} + \frac{v_s - v_i}{Z_i}$$

The design of the d.c. amplifier (assumed in Fig. 1.1) is such that it has a very high input impedance so that its grid (or base in the case of a transistor amplifier)

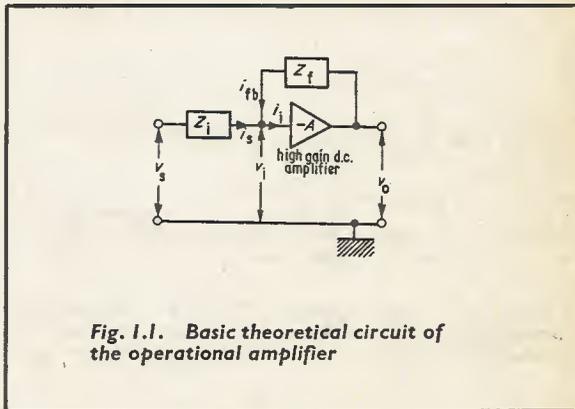


Fig. 1.1. Basic theoretical circuit of the operational amplifier

current i_i is very small indeed—in practice just a few millimicroamps. Consequently we can afford to ignore this in the calculation and put i_i as zero which simplifies the above equation to

$$\frac{v_o - v_i}{Z_f} + \frac{v_s - v_i}{Z_i} = 0$$

Substituting for v_i , and the output voltage v_o divided by the amplifier gain $-A$,

$$\frac{v_o + \frac{v_o}{A}}{Z_f} + \frac{v_s + \frac{v_o}{A}}{Z_i} = 0$$

and since A is very large, usually several tens of thousands or more, the value of v_o/A is very small compared with v_o or v_s and can also be neglected.

Consequently we can write a much simplified equation

$$\frac{v_o}{Z_f} + \frac{v_s}{Z_i} = 0$$

or by rearrangement

$$\frac{v_o}{v_s} = -\frac{Z_f}{Z_i}$$

This is the fundamental and very important relationship of an operational amplifier and shows that the input/output gain of the device depends entirely on the ratio of Z_f/Z_i and will not be affected by the internal characteristics of the amplifier itself.

Thus the transistors or valves used in the amplifier can deteriorate, or applied h.t. voltage fall off considerably, before any change in the gain of an operational amplifier is observed. This, of course, assumes that Z_f/Z_i does not become very large (less than 100) which is always the case with a practical amplifier.

As a consequence of this relationship we can, by suitable choice of components for Z_i and Z_f , make the gain of the amplifier vary in strict accordance with these impedance values. It is this fact which is made use of in the various measuring circuits to be described in the following pages.

AN INDUCTANCE METER

By using such an amplifier (a few typical designs are described later) we now have an accurate device with which to measure a number of electrical values.

Consider first the measurement of inductance. The circuit is shown in Fig. 1.2. Here Z_i is a pure resistance, of value R_i ohms, and the feedback network is an unknown inductance, value L henries. To measure its

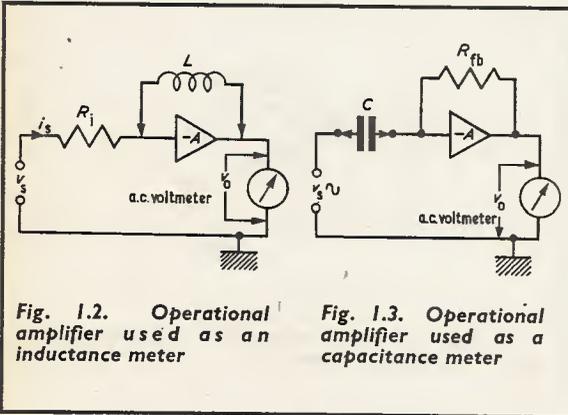


Fig. 1.2. Operational amplifier used as an inductance meter

Fig. 1.3. Operational amplifier used as a capacitance meter

value, set the input alternating voltage at a suitable frequency and measure the output voltage on an r.m.s. reading a.c. voltmeter.

The inductance value is given as

$$L = \frac{v_o R_i}{2\pi f v_s} \text{ henries}$$

If a signal generator is available the frequency can be set to, say, 800Hz, and v_s as 4 volts which simplifies reading the inductance value off the meter scale.

The meter shows the direct-reading in inductance, where 1 volt a.c. represents 0.05H, 0.5H, or 5H depending on the value of R chosen.

This will be made clear in the table given below which shows the inductance range available for different values of R_i .

Table 1.1: INDUCTANCE RANGES ON METER

L-range f.s.d. (henries)	R_i (ohms)	v_o (volts)
0-0.5	1,000	0-10
0-5.0	10,000	0-10
0-50.0	100,000	0-10

If a signal generator is not available a 50Hz voltage from the low voltage secondary of a mains transformer can be used. This is, in any case, more convenient for larger values of inductance (say greater than 1H).

If we choose 6.3V r.m.s. from a transformer secondary winding then the selection of suitable values of R_i will again enable a simple-to-read meter scale relationship to be obtained (see Table 1.1).

If smaller values of inductance are required to be measured then a signal generator must be used and the frequency set at 8kHz, when the inductance ranges in Table 1 will be divided by 10.

Mathematically inclined readers may be interested in how the equation for inductance value was derived.

If the grid current, i_i of the operational amplifier is very small, and tends to zero, then the input current from the signal generator (i_s) passes through R_i and L in series and we can write for this current,

$$i_s = \frac{v_s}{R_i}$$

$$v_s = v_{s(\max)} \sin \omega t$$

where $v_{s(\max)}$ is the maximum value of v_s and ω is 2π times frequency f . The output voltage developed across L is

$$v_o = L \left(\frac{di_s}{dt} \right)$$

Substituting for i_s and evaluating we have,

$$v_o = L \left(\frac{v_{s(\max)}}{R_i} \right) \omega \cos \omega t$$

which gives by rearrangement (ignoring the phase shift),

$$L = \frac{v_o R_i}{2\pi f v_s}$$

The point to note is that the circuit performs the mathematical operation of differentiation and this gives one reason why operational amplifiers are extremely valuable in analogue computer operation.

A CAPACITANCE METER

Exactly the same arrangement can be used in order to measure capacitance. The circuit is shown in Fig. 1.3 and, in this case, the unknown capacitor C takes the place of the input resistance Z_i in the operational amplifier circuit shown in Fig. 1.1. The feedback network is a resistance of value R_{fb} ohms. The capacitance value is given by

$$C = \frac{v_o}{2\pi f R_i v_s}$$

Here again the frequency of the signal generator can be chosen to facilitate meter reading. This can be made 600Hz and v_s as 26.5V r.m.s. The range will then depend on R_i as seen from Table 1.2.

Table 1.2: CAPACITANCE RANGES ON METER

C-range f.s.d. (pF)	R_{fb} (ohms)	v_o (volts)
0-1,000	100,000	0-10
0-10,000	10,000	0-10
0-100,000	1,000	0-10

Table 1.3: HIGHER CAPACITANCE RANGES ON METER

C-range f.s.d. (μF)	R_{fb} (ohms)	v_o (volts)
0-0.1	51,000	0-10
0-1.0	5,100	0-10
0-10.0	510	0-10

For larger values of C (say greater than $0.01\mu F$) the mains frequency of 50Hz can be used. If the signal source is 6.3V r.m.s. as before, then the calibration for the meter (which can be a 0-10V a.c. meter) is simplified as shown in Table 1.3.

The derivation of the capacitance equation follows similar lines to that given for the inductance circuit $v_s = v_{s(max)} \sin \omega t$ as before and

$$i_s = C \left(\frac{dv_s}{dt} \right)$$

The output voltage developed across R is:

$$v_o = i_s R_i = CR \left(\frac{dv_s}{dt} \right)$$

Substituting for v_s and evaluating gives

$$v_o = CR_i \omega v_{s(max)} \cos \omega t$$

From which by rearrangement the original equation for C is

$$C = \frac{v_o}{2\pi f R_i v_s}$$

This too can be described mathematically as a differentiation circuit.

A MEGOHMMETER

Measurement of resistance values up to several hundreds of megohms can be carried out simply with the operational amplifier circuit in Fig. 1.4. A d.c. supply of up to 10V, a 10V d.c. meter, and a precision input resistance R_i are required in addition to the operational amplifier.

The resistance to be measured R_{fb} is connected across the amplifier feedback path; the value may be read on the meter scale. This will be

$$R_{fb} = R_i \left(\frac{v_o}{v_s} \right) \text{ megohms}$$

where R_i is in megohms.

Table 1.4: RESISTANCE RANGES ON THE METER

R-range f.s.d. (megohms)	R_i (megohms)	v_o (volts)
0-5	0.1	0-10
0-50	1.0	0-10
0-500	10.0	0-10

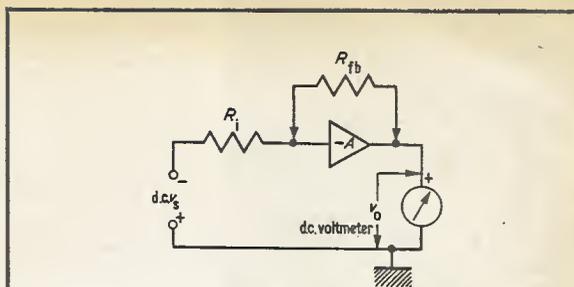


Fig. 1.4. Operational amplifier used as a megohmmeter

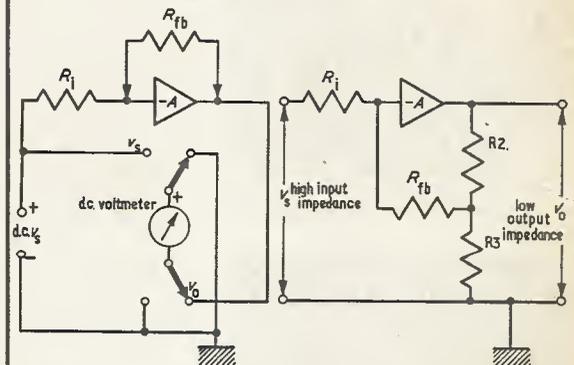


Fig. 1.5. Switching voltmeter between input and output of megohmmeter

Fig. 1.6. Impedance converter attachment

Notice that an accurate source of voltage is not required. Only the ratio v_o/v_s is required; this can be read by putting the meter across input and output terminals in turn (see Fig. 1.5).

From the point of view of easy scale reading it is convenient if v_s is fixed. If v_s is chosen to be 0.2V, then the output meter can be calibrated directly in megohms as given in Table 1.4.

HIGH INPUT IMPEDANCE ATTACHMENT


The need often arises to measure a d.c. voltage at a high impedance point in the circuit where an ordinary multi-range meter will not be suitable. This type of meter usually has an internal resistance of 20,000 ohms/volt and will load the circuit much too heavily.

The operational amplifier circuit in Fig. 1.6 will achieve this type of measurement with very little loading. The input resistance R_i can be made very many megohms; the combination of low impedance meter and operational amplifier will have the characteristics of a vacuum tube voltmeter.

Choice of component values for the feedback network is important since, if R_{fb} is too large, some noise will be introduced into the circuit.

For a gain of -1 we must make $R_2/R_3 = R_i/R_{fb}$. For an input resistance of, say, 10 megohms (R_i) and a reasonable value for R_{fb} , say 1 megohm, then R_2 could be 100 kilohms and $R_3 = 10$ kilohms which will give an extremely satisfactory performance.

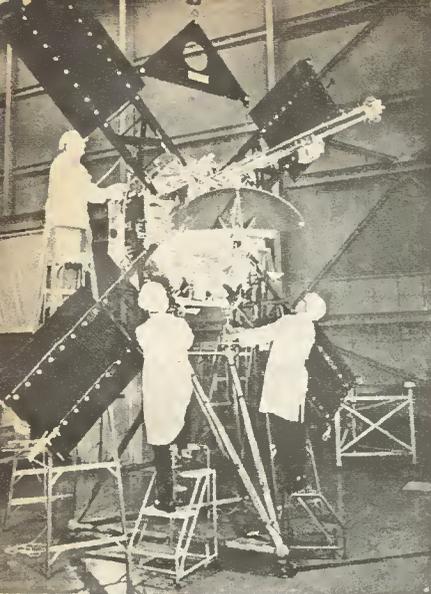Next month: The operational amplifier used to measure very small currents and voltages.



Checking all stages of Mariner-Venus satellite

SPACEWATCH

By Frank W. Hyde

ROBOT REPAIR SATELLITE

The Aero-Propulsion Laboratory of the U.S. Air Force awarded a contract to the General Electric Corp. of America for a study of an android type of satellite which could perform rescue and repair operations in space. It would also be required to maintain satellites in space. The robot would be operated entirely by a remote control system which could be Earth based or in a nearby space vehicle.

The scheme envisages quite sophisticated techniques since there would be a kind of "force feedback" so that the remote operator could "feel" the moment-to-moment contact operations of the manipulators. The application of manipulative methods that have been developed over the past few years, both mechanical and bio-electrical, would enable the operators to be in complete control with all data transmitted back to his hands at any moment.

Present limitations on completely remote control of such delicate actions is one of time lag. In near space, such as for vehicles in earth orbit, there would be no difficulties but for vehicles at moon distances the effect of the communication time lag would become significant. A specification based on previous work has been put forward by Richard H. Blackner of GEC.

The robot repair satellite would consist of two master slave arms and hands, the telemetry system, and a television system mounted on a manoeuvrable satellite under remote control which carries tools and spares.

Remote firing of directional thrusters could bring the roving satellite to that needing attention and the television cameras would enable the remote operator to couple the two together. Experimental packages could be exchanged, mechanical maintenance of parts carried out, and so on.

One of the special purposes would be to keep satellites in longer operational condition by regular maintenance and or replacement of defective parts.

FRENCH WORK IN ROCKET ASTRONOMY

The French National Centre for Space Research have developed a rocket stabilisation system to enable small telescopes to be mounted on a rocket for measurements above the atmosphere.

The inertial platform system called "Cassiopea" can attain fine pointing on certain flights. The system can be used with solid or liquid fuel rockets. The fine pointing device has so far only been used with liquid fuel rockets.

The pointing accuracy is claimed to be one degree using the inertial platform alone and half a degree using fine pointing. Two star trackers are used to lock the system. The size of the mirror system is about 50cm.

WIND PHOTOGRAPHED BY RADIO TELESCOPE

The first photographic records of the extremely violent winds that occur in the fringe areas of the earth's atmosphere have been made in Australia. These were obtained by Dr B. H. Briggs and his team at the University of Adelaide using an aerial system of 89 aerials mounted on poles 10 metres high and carrying 16km of wire covering an area of 2km².

Pulses from a transmitter are reflected from cloud like formations appearing at a height of between 80 and 640km above the Earth and picked up by the aerial system. Each aerial is connected to a radio receiver which carries the reflected impulses to a control system which varies the brightness of lamps. The moving pattern across these light screens corresponds to the upper atmosphere wind.

The array was completed by the staff and students of the University in three years at about one third the cost of putting the work out to contract.

ROCKETS TO PROBE SOLAR ECLIPSE OF 1970

At Quoddy Inlet, Canada, Nova Scotia scientists are planning to use Black Brant III rockets to probe the upper atmosphere during the eclipse of the sun next year. There will be two experiments, one carried out under Dr A. G. McNamara which will make a direct measurement of the variation of electron density and positive ion densities over the complete trajectory of the rocket. This

means that there will be two measurements of the D- and E-regions.

The other experiment will be under the direction of Dr J. S. Belrose and will measure the differences in the propagation of radio waves using a ground based transmitter which radiates circularly polarised pulse pairs. This will provide a measure of the density of the electrons up to a height of 80km.

The sequence of the experiments will be arranged so that the first rocket will be fired six minutes before the moon begins to pass between the earth and the sun so that the undisturbed condition of day-time ionisation can be used as a base level. The other three rockets will be fired when about 80 per cent of the sun's disc is occulted by the moon.

Previous ground based observations have shown that the greatest changes in ionisation occur between this period of obscuration, reaching a maximum some six minutes after total obscuration. The three rockets will therefore be fired at intervals of six minutes starting just before totality and ending just after the sun reappears.

CANADA'S THIRD SATELLITE

Isis-A Canada's third artificial satellite is a follow up of the two previous successful *Alouette I* (1962) and *Alouette II* (1965) both of which are still doing extremely useful work. The new addition is in a near polar orbit which is elliptical and measures 350 nautical miles at perigee and 1,890 nautical miles at apogee.

The purpose of Isis-A is similar to the previous satellites, namely to make a study of the ionosphere in time and space.

In all, ten experiments are planned and one of these will be a fixed frequency device to map horizontal electron density; another will record vertical density. The other experiments will include the measurement of particle temperature, densities, composition, and radio noise. A v.l.f. receiver will pick up signals generated by lightning.

AGAINST THE BIG BANG

A recent experiment has been performed by scientists in a joint effort between Cornell-Sidney University Astronomy Centre and the Naval Research Laboratory in Washington. This has produced results that seem to cast doubts on the big bang theory.

An *Aerobee* rocket was launched carrying a liquid helium cooled telescope to a height of 170km. Also contained in the rocket were four solid state detectors which were sensitive to a wavelength between 1.3 millimetres and 0.5 microns. The signals recorded in the range were found to be two orders of magnitude greater than was to be expected, namely 8.3 degrees Kelvin as against the 3.0 degrees Kelvin required to support the "big bang" theory.

LOOK!

PRACTICAL!

VISUAL!


EXCITING!



a new 4-way method of mastering
ELECTRONICS
 by doing — and — seeing . . .

1 ▶ OWN and HANDLE a

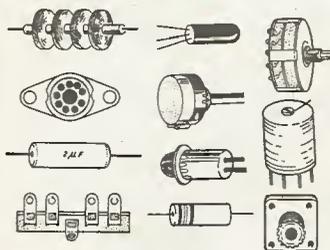complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 ▶ BUILD and USE

a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ READ and DRAW and

UNDERSTAND
CIRCUIT DIAGRAMS

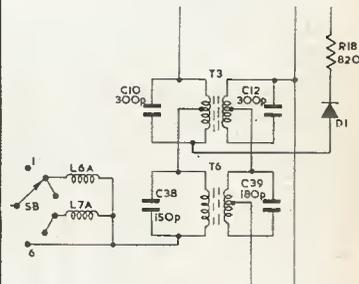

4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
 for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME..... BLOCK CAPS

ADDRESS..... PLEASE PE 4

ELECTRONIC COMPONENTS AND EQUIPMENT



NEW RECOMMENDED LINES AT VALUE FOR MONEY PRICES

★ 3 SPEED 9 VOLT RECORD PLAYER DECK

Brand new British made decks. Plays 78, 45 and 33 $\frac{1}{3}$ rd, 12", 10" and 7" records. Fitted crystal Mono cartridge. Special Price 60/-, p.p. 3/6.

★ STEREO HEADPHONES

Adjustable head-band. High quality 8 + 8 ohm phones with padded earpieces. Fitted jack. Suitable for 3-16 ohms. Frequency range 25c/s to 14kc/s. DHO2S, Price 69/6.



★ TRANSISTOR CHECKER

Complete capacity for checking all transistors npn and pnp for alpha, beta and German. Also diodes complete with leads and instructions. ZQM2, Price £5.19.6, p.p. 3/6.



★ MULTIMETER

Return of a popular model. 2000 ohms/V, 0/10/50/500/1000V a.c./d.c. 0/50 μ A/0/10/250mA d.c. 0/10/100 Ω /1k Ω resistance. dB and capacitance scales. Size 5in x 3 $\frac{1}{2}$ in x 1 $\frac{1}{2}$ in. Robust and easy to use. Complete with leads, batteries and instructions. THL33A, Price 82/6. Leather Case, Price 22/6.



★ SPECIAL OFFER OF EMI TWEETERS

2 $\frac{1}{2}$ in units 6/8W, 5kc/s to 15kc/s, 8 ohms (suitable for 3-8 ohms). Price 12/6, p.p. 1/6.
3in units 10/12W, 3kc/s to 20kc/s. For 3 to 8 ohms—Price 15/-, p.p. 2/-.
For 12 to 16 ohms—Price 20/-, p.p. 2/-.

★ SPRING REVERBERATION UNITS

16 ohms input, 10k Ω output. Twin spring units. Model HR42, 9 $\frac{1}{2}$ in overall, 25-30msec delay. Price 35/-.
Model HR162, 16 $\frac{1}{2}$ in overall, 35-40msec delay. Price £6.10.0.

★ GRID DIP METER

All transistor grid dip meter, absorption wavemeter and osc. detector. Frequency range 440kc/s to 280Mc/s in 6 coils. Uses 3 transistors plus diode with 500 μ A meter. Internal battery. TE15, Price £11.10.0.



★ FIELD STRENGTH METER

Covers 1-250Mc/s. Switches for model control and any application requiring peaking of transmitters and oscillators. 100 μ A meter. Complete with aerial. FSI, Price 45/-.



★ SIGNAL INJECTOR


New model for checking all audio and RF up to VHF. Simple to use. Battery operated. Output approx. 1kc/s, 1-4V pp. Harmonics up to VHF. SE250B, Price 35/-.



TO3 SCOPE £35, p.p. 10/-.

★ QUALITY PANEL METERS



(D.C. RANGES)
38 Series. Face size 42 x 42mm (1 $\frac{1}{2}$ in x 1 $\frac{1}{2}$ in). 50 μ A, 37/6; 100 μ A, 35/-; 200 μ A, 32/6; 500 μ A, 27/6; 1mA, 5mA, 10mA, 50mA, 100mA, 500mA, 25/- each; 10V, 20V, 50V, 100V, 300V and 500V, 25/- each; 1A and 5A, 25/- each. "C" meter, 1mA, 29/6. VAm meter, 37/6, 65 Series. Face size 86 x 78mm (3 $\frac{1}{2}$ in x 3 $\frac{1}{4}$ in). 50 μ A, 62/6; 100 μ A, 52/6; 200 μ A, 47/6; 500 μ A, 45/-; 1mA, 5mA, 10mA, 500mA, 37/6 each. "S" meter, 1mA, 42/6. Other ranges and sizes available. Complete list on request.

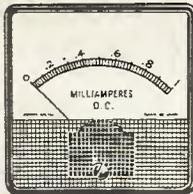

★ 50,000 OHMS PER VOLT MULTIMETER




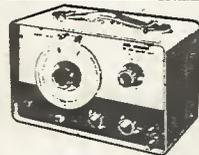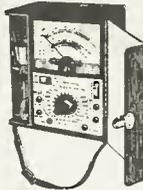Recommended quality instrument with mirror scale and overload protection. 0/0.3/12/60/120/300/600/1200 a.c. 50k Ω /V; 0/6/30/120/300/600/1200V a.c. 10k Ω /V; 0/30 μ A/6/60/300mA, 0/12A; resistance 0/10k Ω /1/10/100M Ω . Meter movement 20 μ A. Polarity reversing switch. Complete with batteries, leads and instructions. AF105, Price £8.10.0, p.p. 2/6; Leather case 28/6.



★ SINE/SQUARE WAVE AUDIO GENERATOR

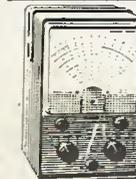Provides audio output on 4 bands. Sine wave 20c/s to 200kc/s, output up to 7V; square wave 60c/s to 30kc/s, 7V p.p. Distortion under 2%. Output impedance 1k Ω . Variable output amplitude control. Supplied with leads and instructions. A.C. mains operated. TE22, Price £16.10.0, carriage, etc., 10/-.




Features low price for such an instrument. Large 6in full view scale meter. 28 ranges. D.C. volts: 0/1 $\frac{1}{2}$ /5/15/50/150/500/1500. A.C. volts: 0/1 $\frac{1}{2}$ /5/15/50/150/500/1500 r.m.s.; 0/1/4/14/40/140/400/1400/4000 p.p. Resistance: R x 10-100-1k-10k-100k-1m-10m. Range 0.2 ohm to 1000M Ω . dB scales: -10 to +65dB. Complete with instructions and leads. H.V. Probe, 50/-, R.F. Probe, 42/6. Model TE65, Price £17.10.0, p.p. 7/6.

★ MULTI-METER 20k Ω /V



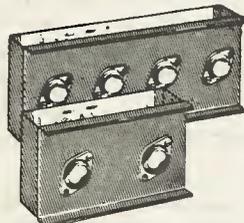Popular model but with extra scale. Range 20,000 ohms per volt. 0/5/25/50/250/500/2500V d.c., 0/10/50/100/500/1000V a.c., 0/50 μ A, 0/2 $\frac{1}{2}$ /250mA. Resistance 0-6k Ω and 6M Ω . Also dB scales or capacitance. 200H, Price 77/6. Leather case, Price 15/-.




★ TRANSISTOR POWER AMPLIFIERS

12W, 3 ohm, 100mV input, 24V supply. Model MPA12/3, £4.10.0, p.p. 3/-.
12W, 12-16 ohm, 100mV input, 40V supply. Model MPA12/15, £5.5.0, p.p. 3/-.
25W, 8-16 ohm, 180mV input, 50/60V supply. Model MPA25, £7.10.0, p.p. 4/6. Power supplies: 24-40V, 90/-, p.p. 3/6; 50-60V, 97/6, p.p. 4/6.
Model PA77W amplifier, 3 ohms 0/1.7mV input operates 12-18V. Price 72/6, p.p. 2/-.


● Henry's 320 page Catalogue has over 6,500 stock items. If you read this magazine and have not obtained one, you should—it will save you a lot of money as Henry's stock most things you require in components and equipment at low prices.

★ EXPERIMENTER'S MODULE

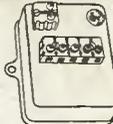Terrific offer of brand new STC time delay electronic units. Adjustable 3-15 sec. 9-12V operated. Supplied complete with suggested used circuits. STC Module Price 35/-.



★ CHASSIS PUNCH KIT

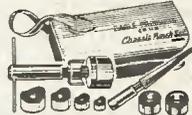

Complete kit with punches $\frac{3}{16}$ in, $\frac{1}{4}$ in, $\frac{1}{2}$ in, $\frac{3}{4}$ in for metal, plastics, etc., up to 16 gauge. Price 35/-, p.p. 4/6.

★ SWR ALIGNMENT METER

Ideal for all transmitter alignment. Built-in field strength meter 100 μ A. Complete. Ready to use. SWR 1:1 to 1:3.



SWR-3, Price 69/6, p.p. 2/6.

★ TRANSISTORISED INTERCOMMS



2-station, £3.10.0; 3-station, £5.15.0; 4-station, £6.12.6. Mains operated. 2-station, uses no wires £11.19.6. Front Door Intercom 90/-.

Did you know we stock over 1,000 Transistors and Devices? Ask for Latest FREE List (No. 36).

★ MAKE YOUR OWN PRINTED CIRCUITS



Supplied complete with copper boards. Templates for shapes, all necessary fluids and pastes. Easy to use. Box forms dishes. Price 17/6, p.p. 2/-.

★ BUILD THIS MW/LW TUNER



Complete high quality superhet tuner. Built-in ferrite rod. Battery operated. Will feed any amplifier. Printed circuit construction, 3 transistors plus diode. To Build, 79/6, p.p. 2/6.

★ CATALOGUE

320 pages with 10/- Discount Vouchers. Price 7/6, p.p. 2/-

● SALES ASSISTANTS WANTED —APPLY TO '303'

HENRY'S RADIO LTD.

303 & 309 Edgware Road, London, W.2

Phones: "303" 01-723 1008/9.

"309" 01-723 6963

Open Mon. to Sat. 9a.m.—6p.m. Thurs. 1p.m (All Mail orders to "303")

Linear Scale OHMMETER

By A. FOORD

This ohmmeter eliminates reading interpolation difficulties, allows the use of standard linear scale meters, and can be used to test transistors safely



A CONVENTIONAL ohmmeter has a non-linear scale (Fig. 1a) which may cover several decades. Whilst this enables a multimeter to cover a wide ohmic range, a meter with a linear scale (Fig. 1b) has several other advantages.

The meter can be read more easily and more accurately, because only a ten to one range is covered and because equal scale divisions make interpolation easier.

Also a standard linear meter scale can be used. This is most important as anyone who has paid several pounds for a microammeter, in order to build a multimeter, is unwilling to attempt to calibrate an extra scale. In any event, most meters have an arrow type of pointer rather than a knife edge, so that there is no room for the extra scale.

BASIC CIRCUITS

The basic circuit for a linear scale ohmmeter is given in Fig. 2. This circuit consists of a constant current generator connected in series with the resistance to be measured (R_x). Since the current through R_x is maintained constant, the voltage measured is directly proportional to its resistance. Thus, by choosing a suitable scale, the voltmeter can be directly calibrated in terms of resistance. No zero or f.s.d. adjustments are

required, because once set up, accuracy depends on the stability of current regulation rather than on adjustments to compensate for changes in battery voltage. With the circuit finally chosen a drop in battery voltage of 15 per cent has little effect on reading accuracy.

If we take an example where I is kept constant at 1mA and we can measure from 0 to 10 volts then, from Ohm's law:

$$E = IR \text{ or } R = \frac{E}{I}$$

then, since I is constant at 1mA: $R \propto V$ in kilohms. For a 1 kilohm resistor we would measure 1V and for a 10 kilohm resistor we would measure 10V. One method of obtaining a constant current is shown in Fig. 3.

The emitter of the transistor will remain at approximately 0V, so that 1mA will flow through the transistor and the unknown resistance.

This circuit has the disadvantage that the voltmeter must take a current which is small in comparison to I , so that the majority of the current does in fact flow through the unknown resistance. While this is possible when I is greater than 1mA (using a meter of 100 μ A f.s.d.) this would no longer be possible if I is reduced to 100 μ A or less.





Fig. 1a. The non-linear scale of a conventional ohmmeter



Fig. 1b. A linear-scale, as used in the linear-scale ohmmeter

Fig. 2 (below). The basic circuit of the linear scale ohmmeter

Fig. 3 (right). A simple constant current generator

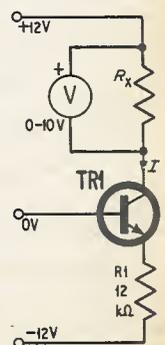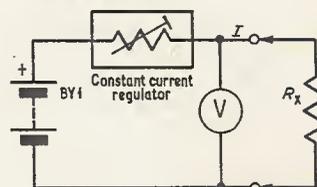

An additional difficulty with this circuit is that the transistor might not have a good current gain at such a low collector current. What we require is a method of sensing the current through R_x regardless of the current through the voltmeter, and this leads to the basic arrangement of Fig. 4.

Here the current I develops a voltage V_R across a standard resistance R and this voltage is compared (by a differential amplifier "A") with a reference voltage (V_r) of 5.6 volts.

If V_R is greater than V_r the amplifier alters the base current of the series transistor (TR2 in Fig. 5) to reduce its collector current, so that V_R is made equal to V_r . The current I is maintained by this negative feedback loop at a value determined by:

$$I = \frac{V_r}{R}$$

By switching R we can obtain constant currents between $10\mu\text{A}$ and 10mA , provided we observe the following points.

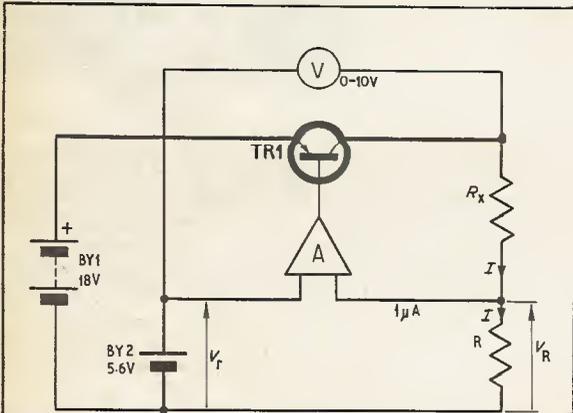


Fig. 4. Block diagram of the linear scale ohmmeter

DESIGN NOTES

The amplifier A must take much less than $10\mu\text{A}$ from the R_x , R chain. It does not matter that, in fact, it takes $1\mu\text{A}$ (10 per cent of the lowest current range) since it remains constant. Hence we can allow for the fact that, on the lowest range, $9\mu\text{A}$ rather than $10\mu\text{A}$ will flow through R ; on the other ranges this $1\mu\text{A}$ drain has no significance.

If R_x is zero, M1 will read zero and no current will flow through the meter, if R_x has a finite value M1 will read and draw current through TR2; however, since this current does not flow through the sensing resistor R , the constant current I is in no way affected.

If a Zener diode is used to provide the 5.6 volt reference, I will remain constant for small changes of Zener current.

In our practical circuit V can be measured by any meter with a 0 to 10V range provided it consumes not more than 1mA for f.s.d. A 1mA meter and appropriate series resistor (10 kilohms less the meter resistance) is used, but the 10V range of a multimeter would serve equally well.

No protection device is needed to prevent damage to the meter, since even with the measuring terminals open circuit only 13V appear across the meter; although this drives the meter over full scale, no harm will result.

Table I

R	560k Ω	56k Ω	5.6k Ω	560 Ω
I	10 μA	100 μA	1mA	10mA
R _x	1M Ω	100k Ω	10k Ω	1k Ω

Values of R from 560 ohms to 560 kilohms give constant currents from 10mA to $10\mu\text{A}$ and ohms ranges from 1 kilohm f.s.d. to 1 megohm f.s.d. (Table 1).

PRACTICAL CIRCUIT

The practical circuit is shown in Fig. 5; there are several points worthy of mention.

On the lower current ranges (less than 1mA) the collector current of TR2 would be 2mA or less (including current demanded by the meter). This current is increased by adding R4, to avoid the drop in transistor current gain which occurs at low collector currents.

To avoid high frequency instability in what is basically a feedback stabilised power supply, two measures are incorporated which are effective on all ranges with the terminals open or short circuited.

Firstly a capacitor C2 is included across the terminals to ensure that they are always connected together as far as h.f. is concerned. Secondly C1 is connected from the collector of TR1 to the negative rail to "roll off" the amplifier frequency response at a low frequency. Since TR1 only passes a collector current of $100\mu\text{A}$, C1 should be a low leakage type, preferably tantalum; its value is not critical.

CONSTRUCTION

Construction is straightforward and shown by the photograph and drawings. Veroboard was used for the amplifier, which is mounted on the meter terminals, as shown in Fig. 6.

The complete amplifier should be constructed and all external wires attached (Fig. 7)—these cannot be added once the amplifier is mounted. The amplifier can then be mounted to the meter terminals.

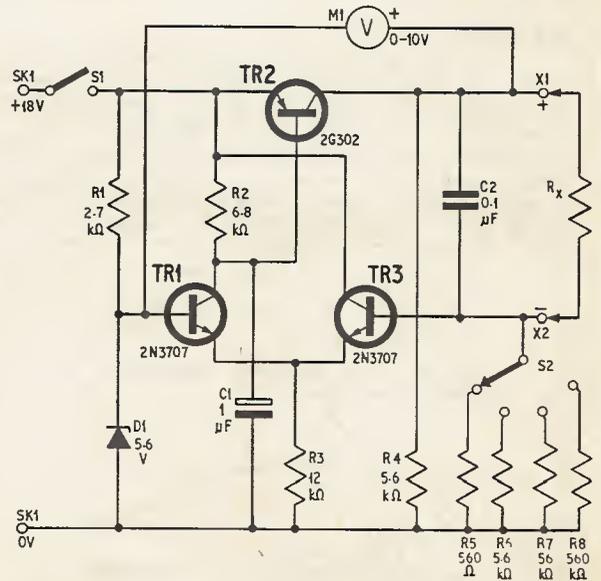


Fig. 5. Practical circuit of the linear scale ohmmeter

COMPONENTS . . .

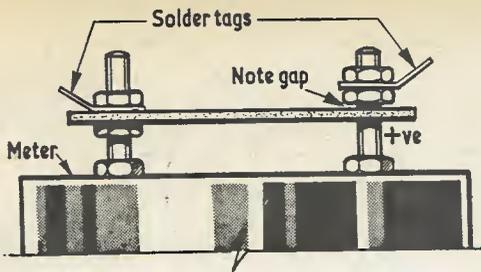


Fig. 6. Amplifier mounting details

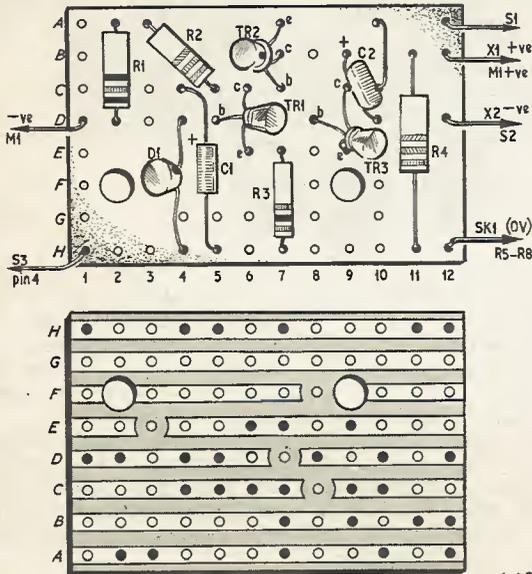


Fig. 7. Layout of the amplifier and underside of the Veroboard

Resistors

- R1 2.7k Ω
- R2 6.8k Ω
- R3 12k Ω
- R4 5.6k Ω
- R5 560 Ω
- R6 5.6k Ω
- R7 56k Ω
- R8 560k Ω
- All $\pm 10\%$, $\frac{1}{4}$ W carbon except where stated

Capacitors

- C1 1 μ F elect. or tantalum 24V
- C2 0.1 μ F polyester

Transistors

- TR1 2N3707
- TR2 2G302
- TR3 2N3707

Miscellaneous

- M1 0-10V f.s.d. (see text)
- S1 Single pole on/off switch
- S2 Single pole, 4 way wafer switch
- SK1 Two way polarised plug and socket
- Terminals, insulated (3 off)
- Diecast box 4 $\frac{1}{4}$ in \times 3 $\frac{1}{2}$ in \times 2in
- Veroboard
- 18V battery

For modification components see Fig. 9

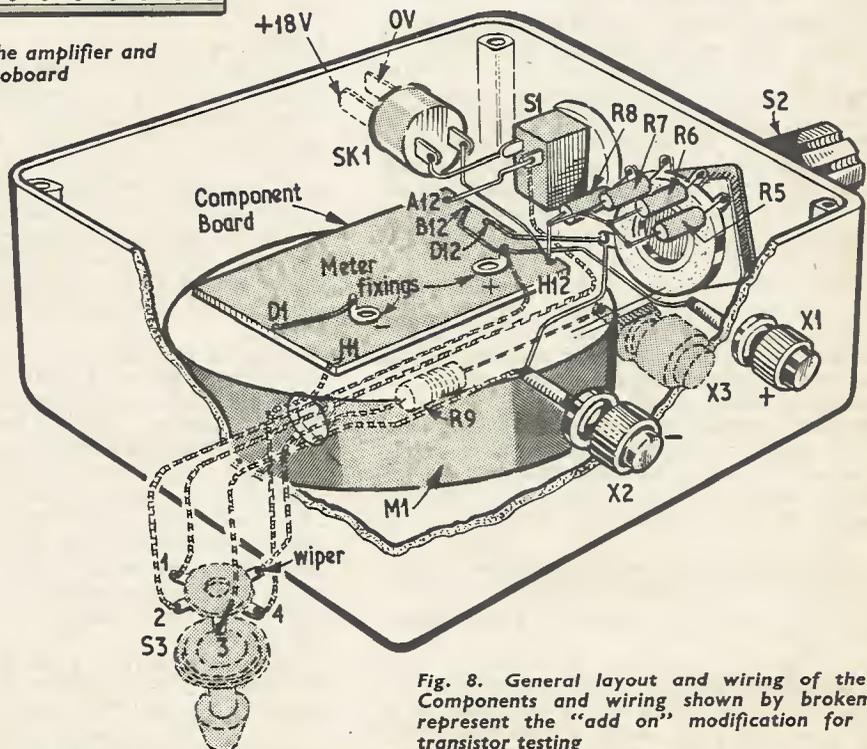
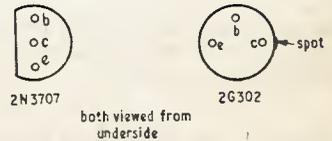


Fig. 8. General layout and wiring of the unit. Components and wiring shown by broken lines represent the "add on" modification for easier transistor testing


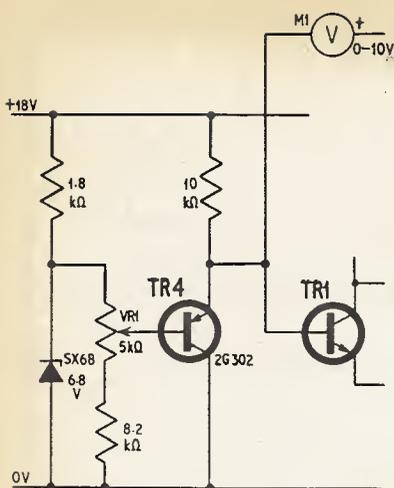


Fig. 9. Circuit modification to provide a calibration control

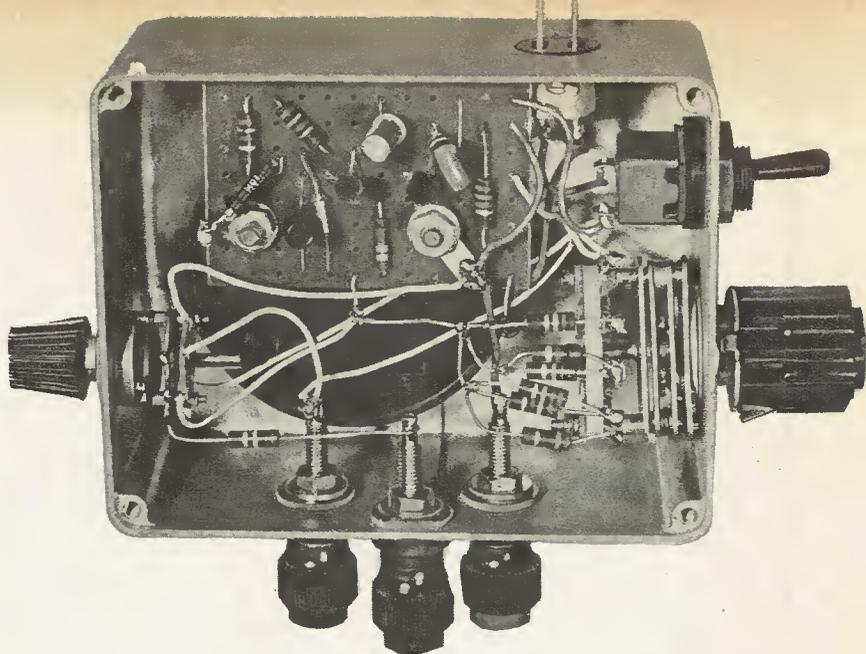

Due to the layout employed there is insufficient clearance on the amplifier board to anchor the board to the positive meter terminal without shorting the copper strips. The board must be spaced above the back of the meter and secured to the positive terminal only (Fig. 6).

The ohmmeter can then be wired up as shown in Fig. 8 but, at this stage, the sensing resistors R5 to R8 should not be connected.

TESTING AND CALIBRATION

Switch to range 2 (1mA current) and solder in R6 (5.6 kilohms), then switch the unit on. With the terminals open circuit the meter should read over full scale; if the battery voltage is reduced to 12 volts the meter should now read about 6.5V (12V-5.6V). If this is satisfactory return the supply to 18V. Next short circuit the terminals and check that the meter reads between 0V and 0.2V. This small voltage represents the difference in base to emitter voltages of TR1 and TR3; the mechanical zero of the meter can be adjusted to obtain a zero reading.

There are several possible methods of calibration depending on the accuracy required. If the Zener voltage is exactly 5.6V and the resistor exactly 5.6 kilohms, then the current would automatically be correct at 1mA. Our readings would then only depend on the accuracy of the voltmeter.

The simplest arrangement is to use close tolerance resistors for sensing and accept any errors due to Zener and voltmeter tolerances. Then the maximum error is:

Voltmeter error (± 2 per cent f.s.d.) + Zener tolerance (± 5 per cent) + Resistor tolerance (± 2 per cent).

Hence, using this method, we could expect an accuracy of ± 10 per cent of f.s.d. for all ranges except the 1 megohm range (we have not allowed for the $1\mu\text{A}$ drawn by the amplifier).

A better approach is direct calibration at f.s.d. against known resistors of 1, 10, 100 kilohm and 1 megohm. If we take the 10 kilohm range as an example; connect the 10 kilohm standard across the terminals (SK1). If the meter reads high then the

constant current is high and must be reduced. It is possible that another 5.6 kilohm resistor would give the required f.s.d. Select a resistor to give a low reading on the meter (going to 6.8 kilohms or 8.2 kilohms if necessary and shunt it with a higher value (start at 68 kilohms) until the meter reads f.s.d.

This can be repeated for the other ranges using appropriate values. A potentiometer and a series resistor could be used for each range provided there is room in the box. With careful setting up an accuracy of ± 2 per cent of f.s.d. can be achieved, using this method for each range.

MODIFICATIONS

The setting up procedure outlined has the disadvantage that it is laborious and depends on the Zener voltage; a change of Zener diode would mean recalibrating to obtain the previous accuracy. To overcome this a modified circuit can be used to provide an f.s.d. setting arrangement (Fig. 9).

In this case the sensing resistors can be 2 per cent high stability types to maintain range to range consistency (the 560 kilohm may need adjustment). VR1 is adjusted to set f.s.d. on a known resistor. The emitter follower TR4 has to be used in order to pass the meter current.

When the test terminals are open circuited the base of TR3 is connected to 0V (via the range selection resistor) while the emitter is maintained positive and 0.6V below the Zener voltage. For Fig. 5 this amounts to a reverse bias on the base-emitter junction of TR3 of 5V, which is within the maximum rating of 6V for the 2N3707.

With the modified circuit (Fig. 9) this reverse bias could reach 6.2V (for a nominal Zener voltage of 6.8V) and is dangerously near the maximum rating. To prevent damage to the transistor should breakdown occur, a 22 kilohm resistor must be included in series with TR3 base to limit the position reverse current to a safe value.

Since under normal working conditions the current bias into the base of TR3 is small, the 22 kilohm resistor in no way affects normal circuit operation, and can also be included in the wiring in Fig. 7 as an added safety measure if required.

USES OF THE OHMMETER

The linear scale ohmmeter can be used for a variety of applications apart from its normal use as an ohmmeter. Some of these uses are described in detail below. The theory behind these uses and the limitations of each method are given where applicable.

ZENER DIODE TESTING

The unit can be used as a constant current source to test Zener diodes. The graph (Fig. 10) shows a normal Zener diode operated from $10\mu\text{A}$ to 10mA , and the reverse breakdown voltage of the base-emitter junction of a 2N709 transistor. Since the junction is quite small currents of less than 1mA were used.

It is interesting to note that the transistor breakdown voltage remained constant down to low levels while the conventional Zener diode voltage fell. This is because the Zener diode was designed to pass currents of up to approximately 50mA , while the base-emitter junction of the transistor was only designed to dissipate a few milliwatts and is inherently a low current Zener diode.

TRANSISTOR TESTING

The unit can be used to test small signal transistors, with the advantage that the possibility of damaging the transistor is reduced. The possible tests have been divided into two sections, one covering tests on *npn* transistors and the other for *pnp* transistors.

NPN TRANSISTORS

Reverse Base-emitter Breakdown Voltage

As suggested in the previous section this can be measured at currents of up to 1mA without damaging the transistor.

Collector Saturation Voltage

This can be measured as shown in Fig. 11. If the base is shorted to the emitter, the transistor will turn off and the meter will read over f.s.d. If the base is connected to $+18\text{V}$ via a resistor, the transistor will turn hard on and the meter will read almost zero (0.3V for a germanium transistor and 0.7V for a silicon transistor).

DC Current Gain

For this arrangement the base is connected to the collector via a resistor (Fig. 12). Most of the constant current (I) is passed through the collector and the base

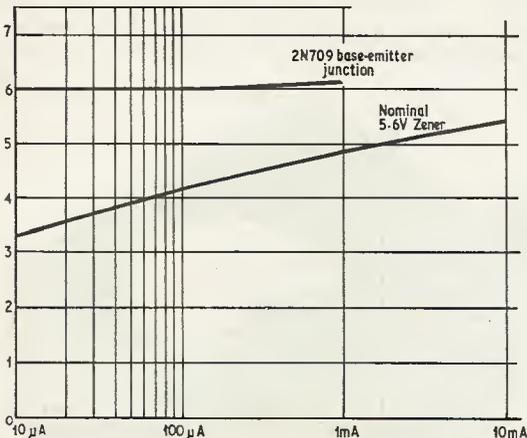


Fig. 10. Graph of results obtained when testing a 5.6V Zener diode and the base-emitter breakdown voltage of a 2N709 transistor

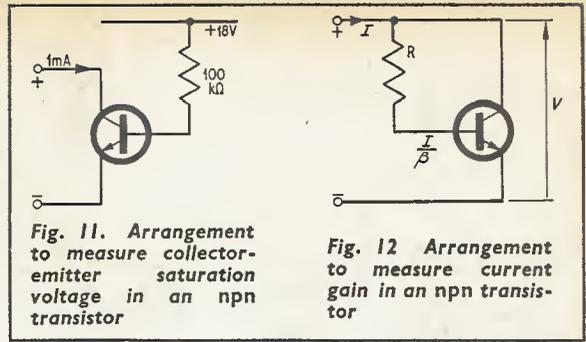


Fig. 11. Arrangement to measure collector-emitter saturation voltage in an npn transistor

Fig. 12 Arrangement to measure current gain in an npn transistor

current has to be (I/h_{te}) which means that the collector voltage must go to $(I/h_{te}) \times R$ volts to maintain the correct base current.

$$\text{Collector current} = I \text{ mA}$$

$$\text{Base current} = (I/h_{te}) \text{ mA}$$

$$\text{Collector voltage } V = (I/h_{te}) R \text{ volts}$$

Rearranging:

$$h_{te} = \frac{IR}{V}$$

We must use resistor values and constant current values appropriate to the transistor.

Example 1:

Choose $I = 1\text{mA}$, $R = 100$ kilohms

The maximum voltage which can appear across the transistor is 13V . Therefore the maximum transistor dissipation = 13mW .

These values are suitable for almost all small signal transistors with gains up to 100 times. A 2N709 transistor gave a reading of 6V .

$$\text{Therefore } h_{te} = \frac{100}{6} \approx 16 (I_c = 1\text{mA})$$

Example 2:

Choose $I = 10\text{mA}$, $R = 10$ kilohms

Maximum transistor dissipation = 130mW

The same 2N709 transistor now read 4V .

$$\text{Therefore } h_{te} = \frac{100}{4} = 25 (I_c = 10\text{mA})$$

Example 3:

To observe the effects of leakage, a high gain germanium transistor was tested (2N1308).

Choose $I = 1\text{mA}$, $R = 1$ megohm

With the base open circuit the meter read 8V showing that leakage was quite high. With the 1 megohm resistor connected, the meter read 4V .

$$\text{Therefore } h_{te} = \frac{1,000}{4} = 250 (I_c = 1\text{mA})$$

With a high leakage transistor it might be necessary to use a collector current of 10mA in order to avoid leakage problems.

PNP TRANSISTORS

Reverse Base-emitter Breakdown Voltage

This can be measured in the same way as for *npn* transistors, but taking note of the reverse polarity required (Fig. 13).



Fig. 13. Arrangement to measure base-emitter reverse breakdown voltage of a pnp transistor

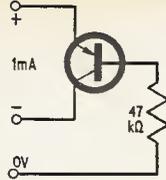


Fig. 14. Arrangement to measure saturation voltage of a pnp transistor

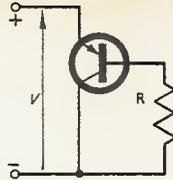


Fig. 15. Arrangement to measure current gain of a pnp transistor

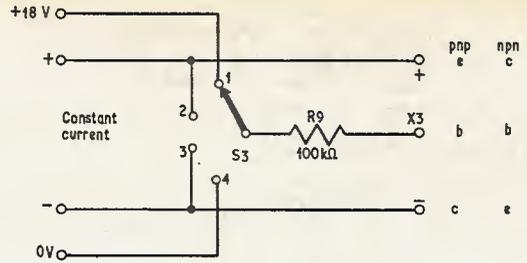


Fig. 16. The circuit of an "add on" unit designed to aid transistor testing

Collector Saturation Voltage

This can be measured at 1mA collector current by connecting a resistor to the 0V rail (Fig. 14).

D.C. Current Gain

Again, this can be measured by using a resistor between base and collector (Fig. 15).

Example 1:

A V205 transistor was tested $I = 1\text{mA}$, $R = 100\text{ kilohms}$, $V = 4\text{V}$

Therefore
$$h_{te} = \frac{100}{4} = 25$$

Example 2:

Transistor was 2G302, $I = 1\text{mA}$, $R = 100\text{ kilohms}$, $V = 1.4\text{V}$

Therefore
$$h_{te} = \frac{100}{1.4} \approx 70$$

Since this collector voltage of 1.4V is lower than we would normally run the transistor, the current should be increased to 10mA (the transistor is rated at 200mW dissipation so we will be within its limits).

Using the same transistor, $I = 10\text{mA}$, $R = 100\text{ kilohms}$, $V = 6.5\text{V}$

Therefore
$$h_{te} = \frac{1,000}{6.5} \approx 150$$

MODIFICATION TO INCORPORATE TRANSISTOR TESTER

By adding an extra terminal and a four-way switch several tests can be made (Fig. 16). For a given switch position the function measured depends on the type of transistor (*pnp* or *npn*), see Table 2. The positions and their uses are set out below for both *pnp* and *npn* transistors.

FOR PNP TRANSISTORS

Position 1

The transistor is held hard off by the resistor to a positive rail and the meter should read over f.s.d. for currents of 10mA or 1mA, unless the transistor is shorted or its collector to emitter breakdown voltage is less than 10V.

Position 2

In this position the transistor is only slightly held off by the resistor between the base and emitter. As an example the 2G302 read over f.s.d. on all ranges except the 10μA where it read 0.1V.

Range	PNP Test	NPN Test
1	Short c-e	Saturation at 1mA
2	Leakage	Gain
3	Gain	Leakage
4	Saturation at 1mA	Short c-e

Position 3

Here the resistor is connected to the collector and gain can be measured from the formula $h_{te} = IR/V$.

Position 4

If I is set to 1mA, the transistor will saturate (meter reads 0.3V or 0.7V) if h_{te} is greater than 10.

FOR NPN TRANSISTORS

Exactly the same tests can be applied, except that the switch positions are reversed.

Position 1


If I is 1mA the transistor will saturate, if it has a h_{te} greater than 20 (the voltage available to force current into the base of the transistor is lower in this configuration).

Positions 2 and 3

These positions are as for the *pnp* transistors.

Position 4

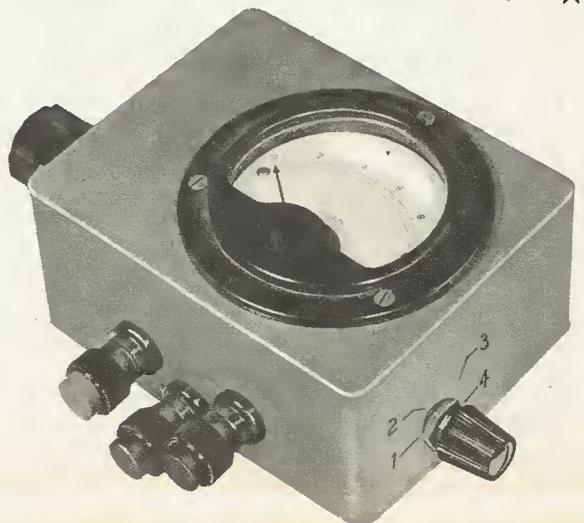Here the transistor is held off by 5-6V, which could cause the base-emitter junction to break down, but this is harmless since the current is limited to less than 0.2mA. ★



USE THE SOLDERING IRONS THE PROFESSIONALS USE

If you want the best in soldering, Antex irons are for you. Pin point precision, fingertip control, interchangeable bits that slide over the elements and do not stick, sharp heat at the tip, reliable elements and full availability of spares. World-wide users, both enthusiasts and professionals solder with Antex. It's time you joined them. Antex soldering irons are stocked by quality electrical dealers, or you can order direct from us. A free colour catalogue will be supplied on request.

CN 15 watts, fitted $\frac{3}{32}$ " Ferraclad bit. The leading iron for miniature and micro miniature assemblies: 18 interchangeable bits from .040 (1 mm) up to $\frac{3}{16}$ " for 240, 220, 110, 50 or 24 volts.

FROM
32/6
ACTUAL SIZE



**PRECISION
MINIATURE
SOLDERING
IRONS**

Made in England

Antex, Mayflower House, Plymouth, Devon.

Telephone: Plymouth 67377/8

Telex: 45296 Giro No. 258 1000




Model CN 240/2
15 watts—240 volts
with nickel plated bit ($\frac{3}{32}$ ") and in a
handy transparent pack.

31/-


COMPLETE PRECISION SOLDERING KIT

Supplied in its own compact, rigid plastic container and includes all of these items:

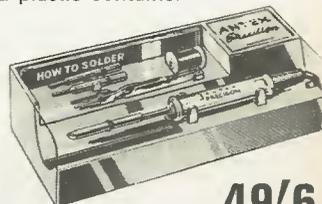
CN 15 watts 240 volts miniature model ($\frac{3}{16}$ ") bit - 2 interchangeable spare bits ($\frac{5}{32}$ " and $\frac{3}{32}$ ") - reel of resin-cored solder - heat sink for soldering transistors - felt cleaning pad - soldering iron stand - storage space for lead and plug.



49/6

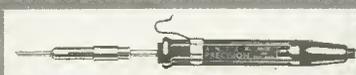

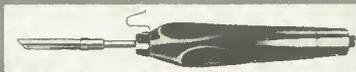Model G — 18 watts. Fitted with $\frac{3}{32}$ " bit. Interchangeable spare bits $\frac{1}{8}$ ", $\frac{1}{16}$ " and $\frac{1}{4}$ ". For 240, 220 or 110 volts. 32/6.



Model E — 20 watts. Fitted with $\frac{1}{8}$ " bit. Interchangeable spare bits $\frac{3}{32}$ ", $\frac{1}{16}$ " and $\frac{1}{4}$ ". For 240, 220 or 110 volts. FROM 35/-.



Model ES — 25 watts. Fitted with $\frac{1}{8}$ " bit. Interchangeable spare bits $\frac{3}{32}$ ", $\frac{1}{16}$ " and $\frac{1}{4}$ ". For 240, 220, 110, 24 and 12 volts. FROM 35/-.



Model F — 40 watts. Fitted with $\frac{1}{8}$ " bit. Interchangeable spare bits $\frac{1}{8}$ ", $\frac{3}{32}$ ", $\frac{1}{16}$ " and $\frac{1}{4}$ ". For 240, 220, 110, 24 and 20 volts. FROM 42/6.

To: Antex, Mayflower House,
Plymouth, Devon.

Quantity Model Bit Size Volts Price NAME.....

Please send me the Antex
colour catalogue.

ADDRESS.....

Please send me the
following irons.

I enclose cheque/P.O. cash value..... Telephone.....

PE.5

MARTIN

IS HIGH FIDELITY

plus

ADD-ON-ABILITY
THRILLING POWER
DEPENDABILITY
GENUINE ECONOMY

How would you like to start with a simple amplifier, say, and add to it until it became a fully stereo twenty watt amplifier with FM tuner and facilities to take the most sensitive low output pickups ever made? With Martin Audiokits it's easy, for with these superbly engineered all-transistor prefabricated units, success is built in from the start and you build to your own preferred plan. IT'S A MONEY SAVING SCHEME, TOO.

Details from:—

● Trade enquiries invited.

MARTIN ELECTRONICS LTD., 155 High Street, Brentford, Middlesex. ISLeworth 1161

To MARTIN ELECTRONICS, 155 High Street Brentford, Middlesex

I have not had your leaflets before. Please send them on
AMPLIFIERS FM TUNER RECORDAKITS
(Tick as required)

NAME.....

ADDRESS.....

PE.....

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1R5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, Set of 4 for 18/6, DAF95, DF95, DK95, DL95, 4 for 26/-.

024	4/6	20F2	13/6	DL35	5/-	EL84	4/9	PEN4A	12/6	UCC84	7/8
1A7GT	7/6	20P3	11/9	DL92	5/9	EL90	5/-	PEN36C15	UCC85	4/9	
1H5GT	7/3	20P4	18/6	DL94	6/-	EM80	5/9	PFL20012/6	UCF80	8/3	
1R5	5/9	25U4GT11/6	DL96	7/-	EM81	6/9	PL36	8/9	UCH82	6/9	
1R5	5/9	30C1	6/9	DY86	5/9	EM84	6/8	PL81	7/3	UCH81	6/9
1R5	4/3	30C15	13/-	DY87	5/9	EM87	7/8	PL82	7/-	UCL82	7/3
1T4	2/8	30C17	16/-	EABC80	6/6	EY51	7/3	PL83	7/3	UCL83	11/8
3S4	4/9	30C18	9/-	EAP42	8/9	EY86	8/9	PL84	8/6	UF41	5/9
3V4	6/-	30F5	16/-	EB01	2/3	EZ40	7/8	PL500	13/-	UF80	7/-
6U4C	4/6	30FL1	13/9	EBC33	7/6	EZ41	7/8	PL504	18/6	UF85	6/9
5Y3GT	5/9	30FL12/14/6	EB04	8/3	EZ80	4/6	PL508	23/6	UF89	6/9	
6AL5	2/3	30L15	14/-	EBF80	6/9	EZ81	4/9	PL802	14/6	UL41	10/6
6X4G	7/6	30FL14	10/6	EBF89	6/8	GZ32	8/9	PM84	7/9	UL44	20/-
6/30L2	12/8	30L1	6/6	EBF89	6/8	KT32	5/-	FX25	10/6	UL84	7/-
6AL5	2/3	30L15	14/-	ECC81	5/9	KT61	8/9	FX31	5/6	UM84	4/6
6AM6	3/6	30L17	15/6	ECC82	4/9	KT61	8/9	FX31	5/6	UY41	7/-
6AQ5	4/9	30P4	12/-	ECC83	7/-	KT66	16/-	FX32	10/-	UY41	7/-
6AT6	4/-	30P12	13/9	ECC84	5/6	ME140015/-	FX33	10/-	UY85	5/9	
6AU6	4/9	30P19	12/-	ECC85	5/9	N78	14/9	FX81	5/3	VP4B	10/-
6BA6	4/8	30PL1	13/9	ECC85	5/9	N78	14/9	FX82	5/3	VP1321	21/-
6BE6	4/9	30PL15	15/6	ECL80	6/9	PC85	6/8	TH21C	9/8	Z77	3/8
6BJ6	7/-	30PL14	15/6	ECP82	6/9	PC88	8/9	U25	15/-	AC107	3/6
6BW6	13/-	35L6GT	8/-	ECH35	6/-	PC96	8/8	FX800	7/8	AC127	2/6
6F13	3/6	35W4	4/6	ECH42	10/6	PC97	8/6	FX801	6/9	AD140	7/8
6F14	9/-	35Z4GT	5/9	ECH81	5/9	PC900	8/3	R19	6/6	AF102	18/-
6F23	14/3	6063	12/6	ECH84	7/6	PC84	6/8	R20	12/6	AF135	3/-
6RA6	2/6	ACVP210/-	ECL80	6/9	PC85	6/8	TH21C	9/8	AF116	3/6	
6K8G	4/3	AZ31	9/-	ECL83	8/3	PC88	8/9	U26	15/-	AF117	3/3
6L18	6/-	B729	12/6	ECL86	8/3	PC180	11/6	U47	13/6	AF125	3/6
6V6GT	6/6	CCH35	10/6	EF39	3/9	PCF80	6/9	U49	18/6	AF126	3/6
6X4	4/3	CL33	18/6	EF41	9/6	PCF82	6/-	U52	4/6	AF127	3/6
6X5GT	5/9	CY81	6/9	EF49	4/9	PCF86	8/8	U78	4/3	OC26	5/9
7B6	10/9	DAC32	7/3	EF80	4/9	PCF86	8/8	U78	4/3	OC26	5/9
7B7	7/-	DAF91	4/3	EF83	6/9	PCF80	18/6	U91	12/6	OC44	2/3
7C6	6/9	DAF96	6/6	EF86	6/3	PCF80	17/-	U90	15/6	OC45	2/3
7Y4	6/6	DF33	7/9	EF89	5/3	PCF802	9/6	U80	19/6	OC71	2/6
10F1	15/-	DF91	2/9	EF91	3/6	PCF805	9/-	UABC80	6/3	OC72	2/6
10F13	15/6	DF96	6/-	EF94	4/9	PCF806	11/6	UAF42	9/6	OC73	2/6
12A7	3/9	DH77	4/-	EF133	6/-	PCF806	10/6	UB41	6/6	OC81	2/3
12AU6	4/9	DH81	10/9	EF184	5/9	PCF82	7/-	UC841	5/6	OC81D	2/3
12AU7	4/9	DK32	7/6	EH90	6/3	PCL83	9/-	UC81	7/-	OC82	2/3
12AX7	4/9	DK91	5/9	EL33	8/9	PCL84	7/8	UBF80	6/-	OC82D	2/3
12K8GT	7/-	DK92	9/3	EL34	9/6	PCL85	9/-	UBF89	6/9	OC82D	2/6
19BG6G17/6	DK96	7/6	EL41	10/6	PCL86	8/6	UC92	5/9	OC170	2/6	

READERS RADIO (P.E.)

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

DIMMASWITCH



This is an attractive dimmer unit which fits in place of the normal wall light switch. The mounting plate is ivory to match modern fittings and the control knob is in bright chrome. An ON/OFF switch is incorporated to control up to 500 watts at mains voltages from 200-250 volts.

These are normally sold at £4 19s. 6d.—our price is £3 5s. We also offer at £2 15s. a complete kit of parts with simple instructions enabling you to build this dimmer yourself.

The circuit uses the latest miniature RCA triac and new diac triggering device to give complete reliability. Radio interference suppression is included.

DEXTER & COMPANY

14 Endsleigh Gardens, Chester CH2 1LT
Chester 26432

NEW 1969 EDITION

RADIO AMATEUR'S HANDBOOK

By A.R.R.L.

45/-

Postage 4/6

SERVICING ELECTRONIC ORGANS, by Carl R. Pittman. 30/- Postage 1/-.

USING SCOPES IN TRANSISTOR CIRCUITS, by Robert G. Middleton. 32/- Postage 1/-.

TRANSISTOR POCKET BOOK, by R. G. Hibberd. 25/- Postage 1/-.

ELECTRONIC MUSICAL INSTRUMENT MANUAL, by Alan Douglas. 55/- Postage 1/-.

TELEVISION ENGINEERS' POCKET BOOK, by J. P. Hawker. 21/- Postage 1/-.

HI FI YEAR BOOK, 1968/9, edited by Miles Henslow. 15/- Postage 1/-.

RAPID SERVICING OF TRANSISTOR EQUIPMENT, by Gordon J. King. 30/- Postage 1/-.

RADIO COMMUNICATION HANDBOOK, by R.S.G.B. 63/- Postage 4/6.

CATALOGUE, 2/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON, W.2

Phone: PADDington 4185

Closed Saturday 1 p.m.

COMPONENTS

BY RETURN OF POST

MULLARD POLYESTER CAPACITORS

(±10%)

400 Volt: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 0.0068µF, 0.01µF, 6d, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 7d, 0.047µF, 8d, 0.068µF, 0.1µF, 9d.

160 Volt: 0.01µF, 0.015µF, 0.022µF, 6d, 0.033µF, 0.047µF, 0.068µF, 7d, 0.1µF, 8d, 0.15µF, 0.22µF, 10d, 0.33µF, 1/2d, 0.47µF, 1/4d, 0.68µF, 2/-, 1.0µF, 2/6d.

250 Volt. P.C. Mounting Miniature; 0.01µF, 0.015µF, 0.022µF, 6d, 0.033µF, 0.047µF, 7d, 0.068µF, 0.1µF, 8d, 0.15µF, 10d, 0.22µF, 1/-, 0.68µF, 0.1µF, 9d.

SUB-MINIATURE ELECTROLYTIC

CAPACITORS (-10%, +50%)

all values in µF

6 Volt 50 100 200 320

10 Volt 6.4 10 16 20

10 Volt 25 64 125 200

15 Volt 10 16 25 40 1/- each

25 Volt 6.4 10 16 25

40 Volt 8 16 32 50

CERAMIC DISC CAPACITORS

150pF, 270pF, (±20%) 330pF,

470pF, 680pF, 1000pF, (-20% +80%)

5d. each

HIGH STAB RESISTORS (CARBON

FILM) Very Low Noise

0.5 watt 5%, 4.7 ohms to 2.2 M ohms 2d each

0.5 watt 10%, 4.7 ohms to 10 M ohms 2d each

SKELETON PRE-SET

POTENTIOMETERS

Miniature, Linear, 100, 250, 500 ohms and

Decades to 1 M ohm 0.3W, ±20% ≤ ±M

±30% > ±M Horizontal or Vertical printed

Circuit Mounting 1/- each.

DIODES—0A85, 0A91, 1/6 each.

SILICON RECTIFIERS

BY236 0.5 amp 800 volt 3/- each 4 for 11/-.

C.W.O. POST AND PACKING ADD 1/-

ON ORDERS UNDER £1.

MAIL ORDERS ONLY TO

YATES ELECTRONICS (FLITWICK)

LTD.

29 LYALL CLOSE, FLITWICK, BEDS.

COLD CATHODE TUBES

By J. B. Dance M.Sc.

Part
TWO

GAS FILLED DIODES

Gas filled cold cathode diodes have many uses in electronic circuits and it will be possible only to give details of some of their more common applications in this article. Miniature neon diodes, operating in the glow discharge region of the characteristic, are used on instrument panels as indicator lights, whilst larger neon diodes can be used for night lighting in sick rooms.

Various types of diode operating in the glow discharge and corona modes have been designed for voltage stabilising purposes. In addition miniature neon diodes are often used as circuit elements, for example, in simple relaxation oscillators, for pulse storage, for routing telephone calls, and for carrying out timing operations. However, these latter are not so widely used as the more versatile trigger tubes in this particular application.

MAIN PROPERTIES

In last month's article, it was stated that as the voltage across a cold cathode tube is increased from zero, hardly any current flows until the striking voltage of the tube is reached. At this point the gas suddenly conducts and the current through the tube is limited by the resistor placed in series with it. The voltage across the conducting tube after striking is known as the maintaining voltage and is lower than the actual striking voltage.

VOLTAGE INDICATORS


Miniature neon diodes containing two small electrodes in a glass envelope are often found in domestic equipment. The type of circuit which may be used is shown in Fig. 2.1. The diodes used have two identical electrodes so that current can flow through them in either direction without undue damage; the diode shown in the circuit is therefore represented by a symmetrical symbol, each electrode combining the anode and cold cathode symbols.

When the switch is closed, the neon diode will strike as soon as the instantaneous voltage of the alternating mains input reaches the striking voltage of the diode used. The tube will be extinguished when the mains voltage falls below the maintaining voltage of the diode towards the end of each half cycle, but will ignite again during the succeeding half cycle. Thus the tube emits 100 flashes of light per second but is seen by the eye to produce a fairly steady glow.

The resistor R1 is the current limiting resistor. If it is too small in value, the maximum current rating of the neon diode will be exceeded and the envelope of the tube may be blackened fairly quickly by sputtered material. If R1 is too large, however, the amount of light emitted by the neon will be very small.

Some neons have the series resistor incorporated in the tube holder. The optimum value of the resistor depends on the type of diode used and the supply voltage. For 240 volt mains a typical value of the series resistor is 470 to 680 kilohms for a diode rated at 0.5mA.

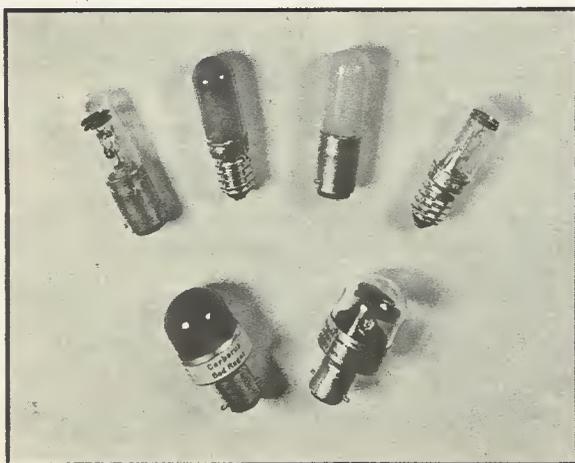Neon indicator lamps have the advantage over tungsten filament lamps that they are almost entirely free from sudden failure and their current consumption



A group of miniature neon diode indicator tubes (Cerberus A.G.)

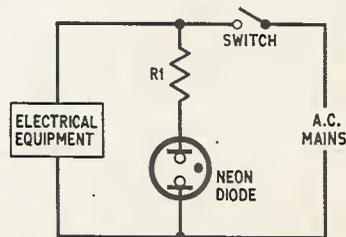


Fig. 2.1. Use of a symmetrical neon diode as a mains indicator

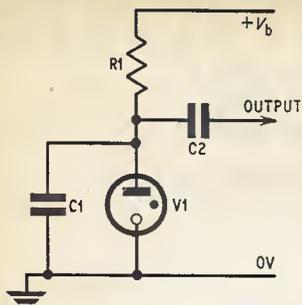


Fig. 2.2a. Simple relaxation oscillator using a neon diode

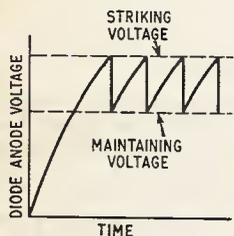


Fig. 2.2b. Graph showing the output voltage from V1 anode



The G42 switching diode designed mainly for use in timer circuits (Cerberus A.G.)

V1	GL6LS	GL10L
R1	8.2M Ω	560k Ω
R2	4.2M Ω	22k Ω
C1	0.33 μ F	0.22 μ F
D1	BXY10	BXY10


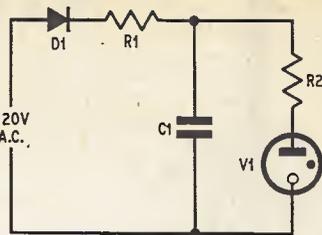


Fig. 2.3. Simple sawtooth waveform generator for a.c. mains

Fig. 2.4. Coupling valves with a neon diode

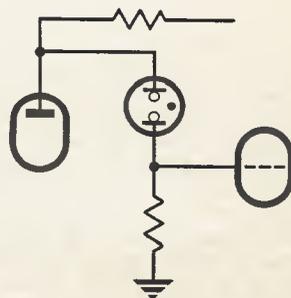

is negligible. After many thousands of hours of use the light emitted by a neon diode falls owing to sputtered material collecting on the envelope of the tube. The diode can then be replaced before total failure occurs.

The use of fluorescent coatings on the inside surface of a neon tube enables neon tubes to be manufactured which emit light of almost any chosen colour.

RELAXATION OSCILLATOR

Neon diodes may be used in a fairly wide variety of pulse circuits, but for many applications they tend to be replaced by the more versatile trigger tubes (to be discussed next month). However, one of the simplest possible oscillator circuits can be constructed using a single neon diode; it is shown in Fig. 2.2.

When a voltage is applied to the circuit, C1 charges up until the voltage across it reaches the striking voltage of the tube. The tube then conducts and remains conducting until the voltage supplied by C1 falls to the maintaining voltage. The tube stops conducting, the capacitor starts to recharge via R1, until the striking voltage is reached again. Fig. 2.3 shows the graph of neon diode anode voltage during charge and discharge of C1. The result is a sawtooth waveform containing even harmonics of the fundamental frequency.

The frequency of oscillation is determined mainly by the time taken for the capacitor C1 to charge through R1, since the discharging time is quite small. Thus the frequency is determined mainly by the values of C1 and R1, but the supply voltage also has some effect. Cold cathode diodes cannot oscillate at very high frequencies and if the product of the values of C1 and R1 is relatively small, the oscillations will cease.

Generally R1 should be greater than about 300 kilohms. If a large value of C1 is required to produce a low output frequency, a resistor should be placed in series with this capacitor to limit the value of the current flowing through the tube. C2 is a d.c. blocking capacitor in series with the output.

The output voltage is approximately equal to the difference between the striking and maintaining voltages. Types of diode known as "difference diodes" are available in which the striking voltage is much greater than the maintaining voltage. Such diodes will provide large output voltages from the circuit in Fig. 2.2. For example, the Cerberus difference diode type G42 has a striking voltage of about 155 volts and a maintaining voltage of about 55 volts. It will therefore provide an output waveform of about 100 volts amplitude.

A practical sawtooth generator circuit (published by the Cerberus Company for their GL range of gas filled diodes) is shown in Fig. 2.3. The value of the capacitor C1 may be altered to provide the desired frequency of oscillation. The electrodes of the GL10L diode are not symmetrical; if this diode is employed, the wire terminal to the inside plate shaped electrode should be used as the cathode connection.

Neon diode relaxation oscillators are sometimes used to provide an audio modulation signal in some of the cheapest types of radio frequency signal generators.

COUPLING

Neon diodes may be used to couple two valve stages as shown in Fig. 2.4. Normally a capacitor would be used, but a neon diode has the advantage that it provides satisfactory coupling for low frequencies.

HIGH CURRENT DIODES

High current switching diodes are rather different from the normal neon diodes; they operate in the arc discharge region and can pass peak currents of up to 10A. The arc voltage across the tube is about 15 volts provided that the current exceeds 50mA. The maximum frequency is limited to about 2kHz. The BD21 tube breaks down at about 200 volts, the BD22 at about 400 volts and the BD23 at about 600 volts.

A typical use of these high current diodes is in electric fence units for keeping farm animals in a field.

GLOW STABILISER TUBES

One of the most commonly used forms of cold cathode tube is the type of voltage stabiliser which operates in the glow discharge region of the characteristic. Such tubes normally contain a central anode wire surrounded by a cylindrical cathode.

The typical circuit in which a glow stabiliser tube is used is shown in Fig. 2.5. This circuit uses the property of the normal glow discharge that the voltage across the tube is almost independent of the current flowing through it.

If the load current passing through R_L increases, the voltage across the load will remain almost constant, but less current will flow through the stabiliser tube. If the h.t. supply voltage is increased, the tube will pass a larger current, but the voltage across it will remain almost constant. A larger voltage drop will therefore appear across R_1 .

Thus the voltage across the load is stabilised against variations in both the load current and the h.t. supply voltage. This simple circuit will, in a typical case, produce a variation of voltage across the load of about 0.1V for an input change of 10V. The supply voltage should not normally be less than about one and a half times the voltage across the load.

The tube data sheets for any stabiliser tube specify a minimum and a maximum operating current. Variations in the load current as the load resistance changes must not exceed the difference between the specified maximum and minimum tube currents. In practice it must be appreciably less than this difference in order to allow for component and voltage tolerances.

The current passing through the series resistor (R_1) is equal to the sum of the tube current (I_{V_1}), and the load current (I_L). Therefore the voltage across R_1 is equal to $(I_L + I_{V_1}) R_1$.

When I_L is small (or zero), I_{V_1} will be a high value which must not exceed the maximum value recommended in the tube data sheets, even if the supply

voltage is at its maximum possible value, and R_1 is at the minimum value to be expected from the tolerance of the resistor used.

Similarly when I_L is at a maximum, the value of I_{V_1} must not be less than the recommended tube current even if the supply is low (for example, due to a low mains voltage). Simultaneously R_1 should be at the maximum value to be expected from the tolerance of this resistor.

When the h.t. voltage is first applied, the voltage across the tube before it conducts will be

$$V_s \left[\frac{R_L}{(R_1 + R_L)} \right]$$

It is essential that this voltage should exceed the striking voltage of the tube or ignition may not occur.

However, some tubes have an additional priming electrode which is connected through a resistor directly to the source of high tension. This ensures that such a tube will strike readily, but only a little current flows to the primary electrode.



REFERENCE TUBES

Voltage reference tubes are a particular type of stabiliser tube which are intended to provide the greatest possible voltage stability at a specified current. They should not be used in circuits in which the tube current is likely to change by more than a small amount, since ordinary stabiliser tubes give a better performance in such circumstances.

Reference tubes should therefore be used only when the load current is almost constant. They are used in the same type of circuit as ordinary stabiliser tubes (see Fig. 2.5), but are also used with thermionic valves in more complicated stabiliser circuits.

Precision spark gap tubes for protection circuits and other applications (Victoreen Instrument Co.)

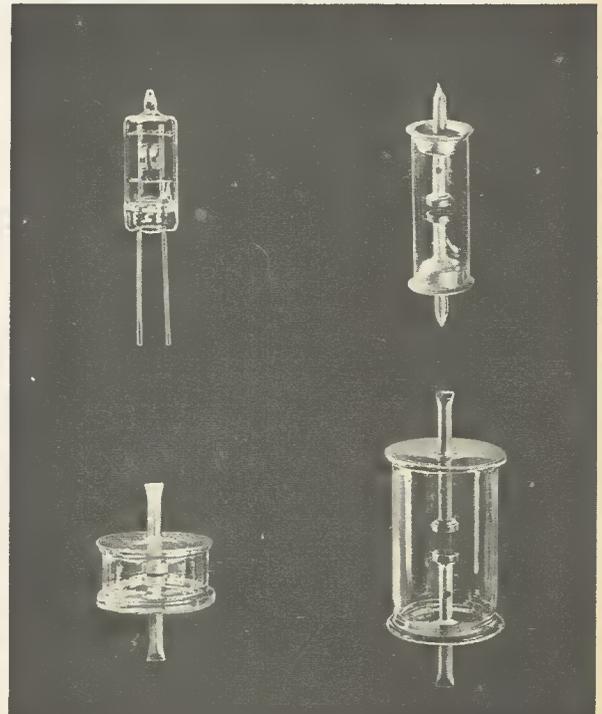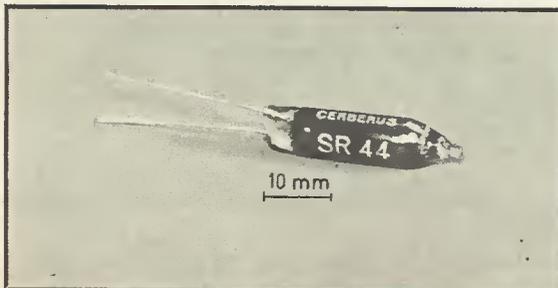The SR44 subminiature stabiliser tube providing a stabilised output of 84 volts (Cerberus A.G.)



CORONA STABILISERS

Corona stabiliser tubes may be employed to stabilise high voltages at small currents. Tubes which will provide outputs in the range 340 volts to 30,000 volts are available, but the maximum permissible tube current is usually of the order of one milliamp—sometimes even less.

Corona stabiliser tubes contain a thin anode wire in the centre of a cylindrical cathode, the gas filling being hydrogen. When they are operated from a high voltage supply in series with a suitable resistor (normally some megohms), a corona discharge takes place in the tube. The circuit in which the tubes are used is like that in Fig. 2.5.

Corona discharges occur from any sharply curved or pointed surface which is at a high potential relative to its surroundings. Corona effects can cause trouble in the e.h.t. supplies of television receivers and lead to some power losses in high voltage power lines. The discharge can often be heard as well as being seen as a faint glow around the curved surface concerned.

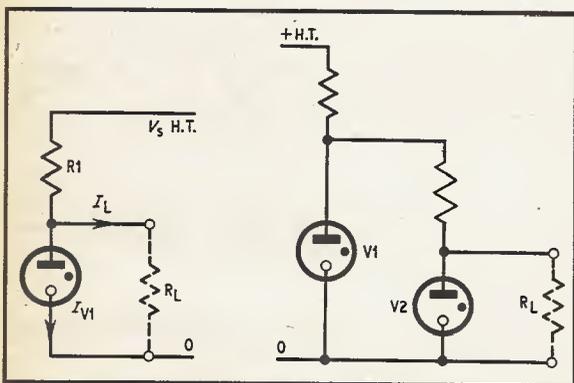


Fig. 2.5. Basic voltage stabiliser circuit


The operating voltage of a corona stabiliser is determined by the electrode dimensions and by the gas pressure. Tubes with maintaining voltages up to about 7,000V can be produced in envelopes similar to those used in thermionic valve manufacture. As it is difficult to make a glass seal when the gas is at a pressure above atmospheric, corona tubes for the highest voltages are normally encased partly in metal.

One of the most notable differences between corona and glow stabiliser tubes is that the striking and maintaining voltages of corona tubes are almost equal. No special arrangements are therefore required to ensure that a corona tube will strike promptly.

CASCADED STABILISER TUBES

Glow stabiliser tubes can be used in cascade in the type of circuit shown in Fig. 2.6. The first tube, V1, reduces any voltage fluctuations in the supply considerably and the second tube, V2, reduces them still further. However, this circuit will not provide better stability against variations in the load current than the simpler circuit of Fig. 2.5. A reference tube is often used for V2, the anode resistor of which must normally be a close tolerance component.

A group of corona stabiliser tubes. The glass tubes on the left are available with maintaining voltages of 400 to a few kilovolts, whilst the metal M42 tube covers the range 6 to 12kV and the M105 12 to 20kV (Victoreen Instrument Co.)

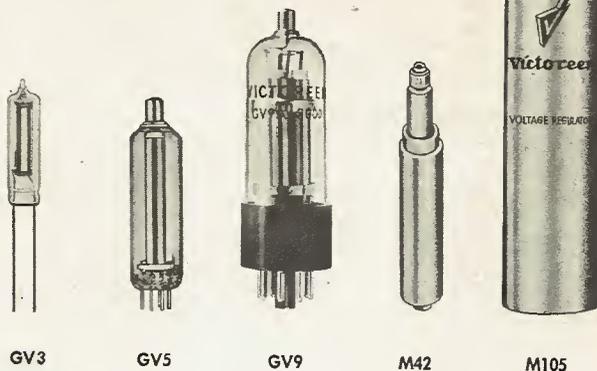

GV3

GV5

GV9

M42

M105

Corona tubes can also be used in cascade, although such use is not very common.

HIGHER STABILISED VOLTAGES

The simple voltage stabiliser circuit can provide only an output voltage equal to the maintaining voltage of the tube employed. Although a potential divider circuit may be connected across the output from the circuit in order to obtain lower stabilised voltages, the stability against variations of the load current will be reduced.

If a higher stabilised output voltage is required than can be provided by a single tube, two or more tubes connected in series may replace the tube shown in Fig. 2.5. However, if the tubes are not all of the same type, care must be taken to ensure that there is an adequate overlap of their current ratings. The output voltage is, of course, the sum of the maintaining voltages of the individual tubes.

An alternative method of obtaining a higher output voltage involves the use of a multi-gap tube. Such tubes contain several discharge gaps in one envelope, so intermediate output voltages are also obtainable from circuits employing such tubes. For example, the G.E.C. "Stabilovolt" tubes provide stabilised output voltages of 70, 140, 210 and 280 volts. Two of these tubes may be connected in series to provide stabilised outputs of up to 560 volts at 70 volt intervals.

Corona tubes may be connected in series, but a capacitor of about 1,000pF should be connected in parallel with each tube to avoid the possibility of spurious oscillation.

Neither glow stabiliser nor corona tubes should be operated with tubes connected directly in parallel, since one of the tubes will probably strike first. It is improbable that any other tube will then conduct, since once one tube has ignited, the voltage across the others will be less than the striking voltage.

Both glow and corona stabiliser tubes can be used with thermionic valves in circuits which provide highly stable outputs at voltages and currents which may be quite high.

Next month: Circuits using cold cathode trigger tubes

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

MODEL CONTROL

For model control enthusiasts a new transmitter and receiver has been released by Radio Control Products, 38 Franche Road, Kidderminster, Worcestershire.

The transmitter is crystal controlled on any of the specified radio control frequencies and gives an r.f. power output of 0.5W. It has a microswitch tone button, a full length telescopic aerial, and is housed in a blue vinyl covered case.

The receiver measures 2½in × 1½in × ¾in and is a superhet operating with an i.f. of 455kHz. A special noise suppression circuit is incorporated in the audio stages of the receiver.

Both relay and relayless versions are available; the relayless receiver has an output transistor capable of switching up to 0.5A. The contacts on the relay versions are fitted with spark quench suppressors. Both units operate from a 4.5V supply and cost £18 18s as a matched pair of units.




Miniature model control transmitter and receiver from Radio Control Products

TELEFILM CONSOLE

Designed as a self-contained unit for showing continuous loop film on television sets, the Beulah Telefilm Console should be of special interest to hotels, motels, advertising agencies, and possibly training establishments. Being completely automatic, it will operate for long periods without any attention. A time switch is built-in to programme its period of operation. The standard model has a video output and the signal can be fed via a modulator unit into a distribution amplifier.

A special optical unit designed by Beulah Electronics couples a television camera to the film projector. The control panel has a 9in monitor.

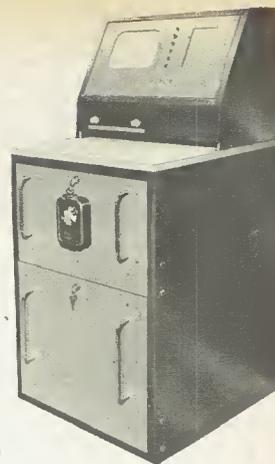The units are usually installed by franchise operators who cover a number of hotels and motels in an area carrying out installation and maintenance. Full details can be obtained from Beulah Electronics Ltd., 126 Hamilton Road, West Norwood, London, S.E.27.



Telefilm Console from Beulah



Eagle HA.10 Stereo Headphone Amplifier

HEADPHONE AMPLIFIER

The Eagle HA.10 is one of the latest pieces of audio equipment to be added to their range of products. The HA.10 is a stereo headphone amplifier that can be used with any record deck and pick-up cartridge and it is claimed to give high fidelity reproduction at headphone listening level.

The output of the headphone amplifier is 50mW per channel and the inputs are: magnetic 5mV (equalised); ceramic 100mV (flat); and tuner 100mV (flat). It is powered by a 9V battery.

The price of the HA.10 stereo headphone amplifier is £11 0s 6d.

AEROSOL CLEANER

Known as Ultracene, a new aerosol industrial cleaner is announced by Automation Facilities Ltd., and available from some retailers. Its uses are numerous and it acts very quickly, the spray removing dirt, grease, and oil. Being in aerosol form it can penetrate some of those otherwise inaccessible areas and enables electrical equipment to be cleaned *in situ*, without dismantling.

Each Ultracene aerosol contains 16 ounces of solvent and is claimed to be a suitable alternative to carbon tetrachloride.

LITERATURE

The fifth edition of the Home Radio Catalogue is now available from Home Radio (Components) Ltd., 234 London Road, Mitcham, Surrey.

The price of the catalogue has been increased for the first time since 1965 to 8s 6d, but an extra 1s coupon has been added and there are now six 1s-in-the-£1 discount coupons enabling some of the cost of the catalogue to be recovered on subsequent orders. These coupons are supplied separately and readers should make sure that they ask for coupons when purchasing this excellent catalogue.

Many sections have been completely revised and brought up to date and numerous new items added. Also supplied with the catalogue is a new component prices supplement.

The 1969 edition of the Mullard Data Book, just published, follows the same successful formula introduced last year and embraces the complete Mullard ranges of valves, television picture tubes, semiconductors and components for entertainment applications.

For easy reference different coloured paper is used for each of the main product sections.

Equivalents and earlier types are listed in the valve section, replacement details are given in the television picture tube section and information about comparables is shown in the semiconductor section. Symbols and abbreviations are explained in a separate section.

Continuing the practice started last year, this 138-page book is available, through radio and television retailers, to electronics enthusiasts outside the trade. This arrangement is being continued and the recommended retail price remains unchanged at 3s 6d a copy. If there is any difficulty in obtaining copies readers should contact Mullard Ltd., at Mullard House, Torrington Place, London, W.C.1.

PE ORGAN PART 2

By Alan Douglas, Sen. Mem. I.E.E.E.

WE left the last instalment with the two keyboards in position. Now they must be removed from the console, as we have to attach the key contact system. In any organ of this kind which uses frequency division, the generators all run continuously. Not only this, but some of the actual notes or pitches may be used simultaneously for the upper manual, lower manual and pedals. So two things have to be considered; how to key the signal and how to prevent this multiple usage from reducing the signal strength.

If one cuts into any waveform abruptly, there will be a transient signal of an unpleasant nature. It will be a click or a thump and it may occur again on releasing the key. Clearly it is an advantage if we can eliminate this irritating effect and this is possible if we use resistance keying.

The really unpleasant transient is of very short duration and often of very high frequency. So if we cause a graphited surface to contact either an incorrodible metal or another graphite surface, we will have a momentarily high resistance, rapidly decreasing with increased pressure to a lower value. This attenuates the transient and in favourable conditions removes it altogether.

MANUAL CONTACT ASSEMBLIES

Unfortunately, such graphited switches require precision in assembly and special treatment if they are to have a long life; so it is not too easy to make them. We also know that we need signals of different pitches from any one playing key, so that a great deal of cross-connecting is called for. For these reasons, we have specified the manual contact assemblies made by Harmonics Ltd.

We require a four bank unit for the upper keyboard, wired for 16, 8, 4 and 2ft; and a two bank unit for the lower keyboard, wired for 8 and 4ft. The distribution of these pitches from common oscillators and dividers is effected by printed wiring as in Fig. 2.1, which shows part of the upper unit. This saves the constructor some hundreds of soldered joints and is very neat, a useful feature as there is not too much room between the keyboards.

In addition to the printed wiring, these contact assemblies have integral anti-robbing resistors. As stated, it is necessary to ensure that use of the same signal more than once does not reduce the overall volume. By inserting resistors in series with the divider outputs, we can control this. Indeed, should two notes coincide on two manuals, or through the use of two pitches, then the resistor value will be halved and the notes will become louder as indeed they should. Therefore, when ordering these switch units, we ask for 100 kilohm resistors to be fitted to each switch contact wire.

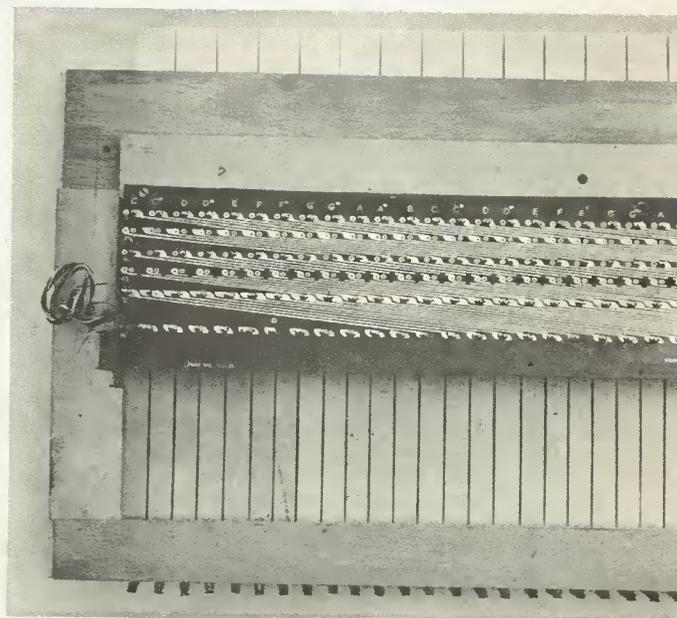


Fig. 2.1. View of the underside of the upper manual contact assembly showing the pitch connections to the printed circuit board. Note the hardwood strip which fixes the board to the keyframe

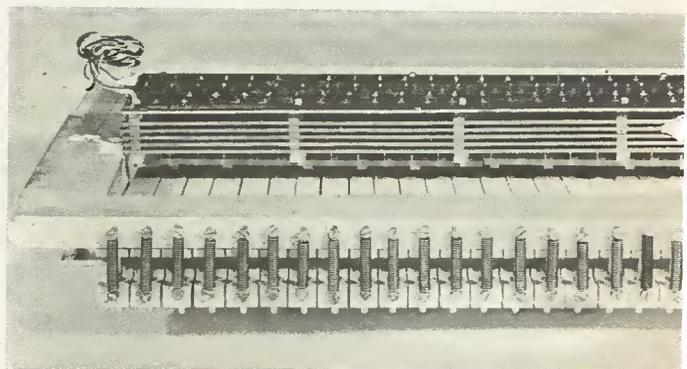


Fig. 2.2. Upper manual contact assembly shown in perspective with one hardwood strip removed

SWITCH UNITS AND OSCILLATORS

This series is expected to extend to 12 parts

Total cost of material for the organ is likely to be around £250

ATTACHING TO THE KEYFRAMES

As supplied, the switches have the printed coupler wiring on the bottom, and the switch finger wiring on a small side panel. This panel faces the front of the keys, when the keyboard is turned upside down.

The plungers contact the respective keys, and the units are fastened down by seven screws each side to strips of hardwood across the keyframes. These strips must be of such a thickness that the flat end of the plungers projects from the printed wiring side by about $\frac{1}{16}$ in with the keys at rest. Do this very carefully, or erratic keying could result.

Fig. 2.2 shows one end of the upper keyboard assembly with one wood strip removed and Fig. 2.3 shows the whole affixed to the keyboards. Note also the fixing of the duralumin thumper bar in this picture.


If the hardwood strips are correct, there will be no clearance between the underside of the keys and the ends of the plastic dollies. Of course, the thumper bars must be in position to check this.

We can now put the two keyboards back to check the touch and clearances, but the next step will be to solder the generator output wires to the printed wiring so they will have to come off again when the dividers are completed.

ALTERNATIVE KEYING

It is possible, of course, to use direct metal-to-metal key contacts such as gold clad bronze wire, and this is much cheaper. However there is almost a certainty of transients at high pitches here.

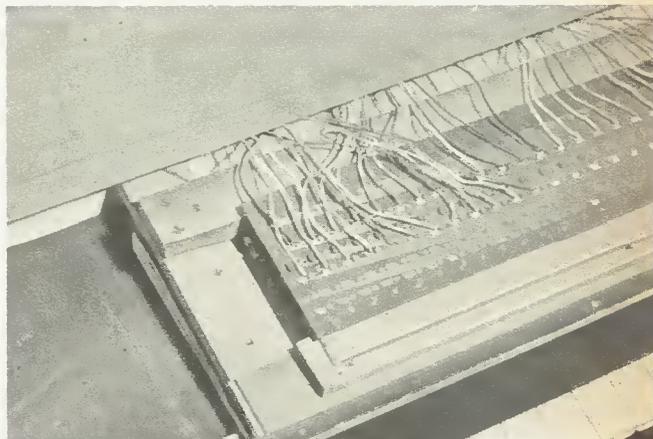Then again, diode or transistor keying could be used; or the electrolytic system devised by Arthur le Boutillier of the Electronic Organ Constructors Society. We have



Underside of the lower manual showing printed board wired and mounted to keyframe via hardwood strips

to try to suggest a system which is known to work well, be little trouble to the builders, and to remain reliable.

Later on, we will discuss possible alternative methods of keying. Suffice it to say that graphite keying has been proved entirely satisfactory by the Baldwin company for more than 20 years.

P.S.U. FOR OSCILLATORS AND DIVIDERS

Now we must turn our attention to the oscillators and frequency dividers, and strange though it may seem, we start by making up the power supply unit (P.S.U.1) for these.

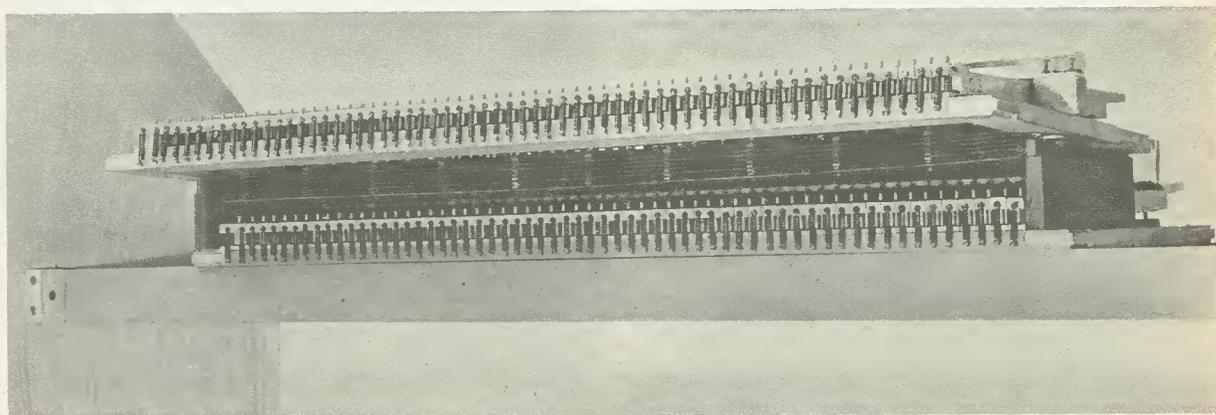


Fig. 2.3. Upper and lower manuals complete with contact units in position on keyboard support rails

P.S.U.I FOR GENERATOR AND DIVIDER UNITS

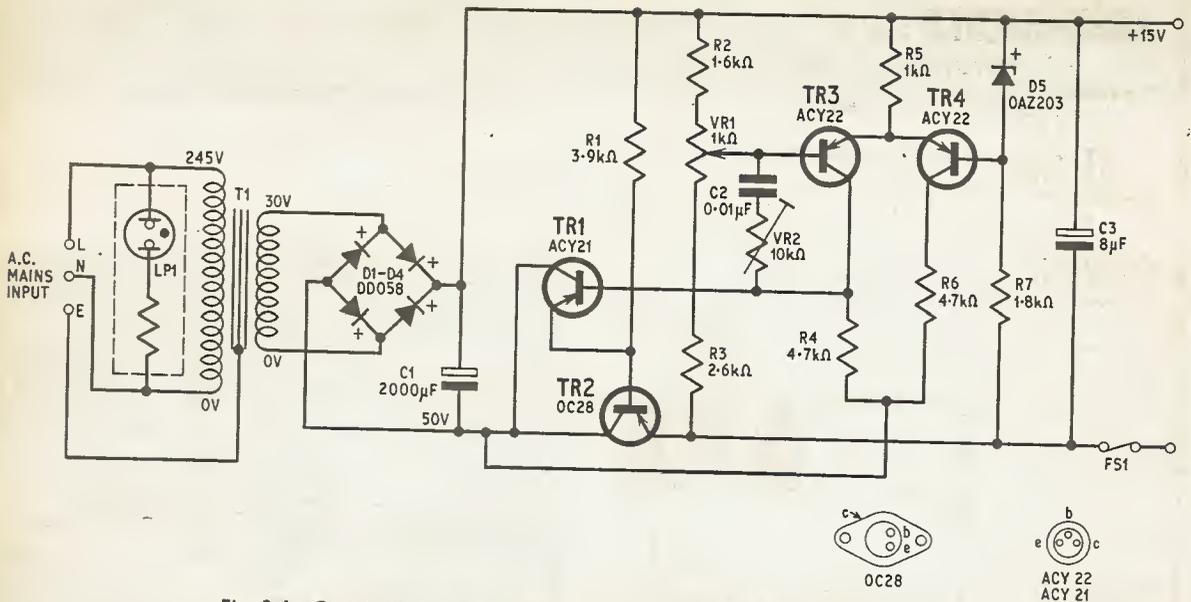


Fig. 2.4. Circuit diagram of power supply unit for generators and dividers

Although the inherent stability of the oscillators is very good, testing such circuits with dry batteries is to be deprecated for two reasons; firstly, the high and variable impedance of a battery. And secondly, the question of earthing and hum pickup which could be misleading with batteries.

The d.c. load on this power unit is constant, about 320 milliamps at 15 volts which together give the low-power consumption figure of under 5 watts. Nevertheless, an inexpensive stabiliser is desirable and this also reduces ripple giving a very low output impedance which in its turn makes decoupling easier.

OPERATION


To achieve the current output and low output impedance, TR1 and TR2 are strapped as a modified Darlington pair as shown in Fig. 2.4.

The comparator transistors TR3 and TR4 are arranged in a long-tailed pair configuration where the voltage across R5 is equal to the difference between the reference voltage of D5 and the base to emitter voltage of TR4.

A change in the emitter to base voltage of TR4 produces an equal and opposite change in the voltage across R5. Since TR3 and TR4 are the same type, the effect of temperature change on the former is nullified by a similar effect on TR4 and the change in voltage across R5.

The value of the output voltage is adjusted by means of potentiometer VR1 which alters the fraction of the output that is compared with the reference voltage. After amplification, this is fed back to the Darlington pair.

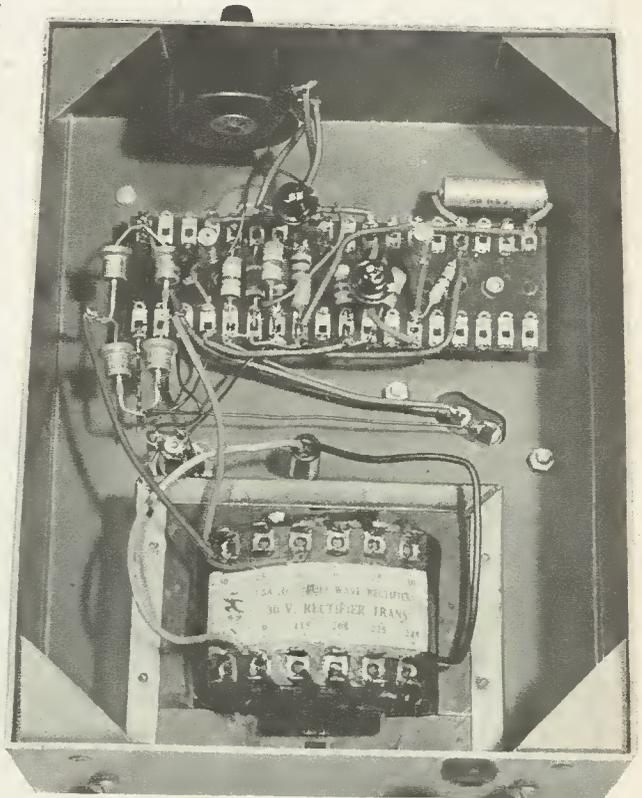C2 and VR2 are included to eliminate any tendency for the circuit to oscillate. If such oscillations are apparent the resistance of VR2 should be increased from zero until such disturbances disappear.



Chassis underside of power supply unit, see Fig. 2.5 for details

POWER SUPPLY WIRING

COMPONENTS . . .

POWER SUPPLY UNIT I

Resistors

R1 3.9k Ω	R5 1k Ω
R2 1.6k Ω	R6 4.7k Ω
R3 2.6k Ω	R7 1.8k Ω
R4 4.7k Ω	

Capacitors

C1 2,000 μ F elect. 50V	
C2 0.01 μ F polyester	C3 8 μ F elect. 25V

Potentiometers

VR1 1k Ω wirewound preset
VR2 10k Ω carbon slider preset

Transistors

TR1 ACY21	TR3 ACY22
TR2 OC28	TR4 ACY22

Diodes

D1-D4 DDO58 (Lucas) 4 off
D5 OAZ203 (Mullard) 6.2V Zener

Transformer

T1 Rectifier transformer. Primary: 200-240V tapped; secondary 30V (Radiospares)

Miscellaneous

FS1 500mA fuse
 Fuse holder
 LP1 Neon indicator
 Miniature tag board 4½in long
 Heat sink 4in × 4.875in
 Terminal strip
 Chassis 9in × 6in × 2½in


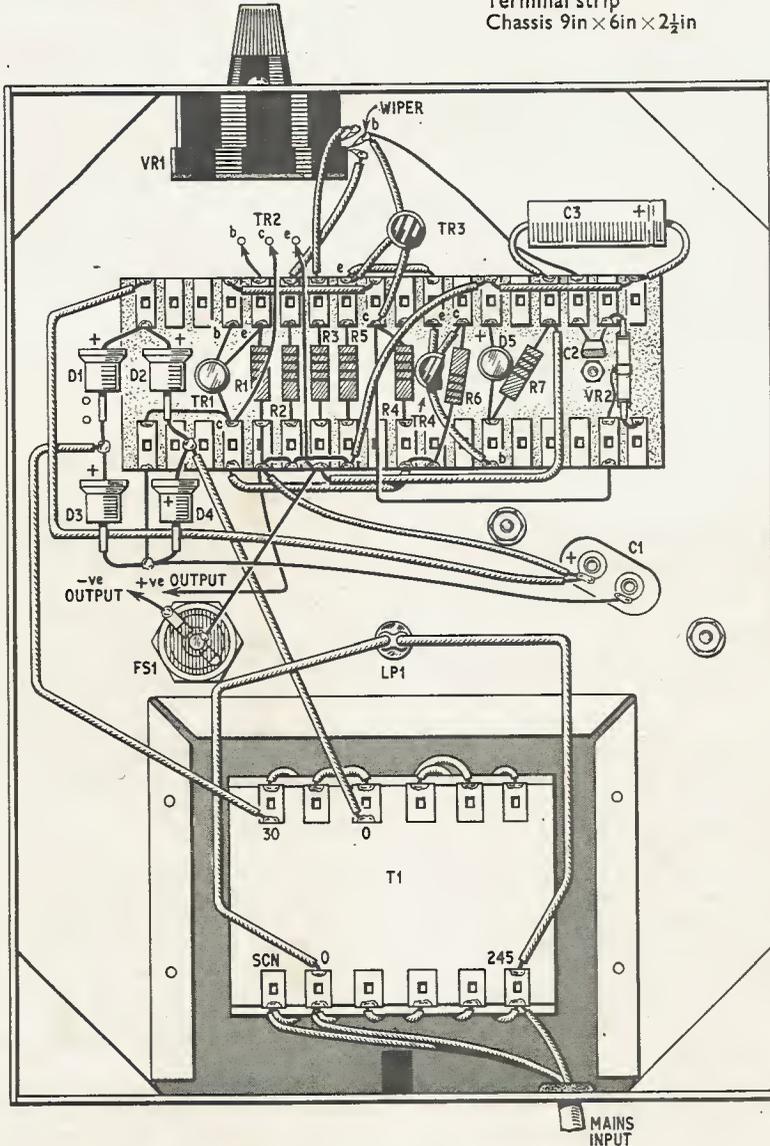


Fig. 2.5. Wiring layout for P.S.U.I. The d.c. output wires are taken to a terminal strip mounted on chassis top, see Fig. 2.6

Fig. 2.6. Topside of P.S.U.I. Here TR2 is connected directly to the heat sink which has meant mounting this on insulating perspex posts. Note chassis cutout for transformer windings

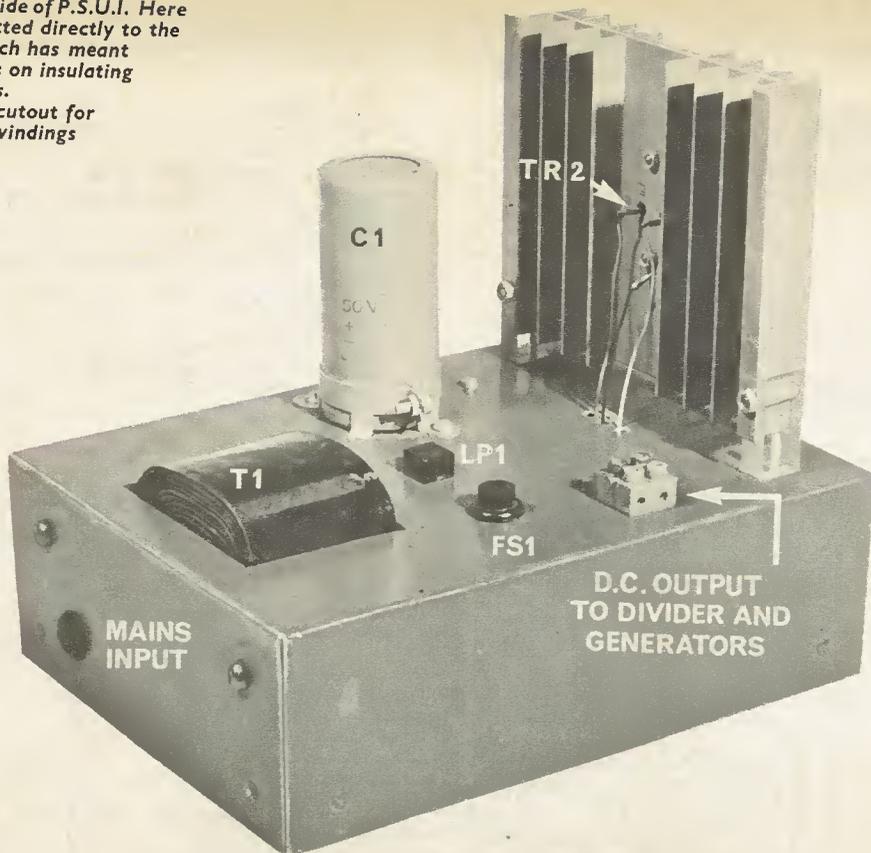

CONSTRUCTION

Nearly all of the small circuit components are assembled on a $\frac{1}{4}$ in miniature tag board as shown in Fig. 2.5. When this is done the chassis should be cut for the transformer and drilled for all chassis mounting screws.

To stand off the tag board, this should be mounted on four $\frac{1}{4}$ in spacers with 1in 6B.A. nuts and bolts.

Wiring of all chassis components should now proceed as shown in Fig. 2.5.

The extruded heat sink for TR2 can be seen in Fig. 2.6 and this is insulated from the chassis unless mica washers are fitted under the transistor; be very careful about this question of insulation or the OC28 will be destroyed.

The output voltage can now be set by adjusting VR1 and to do this we must connect a dummy load across the line. Assuming a current drain of 300mA at 15V, we can use a 3 watt resistor of 50 ohms to simulate the collective oscillator and divider load.

With a meter across the load VR1 can now be adjusted for 15V.

HARTLEY OSCILLATORS

Now that we have the power available, it is time to look at the oscillator units. As we know, there are 12 oscillators for the top 12 notes and all the other octaves downwards are obtained by 2:1 bistable frequency dividers. Thus, there are but 12 notes to adjust to tune the whole organ, a decided advantage in an organ of this kind, although it cannot give the greatest realism.

From the many possible oscillator designs, we chose the circuit invented by J. V. L. Hartley nearly fifty years ago. It is simple, stable, economical and can be adjusted to give different kinds of waveforms. Of course, the original circuit used valves, and some adaptation is required for transistors.

The average amateur finds his greatest difficulty in obtaining stable capacitors. The Hartley oscillator has but one in the critical tuning position, though of course this will require selection and padding to give the correct frequencies. At the present time imported polyester and polystyrene low voltage capacitors are readily available at economical prices, therefore the use of this type of dielectric is recommended throughout the generator system.

SILICON TRANSISTORS

At the outset it was explained that silicon was to be used in preference to germanium transistors. From every point of view the encapsulated planar device scores. For small signals, the leakage current is infinitesimal; for large signals, the danger of thermal runaway is virtually non-existent. Apart from this, the price is in many cases lower than germanium, and this will reduce still more.

The relatively high temperatures which silicon can withstand during processing permit the fabrication of all kinds of complicated integrated circuits. Although we do not use these, one day they will be commonplace for organs. So we are able to use one type only for all the oscillators, dividers, pre and post amplifiers and emitter followers.


MAJOR COMPONENTS

In a project of this magnitude it is to the constructor's advantage to bulk purchase those components which will appear in fairly large numbers. It is for this reason we include the following list of resistors and capacitors required

in quantities of 12 or more. The semiconductor and inductor complement is also included


Individual component lists will, of course, be published with each circuit diagram as they occur

Resistors	Quantity	Capacitors	Quantity	Transistors	Quantity
100Ω	18	1,000pF polystyrene	96	ZTX300 (Ferranti)	216
330Ω	14	2,200pF polystyrene	12	ACY22 (Mullard)	2
470Ω	12	4,700pF polystyrene	253	ACY21 (Mullard)	1
1kΩ	13	0.01μF polyester	33	OC28 (Mullard)	1
2.2kΩ	282	0.1μF polyester	72	ZT1701 (Ferranti)	4
3.3kΩ	13	0.22μF polyester	12	ZT1613 (Ferranti)	6
18kΩ	170	100μF elect. 25V	12	ZT44 (Ferranti)	1
33kΩ	30	Diodes		ZT1700 (Ferranti)	1
68kΩ	13	ZS170 (Ferranti)	7	ZT3055 (Ferranti)	2
100kΩ	92	ZR12 (Ferranti)	4	ZTX302 (Ferranti)	2
All 10% ½ watt carbon		KR54 (Ferranti)	1		
		KR56 (Ferranti)	1		
Inductors		DDO58 (Lucas)	4		
Mullard Vinkor type LA2300	12	OAZ203 (Mullard) 6.2V Zener	1		
Mullard Ferroxcubes type LA2	5				

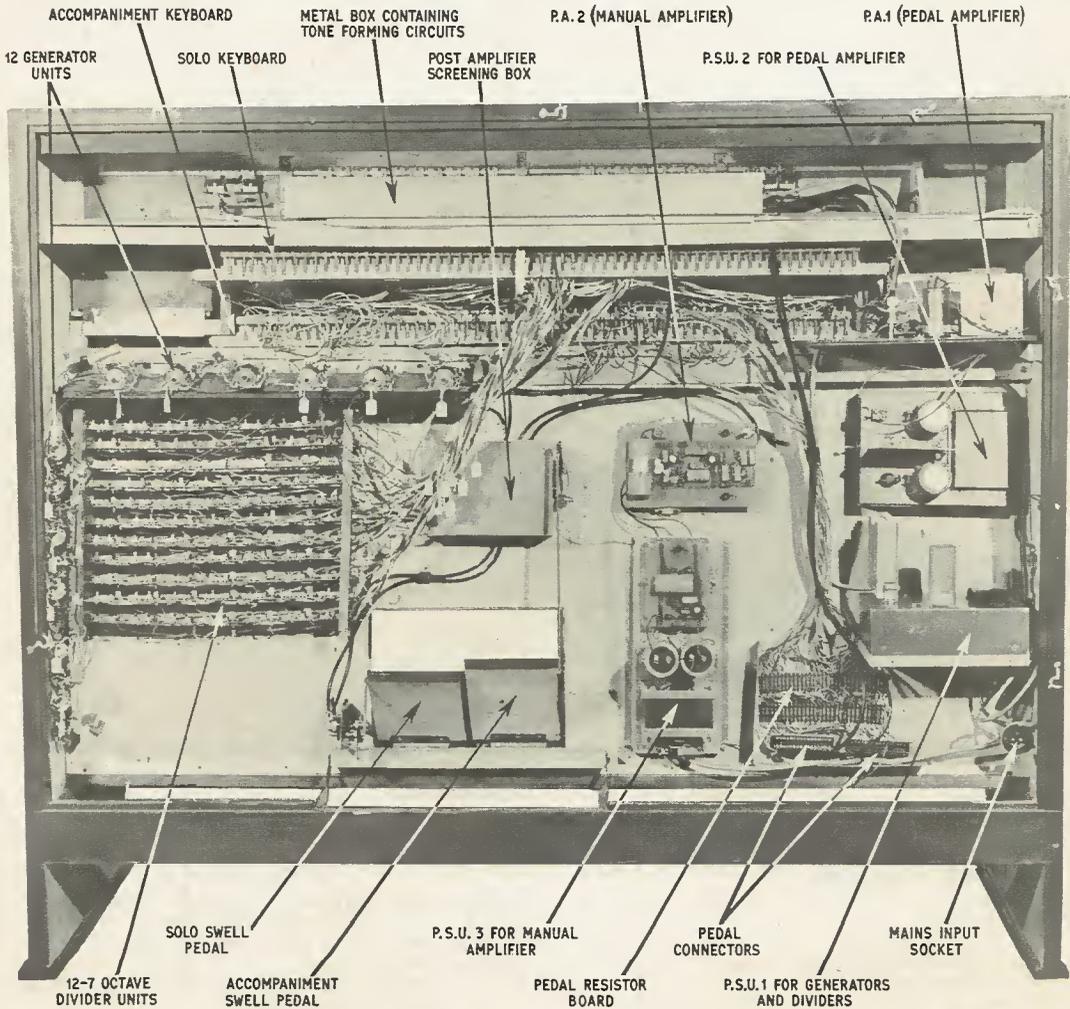


Rear view of organ console showing general layout of all sub-assemblies

OSCILLATOR UNIT

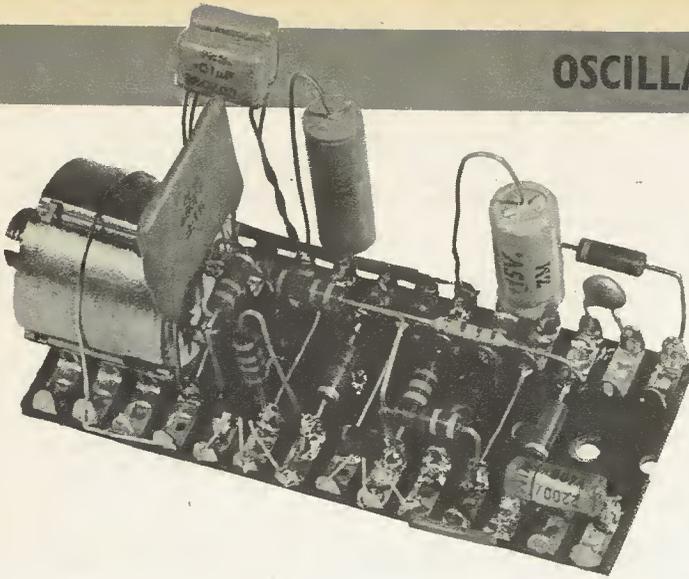

Perspective view of one oscillator unit (tagboard version)

Fig. 2.7. Circuit diagram of an oscillator unit. Here the output F is a 2ft pitch frequency and SYNC the input to the first stage of the relevant divider unit. Values for the tuning capacitor C1 vary for each of the 12 oscillators and these will be given in a later article

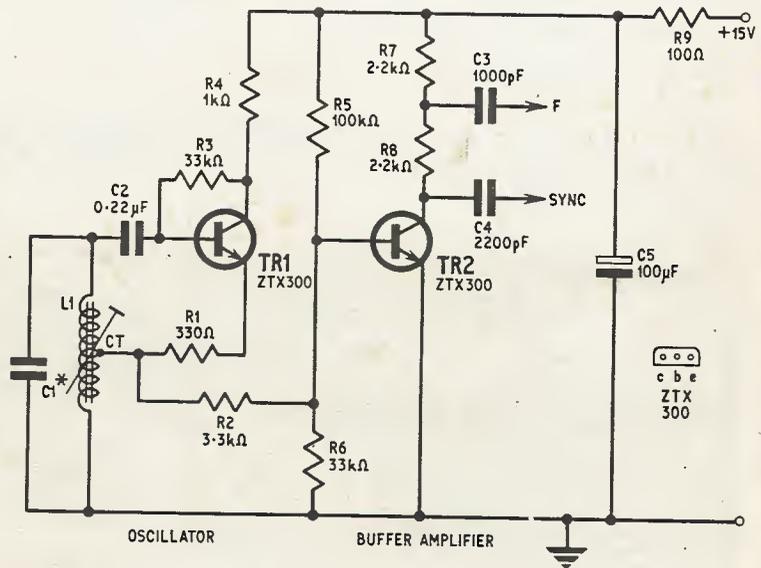

COMPONENTS . . .

OSCILLATOR UNIT (12 required)

Resistors

- R1 330Ω
- R2 3.3kΩ
- R3 33kΩ
- R4 1kΩ
- R5 100kΩ
- R6 33kΩ
- R7 2.2kΩ
- R8 2.2kΩ
- R9 100Ω

all 10% ½ watt carbon

Capacitors

- C1* See text
- C2 0.22μF polyester
- C3 1,000pF polystyrene
- C4 2,200pF polystyrene
- C5 100μF elect. 25V

Transistors

- TR1 ZTX300 (Ferranti)
- TR2 ZTX300 (Ferranti)

Inductors

- L1 100 plus 100 turns of 32 s.w.g. enamelled copper wire wound in Mullard Vinkor type LA2300

Miscellaneous

- Miniature tag board 3½ in long
- Bakelite backing plates to suit

SUPPLIERS

Manual contact assemblies: Harmonics (Bromley) Ltd.
 For 18, 8, 4, and 2ft pitches (loff): Clarion Works
 For 8 and 4ft pitches (loff): Napier Road, Bromley,
 Kent
 When ordering ask for 100 kilohm resistors to be fitted
 to each switch contact wire

OSCILLATOR WIRING

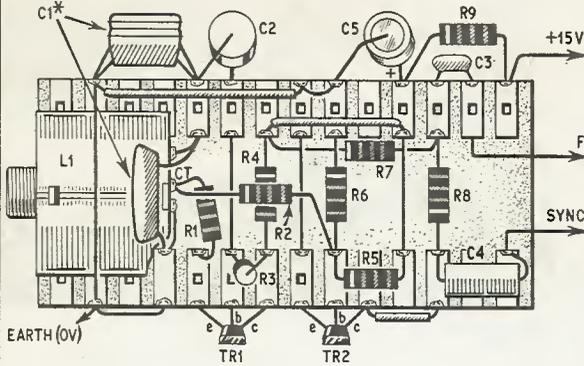


Fig. 2.8. Tagboard mounting and wiring of oscillator components

PRINTED CIRCUIT ALTERNATIVE

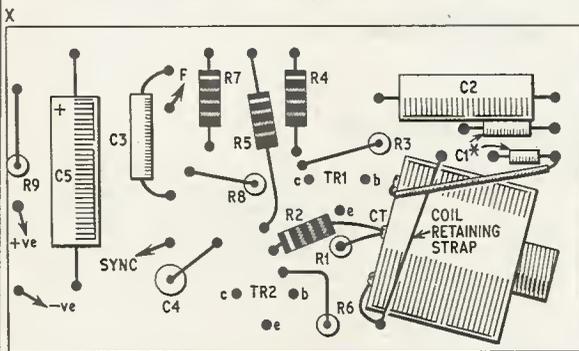


Fig. 2.9. Printed circuit board layout and wiring for oscillator assembly

INDUCTORS

The oscillator circuit is shown in Fig. 2.7. The inductance coil L1 is a Mullard Vinkor type LA 2300, but although this ensures the greatest stability and the minimum of crosstalk, these coils are expensive.

As the frequencies of the oscillators all lie between 8kHz and 4kHz, it is possible to use less costly iron dust cores such as the Denco Neosid. So far as is possible, the Vinkors are to be strongly recommended.

BUFFER STAGE

The Hartley circuit oscillates vigorously, and since we want to use these frequencies for 2ft pitch, a buffer stage is added to isolate the actual oscillator from the keying load. This also shapes the sine wave so that the first divider is properly triggered.

From an audible point of view this high pitched note could have almost any waveshape since the ear would not be able to resolve harmonics above the concordant second which is the octave of the fundamental. But higher harmonics are present, so some slight degree of filtering is applied through later tone forming circuits.

CONSTRUCTION

The oscillators are constructed on miniature tag boards, one of which is shown in Fig. 2.8. This is convenient since the oscillators are spaced somewhat away from the dividers they feed, and in addition the actual dimensions of the components may vary according to the source of supply.

The 12 oscillators used are identical in their component complement with the exception of the tuning capacitors shown as C1 in the circuit diagram of Fig. 2.7. This uniformity means that the component layout on all 12 tag boards follows that of Fig. 2.8.

100 plus 100 turns of 32 s.w.g. enamelled copper wire are wound on to the pot core bobbin. When winding on the second lot of 100 turns it is essential to maintain the same winding sense.

With the wire ends cleaned these are then taken and soldered to the tags. The bobbin is then placed in the core assembly and the clamps tightened down.

The tuning capacitor and associated padders shown as C1 will be given values in a later article.

It is, of course, possible to use a printed circuit board construction for the oscillators and this with component layout is shown in Fig. 2.9.

FUNCTIONAL CHECKS

As each oscillator unit is completed a functional check should be made. To make this test the power supply unit, P.S.U.1, should be set to +15V.

First solder a 30,000pF capacitor across the coil L1 at either one of the C1 connections shown in Fig. 2.8. Now connect the +15V supply.

If an oscilloscope is available, examination of the outputs at either C3 or C4 should provide a square wave. If not, check the output at the collector of TR1. Here a clipped sinusoidal wave should be evident.

These checks will resolve a defective stage.

Providing your hearing is good, these procedures can be undertaken using a pair of high impedance phones.

When you are satisfied that all 12 oscillators are working both these and the power unit should be placed to one side.

Next month we will start construction of the frequency divider units with wiring details of their associated assemblies.

To be continued

Thin Film Circuits

As the use of thin film circuits becomes more widespread in the electronics industry, methods of measuring and improving the properties of thin films are being carefully studied at the National Physical Laboratory (N.P.L.) at Teddington.

Good adhesion of thin films to their substrates and to one another is essential for microelectronic and optical applications. Existing methods of measuring adhesion have always been inadequate; N.P.L. have studied these methods and introduced new ones.

Using the new measuring methods, it has been found that superior adhesion is achieved more efficiently by "glow-discharge" cleaning of the substrate prior to deposition of the thin film. The process of "glow-discharge" cleaning can be introduced into a production line relatively simply.

In order to isolate the factors which most affect adhesion, it is necessary to be able to deposit films in the presence of controlled amounts of contaminants. This is carried out at N.P.L. in the ultra-high vacuum system illustrated right.



Crown copyright: National Physical Laboratory.



Crown copyright: National Physical Laboratory.

N.P.L. Ultrasonic Tank

In conventional ultrasonic flaw detection apparatus a short ultrasonic pulse is transmitted through the solid material. When flaws or discontinuities are present in the material being checked they are shown up at the receiver as secondary ultrasonic sources. In the N.P.L. apparatus shown right, a pulsed beam of ultrasonic sound is propagated through a tank of liquid which can be maintained at any desired temperature. When a sample of material is interposed at an angle in the beam, refraction occurs at the interface and it is possible to transmit both longitudinal and shear waves. A change from one type of wave to the other is made by reorientating the sample. Measurement of the wave velocities in several directions makes it possible to calculate longitudinal elastic stiffness coefficients as well as shear and rigidity coefficients.




Crown copyright: National Physical Laboratory.

ELECTRO

VISITS THE NATIONAL PHYSICAL LABORATORY


Electron Microscopy

The photograph left shows an A.E.I. EM802 electron microscope being used to study grain boundaries in an alloy of considerable technological importance. Investigations aimed at improving the properties of materials require very sophisticated techniques. This instrument is a 100kV electron microscope which allows the specimen to be examined at magnifications up to 160,000 times at resolutions better than 0.5 microns. The National Physical Laboratory have recently taken delivery of a new high voltage microscope to assist in their study of the properties of materials.

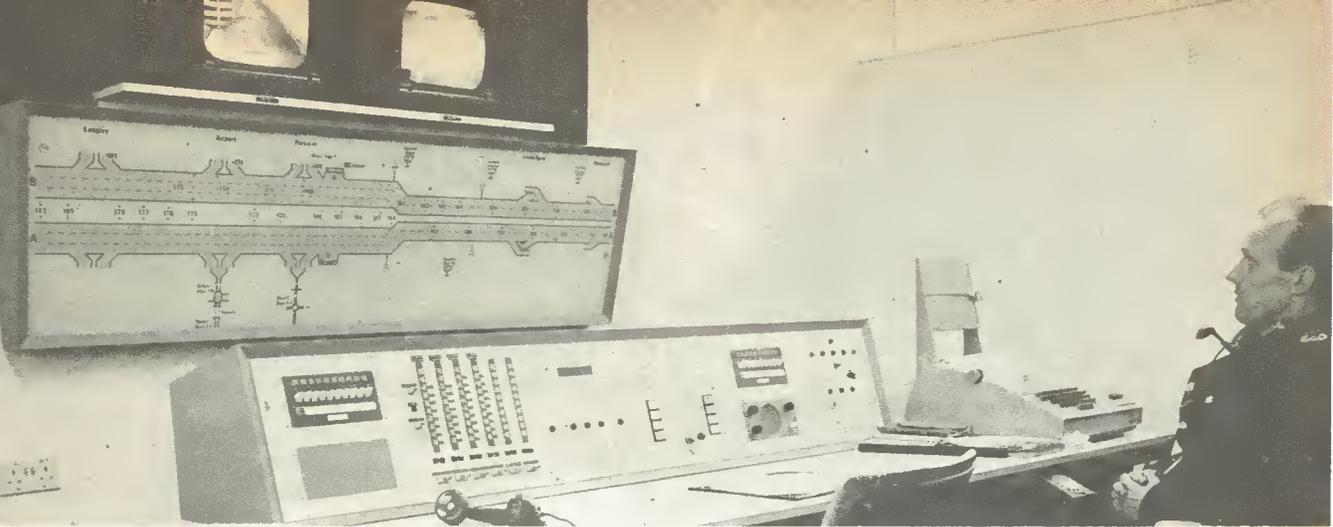

Control centre for M4 Signalling System showing the control desk, mimic diagram and closed circuit television monitors. Situated on the desk is the control for emergency telephones, police radio and closed circuit television

NORAMA

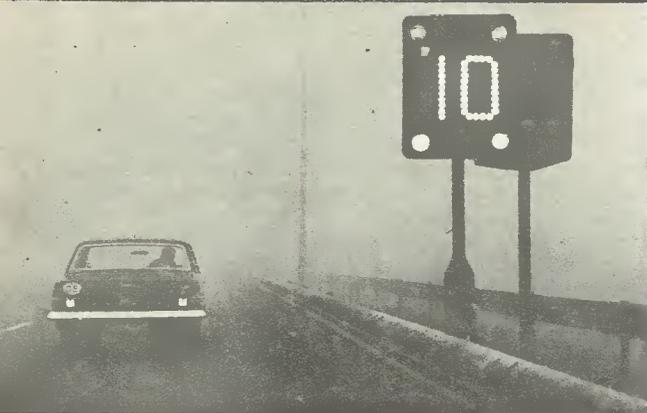

Post mounted signal situated on the central reservation, showing 10 m.p.h. speed restriction

The display of signals is controlled by an Elliott 900 series computer which first checks the typed instructions; if the instruction is valid the computer allows it to be passed to the signals.

The system incorporates check routines that automatically interrogate responders to ensure continued normal operation. In addition, impact detectors on posts and gantries provide immediate alarm should any signal be hit by a vehicle. Meteorological sensors can be added to give automatic warning of weather hazards. Comprehensive protection is also incorporated to prevent dangerous situations arising from power failure or equipment malfunction. The system includes closed circuit TV cameras controlled from Heston, providing surveillance of important points on the motorway.

The proposal to introduce signal systems throughout the motorway network by the mid-1970's was announced in November 1966. Aimed at reducing accidents and securing safer all-weather driving conditions on motorways, these automatic signals will gradually replace the temporary flashing amber signals.


Gantry mounted signals at the Lionel Road Interchange showing a diversion


M4 TRAFFIC CONTROL

At the official opening, on March 21, of the new remotely controlled signals on the M4 motorway, the Joint Parliamentary Secretary to the Ministry of Transport, Mr R. Brown, had the following words to say:

"Today's switch-on is a major step forward in increasing road safety—and we hope it will reduce the number and severity of motorway accidents".

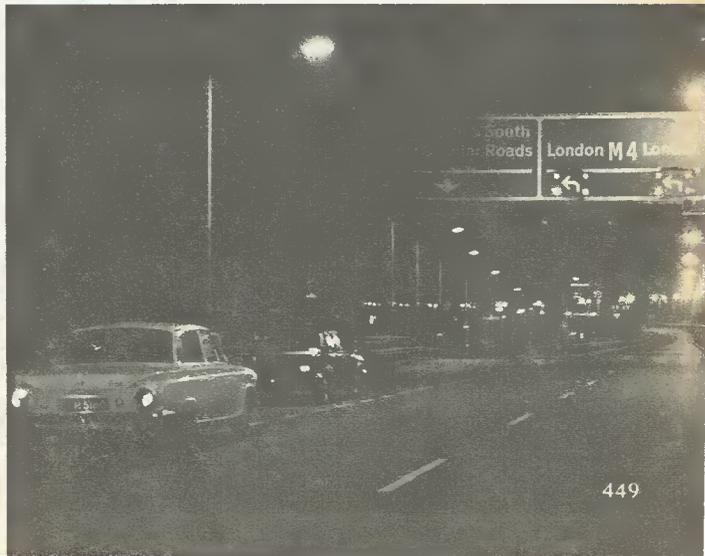The new computer controlled system was manufactured and installed by GEC-Elliott Traffic Automation Ltd., and developed in collaboration with the Ministry of Transport. This first installation covers an 11 mile stretch of the M4 between Chiswick Flyover and Langley Interchange and is operated by the Metropolitan Police from a control centre at Heston Service Area.



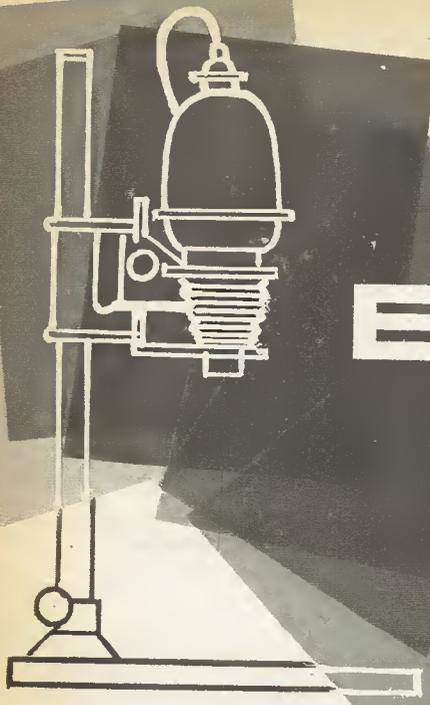

Photographic Enlarger **EXPOSURE METER**

By **A.M.RUDKIN, B.Sc.,(Eng.)**
AND G.D.RUDKIN

THE INSTRUMENT to be described in this article was designed for use with a photographic enlarger to determine the exposure times required for any particular enlargement.

Although it requires calibration for each grade of printing paper, the instrument is very easy to use once calibrated and the results obtained are consistently good.

DESIGN ASPECTS

Any device connected to the mains supply is a potential danger unless it is built very carefully. A low voltage battery operated unit is safer to use.

The exposure meter is operated in low light conditions and it is essential that the operator can adjust it easily in such conditions when the need arises.

The reading of the exposure meter should not change, despite changes in the supply voltage due to mains voltage fluctuations or to battery ageing effects.

The photographer may use a number of different grades of printing paper; the meter has been designed to accommodate any grade.

The total cost of the meter has been kept to a reasonably low level without sacrificing its performance.

In designing this exposure meter the above requirements have been met with a simple transistorised circuit using a photosensitive resistor as the light sensing element.

A photosensitive resistor or light dependent resistor (l.d.r.) has a very high resistance in total darkness. The resistance falls as the light intensity increases until, in bright light, the resistance is as low as 100 ohms.

To meet the stability requirement a bridge circuit is incorporated. Although a d.c. or a.c. bridge circuit could be used, the latter is more convenient in this application since it can provide an audible indication of balance when optimum exposure conditions are set up.

CIRCUIT

The complete circuit diagram is shown in Fig. 1. The first two transistors TR1 and TR2 are used in a simple multivibrator circuit which oscillates at a frequency of about 500Hz. The output of the oscillator is used to feed the bridge circuit containing the photosensitive resistor.

By adjusting the potentiometer VR1 the a.c. voltage developed across the l.d.r. can be balanced against the voltage across the lower part of the potentiometer. In this condition the voltage across the transformer primary will be at a minimum and consequently the sound output from the earpiece will also be at a minimum.

The transformer isolates the bridge circuit from the amplifier circuit formed by transistors TR3 and TR4. TR3 is connected as a common emitter amplifier and is directly connected to the emitter follower stage.

Since the output impedance of this stage is low, almost any magnetic earpiece can be used as the indicator. The prototype used a balanced armature earpiece of 30 ohms impedance.

COMPONENTS AND CONSTRUCTION

A suggested component layout is given in Fig. 2 and the photograph of the complete unit shows the positions of the controls.

The values of R5 and R6 were found to be correct for the l.d.r. used in the prototype (ORP12), but if a different l.d.r. is used these values would probably need adjustment.

The transformer was obtained from a television chassis, but any transformer having a ratio of about 4:1 could be used, for example the Ardenite D239 or D189 which have ratios of 4.5:1 and 3.66:1 respectively.

The circuit has been designed so that almost any transistors can be used in the various stages. The

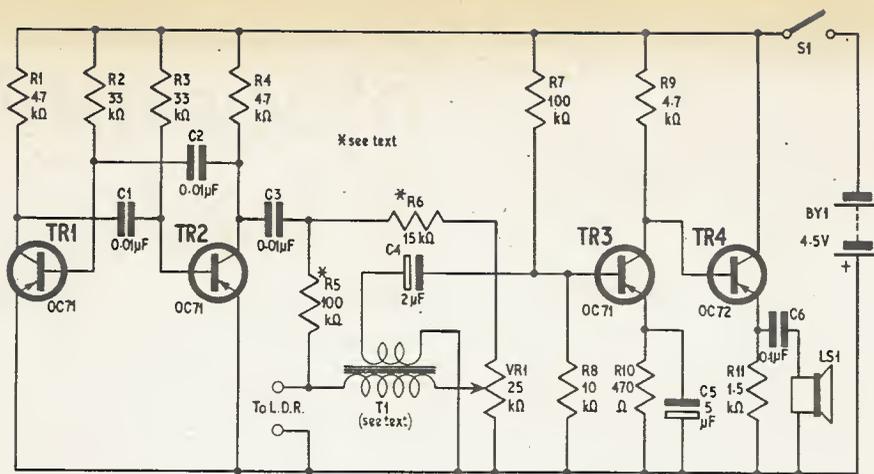


Fig. 1. Complete circuit of the enlarger exposure meter

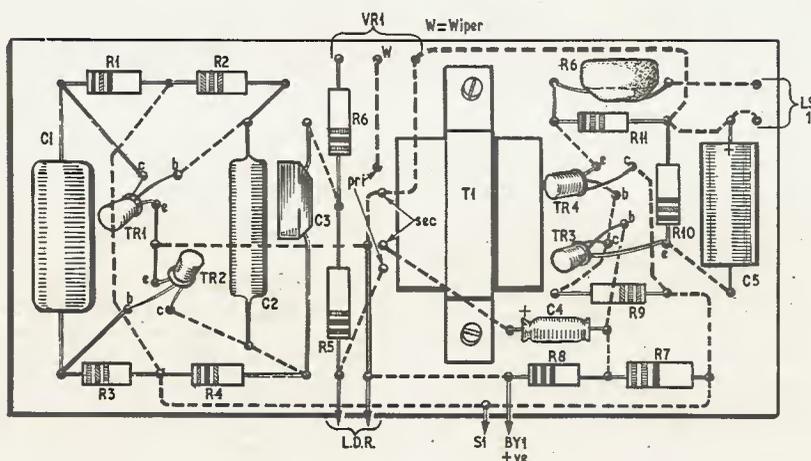


Fig. 2. Layout of components on the perforated wiring board. Underside wiring is shown as dotted lines

COMPONENTS . . .

Resistors

R1	4.7k Ω	R7	100k Ω
R2	33k Ω	R8	10k Ω
R3	33k Ω	R9	4.7k Ω
R4	4.7k Ω	R10	470 Ω
R5	100k Ω	R11	1.5k Ω
R6	15k Ω		

All $\pm 10\%$, $\frac{1}{4}$ watt carbon

Potentiometer

VR1 25k Ω linear carbon

Capacitors

C1	0.01 μ F	} polyester
C2	0.01 μ F	
C3	0.01 μ F	
C4	2 μ F elect. 15V	
C5	5 μ F elect. 15V	
C6	0.1 μ F polyester	

Transistors

TR1, 2, 3 OC71 or OC45 (3 off)
TR4 OC72 or OC84

Transformer

T1 Small signal transformer 4.5:1 (D239 or TT49)

Miscellaneous

LS1 Balanced armature earpiece 30 ohms
X1 Light dependent resistor, type ORP12
BY1 4.5 volt flat battery
S1 Single pole on/off switch
Perforated component board and solder pins
Hardboard or $\frac{1}{4}$ in plywood for case (Fig. 3)
Expanded metal grille, knob with pointer, sockets for l.d.r.

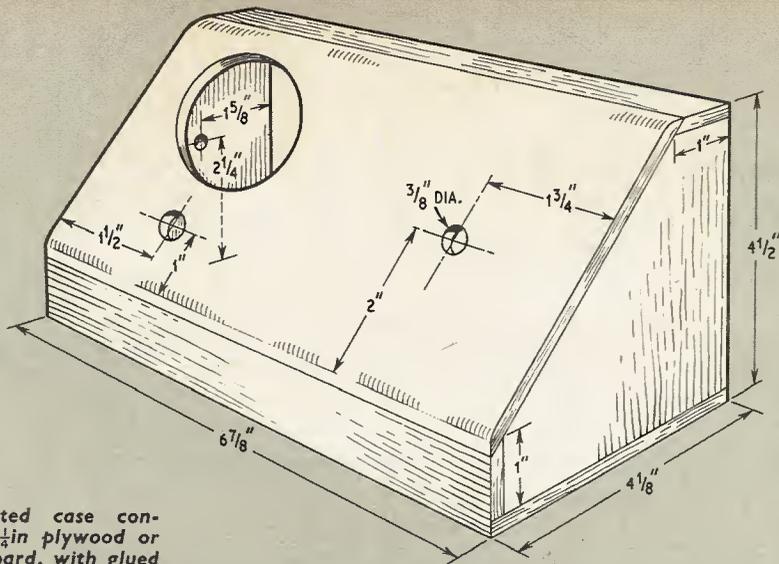


Fig. 3. Suggested case construction from $\frac{1}{2}$ in plywood or standard hardboard, with glued corner fillets

multivibrator circuit will work with transistors having current gains of ten or less. For the TR3 position a transistor having a higher gain is desirable. Satisfactory operation was achieved using four OC71s, but very cheap transistors of low gain are equally suitable.

The majority of the circuit is built on perforated wiring board (Fig. 2), although there is no reason why other construction methods should not be used. The whole unit is assembled in a home-made wooden case (Fig. 3).

The i.d.r. is mounted on a strip of s.r.b.p. with the photosensitive area facing uppermost.

The photograph shows the paper scale with the inked markings. Units were marked every 15 degrees with half-units marked midway between them. This gives

a scale having 20 major divisions since potentiometer spindles usually rotate through 300 degrees between the end stops. Low readings on the scale correspond to high light intensities and the high scale readings to low intensities.

CALIBRATION

The scale on the meter has linear markings and it now remains to show how these markings are used with the printing paper. Calibration graphs are prepared for each different grade of printing paper in the following manner.

The instrument is taken into the darkroom and a clear piece of film from a blank exposure is placed in the enlarger. Having switched off all light sources (except the enlarger) the detector head is placed on the enlarger easel and the balance control is set to some reading on the scale.

The aperture ring of the enlarger is adjusted until a balance point is heard (i.e. when the sound from the earpiece is at a minimum). Having found this balance point the enlarger is switched off and a narrow strip of printing paper is used to make a test strip (see Fig. 4).

Stripes on the test strip can be obtained in steps of one second. After developing and fixing the strip the result will be similar to that shown in Fig. 4 where the gradual transition from white to black can be seen. The numbers below the strip indicate the exposure times in seconds and the arrow indicates the exposure that gives the first black stripe.

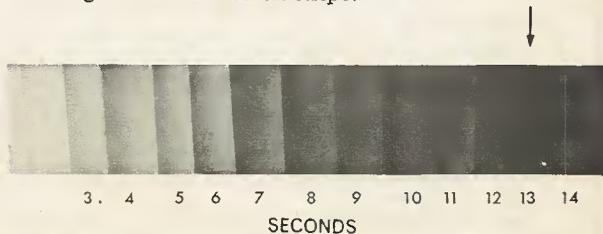
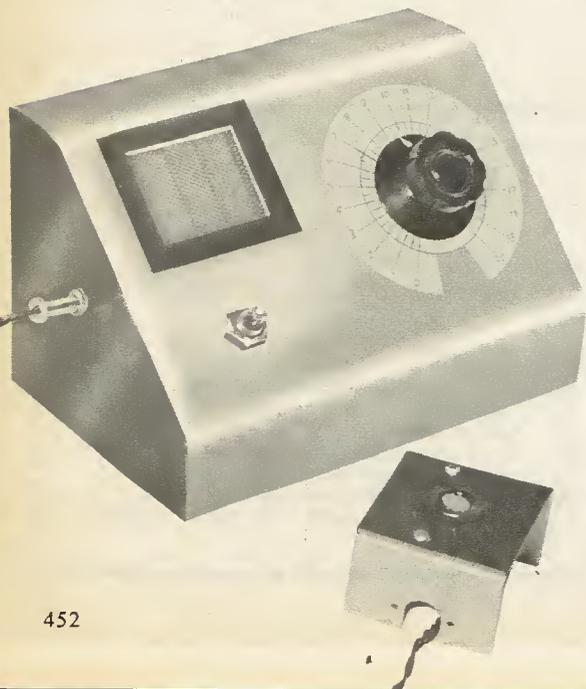


Fig. 4. Graduated tone scale for set exposure times

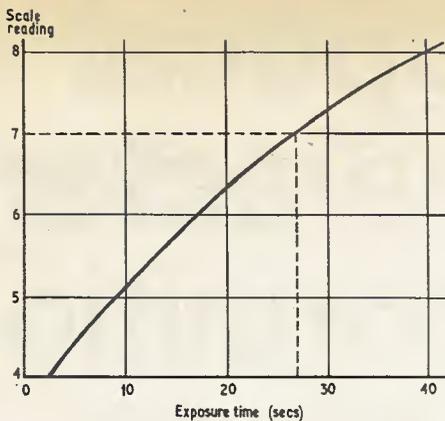


Fig. 5. Calibration graph for indicating exposure time against scale reading

This exposure time is recorded together with the scale reading of the exposure meter and by taking test strips for various scale readings a calibration graph can be drawn. A typical calibration curve is shown in Fig. 5. For higher scale readings it is more convenient to make exposure strips at two or four second intervals.

This procedure must be repeated for all other types of printing paper used but after the first calibration curve has been plotted subsequent calibrations will be easier since the operator will already have some experience of the meter and his paper. For example, an exposure of two seconds would very rarely be encountered for a 10in x 8in print from a 35mm negative!

EXPOSURE TIMING

The correct exposure for any normal negative where all tones are to be preserved may be found by placing the detector head under the magnified image of the clear margin of the negative, and adjusting the balance control until a balance point is found. The correct exposure time is then found from the calibration graph. For example, if the scale reading was 7 and we assume that Fig. 5 is the correct calibration curve, then the correct exposure time would be 27 seconds.

Difficulty is only encountered when extreme negatives are printed on normal grade paper but this is only to be expected and in these cases a reading will provide the basis for making an accurate test strip.

Many special effects may be created by placing the detector under any part of the negative that one wants printed black and exposing for the corresponding time. This is particularly successful for silhouettes.

Some difficulty may be found when attempting to obtain balance points corresponding to high scale readings (i.e. in low light intensity levels) since the minimum is not too distinct, but the error involved is only very small and should not affect the quality of the finished print.

ADVANTAGE

The main advantage of the exposure meter is that it saves the operator having to make test strips for every different enlargement and consequently leads to a saving in time and materials.

This exposure meter can be built for as little as 50s, which is considerably cheaper than any comparable commercial instrument. A wooden cabinet costs only a few shillings to make, but any wood, plastic or metal box could be used with equal success. ★



EXHIBITION

IT is always a pleasure to visit the Public Address Exhibition, as this exhibition is held in one of the most convivial and friendly atmospheres encountered at any such shows. This does not mean that the proceedings are not taken seriously, far from it. The amount of professionalism that is put into the proceedings is immediately apparent when one visits the stands and attends the lectures held each day throughout the exhibition.

This year's exhibition, held at the King's Head Hotel at Harrow-on-the-Hill, on March 11 to 13, was the 21st anniversary of the exhibition and there was a special display on the lower floor devoted to early equipment and papers of historic interest. The exhibition was slightly smaller than previous years; this was due to a similar exhibition held abroad the week before and the lack of time to transport equipment back to England. Nevertheless, the 27 companies taking part represented the best in the P.A. industry, and quality was the main theme.

Customer package deals and interchangeable or add-on units were evident at many of the stands. Of these the Private Communications Division of STC broke new ground with their range of complete public address equipment for particular requirements. The kits are designed to be able to cater for small churches and halls, social and sports centres, office intercom, and background music units.

A complete range of Philips P.A. equipment and a newly styled range of indoor cabinet and column loudspeakers, ranging from a small cabinet handling 1/3 watt to a speech and music column capable of handling up to 20 watts was exhibited on the Philips Sound Division of Pye T.V.T.

Microphones obviously paid an important part in the exhibition, as no equipment can meet manufacturers' data unless the "front end" delivers the "goods". Of the numerous microphones on display the FC range of condenser microphones from Fi-Cord Co., carry an unconditional five year guarantee against any kind of maltreatment. These microphones are suitable for pop music groups due to the falling bass response below 200Hz, thus minimising acoustic feedback—not to mention the current trend of stage acts of complete break-up of instruments during a performance.

Many new and improved design power amplifiers and loudspeakers were evident at most stands. Reliance exhibited their Buxford flameproof loudspeaker, which is claimed to be incapable of causing a fire or explosion.

Finally, the Association took the opportunity to introduce a special 45 r.p.m. double-sided test record of sounds and phrases for microphone and system testing. The record provides 3 minutes of male speech, with a special 30 second off-mic speech to illustrate the importance of correct microphone technique. Female speech follows and runs for 3 minutes.

Side two comprises selected intelligibility phrases for phonetic balance and general performance of the complete installation; 1,000Hz tone and warble tone, for equipment line-up and measurements with sound level meters, and a reference level for individual equipment. The inclusion of white and pink noise, while of limited application without auxiliary equipment, are for aural evaluation of loudspeakers, pick-ups, tone controls, and filter circuits.

Although prepared primarily for A.P.A.E. members the record is available for general (*bona fide*) professional use. The record costs 15s, plus 1s postage and packing, and applications for copies should be made to the A.P.A.E. Sales Office, 394 Northolt Road, South Harrow, Middlesex.



Optical Character Recognition

By P. J. POBGEE (National Physical Laboratory)

As computers play an ever-increasing part in our daily lives the need to communicate with them also increases. We find it convenient to mark symbols on paper in the shape of bills, cheques, and other documents. Before a machine can process this information it has to be translated into another form, such as a code of electrical impulses.

UNFORTUNATELY, the problems in constructing a device to recognise just the numerals 0 to 9 are far from trivial and at the present time large numbers of people are employed merely translating this data into a more acceptable form.

For example, the code, which the Post Office has introduced for postal addresses to aid the sorting of mail, has to be re-marked as a pattern of fluorescent dots to be readily detectable electronically.

Conversely, the software outputs of computers often have to be duplicated in both machine and human languages. An example is the overprinting of punched cards with alphanumeric symbols used by insurance companies.

MAGNETIC INK

A compromise is reached by banks using magnetic ink. The characters printed at the bottom of cheques are specially shaped to be distinguishable by a machine and yet remain intelligible to the human eye. As the cheques are fed through the machine the strip of magnetic printing ink is used in a similar way to a piece of magnetic tape being played back by a tape recorder.

Although the required quality and accuracy of printing is expensive to produce, the reading head is not affected by irrelevant marks such as date stamps or the pattern of the paper.

However, what is really needed is a device capable of recognising ordinary writing. One approach is to imitate the retina of the human eye by constructing an array of light sensitive elements. These divide the field of view into cells and a large number of elements are required to give adequate resolution. They are so connected that when a pattern covers the appropriate cells the machine's logic emits the corresponding signal.

This highlights two difficulties: if the pattern occurs in a slightly different place another group of cells is covered, requiring the logic to be repeated; the logic has also to decide whether each element is seeing ink or blank paper. The latter problem arises because, for

other than perfect printing the patterns are not just black and white but contain intermediate shades of grey.

The intensity we call black depends on the background surrounding that area. For example, a badly printed 5, with a faint top and a heavily smudged bottom, gives false information that the open part of the loop is darker than the top stroke of the character; this must be ignored.

"CYCLOPS"

An interesting alternative known as *Cyclops* will now be discussed in some detail.

If the image of a raster on a cathode ray tube is projected on to a document and the reflected light is collected by a photocell, a video signal is produced. This flying spot technique is the type of television camera often used for transmitting cine films. The three dimensions of horizontal and vertical position and grey value are represented by the two dimensions of time and electrical amplitude.

If this video signal is passed through a pure time delay the effect is the same as if the pattern had been in a different place. Times equivalent to the durations of line scan correspond to horizontal shifts, and fractions of a line period to vertical shifts. (It is most convenient in this case to have the fastest scan in the vertical direction.)

Fig. 1 shows the effect of delaying the signal by a complete line period and also by an additional quarter of a line. If we measure the correspondence between these copies, at any instant we relate the ink density at three points, such as ABC, separated by the distances determined by the time delays.

Since we are comparing the signal only with itself the correspondence is unaffected by the position of the original pattern. We call such an arrangement of points an n -tuple and design it to fit on a characteristic feature of the patterns to be identified. Any number of points may be so grouped, including negative ones. The latter are realised by inverting the video waveform

so that the presence of white, such as the centre of a zero, may also be detected.

LOG CIRCUITS

It is necessary to measure the correspondence by multiplying the signals at each point together, since we wish the answer to be zero whenever any of the points do not fit. Mere addition still gives a sum even when one of the components are zero.

Fortunately the voltage across a forward biased semiconductor junction approximates to the logarithm of the current flowing through it and economic multiplication can be performed by adding the logarithms as in Fig. 2.

The output of the antilog circuit represents a continuous measure of the fit of the n -tuple as the raster scans the input pattern. If this output is integrated over the whole field of view a measurement is obtained which depends on the overall shape of the original pattern but is independent of its actual position.

We may extract a set of such measurements by using several different n -tuples simultaneously. Each one will measure the amount of its appropriate feature but will also vary with the contrast of the ink with paper, although they will tend to move in sympathy with each other. For example, a pattern with a poor contrast will give a low output on all the measurements.

To cope with this problem *Cyclops 1* uses 20 n -tuples feeding 10 numeral wires through resistors, these being chosen to correspond with the relative fits of the n -tuples expected for that numeral. By selecting the wire with the largest signal the answer is only dependent on the ratios of the n -tuple measurements and not their absolute values.

Using these techniques *Cyclops* is able to recognise a strip of ten unknown numerals in inferior printing in less than 4 milliseconds.

HANDPRINTING

There is still a long way to go to approach the performance of a human reader who interpretes the enormous variety of shapes and sizes produced by handwriting.

The n -tuple technique just described has the advantages of speed and simplicity for machine generated printing where the patterns are of predetermined shape, although their outlines are generally not well defined.

A hand printed character, however, often has a sharp outline but consists of a sequence of strokes whose relative positions are variable. The strokes may be treated as mini-characters and recognised by the n -tuple method.

If the order in which they appear is noted, a parts list can be prepared to match with a catalogue built into the machine. For example, if the strokes are labelled horizontal h , diagonal down to right r , diagonal down to left l , and vertical v , then a 5 when scanned from top-to-bottom and left-to-right could be coded $hvrhlvr$. This code may be represented by a series of pulses and compared with similar pulses stored in the machine.

Yet another system ignores positional information by tracing around the outline of the unknown character and forming a list of the directions travelled from point to point. The length of a list obviously depends on both the size and shape of the pattern but Mullard Research Laboratories are successfully reducing such lists to a standard number of measurements. By presenting measurements from typical patterns to a computer they are able to use it to adapt a decision mechanism to recognise handprinted numerals.

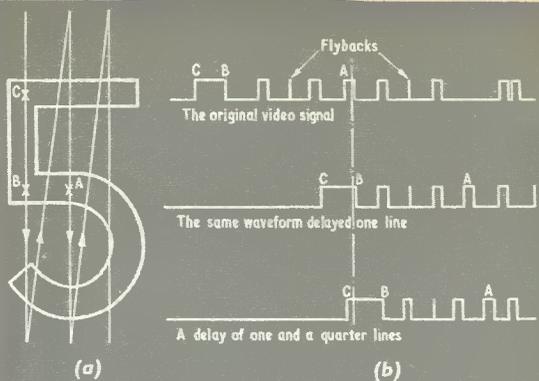


Fig. 1a. Basic raster pattern superimposed on a figure 5. (b) Wave forms corresponding to recognition response on the figure 5

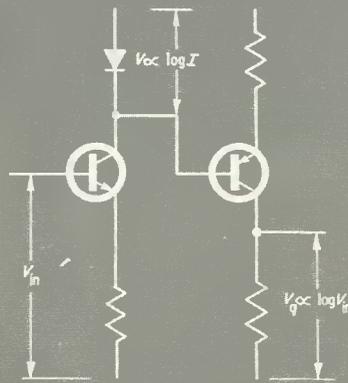


Fig. 2a. Basic theory of the log-generator

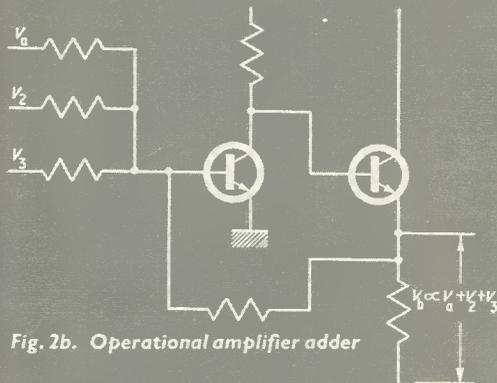


Fig. 2b. Operational amplifier adder

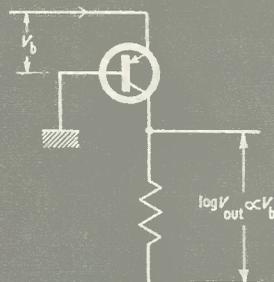


Fig. 2c. Antilog circuit using a base-emitter diode

Fig. 2. Simple analogue multiplier

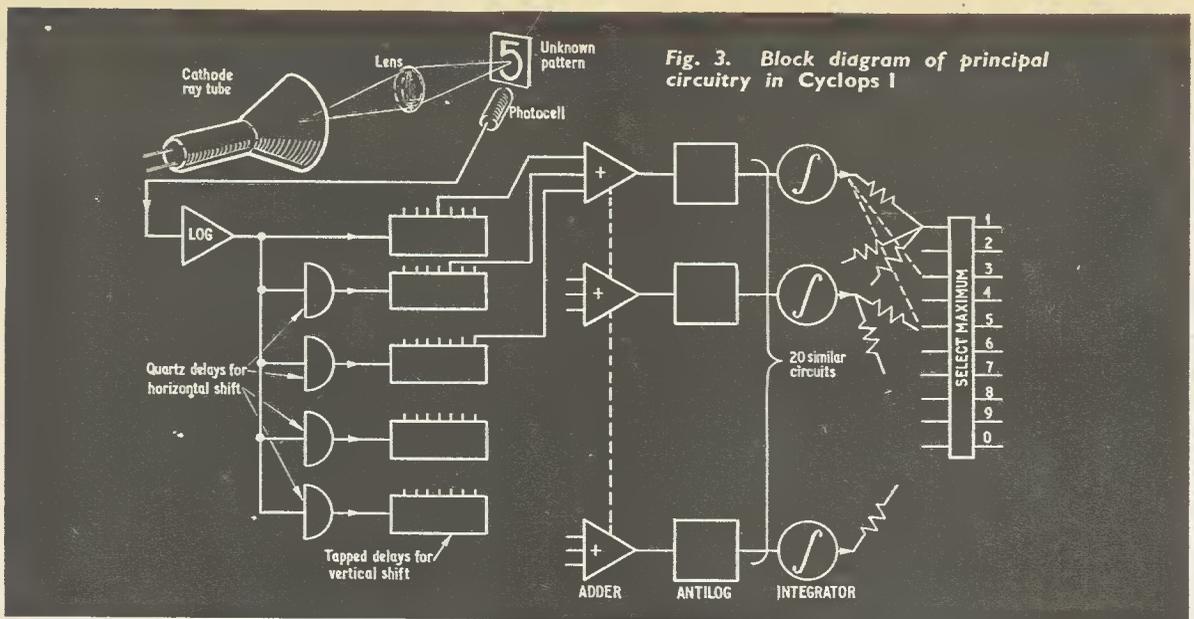


Fig. 3. Block diagram of principal circuitry in Cyclops I

The process is analogous to that of training the resistive network, to which n -tuple measurements are applied, in the *Cyclops* system to modify itself when a wrong answer is obtained.

OPTICAL METHODS

Other investigations being carried out allow processing of all the elements of a pattern in parallel at the speed of light. An obvious method is to compare the unknown with a set of photographic masks. The difficulty arises in fitting the pattern on the masks. Any difference in shape or position reduces the correct fit and may increase the wrong one.

Consider a simple pattern composed of alternate black and white lines. By scanning across it a "temporal" frequency, of so many peaks per second, could be obtained but this value would depend on the speed of the scan. By using the concept of "spatial" frequency, of so many peaks per millimetre, the pattern is described without reference to time. Complex patterns can be built up from a Fourier series of spatial frequencies in the same way that a complex electrical waveform may be obtained from a set of sine waves.

By using a transparent pattern as the aperture of a lens a Fourier transform can be obtained at the focal plane of the lens. This transform is, in effect, a graph

Cyclops I character recognition machine

of the spatial frequencies present in the pattern against axial distance. The finer the detail the more the light is diffracted from the optical axis. A blank pattern produces a bright spot of light at the focus since it corresponds to zero spatial frequency. These transforms are independent of the input position thus removing one variable. Unfortunately, the transformed patterns appear to be even more difficult to separate into character types.

If a filter is placed in the focal plane to suppress certain frequencies the detail present when the original pattern is reformed may be enhanced or reduced as an aid to recognition.

HOLOGRAMS

A recent article explained how holograms can be formed by using a single reference beam. By illuminating the hologram with a similar beam the original pattern may be reconstructed.


One can also make a set of holograms on a single photographic plate using a different beam or code of beams for each example of a character. When this plate is illuminated by a similar pattern the appropriate beam or code is reconstructed. If the unknown pattern is only slightly different from the appropriate one of the hologram the resulting beam may be lost in the spurious light generated by incorrect fits.

Although photographic emulsion can store an enormous amount of information it is obviously impracticable to store examples of every type of distortion expected.

This problem and the need to produce the input data in transparency form appear at present to place optical processing at a disadvantage with the ease with which complex functions can be performed by integrated circuits.


ACKNOWLEDGMENT

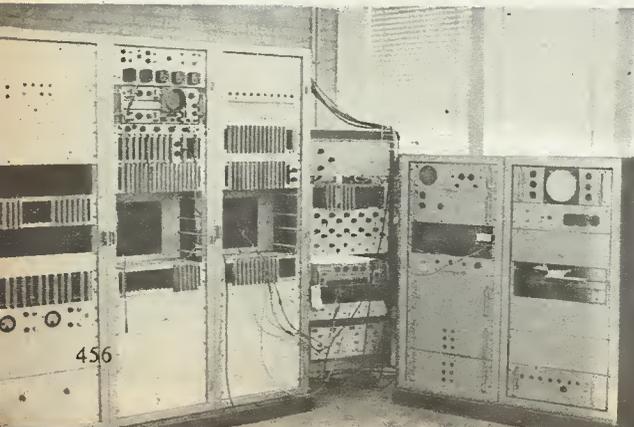The author is grateful to the Directors of National Physical Laboratory, Ministry of Technology, for permission to publish details of the *Cyclops* character recognition machine, built in the Computer Science Division.



S ↓ T ↓ μ

DeC A logical development

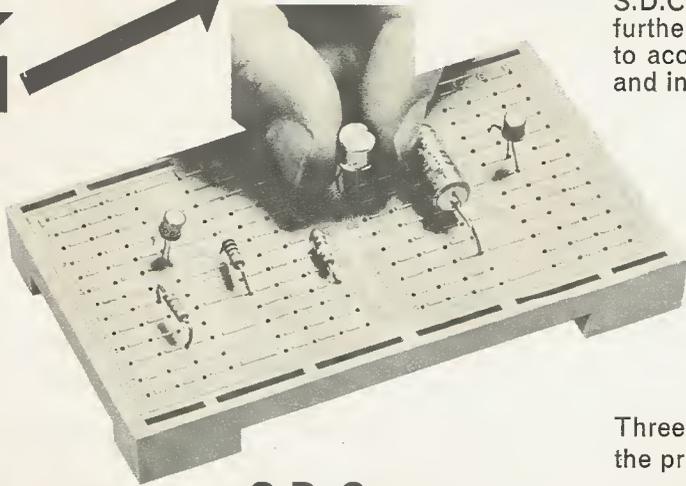

S.D.C. Electronics have now produced a further range of their well-known breadboards to accommodate modern short lead devices and integrated circuits.

The new T-DeC Breadboard is now available to amateurs:

- Greater ability, 208 connection points
- 38 Independent Junctions
- Completely Solderless
- Control Panel with every DeC
- Short lead devices push directly into contacts
- Accommodates integrated circuits using standard carriers.

Three times the capability at less than twice the price. **Unit Pack 50/-**

S-DeCs Now a new pack is available for the Experimenter, the DeCSTOR. This pack consists of:— ● Two S-DeCs ● Set of accessories ● Control Panel ● International Edition of circuits booklet ● Divided Components Tray with its own lid.

All supplied as illustrated in a black plastic Storage Container **ONLY 67/6d.**

Also Available: The single S-DeC Pack (contains one S-DeC, Accessories, Control Panel plus circuit booklet) **ONLY 29/6d.**

4-DeC Pack (Four DeCs, two sets of Accessories and Control Panels plus circuit booklet) **ONLY 117/6d.**

J-DeCs Included in the new range is a breadboard primarily designed for use with integrated circuits—send for further information by completing the coupon.



ACCESSORIES

One of the many features of DeC breadboards is that links may be made with single strand wire but the following Plugs and Leads are available (all supplied in Packs of 10).

- (a) 1mm Plugs (Specify Yellow, Green, Blue or Red) 3/9d. per set.
- (b) Leads with 1mm Plugs fitted at both ends (Specify length 2", 3", 4", 5" and 7") 12/6d. per set.
- (c) 20" Leads with single 1mm Plug 8/6d. per set.

T-DeCs, S-DeCs and Accessories are all obtainable from leading suppliers throughout the U.K. In case of difficulty, complete the coupon and mail without delay.

Post To:

S.D.C. ELECTRONICS (SALES) LTD
34 Arkwright, Astmoor Industrial Estate,
Runcorn, Cheshire (Runcorn 5401)



Please send me:—

..... T-DeC Pack S-DeC Single Pack

..... DeCSTOR Pack 4-DeC Pack

..... Accessories.

Tick here if you require further details of the μ-DeC

I enclose PO/Cheque/Money Order value £ / / d
Money refunded if not satisfied.

Name

Address

.....

.....

NEWS BRIEFS

Computer Aided Design

THREE YEARS ago the Racal Group Chairman, Mr E. T. Harrison, announced the commencement of a research programme at Tewkesbury to study the possibilities of designing electronic circuits and equipment with the aid of a computer. The idea has now become a reality and, with the support of the Ministry of Technology, REDAC (Racal Electronic Design and Analysis by Computer) is being offered as a consultative service to the electronics industry.

The established breadboard development technique using discrete components is replaced by a more reliable method, involving the application of stored information to mathematical and theoretical problems.

Reliability is improved, costs stabilised and predetermined at the design stage, and marketing of an original concept can be considerably speeded up. As an example, where a printed circuit board can take about three weeks to design by conventional methods using drawing office facilities, REDAC can do the work in less than a week at about the same cost. Multilayer integrated circuits can be designed by using a cathode ray tube graphic display machine developed by Elliott Automation.

Mr E. Wolfendale, Deputy Managing Director, has spent much of his time in computer aided design and has travelled to many parts of the world to lecture on the subject. In describing the system, he emphasised the possibilities of taking into account a sensitivity analysis and "worst-case" or statistical tolerance performance, so that the designer can re-analyse, re-optimize and re-tolerance to provide for these factors.

Because electronics is becoming so complex, Racal believe that time and money will not be available in the future for traditional manual design methods employing such a wide range of components. It is not expected that Racal will monopolise the system idea; indeed, they are offering a tutorial service to customers' engineers which will enable them to computerise on their own premises.

Inevitably a design language is needed for the computer and the mathematical and languages group have developed a special circuit calculation language for the designer to use. Input specifications or updating data are sorted by the computer into component generic types, then classified in data form into a manner easily accessible to the designer.

Off-line data links are provided between the design centre and the customer by G.P.O. Datel links.

Skynet

THIS year will see the introduction of Skynet—the United Kingdom's Defence Satellite Communications System. The overall system has been designed by Mintech to satisfy stringent Ministry of Defence requirements. The System will comprise nine earth stations and two satellites, one operational and one standby (procured from and launched by the United States), in a closely defined synchronous orbit some 23,000 miles above the Indian Ocean.

Five of the earth stations will be placed at fixed locations, two installed in the assault ships HMS *Fearless* and HMS *Intrepid*, and two air transportable mobile stations will be held available for rapid deployment to meet contingency requirements. The network of stations and the satellites will provide better and more reliable communications for all arms of Britain's forces, and will provide a national communication capability from the Atlantic to the Far East including Hong Kong.

International Apprentice Competition

SELECTION tests for this year's British entrants in the International Apprentice Competition took place at Southgate Technical College during April. Two sections of the competition, which covers a large variety of skills and involves apprentices from all over the world, were dealt with at Southgate. They were: the Industrial Electronics section, looked after by Mr Smith of Nottingham College of Technology, and the Radio and Television Servicing section under the watchful eye of Mr Hicks of Southgate Technical College.

The results of the examinations are placed before a committee who decide on the placings of apprentices and award Gold, Silver and Bronze medals to the first three apprentices in each section. The first apprentice in each section is sent to the final which is to be held at Brussels in July and the second apprentice is a non-travelling reserve.

This year's winners were:—

Industrial Electronics section:

1st Mr P. Guttridge; Mintech.R.A.E. Farnborough.

2nd Mr G. Clarke; Mintech.E.Q.D. Aquila.

3rd Mr D. Bracknel; Mintech.R.A.E. Farnborough.

Radio and Television Servicing:

1st Mr R. Pheasant; Alex Owen Ltd.

2nd Mr D. Throup; Fairbank Harding Ltd.

3rd Mr M. Hobs; R. P. Jones.

Electronics Help Beat Crime

INDUSTRIALISTS in Birmingham will be the first in the country to have the opportunity of being connected to a new type of equipment to monitor burglar and fire alarms installed on their premises.

Securitas Alarm Limited have developed the Securifon, which will enable a constant "electronic" watch to be kept on alarm systems installed in subscribers' premises in the Birmingham area. The system, operating over normal GPO telephone lines, uses the principle of telemetry.

Data on the current state of burglar alarms in up to 100 subscribers' premises is fed into a satellite station usually located within a two mile radius. Coded signals are then fed from the satellite station via a single telephone line and displayed on a control unit located at a central station, manned 24 hours a day by security personnel.

POINTS ARISING

POCKET RADIATION MONITOR (April 1969)

The specified transformer T1 was made by Messrs Fortiphone three years ago; it was a standard 6V-800V 1 watt inverter type (6V-400V plus doubler). Messrs Fortiphone are still the suppliers of either: L1320/4; L1320/8; L1321/4 and L1321/8, all of which will function well in the circuit.

D.C. FEEDBACK PAIR (December 1968)

In Fig. 7 on page 855 the output from TR2 should be taken from the emitter and not the collector.

ELECTRONIC SPIROGRAPH PATTERNS


(May 1969)

The first caption on page 371 should be: *Hypocycloids, loops now peaked*

Here's money-making repair data for over 1000 POPULAR MODELS

From 1969 right back to 1965!

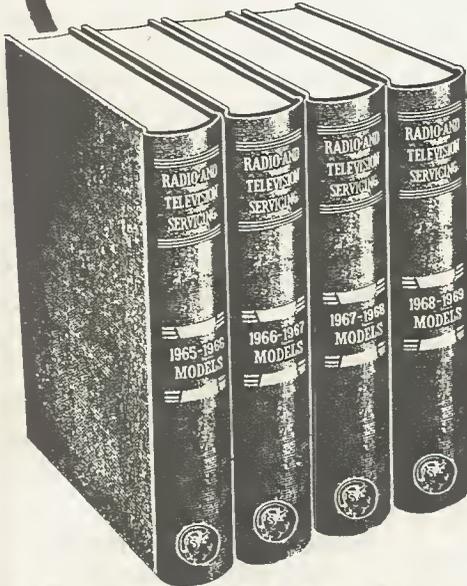**RADIOS • RADIOGRAMS
RECORD PLAYERS • CAR
RADIOS • TAPE RECORDERS
TV's including COLOUR TV**
2,180 pages. 2,657 circuits, component layout diagrams, printed panel diagrams, tables and waveform graphs



RADIO & TELEVISION SERVICING

This big RADIO & TELEVISION SERVICING repair library will help you speed up your repair work and increase your earnings. Packed with circuits, repair data and vital information it covers all the popular 1965-1969 TV's, Radios, Radiograms, Car Radios, Record Players and Tape Recorders—including the latest data on COLOUR TV. Four volumes handsomely bound in maroon and gold. 2,180 pages written by a team of expert Research Engineers—there's no other publication like it! Speeds up repair work year after year. Examine this latest edition at home free for a week. Send no money—just post coupon below—there's absolutely no obligation to buy.

COLOUR TV

All aspects of Colour TV are covered—from installation to static convergence. The vital information in the colour section make this repair library invaluable to the Service Engineer.

SERVICING DATA ON ALL THESE MAKES

Aiwa, Alba, Baird, Beogram, Beolit, B.R.C., Bush, Carousel, Cossor, Dansette, Decca, Defiant, Dynaport, Dynatron, Eddystone, Ekco, Elizabethan, Ever Ready, Ferguson, Ferranti, Fidelity, G.E.C., Grundig, H.M.V., Kolster-Brandes, Hitachi, Invicta, McMichael, Marconiphone, Masteradio, Motorola, Murphy, National, Newmatic, Pam, Perdio, Peto-Scott, Philips, Portadyne, Pye, Radiomobile, R.G.D., Regentone, Roberts' Radio, Sanyo, Sharp, Smith's Radiomobile, Sobell, S.T.C., Sony, Standard, Stella, Stereosound, Teletron, Thorn, Trans Arena, Ultra, Van Der Molen World Radio.

SENT TO YOU BY POST ON 7 DAYS FREE TRIAL


JUST OUT!

New 12th Edition of Electrical Engineer's Reference Book

Over 2,000 pages, more than 2,400 Diagrams, Photographs and Tables. A comprehensive reference work on modern theory, practice, equipment and latest developments written by 75 leading experts.

Main Sections include—

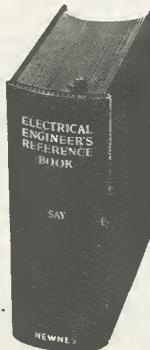Theory and Calculations. Power Station Practice, Cables and Wires, Lighting, Heating, Lifts, Motors, Wiring and Installation, Applied Electronics, Automatic Control, Computers, Latest I.E.E. Reg. requirements. Education, Training, City & Guilds, etc.



To: Buckingham Press Ltd., 18-19 Warren Street, London, W.1.

Please send RADIO & TV SERVICING—4 volumes, without obligation to buy if you accept my application. I will return the books in 8 days or post:

Tick (✓) Full cash price of £16, or

here 20/- deposit and 16 monthly payments of 20/- paying £17 in all.

Also send me on 7 days' trial Electrical Engineer's Reference Book. Cash price £6 6s. or 12/- dep. 12 monthly payments of 10/- paying £6 12s. in all.

If you are under 21 your father must fill in coupon.

Full Name.....
(BLOCK LETTERS PLEASE)

Address.....

County.....

Occupation.....

Signature.....
RTV4/EERB/3998

Please tick (✓) here

The address on left is
Why (your property)

Rented unfurnished

Furnished accom

Temporary address

If none of the above please answer here

Mr.
Mrs.
Miss

BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	2/4	OC171	4/-
AC127	2/4	OC200	3/6
AC128	2/4	OC201	7/-
ACY17	3/-	2G301	2/6
AF114	4/-	2G303	2/6
AF115	3/6	2N711	10/-
AF116	3/6	2N1302-3	4/-
AF117	3/6	2N1304-5	3/-
AF118	3/6	2N1306-7	6/-
AF239	12/6	2N1308-9	8/-
AF186	10/-	2N3844A	3/-
AF139	4/-	Power	
BFY50	7/6	Transistors	
BSY25	3/-	OC20	10/-
BSY26	3/-	OC23	10/-
BSY27	3/-	OC25	8/-
BSY28	3/-	OC26	5/-
BSY29	3/-	OC28	7/6
BSY95A	2/6	OC35	5/-
OC41	2/6	OC36	7/6
OC44	1/11	AD149	10/-
OC45	1/9	AUY10	30/-
OC71	2/6	Diodes	
OC72	2/6	AA742	2/-
OC73	3/6	OA95	2/-
OC81	2/6	OA70	1/9
OC81D	2/6	OA79	1/9
OC83	4/-	OA81	1/9
OC139	2/6	OA73	2/-
OC140	3/6	IN914	1/6

TRY OUR X PAKS FOR UNEQUALLED VALUE

XA PAK
Germanium PNP type transistors, equivalents to a large part of the OC range, i.e. 44, 45, 71, 72, 81, etc.
PRICE £5 PER 1000
POST & PACKING 4/6 U.K.

XB PAK
Silicon TO-18 CAN type transistors NPN/PNP mixed lots with equivalents to OC200-1, 2N706s, BSY27/29, BSY95A.
PRICE £5.50 PER 500
PRICE £10 PER 1000
POST & PACKING 2/6 U.K.

XC PAK
Silicon diodes miniature glass types, finished black with polarity marked, equivalents to OA200, OA202, BAY31-39 and DK10, etc.
PRICE £5 PER 1000
POST & PACKING 2/6 U.K.

ALL THE ABOVE UNTESTED PACKS HAVE AN AVERAGE OF 75% OR MORE GOOD SEMICONDUCTORS. FREE PACKS SUSPENDED WITH THESE ORDERS. ORDERS MUST NOT BE LESS THAN THE MINIMUM AMOUNTS QUOTED PER PAK.

NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries inc. Book of Instructions	10/-
B77	2	AD161-AD162 NPN/PNP Trans. Comp. Output, Pair	10/-
B79	4	IN4007 Sil. Rec. Diodes 1000 P.I.V. 1 amp. Miniature	10/-
B81	10	Reed Switches comp. with Coils and Magnets	10/-
B85	24	Integrated Circuits on Panels. Data supplied with orders	10/-
B89	2	5SP5 Light Sensitive Cells. Light Res. 400Ω Dark 1MΩ	10/-
B90	4	Latest Type Reed Switches. Green Glass GPO type	10/-
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45	10/-
B92	4	NPN Sil. Trans. AO6 = BSX20, 2N2369 500 MHz, 360mW	10/-
B93	5	GET113 Trans. equiv. to ACY17-21 PNP Germ.	10/-
B94	6	NPN Sil. Planar Epitaxial Trans. CS4 similar to BSY38 or BC108	10/-
B96	5	2N3136 PNP Sil. Trans. TO-18, HFE 100-300 I.C. 600mA, 200 MHz	10/-
B98	10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NKT271, etc.	10/-

RETURN OF THE UNBEATABLE P.I PAK. NOW GREATER VALUE THAN EVER

FULL OF SHORT LEAD SEMICONDUCTORS AND ELECTRONIC COMPONENTS, APPROX. 170. WE GUARANTEE AT LEAST 30 REALLY HIGH QUALITY FACTORY MARKED TRANSISTORS PNP AND NPN, AND A HOST OF DIODES AND RECTIFIERS MOUNTED ON PRINTED CIRCUIT PANELS. IDENTIFICATION CHART SUPPLIED TO GIVE SOME INFORMATION ON THE TRANSISTORS.

PLEASE ASK FOR PAK P.I ONLY 10/-
2/- P. & P. on this Pak.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. State 4 or 6 cylinder. **20/- each**

FREE CATALOGUE AND LISTS FOR: -

ZENER DIODES
TRANSISTORS, RECTIFIERS
FULL PRE-PAK LISTS
& SUBSTITUTION CHART

MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

THERE IS ONLY ONE
BI-PRE-PAK LTD
BEWARE OF IMITATIONS

FREE!
PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 10/- WITH ORDERS OVER £4

TRANSISTORS ONLY 1/- EACH

SILICON • PLANAR • N.P.N. • P.N.P

All these types available

2N929	2N706	2S131	2S103	2N696	2N1613	2S733	BFY10
2S501	2N706A	2S512	2S104	2N697	2N1711	2N726	2S731
BC108	2N3011	2S102	2N2220	2N1507	2N1893	2N2484	2S732

All tested and guaranteed for gain and leakage—unmarked. Manufacturers' fall outs from the new PRE-PAK range.

NEW UNMARKED UNTESTED PAKS

B78	12	Integrated Circuits, Data and Circuits of types, supplied with orders	10/-
B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can	10/-
B82	10	OC45, OC81D and OC81 Trans. Mullard glass type	10/-
B83	200	Trans. Newmarket reject and other types NPN and PNP	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	10/-
B66	150	High quality Germ. Diodes. Min. glass type	10/-
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	10/-
B87	100	Germ. PNP Trans. equiv. to OC44, OC45, OC81, etc.	10/-
B88	50	Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, BSY95A, etc.	10/-
B60	10	7 Watt Zener Diodes Mixed Voltages	10/-

PRE-PAK. N.605 POWER TRANSISTOR EQUIVALENT TO NKT301-2-3-4 **5/- each**
COMPLIMENTARY SET NPN/PNP GERM. TRANS. **2/6 pair**



SPECIAL OFFER
G.P.O. TYPE RELAYS
MANUFACTURED BY
A.E.I.
ALL INDIVIDUALLY
BOXED
VARIOUS TYPES
5/- each P. & P. 1/6
5 FOR £1 P. & P. 4/6

FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

BI-PRE-PAK LTD DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

From this series the interlingual form is *aberration del lumine*. What is not shown in the above, however, is how words in the rest of the total paradigm, such as our *luminous*, also influenced the final form.

Of course there are occasional hard nuts to crack when one comes to extract these standard European forms from the control languages. Perhaps those readers who also happen to be linguists would care to advise the author on the problem of the series:

B battery (Eng.)	batterie de tension anodique (Fr.)	batteria B (Sp.)
batteria anodica (Ital.)	B-Batterie (Ger.)	polosa (Russ.)

I would opt for the interlingual form *batteria (de tension) anodic*. Would anybody say that *batteria-B* is a better international form?

WHY NOT ENGLISH?

Some will say that all this is unimportant because English is all set to become the world language of science. It is true that it is a hot favourite, but there are other sturdy competitors like Russian and Chinese.

One would think that the speakers of the most important languages would be able to come to some agreement, especially about technical terms. It is natural that their languages will continue to capture each other's speakers and readers; this is an industrial and commercial struggle as well as a linguistic one. But agreement could avoid the worst effects of the language-struggle.

The "Big Three" would agree to teach each other's languages more than they do at present. Secondly, they would adopt a universal technical code, probably based on the roots common to English and Russian. Chinese and Japanese are importers of these basic words (though the Chinese have probably stopped during the recent cultural revolution). They fit them as best they can into the tone-system of their languages. Here are recent imports into Japanese:

maika chikudenki	mica condenser
maikurohon zatsuron	microphone noise
magunetto sen	magneto wire
rotari shiki	rotary system
refurekkusu zofuku	reflex amplification
homodaim jushiu	homodyne reception
ichi eherugi	potential energy

The basis for agreement upon either a code or an interlingua between Anglo-Saxons and Russians is shown by the following equivalents: (*Eng., Russ.*) crane, crane; electric, electricheski; battery, batereya; telegraph, telegraf; machine, mashina; platinum, platina; hypothesis, gipoteza; selenium, selen; motor, motor.

PRONUNCIATION

The problem of how an interlingua should be pronounced is a highly technical one, which has been written about by Troubetzkoi, the founder of practical phonology and therefore, in a way, of all accoustic and hi fi studies.

The American A. Gode says that the Greek and Latin rootwords can only be given one feasible appearance and pronunciation, a slightly southern European one. That is why the extract at the beginning of this article probably reminded you of Spanish. But it would remind a Spaniard of Italian, an Italian of English. It is Standard European.

Finally, the standardisation of terms has some importance for education. When Greek and Latin studies were more widespread they at least ensured a supply of future scientists who could compose the terminology of their work. Realising that such a class of philologists hardly exists, some Swedish schools have recently introduced classes in General Linguistics for their pupils, along the lines of the interlingua described in this article. ★



ANOTHER international exhibition at Earls Court was nearly postponed due to a go slow by workmen. However, the LABEX exhibition was opened as planned on March 25 by The Rt. Hon. Edward Short, M.P. The completion of some of the stands continued into the second day and at one time there was talk of Pye Unicam's stand—the largest in the exhibition—being taken down and rebuilt, as enthusiastic Pye staff had violated the go-slow over the preceding weekend to finish their stand.

Laboratory apparatus and materials of a fantastic variety were displayed by over 550 firms, half of them from the U.K., some 70 from America and others from Germany, Switzerland, Sweden and Japan in that order. During the exhibition a series of lectures and discussions took place and these, too, covered a wide variety of subjects from "Detection of Flavour in Food" to "Computers in the Laboratory".

Several new instruments made their debut at LABEX. These included the Philips PW 1410 Manual X-ray Spectrometer which allows quicker and more accurate analysis of elements than was previously possible. An experimental computer complex was displayed on the Pye stand, designed to link a number of gas chromatographs and spectrometers to a small computer. Stanton Instruments were displaying a newly developed low temperature differential thermal analyser, which covers a temperature range of between -180 and 450 degrees C. The most interesting feature of this device is its fast cooling rate— from 450°C to ambient temperature in 10 minutes.

Bosch Ltd., and Leitz U.K. Ltd., exhibited a new Iconometric Analysis Microscope which uses an optical electron computer for quantitative analysis and evaluation of optically perceptible structures. The apparatus comprises a very high quality television camera which is attached to a microscope. The video signal from the camera is analysed and evaluated in the main control unit. The picture is also displayed on a monitor, thus enabling an operator to insert marker pulses and an adjustable mask; by this means any area of the picture can be selected for evaluation.

The machine has a wide application in medical, metallurgical and chemical fields.

A number of new low cost Infrared spectrometers were displayed on many stands; some appeared at half the cost of previous instruments: this shows a trend in the laboratory apparatus industry—specialised instruments becoming available at greatly reduced cost and, in many cases, the equipment is more compact and easier to set up and use.

LIND-AIR OPTRONICS LTD

See our vast range of Electronic Components at our new Component Centre 25 Tottenham Court Road




Battery Eliminator. Enables transistor equipment to be operated from AC mains. 6/9 12v. output selector switch and on/off switch. Case size 4 2/3 x 2 1/2 in. complete with mains lead, connecting leads and instructions. 59/6. P. & P. 3/6.

GARRARD DECKS



- SRP25 less cartridge..... £5. 9.6
- 1025 Stereo/Mono with cart..... £7.19.6
- 2025 Stereo/Mono with cart..... £8. 9.6
- 3000S Stereo/Mono with cart..... £9.19.6
- 3000D Stereo/Mono with cart..... £10.19.6
- SR25 less cartridge..... £10.19.6
- SR25 with Decca Deram cart..... £17. 4.6
- SL45 less cartridge..... £18. 9.6
- SL45 with Decca Deram cart..... £18.14.6
- Covers for above..... £2.13.0
- Bases for above..... £3. 0.0
- AP75 less cartridge..... £19.19.0
- SL75 less cartridge..... £25.19.6
- SL95 less cartridge..... £28.19.6
- Bases for above..... £4.19.6
- SPECIAL OFFER!**
- SR25 less cart., with base..... £18. 2.6
- P. & P. Decks 12/6, Cover 4/6, Base 4/6.
- P. & P. Deck/Cover/Base 17/-

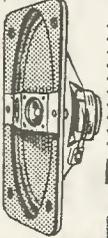EMI COMBINATION LOUSPEAKERS. 131 x 81in. elliptical with two 2 1/2in. tweeters. 15 ohm impedance. Power handling 10 watts. Brand new and guaranteed. 99/6. P. & P. 7/6. (Also available without tweeters. 59/6. P. & P. 7/6.)



"HI-FI" LOUSPEAKER British made full range 10in. unit handles up to 10 watts. Ceramic magnet. Freq. response: 40-10,000 cps. Imp: 15Ω. Flux density: 10,000 lines. 49/6. P. & P. 4/6.



SOLDERING GUN Comfortable grip with trigger control. "U" shaped 3/16in. bit to minimise wear. Light beam is automatically directed on to end of bit when ON/OFF trigger is in use. 230-250 volts. 85 watt element. 49/6. P. & P. 3/6.

"ADASTRA" SOLDERING IRON. 30 watt. Employs its protective cover as a handle. AC 230/250v. With 4ft. lead. 12/6. P. & P. 2/6.



NEW-VHF AIRCRAFT BAND CONVERTER. When placed within lin. of a MW band radio full coverage of VHF Aircraft Band 108-135Mc/s. can be obtained. All transistor. 9v battery operation. Fully tunable 13 1/2in. x 7 section telescopic aerial. Size 4 2/3 x 1 1/2in. 79/6. P. & P. 3/6.


STEREO AMPLIFIERS

ORAL STEREO AMPLIFIER MODEL TS-185. SOLID STATE. 18 TRANSISTORS.



13.5 watts per channel. Free standing unit with black crackle case and satin alloy front panel. Specification: Frequency range 30cps to 20Kcs (+3dB). Harmonic distortion 2% at 10 watt (1Kc). Cross talk 45dB at 1Kcs. Signal to noise ratio 60dB. Inputs: Aux. 100mV, Phono 3mV, Tuner 150mV, Tapehead 4mV. Tone controls: Treble 10Kcs at ±10dB. Loudness (medium frequency cut). Output impedance 8 ohms. Mains operated. Size 4 1/2 x 6 1/2 x 12 1/2in. Price £26.5.0. P. & P. 9/6.

DULCI STEREO AMPLIFIER MODEL 207

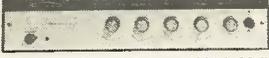

8 watts per channel. Integrated high fidelity transistor Stereo amplifier. An attractive free standing unit with provision for mounting in equipment cabinet. Finish Dark Grey vinyl simulated leather grain. Front panel satin alloy. Specification: Sensitivity. Radio/Tape 100mV into 1Mohm. Phono 100mV into 1Mohm. 3 position selector on front panel. Frequency response: 40c/s to 16Kc/s ±2dB. Separate bass and treble controls with boost and cut, balance control, Mono/Stereo Function switch (both channels work in parallel). Normally £23.2.0. LIND-AIR PRICE £19.19.0. Plus P. & P. 9/-.

SPECIAL PURCHASE!

DE-LUXE STEREO HEADPHONES




With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000cps. With lead and stereo plug. Only 59/6. P. & P. 3/6.

NEW STEREO/MONO HEADPHONES



SDH-7. Soft rubber earpieces with slide switch for mono or stereo listening and ind. vol. controls. Impedance 8-16 ohm. Freq. response 25-15,000 cps. With lead and stereo plug. £8.8.0. P. & P. 3/6.

S-DeC BREAD BOARD

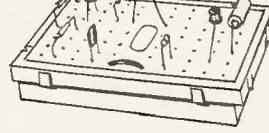

Solderless breadboard panels, for fast reliable component connections. Single DeCs. One S-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DeC" giving construction details for a variety of circuits. 29/6. P. & P. 2/6.

4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. £5.17.6. P. & P. 3/6.

HI-TONE RECORDING TAPE

BRITISH MADE. TOP QUALITY		
J1001	3" Long Play PVC	235ft. 5/6 P. & P. 1/2.
J1002	3" Triple Play PVC	600ft. 10/6 P. & P. 1/2.
J1003	5" Long Play PVC	900ft. 10/- P. & P. 1/8.
J1004	5" Double Play Poly	1200ft. 15/- P. & P. 1/8.
J1005	3 1/2" Long Play PVC	1200ft. 15/6 P. & P. 2/-.
J1006	3 1/2" Double Play Poly	1800ft. 22/6 P. & P. 2/-.
J1007	7" Standard Play PVC	1200ft. 12/6 P. & P. 2/6.
J1008	7" Long Play PVC	1800ft. 17/6 P. & P. 2/6.
J1009	7" Double Play Poly	2400ft. 25/- P. & P. 2/6.
J1010	7" Triple Play Poly	3600ft. 50/- P. & P. 2/6.

NEW TRANSISTOR MODULES

E.1311. PHONO PRE-AMPLIFIER. Size 2 x 1 x 1/2in. Built-in R.I.A.A. characteristics enabling low output magnetic pick-up cartridges to be amplified up to 1 volt. Input 100Kohm: Gain 28dB: Max. output 3v: Max. input 50mV. Distortion 0-15% (at 1v level). Power supply 9-12v. 29/6. P. & P. 2/-.

E.1312. DUAL LAMP FLASHER. Enables a low output microphone to be used with an amplifier or radio. Input imp. 100Kohms: Gain 28dB: Max. output 3v: Max. input 50mV: Distortion 0-15% (at 1v level): Freq. response 10Hz-50KHz. Power supply 9-12v. 29/6. P. & P. 2/-.

E.1313. ELECTRONIC ORGAN TONE OSCILLATOR. Used in conjunction with an organ keyboard, variable resistances and a 9 volt power supply, this module acts as the oscillator unit for an electronic organ. Tone Frequency: 200-1,000Hz: Output 80mW: Current 15mA. 25/- P. & P. 2/-.

E.1314. POWER AMPLIFIER. When used in conjunction with E.1311, E.1312 and E.1313 units this amplifier module produces about 300mW output for speaker connection (8-16 ohms), without necessity for an output transformer. Input imp. 1,000 ohms: Gain 20dB: Output 300mW: Distortion 3% (at 200mW output level). Freq. res. 50Hz-10KHz. Power supply 9v. Current 20mA at no signal, 80mA at max. output. 29/6. P. & P. 2/-.


E.1317. MINIATURE MORSE TRANSMITTER. Will transmit to any adjacent AM Receiver, also makes a useful oscillator for trouble shooting. Audio tone 400c/s. Radio frequency range 400c/s to 30Mc/s. Power supply 9v DC. Current 35mA. 25/- P. & P. 2/-.

E.1312. TAPE PRE-AMPLIFIER. Incorporating N.A.R.T.B. curve characteristics, this amplifies tape head signals up to 1 volt within the frequency range of 30Hz-15KHz. Input imp. 100Kohm: Gain 25dB: Max. output 2v: Max. input 50mV: Distortion 0-15% (at 1v level): Power supply 9-12 volts. 29/6. P. & P. 2/-.

E.1316. MORSE CODE OSCILLATOR. A transistorised morse code oscillator (buzzer) to be used in conjunction with an operating key. Suitable for direct connection to a loudspeaker. Tone freq. 400Hz: Power output 80mW: Power supply 3-9v: Current 45mA. 25/- P. & P. 2/-.

Visit our Brand New Hi-Fi Demonstration Room, Tape Bar, Scientific Show of Microscopes, Binoculars, Telescopes also Watches at 18 Tottenham Court Road

COMPACT 2-WAY INTERCOMS

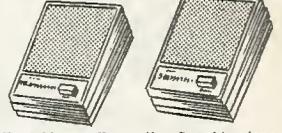

For table or wall mounting. Smart two tone grey cases size 8 1/4 x 2 1/2in. Complete with lead, staples and 9v battery. 55/- P. & P. 3/6.

LIGHT DIMMER AND SWITCH

600 watts. 250 v. Fully suppressed complete with control knob and fully assembled, less casing. Will fit most electrical fittings. Uses 4 silicon rectifiers. 2 transistors and 1 thyristor. Many other uses. £3.15.0 P. & P. 2/-.

MODEL MAKER'S MOTOR No. 15RN. Voltage 11.5v. Current 400mA. Torque 12g-cm. Body size 1 1/2" long x 1" dia. Shaft 1/16" long x 1/16" dia. Ideal for small models and toys. 5/8 each. P. & P. 1/3. 3 for 15/- P. & P. 2/6.

NEW TRANSISTOR CHECKER. For measuring alpha, beta and Ico factors of transistors also for checking germanium and silicon diodes. Internal 9v battery. Wide reading scale. Moulded case size 7 x 4 x 8 1/2in. Ranges: Alpha 0.7-0.9967; Beta 0-300; Ico 0-50,000A. Diode test: forward and 200 ohm-1 megohm. Complete with reverse internal resistances and instruction booklet. £7.19.6. P. & P. 3/6.

SHIRA 62D MULTI-TESTER 20,000 o.p.v. DC voltage: 5-25-50-250-500-2.5K (20,000 ohms per volt). AC Voltage: 10-50-100-500-1000 volts (10,000 ohms per volt). DC Current: 0-50μA, 0-2.5mA, 0-250mA. Resistance: 0-6K, 0-5Mg (300 ohm and 80K at centre scale). Capacitance: 10pf. to .001 mfd., .001μf to .1μf. Decibels: -20 to +22dB. Size 4 1/2 x 3 1/2 x 1in. Complete with case 77/- P. & P. 3/6.

TTC.C1001 MULTITESTER in leather case. 20,000 o.p.v. AC volts 10, 50, 250, 1,000v. DC volts 5-25, 125, 500, 2500v. D.C. Current 0-50μA, 0-250mA. Resistance 0-60K, 0-6 Megohm. Decibels -20 to +22dB. Size of meter 4 1/2 x 3 1/2 x 1in. 55/- P. & P. 3/6.

NEW-SINCLAIR IC-10 INTEGRATED CIRCUIT 10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years. ONLY 59/6. P. & P. 1/8.

LIND-AIR OPTRONICS LTD

18, 25 & 53 TOTTENHAM COURT ROAD, LONDON W.1.

Telephone: 01-580 2259/4532/7679

Shops open 9-6 pm. Monday to Saturday. Thursday until 7 pm.

ALL MAIL ORDERS To Dept. PE 669 54a Tottenham Court Road, London, W1.

EXCEL

in

ELECTRONICS

Through this ICS 3-way Training Method:

1

MASTER THE THEORETICAL SIDE

From basic principles to advanced applications, you'll learn the theory of electronic engineering, quickly and easily through ICS. That's because each course is set out in easy-to-understand terms.

2

MASTER THE PRACTICAL SIDE

ICS show you how to develop your practical abilities in electronic engineering—alongside your theoretical studies. It's the only sure way to success. All training manuals are packed with easy-to-follow illustrations.

3

MASTER THE MATHEMATICAL SIDE

To many this aspect is a bitter problem. Even more so because no electronic engineer is complete without a sound working knowledge of maths. But new ICS teaching makes mathematics easier to learn.

Wide range of courses available include:

Radio/TV Engineering and Servicing, Closed Circuit TV, Electronics, Electronic Maintenance, Servomechanisms, Computer Engineering, Numerical Control Electronics, etc.

EXPERT COACHING FOR:

INSTITUTION OF ELECTRONIC AND RADIO ENGINEERS
CITY AND GUILDS TELECOMMUNICATION TECHNICIANS
CITY AND GUILDS ELECTRONIC SERVICING
R.T.E.B. RADIO/TV SERVICING CERTIFICATE
RADIO AMATEURS' EXAMINATION
P.M.G. CERTIFICATES IN RADIOTELEGRAPHY

Build your own radio, transistor portable, and professional-type test instruments with an ICS Practical Radio and Electronics Course. Everything simply explained and easy to handle. All components and tools supplied. For details post coupon below.

Member of the Association of British Correspondence Colleges

FOR **FREE** HANDBOOK · POST THIS COUPON TODAY

I.C.S., Dept. 151, INTERTEXT HOUSE,
STEWARTS ROAD, LONDON, S.W.8

NAME

ADDRESS

OCCUPATION..... AGE.....


INTERNATIONAL CORRESPONDENCE SCHOOLS

XCELITE

Precision made hand tools
for the professional



74CG

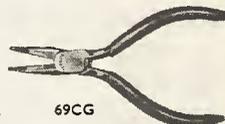


69CG

PLIERS


69CG Radio-TV Pliers
70CG Flat Nose Pliers
71CG Round Nose Pliers

72CG Chain Nose Pliers
73CG Tip Cutting Pliers
74CG Diagonal Close Cutting Pliers

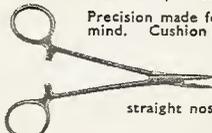A complete range of miniature lightweight pliers especially designed for holding, bending, shaping and cutting of fine wires in electronic, Radio/TV, electrical and jewellery work.



straight nose

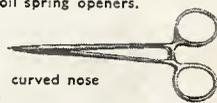

curved nose

SEIZERS

32H 5" Straight Nose Junior 5" Seizer
35H 5" Curved Nose Junior 5" Seizer

42H 6" Straight Nose Seizer
43H 6" Curved Nose Seizer

Box joint construction, two position snap on lock. Precision machined from perfectly tempered steel. Holds like surgical clamp and acts as heat sink. Straight or curved nose, in 5" and 6" sizes.

Distributed by

Special Products Distributors Limited

81 Piccadilly, London, W.1

Tel. 01-629 9556

Cables: SPECIPROD, London, W.1

Full details an request

Made in U.S.A.

WEL'S FARGO now ship E line transistors from Ferranti



E line epoxy transistors include low cost, general purpose amplifiers and switches, high speed switches, neon drivers and low noise VHF amplifiers.

NPN and PNP complimentary types are available for most functions.

Further data and ex stock delivery from:

WEL Components Ltd

5 Loverock Road · Reading · Berks · Tel: Reading 580616-9 · Telex 84529
Ministry of Technology approved distributor.



UNLIMITED!

A selection of readers' suggested circuits. It should be emphasized that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merit.

SPOT ON

THE CIRCUIT in Fig. 1 was designed as a gimmick for a dance, the idea being to have a spotlight directed on to a doorway, so that whenever people walked in or out the spot came on.

With a light focused across the doorway on to a ORP12 light dependent resistor, the resistance is low and insufficient voltage is available to trigger the thyristor SCR2. When the light beam is interrupted the change in resistance value is sufficient to trigger the thyristor. The firing point of the thyristor is controlled by VR2.

If the lamp (load) is allowed to switch from the off to on state rapidly it would have a very short life span, and components R1, C1, D1, VR1, and SCR1 are included in the circuit to protect the lamp. This timing circuit is set by VR1 so that when SCR2 is in the off state the lamp is glowing as dimly as possible, thus when the light beam is interrupted the light flashes from "just-on" to "full-on". This keeps the lamp filament hot enough to prevent large surge currents from flowing.

The photo-beam was provided by a 4.5V 0.5A bulb, powered by a mains transformer, housed in a torch case. The transformer was just small enough to fit into the battery compartment.

The circuit can also provide a "strobe" effect simply by pointing the ORP12 at the controlled light. This sets up a form of feedback and the speed can be varied by VR1 and VR2.

Resistor R2 was placed across VR2 because it was found that VR2 has a tendency to change resistance due to heating, leaving the light permanently on.

A. K. Draper,
Norton St. Philip,
Bath.

TIME SWITCH

NEARLY four years ago I made the clock with the cold cathode numeral indicator tubes as described in PRACTICAL ELECTRONICS.

After a year I had trouble with worn contacts on the first digit single pole 10-way switch, which I replaced with a new one (this switch makes and breaks nearly $\frac{1}{2}$ million times a year!).

I have now substituted a rotary switch made from 10 dry reed switches, type 6-RRS, length 1.45in \times 0.125in diameter. The reed switches are mounted between two perspex discs with a permanent magnet Araldited to the spindle of an old volume control, see below.

As these reed switches are good for 10^8 operations, the estimated life of my clock is now over 2,000 years!

D. B. Pearce,
Abbey Wood,
London, S.E.2.

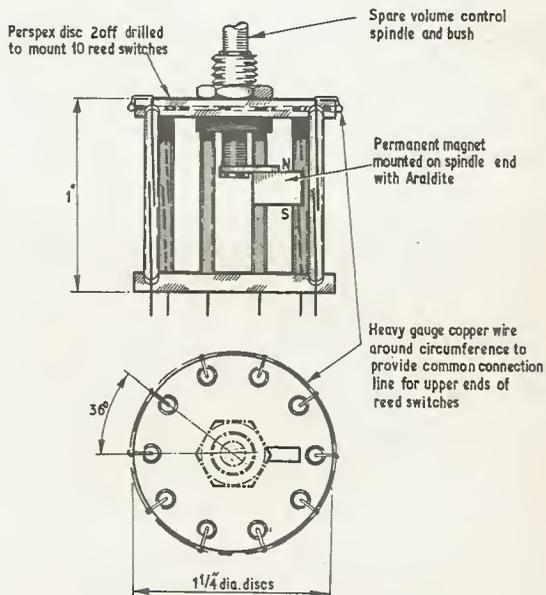


Fig. 2. Single-pole, 10-way reed switch

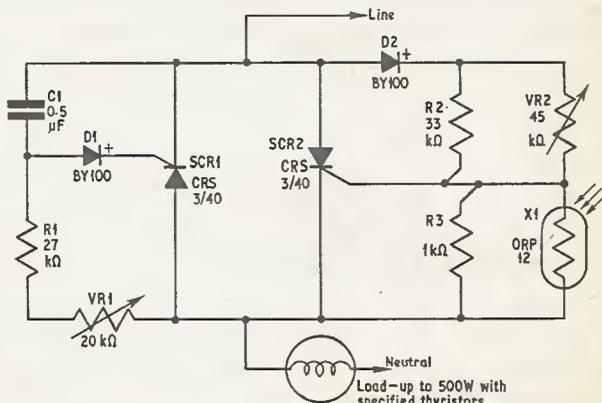


Fig. 1. Automatic spotlight control switch

BASS-MAKER

THE circuit was designed and built for a 6-string "lead" guitar to produce bass guitar notes.

This bass conversion cannot be done satisfactorily using filtering techniques, but must involve frequency division. In this case, the basic string frequencies are effectively halved.

This is achieved by converting the fundamental signal into a pulse train whose p.r.f. (pulse repetition frequency) is equal to fundamental frequency. This pulse train is made to drive a bistable switch, so that the bistable makes one change of state for each input pulse. Since two changes of state in the bistable constitute a complete cycle, it is seen that two pulses in, produce one cycle output. When this square wave train is filtered to remove the unwanted harmonics it can sound remarkably like the true bass sound.

The only, perhaps major, limitation of the device is its inability to cope with a very complex input signal, i.e. this must be predominantly fundamental in nature. For example: one guitar note only must be injected at a time. Two or more produce an erratic bistable drive train, and in general, a "grating" noise at the output.

It is interesting to note that, when using a microphone input, singing or talking produced the grating output (additional to that already present) whilst the human whistle, nearly sinusoidal in form, was nicely lowered an octave, losing, however, its characteristic tone.

DESIGN NOTES

The component values given were arrived at by design and must be considered only as a guide for any adventurous constructors see Fig. 3.

The resistors marked with an asterisk must be found by experiment since they control the base currents of TR1, TR2, TR3 and TR4 and will vary considerably in value between transistors of the same type due to the gain spread. If 6 volts is chosen as the supply voltage, then R3 is adjusted so that TR1 collector is quiescent at about 3V. Resistor R5 is adjusted so that TR2 emitter is quiescent at about 3V, but should be fairly low around 2 kilohms to maintain a low output impedance for TR2.

Resistor R7 is adjusted so that TR3 collector is quiescent at about 5.5V. R10 is adjusted so that TR4 collector is quiescent at about 1V. Transistor TR5 is not biased but acts as a grounding switch for D2 and D3, the bistable steering diodes. R9 is used to "stop" oscillations, but may not be necessary where lower gain devices are used, or where layout is improved. It was found easier to use this resistor rather than decoupling.

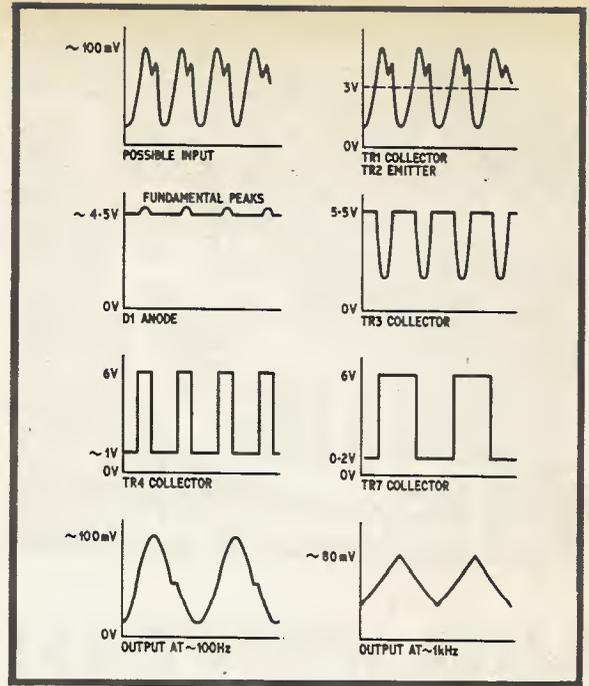


Fig. 4. Wave shapes at different stages of the circuit

Negative feedback in the form of resistance in the emitter, or from collector to base of TR3 and TR4 must be avoided, since such feedback causes spikes on the drive pulses, which can cause malfunction of the bistable. The waveforms shown in Fig. 4 should be observed at the stated points when the circuit is operating correctly.

The amplitude of output is maintained nearly constant over the guitar frequency range due to the use of the low "Q" filter C7/L1. A high resistance (1kΩ) iron cored coil (from a relay) was tuned by increasing the value of C7 until the correct sound was obtained using the guitar 6th string. The bass sound is obtained over a restricted range, but is quite acceptable even on the fourth string.

Resistor R17 reduces the loading on the bistable and attenuates the 6V signal to 100mV. Total quiescent current drain is approximately 4mA. To set up the circuit for use, adjust VR1 until only the fundamental is amplified by TR3.

P. E. Clancy,
Ashton-under-Lyne.

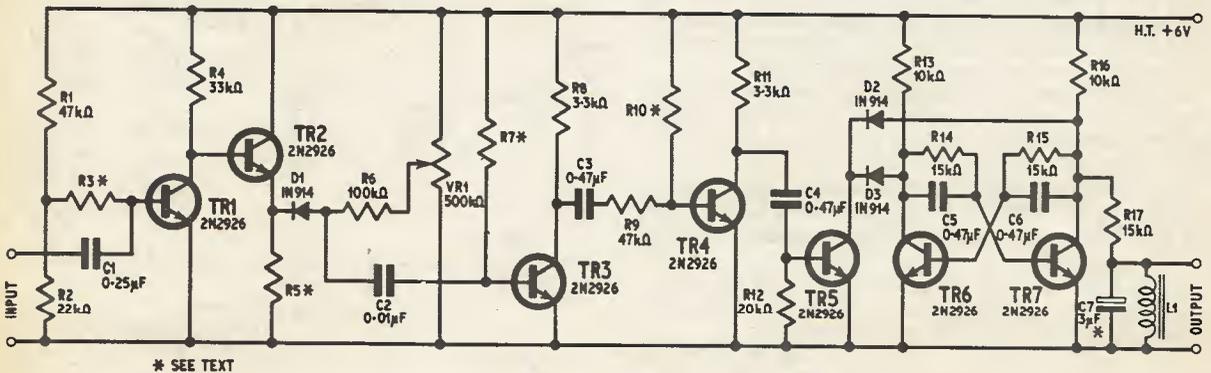


Fig. 3. Circuit diagram of the guitar bass-maker

PROTECT VALUABLE DEVICES




From thermal run-way or overheating. Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected; simply make the contact thermostat part of the heat-sink. Motors and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90°-190°F. or with the dial removed range setting is between 80 to 800°F. Price 10/-.

ROTISSERIE MOTOR




Very powerful 7 r.p.m., operates from standard AC Mains. 29/6, plus 3/6 P. & P.

230 VOLT SOLENOID

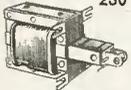


1/2 in. stroke, size 2 1/2 in. x 2 in. x 1 1/2 in. 14/6, postage 2/9.

See in the Dark INFRA-RED BINOCULARS

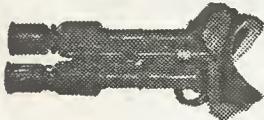

These infra-red binoculars when fed from a high voltage source will enable objects to be seen in the dark, provided the objects are in the rays of an infra-red beam. Each eye tube contains a complete optical lens system as well as the infra-red cell. These optical systems can be used as lenses for TV cameras—light cells, etc. (details supplied). The binoculars form part of the Army night driving (Tabby) equipment. They are unused and believed to be in good working order but sold without a guarantee. Price £3.17.6, plus 10/- carr. and ins. Handbook 2/6.

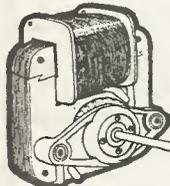

MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blower, heater, etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.

16 RPM GEARED MOTOR

Made by Smith's Electrics, these are almost silent running, but are very powerful. They operate from normal to 240V. mains and the final shaft speed is 16 r.p.m. 15/-. Post & ins. 2/9.


MINIATURE WAFER SWITCHES



4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 3/6 each. 36/- dozen, your assortment.

WATERPROOF HEATING ELEMENT

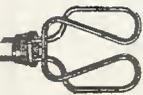26 yards length 70W. Self-regulating temperature control. 10/- post free.




KETTLE ELEMENT

230/240V 1500 watt. Made by Best for kettles with 1 1/2 in. dia. hole including: Best, Bescor, Chalfont, Davidson, Dimplex, Grafton, Hawkins, Monogram, Pico, Revo, Town, Swan. Normally 32/6. Our price 15/- plus 2/6 post.

AC FAN

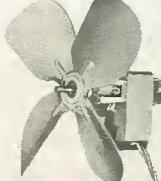Small but very powerful mains motor with 4 1/2 in. blades. Ideal for cooling equipment or as extractor. Silent but very efficient. 17/6, post 4/6. Mounts from back or front with 4BA screws.



ELECTRIC CLOCK WITH 25 AMP. SWITCH

Made by Smith's these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.



DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. 19/6 plus 2/6 post and insurance. Or available made up 29/6, plus 2/6 post.



HI-FI BARGAIN

FULL FI 12 INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for HI-FI load and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S.—Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—specify 3 or 15 ohms—Main resonance 60 c.p.s.—Chassis Diam. 12in.—12in. over mounting lugs—Baffle hole 11in. Diam.—Mounting holes 4, holes—1in. diam. on pitch circle 1 1/2 in. diam.—Overall height 5 1/2 in. A £6 speaker offered for only 23.9.6 plus 7/6 p. & p. Don't miss this offer. 16", 30 watt £7.19.6.



THIS MONTH'S SNIP G.E.C. 13A SOCKETS



Opportunity to re-equip your house or workshop, or if a contractor, to stock up for future jobs. We offer bakelite 13A sockets for flush or surface mounting made by the famous G.E.C. company and listed at 6/6 each. YOU CAN HAVE A BOX OF 12 flush type 24/-, surface type 29/6, post and ins. 4/6. (Gross or more carr. free.)

TIME AND SET SWITCH



Made by Smiths, motorised and mains driven, enables 15A circuit to be started up to 16 hours in advance and to stay on for a period from 15 minutes to 3 hours. Totally enclosed in metal box with glass front and chrome surround. 49/6 plus 4/6 post and ins.

NICAD RECHARGEABLE BATTERIES



3-6V 500mA size 1 1/2 x 1 1/2 in. dia. type ref. DKZ500 really powerful will deliver 1 amp for 1/2 hour. Regular price 22/6 our price 17/6 each. New and guaranteed. Other voltages available, single cell 1.2V 6/6, 5 cell 6V 29/6.

LAST CHANCE FOR THIS BARGAIN



CASSETTE LOADED DICTATING MACHINE

Battery operated and with all accessories. Really fantastic offer a British made £31 outfit for only £24.19.6, brilliantly designed for speed and efficiency—cassette takes normal spools, drops in and out for easy loading—all normal functions—accessories include: stethoscopic earpiece—crystal microphone has on/off switch—telephone pick-up—DON'T MISS THIS UNREPEATABLE OFFER—SEND TODAY, £4.19.6 plus 7/6 post and insurance. Footswitch 18/6 extra. Spare Cassettes at 4/6 each, three for 10/-.

FOR ONLY 99/6.

—telephone pick-up—DON'T MISS THIS UNREPEATABLE OFFER—SEND TODAY, £4.19.6 plus 7/6 post and insurance. Footswitch 18/6 extra. Spare Cassettes at 4/6 each, three for 10/-.


REPAIRABLE RADIOS

7 transistor Key chain Radio in very pretty case, size 2 1/2 x 2 1/2 x 1 1/2 in.—complete with soft leather zippered bag. Specification—Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1600 Kcs. Sensitivity: 5 mv/m. Intermediate frequency: 465 Kcs, or 455 Kcs. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. These radios are complete but require attention. Circuit diagram is not available. 17/6 each plus 2/9 post and insurance. 4 radios 23 post free.



VARYLITE

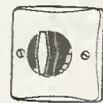Will dim incandescent lighting up to 600 watts from full brilliance to out. Fitted on M.K. flush plate, same size and fixing as standard wall switch so may be fitted in place of this, or mount on surface. Price complete in heavy plastic box with control knob £3.19.6.



INDICATOR LAMP

Panel mounting, consists of neon lamp in red Plastic lens with resistor in leads for mains operation 2/6 each, 24/- doz.



12V BLOWER

Heavy duty motor with centrifugal blower coupled to one end. Ideal for car heater. 12/6 plus 4/6 post.

TELESCOPIC AERIAL



for portable, car radio or transmitter. Chrome plated six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 7/6.

MOVING COIL METER BARGAIN

Panel meters are always being needed and they are jolly costly when you have to buy them in a hurry—so you should take advantage of this offer: 2in. moving coil flush mounting meters only 9/6. These are actually R.F. meters and cost about £3 each but if you don't want them for R.F. then all you have to do is to remove the thermocouple and you will have a 2-3 mA meter which you can make into almost anything by adding shunts or series resistor. New and unused.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6V, 9V, 12V for up to 500mA (Class B working). Takes the place of any of the following batteries: P21, P23, P4, P6, P7, P9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 18/6, plus 3/6 postage.

REED-SWITCH

Suitable for dozens of different applications, such as burglar alarms, conveyor belt switching. These are simple glass encased switches which can be operated by a passing permanent magnet coil. A special buy enables us to offer these at 2/6 each, or 24/- dozen. Suitable magnets are 1/- each.

MINIATURE RELAY

American make—630 ohm coil 20-30 volt operation—2 pole changeover 4/6 each, 48/- dozen.

SPRING COIL LEADS



as fitted to telephones, 4 core 2/6 each, 3 core 2/- each.

5A, 3 PIN SWITCH SOCKETS

An excellent opportunity to make that Dench disc board you have needed or to stock up for future jobs. This month we offer 6 British made (Hicraft) bakelite flush mounting shuttered 5A switch sockets for only 10/10 plus 3/6 post and insurance. (20 boxes post free.)



QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. 19/6, post and insurance 1/6. 12v. car model also available.



MISCELLANEOUS ITEMS


Headphones. Ex-W.D. unused and perfect, single with headband 4/6. Double with headband 6/6. Multi Purpose Neon Test Unit. Robust, useful and instructive, tests insulation, capacity, continuity, resistor, volume controls, also acts as signal injector, and L.T. fault finder, kit comprises neon indicator, 4-way wafer switch, ebonite tubes, resistors-condensers, terminals, etc., with diagram, only 9/6 plus 1/6 post and insurance. Tuning Condenser. Solid dielectric, .0005 mfd. variable 2/6 each, 24/- dozen. A.E.I. Fractional H.P. Motor. 200/250V 50/60c/s enclosed, continuous rating 1/40 h.p., ex. equipment. Perfect order, 19/6, plus 4/6. Experimenting with ultra violet? Philips U.V. lamp, 18/6; holder and control gear 19/6. G.E.C. Black Light Tube for experiments and special lighting effects—40 watt 2ft. tubes only 14/6 each; holders and control gear, 19/6, plus 4/6 post. Clock Motor. 230V 50c/s synchronous—self-starting, 6/6. Pentode Output Transformer. Standard size, 40-1, ex-equipment but OK, 4/3 each, 48/- doz. Post paid. E.H.T. Condenser. 0-1 mfd. 5kV, 8/6 each. Neon Mains Tester, 1/8 each, 12/- doz. Flood Lamp Control. Our dim and full switch is ideal for controlling photo flood lamps; it gives two lamps in series, two lamps full brilliance and lamps off. Similar control of other appliances can be arranged where used in pairs or where circuit can be split exactly in half. Technically the switch is known as a double-pole changeover with off. Our price 4/6. Sub-Miniature Silicon Diodes. General purpose type with gold-plated leads, 1/- each or 7/6 per dozen.

Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

ELECTRONICS (CROYDON) LTD.

Dept. PE, 266 London Road, Croydon CRO-2TH

Also 102/3 Tamworth Road, Croydon

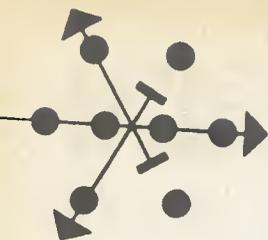

THE PHYSICS EXHIBITION

IN AN exhibition of this kind it is impossible to detect a dominant theme, since it is concerned with the unique display of several developments, from ideas to final production. (The Physics Exhibition, sponsored annually by the Institute of Physics and Physical Society, was held at Alexandra Palace, London, from March 10 to 13.) Out of this event, commercial concerns cannot expect to reap immediate financial rewards. However, it is frequently forgotten that, if it were not for the "back-room seeds-men", many companies would not have any produce to take to market.

The field of technical knowledge covers several acres but the harvest depends largely on the applications to human needs. Typical here is the growing quest for diagnosis and treatment of diseases, in which several branches of physics technology can plough through the problems.

HIDDEN CONTOURS REVEALED

It should come as no surprise to many that holography is an obvious choice in showing three-dimensional views of internal human organs, as opposed to the two dimensions from x-ray plates. Some indication of proportions and contours can become apparent—a breakthrough in diagnostic interpretation. This work is being carried out at A.W.R.E., Aldermaston.

The Acoustics Group of the Institute held a collective display of acoustic and ultrasonic techniques in collaboration with organisations concerned with medical research. Of particular interest was the ultrasonic transducer "Diasonograph" which makes two dimensional scans of, among other organs, the liver. The transducer is moved over the surface of the skin and, using liquid paraffin as a couplant, provides pulse echo information from the liver area to modulate the brightness of a cathode ray tube beam.

Although potentially valuable in finding abnormal shapes due possibly to foreign growth, this method has so far presented difficulties in applications, due to natural variations between individuals in the transmission loss of the anterior abdominal wall.

These variations can reduce diagnostic accuracy, but suspicions of diseases, such as cirrhosis, cancer, and cyst, can help localise and concentrate further investigation on a reasonably sound basis. This work is sponsored by the Medical Research Council with the Board of Governors of United Bristol Hospitals.

CLOSE STUDY IN SCHOOLS

The experimental and close study techniques employed by university laboratories has been attracting the interest of secondary grade schools (with sufficient financial incentive) enough to encourage basic research work in science projects. Consequently it is encouraging to see an enlarged section devoted to school projects and educational techniques at most levels.

Typical in this group is the belief by The King's School, Gloucester, that a precision, frequency locked, electronic counter can be made a basic laboratory instrument, operating at 100kHz, for accurate time and frequency measurement, temperature and electrical resistance, inductance and capacitance measurement. The system developed at this school uses comparison techniques, whereby the oscillator frequency is made the analogue of the parameter under investigation. The actual counter is the means of measuring this frequency.

Watch out for next month's Practical Electronics

CHROMATONE

A thyristor controlled lighting effect unit that can be used with any sound source from a transistor radio to an electric guitar or organ. This portable mains operated unit is particularly suitable for pop groups since it can supply bulbs of up to 750 watts total output on each of its three channels. The intensity of each channel and of the whole display are variable.



OPTICAL REMOTE CONTROLLER

A simple visible light transmitting and receiving system which can be used to control various electronically or electrically operated devices.

PRACTICAL ELECTRONICS

July issue on sale Friday June 13
order your copy now 3/-

Readout —

A SELECTION FROM OUR POSTBAG

correspondents wishing a reply must enclose a stamped addressed envelope

The right level?

Sir—As a regular subscriber to PRACTICAL ELECTRONICS for the past 18 months, I should like to offer some criticism (more praise really) and suggestions, which I hope you may find of interest.

Firstly, a word of praise for your subscription department and general publishing policy. It is much appreciated that overseas subscriptions do not cost more than at home, and that the magazine reaches me here no later than it appears on the newsstands at home. My special thanks, incidentally, for sending on any free gifts at no extra charge—the same can, unfortunately, not be said of many U.K. publishers.

With regard to the magazine itself, I hope you will continue to steer clear of television and radio topics, and in particular of amateur radio. This latter field surely has outlets enough as it is, and the "fraternity's" peculiar love of esoteric abbreviations and home-brewed jargon can make a non-enthusiast's teeth grind.

Through my work, and also through acquaintances, I manage to see most of the amateur "electronics" magazines published in Europe, plus a few of U.S. origin, and I honestly think that yours is the best. This is because, I believe, you have managed to hit on exactly the right level of technical "difficulty" in your practical projects, which are also almost always eminently practical.

This is not intended to imply that I am not in favour of articles such as the recent series on *Bionics*, which I consider to be an excellent idea.

G. J. Phillips,
The Hague,
Netherlands.

... talking of *Bionics*, here are two photos taken from the TV screen during transmission of the Southern Television programme "HOW" a few weeks ago. Our author G. C. Brown is shown demonstrating one of his electronic animals which is shown in close-up in the second picture

Aroused from the chair!

Sir—I have just finished reading my first copy (April 1969) of PRACTICAL ELECTRONICS—prompted by the advertisement in PRACTICAL MOTORIST—and I am most impressed!

Indeed, it has re-awakened my interest in electrical gadgetry. I'm sure your editorial was aimed at me since this browser and second time beginner is about to become a "doer".

I found the constructor's guide supplement most useful—especially the construction materials (I've seen transistors and printed circuits of course, but I hadn't realised it was so readily available to the amateur) and the circuit symbols.

The article *Theory into Practice* is also very useful—comprehensible without being over-simplified, and the *Pocket Radiation Monitor* was most interesting, since I am an X-ray technician, but far too expensive for the amount of radiation I am exposed to, but invaluable to industrial technicians I think.

A little adverse criticism now if I may... I personally would find it very useful if the approximate total cost of materials was quoted in the components box as I am right out of touch with costs these days—and this would indicate whether the project was within spare cash range.

Thankyou for giving me a table-top hobby—it will be a change from being "under the bonnet" after the sun goes down.

B. P. E. Lawrence,
Smethwick,
Worcs.

Kits please

As a schoolmaster running an electronics club I find it difficult to obtain lots of components called for in your various plans and this is a cause for most boys giving up a project early.

Could you not come to some arrangement with some firms to supply a complete set of components as is done with some jobs in other magazines? This would make a lot more people take up the practical work, particularly your coming attraction of the Electronic Organ. I feel sure that the financial attraction would make component suppliers keen to go to some trouble to make up sets of parts to the magazine specifications so that one could order by post or go to one shop and know that the whole job could be purchased.

I am going to try and get the School to finance the making of the Electronic Organ and I do hope that my suggestion of suppliers might be carried out on this job and I feel sure that many more schools and individuals will "make the jobs" to the advantage of everybody concerned with the electronics industry.

S. Orford,
New Eltham,
London, S.E.9.


We would certainly like to see kits advertised, but this is really a matter for the component suppliers rather than ourselves. See this month's editorial comment—Ed.

Of considerable value

Sir—We would very much appreciate it if you could mention in your next issue that anyone who is interested in the British Amateur Electronics Club should contact the Hon. Secretary, Mr J. G. Margetts, 12, Adenfield Way, Rhoose, Barry, Glamorgan.

I would like to take this opportunity of congratulating you on an excellent issue and your supplement (April) will be of considerable value to experimenters, such as the members of the B.A.E.C.

C. Bogod,
Chairman, B.A.E.C.,
Penarth.

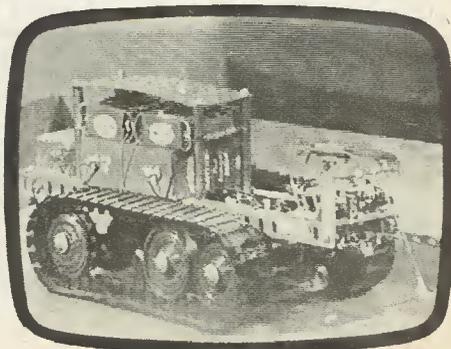

DE LUXE PLAYERS

PORTABLE CABINET Asilustrated. To fit standard 75/- player or autochanger.
RCS AMPLIFIER 3 WATT.
 Ready made and tested.
 This is a 2-stage unit using a triode penode condenser coupled valve, giving 3 watts output into a 3 ohm loudspeaker.
 Tone and volume controls mounted on chassis with knobs. Supplied with loudspeaker and valve UCL82. Frequency response 50-12,000 cps. Sensitivity 200mV. **59/6**



Post 5/6 each item

SINGLE PLAYERS MONO
 EMI Junior Mains £20.19.6
 Garrard SRP22 " " £20.19.6
 Garrard SP25 MkII £14.19.6

AUTOCHANGERS MONO
 Balfour Princess £25.19.6
 BSR Supersim UA25 £26.19.6
 UAT0 Transcription £12.19.6
 3000 Stereo/Mono £12.19.6

All fitted LP78 styli and pickup cartridge complete. Stereo/Mono pickups 20/- extra except 3000.

GARRARD TEAKWOOD BASE WB.1. Ready cut out for mounting 1025, 3000, SP25, AT60, etc. **65/-**
GARRARD PLASTIC COVER SPC.1. for WB.1 BASE. Durable fluted attractive appearance. **65/-**

DE LUXE STEREO GRAM CHASSIS V.H.F. MW. SW 19-50cm. SW 60-180cm. Magic eye, push buttons. 6 valve plus rect. Size 15 x 7 1/2 x 8in. high. 3.5A. S.A.E. **£22.10**

PICK-UP ARM Complete with ACOS LP-78 GP67 Stylus 29/6; KTAL GP67 17/6; Stereo Ceramic 35/-; Powerpoint 58 15/-

CRYSTAL MIKE INSERTS
 11 dia. in. 8/8; ACOS 131 in. dia. 9/6. BM3, 1 dia. 9/6
MOVING COIL MIKE with Remote Control Switch 19/6

PORTABLE TRANSISTOR AMPLIFIER PLUS DYNAMIC MICROPHONE

A self-contained fully portable mini p.a. system. Many uses - ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player, Amplifier, etc. Attractive resin covered cabinet, size 12 x 9 1/2 in. with powerful 7 in. speaker and four transistor one watt power amplifier plus ultra sensitive microphone. Uses PP9 battery. Brand new in Makers' carton with full makers' guarantee. World famous make. Only **90/-** Post Free



WEYRAD P50 - TRANSISTOR COILS

EA2W 6 in. Ferrite Aerial Spare Cores 6d.
 6 in. car aerial coil 12/6
 Driver Trans. LED74 9/6
 Osc. P50/1AC 5/4 Printed Circuit, PCA1 10/6
 I.F. P50/2CC 470 kc/s 5/7 J.B. Tuning Gang 9/6
 3rd I.F. P50/3CC 6/- Weyrad Booklet 2/-
 Telescopic Chrome Aerials 6in. extends to 23in. 5/-
 Ferrite Rods Only 8 x 1/4 in. 4/- 6 x 1/4 in. 5/-

VOLUME CONTROLS

Long spindles. Midset Size 5 K. Ohms to 2 Meg. LOC or LIN. 1/5 3/4. D.P. 5/-
STEREO L/S 10/6. D.P. 14/6
FRINGE LOW LOSS Edge 5K. S.P. Transistor, 5/-
IDEAL 625 lines yd. 1/6

VEROBOARD 0-15 MATRIX

2 1/2 x 5in. 3/8. 2 1/2 x 3in. 3/2. 3 1/2 x 3in. 3/8. 3 1/2 x 5in. 5/2
EDGE CONNECTORS 18 way 5/-, 24 way 7/6.
PINS 30 per packet 3/4. **FACE CUTTERS** 7/6.
 S.R.B.P. Board 0-15 MATRIX 2 1/2 in. wide 6d. per lin., 3 1/2 in. wide 9d. per lin., 5 in. wide 1/- per lin. (up to 17in.).
 S.R.B.P. undrilled 1 in. Board 10 x 8 in. 3/-

BLANK ALUMINIUM CHASSIS

7 x 4in. 5/6; 9 x 7in. 6/6; 11 x 9in. 6/6; 11 x 7in. 7/6;
 13 x 9in. 9/6; 14 x 11in. 12/6; 15 x 14in. 15/-

ALUMINIUM PANELS

18 s.w.g. 12 x 12in. 6/6; 14 x 11in. 5/6; 12 x 8in. 4/6; 10 x 7in. 3/6; 8 x 6in. 2/6; 6 x 4in. 1/6

Q MAX CHASSIS CUTTER


Complete: a die, a punch, an Allen screw and key
 1in. 18/- 1in. 17/6 1 1/2in. 18/6 1 1/2in. 24/- 2 1/2in. 44/3
 1in. 16/- 1in. 19/6 1 1/2in. 20/6 1 1/2in. 29/- 2 1/2in. 57/3
 1in. 16/9 1 1/2in. 19/6 1 1/2in. 21/6 1 1/2in. 39/- 2in. 57/6

"SONOCOLOR" CINE RECORDING TAPE

5" reel, 900' with LP strobe markings, also cine light deflector-mirror for synchronisation. 14/- each.
UNIVERSAL TAPE CASSETTES 600. THREE FOR 30/-

Tape Spools 2/8. Tape Splicer 5/-. Leader Tape 4/6.
 Reuter Tape Heads for Collaro models 2 track 21/- pair.

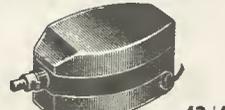"THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER



200/250 v. A.C. Leaflet S.A.E. Post 2/6 **42/6**

Minimum Post and Packing 2/6. RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME.

RADIO COMPONENT SPECIALISTS

List 1/-. Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-684 1665

BARGAIN STEREO/MONO SYSTEM

Attractive SIM PLAYER CABINET with B.B.R. Stereo Autochanger 4 + 4 AMPLIFIER and TWO matched 6 1/2 in. LOUDSPEAKERS. Carr. 10/6 **£19.19.6**
 (Only 4 pairs of wires to join.)

NEW TUBULAR ELECTROLYTICS
 2/350V .. 2/3 100/25V .. 2/-
 4/350V .. 2/3 250/25V .. 2/6
 8/450V .. 2/3 500/25V .. 4/-
 16/450V .. 2/3 8 + 8/450V 3/6
 32/450V .. 3/9 8 + 16/450V 3/9
 25/25V .. 1/9 16 + 16/450V 4/6
 50/50V .. 2/- 32 + 32/350V 4/6
SUB-MIN. ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 25, 30, 50, 100.
250V 15V 2/-; 500, 1000mF 12V 3/6; 2000mF 25V 7/-.
CERAMIC. 500V 1pF 0 to 0.01mF, 9d. Discs 1/-.
PAPER 350V-0.1 9d. 0.5 2/8; 1mF 3/-; 2mF 15/7 2/-.
500V-0.001 to 0.05 9d. 0.1 1/-; 0.25 1/8; 0.5 3/-
1.00V PANEL INDIC. 0.0047, 0.01, 0.02, 1/8; 0.047, 0.1, 2/8
SILVER MICA. Close tolerance 1/-; 5-500pF 1/-; 560-2,200pF 2/-;
2,700-5,800pF 3/6; 8,800pF-0.01, mid 6/-; each
TWIN GANG. "0-0" 208pF + 178pF, 10/8; 365pF, miniature 10/-; 500pF standard with trimmers, 12/6; 500pF midset less trimmers, 7/8; 500pF slow motion, standard 9/-; 500pF 1/2-range 500pF 19/6. Single, "0" 365pF 7/8. Twin 10/6.
SHORT WAVE. Single 10pF, 25pF, 50pF, 75pF, 100pF, 160pF, 200pF, 10/6 each.
TUNING. Solid dielectric. 100pF, 300pF, 500pF, 7/- each. TRIMMERS. Compression 30, 50, 70pF, 1/-; 100pF, 150pF, 1/3; 250pF, 1/8; 800pF, 750pF, 1/9; 1000pF, 2/6.

250V RECTIFIERS. Selenium 1/ wave 100mA 5/-; BY100 10/- CONTACT COILED 1/ wave 60mA 7/6; 85mA 9/6.
Full wave Bridge 75mA 10/-; 150mA 18/6; TV rect. 10/-.
WOUND PANEL INDIC. 0.0047, 0.01, 0.02, 1/8; 0.047, 0.1, 2/8
RESISTORS. Preferred values, 10 ohms to 10 meg. 1/2 w. 1/2 w. 1 w. 20% 3d.; 1 1/2 w. 8d.; 2 w. 1/-; 3 w. 10% 6d. HIGH STABILITY. 1/2 w. 10% 10 ohms to 10 meg., 2/-; Ditto 5%. Preferred values 10 ohms to 22 meg., 9d.
5 watt 0.5 to 8.2 ohm 3 w. 2/-
15 watt WIRE WOUND RESISTORS 2/-
15 watt 10 ohms to 6,800 ohms 2/-
10K, 15K, 20K, 25K, 68K, 10W, 3/-
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 amp, 8/9; 2a., 11/3; 4a., 17/6. CHARGER TRANSFORMERS. P. & P. 5/-.
Input 200/250v. for 6 or 12v., 1 amp, 17/6; 2 amps., 21/-; 4 amps., 30/-

WIRE-WOUND 3-WATT WIRE-WOUND 3-WATT POTS. T.V. Type. Values STANDARD SIZE POTS. 10 ohms to 30 K. LONG SPINDLE. Carbon 30 K to 2 meg. 4/6 50 OHMS to 100 K. 7/6

VALVE HOLDERS, 9d.; CERAMIC 1/-; CANS 1/-.

BRAND NEW TRANSISTORS 6/- each

OC71, OC72, OC81, OC44, OC45, OC171, OC170, AF117, REPANCO TRANSISTOR TRANSFORMERS.
 MAT 100 7/9; MAT 101 8/6; MAT 120 7/9; MAT 121 8/6.
 T45. Push Pull Drive. 8.1 CF, 6/-; T46 Output, CT81 6/-; T49. Interstage, 20V, 10/-; T52 Output 3 ohms, 4.5-1, 6/-; T53 4 VALVE 10 watt amp. Transformers and circuit 45/-
TRANSISTOR MAINS POWER PACKS. FULL WAVE 9 volt 500mA. Size 4 1/2 x 2 1/2 in. Metal case. 49/6
 Crackle finish. Output terminals On/off switch.
 Half Wave 9 volt 50mA. Size 2 1/2 x 1 1/2 in. Snap terminals 32/6
 9 volt 500mA. TRANSFORMER ONLY. 2 1/2 x 1 1/2 in. 10/8
BENCH POWER PACK 230-250V. A.C. £7
 With Meter for 6-8-12v. lamp D.C.

MAINS TRANSFORMERS

250-0-250 50 mA. 6.3 v. 2 amps, centre tapped 19/6
 250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 30/-
 350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 35/-
 300-0-300 v. 120 mA. 6.3 v. 4 a. C.T., 6.3 v. 2 a. 45/-
 MINATURE 200 v. 20 mA. 6.3 v. 1 a. 2/- 2 1/2 in. 12/6
 MIDGET 200 v. 45 mA. 6.3 v. 2 a. 21/- 2 1/2 in. 17/6
 HEATER TRANS. 6.3 v. 1 1/2 a. 8/6; 6.3 v. 4 a. 12/6
 Ditto tapped sec. 1.4 v., 2, 3, 4, 5, 6.3 v. 11 amp. 12/6
GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2a. 30/-
1 amp, 8, 9, 10, 12, 15, 18, 20, 24, 30, 35, 40, 48, 60, 75
AUTO TRANSFORMERS 0-115-230 v. Input/Output, 60w. 18/6; 150w. 30/-; 500w. 92/6; 1000w. 175/-

COAXIAL PLUG 1/3. PANEL SOCKETS 1/3. LINE 2/-

OUTLET BOXES. SURFACE OR FLUSH 4/6.
BALANCED TWIN FEEDERS 1/- yd. 80 ohms or 300 ohms.
JACK SOCKET Std. open-circuit 2/6, closed circuit 4/6;
Chrome Lead Socket 7/6. Phone Plugs 1/3. Phone Socket 1/3.
JACK PLUGS Std. Chrome 3/-; 5-mm Chrome 2/6. DIN SOCKETS Chassis 3-pin 1/8; 5-pin 2/-.
DIN SOCKETS Lead 3-pin 5/8; 5-pin 5/-.
DIN PLUGS 3-pin 3/8; 5-pin 5/-.
WAVE-CHANGE SWITCHES WITH LONG SPINDLES. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 4/8 each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way, 4/8 each. Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 waler 12/-, 2 waler 17/-, 3 waler 22/-
Additional wafers 5/- each up to 12 max.
TOGGLE SWITCHES. Sp. 2/6; sp. 4/2; 3/6; dp. 3/6; dp. 4/2 6/8

MINI-MODULE LOUDSPEAKER KIT

10 WATT 55/- CARR. 5/-

Triple speaker system combining on ready cut baffle. 1 in. chipboard 15 in. x 8 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top-end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 8 ohm. **TEAK VENEERED BOOKSHELF ENCLOSURE. 17 1/2 x 10 1/2 x 7 1/2 in. Specially designed for above. £5.10.0 extra**

BAKER 12in. SUPERB LOUDSPEAKER

Suitable for all Hi-Fi Systems. Provides rich clear reproduction of the deepest bass and remarkable efficiency in the upper register. Response 20-17,000 cps. "Baker" double cone with special "Ferroba" ceramic magnet. Flux density 16,500 gauss. Bass resonance 22-28 cps. 20 watts rating. Voice coil 8 ohms or 15 ohms. **£15** Post Free

48-page Enclosure Manual 5/9 post paid.

LOUDSPEAKER CABINET WADDING 18in wide, 2/6ft

BAKER "GROUP SOUND" SPEAKERS - POST FREE
 'Group 25' 'Group 35' 'Group 50'
 12in 25 watt 6gns 12in 35 watt 8gns 15in 50 watt 18gns.


ALL MODELS "BAKER SPEAKERS" IN STOCK

Super Cone Tweeter 2 1/2 in square, 3-17kc/s. 10W 17/6. Quality Horn Tweeters 2-18kc/s, 10W 29/6. Crossover 16/6. **LOUDSPEAKERS P.M. 3 OHMS. 2in, 3in, 4in, 5in, 7 1/2in, 17/8 each; 6in 37/8; 10in 37/8; 8 1/2in, 21/-; 8 1/2in 21/-.** Double cone 3 or 15 ohm 39/6; 10 6in, 30/-; 2 1/2 in. Double Cone 19/-; 3in, 3 or 15 ohm models, 45/- or with twin tweeters, X over and ceramic magnet 79/8.

SPECIAL OFFER: 8 ohm, 2in; 6 x 4in, 80 ohm, 2in, 2 1/2in; 15/6 EACH 25 ohm, 6 1/2in; 40 ohm, 35 ohm, 3in; TYPE 15 ohm, 10 2 1/2in. x 7 1/2in.
8in LOUDSPEAKER UNITS 3 ohm 27/6; 15 ohm 30/-; 8 in. De Luxe Ceramic 3 ohm 45/-; 15 ohm 50/-.
8in LOUDSPEAKER. TWIN CONE 3 ohm 35/-.
4 in. WOODER. 8 watts max, 20-10,000 cps, 15 ohm, 39/6.
OUTPUT TRANS. EL84 etc. 4G; MIKE TRANS. 50d 1.3 A.
SPEAKER FRET VARIOUS TYGAM SAMPLES. SEND S.A.E.

ALL PURPOSE HEADPHONES
 H.R. HEADPHONES 2000 ohms Super Sensitive... 35/-
 LOW RESISTANCE HEADPHONES 3-5 ohms... 39/6
 DE LUXE PADDED STEREO PHONES 8 ohms... 79/8

MINETTE AMPLIFIER

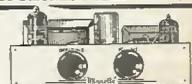

A.c. Mains Transformer. Chassis size 7 x 3 1/2 in. high. Valves ECL82, EZ80. 12 month guarantee. Quality output 3 ohm. With engraved fascia, valves, knobs, volume and tone controls. Wired and tested. Post 5/6 **69/6**

ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES. 45-PAGE EAGLE CATALOGUE 5/- Post free.

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. 79/6

BARGAIN DE LUXE TAPE SPLICER CUTS, trims, joins for editing and repairs. With 3 blades. 17/6

BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. 59/6

BARGAIN FM TUNER 88-106 Mc. Six Transistor. Ready built. Printed Circuit. Combined slide dial tuning. Size 6 x 4 1/2 in. 9 volt. £6.19.6

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. 69/6

★ RADIO BOOKS ★ (Postage 9d.)

Practical Transistor Receivers 5/-
 Practical Stereo Handbook 3/8
 Super-sensitive Transistor Pocket Radio 3/8
 High Fidelity Speaker Enclosures and Plans 5/-
 Radio Valve Guide, Books 1, 2, 3, or 4 ea. 5/- No. 6 ea. 6/-
 Practical Radio Inside Out 4/8
 Shortwave Transistor Receivers 5/-
 Transistor Communication Sets 6/-
 Modern Transistor Circuits for Beginners 7/6
 Sub-Miniature Transistor Receivers 5/-
 Wireless World Radio Valve Data 6/-
 At a glance valve equivalents 6/-
 Valves, Transistors, Diodes equivalents manual 10/8
 Receive foreign T.V. programmes by simple modifications 5/-
 Transistor Circuits Radio-Controlled Models 7/6

MANUFACTURERS SURPLUS! 25/-

TAPE RECORDER CASE. Red/Cream or Grey 2-tone. Resine covered. Size 15 x 12 x 5 1/2 in. POST FREE

POCKET MOVING COIL MULTIMETER. 49/6
 0-1,000 A.C./D.C. ohms 0 to 100k, etc.
SUPERIOR MOVING COIL MULTIMETER. 99/6
 0-2,500V. D.C. 20,000 ohms volt, 0-1,000V. A.C. Ohms 0 to 6 meg. 50 Microamps (Full list Meters S.A.E.)

BRAND NEW QUALITY EXTENSION LOUDSPEAKER

Handsome plastic cabinet, 20cm. lead and adaptors. For any radio, intercom, tape recorder, etc. 3 to 15 ohm. Size: 7 1/2 x 5 1/2 x 3". Post 2/6 **30/-**




VARIABLE VOLTAGE TRANSFORMERS



450 AMPS

1 AMP

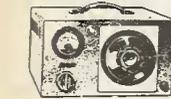

PORTABLE TYPE

INPUT 230/240v. A.C. 50/60—
OUTPUT VARIABLE 0-260v.
BRAND NEW

Keenest prices in the country.
All Types (and Spares) from
1/2 to 50 amp. from stock.

SHROUDED TYPE

1 amp, £5. 10. 0. 2.5 amps,
£6. 15. 0. 4 amps, £9. 0. 0.
5 amps, £9. 15. 0. 8 amps,
£14. 10. 0. 10 amps, £18. 10. 0.
12 amps, £21. 0. 0. 15 amps,
£25. 0. 0. 20 amps, £37. 0. 0.
37.5 amps, £72. 0. 0. 50 amps,
£92. 0. 0.

OPEN TYPE (Panel Mounting)
1/2 amp, £3. 10. 0. 1 amp, £5. 10. 0.
2.5 amps, £6. 12. 6.

PORTABLE TYPE

1.5 amp. portable fitted metal case,
voltmeter, lamp, switch, etc. £9.5.0.
Similar to above 2.5 amp. £11.7.6.

L.T. TRANSFORMERS

All primaries
220-240 volts

Type No.	Sec. Taps	Price	Carr.
1	30, 32, 34, 36 v. at 5 amps.	£4/5/0	6/-
2	30, 40, 50 v. at 5 amps.	£6/5/0	6/6
3	10, 17, 18 v. at 10 amps.	£4/10/0	4/6
4	6, 12 v. at 20 amps.	£5/17/6	6/6
5	17, 18, 20 v. at 20 amps.	£6/12/6	6/6
6	6, 12, 20 v. at 20 amps.	£6/5/0	7/6
7	24 v. at 10 amps.	£4/15/0	5/6
8	4, 6, 24, 32 v. at 12 amps.	£6/10/0	6/6

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250v. A.C. operation.

ECONOMY KIT. Flash rate 1-36 flash per second. All components including Unijunction, thyristor, tube and circuit. £5/5/0 plus 3/6 P. & P.

INDUSTRIAL KIT. Flash rate 1-80 f.p.s. Ideally suitable for schools, laboratories, etc. Incorporates double wound transformer which isolates both tube and timing circuit from mains: Stabilized timing circuit and high power tube. £8/8/0 plus 6/- P. & P.

1/2" POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 8/6 post paid. Regret not sold separately.

PARVALUX TYPE SD19 230/250 VOLTS A.C. REVERSIBLE GEARED MOTOR.

30 r.p.m. 40lb. ins. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Ex-equipment. Tested and in first class running order. A really powerful motor offered at a fraction of makers' price. 6 GNS. P. & P. 10/-.



BODINETYPEN.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p., 50 cycle, .38 amp.
(Type 2) 28 r.p.m. Torque 20lb. inch. Reversible. 1/80th h.p., 50 cycle, .28 amp.
The above two precision made U.S.A. motors are offered in 'as new' condition. Input voltage of motor 115v. A.C. Supplied complete with transformer for 230/240v. A.C. input. Price, either type £2. 17. 6 plus 6/6 P. & P. or less transformer £2. 2. 6 plus 4/6 P. & P.



SPEEDIVAC HIGH VOLTAGE HIGH FREQUENCY GENERATOR

Input 100/110 volts or 200/250 volts AC/DC. Output 19KV variable. Ideal for testing insulation, vacuum, leakage path, gas discharge lamps, neon, etc. A useful ozone and HF supply. Manufactured by Edwards High Vacuum Ltd. Brand new in maker's polished wooden carrying case. Offered at fraction of maker's price. £10.0.0 plus 7/6d. P. & P.

CT82 NOISE GENERATOR

Ideal for alignment of all types of communication and VHF receivers. Self contained audio output meter and mains power supply.
100Kc/s to 160Mc/s Frequency range 43 ohm or 75 ohm impedance. Noise figure range to 20db.
In rugged alloy case with instructions for use. Offered untested but in excellent condition, less mains lead. £7/19/6, P. & P. 10/-.



LIGHT SENSITIVE SWITCH

Kit of parts, including ORP12 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., 6-12 volt D.C. op. price 25/- plus 2/6 P. & P. ORP 12 including circuit, 10/6 each, plus 1/- P. & P.



A.C. MAINS MODEL Incorporates Mains Transformer, Rectifier and special relay with 3, 5 amp mains c/o contacts. Price inc. circuit 47/6 plus 2/6 P. & P.

LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with focusible lens assembly and ventilated lamp housing, to take MBC bulb. Separate photo cell mounting assembly for ORP. 12 or similar cell. Both units are single hole fixing. Price per pair £2.15.0. P. & P. 3/6.



UNISELECTOR SWITCHES NEW

4 Bank 25 Way 24 v. D.C. operation £5.17.6 plus 2/6 P. & P.
8 Bank 25 Way 24 v. D.C. operation. £7.12.6 plus 4/6 P. & P.



MINIATURE UNISELECTOR SWITCH

Ex-Equipment
3 banks of 11 positions plus homing bank. 40 ohm coil. 24-36 v. D.C. operation. Tested. 22/6, plus 2/6 P. & P.



COPPER LAMINATE. Printed Circuit Board. Size 15 1/2" x 5 1/2" 3 for 10/- Post paid. 3 minimum order.

RELAYS

Bulk purchase enables us to offer the following new SIEMENS, PLESSEY, etc. miniature plug in relays complete with base, at a fraction of makers' price

Coil Ω	Working Voltage	Contacts	Price
280	6-12	2 c/o 1	14/6
280	9-18	4 c/o	15/6
700	12-24	2 c/o	12/6
700	16-24	4 c/o	15/6
700	16-24	4M 2B	12/6
1250	20-40	2 c/o H.D.	12/6
2300	30-50	2 c/o H.D.	10/-
5800	50-70	4 c/o	10/-
9000	40-70	2 c/o	10/-

H.D. = Heavy Duty. POST PAID

'AVO' METER MODEL 7

Supplied fully checked and tested on all ranges and in excellent condition. Complete with batteries and leads. Price £13.10. 0. P. & P. 7/6. Avo Leather Carrying Case 30/- Regret not supplied separately.



'AVO' MODEL 47A

Ex-Admiralty in first class condition, complete with instructions, leads and case. £9/19/6, P. & P. 10/-.

'AVO' MODEL 48A

Ex-Admiralty in good condition with instructions, leads, plus D.C. Shunts for 120 Amp and 480 Amp. A.C. Transformer for 60 Amp. and 240 Amp. Multiplier for 3600 volt. Complete outfit in fitted case. £15/0/0, P. & P. 10/-.

INSULATED TERMINALS

Available in red, white, yellow, black, blue and green. New 17/- per doz. 2/- P. & P.

DRY REED SWITCHES

2 x 1 amp Dry Reeds (makes contacts). Mounted in 870 ohm 9-18 v. coil. Size 3" x 3 1/2" x 1/2". New. Price 8/6 per pair. Post Paid. Six of the above mentioned units (12 Reeds). Fitted in metal box. Size 4" x 3 1/2" x 1 1/2". Mfg. by Elliott Bros. New. 45/- each. Post Paid.

NEW FROM ILIFFE

110 SEMI-CONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR

R. M. MARSTON, technical author and design consultant.

This is a book which will appeal equally to the electronics amateur and to the professional engineer.

110 different circuits are described and the operation of each one is explained in simple and precise terms. The main feature of the book is that it fulfils a long-awaited need for readable information on these devices.

CONTENTS

- 30 Silicon-Planar Transistor Projects
- 15 Field-Effect Transistor Projects
- 20 Uni-Junction Transistor Projects
- 15 Silicon Controlled-Rectifier Projects
- 30 Integrated-Circuit Projects

124 pages 110 illustrations

25s. net case 26/- by post

18s. net student edition

19/- by post

ILIFFE BOOKS LTD

42 RUSSELL SQUARE
LONDON, W.C.1

SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space
57 BRIDGMAN ROAD, LONDON, W.4 Phone 995 1560
SHOWROOM NOW OPEN CLOSED SATURDAY

Personal callers only
9 LITTLE NEWPORT ST.
LONDON, W.C.2. Tel. GER 0576

NEW PRICES ON NEW COMPONENTS

RESISTORS

High stability, carbon film, low noise. Capless construction, molecular termination bonding.

Dimensions (mm): Body; $\frac{1}{4}$ W; 8×2.8
 $\frac{1}{4}$ W; 10×4.3

Leads; 35
10% ranges; 10 Ohms to 10 Megohms (E12 Renard Series)
5% ranges; 4.7 Ohms to 1 Megohm (E24 Renard Series)

Prices—per Ohmic value.

	10% each	10 off	25 off	100 off
$\frac{1}{4}$ W 10%	each	10 off	25 off	100 off
$\frac{1}{4}$ W 10%	2d	1/6	3/3	10/4
$\frac{1}{4}$ W 5%	2½d	1/9	3/8	11/8
$\frac{1}{4}$ W 10%	2½d	1/9	3/8	11/7
$\frac{1}{4}$ W 5%	3d	2/-	4/-	12/10

CAPACITORS

Subminiature Polyester film, Modular for P.C. mounting. Hard epoxy resin encapsulation. Radial leads. $\pm 100\%$ tolerance.

Prices—per Capacitance value (μ F)

	each	10 off	25 off	100 off
0.001, 0.002, 0.005, 0.01, 0.02	6d	4/3	8/4	30/-
0.05	8d	6/-	12/6	41/8
0.1	10d	7/1	15/6	51/-
0.2	1/2	10/-	20/10	68/6
0.5	2/-	17/6	37/6	125/-

Polystyrene film, Tubular, Axial leads. Unencapsulated. $\pm 5\%$ or $\pm 1\text{pF}$ tolerance.

Prices—per Capacitance value (μ F)

	each	10 off	25 off	100 off
10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 180, 220, 270, 330, 390	5d	3/7	7/9	24/-
470, 560, 680, 820, 1,000, 1,500	6d	4/-	8/8	26/8
2,200, 3,300, 4,700, 5,600	7d	5/-	10/10	33/4
6,800, 8,200, 10,000, 15,000	8d	6/-	13/-	40/-
22,000	9d	6/9	18/-	45/4

Polystyrene film, Tubular, Axial leads. Professional Grade. Hard Epoxy Resin encapsulation.

Prices—per Capacitance value (μ F)—except where stated

	each	10 off	25 off	100 off
100, 120, 150, 180	1/3	10/2	21/2	64/6
220, 270, 330, 390, 470, 560, 680, 820	1/3	10/8	23/1	71/-
1,000, 1,200, 1,500, 2,200, 2,700	1/6	13/10	29/11	92/-
3,300, 3,900, 4,700, 5,600	1/9	14/1	31/-	96/-
6,800, 8,200, 10,000, 12,000	1/9	15/2	32/10	101/-
15,000, 18,000	2/-	15/11	34/9	107/4
22,000, 27,000	2/3	17/3	37/10	115/-
33,000, 39,000	2/6	20/1	43/6	133/9
47,000, 56,000	2/9	22/1	47/10	147/4
68,000	3/-	24/9	53/8	165/4
82,000	3/3	26/1	56/6	173/9
0.1 μ F	3/6	27/5	59/4	182/8
0.12 μ F	3/9	30/3	65/10	202/-
0.15 μ F	4/3	34/2	73/7	228/-
0.18 μ F	5/-	37/10	81/11	252/3
0.22 μ F	6/-	47/-	101/10	313/4
0.27 μ F	6/9	53/9	116/8	358/4
0.33 μ F	7/3	58/10	126/11	390/-
0.39 μ F	7/9	65/-	140/10	433/4
0.47 μ F, 0.5 μ F	9/9	75/2	137/7	500/-

POTENTIOMETERS (Carbon)

Miniature, fully enclosed, rear tags, carbon brush wiper. Long life, low noise. Body dia. $\frac{3}{16}$ in. Spindle, $\frac{1}{16}$ in. \times $\frac{1}{16}$ in. $\frac{1}{4}$ W at 70°C. $\pm 20\%$ $\frac{1}{4}$ M, $\pm 30\%$ $\frac{1}{4}$ M Lin. 100 Ohms to 10 Megohms, Log. 5 Kohms to 5 Megohms.

Prices—per ohmic value.

	each	10 off	25 off	100 off
	2/3	20/-	45/10	186/8

SKELETON PRE-SET POTENTIOMETERS (Carbon)

High quality pre-sets suitable for printed circuit boards of 0.1in. P.C.M. 100 Ohms to 5 Megohms (Linear only).

Miniature: 0.3W at 70°C. $\pm 20\%$ below $\frac{1}{4}$ M, $\pm 30\%$ above $\frac{1}{4}$ M. Horizontal (0.7in. \times 0.4in. P.C.M.) or Vertical (0.4in. \times 0.2in. P.C.M.).

Subminiature: 0.1W at 70°C. $\pm 20\%$ below 2.5M, $\pm 30\%$ above.

Prices—per ohmic value

	each	10 off	25 off	100 off
Miniature (0.3W)	1/-	8/9	18/9	66/8
Subminiature (0.1W)	10d	7/1	14/7	46/8

JACK PLUGS

$\frac{1}{4}$ in. Type P1. Standard. Screened. Heavily chromed.
 $\frac{1}{4}$ in. Type P2. Standard. Unscreened. Unbreakable moulded cover.
 $\frac{1}{4}$ in. Type SE/P1. Side-entry version of P1 plug.
3.5mm Type P5. Standard. Screened. Aluminium cover.
3.5mm Type P6. Standard. Unscreened. Unbreakable moulded cover.

Prices—

	each	10 off	25 off	100 off
P1.	3/-	26/8	62/6	233/4
P2.	2/6	23/4	54/2	200/-
SE/P1.	3/6	30/10	66/8	280/-
P5.	2/2	19/2	43/9	158/4
P6.	1/8	15/-	33/4	116/8

JACK SOCKETS

$\frac{1}{4}$ in. Type S5. Standard. Moulded body. Chrome insert.
3.5mm Type S6. Specification as above.
Available with make/make, make/break, break/break, break/make contacts.

Prices—

	S5	S6
	2/9	1/6
	25/-	13/4
	56/8	33/4
	216/8	100/-

ELECTROLYTIC CAPACITORS (Mullard). —10% to $\pm 50\%$.

Subminiature (all values in μ F)

	each	10 off	25 off	100 off
4V	8	32	64	125
6.4V	6-4	25	50	100
10V	4	16	32	64
16V	2.5	10	20	40
25V	1.6	6.4	12.5	25
40V	1	4	8	16
64V	0.64	2.5	5	10
Price	1/4	1/3	1/2	1/-

Small (all values in μ F)

	each	10 off	25 off	100 off
4V	800	1,250	2,000	3,200
6.4V	640	1,000	1,600	2,500
10V	400	640	1,000	1,600
16V	250	400	640	1,000
25V	160	250	400	640
40V	100	160	250	400
64V	64	100	160	250
Price	1/6	2/-	2/6	3/-

POLYESTER CAPACITORS (Mullard)

Tubular, 10%, 160V: 0.01, 0.015, 0.022 μ F, 7d. 0.033, 0.047 μ F, 8d. 0.068, 0.1 μ F, 9d. 0.15 μ F, 11d. 0.22 μ F, 1/- 0.33 μ F, 1/3. 0.47 μ F, 1/6. 0.68 μ F, 2/3. 1 μ F, 2/8.

400V: 1,000, 1,500, 2,200, 3,300, 4,700pF, 6d. 6,800pF, 0.01, 0.015, 0.022 μ F, 7d. 0.033 μ F, 8d. 0.047 μ F, 9d. 0.068, 0.1 μ F, 11d. 0.15 μ F, 1/2. 0.22 μ F, 1/6. 0.33 μ F, 2/3. 0.47 μ F, 2/8.

Modular, metallised. P.C. mounting, 20%, 250V: 0.01, 0.015, 0.022 μ F, 7d. 0.033, 0.047 μ F, 8d. 0.068, 0.1 μ F, 9d. 0.15 μ F, 11d. 0.22 μ F, 1/- 0.33 μ F, 1/5. 0.47 μ F, 1/8. 0.68 μ F, 2/3. 1 μ F, 2/9.

SEMICONDUCTORS: OA5, OA81, 1/9. OC44, OC45, OC71, OC81, OC81D, OC82D, 2/- OC70, OC72, 2/3. AC107, OC75, OC170, OC171, 2/6. AF115, AF116, AF117, ACY19, ACY21, 3/3. OC140, 4/3. OC200, 5/- OC139, 5/3. OC25, 7/- OC35, 8/- OC23, OC28, 8/3.

SILICON RECTIFIERS (0.5A): 170 P.I.V., 2/9. 400 P.I.V., 3/- 800 P.I.V., 3/3. 1,250 P.I.V., 3/9. 1,500 P.I.V., 4/- (0.75A): 200 P.I.V., 1/6. 400 P.I.V., 2/- 800 P.I.V., 3/3. (6A): 200 P.I.V., 3/- 400 P.I.V., 4/- 600 P.I.V., 5/- 800 P.I.V., 6/-

SWITCHES (Chrome finish, Silver contacts): 3A 250V, 6A 125V. Push Buttons: Push-on or Push-off 5/-. Toggle Switches: SP/ST, 3/6. SP/DT, 3/9. SP/DT (with centre position) 4/- DP/ST, 4/6. DP/DT, 5/-

PRINTED CIRCUIT BOARD (Vero).

0.15in Matrix: 3 $\frac{1}{2}$ in \times 2 $\frac{1}{2}$ in, 3/3. 5 $\frac{1}{2}$ in \times 2 $\frac{1}{2}$ in, 3/11. 3 $\frac{1}{2}$ in \times 3 $\frac{1}{2}$ in, 3/11. 5in \times 3 $\frac{1}{2}$ in, 5/6.
0.1 Matrix: 3 $\frac{1}{2}$ in \times 2 $\frac{1}{2}$ in, 4/- 5in \times 2 $\frac{1}{2}$ in, 4/6. 3 $\frac{1}{2}$ in \times 3 $\frac{1}{2}$ in, 4/6. 5in \times 3 $\frac{1}{2}$ in, 5/3.


Send S.A.E. for January, 1969 Catalogue

DUXFORD ELECTRONICS (PE)

97/97A MILL ROAD, CAMBRIDGE

Telephone: CAMBRIDGE (0223) 63687

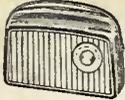(Visit us—at our new Mail Order, Wholesale & Retail Premises) MINIMUM ORDER VALUE 5/- C.W.O. Post and Packing 1/6



THE DORSET (600mW Output)


7-transistor fully tunable M.W.-L.W. superhet portable—with baby alarm facility. Set of parts. The latest modularised and pre-alignment techniques make this simple to build. Size: 12" x 8" x 3". MAINS POWER PACK KIT: 9/6 extra.

Price £5.50 plus 7/6 p. & p. Circuit 2/6 FREE WITH PARTS.

THE ELEGANT SEVEN Mk. III (350mW output)

7-transistor fully tunable M.W.-L.W. portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back prepared for foolproof construction.

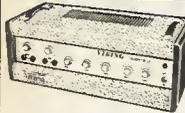Price £4.9.6 plus 7/6 p. & p. Circuit 2/6 FREE WITH PARTS.



50 WATT AMPLIFIER A.C. MAINS 200-250V

An extremely reliable general purpose valve amplifier—with six electronically mixed inputs. Suitable for use with: mics, guitars, gram, tuner, organs, etc. Separate bass and treble controls. Output impedance 3, 8 and 15 ohms.

Price 27 gns. plus 2/6 p. & p.

THE RELIANT LOW SOLID-STATE HIGH QUALITY AMPLIFIER

Specifications: Output: 10 watts R.M.S. Output impedance: 3 to 4 ohms. Inputs: 1. Xtal mic 10mV. 2. Gram/radio 250mV. Tone controls: Treble control range ±12dB at 10KHz; Bass control range ±12dB at 100Hz. 40KHz. Frequency response (with tone controls central): Minus 3dB points are 20Hz and 40KHz. Signal to noise ratio: better than -60dB. Transistors: 4 silicon Planar type and 3 Germanium type. Mains input: 220-250V a.c. Size of chassis: 10 1/2" long, 4 1/2" wide, 2 1/2" deep. A.C. Mains, 200-250V. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control for gram. and mike. Built and tested. 1 1/2" x 5" speaker to suit: Price 14/6 plus 1/6 p. & p. Crystal mike to suit: 12/6 plus 1/6 p. & p. Mk. 1 as above, less teak case 5 1/2 gns. + 7/6 p. & p.

RELIANT MARK II 6 gns + 7/6 p. & p. In teak-finished case

THE VISCOUNT

Integrated High Fidelity Transistor Stereo Amplifier




SPECIFICATIONS: Output: 10 watts per channel into 3 to 4 ohms speakers (20 watts monoaural). Input: 6 position rotary selector switch (3 pos. mono and 3 pos. stereo), P.U. Tuner, Tape and Tape Rec. Sensitivities: All inputs 100mV into 1.3M ohm. Frequency response: 40Hz-20KHz ±2db. Tone controls: Tone controls fit (Baxandall type), separate bass and treble controls. Treble 13db lift and cut at 15KHz. Bass 15db lift and 25db cut at 60Hz. Volume controls: Separate for each channel. AC Mains input: 200-240V. 50-60Hz. Size 12 1/2" x 6" x 2 1/2". In teak-finished case. Built and tested. PRICE 13 1/2 gns. Postage & Packing 7/6 extra.

DUETTO Integrated Transistor Stereo Amplifier

SPECIFICATION: R.M.S. power output: 3 watts per channel into 10 ohms speakers. INPUT SENSITIVITY: Suitable for medium or high output crystal cartridges and tuners. Crosstalk better than 30Ma at 1Kc/s. CONTROLS: 4-position selector switch (2 pos. mono & 2 pos. stereo) dual ganged volume control. TONE CONTROL: Treble lift and cut. Separate on/off switch. A balance preset control is also incorporated inside amplifier, which is set to provide equal gain on both channels. The unit is fuse protected and offered in an elegantly styled teak finished case, size 10 1/2" x 4 1/2" x 2 1/2" with contrasting front panel. Built and tested. PRICE 9 GNS. plus 7/6 p. & p.

THE CLASSIC

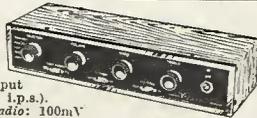Controls: Selector switch. Tape speed equalisation switch (3 1/2 and 7 1/2 i.p.s.). Volume. Treble. Bass. 2 position scratch filter and 2 pos. rumble filter.



Specification: Sensitivities for 10 watt output at 1KHz. Tape head: 3mV (at 3 1/2 i.p.s.). Mag. P.U.: 2mV. Cer. P.U.: 80mV. Radio: 100mV. A.C.: 100mV. T.P.R.: 100mV. Frequency: 20Hz to 20KHz. Gain is correct to within ±2dB (R.I.A.A.) from 20Hz to 20KHz. Tone control range: Bass ±13dB at 60Hz. Treble ±14dB at 15KHz. Total distortion: (for 10 watt output) <1.5%. Signal noise: <-60dB. A.C. mains 200-250V. Size 12 1/2" long, 4 1/2" deep, 2 1/2" high. Teak finished case. Price 8 1/2 gns. p. & p. 7/6.

POCKET MULTI-METER



Size 3 1/2" x 2 1/2" x 1 1/2". Meter size 2 1/2" x 1 1/2". Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1000 D.C. current 0-150mA. Resistance 0-100k p. Complete with test prods, battery and full instructions. 42/6. P. & F. 3/6. FREE GIFT for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

OUR PRICE 12 for 30/- extra Postage 4/6

12 for 21/- extra Postage 4/6

G.E.C. 13 amp surface mounting switched sockets in brown. Listed at 6/6.

W. & D. 13 amp flush sockets in green.

CYLDON 2 TRANSISTOR U.H.F. TUNER. BRAND NEW. COMPLETE WITH CIRCUIT DIAGRAM

£2.10.0 + 1/- p. & p.

B.S.R. TD2 TAPE DECK

This tape deck takes 5 1/2" spools complete with two-track heads. Size 13 1/2" long by 8 1/2" wide.

£8.19.6 plus 7/6 p. & p.

THREE-IN-ONE HI-FI 10 WATT SPEAKER

A complete Loud Speaker system on one frame, combining three matched ceramic magnet speakers with a low loss cross-over network. Peak handling power 10 watts. Impedance 16 ohms. Flux density 11,000 gauss. Resonance 40-60Hz. Frequency range 50Hz to 20Kc/s. Size 13 1/2" x 8 1/2" x 4 1/2". By famous manufacturer. List price 47. Our price 74/6 plus 5/- p. & p. Similar speaker to the above minus tweeters in 3 & 15 ohms 44/6 + 5/- p. & p.

Goods not despatched outside U.K. Terms C.W.O. All enquiries S.A.E.

RADIO & TV COMPONENTS (ACTON) LTD.

21d HIGH STREET, ACTON, LONDON, W.3
323 EDGWARE ROAD, LONDON, W.2
ORDERS BY POST TO OUR ACTON ADDRESS PLEASE

ORGAN BUILDERS! SILICON N.P.N. TRANSISTORS TESTED AND APPROVED BY DESIGNER FOR USE IN "PRACTICAL ELECTRONICS" ORGAN CIRCUIT—1/6 each or £5 per 100.

LATEST LIST OF TRANSISTOR STOCK. ALL BRAND NEW AND TO MANUFACTURERS SPECIFICATIONS

NKT11	8/3NKT261	8/3NKT10419	BDY20	22/32N1803	4/62N2220A			
NKT12	7/3NKT262	8/9	5/-	BFX29	11/62N1304	5/-		
NKT73	5/-NKT264	8/3NKT10619	BFX30	18/32N1305	5/-	2N2904	10/9	
NKT73	5/-NKT271	3/9	6/9	BFX84	8/62N1306	6/62N2904A		
NKT124	8/6NKT272	8/9NKT10339	BFX85	8/-	2N1307	6/6	18/-	
NKT125	8/9NKT274	8/9	6/6	BFX86	6/62N1308	6/62N2905	15/6	
NKT126	5/-NKT275	8/9NKT10439	BFX87	8/-	2N1309	8/62N2905A		
NKT126	5/-NKT281	5/-	7/3	BFX88	7/82N1613	5/9	18/-	
NKT137	6/6NKT302	16/6NKT12329	BFY50	5/-	2N1711	6/62N2906	12/6	
NKT210	5/9NKT304	18/3	11/6	BFY61	4/62N1893	12/62N2906A	18/3	
NKT211	5/-NKT361	11/6NKT12429	BFY62	5/-	2N2217	7/82N2907	14/-	
NKT212	5/-NKT401	15/-	14/-	BFY63	4/62N2217A	2N2907A		
NKT213	6/6NKT402	18/9NKT13329	BFY90	29/6			80/9	
NKT214	4/6NKT403	16/-	5/-	BSX19	4/62N2912	8/62N3053	5/9	
NKT215	5/-NKT404	13/6NKT13429	BSX20	4/62N2218A	2N3055	20/9		
NKT216	10/-NKT405	14/9	5/-	BSX60	16/6	10/-	2G345	4/6
NKT217	10/9NKT406	13/6NKT35219	BSX61	10/-	2N2219	10/62G371	4/-	
NKT218	5/-NKT420	40/-	22/3	BSY95A	3/92N2219A	12/62G378	4/-	
NKT223	5/9NKT451	13/9NKT16229	2N696	5/-	2N2220	7/8OC22	10/-	
NKT224	4/6NKT452	12/6	11/8	2N697	5/-	2N2221	8/6OC204	6/-
NKT225	4/6NKT453	8/-NKT20329	2N706	3/-	2N2211A	OC44	6/-	
NKT229	5/-NKT603F	6/6	12/62N706A	8/-	10/-	OC45	6/-	
NKT237	7/3NKT613F	7/8NKT20339	2N705	4/62N2222	10/9ASZ17	10/-		
NKT238	4/6NKT674F	5/-	8/62N709	11/62N2222A	Quantity			
NKT219	5/-NKT777F	4/6BC107	8/62N914	5/-	12/6	Discount:-		
NKT240	6/6NKT778	5/-BC105	3/-	2N918	11/62N2267	9/32549	5/-	
NKT241	5/-NKT717	8/-BC109	4/62N938	7/82N2385	4/650199	10	10%	
NKT242	3/-NKT734	5/-BCY65	7/82N990	8/-	2N389	4/6100299	10%	
NKT243	14/-NKT736	6/6BCY70	5/-	2N1131	8/62N2689A	5/601999	20%	
NKT244	3/-NKT773	4/6BCY71	9/82N1132	10/-	2N2483	8/61,000	25%	
NKT245	8/9NKT781	5/-BCY72	4/62N1302	4/62N2484	10/8	all one type.		

Unmarked transistors (tested) similar to: 2N753 1/6, BSY28 1/6, BSY65 1/6, OC44 1/6, OC71 1/-, OC72 1/-, LIGHT SENSITIVE TRANSISTORS (similar to OCP71), 2/- each. ORP12, CADMIUM SULPHIDE LIGHT-SENSITIVE RESISTORS 9/- each.

GIANT-SIZE SELENIUM SOLAR CELLS—PRODUCE UP TO 6mA AT 0.6V FROM DAYLIGHT!

67mm diameter, 10/- each, 50mm x 37mm 2 for 10/-.

MULLARD POLYESTER CAPACITORS FAR BELOW COST PRICE!

0-001µF, 400V, 3d; 0-0015µF, 400V, 3d; 0-0018µF, 400V, 3d; 0-0022µF, 400V, 3d; 0-01µF, 400V, 3d; 0-15µF, 160V, 6d; 0-22µF, 160V, 6d; 0-27µF, 160V, 6d; 1µF, 125V, 1/-.

RECORD PLAYER CARTRIDGES. COMPLETE WITH NEEDLES

GP67/2, Mono, 15/-, GL91/3, Compatible, £1, GP93/1, Crystal Stereo, 25/-, GP94/1, Ceramic, 25/-.

TRANSISTORISED SIGNAL INJECTOR KIT 10/-, SIGNAL TRACER KIT 10/-, CAR. REV. COUNTER KIT 10/-.

VEROBOARD

2 1/2in x 1in, 0-15 matrix, 1/3
3 1/2in x 2 1/2in, 0-15 matrix, 3/3
3 1/2in x 3 1/2in, 0-15 matrix, 3/11
5in x 2 1/2in, 0-15 matrix, 3/11
5in x 3 1/2in, 0-15 matrix, 5/6
17in x 2 1/2in, 0-15 matrix, 11/-
17in x 3 1/2in, 0-15 matrix, 14/8
3 1/2in x 2 1/2in, 0-1 matrix, 4/2
3 1/2in x 3 1/2in, 0-1 matrix, 4/9
5in x 2 1/2in, 0-1 matrix, 4/7
5in x 3 1/2in, 0-1 matrix, 5/6
5in x 3 1/2in, 0-1 matrix, 5/7

Spot Face Cutter 7/6. Pin Insert Tool 9/6, Terminals Pins 3/6-36. Special Offer! Spot Face Cutter and Five 2 1/2in x 1in boards, 9/9 only!

PAPER CONDENSERS, Mixed bags 0-001µF to 0-5µF, 12/6 per 100. SILVER-MICA, Ceramic, Polystyrene Condensers. Well assorted. Mixed types and values. 10/- per 100.

RESISTORS. Mixed types and values, 1 to 1 watt. 6/6 per 100. 55/- per 1,000. Wire-wound resistors. 1 watt to 10 watts. Mixed values. 20 for 10/-.

Transistors. Mixed, unmarked, mainly O.K. 7/6 for 50.

12 VOLT TRANSISTORISED FLUORESCENT LIGHTS. HALF NORMAL PRICE!

8 Watt 12in tube. Reflector type £2.19.6. 15 watt 18in Batten type £3.19.6.

IDEAL FOR CAMPING OR CARAVAN HOLIDAYS! A BRIGHT LIGHT FOR VERY LIGHT CURRENT!

ELECTROLYTIC CONDENSERS

0.25µF	3 volt	4µF	4 volt	10µF	25 volt	64µF	9 volt
1µF	6 volt	4µF	12 volt	20µF	6 volt	100µF	9 volt
1µF	20 volt	4µF	25 volt	25µF	6 volt	320µF	4 volt
1.25µF	16 volt	5µF	6 volt	25µF	12 volt	320µF	10 volt
2µF	3 volt	6µF	6 volt	25µF	25 volt	400µF	6-4 volt
2µF	350 volt	8µF	3 volt	30µF	6 volt	All at 1/- each.	
2.5µF	16 volt	8µF	12 volt	30µF	10 volt	20 assorted	
3µF	25 volt	8µF	50 volt	50µF	6 volt	(our selection)	
3.2µF	64 volt	10µF	6 volt	64µF	2-5 volt	10/-	

Orders by post to: G. F. MILWARD, DRAYTON BASSETT, NEAR TAMWORTH, STAFFS.

Please include suitable amount to cover post and packing. Minimum 2/-. Stamped addressed envelope must accompany any enquiries. For customers in Birmingham area goods may be obtained from Rock Exchanges, 231 Alum Rock Road, Birmingham 8.

FOLLOW THE LEADERS

KING SIZE QUALITY-TESTED PAKS

2	Drift Trans. 2N1225 Germ. PNP	10/-
100	Mc/s. PNP Trans.	10/-
6	Matched Trans. OC44/45/81/81D	10/-
20	Red Spot AF Trans. PNP	10/-
16	White Spot RF Trans. PNP	10/-
6	Silicon Rects. 3 A 100-400 PIV	10/-
2	10 A Silicon Rects. 100 PIV	10/-
2	OC140 Trans. NPN Switching	10/-
1	12 A SCR 100 PIV	10/-
3	Sil. Trans. 2S303 PNP	10/-
4	Zener Diodes 250mW 3-12V	10/-
3	200Mc/s. Sil. Trans. NPN BSY26/27	10/-
3	Zener Diodes 400mW 33V 5% Tol.	10/-
4	High Current Trans. OC42 Eqvt.	10/-
2	Power Transistors OC291 OC30	10/-
5	Silicon Rects. 400 PIV 250mA	10/-
4	OC75 Transistors Mullard Type	10/-
1	Power Trans. OC20 100V	10/-
10	OA202 Sil. Diodes Sub-min. Marked	10/-
2	Low Noise Trans. NPN 2N2929/30	10/-
1	Sil. Trans. NPN VCB 100 ZT86	10/-
8	OA81 Diodes	10/-
4	OC72 Transistors	10/-
4	OC77 Transistors	10/-
4	Sil. Rects. 400 PIV 500mA	10/-
6	GET884 Trans. Eqvt. OC44	10/-
5	GET885 Trans. Eqvt. OC45	10/-
2	2N708 Sil. Trans. 300Mc/s. PNP	10/-
6	GT41/45 Germ. Trans. PNP	10/-
3	GT31 LF Low Noise PNP Trans.	10/-
6	IN914 Sil. Diodes 75 PIV 75mA	10/-
8	OA95 Germ. Diodes Sub-min. IN69	10/-
3	NPN Germ. Trans. NK1773	10/-
2	OC22 Low Noise Trans. Germ.	10/-
2	OC25 Power Trans. Germ.	10/-
4	OC72 Trans.	10/-
4	AC128 Trans. PNP High Gain	10/-
4	AC127/128 Comp. pair PNP/NPN	10/-
3	2N1307 PNP Switching Trans.	10/-
10	CG92H Germ. Diodes Eqvt. OA71	10/-
3	AF116 Trans.	10/-

FREE One 10/- Pack of your own choice free with orders value 24 or over.

12	Assorted Germ. Diodes Marked	10/-
4	AC128 Germ. PNP Trans.	10/-
4	Silicon Rects. 100 PIV 750mA	10/-
3	AF117 Trans.	10/-
7	OC81 Type Trans.	10/-
3	OC171 Trans.	10/-
2	2N2926 Sil. Epoxy Trans.	10/-
7	OC71 Type Trans.	10/-
25	Trans. Heatsinks at TO18, SO12, etc.	10/-
2	2S701 Sil. Trans. Texas NPN	10/-
3	12V Zener 400mW	10/-
2	10A 600 PIV Sil. Rects. IS45R	10/-
3	2C108 Sil. NPN High Gain Trans.	10/-
1	2N2410 NPN Sil. Trans. VCB100	10/-
2	1000 PIV Sil. Rect. 1.5A R53310 AF	10/-
3	BSY95A Sil. Trans. NPN 200Mc/s.	10/-
3	OC200 Sil. Trans.	10/-
2	Sil. Power Rects. BYZ13	10/-
1	Sil. Power Trans. NPN 100Mc/s. TK201A	15/-
6	Zener Diodes 3-15V Sub-min.	15/-
1	2N1192 PNP Epitaxial Planar Sil.	15/-
3	2N897 Epitaxial Planar Trans. Sil.	15/-
4	Germ. Power Trans. Eqvt. OC16	15/-
1	1 Unijunction Trans. 2N2646	15/-
2	Sil. Trans. 200Mc/s. 60Vcb ZT86/84	15/-
1	Sil. Planar Trans. NPN 100Mc/s. BSY25	15/-
1	Unijunction Trans. 2N2160 TO-5	15/-
2	Sil. Rects. 5A 500 PIV Stud Type	15/-
2	Germ Power Trans. OC28/29	15/-
1	10A Sil. Stud Rect. 800 PIV	15/-
1	Tunnel Diode AEY11 1050Mc/s.	15/-
2	2N2712 Sil. Epoxy Planar HFE225	15/-
8	BY 100 Type Sil. Rects.	20/-
25	Sil. and Germ. Trans. Mixed, all marked, New	30/-
2	GET890 Low Noise Germ. Trans.	10/-
1	AF139 PNP High Freq. Trans.	10/-
3	NPN Trans. 1 ST141 & 2 ST140	10/-
4	Madt's 2 MAT100 & 2 MAT120	10/-
3	Madt's 2 MAT101 & 1 MAT121	10/-
4	OC44 Germ. Trans. AF	10/-
3	AC127 NPN Germ. Trans.	10/-
1	2N3906 Sil. PNP Trans. Motorola	10/-

CADMIUM CELLS

ORP60	ORP61	8/- each
ORP12		8/8 each

MANY NEW PAK ITEMS

FULL RANGE OF ZENER DIODES
VOLTAGE RANGE 2-16V.
400mW (DO-7 Case) 2/8 each
1.5W (Top-Hat) 3/8 each
10W (SO-10 Stud) 5/- each
All fully tested 5% tol. and marked. Please state voltage required. Full range eqvt. to OAZ Mullard Type Z. Range of STC, I.R. Texas and IN types.

TRANSISTOR EQVT. BOOK

52 pages of cross references for trans. and diodes. Types include British, European, American and Japanese. Specially imported by BI-PAK 10/- each

ANOTHER CROWNING SUCCESS—

2N2060 NPN SIL. DUAL TRANS. CODE DI699 TEXAS. OUR PRICE 5/- each

GERM. RECTIFIER SINGLE-PHASE
BRIDGE, Mullard type. GEX541-B.P. Output Vltts. 48v. Output I.C. 5A. List Price 58/-.
OUR PRICE 12/6 EACH

120 VCB NIXIE DRIVER TRANSISTOR
Sim. BSX21&C407. 2N1893 FULLY TESTED AND CODED
NDI20. 1-24 3/6 each. To-5 N.P.N. 25 up 3/- each.

KING OF THE PAKS SUPER PAKS

Satisfaction GUARANTEED in Every Pak, or money back.

U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	400 Germanium Transistors like OCS1, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	40 Silicon Planar Transistors NPN sim. BSY95A, 2N706	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Volts 1 watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U12	12 Silicon Rectifiers EPOXY BY126/127	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 28104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	30 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	30 Silicon NPN Transistors like BC108	10/-
U20	12 1.5-amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U21	30 A.F. Germanium alloy Transistors 2G300 Series & OC71	10/-
U22	10 1-amp Glass Min. Silicon Rectifiers High Volts	10/-
U23	30 Madt's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26	30 Fast Switching Silicon Diodes like IN914 Micro-min	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc., 8 Assorted Pieces	20/-
U29	10 1 amp SCR's TO-5 can up to 600 PIV CR51/25-600	20/-
U30	15 Plastic Silicon Planar trans. NPN 2N2924-2N2926	10/-
U31	20 Sil Planar NPN trans. low noise Amp 2N3707	10/-
U32	25 Zener diodes 400mW D07 case mixed Vltts. 3-18	10/-
U33	15 Plastic case 1 amp silicon rectifiers 1N4000 series	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked

ADI61 NPN ADI62 PNP MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS.

For mains driven output stages of Amplifiers and Radio receivers.
OUR LOWEST PRICE OF 12/6 PER PAIR

HIGH POWER SILICON PLANAR TRANSISTORS. TEXAS 2S034. NPN TO-3.

VCE100	1c 4A	IT. 15M/cs
VCE100	Ptot. 40W	
VEB8	hFE(min.)	60
	Price	15/- each

NEW SILICON RECTIFIERS TESTED

PIV 400mA 750mA 1-5A	3A	10A	30A
50 104	1/-	1/6	2/9
100 1/-	1/3	2/8	3/8
200 1/3	1/9	2/6	4/-
300	2/-	3/9	4/6
400 2/-	2/6	4/-	5/6
500	3/-	4/3	5/6
600 2/9	3/3	4/3	5/9
800	3/-	4/9	7/6
1,000	5/-	6/-	9/3
1,200	6/6	7/6	11/8

SCR's

PIV 1A 7A 16A 30A	LARGEST RANGE
25	7/6
50	7/6
100	8/6
200	12/6
300	15/-
400	17/6
500	20/-
600	24/-

PLEASE NOTE. To avoid any further increased Postal Charges to our Customers and enable us to keep our "By Return Postal service" which is second to none, we have re-organized and streamlined our Despatch Order Department and we now request you to send all your orders together with your remittance, direct to our Warehouse and Despatch Department, postal address: **BI-PAK SEMICONDUCTORS, Despatch Dept., P.O. BOX 6, WARE, HERTS.** Postage and packing still 1/- per order. Minimum order 10/-.



BI-PAK
Semiconductors

FET'S

2N 3819	10/-
2N 3820	25/-
MPF105	8/-
OCPT1 Type	8/6

UNIUNION

UT46, Eqvt. 2N2646, TIS43, BEN3000	7/6 EACH
25-99 5/-	100 UP 4/-

INTEGRATED CIRCUITS
I.C. Operational Amplifier with Zener output. Type 701C. Ideal for P.E. Projects. 8 Lead TO-5 case. Full data
Our price 12/6 each. Large Qty. 5 off 11/- each. Prices quoted for.

FAIRCHILD EPOXY TO-5 8 Lead

μL390 Buffer	10/6
μL314 Dual Gate	10/6
μL923 J.K. Flip-Flop	14/-
I.C. Data Circuits, etc.	1/6

MULLARD I.C. AMPLIFIERS
TAA243 ORP. Amp. 70/-
TAA263 Min AF Amp. 18/6
TAA293 G.P. Amp. 28/-
RCA CA3020 Audio Amp. 30/-

PRINTED CIRCUITS
EX-COMPUTER
Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards 10/- Plus 2/- P. & P.

CADMIUM CELLS
ORP 60 ORP 61 8/- each
ORP12 8/6

SIL. G.P. DIODES
300mW 30 10/-
25PIV (Min.) 100 15/-
Sub-Min. 500 25
Fully Tested 1,000 29
Ideal for Organ Builders.



**500 CHESHAM HOUSE
150 REGENT STREET
LONDON, W.1**

KING OF THE PAKS BI-PAK GUARANTEE SATISFACTION OR MONEY BACK

VALUE ALL THE WAY

Practical Electronics Classified Advertisements

SERVICE SHEETS

RADIO TELEVISION, over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherd's Bush Rd., London, W.6. SHE 8441.

SERVICE SHEETS, Radio, TV, 5,000 models. List 1/6. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

LARGE SUPPLIER OF SERVICE SHEETS

T.V., RADIO, TRANSISTORS, TAPES, ETC. Only 5/- each, plus LARGE S.A.E. (Uncrossed P.O.'s please, returned if service sheets not available.)

C. CARANNA
71 BEAUFORT PARK, LONDON, N.W.11
MAIL ORDER ONLY

SERVICE SHEETS (1925-69) for televisions, radios, transistors, tape recorders, record players, etc., by return post, with free fault-finding guide. Prices from 1/-. Over 8,000 models available. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

FOR SALE

£6,000 IN VOUCHERS GIVEN AWAY. See free Cat. for details. Tools, Materials, Mechanical, Electrical, thousands of interesting items. WHISTON, Dept. PVE, New Mills, Stockport SK12 4HL.

SONY 625 LINE VIDEO CAMERA, with R.F. output. As new condition, cost £195, will accept £140 o.n.o. Hertford 5230 after 7 p.m.

FOR SALE. Approx. 2 cwt. of Precision and other components, AR88D, RX, Instruments, Valves, Transistors, Dekatrons, Meters, etc. Must be all sold by May 26. Any and all offers considered. (EX-Constructor going overseas.) COAD, Fairend Cottage, Buckland St. Mary, Chard, Somerset.

MORSE MADE EASY !!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-660 2895 or send 8d. stamp for explanatory booklet to: G3HSC (Box 19), 45 GREEN LANE, PURLEY, SURREY

MISCELLANEOUS

RHYTHM MODULES. Build your own rhythm box—simply, cheaply. Realistic sound guaranteed. S.A.E. for details. D.E.W. LTD., 254 Ringwood Rd., Ferndown, Dorset.

BUILD IT in a DEWBOX quality cabinet 2in x 2½in x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

RATES : 1/3 per word (minimum 12 words). Box No. 1/6 extra.

Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Electronics"

IPC MAGAZINES LTD.,
Fleetway House, Farringdon Street,
London, E.C.4

MISCELLANEOUS (continued)

GEARED MOTORS

Rectifiers, Potentiometers
6d Stamp for Catalogue

F. HOLFORD & CO.
6 Imperial Square, Cheltenham

ETCHED PRINTED CIRCUIT BOARD KITS. Full instructions. 19/6, c.w.o. CIR-CUITETCH, 12 Cambridge Rd., St. Albans, Herts.

MAKING AN ORGAN

We can save you £ £ £s

We have acquired the bulk organ stores from a leading British manufacturer. Stocks too numerous to list in full. Examples:

PLAIN STOP TABS	1/6
ENGRAVED STOP TABS from	2/6
GENERATOR P.C. BOARDS from	5/-
AMPLIFIER P.C. BOARDS from	5/-
RESISTORS from	1d.

SPEAKERS, KEYBOARDS, CABINETS, PEDALS, FOOTSWITCHES, MOTORS, TRANSFORMERS, CAPACITORS, ETC., ETC.

Everything you want to build: organs, amplifiers, "Leslie" cabinets...

S.A.E. for full price list.

E.M.C. (Dept. P.E.1), 104 ASHLEY ROAD, PARKSTONE, POOLE, DORSET
TRADE ENQUIRIES INVITED

UFO DETECTOR CIRCUITS, data. 10s. (refundable). Paraphysical Laboratory (UFO Observatory), Downton, Wilts.

ONE OFF PRINTED CIRCUIT BOARDS cheaply made to customers' requirements. Send s.a.e. for details: D. R. MANN, 12 Randolph Street, Nottingham.

ROBOTS

Synthetic Animals with "BRAINS" of their own. The NEW range of projects include: an electronic 'animal' which "LEARNS", an Electro Chemical device capable of "REPRODUCING" itself! Other projects SURE TO INTRIGUE YOU are an audio transmitter/receiver which has quite an amazing range and requires NO LICENCE; also a machine which "recognizes" itself, and an electronic dog whistle, etc., etc. HOSTS OF EASY-TO-CONSTRUCT projects, for anyone with a basic knowledge of Electronics.

SEND 2/6 for your list—NOW!

To: "BOFFIN PROJECTS"

incorporating
BIONIC DESIGNS, 4 CUNLIFFE RD.
STONELEIGH, EWELL, SURREY
Designed by GERRY BROWN and
JOHN SALMON and presented
on T.V.

MISCELLANEOUS (continued)

GOING ABROAD! Must sell all components. 95 Transistors, Mullard and Texas types. 650 assorted resistors and capacitors. Everything brand new. £10 the lot. Lists s.a.e. D. WALTERS, 2 Gorway Road, Walsall, Staffs.

BOOKS AND PUBLICATIONS

GOVT. SURPLUS WIRELESS EQUIPMENT HANDBOOK

This useful Handbook gives detailed information and circuit diagrams for British and American Government Surplus Receivers, Transmitters and Test Equipment, etc.; also contained are some suggested modification details and improvements for the equipment. Incorporated in this revised edition is a surplus/commercial cross referenced valve and transistor guide. This book is invaluable to radio enthusiasts, radio clubs, universities and laboratories. The latest edition, Volume III, priced at 45/- per volume, plus 5/- P. & P., C.O.D. A pleasure, is obtainable from us at

GILTEXT (LEEDS) LTD

Dept. P.E., 24 Stansfield Chambers
Gt. George Street, Leeds 1
S.A.E. with all enquiries, please. Extra postage for all foreign orders.

SURPLUS HANDBOOKS

19 set Circuit and Notes	6/6 P.P. 6d
1155 set Circuit and Notes	6/6 P.P. 6d
H.R.O. Technical Instructions	5/6 P.P. 6d
38 set Technical Instructions	5/6 P.P. 6d
46 set Working Instructions	5/6 P.P. 6d
88 set Technical Instructions	7/- P.P. 6d
BC. 221 Circuit and Notes	5/6 P.P. 6d
Wavemeter Class D Tech. Instr	5/6 P.P. 6d
18 set Circuit and Notes	5/6 P.P. 6d
BC.1000 (31 set) Circuit and Notes	5/6 P.P. 6d
CR.100/B.28 Circuit and Notes	10/- P.P. 9d
R.107 Circuit and Notes	7/- P.P. 6d
A.R.88D. Instruction Manual	18/- P.P. 6d
62 set Circuit and Notes	6/6 P.P. 6d
52 set Sender & Receiver Circuits	7/6 post free
Circuit Diagrams: 5/- each post free.	
R.1116/A, R.1224/A, R.1355, R.F. 24, 25, & 26.	
A.1134, T.1154, CR.300, BC.342, BC.312.	
BC.348, J.E.M.P. BC.624, 22 set.	
Resistor Colour Code Indicator	2/6 P.P. 6d

S.A.E. with all enquiries please.
Postage rates apply to U.K. only.
Mail order only to:
Instructional Handbook Supplies
Dept. P.E., Talbot House, 28 Talbot Gardens
Leeds 8

EDUCATIONAL

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home study organisation. City & Guilds; R.T.E.B., etc. Also practical courses with equipment. No books to buy. Write for FREE Prospectus to ICS (Dept. 577), Intertext House, Stewarts Road, London, S.W.8.

RADIO OFFICERS see the world. Sea going and shore appointments. Trainee vacancies in Sept. and Jan. Grants available. Day and Boarding students. Stamp for prospectus. WIRELESS COLLEGE, Colwyn Bay, Wales.

TECHNICAL TRAINING in Radio, TV & Electronics thro' world-famous ICS. For details of proven home-study courses write: ICS, Dept. 561, Intertext House, Stewarts Road, London, S.W.8.

GET INTO ELECTRONICS—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. A.M.I.E.R.E., R.T.E.B., City & Guilds, Radio, T.V., Telecoms, etc. For FREE 100-page book, write Dept. 856K, CHAMBERS COLLEGE, 148 Holborn, London, E.C.1.

FULL TIME COURSES IN BASIC ELECTRONICS AND TELEVISION SERVICING

Nine-month courses, starting September 1969, leading to City and Guilds Certificates. Part time also available. Details from:
Section 47/48, Southall College of Technology, Beaconsfield Road, Southall, Middlesex

ENGINEERS. A technical certificate or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.T., A.I.O.B. and G.C.E. exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts., Building, etc. For full details write for FREE 132-page guide. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 125K), Aldermaston Court, Aldermaston, Berks.

SITUATIONS VACANT

A.M.I.E.R.E., A.M.S.E. (Elec.), City & Guilds, G.C.E., etc., on "Satisfaction or Refund of Fee" terms. Wide range of Home Study Courses in Electronics, Computers, Radio, T.V., etc. 132-page Guide—FREE. Please state subject of interest. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 124K), Aldermaston Court, Aldermaston, Berks.

RADIO TECHNICIANS VACANCIES TO BE FILLED BY OCTOBER 1969

A number of suitably qualified candidates are required for unestablished posts, leading to permanent and pensionable employment (in Cheltenham and other parts of the UK, including London). There are also opportunities for service abroad.

Applicants must be 19 or over and be familiar with the use of Test Gear, and have had practical Radio/Electronic workshop experience. Preference will be given to such candidates who can also offer "O" Level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications. A knowledge of electro-mechanical equipment will be an advantage.

Pay according to age, e.g. at 19 — £869 at 25 — £1,130.

Prospects of promotion to grades in salary range £1,217-£2,038. There are a few posts carrying higher salaries.

Annual Leave allowance of 3 weeks 3 days rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply.

Application forms available from:

Recruitment Officer (RT/54)
Government Communications Headquarters
Oakley, Priors Road
Cheltenham, Glos. GL52 5AJ

N A G R A

THE WORLD'S FINEST PROFESSIONAL PORTABLE TAPE RECORDER

JUNIOR SERVICE ENGINEER

An excellent opportunity has arisen for a young engineer to work in our Service Department. The successful applicant will be an enthusiastic and diligent worker with a good understanding of basic tape recorder principles and a standard of workmanship consistent with the quality of the product.

Good salary and conditions. Existing holiday arrangements honoured.

Please send full details in writing to:—

**MANAGING DIRECTOR
HAYDEN LABORATORIES LTD.
EAST HOUSE, CHILTERN AVENUE
AMERSHAM, BUCKINGHAMSHIRE**

SERVICE ENGINEERS—we are an old established electronics company, but headed by a young management team, and we need you to help us. Age is no barrier to a high salary as you will find out when you join us. If you have experience in T.V., Radio or Hi-Fi Service and want a job that looks ahead, phone MICHAEL ADLER at 01-636 9606.

AN ELECTRONIC ENGINEER is required to service and maintain Photon 713 and Lumitype 540 photo typesetting equipment on the Night Shift of a large group of weekly newspapers. Experience preferred but not essential as training can be given. Apply Production Manager, KING & HUTCHINGS, Cricketfield Road, Uxbridge. Telephone Uxbridge 37161.

TECHNICAL TRAINING by ICS IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Electronics, Computers, etc. Expert coaching for:

- * C. & G. TELECOMMUNICATION TECHNICIANS' CERTS.
- * C. & G. ELECTRONIC SERVICING.
- * R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- * RADIO AMATEURS' EXAMINATION.
- * P.M.G. CERTIFICATES IN RADIOTELEGRAPHY.

Examination Students Coached until Successful.

NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator, multi-meter and valve volt meter—all under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

INTERNATIONAL CORRESPONDENCE SCHOOLS

A WHOLE WORLD OF KNOWLEDGE AWAITS YOU!

International Correspondence Schools
(Dept. 152), Intertext House, Stewart Road,
London, S.W.8.

NAME
Block Capitals Please

ADDRESS

6/69

**NEWCASTLE UPON TYNE
POLYTECHNIC (Designate)**

RUTHERFORD COLLEGE OF TECHNOLOGY

B.Sc. ELECTRICAL AND ELECTRONIC ENGINEERING
(Honours and Ordinary)

B.Sc. PHYSICAL ELECTRONICS (Honours and Ordinary)

M.Sc. ADVANCED EXPERIMENTAL PHYSICS

Further details of these and other courses and of residential accommodation available, may be obtained from Administrative Officer, Rutherford College of Technology, Ellison Place, Newcastle upon Tyne NE1 8ST quoting PE 693.

RECEIVERS AND COMPONENTS

TINY TRANSISTOR RELAY for model control, light switches, experiments, etc. Only 1in square, 330Ω coil, 30/- post free. H.R. RADIO, 174 Bramall Lane, Sheffield, S24RF.

**L.S.T. ELECTRONIC
COMPONENTS LTD.**

PLEASE SEE
OUR DISPLAY ADVERTISEMENT ON
PAGE 468

ELECTRONIC STOCKMARKET kit of most parts; also "Reactalyser" and Waa-Waa pedal. S.A.E. for list. D.E.W. LTD., Ringwood Rd., Ferndown, Dorset.

**40 WATT DC TO AC CONVERTER
KITS, 2 TRANSISTOR TYPE SUITABLE
FOR LIGHTS, SHAVERS,
COMPRISING:**

- 1 SPECIAL TRANSFORMER 45/-+6/- pp.
- 2 HEAT SINKS 20/-+2/- pp.
- 2 OC28 TRANSISTORS 20/-+1/6 pp.
- 2 CONDENSERS, 2 MICA 4/6+1/6 pp.
- WASHERS, ETC.

All parts available separately. Complete Kit £4.17.0 post paid. CASE 30/-+4/6 post paid. De Luxe type 4 Transistor 60 Watt suitable for Lights, Tape Recorders. 1 Driver Stage comprising Transformer, 2 Transistors wired and tested £3.10.0. pp. 4/-

- 1 60 WATT OUTPUT TRANSFORMER £2.15.0+6/- pp.
- 2 HEAT SINKS 20/-+2/- pp.
- 2 OC28 TRANSISTORS 20/-+1/6 pp.
- 1 250V NEON INDICATOR LAMP,
- 1 SWITCH, CONDENSERS, MICA WASHERS 15/-+2/- pp.
- 1 BULGIN INPUT PLUG/SOCKETS 5/-+1/- pp.
- 1 BULGIN OUTPUT PLUG/SOCKETS 4/6+1/- pp.
- 1 CASE 30/-+4/6 pp.
- COMPLETE KIT £10.5.0.

J. ROBINSON (RADIO TV),
4 HIGHCLIFFE ROAD, MANCHESTER M9 3FX
Tel. 061-740 1175

**RECEIVERS AND COMPONENTS
(continued)**

TERRIFIC TRANSISTORS!

High-gain low-noise npn planars
20V, 220mW, 200mA peak Ic, hfe up to 900.
BC168=BC148 (sim. BC108, BC170, BC183,
2N2925, 2N2926), hfe=250-900
BC169=BC149 (sim. BC109, BC151, BC154,
2N3391A, etc.), hfe=450-900
Prices: BC168, 5 for 10/-, 50 for 90/-,
BC169, 5 for 11/3, 50 for £5.

Brand new, mint, makers' trade marks. Full list with data, components, circuits, kits 6d. FREE WITH ORDERS.



**MINI MAINS
PACK KIT**

Can be built to size of PP6 battery. Components and data sheet, 17/6. Transformer only, 0-230-250/9-0-9V, 80mA, size 1 1/2 x 1 1/2", with data sheet, 11/-. Eagle transformers (same size) MT6, 6-0-6V 100mA, MT12, 12-0-12V, 50mA, 13/6 each. All these can be used with bridge rectifiers giving double the voltage at half the current. Submin. selenium bridge to suit, 3/6.

AMATRONIX LTD. (Mail order only)
396 Selsdon Rd., South Croydon, Surrey
CR2 0DE

**RECEIVERS AND COMPONENTS
(continued)**

D.I.Y.--All materials and components for construction of high fidelity loudspeaker systems (empty enclosures, BAF wadding, Tygan, Vynair fabric, cross-overs, etc.). Many other audio accessories and speaker kits. 6d. in stamps for lists. P. F. & A. R. HELME, Dept. PE, Summerbridge, Harrogate, Yorks.

TRANSISTOR PANELS

New boxed, size 9in x 6in x 1 1/2in with "Valvo" transistors type OC45 or similar, with full length leads, also an equal number of OA85 diodes, H/S resistors, etc. Built on perforated board in a metal frame.

Panel of 20 transistors, diodes, etc. 20/-
30 - 25/- 60 - 40/-
40 - 30/- 70 - 45/- Postage 2/- per panel.
50 - 35/- 80 - 50/-

TRANSISTOR CAPACITORS (ELECTROLYTIC)

500mF 4V 50mF 10V 10mF 25V
320mF 10V 30mF 10V 8mF 12V
250mF 4V 25mF 25V 6.4mF 64V
200mF 10V 20mF 12V 4mF 64V
100µf 4V 16mF 25V 2mF 12V
64mF 40V 1mF 25V

1/- each, 9/- per doz. Min. order 10/-

COMPUTER PANELS with 40 sil. npn or npn transistors, Diodes and res., 22/6 Post Paid.

COMPUTER PANELS WITH SEMI-CONDUCTORS. Postage 6d per panel

8-OC42 or GET875 + 24-OA81 7/6

24-A1678 (V405A) 550 mc/s PNP + 24 Diodes 15/-

4-OC170 + 2-OC139 + 2-OC42 .. 7/6

9-ASZ20 + 1-T2040 + 27 Diodes .. 7/6

4-OC42 + 6-GET875 + Diodes .. 7/6

2-OC170 + 1-OC306 + OC42 .. 4/-

5-OC23 + 15-OA10 .. 25/-

6-2N388 + 2-2G403 + 2-T2040 8/6

4-OC36 + 8-GET103 + 4-ZS31A .. 25/-

8-ASZ20 + 80 Diodes .. 7/6

6-ASZ21 + 15-OA91 .. 6/-

9-SB240 + 18-OA91 .. 10/-

12-2G106 + 24 Diodes .. 9/6

8-OC72 + 8-OA10 .. 10/-

6-OC44 .. 5/-

6-2N388 .. 7/6

8-OC76 + 8-OA10 .. 7/6

12-2N388 .. 10/-

12-A1678 (V405A) 550 mc/s PNP + 22 Diodes 10/-

36-OA5 .. 6/-

6-GET872 + 8-OA10 .. 3/-

4-OC42 .. 3/-

12-ASZ20 + 80 Diodes .. 9/6

4-GET872 + 8-OA10 .. 3 for 12/-

4-2G106 + 1-2N2410 .. 4/-

2-OC42 + 8-OA47 .. 3/-

2-GET872 + 4-OA10 + RF Chokes 3 for 10/-

24-Sil. h.f. Transistors 15/-

3-GET872 + 3-CEX541, ETC. 22/6

3-OC23 + 6-OA10 + 2-OA5 16/-

TEST CARDS. 6 transistors 20 for 20/-

ELECTROLYTICS 25,000 @ 12V, 16,000 @ 12V, 15,000 @ 10V, 10,000 @ 30V, 4,000 @ 60V, 3,000 @ 80V, 2,000 @ 50V, 1,200 @ 180V, 8/6 Post Paid.

ZENER DIODES 2-4, 2.7, 3.6, 4.75, 5.25, 5.75, 6.2, 6.8, 7.5, 13, 15, 16, 18, 20, 27, 30, 33 volts. 3/6 each, mostly 1 watt

POLYSTYRENE CAPACITORS. 125V, 18, 22, 120, 220, 270, 330, 390, 560, 820, 1,000, 1,200, 1,800, 2,200, 2,700, 3,300, 3,900, 4,700, 5,600, 6,800, 8,200, 0.01, 0.012, 0.015, 2/6 doz. Post/Packing, 1/-

BRAND NEW BOXED CHASSIS containing 2-OC35, 2-OC29 12 WW resistors 25/-

Postage 1/6. **NEW CROSS RADIO**

6 OLDHAM ROAD, MANCHESTER 4

Single channel Radio Control at a price you can afford

RADIO CONTROL PRODUCTS

EXCELLENT RANGE AND PERFORMANCE

TRANSMITTER—

- Crystal controlled tone Tx. 12v. operation. Silicon transistors. In smart case with micro-switch.

Tx only **£6 - 5 - 0**

RECEIVER—

- Sub-miniature Wt 40 grms. Size only 3.5 x 2.8 x 2 cms. Working voltage 4.5v.

Rx only **£4 - 5 - 0**

SUITABLE FOR MODELS OF ALL KINDS
ONLY £10 - 10 - 0 COMPLETE

TRADE ENQUIRIES TO
MODEL MART
3 COMBERTON ROAD
KIDDERMINSTER. Tel. 5879

OR DIRECT FROM

RADIO CONTROL PRODUCTS
38 FRANCHE ROAD
KIDDERMINSTER, WORCS.

RECEIVERS AND COMPONENTS

(continued)

CARBON FILM RESISTORS, 13/- per 100. S.a.e. for component catalogue. SRY ELECTRONICS, 11 Rosedene Ave., Croydon, CR0 3DN. 01-684 0402.

50,000 TRANSISTORS to be cleared in lots of 50 for £1. Types available are germanium similar to OC44, and silicon similar to OC202. All transistors fully tested and guaranteed. Post free. WESTEK, P.O. Box 7, Rickmansworth, Herts.

TAPE HEADS

BSR BRAD. 39/6 pair HIGH GAIN REC./PLAY 2 TRACK 45/-
BSR MALL 39/6 pair ROGEN ERASE 4 TRACK 27/6
REUTER - COLLARO COSMOCORD ERASE 4-TRACK 15/-
ERASE T.E. 2 9 4-TRACK 15/-

TRANSISTORISED FM TUNER
 6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in x 4in x 2 1/2in 3 I.F. stages. Double tuned discriminator. Amp. output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. **£6.70**

SUB-MIN. TRANSISTOR LW/MW/FM TUNER
 Similar to above. Complete with aerial, tuners, dial and instructions **£14**

TUNER DULCI FM/TTS STEREO £23

COMPACT TRANSISTOR FM TUNER
 Oiled Walnut cabinet, brushed gold front panel, vertical styling, internal batteries **£9.19.6**

FM MULTIPLE STEREO ADAPTOR
 Printed circuit biscuit, 4 trans. 6 diodes 9V with full instructions **£4.19.6**

LOUDSPEAKERS

12" TWIN CONE 10 12" 25 watt, 15 ohm, watt PEAK 15 or 35/-
3 ohm GUITAR SPEAKER 25-13K **£5.70**

10" 10 watt, 15 ohm, CERAMIC - 49/6 2" 40 ohm 9/6
MAGNET 2 1/2" 80 ohm

CABINET Teak 23 1/2 x 13 1/2 x 9 1/2", contemp. 12" legs for Tape Recorder and Tuner 4 pole changerover, ideal for models. **99/6**

RELAYS 11 1/2 x 1 1/2", 700 ohm 9-24V, 430 ohm 6-24V **10/-**

TWEETER 3" 16 ohm, 10W CR/0.3kΩ, 25/-
 Horn type Hi-Fi 18,000 c/s

CROSSOVER NETWORK 14/-
 3kΩ, 16 or 3 ohm

REFLEX ONE TYPE WATERPROOF SPKR. 32/-
 5 watt, 3 ohm, 300-16,000c/s PA

CHARGER TRANSFORMER. 21/6
 4 Amp, 216/12 volt
 & Music Relay **£3.10.0** 3/- P/P

SUPER SILICON RECT. T.V., etc., 1,200 PIV 800mA, 5/-; or complete with instr. resistor, condenser, 6/8; 400 PIV HW 6A, 6/-; 200 PIV HW 6A, 6/-; BY100 type, 6 for 10/-.

Jumper lead 6". Croc clips to Phono plug and Std. Jack Adaptor **7/6**
 AD140 8/8 BC108 3/8 NKT226 5/6 OC200 5/6 AF186 11/6 NKT213 5/6 OC45 3/3 OA91 1/6 GET103-113-116-118-119-887-889-890-896-7-8 3/-

CHANGER DECKS
 UA25 BSR with template, Mono. List **£8.19.8**
 UA25 BSR with template, Stereo. List **£7.9.6**
 1025 Garrard with template, Mono. List **£7.7.6**
 1025 Garrard with template, Stereo. List **£7.17.6**

PLINTH in simulated teak. Complete with Clearview rigid perspex cover for 1025. **£4.15.0**
 P/P on Decks, Plinth and Cover 7/6

SWITCH ROTARY RECIPROCATING 4 Position, 16amp. Single hole fixing, with instructions. List 14/7 **5/6**

C90 CASSETTE 10/3. C90 14/3. 3 Post free

Stamped envelope for full selection and bargain offers in MULTIMETERS, RADIOS, BABY ALARMS, INTERCOMS, WALKIE-TALKIES, RECTIFIERS, SINCLAIR, DULCI, AND EAGLE Lists. UNDER £1-P. & P. 6d., £1 to £3-1/6. over £3-2/6. C.O.D. 3/6. MAIL ORDER ONLY.

DURHAM SUPPLIES
 367 KENSINGTON STREET
 BRADFORD 8, YORKSHIRE

RECEIVERS AND COMPONENTS

(continued)

BRAND NEW ELECTROLYTICS, 15 Volt, 1, 2, 5, 6, 8, 10, 15, 20, 30, 40, 50, 100, 200 μF. 7/6 dozen, postage 1/-. The C.R. SUPPLY CO., 127 Chesterfield Rd., Sheffield, S8 0RN.

TRANSISTORISED REVERBERATION

Six transistor circuit, all components £7.10.0. post free. (Case 34/- extra, P. & P. 2/6). Circuit and construction details 1/- (free with kit).

TRANSISTORISED SIGNAL INJECTOR 19/6 P. & P. 1/6. Catalogue of components etc. 1/-.
 Wilsic Electronics Ltd, 6 Copley Road, Doncaster, Yorks.

PEAC OPERATIONAL AMPLIFIERS, ready built on printed circuit board. Tested and guaranteed. 34/- each, post free. WESTEK, P.O. Box 7, Rickmansworth, Herts.

R & R RADIO

51 Burnley Road, Rawtenstall

Rossendale, Lancs

Tel.: Rossendale 3152

VALVES BOXED, TESTED & GUARANTEED

BF80	3/-	EBC41	4/6	PY33	5/-
EBF89	3/6	PCC84	3/-	PY81	3/6
ECC82	3/-	PCF80	3/-	PY82	3/-
ECL80	3/-	PCF82	3/6	UI91	4/6
EF80	1/6	PCL82	4/-	6F23	5/-
EF85	3/-	PLC83	4/-	30F5	2/6
EY86	4/-	PL36	5/-	30L15	5/-
EL41	5/-	PL81	4/-	30P12	4/6
EZ40	4/6	PL83	4/-	30C15	5/-

POST. ONE VALVE 9d. TWO TO SIX 6d.

OVER SIX POST PAID.

WE ARE BREAKING UP COMPUTERS

EX COMPUTER PRINTED CIRCUIT PANELS

2in x 4in packed with semiconductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards 10/-, P. & P. 2/-. With a guaranteed minimum of 35 transistors. **SPECIAL BARGAIN PACK.** 25 boards for £1. P. & P. 3/6. With a guaranteed minimum of 85 transistors. 100 boards 65/-. P. & P. 6/6. With a guaranteed minimum of 350 transistors. **TRIMMER POTS** on 2" x 4" boards + other components. 100Ω, 500Ω, 15k or 20k. Please state requirements. 5 bds. for 10/- + 2/- P. & P. **PANELS** with 2 power transistors sim. to OC28 on each board + components. 2 boards (4 x OC28) 10/-. P. & P. 2/-. **NPN GERMANIUM TOS 1 WATT POWER TRANSISTORS** on small heat sink, on 2in x 4in panel. 5 for 10/-, P. & P. 2/-. **POWER TRANSISTORS** sim. to 2N174 ex eqpt., 4 for 10/-, P. & P. 2/-. **POWER TRANSISTORS** sim. to 2N174 on Finned Heat Sink (10D) 4 for £1, P. & P. 5/-. **LONG ARM TOGGLE SWITCHES** ex eqpt. SPST 13/6 doz., DPST 15/- doz. P. & P. all types 2/- doz.

ORGAN BUILDERS' SPECIAL 500 TO 18 TRANSISTORS on panels. £4, P. & P. 6/-. **OVERLOAD CUT OUTS.** Panel mounting in the following values... 5/- each. 2, 3, 4, 7, 10 amp. P. & P. 1/6. **MINIATURE GLASS NEONS, 12/6 doz.** P. & P. 1/6. **150 PIV, 10 amp. DIODE BRIDGE RECTIFIERS** on finned heat sink. 12/- + 2/-, P. & P. ea. **150 PIV, 20 amp. DIODE BRIDGE RECTIFIERS** on finned heat sink. £1 ea. + 3/- P. & P. **LARGE CAPACITY ELECTROLYTICS** 4 1/2in, 2in diam. Screw terminals. All at 6/- each + 1/6 each P. & P. 4,000mF 72V d.c. wkg. 10,000mF 25V d.c. wkg. 6,600mF 45V d.c. wkg. 16,000mF 25V d.c. wkg. 25,000mF 12V d.c. wkg.

KEYTRONICS, 52 Earls Court Road
 London, W.8. Mail order only

ELECTRICAL

AIRCRAFT-PLUS GENERAL V.H.F. TELECOMMUNICATIONS BAND REC.

Listen to the thrills of Aircraft, Pilots, and Airports at work. Also Civil Depts., Fire and Ambulance services. Gas and Electricity Depts. Ideal for receiving 2 metre amateurs. Gives super reception within the range of all transmissions. A fully transistorised receiver covering 97-147Mc/s V.H.F. broadcasts. Robust attractive 2-tone finished metal cabinet size approx. 7 x 4 x 4in. Operates from a 9 volt internal battery. Speaker or earphone output plus chrome telescopic aerial. Only **£8.19.6**. Carr. and insurance 10/6. G.W.O. or COD.

SURPLUS BARGAINS

HEAVY DUTY ACCUMULATORS
 Type 1 (6 volt) 40AH. In metal cabinet. Size approx. 10 x 9 x 8in. Complete with output socket, carrying strap. Brand new and unused. Worth £10 each. Our Price 55/-, carriage and insurance 15/-.

Type 2 (6 volt) 16AH. In sturdy wooden cabinet with carrying strap. Worth 27 each. Brand new and boxed, only 52/6 each, p. & p. 12/6.

FIELD TELEPHONES

Type F. Housed in a portable wooden case. Ideal for indoor/outdoor communication up to 10 miles. Absolutely brand new. Price only **£5.19.6** per pair, carriage and insurance 15/-.

18 1/2 Headphones and Mike. Not new but in working order. Only 7/6 per set, p. & p. 4/6.

Tannoy Mikes. Moving coil. A. New, 9/6 each, p. & p. 3/6 (heavy duty, ideal for P.A. work).

High quality moving coil headphones and hand microphone. Brand new, only 25/-, p. & p. 6/-. Suitable for most applications (cost approx. £3 per pair).

AIR/SEA TRANS/REC.

Compact V.H.F. Trans./Rec. Fits in the pocket. Consists of Mike/Speaker, amplifier, aerial, transmitter and receiver. Were made to operate up to 100 miles depending on terrain. Operates from dry batteries. Completely self-contained. Cost Govt. over 250 each. Regulations state must not be operated in UK so please mention "For Dismantling purposes only" when ordering. Price **£2.19.0** each, p. & p. 10/-. Two sets for **£5.0.0**, post free. Four sets **£8**, carriage free. Bulk sale of 10 sets **£15**, carriage **£1**. Export enquiries invited.

PRECISION PANEL METERS

Brand new, boxed and fully guaranteed. With fixing nuts and bolts. Size approx. 3 1/2in square. 0-500 volts FSD. As used by leading laboratories. Ex-stock, only 35/-, p. & p. 8/-. Two for **£3**, post free.

HEAVY DUTY POWER SUPPLY UNITS

Bulk Purchase. Famous manufacture. Must have cost nearly £50 each. Input 200/250 volts 50/60 a.c. Output 250 volts d.c. at approx. 176mA. 6.3/12 volts at approx. 4 amps a.c. Robust metal rack mounting cabinet, size approx. 19 x 15 x 8in. Price only **85/-**, carriage and insurance 15/-. All units are fully fused and metered.

SMOOTHING UNITS

Beautifully made pieces of equipment. 12 volts or 24 volts d.c. input gives a fully smoothed fully regulated d.c. output. Worth £30 each. Robust metal cabinet with provision for standby battery. Brand new in maker's cartons. Price **65/-**, p. & p. 15/-.

New walk-round scientific store now open at 38 Bridgend, Meadow Lane, Leeds 1. Open weekdays 9 a.m.-6 p.m. Plus all day Saturday. All items available for inspection and demonstration.

SCOOP PURCHASE TRANSFORMER SALE

Bulk purchase enables us to offer the following transformers at these ridiculously low prices. Made by a famous manufacturer and fully tested and guaranteed. **Charger Transformers.** 0.9-16V 2A. 8/8 each, p. & p. 2/6. Two for 17/8 postfree. **Transformer Power Pack Types.** 6.3V at 2A, 7/8 each, p. & p. 2/6. 12V at 2A, 12/6 each, p. & p. 2/6.

GLOBE SCIENTIFIC LTD

DEPT. P.E., 24 CAWOODS YARD,
 MILL STREET, MARSH LANE, LEEDS 9
 Callers welcome for a demonstration

ELECTRICAL (continued)

**240 VOLT
ELECTRICITY
ANYWHERE**



BEST EVER 200/240 VOLT "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY
Exclusive World Scoop Purchase, The fabulous Mk.2D American Heavy Duty Dynamotor Unit with a Massive 220 watt output and giving the most Brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. Brand New and Fully Tested. Only £4.19.6 + 10/6 postage. C.O.D. with pleasure, refund guarantee. Please send S.A.E. for illustrated details.
Dept. PE, STANFORD ELECTRONICS
Rear Derby Road, North Promenade
BLACKPOOL, Lancashire

TAPE RECORDERS

TAPES TO DISC—using finest professional equipment—45 r.p.m. 22/- S.A.E. leaflet, DEROY, High Bank, Hawk Street, Carnforth, Lancs.

BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 9v; 7.1v; 6v; 4.1v (single output) 39/6 each. P. & P. 2/9. 9v + 9v; 6v + 6v; or 4.1v + 4.1v (two separate outputs) 42/6 each. P. & P. 2/9. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.E.), 31 Oliver Road, London. E.17

CRESCENT RADIO LTD.

(electronic component specialists)

For all regular components try
40 Mayes Road, Wood Green, N.22
For surplus components and equipment try
11 Mayes Road, Wood Green, N.22
Printed circuit board, 8 x 6in 2/- each
Zener diode 8.2 volt, 400mW 2/6 each

BARGAIN BOARDS

Transistors, diodes, resistors, capacitors and various components all mounted on computer board, 2/- each, 3 for 5/-, 7 for 10/- and 15 for 20/-

MODEL MOTOR

12 volt, 9,000r.p.m., 400mA 4/6 each

TRANSISTORS & DIODES

AC127 4/6 each
OC19 5/- each
2N2926 3/6 each
BC147 4/6 each
BYZ12 7/6 each
OA47 1/- each
AA120 2/6 each
OA6 1/6 each
M3 1/- each

BARGAIN PACK

50 unmarked and untested transistors 10/6 per pack

SILICON DIODE RECTIFIERS

750mA, 800p.i.v. 3/3 each

COMPONENT BARGAINS

D.P. rotary ON/OFF mains switches 2/- each
Car fuseholders complete with lead and tags 1/3 each
Low impedance transistor earpiece 1/6 each
Slab aerial transistor type 2/9 each
LA3 type pot core 45mh 4/6 each
2 1/2in. transistor loudspeaker 5/6 each
80 ohm Rev counters (tape recorder type) 3/- each

CASSETTES

C60 12/6 each
C90 18/6 each

With our new premises in Mayes Road we can now offer an even wider selection of components for the home constructor and enthusiast.

POSTAGE WITH ORDER PLEASE; P.S.—Our new catalogue is now available at 1/6 per copy

WENTWORTH RADIO

SEND S.A.E. FOR NEW STOCK LIST

104 SALISBURY ROAD
HIGH BARNET

01-449 3087

SPECIAL NO. 1	SPECIAL NO. 2	SPECIAL NO. 3	ACY18	4/6	
AC127	4/-	BC108	3/3	BY127	4/-
NKT123	4/11	OA200	2/-	2N2218	8/9
NKT124	8/9	OA81	1/6	2N2219	8/9
NKT125	5/9	OA95	1/6	2N2368	4/6
NKT126	6/3	OC44	2/6	2N2369	5/6
NKT135	5/3	OC45	1/8	2N2369A	5/6
NKT137	7/6	OC70	4/6	2N2926	2/9
NKT274	4/-	OC71	2/3	2N3391	6/-
NKT275	4/-	OC72	2/6	2N3391A	6/9
NKT281	5/-	OC74	3/9	2N3392	4/9
NKT453	8/-	OC75	3/9	2N3393	3/9
NKT603F	6/-	OC78	5/-	2N3394	3/9
NKT613F	7/-	OC81	2/2	2N3402	6/6
NKT674F	5/6	OC81D	2/3	2N3403	7/9
NKT713	5/3	OC170	2/3	2N3404	7/6
NKT734	5/4	OC171	2/3	2N3405	9/-
NKT736	4/6	OC172	3/6	2N3414	4/6
NKT773	4/9	RESISTORS ±W 3d.		Cash with order	

**BUILD YOUR CIRCUITS
ON
VEROBOARD**



—the Universal Wiring Board—
obtainable from your local Retailer

Trade enquiries to:
NORMAN ROSE (ELECTRICAL) LTD.
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to:
VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford, Hants

Burgess instant heat solder gun

Only the tip heats—but fast! About 7 seconds! Pre-focused lamp lights the job up. Exclusive full-length trigger on pistol grip eases finger fatigue. Finger-tight is right for screw-in tips — no pliers needed. Kit complete with conical tip, chisel tip, 6" extension barrel, double-ended probe, gun and solder. £4 12 6.
Full details and nearest stockist from:



Burgess Products Co Ltd,
Sapcote, Leicester LE9 6JW



10W AMPLIFIER

SSAR3. 10W push-pull output. TW99 output trans. 4 Valve EF94, ECC81, EL90 (2). Fully constructed on chassis. New and boxed with circuit drawing. £2.10.0. P. & P. 10/-.
MIXER UNITS. Type 18. H.F. M.F., L.F. Valve V882. 10/- P. & P. 2/6.

FLEXIBLE METAL TUBING. Galvanised 3/16in. dia. 35/- 100ft. P. & P. 7/6.

FIELD TELEPHONES TYPE "F". 32/6. P. & P. 7/6.

CHASSIS UNIT. 13 valves. ECC82(5), EB91(6), EF91(2). 60 Resistors, Capacitors, etc. Valve cans and bases. Multicon Plugs. 30/- P. & P. 6/-.

RESISTORS. Mixed Parcel of 200. 20/- P. & P. 2/6.

RESISTORS. Variable. Mixed Parcel of 30. 20/- P. & P. 2/6.

TRANSFORMERS


SSTR 894. Pri. 220-230-250V. SSTR 073. Pri. 220-230V.
Sec. 6.3V (2A), 300-350-390V (35mA). Sec. 35V(0.5A).
80-90-100V(10mA). 6.3V(2A). 225-0-225V(27mA). 25/- P. & P. 5/-.

**S.A.E. FULL LIST
STATUS SUPPLIES**

Status House, Wilkinson Avenue, West Park Drive, Blackpool. Tel. 62788 (2 lines)

12in. SUPERB £15

The exceptional quality and performance of the "De-luxe MKII" brings truly exceptional sound from a single loudspeaker, recreating the musical spectrum virtually flat ±5db. 20 to 17,000 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a massive Baker "FERROBA" magnet assembly having a flux density of 16,500 gauss and a total flux of 176,000 Maxwells. Bass resonance 22-26 c.p.s. Rated 20 watts. Voice coils available 8 or 15 ohms. Suitable for all High Fidelity Systems. A high quality loudspeaker providing clear reproduction of the deepest bass and highest treble.

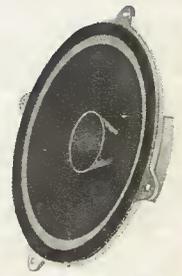

Further details and 48 page Enclosure Manual 5/9 post paid.
Baker Reproducers Ltd
Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684 1665

VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had your copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION OR REFUND OF FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

ELECTRONIC ENG.

Advanced Electronic Eng.—
Gen. Electronic Eng.—
Applied Electronics—
Practical Electronics—
Radar Tech.—
Frequency Modulation—
Transistors.

ELECTRICAL ENG.

Advanced Electrical Eng.—
General Electrical Eng.—
Installations—
Draughtsmanship—
Illuminating Eng.—
Refrigeration—
Elem. Elec. Science—
Elec. Supply—
Mining Elec. Eng.

CIVIL ENG.

Advanced Civil Eng.—
General Civil Eng.—
Municipal Eng.—
Structural Eng.—
Sanitary Eng.—
Road Eng.—
Hydraulics—
Mining—
Water Supply—
Petrol Tech.

RADIO & T.V. ENG.

Advanced Radio—
General Radio—
Radio & TV Servicing—
TV Engineering—
Telecommunications—
Sound Recording—
Automation—
Practical Radio—
Radio Amateurs' Examination.

MECHANICAL ENG.

Advanced Mechanical Eng.—
Gen. Mech. Eng.—
Maintenance Eng.—
Diesel Eng.—
Press Tool Design—
Sheet Metal Work—
Welding—
Eng. Pattern Making—
Inspection—
Draughtsmanship—
Metallurgy—
Production Eng.

AUTOMOBILE ENG.

Advanced Automobile Eng.—
General Auto. Eng.—
Auto. Maintenance—
Repair—
Auto. Diesel Maintenance—
Auto. Electrical Equipment—
Garage Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power?
A.M.I.E.R.E., B.Sc.(Eng.), A.M.S.E., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A.,
A.I.O.B., A.M.I.Ex., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., C.ENG.,
CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
316A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointments Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

132 PAGES OF EXPERT CAREER - GUIDANCE

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Electronics, Radio, T.V., Etc., A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.C. Certificate Practical Electronics Engineering Practical Radio Radio & Television Servicing Automation

INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES"—send for your copy now—FREE and without obligation.



POST COUPON NOW!

TO B.I.E.T., 316A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME

ADDRESS

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

Published about the 15th of the month by IPC Magazines Ltd., Tower House, Southampton Street, London, W.C.2, at the recommended maximum price shown on the cover. Printed in England by THE CHAPEL RIVER PRESS, Andover, Hants. Sole Agents—Australia and New Zealand: GORDON & GOTCH (A/sia) Ltd.; South Africa and Rhodesia: CENTRAL NEWS AGENCY LTD.; East Africa: STATIONERY & OFFICE SUPPLIES LTD. Subscription rate including postage for one year: To any part of the World £2 2s. 0d.

ENGLANDS LEADING COMPONENT & EQUIPMENT CENTRES

SOLID STATE—HIGH FIDELITY

AUDIO EQUIPMENT

Mono or Stereo Audio. Equipment developed from Dinsdale MkII—each unit or system will compare favourably with other professional equipment selling at much higher prices.

COMPLETE SYSTEMS FROM £15.5.0

THE FINEST VALUE IN HIGH FIDELITY—CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS

All units available separately

SEND FOR FREE BROCHURE (No. 21) TODAY!
DEMONSTRATIONS DAILY AT '303' EDGWARE ROAD



ELECTRONIC ORGANS KITS TO BUILD YOURSELF AND COMPLETE UNITS

Acclaimed by everyone The MAYFAIR

A completely new development in portable electronic musical instruments and a new field for the home constructor. The 'MAYFAIR' produces a multitude of the most pleasing sounds with a wide range of tone colours suitable for classic or popular music. The organ is fully polyphonic, that is full chords can be played over the entire keyboard. Supplied as a kit of parts which includes 185 transistors, printed circuit panels, special fully sprung and depth of touch adjusted keyboard, attractive vinyl covered cabinet with carry handle.

Deferred terms available
COMPLETE KIT
Deposit £25.18.0
12 monthly payments of £7. Total £142.18.0
BUILT AND TESTED
Deposit £26.8.0 and 12 monthly payments of £8. Total £144.8.0



THE MAYFAIR 99 GNS BROCHURE?

★ The GROSVENOR

The Grosvenor is designed for the more ambitious musician and has a much wider range than most commercial organs. It comprises two four-octave (48 note) keyboards and a thirteen-note pedal board. It has four pitches (i.e. 8ft, 4ft, 2ft, 1ft) on the upper or solo keyboard, three pitches (i.e. 16ft, 8ft, 4ft) on the lower or accompaniment keyboard, two pitches (i.e., 16ft, 8ft) on the pedal board. Variable sustain on the solo keyboard and variable vibrato on both keyboards. It has 15 voices in the solo tone-forming unit, 10 voices in accompaniment tone-forming unit and 4 voices in the pedal tone-forming unit. All components and kit sections are available separately including the Oak Console at £55.18.0.

A complete detailed and illustrated construction manual is provided gratis and its use may be purchased separately. All parts supplied are fully guaranteed. Full after sales service and advice freely available. Once built the 'MAYFAIR' and 'GROSVENOR' will then provide years of enjoyable entertainment. Call in—See them for yourself.

THE GROSVENOR KITS FROM £220 terms available BROCHURE 98



PRACTICAL ELECTRONICS—ELECTRONIC ORGAN KIT

We are able to supply Parts as described in this series. Details on request

ORGAN COMPONENTS: COMPLETE RANGE IN STOCK + 49 AND 61 NOTE KEYBOARDS + 2 TO 5 PAIR COIL CONTACTS + COILS AND CHOICES + REVERBERATION SPRINGS AND UNITS + STOP TABS AND ASSEMBLES + PEDAL BOARDS + RHODIUM AND GOLD CLAD WIRE, ALSO PRINTED CIRCUITS ETC. COMPLETE RANGES FOR TRANSISTORISED ORGANS. ASK FOR NEW PRICE LISTS WITH DETAILS LEAFLET 95

INTEGRATED TRANSISTOR AMPLIFIERS

MA66 12 WATTS STEREO

We are pleased to offer two new designs with the choice of either mono or stereo systems. These BRITISH DESIGNED UNITS favour the user in so many ways—with fantastic power and quality with far greater adaptability, with freedom for battery or mains operation.



for complete listening satisfaction choose either the—

MA7 MONO OR STEREO MA66 EITHER MODER. £8.10.0 £16.10.0 OPTIONAL MAINS UNIT P520 at 40p 4.

Illustrated leaflets 12 and 14 FREE on request

DO IT YOURSELF MW/LW PORTABLE

New printed circuit design with full power output. Fully tunable on both mw/lw bands. 7 transistors plus diode, push-pull circuit. Fitted 5 inch speaker, large ferrite aerial and Mullard transistors. Easy to build with terrific results. All local and Continental stations.

TOTAL COST £6.19.6. P.P. 4/6 TO BUILD Send for Brochure 1

NEW MODELS NOMBEX TRANSISTORISED

Test Equipment

MODEL	PRICE	Leaflet
	£ s. d.	No.
29s R.F. Generator	21 0 0	—
29x Xtal R.F. Generator	29 10 0	35
30 Audio Generator	19 10 0	24
31 R.F. Generator	12 10 0	25
32 C.R. Bridge	10 0 0	26
33 Inductance Bridge	20 0 0	29

QUALITY CAR RADIOS

A precision engineered car radio that's a perfect companion for long hours on the road. Has quick push-button station for immediate station selection and choice of Medium or Long wave frequency. Output of 50 watts ensures crisp, too quality sound even at high motoring speeds. Includes full accessories and instructions.

POSITIVE/NEGATIVE EARTH PRICE £12.12.0, pp. 4/6 MANUAL as above £2.18.8. but with single MW/LW Push Button.

MULLARD 1 WATT AMPLIFIER

PORTABLE TRANSISTOR UNIT with volume control. Many uses: Intercom, Baby Alarms, Guitar Practice, Telephone or Record Player Amplifier. Optional Revine covered Wood cabinet 12 x 9 x 4, 12.8. Uses PPS battery.



45/- pp. 4/6. Ask for Leaflet 2.

BUILD A QUALITY TAPE RECORDER

To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORDKIT. This comprises a special high quality 6 vave amplifier and pre-amplifier which comes to you assembled on its printed circuit board—in fact everything needed down to the last screw FOR MAKING A SUPERB TAPE RECORDER, which, when built, will compare favourably with instruments costing twice as much, yet you need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY AND SUCCESS ASSURED.



2 Track 28 gns. P.P. 22/6 either model. 4 Track 39 gns. KIT comprises: Deck, Amplifier, Cabinet and speaker, with MICROPHONE 7 in 1,200 Hz, tone, 2 x 1/2 inch. ALL UNITS AVAILABLE SEPARATELY. ASK FOR BROCHURE 6. Today's Value £40.

VHF FM SUPERHET TUNER MKII

5-MULLARD TRANSISTORS & 4 DIODES + 300 Kc/s BANDWIDTH + PRINTED CIRCUIT CONSTRUCTION + HIGH FIDELITY REPRODUCTION MONO AND STEREO. A popular VHF FM Tuner now used throughout the country for quality reception of monophonic and, with the decoder stereophonic broadcasts. There is no doubt about it—VHF FM gives the real sound. Excellent stability, economically priced. TOTAL COST £2.18.8. DECODER £2.18.8. ASK FOR LEAFLET 3. (CABINET 20/-)



NEW—MALLORY LONG LIFE MERCURY BATTERIES

50% OFF LIST PRICES
*RM12 1.35 volts 3600 mAh Pack of 6, Size 2 1/2 dia. OUR PRICE 5/- each
*RM22 1.35 volts 350 mAh Pack of 6, Size 2 1/2 dia. OUR PRICE 10/- each
Easy split into eight 1.35v cells. These cells are ideal for any application where SMALL SIZE HIGH CAPACITY and LONG LIFE are required. QUANTITIES AVAILABLE.



GARRARD RECORD DECKS

NEW LOW PRICES
BRAND NEW All below list price

	£ s d
2025 Mono/Stereo	8 8 0
3000 DM with 9TAHC	9 9 6
SP25 Mk II	11 9 6
A750 Mk II	15 10 0
3500 Mono/Stereo 9TAHC	12 19 6
401	28 10 0
AP75	17 10 0
SL55	11 9 6
SL65	14 14 0
SL75	29 0 0
SL95	35 0 0
A70 Mk II	12 12 0

Send for new 8-page brochures 16, 17. Complete range of accessories available

TRANSISTORS—SEMICONDUCTORS

MANUFACTURERS—DISTRIBUTORS
We publish a QUANTITY, SEMI-CONDUCTOR BULLETIN listing over 500 different devices available FROM STOCK in medium to large quantities at KEEN PRICES coupled with PROMPT DELIVERIES. TO OBTAIN YOUR COPY, WRITE TO US (on Company Headed Note-paper please) requesting our SEMI-CONDUCTOR BULLETIN. FOR TELEPHONE QUOTATIONS, PHONE (01) 723 1068/9 Extn. 4 (01) 723 0401 Extn. 4.

SPECIAL DECK OFFERS
• 3 speed 9 VOLT RECORD DECK. Complete with MONO CARTRIDGE. BRAND NEW. PRICE 60/-, pp. 3/6.
• AS ABOVE BUT MAINS OPERATED FITTED STEREO CARTRIDGE. PRICE 82/-, pp. 3/6.

TRANSISTORS—SEMICONDUCTORS

COMPLETELY NEW 1969 LIST OF 1000 types. Send for your FREE COPY TODAY. (list 36)

S.C.R.'s from 5 -
Field Effect Transistors from 9 6
Power Transistors from 5 -
Diodes and Rectifiers from 1 6

Hi-Fi equipment to suit EVERY POCKET

VISIT OUR NEW HI-FI CENTRE at 309 EDGWARE ROAD AND SAVE UP TO £25 ON SEPARATE UNITS OR THE SYSTEM OF YOUR CHOICE for all leading makes

- AMPLIFIERS
- TUNERS
- DECKS
- SPEAKERS
- MICROPHONES
- TEST EQUIPMENT
- HEADPHONES
- CARTRIDGES, etc.



All with Terrific Savings

It will PAY YOU to pay us a VISIT!

COMPLETE SYSTEMS from £46—Saves £12.10.0!
SEND FOR NEW 8-PAGE ILLUSTRATED HI-FI LIST 16 17

Fully Illustrated CATALOGUE

COMPLETELY NEW 9th EDITION (1969)

The most COMPREHENSIVE—CONCISE—CLEAR COMPONENTS CATALOGUE

Complete with 10 - worth discount vouchers FREE WITH EVERY COPY
• 32 pages of transistors and semi-conductor devices, valves and crystals.
• 210 pages of components and equipment.
• 70 pages of microphones, decks and Hi-Fi equipment.



6,500 ITEMS
320 BIG PAGES
Send today 7/6 Post etc 2/-

HENRY'S RADIO LTD
OPEN MON—SAT. 9 a.m.—6 p.m. THURS. 9 a.m.—1 p.m.

303 Edgware Road, London, W.2. Mail Order Dept. all types of Components, Organ Dept. (01) 723-1008/9
309 Edgware Road, London, W.2. High Fidelity Sales, P.A. and Test Equipment, Record Decks (01) 723-6963