

PRACTICAL

# ELECTRONICS

AUGUST 1971

20 p

## War Games COMPUTER



# ADCOLA Soldering Instruments add to your efficiency

## THE NEW 'INVADER'

### ADCOLA L.646

PRICE  
**£1.85**

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*. Standard temp. 360°c at 23 watts. Special temps. from 250°c—410°c.

#### \*Additional Stock Bits (illustrated) available

#### COPPER

- B 38**  $\frac{1}{4}$ " — 3.2 mm CHISEL FACE
- B 14**  $\frac{3}{8}$ " — 2.4 mm CHISEL FACE
- B 24**  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE
- B 12**  $\frac{1}{4}$ " — 4.75 mm EYELET BIT
- B 58**  $\frac{1}{4}$ " — 6.34 mm CHISEL FACE

#### LONG LIFE

- B 42 LL**  $\frac{1}{4}$ " — 4.75 mm CHISEL FACE
- B 38 LL**  $\frac{1}{4}$ " — 3.2 mm CHISEL FACE
- B 14 LL**  $\frac{3}{8}$ " — 2.4 mm CHISEL FACE
- B 44 LL**  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



\* Write for price list and catalogue

**ADCOLA PRODUCTS LTD.,**  
(Dept. L), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.  
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

# YATES ELECTRONICS (FLITWICK) LTD.

#### RESISTORS

½W Iskra high stability carbon film—very low noise—capless construction. ¼W Mullard CR25 carbon film—very small body size 7.5 × 2.5mm. 4W Erie wire wound.

Power watts	Tolerance	Range	Valves available	Price	100+
½	5%	4.7Ω-2.2MΩ	E24	1-99	0-8p
½	10%	3.3MΩ-10MΩ	E12	1-0p	0-8p
¼	10%	1Ω-3.9Ω	E12	1-0p	0-8p
¼	5%	4.7Ω-1MΩ	E12	1-0p	0-8p
¼	10%	1Ω-10Ω	E12	7½p	7½p

Quantity price applies for any selection. Ignore fractions on total order.

#### DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.  
E12 pack 325 resistors **£2.50**.  
E24 pack 650 resistors **£4.80**.

#### MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2½p. 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p. 0.047μF, 0.068μF, 0.1μF, 4p. 0.15μF, 6p. 0.22μF, 7½p. 0.33μF, 11p. 0.47μF, 13p.  
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p. 0.1μF, 0.15μF, 0.22μF, 4p. 0.33μF, 6p. 0.47μF, 7½p. 0.68μF, 11p. 1.0μF, 12½p.

#### MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p. 0.033μF, 0.047μF, 0.068μF, 3½p. 0.1μF, 4p. 0.15μF, 4p. 0.22μF, 5p. 0.33μF, 6½p. 0.47μF, 8½p. 0.68μF, 11p. 1.0μF, 13p.

#### MYLAR FILM CAPACITORS

100V: 0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 2½p. 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3½p.

#### CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

#### CAPACITOR DEVELOPMENT PACK

Selection of 100 ceramic and polyester capacitors, 100pF to 1.0μF, **£2.90**.

#### ELECTROLYTIC CAPACITORS—One Price—5p Each

Mullard C426 series (μF/V): 25/6.4, 50/6.4, 100/6.4, 200/6.4, 320/6.4, 16/10, 32/10, 64/10, 125/10, 200/10, 10/16, 20/16, 40/16, 80/16, 125/16, 6.4/25, 12.5/25, 25/25, 50/25, 80/25, 4/40, 8/40, 16/40, 32/40, 50/40, 2.5/64, 5/64, 10/64, 32/64.

Miniature P.C. mounting (μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

#### POTENTIOMETERS

Carbon track 5kΩ to 1MΩ, log or linear (log ½W, lin ½W). Single, 12p. Dual gang (stereo), 40p.

#### SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0-1 matrix). Sub-miniature 0.1 watt, 4p each. Miniature 0.25 watt, 5p each.

#### SEMICONDUCTORS

AC126	15p	BFY52	22½p	OC81	15p	2N3055	72p
AC127	15p	BSY56	30p	OC82	15p	2N3702	15p
AC128	15p	BSX21	25p	ORP12	47½p	2N3703	14p
AD140	40p	BY124	7½p	IN4001	7½p	2N3704	17½p
AF115	17½p	BYZ10	30p	IN4002	10p	2N3705	15p
AF117	17½p	BYZ13	20p	IN4003	11p	2N3706	12p
BC107	14p	OA85	7½p	IN4004	12½p	2N3707	18½p
BC108	10p	OA91	7½p	IN4005	14p	2N3708	10p
BC109	10p	OA202	7½p	IN4006	15p	2N3709	11p
BFY50	22p	OC71	15p	IN4007	16p	2N3710	12p
BFY51	19p	OC72	15p	2N2926	11p	2N3711	14p

#### ZENER DIODES

400mW 5% 3.3V to 30V, 17p.

#### VEROBOARD

	0.1	0.15	0.15	0.1
2½ × 3½	22p	16p	17 × 3½ (plain)	52½p
2½ × 5	24p	24p	17 × 2½ (plain)	37½p
3½ × 3½	24p	24p	2½ × 5 (plain)	17½p
3½ × 5	27p	27p	2½ × 3½ (plain)	15p
17 × 2½	75p	57½p	Pin insertion tool	47½p
17 × 3½	100p	75p	Spot face cutter	37½p
17 × 5 (plain)	—	75p	Pkt. 50 pins	20p

#### ROTARY SWITCHES

2P2W, 1P12W, 2P6W, 3P4W, 4P3W, 22½p.

#### PLUGS AND SOCKETS

Standard ½in screened	17½p	2.5mm insulated	7½p
Standard ½in insulated	14p	3.5mm insulated	7½p
Stereo ½in screened	35p	3.5mm screened	12½p
Standard ½in socket	15p	2.5mm socket	7½p
Stereo ½in socket	17½p	3.5mm socket	7½p

#### BRUSHED ALUMINIUM PANELS

12" × 6" = 25p; 12" × 2½" = 10p; 9" × 2" = 7p.

C.W.O. please. Post and packing, please add 10p to orders under £2. Data sheets are available for most of the components listed, and will be sent free on request.


8E39 ELSTOW STORAGE DEPOT, KEMPSTON HARDWICK, BEDFORD

# Discosound

## P. A. AND DISCOTHEQUE EQUIPMENT

— A COMPREHENSIVE RANGE COVERING EVERY REQUIREMENT

AMPLIFIERS, MIXERS, LIGHT CONTROL UNITS.

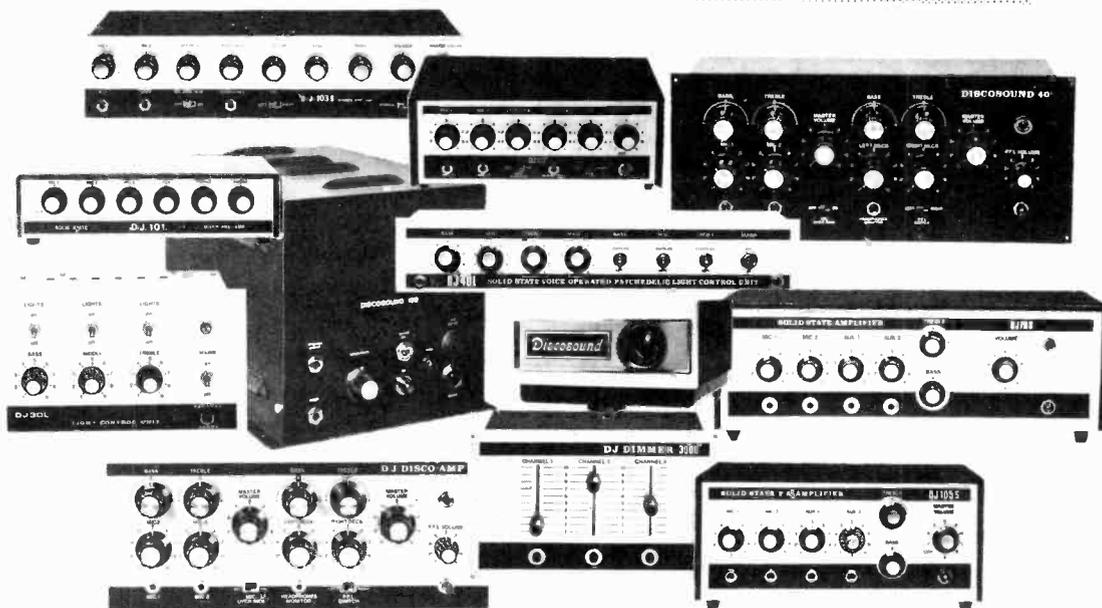

### D.J.101 Mixer Pre-Amplifier

Six inputs allow full mixing facilities for all types of equipment. 9V battery operation.  
Size: 10½in x 2½in x 4¼in.  
Suggested Retail Price £14

### D.J.102 Discotheque Mixer Pre-Amplifier

Four inputs each with its own volume control plus master volume control, PFL monitoring and mic override switches. Size: 10½in x 4in x 4in.  
Suggested Retail Price £25

### D.J.105S P.A. Amplifier

4-channel mixing facilities each with separate inputs and volume controls. 30W r.m.s. power output— a.c. mains 200/250V a.c. Size: 11½in x 5in x 6in.  
Suggested Retail Price £41

### D.J.70S Integrated Mixer Amplifier

Power output 70W r.m.s. 4-channel mixer with separate inputs and volume controls, plus master volume and separate bass and treble controls.  
Size: 16½in x 5in x 6in.  
Suggested Retail Price £63

### D.J. Disco-Amp.

Designed specifically for use with discotheques. Power output 100W r.m.s. Two mic. inputs and two gram inputs, with independent volume controls plus bass and treble controls. Incorporates many exclusive features. Front panel size: 16½in x 7in.  
Suggested Retail Price £85

### Discosound 40 Discotheque Pre-Amplifier

Features independent inputs and volume controls for two microphones and two turntables plus separate bass, treble and master volume controls. Self-powered and ideal for use with Discosound 100 Power Amplifier (is capable of running 10 of these power amplifiers—total 1,000W). Front panel size: 12½in x 7in.  
Suggested Retail Price £40

### Discosound 100 Power Amplifier

100W r.m.s. power amplifier (at 8 ohms) utilising all silicon transistors and features full automatic overload against short or open circuits. Frequency response 20-20,000Hz ±3dB. Distortion less than 1% at 70W r.m.s. ±1dB. Size: 10½in x 8in x 7in.  
Suggested Retail Price £49.50

### D.J.103S Stereo Pre-Amplifier

A high quality stereo discotheque pre-amp unit. Incorporating two microphone and two turntable inputs each with independent volume control, plus bass, treble, balance and master volume control. Offers full mixing and monitoring facilities. Front panel size: 16½in x 3½in.  
Suggested Retail Price £49.50

### D.J.30L Psychedelic Light Control Unit

3-channel light unit enabling bass, middle and treble frequencies from the amplifier to be operated individually. Handles 1,000W per channel. Front panel size: 10in x 6in.  
Suggested Retail Price £37.50

### D.J.40L Sound Operated 3-channel light unit

Features built-in microphone which eliminates the need for connections to any amplifier or sound source. Handles 1,000W per channel. Front panel size: 16½in x 3in.  
Suggested Retail Price £56.25

### D.J. DIMMER 3000

3-channel light dimmer unit offered in two versions: Dimmer 3000—a straight 3-channel dimmer unit with mains input and three light outputs. Dimmer 3000S—for use in conjunction with D.J.30L Light Control unit only and has three mains inputs and three light outputs. Front Panel size: 10in x 6in.  
Suggested Retail Price £32.50

### Discosound Disco-Wheel

A projector designed to project a range of liquid wheels and colour change wheels for special lighting effects, adding colour and variety to any form of entertainment. Size: 7½in x 10½in x 5½in.  
Suggested Retail Price £50

A range of complete Discotheques with matching Speakers also available.

DISCOSOUND PRODUCTS ARE GUARANTEED FOR 12 MONTHS

For full details of the Discosound range of products call at or write to your nearest  
Discotheque Centre — Demonstrations given at any time.

DISCOSOUND

122 Balls Pond Road, London N.1. Tel: 01-254 5779

HENRY'S RADIO LTD.,

309 Edgware Road, London W.2. Tel: 01-723 6963

# The largest selection

## NEW LOW PRICE TESTED S.C.R.'s

PIV	1A TO-5	3A TO-66	7A TO-66	10A	16A TO-48	30A TO-48
50	0.23	0.25	0.47	0.50	0.53	1.15
100	0.25	0.33	0.53	0.58	0.63	1.40
200	0.35	0.37	0.47	0.61	0.75	1.40
400	0.43	0.47	0.67	0.75	0.93	1.75
600	0.53	0.57	0.77	0.81	1.25	
800	0.63	0.70	0.90	1.20	1.50	4.00

## SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	0.04	0.05	0.05	0.07	0.14	0.21	0.47
100	0.04	0.06	0.05	0.13	0.18	0.23	0.75
200	0.05	0.09	0.08	0.14	0.20	0.24	1.00
400	0.06	0.13	0.07	0.20	0.27	0.37	1.25
600	0.07	0.18	0.10	0.23	0.34	0.45	1.85
800	0.10	0.17	0.13	0.25	0.37	0.55	2.00
1000	0.11	0.25	0.15	0.30	0.46	0.63	2.50
1200		0.33		0.33	0.57	0.75	

## TRIACS

VDM	2A	6A	10A
TO-1	TO-66	TO-88	
	5p	5p	5p
100	0.50	0.83	1.00
200	0.70	0.90	1.25
400	0.90	1.00	1.60

## SILICON HIGH VOLT-AGE RECTIFIERS

10-Amp 3-K.V. (3000 P.I.V.) Stud type with Flying Leads, 80p each.

## DIACS

FOR USE WITH TRIACS BR100... 37p each

## 2A POTTED BRIDGE RECTIFIERS 200V 50p

## UNIJUNCTION

UT46. Eqt. 2N2646, Eqt. T1843. BEN3000 27p each, 25-99 25p 100 UP 20p.

## NPN SILICON PLANAR

BC107/8/9, 10p each; 50-99, 9p; 100 up, 8p each; 1,000 off, 7p each. Fully tested and coded TO-18 case.

## FREE

One 50p Pak of your own choice free with orders valued £4 or over.

## AF239 PNP GERM. SIEMENS VHF TRANSISTORS. HP MIXER & OSC. UP TO 900 MHZ. USE AS REPLACEMENT FOR AF139-AF186 & 100's OF OTHER USES IN VHF. OUR SPECIAL LOW PRICE—1-24 37p each, 25-99 34p each 100 + 30p each.

## FET'S

2N 3819 ..... 35p  
2N 3820 ..... 80p  
MFF105 ..... 93p

## CADMIUM CELLS

ORP12 45p  
ORP60, ORP61 40p each

## PHOTO TRANS.

OC71 Type. 43p

## SIL. G.P. DIODES 5p

300mW 30... 0.50  
40PIV (Min.) 100... 1.50  
Sub-Min. 200... 5.00  
Full Tested 1,000... 9.00  
Ideal for Organ Builders.

## D13D1 Silicon Unilateral switch 50p each.

A Silicon Planar, monolithic integrated circuit having transistor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

## FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-33V 400mW (D0-7 Case) 13p ea. 1.1W (Top-Hat) 18p ea. 10W (80-10 Stud) 25p ea. All fully tested 5% tol. and marked. State voltage required.

## BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed  
Pak No. EQVT  
T1 8 2G371A OC71  
T2 8 2G374 OC75  
T3 8 2G374A OC81D  
T4 8 2G381A OC81  
T5 8 2G382T OC82  
T6 8 2G344A OC44  
T7 8 2G345A OC45  
T8 8 2G378 OC78  
T9 8 2G399A 2N1302  
T10 8 2G417 AF117  
All 50p each pak

## 2N2080 NPN SIL. DUAL TRANS. CODE D1699

TEXAS. Our price 25p each.

## 120 VCB NIXIE DRIVER TRANSISTOR.

Sim. BSX21 & C407, 2N1893 FULLY TESTED AND CODED ND120. 1-24 17p each. TO-5 N.P.N. 25 up 15p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqt. ZTX300 5p each. Any Qty.

## EX-EQUIPMENT MILLARD

AF117 transistors. Large cat 4 leads type. Leads cut short but still usable, real value at 15 for 50p.

## KING OF THE PAKS Unequaled Value and Quality

### SUPER PAKS

### NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass sub-min. general purpose germanium diodes	0.50
U2	60 Mixed germanium transistors AF/RF	0.50
U3	75 Germanium gold bonded diodes sim. OA5, OA47	0.50
U4	40 Germanium transistors like OC81, AC128	0.50
U5	60 200mA sub-min. Sil. diodes	0.50
U6	30 Silicon planar transistors NPN sim. BSY95A, 2N706	0.50
U7	16 Silicon rectifiers Top-Hat 750mA up to 1,000V	0.50
U8	50 Sil. planar diodes 250mA, OA/200/202	0.50
U9	20 Mixed volts 1 watt Zener diodes	0.50
U11	30 PNP silicon planar transistors TO-5 sim. 2N1132	0.50
U13	30 PNP-NPN sil. transistors OC200 & 28104	0.50
U14	150 Mixed silicon and germanium diodes	0.50
U15	25 NPN Silicon planar transistors TO-5 sim. 2N697	0.50
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV	0.50
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0.50
U18	8 6-Amp silicon rectifiers BZY13 type up to 600 PIV	0.50
U19	25 Silicon NPN transistors like BC108	0.50
U20	12 1.5-Amp silicon rectifiers Top-Hat up to 1,000 PIV	0.50
U21	30 A.F. germanium alloy transistors 2G300 series & OC71	0.50
U23	30 Mat's like MAT series PNP transistors	0.50
U24	20 Germanium 1-Amp rectifiers GJM up to 300 PIV	0.50
U25	25 300Mc/s NPN silicon transistors 2N708, BSY27	0.50
U26	30 Fast switching silicon diodes like IN914 micro-min	0.50
U28	Experimenters' assortment of integrated circuits, untested. Gates, flip-flops, registers, etc., 8 assorted pieces	1.00
U29	10 1-Amp SCR's TO-5 can up to 600 PIV CR81/25-600	1.00
U31	20 Sil. Planar NPN trans. low noise amp 2N3707	0.50
U32	25 Zener diodes 400mW D07 case mixed volts, 3-18	0.50
U33	15 Plastic case 1 amp silicon rectifiers IN4000 series	0.50
U34	30 8A. PNP alloy trans. TO-5 BCY26, 28302/4	0.50
U35	25 8A. planar trans. PNP TO-18 2N2906	0.50
U36	25 8A. planar NPN trans. TO-5 BFY50/51/52	0.50
U37	30 Sil. alloy trans. SO-2 PNP, OC200 28322	0.50
U38	20 Fast switching sil. trans. NPN, 400Mc/s 2N3011	0.50
U39	30 RF germ. PNP trans. 2N1303/5 TO-5	0.50
U40	10 Dual trans. 6 lead TO-5 2N2060	0.50
U41	25 RF germ. trans. TO-1 OC45 NKT72	0.50
U42	10 VHF germ. PNP trans. TO-1 NKT667 AF117.	0.50

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

## GENERAL PURPOSE GERM. PNP POWER TRANSISTORS

Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACEMENTS FOR: OC25-28-29-30-35-36. NKT401-403-404-405-406-450-451-452-453. T13027-3028, 2N250A, 2N456A-457A-458A, 2N511 A & B, 2G220-222, ETC.

SPECIFICATION  
VCBO 80V VCEO 50V IC 10A PT. 30 WATTS HFE 30-170.  
PRICE 1-24 25-99 100 up  
43p each 40p each 36p each

## GENERAL PURPOSE SILICON NPN POWER TRANSISTORS

Coded GP300. BRAND NEW TO-3 CASE. POSSIBLE REPLACEMENT FOR: 2N3055, BDY20, BDY11.

SPECIFICATION  
VCBO 100V, VCEO 60V, IC 15AMPS, PT. 115 WATTS. Hfe 20-100. FTI MHZ.  
PRICE 1-24 25-99 100 up  
55p each 50p each 47p each

## GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8, BSY27/28/95A.

All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

	5p	10p	For 1.75
20	For 0.50	500	For 7.50
50	For 1.00	1000	For 13.00

## HIGH POWER SILICON PLANAR TRANSISTORS

TO-3.  
FERRANTI ZT1487 NPN  
VCB60 1c 6A FT. 1Mcs  
VCE40 Prot. 75W  
VED8 hFE15-45  
PRICE 30p EACH

## RTL MICROLOGIC CIRCUITS

Price each  
Eoxpy TO-5 case 1-24 25-99 100 up  
uL300 Buffer 35p 35p 27p  
uL914 Dual 2/p  
gate 35p 33p 27p  
uL923 J-K flip-flop 50p 47p 45p  
Data and Circuits Booklet for I.C.'s  
Price 7p.

## NEW QUALITY TESTED PAKS

Pak Description	Price
Q1 20 Red spot trans. PNP AF	0.50
Q2 16 White spot R.F. trans. PNP	0.50
Q3 4 OC77 type trans.	0.50
Q4 6 Matched trans. OC44/45/81/81D	0.50
Q5 4 OC73 transistors	0.50
Q6 4 OC72 transistors	0.50
Q7 4 AC128 trans. PNP high gain	0.50
Q8 4 AC126 trans. PNP	0.50
Q9 7 OC81 type trans.	0.50
Q10 7 OC71 type trans.	0.50
Q11 2 AC127/128 comp. pairs PNP/NPN	0.50
Q12 3 AF116 type trans.	0.50
Q13 3 AF117 type trans.	0.50
Q14 3 OC171 H.F. type trans.	0.50
Q15 5 2N2926 sil. epoxy trans.	0.50
Q16 2 GBT880 low noise germ. trans.	0.50
Q17 3 NPN 1 ST141 & 2 ST140	0.50
Q18 4 Mat's 2 MAT 100 & 2 MAT 120	0.50
Q19 3 Mat's 2 MAT 101 & 1 MAT 121	0.50
Q20 4 OC44 germ. trans. A.F.	0.50
Q21 3 AC127 NPN germ. trans.	0.50
Q22 20 NKT trans. A.F. R.F. coded	0.50
Q23 10 OA202 sil. diodes sub-min.	0.50
Q24 8 OA81 diodes	0.50
Q25 6 IN914 sil. diodes 75PIV 750mA	0.50
Q26 2 10A 600PIV sil. recs. IN699	0.50
Q27 2 10A 600PIV sil. recs. IN699	0.50
Q28 2 Sil. power recs. BZY13	0.50
Q29 4 8A. trans. 2 x 2N696, 1 x 2N697, 1 x 2N698	0.50
Q30 7 8A. switch trans. 2N708 NPN	0.50
Q31 6 8A. switch trans. 2N708 NPN	0.50
Q32 3 PNP sil. trans. 2 x 2N1131, 1 x 2N1132	0.50
Q33 3 8A. NPN trans. 2N1711	0.50
Q34 7 Sil. NPN trans. 2N2989, 500MHZ	0.50
Q35 3 8A. PNP TO-5 2 x 2N2904, 1 x 2N905	0.50
Q36 7 2N3646 TO-18 plastic 300MHZ NPN	0.50
Q37 3 2N3053 NPN sil. trans.	0.50
Q38 7 PNP trans. 4 x 2N3703, 3 x 2N3702	0.50
Q39 7 PNP trans. 4 x 2N3704, 3 x 2N3705	0.50
Q40 3 Plastic NPN TO-18 2N3904	0.50
Q41 6 NPN trans. 2N3172	0.50
Q42 7 BC107 NPN trans.	0.50
Q43 7 NPN trans. 4 x BC108, 3 x BC109	0.50
Q44 3 BC115 PNP TO-18 trans.	0.50
Q45 3 BC115 NPN TO-5 trans.	0.50
Q46 6 NPN high gain 3 x BC167, 3 x BC168	0.50
Q47 4 BCY70 NPN trans. TO-18	0.50
Q48 4 NPN trans. 2 x BFY51, 2 x BFY52	0.50
Q49 7 BSY28 NPN switch TO-18	0.50
Q50 7 BSY95A NPN trans. 300MHZ	0.50
Q51 8 HY100 type sil. rect.	1.00
Q53 25 Sil. & germ. trans. mixed all marked new	1.50

## PRINTED CIRCUITS—EX-COMPUTER

Packed with semiconductors and components. 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards, 50p. Plus 10p P. & P. 100 Boards £3, P. & P. 30p.

## TRANSISTOR EQUIVALENTS BOOK.

A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 75p each.

## GERM. POWER TRANS.

Type	Price each	Type	Price each
OC20	50p	OC29	40p
OC22	30p	OC35	33p
OC23	33p	OC36	40p
OC25	25p	AD140	40p
OC26	25p	AD142	40p
OC28	40p	AD149	45p

OUR STOCKS of individual devices are now too numerous to mention in this Advertisement. Send S.A.E. for our listing of over 1,000 Semiconductors. All available Ex-Stock at very competitive prices.

## Dual-in-Line Low Profile Sockets

14 and 16 Lead Sockets for use with Dual-in-Line Integrated Circuits

Order No.	1-24	25-99	100 up
T80 14 pin type	30p	27p	25p
T80 16 pin type	35p	32p	30p

# - the lowest prices!

## 74 series T.T.L. I.C.'s NOW LOWER THAN EVER PRICES —GREATER RANGE



BI-PAK Semiconductors offer you the largest and most popular range of I.C.'s available at these **EXCLUSIVE LOW PRICES**. TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.

BI-PAK Order No.	Similar Types to: Description	Price and qty. prices		
		1-24 \$p	25-99 \$p	100 up \$p
BP00 = 7400	Quadruple 2-input NAND gate	0-23	0-20	0-16
BP01 = 7401	Quadruple 2-input positive NAND gate (with open collector output)	0-23	0-20	0-15
BP02 = 7402	Quadruple 2-input positive NOR gates	0-23	0-20	0-15
BP03 = 7403	Quadruple 2-input positive NAND gates (with open-collector output)	0-23	0-20	0-15
BP04 = 7404	Hex Inverters	0-23	0-20	0-15
BP10 = 7410	Triple 3-input positive NAND gates	0-23	0-20	0-15
BP13 = 7413	Dual 4-input Schmitt trigger	0-35	0-32	0-29
BP20 = 7420	Dual 4-input positive NAND gates	0-23	0-20	0-15
BP30 = 7430	8-input positive NAND gates	0-23	0-20	0-15
BP40 = 7440	Dual 4-input positive NAND buffers	0-23	0-20	0-15
BP41 = 7441	BCD to decimal nixie driver	0-87	0-77	0-67
BP42 = 7442	BCD to decimal decoder (4-10 lines, 1 of 10)	0-87	0-77	0-67
BP47 = 7447	BCD 2-bit segment decoder/drivers (15V outputs)	1-40	1-30	1-20
BP60 = 7450	Expandable dual 2-input and-or-invert	0-23	0-20	0-15
BP51 = 7451	Dual 2-wide 2-input and-or-invert gates	0-23	0-20	0-15
BP63 = 7453	Quad 2-input expandable and-or-invert	0-23	0-20	0-15
BP64 = 7454	4-wide 2-input and-or-invert gates	0-23	0-20	0-15
BP60 = 7460	Dual 4-input expander	0-23	0-20	0-15
BP70 = 7470	Single-phase J-K flip-flop	0-35	0-32	0-29
BP72 = 7472	Master-slave J-K flip-flop	0-35	0-32	0-29
BP73 = 7473	Dual master slave J-K flip-flop	0-43	0-40	0-37
BP74 = 7474	Dual D type flip-flop	0-43	0-40	0-37
BP75 = 7475	Dual latch	0-47	0-45	0-43
BP76 = 7476	Dual J-K with pre-set and clear	0-47	0-45	0-43
BP80 = 7480	Gated full adders	0-87	0-77	0-67
BP81 = 7481	16-bit read/write memory	1-35	1-25	1-15
BP82 = 7482	2-bit binary full adders	1-30	1-20	1-00
BP83 = 7483	Quad full adder	0-87	0-77	0-67
BP86 = 7486	Quad 2-input exclusive or gates	0-80	0-70	0-60
BP90 = 7490	BCD decade counter	0-87	0-77	0-67
BP91 = 7491	8-bit shift registers	1-21	1-00	0-87
BP92 = 7492	Divide-by-twelve counters	0-87	0-77	0-67
BP93 = 7493	4-bit binary counters	0-87	0-77	0-67
BP94 = 7494	Dual entry 4-bit shift register	0-87	0-77	0-67
BP95 = 7495	4-bit up-down shift register	0-87	0-77	0-67
BP96 = 7496	5-bit parallel in parallel out shift register	1-10	1-00	0-90
BP100 = 74100	8-bit bistable latches	1-75	1-65	1-55
BP118 = 74118	Hex set-reset latches	1-30	1-20	1-00
BP121 = 74121	Monostable multivibrators	0-87	0-77	0-67
BP141 = 74141	BCD-to-decimal decoder/drivers	0-87	0-77	0-67
BP145 = 74145	BCD-to-decimal decoder/drivers	1-80	1-70	1-60
BP151 = 74151	8-bit data selectors (with strobe)	1-40	1-30	1-20
BP153 = 74153	Dual 4-line-to-1-line data selectors/multiplexers	1-40	1-30	1-20
BP191 = 74191	Binary counter reversible	3-60	3-25	3-00

**PRICE-MIX.** Devices may be mixed to qualify for quantity prices.  
**PRICES** for quantities in excess of 500 pieces mixed, on application.  
Data is available for the above Series of Integrated Circuits in booklet form, price 13p.

### TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	PAK No.	PAK No.
UIC00 = 12 x 7400N	UIC42 = 5 x 7450N	UIC80 = 5 x 7480N
UIC01 = 12 x 7401N	UIC50 = 12 x 7450N	UIC82 = 5 x 7482N
UIC02 = 12 x 7402N	UIC51 = 12 x 7451N	UIC83 = 5 x 7483N
UIC03 = 12 x 7403N	UIC60 = 12 x 7460N	UIC86 = 5 x 7486N
UIC04 = 12 x 7404N	UIC70 = 8 x 7470N	UIC90 = 5 x 7490N
UIC05 = 12 x 7405N	UIC72 = 8 x 7472N	UIC92 = 5 x 7492N
UIC10 = 12 x 7410N	UIC73 = 8 x 7473N	UIC93 = 5 x 7493N
UIC20 = 12 x 7420N	UIC74 = 8 x 7474N	UIC94 = 5 x 7494N
UIC40 = 12 x 7440N	UIC75 = 8 x 7475N	UIC95 = 5 x 7495N
UIC41 = 5 x 7441N	UIC76 = 8 x 7476N	UIC96 = 5 x 7496N


UICX1 = 25 x Ass'd 74's £1.50

Paks cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1  
Every PAK carries out BI-PAK Satisfaction or money back GUARANTEE.

### BRAND NEW LINEAR I.C.'s—FULL SPEC.

Type No.	Case	Leads	Description	Price
BP 201C—SL201C	TO-5	8	G.P. Amp	63p 53p 46p
BP 701C—SL701C	TO-5	8	OP Amp	63p 53p 46p
BP 702C—SL702C	TO-5	8	OP Amp Direct OP	63p 53p 46p
BP 702—72702	D.I.L.	14	G.P. OP Amp (Wide Band)	53p 46p 40p
BP 709 —72709	D.I.L.	14	High OP Amp	53p 46p 40p
BP 709P— $\mu$ A709C	TO-5	8	High Gain OP Amp	53p 46p 40p
BP 711— $\mu$ A711	TO-5	10	Dual comparator	58p 50p 46p
BP 741 —72741	D.I.L.	14	High Gain OP Amp (Protected)	75p 60p 50p
$\mu$ A 703C— $\mu$ A703C	TO-5	6	R.F.-E.P. Amp	35p 30p 27p
TAA 263—	TO-72	4	A.F. Amp	70p 60p 58p
TAA 293—	TO-74	10	G.P. Amp	90p 75p 70p

## ANOTHER BI-PAK FIRST!

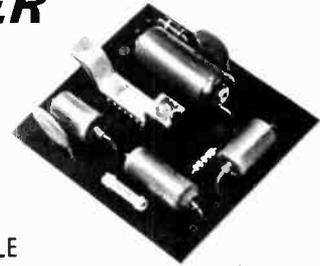

THE NEW S.G.S.  
EA 1000 AUDIO  
AMPLIFIER MODULE

\***GUARANTEED NOT LESS THAN 3 WATTS RMS**

Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TA/621 providing unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for intercom systems, monitoring applications and phone answering machines. **OTHER USES:** portable applications where supply rails as low as 9V are of prime importance.

- Sensitivity 40 mV for 1 watt
- Overall Size 2" x 3" x 1"
- VOLTAGE GAIN 40dB but can be varied up to 73dB for some applications.
- Typical Total Harmonic distortion at 1 watt less than 1%.
- Signal to Noise Ratio 86dB.
- Supply voltage (Vs) = 24V 150hm load.
- Frequency response better than 50 Hz to 25 KHz for -3dB.
- Normal supply Voltage 9-24V.
- Suitable for 8-16 OHM Loads.

Module Tested and Guaranteed

Quantity 1-9 10-25  
Price each £2.63 £2.28  
Larger quantities quoted on request

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

### NOTE THESE PRICES!

IC's	DTL 930 SERIES	LOGIC
Type No.	Function	Price
BP930	Expandable dual 4-input NAND	1-24 25-99 100 up
BP932	Expandable dual 4-input NAND buffer	23p 20p 15p
BP933	Dual 4-input expander	23p 20p 20p
BP935	Expandable Hex Inverter	23p 20p 20p
BP936	Hex Inverter	23p 20p 20p
BP944	Dual 4-input NAND expandable buffer without pull-up	23p 20p 20p
BP945	Master-slave JK or RS	35p 32p 29p
BP946	Quad, 2-input NAND	23p 20p 15p
BP948	Master-slave JK or RS	35p 32p 29p
BP954	Monostable	90p 85p 80p
BP962	Triple 3-input NAND	23p 20p 15p
BP9693	Dual Master-slave JK with separate clock	80p 75p 70p
BP9694	Dual Master-slave JK with separate clock	80p 75p 70p
BP9697	Dual Master-slave JK with Common Clock	80p 75p 70p
BP9699	Dual Master-slave JK Common Clock	80p 75p 70p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

**DTL (Diode Transistor Logic) INTEGRATED CIRCUITS** manufacturers' "Fall outs"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

Pak No.	Pak No.	Pak No.
UIC930 = 12 x $\mu$ A 930	UIC948 = 8 x $\mu$ A 948	UIC950 = 5 x $\mu$ A 950
UIC932 = 12 x $\mu$ A 932	UIC951 = 5 x $\mu$ A 951	UIC951 = 5 x $\mu$ A 951
UIC933 = 12 x $\mu$ A 933	UIC961 = 12 x $\mu$ A 961	UIC961 = 12 x $\mu$ A 961
UIC935 = 12 x $\mu$ A 935	UIC963 = 5 x $\mu$ A 963	UIC963 = 5 x $\mu$ A 963
UIC936 = 12 x $\mu$ A 936	UIC964 = 5 x $\mu$ A 964	UIC964 = 5 x $\mu$ A 964
UIC944 = 12 x $\mu$ A 944	UIC967 = 5 x $\mu$ A 967	UIC967 = 5 x $\mu$ A 967
UIC945 = 8 x $\mu$ A 945	UIC969 = 5 x $\mu$ A 969	UIC969 = 5 x $\mu$ A 969
UIC946 = 12 x $\mu$ A 946	UIC 925 Assorted 930 Series	£1.50

Paks cannot be split but 25 Assorted Pieces (our mix) is available as Pak UICX9. Every Pak carries out BI-PAK Satisfaction or money back guarantee. Data Booklet available for the BP930 Series. PRICE 10p.

All prices quoted in new pence Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 7p. Overseas add extra for airmail.  
Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

## LOW COST ELECTRONIC AND SCIENTIFIC EQUIPMENT AND COMPONENTS

### DIGITAL INDICATORS KGM TYPE M3

A neat compact indicator providing selective display 0-9. Fig. Ht. 18mm. Panel mounting. 6mm tubular midjet flange lamps. Supplied with 28V bulbs. Finished matt black anodized. W. 1in, H. 2in, Wt. 4oz. **£3.25**. Post free.



### OVERHAULED AVOMETERS

Models 40, 47A, 48A. (Models 47A and 48A are Admiralty pattern.)  
D.C. volts: 0-12, 1-2, 12, 120, 480, 1,200.  
Amps: 0-0.12, 0-12, 1-2, 12.  
A.C. volts: 12, 120, 480, 1,200.  
Amps: 0-0.12, 0-12, 1-2, 12.  
Ohms: 1,000, 10,000, 1,000,000 (external voltage source).  
Sensitivity: 166-6 Ohms/Volt, 333-3 Ohms/Volt when divided by two buttons is pressed on both a.c. and d.c. ranges.  
**£18**. P. & P. 75p.  
Complete with voltage multiplier for 480V and 3,600V. Current shunts for 120A and 480A. A.C. current transformer for 20A and 60A. In special wooden box. **£18.50**. P. & P. £1.



### NUMICATOR PRICE LIST

END READING (16mm Fig. Height)	
B13 base	
GR10M/U Clear	0-9 Display
GR10M Amber filter	0-9 Display
Quantity	Price each (less base)
1-3	<b>£1.40</b>
4-10	<b>£1.35</b>
11-25	<b>£1.30</b>
26-100	<b>£1.20</b>

Bases 20p each

### SIDE READING (14mm Fig. Height)

0-9 Display	
XN3F/A	38mm leads Amber Filter
XN3F	38mm leads Red Filter
XN3A/F	6mm leads Red Filter
XN3A	6mm leads Clear Filter
XN11/F	38mm leads Red Filter
XN23/FA	38mm leads Amber Filter

### SPECIAL DISPLAYS

XN9	38mm leads Clear Filter
NX10/C	6mm leads Clear Filter
NX22	38mm leads Clear Filter

Displays Fig. "1"  
Displays "+, - and ~"  
Displays Vx, A, Ω, VmV

Quantity	Price each
1-3	<b>£1.15</b>
4-10	<b>£1.10</b>
11-25	<b>£1.05</b>
26-100	<b>85p</b>

All Post free.

### TELESCOPIC CABINET LID STAYS



Lift lid once stays open. Lift twice catch releases and allows lid to close. Closed length 7in, open length 10in. Finished dull plating brand new. 4 for **£1**. Post free.

### SLIDING CABINET LID STAYS



Similar principle to above closed length 4in, open length 5in. Finished dull plating brand new. 5 for **£1**. Post free.

### NEW MICROSWITCHES— HONEYWELL

1 PL 900 6 contacts. 15 Amp. 125/250 volts. Single pole. ON/OFF. Plunger operated. L1 7/8", W. 5/8", H. 3/4". Price 5 for **£1.25**. Post free.

### NEW FRACTIONAL H.P. CAPACITOR MAINS MOTORS

230V, 50Hz, 0.65A, 1/20 h.p., 2,850 r.p.m. Cont. rated. Shaft 3/16in dia. x 3in long. Circular clamp mounting. **£3.50**. Post free.

### DELAY LINE LEXOR MDN 2484D

Miniature resin encapsulated module. Total delay 50nsec to 10nsec. Tapped at 10% intervals. Impedance 75 ohms to 10 kΩ. 30V wkg. Attenuation 0.5 dB/nsec. Also available MDN 2484C 3 micro-sec 600 ohm impedance. 2 1/2in x 1 1/2in x 3/4in. **£1.50**. Post free.

### MIDGET POWER RELAY OMRON Mk I

230V, 50Hz. 1PDT new. Faulty plating on frame. 5 for **£1.50**. Post free.


**Electronic Brokers Ltd. (Dept. P.E.) 49-53 Pancras Road  
London NW1 Tel. 01-837 7781 Telex 267307**

**OPEN MON-FRI, 9-6pm**

Due to demand it may not always be possible to supply a particular model, and a different type to that ordered may be dispatched. These models are electrically identical.
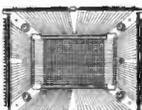
### MEMORY CORE STORES

42 x 52.2kΩ bit ferrite core store. C/W quantity 0-1 load diodes. Ideal for building computer store, holding information, teaching experiments, demonstrations, etc. Price **£2.25**. P. & P. 38p.



### BRAND NEW CAPACITOR REVERSIBLE SINGLE PHASE PARVALUX MOTORS

230/250V, 50Hz, 2,800 r.p.m.; 1/30 h.p. cont. rated; 5/16in dia. shaft; 3in long foot mounting; wt. 6lb. C/W capacitor. **£3.50**. Post free.




### THERMOMETER

Industrial Instrument employing Bourdon tube principle. Scaled 0-102 degrees C. and 92-201 degrees F. 3in dia. scale. 36in capillary tube. Sensing element 1/2in-dia. x 2 1/2in long. Price 75p. P. & P. free.


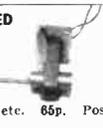
### NEW ENICRON SHADED POLE MOTORS

240/250V, 50Hz, 2,500 r.p.m. (no load). Shaft 1/4in dia. x 1 1/2in long. Suitable record player, blower motor, etc. 65p. Post free.




### TELEPHONE DIALS

Clear Perspex, very good condition. No markings. 75p each. P. & P. 25p.

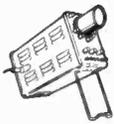
### OSCILLOSCOPE TYPE CT 52

A very handy miniature portable instrument for general purpose applications. 2 1/2in diam. tube. Wave form investigation from 10Hz-20MHz. Pulse monitoring duration 50 microseconds to 0.1 microsecond. Time base free running 10Hz-40kHz. Also single sweep facility from 50 microseconds to 3 microseconds. "Y" Amplifier. Delay Line Calibration Voltage. Power supply 110-250V. 40/60Hz, 50W. Supplied with metal carrying case. L. 13in, H. 8in, W. 5 1/2in. Weight 14 1/2lb (less Graticule, assembly and Viewing Hood). Price **£22**. P. & P. £1.50.



**GOOD QUALITY  
INSTRUMENTS TAKEN  
IN PART EXCHANGE  
OR PURCHASED  
FOR CASH**

# COLBERT WORK POSITIONERS-300 SERIES

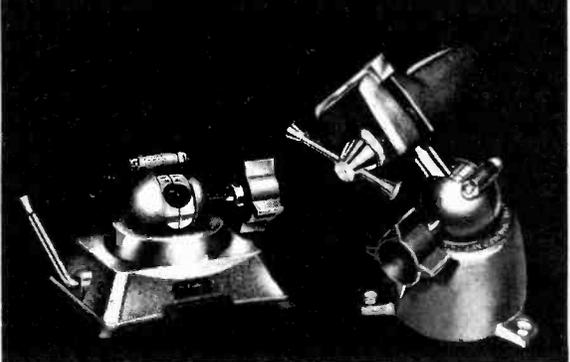

Colbert Pana-Vise WORK POSITIONERS are specially designed to quickly and easily achieve the most CONVENIENT, COMFORTABLE and TIME-SAVING work position.

Available with vacuum clamp or screw-on base. They can be ROTATED, TIPPED, TILTED, ANGLED, ELEVATED, LOWERED.

The required work position is firmly secured with a patented ONE KNOB CONTROL, a unique feature of COLBERT POSITIONERS.

A series of special holders is available for various types of work.

Full details available on request.

*Distributors:*

**SPECIAL PRODUCTS DISTRIBUTORS LTD.**  
81 PICCADILLY, LONDON, W.1. Tel. 01-628 9556  
Cables: SPECIPROD LONDON (made in U.S.A.)

## Joan E. Allen & Company offers a comprehensive range of COIN & METAL DETECTORS

### THE HUNTER

High sensitivity combined with marked stability to give a simple-to-use detector which is a must for the professional man such as tree surgeon, electrical contractor or serious treasure hunter **£24.00**

### THE EXPLORER

Inexpensive but sensitive. Will give hours of treasure hunting fun for the whole family on the beach, whilst walking or at home in the garden. A useful robust general purpose detector **£19.50**

### THE DISCOVERER

1. The Do-It-Yourself kit entails a minimum capital outlay and can be easily assembled in a few hours. The kit is complete except for a standard portable transistor radio as most families have one of these available. As sensitive and stable as the more expensive detectors but a fraction of the cost **£5.40**

2. The "Discoverer" Metal Detector fully assembled and ready for use (transistor radio not included) **£7.50**

3. Portable transistor radio ideal for use with the "Discoverer" Metal Detector **£1.95**

### TREASURE HUNTER'S HANDBOOK

"A Fortune Under Your Feet". This new publication answers all your questions on treasure hunting. Find out the How, Where, When and Why of this fascinating new hobby **45p** plus 6p post and packing

PLEASE ADD 30p TO DETECTOR ORDERS TOWARDS COST OF POST, PACKING AND INSURANCE.

ALL DETECTORS ARE GUARANTEED FOR ONE YEAR.

SHOWROOM DEMONSTRATIONS: MONDAY-FRIDAY 10-5 p.m.  
SATURDAY 9-1 p.m.

FURTHER DETAILS OF ALL DETECTORS AVAILABLE ON REQUEST  
(A 3p stamp would be appreciated).

184 Main Road, Biggin Hill, Kent. Telephone: Biggin Hill 4234

# TRANSISTOR RADIOS TO BUILD YOURSELF


Backed by after sales service

## NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, S.W.1, S.W.2, S.W.3, and Trawler Band. Built-in ferrite rod aerial for Medium and Long Waves. 4 section 24in. retractable chrome plated telescopic aerial for Short Waves for maximum performance. Push-pull output using 600Mw type transistors. Socket for car aerial. Tape record socket. Selectively switch. Switched earpiece socket complete with earpiece for private listening. 8 transistors plus 3 diodes. Famous make 7" 4in speaker. Air spaced ganged tuning condenser. On/off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9" x 7" 4in approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Parts price list and easy build plans 25p (FREE with parts).

**Total building costs** **£6.98**  
Post, packing and insurance 41p

Overseas  
P. & P. 90p

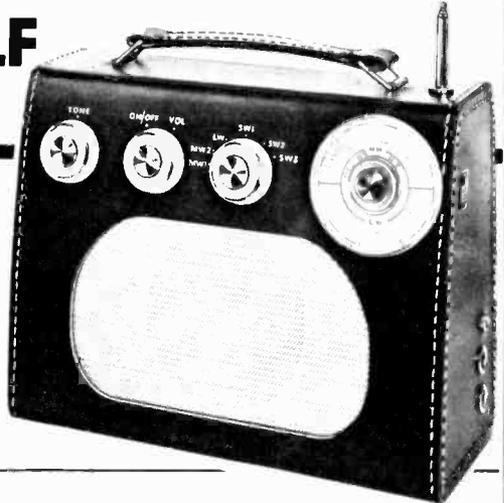

## roamer seven mk IV

7 FULLY TUNABLE WAVEBANDS—M.W.1, M.W.2, L.W., S.W.1, S.W.2, S.W.3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. 7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7" 4in P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9" x 7" 4in approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 10p (FREE with parts).

**Total building costs**  
**£5.98**

Personal Earpiece with plug and switched socket for private listening. 30p extra.

Post, packing and insurance 41p  
Overseas P. & P. 90p




## NEW!
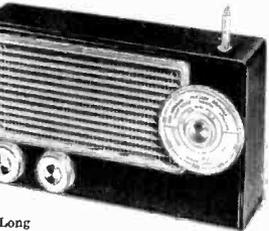
### transeight SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and black knobs and dial with spun brass inserts. Size 9" x 6 1/2" x 2 1/2in. approx. Tunable on Medium and Long Waves, 3 Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8 improved type transistors plus 3 diodes. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).


**Total building costs**  
**£4.48**  
Post, packing and insurance 31p  
Overseas P. & P. 70p



Earpiece with plug and switched socket for private listening. 30p extra.
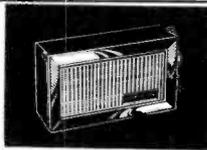
## pocket five MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive black and gold case. Size 5 1/2" x 3 1/2in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening. 30p extra.



**Total building costs**  
**£2.23** Post,  
packing  
and insurance 21p  
Overseas P. & P. 55p

## transona five MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER


Attractive case with red speaker grille. Size 6 1/2" x 4 1/2in x 1 1/2in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening. 30p extra.



**Total building costs**  
**£2.38** Post,  
packing  
and insurance 22p  
Overseas P. & P. 55p
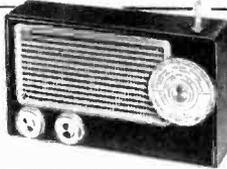
## IMPROVED MODEL! roamer six SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive black case with red grille and black knobs and dial with spun brass inserts. Size 9" x 6 1/2" x 2 1/2in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening. 30p extra.



**Total building costs**  
**£3.98** Post,  
packing  
and insurance 26p  
Overseas P. & P. 70p

## RADIO EXCHANGE LTD

61a, HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSEIGHT	<input type="checkbox"/>	POCKET FIVE	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for.....

Name.....

Address.....

PE 32

\* Callers side entrance Barratts Shoe Shop

\* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

# 28watts, r.m.s. 40Hz to 40kHz $\pm 3$ dB

There are two stereo amplifiers — the RT100 for ceramic cartridges, the RT101 for magnetic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket to plug in headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.



## Viscount III Audio Suite complete £49

### PRICES SYSTEM 1

Viscount III RT101 amplifier £22.00 + 90p p&p  
 2 x Duo Type II speakers, £14.00 + £2 p&p  
 Garrard SP25 Mk. III with  
 MAG. cartridge, plinth  
 and cover

£23.00 + £1 p&p

Total £59.00

Available complete for only £52.00 + £2.50 p&p.

### SPECIFICATION

14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 150mV into 3 Meg. P.U.2 4mV @ 1kHz into 47K, equalised within  $\pm 1$ dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power.) Tape out facilities; headphone socket, power out 250 mW per channel. *Tone controls and filter characteristics.* Bass: + 12 dB to - 17 dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble + 12 dB to - 12 dB @ 15 kHz. Treble filter: 12 dB per octave. *Signal to noise ratio:* (all controls at max) RT101 — P.U.1. & radio — 65dB. P.U.2 — 58 dB. RT100 same as RT101 but P.U.2. 450 mV into 3 Meg. *Cross talk* better than -35dB on all inputs. *Overload characteristics* 26dB on all inputs.

Size 13½" x 9" x 3½".

### SYSTEM 2

As System 1, but with 2 x Duo Type III speakers at pair £32.00 + £3 p&p  
 Available complete for £69 + £4 p&p

### SYSTEM 3

Viscount III Amplifier RT100 £17.00 + 90p p&p  
 2 x Duo Type II speakers, pair £14.00 + £2 p&p  
 Garrard SP25 Mk. III with CER. diamond  
 cartridge, plinth and cover £21.00 + £1 p&p

Total £52.00

Available complete for only £49.00 + £2.50 p&p

### SPEAKERS Duo Type II

Size 17" x 10½" x 6½". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts. 3 ohms  
 Teak veneer cabinet. £14 pair + £2 p&p.  
 Duo Type III Size 23½" x 11½" x 9½". Drive unit  
 13½" x 8½" with H.F. speaker. Max. power 20  
 watts at 3 ohms. Frequency range 20Hz to 20kHz.  
 Teak veneer cabinet. £32 pair + £3 p&p.

Radio and TV Components (Acton) Ltd, 21d High Street, Acton, London, W3 6NG  
 323 Edgware Road, London, W.2. Mail orders to Acton, Terms C.W.O. All enquiries S.A.E.  
 Goods not dispatched outside U.K.

# R+TV

# Give us six months, and we'll turn your hobby into a career.

You have a hobby for a very good reason. It gives you a lot of pleasure.

So if you can find a job that involves your hobby, chances are you'll enjoy your work more, and you'll do better work.

Now CDI can help you find such a job. A job where you'll be responsible for the maintenance of a computer installation. A job that pays well too. If you're interested in mechanics or electronics (without necessarily being a

mathematical genius), have a clear, logical mind and a will to work, then we can train you to be a Computer Engineer inside six months.

So give us a call. CDI. We're the Education Division of one of the world's largest computer manufacturers. And we have the experience to know if you can make it. A ten minute talk with us, and you could be on the way to spending the rest of your life with your hobby.

Ring

**01-637 2171**

between 9 a.m. and 9 p.m. and ask for Mr Pearce

It's quicker and easier to phone, but if you prefer, send this coupon to: Control Data Institute, Wells House, 77 Wells Street, London, W.1.

Please give me further information.

Name \_\_\_\_\_

Address \_\_\_\_\_

Age \_\_\_\_\_

Phone \_\_\_\_\_

4G1

**CONTROL DATA  
INSTITUTE**

**CONTROL DATA  
LIMITED**

The Education Division of one of the world's largest Computer manufacturers.


## TOURIST

### MARK 3 CAR RADIO
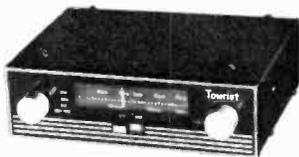
#### ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in 2in 4½in deep.

Circuit diagram 13p, free with parts. Speaker, baffle and fixing kit £1.25 extra plus P. & P. 25p



SET OF PARTS  
**£6.30** Plus P. & P. 50p

Speaker postage free when ordered with parts

## SOUND 50

### 50 WATT AMPLIFIER & SPEAKER SYSTEM

Output Power: 45 watts R.M.S. (Sine wave drive). Frequency response: —3dB points —30Hz at 18KHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Speaker Impedance: 3, 8 or 15 ohms. Bass Control Range: —13dB at 60Hz. Treble Control Range: ±12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power. **SPEAKERS!** Size 20in x 20in x 10in incorporating 12in heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

**COMPLETE SYSTEM** **£50** Plus £4 P. & P. or available separately. Amplifier: £28.50 plus £1.50 P. & P. Speaker: £12.50 each plus £1.75 P. & P.



### ELEGANT SEVEN Mk. III (350mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction. MAINS POWER PACK KIT: 75p extra.

£5.25 Plus P. & P. 50p. Circuit 13p Free with parts.

### THE DORSET (600mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Sizes: 12in x 8in x 3in.

£5.25 Plus P. & P. 50p. Circuit 13p. Free with parts.



### THE RELIANT MK. III SOLID STATE GENERAL PURPOSE AMPLIFIER

in simulated teak case  
£7.25 Plus P. & P. 50p

#### SPECIFICATIONS

Output ±10 watts. Output impedance—3 to 4 ohms. Inputs: 1. xtal mic. 10mV Tone Controls—Treble control range 12dB at 10KHz. 2. gram/radio 250mV. Bass control range 13dB at 100Hz. Frequency Response—(with tone controls central) Minus 3dB points at 20Hz and 40KHz. Signal to Noise Ratio—better than —60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220/250V a.c. Size of chassis—10½in x 4½in x 2½in. For use with Scd. or L.P. records, musical instruments, all makes of pick-ups and mikes. Built and tested.

## R+TV RADIO & TV COMPONENTS (ACTON) LIMITED

21d High Street, Acton, London W3 6NG  
323 Edgware Road, London, W.2

ALL MAIL ORDERS TO OUR ACTON BRANCH  
Terms C.W.O. All inquiries S.A.E. U.K. only

# Mullard

## TECHNICAL BOOKS

### Power Engineering using Thyristors

Part 1. Techniques of  
Thyristor Power Control

A new book to bridge the gap between electrical power engineering and electronics.  
Including postage £1.60.

### Data Book 1970

Gives Mullard abridged data on valves, picture tubes, semiconductors and components used in consumer electronics.

Paper bound. Including postage 24p.

### Transistor Audio and Radio Circuits

For radio receivers, radiograms, record players, tape recorders, hi-fi equipment.

Over 200 pages packed with the most up to date information.

Bound in cloth. Including postage £1.60.

### Electronic Counting Circuits. Techniques. Devices.

The increasing use of mechanization and automation in factories has given rise to an increased interest in counting. This present book is intended to help engineers to use electronics to solve their counting problems as simply or as cheaply as possible.

220 pages fully illustrated. With diagrams.

Including postage £1.50.

### Semiconductor Devices

This book is an introduction to Semiconductor Electronics and its contents should be readily understood. The subject is treated non-mathematically. Numerous illustrations and diagrams. Including postage 42p.

### A programmed book on Semiconductor Devices

This book is an integral programme which is a form of self instructional text.

Size 12ins. x 8ins. Numerous illustrations and diagrams. Including postage 75p.

### Electronic Experiments

The 20 experiments are intended as constructional projects, such as, an Oscilloscope, Logic Gates, Electronic Organ, Electronic Timer, etc. Containing numerous illustrations and diagrams. Including postage 75p.

Post now to: Dept. M  
**SELRAY BOOK COMPANY**  
60 Hayes Hill Bromley BR2 7HP

## Now a screwdriver that holds the screw for you The Chuck Grip

At last, someone's improved the screwdriver. Made it so that you can fix a screw, any screw, with one hand. No more fumbling or dropping, even in awkward situations. Look at these features:



★ Nylon chuck-grip clasps any screw head securely (dome, flat, countersunk) whilst you turn the screwdriver with one hand.



★ Electrically insulated handle stands up to 50,000 volts.



★ Interchangeable blades for either Phillips, Pozidriv, or conventional screw heads.



★ Handy size... 6 1/2 inches fully extended.



★ Blade retracts into handle, so no torn holes when carried in pocket.

Available at D.I.Y. and hardware stores everywhere, recommended retail price 57 1/2p.

Distributed by:

I.X.P. Ltd., Dept. PE8/71, Henshaw Lane, Yeadon,  
LEEDS LS19 7RZ Telephone: Rawdon 4015/6

Manufactured by Unique Small Tool Co. Ltd.

## VALVES

**SAME DAY SERVICE**  
NEW! TESTED! GUARANTEED!

**SETS** 1R5, 1S5, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94.  
Set of 4 for £1.02. DAF96, DF96, DK96, DL96, 4 for £1.48.

1R5	-28	25U4GT	-57	DL96	-38	EL500	-62	PCL82	-36	UABC80	-85
1S5	-28	30C1	-30	DY86	-62	EM80	-41	PCL83	-60	UAF42	-52
1T4	-16	30C15	-63	DY87	-28	EM81	-41	PCL84	-37	UBC41	-52
384	-28	30C17	-80	DY802	-40	EM84	-33	PCL85	-45	UBF80	-34
3V4	-37	30C18	-67	EABC80	-32	EM87	-37	PCL86	-41	UBF89	-33
5U4G	-26	30F5	-76	EAF42	-60	EY81	-38	PCL88	-72	UC84	-35
5V4G	-37	30FL1	-63	EB41	-40	EY86	-32	PCL800	-77	UOC85	-36
5Y3GT	-30	30FL12	-72	EB91	-11	EZ40	-43	PENA4	-42	UCF80	-36
6ZAG	-37	30FL14	-72	EB333	-62	EZ41	-43	PEN36C	-70	UCH42	-62
6J30L2	-58	30L1	-32	EB241	-54	EZ60	-33	PL200	-68	UCH81	-32
6AL5	-11	30L15	-62	EB290	-22	EZ81	-24	PL36	-49	UCL82	-35
6AM6	-13	30L17	-73	EBF80	-33	GZ30	-37	PL81	-46	UCL83	-55
6AQ5	-26	30P4	-65	EBF89	-31	GZ32	-43	PL81A	-51	UF41	-56
6AT6	-22	30P12	-77	ECC81	-18	GZ34	-50	PL82	-33	UF89	-33
6AU6	-22	30P19	-65	ECC82	-23	KT41	-77	PL83	-35	UL41	-60
6BA6	-22	30P11	-63	ECC83	-35	KT61	-55	PL84	-33	UL44	£1.00
6BE6	-23	30P13	-85	ECC85	-23	KT66	-83	PL500	-65	UL84	-35
6B36	-42	30P14	-70	ECC804	-60	LN319	-63	PL504	-67	UM84	-22
6BW7	-60	30P15	-90	ECCF80	-30	LN329	-72	PM84	-37	UY41	-41
6CD6G	£1.10	35L6GT	-45	ECCF82	-30	LN339	-63	PX25	£1.17	UY85	-28
6F14	-45	35W4	-28	ECH35	-30	N78	-87	PY32	-55	VP4B	-77
6F23	-71	35Z4GT	-25	ECH42	-68	P61	-50	PY33	-55	Z77	-22
6F25	-32	387	-45	ECH41	-29	PABC80	-35	PY81	-27	Transistors	
6K7G	-19	6063	-62	ECH83	-62	PC86	-51	PY82	-27	AC127	-17
6K8G	-17	AC/VP2	-77	ECH84	-37	PC88	-51	PY83	-28	AC127	-18
6Q7G	-28	B349	-65	ECL80	-35	PC96	-42	PY88	-35	AD140	-37
68L7GT	-27	B729	-62	ECL82	-33	PC97	-40	PY800	-37	AF115	-20
68N7GT	-30	GCH35	-67	ECL86	-40	PC900	-30	PY801	-37	AF116	-20
6V8G	-23	CL33	-92	EF39	-23	PC884	-32	R19	-32	AF117	-20
6V8GT	-32	DY91	-33	EF84	-32	PCF85	-30	R20	-60	AF118	-12
6X4	-23	DAF91	-92	EF80	-24	PCF88	-45	U25	-68	AF125	-17
6X6GT	-28	DAF96	-36	EF85	-31	PC899	-47	U26	-65	AF127	-17
10P13	-60	DF33	-38	EF86	-31	PC189	-51	U47	-68	OC26	-26
12AH8	£2.25	DF91	-16	EF89	-27	PC805	-65	U49	-65	OC44	-12
12AT7	-18	DF96	-36	EF91	-13	PCF80	-30	U50	-39	OC45	-12
12AU6	-23	DH77	-22	EF183	-29	PCF82	-32	U52	-31	OC71	-12
12AU7	-32	DK32	-22	EF184	-29	PCF86	-47	U78	-24	OC72	-12
12AX7	-23	DK91	-22	EF90	-22	PCF800	-67	U191	-62	OC75	-12
19B6GG	-87	DK92	-42	EL33	-55	PCF801	-33	U193	-42	OC81	-12
20F2	-67	DK96	-38	EL34	-49	PCF802	-45	U251	-72	OC81D	-12
20F3	-85	DL35	-35	EL41	-55	PCF805	-67	U301	-52	OC82	-12
20F4	-92	DL92	-28	EL84	-24	PCF806	-60	U329	-72	OC82D	-12
25L6GT	-25	DL94	-37	EL90	-26	PCF808	-72	U801	-98	OC170	-22

## READERS RADIO


85 TORQUAY GARDENS, REDBRIDGE, ILFORD,  
ESSEX. Tel. 01-550 7441.

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra.  
Any parcel insured, against damage in transit 3p extra.

FIND BURIED TREASURE WITH THIS  
READY BUILT & TESTED


# Treasure Locator Module

Only  
**£4.95**  
(99/-)

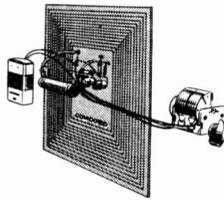

**BRAND NEW FULLY TRANSISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE.** Ready built and tested—just plug in a PP3 battery and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, wood, dirt, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, WATCHES, JEWELLERY, NUGGETS, METALLIC ORE, HISTORICAL RELICS, BURIED PIPES, KEYS, NAIL-IN-TREES, ETC., ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. PRINTED CIRCUIT SEARCH COIL so stable and sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! You could even pay for your holidays with two or three days electronic beeping—it's almost like having a licence to print money! Unclaimed treasure now exceeds the combined wealth of all nations. ORDER NOW WHILE PRESENT STOCKS LAST—TREMENDOUS DEMAND EXPECTED AT THIS REMARKABLY LOW PRICE. DEMONSTRATIONS DAILY. ORDERS DESPATCHED IN STRICT ROTATION. SEND NOW £4.95 + 30p cart. (99/- + 6/-) etc. (High quality Danish Stethoscope headphones £2.75 (55/-) extra if required).
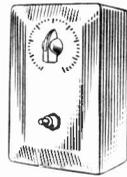
# SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON



ONLY  
**£2.37** Plus P. & P. 23p  
(47/6)

only  
**£2.25**  
(45/-)

**CUTS OUT NOISE POLLUTION—SOOTHE YOUR NERVES!** Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator based on avalanche operated transistors. Besides being able to mask out extraneous unwanted sounds, it has a number of other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. A group of Dentists have experimented on patients with this pink noise—NO ANAESTHETICS WERE USED! The noise ostensibly created a most definite reaction on these patients' nervous systems with the results that their pain systems were blocked. IF YOU WORK IN NOISY OR DISTRACTING surroundings, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. You will never want to be without it—use this amazing pink noise generator whenever you feel uneasy, can't relax or wish to concentrate. TAKE IT ANYWHERE, pocket sized. Uses standard PP3 batteries (current used so small that battery life is almost self-life) CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, Components, Nuts, Screws, Wire, etc. etc. no soldering. Send only £2.25 + 25p (45/- + 5/-) p. & p. parts available separately.)

# GET A GOOD NIGHT'S SLEEP—EVERY NIGHT! INGENIOUS ELECTRONIC SLEEP INDUCER

only  
**£2.75**  
(55/-)




**CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT?** Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sounds gradually become less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times etc., all to suit your concentration. Fully illustrated instructions included. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries—extremely economical. Size only 3" x 4" x 1 1/2"—take it anywhere. All parts including case, loudspeaker, components, nuts, wire, screws, etc. etc. THERE WILL BE A GREAT DEMAND FOR THIS UNIQUE NEW DESIGN—SEND NOW £2.75 + 25p (55/- + 5/-) p. & p. (parts available separately).
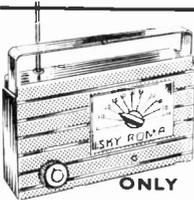
# REAL WORKING ELECTRONIC ORGAN



ONLY  
**£2.75**  
(55/-)

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorized—no valves. Proper self-contained loudspeaker. Fifteen separate keys span two full octaves—the "Yellow Rose of Texas" play "Silent Night", play "Auld Lang Syne", play lots and lots of similar tunes on this real working electronic organ. Although it's no theatre organ it's certainly no tiny thing, it measures 13 1/2 x 10 x 2 1/4". You have the thrill and excitement of building it together with the pleasure of playing a real, live, throbbing electronic organ. Take it anywhere—play it anywhere. NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED—NONE WHATSOEVER. No soldering necessary. It really is as simple as A.B.C. to make. Anyone from nine years upwards can build it easily in one short evening following the fully illustrated, step-by-step, simply worded instructions. BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT at our low, low building price. ONLY £2.75 (55/-) + 23p (4/6) p. & p. for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformer, volume control, wire, nuts, screws, simple (but full) instructions, etc. etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.




ONLY  
**£2.25**  
(45/-)

# SHORTWAVE TRANSISTOR RADIO Can be built in one evening

At last! After trying countless circuits searching for easy build, work first-time short wave. Giving advanced world-wide performance, we chose this 'Sky Roma' Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and every one worked first time) no soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Transistorized (no valves). Size only 3" x 4 1/2" x 1 1/2". As tremendous demand anticipated price held to only £2.25 (45/-) + 17p (3/6) p. & p. for all parts inc. Cabinet, screws, instructions etc. (Part available separately).
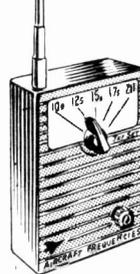
# EAVESDROP ON THE EXCITING WORLD OF AIRCRAFT COMMUNICATIONS—JUST OUT V.H.F. AIRCRAFT BAND CONVERTER



Many thousands of v.h.f. Aircraft Band Converters now selling in U.S.A. Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting cross-talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tensions on talk downs. Be with them when they have to take nerve rippling decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK ETC., ETC. CLEAR AS A BELL. This fantastic fully transistorized instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time). No knowledge of radio or electronics required. No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2" x 3" x 1 1/2". All you do is extend rod aerial, place close to any ordinary medium-wave radio—(even tiny portables) NO CONNECTIONS WHATSOEVER NEEDED. Use indoors or outdoors. THERE WILL BE ENORMOUS DEMAND FOR THIS NEW DESIGN, SEND NOW, ONLY £2.37 (47/6) p. & p. for all parts, including case, nuts, screws, wire, etc., etc. (parts available separately).

# BUILD 5 RADIO AND ELECTRONIC PROJECTS



TOTAL BUILDING PRICE  
**£1.97**  
(39/6)

Amazing Radio Construction set! Become a radio expert for £1.97 (39/6). A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated Step-by-step plans, all Transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Presentation Box 37p (7/6) extra as illus. (if required) (extra parts available separately) no soldering necessary. Send only £1.97 (39/6) + 23p (4/6) p. & p.

# FIND BURIED TREASURE! TREASURE LOCATOR TRANSISTORISED

NOW IT'S HERE AT LAST, after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorized metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, LOOSE COINS, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS ETC. ETC. Outdoors or indoors. Extremely sensitive, will signal presence of certain objects buried several feet below ground! No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions—it really is as easy as A.B.C. transistorized—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13 1/2" x 10" x 2 1/4". Great demand expected at this remarkably low price—ORDER WHILE PRESENT STOCKS LAST. All parts including detector head case, nuts, screws, wire, simple instructions etc. etc. ONLY £2.37 (47/6) + 27p (5/6) p. (Sectional) handle as illustrated 75p (15/-) extra. Parts available separately. Made up looks worth £15!



ONLY  
**£2.37**  
(47/6)

EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

**CONCORD ELECTRONICS LTD (Dept. PE21)** 8 Westbourne Grove, London W.2.  
(STAFF WANTED FOR ALL DEPARTMENTS) (Nr Bayswater & Queensway Tubes. 1 minute ABC Cinema)  
Callers Welcome 9 a.m.-6 p.m. inc. Saturday

**IMPORTANT. THIS LATEST 1971 MODEL INCORPORATES ALL THE LATEST TECHNOLOGICAL IMPROVEMENTS AND SUPERSEDES ALL EARLIER MODELS! YES, THIS SENSATIONAL BRAND NEW VEF 204 RUSSIAN 8 WAVEBAND PORTABLE RADIO, DESIGNED FOR WORLD WIDE RECEPTION, will probably make your present radio seem like a "crystal set"!** It's far better than any other 8 wave radio that even they have produced before! It even incorporates a special **MARINE WAVEBAND** to receive spoken communications from ship-to-shore! Complete with optional battery eliminator for both battery and mains use! It represents the finest value we have ever offered! We're almost giving them away at only £13.97—a mere fraction of even today's Russian miracle price! In fact we challenge you to compare the performance and value with that of £42.00 radios! \*You just can't lose, we'll refund your money instantly if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto, for absolutely "pin-point" station selection! Yes, the Russians have really surpassed themselves this time, proving once again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. **YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO ITS TRUE VALUE!** Yes, 8 separate wavebands, including Standard Long, Medium and Short Waves to cover the world. **PLUS special "ship-to-shore" MARINE BAND!** Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions, and stations at your fingertips 24 hours a day, including ships at sea, etc. and messages from all over the world—truly nothing is secret! The radio enthusiast can have the world in the palm of his hand! You must hear it to believe it! Superb, sweet tone—controlled from a whisper to a roar that will fill a hall! Genuine push-pull output! Separate ON/OFF volume and Treble/Bass tone controls! **Frequency dial illumination!** Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240v AC mains supply. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 31in. length. It's also a fabulous **CAR RADIO**—any speed, requires no additional aerial, **UNIQUE!** Elegant Black and Chrome finish case. **SIZE** 11ins. x 9ins. x 3ins. overall approx. Magnificently designed and superbly made to give years of perfect service. Complete with **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £13.97** (with mains/battery eliminator £1.38 extra). **BOX, POST, ETC., 50p.** Standard batteries 38p extra. Can also be used through extension amplifier, tape recorder or public address system. Send today or call at either store, but **HURRY!** It's the chance of a lifetime. (Sorry—we cannot change these new radios for any earlier model already purchased.) Send quickly or call. Refund guaranteed.

## RUSSIAN WORLD BEATER!

**JUST ARRIVED!**

The Fabulous  
**BRAND NEW**  
1971

**WORLD WIDE RECEPTION**  
THOUSANDS OF TRANSMISSIONS  
AND STATIONS THE WORLD OVER!

THIS OFFER ONLY FROM US!

**VEF 204**  
**8 WAVEBAND**

**10 TRANSISTOR PLUS 2 DIODES PORTABLE RADIO**

**AND NOW WITH 'SHIP-TO-SHORE' MARINE BAND**

**BATTERY MODEL £13.97p**  
BOX POST ETC. 50p

**MAINS/BATTERY ELIMINATOR £1.38p extra**



**WE COULDN'T EVEN MAKE THEM FOR OUR FANTASTIC PRICE!**


**\*COMPARE IT'S PERFORMANCE with £42 RADIOS!**

**SHOPERTUNITIES LTD. SL**

Dept. PE/7, 164 UXBIDGE ROAD, LONDON W12 8AQ  
(facing Shepherd's Bush Green). (Thursday 1 p.m., Friday 7 p.m.)

ALSO AT 37/39 HIGH HOLBORN, LONDON, W.C.1 (opposite Chancery Lane). (Wed. 1, Thurs. 7). Both stores open from Monday to Saturday from 9 a.m. until 6 p.m.

## INTER-LOCKING PLASTIC STORAGE DRAWERS

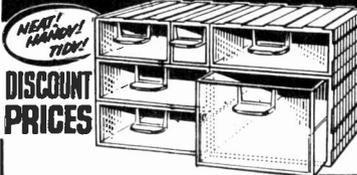

NEARLY HANDED! TRY!  
**DISCOUNT PRICES**

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

**5 SIZES ALL INTERLOCK**

### BUY AT TRADE PRICES!

**SINGLE UNITS (1D)** (5ins x 2½ins x 2½ins) £1.35 DOZEN.

**DOUBLE UNITS (2D)** (5ins x 4½ins x 2½ins) £2.25 DOZEN.

**TREBLE (3D)** £2.35 for 8.

**DOUBLE TREBLE 2 draws, in one outer case (4D2), £3.65 for 8, EXTRA LARGE SIZE (4D1) £3.30 for 8.**

### PLUS QUANTITY DISCOUNTS!

Orders £5 and over DEDUCT 5% in the £  
Orders £10 and over DEDUCT 7½% in the £  
Orders £20 and over DEDUCT 10% in the £  
PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £5. Orders £5 and over, packing/postage/carrriage free.

QUOTATIONS FOR LARGER QUANTITIES ALL PRICES TAX PAID

**IVORYET LIMITED** (Dept. PE8) 124 Cricklewood Broadway, London, N.W.2  
Tel. 01-450 4844

## EX G.P.O. EQUIPMENT

### UNISELECTOR UNIT

Unit contains:  
2 x 3 bank 25 way  
2 x 4 bank 25 way  
2 x 5 bank 25 way  
interconnected to 12 relays plus chokes and condensers. **£6.70**

### TWO MOTION SWITCH UNIT

Unit contains 3 x 10 bank 11 way switch wired to 1,400 position tag board giving possible 660 single pole switch positions. 50V d.c. **£4.75**

### UNISELECTORS

3 bank 25 way .. .. . 80p  
4 bank 25 way .. .. . 90p  
5 bank 25 way .. .. . £1  
6 bank 25 way .. .. . £1.10

**STEP UP SWITCH** with loose contacts .. .. . £1.75

**TOGGLE SWITCH** 3 position 2 pole each .. .. . 25p


**INDICATOR LAMP STRIPS** 10 lamps .. .. . 15p

Post and packing free

### READER MAIL SERVICE

11 ASHDALE DRIVE, WITHINGTON  
MANCHESTER M20 9TF
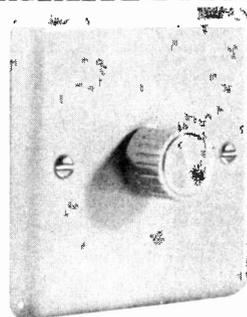
## Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal, light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radiator: 600—£3.20 Kit Form £2.70  
300—£2.70 Kit Form £2.20

All plus 10p post and packing.  
Please send C.W.O. to:—

### DEXTER & COMPANY

1 ULVER HOUSE, 19 KING STREET  
CHESTER CH1 2AH Tel. 0244-25883

As supplied to H.M. Government Departments





**LARGEST STOCKS  
WIDEST RANGE**


**SEMICONDUCTORS & COMPONENTS**

**BRAND NEW  
GUARANTEED**

**TRANSISTORS**

2G391	30p	2N3405	45p	40311	15p	BC172	15p	B8W70	27p	NKT238	25p
2G392	20p	2N3414	22p	40312	35p	BC173	22p	B8X19	17p	NKT240	27p
2G393	20p	2N3415	22p	40314	37p	BC182	22p	B8X20	17p	NKT241	27p
2G396	42p	2N3416	37p	40320	47p	BC183	12p	B8X21	17p	NKT242	27p
2G398	30p	2N3417	37p	40323	32p	BC184	15p	B8X22	17p	NKT243	27p
2G399	30p	2N3570	11.25	40324	47p	BC212L	12p	B8X35	47p	NKT244	17p
2G371	15p	2N3572	8.75	40326	37p	BCY30	27p	B8X26	27p	NKT245	20p
2G374	20p	2N3605	27p	40329	30p	BCY31	30p	B8X60	62p	NKT281	20p
2G381	20p	2N3606	27p	40330	30p	BCY32	50p	B8X61	62p	NKT292	20p
2N404	22p	2N3607	22p	40344	27p	BCY33	25p	B8X76	22p	NKT294	20p
2N696	20p	2N3702	12p	40347	52p	BCY34	30p	B8X77	27p	NKT292	20p
2N697	20p	2N3703	12p	40348	52p	BCY38	40p	B8X78	27p	NKT274	20p
2N698	20p	2N3704	17p	40361	47p	BCY39	60p	B8X78	27p	NKT275	20p
2N706	12p	2N3705	15p	40362	57p	BCY40	50p	B8Y10	27p	NKT401	27p
2N706A	12p	2N3706	15p	40370	52p	BCY42	15p	B8Y11	27p	NKT402	27p
2N709	62p	2N3707	12p	40406	37p	BCY43	15p	B8Y24	15p	NKT403	27p
2N718	25p	2N3709	10p	40407	40p	BCY58	22p	B8Y25	15p	NKT403	27p
2N726	30p	2N3710	11p	40408	52p	BCY59	22p	B8Y26	17p	NKT404	27p
2N727	20p	2N3711	12p	40410	62p	BCY60	97p	B8Y27	17p	NKT406	27p
2N914	17p	2N3715	22.25	40467A	57p	BCY70	20p	B8Y28	17p	NKT406	27p
2N916	17p	2N3716	22.90	40468A	57p	BCY71	42p	B8Y29	17p	NKT452	62p
2N916A	17p	2N3716	22.90	40468A	57p	BCY72	17p	B8Y32	25p	NKT452	62p
2N920	20p	2N3751	25p	40674	81p	BCZ10	27p	B8Y36	25p	NKT603F	32p
2N930	27p	2N3823	37p	AC107	20p	BD116	27p	B8Y38	22p	NKT613F	32p
2N1090	22p	2N3854	27p	AC126	20p	BD121	25p	B8Y38	22p	NKT613F	32p
2N1091	22p	2N3854A	27p	AC127	25p	BD123	82p	B8Y40	32p	NKT677F	32p
2N1131	25p	2N3855	27p	AC128	20p	BD124	82p	B8Y51	32p	NKT771	25p
2N1132	25p	2N3855A	30p	AC154	22p	BD131	75p	B8Y52	32p	NKT781	25p
2N1302	17p	2N3836	30p	AC176	62p	BD132	80p	B8Y53	37p	NKT10419	30p
2N1303	17p	2N3836A	35p	AC187	62p	BD133	80p	B8Y54	40p	NKT10439	37p
2N1305	22p	2N3858	30p	AC189	20p	BDY11	11.25	B8Y54	40p	B8Y22	7p
2N1306	25p	2N3859	30p	AC17	27p	BDY17	11.50	B8Y56	90p	NKT10519	32p
2N1307	25p	2N3859A	32p	AC19	25p	BDY18	11.75	B8Y79	47p	NKT20339	47p
2N1308	30p	2N3860	30p	ACY20	25p	BDY19	11.75	B8Y79	47p	NKT80111	77p
2N1309	30p	2N3866	21.50	ACY21	25p	BDY20	11.25	B8Y82	52p	NKT80112	77p
2N1307	17p	2N3877	40p	ACY22	20p	BDY38	97p	B8Y90	57p	NKT80113	97p
2N1612	20p	2N3984	40p	ACY28	20p	BDY60	61.25	B8Y95A	12p	NKT80113	97p
2N1631	35p	2N3900	37p	ACY28	20p	BDY61	61.25	C111	11.12p	NKT80211	92p
2N1632	30p	2N3900A	40p	ACY40	20p	BDY62	61.25	C424	27p	NKT80212	92p
2N1637	30p	2N3901	97p	ACY41	25p	BF115	25p	C425	55p	NKT80212	92p
2N1638	27p	2N3903	35p	ACY44	40p	BF117	47p	C426	40p	NKT80214	92p
2N1671B	11	2N3904	35p	AD140	52p	BF163	37p	C428	37p	NKT80215	92p
2N1711	35p	2N3905	37p	AD149	47p	BF167	25p	C744	30p	NKT80215	92p
2N1890	32p	2N3906	37p	AD150	42p	BF173	32p	D13T1	62p	OC20	75p
2N1893	37p	2N3908	47p	AD150	42p	BF177	30p	D16P1	37p	OC22	50p
2N2147	82p	2N4059	10p	AD162	37p	BF178	30p	D16P2	40p	OC23	60p
2N2148	57p	2N4060	12p	AD166	42p	BF179	30p	D16P3	37p	OC24	60p
2N2160	67p	2N4061	12p	AD174	25p	BF180	35p	D16P4	40p	OC25	50p
2N2193	40p	2N4062	12p	AF115	25p	BF181	32p	DIET102	30p	OC26	27p
2N2193A	42p	2N4244	47p	AF116	25p	BF184	25p	GET113	20p	OC28	62p
2N2194	30p	2N4286	17p	AF117	25p	BF185	42p	GET114	20p	OC29	62p
2N221	27p	2N4286	17p	AF118	62p	BF195	17p	GET118	20p	OC35	50p
2N2218	32p	2N4287	17p	AF119	62p	BF196	42p	GET119	20p	OC36	62p
2N2219	32p	2N4288	17p	AF120	25p	BF197	42p	GET120	52p	OC41	22p
2N2220	25p	2N4289	17p	AF125	20p	BF198	42p	GET873	12p	OC42	25p
2N2221	25p	2N4290	17p	AF126	20p	BF198	42p	GET880	30p	OC44	20p
2N2222	30p	2N4301	17p	AF127	17p	BF200	52p	GET880	30p	OC45	12p
2N2225	30p	2N4302	17p	AF127	17p	BF204	20p	GET882	20p	OC46	15p
2N2257	11-07	2N4303	17p	AF130	37p	BF225	30p	GET889	22p	OC70	12p
2N2257	11-07	2N4303	17p	AF130	37p	BF225	30p	GET890	22p	OC71	12p
2N2368	17p	2N5027	52p	AF178	42p	BF237	22p	GET897	22p	OC72	12p
2N2369	17p	2N5028	57p	AF179	72p	BF238	22p	GET898	22p	OC73	12p
2N2369A	17p	2N5029	47p	AF180	52p	BF244	32p	GET897	22p	OC74	12p
2N2410	42p	2N5030	42p	AF181	42p	BFW58	27p	GET898	22p	OC74	12p
2N2483	27p	2N5032	42p	AF239	42p	BFW39	25p	MJ400	11.07p	OC75	22p
2N2484	22p	2N5174	55p	AF279	47p	BFW60	25p	MJ420	11.12p	OC76	22p
2N2539	22p	2N5175	55p	AF280	42p	BFW61	47p	MJ421	11.12p	OC77	20p
2N2540	22p	2N5176	45p	AFZ11	22p	BFX12	22p	MJ430	11.02p	OC81D	20p
2N2613	35p	2N5232A	30p	ASY26	37p	BFX13	22p	MJ430	95p	OC83	25p
2N2614	30p	2N5245	45p	ASY27	37p	BFX29	30p	MJ480	97p	OC84	25p
2N2646	52p	2N5246	42p	ASY28	27p	BFX30	30p	MJ480	97p	OC84	25p
2N2689	32p	2N5249	42p	ASY29	27p	BFX43	37p	MJ490	11.25p	OC139	32p
2N2711	25p	2N5265	43.25	ASY34	25p	BFX44	37p	MJ491	11.27p	OC140	32p
2N2712	25p	2N5266	42.75	ASY30	25p	BFX48	67p	MJ491	11.27p	OC140	32p
2N2713	27p	2N5267	42.62	ASY30	25p	BFX84	25p	MJ1800	12.02p	OC171	30p
2N2714	30p	2N5305	40p	ASY51	32p	BFX85	25p	MJ3240	62p	OC171	30p
2N2866	62p	2N5306	40p	ASY54	25p	BFX86	25p	MJ520	87p	OC200	60p
2N2904	30p	2N5307	37p	ASY96	32p	BFX87	27p	MJ521	87p	OC201	60p
2N2904A	30p	2N5308	37p	ASZ21	25p	BFX98	25p	MJ2955	87p	OC202	75p
2N2905	37p	2N5309	62p	AU103	41.25	BFX99	62p	MJ2955	87p	OC203	42p
2N2905A	37p	2N5310	42p	BC107	12p	BFX93A	62p	MJ3065	11-37p	OC204	42p
2N2906	25p	2N5354	27p	BC109	12p	BFY10	32p	MJ3065	42p	OC205	90p
2N2906A	25p	2N5355	27p	BC108	12p	BFY11	42p	MJ3065	42p	OC207	75p
2N2907	15p	2N5356	32p	BC109	12p	BFY12	32p	MJ3065	42p	OC207	75p
2N2923	30p	2N5365	47p	BC113	80p	BFY14	22p	MJ3065	42p	OC207	75p
2N2924	15p	2N5366	32p	BC115	27p	BFY19	32p	MJ3065	42p	OC207	75p
2N2925	15p	2N5367	37p	BC116A	27p	BFY20	11.60p	MJ3065	42p	OC207	75p
2N2926	20p	2N5457	37p	BC118	32p	BFY21	42p	NKT00018	37p	IP29A	24p
.. Green	14p	28005	75p	BC121	20p	BFY24	45p	NKT124	42p	IP30A	24p
.. Yellow	12p	28020	22	BC122	20p	BFY25	25p	NKT125	27p	IP31A	24p
.. Orange	12p	28102	50p	BC125	35p	BFY26	20p	NKT126	27p	IP32A	24p
2N3011	30p	28103	25p	BC126	35p	BFY29	20p	NKT127	27p	IP33A	24p
2N3014	32p	28104	25p	BC140	35p	BFY30	50p	NKT135	27p	IP34A	24p
2N3033	25p	28501	32p	BC147	17p	BFY41	50p	NKT137	27p	IP34A	24p
2N3054	25p	28502	35p	BC148	12p	BFY43	62p	NKT210	30p	T1834	40p
2N3055	75p	28503	37p	BC149	17p	BFY50	22p	NKT211	30p	T1843	40p
2N3133	30p	28128	70p	BC152	17p	BFY51	22p	NKT212	30p	T1845	40p
2N3134	30p	28129	77p	BC157	17p	BFY52	22p	NKT213	30p	T1846	40p
2N3135	25p	28140	77p	BC158	17p	BFY53	22p	NKT214	22p	T1847	40p
2N3136	25p	28141	72p	BC159	20p	BFY56A	57p	NKT215	22p	T1848	40p
2N3390	25p	28142	55p	BC160	62p	BFY76	42p	NKT216	27p	T1849	40p
2N3391	20p	28143	67p	BC167	15p	BFY77	57p	NKT217	27p	T1850	12p
2N3391A	17p	R.C.A.	87p	BC168B	14p	BFY90	67p	NKT219	30p	T1851	12p
2N3393	15p	28129	11.25	BC168C	14p	BFY93	67p	NKT223	27p	T1852	12p
2N3394	15p	40244	22p	BC169B	14p	BPX29	11.80p	NKT224	25p	T1853	12p
2N3402	22p	40251	27p	BC169C	14p	BPY10	11.45p	NKT225	25p	T1860	22p

# NOW AVAILABLE SONY

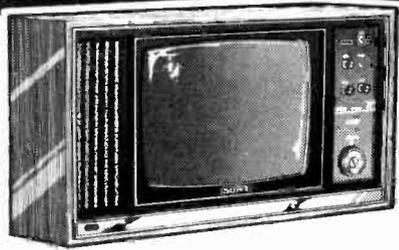

## KV-132 13" COLOUR TELEVISION

This amazing value 13in UHF colour TV is now available from Lasky's. Designed with the new TRINITRON tube to give you superb colour reproduction, sharper focusing with reliability and durability. Its light weight enables it to be moved from room to room with ease and like all Sony products it has solid state circuitry for trouble free operation. Finished in a handsome teak cabinet 20in x 13in x 16in. Weight 39lbs. A.c. mains 240 volts.

**LASKY'S PRICE**  
**£199**

COMPLETE with free Parabolic aerial valued at £6. Post free in UK only

## EXCLUSIVE TM-1 MODEL TM-1 MINI-TESTER



The first of Lasky's top value meters, the TM-1 is a tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to 3% of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case—with white and metallic red/green figuring. Ohms zero. ● DC V: 0-10-50-250-1,000 at 1K/OPV. ● AC V: 0-10-50-250-1,000 at 1K/OPV. ● DC CURRENT: 0-1mA, 100mA. ● Resistance: 0-150KΩ. ● Decibels: 5 size only -10dB to +22dB. ● Complete with test leads, 3 1/2" x 2 1/2" battery and instructions.

**LASKY'S PRICE £1.95** POST 13p

## TM 5 5K/ohms V Pocket Multimeter

Another new look pocket multi-meter from Lasky's providing top quality and value. The "slimline" impact resistant case—size 4 1/2in x 2 1/2in x 1 1/2in, fitted with extra large 2 1/2in square meter. Readability is superior on all low ranges, making this an excellent instrument for servicing transistorised equipment. Recessed click stop selection switch. Ohms zero adjustment. Buff finish with crystal clear meter cover.

- DC V: 3-15-150-300-1,200 at 5K OPV.
- AC V: 6-30-300-600 at 2.5K OPV.
- DC Current 0-300μA, 0-300mA.
- Resistance: 0-10K ohms, 0-1M ohms.
- Decibels: -10dB to 16dB.
- Complete with test leads, battery and instructions.

**LASKY'S PRICE £2.95** POST 13p

## BSR McDONALD MP60

High precision low-mass counterbalanced pick-up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.



**LASKY'S PRICE £12.50** Post 35p

## BSR McDONALD UNITS and PACKAGES

A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cartridge. D. Comp. wired on BSR plinth with cover. E. as D plus AD76K cartridge. Post for packages 50p.

MODEL	A	B	C	D	E
610	£15.45	£18.75	£22.50	£24.50	£28.50
510	£13.45	£16.95	£20.75	£22.00	£26.00
310	£9.95	£13.45	£17.25	£21.00	£23.50
MP60	£12.50	£15.75	£19.50	£21.50	£25.50

## GARRARD UNITS and PACKAGES SL 55B Four-speed auto changer

**LASKY'S PRICE £10.50** POST 35p

Garrard SP25 Mk. III	£11.50	Garrard AP76 without cart.	£20.95
Garrard SP25 Mk. III wired 9TA cart.	£12.00	Garrard 3000 with 9TA cart.	£10.50
Garrard SP25 Mk. III with 9TA cart.	£13.95	Garrard 2025TC with 9TA cart.	£9.85

GARRARD PACKAGES	POST FOR ALL PACKAGES 50p
Garrard AP76 with AD76K cart. and Lasky's plinth and cover	£35
Garrard AP76 with Shure M44E cart. and Lasky's plinth and cover	£40
Garrard SP25 Mk. III, AD76K cart. and Lasky's plinth and cover	£20
Garrard SP25 Mk. III, Micro M2100/e cart. and Lasky's plinth and cover	£25

## DENSHI BOARD KITS EXPERIMENTAL AND EDUCATIONAL ELECTRONIC CIRCUIT SYSTEMS

The DENSHI BOARD system enables the young experimenter and electronics hobbyist to produce a wide range of transistor circuits of increasing sophistication—without soldering or the use of any tools at all! Basically the system comprises of a slotted circuit board into which plug-in components and bridge pieces are set to produce up to 30 different circuits. The components are encapsulated in transparent plastic blocks bearing the appropriate circuit symbol and value. Thus enabling even the complete novice to visually grasp the fundamentals of circuitry after only a few moments study.



### DENSHI BOARD KIT SR 1A

Comprises: Base board, tuner block, 4 resistors, choke coil, transformer, 2 x 8A transistor for RF, 2 diodes, 3 capacitors, battery block, morse key, antenna lead, crystal earphone, various bridge and connecting pieces. This kit permits the building of 16 basic circuits.

DENSHI BOARD KITS come complete with an 80 page manual of circuits and data. Manuals are available separate at 23p. Post 3p refundable if you purchase kit.


**LASKY'S PRICE £3.35** POST 13p

### DENSHI KIT SR 2A as SR 1A with these additional parts:

25B transistor for AF, 2 resistors, capacitor, crystal microphone, test probes, electrode; additional connecting pieces, 9V battery. This kit permits the building of 30 circuits.

**LASKY'S PRICE £5.25** POST 13p

## DIGITAL CLOCK SCOOP

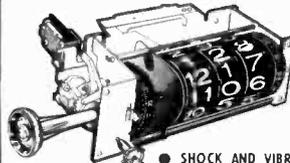

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12-HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION
- SYNCHRONOUS MOTOR

- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

Exclusively from Lasky's for you to mount into any housing. The clock measures 4 1/2 W x 1 1/2 H x 3 1/2 D (overall from front of drum to back of switch). SPEC.: 210/240V a.c., 50Hz operation; switch rating 250V, 3A. Complete with instructions.

HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS.

**LASKY'S PRICE £6.95** POST 18p

SPECIAL QUOTATIONS FOR QUANTITIES

# Lasky's Radio Ltd

207 EDGWARE ROAD, LONDON, W.2.

Tel: 01-723 3271

33 TOTTENHAM CT. RD, LONDON, W1P 9RB.

Tel: 01-636 2605

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

109 FLEET STREET, LONDON, E.C.4.

Tel: 01-353 5812

152/3 FLEET STREET, LONDON, E.C.4.

Open all day Thursday, early closing 1 p.m. Saturday

Tel: 01-353 2833

HIGH FIDELITY AUDIO CENTRE

42-45 TOTTENHAM CT. RD, LONDON, W1P 9RD.

Open all day, 9 a.m. - 6 p.m. Monday to Saturday



ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821

VOL. 7  
August

No. 8  
1971

# PRACTICAL ELECTRONICS

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial Assistants D. BARRINGTON G. GOBOLD M. KENWARD  
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY P. A. LOATES  
Advertisement Manager D. W. B. TILLEARD

## CHANGE OF COMMAND

**W**AR games played with miniature models and conducted on severely objective lines have for long been an essential part of military training. More recently war gaming has been taken by non-professionals and has grown into a popular hobby which its adherents claim is most exciting and mentally stimulating.

Today our professional militarists play a very scientific game. Advanced technical aids are employed to help create realism and to determine accurately the results achieved by every manoeuvre in the simulated battle. The electronic computer has replaced the human adjudicator of former times.

The non-professional devotees playing for fun and recreation are (so we gather) always looking for ways to raise the status of their pastime and to dispel any juvenile "playing with toy soldiers" image it may conjure up in the minds of the uninitiated. Now, thanks to electronics, it is possible to instal more realism into their game by use of a home-made computer.

However, recourse to electronics does not have to end there, we venture to suggest. Come to think of it, why should our amateur, spare-time strategists be satisfied with inanimate models (soldiers, tanks, warships, or what have you) that must be deployed by hand? Each piece in the game could well be a miniature automaton capable of inflicting punishment on the enemy while, being sensitive to missiles directed towards it, able to manoeuvre out of the line of fire.

But steady on, some dire consequences will arise from the unfettered use of electronics. Will our amateur battle commanders be prepared to sit quietly and impotently, merely watching while the automatons fight it out on the carpet or table top, unaided by human minds or hands?

Quite a problem. But not, in actual fact, confined to the world of make-believe and harmless pastimes. It is one the professional militarists will have to face shortly, *for real*. It is reported that in the United States a special Combat Development Command committed to the automation of modern warfare is already at work. The whole paraphernalia of science and technology is being pressed into service, towards this end. Every move of the enemy will be detected by light or heat radiation sensors, robots will replace front line troops, and the wealth of data derived from such sources will be processed by computers which will then advise the most effective tactics to employ.

The next logical step is to let the computers control and fire all weapons, and so dispense with any human intervention at all. A chilling prospect for the top brass, who will presumably be relegated to the role of computer data processors.

## THIS MONTH

### CONSTRUCTIONAL PROJECTS

WAR GAMES COMPUTER	624
VOLTAGE STABILISER	633
P.E. AURORA	638
SEISMOGRAPH	646

### SPECIAL SERIES

RADIO ASTRONOMY TECHNIQUES—3	658
---------------------------------	-----

### GENERAL FEATURES


COMPONENTS SHOW	669
-----------------	-----

### NEWS AND COMMENT

EDITORIAL	623
SPACEWATCH	637
NEWS BRIEFS	653
ELECTRONORAMA	654
MARKET PLACE	656
BOOK REVIEWS	666

*Our September issue will be published on  
Friday, August 20*

© IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2-65 (£2 13s. 0d).  
Practical Electronics, Fleetway House Farringdon St., London, E.C.4. Phone: Editorial 01-634 4452; Advertisements 01-634 4202

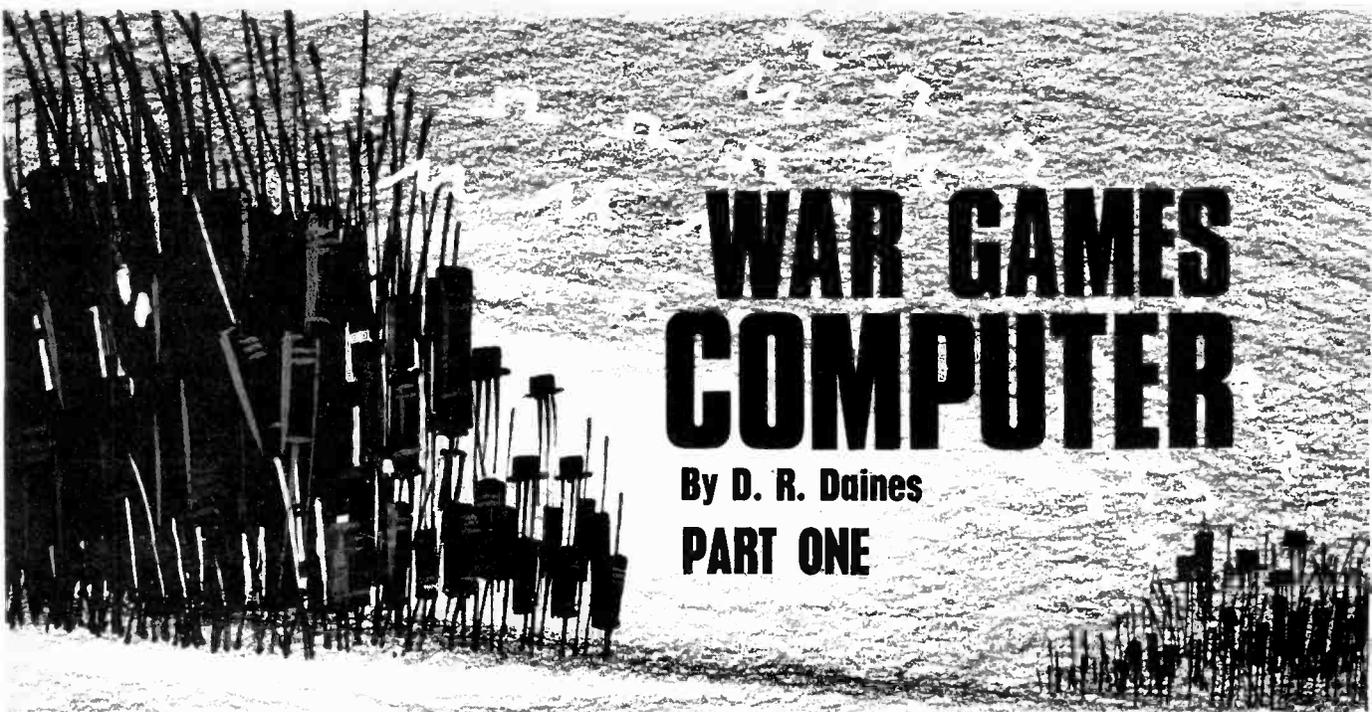

# WAR GAMES COMPUTER

By D. R. Daines

## PART ONE

***It is said that deep in the heart of every Englishman is a sea-dog trying to get out. Whether this is true or not, many people will find the games to be described of great interest, affording as they do real insight into the problems of Naval strategy as well as some fun and excitement.***

**W**AR-GAMING as a hobby suffers under a severe handicap: either chance assumes too large an aspect (six—you're dead!) or else in the search for realism, rules become so complicated and tedious that all pleasure is lost. In either case, interest soon wanes. Again, most war-gamers are tied to the use of dice for their chance effects. War-gaming has been called "chess with a thousand pieces", but whereas there is no chance on the chessboard, there is on the battlefield.

Chance therefore must play some part at least, and it may be that as long as war-gamers continue to use dice they will be considered to be merely "playing soldiers". It follows that electronics—and particularly computerisation—has much to offer war-gaming in accuracy, speed and a carefully controlled modicum of chance.

Constructors of *Operation Seasearch* will perhaps have noticed that the use of dice for chance effects in variations 5 and 6 can lead to some absurd situations—an unarmed supply ship sinking a cruiser, for example. When highly realistic effects are required, we must turn to computerisation since so many variables are involved.

### NAVAL GUNNERY

The computer to be described has been designed as a naval gunnery computer, but it will be shown that by the use of card overlays it may be used

most effectively for any other form of gunnery and for any period; whether for Roman galleys, Napoleonic artillery, American Civil War, modern missiles or what-have-you.

The computer has been designed in stages so that it is usable at each stage, but of course each additional stage adds to the versatility and convenience. There is a built-in ability to handle ten targets, with provision for the external addition of others without number.

Since this external addition is very inexpensive and easily adaptable, whole fleets or armies may be involved. This opens up exciting possibilities, with any number of people taking part. Each could captain his own ship, for example, with admirals able to communicate only by "signal"—slips of paper handed to captains the move after they were written.

The setting-up of the computer requires only a few seconds and the result of a salvo is available immediately, in the complete version. The total cost is in the region of £30, but since it can be built in stages this can be spread over many months, play beginning almost immediately, or left at some suitable stage with limited operations.

### EFFECT OF CHANCE

In a combat between any two contestants, whether war, chess, or other game, it is necessary to draw a distinction between striking strength and resistive strength (Fig. 1). A low resistive strength increases damage sustained, which in turn lowers resistive strength still further as well as affecting striking power. It is well known that soccer teams must keep a fine balance between attack and defence; too much emphasis on one or the other results in lost games. Similarly in war, H.M.S. *Hood* was sunk by *Bismarck* mainly because her power to resist in no way matched her power to strike.

Chance enters at every point. A few yards difference in the landing point of a shell may make all the difference between superficial damage and sinking; in much the same way a gunner's indigestion or personal problems can affect the outcome of a battle.

We might perhaps add that one of the horrors of modern war is that the element of chance is reduced to a mathematical certainty, but the reader is invited to speculate on Fig. 1, considering the effects of chance if two men are shooting at each other with smooth-bore pistols, bow and arrows, or machine guns.

## DAMAGE SUSTAINED

Fig. 2 follows the course and effects of a naval salvo. The number of shells fired in a certain span of time depends on their calibre, the number of guns firing, and the skill of the crew. Not all of the shells fired will be hits. A list of factors determining the proportion of hits has been drawn up in the diagram. It is not definitive, but includes the major factors; readers may like to add their own.

Out of the much smaller number of hits, the amount and severity of damage sustained will vary enormously according to (again) the calibre of the shells, the range, the type of shell, the thickness of armour and chance. A lot of hits will cause fire to break out, which of course assumes a malignancy of its own (particularly in wooden ships) and must be brought under control if the fight is to be carried on.

voltage applied and this is adjusted in analogue form by the CALIBRE and MORALE controls. Strictly speaking, morale and efficiency are two different things and many war-gamers carefully differentiate between them, but for the purpose of this computer they are considered synonymous.

The PROBABILITY multivibrator runs much slower and therefore in conjunction with a gate would reduce the number of pulses passing to a strict proportion of their original.

However, to make the outcome unpredictable there is a third and even more slow-running multivibrator termed CHANCE, in which not only is the repetition rate governed by the SEA control, but the mark/space ratio is altered by the VISIBILITY control.

Now the gate will pass pulses forward only when pulses are present from all three multivibrators. It will be apparent that adjustment of any of the seven controls will affect the pattern of outgoing pulses. Details will be given of a burst fire button circuit which can be used in place of the dial contacts.

The pulses are normally grounded through the pulse contacts at the back of a telephone dial, hence nothing appears beyond this point. Dialling a "1" will allow a few pulses to pass forward; dialling a "2" will pass twice this number, and so on.

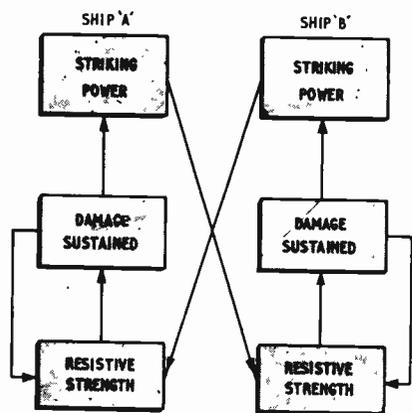


Fig. 1. War game strategy

Many war-gamers use multiple tables and charts, with much dice-throwing, to get realistic results along the lines of the above. The writer has played such games and very good they are too, but when it takes nearly half an hour to work out the result, interest soon wanes.

## ANALOGUE COMPUTER

The outline of Fig. 2 is roughly followed in the design of the computer. This is an analogue computer of a specialised type designed specifically for use in mock naval battle. One could if preferred relabel the controls to suit other kinds of battle.

Fig. 3 shows the full block diagram of the system parameters, although it is sub-divided so that a smaller system can be built.

Individual shells are represented by pulses generated in the "rate of fire" multivibrator. The rate at which they are generated is governed by the

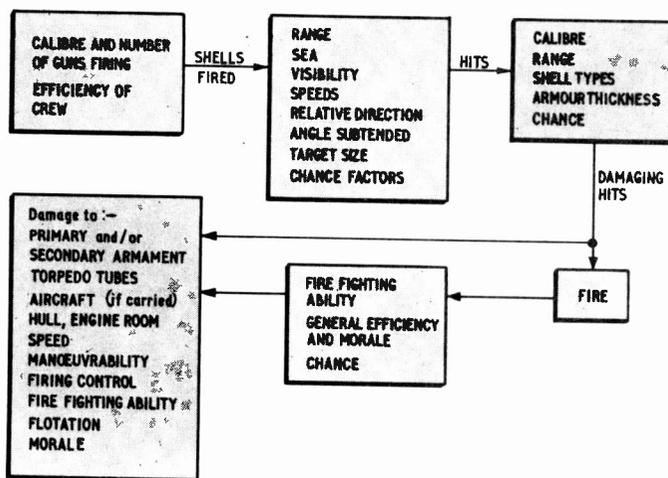


Fig. 2. Parameters affecting the war game strategy

Hence the dial is used to feed the computer with the number of guns firing and also functions as a start switch since nothing can go forward until the dial is operated.

There is a further chance element here since at the heavier calibre settings the rate of fire multivibrator runs at a slower frequency than the dial. In other words, the dial contacts may open at an instant when no pulse is present to pass. This happens to other settings too, but in the case of heavy calibres the pulse may arrive between openings of the dial contacts.

Of course, as in any other chance element, the more samplings that are taken the nearer does the overall result approach to a mathematical proportion.

## HIT ATTENUATION

All pulses passing the dial are considered potential hits, but as yet all are of equal amplitude; light


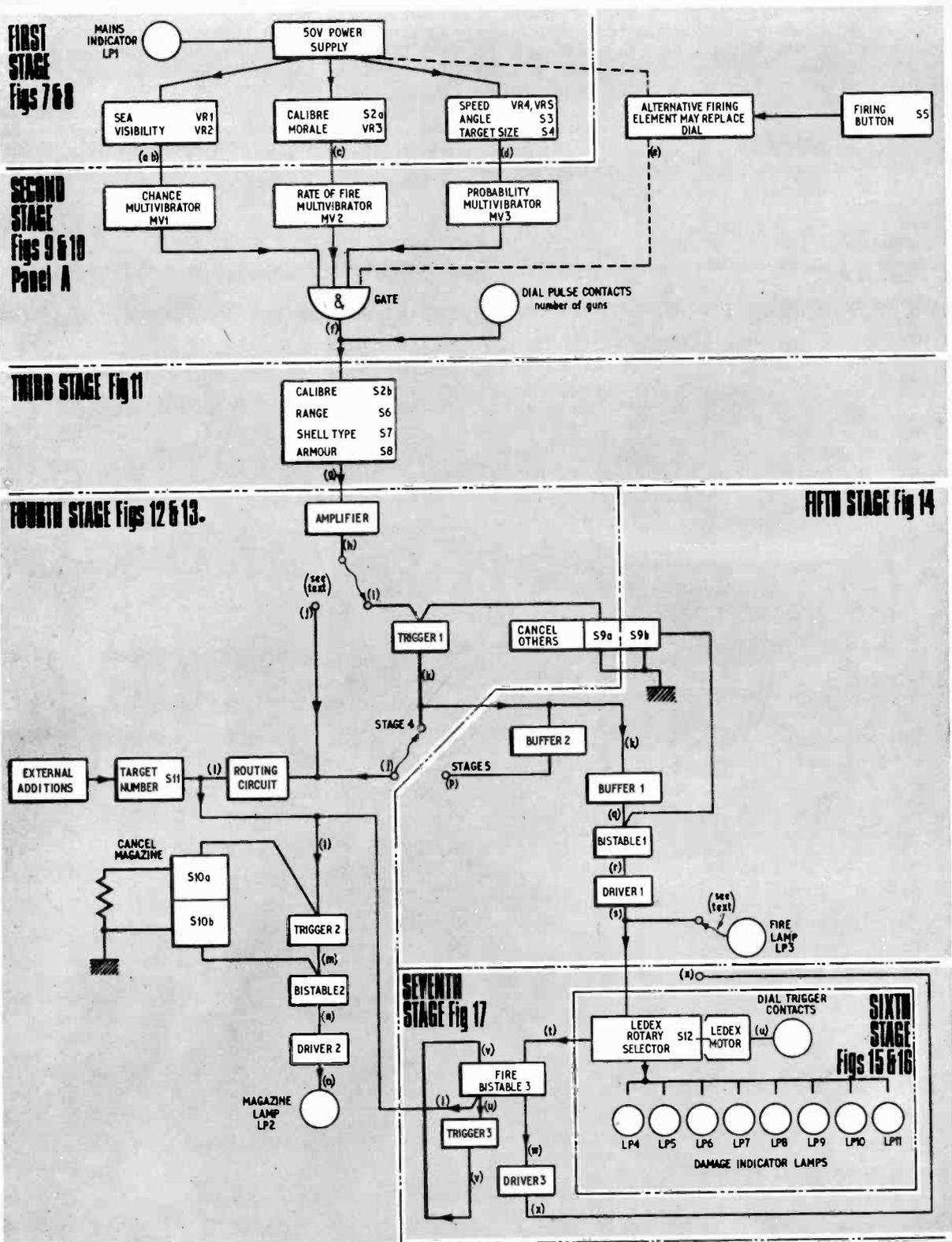


Fig. 3. Block diagram of the complete war game computer with alternative operational modes for smaller systems. The equipment is built up in stages, each stage being a workable progression from the previous

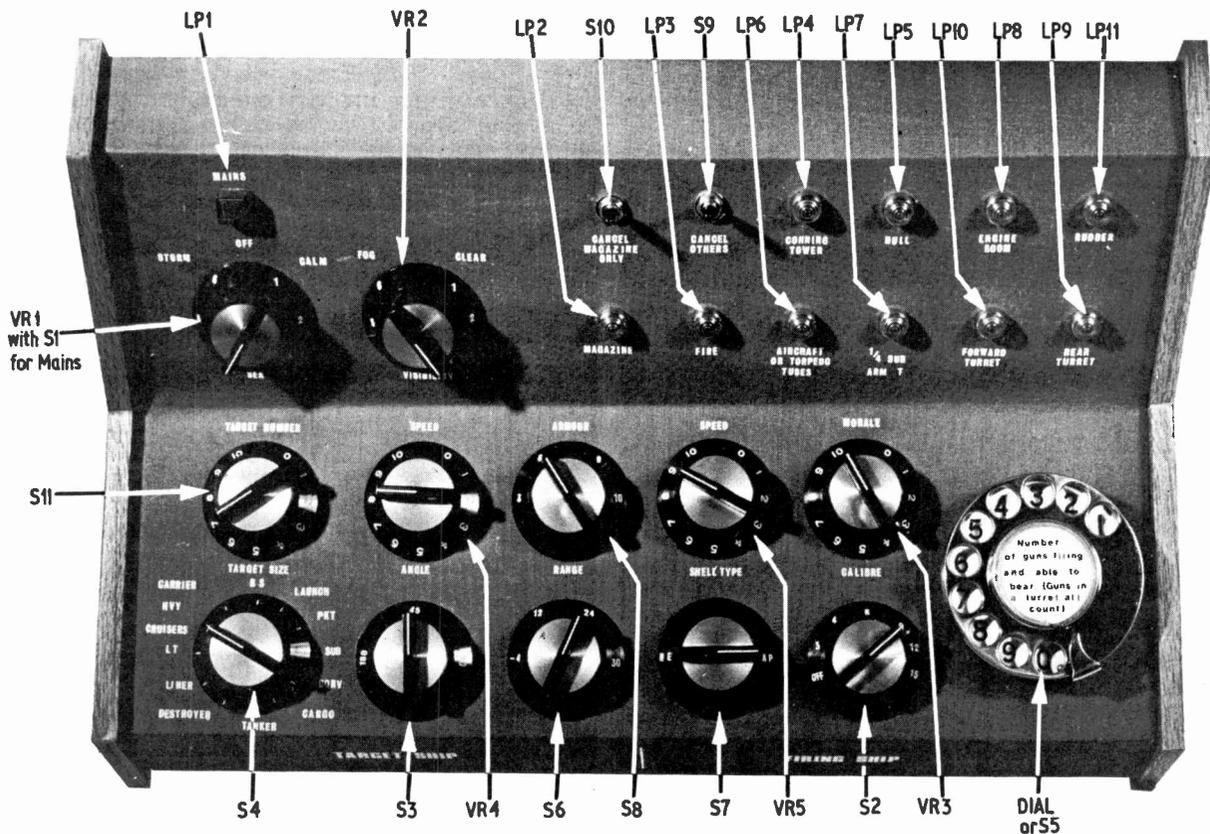

The controls are temporarily fitted for marking stop positions, then removed for lettering

calibre as well as heavy. Now they are attenuated according to their ability to inflict quantitative damage. To this end they pass through voltage dividers on the CALIBRE, RANGE, SHELL TYPE and ARMOUR controls and then passed through an amplifier which also functions as a buffer.

The output is applied to a storage capacitor. When the energy of the incoming pulses has raised the charge on the capacitor to a certain preset level, Schmitt Trigger 1 fires, passing on one pulse of fixed duration and amplitude, which we might term a unit of damage.

In this way, many low amplitude pulses are required to charge the capacitor and produce a damage pulse, but only one high amplitude pulse produces the same damage. Damage pulses may occur only once per salvo, immediately upon completion of dialling.

### MAGAZINE SECTION

The damage pulses are applied equally to two buffers. Buffer 2 presents pulses to another storage capacitor, which fires Trigger 2. There is a separate capacitor for each target ship, of different size to suit the size of the target; a rotary switch S11 switches the appropriate target capacitor into the circuit. The capacitor will of course retain its charge from the time a certain target is under fire to the next and therefore functions as a cumulative damage counter.

When the charge on the capacitor reaches a certain preset level, Schmitt Trigger 2 fires, the outgoing pulse this time switching over Bistable 2. In its second stable state the bistable primes Lamp Driver

2, illuminating a lamp indicating that the magazine has blown up. That particular target ship is of course out of the battle.

### OTHER DAMAGE

A more interesting game results when ships receive damage bit by bit, affecting their fighting capacity. The output from Buffer 1 switches over Bistable 1, which in turn primes Lamp Driver 1.

A single lamp could be taken from this, indicating a unit of damage, but where is the damage? One means of indicating the damage is shown in Fig. 3. Every time the dial is used, a motor-driven rotary switch is made to move round one position of twelve. The switch outputs are used singly and in pairs to indicate eight types of damage—conning tower, hull, rudder, engine room, aircraft or torpedo tubes, sub-armament, forward turret and rear turret.

### FIRE

Another attempt to simulate some realism and to introduce some very real tension into the game is to incorporate a fire. One third of the damage pulses are routed by the Ledex motorised rotary switch to trigger a "fire" bistable, Bistable 3. This lights the "fire" lamp, applies a trickle charge to the storage capacitor in the magazine section and also a third storage capacitor in front of Trigger 3.

When Schmitt Trigger 3 fires, the output switches the bistable off again. Thus in play, when the "fire" lamp lights, the player can do nothing but watch and wait.

If he is lucky, the lamp will go out in ten seconds, but if he is unlucky the magazine lamp will light. Even though the fire lamp will subsequently go out, the magazine lamp will stay on and he is out of the game. This method of using a storage capacitor in conjunction with a bistable and Schmitt trigger is much better than a monostable for long time delays.

That concludes the basic description of the computer functions; more detailed circuits and construction notes follow in seven stages, followed by the final hints of its use in operation.

## CASE CONSTRUCTION

The layout of the computer is in no way critical, so the constructor may lay out his controls as he pleases. He should really decide early on how much of the equipment he is likely to build based on the information given in Fig. 3.

Construction of the case was started with  $\frac{3}{8}$  in thick sheet plywood cut to the dimensions given in Fig. 4. Four rubber feet were screwed to the underside and then the mains transformer T1 bolted on

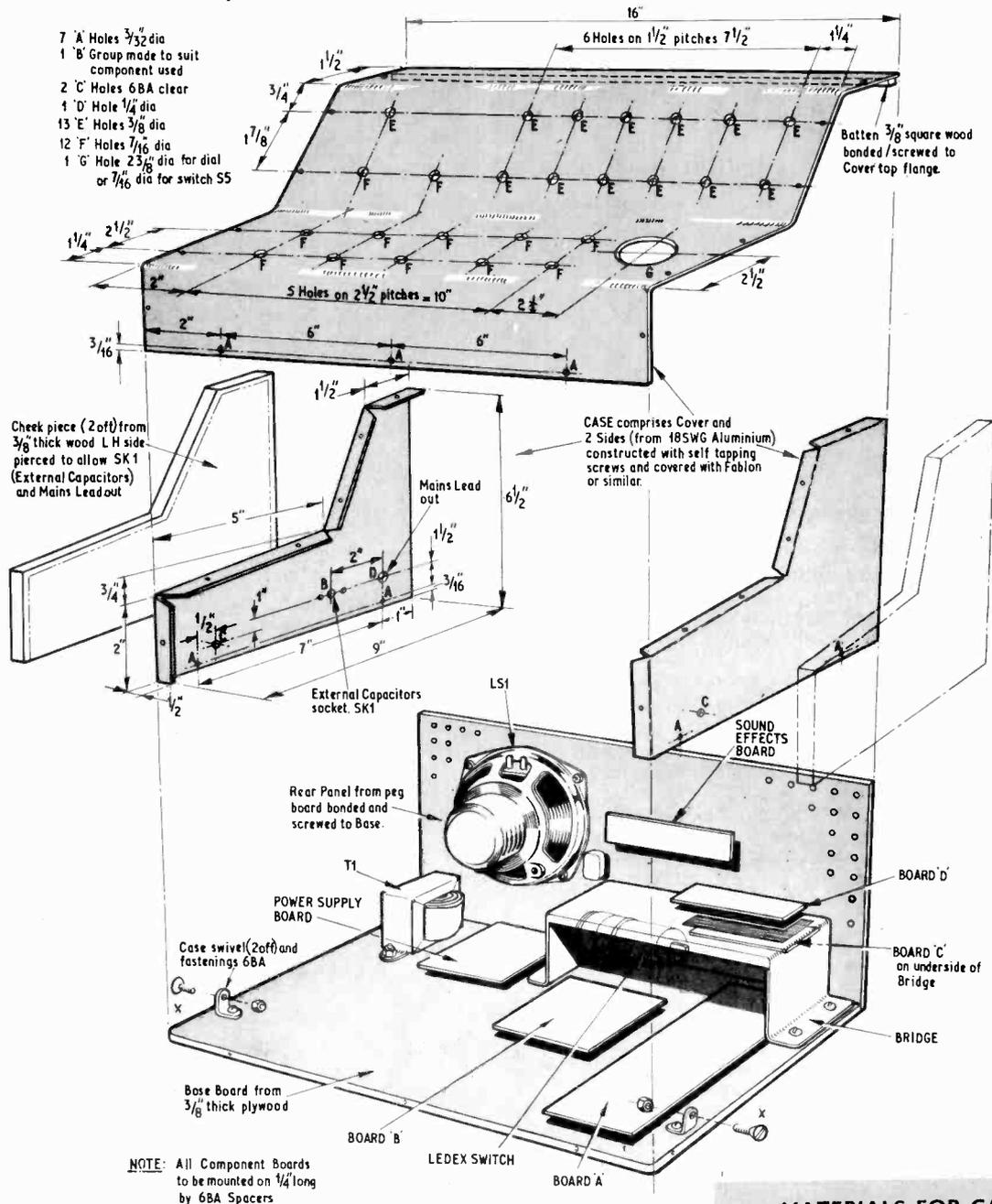


Fig. 4. Construction details of the case and baseboard layout

top. A length of component board was bolted along side to carry the rectifying diodes and smoothing capacitors (Figs. 4 and 7).

The centre tap of T1 secondary was ignored, giving a 50V output. The rectifying diodes can be any type capable of handling 100V at 3 amp, although those shown will handle much more.

The shaped top of the case (Fig. 4) was cut out of heavy-gauge tinplate (which is cheaper than aluminium) and all cutting and drilling completed while the sheet was still flat. Bending was done in a vice, a small-radius curve being left on all corners.

Notice that the bend across the centre is forward, the others all being back. The  $\frac{1}{2}$ in tabs on each side are for soldering or screwing the side pieces on. A gas-torch was used for soldering tinplate since such large sheets of metal conduct away nearly all the heat from a soldering gun.

Many constructors will want to paint the face or use adhesive plastics sheet, but it is wise to make sure all drilling and bending is carried out first. The surface must be absolutely clean and free from grease or finger marks. Excess material at the edges was wrapped round and glued underneath.

The shaped and covered top was then checked against the baseboard for a snug fit and was secured in place by wood screws along the front and at each side. If one screw at each side is left in position (marked "x" on Fig. 4) the top may be pivoted on them, allowing easy access to the panels and underside without disturbing the wiring.

The back of the computer is a piece of perforated hardboard fitting inside the metal top. It is screwed to the edge of the base and to a strip of wood glued and screwed  $\frac{1}{2}$ in inside the top edge.

## LETTERING

With the cover removed from the base, all lamps and controls are temporarily fitted and the positions of all stops marked. Controls are then removed and lettering and spots applied with rub-on Letraset (see photograph).

Note that 12 pointer-type knobs are required with escutcheon plates to match. On the prototype, some escutcheons have numbers 0 to 10 on them, plus one blank space, so they are admirably suited for 12-way switches. The lettering is given a spray of clear lacquer, and the escutcheons replaced.

Lampholders are also fixed at this stage, if required, although they are not wired up until much later. Many "surplus supply" shops will supply an

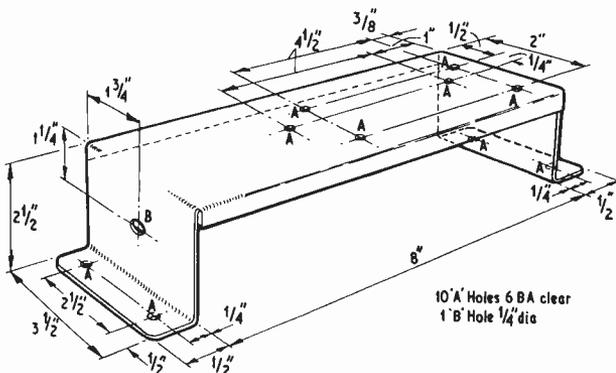


Fig. 5. Panel bridge for mounting the various stage panels

# POWER SUPPLY

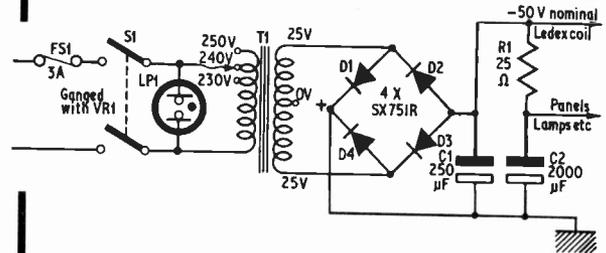


Fig. 6. Circuit diagram of the power supply (stage one)

## COMPONENTS . . .

### STAGE ONE (Power Supply Fig. 7)

#### Resistor

- R1 25Ω 5W wirewound

#### Capacitors

- C1 250μF elect. 50V
- C2 2,000μF elect. 50V

#### Transformer

- T1 Tapped mains primary 0-250; secondary 25-0-25V 2A or 50V 2A

#### Diodes

- D1 to D4 Rectifier diodes SX751R (4 off) or 100V 3A type

#### Switch

- S1 Double pole on/off toggle or may be coupled with VR1

#### Miscellaneous

- FS1 Cartridge fuse 2 amp in mains plug
- LPI Mains neon indicator with ballast resistor
- Rubber grommets, component tag board

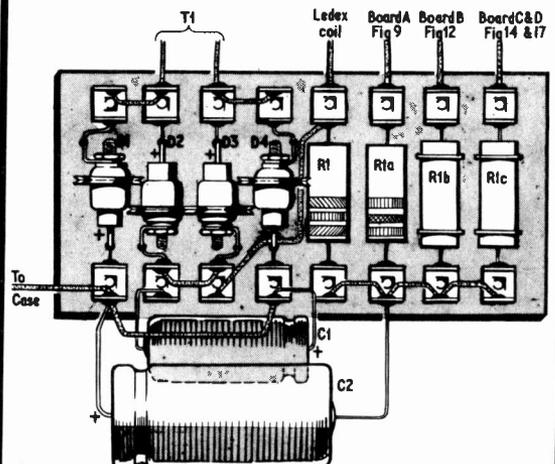


Fig. 7. Wiring of the diodes and capacitors. R1a, R1b, R1c are decoupling resistors 330Ω 3W to supply Boards A, B, C, and D.

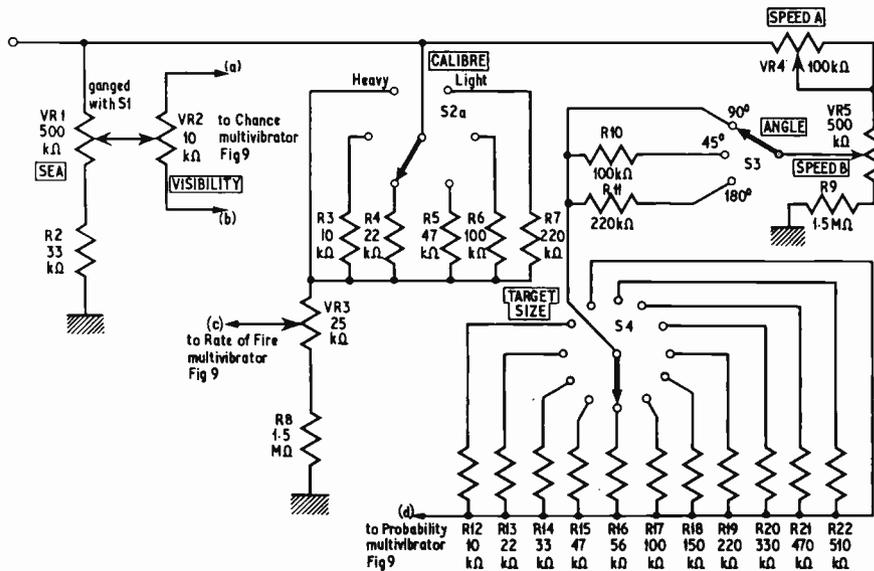


Fig. 8. Analogue parameter controls (stage one)

old telephone dial for about 75 pence or less; after careful cleaning, light oiling and adjusting, it is secured in place with Araldite.

### FIRST-STAGE WIRING

First-stage wiring presents no problems. VR1 has an integral mains double pole on/off switch S1, while the associated mains neon LPI is mounted close by. The incoming three-core mains lead is brought through a rubber grommet and both supply leads soldered to the switch.

Keep the leads from S1 to T1 long enough for the top to open easily. Watch the polarity of the rectifying diodes D1 to D4 very carefully (Fig. 7). Good

smoothing by C1 and C2 is required otherwise the Schmitt Triggers may fire when not wanted. Soldering tags screwed to the base board and metal panel provide convenient take-off points for earth connections.

Wire the controls from Fig. 8, taking off four flying leads of flexible wire, (a), (b), (c) and (d). Resistors to earth such as R2 may be soldered to the tinplate or chassis tags at any convenient spot—there are no problems with earth loops such as occur with audio circuits. One length of flexible wire connects the panel to the positive side of the power pack.

### USING THE FIRST STAGE

For a very small outlay the constructor has an analogue computer giving  $10^7$  variations 10,000,000. If we proceeded no further, this would be worth having. Directions for the full game will be given later, but for the time being we can use what we have built so far in the following way.

Ignore output (b); take output (a) through a 1 megohm resistor and connect it to outputs (c) and (d). The resulting voltage (indicated on a suitable meter) will vary according to the setting of the controls, all resistors acting in a series-parallel divider configuration in a complex manner. The voltage will also depend to a certain extent upon the impedance of the meter used, varying from 48 volts to about 15 volts. This voltage reading is used as the starting point for "damage" points.

For the chance element, one can use a dice, multiply by ten and add to the voltage reading. A points value is accorded to each ship at the commencement of the game and a running total of damage points kept. When damage reaches the awarded value, the ship is sunk.

Many interesting games can be played by varying the chance element (multiplying the dice throw by 5, or squaring) or varying the points value. As a starting point, try 250 for a destroyer and 2,000 for a battleship.

**Next month: Second and third stages**

## COMPONENTS . . .

### STAGE ONE (Analogue Controls Fig. 8)

#### Resistors

R2 33kΩ	R9 1.5MΩ	R16 56kΩ
R3 10kΩ	R10 100kΩ	R17 100kΩ
R4 22kΩ	R11 220kΩ	R18 150kΩ
R5 47kΩ	R12 10kΩ	R19 220kΩ
R6 100kΩ	R13 22kΩ	R20 330kΩ
R7 220kΩ	R14 33kΩ	R21 470kΩ
R8 1.5MΩ	R15 47kΩ	R22 510kΩ
All — 10%, ¼W carbon		

#### Potentiometers

VR1 500kΩ (may have double-pole on/off switch S1)
VR2 10kΩ
VR3 25kΩ All linear carbon types
VR4 100kΩ
VR5 500kΩ

#### Switches

S2 Double-pole, 6-way wafer switch
S3 Single-pole, 12-way (only 3 ways used)
S4 Single-pole, 12-way wafer switch

CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, E0 or 24 volts.

from £1.70

*Sign here..!*

for your miniature soldering iron.


### SK2 Soldering kit

In polystyrene pack, containing 15 watt miniature soldering iron, 240 volts fitted with  $\frac{3}{16}$ " bit, 2 spare bits  $\frac{5}{32}$ " and  $\frac{3}{32}$ ". Coil of resin-cored solder, heat sink, 1A fuse and booklet "How to Solder"



£2.40


### SK1 SOLDERING KIT

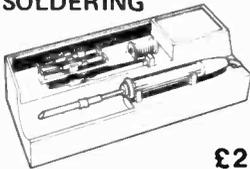

£2.75

In rigid plastic "tool box" containing Model CN - 15 watts - 240 volts miniature iron fitted  $\frac{1}{16}$ " bit. Spare bits  $\frac{3}{32}$ " and  $\frac{1}{32}$ ". Reel of resin-cored solder, heat sink, cleaning pad, stand and booklet "How to Solder"

Model CN 240/2  
15 watts - 240 volts

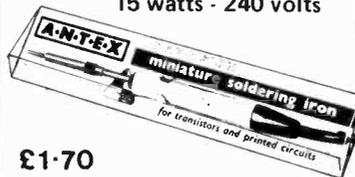

£1.70

Fitted with nickel plated  $\frac{1}{32}$ " bit and packed in handy transparent box.



### PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.  
Telephone: Plymouth 67377/8.  
Telex: 45296. Giro No. 2581000.

- Please send me the Antex colour catalogue
- Please send me the following
- | Quantity | Model | Bit Size | Volts | Price |
|----------|-------|----------|-------|-------|
| .....    | ..... | .....    | ..... | ..... |
| .....    | ..... | .....    | ..... | ..... |

I enclose cheque/P.O./cash value

NAME .....

ADDRESS .....

P.E.8



Model G - 18 watts. Fitted  $\frac{3}{32}$ " bit. Spare bits  $\frac{1}{8}$ ",  $\frac{1}{16}$ " and  $\frac{1}{4}$ " available. For 240 or 220 volts. £1.83



Model F - 40 watts. Fitted  $\frac{5}{16}$ " bit. Spare bits  $\frac{3}{32}$ ",  $\frac{1}{8}$ ",  $\frac{1}{16}$ " and  $\frac{1}{4}$ " available. For 240, 220, 110, 20 volts. From £2.38

Model E - 20 watts. Fitted  $\frac{1}{4}$ " bit. Spare bits  $\frac{3}{32}$ ",  $\frac{1}{8}$ " and  $\frac{1}{16}$ " available. For 240, 220 or 110 volts. From £1.80

Model ES - 25 watts. Fitted  $\frac{1}{8}$ " bit. Spare bits  $\frac{1}{32}$ ",  $\frac{1}{16}$ " and  $\frac{1}{4}$ " available. For 240, 220 or 110 volts. From £1.83

# AUDIO SUPPLIES

## SLASH PRICES! UP TO 60%



### SUPERB PLINTHS & COVERS £3:50

50p P.P.  
for Garrard and B.S.R. SP25, SL65B 3500, 3000, 2025TC, 2000, 1025, 5100, AT6, AT60, 40B, B.S.R. McDonald range. All decks are finished in teak polish and will blend in any modern home. The covers are of tinted Perspex (please state deck when ordering).

**SUPERIOR PLINTHS AND COVERS FOR GARRARD AP75, AP76, SL72B, SL75B and SL95B, £4-99. P.P. 60p (R.R.P. £9-50)**

**FOR ALL YOUR NEEDS IN HI-FI EQUIPMENT SEND A LARGE S.A.E. or PAY A VISIT TO OUR 3-STORY WAREHOUSE**

### SPECIAL OFFER

**GARRARD SP25 Mk. III GOLDRING G800H Superb Plinth and Cover. SINCCLAIR Project 60—Stereo 60 Pre-Amplifier and Control Unit. 2 730's and PZ5. 2 WHARFEDALE Unit 3. List Price £32.31. OUR PRICE £55. P. & P. £1.75.**

#### TURNTABLES P.P. 60p

Garrard SP25 Mk. III	£10-97
Garrard 2025TC with Sonotone 9TAHC Cartridge	£8-75
Garrard A70 Mk. II	£10-97
Garrard SL65B	£12-75
Garrard AP76	£18-75
Garrard SL72B	£25
Garrard SL75B	£27-75
Garrard 401	£27-50
Garrard SL95B	£34
Goldring GL75P	£35
Goldring GL75	£28-50

#### TURNTABLES (continued)

Goldring GL69	£21
Thorens TD125	£32
Thorens TD150AB/2	£38
Pioneer PL11AC complete	£39
Dual 1219	£49
Dual 1209	£34
Philips 202A	£54-00

#### CARTRIDGES P.P. 12p.

Goldring G850	£4-20
Goldring G800H	£5
Goldring G800	£7
Goldring G800/E	£11
Goldring G800/SE	£16
Sonotone 9TAHCD	£1-75
Shure M3D	£4-95
Shure M44E	£8-50
Shure M75E	£15
Shure M55E	£9-20
Shure M445/7	£7-20
SMC101	£3-25
MC15	£5
AT66 5/7 LC/HC	£4-70
ADC 10E Mk. 2	£27

#### TAPES

PHILIPS, BASF, SCOTCH, ETC. BIG DISCOUNTS. SEND FOR LIST.

Open 9.30 a.m. to 7 p.m. Monday to Wednesday; half day Thursday until 1 p.m.; late night Friday until 8 p.m.; Saturday 9.30 a.m. to 6 p.m.

2 Showrooms devoted to specially selected systems.

EASY TO FIND—50 YARDS FROM (B.R.) STOKE NEWINGTON STN. 67, 149, 247, 73, 76, 243 Buses Pass our door.

# AUDIO SUPPLIES

PE8, 50 STAMFORD HILL, LONDON, N.16.

Telephone: 01-806 3611

PERSONAL CALLERS PLEASE NOTE—Cheques are only accepted when accompanied by a Bank Cheque Card (not Barclay Card).

Your STARTER QUESTION is

"What is today's most useful electronics catalogue?"



... and your BONUS QUESTION is

"What goes up and at the same time comes down?"

The answer to the Starter question is obvious—the ubiquitous HOME RADIO COMPONENTS CATALOGUE. You all got that right! And the answer to the Bonus question is—the same! May we explain "this most ingenious paradox?" The price is now 50p, but with each catalogue we now include 10 vouchers each worth 5p when used as directed. This means that if you spend a quite modest sum in ordering components from us over a period the catalogue will have cost you *nothing*—bar 20p for post and packing. So then—for today's most useful electronics catalogue, 50p if you call and collect, or 70p if you send the coupon with a cheque or Postal Order. Join the winning team—act now!



24-hour Phone Service. Ring 01-648 8422

**POST THIS COUPON with your cheque or postal order for 70p**



Please write Name and Address in block capitals

Name  
Address




**HOME RADIO (Components) LTD.**

Dept. PE, 234-240 London Road, Mitcham CR4 3HD

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

## PART TWO

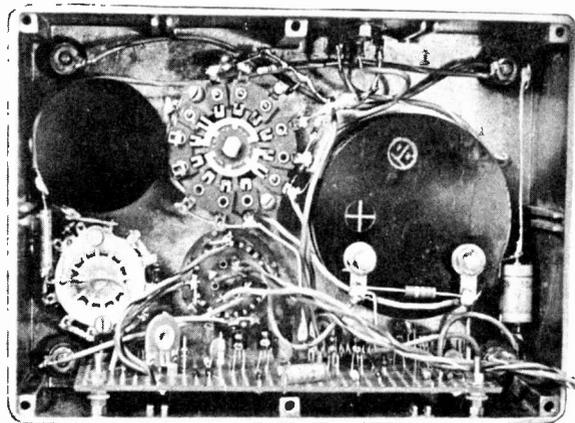

# VOLTAGE

By  
A. J. Ewins

# STABILISER

**T**HIS month we finish the circuit description and give construction and application details of the Voltage Stabiliser.

### RESISTOR MATCHING

Several ways of matching the padded 11 kilohm resistors with the 10 kilohm variable control will no doubt suggest themselves to the constructor. Here are two possible ways. A simple Wheatstone bridge with two, equal in value, 1 per cent resistors for the ratio arms may be rigged up. The 10 kilohm wire-wound control is used as the "known" resistor and the 11 kilohm fixed resistors are connected, in turn, as the "unknown" resistor. The 11 kilohm resistors are then shunted as required until a balance (zero current) is obtained on the meter. See Fig. 3.

Alternatively, when the control unit has been constructed and is working, the 10 kilohm wire-wound control only can be inserted with its full resistance in circuit. The output of the unit is then set to read 2.5 volts by adjustment of the preset control, VR1. (An Avometer or other reliable voltmeter should be used for measuring the output voltage from the unit.)

The 11 kilohm resistors can then be inserted in the circuit, in turn and in place of the 10 kilohm wire-wound control, and shunted until the same

2.5 volts output is obtained. Using the small  $\frac{1}{4}$  watt resistors allows a neat arrangement of the 10 kilohm resistors around the 12 way switch (just visible in the bottom left-hand corner of the photograph of the internal view of the unit). To those constructors who are hesitant about this method of obtaining accurate 10 kilohm resistors, a word of reassurance; the author did not have to use more than two padding resistors per 11 kilohm resistor and in the majority of cases used only one.

### CURRENT RANGES

For full current limiting the voltage developed across the selected value of TR9's emitter resistor is nominally one volt giving a value for  $R_e$  of  $1/I_1$ , depending on the value of  $I_1$  required. For current limiting ranges of 10, 25, 50, 100 and 250mA the required values of resistance are 100, 40, 20, 10 and 4 ohms respectively. If the precise value of the limiting current is not important the 40 and 4 ohm resistors can be replaced by the standard values of 39 and 3.9 ohms. One section of a 4 pole, 5 way rotary switch (S3c; only three poles are needed) was used to switch in the five values of resistance. The other two sections were used to switch in a shunt resistor (R33) across the milliammeter to give an additional range of 0 to 250mA for the three upper current limiting ranges.

The section S3b may appear to be redundant, but omitting it means that heavy currents will flow through the contacts of section S3a. As the contacts of S3a are in series with the shunt resistor, erroneous and erratic readings can be expected on the meter due to the relatively large value of resistance of the contacts compared with the shunt. (This, indeed, was the author's experience). Including the section S3b puts the contacts of S3a effectively in series with the meter, which has a resistance of 9 times the shunt and draws one ninth of the current flowing through the shunt, thus greatly reducing the effect of the contact resistance.

For the 4 pole, 5 way switch, the author was lucky enough to possess a Yaxley type wafer with two 1 pole, 5 way sections on either side. The constructor's best bet, if somewhat of an expensive solution,


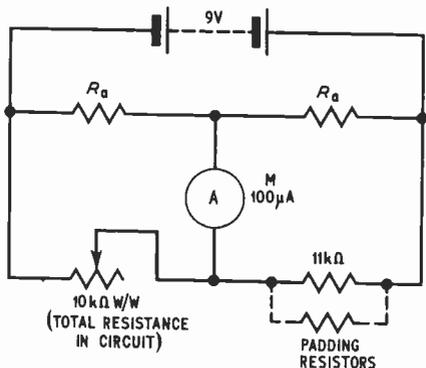


Fig. 3. Wheatstone bridge for resistor matching

Fig. 4. Veroboard layout and wiring

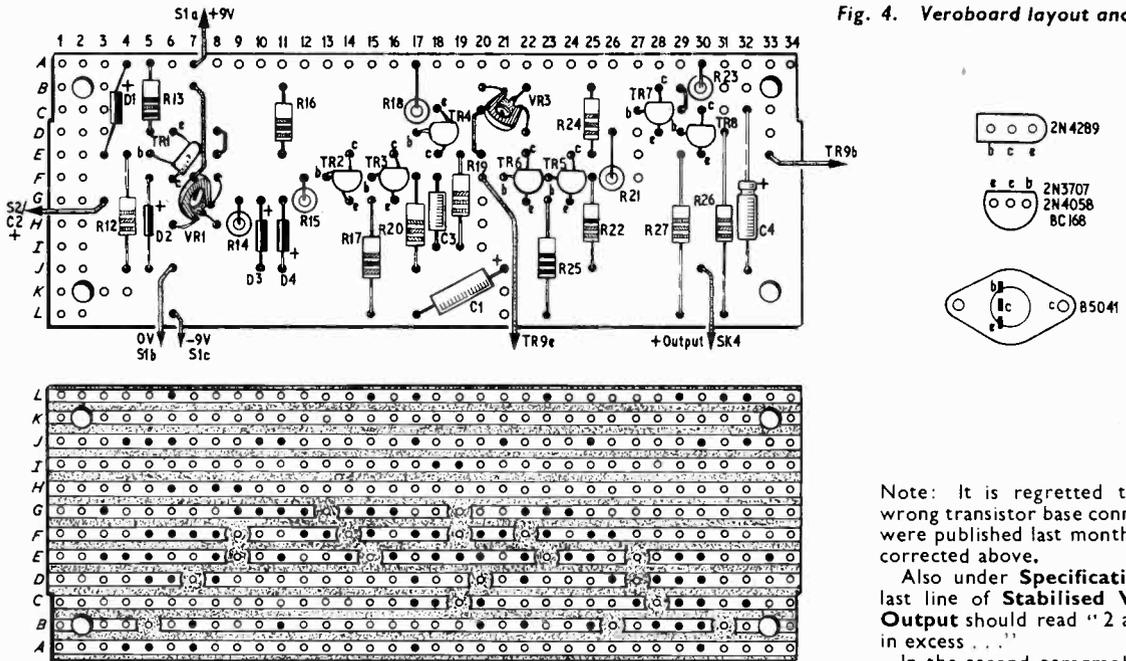

Note: It is regretted that the wrong transistor base connections were published last month; this is corrected above.

Also under **Specification**, the last line of **Stabilised Voltage Output** should read "2 and 35V in excess . . ."

In the second paragraph of the introduction 85 volts should read "65 volts"


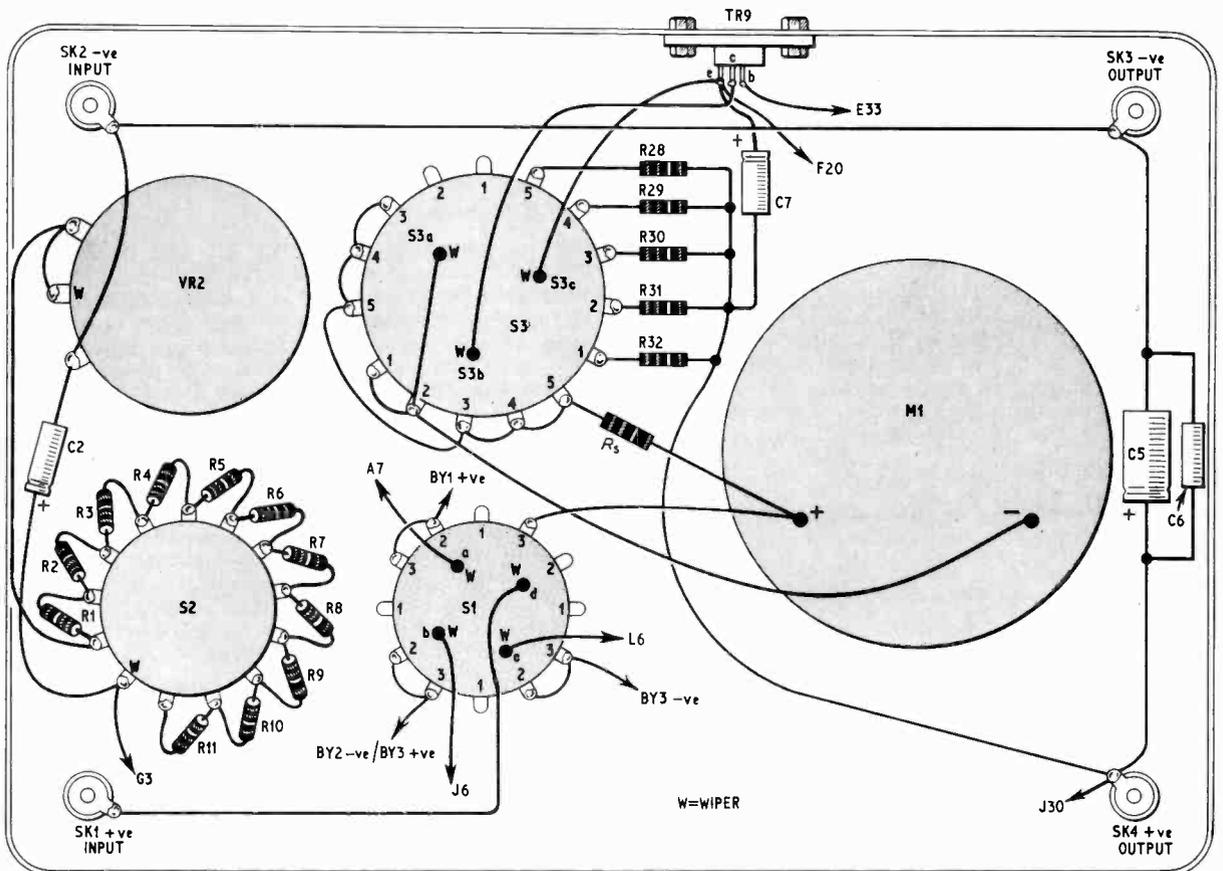


Fig. 5. Internal wiring of the stabiliser

Fig. 6. Front panel drilling details

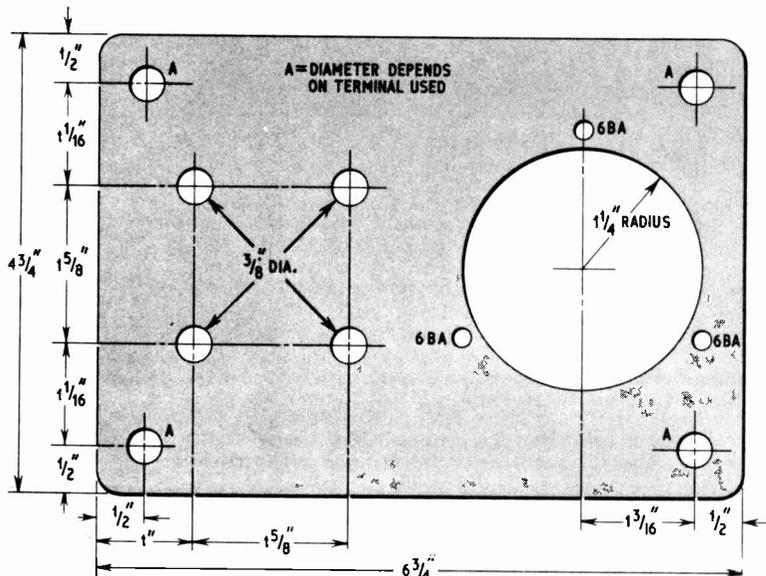

is to construct a "Makaswitch" assembly using two 2 pole, 5 way wafers mounted close together, without using spacers, in order to conserve space.

As stated, the value of  $R_s$  (the meter shunt resistor) will be one ninth of the meter resistance. Where the meter resistance is known the value of  $R_s$  may be easily made up using a coil of 22 s.w.g. Eureka resistance wire. If the meter resistance is not known the best way to determine it is to measure the voltage dropped across the meter, when it is indicating full scale deflection, by means of a suitable voltmeter. (The sensitivity of the voltmeter, in terms of ohms/volt is unimportant). For most meters, other than the popular Japanese types, the voltage dropped will be about 100mV giving a meter resistance of about 4 ohms. A shunt is then required of about 0.44 ohms. This can be made from about 14.5 inches of 22 s.w.g. Eureka resistance wire (2.75ft/ohm for 22 s.w.g. Eureka resistance wire).

### MAIN CONSTRUCTION

Using the type of controls and meter described, the author was able to fit all the components of the unit, including batteries, into a die-cast box of size,  $6\frac{1}{2}$ in  $\times$   $4\frac{1}{2}$ in  $\times$   $2\frac{1}{2}$ in. The two diagrams, Figs. 4 and 5, show Veroboard layout and internal wiring of the completed unit.

It is possible to mount all the electronics of the unit, except of course the controls, on a piece of Veroboard measuring  $5\frac{1}{2}$ in by 2in.

Details of the positioning and size of the holes drilled in the front panel are shown in Fig. 6. The mounting position of the Veroboard layout can be clearly seen in the photograph of the internal view. The series regulator transistor, TR9, can be mounted in any convenient position. In the photograph it can be seen at the top of the unit near M1. The particular transistor specified for TR9 is the B5041, which is on a X53a base.

The mounting of the batteries on the back panel of the box is left to the ingenuity of the constructor. In the prototype a special bracket was manufactured from 16 s.w.g. aluminium.

### USING THE STABILISER

The stabiliser is shown in Fig. 7 being used to provide a stable output voltage. When operating in this manner the difference between the input and output voltages of the unit must not be allowed to exceed 55 volts, which is the maximum  $V_{ce}$  rating of the series regulator transistor. The current meter

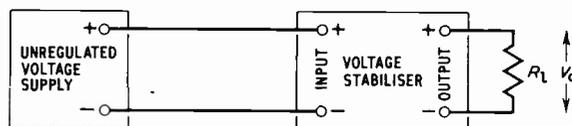


Fig. 7. The voltage stabiliser being used to provide a stable output voltage

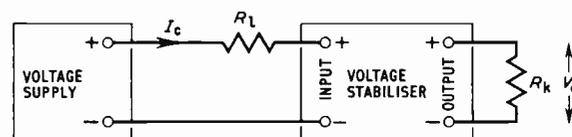


Fig. 8. The stabiliser being used to provide a constant current

is connected in the collector line of the series regulator transistor and hence gives an indication of the current being drawn from the external supply. The current flowing through the load applied to the output terminals will be equal to the meter reading less the sensing current,  $I_s$ , which is  $250\mu\text{A}$ .

The unit being used to provide a constant current is shown in Fig. 8. As the output voltage of the unit is completely insensitive to changes in voltage from the external supply (providing that the external supply volts do not drop below about 2 volts in excess of the output voltage setting), the current drawn from the supply is independent of its voltage.

The precise value of the current drawn from the external supply is equal to the output voltage setting of the unit divided by the value of the load resistor, plus the sensing current which equals  $250\mu\text{A}$ . A range of constant currents from  $250\mu\text{A}$  to  $250\text{mA}$  is thus possible. The current drawn from the external supply will fall below its constant value when the voltage dropped across the external resistor is equal to or greater than the difference between the external supply volts and the voltage output setting of the unit, less about 2 volts. As for the stabilised voltage mode of operation, the difference between the input and output voltages of the unit must never exceed 55 volts.

# NEWS BRIEFS

## Tape Competition

YOUNG tape recordists are invited to enter the Animal Sounds recording competition for under-18's organised by the 3M Company, manufacturer of Scotch magnetic tape. Entry is free, and there are two classes: British birds in song; and Animals (including domestic pets).

For the three best recordings in the birds section a 472-page guide to the identification of all the birds commonly seen in Britain is the prize.

For the three best recordings in the animal section a 428-page Living World of Animals will be awarded.

The recording judged best overall will merit a £30 portable cassette recorder, complete with microphone, carrying case and supply of Scotch low-noise cassettes, and there are certificates for the winning entrants' schools.

Entry forms are being distributed to some 20,000 schools, or can be obtained direct from Magnetic Products Marketing, 3M Company Ltd., 3M House, Wigmore Street, London, W1A 1ET.

Last date for receipt of entries is October 31, 1971.

## PO Copying Service

MEMBERS of the public needing a quick copy of important documents can now use coin-operated (5p) photocopying machines in 20 head and branch post offices. The Post Office has installed the machines for an extended trial following an initial trial at five offices during the past 18 months.

The machines chosen are simple to operate and make copies in A4 size (8½in × 11½in).

The 20 offices involved are the head offices at Harrow, Belfast, Coleraine, Chester, Plymouth, Swindon, Dundee, Portsmouth, Hastings, Bury St Edmunds, Worcester, Blackpool, Sunderland (probable), Leeds, Coventry, Bolton and Cambridge, and branch offices at Great Portland Street, London, Swansea (Kingsway) and Edinburgh (Frederick Street).

If the extended trial is successful, the Post Office plans to install photocopiers on a much wider scale.

## Heated Diagnosis

DOCTORS at Cape Town's Groote Schuur hospital are to use infra-red techniques in diagnosing breast cancer, thrombosis and other ailments following the purchase of a "Thermoscan" thermal imaging system from EMI.

With this electronic equipment, the first British system of its type, the famous South African hospital will be able to assess or investigate quickly disorders which disturb the body's normal heat distribution, by obtaining a heat "picture" of a suspected area of infection.

The thermal imaging equipment comprises a mobile infra-red scanner unit (similar in appearance to a small television studio camera) and a monitor, incorporating a cathode ray tube. The system operates by scanning the distribution of heat over the area of the body being studied and is sensitive enough to detect differences in temperatures as small as 0.2 degrees Centigrade.

The scanner can be operated remotely, with the monitor located up to 30 metres away from it. This facility enables a patient to be separated completely from the clinician, allowing free discussion of the observed symptoms.

The Thermoscan systems are currently being evaluated by Britain's Department of Health and Social Security at selected hospitals where they are aiding diagnosis of a wide variety of conditions which are difficult or impracticable to study by other means.

## Socket Guide

IN RECENT years a good deal of confusion has arisen over the use of connectors for public address equipment. The German DIN connectors are suitable for permanent installations, but where equipment is portable or is available for hire, a more robust connector is needed.

To resolve these problems, the Association of Public Address Engineers has published a technical information sheet which recommends that XLR connectors are used for all professional public address applications. The Information Sheet gives details of the correct use of XLR connectors for microphones, loudspeakers and auxiliary circuits.

The Information Sheet, reference T.I.S.2 is available free to members of the A.P.A.E. or price 5p to non-members on application to the Secretary, 394 Northolt Road, South Harrow, Middlesex HA2 8EY.

## Luxury Viewing

WITHOUT even raising their heads from the pillows, guests at the new Capital Hotel in Knightsbridge can select from nine channels of sound and vision from Top Rank designed remote control panels fitted in the bed headboard.

The h.f. distributor system which makes this remote control possible carries television signals in monochrome and colour. The television sets are bracketed so they can be viewed either from the bed or from the easy chairs.

## Green Diodes

THE Electronic & Display Equipment Division of Ferranti Ltd. has successfully developed the world's first gallium phosphide monolithic green light emitting array. Perfected at the Gem Mill, Chadderton laboratories of the Division, the array is based on a unique masking and diffusion process for use on gallium phosphide to produce high output, low consumption light emitting diodes.

The gallium phosphide is enveloped by a dielectric layer, so protecting it and ensuring that it attains an exceptionally long life to an extent previously obtained only from hermetically-sealed devices.

## Vacation School on Circuit Theory

THE Moscow Institute of Medical Instrument-making has designed an ultrasonic apparatus for the diagnosis of cerebral diseases. It is claimed that scientists regard it as quite promising for neurosurgery and neuropathology.

The instrument makes it possible to examine the patient quickly and painlessly. By touching alternatively various parts of the cranium with a sensor, the physician completely "sounds" the cranium.

Clinical tests have shown its high accuracy in diagnostics. Experts note that the new way is also most reliable in control of the results of intra-cranial operative intervention. Examinations are harmless and can be repeated many times.

The apparatus is now in batch production.



## MARINER INQUEST

The cost of the loss of *Mariner 8* cannot easily be calculated in totality. The spacecraft and its launch vehicle was a £50 million project but the loss of data cannot be measured in terms of money.

Sadly, the cause of the disaster was a part costing a few cents and microscopic in size. It was part of the autopilot system of the vehicle, and the part of the integrated circuit which failed was a diode about the diameter of a human hair.

The investigating team simulated the telemetry which was returned by the *Centaur* vehicle to mission control up to the time of failure. It was possible from this data to determine that the engine, which should have had a swivel range of 3 degrees to enable it to be accurately steered, could only cover a range of 1.3 degrees.

The amplifier which was a part of the system had an output which was between 20 and 30 per cent of what it should have been. This was due to a voltage overload that the diode should have controlled.

Many other tests were carried out to simulate possible faults but only this one produced the conditions radioed back at the time of the failure.

Though there is no way to tell now why the diode malfunctioned, the investigating team have devised tests to make sure that the same thing will not happen with *Mariner 9*. Certain other modifications were made which will help to minimise the loss of the *Mariner 8* experiments. Some of these were added to *Mariner 9* before it was launched.

The launch could have been delayed until the middle of June, but any later launch date would have compromised the mission, as a favourable period would not arise again for 25 months. This means that the next launch would have to

be delayed until 1973 when the Earth and Mars are in correct alignment. However, the amount of power required then would be greater than the capacity of the present *Centaur* vehicle.

The arrival time of *Mariner 9* at its destination will not now be November 14 but more likely November 24.

## SOVIET THOUGHTS ON PULSARS

A Russian Academician, Vitaly Ginzburg, has advanced a new hypothesis on the subject of Pulsars. It is generally accepted that the Pulsars are in fact Neutron Stars and are known to be stars which are in a certain stage of cooling.

Ginzburg is suggesting that his mathematical model fits the known facts about these bodies. He believes they are in a state of compression so great that they are reduced to a thousandth of their original size.

Their speed of rotation, he says, can be measured to a small fraction of a second and that the density of the material is of the order of a thousand million tons for a cubic centimetre, if measured on the earth. The radiation pulses from these bodies, which have been observed by radio astronomers, are the result of the fact that their magnetic and rotational axis do not coincide.

It is also suggested that the temperature of these pulsars is of the order of hundreds of millions of degrees, and that under a plasmic liquid or gaseous outer layer there is a hard crust about one kilometre thick. Inside there would be a superfluid and superconductive mixtures of liquids consisting of elementary particles. The matter is being investigated at the Pulkovo Observatory near Leningrad.

## LUNOKHOD I

The *Lunokhod 1* moon vehicle continues to pursue its programme of exploration of the Moon's surface. It is in its ninth lunar day of operation since it was landed on November 17, 1970. A film of its work compiled from the television pictures sent back to earth has been showing in Russian cinemas to enthusiastic audiences.

The vehicle has successfully overcome many difficulties. For example, it encountered a crater which was full of fair sized boulders and was able to negotiate the rugged terrain. It did have one serious difficulty where the side of a crater proved to have a very loose surface and the telemetry showed a slip of up to 90 per cent of the wheels. Such was the skill of the earth based controllers that the vehicle was got safely out of the crater.

Studies of the chemical composi-

tion of the surface have been made and continuous mapping is being carried out.

## MORE SPIN-OFF BENEFITS

There are a number of medical benefits available from space activities, sometimes relating directly to space medicine, and sometimes to other techniques, which have been turned to medical use on earth.

A special version of the space helmet has been used to measure the oxygen consumption of children while they were undergoing special hard exercise in hospitals. The multilayered principles of the space suit has been adapted and used as a pulsating device to assist in respiration for severely paralysed patients. It may well be possible that this system can be used to replace the iron lung. The advantages of giving possible mobility to such unfortunate sufferers may well open a new avenue of hope for them.

## BODY MONITOR

A personal health monitoring device has been adapted from the space techniques. This is in the form of a battery operated device about the size of a cigarette box which can be strapped to the patient and will then transmit the temperature, blood pressure, respiration, pulse and other vital physiological information.

Seated at a console a nurse will be able to monitor up to 60 or so patients in an intensive care unit with consequent increase in moment to moment observation and a great increase of efficiency in dealing with emergencies.

Another system which was used to improve the detail of pictures returned to Earth from Mars has been applied to X-ray pictures and has resulted in great improvement in these by enhancing detail.

An early study of lunar mobility involved the development of a six-legged walking device for astronauts. This has now been applied to handicapped patients enabling them to negotiate stairs, curbs and avoid obstacles where the ordinary wheelchair could not cope.

## LUNAR EXCHANGE

Samples of lunar rock brought back to earth by *Luna-16* and *Apollo-11* and *12* were exchanged by Soviet and American scientists on June 10.

The exchange took place under an agreement between the U.S.S.R. Academy of Sciences and the United States National Aeronautics and Space Administration. The scientists expressed the hope that the exchange of lunar material would enable them to make, in the laboratories of their respective countries, a comparative analysis of rock samples brought from different areas of the lunar surface.



## PART 5 PROGRAMMING

By M.J. HUGHES M.A.

### CONCLUDING ARTICLE

THE "P.E. Aurora" system has the great advantage that light control is effected by low voltage levels from fairly high impedance sources. This fact enables a wide range of sources for control. This part explores some possibilities which have been tried successfully by the author, and which might provide some hints for further experimentation.

No doubt apart from domestic use the next most likely application for "P.E. Aurora" is in the field of discotheques and clubs. As already shown, sound control of lights can be achieved successfully, but sometimes fast strobing effects may be required. Xenon flash tubes are normally used for this, but they cannot be left running for long periods of time. They do not have a very great power for long range illumination.

### STROBE EFFECT

While a "freeze" strobe cannot be produced from "P.E. Aurora", a very good simulated strobe can be obtained with the advantage that up to eight channels can be independently operated simultaneously with different colours and at different speeds. The basis for this effect is a simple free running multivibrator. The circuit of one is shown in Fig. 1. It is suggested that instead of having eight circuits (for a full system) only four are needed; complementary outputs of the unit being applied to adjacent channels.

Some spectacular effects can thus be obtained if complementary colours are alternately strobed against each other, for example, red with green, or blue with yellow. It is best for the mark/space ratio of the strobe to be approximately 1 to 1, therefore if variable speed is required a ganged potentiometer (VR1 and VR2) should be used so that both sides of the multivibrator are identically controlled.

Note that in this circuit *pnp* transistors are used. The common emitter rail (positive) should be commoned to the +15V rail of the "P.E. Aurora" controller—the 0V rail should *not* be commoned with the 0V rail of the controller if an external power supply is used. If the internal supply of this controller is to be used, apply decoupling in the 0V line as explained in part 3.

### SEQUENTIAL STROBE

Some of the lighting arrangements described last month can be shown to best advantage if the lights appear to move. This can be done by switching lights on and off in a given sequence. For example a set of four lamps A, B, C, and D can be made to look as if they are moving by first of all lighting lamp A, it is then extinguished and B lit; B is extinguished and C lit and so on. As D is extinguished, A lights for the second time.

A sense of movement can be obtained with three lamps but the effect is better with four, especially if the effect is to be repeated down a long string of lamps paralleled together in four groups.

This effect can be produced very simply by using four of the control channels (if more power is required the remaining four channel controls can be paralleled in by strapping the input signals across pairs of channels). Fig. 2 shows one way to produce a sequential step from one lamp channel to the next. It utilises some simple logic controlled by a clock which is used to set the speed of switching.

Integrated circuits are used and the prototype system was designed around DTL. There is no reason why other logic systems should not be used, but TTL could be difficult to use because of the need for short inter-connections.



### POSITIVE LOGIC

Assuming positive logic throughout; the most positive voltage (+15V level of the controller) is "1", therefore a logic "0" (provided the difference in level between it and a "1" is greater than 1V) applied to a control input will turn that lamp on.



Provided we do not excessively load the outputs of gates or flip flops, when they have an output of level "1", the actual output voltage is very close to  $+V_{cc}$ . Thus if the logic system has its  $+V_{cc}$  rail commoned to the +15V rail of the controller, a logic "1" will turn a lamp off and a 0 will do the converse.

Referring back to Fig. 2, the free running multivibrator can be adjusted by VR1 to oscillate from

**Fig. 1.** A simple multivibrator as this can produce some interesting strobe effects especially if the two collector outputs are fed to adjacent channels, thus, for example, strobing red and green in complementary mode. Note that pnp transistors are used; this ensures that an active "pull up" to +15V will ensure that lamps can be totally extinguished

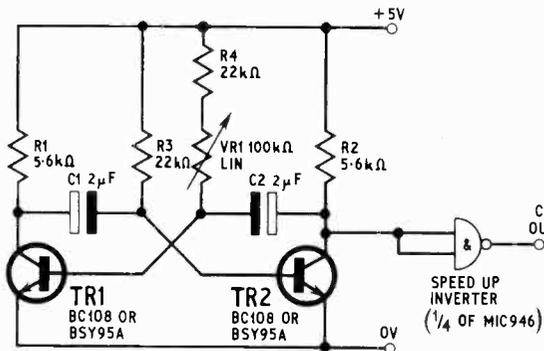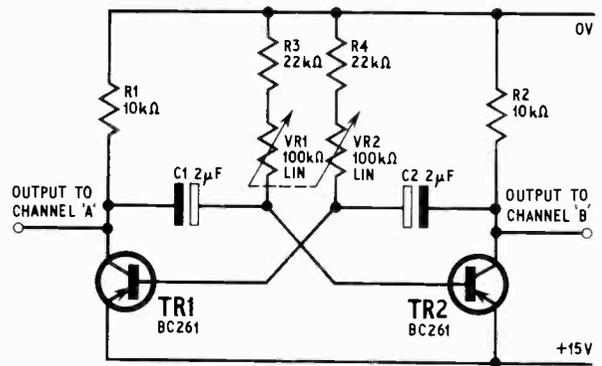

**Fig. 2.** A simple scale of four counter with output gating which produces sequential "O" level pulses on four separate output lines. These can be fed to four separate channels thus producing a sequential strobe. The elements shown are a discrete component clock followed by DTL elements. Note that the +5V above is the positive rail supplying the integrated circuits and is used as the common line when connecting the output gates to the controller. It should be connected to the +15V rail of "P.E. Aurora" system

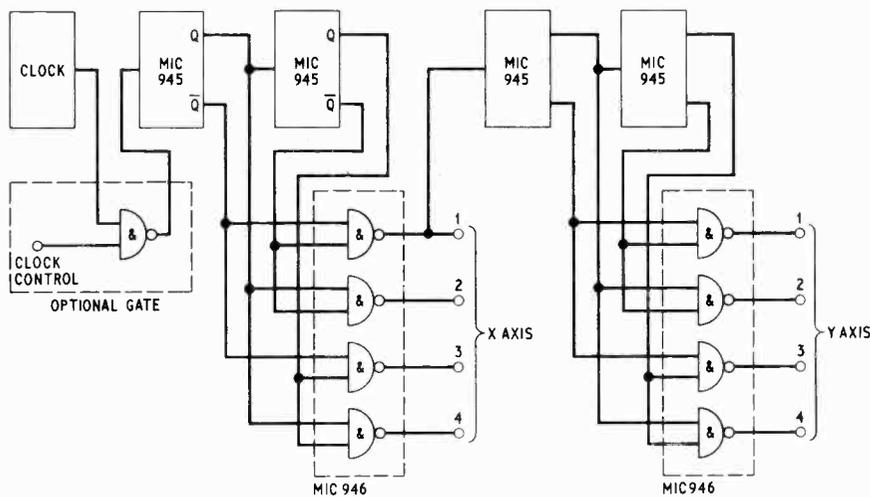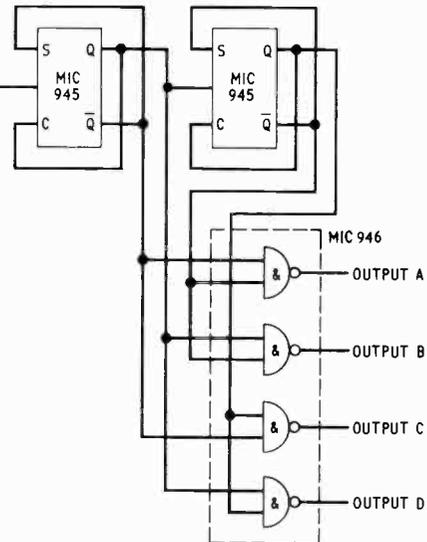

**Fig. 3.** Using the output from one of the gates of Fig. 2 to drive an identical system, we can sequentially switch on every lamp in turn in a 4 × 4 lamp matrix

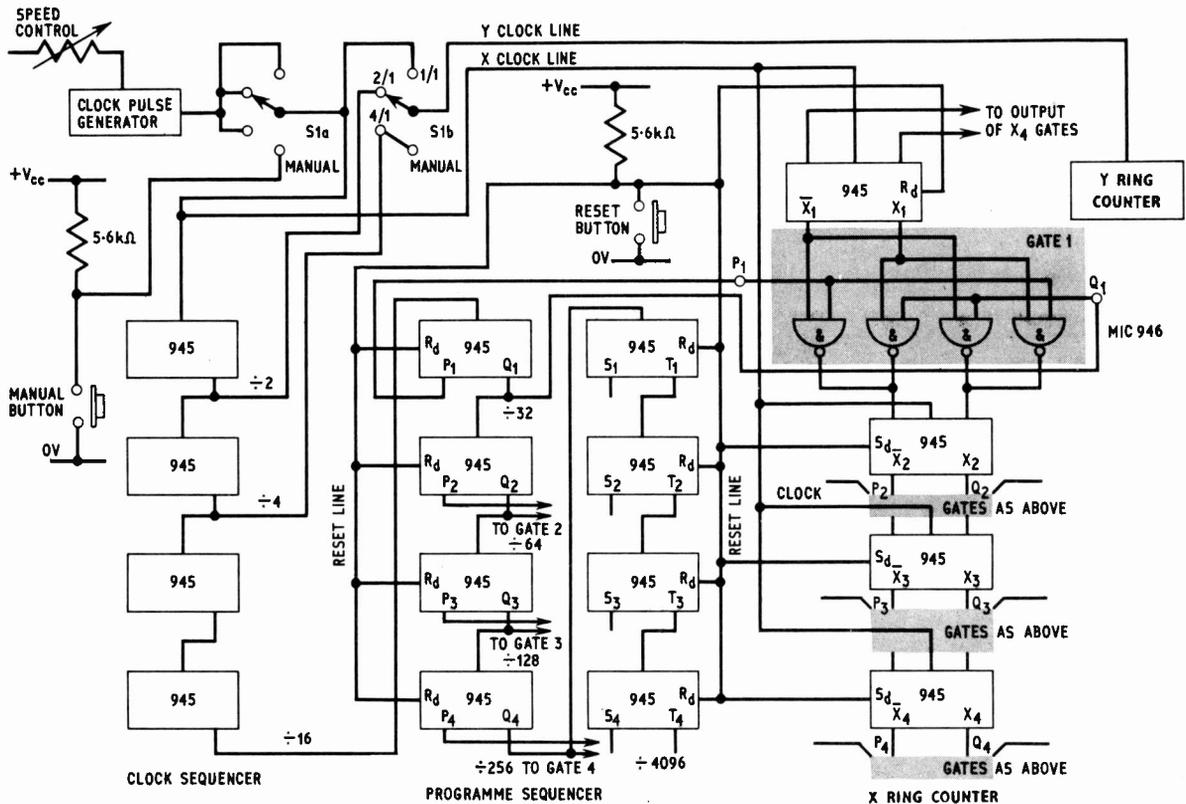


Fig. 4. This shows a much more ambitious system of sequentially switching the lamps. Designed to make full advantage of the matrix display, this unit comprises two multiple twist ring counters whose twists are controlled by a programme sequencer. Discrete DTL units were used in the prototype. It is possible to use MSI circuits to simplify some of the system and smaller systems based on this could be devised. The block labelled Y ring counter is identical to the X ring counter and uses type 945 flip-flops and 946 gates. They are fed in the same way from the S and T series of flip-flops in the programme sequencer

between several pulses per second to approximately one pulse per two seconds. The output waveform of this is speeded up by using a single NAND gate as an inverter. This is then fed to a pair of cascaded binaries which are straightforward clocked RS flip-flops with the outputs cross-coupled back to the inputs. If a JK flip-flop is used no cross coupling is required.

The four discrete output conditions of the two binaries are decoded by the four gates. The decoding sequence is such that there is an output of "0" from only one gate at any instant and this "0" steps from one gate to the next in the sequence A, B, C, D, back to A and so on. These outputs should be connected to respective inputs of the controller. Again note that the 0V rail of the logic system should *not* be commoned to the 0V line of the controller.

### SEQUENTIAL MATRIX SWITCHING

Use can be made of logic to select and switch any given lamp node or nodes within the Aurora matrix (see Part 1). One could envisage, for example, a lamp being lit at the top left-hand corner of a matrix and moving along a horizontal row of four, then back to the beginning of the next line down, across it and down to the next and so on (rather like a television beam scan producing a raster).

Some of the lighting arrangements shown last month are designed around 16 controlled nodes in

a matrix. If the 16 nodes were spacially set in a circle one could use logic to select any one of the 16 lamps in turn and turn it on. With a little more thought one could make this step from one to the next all the way round the circle (this in itself could make an interesting attraction at fetes).

Fig. 3 shows a fairly simple way in which this fixed programme can be obtained. It uses two circuits identical to that shown in Fig. 2. Each time one circuit completes a cycle it steps the other circuit on one position, hence 16 separate lamps can be individually switched on in sequence at any speed selected by the clock. A gate could be inserted between the clock and the first binary so that the clock can be started and stopped after a random period of time by some other circuitry.

### RING COUNTER

The system just described produces an interesting sequence, but cannot accommodate any variation from the simple step-by-step sequence. A much more ambitious system which includes a variable programme is shown in Fig. 4. The circuit as shown uses electronic programme change, but if the constructor so desired he could simplify the system, and cut down on the number of integrated circuits used by using toggle switches to select any particular programme manually.

In this case the X and Y axes are controlled by the outputs of stages in two separate ring counters.

MAIL ORDER DIVISION

**distronic LTD**

**THE POWER HOUSE**

28 BURNT MILL  
ELIZABETH WAY  
HARLOW ESSEX  
HARLOW 32947

Why wait weeks? — ALL OUR ORDERS  
DISPATCHED BY RETURN OF POST!  
Transistors, Diodes and Integrated Circuits

**A) DIODES & RECTIFIERS**

IN4001	7p	AC187K	Matched
IN4002	8p	AC188K	pr. 50p
IN4003	9p	AC191	15p
IN4004	10p	AC192	15p
IN4005	12p	AC193	20p
IN4006	14p	AC194K	pr. 60p
IN4007	20p	AD143	50p
		AD262	Matched
		BD162	pr. 90p
		AD262	35p
		AD263	40p
		AF106	25p
		AF109	35p
		AF139	31p
		AF166	20p
		AF170	18p
		AF172	18p
		AF200	25p
		AF201	30p
		AF239	40p
		AF239S	45p
		AL102	60p
		AL103	50p
		AU103	£1

Compare our prices

W005	40p
W01	45p
W04	48p
W06	50p

**B) TRANSISTORS**

2N696	15p
2N930	25p
2N930A	30p
2N1613	22p
2N1711	25p
2N2369	20p
2N2484	34p
2N2605	45p
2N2904	36p
2N2904A	41p
2N2905	46p
2N2905A	60p
2N3053	22p
2N3055	70p
2N3442	£2
2N3638	25p
2N3866	£1.50
2N4347	£1.50
2N4356	35p
40411	£2.50
AC138	15p
AC141	20p
AC141H	25p
AC142	15p

**Component Discounts**  
10% on orders over £5

AU106	95p	BCY70	26p
AU107	70p	BCY71	26p
AU108	65p	BCY72	26p
AU110	£1	BF152	25p
AU111	70p	BF153	25p
AUY21A	60p	BF158	35p
AUY22A	70p	BF159	35p
AUY35	45p	BF160	28p
AUY37	60p	BF177	25p
BC107	11p	BF178	35p
BC108	11p	BF179C	40p

BC109	11p	BFX86	30p
BC113	20p	BFX87	30p
BC114	20p	BFX88	25p
BC115	25p	BFY34	30p
BC116A	30p		
BC117	30p		
BC125	20p		
BC126	30p		
BC132	20p		
BC134	20p		
BC137	30p		
BC142	35p		
BC143	40p		
BC144	40p		
BC145	30p		
BC147	15p		
BC148	11p		

Please note minimum order 50p

Send 10p for price list or free with order

BFY50	22p
BFY51	20p
BFY52	20p
ME0404-1	12p
ME0404-2	13p
ME1001	10p
ME1002	11p
ME2001	10p
ME2002	11p
ME3001	20p
ME3002	25p
ME4001	10p
ME4002	11p
ME6001	15p
ME6002	18p
ME8001	20p
ME8002	30p
ME8003	30p
ME9001	15p
ME9002	15p
MEL11	40p
MEL12	50p
MEU21	40p
MEU22	50p
OC25	37p

**C) INTEGRATED CIRCUITS**

709C (TO-99)	95p
709C (DIP)	95p
741C (TO-99)	£1.25
741C (DIP)	£1.25

2N3055	70p
115 Watt 15 Amp	
2N3053	22p
1 Amp TO-5	
BC107	11p
Also BC108 and BC109	
AF239	40p
UHF: 5 DB at 800 MHz	
W01	45p
1 Amp, 100 V Bridge Rectifier	
AD262 } PNP Matched	
BD162 } NPN pair	90p
10 Watts, AUDIO OUTPUT PAIR	
ADI42	50p
80 Volts, 10 Amp TO-3	
AU103	£1
155 Volts, 10 Amp TO-3	
AU106	95p
320 Volts, 10 Amps	
BC147/8/9	15p
High gain LOCKFIT	
ME1001	10p
45 Volt high gain	
40411	£2.50
30 Amp, 150 Volts	
IN4001	7p
1 Amp, 100 Volts	
BF179C	40p
250 Volts TO-5	
BFY51/2	20p
2N3866	£1.50
1 Watt output at 400MHz	
BC114	20p
High gain: 200 at 1mA	
741C	£1.25
DIP or TO-99	
High gain operational amp.	
S/C proof	

POSTAGE & PACKING PLEASE ADD 10p TO YOUR ORDER

**SEND FOR BONUS VOUCHER FREE WITH EVERY £1 ORDER**

\*Redeemable upon receipt of subsequent order value £5 or more, received before Dec. 31, 1971

**BONUS VOUCHER**

Send this voucher with your next order to receive a 10% discount on your next order. This voucher is valid for 12 months from the date of issue.

**distronic LTD**

28 BURNT MILL, ELIZABETH WAY, HARLOW, ESSEX



# VARIABLE VOLTAGE TRANSFORMERS

## 230v AC SOLENOID

Extremely powerful with approx. 14lb. pull, 1" travel. Fitted with mounting feet. Size: 4" long, 2 1/2" wide, 3" high. £2.00 incl. P. & P.



## 230-250V SOLENOID

Mfg. by Westool, approx. 1 1/2 lb pull (similar in appearance to above illustration). Size of feet 1 1/2" x 1 1/2". Price 85p incl. Post.

## VENNER Electric Time Switch

200/250V Ex. G.P.O. Tested. Manually set. 2 on, 2 off every 24h. Override switch. 10A £2.75, 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk, OFF dawn. Price as above.



## BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 7 1/2 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p. 50 cycle, 0-38 amp. (Type 2) 28 r.p.m. Torque 20lb. inch. Reversible. 1/80th h.p. 50 cycle, 0-28 amp.

"As new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3.15 plus 35p P. & P. or less transformer £2.13 plus 27p P. & P.

## 12 VOLT DC MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 RPM complete with external gear train (removable) giving final speed of 125 RPM. Size: 4 1/2" x 2 1/2" dia. Price 95p incl. post.



## 230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gearbox.

1 rev. per hour. Clockwise rotation.  
1 rev. per hour. Anti-clockwise rotation.  
2 revs. per hour. Clockwise rotation.  
3 revs. per hour. Anti-clockwise rotation.  
5 revs. per hour. Anti-clockwise rotation.  
15 revs. per hour. Anti-clockwise rotation.  
60 revs. per hour. Clockwise rotation.  
Fraction of makers' price. All at 75p incl. P. & P.

## 200-250V A.C. NEON INDICATOR

Available in red or amber at 20p each. Or in green at 32p each. Minimum order 3 units. P. & P. 5p.



## ELECTRONIC ORGAN KIT

Easy to build, Solid State. Two full octave (less sharps and flats). Fitted hardwood case. Powered by two penlite 1 1/2 batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3.00. P. & P. 22p.

## 50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 30p.

**CRYSTAL RADIO KIT**  
Complete set of parts, including: Crystal Diode, Ferrite Aerial, Drilled Chassis, and Personal Ear Piece. No soldering, easy to build, full step by step instructions. £1.75 inc. post.

## INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V.

**BRAND NEW All Types (and Spares) from 1/2 to 50 amp from stock.**

**SHROUDED TYPE**  
1 amp, £5.50. 2.5 amp, £6.75. 5 amp, £9.75. 8 amp, £14.50. 10 amp, £18.50. 12 amp, £21.00. 15 amp, £25.00. 20 amp, £37.00. 37.5 amp, £72.00. 50 amp, £92.00. Carr. extra.



**OPEN TYPE (Panel Mounting) 1/2 amp, £3.93. 1 amp, £5.50. 2 1/2 amp, £6.63. Carr. 40p on open types.**

## Superior Quality Precision Made NEW POWER RHEOSTATS

100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230 mA; 2.5 kΩ, 140 mA. Diameter 3 1/2 in. Shaft length 3 in, dia. 1/2 in. All at £1.50 each. P. & P. 5p.  
50 WATT. 1/5/10/25/50/100/250/500/1/1.5/2/5/5kΩ. All at £1.12 each. P. & P. 1p.  
25 WATT. 10/25/50/100/250/500/1/1.5/2/5/5kΩ. All at 78p each. P. & P. 15p.



## RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS - COMPETITIVE PRICES

1		2		3		4	
45	6-9	2 HD M	50p	700	12-24	2 c/o	63p*
185	6-12	2 c/o	70p	700	15-35	2 c/o HD	73p*
185	6-12	4 c/o	73p*	700	16-24	6M	63p*
230	9-18	2 c/o HD	63p*	1,250	24-36	4 c/o	63p*
230	9-17	4 c/o	78p*	2,500	36-45	6M	63p*
280	9-12	4 c/o	73p*	2,400	30-48	4 c/o	50p*
600	18-32	4 c/o	78p*	5,800	40-70	4 c/o	63p*
700	16-24	4M 2B	63p*	9,000	40-70	2 c/o	50p*
700	16-24	4 c/o	78p*	15k	85-110	6M	50p*

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price (HD) Heavy Duty. All Post Paid. \*Including Base.

**MAINS RELAY**  
230V a.c. coil 3 c/o. 10 amp a.c. contacts, 50p. plus 8p P. & P.

## STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

**EXPERIMENTERS' ECONOMY KIT**  
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £6.30 plus 25p P. & P.

**NEW INDUSTRIAL KIT**  
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10.50. P. & P. 50p.

**HY-LIGHT STROBE MK III**  
This strobe has been designed and produced for use in large rooms, halls and the photographic field, and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. Price £12.00. P. & P. 50p.

## AND NOW! THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe.

Incorporating:  
● Heavy duty power supply.  
● Variable speed from 1-23 flash per sec.  
● Fantastic Octal based tube with massive electrodes.  
● Reactor control circuit producing an intense white light.

The brilliant light output of the "SUPER" HY-LIGHT gives fabulous effects with colour filters. Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P.

**7-inch POLISHED REFLECTOR**  
Ideally suited for above Strobe kits. Price 53p. P. & P. 13p or post paid with kits.

## MOTOROLA MAC 11/6 PLASTIC TRIAC 400 PIV. 8 AMP

Now available EX STOCK. Supplied with full data and applications sheet. Price £1.05. P. & P. 7p. Suitable DIAC (RCA 40583) 30p each.

# NEW 1971 EDITION RADIO AMATEUR'S HANDBOOK

By A.R.R.L.

£2.60 Postage 20p

**T.V. TECHNICIAN'S BENCH MANUAL**, by G. R. Wilding. £2.50. Postage 10p.

**20 SOLID STATE PROJECTS FOR THE CAR & GARAGE**, by R. M. Marston. £1.20. Postage 5p.

**PICK-UPS & LOUDSPEAKERS**, by John Earl. £3. Postage 10p.

**MAKING TRANSISTOR RADIOS A BEGINNER'S GUIDE**, by R. H. Warring. £1.05. Postage 5p.

**TRANSISTOR CIRCUITS IN ELECTRONICS**, by S. S. Haykin & R. Barrett. £2.50. Postage 10p.

**ABC'S OF FET'S**, by Rufus P. Turner. £1.25. Postage 5p.

**TELEVISION SERVICING HANDBOOK**, by Gordon J. King. £3.80. Postage 10p.

**RADIO VALVE & TRANSISTOR DATA**, by A. M. Ball. 75p. Postage 10p.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone: PADDINGTON 4185 Closed Saturday 1 p.m.


## 4-STATION INTERCOM



Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 60ft. and other accessories. P. & P. 40p.

**MAINS INTERCOM**  
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £13.85. P. & P. 55p extra.

## INTERCOM/BABY ALARM

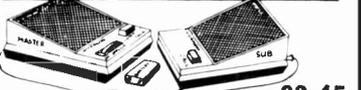

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 60ft. connecting wire. Battery 13p. P. & P. 25p.

## Transistor TELEPHONE AMPLIFIER



Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 13p extra. P. & P. 20p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (FE/8) 169 KENSINGTON HIGH STREET, LONDON, W.8

# SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space  
Dept. P.E. 57 BRIDGMAN ROAD, LONDON W4 5BB  
Phone 01-995 1560 SHOWROOM NOW OPEN MON.-FRI.  
Personal callers only. Open Sat.  
9 LITTLE NEWPORT ST.  
LONDON WC2H 7JJ 01-437 0576

**Table 1: TRUTH TABLE FOR 34 OF THE DIGITAL SEQUENCES**

Sequence	X1	X2	X3	X4	Y1	Y2	Y3	Y4
Reset	0	1	1	1	0	1	1	1
1	1	0	1	1	0	1	1	1
2	1	1	0	1	0	1	1	1
3	1	1	1	0	0	1	1	1
4	0	1	1	1	1	0	1	1
5	1	0	1	1	1	0	1	1
6	1	1	0	1	1	0	1	1
7	1	1	1	0	1	0	1	1
8	0	1	1	1	1	1	0	1
9	1	0	1	1	1	1	0	1
10	1	1	0	1	1	1	0	1
11	1	1	1	0	1	1	0	1
12	0	1	1	1	1	1	1	0
13	1	0	1	1	1	1	1	0
14	1	1	0	1	1	1	1	0
15	1	1	1	0	1	1	1	0
16 X prog. ch.	0	1	1	1	0	1	1	1
17	1	1	1	1	0	1	1	1
18	1	0	1	1	0	1	1	1
19	1	0	0	1	0	1	1	1
20	1	0	0	0	1	0	1	1
21	0	0	0	0	1	0	1	1
22	0	1	0	0	1	0	1	1
23	0	1	1	0	1	0	1	1
24	0	1	1	1	1	1	0	1
25	1	1	1	1	1	1	0	1
26	1	0	1	1	1	1	0	1
27	1	0	0	1	1	1	0	1
28	1	0	0	0	1	1	1	0
29	0	0	0	0	1	1	1	0
30	0	1	0	0	1	1	1	0
31	0	1	1	0	1	1	1	0
32 X prog. ch.	0	1	0	1	0	1	1	1
33	1	0	0	0	0	1	1	1
34	0	1	1	0	0	1	1	1
			etc.					

The stages in each ring counter are connected to the next through a set of crossover gates which can be controlled to "twist" the data between stages. A set of these gates is provided between each pair of stages, thus in one counter there are up to 16 possible ways of coupling (some of the 16 are equivalents).

The state of the cross coupling gates is set for both the X and Y axis by the programme sequencer which is simply an eight-stage binary divider, the first four stages controlling the X counter, and the final four the Y counter. Thus the X counter goes through 16 permutations of programme before the Y counter takes up its next condition.

The clock sequencer allows 16 pulses to be applied to the X counter before the programme sequencer changes the programme. S1b allows pulses to be applied to the Y counter on a one for one basis with the X counter or alternatively one for two or one for four. A fourth position on switch S1a allows manual stepping of the lights and programme by means of a push button.

### PROGRAMME SEQUENCE

To start the whole operation it is useful to know that a precise condition is set and that the programme is at the start, therefore a reset button has been incorporated. Note that this resets everything in the system except the second, third, and fourth stage of each ring counter which is set.

Table 1 shows the movement of "0"s (i.e. lamp illuminating signals) through the X and Y counters for the first 34 clock pulses.

This is a very short extract of the early part of the self-programming switching sequence. It can be seen that at the count of 16 a twist is introduced between stages one and two of the X counter and a further twist is introduced between stages two and three while the first twist is removed at the count of 32. This procedure continues indefinitely and will eventually recycle after going through all combinations of twists and counts.

The Y programme will make its first change after 16 X programme changes.

A "0" in Table 1 indicates that that channel is switched on.

This digital sequencer was successfully built by the author and demonstrated with "P.E. Aurora" at the Audio Fair last year. When left to run through the complete programme some fascinating sequences are obtained, some of an extremely regular nature and some random. Sometimes the unit seems to stop and dwell on certain combinations of lights; this is merely the effect of a freak code cycling through the ring counters.

A word of warning for anyone who wishes to construct this unit—due to the constantly changing combinations of the cross coupling gates it is extremely difficult to keep track of the switching sequence and trouble shooting can become extremely hair raising! Nevertheless certain parts could be abstracted from this complete system for special types of application.

Full constructional details are not provided here since it is expected that anyone interested would be able to translate the logic diagrams into practical wiring. It can prove to be an expensive project, however, and some research into costing is thoroughly recommended before starting.

### PHOTO ELECTRIC CONTROL

Let us move to one of the simplest—and to some extent most amusing—forms of control; namely using light to control light. This is simply done in the case of "P.E. Aurora" by using a photo-sensitive cell and a resistor. Depending on which way round they are connected, a positive or negative logic can be arranged, i.e. light falling on a photo cell to increase the controlled light output of another lamp, or vice versa. Fig. 5 shows both systems.

If the light being controlled is used to illuminate the controlling photocell, some interesting types of positive and negative feedback can be obtained. Even more interesting is to form a ring of control using the light output of one channel to control the next and so on until the loop is closed.

If this is done a delay can be introduced by inserting a capacitor (1 to 10µF) as shown. If one cell is momentarily obscured a ripple can be made to move round the loop—with care and the correct amount of positive feedback coupling one might achieve regenerative oscillation.

### TAPE CONTROL

Quite early on it was envisaged that the "P.E. Aurora" system could be used in conjunction with a loop tape recorder to provide control of shop window or boutique lights. The author has built a system which worked well with three channels. There

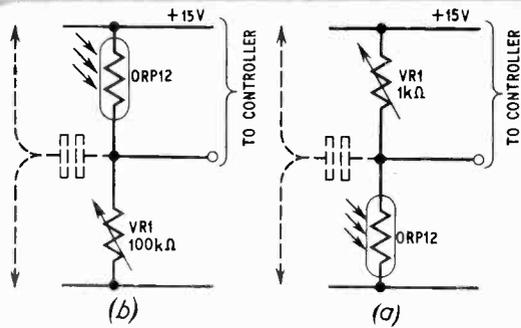


Fig. 5 (above). Two simple control circuits using photo resistive cells. In circuit (a), light falling on the cell will make the controller increase the brightness of a lamp—thus positive feedback could be used to make a self latching system. Circuit (b) does the opposite—light falling on the cell reducing the intensity via the controller. VR1 is made variable to adjust sensitivity. Some interesting ring systems could be made by using the light from one channel to influence the next. Deliberate delays could be introduced with capacitors (as shown dotted)

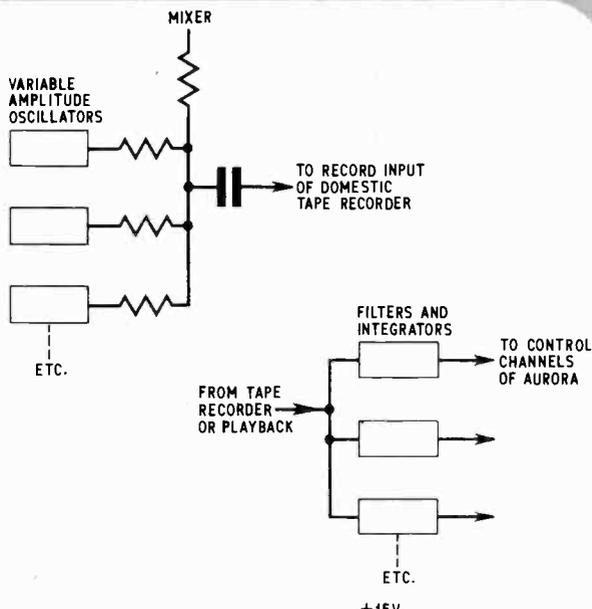


Fig. 6 (top right). Simple schematic for a tape control lighting. The prototype used only three channels to avoid the possibility of interaction. It is quite possible that by careful selection of frequencies harmonic interaction could be avoided if a larger number of channels was desired

Fig. 7 (right). A simple phase shift oscillator. Three mixed together can provide a signal that when recorded could be used with suitable filters (see Fig. 8) to provide tape control of lights. VR2 is used to control the relative levels of signal during recording


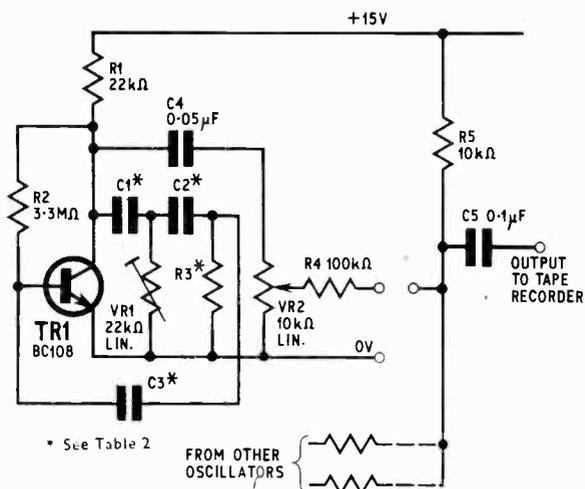


Fig. 8. A more gentle active filter using a series LC tuned circuit for use with a tape recorder if tape control of lights is required. D1 and C9 detect and integrate the filtered audio signal, the amplitude of the resulting d.c. level controls the respective light channel of Aurora, VR3 is used to balance the channels

TABLE 2			TABLE 3		
NOMINAL FREQUENCY	(C1 C2 C3)	R3	NOMINAL FREQUENCY	L1(WOUND ON LA1 FERRITE POT CORE)	C7
1kHz	5000pF	10kΩ	1kHz	800 TURNS	0.1μF
3kHz	1000pF	22kΩ	3kHz	600 TURNS	0.02μF
5kHz	860pF	10kΩ	5kHz	400 TURNS	0.01μF

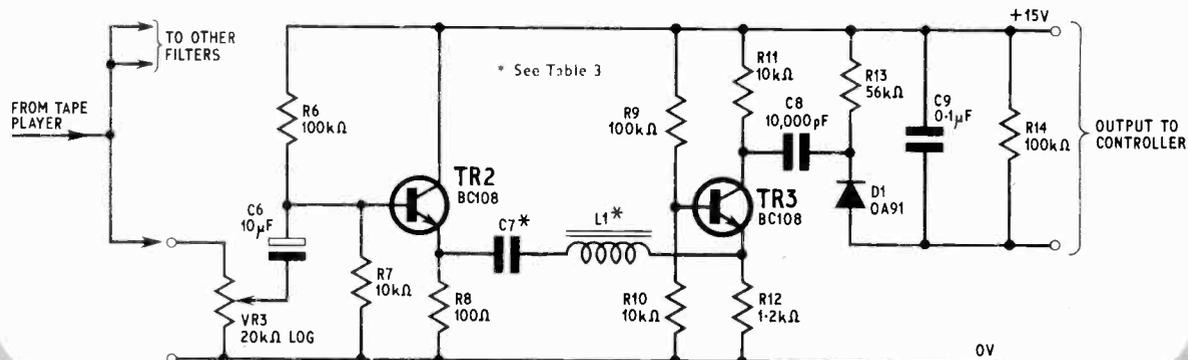

is no reason (apart from interaction between channels) why this should not be extended by using the eight-channel system, but it was thought to be unnecessary expense.

The tape recorder used should be of conventional domestic quality, having a good frequency response up to about 10kHz. Perhaps the most stringent specification is on wow and flutter. If this is undetectable to the ear when a 3kHz pure sine wave is recorded then the recorder is satisfactory. The recorder should also have a manual record level control and should not use a.g.c.

The technique is quite straightforward as shown schematically in Fig. 6. A number of fixed frequency oscillators having frequencies suitably separated (the prototype had three at 1kHz, 3kHz and 5kHz) have their amplitudes adjusted by manual controls. The outputs are mixed together and applied direct to the tape recorder input.

The individual or mixed tones are recorded at various levels, the amplitude being selected to be in proportion to the intensity of illumination ultimately required.

On playback the composite audio signal is applied to a set of tuned audio filters and thence to integrators—rather like the filter unit already described in Part 3.

#### PHASE SHIFT OSCILLATORS AND FILTERS

The prototype phase shift oscillator circuit is shown in Fig. 7 and the tuned filter in Fig. 8. It might be argued that the active RC filter already described would be satisfactory, but it was felt that the characteristic was a little too viscous for precise linear control of amplitude, hence the LC circuit was chosen. Tables 2 and 3 show component values for each of the three frequencies.

Obviously due to component tolerances it will be difficult to obtain precise frequencies and so the oscillators must be tuned to match the respective filter. This is best effected by directly connecting the output of the oscillator in question to the input of the filter; with both VR2 and VR3 set at about mid-range, connect a voltmeter across C9 (range 4V) and adjust VRI until a maximum is read on the meter. If the bandwidth appears excessive, reduce the output level of the oscillator and retune.

When recording it is best to start with a test signal. Set all the oscillator outputs to maximum and set the recording level so that the tape recorder shows maximum level; all other settings of controls will thus be relative to this setting. Record about 30 seconds with all controls at maximum, then record the programme required.

On playback use the maximum level output signal at the leader end to adjust the settings of VR3 for each channel; these should be set so that the light output from "P.E. Aurora" is only just maximum. This equalises the system to counter any devious frequency response of the tape recorder.

It is hoped that the above suggested applications will form the basis for other ideas constructors might have. In an article such as this it is extremely difficult to cover every possibility, but suffice to say any form of input signal in the range of 0 to 1 volt can be used to provide control. ★

Note: The notation of connections of 1R7 into the board (Fig. 19, p. 501, June 1971) may not agree with the configuration of the wires as they appear from the transistor. Check lead notation of the f.e.t. used before soldering into position.

# Safe Reliable Economical!

## BURST-FIRE POWER CONTROLLER...

### FOR ELECTRIC FIRES AND HEATERS

In the control of heating equipment, "burst-fire" has considerable advantages over the "phase-shift" method of thyristor operation.

This compact unit provides continuously variable control of output up to a maximum loading of 1kW.

## TIMER WITH DIGITAL READOUT...

This useful instrument gives direct digital readout with tenths of a second by counting pulses triggered by objects breaking a light beam.


## WAR GAMES COMPUTER

Part 2 of this fascinating project extends the computer to take in elements of chance, rate of fire, and probability of hitting the target.

all in the  
September  
issue of

PRACTICAL  
ELECTRONICS

ON SALE AUGUST 20

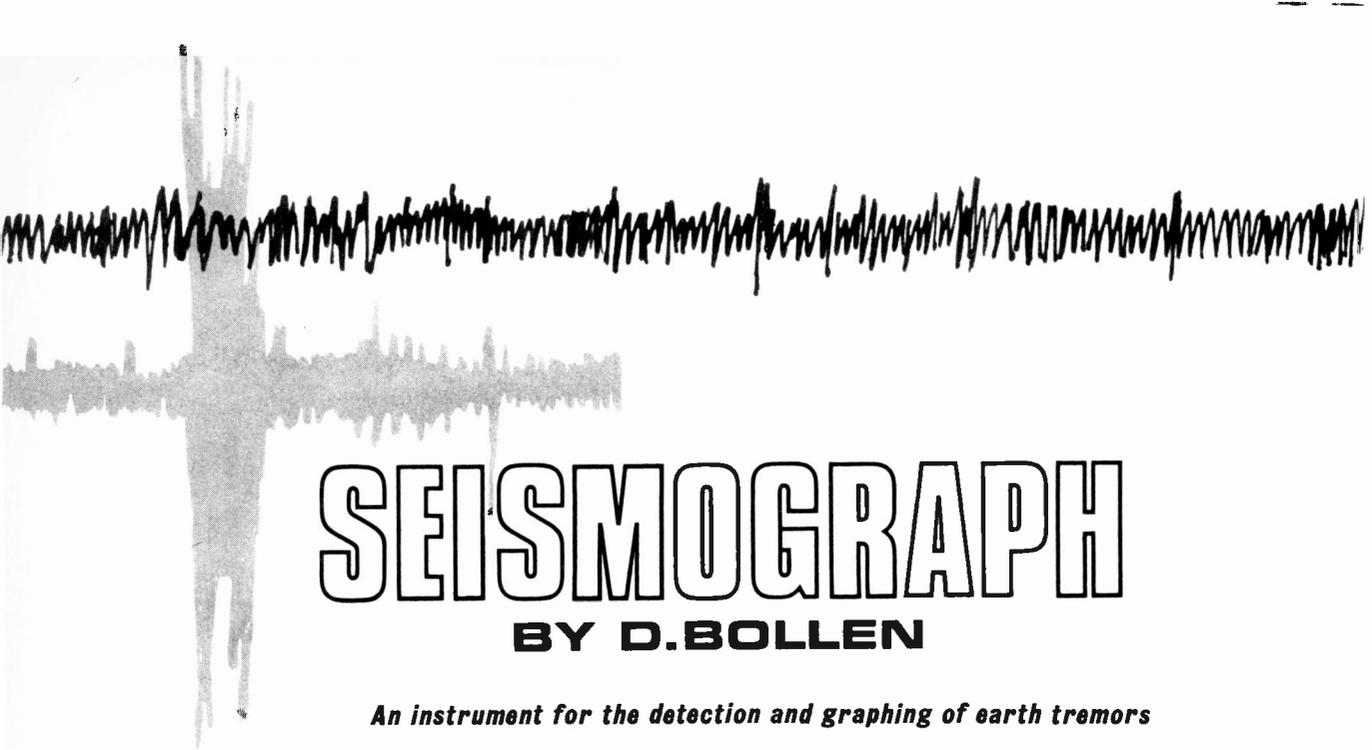

# SEISMOGRAPH

BY D. BOLLEN

*An instrument for the detection and graphing of earth tremors*

**E**LECTRONIC techniques are now extensively employed for detecting and processing signals arising from earth tremors. The circuits and information given in this article are intended to serve as a basis for the construction of a seismograph which has the capability of recording displacements of less than 10 nanometres, roughly the diameter of a medium sized molecule.

Described are a seismometer, a seismometer amplifier, and a pen amplifier which drives an inexpensive chart recorder based on a G.P.O. relay and a clock motor. A block diagram of the complete instrument is shown in Fig. 1.

## SEISMOMETER

A seismometer is the "front end" of a seismograph and consists typically of an inertial mass suspended from a stout frame on a weak spring. When the

ground moves, together with everything resting on it, including the seismometer frame, the mass tends to remain more or less static.

A common form of sensing arrangement, for converting the relative motion of the mass and the seismometer frame into an electrical signal, is a coil of wire free to move between the poles of a powerful magnet, known as a velocity transducer.

The chief advantage of a velocity transducer is that it is insensitive to slow drift caused by thermal and atmospheric displacements of the seismometer mass, but its output is proportional to the energy of the ground movement and not the amplitude.

There are two conflicting requirements in seismometry, on the one hand a faithful response to ground movements covering a wide band of frequencies at low sensitivity, or else a high sensitivity and selectivity with resulting distortion of the signal. A weight suspended from a spring is a

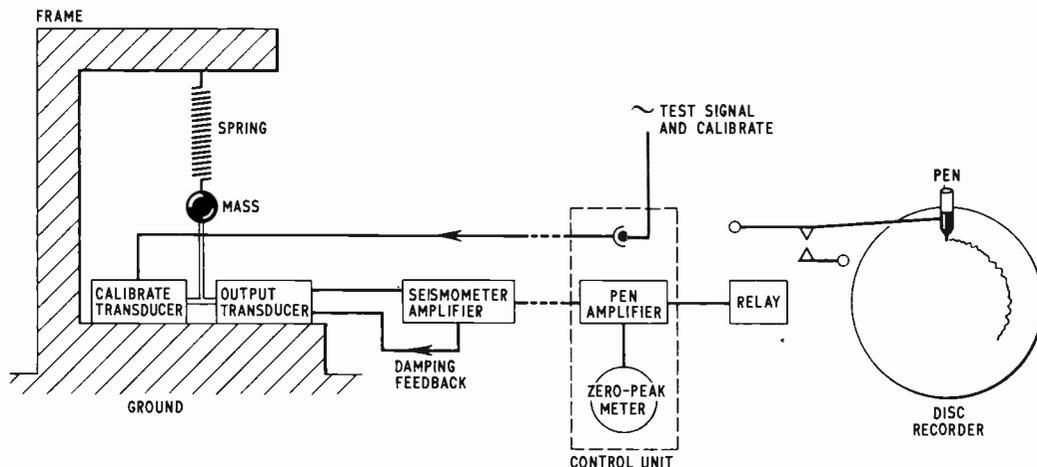


Fig. 1. Block diagram of seismograph

mechanical analogue of a tuned electrical circuit which, when undamped, possesses a high magnification at one particular frequency.

Like the tuned circuit with a high  $Q$ , a seismometer will offer maximum sensitivity when it is sharply resonant, but then exhibits a marked tendency to continue oscillating or "ringing" for some time after the initial disturbance.

The modern trend is to use a damping factor of less than unity and have the seismometer tuned to a relatively narrow range of frequencies, but obviously, much depends on individual requirements.

### SEISMOMETER AMPLIFIER REQUIREMENT

Seismometer amplifiers must be capable of resolving microvolt level signals at frequencies generally lower than 5Hz, and this poses special problems. The noise generated by amplifying devices rises steeply at sub-audio frequencies. For example, a transistor with a noise figure of 5dB at 1kHz could show as much as 25dB at 1Hz.

In order to achieve low noise working at high gains, the frequency range of seismometer amplifiers is usually restricted to a narrow bandwidth. It will be evident from the above remarks, and also bearing in mind the stringent drift performance demanded by continuous operation day after day, that even the best general purpose laboratory type amplifiers would be unsuitable for seismic work.

With a peak noise level of less than 0.2 microvolt over the frequency range of 0.1Hz-10Hz, the seismometer amplifier described here enables the micro-seismic background noise to be recorded even in quiet areas. In terms of ground movement with the transducer used, 0.2 microvolt corresponds approximately to 4 nanometres at maximum gain. In addition, seismometer damping can be adjusted between almost zero and unity by electrical feedback to an extra winding on the transducer coil.

Seismograph response can be varied from a sharply resonant peak at around 1Hz to a substantially flat characteristic extending beyond 0.2Hz-8Hz.

Velocity response curves for the seismometer amplifier combined with a 1Hz vertical seismometer are given in Fig. 2, and this shows how damping affects sensitivity.

### SEISMIC ACTIVITY

One of the mysteries of inner space still waiting to be explained is the origin of some of those tiny earth tremors or microseisms which cause the ground to move continuously. A sensitive seismograph will record microseisms as a noise trace upon which occasional dramatic events, such as earthquakes and large explosions, are superimposed.

It is known that meteorological conditions play some part in influencing the level of microseismic activity. An increase in seismic noise amplitude is often noticed several hours before the approach of a low pressure system and can be used to predict a deterioration in weather conditions.

It is also true that seismic recording stations near the sea have a higher background noise than stations situated in the middle of a continent, and this is attributed to large waves below the ocean surface striking against the continental shelf. However, even when weather conditions are very calm and all known factors have been taken into account, there still remains a significant level of seismic background noise which cannot easily be explained.


### EARTHQUAKE WAVES

An earthquake will cause wave motions to be set up in surrounding rock. Waves of differing character and orientation will move away from the epicentre at various speeds; some will be refracted and reflected by discontinuities in the earth's structure.

First to arrive at a distant location will be the  $P$  or primary wave, causing a movement of earth particles in the direction of travel.  $P$ -waves are, in fact, sound waves transmitted by the inner regions of the globe, and their speed is approximately 5 miles per second.

The slower  $S$  or secondary wave arrives next, at a speed of 3 miles per second, producing a motion transverse to the line of travel. The time lapse between the onset of the  $P$  wave and the arrival of the  $S$  wave can be used to compute the distance of the earthquake.  $S$  waves cannot pass through the liquid core of the earth, and therefore only have a range of about 7,000 miles.

Fig. 2. Seismometer response to constant energy input

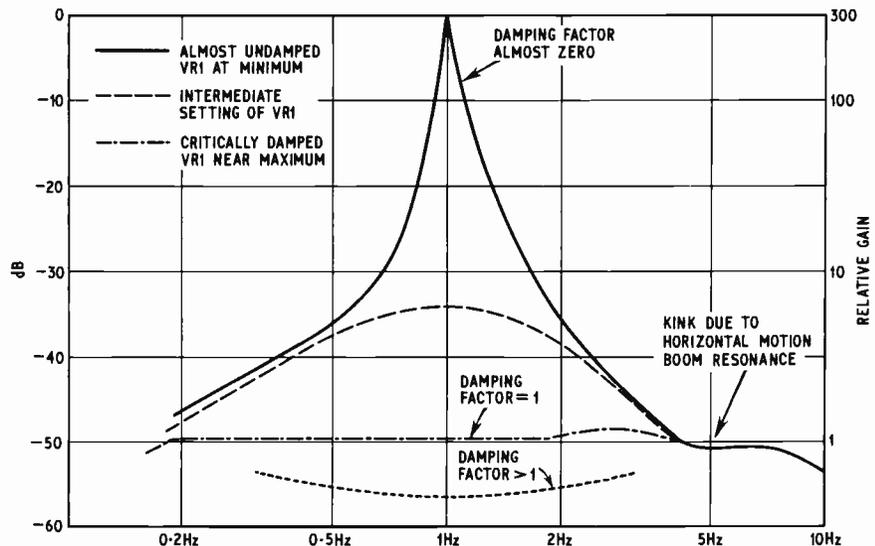

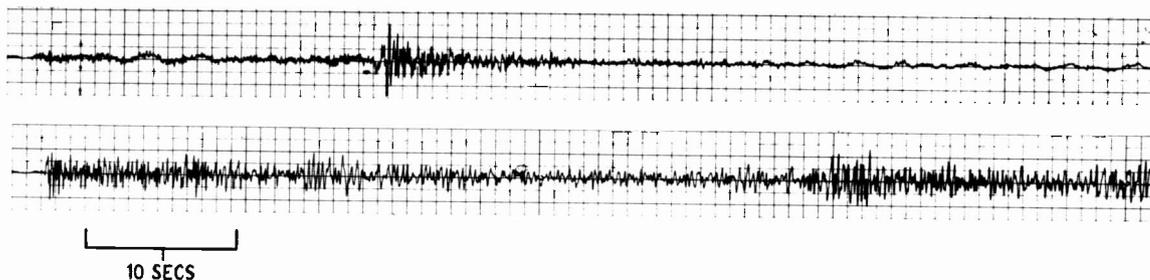


Fig. 3. Professionally recorded traces of earthquakes occurring in the British Isles. Upper trace: earthquake at Glen Spean in Scotland; lower trace: earthquake under South Downs in England (Photo by courtesy U.K.A.E.A. Blacknest)

There are other types of waves which move more slowly and travel on the surface, such as Rayleigh and Love waves, but these are not detected by short-period seismometers of the type described here.

It is important to realise that a *P* or *S* wave may be considerably bent or twisted during its passage through the earth and the actual motion of the ground in response to either could be horizontal, vertical, or a mixture of both, depending on the angle of approach. Therefore, a seismometer which is sensitive to, say, vertical motion only is capable of detecting *P* and *S* waves simultaneously.

Considering an earthquake as a source of broadband noise, over long distances the high frequency components are gradually filtered out, to leave a mixture of waves with periods extending from about 1 second to 1 hour.

Taking rough averages from past records, there are something like 10,000 earthquakes per year of magnitude equivalent to an explosion of 10 tons of T.N.T., 50 per year of about 200 kiloton magnitude, and just two per year of 10 megatons magnitude.

Earthquakes do not receive much publicity unless they are exceptionally large or occur near centres of population. As far as the amateur seismologist is concerned, an event will be recorded perhaps once a week and will either be a large distant earthquake or a local tremor. Much depends on the siting of the seismometer and the manner in which it is coupled to the ground.

To underline the fact that earthquakes occur almost everywhere, two professionally recorded detailed traces of small events in the British Isles are shown in Fig. 3. The upper trace is of an earthquake which had its epicentre at Glen Spean in

Scotland, quite near to the recording station, and the lower trace is of an earthquake under the South Downs in England. It is doubtful if local inhabitants were even aware of these events because they were of small magnitude.

### SEISMOMETER STRUCTURES

It can be seen from Fig. 4, that a modern, professional seismometer is far removed from those early instruments which had masses and booms weighing several tons. The reduction in size is mainly attributable to the use of electrical transducers which need only a small force to drive.

As far as the construction of a seismometer is concerned, this is perhaps less important than the environment in which the instrument is placed. Nearby trees, draughts, loud noises, and local movement caused by animals or humans should be avoided if the best performance is desired.

Successful seismometers have been built by amateurs from pieces of wood and bent wire, but wherever possible the most rigid and durable constructional methods are to be preferred.

Seismometer structures suitable for use with the circuits given here are depicted in Fig. 5. Transducer magnet poles are labelled relatively and can be reversed.

It is important to orientate the transducer coil windings and magnets according to the figures, for maximum electrical output.

### A CHOICE OF FIVE

Looking first at the horizontal pendulum seismometer of Fig. 5a: this uses a triangular shaped boom supported on two spring strip hinges, similar to a garden gate. If the hinge axis was vertical the boom would be unstable, but a slight inclination of the boom downwards, towards the mass, supplies a gravitational restoring force. Strips of 0.002in phosphor bronze or steel shim will serve for hinges.

Although simple to build, with a frame and boom of wood or metal, this seismometer is notoriously difficult to set up and operate, and readily becomes unstable.

In Fig. 5b, the mass-spring seismometer can form a compact and rugged instrument. A mass of several pounds is suspended from a coil spring, and is prevented from moving horizontally by thin cross wires. Resonant frequency is determined by the length of the spring and the weight of the mass.

The vertical pendulum of Fig. 5c consists of a mass secured to an upright boom, which is in turn supported on a strip hinge or knife edge, with restoring force supplied by two coil springs. Resonance can be adjusted by sliding the mass up or down the boom.

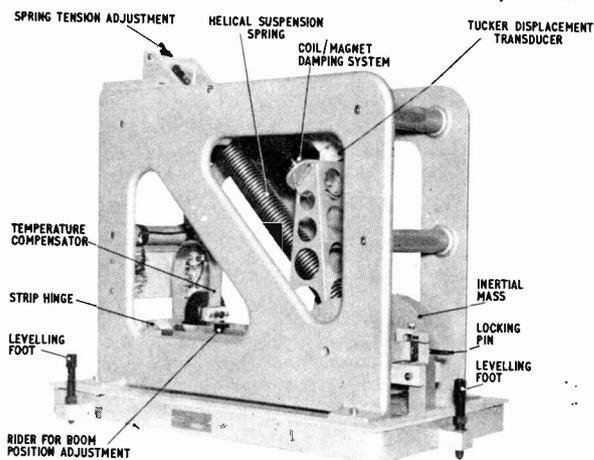


Fig. 4. A professional seismometer

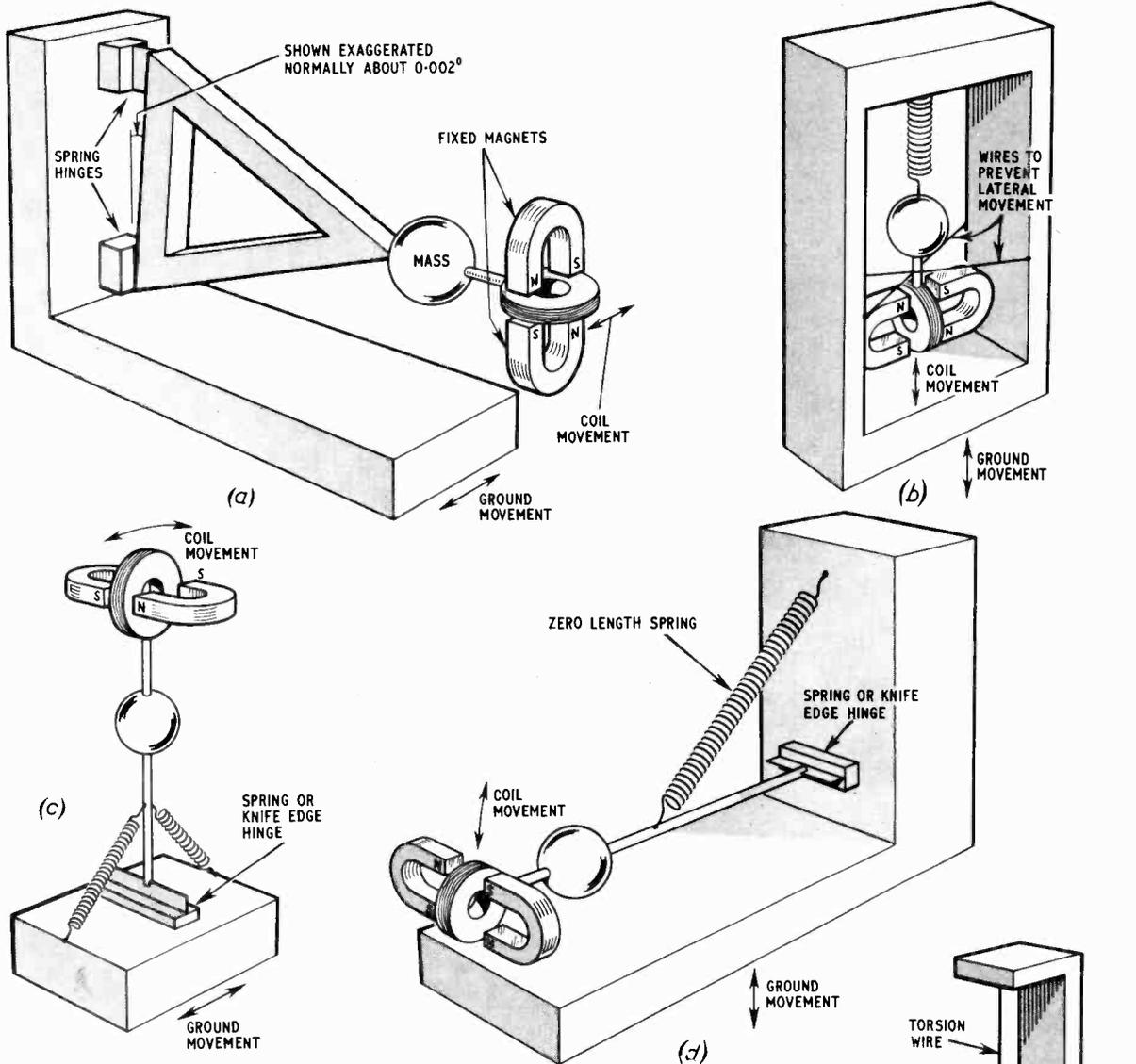



Fig. 5. The five seismometer structures that can be used: (a) horizontal pendulum, (b) mass-spring pendulum, (c) vertical pendulum, (d) spring pendulum, (e) torsion pendulum

Fig. 5d shows a spring pendulum seismometer on the same principle as the Sprengnether of Fig. 4. Resonance is adjusted by sliding the mass along the boom, and moving the spring anchoring points. A special spring must be employed for best results, and the boom pivots on a strip hinge or knife edge.

The choice of seismometer described in this article is based on this principle of operation.

A restoring force is supplied by a tensioned wire in the torsion pendulum instrument of Fig. 5e, and the transducer coil rotates between the poles of a horseshoe magnet. The wire should be about 0.001in in diameter, with the same coefficient of expansion as the upright part of the frame.

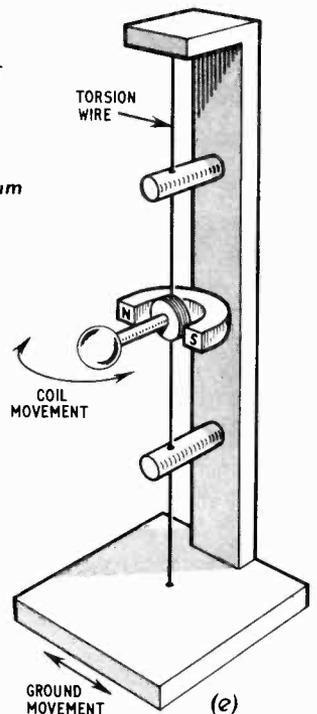To prevent unwanted longitudinal vibrations, the wire is arranged to pass through, but not touch the sides of, holes in two rods. A drop of oil placed in each hole serves to damp the wire. Resonance will depend on the weight of the mass, its distance from the wire, and wire tension.



## SEISMOMETER AMPLIFIER

### Resistors

- R1 390k $\Omega$
- R2\* 1.5M $\Omega$  (see text)
- R3 47k $\Omega$
- R4 330k $\Omega$
- R5 68k $\Omega$
- R6 22k $\Omega$
- R7 4.7k $\Omega$
- R8 1k $\Omega$
- R9 100 $\Omega$
- All 10%,  $\frac{1}{2}$  watt carbon

### Potentiometer

- VR1 22k $\Omega$  sub-min horizontal skeleton

### Capacitors

- C1 160 $\mu$ F elect. 12V
- C2 160 $\mu$ F elect. 12V
- C3 160 $\mu$ F elect. 12V
- C4 0.01 $\mu$ F 250V polyester
- C5 8,000 $\mu$ F elect. 6V
- C6 100 $\mu$ F elect. 12V

### Transistors

- TR1 BC109
- TR2 BC109
- TR3 BC107

### Sockets

- SK1 Two way DIN with plug
- SK2 Non-reversible two way with plug

### Battery

- BY1, BY2 Two Ever-ready 996 6V batteries in series

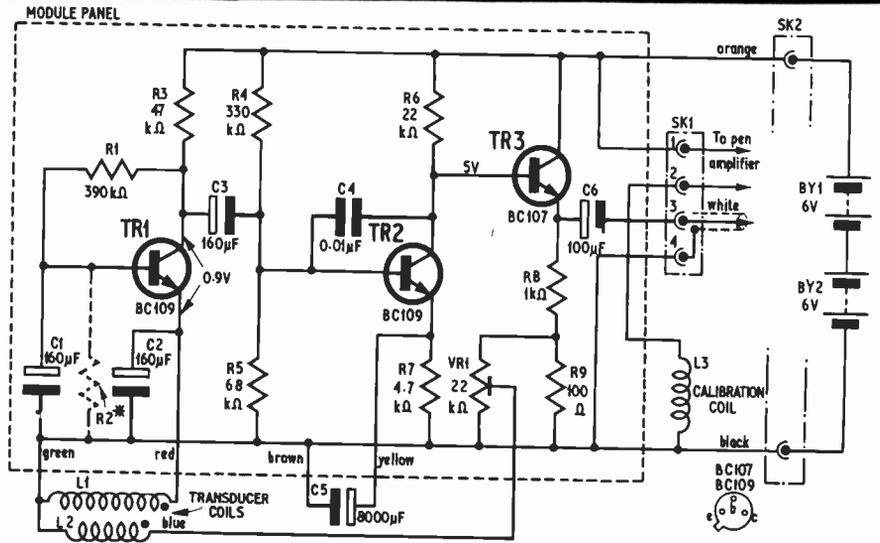


Fig. 6. Circuit diagram of low noise seismometer amplifier

### Miscellaneous

Veroboard 4.3in x 1.9in x 0.1in matrix, 40 s.w.g. enamelled copper wire for transducer coils, four loudspeaker magnets or similar, and one small bar magnet. Aluminium chassis 8in x 3in x  $\frac{1}{2}$ in, s.r.b.p. 8in x  $1\frac{1}{2}$ in, screened microphone cable, capacitor fixing clip to suit C5.

## SEISMOMETER AMPLIFIER CIRCUIT

High gain, low noise transistors are employed for the first two stages of the a.c. coupled amplifier circuit in Fig. 6. Maximum gain of the circuit is in the region of 88dB.

Grounded base silicon transistor TR1 has a collector to emitter voltage of not more than one volt, thus satisfying one of the conditions for minimum noise. Collector current is also low.

The d.c. resistance of the transducer coil in series with the emitter junction of TR1 is about 450 ohms, and this, together with the negative feedback afforded by R1, gives adequate temperature stabilisation.

Resistor R2, shown dotted in Fig. 6, can be adjusted in value, or omitted altogether from the circuit, to allow for transistor gain spreads, and to optimise performance.

Capacitor C1 decouples the base of TR1 to signal frequencies, while C2 across a TR1 emitter input impedance of only a few ohms merely serves to block unwanted high frequencies and mains ripple.

The reactance of the transducer coil is negligible compared with its d.c. resistance at signal frequencies.

TR2 and associated components form a conventional grounded emitter low noise amplifier stage, except for the unusually high value of emitter capacitor C5.


Feedback capacitor C4 largely determines the amplifier high frequency roll off, while C5 controls the low frequency end of the pass band.

Emitter follower TR3 is directly coupled to the collector of TR2, and acts as an impedance converter and buffer stage. A damping feedback current for the seismometer, derived from potential divider R8 and R9, is tapped off by VR1 before being fed to the winding L2 on the transducer coil.

VR1 is pre-set prior to measuring and recording seismic signals, because any human activity in the vicinity of the seismometer is likely to cause overloading.

DIN socket SK1 connects the remote seismometer amplifier output, via a run of screened cable, to the pen amplifier. Two extra wires are included (unscreened) to allow for battery checks and to energise the calibrating coil L3 without the need for going near the seismometer when it is functioning.

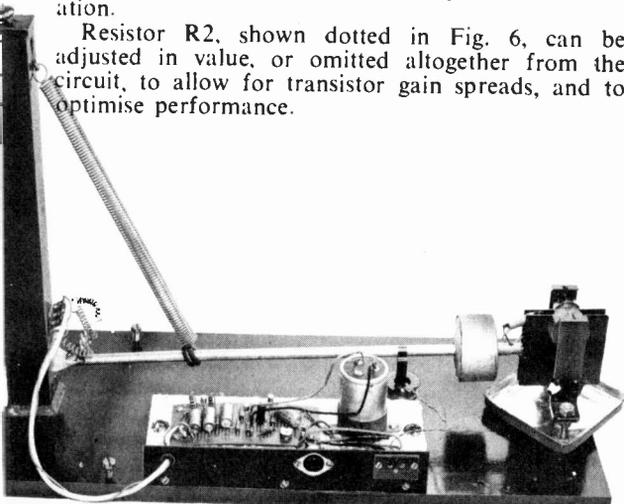A battery power supply was chosen for the seismometer amplifier to avoid a long run of mains cable, and to eliminate troublesome mains borne noise spikes. Two 996, 6V dry batteries in series will power the seismometer amplifier for about three months continuously.



# CONTROL UNIT

### Resistors

- R10 22k $\Omega$
- R11 1.5k $\Omega$
- R12 10 $\Omega$
- R13 1k $\Omega$
- R14 15k $\Omega$
- R15 50k $\Omega$
- R16 5.6k $\Omega$
- R17 180k $\Omega$
- R18 3.3k $\Omega$
- R19 1k $\Omega$
- All 10%, 1/2 watt carbon

### Potentiometers

- VR2 5k $\Omega$  carbon
- VR3 50k $\Omega$  carbon pre-set
- VR4 500k $\Omega$  sub-min skeleton pre-set

### Capacitors

- C7 100 $\mu$ F elect. 12V
- C8 0.01 $\mu$ F polyester 250V
- C9 100 $\mu$ F elect. 12V
- C10\* 160 $\mu$ F elect. 12V
- C11 100 $\mu$ F elect. 12V
- C12 100 $\mu$ F elect. 12V
- C13 2,000-8,000 $\mu$ F elect. 12V
- C14 0.5 $\mu$ F-1,000 $\mu$ F elect. 12V (see text)

### Transistors

- TR4 BC107
- TR5 ACY20
- TR6 BC107

### Diodes

- D1 OA6
- D2 OA6
- D3 ZB12 250mW 12V Zener
- D4, D5 RS210AF 130 p.i.v. 1A (2 off)

### Meter

- M1 50 $\mu$ A Type MR38P

### Lamp

- LPI 6V 60mA m.e.s.

### Transformer

- T1 20-0-20V sub-min mains (Radiospares or Home Radio)

### Sockets

- SK3 DIN 3 way with plug
- SK4/SK5 Two miniature single sockets with plugs
- JK1/PL1 3.5mm jack socket with plug

### Switches

- S1 Push-button or biased toggle single pole changeover
- S2 Miniature toggle single pole changeover

### Miscellaneous

- Veroboard 5.7in  $\times$  1.9in  $\times$  0.1in matrix
- Aluminium chassis 6in  $\times$  4in  $\times$  2.4in
- Panel mounting lamp holder

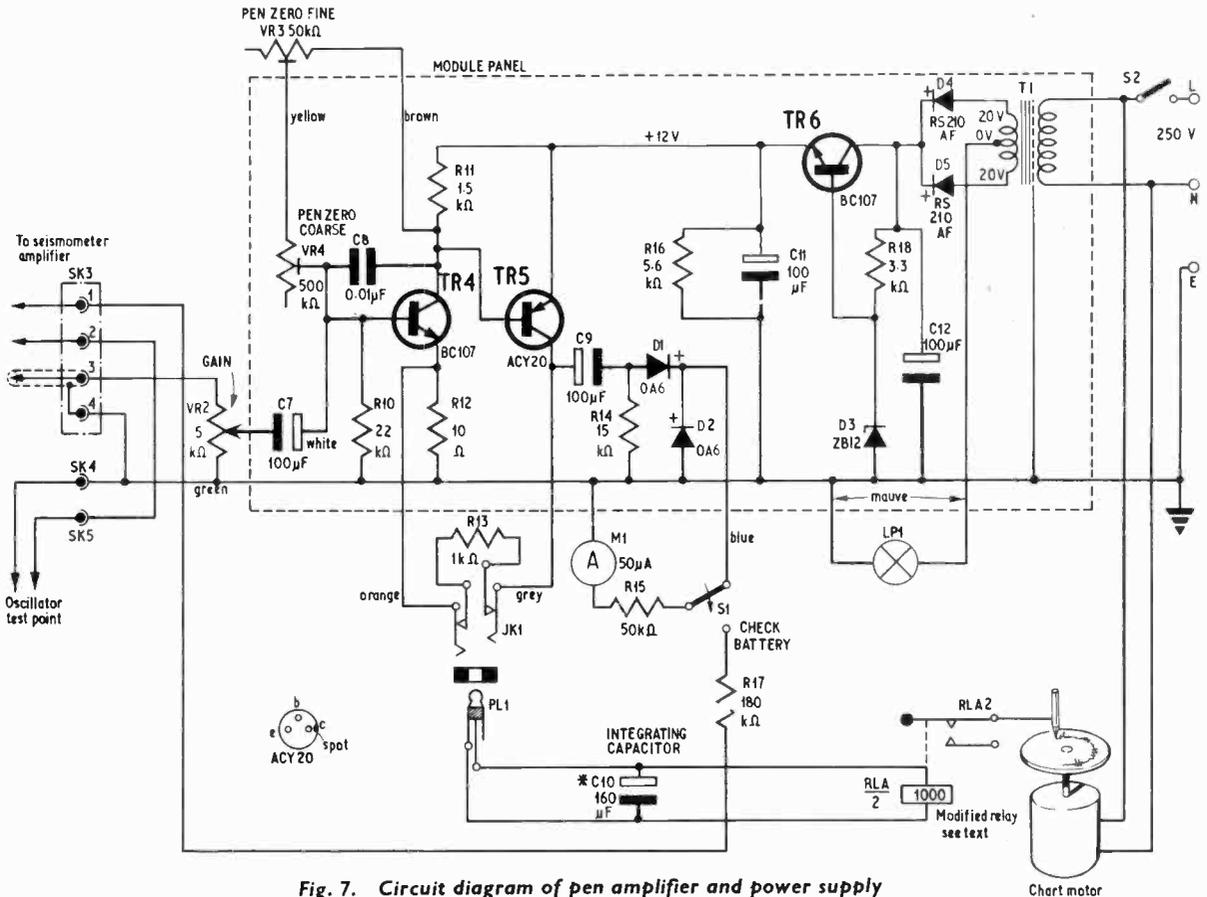


Fig. 7. Circuit diagram of pen amplifier and power supply

## PEN AMPLIFIER CIRCUIT

The pen amplifier of Fig. 7 has a DIN socket SK3 to correspond with the output socket on the seismometer amplifier. VR2 across the pen amplifier input allows adjustment of gain to compensate for day to day changes in microseismic level and anticipated tremor amplitudes.

VR3 and VR4 provide fine and coarse adjustment of the d.c. working point of direct coupled pair TR4 and TR5; this alters the standing current flowing through the pen relay RLA for the purpose of zeroing.

Two negative feedback paths for d.c. and signal frequencies exist in the circuit of Fig. 7. First, feedback given by VR3 and VR4 across the collector and base of TR4, and second the feedback between the collector of TR5 and the emitter of TR4 via the load formed by RLA or substitute resistor R13.

Sufficient feedback is provided to ensure a low impedance output, good linearity, and negligible pen zero drift at normal room temperatures.

A signal from the collector of TR5 is taken via C9 to a special zero-peak meter circuit formed by R14, D1, D2, R15, and 50 $\mu$ A meter. Instead of giving a steady meter reading related to amplitude, the pointer oscillates between zero and peak value at the same frequency as the signal; this technique

offers certain advantages. The smooth, regular movement of the meter pointer when responding to a seismic signal is not confused with the random motion caused by noise or instability, and malfunctions are immediately revealed.

Large amplitude high frequency seismic noise from local sources, such as quarry blasts, is made apparent by the meter pointer not returning to zero between successive cycles, and the frequency of the longer period signals can be determined by counting the oscillations of the meter pointer. Meter reading accuracy is within 3dB over the range 0.2Hz—10Hz.


The pen amplifier is powered by a built-in partly stabilised 12V supply, employing a miniature mains transformer T1, and series regulating transistor TR6.

Lamp LPI serves the double purpose of protecting TR6 in the event of a short circuit, and gives a flashing indication when the pen amplifier is overloaded by a large input signal.

## CHART RECORDERS

Seismograph recorders are usually of the helical trace type, giving a detailed record in convenient form of events separated by many hours. A rectangular piece of paper is wrapped around a drum which revolves, say, once every 24 hours. A pen driving mechanism slowly traverses the drum parallel to its axis on a screw driven carriage, drawing a

## DISC RECORDER

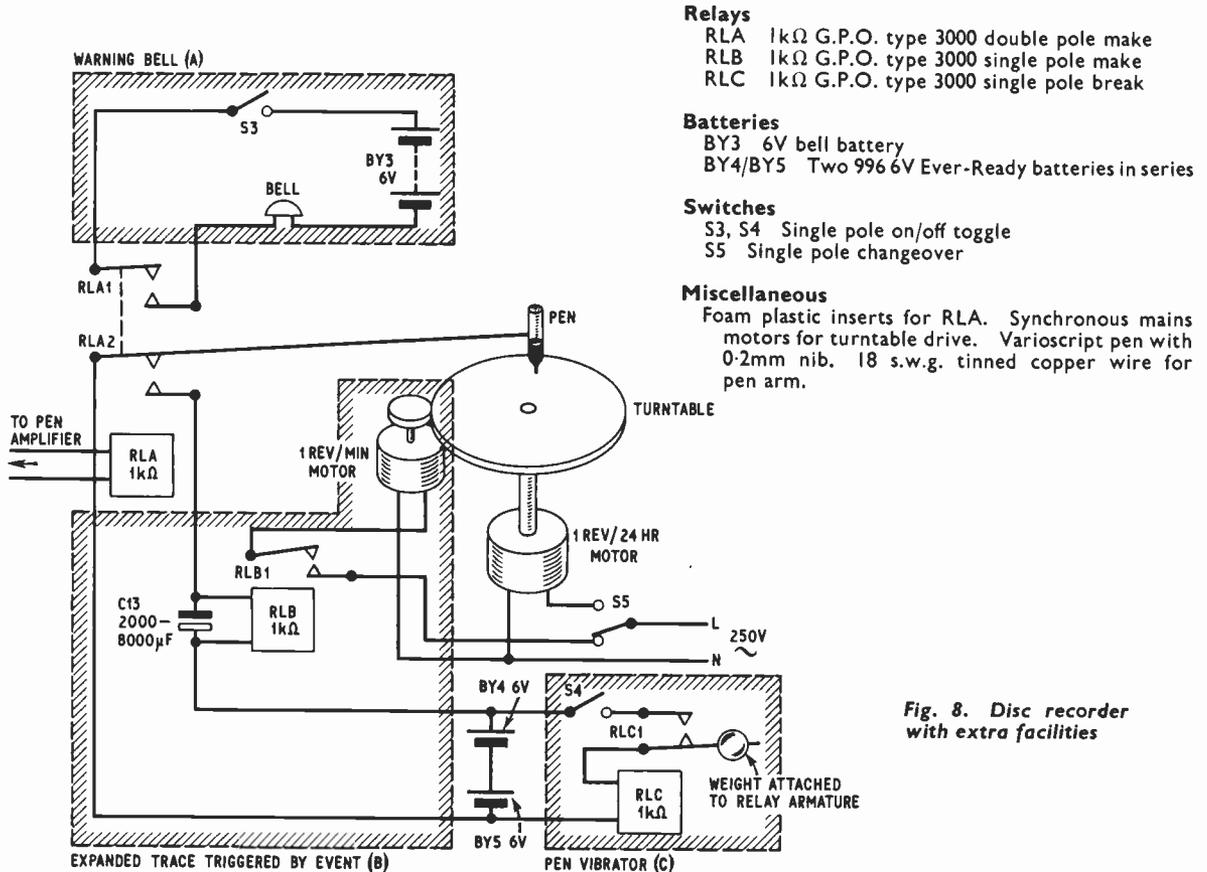

helical trace. Needless to say, a helical recorder is expensive to buy.

Another more familiar alternative, often used by amateur seismologists, is the strip chart recorder, where a roll of paper a few inches wide is fed under the recording pen, but these can use as much as 48 feet of paper per day when employed for seismic work.

If a fully detailed record of seismic events is required then a helical or strip recorder must be purchased or constructed. On the other hand, where the main concern is only with the onset time, duration, and relative amplitude of large scale events, then a trace drawn on a small disc of paper will probably suffice.

A paper disc recorder is simple to construct because there is no elaborate paper feed mechanism. One revolution in 24 hours of the disc will give the approximate time of earthquakes, within a minute or two, and will also show variations in microseismic amplitudes for the purpose of weather forecasting.

Yet another possibility is to have the paper disc revolving, say, once per hour. A signal from the earthquake onset triggers the chart motor on, and an expanded trace of the event will be obtained.

## DRIVING THE PEN

Given a moving piece of paper, the next step is to arrange some way of making the pen traverse the paper in response to a signal. Meter movements are often used to drive pens, but the mechanism is delicate and susceptible to friction.

An ordinary relay can supply a large mechanical force, but the movement of the armature is not linearly related to the current flowing in the relay coil. However, if the armature of a G.P.O. type relay is packed with small pieces of foam plastic, and the coil is supplied with a bias current to offset the pressure of the relay contact springs, it is possible to achieve a linear pen movement over a small arc.

The pen can be attached to the relay armature on a long wire arm, to magnify the movement.

Fig. 8 shows how extra facilities can be added to the basic disc recorder. The warning bell (A) rings at the onset of a tremor, when the seismic amplitude exceeds a pre-set level.

Unit (B) will give an expanded trace for the duration of a large scale event, but does not record between events. RLA2 contacts close, the capacitor C13 is charged to the full battery voltage, which holds RLB on for a period of about 10 seconds, depending on the value of C13.

If the event lasts longer than 10 seconds—and they usually do—repeated closing of RLA2 contacts will keep C13 fully charged, and the turntable will continue to revolve.

To obviate inking difficulties when a fine pen is used, the pen can be made to vibrate up and down slightly by means of a further relay RLC, contained in unit (C), which is wired as a buzzer.

A weight of a few ounces attached to the armature is sufficient to cause a vibration of several thousandths of an inch when relay RLC is mounted under the disc recorder baseboard, and this will keep the ink flowing.

*Next month, constructional details will be given for a 1Hz vertical seismometer, seismometer transducer and amplifier, a pen amplifier and disc recorder, together with information on installing and operating the seismograph.*

# NEWS BRIEFS

## I.E.E. Centenary Exhibition

**T**OMARK the centenary of the Institution of Electrical Engineers, a small special exhibition has been arranged in the main hall entrance of the Science Museum.

Founded one hundred years ago, the I.E.E. then had the title of Society of Telegraph Engineers. This was at a time when the main application of electricity was the telegraph. With expansion this was changed to the Institute of Electrical Engineers in 1888.

The exhibition illustrates the growth of electrical and electronic engineering in the period of the Institution's lifetime, by contrasting state of the art exhibits of the past and present in the fields of medicine, communications and computers.

While telegraphy dominated the electrical scene a century ago, electric lighting was being developed. Two complementary light producers of this period are shown. An arc lamp and its current producing magneto-electric generator for lighthouse use.

One of the show cases of contrasts compared a popular nineteenth century multiplication machine with an Elliott microminiature computer.

Two medical exhibits from the same family tree are the "shocking" machine, an ornate piece of Victoriana which produced high voltage from a hand generator and a modern heart pacemaker. Both the construction and arrangement in the body of the pacemaker are shown.

The show case illustrating the development of electrical communication has a telegraph instrument of a type used in 1871. Also included are an early telephone, a crystal set and one of the first domestic valve radios, these being contrasted with a modern telephone instrument and a small portable radio.

A separate case is devoted to the Institution's activities with examples of its most recent publications.

The exhibition, which opened on May 17, is expected to run for approximately three months.

## British Amateur Electronics Club

**T**HE Secretary of the British Amateur Electronics Club, Mr J. G. Margetts has moved to a new address and anyone who wishes to contact him should write to 17 St Francis Close, Abergavenny, Monmouthshire.

If any readers are interested in the Club, Mr Margetts will be pleased to send details.

## P. E. GEMINI


### REPRINTS AVAILABLE

Because of the continuing interest in the "P.E. Gemini" Dual Purpose Stereo Amplifier it has been decided to reprint all articles (together with any appropriate amendments) in booklet form.

The price of this 32-page booklet is 55p, including postage. Orders for copies, with P.O. or cheque made payable to IPC Magazines Ltd., should be addressed as follows:

The Receiving Cashier (P.E. Gemini)  
IPC Magazines Ltd.,  
Tower House,  
Southampton Street,  
London, W.C.2.

# ELECTRONORAMA

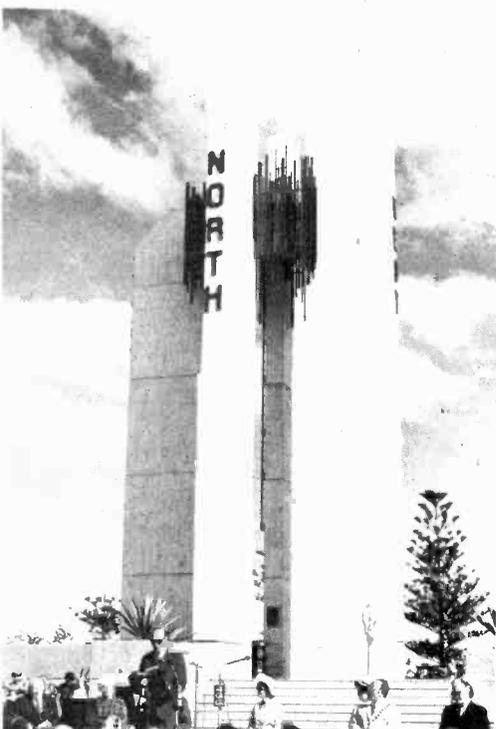

## Laser Lighthouse

**T**HIS gigantic monument was recently completed and opened at Point Danger on the east coast of Australia. It is claimed to be the first laser beam lighthouse in the world combined with a memorial to commemorate the 200th anniversary of Captain Cook's discovery of this east coast point on the border between Queensland and New South Wales.

It is expected that the laser light will penetrate rain and fog for distances up to 22 miles out to sea (six miles beyond the horizon) using only 200 watts of electricity. It shows a red flash every  $7\frac{1}{2}$  seconds which is visible out to sea only.




## Video Tape Recorder To Fly Over North Pole

**A** SPECIAL, compact video tape recorder will film Miss Sheila Scott's attempt to be the first person to fly solo over the North Pole in a light aircraft—a Piper Aztec. It is the lightweight Akai VT 100 self-contained battery-operated video recording system supplied by The Rank Organisation. It provides instant television recording and playback facilities.

Complicated instruments from NASA, the American space Agency, will record and relay her mental and physical state in flight as well as measuring world air pollution. Her North Pole attempt is just part of a 34,000 mile, five week solo flight that will take her one and a half times around the world.

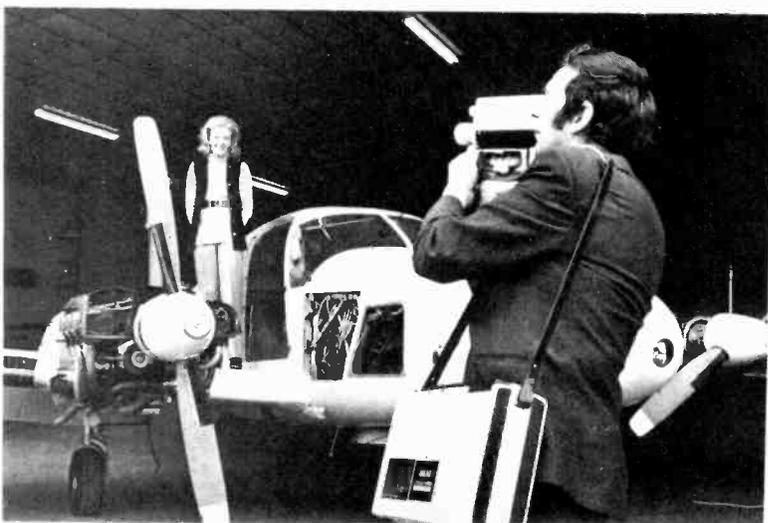The original recorder was stolen from Miss Scott's home just before this magazine went to press, and it was expected that Rank Audio Visual would loan her another.



## PORTABLE ELECTRONIC MUSIC SYNTHESISER

**T**AKE a number of electronic signal generators, add a few effects circuits, mix well and there's no limit—but no limit at all—to the variety and range of the sounds you can produce. Theatrical sound effects, or electronic musical compositions—sounds you create yourself—for the moment or for longer life by transferring to magnetic tape. Add a keyboard, and indeed you become a one-man band. (The pop boys will love it!)

Credit must go to Electronic Music Studios (London) Ltd., who have designed and built this latest wonder in the exciting new field of music synthesisers, "Synthi A".



At £198 it is claimed to be the world's cheapest instrument of its kind. Electronically it is essentially the same as EMS's successful model VCS 3, but scaled down to attaché case size—and is of course, completely portable.

The basic electronic blocks found inside any synthesiser are conventional enough, but devising a system around such circuits and providing maximum flexibility for user control and operation is obviously an art in itself. One of the secrets is that all circuits are voltage controlled.

The important ingredients that make up "Synthi A" are set out below.
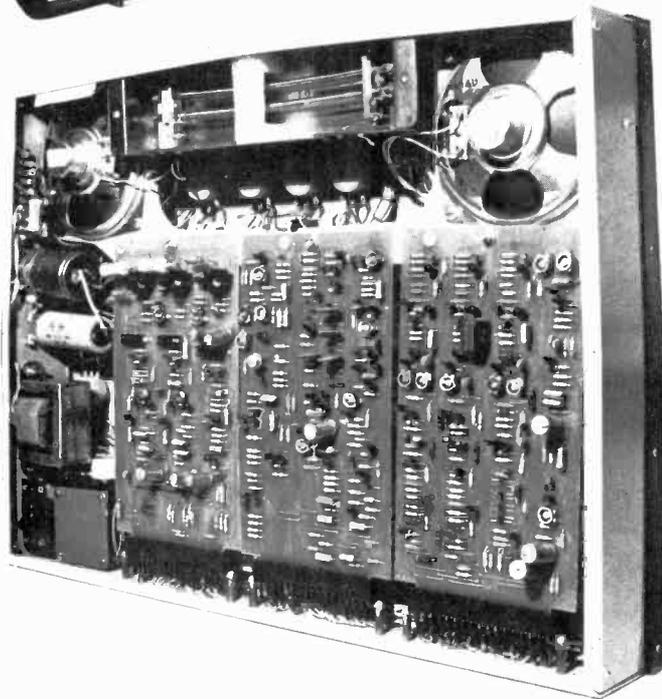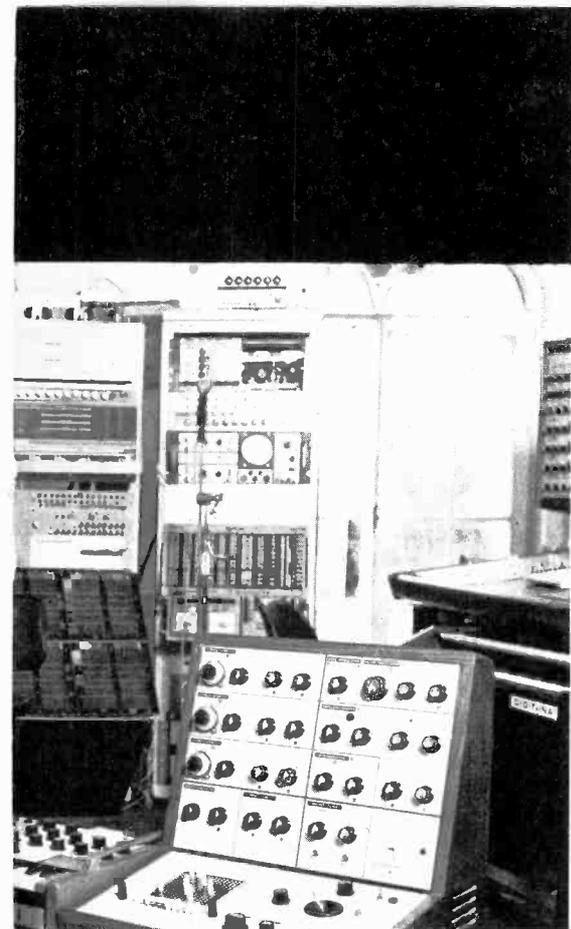
### Signal generation sources

Three tunable oscillators: one gives sine and ramp waveforms, another square and ramp, and both operate over a frequency



range 1Hz to 10kHz. A third oscillator provides square and ramp waveforms but over the exceptionally low frequency range of 0.025Hz (1 cycle every 40 seconds) to 500Hz.

Noise generator with amplitude and colouration controls, so that various bandwidths of noise can be obtained at any level.

Envelope generator, providing a low frequency control waveform.

### Treatment facilities

The foregoing signals can be treated in various ways, for example with reverberation from a spring unit, by filtering via a bandpass filter, which can also be employed as an additional oscillator; and by a ring modulator. Attack/delay can be controlled by the envelope generator.

High and low inputs for microphone and line are provided on the two inputs' amplifiers, both of which have level controls. The two output amplifiers have level controls and, additionally, tone controls, and can be voltage controlled, allowing amplitude modulation and automatic fades and cross fades.

### Monitoring and Patching

Any required signal or control parameter can be monitored on the built-in meter.

Signal patching is by a 16 × 16 way pin-panel matrix—no cords are used. Each of the 256 locations on the matrix board can be identified by a simple map grid reference.

### Manual Control

In addition to the attack/delay the "Synthi A" is equipped with a joystick which enables any two control parameters to be varied simultaneously with one hand, leaving the other hand free for keyboard operation.

### Keyboard Unit

The versatility of "Synthi A" can be further increased by use of a keyboard unit. This additional, optional unit incorporates its own oscillators and it is simply plugged into the front panel of the synthesiser, which can then be played as a musical instrument.

# MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

## CCTV CAMERA KIT

Of particular interest to the amateur and professional engineer is the new and updated version of the **Beulah Electronics** closed circuit television camera kit.

Suitable for education and training establishments, and the keen amateur, this high quality, yet fairly inexpensive 625 line video camera has a claimed resolution in excess of 350 television lines.

A fully comprehensive instruction manual is included with the kit and the original manufacturers' guarantees apply to all parts. Beulah Electronics will also carry out inspection, testing and setting up after assembly, if required, for a charge of £5 excluding the cost of postage and packing.

If the "New Beukit" camera is required to operate in conjunction with an off-air television receiver, an r.f. kit is available as an extra.

The price of the "New Beukit" complete with manual and all parts, excluding vidicon tube, is £45.50. Vidicon tubes are available at various qualities and prices from £5-£15 and first grade tubes at £25. The cost of the r.f. kit is £3.75. Various other extras including lenses and tripods are available if required.

Further information and supplies of the "New Beukit" can be obtained from Beulah Electronics (1970) Ltd., Upper Halliford Road, Shepperton, Middx.

## AUDIO SUITE

A new range of inexpensive audio equipment marketed under the name **Viscount** has been introduced by **Radio and TV Components (Acton) Ltd.** Complete stereo systems are offered.

The heart of each system is the **Viscount** amplifier, of which there are two versions: The **RT100** for ceramic cartridges and the **RT101** which has an additional input stage designed to accept magnetic cartridges. Both versions have an output of 14 watts per channel r.m.s. with a frequency response of 40Hz to 40kHz  $\pm 3$ dB.

The input stages of these amplifiers incorporate f.e.t.s which give excellent signal to noise ratio. Both units have features unusual in the price range such as a headphone socket, and a separate output for a tape recorder is incorporated.

System 1 (available at £52 complete), comprises the **Viscount RT101** amplifier, **SP25** with magnetic cartridge, and a pair of **Duo Type II** speakers.

System 2 (£69), is as System 1, but with **Duo Type III** speakers capable of handling outputs up to 20 watts.

System 3 (£49), comprises the **Viscount RT100** amplifier, **Garrard SP25** turntable with ceramic cartridge, and a pair of **Duo Type II** speakers giving a maximum output of 10 watts.

Postage and package is not included in the above prices.

Examination of the amplifier plus listening tests of the complete systems suggest that this is good all round value for money—the use of imported semiconductors no doubt being a vital factor in keeping the amplifier price to such a modest level. The makers are also modest (and sensible) in that they make no pretensions that this is "hi fi". More to the point, or rather to the ear, and the pocket, the quality is likely to meet the requirements of many who wish to sit down and enjoy music without incurring a tremendous financial outlay.



Audio suite from **Radio and TV Components**

## STEREO AMPLIFIER

A new stereo amplifier incorporating an f.e.t. integrated circuit is the latest product from **Tripletone Manufacturing Co. Ltd.**, 138 Kingston Road, Wimbledon, S.W.19.

Known as the **Tripletone 800 Mk II**, it has a claimed continuous power output of 18W r.m.s. per channel into 4 ohms and 15W r.m.s. per channel into 8 ohms. Power bandwidth is quoted as  $-3$ dB 30 to 25,000Hz and the distortion level is claimed to be less than 0.2 per cent.

Inputs are provided for tape, radio, magnetic and ceramic cartridge. The load for the ceramic cartridge is kept at 2 megohms at all frequencies by the use of the f.e.t. integrated circuit. The magnetic input will take an overload of 120mV before clipping.

A feature of the amplifier is the inclusion of a dual concentric control for the middle frequencies as well as for the volume, bass and treble. A top cut filter is provided by an illuminated push-button and a jack socket is fitted for headphone listening.

The 800 Mk II is housed in a teak case with a black and silver aluminium fascia and is priced at £38.50.

New Beukit camera marketed by **Beulah Electronics**




**Tripletone 800 Mk II** stereo amplifier

# LOOK!

**PRACTICAL!**

**VISUAL!**


**EXCITING!**

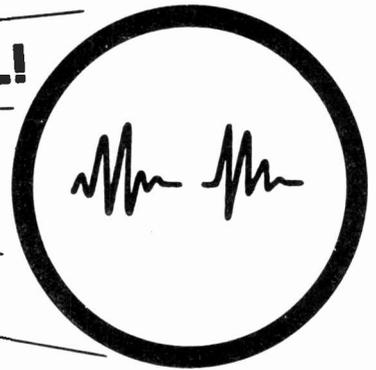

a new 4-way method of mastering  
**ELECTRONICS**  
by doing — and — seeing . . .

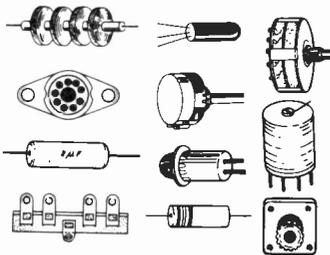
**1** ▶ **OWN and HANDLE a**

complete range of present-day **ELECTRONIC PARTS and COMPONENTS**



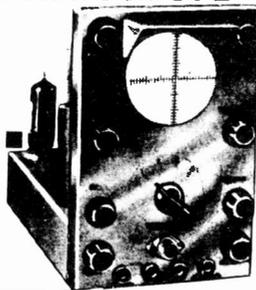
**2** ▶ **BUILD and USE**

a modern and professional **CATHODE RAY OSCILLOSCOPE**



**3** ▶ **READ and DRAW and**

**UNDERSTAND CIRCUIT DIAGRAMS**

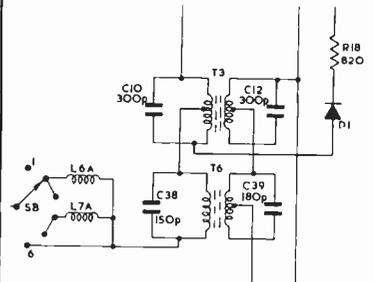

**4** ▶ **CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW  
for  
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: we do not employ representatives

NAME..... BLOCK CAPS

ADDRESS..... PLEASE PE8

The Galaxy M104 in the constellation of Virgo. The dark band across the middle is interstellar dust which obscures the light of the stars. Our own Galaxy might appear like this to an observer seeing it edge on. The M104 is about 40 million light years away

# RADIO ASTRONOMY TECHNIQUES

BY F.W.HYDE · PART 3

IN the previous article the simple two-aerial interferometer was described, the limitations noted, and mention made of a modification which can overcome some of these limitations.

## PHASE-SWITCHED INTERFEROMETER

The first important modification came from Ryle in 1952. In this improved system the receiver does not measure the difference in power between two aerials, but is used to measure the correlation between two voltages when the phase of one aerial is changed in relation to the other.

Theoretically, this could be done by moving one aerial one half-wavelength in relation to the other. However, this is not practical, so it has to be done electrically. It is in fact, quite simple to do this, for by introducing a length of line one half-wavelength long, the same result is achieved. This change is made by a changeover switch, see block diagram in Fig. 3.1. For one half-cycle S1 connects aerial (B) directly to the receiver, and for the next half-cycle brings into circuit a length of cable one half-wavelength at the frequency at which the telescope is operating.

In this system, the background radiation from the galaxy, being an extended source, would give equal

power in the receiver whether the aerials were in phase or anti-phase. On the other hand, a small source passing through the aerial beam would not have the same effect in both positions, so that the output from the receiver would vary at the frequency at which the aerials were switched. If the recorder is connected to this arrangement then the pattern will appear as in Fig. 3.2.

It is possible to use much greater sensitivity in the recording network by this method, and in the first trials; sources only 1/1000 of the background level could be detected. The resolution of the system enabled small sources to be readily distinguished from each other.

## ROTATING LOBE INTERFEROMETER

A variation of the phase-switched system is the rotating lobe interferometer, due to Jennison and Latham. This enables the fringes of the system to be rotated quite independently of the movement of the aerial systems across the sky. The block diagram is shown in Fig. 3.3.

One very important advantage of this system is that it may be used in north/south arrangements and it produces a fringe pattern which cannot be achieved with the phase-switched interferometer.

The limitation mentioned earlier in regard to the area of sky covered by the aerial beam from north to south is overcome by the rotating lobe method.

## GRATING INTERFEROMETER

The combination of aerials as interferometers is often used to obtain special effects. One of such combinations is the grating interferometer. This system uses a number of aerials in line and connected to a receiver by feeders equal in length, see (a) in Fig. 3.4. The reception pattern that results is similar to a diffraction grating, and is shown in (b) in Fig. 3.4.

An example of the pattern resulting when the sun is scanned is given in Fig. 3.5. This shows the very high degree of resolution of the source which is


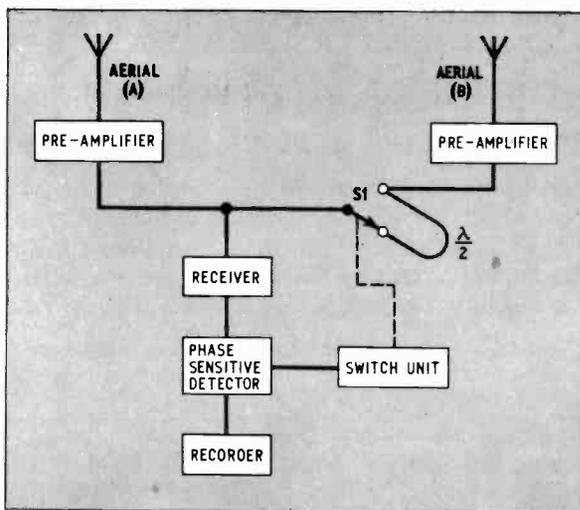


Fig. 3.1. Block diagram of a phase-switched interferometer

<p><b>LOW VOLTAGE AMPLIFIER</b> Few only at plus 13p <b>£1.75</b> P. &amp; P.</p> <p>5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player baby alarm, etc., amplifier.</p> 	<p><b>"VARLEY" MIDGET RELAY</b> 33p</p> <p>D.P.D.T. Switch Contacts. 700 ohm. Coil. Varley V.P.2 CAB/26 Relay. P. &amp; P. on this item Free</p>	<p>Our new shop now open at <b>13 SOUTH MALL, EDMONTON, N.9</b> carries our complete stock of electronic components and hi-fi</p>	
<p><b>CRESCENT RADIO LTD</b> 11 &amp; 40 MAYES ROAD, LONDON N22 6TL 888 3206</p>			
<p><b>PSYCHEDELIC LIGHT CONTROL UNIT</b></p> <p>Three Channel: Bass-Middle-Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 300W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) <b>£18.50</b> plus 38p P. &amp; P.</p> <p>If you require more information please send S.A.E.</p> 	<p><b>STEREO HEADSET</b></p> <p>8 ohm impedance, complete with plug and 3ft lead. A very comfortable phone set. Listen to stereo without noise interrupting the pleasure. Wonderful value. <b>£2.50</b> plus 10p P. &amp; P.</p> <p><b>STEREO JUNCTION BOX</b></p> <p>For stereo amplifiers without stereo jack socket. <b>£1.25</b> plus 8p P. &amp; P.</p> 	<p><b>MAIL ORDER DEPT.</b> No. 11 MAYES RD. LONDON N22 6TL</p> <p><b>MAINS KEYNECTOR</b></p> <p>Keynector connects any Electrical Equipment to the mains supply in seconds. Ideal for bench, garage, demonstrations, etc. Multi connections can be made (max. load 13A fused). P. &amp; P. <b>ONLY £2.75</b> 6p.</p> <p><b>ELECTROLYTIC CAPACITOR</b></p> <p>1,500mF at 150V d.c. working. Plessey U.K. capacitor. Approx. size: 2in. diameter x 4 1/2in. long. A bargain at 40p plus 5p P. &amp; P.</p> 	
<p><b>BATTERY ELIMINATOR</b></p> <p>Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator. 2in x 2in x 3in approx. 4 1/2V <b>£1.50, 6V £1.50, 9V £1.50, 7 1/2V</b> complete with cable and plug for Philips Cassette. <b>£2</b> plus 8p P. &amp; P. each.</p> 	<p><b>CRESCENT CASSETTES</b></p> <p>Top quality cassettes at unbeatable prices (complete with standard storage case): C60 <b>38p</b>, C90 <b>63p</b>, C120 <b>88p</b> plus 6p P. &amp; P.</p>	<p><b>MIDGET FLEX CONNECTOR</b></p> <p>Approx. 2 amp rating. Two-pin non-reversible midget flex connector. Approx. size: 2in x 2in. Ideal for loudspeaker connections, etc. <b>8p</b> plus 2p P. &amp; P.</p>	<p><b>BARGAIN BOARDS</b></p> <p>Components galore for the experimenter. Ex computer boards with Resistors, Capacitors and useful Transistors—at least 4 transistors per board. <b>BARGAIN PRICE 30p</b> per board 5 BOARDS <b>£1.20</b>. P. &amp; P. Free on this item.</p> 
<p><b>BRIGHTNESS CONTROL</b></p> <p>Full control over 300 watts of incandescent lighting. Thyristor light dimmer mounted on a standard switch block ready to fit into a MK. Box. Enjoy the pleasure of having the precise amount of light you require at any time. Our Price <b>£2.75</b> plus 8p P. &amp; P. each.</p> 	<p><b>HIGH QUALITY IMPORTED HEADPHONES</b></p> <p>1,000 Ohm per phone <b>80p</b> TTC 2,000 Ohm per phone <b>88p</b> G1105 Plus 10p P. &amp; P. per pair.</p> 	<p><b>MAINS TRANSFORMER</b></p> <p>Fused. Primary 240V. Secondary 220V @ 50M/A. 6-3V @ 1A. This transformer is made to a very high standard and is a small size: 2in x 2 1/2in x 2 1/2in. <b>68p</b> plus 15p P. &amp; P.</p> 	<p><b>CHROME TV STAND</b></p> <p>28in x 6 1/2in x 16in high. This modern design TV stand would make an ideal base for a coffee table and is a bargain at: <b>£1.63</b> plus 25p P. &amp; P.</p> 
<p><b>"CRESCENT" D.J. PARTY AMPLIFIER "P100"</b></p> <p>A completely new style 100W Amplifier especially designed for the D.J. who expects his equipment to look and sound really good, and still keep a moderate price: 10-30,000Hz response. All loudspeaker systems suitable. Full output into 4 ohm. <b>£42</b></p> <p>All silicon transistors. F.E.T. at front end. Real value at plus £1 P. &amp; P. and insurance.</p> <p><b>£2 DISCOUNT</b></p> <p>If purchased at the same time as the Psychedelic Light Control Unit. If you require more information please send a S.A.E.</p> 	<p><b>COMPONENT BARGAIN</b></p> <p>1 32 + 16 mFd 275V Capacitor; 1 Speaker Output Transformer; 2 B9A Valve Holders; 1 4,700 pF Capacitor; 1 175 ohm W/W Resistor; 1 330 ohm, 1W Resistor; 1 12 kΩ 1W Resistor. All mounted on a small Amplifier Panel. Only <b>38p</b> P. &amp; P. free.</p> 		
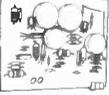
# We'll give you the chance you didn't take at school.



'O' level standard in Maths, and Science or English, could get you a great career in today's Navy. We'll train you to be one of our top technicians, working on space-age equipment and earning £2,000 a year at 24. If you're 15½-17½ send for our free book.

## APPRENTICESHIPS

Name

Address

Date of birth

(Enquiries from U.K. residents only)

Royal Naval Careers Service (877QN1), Old Admiralty Bldg., Whitehall, London S.W.1. Please send me, without obligation, your free booklet, "Royal Navy Technician Apprenticeships".

**RN**  
ROYAL NAVY

# ELECTROVALUE

EVERYTHING BRAND NEW TO SPEC • LARGE STOCKS • NO SURPLUS

## BARGAINS IN NEW SEMI-CONDUCTORS

MANY AT NEW REDUCED PRICES • ALL POWER TYPES WITH FREE INSULATING SETS

40361	55p	2N2905	44p	2N4291	15p	BC148	9p	BFX87	29p
40362	68p	2N2905A	47p	2N4292	15p	BC149	10p	BFX88	26p
2N696	17p	2N2924	20p	AC107	46p	BC153	19p	BFY50	23p
2N697	18p	2N2925	22p	AC126	20p	BC154	20p	BFY51	20p
2N706	12p	2N2926	11p	AC127	20p	BC157	12p	BFY52	23p
2N930	29p	2N3053	27p	AC128	20p	BC158	11p	BSX20	16p
2N1131	29p	2N3055	60p	AC153K	22p	BC159	12p	C407	17p
2N1132	29p	2N3702	13p	AC176	16p	BC167	11p	MCI40	25p
2N1302	19p	2N3703	13p	ACY20	20p	BC168	10p	MPS6531	35p
2N1303	19p	2N3704	13p	ACY22	16p	BC169	11p	MPS6534	30p
2N1304	26p	2N3705	13p	ADI40	63p	BC177	14p	NKT211	25p
2N1305	26p	2N3706	13p	ADI42	50p	BC178	13p	NKT212	25p
2N1306	33p	2N3707	13p	ADI49	58p	BC179	14p	NKT214	23p
2N1307	33p	2N3708	10p	ADI61	33p	BC182L	11p	NKT274	18p
2N1308	36p	2N3709	11p	ADI62	36p	BC183L	10p	NKT403	65p
2N1309	36p	2N3710	13p	AF114	24p	BC184L	11p	NKT405	79p
2N1613	23p	2N3711	13p	AF115	24p	BC212L	16p	OC71	38p
2N1711	26p	2N3819	23p	AF117	22p	BC213L	16p	OC81	25p
2N1893	54p	2N3904	35p	AF124	24p	BC214L	16p	OC81D	25p
2N2147	95p	2N3906	35p	AF127	22p	BCY70	18p	ZTX300	14p
2N2218	34p	2N4058	13p	AF139	33p	BCY71	33p	ZTX301	16p
2N2218A	44p	2N4059	10p	AF239	36p	BCY72	15p	ZTX302	22p
2N2219	38p	2N4060	11p	ASV26	27p	BF115	23p	ZTX303	22p
2N2219A	53p	2N4061	11p	ASV28	27p	BF167	18p	ZTX304	27p
2N2270	62p	2N4062	12p	BC107	12p	BF173	19p	ZTX500	18p
2N2369A	19p	2N4124	18p	BC108	12p	BF194	14p	ZTX501	21p
2N2483	35p	2N4126	27p	BC109	12p	BF195	15p	ZTX502	25p
2N2484	42p	2N4284	15p	BC125	15p	BFX29	31p	ZTX503	22p
2N2646	47p	2N4286	15p	BC126	22p	BFX84	25p	ZTX504	52p
2N2904A	42p	2N4289	15p	BC147	10p	BFX85	52p		

Appointed distributors for  
**SIEMENS (U.K.) LTD.**

Appointed stockists

**NEWMARKET TRANSISTORS  
RADIOHM POTENTIOMETERS**

## SAVE £6.25 ON THE NEW ENGLEFIELD 840 AMPLIFIER

This latest Peak Sound high fidelity amplifier incorporates many strikingly original features including facility for adding in stereo FM tuner. Superb performance characteristics and luxurious styling. Electrovalve choice of simulated soft leather covering in black, blue, red or dark green. As advertised at £45. Our price, net **£38.75**

### MAINLINE AMPLIFIER KITS

70W. power amplifier, £12.60 nett.

### 30 WATT BAILEY AMPLIFIER PARTS

Transistors and PCB for one channel £6.46  
Capacitors, resistors (metal oxide), and transistors, one channel. £8.41.  
Complete unregulated power supply pack. £4.75  
Suitable heatsink 10DN size 400C, 55p  
Suitable heatsink 10DN 400C, 55p

## RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9 (see note below)	10 to 99	100 up
C	1/20W	5%	82Ω-220KΩ	E12	9	8	7
C	1/8W	5%	4.7Ω-470KΩ	E24	1	0.8	0.7
C	1/4W	10%	4.7Ω-10MΩ	E12	1	0.8	0.7
C	1/2W	5%	4.7Ω-10MΩ	E24	1.2	1	0.9
C	1W	10%	4.7Ω-10MΩ	E12	2.5	2	1.9
MO	1/2W	2%	10Ω-1MΩ	E24	4	3.5	3
WW	1W	10% ± 1/20Ω	0.22Ω-3.9Ω	E12	7	7	6
WW	3W	5%	12Ω-10KΩ	E12	7	7	6
WW	7W	5%	12Ω-10KΩ	E12	9	9	8

Codes: C = carbon film, high stability, low noise.  
MO = metal oxide, ElectroXil TR5, ultra low noise.  
WW = wire wound, Plessey.

### Values:

E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

**ZENER DIODES** 5% full range E24 values:  
400mW: 2.7V to 30V, 15p each; 1W: 6.8V to 82V, 27p each; 1.5W: 4.7V to 75V, 60p each.  
Clip to increase 1.5W rating to 3 watts (type 266F), 4p.

**CARBON TRACK POTENTIOMETERS**, long spindles. Double wiper ensures minimum noise level.

Single gang linear 100Ω to 2.2MΩ, 12p; Single gang log, 4.7KΩ to 2.2MΩ, 12p; Dual gang linear 4.7KΩ to 2.2MΩ, 42p; Dual gang log, 4.7KΩ to 2.2MΩ, 42p; Log/antilog, 10K, 47K, 1MΩ only 42p; Dual antilog, 10K only, 42p. Any type with 3A D.P. mains switch, 12p extra.  
Only decades of 10, 22 and 47 available in ranges quoted.

### CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only: 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 4M7, 10MΩ. Vertical or horizontal mounting, 5p each.

**COLVERN** 3 watt Wire-wound Potentiometers, 10Ω, 15Ω, 25Ω, 50Ω, 100Ω, 150Ω, 250Ω, 500Ω, 1K, 1.5K, 2.5K, 5K, 10K, 15K, 25K, 50K, 33p each.

Handbook of transistor equivalent and substitutes, 40p. (Postage 3p if ordered alone).

Prices are in pence each for quantities of the most ohmic value and power rating. NOT mixed values. (Ignore fractions on total value of resistor order.)

### MULLARD polyester C280 series

250V 20%: 0.01, 0.022, 0.033, 0.047 3p each; 0.068, 0.1, 4p each; 0.15, 4p; 0.22, 5p, 10%: 0.33, 7p; 0.47, 8p; 0.68, 11p; 1.1, 14p; 1.5, 14p; 2.2, 14p; 2.2, 14p.

### MULLARD SUB-MIN ELECTROLYTICS

**C246 range, axial lead** 6p each  
Values (μF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/64; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/64; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/64; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/64; 125/4; 125/10; 125/16; 160/2.5; 200/64; 200/10; 250/4; 320/2.5; 320/64; 400/4; 500/2.5.

### LARGE CAPACITORS

High ripple current types: 1000/25, 28p; 1000/50, 41p; 1000/100, 82p; 2000/25, 37p; 2000/50, 57p; 2000/100, £1.44; 2500/64, 77p; 2500/70, 98p; 5000/25, 62p; 5000/50, £1.10; 5000/100, £2.91; 10000/50, £2.40.

### ● ● ● COMPONENT DISCOUNTS

10% on orders for components for £5 or more.  
15% on orders for components for £15 or more.  
(No discount on nett items.)

### POSTAGE AND PACKING

Free on orders over £2. Please add 10p if orders under £2.

Overseas orders welcome: carriage and insurance charged at cost.

Send S.A.E. for latest list. All items in stock at time of going to press. Prices subject to alteration without notice.

## INTEGRATED CIRCUITS

### SIEMENS TTL

We stock full range of all types in stock for very wide range of applications. For full details, see our latest components list. Please send S.A.E.

**PLESSEY SL403D** 7.5ohms. £2.10 nett. Applications data 10p.

### S-DECs put an end to birds nesting

Components just plug in—saves time—allows re-use of components. S-Dec (70 points), £1.00

T-Dec may be temperature-cycled (208 points), £2.50 Also μ-Decs and IC carriers.

### INDICATOR LAMPS

NEON chrome bezel, round red NR/R, 24p; chrome bezel, round amber NR/A, 24p; chrome bezel, round clear NR/C, 24p. Neon, square red type LS5C/R, 18p; amber type LS5C/A, 18p; clear type LS5C/C, 18p. All above are for 240V mains operation. Filament types: 6V, 0.04A square red type LS5C/R-6V, 30p; 6V, 0.04A amber type LS5C/A-6V, 30p; 6V, 0.04A clear type LS5C/C-6V, 30p; 6V, 0.04A green type LS5C/G-6V, 30p; 12V, 0.04A LS5C/R-12V, 34p; 34V, 0.04A LS5C/R-28V, 45p.

## SIEMENS 5% TOLERANCE

### POLYCARBONATE CAPACITORS

250V up to 0.1mF: 100V 0.1mF and above  
0.01, 0.012, 0.015, 0.018, 0.022, 0.027 5p  
0.033, 0.039, 0.047, 0.056, 0.068, 0.082, 0.1, 0.12, 0.15, 0.18, 0.22 6p  
0.27, 0.33 8p

### DIN CONNECTORS

	plug	socket
Loudspeaker	2-pole	12p
Audio	3-pole	13p
Audio	4-pole	14p
Audio	5-pole 180deg.	15p
Audio	5-pole 240deg.	15p
Audio	6-pole	15p

## NOW READY—1971/72

### ELECTROVALUE CATALOGUE

64 pages plus covers. Thousands of items plus classified information and illustrations. Post free **10p**

**ELECTROVALUE** DEPT. P.E.871, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY  
Hours: 9-5.30, 1.0 p.m. Saturdays. Phone: Egham 5533 (STD 0784-3) Telex 264475

obtained with the extremely narrow beam of one degree obtained by this aerial system, using a phase-switched receiver.

An outstanding example of the grating technique is the crossed dish arrangement set up by Christiansen in Australia. This crossed grating consisted of two rows of 19ft dishes, one line north/south and the other east/west. There were 16 aerials in each arm. This system, which became known as the Chris Cross, presents an array of beams pointing skywards. Though it would show confused records of discrete sources, it is specially suitable for the purpose for which it was designed, that is, the detailed study of the sun.

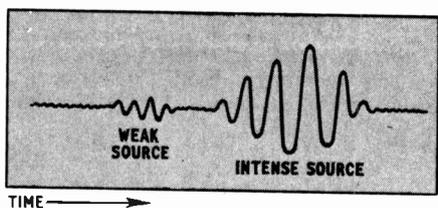


Fig. 3.2. Pattern recorded on phase-switching interferometer

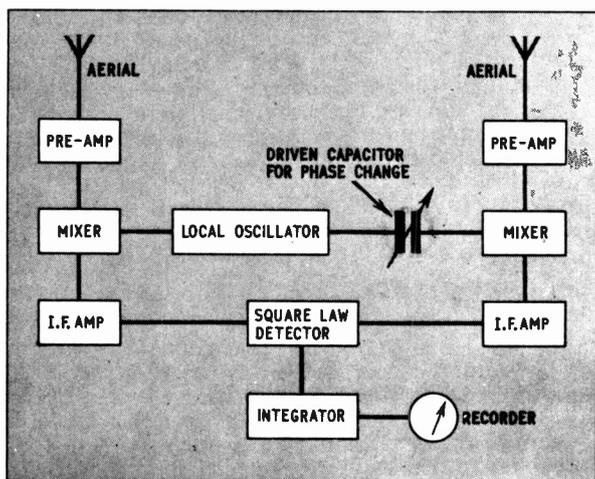


Fig. 3.3. Rotating lobe interferometer


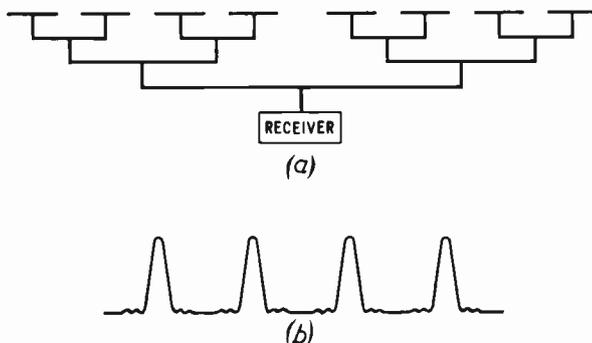


Fig. 3.4. A grating interferometer: (a) arrangement of aerials; (b) reception pattern

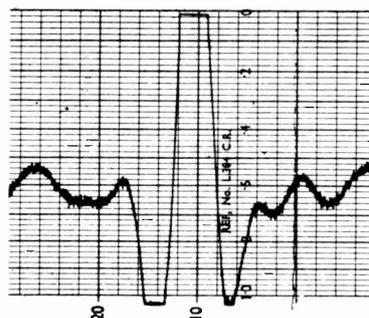

AERIAL BEAM WIDTH 1 DEGREE

Fig. 3.5. Recording of the sun obtained from the aerial system shown in Fig. 3.4 used in conjunction with a phase-switched receiver


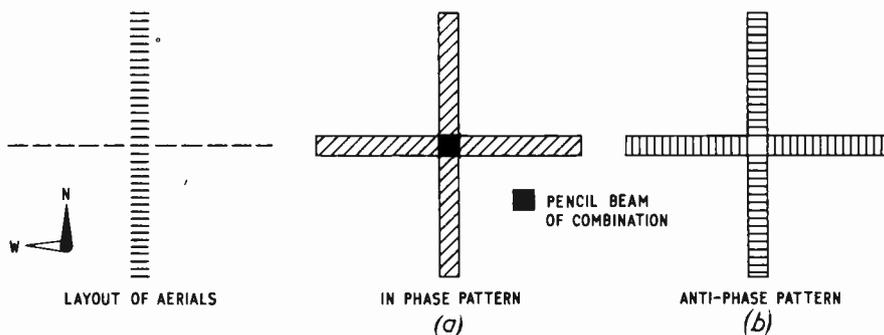
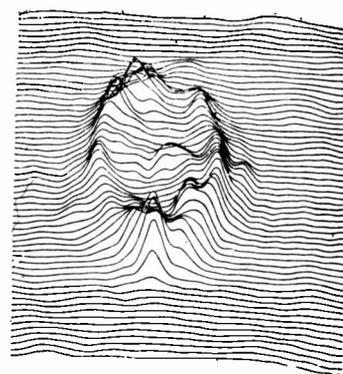


Fig. 3.6. Mills cross grating array

Another type of grating array is that at Nancay in France. It consists of 32 dishes in line and has a resolution of 4 minutes of arc at a frequency of 169MHz. It is the longest in the world, being 1/55km long.

The Mills Cross designed by B. Y. Mills of Australia has two arms which again are arranged north/south, east/west, and consists of rows of dipoles. The result is a pencil beam of small width at the centre; the pattern produced is seen in Fig. 3.6. The system has a very high resolving power, but is not so sensitive as other methods. It is, however, very valuable as a tool to study fine detail of the sky radiation.

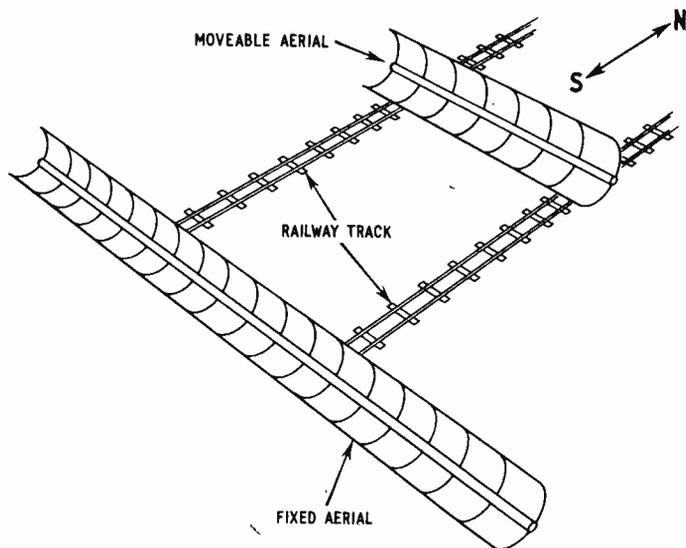

**Fig. 3.8.** The radio source Cassiopeia A. Brightness distribution at 140MHz (part of a survey by Ryle, Elsmore and Neville)

## APERTURE SYNTHESIS

Still another system for increasing resolving power is that of aperture synthesis. If an aerial is moved successively to a number of positions in a given area a detailed plot of that area can be made and detail observed that cannot be equalled by any other method. A number of ways are available to do this.

One system first used at Cambridge by Ryle consisted of a fixed base line of aerials and a smaller movable aerial that could take up any position in a rectangle. By observing at each position, a statistical evaluation could be made of the intensity of variations over the whole area. This was later improved by a system which had one fixed line of aerials and another which ran on a railway track at right angles to it. This is shown in Fig. 3.7.

The one-mile telescope with its three dishes is a further extension of the aperture synthesis technique pioneered by Ryle and his team. Strictly speaking, this should be called "supersynthesis", since its combination of aerials has so many variations of positions. The synthesised results are processed on a computer and fed into a special plotter which shows the intensity variation of the sources like a relief map. An example of this is shown in Fig. 3.8.

## FOUR MAIN TYPES OF RADIATION

The radiation that originates in the galaxy and the universe covers a wide range. However, so far as radio astronomy is concerned, the radiation that can be detected is somewhat restricted and depends very largely upon the site of the observatory, that is whether the radio telescope is on the earth or outside the earth.

The limitation so far as earth based observatories are concerned is the radio window. Within this part of the spectrum there are four main groups of radiation. Not all the stars or star systems that can be observed with optical telescopes have detectable radiation in the radio part of the spectrum, indeed many of them are seen and not heard. Conversely, many sources of radiation that are detected cannot be identified optically.

Much of the limitation is governed by the techniques that are at present available for radio-

astronomy. Within these limits the four main groups of radiation detected are: Synchrotron Radiation, Ionised Hydrogen Gas, Neutral Hydrogen Gas, and Discrete Sources.

## SYNCHROTRON RADIATION

The physics of synchrotron radiation is well understood and is at present applied in particle accelerators used in nuclear investigations. Synchrotron radiation is produced when an electron enters a magnetic field. The field compels the electron to spiral round the lines of force and the high speed that is imparted to it causes it to radiate in the metre-wave band. It is this kind of radiation that is detected in the Milky Way and in the halo of the galaxy. It also appears in the radiation from the planet Jupiter.

## IONISED HYDROGEN GAS

The emission from ionised hydrogen is also known as thermal emission. Near hot stars the hydrogen becomes ionised, that is the electron is ejected from the atom of hydrogen leaving the proton. Under these conditions there exist free electrons and protons. When an electron passes near a proton it is accelerated but may not be captured. The high acceleration of the electron causes the emission of radiation in the centimetre wavelength band. This type of radiation is abundant in the plane of the Milky Way.

## NEUTRAL HYDROGEN GAS

Neutral hydrogen appears in clouds of gas and it was predicted by Van de Hulst in 1944 that this gas would emit radiation at a wavelength of 21 centimetres. It is often referred to as the 21 centimetre line or H.I. line.

Van de Hulst made his prediction as a result of reading a paper by the American Amateur, Grote Reber, who had studied what he called cosmic noise. In 1951 Ewan in America proved the existence of the line. It can be detected by emission and absorption.

In emission the radiation is caused by the change of direction of the spin of the electron as it orbits

## HEARING AID AMPLIFIERS

(Ex behind ear deaf aids) 3 transistors on tiny P.C. board with volume control—whole thing only about half as big as Oxo cube. £17/6 or with sub-miniature microphone and L.S. attached, £3-50.



## MAINS OPERATED SOLENOIDS

Model 778—small but powerful 1 1/2 in. pull—approx. size 1 1/2 x 1 1/2 x 1 1/2 in. 60p.  
Model 400/1 1/2 in. pull. Size 2 1/2 x 2 x 1 1/2 in. 76p.  
Model TT10 1 1/2 in. pull. Size 3 x 2 1/2 x 2 1/2 in. £1-80 plus 20p post. and insurance.


## BEST QUALITY BRITISH MADE ELECTRICAL PLUGS AT APPROX. HALF PRICE

15 amp 3 pin, 10p each or ten for 90p; 5 amp 3 pin, 8p each or ten for 70p; 5 amp 2 pin, 5p each or ten for 45p.
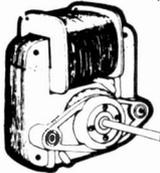
## DRILL CONTROLLER NEW IKW MODEL



Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1-50 plus 13p post. and insurance. Made up model also available, £2-25 plus 13p post & p.



## MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 50p. Postage 5p for first one then 5p for each one ordered.

## NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 8p each, 60p doz. Plastic push rod suitable for operating. 5p each, 45p doz.

## MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 4 way—1 pole, 12 way. All at 18p each. £1-80 dozen, your assortment.

## WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

## MICRO SWITCH

5 amp, changeover contacts, 8p each, £1 doz. 15 amp. On/off 10p each, 15 amp. changeover 15p each, 10 for £1-35.



## MAINS OPERATED CONTACTOR

220/240V, 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10A. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2 in. £1 each.



## PAPST MOTORS

Est. 1/40th h.p. Made for 110-120V working, but two of these work ideally together off our standard 240V mains. A really beautiful motor, extremely quiet running and reversible. £1-50 each. Postage one 23p, two 33p.



## EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, etc., it's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets, £2 plus 36p post and ins.



## MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6V, 9V, 12V for up to 300mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 85p, plus 18p postage.

## OUT OF SEASON BARGAIN TANGENTIAL HEATERS



Once again we are able to make a special bargain offer of these very popular heating units. Tangential heaters although brought out a few years ago are still the latest and best type as nothing has yet been made which could be called an improvement on them. The tangential unit is still the only one used in good quality heaters made by Hoover, G.E.C. and all the famous special bearings, the tangential impeller and a 2 section heater element which allows switching half and full heat in the case of the 2kW and one-third, two-thirds and full heat in the case of the 3kW. These heaters are also fitted with a safety cutout to cut the heaters should the impeller stop or the air flow be impeded. They are free-standing and need only the simplest of cases, even a wooden cabinet, for the simplest of kitchen cabinet. Lots of customers missed our special Summer Offer of these heaters last year so order early. 200/240 3kW model £2-50. 200/240 3kW model £3-50. Control switch heaters only 25p or two-heat, cold-blow and off 35p. Postage and insurance 33p on heaters.

## STANDARD WAFER SWITCHES



Standard size 1 1/2 wafer—silver-plated 5 amp contact, standard 1 in spindle 2 in long—with locking washer and nut.


No. of Poles	2 way	3 way	4 way	4 way 5 way	5 way 6 way	8 way 9 way	10 way 12 way
1 pole	40p	40p	40p	40p	40p	40p	40p
2 poles	40p	40p	40p	40p	40p	40p	70p
3 poles	40p	40p	40p	40p	70p	70p	85p
4 poles	40p	40p	40p	70p	70p	70p	£1-20
5 poles	40p	40p	70p	70p	85p	85p	£1-45
6 poles	40p	70p	70p	70p	85p	85p	£1-70
7 poles	70p	70p	70p	85p	£1-20	£1-20	£1-85
8 poles	70p	70p	70p	85p	£1-20	£1-20	£2-20
9 poles	70p	70p	85p	85p	£1-45	£1-45	£2-45
10 poles	70p	70p	85p	£1-20	£1-45	£1-45	£2-70
11 poles	70p	85p	85p	£1-20	£1-70	£1-70	£2-95
12 poles	70p	85p	85p	£1-20	£1-70	£1-70	£3-20

## AMPLIFIER MAINS TRANSFORMER

50V 1 1/2 amp. Upright mounting with fixing brackets and metal shrouds to contain magnetic field, 30 v secondary, tapped 110V, 117V, 210V, 230V and 250V. Two secondaries, one 30V 1 1/2 amp, other 6V 1 amp for pilot light, etc. £1-95, plus postage 30p.

## THIS MONTH'S SNIP

### BATTERY CONDITION TESTER

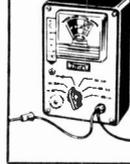

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese-nickel-silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2 x 6 1/2 x 2 in with leads and prods. Price £1-75 plus 20p postage.

### COMPUTER TAPE


2,400ft of the best magnetic tape money can buy. Almost unbreakable and on a metal computer spool. Users have claimed successful results with video as well as sound recordings. 1" wide £1, 1/2" 88p, 1" 75p. P. & P. 33p extra. Spare spools 50p each. Cassette to hold spool 50p each. No extra postage if ordered with tape, otherwise 30p extra.

### CAPACITOR DISCHARGE IGNITION SYSTEM

Well proved that it helps starting and increases petrol economy. Also increases acceleration but saves contact wear. For details see Practical Wireless June. Gives optional capacitor or standard ignition at the flick of a switch. Price £4-85.
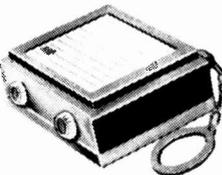
### MICROSONIC KEYCHAIN RADIO

7 transistor Keychain Radio in very pretty case, size 2 1/2 x 2 1/2 x 1 1/2 in.—complete with soft leather zippered bag. 7 transistor, ferrite rod. Loudspeaker. In transit from the East these sets suffered corrosion as the batteries were left in them but when this corrosion is cleared away they should work—offered without guarantee except that they are new. Price only £1-25 less batteries, plus 13p post, 6 for £7 post free. Pair of rechargeable batteries and charger 85p.



### MAINS RELAY BARGAIN

Special this month are some single, double and treble pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V a.c. (Good British Make. Unused. Size approx. 1 1/2 x 1 in. Open construction. Single pole, 25p each, 10 for £2-25. Double pole, 32p each, 10 for £2-90. Treble pole, 40p each, 10 for £3-60.

### 4 AMP VARIAC CONTROLLERS

With this you can vary the voltage applied to your circuit from zero to full mains without generating undue heat. One obvious application therefore is to dim lighting. Ex equipment but little used—as good as new offered at approx. half price. £5 plus 75p post and ins.

### OVEN THERMOMETER WITH ALARM

Basically this is a thermometer which is calibrated between 200°C and 900°C using a sensor on a flexible lead. The second feature, however, is an alarm which can be set anywhere within the temperature range. When the temperature is reached a buzzer sounds. Presumably the buzzer could be replaced by a relay or contactor to work another device. Limited quantity only of these units, price £3-50, includes thermometer—scale—sensor and buzzer.

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semiconductor add 5p post. Over £1 post free. S.A.E. with inquiries please.

## ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only £2, less than the value of the clock alone—post and insurance 14p.



## P.W. TREASURE TRACER

As described in August issue of Practical Wireless  
Send today for price list of parts

## TELESCOPIC AERIAL

For portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47 in. Hole in bottom for 6BA screw. 38p KNUCKLED MODEL FOR F.M. 50p.

## QUICK CUPPA

Mini Immersion Heater, 350W, 200/240V. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1-25, post and insurance 14p. Jug heater £1-50 plus 14p P. & P.



## THYRISTOR LIGHT DIMMERS

Will dim incandescent lighting up to 600W from full brilliance to out. Assembles and wired ready to install, £2.



## 12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 n/f/d smoothing. Price £1-50 plus 20p P. & P.




## REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types:

Miniature. 1 in long x approximately 1/4 in diameter. Will make and break up to 1A up to 300 volts. Price 13p each, £1-20 dozen.  
Standard. 2 in. long x 3/16 in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 10p each, 90p per dozen.  
Flat. Flat type, 2 in long, just over 1/16 in. thick approximately 1 in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 30p each, £2 per dozen.  
Small ceramic magnets to operate these reed switches 8p each, 80p per dozen.
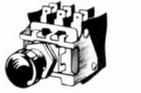
## PUSH BUTTON CHANGEOVER SWITCHES

This is a Honeywell micro switch mounted on a metal frame with spring loaded plunger to operate. Panel fixing by single 2 in hole. Single Changeover switch 25p each or ten for £2-25, 2 changeover switches operated by single plunger, 35p each or ten for £3-15, 3 changeover switches 45p each or ten for £4-05.



Meter Box. Designed to take 3 1/2 in flush mounting meter. This has a 2 1/2 in diameter hole with 3 meter fixing holes. Overall size of box 4 x 4 x 2 1/2 in deep, hinged to a metal base 2 1/2 in by 4 1/2 in by 1 in deep. Price 50p.

Pilot Bulbs. 6-8 Volts 15 amp tubular MES British made good quality. 1 dozen in a box. 25p per box.

5 Amp Connector Strip. This is the normal type of connector strip. Twelve connectors with grub screws mounted in a line and moulded in polythene. 15p each, £1-50 per dozen.

24V Buzzer. Made by G.E.C. in brown heavy bakelite case, these work off a.c. mains through step down transformer. Price 40p each.

9 Pin Plug and Socket. Suitable for connecting multicore flex to equipment. Socket size approx. 1 in diameter. Plug size 9/10 in diameter with flex entry. 25p pair.

A New Service to Readers. A bulletin bringing news of new lines, special snips and "too good to advertise" lines will be posted to subscribers during first week of each month. The bulletin will be called "Advance Advert News" and the Subscription is 60p per year. Subscribers will also receive our completed 1971 catalogue when this is published.

## J. BULL (ELECTRICAL) LTD.

Dept P.E., 7 Park Street, Croydon CRO 1YD  
Callers to Electronics (Croydon) Ltd., 102/3 Tamworth Rd., Croydon

# AT HOME SOLDERING?

Our miniature irons are used all over the world in that most exacting market—the modern electronics industry, the rapidly developing technology of which has made possible the enormous growth of activities available to the technical hobbyist.

He now also requires equipment to the highest commercial standards. Like our soldering irons, for example.

Look at the ADAMIN Model 15. If there is a smaller iron for mains use, we haven't seen it. It weighs a mere ½oz (less flex) and is about 7 inches long.

But it has a big performance. Used with interchangeable bits from 3/32in to 3/16in it is suitable for all work, from Hearing Aids to Colour Television.

Use the mains version at home or clip the 12 volt model to the car battery or 12 volt power unit (consumption only 1.25A).

Send for HOBBY PACK 37 consisting of Model 15 iron with four bits, 3/32in, 3/16in, 1/8in, 3/16in and tube of Bit Lubricant. State voltage required—12V or 220/240V.

**PRICE: HOBBY PACK £2.30**  
**P. & P. FREE**

## LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon CR9 2LL  
Telephone 01-688 8589 and 4559



# LIND-AIR AUDIO

## GARRARD HI-FI TURNTABLES



8P25 Mk. III	£11.97
Base and cover for above	£4.95
AP76	£19.50
8L72B	£24.97
8L75B	£28.35
8L75B	£39.45
Base and cover for above	£8.97
401	£31.50
P. & P. Decks, 62½p; Base and Cover, 30p; Deck/Base/Cover, 87½p.	

### THIS MONTH'S SPECIAL OFFERS!

8P25 Mk. III with base	£13.98
	P. & P. 75p.
8P25 Mk. III with Sonotone	£16.75
9TAHCD cartridge and base	P. & P. 75p.


## VHF AIRCRAFT BAND CONVERTER Model VHF.105

When placed within 1in. of a MW band radio full coverage of VHF Aircraft Band 110-135 Mc/s can be obtained. All transistor, 9V battery operation. Fully tunable 18½in x 7 section telescopic aerial. Size 4in x 2½in x 1½in.



**OUR PRICE**  
£3.80. P. & P. 20p.

## SINCLAIR PROJECT 60

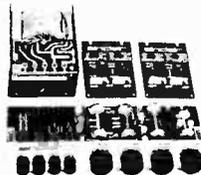

An attractive alternative for the enthusiast prepared to assemble these excellent modules to make a stereo assembly. 2.30 24W Power Amplifier £4.47! (2 required). Stereo Sixty Control/Pre-amplifier £9.97! P2.5 Power Supply Unit £4.97!

**SINCLAIR PROJECT 60.** Package deal price £19.95. P. & P. 62½p. Project 60 is supplied complete with instruction manual and templates for plinth mounting.

## SINCLAIR IC10 INTEGRATED CIRCUIT

10W Amplifier. Size only 1in x 0.4in x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years.

**ONLY £2.97!** P. & P. 8p.

**SINCLAIR IC10** with special transformer to operate from a.c. mains 230/250V. Output 13W at 0.5 amp. £3.98. P. & P. 10p.

All mail orders to: Dept. PE8  
**53 TOTTENHAM COURT ROAD  
LONDON, W.1. Tel. 01-637 1601**

Callers welcome also at:  
18-19 Tottenham Court Road  
London, W.1. Tel. 01-580 2255  
25 Tottenham Court Road  
London, W.1. Tel. 01-580 7679  
149 Fleet St., E.C.4. Tel. 01-353 1419  
94-96 Upper Parliament Street  
Nottingham. Tel. 40403



No fiddly tape threading, just snap in a compact cassette. Amazing performance from all transistorised circuit. Auto level control. Luxurious wood grain and black finish. Runs on 4-U11 batteries. Complete with remote control mike, stand and strap. 90 min. play cassette 65p extra (\*Rec. price of ident. mod. with case £29.40).

## E.M.I. LOUDSPEAKERS

**MODEL 450.** 13½in x 8in elliptical with twin tweeters. 8Ω impedance. 10 watts. Brand new, guaranteed.

Lind Air Price  
**£3.97!**  
P. & P. 22½p each.

**MODEL 150.** 13½in x 8in elliptical, 3 and 15Ω impedance. 10 watts.


Lind Air Price  
**£2.97!**  
P. & P. 22½p each.

## UNILEX AUDIO MODULES



Build a stereo amplifier for as little as £15.00. Send 25p for Mullard "Do It Yourself Stereo" booklet. All items in stock.

## S-DeC BREADBOARD

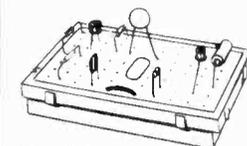

British Made  
Solderless breadboard panels, for fast reliable component connections.

Single DeCs. One S-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DeC" giving construction details for a variety of circuits. £1. P. & P. 17½p.  
4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. £3.95. P. & P. 17½p.  
T-DeC KIT £2.50. P. & P. 17½p.  
S-DeC STOR £2.50. P. & P. 17½p.

## HI-FI CATALOGUE

100 pages fully illustrated with 8 page P.A. section. All leading makes and accessories plus details of Budget Stereo systems. 25p. P. & P. 5p.



round the proton. The action of the reversal of the spin causes the radiation. Because it emits at the single frequency it differs from the other types of radiation which can cover a broad band. Because it is singular in this effect it is possible to detect the radiation in other sources.

If a cloud of neutral hydrogen lies between the observer and a source of radiation, and is sufficiently thick optically, then the hydrogen line will be absorbed. The structure of the galaxy has been plotted using this method of detection of spectral lines. The comparison type of receiver is used for this purpose and is shown in Fig. 3.9. The kind of recording which is made is also shown.

### DISCRETE SOURCES

The discrete sources of radiation emit over a wide range of frequencies. Many of these sources have been identified and much is known about them. The Crab Nebula was one of the first to be identified.

A great deal of continuous observation has been given to this object which was the star which exploded some nine hundred years ago as observed by the Chinese astronomers. It is in our own galaxy

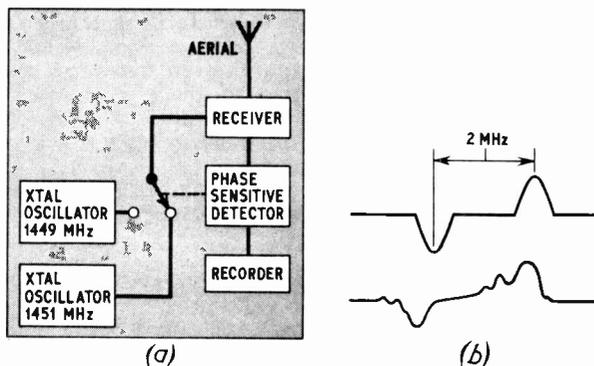


Fig. 3.9. The detection of spectral lines: (a) the switched comparison receiver; (b) typical outputs from receiver

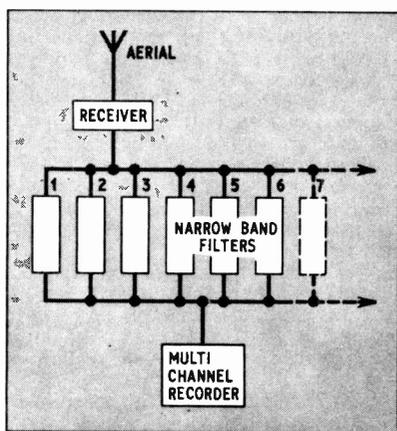


Fig. 3.10. A multi-channel spectrometer

and is about 4,100 light years away from us. This means that the actual explosion took place over 5,000 years ago. It has been a source of great power, much of which was not explainable by ordinary theories.

Now, since certain polarisation measurements have been made, and pulsar investigations carried out, a number of puzzling features have been resolved. Other sources of a similar nature have been mentioned earlier in these articles. Many sources have been found in the galaxy, but many more exist beyond it since they appear to be scattered all over the sky. Some of these sources may be exploding star (or Nova) remnants; some are quasars, and some will be pulsars.

### RADIO SPECTROMETERS

A number of special lines have been discovered at various frequencies, such as the OH line (a hydroxyl radical) and, the latest to be recognised, those of ammonia and formaldehyde.

The instruments used for these measurements are called radio spectrometers. Such instruments fall into two types: one has a number of channels each separated by narrow band filters, and the other a system where the frequency is changed rapidly over a band of frequencies—this is known as the swept frequency spectrometer.

As these spectral lines are very narrow, the spectrum covering as little as 2MHz, the hydrogen line can be used to measure the speed at which the parts of the galaxy are moving. It is therefore an important tool with which to explore the universe.

The first type of radio spectrometer is shown in block diagram Fig. 3.10. Spectrometers are used for other purposes, for example, the study of the sun over a wide frequency range. The swept frequency spectrometer has been used for the study of decimetre radiation from Jupiter. In this case the range of operation was from 10MHz to 42MHz.

### OCCULTATION

So far, apparatus has been described for the techniques employed in radio astronomy, and perhaps these various systems might be called the tools. There are however, a number of "tricks" by which the radiations can be studied. For example, in June each year the Crab Nebula passes (apparently) behind the sun. This fact, and also because the level of radiation from the Crab is very high, is used to study the corona of the sun.

The "radio" sun is very much more extended than the "face" that can be seen and which is called the photosphere. The sun has a corona and this extends way beyond that which can normally only be seen at the time of an eclipse. Radio astronomers however can study this atmosphere of the sun at any time.

When the radio waves from the Crab are behind the corona a reduction of the intensity of the Crab radiation is noted. This reduction continues until the Crab is blotted out completely, but it re-appears as it passes out the other side. By this method the density of the corona at various frequencies can be readily determined. This, incidentally, is another project that amateurs can attempt with modest apparatus.

Another type of occultation measurement is to use the moon and planets. As the moon or planet passes

in front of a radio source, the power of that source is reduced or sometimes blotted out altogether, depending on its size. Predictions of sources to be affected is circulated to those concerned by the Royal Observatory, and regular observations are carried out at various frequencies.

## POLARIMETERS

Generally, the radio waves are received in one plane of propagation, but may well be randomly polarised. To examine this feature, polarimeters are used. Polarimeters consist of aerials which are crossed or arranged in the form of a square with the sections arranged in phase combinations such that the direction of rotation can be detected.

The helical aerial is very useful in this connection, for it can be arranged to give right or left handed polarisation. A system containing helices of both right and left hand polar diagrams can collect a large amount of data. The evaluation is quite a difficult task, for the radiation is rarely consistently polarised in one sense or the other and is more generally elliptical than circular.

## RADAR ASTRONOMY

Radar astronomy is a special branch and has its own techniques. The equipment involved is necessarily complex and costly. It is certainly beyond the resources of private individuals. As with any form of radio transmission, a licence is required to operate radar equipment. Participation in radar astronomy is thus, automatically, the prerogative of certain scientific or research establishments.

Contributions made by radar techniques are of great importance, as the following few examples will indicate. Signals bounced off the moon gave a clue to surface conditions before unmanned and manned landings. Venus has been studied and at last an agreed period of rotation has now been arrived at. Radar has been used to study the sun, though of course, enormous powers are necessary for this work. Active studies of meteors have been carried out by radar methods and represent an enormous amount of pioneering work which began in the early days of Jodrell Bank and still continues. At Sheffield the study of meteors with the aid of radar has made great progress under Dr Kaiser. The temperature of the planets and the moon has been closely studied by radar methods.

The next two articles will deal with the equipment needed to set up a small radio astronomy observatory. A project related to solar observations will be detailed and the methods of recording the results explained.

## BACK NUMBERS

We very much regret that Back Numbers of PRACTICAL ELECTRONICS can no longer be supplied. Consequently, it is now more important than ever to place an advanced order with your newsagent to make sure of getting your copy.

Alternatively by taking out a subscription order your own personal copy will be sent direct by post to your permanent address anywhere in the world. Further details are given on the "Contents" page.



# BOOK REVIEWS

## TELEVISION SERVICING HANDBOOK (3rd edition)

By Gordon J. King

Published by Newnes-Butterworth

357 pages, 10in × 6½in. Price £3.80

THE most significant difference in this the third edition, compared with earlier editions, is the inclusion of colour television techniques and problems. Dual standard and 625-line only sets are also included.

Since all these types have shown how transistors and integrated circuits can be usefully employed, the last chapter is a very good treatise on methods adopted commercially, and shows the significant differences from valve circuits. The part on integrated circuits is naturally very short because, at the time of writing the book, the applications to television were in the experimental stages.

My only other comment on an otherwise excellently written book is that perhaps the chapter headings are a bit misleading, because long circuit descriptions and functions are given before fault finding methods. The amount of space so devoted is sometimes unrelated to the headings and cross reference to other chapters often becomes necessary.

The quality of paper and printing is excellent, as is necessary in the accurate reproduction of the pictorial matter taken directly from the screen.

M.A.C.

## INTRODUCTION TO A.C. MACHINES CAPACITANCE AND CAPACITORS RESISTANCE AND OHM'S LAW INTRODUCTION TO D.C. MACHINES

Four programmed textbooks prepared by Educational Systems Ltd.

Published by Newnes-Butterworths.

Each book has 183 pages, 8½in × 5½in. Price 75p

THESE are four titles from a series of ten uniform textbooks designed for class or private tuition in Engineering fundamentals, both practical and theoretical.

Each book is broken up in a number of sections, or programmes. In studying these sections the only requirement of the student is a pencil and paper with which to record his answers to the questions set out on each page.

All instruction is very well illustrated and contributes in no small measure to the effectiveness of this form of tuition.

As the student progresses through the book he is continually examined on his comprehension of the subject matter. Each section has revision notes and is completed with a short test.

Introduction to D.C. Machines covers generator principles, commutator action, the magnetic circuit, windings and motor principles.

Capacitance and Capacitors deals with atomic charge concepts and electrostatics. A final section of practical capacitors is instructive.

Resistance and Ohm's Law is concerned with the measurement of electricity in series and parallel circuits.

Introduction to A.C. Machines, proceeds from simple a.c. generation through three phase circuits, examines rotors and stator windings and is completed with sections on synchronous and induction motors.

G.G.

## TRANSISTORS

**NEW LIST—NEW PRICES**  
SEND FOR FREE COPY TODAY

Brand New Fully Guaranteed

2N404	20p	BC107	12p	BYZ13	25p
2N406	15p	BC108	12p	BYZ15	20p
2N407	15p	BC109	12p	GET880	37p
2N706	10p	BC113	15p	MAT100	25p
2N706A	12p	BC114	15p	MAT110	30p
2N930	15p	BC115	15p	MAT120	25p
2N1131	25p	BC116	25p	MAT121	30p
2N1132	25p	BC116A	30p	MJ2801L1	37
2N1302	20p	BC118	25p	MJ2901E	25
2N1303	20p	BC119	35p	MJ3270	25
2N1304	25p	BC134	25p	MJE520	87
2N1305	25p	BC135	20p	MJE2955	
2N1306	25p	BC136	22p	MJE3137	
2N1307	25p	BC137	25p	MJE3055	87
2N1308	25p	BC138	25p	MFP102	42p
2N1309	25p	BC147	17p	MFP103	35p
2N1613	22p	BC148	12p	MFP104	37p
2N1711	25p	BC149	20p	MFP105	40p
2N2147	75p	BC154	37p	NK7217	40p
2N2160	60p	BC157	20p	NK7272	20p
2N2168	20p	BC158	17p	NKT403	75p
2N2219	20p	BC159	20p	NKT404	82p
2N2222	20p	BC160	15p	OAS	20p
2N2222A25p		BC177	25p	OA9	10p
2N2369	20p	BC178	25p	OA10	25p
2N2444	35p	BC179	27p	OA47	10p
2N2446	50p	BC182L	12p	OA70	10p
2N2904	20p	BC183	12p	OA79	10p
2N2904A25p		BC184L	15p	OA79	10p
2N2905	25p	BC212	12p	OA81	10p
2N2906	20p	BCY30	25p	OA85	12p
2N2906A25p		BCY31	30p	OA90	10p
2N2907	23p	BCY32	50p	OA91	7p
2N2926	10p	BCY33	25p	OA95	7p
2N3011	25p	BCY34	20p	OA90	7p
2N3054	20p	BCY35	20p	OA202	10p
2N3054A	20p	BCY39	85p	OC16	50p
2N3055	75p	BCY40	50p	OC20	97p
2N3525		BCY58	25p	OC22	50p
	£1.10	BCY69	25p	OC23	60p
2N3702	10p	BCY70	15p	OC24	60p
2N3703	10p	BCY71	20p	OC25	37p
2N3704	15p	BCY72	15p	OC43	40p
2N3705	15p	BCY78	30p	OC28	60p
2N3707	15p	BCY79	30p	OC29	60p
2N3709	10p	BCZ10	35p	OC35	50p
2N3710	10p	BCZ11	45p	OC36	60p
2N3819	35p	BD112	50p	OC41	25p
2N3820	60p	BD121	65p	OC42	30p
2N4053	15p	BD123	80p	OC43	40p
2N4054	75p	BD124	75p	OC44	40p
2N5457	25p	BD125	50p	OC45	15p
2N5458	37p	BD131	75p	OC70	12p
2N5459	50p	BD132	85p	OC71	15p
2S301	50p	BD153	62p	OC72	25p
2S302	50p	BD156	57p	OC73	30p
2S303	60p	BDY10E1	25	OC74	30p
2S304	75p	BDY11E1	63	OC75	25p
40250	50p	BDY12E1	25	OC76	25p
40361	50p	BDY18E1	75	OC77	40p
40362	55p	BDY19E1	87	OC81	25p
AA Y30	10p	BDY6E1	25	OC82	25p
AA Y42	15p	BDY6E2	10p	OC83	25p
AA Z13	12p	BF115	25p	OC89	25p
AA Z14	12p	BF116	25p	OC91	25p
AC107	37p	BF154	40p	OC140	37p
AC126	25p	BF158	30p	OC141	62p
AC127	25p	BF159	60p	OC170	25p
AC128	25p	BF167	25p	OC171	30p
AC127E	25p	BF170	35p	OC200	40p
AC187	40p	BF173	30p	OC201	70p
AC188	30p	BF177	40p	OC202	80p
ACY17	30p	BF178	25p	OC203	40p
ACY18	25p	BF179	40p	OC204	40p
ACY19	25p	BF180	35p	OC205	75p
ACY20	20p	BF181	35p	OC206	80p
ACY21	20p	BF182	30p	OC207	90p
ACY22	10p	BF186	25p	OCY17	97p
ACY39	50p	BF185	20p	OIP12	50p
AD140	50p	BF194	17p	ORP60	40p
AD149	50p	BF196	15p	ORP61	42p
AD161	37p	BF197	15p	TRP29A	50p
AD162	37p	BF200	37p	TF30A	60p
AF114	25p	BF227	37p	TF30B	60p
AF115	25p	BFX13	25p	TF31A	62p
AF116	25p	BFX29	25p	TF32A	75p
AF117	25p	BFX30	25p	TF33A	
AF118	62p	BFX37	32p	TF34A	£1.00
AF124	25p	BFX84	25p	TF843	25p
AF135	20p	BFX85	35p	TF869	25p
AF126	17p	BFX96	25p	TF861	25p
AF127	17p	BFX87	25p	TF862	27p
AF139	30p	BFX88	20p	ZTX107	15p
AF178	47p	BFY18	30p	ZTX108	15p
AF179	65p	BFY50	22p	ZTX300	12p
AF180	52p	BFY51	20p	ZTX301	15p
AF181	42p	BFY52	22p	ZTX302	20p
AF186	40p	BFY56	17p	ZTX303	20p
AF239	40p	BFY90	65p	ZTX304	25p
AS Y26	25p	B8X20	17p	ZTX500	20p
AS Y27	32p	B8X21	20p	ZTX501	25p
AS Y28	25p	B8X76	15p	ZTX502	25p
AS Y29	30p	B8Y95	15p	ZTX503	20p
AS Y67	47p	BSY05	11p	ZTX504	40p
AS Z21	42p	BY100	20p	ZTX531	30p
BA115	7p	BY126	15p		
BA164	10p	BY127	20p	DISCOUNTS	
BA X13	6p	BY182	85p	10% 12+	
BA X16	7p	BYZ10	40p	15% 25+	
BA Y31	7p	BYZ11	35p	20% 100+	
BA Y38	17p	BYZ12	30p	ANY ONE TYPE	

Any one type

# HENRY'S LOW COST INTEGRATED CIRCUITS

**WE OFFER FROM STOCK AN EXCLUSIVE RANGE OF BRAND NEW FULL SPECIFICATION LOW COST TTL 7400 RANGE OF INTEGRATED CIRCUITS**

Part No.	Ceramic	Description	Price and Qty.
7400		Quadraple 2-input NAND Gate	1-24 25 89 100 250+
7401		Quadraple 2-input Positive NAND Gate (with open collector output)	23p 20p 15p 13p
7402		Quadraple 2-input Positive NAND Gate	23p 20p 15p 13p
7403		Quadraple 2-input Positive NAND Gates (with open collector output)	23p 20p 15p 13p
7404		Hex Inverters	23p 20p 15p 13p
7410		Triple 3-input Positive NAND Gates	23p 20p 15p 13p
7413		Dual 4-input Schmitt Trigger	35p 32p 29p 25p
7420		Dual 4-input Positive NAND Gates	23p 20p 15p 13p
7430		8-input Positive NAND Gates	23p 20p 15p 13p
7440		Dual 4-input Positive NAND Buffers	23p 20p 15p 13p
7441		BCD to decimal nixie driver	87p 77p 66p 60p
7442		BCD to decimal decoder (4-10 lines, 1 of 10)	87p 77p 66p 60p
7447		BCD Seven-Segment Decoder/Drivers (15-V Outputs)	£1.40 £1.30 £1.20 £1.05
7450		Expandable dual 2-input AND-OR-INVERT	23p 20p 15p 13p
7451		Dual 2-wide 2-input AND-OR-INVERT GATES	23p 20p 15p 13p
7453		Quad 2-input Expandable AND-OR-INVERT	23p 20p 15p 13p
7454		4-wide 2-input AND-OR-INVERT Gates	23p 20p 15p 12p
7480		Dual 4-input Expander	23p 20p 15p 13p
7472		Single-phase J-K Flip-Flop	35p 32p 29p 25p
7473		Master-slave J-K Flip-Flop	41p 40p 37p 33p
7474		Dual Master slave J-K Flip-Flop	43p 40p 37p 33p
7475		Dual 0 type Flip-Flop	47p 45p 43p 40p
7476		Quad Latch	47p 45p 43p 40p
7478		Dual J-K with pre-set and clear	87p 77p 67p 60p
7481		16-bit read/write memory	£1.35 £1.25 £1.15 £1.00
7482		2-bit Binary Full Adders	£1.30 £1.20 £1.00 85p
7483		Quad Full Adder	87p 77p 67p 60p
7486		Quad 2 input Exclusive OR Gates	80p 70p 60p 50p
7489		BCD decade counter	87p 77p 67p 60p
7491		8-bit Shift Registers	£1.21 £1.00 87p 75p
7492		Divide-by-Twelve Counters	87p 77p 67p 60p
7493		4-bit Binary Counters	87p 77p 67p 60p
7494		Dual entry 4-bit shift register	87p 77p 67p 60p
7495		4-bit up-down shift register	87p 77p 67p 60p
7496		5-bit Parallel in parallel out Shift Register	87p 77p 67p 60p
74100		8-bit Bistable Latches	£1.75 £1.65 £1.55 £1.35
74118		Hex Set-Reset Latches	£1.30 £1.20 £1.00 85p
74121		Monostable Multivibrators	87p 77p 67p 60p
74141		BCD-to-Decimal Decoder/Driver	87p 77p 67p 60p
74145		BCD-to-Decimal Decoder/Drivers	£1.80 £1.70 £1.60 £1.50
74151		4-bit Data Selectors (with Strobes)	£1.40 £1.30 £1.20 £1.05
74153		Dual 4-Line-to-1-Line Data Selectors/Multiplexers	£1.40 £1.30 £1.20 £1.05
74181		Binary Counter reversible	£3.50 £3.25 £3.00 £2.50

Devices may be mixed to quality for quantity price.  
Data available for above series in booklet form, price 10p. (Ref. No. 30).  
Larger quantity prices Extn. 4. Dual Inline 14 Pin Rocket 30p each 16 Pin 35p each.

## SEMI-CONDUCTORS

**LOOK AT THESE PRICES FOR QUANTITIES FROM STOCK**

AF114	Mullard 25p	25 + 20p 100 + 17p 500 + 15p	AF115	Mullard 25p	25 + 20p 100 + 17p 500 + 15p
AF116	Mullard 25p	25 + 20p 100 + 17p 500 + 15p	AF117	Mullard 25p	25 + 20p 100 + 17p 500 + 15p
2N3055	75p	Mullard 115watt Silicon Power	2N3819	Texas 35p	25 + 30p 100 + 25p 500 + 20p 1000 + 18p
BFY90	65p	100 MC/S Motorola Unionjunction	2N2646	40p	25 + 35p 100 + 30p 500 + 25p
AF139	30p	Siemens V.H.F.	AF186	40p	Mullard V.H.F. Mullard 25 + 35p 100 + 30p 500 + 25p
OC170	Mullard 25p	25 + 21p 100 + 17p 500 + 15p	BYZ13	25p	Mullard 6a 200v 25 + 20p 100 + 17p 500 + 15p
OC171	Mullard 30p	25 + 27p 100 + 22p	BC107, BC108, BC109	12p each	I.T.T. Planars 25 + 11p 100 + 10p 500 + 8p
BY127	Mullard 20p	1000V 1 amp Plastic	OC71	Mullard 15p	25 + 12p 100 + 10p 500 + 8p
BC113	SGS 15p	25 + 13p 100 + 11p 500 + 9p	OC71	Mullard 15p	25 + 12p 100 + 10p 500 + 8p
OA202	10p	SILICON Diodes	OC72	Mullard 62p	Mullard Power 25 + 55p 100 + 50p 500 + 42p
OC42	Mullard 30p	25 + 25p 100 + 23p 500 + 21p 1000 + 18p	OC71	Mullard 15p	25 + 12p 100 + 10p 500 + 8p
OC45	Mullard 15p	25 + 13p 100 + 12p 500 + 10p 1000 + 8p	ORP12	Mullard 50p	25 + 45p 100 + 42p 500 + 40p
OC75	Mullard 25p	25 + 21p 100 + 17p 500 + 15p 1000 + 13p	2N930	25p	25 + 23p 100 + 20p 500 + 17p 1000 + 15p
OC20	97p	Mullard 100v 25 + 85p 100 + 80p 500 + 75p	OC72	Mullard 25p	25 + 20p 100 + 17p 500 + 15p 1000 + 13p
OC44	Mullard 17p	25 + 15p 100 + 13p 500 + 11p 1000 + 10p	OC84	25p	25 + 20p 100 + 17p 500 + 15p 1000 + 13p
OC139	Mullard 25p	25 + 20p 100 + 17p 500 + 15p	AF239	42p	25 + 35p 100 + 30p 500 + 25p 1000 + 20p
OC81	Mullard 25p	25 + 20p 100 + 17p 500 + 15p			

**HENRY'S SEMI-CONDUCTOR DEPARTMENT**  
303 EDGWARE RD., LONDON, W2. TEL: 01-723 1008/9  
RADIO LTD. CALLERS 356 EDGWARE ROAD W2.

**NEW LIST - NEW PRICES**  
1371 TRANSISTOR LIST 1500+  
SEND FOR YOUR FREE COPY TODAY

**DISCOUNTS**  
10% 12+  
15% 25+  
20% 100+  
ANY ONE TYPE

We respectfully ask customers to include a minimum £1.00 per order, it helps to plan ahead & saves postage as well.

# G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

## VEROBOARD

2 1/2in x 1in x 0.15in 6p 5in x 3 1/2in x 0.15in 28p 3 1/2in x 3 1/2in x 0.1in 24p  
 3 1/2in x 2 1/2in x 0.15in 16p 17in x 2 1/2in x 0.15in 55p 5in x 2 1/2in x 0.1in 23p  
 3 1/2in x 3 1/2in x 0.15in 20p 17in x 3 1/2in x 0.15in 74p 5in x 3 1/2in x 0.1in 28p  
 5in x 2 1/2in x 0.15in 20p 3 1/2in x 2 1/2in x 0.1in 21p  
 Spot Face Cutter 38p. Pin Insert Tool 40p. Terminal Pins (0-1 or 0-15) 36 for 18p. Special Offer Pack consisting of 5 2 1/2in x 1in boards and a Spot Face Cutter—50p.

## RECORD PLAYER CARTRIDGES. Well below normal prices!

G90 Magnetic Stereo Cartridges, Diamond Needle, 6mV output, £4. ACOS GP 67/2 (Mono, Crystal) 75p. ACOS GP 91/3 (Compatible, Crystal) £1. ACOS GP 93/1 (Stereo, Crystal, Sapphire) £1.25. ACOS GP 93/1D (Stereo, Crystal, Diamond) £1.63. ACOS GP 94/1 (Stereo, Ceramic, Sapphire) £1.50. ACOS GP 94/1D (Stereo, Ceramic, Diamond) £1.88. ACOS GP 95/1 (Stereo, Crystal with two L.P./Stereo needles) £1.25.

**TRANSISTORISED FLUORESCENT LIGHTS, 12 volt. All with reversed polarity protection. 8 watt type with reflector suitable for tents, etc. £3. Postage/Packing 25p. 15 watt type, batten fitting for caravans £4. Postage/Packing 25p. 13 watt type, batten with switch. 22in x 2in. x 1in £5. Postage/Packing 25p. THESE CAN BE SENT ON APPROVAL AGAINST FULL PAYMENT.**

## MULLARD POLYESTER CONDENSERS

1,000pF, 1,200pF, 1,500pF, 1,800pF, 2,200pF, 15p per dozen (all 400V working). 0.15µF, 0.22µF, 0.27µF, 30p per dozen (all 160V working). 25% discount for lots of 100 of any one type.

## RESISTORS

1/2 and 1 watt. Most values in stock. 50p per 100. 10p per dozen of any one value. WIRE WOUND MAINS DROPPERS. Hundreds of values from 0.7 ohm upwards. 1 watt to 50 watts. A large percentage of these are multi-tapped droppers for radio/television. Owing to the huge variety these can only be offered "assorted" at 50p per dozen.

## SILVER MICA/CERAMIC/POLYSTYRENE CONDENSERS

Large range in stock, 75p per 100 of any one value. 15p per dozen. **RECORDING TAPE BARGAIN!** The very best British Made low-noise high-quality Tape! 5in Standard 38p. Long-play 45p. 5 1/2in Standard 45p. Long-play 60p. 7in Standard 60p. Long-play 82p. We are getting a fantastic number of repeat orders for this tape. Might we suggest that you order now whilst we still have a good stock at these low prices!

## STOCK TAKING CLEARANCE! IMPOSSIBLE TO REPEAT!

We have huge numbers of components in quantities too small to advertise individually. In order to "clear the decks" we have made up parcels containing a mixture of carbon and wire-wound resistors, electrolytic and paper condensers, controls, transistors, diodes etc., for a tiny fraction of normal price. It is emphasised that these are mixed parcels only—contents cannot be stipulated! Sold only by weight.

Gross weight 2 lb. . . . . £1 (postage 20p)  
 Gross weight 5 lb. . . . . £2 (postage 30p)

## NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.


Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.

Light sensitive aerosol spray . . . . . £1.00  
 Developer spray . . . . . 50p

**SPECIAL 50p PACKS. ORDER 10 PACKS AND WE WILL INCLUDE AN EXTRA ONE FREE ! ! ! !**

<b>RESISTORS, 1/2 watt</b>		<b>TRANSISTORS</b>	
assorted	100 50p	P.N.P. Untested but mainly O.K.	50 50p
Wire-wound 1 to 3 watt	20 50p	N.P.N. Untested but mainly O.K.	50 50p
5 to 7 watt	15 50p	OC71 equivalent	5 50p
10 watts	10 50p	Light-sensitive Diodes	10 50p
Multi-tapped	12 50p	(These produce up to 1mA from light)	
<b>PAPER CONDENSERS</b>		BY 127 Rectifiers	4 50p
Tv types	50 50p	IN4007 Rectifiers	
Miniature	100 50p	(1200V peak)	4 50p
<b>ELECTROLYTIC CONDENSERS</b>		STC 3/4 Rectifiers	6 50p
Suitable for Mains	10 50p	WIRE	
Transistor types	20 50p	Solid Core. Insulated 100yd	50p
Mixed (both types)	15 50p	Stranded ditto	50yd 50p
<b>POLYSTYRENE CONDENSERS</b>	100 50p	<b>SOLAR CELLS</b>	
<b>MULLARD POLYESTER</b>		Large Selenium	2 50p
50 50p		Small	3 50p
<b>SILVER MICA NUTS AND BOLTS. Mixed length/type</b>	100 50p	(6 cells will power a Micromatic radio)	
8 B.A.	100 50p	<b>CRYSTAL TAPE RECORDER</b>	
6 B.A.	100 50p	MIKES	1 50p
4 B.A.	100 50p	<b>CRYSTAL EARPIECES</b>	
2 B.A.	100 50p	3.5mm Plug 2 50p	
<b>EARPIECES, MAGNETIC</b>		<b>TRANSISTORISED Signal Injector Kit</b>	1 50p
No Plug	6 50p	<b>TRANSISTORISED Signal Tracer Kit</b>	1 50p
2.5mm Plug	4 50p	<b>TRANSISTORISED CAR REV. COUNTER KIT (Needs 1 mA meter as indicator)</b>	A1 50p
3.5mm Plug	4 50p		
<b>500 MICRO-AMP LEVEL METERS</b>	1 50p		

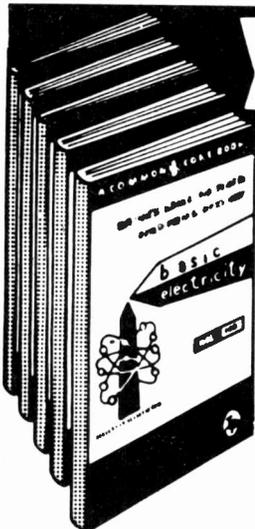G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 15p.



# YOURS FREE FOR 7 DAYS

## The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 vols.)** and **BASIC ELECTRONICS (6 vols.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

### WHAT READERS SAY

"T.V. ENGINEER."  
 "So in two years I have come from a labourer on a building site to a T.V. Engineer, with the help of your books."  
 C.G., Sheppey.

"SIMPLE, CLEAR AND CONCISE."  
 "I would like to endorse the feelings of many purchasers that they are a simple, clear and concise introduction to the study of electronics."  
 E.P.Y., London, S.E.9.

"MONEY WELL SPENT."  
 "I consider this as money well spent. Thank you."  
 F.A. Burton-on-Trent.

■ To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP  
 ■ Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. **BASIC ELECTRICITY £4.50.** Cash Price on Down Payment of £1 followed by 4 fortnightly payments of £1 each (Total £5). **BASIC ELECTRONICS £5.40.** Cash Price or Down Payment of £1 followed by 5 fortnightly payments of £1 each (Total £6). This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

■ Tick Set required (Only one set allowed on free trial)

■ **BASIC ELECTRICITY**  **BASIC ELECTRONICS**

Prices include Postage and Packing.

■ Signature .....  
 (If under 18 signature required of parent or guardian)

■ NAME .....

■ BLOCK LETTERS

■ FULL POSTAL ADDRESS .....

A TECH-PRESS PUBLICATION

**POST NOW FOR THIS OFFER!!**

# components show . . . .

**W**HILE much discussion on component availability prevails on the domestic scene, let us not overlook some of the problems encountered in industry. Any visitor who regularly attends the Components Show at Olympia, organised by the R.E.C.M.F., will have gazed at the ground floor area from the gallery and admired the massive displays put on by large American and British companies. The view this year was not the same. Many of them were not there.

## COMMERCIAL COMBAT

We walked downstairs to the ground floor to find out from close quarters what the electronic components industry is doing, and straight away were confronted by smaller displays, smaller stands (perhaps to suit the smaller components) but many of them. The Goliaths were missing—at least, most of them! There were several Davids finding out that exhibitions are big business (to them at any rate!).

It seems that the bigger the Company, the greater the economies, but are they always in the right direction? Millions of pounds are spent in commercial combat with sling and stone poised; consequently, the customer who is, let's face it, the reason for company existence is often almost cast off as a bore. The customers want the goods and the suppliers shout that they have the goods, but what happens in between is anybody's guess.


When you look more closely, the source of trouble becomes evident—the economic manipulation of hard cash. Are the priorities in the right quarters? Should the supplier spend money to sell any item in any quantity or spend to produce bigger and better cut-out polystyrene lettering with complementary timber and hardboard structures and glossier brochures?

## THE MISSING GIANTS

Well, this year's exhibition, extended over all three halls at Olympia, is a lesson to be learned for anyone in the business and here is the reason why.

It all began with the Vietnam War—no less. The U.S.A. has sunk billions of dollars in mortal combat and in space exploration too. The spin-off of technology from space work has made in-roads into electronics applications all over the world. Since the growth of electronics and associated technology requires capital investment, it is not surprising to learn that the electronics recession in America has spread to other influential countries, while expenditure on space research is reduced.

Consequently, some of the large component manufacturers, companies such as Motorola, Texas Instruments, Honeywell, Marconi-Elliott Microelectronics, Mitsubishi, Muirhead, SGS, were conspicuous by their absence. These are not all American but it does indicate that the U.K. and Japan are influenced by American economics. On the other hand, a large American Government representation incorporating several small companies were apparently quiet.

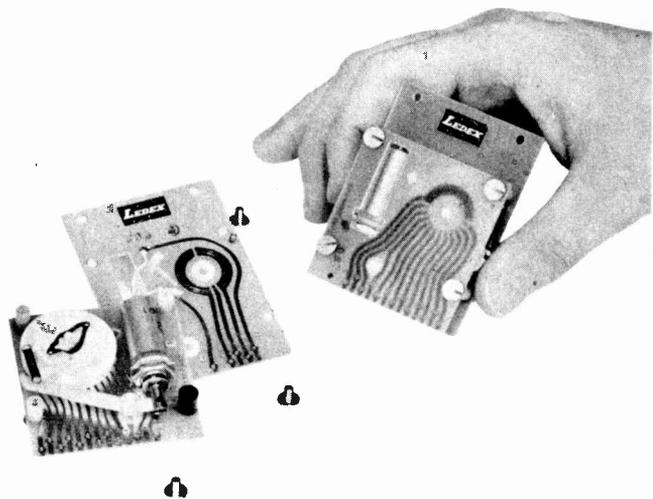

**New approach to the Lexus motorised switch by NSF. Printed circuit board is tracked by a ratchet operated rotating contact wheel (above)**

## CLOSED SHOP

On the home front we see the continued closing down of departments within the larger organisations so as to attempt to save on small outgoings. Of these, the most shattering is the closure of Electronics within the American ITT Company, which absorbed S.T.C. a few years ago. The large white-washed display stand of ITT was mainly devoted to a raised platform, on which were paraded at occasional intervals four luxuriously clad young ladies covered in ITT components—a lavish display—with glib commentary selling the advantages of their components.

"We have it all!" was not our idea of apologising for the closure of *Electronics*—a fine service in the past.

### NEW LINEAR ICs

The foregoing may appear to be a rather grey picture of the exhibition, but should not be taken to imply that the electronics industry is in dire straits. Far from it! It was refreshing to find a buoyant mood among many participants, not the least being the ubiquitous Mullard, who had many new developments on display aimed for both consumer and industrial equipment, via trade outlets, of course.


A new range of eight integrated circuits designed for use in the signal processing stages of colour and monochrome receivers continues the trend for miniaturisation. Portable radio set makers can rejoice in the new integrated circuits, types TBA 690 and TBA 700, for these contain all the active stages of an a.m./f.m. receiver with the exception of the mixer. The TBA 690 will deliver an output of 0.5W, and the TBA 700, 1W.

Integrated circuit type TBA 750 includes the mixer and all stages with the exception of the output stage. It can be used in high performance a.m. or a.m./f.m. receivers. Low power i.c. audio amplifiers have a


is correct here) and wish to eliminate much of the noise that drowns that signal, then Brookdeal Electronics of Bracknell, Berks, may be able to help. Their new "Lock-in" Amplifier type 401 is claimed to be capable of recovering the signal from noise which is 100,000 times greater than that signal. It's frequency range is 1Hz to 50kHz and the amplifier is battery operated.

Amid the problems of supply and demand, it is good to see that one company at least is interested in supplying "one-offs". Tape Recorder Spares Ltd. of London, S.E.17 market pre-pack components for audio equipment, including plugs, sockets, drive belts, fuses, and connecting leads.

Newly introduced by ITT Components Group Europe is the Super-Permacolour television picture tube type A 67-150 X. A 26in shadow mask tube with 110 degree deflection angle and narrow (29mm diameter) neck, the new tube is claimed to give a sharper picture than 90 degree large screen tubes. The overall length of the tube has been reduced by approximately 4.3in (11cm) to approximately 17in (43.1cm). This enables the depth of the receiver cabinet to be reduced accordingly. Specially designed for use with the tube are a new toroidal reflection yoke ITT Type FAS 110-3 and a convergence unit Type FRK 110-3.

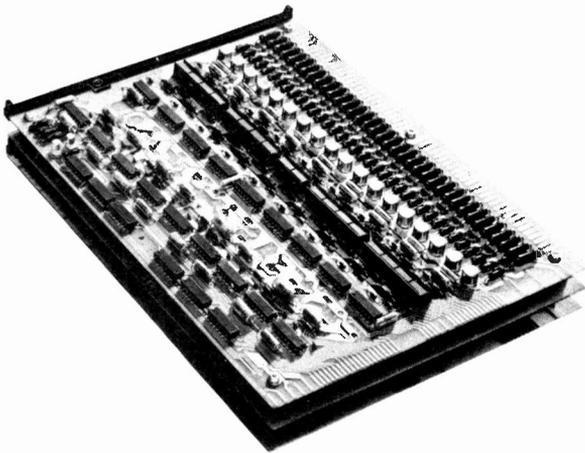

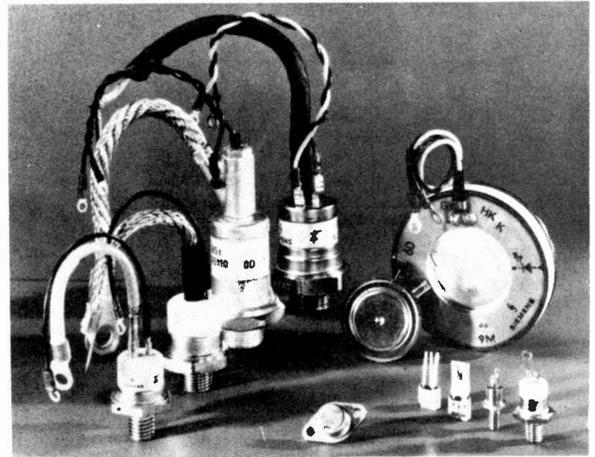*Basic memory module of the Plessey Planar 850 core memory built on three printed circuit boards*



*Range of thyristors and triacs rated from 0.8A to 640A from Siemens (U.K.) Ltd. The Thyblock system is a disc shaped thyristor sandwiched between two aluminium extrusions for cooling*

ready market for use in television receivers, record players, tape recorders and radiograms.

Unfortunately, it is quite easy to irreparably damage these devices by accidentally short circuiting the output. Plessey Microelectronics have successfully overcome this particular problem with the SL403D package (younger brother of SL403C) which is protected against permanent a.c. and d.c. shorts to ground of its input and output terminals.

### LOCK-IN AMPLIFIER

Ever heard of a signal to noise ratio of  $-100\text{dB}$ ? If you encounter such proportions (and that minus

### CORE MEMORY

Plessey displayed a large range of components and equipment extending from optoelectronics to sheet metal work. A completely new product from the Memories Division, is the Planar 850 core memory (see photograph) which meets, in part, the increasing demand from industry of inexpensive core systems. This has a capacity of 4,096 18-bit words and, with other modules, this can be extended to 32,786 words.

Gresham Lion have brought out a higher density recording head. The dual gap read-after-write digital recording head is designed to record 36 separate tracks on lin tape.

A new integrated circuit incorporates the equivalent of 20 TTL packages in one with 30 connec-

# BI-PRE-PAK LIMITED

## FULLY TESTED AND MARKED

	£p		£p
AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
ACY17	0-15	2G303	0-13
AF239	0-37	BC113	0-10
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC171 = BC107	0-13	2N1308-9	0-35
BC172 = BC108	0-13	2N3819FET	0-45
BF194	0-15		
BF274	0-15	<b>Power Transistors</b>	
BFY50	0-20	OC20	0-50
BSY25	0-57	OC23	0-30
BSY26	0-13	OC25	0-25
BSY27	0-13	OC26	0-25
BSY28	0-13	OC28	0-30
BSY29	0-13	OC35	0-25
BSY95A	0-15	OC36	0-37
OC41	0-13	AD149	0-30
OC44	0-13	AUY10	1-25
OC45	0-13	23034	0-25
OC71	0-13	2N3055	0-63
OC72	0-13		
OC73	0-17	<b>Diodes</b>	
OC81	0-13	AA742	0-10
OC81D	0-13	OA95	0-10
OC83	0-20	OA79	0-09
OC139	0-13	OAB1	0-09
OC140	0-17	IN9114	0-07

# FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 50p WITH ORDERS OVER £4

## CLEARANCE LINES

	1-10	10-50	50+
SL403D Audio amp.	£2	£1-95	£1-80
1C 709C Linear Opp. amp	50p	40p	35p
A.E.I. fully marked and tested gates	25p	22p	20p
A.E.I. fully marked and tested flip-flops	50p	40p	30p
OC71/72 fully tested unmarked	5p	5p	4p
Matched sets 1-OC44, 2-OC45 per set	25p	20p	15p
Matched sets OC45's 1st and 2nd IF per set	15p	12p	10p
TIC 45 Thyristors—			
·6 amp 60V Texas	15p	15p	12p
OA47 gold bonded diodes	3p	3p	2p
IW Zener diodes 6-8, 7-5, 24, 27, 30 and 43V	5p	4p	3p
10W Zener diodes 7-5, 11, 13, 20 and 100V	20p	17p	15p
Micro switches, S/P, C/O.	25p	20p	15p
1 amp bridge rec. 25V.	25p	22p	20p
1 amp plastic rectifiers. These are voltage, reversed polarity and other rejects from the BY127 range. Ideal for low voltage power units etc. Price £1 per 100.			

**COLOUR T.V. LINE OUTPUT TRANSFORMERS**  
Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory. **ONLY £1 each** post and packing 23p.

## BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

**2 LBS IN WEIGHT FOR £1**  
Post and packing 25p.

## NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0-3 to 0-5V, 0-5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Postage 13p. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Postage 10p. Approx. quantity, counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values. Postage 8p	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OCPT1 Light Sensitive Photo Transistor	50p
H12	20	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoated black glass type PNP Germ.	50p
H19	10	OC81/81D uncoated white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncoated TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MC52	50p

## F.E.T. PRICE BREAKTHROUGH !!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819.

Data sheet supplied with device.

1-10 30p each, 10-50 25p each, 50+ 20p each.

**Make a Rev. Counter for your Car. The 'TACHO BLOCK'.** This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **£1 each**

## FREE CATALOGUE AND LISTS FOR:—

**ZENER DIODES  
TRANSISTORS, RECTIFIERS  
FULL PRE-PAK LISTS  
& SUBSTITUTION CHART**

MINIMUM ORDER 50p CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

**P.O. RELAYS 8 FOR £1**  
Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

## OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED

TYPE "A" PNP Silicon alloy, metal TO-5 can. 25300 type, direct replacement for the OC200/203 range.

TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.

TYPE "E" PNP Germanium AF or RF—please state on order. Fully marked and tested.

TYPE "F" NPN Silicon plastic encapsulation, low noise amplifier of the 2N3708, 9, 10, 11.

## BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/8, BSY26-29, BSY95A, BCY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc., £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36, £4-50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc. £4-25 per 500; £8 per 1,000.

OC44, OC55 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 5p each.

3823E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

**1 amp Miniature Plastic Diodes:**  
IN4001, 500+ 3p each; 1,000+ 3p each.  
IN4004, 500+ at 5p each, 1,000+ at 4p each.  
IN4006, 500+ at 6p each, 1,000+ at 5p each.  
IN4007, 500+ at 8p each, 1,000+ at 7p each.

## NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes Mixed Voltages	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1½ watt Zeners. Top hat type	50p
H11	30	MAT Series "alloy" pnp Transistors	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers. 1 amp plastic. Mixed volts.	50p

**FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS**

**BI-PRE-PAK LTD** DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344

## SPECIAL PURCHASE!


**BRAND NEW FM MULTIPLEX STEREO DECODER UNITS.** Manufactured by PHILIPS. Size 2" x 3 1/2" x 1 1/2". All transistor 24V. at 6mA. Supplied pre-aligned with full circuit diagram and connection details. £4 each. Post free.

**FEW ONLY—LEAK MK I TRANSCRIPTION PICK-UP ARMS.** Using the world famous gimbal pivot system. Complete but less pick-up head. £2.50. P. & P. 20p.

**INPUT MATCHING TRANSFORMER.** Beautifully made in heavy Mu-netal cylindrical case for minimum hum pick-up. Size 1 1/2" high x 1 1/4" dia. Ratio 150:1 approx. Especially suitable for matching dynamic or ribbon mikes or pick-up from low to high impedance or vice versa. 75p each. Post Free.

**BLACK ANODISED 16g ALUMINIUM HEAT SINKS.** For TO3, complete with mica's and bushes. Size 2 1/2" x 3" approx. 25p pair. P. & P. 5p.
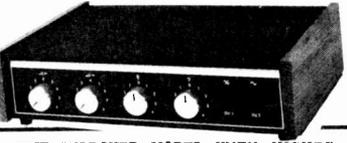
## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



**NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION**

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 8 ohms. Frequency response  $\pm 3dB$  12-20,000Hz. Sensitivity better than 80mV into 1M $\Omega$ . Full power bandwidth  $\pm 3dB$  15-15,000Hz. Bass boost approx. to  $\pm 12dB$ . Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 33V at 1.0 amp. Overall size—12" wide 8" deep 2 1/2" high. Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

**PRICES AMPLIFIER KIT. £10.50 P. & P. 15p.**  
**POWER PACK KIT. £3 P. & P. 30p.**  
**CABINET. £3 P. & P. 30p.**

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £20.50. Post Free.

*Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.*

**SPECIAL PURCHASE OF MANUFACTURER'S SURPLUS.** All transistor F.M. tuner head with twin A.M. Gang incorporated. Beautifully engineered with precision geared reduction drive. F.M. R.F. Transistor, oscillator/Mixer and first I.F. stage (10.7 Mc/s output) with optional AFC connection. Built on printed circuit board and fully screened. Extremely stable over range 88-108 Mc/s. Brand new and pre-aligned. Size 2 1/2" H. x 1 1/2" W. x 2 1/2" D. For 6V D.C. at 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits if required. **LIMITED NUMBER. Only £2.25 post free.** Connection details supplied.

**HIGH GRADE COPPER LAMINATE BOARDS** 8 x 6 x 1/8 in. FIVE for 50p. P. & P. 13p.

**TELESCOPIC AERIALS WITH SWIVEL JOINT.** Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to approx. 22 1/2 in. Maximum diameter 3in. 25p each. P. & P. 5p.

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-340V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-0-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3inL x 3 1/2 inW x 3inD. Price £1.75. P. & P. 30p.

**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240V. Sec. 9-0-9 at 500mA. 70p. P. & P. 13p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 88p. P. & P. 13p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £1.38. P. & P. 30p. Tapped Primary 200-220-240V. Sec. 21-5V at 500mA. 68p. P. & P. 13p.

**Open 9-5.30 Monday to Saturday**  
**Early closing Wed. 1 p.m.**  
*A few minutes from South Wimbledon Tube Station*

## SPECIAL OFFER!! HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2 in high x 10 1/2 in wide x 5 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Power handling 10W. Available 3, 8 or 15 ohm impedance.

**Our Price £8.40** Carr. 65p.

**CABINET AVAILABLE SEPARATELY £4.50.** Carr. 60p.  
Also available in 8 ohm with EMI 13in x 8in. bass speaker with parasitic tweeter. £8.50. Carr. 65p.

### LOUDSPEAKER BARGAINS

3in 4 ohm 50p. P. & P. 13p. 5in 5 ohm 80p. P. & P. 15p. 7 x 4in 3 ohm £1.05. P. & P. 20p. 10 x 6in 3 or 15 ohm £1.90. P. & P. 30p. E.M.I. 8 x 5in 3 ohm with high flux magnet £1.62. P. & P. 20p. E.M.I. 13in x 8in 3 ohm with high flux ceramic magnet £2.10 (15 ohm £2.25). P. & P. 20p. E.M.I. 13 x 8in. 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network £4.20. P. & P. 30p. E.M.I. 13" x 8" twin cone (parasitic tweeter) 8 ohm £2.25. P. & P. 30p.

**BRAND NEW.** 12in 15w H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hi-Fi ceramic ferrobar magnet assembly £5.50. Guitar models: 25w £8.50, 35w £8.50. P. & P. 38p each. E.M.I. 3in **HEAVY DUTY TWEETERS.** Powerful ceramic magnet. Available in 3, 8 or 15 ohm 98p each. P. & P. 13p.

12in "RA" **TWIN CONE LOUDSPEAKER** 10 watts peak handling. 3 or 15 ohm, £2.20. P. & P. 30p. 35 ohm **SPEAKERS 3".** ONLY 68p. P. & P. 13p. **VYNAIR & REXINE SPEAKERS & CABINET FABRICS** app. 5 1/2 in. wide. Usually £1.75 yd., our price 75p yd. length. P. & P. 15p (min. 1 yd.). S.A.E. for samples.

### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-puffs. Wired and fitted with standard stereo 1/4 in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. **PRICE £2.95.** P. & P. 15p.

**SINGLE HEADPHONE.** With aluminium headband. Approx. 200 ohm. 25p. P. & P. 8p.

**CRYSTAL MIKES.** High imp. for desk or hand use. High sensitivity. 93p. P. & P. 8p.

**HIGH IMPEDANCE CRYSTAL STICK MIKES.** OUR PRICE £1.05. P. & P. 8p.

**GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER.** For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-15V. Battery or from H.T. line 200/300P. Frequency response 15Hz-25KHz. Gain 25dB. Solid encapsulation size 1 1/2 x 1 1/2 in. Brand new—complete with instructions. Price 88p. P. & P. 13p.

**BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST.** Fitted mono t/o stylus and cartridge for LP/78, ONLY £1. P. & P. 8p.

**QUALITY RECORD PLAYER AMPLIFIER MK II** A top-quality record player amplifier employing heavy duty double wound mains transformer. ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3 1/2" h. Ready built and tested. **PRICE £3.75.** P. & P. 40p. **ALSO AVAILABLE** mounted on board with output transformer and speaker ready to fit cabinet below. **PRICE £4.88.** P. & P. 50p.

**DE LUXE QUALITY PORTABLE R/P CABINET MK II** Cutout motor board size 14 1/2 x 12 1/2 in., clearance 2in. below, 8 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. **PRICE £3.98.** P. & P. 50p.

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving control and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 13p. (Free with parts). All parts sold separately. ONLY £7.97. P. & P. 55p. Also available ready built and tested complete with std. input sockets, £9.97. P. & P. 55p.

**BRAND NEW TRANSISTOR BARGAINS.** GET 13 (Matched pair) 75p; V15/10p, 50p; OC71 25p; OC76 30p; AF117 18p; 2G339 (NPN) 15p. Set of Mullard 6 transistors OC44, 2—OC45, AC128D, Matched pair AC128 21.25; ORP12 Cadmium Sulphide Cell 58p. All post free.


## SPECIAL PURCHASE!

### SPEAKER CABINET FROM FAMOUS MAKER!

Beautifully made all-wooden construction cabinet with medium walnut finish front, gold anodised expanded aluminium grille and dark sides. Approx. size overall 11" high x 5" deep x 13 1/2" wide at base. Easily removable baffle cut for 8" speaker. Fibre board back. Could accommodate amplifier or radio together with speaker. An expensively made cabinet at a give-away price.

**LIMITED NUMBER ONLY £1.38 Post Free.**

## DE LUXE STEREO AMPLIFIER

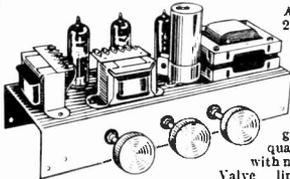

A.C. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:—2 x ECL86 Triode Pentodes 1. E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11 in. w. x 4 in. x. Overall height including valves 5in. Ready built and tested to a high standard. **Price £2.92.** P. & P. 45p.


### 4-SPEED RECORD PLAYER BARGAINS

**Mains models.** All brand new in maker's packing. **LATEST B.S.R. C109/A21 4-SPEED AUTOCHANGER.** With latest mono compatible cartridge £8.97. Carr. 50p. With stereo cartridge £7.97. Carr. 50p.

**SUITABLE PLINTH UNIT FOR ABOVE** with rigid plastic cover. £5.75 complete. P. & P. 50p.  
**LATEST GARRARD MODELS.** All types available 1025, 2025, SP25, 3000, AT60, etc. S.A.E. for Latest Prices!  
**PLINTH UNITS** cut out for Garrard Models 1025, 2025, 2000, 3000, 3500, etc. With rigid transparent plastic cover. Special design cables above models to be used with cover in position. Also suitable for housing AT60 and SP25. **OUR PRICE £5.75 complete.** P. & P. 50p.

**LATEST ACOS GP91/150 Mono Compatible Cartridge** with t/o stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 8p.

**SONOTONE STAHG COMPATIBLE STEREO CARTRIDGE T/O stylus.** Diamond Stereo LP and Sapphire 78. ONLY £2.50. P. & P. 10p. Also available fitted with twin diamond T/O stylus for Stereo LP. £3. P. & P. 10p.  
**LATEST RONETTE T/O Stereo Compatible Cartridge** for EP/LP/Stereo/78. £1.63. P. & P. 10p.  
**LATEST RONETTE T/O Mono Compatible Cartridge** for EP/LP/78 mono or stereo records on mono equipment. £1.50. P. & P. 10p.

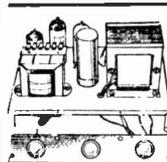

### 3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Really built on plated heavy gauge metal chassis. Size 7 1/2 in. w. x 4 1/2 in. h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and lends extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 35p.

**HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.98. P. & P. 40p.

### HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer. FEW ONLY.

**OUR ROCK BOTTOM BARGAIN PRICE £2.75 P. & P. 35p**

### HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. 1971 edition including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.

## HARVERSON SUPER SOUNDS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

# components show □□□□

tions in a d.i.l. encapsulation. It reduces the number of soldered connections considerably from up to about 280 so adding to time saving and reliability. This MOS-LSI device was developed by Integrated Photomatrix Ltd., of Dorchester for a digital panel meter for Evershed and Vignoles.

The behaviour of TTL and DTL in response to random noise spikes is known to cause quite a few headaches to troubleshooters. A new instrument will help by detecting spikes that an oscilloscope may miss. It is a pencil-size probe produced by Birch-Stolec of Hastings to indicate any operation (1 or 0) by means of a lamp.

## FOR THE MOTORIST

Of particular interest to motorists is the flexible printed circuit aerial that can be fitted around the periphery of the rear window for a car radio. Screening problems are thus avoided and accessibility from outside vandalism is nil (provided doors and windows are locked). MB Metals of Portslade, Sussex, developed the aerial while engaged on producing complete printed circuit type harnesses for cars and aircraft.

While on the subject of cars, piezo-electric ignition is on the way. Although not yet available, advanced work by a Japanese company, Murata Manufactur-

ing, expects to provide this off-shoot from its low cost ceramic ignition systems for lighters and gas cooker ignitors.

Crompton Parkinson have produced a "zinc-air" primary cell capable of up to eight times the output of conventional cells, and is smaller and lighter in weight. This is believed to be the first commercial one of its kind and should be a breakthrough for electric cars.




## THYRISTOR SUPPRESSORS

Demonstration of this new range of interference suppressors puts Birch-Stolec among the progressive British companies.

The suppressors have been designed to meet requirements of the latest technological developments covering thyristor and triac suppression and equipment used in computers, data logging instruments and communications. They combine three facilities—the elimination of discrete inductors and capacitors, the absorption of unwanted interference power and the use of suppressor rather than filter techniques.

Birch-Stolec have also set up a new printed circuit division for custom design of flat flexible cables and cards.

One might be forgiven for thinking that a physiological stimulator was intended as a "wakey-wakey" alarm, but it is intended to be a serious scientific instrument for medical research teams. It emits pulses in sequences, set up by the controls, either in continuous mode or in gated trains. The stimulator is expected to assist neurologists in particular, but can also be used in biological research of broader base. Farnell Instruments of Wetherby, Yorks, are responsible for this equipment.

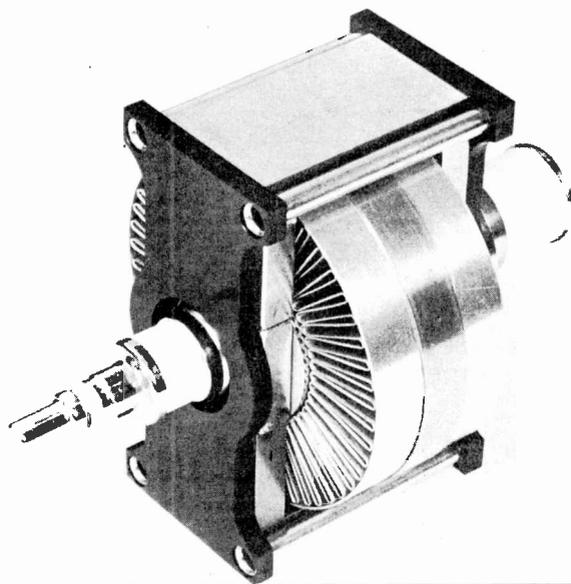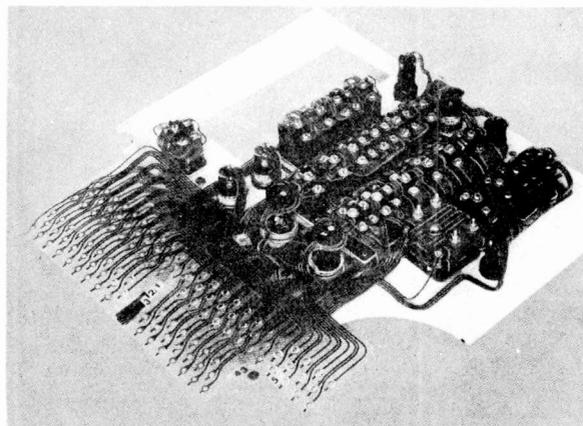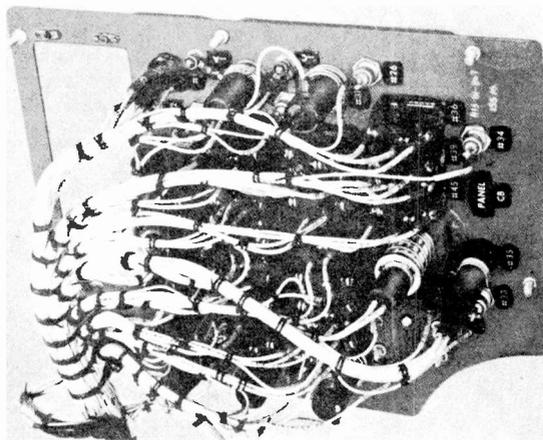

*Magnetron type YJ1371 developed by Mullard for use in microwave cookers (above)*

*MB Metals Ltd. are developing flexible printed wiring harnesses for cars and aircraft. This one (left) is for a helicopter and shows the wiring it replaces (top left)*

A commercial development from experimental work at R.A.E. Farnborough is the high speed television camera and video tape recorder which provides an exposure time of  $10^{-4}$  second while running at a picture rate of 100 per second. The result is that immediate playback either in slow motion or with stop action is obtained. The equipment is being manufactured by Aston Electronic Developments Ltd., Pirbright, Surrey.

## DISCRETE COMPONENTS

For engineers and designers with appetites for small and simple switching solutions, N.S.F. of Keighley, Yorkshire, introduce the Ledex "sandwich stepper". This is a new 1-pole, 12-position stepping switch so-called because of its unusual rectangular design built on a layer of printed circuit board.

It comprises a 12-position circuit wafer together with a restoration or zero reset wafer control system. These, with a complete solenoid drive assembly are sandwiched between two printed circuit boards. The entire unit is only  $\frac{1}{4}$ in thick.

Contact breaking current rating is 120mA at 120V a.c. and 500mA at 28V d.c. (resistive). Current carrying capacity is 2 amperes. The stepping speed (intermittent) is 60 per second.

Vitramon Europe displayed their established range of porcelain and ceramic dielectric capacitors. Among the new exhibits were miniature axial leaded ceramic capacitors 10pF to 100,000pF designed for computer application and an extended range of ceramic chip capacitors for hybrid microcircuit use.

An economical and robust magnetron for use in microwave cooking is the Mullard YJ1371 (see photograph). It requires a heater voltage only when starting and subsequently operates at the low anode voltage of 3.6kV, ensuring a long life and low operational cost.

Wire strippers are common place for p.v.c. covering, but these are hardly suitable for fine enamel coverings. Gardners Transformers Ltd., of Christchurch, Hampshire, have introduced an IGWES


(Inert Gas Wire Enamel Stripper) for enamelled copper wires. The wire is heated in a nitrogen atmosphere to decompose the insulation. As the wire is withdrawn it is cooled by a nitrogen flow which prevents oxidation.

A novel innovation from A. F. Bulgin & Co. of Barking, is their fused crocodile clip CR50 which is designed to protect test meters against false operating conditions, faults, and shorts during fault finding procedures. It is available in clip or probe form.
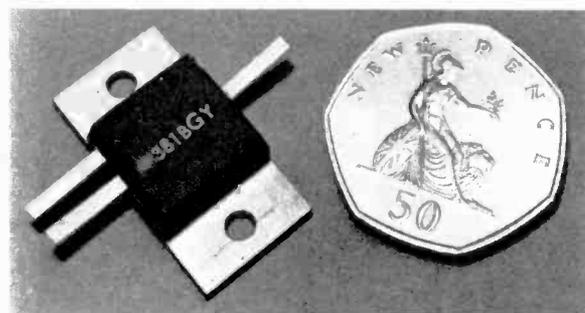
## STANDARD COMPONENT SPECIFICATIONS

The work of the British Standards Institution culminates in an enormous amount of paper work. So much so that one wonders how anyone can find anything. All due credit therefore to BSI for setting up the BS 9000 Scheme for Electronic Parts of Assessed Quality. It is not possible here to go into any detail on the scheme, but briefly the aim is to standardise on manufacturing and usage specifications for electronic components.



Specifications appropriate in the past to the Ministry of Defence, Post Office, and C.E.G.B. are being incorporated in the scheme, which will provide for a universal test procedure for quality control. Over 100 British manufacturers, test centres, and stockists have already applied for approval under the scheme.



One of the new u.h.f. amplifier modules by Mullard compared with a 50 pence piece (above)


Physiological stimulator by Farnell Instruments (top right)

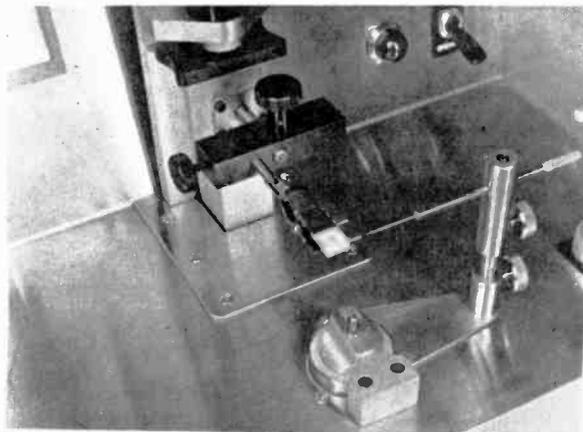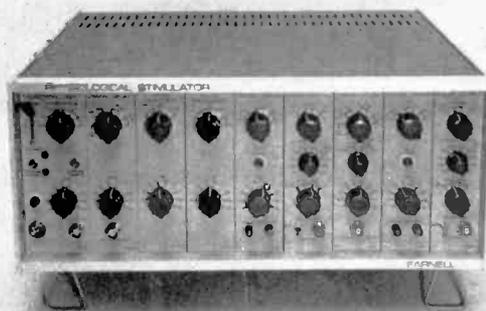Supplementary Parts Kit (Ref. No. 1) for the Multicore Solderability test machine. This kit is used to determine solderability with short leads down to 1.2mm from the component body (right)



# new

## Super IC-12

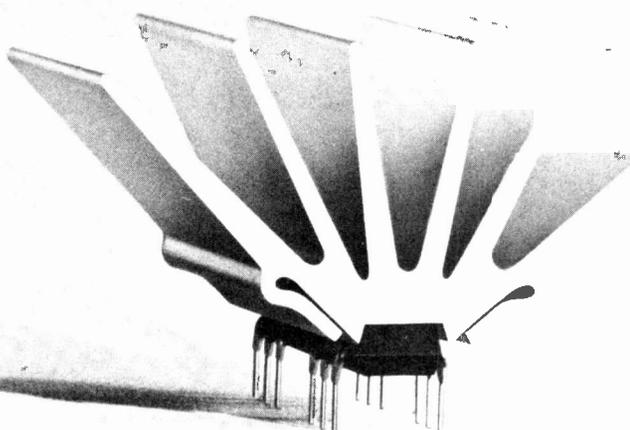

### High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

**Output power** 6 watts RMS continuous (12 watts peak).

**Frequency Response** 5 Hz to 100KHz  $\pm$  1dB.

**Total Harmonic Distortion** Less than 1% (Typical 0.1%) at all output powers and all frequencies in the audio band.

**Load Impedance** 3 to 15 ohms.

**Power Gain** 90dB (1,000,000,000 times) after feedback.

**Supply Voltage** 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

**Size** 22 x 45 x 28 mm including pins and heat sink.

**Input Impedance** 250 Kohms nominal.

**Quiescent current** 8mA at 28 volts.

**Price:** including FREE printed circuit board for mounting. **£2.98** Post free

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project 60 range such as the Stereo 60 and A.F.U. may be added. The comprehensive manual supplied with each unit gives full circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include car radios, oscillators etc. The very low quiescent consumption makes the Super IC.12 ideal for battery operation.

Sinclair Radionics Ltd., London Rd, St. Ives  
Huntingdonshire PE17 4HJ  
Telephone St Ives (048 06) 4311

**sinclair**

# Sinclair Project 60



the world's most advanced high fidelity modules

**Sinclair Project 60** presents high fidelity in such a way that it meets every requirement of performance, design, quality and value and now that the remarkable phase lock loop stereo FM tuner is available, it becomes the most versatile of high fidelity systems. With Project 60, it is possible to start with a

modest mono record reproducer and expand it to a sophisticated stereophonic radio and record reproducing system of fantastically good quality to hold its own with any other equipment, no matter how expensive. Project 60 is a unique high fidelity module system where compactness and ease of assembly are combined with

circuitry that is far in advance of any other manufacturer in the world. Thus it is extraordinarily easy to assemble any combination of modules using nothing more complicated than the simplest of tools, and you certainly do not have to be experienced to build with complete confidence. The 48 page manual free with Project 60 equipment makes everything easy and you can house your assembly in an existing cabinet, motor plinth, free standing cabinet or virtually any arrangement you wish. Once you have completed your assembly you will have superlatively good equipment to give you years of service and enjoyment. You will have obtained superb value for money because Project 60 is the best selling modular system in Europe and can therefore be produced at extremely competitive prices and with excellent quality control.


Sinclair Radionics Ltd., London Road, St. Ives, Huntingdonshire PE17 4HJ.  
Tel: St. Ives (048 06) 4311

**sinclair**

System	The Units to use	together with	Cost of Units
A Simple battery record player	<b>Z.30</b>	Crystal P.U., 12V battery volume control	<b>£4.48</b>
B Mains powered record player	<b>Z.30, PZ.5</b>	Crystal or ceramic P.U. volume control etc.	<b>£9.45</b>
C 20+20 W. R.M.S. stereo amplifier for most needs	<b>2 x Z.30s, Stereo 60, PZ.5</b>	Crystal, ceramic or mag. P.U., most dynamic speakers, F.M. tuner etc.	<b>£23.90</b>
D 20+20 W. R.M.S. stereo amplifier with high performance spkrs.	<b>2 x Z.30s, Stereo 60, PZ.6</b>	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	<b>£26.90</b>
E 40+40W. R.M.S. deluxe stereo amplifier	<b>2 x Z.50s, Stereo 60 PZ.8, mains trsfrmr</b>	As for D	<b>£34.88</b>
F Outdoor P.A. system	<b>Z.50</b>	Mic., up to 4 P.A. speakers controls, etc.	<b>£5.48</b>
G Indoor P.A.	<b>Z.50, PZ.8, mains transformer</b>	Mic., guitar, speakers, etc., controls	<b>£19.43</b>
H High pass and low pass filters	<b>A.F.U.</b>	C, D or E	<b>£5.98</b>
J Radio	<b>Stereo F.M. Tuner</b>	C, D or E	<b>£25.00</b>

# Sinclair Project 60

## Z.30 & Z.50 power amplifiers

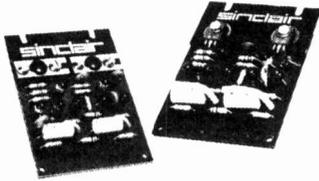

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

**SPECIFICATIONS (Z50 units are interchangeable with Z.30s in all applications).**  
**Power Outputs**

**Z.30** 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.  
**Z.50** 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms, using 50 volts.


**Frequency response:** 30 to 300 000 Hz  $\pm$  1dB.  
**Distortion:** 0.02% into 8 ohms.  
**Signal to noise ratio:** better than 70dB un-weighted.

**Input sensitivity:** 250mV into 100 Kohms.  
For speakers from 3 to 15 ohms impedance.  
Size  $3\frac{1}{2} \times 2\frac{1}{2} \times \frac{1}{2}$  in.

**Z.30**  
Built, tested and guaranteed with circuits and instructions manual **£4.48**

**Z.50**  
Built, tested and guaranteed with circuits and instructions manual. **£5.48**

## Power Supply Units

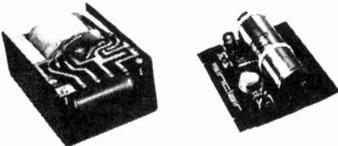

Designed specially for use with the Project 60 system of your choice.

Illustration shows PZ.5 to left and PZ.8 (for use with Z.50s) to the right. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

**PZ-5** 30 volts un-stabilised **£4.98**

**PZ-6** 35 volts stabilised **£7.98**

**PZ-8** 45 volts stabilised

(less mains transformer) **£7.98**

**PZ-8** mains transformer **£5.98**

## Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

## Stereo 60 pre-amp/control unit



Designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

### SPECIFICATIONS

**Input sensitivities:** Radio—up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve  $\pm$  1dB; 20 to 25,000 Hz. Ceramic p.u.—up to 3mV; Aux—up to 3mV.

**Output:** 250mV

**Signal-to-noise ratio:** better than 70dB.

**Channel matching:** within 1dB.

**Tone controls:** TREBLE + 15 to -15dB at 10kHz; BASS + 15 to -15dB at 100Hz.


**Front panel:** brushed aluminium with black knobs and controls.

**Size:**  $8\frac{1}{2} \times 1\frac{1}{2} \times 4$  ins.

Built, tested and guaranteed.

**£9.98**

## Active Filter Unit

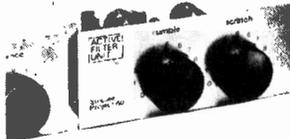

For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two stages of filtering are incorporated—rumble (high pass) and scratch (low pass). Supply voltage — 15 to 35V. Current — 3mA. H.F. cut-off (-3dB) variable from 28kHz to 5kHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1kHz (35V. supply) 0.02% at rated output.

Built, tested and guaranteed

**£5.98**

## Stereo FM Tuner



### first in the world to use the phase lock loop principle

Before production of this tuner, the phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio over other systems. Now, for the first time, the principle has been applied to an FM tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Sensitivity is such that good reception becomes possible in difficult areas. Foreign stations can be tuned in suitable conditions and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

### SPECIFICATIONS:

**Number of transistors:** 16 plus 20 in I.C.

**Tuning range:** 87.5 to 108 MHz

**Capture ratio:** 1.5dB

**Sensitivity:**  $2\mu$ V for 30dB quieting;  $7\mu$ V for full limiting.

**Squelch level:** 20 $\mu$ V.

**A.F.C. range:**  $\pm$ 200 KHz

**Signal to noise ratio:** >65dB

**Audio frequency response:** 10Hz—15kHz ( $\pm$ 1dB)

**Total harmonic distortion:** 0.15% for 30% modulation

**Stereo decoder operating level:** 2 $\mu$ V

**Pilot tone suppression:** 30dB

**Cross talk:** 40dB

**I.F. frequency:** 10.7 MHz


**Output voltage:** 2 x 150mV R.M.S.

**Aerial impedance:** 75 Ohms

**Indicators:** Mains on; Stereo on; tuning indicator

**Operating voltage:** 25-30 VDC

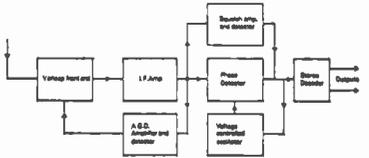**Size:**  $3.6 \times 1.6 \times 8.15$  inches:  $91.5 \times 40 \times 207$  mm



Price: **£25** built and tested. Post free

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

\_\_\_\_\_

\_\_\_\_\_

Name

\_\_\_\_\_

Address

\_\_\_\_\_

for which I enclose cash/cheque/money order.

PE8

### SP25 Mk III SPECIAL!



Garrard SP25 Mk. III Single Record Player. Fitted Goldring 0850 or AT66 Magnetic Stereo Cartridge as available Complete in Teak Plinth with Rigid Perspex Cover.  
Total list Price over £29.  
**PREMIER PRICE £19.90**  
P. & P. 50p



**TAPE CASSETTES**  
C60 (60 min.) 37p 3 for £1.05  
C90 (90 min.) 62p 3 for £1.80  
C120 (120 min.) 87p 3 for £2.55  
P. & P. 5p

All cassettes can be supplied with library cases at 3p extra each.

### PREMIER QUALITY MICROPHONES

Precision made, beautifully designed and offering reliability at a reasonable price.



**FANON MK047 MINIATURE DYNAMIC**  
Frequency response 60-13,000Hz Impedance 50kΩ (-59dB). Can be used with stand, hand held or around neck. Die cast body satin chrome finish. Features removable windscreen. Complete with 8ft cable, stand adaptor and Lavalier cord. **PREMIER PRICE £5.97.** P. & P. 20p.

**FANON MK045 3-WAY DYNAMIC**  
Frequency response 60-12,000Hz. High impedance. Complete with 8ft cable, table stand and Lavalier cord. **PREMIER PRICE £2.87.** P. & P. 20p.

**FANON MKC54 DYNAMIC**  
Frequency response 60-12,000Hz. Impedance 50kΩ (-60dB) and 150 ohms (-71dB). On/off switch. Complete with 20ft cable and stand adaptor. **PREMIER PRICE £2.97.** P. & P. 20p.

### E.M.I. 13x8in. HI-FI SPEAKERS



Fitted two 2in tweeters and crossover network. Available with 8 or 16 ohm impedance. Handling capacity 10W. Brand new.  
**£3.47** P. & P. 40p

### METER BARGAINS



**MODEL GT800 MULTIMETER**  
A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries.  
Ranges—D.C. voltages: 10, 50, 250, 1,000V (1,000 O.P.V.). A.C. voltages: 10, 50, 250, 1,000V (1,000 O.P.V.). D.C. current: 1mA, 100mA. Resistance: 0-150 kohms. Decibels: -10 to +22dB (at a.c. 10V range).  
**£2.47.** P. & P. 17p.



**MULTIMETER 20,000 O.P.V. MULTI-METER**  
Features large easy-to-read meter, wide choice of ranges. With test leads, batteries and manual. Size: 4 1/4 x 3 1/4 x 1 1/4 in.  
Ranges: D.C. voltages: 0-5-25-50-250-500-2,500V. A.C. voltages: 0-10-50-100-500-1,000V. D.C. current: 0-50-500-2,500mA-2500mA. Resistance: 0-6,000 ohms, 0-6 meg ohms (300 ohms and 30 Kohms at centre scale) Capacity: 10 uuf to 100uuf. 0.001uuf to 10uuf. Decibels: -20 to +22dB.  
**£4.90.** P. & P. 17p.



**MODEL CT620 MULTITESTER**  
Ranges: D.C. voltages: 0, 5, 25, 100, 500/1,000V (20,000 ohms/V). A.C. voltages: 0, 5, 25, 100, 500, 1,000V (10,000 ohms/V). D.C. current: 0, 50mA, 500mA, 500mA, 500mA. Resistance: 0, 6kΩ, 600kΩ, 6MΩ, 60MΩ. Decibels: -20 to +62dB in 5 ranges.  
**£5.62.** P. & P. 17p.

### "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.  
TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP3 3'	250'	P.V.C.	28p	DT6 51'	1800'	POLYESTER	£1.12
TT3 3'	450'	POLYESTER	37p	TT6 51'	2400'	POLYESTER	£1.87
DT3 3'	600'	POLYESTER	57p	SP7 7'	1800'	P.V.C.	65p
SP5 5'	800'	P.V.C.	42p	LP7 7'	1800'	ACETATE	75p
LP5 5'	900'	P.V.C.	50p	DT7 7'	2400'	POLYESTER	£1.25
DT5 5'	1200'	POLYESTER	75p	TT7 7'	3600'	POLYESTER	£2.60

**TAPE SPOOLS 3' 5p, 5', 51', 7' 9p.**  
Post and Packing 3' 5p, 5', 51' 8p, 7' 10p. (3 reels and over Post Free.)



# PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639  
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451



**\*\* OPPORTUNITY KNOCKS \*\***  
SAVE £ £ £ £'s

Low cost guaranteed full spec. components from leading manufacturers

7400, 10, 30—Gates	1-24	25-99	100 + 21p	see special offer
7401, 02, 03, 04, 20, 30, 40, 50, 51, 53, 54, 60—Gates	21p	18p	14p	
7413, 70, 72—Dual Schmitt and Single F/F's	33p	31p	27p	
7442, 141—BCD/DEC Decode and Driver	86p	76p	65p	
7446, 47—30V and 15V BCD/7 Seg. Dec. Dr.	£1.40	£1.30	£1.20	
7473, 74, 76—Dual F/F's	42p	38p	35p	
7480, 83—Adders	86p	76p	65p	
7475—Quad Latch	45p	43p	41p	
7481—16bit Memory	£1.33	£1.23	£1.13	
7482—Binary Adder	£1.28	£1.18	98p	
7486—Excl. or Gate	78p	68p	58p	
7490, 92, 93, 94, 95—Cntrs. and Rgstrs.	86p	76p	65p	
74121—Monoscable	86p	76p	65p	
74122—Retriggerable Mono	£1.35	£1.30	£1.28	
74123—Dual Retrig. Mono	£2.30	£2.20	£2.10	
7445, 145—30V and 15V 80mA BCD/DEC. Driv.	£1.78	£1.68	£1.59	
74190, 191—Reversible Cntrs.	£3.30	£3.00	£2.80	

\*SPECIAL OFFER—7400, 10, 30 25 + all one price 12p

\*Mix Devices for quantity price

\*Free 74N wall chart with every TTL order

OP. Amps—709741—8 and 14 Lead Dil and TOS 53p 45p 40p

Dual Op's—709DN, 741DN, 747N £1.30 £1.20 99p

\*Free report on audio amp design using OP amps with every OP amp order over £1. 50 report alone 15p inc. P. & P.

IN 4148/9149/182/83 BC107/108/109/182/183/184—G.P. NPN's 11p 10p 9p

BC212/13/214—PNP comps. 15p 14p 13p

TIS43—Unijunction 40p 38p 37p

Terms: C.W.O. 50p min. ord. P. & P. 10p U.K. 25p Europe. 60p Overseas. Delivery subject to stock. Overseas orders welcome.

ELMTEX LTD. (COMPONENTS DIV.)  
83 HIGH STREET, DUNMOW, ESSEX  
Tel.: Great Dunmow 2202

### NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

**Loft Mounting Arrays.** 7 element, 45'; 11 element, 52'; 14 element, 60'; 18 element, 70';  
**Wall Mounting with Cranked Arm.** 7 element, 65'; 11 element, 75'; 14 element, 82'; 18 element, 90';  
**Chimney Mounting Arrays.** Complete, 7 element, 80'; 11 element, 87'; 14 element, 95'; 18 element, 105'. Complete assembly instructions with every aerial. Low Loss Coaxial Cable, 1.8 yd. King Teleboosters—Lagard U.H.F. Boosters from 75'. Belling Lee "Concord" all Band V.H.F. U.H.F. mains operated pre-amp £7.10. State clearly channel number required on all orders. p.p. Aerials 8'. Accessories 3'. C.W.O. or C.O.D.

### BBC. ITV. FM AERIALS

B.B.C. (Band 1). Loft, 25'; Wall S.D. 32.6'; "H" array, 60';  
I.T.V. (Band 3). 5 element loft array, 45'; 7 element, 55';  
Wall mounting 5 element, 65';  
Combined BBC ITV loft 1 + 5, 55'; 1 + 7, 67.6'. Wall mounting 1 + 5, 77.6'. Chimney mounting 1 + 5, 90'. Pre-amps from 75'.

Combined BBC/ITV BBC2 Aerials, 1 + 5 + 9, 80'; 1 + 5 + 14, 90'; 1 + 7 + 14, 100'. Available loft only.

F.M. Radio Loft S.D. 19.6', "H", 38.6', 3 element array, 57.6'. Standard coax cable, 1 - yd. Coax plugs, 1.8'. Outlet boxes, 6'. Diplexter crossover boxes, 17.6'. p.p. Aerials, 8'; accessories, 3'. C.W.O. or C.O.D. (min. C.O.D. charge 3.6') 1 - for fully illustrated Lists.

CALLERS WELCOMED  
OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS (Dept. P.E.)  
40-41 Monarch Parade  
London Road, Mitcham, Surrey  
01-648 4884

### OSMABET LTD.

We make transformers amongst other things

#### MAINS TRANSFORMERS

Prim. 200/240V a.c. TX6, 425-0-425V, 500 mA, 6.3V, 6A CT, 0-6-6.3V, 3A, £12.75; TX1, 425-0-425V, 250mA, 6.3V 4A CT, 0-5-6.3V, 3A, £7.50; TX2, 250-0-250V, 150mA, 6.3V 4A CT, 0-5-6.3V, 3A, £4.05; TX3, 300-0-300V, 120mA, 6.3V 2A CT, 0-3-3V, 2A, 6.3V, 1A, £4.05; TX8, 250-0-250V, 65mA, 6.3V, 1.5A, £2.10; MT1, 200V, 30mA, 6.3V, 1A, £1.20; MT2, 230V, 45mA, 6.3V, 1.5A, £1.50; MT2A, 250V, 60mA, 6.3V, 2A, £1.95; MT3 Prim. 110/240V, Sec. 250V, 100mA, 6.3V, 2A, £2.25

#### AUTO TRANSFORMERS

30 to 4kVA, up to 10kVA to order.

#### MULTIVOLT TRANSFORMERS

Prim. 200/240V a.c. OMT4/1. One tapped sec. 5-20-30-40-60V giving 5-10-15-20-25-30-40-45-55-60, 10-10-10, 20-20-20; 30-0-30V a.c. 1A, £2.25; OMT4/2 ditto, 2A, £3.45; OMT3/1 one tapped sec. 40-50-60-80-90-100-110V a.c. 1A, £3.45. Duo 12V 4A-12V 4A £3.60; Duo 0-10-20-25V 2A-0-10-20-25V 2A £3.60

#### LOW VOLTAGE TRANSFORMERS

Prim. 200/240V a.c. 6.3V, 1.5A, 85p; 3A, £1.13; 6A CT, £1.20; 12V, 1.5A, £1.13; 3A CT, £1.80; 6A CT, £2.70; 1.5A CT, £1.80; 2A, 1.5A CT, £1.80; 3A CT, £2.70; 5A, £3.75; 8A, £4.28; 12A, £5.32; 24A CT, £3.45

#### MIDGET RECTIFIER TRANSFORMERS

For FW rect. size 1 1/2 x 2 x 1 1/2 in. Prim. 200/240V a.c. output, PPT1 9-0-9V, 0.3A, PPT2 12-0-12V, 0.25A, PPT3 20-0-20V, 0.15A, £1.20 each; ditto, size 2 x 2 1/2 x 1 1/2 in. MTV1 9-0-9V, 1A, 88p; MTV2 12-0-12V, 1A, MTV3 20-0-20V, 0.75A, £1.20 each

#### O/P TRANSFORMERS FOR POWER AMPLIFIERS

P.P. sec. tapped 3-7.5-15 ohms, A-A 6.6kΩ, 30W (KT66, etc.), £4.05; 50W, 3kΩ, A-A, £6.75; 100W, 3kΩ, A-A, EL34 (KT88, etc.), £11.40 with and to 400V.

#### LOUDSPEAKERS, HI-FI, P.A., GUITAR, ETC.

New boxed famous makes, 25W, £5.60; 35W £7.20; 50W, £9.45; 60W, £13.20; 100W, £19.90; E.M.I. 13 x 8 in. 10W, 3, 8 and 15 ohms, £2.25; fitted two tweeter Hi-Fi, 3, 8 and 15 ohms, £4; Horn tweeter 2-16kH, 8 or 15 ohms, 10W, £1.50; 6in, 90p, 6in, £1.10, 8in, £1.75, 10in, £1.95, 7 x 4in, £1.25, 8 x 6in, £1.35, 10 x 6in, £1.90, 3, 8 and 15 ohms.

#### MATCHING AUTO SPEAKER TRANSFORMER

Match speaker impedance to amplifier from 3 to 8 or 15 ohms, step up or down 10W, 75p

#### 12V LT FLUORESCENT LIGHTING

Complete 8 watt 12 in fitting with tube, £3.75; 12V inverter for 20 watt tube, £5.75.

#### PRINTED CIRCUIT ETCHING KITS

Comprehensive factory pack, with all solutions, and equipment to make your own P.C. boards, instructions, £1.25. Carriage extra all orders

S.A.E. INQUIRIES-LISTS, MAIL ORDER ONLY  
46 Kenilworth Road, Edgware, Middx. HA8 9YG  
Tel. 01-958 9314

# Great new OFFER from

# DIOTRAN

## TRANSISTORS

### BRAND NEW FULLY GUARANTEED DEVICES

AC107	15p	AF115	17p	BC140	35p	BCY31	22p	BF272	80p	EC403	15p	ORP60	40p	2N918	30p	2N2714	25p	2N3704	15p
AC113	30p	AF116	17p	BC141	35p	BCY32	25p	BF273	30p	GET880	27p	ORP61	40p	2N929	25p	2N2904	25p	2N3705	12p
AC115	23p	AF117	17p	BC142	45p	BCY33	17p	BF274	30p	MAT100	15p	ST140	13p	2N1131	20p	2N2905	25p	2N3706	12p
AC125	17p	AF118	30p	BC143	40p	BCY34	20p	BF308	35p	MAT101	17p	ST141	17p	2N1132	22p	2N2906	30p	2N3707	13p
AC126	17p	AF124	21p	BC145	45p	BCY70	17p	BF309	37p	MAT120	15p	TIS43	40p	2N1302	17p	2N2906A	25p	2N3708	8p
AC127	17p	AF125	20p	BC147	17p	BCY71	30p	BF310	75p	MAT121	17p	UT46	27p	2N1303	17p	2N2907	25p	2N3709	8p
AC128	17p	AF126	20p	BC148	12p	BCY72	15p	BFV10	55p	MPF102	43p	V405A	25p	2N1304	20p	2N2907A	30p	2N3710	10p
AC141K	17p	AF127	20p	BC149	17p	BCZ11	20p	BFX29	27p	MPF105	43p	V410A	45p	2N1305	20p	2N2923	13p	2N3711	10p
AC142K	17p	AF129	33p	BC150	17p	BD121	85p	BFX84	20p	OC19	30p	2G301	19p	2N1306	20p	2N2924	13p	2N3820	£1
AC151	15p	AF178	50p	BC151	20p	BD123	85p	BFX85	27p	OC20	30p	2G302	19p	2N1307	20p	2N2925	13p	2N3903	25p
AC154	15p	AF179	50p	BC152	17p	BD124	75p	BFX86	27p	OC22	30p	2G303	19p	2N1308	27p	2N2926	13p	2N3905	25p
AC155	17p	AF180	50p	BC153	27p	BD131	80p	BFX87	25p	OC23	33p	2G304	20p	2N1309	27p	2N2926 (G)	12p	2N3906	27p
AC156	17p	AF191	50p	BC154	30p	BD132	80p	BFX88	22p	OC24	45p	2G306	35p	2N1711	20p	2N2926 (Y)	11p	2N4058	15p
AC157	17p	AF186	45p	BC157	20p	BDY20	£1	BFY50	20p	OC25	25p	2G308	35p	2N1889	35p	2N2926 (O)	10p	2N4059	10p
AC165	17p	AF239	37p	BC159	20p	BF115	22p	BFY51	20p	OC26	25p	2G309	35p	2N1990	35p	2N3010	40p	2N4060	12p
AC166	17p	AFZ11	37p	BC159	20p	BF158	40p	BFY52	20p	OC28	40p	2G339	17p	2N1893	37p	2N3011	20p	2N4061	12p
AC167	20p	AFZ12	45p	BC167	13p	BF118	60p	BFY53	17p	OC29	40p	2G339A	15p	2N2160	60p	2N3011	20p	2N4062	12p
AC168	20p	AL102	85p	BC168	13p	BF119	70p	BSX19	15p	OC35	33p	2G344	15p	2N2147	75p	2N3053	20p	2N5172	12p
AC169	14p	AL103	85p	BC169	13p	BF152	35p	BSX20	15p	OC36	40p	2G345	15p	2N2148	60p	2N3054	50p	2N5459	43p
AC176	23p	ASV26	25p	BC170	12p	BF153	35p	BSY25	15p	OC41	20p	2G371	13p	2N2192	30p	2N3055	63p	25034	75p
AC177	20p	ASV27	30p	BC171	13p	BF154	35p	BSY26	15p	OC42	22p	2G371B	10p	2N2193	30p	2N3391	17p	25031	50p
AC187	30p	ASV28	25p	BC172	13p	BF157	45p	BSY27	15p	OC44	15p	2G374	17p	2N2194	27p	2N3391A	20p	25032A	45p
AC188	30p	ASV29	25p	BC173	13p	BF158	40p	BSY28	15p	OC49	15p	2G377	27p	2N2217	27p	2N3392	17p	25032	50p
AC177	25p	ASV50	25p	BC174	13p	BF159	30p	BSY29	15p	OC70	15p	2G378	15p	2N2218	25p	2N3393	15p	25033	60p
AC18	20p	ASV51	25p	BC175	22p	BF160	30p	BSY38	15p	OC71	9p	2G382	15p	2N2219	27p	2N3394	15p	25034	£1-10
AC19	22p	ASV52	25p	BC177	17p	BF162	30p	BSY39	15p	OC72	12p	2G410	30p	2N2220	22p	2N3395	20p	25035	£1
AC20	20p	ASV54	25p	BC178	17p	BF163	35p	BSY40	15p	OC74	12p	2G414	12p	2N2221	22p	2N3402	22p	25036	£1-10
AC21	20p	ASV55	25p	BC179	17p	BF164	35p	BSY41	15p	OC75	15p	2G417	25p	2N2222	27p	2N3403	22p	25037	£1-10
AC22	19p	ASV56	25p	BC180	20p	BF165	35p	BSY95A	12p	OC76	15p	2N388	30p	2N2368	17p	2N3404	32p	25038	60p
AC27	19p	ASV57	45p	BC181	22p	BF167	22p	BSY95A	12p	OC77	15p	2N388A	50p	2N2369	45p	2N3405	45p	25039	50p
AC28	19p	ASV58	25p	BC182	10p	BF173	22p	BU105	£3-90	OC81	15p	2N404	25p	2N2369A	25p	2N3414	20p	25032A	45p
AC29	30p	ASV58	25p	BC182L	10p	BF176	35p	OC81D	£3-90	OC82	15p	2N404A	30p	2N2411	50p	2N3415	20p	25033A	60p
AC30	25p	ASZ21	40p	BC183	10p	BF177	35p	OC82	15p	OC82	15p	2N524	55p	2N2412	50p	2N3417	37p	25034	£1-20
AC31	25p	BC107	10p	BC183L	10p	BF178	45p	OC82D	15p	OC82D	15p	2N527	60p	2N2416	55p	2N3525	74p	25035	£1-20
AC34	18p	BC108	10p	BC184	13p	BF179	50p	OC83	20p	OC83	20p	2N696	12p	2N2711	22p	2N3702	12p	25036	£1-20
AC35	18p	BC109	11p	BC184L	13p	BF180	30p	OC84	20p	OC84	20p	2N697	12p	2N2712	22p	2N3703	12p	25037	£1-20
AC36	30p	BC113	25p	BC186	27p	BF181	30p	OC139	15p	OC139	15p	2N698	24p	2N2712	22p	2N3702	12p	25037	£1-20
AC40	15p	BC114	30p	BC187	27p	BF182	30p	OC140	17p	OC140	17p	2N699	55p	2N2712	22p	2N3702	12p	25037	£1-20
AC41	18p	BC115	30p	BC207	11p	BF183	30p	OC170	15p	OC170	15p	2N706	7p	2N2712	22p	2N3702	12p	25037	£1-20
AC44	35p	BC116	35p	BC209	11p	BF184	25p	OC171	15p	OC171	15p	2N706A	8p	AA119	8p	BYZ11	32p	OA81	7p
AD140	40p	BC117	35p	BC209	11p	BF185	30p	OC200	25p	OC200	25p	2N708	12p	AA120	8p	BYZ12	30p	OA85	7p
AD142	40p	BC118	25p	BC212L	11p	BF188	30p	OC201	27p	OC201	27p	IN709	45p	BA116	22p	BYZ13	25p	OA90	6p
AD149	43p	BC119	45p	BC213L	11p	BF194	30p	C720	12p	OC202	27p	2N711	40p	BA126	22p	BYZ16	35p	OA91	7p
AD161	35p	BC125	35p	BC213L	11p	BF195	34p	C722	25p	OC203	25p	2N717	45p	BY100	15p	BYZ17	35p	OA95	7p
AD162	35p	BC126	35p	BC214L	12p	BF196	30p	C740	25p	OC204	25p	2N718	24p	BY101	12p	BYZ18	30p	OA200	6p
AD161/162(MP)	63p	BC132	25p	BC225	25p	BF197	35p	C742	17p	OC205	35p	2N718A	50p	BY105	15p	BYZ19	25p	OA202	7p
AD1140	50p	BC134	30p	BC226	35p	BF200	45p	C744	17p	OC309	35p	2N726	27p	BY114	12p	OA5	17p	SO10	4p
AD11	£1	BC135	30p	BC317	12p	BF222	80p	C760	17p	P346A	17p	2N727	27p	BY126	15p	OA10	22p	SO19	4p
ADZ11	£1	BC136	30p	BC318	12p	BF257	35p	C762	17p	P397	45p	2N743	17p	BY127	17p	OA47	7p	IN914	6p
ADZ12	£1-10	BC137	35p	BC319	12p	BF270	25p	C764	60p	OCP71	43p	2N744	17p	BY130	15p	OA70	7p	IN916	6p
AF114	17p	BC139	45p	BCY30	20p	BF271	17p	EC401	15p	ORP12	43p	2N914	17p	BYZ10	35p	OA79	8p	IN4148	6p

### DIODES & RECTIFIERS

AA119	8p	BYZ11	32p	OA81	7p
AA120	8p	BYZ12	30p	OA85	7p
BA116	22p	BYZ13	25p	OA90	6p
BA126	22p	BYZ16	35p	OA91	7p
BY100	15p	BYZ17	35p	OA95	7p
BY101	12p	BYZ18	30p	OA200	6p
BY105	15p	BYZ19	25p	OA202	7p
BY114	12p	OA5	17p	SO10	4p
BY126	15p	OA10	22p	SO19	4p
BY127	17p	OA47	7p	IN914	6p
BY130	15p	OA70	7p	IN916	6p
BYZ10	35p	OA79	8p	IN4148	6p

### 1,000,000 SILICON PLANAR NPN-PNP PLASTIC AND TRANSISTORS METAL CAN TYPES

Clearance of manufacturers' seconds, selected in types and guaranteed no open or short circuit units. Ideal cheap transistors for radio enthusiasts, manufacturers, schools and colleges.

**TYPE STN18.** Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: 2N706, 2N2220, BSY27-95A, BSX44-76-77.

Price: 500 £9, 1,000 £15

**TYPE STP18.** Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: BCY70-72, 2N2906-7, 2N2411 and BC186-7. Also used as complementary to the above npn type device type STN18.

Price: 500 £9, 1,000 £15

**TYPE STNL.** Silicon Plastic Epitaxial Planar Transistors TO-92 case. I.C. 200mA, 300mW medium to high gain, available in npn or pnp and types similar to: NPN2N2926-2N2711-2N3391-2N3707-2N3711-BC167-8-9.

Price: 500 £7 50; 1,000 £13

**TYPE STPL.** As above but in pnp and similar to types 2N5354-56, 2N4058-2N4061 and 2N3702-3. Also used as complementary to the above npn devices type STNL.

Price: 500 £7 50; 1,000 £13

**TYPE STNK.** Silicon Planar Plastic Transistor npn with TO-18 pin circular lead configuration. I.C. 200mA, 300mW and similar to BC107-8-9, BC170, BC173, BC182-184, BC237-8-9 and BC337-8.

Price: 500 £9 50; 1,000 £16

When ordering, please state type required, i.e., STNK or STN18, etc.

### 1,000,000 SILICON TRANSISTORS FOR SALE

Clearance of npn Silicon Transistors from the 25300 (TO-5) and 25320 (SO-2) range and similar to the GC200-205 and BCY30-34 series. Ideal for Amateur Electronics, Radio Hams and for experimental use in Schools, Colleges and Industry.

Approximate count by weight:  
 100 off—75p (plus p. & p. 10p)  
 300 off—£1-75 (plus p. & p. 15p)  
 500 off—£2 50 (plus p. & p. 17½p)  
 1,000 off—£4 (plus p. & p. 25p)  
 10,000 off—£35 (plus p. & p. 55p)

Large quantities quoted for on request. EXPORT INQUIRIES WELCOME

## DIOTRAN SALES

PO BOX 5, WARE, HERTS

Full Money-Back Guarantee

POSTAGE & PACKING 7p

### 10 MILLION DIODES

Silicon or Germanium

State which when ordering

200	50p	10,000	£10-00
1,000	£2-00	50,000	£30-00
5,000	£7-00	100,000	£50-00

### 2,000,000 SILICON PLANAR TRANSISTORS TO18 P.N.P. & N.P.N. TYPES

State which when ordering

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way.*

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s Simplified Study Method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

**You LEARN—but it's as fascinating as a hobby.**

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a "non-technical" type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

### New Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of "OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO". This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.



## FREE

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B12, ALDERMASTON COURT, READING RG7 4PF

### POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B12, Aldermaston Court, Reading RG7 4PF  
Please send books and full information — free and without obligation.




NAME..... AGE.....

ADDRESS.....

OCCUPATION.....

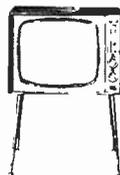**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**



### EX RENTAL TV's

19" — £29-95

23" — £39-95

All Channels 405/625  
**2 Years Guarantee.**  
Free List by return.

17" Slim Line TV's £11-95, 19" Slim Line TV's £15-95. Guaranteed 2 years. Send for List. Carr. & Ins. all sets £1-95. Daily demonstrations to personal shoppers.

### TEAK HI-FI STEREO CABINETS £14-95

Brand New 44" wide x 16" deep x 18" high with Legs. A superb piece of furniture. Carr. £1-00.

TRANSISTOR GANG CONDENSERS 30p. MINIATURE AM POST 5p. PRECISION TAPE MOTORS £1-95. 200/240V. POST 20p.

Transistor Radio Cases: 25p each.  
Size 9 1/2" x 6 1/2" x 3 1/2". P. & P. 15p.  
SPEAKERS 50p 2 1/2" 8Ω BRAND NEW. P. & P. 5p.

### TRANSISTORS Post Free

AC 126 AF 179 OC 81  
AC 128 OC 44 OC 81D  
AF 114 OC 45  
AF 117 OC 71 15p each

### POTENTIOMETERS 23p each

Double & Switched	500 KΩ/500 KΩ	3 1/2" shaft
Double & Switched	500 KΩ/100 KΩ	2" shaft
Double & Switched	1 MEG/100 KΩ	1 1/2" shaft

Post. & Pack. 5p.—4 for 10p

### KNOBS 100,000 to clear (Brand New)

100 assorted Radio & T.V. knobs 50p. Postage 25p. (If you require sets 2 to 6 just ask)


## DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12

Phone 01-478 6001-2-3

Stamp for Free List

### TV TUBES REBUILT GUARANTEED 2 YEARS

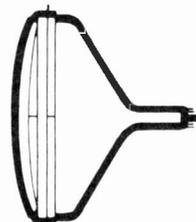

14"—£3-95, 17" & 19"—£5-95,  
21" & 23"—£6-45.

Exchanged Bowls. Carr. 53p.

# FERRANTI

### SEMICONDUCTORS AT LOWEST PRICES

ZTX107 10p	ZTX501 11p	ZS142 30p	K8036A 17p
ZTX108 9p	ZTX502 15p	ZS170 9p	K8039A 17p
ZTX109 10p	ZTX503 12p	ZS171 11p	K8043A 17p
ZTX300 10p	ZTX504 39p	ZS172 14p	K8047A 17p
ZTX301 11p	ZTX510 15p	ZS174 15p	K8051A 17p
ZTX302 15p	ZTX530 19p	ZS176 21p	K8056A 17p
ZTX303 12p	ZTX531 20p	ZS178 34p	K8062A 17p
ZTX304 18p	BF859 15p	ZS270 10p	K8068A 17p
ZTX310 7p	BF860 19p	ZS271 14p	K8075A 17p
ZTX311 9p	BF861 19p	ZS272 15p	K8082A 17p
ZTX312 9p	BF896 16p	ZS274 17p	K8091A 17p
ZTX313 10p	BF897 21p	ZS276 23p	K8100A 17p
ZTX314 11p	BF898 21p	ZS278 33p	K8110A 17p
ZTX320 28p			K8120A 17p
ZTX330 18p	Diodes	Zeners	K8130A 17p
ZTX331 14p	ZS140 22p	K8030A 17p	K8130A 17p
ZTX500 10p	ZS141 39p	K8033A 17p	K8150A 17p

Postage and Packing 10p. Free above £2. Send S.A.E. for data.

**DAVIAN ELECTRONICS**  
P.O. Box 38, Oldham, Lancs.

### BUILD THIS WAH-WAH PEDAL KIT



AND SAVE £££'s

The Wilcic Wah-Wah pedal comprises a **SELECTIVE AMPLIFIER MODULE KIT**, containing all the components to build a two transistor circuit module, which may be used by the constructor for his own design or fitted to the **FOOT VOLUME CONTROL PEDAL** (as photo) converting it to Wah-Wah operation. This pedal is in strong fawn plastic and fitted with output lead and screened plug.

Please send me  
Selective amplifier module £1-75  
Foot Volume control pedal £5-13  
**COMPLETE KIT £6-50**  
add 38p for assembly of module  
Send 15p for latest catalogue

Name.....

Address.....

\*Tick as required

**WILSIC ELECTRONICS LTD.**  
6 COPLEY RD. DONCASTER, YORKS.

# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS! CLEAR PLASTIC METERS BAKELITE PANEL METERS

TYPE SW. 100 100 x 80 mm		TYPE S-80 80 mm square fronts	
500µA	23-12	50µA	23-12
1mA	23-71	50-0-500µA	23-97
50-0-500µA	23-37	100µA	23-97
20V d.c.	23-90	100-0-100µA	23-87
50V d.c.	23-97	500µA	23-82
300V d.c.	23-97	1A d.c.	23-47
1A d.c.	23-97	20V d.c.	23-47
50-0-50µA	23-37	5A d.c.	23-47
100µA	23-37	300V a.c.	23-82
100-0-100µA	23-25	VU Meter	23-71

### "SEW" CLEAR PLASTIC METERS


Type MR.35P. 4 1/2in. 4 1/2in. fronts.		Type MR.38P. 1 21/32in square fronts.	
50µA	23-60	150mA	21-80
500-0-500µA	23-30	200mA	21-87
100µA	23-10	300mA	21-87
100-0-100µA	23-10	500mA	21-87
200µA	23-87	750mA	21-87
500µA	23-75	1A	21-87
500-0-500µA	23-60	2A	21-87
1mA	23-60	5A	21-87
1-0-1mA	23-60	10A	21-87
5mA	23-60	20mA	21-87
10mA	23-60	50mA	21-87
		100mA	21-87
		200µA	21-75
		500µA	21-50
		500-0-500µA	21-37
		1-0-1mA	21-37
		1mA	21-37
		2mA	21-37
		5mA	21-37
		10mA	21-37
		20mA	21-37
		50mA	21-37
		100mA	21-37

Type MR.55P. 2 1/2in square fronts.		Type MR.45P. 2in square fronts.	
50µA	23-10	50µA	23-25
50-0-50µA	23-60	50-0-50µA	23-10
100µA	23-60	100µA	23-10
100-0-100µA	23-37	100-0-100µA	23-10
500µA	23-25	200µA	21-87
1mA	23-20	500µA	21-60
5mA	23-20	500-0-500µA	21-50
10mA	23-20	1mA	21-50
		10mA	21-50
		50mA	21-50
		100mA	21-50
		500mA	21-50
		1A	21-50
		5A	21-50
		10V d.c.	23-00

Type MR.65P. 3 1/2in. 3 1/2in. fronts.		Type MR.65 3 1/2in square fronts.	
50µA	23-37	500µA	21-75
50-0-50µA	23-75	1A	21-75
100µA	23-75	5A	21-75
100-0-100µA	23-60	15A	21-75
200µA	23-60	30A	21-75
500µA	23-37	50A	21-75
500-0-500µA	23-10	5V d.c.	21-75
1mA	23-10	10V d.c.	21-75
5mA	23-10	20V d.c.	21-75
10mA	23-10	50V d.c.	21-75
50mA	23-10	150V d.c.	21-75
100mA	23-10	300V d.c.	21-75
500µA	23-10	30V a.c.	21-75
500-0-500µA	23-10	50V a.c.	21-75
1A	23-10	150V a.c.	21-75
5A	23-10	300V a.c.	21-75
10A	23-10	500mA a.c.	21-75
50A	23-10	1A a.c.	21-75
5V d.c.	23-10	5A a.c.	21-75
10V d.c.	23-10	10A a.c.	21-75
		20A a.c.	21-75
		30A a.c.	21-75

**\* MOVING IRON — ALL OTHERS MOVING COIL**  
 Please add postage


### "SEW" EDUCATIONAL METERS

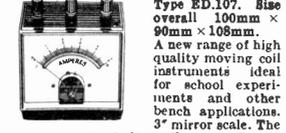

Type ED.107. Size overall 100mm x 90mm x 108mm.  
 A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The easily accessible to demonstrate internal working. Available in the following ranges:

50µA	24-50	20V d.c.	23-97
100µA	24-25	50V d.c.	23-97
1mA	23-97	300V d.c.	23-97
50-0-50µA	24-25	5V/50V d.c.	24-25
1-0-1mA	23-97		
1A d.c.	23-97		
5A d.c.	23-97		
10V d.c.	23-97		

### EDGWISE METERS

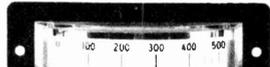

PE.70 3 17/32in 1 15/32in 2 1/2in deep.

50µA	23-00	500µA	23-60
50-0-50µA	23-87	1mA	23-71
100µA	23-87	300V a.c.	23-71
100-0-100µA	23-25	VU meter	23-25
200µA	23-75		

# MULTIMETERS for EVERY purpose!

**TECH PT-34.** 1,000 O.P.V. 0/10/50/250/500/1,000V a.c. and d.c. 0/1/100/500mA. d.c. 0/100K. **21-97.** P. & P. 12 1/2p.

**MODEL TE-300.** 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V d.c. 0/50/250/1,000V a.c. 0/50µA/250MA. 0/60K/6 meg. **23-75.** P. & P. 15p.

**MODEL TE-70.** 30,000 O.P.V. 0/3/15/60/300/600/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30µA/3/30/300MA. 0/16K/160K/1-6M/16 meg. **23-50.** P. & P. 15p.

**MODEL TE12.** 20,000 O.P.V. 0/0-6/30/120/600, 1,200/3,000/6,000V d.c. 1/6/30/120/600/1,200V a.c. 0/60µA/6/60/600MA/0/6K/600K/6meg/60. Megohm 50PF. 2 MFD **23-97.** P. & P. 17 1/2p.

**MODEL PL43B.** 20kΩ/Volt d.c. 8kΩ/Volt a.c. Mirror scale. 0/6/3/12/30/120/600V d.c. 3/30/120/600V a.c. 50/600µA/60/600MA. 10/100K/1Meg/10 meg. — 20 to +63dB. **23-97.** P. & P. 12 1/2p.

**MODEL 500.** 30,000 O.P.V. with overload protection, mirror scale 0/5/2-5/10/25/100/250/500/1,000V d.c. 0/2-5/10/25/100/250/500/1,000V a.c. 0/50µA/500/500 mA. 12 amp. d.c. 0/60K/6 Meg/60 Meg. **23-87.** Post paid.

**TMK MODEL TW-20CB.** Features Resettable Overload Button. Sensitivity: 20KΩ/Volt d.c. 5KΩ/Volt a.c. D.c. volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. D.c. currents: 0-0.05, 0.5, 5, 50, 500mA. Resistance: 0-5K, 50K, 0-500K, 5 meg. Decibels: — 20 to +52dB. **21-50.** P. & P. 17 1/2p.

**TMK LAB TESTER.** 100,000 O.P.V. 6 1/2in scale buzzer short circuit check. Sensitivity: 100,000 Ω/V d.c. 5/10V a.c. D.c. volts: 0-2.5, 10, 50, 250, 1,000V. D.c. current: 10, 100µA, 10, 100, 500mA, 2.5, 10A. Resistance: 1K, 10K, 100K, 10 meg, 100 meg. Decibels: — 10 to +49dB. Plastic case with carrying handle, size 7 1/2in x 6 1/2in x 3 1/2in. **21-90.** P. & P. 25p.

**270° WIDE ANGLE 1mA METERS**  
 MW1-6 60mm square **23-97.** MW1-8 80mm square **24-97.** P. & P. extra.

**T.E.40 HIGH SENSITIVITY A.C. VOLTMETER**  
 10 meg. input 10 ranges: -01/003/1/3/10/30/300/3000 R.M.S. 4c/a-1-2Mc/s. Decibels — 40 to +60dB. Supplied brand new complete with leads and instructions. **21-70.** P. & P. 30p. Additional Probes available: R.F. **22-12.** H.V. **22-50.**

**TE-65 VALVE VOLTMETER**  
 High quality instrument with 28 ranges. D.c. volts 1-5-1,500V. A.c. volts 1-5-1,500V. Resistance up to 1,000 megohms, 220/240V a.c. operation. Complete with probe and instructions. **21-70.** P. & P. 30p. Additional Probes available: R.F. **22-12.** H.V. **22-50.**

**HONOR TE.10A.** 20kΩ/Volt 5/25/50/250/500/2,500V d.c. 10/50/100/500 1,000V a.c. 0/50µA/2-5mA 250mA d.c. 0/6K/6 meg. ohm. — 20 to +22dB. 10-0/100 mfd. 0-100-0-1 mfd. **23-47.** P. & P. 15p.

**MODEL TE-300.** 30,000 O.P.V. Mirror scale, overload protection 0/0-5/15/60/300/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30µA/6mA/60mA/300MA/600MA. 0/8K/80K/800K/8 meg. — 20 to +63dB. **23-97.** P. & P. 15p.

**TMK MODEL MD.120.** Mirror scale. 20kΩ/Volt d.c., 10kΩ/Volt a.c. 30/60/300/600/3,000V d.c. 6/120/1,200V a.c. Current — 60µA/0-12/0-300mA. 0-60K/0-63MΩ. — 20 to +63dB. **24-82.** P. & P. 15p.

**MODEL TE-90.** 50,000 O.P.V. Mirror scale, overload protection. 0/3/15/60/300/600/1,200V d.c. 0/6/30/120/300/1,200V a.c. 0-0-0-3/60/600MA. d.c. 16K/160K/1-6/16 meg. — 20 to +63dB. **27-50.** P. & P. 15p.

**SKYWOOD SW-500**  
 50 KΩ/Volt. Mirror scale. D.c. Volts 0/6/3/12/30/300/600V. AC Volts 3/30/300/600. DC Current 20µA/6/60/600mA. Resistance 10K/100K/1Meg/10 Meg. Decibels — 20 to +57dB. **27-50.** P. & P. 15p.

**MODEL AS-100D.** 100KΩ/Volt. 5in. mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200V d.c. 0/6/30/120/300/600V a.c. 0/10µA/6/60/300MA/12A. 0/2K/200K/2M/200M. — 20 to +17dB. **21-50.** P. & P. 17 1/2p.

**TE-900 20,000Ω/VOLT GIANT MULTIMETER.** Mirror scale and overload protection. 6in full view meter. 2 colour scale. 0/2-5/10/250/1,000/5,000V a.c. 0/25/12-5/10/50/250/1,000/5,000V d.c. 0/50µA/110/100/500MA/10A d.c. 0/2K/200K/2 meg. ohm. **21-5.** P. & P. 25p.

**FTC-401 TRANSISTOR TESTER**  
 Full capabilities for measuring A, B and IC0, *npn* or *ppn*. Equally adaptable for checking diodes. Supplied complete with instructions, probes and leads. **23-97.** P. & P. 15p.

**HONEYWELL DIGITAL VOLTMETER VT.100**  
 Can be panel or bench mounted. Basic meter measures 1 volt d.c. but can be used to measure a wide range of a.c. and d.c. volt, current and ohms with optional plug-in cards. Specification:— Accuracy: ± 0.2%, ± 1 digit. Resolution: 1mV. No. of digits: 3 1/4 (fourth overrange digit. Overrange: 100%, (up to 1999) Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V d.c. Input: Fully floating (3 poles). Input power: 110-230V a.c. 50/60 cycles. Overall size: 5 1/2in x 2 1/2in x 8 3/16in AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE **24-97-97** Carr. 50p

**G. W. SMITH & CO (RADIO) LTD.**  
 Also see next two pages

# SEMI-CONDUCTORS/VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

## TRANSISTORS

2C301	20p	2N3934	15p	2N3935	45p	BF154	38p	GET898	22p	CA3000	1.80	FCY101	11.00	SN7400	25p	0A2	38p	23L6	45p	FL85	43p
2C302	10p	2N3402	22p	2N3935	37p	AF181	40p	BF158	28p	CA3003	1.17	FJH101	25p	SN7401	25p	0B2	45p	23L7	45p	FL86	43p
2C303	20p	2N3403	22p	2N3936	40p	BF186	30p	BF159	57p	CA3007	1.82	FJH111	70p	SN7410	50p	0B24	30p	23Z5	42p	EL05	35p
2C306	30p	2N3404	32p	2N3937	37p	AF239	30p	BF163	35p	CA3011	75p	FJH121	25p	SN7420	25p	1L4	20p	23Z6	65p	EM80	40p
2C308	30p	2N3405	45p	2N3938	37p	AF279	47p	BF167	25p	CA3012	85p	FJH131	25p	SN7430	25p	1R5	35p	30C15	60p	EM81	50p
2C309	30p	2N3414	22p	2N3939	82p	AF280	47p	BF170	33p	CA3020	1.07	FJH141	25p	SN7440	25p	1R5	25p	30C17	65p	EM84	35p
2C371	15p	2N3415	42p	2N3910	42p	AF211	32p	BF173	30p	CA3024	1.12	FJH151	25p	SN7441AN	11	1T4	25p	30C18	75p	EM85	42p
2C374	20p	2N3416	27p	2N3934	27p	AS726	25p	BF177	30p	CA3025	1.28	FJH161	70p	SN7442	11	1C4	42p	30P11	70p	EY34	40p
2C381	22p	2N3417	27p	2N3935	27p	AS727	31p	BF178	25p	CA3018A	1.10	FJH171	25p	SN7446	11	1U5	50p	30P12	70p	EY38	40p
2N388A	42p	2N3439	1.30	2N3936	38p	AS728	24p	BF179	30p	CA3019	84p	FJH181	25p	SN7447	11.10	2D21	35p	30P13	70p	EY88	40p
2N404	21p	2N3440	97p	2N3665	47p	AS729	27p	BF180	35p	CA3020	1.28	FJH221	25p	SN7448	11	3Q4	40p	30P14	70p	EY87	42p
2N696	15p	2N3454	17p	2N3666	38p	AS730	25p	BF181	35p	CA3020A	1.00	FJH231	25p	SN7450	25p	3R4	35p	30L15	85p	EZ40	45p
2N697	16p	2N3565	15p	2N3667	37p	AS731	32p	BF182	30p	CA3021	1.50	FJH241	25p	SN7451	25p	3V4	45p	30L17	80p	EZ41	45p
2N698	25p	2N3566	22p	2N3457	48p	AS734	25p	BF184	25p	CA3022	1.30	FJH251	25p	SN7453	25p	3R4	40p	30P12	80p	EZ80	25p
2N699	25p	2N3567	25p	2N3458	48p	AS737	45p	BF185	25p	CA3023	1.28	FJH261	50p	SN7454	25p	3U4	42p	30P19	80p	EZ81	28p
2N706	11p	2N3570	1.25	2N3910	45p	AS786	32p	BF194	17p	CA3028	1.1	FJH111	60p	SN7460	35p	3V4	35p	30P19	70p	EZ82	48p
2N708	15p	2N3572	97p	2N103	25p	AS221	37p	BF195	15p	CA3028A	74p	FJH121	60p	SN7472	40p	3Y3	32p	30P13	80p	EZ84	30p
2N709	45p	2N3657	97p	2N103	25p	AU110	1.50	BF196	15p	CA3028B	1.05	FJH131	60p	SN7473	45p	4Z4G	40p	30P14	90p	KT86	22.05
2N718	25p	2N3606	27p	2N801	25p	BC107	10p	BF197	10p	CA3029	87p	FJH141	11.25	SN7474	45p	630L2	75p	35L6	40p	KT88	22
2N726	25p	2N3607	27p	2N802	25p	BC109	10p	BF198	40p	CA3029A	1.65	FJH181	75p	SN7475	45p	6A7G	25p	33W4	30p	MU14	60p
2N727	25p	2N3638A	80p	2N804	75p	BC114	15p	BF199	45p	CA3030	1.37	FJH191	65p	SN7476	45p	6A7G	40p	33Z4	30p	PA3C80	40p
2N914	17p	2N3641	18p	2N805	75p	BC115	15p	BF207	30p	CA3031	1.28	FJH201	11.25	SN7483	45p	6A7G	30p	33Z5	40p	PC86	60p
2N916	17p	2N3642	18p	2N802	35p	BC116	15p	BF238	30p	CA3036	72p	FJH251	11.25	SN7486	60p	6A7G	30p	50C5	40p	PC87	60p
2N918	30p	2N3643	20p	2N803	27p	BC118	15p	BF244	32p	CA3041	1.09	FJY101	25p	SN7492	11	6AM6	33p	80	50p	PC90	48p
2N929	22p	2N3644	25p	2N863	40p	BC119	47p	BFW61	47p	CA3042	1.09	IC10	22.50	SN7493	11	6AQ5	33p	85A2	40p	PC94	40p
2N930	24p	2N3645	25p	2N128	70p	BC121	20p	BFW87	25p	CA3043	1.37	IC12	22.50	SN7495	11	6AR6	37p	807	50p	PC95	40p
2N987	25p	2N3689	15p	2N140	72p	BC129	15p	BFW89	25p	CA3044	1.20	L800	40p	SN7496	11	6AT6	20p	16Z5	50p	PC98	55p
2N1090	22p	2N3692	18p	3N141	72p	BC125	15p	BFW89	20p	CA3045	1.24	MC792P	65p	SN74107	45p	6AV6	30p	6146	1.50	PC180	55p
2N1091	22p	2N3693	15p	3N142	55p	BC126	25p	BFW90	20p	CA3047	1.17	MC724P	65p	SN74103	1.90	6BA6	25p	AZ31	50p	PCF80	30p
2N1131	25p	2N3694	18p	3N143	67p	BC134	15p	BFW91	30p	CA3048	1.24	MC780P	22.47	SN74154	22.20	6BE6	30p	CY31	25p	PCF82	34p
2N1132	25p	2N3702	12p	3N152	87p	BC135	15p	BFX12	22p	CA3049	1.40	MC788P	62p	SN74161	22.20	6BH6	45p	DAF91	25p	PCF84	50p
2N1802	17p	2N3703	10p	40050	55p	BC136	15p	BFX13	22p	CA3050	1.84	MC790P	11.24	SN74164	22.20	6BJ6	45p	DAF96	42p	PCF86	60p
2N1803	17p	2N3704	10p	40050	55p	BC147	15p	BFX29	32p	CA3051	1.24	MC792P	65p	SN74165	22.25	6BQ7A	40p	DF91	25p	PCF80	60p
2N1804	22p	2N3705	10p	40251	35p	BC138	37p	BFX30	30p	CA3052	1.24	MC799P	65p	SN74166	22.25	6BR8	65p	DF96	30p	PCF86	60p
2N1805	22p	2N3706	10p	40300	32p	BC140	30p	BFX37	30p	CA3053	1.49	MC838P	25.45	SN74192	22.25	6BR8	65p	DK91	35p	PCF80	50p
2N1806	24p	2N3707	12p	40309	45p	BC141	35p	BFX44	37p	CA3054	1.09	MC1303L2	22.62	SN74193	22.25	6BR8	65p	DK92	50p	PCF80	50p
2N1807	24p	2N3708	8p	40311	35p	BC147	15p	BFX68	67p	CA3055	1.40	MC1304P2	22.75	SN74194	22.25	6BW7	70p	DK96	42p	PCF86	70p
2N1808	25p	2N3709	10p	40312	47p	BC148	11p	BFX84	11p	CA3059	1.45	MC1305P2	22.86	SN74195	22.25	6BZ6	35p	DL92	35p	PCF80	60p
2N1809	25p	2N3710	10p	40314	32p	BC149	15p	BFX85	25p	CA3064	1.20	MC1435P	22.45	SN74166	22.25	6C4	33p	DL94	45p	PCF82	35p
2N1807	25p	2N3711	10p	40315	37p	BC152	17p	BFX86	25p	CA3064	1.20	MC1435P	22.45	SN74166	22.25	6C4	33p	DL94	45p	PCF82	35p
2N1813	21p	2N3713	1.87	40316	47p	BC153	35p	BFX87	25p	CA3067	1.11	MC1709CG	94p	SN74293	97p	6CL6	50p	DM70	32p	PCF84	45p
2N1831	35p	2N3714	22	40317	37p	BC154	35p	BFX88	25p	CA3068	1.05	MFC4000P	25p	SN74300	11	6CW4	35p	DM86	35p	PCF85	40p
2N1832	30p	2N3715	22	40319	55p	BC157	15p	BFX89	65p	CA3069	1.11	MC1709CG	94p	SN74301	11	6F1	62p	DM87	35p	PCF86	45p
2N1833	30p	2N3716	22	40320	47p	BC158	15p	BFX93A	70p	CA3070	1.05	PA222	24.37	SN74302	72p	6F64	30p	DM88	65p	PCF200	70p
2N1834	27p	2N3717	22	40321	32p	BC159	15p	BFY11	42p	CA3071	1.05	PA230	21	SN74303	11	6F64	33p	DM89	65p	PCF86	50p
2N1839	27p	2N3791	22	40324	47p	BC160	35p	BFY18	55p	CA3072	1.05	PA237	21.85	SN74304	11	6F14	65p	EA3C80	35p	PCF81	50p
2N1701	1.10	2N3819	34p	40326	30p	BC167	15p	BFY19	25p	CA3073	1.05	PA246	22.45	SN74305	11	6F18	65p	EA3F2	35p	PCF82	45p
2N1889	32p	2N3823	75p	40344	27p	BC168B	40p	BFY21	42p	CA3074	1.05	PA264	24.47	SN74306	11	6F23	60p	EA3J1	30p	PCF83	45p
2N1893	32p	2N3824	75p	40347	27p	BC169B	40p	BFY29	42p	CA3075	1.05	PA265	24.97	SN74307	11	6F23	60p	EA3J2	30p	PCF84	45p
2N2147	25p	2N3834	27p	40348	27p	BC169C	40p	BFY30	40p	CA3076	1.10	PA266	24.97	SN74308	11	6F23	60p	EA3J3	30p	PCF85	45p
2N2160	57p	2N3852A	27p	40360	42p	BC170	15p	BFY41	40p	CA3077	1.10	PA267	24.97	SN74309	11	6F23	60p	EA3J4	30p	PCF86	45p
2N2193	40p	2N3853A	30p	40361	47p	BC171	15p	BFY42	40p	CA3078	1.10	PA268	24.97	SN74310	11	6F23	60p	EA3J5	30p	PCF87	45p
2N2193A	40p	2N3854	30p	40362	47p	BC172	15p	BFY50	22p	CA3079	1.10	PA269	24.97	SN74311	11	6F23	60p	EA3J6	30p	PCF88	45p
2N2194	42p	2N3856A	35p	40370	32p	BC175	22p	BFY51	20p	CA3080	1.10	PA270	24.97	SN74312	11	6F23	60p	EA3J7	30p	PCF89	45p
2N2194A	42p	2N3858	25p																		



# Practical Electronics Classified Advertisements

RATES: 7½p per word (minimum 12 words). Box No. 7½p extra. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD

## MISCELLANEOUS

### NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for HOUSE-TO-HOUSE USE, SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.20 NOW

TO: 'BOFFIN PROJECTS'  
DEPT. KE2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

### ★ ELECTRONIC MUSIC ★

Ring Modulators • Electronic Phasing Oscillators • Sub-Octave Generators  
Fuzz and Waa-Waa • White Sound  
Complete units or P.C. assemblies

3p stamp for fullest details, from:

**TAYLOR ELECTRONIC MUSIC DEVICES**  
TEGID HOUSE - BALA - MERIONETH

### INSTRUMENT KITS

New range of laboratory instruments in kit form! Sine-square wave oscillator, Pulse generator, Distortion meter, Frequency meter. E.g. sine-square wave oscillator kit <1% distortion at 10Vpp and <100ns square wave rise time.—£25.

Send SAE for literature to:—

**INTEK ELECTRONICS LTD.**  
4 Lowfield Lane, Hoddesdon, Herts.

### JOHN SAYS . . .

**RING MODULATOR** by Dewtron is professional, transformerless, 5-transistor, has adjustable FI F2 rejection. Module £7. Unit £8.90. **WAA-WAA** Pedal kit of all parts, including all mechanics and instructions ONLY £2.45. **AUTO RHYTHM** from Dewtron modules. Simple unit for waltz, fox-trot, etc. Costs £16.55 in modules. **ORGAN PERCUSSION** and other fascinating effects. Send 15p for illustrated list. **D.E.W. LTD.**, 254 Ringwood Road, Ferndown, Dorset

### TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or

Any 12 transistors for only £1

ACV22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708


Money back guarantee. P. & P. 10p.

J. M. KING (J)

17 Buckridge, Portpool Lane, London, E.C.1

**PRINTED CIRCUITS.** Capacity now available for prototype or production runs. Artworks, Photographs, Etched S.A.E.s, and Assembly. Fast turn round. Send S.A.E.s for quotations. Also copper laminated fibreglass board. Single sided 1½p per sq. inch. Double sided 2½p per sq. inch. Any size cut. Minimum order 50p. P. P. plus 10%. **SYSTEMATICS**, 18 Pennine Road, Millbrook, Southampton, Hants.

## MISCELLANEOUS (continued)

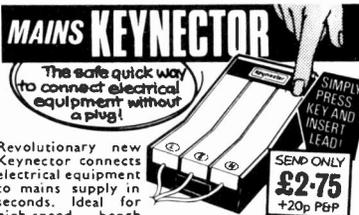

Revolutionary new Keynector connects electrical equipment to mains supply in seconds. Ideal for high-speed bench testing, shop demonstrations or do-it-yourself experts. Keynector can take multi-parallel connections up to 13 amp. maximum loading off one mains point, is easy to operate, and pays for itself by saving time. Safety features include wall or bench fixing, built-in safety switch with 13 amp. fuse, no protruding parts eliminates accidental shocks, special neon safety light shows Keynector is working. As selected for the Design Centre.

**MARKTYME** (MAIL ORDER) LTD Dept. PE1  
72 Willesden Lane  
London, N.W.6  
01-624 6643

**BARGAINS P.S.U.'S**, test gear, lists S.A.E. DON SMITH, 12 Channel Heights, Weston-super-Mare, Somerset.

**3 WATT TRANSISTORISED AUDIO AMPLIFIER.** Volume, tone controls, input: Crystal Cartridge. Output for 12-15Ω speaker. Supply 18-24V. £2.90 post paid. M. COOK, 314 Spinney Hill Road, Northampton.

### TOP MANUFACTURERS' PRODUCTS AT TRADE PRICES!!!

**ADCOLA SOLDERING IRONS AND ACCESSORIES:** 60/40 SOLDER

**ELECTROSIL RESISTORS:** TR4, TR5, TR6, TR8, C5

**T.M.C. RELAYS, PUSH BUTTON KEYS AND LEVER KEYS**

**B.I.C.C. P.V.C. EQUIPMENT WIRE—ALL COLOURS**

Send large s.a.e. for price lists

**SPEEDY COMPONENTS SUPPLY LTD.**

High Street - Handcross  
Haywards Heath - Sussex  
Handcross S69

CALLERS WELCOME

### PSYCHEDELIC LUMINOPHONICS

Or is this just another way of referring to FANTASY? Either way, our Projects 24 and 1014 probably come within this category—THINK OF THE FUN YOU WOULD HAVE WITH SOMETHING LIKE THIS AT A PARTY! There are MANY OTHER UNUSUAL PROJECTS TO—how about an ELECTRONIC STETHOSCOPE for LISTENING THROUGH WALLS, etc., or a TRANSMITTER/RECEIVER that doesn't use RF, SO LICENCE WORRIES ARE OVER! Then there's another project for a "LEARNING" MACHINE—imagine one of these in YOUR BACKROOM; YOUR FRIENDS WOULD BE AMAZED! If REALLY UNUSUAL projects interest you, then WE'VE GOT WHAT YOU WANT. In a few days from now YOU COULD BE IN THE "SCIENCE-FICTION" WORLD OF "BOFFIN"! DON'T PUT IT OFF! SEND 15p for your list—NOW

### BOFFIN PROJECTS

4 CUNLIFFE RD., STONELEIGH, EWELL, SURREY  
Designs by GERRY BROWN and JOHN SALMON and presented on TV

**CLEARING LABORATORY**, scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

## MISCELLANEOUS (continued)

**RECORD T.V. SOUND** using our loudspeaker isolation transformer. Provides safe connection to recorder. Instructions included, 70p + 10p P. & P. **CROWBOROUGH ELECTRONICS (P.E.)**, Eridge Road, Crowborough, Sussex.

### 12 VOLT FLUORESCENT LIGHTS




Beat Power Cuts, 12 ins 8 watt Tube, ideal for Caravan, Tent, Emergency Lighting, etc. Fully Transistorised, Low Battery Drain. With ON/OFF Switch and 12v Socket to run other Lights or 12v Equipment.

Unbeatable at £3.30 post paid  
or in kit form £2.90
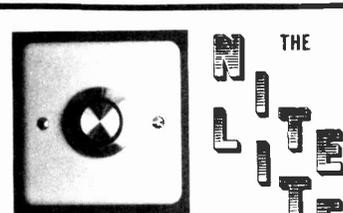
### 4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed £3.63 POST PAID

**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop  
Shrewsbury, Shropshire S.A.E. for lists



### Dimmerswitch

Will dim up to 400 watts of incandescent lighting from zero to full brilliance. This unit simply replaces the normal light switch, and is fitted in a matter of minutes. An MK mounting frame is supplied, for use when more depth is required.

Price—complete kit £2.80  
built and tested £3.20

as supplied to Industry, Schools, Hospitals  
Government Depts. etc.

### Diathane Ltd.

111, Sheffield Road, Wymondham, NORFOLK.

£0-10 postage & packing

**BUILD IT** in a DEWBOX quality cabinet 2½ x 2½ in x any length. DEW LTD., Hingwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

**FASCIA PANELS**, hi-fi equipment, etc., etched aluminium to individual specifications, S.A.E. details. R. MARSH, 29 Shelbourne Road, Stratford on Avon, Warwicks.

### PROFESSIONAL CONTROL PANELS

with **FASCIA KIT**

MAKE YOUR OWN PANELS IN PERMANENT, ANODISED, SELF-ADHESIVE ALUMINIUM. NO SPECIAL EQUIPMENT NEEDED. EASY TO FOLLOW INSTRUCTIONS. CHOICE OF SILVER ON BLACK, GOLD, RED, BLUE, GREEN.

TRIAL KIT (Approx. 50 sq in.) 98p + p.p. 30p  
No. 2 KIT (Approx. 100 sq in.) £1.58 + p.p. 30p  
**M.P.E. Ltd., BRIDGE ST., CLAY CROSS, DERBYS.**

# Electronics at The Open University

**Catch up in your spare time** by studying at home a new, introductory university course in Electromagnetics and Electronics which the Open University is offering in 1972.

Accepted students each receive an oscilloscope, and other equipment, to augment tuition by text, tutor, TV and radio. Whilst applicants are expected to have a scientific or technical background, no formal qualifications are needed. Further information can be obtained by writing to

G. A. H. Kiloh,



## The Open University

Walton Hall, Bletchley, Bucks.

**HUNDREDS OF TOP PAID JOBS** in engineering await qualified men. Get a certificate through B.I.E.T. Home Study—Mech., Elec., Auto., Radio, TV, Draughts., Electronics, Computers, Building, etc. Send for helpful **FREE** book, B.I.E.T., Department 125K, Aldermaston Court, Reading, RG7 4PF.

### FOR SALE

**SEEN MY CAT?** 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

**CATALOGUE NO. 18**, Electronic and Mechanical Components, new and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

**SHIBADEN VIDEO RECORDER**, condition as new £175. Phone 061-998 3494.

### MORSE MADE EASY !!

**FACT NOT FICTION.** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-680 2896 or send 4p stamp for explanatory booklet to:

GSHSC (Box 19), 45 GREEN LANE, PURLEY, SURREY

### SITUATIONS VACANT

**EAGLE INTERNATIONAL** require Audio Engineers. Excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact MR. MORROW 01-636 0961.

**GET INTO ELECTRONICS**—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. R.T.E.B., City & Guilds, Radio, TV, Telecoms, etc. For **free** informative Guide, write CHAMBERS COLLEGE (Dept. 866K), Aldermaston Court, Reading, RG7 4PF.

**A.M.S.E. (Elec.)**, City & Guilds, R.T.E.B. Cert., Radio Amateurs' Cert., etc., on "Satisfaction or Refund" terms. Wide range of courses in Elec. Engineering, Design, Installation, Repairs, Refrigeration, Electronics, Radio and TV, etc. Send for full details and illustrated book — **FREE**. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, Dept. 124K Aldermaston Court, Reading, RG7 4PF.

**MEN!** You can earn £50 p.w. Learn Computer Operating. Send for **FREE** brochure—LONDON COMPUTER OPERATORS TRAINING CENTRE, C95 Oxford House, 9-15 Oxford Street, London, W.1.

**FULL TIME COURSES IN ELECTRONICS AND TELEVISION.** These are nine month courses, starting next September, which lead to City and Guilds certificates. Extensive laboratory work is included, and there are, in most cases, no fees for those under 18 at enrolment. Full details from—Section 47, Electrical and Electronic Engineering Department, Southall College of Technology, Beaconsfield Road, Southall, Middx.

### EDUCATIONAL

Young men (and women) trained as Radio Officers on liners and other ships. Salaries rising to £2,500 per year (all found). Immediate vacancies. Grants available for Day full time course. For details of training write to: The Radio College, 91 Lancaster Road, Preston, Lancs., stating if interested in Day or Postal course.



Established 1891

# TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Colour TV Servicing, also Electronics, Computers, etc.

Expert coaching for:

- C. & G. TELECOMMUNICATION TECHNICIANS' CERTIFICATES.
- C. & G. ELECTRONIC SERVICING.
- R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- RADIO AMATEURS' EXAMINATION.
- RADIO OPERATOR CERTIFICATES.

Examination Students coached until successful.

### NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator and multi-meter. **All under expert guidance.**

**POST THIS COUPON TODAY** and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

**INTERNATIONAL  
CORRESPONDENCE  
SCHOOLS**

**A WHOLE WORLD  
OF KNOWLEDGE  
AWAITS YOU!**

**International Correspondence Schools**  
(Dept. 152), Intertext House, Stewarts Road,  
London SW8 4UJ

NAME.....  
Block Capitals Please

ADDRESS.....  
.....  
.....

AGE..... OCCUPATION..... 8/71

## SERVICE SHEETS

**RADIO TELEVISION**, over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London, W.6 (01-743 8441).

**SERVICE SHEETS**. Radio, TV, etc., 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

**SERVICE SHEETS** (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

## LARGE SUPPLIER OF SERVICE SHEETS

T.V., RADIO, TRANSISTORS, TAPES, CAR RADIOS  
25p EACH. MANUALS FROM 50p  
PLEASE ENCLOSE LARGE S.A.E. WITH ALL INQUIRIES AND ORDERS.  
OTHERWISE LETTERS NOT ATTENDED TO  
(Uncrossed P.O.'s please, original returned if service sheets not available.)  
FREE TV FAULT TRACING CHART OR TV LIST ON REQUEST WITH ORDER  
**C. CARANNA**  
71 BEAUFORT PARK, LONDON, N.W.11  
MAIL ORDER ONLY

## WANTED

**CASH PAID** for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

**HIGHEST POSSIBLE CASH** prices for Itevox, Ferrograph, Brenell, Vortexion, Tandberg. 9.30 - 5.00. 01-837 8200.

**PRACTICAL ELECTRONICS** any back issues required. BANCROFT, St. Wilfrids, Halton, Nr Lancaster.

**PRACTICAL ELECTRONICS**. Volumes 1 to 4, November and December issues in particular. Price and condition, please to—MR. BLAKE, 124 Windsor Avenue, Hillingdon, Middx.

**WE PAY THE HIGHEST PRICES** for new valves. Cash sent by return. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

## TOP PRICES PAID

for new valves and components

Popular T.V. and Radio types

**KENSINGTON SUPPLIES**

(B) 367 Kensington Street  
Bradford 8, Yorks.

## RECEIVERS AND COMPONENTS

### BRAND NEW COMPONENTS BY RETURN.

Electrolytics 15 or 25 volts, 1, 2, 5, 10 mfd, 30p; 25, 50, 4p; 100, 5p. Mylar Film 100V 0-001, 0-002, 0-005, 0-01, 0-02, 2p; 0-04, 0-05, 0-1, 2-5p. Mullard miniature Carbon Film Resistors 1W-10MΩ. 8 for 5p. Postage 5p. THE C.R. SUPPLY CO., 127, Chesterfield Road, Sheffield, S8 0RN.

## DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts. 62p per doz.: £3.75 per 100; £27.50 per 1,000; £250 per 10,000. All carriage paid.

**G.W.M. RADIO LTD.**  
40/42 Portland Road, Worthing, Sussex 0903 34897

## RECEIVERS AND COMPONENTS

(continued)

**EX COMPUTER PRINTED CIRCUIT PANELS** 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p. P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

**SPECIAL BARGAIN PACK**. 25 boards for £1. P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 50p. P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 876. All long leaded on panels 13in x 4in. 4 for £1, P. & P. 25p.

**LARGE CAPACITY ELECTROLYTICS**  
10,000MFD 30V } 40p each, P. & P. 6p.  
16,000MFD 12V }  
or £3-50 per doz. Carr. 50p.

**250 MIXED RESISTORS** 62p  
1/2 & 1 watt.

**150 MIXED HI STABS** 62p  
1/2, 1 & 1 watt 5% & better.

### QUARTZ HALOGEN BULBS

With long leads. 12V 55W for car spot lights, projectors, etc. 50p each. P. & P. 5p.

### DIODES EX EQPT. SILICON

1 Amp 1,000 PIV 4 for 50p  
20 Amp 150 PIV 4 for £1.  
P. & P. 5p.

### BARGAIN RELAY OFFER

Single pole change over silver contacts 25V to 50V. 2-5kΩ coil. 8 for 50p. P. & P. 5p.

**KEYTRONICS** mail order only  
44 EARLS COURT ROAD  
LONDON, W.8 01-478 8499

**MULLARD TRANSISTORS**, ex. eqpt. Perfect. OC23 20p (Heat Sink 5p), OC72 10p. Diodes OA10 10p. LESMAR, 15 Conholt Road, Andover, Hants.

**BIG BARGAIN PACK** containing varied assortment of semiconductors, pots and larger components. 75p post free. PAXTON, 108 The Chesils, Coventry.

**P. E. AURORA**. Complete sets of electronic components for assembly on Vero board. We also have specially designed printed circuit cards for a combined controller/filter system readily available. (S.A.E. for lists).

### OPTELMEC LTD.

1, 2 & 3 Nelson Works  
Back Road, SIDCUP, Kent

## CHROMASONIC ELECTRONICS

supply only 1st grade branded goods  
subject to makers' guarantees

SN7400N, 1, 2, 4, 5, 10, 20, 26, 30, 40, 50, 51, 54  
SN7460N ..... all 25p ea.  
SN7441AN, 42, 75, 81, 82, 90, 92, 93, 94, 95 all £1 ea.

PA230 92p PA246 22-45 TAA310 21-25  
PA234 87p TAA283 70p TAA320 65p  
PA237 21-57 TAA293 90p TAD100 21-95  
PA239 22-50 TAA300 21-50 TAD110 21-95

### LOW NOISE HI-STABS

1/2 watt 5%, all E24 values 3 for 2p plus p. & p. 6p up to 50 resistors + 1p for each additional 50.

**FREE CATALOGUE p. & p. 3p**

p. & p. on all orders other than resistors 6p.

56 Fortis Green Road, London  
N10 3HN

## RECEIVERS AND COMPONENTS

(continued)

**COMPUTER PANELS**. 5-BC108 diodes 15p, post 5p, 4-50p, post 10p. **AMERICAN PANELS**. Total at least 30 transistors, first grade components, details provided. 3-55p, post 10p. 6-OC170 DIODES. 85p, post 8p each. 8-OC72/73/42, 8-OA10 DIODES. 40p, post 10p each. 4-MD634, 5-100mF ELECTROLYTICS, 12V potcore, etc., 30p, post 8p each. **NEW COIL PACKS**. L.M.S.W. Push button or piano key. No dope, 80p, post 10p each. **ORP12** on panel ex-18p component, 35p c.p. **MICRO SWITCHES** on or off, 15p c.p., discount for quantities. **FERRITE ROD** 7" x 1/2", 12p, post 8p each. **LAZ POT CORES**. 20 in ALI box with 20 1% caps, £1-50, post 27p. Singles, 15p c.p. **COMPUTER RELAYS**, D.P.D.T., 700 ohm coil, weigh 1oz, 55p with base, 65p post free. **SMALL SYNCHRONOUS MOTORS** with train of gears, 200-250V, 80p post free.

**POLYETHYLENE CAPACITORS**. 125V, 150, 180, 220, 330, 390, 560, 680, 820, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 8,200, 0-01, 0-012, 0-015, 10p dozen, post 10p.

Assorted. 1/2" leads, 100 for 30p, post 10p.

**ASSORTED COMPONENTS**. 7lb. £1-25 c.p.

**ASSORTED COMPUTER PANELS**. 2lb. £1-25 c.p.

**J.W.B. RADIO**

75 HAYFIELD ROAD, SALFORD 6, LANCs.

MAIL ORDER ONLY

## C-CORE TRANSFORMER KITS

Consisting of:—

CLAMPS, WINDING BOBBIN,  
TWO C-CORES AND BANDS

Rating	Price	P. & P.
5 VA	35p	5p
10 VA	40p	10p
15 VA	50p	15p
25 VA	60p	20p
50 VA	90p	25p
100 VA	£1-50	35p
500 VA	£2	40p
1000 VA	£3	50p

Above for 50 Hz operation

Inquiries invited for other sizes, also toroids, E-cores, transformers for other frequencies, and enamelled copper wire.

Design advice given F.o.C.

Supplied by:—

Trankit Electrical  
192 Silvertonhill Avenue  
Hamilton ML3 7PP

## 30 WATT POWER AMPLIFIER

IDEAL BASIS FOR HI-FI SYSTEM

30 watts rms into 8Ω. <20 Hz-40 KHz ± 1dB at full output. 0-04% distortion at full output. Differential input stage -300 mV for full output. Tested, ready to mount £7-35. 2 for £14-50. Quantity/Trade discount.

Kit with drilled glass fibre board, heatsink and all components, etc., £5-70. P. & P. 15p. Overload protection 25p extra.

S.A.E. details of above, also 50 WATT, 100 WATT IC POWER AMPS, power supplies, etc., to:

## FIELDSIDE ELECTRONICS

120A Richmond Road, London, S.W.20 01-428 8076

### Microcircuits:

709	40p	7400	21p
741	73p	7410	21p
PA230	97p	7420	21p
PA234	97p	7430	21p
PA237	£1-63	7473	43p
SL402A	£1-75	7474	43p
MEL 11	35p	DIL Conn.	25p
D40C1	55p		

### Transistors

MEF104	30p	ME4102	12p
ME0402	21p	ME6101	15p
ME0412	20p	MP8111	35p
ME0413	15p	2N5172	21p
ME1002	12p	2N3055	60p
ME4101	11p	BFX 86	21p

### 1W Zener Diodes:

4.7V	12p	6-2V	12p
9-1V	12p		

Etch resist filled Marker Pen for making printed circuits 80p

### JEF ELECTRONICS (P.E.8)

York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only  
C.V.O. P. & P. 5p per order. Overseas 40p  
Money back if not satisfied  
List free on application.

## RECEIVERS AND COMPONENTS

(continued)

### NEW SILICON TRANSISTORS

Texas markings. NOT seconds, etc., or rejects. Both are for general-purpose, low-level, high-gain applications. Both have hfe 45-800 and max dissipation 250 mw.  
**2N3708 7p each.** (N-P-N, coll-emitter 30v max, coll current 30ma max).  
**2N4059 9p each.** (P-N-P, coll-emitter -30v max, coll current -30ma max).  
 Ratings at 25°C free-air temp. Data sheets 1 p ea. Mail order only. Post etc. 6p per order.  
**K. M. GRAPHIC (Components Dept.) Ref. D1**  
 8 Gower Street, Derby DE1 1SB

**MAGNETIC RECORDING TAPE.** Fully Guaranteed. 5in L.P., 60p. 5in D.P., \$1. 5in T.P., \$1.50. 7in L.P., \$1. 7in D.P., \$1.55. 7in T.P., \$3. Inverter. 15 W 12 to 240 V, \$1.50. Postage, 15p. Send 10p for full lists of electronic components. **MFJ ELECTRONICS**, 495 Alum Rock Road, Birmingham, 8.

**DUAL GATE MOSFET MEM 564C**, ruggedised 3N140, sim. 40673. For WW Communic. Rx, Stereo FM, etc., only 65p. U.K. post 5p. **AMATRONIX LTD.**, 396 Selsdon Rd., S. Croydon, Surrey, CR2 9DE.

### LADDERS

**VARNISHED TIMBER LADDERS** from manufacturer, **LOWEST PRICES** anywhere: 15ft ext., \$8.20; 17ft ext., \$8.50; 20ft ext., \$7; 21ft ext., \$7.75; 24ft ext., \$8.90; 29ft ext., \$10.25; 31ft triple ext., \$12.25; 36ft. triple ext., \$16. Carr. 80p. Free Lists. Also Aluminium Ext. and Loft Ladders. Callers welcome. Dept. PEE, HOME SALES, Baldwin Road, Stourport, Worcs. Phone: 02-993 2574. Placing order on C.O.D.

### BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 6v, 9v, 12v, 18v (single output) £2 each. P. & P. 15p. 9v + 9v; 6v + 6v; or 4iv + 4iv (two separate outputs) £2.50 each. P. & P. 15p. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.  
**R.C.S. PRODUCTS (RADIO) LTD.**  
 (Dept. P.E.), 31 Oliver Road, London, E.17

Your local component stockist

ast Anglia

EAGLE  
 Electronics

Eagle St.

PSWICH 58075


HOW TO BUILD A MULTI-CHANNEL DIGITAL RADIO REMOTE CONTROL SYSTEM FOR CARS, BOATS OR PLANES.

MANUAL 75p plus 8p post.

TELERADIO ELECTRONICS

325/7 Fore Street, Edmonton, N.9

# DABAR audio mixer modules

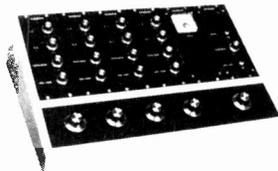

A range of audio Pre-amplifier Modules is now available enabling the construction of custom-built audio mixers for studio, P.A. and discotheque installations; at reasonable cost and with many facilities usually available only on expensive systems. The Modules, constructed on glass fibre printed-circuit boards, are complete with anodised aluminium black fascia plates and four control knobs indentified: L.F., H.F., Echo Send and P.F.L. The modules are designed for use with external faders or volume controls and fulfil most requirements in the audio field. Up to ten input modules may be mixed into the combined Mixer/Line Amplifier Type MX/LNTA which is available on a matching fascia plate with V.U. meter. The line amp will deliver 20dBm. All mixing may be effected with 10k log faders.

The modules are fixed with four screws and dimensions are 7 1/2in x 2 1/2in.

Input modules available:

- UM1 200-600 ohm MIC
- UM2 50k ohm MIC
- UM3 Mag P/U 1.5mV R.I.A.A.
- UM4 Mag P/U 5mV R.I.A.A.
- UM5 Crystal P/U 500mV
- UM6 High Level Tape/Tuner 500mV

**Mixer/Line amp MX/LNTA:** 10 inputs plus expander input; 600 ohm line out with preset for V.U. adjustment.

**Power Unit for above Modules:** Type PU11/30, 30V, 500mA. 100W slave amplifier—100W into 4 ohm load 13 1/2in 10 1/2in 7 1/2in.


**Prices:** UM1-6, £9 each. MX/LNTA, £12. PU11/30, £8. 100W Slave Amp £60.

Manual showing mixing arrangements, connection data, etc., 25p. S.A.E. all inquiries. Trade inquiries welcome.

### DABAR ELECTRONIC PRODUCTS

98a LICHFIELD STREET  
 WALSALL, STAFFS WS1 1UZ  
 WALSALL 34365

# UNIQUE TWIN TAPE DECK UNITS

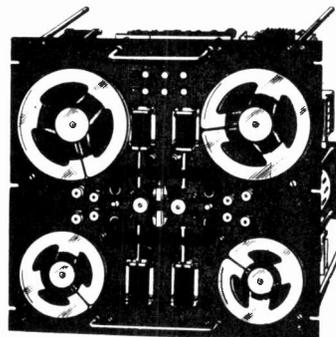

OFFERED AT A FRACTION OF THEIR ORIGINAL COST

**£35 EACH TESTED WORKING**

(Few available requiring attention at £25 each)

Carriage £3.50 each, including wooden packing case, insurance, etc.

These superb twin tape deck units were originally designed for installations requiring the continuous replay of music or speech when connected to suitable amplifiers and cost approx. £450 each to manufacture. Consisting of two completely self-contained tape decks operating at either 3 1/2in (3 button; track model) or 7 1/2in (6 button; track model). Each tape drive unit is fitted with a unique automatic solenoid operated tape drive reverse mechanism actuated by metallic stop foil at end of tape or inserted where reversal is desired. Constructed to the highest specification with the finest components available to ensure the utmost reliability. Nothing has been spared in the construction and the superb heavy duty capstan motors (2 off) and rewind motors (4 off), top grade relays, solenoids, etc., all bear witness to the high standards set.

Available in two basic versions with either 3 or 6 button operation. The three pushbutton model 3 1/2 in. has interlocked controls operating both tape drive units simultaneously and is fitted with 2 Ferrograph 1/2 track stereo heads. The 6 button 7 1/2 in. model has independent control over each tape drive unit and is fitted with 2 Marriott 1/2 track stereo heads. A.C. 230/250V. 50c/s. Vertical or horizontal operation. Size 19in x 8in deep. Weight 54lb.

### TECHNICAL SPECIFICATION

Power requirements 230/250V a.c. 50c/s. Vertical or horizontal operation. Overall dimensions: 19in x 8in deep. Weight 54lb. 3 button model operates at 3 1/2 in. 6 button model operates at 7 1/2 in. **TAPE REEL SIZES:** Upper deck 5 1/2in. Lower deck 5in. Capstan drive motors: 2 AEI a.c. motors continuous rating Type BC1504-B. 230/250V a.c. 50c/s 1/75th h.p. 1,500 r.p.m. **REWIND AND TAPE UP MOTORS:** 4 Garrard a.c. motors continuous rating Type DHP5C 100-130/200-250V. 50/60c/s 0.3A-0.15A 24W. **RELAY SUPPLY TRANSFORMER:** Primary 210-230-240V a.c. 50c/s. Secondary 24-26-32V. **RECTIFIER:** Sentercel selenium rectifier type 460 SC 21B1 5. **CONDENSERS:** Tessey 2,000uf 50V d.c. 2 AEI 2uf 400V. **SOLENOIDS:** 8 Magnetic Devices Ltd Type. 42766 120 ohms. **RELAYS:** 2 Type 59E14/590/AE2/24. 2 Type 59E/E9/890/G2/24. 2 Type 596E8/590/E2/24 (3 button unit only I). **RECORD/REPLAY HEADS:** 3 button unit fitted 2 Ferrograph 350 ohms impedance half track stereo heads. 6 button model fitted 2 Marriott 4 track heads 500 ohms impedance.

### SYPHA SOUND SALES LTD.

82 HIGH HOLBORN, LONDON, W.C.1

Telephone 01-242 7401

Few mins. Holborn Tube. Half day Sat.



# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering ...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

**Mechanical**  
A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

**Draughtsmanship**  
A.M.I.E.D.  
Gen. Draughtsmanship  
Die & Press Tools  
Elec. Draughtsmanship  
Fit & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

**Electrical & Electronic**  
A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

**Radio & Telecomms.**  
C. & G. Telecomms.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

**Auto & Aero**  
A.M.I.M.I.  
M.A.A./M.I. Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

**Management & Production**  
Computer Programming  
Inst. of Marketing  
A.C.W.A.  
Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing  
Numerical Control  
Planning Engineering  
Materials Handling  
Operational Research  
Metriation

**Constructional**  
A.M.S.E. (Civ.)  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpentry & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating  
Architecture  
Builders' Quantities

**General**  
C.E.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing.  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

**General Certificate of Education**  
Choose from 42 'O' and 'A' Level subjects including:  
*English*  
*Chemistry*  
*General Science*  
*Geology*  
*Physics*  
*Mathematics*  
*Technical Drawing*  
*French*  
*German*  
*Russian*  
*Spanish*  
*Biology*  
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

**WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.**

*Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.*

## THEY DID IT— SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

## FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B4, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



## POST THIS COUPON TODAY

To: B.I.E.T., Dept B4, Aldermaston Court, Reading RG7 4PF  
Please send me book and details of your Courses in

Name ..... Age .....

Address .....

Occupation .....

**B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE**

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon & Gotch (A/asia) Ltd.; South Africa - Central News Agency Ltd.; Rhodesia and Zambia - Kingstons Ltd.; East Africa - Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2.65 (£2.13.0.). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.


# HENRY'S RADIO LIMITED

HENRY'S RADIO

## ENGLAND'S LEADING ELECTRONIC CENTRES

HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER
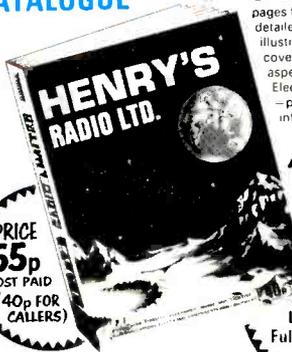
### COMPLETELY NEW 10th EDITION CATALOGUE



**350** pages fully detailed and illustrated covering every aspect of Electronics — plus data and information

**PRICE 55p**  
POST PAID  
(40p FOR CALLERS)

**10,000** Stock lines at Special Low Prices and Fully Guaranteed

**PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES**

**FREE** to Industry, Educational or any Organisation, including Schools and Colleges, etc. Apply on Official heading to our "303" address.

**A NEW HENRY'S CATALOGUE IS A MUST FOR ELECTRONICS TODAY!**

To Henry's Radio Ltd. (Dept. PE)  
3 Albemarle Way, London, E.C.1.

Please send.....copies at 55p each Post Paid.

I enclose Cheque/PO for

(Use **BLOCK CAPITALS**—cut out and send with Cheque or Postal Order (No cash please). Use only for ordering catalogue).

Name .....

Address .....

Allow 7-10 days from date of posting.

**MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S**

\*Components from stock for almost all published designs.

### TRANSISTOR AMPLIFIERS

NEW RANGES NOW IN STOCK

(Leaflets Ref. Nos. 6 and 8).

Post, etc., 20p.

4-300 4TR 9V 300mW	£1.75
104 4TR 9V 1W	£2.12
304 4TR 9V 3W	£2.47
555 6TR 12V 3W	£2.75
PA7 6TR 16V 7W	£3.62
608 6TR 24V 10W	£4.12
410 4TR 28V 10W	£4.97
MPA12/3 6TR 18V 12W	£4.50
MPA12/15 6TR 36V 12W	£5.25
Z30 9TR 30V 20W	£3.75
PA25 10TR (Special) 25W	£7.50
Z50 30V 40W	£5.47
PA50 12TR (Special) 50W	£9.50
100 100W with power supply	£45

post 45p

#### OPTIONAL POWER SUPPLIES


P500 (One or Two) for 104, 304	£2.62
PS20 (One or Two) for PA7	£3.47
MU24/40 (One or Two) for PA7	£4.50
PZ5 for Z30 £3.97	or PZ6 for Z30 £6.97
PZ8 for Z50 £5.97	Transformer £2.25
P11 for 200 £2.87	P15 for 410 £2.62
MU442 for 1 or 2 PA25 or 1 only PA50	£6.50



Post, etc., 20p
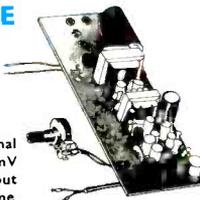
### NEW MINIATURE LOW COST AMPLIFIER MODEL 4-300

9V operated or mains unit optional transformer (MT98 70p), 1-10mV adjustable sensitivity. P/P output for 3-8 ohms. Fitted volume control and leads. Size 5 1/2" x 1 1/2" x 3/4". Thousands of uses—takes magnetic, dynamic and crystal inputs direct. Output 300mW—very high gain—built in rectifier circuit.



**Price £1.75**  
P.P. 15p. Complete with FREE leaflet No. 8.

### HI-FI TO SUIT EVERY POCKET



**CHOOSE 100 STEREO FROM SYSTEMS**

and a complete range of individual units in stock—Demonstrations all day—visit our new Hi-Fi Store—LOW CASH OR CREDIT/HP TERMS (Credit terms from £30 purchase—callers only), FREE—Stock Lists Nos. 16/17 on request. **BEST VALUE IN U.K.**

### GARRARD TAPE DECK



9V operated 2-speed tape deck fitted Record/Replay 1/2 track and Erase/Bias Osc. Head. Complete with Oscillator/Record head circuit. Unit size 9in x 6 1/2in x 1 1/2in and 2 1/2in below motor board. Takes up to 4in spools. Supplied Brand New.

**Price £9.97**

P.P. 33p (3 1/2in. tape 300ft.) and spool 40p.



### HENELEC EQUIPMENT

(as previously advertised)

**SELF-POWERED SILICON PRE-AMPLIFIERS**  
FET154 Stereo £16.50, post 25p.  
FET9/4 Mono with mike mixer £12.50, post 20p.

**SILICON POWER AMPLIFIERS FOR USE WITH ABOVE**  
PA25 25W into 8Ω £7.50, post 20p.  
PA50 50W into 4Ω £9.50, post 20p.  
MU442 power supply for 1 or 2 PA25's or 1 only PA50 £6, post 20p.

**PACKAGE DEALS**  
FET9/4 plus PA25 plus MU442 £25, post 40p.  
FET9/4 plus PA50 plus MU442 £27, post 40p.  
FET154 plus 2 x PA25 plus MU442 £36, post 50p.  
FET154 plus 2 x PA50 plus 2 x MU442 £40, post 50p.

No soldering—just edge connectors and din plugs/sockets.  
Free Brochure No. 25.

### BUILD YOURSELF A QUALITY RADIO



Excellent printed circuit design with full power output. Fully tunable on both MW/LW bands. 7 Mullard transistors. Fitted 5in speaker. Room filling power. Easy to build with terrific results. Two colour leathercloth cabinet with silvered front. All local and continental stations. Complete detailed instructions.


Total cost £6.98, p.p. 35p. All parts sold separately. Ask for Leaflet No. 1.

#### PROJECT 60 PACKAGE DEALS

2 x Z30 amplifier, stereo 60 pre-amp. PZ5 power supply, £16.75. Carr. 40p. Or with PZ6 power supply, £18.25. Carr. 40p. 2 x Z50 amplifier, stereo 60 pre-amplifier PZ8 power supply, £20.25, p.p. 40p. Transformer for PZ8 £2.25 extra. Any of the above with Active Filter unit add £4.75 or with pair Q16 speakers add £15. Also NEW FM TUNER, £21.
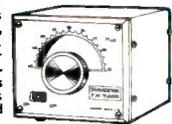
### BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.  
Free Leaflet Nos. 3 and 7.  
TOTAL £6.97, p.p. 20p. Cabinet £1, Decoder Kit £5.97. Tuning meter £1.75. Mains unit (optional) Model PS900 £2.47. Mains unit for Tuner and Decoder PS1200 £2.62.



Electronic Components,  
Audio and Test Gear Centre  
356 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-402 4736

High Fidelity Sales &  
Demonstrations Centre  
354 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-402 5854

Electronic Organs,  
P.A. & Discotheque Centre  
309 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-723 6963

Mail Orders, Special Bargain  
Shop, Industrial Sales  
303 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-723 1008/9

"354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY