

PRACTICAL

ELECTRONICS

JANUARY 1978

45p

Rhythm GENERATOR



...for the Musician

12 Switch Selected Rhythms
8 Percussion Voices

Also inside...

- **Battery Condition Indicator**
- **9v Stabilised P.S.U.**



Plus... **NEW SERIES** ELECELECTRONIC FAULT DIAGNOSIS

PRACTICAL ELECTRONICS

VOLUME 14 No. 5 JANUARY 1978

CONSTRUCTIONAL PROJECTS

- RHYTHM GENERATOR** *by N. A. Cooke* 322
A low cost unit capable of 12 basic rhythms
- BATTERY CONDITION INDICATOR** *by P. Scargill* 330
Tri-state car battery voltage monitor
- BREADBOARDING SYSTEM** *by D. F. McGinley* 339
A versatile and inexpensive d.i.y. breadboard
- ELECTRONIC DIE** *by I. J. Dillworth* 340
H format l.e.d. die with some unusual features
- 9 VOLT STABILISED P.S.U.** *by C. H. Banthorpe* 344
An overload protected 9V stabiliser for car cassette recorders etc
- P.E. CHAMP-5** *by R. W. Coles and B. Cullen* 352
The keyboard/display unit using a calculator

GENERAL FEATURES

- SEMICONDUCTOR UPDATE** *by R. W. Coles* 332
A look at some recently released devices
- FAULT FINDING** *by G. Loveday* 333
Introduction and component faults in simple circuits
- INGENUITY UNLIMITED** 347
Simple Lie Detector—Tape Recorder Peak Level Indicator—XY Burn Eliminator—
Model Train Speed Controller—Two Way/Two Wire Bell System—Touch Actuated
Generator—Timesetting For The MK50250

NEWS AND COMMENT

- EDITORIAL** 321
- STRICTLY INSTRUMENTAL** *by K. Lenton-Smith* 329
Keyboard instruments at the British Musical Instrument Trade Fair
- SPACEWATCH** *by Frank W. Hyde* 336
Soyas/Salyut, Soviet Meteor 2, Intelstat 5
- MARKET PLACE** 346
Interesting new products
- POINTS ARISING** 357
Burglar Alarm—Frequency Counter/Timer
- PATENTS REVIEW** 358
Thought provoking ideas on file at the British Patents Office
- CHROMA-CHIME KIT REVIEWED** 360
The assembly and performance of this computerised doorbell
- NEWS BRIEFS** 361
GEC Computer For RNIB—Solar Water Heaters—IBC
- INDUSTRY NOTEBOOK** 362
What's happening inside industry
- READOUT** 366
A selection of readers' letters
- BOOK REVIEWS** 366
Selected new books we have received

Our February issue will be on sale Friday, 13 January, 1978
(for details of contents see page 351)

© IPC Magazines Limited 1978. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

NEW BOOK

Master *In-Car Entertainment*

Author: Vivian Capel

CONTENTS:

The Car Equipment scene mono, Stereo or Quad? Mobile Tape Players. The Cartridge Player. The Cassette Player. Cassette or Cartridge? Car Radios. Car Antennas. Interference Suppression. Installing the System. Trouble Shooting.

Whether you are stuck in the frustrating immobility of a traffic jam, or suffering the boredom of a long car journey, you are sure to find facilities for in-car entertainment a great boon. Published information on the choice and installation of mobile audio equipment has not kept pace with the rapidly growing interest in the subject. This book fills the gap in a highly informative easy-to-read manner. Written by an expert, and illustrated with many attractive two-colour diagrams, it sets out the relative merits of mono, stereo and quad in the car, and describes cartridge and cassette players as well as giving helpful advice on choosing between the systems.

1977

128 pages

£2.50

LOOK More books for the enthusiast:

Foundations of Wireless and Electronics — 9th Edition — M.G. Scroggie 1975	552 pages	£3.75
Newnes Tape Recorder Servicing Manual — 2nd Edition — John Gardner Volume 1 1977	224 pages £7.80	Volume 2 1977 224 pages £7.80
Radio, TV and Audio Technical Reference Book — S.W. Amos 1977	1272 pages	£24.00
Questions and Answers On Integrated Circuits — R.G. Hibberd 1974	96 pages	£1.00
Questions and Answers On Transistors — 3rd Edition — C. Brown 1972	96 pages	£1.00
Questions and Answers On Colour Television — 2nd Edition — J.A. Reddihough and D. Knight 1975	108 pages	£1.15
Questions and Answers On Electronics — C. Brown 1967	112 pages	£1.15



Newnes Technical Books
BOROUGH GREEN, SEVENOAKS, KENT TN15 8PH




Random FLASHER UNIT
Wired ready for use. Complete with three 100 watt coloured lamps that flash independently at random.
£18.95



TWIN BANK 6 LIGHT UNIT
(less lamps) LENGTH 14 1/2 inches
BC Fitting **£9.55**
ES Fitting **£10.35**



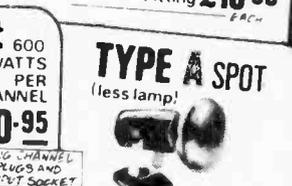Sound to Light MASTER UNIT
600 WATTS PER CHANNEL
£30.95
INCLUDING CHANNEL OUTPUT PLUGS AND MAINS WPT SOCKET



TYPE A SPOT
(less lamp)
BC Fitting **£1.95** ES Fitting **£2.12**



TYPE B 3 BANK UNIT
(less lamps)
BC Fitting **£6.90** ES Fitting **£7.26**




TWIN BANK 12 LIGHT UNIT
Length 31 1/2
(less lamps)
BC Fitting **£15.60** ES Fitting **£17.00**

100 WATT SPOT LAMPS
RED, YELLOW, GREEN
BLUE, CLEAR **£1.50** each
Minimum 3 lamps
B.C. or E.S. Fitting

ALL PRICES INCLUDE V.A.T. and POST & PACKING (These prices apply to the United Kingdom only)

Send 20p for illustrated leaflet & price list

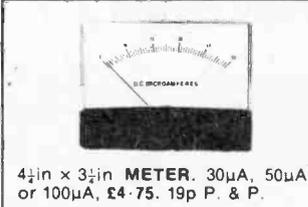
ALBEN ENGINEERING CO. LTD.
DEPT. PE THE CRESCENT, WORSTHORNE,
BURNLEY, LANCs. Tel. Burnley 20940



4 1/2 in x 3 1/2 in **METER**. 30µA, 50µA or 100µA, £4.75. 19p P. & P.

2in x 2in meters 1mA, 500mA, £2.92. 16p P. & P.
60 x 45mm meters 50µA, 100µA 500µA and 1mA VU meter, £4.14! 11p P. & P.
Edgewise meters 90mm x 34mm, 500µA, and 1mA, £3.40. 19p P. & P.

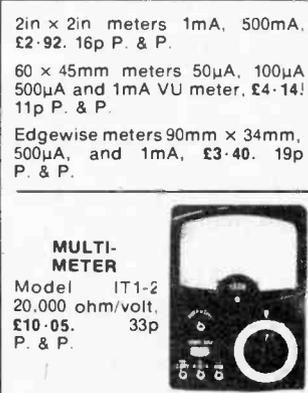MICROPHONES FOR TAPE RECORDERS
DM228R 200 ohm with 3.5 and 2.5mm Jack Plugs **£1.30**
DM229R 50K with 3.5 and 2.5mm Jack Plugs **£1.60**
DM18D 200 ohm with 5 and 3 pin Din Plugs **£1.75**
Postage on above microphones 11p



MULTI-METER
Model IT1-2
20,000 ohm/volt, £10.05. 33p P. & P.



CARDIOID DYNAMIC MICROPHONE
Model UD-130 Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £8.02. 26p P. & P.

TRANSFORMERS Primary 240V
6-0-6V 100mA **£0.75**
9-0-9V 75mA **£0.75**
12-0-12V 50mA **£0.85**
12-0-12V 100mA **£1.05**
Post on above transformers 30p.
9-0-9V 1A **£1.80**
12-0-12V 1A **£2.15**
15-0-15V 1A **£2.36**
30-0-30V 1A **£3.10**
6-3V 1 1/2A **£1.80**
6-0-6V 1 1/2A **£2.20**
Post on above transformers 45p.

All above prices include V.A.T. Send 40p for new fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

STRIKE YOUR OWN BARGAIN WITH Stirling Sound

NO EXTRAS TO PAY FOR POSTAGE OR V.A.T.

THE SCHEME

Choose from any of the 9 power amplifier modules shown in our ad. and then the Stirling Sound power supply unit best likely to suit the job. Refer to the published prices (which already include V.A.T. and post free in U.K.). When you send the money

DEDUCT 5% FROM THE TOTAL PRICE OF THE TWO ITEMS

If you order UNIT ONE at the same time that you order a power amp. and power unit as above

DEDUCT A FURTHER £1.00 FROM THE TOTAL PRICE

If you order UNIT TWO at the same time that you order a power amp. and power unit as above

DEDUCT A FURTHER £1.18 FROM THE TOTAL PRICE

UNIT ONE

Combined stereo pre-amp & active tone control unit. Input sensitivity 50mV for 200mV out. 10-16V operation. Boss ± 15 dB at 30Hz; Treble ± 15 dB at 10KHz; Balance control; Volume control. For ceramic p.u., radio or tape inputs. WITH FREE CONTROL PANEL FASCIA. £9.00

UNIT TWO

With control facilities similar to UNIT ONE but for magnetic cartridge input. Input sensitivity - 5mV for 200mV out (can be varied). WITH FREE CONTROL PANEL FASCIA £12.43

CONTROL PANEL FASCIA available separately 50p

SS.100

Basic active stereo tone control module to provide ± 15 dB on bass at 30Hz and on treble at 10KHz. £3.00

SS.101

Stereo pre-amp suitable for ceramics, tape, radio, etc. £2.75

SS.102

Stereo pre-amp for mag. pick-ups. £4.45

F.M. STEREO DECODER, phase lock loop type, with LED indicator showing when a stereo transmission is being received. £5.25

WHEN ORDERING ALL PRICES QUOTED INCLUDE V.A.T. AND GOODS ARE SENT POST FREE IN U.K. Owing to time between sending our ad. to this journal and the time it appears, prices may be subject to alteration without notice. E.&O.E. ORDER BY ACCESS OR BARCLAYCARD - SIMPLY LET US HAVE YOUR NUMBER.


Stirling Sound Dept. PE178

37 VANGUARD WAY, SHOEBURYNNESS, ESSEX.
Telephone (03708) 5543.

Shop - 220-224 West Rd., Westcliff-on-Sea, Essex.
Telephone Southend (0702) 351048.


Britain's most go-ahead module manufacturers

CHOOSE THE ITEMS YOU WANT AND BUY THEM THE STIRLING SOUND BARGAIN WAY whether for a new system, to up-grade what you use now, to build a disco or P.A. outfit, a domestic intercom or any other device where an amplifier might be used. Whatever it be, there's a Stirling Sound power amp for it up to 100 watts R.M.S., together with a choice of stereo tone control/pre-amps. Build with Stirling Sound now! See what you save and hear how good it sounds.

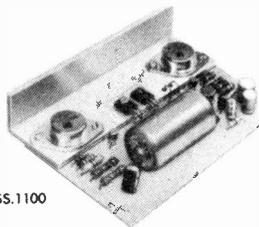

SS.1100

Made in our own Essex factory and sold direct to you, the user.

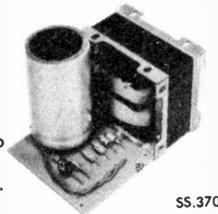

SS.370

INFO SHEETS - the new way to build your Stirling Sound Catalogue. LARGE 12½p S.A.E. brings first set (A.4 size) covering items advertised here.

AMPLIFIERS 3 to 100 WATTS R.M.S.

Ready assembled on P.C.B.s, tested and guaranteed. Easy to connect. With instructions. Outputs rated ± 1 dB.

SS.103	I.C. amp. 3 watts R.M.S. using 20V/8 Ω or 14V/4 Ω . Input 100mV. Stereo version of above, 2 I.C.s	£2.85 £5.00
SS.103-3	5 watts R.M.S. into 3 Ω using 13.5V. Sensitivity - 30mV. THD - 0.3%. 3½" x 2" x 1"	£3.95
SS.110	10 watts R.M.S. into 4 Ω using 24V. Sensitivity - 60mV. THD - 0.3%. 3½" x 2" x 1"	£4.65
SS.120	20 watts R.M.S. into 4 Ω using 34V. Sensitivity - 80mV. THD - 0.3%. 3½" x 2" x 1"	£5.15
SS.125	25 watts R.M.S. into 8 Ω using 50V. Sensitivity - 140mV. Distortion - Less than 0.05% into 8. S/N better than 70dB.	£7.25
SS.140	40 watts R.M.S. into 4 Ω using 45V. Sensitivity - 300mV. Distortion typically 0.1%. 5" x 3½" x 1½"	£6.50
SS.160	64 watts R.M.S. into 4 Ω using 50V. Sensitivity - 350mV. Distortion typically 0.1%. 5" x 3½" x 1½"	£8.50
SS.1100	100 watts R.M.S. into 4 Ω using 70V/2A. Input sensitivity - 500mV. Distortion at half-power, typically 0.1%. 5" x 3½" x 1½"	£10.50
HS.160	Multi-finned heatsink for SS.140 or SS.160.	75p
HS.1100	Ditta for SS.1100	£1.50

POWER UNITS

Every Stirling Sound Power Unit is tested and guaranteed under working conditions before despatch. All units except SS.312 include a stabilised low voltage take-off point (13-15V) for pre-amp, tone control, radio tuner, etc. Outputs quoted minimal unloaded ratings.

SS.312	12V/1A	£6.60
SS.318	18V/1A	£6.95
SS.324	24V/1A	£7.65
SS.334	34V/2A	£8.75
SS.345	45V/2A	£10.75
SS.350	50V/2A	£11.75
SS.360	60V/2A	£12.75
SS.370	70V/2A	£14.75

SS.310/50 Stabilised power supply unit with variable output from 10V to 50V/2A. Short circuit protected £17.75

SS.300 Power stabilising unit variable from 10 to 50V/8A for adding to un-stabilised supply units £5.50

Improved circuitry and performance standards. More to choose from.

To STIRLING SOUND	NAME
Please supply	ADDRESS
.....
.....
.....	My Access or Barclaycard No. is
for which I enclose £	PE/178

BD103 - The Connoisseur's Professional Choice

An exceptional transcription unit that performs to truly professional standards. Fitted with a new specially designed arm, the BD 103 will form the start, or an integral part, of a system for those who never believed they could achieve this level of quality at a reasonable price, simply compare specifications. *Low voltage DC servo controlled motor with electronic speed variation on all 3 speeds - 33 $\frac{1}{3}$, 45 and 78 rpm. *Externally housed power source, thereby eliminating hum fields, convertible for 120 or 230v mains supply. *Belt drive with precision ground natural rubber moulded belt of round cross section. *Neon illuminated stroboscope underneath 12" aluminium turntable is viewed through a mirror in the platform; available with either 50 or 60Hz stroboscope. *Pick-up arm automatically raises at the end of the playing section of the record. Automatic lift-off can be overridden for non-standard records. *Low friction pick-up bearings - unipivot for horizontal motion, knife edges for vertical motion - with a unique system of magnetic stabilization on the unipivot bearings. *Playing weight adjusted by sliding weight on arm tube, which is calibrated. Additional counter weights provided for accommodation of a full range of cartridges. Adjustable magnetic bias, calibrated for varying playing weights. *Inter-changeable lightweight plug in head shell accepts cartridges with $\frac{1}{2}$ " mounting centres. The turntable unit is solidly mounted on to a walnut plinth, which stands on a sprung and damped anti-vibration suspension system, thereby using maximum mass to improve performance, and fitted with a hinged acrylic dust cover with lid stay.

Dimensions: 15" x 18" x 5 $\frac{1}{2}$ ".

An alternative version is available without the pick-up arm and lifting device, incorporating a larger walnut/plastic cover, enabling most high quality pick-up arms to be used.

Dimensions: 15" x 18" x 7".

BD 103 Alternative unit without arm and lifting device.



The BD 103 Transcription turntable and External Power unit



Connoisseur

Write for further details to:
A. R. Sugden & Co. (Engineers) Ltd.
 Manufacturers of Connoisseur Sound Equipment, Connoisseur Works, Atlas Mill Road, Brighouse, West Yorkshire HD6 1ES
 Telephone: Brighouse (0484) 712 142, Telex: 517144 Sugden G,
 Telegrams & Cables: Connoisseur Brighouse.

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT 8%

12 AND 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS				
Ref	12V Amps	24V Amps	£	P & P
111	0.5	0.25	2.20	0.45
213	1.0	0.5	2.64	0.78
71	2	1	3.41	0.78
18	4	2	4.03	0.96
70	6	3	5.35	0.96
108	8	4	6.98	1.14
72	10	5	7.67	1.14
116	12	6	8.99	1.32
17	16	8	10.39	1.32
115	20	10	13.18	2.08
187	30	15	17.05	2.08
226	60	30	26.82	0A

30 VOLT RANGE				
Prim 220/240V Sec 0-12-15-20-24-30V				
Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V 15-0-15V, 12-0-12				
Ref	12V Amps	15V Amps	£	P & P
112	0.5	0.5	2.64	0.78
79	1.0	1.0	3.57	0.96
3	2.0	2.0	5.27	0.96
20	3.0	3.0	6.20	1.14
21	4.0	4.0	7.44	1.14
51	5.0	5.0	8.37	1.32
117	6.0	6.0	9.92	1.45
88	8.0	8.0	11.73	1.64
89	10.0	10.0	13.33	1.84

50 VOLT RANGE				
Prim 220/240V Sec 0-20-25-33-40-50V				
Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40, 25-0-25 or 20-0-20V.				
Ref	5V Amps	10V Amps	£	P & P
102	0.5	0.5	3.41	0.78
103	1.0	1.0	4.57	0.96
104	2.0	2.0	6.98	1.14
105	3.0	3.0	8.45	1.32
106	4.0	4.0	10.70	1.32
107	6.0	6.0	14.62	1.64
118	8.0	8.0	17.05	2.08
119	10.0	10.0	21.70	0A

60 VOLT RANGE				
Prim 220/240V Sec 0-24-30-40-48-60V				
Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V or 24-0-24V or 30-0-30V				
Ref	6V Amps	12V Amps	£	P & P
124	0.5	0.5	3.88	0.96
125	1.0	1.0	5.58	0.96
127	2.0	2.0	7.60	1.14
126	3.0	3.0	10.54	1.32
123	4.0	4.0	12.23	1.64
40	5.0	5.0	13.95	1.84
120	6.0	6.0	15.66	1.84
121	8.0	8.0	20.15	0A
122	10.0	10.0	24.03	0A
189	12.0	12.0	27.13	0A

MAINS ISOLATING (SCREENED)				
PRIM 120/240 SEC 120/240 CT				
Ref	VA (Watts)	£	P & P	
07*	20	4.40	0.79	
149	60	6.20	0.96	
150	100	7.13	1.14	
151	200	11.16	1.50	
152	250	12.79	1.34	
153	350	16.28	1.84	
154	500	19.15	2.15	
155	750	29.06	0A	
156	1000	37.20	0A	
157	1500	45.60	0A	
158	2000	54.80	0A	
159	3000	79.05	0A	

AUTO TRANSFORMERS				
Ref	VA (Watts)	Volts	£	P & P
113	20	0-115-210-240	2.48	0.71
64	75	0-115-210-240	3.95	0.96
4	150	0-115-200-220-240	5.35	0.96
66	300	0-115-200-220-240	7.75	1.14
67	500	0-115-200-220-240	10.99	1.64
84	1000	0-115-200-220-240	18.76	2.08
93	1500	0-115-200-220-240	23.36	0A
95	2000	0-115-200-220-240	34.82	0A
73	3000	0-115-200-220-240	48.00	0A

HIGH VOLTAGE MAINS ISOLATING				
Prim 200/220V or 400/440V				
Sec 100/120V or 200/240V				
Ref	VA	£	P & P	
60	243	5.89	1.32	
350	247	14.11	1.84	
1000	250	35.65	0A	
2000	252	54.25	0A	

CASED AUTO TRANSFORMERS				
240V cable in & 115V USA 2 pin outlet				
VA	£	P & P	Ref	
20	4.96	0.96	113W	
150	8.48	1.14	4W	
200	9.92	1.45	65W	
250	10.49	1.45	69W	
350	12.53	1.64	53W	
500	15.73	1.64	67W	
750	18.55	1.76	83W	
1000	22.88	0A	84W	
1500VA	26.02	0A	93W	
2000	37.65	0A	95W	

SCREENED MINIATURES			
Ref	mA	Volts	£
238	200	3-0-3	1.99
212	1A, 1A	0-6, 0-6	2.85
13	100	9-9-9	2.14
235	330, 330	0-9, 0-9	1.99
207	500, 500	0-8-9, 0-8-9	2.69
208	1A, 1A	0-8-9, 0-8-9	3.53
236	200, 200	0-15, 0-15	1.99
214	300, 300	0-20, 0-20	2.56
221	700 (DC)	20-12-0-12-20	3.41
206	1A, 1A	0-15-20-0-15-20	4.63
203	500, 500	0-15-27-0-15-27	3.99
204	1A, 1A	0-15-27-0-15-27	5.39
S112	500	12-15-20-24-30	2.64
239	50	12-0-12	1.99

TEST METERS		£71.00
AVO 8 MK5		
AVO 71		£29.00
AVO 73		£39.10
AVO MM5		£24.00
AVO TT169 in circuit		
Transistor Tester		£30.00
U4315 Budget Meter 20kΩ/V		
VDC 2kVAC 1000V AC/DC		
2.5A AC/DC 500k res. in		
robust steel case & lead etc.		£14.95
VAT 8% P & P	£1.15	
AVO cases and accessories		ex-stock.
Wee Megger		£58.80

BRIDGE RECTIFIERS			
		P & P	
200V	2A	£0.45	0.29
400V	2A	£0.55	0.29
200V	4A	£0.65	0.29
400V	4A	£0.80	0.29
400V	6A	£1.05	0.29
500V	10A*	£2.35	0.29

PLUS

HIGH QUALITY MODULES		
10 WATT RMS AMPLIFIER		£3.66
25 WATT RMS AMPLIFIER		£4.57
35 WATT RMS AMPLIFIER		£6.95
125 WATT RMS AMPLIFIER		*£15.95
PRE-AMP for 5-10 WATT		£6.70
PRE-AMP for 25 WATT		£13.68
POWER SUPPLIES 5-10 WATT		£1.30
POWER SUPPLIES 25 WATT		£3.75
TRANSFORMER 5-10 WATT		£3.09
*TRANSFORMER 25 WATT		£4.79
P & P Modules 35p. Trans. 96p. VAT 12 $\frac{1}{2}$ %		
STEREO 30 - Complete chassis in 7.7W rms amp. pre amp. power supply front panel knobs. (Need Trans.) £19.05. Trans. £3.57. Teak cab. £5.25. P & P £1.02. VAT 12 $\frac{1}{2}$ %.		

OSCILLOSCOPE CL-5		£58.80
10 meg. 3 inch tube. £55.00.		
Carriage £4.00, 8% VAT.		

RECORD DECK		
BSR P128R Single Player with Cartridge		£16.90 P & P £1.50 VAT 12 $\frac{1}{2}$ %

BLOB BOARD (Pack of 3)		
2.5" x 5.1" -1" or 2.5" x 5.1" -15"		£0.75
3.75" x 5.1" -1" or 3.75" x 5.1" -15"		£1.14
10" x 6" -1" or 10" x 6" -15"		£3.78
IC Range		
4.8" x 3.2" £0.96. 4.75" x 7.5" £2.13		
P & P 35p. VAT 8%		

MUSIC CENTRE CHASSIS		
FM (STEREO)/MW/LW 15 + 15W		£6.95
Musical Power Inc. Tran.		
Price £22.50 inc. VAT P & P £1.50		
VAT 8%		

POWER UNITS		
Stabilised 3-6-7.9V/400mA		
multiplug outlet		£5.95
3300 fits into 13A socket 6-7.5-9V		
300mA voltage outlet		£3.30
B12-3, 4, 5, 6, 7.5, 9, 12V 500mA		
DC plug outlet		£5.32
VAT 12 $\frac{1}{2}$ % P & P 55p		

ELECTRONIC CONSTRUCTION KIT		
10 projects (Including electronic organ). No soldering needed £7.29. VAT 8% P & P 70p		

DECS SOLDERLESS BREAD-BOARDING		
S Dec 70 contacts		£1.98
T Dec 208 contacts		£3.63
U Dec "A" for I.C.s etc		£3.99
U Dec "B" for I.C.s etc		£6.99
VAT 8% P & P 40p		

TRANSFORMERS SPECIAL OFFER (Limited Stocks)	
BE1 Prim 0-120, 0-120V (120 or 240V) Sec 24V 10A	£5.50 P & P £1.66
BE2 Prim 0-90-110, 200-220-240V Sec 0-110V 0-20-24V. 2.5A. £2.25 P & P 95p. VAT 8%	
BE3 100V line to 4Ω 7/10W £2.05 P & P 66p	
BE4 0-120 x 0-120, 9-0-9 1A. £2.40 P & P 71p	
BE5 15W matching trans. sec 15Ω suit EB9 £1.50 P & P 30p	
Ref 30 240-240 Isolators 200VA £4.20 P & P 96p	
Ref 62 240-240 Isolators 250VA £5.20 P & P 96p	

COMPONENT PACKS		
200 Mixed value resistors (count by weight)		
150 Mixed value capacitors (count by weight)		
30 Mixed value precision resistors $\frac{1}{2}$ W 2%		
15 Assorted pots		
10 Reed switches		
15 Wire wound resistors—mixed wattage		
1 Pack wire 50 metres assorted colours		
25 pre-sets assorted types and values		
Please state pack required.		
60p per pack. VAT 12 $\frac{1}{2}$ % P & P 40p		

MINI-MULTIMETER		
DC-1000V AC-1000V DC-100mA		
Res-150kΩ 1000Ω/V Bargain		£5.86
P & P 62p VAT 8%		

STEREO FM TUNER WITH PHASE-LOCK LOOP		
4 Pre-selected stations, varicap tuning, switched AFC, LED Beacon		£20.45
VAT 12 $\frac{1}{2}$ % P & P 40p.		

Barrie Electronics Ltd.
 3, THE MINORIES, LONDON EC3N 1BJ
 TELEPHONE: 01-488 3316/7/8
 NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST



TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
PHONE 01-672 3137/672 9080
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING
CONTROL SYSTEMS

PRICES INCLUDE VAT. P & P FREE
correct at 1/9/77

TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD. (PE127) or quote
Access/Barclaycard No. and post to TUAC LTD. (PE127) 119
Charlmont Road, London SW17 9AB. We accept phone orders
from Access/Barclaycard Holders. Phone 01-672 9080.

PRE AMPLIFIERS

Designed for use with TUAC power amplifier modules.



VA08

Vol. Treb. Mid and Bass controls. HI. IMP. FET. I/P suitable Mid.
Guitar, Radio Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at
16kHz. Mid +20 -15dB at 1kHz. Bass +20 -10dB at 40Hz.


VA06 **£9.00**

Vol. Treb. and Bass controls. Sensitivity 8mV. Treb +28 -15dB at
12kHz. Bass +18dB and 40Hz.

SVA08 STEREO PRE AMP **£7.75**

Vol. Treb. Mid and Bass controls. I/P suitable Guitar, Radio,
Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +
20 -7dB at 4kHz. Bass +20 -18dB at 30Hz Plus Full Balance Control.
Fully I/C operation supply voltage \pm 25VDC. **£15.00**

POWER SUPPLIES

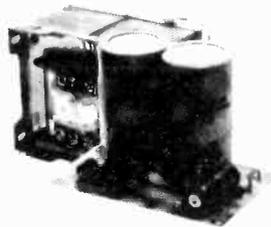

Vacuum varnish impregnated. Transformers
with supply board incorporating pre-amp supply:

PS250 for supplying 2 TP125s **£28.50**

PS200 for supplying 2 TP100s **£28.50**

PS60/60 for supplying 2 TL60s **£25.00**

PS125 \pm 45 volts for TP125 **£17.75**


PS100 \pm 43 volts for TL100 **£16.25**

PS60 \pm 38 volts for TL60 **£15.25**

PS30 \pm 25 volts for TL30 **£11.75**

PSU 2 for supplying disco mixer **£7.50**

AMPLIFIER MODULES

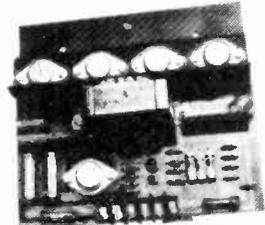

TL30 D.C. COUPLED 5 x 5 x 1 1/4 in.

• 35 watt R.M.S. continuous sine wave output
• 8 transistors 4 diodes **£12.75**

TL60 5 x 5 x 3 in

• 60 watt R.M.S. continuous sine wave output
• 2 R.C.A. 110 watt 15 amp transistors **£18.25**


TL100

• 100 watt R.M.S. continuous sine wave output
• 2 R.C.A. 150 watt 15 amp transistors **£20.75**

TP125 7 x 6 1/2 x 3 in

• 125 watt R.M.S. continuous sine wave output
• 4 R.C.A. 150 watt 15 amp output transistors **£25.75**

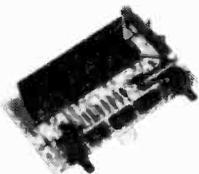4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSM1



- Full wave control
- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1/2W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection

£20.75

Model 501 500W per channel as above without
sound triggering **£12.25**

FRONT PANEL FOR LIGHTING EFFECT MODULES

(complete with switches, neons and knobs)
as illustrated



For S1LMB **£6.50**
Size 8" x 4 1/2"




4LSM1 **£5.50**
Size 6 1/2" x 4 1/2"



FUZZ LIGHTS
Red, Green, Blue,
Amber. **£23.50**



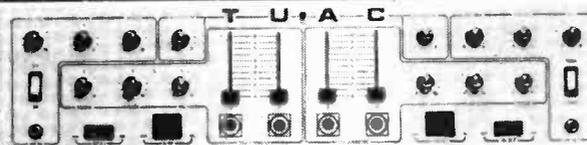S1LMB **£7.50**
Combined with 3SDM1
Size 9" x 4 1/2"



STEREO DISCO MIXER

With touch sensitive switching and auto fade

INPUTS: Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble and bass controls for each pair of sliders. Sensitivity mag. 3mV (R.I.A. A. comp.). Flat 50mV at 1kHz. Bass controls \pm 18dB at 60Hz. Treble controls \pm 18dB at 15kHz.

OUTPUT: Up to 3 volts (\pm 12dB) available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz - 25kHz \pm dB.

P.F.L.: Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.


Miscellaneous Facilities: Two illuminated deck on/off switches. Mains illuminated on/off switches. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions

Size: 25in long x 6in high x 3in deep.

£129.00

Mono Disco Mixer with autofade **£45.00**

3 CHANNEL LIGHT MODULATOR SILMB

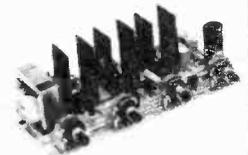

new from TUAC... ULTRA QUALITY HIGH POWER TD 500 POWER AMPLIFIER New DC coupled design

Output power using PS250
300w into 2 Ohms
220w into 4 Ohms
140w into 8 Ohms
75w into 15 Ohms
RMS continuous sine wave
output
INPUT Sensitivity 0.775V
RMS (ODB) at 25 KOHMS
Hum and Noise - 100dB
Relative full output
THD = at Full Power 0.1%



7" x 9" x 1 3/8" **£45**

PIEZO SUPER HORN £10.95

STOCKISTS - CALLERS ONLY

A1 Music, 88 Oxford Street, Manchester (Tel. 061-236 0340)
Geo Mathews, 85-87 Hurs! Street, Birmingham (Tel. 021-622 1941)
Bristol Disco Centre, 25 The Promenade, Gloucester Road (Tel. Bristol
41666).
Soccodi, 9 The Friars (Tel. Canterbury 60948)
Cookies Disco Centre, 132 West Street (Tel. Crewe 4739)
Garland Brog. Ltd., Deptford Broadway, London 01-692 4412
Luton Disco Centre, 88 Wellington Street, Luton (Tel. Luton 411733)
Mitchell Electronics, 7 Queen Street (Tel. Salisbury 23889)


Session Music, 163 Mitcham Road, Tooting (Tel. 01-672 3413).
Mon-Sat 10 a.m. - 6 p.m. Closed Wed.

- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 125W
- Full wave control

£20.25

Single Channel Version 1500 Watts **£9.75**

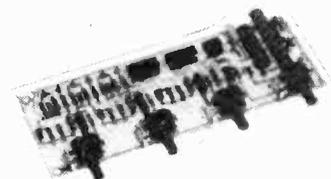ADD SEQUENCE CHASING + DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel

3SDM1 **£14.50**

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED
SEND NOW FOR OUR FREE 20 PAGE ILLUSTRATED CATALOGUE. S.A.E. STAMPED PLEASE

SPECIAL OFFER

FOR THIS MONTH

All
Prices Inc
VAT and
P. & P.
U.K. only

NO
EXTRA
CHARGES

Top Spec.
Branded
555 Timers
32p

TTL	74 Series	74xx	CMOS	R.C.A.	CD4050	CD4082
7400 13p	7441 74p	7494 85p	CD4002 18p	CD4022 94p	CD4054 129p	CD4086 24p
7401 15p	7442 74p	7495 75p	CD4001 18p	CD4023 21p	CD4055 129p	CD4088 200p
7402 15p	7443 74p	7496 85p	CD4002 18p	CD4024 21p	CD4056 144p	CD4501 100p
7403 16p	7444 123p	7497 85p	CD4003 18p	CD4025 29p	CD4060 117p	CD4502 139p
7404 22p	7447 182p	7498 85p	CD4007 28p	CD4026 199p	CD4068 79p	CD4503 34p
7405 23p	7448 182p	7499 85p	CD4008 27p	CD4027 199p	CD4071 22p	CD4510 132p
7406 44p	7454 139p	7500 85p	CD4009 27p	CD4028 99p	CD4072 22p	CD4511 173p
7407 44p	7470 29p	7501 85p	CD4010 13p	CD4029 182p	CD4076 22p	CD4516 132p
7408 23p	7472 29p	7502 85p	CD4011 13p	CD4030 52p	CD4077 22p	CD4518 114p
7409 23p	7473 29p	7503 85p	CD4012 13p	CD4031 52p	CD4078 22p	CD4522 100p
7410 18p	7474 33p	7504 85p	CD4013 56p	CD4041 87p	CD4078 187p	CD4528 100p
7411 24p	7475 44p	7505 85p	CD4015 87p	CD4042 87p	CD4077 22p	CD4528 100p
7412 24p	7476 44p	7506 85p	CD4016 87p	CD4043 87p	CD4078 22p	CD4528 100p
7413 38p	7480 46p	7507 85p	CD4017 87p	CD4044 86p	CD4078 22p	CD4528 100p
7414 41p	7482 81p	7508 85p	CD4018 87p	CD4045 199p	CD4078 22p	CD4528 100p
7416 33p	7483 85p	7509 85p	CD4019 87p	CD4046 131p	CD4081 23p	CD4528 100p
7417 33p	7485 106p	7510 85p	CD4020 118p	CD4047 99p		
7425 28p	7486 36p	7511 85p	CD4021 99p	CD4048 85p		
7427 28p	7487 36p	7512 85p				
7428 28p	7488 36p	7513 85p				
7432 28p	7489 36p	7514 85p				
7437 28p	7493 57p	7515 85p				

DIODES	BRIDGE RECS	TRIAKES	ZENERS
BY127 16p	1 amp 50 P.I.V. 25p	2 amp 100 P.I.V. 26p	Range 2 - 25 volts
OA47 9p	1 amp 100 P.I.V. 25p	2 amp 200 P.I.V. 42p	400m watts 10p
OA73 16p	1 amp 200 P.I.V. 28p	4 amp 400 P.I.V. 71p	1.3 watts 29p
OA81 15p	1 amp 500 P.I.V. 42p	6 amp 600 P.I.V. 86p	
OA85 14p	1 amp 1000 P.I.V. 62p	10 amp 1000 P.I.V. 100p	
OA81 15p		10 amp 400 P.I.V. 43p	
OA85 14p		10 amp 600 P.I.V. 62p	
OA81 15p		10 amp 1000 P.I.V. 100p	
OA85 14p			
OA81 15p			
OA85 14p			

TRANSISTORS	ROTARY SWITCHES	TRANSFORMERS
BC148 18p	1 Pole 2 way 44p	LT44 60p
BC157 11p	2 Pole 2 way 44p	LT700 60p
BC158 13p	2 Pole 4 way 44p	6-0-6 100MA 93p
BC168 12p	2 Pole 6 way 44p	7-0-7 100MA 93p
BC169 12p	3 Pole 2 way 44p	7-0-9 100MA 93p
BC171 12p	3 Pole 4 way 44p	7-0-9 220-100 2A 23p
BC172 12p	3 Pole 6 way 44p	12-0-12 100MA 93p
BC173 12p	4 Pole 2 way 44p	0-0-0-0 280MA 146p
BC174 12p	4 Pole 4 way 44p	0-10-12 150MA 156p
BC175 12p	4 Pole 6 way 44p	6.3V-1.5A 264p
BC176 12p	Meaning DPDT 45p	
BC177 12p	BUILD-IN Foot Switch 160p	
BC178 12p	DPDT 180p	
BC179 12p	SPST 115p	
BC180 12p		
BC181 12p		
BC182 12p		
BC183 12p		
BC184 12p		
BC185 12p		
BC186 12p		
BC187 12p		
BC188 12p		
BC189 12p		
BC190 12p		
BC191 12p		
BC192 12p		
BC193 12p		
BC194 12p		
BC195 12p		
BC196 12p		
BC197 12p		
BC198 12p		
BC199 12p		
BC200 12p		

SWITCHES	OPTO	ROTATIONERS	SLIDERS
Toggle SPST 27p	111 201 Red 24p	1K-2MΩ Single gang LIN or LOG 57p	0.33W 10Ω-1MΩ E24 30p
DPST 27p	111 201 Green 24p	5K-2MΩ Single gang D/P switch LOG 27p	0.5W 10Ω-10MΩ E24 21p
DPDT 27p	111 201 Yellow 24p	5K-2MΩ Dual gang stereo LIN or LOG 79p	2.5W 0.22Ω-10Ω w/w 23p
SPST 44p	7 Red 18p	5K-2MΩ Dual Gang Stereo LIN or LOG 86p	5W 4 7Ω-10Ω w/w 12p
SPDT 75p	7 Yellow 30p	5K-500K Single Gang LIN or LOG 79p	10W 10Ω-10KΩ w/w 210p
DPDT 75p	7 Green 30p	5K-500K Dual Gang Stereo LIN or LOG 86p	5 DEC 12p
SPST 54p	111 201 Clip 4p	Present sub. min. var. Horiz 100Ω-5MΩ 10p	7 DEC 30p
SPDT 56p	111 201 Clip 5p	Slider Bezels 21p	4 DEC A 61p
DPDT 60p			4 DEC B 71p
Push Button SPST Locking 46p			
Push Button SPDT Locking 46p			
Push Button DPDT Locking 46p			
Beas push to make 15p			
Beas push to break 20p			
Slide DPDT SUB MIN 13p			
Slide DPDT STD 13p			
Slide DPDT OFF 13p			

LOUD SPEAKERS

1 1/2" 8Ω	72p	Desoldering Gun	640p
2" 8Ω	72p	Spare Nozzle	95p
2 1/2" 8Ω	72p	Antex X25 Watt Iron	387p
2" 16Ω	64p	Antex C 2.15 Watt Iron	387p
2 1/2" 16Ω	64p	Antex CX 15 Watt Iron	387p
2" 8Ω	72p	PP3 Battery Clips	4p
2 1/2" 8Ω	72p	PP3 Battery Clips	4p
2" 16Ω	64p	Battery Holder 4 pen Cells	29p
2 1/2" 16Ω	64p	Etching Pen	81p
3 1/2" 16Ω	72p	Ferric Chloride	95p
6 3 Mono	26p	Etching Kit	249p
6 3 Stereo	35p	Telephone Pick-Up Coil	70p
8CA Phono	12p	Ear Piece 2.5mm or 3.5mm	16p
DIN 2, 3, 4, 5, 6, 7 pin	15p	Ear Piece Crystal	33p
SKT 2, 3, 4, 5, 6, 7 pin	15p		

Minimum Order £2
Brand new full spec. and fully guaranteed devices—
Orders despatched by return of post—cheque/P/O with
order.
We are situated 2 min. from Watford Junction Station.
Our retail shop carries a comprehensive range of
electronic and audio component parts and accessories.
Send 40p for our latest catalogue.
Government, Colleges and Educational Institution orders
accepted.
Trade and export enquiries welcome.

THE COMPONENT CENTRE

7 Langley Road, Watford, Herts WD3 2PR
Tel: Watford 45333
Open Mon-Sat 9.30-5.30 Closed Wed

A new professional instrument case from

AMATEK



Size:
Panel 7" x 3"
Depth 6"

AMATEK's new Instrument Case Type PDS - professionally designed for you. Everything just drops into place. It's assembled in minutes - no drilling or filing.

CHECK THESE FEATURES.

1. Front panel moulding ready pierced, with fixing brackets for up to 10 pushbutton switches (Doram etc); recessed fixing for full sized rotary switch; panel drilled for input sockets or terminals; blank adhesive label supplied; easily worked and lettered.
2. Aluminium PVC-coated body with ready-punched back panel for fuseholder and mains cord; holes easily blanked off for battery use.
3. Display aperture with bezel and filter accepts up to seven digits, or meter movement.

With AMATEK's new PDS Case, range of hardware accessories, and display, DVM and counter modules, you can make a really professional instrument - and fast!

Case PDS with red filter and screw kit: £8.50 + 30p postage + 8% VAT. Display Module DB 4-500 (multiplexed, 3 1/2 or 4 digits, 0.5"): £6.20 + 30p postage + 8% VAT (state common anode or common cathode).

SAE brings illustrated leaflet and price list.


22 Bardsley Lane, Greenwich, London SE10 9RF. Phone Orders 01-853 0868. Access, Barclaycard, Visa accepted. Trade and OEM enquiries welcome.

AMATEK

AUDIBLY SUPERIOR AMPLIFICATION

HIGH DEFINITION - 'MUSICAL' - POWER AMP MODULES

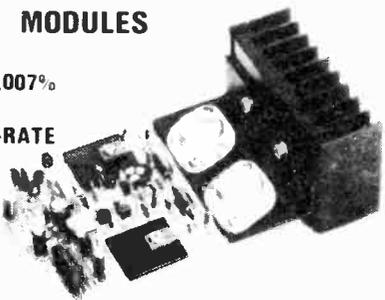- ★ T.H.D. TYPICALLY .007%
- @ 10W, 500Hz
- ★ ZERO T.I.D. (SLEW-RATE LIMIT 16 V/μS)



Module size:
120 x 80 x 25 mm. using
glass fibre pcb with ident
and solder resist.
Illustrated with light duty
heatsink.

CRIMSON ELEKTRIK power amplifier modules are fast gaining a reputation as the best sounding, most musical modules available. Perhaps the most important features of this design are exceptional freedom from crossover distortion (due to the use of output triodes) and zero T.I.D. The amplifier is protected against open and short circuit loads and yet will drive a highly reactive low impedance load which is more representative of a real loudspeaker. Square waves maintain their rise times up to full power whilst simulated electrostatic loads are easily handled with negligible overshoot and a settling time of 12μs. Other specs S/N > 110dB. Rise time 10μs. Sensitivity 775mV. DC coupled. 5Hz-35kHz (-3dB). THD < 0.01%. 100mV clipping, 500Hz.

CRIMSON ELEKTRIK power supplies are in kit form for maximum flexibility and feature a low field aluminium toroidal transformer with a 120-240v primary and screen, two large capacitors bridge rectifier and all fixings.

Heatsinks are attractive black anodised extrusions, 80mm wide.

POWER AMP MODULES	HOME	EUROPE
CE 500 8watts 8 ohms 35v dc	£16.30	£16.30
CE 100A 100Watts 1 ohms 35v dc	£19.22	£19.00
CE 100B 100Watts 8 ohms 45v dc	£23.22	£22.70
POWER SUPPLIES		
CPS 1 for 2xCE100B or 1xCE100A	£12.85	£14.20
LP 2 for 2xCE100A or 2 or 4xCE100B	£14.55	£17.90
EPS 3 for 2xCE100B	£15.85	£19.20
HEATSINKS		
Light Duty 50mm 2 C W	.90	£1.30
High power 100mm 1.4 C/W	£1.60	£2.40
Disc group 150mm 1.1 C/W	£2.30	£3.65

CRIMSON ELEKTRIK (PE)
1A STAMFORD STREET, LEICESTER LE1 6NL.
Telephone: (0533) 537722.

Home prices include VAT and carriage. Payment by cheque. PO COD 60p (£50 limit). Export no problem. European prices include carriage, insurance and handling payment in Sterling by bank draft, PO. International Giro or Money Order. Outside Europe please write for specific quote by return. Send SAE or two International Reply Coupons for full literature. Favourable trade quantity price flat on request. Suitable pre-amp circuit 20p.



Wilmslow Audio

THE firm for speakers!

SEND 10p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND DISCOUNT PRICE LIST

ACT ● AUDAX ● BAKER
 BOWERS & WILKINS ● CASTLE ● CELESTION
 CHARTWELL ● COLES ● DALESFORD
 DECCA ● EMI ● EAGLE ● ELAC ● FANE
 GAUSS ● GOODMAN'S ● HELME ● I.M.F.
 ISOPHON ● JR ● JORDON WATTS
 KEF ● LEAK ● LOWTHER ● MCKENZIE
 MONITOR AUDIO ● PEERLESS ● RADFORD
 RAM ● RICHARD ALLAN ● SEAS
 TANNOY ● VIDEOTONE ● WHARFEDALE

WILMSLOW AUDIO (Dept. P.E. 8)
SWAN WORKS, BANK SQUARE, WILMSLOW,
CHESHIRE SK9 1HF


Discount Hi-Fi, etc. at 5 Swan Street and 10 Swan Street
Tel.: Wilmslow 29599 for Speakers Tel.: Wilmslow 26213 for Hi-Fi

CHINAGLIA DINO—ELECTRICAL AND ELECTRONIC TEST EQUIPMENT MANUFACTURERS

PRESENT THE

DOLOMITI

20k Ω /V a.c. and d.c.

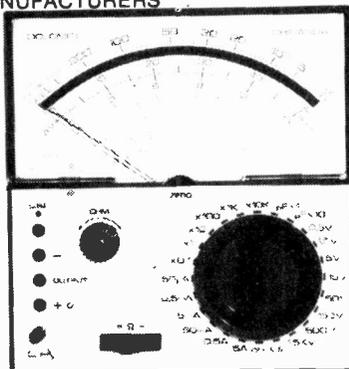

A NEW HIGH SENSITIVITY MULTIMETER WITH ALL THE FEATURES YOU WILL EVER NEED

Accuracy: D.C. ranges, $\pm 2.0\%$, A.C. & Ω ranges $\pm 2.5\%$.
39 ranges: d.c. V, 0-150mV, 500mV, 1-5V, 5V, 15V, 50V, 150V, 500V, 1-5kV; d.c.I, 0-50 μ A, 500 μ A, 5mA, 50mA, 0-5A, 5A; a.c. V, 5V, 15V, 50V, 150V, 500V, 1-5kV; a.c.I, 5mA, 50mA, 0-5A, 5A; dB -10 to +65 in 6 ranges; Ω 0-0.05k Ω , 5k Ω , 50k Ω , 500k Ω , 5M Ω , 50M Ω , pF 50k pF, 500k pF.

Automatic overload protection and high current range fusing. Scale mirror and fine pointer for accuracy of reading. Single knob main range switching and all panel controls. C.E.I. Class 1 movement with sprung jewel bearings. Extended 92mm scale length for extra clarity. Compact ABS case 125 x 131 x 37mm. Weight 750g with batteries. Supplied complete with carrying case, fused leads, handbook and full 12-month guarantee. Optional 30kV d.c. probe available.

Meter £45.90 incl. VAT (£1 P. & P.)
30kV Probe £12.85 incl. VAT

For details of this and the many other exciting instruments in the Chinaglia range, including multi-meters, component measuring, automotive and electronic instruments please write or telephone.

ALCON

 Instruments Ltd.

19 MULBERRY WALK, LONDON SW3 6DZ TEL: 01-352 1897

Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11 $\frac{1}{2}$ in x 8 $\frac{1}{2}$ in and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

Design of Digital Systems.



£7.10

plus 90p packing and surface post anywhere in the world.

Overseas customers should send for proforma invoice

Quantity discounts available on request. VAT zero rated.

Also available—a more elementary course assuming no prior knowledge except simple arithmetic.

Digital Computer Logic and Electronics

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

£4.60

plus 90p P. & P.

Offer Order both courses for the bargain price £11.10, plus 90p P. & P.—a saving of £1.50.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

NEW from Cambridge Learning Enterprises:
FLOW CHARTS AND ALGORITHMS—use, design and layout; vital for computing, training, wall charts, etc. **£2.95** plus 45p P. & P.

Guarantee—If you are not entirely satisfied your money will be refunded.

Cambridge Learning Enterprises, Unit 2, Rivermill Lodge, St. Ives, Cambs. PE17 4BR. Proprietors: Drayridge Ltd. Reg. Office: as above. Regd. in England No. 1328762.

To: Cambridge Learning Enterprises, FREEPOST, Unit 2, Rivermill Lodge, St. Ives, Huntingdon, Cambs. PE17 4BR

- *Please send me . . . set(s) of Design of Digital Systems at £8.00 each, P. & P. included
- *or . . . set(s) of Digital Computer Logic and Electronics at £5.50 each, P. & P. included
- *or . . . combined set(s) at £12.00 each, P. & P. included
- *or . . . the Algorithm Writers Guide at £3.40 each, P. & P. included

Name

Address

*delete as applicable
No need to use a stamp—just print FREEPOST on the envelope.

PE1

FIRST GRADE DEVICES BY MAJOR MFRRS

SPECIAL XMAS OFFER

OF POPULAR ITEMS SELECTED
FOR REGULAR REQUIREMENTS

TEXAS TTLs

7400 12p
7402 12p
7404 15p
7408 16p
7410 12p
7413 28p
7414 54p
7420 12p
7430 12p
7441 60p
7442 45p
7447 60p
7474 25p
7475 34p
7486 25p
7490 30p
7493 30p
7496 55p
74121 26p

74123 48p
74141 59p
74145 60p
74151 50p
74153 50p
74154 90p
74157 52p
74160 65p
74164 80p
74190 90p
74192 75p
74193 75p
74196 70p

TEXAS DIL SOCKETS

14 pin 11p 24 pin 24p
16 pin 12p 40 pin 43p
AY-5-1013P UART £5

CMOS

4009 35p
4011 16p
4013 35p
4016 35p
4017 65p
4024 55p
4046 100p
4049 35p
4510 80p
4518 70p
4528 75p

STAR OFFERS

741 8 pin DIL 18p
555 8 pin DIL 25p
723 14 pin DIL 30p
LM309K TO3 110p
TIL209 LED 10p
2102-2 RAM 125p

301A 28p
748 28p
LM380N 75p
TBA800 80p
TBA810S 85p

VOLTAGE REGULATORS Plastic - TO 220

1 Amp Positive
5V 7805 85p
12V 7812 85p
15V 7815 85p

1 Amp Negative
5V 7905 110p
12V 7912 110p
15V 7915 110p

100mA Positive - TO92
5V, 12V, 15V 35p each

OPTO DEVICES

LEDs: 0.2" Red 14p, Green 16p
FND500/507 0.5" RED CC/CA 100p
TIL321/322 0.5" RED CA/CC 110p

MINIMUM ORDER £10 EXC. VAT

DISCOUNTS 10% on order over £50
 20% on order over £100

OFFER CLOSES ON 21/1/1978

Please send SAE for complete offer lists. We stress the fact that we are totally quality conscious and do not offer sub-standard or re-branded products for sale.

Please add VAT to total.
Please add Ins. + P & P 54p

**MAIL
ORDER
ONLY**

TECHNOMATIC LTD (PE)
54 SANDHURST ROAD
LONDON NW9 9LR

CRESCENT RADIO LTD.

MAIL ORDER DEPT.

1 ST. MICHAELS TERRACE, WOOD GREEN,

LONDON N22 4SJ

PHONE: 888-4474

POPULAR HIGH POWER AMPLIFIER
70 watts R.M.S. continuous into 8 ohms. Ready to use. S.A.E. for further details. Size: 540mm x 250mm x 145mm approx. Cost: £71 + 8% VAT.

PIEZO ELECTRIC HORN UNITS

New High Quality. High Power tweeter (100 watts). No Xover required. Response: 3-8kHz to 28kHz. Spec. sheet sent on receipt of S.A.E.

Our price: £7.80 each + 8% V.A.T.



CLEAR PLASTIC PANEL METERS (FULL SCALE)

Size 59 x 46 x 35mm. These meters require a 38mm dia. hole for mounting.

ME 6 - 0-50µA ME13 - 0-100mA
ME 7 - 0-100µA ME14 - 0-500mA
ME 8 - 0-500µA ME16 - 0-50V DC
ME 9 - 0-1mA ME17 - 0-300V AC
ME10 - 0-5mA ME18 - 'S' METER
ME11 - 0-10mA ME19 - 'VU' METER
ME12 - 0-50mA

Our Price: £5.00 + 8% V.A.T.

"CRESCENT" 100 WATT R.M.S. AMPLIFIER KIT

This kit consists of three modules, power amp. module, pre-amp. module and power supply module including mains transformer. Requires no technical knowledge as full instructions are supplied. S.A.E. for further details.

Limited Stock—Buy Now While Stocks Last. Cost: £30 + 8% VAT.

ACCESS AND BARCLAYCARD ACCEPTED—PHONE ORDERS WELCOMED
ALL PRICES INCLUDE POSTAGE—PLEASE ADD V.A.T. AS SHOWN—S.A.E.
WITH ALL ENQUIRIES PLEASE

Personal callers welcome at: 164-166 High Road, Wood Green, N22. Phone: 888 3206
and 13 South Mall, Edmonton N9. Phone: 803 1685

EFFECTS PROJECTOR "150" (150 watt)

Ideal for disco work, this versatile machine takes a range of accessories and is of a sturdy metal construction. Comes complete with bulb and 6in. Liquid Wheel. Ready to use.



A bargain at £34 + 8% V.A.T.

3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT (1000 Watt per channel)

Three channel: Bass, Middle, Treble. The input of this unit is connected to the loudspeaker terminals of an amplifier and the required lighting is connected to the output terminals of the unit thus enabling you to produce a fascinating sound to light display. Full instructions supplied or S.A.E. for details.

Fantastic Value at £20.00 + 8% V.A.T.

LOUDSPEAKER SELECTION + 12½% V.A.T.

2½in. 8, 40, and 75 ohm at £1.10 (please state which impedance is required)
5in. 8 ohm Ceramic at £1.70
8in. Goodmans "Audiom 8PA" 8 ohm 15W £5.26.
10in. "ELAC" Dual Cone 8 ohm 10 watt at £4.75

THE IDEAL ANYTIME PRESENT

MINIATURE SOLDERING IRON

for HOBBY or TRADE

MAIL ORDER PRICES:
(including VAT and P and P)

Irons £3.70 each

Bits 41p each

(Bit type 20 fitted as standard).

Stands
£3.90 each

Solder 28p & 56p

18 watts of power at 240v. straight to the bit

BIT SIZES:

19 (1.5 mm) 20 (3.0 mm)
21 (4.5 mm) 22 (6.0 mm)


Trade Enquiries Welcome

From your Local Dealer or Direct from the Manufacturers:

S. & R. BREWSTER Ltd.
86-88 UNION ST · PLYMOUTH Tel 0752-65011

LOOK! Here's how you master electronics




... the practical way

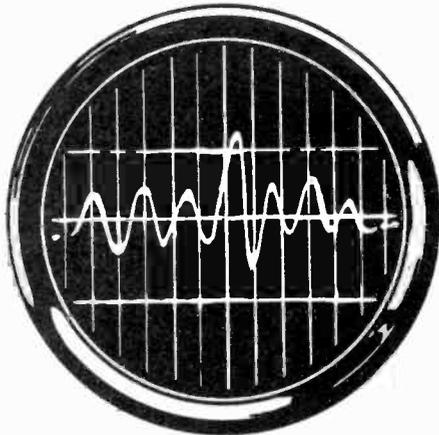

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

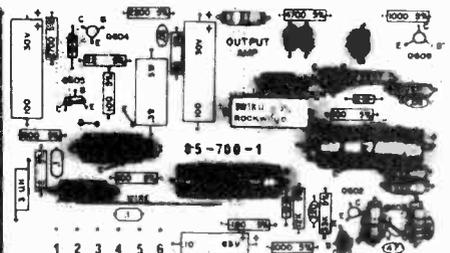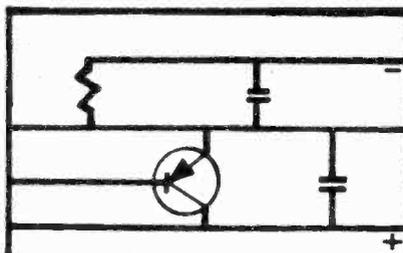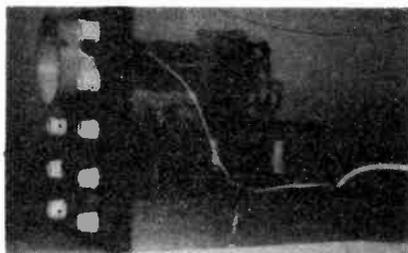All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



1 Build an oscilloscope

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.


2 Read, draw and understand circuit diagrams

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3 Carry out over 40 experiments on basic circuits

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

FREE GIFT

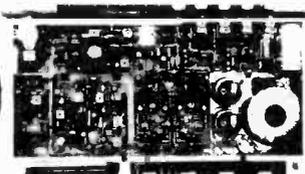

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Free!

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free-colour brochure and full details of enrolment.

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME

ADDRESS

PEB1

Block caps please

SAXON ENTERTAINMENTS LTD

THE PIONEERS OF MODULAR DISCO/P.A. EQUIPMENT
NOW OFFER PACKAGE DEALS AT INCOMPARABLE PRICES

CENTAUR STEREO DISCOS

C/W LIGHT SHOW & DISPLAY,
TWIN SPEAKERS & LEADS

Standard 100W

£225 or Deposit £28.80
12 Months @ £21.18 or 24 Months @ £11.81

Super 200W

£275 or Deposit £32.80
12 Months @ £25.89 or 24 Months @ £14.44

GXL 200W (with twin 200 watt cabinets)

£349 or Deposit £42.72
12 Months @ £32.49 or 24 Months @ £18.11

BSR Decks – 17,000 Line Loudspeakers – Rugged Aluminium Trimmed Cabinets – Cue Light And Phones
Output – Slave Output – Deck Lights/Motor Starts (GXL)

COMPLETE STEREO
ROADSHOWS – BUILT IN
SOUND TO LIGHT/SEQUENCER
& DISPLAY
TWO YEAR GUARANTEE

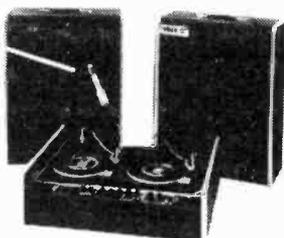


Illustration shows GXL Centaur System

These systems feature full mixing for two decks tape & mic with monitoring facilities – override and are supplied complete with sound to light + sequencer, display, speaker leads etc.

JUST PLUG IN AND GO!

MINI DISCO 100 WATT MONO SYSTEM

£159.50 Deposit £22.66

12 Months @ £14.60
or 24 Months @ £8.14

Similar in appearance to the Centaur and complete with loudspeakers and leads.

Headphones to suit any system £7.50
EM507 Electret Mic £15.00
ECM 81 Electret Mic £19.95
Boom Stand £15.50
Carriage on all disco systems £10.00
(Included in H.P. Prices)


**10% Deposit Terms
On All Orders
Over £150 – 12 or 24
Months – Low Interest**

D.I.Y. MODULES FOR ALL DISCO/P.A. AMPLIFIERS

SA308 30W 8 ohms 45V	£9.95*	SUPPLY FOR TWO MODULES	£10.90*
SA604 60W 4 ohms 50V	£13.25	SUPPLY FOR TWO MODULES	£13.50
SA608 60W 8 ohms 65V	£14.25	SUPPLY FOR TWO MODULES	
SA1204 120W 4 ohms 75V	£15.95	SUPPLY FOR ONE MODULE	£22.50
SA1208 120W 8 ohms 95V	£21.00	SUPPLY FOR TWO MODULES	
SA2404 240W 4 ohms 95V	£29.50	SUPPLY FOR ONE MODULE	

0.2% Distortion, 30Hz-20, KHz ± 2dB, Fully Short/Open Circuit proof input sensitivity 240 mV to suit most mixers – D.C. & Output Fuses fitted.

TOP QUALITY COMPONENTS THROUGHOUT

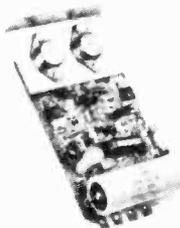

DISCO MIXERS – COMPLETE OR MODULAR



MONO OR STEREO
WITH AUTOFADE

Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted – full instructions supplied.

FEATURES INCLUDE:


Twin Deck – Mic & Tape Inputs – Wide range bass & treble controls – Full headphone monitoring – Crossfade – Professional standard performance.

MODULES	
Mono module	£22.50
Stereo module	£33.50
Panel	£3.95
Kit of knobs/sockets etc	£5.50
COMPLETE MIXERS (with case)	
Mono 18V	£39.50
Stereo 18V	£57.50
Mono mains	£45.75
Stereo mains	£63.75

COMPLETE LIGHTING CONTROL AT YOUR FINGERTIPS!



Lighting Control Unit Mk II	£44.50
4kW Sequencer + Sound Light + Dimmers	
+ Automatic Level Integrated Logic Circuitry	Module £32.50 Panel £2.95
Three Channel Sound to Light	£26.75
3kW 1-240W input – master	Module £19.75 Panel £2.95
Plus channel controls	

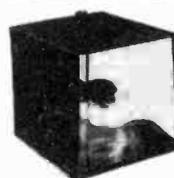

STROBE UNITS

Pro-Strobe 4-6 Joules £37.50
Super Strobe 2-3 Joules £22.50
(Pro-Strobe has external trigger facility).

SPARES & ACCESSORIES – LOUDSPEAKERS & CABINETS

Rope Lights – Red or Multicolour	£22.00	Melos Echo Chamber	£59.00
per 12 ft.		Headphones	£7.50*
Rope Light Controller for up to 120 ft	£30.00	Sirens: English Police, USA Police,	
Fuzz Lights – Red/Blue/Yellow/Green	£22.80	Destroyer	£8.90
Magnetic Cartridge Equalisers	£3.50*	Bulgin 8 way lighting plug/socket	£1.90

PROJECTORS – PLUTO –

CHOICE OF WHEEL/CASSETTE

P150 150W Tungsten	£37.50	Liquid wheels	£7.50
P500 100W Q.I.	£79.50	Cassettes	£8.00
P500 250W Q.I.	£89.50	Picture wheels from	£5.00
		(Wide choice available)	

100 Watt Chassis Loudspeakers 12"	£23.50	18"	£47.50	(Add £1.50 carr.)
Empty Loudspeaker Cabinets: Small 12"	£14	Large 12"	£18	Small 2 x 12"
Large 2 x 12"	£28	1 x 18"	£28	

Projector lamps: A1167 £2.90. M6 £5.65.
100W Spot lamps Red/Blue/Yellow/Green
£1.50 ea £13.50 for 10
Spot banks: 3 way £7.50 6 way £11.50
12 way £18.50
Bubble machines (optokinetics) £36.50


Strobe tubes 80W £8.50
ICI Vynide 50" wide £3.50 Metre
Kickproof Grille 24" wide £3.25 Metre
Kick Resistant Grill 50" wide £3.25 Metre.
FULL RANGE OF RE-AN PRODUCTS IN STOCK
SEND FOR OUR BROCHURE NOW!!

PIEZO HORNS only £7.50 YES! – only £7.50

(As fitted to our package PA system)

Direct from Motorola Inc., USA at an
UNBEATABLE PRICE

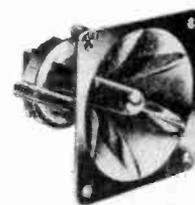No crossover required 4kHz – 30kHz rated
75W/8 ohms 150W/4 ohms use two per 100W
amplifier – Full instructions supplied.





PACKAGE P.A. SYSTEMS (2 Year Guarantee)

Complete with PIEZO horn columns fitted with 100 watt units (100 watt system illustrated)


100 Watt £145
Deposit £19.70

12 Months @ £13.66 or 24 Months @ £7.61

200 Watt £225
Deposit £28.80

12 Months @ £21.18
24 Months @ £11.81

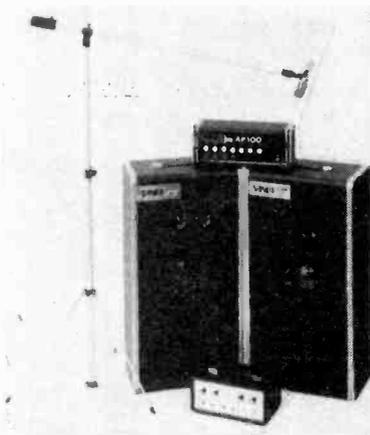These systems come complete with a Four Channel Amplifier, Leads etc. The 200 Watt system features Twin 100 Watt drive units in each cabinet.




ALSO ILLUSTRATED:

Melos Echo Unit **£59.00** Boom Stand **£15.50** Electret Mic ECM81 **£19.95*** Floor Stands **£9.90** EM507 Mic* **£15.00** Phasers **£19.80**

D.I.Y. MODULES FOR P.A. SYSTEMS Mono or Stereo

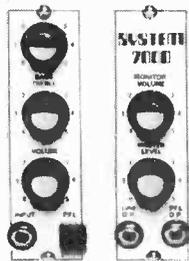Make your own mixer - Mono/Stereo - up to 20 channels with these, easy to wire modules - Available as PCB's or assembled on panels.



Input Stages Up to 20	Mono PCB	£5.95	Mono C/W panel etc.	£8.95
	Stereo PCB	£9.50	Stereo C/W panel etc.	£12.50
Mixer/Monitor (One only per system)	Mono PCB	£5.95	Mono C/W panel etc.	£8.95
	Stereo PCB	£9.50	Stereo C/W panel etc.	£12.50
Power supply for up to 20 channels		£9.50	Blank panel	£1.00

Send for free brochure for complete specification

Saxon AP100 Amplifier £45

Four mixing inputs - 100W into 4 ohms
Wide range bass & treble controls
+ master - Twin outputs

Saxon 150 Amplifier £59

Four mixing inputs - 100W into 8 ohms
150W into 4 ohms - wide range bass & treble controls + master



All prices subject to 8% VAT except where asterisked (12 1/2%)
Shop premises open Mon to Sat 9 am - 5 pm Lunch 12.30 - 1.30 pm
Mail order dept open Mon to Fri 10 am - 4 pm - Ring 01-684 6385

TO ORDER

By Post Send your requirements with cheque crossed P.O. or 60p COD charge to address below - or just send your Access or Barclay Card Number NOT THE CARD

By Phone You may order COD, Access or Barclay Card

Post & Packing 50p on all orders except where stated.

SAXON ENTERTAINMENTS LTD.

327 Whitehorse Road, Croydon, Surrey.

All Enquiries Large SAE Please Brochures on request.

Sparkrite mk2

Capacitive discharge electronic ignition kit



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Optimum fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch.
Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service - phone (0922) 33008

PRICES INCLUDE VAT, POST AND PACKING. Improve performance & economy NOW

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT, post & packing

ELECTRONICS DESIGN ASSOCIATES, 82 Bath St., Walsall, WS1 3DE

POST TODAY!

Quick installation
No engine modification required

Electronics Design Associates, Dept. PE1
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name
Address

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY REQD.	I enclose cheque/PO's for £
Mk. 2 Ready Built Negative Earth @ £14.97		
Mk. 2 Ready Built Positive Earth @ £14.97		Cheque No. _____
Ignition Changeover switches @ £4.30		
R.P.M. Limit systems in above units @ £2.42		Send SAE if brochure only required.

PAKS—PARTS—AUDIO MODULES

PANEL METERS

4in RANGE

Size 4½ x 3½ x 1½in

Value	No.	Price
0-50µA	1302	£5.75
0-100µA	1303	£5.75
0-500µA	1304	£5.75
0-1mA	1305	£5.75
0-50V	1306	£5.75

2in RANGE

Size 2½ x 1½ x 1½in

Value	No.	Price
0-50µA	1307	£4.50
0-100µA	1308	£4.50
0-500µA	1309	£4.50
0-1mA	1310	£4.50
0-50V	1311	£4.50

MR2P TYPE

Size 42 x 42 x 30mm

Value	No.	Price
0-50µA	1313	£4.95
0-1mA	1315	£4.95

EDGEWISE

Size 3½ x 1½ x 2½in

Cut out 2½ x 1½in

Value	No.	Price
0-1mA	1316	£3.80
0-500µA	1317	£3.80

MINIATURE BALANCE/TUNING METER

Size 23 x 22 x 26mm

Sensitivity 100/0/100mA

No.	Price
1318	£1.95

BALANCE/TUNING

Size 45 x 22 x 34mm

Sensitivity 100/0/100µA

No.	Price
1319	£2.00

MIN. LEVEL METER

Size 23 x 22 x 26mm

Sensitivity 200µA

No.	Price
1320	£1.95

Vu METER

Size 40 x 40 x 29mm

Sensitivity 130µA

No.	Price
1321	£2.00

MINI MULTI-METER

Size 60 x 24 x 90mm

Sensitivity 1000 ohms/V

A.C. VOLTS 0-10, 50, 250, 1000

D.C. VOLTS 0-10, 50, 250, 1000

D.C. CURRENT 0-1 100mA

Resistance 0-150kΩ

No.	Price
1322	£5.95

P&P

Postage and Packing add 25p unless otherwise shown. Add extra for airmail. Minimum order £1.

TRANSISTORS BRAND NEW—FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC126	£0.18	BC109B	£0.08	BC549	£0.12	BFY51	£0.14	TIP2955	£0.95
AC127	£0.18	BC109C	£0.08	BC550	£0.12	BFY52	£0.14	TIP3055	£0.75
AC128	£0.18	BC147	£0.10	BC556	£0.14	BIP19	£0.38	TIS43	£0.24
AC128K	£0.26	BC148	£0.10	BC557	£0.13	BIP20	£0.38	TIS90	£0.22
AC132	£0.20	BC149	£0.10	BC558	£0.12	BIP20/20MP	£0.80	UT46	£0.22
AC134	£0.20	BC152	£0.10	BC559	£0.14	BRY39	£0.45	ZTX107	£0.10
AC137	£0.20	BC158	£0.10	BD115	£0.50	BU105	£1.70	ZTX108	£0.10
AC141	£0.22	BC167	£0.12	BD121	£0.60	BU105/02	£1.95	ZTX109	£0.10
AC141K	£0.30	BC168	£0.12	BD123	£0.65	BU204	£1.70	ZTX300	£0.12
AC176	£0.18	BC169	£0.12	BD124	£0.70	BU205	£1.70	ZTX500	£0.14
AC176K	£0.26	BC169C	£0.12	BD131	£0.38	BU208	£2.40	2N1171	£0.20
AC178	£0.25	BC170	£0.10	BD132	£0.40	BU208/02	£2.95	2N1189	£0.45
AC178	£0.25	BC171	£0.10	BD131/132MP	£0.70	E1222	£0.38	2N1890	£0.45
AC180	£0.20	BC172	£0.10	BD133	£0.65	MJE2955	£0.98	2N1893	£0.30
AC180K	£0.28	BC173	£0.12	BD135	£0.40	MJE3055	£0.60	2N2147	£0.75
AC181	£0.20	BC177	£0.16	BD136	£0.40	MJE3440	£0.52	2N2148	£0.70
AC181K	£0.28	BC178	£0.16	BD140	£0.40	MP8113	£0.52	2N2160	£0.80
AC187	£0.18	BC179	£0.16	BD137	£0.42	MPF102	£0.35	2N2192	£0.38
AC187K	£0.20	BC180	£0.25	BD138	£0.45	MPF104	£0.38	2N2193	£0.38
AC188	£0.18	BC181	£0.25	BD139	£0.54	MPF105	£0.38	2N2194	£0.38
AC188K	£0.20	BC182L	£0.10	BD140	£0.60	MPSA05	£0.30	2N2217	£0.22
AD140	£0.60	BC183	£0.10	BD139/140MP	£1.20	MPSA06	£0.30	2N2218	£0.22
AD142	£0.85	BC183L	£0.10	BD155	£0.60	MPSA55	£0.28	2N2218A	£0.20
AD143	£0.75	BC184	£0.10	BD175	£0.60	MPSA56	£0.28	2N2192A	£0.20
AD149	£0.60	BC184L	£0.10	BD176	£0.60	OC22	£1.50	2N2199A	£0.24
AD161	£0.42	BC207	£0.11	BD177	£0.68	OC23	£1.50	2N2904	£0.18
AD162	£0.42	BC208	£0.11	BD178	£0.68	OC24	£1.35	2N2904A	£0.21
AD161/162MP	£0.85	BC209	£0.12	BD179	£0.68	OC25	£0.60	2N2905	£0.18
AF114	£0.21	BC212	£0.11	BD178/179	£0.75	OC26	£0.60	2N2905A	£0.21
AF115	£0.21	BC213	£0.11	BD201/202MP	£1.70	OC28	£0.80	2N2906	£0.18
AF116	£0.21	BC213L	£0.11	BD203	£0.70	OC29	£0.80	2N2906A	£0.19
AF117	£0.21	BC214	£0.12	BD203	£0.80	OC36	£0.80	2N2907	£0.22
AF118	£0.40	BC214L	£0.12	BF203/204MP	£1.70	OC70	£0.24	2N2926G	£0.09
AF124	£0.30	BC237	£0.16	BDY20	£0.90	OC71	£0.15	2N2926Y	£0.08
AF125	£0.30	BC251	£0.15	BDX77	£0.90	TIC45	£0.35	2N2926B	£0.08
AF126	£0.30	BC251A	£0.16	BF457	£0.37	TIP29A	£0.44	2N2926B	£0.08
AF127	£0.32	BC301	£0.28	BF458	£0.37	TIP29B	£0.52	2N3053	£0.16
AF139	£0.58	BC302	£0.28	BF459	£0.38	TIP29C	£0.62	2N3054	£0.40
AF180	£0.60	BC303	£0.28	BF584	£0.30	TIP30A	£0.50	2N3055	£0.40
AF181	£0.60	BC304	£0.28	BF596	£0.28	TIP30B	£0.50	2N3414	£0.16
AF186	£0.58	BC327	£0.16	BFR39	£0.25	TIP30C	£0.70	2N3415	£0.16
AF239	£0.50	BC328	£0.16	BFR40	£0.25	TIP31A	£0.45	2N3416	£0.29
AL102	£1.20	BC337	£0.15	BFR79	£0.28	TIP31B	£0.47	2N3417	£0.29
AL103	£1.20	BC338	£0.15	BFR80	£0.28	TIP31C	£0.49	2N3615	£0.90
AU110	£1.00	BC440	£0.30	BFX29	£0.25	TIP32A	£0.49	2N3616	£0.90
AU113	£1.00	RC441	£0.30	BFX30	£0.30	TIP32B	£0.51	2N3616	£0.90
BC107A	£0.08	BC460	£0.38	BFX84	£0.23	TIP32C	£0.53	2N3646	£0.09
BC107B	£0.08	BC461	£0.38	BFX85	£0.24	TIP41A	£0.49	2N3702	£0.08
BC107C	£0.08	BC477	£0.20	BFX86	£0.25	TIP41B	£0.51	2N3703	£0.08
BC108A	£0.08	BC478	£0.20	BFX87	£0.22	TIP42A	£0.53	2N3704	£0.07
BC108B	£0.08	BC479	£0.20	BFX88	£0.22	TIP42B	£0.55	2N3705	£0.07
BC108C	£0.08	BC547	£0.12	BFX90	£0.25	TIP42C	£0.57	2N3706	£0.08
		BC548	£0.12	BFY50	£0.14			2N3707	£0.08

74 SERIES TTL ICs

FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.14	7409	£0.15	7441	£0.64	7482	£0.85	7493	£0.40	74122	£0.50
7401	£0.14	7410	£0.14	7442	£0.64	7483	£0.85	7494	£0.88	74123	£0.70
7402	£0.15	7411	£0.23	7443	£0.90	7484	£0.98	7495	£0.75	74141	£0.80
7403	£0.15	7412	£0.23	7446	£0.90	7485	£1.20	7496	£0.80	74154	£1.30
7404	£0.15	7413	£0.27	7447	£0.78	7486	£0.30	74100	£1.00	74180	£1.10
7405	£0.15	7414	£0.58	7448	£0.80	7489	£2.90	74110	£0.50	74181	£2.00
7406	£0.30	7416	£0.28	7475	£0.48	7490	£0.42	74118	£0.90	74190	£1.50
7407	£0.30	7417	£0.28	7480	£0.50	7491	£0.75	74119	£1.85	74198	£2.00
7408	£0.15	7440	£0.15	7481	£0.95	7492	£0.45	74121	£0.30	74199	£1.90

CMOS ICs

Type	Price								
CD4000	£0.20	CD4012	£0.20	CD4022	£0.98	CD4031	£2.20	CD4046	£1.30
CD4001	£0.20	CD4013	£0.52	CD4023	£0.20	CD4035	£1.90	CD4047	£1.10
CD4002	£0.20	CD4015	£0.98	CD4024	£0.80	CD4037	£0.85	CD4049	£0.55
CD4006	£0.98	CD4016	£0.52	CD4025	£0.20	CD4040	£0.95	CD4050	£0.55
CD4007	£0.98	CD4017	£0.98	CD4026	£1.95	CD4041	£0.82	CD4054	£1.20
CD4008	£0.98	CD4018	£1.00	CD4027	£0.60	CD4042	£0.82	CD4055	£1.85
CD4009	£0.58	CD4019	£0.55	CD4028	£0.98	CD4043	£0.98	CD4056	£1.35
CD4010	£0.58	CD4020	£1.10	CD4029	£1.15	CD4044	£0.94	CD4069	£0.40
CD4011	£0.20	CD4021	£0.98	CD4030	£0.55	CD4045	£1.40	CD4070	£0.40

LINEAR ICs

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
CA3011	£1.05	LM320-12V	£1.85	MC1456G	£1.40	UA709C	£0.25	TL414A	£1.95
CA3014	£1.70	LM320-15V	£1.85	MC1466L	£4.50	UA747C	£0.70	TAA550B	£0.35
CA3018	£0.75	LM320-24V	£1.85	MC1469G	£2.95	UA748	£0.79	TAA621A	£2.00
CA3020	£1.70	LM380-14P</							

THE 'NUTS & BOLTS' OF THOSE PROJECTS

TRANSFORMERS

MINIATURE MAINS Primary 240V
with two independent secondary windings

No.	Type	Price
2024	MT280 0-6V, 0-6V RMS	£1.30*
2025	MT150 0-12V, 0-12 VRMS	£1.30*

MINIATURE MAINS Primary 240V

No.	Secondary	Price
2021	6V-0-6V 100mA	90p*
2022	9V-0-9V 100mA	90p*
2023	12V-0-12V 100mA	95p*

1 AMP MAINS Primary 240V

No.	Secondary	Price	P & P
2026	6V-0-6V 1 amp	£2.70*	P & P 30p
2027	9V-0-9V 1 amp	£2.20*	P & P 30p
2028	12V-0-12V 1 amp	£2.60*	P & P 30p
2029	15V-0-15V 1 amp	£2.75*	P & P 30p
2030	30V-0-30V 1 amp	£3.45*	P & P 30p

STANDARD MAINS Primary 240V

Multi-tapped secondary mains transformers available in ½ amp, 1 amp and 2 amp current rating. Secondary taps are 0-19-25-33-40-50V.

Voltages available by use of taps:

4, 7, 8, 10, 14, 15, 17, 19, 25, 31, 33, 40, 50, 25-0-25V.

No.	Rating	Price	P & P
2031	½ amp	£3.42*	P & P 30p
2032	1 amp	£4.40*	P & P 50p
2033	2 amp	£5.45*	P & P 85p

AUDIO LEADS

S127	5 pin DIN plug to 4 phono plugs length 1.5m	£1.30*
S128	5 pin DIN plug to 5 pin DIN socket length 1.5m	£1.05*
S129	5 pin DIN plug to 5 pin DIN plug mirror image length 1.5m	£1.05*
S130	2 pin DIN plug to 2 pin DIN socket length 5m	68p*
S131	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5 length 1.5m	83p*
S132	2 pin DIN plug to 2 pin DIN socket length 10m	98p*
S133	5 pin DIN plug to phono plugs connected to pins 3 & 5 length 1.5m	75p*
S134	5 pin DIN plug to 2 phono sockets connected to pins 3 & 5 length 23cm	68p*
S123	5 pin DIN socket to 2 phono plugs connected to pins 3 & 5 length 23cm	68p*
S136	Coiled stereo headphones extension cord extends to 7m	£1.75*
S124	3 pin DIN plug to 3 pin DIN plug length 1.5m	75p*
S125	5 pin DIN plug to 5 pin DIN plug length 1.5m	75p*
S113	3.5mm Jack to 3.5mm Jack length 1.5m	75p*
S114	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5 length 1.5m	85p*
S115	5 pin DIN plug to 3.5 Jack connected to pins 1 & 4 length 1.5m	85p*

G.P. SWITCHING TRANS.

TO18 SIM. TO 2N706/8

BSY/27/28/95A. All useable devices. No open and shorts. ALSO AVAILABLE IN PNP similar to 2N2906. 8CY 70. 20 for 50p, 50 for £1, 100 for £1.80, 500 for £8, 1,000 for £14.

When ordering please state NPN or PNP.

SIL G.P. DIODES

300mW 40 PIV (min) SUB-MIN FULLY TESTED

Ideal for organ builders

30 for 50p, 100 for £1.50, 500 for £5, 1,000 for £8

L.E.D.s

Type	Size	Order No.	Colour	Price
TIL209	0-125in	1501	RED	12p
TIL211	0-125in	1502	GREEN	25p
TIL213	0-125in	1503	YELLOW	25p
FLV115	0.2in	1504	RED	12p
FLV310	0.2in	1505	GREEN	25p
FLV410	0.2in	1506	YELLOW	25p

2nd Grade L.E.D.s

A pack of 10 standard sizes and colours which fail to perform to their very rigid specification, but which are ideal for experiments.

Order No. 1507

£0.90

L.E.D. CLIPS

Pack of	Size	Order No.	Price
Pack of 5	0-125in	1508/0-125	15p
Pack of 5	0-2in	1508/0-2	13p

NUTS AND BOLTS

BA BOLTS – packs of BA threaded cadmium-plated screws, slotted cheese head.

Supplied in multiples of 100

Type	No.	Price	Type	No.	Price
1in OBA	839	£1.50	1in 4BA	845	£0.51
½in OBA	840	£0.83	½in 4BA	846	£0.38
1in 2BA	842	£0.69	½in 4BA	847	£0.33
½in 2BA	843	£0.54	1in 6BA	848	£0.50
½in 2BA	844	£0.63	½in 6BA	849	£0.30
		½in 6BA	850	£0.33	

BA NUTS – packs of cadmium-plated full nuts in multiples of 100

Type	No.	Price	Type	No.	Price
OBA	855	£0.90	4BA	857	£0.42
2BA	856	£0.60	6BA	858	£0.36

BA WASHERS – flat cadmium-plated plain stamped washers supplied in multiples of 100

Type	No.	Price	Type	No.	Price
OBA	859	£0.20	4BA	861	£0.15
2BA	860	£0.15	6BA	862	£0.12

SOLDER TAGS – hot tinned supplied in multiples of 100

Type	No.	Price	Type	No.	Price
OBA	851	£0.42	4BA	853	£0.30
2BA	852	£0.36	6BA	854	£0.30

CASES

INSTRUMENT CASES. In two sections, vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5½in	2in	£1.40*
156	11in	6in	3in	£1.80*
157	6in	4½in	1½in	£1.25*
158	6in	5½in	2½in	£1.60*

ALUMINIUM BOXES. Made from bright all. folded construction, each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5½in	2½in	1½in	62p*
160	4in	4in	1½in	62p*
161	4in	2½in	1½in	62p*
162	5½in	4in	1½in	64p*
163	4in	2½in	2in	44p*
164	3in	2in	1in	£1.04*
165	7in	5in	2½in	£1.32*
166	8in	6in	3in	86p*
167	6in	4in	2in	86p*

BRIDGE RECTIFIERS

SILICON 1 amp		Order No.	Price
Type		BR 1/50	£0.28
50V RMS		BR 1/100	£0.30
100V RMS		BR 1/200	£0.32
200V RMS		BR 1/400	£0.36

SILICON 2 amp		Order No.	Price
Type		BR 2/50	£0.45
50V RMS		BR 2/100	£0.48
100V RMS		BR 2/200	£0.52
200V RMS		BR 2/400	£0.58
400V RMS		BR 2/1000	£0.68

FUSE HOLDERS AND FUSES

Description	Order No.	Price
20mm x 5mm chassis mounting	506	£0.07*
1½in x ½in chassis mounting	507	£0.12*
1½in car inline type	508	£0.15*
Panel mounting 20mm	509	£0.29
Panel mounting 1½in	510	£0.30

QUICK BLOW 20mm		Type	No.	Price
Type	No.	3A	619	
150mA	611	1A	615	
250mA	612	1.5A	616	
550mA	613	2A	617	
800mA	614	2.5A	618	
		All 5p each		

ANTI-SURGE 20mm		Type	No.	Price
Type	No.	2.5A	628	
100mA	622	1A	625	
250mA	623	2A	626	
500mA	624	1.5A	627	
		All 7p each		

QUICK BLOW 1½in		Type	No.	Price
Type	No.	800mA	634	
250mA	631	500mA	632	
		All 7p each		
Type	No.	Type	No.	Price
1A	635	2-5A	638	4A 641
1.5A	636	3A	639	5A 642
2A	637	All 6p each		

SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0.10*
DPDT standard slide	1974	£0.12*
Toggle switch SPST		
1½in amp 250V a.c.	1975	£0.33*
Toggle switch DPDT		
1 amp 250V a.c.	1976	£0.36*
Rotary on-off mains switch	1977	£0.42*
Push switch – Push to make	1978	£0.13*
Push switch – Push to break	1979	£0.18*

ROCKERSWITCH		Colour	No.	Price
A range of rocker switches SPST – moulded in high insulation. Material available in a choice of colours, ideal for small apparatus		RED	1980	£0.22*
		BLACK	1981	£0.22*
		WHITE	1982	£0.22*
		BLUE	1983	£0.22*
		YELLOW	1984	£0.22*
		LUMINOUS	1985	£0.22*

Description	No.	Price
Miniature SPST toggle, 2 amp 250V a.c.	1958	£0.50*
Miniature SPST toggle, 2 amp 250V a.c.	1959	£0.55*
Miniature DPDT toggle, 2 amp 250V a.c.	1960	£0.65*
Miniature DPDT toggle, centre off, 2 amp 250V a.c.	1961	£0.85*
Push button SPST, 2 amp 250V a.c.	1962	£0.65*
Push button SPST, 2 amp 250V a.c.	1963	£0.68*
Push button DPDT, 2 amp 250V a.c.	1964	£0.80*

MIDGET WAFER SWITCHES

Single-bank wafer type – suitable for switching at 250V a.c. 100mA or 150V d.c. in non-reactive loads make-before-break contacts. These switches have a spindle 0.25in dia. and 30° indexing.

Description	Order No.	Price
1 pole 12 way	1965	£0.48*
2 pole 6 way	1966	£0.48*
3 pole 4 way	1967	£0.48*
4 pole 3 way	1968	£0.48*

MICRO SWITCHES		Order No.	Price
Plastic button gives simple on-off action			
Rating 10 amp 250V a.c.		1969	£0.20
Button gives 1 pole change over action			
Rating 10 amp 250V a.c.		1970	£0.25

DISPLAYS

Type	Order No.	Price
BDL707 0-3in single	1510	£0.80
BDL747 0-6in single	1511	£1.50
BDL727 0-5in double	1512	£1.80

COLD CATHODE ITT 5087 ST

Side viewing indicator tubes. Displays 0-9 and decimal points. Wide viewing angle – operates from 180V with 16kΩ series anode resistors – character height 16.5mm pin connections supplied.

Order No. 1513 Price £0.60

VOLTAGE REGULATORS

Positive Regulators TO220 case		MVR 7815 15V	£1.25
MVR 7805 5V	£1.25	MVR 7824 24V	£1.25
MVR 7812 12V	£1.25		
Negative Regulators TO220 case		MVR 7915 15V	£1.85
MVR 7905 5V	£1.85	MVR 7924 24V	£1.85
MVR 7912 12V	£1.85		

ORDERING

PLEASE WORD YOUR ORDERS EXACTLY AS PRINTED, NOT FORGETTING TO INCLUDE OUR PART NUMBER.

VAT

ADD 12½% TO PRICES MARKED*. ADD 8% TO OTHERS EXCEPTING THOSE MARKED†. THESE ARE ZERO RATED

POSTAGE & PACKING

Add 25p for postage and packing unless otherwise shown. Add extra for airmail. Min. order £1.

Just a selection from our huge stocks

SEE OUR 1977 CATALOGUE

126 pages packed with valuable information

ORDER NOW ONLY 50p


plus 15p p. & p.

BI-PAK

Dept. PE.1, P.O. Box 6, Ware, Herts

COMPONENTS SHOP:
18 BALDOCK STREET, WARE, HERTS.

KITS FOR SYNTHESISERS, SOUND EFFECTS

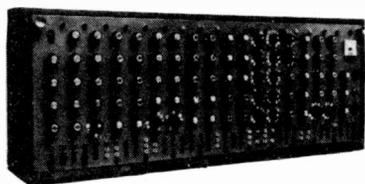

COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

CIRCUIT AND LAYOUT DIAGRAMS are supplied free with all PCBs designed by Phonosonics.

PHOTOCOPIES of the P.E. texts for most of the kits are available—prices in our lists.

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

P.E. MINISONIC Mk. 2 SYNTHESIZER

A portable mains-operated Miniature Sound Synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser the functions offered by this design give it great scope and versatility. Consists of 2 log VCOs, VCF, 2 envelope shapers, 2 voltage controlled amps, keyboard hold and control circuits, HF oscillator and detector, ring modulator, noise generator, output amp and mixer, power supply.

Set of basic component kits £84-25
Set of printed circuit boards £9-71

P.E. SYNTHESIZER (P.E. Feb. 73 to Feb. 74)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. Other circuits in our lists may be used with the Synthesiser to good advantage, notably P.E. Minisonic, Phasing Unit, Wind and Rain, Rhythm Generator, Sound Bender, Voltage Controlled Filter, Guitar Effects Pedal and Overdrive, Fuzz, Tremolo and Wah-Wah units.

The Main Synthesiser: PSU, 2 linear VCOs, 2 ramp generators, 2 input amps, sample hold, noise generator, reverb amp, ring modulator, peak level circuit, envelope shaper, voltage controlled amp. Full details in lists.

Set of basic component kits £83-03
Set of printed circuit boards £13-20

The Synthesiser Keyboard Circuits (can be used without the Main Synthesiser to make an independent musical instrument): 2 logarithmic VCOs, divider, 2 hold circuits, 2 modulation amps, mixer, 2 envelope shapers and additional PSU. Full details in our lists.

Set of basic component kits £48-18
Set of printed circuit boards £7-68

GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches £7-59

Alternative component set with panel mounting switches £4-96

Printed circuit board £1-43

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.

Component set for above functions (excl. SWs) £7-84

Printed circuit board £1-81

Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce "jungle-drum" rhythms.

Component set (incl. PCB) £2-88

PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB) £2-87

PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl. PCB) £4-48

SOPHISTICATED PHASING AND VIBRATO UNIT

A slightly modified version of the circuit published in "Elektron", December 1976, and includes manual and automatic control over the rate of phasing and vibrato.

Component set £17-69

Printed circuit board £2-33

WAH-WAH UNIT (P.E. Apr. 76)

The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller.

Component set (incl. PCB) £3-55

AUTOWAH UNIT (P.E. Mar. 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played.

Component set, PCB, special foot switches £7-27

Component set and PCB, with panel switches £4-83

P.E. JOANNA (P.E. May/Sept. 75)

A five-octave electronic piano that has switchable alternative voicing of Honky-Tonk piano, ordinary piano, harpsichord, or a mixture of any of the three, together with facilities including fast and slow tremolo, loud and soft pedal switching, and sustain pedal switching. The power amplifier typically delivers 24 watts into 8 ohms. The PCBs have been redesigned by ourselves making improved use of the space available.

Main power supply, tone generator, 61 envelope shapers, voicing and pre-amp circuits.

Set of basic component kits for above £75-29

Set of printed circuit boards for above £20-35

Power amplifier £15-97

Printed circuit board for power amp 95p

ELECTRONIC ORGAN

5-octave electronic organ with 5 basic voices that can be used individually or together, 5 pitches (2ft, 4ft, 8ft, 16ft, 32ft), variable attack, tremolo, vibrato, phasing, and variable sustain. Details in our list.

ORGAN CONVERSION KIT

Converts the P.E. Joanna electronic piano to also provide most of the facilities offered by the above electronic organ.

Basic component set and PCB £12-34

SYNTHESIZER TUNING INDICATOR (P.E. July 77)

A simple 4-octave frequency comparator for use with synthesizers and other instruments where the full versatility of the P.E. Tuning Fork is not required.

Component and PCB (but excl. sw.) £7-45

GUITAR FREQUENCY DOUBLER (P.E. Aug. 77)

A modified and extended version of the circuit published. Details in list.

SEE OTHER PAGE FOR KEYBOARDS, AND OUR LISTS FOR OTHER COMPONENTS AND ACCESSORIES STOCKED

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set (incl. PCB) £3-72

GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual slider pot £6-86

Component set using dual rotary pot £6-20

Printed circuit board £1-62

FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) £2-03

TREMOLO UNIT

Based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) £3-64

TREBLE BOOST UNIT (P.E. Apr. 76)

Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable.

Component set (incl. PCB) £2-40

P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic and electronic musical instruments alike.

Main component set (incl. PCB) £15-59

Power supply set (incl. PCB) £7-03

P.E. SYNCHRONOME (P.E. Mar. 76)

An accented-beat electronic metronome, providing duplet, triple and quadruple times with full control over the beat rate. Can also be used as a simple drum-beat rhythm generator, includes power supply.

Component set (incl. loudspeaker) £11-62

Printed circuit board £2-04

TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings. All kits include PCBs

Standard tolerance set of components £2-96

Superior tolerance set of components £3-76

Regulated power supply (will drive 2 sets) £4-89

ENVELOPE SHAPER WITHOUT VCA (P.E. Oct. 75)

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing voltage controlled amplifier.

Component set (incl. PCB) £4-66

ENVELOPE SHAPER WITH VCA (P.E. Apr. 76)

This unit has its own voltage controlled amplifier and has full manual control over attack, decay, sustain and release functions.

Component set (incl. PCB) £6-68

TRANSIENT GENERATOR (P.E. Apr. 77)

An envelope shaper, without VCA, having the usual attack, decay, sustain and release functions, and in addition it also provides a "Repeat Effect" enabling a synthesiser to be programmed to imitate such instruments as a mandolin or banjo.

Component set £4-52

Printed circuit board £1-82

WAVEFORM CONVERTER

Slightly modified from a circuit published in a German edition of "Elektron". Converts a saw-tooth waveform into four different waveforms: sine-wave, mark-space saw-tooth, regular triangle form, and squarewave with an externally variable mark-space ratio.

Component set (incl. PCB but excl. sw's) £8-19

VOLTAGE CONTROLLED FILTER (P.E. Dec. 74)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesizers.

Component set (incl. PCB) (Order as Kit 65-1) £8-22

RING MODULATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesizers.

Component set (incl. PCB) (Order as Kit 59-1) £5-50

NOISE GENERATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesizers.

Component set (incl. PCB) (Order as Kit 60-1) £3-35

SOPHISTICATED POWER SUPPLIES

A wide range of highly stabilised low noise power supply kits is available—details in our lists.

MICROPHONE PRE-AMP (P.E. Apr. 77)

Component set (incl. PCB) £3-78

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows.

Component set (incl. PCB) £3-97

DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

Component set (incl. PCB) £4-58

POST AND HANDLING

U.K. orders—under £15 add 25p plus VAT, over £15 add 50p plus VAT. Keyboards £2-00 plus VAT. Optional insurance for compensation against loss or damage in post, add 35p in addition to above post and handling. Eire, C.I., B.F.P.O., and other countries are subject to Export postage rates.

DON'T FORGET VAT!

Add 12½% (or current rate if changed) to full total of goods, post and handling. (Does not apply to export orders).

EXPORT ORDERS are welcome, though we advise that a current copy of our list should be obtained before ordering as it also shows Export postage rates. All payments must be cash-with-order, in Sterling and preferably by International Money Order or through an English Bank. To obtain list send 40p.

PHONOSONICS · DEPT. PE5N · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

MAIL ORDER AND C.W.O. ONLY
SORRY BUT NO CALLERS PLEASE

AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list Europe—send 20p, other countries—send 40p.



KEYBOARDS AND CONTACTS

Kimber-Alien Keyboards are required for many published circuits, including the P.E. Joanna, P.E. Minisonic, and P.E. Synthesiser. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C. The keys are plastic, spring-loaded and mounted on a robust aluminium frame
3 Octave (37 notes) £25.50. 4 Oct (49 notes) £32.25. 5 Oct (61 notes) £39.75.
Contact Assemblies for use with above keyboards. Single-pole change-over (type SP) as for P.E. Joanna and P.E. Minisonic. Two-pole normally-open make-break (type DP) as for P.E. Synthesiser. Special contact assembly (type APS) having 4 poles, 3 of which are normally-open make-break contacts and the fourth is a change-over contact—this special assembly enables THE SAME KEYBOARD to be used with the P.E. Synthesiser, P.E. Minisonic and the P.E. Joanna simultaneously thus avoiding the cost of more than one keyboard. See our list for other contacts.

Contact	Each	3 Octave Set	4 Octave Set	5 Octave Set
SP	24p	£ 8.88	£11.78	£14.64
2P	27p	£ 9.99	£13.23	£16.47
4PS	53p	£19.61	£25.97	£32.33

PRINTED CIRCUIT BOARDS for use with the above contacts and thus eliminating most of the inter-wiring required, are available. Details in our lists.

MORE NEW KITS!

NEW RHYTHM GENERATOR

Redesigned, improved and extended version of the PE 1974 design and including new automatic rhythm programme selector.

TUNE-PROGRAMMABLE SEQUENCER

(PE Nov. 77) The new music unit currently being published.

FORMANT SYNTHESISER

(Elektron Magazine 1977). Very sophisticated music synthesiser for the advanced constructor and for whom cost is secondary to performance.

GUITAR SUSTAIN UNIT

(PE Oct. 77). Details in lists. Please send S.A.E.

SOUND-TO-LIGHT (P.E. Aurora) (P.E. Apr.-Aug. 71)

Four channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities.

Basic component set (excl. thyristors)	£15.92
Printed circuit board for above	£3.90
Power supply	£5.78
PCB for power supply	£1.79

3-CHANNEL SOUND-TO-LIGHT (P.E. Apr. 76)

A simple but effective sound-to-light controller capable of operating 3 lamps each of approximately 700 watts. Includes power supply, thyristors, and by-pass switches

Component set (incl. PCB)	£11.95
---------------------------	--------

DISCOSTROBE (P.E. Nov. 76)

4-channel light-show controller giving a choice of sequential, random, or full strobe mode of operation

Basic component set	£18.19
Printed circuit board	£3.45

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie-detector, alaphone, cardiophone etc.

Pre-Amp Module Component set (incl. PCB)	£4.22
Basic Output Circuits—combined component set with PCBs, for alaphone, cardiophone, frequency meter and visual feed-back lampdriver circuits	£6.59
Audio Amplifier Module Type PC7	£7.35

SEMI CONDUCTOR TESTER (P.E. Oct. 73)

Essential test equipment for the enterprising home constructor. While stocks last.

Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and PCB	£9.63
Panel meter (500µA)	£5.70

TRANSISTORS

AC128	26p
AC176	26p
BC107	14p
BC108	14p
BC109	14p
BC147	12p
BC148	12p
BC149	12p
BC157	13p
BC158	13p
BC159	13p
BC182L	12p
BC184	12p
BC187	25p
BC204	14p
BC209C	14p
BC212L	15p
BC213	15p
BC478	29p
BCY11	22p
BD131	44p
BD132	54p
BFY50	22p
BFY51	22p
BFY52	24p
BSY95A	22p
MD8001	172p
OC28	60p
OC71	20p
OC72	25p
OC84	25p
ORP12	70p
ZTX107	12p
ZTX108	9p
ZTX501	13p
ZTX503	15p
ZTX531	23p
2N706	13p
2N914	22p
2N1304	22p
2N2219	27p
2N2905	35p
2N2905A	39p
2N2907	22p
2N3053	18p
2N3054	66p
2N3055	48p
2N3702	12p
2N3703	12p
2N3704	12p
2N3819	35p
2N3820	64p
2N3823E	39p
2N4060	12p
2N5245	51p
2N5459	33p
2N5777	45p

INTEGRATED CIRTS.

318	230p
709 T05	40p
709 8-pin DIL	48p
723 T05	105p
741 8-pin DIL	32p
748 T05	63p
748 8-pin DIL	63p
µA7805 TO220	205p
µA7808 TO220	205p
µA7812 TO220	205p
µA7815 TO220	205p
µA7818 TO220	205p
AY-1-0212	650p
AY-1-8721/6	195p
CA3046	90p
MC3340	150p
SG3402N	282p

BARGAIN PARCELS SAVE POUNDS

Huge quantities of electronic components must be cleared as space required. 1000's of capacitors, resistors, transistors. Ex equipment panels etc. covered in valuable components. No time to sort. Must sell by weight 7 lbs — £4.95; 14lbs — £7.95; 28 lbs — £12.00; 56lbs — £20.00; 112 lbs — £30.00.

Handy Packs

4 aluminium boxes 128 x 44 x 38 mm ideal for signal injectors, etc. £1.00
Self fluxing enamelled copper wire 1B & 22 swg on 2 oz reels. 2 for £1.10
100 miniature reed switches ideal for burglar alarms, model railways, etc. £2.20
15 x 2-pole reed relays on board operate at 12 volts £2.45.
6 x 6-pole 12 volt reed relays on board £2.45
High quality computer panels smothered in top grade components: 5 lbs £4.75; 10 lbs £8.95

BARGAIN PACKS

New U.H.F. transistor TV tuners 4 pushbutton type £2.50
Rotary type with slow motion drive £2.50
Aluminium TV coax plugs. 10 for £1.00
Miniature 5K log pots with s/p switch. 4 for £1.
Hardware Packs each containing 100's of items including: BA nuts and bolts, Nylon, Self-tapping, Posidrive, "P" clips, Cable clamps, Fuse holders, Spire nuts etc. £1 per pound. 100 assorted "P" clips £1.
Belling Lee outdoor Triplexers, U.H.F., Band 1, Band 2, 50p each, 3 for £1.

DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS

Includes 150 sq. ins. copper clad f/g board, 1 lb ferric chloride, 1 dolo etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions / only £5.30

REFILL PACKS FOR ABOVE

150 sq. in fibre glass board £2
Dolo pen 90p
1 lb ferric chloride to mil spec £1.25

TV SURPLUS

Brand New IIT C.T.V. Triplers, fit Decca "Bradford" chassis £2.50 each. 5 for £10.
Pye and Philips "GB" C.T.V. panels, various types. All incomplete but invaluable for spares or completing. 6 assorted panels for £7.50.
Thorn B & W T.V. bottom panel "950" series, manufacturers surplus £1.50 each.
Pye 11U contrast controls. 10 for £1.
Thorn tape motors mains £1.20 each.
Pye EHT bases, DY51 etc. 10 for £1.
Ceramic P/C mounting valve bases. For PL509, PL508, etc. 10 for £1.

Semiconductor Bargains

TH3 Thermistors. 10 for £1.
100 new & marked silicon and germanium transistors including BC148, BF194, BC183, etc. £3.95
200 new & marked transistors, including 2N3055, AC128, BFY50, BD131, etc. £6.95
100 mixed diodes IN4148, etc. £1.20
100 mixed diodes including zener, power and bridge types £3.30

40p P & P ON ALL ABOVE ITEMS. SEND CHEQUE OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY, DEPT PE, 20A WADDON ROAD, CROYDON, SURREY.

PHILIPS



NEW!

The latest catalogue from S.S.T. includes even more Philips electronic home assembly kits — mixers, amplifiers, speakers, etc. Plus P.B. Electronics Dec and Blob Boards for circuit proving and construction. Send today to: S.S.T. Distributors (Electronic Components) Ltd., West Road, Tottenham, London, N17 0RN.

free

SEND TODAY!

Please send me, quickly, the new S.S.T. Catalogue.

S.S.T. Distributors is a member of the Philips Group of Companies.

Name


Address

Postcode

PE(A)1/78

PHONOSONICS

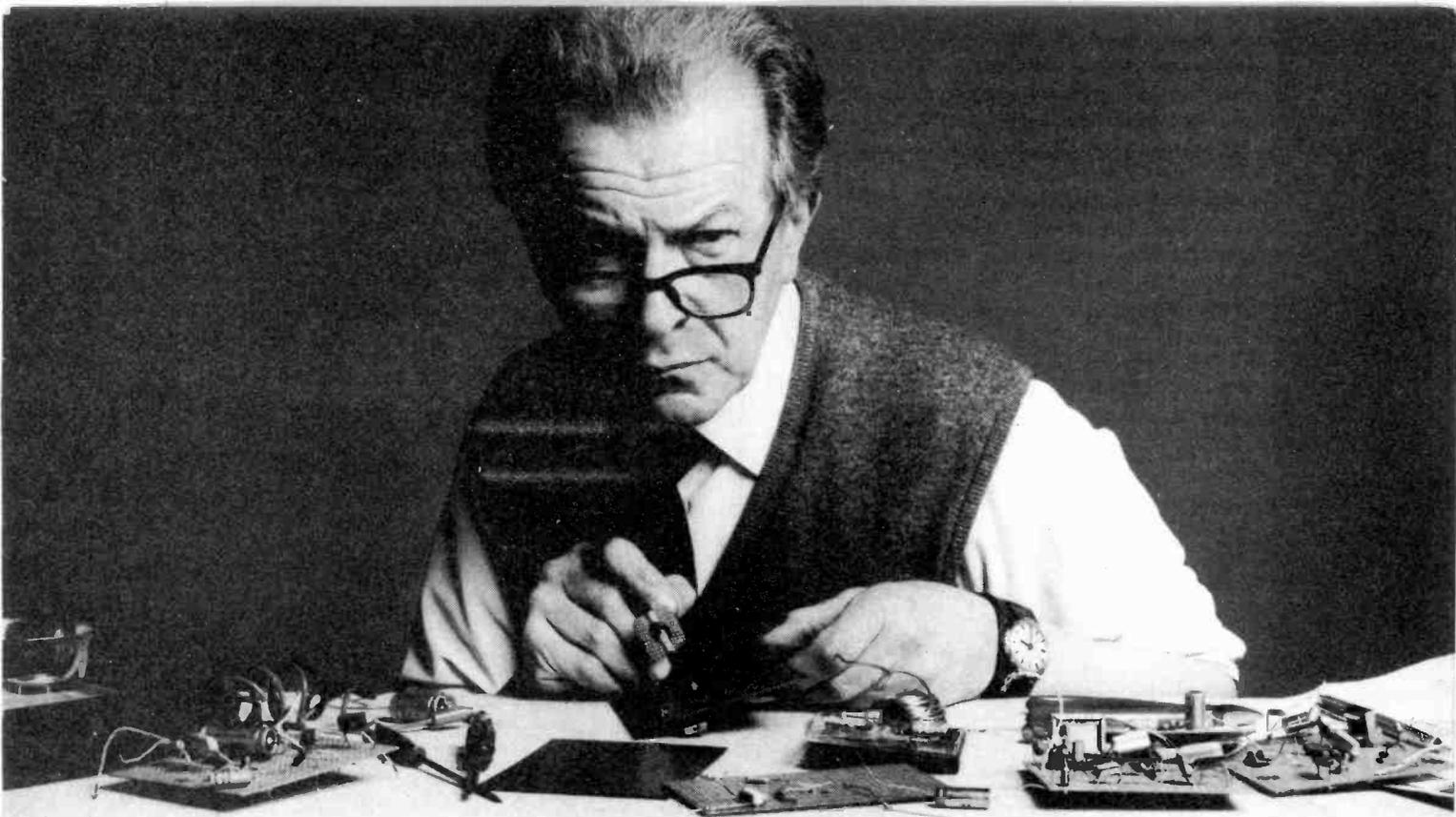PRICES ARE CORRECT AT TIME OF PRESS.
E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.



Still soldering on?

You may be that rare person who gets his circuit designs right first time, everytime.

But it's much more likely that you experiment to see what works, and what doesn't.

In which case you ought to know about Bandridge Decs.

Bandridge Decs enable you to try almost any number of possible circuits, without having to use your soldering iron.

You simply push the wires of your circuit components into the holes in the Dec to make a perfect solderless contact.

Which means that you can use the components over and over again.

And, of course, we don't have to tell you how much time it will save you.

There are four Decs available

to suit every possible circuitry requirement.

From simple discrete work to 2xDIL or 4xTO5 Station work.

And for larger or more complex circuits you can use any number of Decs linked together.

Eventually of course, you'll need that soldering iron to make up the permanent version of your circuit design.

And when you do you'll probably want to use one of the matching Bandridge Blob boards, to make your job that much easier.

But until then we suggest you put your soldering iron aside and get yourself a Bandridge Dec.

Bandridge Decs - Available at all good component stockists, where you see the Bandridge sign.



S-DEC: for use with discrete components only. (70 contacts)

T-DEC: for discrete work, or linear ICs. (208 contacts)

U-DEC 'B': As DEC A but includes two 16 lead IC sockets. (208 contacts)

U-DEC 'A': allows 2xDIL or 4xTO5 Stations but also takes discrete components. (208 contacts)

A free circuit design booklet is supplied with every Dec.

For your nearest stockist contact Bandridge Ltd., 80a Battersea Rise, London SW11 1EH. Tel: 01-228 9227.

SIGNING OFF

AS MANY readers will have noted, Fred Bennett signed off as Editor of P.E. in his editorial last month. Regular readers—and P.E. has many who have been loyal from the first issue—will know that Fred Bennett was the driving force behind this magazine from the word go.

Having personally worked under him for nearly nine years I can safely say that his professionalism, foresight and planning have put the magazine where it is today—the highest selling electronic hobby magazine in Britain—that alone is testimony to his abilities.

Being the man he is, Fred Bennett would give credit to the staff of P.E. for their part in this achievement. With the move to Poole the magazine has also lost other staff. One ex-member who has been “in the thick of it” was the Production Editor, Dave Barrington; a loyal employee since the word go. The magazine will miss them.

SIGNING ON

Having said my piece about departing colleagues—continued, as Fred Bennett left off, in the first person—I suppose the next logical step is to introduce myself before continuing in the normal way.

Perhaps some readers will have seen the name Mike Kenward in past issues of P.E.; in fact I started my

career as a journalist with P.E. in 1968, having previously been employed by the then Ministry of Aviation. Later, after being involved in the launch of *Everyday Electronics*, I moved on to become Assistant Editor of that publication. More recently I have been the Editor of a similar hobbyist publication in Canada and now find myself in the position of taking on P.E. as a result of the move to Poole.

NEW

A new year, a new editor, a new address and some new subjects for your magazine! One topic that we are continually being asked about is fault finding and this month sees the start of an important series which takes a look at ways and means of getting things going again.

Perhaps one of the most difficult tasks of the editorial team of P.E. is answering readers' queries regarding equipment built, or even part built, that has a strange fault or is missing a few parts. Some carefully chosen words may help.

We say “carefully chosen” because, as we would be the first to acknowledge, we, as a team, play an important role in feeding you “the truth, the whole truth and nothing but the truth” and though this is our continual aim we are only human and sometimes things can go awry! It has always been the policy of this magazine to keep readers

fully informed of any corrections, corrigenda, general developments or improvements on all the constructional articles we publish, and that will continue to be our policy.

Having explained our “carefully chosen words” we had better choose them: Our fault finding series is, we feel, excellent material for hobbyist and technician alike, it does however leave some of the more obvious statements unsaid. This is simply because it is a fault finding series rather than a guide to the successful completion of equipment.

We are often asked to provide additional information on components or test and setting up procedures for equipment when, in fact, the information is contained in the article; please read carefully. So often we can only ask constructors to check their unit carefully as we know of no corrections or additions.

We feel this illustrates our point perfectly—it's not easy to diagnose faults if part of your equipment is not there in the first place!

Good fault finding is a peculiar skill, usually practised better by the humble repairman than by the honours-degree-engineer. It is a skill that can be learnt and one that can be improved with practice. A good TV repairman can find the “impossible” in a few minutes; however, even for him, miracles take a little longer!

Mike Kenward.

EDITORIAL

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

Jack Pountney ART EDITOR

Keith Woodruff GENERAL ARTIST

D. J. Gooding TECHNICAL ILLUSTRATOR

R. J. Goodman TECHNICAL ILLUSTRATOR

Editorial Offices:
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: Editorial Poole 71191

ADVERTISEMENTS

ADVERTISEMENT MANAGER

D. W. B. Tilleard

P. J. Mew REPRESENTATIVE

C. R. Brown CLASSIFIED MANAGER

Make Up and Copy Dept.
Phone: 01-261 5000

Advertising Offices:
King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Phone: Advertisements 01-261 5000
Telex: 915748 MAGDIV-G

Back Numbers and Binders

Copies of our June 1977 and subsequent issues are available from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 65p each including Inland/Overseas p & p.

Binders for PE are available from the same address at £2.10 each to UK addresses, £2.70 overseas, including postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Cheques and postal orders should be made payable to IPC Magazines Limited.

Letters

Queries regarding articles published in PE should be addressed to the Editor, at the Editorial Offices, and a stamped, addressed envelope enclosed. We cannot undertake to answer questions regarding other items, nor to answer technical queries over the telephone.



PART 1

GENERATOR

N.A. COOKE

With twelve rhythms that can be superimposed and eight sound generators

THIS Rhythm Generator design compacts eight percussion instruments and a percussionist into a neat professionally styled case measuring some 300 × 130 × 60mm.

The advantage of this unit over many others is that rhythms are selected directly and can be superimposed to create new and musically more interesting patterns. There are 12 basic rhythms and these are as follows:—Tango, Waltz, Shuffle, March, Slow Rock, Swing, Pop Rock, Rumba, Beguine, Cha Cha, Samba and Bossa Nova. By simply selecting two or more, their patterns will be superimposed and a blend of the selected rhythms will result.

CIRCUIT BREAKDOWN

The block diagram (Fig. 1) shows the complete Rhythm Generator. The various circuits can be placed within four main groups:

1. Rhythm pattern generation.
2. Musical instrument simulators.
3. Pre-amplification.
4. Power supply.

To assist in understanding the complete circuit it is best to deal with each of the above groups in turn.

RHYTHM PATTERN GENERATION

The object of this circuit is to provide the instrument simulators with rhythmically pulsed information which in turn is transformed into recognisable percussion sounds.

The heart is the M253AA chip which contains a read only memory matrix pre-programmed with the 12 basic rhythm patterns. All that is required to obtain this information is to provide the chip with a square wave at the clock input, pin 24. By varying the frequency of this square wave the tempo of the rhythm may be controlled.

Fig. 2 shows the circuit diagram of the Rhythm Generator with rhythm selection stop and reset switches and downbeat indicator.

To select a rhythm the desired input must be clamped to the 0V rail (logic 0) with the other inputs tied to 4.7V (logic 1). Change-over switches S1-12 are required for this function. Here the other change over section of the switches is used to select Claves or Snare Drum as appropriate for the particular rhythm.

The square wave for the clock input is generated by a simple astable multivibrator using two CMOS NAND gates together with the associated timing components C2, R2 and VR1 which control the operational frequency. This frequency may be adjusted from approximately 5 to 50Hz

COMPONENTS . . .

Resistors

R1	22k Ω	R31	150k Ω
R2	100k Ω	R32	68k Ω
R3	22k Ω	R33	68k Ω
R4	10k Ω	R34	27k Ω
R5	22k Ω	R35	12k Ω
R6	2.2M Ω	R36	47k Ω
R7	510k Ω	R37	10k Ω
R8	2.7k Ω	R38	470k Ω
R9	220k Ω	R39	390k Ω
R10	150k Ω	R40	390k Ω
R11	68k Ω	R41	390k Ω
R12	68k Ω	R42	10k Ω
R13	27k Ω	R43	22k Ω
R14	12k Ω	R44	1M Ω
R15	47k Ω	R45	100k Ω
R16	10k Ω	R46	470k Ω
R17	150k Ω	R47	1M Ω
R18	68k Ω	R48	22k Ω
R19	68k Ω	R49	2.2k Ω
R20	27k Ω	R50	1M Ω
R21	12k Ω	R51	1M Ω
R22	47k Ω	R52	1M Ω
R23	10k Ω	R53	4.7k Ω
R24	150k Ω	R54	4.7k Ω
R25	68k Ω	R55	22k Ω
R26	68k Ω	R56	10k Ω
R27	27k Ω	R57	390k Ω
R28	12k Ω	R58	10k Ω
R29	47k Ω	R59	2.2k Ω
R30	10k Ω	R60	22k Ω
		R61	33k Ω

All $\frac{1}{4}$ W 5% Carbon Film

Potentiometers

VR1	1M Ω lin	} All 0.1W sub min. horizontal preset
VR2	25k Ω lin	
VR3	10k Ω log	
VR4	470k Ω	
VR5	470k Ω	
VR6	470k Ω	
VR7	470k Ω	
VR8	100k Ω	
VR9	220k Ω	
VR10	10k Ω	

Capacitors

C1	0.01 μ F mylar
C2	0.1 μ F polyrad
C3	0.22 μ F polyrad
C4	0.1 μ F polyrad
C5	0.15 μ F polyrad
C6	0.047 μ F polyrad
C7	0.047 μ F polyrad
C8	0.15 μ F polyrad
C9	0.033 μ F mylar
C10	0.01 μ F mylar
C11	0.01 μ F polyrad
C12	0.033 μ F mylar
C13	0.047 μ F polyester axial
C14	0.015 μ F polyester axial
C15	0.015 μ F polyester axial
C16	0.047 μ F mylar
C17	4.7nF ceramic
C18	1.5nF ceramic
C19	1.5nF ceramic
C20	4.7nF polyrad
C21	0.22 μ F polyrad

C22	0.1 μ F polyrad
C23	0.33 μ F polyrad
C24	0.068 μ F polyrad
C25	0.22 μ F polyrad
C26	0.1 μ F polyrad
C27	0.05 μ F ceramic
C28	4.7nF ceramic
C29	4.7nF ceramic
C30	0.02 μ F mylar
C31	0.1 μ F 16V radial electrolytic
C32	0.1 μ F polyrad
C33	0.22 μ F polyrad
C34	2500 μ F 25V electrolytic
C35	100 μ F 25V electrolytic
C36	470 μ F 16V electrolytic
C37	10 μ F 16V electrolytic
C38	1000 μ F 16V electrolytic
C39	1000 μ F 16V electrolytic
C40	100 μ F 16V electrolytic

All Electrolytics are vertical p.c.b. mounting types
Note: polyrad means polyester radial lead capacitors Mullard C280 Range

Semiconductors

TR1	BC108B	D11	12V 400mW Zener
TR2	BC108B	D12-D15	Bridge Rectifier 50V, 1A, type W0-005
TR3	BC108B		0.15in l.e.d.
TR4	BC108B	D16	M523AA
TR5	BC108B	IC1	CD4011AE
TR6	2N1132	IC2-IC4	741 Op Amp
D1-10	1N4148	IC5	78L12 AWC Regulator
	(10 off)	IC6	+12 Volt Bridge Rectifier 100V 1 amp
		IC7	78L05 AWC Regulator +5V

Miscellaneous

1	8 pin d.i.l. socket
3	14 pin d.i.l. socket
1	24 pin d.i.l. socket
13	D.p.d.t. sub min toggle (S1-S13)
1	S.p.s.t. sub min toggle (S14)
1	Neon indicator (LP1)
T1	12-0-12V 100ma transformer
L1, L2	SC60 100mH min choke
SK1	3.5mm jack socket
SK2	5 pin DIN socket
FS1	20mm panel fuse-holder and 250mA "quick blow" fuse
1	$\frac{1}{4}$ in rubber grommets
1	Earth tag; $\frac{1}{4}$ in fixing lug
10	6BA nuts and bolts
7	6BA clearance spaces $\frac{3}{16}$ in
1	Wire clamp ("P" Clip)
	1 metre 22 s.w.g. tinned copper wire
	2 metres 3 core mains cable
	2 metres single screen cable
35	Veropins 0.1in pitch
2	Printed circuit boards
3	K15 knobs
1	"AWAB" case 12in x 5in x 2 $\frac{1}{2}$ in. 1 $\frac{1}{2}$ metres stranded connecting wire
1	Foot switch press-to-break fitted with 3.5mm jack plug (optional extra)

Note: The inside cover page for Watford Electronics shows i.c.s. M252AA and MC253AA incorrectly priced. These should be 750p and 795p respectively

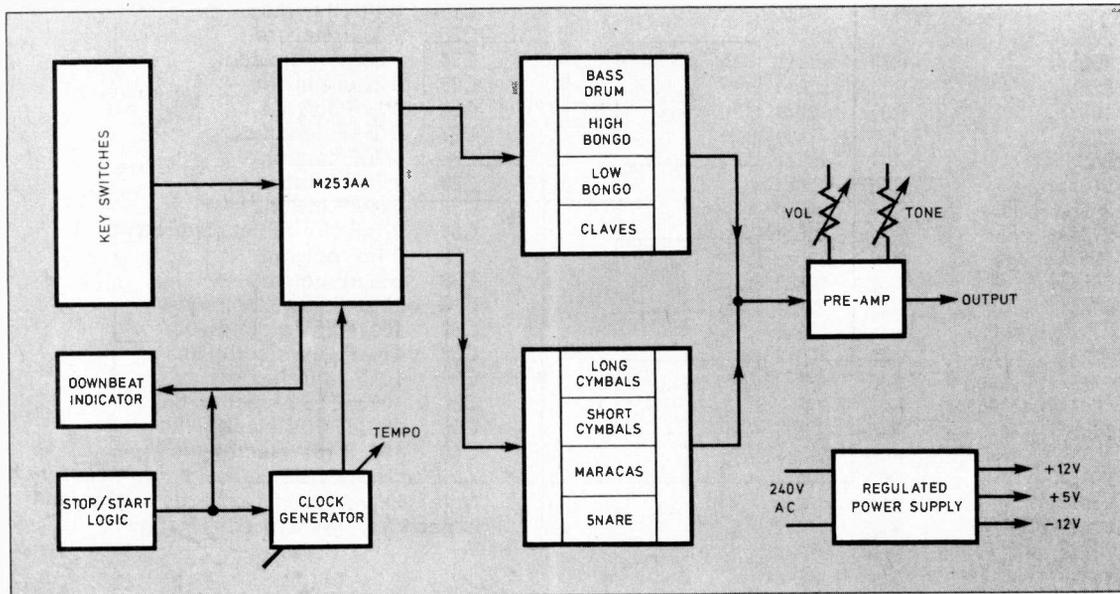


Fig. 1. Block diagram of Rhythm Generator

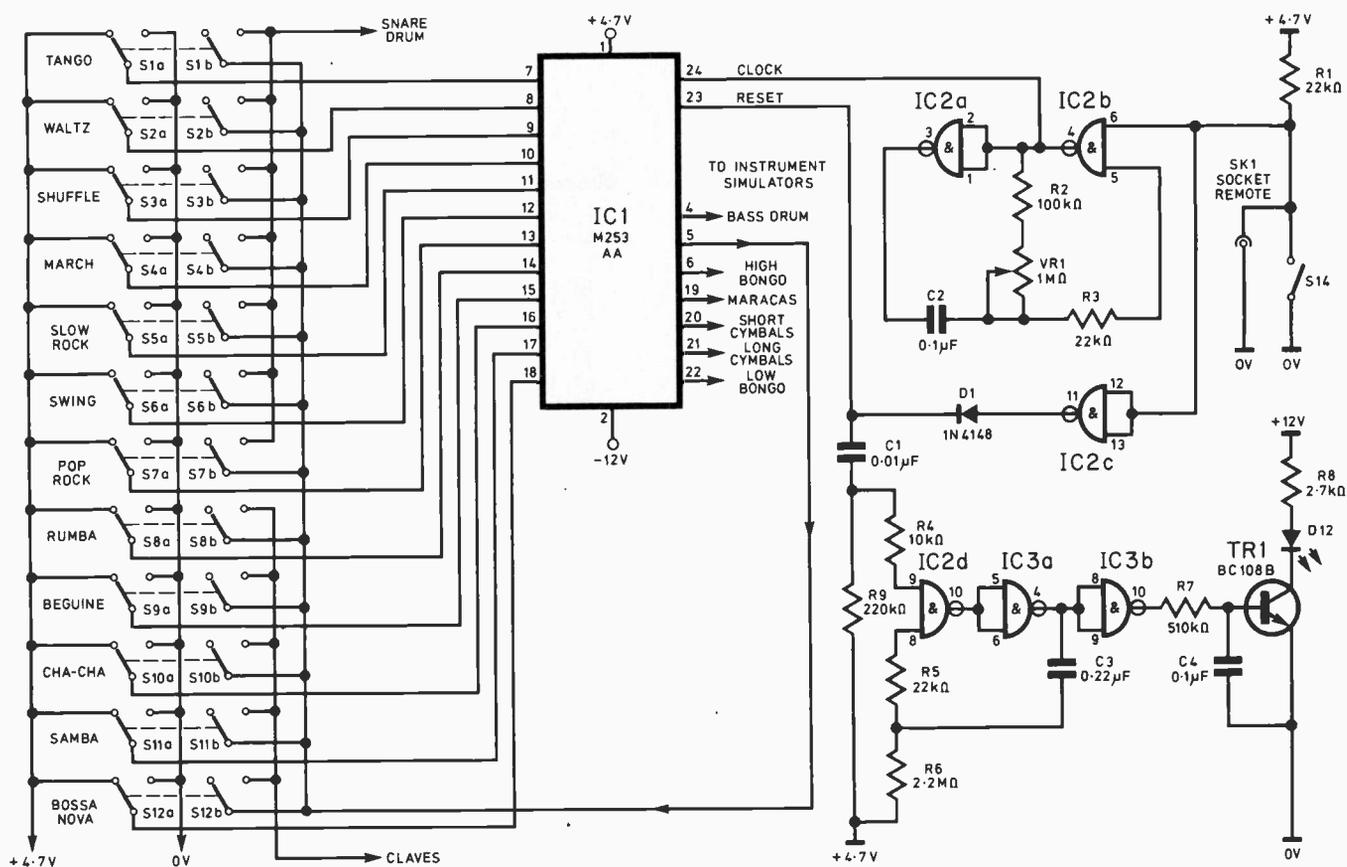


Fig. 2. Rhythm generation circuit

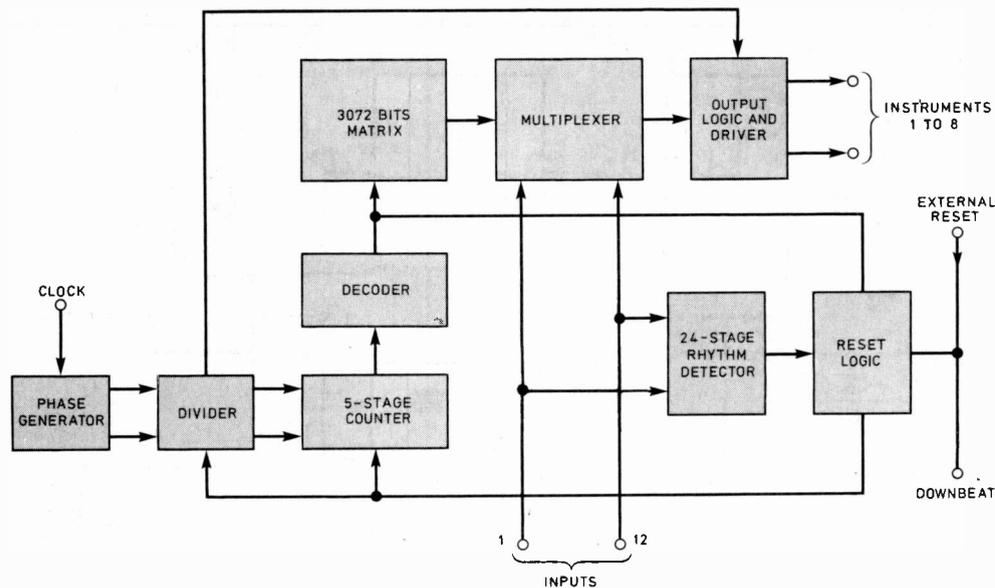


Fig. 3. Block diagram of M253AA

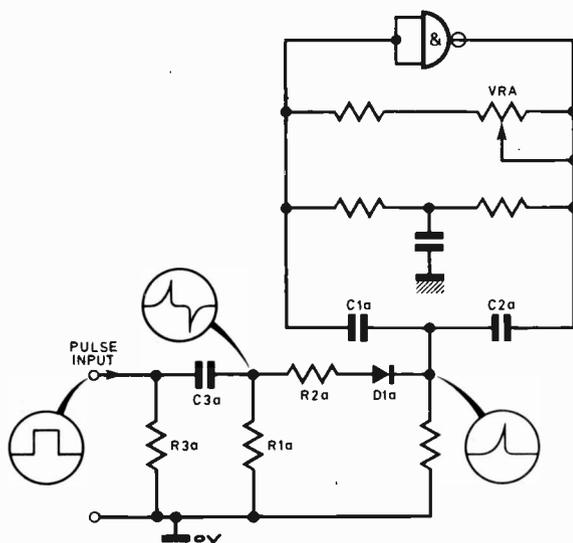


Fig. 4. The basic sinusoidal oscillator

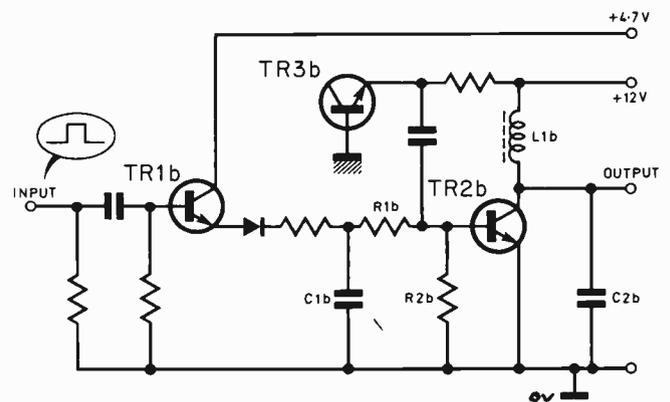


Fig. 5. Fundamental white noise circuit

by the tempo control VR1. The output of the clock generator is fed to the clock input pin 24 of the M253AA.

The rhythm stop/start switch S14 is connected through a NAND gate, operating as an inverter, to the external reset pin 23. When this switch is closed the clock generator is inhibited with its output remaining at logic 1. A pulse is also supplied via the inverter through the blocking diode D1 to reset the rhythm pattern to the beginning of the bar.

On opening the switch the output of the oscillator will immediately go to logic 0 generating the first command pulse which is the first beat in the bar.

DOWNBEAT START

The rhythm pattern always begins on the downbeat, it

then lights the l.e.d. with successive downbeats until S14 is closed.

A short pulse is present at the external reset/downbeat pin of the M253AA when the internal logic resets at the end of the rhythm pattern. This pulse is of very short duration only about 2 to 3µs which is obviously too short to light the l.e.d. The lamp must also light at the beginning of the beat and not at the end of a bar which is when the downbeat pulse is present.

Two NAND gates together with R5, R6 and C3 operate as a monostable and extend this pulse to some 350ms. The third NAND gate inverts the output of the monostable in order that TR1 is switched on and this lights the l.e.d. during the set state of the monostable.

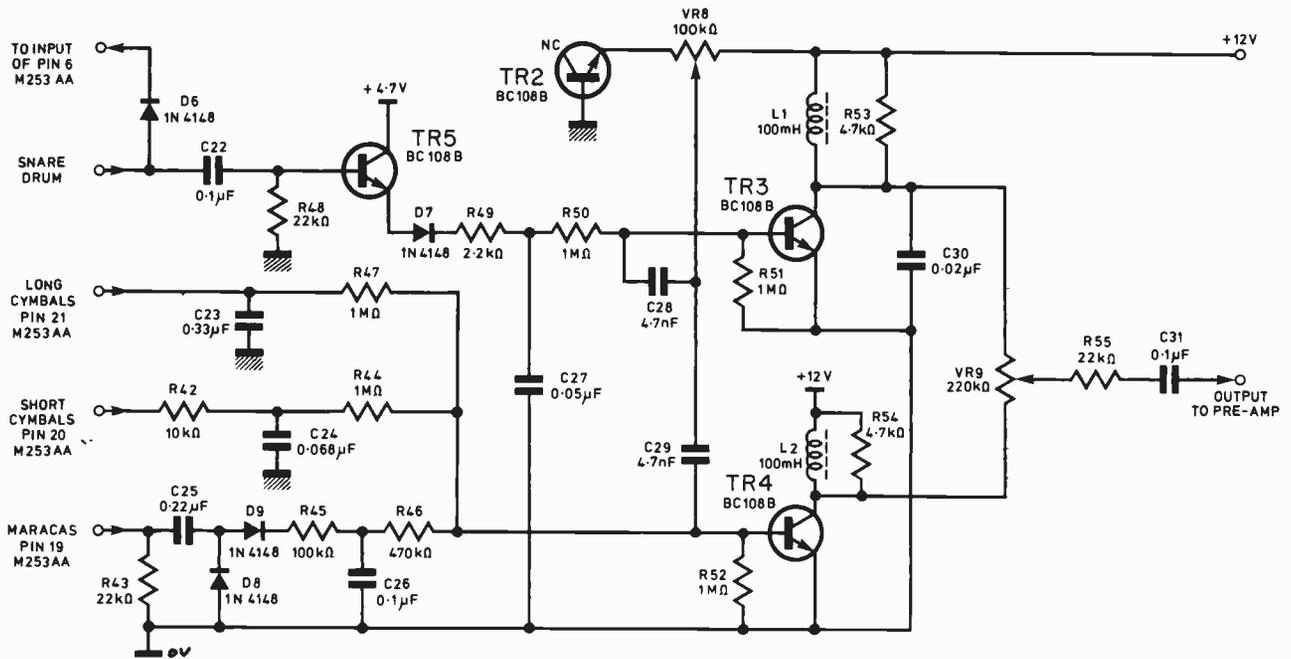


Fig. 6. The four white noise instrument simulators

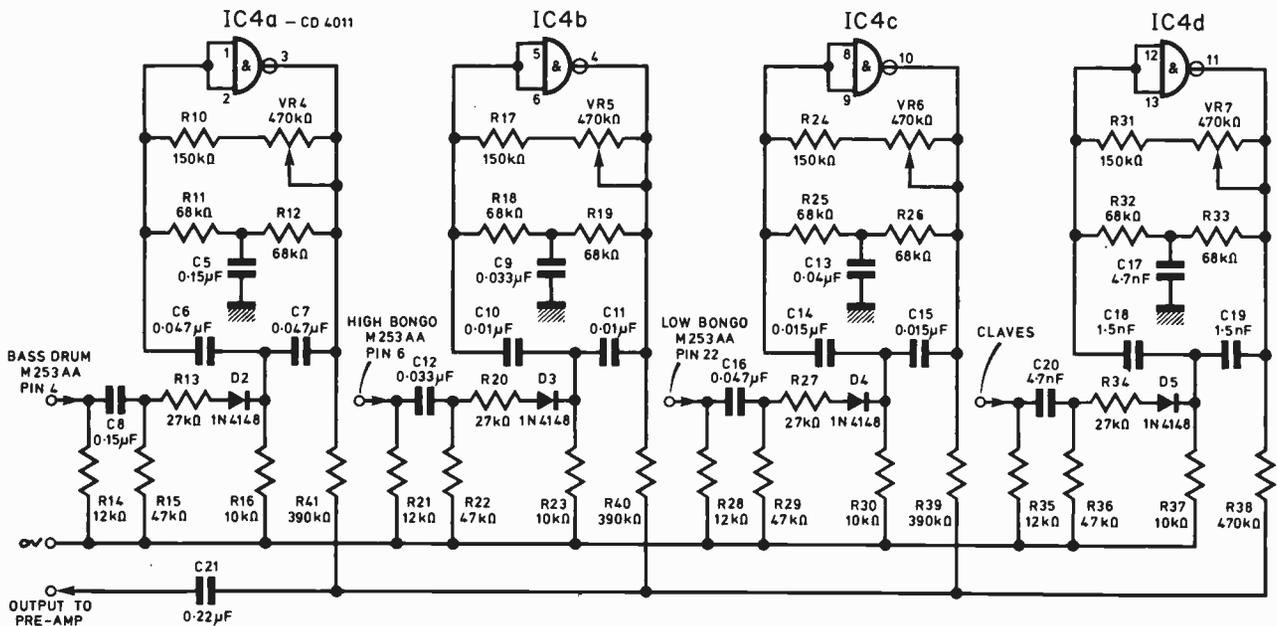


Fig. 7. The four sinusoidal oscillators

THE M253AA IC

Internal operation of the M253AA is shown in Fig. 3. Here the clock input is first divided by two and the output fed to a five-stage counter. The counter resets after 32 pulses for 3/4 time and after 24 pulses for 4/4 time. The counter states are then decoded to drive the ROM (read only memory) matrix which has been pre-programmed with the 12 different rhythm patterns. These, of course, are defined at manufacture but customer options do exist at a price!

The rhythm selection input is decoded to determine the reset point of the counter and to programme the multiplexer to read the memory matrix. Its outputs are then modified to become suitable to drive the eight instrument simulators by means of a driver stage. This driver stage also includes the logic to reset the memory output after each reading in order that successive readings occur on the correct triggering edge of the following beat.

The internal reset pulse is fed to the external pin 23 to provide downbeat indication and to allow external resetting when the generator is stopped.

PERCUSSION VOICES

The Bass Drum, High Bongos, Low Bongos and Claves are created by the use of damped sinusoidal oscillators. The long and short Cymbals and Maracas are simulated by the use of damped filtered white noise.

An example of the simple twin T oscillator used is shown in Fig. 4. The NAND gate is held just below continuous oscillation by the use of VRA.

All four oscillators in this group are identical with the exception of the values of the timing capacitors which set the frequency of oscillation (Fig. 7). The values of the capacitors are chosen to suit the instrument being simulated.

VRA regulates the decay of the oscillation and should be adjusted to give the most realistic effect. The pulsing output of the M253AA is a square wave and this is differentiated by C3a and R1a into two opposite spikes

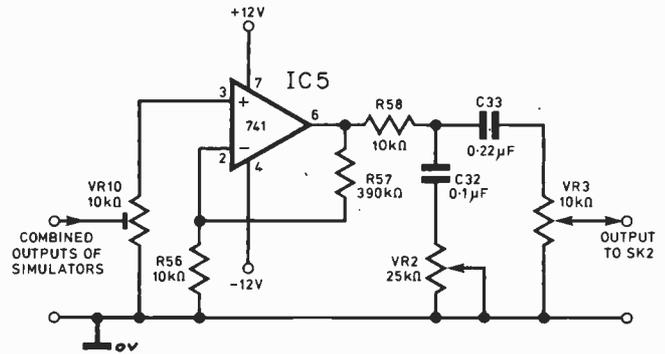


Fig. 8. Pre-amplifier circuit

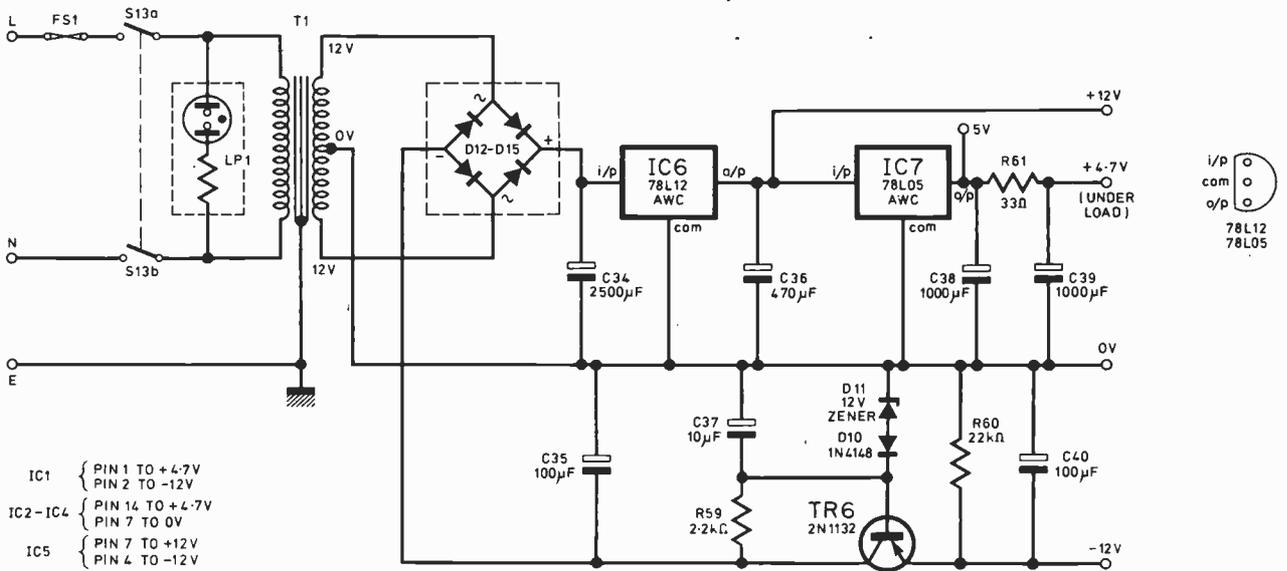


Fig. 9. Circuit of p.s.u.

which are attenuated by R2a and rectified to a single positive spike by D1a. Resistor R3a is necessary to tie the input to earth when no pulse is present as the outputs of the M253AA are open drain types.

Fig. 5 shows the basic circuit of the white noise generators. Transistor TR1b turns on during a command pulse from the M253AA. This charges capacitor C1b which then discharges through R1b to the base of transistor TR2b.

White noise is produced by the reverse biased Zener effect of TR3b which is selectively filtered by C2b and L1b. The level of the white noise at the output of the transistor follows the decaying voltage at the base until the potential across C1b has fallen to a level which causes the transistor to switch off.

The metallic timbre of the Snare Drum is produced on a real instrument by a set of steel springs—the snares which run across the diameter of the underside of the drum. It is the snares vibrating against the skin of the drum that give it its characteristic sound.

This sound is recreated in this unit by combining filtered white noise with the damped oscillation of the High Bongo. The two separate simulators are combined via a diode which prevents the Snare Drum from sounding when the High Bongo is activated.

The Maracas simulator is unusual in that it is the only


instrument in which the sound increases gradually and then decreases. This effect is produced by means of the integrator/differentiator circuit C25, D8, D9, R45, R46 and C26 (Fig. 6).

PRE-AMPLIFICATION AND P.S.U.

Fig. 8 shows the circuit of the pre-amplifier. All eight instruments are combined by means of a resistor, capacitor network. This composite signal is applied through a potential divider VR10 to the non-inverting input of a 741. Feedback resistors R57 and R58 set the gain and a simple high cut filter, adjusted by means of VR2, acts as a tone control. The output to the external amplifier may be varied by the potentiometer VR3.

Fig. 9 shows the complete power supply unit. A 12-0-12V miniature transformer is used, its output being rectified by the bridge rectifier D12-15. The centre tap is at 0 volts providing a dual supply. Three regulators, two of which are cascaded, are used to provide the output voltages of +12, +5 and -12 volts. The supplies must be stable and ripple free to prevent spontaneous oscillation from the sensitive instrument simulators. To prevent an earth loop, which might cause hum, the case and transformer are earthed to the mains supply and the 0V circuit line is left floating.

Next month: Construction and setting up.

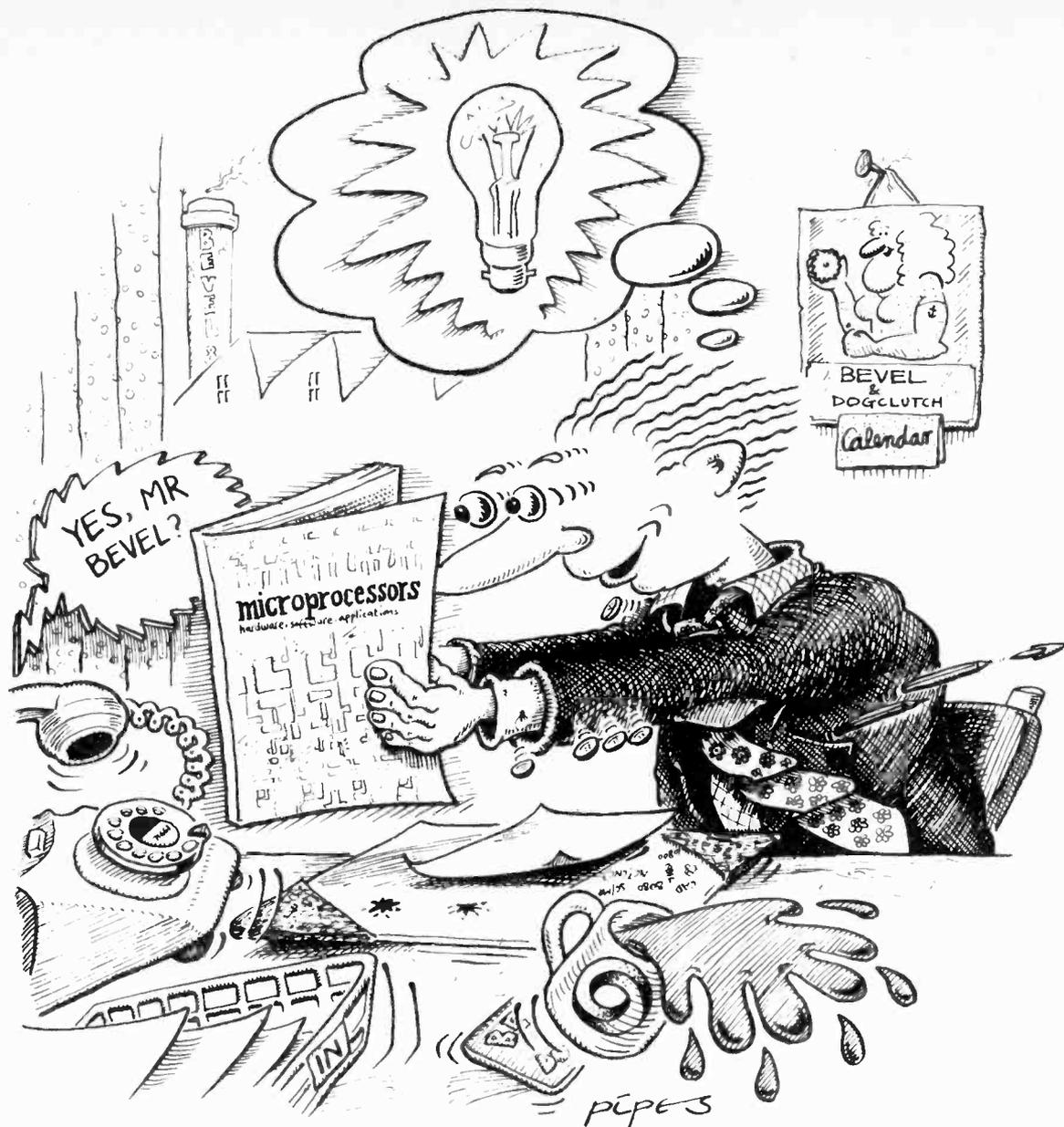

can we inspire you?

Microprocessor technology is changing the face of the electronic and computer industry, allowing existing products to be more effective and revealing new application areas in industry and the home.

MICROPROCESSORS is a new bimonthly technical journal covering the hardware, software and applications of microprocessors and microcomputers.

For further details please complete and return the coupon.

Annual subscription (six issues) is £23 UK, £31 overseas.

TO: MICROPROCESSORS,
IPC Science and Technology Press Ltd,
IPC House, 32 High Street, Guildford,
Surrey, GU1 3EW, England.
Telephone: Guildford (0483) 71661

Please send me further details on
MICROPROCESSORS

Name _____

Organization and address _____

Strictly

by K. Lenton-Smith

The British Musical Instrument Trade Fair is held at three London centres simultaneously each year. One of these concentrates on keyboard instruments and, as these interest me primarily, my visit to the Fair mainly consisted of re-exploring the veritable warren of hotel rooms to see what the Electronic Organ Distributors Association (E.O.D.A.) had been hatching over the past year.

AIDE MÉMOIRE

When the programmable calculator started to become commonplace, I wondered how long it would be before certain of its principles were applied to electronic music. The Trade Fair produced one example—the EKO Tivoli Elite Automatic Chord Organ, distributed by John Hornby Skewes of Leeds.

In many respects, this chord organ is conventional, with rhythm unit able to trigger fundamental basses and chords. For the raw beginner finding difficulty in coping with playing both keyboard and chord buttons, the Tivoli Elite provides three memory controls: Program/Play, Reset and Clear.

The sequence of chords is loaded into the memory bank by pressing Major or Minor chord buttons (but not Fundamentals) in the same order that the sheet music suggests, this being a silent operation. Once the sequence has been banked, it can be recalled by use of "Memory Play" control. Each time this control is operated, the next chord is released.

The tiro, thus armed with a memorised chord sequence, can concentrate on reading the right hand part, using "Memory Play" as a master chord button.

SALES

The E.O.D.A. is in business to sell musical instruments and, perhaps surprisingly, the majority of organs are sold to private individuals, rather than groups or clubs. Any demonstrator will confirm that he can sell an instrument if it sounds good in the hands of a prospective purchaser, however inexperienced. Today's instruments are bristling with gadgets to this end and it is difficult to find a "straight" organ on sale anywhere; attempting to buy such an organ inevitably will mean taking a number of non-optional extras.

BAFFLED

Rotating-baffle speaker systems and the name of Leslie are synonymous, their addition on an organ system giving a new and exciting dimension. These cabinets are a difficult proposition for the home-constructor, who usually ends up buying the commercial article.

If considering a purchase, I suggest the Sharma range of speakers is studied. These are manufactured in England despite the Japanese-sounding name (derived from Sharon and Mark, children of the company's owner) and represent very good value.

Two ranges of cabinet are available, for professional and home use, with power outputs ranging between 30W and 300W.

All but the least expensive model in each range is fitted with a treble pressure driver, revolving horns and bass rotor giving tremolo, chorale or straight signals. The technical details are less important than the end result, which is excellent throughout the range.

THE LEADER

The Allen RMI Keyboard Computer has been mentioned previously in this column, but has since been re-designed in some respects. It is neither piano, synthesiser nor organ and contains no oscillators, dividers or filters. It is a musical digital computer and unique in its field.

The present model includes presets for instant changes of contrasting sounds through its stereo system, though a single manual instrument, left and right channel volume pedals allow delicate answering between "Alto Recorder" and "Harpsichord", for example. "Organ" and "Bells" or "Jazz Flute" and "Clavichord" can also be obtained by use of the stereo presets.

This highly expressive instrument has eight foot-controls and, apart from volume, are used for percussion length, sustain, attack/decay, pitch bending, staccato and vibrato. One of the new presets, "Electric Organ", imitates to perfection the drawbars, third harmonic percussion and two-speed doppler speakers of a well known competitor company! All told, this is the perfect keyboard for modern jazz group with money no object.

The Allen organs use digital techniques for tone generation in their instruments. Musical waveshapes, often those of wind-blown pipes, are stored in digital form and can be re-created at any frequency by a high-speed signal processor. Scaling is even across the keyboards and, though complex, the microcircuits are extremely reliable and never need adjustment or tuning. The Digital Theatre Compact organ has its complete generator on a single plug-in board about 25 x 50cm in size.

In addition to the usual tabs round the horseshoe console, most Allen models (including the RMI) have card readers; inserting punched cards will give an endless variety of extra tone colours. The transposer, through five semitones upward and seven downward, provides brilliant key changes without involvement in double flats! This facility might be useful for accompanying singers with a poor sense of pitch.

A feature of the Theatre Compact is the reality of its 16' solo voices, usually a weak point with electronic organs. Pipe organ realism is enhanced by the "Chiff" stoptab. This makes upper harmonic pitch components speak slightly in advance of the fundamental.

Though expensive by most standards owing to the complexity of the digital generator, the Allen organ is the leader in its field both for serious music or the theatre organ enthusiast.

SYNTHESISERS


The small performance keyboard is now commonplace and selling at a price within reach, often being part of an organ's circuitry. A tab found on many organs this year is "Auto Wah" implying that a v.c.f. is included in the tone forming department even if the specification does not include a complete synthesiser.

The complexity of arpeggiators and automatic chord systems seems to have grown over the past year. Used sparingly and with good taste, these can be a definite performance asset. The Yamaha D Series of organs have an interesting "walking bass", where the pedal notes go through a sequence. This is useful for twelve bar blues and, linked to the rhythm unit, can be made to follow any dance pattern.

Electronic vibrato of the "motorphaser" type appears to be popular in certain quarters, giving a good imitation of the run-up and run-down of a mechanical rotor. However, the high-frequency modulation is never as deep as could be wished for and is more characteristic of a v.c.o. modulated phase-shift system according to my experiments with such circuitry.

The E.O.D.A. might like to consider a gimmick for the 1978 show—a straight-forward organ! They may be assured that there is a market for a realistic instrument at a sensible price, as there are plenty of musicians who can already read fluently and are prepared to take up organ-playing as a new venture.

ANYONE who has experienced the discovery of a flat car battery, particularly at the *wrong* end of a journey in the pouring rain, will appreciate the value of being able to watch the battery voltage. Since most modern cars do not have a voltmeter fitted as standard, it was decided to "dream up" a small indicator unit. The circuit arrived at gives the tri-state indication of HIGH, NORMAL, and LOW voltage condition; the two presets providing a wide range of possible settings.

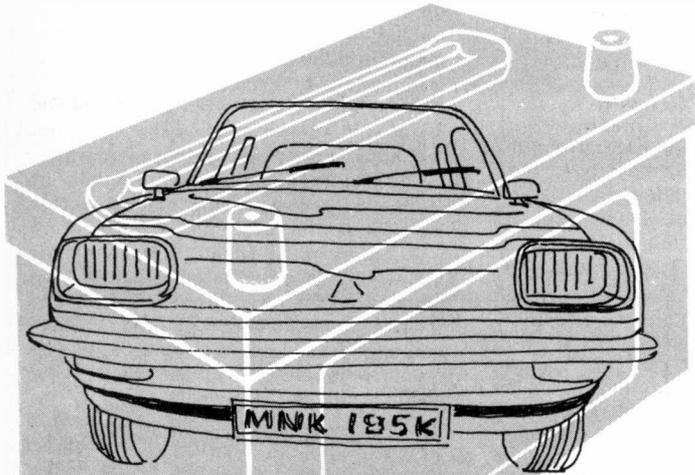

BATTERY CONDITION INDICATOR

P. SCARGILL

PRINCIPLE OF OPERATION

The circuit works by comparing a stable reference voltage level to a fixed ratio of the battery's actual supply level. The reference chosen was about half the theoretical battery voltage, which for most modern cars will be 6V. Zener diodes of around this value do not create too much trouble with temperature variations, although in the final analysis the Zener voltage will not be entirely critical anyway.

As the battery voltage fluctuates due to loading, charging, and its general state of health, it will be compared to the relatively stable reference voltage, and the difference between the two levels magnified by the comparator to drive the l.e.d.s. These will not indicate by how much the reference voltage has been exceeded or fallen short of, only that one of the preset limits either side of it has been crossed over. Crossing the upper limit will indicate overcharging, and crossing the lower limit will indicate undercharging or overloading.

CIRCUIT DESCRIPTION

Referring to Fig. 1, the reference voltage is generated by R4 and D1, and is fed to the non-inverting input of IC1; the current through R4 being just under 2.4mA. This is compared to (or amplified with reference to) a fixed proportion of the car battery voltage, the ratio being determined by VR1.

Sensitivity to change is controlled by VR2 and R1. This is simply the gain control of the amplifier, and is used to determine how little voltage difference at the input, is needed to reach the l.e.d. threshold levels after amplification.

COMPONENTS . . .

Resistors

R1 1.5k Ω
R2, R3 330 Ω
R4 2.7k Ω
All 10% $\frac{1}{2}$ W carbon

Potentiometers


VR1 10k Ω lin preset
VR2 4.7M Ω lin preset
All miniature horizontal

Semiconductors

IC1 741 d.i.l.
D1 5.6V 400mW Zener
D2 T1L209 red (or similar)
D3 T1L209 green (or similar)

Miscellaneous

FS1 200mA
Flying fuse holder for FS1
Printed circuit board, etc.

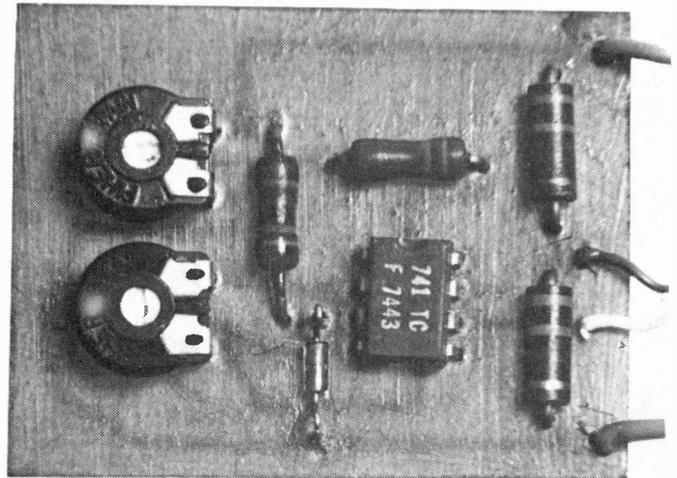

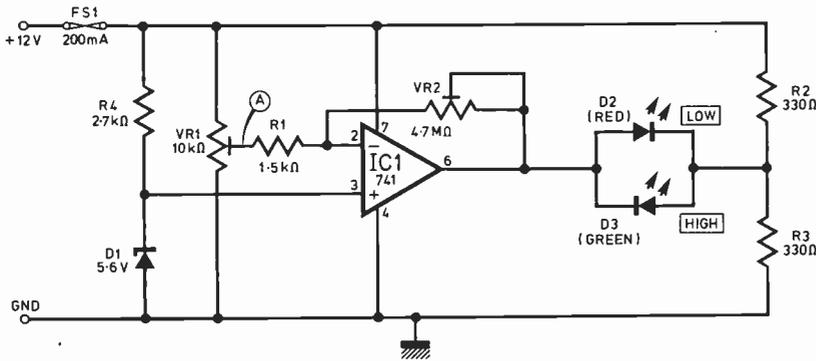


Fig. 1. Circuit diagram of Battery Condition Indicator. (For positive earth vehicles, simply connect the input supply wires the opposite way around, so that the line through FS1 connects to chassis instead)

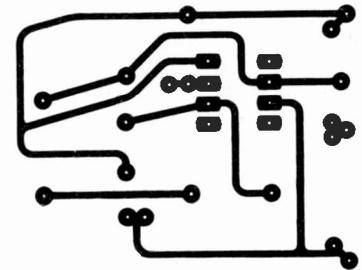


Fig. 2. Printed circuit layout. (Full size)

Since the reference is approximately half the supply voltage, then it follows that the switching mid-point will be roughly correct when VR1 is set halfway. If the battery voltage *increases*, the voltage at point "A" will also increase, and eventually exceed the reference voltage. When this happens, the output of IC1 swings low and illuminates D3. Conversely, if the battery voltage *falls* D2 will light up; and of course the nominal battery voltage will leave both l.e.d.s off. Resistors R2 and R3 limit the current in D3 and D2 respectively, and the maximum current, as a result of these will be around 20mA. Therefore the unit can be wired independently of the ignition switch, since this would take months to drain the average car battery.

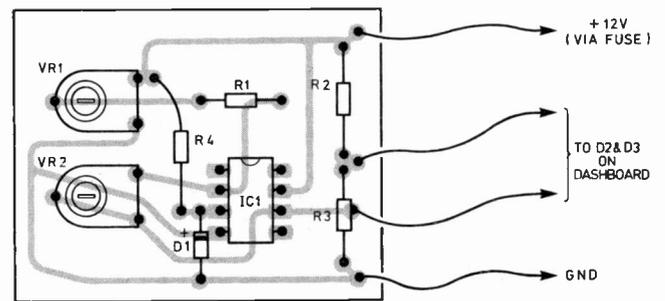


Fig. 3. Component layout for Battery Condition Indicator. A fuse (FS1) should be inserted into the +ve supply wire using a flying lead type fuse holder

CONSTRUCTION

A full size p.c.b. layout is shown in Fig. 2, the component layout of which is shown in Fig. 3. Care should be taken over the correct orientation of IC1 and D1. The l.e.d.s are mounted on the vehicle dashboard in an eye-catching position, and only two leads are necessary for the connection of these. The type of l.e.d.s used is completely a matter of choice, but larger ones will be noticed more readily. It would be a good policy to mount these l.e.d.s away from too much ambient light.

Note that in the photograph the posture of R4 is slightly different to that in Fig. 3. This is of no significance. If the component board is to be mounted behind the fascia panel, there is ample space on the p.c.b. to drill fixing holes.


Tri-state l.e.d.s are now available which will illuminate either red, green, or remain off. These are merely two back to back l.e.d.s in one package, and although one of these is "made for the job", they are considerably more expensive than using two discrete diodes.

The circuit board can be mounted in a box, or simply screwed behind the fascia panel, but it is a good idea to lacquer the component board to protect it against moisture.

SETTING UP

Both presets should be set to midway position, and the unit connected to the car battery *ensuring that the correct polarity is applied*, otherwise IC1 will be damaged.

Assuming that the car battery is at the correct voltage to start with, adjust VR1 until both l.e.d.s are off. If this cannot be achieved, set VR2 for less sensitivity (clockwise) and try again. VR1 should be adjusted to the centre of the "dead zone", and then VR2 re-adjusted to give a dead zone supply variation of $\pm 1V$ either side of nominal (13V) before a l.e.d. lights up. A wider range than this can be adjusted for, if other applications are envisaged. ★

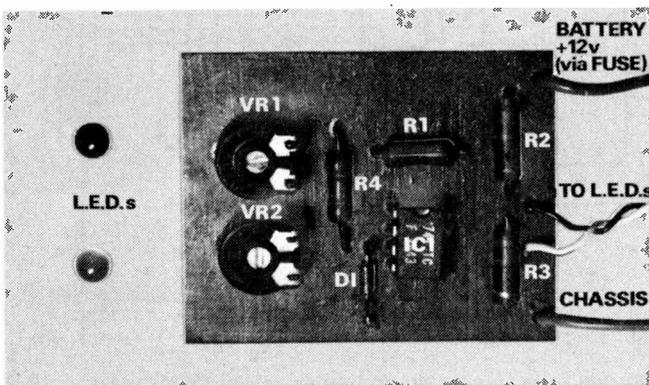



FAULT FINDING PART 1

G. LOVEDAY

A vital new series on the rudiments of faults diagnosis

PROBABLY every experimenter or constructor has experienced the frustration of finding that the circuit he has just built fails to work correctly at switch on, or after a short time in use. Assuming that the circuit has been designed and built correctly, the failure is generally caused by some component fault.

For the newcomer to electronics this can be very discouraging and the causes of failures can seem baffling. However, there are some basic rules to follow in diagnosing faults, and one learns more about electronics in the process.

The skill of rapid fault diagnosis is also very important in Test and Service Departments of the electronic industry, and anyone wishing to enter the profession usually has to complete a suitable course of study at a technical college. For example, the City and Guilds 272 and 222, or one of the new T.E.C. courses. In the final year an examination in fault diagnosis has to be passed.

BASIC REQUIREMENTS

What then are the basic requirements for fault diagnosis? A short list would include the following:

- An understanding of the way in which components work and how they fail.
- A good understanding of how the circuit or instrument operates.
- Skill in recognising fault symptoms.
- A systematic common sense approach to the problem.

When, for example, a faulty instrument is returned to a service department the engineer's first job is to define the fault. To do this he has to check the functional performance of the instrument and then list the symptoms associated with the fault. For a complex instrument he then has to narrow down the search for the faulty component by dividing the unit into functional blocks: power supply, oscillator, amplifier, etc. The various methods used for this are dealt with next month.

Let's first of all consider how to diagnose faults in a single electronic circuit such as the simple oscillator shown in Fig. 1.1. Like most oscillators it is made up of an amplifier, a tuned circuit, and a positive feedback loop. R1 and R2 provide forward bias for the transistor amplifier, L1, C1 and C2 determine the operating frequency and a portion of the output is fed back to the emitter in order to maintain the oscillations. All the components are vital for correct operation and should any one of them fail the circuit would stop producing oscillations.

HOW AND WHY DO COMPONENTS FAIL?

Just like everything else an electronic component has a finite operating life. Stresses are acting continuously on all components. These stresses are of two kinds, operating and environmental. The operating conditions of current, voltage, and power are determined by the design and naturally the life can be extended by operating the component well within its maximum rating. Environmental stresses are those caused by the surrounding conditions.

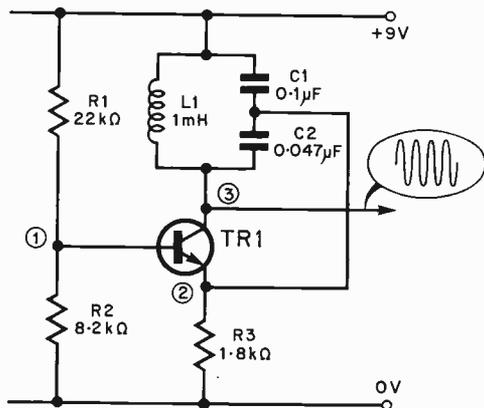


Fig. 1.1. Sine wave oscillator

High humidity, extremes of temperature and mechanical shock and vibration being three that will, if excessive, rapidly reduce the life of a component.

Take for example a resistor. It is subjected to continuous cycles of heating and cooling; this causes it to expand and contract and very slowly its chemical properties change. It becomes brittle and one day it will suddenly fail open circuit. Of course, not all failures are sudden and complete; a component may gradually drift out of specification causing a gradual loss of circuit performance.

Another common cause of component failure is where high voltage pulses or "spikes", generated from switched reactive loads, are transmitted along the mains lines and appear on internal power supply leads. These "spikes" can easily lead to the breakdown of semiconductors.

Table 1 shows the most likely type of failure for different types of components which would appear as follows:

Table 1

Component	Common type of fault
Resistors	high in value or open circuit
Variable resistors (pots)	open circuit or intermittent contact resulting from mechanical wear
Capacitors	short or open circuit
Wound components (inductors and transformers)	open circuit or shorted turns or short circuit coil to frame
Semiconductor devices, diodes, transistors, thyristors, etc.	open or short circuit at any junction

DIAGNOSING FAULTS IN THE CIRCUIT

One component failure usually gives a unique set of symptoms. These being changes in the output signals and changes in d.c. bias levels. Returning to the oscillator, let us imagine that L1 becomes open circuit. A possible fault since the coil is made of relatively thin wire. The signal

output would be zero and the d.c. bias voltages, measured with a standard (20kΩ/volt) multimeter at the three test points with respect to zero volts will be:

Test Point	1	2	3
Voltage	1.2V	0.6V	0.7

(meter readings with L1 open circuit)

Whereas the expected readings should be:

Test Point	1	2	3
Voltage	2.4V	1.8V	+9V

(normal readings)

How can we use the first set of voltages to guide us to the faulty component? When L1 is open circuit an equivalent circuit of the fault conditions is as shown in Fig. 1.2. There is no d.c. path for collector current, so the base emitter junction acts as a forward biased diode passing base current only. The voltage at TP2 will be low because current through R3 has fallen. Given the values and the equivalent circuit for the fault you can readily calculate that the voltage on the emitter will be approximately 0.7V and the voltage on TP1 will be about 0.6V above that at 1.25V.

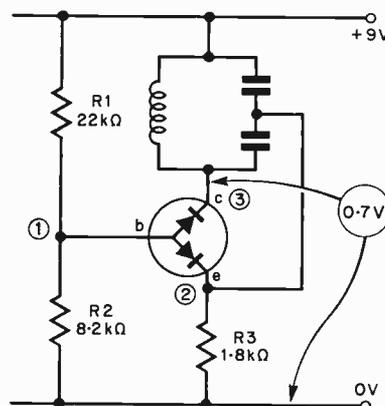


Fig. 1.2. Fault conditions for L1 open circuit

Most readers might assume that TP3 would read zero volts but when a meter is connected from the collector to the 0V rail, the base collector junction acts as a forward biased diode and so a small voltage is indicated.

When you have a set of symptoms for a particular fault try and fit the effects of the component you suspect with these results. Take for example a fault with the following symptoms:

TP	1	2	3
Voltage	0.7V	0.7V	9V

(Fault readings)

Note that the voltage on TP1 is the same as that of TP2 and this indicates a possible short circuit between those points. This would mean a short circuit between the base and emitter of the transistor. If this happens all transistor action ceases, since no emitter current is going to flow across the base into the collector, and the collector voltage should rise. This then is the correct fault, since it fits the symptoms.

Now try your hand at diagnosing the following oscillator fault conditions. The answers are given at the end of the article (Answer (1)). The symptom is no oscillations.

TP	1	2	3
Fault A	0V	0V	+9V
Fault B	2.5V	0V	+9V
Fault C	1.2V	0.6V	+9V
Fault D	2.5V	2V	+9V

FAULTS IN A MORE DIFFICULT CIRCUIT

Many circuits contain d.c. negative feedback loops which tend to complicate diagnosis since a change in bias level at one point usually effects all voltages. A simple series regulator is a good example of this. The circuit shown in Fig. 1.3 is designed to give a relative stable output of 10 volts at 200mA from an un stabilised 15 volt supply. A larger output current can be obtained by mounting TR1 on a heat sink. Remember, if you build the circuit for fault diagnosis, the circuit is not short circuit proof.

Most readers will have a good understanding of the operation but it's worth going over it briefly. TR1, the so called series control transistor, acts like an emitter follower so that an output voltage is provided across the potential divider R3, VR1 and R4.

A portion of the output voltage selected by VR1 appears on the base of TR2, the error amplifier, and this voltage is compared with the reference voltage from the Zener diode. Since the Zener has a fairly constant voltage across it any change in output voltage causes more or less current to flow through TR2. The output of TR2 is used to control the base of the series element TR1. Thus, if the output voltage falls, caused by an increase in load, TR2 conducts less, its collector voltage rises and TR1 is turned on more to correct the original fall in output.

When the circuit is working correctly and supply a 200mA load current the voltages at the test points are:

Test Point	1	2	3	4	normal readings
Voltage	10.7V	6.05V	5.2V	19V	

Let us start by imagining a fault caused by an open circuit Zener diode. We should expect an un stabilised output with higher ripple, and this in fact would happen. Since the emitter voltage of TR2 rises towards the un stabilised input (+15V) the output must also rise because TR2 is cut off. However, the output voltage will not rise much above +12V because the load current requires that TR1 be supplied with base current resulting in a volt drop across R2. If the load is disconnected the output voltage will increase.

The fault conditions are:

Test Point	1	2	3	4	D1 open circuit.
Voltage	13V	12.3V	15.2V	12.3V	

Naturally other faults will cause the output voltage to rise and for stabilisation to be lost. For example R3, VR1 or TR2 base emitter open circuit would do this. The particular symptom that points to D1 open circuit is of course

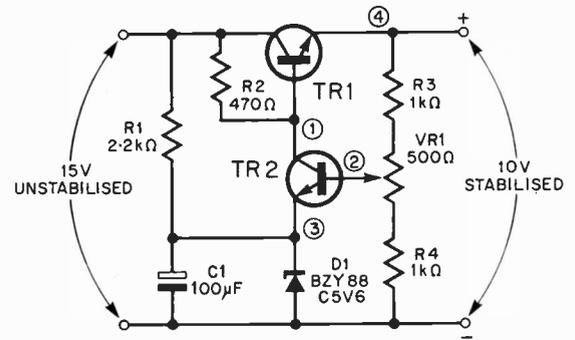


Fig. 1.3. Representative series regulator

that TP3 has risen to +15.3V. What then would be the symptoms for R3 open circuit? (See Answer (2) at end of article.)

Electrolytic capacitor C1 is included to reduce the amount of ripple on the reference voltage. Consider the effect of this becoming short circuit. The emitter of TR2 becomes zero volts, and this causes TR2 to conduct hard. TP2 falls to about 0.7V setting up a voltage of about 1.3V at the output (TP4). This means that TP3 must be at about 2V, that is 0.7V greater than TP4. The output voltage must be about twice V_{be} of TR2 because of the potential divider R3, VR1 and R4.

Voltages for C1 short circuit:

Test Point	1	2	3	4
Voltage	2V	0.7V	0V	1.3V

Finally, try and diagnose faults from these symptoms. Voltages measured with 200mA load. (Answer below)

Test Point	1	2	3	4
Fault A	0V	0V	5.2V	0V
Fault B	14.8V	0V	5.2V	0V
Fault C	7V	5.9V	5.3V	6.2V
Fault D	1.5V	0.67V	5.2V	1.5V
Fault E	13V	7V	5.2V	12.3V

ANSWERS

- (1) **Fault A** R1 open circuit.
Fault B Base-emitter open circuit.
Fault C Collector open circuit.
Fault D R3 open circuit.

TP	1	2	3	4
(2) Voltage	13V	12.3V	5.2V	0V

- (3) **Fault A** R2 open circuit.
Fault B Base/emitter open circuit.
Fault C R4 open circuit.
Fault D TR1 b/e short circuit.
Fault E TR2 b/e open circuit.

Next Month: Fault finding on systems



FRANK W. HYDE

SOYUS/SALYUT

The failure of the Soyus 25-Salyut 6 mission was the eighth time of disappointment for the Soviet space commission. Thirteen launches of spacecraft had been made during the year, so it would appear that there is some special reason for such a high rate of loss. In proportion this failure was the second for 1977 in the Soyus/Salyut programme, and the sixth mission in which procedural errors or the malfunction of equipment was involved during docking or in the rendezvous area.

There is a standard procedure in the Soyus/Salyut docking missions for the Soyus to be automatically guided through the rendezvous stage until it closes within 300 feet of the Salyut space station. At this point control is taken over by the commander who executes the remaining manoeuvres and docking. This is done by manual control of the thrusters. The vehicle had reached this point when the trouble became such that the mission could not be completed normally. It seems that during the manual sequence it was not possible to reach a safe closing-in speed for the Soyus. One thing that seems to have had some place in the failure, was that the final positioning of the spacecraft took somewhat longer than usual. Normally the actual link up would take place at the 17th orbit. In this case it was necessary to go to 18 orbits.

Some direct information on the activities of the cosmonauts has been given by the Observer Group at Kettering School, who have become very expert under the guidance of Mr. Cooper in plotting Soviet space activities. Several conversations between the cosmonauts and the ground station were recorded at

this time. This indicated that there had been an attempt at orbit 17 to initiate the preliminary techniques. However on the 18th revolution Kettering heard none of the usual discussion about the equalising of pressures which takes place after a docking. On revolution 19, Kettering heard a systems check which was normal and suggested that no problems seemed to be involved. American observations revealed that the two spacecraft were close together, and seen as one object up to at least orbit 25.

The inability of the Soyus to dock certainly meant an immediate return to earth of the vehicle and crew. Soyus missions have the facility to operate on batteries for at least two days. This enables the solar sails to be jettisoned to allow for speedier manoeuvring. The return to earth of a vehicle means in any case that the docking section cannot be examined, because it is jettisoned before re-entry.

SOVIET METEOR 2

On June 29, 1977, the Soviet Space Agency launched their first vehicle into a 98 degree sun-synchronous orbit. This is a multispectral equipped vehicle, and two scanners are involved. One is two-band and the other is four-band.

The two-band unit is designated the MSUS, and this instrument operates in the 0.5 to 0.7, and the 0.7 to 1.1 micron bands. The resolution in these bands is 250m, with a swath of 2,000km at a height of 900km. The four-band unit operates on the same band as the USA Landsat spacecraft. The resolution on these bands is 1,000 × 1,600km, with a swath of 2,800km at a height of 900km.

Although this degree of resolution does not approach that of the US spacecraft, there is the advantage that repetitive plots are made every two-three days as against the US nine day intervals. The level of resolution is, however, not sufficiently high to merit computer enhancement. In the Soviet Union the data obtained is being put to use in a number of environmental and economic spheres. These are:

Atmospheric Research. The effect of air pollution was being studied by monitoring the amount of snow melting due to increased absorption of solar energy caused by pollution laden air. Dust storm boundaries were being monitored by the four-band instrument.

Snow Surveys. Snow cover registered over Siberia was to within 5% of the total area by the two-band equipment, and within 15% of the total by the four-band equipment.

Geology. Continental and regional structural units have been monitored, and geotectonic maps have been produced, on a scale of 1:5 million for 50 million kilometres. The extremely wide field of view has been used to define extra large fault lines and massive circular

structures which would have required image mosaics to observe by any other method.

Agriculture. Both the two- and four-band instruments have been used to examine vegetation stress conditions. The grazing grass over an area of 50 million hectares has been assessed to within 100kg.

INTELSTAT 5

This satellite, to be launched in late 1979 will be provided with flight tested instrumentation which has been emphasised as a prerequisite for efficient missions in the future. This design will have an improved capacity over the Intelstats 4A. There will be 12,000 two-way circuits which will double the capacity compared to the 4A design. There will, however, be a number of departures from the previous designs. Intelstat 5 will be the first to use the 14/11GHz (K band) region of the radio frequency spectrum as well as the traditional 6/4GHz (C band) region. The total band width will therefore be 1GHz. The up-link is at the higher frequency and the down link is at the lower frequency. Frequency re-use is by both spacial and polarisation diversity. Three axis stabilisation of the vehicle is installed, and is to be launched by shuttle.

New technology is going to be introduced. Although the tried and tested travelling wave guide systems are being retained, the introduction of graphite fibre reinforced plastics for antennas will be a great advantage. The structures too will benefit from these techniques. In some cases the solid state technology will be fully exploited in order to reduce weight. But since the innovation of new techniques is largely governed by ministries, it may be some time before the field effect transistor replaces the tunnel diode in spite of superior performance.

There are six communications antennas which link the spacecraft with the Earth. The down link operates on 4GHz having an 88 element feed array. Each feed horn produces a small spot beam whose phase and amplitude are controlled by an associated feed network. The individual beams merge to form a composite beam of the proper shape and offset to serve the desired area of the Earth's surface.

There is a 6GHz hemizone receive up-link antenna, a 4GHz global coverage transmit horn, a 6GHz global coverage receive horn, and two identical 14/11GHz spot beam antennas. Each of these spot beams generate uplink and downlink beams.

The spacecraft is to be kept to within ± 0.1 deg. of its assigned longitude, and ± 0.1 deg. of its equatorial plane. Other limits for pitch, roll and yaw are not yet given, but it is expected that they may be in the region of ± 0.2 deg. in roll and pitch, with a limit of ± 0.4 in yaw. The power supply is by solar cell, and cadmium batteries which will operate during eclipse periods. The total power available will be 1,205 watts.

The amazing, automatic Logic Monitor LM-1.

Just clip it over your IC.
It instantly and accurately shows both static and dynamic logic states, on a bright, 16-LED display.

It finds its own power.

It cuts out guesswork, saves time, and eliminates the risk of short-circuits.

LM-1 is suitable for all dual-in-line logic ICs; DTL, TTL, HTL, CMOS; up to 16 pins.

LED on = logic state 1 (high), LED off = logic state 0 (low), and each LED is clearly numbered 1 to 16 in the conventional IC pattern.



Try the LM-1 and you won't know how you ever managed without it!

Brief specification

Input Threshold	2V ± 0.2 volts.
Input Impedance	100,000 Ohms
Input Voltage Range	4 volts minimum 15 volts maximum across any two or more input leads
Maximum Current Drain	200 mA @ 10 volts
Maximum Input Frequency*	10,000 Hz 50% duty cycle
Operating Temperature Range	0°C to 50°C
Weight	3 ounces (85 grams)
Maximum Dimensions	4.0 x 2.0 x 1.8"
	102 x 51 x 45 mm

*LM-1 will respond to signals up to 0.1MHz when the input signal swing exceeds the threshold voltage by more than 0.5 volts.

Applications

Design, breadboarding, testing and checking new logic systems.
Direct real-time monitoring of logic function in operating equipment.
Long-term testing of individual ICs.
Identification of unused elements, to find room for an extra gate, clock etc.
Observing relationships between ICs on different boards of multiple board systems (you need more than one LM-1 to observe simultaneously, of course).
Plus dozens of other uses. You'll find them.

It's Easy to Order

Ring us (01-890 0782) with your Access, Barclaycard or American Express number and your order will be in the post that night. Alternatively, send a cheque, or postal order (don't send credit cards!) and it still only takes a few days. Otherwise ask for our complete catalogue.

ONLY £28.70

Plus 8% VAT, plus post and packaging, total £31.50, including box and instruction manual.





EASY BUILD SPEAKER DIY KITS
Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-simulate enclosures, two EM113" x 8" (approx.) woofers, two tweeters and a pair of matching crossovers. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms, 30 watts peak, each unit. + p & p £5.50 Cabinet size 20" x 11" x 9 1/2" (approx.).

SPEAKERS AVAILABLE WITHOUT CABINETS.
It's the units which we supply with the enclosures illustrated. Size 13" x 8" (approx.) woofer. (EM1), 2 1/2" app. £1.700 per tweeter, and matching crossover components. stereo pair Power handling 15 watts rms, 30 watts peak. + p & p £3.40

COMPACT FOR TDP VALUE These infinite baffle enclosures come to you ready mitted and professionally finished. Each cabinet measures approx. per stereo pair 12" x 9" x 5" deep, and is in wood simulate. £8.50 Complete with two 8" (approx.) speakers for maximum power handling of 7 watts. 8Ω. + p & p £2.20

SPEAKERS Two models - Duo Hb, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/2" (approx.). Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2" app. Duo Hb £17 PER PAIR Duo III £52 PER PAIR p & p £6.50 p & p £7.50

DECCA 20 WATTS STEREO SPEAKER stereo pair This matching loudspeaker system is hand made, kit comprises of two 8" diameter approx. base drive unit, with heavy die cast chassis laminated cones with rolled P.V.C. surrounds, two 3 1/2" diameter approx. domed tweeters complete with crossover networks. 8Ω. £4.00 p & p £20.00

PERSONAL SHOPPERS

- STEREO CASSETTE record/replay fully built P.C. board £275
- AM. FM. TUNER P.C.B. with Mullard L.P. 1186. £9.50 1185, 1181 modules.
- 100K Multiturn Varicap tuning pots, 6 for £1.00
- PAIR STEREO 8 WATT SPEAKERS £12.95 8" bass units with 3 1/2" approx. tweeters Size 16 1/2" x 11" x 8 1/2".
- Plinth & cover BSR or Garrard teak finish £6.00
- DECCA DC1000 Stereo Cassette P.C.B. £2.95 complete with switch oscillator coils and tape-heads
- AM. FM. Stereo Multiplex Car Radio/cassette player in dash fixing Negative earth 5 watts output I.C. Stereo 8 Track to Cassette adaptor converts. £18.95 any 8 track player to cassette player.



20 x 20 WATT STEREO AMPLIFIER £29.90
Superb Viscount IV unit in teak-finished cabinet. Silver fascia with aluminium rotary controls and p & p pushbuttons, red mains indicator and stereo jack £2.50 socket. Function switch for mic. magnetic and crystal pick-ups, tape, tuner, and auxiliary Rear panel features two mains outlets, DIN speaker and input sockets, plus fuse. 20 + 20 watts rms, 40 + 40 watts peak.

30 x 30 WATT AMPLIFIER KIT Specially designed by RT-VC for the experienced constructor, complete in every detail. Same facilities as Viscount IV amplifier. 60 + 60 peak p & p £2.50 £29.00 NOW AVAILABLE fully built and tested. £35.00 Output 30 + 30 watts rms, 60 + 60 peak. p & p £2.50

FREE To cash or cheque personal shoppers A 4 channel Stereo Adaptor to all buyers of the Viscount 20 x 20 £29.90 Available separately £3.95 Amplifier at + £1.00 p & p.

ADD-ON STEREO CASSETTE TAPE DECK KIT Designed for the experienced D.I.Y. man. This kit comprises of a tape transport mechanism, ready built and tested record/replay electronics with twin V.U. meters and level control for mating with mechanism. Specifications: Sensitivity - Mic. 0.85 mV @ 20K OHMS; 0in. 40mV @ 400K OHMS; Output - 300mV RMS per channel @ 1KHz from 2K OHMS source; Cross Talk - $30dB$; Tape Counter - 3 Digit - Resettable; Frequency Response - 40Hz - 8KHz $\pm 6dB$; Deck Motor - 9 Volt DC with electronic speed regulations; Key Functions - Record, Rewind, Mains Transformer £19.95 Fast Forward, Play, Stop & Eject. £2.50 + £1.00 p & p £2.50 Opt. extras: Pair of Dynamic microphones £3.95 + £1.00 p & p.



323 EDGWARE ROAD, LONDON W2 21D HIGH STREET, ACTON W3 6NG ALL PRICES INCLUDE VAT AT 12 1/2%

All enquiries send stamped addressed envelope



45 WATT MONO DISCO AMP £35.00 p & p £2.50 Size approx. 13 1/2" x 5 1/2" x 6 1/2" 45 watts rms, 90 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



70 & 100 WATT MONO DISCO AMP Size approx. 14" x 4" x 10 1/2" Brushed aluminium fascia and rotary controls. Five vertical slide controls - master volume, tape level, mic level, deck level, PLUS INTER-DECK FADE for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control (PFL) lets YOU hear next disc before fading 70 watt peak (PFL) lets YOU hear next disc before fading 140 watt peak in. VU meter monitors output level. p & p £2.00 Output 100 watts RMS 200 watts peak. 100 watt £65

CHASSIS RECORD PLAYER DECKS BSR BD S 95 SERIES illus. £24.95 Belt drive turntable unit, 2 speed, semi automatic p & p £2.55, BSR MP60 TYPE Single play record deck, less cartridge, p & p £2.55 Cartridges to suit above Acos, magnetic stereo £4.95 Ceramic stereo £1.95 BSR automatic record player deck cueing device and stereo ceramic head, p & p £2.55 £9.95

BSR MP 60 type, complete with magnetic cartridge, £29 diamond stylus, and de luxe plinth and cover. p & p £4.50 Home 8 Track cartridge player This unit will match with the Viscount IV 9" x 8" x 3 1/2". p & p £2.50 £16.50

Tourist IV CAR RADIO KIT For the experienced constructor only Output 4 watts into 4 ohms. 12 volts pos or neg (altered internally) £12.50 p & p £1.50

FREE TO PERSONAL SHOPPERS BUYING CAR RADIO KIT worth ELECTROMATE Rear window heater, modern line element, £3.00

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm, Half day Thursday. ACTON: Mail Order only, No callers GOODS NOT DESPATCHED OUTSIDE UK

P.E. JOANNA
ELECTRONIC PIANO
ALL PARTS CAN BE SUPPLIED
Keyboard, Keyswitch, P.C.B.s, Hardware, Semiconductors, Resistors, Capacitors, Cabinets Complete kits or easy stages Send S.A.E. for details
Clef Products
16 Mayfield Road
Bramhall, Stockport, Cheshire SK7 1LY

4-STATION INTERCOM £19.95 + VAT £1.80
Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Sub), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Sub and Sub to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. 99p.

MAINS INTERCOM
NO BATTERIES NO WIRES ONLY £29.99 PER PAIR + VAT £3.75
The modern way of instant 2-way communications. Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range 1 mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom, between office and warehouse, in surgery and in homes. P. & P. 99p.

WEST LONDON DIRECT SUPPLIES (PE1)
169 KENSINGTON HIGH STREET, LONDON W8 6SN
Tel: 01-937 5548.

All prices include V.A.T. Carriage & packing add 25p (U.K.). Add extra for overseas. C.W.O. only. Discounts over £5 less 5%, over £10 less 10%, over £25 less 15%, over £50 less 20%.


BEAD TANTALUM		ELECTROLYTICS					
1	22 33 47 68 1µF 35V all values	1µF	16V	25V	40V	63V	
	11p	1	0.4p	0.5p	0.5p	0.6p	
2	2 3 4 7 6 8µF 35V all values 12p	1	1.5	0.4p	0.5p	0.5p	0.6p
	10µF 25V 22µF 16V both values 13p	2	2	0.4p	0.5p	0.5p	0.6p
	33µF 10V 14p	3	3	0.4p	0.5p	0.5p	0.6p
	47µF 6.3V 68 and 100µF 3V all values 16p	4	4	0.4p	0.5p	0.5p	0.6p
	100µF 16V 20p	6	6	0.5p	0.5p	0.5p	0.7p
	100µF 10V 48p	10	0.5p	0.5p	0.7p	0.9p	
CARBON FILM RESISTORS		22	0.6p	0.7p	0.9p	1.3p	
1/2Watt 1Ω-10MΩ-E12 Series 1p each. 5p for 10 of any one value. 75p for 100 of any one value.		33	0.7p	0.8p	1.0p	1.5p	
I.C. SOCKETS		47	0.8p	1.0p	1.2p	1.9p	
8 pin	11p	100	1.0p	1.3p	1.8p	2.6p	
14 pin	12p	150	1.1p	1.5p	2.0p	2.8p	
16 pin	13p	220	1.2p	1.6p	2.2p	3.2p	
24 pin	48p	330	1.4p	1.8p	2.6p	3.8p	
28 pin	60p	470	1.6p	2.0p	2.9p	4.0p	
		680	1.8p	2.4p	3.5p	4.9p	
		1000	2.0p	2.9p	4.1p	5.6p	
		2200	2.4p	3.8p	6.0p	8.2p	
		4700	3.9p	6.2p	8.5p		
4000mW ZENER DIODES		POLYESTER 100V Radial lead					
1Amp 200V 40p	S.C.R.'s	001	.0012	0015	0018	0022	
4Amp 200V 40p	2 TV-33V	0027	0033	0039	0047	0052	
9p each	4Amp 400V 50p	0068	0082	01	045	012 015	
£3-50 for 50	7Amp 100V 60p	018	022	026	027	033 039	
£6.25 for 100	7Amp 400V 65p	047	.065	056	068	07 082	
	16Amp 100V 75p	1	12	15	075	18 22 27 09	
	150 amp 100V stud rectifier - 1.00 anode	33	10	39	11	47 12	

ASTRA-PAK
92 GODSTONE ROAD
WHYTELEAFE SURREY CR3 0EB

7400	14p	7433	34p	7484	£1	74150	£1.58
7401	14p	7437	25p	7485	58p	74151	64p
7402	14p	7438	25p	7486	30p	74153	64p
7403	14p	7440	15p	7489	£2.45	74154	£1.17
7404	14p	7441	64p	7491	35p	74155	68p
7405	14p	7442	60p	7491	70p	74156	88p
7406	32p	7443	£1.10	7492	44p	74157	68p
7407	32p	7444	£1.10	7493	40p	74159	£2
7408	16p	7445	78p	7494	87p	74160	88p
7409	16p	7446	83p	7495	60p	74161	88p
7410	15p	7447A	74p	7498	65p	74182	88p
7411	20p	7448	68p	74100	94p	74163	88p
7412	21p	7450	15p	74107	30p	74164	£1
7413	28p	7451	15p	74109	50p	74165	£1
7414	80p	7453	15p	74121	25p	74166	£1.23
7416	30p	7454	15p	74122	40p	74170	£1.58
7417	30p	7460	15p	74123	60p	74173	£1.45
7420	15p	7470	30p	74125	50p	74174	99p
7421	35p	7472	25p	74126	50p	74175	74p
7422	20p	7473	30p	74132	75p	74176	99p
7425	20p	7474	30p	74135	68p	74177	99p
7426	25p	7475	30p	74137	94p	74178	£1.38
7427	25p	7475	30p	74141	80p	74180	99p
7428	35p	7480	50p	74145	72p	74181	£1.95
7430	15p	7481	58p	74147	£1.40	74184	£1.45
7432	25p	7483	83p	74148	£1.58	74185A	£1.45

*** NEW * FULLY GUARANTEED COMPONENTS * FULL SPEC SEMICONDUCTORS * QUANTITY DISCOUNTS * SEND S.A.E. FOR COMPLETE LIST ***

74190	£1.38	4023	19p	4069	24p	7905 TO220	
74191	£1.38	4024	75p	4070	28p		£1.95
74192	£1.18	4025	19p	4071	25p	7912 TO220	£1.95
74193	£1.18	4026	£1.85	4072	23p	7915 TO220	
74194	99p	4027	60p	4073	19p		£1.95
74195	95p	4028	85p	4081	19p		
74196	95p	4029	£1.15	4093	80p	OP AMPS	
74197	99p	4030	85p	4098	£1.12	301A-8	35p
74198	£1.80	4031	£2.34	4501	20p	709-14	48p
74199	£1.80	4033	£1.50	4502	95p	741-8	22p
74293	£1.35	4034	£2	4507	60p	741-14	20p
CMOS		4035	£1.28	4508	£2.84	741-T099	48p
4000	15p	4036	£2.40	4511	£1.50	747-14	70p
4001	19p	4037	99p	4515	£2.80	3900	50p
4002	19p	4038	£1	4518	£1.13	LINEAR	
4006	£1	4040	£1	4520	£1.28	TAAS50B	35p
4007	19p	4041	88p	4527	£1.00	TAAB61B	£1.40
4008	98p	4042	80p	4528	£1.05	TBA120S	68p
4010	56p	4043	95p	4536	£3.85	TBA641A	£1.88
4011	19p	4044	99p	4536	£3.85	TBA800	90p
4012	19p	4046	£1.32	4556	85p	TBA810S	£1.10
4013	90p	4047	96p	VOLTAGE REGS		TC2270SQ	£2.20
4014	£1	4048	63p	300	£1.25	TD2020	£3.56
4015	88p	4049	55p	309K-T03	£1.30	380-14	£1
4016	50p	4050	80p	723-14	46p	555-B	38p
4017	96p	4051	92p	7905 TO220		556-14	80p
4018	96p	4052	82p			710-14	32p
4019	52p	4053	95p	7812 TO220		711-14	32p
4020	£1.05	4054	£1.10			1310-14	£1.78
4021	95p	4060	£1.10	7815 TO220		2501B	£2.20
4022	95p	4066	50p			3045-14	45p

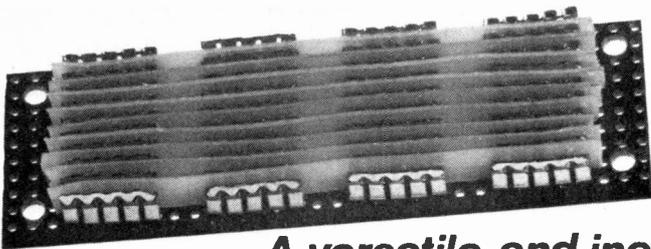

Build it yourself... BREADBOARD SYSTEM

A versatile and inexpensive experimenters breadboard

By D.F. McGINLEY B.Sc.

THIS breadboard system is designed to facilitate developing, or experimenting with circuits without the need for continual soldering and desoldering. It not only saves time, but also reduces the risk of burning components and/or fingers.

The board can accommodate i.c. packages with up to 20 pins, as well as discrete components, but the concept is capable of being expanded to any desired size. It is constructed from Veroboard and i.c. socket strip (200 sockets).

CONSTRUCTION

The Veroboard is cut according to Fig. 1 which gives four groups of 10 electrically separate modes, each mode having sockets. The i.c. socket strip is cut and trimmed as

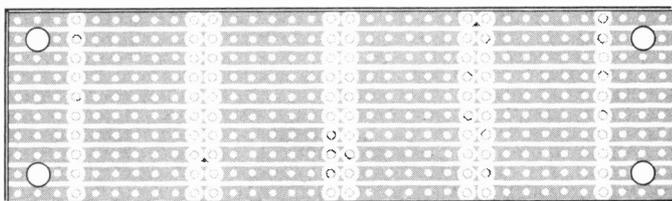


Fig. 1 (above) Veroboard cutting arrangement

Fig. 2 (above right) Modification to the i.c. socket strips


in Fig. 2, and the sharp edges are removed with a file. The socket strips are then inserted in the Veroboard.

SOLDERING

Each group of ten strips is retained in the Veroboard using a spare finger, and one end of each strip is soldered. When all strips are secure, each joint is resoldered while its respective strip is positioned perpendicular to the board. The other end pins of the strips are then soldered. The three inside pins of each strip are not soldered.

INSULATION

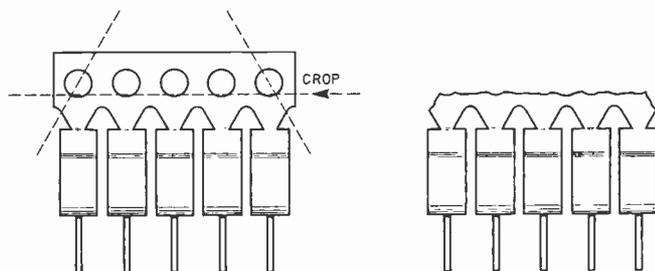Because of the close proximity of the socket strips on the board, it is necessary to provide insulation between




adjacent rows of sockets, to avoid accidental shorts between rows. Any insulating material will be sufficient, but 6mm strips of thin plastics material, 110mm long, cut from an ice cream container proved to be very suitable. These are inserted between the socket strips and also help to maintain the alignment of the four groups of sockets.

MOUNTING

The board is mounted on a small block of wood, being held just clear by spacers on the screws. A piece of hardboard, with several suitably sized holes drilled in it, may be screwed to the block to serve as a panel for holding switches, pots and sockets.

USE

External connections to the board, and jumper leads between strips should be made from single core bell wire. The board as designed is capable of accommodating a wide variety of circuits, and with reasonable care, should give long and trouble free service. Should any of the sockets become deformed after prolonged or over enthusiastic use, it is an easy and inexpensive matter to remove the offending strip, and replace it with a new one. ★

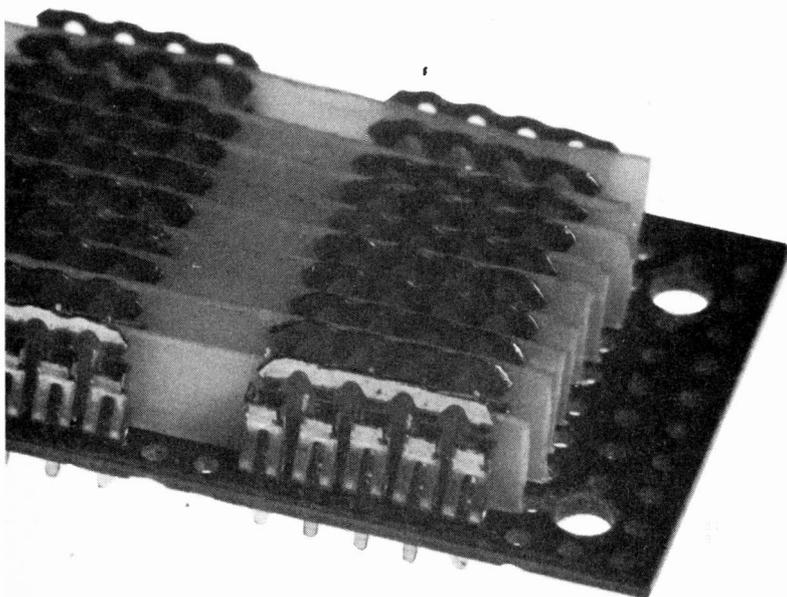

ELECTRONIC DIE

I.J. DILWORTH

Ideal for many board games

THE basic idea for this electronic die developed with the idea of having a hand-held unit that would be small and have a long battery life. Because of the latter it was desirable to display a number from the die by simply switching the unit on by depressing a pushbutton; releasing the push-switch isolates the battery and switches the unit off.

The display, in the H format, consists of seven light emitting diodes gated in such a way to produce the six required numbers.

To obtain a random number from the die a high frequency multivibrator is gated on and off by a much slower read rate oscillator. By making the mark to space ratio of this read rate oscillator large and the frequency of the other multivibrator high, sufficient difference in the number of cycles allowed through into the display each read rate pulse is assured and the randomness in the decoded number does not appear weighted toward any number.

DESCRIPTION

To decode in binary the required number of states, three JK flip-flops are required. In this design DTL 9093 devices are used, two being contained in one 14 pin dual-in-line package.

To fully decode the seven diode matrix of l.e.d.s the minimum gating required is two, two input NAND gates and one three input NAND. Conveniently one can use three, three input NAND gates contained in one package, i.e. SN7410 strapping the inputs on two of the gates.

Reference to Fig. 1 the circuit diagram, will show that the three JK flip-flops are connected in series, the decoding takes place as indicated in Fig. 2 which shows total display.

On binary seven Q2 and Q3 are reset leaving inverse Q1 output high and hence D1 on since this is connected to Q1.



Author's prototype, although any box can be used

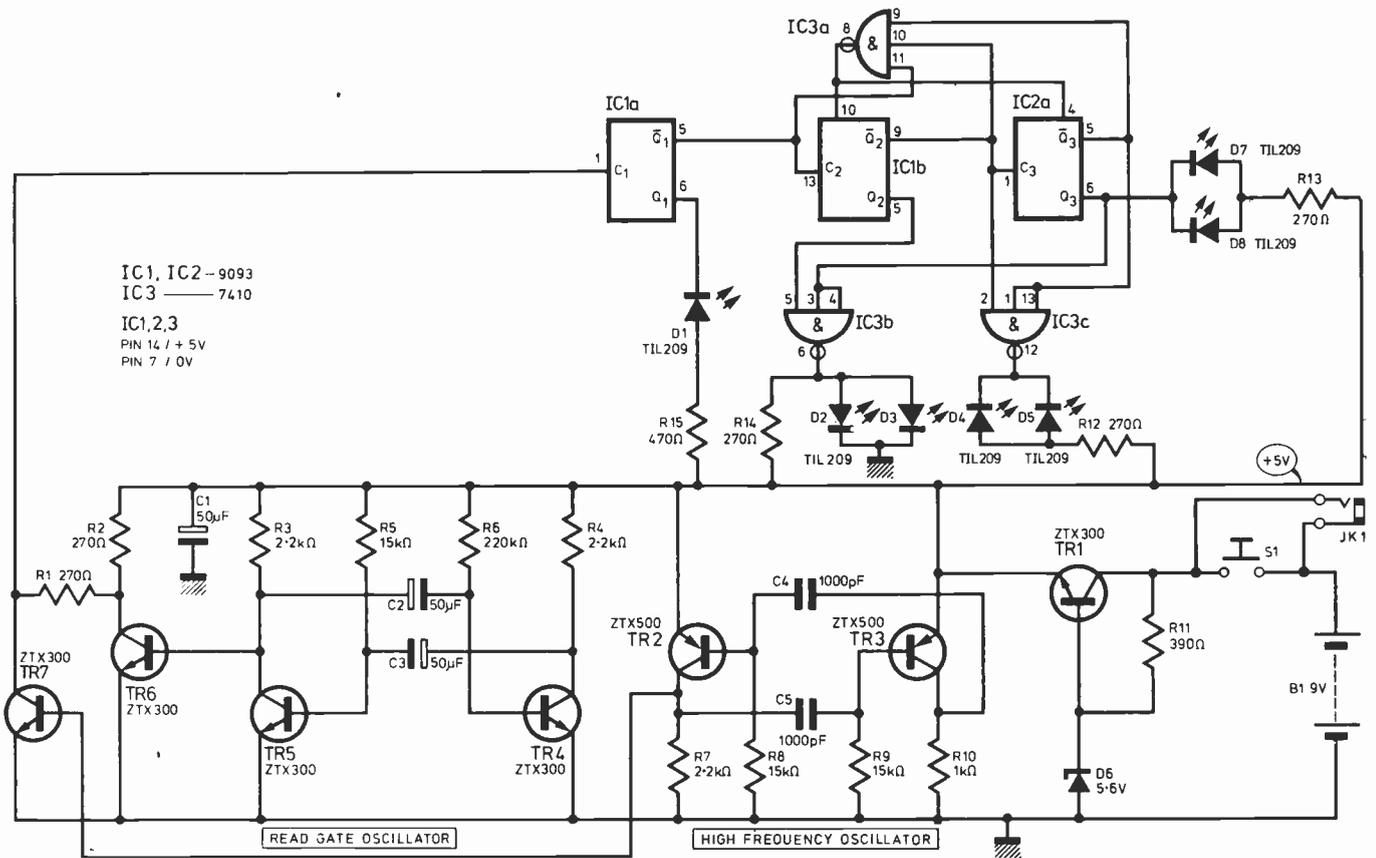


Fig. 1. Circuit of die

No.	LED DISPLAY
1	
2	
3	

No.	LED DISPLAY
4	
5	
6	

Fig. 2. Showing the l.e.d. display for a count up to six

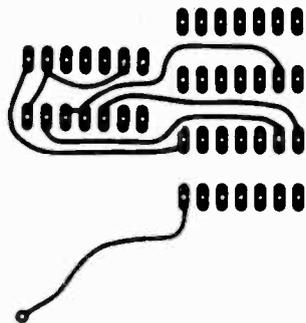


Fig. 3. Upper side pattern of the main p.c.b. shown full size

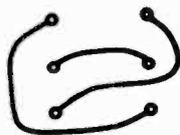


Fig. 5. Upper side pattern of the display board shown full size

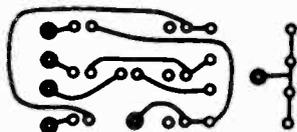


Fig. 6. Lower side pattern of the display board shown full size

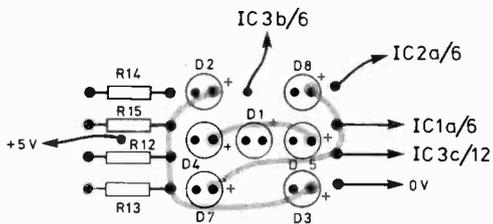


Fig. 7. Component layout of the display p.c.b. (upper side) note that the print pattern shown is of the upper side with underside connections shown with blobs

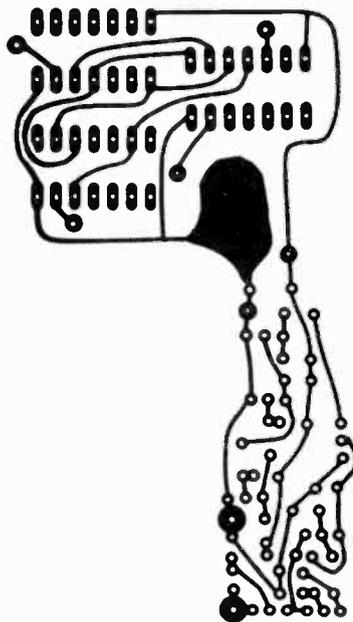


Fig. 4. Lower side pattern of the main board shown full size

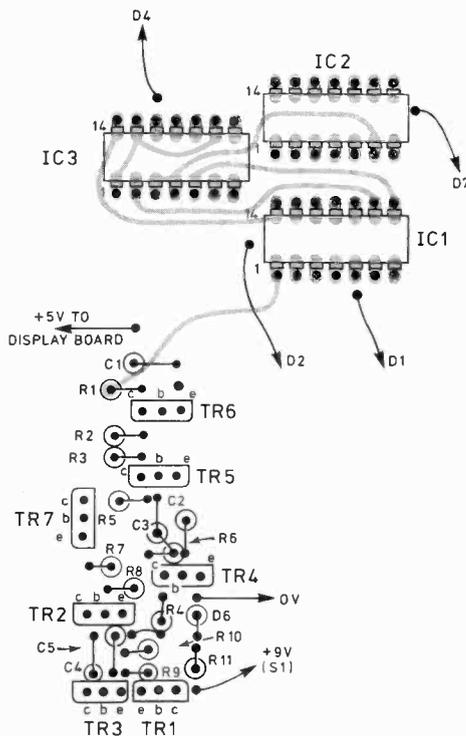


Fig. 8. Component layout of the main board (upper side). Print pattern shown is of the upper side with all underside connections shown with blobs

Table 1

No.	\bar{Q}_1	\bar{Q}_2	\bar{Q}_3
1	1	0	0
2	0	1	0
3	1	1	0
4	0	0	1
5	1	0	1
6	0	1	1
7	1	1	1

Table showing the binary decoding necessary to drive the l.e.d. display

As can be seen gate IC3a resets the two flip-flops when the three input lines correspond to 111. Similarly gate IC3c decodes two l.e.d.s concerned only with displaying six. By considering the various states indicated in Table 1 one can follow how the decoding works.

Transistor TR7 feeds 0-5 volt pulses into IC1a on the first JK flip-flop input. TR3 and TR2 constitute a multivibrator oscillating at approximately 50kHz. This square wave is fed into the base of TR7 continuously but only appears at the output on collector TR7 when TR6 is off. TR6 is gated on and off by the multivibrator TR5, TR4.

TR1 drops the 9 volt battery to 5 volts while providing good regulation until the battery is finished. C1 is included to avoid the 50kHz being modulated with multivibrator pulses from TR4, TR5 so avoiding any possible synchronisation.


CONSTRUCTION

A double sided printed circuit board is shown in Figs. 3 through to 8. Construction whether on the printed circuit board or other means is straightforward but it is very necessary to ensure the l.e.d.s are the correct way round before soldering them in.

THE DIE IN USE

Once S1 is depressed pulses are immediately fed into C₁ because TR6 should be hard off in this initial condition. The first number to be displayed will thus appear almost simultaneously, keeping the button down; the display will be seen to gate again after a display period of approximately 1-2 seconds. This will be recognisable because all the l.e.d.s will glow softly for a very short period, another number will then be displayed; this process continues as long as the die is left on.

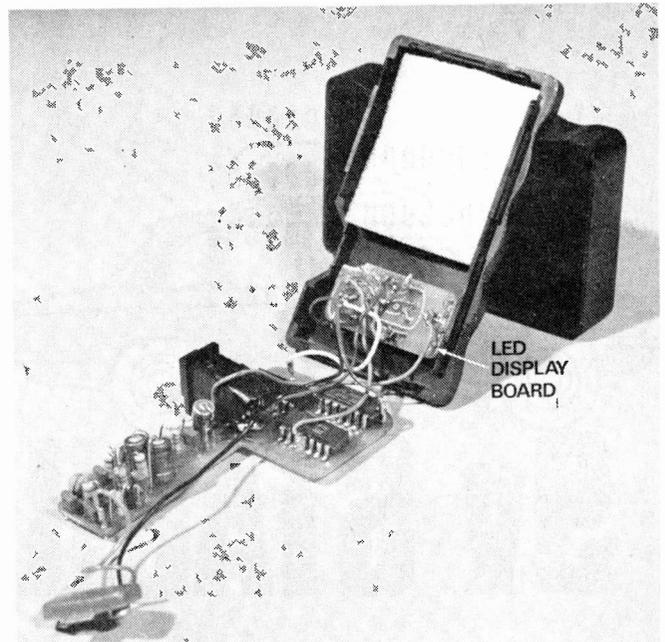Games such as Monopoly require two throws of the die and conveniently by leaving the die on, two numbers are



Interior view of die

COMPONENTS . . .

Resistors

R1, R2, R12, R13, R14	270Ω (5 off)
R11	390Ω
R15	470Ω
R10	1kΩ
R3, R4, R7	2.2kΩ
R5, R8, R9	15kΩ
R6	220kΩ
½ watt (carbon)	

Capacitors

C1, C2, C3	50μF 6 volt electrolytic
C4, C5	0.001μF disc ceramic


Semiconductors

TR2, TR3	ZTX500
TR1, TR4, 5, 6, 7	ZTX300
IC1, IC2	9093 (Bi-Pak)
IC3	SN7410
D1-5, D7-8	TIL209
D6	5.6V 200mW Zener

Miscellaneous

PP3 battery snap and 9V battery	
Pushbutton switch	
Miniature jack socket	

displayed then the die is passed around. Unfortunately in the heat of play distrust does sometimes creep in when getting say two sixes. To avoid this a jack socket with a plug and extension lead complete with pushbutton wired in parallel with S1 facilitates leaving the die in the middle of the board where everyone can see the number thrown, merely passing the pushswitch round when one has had a go. The PP3 battery when used in this way proves economical, consequently a larger battery is not needed making miniaturisation of the whole unit easy. ★

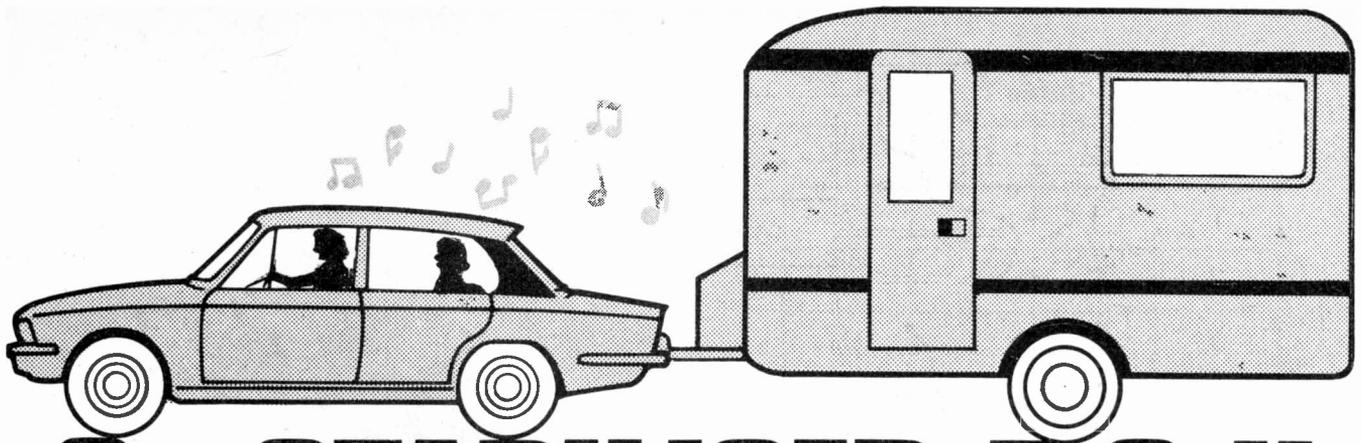

9V STABILISED P.S.U.

C.H. BANTHORPE

ALTHOUGH car radios and tape players are fitted into some cars, many less endowed motorists would like to use their domestic battery-operated radios, radio/recorders or recorders in their cars at times such as during holidays, long journeys or more permanently and would prefer to use the car battery supply instead of the internal costly dry batteries. This article describes a unit which can be used for such a purpose.

Measurements have shown that under normal operating conditions the nominal 12V available from the car battery can vary from 10V to 14.5V, a tremendous variation, and means must therefore be provided to obtain from such a varying input voltage an output voltage which varies very little from the one required, such as 6V, 7.5V or 9V.

It is a highly desirable feature of any circuit but particularly one for constructors that excellent performance is designed in and no adjustments or tailoring of component values is necessary when it is made up. This circuit has this feature.

CURRENT LIMITING

The energy available from a car battery is very considerable indeed and it is not impossible for wiring damage to result from breakdowns or accidental short circuits in equipment connected to a car battery system unless safety measures are taken. This unit includes such measures and its outputs can be short-circuited indefinitely without any ill effects. Under such conditions the output current falls to a low value and remains almost cut off until the short circuit is cleared.

The components used are not critical and similar alternatives should be quite satisfactory. Silicon transistors and diodes should be used, however, because they operate satisfactorily at higher temperatures than germanium types.

THE CIRCUIT

The circuit is shown in Fig. 1 and may first of all be considered with D3 omitted and D2 short-circuited. It will then be seen to consist of a stabilised voltage provided by the Zener diode D1 fed from the un-stabilised input via R1.

To this stabilised voltage point is connected a complementary emitter follower TR1 and TR2, the output being

taken from the emitter of TR1 which is also connected to the collector of TR2. If the circuit was used in this form it would provide a stabilised output voltage of about 0.5V lower than that of the Zener diode, but if the output was overloaded, particularly if it was short-circuited, the transistors would be destroyed.

The inclusion of D2 prevents the output current rising beyond a chosen limit. For a given set of other components the maximum current is determined by the value of R2 and when this current is reached D2 becomes reverse biased and ceases to conduct. Even if the output is short-circuited the output current will not increase beyond the chosen value. However, under such conditions TR2 would have the full input voltage applied across it and as it would also be passing maximum current it would be dissipating maximum wattage. Unless means were provided to dissipate the heat generated by this wattage, TR2 would become overheated and damage result. Much more cooling would therefore have to be provided than necessary

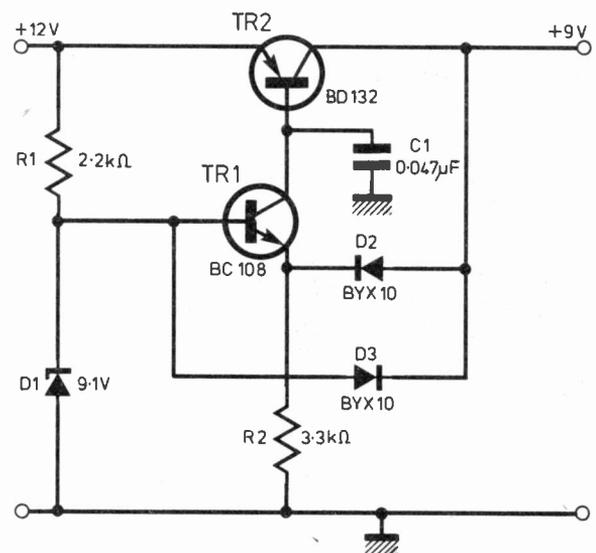


Fig. 1. Circuit of stabilised p.s.u.

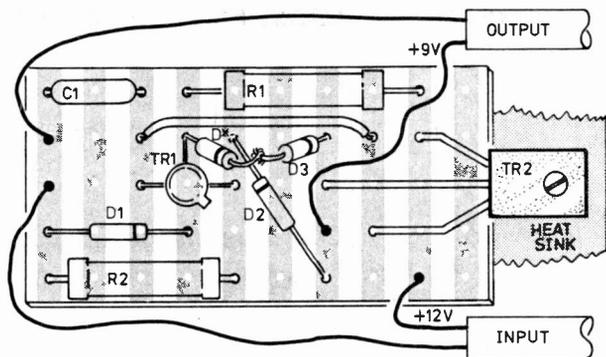


Fig. 2. Veroboard layout and track cutting details

under all conditions except severe overload such as a short circuit.

If D3 is included such a severe overload causes the diode to conduct, the Zener diode is almost shorted out, TR1 and TR2 become almost non-conducting and the short circuit output current is determined mainly by R1 in series with D3 and the output load or short circuit all across the battery circuit. This current is very small so under severe overload conditions the power dissipated in TR2 is negligibly small and cooling arrangements for normal output only need be provided.

CHANGING THE OUTPUT

In this circuit the output voltage is almost exactly that of the Zener diode used and an output of 6V, 7.5V or 9V may be obtained by merely fitting a Zener of the appropriate voltage. No meter is needed for setting-up purposes. The normal current required by the sort of load for which this unit was designed is up to 150mA and a current of at least 250mA has therefore been made available to provide an adequate margin.

There is a possible problem of starting current which in the case of brush type recorder motors is very much higher than the run current. It is this characteristic which makes them attain their running speed very quickly and is why they are so suitable for cassette recorders. However, the starting current can be up to ten times the run current and it is possible that with some recorders the unit as shown will not start up if the recorder is switched on before power is applied to the input of the stabiliser.

COMPONENTS . . .

Resistors

R1 2.2k Ω
R2 3.3k Ω
 $\frac{1}{2}$ W 10% carbon

Capacitor


C1 0.047 μ F polyester film

Semiconductors

TR1 BD132
TR2 BC108
D1 BZY88C9V1 9.1V 400mW Zener
D2, D3 BYX10 (2 off)

Miscellaneous

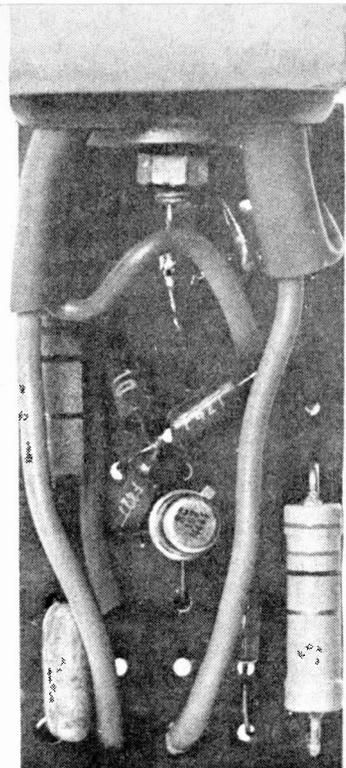Veroboard, heat sink, nuts, bolts and lock washers.



If this is regarded as a drawback it can be overcome by putting another similar diode in series with D3. Although the short circuit current is then somewhat higher than when one diode is used it is very much less than with no diode and no starting problem will arise.

Capacitor C1 is included to eliminate any possibility of the circuit oscillating at high frequencies.

PERFORMANCE

The unit described has been used in a typical family car to operate a cassette recorder and has given no trouble. At an output of 100mA the voltage varies from 9.08V to 9.13V if the input voltage varies from 10V to 15V.

At a steady 12V input the output voltage varies from 9.1V to 9.05V if the output current varies from 100mA to 250mA.

The output current into a short circuit is 10mA.

CONSTRUCTION

The layout of this unit is not critical as indicated in Fig. 2.

It is not always realised just how difficult are the conditions in which the "electrics" in cars operate. Vibration and temperature variations are two of the real environmental hazards. Anything which can vibrate loose or break loose will do so. Leads, components and screws must be very secure, particularly with any sub-assemblies constructed.

The temperature in a car can vary from below freezing to 55°C or above during a year and due regard of this must be taken when choosing components.

Where no convenient connection, such as a cigarette lighter socket, is available it is quite simple to run a separate lead or leads to the car battery or fuse box, but a fuse should be incorporated somewhere in the "live" lead.

The easiest way of doing this is by means of a lead mounted fuse if a lead is taken directly to the battery. If the lead is taken to the fuse box it is best to choose the position, often marked "AUX", which connects to such things as the clock, roof lamp, heater, etc. Failure of wiring will not then put the car out of action. ★

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

GOOD STYLING


Futuristic designs is the aim of a newly formed design and fabrication house, **Viglen Acrylics Ltd.**, who offer a full range of services in the supply of acrylic parts and components. The company's particular skills are in the forming and blending of nitricate shapes to customers' designs or even undertaking the complete design themselves.

A team of artists and designers work closely with the formers and "blowers" to produce new and novel combinations. Thus customers seeking to update existing products can place the project with them even if the original object was made, for example, in wood or metal.

A typical example of their work is shown in our photograph of a hi fi console. This complete system consists of a cassette player/recorder, transcription turntable, amplifier and tuner installed and tested in a plastics pod. The complete system would retail for less than £500.

The console comprises a pair of 750mm acrylic hemispheres, the lower opaque and the upper translucent. Standard colours are white base and bronze lid, but other combinations can be supplied to customers' choice. Provision of cut-outs and apertures, upper deck and internal shelving, and, if required, the angled mounting or operating controls.

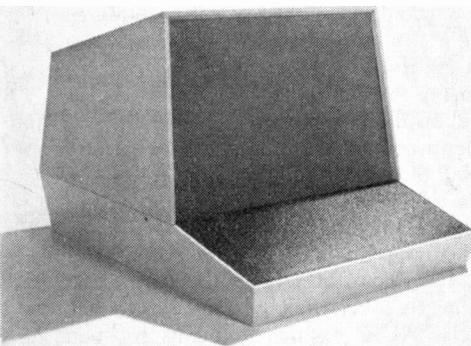Jubilee universal cabinet from Mentor Electronics



Final parameters are material and application dependent, but in general bubbles can be supplied to 812mm (32in) diameter and beyond. Other shapes are available but this is dependent on sheet dimensions. In-house facilities include normal engineering functions such as turning, drilling and bending.

Further particulars of this design service can be obtained from **Viglen Acrylics Ltd., Dept. P.E., 2 Madrid Road, London, SW13.**

DISPLAY CABINET

With so much happening recently in the field of microprocessors and t.v. games, particularly in the constructor magazines, it is interesting to see that **Mentor Electronics** have just introduced a universal cabinet for V.D.U's.

Ideal for such applications as computer terminals, t.v. games, audio equipment and test gear, the Jubilee cabinet is injection moulded from Noryl high-impact thermoplastic material. It has a moulded-in blower opening, which could be used for a small speaker grille, ventilation grilles and component mounting pillars and bosses.


The front keyboard plate is held in place by an acrylic screen. The cabinet is available unpainted or painted in a textured black and light grey.

The Jubilee housing measures 533mm x 493mm x 387mm, costs £79 and is available from **Mentor Electronics Ltd., Dept P.E., Ryefield Crescent, Northwood, Middlesex, HA6 1NN.**

ADJUSTABLE VICE

A precision made bench vice which should interest both the model making and electronic constructor enthusiast is now available from **Greenwood Electronics**, manufacturers of professional soldering irons and equipment.

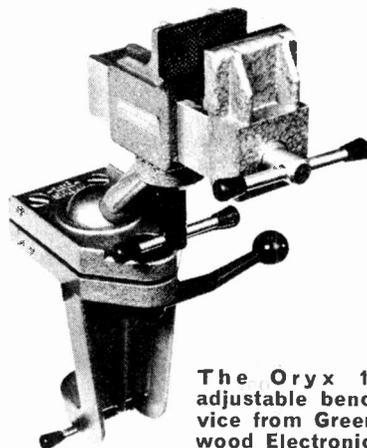The Oryx Model 1B vice is a versatile tool with 89mm jaws and is fully



The Oryx 1B adjustable bench vice from Greenwood Electronics

adjustable to rotate through 360 degrees and can be locked in any position. The vice is equipped with nylon jaw linings giving a firm grip with no damage to the work piece. Jaw linings are replaceable. The main components of the vice are cast in high tensile strength light-weight alloy and finished in stove enamelled green.

Cost of the Oryx 1B bench vice is £19.95 plus VAT at 8 per cent and is available from **Greenwood Electronics, Dept P.E., Portman Road, Reading, Berks, RG3 1NE.**

NEW TURN

Coinciding with their move to new trading premises, **Trueturn Electronics** have regraded their popular standard TT wirewound potentiometer series into three classes. Grade "A" devices are guaranteed to have a ± 1 per cent linearity and resistance tolerance. Grade "B" are guaranteed to ± 3 per cent and grade "C" ± 5 per cent, but nearer to 3 per cent linearity in practice.

The overall resistance range has been extended to 47 ohms and 47 kilohms.

The grade "A" range is more suited to applications in telecommunications and instrumentation. While grade "C" range is more suited to commercial and constructors less stringent requirements.

Further details, prices and nearest stockists can be obtained from **Trueturn Electronics Ltd., Dept. P.E., 2/3 Golden Square, London, W1R 3AD.**


NOTE

We have been asked by **Semiconductor Specialists** to point out that they are not able to deal with individual enquiries or orders for the kit of piano i.c.s mentioned on page 7 of our Supplement in the November 1977 issue.

All enquiries and orders for these chips should be placed with **Maplin Electronic Supplies, P.O. Box 3, Rayleigh, Essex SS6 8LR.**

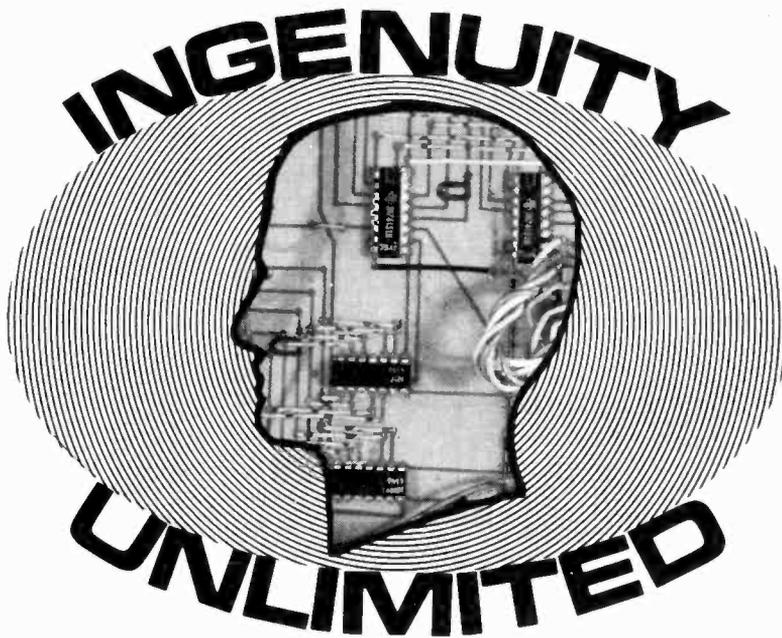Futuristic plastics hi fi console by Viglen Acrylics





A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit your idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

TOUCH ACTUATED GENERATOR

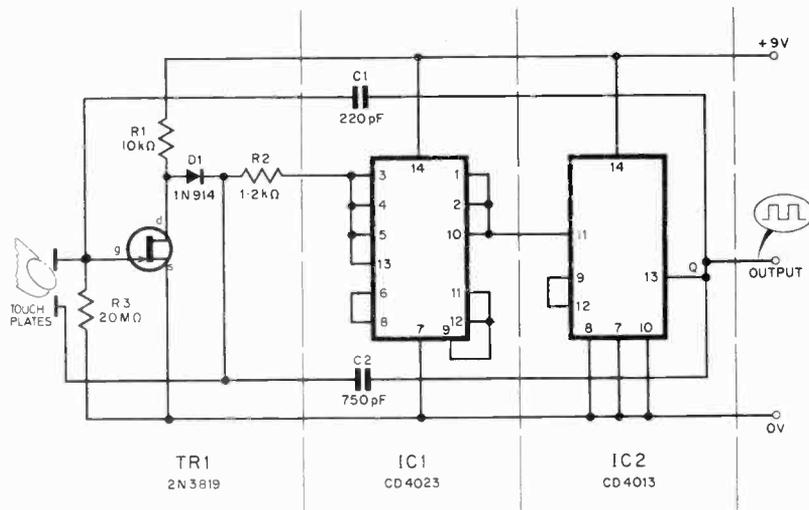


Fig. 1

THIS pulse generator provides extended pulses and is controlled by finger contact. It has the added advantage of the output being able to be held in a low or a high state.

The NAND gates of IC1 (Fig. 1), form a Schmitt trigger fed from the series diode/resistor combination D1-R2, connected to the gate of the f.e.t. The output from the Schmitt is fed to the clock of a D-type flip-flop (IC2) connected in the divide by two mode. Two capacitors provide feedback from the output of the flip-flop.

Capacitor C1, feeds the gate of the f.e.t., which, in turn controls the current flowing through R1, D1, and R2.

Hence the potential at the input to the Schmitt will rise and fall according to the state of charge of C1. The rate at which this potential changes is governed by the value of C2. With this absent the highest pulse frequency attained is 25Hz.

When the gate is low less current will flow through D1 and vice versa. Thus, the input at IC1/pin 3 is alternately low and high, giving a low and high output at Q, which is at one half the frequency.

It is interesting to note that if C2 is very much greater than C1, then it is C2 that controls the pulse width. For example when C2 is 4,700pF,

the pulse width is about 10s.

The values of capacitors shown in the diagram, give a pulse frequency of about 0.5Hz.

The generator is initiated, merely by finger contact on the lower plate. If it is desired to hold the output at one level or another, finger contact on the upper plate will hold the output until released. Both the touch plates should be situated close to mains wiring.

P. R. G. Reynolds,
Benfleet,
Essex

SIMPLE TIMESETTING FOR THE MK50250/253

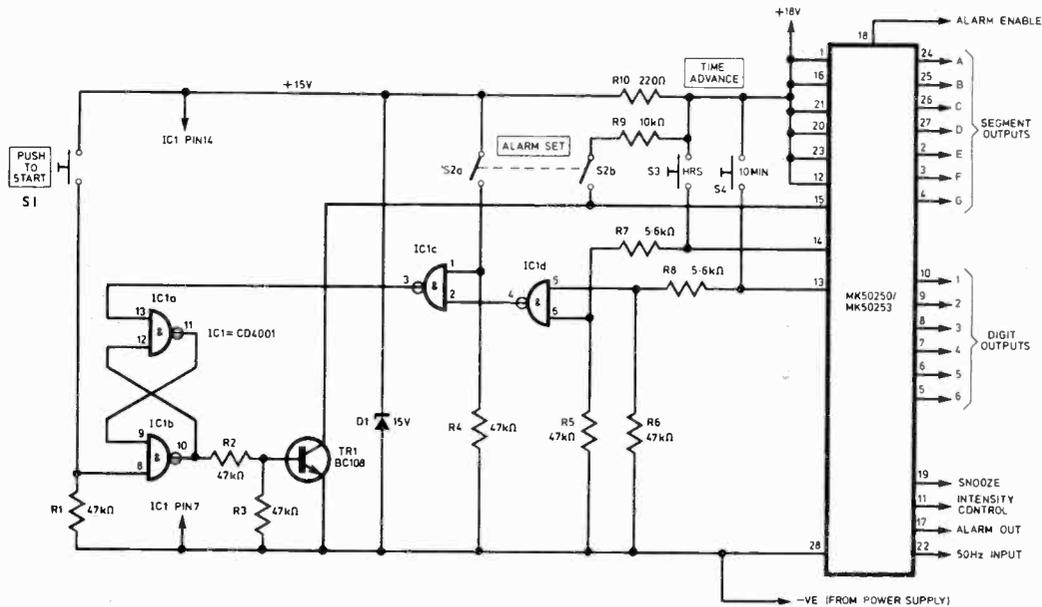


Fig. 1

HAVING recently built an alarm clock using the MK50250/253 range of digital clock i.c.s it was found that the less technical members of the family had some difficulty in understanding the correct procedure for setting the clock accurately, so it was decided to simplify the time setting procedure, the new arrangement being as follows:

(1). On altering the time, i.e. depressing one or more of the time advance buttons S3 and S4, the clock will automatically be stopped from counting.

(2). A single push switch (S1) should be used to re-start the clock.

(3). The clock will not stop on altering the alarm time.

The circuit shown in Fig. 1 uses a CD4001 CMOS quad NOR gate to perform the required logic functions, and is shown with connections to the MK50250/253 clock i.c. The 18V clock supply is dropped to the 15V required by the CMOS. The required level interfacing is achieved using R5, R7 and R6, R8.

It should be noted that with this particular i.c. in this arrangement the alarm time cannot be set unless the clock time is set and running. The circuit can be adapted to suit other clock i.c.s that have similar time setting arrangements to the MK50250/253.

F. Dart,
Glasgow

NOVEL STABILISER CIRCUIT


IF an *n*-channel field effect transistor is used to drive an *n.p.n.* bipolar device, benefit can be derived from the fact that, for normal operation within the characteristics of both devices, the gate of a low- or medium-tolerance f.e.t. will lie some volts negative to the bipolar emitter.

One useful application of such a combination is an adaptation of the familiar source-resistor-biased f.e.t. constant current device, when more current is required than the f.e.t. alone would provide.

A conventional *n.p.n.* series voltage stabiliser suffers the disadvantage that its base must be positive to the stabilised output and must therefore be

fed either from the crude d.c. at the reservoir capacitor or from a separately controlled supply. An f.e.t. driving the series element overcomes this disadvantage and enables a novel circuit (Fig. 1) to be constructed with both the gate and the reference diode fed from the output.

Fig. 1

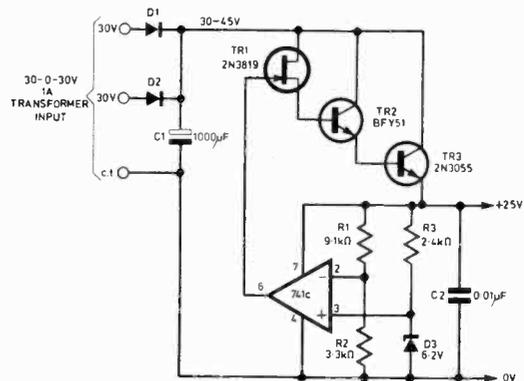

The simple arrangement shown will provide 1A at an output impedance of 50 milliohms.

P. Smith,
Burnley,
Lancs

SIMPLE LIE DETECTOR

IN this skin resistance indicator the output from a 741 operational amplifier is used to control the frequency of a CMOS voltage controlled oscillator. The base frequency, with the components shown is 300Hz with a control voltage V_c at zero rising to 5kHz at a control voltage of 10V.

The 741 is operated in the differential mode. Here, the voltage applied to the non-inverting terminal (pin 3) via the probes, is compared to the voltage at the inverting terminal (pin 2). This latter voltage will be held at one half of the supply voltage by the two 100k Ω resistors. Thus, as the skin resistance decreases, the voltage at pin 3 increases to become more positive than that at pin 2. The point at which this occurs is set by means of VR2.

The increase in the output voltage, causes an increase in the output frequency from the v.c.o. Potentiometers VR1/2 are interactive and are adjusted to give a suitable starting frequency at the v.c.o. output.

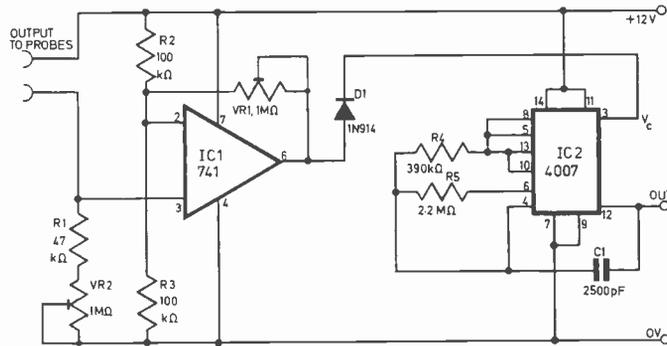


Fig. 1

The circuit may be used to monitor changes in skin resistance under stress (or relaxation!) for biofeedback or other purposes. Supply rails down to 6V may be used without any real degradation in performance.

The output may be quite easily detected using a crystal earpiece.

For the greatest sensitivity the probes should be connected to alternate strips of copper if the circuit is made up on Veroboard.

P. R. G. Reynolds,
Benfleet,
Essex

BURN ELIMINATOR FOR AUDIO XY OSCILLOSCOPE

AN XY oscilloscope is used in audio systems basically for two purposes. One is to plot the two stereo channel waveforms against each other, thus providing a measure of the separation achieved, and the other is to plot the output from the FM tuner against the a.g.c. output (before filtering) as a check against multipath reception. However, if the apparatus is left switched on for any length of time with no signal applied, or at any rate with a very low signal applied, the spot on the c.r.t. is bright enough to leave a burn mark on the screen. The circuit shown in Fig. 1 was devised to eliminate this.

Connection was made to one output of each of the deflection amplifiers by a 10M Ω resistor, the high value being to prevent any disturbance of the amplifiers. An emitter

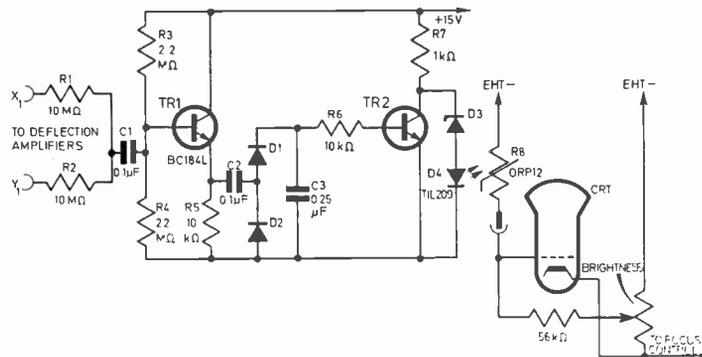


Fig. 1

follower drives a voltage doubling rectifier whose output causes the other transistor to conduct should any signal sufficient to deflect the c.r.t. beam be present. If no signal is present the 8.2V Zener conducts and the i.e.d. lights up, its current being limited by the collector resistor of the second transistor.

When the i.e.d. is illuminated, the i.d.r. goes low and drives the c.r.t. grid negative cutting off the beam. The circuit can be overridden with the brilliance control if required.

When experimenting with c.r.t. circuits extreme care should be taken, switching off and discharging the e.h.t. circuit each time before touching the circuit. The shaft of the brightness and focus controls should either be earthed (if the insulation of the pot can stand it) or be of non conducting material.

John de Rivaz,
Harlow,
Essex

TAPE RECORDER PEAK LEVEL INDICATOR

MANY of the high quality tape decks presently available utilise VU meters to monitor the recording levels in each stereo channel. Unfortunately, only the most sophisticated and expensive models provide any indication of the peak level rather than the average level. Because of this, it is possible for overloads to go unnoticed, especially in percussive music.

The purpose of this circuit is to form an add-on unit to perform this function. The input level is sensed for each channel by gates acting as

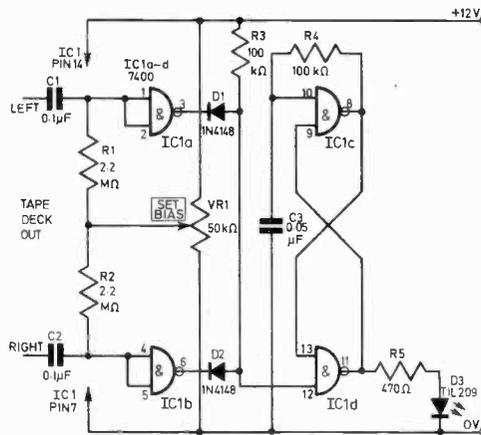


Fig. 1

Schmitt triggers (Fig. 1). They have present a d.c. bias which sets the input level at which triggering occurs. Their outputs are fed to a monostable type circuit which lights the l.e.d. in a short pulse for each input peak.

I have found the best setting for the bias pot. to be at the point

where the l.e.d. is just turning on with a two-tone sine wave input to the deck which gives a level of about +2VU.

R. J. Crowther,
Stourbridge

MODEL TRAIN SPEED CONTROLLER

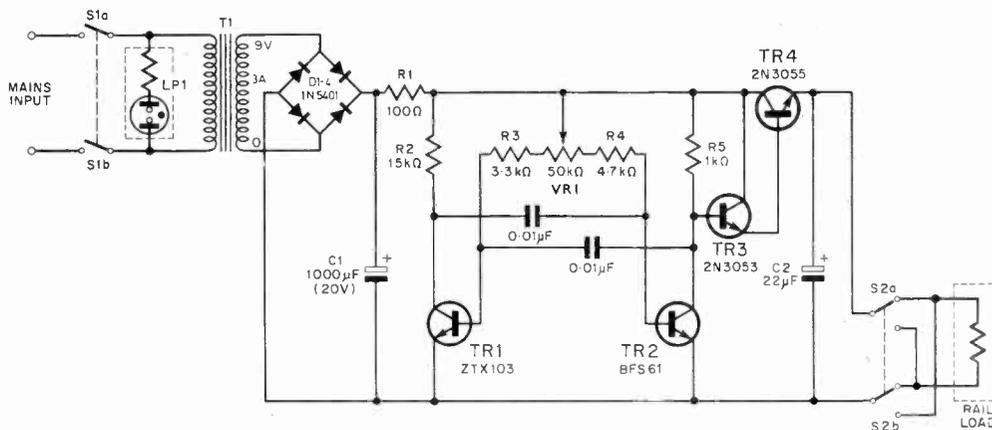


Fig. 1

THE main disadvantage with many model train controllers is that they do not give a linear control of train speed. The following circuit gives a linear control enabling the train's speed to be set anywhere between a very slow pace and full speed (Fig. 1).

Mark-space variation in oscillator output is used to change the power output to the motor. Circuit operation is as follows: T1, the bridge rectifier and C1 provide a smooth d.c.

supply of about 12V to the motor. S2 reverses the train's direction of travel. TR1 and TR2 form an astable multivibrator whose frequency of operation is about 200Hz and whose mark-space ratio is variable from about 1:11 to about 18:1.

The output from TR2 is current amplified by the Darlington pair TR3 and TR4 and applied to C2 and the motor. S2 reverses the train's direction of travel.

R1 serves as a current limiting re-

strict in the event that the rails are shorted together.

Transistor types and component values are not too critical and the circuit can probably be built up from near value components. Component layout is not critical and the circuit can easily be built on a small piece of Veroboard.

G. Hughes,
Bristol

TWO WIRE/TWO WAY BELL SYSTEM

IN the home the use of an intercom is seldom necessary as the most usual "calls" are to come in for meals, to answer the door/telephone or even to watch a particular television programme. I think that it is also fair to say that a bell is louder than an intercom so if communication with a shed, garage or workshop is required a bell is the best bet to be heard above the noise of the drilling, filing, sawing and hammering that can often be present.

Having decided to use a bell system for two way communication, there are two existing ways. The first (Fig. 1a) uses one battery/transformer with three connecting wires. The second (Fig. 1b) uses two batteries/transformers and only two connecting wires. Batteries are very expensive and decay with time, even without use, so a transformer is cheaper in the long-run.

This leaves the choice of using an extra transformer or an extra core in the connecting cable. These can easily work out at the same cost, so how about using neither?

This is the object of my circuit in Fig. 1c. Here the direction of the current determines which bell rings, the direction being set by the push switches. Since each bell runs on alternate mains half cycles, it is run

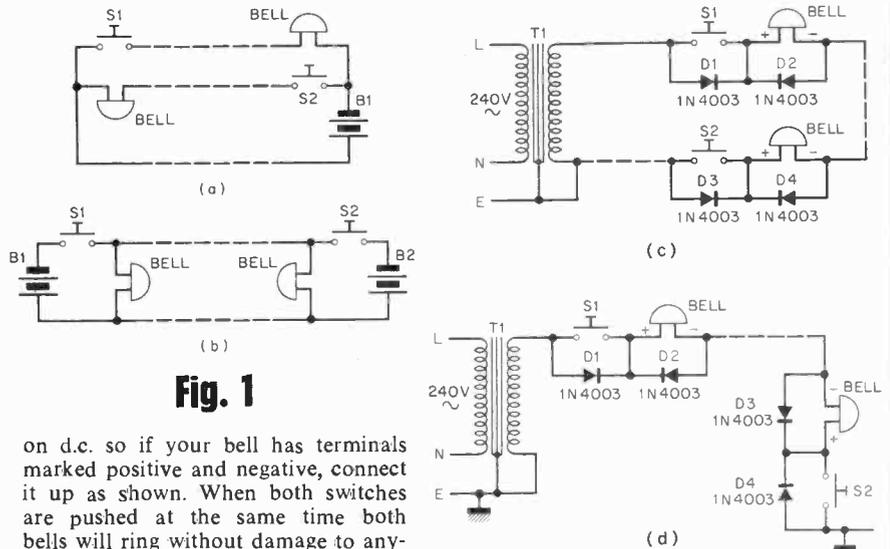


Fig. 1

on d.c. so if your bell has terminals marked positive and negative, connect it up as shown. When both switches are pushed at the same time both bells will ring without damage to anything.

If you have to run a long length of cable it will be much cheaper to use one conductor with the earth as the common. This is shown in Fig. 1d.

No details about the bells/buzzers or transformer have been given as they do not have to be matched precisely at all. Transformers which could not supply the necessary current continuously, because of the heating effect of the current, can be

used as the bells will only be on for a very short time. In the same way the transformer voltage can be in excess of the rated value for the bells. In fact it is desirable to run the bells from a higher voltage transformer than recommended by the manufacturers as it is being run from a half wave rectified supply.

L. O. Green,
Norwich

All in **NEXT MONTH'S** *issue*




AUTO RANGING D.C. VOLTMETER

Plus... Part 2. of our Important New **FAULT FINDING** Series

And... Construction Details of The **RHYTHM GENERATOR**

PRACTICAL ELECTRONICS

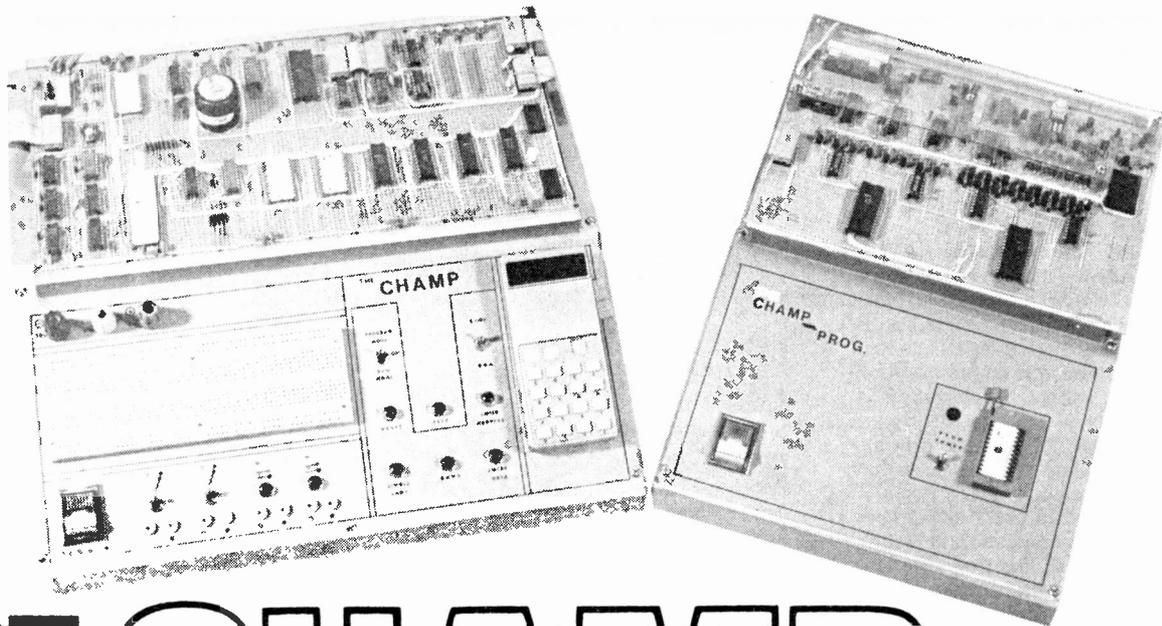OUR FEBRUARY ISSUE WILL BE ON SALE FRIDAY, JANUARY 13



PE CHAMP

PART FIVE

R.W. COLES
B. CULLEN

THE only language that CHAMP is programmed to understand is hexadecimal, and therefore to be able to talk to *it* a hexadecimal keyboard is required, and for it to talk *back*, a hexadecimal display is required. Hexadecimal is a base 16 number system which we human beings represent with 16 separate characters, namely 0 to 9 and A to F; and which CHAMP represents with a four bit binary word from 0000 to 1111 (0000 = 0, and 1111 = F). Every time we press a single key therefore, we enter a four bit word or "nibble" into CHAMP's internal registers, two presses being necessary to enter a single instruction word of eight bits, and three presses being necessary to enter a single address word of 12 bits.

The hexadecimal notation is useful because it enables us to enter data much quicker than would be possible with binary notation, and because codes for the various instructions in the 4040 instruction set are much easier to remember and use in this format. This makes program writing and debugging much simpler than would be possible if binary, or even octal were employed. The hexadecimal character set can also be represented on the cheap and freely available seven segment l.e.d. display devices, albeit in a stylised form.

CALCULATOR

As the basis of our hexadecimal keyboard/display unit we need 16 separate keys and several seven segment display digits, and of course, this combination is handily available in the form of any cheap four function calculator, making the use of such a unit the natural choice. The advantages of using a calculator rather than building

from scratch are that firstly, all the case and hardware construction has been done already, and secondly, it is unlikely that you can buy a 16 digit keyboard and an eight digit display, with drivers, for the price! Cheap "throw away" calculators can now be found for less than five pounds, and there are numerous first generation machines no longer in use, and left lying around gathering dust. For CHAMP we chose to use one of the early Sinclair Cambridge machines which were produced in very large numbers, and the result was a very compact and economical keyboard/display unit at very low cost.

We realise that you may not be able to lay your hands on such a machine, and if this is the case it should be possible, using the design and notes presented in CHAMP-5, to adapt most cheap four function calculators to suit, or even to build from scratch if you prefer.

HOW THE DISPLAY WORKS

Referring back to Fig. 2.3, you will see that there are two 75491 i.c.s (top right,) and these drive the segments of the seven segment display in the calculator. The eight inputs for the 75491 (seven segments plus decimal point) are provided by the 4265 programmable I/O chip which uses ports X and Y for this purpose. The CHAMP display is an eight digit unit and is of course driven in multiplex fashion, and this requires an additional eight control lines to select the currently active digit.

Rather than produce these digit strobes on the CHAMP board itself, a shift register controlled by only two wires from CHAMP, is used instead. The shift register, along with other circuitry, is situated inside the calculator case.

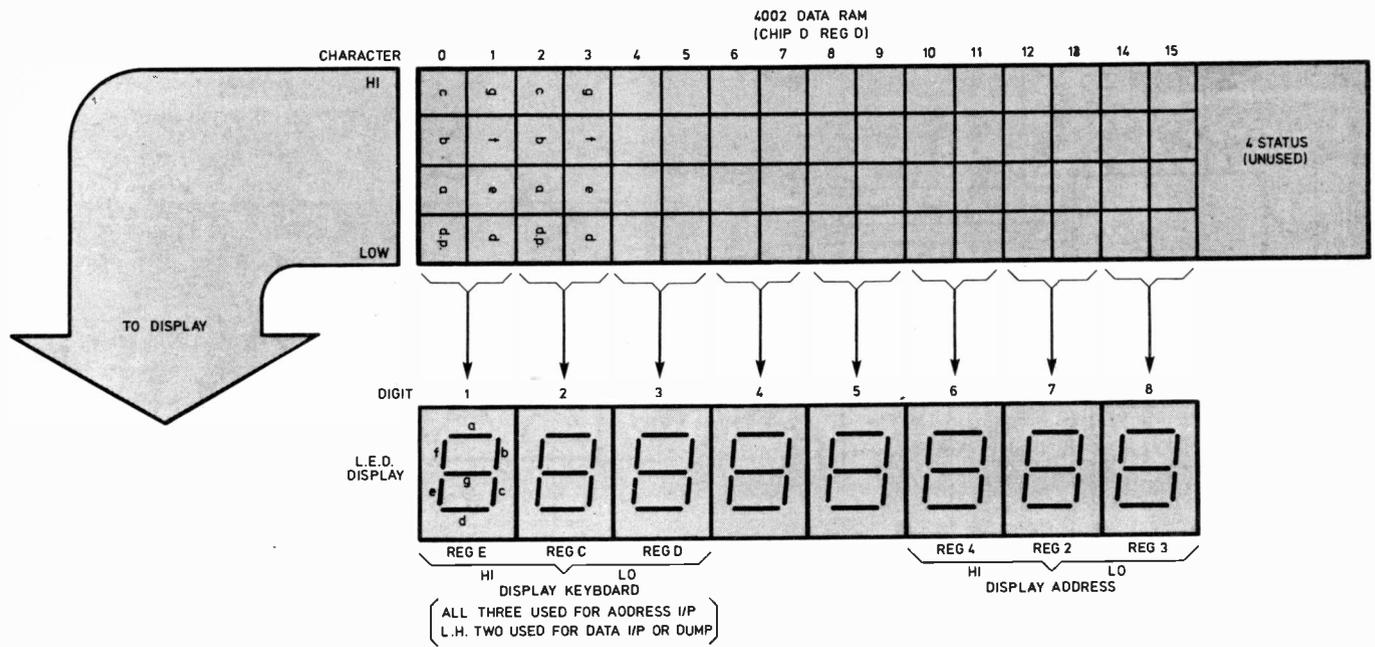


Fig. 5.1. Method of driving the display direct from RAM. A "replica" of the energised segments is stored, so that no decoding i.c.s. are necessary. Logic 1 in 4002 = Lo'. Logic 1 on 4265 o/p = Hi' = segment "on"

The CHOMP display/driver software loads a single logic 1 into the shift register, and then clocks it along to enable each digit in turn. When the logic 1 "drops off the end" of the shift register it is replaced, at the correct time, by a new one at the data input to the register.

The display driver software is responsible for making sure that the correct segment information is presented to the display at the correct digit time. It achieves this by keeping a replica code for the required display in the 4002 data RAM; reading out the data for each segment in turn to the 4265, and then going back to do it again when digit eight has been displayed, and a fresh logic 1 has been presented to the register.

The display replica is held in 4002 chip zero, register zero, where the available 16 four bit characters are used in pairs to hold the complete eight digit by eight segment display readout. This can be seen more clearly by referring to Fig. 5.1, which shows how the RAM characters map onto the display digits. Notice that the replica is already in seven segment code when stored in the RAM by CHOMP. Because the replica is not in binary, no external decoder chips are necessary to drive the display. The decoding is executed using software by means of a "look-up" table, and this will be examined in detail next month.

One advantage of driving the display in this fashion is that user programmes can drive the segments in any way they please. For example, as decimal digits only, as a full alphabet of characters (which can just about be done with some improvisation), or simply as a "0" and "1" binary display.

When CHOMP is running, only six of the possible eight display digits are used, the left-most three being used for address or data entries and dumps, and the three right-most digits being used to show the current value of the address pointer maintained by CHOMP. User programmes can of course employ all eight digits, and there is no need to write any display driver software because the CHOMP subroutine DDRV handles all eight digits, and can be called by a user programme when required.

HOW THE KEYBOARD WORKS

By using a four bit output port, a four bit input port, and some software, the 4040 chip can easily encode and debounce a 16 key keyboard, and even has a special instruction, K:BP (keyboard process), available to make the job simple. Despite this, CHAMP does not use software for this purpose, and uses instead a hardware keyboard encoder and debounce circuit; so perhaps a word of explanation is called for. During the CHAMP design process it was realised that the addition of software for keyboard purposes would make the use of two 4702A chips necessary to house CHAMP, and for economy reasons this was not desirable. In addition, the two four bit ports required would not be available on the 4265 and so some extra port hardware would be necessary, which could either be an extra 4265 or some TTL to do the same job. These two things together made the apparently simple software solution untenable in this particular case, and this constitutes, we think, an interesting example of the hardware/software trade off which is necessary in any micro-processor system design.

The hardware encoder/debouncer is in fact quite simple, and requires just four TTL packages, three of which are housed in the calculator case itself. Two 74148 eight input priority encoders with their active-low outputs NORed together by a 7400 gate provide the 16 key to four bit binary encoding function, and the debouncing is achieved with the aid of a 74123 dual monostable.

KEYBOARD/DISPLAY CIRCUIT

Figure 5.2 shows the internal circuitry of the keyboard and display and also covers the interface of this unit to the CHAMP main board. This circuit is intended for direct use by those who have a Sinclair Cambridge calculator of the correct type, but can also be used by those with a similar calculator, and by those who intend to build a unit from scratch. All that is in fact required from the calculator is the eight digit seven segment display

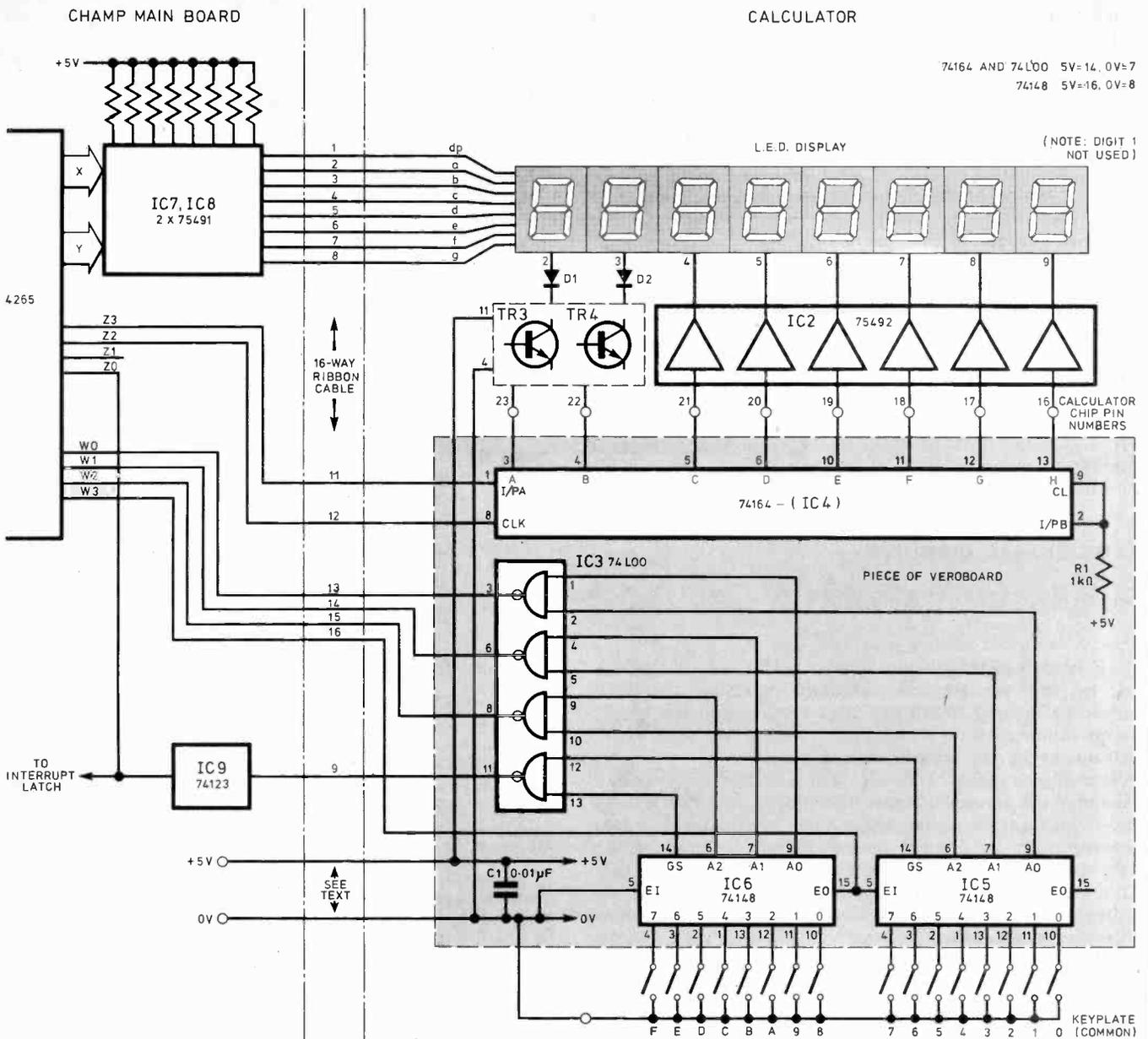


Fig. 5.2. Complete keyboard/display system showing the interconnections to CHAMP board. The shaded area shows which components are mounted on the Veroboard within the calculator case

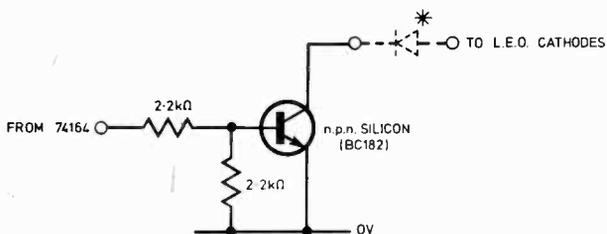


Fig. 5.2a. Driver circuitry for 0-125 inch I.e.d. display digits. The diode (1N4148) is only required when some of the cathodes are driven by a 75492 i.c.

unit (which must be a small common cathode i.e.d. unit), the digit drive circuitry (which may be discrete transistors or a 75492 chip), and the keyboard array itself (which must be capable of being rewired as 16 single keys with one common connection). The calculator MOS chip and all other circuitry is not required and can be removed. Some more recent calculator designs drive the digit lines directly from the LSI chip without separate digit drivers, and if you have one of these, then the required drivers can be added by using either a pair of 75492s or eight silicon n.p.n. transistor stages of the type shown in Fig. 5.2a. Anyone building from scratch (why not build it on the breadboard?) can use the Fig. 5.2a driver circuitry, and must add their own i.e.d. display. In this case it is important *not* to use the 0.3in or 0.6in type of discrete i.e.d. because these have a voltage drop which is "too high for comfort" on the 5V supply scheme employed here. *Only small 0.125in common cathode arrays are suitable.*

Those using other calculators, or building from scratch, may also find it necessary to alter the value of the current limiting resistors R51 to R58 on the main board to achieve a satisfactory display intensity.

ADDITIONAL CIRCUITRY

Returning to Fig. 5.2, display, drivers, and keyboard components can be identified which form part of the original calculator, and also the additional components which must be mounted inside the calculator case.

Four integrated circuits are added to the calculator, as we shall see later, and these are mounted on a small piece of Veroboard which may be housed in the battery compartment of the Sinclair Cambridge. The digit drive shift register is formed by IC4, with its A data input driven by output Z3 of the 4265, and its clock input driven by output Z2, under the control of the CHOMP software. The eight outputs of the 74164, are the digit strobes and are applied to the display via digit drivers which in the case of the Sinclair unit, are already available on the calculator p.c.b. The 75492 driver has only six stages, and to make this up to eight, Sinclair have added two discrete transistor stages, but this poses a small problem when working from 5V supplies because the difference in voltage drops between the two types of driver causes a difference in i.e.d. digit brightness. This was easily cured in our keyboard unit by adding silicon diodes in series with the *discrete* driver outputs. Anyone who used all 75492 drivers, or all transistor drivers, should of course omit these diodes.

Integrated circuits IC3, IC5 and IC6 form the keyboard encoder, where IC5 and IC6 are 74148 eight input priority encoders, which give a three bit binary output code corresponding to the active input line with the highest numerical weighting. To get a full 16 line encoder, two 74148 devices are cascaded using the OUTPUT ENABLE and INPUT ENABLE facility provided on these chips. Chip IC3 provides the final three low order BCD bits and the common "group strobe" which is present when any key is pressed, the high order BCD bit being taken directly from the ENABLE output of the 8 to F encoder. This encoder scheme is simple and very effective, having the advantage of requiring a very simple switching array of 16 s.p.s.t. keys with one side of all of these wired common to 0V. This overcomes a major obstacle when using a cheap calculator keyboard, because almost any design can be rewired into this configuration from the "row and column" matrix usually employed. The type of matrix used in a calculator design varies a great deal, but a little careful thought should be

enough to enable a CHAMP builder to adapt any design to suit this simple new requirement.

As you can see, a total of 17 connections are required between the keyboard unit and the CHAMP main board, which poses a bit of a problem because 16-way sockets have been chosen as Standard. The solution was to carry the 15 logic signals using the standard 16-way ribbon cable connection system, and to add two extra wires for the 0V and +5V power supply to the keyboard. As you can see in the photographs, these two extra wires were the two "outers" of an 18-way ribbon cable connection, and were terminated at the CHAMP end by means of sleeved Solder-con pins which can be pushed on to terminal pins adjacent to SK3 on the main board. This arrangement has worked well in practice, and allows the keyboard to be disconnected easily when required.

KEYBOARD CONSTRUCTION

From now on, we will be considering the keyboard design used with the CHAMP prototype, and this means that details which follow relate *only* to a particular version of the Sinclair Cambridge which uses the Texas Instruments' TMS0801 calculator chip. This type of Cambridge can be recognised by the fact that it has a CE button between the C button and the ON/OFF switch, whereas some others have a K button.

Start by dismantling the case. This is achieved by locating a screwdriver in the slot around the side of the case and twisting. The buttons and keyplates are held in position by means of a plastics retaining frame which has three studs protruding through the circuit board which are welded on the component side. Lay the calculator circuit board face down on a flat surface and snip the welded studs away, then lift the circuit board off and you should be left with the key buttons and their retaining frame. The stainless steel keyplate will be left attached to the circuit board by means of the ON/OFF switch, and this should be removed, together with its thin plastics insulating spacer. Put these parts aside for later use. If you have any trouble with this part of the modification, refer to Fig. 5.3.

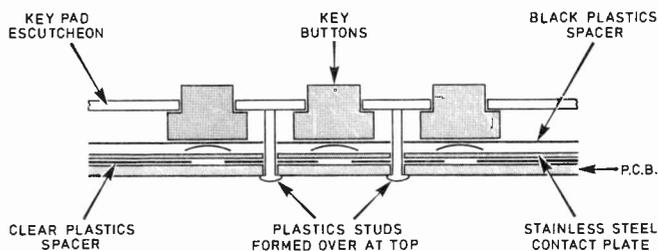


Fig. 5.3. A guide to the basic construction of the Sinclair 0801 keyboard assembly

COMPONENT REMOVAL

Using Fig. 5.4, identify and remove the following unwanted components:

- C1, C2, C3, C4.
- D1, D2, D3, D4.
- R1, R2, R3, R4, R6.
- TR1, TR2.
- L1.
- IC1.

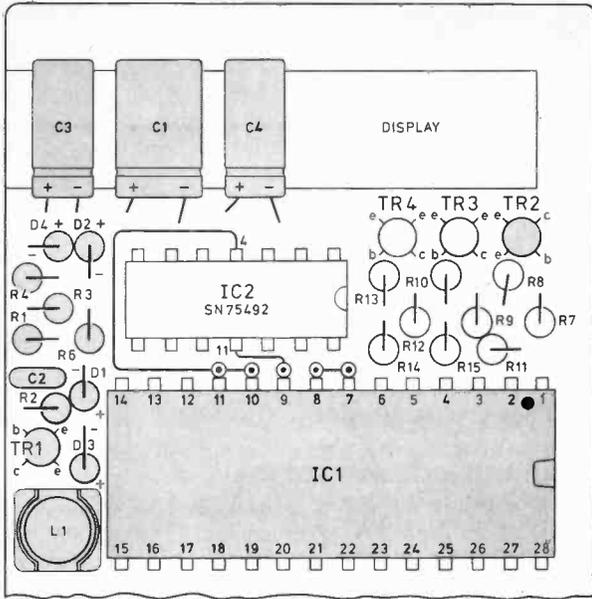


Fig. 5.4. Component layout of the Sinclair calculator. The shaded components should be removed (see text)

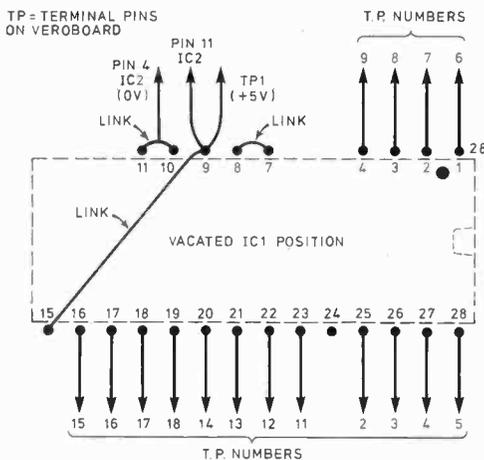


Fig. 5.5. After the calculator chip (IC1) has been removed from the Cambridge, terminal pins should be inserted through the lead holes. The vacated i.c. pad can then be wired as shown in the diagram

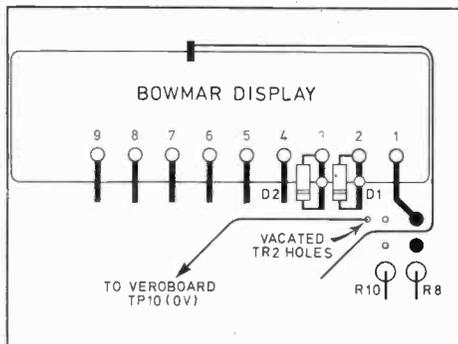


Fig. 5.6. Modifications to be made around the calculator display

The removal of IC1 in particular should be carried out with great care, since the board is double sided and uses plated-through holes. A "Solder Sucker" or de-solder braid *must* be used.

With IC1 removed, refer to Fig. 5.5, insert the terminal pins and make the links (except those to PL1 and the Veroboard) as indicated.

Using Fig. 5.6, identify the Bowmar i.e.d. display and then, working from left to right, break the tracks connecting display digits 2 and 3 to the circuit board proper, and bridge the gaps with two IN4148 Silicon diodes as shown. Next, add a flying lead from the hole location shown, to act as a 0V connection to the Veroboard, to be added later. Using Fig. 5.7, which shows the component side of the calculator circuit board, make the 16 track breaks required with a sharp modelling knife or similar implement, and be sure to get rid of any swarf which may cause shorts later. The flying leads from individual keypads can now be added, and these should be of Kynar wire (or similar) left long at first, and trimmed to size when the Veroboard is added. To avoid disaster, these wires should be soldered very carefully to *avoid solder running through the plated hole to the keyplate side* where it will cause trouble.

THE VEROBOARD

The Veroboard layout is shown in Fig. 5.8, and this board can now be cut to size and assembled in the usual way. Soldercon pins were used for all four i.c.s in the prototype although this is not essential. Make sure that all track breaks, terminal pins, wire and fixing holes are correctly located, and then wire up the board with the fine wire in accordance with Fig. 5.2. Notice that PL1 does not mate with a socket, but is soldered directly to the board.

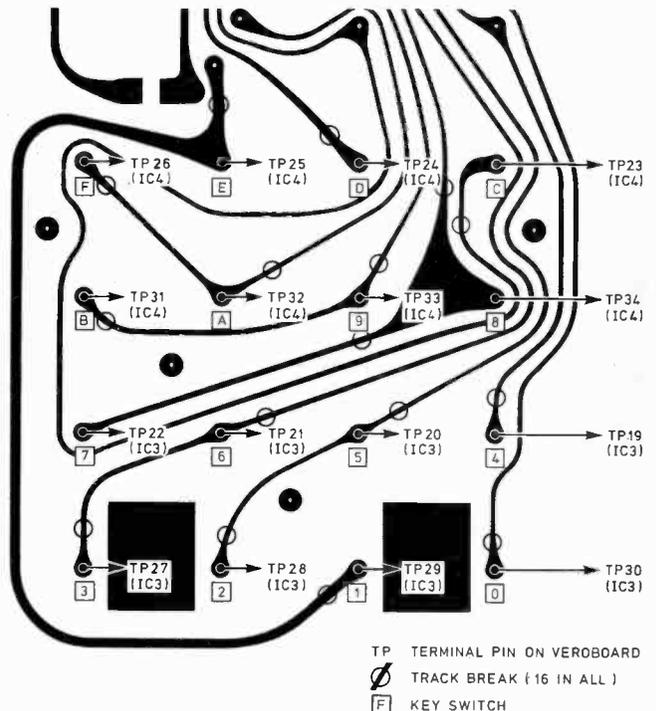


Fig. 5.7. Proprietary p.c.b. inside the Sinclair Cambridge, showing the keyboard end where track cuts are necessary

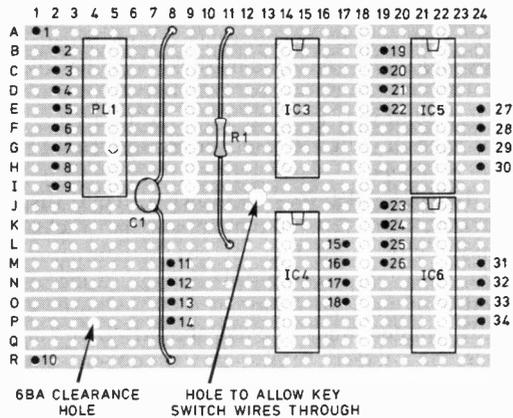


Fig. 5.8. Component layout for Veroboard to be mounted inside the calculator case

Terminal pins could be used for this termination instead of the 16-way plug, but in this case some kind of "strain relief" should be provided for the loom to prevent wires breaking during everyday use of the keyboard.

Using the circuit diagrams the Veroboard can now be connected up to the rest of the calculator circuitry. This involves:

- 16 connections to keypads
- 17 connections to IC1 (now removed)
- one connection to the hole left by the emitter of TR2 (now removed).

KEYBOARD ASSEMBLY

In the prototype, the Veroboard was attached to the calculator p.c.b. by means of a countersunk 6BA screw, which made it necessary to drill and countersink a hole in the main circuit board. This had the advantage of easy dismantling should it be required, and the addition of two insulating strips act as spacers. Perhaps a better solution would be the use of double sided sticky pads.

Reassembly of the calculator can be achieved fairly easily by reversing the dismantling procedure, the separate parts of the keyboard assembly being adequately retained by the case when it is snapped together.

POINTS ARISING

BURGLAR ALARM (May 1977)

Constructors may find that in the GUARD condition, sufficient current can leak through LP1 and LP2 to energise WD1, (see Fig. 1). This can be overcome either by replacing these bulbs with l.e.d.s (in series with 560Ω resistors), or placing a OA47 diode in series with LP2 *only*, wired in forward bias.

In order that the TAMPER SWITCH (S3) will operate at any time, it should be wired between points "12" and "11" via a 330Ω resistor, and *not* points "12" and "11" as shown in Fig. 1.

FREQUENCY COUNTER/TIMER (September 1977)

Some readers have found that the crystal XL1, in Fig. 4, does not control the oscillator frequency as it should do. Anyone experiencing this difficulty should try reducing the value of C6 to around 330pF.

COMPONENTS . . .

KEYBOARD/DISPLAY UNIT

Resistors

1 off 1kΩ R1

Capacitors

1 off 0.01μF ceramic C1

Semiconductors

2 off 1N4148 D1, D2
 1 off 74L00 IC3
 1 off 74164 IC4
 2 off 74148 IC5, IC6

Miscellaneous

Sinclair Cambridge calculator (type using TMS 0801 chip)
 Stripboard, 0.1 inch matrix
 Terminal pins
 16-way d.i.l. plug (PL1) and ribbon cable
 Kynar, or similar wire

CONSTRUCTOR'S NOTE

The keyboard/display unit, as with other system parts extraneous to the CHAMP board, can be linked using ribbon cable and d.i.l. plugs and sockets. The sockets are readily available, but the plugs may be obtained from: **P.S.P. Electronics, 228 Preston Road, Wembley, Middlesex, HA9 8PB.** The plugs are made by T & B Ansley, part No. 609-M165 (16-way).

TESTING

The keyboard encoder can be checked in isolation by wiring four l.e.d. lamps with 1kΩ resistors in series to pins 13, 14, 15 and 16 of the 16-way d.i.l. plug on the end of the flat cable. The anodes of the l.e.d.s should be connected to +5V, and the supplies should be connected to the keyboard as if for normal use. Pressing any key should generate the correct binary code on the four l.e.d.s, though in inverted form (light off equals logic 1). The strobe output on pin 9 should always be generated regardless of which key is pressed, and this can be checked with a fifth l.e.d. or by means of a voltmeter. Checking the display is more difficult, although if trouble is experienced, ohmmeter checks between the segment drive lines and the outputs of the digit drives can be carried out as a starting point.

WIDE USE

The CHAMP keyboard/display described this month is by no means dedicated only to the CHAMP system, and could, if required, be interfaced to almost any micro-processor system where its ready encoded keyboard output and flexible display format would be an advantage.

NEXT MONTH: CHOMP Firmware

PATENTS REVIEW

Copies of Patents can be obtained from :
the Patent Office Sales, St. Mary Cray, Orpington, Kent Price 95p each

TOUCH SWITCH


BP 1 477 252

An outline of the various techniques adopted to-date to provide stray field capacitor switching is given in BP 1 477 252 by Robert Bosch GmbH, Stuttgart.

Essentially, such switches incorporate two flat electrodes, spaced apart, so that one transmits and the other receives a signal, in a manner responsive to any change in the signal path, for instance by the approach of a finger. The new patented circuit is intended to overcome disadvantages of this basic type, for instance sensitivity to moisture and humidity.

In Fig. 1 a transmitting electrode is connected to a high frequency generator and capacitively coupled to the receiving electrode by the stray field. The receiver is connected to a compensating amplifier, which also directly receives the output of the generator for comparison with the received signal. Between the two electrodes there is a further central electrode which is earthed.

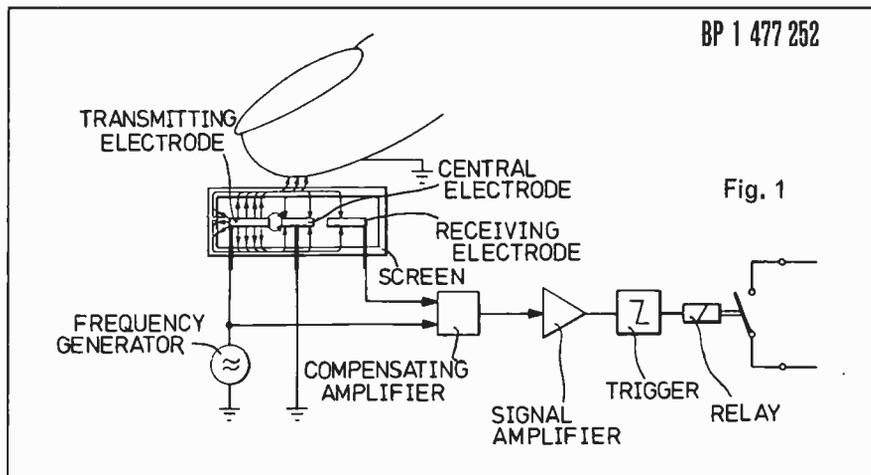Under a normal condition, the compensating amplifier senses the presence of a reasonable signal from the receiver and holds the relay (operative



on a load such as a horn) open. When the tip of a finger is moved towards the surface of a metal screen covering the three electrodes, some of the field is diverted upwards by capacitive coupling and this attenuates the signal received. Accordingly, the difference between inputs to the compensating amplifier increases, as does the output. This triggers the changeover of the relay contacts.

It is claimed that the comparison technique overcomes the difficulties caused to conventional trigger circuits when they become dirty or wet.

IN BRIEF

BP 1 459 902—Stiefenhofer KG: *Control Switch*. Control apparatus for use by at least partially paralysed persons. A cyclically stepped switch, which can, for instance, be used to control a telex machine, is itself controlled by the logic interpretation of very basic pulses generated by a simple switch which can be controlled by a paralysed person, e.g. by light finger pressure or air pressure from the mouth.

PATENT COPIES

Every month we carry a note telling readers how to go about buying copies of British Patents mentioned by number. Unfortunately the British Patent Office still maintains its flat-rate pricing policy, whereby a simple patent of two or three pages costs the same (currently 95p) as a four-volume computer specification.

Inevitably this deters many people from buying copies of patents, for instance of new electronic circuits, which they would otherwise like to have

for reference at home. As we have previously reminded readers, however, it is possible to economise by visiting any one of the two dozen libraries around the country which have copies of British Patents, or at least abridgements of them, on their public shelves.

This also presents a useful and quite legal way of beating the pricing system. In virtually all the British libraries with patents on their shelves (except the main patents library housed in the building of the London Patent Office in Chancery Lane) it is possible to have on-the-spot photocopies made of selected pages of a patent. Average cost is around 6p per page.

The main London library will not make selective photocopies in this way

at page rate, because they very rightly fear that so many people would use the system and so many bound volumes of patents would be continually off the shelves and in the photocopying room that the library would cease to be useful for reference. But the provincial patent libraries are far less busy, and anyone wanting a copy of just a couple of pages of a patent, for instance the main circuit diagram and a list of component values, will be able to get it for just a few new pence if they go to a provincial patents library.

Most of the major cities have such libraries, but if in doubt readers can phone 01-405 8721, ask for Library information, and check their nearest source of patents.

...TWO-DAY COURSE

Sponsored by **PE**

SYSTEM DESIGN with MICROPROCESSORS

Organised by INTERPROJECTS Limited
Technical Services

JANUARY 6 and 7 1978
9 a.m. to 5 p.m.

at the **INSTITUTION of ELECTRICAL ENGINEERS**
SAVOY PLACE LONDON W.C.2

Conducted by **D. ZISSOS**
Professor of Computer Science University of Calgary Canada

An intensive two-day course aimed to enable practising engineers, technical managers and hobbyists to design and implement their own microprocessor systems using methods that require no specialist knowhow of electronics or programming other than a basic knowledge of logic.

Professor D. Zissos is an established authority on logic design, on both sides of the Atlantic. He has written numerous books and articles on the subject. Professor Zissos is also a practising design consultant known for his pragmatic approach, with several projects to his credit.

Registration

The course is of limited enrolment and applicants will be dealt with strictly in order of receipt of completed coupon and remittance.

Fee : £45 (plus £3.60 VAT) includes a book "Problems and Solutions in Logic Design" by D. Zissos and comprehensive lecture notes.

The proceedings will be opened by Professor C. Turner, King's College, London.

Please use **BLOCK CAPITALS**

To INTERPROJECTS LTD.,
29, Church Street, Edmonton, London N9 9DY

Please make the following reservations for the 2-day course System Design with Microprocessors.

Signature

Name

Address Home/Company

Delegates name


1

2

3

4

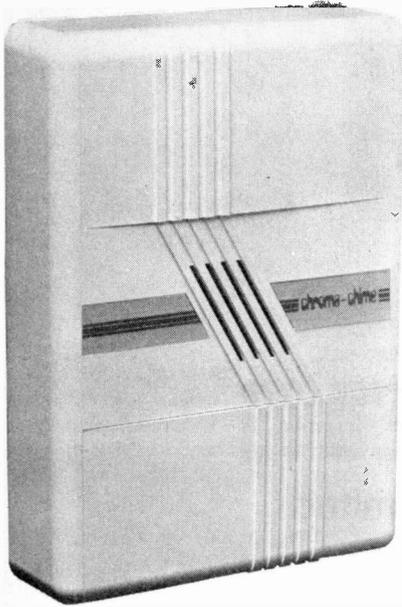Enclose cheque/PO £..... at £45 plus £3.60 VAT each. Payable to Interprojects Ltd



CHROMA-CHIME

kit review

BRAIN child of a young British engineer, Robin Palmer, the Chroma-Chime is claimed to be the world's first microprocessor-driven electronic door chime. The Chroma-Chime has been on the market for some months, and more recently has been made available in kit form for constructors.

The Chroma-Chime Kit is of particular interest since it brings the microprocessor (in a dedicated form) into the hands of the constructor in a reasonably priced project which has the great merit of being a useful and attractive item for installing in one's home. Thus the constructor can satisfy his curiosity concerning these latest devices, gain experience using them, and at the end of a five-hour building stint possess an article whose functioning will never fail to amuse and amaze friends and all callers!

THE HEART

The heart of this electronic door chime is a 4 bit microprocessor, Texas TMS1000. This 28-pin *p*-channel device incorporates a clock generator, RAM, ROM and I/O, as well as CPU and therefore is correctly described as a one-chip micro-computer.

It is of interest to note that the TMS1000 is currently in use in various dedicated applications, including taximeters, scientific calculators, a board game and, perhaps the most sophisticated use so far, as an electric cooker controller where it times the on/off periods according to recipes and fires the triacs in the power circuits.

In each of its customised forms, the TMS1000 is marked additionally with a unique code number. In the case of the Chroma-Chime, this is MP0027A.

For this particular dedicated application the original software programme written by the Chroma-Chime designer has been built into the ROM during chip manufacture by Texas Instruments.

CHROMA-CHIME DETAILS

All the notes necessary to produce the 24 tunes are generated by counting down from the master clock oscillator. Since they all have precise digital relationships they cannot go out of tune to each other.

Five transistors are included in the twenty-odd discrete components that go to make up the overall circuit. Three are used in control circuits and two form a Darlington pair driving the loudspeaker.

Twenty-four tunes are "in-store". Selection is made via two control knobs readily accessible at the front of the unit. Other controls are provided for volume, tempo (speed) and tone.

The Chroma-Chime can be operated from two separate bell-pushes. One circuit provides access to the full repertoire, the other (intended for the back door) allows a choice of two tunes only.

The jingles include Greensleeves, God Save The Queen, Oranges and Lemons, and Beethoven's "Fate Knocking".

THE KIT

The Kit was well organised. Everything in the component and material line (including solder) was provided. (With our kit was an Erratum slip: the five

points covered were duly noted and the relevant parts of the Manual amended accordingly.)



An excellent Assembly Manual explained everything very clearly, with many line diagrams and photographs illustrating different operations in the assembly. If the maker's advice to read the Manual through before starting construction, and then to follow it through paragraph by paragraph in practice is adopted, success should be achieved first time.

PREPARATION

Close examination of the parts, checking every item against the list provided, is an important first step. We discovered a bonus in our kit, in the form of a spare 39k Ω resistor.

The microprocessor chip was supplied mounted on a piece of expanded polystyrene, with a piece of tin foil sandwiched between. The chip was not removed from this packing until the time had arrived to mount the i.c.

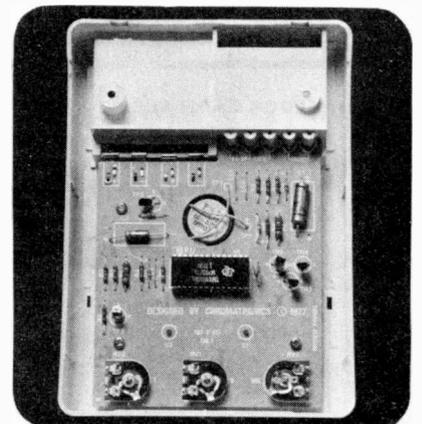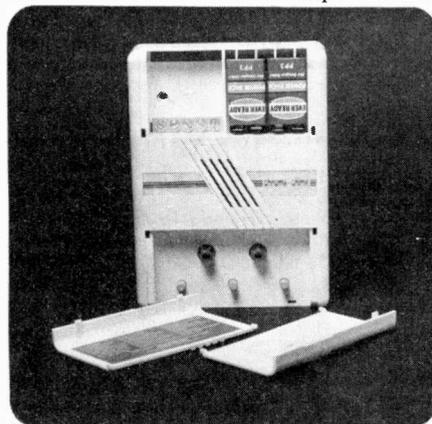To the tools specified for the job, we would suggest adding a bench light or torch, and a magnifying glass. It's best to have no doubts or uncertainty as to



whether a connection point has been well and truly soldered.

Do not forget to acquire the two PP3 batteries. To finish the construction work (say one evening) and then be unable immediately to test one's workmanship must be frustrating, to say the least.

ASSEMBLY

The actual assembly work on the p.c.b. is not difficult, provided one has had some experience with small-scale operations, and has a certain adroitness with a miniature soldering iron. The Manual recommends a bit less than $\frac{1}{16}$ in (3mm). We used a 1.5mm bit, which proved ideal; except for sweating the four battery contacts, when we switched on a 3mm bit. The amount of 22s.w.g. multi-core solder provided was well in excess of actual requirements.

We took time over the assembly of components on the p.c.b., double-checking values and positions of every component.

The big moment was mounting the i.c. socket and fitting the i.c. in position. Having first carefully aligned the pins with the sockets, a good firm downward pressure was applied and i.c. was home,

safe and secure. The i.c. socket connecting strips came away cleanly after repeated bending with pliers.


When the p.c.b. assembly work was completed there were only two further soldered connections to make—to the loudspeaker. This unit is clamped to the case with three "Starlok" washers. We adopted the Manual's advice and found that an old ball point pen case served admirably as a box spanner for this purpose.

The completed p.c.b. was then fitted into the case. The control knobs were located in the holes at the front of the case and they then engaged with their respective parts on the p.c.b. Finally, a few screws were fitted and a pair of PP3 batteries inserted into the compartment.

TESTING

Still carefully following the Manual, we set the various controls as stated, placed a screwdriver blade over terminals three and four and were almost immediately regaled with the opening theme from Beethoven's Fifth.

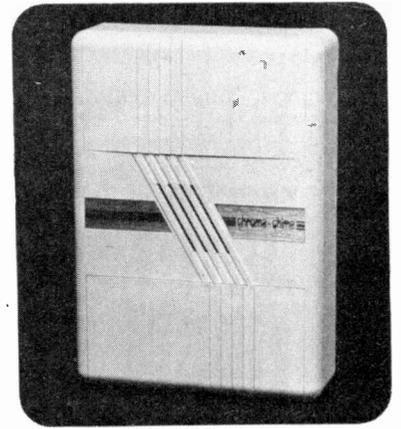After carrying out the full testing procedure we fixed the labels (decorative



and informative) to their respective places on the case, and fitted the two access covers and the base cover.

INSTALLATION

Installation should present no problems. Any lamp incorporated in a bell-push must be removed before connecting up, otherwise the Chroma-Chime will sound continually. Detailed instructions concerning Installation and Operation are provided in a separate leaflet accompanying the kit.

NEWS BRIEFS

GEC Computer System for RNIB

THE Royal National Institute for the Blind has placed an order on GEC Computers Limited, valued in the region of £175,000, for the supply and maintenance of GEC 4070 computer equipment to be used in the production of braille literature. The order is part of a major expansion and modernisation exercise which will make the RNIB's work in this field the most advanced in the world.

The computer equipment will be used in the RNIB's new printing centre and will speed publication of a greatly increased range of braille books and periodicals for educational, vocational and recreational purposes.

Operators at 16 text-entry visual display terminals will key in text from English originals. The computer system will directly accept these inputs and translate the data into braille output coded onto magnetic tape cassettes. These are used to control embossing machines which automatically punch the braille characters (called cells) onto zinc plates suitable for use on a printing press. Alternatively, for single copies of a document, the computer can itself drive a paper embosser thus eliminating the need to manufacture a metal printing plate. The use of visual display units as input terminals gives the operators the facility to edit text on entry. Separate purpose-built refresh graphics display terminals are used to edit the braille cells prior to committing the output to embossed paper or zinc.

The new GEC system will replace an existing system which uses punched cards as the text input medium.

At present if edits are necessary which cannot be contained on one single source card—and this really means changes of a very minor nature indeed—then repunching and re-translating of all subsequent cards may be necessary. Editing, particularly on a large work, is thus a very laborious procedure, wasteful in time and materials. It is only then this stage is completely

satisfactory that the output deck of punched cards, representing braille, can be produced.

Solar Water Heaters

A ONE day technical meeting organised by the UK Section of The International Solar Energy Society held at the Royal Institution, London, in October was devoted to Practical Aspects of Domestic Solar Water Heaters. Papers were delivered by specialists in various subjects, dealing with component parts such as collector plates, control systems and complete solar installations in houses.


Of the latter, two examples of conversions for solar energy collection and storage in existing properties were described: one was an energy saving house project sponsored by Granada TV, the other concerned experiences with a pilot domestic solar-assisted water heating system installed in a modern flat, under the auspices of a South London Consortium of Local Authorities. Finally, a lecturer from Ayr (Scotland) Technical College described progress in the house he is building himself, in which solar heating has been planned-in right from the start.

Electronics came into the picture during the discussions on control systems. Standard modules containing most of the electronics are normally used. The thermistor is the generally used and favoured sensor, and thermal-couples were not recommended because of attendant problems with pipes. There was some discussion about the position of the sensor: important that it be *within* the collector panel, and critical in placing on cylinder (about one-third up from bottom being suggested), incorrect positioning could cause feedback to occur.

International Broadcasting Convention

BECAUSE it has outgrown the facilities available at Grosvenor House, its traditional home since 1968, the next International Broadcasting Convention will be held at the Wembley Conference Centre, London, September 25-29, 1978.

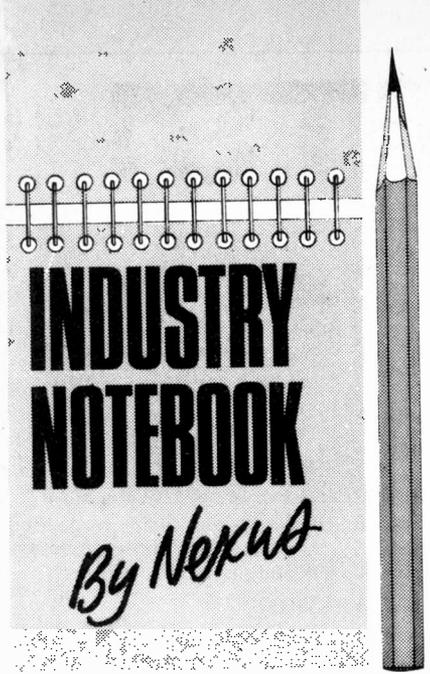The IBC is a biennial event; it provides an international forum for engineers with interests in the wide field of broadcasting to discuss technical developments, and to exhibit and demonstrate the latest equipment. Further information can be obtained from The Secretariat, International Broadcasting Convention, IEE, Savoy Place, London WC2R 0BL.



INDUSTRY NOTEBOOK

By Nexus

BERLIN SHOW

Old-timers in the UK look back with nostalgia to the great Radiolympia shows of the late '30s when thousands of the listening and looking (high-definition TV had just started) public flocked to the Olympia exhibition halls to see what was new. Attempts were made to revive the shows in the post-war years but without commercial success.

For a taste of the excitement of a huge radio show you now need to visit Berlin. The international show this year attracted over 600,000 visitors, an all-time record reflecting the many attractions and brilliant organisation laid on. There were 468 exhibitors from 27 countries so there was plenty to see.

Perhaps the most interesting statistics to emerge from the show post-mortem was the result of a special poll of private, as distinct from professionally engaged, visitors on whether they were familiar with Teletext and Viewdata. Of those questioned 69 per cent knew about Teletext and 60 per cent Viewdata. And of those polled, 33 per cent said they would be prepared to buy both systems.

One sector which is flourishing is Citizen's Band radio. German manufacturers were complaining that the Bundespost didn't give enough warning before the facility became available. Now, however, at least seven German manufacturers are making equipment to meet a demand estimated at 50,000 sets a month.

All equipment has to be submitted for approval to the Bundespost and this may hamper some of the cheaper imports from the Far East. Twelve channels have been allocated for CB in the 27MHz band and it appears there is already much channel congestion in centres of high population.

Overall the German market in entertainment electronics is expected to grow

between eight and ten per cent in 1977, certainly not exciting but not unsatisfactory in the prevailing economic climate.

Meantime, back in the UK there is still considerable pressure to restrict the imports of Asian consumer electronics goods and, at the time of writing, the Hitachi affair is still unresolved. For those who haven't been following the story, the Government is anxious to encourage foreign investment and two Japanese companies have already set up TV manufacturing plants in the UK. They are National Panasonic (Matsushita) and Sony. Now Hitachi wants to come in and set up a TV plant to employ 400 people.

Mullard, Britain's largest component manufacturers and only TV tube maker is objecting, supported by Thorn, Britain's largest TV manufacturer who say that if Hitachi comes in and competes in the UK they may be forced to buy far more components from the Far East to compete in price, thus withdrawing component orders from Mullard and other UK suppliers. It is argued that to create 400 new jobs in the proposed Hitachi plant may result in the loss of 1,500 jobs or more elsewhere and lead to the eventual collapse of British component manufacturers.

Among those lobbying are the trade unions, members of Parliament, component and set manufacturers. The Department of Industry is split in its views and so, it is said, are working parties discussing the problem in the National Economic Development Council.

British companies have a production capacity of 2.4 million TV sets a year. Total output in 1977 is expected to be only 1.5 million. So clearly the nation doesn't need any more capacity for manufacturing. But, perversely perhaps, the buying public likes Japanese sets. So better to make them in the UK with British labour rather than import them. Or is it? The debate continues.

ON THE MOVE

Apart from microwave ovens and Doppler-shift type intruder detectors, neither of which are yet in the real mass-market, it is hard to see microwave devices catching on with the general public. But in the USA where they are more liberal on such matters, car-mounted radar speed-trap detectors have been making good progress. One forecast is that a million will have been sold by the end of 1977.

The only snag is that nearly all the detectors work on X-band while the American police have been moving their speed measuring equipment up to K-band. The police use hand-held equipment like a gun pointed at the suspect and momentarily press a trigger to obtain a measurement instead of the X-band method of continuous radiation. So not only are the road-hogs' detectors foiled by being in the wrong waveband

but the momentary radiation on K-band will be very hard to detect in time to avoid a fine.

THE MIDDLE EAST

The £500 million extension of British Aircraft Corporation's defence contract with Saudi Arabia was heartening. BAC employs 2,000 people overseas in a massive training and equipment programme for the Royal Saudi Air Force and 750 other companies, including electronics suppliers, stand to gain through sub-contracts.

Rumours that Racal Electronics Group had set up a factory in Egypt were confirmed at the recent Racalex exhibition in London. Racal chairman, E. T. Harrison, stated that the Egyptian and other joint manufacturing agreements overseas had been worth £25 million and that the need to collaborate with overseas governments was recognised and would continue.

The contract with the Egyptian Government involves the training and supervision of a local labour force of over 200 people for manufacture of Racal-designed SSB communications equipment in a purpose-built factory.

Selling technology is good business but it also exports jobs.

The counter argument is that if companies like Racal don't step in then others will. Harrison said that Racal held off powerful competition for the Egyptian contract from leading French, American and other British firms. And it is a fact of life today that when a large contract is negotiated through overseas governments that some measure of local production is stipulated. Only in such ways can a developing country establish an indigenous electronics manufacturing capability.

Another good contract from Arab sources is for Marconi Marine equipment for the United Arab Shipping Company. Forty of the company's fleet of 60 ships are already fully equipped with Marconi radar, radio, ADF and echo sounders. The older Russian-built vessels in the fleet are now being re-equipped as necessary with Marconi equipment.

SHAKE-OUT

The South African electronics industry, dominated largely by subsidiaries of British, French and American companies, is now virtually self-sufficient and, under Government pressure, is currently moving to completely local control, especially in key areas of defence electronics and "strategic" products. The trend is for majority shareholdings to be acquired by local interests with the former principals permitted to retain a minority interest.

ITT, for example, has already relinquished control of one of their South African groups of companies, retaining some 30 per cent of the equity.

15-240 WATTS!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.


FEATURES: complete pre-amplifier in single pack; multi-function equalisation; low noise; low distortion; high overload; two simply combined for stereo.

APPLICATIONS: hi-fi; mixers; disco; guitar and organ; public address.

SPECIFICATION: Inputs—magnetic pick-up 3mV; ceramic pick-up 30mV; tuner 100mV; microphone 10mV; auxiliary 3-100mV; input impedance 47k Ω at 1kHz. Outputs—tape 100mV; main output 500mV R.M.S. Active Tone Controls—treble \pm 12dB at 10kHz; bass \pm 12dB at 100Hz. Distortion—0.1% at 1kHz; signal/noise ratio 68dB. Overload—38dB on magnetic pick-up. Supply Voltage— \pm 16-50V.

Price \pounds 5.22 + 65p VAT. P. & P. free

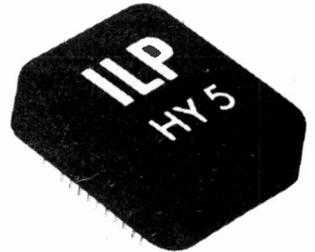HY5 mounting board B.1. 48p + 6p VAT. P. & P. free



HY30 15W into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

FEATURES: complete kit; low distortion; short, open and thermal protection; easy to build.

APPLICATIONS: updating audio equipment; guitar practice amplifier; test amplifier; audio oscillator.

SPECIFICATION: Output Power—15W R.M.S. into 8 Ω . Distortion—0.1% at 15W. Input Sensitivity—500mV. Frequency Response—10Hz-16kHz -3dB.

Price \pounds 5.22 + 65p VAT. P. & P. free

HY50 25W into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: low distortion; integral heatsink; only five connections; 7 amp output transistors; no external components.

APPLICATIONS: medium power hi-fi systems; low power disco; guitar amplifier.

SPECIFICATION: Input Sensitivity—500mV. Output Power—25W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 25W at 1kHz. Signal/Noise Ratio—75dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 25V. Size—105 x 50 x 25mm.

Price \pounds 6.82 + 85p VAT. P. & P. free



HY120 60W into 8 Ω


The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: very low distortion; integral heatsink; load line protection; thermal protection; five connections; no external components.

APPLICATIONS: hi-fi; high quality disco; public address; monitor amplifier; guitar and organ.

SPECIFICATION: Input Sensitivity—500mV. Output Power—60W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 60W at 1kHz. Signal/Noise Ratio—90dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 35V. Size—114 x 50 x 85mm.

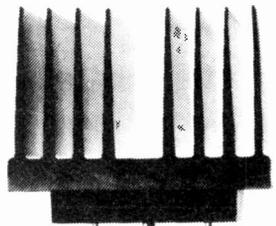Price \pounds 15.84 + \pounds 1.27 VAT. P. & P. free



HY200 120W into 8 Ω


The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

FEATURES: thermal shutdown; very low distortion; load line protection; integral heatsink; no external components.

APPLICATIONS: hi-fi; disco; monitor; power slave; industrial; public address.

SPECIFICATION: Input Sensitivity—500mV. Output Power—120W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.05% at 100W at 1kHz. Signal/Noise Ratio—96dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 45V. Size—114 x 50 x 85mm.

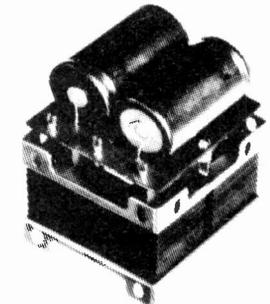Price \pounds 23.32 + \pounds 1.87 VAT. P. & P. free



HY400 240W into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: thermal shutdown; very low distortion; load line protection; no external components.

APPLICATIONS: public address; disco; power slave; industrial

SPECIFICATION: Output Power—240W R.M.S. into 4 Ω . Load Impedance—4-16 Ω . Distortion—0.1% at 240W at 1kHz. Signal/Noise Ratio—94dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 45V. Input Sensitivity—500mV. Size—114 x 100 x 85mm.

Price \pounds 32.17 + \pounds 2.75 VAT. P. & P. free

POWER SUPPLIES: **PSU36**—suitable for two HY30s \pounds 5.22 + 65p VAT. P. & P. free. **PSU50**—suitable for two HY50s \pounds 6.82 + 85p VAT. P. & P. free. **PSU70**—suitable for two HY120s \pounds 13.75 + 1.10 VAT. P. & P. free. **PSU90**—suitable for one HY200 \pounds 12.65 + \pounds 1.01 VAT. P. & P. free. **PSU100**—suitable for two HY200s or one HY400 \pounds 23.10 + \pounds 1.85 VAT. P. & P. free.

I.L.P. Electronics Ltd., Crossland House, Nackington, Canterbury, Kent CT4 7AD

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please supply

Total Purchase price

Enclose: Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

Signature

Registered office No. 1032630

TV GAMES IN FULL COLOUR



AY-3-8500-£6.30. Black and White TV games kits—Standard model £11.95. Economy model £6.95. Colour TV games kits—Standard £19.45. Economy £14.45. Colour Generator Kit adds colour to most black and white games £7.50. Rifle Kit £4.95. Send s.a.e. for giant data.

NEW COMPONENT SERVICE

Resistors 5% Carbon E12 10 to 10M 1/4W 1/2p. 1W 3p. Preset pots miniature 0.1W 100Ω to 4M7 9p. Potentiometers 1/4W 4K7 to 2M2 log or lin. Single 30p. Dual 95p. Polystyrene capacitors E12 63V 22pf to 8200pf 3/4p. Ceramic capacitors 50V E6 22pf to 47000pf 3p. Polyester capacitors 250V E6 0.1 to 1.1mf 5/4p. 15, 22, 33mf 7p. 47mf 11p. Electrolitics 50V .47, 1, 2mf 5p. 25V 5, 10mf 5p. 16V 22, 33, 47mf 6p. 100mf 7p. 220, 330mf 9p. 470mf 11p. 1000mf 18p. Zener diodes 400mW E24 3V3 to 33V 8/4p.

MAINS TRANSFORMERS

6-0-6V 100mA 94p. 9-0-9V 75mA 94p. 0/12/15/20/24/30V 1A £3.85. 12-0-12V 50mA 94p. 0/12/15/20/24/30V 2A £5.15. 6-3V 1 1/2A £2.30. 6-0-6V 1 1/2A £2.75. 9-0-9V 1A £2.39. 12-0-12V 1A £2.69. 15-0-15V 1A £2.89. 30-0-30V 1A £3.59.

PRINTED CIRCUIT MATERIALS

50 sq in pcb 40p. 1 lb FeCl £1.05. Etch resist pens—Economy type 45p. Dalo type 83p. Small drill bit 20p. Laminate cutter 75p. Etching dish 68p.

S-DECS AND T-DECS*

S-DeC £2.23. T-DeC £3.98. u-DeCA £3.97. u-DeCB £6.67. IC carriers with sockets—16 diel £1.91. 10T05 £1.91.



SINCLAIR CALCULATORS AND DVM*

Cambridge scientific programmable £13.95. Prog. library £4.95. Cambridge scientific £8.45. Oxford scientific £10.60. mains adaptors £3.20. PDM35 digital multimeter £26.95.

BATTERY ELIMINATOR BARGAINS

TV GAMES POWER UNIT
Stabilised 8 1/2V 100mA £3.35.

3-WAY MODELS

With switched output
Type 1: 3/4 1/2V at 100mA £2.60.
Type 2: 6/7 1/2V 300mA £3.30.

100mA RADIO MODELS

With press-stud connectors. 9V £3.45. 6V £3.45. 9V + 9V £5.15. 6V + 6V £5.15. 4 1/2V + 4 1/2V £5.15.

CASSETTE MAINS UNIT

7 1/2V with 5 pin din plug 150mA £3.65.

FULLY STABILISED MODEL £6.40. Switched output of 3/6 7/8 9V 400mA stabilised.

CAR CONVERTORS 12V INPUT

Output 9V 300mA £1.80. Output 7 1/2V 300mA £1.80.

BATTERY ELIMINATOR KITS

Send s.a.e. for free leaflet on range.
100mA radio types with press-stud battery terminals.
4 1/2V £2.10. 6V £2.10. 9V £2.10. 4 1/2V + 4 1/2V £2.50. 6V + 6V £2.50. 9V + 9V £2.50.
Cassette type 7 1/2V 100mA with din plug £2.10.
Transistor stabilised 8-way type for low hum.
3/4 1/2V 9V 12V 15V 18V 100mA £3.20. 1A £6.40.
Heavy duty 13-way types 4 1/2V 6V 7V 8V 11V 13V 14V 17V 21V 25V 28V 34V 42V. 1 Amp £4.85. 2 Amp £7.95.
Car Converter kit. Input 12V DC. Output 6/7 1/2V 9V DC 1A transistor stabilised £1.95.
Stabilised power kits. 3-18V 100mA £3.60. 3-30V 1A £9.95. 3-60V 1A £10.95. 3-60V 2A £13.95.

BI-PAK AUDIO MODULES

S450 tuner £21.95. AL60 £4.86. PA100 £14.95. MK60 audio kit £36.45. Stereo 30 £17.95. SPM80 £3.75. BM180 £5.95. Send s.a.e. for free data.

JC12, JC20, JC40 AMPLIFIERS

JC12 6W IC audio amp with free data and printed circuit £1.95. Also new JC40 20W model with pcb £3.95. Sensational new JC20, 10W integrated circuit amp with pcb £2.95. Send s.a.e. for free leaflet on all 3 models and associated power supply and pre-amp kits.



FERRANTI ZN414

IC radio chip £1.44. Extra parts and pcb for radio £3.85. Case £1. Send s.a.e. for free data.

SWANLEY ELECTRONICS

Dept. PE, PO Box 68, 32 Goldsel Rd., Swanley, Kent. Post 30p. Prices include VAT. Official orders welcome. Overseas customers deduct 7% on items marked * and 11% on others.

SEMI-CONDUCTOR OFFERS ALL FULL SPEC
BC212, BC182, C237, BF197, BC159, 1A1 8p each. RCA 2015 TOS POWER TRANSISTOR (SIM TO 2N3055) 35p. ACY18 18p. BE200 MOTOROLA MRD 3051 PHOTO TRANSISTORS 35p. N. CHANNEL FET'S SIMILAR TO 2N6819 18p. MOSFET SIM. TO 40673 35p. 3N140 MOSFETS 50p. M203 DUAL MATCHED PAIRS MOSFETS SINGLE GATE PER F.E.T. 40p. SL301 DUAL MATCHED PAIR SIL. N.P.N. POWER TRANSISTORS FT 300MHz 30p. INTEL 1024 BIT MOS RAMS 95p. MULLARD BR113 TRIPLE V.A.C. DIODE 35p. MC1310 STEREO DECODER I.C.S. £1.20. TBA001 I.C. AMPS 90p. CD4051 CMOS 50p. MC1303N ST. PREAMP I.C. £1.30. 741 8 PIN D.I.L. 23p. MM5316 CLOCK CHIPS £3.50. 400v 15 amp STUD S.C.R. 75p. 500v 600mA BRIDGE RECS. (EX. EQUIP.) 40p. CV7556 200v 150 amp STUD RECS. £1.25. E.H.T. SIL. REC. 15kV 2.5 mA, 15mm x 5mm 85p. 7812 12v 1A PLASTIC V. REGS. 95p. MIN. NIXIES IIT 5870ST 13 x 6mm fig SIZE 85p. NIXIES IIT GN/9A 13 x 8mm 65p. 0.2" OR 0.125" RED LED'S 12p each. MAN3A 3mm LED DISPLAYS 50p. MONSANTO 4640A 0.3" 7 SEG. C. CATH. DISPLAYS 95p. MICROPHONES—GRUNDIG ELECTRET INSERTS WITH BUILT IN F.E.T. PREAMP £1.50. CRYSTAL MIKE INSERTS 37mm 50p. ELECTRET CONDENSER MIKES 1KQ IMP. WITH STD JACK PLUG £2.85. CASSETTE CONDENSER MIKES WITH 2.5 AND 3.5 JACK PLUGS £2.85. STANDARD CASSETTE MIKES 200 OHM IMPED. WITH 2.5 AND 3.5 JACK PLUGS £1.20. P.A. MIKES MOBILE TYPE 50KQ, THUMB SWITCH £4.20. MORSE KEYS—PLASTIC TYPE 95p. HI-SPEED TYPE ALL METAL £2.25. HI-IMP. PHONES 2KQ £1.65. AERIAL COAX SWITCH 3 POSITION, 3 OUTPUTS, 0-30MHz, 150 watts MAX. USES SO239 SOCKETS £4.95. LOW PASS IN-LINE FILTERS, 30MHz CUT OFF, 50 OHM IMP. £3.30. S.W.R. METER, 50 OHM IMP. WITH POWER SCALE £10.50. XTAL MARKER GEN. 300kHz STEPS TO 60MHz, SUPPLIED WITH XTAL FOR THIS COVERAGE £7.90. CRYSTALS—300kHz HCGU 40p. 4.43MHz C.T.V. XTALS 45p. RELAYS—MIN. SEALED RELAYS ALL 4 POLE CHANGEOVER, 36V (6V DC) 45p. 700Q (24V DC) 55p. MIN. 220V AC SEALED RELAY 2 POLE C/O 45p. 240v AC SEALED RELAY 3 POLE C/O 5 AMP CONTACTS 11 PIN BASE 80p. 12 VOLT 4 POLE N.C. REED RELAY 20p. MOTORS—1.5 TO 6V DC. MODEL 20p. 115v AC MIN. 3 R.P.M. WITH GEARBOX 30p. 240v AC SYNCH. MOTOR 1/5TH R.P.M. 65p. 240v AC SYNCH. MOTOR 1/24TH R.P.M. 65p. BOXES—BLACK A.B.S. PLASTIC WITH BRASS INSERTS AND LID. 75 x 56 x 35mm 40p. 95 x 71 x 35mm 45p. 115 x 95 x 36mm 57p. GREY POTTING BOXES WITH LUGS, 23 x 48 x 23mm 11p. 38 x 52 x 25mm 13p. 60 x 80 x 42mm 28p.

ORDER ADDRESS:

PROGRESSIVE RADIO 51 CHEAPSIDE, LIVERPOOL 2. 051-236 0982.

OSMABET LTD

We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS: Prim 240V a.c.
6.3V 1.5A £2; 3A £3; 6A CT £4.25; 12V 1.5A £2.90; 3A £2.25; 6A CT £3; 18V 1.5A CT £4.25; 24V 1.5A CT £4.25; 3A CT £3; 5A CT £16; 8A CT £15; 12A CT £21; 40V 3A CT £10; 50V 6A CT £21.

TWIN SEC TRANSFORMERS: Prim 240V a.c.
6V 0.6A + 6V 0.6A; 9V 0.4A + 9V 0.6A; 12V 0.25A + 12V 0.25A; 20V 0.15A + 12V 0.15A all at £2.85 each; 15V 0.75A + 15V 0.75A £4; 15V 1.5A + 15V 1.5A £5; 18V 1A + 18V 1A £4.50; 18V 1.5A + 18V 1.5A £5.75; 20V 1.5A + 20V 1.5A £5.75; 12V 4A + 12V 4A £7.50; 25V 2A + 25V 2A £7.50.

MIDGET RECTIFIER TRANSFORMERS: Prim 240V a.c.
6-0-6V 1.5A or 9-0-9V 1A £2.25 each; 12-0-12V 1A or 20-0-20V 0.75A £2.85 each; 9-0-9V 0.3A or 12-0-12V 0.25A or 20-0-20V 0.15A £2 each.

L.T. TRANSFORMERS TAPPED SEC: Prim 240V a.c.
0-10-12-14-16-18V 2A £4; £4.25; 0-12-15-20-24-30V 2A £4.50; 4A £7.50; 0-5-20-30-80V 1A £3.25; 2A £7.50. 0-40-50-60-80-100-110V 1A £7.50.

MAINS TRANSFORMERS: Prim 240V a.c.
250-0-250V 60mA 8 3V 1A £1.85 inc. P & P and VAT.
250V 100mA 6 3V 2A £2.50 inc. P & P and VAT.
23V 0.5A £1.50 inc. P & P and VAT.
110/240V a.c. Auto 20W £2.15 inc. P & P and VAT.

SPEAKER MATCHING AUTO TRANSFORMERS
12V, 3 to 8 or 15, up or down, £2.25 inc. P & P. and VAT.
LOUDSPEAKERS
2 1/2in 8Ω, 2 1/2in 8 or 25Ω, 2 1/2in 8 or 80Ω; 3in 35Ω, 3 1/2in 3, 16 or 80Ω, 7 x 4ins 3, 16, 25 or 80Ω, £2 each. 8 x 5in 4, 8 or 25Ω, £2-70; 8ins 8Ω £2-70 inc. P & P and VAT.

"INSTANT" BULK CASSETTE/TAPE ERASER
Instant erasure of cassettes and tape spool, any diameter, demagnetises tape heads. 200/240V a.c. £8 inc. P & P and VAT.

POWER SUPPLY, TWIN OUTPUT: Prim 240V a.c.
New, ex British manufacture Smoothed d.c. output 20V 1.5A, plus stabilised 15V 100mA, plus 12V a.c. 0.5A, with diagram. £4.75 inc. P & P and VAT.

CONDENSERS
Electrolytic, W/E. 1000/50V 30p; 4700/40V 60p; Paper tubular, W/E. 47/600V, 2/400V, 4/7160V all 25p each (£15 per 1000).
Electrolytic screw terminal 1200/75V 50p.

EDGEWISE LEVEL METERS: Prim 240V a.c.
Size, 19 x 18 x 20mm, 800, £1-35 inc. P & P and VAT.

PRINTED CIRCUITS ETCHING KIT
Make your own PC Boards. Comprehensive commercial kit, instructions. £4 inc. P & P and VAT.

MULTI WAY CABLE, SCREENED PVC COVERED
36 way £3; 25 way 75p; 14 way 50p; 6 way 25p; 4 way 20p; 2 way 10p; 1 way 8p per metre. Fig. 8 stereo twin, £1-25 15 metres.

MINI 3-CORE CABLE. 19/0, 10mm
Ideal for speakers, intercoms, etc. £4.85 inc. P & P and VAT.

TWIN FIG. 8 CABLE
Polarised, 100m. £5-00 inc. P & P and VAT.
All types domestic and commercial cables.
Enquiries invited.

Carriage and VAT EXTRA on all orders

except where otherwise stated.

Callers by appointment only
S.A.E. Enquiries, lists.

46 Kenilworth Road, Edgware, Middx HA8 8YG
Tel. 01-858 9314

TRANSFORMERS—6-0-6V 100mA, 9-0-9V 75mA, 12-0-12V 50 mA 75p each. 12-0-12V 100mA 95p. 12V 500mA 95p. 35V 2A AND 2.5V 2A TOROID £2.75 + 35p P & P. 18v 1 amp RECTIFIED £1.95 + 35p P & P. 25v 2 amp £1.75p + 35p P & P. 0-12-15-20-24-30v 1 amp £3.25 + 35p P & P (2 amp VERSION £4.45 + 35p P & P). 30-0-30v 1A £3.00 + 35p P & P. 25-0-25v 2A £3.95 + 35p P & P. 100 volt LINE TRANSFORMER 15 watts MAX - 0.8-15 £1.80 + 35p P & P. 1 TRIAC XENON PULSE TRANSFORMER 30p. 6MH 3 amp CHOKES 30p. SWITCHES—MIN. TOGGLE, SPST 12 x 6 x 9mm 54p. D.PDT 12 x 11 x 9mm 60p. DPDT CENTRE OFF 12 x 11 x 9mm 75p. 4P 2W SLIDERS 20p. 6P 3W SLIDERS 30p. DPDT C/O SLIDERS 20p. SPST 10 amp ROCKERS 12p. R.S. SINGLE POLE C/O PUSH-BUTTONS 45p. ROLLER MICRO SWITCHES 15p. MIN. MICRO SWITCHES 13 x 10 x 4mm 20p. G.P.O. KEYSWITCH ASSY. 3 SWITCHES 2-3 WAY, 1-2 WAY MULTI-POLE 35p. MIN. PUSH TO MAKE OR PUSH TO BREAK SWITCHES 16 x 6mm 15p. PLESSEY WINKLER STUD SWITCHES 2 BANK, 1 POLE 30 WAY ADJ. STOP 75p. D.P.D.T. MIN. ROCKERS 15p. TAPE HEADS—JAP. CASSETTE MONO 90p. CASSETTE STEREO £3.00. BSR MN1330 1/2 TRACK DUAL IMPEDANCE REC/PLAYBACK 50p. BSR SR990 1/2 TRACK STEREO REC/PLAYBACK £1.95. DSR ASSEMBLIES TWO HEADS 1/2 TRACK REC/PLAYBACK STAGGERED STEREO WITH BUILT IN ERASE PER HEAD £1.20. TAPE HEAD DEMAG 240v AC £1.95.

BUZZERS—GPO TYPE 6-12v 30p. 6-12v HOOTERS 50p. MIN. SOLID STATE BUZZERS 6-9-12 OR 24V 15MA 75p. COMPUTER CAPS—60,000 MFD 30V DC 75p. 14,000 MFD 35V 75p. 20,000 45v (EX. EQUIP.) 40p. POT CORES—ADJ. VINKOR 250-370 MICRO H 20p. 260 OR 500 MILLI HENRY CORES 10p each.

METERS—100-0-100µA LEVEL METERS 75p. STEREO TUNING METERS 100µA PER MOVEMENT £2.75. GRUNDIG BATT. LEVEL METER 1mA 40 x 40mm £1.10. MIN. LEVEL METER 200µA 25 x 15mm 75p. FERRANTI 1mA PANEL METER 55 x 70mm £2.95. FERRANTI PANEL METER 100µA 55 x 70mm £3.50. FERRANTI 600V AC METER £3.95.

BOARDS—G.P.O. BOARD WITH 64, BC107 TYPE TRANSISTORS, 2 REED, 1 MERCURY RELAY ETC. £2.00. + 55p P & P. SINGLE STAGE STEREO PRE-AMP BOARDS MAX 1/P 700 M/V (HI-Z) GAIN 26 DB 40p. 465kHz I.F. PANELS, 6 I.F.'s, 3 TRANSISTORS 30p. BOARD WITH 14 12v N.C. REED RELAYS £2.40. BOARD WITH 6v C/O REED RELAY £1.20.

AEROSOLS—SERVISOL SWITCH CLEANER + LUBRICANT 8ozs 55p. FREEZER 6ozs 50p. GEAR CLEANER & TAR REMOVER 14ozs 85p.

SOLENOIDS—240v AC 45p. 12v DC H DUTY 75p. 240v AC LARGE 25lbs PULL 4" TRAVEL £3.75 + 50p P & P.

POSTAGE 30p UNLESS OTHERWISE SHOWN (EXCESS POSTAGE REFUNDED WITH ORDER). OVERSEAS POST AT COST. VAT INCLUDED IN ALL PRICES.

SOLID STATE DESIGN FOR THE RADIO AMATEUR

by A. R. R. L.

Price £6-10

IC TIMER COOKBOOK by W. G. Jung

Price £7-50

HI FI YEAR BOOK 1978 by IPC

Price £3-65

RADIO & T.V. SERVICING 1976/77 MODELS by R. N. Wainwright

Price £10-25

RADIO DATA REFERENCE BOOK by T. G. Giles

Price £4-10

MICROPROCESSORS & SMALL DIGITAL COMPUTER SYSTEMS FOR ENGINEERS & SCIENTISTS by G. A. Korrn

Price £19-00

MASTER TRANSISTOR/IC SUBSTITUTION HANDBOOK by TAB BKS No. 970

Price £5-60

OP-AMP CIRCUIT DESIGN & APPLICATIONS by J. Carr

Price £3-85

INTRODUCTION TO MICROPROCESSORS by D. Aspinall

Price £5-30

HOW TO BUILD & USE ELECTRONIC DEVICES WITHOUT FRUSTRATION, PANIC, MOUNTAINS OF MONEY, OR AN ENGINEERING DEGREE by S. A. Hoenig

Price £7-70

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP


Phone 01-723 4185.

Closed Saturday 1 p.m.

I.C.E. MULTIMETERS

TWICE the information in HALF the size

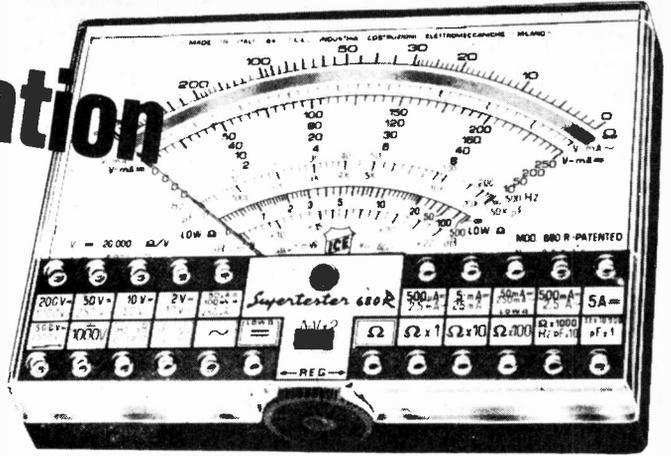The I.C.E. range of multimeters provide an unrivalled combination of maximum performance within minimum dimensions, at a truly low cost. Plus, a complete range of add-on accessories for more ranges, more functions.



Supertester 680R (illustrated)

- * 20kΩ/V, ±1% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- * 80 Ranges - 10 Functions
- * 140 × 105 × 55mm

£25.25 + VAT

(For Mail Order add 80p P&P)

Supertester 680G

- * 20kΩ/V, ±2% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- * 48 Ranges - 10 Functions
- * 109 × 113 × 37mm

£19.95 + VAT

(For Mail Order add 80p P&P)

Microtest 80

- * 20kΩ/V, ± 2% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- * 40 Ranges - 8 Functions
- * Complete with case - only 93 × 95 × 23mm

£14.95 + VAT

(For Mail Order add 80p P&P)

All I.C.E. multimeters are supplied complete with unbreakable plastic carrying case, test leads, etc. and a 50-plus page, fully detailed and illustrated Operating and Maintenance Manual.

Now available from selected stockists. Write or phone for list, or for details of direct mail-order service.




Electronic Brokers Ltd.
49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781

TRAMPUS

A SEMICONDUCTOR POWER HOUSE.
TRAMPUS ELECTRONICS LTD, 58-60 GROVE ROAD, WINDSOR, BERKS SL4 1HB. TELEPHONE WINDSOR (07535) 54523
CALLERS WELCOME MON-SAT 9AM-5PM.
Fast service, on ex stock product, normally 24 hour turn around. Quality devices to manufacturers specifications. Barclay Card & Access by post c. telephone. £5 minimum. Send C.W.O. Add 20p Post and Packing plus 8% VAT to items marked*. 12½% VAT to unmarked items. No minimum order charge for cheque or postal orders. Government Dept. Schools N.M.A. £5 min. order. Free catalogue sale list. Send SAE. Money back if not satisfied. (Prices may change.)

IC's	All price each	TRANSISTORS		FULL SPEC PAKS & E1	
555 DIL 8 Timer	34p*	BC107, 108	7p*	PAK A: 10 x Red LED	£1*
723 Regulator	69p*	BC109	8p*	PAK B: 4 x 741 DIL 8	£1*
741 DIL 8 pin	26p*	BC107, 108, 109 B	15p*	PAK C: 3 x 2N3055	£1*
741 DIL14/TO99	36p*	BC108 or 109 C	15p*	PAK H: 8 x 2N3819e	£1*
747 Dual 741	89p*	BC147/8/9	12p*	PAK K: 40 x 1N814	£1*
748 DIL 14 pin	29p*	BC187/8/9	10p*	PAK N: 25 x OA81/91	£1*
748 DIL 8 pin	49p*	BC177/8/9	20p*	PAK T: 4 x LM301	£1*
7805 plastic or TO3	£1.10*	BC182/3/4 A or L	9p	PAK W: 20 x Electrolytics	£1*
7812 or 15	£1.40	BC212/3/4 A or L	12p	MORE PAKS IN LISTS.	
7803 or 78023	£1.40	BCY70/71/72	20p*	CAPACITORS: Ceramic	5p
8038 Sig. Gen.	£5*	BD131 or 132 each	39p*	Electrolytic 1vt-200V	7p
AY1224 Clock	£2.25*	BFY 50, 51 or 52	20p*	HEATSINKS TO18/TO5	5p*
LM301 DIL 14	29p*	MJ295 (NP)	£1.50*	TO3 Small	29p*
LM301 DIL 8	59p*	MJE2955	£1.40*	Big	89p*
LM309K TO3, 5V	£1*	MJE 3055	55p*	DIL SOCKETS	
LM382 (LM381)	£2	ORP 12 plastic	50p*	Low Profile 8 pin	12p*
LM380/80745	8p	TIP28, 30, 31, 32C	60p*	14 or 16 pin	15p*
LM330/CA3130	95p*	TIP41A or 42A	65p*	VERO All 0.1 in. stocked	
LM3900	75p*	TIP41C or 42C	£1*	2½ x 3½	42p*
MC1310 MPX DR	75p*	TIP2855	65p*	3½ x 5	56p*
NE555 Timer	34p*	TIP3055	55p*	3½ x 17	£2.50
NE558 2 x 555	£1*	T1843 or 2N2646	50p*	21" x 5"	50p*
TBA 910 or 820	£1	2N2904 & 2905	30p*	DIL Board 8" x 4"	£2.44*
LEDs ½" & 2" dia.		2N2907 V/G	15p	POTS 25p PRESETS	8p
Red no clip	11p*	2N3055 115W	45p*	RESISTORS	2p
2" or 209 & clip	19p*	2N3442/472 120V	£1.50*	CMOB: Range in Lists	
Colour LEDs all	19p*	2N3702/3/4/5/6	10p	4009/10	23p*
New Bezel LED Cover	Clip	2N3819e & 23e	18p	4011 20p* 4049/89	23p*
DISPLAYS (Red LED)		2N3820 FET	38p	TTL 7400N SERIES	
0.3" DL704/2	89p*	2N457 low noise	50p	7400 14p*	7485/8610p*
0.3" DL707/2	59p*	INS BUSH SETS	10p	7401 10p*	7490 49p*
0.6" DL747/2 No DP	£1*	MATCHING	Add 20p	7404/5 20p*	7491/2 50p*
TGS 308 GAS D	£5*	DIOIDES OA81/91	5p	7408/10/17p*	7493/5 50p*
390pF Tuning Cap	£1	1N914 & 4148 all	4p*	7408/10/17p*	74107 20p*
Bleeder RS type	£1.49*	1N4001 5p* 4004	7p*	7417/2025p*	74121 33p*
DALO PCB PEN	89p*	BRIDGE 1A 50V	25p*	7430 19p*	74123 39p*
SRBP 6" x 4"	60p*	BZV88 400mW	10p*	7440 15p*	74141 80p*
JKG FERRIC TUB	£1*	ZEMERS 3-30V	10p*	7441 79p*	74157 50p*
PCB etch KIT	£2*	SCR & TRIACS	10p*	7445 49p*	74183 50p*
VU METERS	£1.50*	DISCO TRIAC 10A 400V	£1*	7447 84p*	
		DISCO SCR C108 4A 400V	49p*	7470/72 29p*	
TUNER SALE		SCR 14A 400V	50p*	7473/74 35p*	
MW/LW & FM WITH		1A 600V	89p*	7475 49p*	
MPX DECODER & PUSH		DIAC - ST2	25p*	7476 39p*	
BUTTONS ONLY	£10	BR100	40p*	7480/2/5	10p*
SYNERO 7w AMP	£2.89	Silicon Grease (mini)	25p*		

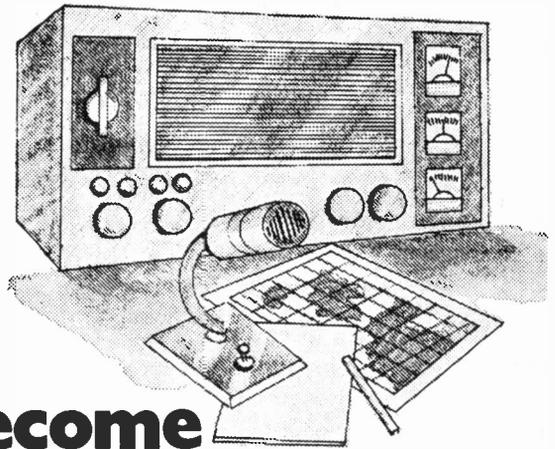

Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free!


Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,
P.O.Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

(Block caps please)

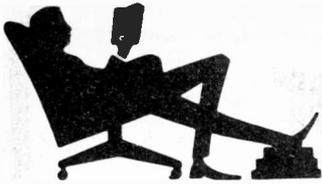

BOOK REVIEWS

HAM RADIO

By K. Ulyett

Published by David & Charles

163 pages, 145 × 225mm. Price £4.50

WITH no mathematics, and only simplified written theory not backed up with diagrams, this hardback really only serves as an introduction at a very general level to ham radio. It begins with a brief history of ham radio activities (world-wide), bringing you up to the present time. Various interesting black and white photographs are included. The book does, however, serve as an excellent insight into the field of interest as a whole, revealing such unexpected aspects as ham television, something which many "outsiders" do not realise exists!

If the numerous call signs and codes associated with ham radio are a complete mystery to you, then the information given in the tables at the back of this book (including international ham prefixes and abbreviations) should reveal all. There is a chapter entitled "Getting A Permit" telling you everything you need to know about this first step, and to further help you into the fraternity, should you be interested, is a list of useful international addresses for both ham radio

and television organisations and societies.

Other information given under the heading "Miscellaneous Data" is various charts covering component identification marks, and frequency band allocations.

M.A.

HOW TO BUILD ADVANCED SHORT WAVE RECEIVERS

By R. A. Penfold

Published by Bernards (Publisher) Ltd

117 pages, 110 × 180mm. Price £1.20

LISTENING to short wave transmission holds a fascination for certain people, and if you wish to discover if this includes yourself, *How To Build Advanced Short Wave Receivers* might be a good starting point!

Proprietary receivers are not cheap, and if you are a constructor, why not build your own? The author proposes that sets with a performance equal to that of commercial equipment are not too difficult to put together, and are certainly a lot cheaper when home made. Also, a greater understanding of the principles involved will result from such activity.

There are no constructional details in the sense of nuts and bolts, but the component manufacturers are given, and physical layout requirements where necessary. Circuit theory is explained on everything in the four chapters, which work upwards from simple sets to those comparable with commercial receivers.

The principles of superhet, a.g.c., i.f., b.f.o. and alignment, are a few of the things you'll be wiser about after reading the book. Stages using f.e.t. devices and varicap diodes are described too.

Chapter Four is called "Add-On Circuits" and covers those extra "odds and ends" such as the "S" Meter, Crystal Calibrator, and Power Supply Unit.

M.A.

Readout — A SELECTION FROM OUR POSTBAG

Readers requiring a reply to any letter must include a stamped addressed envelope. We regret that we cannot answer any technical queries on the telephone.

On The Air

Sir—May I comment on your mention of Citizens' Band Radio in October's PRACTICAL ELECTRONICS, see "Industry Notebook".

The Citizens' Band Association, who are the most powerful CB lobby in Britain, propose a v.h.f. f.m. Citizens' Band using 230–232MHz and having 40 to 80 25KHz channels. Such a service would cause far less spectral pollution than the 27MHz a.m. used elsewhere and

would also provide a welcome boost to the British Radio Industry. Three British firms are already developing sets for use in such a CB service and if the type-approval procedure was arranged to favour domestic sets for the first two or three years we would not need to fear the Japanese.

Our studies suggest that the introduction of CB in Britain would lead to sales of over £150M in the first two years, creating 5,000 direct jobs and up to 10,000 indirect ones and yielding over £30M in VAT and licence revenue. Even

if the Japanese did all the manufacturing (and, as suggested above, this could be prevented) the cost to our balance of payments would be under £70M and the 10,000 indirect jobs and £30M tax revenue would still be created.

If any of your readers would like to support our campaign may I suggest that they contact our membership secretary, Pamela Webster, at 16 Church Road, St. Marks, Cheltenham, Gloucestershire.

J. M. Bryant, President,
Cheltenham.

Instant Wipe

Sir—I noted with interest K. D. Horton's "Wiper Delay Circuit" in your *Ingenuity Unlimited*, September issue, since I have used an almost identical circuit for the past year or so.

However, I have found it an advantage to connect C1 to the 12V switched line instead of 0V (reversing the polarity of course). This gives an immediate sweep of the wipers on switching on.

C. J. Collins,
Letchworth.

BEFORE YOU BUY AN AMPLIFIER MODULE—CHECK:


DOES IT HAVE

- ★ 30A power transistors
- ★ 2-year guarantee
- ★ 3A drivers (100W unit)
- ★ Integral output capacitor

Then compare with the Tamba range—excellent value—25, 50 and 100W R.M.S

TAM1000 100W 4 ohms 65V	£9.80
TAM500 50W 4 ohms 45V	£7.50
TAM250 25W 8 ohms 45V	£5.75

POWER SUPPLIES	
For 1 or 2 TAM250/500	£7.50
For 1 or 2 TAM1000	£9.80
(Carriage 50p on supplies)	

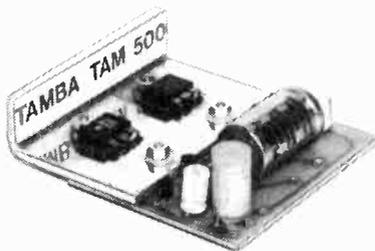

ALL PURPOSE MIXER/PRE-AMP.

(with 60mm slider volume)

- Suitable for multiple input systems
- High and low impedance inputs
- High sensitivity
- Built-in supply smoothing
- 20-20,000 Hz \pm 1dB
- -80dB noise level
- Accepts a wide variety of inputs
- Wide range bass and treble controls

Use up to 10 PRE-AMPS with 1 power supply

Printed circuit board assembly with treble and bass controls plus slider volume control

£6.50

- Suits loads 4-16 ohms
- 20-20,000 Hz \pm 1dB
- Silicon circuitry throughout
- Glass fibre P.C.B.
- High sensitivity (100mV 10k)

- Low distortion (0.1%)
- Low profile (1in high 3½in. x 3in)
- 75% efficient
- Accepts most mixer/pre-amplifiers
- Four simple connections

High grade components used throughout: Texas, Mullard, R.C.A., Plessey, etc.

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s etc)—C.O.D. (60p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50 and 100W systems and at 12½% for 25W systems (including preamp if ordered at same time).

Hours, 9.30 a.m.-5 p.m.
Monday — Saturday.
Callers welcome. Tel. (01) 684 0098

TAMBA ELECTRONICS

Bensham Manor Road Passage, Bensham Manor Road, Thornton Heath, Surrey.



PHOENIX ELECTRONICS

(SOLENT) LTD

46 Osborne Road, Southsea, Hants

All prices include VAT
Include 20p extra for carriage

SOME SEMICONDUCTORS

BC107/8/9	11p
BC177/8/9	15p
BC204/5/6	14p
BC207/8/9	9p
BDY56	£1.72
1N4001	7p
1N4004	10p
1N4148	5p
2N2218/19/21/22	22p
2N2904/5/6/7	24p
2N3442	88p
2N3702-11	12p

RESISTORS

½W carbon film (10)	18p
½W metal film (5)	18p

CAPACITORS

Disc ceramic. Aluminium electrolytic. Tantalum bead.

PANEL HARDWARE

Connectors, lampholders, switches, fuses, knobs.

MISCELLANEOUS

Hand tools, instrument cases, Veroboard, relays, transformers.

SOLDERING EQUIPMENT

Weller and Adcola irons, tips, desoldering tools, instant-heat guns.

INTEGRATED CIRCUITS


DTL 930 series.
TTL 74 series.
Linear series.
Consumer circuits.

Buy More for Less Outlay with Our Bargain Packs

Please send your 1977 catalogue—free!

Name

Address

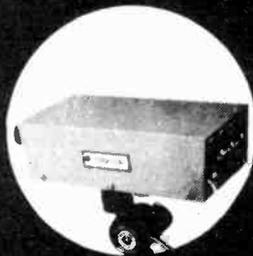

INTRODUCING THE NEW CROFTON C1 CCTV CAMERA



The C1 Camera is a completely new design offering a high specification CCTV camera suitable for both professional and amateur use.

The design offers high sensitivity with good signal to noise ratio by incorporating an F.E.T. front end. Wide range and stable automatic sensitivity control circuit allows camera to be operated in a wide range of lighting conditions. All controls are internal and once set remain stable over long time periods.

Small size and weight make this a most versatile camera for general usage. Special one off retail price including Vidicon (less lens) £140.59 inclusive. Kits also available.

Send S.A.E. for information.

CROFTON ELECTRONICS LTD

Dept. E, 35 Grosvenor Road, Twickenham, Middx. Tel. 01-891 1923

Secondhand cameras and monitors always available

Get a great deal from

Marshall's

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Trade and export enquiries welcome

A. MARSHALL (LONDON) LTD. DEPT. P. E.
LONDON—40-42 Cricklewood Broadway NW2 3ET
 Tel: 01-452 0161. Telex: 21492
LONDON—325 Edgware Rd W2. Tel: 01-723 42473
GLASGOW—85 West Regent Street G2 2QD
 Tel: 041-332 4133
BRISTOL—1 Straits Parade, Fishponds Rd BS16 2LX
 Tel: 0272 654201

CATALOGUE NEW 1977 AUTUMN ★
 COMPLETE BUYERS GUIDE TO ELECTRONICS COMPONENTS
 PRICE 35p POST PAID. 25p FOR CALLERS

TOP 400 SEMICONDUCTORS FROM THE LARGEST RANGE IN THE U.K.

EXPRESS M.O. SERVICE BY RETURN POST—all orders received despatched same day on stock items

Please add VAT to your order. P & P 40p

2N696	0-35	2N3703	0-15	2N6126	0-45	BC159	0-16	BD116	1-20	BF585	0-35
2N697	0-30	2N3705	0-15	40362	0-55	BC161	0-35	BD131	0-51	BF587	0-30
2N699	0-55	2N3706	0-15	40363	1-30	BC167	0-12	BD135	0-37	BF588	0-30
2N706	0-28	2N3707	0-18	40406	0-60	BC168	0-12	BD136	0-37	BF590	0-25
2N705A	0-28	2N3708	0-13	40407	0-52	BC169	0-12	BD137	0-38	BF591	0-25
2N708	0-28	2N3709	0-15	40408	0-75	BC170	0-18	BD138	0-38	BF592	0-20
2N709	0-50	2N3710	0-16	40409	0-75	BC171	0-18	BD243	0-60	BF593	0-24
2N718	0-27	2N3711	0-16	42410	0-75	BC172	0-14	BD140	0-40	BF590	0-20
2N718A	0-20	2N3712	1-20	40411	2-85	BC177	0-20	BD239	0-40	BRY39	0-50
2N720A	0-80	2N3713	2-30	40594	0-80	BC178	0-20	BD240	0-45	BSX20	0-33
2N914	0-35	2N3714	2-45	40595	0-90	BC179	0-23	BD241	0-45	BSX21	0-32
2N916	0-30	2N3715	2-55	40773	0-75	BC182	0-11	BD242	0-50	BU105	1-40
2N918	0-38	2N3716	3-00	AC126	0-45	BC182L	0-14	BD243	0-60	BU202	2-20
2N929	0-25	2N3717	1-95	AC127	0-45	BC183	0-13	BD244	0-65	ME0402	2-20
2N930	0-26	2N3772	2-00	AC129	0-45	BC183L	0-14	BD245	0-65	ME0404	1-15
2N1131	0-30	2N3773	2-90	AC151V	0-40	BC184	0-12	BD246	0-66	ME0412	0-20
2N1132	0-37	2N3789	2-90	AC152V	0-50	BC184L	0-14	BD529	0-45	ME102	1-10
2N1613	0-30	2N3790	3-10	AC153	0-55	BC207	0-16	BD530	0-50	ME104	1-10
2N1711	0-30	2N3791	3-10	AC153K	0-55	BC208	0-16	BD520	1-00	MJ461	1-55
2N2220	0-35	2N3792	3-10	AC127	0-45	BC212	0-14	BF115	0-38	MJ490	1-35
2N2102	0-98	2N3794	2-20	AC176K	0-65	BC212L	0-17	BF121	0-55	MJ491	1-85
2N2218	0-33	2N3795	3-10	AC177K	0-60	BC213	0-14	BF123	0-55	MJ2955	1-25
2N2218A	0-37	2N3820	0-38	AC188K	0-60	BC213L	0-16	BF152	0-25	MJ340	0-58
2N2219	0-35	2N3823	0-80	AD161	1-00	BC214	0-16	BF153	0-25	MJE370	0-58
2N2219A	0-36	2N3824	0-21	AD162	1-00	BC214L	0-17	BF154	0-25	MJE371	0-60
2N2220	0-35	2N3826	0-22	AF106	0-55	BC217	0-16	BF159	0-35	MJE520	0-45
2N2221	0-25	2N4036	0-67	AF109	0-75	BC238	0-12	BF160	0-30	MJE521	0-65
2N2221A	0-26	2N4037	0-55	AF124	0-65	BC239	0-15	BF161	0-60	MJE525	1-50
2N2222	0-25	2N4058	0-20	AF125	0-65	BC251	0-16	BF166	0-40	MJE2955	0-95
2N2222A	0-25	2N4059	0-15	AF126	0-65	BC252	0-22	BF167	0-35	MP8111	0-35
2N2368	0-25	2N4060	0-20	AF139	0-69	BC257A	0-17	BF173	0-35	MP8112	0-40
2N2369	0-25	2N4061	0-20	AF139	0-69	BC257B	0-17	BF177	0-35	MP8113	0-45
2N2369A	0-25	2N4062	0-18	AF200	1-20	BC259B	0-18	BF178	0-25	MP102	3-30
2N2646	0-75	2N4126	0-17	AF233	0-65	BC261A	0-24	BF179	0-30	MPSA05	0-25
2N2647	1-40	2N4289	0-20	AF240	1-14	BC262B	0-24	BF180	0-35	MPSA06	0-25
2N2904	0-36	2N4919	0-65	AF279	0-80	BC263C	0-30	BF181	0-35	MPSA12	0-40
2N2904A	0-37	2N4920	0-75	AF280	0-85	BC300	0-40	BF182	0-35	MPSA25	0-25
2N2905	0-25	2N4921	0-50	AF281	0-85	BC301	0-40	BF183	0-35	MPSA26	0-25
2N2905A	0-28	2N4922	0-55	BC108	0-15	BC303	0-50	BF184	0-38	MPSU05	0-50
2N2906	0-28	2N4923	0-70	BC109	0-15	BC307	0-15	BF185	0-35	MPSU06	0-56
2N2906A	0-35	2N4924	0-60	BC113	0-20	BC308	0-15	BF194	0-15	MPSU55	0-55
2N2907	0-25	2N4925	0-70	BC115	0-20	BC309C	0-15	BF195	0-15	MPSU56	0-60
2N2907A	0-25	2N4926	0-75	BC116	0-19	BC317	0-14	BF196	0-15	TI29A	0-45
2N2924	0-15	2N4927	0-90	BC118	0-20	BC318	0-13	BF197	0-17	TI29C	0-60
2N2925	0-25	2N4928	0-34	BC117	0-22	BC327	0-20	BF198	0-18	TI30A	0-40
2N3019	0-55	2N4929	0-40	BC118	0-20	BC328	0-19	BF200	0-35	TI30C	0-65
2N3053	0-26	2N4930	0-40	BC119	0-30	BC337	0-19	BF225J	0-25	TI31A	0-50
2N3054	0-26	2N4931	0-40	BC121	0-45	BC338	0-21	BF244	0-35	TI31C	0-66
2N3055	0-26	2N4932	0-40	BC132	0-30	BC347	0-12	BF245	0-40	TI32A	0-55
2N3390	0-20	2N4947	0-15	BC134	0-20	BC348	0-10	BF246	0-40	TI32C	0-55
2N3391	0-20	2N4948	0-15	BC135	0-20	BC349	0-13	BF247	0-40	TI33A	0-80
2N3391A	0-20	2N4949	0-19	BC136	0-19	BCY30	1-00	BF255	0-24	TI33C	1-10
2N3392	0-16	2N4957	0-32	BC137	0-20	BCY31	1-00	BF257	0-37	TI34A	0-90
2N3393	0-15	2N4958	0-33	BC140	0-35	BCY32	1-00	BF258	0-45	TI34C	1-00
2N3394	0-15	2N4959	0-29	BC141	0-40	BCY33	1-00	BF259	0-49	TI35A	2-50
2N3439	0-88	2N4964	0-34	BC142	0-40	BCY34	1-00	BF260	0-50	TI35B	2-50
2N3440	0-64	2N4965	0-36	BC143	0-30	BCY38	0-13	BF261	0-50	TI35C	2-50
2N3441	0-81	2N4967	0-60	BC147	0-12	BCY42	0-60	BFS21A	2-60	TI41C	0-90
2N3442	1-35	2N6101	0-45	BC148	0-12	BCY58	0-25	BFS28	1-38	TI42A	0-80
2N3638	0-16	2N6107	0-42	BC149	0-14	BCY59	0-25	BFS61	0-30	TI42C	1-00
2N3638A	0-16	2N6109	0-50	BC153	0-27	BCY70	0-25	BF295B	0-65	TI2955	0-65
2N3639	0-30	2N6121	0-38	BC154	0-27	BCY71	0-25	BF299	0-35	TI3555	0-55
2N3641	0-20	2N6122	0-41	BC157	0-14	BCY72	0-24	BFX30	0-35	TIS43	0-43
2N3702	0-13	2N6123	0-43	BC158	0-14	BD115	0-60	BFX84	0-35		

INTEGRATED CIRCUITS

Please add VAT to your order. P & P 40p

CA320	2-00	LM1800	1-76	TA570	2-30
CA320A	2-20	LM1808	1-92	TA611B	1-85
CA320B	1-29	LM1828	1-75	TA621	2-15
CA320B2	1-01	LM3301N	0-85	TA661A	1-50
CA330	1-35	LM3302N	0-85	TA661B	1-50
CA330A	2-00	LM3401	0-70	TA700	3-91
CA345	1-40	LM3900	0-75	TA930A	1-30
CA346	0-80	LM3905	0-60	TA930B	1-30
CA348	0-23	LM3909	0-68	TA100	1-95
CA349	1-80	MC1035	1-75	TA120	0-75
CA350	2-42	MC1303	1-03	TA400	2-00
CA350A	1-52	MC1304	1-40	TA500	2-21
CA360	0-75	MC1305	1-40	TA500Q	2-30
CA380A	1-68	MC1310	1-91	TA510	2-21
CA386	0-80	MC1327	1-54	TA510Q	2-30
CA388	1-70	MC1330	1-00	TA520	2-21
CA389	2-52	MC1350	0-90	TA520Q	2-30
CA390	4-00	MC1351	1-40	TA530	1-98
CA3130	0-98	MC1352	1-10	TA530Q	2-21
LM301A	0-67	MC1458	1-91	TA540	2-21
LM301N	0-40	NE555	0-40	TA540Q	2-30
LM304	0-25	NE565	1-10	TA550	3-13
LM307N	0-85	NE566	1-30	TA550Q	3-22
LM308C	1-82	NE566B	1-50	TA560Q	3-22
LM308N	0-85	NE567	1-80	TA570	1-28
LM309K	1-85	SAS560	2-50	TA570Q	1-38
LM317	3-00	SAS570	2-50	TA641B	2-70
LM318N	2-26	SQ42P	1-25	TA651	2-20
LM323K	4-48	76001N	1-30	TA700	1-52
LM339N	1-40	76002N	2-20	TA700Q	1-61
LM348	1-50	76008K	1-50	TA720Q	2-30
LM360N	2-75	76013N	1-50	TA750	1-98
LM370N	2-50	76013ND	1-30	TA750Q	2-07
LM371N	1-70	76018K	1-50	TA800	1-25
LM372N	1-70	76023N	1-45	TA810	1-25
LM380C	1-82	76023N	1-56	TA820	1-25
LM374N	1-10	76033N	2-20	TA820Q	2-90
LM377N	1-75	75110N	1-18	TA820Q	2-99
LM378N	2-25	76115N	1-51	TA840	1-62
LM379S	0-95	76116N	1-66	TA840Q	1-85
LM380-8	0-90	76131N	1-20	TA850	1-62
LM380N	0-98	76226N	1-50	TA850Q	1-61
LM381A	2-45	76227N	2-20	TA880A	1-25
LM381N	1-60	76228N	1-45	TA890A	3-13
LM382N	1-25	76530N	0-71	TA890Q	1-84
LM384N	1-45	76532N	1-40	TA890Q	3-22
LM386N	0-80	76533N	1-20	TA890Q	3-22
LM387N	0-75	76544N	1-44	TA890Q	3-22
LM388N	1-00	76545N	1-65	TA890Q	3-22
LM389N	1-00	76546N	1-44	TA890Q	3-22
LM702C	0-75	76550N	0-35	UA170	2-00
LM709C	0-65	76552N	0-55	UA180	2-00
LM709N	0-45	76570N	1-58		
LM710C	0-60	76620N	0-90		
LM710N	0-80	76620N	1-10		
LM723C	0-75	76660N	0-92		
LM723N	0-85	76666N	0-60		
LM741C	0-65	TA320A	2-48		
LM741N	0-40	TA351A	1-00		
LM747N	0-80	TA522	1-90		
LM748-8	0-55	TA550	6-00		
LM748N	0-55	TA560	1-75		




Handy size Reels and Dispensers

**OF THE WORLD'S FINEST CORED SOLDER TO DO
A PROFESSIONAL JOB AT HOME**

Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.

SAVBIT

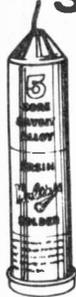

handy solder dispenser

Contains 2-3 metres approx. of 1.22mm Ersin Multicore Savbit Solder. Savbit increases life of copper bits by 10 times.

Size 5 58p

For soldering fine joints

Two more dispensers to simplify those smaller jobs. PC115 provides 6-4 metres approx. of 0.71mm solder for fine wires, small components and printed circuits.

PC115 69p

Or size 19A for kit wiring or radio and TV repairs. 2-1 metres approx. of 1.22mm solder.

Size 19A 63p



handy size reels of **SAVBIT, 40/60, 60/40 and ALU-SOL** solder alloys

These latest Multicore solder reels are ideal for the toolbox. Popular specifications cover all general and electrical applications, plus a major advance in soldering aluminium. Ask for a free copy of 'Hints on Soldering' containing clear instructions to make every job easy.

Ref.	Alloy	Diam. (mm)	Length metres approx.	Use	Price
Size 3	40/60 Tin/Lead	1.6	10.0	For economical general purpose repairs and electrical joints.	£2.16
Size 4	ALU-SOL	1.6	8.5	For aluminium repairs. Also solders aluminium to copper, brass etc.	£2.46
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits.	£2.16
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold.	£2.16



BIB WIRE STRIPPER and CUTTER

Fitted with unique 8-gauge selector and handle locking device. Sprung for automatic opening. Strips flex and cable in seconds.

Pat. No. 1443913

Model 8B 97p

SOLDER-WICK



Absorbs solder instantly from tags, printed circuits etc. Only needs 40-50 watt soldering iron. Quick and easy to use. Non-corrosive.

Size 18 97p


Sole U.K. Sales Concessionaires:

Bib Hi-Fi Accessories Limited,

Kelsey House, Wood Lane End, Hemel Hempstead, Herts. HP2 4RQ

Prices shown are recommended retail, inc. VAT. From electrical and hardware shops. In difficulty send direct, plus 20p P. & P. Prices and specifications subject to change without notice.

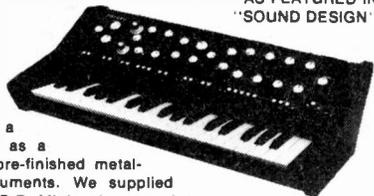The **Amazing Mk. 2 MINISONIC** IS HERE TO STAY



AS FEATURED IN "SOUND DESIGN"

A sound investment and a pleasure to build, available as a complete kit, module kits, pre-finished metal-work kit or complete instruments. We supplied components for the original P.E. Minisonics, now let us supply yours.

Send S.A.E. for full price structure.

Kits for the P.E. Sound Synthesiser are still available.

BUY FROM THE SPECIALISTS . . .

EATON AUDIO

P.O. Box 3 (6 Jutland Rise)
St. NEOTS, CAMBS. PE19 3JB

TERMS: MAIL ORDER ONLY, C.W.O. MINIMUM ORDER £1. VAT: Please add 12½% to value of order inc. P. & P. unless otherwise stated. Cheques or P.O.s payable to Eaton Audio. Orders over £5 free of P. & P., otherwise please add 10p in the £1. Callers by appointment only.

STOCK CLEARANCE BARGAINS!!

We are proud and privileged to announce that we have been appointed to dispose of the surplus stock requirements of a major

PROFESSIONAL EQUIPMENT MANUFACTURER

All these first grade, top specification devices are available for immediate delivery by means of our

FAST-RETURN DELIVERY SERVICE

check our prices:-

BC1841C	0.09	CA741G	0.23	100nF	0.035
BC2141C	0.10	LM301	(high rel) 0.34	470nF	0.08
(low noise select)		CA3900	0.65	10uF 16V	0.035
BF244B	0.25	IN4148	0.03	10uF 35V	0.04
BFR39	0.30	IN4002	0.06	6800uF 63V	1.40
2N1132	0.21	1A Bridge	0.22	10 for	0.15
2N3953	0.17	10A Bridge	1.30	100 for	0.98
2N3053	0.45	33pF	0.025	6W 0.33ohm	0.20
2N5415	0.55	3n3	0.03	Wirewound	
2N6254	0.95	4n7	0.03	Mono jack sckt	0.21
(150W 85V)		15nF	0.035	Stereo jack sckt	0.30
		33nF	0.035	TTL 220 LED	0.15

Full component lists available on request. For further details please send SAE to:-

aea

4 Greens Road,
CAMBRIDGE CB4 3EF.
(0223) 54093.

For Semi-Conductors

including
Small Signal Transistors
Power Semi-conductors
TTL, CMOS, I.C.s
Linear I.C.s
Signal and Power Diodes
Zener Diodes
Magneto Resistors
Hall-effect devices
Magnetic Proximity Switches
Opto-electronic devices

Go to

ELECTROVALUE

TO MAKE THE BEST OF

For passive components

including
Plastic Film Capacitors
Electrolytics
Semi-precision capacitors
Transformers
Pot Cores
R. M. Cores
Ring Cores, etc.

Go to

ELECTROVALUE

THE PROJECTS YOU BUILD

The Open Door to Quality

It's the Electrovalue Catalogue No. 8 (4th edition black and white cover) with completely up-dated prices. 144 pages, well illustrated. 40p post free with 40p voucher usable on orders for £5 or more. Send for yours now and order in confidence.

GOODS SENT POST FREE IN U.K. FOR C.W.O. ORDERS. Keenly competitive prices plus **ATTRACTIVE DISCOUNTS** and only best quality goods.


ELECTROVALUE LTD

(Dept. PE11) 28 St. Jude's Road, Englefield Green,
Egham, Surrey TW20 0HB.
Tel. Egham 3603. Telex 264475.
North: 680 Burnage Lane, Burnage, Manchester.
Tel. (061) 432 5945



Half Price Christmas Offer


MR. BLOBS

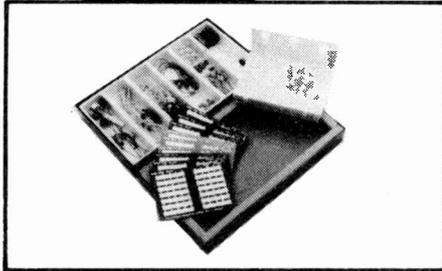

S - Decnology
Build all the projects on the S-DeC

The perfect kit for beginners, students, professionals and all users of discrete components. This S-DeC-IT contains 1 S-DeC + control panel, 9 Blob-Boards, 20 double ended Leads + Instruction book S-DeC-IT complete in ABS box, with component tray.

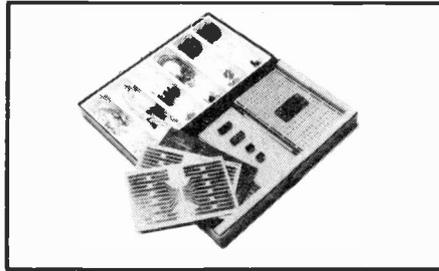
Normally £6.38
HALF PRICE OFFER £3.19 + £1.00 post and VAT



T-Decnology
Build projects using ICs on your T DeC

This De-K-It contains 1 T-DeC + control panel + 1 16 Dil Carrier + 4 Blob-Boards + components + Circuit Diagrams and step by step instructions to build Burglar Alarm Sound Fuzz Circuit, SR Latch, and Two Tone Siren Complete Kit with Components

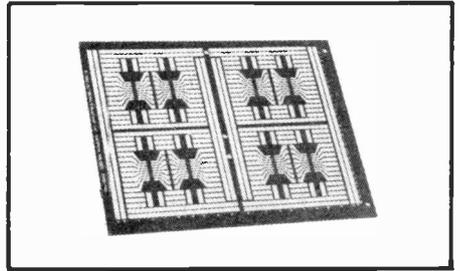
Normally £13.00
HALF PRICE OFFER £6.50 + £1.20 post & VAT



BLOB BOARD CHRISTMAS PACK

Includes
8 IC for doing Digital Electronics by Experiment
5D for doing S DeCnology
8D for doing Blob-a-Job

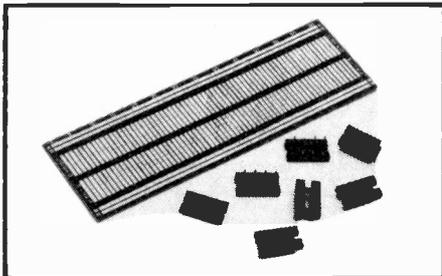
Normally £3.00
HALF PRICE OFFER £1.50 + 40p post and VAT



BRED-CIRCUIT BOARD
Combines versatility of Breadboard with usefulness of Blob-Board

BCB2 board size 6" x 2" with 5 16 DIL Sockets
Pack of 3 boards with 15 sockets

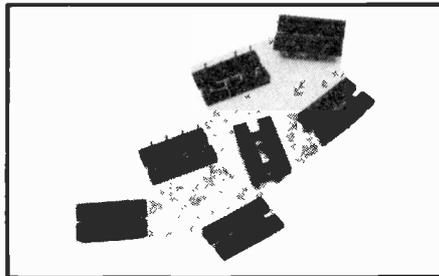
normally £3.84
ONLY £1.92 + 50p post & VAT



SOCKETS

16 DIL IC Sockets with stepped legs

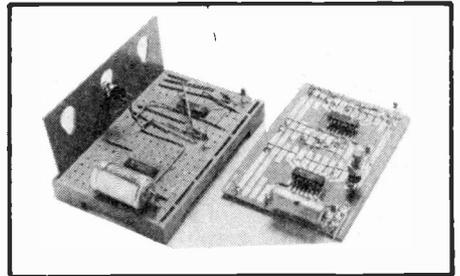Normally 20p each
Pack of 20 for only £2.00 + 35p Post and VAT



I.C. BREADBOARD

U DeC B Breadboard + 21 2 IC Blob Boards

Normally £14.00
HALF PRICE OFFER £7.00 + £1.30 post & VAT



TO MR. BLOB  Electronics (Scotland) Ltd, 9 Radwinter Road, Saffron Walden, Essex, CB11 3HU

Please rush me:

..... S-DeC-ITs at £3.19 each
+ £1.00 post & VAT
..... T-DeC-ITs at £6.50 each
+ £1.20 post & VAT
..... Blob Board packs at £1.50
each + 40p post & VAT

..... Bred Circuit Board +
Socket Packs at £1.92 each + 50p post &
VAT
..... Pack of 20 sockets at £2.00
+ 35p post & VAT
..... U DeC B + 21 off 2 IC Blob
Boards at £7.00 each + £1.20 post & VAT

We wish you a Happy Christmas

and suggest that one of the best ways
to ensure it is to treat yourself to a
Home Radio Components Catalogue.

Only £1.40 including p.&p.
The best Christmas present you
could buy - for yourself or for
any of your electronics
friends or relations.



SEND THE
COUPON
TODAY

Please write your Name and Address in block capitals

NAME _____

ADDRESS _____

HOME RADIO (Components) LTD. Dept. PE
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd No
517088 London

POST THIS COUPON
with cheque or P.O. for £1.40

T.T.L. 74 I.C.'s By TEXAS, NATIONAL, I.T.T., FAIRCHILD etc

7400	14p	7426	25p	7473	30p	74121	25p	74151	65p	74179	140p
7401	14p	7427	25p	7474	30p	74122	40p	74153	65p	74180	100p
7402	14p	7428	25p	7475	30p	74123	60p	74154	120p	74181	200p
7403	14p	7430	15p	7476	30p	74125	50p	74155	70p	74182	75p
7404	14p	7432	25p	7483	85p	74126	50p	74156	70p	74184	150p
7405	14p	7437	25p	7485	100p	74130	30p	74157	70p	74185	150p
7406	40p	7438	25p	7486	30p	74131	100p	74180	90p	74188	350p
7407	40p	7440	15p	7489	250p	74132	65p	74161	90p	74189	350p
7408	20p	7441	65p	7490	35p	74135	100p	74162	90p	74190	140p
7409	20p	7442	65p	7491	75p	74136	90p	74163	90p	74191	140p
7410	15p	7445	80p	7492	45p	74137	100p	74164	125p	74192	120p
7411	20p	7446	65p	7493	40p	74138	125p	74165	125p	74193	120p
7412	20p	7447	75p	7495	60p	74139	100p	74166	125p	74194	100p
7413	30p	7448	70p	7496	70p	74141	80p	74167	325p	74195	100p
7414	60p	7450	15p	74100	95p	74142	270p	74170	290p	74196	100p
7415	30p	7451	15p	74104	40p	74143	270p	74173	150p	74197	100p
7417	30p	7453	15p	74105	40p	74144	270p	74174	100p	74198	185p
7420	15p	7454	15p	74107	30p	74145	75p	74175	75p	74199	185p
7422	20p	7460	15p	74109	50p	74147	230p	74176	100p		
7423	25p	7470	30p	74118	90p	74148	160p	74177	100p		
7425	25p	7472	25p	74120	90p	74150	120p	74178	140p		

CMOS

4000	20p	4030	60p
4001	20p	4032	150p
4002	20p	4043	220p
4006	120p	4046	150p
4007	20p	4047	115p
4009	70p	4049	70p
4011	20p	4050	50p
4012	20p	4054	130p
4013	55p	4055	140p
4015	90p	4056	145p
4016	50p	4060	130p
4017	110p	4065	55p
4018	250p	4069	30p
4021	140p	4071	30p
4022	180p	4072	30p
4023	20p	4081	20p
4024	100p	4082	30p
4025	20p	4510	145p
4026	200p	4511	200p
4027	85p	4516	140p
4028	155p	4518	110p
4029	130p	4528	130p

SPECIAL OFFERS

IN418 100 for £1.50
555 Timers 35p each
(100 for £30.00)
741 op. amps. 25p each
(100 for £20.00)
7410 I.C.'s 10 for £1.00
(100 for £9.00)

PLEASE NOTE ALL
PRICES INCLUDE
POSTAGE AND VAT
AT 8% OR 12% AS
APPROPRIATE

MULLARD POT CORES

LA3 100-500kHz 75p
LA4 10-30kHz 100p
LA5 30-100kHz 100p
LA7 10kHz 100p
LA13 for W.W. Oscillo-
scope 200p

WIRE WOUND RESISTORS BY VTM

5K 9 Watts
10 for £1.00
100 for £6.00
1,000 for £50.00
10,000 for £400.00


XEROZA RADIO

306 ST. PAUL'S ROAD,
HIGHBURY CORNER, LONDON N.1

Telephone: 01-226 1489

Easy access to Highbury via Victoria Line (London Transport) British Rail

SUPERSOUND 13 HI-FI MONO AMPLIFIER

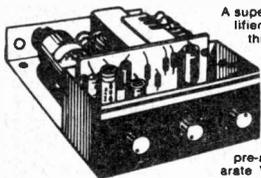

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30kHz ± 3db. Fully integrated pre-amplifier stage with separate volume. Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep. AC 200/250V. PRICE £15.00 P. & P. £1.20.

HARVERSONIC MODEL P.A. TWO ZERO



An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram., etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1-5mV into 47k. Input 2-5mV into 47k (suitable for use with mic. or guitar etc.). Input 3 100mV into 1 meg. suitable for gram. tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240 volts. Size approx. 12in. wide x 5in high x 7in deep. Special introductory price £28.00 + £2.50 carriage and packing.

Mullard LP1159 RF-IF module 470 kHz £2.25 + P. & P. 20p Full specification and connection details supplied
Pye VHF/FM Tuner Head covering 88-108 MHz. 10.7 MHz I.F. output. 7.8V - earth. Supplied pre-aligned, with full circuit diagram with precision-ganged F.M. gang and 323PF + 323PF A.M. Tuning gang only £3.15 + P. & P. 35p.

STILL AVAILABLE
HA34 3 Valve Audio Amp. 4jw o/p. Ready built and tested £8.50 + £1.40 P. & P.
Also HSL "Four" Amp. Similar to above but in kit form. £8.00 + £1.40 P. & P.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State F.M. A.M. Stereo Tuner. Covering M.W. A.M. 540-1605kHz V.H.F. F.M. 88-108MHz.
Built-in Ferrite rod aerial for M.W. Full AFC and AGC on A.M. and F.M. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set finish cabinet. Will match almost any amplifier. Size 8in wide x 4in high x 9in deep approx.

Limited number only at £28.00 + £1.50 P. & P.

Push Button Switch bank. 8 buttons giving 16 S/P C/O interlocked switches plus 1 Cancel Button plus 3 D/P C/O. Overall size 6in x 2in x 1in. Supplied complete with chrome finished switch buttons 2 for £1.80 + 20p P. & P.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 25p + S.A.E. (Free with parts). All parts sold separately. ONLY £13.50 P. & P. £1.40. Also available ready built and tested £18.00 P. & P. £1.40.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 1 1/2in x 1 1/2in x 1 1/2in deep. Weight 19oz. Power handling 20W R.M.S. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffles. Send S.A.E. for full details. Only £8.40 each + P. & P. (one 90p, two £1.10). Now available in either 8in round version or 4 1/2 x 8in rectangular. 10 watts R.M.S. 60Hz-20kHz £5.25 + P. & P. (one 85p, two 75p.).

SPECIAL OFFER. 6in long throw, roll surround, ceramic magnet 8 ohm 10 watt speaker chassis. Specially suitable for HI FI. £3.95 + 75p P. & P.

2in PLASTIC CONE HF TWEETER 4 ohm, £3.50 per matched pair + 50p P. & P.

HIGH POWER HI-FI 8 ohm Dome Tweeter. 1in voice coil. Magnet size 3in dia. Suitable for use in up to 50 watt systems. £4.50 each + 60p P. & P.

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts R.M.S. per channel into 8 ohms. Frequency response ±3dB 12-30,000Hz. Sensitivity: better than 80mV into 1mΩ. Full power bandwidth: ±3dB 12-15,000Hz. Bass boost approx. to ±2dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1A overall size 12in wide x 8in deep x 2 1/2in high.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT (including 14 transistors) £13.50 P. & P. 80p (Magnetic input components 33p extra)

POWER PACK KIT £5.50 P. & P. 95p

CABINET £5.50 P. & P. 95p

SPECIAL OFFER—only £23.75 if all 3 items ordered at one time plus £1.25 P. & P.

Full after sales service

Also available ready built and tested £31.25 P. & P. £1.50

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets and 5 pin din tape rec./play socket are mounted on the printed circuit panel. Size approx. 9in x 2in x 1in max. depth. Supplied brand new and tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically), at only £9.00 + 50p P. & P. Mains transformer with an output of 17V a.c. at 500mA can be supplied at £1.50 + 40p P. & P. if required. Full connection details supplied.

STEREO DECODER

SIZE 2" x 3" x 1/2" ready built. Pre-aligned and tested for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6.00 plus 20p P. & P. Stereo beacon light if required 40p extra.

Open 9.30-5.30 Monday to
Friday. 9.30-5 Saturday
Closed Wednesday.
Prices and specifications correct
at time of press. Subject to
alteration without notice

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES
QUOTED APPROPRIATE. ONLY
P. & P. ON OVERSEAS ORDERS
CHARGED EXTRA.

MICROSYSTEMS '78 MICROSYSTEMS '78 MICROSYSTEMS '78

SEMINAR & EXHIBITION

West Centre Hotel, London

February 8 9 10 1978

Sponsored and organised by IPC Business Press

Keeping in touch with a fast developing technology like microelectronics can be difficult. And, like jumping on a moving train, the initial contact can be hazardous, if not actually painful.

That's why a unique line-up of IPC Business Press journals have got together. To organise three days of talks and presentations plus an exhibition which will give you a chance to come to grips with the new technology of microsystems.

That means not just microprocessors, but also interfaces, peripherals and software. Everything, in fact, which is needed to transform a microprocessor into an operational system.

So climb on board Microsystems '78. To learn more about the world's fastest moving technology. Without being thrown off balance or having the door slammed in your face.

We can think of lots of reasons why you should attend Microsystems '78. But we'll give you just eight of them

Electronics Weekly

COMPUTER WEEKLY

data
processing

microprocessors

Electrical Times

ELECTRON

electrical review

wireless
world

All top journals in their fields and all sponsors of Microsystems '78. Need we say more? Except please complete and return the coupon.

I am interested in Microsystems '78.

Please send me details of the seminar programme, when finalised.

I would like to submit a paper to be delivered at Microsystems '78.

My company is interested in participating in Microsystems '78 as an exhibitor.

My company would like to make an industry presentation at Microsystems '78.

(Please tick the appropriate box):

Name _____

Job Title _____

Company Name _____

Company Address _____

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

- * **SAVE ON TIME** - No delays in waiting for parts to come or shops to open!
- * **SAVE ON MONEY** - Bulk buying means lowest prices - just compare with others!
- * **HAVE THE RIGHT PART** - No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES - SENT BY RETURN OF POST. VAT INCLUSIVE PRICES

K001 50V ceramic plate capacitors. 5%. 10 of each value 22pF to 100pF. Total 210, £3.35

K002 Extended range, 22pF to 0.1µF. 330 values £4.90

K003 Polyester capacitors. 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for £4.75
K004 Mylar capacitors, min 100V type, 10 each all values from 1000pF to 10,000pF. Total 130 for £4.45

K005 Polystyrene capacitors. 10 each value from 10pF to 10,000pF. E12 series 5% 160V. Total 370 for £12.30

K006 Tantalum bead capacitors. 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25 15/16 22/16 33/10 47/6 100/3. Total 170 for £14.20

K007 Electrolytic capacitors 25V working, small physical size. 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.50

K008 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for £5.90

K021 Miniature carbon film 5% resistors, CR25 or similar. 10 of each value from 10R to 1M. E12 series. Total 610 resistors, £6.00

K022 Extended range, total 850 resistors from 1R to 10M £8.30

K041 Zener diodes. 400mW 5%. BZ88 etc. 10 of each value from 27V to 36V, E24 series. Total 280 for £15.30

K042 As above but 5 of each value £8.70

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.15.

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs. 1lb £1.00; 3lb £2.18; 10lb £5.80; 100lb £39.00

SIRENS

Work off 4 x HP7 batteries, emit very loud noise. Overall size 110 x 75 x 60mm. Use as Burglar Alarm in car, house, workshop etc. ONLY £1.95.

VIDEO OFFSETS

Pack A. All 0.1"

Pack B. All 0.15"

Pack C. Mixed

Pack D. All 0.1" plain

Each pack contains 7 or 8 pieces with a total area of 100 sq in. Each pack is £1.30. Also available by weight. 1lb £3.45, 10lb £31.

VEROCASES

Plastic top and bottom, ally panels front and back.

Type	Price
1410 205 x 140 x 40mm	£3.70
1411 205 x 140 x 75mm	£4.17
1412 205 x 140 x 110mm	£5.20
1237 154 x 85 x 40mm	£2.83
1238 154 x 85 x 60mm	£3.05
1239 154 x 85 x 80mm	£3.75

TRANSFORMERS

Special - 12V 8A for only £4.00. 6-0-6V 100mA 85p; 9-0-9V 75mA 85p; 12-0-12V 50mA 85p; 100mA 95p; 12-0-12V 1A £2.90; 20-0-20V 2A £4.70; 20V 2.75A £4.

VERO PLASTIC BOXES

Professional quality, two tone grey polystyrene with threaded inserts for mounting PC Boards.

Type	Price
2518 120 x 65 x 40mm	£2.24
2520 150 x 80 x 50mm	£2.68
2522 188 x 110 x 60mm	£3.72

Sloping front versions:

Type	Price
2523 220 x 174 x 100/52mm	£6.90
1798 171 x 121 x 75/37.5mm	£4.85

Gen. purpose plastic potting box 71 x 49 x 24. In black or white 40p. Hand controller box, shaped for ease of use in the hand, 94 x 61 x 23mm 64p.

S-DECS & T-DECS

S-DEC Breadboard	£2.10
T-DEC Breadboard	£3.75

RELAYS AND SOLENOIDS
12V DC enclosed, 2 10A c/o contacts £1.00

Open construction relay with 2 10A c/o contacts, coil rated 24V AC, but works well on 6V DC 60p

240V AC enclosed, 11 pin plug in base. 3 10A c/o contacts. £1.20

240V AC open, 2 15A c/o contacts £1.50

6V miniature low profile for PC mounting, 0.1" pitch 2 pole c/o 137R coil - RS price £2.71 - our price £1.00

Solenoid, rated 48V DC, but work on 24V. 10mm push or pull action. Single hole fixing. Size 27 x 18 x 15mm. Made by Varley. Only 40p.

1977/8 CATALOGUE NOW AVAILABLE - MUCH BIGGER AND BETTER, WITH 50p DISCOUNT VOUCHERS. ONLY 30p plus 15p POST.

WIRE AND FLEX

Flex pack - 5m of 5 diff colours, thick or thin. 25m for 25p. 25 way (14/0076) cable with braided overall screen and PVC sheath. 40p/m.

POWER PACK

Wood grained metal case 90 x 80 x 75mm containing mains transformer giving 6V at 200mA, 2 co-ax sockets, PC board with 1 1/2 fuseholder R's C's etc. Only £1.

EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold plated connectors enables us to offer them at less than 1/3rd their original list price! 18 way 41p 21 way 47p 32 way 72p 40 way 90p 43 way 97p 49 way 111p.

SOLAR CELLS

As used on space labs etc., these tiny cells give 50µA at 0.5V in sunlight. Ideal for powering small C-MOS projects etc. Can be banked for greater power output. Size 19 x 6.5mm. 3 for £1; 10 for £3; 25 for £7; 100 for £25.

SCH PANEL

Has 12 60V 0.8A thyristors (gate current only 200µA), MEU21, 2N3904, 1N4004 x 14, + R's C's etc. Only £4.00.

MISCELLANEOUS IC's

All supplied with data.
MC3302 Quad comparator £1.20.
ITT7105 LED Digit driver, 8 for £1.
710 TO99 case Diff. comparator, MC1469R Voltage reg. £1.50.
ZN1034E Precision timer £2.25.
LM1303 Dual stereo preamp £1.40.
733 Diff. video amp £1.20. LM301 Op amp 40p. ITT326 2 x 2 & 2 x 3 1/2 TTL NAND gate, 10 for £1. SLD2128 Dual 128 bit static shift reg. £1.50.

Our retail shops at 21 Deptford Broadway, London, SE8 (01-892 2009) and 38 Lower Addiscombe Road, Croydon (01-888 2950) stock some of the advertised goods for personal callers only. Ring them for details.

All prices quoted include VAT and UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

QUALITY FOR CHRISTMAS

Superb CASIO watches - probably the best value for money available today. Constant LCD display of 7 functions plus night light, plus automatic calendar, plus STOPWATCH to 13 hours and, except 31QR-12B, plus DUAL TIME ZONE. The all stainless steel cases are WATER RESISTANT to 100ft. (3at) Mineral glass faces. Not illustrated: As above but ultra-slim (1/2") on bracelet, 31CS-10B £59.95. On strap, 31CS-15L, £49.95. LADIES CASIO. Five models, as above but without dual time zone. Prices from £29.95 to £79.95.




21QS-10B (ST, TM) 9.6 mm £34.95



31QR-12B (ST) 8.5 mm thick £29.95



S21B (ST, TM) £49.95

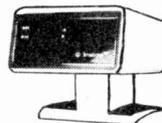

C500 Alarm Black or white £14.35



Ladies LCD 5 & 3 functions Light



Western Time

Chrome £23.95 G.P. £25.95

LED 6 & 3 functions S/S finish

Quality for £11.95

New ultra-slim Ibcico 407. 6 digit display of hrs., mins., secs. (or date), day £39.95. New slim analogue 701. Hrs., mins., secs., date. Luminous. Precise second setting. £54.50. Many other digital and Q. Analogue watches, stopwatches, clocks, car clocks, etc. from Accurist, Casio, Citizen, Ibcico, Fairchild Timeband, N-S, etc. Calculators. Send 15p for our illustrated catalogue. Lowest Discount prices.

Prices include VAT, P & P. Send cheque, P.O. or phone your credit card number to-

Dept. P.E.
19/21 Fitzroy Street
Cambridge CB1 1EH
Telephone (0223) 312866


TEMPUS

PINNER ELECTRONICS

	£	TRANSFORMERS	£
S-DEC	1.99	6-0-6 100 MA	.92*
T-DEC	3.51	9-0-9 75 MA	.92*
U-DEC A	3.51	12-0-12 50 MA	.98*
U-DEC B	5.99	6-0-6 1.5 A	2.66
ANTEX IRON C240 - 15W	3.30	9-0-9 1 A	2.25
ANTEX IRON CCN240 - 15W	3.54	12-0-12 1 A	2.84
ANTEX IRON CX240 - 17W	3.30	12-15-20-24-30V 1 A	4.24
ANTEX ST3 STAND	1.50		
ANTEX C240 ELEMENT	1.43	3 1/2 x 1 1/2 x 1 1/2	1.08
TOWERS TRANSISTOR DATA & EQUIV. BOOK	4.36(Z)	4 1/2 x 2 1/2 x 2 1/2	1.25
TOWERS FET DATA & EQUIV. BOOK	3.40(Z)	4 1/2 x 3 1/2 x 2 1/2	1.15
SERVISOL SWITCH CLEANER Box	.89	6 1/2 x 4 1/2 x 2 1/2	1.99
SERVISOL FREEZER Box	.69		2.41
TMK500 M/METER 30,000 O.P.V.	24.30		
TMK500 CARRY CASE	5.00		
SP25 MK. III MOTORS	8.82*		
SP25 MK. IV MOTORS	10.64*		
DE SOLDA BRAID	.86		

PLEASE ADD 8% V.A.T. except those marked * when you zero add 12 1/2% V.A.T. (Z) = Zero V.A.T. All prices include postage and packing. Ten of any individual item - less 10%. CASH WITH ORDER TO:

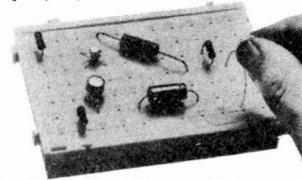PINNER ELECTRONICS, 4 Village Way East, Rayners Lane, Harrow, Middlesex. Telephone: 01-888-6500



ADD A VDU TO YOUR OSCILLOSCOPE

For just £57.30 you can turn any oscilloscope with Z mod input into a versatile computer display capable of displaying alphanumeric data, graphs, or pictures. It can be used with any 8 bit computer output port or without a computer from any TTL or MOS circuit capable of driving it. This unit can form the basis of other interesting projects, e.g. a low frequency storage scope, a spectrum analyser, or a multi-channel logic analyser. Price for kit including PCB, components, documentation, VAT and P&P, £57.30 from: Computabits Ltd., 41 Vincent Street, Yeovil, Somerset. Tel: (0935) 26522.

LYNX ELECTRONICS (LONDON) LTD

92 Broad Street, Chesham, Bucks. Tel. (02405) 75154

P. & P. 30p—Overseas 90p—Matching 20p per pair.

VAT 8% except * which are 12½%. Prices correct at 31st October 1977.

TTL 7400 SERIES			
7400	0-16	7480	0-55
7401	0-16	7482	0-75
7402	0-16	7486	0-32
7403	0-16	7489	2-02
7404	0-18	7490AN	0-49
7405	0-18	7491AN	0-65
7408	0-18	7492	0-57
7409	0-18	7493	0-45
7410	0-16	7494	0-85
7412	0-25	7495	0-67
7413	0-40	7496	0-82
7414	0-72	74100	1-07
7417	0-43	74107	0-35
7420	0-16	74121	0-34
7425	0-30	74122	0-47
7427	0-30	74123	0-65
7430	0-16	74141	0-78
7432	0-28	74145	0-68
7437	0-30	74154	1-30
7441AN	0-76	74164	0-93
7442	0-65	74165	0-93
7445	0-90	74174	1-40
7447AN	0-81	74175	0-94
7448	0-81	74180	1-06
7470	0-32	74181	2-70
7472	0-26	74191	1-33
7473	0-30	74192	1-20
7474	0-32	74193	1-35
7475	0-47	74194	1-20
7476	0-36	74196	1-64

LINEAR I.C.s	
301A	0-40*
307	0-55*
380	0-90*
381	1-60*
3900	0-70*
709	0-27
741	0-28
748	0-35
NE555	0-45
NE565	2-00*
NE566	1-50*
NE567	2-00*
CA3045	0-85*
CA3046	0-80*
CA3130	0-90
MC1304P	1-60*
MC1307P	0-85*
MC1310P	0-95*
MC1351P	1-20*
MC1352P	0-75*
MC1353P	0-75
MC1458P	0-77
MC1496L	0-82*
SAS560	2-25
SAS570	2-25
TAA300	1-61
TAA310A	1-38
TAA550	0-45*
TAA611B	1-25*
TAA861	0-65
TBA530	1-85*
TBA530Q	1-90*
TBA560	2-80*
TBA570	0-98
ZN414	0-95

CLOCK CHIPS	
MM5314	3-25
MM5316	3-85
AA5-5-1224A	3-25
AA5-5-4007D	9-95

I.C. SOCKETS	
8 PIN	0-13
14 PIN	0-14
16 PIN	0-15
24 PIN	0-45
40 PIN	0-80

REGULATORS	
723	0-45
7805	1-50
7812	1-50
7815	1-50

SPECIAL OFFER SECTION	
NPN TO-3 POWER TRANSISTORS Fully tested but unmarked. Similar to 2N3055 except BVCEO = 50 HFE (gain) = 20+ at 3A. VCE SAT < 1.3V at 3A. 5 pcs £1; 25 pcs £4; 50 pcs £7-50; 100 pcs £13.	
TO-18 NPN TRANSISTORS Medium voltage high gain. Similar to BC107/8/9—unmarked. 25 pcs £1-20; 100 pcs £3-50.	
TO-3 HARDWARE Mica, washers, solder tag, nuts, bolts. 50 sets £1.	
RECTIFIERS DO-4 PACKAGE 10A 50V 45p; 10A 100V 50p; 10A 200V 60p; 10A 400V 75p. Please specify Polarity. Stud Cathode or Stud Anode. Ideal for power supplies, inverters etc.	

OPTOELECTRONICS	
DISPLAYS Class II	704
	707
	707
	727
	728
	747
	750

MEMORIES	
2102A-6	3-60
2112A-4	4-75
6508	7-95
2102	2-50
2107	10-00
2112	4-50
2513	8-50
2602	2-50

REGULATORS	
7818	1-50
LM309K	0-95
LM340-5	1-35
LM340-12	1-35
LM340-15	1-35
LM340-18	1-35

OPTOELECTRONICS	
704	0-99
707	0-99
727	1-95
728	1-95
747	1-80
750	1-80

RETURN POST SERVICE
ACCESS AND BARCLAYCARD WELCOME



MEMORIES
2102A-6 3-60
2112A-4 4-75
6508 7-95
2102 2-50
2107 10-00
2112 4-50
2513 8-50
2602 2-50

Z80 Programming Manual
only £3.50
POST FREE

SUPER SAVERS	
SG309K	0-95
MC1310P	0-95
TIL209	0-10
2 Clear led	0-10
MM5314	3-25
MM5316	3-85
FCS8000	
3 1/2 Digit Dspl	2-95
FCS8024	
4 Digit Dspl	3-50

THYRISTORS										
PIV	1A	3A	3A	4A	6A	8A	10A	10A	16A	
(TO5)	(STUD)	(C106)	(TO220)							
200	0-35	0-50	0-45	0-40	0-58	0-60	0-68	0-68	1-14	
400	0-40	0-60	0-50	0-45	0-87	0-88	0-89	0-89	1-40	
600	0-65	0-85	0-70	—	1-09	1-19	1-26	1-26	1-80	

BT106 £1-00, BT107 £1-60, BT108 £1-60, BT109 £1-00,
BT116 £1-00, 2N3525 £0-50

TRIACS—Plastic TO-220 Package Isolated Tab										
	4A		6-5A		8-5A		10A		15A	
	(a)	(b)								
100V	0-60	0-60	0-70	0-70	0-78	0-78	0-83	0-83	1-01	1-01
200V	0-84	0-84	0-75	0-75	0-87	0-87	0-87	1-01	1-17	1-17
400V	0-77	0-78	0-80	0-83	0-97	1-01	1-13	1-19	1-70	1-74
600V	3-96	0-99	1-01	1-10	1-21	1-26	1-42	1-50	2-11	2-17

N.B. Column (a) without internal trigger; (b) with internal trigger.

CMOS PLASTIC		
4000BE	0-20	4015BE 0-95
4001BE	0-20	4016BE 0-54
4002BE	0-20	4017BE 1-00
4006BE	0-05	4018BE 1-10
4007BE	0-20	4019BE 0-50
4008BE	0-93	4020BE 1-12
4009BE	0-52	4021BE 1-03
4010BE	0-52	4022BE 0-95
4011BE	0-20	4023BE 0-20
4012BE	0-20	4024BE 0-86
4013BE	0-50	4025BE 0-20
4014BE	1-00	4026BE 1-55
4027BE	0-62	4028BE 0-91
4029BE	1-10	4030BE 0-55
4041BE	0-80	4042BE 0-83
4043BE	1-00	4044BE 0-94
4046BE	1-32	4049BE 0-54
4050BE	0-54	4059BE 0-30
4070BE	0-50	

NASCOM I Microcomputer for the Hobbyist

HARDWARE FEATURES:

- ★ Supplied in kit form for self-assembly.
- ★ Full documentation supplied.
- ★ Includes printed circuit board.
- ★ Full keyboard included.
- ★ Interfaces to keyboard, cassette recorder & T.V.
- ★ 2K x 8 Ram
- ★ 1K x 8 Eprom monitor programme.
- ★ Powerful Z80 CPU.
- ★ 16 line x 48 character display interface to standard, unmodified T.V. set.
- ★ On board expansion to 2K x 8 Eprom.
- ★ On board expansion facility for additional 16 lines I/O.
- ★ Total expansion to 64K x 8 memory.
- ★ Total expansion to 256 input ports and 256 output ports.

SOFTWARE FEATURES:

- ★ 1K x 8 'Nasbug' programme in Eprom.
- ★ Provides 8 basic operator commands including single step.
- ★ Expandable software system via additional user programmes in Ram or Eprom.

Cost £197.50 (ex. VAT)
Phone or write for details.

You can work wonders with your free time.

There's immense satisfaction in making your own equipment. And you'll get excellent results with Heathkit.

Every kit is absolutely complete down to the last nut and bolt. The quality is the best. And each kit has an easy to follow instruction manual that explains exactly what to do at each step.


So you enjoy assembling your kit and you finish with first-class equipment every time.

That's why Heathkit are so successful. And that's why the range is the biggest in the world.

It's all in the new edition of the free Heathkit catalogue. Everything from the simplest to the most sophisticated. Alarms, digital clocks, testers, transceivers and lots more... even the tools are there!

See for yourself. Send the coupon now.

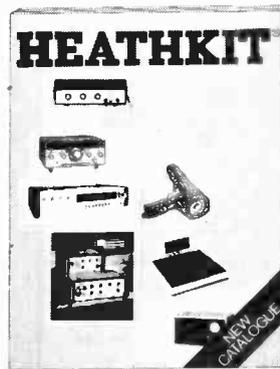- NEW CATALOGUE**
- NEW TEST INSTRUMENTS**
- NEW DIGITAL BATHROOM SCALES**
- NEW AMATEUR RADIO EQUIPMENT**
- NEW AUDIO SYSTEMS AND MANY OTHER NEW ITEMS**



The new Heathkit catalogue. Out now FREE.

To: Heath (Gloucester) Ltd., Dept. PE 18, Gloucester, GL2 6EE. Please send me my Heathkit catalogue.

I enclose an 11p stamp for postage.



Name _____

Address _____

Postcode _____

ACCESS AND BARCLAYCARD WELCOMED

Showrooms at 233 Tottenham Court Road, London (Phone 01-636 7349) and Bristol Road, Gloucester (Phone Gloucester 29451).

B. BAMBER ELECTRONICS

Dept. P. E. 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

**A MERRY XMAS
TO ALL OUR CUSTOMERS
PLUS A XMAS PRESENT FROM US
IN THE FORM OF A**

**10% DISCOUNT
ON ALL ORDERS RECEIVED
FROM 1st to 31st DECEMBER**

For items in our current
ads and lists only

THIS OFFER IS FOR 1 MONTH ONLY

Slider Switches, 2 pole make and break (or can be used as a 1 pole change-over by linking the two centre pins), 4 for 50p.

A NEW RANGE OF QUALITY BOXES & INSTRUMENT CASES.

Aluminium Boxes with Lids.		
AB10	5 1/2 x 4 x 1 1/2	60p
AB13	6 x 4 x 2	80p
AB14	7 x 5 x 2 1/2	£1.00
AB15	8 x 6 x 3	£1.30
AB16	10 x 7 x 3	£1.50
AB17	10 x 4 1/2 x 3	£1.30
AB25	6 x 4 x 3	£1.00

Vinyl Coated Instrument Cases

Light Blue tops and White lower sections. Very smart finish.

WB1	5 x 2 1/2 x 2 1/2	60p
WB2	6 x 4 1/2 x 1 1/2	£1.10
WB3	8 x 5 x 2	£1.60
WB4	9 x 5 1/2 x 2 1/2	£1.80
WB5	11 x 6 1/2 x 3	£2.00
WB6	11 x 7 1/2 x 3 1/2	£2.25
WB7	12 x 6 1/2 x 5 1/2	£2.60
WB853	8 x 5 1/2 x 3 1/2	£2.00

MAINS TRANSFORMERS. Type 60/2. Mains input, 200-210-220-230-240-250V a.c., output 0-20-40-80V at 2A, in Metal and Plastic case, approx. 7 1/2 x 4 1/2 x 4, fully fused (ideal for PSU) £3.00 each.

MAINS TRANSFORMERS. Type 15/300 240V Input, 15V at 300mA output, £1.50 each.

MAINS TRANSFORMERS. Type 45/100, 240, 220, 110, 20. 0V input, 45V at 100mA output, £1.50 each.

MAGNETIC DEVICES PROGRAMMERS. Contain 9 fully adjustable cams and 9 change over micro-switches (rated approx. 1A at 240VAC). Needs slow-motion motor to drive (not supplied). Ideal for disco lights, sequence switching etc. ex equipment £1.50 each.

VIDICON SCAN COILS (Transistor type, but no data) complete with vidicon base £6.50 each. Brand New.

FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK. S.A.E. FOR LIST.

NEW FOR THE VHF CONSTRUCTOR. A range of tuned circuits on formers with slugs and screening cans. Frequencies quoted are approximate, and range can be greatly extended by using varying capacitors in parallel.

Type S (1/4 in square, dummy type)
Type SA 20 to 30MHz (when 33pF fitted in parallel)
Type SB 35 to 50MHz (with link winding)
Type SC 70 to 100MHz (with link winding)
Type SD 135 to 175MHz (with link winding)
Type M (Min. 1/4 in square types)
Type MA 19 to 28MHz (when 33pF fitted in parallel)
Type MB 22 to 32MHz (when 33pF fitted in parallel)
Type MC 25 to 35MHz (when 33pF fitted in parallel)
Type MD 38 to 50MHz (when 33pF fitted in parallel)
Type ME 45 to 60MHz (when 33pF fitted in parallel)
Type MF 100 to 200MHz (without slug) when 0 to 30pF variable fitted in parallel.
All the above coils available in packs of five only (same type) at 50p per pack of 5.

SEMICONDUCTORS

BSX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC108 (plastic BC108), 5 for 50p.
BFV51 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 50p.
PNP audio type TOS Transistors, 12 for 25p.
BF152 (UHF amp/mixer), 3 for 50p.
2N3819 Fet., 3 for 60p.
BC148 NPN SILICON, 4 for 50p.
BC158 PNP SILICON, 4 for 50p.
BAV31 Signal Diodes, 10 for 35p.
BA121 Varicap Diodes, 4 for 50p.

741CG op amps by RCA, 4 for £1

RED LEDs (Min. type) 5 for 70p.

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

PLASTIC PROJECT BDXES with screw on lids (in black ABS) with brass inserts.
Type NB1 approx 3in. x 2 1/2in. x 1 1/2in. 40p each.
Type NB2 approx. 3 1/2in. x 2 1/2in. x 1 1/2in. 50p each.
Type NB3 approx. 4 1/2in. x 3 1/2in. x 1 1/2in. 60p each.

MULLARD 85A2 85V STABILISER VALVES

(Brand New) 70p each or 2 for £1.20.

TOS transistor insulator sets, 10 for 50p

PERSPEX TUNER PANELS (for FM Band 2 Tuners) marked 88-108MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx. 8 1/2in x 1 1/2in., 2 for 35p.

PLUGS AND SOCKETS

N-Type Plugs 50 ohm, 60p each, 3 for £1.50.
PL259 Plugs (PTFE) brand new, packed with reducers, 65p each.
SO239 Sockets (PTFE) brand new (4-hole fixing type), 50p each.

SOLDER SUCKERS (Plunger type). Standard Model. £5. Skirted Model £5.50. Spare Nozzles 60p each.

NEW MARKSMAN RANGE OF SOLDERING IRONS.

S125D 25W 240V £3.80.
S140D 40W 240V £4.20.
S125DK 25W 240V + bits etc., KIT £4.90.

BENCH STAND with spring and sponge for Marksmen irons £2.38.

Spare bits MT9 (for 15W), MT5 (for 25W) 45p, MT10 (for 40W) 50p.
All prices + 8% VAT.

TC2P TEMPERATURE CONTROLLED IRON.

Temperature controlled Iron and PSU. £30 + VAT (£2.40).

SPARE TIPS

Type CC single flat, Type K double flat fine tip, Type P very fine tip. £1 each + VAT (8p).

MOST SPARES AVAILABLE.

MULTICORE SOLDER

Size 5 Savbit 18 s.w.g. in alloy dispenser, 30p + VAT (3p).
Size C15AV18 Savbit 18 s.w.g., 56p + VAT (4p).
1/2 Kg. (1.1lb) 80 x 40, 20 s.w.g. on plastic reel £3 + VAT (24p).

WELLER SOLDERING IRONS

EXPERT. Built-in spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.
EXPERT SOLDER GUN #1000D £9.90.
EXPERT SOLDER GUN KIT (spare bits, case, etc.) £12.90.
Spare bits 35p pair.

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

MIXED COMPONENT PACKS, containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

ALU-SOL ALUMINIUM SOLDER (made by Multicore). Solders aluminium to itself or copper, brass, steel, nickel or tinplate, 16 s.w.g. with multicore flux, with instructions. Approx. 1 metre coil 40p pack. Large reel £2.75.

VARICAP TUNERS Mullard type ELC1043.05. Brand New, £4.40 + 12 1/2% VAT.

BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS. Up to 50V working. Seatronic Manufacture. Approx. 100. £1.50 per pack + 12 1/2% VAT.

OSMOR REED RELAY COILS (for reed relays up to 5in dia., not supplied) 12V, 500 ohm coil, 2 for 50p.

We now stock Spiralux Tools for the electronic enthusiast. Screwdrivers, Nut spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

Dubilier Electrolytics, 500uF, 450V, 2 for 50p.
Dubilier Electrolytics, 100uF, 275V, 2 for 50p.
Plessey Electrolytics, 470uF, 63V, 3 for 50p.
TCC Electrolytics, 1000uF, 30V, 3 for 60p.

Dubilier Electrolytics, 5000uF, 35V, 50p each.
Dubilier Electrolytics, 5000uF, 50V, 60p each.
ITT Electrolytics, 680uF, 25V, high grade, screw terminals, with mounting clips, 50p each.

PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS.

TV PLUGS AND SOCKETS

TV Plugs (metal type), 4 for 50p.
TV Sockets (metal type), 4 for 50p.
TV Line Connectors (back-to-back sockets), 4 for 50p.

PLEASE ADD 12 1/2% VAT.

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE WITH ALL ENQUIRIES. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS WELCOME BY APPOINTMENT ONLY.

UNIJUNCTIONS TIS43 Type a 20p, MEU 21 a 22p, 2N 4B71 a 22p, MU 4894 a 22p, GE4JD5E9 a 22p, D13T1 a 25p, 2N 6028 a 30p.
NPN PHOTO TRANSISTORS a 15p, DARLINGTONS a 20p.
100-0-100uA TUNING METER 1 1/2 x 1 1/2 a 90p.
MINIATURE Buf 300V. w. ELECTROLYTICS 10 for 57p.
NKT 214 equivalent to OC 71 at 10p each.
100 ASSORTED SILVER MICA CAPACITORS a 57p.
100 ASSORTED POLYSTYRENE CAPACITORS a 57p.
50 BC 107-8-9 TRANSISTORS Assorted Untested a 57p.
50 AC 128 TRANSISTORS Branded but untested a 57p.
100 MULLARD C2B0 CAPACITORS Assorted a 57p.
TV COAX PLUGS a 15p, **SOCKETS** a 15p.
2 PIN DIN SOCKETS Single a 10p, Double a 18p.
TUNING CAPACITORS 250 + 250 + 20 + 20 + 20p + 75p.
AUDIO AMPLIFIER I.C. SL 414 a £1.50 each.
SUB MINIATURE ROTARY SWITCH 2 Pole 4 way at 20p.
PLASTIC 90 WATT NPN POWER TRANSISTORS type BD 207 a 55p each.
500v.dv. of PVC CABLE 25 strand .004 at £3.
F.M. TUNER FRONT HEAD 88 to 108 MHz with conversion data to Aircraft Band or 144 MHz a £3.
DAU MINIATURE TRIMMERS 2 to 9pF a 10p, 5 to 38pF a 10p, 6 to 45pF a 10p, 8 to 125pF a 12p, 8 to 140pF a 15p.
UNMARKED GOOD 400mV ZENERS 6.8v, 10v, 11v, 12v, 13v, 16v, 24v, 30v, 33v, 36 Volt. All at 10 for 40p.
FERRANTE ZTX 108 TRANSISTORS at 7 for 57p.
TANTALUM BEAD CAPACITORS .1uf 35v.w., .33uf 35v.w., .47uf 35v.w., 1uf 35v.w., 2.2uf 35v.w., 3.3uf 16v.w., 4.7uf 10v.w., 4.7uf 35v.w., 5uf 25v.w., 6.8uf 25v.w., 10uf 25v.w., 15uf 25v.w., 20uf 6v.w., 22uf 16v.w., 33uf 25v.w., 47uf 6v.w. All at 9p each.
TO 39 5 WATT NPN DARLINGTON TRANSISTOR a 20p.
6 to 1 FRICTION SLOW MOTION DRIVE a 55p.
NUT FIXING 1000pF 500v.w. FEED THRU's a 15p each.
3 DIGIT A to D CONVERTER I.C. TYPE LD 130 with data a £6.
50 ASSORTED TANTALUM BEAD CAPACITORS for £1.50.
BD 187.4 amp NPN PLASTIC POWER TRANSISTOR a 25p, 5 for £1.
MAINS TRANSFORMERS 240V Input. Type 1. 22v 1 amp a 88p (20p P & P). Type 2. 22v 300mA, 7.5v 1 amp a 99p (20p P & P). Type 4. 9v 500mA a 88p (20p P & P). Type 5. 12v 300mA a 88p (20p P & P). Type 6. 50v 2 amp, 45v 500mA a £3.50 (85p P & P). Type 7. 20v 1 amp twice, 10v 1 amp twice a £4.50 (95p P & P). Type 8. 16v 500mA a 88p (20p P & P). Type 9. 14v 2 amp a £1.60 (25p P & P). Type 10. 20v 1.5 amp, 6v 1 amp a £1.60 (25p P & P). Type 11. 25v 1 amp Tapped at 14v a £1.25 (20p P & P). Type 12. 22v 1 amp, 7.5v 500mA, 6v 1 amp a £1.60 (20p P & P). Type 13. 22v 1 amp Tapped 6v 500mA a £1.30 (25p P & P). Type 14. 22v 1 amp, 7.5v 500mA, 6v 1 amp a £1.60 (25p P & P).
TBA 1205 FM I.C.'s Untested with data a 6 for 60p.
30 ASSORTED 10XAJ CRYSTALS between 5100 To 7900 KHz a £1.10.
200 ASSORTED RESISTORS 1/2 watt for 75p.
RCA 40410 PNP 3 WATT 90 VOLT 100 MHZ TRANSISTORS a 15p each.
100 ASSORTED DISC CERAMICS for 57p.
Please add 20p for post and packing on UK orders, unless otherwise stated. Overseas orders at cost.

**J. BIRKETT
RADIO COMPONENT SUPPLIERS
25 The Strait, Lincoln LN2 1JF
Tel. 20767.**

C-MOS	4066	80p	7410	20p	7492	54p	74172	860p
4000	4069	27p	7411	30p	7493	44p	74173 <td>817p</td>	817p
4001	4070	50p	7412	20p	7494	88p	74174	100p
4002	4071	7413	38p	7495	85p	74175	98p	
4006	4072	25p	7414	96p	7496	90p	74176	123p
4007	4073	26p	7416	35p	7497	358p	74177	123p
4008	4076	118p	7417	40p	74100	120p	74178	110p
4009	4077	48p	7420	20p	74104	73p	74179	138p
4010	4081	20p	7421	40p	74105	73p	74180	108p
4011	4082	25p	7422	20p	74106	36p	74181	262p
4012	4093	95p	7423	32p	74109	75p	74182	83p
4013	4502	123p	7425	32p	74110	50p	74184	234p
4014	4510	139p	7426	107p	74111	86p	74185	187p
4015	4511	150p	7427	89p	74116	251p	74189	134p
4016	4512	81p	7428	81p	74120	155p	74191	134p
4017	4514	264p	7430	20p	74121	35p	74192	115p
4018	4515	284p	7432	29p	74122	53p	74193	115p
4019	4516	123p	7433	118p	74123	81p	74194	107p
4020	4518	123p	7437	38p	74125	58p	74195	102p
4021	4520	123p	7438	38p	74126	59p	74196	134p
4022	4522	122p	7440	20p	74128	98p	74197	130p
4023	4526	122p	7442	68p	74132	75p	74198	124p
4024	4527	140p	7443	130p	74142	302p	74199	198p
4025	4528	115p	7444	130p	74143	346p	74221	109p
4026	4531	115p	7445	105p	74144	346p	74246	205p
4027	4543	115p	7447	90p	74145	90p	74247	195p
4028	4555	115p	7448	90p	74147	148p	74248	171p
4029	4556	115p	7450	20p	74148	102p	74249	171p
4030	4581	348p	7451	20p	74150	150p	74251	170p
4031	4582	140p	7453	20p	74151	78p	74265	94p
4033	4584	99p	7454	20p	74153	78p	74278	331p
4034	4585	108p	7460	20p	74154	138p	74279	75p
4035	4585	108p	7470	30p	74155	90p	74283	94p
4040	4585	108p	7472	30p	74156	90p	74284	712p
4041	84p		7473	33p	74157	82p	74285	712p
4042	7400	18p	7474	33p	74158	140p	74290	122p
4043	7401	18p	7475	46p	74159	265p	74293	122p
4044	7402	18p	7481	125p	74160	102p	74298	173p
4045	7403	20p	7483	95p	74161	102p	74365	93p
4046	7404	24p	7484	118p	74162	102p	74366	93p
4050	7405	24p	7485	128p	74163	102p	74367	93p
4051	7406	42p	7486	33p	74164	115p	74368	93p
4052	7407	58p	7489	340p	74165	115p	74390	189p
4053	7408	25p	7490	43p	74167	358p	74393	189p
4060	7409	25p	7491	77p	74170	213p	74490	254p


Full price list of linears, discretes, capacitors, resistors, potentiometers, tools, soldering irons and accessories available. Send 20p or large S.A.E. This list is sent free with the first order.

Prices correct November 1977.

Terms C.W.O. Add VAT to prices at 8%. Post, etc.: U.K. 25p, overseas 75p. Access and Barclaycard, and all convertible currencies accepted.

TIRRO ELECTRONICS
Grenfell Place, Maidenhead, Berks.
Tel. (0628) 36229
Mail order division of RITRO Electronics UK Ltd.

THE DYNAMIC DUO

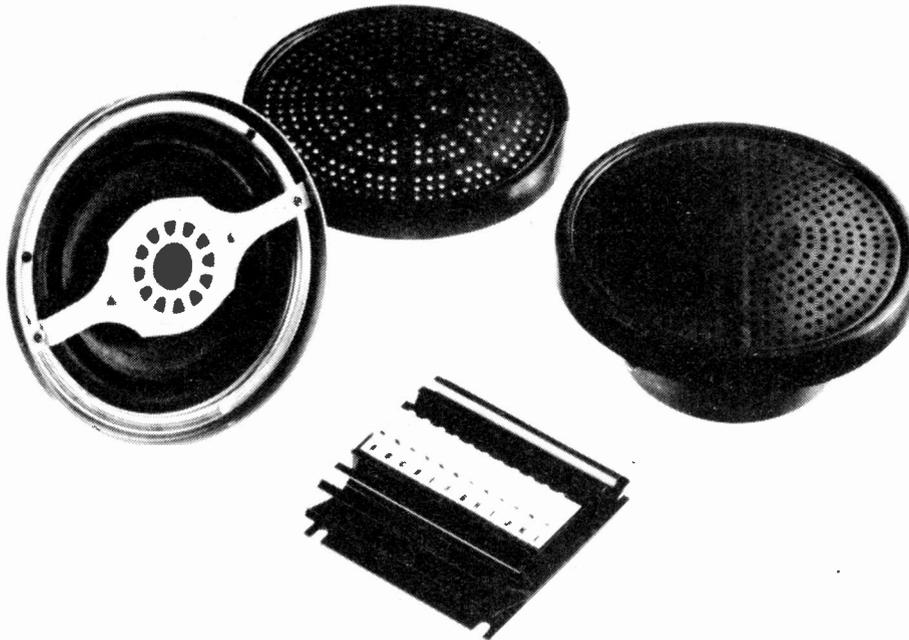

The C15/15 is a unique Power Amplifier providing Stereo 15 watts per channel or 30 watts Mono and can be used with any car radio/tape unit. It is simply wired in series with the existing speaker leads and in conjunction with our speakers S15 produces a system of incredible performance.

A novel feature is that the amplifier is automatically switched on or off by sensing the power line of the radio/tape unit hence alleviating the need for an on/off switch.

The amplifier is sealed into an integral heatsink and is terminated by screw connectors making installation a very easy process.

The S15 has been specially designed for car use and produces performance equal to domestic speakers yet retaining high power handling and compact size.

C15/15

15 watts per channel into 4Ω
 Distortion 0.2% at 1kHz at 15 watts
 Frequency response 50Hz-30kHz
 Input Impedance 8Ω nominal
 Input sensitivity 2V R.M.S. for 15 watts output
 Power line 10-18V
 Open and Short circuit protection
 Thermal protection
 Size 4 × 4 × 1 inches

Data on S15

6in Diameter
 5½in air Suspension
 2in Active Tweeter
 20oz Ceramic magnet
 15 watts R.M.S. handling
 50Hz-15kHz frequency response
 4Ω Impedance

C15/15 Price £17.74 + £2.21 VAT. P. & P. free

S15 Price per pair £17.74 + £2.21 VAT. P. & P. free

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd
Crossland House
Nackington, Canterbury
Kent CT4 7AD
Tel. (0227) 63218

Please Supply

Total Purchase Price

I Enclose Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

Signature

RST

VALVE MAIL ORDER CO.

Climax House
Fallsbrook Road, London SW16 6ED

**SPECIAL EXPRESS
MAIL ORDER SERVICE**


Ep	Ep	Ep	Ep	Ep	Ep
AA119	0-20	BCY71	0-22	*MPSU01	0-32
AA130	0-13	BCY72	0-17	*MPSU06	0-40
AA132	0-15	BD111	0-50	*MPSU56	0-45
AA213	0-25	BD115	0-80	NKT401	2-00
AA215	0-31	BD121	1-50	NKT403	1-73
AA217	0-25	BD123	1-50	NKT404	1-73
AC107	0-75	BD124	1-00	NE555	0-45
AC125	0-30	BD131	0-51	OA5	0-75
AC126	0-25	BD132	0-54	OA7	0-55
AC127	0-25	*BD135	0-35	OA10	0-55
AC128	0-25	*BD136	0-36	OA47	0-14
AC141	0-20	*BD137	0-37	OA70	0-30
AC141K	0-30	*BD138	0-40	OA79	0-30
AC142	0-20	*BD139	0-43	OA81	0-30
AC142K	0-25	*BD140	0-47	OA85	0-30
AC176	0-25	BD144	2-00	OA90	0-08
AC187	0-25	BD181	1-38	OA91	0-08
AC188	0-25	BD182	1-48	OA95	0-08
ACY21	0-85	BD237	0-80	OA200	0-10
ACY18	0-85	BD238	0-85	OA202	0-11
ACY19	0-85	BDX10	0-75	OA210	0-75
ACY20	0-85	BDX32	2-25	OA211	0-75
ACY21	0-85	BDY20	1-42	OA220	0-85
ACY39	1-25	BDY60	0-75	OA221	0-85
AD149	0-70	BF115	0-38	OA226	0-85
AD161	0-75	BF152	0-25	OAZ207	0-85
AD182	0-75	BF153	0-25	OC16	1-25
AF106	0-25	BF154	0-25	OC20	2-00
AF114	0-25	BF159	0-35	OC22	2-50
AF115	0-25	BF160	0-30	OC23	2-75
AF116	0-25	BF167	0-38	OC24	3-50
AF117	0-25	BF173	0-38	OC25	0-90
AF139	0-30	BF177	0-45	OC26	0-90
AF186	0-30	BF178	0-45	OC28	2-00
AF239	0-45	BF179	0-48	OC29	2-00
AFZ11	2-75	BF180	0-45	OC35	1-50
AFZ12	2-75	BF181	0-45	OC36	1-50
AS26	0-45	BF182	0-45	OC41	0-50
AS27	0-50	BF183	0-45	OC42	0-50
ASZ15	1-25	BF184	0-38	OC43	1-50
ASZ16	1-25	BF185	0-37	OC44	1-50
ASZ17	1-25	*BF194	0-12	OC45	0-50
ASZ20	0-75	*BF195	0-11	OC71	0-45
ASZ21	1-50	*BF196	0-13	OC72	0-45
AU113	1-70	*BF197	0-14	OC73	0-45
AU110	0-15	BF200	0-32	OC74	0-75
BA145	0-15	*BF224	0-20	OC75	0-50
BA148	0-15	*BF244	0-35	OC76	0-80
BA154	0-10	BF257	0-37	OC77	1-20
BA155	0-12	BF258	0-42	OC81	0-75
BA156	0-13	BF259	0-45	OC82	0-75
BAW62	0-07	*BF336	0-50	OC83	0-55
BAX13	0-07	*BF337	0-53	OC84	0-80
BAX16	0-07	*BF338	0-55	OC88	1-50
BC107	0-12	BFS21	2-27	OC122	1-50
BC108	0-12	BFS28	1-38	OC123	1-50
BC109	0-13	*BF561	0-25	OC130	2-25
*BC113	0-15	*BF598	0-25	OC140	1-95
*BC114	0-18	BFW10	0-90	OC141	2-25
*BC115	0-18	BFW11	0-90	OC170	0-75
*BC116	0-18	BFX84	0-38	OC171	0-75
*BC117	0-22	BFX85	0-35	OC200	1-00
*BC118	0-16	BFX86	0-38	OC201	1-00
*BC125	0-18	BFX88	0-32	OC202	1-25
*BC126	0-25	BFY50	0-28	OC203	1-25
*BC135	0-15	BFY51	0-28	OC204	1-25
*BC136	0-15	BFY52	0-28	OC205	1-75
*BC137	0-16	BFY54	0-34	OC206	1-75
*BC147	0-18	BSX19	0-32	OC207	1-25
*BC148	0-18	BSX19	0-34	OC207	1-25
*BC149	0-13	BSX20	0-34	ORP12	0-83
*BC157	0-12	BSX21	0-32	*R2008B	2-25
*BC158	0-11	BT106	1-25	*R2009	2-25
*BC159	0-13	BTY79/400R	3-18	*R210B	2-25
*BC167	0-13	*BU205	2-25	TIC222	1-30
*BC170	0-18	*BU206	2-25	TIC226D	1-30
*BC171	0-14	*BU208	2-50	TIL209	0-25
*BC172	0-13	BY100	0-45	*TIP29A	0-80
*BC173	0-15	BY126	0-45	*TIP30A	0-50
BC177	0-18	BY127	0-15	TIP31A	0-82
BC178	0-18	BZK15	0-20	TIP32A	0-75
BC179	0-20	Series		TIP33A	1-00
*BC182	0-11	BZY88	0-13	TIP34A	1-20
*BC183	0-11	Series		TIP41A	0-70
*BC184	0-12	CRS1/05	0-45	TIP42A	0-80
*BC212	0-14	CRS1/40	0-80	TIP2955	1-00
*BC213	0-14	CRS3/05	0-45	TIP3055	0-50
*BC214	0-14	CRS3/40	0-75	*TIS43	0-35
*BC237	0-17	CRS3/60	0-90	*ZS140	0-25
*BC238	0-12	GEX66	1-50	*ZS170	0-12
BC301	0-45	GEX541	1-75	*ZS178	0-54
BC303	0-80	GJ5M	0-75	*ZS271	0-22
*BC308	0-18	GJ7M	0-75	*ZS278	0-56
*BC327	0-22	GMO378A	1-50	*ZTX107	0-11
*BC328	0-18	*KS100A	1-40	*ZTX108	0-18
*BC337	0-18	MJE340	0-56	*ZTX109	0-12
*BC338	0-18	MJE370	0-45	*ZTX300	0-12
BCY30	1-00	MJE371	0-81	*ZTX301	0-13
BCY31	1-00	MJE520	0-85	*ZTX302	0-17
BCY32	1-00	MJE521	0-75	*ZTX303	0-17
BCY33	0-90	MJE2955	1-25	*ZTX304	0-19
BCY34	0-90	MJE3055	0-75	*ZTX311	0-12
BCY39	3-00	*MPF102	0-30	*ZTX314	0-20
BCY40	1-25	*MPF103	0-30	*ZTX500	0-13
BCY42	0-30	*MPF104	0-30	*ZTX501	0-14
BCY43	0-32	*MPF105	0-30	*ZTX502	0-16
BCY58	0-23	*MPSA06	0-25	*ZTX503	0-17
BCY70	0-18	*MPSA56	0-28	*ZTX504	0-20
				*ZTX531	0-26
				*ZTX550	0-18
				IN914	0-87
				IN916	0-07
				1N4001	0-06
				1N4002	0-07
				1N4003	0-08
				1N4004	0-09
				1N4005	0-13
				1N4006	0-15
				1N4007	0-15
				1N4009	0-15
				1N4148	0-07
				1N5400	0-14
				1N5401	0-16
				1S44	0-00
				1S920	0-08
				1S921	0-08
				2G301	1-00
				2G302	1-00
				2G306	1-10
				2N404	0-80
				2N696	0-25
				2N697	0-16
				2N698	0-30
				2N705	0-80
				2N706	0-80
				2N708	0-21
				2N930	0-28
				2N1131	0-28
				2N1132	0-28
				2N1302	0-37
				2N1303	0-37
				2N1304	0-45
				2N1305	0-45
				2N1306	0-50
				2N1307	0-50
				2N1308	0-80
				2N1309	0-80
				2N1613	0-50
				2N1671	1-50
				2N1893	0-33
				2N2147	1-40
				2N2148	1-65
				2N2218	0-33
				2N2219	0-33
				2N2220	0-35
				2N2221	0-22
				2N2222	0-25
				2N2223	2-75
				2N2368	0-17
				2N2369A	0-00
				2N2484	0-21
				2N2646	0-50
				2N2904	0-35
				2N2905	0-35
				2N2906	0-25
				2N2924	0-21
				*2N2925	0-17
				*2N2926	0-13
				2N3053	0-25
				2N3054	0-50
				2N3057	0-85
				2N3440	0-60
				2N3441	0-80
				2N3442	1-20
				2N3525	0-90
				2N3614	1-20
				*2N3702	0-15
				*2N3703	0-15
				*2N3704	0-15
				*2N3705	0-15
				*2N3706	0-14
				*2N3707	0-16
				*2N3708	0-16
				*2N3709	0-15
				*2N3710	0-14
				*2N3711	0-15
				*2N3712	0-15
				*2N3713	1-70
				*2N3714	0-90
				*2N3715	2-50
				*2N3820	0-48
				*2N3823	0-80
				2N3866	1-00
				2N3904	0-21
				*2N3905	0-22
				*2N3906	0-22
				*2N4058	0-20
				*2N4059	0-15
				*2N4060	0-20
				*2N4061	0-17
				*2N4062	0-18
				*2N4124	0-17
				*2N4126	0-17
				*2N4288	0-20
				*2N4288	0-25
				*2N4289	0-25
				*2N4547	0-35
				*2N4548	0-35
				*2N4549	0-35
				3N125	1-75
				3N141	0-85
				*76013N	1-75

Plug in socket
—low profile
7400 0-20
7401 0-20
7402 0-20

AITKEN BROS.

35, High Bridge, Newcastle upon Tyne

Tel: 0632 26729

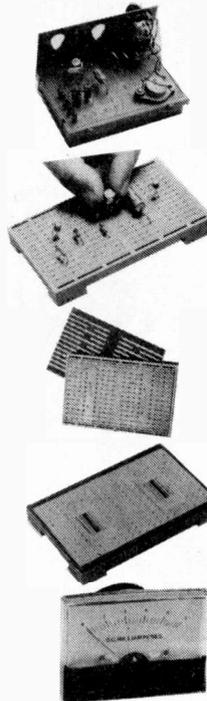

S-DEC

This, the most popular Board is designed solely for the use of discrete components and is particularly useful for basic educational purposes. (No. of Contacts: 70) PRICE £2.13 inc. VAT

T-DEC

This Board allows 2 TO5 or 1 DIL IC Station to be used and so is primarily intended for discrete work or for linear IC application where considerable numbers of discrete components may be required. (No. of Contacts: 208) PRICE £3.93 inc. VAT.

μ-DEC 'A'

The μ-Dec 'A' is specially designed for ease of use with IC's and allows 2 DIL or 4 TO5 stations to be used but will accommodate discrete components with equal facility. (No. of Contacts: 208) PRICE £4.31 inc. VAT.

μ-DEC 'B'

The μ-Dec 'B' is for similar uses as μ-Dec 'A', but has two 16 lead IC sockets as part of the Board. (No. of Contacts: 208) PRICE £7.55 inc. VAT.

PANEL METERS

Dims: 80mm x 45mm. 50μ amp, 100μ amp, 500μ amp, 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25v dc, 30v dc, 50v ac, 300v ac, "S", "VU", 50-0-50μa, 100-0-100μa, 500-0-500μa. PRICE £4.13 inc. VAT.

POTS* CAPACITORS, BOXES, INST. CASES, DIN PLUGS, RESISTORS, ETC., ALWAYS IN STOCK. POSTAGE AND PACKING 20p EXTRA. 1978 CAT. AVAILABLE JAN. PLEASE SEND 40p.

complete digital clock kits



TEAK OR PERSPEX CASE

NON ALARM £12.50

ALARM £15.50

All prices include P. & P. and VAT

FEATURES: 4 LED digits in high. Red. ● 12 hour display with a.m./p.m. indication. ● Mains frequency accuracy. ● Easy to build: all components included. ● Beautiful real wood case or perspex.

U.K. RETURN OF POST MAIL ORDER SERVICE also WORLDWIDE EXPORT SERVICE

R.C.S. 10 WATT AMPLIFIER KIT



This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume, bass and treble controls. Spec. 10W output into 8 ohms, 7W into 15 ohms. Response 20c/s to 30kc/s. Input 100mV. High imp. Size 9 1/2 x 3 x 2 1/2 in. A/C mains operated.

Mono kit **£11.25** Stereo kit **£18** post 45p
Easy to build. Full instructions supplied.



ELAC 10 inch £4.50

Ribbed cone. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 10W. 15 ohm impedance.

ELAC 9 x 5 in HI-FI SPEAKER TYPE 59RM **£3.45** Post 35p
This famous unit now available. 10W. 8 ohm.

ELAC HI-FI SPEAKER 8in TWIN CONE

Dual cone plastic roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 40 c/s. 8 ohm impedance. 15 watts. RMS. **£5.95** Post 35p

MAINS TRANSFORMERS

ALL POST 50p each

250-0-250V 70mA, 6-3, 2A	£3.45
250-0-250 80mA, 6-3V 3-5A, 6-3V 1A or 5V 2A	£4.80
350-0-350 80mA, 6-3V 3-5A, 6-3V 1A or 5V 2A	£5.80
300-0-300 120mA 2 x 6-3V 2A C.T., 6-3V 2A	£8.50
220V 45mA, 6-3V 2A	£1.75
HEATER TRANS. 6-3V 3A, £1.45. 1 amp. £1.00	
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2A 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V	£5.30
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£5.30
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£8.50
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£11.00
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£14.50
5, 8, 10, 16V 1A £2. 12V 100mA £1. 12V 300mA £1. 12V 750mA £1.30. 40V 2A tapped 10V or 30V £2.95. 20V 3A £2. 40V 2A £2.95. 30V 5A + 34V 2A ct. £3.75. 2 x 18V 6A £11. 20-0-20V 1A £2.95. 20V 1A £2. 75 20V 1A £2.20. 60V, 40V, 20V or 20-0-20V, 1A £3.50. 30-0-30 2A £7. AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £5; 250W £6; 400W £7; 500W £8. CHARGER TRANSFORMERS. Input 200/250V for 6 or 12V 1A £2.75; 4A £5.20. FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs 1A 40p; 2A 55p; 4A 85p. HALF WAVE 12V 1A 25p.	

GOODMAN'S COMPACT 12in BASS WOOFER

Standard 12in diameter fixing with cut sides 10 1/2in square, 14,000 gauss magnet, 30 watt r.m.s., 4 ohm impedance. Bass resonance; 30 c.p.s. Frequency response; 30-8,000 c.p.s. £10.95 each. Post £1.00. 20 Watt model £9.95.



ADAstra 3+3W STEREO AMPLIFIER.

10 Transistor Push-Pull Ready built with volume, treble and bass controls. 240V operated.



Size 8 x 3 x 6in. **£10.95**

HEATING ELEMENTS

Size 10 1/2 x 8 1/2 in Operating voltage 200/250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos.

ONLY **40p** EACH (FOUR FOR £1.50)

ALL POST PAID—Discounts for quantity.

E.M.I. 13 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover. Size 4 or 8 ohm

10W Model **£7.95** Post 45p

15W model **£10.50** Post 65p

20W model **£11.50** Post 75p


TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A" 20 x 13 x 12in. For 12in. dia. or 10in. speaker. Illustrated **£14.50** Post £1.60

MODEL "B" BOOKSHELF For 13 x 8in. EMI **£8.50** Post £1

R.C.S. BOOKSHELF complete with speakers. Size 14x9x6in. approx. Response 50 to 14,000 cps 6 watt rms 8 ohms **£16 pair** Post £1.30

ACOUSTIC WADDING 18in. wide, 20p ft.

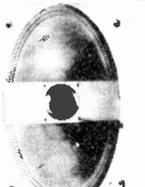

MONO PRE-AMPLIFIER

A mains operated solid state pre-amplifier unit designed to compliment amplifiers with low level phono and tape input stages. This free standing cabinet incorporates circuitry for automatic R.I.A.A. equalisation on magnetic phono input and N.A.B. equalisation for tape heads. Power ON/OFF, PHONO/TAPE switches and pilot lamp are on the front panel; phono socket input and output are rear located. AC mains 240V. Size 6 x 3 1/2 x 2in.



£4.50 ea. — 2 for £8. Post 50p.

BAKER MAJOR 12 INCH £15

30-14,500 c/s. 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W. NOTE: 4 or 8 or 16 ohms available.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle, 19 x 12in. instructions. As illustrated. **£19** Post £1.60

"BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos. Useful response 30-13,000 c/s. Bass Resonance 55 c/s.

GROUP "25"

12in 30W **£12** Post £1

GROUP "35"

12in 40W **£14** Post £1

GROUP 50/12in

12in 60W **£21** Post £1.60

GROUP 50/15in

15in 75W **£26** Post £1.60

Discs, Group + PA Cabinets in stock. Send for Leaflet, Cabinet Fittings, Handles, Corners, Feet, Covering Material all in stock.



BAKER 150 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

Ideal for Groups, Disco, P.A. and Musical Instruments. 4 inputs speech and music. 4 way mixing. Output 4/8/16 ohm. a.c. Mains 240V. Separate treble and bass controls. **£72** Carr. £1.50

NEW "DISCO 100 WATT"

ALL TRANSISTOR AMPLIFIER CHASSIS Carr. £1. 2 inputs. outputs separate volume treble and bass controls. Ideal disco or slave amplifier chassis. Made by Jennings BLACK CARRYING CABINET AVAILABLE £9.



PW SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three 1,000W channels. As featured in Practical Wireless **£14.00** CABINET extra £3.

GOODMANS CONE TWEETER

18,000 c/s. 25W 8 ohm. Price **£3.25**
E.M.I. 5in. mid range 25W £4.95.
E.M.I. 13 x 8in. 25W Bass Unit £10.50

R.C.S. 100 WATT VALVE AMPLIFIER CHASSIS



Professional model. Four inputs. Treble, Bass, Master Volume Controls. Ideal disco, P.A. or groups. S.A.E. for **£94** details. 5 speaker outputs. 3 or 8 or 15 ohm. 100V line to order. Suitable carrying case £16.50. plus £2.50 carr.

LOW VOLTAGE ELECTROLYTICS
1. 2. 4. 5. 8. 16. 25. 30. 50. 100. 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p. 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p; 2000mF 6V 25p; 25V 42p; 2500mF 50V 62p; 3000mF 25V 47p; 50V 65p; 3000mF 100V £1.60. 4700mF 63V £1.20. 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 5600mF 76V £1.80.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS

All parts and instructions with Zener diode, printed circuit rectifiers and double wound mains transformer. Input 200/240V a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required. **£2.95** Post 45p

R.C.S. POWER PACK KIT

12V, 750mA. Complete with printed circuit board and assembly instructions. **£3.35** Post 30p

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER—BRITISH MADE £1.45

Ideal for Mike, Tape, P.U., Guitar, Battery 9-12V or H.T. line 200-300V d.c. operation. Size 1 1/2 x 1 1/2 x 1 1/2 in. 25 c/s to 25 kc/s. 26 dB gain. For valve or transistor equipment. Instructions supplied.

ELECTRO MAGNETIC PENDULUM MECHANISM 95p

1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronome, strobe, etc.



BSR HI-FI AUTOCHANGER

Plays 12in, 10in or 7in records Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. a.c. 200/250V. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. Below motor board 2 1/2 in. With STEREO/MONO CARTRIDGE. **£12.95** All Post 75p

Single Player version £13.50. BSR P128 with Magnetic Cartridge **£24.50** GARRARD MINICHANGER plays all records **£9.95** BSR P163 BELT DRIVE DECK, less cartridge **£27.50**

BSR DE LUXE AUTOCHANGER

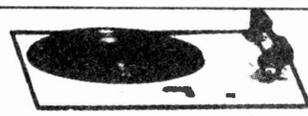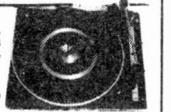Features balanced arm. Cusling device, stylus pressure gauge, 3 pressure plays all size records. Fitted with stereo ceramic cartridge. Size: 13 x 12ins. Post £1. With Sonotone V100 magnetic cartridge **£21.50**



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo compatible cartridge. Baseplate. Size 11 x 8 1/2 in. Turntable. Size 7in diameter. a.c. mains. 220/250V 3 speeds plays all size records **£7.95** Post 45p

HEAVY METAL PLINTHS

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Model "A". Size 12 1/2 x 14 1/2 x 7 1/2 in. Model "B". Size 16 x 13 1/2 x 7 in. £7.50. Extra Large Plinth and Cover. For transcription decks. Size 20 x 17 1/2 x 9 in. uncut board. Callers only £18.50. **£6.50** Post £1.30

TINTED PLASTIC COVERS ONLY

Sizes: "A"—14 1/2 x 12 1/2 x 4 1/2 in. £3. "B"—14 x 12 1/2 x 2 1/2 in. £3.50. "C"—16 1/2 x 14 1/2 x 3 in. £3.75. "D"—16 1/2 x 14 x 4 in. £4. "E"—18 x 14 1/2 x 4 1/2 in. £4. 15 x 13 1/2 x 3 in. £3.50. Ideal for record decks, tape decks, etc. Post 75p.

BAKER HI-FI SPEAKERS

HIGH QUALITY—BRITISH MADE

SUPERB £22

12in 25 watt Post £1.80

Quality loudspeaker. low cone resonance ensures clear reproduction of the deepest bass. Special copper drive and concentric tweeter cone. Full range reproduction with remarkable efficiency in the upper register.

| | |
|----------------------|---------------|
| Bass Resonance | 25 c/s |
| Flux Density | 16,500 gauss |
| Useful response | 20-17,000 c/s |
| 8 or 16 ohms models. | |

AUDITORIUM £21

12in 35 watt Post £1.60

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electronic organs. Ideal for Hi-Fi and Discotheques

| | |
|----------------------|---------------|
| Bass Resonance | 35 c/s |
| Flux Density | 15,000 gauss |
| Useful response | 25-16,000 c/s |
| 8 or 16 ohms models. | |

AUDITORIUM £26

15in 45 watt Post £1.60

BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2 in. sides, 6 x 4 in. 85p; 8 x 6 in. £1.40; 10 x 7 in. £1.55; 14 x 6 in. £1.90; 18 x 6 in. £1.95; 12 x 3 in. £1.20; 16 x 10 in. £2.20; 12 x 8 in. £1.70.

ALUMINIUM PANELS, 18 s.w.g. 6 x 4 in 20p; 8 x 6 in. 40p; 10 x 7 in. 50p; 12 x 5 in. 50p; 12 x 8 in. 50p; 16 x 6 in. 75p; 14 x 9 in. 80p; 12 x 12 in. 80p; 16 x 10 in. 95p.

ALUMINIUM ANGLE BRACKET, 6 x 1/2 x 3 in. 15p. ALUMINIUM BOXES, MANY SIZES IN STOCK. 4 x 2 x 2 in. 55p; 3 x 2 x 1 in. 55p; 6 x 4 x 2 in. 85p; 8 x 6 x 3 in. £1; 8 x 4 x 4 in. £1.20; 12 x 4 x 4 in. £1.50

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER

Suitable for cassettes, and all sizes of tape reels. a.c. mains 200/240V. Leaflet S.A.E. **£4.95** Post 40p



RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K. Tel. 01-684 1665

Minimum post 30p. Access/Eurocard and Barclaycard/Visa. Same day despatch. Radio Books and Components Lists 20p. Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)

SMALL ADS

The prepaid rate for classified advertisements is 18 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

RECEIVERS AND COMPONENTS

TTL AT NEW LOW PRICES INCLUDING VAT!

All full spec. by famous manufacturers

| | | | | | |
|----------|-----|----------|-------|---------|-------|
| 7400 | 13p | 7460 | 15p | 74141 | 58p |
| 7401/2/3 | 14p | 7472 | 22p | 74145 | 69p |
| 7404/5 | 16p | 7473/4/6 | 27p | 74150 | £1.09 |
| 7406 | 32p | 7485 | 43p | 74151 | 64p |
| 7408 | 18p | 7480 | 38p | 74153 | 63p |
| 7410/20 | 14p | 7483 | 70p | 74154 | £1.08 |
| 7411 | 18p | 7484 | 90p | 74155 | 67p |
| 7412 | 26p | 7485 | £1.00 | 74157 | 64p |
| 7413 | 30p | 7486 | 27p | 74160 | 75p |
| 7414 | 64p | 7489 | £2.20 | 74164 | £1.06 |
| 7417 | 27p | 7490/2/3 | 44p | 74174 | 94p |
| 7422 | 18p | 7491 | 58p | 74175 | 75p |
| 7425/7 | 27p | 7495 | 60p | 74181 | £2.56 |
| 7430 | 15p | 7496 | 73p | 74190 | £1.24 |
| 7432 | 24p | 74100 | 97p | 74191 | £1.06 |
| 7437 | 27p | 74107 | 31p | 74192/3 | £1.00 |
| 7440 | 14p | 74109 | 40p | 74195 | 67p |
| 7441 | 61p | 74121 | 31p | 74196 | 84p |
| 7442 | 54p | 74122 | 40p | IN4148 | 2p |
| 7445/7/8 | 75p | 74123 | 53p | DL707E | 69p |
| 7450/3/4 | 15p | 74125/6 | 44p | 2102A-6 | £2.50 |

S.A.E. for full lists. P. & P. (1st class) 20p. C.W.O.

J. C. JONES (PE28) Mail Order only.

46 Bursellars, St. Ives, Cambs., PE17 4XX.

VALVES - Radio, TV, industrial, transmitting. We dispatch to any part of the world by return of post, Air or Sea Mail. 2,700 types in stock. 1930 to 1976 obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers. Mon to Sat. 9.30-5.00, closed Wed. 1.00. We purchase all types of new and boxed valves. COX RADIO (Sussex) Ltd., Dept. P.E., The Parade, East Wittering, Sussex, PO20 8BN. West Wittering 2023. (STD code 024366).

P.C.Bs Paxolin 8 1/2 in x 7 in, 50p. 12 in x 8 in 70p. 17 1/2 in x 9 1/2 in, £1.15. Fibre glass double sided 7 in x 8 in, 90p. 12 in x 6 in, £1.20. 10 7/4 Series I.C.s on panels) 75p. Three assorted meters £2.40. T.V. Convergence panels, full of good gear, £1.50. S/Mica caps 100 assorted 75p. 300 Small components, Trans. Diodes £1.30. 7 lb Assorted components £2.85. List 15p. Refundable. Post 20p under £1. Insurance add 15p.

J. W. B. RADIO

2 Barnfield Crescent, Sale, Cheshire, M33 1NL

TRANSISTORS: BC107 8p, BC118 11p, BC132 10p, BC204B 10p, BC348 9p, BC351 10p, BD131 32p, BU205 £1.90, BU208 £2.10, ME1075 9p, TIP29 30p, XK1152 7p, ZTX212B 8p, ZTX502 9p.

DIODES: IS940 3p; BY126 10p, BY127 10p.

BRIDGE: IS 805 (1A/50V) 16p.

LINEAR I.C.: M252 B1 A £6.00.

CAPACITOR: (Mixed Dielectric) 0.1/600V 4p.

WIRE WOUND RESISTORS: 0.5 ohms to 2K 2.5W Radial Lead 5p, 5W Radial Lead 6p, 10W Axial Lead 7p, 15W Radial Lead 8p, 20W Radial Lead 10p.

HORIZONTAL PRESET: 1 Megohm 0.25W 12p. MIN ORDER £3.

K & A DISTRIBUTORS, 9 St. Peter's St, Syston, Leics. MAIL ORDER ONLY. P & P 25p.

LED's. Mixed bags of 4 different sizes and 4 different colours. 50 at 25-25, 100 at 29-25 including VAT and post and packing. C.W.O. MICHAEL WILLIAMS ELECTRONICS, 47 Vicarage Avenue, Cheshire Hulme, Cheshire SK8 7JP.

ORCHARD ELECTRONICS

I.C.s. TTL. C/MOS. Linear. Capacitors. Resistors (E12). SIL/Rectifiers. Diodes. LED. Thyristors. Zeners. Voltage Reg. DIL Sockets. Bridge Rectifiers. Potentiometers. Presets. Triacs. Diac. Plugs. Sockets. Cable. Vero. Carefully selected range, excellent despatch service. Same day turn round. S.A.E. List. Suppliers to A.E.R.E. U.K.A.E.A. Government Depts. Schools. Universities. Manufacturers. Accounts opened for trade and amateur. Join the professionals. Phone by 4 p.m. Goods out 1st class by 5 p.m. Try us and prove it!

ORCHARD ELECTRONICS

Flint House, High Street, Wallingford, Oxon
Telephone 0491-35529

TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains rewiring required. Insulated Touch Plates. Easy to follow instructions. TSD300K—TOUCHSWITCH and DIMMER combined.

- ONE touch plate to switch light on or off.
- Brightness controlled by small knob—£5.62
- TS300K—TOUCH SWITCH. TWO touch plates ON and OFF—£4.32
- TSA300K—AUTOMATIC. One touch plate. Light turns off after preset delay—£4.32
- LD300K LIGHT DIMMER KIT—£3.02

SPECIAL OFFER

LM3911 Thermometer Temperature Control IC £1.00

| TRIACS 400V Plastic | CMOS—LOW PRICES | TRANSFORMERS Miniature Mains |
|---------------------------|-----------------|------------------------------|
| 3A.....68p | 4001.....19p | 250V 100mA |
| 8.5A.....85p | 4007.....19p | 6.0-6V.....92p |
| 12A.....91p | 4011.....19p | 12.0-12V.....103p |
| 16A.....113p | 4015.....98p | 555.....39p (3 @ £1.08) |
| 20A.....178p | 4016.....55p | 741.....26p (5 @ £1.08) |
| 6.5A with trigger.....86p | 4017.....98p | 2N6027 (PUT).....37p |
| Diac.....23p | 4040.....106p | 2N3055.....43p |
| | 4049.....54p | CI060 5A/400V.....52p |

Clock 1kW Appliance Timer KIT inc AY 5 1230 0 5 LED display triac switches, box, pcb's etc. £17.55
AY 5-1230 Clock Appliance Timer IC £5.24

QUANTITY DISCOUNTS ON REQUEST

Prices inclusive of VAT. Add 25p. P. & P.

Mail order only to:

T. K. ELECTRONICS (PE)
106 Studley Grange Road, London W7 2LX

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., 103 South Brink, Wisbech, Cambs. Tel. 0945 4188. Immediate settlement.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 15V, 25V, 50V—0.47, 1.0, 2.2, 4.7 and 10µF 8p; 22, 47 5µF (50V); 100 7p (50V 8p); 220 8p (50V 10p); 470 11p (50V 16p); 1,000 (16V) 15p, 1,000 (25V) 18p, 1,000 (50V) 22p.
Subminiature Bead Tantalum Electrolytics—0.1, 0.22, 0.47, 1.0, 2.2 at 35V, 4.7/25V 11p; 10/25V 13p; 22/16V, 47/6V and 100/3V 15p.
Mullard Min. Ceramic E12 Series 63V 2%—10pF to 47pF—3p; 56pF to 330pF 4p.
Vertical Mounting Ceramic Plate 50V—E12 series 22-1,000pF and E6 series 1,000-47,000pF 2p.
Polystyrene E12 Series 63V Horizontal Mounting—10-1,000pF 3p; 1,200-10,000pF 4p.
Mullard Polyester 250V Vertical Mounting E6 Series—0.01-0.1 4p; 0.15, 0.22 5p; 0.33, 0.47 8p; 0.68 11p; 1.0 13p; 15 20p; 2.2 22p.
Mylar (Polyester) Film 100V Vertical Mounting—0.001, 0.002, 0.005 3p; 0.01, 0.02 4p; 0.04, 0.05 4 1/2p.
Carbon Film Miniature Resistors Highstab E12 Series 5%. Carbon Film Miniature Resistors 250V Vertical Mounting E6 Series—0.125W, 0.25W and 0.5W 10Ω to 2MΩ 1 1/2p. Metal Film 1W 27Ω to 10MΩ 2p.
IN4148 3p; IN4002 5p; IN4006 7p; IN4007 8p; BC107/8/9, BC147/8/9, BC157/8/9, BF194, 197 9p.
Fuses 20mm glass, 1 1/2 in glass, 1 in ceramic 2 1/2p.
Post 10p (free over £4). Prices inclusive of VAT.

THE C.R. SUPPLY CO.

127 Chesterfield Road, Sheffield S8 0RM

L.B. ELECTRONICS, MJE3055 40p, BF195 9p, BC213 9p, BC108C 10p, OCP70 16p, BXY49 38p, IN4148 4p, 3.3V, 24V, zeners 5p. 2102 (500NS) + data £1.50, 8080A £16, 1702A £7.50, CD4250 70p, 741 20p, 741 TO99 (DIL) 30p, 555 45p, 74H00 20p, 7 way DIL switches 60p, min push button switches (change over) 40p, 75450 30p, Fenwell Thermistors, pair potted + lead-plug 20p, PCB 1 watt amplifier LM 380 etc £1.20, ITT 5870ST nixi + data 50p, Sperry SP425-09 (9 digit 7 seg) + data £1, 747 6" (Red) £1.35, D.P.M. Display 4 1/2 digit (LED) with bezel £2.50. P & P 10p. L.B. ELECTRONICS, 43 Westcott, Hayes, Middx. UB4 8AH.

SOLAR CELLS

- 2.25" Dia. 250mW at 0.5V—£8.00
- 1.00" Dia. 35mW at 0.5V—£4.50
- 5.3 x 6.3mm 2.5mW at 0.5V—£1.25

Cells are supplied with leads attached and are coated with varnish. "Solar Cells" booklet 75p. Data sheets on above devices 20p. Mail Order only, Speedy service.

EDENCOMBS LIMITED

16 Princes Avenue, Kingsbury, London NW9 9JB

FML SPECIAL OFFERS.

Buy NOW while stocks last. PRICES INCLUDE V.A.T.

| | |
|---|--------|
| RESISTORS 1W 5% carbon film E24 range 10R-1M, 2p each, 100 of one value £1.05, 1000 of mixed 100s | £8.95 |
| E12 series pack 10R-1M, 10 of each value (610 resistors) | £6.40 |
| E24 series pack 10R-1M, 10 of each value (1210 resistors) | £12.70 |
| E12-E24 expansion packs 10 of each value (600 resistors) | £6.30 |

| | | | |
|--------------------|-----|------------|-----|
| TRANSISTORS | | | |
| BC107/8/9C | 10p | BC122/184L | 12p |
| BCY71 | 15p | BC212L | 12p |
| 2N2926G | 10p | 2N2926G | 11p |
| 2N3054 | 48p | 2N3055 | 48p |

| | | | |
|----------------------------|-------|-------------------------|-------|
| INTEGRATED CIRCUITS | | | |
| CA3089E I/F System | £1.99 | CA3090AQ Ster. Decoder | £3.99 |
| 741 8 pin DIL Op Amp | 26p | 748 LN Op Amp | 38p |
| 709 8 pin DIL Op Amp | 27p | 723 Voltage Regulator | 54p |
| LM3900 Quad Amp | 76p | LM380 2W Amp | 99p |
| LED's Red 3 or 5mm | 13p | Pack 10 LED's (seconds) | 89p |
| RECTIFIERS IN4001 | 5p | 1A/50V Bridge | 29p |

POLYESTER CAPACITORS (250V)
0.1µF 3p, 0.22µF 4p, 0.47µF 7p, 1.0µF 12p.
Please add 15p for Postage. Send 2 stamps for Catalogue.
BARCLAYCARD 'phone service available. Tel. 0473 50975.
FRASER-MANNING LTD.,
26 HERVEY STREET, IPSWICH, IP4 2ES.

MAINS TRANSFORMERS 240V Pri two separate secs each. TV at 500mA. £1.30 each + 35p P & P. Two for £2.40 + 55p P & P. NF ELECTRONICS, Church Lane, Flax Bourton, Bristol.

CHIPS AND THINGS

I.C.s at give-away prices!—you test you save!
Untested devices (NOT manufacturers rejects, faults etc.)

- PACK E1** (80% guaranteed good). 5 x MANK 0.127" 7 segment LED displays £1.00
- PACK E2** (100% good). 1 x 8 digit (plus overflow) 0.33" 7 segment Liquid Crystal calculator style display £2.95
- PACK M1** (100% guaranteed good). 2 x Calculator keyboards £1.00
- PACK D1** (80% guaranteed good). 15 x Logic I.C.s mainly dual J-K DTL flip-flops, compatible with TTL. Could replace those costly DTL flip-flops in most projects. £1.25
- PACK D2**. 25 x SN7400 type I.C.s. 100 two i/p nand gates. We guarantee 50 good. £1.25
- PACK L1** (marked and unmarked). 20 x Assorted Op-Amps. Could include LM301, 741, 709, 555 etc. £1.25
- PACK L2**. 20 x LM709 Op-Amps. (8 load 105) £1.50
- PACK M2** (No guarantees). 50 Minidip I.C.s for £1.00. Mostly unmarked. We don't know what they are. (At 2p each can you go wrong?)
Could be they are all O.K., but as they're untested—we don't know. For packs with no stated guaranteed minimum, we'll guarantee it works out much cheaper than average mail order prices bying this way. Satisfaction guaranteed or return complete pack for replacement or refund.

MAIL ORDER ONLY—NO CALLERS
Orders under £3.00 add 20p. P & P
CODESPEED, P.O. Box 23, 34 Seafield Road, Copnor, Portsmouth, Hants. PO3 5BJ.

CARBON FILM RESISTORS 5% E12 1/4W, 1/2W, 1W. Your mix, 90p—100. Metal Film 1/4W. £1.10—100. P & P 15p. Mail Order Only. CANDAR, 9 Galloway Close, Bletchley.

AERIALS

| | | | |
|--|--------|---------------------|--------|
| AERIALS FOR FM & TV Types for all Bands I to V available. | | | |
| TV UHF | | | |
| Fuba XC 391 | £38.90 | DX 87 Ch21-60 | £22.75 |
| DX43 Ch21-68 | £14.50 | Exa08 Panel Ch21-68 | £11.25 |
| FM | | | |
| Fuba Uka St. 8 | £33.33 | DX8-H | £22.75 |
| DX7-H | £19.00 | DX5-H | £12.50 |

All above have anodised alloy finish. Cables, Rotators, Masts, Lashing, M/H Amps, Dist. Amps etc., Carriage free mainland UK orders above £25. Carr. £1 otherwise. Audio Workshops Ltd., 33 London Road, Southborough, Tunbridge Wells, Kent, TN4 0PB. Tel: Tun. Wells (0892) 39222. Access/Barclaycard.

SERVICE SHEETS

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc. With free Fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc. 75p plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

AMATEUR CLUB

THE BRITISH AMATEUR ELECTRONICS CLUB for all interested in electronics. Four Newsletters a year with help and special offers for members. Major projects sponsored by the B.A.E.C. designed and made by members, currently the B.A.E.C. Z.80 Computer. Membership fee for 1978 £3.50 U.K. overseas £4.50 surface and £5.50 airmail payable in sterling. S.A.E. for details and application form to the Hon. Sec. J. G. Margetts, 42 Old Vicarage Green, Keynsham, Bristol.

EDUCATIONAL

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 272R, Intertext House, London SW8 4UJ.
Tel. 01-622 9911 (all hours)
State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 272R, Intertext House, London SW8 4UJ.
Tel. 01-622 9911 (all hours)
State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 272R, Intertext House, London SW8 4UJ.
Tel. 01-622 9911 (all hours)
State if under 18

COURSES—RADIO AMATEURS EXAMINATION. City and Guilds. Pass this important examination, and obtain your G8 licence, with an RRC Home Study Course. For details of this, and other courses (GCE, Professional Examinations etc) write or phone **THE RAPID RESULTS COLLEGE**, Dept. J.S.1, Tuition House, London SW19 4DS. Tel. 01-947 7272 (Careers Advisory Service) or for a prospectus only ring 01-946 1102. (24hr recording service).

TELEVISION TRAINING

12 MONTHS' full-time course in Radio and TV for beginners (GCE—or equivalent—in Maths and English).

26 WEEKS' full-time course in Mono and Colour TV (basic electronics knowledge essential).

13 WEEKS' full-time course in Colour TV (Mono TV knowledge essential).

These courses incorporate a high percentage of practical training.

Next session starts on January 3rd.

Prospectus from London Electronics College, Dept. A1, 20 Penywern Road, London SW5 9SU. Telephone 01-373 8721

ELECTRICAL

STYLI, CARTRIDGES, AUDIO LEADS etc. For keenest prices send S.A.E. for free list to: **FELSTEAD ELECTRONICS (PE)**, Longley Lane, Gatley Cheshire, Cheshire, SK8 4EE.

WANTED

WANTED-NEW VALVES, Transistors. Top Prices, popular types. **KENINGTON SUPPLIES**, (B) 367 Kensington Street, Bradford 8, Yorkshire.

ORIGINAL OR COPY. Darkroom Timer Plan. P.E. January 1965. Potters Bar (0707) 54856.

SITUATIONS VACANT

RADIO TECHNICIANS

Government Communications Headquarters has vacancies for Radio Technicians. Applicants should be 19 or over.

Standards required call for a sound knowledge of the principles of electricity and radio, together with 2 years experience of using and maintaining radio and electronic test gear.

Duties cover highly skilled telecommunications/electronic work, including the construction, installation, maintenance and testing of radio and radar telecommunications equipment and advanced computer and analytic machinery.

Qualifications: Candidates must hold either the City and Guilds Telecommunications Part 1 (Intermediate) Certificate or equivalent HM Forces qualifications.

Salary scale from £2,230 at 19 to £2,905 at 25 (highest pay on entry) rising to £3,385 with opportunity for advancement to higher grades up to £3,780 with a few posts carrying still higher salaries. Pay supplements total between £443 and £522 per annum.

Annual leave allowance is 4 weeks rising to 6 weeks after 27 years service.


Opportunities for service overseas.

Candidates must be UK residents.

Further particulars and application forms available from:
Recruitment Officer, Government Communications Headquarters
Oakley, Priors Road, Cheltenham, Glos. GL52 5AJ
Tel.: Cheltenham (0242) 21491 (Ext. 2270)

FOR SALE

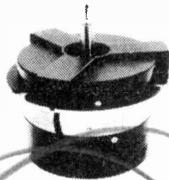NEW ISSUES of "Practical Electronics" available from April 1974 edition up to date. Price 65p each. Post free. **BELL'S TELEVISION SERVICES**, 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.



BUILD YOUR OWN HIGH QUALITY TURNTABLE

Direct Drive Turntable Motors and Die Cast Turntables. £17.50 incl. VAT. SAE for details. Frequency Generator D.C. Servo Motors for Belt Drive Turntables. As used by many well known makers. £3.50 incl. VAT. SAE for details. Selection of External Rotor A.C. Motors as used on top quality tape recorders. Spooling motors and capstan motors from £2.50. SAE for details.

SYMOT LIMITED, 22a Reading Road, Henley-on-Thames, Oxon RG9 1AG. (Tel. (04912) 2663).

SYNTHESISER in Cabinet. (Needs attention), 37 note K.B.D. and contacts + cab. Tel: Wolverhampton 732306.

P. E. MULTIMETER

P.C. BOARD SET £2.65 inc.
LD130 - £5.50 inc., Switch Set £12.18.

Complete Kits £42.50.

S.A.E. for details:

SPARKS DEVELOPMENTS

53 North Street, Melbourne, Derby.

COMPLETE SET OF PRACTICAL ELECTRONICS from Vol. 1 No. 1 (Nov. 64) to date. Offers Box. No. 72.

MICROPROCESSOR KIT (SC/MP Introkit & Keyboard Kit). New, unopened. Details in Nov. 76 PE. Offers - Tel: Glossop 4015.

BOOKS AND PUBLICATIONS

SIMPLIFIED TV Repairs. Full repair instructions individual British sets £4.50, request free circuit diagram. Stamp brings details unique. **TV PUBLICATIONS** (Ausepe), 76 Church Street, Larkhall, Lanarkshire.

MISCELLANEOUS

ARMATURE AND COIL WINDING ENAMELLED COPPER WIRE

Only top quality materials supplied. All orders despatched within 24 hours.

| S.W.G. | 1 lb reel | 1/2 lb reel |
|----------|-----------|-------------|
| 10 to 19 | £2.95 | £1.60 |
| 20 to 29 | £3.15 | £1.80 |
| 30 to 34 | £3.45 | £1.90 |
| 35 to 40 | £3.65 | £2.10 |

All prices inclusive of P. & P. in U.K.

COPPER SUPPLIES
102 Parrswood Road, Withington, Manchester 20 Telephone 061-445 8753

INVENTORS. "Profit from Your Invention". Sources of Finance and other assistance. Details: Large S.A.E. DELTA (PE), 15 St. Mary Street, Southampton, Hants.

MAKE YOUR OWN PRINTED CIRCUITS

RUB-ON TRANSFERS - Starter pack (5 sheets, lines, pads, I.C. pads) £1.30, Single Sheets 27p. **FERRIC CHLORIDE** - 1 lb bags 70p (P. & P. 40p). **SOLDERCON SOCKETS** - 100 65p. (quantity rates). **PLASTIC SUPPORTS** - 7 or 8 hole 6p./pair. S.A.E. lists sample. P. & P. 15p/order except*.

P.K.G. ELECTRONICS

OAK LODGE, TANSLEY, DERBYSHIRE

100 WATT GUITAR/PA/Music Amplifier superb treble bass overdrive slimline solidstate. 2 months guarantee unbeatable offer at £39. Money returned if not absolutely delighted within 7 days. Send cheque or P.O. to: **WILLIAMSON AMPLIFICATION**, 62 Thorncliffe Avenue, Dukinfield, Cheshire.

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £9.75 plus 25p P. & P.

'Brain-Freeze' 'em with a **MINI-STROBE** Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4.30 plus 20p P. & P. Experiment with a psychedelic **DREAM LAB**, or pick up faint speech/sounds with the **BIG EAR** sound-catcher; ready-made multi-function modules. £5 each plus 20p P. & P.

LOTS MORE! Send 20p for lists. Prices include VAT. (Mail order U.K. only).

BOFFIN PROJECTS

Cunliffe Road, Stoneleigh
Ewell, Surrey (P.E.)

100 Resistors 75p

1/2W 5% c/FILM 2-2Ω-2.2MΩ (E12)
10 each of any value. Send S.A.E. for free sample

C60 CASSETTES 30p
C90 CASSETTES 45p

All Cassettes in Plastic Case with Index and Screwed Assembly

All prices include VAT.

Add Postage 10p in £1

Quantity Discounts
10 Units 5%
50 Units 7%
100 Units 10%

SALOP ELECTRONICS
23 WYLE COP
SHREWSBURY
Tel. 53206

OUTSTANDING 2200 HI-FI FM TUNER. Full Coverage 88-102MHz. Varicap tuning. Latest silicon superhet design. Ideal for push button/manual tuning. Only £9.95. Unique 3300 stereo class A amplifier, power 32 watts peak, complete stereo pre-amplifier, 2 power amplifiers, all inputs accepted. Only £10.95. 5500 Tuner amplifier, specification as above 2. Only £19.95. All equipment built, tested & guaranteed with full instructions (P&P 50p). **GREGG ELECTRONICS**, 86-88 Parchmore Road, Thornton Heath, Surrey.

DIRECT READING FREQUENCY METER



- ★ Complete kit £29.50
- ★ Linear scale
- ★ 6 ranges up to 100 KHz
- ★ Accepts any waveform
- ★ Easy to calibrate—quartz standard supplied on loan.

Send S.A.E. for details to: James Cooper (Elec.) Ltd.
120 Castle Lane, Solihull, Warwickshire.

HIGH ENERGY LITHIUM BATTERIES outperform conventional dry cells for less volume and weight. Remarkable voltage stability, long shelf life. S.A.E. for details: **HIRST JACOBSON LTD.**, 91 Marylebone High Street, London W.1.

THE FABULOUS D2 MICROPROCESSOR EVALUATION KIT FROM MOTOROLA.

Featuring *24 key keyboard *Seven segment display *Cassette interface *Erom & Ram Expandable *Interface Capability *Full Documentation *5 Volt power supply Required *One years FREE membership of The Amateur Computer Club with every purchase*. £176 + £1.50 P & P + 8% VAT.

ENAMELLED COPPER WIRE

| SWG | 1 lb | 8 oz | 4 oz | 2 oz |
|-------|-------|------|------|------|
| 14-19 | 2.60 | 1.40 | .66 | .55 |
| 20-29 | 2.80 | 1.60 | .85 | .65 |
| 30-34 | 3.00 | 1.70 | .95 | .70 |
| 35-40 | 3.35 | 1.90 | 1.10 | .79 |
| 40-43 | 4.50 | 2.50 | 1.90 | 1.25 |
| 44-46 | 5.00 | 3.00 | 2.10 | 1.65 |
| 47 | 8.00 | 5.00 | 3.00 | 1.76 |
| 48 | 15.00 | 9.00 | 6.00 | 3.30 |

Tinned Copper, Even Gauges 14-30 £3 per lb. Multicore 60/40 Solder 18SWG £3.24 per lb. Prices include P & P and VAT. SAE brings list of copper and resistance Wires.

THE SCIENTIFIC WIRE COMPANY

PO Box 30 London E.4.
Reg. Office, 22 Coningsby Gdns.

GLASS FIBRE P.C.B.'s

From your own tape, film or ink master. Send S.A.E. for quotation. **PRACTICAL ELECTRONICS P.C.B.'s** in glass fibre, tinned and drilled. Complete set of Radio Control boards, June to Aug. 76 £5.80p. Cross Hatch Generator £2.85p. May 77 Burglar Alarm (1305-1) £1.68. June 77 Sports Centre (1306-1) and power supply p.c.b. £2.66. July 77 Digital Stopwatch (1307-1) £1. Oscilloscope trace doubler 95p. Earth Leakage C.B. (1307-2) £1.96p. Aug. 77 C/R Meter (1308-1) 97p. Sept. 77 Freq. Counter Timer (1309-2/3) £3.98 set of two boards. Scope Probe (1309-1) 56p. Oct. 77 Digital Multimeter (1401-1/2) £3.15, set of two boards. Guitar Sustain (1410-3) 55p. Send S.A.E. for information on current boards and a full list. C.W.O. please.

PROTO DESIGN

4 Highcliffe Way, Wickford, Essex SS11 8LA

BUILD YOUR OWN TV CAMERA



ONLY KNOWN HIGH PERFORMANCE SOLID STATE CAMERA IN KIT FORM. Also available factory assembled. Ideal for experimenters, industry security, education etc. *Will work with most other CCTV equipment. *Fully guaranteed. *Completely self-contained. With our modulator will connect to any domestic TV set. Model C1 complete with Vidicon E99. Less Vidicon E82.35. (Lens available as optional extra). SAE for info or phone your order through using your Barclay or Access Card.

CROFTON ELECTRONICS LIMITED

35 Grosvenor Road, Twickenham, Middlesex. 01 - 891 1923

CLEARING LABORATORY. Scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.N.U.s, sweep generators, test equipment, etc. Tel. Lower Beeding 236.

CABINET FITTINGS

FOR

Stage Loudspeakers and Amplifier Cabs
Fretcloths, Coverings, Strap & Recess Handles, Feet, Castors, Jacks & Sockets, Cannons, Bulgin 8 ways, Reverb Trays, Locks & Hinges, Corners, Trim, Speaker Bolts etc.

Send 2 x 9p Stamps for samples and list.

ADAM HALL (P.E. SUPPLIES)
Unit 6, Starline Works, Grainger Road
Southend-on-Sea, Essex.

BUILD THE TREASURE TRACER

MK III Metal Locator

- Varicap tuning
- Britain a best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- 4,000 already sold
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screw-driver, pliers and snips
- As seen on BBC-1 and BBC 2 TV

Send stamped, addressed envelope for leaflet

| | | | |
|--------------|-----------|------------------|-----------|
| Complete Kit | £15.95 | Built and tested | £20.95 |
| Post £1.20 | £1.37 VAT | Post £1.20 | £1.77 VAT |

MINIKITS ELECTRONICS 6g CLEVELAND ROAD
LONDON E18 2AN (Mail Order Only)

AMPEX FR1200 24 track instrumentation recorder, six speed, solid state, inc. tapes etc. Ideal for use with microprocessor or conversion to Audio. £400. Dursley 3768.

DEWTRON SYNTHESIZER Modules for sale, VCO's, P-V, SEQ etc. Mostly unused. Dursley 3768.

SINTEL FOR BOOKS, CMOS AND COMPONENTS

6800 Booklet 1.80, MOT CMOS Databk 3.50, 6800 Appl Man 12.95, 6800 Prog Man 5.35, SC/MP Intrakit Man 0.75 NS TTL Databk 2.10, RCA CMOS Databk 5.45, 8085 User's Man 5.15, Z80 Ass Lang Prog Man 7.50, Z80 CPU Man 5.60, Z80 CTC Spec 0.80, Z80 P10 Man 3.30. Also a full range of CMOS - send for free catalogue. MPUs: MEK6800D2 205.20, MC6820 8.66, Z80 30.72, Z80A 39.94, Z80CTC 13.82, Z80P10 13.82, Memories: 2102-A 2.55, 2112A-4 3.13. Displays: Type FND500 C.C. 1.40, Type TL321 C.A. 1.61, 5LTO1 5.29. Crystals: 32.768KHz 3.78, 5.12MHz 3.89. Clock ICs: AY51202 4.35, AY51224 3.78, MK50253 6.05. Soldercan Pins: 100 0.54, 1000 4.32, 3000 11.34. Free catalogue by return. All items C.W.O. Prices inclusive of VAT. Add 35p p&p. SINTEL, P.O. Box 758, 209 Cowley Road, Oxford. Tel. (0865) 49791

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p, chassis punching facilities at very competitive prices. 400 models to choose from, free literature (stamp would be appreciated). **BAZELLI**, Dept. No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

H. M. ELECTRONICS
275s Fulwood Road, Broomhill, Sheffield S10 3BD

Give your project that professional looking finish. Build it in a BEC. Dry transfer lettering now available...

BEC CABINETS

.ORION Cabinet still available punched or unpunched. Send 15p (refundable) for leaflets.

LOW COST BOXES, Instrument cases, aluminium, self tapping screws, BA nuts bolts and washers. Send a stamped self addressed envelope for pamphlet to **HARRISON BROS.** P.O. Box 55, Westcliffe-on-Sea, Essex SS0 7LQ.

BURGLAR ALARM equipment, safes, trade supplies. **ASTRO-ALARMS**, 25 Stockton Rd., Sunderland. Tyne and Wear. Tel.: 77825. Free list S.A.K.

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware. Printed circuit boards, top quality for individual designs. Prompt service. Send 25p for catalogue. From:

RAMAR CONSTRUCTOR SERVICES,
Masons Road, Stratford upon Avon, Warwicks.
Tel. 4879.

PRINTED CIRCUIT BOARDS supplied in glass fibre, drilled, tinned or varnished, from your own or published designs. Send S.A.E. for quotations. **UNIVERSAL APPLICATIONS**, 12 Whiteoaks Road, Oadby, Leicester.

LADDERS

LADDERS. Varnished 25ft extd. £30-41. Carr. £1-90. Leaflet. Immed. despatch. **THE LADDER CENTRE (PEE3)**, Halesfield (1), Telford, Salop. Tel. 586644.

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

PLEASE
MENTION
PRACTICAL
ELECTRONICS
WHEN
REPLYING TO
ADVERTISEMENTS

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour T.V. Servicing
- Electronic Engineering & Maintenance
- Computer Engineering and Programming
- Radio, T.V. and Audio, Engineering & Servicing
- Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name _____

Address _____

Age _____

ICS

To ICS, Dept. 273R, Intertext House,
London SW8 4UJ
or telephone 01-622 9911 (all hours)



VERO

For the Professional Amateur

Veroboard can offer a complete package to help you build your product to a truly professional standard. Full range of veroboards, accessories and housings. Please send 10p plus S.A.E., size 7" x 9" for catalogue.

Veroboard Limited, Industrial Estate,
Chandler's Ford, Eastleigh, Hampshire, SO5 3Z.
Telephone: (04215) 2956 Telex 47551 VEROEL G
Available worldwide through 3 subsidiary Companies and 25 Agents.

FREE CATALOGUE/ORDER FORM SEND S.A.E.

500+ Top quality Transistors, I.C's, Resistors, Capacitors, Plugs/Sockets, Veroboard/cases, Indicators, Knobs, Switches, Wire and Books at prices you can afford.

| | | | |
|----------------------------------|----------------------------------|-------------------------------------|------------------------------------|
| 741
ONLY
30p | 555
ONLY
50p | TIL209
ONLY
15p | IN4001
ONLY
5p |
|----------------------------------|----------------------------------|-------------------------------------|------------------------------------|

All prices include VAT. P&P FREE over £2.

Name _____
Address _____

Get an ACE up your sleeve!

ACE MAILTRONIX LTD
Dept. PE Tootal Street
Wakefield, W. Yorkshire WF1 5JR

Mail Order Protection Scheme

The Publishers of *Practical Electronics* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Practical Electronics* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence. For the purpose of this scheme, mail order advertising is defined as—

'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.

| | | | | | |
|--|---|---|---|--|---|
| TTLs by TEXAS
7400 14p 17412 80p
7401 14p 74118 210p
7402 18p 74118 180p
7403 18p 74119 220p
7404 24p 74120 130p
7405 25p 74121 33p
7406 43p 74122 75p
7407 43p 74123 75p
7408 22p 74125 70p
7409 22p 74126 65p
7410 18p 74126 63p
7411 28p 74132 81p
7412 25p 74136 100p
7413 46p 74141 85p
7414 85p 74142 300p
7415 40p 74145 95p
7416 40p 74147 100p
7417 40p 74148 100p
7420 15p 74150 130p
7421 30p 74151 81p
7422 28p 74153 81p
7423 28p 74154 100p
7425 33p 74155 97p
7426 43p 74156 97p
7427 46p 74157 97p
7428 40p 74159 250p
7430 18p 74160 90p
7432 37p 74161 130p
7433 43p 74166 130p
7437 37p 74163 130p
7438 37p 74164 120p
7440 18p 74165 100p
7441 85p 74167 320p
7442 75p 74167 320p
7443 120p 74170 200p
7444 120p 74172 750p
7445 100p 74173 100p
7446 100p 74174 130p
7447 73p 74175 97p
7448 85p 74176 130p
7450 18p 74177 100p
7451 18p 74180 100p
7453 18p 74181 32p
7454 18p 74182 150p
7460 18p 74184 250p
7470 38p 74185 100p
7472 32p 74186 90p
7473 30p 74190 140p
7474 37p 74191 140p
7475 43p 74192 120p
7476 37p 74193 120p
7480 54p 74194 180p
7481 100p 74195 110p
7482 90p 74197 130p
7483 99p 74197 130p
7484 100p 74198 270p
7485 120p 74199 210p
7486 30p 74201 175p
7489 340p 74251 150p
7490 30p 74255 87p
7491 80p 74278 200p
7492 150p 74279 200p
7493 38p 74283 220p
7494 90p 74284 470p
7495 75p 74285 470p
7496 80p 74290 100p
7497 200p 74293 100p
74100 140p 74298 220p
74104 75p 74305 100p
74105 75p 74306 100p
74107 30p 74307 100p
74109 80p 74309 220p
74110 80p 74313 240p
74111 75p 74490 250p | CMOS I.C.s.
4000 21p
4001 21p
4002 21p
4008 127p
4007 21p
4008 100p
4010 87p
4011 21p
4012 23p
4013 55p
4014 90p
4015 90p
4016 90p
4017 120p
4018 110p
4019 97p
4020 140p
4021 120p
4022 140p
4023 23p
4024 23p
4025 23p
4026 23p
4027 84p
4028 110p
4029 110p
4030 110p
4031 87p
4032 87p
4033 100p
4034 100p
4035 120p
4036 120p
4037 120p
4038 120p
4039 120p
4040 120p
4041 120p
4042 120p
4043 120p
4044 120p
4045 120p
4046 120p
4047 120p
4048 120p
4049 84p
4050 120p
4051 120p
4052 120p
4053 120p
4054 120p
4055 120p
4056 145p
4057 130p
4058 130p
4059 38p
4060 38p
4061 38p
4062 38p
4063 38p
4064 38p
4065 38p
4066 38p
4067 38p
4068 38p
4069 38p
4070 38p
4071 38p
4072 38p
4073 45p
4074 45p
4075 45p
4076 45p
4077 45p
4078 45p
4079 45p
4080 45p
4081 45p
4082 45p
4083 45p
4084 45p
4085 45p
4086 45p
4087 45p
4088 45p
4089 45p
4090 45p
4091 45p
4092 45p
4093 45p
4094 45p
4095 45p
4096 45p
4097 45p
4098 45p
4099 45p
4100 45p
4101 45p
4102 45p
4103 45p
4104 45p
4105 45p
4106 45p
4107 45p
4108 45p
4109 45p
4110 45p
4111 45p | OP. AMPS.
CA3130 100p
CA3140 100p
CA3160 120p
LM318 74p
LM319 74p
LM324N 77p
MC1458P 75p
LINEAR I.C.s.
AY-10212 650p
AY-3-8500 775p
CA3026A 112p
CA3046 85p
CA3048 250p
CA3053 75p
CA3085 300p
CA3080E 87p
CA3089E 250p
CA3090AE 425p
ICL8038CC 400p
LM339N 175p
LM339N 200p
LM339N 112p
LM339N 100p
LM339N 150p
LM339N 150p
M525AA 850p
MC1310P 112p
MC1351P 110p
MC1495L 87p
MC1496L 112p
MC3340P 100p
MC3360P 100p
VOLTAGE REGULATORS—Fixed
Plastic—TO220—3 Terminals
1 Amp +ve 1 Amp -ve
5V 7805 115p 5V 7905 160p
6V 7806 115p 6V 7906 160p
8V 7808 115p 8V 7908 160p
12V 7812 115p 12V 7912 160p
15V 7815 115p 15V 7915 160p
24V 7824 115p 24V 7924 160p
Heat Sink 17 1/2 W suitable for TO220 25p
100mA +ve TO92 100mA -ve TO92
5V 78L05 70p 5V 79L05 90p
6-2V 78L62 70p 5V 79L62 90p
12V 78L12 70p 12V 79L12 90p
15V 78L15 70p 15V 79L15 90p
LM309K TO3 150p MC1468 DIL 300p
LM323K TO3 700p TB625B TO5 120p
LM327N DIL 275p 7805K TO3 150p
VARIABLE:
723 DIL 45p LM317 TO220 325p
78MG2C DIL 145p TL430 TO92 70p
OPTO-ELECTRONICS
OCF71 190p LEDs
ORP12 100p TL1208 Red 140p
ORP60 90p TL1211 Green 22p
ORP81 90p TL132 Infrared 61p
ORP77 40p 0-2in Red 81p
0-2in Green 20p
0-2in Amber 30p
DRIVERS
Minitron 300p 15401 84p
FN0500/507 Red 130p 75492 30p
DL70A Red/Green 100p 9368 200p
DL707 Red/Green 100p 9370 200p
DL747 Red/Green 250p 9374 200p
TL321/2 Red 130p | MEMORY I.C.s.
AD210 625p 4801 550p
D4288 900p 1702A 800p
B4702A £12 2102-2 216p
P4002-1 485p 2107 804p
P4201A 400p 212-2 450p
P428 410p 8000A £14
P205 300p A75-1013 650p
P5101-8 500p R03-2513 850p
LOW PROFILE DIL SOCKETS BY TEXAS
8 pin 12p 22 pin 30p
14 pin 13p 24 pin 40p
16 pin 14p 28 pin 40p
54 pin 30p 40 pin 60p
TRANSISTORS
AC125/6 20p BDY56 225p
AC127/8 20p BF167 25p
AC176 20p BF170 25p
AC187/8 20p BF173 27p
AD181 40p BF178 30p
AD181 40p BF179 35p
AD182 40p BF180-1 35p
AF114/5 20p BF184/5 24p
AF116/7 20p BF184 13p
AF127 40p BF195 11p
AF139 40p BF196 17p
AF239 40p BF197 19p
BC107/B 70p BF200 40p
BC108/B 10p BF248 40p
BC109 10p BF258 60p
BC109C 11p BF257 34p
BC147 9p BF258 39p
BC148 8p BF259 40p
BC157 11p BF337 32p
BC158/9 11p BFR39 34p
BC169C 15p BFR40-1 34p
BC172 11p BFR79 34p
BC177 20p BFR80-1 34p
BC178 17p BFR88 37p
BC179 20p BFW10 30p
BC182/3 12p BFX30 34p
BC184 14p BFX84-5 30p
BC187 32p BFX86-7 30p
BC192 15p BFX88 34p
BC213 12p BFX90 32p
BC214 18p BFX51 22p
BC481 40p BFX52 22p
BC478 32p BFX59 90p
BCY70 20p BRY38 30p
BCY71 24p BSX19/20 20p
BD124 100p MJE340 70p
BD131/2 85p MJE481 175p
BD135/6 54p MJE491 210p
BD139 50p MJE501 250p
BD140 60p MJE295 130p
MJE295 130p
MJE305 90p
MJE1025 45p
MPE104/5 40p
MPSA06 37p
MPSA12 82p
MPSA06 £14
MPSU05 72p
MPSU06 72p
MPSU55 90p
MPSU56 90p
OC28 90p
OC35 90p
OC71 35p
R2000B 225p
R2010B 225p
TIP29A 50p
TIP29C 82p
TIP29E 90p
TIP30C 72p
TIP31A 50p
TIP31C 50p
TIP32A 53p
TIP32C 85p
TIP33A 87p
TIP33C 120p
TIP34A 124p
TIP34C 100p
TIP35A 243p
TIP35C 290p
TIP36A 237p
TIP36C 200p
TIP41A 70p
TIP41C 84p
TIP42A 70p
TIP42C 90p
TIP295 70p
TIP305 60p
2N897 25p
2N898 43p
2N706/8 22p
2N918 43p
2N930 30p
2N131/2 25p
2N1304/5 75p
2N1306/7 75p
2N1613 22p
2N1711 22p
2N1893 32p
2N1902 60p
2N2180 120p
2N2219 22p
2N2222 22p
2N1306/7 75p
2N2484 15p
2N2646 50p
2N2904/A 22p
2N2905/A 22p
2N2906/A 22p
2N2907/A 25p
2N2928B 9p | DIODES
BY127 12p
OA47 9p
OA81 15p
OA85 15p
OA90 9p
OA91 9p
OA95 9p
OA200 9p
OA202 10p
1N914 4p
1N916 7p
1N4001/2 6p
1N4003/4 7p
1N4005/7 8p
1N4148 4p
1N5401/3 15p
1N5407/2 15p
TRIACS
Plastic
3A 400V 85p
6A 400V 107p
6A 50V 27p
10A 50V 140p
10A 500V 100p
15A 400V 200p
15A 500V 225p
40A 50V 130p
BR100 36p
ZENERS
2-7V-33V
400mW 11p
1W 22p
1A 50V TO5 85p
1A 400V TO5 95p
3A 400V STUD 100p
12A 400V Plastic 180p
16A 400V Plastic 220p
16A 600V Plastic 270p
BT108 1A 700V STUD 130p
C106D 4A 400V Plastic 43p
MCR181 1A 15V TO92 42p
2N3325 5A 400V TO92 120p
2N4444 8A 800V Plastic 200p
2N5062 0-8A 30V TO92 36p
2N5062 0-8A 100V TO92 40p
2N5064 0-8A 200V TO92 43p | BRIDGE RECTIFIERS
1A 50V 25p
1A 100V 27p
1A 400V 31p
2A 50V 40p
2A 100V 48p
2A 200V 58p
3A 200V 70p
3A 600V 80p
4A 100V 90p
4A 200V 95p
6A 50V 90p
6A 100V 100p
6A 500V 120p
2A 200V 58p
2A 400V 43p
SCR THYRISTORS
1A 50V TO5 85p
1A 400V TO5 95p
3A 400V STUD 100p
12A 400V Plastic 180p
16A 400V Plastic 220p
16A 600V Plastic 270p
BT108 1A 700V STUD 130p
C106D 4A 400V Plastic 43p
MCR181 1A 15V TO92 42p
2N3325 5A 400V TO92 120p
2N4444 8A 800V Plastic 200p
2N5062 0-8A 30V TO92 36p
2N5062 0-8A 100V TO92 40p
2N5064 0-8A 200V TO92 43p |
|--|---|---|---|--|---|

MCM6810
128 x 8 STATIC RAM
24 pin DIL £4.32

ZN425E
£4.20

PLEASE SEND SAE FOR OUR CATALOGUE

VAT INCLUSIVE PRICES—ADD 25p P. & P.—No other extras

MAIL ORDER ONLY
TECHNOMATIC LTD.
54 SANDHURST ROAD, LONDON NW9
Govt., Colleges orders accepted
Tel: 01-204 4333
Telex: 922800

INDEX TO ADVERTISERS

| | | |
|--|---|---------------------------------------|
| Ace Maitronix Ltd. 383 | E.D.A. 315 | Phononics 318, 319 |
| Adam Hall (P.E. Supplies) 382 | Edencombe Ltd. 380 | Pinner Electronics 374 |
| Advanced Electronic Applications 370 | Electronic Brokers 365 | Progressive Radio 364 |
| Aitken Bros. 378 | Electrovalue Ltd. 370 | Proto Design 382 |
| Alben Engineering 306 | Fraser-Manning Ltd. 380 | Radio Component Specialists 379 |
| Alcon Instruments 311 | Government Agencies | Radio and T.V. Components 338 |
| Ametek 310 | Headquarters 381 | Ramar Constructor Service 382 |
| Astra-Pak 338 | Greenwell Electronics 374 | R.S.T. Valve Mail Order 378 |
| Audio Workshops Ltd. 380 | H. M. Electronics 382 | Salop Electronics 382 |
| Bamber B. Electronics 376 | Harversons 372 | Saxon Entertainments 314, 315 |
| Bandridge Ltd 320 | Heathkit Ltd 375 | Scientific Wire Co. 382 |
| Baron 308 | Home Radio 372 | Sentinel Supply 319 |
| Barrie Electronics 378 | I.C.S. Intertext 381, 383 | Service Trading Co. cover iii |
| Bib Hi-Fi 370 | I.L.P. Electronics 363, 377 | Sintel Limited 382 |
| Bi-Pak 316, 317 | J. C. Jones 380 | Sparks Developments 381 |
| Birkett J 376 | J. W. B. Radio 380 | S.S.T. Distributors 319 |
| Boffin Projects 381 | James Cooper (Electronics) Ltd. 382 | Stirling Sound 307 |
| Brewster S & R 312 | K & A Distributors 380 | Sugden A. R. 308 |
| British National Radio & Electronics | London Electronics College 381 | Swanley Electronics 364 |
| School 313, 365 | Lynx Electronics 375 | Symot Limited 381 |
| Butterworths 306 | Maplin Electronic Supplies cover iv | Tamba Electronics 368 |
| Cambridge Learning 311 | Marshall A. & Sons 369 | Technomatic Ltd. 312, 384 |
| Chromatronics 367 | Microsystems '78 373 | Tempus 374 |
| Clef Products 338 | Mikinitis Electronics 382 | Tirro Electronics 376 |
| Component Centre, The 310 | Modern Book Co. 364 | T.K. Electronics 380 |
| Computabits Ltd 374 | Orchard Electronics 380 | Trampus Electronics Ltd 365 |
| Continental Specialties 337 | Osmabet 364 | T.U.A.C. 309 |
| Codespeed 380 | P.B. Electronics 371 | Vero Electronics 383 |
| Copper Supplies 381 | P.K.G. Electronics 381 | Watford Electronics cover ii |
| Crescent Radio Ltd 312 | Phoenix Electronics Ltd. 368 | West London Direct Supplies 338 |
| Crimson Elektrik 310 | | Wilmslow Audio 311 |
| Crofton Electronics 368, 382 | | Xeroza Radio 372 |
| C. R. Supply Co. 380 | | |
| Dziubas M. 306 | | |
| Eaton Audio 370 | | |

RELAYS SIEMENS, PLESSEY, etc. MINIATURE RELAYS

RELAYS. WIDE RANGE OF A.C. and D.C. RELAYS AVAILABLE from stock—phone or write in your enquiries

FT3 NEON FLASH TUBE


High intensity multi turn high voltage neon glow discharge flash tube. Design for ignition timing etc. £1.50. P & P 25p (£1.89 inc VAT). 3 for £3. P & P 50p (£3.78 inc VAT & P.)

| NI-CAD BATTERIES | Height (mm) | Width (mm) | Length (mm) |
|------------------------------|-------------|------------|-------------|
| 23AH 1.2V Plastic Case £4.86 | 214 | 79 | 27 |
| 35AH 1.2V Metal £7.56 | 219 | 75 | 29 |
| 40AH 1.2V Plastic Case £9.18 | 275 | 80 | 35 |

Post 50p per unit

21 WAY SELECTOR SWITCH WITH RESET COIL. The ingenious electro-mechanical device can be switched up to 21 positions and can be reset from any position by energising the reset coil. 230/240V a.c. operation. Unit is mounted on strong chassis, complete with cover. Price £7. P & P 75p (£8.37 inc VAT & P.) Similar to above approx 10lb pull £3.50 P & P 60p (£4.43 inc VAT & P.)

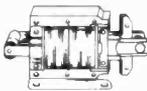NEW HEAVY DUTY SOLENOID. mfg by Magnetic Devices. 240V a.c. operation approx. 20lb pull at 1.25in. Price £7. P & P 75p. Similar to above approx 10lb pull £3.50. P & P 60p. 230/250V a.c. Solenoid Similar in appearance to illustration. Approx 1 1/2lb pull. Size of feet 1 1/2. Price £1. P & P 25p.



UNISELECTOR SWITCHES

4 bank 25 way 75 ohm. Coil. 36-48V d.c. operation. Ex-NEW equipment. £4.25. P & P 75p. Total price inc VAT £5.40.



MINIATURE UNISELECTOR

12 volt 11-way 4 bank (3 non-bridging, 1 homing). £2.50. P & P 35p (£3.08 inc VAT & P.)

RODENE UNISET TYPE 71 TIMER

0-60 sec. 230V a.c. operation incorporating a lapsed time indicator and repeat facilities. A precision motorised timer ideal for process timing, photography, welding mixing etc. Price £6. P & P 60p (£7.13 inc VAT & P.)



MICRO SWITCHES

As illustrated but fitted with 3in lever. 10 for £2. P & P 30p (£2.48 inc VAT & P.) Sub-miniature Burgess type v.41 1. 10 for £2.50. P & P 30p (£3.02 inc VAT & P.) 50 for £10. post paid (£10.80 inc VAT & P.) Sub-mini Honeywell roller m.s. type 3115m 9061. 10 for £2.50 post paid. BF LEVER OPERATED 20 amp C.O. Mfg. by Unimax USA. 10 for £4. P & P 50p (1m order 10).



24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx 25lb pull 1 inch travel. Two approx 1lb pull in travel. 6 approx 4oz pull in travel. One 24V d.c. 1 heavy duty single make relay. Price £3. Post £1 (£4.32 inc VAT & P.) ABSOLUTE BARGAIN

VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced totally enclosed 9in rotor with max air delivery of 1.5 cubic metres per min. Max static pressure 600mm W.G. Suction or blow from 2 side-by-side 37mm i.d. circular apertures fitted to base of unit. Powerful continuously rated 115V a.c. motor mounted on alloy base with fixing facilities. Dimensions length 22cm - width 25cm - height 25cm. These units are ex equipment but have had minimum use. Fully tested prior to despatch. Price £12. £1.50 P & P (£14.58 inc VAT & P.) Suitable transformer for 230/240V a.c. £6 - £1 P & P (£7.56 inc VAT & P.)



CENTRIFUGAL BLOWER

Mfg by Smiths Industries 230/240V a.c. Miniature model. Series SE 200 size 95mm - 82mm - 82mm. Aperture 38mm - 31mm 12 c.f.m. Price £2.75. post 50p (£3.51 inc VAT & P.). 115/230V a.c. 2800/3400 r.p.m. Fan type aperture 3" x 2 1/2" UBL4/L. Price £12.00. Post £1 (£14.58 inc VAT & P.). Also available, extremely powerful blower mfg. by Fracmo.



INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction suitable for bench or field work. constant speed clutch. Size L 8in W 4in H 6in weight 6lb 500V 500 megohms £40. Post 80p (£44.06 inc VAT & P.). 1000V 10000MΩ £46. Post 80p (£54.06 inc VAT & P.) SAE for leaflet



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V All Types SHROUDED TYPE

| | |
|--------------------------------------|--------|
| 200 watt (1 amp) inc. a.c. voltmeter | £12.50 |
| 0.5 KVA (2 amp) (MAX) | £15.00 |
| 1 KVA (5 amp) (MAX) | £19.50 |
| 2 KVA (10 amp) (MAX) | £32.00 |
| 3 KVA (15 amp) (MAX) | £39.50 |
| 4 KVA (20 amp) (MAX) | £60.00 |

CARRIAGE AND PACKING EXTRA



L.T. TRANSFORMERS

0-12V 24V at 1 amp £2.50. P & P 50p (£3.24 inc VAT & P.)
0-15V at 1 amp - 0-15V at 1 amp (30V 1 amp) £2.50. P & P 50p (£3.24 inc VAT & P.)
25-0-25V at 2 amp £4.50. P & P 75p (£5.67 inc VAT & P.)
0-12V 24V 10 amp £12.35. P & P £1.50 (£14.96 inc VAT & P.)
0-4V 6V 24V 32V at 12 amp £13. P & P £1.50 (£15.66 inc VAT & P.)
0-12V at 20 amp or 0-24V at 10 amp £12.00. P & P £1.50 (£15.01 inc VAT & P.)
0-6V 12V 17V 18V 20V at 20 amp £14. P & P £1.50 (£16.74 inc VAT & P.)
0-6V 12V at 20 amp £11.85. P & P £1 (£13.88 inc VAT & P.)
Other types in stock—phone your enquiries.

STROBE! STROBE! STROBE!

HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. Price £18. Post £1 (£20.56 inc VAT & P.) Specially designed case and reflector for Hy-Light £8.25. Post £1 (£9.99 inc VAT & P.)

XENON FLASHGUN TUBES

Range available from stock SAE for details



ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt, £7.75 (callers only). 2ft 20 watt, £5.50. Post 60p. (For use in standard bi-pin). MINI 12in, 8 watt, £1.95. Post 25p (£2.37 inc VAT & P.). 9in, 6 watt, £1.75. Post 25p (£2.16 inc VAT & P.). 6in, 4 watt, £1.75. Post 25p (£2.16 inc VAT & P.). Complete ballast unit and holders for 6in, 9in and 12in tube. £3.50 plus P & P 40p (£4.21 inc VAT & P.). Also available for 12V d.c. operation. £3.50 plus P & P 40p (£4.21 inc VAT & P.)

GALVANOMETER

50 micro mirror galvo. Calibrated 50-0-50 and 0-100 Mfg. by Griffin & George Ltd. Offered at a fraction of maker's price in original ministry packing. £12. P & P 60p (£13.60 inc VAT & P.)



WIDE RANGE OF DISCO LIGHTING EQUIPMENT

SAE (foolscap) for details

CONTACTOR

Mfg by Hendrey Relays type C2839 220/250 a.c. ops. Contact 4C O at 20 amp at 440V a.c. Price £6. P & P 75p



RESET COUNTER

230V a.c. 3 digits mfg. Veeder Root Type LL 1441 £1.75. P & P 25p (£2.16 inc VAT & P.) 7 Fig 24V d.c. non set £1.50. P & P 25p (£1.89 inc VAT & P.) 230V a.c. Fan Assembly. Powerful continuously rated a.c. motor complete with 5 blade 6in Aluminium fan. Price £3.95. P & P 65p. 6 fig 24V d.c. resettable £3. P & P 25p (£3.31 inc VAT & P.)



BIG INCH

Tiny precision built 3RPM U.S.A. motor size only 1-1/2 100V a.c. opp. supplied with resistor for 230V a.c. Price £2. P & P 20p (£2.37 inc VAT & P.) 4 for £5 post paid (£5.40 inc VAT & P.)



VAT

AT CURRENT RATE MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED

SERVICE TRADING CO.

GEARED MOTORS

100 r.p.m. 115lb.in. 110V 50Hz 2.8A. single phase split capacitor motor. immense power. Continuously rated. Totally enclosed. Fan cooled in-line gearbox. Length 250mm Dia. 135mm Spindle dia 15.5mm Length 145mm. Ex-equipment tested £12. Post £1.50 (£14.58 inc VAT & P.) Suitable transformer 230/240V operation £8. Post 75p (£9.45 inc VAT & P.)



CITENCO

FHP motor type C 7333/15 220/240V a.c. 19 r.p.m. reversible motor. torque 14.5 kg gear ratio 144-1. Brand new incl. capacitors. our price £14.25. P & P £1.25 (£16.20 inc VAT & P.)



BODINE TYPE N.C.I. GEARED MOTOR

(Type J) 71 r.p.m. torque 10lb.in. Reversible 1 7/10th h.p. 50Hz. The above precision made U.S.A. motor is offered in as new condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. Input. Price either type £6.25. Post 75p (£7.56 inc VAT & P.) or less transformer £3.75. Post 65p (£4.75 inc VAT & P.) (Type 3) 71 r.p.m. 4 lb.in. 230V a.c. Continuously rated Reversible £6.50. Post 75p (£7.83 inc VAT & P.)



FRACMO

56 r.p.m. 50lb.in. 240V a.c. 50Hz. 0.7 amp sharp length 35mm, dia. 16mm, weight 6 kilos 600 grammes. Price £15.00 P & P £1.50 (£17.82)



15 R.P.M.

Type SD48 80lb.in. Input 100/110V AC. Length incl. gearbox 270mm. Height 135mm. Width 150mm. Drive shaft 16mm. Weight 8.5 kg. BRAND NEW. Price £10. Carr £1 (£11.88 inc VAT & P.) Suitable transformer for use on 220/240V a.c. £6. Post 50p (£7.02 inc VAT & P.)

A.E.G. WATER PUMP

200/240V a.c. motor 2.850 r.p.m. 480W approx 1/2 h.p. Driving a centrifugal pump with 1/2 in inlet and outlet delivering approx 40 gallons per min at 10ft head. Ideal for pumping or circulating any non-corrosive light viscosity liquid. Dozens of uses in industrial labs, etc. Note this pump is not self priming. Price £15. Post 75p (£17.01 inc VAT & P.)



PROGRAMME TIMERS

12 cam model £8.74. Post 60p. Also available for 50V operation. Price as above



METERS NEW—90mm Diameter

Type: 65C d.c. Mc 0-2, 0-5, 0-20, 0-50, 0-100 amp 0-15V d.c. 0-30V d.c. Type: 62T2 a.c. M 10-1V, 0-50 amp 0-15V 0-30V Type 65L5 R m.c. 0-30V a.c. All at £3.50 each P & P 50p (£4.32 each inc VAT & P.)



WHY PAY MORE?

MULTI RANGE METER Type MF15A a.c. d.c. volts 10 50 250 500 1000 Mc 0-5 0-10 0-100 Sensitivity 2000V 24 range diameter 133 by 93 by 46mm. Price £6.50 plus 50p P & P (£7.56 inc VAT & P.)



Time Switch

Venner Type ERD Timeswitch 200/250V a.c. 2 on/2 off every 24 hrs. at any manually pre-set time. 36 hour Spring Reserve and day omitting device. Built to highest Electricity Board specification. Price £7.50 P & P 75p (£9.18).



600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600W of lighting except fluorescent at mains voltage. Complete with simple instructions £3.95, post 25p (£4.53 inc VAT & P.) 1,000 watt model £5.60, post 25p (£6.32 inc VAT & P.) 2,000 watt model £9.75, post 40p (£10.96 inc VAT & P.)



Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction vitreous enamel embedded winding, heavy duty brush assembly continuously rated. 25 WATT 10/25/50/100/150/250/500/1kΩ 1.5kΩ £2.40. Post 20p (£2.81 inc VAT & P.) 50 WATT 100/250/500/1kΩ £2.90. Post 25p (£3.40 inc VAT & P.) 100 WATT 1.5/10/25/50/100/250/500/1kΩ 1.5kΩ 2.5kΩ 3.5kΩ £4.90. Post 35p (£5.67 inc VAT & P.) Black Silver Skined knob calibrated in Nos. 1-9 1/4in dia brass bush. Ideal for above Rheostats 24p each



Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

All Mail Orders—Callers—Ample Parking
Dept. PE11, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560

Showroom open Mon—Fri

MAPLIN

in a modern world of electronics

AUDIO MIXER

A superb stereo audio mixer. It can be equipped with up to 16 input modules of your choice and its performance matches that of the very best tape recorders and hi-fi equipment. It meets the requirements of professional recording studios, FM radio stations, concert halls and theatres. Full construction details in our catalogue. A component schedule is available on request



10 CHANNEL STEREO GRAPHIC EQUALISER

A new design with no difficult coils to wind, but a specification that puts it in the top flight hi-fi class. All this for less than £70 including fully punched and printed metalwork and woodwork. Send for our component schedule now. Full construction details price 40p.




INTEGRATED CIRCUITS

Over 35 pages in our catalogue devoted to hundreds of useful I.C.s. All with data, pin connections and many with applications circuits and projects to build. Post the coupon now!



PEDAL UNIT

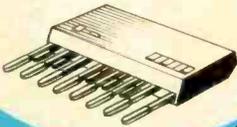A completely self-contained pedal unit. 13-note, 2-Octave range. 4 organ stops. It can be added to any organ. A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue—post the coupon below now!



SYNTHESISER

The International 4600 Synthesiser. A very comprehensive unit. Over 400 sold. We stock all the parts costing less than £500 including fully punched and printed metalwork and a smart teak cabinet. Far less than half what you'd pay for a ready made synthesiser of equal quality. Specification on request, full construction details in our construction book £1.50.



Who says the Maplin Catalogue's worth having?

"in our 'musts' for readers-to-collect list"
—P.E.

"contains . . . just about everything the DIY electronic enthusiast requires"
—P.W.

"probably the most comprehensive catalogue we have ever come across"
—E.E.

"has been carefully prepared and is very well presented"
—R.E.C.

"makes the job of ordering components an easy, accurate and enjoyable pastime"
—P.W.

"Only one word describes the publication—superb!"
—E.T.I.

OVER 60,000 COPIES SOLD. DON'T MISS OUT!
SEND 60p NOW

MAPLIN ELECTRONIC SUPPLIES

P.O. Box 3, Rayleigh, Essex SS6 8LR
Telephone: Southend (0702) 715155
Shop: 284 London Road, Westcliff-on-Sea,
Essex. (Closed on Monday). Tele-
phone: Southend (0702) 715157.

Our bi-Monthly newsletter keeps you up to date with latest guaranteed prices—our latest special offers—details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

POST THIS COUPON
NOW FOR YOUR COPY OF
OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue. I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

Name _____

Address _____

