

Australia 85c South Africa 80c  
New Zealand 85c Malaysia \$2.25

PRACTICAL

# ELECTRONICS

JULY 1978

45p



## PE TV GAME CENTRE

14 GAMES – COLOUR or BLACK and WHITE

ALSO... OSCILLOSCOPE LOGIC MONITOR

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P add 30p\* TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE.

MINIMUM ORDER £2.00 PLEASE.

**VAT** Export orders no VAT. \*Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked \*. To the rest add 12%.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Bus Station: Watford High Street. Open Monday to Saturday 9.00 am - 6.00 pm. Ample Free Car Parking space available.

**POLYESTER CAPACITORS:** Axial lead type. (Values are in  $\mu F$ )  
400V: 0.001 0.0015 0.0022 0.0033 8p; 0.0047 0.0068 0.01 0.015 0.018 9p; 0.022 0.033 10p; 0.047 0.068 14p; 0.10 15p; 0.15 0.22 22p; 0.33 0.47 39p; 0.68 45p; 1.50V: 0.039 0.15 0.22 13p; 0.33 0.47 22p; 0.68 1.0 29p; 1.5 33p; 2.2 39p; 4.7 47p.  
DUBILIER: 1000V: 0.01 0.015 16p; 0.022 16p; 0.047 16p; 0.1 34p; 0.47 43p.

**POLYESTER RADIAL LEAD (Values in  $\mu F$ ) 250V:**  
0.01 0.015 6p; 0.022 0.027 7p; 0.033 0.047 0.068 0.1 0.15 12p; 0.15 12p; 0.22 0.33 0.47 16p; 0.68 20p; 1.0 24p; 1.5 27p; 2.2 31p.

**ELECTROLYTIC CAPACITORS:** Axial lead type (Values are in  $\mu F$ )  
63V: 0.47 1.0 1.5 2.2 2.5 3.3 4.7 6.8 8 10 15 22 9p; 47 32 50 12p; 63 100 27p;  
50V: 1.0 2p; 50 100 220 25p; 470 50p; 1000 2200 68p; 40V: 22 33 9p; 100 12p; 3300 62p; 4700 64p; 35V: 10 33 7p; 33 40 32p; 100 49p; 25V: 10 22 47 6p; 80 100 160 8p; 220 250 13p; 470 640 25p; 1000 27p; 1500 30p; 2200 41p; 3300 52p; 4700 54p; 16V: 10 40 47 68 7p; 100 125 8p; 330 470 16p; 1000 1500 22p; 2200 34p; 10V: 4 100 6p; 640 10p; 1000 14p.

**TANTALUM BEAD CAPACITORS**  
35V: 0.1  $\mu F$  0.22 0.33 0.47 0.68 1.0 2.2  $\mu F$  3.3 4.7 6.8 25p; 1.5 10p; 20V: 1.5 16V: 10  $\mu F$  13p each; 47 100 40p; 10V: 2.2  $\mu F$  33 47 6V: 47 68 100 3V: 68 100  $\mu F$  20p each

**MYLAR FILM CAPACITORS**  
100V: 0.001 0.002 0.005 0.01  $\mu F$  5p; 0.015 0.02 0.04 0.05 0.05  $\mu F$  4p; 0.1  $\mu F$  0.15 0.2 9p; 50V: 0.47 11p

**CERAMIC CAPACITORS: 50V**  
0.5pF to 10nF 3p each; 15nF 22nF 33nF 47nF 4p each; 0.1  $\mu F$  6p

**POLYSTYRENE CAPACITORS**  
10pF to 1nF 6p; 1.5nF to 47nF 10p

**SILVER MICA (Values in pF) 3.3 4.7 6.8 10 12 18 22 33 47 50 68 75 82 85 100 120 150 220 9p each; 250 300 330 360 390 600 820 15p each; 1000 1800 2000 2200 20p each**

**CERAMIC TRIMMER CAPACITORS**  
2 7pF 4 15pF 6 25pF 8 30pF 20p

**MINIATURE TYPE TRIMMERS**  
2.5 5pF 3 10pF 10 40pF 22p; 5 25pF 5 45pF 60pF 88pF 30p

**COMPRESSION TRIMMERS**  
3 40pF 10 80pF 25 190pF 25p; 100 500pF 1250pF 38p

**PE String ENSEMBLE**  
Components now available.

**JACK PLUGS** Screened chrome 12p; Plastic body 8p; open metal 8p; moulded with break 11p; in line couplers 11p; 2.5mm 15p; 3.5mm 15p; MONO 23p; STEREO 31p

**SOCKETS** 1A DPDT 14p; 1A DP 16p; 1A DP 13p; 4 pole DPDT 24p; PUSH BUTTON Spring loaded SPST on/off 55p; SPDT 4 lever 85p; DPDT 6 Tag 88p

**DIN** 2 Pin Loudspeaker 3p; 3 4 Pin Audio 13p; PLUGS 13p; SOCKETS 20p; In Line 14p

**CO-AXIAL (TV)** 14p; **PHONO** assorted colours 9p; Metal Screened 10p; 5p single 15p; 8p double 10p; 3-way 10p

**BANANA** 4mm 10p; 2mm 10p; 1mm 8p; 9p; **WANDER** 3mm 9p

**SWITCHES \* Miniature Non-Locking**  
Push to Make 15p; Push to Break 26p; ROCKER (white) 10A 250V 28p; SP changeover centre off 23p; ROCKER: (black) on/off 10A 250V 23p; ROCKER: (Illuminated) (white) 52p; Lights when on: 3A 240V 52p; ROTARY: (ADJUSTABLE STOP) 1 pole / 2-12 2p; 2p / 2-6W 3p; 2p / 4W 4p; 2p / 3W 41p; ROTARY: Mains 250V AC 4 Amp 42p

**DIL SOCKETS\* (Low Profile - Texas)**  
8 pin 10p; 14 pin 12p; 16 pin 13p; 18 pin 20p; 20 pin 26p; 24 pin 30p; 28 pin 42p; 40 pin 58p.

**DALO ETCH** Resist Pen Spare Tip 75p\*

**COPPER BOARDS\*** Fibre Glass Single Sided 6 x 8 76p; 6 x 12 81p; 6 x 18 100p; S R B\* 70p

**VOLTAGE REGULATORS** 723C 45p; TBA625B 95p; TO3 Can -ve 1A 5V 140p; 1A 15V 145p; 1A 12V 145p; 1A 18V 150p; LM323K 625p; 1A - 5V 220p; 1A - 12V 220p

**Plastic + 2p** 1A 5V 12V 15V 18V 24V 99p each; 0.1A 15V 145p; 12V 15V 51p each

**Plastic -ve** 0.5A 5V 6V 9V 12V 15V 95p each

**LM320-12 145p; LM320-15 155p; LM324-15 240p; LM325N 240p; LM328N 240p; LM329N 260p**

**IC AY-3-8710 £9.78\***  
Basic Kit (just add controls) Price: Only £17.98\* (p&p 30p)

Complete Kit incl. cases & controls Price: Only £24.30\* (p&p 30p)

Build this fantastic TV GAME with realistic battle sounds - Steerable Tanks - Controllable Shell trajectory and Minefields to avoid.

A really exciting and skilful game simply constructed with our easy to follow instructions.

Build this fantastic TV GAME with realistic battle sounds - Steerable Tanks - Controllable Shell trajectory and Minefields to avoid.

TTL 74*	7494	78	74194	105	4056	134	4513	206	4518	102	4526	199
	7495	65	74195	95	4057	2570	4514	265	4519	59	4527	152
	7496	57	74196	99	4058	480	4515	299	4520	108	4528	99
	7497	189	74197	85	4059	99	4516	125	4521	268	4529	165
	7498	119	74198	150	4060	2380	4517	382	4522	199	4530	85
	7499	62	74199	89	4061	11						
	7499	75	74199	75	4062	110						
	7499	80	74199	54	4063	58						
	7499	88	74199	68	4064	702						
	7499	198	74199	40	4065	22						
	7499	17	74199	21	4066	380						
	7499	119	74199	4002	4067	110						
	7499	105	74199	105	4068	22						
	7499	18	74199	4073	4069	22						
	7499	97	74199	4076	4070	85						
	7499	45	74199	4078	4071	32						
	7499	45	74199	4078	4072	21						
	7499	45	74199	4078	4073	21						
	7499	45	74199	4078	4074	85						
	7499	45	74199	4078	4075	85						
	7499	45	74199	4078	4076	85						
	7499	45	74199	4078	4077	85						
	7499	45	74199	4078	4078	21						
	7499	45	74199	4078	4079	21						
	7499	45	74199	4078	4080	21						
	7499	45	74199	4078	4081	21						
	7499	45	74199	4078	4082	21						
	7499	45	74199	4078	4083	21						
	7499	45	74199	4078	4084	21						
	7499	45	74199	4078	4085	21						
	7499	45	74199	4078	4086	21						
	7499	45	74199	4078	4087	21						
	7499	45	74199	4078	4088	21						
	7499	45	74199	4078	4089	21						
	7499	45	74199	4078	4090	21						
	7499	45	74199	4078	4091	21						
	7499	45	74199	4078	4092	21						
	7499	45	74199	4078	4093	21						
	7499	45	74199	4078	4094	21						
	7499	45	74199	4078	4095	21						
	7499	45	74199	4078	4096	21						
	7499	45	74199	4078	4097	21						
	7499	45	74199	4078	4098	21						
	7499	45	74199	4078	4099	21						
	7499	45	74199	4078	4100	21						
	7499	45	74199	4078	4101	21						
	7499	45	74199	4078	4102	21						
	7499	45	74199	4078	4103	21						
	7499	45	74199	4078	4104	21						
	7499	45	74199	4078	4105	21						
	7499	45	74199	4078	4106	21						
	7499	45	74199	4078	4107	21						
	7499	45	74199	4078	4108	21						
	7499	45	74199	4078	4109	21						
	7499	45	74199	4078	4110	21						
	7499	45	74199	4078	4111	21						
	7499	45	74199	4078	4112	21						
	7499	45	74199	4078	4113	21						
	7499	45	74199	4078	4114	21						
	7499	45	74199	4078	4115	21						
	7499	45	74199	4078	4116	21						
	7499	45	74199	4078	4117	21						
	7499	45	74199	4078	4118	21						
	7499	45	74199	4078	4119	21						
	7499	45	74199	4078	4120	21						
	7499	45	74199	4078	4121	21						
	7499	45	74199	4078	4122	21						
	7499	45	74199	4078	4123	21						
	7499	45	74199	4078	4124	21						
	7499	45	74199	4078	4125	21						
	7499	45	74199	4078	4126	21						
	7499	45	74199	4078	4127	21						
	7499	45	74199	4078	4128	21						
	7499	45	74199	4078	4129	21						
	7499	45	74199	4078	4130	21						
	7499	45	74199	4078	4131	21						
	7499	45	74199	4078	4132	21						
	7499	45	74199	4078	4133	21						
	7499	45	74199	4078	4134	21						

# PRACTICAL ELECTRONICS

VOLUME 14 No. 11 JULY 1978

---

## CONSTRUCTIONAL PROJECTS

- P.E. TV GAME CENTRE—1**  
Ten ball games and four motorcycle games in colour 810
- GENERAL PURPOSE TIMER** *by M. Plant*  
An accurate wide range timer with both audio and visual alarms 826
- STRING ENSEMBLE—5** *by A. J. Boothman*  
Cabinet construction 834
- DIMWIT** *by M. J. Carter*  
A bedside lamp that can be simply switch programmed 842
- C.R.O. LOGIC MONITOR GENERATOR** *by R. Derry*  
Serially displays logic states of i.c.s under test 838

## GENERAL FEATURES

- INGENUITY UNLIMITED**  
Prom programmer—Radio Control Servo Tester—Overflow Indicator 832
- TOMORROW'S BROADCASTING** *by Dr. Boris Townsend*  
Audio/Visual projections 854
- SEMICONDUCTOR UPDATE** *by R. W. Coles*  
A look at some recently released devices 860

## NEWS AND COMMENT

- EDITORIAL** 809
- MARKET PLACE**  
Interesting new products 817
- SPACEWATCH** *by Frank W. Hyde*  
Soviet activity, Salyut mission, Future plans, Black hole?, Comets 820
- INDUSTRY NOTEBOOK** *by Nexus*  
What's happening inside industry 825
- NEWS BRIEFS** IERE Conference—Sony Launch Betamax 846  
Compilers for Micros, Laser for Nasa, Card Counting, Automated Blinds, Standards 852
- INVENTORS COMPETITION**  
Last chance to win financial backing and a 'scope for your ideas 850
- READOUT**  
A selection of readers' letters 853

Our August issue will be on sale Friday, 14 July 1978  
(for details of contents see page 849)

---

© IPC Magazines Limited 1978. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

# TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT 8%

12 AND 24 VOLT OR 12-0.12V PRIMARY 220-240 VOLTS				
Ref	12V 24V	£	P & P	
111	0.5	0.25	2.20	0.45
213	1.0	0.5	2.44	0.78
71	2	1	3.51	0.78
18	4	2	4.03	0.96
70	6	3	5.35	0.96
108	8	4	6.98	1.14
107	10	5	7.47	1.14
116	12	6	8.99	1.32
17	16	8	10.39	1.32
115	20	10	13.18	2.08
187	30	15	17.05	2.08
226	60	30	26.82	0A

30 VOLT RANGE				
Ref	Amps	£	P & P	
112	0.5	2.44	0.78	
79	1.0	3.57	0.96	
3	2.0	5.27	0.96	
20	3.0	6.20	1.14	
21	4.0	7.44	1.14	
51	5.0	8.37	1.32	
117	6.0	9.92	1.45	
88	8.0	11.73	1.64	
89	10.0	13.33	1.84	

50 VOLT RANGE				
Ref	Amps	£	P & P	
102	0.5	3.41	0.78	
103	1.0	4.57	0.96	
104	2.0	6.98	1.14	
105	3.0	8.45	1.32	
106	4.0	10.70	1.50	
107	5.0	14.62	1.64	
118	8.0	17.05	2.08	
119	10.0	21.70	0A	

60 VOLT RANGE				
Ref	Amps	£	P & P	
124	0.5	3.88	0.96	
126	1.0	5.58	0.96	
127	2.0	7.60	1.14	
125	3.0	10.54	1.32	
123	4.0	12.23	1.84	
40	5.0	13.95	1.64	
120	6.0	15.66	1.84	
121	8.0	20.15	0A	
122	10.0	24.03	0A	
189	12.0	27.13	0A	

MAINS ISOLATING (SCREENED)				
Ref	VA (Watts)	£	P & P	
07*	20	4.40	0.79	
149	60	6.20	0.96	
150	100	7.13	1.14	
151	200	11.15	1.50	
152	250	12.79	1.84	
153	350	16.28	1.84	
154	500	19.15	2.15	
155	750	28.06	0A	
156	1000	37.20	0A	
157	1500	45.60	0A	
158	2000	54.80	0A	
159	3000	78.95	0A	

AUTO TRANSFORMERS				
Ref	VA (Watts)	Voits	£	P & P
113	15	0-115-210-240	2.48	0.71
64	75	0-115-210-240	3.95	0.96
4	150	0-115-200-220-240	5.35	0.96
67	500	0-115-200-220-240	10.99	1.64
84	1000	0-115-200-220-240	18.76	2.08
93	1500	0-115-200-220-240	23.36	0A
95	2000	0-115-200-220-240	34.82	0A
73	3000	0-115-200-220-240	48.00	0A

HIGH VOLTAGE MAINS ISOLATING				
VA	Ref	£	P & P	
60	243	5.89	1.32	
200	247	14.11	1.84	
1000	250	35.65	0A	
2000	252	54.25	0A	

CASED AUTO TRANSFORMERS				
VA	£	P & P	Ref	
15	4.95	0.96	113W	
150	8.48	1.14	4W	
200	9.92	1.45	65W	
250	10.49	1.45	69W	
500	15.73	1.64	67W	
750	18.55	1.76	83W	
1000	22.68	0A	84W	
1500	26.02	0A	83W	
2000	37.65	0A	95W	

Ref	mA	Volts	£	P & P
238	200	3-0-3	1.99	0.55
212	1A, 1A	0-6-0-6	2.85	0.78
13	100	9-0-9	2.14	0.38
203	330, 330	0-9-0-9	1.99	0.38
207	500, 500	0-8-9-0-8-9	2.59	0.71
208	1A, 1A	0-8-9-0-8-9	3.53	0.78
236	200, 200	0-15-0-15	1.99	0.38
214	300, 300	0-20-0-20	2.56	0.78
221	700 (DC)	20-12-0-12-20	3.41	0.78
206	1A, 1A	0-15-20-0-15-20	4.63	0.96
204	1A, 1A	0-15-27-0-15-27	3.99	0.96
204	1A, 1A	0-15-27-0-15-27	5.39	0.96
S112500		12-15-20-24-30	2.64	0.78
239	50	12-0-12	1.99	0.38

MINI-MULTIMETER		
DC-1000V AC-1000V DC-100mA Res-150kΩ		
1000Ω/V Bargain £5.86P & P 62p VAT 8%		
£11.09 P & P £1.05 VAT 8%		

20,000 ohm/V Multimeter, mirror scale. Ranges AC/DC to 1000V, DC currents to 250mA.		
Resistance to 3 Mohms. 5" x 3 1/2" x 1 1/2"		
£11.09 P & P £1.05 VAT 8%		

TEST METERS		
UA315 Budget Meter 20kΩ/V DC 2K/V AC 1000V AC/DC 2-5A AC/DC 500k res. in robust steel case and leads £15.85.		
BX505 Sanwa £33.68 MM5 £26.10		
AV08 £77.10 TT169 £32.50		
AV071 £31.10 DA116 digital £100.00		
AV073 £42.50 Wee Megger £42.50		
EM272 £50.70 Battery Megger BM7		

Special Offer AVO Meter (107)		
Ranges DC volts 2.5, 10, 50, 100, 500, 1000V - current 1mA, 2.5, 10, 50, 100, 500, 1 amp, AC 10V, 100V, 1000V, 3 ohmic ranges to 10M ohms. 10,000V/DC, 1000V AC Safety cut out £40.00. P & P £1.15. VAT 8%.		

ELECTRONIC CONSTRUCTION KIT		
10 projects (including electronic organ). No soldering needed £7.29. VAT 8% P & 70p		

PANEL METERS		
2" 0-50µA 5.50 4" 0-50µA 6.70		
0-500µA 5.50 0-500µA 6.70		
0-1mA 5.50 0-1mA 8.40		
0-50V 5.50 0-50V 8.40		
0-100µA 5.50 0-100µA 6.70		

VU Indicator Panel 48 x 45 250µA FSD		
£2.60		
VU Indicator Edge 54 x 14 250µA FSD		
£2.60		

Prices correct 7.11.77. Please add VAT after P & P.

50 High Quality Metal Oxide 2.5% 1/4W Resistors.		
150 Mixed Value Capacitors		
10 Read Switch.		
30 Wire Wound Resistors, mixed.		
25 assorted Presets.		
50 3 Tag Terminal Strips.		
Hardware pk. bolts, nuts, washers, insulators 70p + 12 1/2% P & P 40p.		
12 way Greco heavy block plastic terminal block 35p P & P 15p.		
Fuse holder 1 1/2" completely enclosed internal screw connection 25p P & P 15p.		
2x Fuse boards - 2 open 1 1/2" fuse holders 2 1/2" x 3" 30p P & P 15p.		

NEW RANGE HIGH QUALITY TRANSFORMERS		
45-36-0-36-45. 2A 9.89 1.38		
45 to give 3A 11.47 1.48		
36-0-36. 4A 13.90 1.84		
45-0-45. 5A 16.74 2.15		
72V or 90V. 6A 20.77 2.30		

PLUG IN SAVE BATTERIES		
3300 fits into 13A socket 6-7, 5-9V 300mA multipin outlet £3.30		
Stabilised 3-6-7-9/400mA multipin outlet £6.61		
VAT 12 1/2% P & P 55p		

DECS SOLDERLESS BREAD-BOARDING		
S Dec 70 contacts £1.98		
T Dec 208 contacts £3.63		
U Dec "A" for I.C.s etc £3.99		
V Dec "B" for I.C.s etc £6.99		
VAT 8% P & P 40p		

ANTENX SOLDERING IRONS		
15W £3.75 18W £3.75		
25W £3.95 Stand £1.40		
P & P 46p VAT 8%.		


STEREO FM TUNER WITH PHASE-LOCK LOOP		
4 Pre-selected stations, varicap tuning, switched AFC. LED Beacon £20.45		
VAT 12 1/2% P & P 40p.		

TRANSFORMERS SPECIAL OFFER (Limited Stocks)		
BE1 Prim 0-120, 0-120V (120 or 240V) Sec 24V 10A £5.50 P & P £1.66		
7559. 250-0-250V, 16-3V, 12 9-0-12 9V, £6.50 P & P 90p		
BE3 100V line to 4Q 710V £2.05 P & P 66p		
BE4 0-120V x 2 (120V or 240) Screen sec 9-0-9V 1A £2.40 P & P 71p		
BE5 15W matching trans. sec 15Q suit EL89 £1.50 P & P 30p		
BE6 PR1. 0-220V sec 4500V. 10 mA £4.50 P & P £1.00		
Ref 30 240-240 Isolators 200VA £4.20 P & P 96p		
Ref 62 240-240 Isolators 250VA £5.20 P & P 96p		

TRANSFORMERS SPECIAL OFFER (Limited Stocks)		
BE1 Prim 0-120, 0-120V (120 or 240V) Sec 24V 10A £5.50 P & P £1.66		
7559. 250-0-250V, 16-3V, 12 9-0-12 9V, £6.50 P & P 90p		
BE3 100V line to 4Q 710V £2.05 P & P 66p		
BE4 0-120V x 2 (120V or 240) Screen sec 9-0-9V 1A £2.40 P & P 71p		
BE5 15W matching trans. sec 15Q suit EL89 £1.50 P & P 30p		
BE6 PR1. 0-220V sec 4500V. 10 mA £4.50 P & P £1.00		
Ref 30 240-240 Isolators 200VA £4.20 P & P 96p		
Ref 62 240-240 Isolators 250VA £5.20 P & P 96p		

TRANSFORMERS SPECIAL OFFER (Limited Stocks)		
BE1 Prim 0-120, 0-120V (120 or 240V) Sec 24V 10A £5.50 P & P £1.66		
7559. 250-0-250V, 16-3V, 12 9-0-12 9V, £6.50 P & P 90p		
BE3 100V line to 4Q 710V £2.05 P & P 66p		
BE4 0-120V x 2 (120V or 240) Screen sec 9-0-9V 1A £2.40 P & P 71p		
BE5 15W matching trans. sec 15Q suit EL89 £1.50 P & P 30p		
BE6 PR1. 0-220V sec 4500V. 10 mA £4.50 P & P £1.00		
Ref 30 240-240 Isolators 200VA £4.20 P & P 96p		
Ref 62 240-240 Isolators 250VA £5.20 P & P 96p		

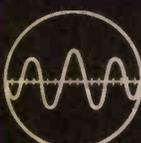**Barrie Electronics Ltd.**  
3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/7/8  
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST



# TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.  
PHONE 01-672 3137/672 9080  
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING CONTROL SYSTEMS

## NEW FROM TUAC



TD500



TD150

### ULTRA QUALITY HIGH POWER New D.C. Coupled Design AMPLIFIERS

Featuring Electronic Short Open and Thermal Overload Protection. Brief Spec.  
Input Sensitivity 0.775 v. R.M.S. (O.D.B.) at 25K Ohms.  
Frequency Response 20 Hz - 20KHz.  
Hum and Noise—100 dB Relative full output.  
T.H.D. at full power 0-1%.

T.D. 500	300W into 2 Ohms.	
	220W into 4 Ohms.	
Size 7" x 9" x 1 1/2"	140W into 8 Ohms.	£45.00
Power supply P.S. 300		£28.50
T.D. 150	150W into 4 Ohms	
5" x 5" x 2"	100W into 8 Ohms	£26.25
Power supply P.S. 150		£17.75
T.D. 150		
60 Variation	60W into 8 Ohms	£17.75
5" x 5" x 2"	40W into 15 Ohms	
Power supplies P.S. 60		£15.25

Note—P.S. 300 will drive 2 T.D. 150 amplifiers.  
All output ratings are R.M.S. continuous sine wave output.

**TO ORDER BY POST**  
Make cheques/P.O.s payable to TUAC LTD., (PE78), or quote Access/Barclay Card No. (We accept holders phone orders 01-672 9080.)  
Post to—  
TUAC LTD., (PE78), 119 CHARLMOLE ROAD, LONDON SW17 9AB.  
Send stamp for our free 28 page catalogue of LIGHTING & AMPLIFIER MODULES, etc.

# the MIGHTY MIDGETS



## MINIATURE SOLDERING IRONS AND ACCESSORIES

	RETAIL PRICE each inc. v. a. t.	POSTAGE extra.
18 WATT IRON inc. No. 20 BIT	£3.78	22p
SPARE BITS	44p	—
STANDS	£3.25	65p
SOLDER: SAVBIT 20'	52p	9p
" 10'	26p	4p
LOWMELT 10'	65p	9p
I.C. DESOLDERING BIT	88p	9p

BIT SIZES: No. 19 (1.5 mm) No. 20 (3 mm)  
No. 21 (4.5 mm) No. 22 (6 mm)


From your Local Dealer or Direct from Manufacturers

# S & R BREWSTER LTD

86-88 Union St · Plymouth PL1 3HG  
Tel: 0752 65011 TRADE ENQUIRIES WELCOME

# LOOK! Here's how you master electronics




... the practical way

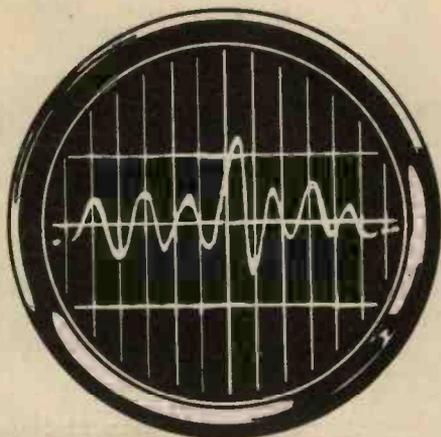

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

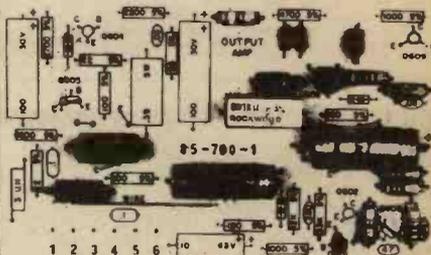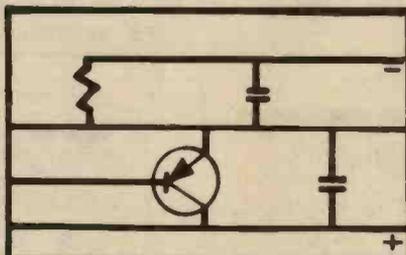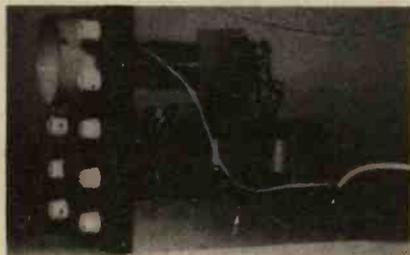All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



## 1 Build an oscilloscope

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

## 2 Read, draw and understand circuit diagrams

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

## 3 Carry out over 40 experiments on basic circuits

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

**FREE GIFT**



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

## British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME .....

ADDRESS .....

PEB7

Block caps please

**Free!**

# GREENWELD

443 Millbrook Road Southampton  
SO1 0HX Tel: (0703) 72501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted

from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

## SEMICONDUCTORS

Diodes: 1N4001/2 5p; 4004/5 7p; 4006 8p; 4007 9p; 1250V 1A, 10p; 1250V 1.5A, 12p; 50V 3A 10p; 100V 3A, 12p; 400V 3A, 15p; 200V 10A stud, 40p; 400V 10A stud, 48p.

Bridge Rectifiers.  
50V 1A 26p; 200V 1A 32p; 400V 1A 36p; 100V 2A 48p; 400V 2A 58p; 100V 4A 65p; 400V 4A 80p; 100V 6A 74p; 400V 6A 98p.

400mW Zeners 2V 7 to 36V, 10p each. 1.3W Zeners 3V3-200V, 20p. 10 watt zeners from 4V3 to 200V 93p.

0A81 5p; 0A91, 8p; 1N4148, 4p.

## SCR's

0.8A	60V	TO92	35p
1A	400V	TO5	60p
4A	200V	TO220	52p
4A	400V	TO220	70p
6A	200V	TO220	56p
6A	400V	TO220	75p
6A	400V	TO66	80p
10A	100V	TO220	82p
10A	200V	TO220	87p
10A	400V	TO220	120p
10A	600V	TO220	148p

## Triacs

6A	400V	TO220	98p
8A	600V	TO220	135p
15A	200V	TO220	135p
15A	400V	Stud	220p

## TRANSISTORS

AC127	18p	BC548	10p	BRV56	40p
AC128	18p	BC549	10p	OC71	120p
AC176	18p	BCV70	15p	TP14A	56p
AC187	20p	BCV71	15p	TP42A	66p
AC188	20p	BCV72	14p	TP2955	86p
AD149	70p	BC131	38p	TP3055	42p
AD161	40p	BD132	40p	TI543	35p
AD162	40p	BD133	48p	2N2846	60p
AF279	75p	BD137	40p	2N2905	21p
BC107	12p	BD138	40p	2N2926	12p
BC108	10p	BD139	42p	2N3053	28p
BC108C	12p	BD140	44p	2N3054	52p
BC109	12p	BF173	20p	2N3055	50p
BC109C	15p	BF181	30p	2N3442	130p
BC147	10p	BF194	10p	2N3702	10p
BC148	10p	BF195	10p	2N3703	10p
BC149	10p	BF196	10p	2N3704	10p
BC157	10p	BF197	12p	2N3705	10p
BC158	10p	BF200	28p	2N3706	10p
BC159	10p	BF338	24p	2N3708	10p
BC182	12p	BF379	26p	2N3710	10p
BC183	12p	BFX29	22p	2N3819	28p
BC184	12p	BFX48	32p	2N3904	15p
BC212	14p	BFX84	22p	2N3906	15p
BC213	14p	BFX88	22p	2N6027	55p
BC214	14p	BFY50	18p	2N6028	60p
BC441	32p	BFY51	18p	40673	65p
BC461	32p	BFY52	18p		
BC547	10p	BRV39	40p		

## 74 Series TTL

7400	12p	7447	84p	7410.	37p
7401	14p	7450	15p	74121	36p
7402	14p	7451	14p	74122	51p
7404	17p	7453	14p	74123	64p
7405	23p	7454	14p	74132	56p
7406	28p	7480	14p	74141	63p
7408	14p	7472	29p	74150	173p
7410	14p	7473	29p	74151	79p
7413	28p	7474	29p	74154	144p
7414	62p	7475	51p	74155	73p
7420	14p	7476	29p	74157	66p
7427	36p	7483	91p	74159	200p
7430	14p	7485	132p	74164	126p
7432	28p	7486	40p	74174	110p
7437	36p	7490	46p	74178	120p
7438	36p	7491	75p	74180	120p
7440	15p	7492	52p	74190	188p
7442	65p	7493	52p	74191	158p
7445	88p	7495	73p	74192	120p
7446	88p	7496	85p	74193	120p
				74367	120p

## C-MOS

4000	18p	4018	84p	4054	100p
4001	18p	4022	90p	4055	110p
4002	18p	4023	18p	4080	96p
4007	18p	4024	84p	4071	18p
4011	18p	4027	48p	4081	18p
4012	48p	4028	78p	4510	132p
4013	48p	4040	110p	4511	212p
4016	48p	4047	78p	4528	124p
4017	84p	4049	48p	4588	256p

## LINEAR & MISC IC's

741 25p. \*MC3302 Quad comp 120p. \*555 40p. \*710 diff comp (TO99) 40p. 555 100p. \*7105 LED digit driver 8 for £1. LM380 100p. \*ZN1034E Precision timer £2.25. LM301 30p. \*SLD2128 Dual 128 bit static shift register £1.50.  
\*Supplied with data. If requested.

## 1977/8 CATALOGUE

48 BIG pages packed with over 4,000 items, many of them illustrated. Discount vouchers worth 50p. PRICE 30p + 15p post. (Overseas send 60p surface or £1 airmail.) Also included is our current Bargain List. Send SAE for bargain list alone.

## BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

★ **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!

★ **SAVE ON MONEY**—Bulk buying means lowest prices—just compare with others!

★ **HAVE THE RIGHT PART**—No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES—SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors. 5%. 10 of each value 22pF to 1000pF. Total 210. £3.35

K002 Extended range, 22pF to 0.1µF. 330 values £4.90

K003 Polyester capacitors. 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for £4.75

K004 Mylar capacitors, min 100V type. 10 each all values from 1000pF to 10,000pF. Total 130 for £3.75

K005 Polystyrene capacitors. 10 each value from 10pF to 10,000pF. E12 series 5% 160V. Total 370 for £12.30

K006 Tantalum bead capacitors. 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25 15/16 22/16 33/10 47/6 100/3. Total 170 tans for £14.20

K007 Electrolytic capacitors 25V working, small physical size. 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.50

K008 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for £5.90

K021 Miniature carbon film 5% resistors, CR25 or similar. 10 of each value from 10R to 1M. E12 series. Total 610 resistors. £6.00

K022 Extended range, total 850 resistors from 1R to 10M £8.30

K041 Zener diodes, 400mV 5% BZY88, etc. 10 of each value from 2.7V to 36V. E24 series. Total 280 for £15.30

K042 As above but 5 of each value £8.70

## PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £3.90

## CALCULATOR CHIP

Type C500 by G1. 4 function + constant. 8 digit. Multiplexed output for simple keyboard interfacing. 24 pin DIL With comprehensive data + socket £1.50

## DARLINGTON COMP PAIR

BD696A and BD696A—45V 8A 70W plastic powerII gain 750 @ 4A. PNP-NPN pair £1.50

## VERO OFFCUTS

Pack A, All 0.1" Pack B, All 0.15" Pack C, Mixed Pack D, all 0.1" Plain Each pack contains 7 or 8 pieces with a total area of 100 sq. in. Each pack is £1.30. Also available by weight. 1lb £4.20, 10lb £32.50. 17 x 3 1/4" Strips: 0.1" £2.20; 10 for £15 0.15" £1.96 0.1" Plain £1.83

## EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third of their original list price! 18 way 41p; 21 way 47p; 32 way 72p; 40 way 90p; 49 way 111p.

## DIGITAL VOLTMETER/THERMOMETER KIT



Based on the 7106 single IC 3 1/2 digit D.V.M. the Kit contains a PCB, resistors, capacitors, pre-sets, I.C. and 0.5" liquid crystal display. Components are also included to enable the basic D.V.M. kit to be modified to a Digital Thermometer using a single transistor as the sensor.

ONLY £23.75

## TRIAC BARGAINS

400V Plastic Case	
3A	68p
6.5A with trigger	86p
8A	85p
12A	90p
16A	113p
20A	178p
26A	205p
SCR (C108D) 5A/400V	54p
Diac	23p

## \* SPECIALS \*

4 x 555	£1.08
4 x 2N3055	£1.19
5 x 741	£1.08
LM3911	97p

## OPTO ELECTRONICS

0.2" L.E.D.s	
Red 11p (86p/10)	
Green 23p	
Yellow 27p	
DL727 0.5" display	£1.62

## TIMER I.C.s

555	31p
ZN1034E	£1.94
AY-5-1230	£5.24
AY-5-1224	£3.51

## MINI MAINS TRANSFORMERS

Standard 240V mains primary 100mA secondary	
6-0-6V	92p
9-0-9v	97p
12-0-12V	102p

## 24HR CLOCK/APPLIANCE TIMER KIT



Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, complete with PCBs and full instructions. £14.85 White box (56 x 131 x 71mm) — drilled £2.70 — undrilled £2.38

## TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains rewiring. Insulated Touch Plates. Easy to follow instructions.

TSD300K — TOUCHSWITCH & DIMMER combined. One touch plate for on/off. Small knob controls brightness.	£5.62
TS300K — TOUCHSWITCH. TWO touch plates. ON and OFF.	£4.32
TA300K — AUTOMATIC. ONE touch plate. Preset time delay OFF.	£4.32
LD300K — 300W LIGHT DIMMER KIT.	£3.02

## ABOVE PRICES INCLUDE V.A.T.

Quantity discounts on request. Add 25p postage and packing. Mail order only to:

T.K. ELECTRONICS (PE) 106 Studley Grange Road, London, W7 2LX.

### Random FLASHER UNIT

Wired ready for use  
Complete with three 100 watt coloured lamps that flash independently at random

£19.95

### TWIN BANK 6 LIGHT UNIT

(less lamps) LENGTH 14 1/2 inches

BC Fitting £11.35  
ES Fitting £11.35

### Sound to Light MASTER UNIT

600 WATTS PER CHANNEL

£30.95

INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INPUT SOCKET

### TYPE A SPOT

(less lamp)

BC Fitting £2.30  
ES Fitting £2.30

### TYPE B 3 BANK UNIT

(Less Lamps)

BC Fitting £7.99  
ES Fitting £7.99

### TWIN BANK 12 LIGHT UNIT

Length 31 1/4

BC Fitting £18.50  
ES Fitting £18.50

### 100 WATT SPOT LAMPS

RED, YELLOW, GREEN, BLUE, CLEAR

3 lamps £4.50  
each £1.50

B.C. or E.S. Fitting

ALL PRICES INCLUDE V.A.T. AND POST & PACKING (These prices apply to the United Kingdom only)

Send 20p for illustrated leaflet & price list

**ALBEN ENGINEERING CO. LTD.**  
DEPT. PE THE CRESCENT, WORSTHORNE,  
BURNLEY, LANCs. Tel Burnley 20940

# THE COMPONENT CENTRE

7 LANGLEY ROAD - WATFORD - HERTS - WD1 3PS

Phone Watford 45353 Callers welcome 9.30-5.30 Mon-Sat. EC. Wed.

TRANSISTORS			DIODES			LINEAR I.C.'s			
AC126	21p	BC647	14p	MJ2955	99p	BY127	16p	CA3011	86p
AC127	21p	BC648	14p	MJE340	64p	0A47	9p	CA3014	190p
AC128	21p	BC649	14p	MJE2955	99p	0A70	9p	CA3018	86p
AC176	21p	BC657	14p	MJE3055	88p	0A79	14p	CA3020	174p
AC187	23p	BCY32	77p	OC28	108p	0A81	15p	CA3023	186p
AC188	23p	BCY70	17p	OC35	108p	0A85	14p	CA3028	85p
AD149	65p	BCY71	20p	OC71	19p	0A91	7p	CA3030	120p
AD161	50p	BCY72	17p	OC84	46p	0A95	9p	CA3035	190p
AD162	50p	BD115	59p	PT29	50p	0A200	9p	CA3036	115p
AF114	30p	BD124	97p	TIP30	52p	0A202	9p	CA3042	198p
AF115	27p	BD131	47p	TIP31	59p	IN914	4p	CA3045	275p
AF116	25p	BD132	47p	TIP32	59p	IN916	6p	CA3046	90p
AF117	23p	BD135	43p	TIP33	107p	IN4001	6p	CA3048	205p
AF118	30p	BD136	50p	TIP34	60p	IN4002	6p	CA3049	154p
AF124	32p	BD137	50p	TIP35	263p	IN4003	6p	CA3052	152p
AF125	32p	BD138	51p	TIP36	389p	IN4004	7p	CA3054	73p
AF126	32p	BD139	51p	TIP41	59p	IN4005	10p	CA3078	136p
AF139	40p	BD140	52p	TIP42	59p	IN4006	10p	CA3080	57p
AF239	45p	BF173	30p	TIP2955	126p	IN4007	11p	CA3081	148p
BC107	9p	BF179	37p	TIP3055	64p	3A-50V	16p	CA3086	47p
BC108	9p	BF180	37p	ZTX108	12p	3A-100V	16p	CA3090	329p
BC109	9p	BF181	37p	ZTX300	12p	3A-200V	18p	CA310E	113p
BC147	10p	BF182	37p	ZTX600	12p	3A-400V	20p	CA3140E	74p
BC148	10p	BF183	37p	ZN1305	25p	3A-600V	25p	CA3160E	140p
BC149	10p	BF194	13p	2N1306	39p	10A-50V	25p	LM301	38p
BC157	11p	BF195	13p	2N1711	21p	10A-100V	25p	LM308	54p
BC158	11p	BF196	13p	2N2219	21p	10A-200V	28p	LM380	106p
BC159	11p	BF197	16p	2N2904	26p	10A-400V	36p	LM381	120p
BC168	12p	BF200	36p	2N2905	26p	10A-600V	42p	LM710	41p
BC169	12p	BF201	36p	2N2906	26p			LM741	24p
BC171	12p	BF257	37p	2N2926G	9p			LM747	73p
BC172	12p	BF258	40p	2N2926R	9p			LM748	38p
BC173	12p	BF259	44p	2N2955	99p	1A 50V	22p	LM3900	73p
BC177	16p	BF339	30p	2N3053	17p	1A 100V	24p	MC1304	292p
BC178	16p	BF329	34p	2N3054	54p	1A 200V	27p	MC1310	197p
BC179	16p	BF330	38p	2N3055	54p	1A 400V	30p	MC1458	78p
BC182L	13p	BF384	27p	2N3702	10p	2A 100V	34p	MC1496	78p
BC183L	13p	BF385	29p	2N703	10p	1A 600V	34p	NE555	33p
BC184L	13p	BF386	31p	2N3704	12p	2A 50V	34p	NE566	76p
BC212L	13p	BF387	31p	2N3705	12p	2A 100V	38p	NE567	175p
BC213L	13p	BF388	29p	2N3706	12p	2A 200V	38p	NE568	126p
BC214L	14p	BF390	17p	2N3708	12p	2A 400V	42p	NE569	175p
BC228	14p	BF391	17p	2N3709	12p	2A 600V	42p	NE569	175p
BC303	30p	BSX20	21p	2N3711	10p			SN76003	185p
BC328	15p	BU105	191p	TS43	40p	2A 100V	26p	SN76013	185p
BC338	15p	BU208	299p	2N2646	56p	2A 200V	42p	SN76023	160p
						6A 100V	50p	SN76033	259p
						6A 200V	66p	TAA621	257p
						6A 400V	83p	TAA661	175p
						10A 100V	69p	TBA40	236p
						10A 200V	100p	TBA641	281p
						10A 400V	113p	TBA800	102p
						10A 400V Plus	130p	TBA810	113p
								TBA820	90p

C.-MOS		T.T.L.		D.I.L. SOCKETS			LOUDSPEAKERS				
4000	16p	7400	13p	8 pin	10p	16 pin	14p	1 1/2 in	80	72p	
4001	18p	7401	15p	14 pin	13p	28 pin	30p	1 1/2 in	80	72p	
4002	18p	7402	16p					2 in	80	72p	
4006	110p	7403	17p					2 1/2 in	80	64p	
4007	20p	7404	22p					2 1/2 in	80	64p	
4008	97p	7405	22p					2 1/2 in	640	72p	
4009	62p	7406	44p					18p	2 in	80	76p
4010	62p	7407	44p					30p	2 in	80	118p
4011	19p	7408	22p					4p			
4012	20p	7409	23p					5p			
4013	59p	7410	16p								
4014	106p	7411	24p								
4015	97p	7412	24p								
4016	59p	7413	38p								
4017	99p	7414	66p								
4018	99p	7416	33p								
4019	65p	7417	33p								
4020	119p	7420	15p								
4021	99p	7425	28p								
4022	94p	7427	28p								
4023	21p	7430	20p								
4024	83p	7432	28p								
4025	20p	7437	29p								
4026	20p	7437	29p								
4027	89p	7442	74p								
4028	96p	7445	123p								
4029	118p	7446	123p								
4030	62p	7447	102p								
4031	248p	7448	130p								
4032	108p	7454	18p								
4033	157p	7470	39p								
4035	130p	7472	28p								
4041	87p	7473	39p								
4042	85p	7474	33p								
4043	99p	7475	48p								
4044	96p	7476	40p								
4045	150p	7480	46p								
4046	131p	7482	91p								
4047	95p	7483	90p								
4049	65p	7485	106p								
4050	65p	7486	36p								
4054	120p	7489	39p								
4055	140p	7490	57p								
4056	140p	7491	82p								
4060	117p	7492	57p								
4066	70p	7493	57p								
4067	410p	7494	83p								
4068	24p	7495	70p								
4069	22p	7496	83p								
4070	60p	74100	130p								
4071	22p	74107	36p								
4072	23p	74118	125p								
4073	167p	74121	38p								
4077	65p	74122	55p								
4078	24p	74123	103p								
4081	23p	74148	345p								
4082	23p	74145	83p								
4086	24p	74153	62p								
4501	19p	74154	136p								
4502	130p	74165	115p								
4507	59p	74174	132p								
4510	132p	74175	93p								
4516	132p	74180	85p								
4518	114p	74181	295p								
4519	60p	74192	131p								
4532	138p	74193	131p								
4539	119p	74198	185p								

### OPTO

TIL209	Red	14p
TIL209	Yellow	24p
TIL209	Green	24p
	Red	18p
	Yellow	30p
	Green	30p
TIL209 Clip		4p
Clip		5p

### NEONS

Red	39p
Green	39p
Amber	39p
Neon Bulb	20p

### RESISTORS

0.3 watt 100 to 1MΩ E24	2p
0.5 watt 10Ω to 10MΩ E24	24p
2.5 watt 0.22Ω to 100Ω w/w	23p
5 watt 4.7Ω to 10KΩ w/w	12p
10 watt 10Ω to 10KΩ w/w	15p

### POTENTIOMETERS

1KΩ-2MΩ S/G Lin-Log	27p
5KΩ-2MΩ S/gang Switch Log	55p
5KΩ-2MΩ D/gang Lin-Log	70p

### SLIDERS

5KΩ-500KΩ S/G Lin-Log	73p
5KΩ-500KΩ D/G Lin-Log	98p
Presets sub. min. 100Ω-5MΩ	10p
Slider Bezels	21p
Slider knobs	10p

### CAPACITORS

Min ceramic	4p each
22 pf to 3300 pf	

### SWITCHES

Large Toggle	27p
SPST	29p
DPDT	35p
SPDT	66p
Toggle	58p
Min Toggle	55p
DPDT	58p
SPDT	70p
C. off	58p
Sub. min.	58p
Toggle	52p
DPDT	60p
SPST	60p
DPDT	69p
SPST	69p

# KITS FOR SYNTHESISERS, SOUND EFFECTS



**COMPONENTS SETS** include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

**CIRCUIT AND LAYOUT DIAGRAMS** are supplied free with all PCBs unless "as published".

**PHOTOCOPIES** of all P.E. texts for most of the kits are available—prices in our lists.

# PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

## P.E. MINISONIC Mk. 2 SYNTHESISER

A portable mains-operated Miniature Sound Synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser the functions offered by this design give it great scope and versatility. Consists of 2 log VCOs, VCF, 2 envelope shapers, 2 voltage controlled amps, keyboard hold and control circuits, HF oscillator and detector, ring modulator, noise generator, mixer, power supply.

Set of basic component kits from **£62.23**  
Set of printed circuit boards **£9.71**

## P.E. SYNTHESISER (P.E. Feb. 73 to Feb. 74)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. Other circuits in our lists may be used with the Synthesiser to good advantage.

**The Main Synthesiser:** PSU, 2 linear VCOs, 2 ramp generators, 2 input amps, sample hold, noise generator, reverb amp, ring modulator, peak level circuit, envelope shaper, voltage controlled amp.

Set of basic component kits **£83.03**  
Set of printed circuit boards **£13.20**

**The Synthesiser Keyboard Circuits** (can be used without the Main Synthesiser to make an independent musical instrument): 2 logarithmic VCOs, divider, 2 hold circuits, 2 modulation amps, mixer, 2 envelope shapers and PSU.

Set of basic component kits **£48.18**  
Set of printed circuit boards **£7.66**

## GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches **£7.59**  
Alternative component set with panel switches **£4.96**  
Printed circuit board **£1.43**

## SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.

Component set for above functions (excl. SWs) **£7.84**  
Printed circuit board **£1.81**  
Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce "jungle-drum" rhythms.  
Component set (incl. PCB) **£2.88**

## PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB) **£2.87**

## PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl. PCB) **£4.48**

## SOPHISTICATED PHASING AND VIBRATO UNIT

A slightly modified version of the circuit published in "Elektron", December 1976, and includes manual and automatic control over the rate of phasing and vibrato.

Component set **£17.69**  
Printed circuit board **£2.33**

## WAH-WAH UNIT (P.E. Apr. 76)

The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller.

Component set (incl. PCB) **£3.55**

## AUTOWAH UNIT (P.E. Mar. 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played.

Component set, PCB, special foot switches **£7.27**  
Component set and PCB, with panel switches **£4.83**

## P.E. JOANNA PLUS ORGAN VOICING

The basic five octave electronic piano (P.E. May/Sept 75 and Sound Design) has switchable alternative voicings for Honky-Tonk, ordinary piano, and Harpsichord or a mixture of any of these three, together with facilities including fast and slow tremolo, loud and soft pedal switching, and sustain pedal switching. The modification retains all the circuitry associated with the piano but in addition provides an organ-voice envelope facility with 5 switchable pitches, variable attack and sustain, phasing and vibrato.

Set of components (excl switches) for PSU, Frequency generator, Pitch and Note Divider, Envelope Shapers, Voicings, and Control circuitries. (Order as KIT 71-5) **£109.75**  
Set of PCBs (Order as PCB SET 71-6) **£29.18**

## SYNTHESISER TUNING INDICATOR (P.E. July 77)

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of the P.E. Tuning Fork is not required.

Component and PCB (but excl sw.) **£7.45**

## GUITAR FREQUENCY DOUBLER (P.E. Aug. 77)

A modified and extended version of the circuit published.

Component set and PCB **£4.22**

## GUITAR SUSTAIN (P.E. Oct 77)

Maintains the natural attack whilst extending note duration.

Component set, PCB and foot switches **£4.90**  
Component set, PCB and panel switches **£3.48**

## WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set (incl. PCB) **£3.72**

## GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual slider pot **£6.86**  
Component set using dual rotary pot **£6.20**  
Printed circuit board **£1.62**

## FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) **£2.05**

## TREMOLO UNIT

Based upon P.E. "Sound Design" circuit.

Component set (incl. PCB) **£3.64**

## TREBLE BOOST UNIT (P.E. Apr. 76)

Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable.

Component set (incl. PCB) **£2.40**

## P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments: Ideal for tuning acoustic or electronic musical instruments.

Main Component set (incl. PCB) **£15.59**  
Power supply set (incl. PCB) **£7.03**

SEE OTHER PAGE FOR KEYBOARDS, AND OUR LISTS FOR OTHER COMPONENTS AND ACCESSORIES STOCKED

## P.E. SYNCHRONOME (P.E. Mar. 76)

An accented-beat electronic metronome, providing duple, triple and quadruple times with full control over the beat rate. Can also be used as a simple drum-beat rhythm generator. Includes power supply.

Component set (incl. loudspeaker) **£11.62**  
Printed circuit board **£2.04**

## TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings. All kits include PCBs

Standard tolerance set of components **£2.96**  
Superior tolerance set of components **£3.76**  
Regulated power supply (will drive 2 sets) **£4.69**

## ENVELOPE SHAPER WITHOUT VCA (P.E. Oct. 75)

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing voltage controlled amplifier.

Component set (incl. PCB) **£4.66**

## ENVELOPE SHAPER WITH VCA (P.E. Apr. 76)

This unit has its own voltage controlled amplifier and has full manual control over attack, decay, sustain and release functions.

Component set (incl. PCB) **£6.68**

## TRANSIENT GENERATOR (P.E. Apr. 77)

An envelope shaper, without VCA, having the usual attack, decay, sustain and release functions, and in addition it also provides a "Repeat Effect" enabling a synthesiser to be programmed to imitate such instruments as a mandolin or banjo.

Component set **£4.52**  
Printed circuit board **£1.82**

## WAVEFORM CONVERTER

Slightly modified from a circuit published in "Elektron". Converts a saw-tooth waveform into four different waveforms: sine-wave, mark-space saw-tooth, regular triangle form, and squarewave with an externally variable mark-space ratio.

Component set (incl. PCB but excl. sw/s) **£8.19**

## VOLTAGE CONTROLLED FILTER (P.E. Dec. 74)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 65-1) **£8.22**

## RING MODULATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 59-1) **£5.50**

## NOISE GENERATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 60-1) **£3.35**

## SOPHISTICATED POWER SUPPLIES

A wide range of highly stabilised low noise power supply kits is available—details in our lists.

## MICROPHONE PRE-AMP (P.E. Apr. 77)

Component set (incl. PCB) **£3.78**

## VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows.

Component set (incl. PCB) **£3.97**

## DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

Component set (incl. PCB) **£4.58**

## POST AND HANDLING

U.K. orders—under £15 add 25p plus VAT, over £15 add 50p plus VAT. Keyboards £2.00 plus VAT.

Optional Insurance for compensation against loss or damage in post, add extra 50p for cover up to £50, £1.00 for £100 cover, £2.00 for £200 cover.

Eire, C.I., B.F.P.O., and other countries are subject to Export postage rates.

## DON'T FORGET VAT!

Add 12½% (or current rate if changed) to full total of goods, post and handling. (Does not apply to export orders).

**EXPORT ORDERS** are welcome, though we advise that a current copy of our list should be obtained before ordering as it also shows Export postage rates. All payments must be cash-with-order, in Sterling and preferably by International Money Order or through an English Bank. To obtain list send 50p.

PHONOSONICS · DEPT. PE67 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH MAIL ORDER AND C.W.O. ONLY SORRY BUT NO CALLERS PLEASE

# AND OTHER PROJECTS

**PHOTOGRAPHS** in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

**LIST**—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

**OVERSEAS** enquiries for list: Europe—send 20p; other countries—send 50p.



## KIMBER-ALLEN KEYBOARDS AND CONTACTS

Kimber-Allen Keyboards as required for many published circuits. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

- 3 Octave (37 notes) £25-50
- 4 Octave (49 notes) £32-25
- 5 Octave (61 notes) £39-75

**Contact Assemblies** (gold-clad wire) for use with the above keyboards (1 required for each note):

- Type GJ: Single-pole change-over each 24p
- Type GB: 2 pairs of contacts, each pair normally open each 27p
- Type GC: 3 pairs of contacts, each pair normally open each 36p
- Type GE: 4 pairs of contacts, each pair normally open each 45p
- Type GH: 5 pairs of contacts, each pair normally open each 57p
- Type 4PS: 3 pairs of contacts plus single-pole changeover each 53p

Printed Circuit Boards for use with GJ, GB and 4PS contacts (thus eliminating much interwiring) are available. Details in our lists.

### RHYTHM GENERATOR

- 15-Rhythm Tempo, Timing and Logic control unit (excl. sw's but incl. PCB) £12-90
- 10-Instrument Effects circuits £13-56
- PCB for Effects circuits £4-25
- Power Supply incl. PCB £12-00

### 128-NOTE TUNE-PROGRAMMABLE SEQUENCER

(P.E. Nov/Dec 77)

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable. (Please use order codes quoted in brackets.)

- Main Circuit (Nov) excl. sw's (KIT 76-1) £20-60
- Power Supply (KIT 76-3) £6-05
- Trigger Inverter and Alt. Output (KIT 76-2) £1-35
- LED Counter (KIT 76-4) £2-45
- PCB (as published) for KITS 76-1 & 3 (PCB 76A) £2-61
- PCB for KITS 76-2 & 4 (PCB 76B) £2-54

### P.E. STRING-ENSEMBLE (P.E. commencing Mar 78)

The new keyboard string-instrument synthesiser.

- Power Supply Basic component set £9-22
- Tone Generators (incl. Test components) £14-93
- PCB for PSU and Tone Generator £3-40

Details of further kits and PCBs in our list.

### FORMANT SYNTHESISER (Elektr 1977/78)

Very sophisticated music synthesiser for the advanced constructor who puts performance before price. Details in our lists.

### 3-CHANNEL SOUND-TO-LIGHT (P.E. Apr. 76)

A simple but effective sound-to-light controller capable of operating 3 lamps each of approximately 700 watts. Includes power supply, thyristors, and by-pass switches.

- Component set (incl. PCB) £11-95

### DISCOSTRDBE (P.E. Nov. 76)

4-channel light-show controller giving a choice of sequential, random, or full strobe mode of operation.

- Basic component set £18-19
- Printed circuit board £3-45

### BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie-detector, alphaphona, cardiophone etc.

- Pre-Amp Module Components set (incl. PCB) £4-22
- Basic Output Circuits—combined component set with PCBs, for alphaphona, cardiophone, frequency meter and visual feed-back lampdriver circuits. £6-59
- Audio Amplifier Module Type PC7 £7-75

### 10% DISCOUNT VOUCHER (PE67)

**TERMS:** Correctly costed, C.V.O., U.K. orders over £40 goods value. Valid until end of month on cover of P.E. This voucher must accompany order.

**PRICES ARE CORRECT AT TIME OF PRESS.**  
E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

### TRANSISTORS

- AC128.....26p
- AC176.....26p
- BC107.....14p
- BC108.....14p
- BC109.....14p
- BC109C.....15p
- BC177.....14p
- BC184.....12p
- BC187.....25p
- BC204.....14p
- BC209C.....14p
- BC213.....15p
- BC214.....15p
- BC262.....25p
- BC415.....19p
- BC478.....26p
- BD131.....44p
- BD132.....54p
- BF244A.....44p
- BF245A.....24p
- BSY95A.....22p
- MD8001.....172p
- OC72.....30p
- RPY58A.....48p
- TI543.....60p
- ZTX108.....9p
- ZTX301.....13p
- ZTX384.....16p
- ZTX501.....27p
- 2N2219.....21p
- 2N2646.....50p
- 2N2905.....35p
- 2N2905A.....36p
- 2N2906.....22p
- 2N2907.....22p
- 2N3054.....66p
- 2N3055.....60p
- 2N3702.....12p
- 2N3704.....12p
- 2N3819.....35p
- 2N3820.....64p
- 2N3823E.....39p
- 2N5459.....45p

### INTEGRATED CIRCUITS

- 301 8-pin DIL 48p
- 318 8-pin DIL 230p
- 320-15 58p
- 324 14-pin DIL 87p
- 341-15 195p
- 709 8-pin DIL 48p
- 723 705 105p
- 723 14-pin DIL 58p
- 726 T05 980p
- 741 8-pin DIL 32p
- 748 8-pin DIL 63p
- 4024 14-pin DIL 461p
- 4069 14-pin DIL 15p
- 4136 14-pin DIL 126p
- 7805 T0220 205p
- 7806 T0220 205p
- 7808 T0220 205p
- 7812 T0220 205p
- 7815 T0220 205p
- 7818 T0220 205p
- AY10212 16-pin DIL 650p
- AY16721/6 195p
- CA3046 14-pin DIL 90p
- CA3080 8-pin DIL 82p
- CA3084 14-pin DIL 208p
- M252 16-pin DIL 420p
- MC3340 8-pin DIL 150p
- MC6810 24-pin DIL 870p
- SG3402N 14-pin DIL 262p
- STK005 595p
- TDA1022 16-pin DIL 672p
- KR2207 14-pin DIL 420p
- ZN425E 16-pin DIL 375p

## PHONOSONICS

# WIRE WRAPPING CENTRE

**HOBBY WRAP**  
Model BW 630

Battery wire-wrapping tool. Complete with bit and bit liner.

NEW

AC24-77 BT29-58 CE2-61 DE-69

**WIRE WRAPPING TOOL**  
For .025" (0.63mm) sq. cost "MODIFIED" wrpd. positive indexing, anti-overwrapping device.

A For AWG 30 BW-630  
B For AWG 26-28 BT-2628

C Bit for AWG 30 BT-30  
D Bit for AWG 26-28 BT-2628

£3.77

**OK PLIERS AND CUTTERS**

**UNIVERSAL CUTTER**  
Cuts everything. Leather, wire, plastic, tin-plate, cardboard, stainless steel blades.

Cuts in one of the ranges of high quality pliers, cutters, tweezers and screwdrivers.

3136 £3-20

**3 IN 1 WIRE DISPENSER**  
New wire dispenser cuts and strips three different counts of wire. Quick and easy to use pocket size.

£3.77

**WIRE WRAPPING KIT**  
Contains: Hobby Wrap Tool WSU-30, Wire Dispenser WD-308, (2) 14 DIP's, (2) 16 DIP's, Hobby Board HB-1, DIP/IC Insertion Tool EX-146 and Dip/IC Extractor Tool EX-1.

Wire Wrapping Kit (Burg)  
£17-80

**HOBBY WRAP TOOL**  
Wire-wrapping, stripping, unwrapping tool for AWG 30 on .025" (0.63mm) Square Post.

Regular wrap WSU-30 £4-39  
Modified wrap WSU-30M £4-69

**TERMINAL AND DISTRIBUTION STRIPS**  
Bread boarding building blocks with universal matrices of solderless plug-in leads.

Facilitates quick, solderless circuit build-up and check-out on universal .1" x .1" matrix.

FROM 75p

- Are offered in ten configurations.
- Accept all components with leads up to .032" diameter.
- Require no special patch cords.
- Includes integral non-shorting instant mounting backing.

**IC TEST CLIPS**

**FOR DUAL-IN-LINE PACKAGES**

- Provide full access to integrated circuit DIP leads.
- Remove DIP's damage free.
- Available in sizes to accommodate all DIP's, IC-14 line 14-pin DIP's, etc.

£2-75

**DIP/IC INSERTION TOOL WITH PIN STRAIGHTENER**

Facilitates quick, solderless circuit build-up and check-out on universal .1" x .1" matrix.

FROM 14p

**IC SOCKET**  
Quasi-in-line package. 3 level wire-wrapping, pin-through bronze contact, gold plated pins. .025" (0.63mm) dia. x .100" (2.54mm) centre spacing.

14 Pin Dip Socket 14 Dip  
16 Pin Dip Socket 16 Dip

**RIBBON CABLE ASSEMBLY** FROM £2-70

- With 14 Pin Dip Plug 2 Long (DL 12)
- With 16 Pin Dip Plug 4 Long (DL 14)
- With 14 Pin Dip Plug 2 Long (DL 12)
- With 16 Pin Dip Plug 2 Long (DL 12)
- With 14 Pin Dip Plug 2 Long (DL 12)
- With 16 Pin Dip Plug 2 Long (DL 12)

**OK Machine & Tool UK Limited**

48a The Avenue, Southampton SO1 2SV

Telephone Southampton (0703) 38966 7 Telex 477222 Cablegram OKMAC

**DISTRIBUTORS WANTED\*\***

**OK Machine & Tool UK Limited**

**DISTRIBUTORS WANTED\*\***

# ASTRA-PAK

92 GODSTONE ROAD  
WHYTELEAF SURREY CR3 0EB

All prices include V.A.T. Add 25p for P&P (Extra for overseas). Discounts over £10 less 5%, over £20 less 10%, over £50 less 15%, over £100 less 20%.

Send SAE for complete list of components.

7400 0.12	7492 0.44	74181 1.92	74LS75 0.45	74LS293 0.90	4052 0.84
7401 0.12	7493 0.40	74182 0.75	74LS76 0.32	74LS298 1.60	4053 0.84
7402 0.12	7494 0.80	74184 1.20	74LS78 0.32	74LS352 0.92	4054 1.10
7403 0.12	7495 0.54	74185A 1.20	74LS83 0.78	74LS353 1.05	4055 1.00
7404 0.13	7496 0.60	74186 7.20	74LS85 0.90	74LS365 0.50	4060 0.98
7405 0.13	7497 2.36	74188 2.70	74LS86 0.35	74LS366 0.50	4065 0.48
7420 0.28	74100 0.94	74190 1.05	74LS93 0.95	74LS367 0.50	4067 3.80
7407 0.28	74104 0.40	74191 0.99	74LS95 1.10	74LS368 0.50	4068 2.20
7408 0.14	74105 0.40	74192 0.99	74LS107 0.36	74LS386 3.37	4069 0.17
7409 0.14	74107 0.28	74193 1.05	74LS109 0.36	74LS670 2.00	4070 0.17
7410 0.13	74109 0.45	74194 0.90	74LS112 0.38		4071 0.17
7411 0.18	74110 0.46	74195 0.89	74LS113 0.38		4072 0.17
7412 0.21	74111 0.70	74196 0.90	74LS114 0.38	4000 0.14	4073 0.17
7413 0.25	74116 1.60	74197 0.90	74LS123 0.82	4001 0.15	4075 0.17
7414 0.54	74118 0.82	74198 1.48	74LS124 2.45	4002 0.16	4076 1.05
7416 0.27	74119 1.30	74199 1.48	74LS125 0.44	4006 0.92	4077 0.46
7417 0.27	74120 0.82	74211 1.97	74LS126 0.44	4007 0.46	4078 0.22
7420 0.13	74121 0.25	74273 2.15	74LS132 0.89	4008 0.92	4081 0.17
7421 0.28	74122 0.40	74279 1.25	74LS136 0.40	4009 0.45	4082 0.20
7422 0.17	74123 0.53	74283 1.70	74LS138 0.53	4010 0.48	4085 0.72
7423 0.25	74125 0.44	74284 6.85	74LS139 0.53	4011 0.15	4086 0.76
7425 0.20	74126 0.45	74283 1.35	74LS151 1.05	4012 0.16	4089 1.55
7426 0.25	74128 0.62	74298 1.92	74LS153 1.50	4013 0.42	4093 0.65
7427 0.25	74132 0.88	74390 1.92	74LS154 1.20	4014 0.80	4094 1.80
7428 0.34	74135 0.68	74393 2.12	74LS155 0.86	4015 0.77	4095 1.10
7430 0.13	74136 0.75		74LS156 0.86	4016 0.42	4096 1.10
7432 0.24	74137 0.94		74LS157 0.47	4017 0.77	4097 3.50
7433 0.32	74141 0.58	74LS00 0.19	74LS158 0.53	4018 0.87	4098 1.12
7437 0.24	74142 2.00	74LS01 0.19	74LS160 1.22	4019 0.42	4099 1.90
7438 0.24	74143 2.00	74LS02 0.19	74LS161 0.69	4020 0.92	4404 1.00
7440 0.13	74144 2.00	74LS03 0.19	74LS162 1.22	4021 0.82	4412 0.30
7441 0.52	74145 0.64	74LS04 0.20	74LS163 0.69	4022 0.82	4428 0.80
7442 0.55	74147 1.30	74LS05 0.20	74LS164 1.20	4023 0.15	4445 1.50
7443 0.90	74148 1.18	74LS08 0.19	74LS168 2.00	4024 0.66	4449 0.30
7444 0.90	74150 0.89	74LS09 0.19	74LS169 2.00	4025 0.15	4501 0.17
7445 0.70	74151 0.60	74LS10 0.19	74LS170 1.76	4026 1.28	4502 0.88
7446 0.70	74153 0.60	74LS11 0.19	74LS173 1.05	4027 0.50	4507 5.00
7447A 0.64	74154 1.05	74LS12 0.19	74LS174 1.12	4028 0.67	4508 2.25
7448 0.60	74155 0.63	74LS13 0.46	74LS175 1.05	4029 0.86	4510 1.05
7450 0.13	74156 0.63	74LS14 1.10	74LS189 2.85	4030 0.48	4511 0.98
7451 0.13	74157 0.63	74LS15 0.19	74LS190 0.81	4031 2.84	4512 2.00
7452 0.13	74159 1.70	74LS20 0.19	74LS191 0.81	4032 1.25	4514 2.95
7454 0.13	74160 0.80	74LS21 0.19	74LS192 1.80	4034 2.00	4515 2.80
7460 0.13	74161 0.80	74LS22 0.19	74LS193 1.80	4035 1.00	4516 1.20
7470 0.28	74162 0.80	74LS26 0.24	74LS195 1.12	4036 2.40	4518 0.99
7472 0.22	74163 0.80	74LS27 0.40	74LS196 1.20	4037 0.99	4519 0.50
7473 0.26	74164 0.89	74LS30 0.19	74LS197 1.20	4038 1.00	4520 1.05
7474 0.26	74165 0.89	74LS32 0.25	74LS221 1.12	4039 1.40	4521 2.00
7475 0.30	74166 0.99	74LS37 0.27	74LS247 0.97	4040 0.88	4522 1.35
7476 0.26	74167 2.70	74LS38 0.27	74LS248 0.97	4041 0.77	4527 1.60
7480 0.45	74170 1.68	74LS40 0.19	74LS249 0.97	4042 0.72	4528 0.92
7481 0.90	74172 4.00	74LS42 0.53	74LS251 1.00	4043 0.82	4529 1.10
7482 0.80	74173 1.18	74LS47 0.97	74LS253 1.05	4044 0.82	4536 3.56
7483 0.72	74174 0.89	74LS48 0.97	74LS257 1.05	4045 1.40	4537 2.20
7484 0.90	74175 0.68	74LS49 0.97	74LS258 1.05	4046 1.32	4555 0.85
7485 0.88	74176 0.88	74LS51 0.19	74LS266 0.39	4047 0.96	4556 0.85
7486 0.26	74177 0.88	74LS54 0.19	74LS273 2.50	4048 0.60	4558 1.25
7489 2.00	74178 1.20	74LS55 0.20	74LS279 0.50	4049 0.42	4566 1.40
7490 0.35	74179 1.10	74LS73 0.30	74LS283 1.00	4050 0.42	4583 0.75
7491 0.65	74180 0.90	74LS74 0.34	74LS289 2.85	4051 0.84	4585 1.03

# You'll learn a lot from the free Heathkit catalogue.



**NEW Computer Systems**  
Send for a special 16 page brochure.



**NEW Bi-directional RF Wattmeter**



**NEW De-luxe Coin-tracking Metal Locator**



**NEW De-luxe 12" CRT Ignition Analyser**

The Heathkit catalogue is packed with scores of top quality electronic kits. Educational, practical and fascinating items which you can build yourself.

## Send for the catalogue now.

To Heath (Gloucester) Limited,  
Department PE78, Bristol Road,  
Gloucester, GL2 6EE.

Name

Address

Please tick the literature you want and enclose the appropriate amount in postage stamps.  
Heathkit catalogue only  (enclose 11p to cover postage) 16 page computer brochure only  (enclose 20p to cover postage and part costs). N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest catalogue without having to use this coupon.



When you receive your catalogue you'll get details of this free offer worth approximately £4.75.

**HEATH**  
**Schlumberger**  
The world's biggest producers of electronic kits.

**ACCESS AND BARCLAY CARD WELCOMED**

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (Gloucester 29451).

## New from Mantec

**A comprehensive Home Study Course in Electronics**

*Suitable for Beginners and Students*

The Course which gives you "Right from the Start" the practical experience as well as the all important back-up theory.

Suitable preparation for C and G examinations  
**Ensure your future in tomorrow's technology**

The home study course that tells not only how but why

The Course includes:- 1 The Manual. Easy to read and understand, set out in a clear and concise way, includes numerous experiments and diagrams.  
2 The Kit. All components necessary for the experiments and projects covered. Mantec also provides a tutorial support service for students requiring further advice.

Send today for your "Right from the start" Home Study Course. Price £35.00 including VAT.

Fill in the coupon Now!

**Mantec the leaders in Manufacturing Technology**  
Mantec, 7 Dellsome Lane, Welham Green, Hatfield, Herts.

To: Mantec, 7 Dellsome Lane, Welham Green, Hatfield, Herts.

Please send me..... "Right from the Start" home study course(s).

I enclose Cheque/Postal Order for £.....

Name:

Address:

## BARGAIN PARCELS SAVE POUNDS

Huge quantities of electronic components must be cleared as space required. 1000's of capacitors, resistors, transistors. Ex equipment panels etc. covered in valuable components. No time to sort. Must sell by weight 7 lbs - £4.95; 14 lbs - £7.95; 28 lbs - £12.00; 56 lbs - £20.00; 112 lbs - £30.00.

### BARGAIN PACKS

Don't let your environment dehydrate you. Buy a Honeywell Humidity Controller membrane operated with 1/4" shaft, ideal for greenhouses, centrally heated homes, etc. Build your own humidity alarm, 3-75A. Contacts at 250V £1.50 each. 3 for £4.00

4 aluminium boxes 128 x 44 x 38 mm ideal for signal injectors, etc. £1.00.

100 miniature reed switches ideal for burglar alarms, model railways, etc. £3.30.

6 x 6-pole 12 volt reed relays on board £2.45.

High quality computer panels smothered in top grade components: 5 lbs £4.75; 10 lbs £8.95.

Miniature edgewise panel mounting level meters 200 uo. 1sd £1.00.

Miniature transistorised f.m. front end with integral tuning gain 88-108MHz. £2.50.

New U.H.F. transistor TV tuners 4 pushbutton type £3.50.

Rotary type with slow drive and AE. socket £3.50.

Aluminium TV coax plugs. 10 for £1.00.

Miniature 5K log pots with s/p switch. 4 for £1.00.

Hardware Packs each containing 100's of items including: BA nuts and bolts, Nylon, Self-tapping, Posidrive, "P" clips, Cable clamps.

Fuse holders, Spire nuts etc, etc. £1.00 per pound. 100 1/4 in. "P" Clips 60p, 200 for £1.00.

Heavily insulated E.H.T. Discharging Probe with lead and earth connector 60p each.

Ultrasonic transducers, transmitter and receiver 14mm diam. 40kcs £4.25 per pair.

Magnetic earpieces with plug and lead 25p each. 5 for £1.00.

Crystal earpieces with lead 40p each. 3 for £1.00.

DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS

Includes 150 sq. ins. copper clad f/g board, 1 lb ferric chloride, 1 data etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions - only £5.30.

150 sq. in. fibre glass board.....£2.00

Data pen.....90p

1 lb ferric chloride to mil spec.....£1.25

5 lbs ferric chloride to mil spec.....£5.00

Instruction sheet.....20p

40p P & P ON ALL ABOVE ITEMS. SEND CHEQUE OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY, DEPT PE, 149A BROOKMILL RD., DEPTFORD SE8

**VERNITRON FM4 10-7mHz** miniature ceramic filters 50p each. 3 for £1.00.

Miniature mains transformers, fully shrouded. 240V in 6-0-6V at 100MA, out. Ex. New equipment, complete with mains lead and plug on input and short leads on output. 95p.

100K slider pots, slim type, good quality mono or stereo 50p each. 3 for £1.00.

Varicap tuning thumb wheel slider pots, very neat, can be banked side by side 100K. 6 for £1.00.

**Semiconductor Bargains**

TH3 Thermistors. 10 for £1.00.

100 new and marked silicon and germanium transistors including 8C148, BF194, BC183, etc. £3.95

200 new and marked transistors, including 2N3055, AC128, BFY50, BD131, etc. £6.95.

100 mixed diodes IN4148, etc. £1.20.

100 mixed diodes including zener, power and bridge types £3.30.

Bridge rectifier 100V 2.5 amp. 4 for £1.00.

Brand new ITT 25kV T.V. triplers for Decca Bradford chassis £2.50. 5 for £10.00.

50 Germanium diodes ideal for crystal sets etc. £1.00.

Motorola 1 watt audio amplifier I.C. 9-16V, 8-16Q, 10-400MV sensitivity, S.C. proof, no heat sink required. Supplied with data and circuits £1.00.

Data and circuits alone, 20p + SAE.

Full spec. I.R. diodes, 200V 1A. 20 for £1.00.

100 for £4.50. SN7611SN £1.00.

**Component Bargains**

300 mixed resistors 1/4 and 1/2 watt £1.50. 300 modern mixed caps, most types, £3.30. 200 mixed resistors, mostly 1 & 2 watt, £1.50. 100 mixed polyester caps £2.20. 100 mixed modern miniature and ceramic plate caps £1.20. 100 mixed electrolytics £2.20. 300 printed circuit resistors £1.00. 25 mixed pots and presets £1.50. 100 mixed carbon film and metal film resistors mostly miniature lots of values, £1.20. 500 for £4.90. 100 mixed high wattage resistors, wirewound, etc. £2.20. 20 assorted VDRs and Thermistors £1.20. 25 assorted preset pots, skeleton, etc. £1.20.

# 15-240 WATTS!

## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** complete pre-amplifier in single pack; multi-function equalisation; low noise; low distortion; high overload; two simply combined for stereo.

**APPLICATIONS:** hi-fi; mixers; disco; guitar and organ; public address.

**SPECIFICATION:** Inputs—magnetic pick-up 3mV; ceramic pick-up 30mV; tuner 100mV; microphone 10mV; auxiliary 3-100mV; Input Impedance 47k $\Omega$  at 1kHz. Outputs—tape 100mV; main output 500mV R.M.S. Active Tone Controls—treble  $\pm$ 12dB at 10kHz; bass  $\pm$ 12dB at 100Hz. Distortion—0.1% at 1kHz; signal/noise ratio 68dB. Overload—38dB on magnetic pick-up. Supply voltage— $\pm$ 16-50V.

Price  $\pounds$ 5.22 + 65p VAT. P. & P. free

HY5 mounting board B.1. 48p + 6p VAT. P. & P. free



## HY30 15W into 8 $\Omega$

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

**FEATURES:** complete kit; low distortion; short, open and thermal protection; easy to build.

**APPLICATIONS:** updating audio equipment; guitar practice amplifier; test amplifier; audio oscillator.

**SPECIFICATION:** Output Power—15W R.M.S. into 8 $\Omega$ . Distortion—0.1% at 15W. Input Sensitivity—500mV. Frequency Response—10Hz-16kHz -3dB.

Price  $\pounds$ 5.22 + 65p VAT. P. & P. free

## HY50 25W into 8 $\Omega$

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** low distortion; integral heatsink; only five connections; 7 amp output transistors; no external components

**APPLICATIONS:** medium power hi-fi systems; low power disco; guitar amplifier.

**SPECIFICATION:** Input Sensitivity—500mV. Output Power—25W R.M.S. into 8 $\Omega$ . Load Impedance—4-16 $\Omega$ . Distortion—0.04% at 25W at 1kHz. Signal/Noise Ratio—75dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— $\pm$ 25V. Size—105 x 50 x 25mm.

Price  $\pounds$ 6.82 + 85p VAT. P. & P. free



## HY120 60W into 8 $\Omega$


The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

**FEATURES:** very low distortion; integral heatsink; load line protection; thermal protection; five connections; no external components.

**APPLICATIONS:** hi-fi; high quality disco; public address; monitor amplifier; guitar and organ.

**SPECIFICATION:** Input Sensitivity—500mV. Output Power—60W R.M.S. into 8 $\Omega$ . Load Impedance—4-16 $\Omega$ . Distortion—0.04% at 60W at 1kHz. Signal/Noise Ratio—90dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— $\pm$ 35V. Size—114 x 50 x 85mm.

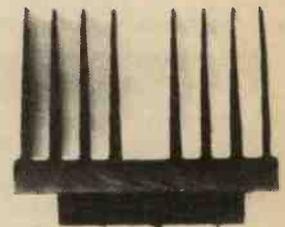Price  $\pounds$ 15.84 +  $\pounds$ 1.27 VAT. P. & P. free



## HY200 120W into 8 $\Omega$


The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

**FEATURES:** thermal shutdown; very low distortion; load line protection; integral heatsink; no external components.

**APPLICATIONS:** hi-fi; disco; monitor; power slave; industrial; public address.

**SPECIFICATION:** Input Sensitivity—500mV. Output Power—120W R.M.S. into 8 $\Omega$ . Load Impedance—4-16 $\Omega$ . Distortion—0.05% at 100W at 1kHz. Signal/Noise Ratio—96dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— $\pm$ 45V. Size—114 x 50 x 85mm.

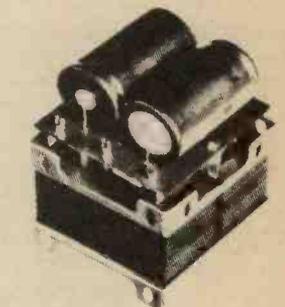Price  $\pounds$ 23.32 +  $\pounds$ 1.87 VAT. P. & P. free



## HY400 240W into 4 $\Omega$

The HY400 is I.L.P.'s 'Big Daddy' of the range producing 240W into 4 $\Omega$ ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** thermal shutdown; very low distortion; load line protection; no external components.

**APPLICATIONS:** public address; disco; power slave; industrial.

**SPECIFICATION:** Output Power—240W R.M.S. into 4 $\Omega$ . Load Impedance—4-16 $\Omega$ . Distortion—0.1% at 240W at 1kHz. Signal/Noise Ratio—94dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— $\pm$ 45V. Input Sensitivity—500mV. Size—114 x 100 x 85mm.

Price  $\pounds$ 32.17 +  $\pounds$ 2.57 VAT. P. & P. free

**POWER SUPPLIES:** PSU36—suitable for two HY30s  $\pounds$ 5.22 + 65p VAT. P. & P. free. PSU50—suitable for two HY50s  $\pounds$ 6.82 + 85p VAT. P. & P. free. PSU70—suitable for two HY120s  $\pounds$ 13.75 + 1.10 VAT. P. & P. free. PSU90—suitable for one HY200  $\pounds$ 12.65 +  $\pounds$ 1.01 VAT. P. & P. free. PSU100—suitable for two HY200s or one HY400  $\pounds$ 23.10 +  $\pounds$ 1.85 VAT. P. & P. free.

I.L.P. Electronics Ltd., Crossland House, Nackington, Canterbury, Kent CT4 7AD

## TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.  
Crossland House,  
Nackington, Canterbury  
Kent CT4 7AD  
Tel (0227) 63218

Please supply .....

Total Purchase price .....

Enclose: Cheque  Postal Orders  Money Order

Please debit my Access account  Barclaycard account

Account number .....

Name and Address .....

Signature .....

Registered office No. 1032630

# BOOKS AND COMPONENTS

## BOOKS BY BABANI

Purchase books to the value of £5.00 from the list below and choose any 60p pak from this page **FREE**.

BP2	Handbook of Radio, TV & Industrial & Transmitting Tube & Valve Equivalents	60p†
BP3	Handbook of Tested Transistor Circuits	40p†
BP6	Engineers and Machinists Reference Tables	40p†
BP7	Radio & Electronic Colour Codes and Data	15p†
BP10	Modern Crystal and Transistor Set Circuits for beginners	35p†
BP15	Constructors Manual of Electronic Circuits for the Home	50p†
BP16	Handbook of Electronic Circuits for the Amateur Photographer	60p†
BP18	Boys and Beginners Book of Practical Radio and Electronics	60p†
BP22	79 Electronic Novelty Circuits	75p†
BP23	First book of Practical Electronic Projects	75p†
BP24	52 Projects Using IC741 (or equivalents)	75p†
BP26	Radio Antenna Handbook for Long Distance Reception and Transmission	85p†
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	60p†
BP29	Major Solid State Audio Hi-Fi Construction Projects	85p†
BP32	How to Build Your Own Metal & Treasure Locators	85p†
BP34	Practical Repair & Renovation of Colour TVs	95p†
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	95p†
BP36	50 Circuits Using Germanium, Silicon & Zener Diodes	75p†
BP37	50 Projects Using Relays, SCR's and TRIACS	£1.10†
BP39	50 (FET) Field Effect Transistor Projects	£1.25†
129	Universal Gram-motor Speed Indicator	10p†
160	Coil Design and Construction Manual	75p†
161	Radio, TV and Electronics Data Book	60p†
196	AF-RF Reactance—Frequency Chart for Constructors	15p†
202	Handbook of Integrated Circuits (ICs) Equivalents and Substitutes	75p†
205	First Book of Hi-Fi Loudspeaker Enclosures	75p†
213	Electronic Circuits for Model Railways	85p†
214	Audio Enthusiasts Handbook	85p†
216	Electronic Gadgets and Games	85p†
217	Solid State Power Supply Handbook	85p†
219	Solid State Novelty Projects	85p†
220	Build Your Own Solid State Hi-Fi and Audio Accessories	85p†
222	Solid State Short Wave Receivers for Beginners	95p†
223	50 Projects Using IC CA3130	95p†
224	50 CMOS IC Projects	95p†
225	A Practical Introduction to Digital IC's	95p†
226	How to Build Advanced Short Wave Receivers	£1.20†
RCC	Resistor Colour Code Disc Calculator	10p†

## BOOKS BY NEWNES

No. 229	Beginners Guide to Electronics	Price £2.25†
No. 230	Beginners Guide to Television	Price £2.25†
No. 231	Beginners Guide to Transistors	Price £2.25†
No. 233	Beginners Guide to Radio	Price £2.75†
No. 234	Beginners Guide to Colour Television	Price £2.25†
No. 235	Electronic Diagrams	Price £1.80†
No. 236	Electronic Components	Price £1.80†
No. 237	Printed Circuit Assembly	Price £1.80†
No. 238	Resistor Pocket Book	Price £3.90†
No. 225	110 Thyristor Projects Using SCRs & Triacs	Price £2.50†
No. 227	110 COS/MOS Digital IC Projects For the Home Constructor	Price £2.75†
No. 226	110 Operational Amplifier Projects for the Home Constructor	Price £2.50†
No. 242	Electronics Pocket Book	Price £3.90†
No. 239	30 Photoelectric Circuits & Systems	Price £1.80†

## NUTS AND BOLTS

**BA BOLTS** - packs of BA threaded cadmium plated screws slotted cheese head.  
Supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
1in OBA	839	£1.20	1in 4BA	846	£0.32
1in OBA	840	£0.75	1in 4BA	847	£0.25
1in 2BA	842	£0.65	1in 6BA	848	£0.40
1in 2BA	843	£0.45	1in 6BA	849	£0.21
1in 2BA	844	£0.52	1in 6BA	850	£0.25
1in 4BA	845	£0.44			

**BA NUTS** - packs of cadmium plated full nuts in multiples of 50.

Type	No.	Price	Type	No.	Price
OBA	855	£0.72	4BA	857	£0.30
2BA	856	£0.48	6BA	858	£0.24

**BA WASHERS** - flat cadmium plated plain stamped washers supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
OBA	859	£0.14	4BA	861	£0.12
2BA	860	£0.12	6BA	862	£0.12

**SOLDER TAGS** - hot tinned supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
OBA	851	£0.40	4BA	853	£0.22
2BA	852	£0.28	6BA	854	£0.22

## SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0.11*
DPDT standard slide	1974	£0.14*
Toggle switch SPST		
1 amp 250V a.c.	1975	£0.33*
Toggle switch DPDT		
1 amp 250V a.c.	1976	£0.42*
Rotary on-off mains switch	1977	£0.50*
Push switch - Push to make	1978	£0.13*
Push switch - Push to break	1979	£0.18*

ROCKER SWITCH	Colour	No.	Price
A range of rocker switches SPST - moulded in high insulation.	RED	1980	£0.30*
	BLACK	1981	£0.30*
	WHITE	1982	£0.30*
Material available in a choice of colours ideal for small apparatus.	BLUE	1983	£0.30*
	YELLOW	1984	£0.30*
	LUMINOUS	1986	£0.30*

Description	No.	Price
Miniature SPST toggle, 2 amp 250V a.c.	1958	£0.50*
Miniature SPST toggle, 2 amp 250V a.c.	1959	£0.55*
Miniature DPDT toggle, 2 amp 250V a.c.	1960	£0.70*
Miniature DPDT toggle, centre off, 2 amp 250V a.c.	1961	£0.85*
Push button SPST, 2 amp 250V a.c.	1962	£0.78*
Push button SPST, 2 amp 250V a.c.	1963	£0.83*
Push button DPDT, 2 amp 250V a.c.	1964	£0.98*

**MIDGET WAFER SWITCHES**  
Single-bank wafer type - suitable for switching at 250V a.c. 100mA or 150V d.c. in non-reactive loads make before-break contacts. These switches have a spindle 0.25in dia. and 30° indexing.

Description	Order No.	Price
1 pole 12 way	1965	£0.48*
2 pole 6 way	1966	£0.48*
3 pole 4 way	1967	£0.48*
4 pole 3 way	1968	£0.48*

MICRO SWITCHES	Order No.	Price
Plastic button gives simple on-off action		
Rating 10 amp 250V a.c.	1969	£0.20
Button gives 1 pole change over action		
Rating 10 amp 250V a.c.	1970	£0.25

## FUSE HOLDERS AND FUSES

Description	Order No.	Price
20mm x 5mm chassis mounting	506	£0.07*
1 1/2 in x 1/2 in chassis mounting	507	£0.12*
1 in car inline type	508	£0.15*
Panel mounting 20mm	509	£0.20*
Panel mounting 1 1/2 in	510	£0.30*

QUICK BLOW 20mm					
Type	No.	Type	No.	Type	No.
150mA	611	1A	615	5p	3A
250mA	612	1.5A	616	6p	4A
550mA	613	2A	617	6p	5A
800mA	614	2.5A	618	6p	6A

ANTI-SURGE 20mm					
Type	No.	Type	No.	Type	No.
100mA	622	1A	625	2.5A	628
250mA	623	2A	626	3.15A	629
500mA	624	1.6A	627	5A	630

QUICK BLOW 1 1/2 in					
Type	No.	Type	No.	Type	No.
250mA	631	500mA	632	800mA	634

All 7p each

## CASES AND BOXES

INSTRUMENT CASES. In two sections vinyl covered top and sides, aluminium bottom, front and back.					
No.	Length	Width	Height	Price	
155	8in	5 1/2 in	2 1/2 in	£1.25*	
156	11in	6in	3in	£2.12*	
157	6in	4 1/2 in	1 1/2 in	£1.30*	
158	9in	5 1/2 in	2 1/2 in	£1.76*	

**ALUMINIUM BOXES.** Made from bright anodized aluminium. Each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2 in	2 1/2 in	1 1/2 in	62p*
160	4in	4in	1 1/2 in	62p*
161	4in	2 1/2 in	1 1/2 in	62p*
162	5 1/2 in	4in	1 1/2 in	70p*
163	4in	2 1/2 in	2in	64p*
164	3in	2in	1in	44p*
165	7in	5in	2 1/2 in	£1.04*
166	6in	6in	3in	£1.32*
167	6in	4in	2in	86p*

## MIDGET WAFER SWITCHES

1965	1 pole 12 way	48p*
1966	2 pole 6 way	48p*
1967	3 pole 4 way	48p*
1968	4 pole 3 way	48p*

## TRANSFORMERS

MINIATURE MAINS Primary 240V			
No.	Secondary		Price
2021	6V-0-6V	100mA	90p*
2022	9V-0-9V	100mA	90p*
2023	12V-0-12V	100mA	95p*

MINIATURE MAINS Primary 240V with two independent secondary windings			
No.	Type		Price
2024	MT280-0-6V, 0-6V RMS		£1.50*
2025	MT150-0-12V, 0-12V RMS		£1.50*

1 AMP MAINS Primary 240V			
No.	Secondary	Price	
2026	6V-0-6V	1 amp	£2.50*
2027	9V-0-9V	1 amp	£2.00*
2028	12V-0-12V	1 amp	£2.60*
2029	15V-0-15V	1 amp	£2.75*
2030	30V-0-30V	1 amp	£3.45*

**STANDARD MAINS Primary 240V**  
Multi-tapped secondary mains transformers available in 1 amp, 1 amp and 2 amp current rating. Secondary taps are 0-19-25-33-40-50V.

Voltages available by use of taps: 4, 7, 8, 10, 14, 15, 17, 19, 25, 31, 33, 40, 25, 0-25V.			
No.	Rating	Price	
2031	1 amp	£5.50*	P. & P. 86p
2032	1 amp	£6.60*	P. & P. 86p
2033	2 amp	£8.40*	P. & P. £1.10

## AUDIO LEADS

107	FM Indoor Ribbon Aerial	£0.60*
113	3.5mm Jack plug to 3.5mm jack plug. Length 1.5m	£0.75*
114	5 pin DIN plug to 3.5mm. Jack connected to pins 3&5. Length 1.5m	£0.85*
115	5 pin DIN plug to 3.5mm. Jack connected to pins 1&4. Length 1.5m	£0.85*
116	Car aerial extension. Screened insulated lead. Fitted plug & skt.	£1.10*
117	AC mains connecting lead for cassette recorders & radios. 2 metres	£0.68*
118	5 pin DIN phono plug to stereo headphone jack socket	£1.05*
119	2 x 2 pin DIN plugs to stereo jack socket with attenuation network for stereo headphones. Length 0.2m	£0.90*
120	Car stereo connector. Variable geometry plug to fit most car cassette, 8 track cartridge & combination units. Supplied with inline fused power lead and instructions.	£0.60*
123	6.6m Coiled Guitar Lead Mono Jack Plug to Mono Jack Plug BLACK	£1.50*
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	£0.75*
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	£0.75*
126	5 pin DIN plug to Tinned open end. Length 1.5m	£0.75*
127	5 pin DIN plug to 4 Phono Plugs. All colour coded. Length 1.5m	£1.30*
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	£0.80*
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	£1.05*
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	£0.68*
131	5 pin DIN plug to 3 pin DIN plug, 1 & 4 and 3&5. Length 1.5m	£0.83*
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	£0.98*
133	5 pin DIN plug to 2 phono plugs. Connected pins 3&5. Length 1.5m	£0.75*
134	5 pin DIN plug to 2 phono sockets. Connected pins 3&5. Length 23cm	£0.68*
135	5 pin DIN socket to 2 phono plugs. Connected pins 3&5. Length 23cm	£0.68*
136	Coiled stereo headphone extension lead. Black. Length 6m	£1.75*
178	AC mains lead for calculators etc.	£0.45*

## AVDEL BOND

### CYANOACRYLATE G2

The wonder adhesive which works in seconds. Bonds plastic, rubber, transistors, components, permanently - immediately!  
O/D143. ONLY 70p\* for a 2gm phial.

## BI-PAK CATALOGUE

### NEW EDITION NOW AVAILABLE

Send for your copy of our revised catalogue and price list NOW! It contains 127 pages packed with literally hundreds of semiconductor, components and our famous range of BI-KITS audio modules.

ONLY 65p POST FREE

**ORDERING** Do not forget to state order number and your name and address.

V.A.T. Add 12 1/2% to prices marked\*. 8% to those unmarked. Items marked are zero rated.

P & P. 35p unless otherwise shown.

# BI-PAK

DEPT. PE7, P.O. Box 6, Ware, Herts

COMPONENTS SHOP: 18 BALDOCK

STREET, WARE, HERTS.

# High quality audio modules for Stereo and mono

## S450

**STEREO FM TUNER**  
Fitted with phase lock-loop  
**£22.30**  
+ 40p p&p  
+ 12½% VAT




FREQUENCY RANGE	88-108 Mhz
SENSITIVITY	3.0 µV
BANDWIDTH	250 kHz
SPURIOUS REJECTION	50 dB
SELECTIVITY ± 400 kHz	55 dB
AUDIO OUTPUT (22.5 kHz deviation)	100 mV
STEREO SEPARATION	30 dB
SUPPLY REQUIREMENTS	20 to 30V (90mA max)
AERIAL IMPEDANCE	75 ohms
DIMENSIONS	240mm x 110mm x 32mm

The 450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, simply by changing the settings of the pre-set controls. Features include FET Input stage. Vari-Cap diode tuning. Switched AFC LED Stereo Indicator.
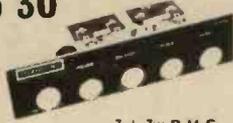
## Stereo 30

**COMPLETE AUDIO CHASSIS**  
**£18.95**  
+ 40p p&p  
+ 12½% VAT




7 + 7w R.M.S.

OUTPUT POWER	7 Watts RMS
LOAD IMPEDANCE	8 ohms
TOTAL HARMONIC DISTORTION	Less than .5% (Typically .3%)
FREQUENCY RESPONSE	50 Hz to 20 kHz ± 3dBs
TONE CONTROL RANGE	± 12 dBs at 100Hz and 10kHz
SENSITIVITY	190 mV for full output
INPUT IMPEDANCE	1 M ohms
TRANSFORMER REQUIREMENTS	22 V. A.C. rated at 1A
DIMENSIONS (Less controls and panel)	200mm x 130mm x 33mm

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel, knobs, main switch, fuse and fuse holder and universal mounting brackets.
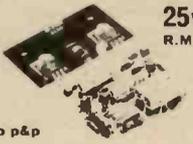
## AL60

**AUDIO AMPLIFIER MODULE**  
25 Watts RMS  
**£4.55** + 25p p&p  
+ 12½% VAT



25w R.M.S.

OUTPUT POWER	25 Watts RMS
SUPPLY	30-50 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz x 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

This high quality audio amplifier module is for use in audio equipment and stereo amplifiers and provides output powers up to 25 RMS with distortion levels below 0.1%.

## AL80

**AUDIO AMPLIFIER MODULE**  
**£7.15\*** + 25p p&p  
+ 8% VAT



35w R.M.S.

OUTPUT POWER	35 Watts RMS
SUPPLY	40-60 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz x 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

The AL80 is similar in design to the AL60 above and is of the same high quality but provides output powers up to 35W with distortion levels below 0.1%.

## AL250

**POWER AMPLIFIER**



125w R.M.S.

OUTPUT POWER	125 Watts RMS continuous
OPERATING VOLTAGE	50-80 V
LOADS	4-16 ohms
FREQUENCY RESPONSE	25 Hz 20 kHz measured at 100 Watts
SENSITIVITY FOR 100 WATTS O/P AT 1 kHz	450 mV
INPUT IMPEDANCE	33 K ohms
TOTAL HARMONIC DISTORTION	
50 WATTS into 4 ohms	0-1%
50 WATTS into 8 ohms	0-06%

**£17.25\*** + 40p p&p + 8% VAT

This unit, designated AL250, is a power amplifier providing an output of up to 125W RMS, into a 4 ohm load.

## AL30A

**AUDIO AMPLIFIER MODULES**



10w R.M.S.

MAXIMUM SUPPLY VOLTAGE	30 V
POWER OUTPUT for 2% THD	10 Watts RMS
TOTAL HARMONIC DISTORTION	Less than .25%
LOAD IMPEDANCE	8-16 ohms
INPUT IMPEDANCE	100 K ohms
FREQUENCY RESPONSE	50 Hz-25 kHz ± 3 dBs
SENSITIVITY	75 mV for full output
DIMENSIONS	74mm x 63mm x 28mm

**£3.75** + 25p p&p  
+ 12½% VAT

These low cost 5 and 10 watt modules offer the utmost in reliability and performance, whilst being compact in size.

## SPM80

**STABILISED POWER SUPPLY**  
**£4.25** + 25p p&p  
+ 12½% VAT



INPUT A.C. VOLTAGE	33-40V
OUTPUT D.C. VOLTAGE	33 V nominal
OUTPUT CURRENT	10 mA-1.5 amps
OVERLOAD CURRENT	1.7 amps approx.
DIMENSIONS	105mm x 63mm x 30mm

Designed to power two AL60s at 15 Watts per channel simultaneously. Circuit Techniques include full short circuit protection.

## PA100

**STEREO PRE-AMPLIFIER**



FREQUENCY RESPONSE	20 Hz to 20 kHz x 1 dB
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .07%)
SENSITIVITY	1. TAPE 100 mV/100 K ohms } For an
INPUTS	2. RADIO TUNER 100 mV/100 K ohms } output
	3. MAGNETIC P.U. 3.5 mV/50 K ohms } 250 mV
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
BASS CONTROL RANGE	± 15 dBs at 75 Hz
TREBLE CONTROL RANGE	+ 10-20 dBs at 15 kHz
SIGNAL/NOISE RATIO	Better than 65 dBs (All inputs)
INPUT OVERLOAD	Better than 26 dBs (All inputs)
SUPPLY	20 to 40 V
DIMENSIONS	300 x 90 x 33mm (less controls)

**£15.80**

+ 40p p&p  
+ 12½% VAT

A top quality stereo pre-amplifier and tone control unit, the PA100 provides a comprehensive solution to the front end requirements of stereo amplifiers or audio units. The six push button selector switch gives a choice of inputs together with two filters for high and low frequencies.

## MPA30

**MAGNETIC CARTRIDGE PRE-AMPLIFIER**



**£2.95**  
+ 25p p&p  
+ 12½% VAT

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the MPA 30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only.

SENSITIVITY	3.5 mV for 100 mV output
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
INPUT IMPEDANCE	50 K ohms
SUPPLY	18 to 30 V—re earth
DIMENSIONS	110 x 50 x 25mm (inc DIN socket)

## PA12

**STEREO PRE-AMPLIFIER**



**£7.10**  
+ 30p p&p  
+ 12½% VAT

The PA12 Stereo Pre-Amplifier chassis is designed and recommended for use with the AL 20/30 Audio Amplifier Modules, the PS12 power supply and the T538 Transformer. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

FREQUENCY RESPONSE	20 Hz-20 kHz (-3dB)
BASS CONTROL	± 12 dB at 60 Hz
TREBLE CONTROL	± 14 dB at 10 kHz
INPUT IMPEDANCE	1 Meg. ohm
INPUT SENSITIVITY	300 mV
CROSSTALK	-60 dB
SIGNAL/NOISE RATIO	-65 dB
OVERLOAD FACTOR	± 20 dB
TAPE OUTPUT IMPEDANCE	25 K ohms
DIMENSIONS	152mm x 84mm x 25mm

## PS12 POWER SUPPLY

Designed for use with the AL30A S.450 and MPA30 in conjunction with transformer T538.

INPUT VOLTAGE	17-20v AC	<b>£1.30</b> + 25p p&p + 12½% VAT
OUTPUT VOLTAGE	27-30v DC	
OUTPUT CURRENT	800mA	
SIZE	60mm x 43mm x 26mm	

## GE 100 NINE CHANNEL MONO-GRAPHIC EQUALIZER

The GE100 has nine 1 octave adjustments using integrated circuit active filters. Boost and Cut limits are ± 12dB. Max. voltage handling 2 V RMS, T.H.D., 0-05%, input impedance 100K. Output impedance less than 10 K. Frequency response 20 Hz-20 kHz (3dB).

The nine gain controls are centred at 50, 100, 200, 400, 800, 1,500, 3,200, 6,400 and 12,800 Hz. The suggested gain controls are 10 K LIN sliders (not supplied with the module) See Paks S31 and 16192. **£22.00** + 25p p&p + 12½% VAT

SG30 POWER SUPPLY BOARD for GE100 15-0-15 VOLT £5.50 + 12½% VAT + 25p p&p

## SIREN ALARM MODULE

American Police siren powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer breakdown and other security purposes. Order No. S15. No. BP124. **Only £3.50 + 12½% VAT + 25p p&p**

## MA60 HI-FI AMPLIFIER KIT

Build your own top quality amplifier, save yourself pounds. The MA60 kit comprises the following BI-kits modules, 2 x AL60 amps, 1 x PA100 pre-amp, 1 x SPM80 stab. power supply, 1 x BM780 transf. giving 17 watts RMS per channel STEREO. All modules covered by the BI-PAK satisfaction or money back guarantee. Details of the above modules are in this ad. **Price £32.00 + 12½% VAT + 62p p&p.**

## TC60 KIT

A beautifully designed genuine TEAK WOOD veneered cabinet to put the professional touches to your home built amplifier. Full set of parts incl. Front & Back Panels, Knobs, Chassis, Fuses, Sockets, Nuts, etc. Ideal for the MA60. Size: 425mm x 290mm x 95mm. **Price £19.95 + 12½% VAT + 86p p&p**

## TRANSFORMERS

T538 For use with S.450 AL30A MPA30  
Order No. 2036 Price: £3.20 + 55p p&p + 12½% VAT  
T2050 For use with Stereo 30  
Order No. 2050 Price: £3.25 + 55p p&p + 12½% VAT  
BM780 For use with AL60 SPM80  
Order No. 2034 Price: £5.40 + 86p p&p + 12½% VAT  
BM T250 For use with AL250  
Order No. 2035 Price: £6.35 + £1.10 p&p + 12½% VAT

# BI-PAK

DEPT. PE7, P.O. Box 6, Ware, Herts

# SAXON ENTERTAINMENTS LTD

THE PIONEERS OF MODULAR DISCO/P.A. EQUIPMENT  
NOW OFFER PACKAGE DEALS AT INCOMPARABLE PRICES

## CENTAUR STEREO DISCOS

C/W LIGHT SHOW & DISPLAY,  
TWIN SPEAKERS & LEADS

Standard 100W

£225 or Deposit £50.80  
12 Months @ £19.11 or 24 Months @ £10.66

## Super 200W

£275 or Deposit £61.80  
12 Months @ £23.17 or 24 Months @ £12.92

## GXL 200W (with twin 200 watt cabinets)

£349 or Deposit £77.72  
12 Months @ £29.19 or 24 Months @ £16.28

BSR Decks - 17,000 Line Loudspeakers - Rugged Aluminium Trimmed Cabinets - Cue Light And Phones Output - Slave Output - Deck Lights/Motor Starts (GXL)

COMPLETE STEREO  
ROADSHOWS - BUILT IN  
SOUND TO LIGHT/SEQUENCER  
& DISPLAY  
TWO YEAR GUARANTEE

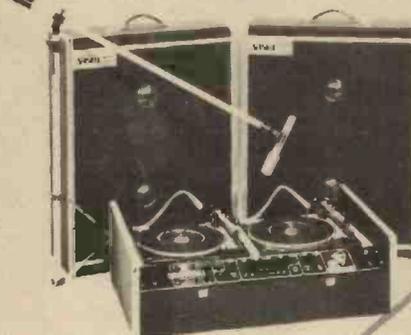


Illustration shows GXL Centaur System

These systems feature full mixing for two decks tape & mic with monitoring facilities - override and ore supplied complete with sound to light sequencer, display, speaker leads etc.

JUST PLUG IN AND GO!

## MINI DISCO 100 WATT MONO SYSTEM

£179.50 Deposit £40.66  
12 Months @ £15.45  
or 24 Months @ £8.61

Similar in appearance to the Centaur and complete with loudspeakers and leads.

Headphones to suit any system £7.50  
EM307 Electret Mic £15.00  
ECM BT Electret Mic £19.95  
Boom Stand £18.50  
Carriage on all disco and PA systems £10.00  
(Included in H.P. Prices)

**20% Deposit Terms  
On All Orders  
Over £150 - 12 or 24  
Months - Low Interest**

### D.I.Y. MODULES FOR ALL DISCO/P.A. AMPLIFIERS

SA308 30W 8 ohms 45V	£9.95*	SUPPLY FOR TWO MODULES	£10.90*
SA604 60W 4 ohms 50V	£13.25	SUPPLY FOR TWO MODULES	£13.50
SA608 60W 8 ohms 65V	£14.25	SUPPLY FOR TWO MODULES	
SA1204 120W 4 ohms 75V	£15.95	SUPPLY FOR ONE MODULE	£22.50
SA1208 120W 8 ohms 95V	£21.00	SUPPLY FOR TWO MODULES	
SA2404 240W 4 ohms 95V	£29.50	SUPPLY FOR ONE MODULE	

0.2% Distortion, 30Hz-20, KHz - 2dB, Fully Short/Open Circuit proof input sensitivity 240 mV to suit most mixers - D.C. & Output Fuses fitted

TOP QUALITY COMPONENTS THROUGHOUT

### DISCO MIXERS - COMPLETE OR MODULAR



MONO OR STEREO WITH AUTOFADE

Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted - full instructions supplied.

MODULES	£22.50
Mono module	£33.50
Stereo module	£3.95
Kit of jacks/sockets etc	£5.50
COMPLETE MIXERS (with case)	
Mono 18V	£39.50
Stereo 18V	£57.50
Mono mains	£45.75
Stereo mains	£63.75


FEATURES INCLUDE:  
Twin Deck - Mic & Tape Inputs - Wide range bass & treble controls - Full headphone monitoring - Crossfade - Professional standard performance

### COMPLETE LIGHTING CONTROL AT YOUR FINGERTIPS!



Lighting Control Unit Mk II	£44.50
4kW Sequencer - Sound light - Dimmers	
- Automatic Level Integrated Logic Circuitry	Module £32.50 Panel £2.95
Three Channel Sound to Light	£26.75
3xW 1-240W input - master	Module £19.75 Panel £2.95
Plus channel controls	

### STROBE UNITS

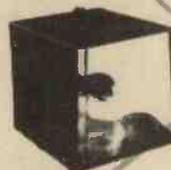

Pro-Strobe 4-6 Joules £37.50  
Super Strobe 2-3 Joules £22.50  
(Pro-Strobe has external trigger facility).

### SPARES & ACCESSORIES - LOUDSPEAKERS & CABINETS

Rope Lights - Red or Multicolour	£22.00	Melos Echo Chamber	£59.00
per 12 ft.		Headphones	£7.50*
Rope Light Controller for up to 120 ft	£30.00	Sirens: English Police, USA Police,	
Fuzz Lights-Red/Blue/Yellow/Green	£22.80	Destroyer, Alien Voice Simulator	£7.50
Magnetic Cartridge Equalisers	£3.50*	Bolgin 8 way lighting plug/socket	£1.90

### PROJECTORS - PLUTO - NEW LOW PRICES!!! CHOICE OF WHEEL/CASSETTE

P150 150W Tungsten	£37.50	Liquid wheels	£7.50
P500 100W Q.I.	£74.95	Cassettes	£8.00
P500 250W Q.I.	£84.95	Picture wheels from	£4.75
		(Wide choice available)	

100 Watt Chassis Loudspeakers 12"	£23.50	18"	£47.50	(Add £1.50 carr.)
Empty Loudspeaker Cabinets, Small 12"	£15.50	Large 12" x 18"	£21.50	Small 2 x 12"
			£22.50	
		1 x 18"	£29.50	

Projector lamps: A1167 £2.90, M6 £5.65.  
100W Spot lamps Red/Blue/Yellow/Green  
£1.50 ea £13.50 for 10  
MD Spot Banks: 3-way 300W £19.50,  
4-way 400W £22.50.  
Bubble machines (optokinetics) £36.50


Strobe tubes 80W £8.50  
ICI Vynide 50" wide £3.50 Metre  
Kickproof Grille 24" wide £3.25 Metre  
Kick Resistant Grille 50" wide £3.25 Metre.  
FULL RANGE OF RE-AN PRODUCTS IN STOCK  
SEND FOR OUR BROCHURE NOW!!

### PIEZO HORNS only £7.50 YES! - only £7.50

(As fitted to our package PA system)

Direct from Motorola Inc., USA at an  
UNBEATABLE PRICE

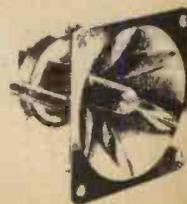No crossover required 4kHz - 30kHz rated  
75W/8 ohms 150W/4 ohms use two per 100W  
amplifier - Full instructions supplied.



**AND**

# PACKAGE P.A. SYSTEMS ( 2 Year Guarantee )

Complete with PIEZO horn columns fitted with 100 watt units (100 watt system illustrated)

**100 Watt £149.50**  
**Deposit £35.26**

12 Months @ £12.91 or 24 Months @ £7.20  
 Includes 4-Channel 100 Watt Amplifier with Treble, Bass and Master Controls plus Lead and Twin Piezo Horn Columns (shown on right).

**200 Watt £225.00**  
**Deposit £50.80**

12 Months @ £19.11 or 24 Months @ £10.66  
 zsix Mixed inputs plus Three Sets of Bass and Treble Controls plus Slave Output and Master Control.



## ACCESSORIES


**Melos Echo Unit £59.00**

A high quality Cassette Tape Echo Unit giving long tape life, infinitely variable echo depth and speed control. Suitable for all mics. and instruments.

High quality Boom Stand £15.50 Floor Stand £9.90. ECM81 Condense Mic. - Removable Lead - Good Anti-Feedback £19.95.\* EM507 Condense Mic. - Good Value £15.00. Phasers £19.80.
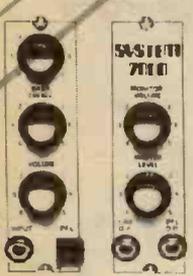
## D.I.Y. MODULES FOR P.A. SYSTEMS Mono or Stereo

Make your own mixer - Mono/Stereo - up to 20 channels with these, easy to wire modules - Available as PCB's or assembled on panels.



Input Stages Up to 20	Mono PCB	£5.95	Mono C/W panel etc.	£8.95
	Stereo PCB	£9.50	Stereo C/W panel etc.	£12.50
Mixer/Monitor (One only per system)	Mono PCB	£5.95	Mono C/W panel etc.	£8.95
	Stereo PCB	£9.50	Stereo C/W panel etc.	£12.50
Power supply for up to 20 channels		£9.50	Blank panel	£1.00


Send for free brochure for complete specification

## Saxon AP100 Amplifier £45

Four mixing inputs - 100W into 4 ohms Wide range bass & treble controls + master - Twin outputs
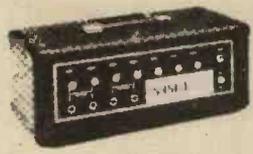
## Saxon 150 Amplifier £59

Four mixing inputs - 100W into 8 ohms 150W into 4 ohms - wide range bass & treble controls + master



All prices subject to 8% VAT except where asterisked (12½%)  
 Shop premises open Mon to Sat 9 am - 5 pm Lunch 12.30 - 1.30 pm  
 Mail order dept open Mon to Fri 10 am - 4 pm - Ring 01-684 6385

## TO ORDER

By Post Send your requirements with cheque crossed P.O. or 60p COD charge to address below or just send your Access or Barclay Card Number NOT THE CARD.

By Phone You may order COD, Access or Barclay Card.  
 Post & Packing 50p on all orders except where stated.

**SAXON ENTERTAINMENTS LTD.**  
 327 Whitehorse Road, Croydon, Surrey.  
 All Enquiries Large SAE Please Brochures on request.

SEMICONDUCTORS. ALL FULL SPEC., BC212, BC182, BC237, BF197, BC159 all 8p each. LM380 80p. LM381 95p. NE655 33p. 741 8 pin 23p. 741S (wide bandwidth) 8 pin 35p. TIL305 Alpha numerical display (with data) £2.50. BX504 opto isolators infra red led to photo cell, lead 25p. BFY50 plastic 14p. STC 3 volt 1 watt zener diodes 7p each. OC45 14p. MFD3051 photo transistors 35p. FETS similar to 2N3819 18p. MOSFET similar 40673 35p. SL301 dual matched pair sil npn transistors fl. 300mhz 30p. Intel C1103 1024 bit mos rams 95p. TBA800 80p. CD4051 45p. 723 14 pin I.C.'s 35p.

DIODES, BY127 9p. IN4002 4p. IN4005 7p. 600V 3 amp 17p. Lucas bridge recs. 400V 1.5 amp 30p.

MAN 3A 3mm led displays 50p. Min. Nixie 5870ST 75p. Pot core unit, has six pot cores including one FX2243 (45mm) and two FX2242 (35mm) 3 TO3 sil. power transistors on heat sink. 3 20mm panel fuseholders and panel with various transistors. diodes and a 5 amp plastic SCR. £1.75 plus 75p postage.

MOTORS, Model type 1.5-6 volts 20p. 'BIG INCH' sub min motor 115V AC. 3 rpm 25p. 240V AC SYNCH., MOTORS WITH GEARBOX. ¼ rpm 75p. ½th rpm 75p. 15 rpm £1.20. Crouzet 115V AC 4 rpm 95p.

HI-SPEED MORSE KEY, ALL METAL £2.25.

HI-IMP MONO HEADPHONES 2K IMP £1.95. Crystal microphone inserts 37mm 45p. Grundig electret condenser inserts with built in FET pre-amp £1.50. ELECTRET PENCIL HAND MICROPHONES 1K IMP WITH STANDARD JACK PLUG £2.85. TIE CLIP CONDENSER MIKES OMNI, 1K IMP fuses deaf aid battery, supplied £4.95.

SOLDER SUCKER, High suction, eye protection shield £4.95.

PROJECT BOXES, BLACK ABS PLASTIC WITH BRASS INSERTS AND LID. 75 x 56 x 35mm 44p. 95 x 71 x 35mm 52p. 115 x 95 x 36 60p.

BUZZERS, GPO open type 3-6V 30p. Large plastic domed type loud note 6 or 12 volts 50p. Solid State buzzers, miniature, 6-9-12-24 volt 15ma 75p each.

TAPE HEADS, Mono Cassette £1.30. Stereo cassette £3.00. BSR MNI330 half track dual imp. heads 50p. BSR SRP90 ¼ track R/P Heads £1.95. 8 track heads £1.75. TD10 Dual head assemblies 2 heads both ¼ track R/P with built in erase, mounted on bracket. £1.20. Relays, Min. sealed 12V DC type 4 pole changeover 55p. Min 24V DC 2 pole c/o 3 amp contacts 55p. Min sealed 220V AC 2 pole c/o 40p. Open type 12V DC 4 pole c/o 50p. 4 pole reed relays r/o 20p.

CRYSTALS, 300KHz 40p. 4.43MHz CTV 45p.

AEROSOL Touch up paint one colour yellow/grey, 6oz can 35p. 50V AC cam units, motor switching ten c/o micro switches, supplied with capacitor for 240V AC use £1.95 plus 35p postage. Belling Lee L4305 masthead amplifiers and mains power unit, new but only for group A UHF £7.50.

TRANSFORMERS, 6-0-6V 100ma, 9-0-9 75ma, 12-0-12 50ma 75p each, 12-0-12 100ma 95p. 12V 500ma 95p. 1:1 triac/xenon pulse transformers 30p. CHOKES 6MH 3 amp 20p. U.H.F. TV Tuners, push button (not varicap) new and boxed £2.50. Miniature toggle switches, SPST 8 x 5 x 7mm 45p. DPDT 8 x 7 x 7mm 50p. DPDT c/o 12 x 11 x 9mm 75p. Min. push to make or push to break 16 x 6mm 15p each type. Slider switches, DPDT standard 15p. Min 12p. Std. c/o 20p. Roller action micro switches 15p.


TOOLS, Small side cutters 5" insulated handles £1.35. Snub nosed pliers 5" insulated handles £1.35. Watchmakers screwdriver sets, 5 drivers in wallet £1.00. Large mains tester screwdrivers, fully insulated 8" 44p. Test lead jumper sets, 10 leads with insulated croc clips each end, different colours 80p. Telephone pick up coil, suction type with 3.5mm jack plug 50p. 9 volt battery eliminators, 240V AC input 9V DC out at 120ma stabilised replaces PP3, PP6, PP7, PP9 £2.45. Edge connectors, 0.1 64 way 65p, 34 way 40p, 0.2 18 way 15p. Amplifier modules, OTL410 10 watt mono into 8 ohms 28V DC max £4.65. 555S Stereo module, 3 watt output into 8 ohms, 12V DC £3.35. Tape head demagnetizers, 240V AC with on/off switch, straight probe £2.00. curved probe (cassette) £2.35.

TERMS: Cash with order (or official orders from colleges etc). Postage 30p unless otherwise shown, overseas post at cost. VAT inclusive prices. S.A.E. for lists.

80p/h PROGRESSIVE RADIO 18p  
**31 CHEAPSIDE, LIVERPOOL L2 2DY. TEL. 051-236 0982.**

# Test Equipment

## Multimeters

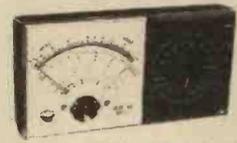

The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.



Please send me details of all your test equipment.

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

Eagle International, Precision Centre, Heather Park Drive, Wembley HA0 1SU Tel: (01)-902 8832



# Eagle

# RST VALVE MAIL ORDER CO.

Climax House  
Fallsbrook Road, London SW16 6ED


**SPECIAL EXPRESS  
MAIL ORDER SERVICE**

Ep	Ep	Ep	Ep	Ep	Ep				
AA119	0-20	BCY71	0-22	*MPSU01	0-32	*ZTX550	0-16	7403	0-20
AA30	0-13	BCY72	0-17	*MPSU06	0-46	1N314	0-07	7404	0-26
AA32	0-15	BCZ11	1-50	*MPSU56	0-45	1N315	0-07	7405	0-26
AA36	0-23	BD115	0-60	NKT401	2-00	1N4001	0-06	7406	0-55
AAZ15	0-31	BD121	1-50	NKT403	1-73	1N4002	0-07	7407	0-55
AAZ17	0-25	BD123	1-50	NKT404	1-73	1N4003	0-08	7408	0-28
AC107	0-75	BD124	1-30	NE555	0-45	1N4004	0-09	7409	0-28
AC125	0-30	BD131	0-81	OA5	0-75	1N4005	0-13	7410	0-20
AC126	0-25	BD132	0-84	OA7	0-55	1N4006	0-15	7412	0-26
AC127	0-25	*BD135	0-35	OA10	0-55	1N4007	0-15	7413	0-45
AC128	0-25	*BD136	0-36	OA47	0-14	1N4009	0-15	7416	0-40
AC141	0-20	*BD137	0-37	OA70	0-30	1N4148	0-07	7417	0-40
AC141K	0-35	*BD138	0-40	OA79	0-30	1N5400	0-14	7420	0-20
AC142	0-20	*BD139	0-43	OA81	0-30	1N5401	0-16	7422	0-25
AC124K	0-30	*BD140	0-40	OA85	0-30	1S44	0-08	7423	0-35
AC176	0-25	BD144	2-00	OA90	0-04	1S920	0-08	7425	0-35
AC187	0-25	BD181	1-38	OA91	0-04	1S921	0-08	7427	0-35
AC188	0-25	BD182	1-44	OA95	0-04	2G301	1-00	7428	0-50
AC17	0-65	BD237	0-80	OA200	0-10	2G302	1-00	7430	0-20
AC18	0-65	BD238	0-85	OA202	0-11	2G306	1-10	7432	0-36
AC19	0-65	BDX10	0-75	OA210	0-10	2N404	0-08	7433	0-37
AC19	0-65	BDX32	2-25	OA211	0-75	2N695	0-25	7439	0-42
AC21	0-85	BDY20	1-42	OA220	0-65	2N697	0-16	7438	0-37
AC29	1-25	BDY60	0-75	OA221	0-65	2N698	0-30	7440	0-22
AD149	0-70	BF115	0-39	OA206	0-65	2N705	0-80	7441AN	0-82
AD161	0-75	BF152	0-25	OA207	0-65	2N706	0-12	7442	0-78
AD162	0-75	BF153	0-25	OC16	1-25	2N708	0-21	7447AN	1-20
AF106	0-45	*BF154	0-25	OC20	2-00	2N830	0-26	7450	0-20
AF114	0-25	BF159	0-35	OC22	2-50	2N1131	0-26	7451	0-20
AF115	0-25	BF160	0-30	OC23	2-75	2N1132	0-26	7453	0-20
AF116	0-25	BF167	0-39	OC24	3-50	2N1302	0-37	7454	0-20
AF117	0-25	BF173	0-39	OC25	0-90	2N1303	0-37	7460	0-20
AF139	0-40	BF177	0-45	OC26	0-90	2N1304	0-45	7470	0-35
AF186	1-15	*BF178	0-45	OC28	1-50	2N1305	0-45	7472	0-60
AF239	0-45	BF179	0-45	OC29	2-00	2N1306	0-50	7473	0-38
AFZ11	2-75	BF180	0-45	OC35	1-50	2N1307	0-50	7474	0-40
AFZ12	2-75	BF181	0-45	OC36	1-50	2N1308	0-60	7475	0-59
AS26	0-45	BF182	0-45	OC41	0-50	2N1309	0-60	7476	0-42
AS27	0-50	BF183	0-45	OC42	0-50	2N1613	0-33	7480	0-60
ASZ15	1-25	*BF184	0-38	OC43	0-50	2N1611	1-50	7482	0-85
ASZ16	1-25	BF185	0-37	OC44	0-50	2N1693	0-33	7483	1-00
ASZ17	1-25	*BF194	0-12	OC45	0-50	2N2147	1-40	7484	1-00
ASZ20	0-75	*BF195	0-11	OC71	0-45	2N2148	1-65	7486	0-40
ASZ21	1-50	*BF196	0-13	OC72	0-45	2N2218	0-33	7490	0-52
AU113	1-70	*BF197	0-14	OC73	1-00	2N2219	0-42	7491AN	0-85
AU110	1-70	BF200	0-32	OC74	0-75	2N2220	0-35	7492	0-60
BA145	0-15	*BF224	0-20	OC75	0-60	2N2221	0-22	7493	0-70
BA148	0-15	*BF244	0-35	OC76	0-50	2N2222	0-25	7494	0-80
BA154	0-10	BF257	0-37	OC77	1-20	2N2223	2-75	7495	0-80
BA155	0-12	BF258	0-42	OC81	0-75	2N2368	0-17	7496	0-90
BA156	0-13	BF259	0-45	*OC82	1-00	2N2369A	0-21	7497	3-67
BAW62	0-05	*BF326	0-50	OC82	0-75	2N2484	0-21	7499	1-75
BAX13	0-07	*BF337	0-53	OC83	0-55	2N2646	0-50	7499	0-45
BAX16	0-07	*BF338	0-55	OC84	0-60	2N2904	0-35	7499	0-86
BC107	0-12	BFS21	2-27	OC122	1-50	2N2905	0-35	7499	0-57
BC108	0-12	BFS28	1-38	OC123	1-55	2N2906	0-25	7499	0-86
BC109	0-13	*BFS61	0-25	OC139	2-25	2N2907	0-21	7499	1-69
*BC113	0-15	*BFS98	0-25	OC140	1-50	*2N2924	0-15	7499	0-95
*BC115	0-19	BFW10	0-90	OC141	2-25	*2N2925	0-17	7499	2-00
*BC116	0-19	BFW11	0-90	OC170	0-75	*2N2926	0-13	7499	1-10
*BC117	0-22	BFX84	0-38	OC171	0-75	2N3053	0-25	7499	0-45
*BC118	0-22	BFX85	0-41	OC200	1-00	2N3054	0-50	7499	0-80
*BC125	0-18	BFX87	0-35	OC201	1-50	2N3055	0-65	7499	1-00
*BC126	0-18	BFX88	0-32	OC202	1-25	2N3440	0-60	7499	0-80
*BC135	0-15	BFY50	0-28	OC203	1-75	2N3441	0-80	7499	0-80
*BC136	0-19	BFY51	0-26	OC204	1-25	2N3442	1-20	7499	0-80
*BC137	0-16	BFY52	0-26	OC205	1-75	2N3525	0-90	7499	0-80
*BC138	0-16	BFY64	0-30	OC206	1-75	2N3614	1-20	7499	0-68
*BC147	0-10	BFY90	1-32	OC207	1-25	*2N3702	0-15	7499	0-85
*BC148	0-10	BSX19	0-34	OC207	1-25	*2N3703	0-15	7499	3-00
*BC149	0-11	BSX20	0-34	DRP12	0-83	*2N3704	0-15	7499	3-00
*BC157	0-12	BSX21	0-32	*R2008B	2-25	*2N3705	0-15	7499	3-00
*BC158	0-11	BT106	1-25	*R2009	2-25	*2N3706	0-14	7499	1-00
*BC159	0-13	BTY79/400R	3-19	*R2010B	2-25	*2N3707	0-18	7499	2-45
*BC167	0-13	*BU205	2-25	T1C44	0-36	*2N3708	0-14	7499	2-00
*BC170	0-16	*BU206	2-25	T1C26D	1-30	*2N3709	0-15	7499	1-75
*BC171	0-16	*BU208	2-50	*T1P209	0-25	*2N3710	0-14	7499	1-00
*BC172	0-13	BY100	0-40	*T1P29A	0-50	*2N3711	0-15	7499	2-00
*BC173	0-15	BY126	0-14	*T1P30A	0-60	2N3711	1-60	7499	0-90
BC177	0-19	BY127	0-15	T1P31A	0-62	2N3712	1-70	7499	0-90
BC178	0-18	BZXB1	0-20	T1P32A	0-75	2N3713	2-85	7499	0-90
BC179	0-20	Series		T1P33A	1-00	*2N3818	0-36	7499	2-50
*BC182	0-11	BZY88	0-13	T1P34A	1-20	*2N3820	0-46	7499	2-60
*BC183	0-11	Series		T1P41A	0-70	*2N3823	0-60	7499	5-00
*BC184	0-12	CRS10/5	0-45	T1P42A	0-90	2N3866	1-00	7499	1-75
*BC212	0-14	CRS1/40	0-60	T1P2955	1-00	*2N3904	0-21	7499	1-57
*BC213	0-14	CRS3/05	0-45	T1P3055	0-50	*2N3905	0-22	7499	1-00
*BC214	0-17	CRS3/40	0-75	*T1S49	0-35	*2N3906	0-22	7499	1-10
*BC237	0-17	CRS3/60	0-90	*ZS140	0-25	*2N4058	0-20	7499	1-65
*BC238	0-12	GEX66	1-50	*ZS170	0-12	*2N4059	0-15	7499	1-65
BC301	0-45	GEX541	1-75	*ZS178	0-54	*2N4060	0-20	7499	1-85
BC303	0-60	GJM	0-75	*ZS271	0-22	*2N4061	0-17	7499	1-48
*BC307	0-20	GJM	0-75	*ZS278	0-58	*2N4062	0-18	7499	1-48
*BC308	0-22	GMO378A	1-50	*ZTX107	0-11	*2N4124	0-17	7499	1-25
*BC327	0-22	*KS100A	0-40	*ZTX108	0-10	*2N4126	0-17	7499	1-25
*BC328	0-18	MJE340	0-58	*ZTX109	0-12	*2N4286	0-20	7499	1-10
*BC337	0-18	MJE370	0-65	*ZTX300	0-12	*2N4288	0-25	7499	1-10
*BC338	0-18	MJE371	0-81	*ZTX301	0-13	*2N4289	0-25	7499	1-20
BCY30	1-00	MJE520	0-65	*ZTX302	0-17	*2N5437	0-35	7499	1-00
BCY31	1-00	MJE521	0-75	*ZTX303	0-17	*2N5458	0-35	7499	2-25
BCY32	1-00	MJE2955	1-25	*ZTX304	0-19	*2N5459	0-35	7499	2-25
BCY33	0-90	MJE3055	0-75	*ZTX311	0-12	3N125	1-75	*76013N	1-75
BCY34	0-90	*MPP102	0-30	*ZTX314	0-20				
BCY36	0-30	*MPP103	0-30	*ZTX500	0-13				
BCY40	1-25	*MPP104	0-30	*ZTX501	0-14	INTEGRATED			
BCY42	0-30	*MPP105	0-30	*ZTX502	0-16	CIRCUITS			
BCY43	0-32	*MPSA06	0-25	*ZTX503	0-17	7400	0-20	8 pin DIL	0-15
BCY58	0-23	*MPSA56	0-25	*ZTX504	0-20	7401	0-20	14 pin DIL	0-15
BCY70	0-18			*ZTX531	0-20	7402	0-20	16 pin DIL	0-17

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.  
Valves, Tubes and Transistors · Closed Saturday  
Terms C.W.O. only · Tel. 01-677 2424-7  
Quotations for any types not listed S.A.E.  
Post and Packing 25p per order + 8% V.A.T.  
Items marked \* 12½%

Prices correct  
when going  
to press

Announcing:

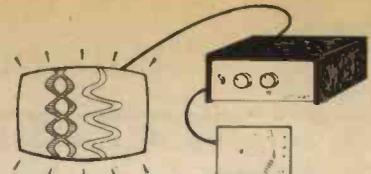

## THE VIDEOGRAPH®

by Stuart

**THE AUDIO-VISUAL MIRACLE**  
This all-British invention now leads the way in audio-visual entertainment!  
**SOUND WAVES IN COLOUR**  
At last you can actually see your records and tapes displayed as beautiful sound waves on any domestic television set... black and white or colour.

**STEREO OR MONO**  
Two inputs are provided, allowing direct display of stereo sound as independent left and right hand channels. Alternatively a mono signal may be used to feed, for example, low frequencies to one channel and high frequencies to the other.

**CHANGING BACKGROUND COLOURS**  
When used with a colour television the waves are orange and blue, while the background performs an eight stage colour cycle, triggered by peak audio signals.

**EASILY CONNECTED**  
The Videograph connects directly to your television's aerial socket, and accepts inputs from almost any tape-recorder, gramophone, radio, organ or synthesiser.

**BUILD ONE YOURSELF AND SAVE MONEY**  
The Videograph is available as a straightforward construction kit which can be assembled in a couple of hours using only simple tools.

Price: Videograph Generator Kit £12.00  
UHF Colour Modulator Kit £6.95  
TOTAL £18.95  
Cabinet and Controls, if required £6.95

**COLOUR MODULATOR FOR ALL T.V. GAMES £6.95**  
The only design to offer 3 separate inputs RG and B. Easily interfaced to any game with dramatic explosion for the TANK BATTLE.

READY-BUILT UNITS are available £39.95. Prices include VAT etc.

**STUART-BRUGES, 137 Billericay Road, Herongate, Brentwood, Essex. Telephone 0277-810244**  
cheques/P.O.s payable to J. M. Stuart-Bruges

4 1/2 x 3 1/2 INCH METER. 30µA, 50µA or 100µA, £5.43. 19p P. & P.

**MICROPHONES FOR TAPE RECORDERS**  
DM228R 200 ohm with 3-5 and 2-5mm Jack Plugs £1-30  
DM229R 50K with 3-5 and 2-5mm Jack Plugs £1-60  
DM18D 200 ohm with 5 and 3 pin Din Plugs £1-75  
Postage on above microphones 11p

**CARDIOID DYNAMIC MICROPHONE**  
Model UD-130 Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £8-02. 26p P. & P.

2in x 2in meters 1mA, 500mA, £3-65. 16p P. & P.

60 x 45mm meters 50µA, 100µA 500µA and 1mA VU meter, £4-46. 11p P. & P.

6V BUZZERS. 50mm diameter 30mm high, 52p. 15p. P. & P.



### EASY BUILD SPEAKER DIY KITS

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak simulate enclosures, two EMI 13" x 8" (approx.) woofers, two tweeters and a pair of matching crossovers. Supplied complete with an easy-to-follow circuit diagram, and crossover components.

**£28.00**

**STEREO PAIR** Input 15 watts rms, 30 watts peak, each unit. + p & p **£5.50** Cabinet size 20" x 11" x 9" (approx.)

#### SPEAKERS AVAILABLE WITHOUT CABINETS.

It's the units which we supply with the enclosures illustrated. Size 13" x 8" (approx.) woofer (EMI), 2 1/2" 300. **£17.00** per tweeter, and matching crossover components. stereo pair Power handling 15 watts rms, 30 watts peak. + p & p **£3.40**

**COMPACT FOR TOP VALUE** These infinite baffle enclosures come to you ready mitred and professionally finished. Each cabinet measures approx. per stereo pair 12" x 9" x 5" deep, and is in wood simulate. **£8.50**

Complete with two 8" (approx.) speakers for maximum power handling of 7 watts 8Ω + p & p **£2.20**

**SPEAKERS** Two models Duo IIb, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/2" (approx.)

Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2" approx

Duo IIb **£17 PER PAIR** Duo III **£52 PER PAIR** p & p **£6.50** p & p **£7.50**

**DECCA 20 WATTS STEREO SPEAKER** stereo pair This matching loudspeaker system is hand made, kit comprises of two 8" diameter approx. base drive unit, with heavy die cast chassis laminated cones with rolled P.V.C. surrounds, two 3 1/2" diameter approx. domed tweeters complete with crossover networks 8Ω **£4.00** p & p **£20.00**



### PORTABLE DISCO CONSOLE

Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. **£64.00** Simply connects into your existing slave or external amplifier. p & p **£6.50**

# Mullard

## AUDIO MODULES IN BARGAIN PACKS CURRENT CATALOGUE


PRICE **£** AT OVER **25** PER PACK

### SEE OUR PRICES

**1** PACK 1, 2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE p+p £1.00 £4.95**

**2** PACK 2, 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2, Stereo pre amp for magnetic, ceramic and auxiliary inputs. **OUR PRICE p+p £1.00 £6.95**

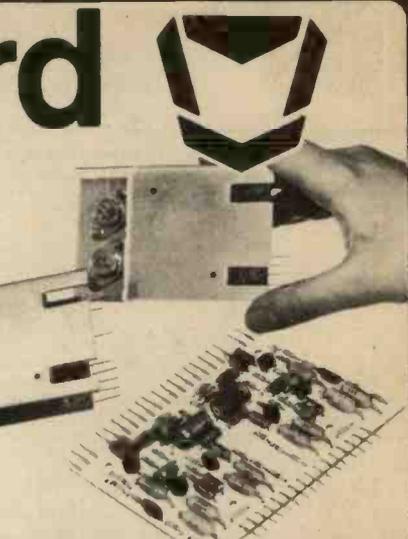**3** PACK 3, 1 x LP1179/2 FM Tuning head with AM gang, 1 x LP1165/1 AM/FM IF module, 2 x LP1173/10w. RMS output power audio amp modules + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE p+p £1.00 £9.95**



### ACCESSORIES

Suitable power supply parts including mains transformer, rectifier, smoothing and output capacitors. **£1.00** p+p **£1.95**

Recommended set of rotary stereo controls comprising BASS, TREBLE, VOLUME and BALANCE. **p+p 50p 95p**



### TRADE ENQUIRIES INVITED



### Tourist IV CAR RADIO KIT

For the experienced constructor only Output 4 watts into 4 ohms. Complete with speaker, baffle and fixing strip, for the experienced constructor only. The Tourist IV has five push buttons, four medium band and one for long wave band. The tuning scale is illuminated and attractive small aluminium control knobs for manual tuning and volume control. 12 volts pos or neg (altered internally). Size approx. 7"x2" 1/4". **£12.50** A MOTOR TOP 10 ACCESSORY WINNER p & p **£1.50** FREE TO PERSONAL SHOPPERS BUYING CAR RADIO KIT worth **£3.00** ELECTROMATE Rear window heater, modern line element.



### 20 x 20 WATT STEREO AMPLIFIER

Superb Viscount IV unit in teak finished cabinet. Silver fascia with aluminium rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary. Rear panel features two mains outlets, DIN speaker and input sockets, plus fuse. 20 + 20 watts rms, 40 + 40 watts peak. **£29.90** 30 x 30 WATT AMPLIFIER KIT For the experienced constructor complete in every detail. Similar facilities as Viscount IV amplifier. p & p **£2.50** 60 + 60 peak. **£39.00** AVAILABLE NOW built and fully tested with output 30 + 30 watts rms, 60 + 60 peak. p & p **£2.50** SPECIAL OFFER: PACKAGE PRICE WITH 30 x 30 KIT MK II version, operates into 4 to 15 OHMS speakers. Designed by R & TVC for the experienced constructor. Complete in every detail, facilities as Viscount IV amplifier 60 + 60 peak. Supplied with 2 Goodmans Compact 12" bass woofer with cropped 14,000 Gauss Magnet, 30 watt, rms. handling + 3 1/2" approx. tweeters and crossovers. **£49.00** p & p **£4.00**



### 45 WATT MONO DISCO AMP

**£35.00** p & p **£2.50** Size approx. 13 1/2" x 5 1/2" x 6 1/2" 45 watts rms, 90 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push pull switches. Independent bass and treble controls and master volume. **£57**



### 70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/2" Brushed aluminium fascia and rotary controls. Five vertical slide controls: master volume, tape level, mc level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control. 70 watt peak (PFL) lets YOU hear next disc before fading. 140 watt peak (1 in. VU meter monitors output level). **£57** Output 100 watts RMS 200 watts peak. 100 watt **£65**

### PERSONAL SHOPPERS

- UNIK electronic digital alarm clock mains operated, large bright LED display tilted display for easy viewing, silent operation. Alarm and 9 minute repeater, PM and sets display size 105mm x 115mm x 50mm approx. **£7.95**
- 16016 VOLT MAINS TRANSFORMER, 2 1/2 amp. **£2.50**
- BSR Record auto deck on plinth with stereo cartridge ready wired. **£11.95**
- LED 5 function men's digital watch stainless steel finish **£5.95**
- LCD 5 function men's digital watch stainless steel finish **£7.95**
- LCD 8 function CHRONOGRAPH men's digital watch stainless steel finish **£13.95**
- STEREO CASSETTE record/replay fully built P.C. board. Used, without guarantee. (Ex Equipment.) **£1.95**
- AM. FM. TUNER P.C.B. with Mullard LP.1186, 1185, 1181 modules. **£9.50**
- 100K Multiturn Varicap tuning pots. 6 for **£1.00**
- MUSIC CENTRE CABINET with hinged smoke acrylic top, finished in natural teak veneers, size 30 1/4" x 14 1/2" x 7 1/4" approx. **£5.95**
- MULLARD Built power supply **£1.50**
- DECCA DC1000 Stereo Cassette P.C.B. complete with switch oscillator coils and tape-heads. **£2.95**
- FERGUSON, 3-speed, 7" HIFI tape transport mechanism, complete with top covers. **£15.95**

### ADD-ON STEREO CASSETTE TAPE DECK KIT

Designed for the experienced D.I.Y. man. This kit comprises of a tape transport mechanism, ready built and tested record/replay electronics with twin V.U. meters and level control for mating with mechanism. Specifications: Sensitivity - Mic. 0.85 mV // 20K OHMS; Din. 40mV // 400K OHMS; Output - 300mV RMS per channel // 1KHz from 2K OHMS source; Cross Talk - -30db; Tape Counter - 3 Digit, Resettable; Frequency Response - 40Hz - 8KHz ± 6db; Deck Motor - 9 Volt DC with electronic speed regulations. Key Functions - Record, Rewind, Fast Forward, Play, Stop & Eject. **£19.95** p & p **£2.50** Opt. extras: Mains transformer to suite **£2.50** + **£1** p & p.



### CHASSIS RECORD PLAYER DECKS

**GARRARD DECK CC10A** **£7.95** Record changer with cue, stereo ceramic cartridge. p & p **£2.00**  
**BSR MP60 TYPE Single** **£15.95** play record deck less cartridge. p & p **£2.55**  
Cartridges to suit above  
Acos, magnetic stereo **£4.95**  
Ceramic stereo **£1.95**  
BSR automatic record player deck cueing device and stereo ceramic head. p & p **£2.55** **£9.95**  
BSR MP 60 type, complete with magnetic cartridge, **£29** diamond stylus, and de luxe plinth and cover. p & p **£4.50**  
Home 8 Track cartridge player. This unit will match with the Viscount IV 9" x 8" x 3 1/2". p & p **£2.50** **£16.50**



323 EDGWARE ROAD, LONDON W2  
21D HIGH STREET, ACTON W3 6NG  
ALL PRICES INCLUDE VAT AT 12 1/2%  
All items subject to availability. Price correct at 1.4.78 and subject to change without notice



### EASY TO BUILD RECORD PLAYER KIT

For the D-I-Y man who requires a stereo unit at a budget price, comprising ready assembled stereo amp, module, Garrard auto/manual deck with cueing device, pre-cut and finished cabinet work. Output 4 watts per channel, phones socket and record/replay socket, including 2 SPHERICAL HIFI speakers **£19.95** p & p **£4.05**

# PE TV GAME CENTRE. 14 GAMES

ALL PARTS AVAILABLE FOR THE 14-GAME PROJECT

PCB and information	£3.50	220 mfd capacitor	each	.10
Colour encoder UM1164E36	£2.50	100 mfd capacitor	each	.10
Sound modulator UM1263	£2.90	All resistors	each	.03
Vision modulator UM1163E36	£2.90	All diodes	each	.03
AY-3-8760 Motorbike chip	£9.90	All capacitors	each	.04
AY-3-8600 10-Game chip	£7.50			
Crystal	.90			
Choke	.45	Extra parts for finishing complete Game		
CD 4013	.90	3.5 m.m. power socket		.12
CD 4081	.45	Pair of joysticks		£3.50
CD 4071	.20	2 metres of 6 core cable		.90
CD 4012	.20	Pushbuttons	each	.15
CD 4089	each .20	Knob		.45
8V2 Zener	.20	Toggle switch	each	.65
BC 182	each .15	Box-set with fascia (printed)		£4.90
BC 337	each .15	Aerial lead		.45
28 pin socket	each .45	Power supply		£3.25
14 pin socket	each .25	Complete kit, no extras needed		£47.50



All prices include VAT. For orders under £10 add 20p p&p. Cheques and postal orders to be made payable to TELEPLAY; send your order (No stamp needed,) to Teleplay, Freepost, Barnet, EN5 2BR. or telephone your order quoting your Barclaycard or Access number



**SHOP OPEN - 10am to 7pm - Monday to Saturday**

CLOSE TO NEW BARNET BR STATION - MOORGATE LINE



TRADE ENQUIRIES WELCOME

**teleplay** (formerly TELECRAFT)

14 Station Road, New Barnet, Herts EN5 1QW Tel: 01-440 7033/01-441 2922

The better catalogue

IT CAN SAVE YOU POUNDS!

Modules - power amps 3 to 100 watts R.M.S., power supplies, control units, etc. - electronic ignition for your car - D.I.Y. disco/P.A. - bargain disco assemblies - plenty to choose from with technical gen, diagrams and good instructions. Send only 20p for postage and handling for your copy by return. You can't be without it!




**Stirling Sound**

Dept. PE7, 37 VANGUARD WAY, SHOE BURYNESS, ESSEX. Phone (03708) 5543  
Shop & Showroom (personal callers only)  
222-224 West Road, Westcliff-on-Sea.  
Phone: Southend (0702) 35-1048.

SEND FOR YOURS NOW

## STORAGE CABINETS

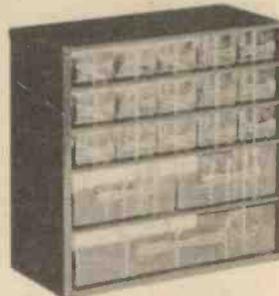

Type 1118

Metal cabinets with transparent plastic drawers. Ideal for components, small parts, nuts, bolts etc. Many other uses in the home, workshop, laboratory etc.

Choose from the following range to suit your own needs:

Type	Height (ins.)	No. of Drawers			Price
		Total	Small	Medium Large	
1118	11	18	15	2 1	£8.65
1130	11	30	30	- -	£8.95
1633	16	33	30	2 1	£10.95
1150	18	50	50	- -	£12.95
1860	22	60	60	- -	£14.95

All cabinets are finished Blue, 12" wide x 5 3/4" deep. Prices include VAT and Post. Satisfaction or money refunded. Cheque/P.O. to:

## MILLHILL SUPPLIES (TOOLS)

35 PRESTON CROWMARSH, BENSON, OXON. OX9 6SL

## TV GAMES

**I**N THIS issue we present what we feel is the best combination of TV games available. The *P.E. TV Game Centre* has 14 different game options and can provide hours of amusement for a single player or for the whole family. When we tested this unit we found that a couple of four-year-olds could play at least one of the games and, in fact, they got very upset when we took the Centre away to work on the article. The Centre has also provided an afternoon's enjoyment for a large family and even "grandad" got quite enthusiastic—well he was unable to watch the football!

We must point out that with colour, sound-through-the-set and all those game options, the unit is quite complex and not one for the beginner to tackle. However, there is much enjoyment to be gained from both building and using the unit. (The main part of the project is in this issue and concludes with construction details next month).

## TV ENGINEERING

A recent lecture by Dr Boris Townsend, head of the IBA's Engineering Information Service, has given rise to

various comments in the technical press about some of his predictions. We have taken the trouble to bring you most of what he said in this issue. We do not feel that the predictions require further comment from us as Dr Townsend is in a much better position to make such predictions than we are, and no doubt most readers will have their own opinions anyway.

To many the review of the present state of the art may be an eye opener but we are sure that to most readers the 1984 and 1989 sections will start some thoughts.

Having made a few predictions in the past and been hounded by them later, we do not intend to start exploring the future of this or other fields. Reference to the editorial of March '78 is recommended for those who would like to try this particular pastime—we will not be drawn into the trap.

Part of Dr Townsend's lecture which, due to space restrictions, we have had to omit said:

"Samuel Butler once said that a hen is merely an egg's way of making another egg. Now, I don't know how many of you would regard that as a valid statement, but I warn you that I

may not say anything which has greater validity—nor indeed shall I say much that is capable of proof, though perhaps some of my remarks may turn out to have been correct.

Neither am I intent on arguing that an engineer is merely a television studio's way of making another television studio—although financial controllers firmly believe that studios do spawn engineers. No, any engineer is far too arrogant to denigrate his importance in the scheme of things. But since I am here not so much as an engineer but as a soothsayer, it behoves me to begin modestly, once I have gently indicated that peering into our future may call for a little lateral thinking."

## TV COMPETITION

It is also interesting to note that the use of the TV set for purposes other than watching broadcasts will probably mean the TV companies have more to compete with than each other. We could be said to be adding to this competition by presenting our Game Centre—not a bad thing perhaps?

Mike Kenward

## EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

Alan Turpin PRODUCTION EDITOR

David Shortland TECH. SUB EDITOR

## ADVERTISEMENT MANAGER

D. W. B. Tilleard

Jack Pountney ART EDITOR

Keith Woodruff SENIOR ARTIST

Isabelle Greenaway TECH. ILLUSTRATOR

Jenny Best SECRETARY

P. J. Mew REPRESENTATIVE

C. R. Brown CLASSIFIED MANAGER

### Editorial Offices:

Westover House,  
West Quay Road, Poole,  
Dorset BH15 1JG  
Phone: Editorial Poole 71191

**We regret that lengthy technical enquiries cannot be answered over the telephone.**

### Advertising Offices:

King's Reach Tower,  
King's Reach, Stamford Street, SE1 9LS  
Phone: Advertisements 01-261 5000  
Telex: 915748 MAGDIV-G

Make Up and Copy Dept.

Phone: 01-261 6601

## Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

## Back Numbers and Binders

Copies of most of our recent issues are available from: Post Sales Department, IPC

Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 65p each including Inland/Overseas p & p.


Binders for PE are available from the same address at £2.85 each to UK addresses, £3.45 overseas, including postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Cheques and postal orders should be

made payable to IPC Magazines Limited.
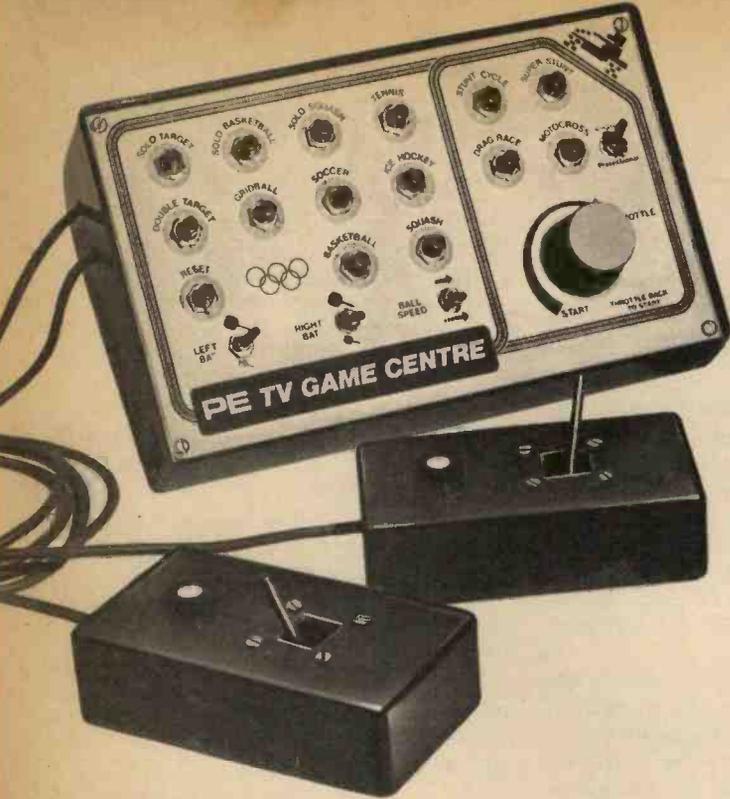
## Letters

Queries regarding articles published in PE should be addressed to the Editor, at the Editorial Offices, and a stamped, addressed envelope enclosed. We cannot undertake to answer questions regarding other items, nor to answer technical queries over the telephone.



THIS is really two separate t.v. games circuits combined in one box to give a selection of stunt motorcycle games and a large variety of ball games too.

The four "bike" games comprise: *Stunt Cycle*, *Drag Race*, *Super Stunt Cycle*, and *Motocross*. These are provided by the AY-3-8760-1 games chip, and occupy the right-hand side of the Game Centre fascia.

There are ten ball games comprising *Solo Target*, *Solo Basketball*, *Solo Squash*, *Tennis*, *Double Target*, *Gridball*, *Soccer*, *Ice Hockey*, *Basketball* and *Squash*.

### STUNT CYCLE SECTION

These are games for one player who controls the speed of a motorbike and rider. At the start of each game, the motorbike and rider are stationary at the upper left-hand side of the TV screen. As the player turns the throttle controller, the motorbike and rider move across the screen on track 1. The motorbike sound starts with the bike movement and as the bike and rider accelerate, the motorbike sound reflects these speed changes. The motorbike wheels have an appearance of rotating at a speed also related to the throttle setting. At the end of track 1, the bike and rider reappear on track 2 at the left-hand side, and likewise at the end of track 2, the bike appears on track 3 at the left-hand side of the screen. Movement of the bike and rider on track 3 over the right-hand edge of the screen causes a reinitialisation of the bike and rider to the left of the screen on track 1. There is no further movement until the throttle is reset to a slow speed and then increased again. The playing field for each game is shown opposite.

# PE TV GAME CENTRE




## DRAG RACE

The object of this game is to reach the end of track 3 in the shortest time. The three-digit score is automatically reset as the rider first begins to move on track 1 and the score is incremented until the game is over. The score appears centred on the screen above track 1, and remains until the start of the next game.

Drag Race requires a speed shifting to achieve the lowest time scores. As the throttle speed is increased and the rider begins to move, the bike is in speed one and moves at a set rate across the screen. The only way to accelerate the bike motion is to return the throttle to a "slow" position and then return to a "fast" position. This shifting procedure will move the bike into speed 2, which will then go across the screen at a faster rate. Another "shift" will allow speed 3.

A PROFESSIONAL/AMATEUR switch is provided to select a difficulty factor. In the professional mode, a crash occurs if the player tries to increase the throttle speed too rapidly. A crash will flip the bike and rider upside down, and the sound will be a high-pitch screech. At the end of the crash, the bike and rider are reinitialised on track 1, and the score reset. In the easy mode, no crash is allowed.

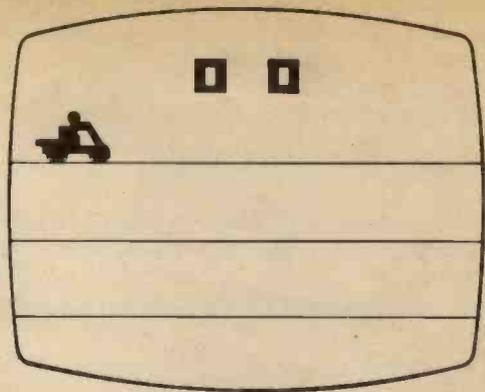


DRAG RACE

## MOTOCROSS

As the throttle speed is increased, the bike and rider move across track 1 at a rate determined by the throttle controller setting. Motocross has no speed shifting. Located on each of the three tracks are obstacles. The PRO'/AM' option switch selects the number of obstacles per track. The easier mode has one obstacle per track and the harder mode has two obstacles per track.

The object of this game is to traverse the three tracks in the shortest time, doing a "wheelie" over each obstacle. The score counters record the run time in the same manner as the Drag Race game.

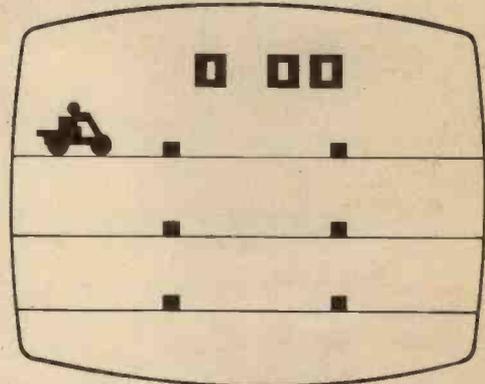In Motocross the crash is not caused by accelerating too rapidly. The crash is caused by not doing a "wheelie" over an obstacle. In the "wheelie" position, the bike will have the front wheel lifted off the track. A crash into an obstacle will flip the bike upside down and produce the screech sound. The score resets at the end of the crash.




MOTOCROSS
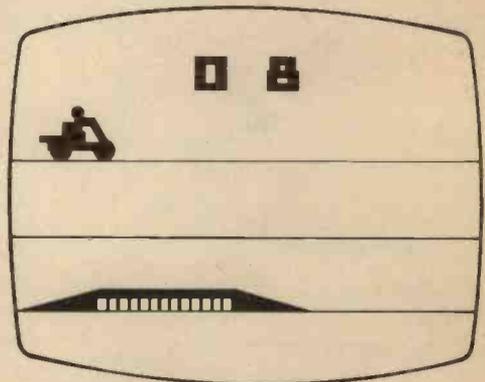
## STUNT CYCLE

The object of this game is to control the throttle speed to properly jump the ramp and buses located on track 3. The game begins with 8 buses and with each successful jump over the ramp and buses, an additional bus appears. The game is over when the maximum number of errors has been reached, which is 3 or 7 errors depending on the position of the PRO'/AM' switch or when 36 buses have been jumped, in which case the screen will fill up with buses. The game is then started by reselecting the Stunt Cycle game input.


Errors are caused by accelerating too rapidly, insufficient speed to clear the buses, or landing too far past the back ramp after the jump. The bike and rider flip upside down and a screeching sound indicates an error. The score records the number of errors in the first digit and the number of displayed buses in the next two digits.



STUNT CYCLE
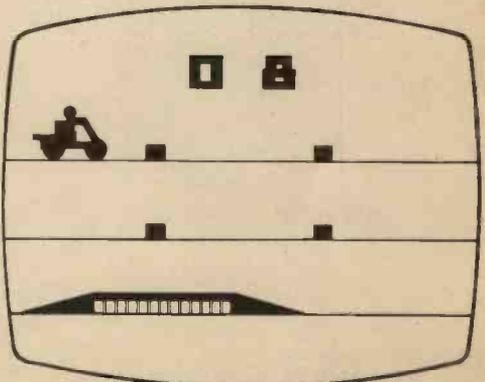
## SUPER STUNT CYCLE

This game is similar to Stunt Cycle with the addition of obstacles on track 1 and track 2. The object is to do a "wheelie" over each obstacle and then adjust the throttle for the correct speed to jump the buses on track 3. The PRO'/AM' option switch selects 2 obstacles per track and allows 3 errors per game in the harder mode, and 1 obstacle per track and 7 errors per game in the easy mode. Errors are



SUPER STUNT

caused by accelerating too rapidly, not being in the "wheelie" position over the obstacles, insufficient speed to clear the buses, or landing too far past the back ramp after the jump. The score records the number of errors and the number of buses displayed, the same as in the game of Stunt Cycle.

### BALL AND PADDLE SECTION


In all games, the ball starts at slow speed. If the high speed mode has been selected the ball will switch to high speed after seven consecutive hits by the players without a goal being scored.

The bats are segmented into five zones, each zone defining


a different rebound angle. The zones listed from top of bat to bottom are nominally 40° up, 20° up, horizontal, 20° down, 40° down. A ball passing through a bat from behind will have its angle influenced as above, but not its left/right direction.

All two player games terminate when one player has 15 points at which time the score flashes and the bats have no further effect on the ball.

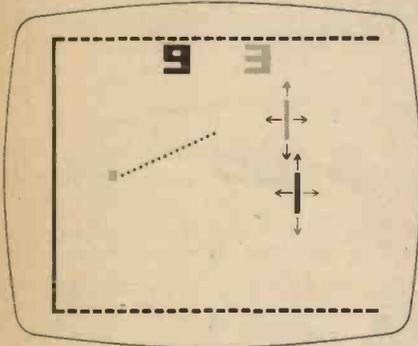
A tone of approximately 500Hz, 1kHz and 2kHz will be generated for a nominal period of 32ms for "ball hits wall", "ball hits bat" and "score". The output is capable of direct driving a 100Ω speaker.




SQUASH

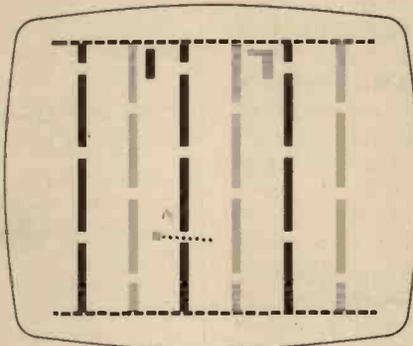


GRIDBALL

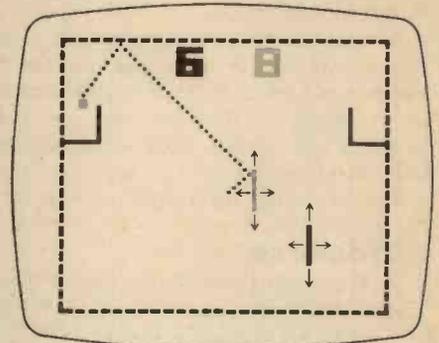


BASKETBALL

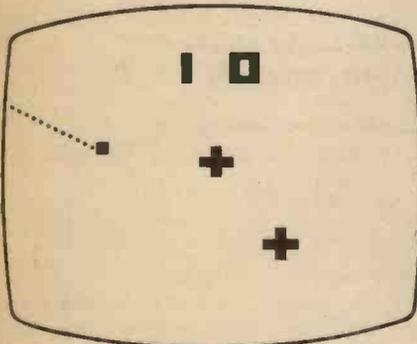


TARGET

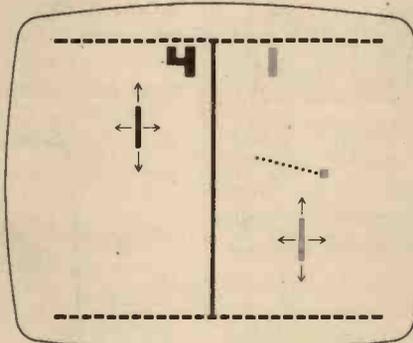


TENNIS

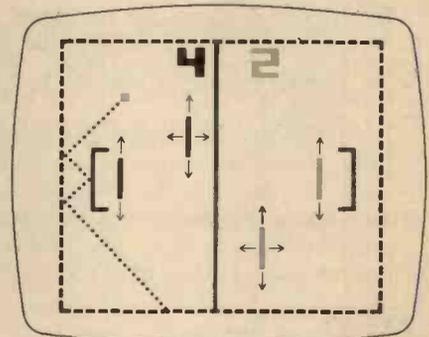


ICE HOCKEY

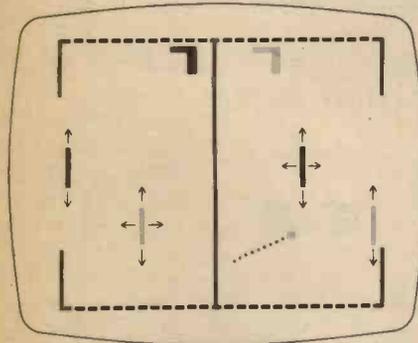


SOCCER

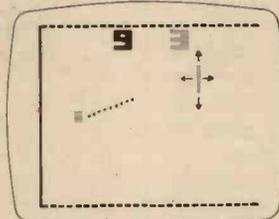

SOLO SQUASH

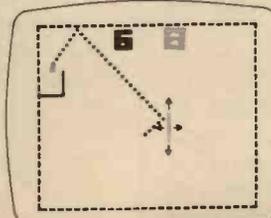

SOLO BASKETBALL

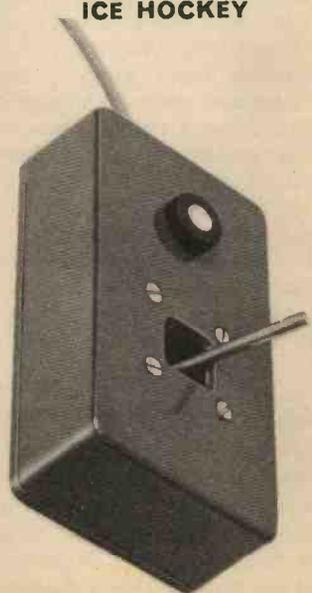

## BALL GAMES

## SQUASH

This game uses the playing area shown opposite. Each player can move over the whole court. The game will start when the player whose service it is, depresses his SERVICE button. The ball moves off with a random angle towards the front wall. The colour of the ball will change to the colour code of the next player to hit the ball. Should the wrong player intercept or be hit by the ball it will be considered a fault. Points will only be given if won on player's own service. Points won on opponent's service will only cause a service change.

## SOLO SQUASH

This game is for a single player. The right score counts the number of successive hits in the current game (to a maximum of 15), the left score the number of volleys played.

## GRIDBALL

This is a game of considerable mental agility. Each player has three sets of vertically moving barriers to block the ball from approaching his end of the field, and openings in the barriers to permit the ball to advance towards the opponent's end. The game starts when both players have depressed their SERVICE buttons. The ball moves away from the face off point with a random angle in either direction.

## BASKETBALL

The basketball games use the closed playing area shown. Participant players must deflect the ball and cause it to enter the top of the goal to score. The game starts when both players depress their SERVICE buttons simultaneously. The ball moves from the service point with a random angle in either direction.

## SOLO BASKETBALL

Basketball practice is a one player game which utilises only the left basket (see opposite). The right counter displays the number of hits the player makes without scoring while the left counter shows the number of baskets made. Play starts when the right SERVICE button is depressed.

## TARGET

In the double game each player has a cross which he can move to any point on the screen. From the edge of the field will come moving targets one at a time, and a player must position his cross over the target and simultaneously push the SERVE button to get a hit. Moving the cross towards the origin of the moving target will give a player the chance to beat his opponent to a score, but will also give him less thinking time in which to react when the target flies out. All scores are shown at the top of the screen.

Only one cross appears for the single player version of this game.

## TENNIS

The game uses the playing area shown (opposite). Each player can only move around his side of the court. The game will start when the player whose turn it is to serve, pushes his SERVICE button. The service will automatically change every five points scored. At service the ball will move away from the service point with a random angle but always towards the net.

## HOCKEY

Forwards on both sides have freedom to move over the entire playing area. The goal keepers will be locked in the horizontal axis in front of their respective goals, but will move in the vertical axis in the same manner as the forwards.

The game starts when both players have depressed their SERVICE buttons. The ball will move away from the face-off point with a randomly selected angle in either direction.

## SOCCER

Motion of the players is as in the hockey game. The game will start when the loser of the previous goal depresses his SERVICE button. The ball will move away from the kick-off point with a randomly selected angle but always towards the goal of the winner of the previous goal.

## CIRCUIT DESCRIPTION

No simple description can be given for the extensive internal workings of the two l.s.i. games chips, and most of the remaining electronics fall into two categories: game selection and t.v. interfacing, so that the games unit may be plugged directly into the t.v. aerial socket. See Fig. 1.

Because there are two games chips, a system is necessary to switch from one to the other and this is the function of IC9. The ball and paddle games are selected on IC1 by momentarily connecting certain combinations of Strobe (STR) and select (SEL) lines, but when any of these selection switches (S1-8, S10, S11) are pushed, generating a low input to the IC10(a) NAND gate, the output IC10(a) pin 13 goes high which will reset the D-type flip-flop IC9(a.) By the same mechanism IC9(a) can be set via IC10(b) when a motor-cycle game is selected.

The Q and  $\bar{Q}$  outputs from the flip-flop are used to control the 6.5V power supply lines to both games i.c.s, thus shutting down the one not in use.

## POWER SUPPLY


The d.c. input enters via a miniature jack socket, and is generated by an external mains power pack which plugs directly into a 13A socket. The Zener stabiliser comprising TR3 and D11, etc. produces 6.5V to supply the unit. Both games i.c.s are motivated by a clock signal which is provided by the oscillator designed around TR4.

## COLOUR ENCODER UNITS

As can be seen in Fig. 1, the colour encoder has four inputs: yellow, blue, green and red. The bus carrying the video outputs from IC1 can be identified, and these are ORED at IC7 with the video outputs from IC2. This is arranged so that whichever games chip is in use, the colour encoder will receive the necessary signals. It is in this "colour bus" that the colour system departs from a black and white system, where a composite signal only is generated. In this game, the right video output (for right player) is fed to the blue input, and likewise the left video goes to yellow. The players' bats then comply with this colour coding. Some diode OR signal processing is also necessary, and can be seen around IC5. A composite signal is generated, and the cycle games composite signal is produced by the summing amplifier TR5. The ball games signals are similarly summated at amplifier TR6. These two composite signals are then ORED by means of the mutual emitters of TR5 and TR6, and fed to the composite video input of the modulator system.



Fig. 1. Full circuit diagram of game centre

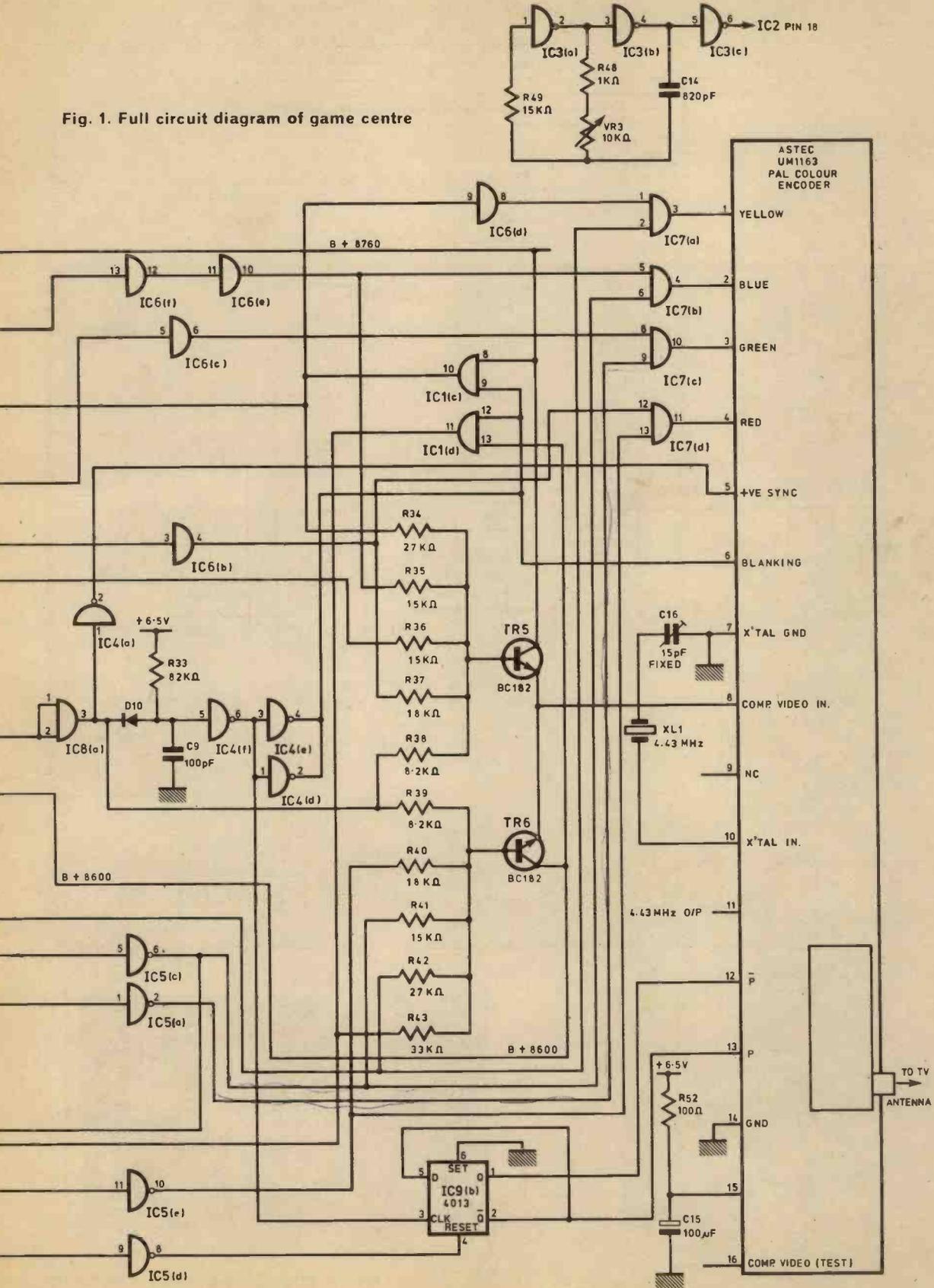

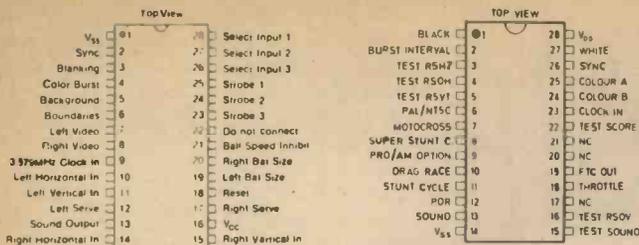


Fig. 2. Pinouts for games i.c.s  
(a) AY-3-8600 (b) AY-3-8760

## COMPONENTS . . .

### Resistors

R1-R4, R31, R32, R50, R51	3.3k $\Omega$ (8 off)
R5, R6, R11-R13, R24, R28, R45, R47	10k $\Omega$ (9 off)
R7-R10	3.9k $\Omega$ (4 off)
R14-R16	5.6k $\Omega$ (3 off)
R17, R30, R48, R18	1k $\Omega$ (4 off)
R52	100 $\Omega$ (1 off)
R19	100k $\Omega$ (1 off)
R20-R23, R25-27, R29	2.2k $\Omega$ (8 off)
R33	8.2k $\Omega$ (1 off)
R34, R42	27k $\Omega$ (2 off)
R35, R36, R41, R49, R44, R46	15k $\Omega$ (6 off)
R37, R40	18k $\Omega$ (2 off)
R43	33k $\Omega$ (1 off)

All resistors  $\frac{1}{4}$ W 5%

### Potentiometers

VR1	200k $\Omega$ lin carbon (dual axis)
VR2	200k $\Omega$ lin carbon (dual axis)
VR3	10k $\Omega$ lin carbon

### Capacitors

C1, C2	100 $\mu$ F/6.3V (2 off)
C3, C4	220 $\mu$ F/10V (2 off)
C5	100pF silvered mica (1 off)
C6	33pF silvered mica (1 off)
C7	56pF silvered mica (1 off)
C8, C14	820pF silvered mica (2 off)
C9	100pF silvered mica (1 off)
C10, C12	0.8 $\mu$ F Mullard C280 (2 off)
C11, C13	470pF silvered mica (2 off)
C15	100 $\mu$ F/6.3V (1 off)
C16	10-40pF trimmer (1 off)

### Transistors and Diodes

TR1-TR3	BC357 (3 off)
TR4-TR6	BC182 (3 off)
D1-D10	Silicon signal diode (10 off)
D11	BZY88 8V2 (1 off)


### Integrated Circuits and Modules

IC1	AY-3-8600 (1 off)
IC2	AY-3-8760-1 (1 off)
IC3-IC6	CD4069B (hex inverter) (4 off)
IC7	CD4071B (quad OR) (1 off)
IC8	4081B (1 off)
IC9	4013A (dual D/) (1 off)
IC10	4012B (quad NAND) (1 off)

### Miscellaneous

Module 1	UM1263 sound modulator (Astec)
Module 2	UM1163E36 vision modulator (Astec)
Module 3	UM1164E36 sub-assembly
L1	100 $\mu$ H tunable choke (screened)
XL1	4.4336MHz crystal
	28-pin i.c. socket (2 off)
	14-pin i.c. socket (8 off)
	Plastics boxes for hand held units, 113 x 63 x 30mm (2 off)
	Plastics box for main unit, 215 x 130 x 70mm sloped (1 off)
	Push-to-make switches for S1-S15, S19, S20 (17 off)
	Single-pole, single-throw toggle switches for S16-S19 (4 off)
	Knob for "throttle" control. Mains power pack (V)
	Low loss coaxial cable and TV aerial plug
	4-way screened cable for hand held units
	Printed circuit board

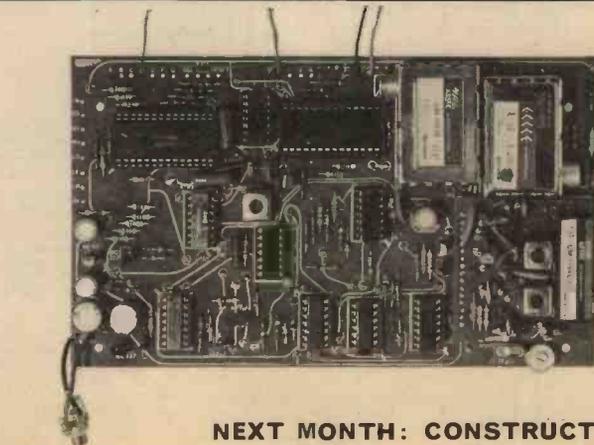All components are available from Teleplay



NEXT MONTH: CONSTRUCTION

# Market Place

Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

## ARALDITE RESIN PACKS

Araldite, the two-part mineral-filled epoxy resin system which is widely used throughout the electronic industry for potting small components, is now available in the form of a two-part sachet containing 200g of material from Ciba-Geigy Plastics.

The pack is in two sections, one containing the resin and the other containing the hardener: the two parts are separated by a clip. When the clip is removed, the two components come into contact with each other and can be mixed thoroughly by manipulation. To use, the bag is pierced at one end and the mixture squeezed out to be used as required.

The performance of the epoxy resins can vary if the two components are not mixed in the correct ratio, and the two-part sachet is a good way of ensuring that the optimum performance is achieved, and as the two components differ in colour the operator has a visual means of checking that the two parts are thoroughly mixed before use.


The hardener was chosen to give the system rapid curing properties at moderate temperatures, and is therefore particularly suitable for small castings. The mixture will cure fully at 25°C in between 24 and 36 hours, but will cure in as little as three hours at 60°C. Once mixed, the system has a life at 25°C of about 2-3 hours.

For further information contact Ciba-Geigy Plastics and Additives Company, Plastics Division, Duxford, Cambridge.
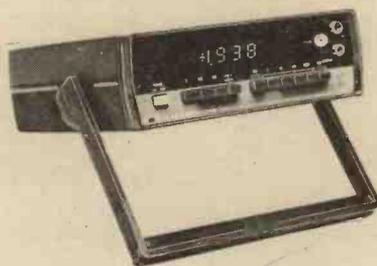
## DIGITAL MULTIMETER

The new digital multimeter available from Farnell Instruments Ltd will be of interest to anyone who has used a multimeter switched to the incorrect range with disastrous results.

This meter, called the Data Precision 1350 can withstand 500V on its resistance ranges; and a 6,000V spike on any voltage range for 500nS.




The 1350 offers a basic accuracy of 0.1 per cent and the instrument has a total of 26 ranges; a.c. and d.c. voltages from 100mV f.s.d. to 1,000V, resistance from 100mΩ to 20MΩ and a.c. and d.c. currents from 0.1μA to 2A.

The instrument is mains powered and has a 0.43 inch 3½ digit l.e.d. display. Recalibration is required once a year with only two adjustments necessary.

The cost of the unit is £115 excluding VAT and further details can be obtained from Farnell International Instruments Ltd, Sandbeck Way, Wetherby, West Yorkshire LS22 4DH.
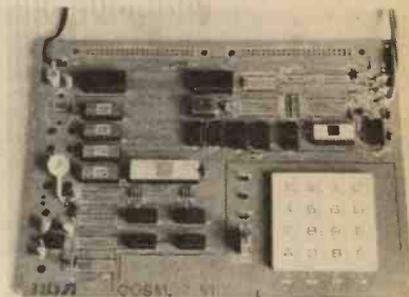
## COMPUTER KIT

A new do-it-yourself computer kit, the COSMAC VIP (Video Interface Processor) has been launched by RCA Limited. The system is designed to interface with a cathode-ray display or, via a suitable modulator, with a TV receiver and allows the user to assemble a complete microcomputer for creating and playing video games, generating computer graphics and developing microprocessor control functions.



The VIP offers a complete computer system on a printed-circuit board, using only 4k bits of ROM. Programs can be generated and stored in an audio cassette tape recorder for easy retrieval and use.

At the heart of VIP is RCA's COSMAC CDP1802 microprocessor, incorporating C-MOS circuitry for low power consumption and an 8-bit architecture for ease of application.

The CDP1802 microprocessor chip has a 2048 byte RAM, a single-chip graphic video display interface, a built-in hexadecimal keyboard, a 100 byte audio tape cassette interface, power supply and facilities for expanding both memory and input/output interfaces. An interpretive programming language known as CHIP-8 simplifies the programming of video games using hexadecimal code.

The VIP system is readily expandable, both on the printed-circuit board and through connectors. RAM capacity can be doubled on the board to 4096 bytes by adding four 4k bit devices, and can be expanded to 32 kilo bytes by adding further memory capacity through a 44-pin connector socket in the board. Parallel input/output expansion to 19 lines can be achieved for use with music synthesisers, relays, a low-cost printer or an ASCII keyboard.

The VIP hobbyist manual contains detailed information on kit assembly, operating procedures, CHIP-8 interpreter programming technique, machine-language programming, logic description, test programs, troubleshooting guides and system expansion. The manual also includes program listings for 20 video games, with simple instructions to non-programmers for using the hexadecimal keyboard.

VIP is usable with NTSC monochrome TV standards, but a PAL interface chip with colour and programmable sound capability will be available soon.

For further details contact: RCA, Sunbury-on-Thames, Middlesex.

## VIDEO AGE BEGINS

Sony's Betamax home video recorder will be in the shops from June at an expected price of £750, with half hour cassettes at £7.

The PAL colour recorder/player can record programmes via its own tuner. In fact it can be timed to record a chosen programme up to three days in advance.

By having its own tuner, recording and viewing of two different channels can take place simultaneously. Also the potential fire hazard of an unattended live TV is avoided.

Recording duration can be set to 15, 30 or 60 minutes, any multiple of 15 minutes, or to the end of the cassette. A ¾ hour cassette will cost £13.50.

Pre-recorded video material will presumably become as readily available as sound cassettes are now. In 1971 Sony and Time Life jointly announced plans to produce video programmes.

With a small video camera and microphone, simple home video programmes can be produced on the Betamax.

During recording a remote pause control enables material to be edited from the armchair.



Sony claim head life of over 1,000 hours with replacement heads very approximately costed at £60. The slanted azimuth head was developed by Sony and the tape

speed is an incredible 19mm per second. Tape width is 13mm. Recorded picture quality is visibly indistinguishable from transmitted pictures.

## TELEPHONE CHARGE CLOCK

A new microprocessor based product will, for the first time, enable telephone users to control the cost of each call as it is being made.

The Monitel telephone charge clock, computes and displays the actual cost of the call in pounds and pence, automatically accounting for the day of the week, the time of day, charge band tariffs and the VAT rate.

The unit is based on the Rockwell PPS4/1 microprocessor range and is programmed by insertion of a punch card. When the telephone rates change a new card is automatically supplied for a nominal fee.

Two models cater for world wide needs;

a UK type and an International version. Designed to complement Post Office telephones the Monitel is available in all seven standard colours; ivory, grey, green, black, red, blue and yellow.

It does not infringe the Post Office Act because it is not directly connected to the telephone, but runs off mains power and is activated by the user.


When not being used to monitor calls the Monitel reverts to a 12 hour clock which can be set by keys hidden from view on the top surface of the unit where the telephone is placed.

The only manual selections required by the user are operation of the touch keys on the face of the display which coincide

with the Post Office charge bands "1" local, "a" up to 56km, "b" over 56km, which are given in the telephone dialling code booklet, and touching the start/stop keys when the call is connected and again when it is completed.

The International model incorporates six alternatives, the three UK charge bands plus international bands 1, 2 and 4 which cover all of Europe, North America and the Caribbean.

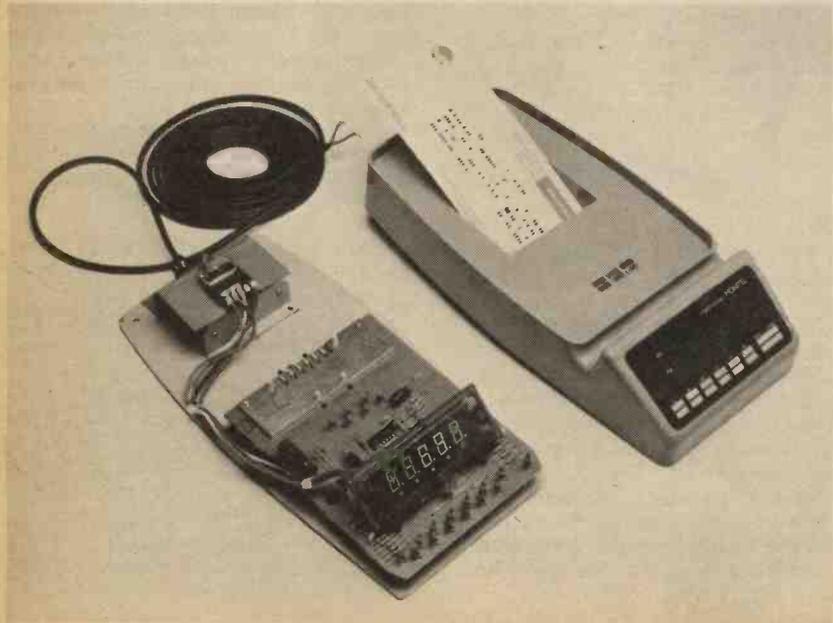The price of the UK model is £29.00 and the International version £39.00 both inclusive of VAT. Further details are available from Monitel Limited, Berechurch Road, Colchester, Essex.



## MULLARD MODULES

Three new economy priced amplifier packages which utilise proven Mullard modules have been introduced by Radio and Television Component's Ltd.

Package One consists of two LP1173 audio modules and an LP1182/2 stereo preamplifier module.

Package Two features two LP1173 modules plus an LP1184/2 stereo pre-amp with integral magnetic pre-amp.

Package Three includes two simple LP1173 audio modules, LP1182/2 stereo pre-amp, LP1179 FM tuner and a 1165 AM/FM IF strip.

Each package comes complete with application sheets detailing the performance and termination of each module. To complete the construction of an amplifier or tuner amplifier, volume controls and power supply can also be obtained from the company.

A very substantial saving over list prices being offered on these units: Package One components are £4.95 (normally £25.50), Package Two £6.95 (normally £27.50) and Package Three £9.95 (normally £37.00). Post and packing is £1.00 for any of the packages.

Further details can be obtained from R & TVC, 323 Edgware Road, London W2.


## LINEAR CAPACITANCE METER PROJECT

We are informed that Watford Electronics can supply all the components for the Linear Capacitance Meter project as given in last month's issue. Perplexed hobbyists will be pleased to know that that includes the 1 $\mu$ F 1% polycarbonate capacitor and the 10M $\Omega$  1% resistor.

Watford Electronics, 35 Cardiff Road, Watford, Herts.
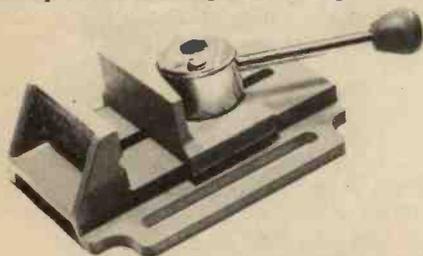
## FRENCH VICE


The Nodex Quick Grip can be mounted horizontally on a bench top or on the bench edge. As a vice or a press its patented hand lever locking system makes for quick firm locking or loosening.



V notched jaws enable a wide variety of profiles to be held and the vice is adaptable on all drill supports. Maximum jaw opening is 70mm and jaw area is 70 x 35mm.

At 850gms it is easily carried in a tool kit.

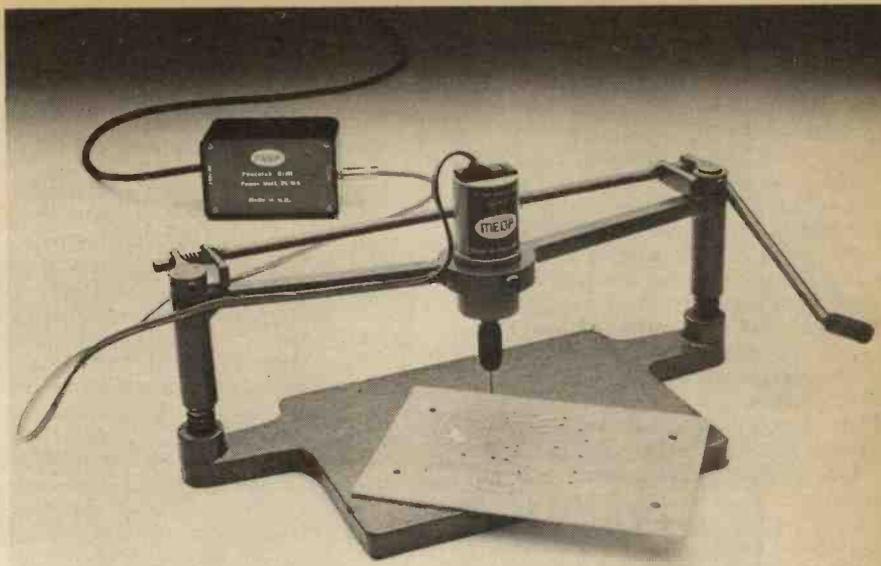This French vice is only £6.50 and is distributed by Special Products Distributors Ltd., 81 Piccadilly, London W1V 0HL.



## P.C.B. DRILL STAND

The Mega Photolab is a new, low cost p.c.b. drill stand designed for use with conventionally hand-held p.c.b. drill units. It has been specifically introduced to meet requirements in the production of prototype p.c.b.s.

A strong base of machined cast iron supports precision steel guides by means of which the standard 12V drill is raised and lowered.

Important features are its combined simplicity and accuracy, and the fact that

it will accept Mega and other proprietary drills of 34mm diameter as well as drills such as the Titan, at 41mm.

Additionally, the same basic drill stand is available to special order capable of accepting drills between 20 and 41mm diameter, at marginal extra cost.

The stand will accept p.c.b.s up to 10 x 9 in.

Priced at £14.50, the PLST-12A is manufactured by Mega Electronics Ltd., 9 Radwinter Road, Saffron Walden, Essex CB11 3HU.

## TEN YEARS ON

Bandridge, the component and accessory wholesalers, recently celebrated their tenth anniversary. Operations started in the founder's front room and today the turnover is over £ $\frac{1}{2}$ M. Bandridges "own brand" sales now account for more than half of their turnover.

Most of their customers are one or two man retailers, 90 per cent of the company business being in the UK.

Speed of delivery is thought to be so important that Securicor is used and despatch occurs within 24 hours.

The company's motto is *fast and friendly* and special effort is made to train staff to be familiar with items, prices and stock availability to ensure quick telephone replies.

Initially they specialised in components only but now accessories are as important. Constructors must be particularly pleased that Bandridge made available the S-DECs, T-DECs,  $\mu$ -DECs and Blob Boards.

New products are shortly to accompany the already established range of audio accessories under the "Bandridge" banner. They include a range of intercoms and a range of quality amplifiers to supplement the already highly successful Quantum 150.

Plenty of literature are available to retailers from Bandridge at 80a Battersea Rise, London, SW11 1EH (01-228 9227).

## INSTRUMENT CASES


A new range of instrument cases has just been launched by Vero Electronics.


The new cases are designed to present the same appearance as the existing range, ensuring users of continuity of design, but have been modified to allow the top panel to be easily removed for servicing and calibration.

The range includes 19in and half width models, which are available with or without front handles as required.

The standard colour of the cases is blue/grey but four other colours are available to special order.

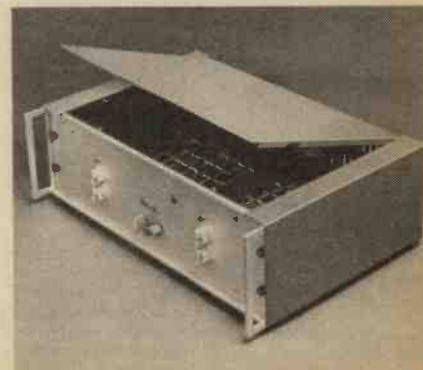For more information about the Mk II D-Case ABO17 contact Vero Electronics Limited, Industrial Estate, Chandler's Ford, Eastleigh, Hampshire.



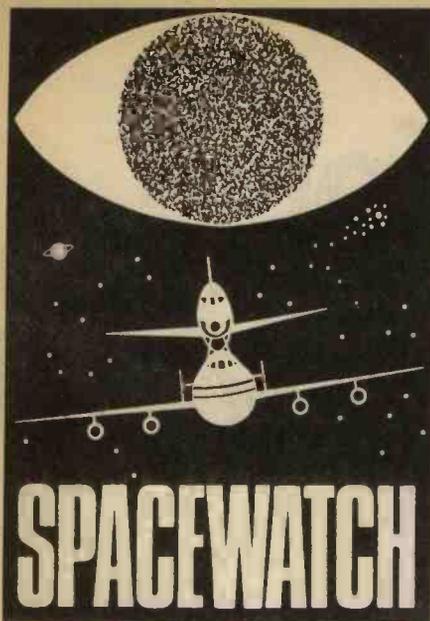

**FRANK W. HYDE**

#### SOVIET ACTIVITY

The launching of the Cosmos research satellite in March marked two important events. The first was that the 1,000th Cosmos was put into orbit with 83° inclination, a period of revolution of 104.9 minutes, apogee of 1,024 kilometres and perigee of 978 kilometres.

This satellite is a navigational vehicle to aid shipping and establish precise parameters and geographic coordinates. Like other satellites of this class Cosmos 1000 has influenced the weather forecasting techniques and aided geological prospecting. Though of the same class the Cosmos series vary considerably in design depending upon the tasks they have to carry out. In most cases the end of life of each vehicle has been to burn up in the higher atmosphere after their individual missions were completed. Some however were designed to have a soft landing return.

The most famous of these was Cosmos 110. This satellite made a 22 day trip with two dogs aboard. The successful return provided vital information for the design of future manned missions. No regular pattern has been followed in the launches but the general level of activity was increased as the programmes advanced. It took more than ten years for the first 500 of these vehicles to be launched. The second 500 of the programme was accomplished in half that time.

#### THE SALYUT MISSION

The two astronauts who made the record for the longest weightless mission ceased to feel the effects of the prolonged space conditions a short time after their return to Earth. They celebrated it by going for a walk. This marked the end of

their first re-adjustment to Earth conditions. Some fatigue was felt at first when standing up for a prolonged period. However each day this condition was improved. After four days they began to put on some of the 11lbs they had lost in weight.

Geori Grechko when commenting on his space walk, recalled that the sky had seemed more vast and more colourful than it had appeared from the portholes of the satellite. He also said that the Sun had felt hot in spite of the special space suit. In assessing the work programme both Grechko and Romanenko made reports of the success of the newly designed spacesuits. The load suit and the "Chibis" suit, designed to control the blood flow in the normal pattern on Earth, were highly beneficial. The space "bike" and the running track had also contributed a great deal to their comfort and well-being.

A point was made by the controller of the medical group, Professor Anatoli Yegorov, that the compatibility of these two men was a very important factor in the success of the mission and had now contributed enough data to show that man could live quite satisfactorily for over a year, without disturbance of physical or mental conditions.

#### FUTURE PLANS

A Polish and a German cosmonaut will take part in the next missions, following the Soviet members to start the new series. The exact details are not yet ready for release as further study of the data is still proceeding. It is however certain that another supply ship will be part of the programme and that a regular set of shifts will be the main object of the missions. The fact that efficiency improved with time during the first group of multiple manning, will certainly mean that extra experiments will be added. The timing of the tasks and the days according to the normal Moscow time seemed to contribute not only to the efficiency but also to the high morale. It would appear that the biological clock is also an important factor in success in space.

Is it perhaps possible that a "special" atmosphere contains some special merit where the efficiency of the biological machine is concerned.

No doubt the new plans will include the dropping of sub-satellites as in the past. Remote control and operation of surveillance, both radar and photographic missions, have covered many fields. All of the missions in the past seem to have had multiple purpose types of programme. Many of the missions have appeared rather puzzling. For example Cosmos 881 and 882 launched by the same rocket and in different conditions returned to earth the same day or shortly after. Similarly Cosmos 997 and 998. Certain of this group of Cosmos vehicles such as 921 and 972 went into an unusual orbit at 75.8° inclination. Cosmos 929 was made to perform extensive changes of parameters. This was

a rather larger vehicle than the others. The success of the geodesy and the weather forecasting enable very close touch to be maintained with the Soviet fleet of ships and submarines in all parts of the world.

It would seem logical that with all the increasing activity the Soviet space programme must include some form of shuttle system. Clearly it would be more economic and it is known that drop tests have been made with a delta-wing spaceplane. One possibility is that, in accordance with their usual testing of unmanned vehicles in assessing new designs, some of the more recent launches are the precursors of a new series of vehicles.

#### A NEW CANDIDATE

Another candidate for the honour of black hole has now appeared. The "Jet" Galaxy M87 has been under extensive examination at Kitt Peak National Observatory in Arizona; there is an increase in the velocity of matter circling the nucleus. The increase is of the order of 100 kilometres a second. This is the strongest evidence for a massive black hole in the centre of M87.

This work began at Mount Palomar Observatory where J. Kristian and his colleagues found that the galaxy had a brilliant pin point of light.

The next step in obtaining confirmation of this theory will be to scan other elliptical galaxies for similar evidence of massive black holes.

#### COMETS AND ICE AGES

Comets have been very much in the news of late so it is not surprising that there should be a follow up from Fred Hoyle and Wickramasinghe. They have suggested that passing comets may have been responsible for large masses of dust particles injected into the solar system. These are perhaps the cause of a cooling process. It would be necessary for the Earth to pass through the dense inner halo of the comet. If it is assumed that there is an average of say five comets per year which come within one astronomical unit of the Earth, the chances of a mass acquisition of cometary dust is of the order of  $10^8$ . Such an order of real happening would agree very roughly with the chronological order of geology.


It could be possible that the size of the particles would lead to an effective reduction in light reaching the Earth. Many things could happen, from the reduction of photosynthesis to the disruption of the food chains within a short time. The picture painted by Hoyle and Wickramasinghe of an initial fast freezing which would see the rapid demise of large animals but the longer continued existence of seeds and nuts with small animals and freshwater organisms surviving. This situation does roughly compare with the conclusions for the past eras. The recovery it is suggested would be quite rapid, something of the order of 1,000 years.

# Mini-priced breadboards for maxi-sized projects.


Experimenter<sup>SM</sup> low-cost solderless breadboards are the first in the world specially designed for 0.3" and 0.6" pitch DIP's.

They clip together by an exclusive interlocking system in any configuration, (just like dominoes), so you arrange the breadboards to suit your circuit, not vice-versa.

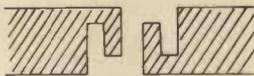They are precision moulded from durable, flame-retardant plastic, and feature alphanumeric coding for easy circuit building, and non-corrosive, pre-stressed nickel-silver alloy contacts—reliable for well over 10,000 insertions.




EXCLUSIVE INTERLOCKING SYSTEM.

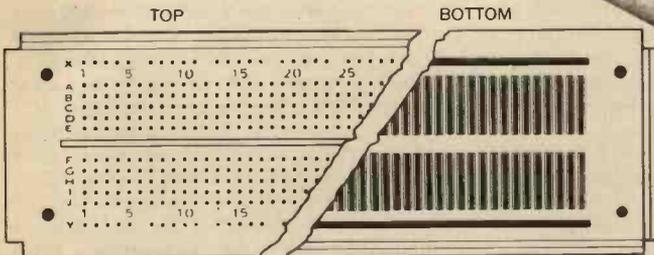

Contact resistance is a mere 0.4 mΩ and interterminal capacitance is typically less than 5 pF. The Experimenter is usable to over 100 MHz.

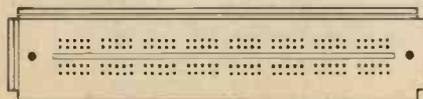Experimenter 600 and 650 models are ideal for RAM's ROM's and PROM's (0.6" centre IC's) while the 300 and 350 models are for smaller DIP's (0.3" centres). All four models, of course, also take all standard components, the 0.1" grid being compatible with transistors, diodes, LED's, capacitors, resistors, pots—in fact any component with lead sizes between 0.015" and 0.032"



A useful quad bus strip (EXP4B) further

Model	Length"	Width"	Centre channel"	5-way tie points	Bus	Price	All units are 0.330" deep.
EXP300	6.0	2.1	0.3	94(470)	2(80)	£7.29	Prices include VAT (8%) and p&p for
EXP350	3.6	2.1	0.3	46(230)	2(40)	£4.21	UK Orders.
EXP600	6.0	2.4	0.6	94(470)	2(80)	£7.88	Add 5% to all orders outside UK.
EXP650	3.6	2.4	0.6	46(230)	2(40)	£4.69	All prices and specifications correct
EXP4B	6.0	1.0	N/A	N/A	4(160)	£3.29	at the time of going to press.

expands the versatility of the system for the MPU user.

Experimenter breadboards can be used alone or mounted on any convenient flat surface, thanks to moulded-in mounting holes and vinyl insulation backing that prevents short circuits. Mount them from the front with 4-40 flathead screws or from the rear with 6-32 self tapping screws.

But however you use them, Experimenter breadboards are the quickest and easiest way to build and test circuits.

If you're working on IC's, MPU's, memories,

Get your hands on an Experimenter and stop wasting time!

displays or any other circuits, buy the breadboards that are designed for you. Ring us (01-890 0782) with your Access, Barclaycard or American Express number and your order will be in the post that night.


Alternatively, send a cheque, or postal order (don't send credit cards!) and it still only takes a few days. Otherwise ask for our complete catalogue.



# I.C.E. MULTIMETERS
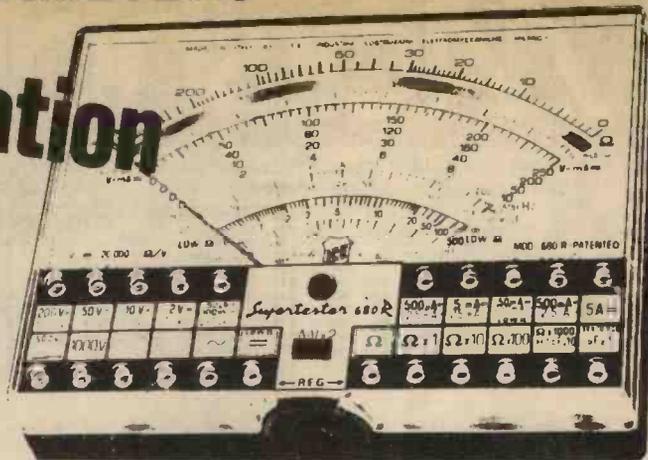
## TWICE the information in HALF the size

The I.C.E. range of multimeters provide an unrivalled combination of maximum performance within minimum dimensions, at a truly low cost. Plus, a complete range of add-on accessories for more ranges, more functions.



### Supertester 680R (illustrated)

- \* 20kΩ/V, ±1% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- \* 80 Ranges - 10 Functions
- \* 140 × 105 × 55mm

**£32.00 + VAT**

(For Mail Order add 80p P&P)

### Supertester 680G

- \* 20kΩ/V, ±2% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- \* 48 Ranges - 10 Functions
- \* 109 × 113 × 37mm

**£24.50 + VAT**

(For Mail Order add 80p P&P)

### Microtest 80

- \* 20kΩ/V, ±2% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- \* 40 Ranges - 8 Functions
- \* Complete with case - only 93 × 95 × 23mm

**£16.60 + VAT**

(For Mail Order add 80p P&P)


All I.C.E. multimeters are supplied complete with unbreakable plastic carrying case, test leads, etc. and a 50-plus page, fully detailed and illustrated Operating and Maintenance Manual.

Now available from selected stockists. Write or phone for list, or for details of direct mail-order service.



Electronic Brokers Ltd.  
49-53 Pancras Road, London NW1 2QB  
Tel: 01-837 7781

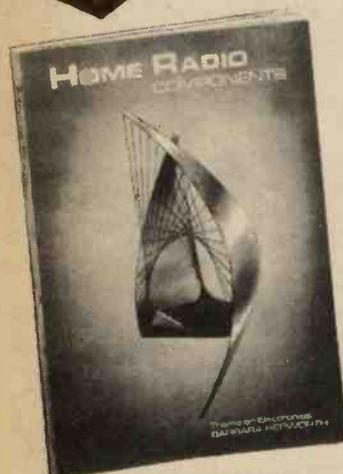**THIS is the Catalogue you need  
to solve your  
component  
buying  
problems!**



- The finest components catalogue yet published.
- Over 200 A-4-size pages.
- About 5,000 items clearly listed and indexed.
- Nearly 2,000 illustrations.
- Bargain List sent free.
- At £1.40, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.

HOME RADIO (Components) LTD., 234-240 London Road, Mitcham, Surrey CR4 3HD

Please write your Name and Address in block capitals

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

HOME RADIO (Components) LTD Dept. PE  
234-240 London Road, Mitcham, Surrey CR4 3HD



Regs No  
91796 London

POST THIS COUPON  
with cheque or P.O. for £1.40

## TRAMPUS

TRAMPUS ELECTRONICS LTD. 58-60 GROVE ROAD, WINDSOR, BERKS. SL4 1HS. TELEPHONE WINDSOR (07535) 54525.

Cash & cheque orders over £5 post free. Credit cards by post or phone £5 min. Post & packing 20p. CWO add VAT to prices marked \* 8%, others 12 1/2%. Free price list of our full range send addressed envelope. Quote this ad as prices may change. All devices to makers specifications. Normally 24 hour turn around on orders. For ex-stock product.

LEDS	FULL SPEC PAKS	DEVELOPMENT PARCELS	REDUCED LINES
Red no clip 9p	PAK A: 12 red LEDs £1*	SET 1: 250 x 50V ceramics 5% 10 each £1*	A small selection from our lists. 7815 1A15V 60p*
PAK of 100 LEDs £3*	B: 5 x 7A1 8 pin £1*	SET 2: 22pf to 0.1uf £1*	7805AM309K £1*
T11 20S & clip 11p	C: 4 x 2N3055 T03 £1*	SET 3: TANTALUMS £5	BC107 or BC108 8p*
0.2" LED Red & clip 12p	PAK D: 12 x BC109 £1*	SET 4: Electrolytics £5	BC109 10p* BC109C 15p*
Color LEDs All 16p	PAK E: 7 x BFV51 £1*	SET 5: 1000/220/500/1000uf £5	AC176 only 10p
	H: 7 x 2N3819E FET £1*	SET 6: Resistors 10 each 10Ω to 1 MEG total 500 £5	741 8 pin 21p*
	K: 40 x 1N4148 £1*	SET 7: Zeners 400mW £1	BC212, 3.4 A or L 11p
	M: 4 x pair 2A NPN/PNP £1*	SET 8: 5 x 20 valves 3V to 33 volts (100 ohm) £5	2N3055 90W 29p*
	PAK N: 50 x OA81/91 £1*	SET 9: Presets PR £5	2N3819E FET 16p
	PAK P: 20 x P/BC109 £1*	SET 10: VERT 100 mixed £5	ORP12 60p*
	PAK R: 14 x BC 107 £1*	SET 11: Heatinks 10 off each, T018, T05, TV4, small T03 £1	741 8 pin 21p*
	PAK S: 14 x BC 108 £1*		BC212, 3.4 A or L 11p
	T: 10 x BC131 type £1		2N3055 115W T03 45p*
	V: 50 x 5 mild 10V £1		2N3819E FET 16p
	X: 4 x 555 timer £1		ORP12 60p*
	Z: 20 x PNP 3702 type £1		741 8 pin 21p*
	Y: 4 x LM301/14P £1		LM380 amp 75p
	U: 4 x 1A 50V SCR £1		LM3900 69p
	NEW PAK O: 50 x 220 mfd 6.3V electrolytes £1		CMDS 4011 15p
			4013, 4049 39p
			TTL 7400 8p
			£5 14121 25p etc etc.

Recommended Retail Price **£16.09** INC V.A.T.

## FANTASTIC VALUE

Send Cheque or P/Order for £11.95 (includes P&P) to: MAIL SALES, EROS HOUSE, P.O. BOX 2, FELTHAM, MIDDIX.

Money refunded if not satisfied. Allow 14 days for delivery.

Name \_\_\_\_\_

Address \_\_\_\_\_

ONLY **£11.95** INC V.A.T. and P&P



### Welter EXPERT INSTANT SOLDER GUN KIT

Gun has built in Spotlight and high efficiency copper soldering tip. Kit comes complete with two spare soldering tips, one plastic smoothing soldering tip, soldering aid tool, flux brush, tip wrench, coil of 60/40 resin core solder and a 18-page hobby hints booklet full of instruction.

BLOCK CAPITALS PLEASE Pe1



# WHAT'S NEW?

**ME**, semiconductor teaching kit



The most MODERN, RAPID ECONOMIC way to master space age electronics. Starting even from ZERO by performing over

**100 EXPERIMENTS**

creating more than 20 practical applications

You learn all about the most up to date electronic circuits; how to calculate, repair, and design them, while pursuing your favourite hobby. Start from scratch, or improve your present knowledge, train and earn money in your spare time, turn your pastime into valuable job opportunities.

Compare our prices: you receive the entire course, "mini laboratory" and components for LESS than the price of the components alone.

**COMPLETE KIT: nothing else to buy\***

### You get:

— Instruction manual: over 200 pages of detailed step-by-step instructions. Start from scratch, explains basic laws and physics of Electricity, semiconductor principles and operation electronic circuits: form diodes (including diac, zener) transistors, triacs to integrated circuits (C.MOS, operational amplifiers) etc. . . .

Over 200 Electronic components: aerospace technology. Printed circuit experiment board, photo-transistor, triac, thyristor, I.C.S. transistors (including FET, MOSFET) LEDs plus resistors, capacitors, millimeter, potentiometers, variable capacitor, etc. . . . etc. . . . etc. . . . measuring instruments (you assemble yourself from among components furnished in kit). ELECTRONIC VOLTMETERS, LOW FREQUENCY MEASURING AMPLIFIER, LOGIC INDICATORS, REGULATED POWER SUPPLY, MULTIAMTER.

### You perform:

Over 100 different experiments: from the most basic voltage measurements to radio transmitter circuits and including Hi Fi, Flip Flops, Ic applications, Triac use, etc. . . . etc. . . . etc. . . .

### You construct:

More than 20 complete functional systems: light modulator, high fidelity amplifier, radio control set, radio receiver and transmitter, electronic gadgets and games and many, many more.

\*Hand tools not furnished.



SAVE £10 - mail coupon today - SAVE £10

**saga**

SAGA ENGLAND, P.O. Box 401, King's Mead, King's Lane, Chipperfield, Nr King's Langley, Herts. WD4 9PB.

Please send me (QTY) 1K2 KIT(S)  
I enclose cheque (money order) for

£


Name

Address

B

# ALCON

BRING YOU THE NEW CHINAGLIA

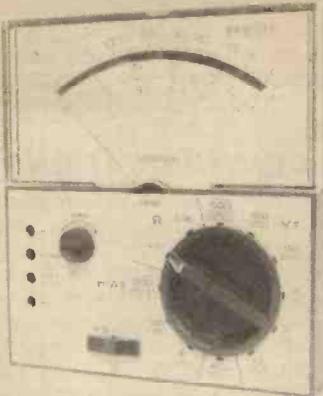

## MINOR POCKET MULTIMETER

THE  
PROFESSIONAL  
SOLUTION  
TO  
GENERAL  
MEASUREMENT  
PROBLEMS

The best instrument for the workshop, school, toolbox, T.V. shop and anywhere accurate information is needed quickly and simply.

### IT OFFERS:

- ★ Single-knob range selection
- ★ 110° Full-view mirror scale and fine line pointer
- ★ Clear unambiguous scales
- ★ A well-damped cylindrical magnet movement with resilient bearings
- ★ 31 ranges providing coverage from 100mV to 1.5kV d.c.; 7.5V to 1.5kV a.c.; 50µA to 2.5A d.c.; 25mA to 12.5A a.c.; 10kΩ and 10MΩ resistance and six signal level ranges.
- ★ Accuracy ±2.5% d.c. and ohms, ±3% a.c.

Make your first multimeter a MINOR from

# ALCON

Instruments Ltd.

19 MULBERRY WALK, LONDON SW3 6DZ TEL: 01-352 1897

## OSMABET LTD

We make transformers amongst other things

### LOW VOLTAGE TRANSFORMERS: Prim 240V ac.

6.3V 1.5A £2.45; 3A £2.85; 6A CT £5.30; 12V 1.5A £2.85; 3A CT £5.30; 6A CT £6.85; 18V 1.5A CT £5.30; 24V 1.5A CT £5.30; 3A CT £6.85; 5A CT £14.00; 8A CT £23.75; 12A CT £30; 40V 3A CT £9.75.

### TWIN SEC TRANSFORMERS: Prim 240V ac.

6V 0.6A + 6V 0.6A; 9V 0.4A + 9V 0.4A; 12V 0.25A + 12V 0.25A; 20V 0.15A + 20V 0.15A; all at £3.25 each; 15V 0.75A + 15V 0.75A £4.85; 15V 1.5A + 15V 1.5A £6.85; 18V 1A + 18V 1A £6.10; 18V 1.5A + 18V 1.5A £7.30; 20V 1.5A + 20V 1.5A £7.30; 12V 4A + 12V 4A £8.10; 25V 2A + 25V 2A £8.10.

### MIDGET RECTIFIER TRANSFORMERS: 240V ac.

6-0-6V 1.5A or 9-0-9V 1A £2.45 each; 12-0-12V 1A or 20-0-20V 0.75A £2.95 each; 9-0-9V 0.3A or 12-0-12V 0.25A or 20-0-20V 0.15A £2.95 each.

### LT TRANSFORMERS TAPPED SEC: Prim 240V ac.

0-10-12-14-16-18V 2A £4.85; 4A £6.50; 0-12-15-20-24-30V 2A £5.65; 4A £8.90; 0-5-20-30-60V 1A £6.75; 2A £9.75; 0-40-50-60-80-100-110V 1A £9.70.

### MAINS TRANSFORMERS SPECIAL OFFER: Prim 240V ac.

250-0-250V 60Ma 6.3V 1A £1.50; 250V 100Ma 6.3V 2A £2; 9V 3A £2; 23V 0.5A £1.25; 20V Auto. 110/240V £1.75.

### SPEAKER AUTO MATCHING TRANSFORMERS

12W, 3 to 8 or 15 up or down: £2.50.

### LOUDSPEAKERS

38 or 45mm or 2 1/2 in 80, 2 1/2 in 8 or 250, 2 1/2 in 8 or 800, 3 in 350, 3 1/2 in 3, 16 or 800, all at £1.10 each; 5 x 3 in 3, 8, 15 or 250, £1.25; 7 x 4 in 3, 8, 16, 25 or 800, £1.75; 8 x 5 in 4, 8 or 250, £2.50; 8 in 80, £2.50.

### "INSTANT" BULK CASSETTE/TAPE ERASER

Instant erasure of cassettes and tape spools, any diameter, demagnetises tape heads, 200/240V ac £5.50.

### POWER SUPPLY, TWIN OUTPUT: Prim 240V ac.

New, British manufacture, smoothed d.c. output 20V 1.5A, plus stabilised output of 15V 100mA, plus 12V ac 0.5A output, complete with diagram: £3.00.

### CONDENSERS

Electrolytic 1000/50V 30p; 2000/30V 30p; 1200/75V 50p; 3900/100V £1.25; Paper tubular W/E 0.47/600V, 2.2/400V, 4.7/160V all at 25p each, £10 per 100.

### EDGWISE LEVEL METER FSD 200 µA

Size 19 x 18 x 20mm 8000, £1.10.

### SYNCHRONOUS GEARED MOTORS, 240V ac.

Brand new, built in gearbox, 1, 6, 8 or 20 RPH all at £1.20 each.

### O/P TRANSFORMERS FOR VALVE POWER AMPLIFIERS

P.P. sec tapped 3-8-15, A-A 6K 30W £11.50; A-A 3K 50W £17.00; 100W (EL34, KT88, etc) £22.00.

### G.E.C. MANUAL OF POWER AMPLIFIERS

Covers valve amplifiers 30W to 400W 75p.

### MULTI WAY CABLE, SCREENED PVC COVERED

36 way £1.00; 25 way 75p; 14 way 50p; 6 way 25p; 4 way 20p; 2 way 10p; 1 way 8p; fig 8 stereo 15p per metre. 4 way individually screened 20p per metre.

### TWIN FIG 8 CABLE

Potlansed, 100 metre £4.50.

### MINI 3 CORE CIRCULAR CABLE, 19 x .10mm

Ideal for speakers, intercoms, telephones, etc £4.50 100m.

### ALL PRICES INCLUDE V.A.T.

### CARRIAGE EXTRA ON ALL ORDERS

Callers by appointment only

S.A.E. enquiries, lists

46 Kenilworth Road, Edgware, Middx HA8 5YG

Tel: 01-958 9314

## AN INTRODUCTION TO MICROCOMPUTERS

**VOL 0 - BEGINNERS BOOK** Price: £5.30  
written for the complete beginner explains what a computer system consists of - its component parts and what they can do for you.

**VOL I - BASIC CONCEPTS** Price: £5.30  
takes you by the hand from elementary logic and simple binary arithmetic, every aspect of microcomputers is covered.

**VOL II - SOME REAL PRODUCTS** Price: £10.80  
covers real microcomputers in considerable detail. Every major microcomputer 4 bit, 8 bit or 16 bit is described. More than 20 microcomputers in all.

**Z80 PROGRAMMING** Price: £5.30  
for logic design.

**8080A/8085** Price: £5.30  
Assembly language programming.

**6800 PROGRAMMING** Price: £5.30  
for logic design.

★ ALL PRICES INCLUDE POSTAGE ★


## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST  
of British and American Technical Books

19-21 PRAED STREET  
LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

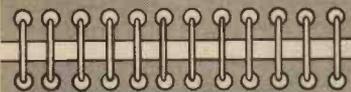

# INDUSTRY NOTEBOOK

By Nexus



## MATS

There's nothing quite like having a telephone in your car linked into the public network. Once a toy for the affluent it is now appealing to ordinary business people.

In the UK the service is manual. That is, you need to call up by radio from your car and an operator will connect you to the telephone number you want.

A big advance on this system is now appearing in the Middle East whereby you can dial the number directly from your car to any subscriber in the world who can be accessed through local or international STD. Similarly a fixed or mobile subscriber can call a remote mobile just by dialling his number and be connected automatically without operator intervention.

Cable & Wireless engineers have recently engineered such a system for Bahrain Telephones and the Mobile Automatic Telephone System (MATS) went into service on April 25 with a capacity of 50 mobile subscribers with facilities to expand the service to as many as 1,500 subscribers. A similar system has been operating in Qatar but the Bahrain system is said to use more advanced technology.

There seems to be an insatiable demand for communications in the whole of the Middle East. Bahrain, of course, is now emerging as a major business centre for the area, displacing Beirut where political problems and civil disturbances have forced many companies to look elsewhere for a secure operating base.

So great is the demand for communications and the ensuing business for equipment suppliers that Bahrain is to have its own communications exhibition and conference. It is called MECOM 79 and opens on April 23 next year. Organised by a British exhibition

company, it is sponsored by the Bahrain Ministry of Communications and Transport and also has the support of the PTT administrations of Saudi Arabia and Qatar.

The associated technical conference has the support of the Bahrain Society of Engineers and the British journal *Communications International*.

## COMMUNICATIONS 78

From looking forward we now look back on Communications 78 which, this year, moved from Brighton to Birmingham. I didn't welcome the move and I was not alone in preferring the civilised pleasures of Regency Brighton to those of Britain's second largest city. But arriving for the show on the first day it was quite obvious that the facilities at Brighton's Metropole exhibition centre could not have physically accommodated the enormous expansion since 1976.

So we suffered in silence in the courtesy coaches from the remote car parks to the exhibition hall and the ten-minute trudge in chilling gales from the hall to the conference centre, knowing it was in a good cause and finally dispelling any doubts that communications is the great growth area of this decade and, for that matter, decades ahead.

The event was a triumph for Tony Davies, the organiser, and his committee drawn from Government departments, the armed forces and from industry, right through from the inaugural luncheon graced by the Duke of Kent to the final attendance count of over 15,000 registered visitors from over 40 countries, more than twice as many as attended the 1976 event. The conference, too, broke all records with 825 registered delegates and proceedings which ran to more than 400 pages of condensed print.

Although not a direct result of the exhibition, some exciting contracts were announced at the same time. One was a multi-million pound contract from Saudi Arabia awarded to Cable and Wireless to equip the para-military Saudi National Guard with a communications system. The other was awarded to Marconi Space and Defence Systems who are to develop, in conjunction with Cincinatti Electronics, the next generation of v.h.f. mobile radio equipment for the United States Army, the Sincgars project.

Racal and Plessey were also in the bidding for the US Army contract, both with American partners. It was understood at one time that of all those bidding only one winner would be selected. In the event the Americans selected two winners (the other being ITT) and each will have to produce evaluation models for a final play-off to determine the ultimate winner who then gets the jackpot of orders which some observers estimate as being worth 500 million pounds.

Meanwhile the Ptarmigan tactical trunk communications system for the British Army is forging ahead with Plessey as main contractors. A Plessey spokesman told me that the project was on target both in performance and time-scale and, in fact, system hardware was on public show for the first time and is already in the hands of the users who describe the system as a "healthy bird". Project development started in 1973 on a seven-year time scale. Plessey also introduced two new military radios at the show, both private venture, claimed to fill gaps in the present Clansman range for military use.

## HANDS OFF!

When Racal Electronics Group purchased Milgo of Miami, Florida, last year they also bought some outstanding litigation which involved patent infringement against United Business Communications Inc. The company, wholly British-owned and re-named Racal-Milgo Inc., has received awards of about three million dollars by the US District Court in Kansas in court costs, damages and interest since 1972. Three patents were involved and the infringement, according to Senior Judge George Templar, was so serious that he ruled that Racal-Milgo were entitled to treble damages.

## INVESTMENT OVERSEAS

British companies, still nervous of industrial unrest, creeping nationalisation and inflation at home, are continuing to search for better returns overseas. Thorn, for example, has just bought two US companies, spending six million pounds in the process. Both will complement the Thorn Industrial Control Engineering Group. This at the time when Thorn was facing the prospect of strikes at the company's Yorkshire TV factories over proposed redundancies.

And, Racal, always on the look-out for acquisitions has gathered in California-based Vadic Corporation in the low-speed modem business and its first French company, Dana Electronics France SA. Vadic complements the high-speed modem business of Racal-Milgo giving Racal a complete modem product range, while Dana in France is the tail-end of the purchase of Dana Laboratories Inc. of California, the acquisition of which was announced last October.

Racal paid nearly 5.4 million pounds for Vadic Corporation (now to be known as Racal-Vadic Inc.) which has only 200 employees producing a profitable turnover of five million pounds per annum and expanding fast. This is a turnover of 25,000 pounds per employee representing a level of productivity which good business demands and expects, and it well illustrates the sinking labour content of modern electronic equipment.



# GENERAL PURPOSE TIMER

M. PLANT

## An accurate wide range timer with audio and visual alarms

THE electronic timer described here was developed to meet two requirements: the need for a general purpose twelve hour timer capable of switching on an external load (low voltage d.c. to 240V mains a.c.) at the end of preset time periods; and also capable of enabling a cine camera to take time lapse sequences so that observations could be made of growing plants, etc.

For the latter technique the timer is able to switch on a flood lamp at the end of a preset period and then to release a camera shutter while the subject is illuminated; the timer then resets itself automatically for another sequence.

The meeting of these two needs has resulted in a very versatile timer which has the following specification:

- (a) Mains or battery operation.
- (b) Battery operation provides a portable timer (with optional audio alarm) which can be used to switch on low voltage battery-operated equipment.
- (c) Mains operation provides, in addition to (b), triac control of mains powered loads up to 1,000W.
- (d) In both battery and mains modes of operation, "one shot" or "repeat" timing can be selected.
- (e) Two linked 12-way wafer switches select 11 delay periods of 1 hour and 11 delay periods of 5 minutes giving a maximum delay of 11 hours 55 minutes in 121 intervals of 5 minutes.
- (f) A range switch divides the above intervals by factors of 10, 100 and 500 giving, on the "1 hour" wafer switch, intervals of 6 minutes, 36 seconds and 7.2 seconds respectively; and on the "5 minutes" wafer switch intervals of 30 seconds, 3 seconds and 0.6 seconds, respectively.
- (g) When the timer is operated from the mains and is in the "repeat" mode, the triac drive circuitry can be used to switch on a flood lamp (max 1,000W) for 2.5 seconds. During this period, a low voltage pulse is available of about 0.5 seconds duration for driving

a solenoid to operate a camera shutter. The lamp then goes out with the timer having already set itself for another cycle. In the "one shot" mode, once mains switching is initiated the load remains energised.

- (h) Repeatability of any time intervals is to within 0.01 per cent but the accuracy of the preselected intervals depends on the care with which the constructor selects the values of 22 resistors and 3 capacitors and upon the stability of these components.

## CIRCUIT OPERATION

The complete circuit diagram of the unit is shown in Fig. 1. IC1 is a precision digital timer which makes use of an "on chip" oscillator the frequency of which is set by an externally connected CR network. Pulses from this oscillator are fed through a twelve stage binary counter which switches the output stage after 1,095 counts.

Timing is started by closing S4 to provide power to the timer, the time period being set by the values of R22 to R32 and R33 to R43 which are in series and selected by the wafer switches S5 and S6, and the values of the capacitors C6, C7 or C8 selected by S7. This CR combination across pins 13 and 14 sets the frequency of the internal oscillator which times out after a time T given by  $T=2736 CR$ .

During the count down period, pin 3 of IC1 is high, allowing D2 to light. At the end of the count down, output pin 2 goes "high" and pin 3 goes "low": D2 goes out and TR1 is switched on. What happens subsequently depends upon the settings of the various switches.

Firstly, if S1a is open, the voltage at pin 3 stays "low" and TR1 remains switched on: if S1a is closed, R2 and C5 ensure that the timer automatically resets after about one second via the trigger of IC1 (pin 1). The period "t" before resetting takes place is given by  $t = 0.6 R2 C5$ , approximately.

If S3 is closed, the audio alarm signal of IC2 is switched on

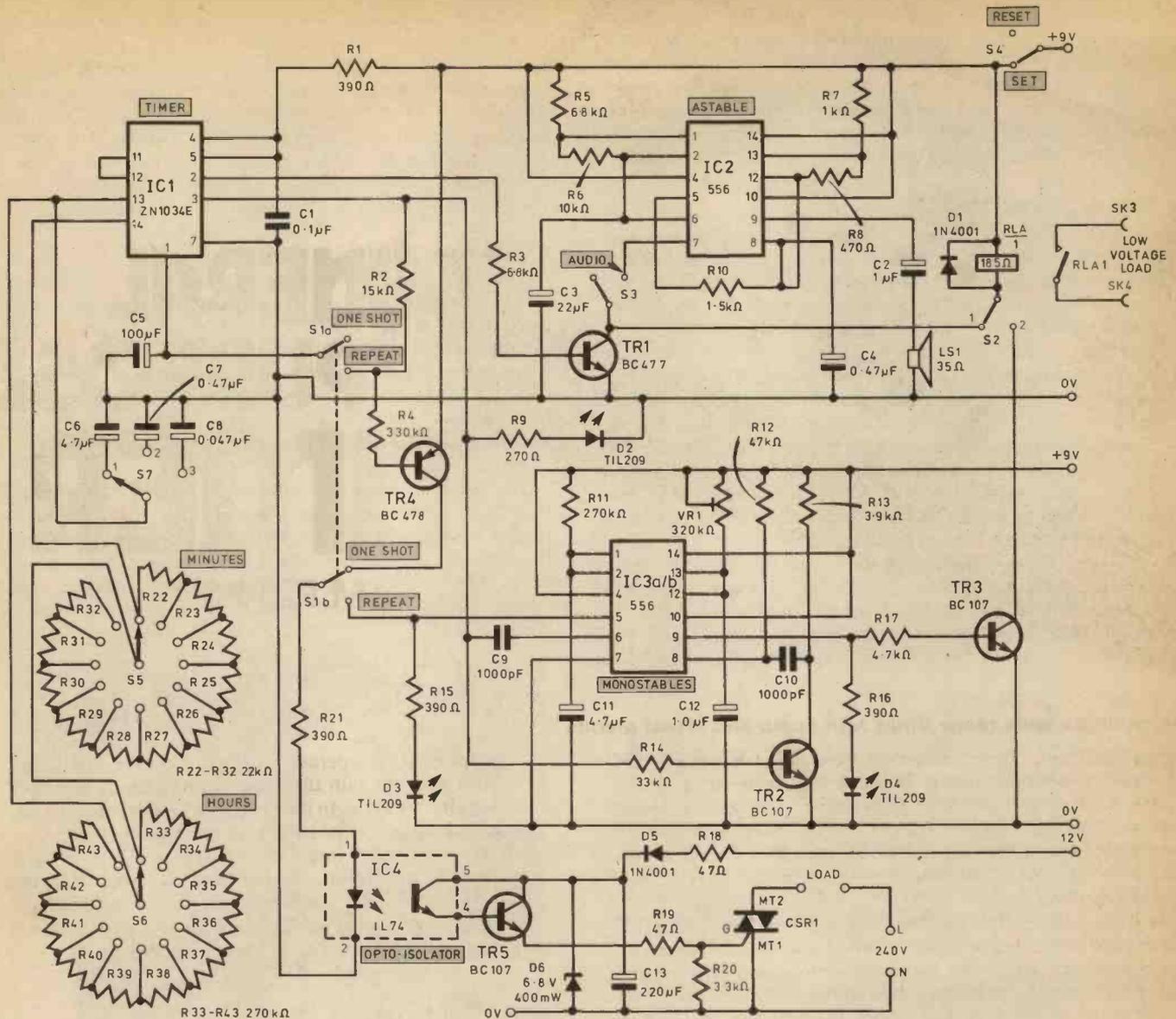


Fig. 1. Circuit diagram of the General Purpose Timer

whilst TR1 is on. This dual "555" timer (IC2) is operated as a dual astable multivibrator which is d.c.-connected via R10 so as to produce a repeated "pip" from the speaker. With or without S3 closed, transistor TR1 can energise relay RLA if S2 is in position 1. In the "one shot" mode, RLA remains energised and can be used to switch on a low voltage load (not mains) for an indefinite period at the end of the timing period. In the "repeat" mode, TR1 is energised for about one second so the alarm and RLA are energised briefly at the end of the time period.

If S2 is in position 2, RLA is energised via a positive pulse appearing at pin 9 of IC3. Once again a dual "555" timer integrated circuit is used for IC3 but each individual timer is wired as a monostable multivibrator. These two monostables are arranged to be triggered one after the other by the square wave pulse appearing at pin 3 of IC1 when operating in the "repeat" mode. But the trigger pins 6 and 8 of IC3 require negative-going trigger pulses via capacitors C9 and C10, respectively, in order to initiate delays determined by the values of R11/C11 and VR1/C12 respectively.

When the voltage at pin 3 of IC1 rapidly goes negative at the end of the timing period, monostable IC3a is triggered for a period of about 2.5 seconds; this negative going pulse keeps transistor TR2 turned off allowing pin 8 to remain "high" via R12. However, if IC1 is in the "repeat" mode, one second after IC3a has been triggered pin 3 goes "high" once again for another timing period "T".

This rapidly rising positive voltage switches on TR2 so that the sharp rise in current through R13 provides the required negative pulse at the collector of TR2 which, applied to pin 8 by C10, triggers the second monostable IC3b. Thus a positive pulse of about  $\frac{1}{2}$  second duration appears at pin 9 approximately one second after the positive pulse has appeared at pin 5.

The "on" states of the monostables are indicated by diodes D3 and D4. Transistor TR3 enables RLA to be energised for about 0.5 second if required so that its normally open contacts can be used for providing solenoid drive for a camera release button.

Note that RLA can be energised by either the positive

pulse from IC1 pin 2 (for one second or for an indefinite period at the end of the timing period depending upon the position of S1), or by the positive pulse at pin 9 of IC3b thereby not being energised when IC1 is operating in the "one shot" mode or for one second after IC1 has timed out if in the "repeat" mode. This latter pulse lasts only long enough to provide camera shutter drive through a solenoid.

### TRIAC OPERATION

Whether the triac provides switching for a mains load over an indefinite period or for about 2.5 seconds at the end of the timing period depends on the position of S1b. In the "repeat" mode, S1b directs the 2.5 second pulse from pin 5 of IC3a to the opto-isolator IC4 to energise the load.

At the end of this period the triac automatically switches off this a.c. load. In the "one shot" mode, S1b directs the negative going pulse from IC1 (pin 3) to pin 1 of IC4 (after inversion by TR4) in order to switch on the load for an indefinite period. Transistor TR4 was found necessary to ensure that pin 3 was not too heavily loaded for this caused erratic operation of IC1 in the "repeat" mode. Note that TR4 is base biased by R4 just sufficient for its collector current to bring on the internal l.e.d. of IC4.

The one shot operation of the timer means that mains operated appliances can be switched on after any one of the preselected time periods up to a maximum of 11 hours 55 minutes. The mains load can be switched off using either the "set/reset" switch or, of course, by switching off the mains.

### AUDIO ALARM

This can be switched in and out by means of S3 and is based on IC2; it can be operated in both the mains and battery modes. In the "repeat" mode operation of timer IC1, a one second burst of "pips" is heard at the end of each delay period. In the "one shot" mode the pips sound continuously until the timer is switched off.

The alarm will work on battery or mains; care should be taken to ensure that, when the timer is operated using a battery, it does not become discharged during long preset delay periods.

### POWER SUPPLY

The circuit diagram of the p.s.u. is shown in Fig. 2. Switch S8 selects mains or battery operation. Approximately 9V is derived from the mains using one winding of the transformer

and the bridge rectifier (D8 to D11). This voltage is stabilised by the Darlington series regulator.

The other winding provides the supply for TR5 on the triac drive board and for the internal phototransistor of IC4. The 12V a.c. from the transformer is rectified by D5 before being applied to the collector of TR5. The Zener diode D6 and the electrolytic capacitor C13 ensure that the voltage is sufficiently steady for reliable operation of the triac. It is the rising emitter voltage of TR5 which switches on the triac.

### CONSTRUCTION

Three pieces of 0.1 inch matrix stripboard were used for the circuit assembly: the main timer board, the triac drive board and the low voltage board. The component layouts for these boards are shown in Figs. 3, 4 and 5. All external connecting wires to the boards should be made longer than required and then cut to the correct length prior to being soldered to the l.e.d.s and switches. Note that the l.e.d.s have polarised leads and care should be taken to ensure correct connection to the circuit board.

The timer was housed in a polystyrene case with a sloping front panel. The aluminium panel was removed and replaced by a polystyrene one to avoid the necessity of having to earth it although no mains connection is made to this panel. The stripboard circuit of the timer is attached to this control panel by stand-off studding to clear the switches and the l.e.d.s, etc.

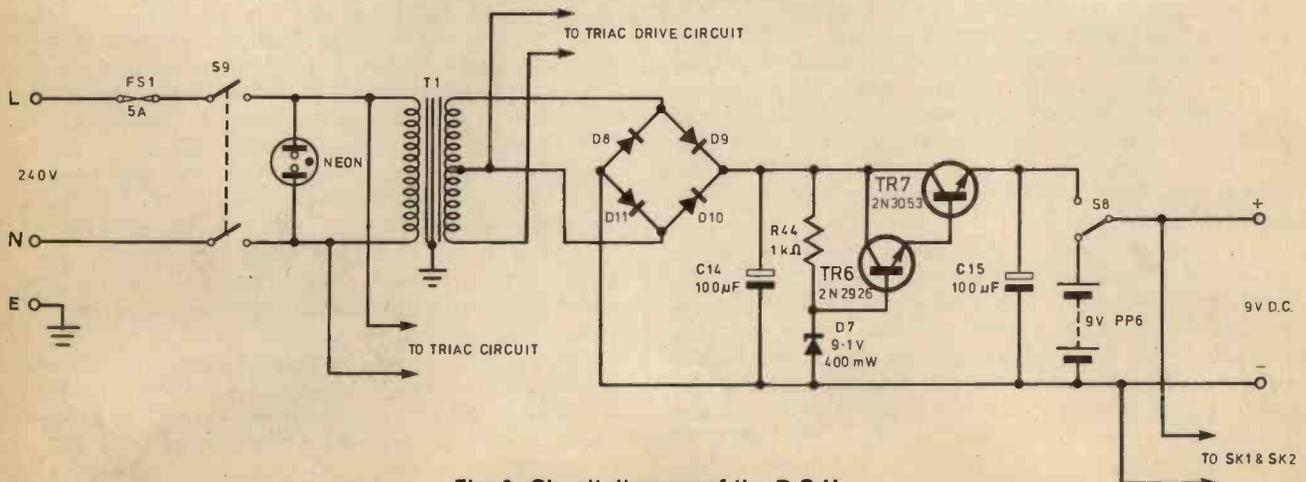
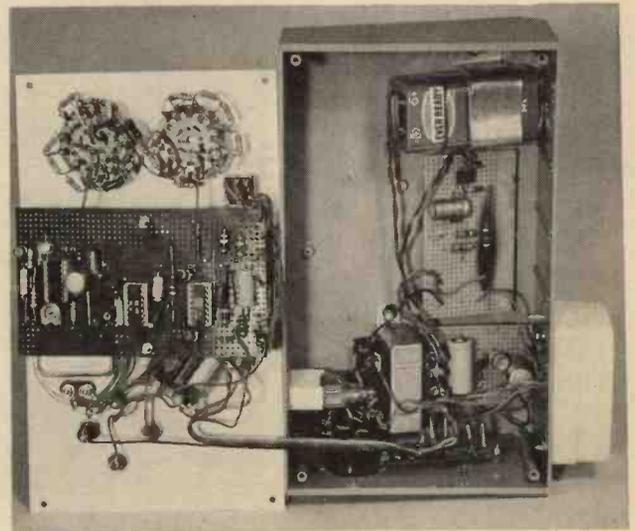


Fig. 2. Circuit diagram of the P.S.U.

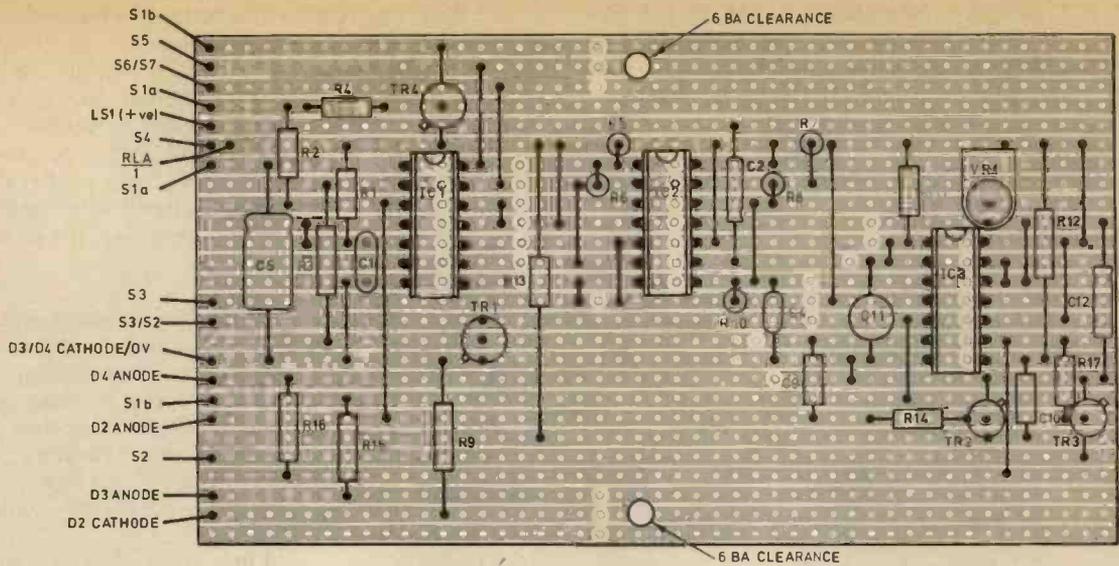


Fig. 3. Main timer board layout

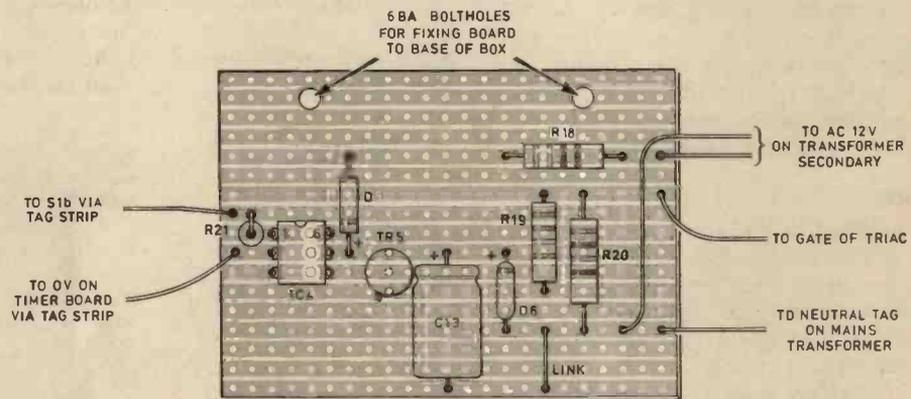


Fig. 4. Triac drive board layout

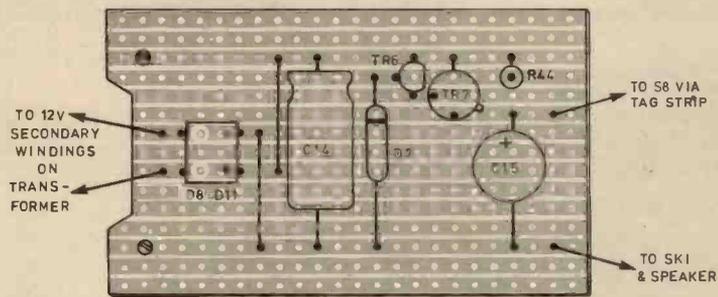


Fig. 5. Low voltage board layout

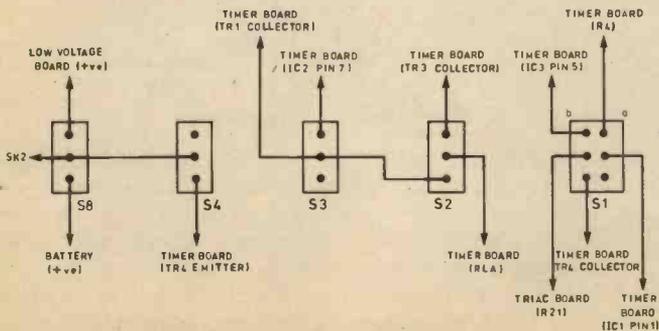


Fig. 6. Wiring of the front panel switches



## COMPONENTS . . .

### Resistors

R1, R15, R16, R21	390Ω (4 off)
R2	15kΩ
R3, R5	6.8kΩ (2 off)
R4	330kΩ
R6	10kΩ
R7	1kΩ
R8	470Ω
R9	270Ω
R10	1.5kΩ
R11	270kΩ
R12	47kΩ
R13	3.9kΩ
R14	33kΩ
R17	4.7kΩ
R18, R19	47Ω (2 off)
R20	3.3kΩ
R22-R32	22kΩ (11 off) ½W 2% metal oxide
R33-R43	270kΩ (11 off) ½W 2% metal oxide
R44	1kΩ ½W 10% carbon
All resistors ½W 5% carbon except where stated	

### Potentiometers

VR1	220kΩ preset
-----	--------------

### Capacitors

C1	0.1μF polyester
C2, C12	1μF 25V tant. (2 off)
C3	22μF 25V tant.
C4	0.47μF 25V tant.
C5	100μF 25V tant.
C6	4.7μF polyester
C7	0.47μF polyester
C8	0.047μF polyester
C9, C10	1,000pF polystyrene (2 off)
C11	4.7μF 25V tant.
C13	220μF 25V elect.
C14, C15	100μF 25V elect. (2 off)

### Semiconductors


D1, D5	1N4001 (2 off)
D2, D4	TIL209 l.e.d. red (2 off)
D3	TIL209 l.e.d. green
D6	6.8V Zener (400mW)
D7	9.1V Zener (400mW)
D8, D9, D10, D11	Bridge rectifier 0.9A R.S. type 261-772
TR1	BC107
TR2, TR3, TR5	BC107 (3 off)
TR4	BC478
TR6	2N2926
TR7	2N3053
IC1	ZN1034E
IC2, IC3	556 (2 off)
IC4	IL74 Opto-isolator
CSR1	Triac 8A 400V R.S. type 261-801

### Switches

S1	D.P.D.T. sub min toggle
S2, S3, S4, S8	S.P.D.T. sub min toggle (4 off)
S5, S6	12 way rotary type
S7	4 way rotary type
S9	D.P.D.T. 5A toggle

### Miscellaneous

1 off	Moulded case 216 × 130 × 79mm
4 off	4mm socket
1 off	13A socket
1 off	Neon indicator
3 off	Pointer knobs
1 off	Relay 12V 185Ω
1 off	Mains 5A plug and socket (round type)
1 off	Transformer 12-0-12V 0.5A
1 off	Speaker 35Ω
1 off	PP6 battery
1 off	Chassis mounted fuse holder
1 off	Battery clip
1 off	Veroboard
1 off	6 way barrier strip
1 off	Holders for i.c.s

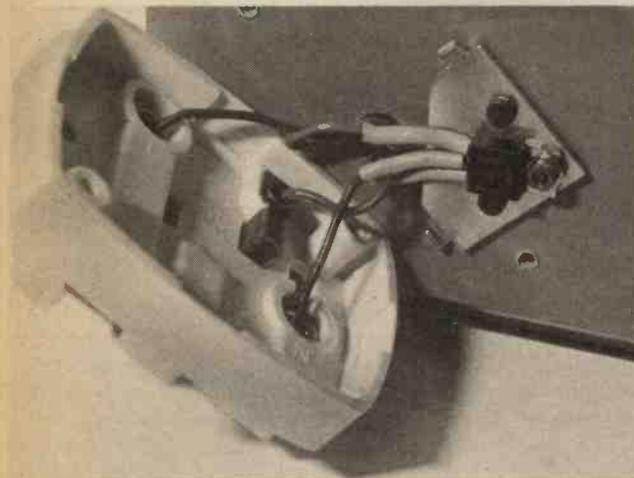

A solder tag attached to one of the terminals of the speaker is used as a common low voltage negative connection. The wiring of the switches S1, S2, S3, S4 and S8 is shown in Fig. 6.

The triac drive board is bolted to the bottom of the box adjacent to the low voltage board. The component layouts in Figs. 5 and 6 show the external connections which are to be

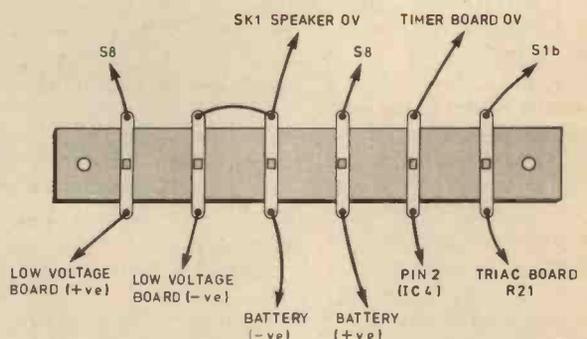


Fig. 7. Barrier strip wiring

made to these two boards. These connections should not be made to the timer board until the latter has been tested.


The mains switch (S9) is mounted on the front of the box and isolates both live and neutral wires when off. Also, with the switching arrangements employed, the battery may be switched in by S8 to control timing functions and to provide triac drive whilst mains loads are switched via the triac.

The triac was mounted inside the base of the surface

mounted 13A load socket on a small piece of aluminium which acted as a heat sink.

In order to facilitate the fitting and removal of the control panel, a six-way length of barrier strip was bolted to the side of the timer box adjacent to the transformer. In this way the wires from the control panel can be routed neatly to the power supply circuits and the triac control panel. The leads requiring connections to this barrier strip are shown in Fig. 7.

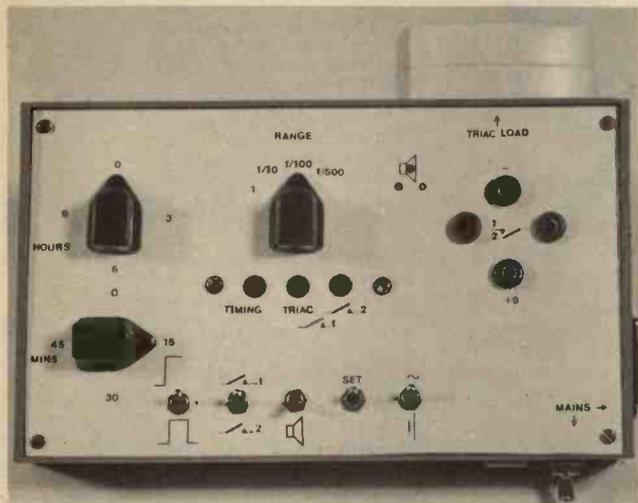The mains connection to the unit should be made via a 3 pin non-reversible plug and socket. In the prototype the plug was fitted in the side of the case near the mains switch.



### SETTING UP AND TESTING

When the timer board has been assembled and mounted on the control panel and before connections are made to the low voltage and triac drive boards, the timer circuit can be connected to the 9V battery and tested. Switch S8 should be in the "battery" position and the audio alarm switch S3 "on". Set switch S5 (the "hours" switch) to zero and S6 (the "minutes" switch) to 5 minutes—the first position clockwise.

The range divider switch S7 should be set to divide this 5 minute period by a factor of 100. Now operate the "set/reset" switch to provide power to the timer circuit and the green l.e.d. (D2) should light and go out after 5 minutes  $\times$  60/100 seconds or 3 seconds. Immediately the l.e.d. goes out indicating the end of the timing period, the audio alarm should sound and the red l.e.d. (D3) should light up for about 2.5 seconds before going out.

What happens after this sequence depends on the setting of S1. With S1 in the "repeat" mode, D2 will relight about 1 second after it has gone out at the end of the timing period, i.e. the timer has reset itself for another delay period; and the audio alarm stops. As soon as D2 relights, D4 lights briefly indicating that a solenoid can be operated to drive a camera button if S2 is in position 2.

This sequence of switching will repeat every 3 seconds but can be altered to any other delay period as described at the beginning of this article. With S1a in the "one shot" mode, D2 will go out and stay out, D3 will come on for 2.5 seconds and go out but D4 will not light.

Simultaneously with the above sequences, the low voltage relay will be heard to operate. With S2 in position 1 and S1a in the "repeat" position, the relay will energise as D2 goes out at the end of the delay period (closing the contacts of the relay) and de-energise as D2 comes on again: the relay energises for about one second at the end of every delay period.

With S2 in position 2 and S1a in the "repeat" mode, the relay energises for the time S3 is alight thus providing automatic switching for a camera shutter drive. With S1a in the "one shot" mode, and S2 in position 1 the relay will energise at the end of the time and remain energised.

If S2 is in position 2 the relay will not energise and TR2 will not be switched on since the monostable based on IC3a is not triggered. These sequences are summarised in Table 1.

The low voltage board should be checked to see the voltage available from the circuit is about 9.0V. If it is, the leads from this circuit board can be connected to the timer board

SWITCH S1a	SWITCH S2	RELAY RLA
"Repeat"	Position 1	"On" at end of delay period (D2 goes out)  "Off" one second later as timer resets (D2 comes on)
"Repeat"	Position 2	"On" as D4 lights  "Off" as D4 goes out
"One shot"	Position 1	"On" at end of delay period and stays on
"One shot"	Position 2	Does not energise

Table 1. Relay operation for the different switching sequences of S1a and S2

via the barrier strip, the negative lead to the solder tag on the speaker and positive lead via switch S8 to the timer board. The whole sequence of timing operations described in Table 1 can also now be checked for correct operation from the mains.


Finally the triac drive board should be tested. The lead from S1b should be connected to R21 on the triac drive board and the lead from pin 7 of IC1 on the main timer board to the 0V line and pin 2 of IC4 in the triac drive board also to the 0V line. With the timer being operated from the battery, check that the opto-isolator is working as follows. Set the timer to operate in the "repeat" mode every 9 seconds, say. Use a multimeter set to the "Ohms  $\times$  1k" range and connect the black lead to pin 5 of the IC4 and the red lead to pin 4 of the same i.c.

Now every time monostable IC3a is triggered and D3 lights the resistance between these two terminals will fall to a low value. This connection is actually across the collector-emitter connections of the internal phototransistor of the opto-isolator, and when the resistance between these connections falls it indicates that it is receiving light from the internal diode.

The energising of this phototransistor switches on TR5 and the triac when the triac drive board is connected to the mains. Now switch S1b to the "one shot" position and note that the resistance across pins 4 and 5 of IC4 falls at the end of the delay period and remains low. If all is well the triac drive board can be wired to the neutral and the 3 pin load socket.

★

# INGENUITY UNLIMITED

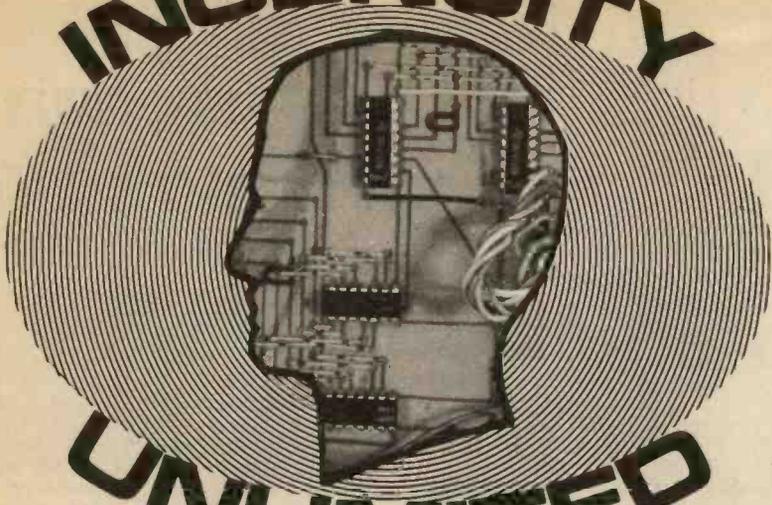

A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit *your* idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

WHEN working with digital systems, the designer often has need of a cheap TTL compatible PROM. One very interesting device released is the 256x4 bit DM8574 by National Semiconductors Ltd. This i.c., with the exception of certain drive requirements, is pin for pin compatible with the popular 16 pin d.i.l. 2112 256x4 bit RAM, whose R/W pin is replaced by a CE input on the PROM. It is therefore quite simple to design a general purpose memory board for most micro-processor systems which mixes RAM and ROM in any combination on the same printed circuit board.

The only problem with the use of PROM is the need for a device programmer. Fortunately, the DM8574 is a "Field Programmable" device of the fusible link variety and a simple programmer can be constructed as shown.

The PROM may be programmed by supplying a single 5V supply to the device and selecting the address of the 4 bit word which is to have some of its fusible links blown. (Blowing a link creates a logical zero at the bit address selected; leaving the link unblown leaves a logical one at that position). A logical one is then applied to both the enable inputs, and the programming pulse (see figure) is fed to the output where a low level is required. Verification that the bit has been programmed may be obtained by bringing the enable inputs low and checking the logical level at the appropriate output.

The programmer utilises a 555 timer working from a 15V supply derived from a split 30V supply so that when the 555 output goes high the base of the BC108, whose emitter potential is held at 24V, is driven

hard on, causing some 70mA to flow from its output. The 555 is arranged to provide a 1kHz 50% duty cycle square wave at its output when pin 4 on this i.c. is brought high by pressing the "PROGRAM" push-button, this output then being used as explained to drive the BC108 when programming the PROM bit-by-bit as explained.

Microcomputer addicts might like to consider the possibility of automating the programming sequence in order to provide a quick and easy way of obtaining custom-programmed ROM chips suitable for inclusion in their system.

J. A. Murdie,  
Darlington,  
Durham.



## PROM PROGRAMMER


*Fact sheet S+8*

*Room 8007*

*New Broadbent*

*Mandates*

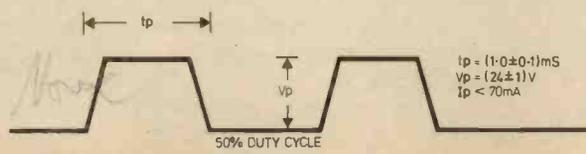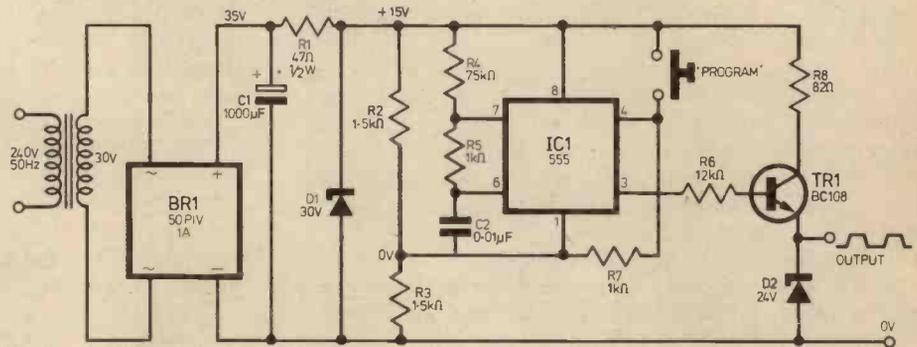

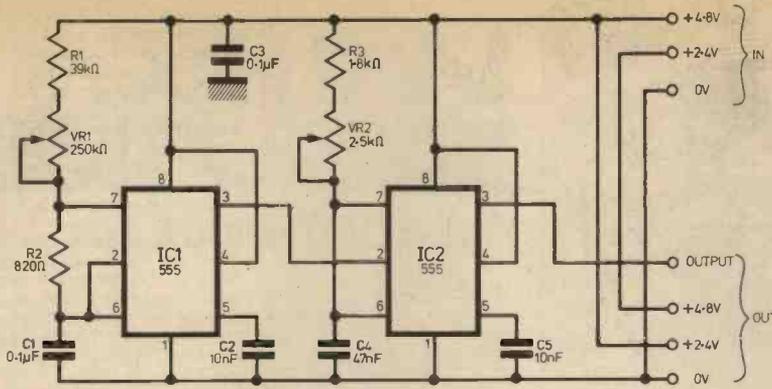

## RADIO CONTROL SERVO TESTER

THE servo mechanisms currently used in radio controlled models use a variable width pulse to convey the information concerning the required position. This pulse has been standardised as varying between 1-2ms and is nearly always positive going. Most receivers and decoders use 4.8V or 6V batteries and the amplitude of the pulse is almost equal to the supply voltage.

The information for each channel of a multi-channel system is transmitted sequentially, followed by a synchronising pulse to maintain lock between receiver and transmitter. Models using several channels are commonplace; aircraft often use six.

When setting up the control systems in a model, it is usual to have to use the transmitter and receiver together. This can be inconvenient especially at a flying field where spurious signals are most definitely not wanted! This

servo tester overcomes the need for using all the gear just to test one function by simulating the decoder output for one channel only. It is simply connected between the battery and the required servo. The pulse width is adjustable over the full range, and the repetition rate may be set for any number of channels, although this is not really necessary and this adjustment may be omitted. (Servos work in equipment of one to seven channels without adjustment, and the variable rate function was built in when servos were being designed, purely to check this fact.)

The circuit consists of an NE555 wired as an astable pulse generator, producing narrow, negative going spikes at a repetition rate of between 3 and 20 ms. A good compromise, to eliminate one adjustment, would be 10 ms. This is achieved by replacing R1 and VR1 with 100kΩ. The narrow

pulses produced trigger a second 555 wired as a monostable, the duration of which is adjustable between 1 and 2ms. The internal design of the 555 is such that varying battery voltages do not affect pulse width so that the circuit will work from 4 to 15V supplies.

The output pulse is almost as great as the supply voltage.

Both circuits are assembled on commercially available circuit boards. It is not necessary to calibrate the device, the central position of the width control potentiometer will be very close to 1.5ms, the mid-range value. It may be checked against a new servo; here the end positions should be at the limits of useable travel, usually  $\pm 45^\circ$ . The centre tap from the battery is not necessary for the working of the device, and is included as some of the older servos require it.

A. Langton,  
Aberdeen.


## OVERFLOW INDICATOR

GATES IC1a and IC1b form a pulse generator. C1 determines the frequency of the pulses, and the value of this should lie between 10μF and 50μF, the larger the value the longer

the duration of tone. Gates IC1c and d together form a multivibrator to produce the required tone. The multivibrator is controlled by the pulse generator through pin 13, so when the

generator is not producing pulses, no tone is heard from the transducer. TR1 forms the switch that is required to control the pulse generator. When water or any conductive liquid bridges the sensor probes, bleeps are heard from the earpiece.


V. J. Guillaumier, Malta.

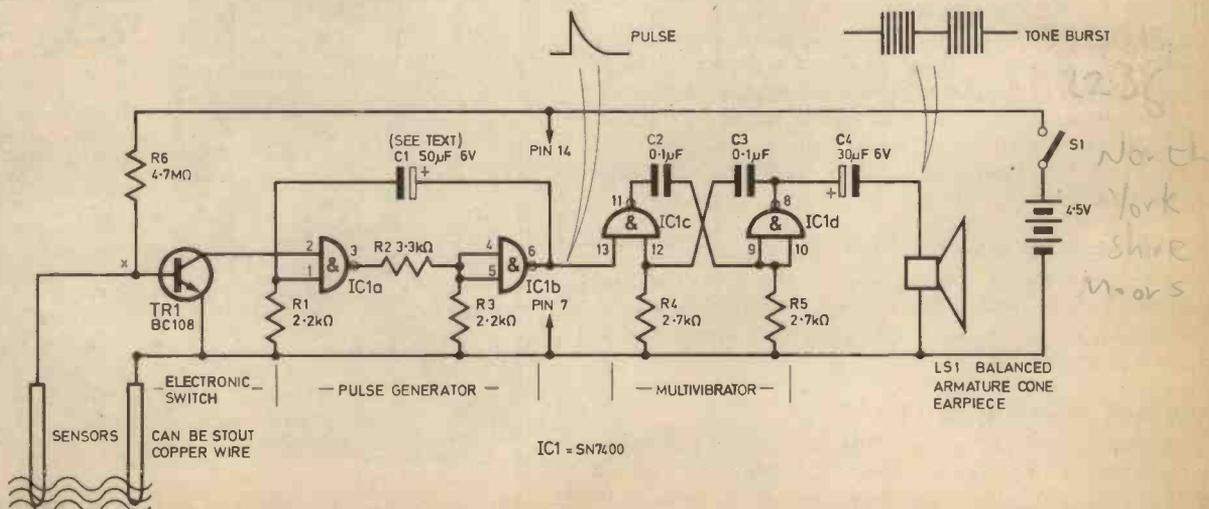

# PE STRING ENSEMBLE

A.J. BOOTHMAN B.Sc.

## Part 5

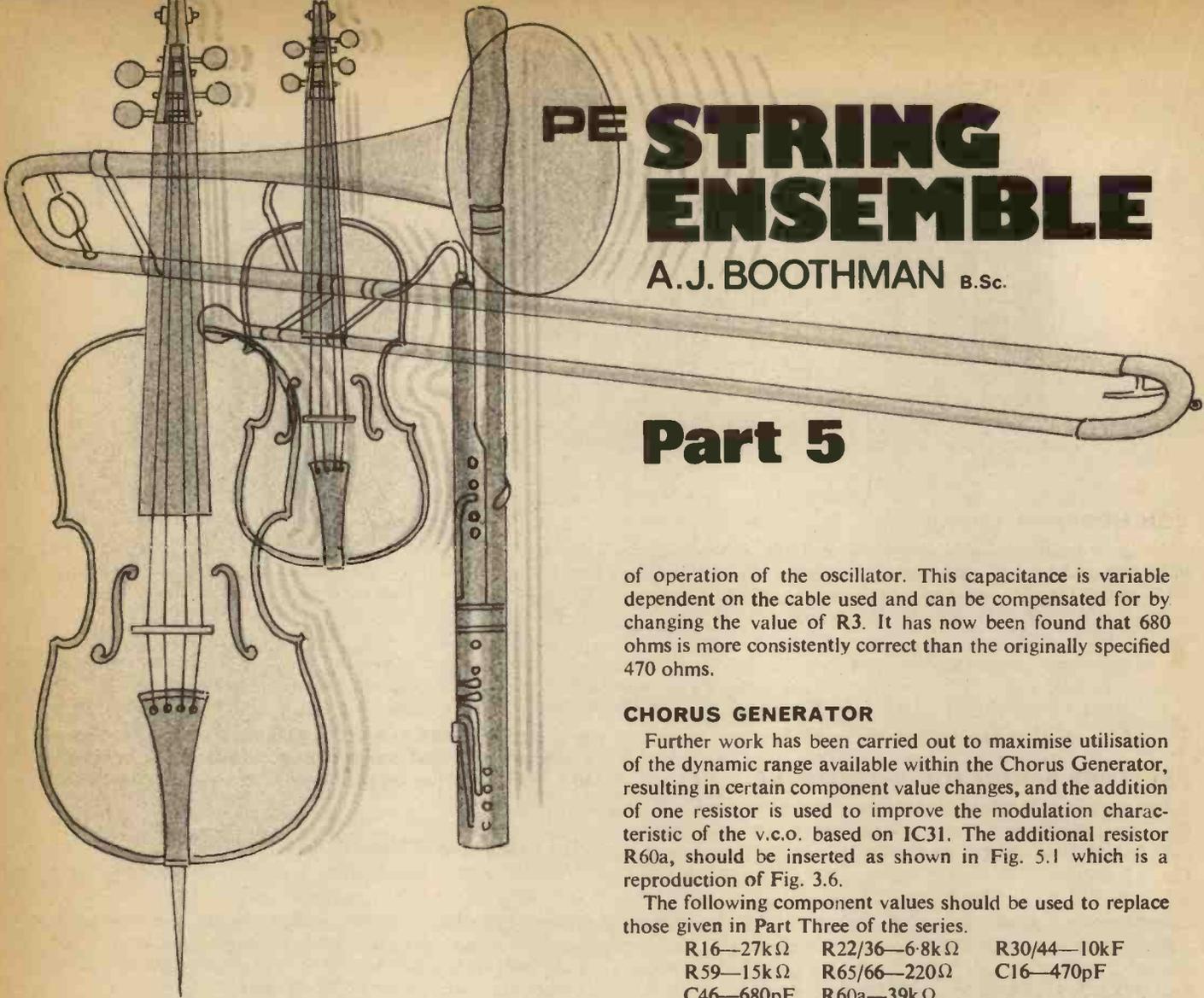

of operation of the oscillator. This capacitance is variable depending on the cable used and can be compensated for by changing the value of R3. It has now been found that 680 ohms is more consistently correct than the originally specified 470 ohms.

### CHORUS GENERATOR

Further work has been carried out to maximise utilisation of the dynamic range available within the Chorus Generator, resulting in certain component value changes, and the addition of one resistor is used to improve the modulation characteristic of the v.c.o. based on IC31. The additional resistor R60a, should be inserted as shown in Fig. 5.1 which is a reproduction of Fig. 3.6.

The following component values should be used to replace those given in Part Three of the series.

R16—27k $\Omega$	R22/36—6.8k $\Omega$	R30/44—10kF
R59—15k $\Omega$	R65/66—220 $\Omega$	C16—470pF
C46—680pF	R60a—39k $\Omega$	

**T**HE final part of the series gives details of the cabinet construction, a number of component value changes for improved optimum results, and further interwiring information and clarification.

### CABINET CONSTRUCTION

The component parts for the cabinet are given in the cutting list with assembly details shown in Fig. 5.2. Some variation in dimensions may be required to suit alternative keyboards, but the construction has been kept simple for ease of adaptability. Corner joints can be made from short lengths of  $\frac{3}{8} \times \frac{3}{8}$  in (15.875  $\times$  15.875mm) timber, screwing from the inside of the cabinet.

### IMPROVEMENTS ON PROTOTYPE

Since commencement of publication of this series the construction of further models has resulted in information from which certain component value changes are recommended to give the best results.

### TONE GENERATOR/PSU

Connections from the p.c.b. to the front panel transposer switch and the tuning potentiometer are made with screened cable (see Fig 5.2), and the capacitance of the cable contributes to the capacitance C8 which determines the frequency


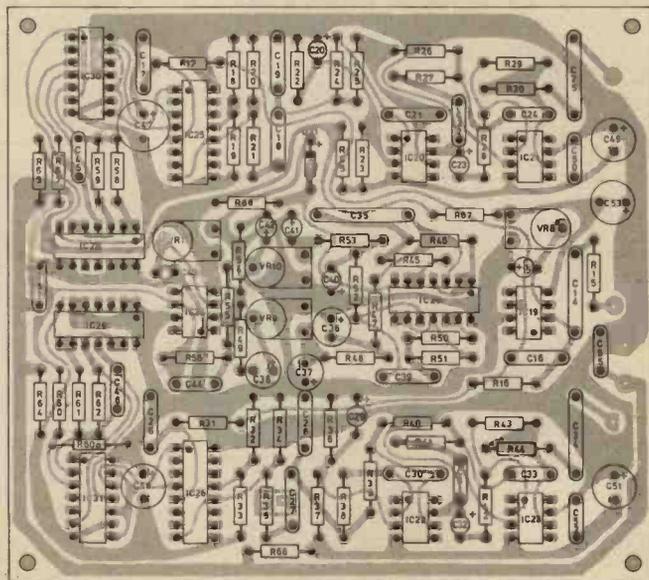


Fig. 5.1. Showing position of additional resistor on chorus p.c.b. Orientation of the i.c.s is also given

SUB-PANEL

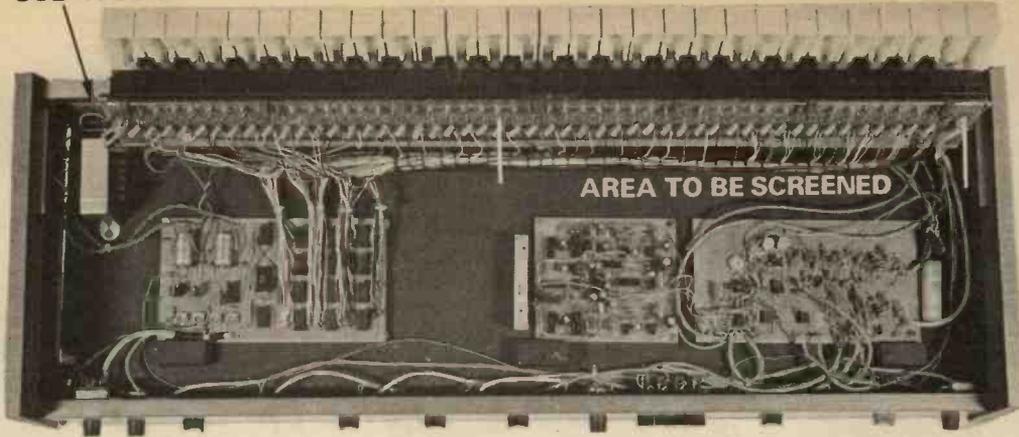

### VOICE/PREAMP CIRCUITRY

Noise contribution from the Woodwind and Brass filters has been reduced to negligible proportions by replacing R107 and R116 with shorting links, removing C76 and C83 and connecting  $1M\Omega$  resistors across pins 2 and 6 of ICs 33 and 34.

The following components on this figure should also be changed as follows:

- R124— $150k\Omega$ , R131— $470k\Omega$ , R135— $68k\Omega$
- C81— $47nF$ , C88— $47nF$ , C101— $220pF$

### PSU/TONE GENERATOR INTERWIRING

Last month an interwiring diagram (Fig. 4.6) was given for the Chorus Generator and Voice/Preamplifier p.c.b., which included details of most of the front panel control connections. Fig. 5.2 shows the wiring for the remaining controls, which are connected to the P.S.U./Tone Generator p.c.b., and the mains input sub-panel.

The sub-panel is mounted at the rear of the cabinet, at the top left-hand end (see photo) and contains the mains switch, fuse and socket which are wired to the mains transformer as shown. Earth leads are also required both to the keyboard chassis and  $0V$  pin on the Voice/Preamplifier p.c.b.

Low voltage a.c. connections are made in pairs between the transformer and the p.c.b. supplies  $+15V$ ,  $0V$ , and  $-15V$  are taken direct to the Voice Board, and can be routed behind the key bar to avoid entanglement with the Tone Generator output leads.

Connections to D13 on the front panel are shown, the polarity being indicated by the "flat" on the skirt of the l.e.d. The lead adjacent to the flat should be wired to the l.e.d. pin on the p.c.b. D13 is fitted adjacent to the pitch control. The  $20V$  supply is wired to Attack and Sustain Controls as shown in the diagram and connections are made to the keyswitch rod and sustain line on the Diode Gate assembly from these controls.

### TRANSPOSER/TUNING CONNECTIONS

A four core screened cable is used to connect the Tone Generator p.c.b. to the Transposer Switch, the screen is connected to the ground terminal on the p.c.b., but not to the switch. A single wire link should be connected between the switch and tuning potentiometer VR5, and a screened cable between the potentiometer and the p.c.b.

In this case the screen should be soldered to the p.c.b. at one end and the body of the potentiometer at the other end.

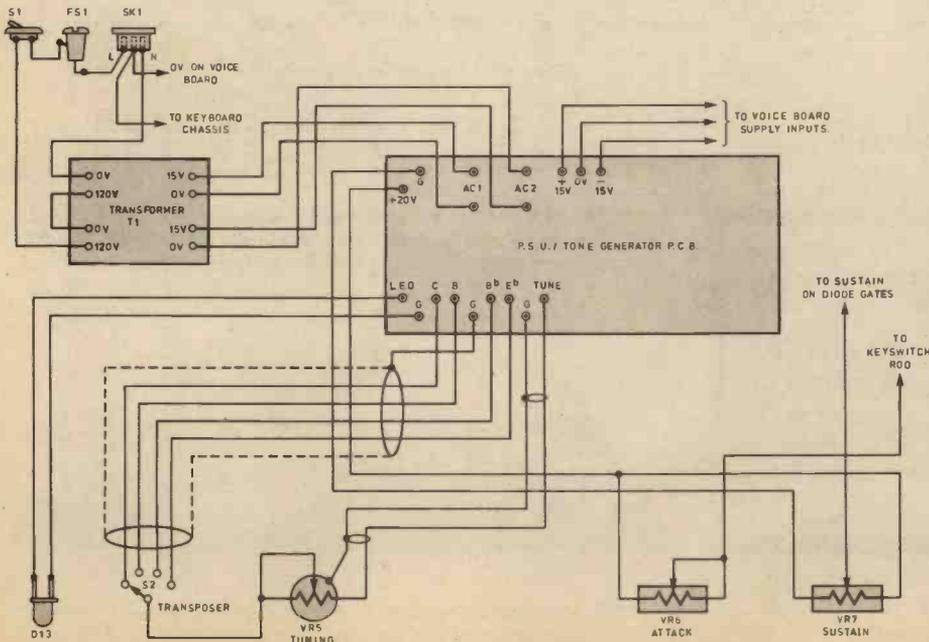


Fig. 5.2. Interwiring of P.S.U./Tone Generator to controls

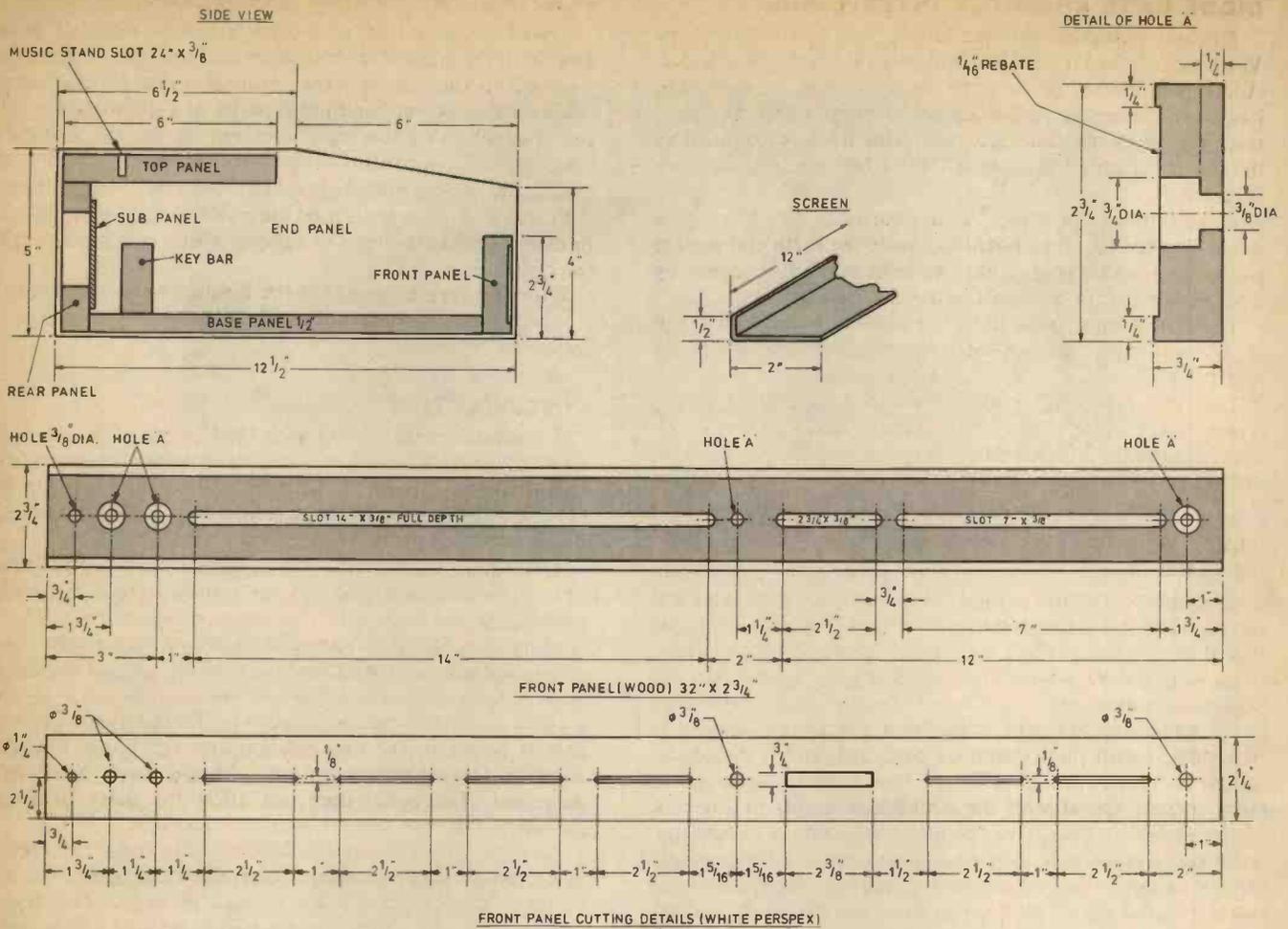


Fig. 5.3. Cutting details of casing and fascia

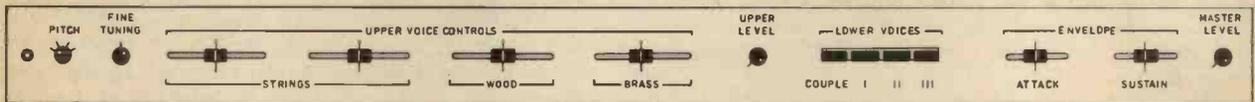


Fig. 5.4. (Above) Showing fascia legends. (Below) Showing rear panel and attached sub-panels. Right is for mains input and left for output sockets

**CUTTING LIST**

End Panels	(2 off)	12½ in × 5 in × ½ in Veneered
Base Panel		32 in × 10½ in × ½ in Chipboard
Rear Panel		32 in × 3½ in × ½ in Veneered
Front Panel		32 in × 2½ in × ½ in Veneered
Top Panel		32 in × 6 in × ½ in Veneered
Key Bar		22 in × 1½ in × ½ in Timber
Sub-Panels	(2 off)	4 in × 3 in × ½ in Plywood
Keyboard Ends	(2 off)	To suit Keyboard
Metal Screen		12 in × 2½ in Bent as shown in (Fig. 5.3)

Sub-Panels are mounted against 2 in holes in Rear Panel

## DIODE GATE ASSEMBLY INTERWIRING

The interwiring between the Diode Gate assembly and the Voice Board, Sustain control and earth is shown in Fig. 5.2. A lead is connected between the point at which the earth lead has been connected to the keyboard chassis and the earth track on the Diode Gate assembly. This track is identified as the one to which all capacitors C13 (4.7 $\mu$ F electrolytics), are soldered.

In assembling the Diode Gate boards earlier, links were made between the three boards to make the earth and sustain tracks continuous (Fig. 2.6). The sustain track is joined by a single wire to the Sustain Control VR7.

The four output track links are made between PCB2 and PCB3 only since the keyboard split occurs between PCB1 and PCB2.

Low and high output groups are each connected to the Voice Board using a four-core screen cable, with the screen connected at the Voice Board end only. The low output cable should be routed behind the key bar.

## GATE ASSEMBLY—TONE GENERATOR WIRING

The interconnection pattern for the Diode Gate p.c.b.s was given in Fig. 2.8 in the second part of the series. This illustrated the three p.c.b.s, making up a single assembly, with arrows indicating the 85 points at which leads are taken from the Diode Gate assembly to the Tone Generator board. The track leads associated with the connection points can be seen in the single board photograph on page 596, and if the photograph is turned through 180° the four rows of leads can be seen to correspond with the connection points in Fig. 2.8. As described in Part Two the interconnection is carried out with easily solderable insulated copper wire; a single length acting as both the interconnecting wire on the Diode Gate assembly and the flying lead to the Tone Generator board.

In Fig. 2.8 the numbers in circles (1-8) correspond with the numbers on the outputs of IC7-18 (1-8) on the Tone Generator p.c.b. shown in Fig. 1.7 in the First Part of the series.

Each arrow represents a lead back to the Tone Generator with the note identified by checking the vertical correlation with the letters below the arrows and the circled number under the row concerned. On the left-hand end the circled number changes for the last note in a row, as also occurs in the case of C5.

## SCREENING

In the design of the String Ensemble great attention has been paid to ensuring that the instrument is free from beehive (background noise from the Tone Generation circuitry). This has been achieved in respect of blocking any direct beehive through the Diode Gates into the voice circuitry. However, it is important to ensure that this is not negated by pick up into the voice circuits from the Tone Generator harness. The use of screened leads where recommended will prevent this, and care should be taken not to strip the screening back too far, leaving unscreened lengths, particularly in connections to the Woodwind slider potentiometer.

An earthed metal screen is also required to isolate the Tone Generator harness from the Voice and Chorus boards when the keyboard is lowered, and whilst the original prototype incorporated a screen fixed above the boards on stand-offs from the baseboard (see photo on page 598), it has now been found more convenient to mount the screen onto the keyboard chassis with equal success. Dimensions for the screen are given in Fig 5.3.

## PLAYING THE STRING ENSEMBLE

Prototypes have now been used on a wide range of power amplification systems in both domestic and stage settings. A normal hi-fi amplifier/speaker combination has given excellent results with a power handling capacity of approximately 15W per channel using the high level output for the Ensemble into the auxiliary channel of the amplifier. With a commonly used guitar combo-amplifier rated at 100W the "Bright Input" with treble lift, has been used successfully to give either solo or chordal backing effects in a group which includes an organ for general use.

With this type of amplifier the Ensemble low level output is recommended to prevent overloading of the first stage of the combo-amplifier.

## LEVEL SETTING

The Upper Voice controls plus the Upper and Master Level controls give six variable signal levels which when coupled with the Lower Voice switches and the variation in the number of notes playing at any time results in a very wide signal range driving into the chorus delay lines.

For a good signal/noise performance it is important to set the instrument such that the delay lines have a reasonable signal level, but due to the wide range of signal available it is possible to overload the delay lines under extreme conditions.

The new component values given earlier for the Chorus and Voice boards give a good optimum condition where in normal playing circumstances the Upper and Master Level Controls should be set in the mid-position and the power amplifier adjusted for maximum output with the swell pedal fully depressed. The pedal does not affect the delay lines and should be used for normal volume adjustment.

A single Upper Voice can be used with the slider control at maximum. Two voices can be used with each slider control in the mid-position. Similar compensation can be made if more voices are mixed, but since an overload safety factor has been incorporated it will probably not be necessary.


An alternative mode of operation when mixed voices are to be used regularly, organ simulation, is to turn the Upper Level control anticlockwise to, say, the one third position which will then allow all voices to be mixed additively with heavy chordal fingering without overloading the delay lines.


For solo playing on single voice the Upper Level control can be turned to maximum. The Master Level controls the entire keyboard and can be used to increase the lower keyboard level, whilst the upper keyboard level is reduced by the Upper Level control, or to further increase the upper keyboard level on single note solo playing.
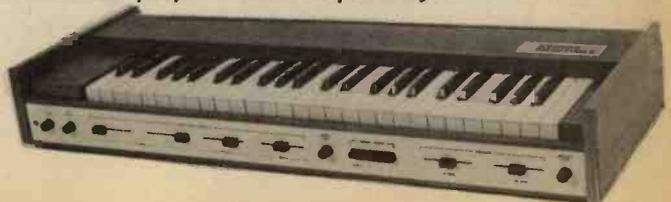
## OPTIMUM VOICING

The best effects are obtained with simple voice settings, that is with one voice control in use at any particular time. However, experimentation with the wide range of controls available can lead to the creation of other sounds which with subjective opinion can enhance the motives of an individual to construct the project. ★

*Constructors who would like a cleaner copy of Fig. 3.5 should write in including a stamped addressed envelope. In Fig. 4.3 and the Components List last month C81 and C82 should be 4,700pF and 47nF respectively.*



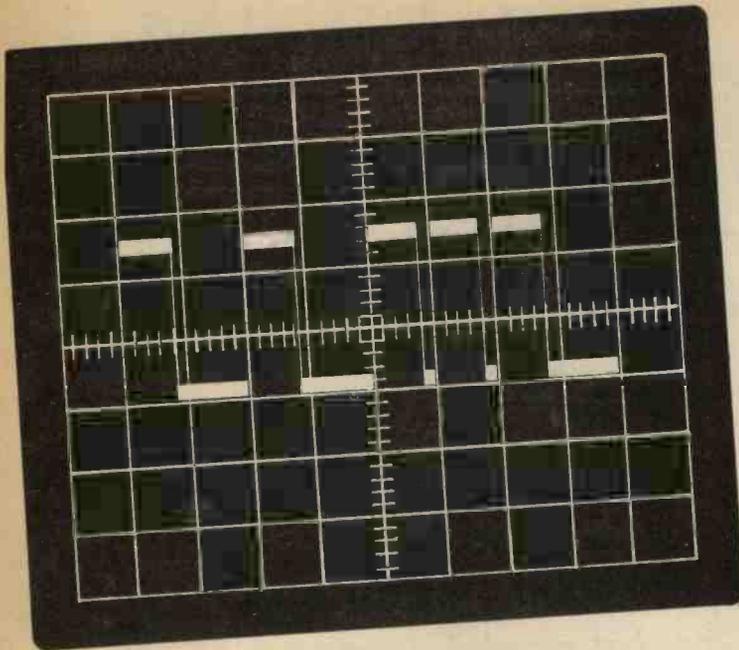

# C.R.O. LOGIC MONITOR GENERATOR

R. DERRY

THE device to be described uses two MSI TTL logic chips with a minimum of additional components to generate an analogue waveform which gives a histogram type of display when fed to an oscilloscope. In addition, marker pulses can be added to the display to add to its clarity. An eight channel version is described which can be built for about £5, assuming that an oscilloscope is already available.

Also described is a way of using the display to test logic displays which is particularly useful for general bench work with logic circuits. The basic design can be extended to cope with more than eight channels if required.

## CIRCUIT DESCRIPTION

The heart of the circuit is a 74151 i.c. as seen in Fig. 1. This is an eight line to one line data multiplexer operated conventionally being addressed by a divide by eight counter (a 7490 counter wired to divide by eight). The counter is driven from an asymmetrical oscillator fed via a Schmitt trigger to give sharp transitions. The reasons for the asymmetrical output of the oscillator are described later in the section on the marker blips. The histogram display that results is particularly vivid which will indicate not only "0" and "1" states but also invalid voltage levels between these two states.

As the 'scope's spot begins its travel at the left of the screen, Channel 1 (input "0" of the 74151) is addressed and the spot will indicate either a nominal 0V or 5V. After it has traced out a line of one eighth of the display length, Channel 2 is addressed and the spot will either continue along the same line or switch to indicate the other value. This will continue until all eight channels have been displayed. As Channel 1 is about to be addressed again the synchronising pulse causes the spot to return to the left-hand side.

Provided that this happens fast enough a histogram display will result (although without marker blips). The rate of addressing is dependent entirely on the frequency of the oscillator. This is not critical but if the rate is too slow a disturbing flicker will mar the display: if too high, the quality of the image deteriorates due to pulse rounding and distortion due to stray capacitance in the connecting leads. While the display could be sharpened using a Schmitt trigger at the input to the 'scope or by using low capacitance connecting

leads, there is really nothing to be gained by a very fast addressing rate. Bear in mind that harmonics of the order of twenty to thirty times the oscillator frequency are present on the output of the unit as it is giving a square wave output.

It was found that an oscillator frequency of the order of 1.5kHz gave a clean flicker free display using two feet of connecting lead from the board to the 'scope.

The lead used was ordinary connecting wire, the data, sync and earth lines being just simply twisted together.

## SYNCHRONISATION

Obviously if the oscilloscope used the data stream from the board to operate its internal synchronisation circuits, the display would lock into a random position. A convenient source of a synchronising pulse is available from pin 8 of the counter. This goes negative as Channel 1 is about to be addressed. Provided the 'scope can be set to lock on a negative edge, Channel 1 will be on the extreme left.

If it is preferred to lock on a positive pulse the sync output can be inverted or the inputs renumbered so that what would have been Channel 5 is numbered Channel 1, Channel 6, Channel 2, etc.

## COMPONENTS...

### Resistors

R1	620Ω	R7	10kΩ
R2	10kΩ	R8	360Ω
R3	10kΩ		
R4	620Ω		
R5	360Ω		
R6	10kΩ		

### Capacitors

C1	0.047μF
C2	0.1μF
C3, C4	10μF (2 off) 25V elect.
C5	0.1μF

### Integrated Circuits

IC1	7413
IC2	7490
IC3	74151

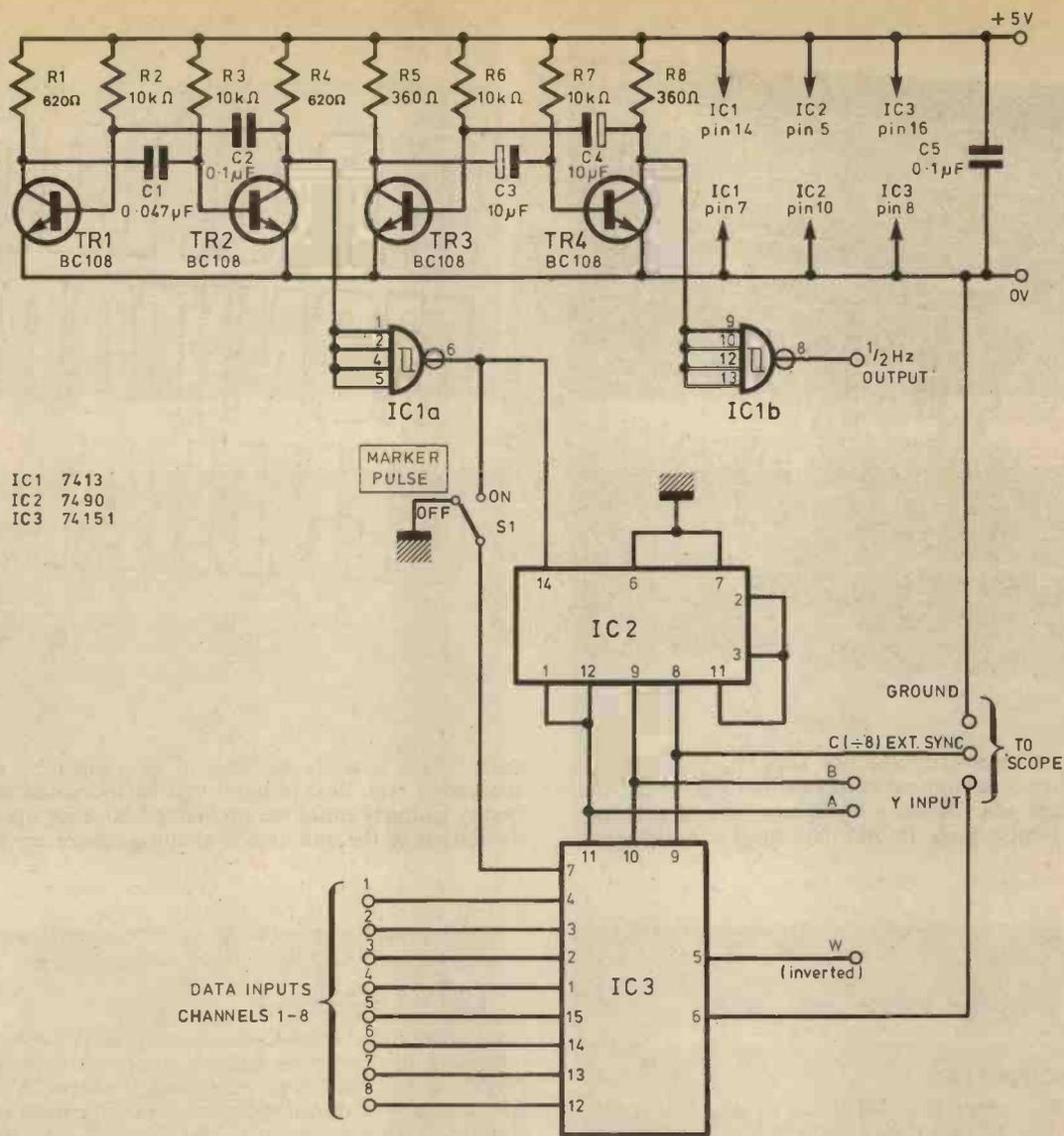


Fig. 1. Circuit of Logic Monitor

## OPERATION

There are three 'scope connections: data output, sync output and common earth.

The 'scope should be set to give a reasonable size of display using an input sensitive down to d.c. as otherwise the display will keep moving around the screen. Unconnected inputs will give a "1" display so ground one input, say Channel 2 and adjust the 'scope timebase until the image locks. If the time base is running too slow more than one image of the display will appear side by side.

Increase the timebase rate until a single image appears. If the timebase is too fast the image will fold over on itself. Experiment with grounding various combinations to check that each input has been connected correctly.

A length of 10 way colour coded ribbon cable can be used, allocating colours to the channels following the resistor code. (Channel 1=brown, Channel 2=red, Channel 3=orange, etc).

The black and white wires are used to carry the 0V and 5V supply from the circuit under test to power the board. The connecting leads can be terminated in any convenient way.


## MARKER PULSES

As described so far the circuit is fairly conventional and gives a straight histogram display so that if all the inputs are at "1" or "0" a straight line results which can be less than clear as a display and some form of marker blip is desirable.


This can be achieved without additional components in two ways. The first makes use of the strobe input of the 74151. Unless this is grounded its output stays at 0V. If this input is fed with the output of the oscillator the output is returned to "0" for the duration of the positive half cycle and follows the condition of the selected input for the duration of the negative half cycle. This is why the oscillator is given an asymmetrical output.

By making the positive excursion about one sixth the length of the negative excursion, small blips are created on the zero line.

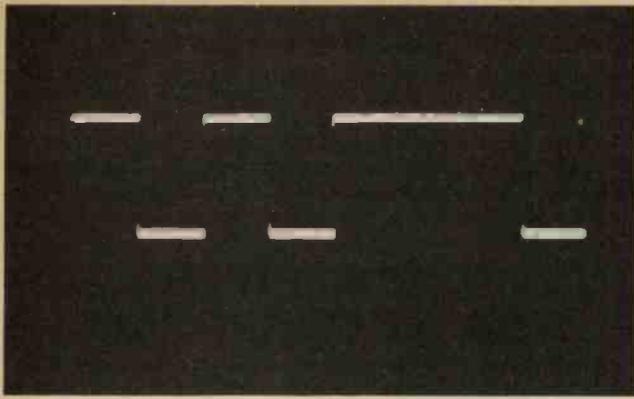
If you have an oscilloscope with a sensitive "Z-axis" modulation input the asymmetrical oscillator can be fed to this instead. The display will be blanked between each section of the display, giving discrete dashes.




(a)

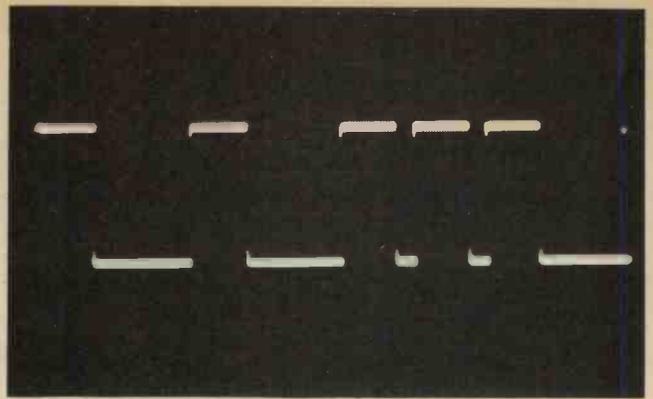


(b)

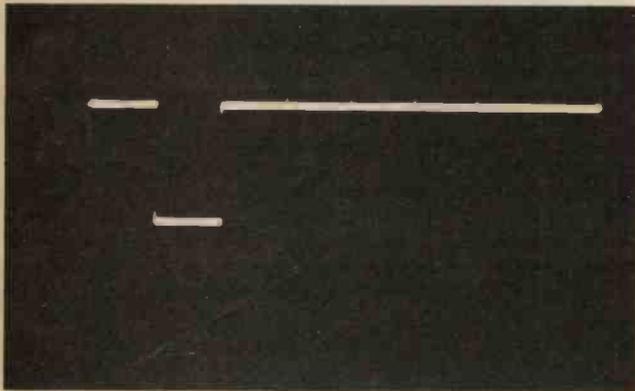


(c)

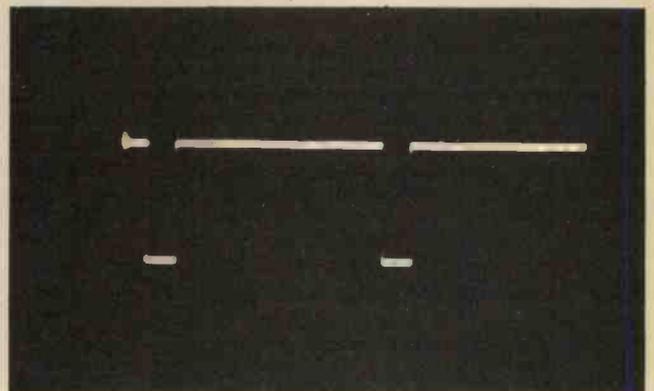


(d)

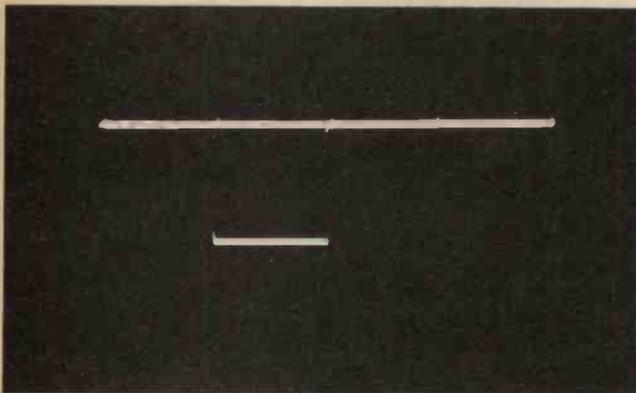

(e)

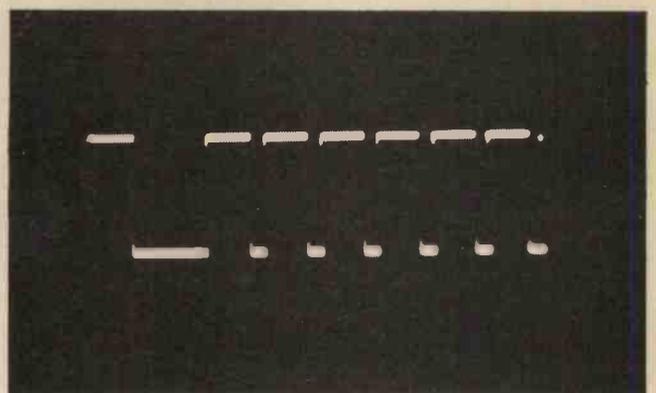

(f)

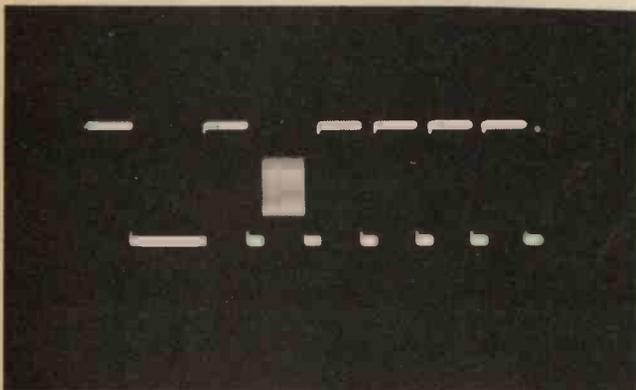

(g)

**Fig. 2(a).** Display without blips; (b) display with blips; (c) Test waveform correct appearance; (d) Test waveform—timebase too slow (half speed); (e) Test waveform—timebase too fast (double speed); (f) Test waveform—correct appearance; (g) Channel 5 invalid input voltage

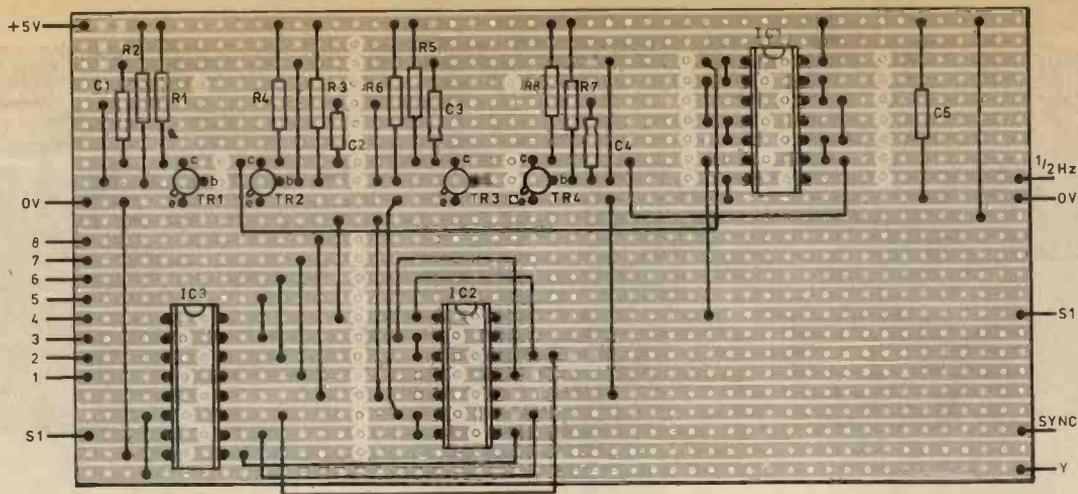


Fig. 3. Veroboard layout

### PERMANENT INSTALLATION

If desired, the board can be permanently mounted in a box on the workbench. In this case it is convenient to provide a "Marker Blip" on/off switch.

This is a simple changeover switch that connects either an earth or the oscillator to the strobe input. A second switch could be added to switch the 'scope away from the logic monitor circuits to look at logic waveforms directly—care being taken to keep stray capacitance to a minimum. An additional convenience would be switches that would disconnect individual input channels and substitute an earth so that unconnected inputs will indicate "0".

It was found convenient to mount a 0.5Hz oscillator on the same board. This is useful for cycling circuits under test slowly for examination of their working.

### TESTING INTEGRATED CIRCUITS

The testing of TTL i.c.s and i.c.s that are feared to have been damaged is speeded using the display. Using a  $\mu$ Dec breadboard, a 7493 divide by sixteen counter is used to provide inputs to the gates under test. Both inputs and outputs are monitored. For example, to test a 7410 triple 3-input NAND gate i.c. the A, B and C outputs of the counter are connected to the three inputs of each gate and also Channels 1, 2 and 3 of the display. The gates can now be seen cycled through all eight possible input conditions as the counter is pulsed by the l.f. oscillator. Channels 4 and 5 are grounded for clarity of display and Channels 6, 7 and 8 connected to one each of the three outputs.

With a correctly operating i.c. all three outputs will go to zero simultaneously when three "1s" are at the inputs of the gates. A faulty gate will be seen to be behaving differently. By examining the display as the circuits are cycled it can soon be seen if the faulty gate can be used as a 2-input gate or as an inverter. Once the breadboard has been set up it is a quick and simple matter to unplug one i.c. and substitute another of the same kind.

If you regularly use "untested" i.c.s it might well be worth your while to wire up a series of plug-in pieces of Veroboard that would instantly set up the correct conditions of a range of commonly used i.c.s. Some of these boards might need subsidiary logic on the plug-in board but the necessary i.c. need only be plugged into a socket and can be borrowed from another logic circuit not in use at the time of testing. (see Fig. 4)

### INCREASING THE CHANNELS

The number of channels can be increased to sixteen by replacing the 74151 with a 74150 sixteen to one line multiplexer driven by a 7493 divide by sixteen counter. A lesser number of inputs can be arranged by resetting the counter before it reaches sixteen.

The 74150 gives an inverted output and will give an "upside-down" display unless its output is fed through an inverter.

Theoretically the number of channels can be increased indefinitely by using additional data detectors and counters combined with additional analogue circuitry to give pseudo double, triple or quadruple beam displays. However, the more channels that are used the higher are the harmonic frequencies that have to be handled with the resulting difficulties of keeping a good pulse shape on the 'scope along with the screen becoming cluttered with too much data. In practice eight channels are more than adequate.

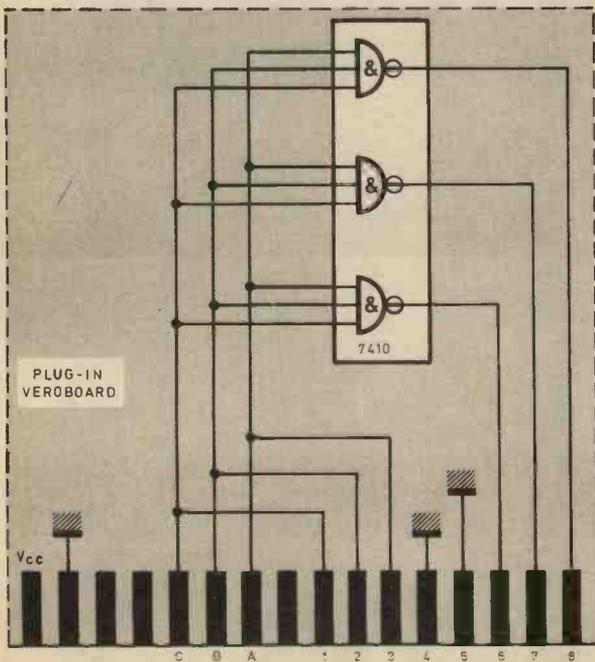


Fig. 4. Typical test set-up

# DIMWIT



M.J. CARTER

## *A sympathetic bedside light!*

ONE of my vices is that I read in bed, and tend to fall asleep with the bedside light still on. Those similarly afflicted will confirm what this can mean in disturbed sleep, not to mention electricity costs. Moreover, those attempting to help me, by turning off the light when I am found asleep, only succeed in waking me up again; as much by the transition from light to dark as by any noise they might make.

### APPLICATIONS

In its original role of "humane bedside light", the prototype Dimwit has given many months of appreciated service. It has also been found suitable for ordinary lamp-dimmer applications, and to have "entertainment value" when soft lighting is called for—with an inbuilt practical joke. Other applications include porch and corridor timed lights, and nightlights for reluctant progeny.

### CIRCUIT DESCRIPTION

The lamp is controlled by a mains triac circuit based on Fig. 13 from "Power Control With Triacs" by W. Williamson, P.E., March 1971. Automatic control is achieved by putting a light dependent resistor in series with the potentiometer, and illuminating it by an l.e.d. This home-made optoisolator is very much slower than the packaged sort, and requires a lightproof container, but its output is more amenable to this application.

The sequence is started by pressing the GO button S1 in Fig. 1, which applies mains power to the PSU via S1b and starts the Timer via S1a. The l.e.d. is then turned on, which causes the load lamp to be dimmed up. The relay RLA is also energised, thus bypassing S1b so that power is maintained when S1 is released. At the end of the timed period, D1 and hence the lamp, will dim out slowly. Then the current in RLA coil is also reduced until it drops out, which switches off the whole circuit. The sequence of events may be followed in more detail in Fig. 2. In addition, the timer is arranged to restart if S1 is pressed during the timing period, and to "time out" prematurely if the KILL button S2 is pressed.

Referring to the circuit diagram of Fig. 3, the timer is a standard 555 arranged as a monostable, whose timing is set by R1 and C1; the value of R1 was chosen empirically to give a period of about fifteen minutes. The values used give a theoretical time of:

$$T = 1.1 \cdot C1 \cdot R1 = 453.75s \approx 7\frac{1}{2} \text{ minutes.}$$

There are three reasons why the time achieved in practice is twice the calculated time.

Firstly, the tolerance of high value electrolytic capacitors (typically  $\pm 10\%$ ,  $\pm 50\%$ ) often make the nominal value an underestimation.

Secondly, the threshold current drawn by IC1 (pin 6) shunts some of the charging current in C1, and this stretches the timing period. Using a low leakage tantalum capacitor, this effect was found to extend the period by some 20% over the calculated time.

Thirdly, charging current in C1 is reduced by its own leakage current, which, together with the threshold current, extends the period by just over 80%. Unfortunately, the leakage current of aluminium electrolytics tends to increase with storage time, due to deforming of the insulating layer in the absence of a polarising voltage. Although this leakage is small, it is enough for a previously unused capacitor in the C1 position to give extra long periods for the first few timings (up to an hour or more), and in some cases preventing triggering altogether. Before soldering C1 into place, therefore, it would be advisable to re-form it as completely as possible, by, for example, leaving it connected (the right way round!) across a PP3 for a day or two. An extended series of measurements with the prototype Dimwit showed that, once the leakage current had settled down, the period varied by no more than twenty seconds in sixteen minutes, which is well within the required accuracy. For those who wish to avoid this "running in" by using a tantalum timing capacitor, it should be noted that C1 would need to be increased to about 200 $\mu$ F to compensate the absence of

## SPECIFICATION

- (i) When started manually, by pressing the GO button, the bedside light comes on, and remains on for 15 minutes.
- (ii) At the end of this period, the light is dimmed slowly to extinction, and the unit switches itself off.
- (iii) When the sequence is started, the lamp "dims" up quickly (rather than be switched straight on), which reduces sudden dazzle, and increases the life of the lamp.
- (iv) The maximum brightness of the lamp, during its "on" period, is under manual control.
- (v) Pressing the GO button re-starts the sequence, whenever it may be pressed.
- (vi) Pressing the KILL button prematurely ends the timing period in (i), and the unit proceeds to shut down as in (ii).



leakage-current. Increasing R1 is not advisable.

To trigger the 555 Timer, a value of  $1k\Omega$  was chosen for R2, giving a source resistance to S1a which is low enough to be immune to the triac switch-on spike. The more conventional value of around  $12k\Omega$  proved troublesome.

Diode D1 has been added to fulfil specification (v), and if S1 is pressed before IC1 "times out", C1 is discharged by D1 and S1a, thus restarting timing. Normally D1 is reverse biased, and takes no part in circuit action.

When IC1 turns on at the beginning of the sequence see Fig. 2 (a), C3 charges rapidly via D2, D3, and D4, then completes its charging via R4, see Fig. 2 (b). This is transmitted through the buffer stage TR1, TR2 to D1, which dims up rapidly *but not instantaneously*, see Fig. 2 (c). This is in order to fulfil specification (iii), and the resistance of R13 then falls. Fig. 2 (d) shows the inverse of this, so that the triac control circuit dims up the load lamp rapidly. R13, the ORP12 light dependent resistor, particularly in the low illumination levels used in this application, has a somewhat slow response, as indicated in Fig. 2 (d); the only effect this has on the completed Dimwit being however, that the mains lamp is a little more sluggish in dimming up after an hour's rest than after only a few minutes. Since the maximum peak voltage rating of the ORP12 is 110V, the potential divider

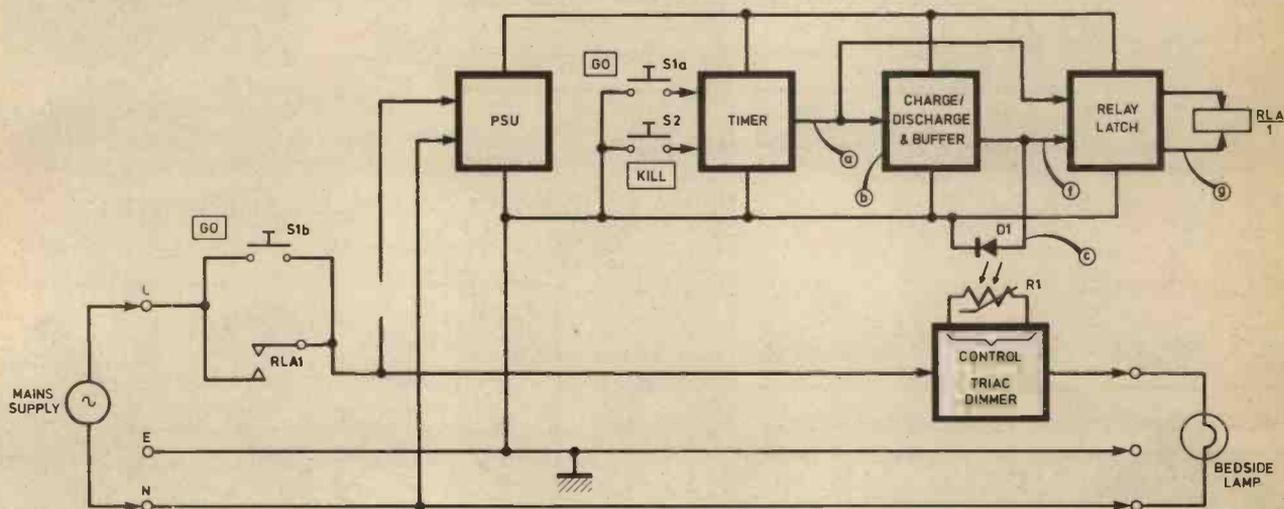


Fig. 1. Block diagram of Dimwit

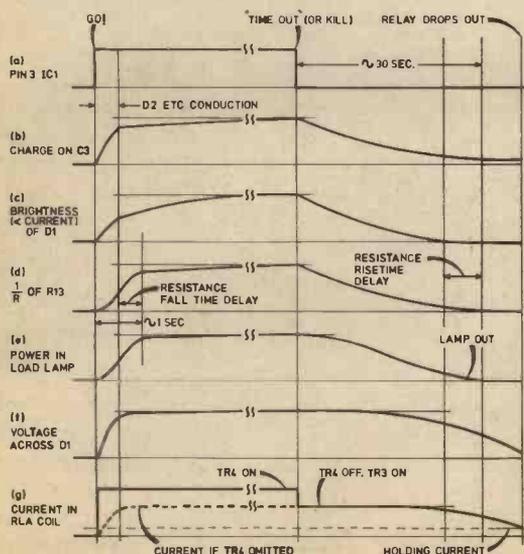


Fig. 2. Waveform timing diagram

comprising R11 and R12 has been included. This limits the maximum output power a little, but does extend the life of most tungsten lamps.

## RELAY DRIVE

The relay is energised by TR4, Fig. 2 (g), which is turned on by IC1 via R8. A handy miniature relay was used for convenience, and a possible type is the 6V miniature open relay from RS Components (part no. 349-125), for which there is enough space on the p.c.b., but which has different mounting arrangements. Since S1b carries the switch-on current surge for the lamp, which in any case is considerably reduced by the dimming-up process, see Fig. 2 (e), the relay contacts need only be rated for the continuous current of mains lamp and Dimwit. Moreover, as will be seen, the current broken by the relay at the end of the cycle is smaller still. Thus, if need be, a reed relay may be used.

Once IC1 has timed out (or when the KILL button S2 is pressed), C3 starts discharging slowly via R4, Fig. 2 (a), (b); thus the load lamp, Fig. 2 (c), (d), (e), starts dimming down


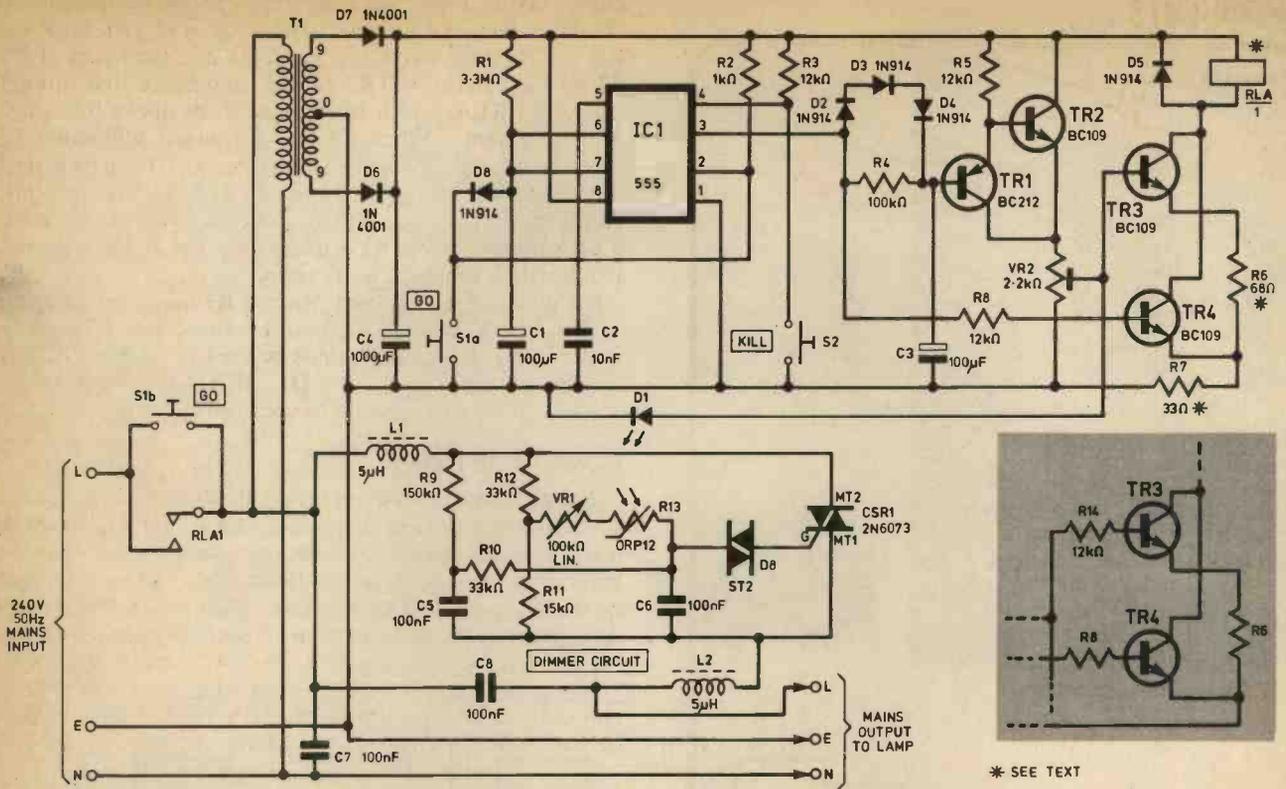
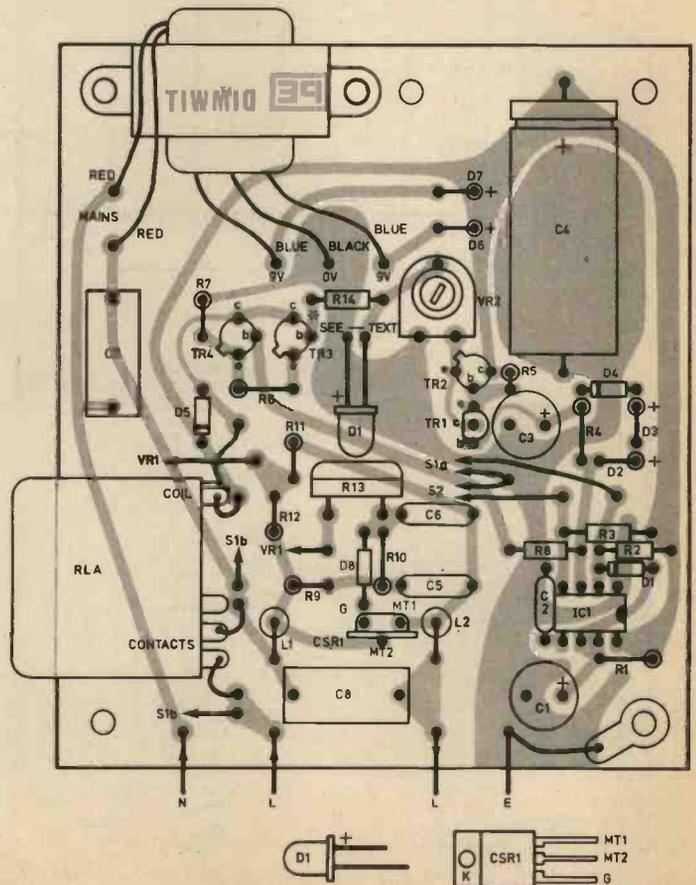


Fig. 3. Full Dimwit circuit. The shaded area shows the modification referred to in the text

Fig. 5. Component layout

Fig. 4. Printed circuit layout (actual size)

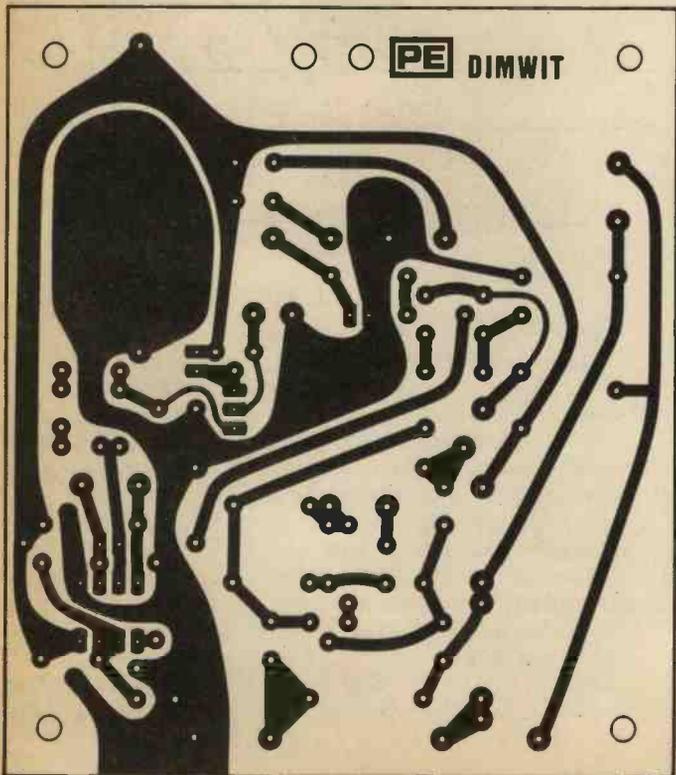

# COMPONENTS . . .

## Resistors

R1	3.3M $\Omega$
R2	1k $\Omega$
R3	12k $\Omega$
R4	100k $\Omega$
R5	12k $\Omega$
R6	68 $\Omega$ (see text)
R7	33 $\Omega$ (see text)
R8	12k $\Omega$
R9	150k $\Omega$ $\frac{1}{2}$ W
R10	33k $\Omega$ $\frac{1}{2}$ W
R11	15k $\Omega$ $\frac{1}{2}$ W
R12	33k $\Omega$ 1W
R13	ORP12

All  $\frac{1}{2}$ W 5% unless otherwise stated

## Potentiometers

VR1	100k $\Omega$ linear
VR2	2.2k $\Omega$ min horizontal

## Capacitors

C1	100 $\mu$ F/16V electrolytic
C2	10nF
C3	100 $\mu$ F/16V electrolytic
C4	1000 $\mu$ F/25V electrolytic
C5	100nF/160V
C6	100nF/160V
C7	100nF/400V
C8	100nF/400V

## Inductors etc

L1	5 $\mu$ H v.h.f. choke, 1A (RS: 238-255)
L2	5 $\mu$ H v.h.f. choke, 1A (RS: 238-255)
T1	Miniature mains to 9-0-9V transformer (Altai 909 or similar)
RLA	9V min 1-pole c/over relay: 280 $\Omega$ coil, mains contacts

## Semiconductors

D1	clear plastics red l.e.d. (5mm dia)
D2-D5	1N914 (or any surplus low-current silicon diode)
D6-D8	1N4001
D9	Diac ST2 (or similar)
CSR1	Mains triac, 3A minimum (2N6073 or similar)
TR1	BC 212
TR2	BC 109
TR3	BC 109
TR4	BC 109
IC1	555 Timer

## Switches

S1	d.p. momentary make; 250V, $\frac{1}{2}$ A (RS: 337-920)
S2	s.p. momentary make, low voltage

## Miscellaneous

1 off	aluminium box, 152 x 101 x 51mm
2 off	self-tap screws (for above)
4 off	13mm 6BA countersunk screws
1 off	6mm 6BA countersunk screw
5 off	6BA nuts
5 off	6BA locking washers
1 off	solder tag
4 off	4mm x 6BA insulating pillars
2 off	mains cable grommets
1 off	potentiometer knob
2 off	25 mm No. 8 roundhead woodscrews, with matching Rawlplugs (for wall mounting)
80mm	double-sided foam-backed adhesive tape



slowly, taking about half a minute to go out altogether. At the same time TR4 turns off, Fig. 2 (g), and TR3 turns on. The voltage drop across D1, Fig. 2 (f), and the values of R6, R7 set the current in TR3 emitter, and hence that through the coil of RLA, which is arranged to be above the relay's holding current. When C3 has discharged sufficiently for D1 to be off, Fig. 2 (c), the voltage across D1 begins to fall, and reduces the energising current in RLA until it drops out. This turns off the whole circuit, and thus completes the cycle. If S1 is pressed before RLA drops out, then IC1 is triggered, and the whole sequence starts again.

If a different relay is used, R6 and R7 may need adjusting to give correct action of RLA; if it is found that R7 must be omitted, then R14, Fig. 3, must be used to prevent TR3 base shunting all the current from D1. If R13 is not needed, its position on the p.c.b. should be occupied by a short circuit.
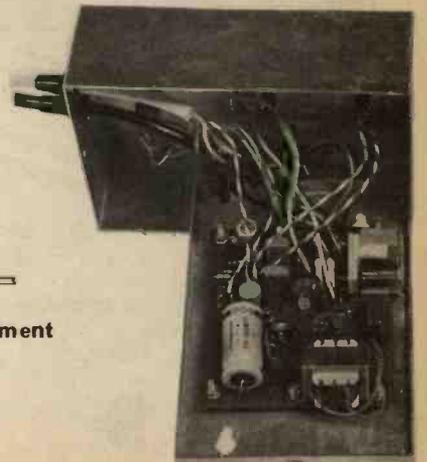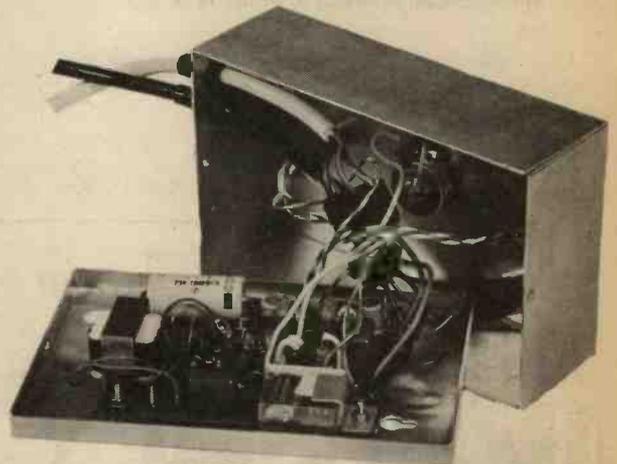
## CONSTRUCTION

The p.c.b. and component layout are shown in Figs. 4 and 5. Construction is straightforward, as long as care is taken on the mains-voltage section to minimise the risk of flashover between tracks or to the (earthed) case. D1 and R13 are mounted as shown below. If the stiffness of the lead-out wires is not considered enough to keep them in place, they may be secured to the p.c.b. with a plastics filler. D1 should illuminate all of the active area of R13 and this may be checked visually in semi-darkness. RLA is mounted as shown below using double-sided foamback adhesive

A most chivalrous bedside light (internal view), showing the relay mounting arrangement



Opto coupling arrangement

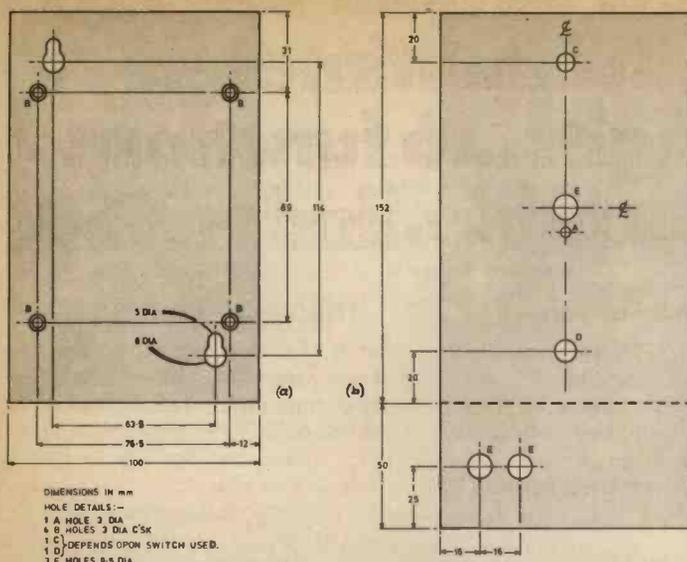



Fig. 6. Metalwork drillings. (a) Keyhole slots on backpanel, for wall mounting. (b) Front panel. Hole sizes will depend upon switch types used.

tape. The tape is wrapped around the relay case, and the relay then stuck into place. For added security, the metal clamp shown may be added. The mains transformer is also secured at one end by a p.c.b. mounting screw, and at the other with a 6BA nut and screw. Connect to mains earth.

After assembling the p.c.b., and drilling the metal box as indicated in Fig. 6, mount the circuit board on the back panel using 6BA countersunk screws and insulating pillars. Set VR2 to mid-position, and VR1 fully clockwise. Close the case but leave it unscrewed.

By connecting to a load lamp of the same wattage as is intended to be used with the unit, and connecting to the mains, full operation of the completed Dimwit may be checked. VR2 can now be set to give the desired dimming performance: turning it anticlockwise increasing the dimming-up time and decreasing maximum brightness, while shortening the dimming-out sequence. (Remember to reassemble the case after each adjustment, if a lightproof assembly is not used for R13). When adjustment is complete, screw the case together and Dimwit is now ready for use.

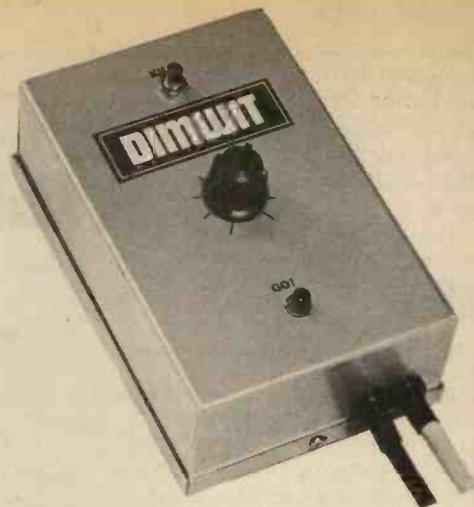The completed Dimwit is intended for wall mounting. The



In the old days they managed with crude "ON/OFF" bedside lamps

"saucepan" slots, which allow the unit to be hooked onto No. 8 roundhead woodscrews, are best made by drilling a 8mm hole and a 5mm hole, and joining them with the aid of a "rat tail" file. To mount Dimwit, drill and plug the wall, to accept the woodscrews, and screw them nearly home.

### CONSIDERATIONS

The "dimming up" time which occurs at the beginning of the sequence may be increased by replacing D3 and/or D4 with a 1kΩ resistor, which slows the charging up of C3.

There is a faintly audible "clunk" when the relay drops out, which might be sufficiently loud to *reawaken* the more highly strung sleeper. If this becomes a problem, an electrically suitable type reed relay might provide an easier solution to further sound proofing, although fitting it into the available space may present problems.

It would take a number of years to recover the cost of the project, from saved electricity and enhanced bulb life, but its *true* value becomes apparent as you begin to take Dimwit for granted! ★

## News Briefs

### IERE CONFERENCE

THE advances made in the field of radio receivers since the days of the cat's whisker crystal detector have been considerable. It is proposed to survey the subject at a conference on Radio Receivers and Associated Systems organised by the IERE which is to be held at the University of Southampton from July 11-14 1978.

Thirty seven papers will be delivered formally and a further twenty will be presented in poster booth sessions. An exhibition of relevant equipment and systems is to be organised by the Electrical Research Association.

Further information can be obtained from The Conference Secretariat, IERE, 99 Gower Street, London WC1.

### SONY BETAMAX

IN April Sony announced to the press the launch of its Betamax home video recorder. With over 500,000 people using Betamax on N.T.S.C. systems in the U.S.A. and Japan Sony believe the time is right to offer a PAL standard Betamax to Europe.

Mr Akio Morita, chairman and co-founder of Sony Corporation, heralded the coming of a "Video Age". He said that Sony were not looking to capture the home video market in a rush of sales. The Sony policy is to establish highly qualified outlets for Betamax and for the after sales service to be faultless.

On International Standards Mr Morita said he obviously hoped that video cassette manufacturers would together establish a common system, but the inference is that Sony think their system is the best and others may follow.

Costly and specialised machinery is used to manufacture the slanted azimuth video head. This equipment is in Japan and production is likely to be based in Japan for some time to come. Sony have a TV production line at Bridgend in Wales and although it is possible that assembly of some Betamax may happen at some time in the future it must be little comfort to the Mullard TV tube work force.

# The new Sinclair DM 235 digital multimeter.

## 3½ digits...6 functions fully portable. Under £50!

The new Sinclair DM235 is yet another example of outstanding Sinclair value-engineering. Developed from the Sinclair DM2 and world-beating PDM35 (already outselling all other digital multimeters), the DM235 provides full facilities for every application, including field servicing, testing and laboratory work. At a price no comparable digital meter can approach.

### A new dimension in styling

Up till now, choosing a meter suitable for use on the bench *and* in the field hasn't been easy. Either you bought a bulky bench instrument (awkward to carry around) or a hand-held portable (difficult to use on the bench). The Sinclair concept is different. By keeping the thickness down to only a fraction over 1½ in,



and the weight down to under 1½ lb, we've produced an instrument that has all the advantages of conventional bench meters, but that packs neatly into any tool kit or brief case.

### A big, bright, unambiguous display

The DM235 has a full 3½ digit display reading to ±1999. Large, high-brightness 8 mm LEDs give clear, unambiguous readings with an ultra-wide angle of view. And an LED display means proven lifetime reliability.

### Six functions in 26 ranges

DC Volts..... 1 mV to 1000 V  
 AC Volts..... 1 mV to 750 V  
 DC Current..... 1 μA to 1 A  
 AC Current..... 1 μA to 1 A  
 Resistance..... 1 Ω to 20 M Ω  
 Diode test..... 0.1 μA to 1 mA  
 10 M Ω input impedance

### High accuracy

Basic accuracy of 0.5% (2 V DC range), other DC ranges and Resistance 1.0%, AC ranges 1.5% 30 Hz-10 kHz. Temperature coefficient <0.05 of applicable accuracy per °C.

### Easy to use by anyone, anywhere

Automatic polarity operation, automatic placement of decimal point, and automatic out-of-range indication. Unambiguous reading of function and range selected from a single input terminal pair.

### The Sinclair credentials

Sinclair have pioneered a whole range of electronic world-firsts from programmable pocket calculators to miniature TVs - holding a world lead in innovative electronics. The DM235 embodies six years' experience in digital multimeter design, in which time Sinclair have become one of the world's largest producers.

Like every other Sinclair product, the DM235 comes to you with a full 12 month repair-or-replacement guarantee.

### Find out more!

If you'd like full details of the DM235, its operation and its performance, and a complete distributor list, just send the coupon below. We'll send you all the facts by return.

The DM235 has all the performance you need - at around half the price of its competitors. Send the coupon for the full story.

Sinclair Radionics Ltd, St Ives, Huntingdon, Cambs, PE17 4HJ.

**sinclair**  
 World leaders in fingertip electronics



### A rugged construction giving total portability

Very rugged mechanical construction using all solid-state components.

Protected against accidental overload.

Size only 10 in x 5.8 in x 1.6 in, weight less than 1½ lb.

Basic operation from four standard C size disposable cells, providing complete independence of AC supply.

Line operation available via optional AC adaptor/charger.

### A full range of optional accessories

DM235 meter complete with test leads and prods..... £49.80

Ever-ready carrying case with lead stowage compartment..... £8.50

Rechargeable battery units..... £8.00

AC adaptor/charger 240 V 50 Hz.. £3.50

30 KV high voltage probe..... £15.00

(All prices subject to 8% VAT)

To: Sinclair Radionics Ltd, St Ives, Huntingdon, Cambs, PE17 4HJ.  
 Please send me full illustrated details of the new Sinclair DM235.

Name \_\_\_\_\_

Position \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

PE/7

**BEFORE YOU BUY AN AMPLIFIER MODULE—CHECK:**


**DOES IT HAVE**

- ★ 30A power transistors
- ★ 2-year guarantee
- ★ 3A drivers (100W unit)
- ★ Integral output capacitor

Then compare with the Tamba range—excellent value—25, 50 and 100W R.M.S

TAM1000 100W 4 ohms 65V	£9.80
TAM500 50W 4 ohms 45V	£7.50
TAM250 25W 8 ohms 45V	£5.75

POWER SUPPLIES	
For 1 or 2 TAM250/500	£7.50
For 1 or 2 TAM1000	£9.80
(Carriage 50p on supplies)	

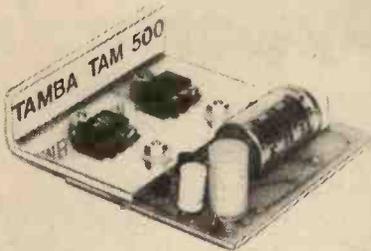

**NEW**

**ALL PURPOSE MIXER/PRE-AMP.**

(with 60mm slider volume)

- Suitable for multiple input systems
- High and low impedance inputs
- High sensitivity
- Built-in supply smoothing
- 20–20,000 Hz ± 1dB
- –80dB noise level
- Accepts a wide variety of inputs
- Wide range bass and treble controls

Use up to 10 PRE-AMPS with 1 power supply

Printed circuit board assembly with treble and bass controls plus slider volume control **£6.50**

- Suits loads 4–16 ohms
- 20–20,000 Hz ± 1dB
- Silicon circuitry throughout
- Glass fibre P.C.B.
- High sensitivity (100mV 10k)

- Low distortion (0.1%)
- Low profile (1in high 3½in. x 3in)
- 75% efficient
- Accepts most mixer/pre-amplifiers
- Four simple connections

High grade components used throughout: Texas, Mullard, R.C.A., Plessey, etc.

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s etc)—C.O.D. (60p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50 and 100W systems and at 12½% for 25W systems (including preamp if ordered at same time).

Hours, 9.30 a.m.–5 p.m.  
Monday — Saturday.  
Callers welcome. Tel. (01) 684 0098

# TAMBA ELECTRONICS

Bensham Manor Road Passage, Bensham Manor Road, Thornton Heath, Surrey.

## JONES SUPPLIES

TTL				CMOS			
7400	.13	7447	.08	4001	.17	4047	.95
7401	.13	7451	.16	4002	.17	4049	.48
7402	.16	7470	.30	4011	.19	4050	.53
7403	.16	7472	.28	4013	.45	4070	.53
7404	.19	7473	.30	4014	.85	4502	.95
7406	.36	7474	.03	4015	.85	4508	2.09
7407	.36	7475	.04	4016	.52	4510	1.51
7408	.19	7476	.35	4017	.85	4511	1.75
7410	.14	7486	.35	4018	.85	4514	2.98
7413	.36	7479	.85	4023	.19	4516	1.09
7414	.74	7493	.35	4027	.52	4518	1.02
7416	.36	7496	.82	4028	.97	4528	1.02
7420	.16	74107	.32	4042	.85	4536	5.00
7442	.35	74141	.70	4046	1.40		

MAINS TRANSFORMERS (P&P 60p each)			MISCELLANEOUS		
6-0-6	100mA	£1.10	U2 size Ni Cad Bat.		
9-0-9	75mA	£1.10	(P&P 30p)		£1.95
12-0-12	50mA	£1.15	8 pin 741		.18
12-0-12	100mA	£1.40	Scope Probe, BNC Plug		£14.99
9-0-9	1 Amp Sh.	£2.44	BNC Socket		.90
12-0-12	1 Amp Sh.	£3.12	Signal Injector		£5.20
15-0-15	1 Amp Sh.	£3.60	Multimeter 1,000 OPV.		
30-0-30	1 Amp Sh.	£4.24	11 Ranges (P&P 50p)		£6.25
20-0-20	2 Amp Unsh.	£5.75	Telephone Pick-up Coil		.92
30-0-30	2 Amp Unsh.	£7.00	3" 8Ω Spkr. (P&P 20p)		.99
Stereo Amp Module 6 + 6 watts			4" 8Ω Spkr. (P&P 30p)		£1.44
O.P. Imp. 8Ω. 24v DC		£7.99	0-1mA Panel Meter		£4.20
F.M. Tuner. Module. 9v DC		£7.99	240v AC/9v 120mA Regulated		
			Supply in Plastic Case		£3.78

PRICES: PLEASE ADD 8% VAT, P&P 10p EXCEPT WHERE SHOWN  
RETAIL & MAIL ORDER OPEN 7.30 p.m. M. TH. FRI. SAT.

### JONES SUPPLIES

588 ASHTON ROAD, HATHERSHAW, OLDHAM, LANCs. 061-652 9879

### NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £15.95 +VAT £1.28

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume. Conversation recording model at £18.95 + VAT £1.52. P. & P. 89p. 10-day price refund guarantee on all items.

### MAINS INTERCOM



NO BATTERIES NO WIRES ONLY £32.99 PER PAIR +VAT £4.13  
The modern way of instant 2-way communications. Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range ¼-mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom, between office and warehouse, in surgery and in homes. Model with Buzzer Call. £36.99 + VAT £4.62. P. & P. 99p for either model.

### WEST LONDON DIRECT SUPPLIES (PE3)

169 KENSINGTON HIGH STREET, LONDON W8 6SN  
Tel: 01-937 5548

## HAVE YOU DONE IT LATELY!

Fit a new tape head and transform the performance of your tape recorder

**MONOLITH**  
THE MONOLITH ELECTRONICS CO. LTD.

QUALITY REEL TO REEL AND CASSETTE TAPE HEADS



Full Catalogue 25p

Please enclose 20p P&P with order

B24-RP stereo cassette glass/ferrite record/playback £9.84  
B12-01 mono cass. playbk. £1.60 B24-01 stereo cass. playbk. £2.80  
A28-05 stereo 8tk cartridge £1.80 E12-09 stereo/mono cass. erase £1.80

5/7 Church St, Crewkerne, Som. Tel. (0460) 74321

# ALL IN OUR AUGUST ISSUE!

## Digital Thermometer


Achieves a measurement range of  $-99.9^{\circ}\text{C}$  to  $+99.9^{\circ}\text{C}$  with a three digit seven segment display. Previously, analogue-to-digital conversion involved many discrete and integrated circuit devices. This unit dramatically reduces this problem by using a Siliconix LSI chip plus a few additional components.

## CONSTANT DISPLAY FREQUENCY COUNTER
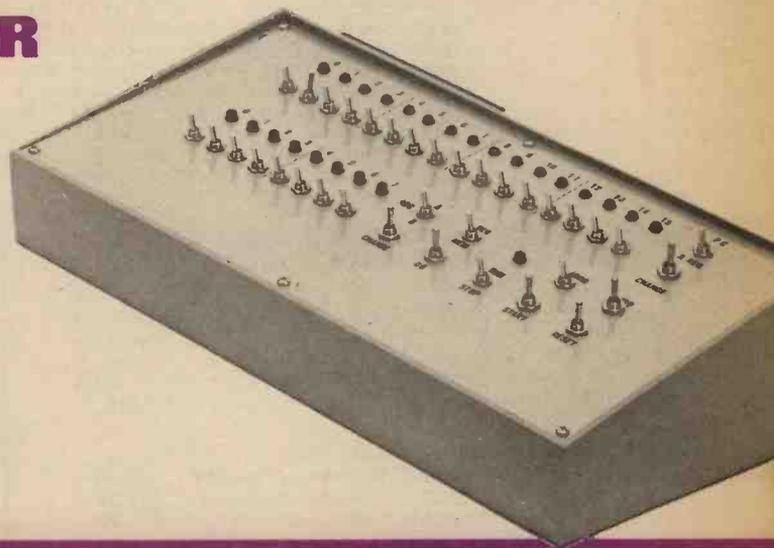
## AMI-COS MICROPROCESSOR KIT REVIEW

The home computer industry which has recently been booming has produced a bewildering number of "systems" for the amateur. We look at one particular kit in this review.

A straightforward unit to give frequency count capability in the range 1 to 99.999kHz with a 1Hz sampling rate. The readout does not count visibly or flicker due to display blanking. All components are readily available, and this would be an ideal project for the beginner.



# PRACTICAL ELECTRONICS

OUR AUGUST ISSUE WILL BE ON SALE FRIDAY, 14 JULY, 1978

# FREE ENTRY COMPETITION!

AN OPPORTUNITY FOR INVENTORS  
FINANCIAL BACKING and £490  
worth of SCOPEX 'SCOPES  
TO BE WON

**1st Prize** A Scopex 4D10A dual beam oscilloscope worth over £200.

**Runner up Prizes** Two Scopex 4S6 single beam oscilloscopes each worth over £140.

Can you invent or design a novel project that could form a commercial product? We give you the chance to win the financial backing your ideas might deserve. Successful designs may be backed commercially by a Venture Capitalist to develop saleable products and you—as the designer—would receive financial benefit.

Even if your design is not deemed suitable for development you could still win yourself a piece of test gear worth over £200. Some designs may also be published in P.E. as constructional projects and payment will be made at the time of publication—so you could gain in any or all of three ways!

If you do come up with a winning design, who knows, you could soon be a partner in a going concern.

## HOW TO ENTER

The contest is for practical items incorporating electronics as a major part of the overall system. There is no restriction on the application, e.g. it could be a video tape recorder or a door bell. It may be for domestic use or for industry.

Entries must be written/drawn clearly on one side of plain paper with the entrant's full name and address at the top of every sheet. Each entry to comprise:

- a brief summary of the design (about 50 words);
- any such further descriptions, drawings, sketches, photographs and circuit diagrams, etc., you consider the judges may need to form the best appraisal of your design. **DO NOT SEND ACTUAL MODELS.**

Each entry must have a properly completed entry coupon cut from P.E. firmly affixed to the back of the summary. Entrants may be requested to supply prototypes for evaluation at later stages of the judging. All entries must be in English.

Readers may be assured by P.E. that ideas submitted will not be misused or transmitted to other parties by anyone concerned with the competition.

## SEND YOUR ENTRY TO

Practical Electronics Inventors Competition  
55 Ewer Street, London, SE99 6YP

## FREE ENTRY COUPON

PRACTICAL ELECTRONICS INVENTORS COMPETITION  
(Block letters please)

NAME (Mr/Mrs/Miss).....

ADDRESS.....

TELEPHONE NUMBER if any.....  
I certify that

\* delete clause NOT applicable


\* (a) This entry is my own original idea and has not been copied from any other source;

\* (b) This entry has been made on behalf of the company/group members listed and is our own original idea not copied from any other source;

(c) This idea has not been published or offered for publication elsewhere.

I/We agree to abide by the rules and conditions.

SIGNED.....

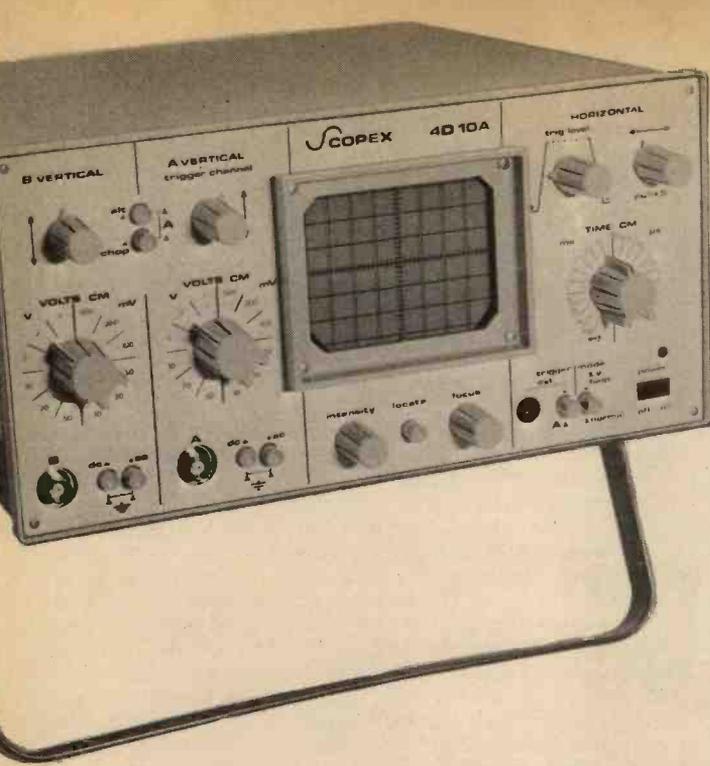

The closing date is August 31st 1978.

#### RULES AND CONDITIONS

There is no entry fee nor limit to the number of entries a reader may submit but each entry must be accompanied by a proper printed entry coupon, cut from PRACTICAL ELECTRONICS, and must bear the entrant's own full name and address. Entries will also be accepted from groups or companies, in which case the entry must be submitted and represented by an individual and the other involvements declared on a separate sheet of paper attached to the back of the summary with the coupon.

All accepted entries will be examined by a panel of expert judges including the Editor of Practical Electronics, and assessed on (a) originality of the idea, (b) technical merit, (c) practicability, (d) economic viability, (e) market potential, (not necessarily in that order). The prizes will be awarded for the best entries in order of merit. In the event of the same idea being submitted by two or more entrants, presentation of the entry (clarity, best expression, etc.) will decide such winner(s) or winning order.

In the event that the judges consider there are not enough entries of a sufficiently high standard, the Editor reserves the right not to award any prize(s) at his discretion.

Entries arriving after closing date will not be considered, nor will any received that are illegible, not wholly understandable, are not accompanied by a properly completed entry coupon or in any other way do not comply exactly with the instructions and rules.

No responsibility can be accepted for entries lost or delayed in the post or otherwise; proof of posting will not be accepted as proof of receipt. No entries can be returned.

The competition sponsors reserve the right to adapt or amend any entry—after judging has been completed—for purposes of publication and/or commercial development. They also reserve the right to consider any other entries for commercial production. Where any idea is adapted or developed for commercial production payment and/or royalties and/or direct involvement in the company concerned will automatically be negotiated with the designer or person named on the entry coupon.

Winning entries will not necessarily be developed commercially, but Practical Electronics will pay the usual reproduction fee for any entries published.

Ideas already covered by a patent owned by the representer, but not already in or on offer for commercial production, may be submitted but this fact must be clearly stated together with the relevant patent number.

Decisions of the judges, and of the Editor in all other matters affecting the competition, will be final and legally binding. No correspondence will be entered into nor interviews granted.

Winners will be notified by post and brief details of winning entries published later in Practical Electronics.

The contest is open to all readers, but those outside the U.K. may be requested to provide a British address to which any prize may be sent. Development of any idea must take place within the U.K.

Employees and the families of employees of IPC Magazines Ltd., and the printers of Practical Electronics and anyone directly connected with the competition are not eligible to enter.

# SOUND DESIGN

A PRACTICAL ELECTRONICS PUBLICATION

## A SPECIAL SELECTION OF MUSICAL PROJECTS FROM PE

### THE MINISONIC MK2 SOUND SYNTHESISER

An up-dated version of the published Mk 1, the Mk 2 has an integral keyboard, two 250 mW monitoring channels and loudspeakers, and facilities for amplitude, frequency and harmonic modulation.

### THE JOANNA ELECTRONIC PIANO

has realistic piano effect with touch-sensitive keyboard and additional choice of harpsichord or honky-tonk voicing.

### THE ORION STEREO AMPLIFIER

A hi-fi amplifier with output of over 20 + 20 watts. Compact and complete in one unit, it measures only 14" x 6" x 2".

#### PLUS

Some great sound effects units for guitars, keyboard instruments and general recording.

Available  
Now  
**£1.20**  
POST PAID

*(Please allow at least 2 weeks for delivery)*

*If you do not wish to mutilate your copy of the magazine, please send your order on a separate sheet.*

To: Practical Electronics  
IPC Magazines Ltd., Receiving Cashiers Dept.,  
King's Reach Tower, Stamford Street, London SE1 9LS

Please send me ..... copy(ies) of  
"Sound Design". I enclose a Postal Order/Cheque  
for £1.20 (post paid) or (state amount for  
more than one copy) ..... (£2.35 post paid  
for 2 copies)

PLEASE WRITE IN BLOCK LETTERS

Name .....

Address .....

Post code .....

*Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only. PE.81*

*Company registered in England. Regd. No. 53626.  
A subsidiary of Reed International Limited.*

# News Briefs

## MICRO-MUSCLE THROUGH COMPILERS

As microprocessor based systems are doubtless going to be designed into ever more complex systems as time goes by, Zilog, with the introduction of high level Cobol and Fortran compilers, plan to have six languages for all of its microprocessors, including the familiar Z80. Business and scientific versions of Basic, and two members of Zilog's own high level family of systems orientated languages (called PLZ), have recently been announced. High level languages, it is felt, will be absolutely essential in the next few years. "If you don't offer them", declared Ralph K. Ungerman, who is the company's executive vice-president, "you'll be locked out of the market!"

Since software generally amounts to most of the cost in microcomputer systems, Zilog have established the PLZ family to meet three basic criteria: Although high level, the language has to be able to get into the architecture of the machine and deal with interrupts. It also has to generate efficient codes because of a microcomputer's limited address capability. And finally, the compiler must be simple to implement, since a micro system has limited memory.

The full power of the Z80 is made available to you using the PLZ/ASM assembly language, and the common syntax among the PLZ programs should be easy for someone familiar with any Algol-like language.

## LASER RECORDER

FOR space photography, RCA has provided NASA with a laser beam recorder which generates images from all of the U.S. space agency's satellite sensors, resulting in higher quality and faster production of photographs.

Called the Operational Laser Beam Recorder (OLBR), it will be the primary photo production system at NASA's Goddard Space Flight Center. The OLBR can generate images requiring up to 20,000 picture elements per line.

NASA also has installed an RCA computerised pre-processing system to enhance the quality of the Return Beam Vidicon (RBV) camera signals from Landsat satellites which photograph the earth's resources. The OLBR and the pre-processing system allow rapid production of RBV colour composite photos that are of quality previously considered unattainable, according to RCA officials.

The OLBR is completely self-contained and self-calibrated, and is operated and maintained by a single operator. It controls, selects and accepts digital image data from high-density tape and transforms it into high resolution, geometrically and radiometrically correct, annotated latent images on 214mm strip film. The film then is developed and processed at Goddard to produce high resolution transparencies which are distributed to Landsat data subscribers throughout the world.

The film recorder subsystem accepts the timed and formatted digital words representing the picture elements and performs digital to analogue conversion and video signal processing. The processed video drives the modulation and scanning film transport subsystem which exposes the film with a shared spot, one scan at a time. All electro-mechanical adjustments and optical path film transport are of the highest possible precision to assure long-term repeatability and freedom from drifts which could affect image quality.

The preprocessor system is claimed to be unique because it provides both completely automatic and interactive handling of RBV data collected on tape at Landsat receiving sites in Alaska, California and at Goddard. Wideband video tapes are quickly analysed for quality with the locations of the

images automatically noted and indexed. The output of the system is a high-density digital tape and a computer tape summary indicating the tape contents to the operator. The high-density digital tape is the primary input to NASA's master data processing which, in turn, drives the OLBR.

## ACCURACY ON THE CARDS

THINK of cards. Postcards, bingo cards, computer cards, carton blanks, book covers, in fact units of anything thicker than paper, and *that* could include labels, plastics sheet, film, you name it. Now supposing you need to count large quantities of these, in stacks. Counting by weight or measurement is quick, maybe, but inaccurate. By hand? Not even quick! If you're in business you might give 5 per cent over the top to be on the safe side. This eats into margins; but short measure loses customers.

You could go in for complicated machinery which separates the stack one at a time, and then counts, or you could go in for a static opto-electronic counting system. Such a machine exists, called the Optomat 520 Card Counter made by Vacuumatic Ltd., of Harwich, Essex. A beam of light is projected onto the edge of the stack to be counted, and sensing of the Lambertian reflected light to activate multiple photocells is utilised to differentiate between the light and dark transitions, caused by individual sheets and spaces. These spaces, by the way, are encouraged by the application of a compressed air stream. The photocell outputs are amplified and filtered to obtain distinct steps which then drive an electronic counter. So easy!

One of the sheets is taken at the outset, and put into a gauge so that the thickness dial can be set to control the optical scanner. A twelve inch stack is then placed against the backplate, and with the press of a foot pedal and a two second wait, hey presto, the total count appears. It is claimed that a count of 25,000 can be made in one minute with 100 per cent accuracy, and the machine will work over a caliper range of 0.005 inches to 0.02 inches at the same speed. So, humans and weighing machines collect your cards.

## BLIND AUTOMATION

MOST human beings *look forward* to the sun coming out, but a new compact control system, the Junior 10, has been developed for use with sun blinds mounted on the outside of buildings by Solar Protection Equipment Ltd., a Hampshire-based company which specialises in the design and manufacture of equipment and systems to protect buildings from the effects of the sun. The new system was field tested in a range of applications where accurate, reliable automatic control of blinds, awnings and solar screens is needed.

The package consists of a light cell, anemometer, control unit, and features include a light level selector, a wind override, and adjustable delays to control the "in" and "out" response so that instant reaction to short duration cloud patterns is avoided. There are l.e.d.s to indicate when the selected wind and light levels have been reached.

The light intensity range is approximately 3,000 to 30,000 lux, and wind speed range from 2 to 40m/sec (Force 2 to 12). Time delays on the solar bands may be set from 30 seconds to 10 minutes for the "out" mode, and between 1 and 20 minutes for the "in" position. The response delay from when the wind threshold value is exceeded to activation of the raise mechanism is permanently set at 15 seconds. Actuation of the downward movement corresponds to the delay selected on the "out" mode of the solar band. There is a manual override facility for the solar function of the unit, but which, for safety reasons, does not by-pass anemometer-controlled functions.

The Junior 10 will provide automatic operation for any number of blinds or screens on a single façade of a building. Other Solar Protection Equipment units are available to automate blinds fitted on two or more façades. The system can be used with any type of existing or new installation where the blinds are powered by electric motors.

## IMPROVING BRITISH STANDARDS

**B**SI has published two further parts of BS 5428 *Methods for specifying and measuring the characteristics of sound system equipment*, a series of specifications covering the various major elements of audio equipment.

The first of the new publications is Part 3 *Microphones* which specifies the characteristics and methods of measurement for microphones used both in professional and domestic applications, notably wide band microphones, close-talking microphones and those used for normal speech.

Similar data is given in the second document, Part 11 *Loudspeakers*, which relates to systems comprising one or more loudspeaker elements and such relevant devices as built-in-cross-over filters, transformers and any other passive elements.

Both specifications are identical with the corresponding parts of the International Standard, IEC 268. Additional British Standards, now in course of preparation, will deal with *Performance specifications for high-fidelity audio equipment*.

BS 5428 Part 3 (Price £7.80) and Part 11 (Price £5.60), may be obtained from BSI Sales Department, 101 Pentonville Road, London N1 9ND.

## IMPROVING WORLD STANDARDS

**S**TAND to attention, you are about to be standardised still further, this time by the International Electrotechnical Commission (IEC), the organisation responsible for the preparation of worldwide standards in the electrical and electronic fields. They have just issued IEC Publication 268, Part Nine—*Sound System Equipment: Artificial Reverberation, Time Delay and Frequency Shift Equipment*—applicable to equipment commonly used for obtaining special effects on sound recording, broadcasting and public-address systems.

The latest standard now provides engineers with the list of characteristics to be specified for artificial reverberation equipment, broadly described as amplifiers designed for special purposes. In addition this publication includes not only reverberation times, frequency responses, ambient acoustical noise levels and echo and delay times, but also describes relevant methods of measurements. IEC standards for other amplifier characteristics are outlined in IEC Publication 268: *Sound System Equipment—Part Three: Sound System Amplifiers*.

# readout

## ... a selection from our postbag

Readers requiring a reply to any letter must include a stamped addressed envelope. We regret that we cannot answer any technical queries on the telephone.

### Word Cost

Sir—It seems to be a common misconception that the cost of a microprocessor increases with the size of the word.

The reverse is probably true if one's aim is to run useful programs rather than merely play with a toy.

A minimal useful system is a Central Processor Unit (CPU) plus a hex keyboard and a 4 digit hex display. For 4, 8 or 16 bit systems the cost difference is not likely to be very great. The real expense comes in buying a memory of useful size. For a given end result this last cost is likely to be least with the 16 bit system.

Program storage is approximately the same, at about 2 bytes for each instruction, for the 3 word sizes, but increased word size gives vast improvements in program efficiency. A single 2 byte instruction in the 16 bit system may equal as many as 20 instructions in 4 bits and somewhere in between for 8 bits. Programming is thus much simpler with less chance of errors and the saving in memory is immense.

Evaluation studies have shown that the National Pace 16 bit CPU offers the most to the beginner with aims for the future. It costs under £20, can work with both 8 and 16 bit data and, if necessary, will address up to 128 kilobytes of memory. One does not have to buy it all at once, as some writers have suggested with other CPUs, but can start with as little as 256 words, at about £10, and add as required

to any limit. A special feature of the Pace chip is the instruction set which seems especially designed for easy programming with hex machine code, permitting easy relocation of sub routines even in complex programs. It certainly seems easier to program than the various, much lauded, 8 bit CPUs.

R. G. Silson,  
Tring, Herts.

*Any readers with differing ideas?—Ed.*

### Cover Blow

Sir—As professional engineers of some standing, we are, to put it mildly, somewhat amused to see the May cover of P.E. The advertised article is for a TTL logic tester, yet on the cover photograph the tester is shown in "action" on a circuit containing CMOS logic.

This anomaly unfortunately confirms a few suspicions held by the writers regarding the integrated circuit industry; namely that CMOS is really TTL with a self-destruct facility.

Yours explosively,  
Messrs. Maclean and Stanbury,  
Brentwood.

*Well done lads. You may endorse our photographic licence as it was not thought that the numbering on the CMOS devices would show up so clearly. Full marks for our photographer.*

*Readers familiar with the Linear Capacitance Meter p.c.b. may have realised that the test clip was held over a blank area of board.—Ed.*

### TV Radiation

Sir—I note with interest the comments made in the May issue of Practical Electronics regarding the difficulties of establishing a Citizens Band service in the U.K.

Previously, I was indifferent to the proposal, but after reading the point raised in Industry Notebook, I am now wholeheartedly in favour!

It was stated that T.V. viewers in the U.S.A. were being subjected to interference from CB sets, and that Texas Instruments, in conjunction with the FCC were developing a high performance T.V. receiver less susceptible to such interference.

Speaking as a short wave listener, I would welcome any proposal to reduce interference from T.V. sets, and clear the airwaves of the pollution they produce. Everywhere you look, it is emphasised that no disruption of T.V. viewing is to be caused by any electrical or electronic equipment, but the problem of radiation from T.V. receivers is never mentioned. It is the age-old dual standard rearing its ugly head again, one law for the powerful, and another for the weak. To be blunt, I would rather allow C.B.'ers a couple of MHz airspace than be deprived, as I am at present, of five MHz which is totally submerged beneath a sea of T.V. radiation, and I am sure there are thousands like me.

Steve Price,  
Doncaster, Yorks.

# Tomorrow's Broadcasting

## THE TECHNICAL POSSIBILITIES

**DR. BORIS TOWNSEND**, Head of the IBA's Engineering Information Service, gave the first of this year's IBA Lectures at the Authority's headquarters in February of this year; this feature is based on his lecture.

ONE sees clearly the road a few yards ahead, makes out the shape of the cross-roads shortly to be reached, and even discerns the outlines of the hills in the distance. So whereabouts on our journey through time are we now? From where does our future begin?

We nightly bring into the majority of our homes pictures and sound which are beautiful to the eye and a delight to the ear, and often to the intellect, at a price which most of us could once afford. I think our broadcasting is great! We roam the earth at will—not at our will, of course, but at the will of the programme director.

But it has to be said categorically that, in the same way as America has the largest backlog of antiquated technology of any country in history, so we are stuck with old-fashioned television transmissions which are a hybrid rag-bag of improvisation and almost incompatible technologies, which carry a quite unnecessary amount of repetitive data yet still reproduce inadequate detail, inadequate contrast, inadequate colour gamut, and pictures which lack most of the attributes of real life. It is a system which gives the viewer and listener little choice and to which any graduate tea-boy engineer could now suggest improvement.

What are we going to do about it? In the next few years— not much. We did something about our equally out-moded radio transmissions, and duplicated our use of precious wavelengths with our stereo f.m. transmissions using circular polarisation. These transmissions are glorious. What happened? Nothing! The public ignored them. Everyone still listens on antiquated amplitude modulation receivers— statistically, so to speak. But engineers are not easily discouraged.


## SMALL IS BEAUTIFUL—AND CHEAP

As an expatriate Londoner perhaps you will forgive me if I quote my favourite piece of London graffiti: "God is not dead—he is alive and well and working on a less ambitious project!" The same goes for engineers.

The other end of the television system from the home and hearth is, to engineers, more amenable to radical change. And radical the change is going to be.

Engineers are making a two-pronged thrust forward. One is a miniaturisation of the analogue techniques which have been used in our studios since Savoy Place and Alexandra Palace, while the other is based not on smooth, continuous signal waveforms but on abrupt discontinuities, or digits. Both advances are dependent on the new technology of micro-electronics.

It is not possible to live in a developed country in 1978 and be unaware of the incredible reduction in the size of electronic circuits which has been made in the last decade. Gone are the separate valves, resistors, condensers and wires of yesterday. Today's large-scale integrated semi-conductor micro-circuit can house thousands of individual electronic components on a small chip of silicon the size of a screw head.

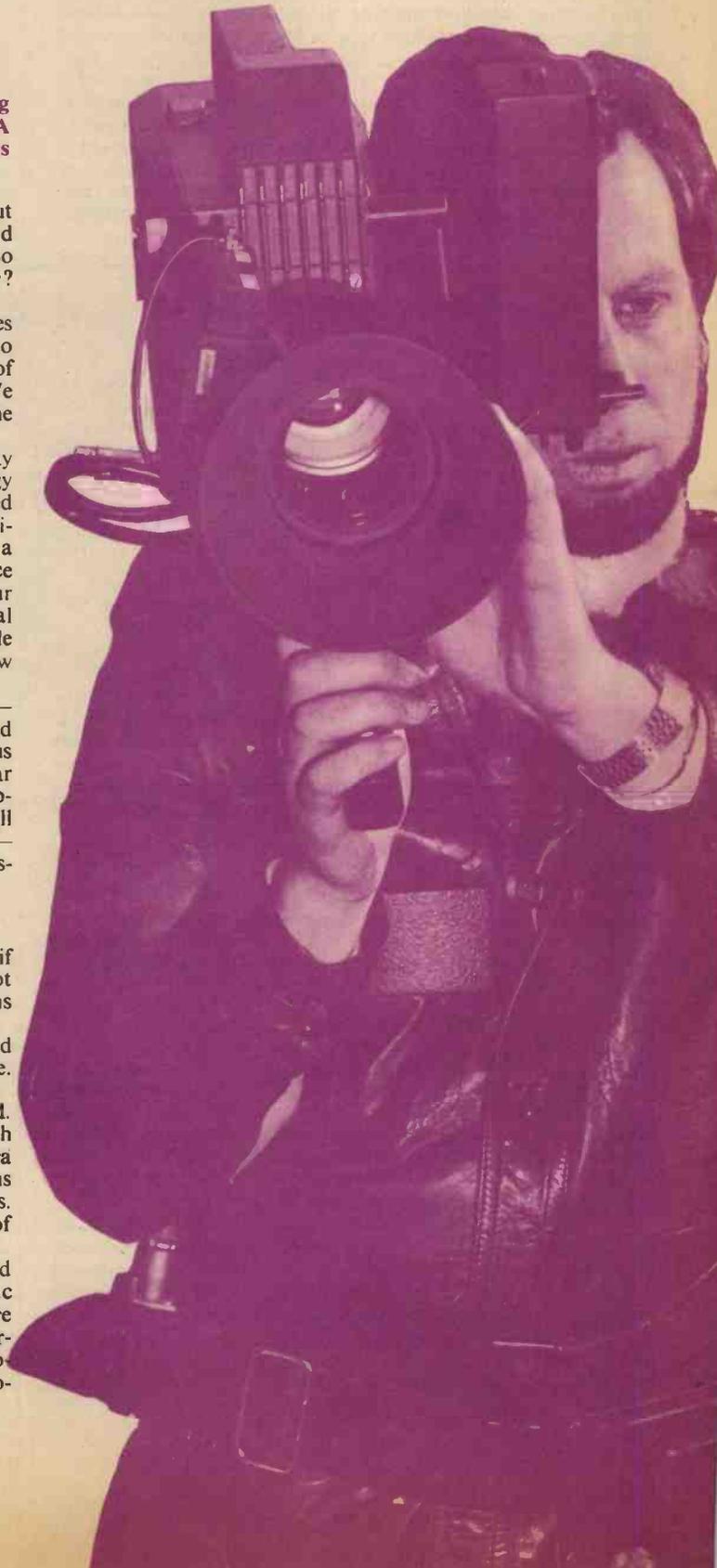

With small size comes a reduction in the cost of materials, a reduction in weight, usually a reduction in power consumption and a reduction in operating time, since the signals moving through the circuits have less distance to travel. The failure rate also falls since the number of mechanical or soldered joints and the opportunities for operator mistakes are alike reduced. The cost of making an integrated circuit is proportional to its area and is more or less independent of its circuit complexity. The reduction in cost is staggering. An integrated circuit now costs about the same as an apple. As a result it is now practicable on the one hand to undertake electrical processes and functions of great complexity, and on the other hand to mass-produce cheaply for the home, devices which were once only to be found in capital-intensive studios.

Will this trend continue? It can. The latest microcircuits are approaching size-reduction limits imposed on the photo-etching process by the wavelength of light—that is to say, individual parts of the circuit are not more than a few wavelengths of light in size. Further reductions require radiations of shorter wavelengths than light, and laboratories are currently utilising ultra-violet, X-rays, and electron-beam pattern-generation machines to continue this reduction in size. It is an industry which is aiming at a dimensional precision two orders better than that to which mechanical engineering machine shops can work.

### MECHANISMS INTO MICROCIRCUITS

Which brings me to a point of fundamental importance in our forecasting. The more recent history of manufacturing industry is that, despite the advantages of large-scale production and the replacement of labour by automatic machines, mechanisms grow more and more expensive to produce, while electronics become cheaper and cheaper.

Compare the £70 monochrome television receiver, of dubious performance, which sold in 1938, with its contemporary £100 small motor-car: and then take today's large, bright, reliable monochrome television receiver, still at £70, and its contemporary £2,000 mini. So whenever we can replace mechanisms by electronics we shall. Whenever we can transfer a problem from the mechanical domain into the electronic domain, we shall—and indeed already do.

These tiny microcircuits already make broadcasting equipment portable in a sense little dreamt of by the early pioneers. Every swinging teenager has the ability to make an audio broadcast tape of better quality than the phone-in programmes we permit. Sophisticated editing is possible in anyone's back-room, while multitrack tape-recording and its subsequent re-processing can restore a semblance of professionalism to any amateur pop group. All this opens up new avenues of exploration to enterprising programme directors. And a parallel development is going to take place in television. Yet there are still surprising weaknesses in the equipment available for radio reporting, as will be testified by roving radio news crews attempting to establish a link back to base, or even to aim a microphone at an American President.

### ENG

In television, the evolutionary reduction in size and weight of television equipment has produced a revolutionary change in the medium, for as Valéry said, rephrasing Engels—similar figures exist only in pure geometry. Small, electronic, colour-cameras of low power-consumption are now in production and are giving immediate world coverage of important news events. These Electronic News Gathering developments will spread to the field production of drama and even to light entertainment programmes. If we wanted so to do, we could now operate a television service without much in the way of television studio complexes.

An essential ingredient of this light-weight facility is a portable battery-operated colour video-tape-recorder. Now to make satisfactory replays of colour video-tape-recordings the machine has to work to a timing accuracy of around one

thousandth part of one millionth of a second. It is not possible to pull a magnetic tape through a VTR with this precision, even on a massive and expensive studio machine and certainly not on a small portable recorder subject to the gyroscopic effects of being carried or even of being used on a motor-cycle.


The technological solution has been to transcend the problem by abandoning the attempt to make such a precision mechanism. Instead, we make a small, cheap tape-transport mechanism and then correct all the recorded and replay timing-errors electronically, and subsequently, back at base—a typical example of our foresaking mechanisms for microcircuits. The ability to carry out this electronic correction in a Time Base Corrector depends not only on a high complexity of microcircuits but also on the digital techniques of the second prong of our forward development thrust—of which more in a moment.

ENG equipment is now sufficiently automatic to be used by any sensible person—providing maintenance back-up is available. Thus, last year, when NBC was suffering a technicians' strike, the manager of one station gave two of his girl secretaries half-an-hour's instruction in the use of the ENG equipment and then sent them out to cover a story—which was later transmitted. This is not so much a cautionary tale for strikers and strike-breakers but more an encouragement to all actual and budding directors. Television programme-making is no longer necessarily capital intensive. Television directors need no longer rant about there being 20 engineers between them and their actors, while programme-makers are no longer dependent on the owners of expensive studio complexes for permission to ply their trade.
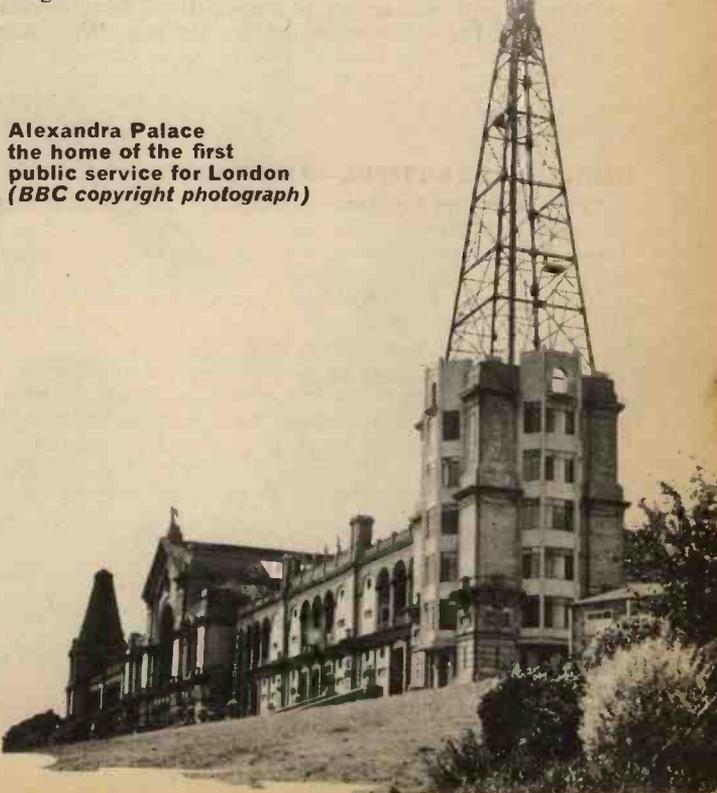
### FILM

Whilst I am still talking about analogue television I should not ignore film. CBS, of course, would say "Why not?—film has gone from television!" As a forecast rather than a contemporary fact, CBS may have it right. But I cannot refrain from observing that the period of greatest innovation in the history of the sailing boat was in the 50 years following the invention of the steamship. We have not heard the last of film. I have held in the palm of one hand a working prototype of a professional 16mm film camera which is so much smaller than any 3-tube electronic camera that the uncommitted observer is bound to say, why all the fuss about light-weight ENG?

Alexandra Palace  
the home of the first  
public service for London  
(BBC copyright photograph)



Certainly, live ENG is more immediate than film—but most ENG is not live. Film processing times are already shorter than the average time between ENG recording and ENG transmission, whilst Dr Land has demonstrated more or less instant-processing polaroid colour cine film using an additive colour process.

It may be that electronics, rather than killing off film, will save it; for as our electronic picture processing becomes more sophisticated, so we can rescue film from its own defects of colour mistracking, variable colour grading, frame bounce, spots, even grain—but we may not wish to do so.

## DIGITS

But I keep straying, inevitably, in this review of where our technology is at the moment, into the second prong of our forward development thrust, which is based on computer technology. From continuously varying analogue signals in the studio and network we are about to change over to trains of constant amplitude pulses—to digital radio and digital television, using components developed for defence and for computers. Why?—you may ask. Are our pictures going to be sharper, or more colourful, or bigger, or be stereoscopic? Is our sound going to encompass a wider frequency range or have more attack? The honest answer is NO.

Certainly digital signals will travel long distances better than analogue signals; that is to say, with less distortion and without picking up noise *en route*. Certainly digital—or television-by-numbers—equipment can eliminate the line-up time of studio equipment and can reduce maintenance routines; however, for most of our present-day studio processes, digits do not yet offer any cost saving. Certainly they permit us to undertake an incredible range of picture processing and correction and special effects.

## DICE

Digits enabled us to put into everyday operation, some five years ago, an all-electronic colour-picture standards-converter to change programmes from the American System to the British System, and conversely, using electronic arithmetic. This converter, named DICE, needed the equivalent of some five million valves, packed into a space about the size of a wardrobe. In Venice last April we demonstrated to the Technical Committee of the European Broadcasting Union most of the components of an all-digital television studio; and we are now negotiating licences for the manufacture of digital video-tape-recorders to our IBA patents.


Almost anything goes in the field of special effects, including compressing and inserting one camera picture into part of another, flipping the picture about an axis, reprocessing ENG signals to remove noise, and most of the other defects due to simple cameras, and lots of other processes which engineers had long regarded as impracticable. And, unlike film special effects, the results are available immediately.

Digital pulses also enable us to add services to our existing broadcasts. By placing a string or two of fast pulse trains in the upper blank margin of our television pictures, engineers have given us a new information service—our ORACLE Teletext service, complete with simple computer graphics as well as typefaces. It uses a great deal of computer technology both at the studio and in the home receiver. Although the receiver ORACLE circuits are much more complex than all the rest of the colour set put together, the additional cost of the ORACLE decoder is going to fall well below the cost of the colour receiver alone.
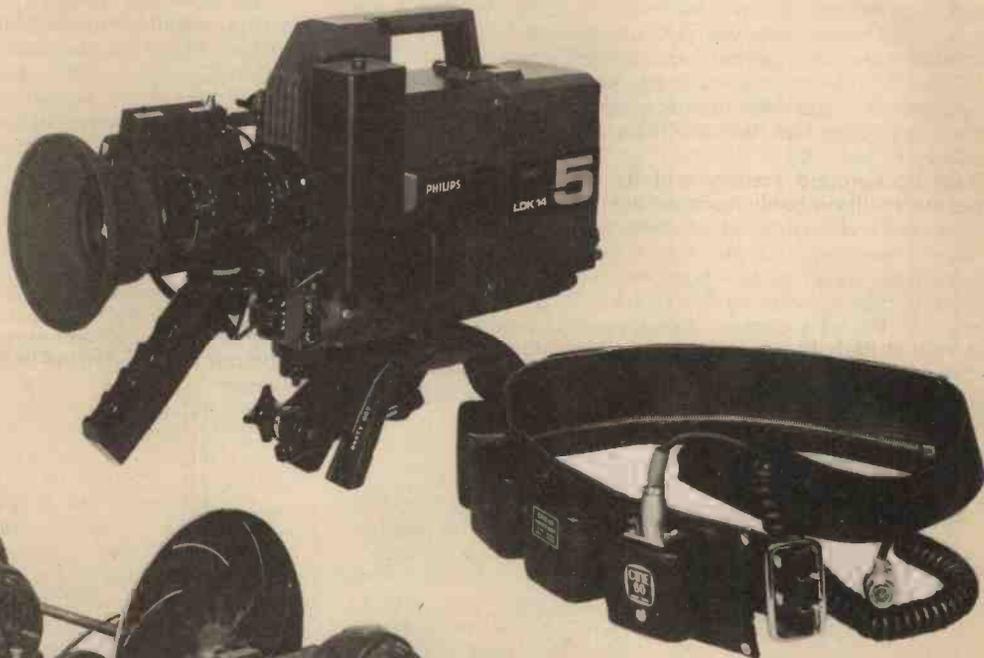
## MICROPROCESSED NETWORKS

Computer technology can make decisive inroads into television operations as well as into television signals. The microprocessor, which is the central brain of computers, is now controlling many routine functions in television as well as in industry at large. It is this kind of innovative technology,

The Philips LDK14  
ENG/EFP Camera  
and battery belt



A replica of the TV camera with which John Logie Baird first demonstrated his system in 1926. From the IBA Broadcasting Gallery. Compare this with the ENG camera above

and the management which is needed with it, that enables us to operate and maintain 400 transmitters with the same number of staff as we needed for only 40 transmitters some dozen or so years ago.

The automation of our network continues at an increasing pace. In the next few years we shall reduce the control rooms for our country-wide transmitter network from fourteen to four. Our new Regional Operations Centre, or ROC, at Croydon is controlling and monitoring some sixteen main stations with their nineteen relay transmitters stretching from the Channel Islands to the Wash.

Microprocessors measure the signals pouring out from our transmitters and then display on our central television monitors, which are now more like computer-type visual display screens, not only data on the state of our transmissions, but coloured computer graphics of the circuits of any faulty transmitter, the fault diagnosis, the action which the transmitter may have already taken to cure its own problem, or the recommended repair procedure if human intervention is called for. This is all daily, routine, run-of-the-mill operations for us. This is our IBA present, the base from which I shall be leaping into the future. Of course, it will be a radio future as well as a television future.

In radio, engineers are experimenting with surround sound systems as the next step forward from stereophonic sound—or perhaps I should describe it as a step backwards from two loudspeakers in front to two more behind you. Our ILR companies have already made several successful quadraphonic broadcasts.

## NEW STUDIOS

In television studios the 2 inch quadruplex video-tape-recorder is now clearly in its death throes, and will shortly be delegated to archival replay only. The 1 inch analogue helical scan recorders offer reductions in capital and running costs but will not have time to replace the 2 inch quadruplex machines before the 1 inch digital recorders get into large-scale production.

Digital telecine machines with one-line readouts and simple mechanical transports with zero line-up time will appear. The studio camera pedestal can give way to the stabilised hand-held camera, and studio floors can develop ridges if they like, while developments in fade-reduction techniques for radio-microphones, together with a marked reduction in their size, will eliminate, at long last, the boom shadow.

Real background scenery will be unnecessary, although super-stars will probably insist on having it. Toy scenery and chroma-key techniques will do, with computer control of the scenery camera, which looks into the miniature stage through a periscope, keeping the perspective of the background correct as the foreground camera is crabbed. After a few years, even the toy scenery will disappear. The scenery camera will look at flatly lit photographs of the required background and the graphics computer will adjust the perspective and the shadows of the transmitted image as required.

Post-production editing will increase and clever micro-processor control systems will speed-up editing for both film and tape. The acceptance of more natural-looking lighting in television pictures will combine with continuous and simultaneous tape recording of the action as seen by each of several electronic cameras, with all cutting, mixing and editing taking place in the calm atmosphere of the post-production suite.

The technical need for special lighting for television will disappear. Already the Lincoln Centre in New York televises its theatre productions of the Metropolitan Opera on the simple basis that the cameras must not intrude on the audience, and that the lighting and stage production will be exactly those which the stage director wants for his theatre audience; that is to say, many scenes have a huge contrast range and the mean lighting level between scenes ranges from deep gloom to high intensity. The severe technical constraints thus placed on the television crew are giving rise to novel signal-processing ideas of wide application. By 1984, cameras

Internal view of the LDK14 camera



will automatically produce suitable television pictures almost regardless of the scene lighting.

Microprocessors and computers can play a major role in studios as well as in networks. Several broadcasters have already built very large studio complexes in which the technical facilities are assigned between studios by computer. It is technically feasible to operate the whole television system from VTR and telecine replay, through the continuity suite and master control, to network switching and transmitter, under the immediate control of computers rather than operators. The day's transmission schedule can be compiled in the computer memory over the preceding fortnight or so, item by item, as convenient. On the day itself, the computer will give a running commentary to the presentation controller on what it is doing, and on what it is going to do, and on the optimum way of slotting-in last minute re-arrangements.

International discussions are going on about standardising the coded data which should be placed on the leader of every recorded programme to ensure correct transmission from automatic studios anywhere in the world, once the machine-minders have loaded the reel onto a replay machine—any replay machine. If the machine-minders put it on the wrong machine, the computer will merely change the machine assignments. If they don't put it on any machine, then the computer will ring alarms in the rest room as transmission time approaches, and will indicate the immediate action which it requires of the humans.

## DESIGNING ENGINEERS OUT

The design engineers will engineer the operational engineers out of television. The design engineers will also engineer the scenery makers and the graphic designers out of television, with chroma-key, Magicam, electronic captions and even more sophisticated electronic graphics-generators. It will be possible to quadruple the output of a graphics designer by giving him an electronic drawing board. By moving his

electronic pen over his action area he will instruct a computer to store his design and/or display it on television monitors. The designer will be able to ask the machine to do it again in a different colour, to draw it larger or smaller, to replicate the design twenty times around the edge of the frame, or to add the company logo, or to overlay any other design which he already has in the machine store, or to show it from a different perspective, or with different lighting.

Design engineers are also designing maintenance engineers out of television. One large television equipment manufacturer with a world-wide market is considering building into its products a self-diagnostic fault-analysis routine so that if one of its video-tape machines, say in the remoter parts of the Upper Volta, is too sophisticated for the local operator to handle, then the factory computer can interrogate the Upper Volta VTR via a satellite. The factory computer will then either adjust the remote television machine or will instruct the overseas human operator on which module to replace. The faulty module will then be airmailed back to the factory for repair.

### π IN THE SKY?

Satellites, of course, are going to play an increasingly important role in television, despite the fact that the geostationary orbit already has some 400 man-made objects in its rather narrow equatorial annulus. We are only two years or so away from our ENG crews being able to send their news pictures straight into the sky, to a satellite, for immediate world-wide distribution, rather than going through the slow and tedious procedures of arranging terrestrial links with their PTTs.

Networked programmes can be fed to our earthbound television and radio transmitters from a satellite in space, which could be cheaper than paying Post Office charges for terrestrial links. It is clear that direct broadcasting from satellites straight into everyone's home will become practicable in the 1980s. The service is already planned. Five television channels in the 12GHz frequency band have been allocated to each European country. The heavy-platform satellite will be launched in 1981, carrying sufficient power generation to lay down adequately strong signals in European homes, and a year later it will begin to do precisely that, with television programmes.

### TELEVISION SET FOR TELEVISION?

By the 1980s we can also expect the domestic television receiver to be as much a computer visual display unit as it is a television set and television will face even more competition than does radio. Microprocessors and LSIs will turn this colour VDU into an indoor games centre, covering everything from chess to clay pigeon shooting; children could do their homework on it and perhaps hand-in a magnetic print-out to their teacher next day, eliminating complaints about illegible hand-writing, and permitting machine checking of the answers. It could be that the television set will be in continual use—but rarely for television, for domestic video recorders and domestic video disc players will be commonplace. I forecast further improvements in receiver safety and reliability, and that we shall have no hesitation in leaving our home equipment running all night.

All transmissions will carry coded pulses identifying themselves and their programme classification. It will be practicable to instruct the home recorder to record automatically our own selection of programmes or any programmes bearing a specified teletext code, to be stored ready for viewing, as convenient.

Thus the recorder could play back to us over breakfast our own telenews paper with a make-up previously decided by ourselves, such as only news items concerned with football or the international price of tin, or the Middle East situation. Our transmitters and studios could run all night churning out recorded, labelled, programmes mixed with live news reports, while our domestic recorder compiled our own minority-taste programmes. Of course, one of the ORACLE Teletext

pages will be providing captions to the programmes for the benefit of the hard of hearing.

I am saying that we could now take broadcasting out of real time, with a more convenient service to everyone, better utilisation of our capital investment in transmitters and receivers, and a better service to minority viewers and listeners. It seems to me that our development engineers may do more to save the Welsh language by keeping our transmitters on-air throughout the night, than do those who put them off-air in the evening.

### WANTED

What of things which we may not have in the 1980s? At the moment I see no signs of a large, bright, practical, flat semi-conductor colour television display screen. We are waiting for the unpredictable breakthrough in material technology, which I expect to come in the middle of the next decade.


I see no indication that anyone is anxious to have 3-D television, although it is practicable with small screens if the viewer will wear polaroid spectacles, while the more dreamy-eyed physicists can visualise moving colour pictures in depth using holography.

An improved light valve, and practical methods of scanning laser beams, are still awaited; but perhaps the race for a better television display will be won by a fast-acting colour liquid-crystal display. Very fast, but dim, light modulators are already in use as sending-transducers in fibre-optic communication channels.

The cheapness of such glass telecommunication cables will make it economical to provide a wideband communication channel into every home, perhaps with a two-way interactive connection back to the local exchange. But I see no effective use of such a system until we have small, very high-density, electronic memories with multiple simultaneous access, so that central television programme libraries become practicable. Considerable research is in progress into such memories, for both defence and the computer industry, but I do not see it happening until the 1990s. When it does, we may need to redefine the terms "wireless" and "broadcasting".
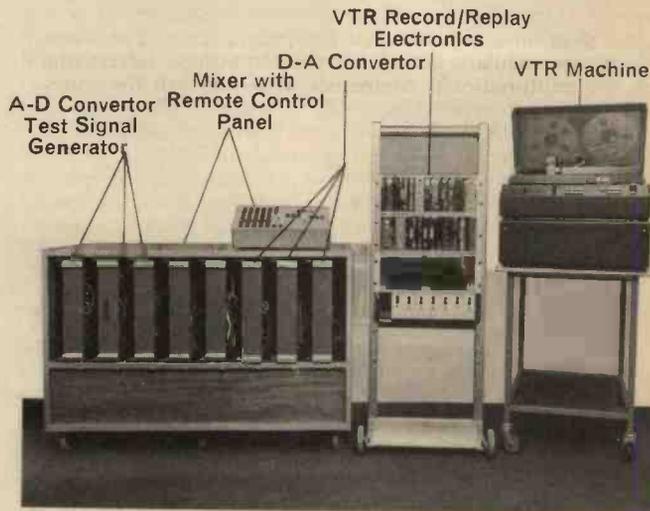
### RADIORACLE

Our radio transmissions will carry additional pulses to indicate on the receiver tuning display the name and frequency of the station we are tuned to—further pulses will be relayed from the radio to our visual display unit—sorry, part-time television set—to give us sleeve notes on the music being played, or the developing synopsis of the radio drama for the benefit of those listeners who missed the beginning of the story; that is to say, a form of RADIORACLE.



Experimental digital video recording systems developed by the IBA

I expect to see further development of our medium-wave radio. It is possible to extend the top note response of medium-wave radio reception in an artificial but adequate manner, and it is also possible to transmit stereo on medium-wave.

It will be possible to provide out-of-city radio to motorists from a broadcasting radio satellite, but further advances in receiver aerial design are needed and will take a few years to develop. However, this could be the cheapest way of providing multi-channel radio services designed for motorists.

### SMALL IS DEMOCRATIC

The television technical developments which I am forecasting carry with them their specific logic for their own exploitation, and I see two quite different forms of television service emerging.

Firstly, any local community will be able to produce its own television news and local affairs programmes, and intersperse them with old films or even dramas shot in the neighbouring National Trust Property. The small light-weight equipment, backed-up by magic black-boxes of electronics which remove all the picture defects of the tiny cameras and recorders, will be combined with cassette video recorders and video disc players to give us community television, using transmission frequencies in, or just above, our current u.h.f. bands.

Such community-television studios will be modelled on our successful Independent Local Radio stations, for it will be technically feasible to operate a television company with not much more equipment than one of our present-day ILR stations. The IBA Quality Control engineer will call to carry out regular tests on the magic black-box picture processor to ensure that the station output meets our engineering Code of Practice. The sales staff will carry ENG equipment in their cars, and between calls on advertisers will cover the local action, such as it may be. Small, in television, will be beautiful, local, democratic and very profitable.

### EUROPEAN PROGRAMME COMPLEX


The second option which I see unfolding before us is very different, but is also based on the inexorable logic of the new technologies. A geostationary broadcasting satellite, positioned over Uganda with a reasonable northward-facing aerial, can see at least half-a-billion viewers. This size of ad-mass is worthy of a moment's thoughtful contemplation. Half a billion. There is no technical difficulty in associating numerous sound channels with each of the vision programmes, and each sound channel can be in a different language.

The size of such an audience warrants spending prodigious sums on international spectaculars, which I expect to see produced in a massive computer-run television complex equipped with every technical refinement, including security against electronic hi-jacking of the programmes. The international spectaculars would carry international advertising from the multi-national companies. It would call for entrepreneurs of stature, but then we have them in ITV.

Although I have only strayed into the middle of the next decade in my forecasting, I am already into a "Gee Whiz" situation, and I have ignored the two or three unpredictable breakthroughs in basic science and materials engineering which we can reasonably and statistically expect in this period. One could assert that there will be nothing remarkable in the 1980s, because almost anything we wish to do with our technology will be feasible. We shall have lost our ability to impress ourselves.
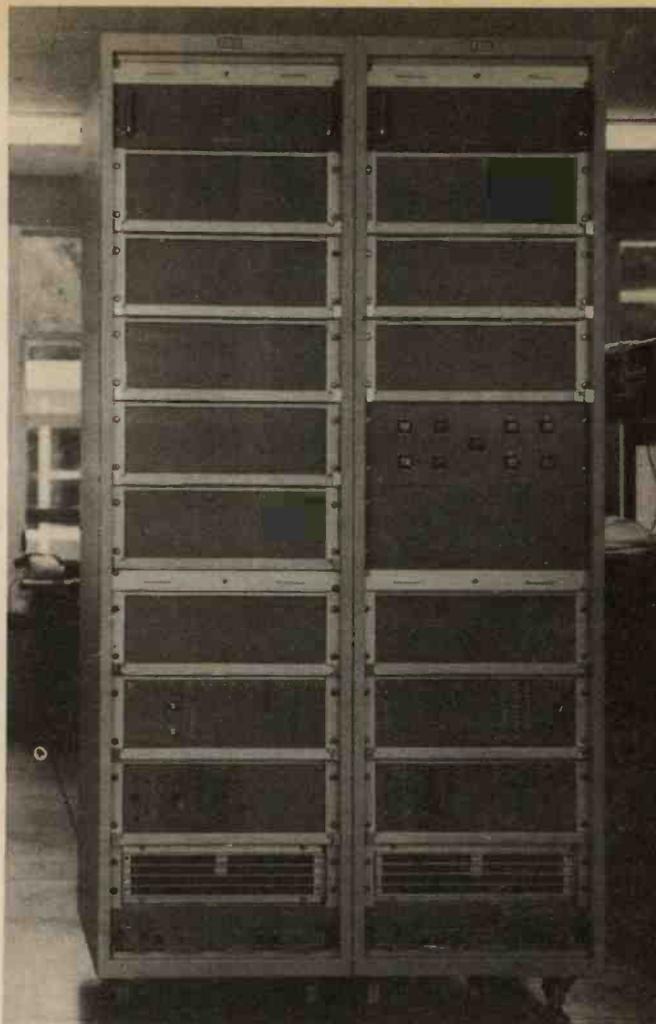
### 1984

But one of the things we may have to do by 1984 is to replan our then obsolete v.h.f. 405-line monochrome transmissions. I expect that we shall lose the use of these frequencies for television, which will be a pity, for Band III has excellent propagation characteristics for our purposes. Nevertheless, I expect the engineers to put up a case for a new television service in the band using the latest technologies—that is to



The DICE colour picture standards converter

say, they will propose a type of service which is an advance in engineering terms; for example, better definition, more scanning lines, larger pictures, tone gradation scales tailored to human physiology (and I hope a certain technical flexibility to make television more helpful in teaching the handicapped child with abnormal physiology).

### 1989

Our technology has reached a rather exciting stage—a very democratic stage—an open stage. Television research engineers have some powerful technologies at their disposal, and organisational methods which enable them to move fast in meeting a demand. The question is no longer "What is possible?" We have to decide between a bewildering array of possibilities. Almost anything materialistic is now technically plausible. The problem for us is of a distinctly different character from the problem facing Nipkow. And it seems to me that it is not a problem which should be left to engineers.

It is no longer a question of what can the engineers do? It is a case of what will the programme makers of the 1980s want? What will the governments of the 1980s permit? What will the public of the 1980s pay for? Who will tell us? Or is everyone saying with Thurber "Progress is all very well, but it has gone on long enough!"?

My own inclination is to tell the engineers to press on and take their own foolhardy decisions, for I believe with Francis Bacon that truth comes out of error more readily than out of confusion. But at least you should know that engineers are listening for an answer. ★

# Semiconductor UPDATE...

FEATURING : ICH 8510/20/30 NE590/591

R. W. Coles

## HORSEPOWER DRIVER

The ready availability of pre-packaged analogue circuit blocks (for example the 741 operational amplifier) has made it possible for anyone who can read a data sheet to become a designer in what used to be a difficult and complex field. The new found ability to carry out system level design has done a lot to make our hobby more rewarding, and so any extension of the "building-block" principle into new areas is always welcome.

The trouble is that the system design approach has its limitations. There are always problems turning up which cannot be solved with off-the-shelf integrated circuits, and at this point we can sometimes feel our design knowledge wearing a bit thin!

Consider the problem of building an operational amplifier which can source and sink not the few milliamps of the 741, but let's say a couple of amps to drive a d.c. servo motor. You could of course hang a couple of Darlington transistors on the output of a 741 and perhaps even build in some fancy current limiting circuitry to stop the thing exploding when the motor stalls, but this would mean quite a lot of work, even if you knew how!

Well this is one particular problem which need not stump you anymore thanks to Intersil who have brought out a sort of hairy-chested 741 which, in one of its three versions, can deliver 2.7 amps with a 48 volt output swing. Coded ICH 8510/20/30, the new circuits are mounted in eight lead TO3 power transistor packages and feature full short circuit protection so that they can be used to drive up to 0.1 horsepower motors as well as solenoids, actuators and what-have-you.

Inside the can is not a single monolithic chip but a standard 741 chip married with a special driver chip on a beryllium oxide substrate to form what is termed a hybrid circuit.

## DIGITALLY PROGRAMMABLE P.S.U.

One particular application example in the data sheet attracted my attention; an ICH 8530 was shown connected to a digital to analogue converter (DAC) to provide a precision variable regulated d.c. power supply which could be programmed with an eight bit word over an output voltage range of minus 25 volts to plus 25 volts with a 3 amp output current rating. Using a binary coded decimal type DAC would enable thumbwheel switches to be used to set the output voltage, and with three decades, a 0.1 volt resolution could be achieved (Fig. 1).

If power supplies and motors are not your line, well these versatile building blocks make useful audio power amplifiers too!

## CHEAPER PORTS

When you start to get ambitious with your pet microprocessor, you will want to wire it up to all the switches, lamps, and lawn sprinklers which live in the outside world, and that means that you will want ports.

You will no doubt be tempted to use the all-powerful, programmable LSI parallel interface chips such as the Intel 8255A, which offers 24 I/O lines which can be programmed in groups of eight into any of three modes (Input-Output-Bidirectional).

If you need flexibility and relatively few I/O lines, this is the best choice, but if you need lots of inputs and outputs which are defined in advance, the job can be done much cheaper with standard TTL, if you know how!

TTL is best when you can justify around 64 input lines and 64 output lines as sixteen eight bit ports, and obviously not all applications need this sort of capability. For the inputs use eight SN74251 three-state-output, eight input, data selectors. Each input to a particular chip will form one line at a particular port address, the eight chips give the eight lines per port needed by most micros, and no additional address decoding will be needed.

Outputs have posed more of a problem until recently, because output information is only available on the bus for a short period, and therefore needs to be latched by the output port itself. Signetics have now introduced an ideal TTL solution to the output problem in the shape of their NE590 and NE591 eight bit addressable, latched, peripheral drivers which not only have the correct logical formulation but also the benefit of sturdy Darlington output stages which can sink (NE590) or source (NE591) up to 300 milliamps each.

The 590 comes in cheap sixteen pin d.i.l. form, like the SN74251, while the 591 uses an eighteen pin d.i.p. to allow the output stages to operate from a "higher-than Vcc" supply.

## CHIP CONNECTIONS

To use these chips, connect the three least significant bits of the address bus to the address inputs and use the appropriate control signal to drive CE which latches the data into the ports. As with the input scheme, each chip latches one bit for each port, and again no extra decoders are needed.

To ensure no random states at power on time, these new devices have a built in power-on-clear, and to keep your buses healthy, the inputs are of the low power type.

You should be able to get 64 in and 64 out for less than £15; compare that to the cost of LSI chips!

20	21	22	23	24	25	26	27	Bit	Vout
1	1	1	1	1	1	1	1	1	+25V
1	1	1	1	1	1	1	1	0	-25V
0	1	0	1	1	0	0	1	1	+15V
0	1	0	1	1	0	0	1	0	-15V
1	0	0	0	0	0	0	0	1	+0.098V
1	0	0	0	0	0	0	0	0	-0.098V

Etc.

The power supply can be set to  $\pm 0.1V$  d.c.

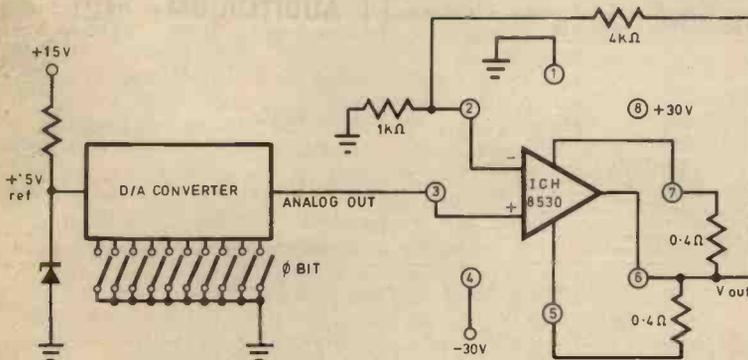


Fig. 1. A circuit which provides a precision power supply voltage. The switch program is shown in part on the right

**R.C.S. 10 WATT AMPLIFIER KIT**



This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume, bass and treble controls. Spec. 10W output into 8ohms. 7W into 15 ohms. Response 20c/s to 30Kc/s. Input 100M.V. high imp. Size 9 1/2 x 3 x 2 1/2 in. A/C mains operated.

Mono kit **£12.50** Stereo kit **£20.45p**  
Easy to build. Full instructions supplied.

**MONO PRE-AMPLIFIER**

A mains operated solid state pre-amplifier unit designed to compliment amplifiers with low level phono and tape input stages. This free standing cabinet incorporates circuitry for automatic R.I.A.A. equalisation on magnetic phono input and N.A.B. equalisation for tape heads. Power ON/OFF, PHONO/TAPE switches and pilot lamp are on the front panel; phono socket and input and output are rear located. AC mains 240V. Size 6 x 3 1/2 x 2 1/2 in.



**£4.50 ea. - 2 for £8.** Post 50p.



**ELAC SPEAKER 10 inch £4.50**  
Ribbed cone. Large ceramic magnet 50-16,000 c/s. Bass resonance 55 c/s. 10W. 15 ohm impedance.

**RCS STEREO PRE-AMP KIT.** All parts to build this pre-amp. Inputs for high, medium or low imp. per channel, with volume control and P.C. Board. Can be ganged to make multi-way mixers. **£2.95** Post 35p

**MAINS TRANSFORMERS**

	ALL POST 50p each
250-0-250V 70mA. 6-3, 2A	£3.45
250-0-250 80mA. 6-3V 3-5A. 6-3V 1A or 5V 2A	£4.60
350-0-350 80mA. 6-3V 3-5A. 6-3V 1A or 5V 2A	£5.80
300-0-300 120mA 2 x 6-3V 2A C.T.. 6-3V 2A	£8.50
220V 45mA. 6-3V 2A	£1.75
HEATER TRANS. 6-3V 3A. £1.45. 1/2 amp. £1.00	
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2A 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V	£5-30
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£5-30
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£8-50
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£11.00
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£14.50
5, 8, 10, 16V 1/2 A £2. 12V 100mA £1. 12V 300mA £1.	
12V 750mA £1.30. 40V 2A tapped 10V or 30V £2.95.	
20V 2A £2. 40V 2A £2.95. 30V 5A 34V 2A c.t. £2.75.	
2 x 16V 6A £9. 12-0-12V 2amp £2.95.	
20V 1A £2.95. 30V 1A £2.75. 20V 1A £2.20.	
8V 3 amp £2.78. 80V. 40V. 20V or 200-20V. 1A £2.50.	
30-0-30 2A £7. 3V 250mA £1.30.	
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V	
150W £5; 250W £6; 400W £7; 500W £8.	
CHARGER TRANSFORMERS. Input 200/250V for 6 or 12V	
1 1/2A £2.75; 4A £5.20.	
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs	
1 1/2A 40p; 2A 55p; 4A 95p. HALF WAVE 12V 1 1/2A 25p.	

**GOODMAN'S COMPACT 12in BASS WOOFER**

Standard 12in diameter fixing with cut sides 10 1/2in square. 14,000 gauss magnet. 30 watt r.m.s. 4 ohm impedance. Bass resonance: 30 c.p.s. Frequency response: 30-8,000 c.p.s. £10.95 each. Post £1.00. 20 Watt model £9.95.



**10 WATT PER CHANNEL STEREO AMPLIFIER** In chassis form. A.C. mains operated. Volume, balance, treble and bass slider controls. Pick up and tape inputs. Recording output. Socket. Front panel size: 16 1/2 x 1 1/2 in. Chassis size: 13 x 15in. Bargain **£18.50** Post 50p

**HEATING ELEMENTS WAFER THIN**


Size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos.

ONLY 40p EACH (FOUR FOR £1.50)

ALL POST PAID—Discounts for quantity.

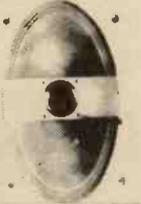**E.M.I. 13 1/2 x 8in SPEAKER SALE!**

With tweeter. And crossover. State 4 or 8 ohm.  
10W Model **£7.95** Post 45p  
15W model **£10.50** 8 ohms. Post 65p  
20W model **£11.50** 8 or 15 ohms. Post 75p



**TEAK VENEER HI-FI SPEAKER CABINETS**

MODEL "A" 20 x 13 x 12in. For 12in. dia. or 10in. speaker. Illustrated **£14.50** Post £1.60  
MODEL "B" BOOKSHELF For 13 x 8in. EMI **£8.50** Post £1 Loudspeakers. R.C.S. BOOKSHELF complete with speakers. Size 14 x 9 x 6in. approx. Response 50 to 14,000 cps  
12 watt rms 8 ohms **£19 pair** Post £1.50  
ACOUSTIC WADDING 18in. wide, 20p ft.



**BAKER MAJOR 12 INCH £15**



30-14,500 c/s. 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W.  
NOTE: 4 or 8 or 16 ohms available.

Module kit. 30-17,000 c/s with tweeter, crossover, baffle, 19 x 12in. Instructions. As illustrated. **£19**  
Please state 4 or 8 or 16 ohms. Post £1.60

**"BIG SOUND" BAKER SPEAKERS**

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos. Useful response 30-13,000 c/s. Bass Resonance 55 c/s.

**GROUP "25"**

12in 30W 4, 8 or 16 ohms. **£12** Post £1

**GROUP "35"**

12in 40W 4, 8 or 16 ohms. **£14** Post £1

**GROUP 50/12in**

12in 60W 4 or 8 or 16 ohms with aluminium presence dome. **£21** Post £1.60

**GROUP 50/15in**

15in 75W 8 or 16 ohms. **£26** Post £1.60

Disco, Group + PA Cabinets in stock. Send for Leaflet. Cabinet Fittings, Handles, Corners, Feet, Covering Material all in stock.

**BAKER 150 WATT ALL PURPOSE TRANSISTOR AMPLIFIER**

Ideal for Groups, Disco, P.A. and Musical Instruments. 4 inputs speech and music. 4 way mixing. Output 4/8/16 ohm. a.c. Mains 240V. Separate treble and bass controls. **£79** Carr. £1.50



**NEW "DISCO 100 WATT" £59**

ALL TRANSISTOR AMPLIFIER Carr. £1  
2 inputs. 4 outputs separate volume treble and bass controls. Ideal disco or slave amplifier chassis. Made by Jennings

**R.C.S. SOUND TO LIGHT DISPLAY MK II**

Complete kit of parts with R.C.S. printed circuit. Three 1000W channels. Will operate from 20mV signal source. CABINET extra £4. **KIT = £17.00**

**GOODMANS CONE TWEETER**

18,000 c/s. 25W 8 ohm. Price **£3.25**  
3 WAY CROSSOVER WITH TREBLE & MID RANGE CONTROLS. 50 WATT. £5 POST £1.

**R.C.S. 100 WATT VALVE AMPLIFIER CHASSIS**



Professional model. Four inputs Treble, Bass, Master Volume Controls. Ideal disco. P.A. or groups. S.A.E. for details. 5 speaker outputs. 3 or 8 or 15 ohm. 100V line to **£94** order. Suitable carrying case **£16.50** plus £2.50 carr.

**LOW VOLTAGE ELECTROLYTICS**  
1. 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p, 500mF 12V 15p; 25V 20p; 50V 30p; 100mF 12V 17p; 25V 35p; 50V 47p; 100V 70p; 200mF 6V 25p; 25V 42p; 2500mF 50V 62p; 3000mF 25V 47p; 50V 65p; 3900mF 100V £1.60; 4700mF 63V £1.20; 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 5600mF 76V £1.60; 12000/76V 80p.

**R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS**

All parts and instructions with Zener diode, printed circuit rectifiers and double wound mains transformer. Input 200/240V a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required. **£2.95** Post 45p

**ROBUST BLACK PLASTIC BOX £1.50**  
Size 6 1/2 x 3 1/2 x 2 1/2 in with brushed aluminium fascia. Ideal for constructional projects. Post 30p

**R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER—BRITISH MADE £1.45**

Ideal for Mike, Tape, P.U., Guitar. Battery 9-12V or H.T. line 200-300V d.c. operation. Size 1 1/2 x 1 1/2 x 1 1/2 in. 25 c/s to 25 kc/s. 26 dB gain. For valve or transistor equipment. Instructions supplied.

**ELECTRO MAGNETIC PENDULUM MECHANISM 95p** Post 30p

1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronome, strobe, etc.

**BSR AUTOCHANGER**

Plays 12in, 10in or 7in records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee, a.c. 200/250V. Size 13 1/2 x 1 1/2 in. Above motor board 3 1/2 in. Below motor board 2 1/2 in. With STEREO/MONO CARTRIDGE **£12.95** All Post 75p  
Single Player version **£15.50**  
BSR P128 with Magnetic Cartridge **£24.50**  
GARRARD AUTOCHANGER plays all records **£14.95**  
BSR P163 BELT DRIVE DECK, less cartridge **£27.50**  
GARRARD AP76 Single Player less cartridge **£27.50**



**BSR DE LUXE AUTOCHANGER**

Features balanced arm, Cueing device, stylus pressure gauge, 3 speed—plays all size records. Fitted with stereo ceramic cartridge. Size: 13 x 12in. Post £1.  
Or with Sonotone V100 magnetic cartridge **£21.50**



**R.C.S. DISCO DECK SINGLE RECORD PLAYER**  
Fitted with auto stop, stereo compatible cartridge. Baseplate. Size 11 x 8 1/2 in. Turntable. Size 7in diameter. a.c. mains. 220-250V. 3 speeds plays all size records **£7.95** Post 45p  
Two for £15. Post 75p.

**HEAVY METAL PLINTHS £6.50**

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Model "A": Size 12 1/2 x 14 1/2 x 7 1/2 in. Model "B": Size 16 x 13 1/2 x 7 1/2 in. £7.50.  
Extra Large Plinth and Cover, for transcript on decks. Size 20 x 17 1/2 x 8 in. uncut board. Shop callers only £18.50.

**TINTED PLASTIC COVERS ONLY**

Sizes: 16 1/2 x 12 1/2 x 4 1/2 in. £3.  
16 1/2 x 14 1/2 x 3 1/2 in. £3.75. 16 1/2 x 14 x 4 in. £4.  
15 x 13 1/2 x 3 1/2 in. £3.50. 17 1/2 x 9 1/2 x 3 1/2 in. £3.  
14 1/2 x 14 1/2 x 2 1/2 in. Rosenwood sides £4.  
Ideal for record decks, tape decks, etc. Post 75p.


**BAKER HI-FI SPEAKERS**

**HIGH QUALITY—BRITISH MADE**

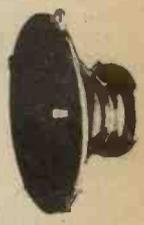**SUPERB £22**

12in 25 watt Post £1.60

Quality loudspeaker, low cone resonance ensures clear reproduction of the deepest bass. Special copper drive and concentric tweeter cone. Full range reproduction with remarkable efficiency in the upper register.  
Bass Resonance 25 c/s  
Flux Density 16,500 gauss  
Useful response 20-17,000 c/s  
8 or 16 ohms models



**AUDITORIUM £21**

12in 35 watt Post £1.60

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques.  
Bass Resonance 35 c/s  
Flux Density 15,000 gauss  
Useful response 25-16,000 c/s  
8 or 16 ohms models



**AUDITORIUM £26**

15in 45 watt Post £1.60

BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2 in. sides, 6 x 4 in. 95p; 8 x 6 in. £1.40; 10 x 7 in. £1.55; 14 x 9 in. £1.90; 16 x 6 in. £1.85; 12 x 3 in. £1.20; 16 x 10 in. £2.20; 12 x 8 in. £1.70.  
ALUMINIUM PANELS, 18 s.w.g. 6 x 4 in. 24p; 8 x 6 in. 38p; 10 x 7 in. 54p; 12 x 5 in. 50p; 12 x 8 in. 70p; 16 x 6 in. 70p; 14 x 9 in. 94p; 12 x 12 in. £1.16; 16 x 10 in. £1.16.  
ALUMINIUM ANGLE BRACKET, 6 x 1/2 x 1 in. 15p.  
ALUMINIUM BOXES, MANY SIZES IN STOCK  
4 x 2 x 2 in. 86p; 3 x 2 x 1 in. 85p; 6 x 4 x 2 in. 95p; 8 x 6 x 3 in. £1.50; 9 x 4 x 4 in. £1.70; 12 x 4 x 4 in. £1.95.

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. a.c. mains 200/240V Leaflet S.A.E. **£4.95** Post 50p



**RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K. Tel. 01-684 1665**

Minimum post 30p. Access/Eurocard and Barclaycard/Visa. Same day despatch. Radio Books and Components Lists 20p. Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)

# TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

## City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

## Diploma Courses

Colour T.V. Servicing  
Electronic Engineering & Maintenance  
Computer Engineering and Programming  
Radio, T.V. and Audio, Engineering & Servicing  
Electrical Engineering, Installations & Contracting

## Other Career Courses

A wide range of other technical and professional courses are available including GCE.

**FREE BOOK**

Post this coupon or 'phone today for free ICS careers guide.

Name \_\_\_\_\_

Address \_\_\_\_\_

Age \_\_\_\_\_

**ICS**

To ICS, Dept. 273W, Intertext House, London SW8 4UJ or telephone 01-622 9911 (all hours)

# ELECTROVALUE

All the many types of components we supply are BRAND NEW and guaranteed and only from manufacturers direct or approved suppliers. No surplus, no seconds

## CMOS - buffered and protected

4000 23p	4013 51p	4023 23p	4043 1.00	4081 23p
4001 23p	4014 1.04	4024 1.04	4044 94p	4082 26p
4002 23p	4015 1.14	4025 23p	4045 1.40	4510 1.42
4006 1.14	4016 51p	4026 1.75	4049 54p	4511 1.50
4007 23p	4017 1.14	4027 60p	4050 53p	4514 3.30
4008 99p	4018 1.32	4028 95p	4060 1.40	4516 1.44
4009 62p	4019 62p	4029 1.23	4069 30p	4518 1.26
4010 62p	4020 1.32	4030 51p	4070 50p	4520 1.26
4011 23p	4021 1.14	4041 84p	4071 26p	4543 1.30
4012 23p	4022 1.13	4042 96p	4072 26p	4583 1.45

## OUR COMPUTER TAKES GOOD CARE OF YOUR ORDERS

### SIEMENS CAPACITORS\*

World famous for quality and dependability - PCB TYPES - 7.5mm PCM 0.001 to 0.01 5p each; 0.15 to 0.047 6p ea. 5mm PCM 0.068, 0.1 7p, 0.22 10p. CERAMIC 2.5mm PCM 0.01, 0.022 4p; 0.033, 0.047 5p ea; 0.088 6p ea; 0.1 7p. ELECTROLYTICS - 1/100, 10/25, 10/63, 100/25, etc. For full range see our current lists.

### RESISTORS

1/2, 3/4 watts\* - 2p each; metal film, metal oxide and 1 watt carbon 5p ea; good quantity discounts. Magnetic field dependent from £1.50. Hall Effect from £1.23.

### SIEMENS TRANSISTORS

Silicon npn and pnp from 8p ea; LEDs, red 19p; yellow or green 23p (3 or 5mm); Photo transistors from 76p.

## KEEN PRICES ★ GOOD SERVICE ★ WIDE RANGES

### DISCOUNTS

5% if list value of order over £10

10% if list value of order over £25. Discounts available where cash (P.O. or cheque) is sent with order.

V.A.T. - Add 8% to value of order or 12 1/2% with items marked\* (No V.A.T. on overseas orders) Goods sent post free on C.W.O. orders in U.K. over £5 list value. If under, add 27p per order.

### MONTHLY BARGAIN LISTS

S.A.E. brings monthly list of bargains. Also current quick reference price list of all ranges.

Cash with order (P.O. or cheque payable to Electrovalue Ltd) or your Access or Barclaycard number.

TRADE AND INDUSTRIAL ENQUIRIES INVITED

For all round satisfaction - be safe - buy it from ELECTROVALUE


**ELECTROVALUE LTD**

Dept PE7, 28 St Judes Rd, Englefield Green, Egham, Surrey TW20 0HB.

Phone Egham 3603; Telex 264475.

Northern Branch (Personal shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.
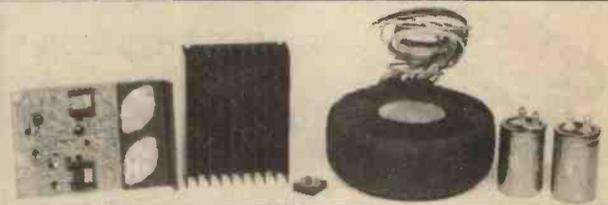
## TWO NEW SUPERMODULES: 170W INTO 4 OR 8 OHMS



By popular demand we have designed higher powered versions of our well known modules. The CE 1704 which gives 170W into 4 ohms and the CE 1708 which gives 170W into 8 ohms are physically similar to the original types and have the same combination of compatible performance features which makes CRIMSON amplification audibly superior to the competition and the only choice if you have an ear for music. We have also produced suitable power supplies which again use our superb TOROIDAL TRANSFORMERS, only 50mm high, with a 120-240 primary and single bolt fixing. Write or phone for more information and biased opinions.

POWER AMPLIFIER MODULES	Home	Europe
CE 608 60W/8 ohms 35-0-35V	£16.30	£16.60
CE 1004 100W/4 ohms 35-0-35V	£19.22	£19.30
CE 1008 100W/8 ohms 45-0-45V	£23.22	£23.00
CE 1704 170W/4 ohms 45-0-45V	£29.12	£28.46
CE 1708 170W/8 ohms 60-0-60V	£31.50	£31.04

TOROIDAL POWER SUPPLIES	Home	Europe
CPS 1 for 2 x CE 608 or 1 x CE 1004	£14.47	£18.40
CPS 2 for 2 x CE 1004 or 2/4 x CE 608	£16.62	£20.57
CPS 3 for 2 x CE 1008 or 1 x CE 1704	£17.66	£21.35
CPS 5 for 1 x CE 1008	£15.31	£19.18
CPS 5 for 1 x CE 1708	£22.68	£26.50
CPS 6 for 2 x CE 1704 or 2 x CE 1708	£23.98	£27.70

HEATSINKS	50mm 2°C/W	Home	Europe
LIGHT DUTY	50mm 2°C/W	£0.90	£1.30
MEDIUM POWER	100mm 1.4°C/W	£1.60	£2.40
DISCO/GROUP	150mm 1.1°C/W	£2.30	£3.65

THERMAL CUT-OUTS	Home	Europe
Recommended for improved reliability	£1.60	£1.90
70°C for use with Free Air Heatsink	£1.60	£1.90
40°C for use with Fan Cooled Heatsink	£1.60	£1.90

T.H.D. : TYPICALLY <0.2% ANY POWER, 1kHz, 8 OHMS

T.I.D. : INSIGNIFICANT

SLEW RATE LIMIT: 20V/μS

S/N RATIO : 110dB

FREQ. RESPONSE: 10Hz - 35kHz, -3dB

STABILITY : UNCONDITIONAL

PROTECTION : DRIVES ANY LOAD SAFELY

SENSITIVITY : 775mV (250mV or 100mV ON REQUEST)

SIZE : 120 x 80 x 25mm

## CRIMSON ELEKTRIK

Please note our new address and telephone number:

1A STAMFORD STREET, LEICESTER LE1 6NL Telephone: (0533) 537722

Home prices include V.A.T. and postage. C.O.D. 90p extra, £100 limit. Export no problem. European prices include carriage, insurance and handling, payment in Sterling by bank draft, P.O., International Giro or Money Order. Outside Europe, please write for specific quote by return. Send SAE or two International Reply Coupons for full literature. Favourable trade quantity price list on request. High quality pre-amp circuit 20p.





# HOME MICROCOMPUTER

Z80  
Monitor Program  
2K R.A.M.  
P.C.B.

Querty Keyboard  
VDU Interface (TV)  
Cassette Interface  
Teletype Interface

Expandable System

**NASCOM I £197.50 + VAT**


**LYNX ELECTRONICS (LONDON) LTD, 92 BROAD STREET, CHESHAM, BUCKS. 02405 75151**

## CRESCENT RADIO LTD.

MAIL ORDER DEPT.  
1 ST. MICHAELS TERRACE, WOOD GREEN,  
LONDON N22 4SJ  
PHONE: 888-4474
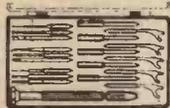
### MINIATURE TOOL SET

A 20 pc. Tool Set, precision made from quality industrial forged steel. Contents: 1 swivel handle, 3 screwdrivers 1.5 to 3.5 mm., 2 Philips type screwdrivers, 1 awl, 3 Allen keys 1.5 to 2.5 mm., 5 sockets 3 to 5 mm., 5 hex. keys 4 to 6 mm. Supplied in plastic case. Our price: only £3.25 + 8% VAT.



### STEREO JUNCTION BOX

This popular stereo junction box has the facility for two pairs of headphones and two L-speakers. A 3 position switch enables you to select headphones, loudspeakers or both. All speaker terminations are 2 pin din type. OUR PRICE: £3.20 + 12% VAT.



### ITI 1 SIGNAL INJECTOR

AF/RF signal for quick fault-finding on audio and allied equipment. Detachable probe; indicator light. Complete with battery and instructions. PRICE: £4.95 + 8% VAT.

### TI 206 2-STATION INTERCOM

Ideal for home, office or shop. Resilient high-quality plastic housing with concealed speaker. Master station has call/talk button and on/off/volume control. 4 transistor circuit gives clear speech. Supplied ready for table-top or wall mounting with approx. 12 metres of connecting lead, staples and battery. Dimensions: 115 x 78 x 38 mm. OUR PRICE: £6.75 + 12% VAT.

ACCESS AND BARCLAYCARD ACCEPTED—PHONE ORDERS WELCOMED  
ALL PRICES INCLUDE POSTAGE—PLEASE ADD V.A.T. AS SHOWN—S.A.E.  
WITH ALL ENQUIRIES PLEASE

Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N13. Phone: 888 3206  
and 13 SOUTH MALL, EOMONTON NS. Phone: 803 1685

### EFFECTS PROJECTOR "150"

(150 watt)  
Ideal for disco work, this versatile machine takes a range of accessories and is of a sturdy metal construction. Comes complete with bulb and 6in. Liquid Wheel. Ready to use. A bargain at £34 + 8% V.A.T.



### 3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT (1000 watt per channel)

Three channel: Bass, Middle, Treble. The input of this unit is connected to the loudspeaker terminals of an amplifier and the required lighting is connected to the output terminals of the unit thus enabling you to produce a fascinating sound to light display. Full instructions supplied or S.A.E. for details.  
Fantastic Value at £20.00 + 8% V.A.T.

### LOUDSPEAKERS + 12 1/2% V.A.T.

2 1/2in. 8 and 75 ohm at £1.10 (please state impedance req'd.)  
5in. 8 ohm Ceramic at £1.70  
8in. Goodmans "Audiom 8PA" 8 ohm 15W £5.26.

### PIEZO ELECTRIC HORN UNITS

High Quality, High Power Tweeter. No Xover req'd. Freq. Response: 3.8KHz-28KHz. S.A.E. for spec. sheet.  
PRICE: £6.50 + 8% V.A.T.

### SINCLAIR PRODUCTS\*

PDM35 digital multimeter £25-95. Mains adaptor £3-24. Deluxe padded carry case £3-25. 30kV probe £18-36. New DM235 digital motor P.O.A. cambridge scientific programmable calculator £13-15. Prog. library £4-65. Microvision TV £200.

### CUT PRICE TELETEXT

Texas Instruments XM11 tifax module £120. Labgear 7026 ready to use, attractively cased, complete unit. Plugs into TV aerial socket. Full colour. Remote control page select £355-00.

### TV GAMES KITS

Send see for free data. Tank battle chip AY-3-8710 plus economy kit £17-95. Stunt motor cycle chip AY-3-8760-1 plus economy kit £17-95. 10 game paddle 2 chip AY-3-8600 plus economy kit £14-70. AY-3-8500 chip plus economy kit £8-95. Modified shoot kit £4-95. Rifle kit £4-95. Colour generator kit £7-50. Joystick controls £1-90. 4.43MHz pal crystals 90p.

### ASSEMBLED TV GAMES

All attractively cased: 4 game black and white model (tennis, football, squash and polo) £11-95. 6 game colour model with pistol attachment £21-95. Tank battle game £39-95. Stunt motor cycle game £39-95. Stabilized mains adaptor for all games £3-10.

### MAINS TRANSFORMERS

6-0-6V 100ma 79p. 1 1/2A £2-35. 6.3V 1 1/2A £1-89. 9-0-9V 75ma 79p. 1A £1-99. 2A £2-60. 12-0-12V 50ma 79p. 100ma 90p. 1A £2-49. 13V 1A 95p. 15-0-15V 1A £2-79. 30-0-30V 1A £3-69.

### JC12, JC20 AND JC40 AMPLIFIERS

A range of integrated circuit audio amplifiers supplied with free data and printed circuits. JC12 6 watts £1-60. JC20 10 watts £2-95. JC40 20 watts £4-20. Send see for free data on our range of matching power and preamp kits.

### BATTERY ELIMINATOR BARGAINS

TV Game power unit stabilized 7.7V 100ma £3-10. 3-way models with switched output and 4-way multi-jack—3 1/4/6V 100ma £2-92. 6 7/8/9V 300ma £3-30. 100ma radio models same size as a PP9 battery. With press stud connectors. 9V £2-85. 6V £2-80. 4 1/2V £2-85. 9V + 9V £4-50. 6V + 6V £4-50. 4 1/2V + 4 1/2V £4-50. Cassette recorder mains unit 7 1/2V 100ma with 5 pin din plug £2-85. Car converters 12V dc input. Output 9V 300ma £1-50. Output 7 1/2V 300ma £1-50.

### FERRANTI ZN414

IC radio chip £1-05. Extra parts and pcb for radio £3-85. Case £1. Send see for free data.

### PRINTED CIRCUIT MATERIALS

PC etching kits—economy £11-70, standard £3-82. 50 sq ins pcb 40p. 1 lb FeCl £11-05. Etch resist pens—economy 45p. dialo 73p. Small drill bit 20p. Etching dish 68p. Laminate cutter 75p.

### BATTERY ELIMINATOR KITS

Send see for free leaflet on range. 100ma radio types with press stud connectors. 4 1/2V £1-80. 6V £1-80. 9V £1-80. 4 1/2 + 4 1/2V £2-50. 6 + 6V £2-50. 9 + 9V £2-50. Cassette type 7 1/2V 100ma with din plug £1-80. Transistor stabilized 8-way types for low hum 3 1/4/6 7 1/2/9/12/15/18V. 100ma £3-20. 1Amp £6-40. Heavy-duty 13 way types 4 1/2/6/7/8 1/2/11/13/14/17/21/25/28/34/42V. 1Amp £4-65. 2Amp £7-25. Car converter kit input 12V dc. Output 6 7/8/9V 1A stabilized. Stabilized power kits 3-18V 100ma £3-60. 3-30V 1A £9-95. 3-30V 2A £14-95.

### S-DECS AND DECS\*

S-DeC £3-39. T-DeC £4-44. u-DeCa £4-52. u-DeCb £6-73. 16 diil or 10T05 adaptors—with socket £2-14. New S-de-kit £4-95.

### CONTINENTAL SPECIALITIES PRODUCTS\*

EXP300 £6-21. EXP350 £3-40. EXP600 £6-80. EXP650 £3-89. EXP4B £2-48. PB8 £9-94. PB100 £12-74. LMT £30-99. LP1 £33-48. LP2 £19-44.

### BI-PAK AUDIO MODULES

Send see for data. S450 tuner £23-51. AL60 £4-86. PA100 £16-71. SPM80 £4-47. BMT80 £5-95. MK60 £38-74. Stereo 30 £20-12.

### COMPONENTS

Resistors 5% carbon E12 10 to 10M. 1W 1p. 1W 2p. Polyester capacitors 250V E6 01 to .068mf 3 1/2p. 0.1mf 2p. 15mf 5p. 22mf 4p. 33. 47mf 6p. Polystyrene capacitors E12 63V 15pf to 6800pf 2 1/2p. Ceramic capacitors 50V E12 22pf to 1000pf 2 1/2p. E6 1500pf to 47000pf 2 1/2p. Mylar capacitors 100V 001. 002. 005mf 4p. 01. 02mf 4 1/2p. 04. 05mf 5 1/2p. Electrolytics 50V 47 1/2mf 5p. 25V 5mf 5p. 10mf 4p. 16V 22mf 5p. 33.47.100mf 6p. 220.330mf 9p. 470mf 11p. 1000mf 8 1/2p. Zeners 400mW E24 2V7 to 33V 7 1/2p. Preset pots sub-miniature 0.1W horiz or vert 100 to 4M/7 8 1/2p. Potentiometers 1/2W dc up to 2M2 log or lin. single 28p. dual 76p.

## SWANLEY ELECTRONICS

DEPT. PE, PO Box 68, 32 Goldsel Rd., Swanley, Kent BR8 8TQ.

Mail order only. Please add 30p to the total cost of order for postage. Prices include VAT. Overseas customers deduct 7% on items marked \* and 11% on others. Official credit orders welcome.

# THE MOST COMPREHENSIVE RANGE OF TUNER MODULES EVER DISPLAYED

## HF 7948 FRONT END



**£13.12**  
Inc. VAT P&P

### TECHNICAL CHARACTERISTICS:

Output terminal for digital frequency meter; Antenna impedance - 75 to 300 Ohms; Frequency ranges 87.5 to 104 MHz or to 108 MHz; Sensitivity - 0.9 uV 26dB signal to noise ratio + 75 kHz deviation; Inter-modulation 80dB Image rejection - 60dB; Tuning voltage - 1V to 11V; Total gain - 33dB; Intermediate frequency - 10.7 MHz; Power supply voltage + 15V; Power consumption 15mA; Dimensions 104 x 50 mm.

### TECHNOLOGY:

Double sided epoxy printed circuit board with plated through holes. Dual gate effect transistors; Silvered coils.

## FI 2846 IF AMP AND DECODER



**£9.86**  
Inc. VAT P&P


### TECHNICAL CHARACTERISTICS:

Intermediate frequency - 10.7MHz. IF Bandwidth - 280kHz; Signal to noise ratio - 70dB with 1mV input; Distortion - mono 0.1%, stereo 0.3%; Sensitivity - 30uV up to the 3dB limit; Channel separation - 40dB at 1kHz; Pass band - 20 to 15,000Hz; Rejection at 38kHz greater than 55dB; Am rejection - 45dB; De-emphasis - 50 to 75µs; Pilot capture at 19kHz + 4%; Channel matching within less than 0.3dB; Output impedance - 100 Ohms; Output voltage - 500mV; Phase locked loop stereo decoder; Output for LED VU-meter; Null indicator; Outputs for AGC AFC and inter-station muting; Consumption - 55mA LEDs extinguished; 100mA LEDs illuminated; Power supply - 15V; Dimensions 195 x 76mm.

### CIRCUIT TECHNOLOGY

Epoxy printed circuit board; Monolithic integrated circuits; ceramic filter.

## ALS 1500 STABILISED POWER SUPPLY

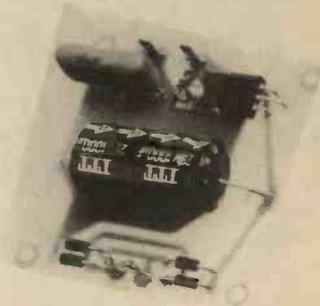

**£2.53**  
Inc. VAT P&P

### TECHNICAL CHARACTERISTICS:


Output voltage - 15V; Max. output current - 500mA; Thermal coefficient less than 1mV/C; 15V power supply for modules HF 7948 and FI 2846; Supply protected against short circuit (power and current protection); Dimensions - 65 x 55mm.

### TECHNOLOGY:


Double sided epoxy circuit board; Monolithic integrated circuit.

# OPTOELECTRONIC OPTIONS


**£8.06**  
Inc. VAT P&P

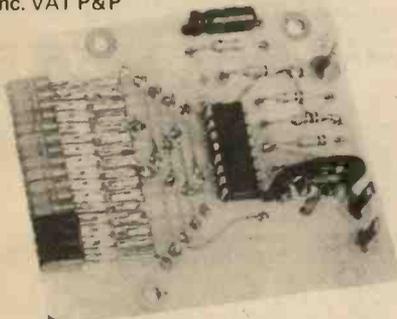

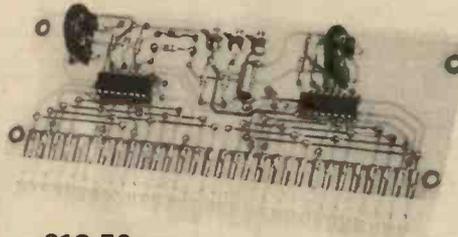
**LED VU-METER**  
Station strength indicator



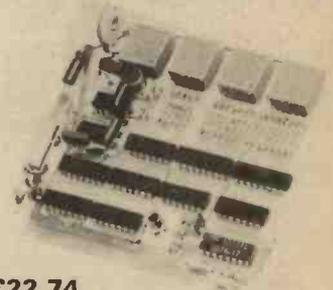**£13.50**  
Inc. VAT P&P  
**ILLUMINATED POINTER**  
Station finder



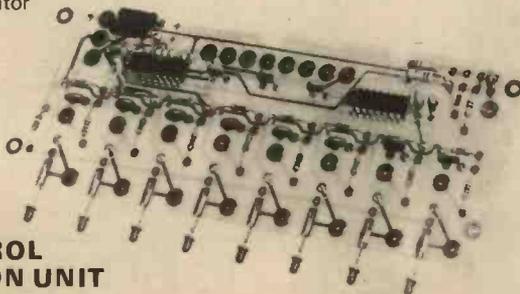**£22.74**  
Inc. VAT P&P  
**FREQUENCY METER**  
Digital display of received station frequency.



**£8.77**  
Inc. VAT P&P  
**TOUCH CONTROL  
PRE-SELECTION UNIT**  
LED channel indication



**£4.35**  
Inc. VAT P&P  
**NUMERICAL DISPLAY**  
Pre-selected channel number

**CROSSLAND HOUSE**  
Telephone (0227) 63218

**NACKINGTON**


**CANTERBURY · KENT**  
Telex 965780

# The latest kit innovation!
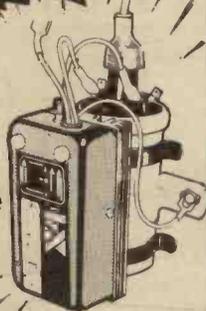
## from Sparkrite

*Sparkrite is featured by Shaw Taylor in "DRIVE IN"*

the quickest fitting  
**CLIP ON**  
capacitive discharge  
electronic ignition  
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

**THE KIT COMPRISES EVERYTHING NEEDED**  
Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT, post & packing.  
Electronics Design Associates, Dept. PE7, 82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Electronics Design Associates, Dept. PE7  
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name   
Address

Phone your order with Access or Barclaycard  
Inc. V.A.T. and P.P. QUANTITY REQ'D. Send SAE if brochure only required.

X4 KIT	£14.95
TACHS PULSE SLAVE UNIT	£3.35

Please state polarity pos or neg earth.  
Access or Barclaycard No.

I enclose cheque/PO's for  
£   
Cheque No.

**SPORTS**

## NEW WATCHES FROM CASIO

**ALARM**

### SPORTS WATCHES.

Chronograph with up to 25 functions. 6 digit display of hours, minutes, seconds (am/pm) and day, date and month. Measures net times, lap times and 1st & 2nd place times to 1/10 second. Water resistant (100 ft.) F-100. Plastic case (£24.95) £19.95. 52QS-14B. Metal encased version of F-100. S/S bracelet (£44.95) £34.95

### ALARM WATCHES

Six digit display of hours, minutes and seconds or hours, minutes and date, day of week and am/pm indication. Day, date, month and year. Perpetual calendar. 24 hour alarm with on/off indicator. 15 months battery life. S/S case water resistant to 100 ft. 25CR-16B. Round face (£64.95) £49.95. 26CS-16B. Square (£74.95) £59.95

### NEW AQ-1000 CALCULATING ALARM CLOCK PLUS 3-WAY STOPWATCH

Hours, minutes, seconds, am/pm. 24 hour Alarm with sign. Stopwatch: Net times, lap times. 1st & 2nd place times from 1/10 sec. to 10 hrs. with ST & LAP signs. Calculator: 4 key memory, %, √, 1 year batteries. ± 20 secs/month. 1/2" x 2 1/4" x 4 1/4". (£24.95) £19.95

SEIKO Calculator watch (£165) £135. CITIZEN Multi-Alarm (£135) £108

Send 25p for our illustrated catalogue. Accurist, Casio, Citizen etc. Prices include VAT P.&P. Send cheque, P.O. or phone your credit card No. to:

## TEMPUS

Dept. P.E.  
19/21 Fitzroy Street  
Cambridge CB1 1EH  
Tel. 0223 312866

### T.T.L. 74 I.C.'s By TEXAS, NATIONAL, I.T.T., FAIRCHILD etc

7400 14p	7426 25p	74121 30p	74151 65p	74179 140p
7401 14p	7427 25p	74122 40p	74153 65p	74180 100p
7402 14p	7428 40p	74123 60p	74154 120p	74181 200p
7403 14p	7430 15p	74125 50p	74155 70p	74182 75p
7404 14p	7432 25p	7483 85p	74156 70p	74184 150p
7405 14p	7437 25p	7485 100p	74157 70p	74185 150p
7406 40p	7438 25p	7486 30p	74131 100p	74186 350p
7407 40p	7440 15p	7489 250p	74132 65p	74189 350p
7408 20p	7441 65p	7490 35p	74135 100p	74192 90p
7409 20p	7442 65p	7491 75p	74136 80p	74193 140p
7410 15p	7445 80p	7492 45p	74137 100p	74194 120p
7411 20p	7446 85p	7493 40p	74138 125p	74193 120p
7412 20p	7447 75p	7495 60p	74139 100p	74194 100p
7413 30p	7448 70p	7496 70p	74141 65p	74195 100p
7414 60p	7450 15p	74100 95p	74142 270p	74196 100p
7416 30p	7451 15p	74104 40p	74143 270p	74197 100p
7417 30p	7453 15p	74105 40p	74144 270p	74198 185p
7420 15p	7454 15p	74107 30p	74145 75p	74199 185p
7422 20p	7460 15p	74109 50p	74147 230p	
7423 25p	7470 30p	74116 30p	74148 165p	
7425 25p	7472 25p	74120 90p	74150 120p	

<b>C. MOS.</b>	4030 55p	IN4148 by ITT/TEXAS 100 for £1.50.	2112-4 256 x 4 BIT 450 NANO SEC. STATIC RAM. £2.95 each. 4/£11.60. 8/£22.80.
4000 14p	4032 95p	UNCODED	2513 CHARACTER GENERATOR. UPPER CASE £7.00.
4001 14p	4033 120p	HEXADECIMAL 19 KEYBOARD. 1-10 A.B.C.D.E.F. 2 OPTIONAL KEYS. SHIFT KEY £12.50.	2513 CHARACTER GENERATOR. LOWER CASE £7.00.
4002 14p	4047 100p	555 Timer. 10 for £2.50.	MM5204AQ PROM 4096 BIT READ ONLY MEMORY £8.00.
4006 90p	4048 55p	741 Op. amp. 10 for £2.00.	8212 8 BIT IN/OUT PORT £3.00.
4007 16p	4049 40p	RCA SCR TO3 case 100V 12.5A £2.50.	8831 TRI-STATE QUAD LINE DRIVER £2.00.
4011 14p	4050 40p	MURATA ULTRASONIC TRANSDUCERS MA40LIR £2.50 each. £4.00 pair.	8833 TRI-STATE TRANSCEIVER (TRUE) £2.00.
4012 14p	4054 120p	2102AN-2L 1024 x 1 BIT 250 NANO SEC. STATIC RAM. £2.20 each. 4/£8.40. 8/£16.00.	8835 TRI-STATE TRANSCEIVER (INVERTING) £2.00.
4013 50p	4055 140p	2102AN-4L 1024 x 1 BIT 450 NANO SEC. STATIC RAM. £1.60. 4/£6.00. 8/£11.60.	AYS-1013 UAR/T £6.00. LM309K/LM340K VOLTAGE REGULATOR £1.00 each.
4015 90p	4058 135p		
4016 40p	4060 120p		
4017 90p	4066 55p		
4018 90p	4069 20p		
4020 100p	4071 16p		
4022 90p	4072 16p		
4023 16p	4081 16p		
4024 65p	4082 16p		
4025 16p	4510 120p		
4026 160p	4511 150p		
4027 50p	4516 110p		
4028 90p	4518 130p		
4029 110p	4528 100p		



## T. POWELL

306 ST. PAUL'S ROAD, HIGHBURY CORNER, LONDON N.1

Telephone: 01-226 1489

ALL PRICES INCLUDE POST AND V.A.T.



# TUNE IN TO THE WORLD OF MICROPROCESSORS

Greensleeves • God Save the Queen • Rule Britannia  
 Land of Hope and Glory • O Come All Ye Faithful  
 Oranges and Lemons • Westminster Chimes • Sailor's Hornpipe  
 Beethoven's "Fate Knocking" • The Marseillaise • Mozart  
 Wedding March • Cook House Door • Star Spangled Banner  
 Beethoven's Ode to Joy • William Tell Overture  
 Soldier's Chorus • Twinkle, Twinkle Little Star  
 Great Gate of Kiev • Maryland • Deutschland über Alles  
 Bach • Colonel Bogie • The Loralie



Build this  
**24 Tune Electronic  
 Door Chime for  
 only £18\***

**DUE TO THE  
 FANTASTIC SUCCESS  
 OF CHROMA-CHIME\*  
 NOW ONLY £16-50  
 PRICE INCLUDES P.P.VAT**

- Handsome purpose built ABS cabinet
- Easy to build and install
- Uses Texas Instruments TMS1000 microcomputer
- Absolutely all parts supplied including I.C. socket
- Ready drilled and legended PCB included
- Comprehensive kit manual with full circuit details
- No previous microcomputer experience necessary
- All programming permanently retained is on chip ROM
- Can be built in about 3 hours!
- Runs off 2 PP3 type batteries.
- Fully Guaranteed

Here's the Chroma-Chime—a perfect example of British scientific achievement brought right to your own front door. Now—you can be among the first enthusiasts in the world to build your own electronic musical door chime—a door chime with no moving parts. There are 24 of the world's favourite and best known tunes pre-programmed onto the microcomputer chip so that all you have to do is to set the Chroma-Chime's built-in selector switches to a code to index the "tune of the day" from the repertoire.

Since everything is done by precise mathematics, it cannot play the notes out of tune.

The unit has comprehensive built-in controls so that you can not only select the "tune of the day" but the volume, tempo and envelope decay rate to change the sound according to taste.

Not only visitors to the front door will be amazed, if you like you can connect an additional push button for a back door which plays a different tune!

This kit has been carefully prepared so that practically anyone capable of neat soldering will have complete success in building it. The kit manual contains step-by-step constructional details together with a fault finding guide, circuit description, installation details and operational instructions all well illustrated with numerous figures and diagrams.

The CHROMA-CHIME is exclusively designed by

## CHROMATRONICS

River Way, Harlow, Essex.

To CHROMATRONICS, River Way, Harlow, Essex, U.K.

Please send  Chroma-Chime Kits at ~~£18-50~~ **£16-50** each including VAT and post and packing

PLEASE USE BLOCK CAPITALS

Name \_\_\_\_\_

Address \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

I enclose cheque/PO value £ \_\_\_\_\_  
 or debit my ACCESS/BARCLAYCARD account No.

--	--	--	--	--	--	--	--	--	--

Signature \_\_\_\_\_

N.B. The CHROMA-CHIME is also available, fully assembled, price £ 19-95 inc VAT and post and packing.

PE 7/78.

# SMALL ADS

The prepaid rate for classified advertisements is 18 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

## NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

## RECEIVERS AND COMPONENTS

ASSORTED SMALL JAPANESE IF. Transformers 20 for £1.25, Assorted Nuts, Bolts, Washers, Eyelets Self Tapping, Self cutting screws a real bargain 1 lb weight £1.75, Assorted Ceramic Capacitors 100 for £1.00, Assorted Polystyrene Capacitors 100 for £1.50, Assorted Polyester Capacitors 100 for £2.00, Assorted Carbon and Carbon Film Resistors 100 for £1.00, Assorted Wire-Wound Resistors 100 for £2.00, Assorted Transistors/Zeners Diodes all marked 100 for £2.00, Mullard Modules CP 1152 £1.00; LP 1153 £4.00; LP 1165 £4.00; LP 1166 £4.00; LP 1169 £4.00; LP 1173 £4.00; LP 1181 £4.00. All above prices include VAT & Postage. T. Powell, 306 St. Paul's Road, London N.1. Telephone 01-226 1489.

COMPONENTS FOR P.E. PROJECTS. Components lists with prices available for P.E. Projects from November 1977 onwards. Send SAE stating project and month of publication (Maximum four projects per SAE). Lists sent by return together with ACE order form/catalogue. ACE MAILTRONIX, Tontal Street, Wakefield, W. Yorks. WF15JR.

## BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V, 0.47, 1.0, 2.2, 4.7 & 10 mfd. —5p.  
22, 47—5p. (50V—6p), 100—7p. (50V—8p), 220—9p. (50V—10p), 470—11p. (50V—16p), 1000/15p.—15p. 1000/25V—18p. 1000/50V—22p.

Subminiature bead tantalum electrolytics. 0.1, 0.22, 0.47, 1.0 @ 35V, 4.7 @ 63V—8p. 2.2/35V & 4.7/25V—9p. 10/25V, 15/16V—12p. 22/16V, 33/10V, 47/6V, 68 & 100 @ 3V—14p.  
Mullard Miniature Ceramic E12 Series 63V 2%. 10 pf to 47 pf.—3p. 56 pf. to 330 pf.—4p. Vertical Counting Ceramic Plate Caps. 50V. E12 22 pf.—1000 pf. E6 1500 pf.—47000 pf.—2p.

Polystyrene E12 Series 63V, Hor. Mounting. 10 pf. to 1000 pf.—3p. 1200 pf. to 10000 pf.—4p.  
Mullard Polyester 250V Vert. Mtg. E6 Series. .01 to 1—4p., .15, .22—5p., .33, .47—8p., .68—11p. 1.0—14p., 1.5—20p., 2.2—24p.

Mylar (Polyester) Film .100V. Vertical Mtg. .001, .002, .005—3p., .01, .02—4p., .04, .05—5p.

Miniature Film Resistors Highstab. E12 5%. 0.125 watt 10Q to 2MΩ ..... 1p.  
0.250 watt 1Q to 10MΩ (10% over 1M)..... 1p.  
0.500 watt 10Q to 2MΩ ..... 1p.  
1.000 watt 10Q to 10MΩ ..... 2p.

1N4148—3p. 1N4002—5p. 1N4006—7p. 1N4007—8p. BC107/8/9. BC147/8/9. BC157/8/9. BF194 & 7—9p. 20mm. fuses .15, .25, .5, 1.0, 2.0, 3.0 & 5A—3p. Printed Circuit Holders for 20mm. fuses—5p. Post 10p (Free over £4). Prices VAT inclusive.

THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN

PCBs Rexolin 9 1/2" x 8" 55p. 12" x 9" 70p. 17 1/2" x 9" £1.15. Fibre Glass Double Sided 13" x 6" £1.30, 12" x 10 1/2" £2.10. Unit with 8 Silicon Diodes 600V 20 amp. 8 SCRs 400V 16 amp. 6 Vinkors w.w. resistors etc. £8.75. 300 Small Components Trans. Diodes £1.30. 7lbs. Assorted Components £2.95. List 15p Refundable. Post 20p under £1. Insurance add 15p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL

## CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

- Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
- The publishers reserve the right to refuse or withdraw any advertisement.
- Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

VALVES. Radio - T.V. - Industrial - Transmitting and Projector Lamps. We dispatch Valves to all parts of the world by return of post, Air or Sea mail, 4000 Types in stock. 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors. COX RADIO (SUSSEX) LTD., Dept. P.W. The Parade, East Wittering, Sussex, PO20 8BN, West Wittering 2023 (STD Code) 024366.

## ELECTROLYTICS (MULLARD/ITT)

R=RADIAL LEADS A=AXIAL (double ended)

10µF/25V R 0.15. 10µF/250V R 0.20. 47µF/25V R 0.15. 500µF/35V R 0.20. 400µF/10V A 0.12. 680µF/10V A 0.12. 680µF/63V R 0.40. 1000µF/6V A 0.12. 1000µF/10V R 0.15. 1000µF/16V A 0.20. 1000µF/25V R 0.25. 2200µF/63V R 0.20.

Above capacitors less 10% for 10 mix - full list send SAE please.

RCA 2N3055H (extra rugged) with mounting kit 0.70. RCA TRIACS 400V/8A 0.85. TIP 31C/32C 0.55 each. PRICES INCLUDE VAT, POST ADD 0.20. GOODIES LIST SEND SAE

CLACTON ELECTRONICS (0255) 27505

10 Douglas Road, Clacton-on-Sea, Essex

Transistors	BFY51	23p	BY238	20p	741	45p	7420	18p		
	ACV21	54p	BSX20	24p	IN914	4p	TTL	7430	18p	
	ACV22	64p	OC35	150p	IN4001	5p	7400	15p	7432	37p
	AF12	260p	TIS43	43p	IN4002	5p	7402	16p	7437	37p
	AS151	120p	ZKX30	14p	IN4003	6p	7403	16p	7442	75p
	BC107	9p	ZTX450	15p	IN4004	6p	7404	25p	7446	108p
	BC108	10p	ZTX500	17p	IN4006	7p	7407	41p	7474	37p
	BC109C11p		2N3053	24p	IN4148	3p	7408	23p	7475	43p
	BC154	10p	2N3055	65p	IC		7410	19p	7476	37p
	BC214	17p	Diodes	NE555	28p	7411	26p	7490	39p	
	BC413	16p	AA215	15p	709	55p	7413	41p	7493	39p

ELECTROLYTIC CAPACITORS (M/F) 6.3V/470 5p; 1000 13p; 2200 14p; 3300 15p; 4700 20p; 10W/10, 47, 220 5p; 470 9p; 2200 15p; 3300 16p; 16V/100, 220 8p; 330, 470 16p; 1000 15p; 25V/22, 33 8p; 100, 220 8p; 330, 470 12p; 1000 18p; 33V/47, 100, 7p; 220, 330 15p; 50V/1, 22, 33 7p; 47, 100 8p; 330, 470 16p; 1000 23p.

RESISTORS CARBON FILM

0.25W 2.2Ω—4.7 MΩ E24 1p

0.5W 2.2Ω—4.7 MΩ E12 1.5p

METAL FILM CAPACITORS µF/80V

.0055, .0068, .0082 3p; .01, .012, .015, .022, .033,

.037, .047, .056 4p; .068, .082, .1, .12, .15, .18,


2.2 5p; .33, .47 6p; .56, .88 7p; .82, 1.5 10p.

Mail Order only P&P 25p. Prices include VAT, CWO.

STE LTD. System Techniques (Electronics) Limited, PEZ.

Defield, Stace Hill, Ectonbridge, Kent, TN8 5NL

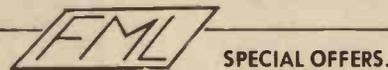LED'S. Mixed bags of 4 different sizes and 4 different colours. 50 @ £5.25, 100 @ £9.25 including VAT and post and packing. CWO. Michael Williams Electronics, 47 Vicarage Avenue, Cheshire Hulme, Cheshire. SK8 7JP.



Buy NOW while stocks last. PRICES INCLUDE V.A.T.

2N3055 33p each  
TIP31 or TIP32 39p each  
TIP41 or TIP42 39p each

0.022µF Polyester 3p each  
0.033µF Polyester 6p each

22µF 450V Electrolytic 19p each  
47µF 25V Electrolytic 5p each  
150µF 16V Electrolytic 5p each  
680µF 16V Electrolytic 12p each

Red LED'S (5mm) 10 for £1.00

ALL COMPONENTS ARE BRAND NEW AND GUARANTEED ONLY AVAILABLE AT THESE PRICES WHILE STOCKS LAST

Please add 15p for Postage. Send 2 stamps for Catalogue.

BARCLAYCARD phone service available.

Tel. 0473 50975.

FRASER-MANNING LTD.,

26 HERVEY STREET, IPSWICH, IP4 2ES.

SEMI-CONDUCTORS	BY 127	10p	CAPACITORS		
BC 107	TIP 29	35p	0.1/800V	5p	
BC 132	1N 645	11p	25/25V	5p	
BC 147	1S 940	4p	W/W RESISTORS		
BC 2048	INTEGRATED		2.5W Axial	12p	
BC 351	CIRCUITS		5W Radial	6p	
8D 131	LM 741 BP DIL	13p	10W Axial	9p	
8D 138	M252 B1 AA	£7.00	15W Radial	11p	
8T 106	(Rhythm Gen.)				
8U 205	£1.10	BRIDGE	S.A.E. FOR LISTS		
8U 208	£1.80	RECTIFIER	Min Order £2. P&P 25p.		
BU 208	£1.90	1S 805 (1A/50V) 16p	Prices Include VAT.		
		Export and Wholesale enquiries welcome			
		K & A DISTRIBUTORS, 52 BARKBY ROAD, SYSTEM, LEICESTER.			
		TEL: 0533 609381.			

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

## DIGITAL BONANZA Full Spec. Devices

PACK P1 1 x MM5330 digital voltmeter I.C. With full instructions on how to build a digital multimeter or panel meter. £3.95  
PACK G1 1 x 2 1/2" solar cell. Gives 0.5V at 0.5 amps. in good sunlight. £3.95  
PACK T3 1 x MM5316 digital alarm clock I.C. 12 or 24 hour. Will drive LED, LCD or fluorescent displays. With full instructions. £2.75  
PACK T4 1 x 0.8" giant red LED clock display. 3 1/2 digit with am/pm indicator. A good display for clocks, test equipment etc. £5.50  
PACK M1 2 calculator keyboards £1.00  
PACK M2 1 x 2102L-1, 1024 bit static RAM. Low current version of the famous 2102. With full data. £1.25  
PACK M3 1 x MM5725 4 function calculator chip (not designed for use with Pack M1). With data book. £1.00  
PACK E2 1 x 8 digit 0.33" high 7 segment liquid crystal calculator style display. With data. £2.95  
PACK E3 1 x 8 digit 0.5" high 7 segment liquid crystal calculator style display. With data. £4.25  
PACK DM1 5 x 14 pin dual in line chips each containing 23 matrix signal diodes. With data. 50p

## Untested Packs

PACK E1 (80% Guaranteed Good) 3 x MAN3 7 segment 0.127" LED displays. Excellent value. £1.00  
PACK DLT (Untested - so no guarantees) Fantastic value for money. A jumbo pack of 30 mixed I.C.'s. There could be anything in this pack, linear, digital - who knows? Guaranteed a sellout at only £1.00  
PACK MU1 (Untested - so no guarantees) Another bargain. 2 x Upper half of a calculator case with built in keyboard. A snip at only 60p the pair.

Satisfaction Guaranteed or return complete Pack for replacement or refund.

MAIL ORDER ONLY - NO CALLERS PLEASE

Postage and Packing please add 25p

## CODESPEED

P.O. Box 23, 34 Seafield Road Copnor, Portsmouth, Hants., PO3 5BJ

## ELECTRICAL

STYL - Illustrated equivalents (List 28) also cartridges, leads, etc. Superb quality and service at lowest prices: Fully guaranteed, free for SAE from FELSTEAD ELECTRONICS (PE), Longley Lane, Gatley, Cheshire, Cheshire SK8 4EE.

## BOOKS AND PUBLICATIONS

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £4.50, request free circuit diagram. Stamp rings details unique. TV Publications. (AUSEPE) 76 Church Street, Larkhall, Lanarkshire.

## LADDERS

LADDERS. Varnished 25ft. Extd. £35.70. Carr. £2.40. Leaflet. Callers welcome. Open Sat. Ladder Centre, (PEE4) Halesfield (1) Telford, Salop, Tel: 586644.

## TAPE EXCHANGES

RECORDER OWNERS (cassette/reel) can now speak to the world! All ages ... every interest. Send stamp: WORLD-WIDE TAPETALK, 35 The Gardens, Harrow.

## SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc. 75p plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 57885.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc. With free Fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

# Radio Technicians

Government Communications Headquarters has vacancies for Radio Technicians. Applicants should be 19 or over

**STANDARDS** required call for a sound knowledge of the principles of electricity and radio, together with appropriate experience of using and maintaining radio and electronic test gear.

**DUTIES** cover highly skilled telecommunications/electronic work, including the construction, installation, maintenance and testing of radio and radar telecommunications equipment and advanced computer and analytic machinery.

**QUALIFICATIONS:** Candidates must hold either the City and Guilds Telecommunications Part 1 (Intermediate) Certificate or equivalent HM Forces qualification.

**SALARY** (inc. supps.) from £2,673 at 19 to £3,379 at 25 (highest pay on entry) rising to £3,883 with opportunity for advancement to higher grades up to £4,297 with a few posts carrying still higher salaries.

Opportunities for service overseas.

Further particulars and application forms available from:

## GCHQ

Recruitment Officer. (Ref PE/7)  
GCHQ, Oakley,  
Priors Road, Cheltenham, GL52 5AJ.  
Cheltenham (0242) 21491 Ext 2270

**NEW BACK ISSUES** of "PRACTICAL ELECTRONICS" available 65p each Post Free. Open P.O./Cheque returned if not in stock - Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

**LOGIC PROBE SUITABLE.** TTL/CMOS 5-15V indicates Logic states and Trigger Pulses £12 inc. C. Marshall, 22 Oakfield Road, Croydon, Surrey. CRO 2UA.

**P. E. ORGAN** combined with Joanna, Synthesiser, Rhythm generator, Reverberation etc. Parts cost over £300. Beautiful laminate case. £220. Telephone Cleethorpes 68799.

**INTROKIT, KEYBOARD KIT.** assembled, functioning, full documentation, software, additional literature £120. Johnson, Stonesfield 318.

**HEATHKIT DUAL-TRACE OSCILLOSCOPE.** Model 10-4510. Partly assembled, with some circuit boards required to complete. Offers over £300. Norfolk. Box No. 73.

**FORMANT SYNTHESIZER.** V.C.O., Keyboard, interface + receiver, reverb. Amp. + Springline. All working. 36 Albert Street, Chilton, Co. Durham.

**SEEN MY CAT7 5000** Odds and ends. Mechanical Electrical. Cat free. Whiston, Dept. PRE. New Mills, Stockport.

**TEKTRONIX 545A** Oscilloscope with C A dual trace plug-in. £330 o.n.o. Phone Aughton Green (Lancs) 421755.

**SYNTHESIZER E.T.I. 4600.** Complete and working £550. Chelmsford 59249. (0245) after 6p.m.

**ELECTRONIC KITS SAE** for new catalogue, and clearance list of obsolete kits. AMTRON U.K. 7 Hughenden Road, Hastings, Sussex.

### MISCELLANEOUS

#### SPECIAL OFFER



Magnetic Contacts for Burglar Alarms, etc. 101 flush 4 wire 55p. 104 surface 5 terminal 69p. 105 flush 2 terminal 55p. Prices fully inclusive. Send crossed cheque, P.O. to: **CWAS ALARM**, 11 Denbrook Walk, Bradford BD4 0QS, W. Yorks. or S.A.E. for complete Price List of Professional Alarm Equipment.

### EDUCATIONAL

## TELEVISION TRAINING

**15 MONTHS** full-time course for beginners to include all the undermentioned subjects. Short courses, combining one or more subjects, for applicants with previous electronics knowledge.

**13 WEEKS** ELECTRONICS AND RADIO  
**13 WEEKS** MONOCHROME TELEVISION  
**13 WEEKS** COLOUR TELEVISION  
**13 WEEKS** CLOSED CIRCUIT TV AND VCR

The training incorporates a high percentage of practical work.

**NEXT SESSION** starts on September 11th

Prospectus from:  
**LONDON ELECTRONICS COLLEGE,**  
DEPT A7 20 Penywern Road,  
London SW5 9SU.  
Tel: 01-373 8721.

### WANTED

"RADIO AND TELEVISION Servicing". Books wanted from 1964-1965 edition up to date. £3.00 plus postage paid per copy by return of post. Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Telephone (0423) 55885.

#### CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. 273W Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

#### COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. 273W Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

#### TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. 273W Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

## THE FABULOUS D2 MICROPROCESSOR EVALUATION KIT FROM MOTOROLA.

Featuring \*24 key keyboard \*Seven segment display \*Cassette interface \*Erom & Ram Expandable \*Interface Capability \*Full Documentation \*5 Volt power supply Required \*One years FREE membership of The Amateur Computer Club with every purchase\*. £176 + £1.50 P & P + 8% VAT.

#### ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10-19	2.60	1.40	.66	.55
20-29	2.80	1.60	.85	.65
30-34	3.00	1.70	.95	.70
35-40	3.35	1.90	1.10	.79
40-43	4.50	2.50	1.90	1.25
44-46	5.00	3.00	2.10	1.65
47	8.00	5.00	3.00	1.76
48	15.00	9.00	6.00	3.30

Tinned Copper, Even Gauges 14-30 £3 per lb.  
Multicore 60/40 Solder 18SWG £3.24 per lb.  
Prices include P & P and VAT.  
SAE brings list of copper and resistance Wires.

## THE SCIENTIFIC WIRE COMPANY

PO Box 30 London E.4.  
Reg. Office, 22 Coningsby Gdns.

**NEW PREAMPS** 14-50p, 2 inputs bass + Treble, also 100 watts into 80MHS Amp Modules 17-50p. Mail Orders to Panther Audio, 2 Lower Addiscombe Road, Croydon. Barclay and Access taken. Tel: 680 1476.

**CLEARING LABORATORY.** Scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

### PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware. Printed circuit boards, top quality for individual designs. Prompt service. Send 25p for catalogue. From:

**RAMAR CONSTRUCTOR SERVICES,**  
Masons Road, Stratford upon Avon, Warwicks.  
Tel. 4879.

### CABINET FITTINGS

FOR  
Stage Loudspeakers and Amplifier Cabs  
Fretcloths, Coverings, Strap & Recept Handles, Feet, Castors, Jacks & Sockets, Cannons, Bulgun 8 ways, Reverb Trays, Locks & Hinges, Corners, Trim, Speaker Bolts etc.  
Send 2 x 9p Stamps for samples and illustrated catalogue.

**ADAM HALL (P.E. SUPPLIES)**  
Unit 3, Carlton Court, Grainger Road  
Southend-on-Sea, Essex.

## BUILD YOUR OWN TV CAMERA



ONLY KNOWN HIGH PERFORMANCE SOLID STATE CAMERA IN KIT FORM. Also available factory assembled. Ideal for experimenters, industry security, education etc. \*Will work with most other CCTV equipment. \*Fully guaranteed. \*Completely self-contained. With our modulator will connect to any domestic TV set. Model C1 complete with Vidicon £99. Less Vidicon £82.35. (Lens available as optional extra). SAE for info or phone your order through using your Barclay or Access Card.

### CROFTON ELECTRONICS LIMITED

35 Grosvenor Road, Twickenham, Middlesex. 01 - 891 1923



### RADIO CONTROL SPECIALISTS

Kits for multi channel systems. Special parts and accessories.

S.A.E. FOR LEAFLETS  
Tel: 0602 395418

**MICRON R/C, Hayworth Road,  
Sandiacre, Nottingham.**

### NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £9.75 plus 25p P. & P.

'Brain-Freeze' 'em with a MINI-STROBE Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4.30 plus 20p P. & P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5 each plus 20p P. & P.

LOTS MORE! Send 20p for lists. Prices include VAT. (Mail order U.K. only).

### BOFFIN PROJECTS

Cunliffe Road, Stoneleigh  
Ewell, Surrey (P.E.)

### TRANSFORMER PROBLEMS?

Send SAE with requirements for return of post quote.

**TRENT TRANSFORMERS LTD**  
Chapel Street,  
Long Eaton, Nottm. 06076 66716

### PROGRAM YOUR OWN

TUNES with this MUSICAL DOORBELL. Have a new JINGLE each DAY, with 119 tunes, just needs bell transformer and speaker, £19-50.

NEW! MSF Receiver gives digital SECONDS, MINUTES and output for MONTH, DATE and YEAR, internal ferrite rod, only £13-70.

NO LONG WAVE? 100-600 KHz Converter feeds your 4.1-4.6 MHz receiver, only £9-90.  
SIG. GEN. 10 Hz-200 KHz, sine/square, £10-80.

Each easy-assembly kit includes all parts, printed circuit, case, postage etc. instructions, money back assurance so **SEND off NOW.**

### CAMBRIDGE KITS

45 (FG) Old School Lane, Milton, Cambridge

**MARDENBROOK (electronics) LIMITED** will construct electronic projects e.g. wiring of units, p.c.bs assembly etc. Please write to us at Concept House, 3 Dene Street, Dorking, Surrey.

**ARMATURES ARMATURES.** B and D, Wolf, Bridges, Makita etc. Exchange Armatures and Fields for most power tools. Obsolete models covered. S.A.E. for quotation or Ring 061-799 0624. Inter-Q-Control, 26 Broadway, Worsley, Manchester.

### PRACTICAL ELECTRONICS P.C.B.'s

in glass fibre tinned and drilled  
Dec. 77 Car Burglar Alarm 1412-1 88p.  
Feb. 78 Auto Ranging Volt Meter incl. power £3.10.  
May 78 Moving Light Display £2.96.  
May 78 Workshop Power Supply £1.97.  
C.W.O. Please.  
For full list and current boards please send S.A.E. P.C.B.'s also produced from customer's own master - please send for quote.

### PROTO DESIGN

14 Downham Road, Ramsden Heath, Billericay, Essex

### SINTEL FOR BOOKS, CMOS AND COMPONENTS

6800 Booklet 1.80, MOT CMOS Databk 3.50, 6800 Appl Man 12.95, 6800 Prog Man 5.35, SC/MP Introkit Man 0.75 NS TTL Databk 2.10, RCA CMOS Databk 5.45, 8085 User's Man 5.15, 280 Ass Long Prog Man 7.50, 280 CPU Man 5.60, 280 CTC Spec 0.80, 280 PIO Man 3.30. Also a full range of CMOS - send for free catalogue. MPU's: MEK6800D2 205.20, MC6820 7.50, 280 18.14, 280A 24.19, 280CTC 10.96, 280PIO 10.96, Memories: 2102-A 2.00, 2112A-4 3.13. Displays: Type FND500 C.C. 1.40, Type TIL321 CA. 1.40, S/TOI 5.29. Crystals: 32.768KHz 3.19. Clock ICs: AY51202 3.35, AY51224 3.73, MK50253 5.83. Soldercon Pins: 100 0.54, 1000 4.32, 3000 11.34. Free catalogue by return. All items C.W.O. Prices inclusive of VAT. Add 35p p&p. SINTEL, P.O. Box 758, 209 Cowley Road, Oxford. Tel. (0865) 49791.

### ARMATURE AND COIL WINDING ENAMELLED COPPER WIRE

Only top quality materials supplied.

All orders despatched within 24 hours.

S.W.G.	1 lb reel	1/2 lb reel
10 to 19	£2.95	£1.60
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All prices inclusive of P. & P. in U.K.

### COPPER SUPPLIES

102 Parrswood Road, Withington,  
Manchester 20 Telephone 061-445 8753

### MAKE YOUR OWN PRINTED CIRCUITS

ETCH RESIST TRANSFERS - Starter pack (5 sheets, lines, pads, I.C. pads) £1.30. Single Sheets 27p.  
FERRIC CHLORIDE - 1 lb bags 70p (P. & P. 20p).  
SOLDERCON SOCKETS - 100 65p. (quantity rates).  
PLASTIC SUPPORTS - 7 or 8 hole 6p./pair.  
S.A.E. lists sample. P. & P. 15p/order except\*.

### P.K.G. ELECTRONICS

OAK LODGE, TANSLEY, DERBYSHIRE

### 100 Resistors 75p

±W 5% c/FILM 2-20-2-2MΩ (E12)

10 each of any value. Send S.A.E. for free sample

C60 CASSETTES 30p All Cassettes In Plastic Case with Index and Screwed Assembly

C90 CASSETTES 45p

All prices include VAT. Add Postage 10p in £1

Quantity Discounts  
10 Units 5%  
50 Units 7%  
100 Units 10%

SALOP ELECTRONICS  
23 WYLE COP  
SHREWSBURY  
Tel. 53208

### BUILD THE TREASURE TRACER



### MK III Metal Locator

- Variable tuning
- Contains a best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- 4,000 already sold
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC 1 and BBC 2 TV

Send stamped, addressed envelope for leaflet

Complete Kit	£15.95	Built and tested	£20.95
Post £1.20	£1.37 VAT	Post £1.20	£1.77 VAT

MINIKITS ELECTRONICS 69 CLEVELAND ROAD  
LONDON E18 2AN (Mail Order Only)

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p, chassis punching facilities at very competitive prices, 400 models to choose from, free literature (stamp would be appreciated). BAZELLI, Dept: No. 23, St. Wilfred's, Foundry Lane, Halton, Lancaster. LA2 6LT.

We would like you to know that we make -

- BEC Cabinets
- Special cabinets
- Prototype printed circuits
- Instrument panels

We also have a quantity punching service, and undertake artwork.

G83/AT  
Cabinet



### H.M. ELECTRONICS

275a Fulwood Rd : Sheffield S10 3BD TEL: (0742) 669676  
Send 15p (refundable) for leaflets

### ETCH RESIST TRANSFER KIT SIZE 1:1

COMPLETE KIT 13 SHEETS 6in x 4 1/2in £2.50 WITH ALL SYMBOLS FOR DIRECT APPLICATION TO P.C. BOARD. INDIVIDUAL SHEETS 25p EACH. (1) MIXED SYMBOLS (2) LINES 0-05 (3) PADS (4) FISH PLATES AND CONNECTORS (5) 4 LEAD AND 3 LEAD AND PADS (6) DILs (7) BENDS 90° AND 130° (8) 8-10-12 T.O.S. CANS (9) EDGE CONNECTORS 0-15 (10) EDGE CONNECTORS 0-1 (11) LINES 0-02 (12) BENDS 0-02 (13) QUAD IN LINE.

### CIRCUIT LAYOUT TRANSFERS SIZE 2:1

ONE SHEET 12in x 9in GIVING ALL TRANSFERS AS IN ETCH RESIST FROM NO. 3 TO NO. 10 INCLUSIVE MAKES CIRCUIT LAYOUT EASY. BLACK ONLY. PRICE £1. ALSO LINES AND BENDS PRICE £1.

### FRONT AND REAR PANEL TRANSFER SIGNS

ALL STANDARD SYMBOLS AND WORDING. OVER 250 SYMBOLS, SIGNS AND WORDS. ALSO AVAILABLE IN REVERSE FOR PERSPEX ETC. CHOICE OF COLOURS RED, BLUE, BLACK OR WHITE. SIZE OF SHEET 12in x 9in. PRICE £1.

### GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

AVAILABLE ALSO IN REVERSE LETTERING. COLOURS RED, BLUE, BLACK OR WHITE. EACH SHEET 12in x 9in CONTAINS CAPITALS, LOWER CASE AND NUMERALS. 1/2in KIT OR 1/4in KIT £1 COMPLETE. STATE SIZE REQ.

ALL ORDERS DISPATCHED PROMPTLY. ALL POST AND VAT PAID.

EX. U.K. ADD 50p FOR AIR MAIL SHOP AND TRADE ENQUIRIES WELCOME.

### E. R. NICHOLLS

P.C.B. TRANSFERS, DEPT. PE  
46 LOWFIELD ROAD, STOCKPORT, CHES.  
061-480 2179



**Make  
your  
hobby  
more  
Constructive  
and  
Profitable!**

Become an

**ELECTRONICS ENGINEER  
or a TECHNICIAN ENGINEER**

At PNL we offer two, interesting, full time courses.

\* B.Sc. in Electronic and Communications Engineering.

2 'A' levels, usually Maths and Physics could qualify you for this 3 year full time degree. Specialise in Acoustics, Digital Electronics and/or Radar and Microwaves in the final year.

\* Technician Engineer Certificate.

3 'O' levels, usually Maths, Physics and English, are the entry requirements for this two year full time certificate, specialising in Computer Engineering, Sound Studio Engineering and Radar and Microwaves.

Details from: Secretary, DECE, PNL, Holloway Road, London N7 8DB.

**The Polytechnic of North London**



**Wilmslow  
Audio**

**THE firm for speakers!**

SEND 15p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND DISCOUNT PRICE LIST

ACT ● AUDAX ● BAKER  
BOWERS & WILKINS ● CASTLE ● CELESTION  
CHARTWELL ● COLES ● DALESFORD  
DECCA ● EMI ● EAGLE ● ELAC ● FANE  
GAUSS ● GOODMAN'S ● HELME ● I.M.F.  
ISOPHON ● JR ● JORDON WATTS  
KEF ● LEAK ● LOWTHER ● McKENZIE  
MONITOR AUDIO ● PEERLESS ● RADFORD  
RAM ● RICHARD ALLAN ● SEAS  
TANNOY ● VIDEOTONE ● WHARFEDALE

**WILMSLOW AUDIO (Dept. P.E. 8)  
SWAN WORKS, BANK SQUARE, WILMSLOW,  
CHESHIRE SK9 1HF**

Discount HI-FI, etc. at 5 Swan Street and 10 Swan Street  
Tel.: Wilmslow 29599 for Speakers Tel.: Wilmslow 26213 for Hi-Fi

**ORDER FORM PLEASE WRITE IN BLOCK CAPITALS**

Please insert the advertisement below in the next available issue of Practical Electronics for ..... insertions. I enclose Cheque/P.O. for £ .....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)


NAME .....

ADDRESS .....

Send to: Classified Advertisement Manager  
**PRACTICAL ELECTRONICS**  
GMG, Classified Advertisements Dept., Room 2337,  
King's Reach Tower, Stamford Street,  
London SE1 9LS. Telephone 01-261 5846

Rate:  
18p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.



## RELAYS SIEMENS, PLESSEY, etc. MINIATURE RELAYS

RELAYS. WIDE RANGE OF A.C. and D.C. RELAYS AVAILABLE from stock, phone or write in your enquiries.

### FT3 NEON FLASH TUBE

High intensity, multi turn, high voltage, neon glow, discharge flash tube. Design for ignition timing, etc. £1-50. P. & P. 25p. (£1-89 inc. VAT). 3 for £3. P. & P. 50p (£3-78 inc. VAT & P.).

### NI-CAD BATTERY

Height (mm)	Width (mm)	Length (mm)
219	75	29

35AH 1.2V Metal £7-56  
Post 50p per unit

### WHY PAY MORE?

MULTI RANGE METER. Type MF15A a.c. d.c. volts 10-50, 250, 500, 1000. Ma 0-5, 0-10 0-100. Sensitivity 2000V. 24 range, diameter 133 by 93 by 46mm. Price £6-50 plus 50p P. & P. (£7-56 inc. VAT & P.).

### METERS NEW—90mm Diameter

Type: 65C5 d.c. Mc 0-2, 0-5, 0-20, 0-50, 0-100 amp. 0-15V d.c. 0-30V d.c. Type: 62T2 a.c. M10-1V, 0-50 amp. 0-15V, 0-30V Type 65L5 R/m.c. 0-30V a.c. All at £3-50 each. P. & P. 50p (£4-32 each inc. VAT & P.).

### NEW HEAVY DUTY SOLENOID. mfg.

By Magnetic Devices. 240V a.c. operation approx. 10lbs pull at 1-25in. Price £4-00 P. & P. 60p. (£4-96 inc. VAT & P.). Similar appearance to illustration. Approx. 1 1/2" pull. Size of feet 1 1/2" x 1/2". Price £1-00 P. & P. 25p.

### MINIATURE UNISELECTOR

12 volt 11-way, 4 bank (3 non-bridging, 1 homing), £2-50. P. & P. 35p (£3-08 inc. VAT & P.).

### 600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600W of lighting except fluorescent at mains voltage. Complete with simple instructions £3-95, post 25p (£4-53 inc. VAT & P.). 1,000 watt model £5-60, post 25p (£6-32 inc. VAT & P.). 2,000 watt model £9-75, post 40p (£10-96 inc. VAT & P.).

### MICRO SWITCHES

Sub min Honeywell roller m/s type 3115m 9061. 10 for £2-50 post paid.  
LEVER OPERATED 20 amp. C/O. Mfg. by Unimac USA. 10 for £4, P. & P. 50p (min. order 10) (£4-86 inc. VAT).  
D.P. C/O lever m/s switch mfg. by Cherry Co. USA. Precious metal low resistance contacts. 10 for £2-25 P. & P. 30p. Total inc. VAT £3-02 (min. 10).  
Sub min lever m/s switch type MML 46 10 for £2-50.

### 24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25lb pull 1 inch travel. Two x approx. 1 1/2 pull jin travel. 6 x approx. 4oz pull jin travel. One 24V d.c. 1 heavy duty single make relay. Price £3. Post £1 (£4-32 inc. VAT & P.). ABSOLUTE BARGAIN.

### VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced totally enclosed 9in rotor, with max. air delivery of 1.5 cubic metres per min. Max static pressure 600mm WG. Suction or blow from 2 side-by-side 37mm I.D. circular apertures fitted to base of unit. Powerful continuously rated 115V a.c. motor mounted on alloy base with fixing facilities. Dimensions length 22cm x width 25cm x height 25cm. These units are ex equipment but have had minimum use. Fully tested prior to despatch. Price £12 - £150 P. & P. (£14-58 inc. VAT & P.). Suitable transformer for 230/240V a.c. £6 - £1 P. & P. (£7-56 inc. VAT & P.).

### CENTRIFUGAL BLOWER

Smith type FFB  
1806 022 220/240V A.C. Aperture 10 x 43cm overall size 16 x 14cm. Price £3-75 P. & P. 75p. (inc. VAT £4-86). Other types available on request.

### INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for field work, constant speed clutch. Size L 8in. W 4in. H 6in weight 6lb, 500V, 500 megohms, £49. Post 80p (£53-78 inc. VAT & P.). 1,000V, 1,000MΩ, £55. Post 80p (£60-26 inc. VAT & P.). SAE for leaflet.

## VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V All Types SHROUDED TYPE

200 watt (1 amp) inc. a.c. voltmeter	£12-50
0-5 KVA (2 1/2 amp) (MAX)	£15-00
1 KVA (5 amp) (MAX)	£19-50
2 KVA (10 amp) (MAX)	£32-00
3 KVA (15 amp) (MAX)	£39-50
4 KVA (20 amp) (MAX)	£60-00

CARRIAGE AND PACKING EXTRA

### L.T. TRANSFORMERS PRIMARY

0-220V/240V  
0-12V/24V at 1 amp, £2-50. P. & P. 50p (£3-24 inc. VAT & P.).  
13-0-13V at 1 amp, £2-50. P. & P. 50p (£3-24 inc. VAT & P.).  
25-0-25V at 2 1/2 amp, £4-50. P. & P. 75p (£5-67 inc. VAT & P.).  
0-12V/24V 10 amp, £12-35. P. & P. £1-50 (£14-96 inc. VAT & P.).  
0-10-15V at 3 amp, (ex new equip) £2-50. P. & P. 50p (£3-24 inc. VAT & P.).  
0-4V/6V/24V/32V at 12 amp, £13. P. & P. £1-50 (£15-66 inc. VAT & P.).  
0-12V at 20 amp or 0-24V at 10 amp, £12-00. P. & P. £1-50 (£15-01 inc. VAT & P.).  
0-6V/12V/17V/18V/20V at 20 amp, £14. P. & P. £1-50 (£16-74 inc. VAT & P.).  
0-6V/12V at 20 amp, £11-85. P. & P. £1 (£13-88 inc. VAT & P.).

Other types in stock—phone your enquiries.

### STROBE! STROBE! STROBE!

#### HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. Price £18. Post £1 (£20-56 inc. VAT & P.). Specially designed case and reflector for Hy-Light £8-25. Post £1 (£9-99 inc. VAT & P.).

#### XENON FLASHGUN TUBES

Range available from stock S.A.E. for details

### WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (foolscap) for details.

#### Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding heavy duty brush assembly, continuously rated.  
25 WATT 10/25/50/100/150/250/500/1kΩ/1-5kΩ. £2-40. Post 20p (£2-81 inc. VAT & P.).  
50 WATT 100/250/5kΩ £2-90. Post 25p (£3-40 inc. VAT & P.).  
100 WATT 1/5/10/25/50/100/250/500/1kΩ/1-5kΩ/2-5kΩ/3-5kΩ £5-40. Post 35p (£6-21 inc. VAT & P.).  
Black, Silver, Skirted knob calibrated in Nos. 1-9 1 1/2in. dia. brass bush. Ideal for above Rheostats 24p each.

### RESET COUNTER

230V a.c. 3 digits mfg. Veeder Root Type LL 1441 £1-75. P. & P. 25p (£2-16 inc. VAT & P.). 7 fig 24V d.c. non set £1-50. P. & P. 25p (£1-89 inc. VAT & P.). 6 fig 24V d.c. resettable £3. P. & P. 25p (£3-51 inc. VAT & P.).

### 230V a.c. FAN ASSEMBLY.

Powerful continuously rated a.c. motor complete with 5 blade 6 1/2in. Aluminium fan. Price £3-00. P. & P. 65p (£3-94).

### BIG INCH

Tiny precision built 3RPM U.S.A. motor size only 1 x 1 1/2in. a.c. op. supplied with resistor for 230V a.c. Price £2. P. & P. 20p (£2-37 inc. VAT & P.). 4 for £5 post paid (£5-40 inc. VAT & P.).

### CITENCO 19 RPM

FHP motor type C 7333/15 220/240V a.c. 19 r.p.m. reversible motor. torque 14.5 kg. gear ratio 144-1. Brand new incl. capacitors. our price £14-25. P. & P. £1-25 (£16-20 inc. VAT & P.).

## VAT

AT CURRENT RATE MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED

# SERVICE TRADING CO.

ACCOUNT CUSTOMERS MIN. ORDER £10-00

## GEARED MOTORS

100 r.p.m. 115lb.in. 110V, 50Hz 2.8A. single phase split capacitor motor. Immense power. Continuously rated. Totally enclosed. Fan cooled in-line gearbox. Length 250mm. Dia 135mm. Spindle dia. 15.5mm. Length 145mm. Ex-equipment tested £12. Post £1 50 (£14-58 inc. VAT & P.). Suitable transformer 230/240V operation £8. Post 75p (£9-45 inc. VAT & P.).

### BODINE TYPE N.C.I. GEARED MOTOR

(Type J) 71 r.p.m. torque 10lb.in. Reversible 1/70th h.p. 50Hz. The above precision made U.S.A. motor is offered in as new condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. Input. Price, either type £6-25. Post 75p (£7-56 inc. VAT & P.) or less transformer £3-75. Post 50p (£4-75 inc. VAT & P.). (Type 3) 71 r.p.m. 4 lb.in. 230V a.c. Continuously rated Reversible. £6-50. Post 75p (£7-83 inc. VAT & P.). 28 rpm 20lbs inch 115v. a.c. Reversible similar to above drawing. Mfg. by Wynstruments. Price £4-75 + 75p P. & P. Total inc. VAT £5-94. Supplied complete with transformer for 240V. a.c. operation £7-25. P. & P. £1-00. Total inc. VAT £8-91.

Crouzet 230/240V, AC 2RPM synchronous geared motor. Brand new £2-90 p&p 30p. (£3-45 incl VAT) (quantity discount available.)

### FRACMO

56 r.p.m., 50lb.in. 240V a.c. 50Hz, 0.7 amp, sharp length 35mm, dia 16mm, weight 6 kilos 600 grammes. Price £15 00 P. & P. £1-50 (£17-82).

### PARVALUX GEARED MOTOR

230/240V A.C. 30 rpm 50lbs inch. Price £15 00 P. & P. £1-00 (£17-82 inc. VAT).

### COMPRESSOR

Precision built by Emerson USA. Horizontally opposed twin head diaphragm type producing 20lbs. Plus P.S.I. per head. 3-5 plus C.F.M. Output virtually pulse free. Powered by 110V A.C. motor size 30x23x15cm, weight 7 kilos. Price £20 p&p £2-00 (inc. VAT £23-76). Suitable transformer for 230/240V A.C. £8-00 p&p £1-00 (inc. VAT £9-72).

### A.E.G. WATER PUMP

200/240V a.c. motor, 2,850 r.p.m. 480W approx. 1/2 h.p. Driving a centrifugal pump with 1 1/2" inlet and outlet delivering approx. 40 gallons per min. at 10ft head. Ideal for pumping or circulating any non-corrosive light viscosity liquid. Dozens of uses in industrial labs, etc. Note this pump is not self-priming. Price £15. Post 75p (£17-01 inc. VAT & P.).

### PROGRAMME TIMERS

12 cam model £7-50. Post 60p (£8-75 inc. VAT & P.). Also available for 50V operation. Price as above.

### Time Switch

Venner Type ERD Time switch 200/250V a.c. 30 amp contact 2 off every 24 hrs. at any manually pre-set time. 36 hour Spring Reserve and day omitting device. Built to highest Electricity Board specification. Price £7.75. P. & P. 75p (£9-18).

### SANGAMO WESTON TIME SWITCH

Type S251 200/250v. a.c. 2 on/2 off every 24 hours. 20 amps. contacts with override switch. dia. 4 x 3 price £6-00. P. & P. 50p inc. VAT £7-02. Also available with Solar dial.

### AEG TIME SWITCH 200/250v. a.c.

1 on/1 off every 24 hours 80 amps contact (ideal storage heaters) spring reverse £10-00. P. & P. 50p inc. VAT £11-34.

11 pin top entry plug complete with 11 pin PC socket 35p for pair. 10 for £3-50. P. & P. 60p + VAT £4-43. Min. 10 pair.

### FRACMO

1400 rpm H.P. 1/30 continuously rated 115V a.c., supplied complete with transformer for 230/240V a.c. op. Complete with anti vibration cradle mounting £10-00. P. & P. £1-00 (£11-88 inc. VAT & P.).

### PARVALUX 230/250V a.c.

500 (bold) rpm, 3 1/2 lbs inch. 2 right angled spindles £11-00 P. & P. £1-00 (£12-96 inc. VAT & P.).

Personal callers only. Open Sat.


9 LITTLE NEWPORT STREET  
LONDON WC2H 7JJ  
Phone 01-437 0576

All Mail Orders—Callers—Ample Parking  
Dept. PE12, 57 BRIDGMAN ROAD  
CHISWICK, LONDON W4 5BB  
Phone 01-995 1560

Showroom open Mon.-Fri.

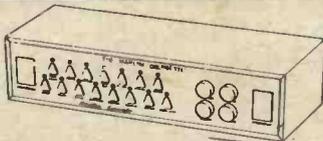
# MAPLIN

everything for the modern D.I.Y. electronics enthusiast and more.



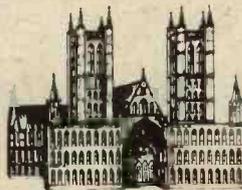
## THE 'DRUMSETTE' RHYTHM GENERATOR

Organists, pianists, guitarists... an automatic drum set to accompany you! Nine highly realistic instruments play fifteen different rhythms. Fifteen rhythm-select touch switches and a touch plate for stop/start without rhythm change gives absolute ease of operation. Build it yourself for under £65 including smart teak-effect cabinet. See it and hear it in our shop! Send for full construction details now: MES49 price 25p. (All prices include V.A.T. and postage & packing).


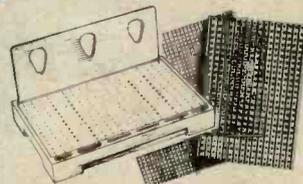
## REVERBERATION SYSTEMS

High quality spring line driver module uses 4 integrated circuits and two transistors. Built and tested circuit board with wiring instructions for spring line. XB85G, price £6.00. Power supply to suit driver module costs around £2.50 and construction details are in catalogue, or ask for leaflet MES24. Mechanical spring lines: Short line (XL08J): £4.49; Long line (XB84F): £10.39. (All prices include V.A.T. and p & p.)



## BOARDS AND PCB's


Pages 59 to 61 of our catalogue show you our range of Veroboards and S-Decs or if you prefer to make your own pcb's a range of etching systems including the novel etch-in-a-bag system, plus printed circuit transfers for the professional finish to your boards.

## 9-CHANNEL RADIO CONTROL SYSTEM

A comprehensive model control system, featuring nine independent fully proportional channels achieved by a design using very few components thus keeping the cost to a minimum. Full construction details in our booklet (XF03D)

price £1.20.

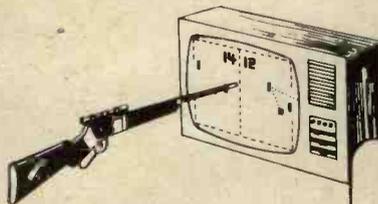All prices include V.A.T. and postage & packing.




## T.V. GAME

A fascinating TV game kit that plays football, tennis, squash and practice for only £21.59. Reprint of construction details 25p. Add on rifle kit only £10.60. (All prices include V.A.T. and p&p).


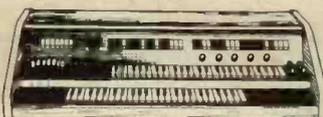
## AUDIO MIXER

A superb stereo audio mixer. It can be equipped with up to 16 input modules of your choice and its performance matches that of the very best tape-recorders and hi-fi equipment. It meets the requirements of professional recording studios, FM radio stations, concert halls and theatres. Full construction details in our catalogue. A component schedule is available on request.




## ELECTRONIC ORGAN

The only organ you can build in stages and tailor to your requirements as you go along—and at each stage you'll have a fully working instrument. We haven't got the gimmicks yet—(they're coming soon) but we have got the most beautiful sounds—you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.



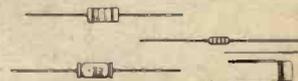
## MICROPROCESSOR

Build a mini-computer with our microprocessor kit. Features: 48 different instruction types; 256 bytes of read/write memory (more are easily added) microprocessor can address up to 65,536 8 bit-bytes. Complete kit for use with teletype etc (XB91Y) £74.10. 20-key keyboard for use with above (in place of teletype) (XB92A) £71.11. Both kits with detailed instruction books. See our newsletters for details of additional RAM's, tri-state interfacing chips, number-cruncher and standard cassette tape-recorder interface to store your programmes. (All prices include V.A.T. and p&p.)


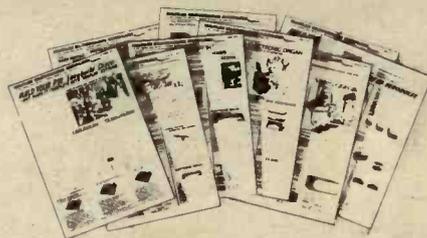
## MASSIVE RANGE OF COMPONENTS

For instance the capacitor section in our catalogue includes non-polarised electrolytics and our resistor section includes even 1% tolerance types. Get our fascinating catalogue now—you won't regret it.



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices - our latest special offers - details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).



## IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations! Over 30 pages of complete projects to build! Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!

**DON'T MISS OUT! SEND 60p NOW!**

## MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155

Shop: 284, London Road, Westcliff-on-Sea, Essex

(Closed on Mondays) Telephone: Southend (0702) 715157

## POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_