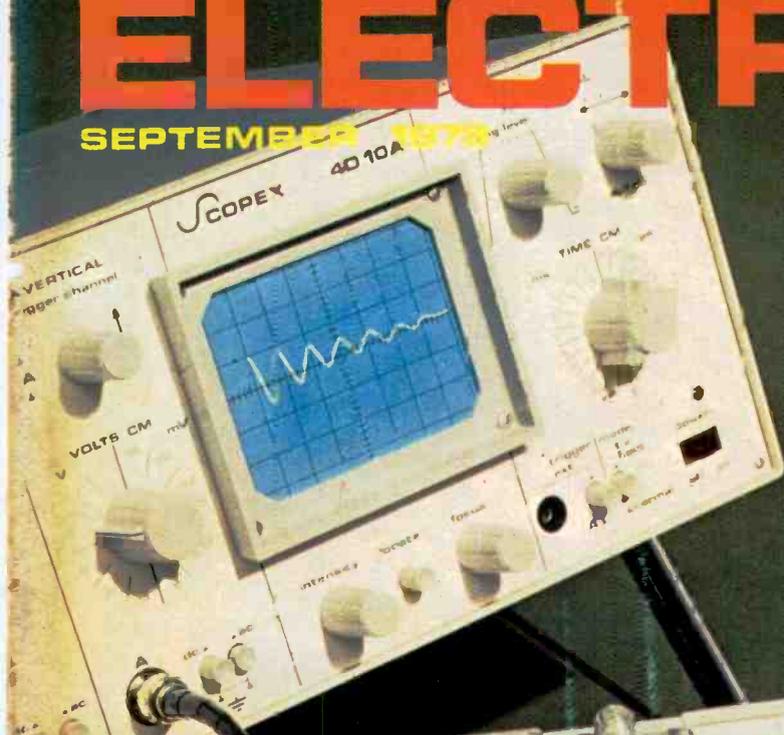


PRACTICAL

ELECTRONICS

SEPTEMBER 1978

45p



ANALOGUE COMPUTER



ALSO INSIDE...

Electronic COMBINATION LOCK • METRONOME

Teleplay now presents COLOURCARTS WITH FREE STAR* OFFERS

A whole library of easy to assemble cartridge games for you and all the family to enjoy
- all in full colour - works OK on Black and White TV
- will save you pounds in the long run.

Our INTRODUCTORY OFFER consists of a bargain that cannot be snuffed at - a Kit consisting of a Professional Finished Inject Moulded Box - Joystick Hand Controls - one cartridge on which consists of 10 games - Football, Tennis, Solo Squash (1 & 2 players), Hockey, Basketball (1 & 2 players), Shoot etc. Mains Adaptor. All holes are pre-drilled - No Special equipment required. You'll be surprised how easy it is to assemble this superbly enjoyable kit!

We offer
all this to you
for ONLY
£28.90
inc. VAT and P&P.
Fully Assembled
Add £7.00

Every 3 months a NEW game will become available to you and those already under production include Submarines, Space War, Wipe Out and many more. The price of these will vary from £12 to £19 depending upon the complexity of the game.

Additional Cartridges NOW available include:
Stunt Cycle - 4 games - Cartridge and Hand Controls - £14.90
Tank Battle - Cartridge and Hand Controls - £18.90
Road Race - 2 games - Cartridge - Controls already with basic kit - £12.90

Watch this page each month for new cartridges, as they become available.

Cartridges come complete with printed case and easy to follow assembly instructions.

Electrical knowledge is not a necessity to assemble this project - just simple soldering.

Cheques and Postal Orders to be made payable to TELEPLAY: send your order (No Stamp Needed) to Teleplay, Freepost, Barnet, EN5 2BR or telephone your order quoting your Barclaycard or Access number. Queries and Technical Advice offered either by phone or by calling at our shop.



SHOP OPEN - 10am to 7pm - Monday to Saturday

CLOSE TO NEW BARNET BR STATION - MOORGATE LINE



All parts fully guaranteed.

EUROPE'S LARGEST STOCKIST OF TV GAME COMPONENTS.

teleplay

14 Station Road, New Barnet, Herts EN5 1QW Tel: 01-440 7033/01-441 2922

PRACTICAL ELECTRONICS

VOLUME 14 No. 13 SEPTEMBER 1978

CONSTRUCTIONAL PROJECTS

ANALOGUE COMPUTER-1 <i>by P. J. Kronis BSc</i> Mathematical operations and circuits	970
COMBINATION LOCK <i>by E. A. Parr</i> Double combination for added security	990
THERMOSTAT CONTROL <i>by M. Edmunds</i> For the photographer who does his own developing	1002
SOUND TRACK MONITOR <i>by J. Schmid</i> Alerts the operator when the end of a recording is reached	1006
METRONOME <i>by M. Butt</i> Simple emphasised beat unit	1010
KEYBOARD <i>by L. G. Parkin BA</i> Provide an eight bit binary word by pressing two keys	1014

GENERAL FEATURES

WAVE ENERGY <i>by M. Abbott</i> Can the sea provide the UK with electricity?	976
STRICTLY INSTRUMENTAL <i>by K. Lenton-Smith</i> Signetics TDA 1008 electronic music i.c.	988
INGENUITY UNLIMITED Simple Clock—Beethoven's Doorbell—Electronic Combination Lock—Distortion Assessment—Protection for a Model Train Speed Controller—Simple Alarm	993
SEMICONDUCTOR UPDATE <i>by R. W. Coles</i> A look at some recently released devices	998

NEWS AND COMMENT


EDITORIAL	969
READOUT A selection of readers letters	974
BOOK REVIEWS Selected new books we have received	980, 1013
MARKET PLACE Interesting new products	985
INDUSTRY NOTEBOOK <i>by Nexus</i> What's happening inside industry	1001
SPACEWATCH <i>by Frank W. Hyde</i> Soyus-29 and Salyut-6, USSR Launchings, India and the USSR, GOES-3, Place in Space	1005
PATENTS REVIEW Thought provoking ideas on file at the British Patents Office	1020

Our October issue will be on sale Friday, 8 September 1978
(for details of contents see page 975)

© IPC Magazines Limited 1978. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

I.C.E. MULTIMETERS

TWICE the information in HALF the size

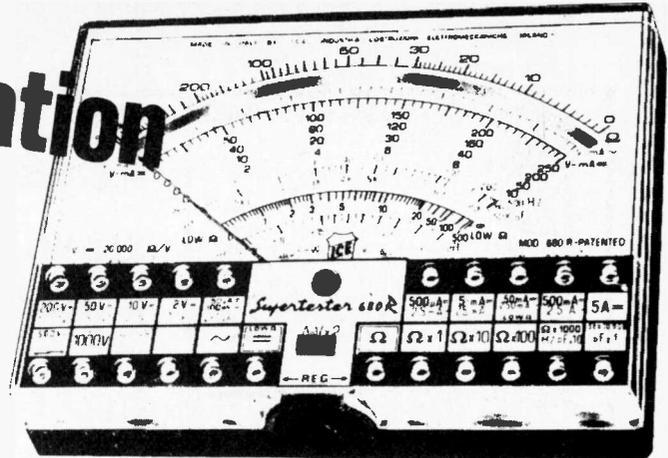

The I.C.E. range of multimeters provide an unrivalled combination of maximum performance within minimum dimensions, at a truly low cost. Plus, a complete range of add-on accessories for more ranges, more functions.

Supertester 680R (illustrated)

- * 20k Ω /V, $\pm 1\%$ fsd on d.c.
- 4k Ω /V, $\pm 2\%$ fsd on a.c.
- * 80 Ranges - 10 Functions
- * 140 x 105 x 55mm

£32.00 + VAT

(For Mail Order add 80p P&P)

Supertester 680G

- * 20k Ω /V, $\pm 2\%$ fsd on d.c.
- 4k Ω /V, $\pm 2\%$ fsd on a.c.
- * 48 Ranges - 10 Functions
- * 109 x 113 x 37mm

£24.50 + VAT

(For Mail Order add 80p P&P)

Microtest 80

- * 20k Ω /V, $\pm 2\%$ fsd on d.c.
- 4k Ω /V, $\pm 2\%$ fsd on a.c.
- * 40 Ranges - 8 Functions
- * Complete with case - only 93 x 95 x 23mm

£16.60 + VAT

(For Mail Order add 80p P&P)


All I.C.E. multimeters are supplied complete with unbreakable plastic carrying case, test leads, etc. and a 50-plus page, fully detailed and illustrated Operating and Maintenance Manual.

Now available from selected stockists. Write or phone for list, or for details of direct mail-order service.



Electronic Brokers Ltd.
49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781

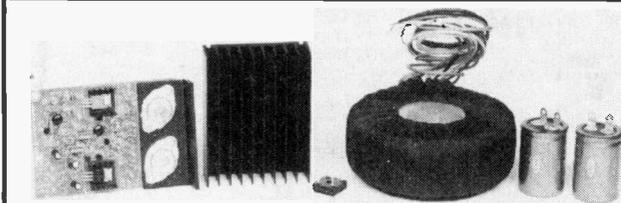TWO NEW SUPERMODULES: 170W INTO 4 OR 8 OHMS



By popular demand we have designed higher powered versions of our well known modules. The CE 1704 which gives 170W into 4 ohms and the CE 1708 which gives 170W into 8 ohms are physically similar to the original types and have the same combination of compatible performance features which makes CRIMSON amplification audibly superior to the competition and the only choice if you have an ear for music. We have also produced suitable power supplies which again use our superb TOROIDAL TRANSFORMERS, only 50mm high, with a 120-240 primary and single bolt fixing. Write or phone for more information and biased opinions.

POWER AMPLIFIER MODULES	Home	Europe
CE 808 80W/8 ohms 35-0-35V	£18.30	£18.80
CE 1004 100W/4 ohms 35-0-35V	£18.22	£18.30
CE 1008 100W/8 ohms 45-0-45V	£23.22	£23.00
CE 1704 170W/4 ohms 45-0-45V	£28.12	£28.46
CE 1708 170W/8 ohms 60-0-60V	£31.90	£31.04

TOROIDAL POWER SUPPLIES	Home	Europe
CPS 1 for 2 x CE 608 or 1 x CE 1004	£14.47	£18.40
CPS 2 for 2 x CE 1004 or 2/4 x CE 608	£16.82	£20.57
CPS 3 for 2 x CE 1008 or 1 x CE 1704	£17.66	£21.35
CPS 4 for 1 x CE 1008	£15.31	£19.18
CPS 5 for 1 x CE 1708	£22.68	£28.50
CPS 6 for 2 x CE 1704 or 2 x CE 1708	£23.98	£27.70

HEATSINKS	Home	Europe
LIGHT DUTY 50mm 2°C/W	£0.90	£1.30
MEDIUM POWER 100mm 1.4°C/W	£1.60	£2.40
DISCO/GRDUP 150mm 1.1°C/W	£2.30	£3.85

THERMAL CUT-OUTS	Home	Europe
Recommended for improved reliability		
70°C for use with Free Air Heatsink	£1.80	£1.90
40°C for use with Fan Cooled Heatsink	£1.80	£1.90

T.H.D.	: TYPICALLY < .01% ANY POWER, 1kHz, 8 OHMS
T.I.D.	: INSIGNIFICANT
SLEW RATE LIMIT	: 25V/ μ S.
S/N RATIO	: 110dB
FREQ. RESPONSE	: 10Hz - 35kHz, -3dB
STABILITY	: UNCONDITIONAL
PROTECTION	: DRIVES ANY LOAD SAFELY
SENSITIVITY	: 775mV (250mV or 100mV ON REQUEST)
SIZE	: 120 x 80 x 25mm

CRIMSON ELEKTRIK
Please note our new address and telephone number:
1A STAMFORD STREET, LEICESTER LE1 6NL
Telephone: (0533) 537722

Home prices include V.A.T. and postage. C.O.D. 90p extra, £100 limit. Export no problem. European prices include carriage, insurance and handling, payment in Sterling by bank draft, P.O., International Giro or Money Order. Outside Europe, please write for specific quote by return. Send SAE or two International Reply Coupons for full literature. Favourable trade quantity price list on request. High quality pre-amp circuit 20p.

TRANSISTORS Medium Power MP 8112 @ 15p, MP 8512 @ 15p.
50 VARI-CAP DIODES LIKE BA 102 Untested @ 57p.
CMOS MOTOROLA CD 4011 25 for £2.75.
MOS LEVEL SENSOR TAA 320A with data @ 35p.
SUB-MIN TANTALUMS 4.7uf 10v.w. @ 6 for 25p.
ITT .1uf 100v.w. POLYESTER CAPACITORS @ 20p doz.
100 ASSORTED C 280 CAPACITORS @ 57p.
MAINS TRANSFORMERS 240 volt Input Type 1, 55 volt 10 Amp @ £5.50 (P&P 25p); Type 2, 24 volt Tapped at 14 volt 1 Amp @ £1.30 (P & P 25p); Type 3, 22-0-22 volt 500mA @ £1.80 (P&P 25p).
MC 1350 WIDE BAND AMPLIFIER 400kHz to 45MHz @ 45p.
1" COIL FORMERS with core. 6 for 25p.
50 BC 107-8-9 TRANSISTORS Assorted Untested @ 57p.
VHF FETS J310 @ 20p each.
1000uf 40v.w. ELECTROLYTICS at 3 for 35p.
80 ASSORTED WIRE WOUND RESISTORS 1 to 10 watt @ 57p.
2200uf 100v.w. ELECTROLYTICS for 80p.
1000pf SOLDER-IN FEED THRU's @ 20p doz.
DISC CERAMICS .22uf 6v.w., .1uf 18v.w., .02uf 50v.w., .01uf 50v.w., 1000pf 100v.w. All 20p doz.
1 Amp TRANSISTORS PNP BCX 36 @ 12p, BCX 37 @ 10p.
12" 8 ohm LOUDSPEAKERS at 75p.
200 ASSORTED 1/2 watt RESISTORS for 75p.
FERRANTI ZTX 108 TRANSISTORS 7 for 50p.
ERIE REDCAP SUB-MINIATURE .01uf 100v.w. CAPACITORS 5p each.
30 ASSORTED 10XAJ CRYSTALS 5100 to 7900kHz for £1.10.
MULLARD PRE-AMPLIFIER I.C. TAA 435 with data @ 40p.
1MHz PLUS 100kHz CRYSTAL with Calibrator circuit @ £2.
400mW UNMARKED GOOD ZENERS 3.6v, 6.8v, 10v, 11v, 12v, 13v, 16v, 24v, 30v, 33v, 36v. All at 10 for 40p.
1.2k 6 WATT VARIABLE WIRE WOUND RESISTORS 1" Spindle @ 22p.
STUD MOUNTING DIODES 100 PIV 10 Amp @ 15p, 4 for 50p, 100 PIV 30 Amp @ 40p.
S.A.W. TV FILTERS Untested 3 for 35p.
ELECTROLYTIC CAPACITORS 20+20uf 450v.w. @ 20p, 32+32uf 275v.w. @ 10p, 32+32uf 350v.w. @ 20p, 50+50uf 275v.w. @ 15p, 3300uf 63v.w. @ 50p, 4700uf 63v.w. @ 60p.
100 ASSORTED MULLARD C280 CAPACITORS for 57p.
ELECTRET MICROPHONE INSERTS with FET PRE-AMP @ £1.85.
TEXAS S.C.R.'s TIC 47. 200 PIV 300mA @ 18p each.
SPECIAL F.M. FRONT END with Manufacturer's circuit @ £4.
3 PIN MAINS PLUG AND SOCKET like R.C. European type with 2 metres of Cable 75p pair.
1uf 25v.w. ELECTROLYTIC CAPACITORS 6 for 25p.
100 ASSORTED DISC CERAMICS for 57p.
.01uf 125v.w. 1% CAPACITORS at 10p each.
5 WATT NPN DARLINGTON TRANSISTORS @ 20p, 3 for 50p.
AUDIO I.C. LM380 with circuits @ 80p.
MINIATURE 2 POLE 4 WAY SWITCHES @ 20p.
WIRE ENDED SPARK GAPS at 10p each.
0.2" LEDs with Holders. Red @ 15p, Green @ 18p.
30mA 0.5 Volt SILICON SOLAR CELLS @ 50p.

Please add 20p for post and packing, unless otherwise stated, on U.K. orders under £2. Overseas orders at cost.

J. BIRKETT
RADIO COMPONENT SUPPLIERS
25 The Strait, Lincoln LN2 1JF Tel. 20767

EASY BUILD SPEAKER DIY KITS
Specially designed by RT-VC for cost conscious hi-fi enthusiasts, these kits incorporate two teak simulate enclosures, two EMI 13" x 8" (approx.) woofers, two tweeters and a pair of matching crossovers. Supplied complete with an easy-to-follow circuit diagram, and crossover components.

STEREO PAIR Input 15 watts rms, 30 watts peak, each unit. Cabinet size 20" x 11" x 9 1/2" (approx.). **£28.00** + p & p £5.50

SPEAKERS AVAILABLE WITHOUT CABINETS. It's the units which we supply with the enclosures illustrated. Size 13" x 8" (approx.) woofer (EMI) 2 1/2" app. **£17.00** per tweeter, and matching crossover components. stereo pair. Power handling 15 watts rms, 30 watts peak. + p & p £3.40

COMPACT FOR TOP VALUE These infinite baffle enclosures come to you ready mitered and professionally finished. Each cabinet measures approx. 12" x 9" x 5" deep, and is in wood simulate. Complete with two 8" (approx.) speakers for maximum power handling of 7 watts. **£8.50** + p & p £2.20

SPEAKERS Two models - Duo I lb. teak veneer, 12 watts rms, 24 watts peak, 10 1/2" x 13 1/2" x 7 1/2" (approx.). Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2" approx. Duo I lb **£17** PER PAIR + p & p £6.50 Duo III **£52** PER PAIR + p & p £7.50

DECCA 20 WATTS STEREO SPEAKER stereo pair. This matching loudspeaker system is hand made, kit comprises of two 8" diameter approx. base drive unit, with heavy die cast chassis laminated cones with rolled P.V.C. surrounds, two 3 1/2" diameter approx. domed tweeters complete with crossover networks. **£4.00** p & p **£20.00**

PORTABLE DISCO CONSOLE Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. Simply connects into your existing slave or external amplifier. **£64.00**

AM/FM STEREO TUNER AMPLIFIER CHASSIS COMPLETE
Ready built. Designed in a slim form for compact, modern installation. Rotary Controls Vol On/Off, Bass, Treble, Balance. Push Buttons for Gram, Tape VHF, MW, LW and 5 button rotary selection switch.

Power Supply Selenium Bridge—350V DC from 210-250V AC, 50Hz input. Aerial Ferrite 8" x 1/2" built into chassis for LW and MW plus flying lead for FM aerial.

Power Output 5 watts per channel. Sine at 2% THD into 15 Ohm, 7 watts speech and music.

Tape Sensitivity Playback 400mV/30K OHM, for max. output. Record 200mV/50K output available from 25kHz (150mV/100K) deviation FM signal. Frequency Range (Audio) 50Hz to 17kHz within +1dB.

Radio: FM sensitivity for 3dB below limiting better than 10uV. AM sensitivity for 20dB S/N, MW 350uV/Metre, LW 1mV/Metre. Size approx. length 16" x height 2 1/2" x depth 4 1/2". **£19.95** p & p £2.50

PERSONAL SHOPPERS

'VIDEOMASTER' Super Score TV Game with Pistol. Mains operated. **£14.95**

'VIDEOMASTER' Door Tunes (24 different tunes). **£9.95**

16016 VOLT MAINS TRANSFORMER, 2 1/2 amp. **£2.50**

BSR Record auto deck on plinth with stereo cartridge ready wired. **£11.95**

LED 5 function men's digital watch stainless steel finish. **£5.95**

LCD 5 function men's digital watch stainless steel finish. **£7.95**

LCD 8 function CHRONOGRAPH men's digital watch stainless steel finish. **£12.95**

STEREO CASSETTE record/replay fully built P.C. board. Used, without guarantee. (Ex Equipment.) **£1.95**

MICRO CASSETTE Tape Recorder. **£13.95**

100K Multiturn Varicap tuning pots, 6 for **£1.00**

MUSIC CENTRE CABINET with hinged smoke acrylic top, finished in natural teak veneers, size 30 1/4" x 14 1/2" x 7 1/4" approx. **£5.95**

MULLARD Built power supply **£1.50**

DECCA DC1000 Stereo Cassette P.C.B. complete with switch oscillator coils and tape-heads. **£2.95**

7" TAPE Transport Mechanisms. A selection from **£8.95**

Opportunity!

AUDIO MODULES IN BARGAIN PACKS
CURRENT CATALOGUE

PRICE £ AT OVER 25 PER PACK

- SEE OUR PRICES**
- 1** PACK 1. 2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE £4.95** p+p £1.00
 - 2** PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **OUR PRICE £7.45** p+p £1.00
 - 3** PACK 3. 1 x LP1179/2 FM Tuning head with AM gang, 1 x LP1165/1 AM/FM IF module, 2 x LP1173/10w. RMS output power audio amp modules + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE £9.95** p+p £1.00



ACCESSORIES
Suitable power supply parts including mains transformer, rectifier, smoothing and output capacitors. **£1.00** p+p **£1.95**

Recommended set of rotary stereo controls comprising BASS, TREBLE, VOLUME and BALANCE. **p+p 50p 95p**

THIS MONTH'S OFFER
added to our bargain packs
When you buy Pack 3 at £9.95, together with a mains transformer at £1.95 and a set of controls for 35p you receive FREE a Mullard LP1400 Decoder to match. **£12.85** p & p £2.50

TRADE ENQUIRIES INVITED

20 x 20 WATT STEREO AMPLIFIER **£29.90**
Superb Viscount IV unit in teak finished cabinet. Silver fascia with aluminium rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary. Rear panel features two mains outlets, 01N speaker and input sockets, plus fuse. 20 x 20 watts rms, 40 + 40 watts peak.

30 x 30 WATT AMPLIFIER KIT **£29.00**
For the experienced constructor complete in every detail. Similar facilities as Viscount IV amplifier. **p & p £2.50** 60+60 peak.

AVAILABLE NOW built and fully tested with output 30 + 30 watts rms, 60 + 60 peak.

SPECIAL OFFER: PACKAGE PRICE WITH 30 x 30 KIT Mk. II version, operates into 4 to 15 OHMS speakers. Designed by R & TVC for the experienced constructor. Complete in every detail, facilities as Viscount IV amplifier 60 + 60 peak. Supplied with 2 Goodmans Compact 12" bass woofer with cropped 14,000 Gauss Magnet, 30 watt rms, handling + 3 1/2" approx. tweeters and crossovers. **£49.00** p & p **£4.00**

ADD-ON STEREO CASSETTE TAPE DECK KIT
Designed for the experienced O.I.Y. man. This kit comprises of a tape transport mechanism, ready built and tested record/replay electronics with twin V.U. meters and level control for mating with mechanism. Specifications: Sensitivity - Mic. 0.85 mV or 20K OHMS; Din. 40mV or 400K OHMS; Output - 300mV RMS per channel or 1KHz from 2K OHMS source; Cross Talk - -30db; Tape Counter - 3 Digit; Resettable; Frequency Response - 40Hz - 8KHz ± 6db; Deck Motor - 9 Volt DC with electronic speed regulations; Key Functions - Record, Rewind, Fast Forward, Play, Stop & Eject. **£19.95** p & p **£2.50**

Opt. extras: Mains transformer to suite **£2.50** + **£1** p & p

45 WATT MONO DISCO AMP **£35.00** p & p **£2.50**
Size approx. 13 1/2" x 5 1/2" x 6 1/2"
45 watts rms, 90 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push pull switches. Independent bass and treble controls and master volume.

70 & 100 WATT MONO DISCO AMP **£57**
Size approx. 14" x 4" x 10 1/2"
Brushed aluminium fascia and rotary controls. Five vertical slide controls: master volume, tape level, mic level, deck level, PLUS INTER-DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control. 70 watt (PFL) lets YOU hear next disc before fading. 140 watt peak it in. VU meter monitors output level. **p & p £4.00**

Output 100 watts RMS 200 watts peak. 100 watt **£65**

CHASSIS RECORD PLAYER DECKS
Record changer with cue, stereo ceramic cartridge. **p & p £2.00**

GARRARD DECK CC10A **£7.95**
BSR MP60 TYPE Single play record deck less cartridge. **p & p £2.55**

Cartridges to suit above:
Acos, magnetic stereo **£4.95**
Ceramic stereo **£1.95**
BSR automatic record player deck cueing device and stereo ceramic head. **p & p £2.55** **£9.95**

BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and de luxe plinth and cover. **p & p £4.50**

Home 8 Track cartridge player. This unit will match with the Viscount IV 9" x 8" x 3 1/2". **p & p £2.50** **£16.50**

RTVC Order by giving credit card number ONLY.

323 EDGWARE ROAD, LONDON W2
210 HIGH STREET, ACTON W3 6NG
ALL PRICES INCLUDE VAT AT 12%
All items subject to availability. Price correct 1.7.78 and subject to change without notice.

EASY TO BUILD RECORD PLAYER KIT
for the D-I-Y man who requires a stereo unit at a budget price, comprising ready assembled stereo amp, module, Garrard auto/manual deck with cueing device, pre-cut and finished cabinet work. Output 4 watts per channel, phones socket and record/replay socket including 2 SPHERICAL HIFI speakers. **£19.95** p & p **£4.05**

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Half day Thursday. ACTON: Mail Order only. No callers. GOODS NOT DESPATCHED OUTSIDE UK

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

Colour T.V. Servicing
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name _____

Address _____

Age _____

ICS

To ICS, Dept. 273Y, Intertext House,
London SW8 4UJ
or telephone 01-622 9911 (all hours)

CRESCENT RADIO LTD.

1 ST. MICHAELS TERRACE,
WOOD GREEN, LONDON,
N22 4SJ (MAIL ORDER DEPT.)

01-888 4474

TELESCOPIC AERIAL

11 Section Telescopic Aerial
Length, extended: 1 metre (39 1/2")
Length, closed: 135mm (5 1/2")
Nut and bolt fixing through recess at base of aerial.
Only 75p each + 12 1/2% VAT

"FLIP" I

AN ELECTRONIC VERSION OF TWO-UP OR ODDS AND EVENS.
We supply a complete kit of parts which includes a strong case and attractive front panel to give the finished game a long life and professional appearance.
Full assembly instructions are supplied. If you can solder you can make this great game.
An ideal first project to introduce you to electronics.
Not only will 'FLIP' start you on a great hobby but you will own a game which will amuse you and your friends for hours.
Complete Kit: £5.25 + 8% VAT
Post Free!

BARGAIN LOUDSPEAKER

Goodmans 5" 8 ohm long throw heavy duty L/SPKR.
Mounting plate is integral with L/S chassis and has fixing holes with centres spaced at 5 1/2" (diagonally).
Only £5.00 + 12 1/2% VAT.

2 WAY 8 OHM

HEAVY DUTY COVER.

A 2 way 8 ohm H/D Cover suitable for L/S systems up to 100W. Input via screw terminals. Fitted with a 3 position 'HF LEVEL' switch which selects either Flat, -3dB or -6dB.
Buy now while stocks last!
Only £3.00 + 8% VAT.

3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT

1000W lighting per channel, max.
A 3 channel sound to light unit housed in a robust metal case, with a sensitivity control for each channel i.e. Bass, middle and treble. Full instructions make this unit easy to connect to your present amplifier.
S.A.E. for spec. sheet.
Still only £20.00 + 8% VAT.

POWER SUPPLY UNIT

PP1 - switched 3, 4 1/2, 6, 7 1/2, 9 and 12 volts at 500mA, with on/off switch and pilot light.
Size: 130 x 55 x 75mm approx.
Our Price: £6.00 + 8% VAT

SIX-PIECE MINIATURE SCREWDRIVER SET

Six precision screwdrivers in a hinged plastic box. Blade sizes: 0.8mm, 1.4mm, 2mm, 2.4mm, 2.9mm, 3.8mm.
Our Price: £1.75 + 8% VAT



PIEZO ELECTRIC HORN UNITS

High Quality, High Power Tweeter. No Xover reqd. Freq. Response: 3.8kHz-28kHz. Spec. sheet sent on receipt of S.A.E.
Our Price: £6.50 + 8% VAT.

BARGAIN TRANSFORMER

240V Primary 12-0-12V 500mA sec.
Approx. size: 60 x 40 x 50mm. Fixing centres: 75mm.
Price: £1.50 + 8% VAT.



'P&P' orders up to £5, Add 30p.
Orders £5-£10, Add 50p.
All orders over £10 post free!
Please add V.A.T. as shown.
S.A.E. with all enquiries please.



Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N.13.

Random FLASHER UNIT
Wired ready for use
Complete with three
100 watt coloured lamps
that flash independently
at random
£19.95

TWIN BANK 6 LIGHT UNIT
(less lamps) LENGTH 14 1/2 inches
BC Fitting £11.35
ES Fitting £11.35
EACH

Sound to Light MASTER UNIT
600 WATTS PER CHANNEL
£30.95
INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INPUT SOCKET

TYPE A SPOT
(less lamp)
BC Fitting £2.30
ES Fitting £2.30
EACH

TYPE B 3 BANK UNIT
(Less Lamps)
BC Fitting £7.99
ES Fitting £7.99

TWIN BANK 12 LIGHT UNIT
(less lamps) Length 31 1/2
BC Fitting £18.50
ES Fitting £18.50
EACH

100 WATT SPOT LAMPS
RED, YELLOW, GREEN
BLUE CLEAR £1.50 each
Maximum 3 lamps
E4-50
B.C. or E.S. Fitting

ALL PRICES INCLUDE V.A.T. AND POST & PACKING
(These prices apply to the United Kingdom only)

Send 20p for illustrated leaflet & price list.

ALBEN ENGINEERING CO. LTD.
DEPT. PE THE CRESCENT, WORSTHORNE,
BURNLEY, LANCS. Tel: Burnley 20940

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. or BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P ADD 30p* TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE.

MINIMUM ORDER £2.00 PLEASE.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked *. To the rest add 12%.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground, Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday 9.00 am - 6.00 pm. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type. (Values are in μ F)
400V: 0.001, 0.0015, 0.0022, 0.0033 8p; 0.0047, 0.0068, 0.01, 0.015, 0.018 9p; 0.022, 0.033, 10p; 0.047, 0.068, 14p; 0.10, 15p; 0.15, 0.22, 22p; 0.33, 0.47 39p; 0.68 45p.
160V: 0.039 0.15 0.22 13p; 0.33 0.47 22p; 0.68 0.29p; 1.5 33p; 2.2 39p; 4.7 47p.
DUBILIER: 1000V: 0.01 0.015 16p; 0.022 18p; 0.047 16p; 0.1 34p; 0.47 43p.

POLYESTER RADIAL LEAD (Values in μ F) 250V:
0-01 0.015; 0-022 0.027 5p; 0-033 0.047; 0-068 0.1 7p; 0-15 12p;
0-22 0.33 14p; 0.47 16p; 0-68 20p; 1-0 24p; 1-5 27p; 2-2 31p.

FEED THROUGH CAPACITORS
100 μ F 350V 8p

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in μ F)
6.3V: 0.47 1.0 1.5 2.2 2.5 3.3 4.7 6.8 8 10 15 22 25p; 47 32 50 12p; 63 100 27p;
50V: 1.0 7p; 5.0 100 220 25p; 470 50p; 1000 2200 68p; 40V: 22 33 9p; 100 12p; 330 62p; 470 64p; 35V: 10 33 7p; 330 470 32p; 1000 45p; 25V: 10 22 47 6p; 80 100 16p;
220 250 13p; 470 640 25p; 1000 27p; 1500 30p; 2200 41p; 3300 52p; 4700 54p; 16V:
10 40 47 68 7p; 100 125 8p; 330 470 16p; 1000 1500 20p; 2200 34p; 10V: 4 10 6p;
640 100 10p 14p.

TAG-END TYPE: 70V, 200V 98p; 400V 121p; 50V, 300V 75p; 40V, 4000V 70p; 250V 65p;
25V, 4700 48p; 2000 37p; 40V, 2000 100p; 2000 95p; 325V 20p; 100 50 100 190p.

TANTALUM BEAD CAPACITORS
35V: 0.1 μ F 0.22 0.33 0.47 0.68 1.0 2.2 μ F 3.3 4.7 6.8 25V: 1.5 1.0 20V: 1.5 1.6V: 10 μ F 13p each
47 100 40p, 10V: 2.2 μ F 33 47 6V:
47 68 100 31p; 68 100 μ F 20p each

MYLAR FILM CAPACITORS
100V: 0.001 0.002 0.005 0.01 μ F 5p
0.015 0.02 0.04 0.05 0.05 μ F 7p
0.1 μ F 0.15 0.2 9p 50V: 0.47, 11p

CERAMIC CAPACITORS - 50V
0.5p to 10nF 3p each
15nF 22nF 33nF 47nF 4p each
0.1 μ F 6p

POLYESTER CAPACITORS
100pF to 1nF 6p; 1.5nF to 47nF 10p.

SILVER MICA (Values in pF) 3:3 4.7 6.8 10 12 15 22 33 47 50 68 75 80 85 100 120 150 220 250 330 360 390 600 820 18p each
1000 1800 2000 2200 20p each

CERAMIC TRIMMER CAPACITORS
2 7pF 4 15pF 6 25pF 8 30pF 20p

MINIATURE TYPE TRIMMERS
2.5 6pF 3 10pF 10 40pF 22p
5 25pF 5 45pF 60pF 88pF 30p

COMPRESSION TRIMMERS
1 300pF 10 80pF 25 190pF 100 50pF 1250pF 25p 38p

JACK PLUGS
Screened chrome Plastic body open metal sockets
2.5mm 2p 8p
3.5mm 1p 10p
MONO 23p 13p
STEREO 31p 18p

SOCKETS
in line couplers
moulded with break contacts
11p 11p
12p 12p
13p 13p
15p 15p

POTENTIOMETERS (AB or GENI)
Carbon Track, JW Log & JW Linear values
5000, 1K & 2K (lin only) Single 27p
5K:2M:20 single gang 13
5K:0.2M:20 dual gang DP switch 60p
5K:0.2M:20 dual gang stereo 70p

SLIDER POTENTIOMETERS
0.25W log and linear values 60mm
5K:0.500K:20 single gang 70p
10K:0.500K:20 dual gang 80p
Self Stick Graduated Bezels 20p

PRESET POTENTIOMETERS
Vertical & Horizontal
0.1W 500 - 3M Miniature 8p
0.25W 1000 - 5M Miniature 10p
0.25W 2000 - 4.7M Vert 10p

RESISTORS - E-rie make 5% Carbon
Miniature High Stability Low noise
RANGE VAL 1.99 100 100 100
1W 2.0 4.7M £24 1.5p 1p
1W 2.0 4.7M £12 2p 1.5p
1W 2.0 10M £12 5p 4p
2% Metal Film 100:1M 6p 4p
1% Metal Film 50:1M 10p 8p
100 price applies to Resistors of each type
not mixed values.

PE String ENSEMBLE
Components now available.

OPTO ELECTRONICS*
LEDs plus clip 27p
TL1209 Red 13
TL1211 Gm 18
TL1212 Yellow 22
2" Red 17
2" Yellow Green 21
Spare Clips 2
LS400 299
TL307 675
ORP12 68
2N5777 54
7 Seg Displays
TL312 C An 3" 105
TL313 C Cth 3" 105
TL321 C An 5" 115
TL322 C Cth 5" 115
DI704 C Cth 3" 99
DL707 C.A. 3" 99
FND357 140
LCD 3 1/2 digit 975
LCD 4 digit 975

SWITCHES*
TOGGLE 2A 250V 59p
SPST 28p
DPDT 38p
4 pole on/off 54p
SUB-MIN TOGGLE SP changeover 59p
SPST on/off 54p
DPDT 6 tags 70p
DPDT Centre off 79p
SLIDE 250V: 115p
1A DPDT 14p
1A DP c/over 15p
4A DPDT 13p
4 pole c/over 24p
PUSH BUTTON Spring loaded
ACY39 78 BC214L 10
ACY40 48 BC307B 14
ACY44 39 BC308 13
AD140 10 BCX27 15
AD149 90 BC338 12
AD161 42 BC41 30
AD162 42 BC461 30
AF114 25 BC547 11
AF115 25 BC549 11
AF117 25 BC557 13
AF118 55 BC558 12
AF121 48 BCY30* 57
AF124 55 BCY34* 75
AF125 55 BCY36A* 40
AD127 78 BCY40* 78
AF139 35 BCY43* 22
AF178 70 BCY58* 22
AF180 70 BCY59* 22
AF186 50 BCY70* 15
AF239 42 BCY71* 15
ASV26 45 BCY72* 16
ASV27 45 BCY78* 16
BC107 9 BD115 62
BC107B 10 BD121 95
BC108 9 BD123 98
BC108B 12 BD124 115
BC108C 12 BD131 16
BC109 9 BD132 38
BC109B 12 BD133 43
BC109C 12 BD135 36
BC113 17 BD136 37
BC114 19 BD137 36
BC115 20 BD138 36
BC116 19 BD139 36
BC117 15 BD140 36
BC118 19 BD142 59
BC119 26 BD145 198
BC134 19 BD222* 60
AD135 20 BD65A* 75
BC136 18 BD696A* 75
BC137 20 BDY17 195
BC138 20 BDY60 110
BC142 25 BDY61 165
BC143 25 BF115 22
AD132 25 BF154 47
BC148 7 BF156 29
BC149 8 BF167 25
BC153 14 BF173 25
BC154 10 BF177 24
BC157 10 BF178 25
BC159 11 BF180 20
BC160 27 BF181 20
BC167A 11 BF182 20
BC168C 12 BF183 30
BC169C 10 BF184 30

TRANSISTORS
BF194 10 OC42 32
BF195 10 OC43 55
BF196 10 OC44 31
BF197 10 OC45 20
BF198 10 OC46 28
BF200* 28
BF201 19
BF202 14
BF203 14
BF204 14
BF1000 14

SWITCHES* Miniature Non-Locking
Push to Make 15p Push to Break 25p
ROCKER (white) 10A 250V
SP changeover centre off 30p
ROCKER: (black) on/off 10A 250V 23p
ROCKER: (illuminated) (white) Lights when on 3A 240V 52p
ROTARY: (ADJUSTABLE STOP) 1 pole/2-12 way 2p/2-6W 3p/2.4W 4p/2-3W 41p
ROTARY: Mains 250V AC, 4 Amp 45p

DIL SOCKETS* (Low Profile - Texas)
9 pin 10p; 14 pin 12p; 16 pin 13p; 18 pin 20p;
20 pin 27p; 24 pin 30p; 28 pin 42p; 40 pin 55p.

DIGITAL MULTIMETER

Announcing DM900 - The Digital Multimeter with a difference - It measures Capacitance too. (as published in E.T.I. August 1978)

Throw away your analogue meters, here's digital accuracy at only half the price of an equivalent commercial Multimeter.

The DM900 is a 3 1/2 digit multimeter with an 0.5in L.C.D. display incorporating:
5 AC & DC Voltage ranges; 6 Resistance ranges.
5 AC & DC Current ranges; 4 Capacitance ranges.

The prototype accuracy is better than 1%.

This is a unique design using the latest MOS ICs and

SAXON ENTERTAINMENTS LTD

THE PIONEERS OF MODULAR DISCO/P.A. EQUIPMENT
NOW OFFER PACKAGE DEALS AT INCOMPARABLE PRICES

CENTAUR STEREO DISCOS

C/W LIGHT SHOW & DISPLAY,
TWIN SPEAKERS & LEADS

Standard 100W

£249 or Deposit £57.12
12 Months @ £21.75 or 24 Months @ £12.26

Super 200W

£299 or Deposit £68.12
12 Months @ £25.86 or 24 Months @ £14.56

GXL 200W (with twin 200 watt cabinets)

£389 or Deposit £87.32
12 Months @ £33.31 or 24 Months @ £18.76

COMPLETE STEREO
ROADSHOWS – BUILT IN
SOUND TO LIGHT/SEQUENCER
& DISPLAY
TWO YEAR GUARANTEE

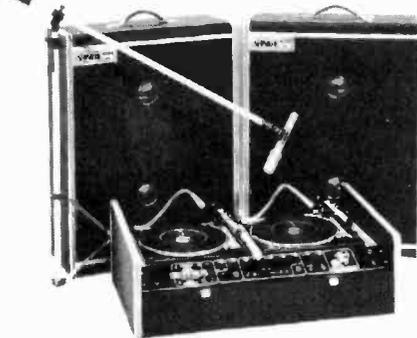


illustration shows GXL Centaur System

These systems feature full mixing for two decks tape & mic with monitoring facilities – override and are supplied complete with sound to light + sequencer, display, speaker leads etc.

JUST PLUG IN AND GO!

BSR Decks – 17,000 Line Loudspeakers – Rugged Aluminium Trimmed Cabinets – Cue Light And Phones Output – Slave Output – Deck Lights/Motor Starts (GXL)

MINI DISCO 100 WATT MONO SYSTEM

£179.50 Deposit £41.66
12 Months @ £15.56

Similar in appearance to the Centaur and complete with loudspeakers and leads.

Headphones to suit any system £7.50
EM507 Electret Mic £15.00
ECM 81 Electret Mic £19.95
Boom Stand £15.50
Carriage on all disco and PA systems £10.00
(Included in H.P. Prices)


**20% Deposit Terms
On All Orders
Over £150 – 12 or 24
Months – Low Interest**

D.I.Y. MODULES FOR ALL DISCO/P.A. AMPLIFIERS

SA308 30W 8 ohms 45V	£9.95*	SUPPLY FOR TWO MODULES	£10.90*
SA604 60W 4 ohms 50V	£13.25	SUPPLY FOR TWO MODULES	£13.50
SA608 60W 8 ohms 65V	£14.25	SUPPLY FOR TWO MODULES	
SA1204 120W 4 ohms 75V	£15.95	SUPPLY FOR ONE MODULE	£22.50
SA1208 120W 8 ohms 95V	£21.00	SUPPLY FOR TWO MODULES	
SA2404 240W 4 ohms 95V	£29.50	SUPPLY FOR ONE MODULE	

0.2% Distortion, 30Hz-20, KHz ± 2dB, Fully Short/Open Circuit proof input sensitivity 240 mV to suit most mixers – D.C. & Output Fuses fitted.

TOP QUALITY COMPONENTS THROUGHOUT

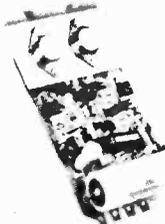

DISCO MIXERS – COMPLETE OR MODULAR



MONO OR STEREO
WITH AUTOFADE

Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted – full instructions supplied.

FEATURES INCLUDE:

Twin Deck – Mic & Tape Inputs – Wide range bass & treble controls – Full headphone monitoring – Crossfade – Professional standard performance.


MODULES	£22.50
Mono module	£33.50
Stereo module	£39.95
Panel	£5.50
Kit of knobs/sockets etc	£5.50
COMPLETE MIXERS (with case)	
Mono 18V	£39.50
Stereo 18V	£57.50
Mono mains	£45.75
Stereo mains	£63.75

COMPLETE LIGHTING CONTROL AT YOUR FINGERTIPS!



Lighting Control Unit Mk II	£44.50
4kW Sequencer + Sound Light + Dimmers	
+ Automatic Level Integrated Logic Circuitry	Module £32.50 Panel £2.95
Three Channel Sound to Light	£26.75
3kW 1-240W input – master	Module £19.75 Panel £2.95
Plus channel controls	

STROBE UNITS

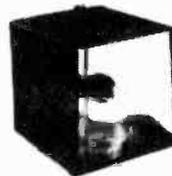

Pro-Strobe 4-6 Joules £37.50
Super Strobe 2-3 Joules £22.50
(Pro-Strobe has external trigger facility).

SPARES & ACCESSORIES – LOUDSPEAKERS & CABINETS

Rope Lights – Red or Multicolour	£39.50	Melos Echo Chamber	£59.00
per 30ft.		Headphones	£7.50*
Rope Light Controller for up to 120 ft	£30.00	Sirens: English Police, USA Police,	
Fuzz Lights – Red/Blue/Yellow/Green	£22.80	Destroyer, Alien Voice Simulator	£7.50
Magnetic Cartridge Equalisers	£3.50*	Bulgin 8 way lighting plug/socket	£1.90

PROJECTORS – PLUTO – NEW LOW PRICES!!! CHOICE OF WHEEL/CASSETTE

P150 150W Tungsten	£37.50	Liquid wheels	£7.50
P500 100W Q.I.	£74.95	Cassettes	£8.00
P500 250W Q.I.	£84.95	Picture wheels from	£4.75
		(Wide choice available)	

100 Watt Chassis Loudspeakers 12"	£23.50	18"	£47.50	(Add £1.50 corr.)
Empty Loudspeaker Cabinets: Small 12"	£15.50	Large 12" x 12"	£21.50	Small 2 x 12" £22.50
		1 x 18"	£29.50	

Projector lamps: A1167 £2.90. M6 £5.65.
100W Spot lamps Red/Blue/Yellow/Green
£1.50 ea £13.50 for 10
MD Spot Banks: 3-way 300W £19.50,
4-way 400W £22.50.
Bubble machines (optokinetics) £41.50


Strobe tubes 80W £8.50
ICI Vynide 50" wide £3.50 Metre
Kickproof Grille 24" wide £3.25 Metre
Kick Resistant Grill 50" wide £3.25 Metre.
FULL RANGE OF RE-AN PRODUCTS IN STOCK
SEND FOR OUR BROCHURE NOW!!

PIEZO HORNS only £7.50 YES! – only £7.50

(As fitted to our package PA system)

Direct from Motorola Inc., USA at an
UNBEATABLE PRICE

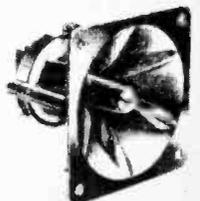No crossover required 4kHz – 30kHz rated
75W/8 ohms 150W/4 ohms use two per 100W
amplifier – Full instructions supplied.





PACKAGE P.A. SYSTEMS (2 Year Guarantee)

Complete with PIEZO horn columns fitted with 100 watt units (100 watt system illustrated)

100 Watt £159.90

Deposit £38.46


12 Months @ £14.28

Includes 4 Channel 100 Watt Amplifier with Treble, Bass and Master Controls plus Leads and Twin Piezo Horn Columns (shown on right).

200 Watt £249.00

Deposit £57.12

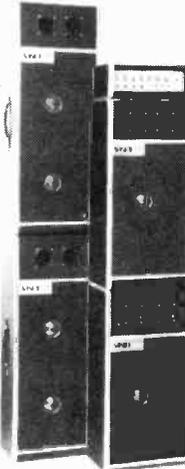12 Months @ £19.11 or 24 Months @ £10.66
zsix Mixed Inputs plus Three Sets of Bass and Treble Controls plus Slave Output and Master Control.



ACCESSORIES


Melos Echo Unit £59.00

A high quality Cassette Tape Echo Unit giving long tape life, infinitely variable echo depth and speed control. Suitable for all mics. and instruments.

High quality Boom Stand £15.50. Floor Stand £9.90. ECM81 Condenser Mic. - Removable Lead - Good Anti-Feedback £19.95.* EM507 Condenser Mic. - Good Value £15.00. Phasers £19.80.

D.I.Y. MODULES FOR P.A. SYSTEMS Mono or Stereo

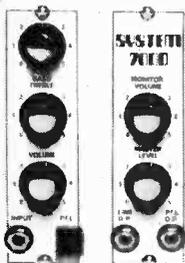Make your own mixer - Mono/Stereo - up to 20 channels with these, easy to wire modules - Available as PCB's or assembled on panels.



Input Stages Up to 20	Mono PCB	£5.95	Mono C/W panel etc.	£8.95
	Stereo PCB	£9.50	Stereo C/W panel etc.	£12.50
Mixer/Monitor (One only per system)	Mono PCB	£5.95	Mono C/W panel etc.	£8.95
	Stereo PCB	£9.50	Stereo C/W panel etc.	£12.50
Power supply for up to 20 channels		£9.50	Blank panel	£1.00

Send for free brochure for complete specification

Saxon AP100 Amplifier £45

Four mixing inputs - 100W into 4 ohms
Wide range bass & treble controls
+ master - Twin outputs

Saxon 150 Amplifier £59

Four mixing inputs - 100W into 8 ohms
150W into 4 ohms - wide range bass
& treble controls + master



All prices subject to 8% VAT except where asterisked (12½%)
Shop premises open Tues to Sat 9 am - 5 pm Lunch 12.30 - 1.30 pm
Mail order dept open Mon to Fri 10 am - 4 pm Ring 01-684 6385

TO ORDER

By Post. Send your requirements with cheque crossed P.O. or 60p COD charge to address below or just send your Access or Barclay Card Number NOT THE CARD.

By Phone. You may order COD. Access or Barclay Card.

Post & Packing 50p on all orders except where stated.

SAXON ENTERTAINMENTS LTD.

327 Whitehorse Road, Croydon, Surrey.

All Enquiries Large SAE Please Brochures on request

The latest kit innovation! from Sparkrite




the quickest fitting

CLIP ON

capacitive discharge

electronic ignition

in KIT FORM

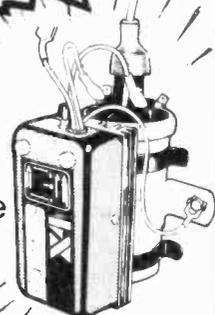

- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT, post & packing.

Electronics Design Associates, Dept. PE9, 82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Electronics Design Associates, Dept. PE9
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name

Address

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQ'D.

Send SAE if brochure only required.

X4 KIT	£14.95
TACHS PULSE SLAVE UNIT	£3.35

I enclose cheque/PO's for

£

Cheque No.

Please state polarity pos or neg earth.

Access or Barclaycard No.

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted

from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

- ★ **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!
- ★ **SAVE ON MONEY**—Bulk buying means lowest prices—just compare with others!
- ★ **HAVE THE RIGHT PART**—No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW. MARKED DEVICES—SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

- K001** 50V ceramic plate capacitors, 5%. 10 of each value 22pF to 1000pF. Total 210, **£3-35**
- K002** Extended range, 22pF to 0.1µF. 330 values **£4-90**
- K003** Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for **£4-75**
- K004** Mylar capacitors, min 100V type, 10 each all values from 1000pF to 10,000pF. Total 130 for **£3-75**
- K005** Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 series 5% 160V. Total 370 for **£12-30**
- K006** Tantalum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2, 3, 4, 7, 8, all 35V; 10/25 15/16 22/16 33/10 47/6 100/3. Total 170 tants for **£14-20**
- K007** Electrolytic capacitors 25V working, small physical size, 10 each of these popular values: 1, 2, 4, 7, 10, 22, 47, 100µF. Total 70 for **£3-50**
- K008** Extended range, as above, also including 220, 470 and 1000µF. Total 100 for **£5-90**
- K021** Miniature carbon film 5% resistors, CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors, **£6-00**
- K022** Extended range, total 850 resistors from 1R to 10M **£8-30**
- K041** Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 2.7V to 36V. E24 series. Total 280 for **£15-30**
- K042** As above but 5 of each value **£8-70**

DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices—signal diodes, high voltage rects and zeners may all be included. These are being offered at the incredibly low price of £1.25/1000— or a bag of 2500 for £2.25. Bag of 10,000 £8. Box of 25,000 £17.50. Box of 100,000 £60.

SPECIAL SUMMER OFFERS

Audio IC's	£1-40	76013N	£1-00
76023N	£1-00	76033N	£1-40
LM380	80p	TBA8105	70p
Linear IC's etc.			
741 (BDIL)	18p	8D131	24p
555	25p	8D132	28p
1N4148	2p	2N3819	18p

74 SERIES PACK

Selection of boards containing many different 74 series IC's. 20 for £1; 50 for £2.20; 100 for £4.

TTL PANEL

52 logic IC's including 32 x 74161 (4 bit binary counter) + 16 tant bead caps, R's, C's, etc. Over £30 worth of TTL alone!! ONLY **£3-00**

DISC CERAMIC PACK

Amazing variety of values and voltages from a few pF to 2.2µF 3V to 3kV! 200 £1, 500 £2.25, 1000 £4-00

EXPERIMENTERS CALCULATOR

Based on the C500 chip, this pack of parts enables the more experienced constructor to make an 8 digit 4 function calculator. The comprehensive data supplied includes full size layout of PCB required, types of suitable display and keyboard that can be used etc. Components included in the pack are C500 calculator chip, driver IC, all components for inverter/clock circuits, R's C's etc. All for only **£3-50**.

TRANSFORMERS

All mains primary: 12-0-12V 50mA 85p; 100mA 95p; 1A £2-50, 6-0-6V 100mA 85p; 1½A £2-40, 9-0-9V 75mA 85p; 1A £2-10, Multitapped type 0-12-15-20-24-30V, 1A £3-95; 2A £5-35; 3A £6-90 20V 2A £3-90; 25V 1½A £2-25; 12V 8A £4; 24V 5A £7-50; 0-22-34-41V 4A £7-50; 20V @ 300mA twice £2-50; 12V @ 250mA twice £2-00

RELAYS

W847 Low profile PC mntg 10x33x20mm 6V coil, SPCO 3A contacts **93p**

W832 Sub. min type, 10x19x10mm 12V coil DPCO 2A contacts **£1-15**

W701 6V SPCO 1A contacts 20x30x25mm Only **56p**

W817 11 pin plug in relay, rated 24V ac, but works well on 6V DC. Contacts 3 pole c/o rated 10A, 95p

W819 12V 1250R DPCO 1A contacts. Size 29x22x18mm, min plug-in type **72p**

W839 50V ac (24V DC) coil, 11 pin plug in type, 3 pole c/o 10A contacts Only **88p**

W848 Open construction mains relay, 3 sets 10A c/o contacts, **£1-20**

Send SAE for our relay list—84 types listed and illustrated.

STEREO AMPLIFIER CHASSIS £5-50

Complete and ready built. Controls: bass, treble, volume/on-off, balance. 8 transistor circuit gives 2 watts per channel output. Just needs transformer and speakers for low cost stereo amp. Suitable metal cabinet (W374) **£2-00**— or buy the amp, case and transformer for **£10-00** and get DIN speaker sockets and knobs free!!

AMPLIFIER KIT £1-75

Mono gen. purpose amp with tone and Vol/on-off controls. Utilizes sim. circuitry to above amp. Output 2W into 8 ohms. Input matched for crystal cartridge. 4 transistor circuit. Simple to build on PCB provided. Can be either battery or mains operated. (For mains powered version add £2.20 for suitable transformer.) Blue vinyl covered aluminium case to suit (W372) **£1-30**

TMS4030 RAM

4096 bit dynamic RAM with 300ns access time; 470ns cycle time; single low capacitance high level clock I/p; fully TTL compatible; low power dissipation. Supplied with data **£2-75**

MISCELLANEOUS IC's

Supplied with data if requested. MC3302 quad comp. 120p; 710 diff comp. (I099) 40p; ZN1045 precision timer £2-25; LM711 Dual diff comp 65p; LM1303 dual stereo pre-amp 75p; MC1469R voltage reg £1-50; UPIC1025H audio £3-60; 575C2 audio £2-88; TDA2640 audio £2-92; SN75110 dual line driver 70p; MC8500 CRCC gen POA

HEAT SINK OFFER

Copper T05 sink 17mm dia x 20mm, 10 for 40p; 100 for £3; 1000 for £25

PC ETCHING KIT MK III


Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, D410 etch-resist pen, abrasive cleanser, two miniature drill bits, etching dish and instructions. **£4-25**

VERO OFFCUTS

Pack A, All 0-1" Pack B, All 0-15" Pack C, Mixed Pack D, all 0-1" Plain Each pack contains 7 or 8 pieces with a total area of 100 sq. in. Each pack is **£1-30**. Also available by weight, 1lb **£4-20**, 10lb **£32-50**, 17 x 3½" Strips: 0-1" **£2-20**; 10 for **£15** 0-15" **£1-98** 0-1" Plain **£1-83**

EDGE CONNECTORS

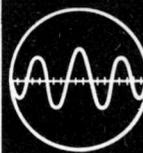
Special purchase of these 0-1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third of their original list price! 18 way 41p; 32 way 72p; 40 way 90p.



TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
PHONE 01-672 3137/672 9080
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING CONTROL SYSTEMS

NEW FROM TUAC

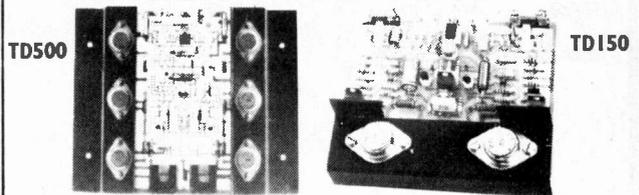

7" x 9" x 1½" ULTRA QUALITY HIGH POWER 5" x 5" x 2" New D.C. Coupled Design AMPLIFIERS

Featuring—Electronic Short Open and Thermal Overload Protection.
Brief Spec.—Input Sensitivity 0.775 v. R.M.S. (O.D.B.) at 25K Ohms. Frequency Response 20 Hz – 20 KHz. T.H.D. at full power 0.1%. Hum and Noise—100 dB Relative full output.

T.D. 500	300W into 2 Ohms. 220W into 4 Ohms. 140W into 8 Ohms.	£45-00
Power supply P.S.300		£30-00
T.D.150	150W into 4 Ohms. 100W into 8 Ohms.	£26-25
Power supply P.S. 150		£18-50
T.D. 150	60 Version 60W into 8 Ohms. 40W into 15 Ohms.	£17-75
Power supply P.S.60		£15-50

Note—P.S. 300 will drive 2 T.D. 150 amplifiers
All output ratings are R.M.S. continuous sine wave output.

TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD., (PE98) or quote Access/Barclay Card No (We accept holders phone orders 01-672 9080)

Post to—

TUAC LTD., (PE98), 119 CHARLTON ROAD, LONDON SW17 9AB.

Send stamp for our free 28 page catalogue of LIGHTING & AMPLIFIER MODULES, etc.

ELECTROVALUE

All the many types of components we supply are **BRAND NEW** and guaranteed and only from manufacturers direct or approved suppliers. *No surplus, no seconds*

ICS – TTL 7400 series			
7400 14p	7413 22p	7451 14p	7483 58p
7401 14p	7414 60p	7453 14p	7485 74p
7402 14p	7420 14p	7454 14p	7486 27p
7403 14p	7430 14p	7460 14p	7490 40p
7404 18p	7440 14p	7470 24p	7491 71p
7405 14p	7442 54p	7472 24p	7492 48p
7407 22p	7443 60p	7473 23p	7493 40p
7408 18p	7444 60p	7474 23p	7494 68p
7409 18p	7447 70p	7475 45p	7495 57p
7410 14p	7450 14p	7476 32p	7496 63p
		7477 40p	74100 73p
		7482 61p	74104 40p

OUR COMPUTER TAKES GOOD CARE OF YOUR ORDERS

SIEMENS CAPACITORS*
World famous for quality and dependability—PCB TYPES—7.5mm PCM 0.001 to 0.015 6p each; 0.15 to 0.047 7p ea. 5mm PCM 0.068 8p, 0.1 9p, 0.22 12p. CERAMIC 2.5mm PCM 0.01 4p, 0.022, 0.033, 0.047 5p, 0.068 6p, 0.01 7p. ELECTROLYTICS—1/100, 10/25, 10/63, 100/25, etc. For full range see our current lists.

RESISTORS
½, ¼, ⅓ watts*—2p each*; metal film, metal oxide and 1 watt carbon 5p ea*; good quantity discounts. Magnetic field dependent from **£1.50**. Hall Effect from **£1.23**.

SIEMENS TRANSISTORS
Silicon npn and pnp from 8p ea; LEDs, red 19p; yellow or green from 23p (3 or 5mm!); Photo transistors from 78p.

KEEN PRICES ★ GOOD SERVICE ★ WIDE RANGES

DISCOUNTS
5% if list value of order over £10
10% if list value of order over £25. Discounts available where cash (P.O. or cheque) is sent with order.

V.A.T. — Add 8% to value of order or 12½% with items marked* (No V.A.T. on overseas orders)
Goods sent post free on C.W.O. orders in U.K. over £5 list value. If under, add 27p per order.

MONTHLY BARGAIN LISTS
S.A.E. brings monthly list of bargains. Also current quick reference price list of all ranges.

Cash with order (P.O. or cheque payable to Electrovalue Ltd) or your Access or Barclaycard number. TRADE AND INDUSTRIAL ENQUIRIES INVITED


For all round satisfaction — be safe — buy it from **ELECTROVALUE**

ELECTROVALUE LTD

Dept PE9.28 St Judes Rd, Englefield Green, Egham, Surrey TW20 0HB.
Phone Egham 3603; Telex 264475.
Northern Branch (Personal shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

LOOK! Here's how you master electronics




... the practical way

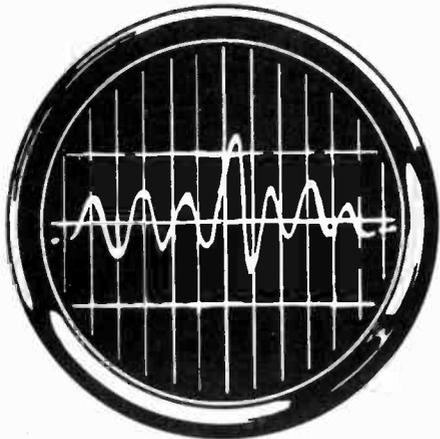

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

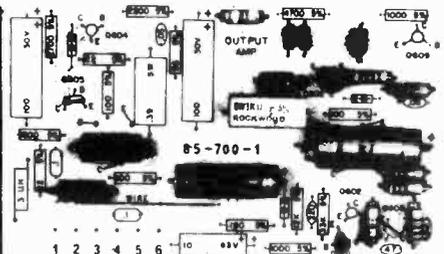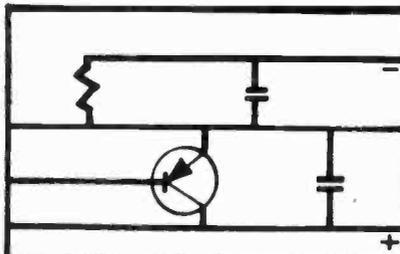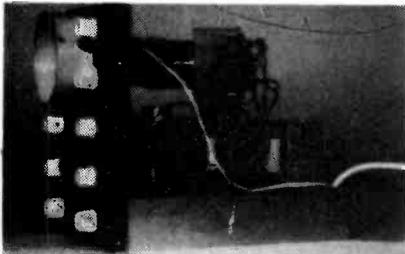All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



1 Build an oscilloscope

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.


2 Read, draw and understand circuit diagrams

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3 Carry out over 40 experiments on basic circuits

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

FREE GIFT

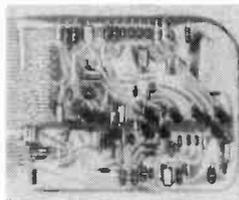

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Free!

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.


NAME

ADDRESS

PEB9

Block caps please

SUPERSOUND 13 HI-FI MONO AMPLIFIER

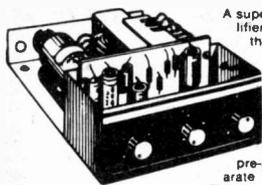

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for

8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep. AC 200-250V. PRICE £15.00 P. & P. £1.20.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State F.M. A.M. Stereo Tuner. Covering M.W. A.M. 540-1605KHz V.H.F. F.M. 88-108MHz.

Built-in Ferrite rod aerial for M.W. Full AFC and AGC on A.M. and F.M. Stereo Beacon Lamp Indicator Built-in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV R.M.S. into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2in wide x 4in high x 9 3/4in deep approx. Limited number only at £28.00 + £1.50 P. & P.

MAINS TRANSFORMER. PRI. 0:110 and 240. SEC. 28V at 1.8 amps. Also tapped at 12V .3 amp. Overall size 2 1/2" h x 3 1/2" w x 2 1/2" d. £2.50 + P & P £1.00.

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked. smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts R.M.S. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000Hz. Sensitivity better than 60mV into 1 M Ω . Full power bandwidth \pm 3dB 12-15,000Hz. Bass boost approx to \pm 12dB. Treble cut approx. to \pm 16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1A. Overall size 12in wide x 8in deep x 2 1/2in high. Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT £13.50 P. & P. 80p
(Magnetic input components 33p extra)
POWER PACK KIT £5.50 P. & P. 95p
CABINET £5.50 P. & P. 95p
SPECIAL OFFER—only £23.75 if all 3 items ordered at one time plus £1.25 P. & P.
Full after sales service
Also available ready built and tested £31.25 P. & P. £1.50

HARVERSONIC MODEL P.A. TWO ZERO



An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp.). Input 1, 15mV into 47k. Input 2, 15mV into 47k (suitable for use with mic. or guitar etc.). Input 3, 200mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240 volts. Size approx 12in wide x 5in high x 7in deep. Special introductory price £28.00 + £2.50 carriage and packing.

Mullard LP1159 RF-IF module 470 kHz £2.25 + P & P 20p. Full specification and connection details supplied.
Pye VHF FM Tuner Head covering 88-108 MHz 10.7 MHz I.F. output. 7.8V + earth. Supplied pre-aligned, with full circuit diagram with precision-gear F.M. gang and 323PF + 323PF A.M. Tuning gang only £3.15 + P. & P. 35p.
STILL AVAILABLE
HA34 3 Valve Audio Amp. 4 1/2 w/o/p. Ready built and tested £8.50 + £1.40 P. & P.
Also HSL 'Four' Amp. Similar to above but in kit form. £8.00 + £1.40 P. & P.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monoaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 25p + S.A.E. (Free with parts). All parts sold separately. ONLY £13.50 P. & P. £1.40. Also available ready built and tested £18.00 P. & P. £1.40.

'POLY PLANAR' WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 1 1/2in x 1 1/2in x 1 1/2in deep. Weight 19oz. Power handling 20W R.M.S. (40W peak) impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only £8.40 each + P. & P. (one 90p, two £1.10). Now available in either 8in round version or 4 1/2 x 8in rectangular. 10 watts R.M.S. 60Hz-20KHz £5.25 + P. & P. (one 85p, two 75p).

SPECIAL OFFER. 6 1/2in long throw, roll surround, ceramic magnet 8 ohm 10 watt speaker chassis. Specially suitable for Hi Fi £3.95 75p P. & P.
2in PLASTIC CONE HF TWEETER 4 ohm, £3.50 per matched pair + 50p P. & P.
HIGH POWER HI-FI 8 ohm Dome Tweeter, 1in voice coil. Magnet size 3in dia. Suitable for use in up to 50 watt systems. £4.50 each 60p P. & P.

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets and 5 pin din tape rec play socket are mounted on the printed circuit panel. Size approx 9 1/2in x 2 1/2in x 1in max depth. Supplied, brand new and tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £9.00 + 50p P. & P. Mains transformer with an output of 17V a.c. at 500mA can be supplied at £1.50 + 40p P. & P. if required. Full connection details supplied.

STEREO DECODER

SIZE 2" x 3" x 1/2" ready built. Pre-aligned and tested for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6.00 plus 20p P. & P. Stereo beacon light if required 40p extra.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday. Prices and specifications correct at time of press. Subject to alteration without notice.

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 MERTON HIGH ST., MERTON, LONDON, S.W.19 Tel: 01-540 3985

A few minutes from South Wimbledon Tube Station

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

CHROMASONIC electronics

56 FORTIS GREEN ROAD, MUSWELL HILL, N10 3HN
TELEPHONE: 01-883 3705

OUR LATEST CATALOGUE CONTAINS FREE 45 pence WORTH OF VOUCHERS



CONTAINS MICROPROCESSORS + BOARDS, MEMORIES, TTL, CMOS, ICs, PASSIVES, ETC., ETC.

SUPERSAVERS

ALL FULL SPEC DEVICES

TEXAS 741	TIMER 555	RED LED TIL209 (INC CLIP)
5 for	4 for	10 for
£1.00	£1.00	£1.00
VAT INCLUSIVE PRICE + 25p P. & P.		

A4 IC BOOKLET

SUPPLIED FREE WITH ORDERS OF ANY ICs WORTH £5.00 OR MORE, CONTAINS CIRCUITS, PIN CONNECTIONS AND DATA (35p + SAE IF SOLD ALONE).



4 1/2in x 3 1/2in METER. 30 μ A, 50 μ A or 100 μ A, £5.43. 19p P. & P.

MICROPHONES FOR TAPE RECORDERS

DM228R 200 ohm with 3-5 and 2.5mm Jack Plugs £1.30
DM229R 50K with 3-5 and 2.5mm Jack Plugs £1.60
DM18D 200 ohm with 5 and 3 pin Din Plugs £1.75
Postage on above microphones 11p



CARDIOID DYNAMIC MICROPHONE

Model UD-130 Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £8.02. 26p P. & P.

2in x 2in meters 1mA, 500mA, £3.65. 16p P. & P.

60 x 45mm meters 50 μ A, 100 μ A 500 μ A and 1mA VU meter, £4.46. 11p P. & P.

6V BUZZERS. 50mm diameter 30mm high, 52p. 15p. P. & P.

MULTI-METER

Model IT 1-2 20,000 ohm/volt, £10.38. 33p P. & P.



TRANSFORMERS Primary 240V
6-0-6V 100mA £0.75
9-0-9V 75mA £0.75
12-0-12V 50mA £0.85
12-0-12V 100mA £1.05
Post on above transformers 30p.
9-0-9V 1A £1.80
12-0-12V 1A £2.15
15-0-15V 1A £2.36
30-0-30V 1A £3.10
6-3V 1 1/2A £1.80
6-0-6V 1 1/2A £2.20
Post on above transformers 45p.

All above prices include V.A.T. Send 40p for new fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

It's SUMMER SALE time again!

THYRISTORS

No. THY1A/50	1 Amp	50 volt	TO5	18p
No. THY1A/400	1 Amp	400 volt	TO5	32p
No. THY3A/50	3 Amp	50 volt	TO64	32p
No. THY3A/200	3 Amp	200 volt	TO64	32p
No. THY3A/400	3 Amp	400 volt	TO64	40p
No. THY5A/50	5 Amp	50 volt	TO66	25p
No. THY5A/400	5 Amp	400 volt	TO66	40p
No. THY5A/600	5 Amp	600 volt	TO66	50p
No. C106/4	6 Amp	400 volt	TO220	45p

TRIAC

S84	10 Amp 400 volt TO220 Plastic (Non Isolated Tab)	90p
-----	--	-----

DIACS

ITT V413	Equivalent to BR100 & D32 each	12p
----------	--------------------------------	-----

SWITCHES

No. 1617B	5 x Mains Slide Switches	40p*
No. S17	5 x Miniature Slide Switches	40p*
No. S18	4 x Standard Slide Switches	40p*
No. S19	4 x Miniature Push to Make single hole mounting	40p*
No. S20	3 x Miniature Push to Break single hole mounting	40p*
No. S21	Push button Switch Pak 4 x Assorted types multi bank and singles Latching and non-Latching	£1.00*

SPECIAL OFFER! COMPONENT PAKS

Order No.	Quantity	Price
16168	5 pieces Assorted Ferrite rods	40p
16169	2 pieces Tuning gangs MW/LW	40p
16170	50 metres Single strand wire assorted wire	40p
16171	10 Reed switches	40p
16172	3 Micro switches	40p
16176	20 Assorted electrolytics	40p
16177	1 pack Assorted Hardware nuts/bolts etc.	40p
16179	20 Assorted tag strips and panels	40p
16180	15 Assorted control knobs	40p
16184	15 Assorted Fuses 100mA-5 amp	40p
16188	60W resistors mixed values 30 metres stranded wire assorted colours	40p
16187	120 1/2 watt resistors. Pre-formed. 1978 Prod. Our mix	60p*
S101	120 1/2 watt resistors. Pre-formed. 1978 Prod. Mixed values	60p*
S102	250 1/2 watt resistors. Range 100 ohms - 10 meg.	£2.00*
S103	220 1/2 watt resistors. Range 100 ohms - 10 meg.	£2.00*
S104	60 Low ohms 1/2 watt resistors. 10 - 100 ohms	60p*
S105	40 Low ohms 1/2 watt resistors. 10 - 100 ohms	60p*
S106	25 Mixed wirewound resistors	60p*
S107	20 Tantulum bead caps 0.22 - 100mF Our mix	£1.00*
S108	High quality electrolytics 10mF-500mF voltage range 15-50v. Our mix. 40 for	£1.00*
16204	C250 Pak. Contains 50 metal foil caps	£1.00*
3136	Ribbon cable flat standard 15-way multi-coloured P.V.C. insulated, stranded tin copper. 1 m	25p

SILICON POWER TRANS. N.P.N.

S97	BD371 2 Amp 1.2w. 60Vceo Hfe 40-400, Case TO92 with heat tab	5 for 60p*
S98	2N5293 R.C.A. 36w 4 Amps 75Vceo Hfe 30-120	5 for £1.00*

SILICON BRIDGE RECTS.

S99	Mixed Pak 2 - 5 Amp. 50-600v. All coded. 4 for	£1.00*
-----	--	--------

P.C. BOARD

S110	Mixed Butle, P.C.B., Fibreglass/paper, single and double-sided. Fantastic value	75p
------	---	-----

I.C. SOCKET PAKS

No. S66	11 x 8 pin DIL Sockets	£1.00
No. S67	10 x 14 pin DIL Sockets	£1.00
No. S68	9 x 16 pin DIL Sockets	£1.00
No. S69	4 x 24 pin DIL Sockets	£1.00
No. S70	3 x 28 pin DIL Sockets	£1.00

MAMMOTH I.C. PAK

Approx. 200 pieces Assorted full-out integrated circuits, including Logic 74 series, Linear, Audio and D.T.L. Many coded devices, but some unmarked - you to identify.

Order No. 16223	£1.00
-----------------	-------

CMOS I.C.'s

Type	Price	Type	Price	Type	Price	Type	Price
CD4000	14p	CD4018	85p	CD4035	£1.40	CD4056	£1.15
CD4001	16p	CD4019	45p	CD4037	78p	CD4069	32p
CD4002	16p	CD4020	95p	CD4038	78p	CD4070	32p
CD4006	80p	CD4021	85p	CD4039	68p	CD4071	20p
CD4007	16p	CD4022	80p	CD4042	85p	CD4072	20p
CD4008	80p	CD4023	18p	CD4043	78p	CD4081	20p
CD4009	50p	CD4024	64p	CD4044	78p	CD4082	20p
CD4010	50p	CD4025	18p	CD4045	£1.15	CD4510	£1.10
CD4011	18p	CD4026	£1.85	CD4046	95p	CD4511	£1.25
CD4012	17p	CD4027	48p	CD4047	78p	CD4516	£1.10
CD4013	16p	CD4028	80p	CD4048	£1.10	CD4518	£1.10
CD4015	80p	CD4029	95p	CD4050	48p	CD4520	£1.10
CD4016	42p	CD4030	48p	CD4054	95p		
CD4017	80p	CD4031	£2.20	CD4055	£1.60		

TRANSISTORS

BRAND NEW - FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price
AC107	25p	BC177	12p	BF194	*9p	TIP32A	34p
AC126	14p	BC178	12p	BF195	*9p	TIP32B	35p
AC127	16p	BC179	12p	BF196	*12p	TIP32C	36p
AC128	16p	BC182	*9p	BF200	25p	TIP41A	34p
AC128K	24p	BC182L	*9p	BF200	25p	TIP41B	35p
AC176	16p	BC183	*9p	BF200	25p	TIP41C	36p
AC176K	24p	BC183L	*9p	BF200	25p	TIP42A	36p
AC187	16p	BC184	*9p	BF500	12p	TIP42B	37p
AC187K	26p	BC184L	*9p	BF501	12p	TIP42C	38p
AC188	16p	BC212	*10p	BF52	12p	TIP2955	65p
AC188K	26p	BC212L	*10p	MPSA05	*22p	TIP3055	42p
AD161	80p	BC213	*10p	MPSA06	*22p	ZTX107	*7p
162MP	80p	BC213L	*10p	MPSA55	*22p	ZTX108	*7p
AF139	30p	BC214	*10p	MPSA56	*22p	ZTX109	*7p
AF239	30p	BC214L	*10p	OC44	12p	ZTX300	*7p
BC107	8p	BC251	*10p	OC45	12p	ZTX301	*7p
BC108	6p	BCY70	12p	OC71	9p	ZTX302	*9p
BC109	6p	BCY71	12p	OC72	12p	ZTX500	*8p
BC118	*10p	BCY72	12p	OC75	10p	ZTX501	*10p
BC147	*8p	BD115	*40p	OC81	14p	ZTX502	*12p
BC148	*8p	BD131	*35p	TIP29A	35p	2N696	10p
BC149	*8p	BD132	*37p	TIP29B	36p	2N697	10p
BC154	*16p	BF115	17p	TIP29C	38p	2N706	7p
BC157	*9p	BF167	19p	TIP30A	38p	2N706A	8p
BC158	*9p	BF173	20p	TIP30B	37p	2N708	8p
BC159	*9p	BF180	25p	TIP30C	38p	2N1302	12p
BC169C	*10p	BF181	25p	TIP31A	32p	2N1303	15p
BC170	*8p	BF182	25p	TIP31B	33p	2N1304	15p
BC171	*8p	BF183	25p	TIP31C	34p	2N1307	18p
BC172	*8p	BF184	25p	TIP31C	34p	2N1308	22p
BC173	*7p	BF185	25p			2N1309	22p

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA119	5p	8AX16/	5p	BY216	30p	OA85	7p
AAZ13	4p	OA202	5p	BY217	28p	OA90	7p
BA100	6p			BY218	28p	OA91	7p
BA115	5p	BY100	15p	BY219	28p	OA95	7p
BA144	5p	BY127	*10p	OA47	5p	IN34	5p
BA148	10p	BY210	32p	OA70	5p	IN60	6p
BA173	10p	BY211	32p	OA79	7p	IN914	4p
BAX13/	10p	BY212	32p	OA81	7p	IN4148	4p
OA200	5p	BY213	30p				

LINEAR I.C.'s

TBA800	12 pin OIL	*75p	UA711C	TO99	25p	UA748	TO99	28p	
TBA810	12 pin OIL	*£1.00	UA703	TO99 (Plastic)	20p	7558	Dual 748T	TO99	45p
TBA820	14 pin OIL	*80p	741P	8 pin DIL	18p	MC1310P	14 pin DIL	*£1.25	
LM380	14 pin DIL	*80p	7274	14 pin DIL	20p	76115	14 pin OIL	*£1.25	
LM381	14 pin DIL	*£1.35	UA741C	TO99	20p	NE555	8 pin DIL	25p	
72709	14 pin DIL	28p	72747	14 pin DIL	55p	NE556	14 pin DIL	60p	
UA709	TO99	748p	8 pin DIL	28p	SL414A	10 pin	*£1.80		

NEW CONSIGNMENT ZN 414 RADIO CHIP 75*

OPTOELECTRONICS

Displays	No.	Description	Price
No. 1510	707 LED Display	each 70p	
No. 1511	747 LED Display	each £1.50	
No. S53	DL33 Triple 7 Segment LED Display Character height 1"	each 30p	
	Common Cathode 12 pin DIL	each 30p	

2nd QUALITY LED PAKS

No. 1507	10 x LED's Assorted	75p
----------	---------------------	-----

LED CLIPS

No. 1508/125	.125	5 for 12p
No. 1508/2	.2	5 for 15p

P.O. RELAYS

S85	2 Off Post Office relays	40p
-----	--------------------------	-----

BATTERY HOLDERS

Order No. 202	to take 6 x HP7's	each 10p
---------------	-------------------	----------

EX. G.P.O. MICROSWITCHES

Order No. S51	4 for	50p
---------------	-------	-----

CABLE CLIPS

S84	50 2.5mm round single pin fixing	30p
-----	----------------------------------	-----

ZENER PAKS

No. S55	20 mixed values 400mW Zener diodes 3-10V	£1.00
No. S56	20 mixed values 400mW Zener diodes 11-33V	£1.00
No. S57	10 mixed values 1W Zener diodes 3-10V	£1.00
No. S58	10 mixed values 1W Zener diodes 11-33V	£1.00

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
BY216	30p	OA85	7p	IN34	5p	IN60	6p
BY217	28p	OA90	7p	IN914	4p	IN4148	4p
BY218	28p	OA91	7p	IN5400	10p	IN5401	11p
BY219	28p	OA95	7p	IN5402	12p	IN5403	12p
OA47	5p	IN34	5p	IN5404	13p	IN5406	16p
OA70	5p	IN60	6p	IN5407	17p	IN5408	19p
OA79	7p	IN914	4p	IN5409	19p		
OA81	7p	IN4148	4p				

SPECIAL REDUCTIONS

No. 1514	NORP 12	each 45p
No. S76	OC71	5 for £1.00
No. S83	5 NIXIE Tubes ITT 5870 ST (including Data)	£2.00

SILICON SOLAR CELLS

S109	Output 5mA at 1/2 volt	each 50p
------	------------------------	----------

AUDIO LEADS

Order No. 117	A.C. Mains connecting lead for cassette recorders and radios Telefunken type	45p*
118	5 pin DIN headphone plug to stereo socket	78p*
119	2 x 2 pin plug to inline stereo socket for headphones	60p*
123	20 ft. of coiled guitar lead	£1.15*
124	3 pin to 3 pin DIN plug	50p*
125	Audio lead 5 pin plug to 5 pin DIN plug	50p*
126	Audio lead 5 pin Din plug to tinned open ends	50p*
127	Audio lead 5 pin DIN plug to 4 phono plugs	90p*
129	Audio lead 5 pin plug to 5 pin DIN plug - Mirror Image	70p*
130	5 metre lead 2 pin DIN plug to 2 pin DIN inline socket	45p*
132	10 metre lead 2 pin DIN plug	65p*

AUDIO MODULE SALE

Type	Description	Normal Price	Sale Price
AL20A	5W RMS Power Amp	£3.35	£2.65
AL30A	10W RMS Power Amp	£3.85	£2.95
AL60	25W RMS Power Amp	£4.35	£3.55
AL80	35W RMS Power Amp	£6.95	£5.95
AL250	125W RMS Power Amp	£15.95	£14.45
SPM90	35V Power Supply	£3.75	£3.10
PA12	20-30V Power Supply for AL30A/AL20A	£1.30	£1.15
PA100	Stereo Pre-Amp for AL30A/AL20A	£6.70	£5.95
S450	Stereo Pre-Amp for AL60/AL80	£13.75	£12.45
S450	Stereo F.M. Tuner	£20.45	£18.65
MPA30	Magnetic-Ceramic Pre-Amp	£2.85	£2.55
Stereo 30	Complete Audio Chassis 7W + 7W RMS	£16.25	£14.95

POTENTIOMETERS

Slider 40mm TRAVEL

Order No.	Description	Price
16191	6 x 470 Ohm LIN Single	40p*
S24	6 x 1 K LIN Single	40p*
S25	6 x 5 K LIN Single	40p*
16192	6 x 10 K LIN Single	40p*
S26	6 x 10 K LOG Single	40p*
16193	6 x 22 K LIN Single	40p*
16195	6 x 47 K LIN Single	40p*
16194	6 x 47 K LIN Single	40p*
S27	6 x 100 K LIN Single	40p*
S28	6 x 100 K LOG Single	40p*
S29	6 x 500 K LOG Single	40p*

Slider 60mm TRAVEL

Order No.	Description	Price
S30	6 x 2.5 K LOG Single	40p*
S31	6 x 10 K LIN Single	40p*
S32	6 x 50 K LIN Single	40p*
S33	6 x 250 K LOG Single	40p*
S34	4 x 5 K LOG Dual	40p*
S35	4 x 10 K LIN Dual	40p*
S36	4 x 100 K LOG Dual	40p*
S37	4 x 1.3 MEG LOG Dual	40p*
S38	6 x 220 K LIN Single	40p*
S95	6 x 100 K LOG Single	40p*
S96	6 x 500 K LIN Single	40p*
S38	Mixed slider pots - various values and sizes - our mix	only £1.00*
S39	6 x Chrome slider knobs	40p*

WIREWOUND

Wirewound Pots. Linear 1 Watt rating. Mixed useful values. 5 for £1.00*

CARBON TYPES

S91	Car Radio type, Dual Switched Pot P.C. mounting 100 K Lin switched 2.5 K Lin	each 60p*
-----	--	-----------

DUAL POTS P.C. MOUNTING

6mm Shaft	Description	Price
S92	4 x 100 K Lin	£1.00*
S93	4 x 100 K Log	£1.00*
16173	15 Rotary Pots Assorted	40p*
16186	25 Pre-sets Assorted Values	40p*


MULTI-TURN PRE-SETS

S40	3 x 100 K Lin	only 50p*
-----	---------------	-----------

VOLTAGE REGULATORS

Positive	No.	µA	TO	Price
No. MVR7805	µA7805	TO220	85p	
No. MVR7812	µA7812	TO220	85p	

KITS FOR SYNTHESISERS, SOUND EFFECTS

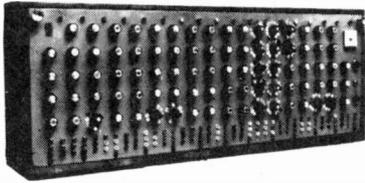

COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

CIRCUIT AND LAYOUT DIAGRAMS are supplied free with all PCBs unless "as published".

PHOTOCOPIES of all P.E. texts for most of the kits are available—prices in our lists.

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

P.E. MINISONIC Mk. 2 SYNTHESIZER

A portable mains-operated Miniature Sound Synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser the functions offered by this design give it great scope and versatility. Consists of 2 log VCOs, VCF, 2 envelope shapers, 2 voltage controlled amps, keyboard hold and control circuits, HF oscillator and detector ring modulator, noise generator, mixer, power supply.

Set of basic component kits £62.23
Set of printed circuit boards £9.94

P.E. SYNTHESIZER (P.E. Feb. 73 to Feb. 74)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. Other circuits in our lists may be used with the Synthesiser to good advantage.

The Main Synthesiser: PSU, 2 linear VCOs, 2 ramp generators, 2 input amps, sample hold, noise generator, reverb amp, ring modulator, peak level circuit, envelope shaper, voltage controlled amp.

Set of basic component kits £83.03
Set of printed circuit boards £13.20

The Synthesiser Keyboard Circuits (can be used without the Main Synthesiser to make an independent musical instrument): 2 logarithmic VCOs, divider, 2 hold circuits, 2 modulation amps, mixer, 2 envelope shapers and PSU.

Set of basic component kits £48.18
Set of printed circuit boards £7.65

GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches £7.59
Alternative component set with panel switches £4.96
Printed circuit board £1.43

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.

Component set for above functions (excl SWs) £7.84
Printed circuit board £1.81
Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce jungle-drum rhythms

Component set (incl PCB) £2.88

PHASING UNIT (P.E. Sept 73)

A simple but effective manually controlled unit for introducing the phasing sound into live or recorded music.

Component set (incl PCB) £2.87

PHASING CONTROL UNIT (P.E. Oct 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl PCB) £4.48

SOPHISTICATED PHASING AND VIBRATO UNIT

A slightly modified version of the circuit published in "Elektron", December 1976, and includes manual and automatic control over the rate of phasing and vibrato.

Component set £17.69
Printed circuit board £2.33

WAH-WAH UNIT (P.E. Apr 76)

The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller.

Component set (incl PCB) £3.55

AUTOWAH UNIT (P.E. Mar 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played.

Component set, PCB, special foot switches £7.27
Component set and PCB, with panel switches £4.83

P.E. JOANNA PLUS ORGAN VOICING

The basic five octave electronic piano (P.E. May/Sept 75 and Sound Design) has switchable alternative voicings for Honky-Tonk, ordinary piano, and Harpsichord or a mixture of any of these three, together with facilities including fast and slow tremolo, loud and soft pedal switching, and sustain pedal switching. The modification retains all the circuitry associated with the piano but in addition provides an organ-voice envelope facility with 5 switchable pitches, variable attack and sustain, phasing and vibrato.

Set of components (excl switches) for PSU, Frequency generator, Pitch and Note Divider, Envelope Shapers, Voicings, and Control circuitries. (Order as KIT 71-5) £109.75
Set of PCBs (Order as PCB SET 71-6) £29.18

SYNTHESIZER TUNING INDICATOR (P.E. July 77)

A simple 4-octave frequency comparator for use with synthesizers and other instruments where the full versatility of the P.E. Tuning Fork is not required.

Component and PCB (but excl sw.) £7.45

GUITAR FREQUENCY DOUBLER (P.E. Aug. 77)

A modified and extended version of the circuit published.

Component set and PCB £4.22

GUITAR SUSTAIN (P.E. Oct 77)

Maintains the natural attack whilst extending note duration.

Component set, PCB and foot switches £4.90
Component set, PCB and panel switches £3.48

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set (incl PCB) £3.72

GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual slider pot £6.88
Component set using dual rotary pot £6.20
Printed circuit board £1.62

FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit.

Component set (incl PCB) £2.05

TREMOLO UNIT

Based upon P.E. "Sound Design" circuit.

Component set (incl PCB) £3.64

TREBLE BOOST UNIT (P.E. Apr. 76)

Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable.

Component set (incl PCB) £2.40

P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic or electronic musical instruments.

Main component set (incl PCB) £15.59
Power supply set (incl PCB) £7.03

CONSTANT DISPLAY FREQUENCY COUNTER (P.E. AUG. 78) FULL DETAILS IN OUR LIST.

P.E. SYNCHRONOME (P.E. Mar. 76)

An accented-beat electronic metronome, providing duple, triple and quadruple times with full control over the beat rate. Can also be used as a simple drum-beat rhythm generator. Includes power supply.

Component set (incl. loudspeaker) £11.82
Printed circuit board £2.04

TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings. All kits include PCBs.

Standard tolerance set of components £2.96
Superior tolerance set of components £3.78
Regulated power supply (will drive 2 sets) £4.69

ENVELOPE SHAPER WITHOUT VCA (P.E. Oct. 75)

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing voltage controlled amplifier.

Component set (incl PCB) £4.66

ENVELOPE SHAPER WITH VCA (P.E. Apr. 76)

This unit has its own voltage controlled amplifier and has full manual control over attack, decay, sustain and release functions.

Component set (incl. PCB) £6.68

TRANSIENT GENERATOR (P.E. Apr. 77)

An envelope shaper, without VCA, having the usual attack, decay, sustain and release functions, and in addition it also provides a "Repeat Effect" enabling a synthesiser to be programmed to imitate such instruments as a mandolin or banjo.

Component set £4.52
Printed circuit board £1.82

WAVEFORM CONVERTER

Slightly modified from a circuit published in "Elektron". Converts a saw-tooth waveform into four different waveforms: sine-wave, mark-space saw-tooth, regular triangle form, and squarewave with an externally variable mark-space ratio.

Component set (incl. PCB but excl. sw/s) £8.19

VOLTAGE CONTROLLED FILTER (P.E. Dec. 74)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesizers.

Component set (incl PCB) (Order as Kit 65-1) £8.22

RING MODULATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesizers.

Component set (incl. PCB) (Order as Kit 59-1) £5.50

NOISE GENERATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesizers.

Component set (incl. PCB) (Order as Kit 60-1) £3.35

SOPHISTICATED POWER SUPPLIES

A wide range of highly stabilised low noise power supply kits is available—details in our lists.

MICROPHONE PRE-AMP (P.E. Apr. 77)

Component set (incl PCB) £3.78

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows.

Component set (incl. PCB) £3.97

DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

Component set (incl. PCB) £4.58

POST AND HANDLING

U.K. orders—under £15 add 25p plus VAT, over £15 add 50p plus VAT. Keyboards £2.00 plus VAT.

Optional insurance for compensation against loss or damage in post, add extra 50p for cover up to £50, £1.00 for £100 cover, £2.00 for £200 cover.

Ire, C.I., B.F.P.O., and other countries are subject to Export postage rates.

DON'T FORGET VAT!

Add 12½% (or current rate if changed) to full total of goods, post and handling. (Does not apply to export orders).

EXPORT ORDERS are welcome, though we advise that a current copy of our list should be obtained before ordering as it also shows Export postage rates. All payments must be cash-with-order, in Sterling and preferably by International Money Order or through an English Bank. To obtain list send 50p.

PHONOSONICS · DEPT. PE68 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH MAIL ORDER AND C.W.O. ONLY SORRY BUT NO CALLERS PLEASE

AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquires for list Europe—send 20p; other countries—send 50p.



KIMBER-ALLEN KEYBOARDS AND CONTACTS

Kimber-Allen Keyboards as required for many published circuits. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves a. C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

- 3 Octave (37 notes) £25.50
- 4 Octave (49 notes) £32.25
- 5 Octave (61 notes) £39.75

Contact Assemblies (gold-clad wire) for use with the above keyboards (1 required for each note):

- Type GJ: Single-pole change-over each 24p
- Type GB: 2 pairs of contacts, each pair normally open each 27p
- Type GC: 3 pairs of contacts, each pair normally open each 36p
- Type GE: 4 pairs of contacts, each pair normally open each 45p
- Type GH: 5 pairs of contacts, each pair normally open each 57p
- Type 4PS: 3 pairs of contacts plus single-pole changeover each 53p

Printed Circuit Boards for use with GJ, GB and 4PS contacts (thus eliminating much wiring) are available. Details in our lists.

RHYTHM GENERATOR

- 15-Rhythm Tempo, Timing and Logic control unit (excl. sw's but incl. PCB) £12.90
- 10-Instrument Effects circuits £13.56
- PCB for Effects circuits £4.25
- Power Supply incl. PCB £12.00

128-NOTE TUNE-PROGRAMMABLE SEQUENCER

(P.E. Nov/Dec 77)

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable. (Please use order codes quoted in brackets.)

- Main Circuit (Nov) excl. sw's (KIT 76-1) £20.80
- Power Supply (KIT 76-3) £6.05
- Trigger Inverter and Alt. Output (KIT 76-2) £1.35
- LCD Counter (KIT 76-4) £2.45
- PCB (as published) for KITS 76-1 & 3 (PCB 76A) £2.81
- PCB for KITS 76-2 & 4 (PCB 76B) £2.54

P.E. STRING ENSEMBLE (PE Mar-July 78)

The new keyboard string-instrument synthesiser.

- Basic component sets:
 - Power Supply (KIT 77-1) £9.22
 - Tone Generator (KIT 77-2) £14.93
 - Diode Gates (KIT 77-3) £19.78
 - Chorus Generator (KIT 77-4) £19.06
 - Voicing System (KIT 77-5) £9.38

Printed Circuit Boards:

- Double-sided PCB for Power Supply, Tone Generator & Diode Gates with most of the Matrix wiring as printed tracking (PCB 77L/R) £18.40
- PCB for Chorus Generator (PCB 77C) £2.65
- PCB for Voicing System (PCB 77D) £2.82

FORMANT SYNTHESISER (Elektr 1977/78)

Very sophisticated music synthesiser for the advanced constructor who puts performance before price. Details in our lists.

DISCOSTROBE (P.E. Nov. 76)

- 4-channel light-show controller giving a choice of sequential, random, or full strobe mode of operation.
 - Basic component set £18.19
 - Printed circuit board £3.45

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie-detector, alphaphone, cardiophone etc.

- Pre-Amp Modula Components set (incl. PCB) £4.22
- Basic Output Circuits—combined component set with PCBs, for alphaphone, cardiophone, frequency meter and visual feed-back lampdriver circuits. £6.59
- Audio Amplifier Module Type PC7 £7.75

10% DISCOUNT VOUCHER (PE68)

TERMS: Correctly coded, C.W.O., U.K. orders over £50 goods value. Valid until end of month on cover of P.E. This voucher must accompany order.

TRANSISTORS

- AC128 26p
- AC176 26p
- BC107 14p
- BC108 14p
- BC109 14p
- BC109C 15p
- BC177 14p
- BC184 12p
- BC187 25p
- BC200 14p
- BC209C 14p
- BC213 15p
- BC214 15p
- BC262 25p
- BC415 16p
- BC478 29p
- BD131 44p
- BD132 54p
- BF244A 24p
- BF245A 24p
- BSY95A 22p
- MD8001 17p
- OC71 20p
- OC72 20p
- RPY58A 48p
- TIS43 50p
- ZTX108 9p
- ZTX301 13p
- ZTX384 16p
- ZTX501 13p
- 2N2219 27p
- 2N2646 50p
- 2N2905 35p
- 2N2905A 36p
- 2N2906 22p
- 2N2907 22p
- 2N3054 66p
- 2N3055 60p
- 2N3702 12p
- 2N3704 12p
- 2N3919 84p
- 2N3820 84p
- 2N3823E 39p
- 2N5459 45p

INTEGRATED CIRCUITS

- 301 8-pin DIL 48p
- 318 8-pin DIL 230p
- 320-15 58p
- 324 14-pin DIL 87p
- 341-15 195p
- 723 TO5 105p
- 723 14-pin DIL 58p
- 726 TO5 980p
- 741 8-pin DIL 32p
- 748 8-pin DIL 63p
- 4024 14-pin DIL 461p
- 4089 14-pin DIL 128p
- 4136 14-pin DIL 18p
- 7805 TO220 205p
- 7806 TO220 205p
- 7808 TO220 205p
- 7812 TO220 205p
- 7815 TO220 205p
- 7818 TO220 205p
- AY10212 16-pin DIL 650p
- AY1672/16 1954p
- CA3046 14-pin DIL 90p
- CA3080 8-pin DIL 82p
- CA3084 14-pin DIL 209p
- M252 16-pin DIL 680p
- MCS340 8-pin DIL 150p
- MCM6810 24-pin DIL 670p
- SG3402N 14-pin DIL 282p
- STK025 595p
- TDA1022 16-pin DIL 872p
- XR2207 14-pin DIL 420p
- ZN425E 16-pin DIL 375p

RST VALVE MAIL ORDER CO.

Climax House
Fallsbrook Road, London SW16 6ED

SPECIAL EXPRESS MAIL ORDER SERVICE

Ep	Ep	Ep	Ep	Ep	Ep
AA119 0-20	BCV71 0-22	*MPSU01 0-32	*ZTX550 0-16	7403 0-20	Ep
AA130 0-13	BCV72 0-17	*MPSU06 0-40	1N914 0-07	7405 0-28	Ep
AA132 0-15	BC211 1-50	*MPSU56 0-45	1N916 0-07	7406 0-55	Ep
AA213 0-25	BD115 0-60	NK7401 2-00	1N4001 0-06	7407 0-55	Ep
AA215 0-31	BD121 1-50	NK7403 1-73	1N4002 0-07	7408 0-28	Ep
AA217 0-25	BD123 1-50	NK7404 1-73	1N4003 0-08	7409 0-28	Ep
AC107 0-75	BD124 1-30	NE555 0-45	1N4004 0-09	7410 0-20	Ep
AC125 0-30	BD131 0-51	OA5 0-75	1N4005 0-13	7411 0-20	Ep
AC126 0-25	BD132 0-54	OA7 0-55	1N4006 0-15	7412 0-28	Ep
AC127 0-25	*BD135 0-35	OA10 0-55	1N4007 0-15	7413 0-45	Ep
AC128 0-25	*BD136 0-36	OA47 0-14	1N4009 0-15	7416 0-40	Ep
AC141 0-20	*BD137 0-37	OA70 0-30	1N4148 0-07	7417 0-40	Ep
AC141K 0-35	*BD138 0-40	OA79 0-30	1N5400 0-14	7420 0-20	Ep
AC142 0-20	BD139 0-43	OA81 0-30	1N5401 0-16	7422 0-25	Ep
AC142K 0-30	BD140 0-47	OA85 0-30	1S44 0-06	7423 0-35	Ep
AC176 0-25	BD144 2-00	OA90 0-65	1S820 0-18	7428 0-37	Ep
AC187 0-25	BD181 1-30	OA91 0-08	1S921 0-08	7427 0-35	Ep
AC188 0-25	BD182 1-48	OA95 0-06	2G301 1-00	7428 0-50	Ep
ACY17 0-85	BD237 0-80	OA200 0-10	2G302 1-00	7430 0-20	Ep
ACY18 0-85	BD238 0-85	OA202 0-11	2G306 1-10	7432 0-36	Ep
ACY19 0-85	BDX10 0-75	OA210 0-75	2A04 0-60	7433 0-37	Ep
ACY20 0-85	BDX32 0-25	OA211 0-75	2N696 0-26	7437 0-42	Ep
ACY21 0-85	BDY20 1-42	OA220 0-65	2N697 0-18	7438 0-37	Ep
ACY39 1-25	BDY60 0-75	OA2201 0-85	2N698 0-30	7440 0-22	Ep
AD149 0-70	BF115 0-39	OA2206 0-85	2N705 0-80	7441AN 0-92	Ep
AD161 0-75	BF152 0-25	OA2207 0-85	2N706 0-12	7442 0-78	Ep
AD162 0-75	BF153 0-25	OC16 1-25	2N790 0-21	7447AN 1-20	Ep
AF106 0-45	BF154 0-25	OC20 2-00	2N930 0-26	7450 0-20	Ep
AF114 0-25	BF159 0-35	OC21 0-75	2N1131 0-26	7451 1-00	Ep
AF115 0-35	BF160 0-30	OC23 2-75	2N1132 0-26	7453 0-20	Ep
AF116 0-25	BF167 0-39	OC24 3-50	2N1302 0-37	7454 0-20	Ep
AF117 0-35	BF173 0-39	OC25 0-90	2N1303 0-37	7460 0-20	Ep
AF139 0-40	BF177 0-38	OC26 0-90	2N1304 0-45	7470 0-35	Ep
AF186 1-50	BF178 0-45	OC28 2-00	2N1305 0-45	7472 0-36	Ep
AF239 0-45	BF179 0-45	OC29 2-00	2N1306 0-50	7473 0-36	Ep
AFZ11 0-75	BF180 0-45	OC35 1-50	2N1307 0-50	7474 0-40	Ep
AFZ12 2-75	BF181 0-45	OC36 1-50	2N1308 0-60	7475 0-59	Ep
AS226 0-45	BF182 0-45	OC41 0-50	2N1309 0-60	7476 0-42	Ep
AS227 0-50	BF183 0-45	OC42 0-50	2N1613 0-33	7480 0-80	Ep
ASZ15 1-25	BF184 0-39	OC43 1-50	2N1671 1-50	7482 0-85	Ep
ASZ16 1-25	BF185 0-37	OC44 0-50	2N1693 0-33	7483 1-00	Ep
ASZ17 1-25	*BF194 0-12	OC45 0-50	2N2147 1-40	7484 1-00	Ep
ASZ20 0-75	*BF195 0-11	OC71 0-45	2N2148 1-65	7486 0-40	Ep
ASZ21 1-50	*BF196 0-13	OC72 0-45	2N2218 0-33	7490 0-52	Ep
AU113 1-70	*BF197 0-14	OC73 1-00	2N2219 0-42	7491AN 0-85	Ep
AU10 1-70	BF200 0-32	OC74 0-75	2N2220 0-35	7492 0-60	Ep
BA145 0-15	*BF224 0-20	OC75 0-60	2N2221 0-22	7493 0-70	Ep
BA148 0-15	*BF244 0-35	OC78 0-60	2N2222 0-26	7494 0-80	Ep
BA154 0-10	BF257 0-37	OC77 1-20	2N2223 2-75	7495 0-80	Ep
BA155 0-12	BF258 0-42	OC81 0-75	2N2368 0-17	7496 0-90	Ep
BA156 0-13	BF259 0-45	OC82 1-00	2N2369A 0-21	7497 3-67	Ep
BAW62 0-05	*BF336 0-50	OC82 0-75	2N2484 0-21	74100 1-75	Ep
BAX13 0-07	BF337 0-53	OC83 0-55	2N2646 0-50	74107 0-45	Ep
BAX16 0-07	BF338 0-53	OC83 0-55	2N2904 0-35	74109 0-57	Ep
BC107 0-12	BF521 2-27	OC122 1-50	2N2905 0-35	74110 0-80	Ep
BC108 0-12	BFS28 1-38	OC123 1-55	2N2906 0-25	74111 0-86	Ep
BC109 0-13	*BFS61 0-25	OC138 2-25	2N2907 0-21	74116 1-89	Ep
*BC113 0-15	*BFS98 0-25	OC140 1-85	*2N2924 0-15	74118 0-95	Ep
*BC114 0-18	BFW10 0-90	OC141 2-25	*2N2925 0-17	74119 2-00	Ep
*BC115 0-19	BFW11 0-75	OC170 0-75	*2N2926 0-13	74120 1-10	Ep
*BC116 0-19	BFX64 0-38	OC171 0-75	*2N2927 0-25	74121 0-45	Ep
*BC117 0-22	BFX85 0-41	OC200 1-00	2N3054 0-50	74122 0-60	Ep
*BC118 0-16	BFX87 0-35	OC201 1-50	2N3055 0-65	74123 1-00	Ep
*BC125 0-18	BFX88 0-32	OC202 1-50	2N3440 0-60	74125 0-80	Ep
*BC126 0-25	BFY50 0-28	OC203 1-75	2N3441 0-60	74126 0-80	Ep
*BC135 0-15	BFY51 0-28	OC204 1-25	2N3442 1-20	74128 0-80	Ep
*BC136 0-19	BFY52 0-28	OC205 1-75	2N3525 0-90	74132 0-80	Ep
*BC137 0-16	BFY64 0-40	OC206 1-75	2N3614 1-20	74136 0-68	Ep
*BC147 0-10	BFY90 1-32	OC207 1-25	*2N3702 0-15	74141 0-85	Ep
*BC148 0-10	BSX19 0-34	OC271 1-25	*2N3703 0-15	74142 3-00	Ep
*BC149 0-13	BSX20 0-34	ORP12 0-83	*2N3704 0-15	74143 3-00	Ep
*BC157 0-12	BSX21 0-32	*R2008B 2-25	*2N3705 0-15	74144 3-00	Ep
*BC158 0-11	BT106 0-25	*R2009 2-25	*2N3706 0-14	74145 1-00	Ep
*BC159 0-13	BTY79/400R 3-19	*R210B 2-25	*2N3707 0-18	74147 2-45	Ep
*BC167 0-13	*BU205 2-25	T1C44 0-36	*2N3708 0-14	74148 2-00	Ep
*BC170 0-16	*BU206 2-25	T1C226D 1-30	*2N3709 0-15	74150 1-75	Ep
*BC171 0-14	*BU208 2-50	T1L209 0-25	*2N3710 0-14	74151 0-90	Ep
*BC172 0-13	BY100 0-45	*T1P29A 0-80	*2N3711 0-15	74154 2-00	Ep
*BC173 0-15	BY126 0-17	*T1P30A 0-80	2N3771 1-60	74155 0-90	Ep
BC174 0-18	BY127 0-15	*T1P31A 0-80	2N3772 1-70	74156 0-90	Ep
BC178 0-18	BX261 0-20	T1P32A 0-75	2N3773 2-65	74157 0-90	Ep
BC179 0-20	Series	T1P33A 1-00	*2N3819 0-36	74159 2-50	Ep
*BC182 0-11	BZY88 0-13	T1P34A 1-20	*2N3820 0-46	74170 2-80	Ep
*BC183 0-11	Series	T1P41A 0-70	*2N3823 0-60	74172 5-00	Ep
*BC184 0-12	CRS1/05 0-45	T1P42A 0-80	2N3866 1-00	74173 1-75	Ep
*BC212 0-14	CRS1/40 0-60	T1P2955 1-00	*2N3904 0-21	74174 1-57	Ep
*BC213 0-14	CRS3/05 0-45	T1P3055 0-50	*2N3905 0-22	74175 1-00	Ep
*BC214 0-17	CRS3/40 0-75	*T1S43 0-35	*2N3906 0-22	74176 1-10	Ep
*BC237 0-17	CRS3/60 0-90	*ZS140 0-25	*2N4058 0-20	74178 1-85	Ep
*BC238 0-12	GEX66 1-90				

ALL PRICES INCLUDE VAT & P/P CATALOGUE 40p
MIN ORDER £2.00

THE COMPONENT CENTRE

7 LANGLEY ROAD - WATFORD - HERTS - WD1 3PS
Phone Watford 45335 Callers welcome 9.30-5.30 Mon-Sat. EC. Wed.

C.-MOS		T.T.L.		D.I.L. SOCKETS		LOUDSPEAKERS	
4000	18p	7400	13p	8 pin	10p	16 pin	14p
4001	18p	7401	15p	14 pin	13p	28 pin	30p
4002	18p	7402	16p				
4006	110p	7403	17p				
4007	20p	7404	22p				
4008	97p	7405	22p	TIL209	Red		
4009	62p	7406	44p	TIL209	Yellow		
4010	62p	7407	44p	TIL209	Green		
4012	20p	7408	22p	-2	Red		
4013	59p	7410	16p	-2	Yellow		
4014	108p	7411	24p	-2	Green		
4015	97p	7412	24p				
4016	59p	7413	38p				
4017	99p	7414	66p	Red			
4018	99p	7416	33p	Green			
4019	65p	7417	33p	Amber			
4020	119p	7420	18p	Neon Bulb			
4021	99p	7425	28p				
4022	94p	7427	28p				
4023	21p	7430	20p				
4024	83p	7432	28p				
4025	20p	7437	29p				
4026	190p	7441	74p				
4027	59p	7442	74p				
4028	96p	7445	123p				
4029	118p	7446	123p				
4030	62p	7475	102p				
4031	249p	7448	130p				
4032	108p	7454	19p				
4033	157p	7470	39p				
4035	130p	7472	28p				
4041	87p	7473	39p				
4042	85p	7474	33p				
4043	99p	7477	48p				
4044	96p	7476	40p				
4045	150p	7480	46p				
4046	131p	7482	91p				
4047	95p	7483	90p				
4049	65p	7485	106p				
4050	65p	7486	36p				
4054	120p	7489	399p				
4055	140p	7490	57p				
4056	140p	7491	82p				
4060	117p	7492	57p				
4066	70p	7493	57p				
4067	410p	7494	83p				
4068	24p	7495	70p				
4069	22p	7496	83p				
4070	60p	74100	130p				
4071	22p	74107	36p				
4072	23p	74118	125p				
4076	167p	74121	38p				
4077	65p	74122	55p				
4078	24p	74123	103p				
4081	23p	74144	345p				
4082	23p	74145	83p				
4086	24p	74153	62p				
4501	19p	74154	138p				
4502	130p	74155	115p				
4507	59p	74174	132p				
4510	132p	74175	79p				
4516	132p	74180	85p				
4518	114p	74181	295p				
4519	60p	74192	131p				
4532	138p	74193	131p				
4539	119p	74198	185p				

TRANSISTORS		DIODES		LINEAR I.C.'s	
AC126	21p	BC547	14p	MJ2955	99p
AC127	21p	BC548	14p	MJE340	64p
AC128	21p	BC549	14p	MJE2955	99p
AC176	21p	BC567	14p	MJE3055	68p
AC187	23p	BCY34	74p	OC28	108p
AC188	23p	BCY70	17p	OC35	108p
AD149	65p	BCY71	20p	OC71	19p
AD161	50p	BD115	17p	OC84	46p
AF114	30p	BD124	97p	TIP29	50p
AF115	27p	BD131	47p	TIP30	52p
AF116	25p	BD132	47p	TIP31	59p
AF117	23p	BD135	43p	TIP32	59p
AF118	30p	BD136	50p	TIP33	107p
AF124	32p	BD137	50p	TIP34	60p
AF125	32p	BD138	51p	TIP35	253p
AF126	32p	BD139	51p	TIP36	389p
AF139	40p	BD140	52p	TIP41	59p
AF239	45p	BF173	30p	TIP42	59p
BC107	9p	BF179	37p	TIP2955	126p
BC108	9p	BF180	37p	TIP3055	64p
BC109	9p	BF181	37p	ZTX108	12p
BC147	10p	BF182	37p	ZTX300	12p
BC148	10p	BF183	37p	ZTX500	12p
BC149	10p	BF194	13p	2N1305	25p
BC157	11p	BF195	13p	2N1306	39p
BC158	11p	BF196	13p	2N1711	21p
BC159	11p	BF197	16p	2N2219	21p
BC168	12p	BF200	36p	2N2250	25p
BC169	12p	BF224	16p	2N2905	26p
BC171	12p	BF257	37p	2N2906	20p
BC172	12p	BF258	40p	2N2926G	99p
BC173	12p	BF259	44p	2N2926R	99p
BC177	16p	BF339	30p	2N2955	99p
BC178	16p	BF340	34p	2N3053	17p
BC179	16p	BF330	38p	2N3054	54p
BC182L	13p	BFX84	27p	2N3055	54p
BC183L	11p	BFX85	29p	2N3702	10p
BC184L	13p	BFX86	31p	2N703	10p
BC212L	13p	BFX87	31p	2N3704	12p
BC213L	13p	BFX88	29p	2N3705	12p
BC214L	14p	BFY50	17p	2N3706	12p
BC238	14p	BFY51	17p	2A100V	36p
BC303	30p	BSX20	21p	2A200V	38p
BC328	15p	BU105	191p	2A400V	40p
BC338	15p	BU208	299p	2A600V	42p

Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, PEK9

P.O.Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____ (Block caps please)


Our new 1978 catalogue lists a whole range of metal cases to house all your projects. And we've got circuit boards, accessories, module systems, and plastic boxes - everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956

EXCELLENT VALUE
ONLY **£10.95**

Understanding Digital Electronics

New teach-yourself courses

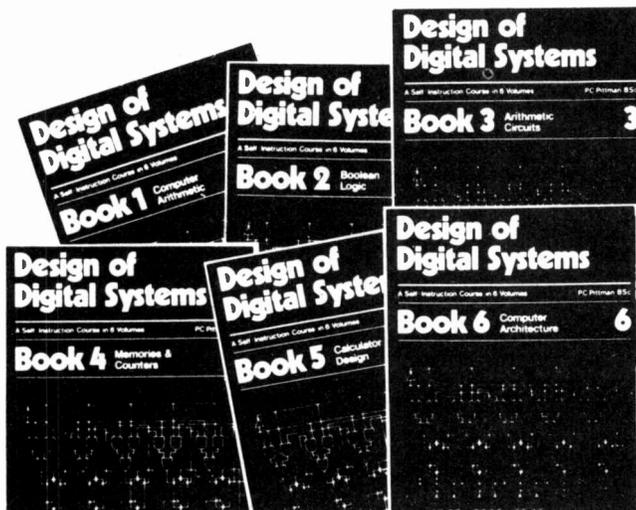

Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes – each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers.

The contents of Design of Digital Systems include:

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.

Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.

Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.



Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes – each A4 size – and serves as an introduction to the subject of digital electronics. Everyone can learn from it – designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

CAMBRIDGE LEARNING ENTERPRISES, Unit 20, Rivermill Site, FREEPOST, ST. IVES, HUNTINGDON, CAMBS. PE17 4BR, ENGLAND. TELEPHONE ST. IVES (0480) 67446. PROPRIETORS: DRAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES. Giro Ac. No. 278 9159. REGD. IN ENGLAND NO. 1328762

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be calling people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

The six volumes of Design of Digital Systems cost only: **£8.10** +90p post & packing

And the four volumes of Digital Computer Logic and Electronics cost only: **£4.60** +90p post & packing

But if you buy both courses, the total cost is only: **£12** +£1 post & packing

Price includes surface mail anywhere in the world: Airmail extra.

Flow Charts & Algorithms

HELP YOU PRESENT:

safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

THE ALGORITHM WRITER'S GUIDE explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.

£2.95 + 45p post and packing by surface mail anywhere in the world. Airmail extra.

GUARANTEE

If you are not entirely satisfied your money will be refunded.

Cambridge Learning Enterprises, Unit 20, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR, England.

Please send me the following books:

.....sets Digital Computer Logic & Electronics' @ £5.50, p & p included
sets Design of Digital Systems @ £9.00, p & p included
 Combined sets @ £13.00, p & p included
 The Algorithm Writer's guide @ £3.40, p & p included

Name

Address

I enclose a *cheque/PO payable to Cambridge Learning Enterprises for £.....

Please charge my *Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number.....

Signature..... *delete as appropriate.

Telephone orders from credit card holders accepted on 0480-67446 (Ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank. PE 20

RELAYS SIEMENS, PLESSEY, etc. MINIATURE RELAYS

RELAYS. WIDE RANGE OF A.C. and D.C. RELAYS AVAILABLE from stock, phone or write in your enquiries.

FT3 NEON FLASH TUBE

High intensity multi turn, high voltage, neon glow discharge flash tube. Design for ignition timing, etc. £1.50. P. & P. 25p (£1.80 inc. VAT). 3 for £3. P. & P. 50p (£3.78 inc. VAT & P.).



NI-CAD BATTERY

35AH 1.2V Metal £7.56
Height (mm) 219
Width (mm) 75
Length (mm) 29
Post 50p per unit

WHY PAY MORE?

MULTI RANGE METER TYPE MF15A a.c. d.c. volts 10 - 50, 250, 500, 1000. Ma 0-5, 0-10, 0-100. Sensitivity 2000V. 24 range, diameter 133 by 93 by 46mm including test leads. Price £7.00 plus 50p P. & P. (£8.10 inc. VAT & P.).




METERS NEW—90mm Diameter

Type: 65C5 d.c. Mc. 0-2, 0-5, 0-20, 0-50, 0-15V d.c. 0-30V d.c. Type: 62T2 a.c. M/10-1A, 0-50 amp. 0-15V, 0-30V. Type: 65L5 R/mc. 0-30V a.c. All at £3.50 each. P. & P. 50p (£4.32 each inc. VAT & P.). Type: 65C5 d.c. 0-100 amp. £5.00 P. & P. 50p (£5.94 inc. VAT).



NEW HEAVY DUTY SOLENOID. mfg.

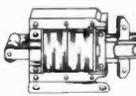by Magnetic Devices. 240V a.c. operation approx. 10lbs pull at 1.25in. Price £4.00 P. & P. 50p (£4.96 inc. VAT & P.). Similar in appearance to illustration. Approx. 1 1/2lb pull. Size of feet 1 1/2 x 1 1/2in. Price £1.00 P. & P. 25p.



MINIATURE UNISELECTOR

12 volt 11-watt, 4 bank (3 non-bridging, 1 homing), £2.50. P. & P. 35p (£3.08 inc. VAT & P.).



600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600W of lighting except fluorescent at mains voltage. Complete with simple instructions. Price £1.95, post 25p (£4.33 inc. VAT & P.). 1,000 watt model £5.60, post 25p (£6.32 inc. VAT & P.). 2,000 watt model £9.75, post 40p (£10.96 inc. VAT & P.).



MICRO SWITCHES

New Manufacturers Surplus

Sub min Honeywell roller m/s type 3115m 906t. 10 for £2.50 post paid.
LEVER OPERATED 20 amp. C/O. Mfg. by Unimax USA. 10 for £4. P. & P. 50p (min. order 10) (£4.86 inc. VAT).
D.P. C/O lever switch mfg. by Cherry Co. USA. Precious metal low resistance contacts. 10 for £2.25 P. & P. 30p. Total inc. VAT £3.02 (min. 10).
Sub min lever m/s switch type MML 46 10 for £2.50.



24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25lb pull 1 inch travel. Two x approx. 1lb pull 1/2 inch travel. 6 x approx. 4oz pull 1/4 inch travel. One 24V d.c. 1 heavy duty single make relay. Price £3. Post £1 (£4.32 inc. VAT & P.). ABSOLUTE BARGAIN.

VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced totally enclosed 9in rotor with max air delivery of 1.5 cubic metres per min. Max static pressure 600mm W.G. Suction or blow from 2 side-by-side 37mm I.D. circular apertures fitted to base of unit. Powerful continuously rated 115V a.c. motor mounted on alloy base with fixing facilities. Dimensions length 22cm x width 25cm x height 25cm. These units are ex equipment but have had minimum use. Fully tested prior to despatch. Price £12 - £150 P. & P. (E14.58 inc. VAT & P.). Suitable transformer for 230/240V a.c. E6 - E1 P & P. (£7.56 inc. VAT & P.).



CENTRIFUGAL BLOWER

Smith type FFB
1906 022 220/240V A.C. Aperture 10 x 43cm overall size 16 x 14cm. Price £3.75 P. & P. 75p (£4.86). Other types available on request.



INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction suitable for bench or field work. constant speed clutch. Size L 8in. W 4in. H 6in. weight 6lb. 500V, 500 megohms, £49. Post 80p (£53.78 inc. VAT & P.). 1,000V, 1,000MΩ, £55. Post 80p (£60.26 inc. VAT & P.). SAE for leaflet



All Mail Orders—Callers—Ample Parking

Dept. PE, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560

Showroom open Mon.-Fri.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V All Types SHROUDED TYPE

200 watt (1 amp) inc. a.c. voltmeter £14.50
0.5 KVA (2 1/2 amp) (MAX) £17.00
1 KVA (5 amp) (MAX) £22.50
2 KVA (10 amp) (MAX) £37.00
3 KVA (15 amp) (MAX) £45.50
4 KVA (20 amp) (MAX) £70.00
CARRIAGE AND PACKING EXTRA



LT TRANSFORMERS

0-10-15V at 3 amp (ex new equip) £2.50 P. & P. 50p (£3.24 inc. VAT)
13-0-13V at 1 amp £2.50 P. & P. 50p (£3.24 inc. VAT)
25-0-25V at 2 1/2 amp £4.50 P. & P. 75p (£5.67 inc. VAT & P.)
0-4V/6V/24V/32V at 12 amp £15.00 P. & P. £1.50 (£17.82 inc. VAT & P.)
0-6V/12V at 20 amp £13.50 P. & P. £1.50 (inc. VAT £16.20)
0-12V at 20 amp or 0-24V at 10 amp £12.00 P. & P. £1.50 (£14.58 inc. VAT & P.)
0-6V/12V at 10 amp £8.25 P. & P. £1.25 (inc. VAT £10.26)
0-6V/12V/17V/18V/20V at 20 amp £16.50 P. & P. £1.50 (£19.44 inc. VAT & P.)
0-10V/17V/18V at 10 amp £10.00 P. & P. £1.40 (inc. VAT £12.31)
0-6V/12V at 20 amp £11.85 P. & P. £1.00 (£13.88 inc. VAT & P.)
Other types in stock, phone for enquiries or send sae for leaflet.


STROBE! STROBE! STROBE!

HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. Price £18. Post £1 (£20.56 inc. VAT & P.). Specially designed case and reflector for Hy-Light £8.25. Post £1 (£9.99 inc. VAT & P.).

XENON FLASHGUN TUBES

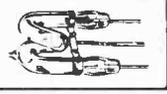Range available from stock
S A E for details



WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S A E (foolscap) for details

Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding heavy duty brush assembly, continuously rated.
25 WATT 10/25/50/100/150/250/500/1kΩ/1.5kΩ £2.40. Post 20p (£2.81 inc. VAT & P.).
50 WATT 100/250/5kΩ £2.90. Post 25p (£3.40 inc. VAT & P.).
100 WATT 1/5/10/25/50/100/250/500/1kΩ/2.5kΩ/3.5kΩ £5.90 p & p 35p (£6.75 inc. VAT).
Black, Silver, Skirted knob calibrated in Nos. 1-9 1/2in. dia. brass bush. Ideal for above Rheostats 24p each.



RESET CENTER

230V a.c. 3 digits mfg. Veeder Root Type LL 144-1 £1.75. P. & P. 25p (£2.16 inc. VAT & P.).
7 Fg 24V d.c. non set £1.50. P. & P. 25p (£1.89 inc. VAT & P.).
6 fig. 24V d.c. resettable £3. P. & P. 25p (£3.51 inc. VAT & P.).
New Manufacturers Surplus



230V a.c. FAN ASSEMBLY.

Powerful continuously rated a.c. motor complete with 5 blade 6 1/2in. Aluminium fan. Price £3.00. P. & P. 65p (£3.94).
New Manufacturers Surplus



CITENCO 19 RPM

FHP motor type C 7333/15 220/240V a.c. 19 r.p.m. reversible motor. torque 14.5 kg. gear ratio 144-1. Brand new incl. capacitors. our price £14.25. P. & P. £1.25 (£16.20 inc. VAT & P.).
New Manufacturers Surplus



PARVALUX 230/250V a.c. MOTOR

500 rpm, 3 1/2in. 2 right angled spindles £11.00 P. & P. £1.00 (£12.96 inc. VAT & P.).

GEARED MOTORS

100 r.p.m. 115lb. in. 110V. 50Hz. 2.8A single phase split capacitor motor. Immense power. Continuously rated. Totally enclosed. Fan cooled in-line gearbox. Length 250mm. Dia. 135mm. Spindle dia. 15 5mm. Length 145mm. Ex-equipment tested £12. Post £1.50 (£14.58 inc. VAT & P.). Suitable transformer 230/240V operation £8. Post 75p (£9.45 inc. VAT & P.).



GEARED MOTORS

New Manufacturers Surplus

28 r.p.m. 20 lbs inch
115V a.c. Reversible motor.
71 r.p.m. 10 lbs inch
115V a.c. Reversible motor.



The above precision made USA motor is offered in 'as new' condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. Input. Price, either type £5.25. Post 75p (£5.76 inc. VAT & P.) or less transformer £3.75. Post 65p (£4.75 inc. VAT & P.). Both types similar to above drawing. Price either type £4.75 p&p 75p (£5.94 inc. VAT + p&p). Supplied complete with transformer for 240V a.c. operation £7.25 p&p £1.00 (£8.91 inc. VAT + p&p).

Crouzet 230/240V. AC 2RPM synchronous geared motor. Brand new £2.90 p&p 30p. (£3.45 inc. VAT) (quantity discount available).

FRACMO GEARED MOTOR

56 r.p.m., 50lb. in. 240V a.c. 50Hz. 0.7 amp. shaft length 35mm. dia. 16mm. weight 6 kilos 600 grammes. Price £15.00 P. & P. £1.50 (£17.82).
New Manufacturers Surplus



PARVALUX GEARED MOTOR

230/240V A.C. 30 rpm 50lbs inch. Price £15.00 P. & P. £1.00 (£17.82 inc. VAT).
New Manufacturers Surplus



COMPRESSOR

Precision built by Emerson USA. Horizontally opposed twin head diaphragm type producing 20lbs. Plus P.S.I. per head. 3.5 plus C.F.M. Output virtually pulse free. Powered by 110V A.C. motor size 30x23x150mm. weight 7 kilos. Price £20 p&p £2.00 (inc. VAT £23.76).
Suitable transformer for 230/240V A.C. £8.00 p&p £1.00 (inc. VAT £9.72). New Manufacturers Surplus



A.E.G. WATER PUMP

200/240V a.c. motor. 2,850 r.p.m. 480W approx. 1/2 h.p. Driving a centrifugal pump with 1 1/2in. inlet and outlet delivering approx. 40 gallons per min. at 10in. head. Ideal for pumping or circulating any non-corrosive light viscosity liquid. Dozens of uses in industrial labs., etc. Note this pump is not self-priming. Price £15. Post 75p (£17.01 inc. VAT & P.).



PROGRAMME TIMERS

12 cam model £7.50. Post 60p (£8.75 inc. VAT & P.). Also available for 50V operation. Price as above.
New Manufacturers Surplus



Time Switch

Venner Type ERD Time switch 200/250V a.c. 30 amp contact 2 on/2 off every 24 hrs. at any manually pre-set time. 36 hour Spring Reserve and day omitting device. Built to highest Electricity Board specification. Price £7.75. P. & P. 75p (£9.18).
Reconditioned and tested



SANGAMO WESTON TIME SWITCH


Type S251 200/250V. a.c. 2 on/2 off every 24 hours. 20 amps contacts with override switch dia. 4 x 3 price £6.50 F & P. 50p inc. VAT £7.56. Also available with Solar dial. Reconditioned and tested

FRACMO MOTOR

1400 rpm H.P. 1/30 continuously rated 115V a.c., supplied complete with transformer for 230/240V a.c. op. Complete with anti vibration cradle mounting £10.00 P. & P. £1.00 (£11.88 inc. VAT & P.).

ROTARY VACUUM AIR COMPRESSOR & PUMP

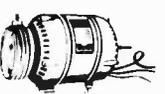Carbon vane oil free vacuum pump and compressor. Approx. 20 inch vacuum, 10 PSI at 79 CFM. Powered by 110V a.c. 1.8 amp. Parvalux motor fitted with additional shaft at rear, suitable light loads. inc. capacitor £14.00 p&p £1.50 (£16.74 inc. VAT + p&p). Suitable transformer for 230/240V a.c. operation £5.00 p&p £1.00 (£6.48 inc. VAT + p&p) (New manufacturers surplus).



Yet another outstanding offer.

New IMFD 600V Dubilier wire ended capacitors. 10 for £1.50 p&p 50p. (£2.16 inc. VAT + p&p) (Min 10)

RELAY

Diamond H heavy duty A.C. relay 230/240V a.c. two C/O contacts 25 amps res. at 250 a.c. £2.50 p&p 50p. (£3.24 inc. VAT + p&p) Special base 50p.

Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

VAT
AT CURRENT RATE MUST BE
ADDED TO ALL ORDERS FOR THE
TOTAL VALUE OF GOODS
INCLUDING POSTAGE UNLESS
OTHERWISE STATED

SERVICE TRADING CO.
ACCOUNT CUSTOMERS MIN. ORDER £10.00

ANALOGUE?

IN THIS fast moving world of digital technology where even the Government discusses 64K RAM (though one wonders just how many in such circles really understand what it is they are considering pouring our money into), it is all too easy to overlook and even dispense with other modes of operation. It is not infrequent that we see highly complex logic designs for equipment that could more easily be realised with simple analogue techniques.

Wonderful as digital technology is, it must never become such an overwhelming part of our lives that we overlook other more suitable circuitry. It is all too easy for any designer—amateur or professional—to become so deeply immersed in one small discipline that others are not even considered.

Most of us have seen and tried such digital games as "moon landing". All that technology, hardware and software to provide a game with a few simple variables. It really is an unnecessary use of a digital system and can be easily achieved with analogue techniques. Surely a case of technology for its own sake.

HISTORY!

It may be something of an eye opener to many readers to see an analogue computer on the front cover of P.E. "Surely these ancient devices have all but disappeared in the face of microprocessors? So what is a leading highly technical magazine doing with this—showing us some history?"

Well, if your feelings are such, then perhaps you are one of those designers who is getting out of touch with the real world and too deeply involved in digital technology! Our analogue computer is a serious instrument for the student and engineer.

It is now more than ten years since PEAC (P.E. Analogue Computer) appeared in our pages. Part of the introduction to that series stated: "A useful tool which is capable of solving complicated problems at high speed. Can be used as a model to simulate mechanical systems." Those statements are equally true of our latest design and such a system has many advantages over digital circuitry when used for certain problems. So don't overlook or dismiss the design, it could be very useful to you.

DIGITAL

What goes before does not mean we will be turning away from the microprocessor—far from it—we have some very exciting projects planned that will interest those at all levels of knowledge and interest in micros. You will find mention of what some might term a "one chip VDU" on our carryover page (p. 975). This, for those that want it, is digital technology that's bang up to date.

Over the coming months we will also be catering for those that want to build a basic microprocessor system and learn how to start programming it.

GENERAL

We know many readers will not be interested in these "computer" areas but a look at the contents page of this issue will assure them that they are not being overlooked. The variety of areas covered within our pages is vast and we hope you will find something of interest in each issue.

We give a glimpse into the future with our wave power feature and wonder just how long it will be before some of our projects are supplied from such systems!

Mike Kenward

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

Alan Turpin PRODUCTION EDITOR

David Shortland TECH. SUB EDITOR

Jack Pountney ART EDITOR

Keith Woodruff SENIOR ARTIST

Isabelle Greenaway TECH. ILLUSTRATOR

Judith Kerley SECRETARY

Editorial Offices:

Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: Editorial Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone.

Advertising Offices:

King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Phone: Advertisements 01-261 5000
Telex: 915748 MAGDIV-G

Make Up and Copy Dept.

Phone: 01-261 6601

ADVERTISEMENT MANAGER

D. W. B. Tilleard

P. J. Mew REPRESENTATIVE

C. R. Brown CLASSIFIED MANAGER

Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perry Mount Road, Haywards Heath, West Sussex RH16 3DH.

Back Numbers and Binders

Copies of most of our recent issues are available from: Post Sales Department, IPC

Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 65p each including Inland/Overseas p & p.


Binders for PE are available from the same address at £2.85 each to UK addresses, £3.45 overseas, including postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Cheques and postal orders should be

made payable to IPC Magazines Limited.

Letters

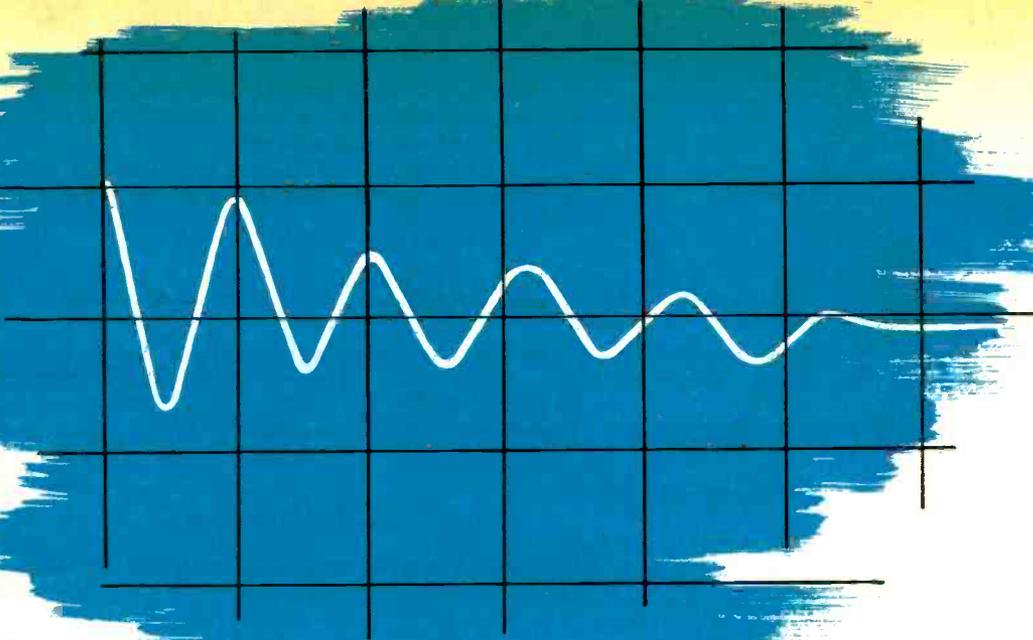Queries regarding articles published in PE should be addressed to the Editor, at the Editorial Offices, and a stamped, addressed envelope enclosed. We cannot undertake to answer questions regarding other items, nor to answer technical queries over the telephone.



- ★ Ten Amplifiers
- ★ Eight Coefficient Multipliers
- ★ Two Four Quadrant Multipliers
- ★ Over Voltage Indicators on all Amplifiers
- ★ Provision for "Initial Conditions"
- ★ Offset Null on all Amplifiers

ANALOGUE COMPUTER

P. J. KRONIS B.Sc.

PART 1

THE analogue computer is a piece of equipment designed to satisfy mathematical equations, usually differential. Mathematics in general and differential equations in particular are the subjects of an exact science which describes the behaviour of physical systems.

Because computers cannot tell us how to solve a physical problem a mathematical model of the problem has first to be formed by the programmer. This is where computers are useful because the formation of the mathematical model is usually easier than the solution of the equations especially as differential equations can be particularly difficult to solve manually and some virtually impossible.

The analogue computer works by handling continuously changing variables using electrical potential or voltage as the analogue, in contrast to the digital computer which manipulates discrete pulses to obtain the solution to a problem.

Fig. 1.1 was produced by the analogue computer to be described here and it will be explained in this article how to program the computer to produce these interesting and artistic designs.

The analogue computer can be used in engineering to simulate the behaviour of complex systems before they are constructed, the behaviour of these complex systems can be thoroughly studied and various parameters changed simply by turning a potentiometer until the system functions in a satisfactory manner. This procedure allows considerable savings both in the cost and time of development.

Analogue circuits similar to those used in analogue computers are employed in a variety of applications, i.e. automatic control in industry, aircraft and spacecraft.

One of the examples to be given in this article will be a simple program to simulate the vertical take-off of an aircraft like the Harrier jump jet, and also a spacecraft moonlanding.

MATHEMATICAL OPERATIONS AND CIRCUITS

The advances in miniaturisation have enabled more computing power to be packed into a smaller space and it is these advances that have helped the digital computer on its way towards becoming a household object. In the analogue



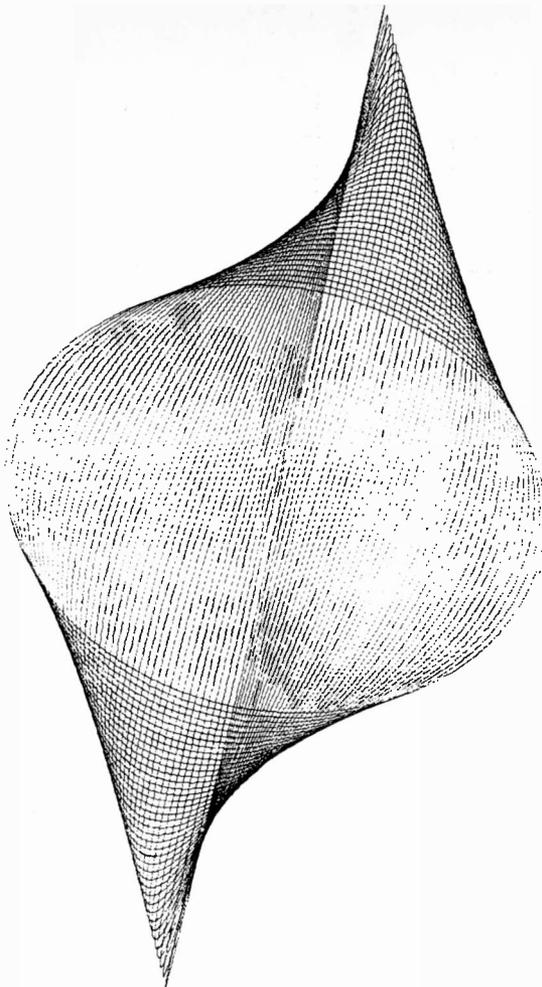


Fig. 1.1. A typical lissajous figure produced using the Analogue Computer and an X-Y plotter

field the high gain d.c. amplifier or operational amplifier which is the main element of the analogue computer, has also come a long way since its inception. It was originally designed for use in computers but has since found many applications in other fields. This large market for other applications has reduced the cost of such devices to very low levels. Of the numerous op-amp i.c.s available on the market the 741 was chosen for the prototype because it is both cheap and easy to handle. More advanced op-amps are available albeit at a higher price and constructors can experiment with these if they wish.

By connecting an op-amp to input and feedback components certain mathematical operations can be performed; addition (and subtraction) integration, and multiplication by a constant. Differentiation can also be performed but is generally avoided due to problems associated with noise generated by components. Multiplication by constant coefficients between zero and one is also performed using potentiometers with some special circuits being employed to enable the multiplication of two variable voltages.

THE ADDITION CIRCUIT

It is possible to add various voltages by means of a resistance network with the output voltage being proportional to the sum of the input voltages. The serious drawback of this method is that this is only true if the load resistance remains constant.

This would be an unacceptable constraint since the output voltage may be applied to other points in the circuit which have different values of load resistance.

To overcome this difficulty a high gain d.c. amplifier is employed in the feedback circuit as shown in Fig. 1.2.

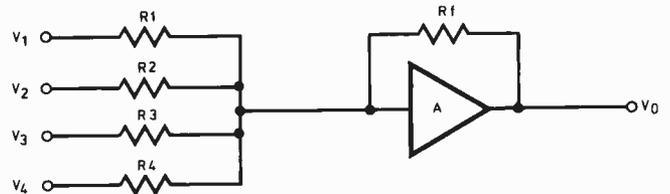


Fig. 1.2. "Addition" circuit

If a voltage V_1 is applied via R_1 to the summing junction the output voltage V_0 is equal to

$$-V_1 \frac{R_f}{R_1}$$

The polarity of the input voltage is also changed by the operational amplifier.

With the output voltage now independent of the load resistance each input voltage is factored by the same ratio of feedback resistance to input resistance.

$$V_o = - \left(V_1 \frac{R_f}{R_1} + V_2 \frac{R_f}{R_2} + V_3 \frac{R_f}{R_3} + V_4 \frac{R_f}{R_4} \right)$$

THE INTEGRATOR CIRCUIT

As with the addition circuit integration can be achieved by using an R.C. network but this method also suffers from a number of serious drawbacks.

The circuit in Fig. 1.3 shows how an operational amplifier can be used to perform integration.

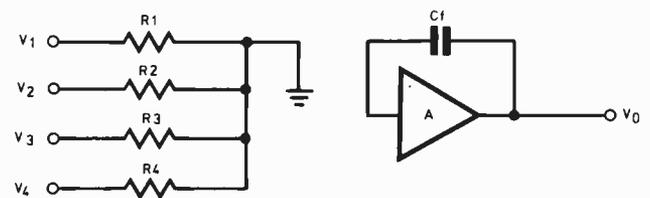


Fig. 1.3. "Integrator" circuit

With a capacitor connected in the feedback loop, and if the open loop gain of the amplifier is very large, the output voltage is given by

$$V_o = - \left(\frac{1}{R_1 C_f} \int V_1 dt + \frac{1}{R_2 C_f} \int V_2 dt + \frac{1}{R_3 C_f} \int V_3 dt + \frac{1}{R_4 C_f} \int V_4 dt \right)$$

The output voltage is the sum of the integrals, with respect to the time the voltage is applied to the inputs,

factored by $-\frac{1}{R_{in} C_f}$.

By choosing suitable values of R_{in} and C_f the factors can be given the required values.

THE COEFFICIENT MULTIPLIER

The coefficient multiplier is used to multiply a voltage by a constant between zero and one. This is the only mathematical operation that is usually performed without the use of an op-amp. A potentiometer is connected as shown in Fig. 1.4.

At one extreme of the slider's travel $V_o = V_{in}$, i.e. V_{in} is multiplied by 1, whereas at the other extreme $V_o = 0$ i.e. V_{in} is multiplied by zero.

Any intermediate value can be set up by moving the slider. The dial of the potentiometer can be calibrated to facilitate this. However, it is not normal practice to set up a value on

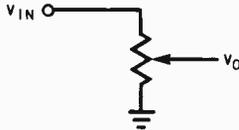


Fig. 1.4. Coefficient Multiplier

the dial of the potentiometer because this circuit also suffers from the effects of load resistance.

An op-amp employed as a voltage follower could be connected as a buffer to isolate the effects of the load resistance, but this is an unnecessary addition because the problem can be overcome by measuring the output of the potentiometer using a voltmeter, after the circuit has been connected, i.e. in the presence of the real load to be applied in the particular problem being examined. The value desired is then set by adjusting the potentiometer and ignoring the graduations on the dial.

The circuits described so far form the fundamental building blocks of the analogue computer. Various special circuits have been developed over the years for other operations. The most important of which is the formation of the product of two variables. One of the early methods developed was the cumbersome servo multiplier. This involved the control of potentiometers using servos. Nowadays this operation can be achieved electronically using four-quadrant multiplier integrated circuits.

INTEGRATION

Addition, subtraction and multiplication are concepts that are easily understood; integration, however, is not so easily grasped by the non-mathematically minded and so a simple explanation may be useful at this point.

If for example a motor car is cruising on a motorway at 50 miles per hour this can be represented by a graph of speed against time (Fig. 1.5). Since the speed is constant the distance travelled will increase by equal amounts in equal

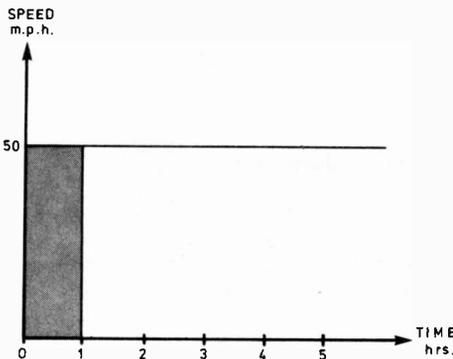


Fig. 1.5. Graph of speed against time

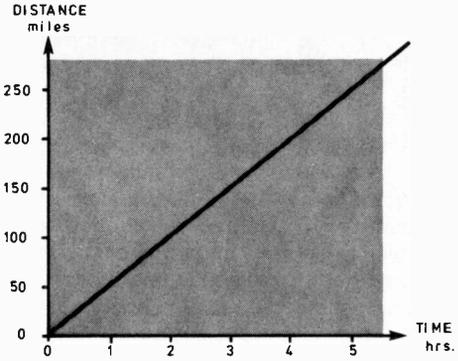


Fig. 1.6. Graph of distance against time

time intervals. These distances are shown plotted on a graph of distance against time for intervals of one hour (Fig. 1.6).

It can be seen from Fig. 1.5 that the distance travelled during a period of time is represented by the area shown shaded on the velocity-time graph. (Velocity \times time representing the height \times base of the shaded rectangle.) Now if the results of all these intervals were added up, the result would be the total distance travelled in a period of time.

The mathematical way of saying this is that the distance travelled is the integral of velocity with respect to time between two time limits. In the above example since the speed was constant one could have arrived at the required result by multiplying the total period of 5 hours say, by the velocity of 50 m.p.h. to obtain 250 miles travelled, without going into the trivial process of integrating, by considering small time intervals.

In reality the velocity may vary as shown in Fig. 1.7, i.e. in a random manner. To obtain the required result then, the velocity would have to be integrated over the required period of time by considering small time intervals. This is how a digital computer would be programmed to solve the problem. The accuracy in that case would depend on how small the time intervals were made. This is left to the discretion of the programmer. If the intervals were made too big, then the result would be inaccurate. On the other hand too small a time interval would mean that the computer would take longer to solve the problem and involve the programmer in unnecessary expense. The analogue computer programmer need not worry about this since the computer integrates continuously, i.e. it deals with

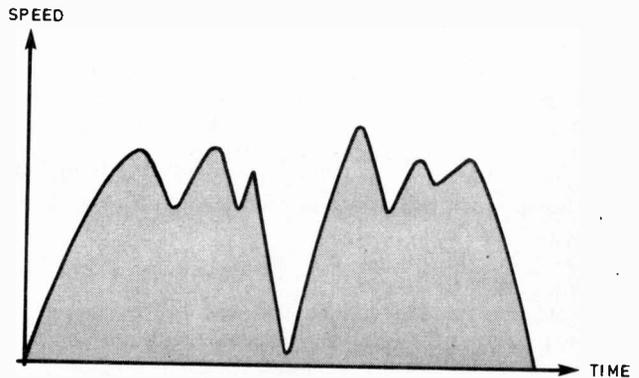


Fig. 1.7. Graph showing variations in velocity

infinitesimally small time intervals and does this at high speed.

Each of the circuits that have been described so far constitutes a computing element. When the computer is programmed to solve a problem, systems of equations can be set up by connecting together combinations of computing elements, and the results can be obtained by measurements taken at various points in the system.

The computer will of course be required to solve many different problems and the computing elements will have to be rewired every time. To facilitate this a patch panel is used, with sockets connected to each computing element in the computer. By using wire leads the computing elements can be connected in any order.

At the beginning of a computation the variables of the problem will have certain values, not all of which need be zero. The requirement here is that it should be possible, if desired, to give the output of integrators a value, before the computation commences. This facility is called "Initial Conditions".

Fig. 1.7 shows how the "Initial Conditions" for the "Compute", "Hold" and "Reset" facilities are achieved for summers and integrators. In the case of the summers no change in the circuit is necessary. For the integrators, the "Hold" mode requires that the input resistors are disconnected from the op-amp and grounded. In this way the charging or discharging of the capacitor stops and the op-amp maintains the charge at a constant level.

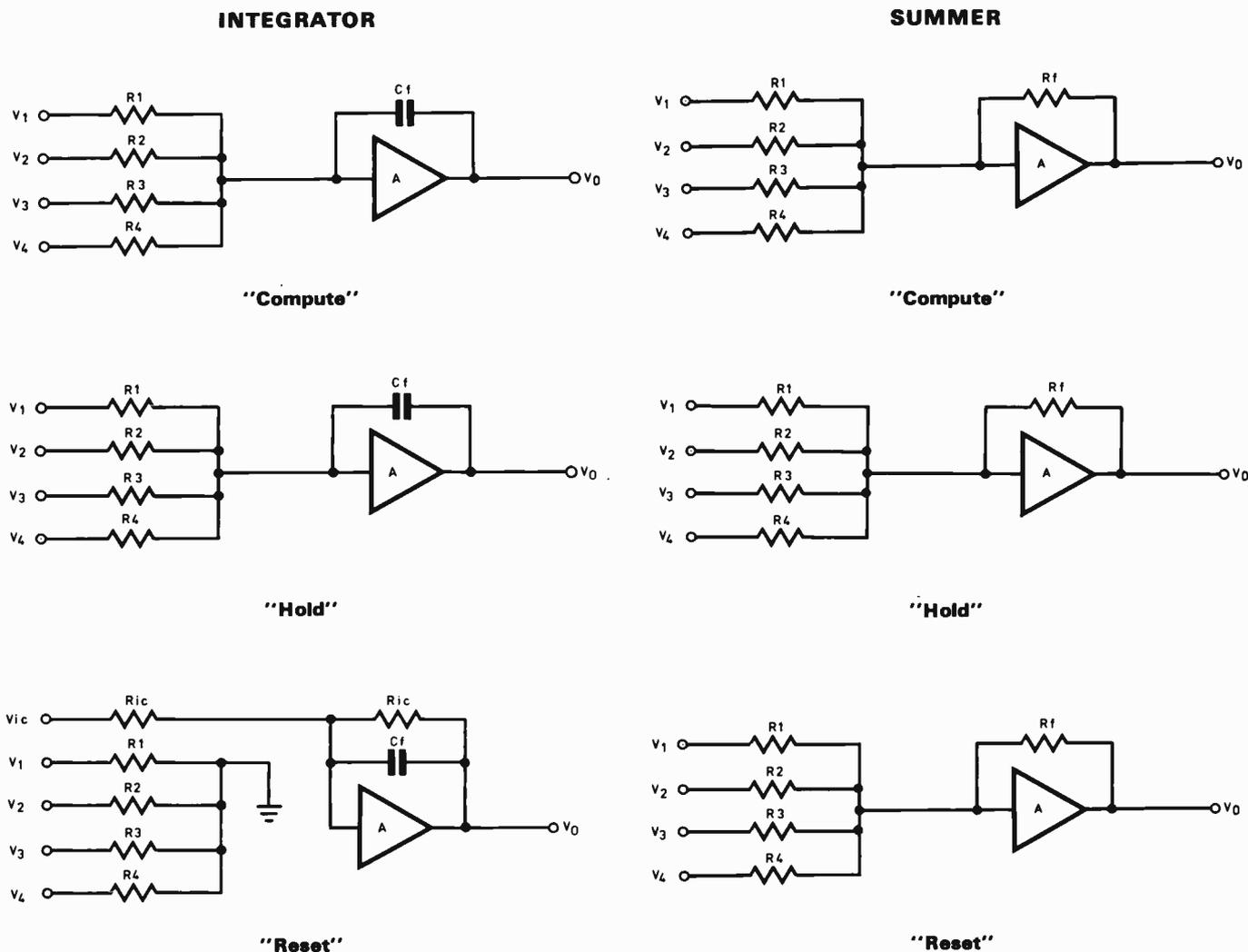


Fig. 1.8. "Initial Condition" circuits for Integrators and Summers

MODE CONTROL AND INITIAL CONDITIONS

The main modes of operation are compute, hold and reset. When in the compute mode the computer proceeds to solve the problem. As it is sometimes desirable to stop the computation after a certain period of time this is achieved by putting the computer into the "Hold" mode. The "Reset" mode is used to make the output of all computing elements take their initial value. Sometimes this mode is called "problem check".

The calculation is therefore frozen and the results can then be observed at leisure. This, however, should not be practised literally, since electronic components, like everything else, are not perfect and some drift will always affect the results. These should therefore be noted as soon as the "Hold" mode has been selected.

The "Reset" mode for the integrators has two resistors R_{ic} in the circuit. These are the "Initial Conditions" resistors and when an initial condition voltage, V_{ic} is applied as shown, the

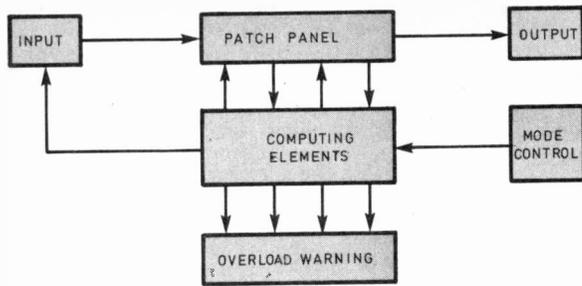


Fig. 1.9. Block diagram of the Analogue Computer

feedback capacitor charges up to this value. When "Compute" is selected these resistors are disconnected and the output of the amplifier, i.e. the voltage across the feedback capacitor, may vary above or below the initial condition value. When "Reset" is reselected the feedback capacitor discharges or charges, through R_{ic} to V_{ic} and the computer is again ready for a repeat of the calculation.

THE OVERLOAD WARNING FACILITY

This facility, usually employed in analogue computers, is necessary because the voltage range over which operational amplifiers operate linearly, is limited to approximately $\pm 13V$ for readily available i.c.s. In the course of the solution of a problem, all computing elements must operate within this range, otherwise the wrong results will be obtained. The overload warning circuit warns the programmer of any amplifiers that have saturated. Measures can then be taken to scale down the values of the variables.

It is now possible to imagine the general arrangement of an analogue computer and this is depicted by Fig. 1.9 in a block diagram form.

To summarise, input signals are fed to the computing elements via the patch panel and are processed. The results are fed back through the patch panel to the output, which may be an ordinary voltmeter, a CRO or an X-Y recorder. The operation of the computing elements is controlled by the Mode Control and the overload warning circuit monitors the output of the computing amplifiers and warns the programmer of any saturating amplifiers.

NEXT MONTH: CONSTRUCTION DETAILS

readout

... a selection from our postbag

Readers requiring a reply to any letter must include a stamped addressed envelope. Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

Champ Waves

Sir—I hope you can clear up the confusion that has arisen about your EPROM programmer in the CHAMP series.


When purchasing INTEL 1702A EPROMS I was sent a data sheet, which detailed the programming voltages as completely different from those produced by CHAMP-PROG. Since you said that INTEL had supplied the basic circuit for your project, and use it in their "Intellec" development systems, it has resulted in much head scratching on my part.

The waveforms given on the data sheet are as shown.

Any clarification you can give will be greatly appreciated.

T. G. Keslake
Romford
Essex

I can understand your confusion over the difference between the 1702A data sheet and the operation of the CHAMP-PROG board, but really it is quite simple. You will notice in the data sheet that all voltages are related to GND or 0 Volts, and this means that all chip voltages are related to the Vcc pins. In CHAMP-PROG the voltages appear to be positive going, but if you look at the Vcc reference pins you will find that they rise to +47V during programming, and this means

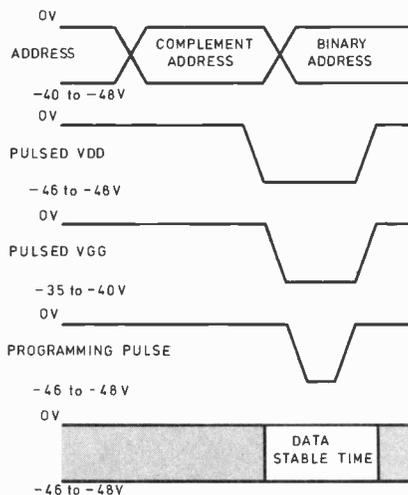

that the program pulse is a 3ms -47V pulse as required. As with many things in electronics, the secret lies in viewing the circuit operation with one's feet firmly on the ground (or in this case, the ceiling!). If you check the other supplies with this new perspective, you will find that they are substantially as dictated in the data sheet.

Once again, I quite understand your initial confusion!

R. W. COLES

Too Powerful

Sir,—Working as Product Marketing Engineer for the UK's largest distributor of National Semiconductor products I was highly amused by the letter which appeared in the July issue of P.E. from reader R. G. Silson.


I can only assume from reading his letter that he must be extremely well versed in the world of microprocessors—indeed he must know far more than the vast majority of industry's electronics engineers.

Dealing with engineers every day from all fields of the electronics world I quite naturally get a very good indication of their thoughts and feelings towards various projects.

The number of times I have spoken to customers about the Pace microprocessor, only to be told "Not interested—it's too powerful for what we need", is more than ample evidence for myself that Mr Silson is completely out of touch with the amount of knowledge possessed by the average amateur actively engaged in microprocessors. Further proof of this is the vast amount of 8 bit SC/MP chips sold related to the relatively slow moving Pace.

P. V. Hodson,
Melton Mowbray,
Leicestershire.

...all in our
OCTOBER issue!

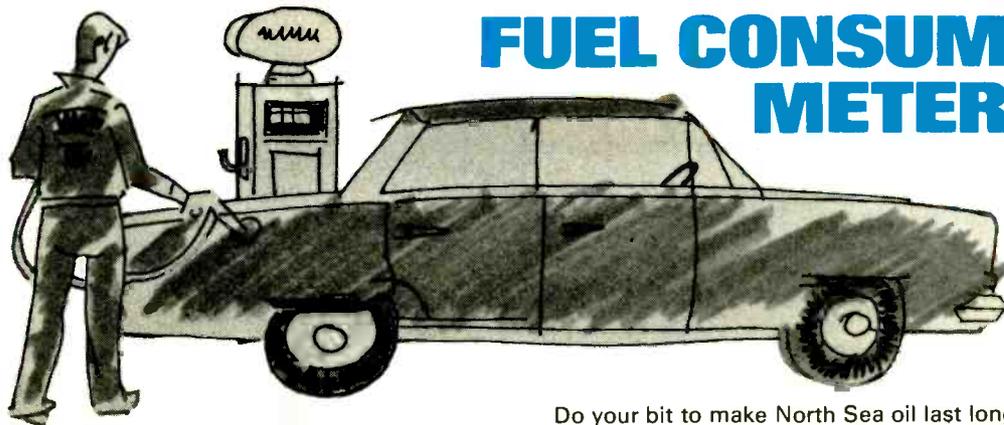

FUEL CONSUMPTION METER...

Do your bit to make North Sea oil last longer, and save yourself some money. This two digit display shows a consumption factor, derived, via six low priced TTL chips, from an electric fuel pump and the car's speedometer. An alternative analogue display circuit is also given.

HIGH PERFORMANCE POWER SUPPLY UNIT

Sooner or later you will need to treat yourself to a high performance power supply unit. This design has voltage control down to zero, yes zero volts, and current limitation from a few milliamps to several amps. It uses readily available components and has a regulation system which does not employ foldback and thus can give true constant current operation.

V.D.U. SYSTEM

A complete output peripheral for almost any computer, this memory mapped system is inexpensive, easy to construct, has one chip to control all basic functions.

FREE!

...IN NEXT
MONTH'S ISSUE


Stickies

One sheet of 120 Stickies worth 60p.

These self-adhesive labels identify pin-outs for a range of i.c.s. Useful for building and debugging prototypes, fault finding and designing p.c.b. layouts.

PRACTICAL ELECTRONICS

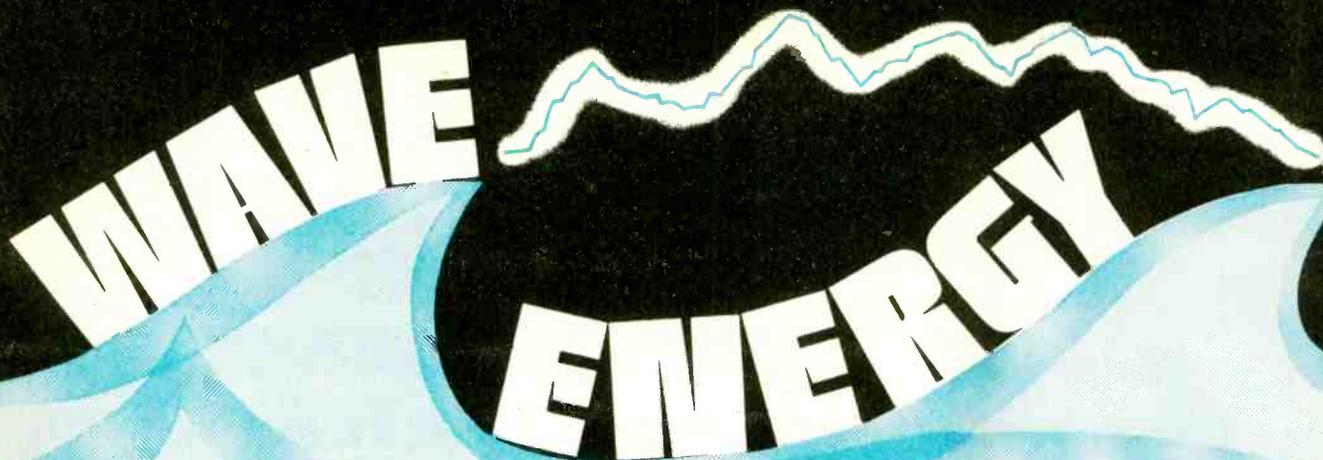OUR OCTOBER ISSUE WILL BE ON SALE FRIDAY, 8 SEPTEMBER, 1978.



WAVE ENERGY

OUR modern world is a power assisted machine; an energy-hungry life support system for concentrated populations. The threat of *that energy* expiring with nothing to replace it is depressing, yet much publicity is given to such gloom.

Many natural sources of energy are being explored, and too often, propositions are regarded by those who seal our fate, as "pipe dreams", but put two gloomy facts together; Britain's increasing need of energy, and the pounding of winter seas against our shores, and they begin to cancel out! Wave energy is turning that power into electricity. It is possible! *It is even considered practical!*

Oceanographic data indicates that a wave-power installation 500km (310 miles) long, with 50 per cent efficiency, could in principle provide a very substantial proportion of the UK's electrical power requirement, with peak outputs meeting total demand. This calculation is doubtless intended only to allow a grasp of the kind of energy levels existing in the waves off our shores, and is not meant to be a serious suggestion; *for a few generations at least!*

The Government has recently increased its wave-power research budget from £2.5 million to £5.4 million, and to the critics who complain that it's not enough, it has been pointed out that at this early stage technical problems are not going to vanish simply by having large sums of government money thrown at them. Four inventions are being studied, and it is hoped that one of these will emerge to become the blueprint for full-blooded wave-power stations. Money spent on the three "runners-up" will presumably be deemed as having gone towards proving that the fourth was best, or perhaps different designs will prove appropriate for different working locations. In any case, the real money will be spent when a design stands ready for full scale construction.

COCKERELL CONTOURING RAFT

When the wats come rolling in, the CCR could well be at the source, and is currently under development by Wavpower Ltd., a company comprising Sir Christopher Cockerell (inventor of the hovercraft), and a partnership of consulting engineers. Early small scale tests conducted in simulating tanks gave such good results that one-tenth scale trials are now taking place in the Solent, where the waves are obligingly also about one-tenth full scale. The photographs show a scaled down raft, and it can be seen to consist of adjacent pontoons whereby the energy may be extracted at their hinges, either via gearing, or by hydraulic rams, to drive alternators.

The probable location of such a wave-power station, it seems, would be five to ten miles off the coast of Scotland, or the western approaches to the English Channel. A string of rafts about 24km (15 miles) long would generate perhaps 500 megawatts. Fifteen miles sounds alarming, but remember that a conventional power station can occupy a mile of coastline and 200 acres of land. A wave-power station would not require the continual comings and goings of ugly tankers or coal trains, nor has it any nuclear risk.

The Solent trials are being monitored by a complex computer controlled digital tape recorder system, housed in a 25m sea-going barge anchored nearby, and linked by a sea-bed cable. A considerable list of parameters has to be recorded in connection with the CCR's performance and survival characteristics before construction of a full scale station can be undertaken. Not only power outputs related to wave heights, directions and tidal forces have to be logged, but mooring and hinge loadings, wind, and barometric pressures have to be recorded too, and much more data still. On the equipment barge an EMI p.c.m. recorder is used, which is particularly sophisticated, enabling 21 data channels to be recorded on each track of a 14 track tape.

It may not be until the late 1980s that we see a full scale prototype wave-power station, but an artist's impression illustrates the magnitude of such a system.

SALTER DUCKS


Another device for extracting power from the waves is the Salter Duck, the brainchild of Stephen Salter of the Department of Engineering, Edinburgh University.

Tank tests showed that the more obvious bobbing up and down action of a "ball-cock" connected to a dynamometer would only extract about 15 per cent of the available energy in a wave; but re-orientating it to obtain a to and fro movement increased energy extraction to about 60 per cent.

So, a vertical flap was tried; however, this was found to displace water behind it, the extra impedance causing about 20 per cent of the wave energy to bounce back at the source. What was called for was a "flap with no back". The end product of this quest is shown (opposite page), and makes the oncoming wave think it's driving another wave—the optimum and natural loading situation!




The strange cam shaped segments are the ducks, and these revolve with respect to the shaft, or backbone as it is called. The combination is referred to as a string. A 500m (approx $\frac{1}{2}$ mile) backbone is clearly going to come in for some enormous

COCKERELL CONTOURING RAFT

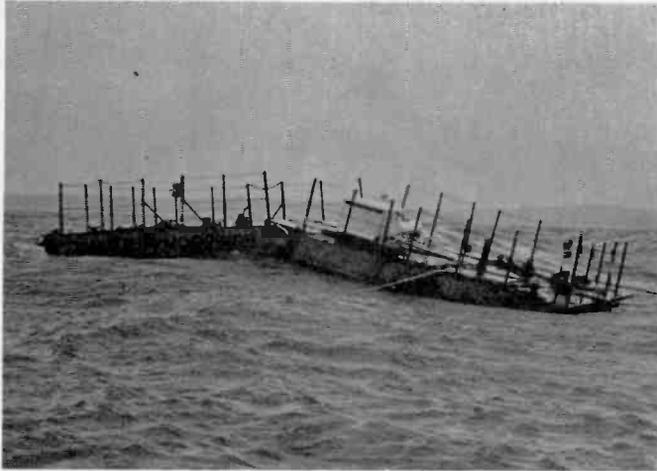

Above: One-tenth scale Wavpower Raft under test in the Solent

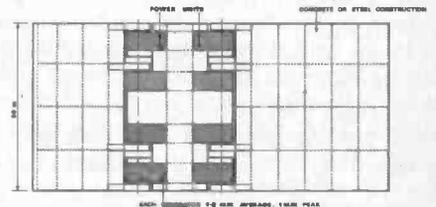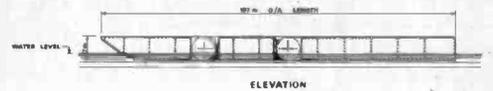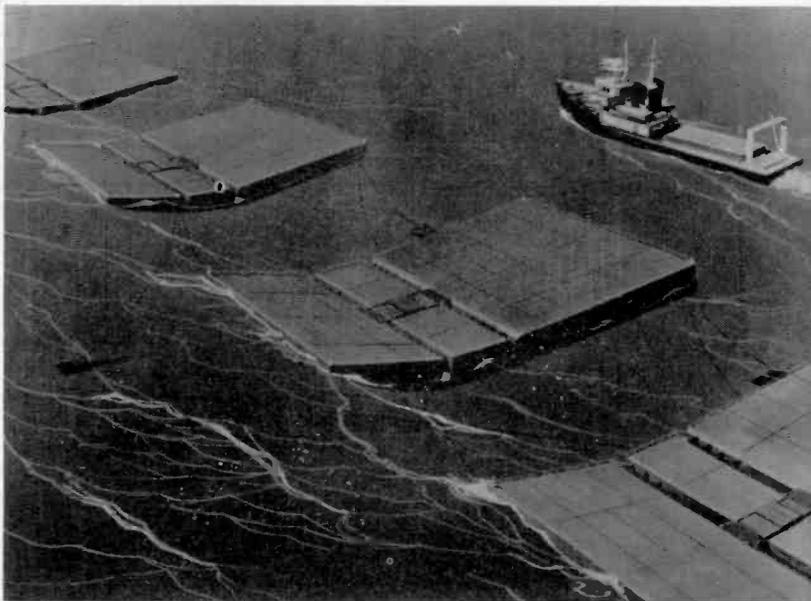Below: Dimensions of a full-scale raft suitable for Hebridean location





PLAN
SCHEMATIC RAFT LAYOUT POWER OUTPUT: 8 MEGAWATTS (PEAK), 1.0 MEGAWATTS (AVERAGE)
 DIMENSIONS QUOTED ARE SUITABLE FOR HEBRIDIAN LOCATION

WAVEPOWER LIMITED


An artist's Impression of a full-scale installation. All illustrations courtesy of Wavpower Ltd

SALTER DUCK

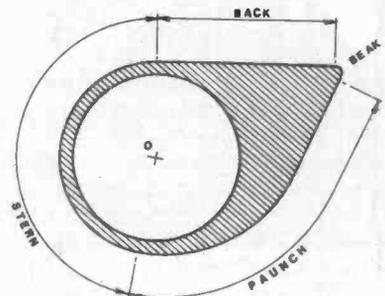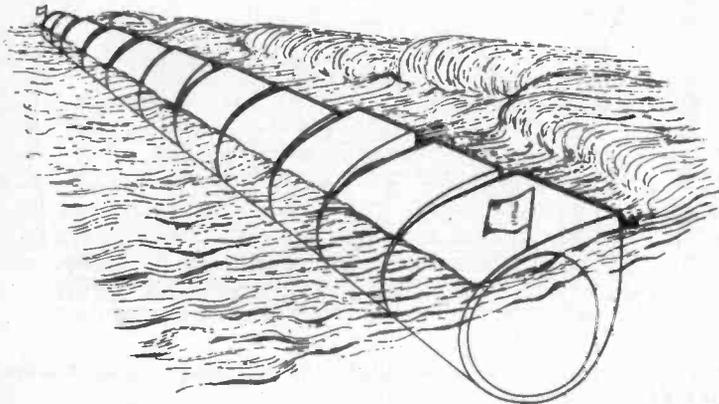Artist's impression of full-scale equipment



Duck anatomy

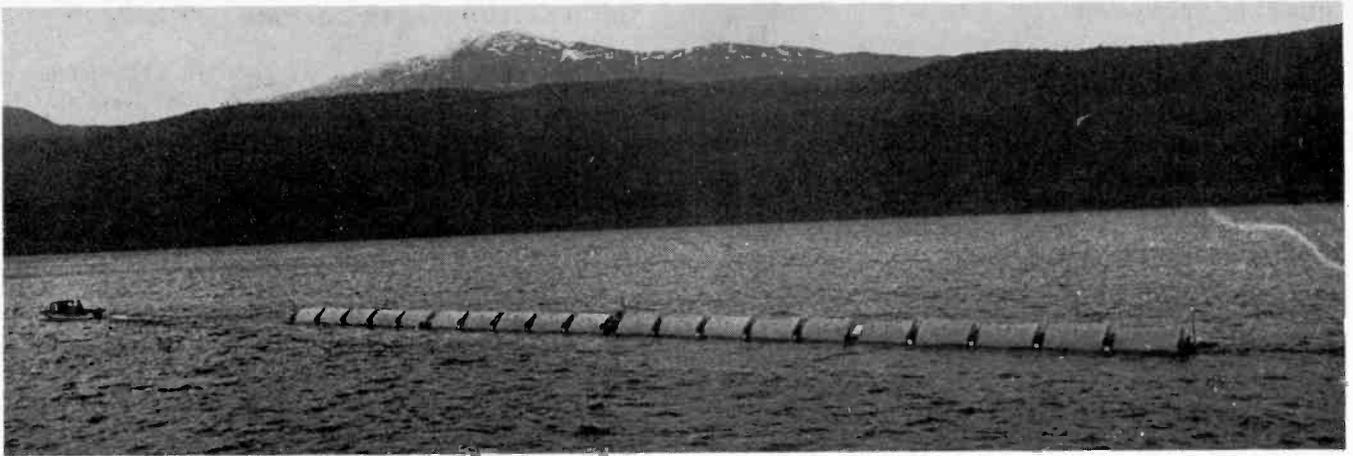

At Edinburgh University where the Salter Duck was originally developed, study is now concentrated on the theoretical and behavioural nature of the machine. On a more practical level at Lanchester Polytechnic (Coventry), Sea Energy Associates build scale models for testing. Shown above are one-fifteenth scale machines (50m string with 30 tonnes displacement) undergoing trials on Loch Ness. Illustrations courtesy of Lanchester Polytechnic

bending moments, and of the "flexible" or "rigid" alternatives for construction, the "long and strong" approach is favoured, since the backbone will experience a variety of phases of wave along its length at any one time, causing a certain amount of averaging. A design has been put forward for a kind of "bistable" backbone which will become flexible when hit by any freakishly powerful waves.



Power take-off is an inherent problem with any wave-power device, and here the ducks will have an angular amplitude of less than half a radian. In addition, duck velocities are far too low for conventional electricity generation, but such things as radial pistons (perhaps around 100 per duck) might produce a flow of hydraulic fluid at pressures of up to 3,000lb/in². Electricity can then be generated via hydraulic "swash plate" motors, whereby swash plate angle control will allow constant speed, irrespective of duck "nod" periodicity. Economic considerations leave their

fingerprint on everything in life, and so it is fortunate that a wealth of hydrostatic rotary transmission components exist already in the commercial world.

Interesting problems are legion; such as how do you permanently moor a floating structure of some 500m in length, at over 100 tons displacement per metre, in 40 fathoms of fully exposed ocean? And how do you connect this vertically mobile object to high capacity seabed cables? Answers to these and other questions are crystallising, however, and optimism is high. Above photograph shows working model.

Electricity transmission itself poses a dilemma. Cheaper terminal equipment results with a.c. but heavier conductor is necessary to carry the capacitive currents, whereas d.c. requires rectification etc., but evades synchronisation difficulties. For long distances d.c. cables are cheaper, but the crossover distance is roughly that expected with Salter Duck positioning.

RUSSELL RECTIFIER

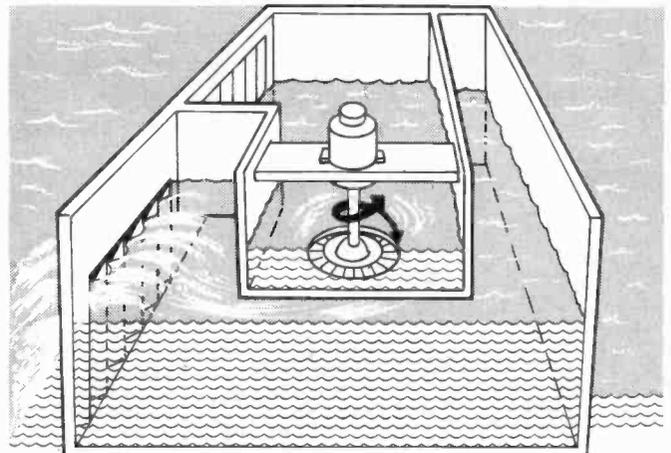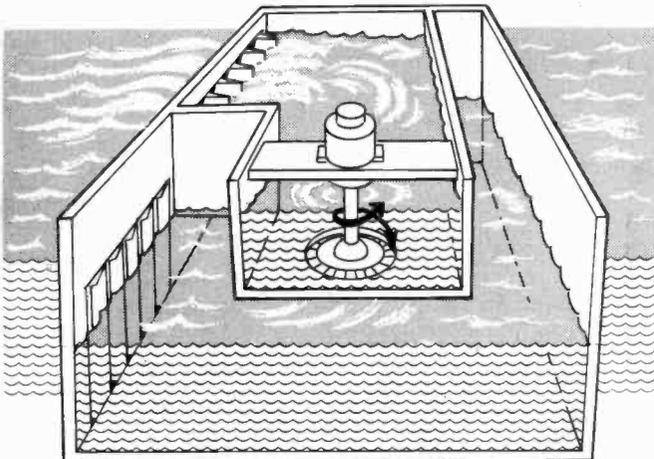

The Russell Rectifier is shown above in both states of flux. (left) The upper chamber fills as the wave rises. (right) The lower chamber empties during the trough of a wave. Courtesy of HRS

RUSSELL RECTIFIER

Using a rather more straightforward approach to the extraction of wave energy, the RR has a simple one-way system, (hence the name rectifier) which stores a head of water, to release it again when the wave level has dropped. Of course, on finding its way back to the sea, the water has to drive a turbine. This system, which is being developed at the Hydraulics Research Station, Wallingford, is shown on the opposite page in both states of flux.

The upper chamber allows water to enter only, via one-way flaps, and this fills up at the peak of a wave. The lower chamber allows water to leave only, using outlet ports with one-way flaps working in the other direction. These flaps are self-operating due to the pressure differentials generated by the wave motion.

Because the rise and fall of pressure from top to bottom outside the reservoir does not occur simultaneously at all points, the vertical flaps must be capable of twisting, so that they can be open at the top whilst being closed at the bottom. Large numbers of these chambers would be used in this wave-power system, and if used in shallow waters might sit on the sea-bed, but to utilise the more powerful Atlantic swell would probably form some kind of stable floating installation a few miles offshore.

An investigation into suitable low-head turbines is currently taking place, and no efficiency figures were supplied. A model at


OSCILLATING WATER COLUMN

The National Engineering Laboratory found its inspiration in the Air Pressure Ring Buoy used in Japan (developed by Masuda), and which contains an air turbine-driven generator with storage batteries to provide self-energising navigational lights. The air pressure to drive the buoy's turbine comes from a cylinder in which a column of water moves up and down like a piston, the "push" being provided from underneath by oncoming waves.

This principle has been evolved to a greater level of sophistication by the NEL, who have been examining the cost/efficiency trade-off involved in intensifying the primary conversion force (that produced by the oscillating column of water), from low pressure high volume energy to a more optimum ratio.

Another aspect is that of rectification, since with the simplest form of oscillating water column, *which is nothing more than an inverted "can" with an air-hole at the top*, as air is forced out by rising water within, the air turbine would revolve in one direction. However, as the water level dropped, air would be sucked in, which would then revolve the turbine in the opposite direction. This rapid reversal of the rotor, overcoming its momentum and inertia at every cycle, is clearly not an efficient mode of operation.

OSCILLATING WATER COLUMN

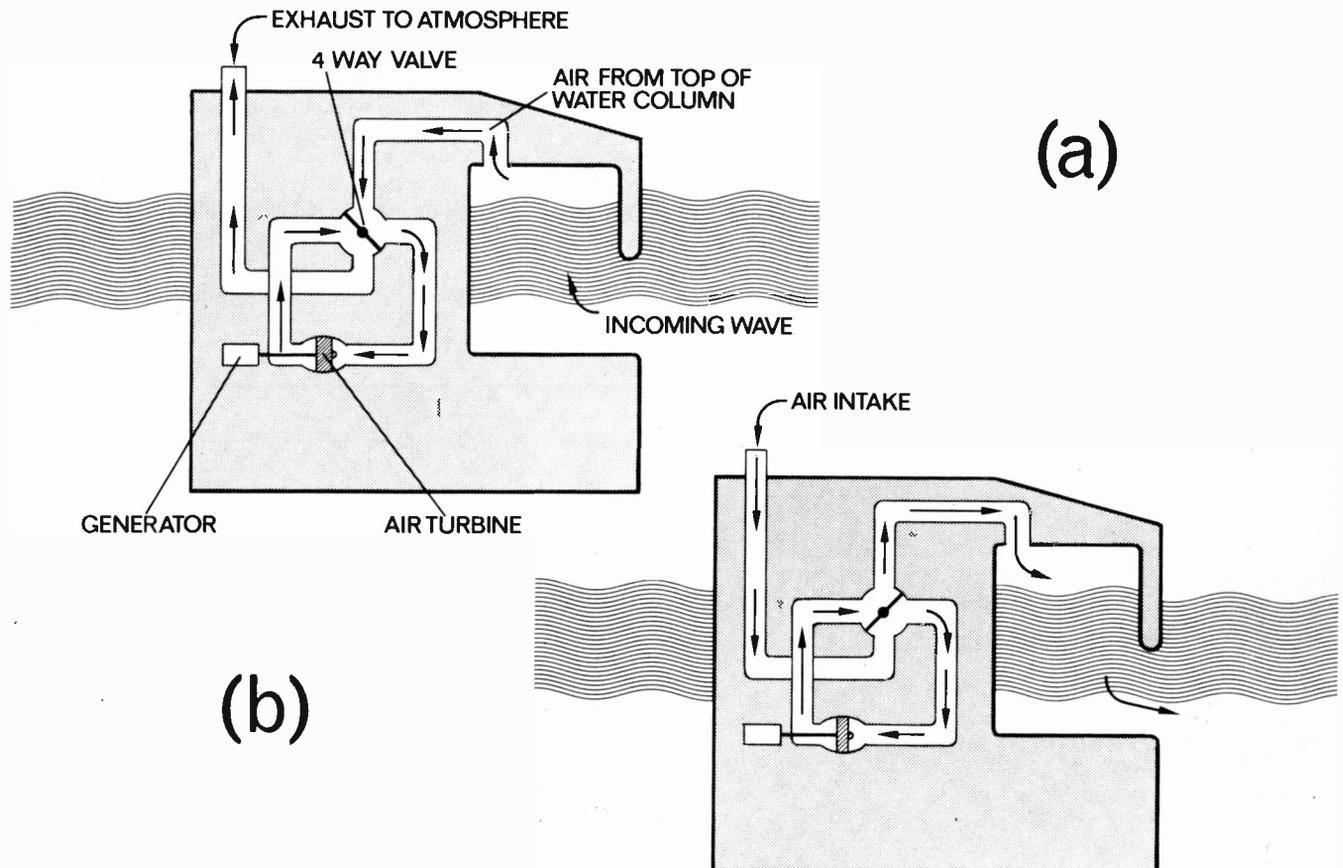

Rectification is achieved by the system shown above, which illustrates the simple OWC principle in its entirety. It employs a kind of pneumatic version of the familiar bridge rectifier circuit. A four-way valve is used to re-route the flow of air in each half cycle so that it always passes through the turbine blades in the same direction. (a) shows the airflow whilst the wave is rising, and (b) shows the situation as a wave trough develops.

Ideally the OWC should remain motionless when in action, as it wouldn't be very effective if it bobbed up and down on the waves it was supposed to convert. But it is no simple matter to build a structure rising from the seabed, out where the swell is strong, that will not bend during its first storm, particularly at a reasonable cost! It became necessary to confine investigation to the stability of *floating* structures. There are two simple guides to efficiency, one is to consider the amount of surviving wave to appear leeward of the wave-power machine, and the other is the amount of wave bounced back on impact. The OWC's cylinder has a good damping action so that the latter inefficiency is minimal.

Computer models and actual scale models have been used to arrive at the shape of structure shown, which uses the phenomenon of wave cancellation to achieve a stability which gives high efficiency of primary conversion (up to 80 per cent). Of course, the machine *could* be made so large that it hardly moves at all, but the OWC shown experiences relatively low stress, requiring only a soft mooring arrangement, and in a survival situation will limit the maximum stress by being able to ride out the "punch".

ENERGY ENOUGH?

Power from the waves should not be confused with tidal-power, although they both fall into the category known as "renewable" or natural energy sources.

The world's waves, it is estimated, have a potential energy of several times the present global demand for all forms of energy, and it seems Britain has some of the best waves in the world! Couple this with the fact that being a small island, we have a fairly favourable coastline-to-land-area ratio, and it begins to look as though the U.K. should capitalise on its pounding waves for electricity in much the same way that mountainous countries employ hydro-electric power.

Waves cannot approach solar radiation in total amounts of energy, but do exceed wind power. The waves do, however, have a unique advantage over solar energy in that they are most powerful during those winter months when electricity demands are highest, thus corresponding more usefully with our needs.

Measurements made by British Oceanographic Services lead Stephen Salter to conclude that the average power density in the North Atlantic is 80 or 90 kilowatts per metre of wave front. Other observations show that the open oceans are seldom less than 10kW/m.



Another peep into the crystal ball. Huge volumes of air rushing beneath those cowls would surely sound like a giant in deep slumber. Illustrations courtesy of NEL

In British waters, wave-power is worth having for 80 per cent of the time, and this figure moves to 90 per cent during the winter. It is possible for "no power" periods to occur (although rare), and for this reason a secondary source of electricity would be necessary. This could come from a regenerative storage system which had been accumulating energy when power exceeded demand.

CONSEQUENCES

On looking into the wave-power programme, the "contestants" in this technological race, with their ingenious contraptions, are reminiscent of the film *Those Magnificent Men And Their Flying Machines*, and if any natural energy source ever does "take off" it could well be wave-power. But like the aeroplane, which grew from a few struts to the jumbo jet with vast airport complexes and deafening noise, *could* great stretches of coastline, becalmed by strings of wave-power machinery, be ecologically altered? It has been estimated that in-shore water temperatures could drop, and even harbours silt up. There would inevitably be shipping accidents too.

The nation has to ask: Is the price worth paying? One view is: The more wave-power, the less nuclear power.



BOOK REVIEWS

MOBILE DISCOTHEQUE HANDBOOK

By Colin Carson

Published by Bernard Babani Ltd

127 pages, 180 x 108mm. Price £1.35

SETTING up as a mobile D.J. can be done in a bits and pieces way but any serious disco entertainer should know a fair amount about all the elements involved.

This paperback starts with a run down of electricity basics and goes on to explain audio systems.

Quite a lot of money can be saved by studying the great range of record decks available and buying sensibly sturdy gear without being swayed by glossy exteriors. Similarly, cartridges and styli can cost a fortune but for a possibly roughly handled disco outfit the selection of a not too expensively replaced delicacy will be the best bet.

Mixers, decibels, tone controls, input impedance, attenuation, distortion, dynamic range, and wiring up a mixer are explained in some detail.

Designing and building a console is covered and advice is given on ancillary equipment—microphones, stands, headphones, cassette players, jingles.

The many types and sizes of plugs and sockets are rationalised in the section on cables and plugs.

Loudspeakers and their enclosures are very important. The relative advantages of cabinets, columns and bass bins are discussed, as is frequency splitting.

No disco is complete without lighting of some kind. Sound to light units and sequence controlled units are described, but no detailed circuitry is given.

This book may well prevent unnecessarily expensive gear being bought.

A.T.

The most economical, compact and convenient breadboards on the market!

They are the PROTO-BOARD® PB-6 and PB-100 solderless breadboard kits.

Buy them, and you are only minutes away from the first circuit.

Contacts are made from non-corrosive nickel-silver alloy, and are reliable for more than 10,000 insertions.

Contact resistance is a mere 0.4 mΩ, insertion force is typically 3 ozs per lead, and interterminal capacitance is typically less than 5 pF.



The kits are a must for experimental and development work in digital, audio, RF, video and beyond.

Resistors, capacitors, transistors, DIP's, LED's, transformers, pots, jumpers and any other component with leads between 0.015" and 0.032" will fit the contacts.

You can run circuits well beyond the recommended ambient operating temperature (100°C) if you wish, because the plastic used in the PROTO-BOARD is rated to over 200°C.


The kits come complete with instruction manual, assembly hardware, binding posts, non-scratch feet and the appropriate number of preassembled sockets and bus strips.

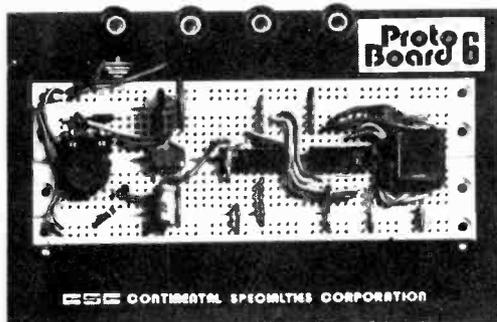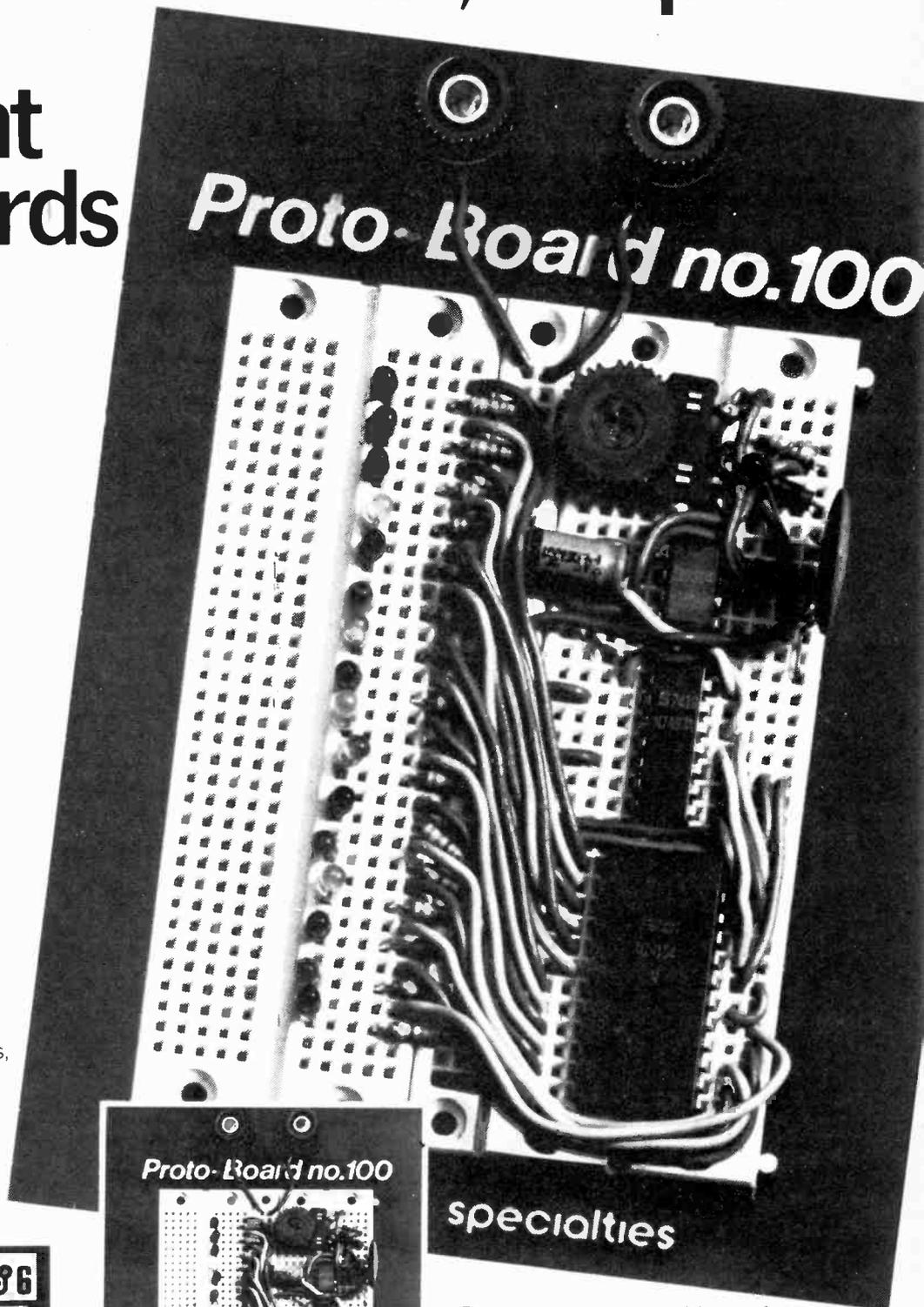The sooner you order, the sooner you'll have that first circuit operating.



THE PB-6 630 SOLDERLESS CONTACTS. TAKES UP TO SIX 14-PIN DIP'S OR EQUIVALENT IN LARGER AND SMALLER IC'S. FOUR 5-WAY BINDING POSTS. 6" x 4"

ONLY COSTS £11.01

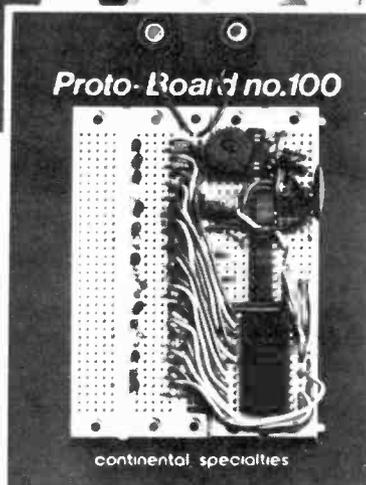

THE PB-100 760 SOLDERLESS CONTACTS. TAKES UP TO TEN 14-PIN DIP'S OR EQUIVALENT IN LARGER AND SMALLER IC'S. TWO 5-WAY BINDING POSTS. 6" x 4.5"

ONLY COSTS £13.82

Ring us (01-890 0782) with your Access, Barclaycard or American Express number and your order will be in the post that night. Alternatively, send a cheque, or postal order (don't send credit cards!) and it still only takes a few days. Otherwise ask for our complete catalogue. Our prices include VAT (8%) and postage. All prices and specifications correct at the time of going to press.

CONTINENTAL SPECIALTIES CORPORATION



TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT 8%

12 AND 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS

Ref	12V Amps	24V £	P & P
111	0.5	0.25	2.20
213	1.0	0.5	2.64
71	2	1	3.51
18	4	2	4.03
70	6	3	5.35
108	8	4	8.98
72	10	5	7.67
116	12	6	8.99
17	16	8	10.39
115	20	10	13.18
187	30	15	17.05
226	60	30	26.82

30 VOLT RANGE

Prim 220/240V Sec 0-12-15-20-24-30V. Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V, 15V-0-15V.

Ref	Amps	£	P & P
112	0.5	2.84	0.78
79	1.0	3.57	0.96
3	2.0	5.27	0.96
20	3.0	6.20	1.14
21	4.0	7.44	1.14
51	5.0	8.37	1.32
117	6.0	9.92	1.45
88	8.0	11.73	1.64
89	10.0	13.33	1.84

50 VOLT RANGE

Prim 220/240V Sec 0-20-25-33-40-48-60V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V or 24V-0-24V, 30V-0-30V.

Ref	Amps	£	P & P
124	0.5	3.88	0.96
126	1.0	5.58	0.96
127	2.0	7.60	1.14
125	3.0	10.54	1.32
123	4.0	12.23	1.84
40	5.0	13.95	1.64
120	6.0	15.66	1.84
121	8.0	20.15	OA
122	10.0	24.03	OA
189	12.0	27.13	OA

60 VOLT RANGE

Prim 220/240V Sec 0-24-30-40-48-60V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V or 24V-0-24V, 30V-0-30V.

Ref	Amps	£	P & P
124	0.5	3.88	0.96
126	1.0	5.58	0.96
127	2.0	7.60	1.14
125	3.0	10.54	1.32
123	4.0	12.23	1.84
40	5.0	13.95	1.64
120	6.0	15.66	1.84
121	8.0	20.15	OA
122	10.0	24.03	OA
189	12.0	27.13	OA

MAINS ISOLATING (SCREENED) PRIM 120/240 SEC 120/240 CT TAPPED

Ref	VA (Watts)	£	P & P
07*	20	4.40	0.79
149	60	6.20	0.96
150	100	7.13	1.14
151	200	11.16	1.50
152	250	12.79	1.84
153	350	16.28	1.84
154	500	19.15	2.15
155	750	29.06	OA
156	1000	37.20	OA
157	1500	45.60	OA
158	2000	54.80	OA
159	3000	79.05	OA

AUTO TRANSFORMERS

Ref	VA (Watts)	Volts	£	P & P
113	15	0-115-210-240	2.48	0.71
64	75	0-115-210-240	3.95	0.96
4	150	0-115-200-220-240	5.35	0.96
67	500	0-115-200-220-240	10.99	1.64
84	1000	0-115-200-220-240	18.76	2.08
93	1500	0-115-200-220-240	23.36	OA
95	2000	0-115-200-220-240	34.82	OA
73	3000	0-115-200-220-240	48.00	OA

HIGH VOLTAGE MAINS ISOLATING

Prim 200/220V or 400/440V Sec 100/120V or 200/240V

VA	Ref	£	P & P
60	243	5.89	1.84
350	247	14.11	1.84
1000	250	35.65	OA
2000	252	54.25	OA

CASED AUTO TRANSFORMERS

240V cable in & 115V USA 2 pin outlet

VA	£	P & P	Ref
4	9.96	0.96	113W
150	8.48	1.14	4W
200	9.92	1.45	65W
250	10.49	1.45	69W
500	15.73	1.64	67W
750	18.55	1.76	83W
1000	22.88	OA	84W
1500	26.02	OA	93W
2000	37.65	OA	95W

SCREENED MINIATURES

Ref	mA	Volts	£	P & P
238	200	3-0-3	1.99	0.55
212	1A, 1A	0-6, 0-6	2.85	0.78
13	10	0-9-9	2.14	0.38
235	330, 330	0-9, 0-9	1.99	0.38
207	500, 500	0-8-9, 0-8-9	2.59	0.71
208	1A, 1A	0-8-9, 0-8-9	3.53	0.78
236	200, 200	0-15, 0-15	1.99	0.38
214	300, 300	0-20, 0-20	2.56	0.78
221	700 (DC)	20-12-0-12-20	3.41	0.78
206	1A, 1A	0-15-20-0-15-20	4.43	0.96
203	500, 500	0-15-27-0-15-27	3.99	0.96
204	1A, 1A	0-15-27-0-15-27	5.39	0.96
S112	500	12-15-20-24-30	2.64	0.78
239	50	12-0-12	1.99	0.38

COMPONENT PACKS

50 High Quality Metal Oxide 2.5% 1/2W Resistors.
150 Mixed Value Capacitors
10 Read Switch.
30 Wire Wound Resistors, mixed.
25 assorted Presets.
50 3 Tag Terminal Strips.
Hardware pk. bolts, nuts, washers, insulators 70p + 12 1/2% P & P 40p.

AMPLIFIER MODULES

10W	(AL30)	£3.75
25W	(AL60)	£4.57
35W	(AL80)	£7.15
125W	(AL250)	£17.25

Power Supply PS12 £1.30
Power Supply SPM80 £4.25
VAT 12 1/2% P & P 35p

MINI-MULTIMETER

DC-1000V AC-1000V DC-100mA Res-150kΩ
1000Ω/V Bargain £5.96/P & P 62p VAT 8%

NEW RANGE TRANSFORMERS

Ref	VA	£	P & P
45-36-0-36-45	2A	9.89	1.48
45 to give	3A	11.47	1.48
36 to 36	4A	13.90	1.45
45-0-45	5A	16.74	2.15
72V or 90V	6A	20.77	2.30

ABS Plastic Boxes inset brass nuts, slots to take PC cards, flush fitting lid.

PB1	80mm x 62 x 40	56p
PB2	100mm x 75 x 40	63p
PB3	120mm x 100 x 45	70p

P & P 29p, VAT 8%

20,000 ohm/V Multimeter, mirror scale. Ranges AC/DC to 1000V. DC currents to 250mA. Resistance to 3 Mohms 5" x 3 1/2" x 1 1/2" £11.34 P & P £1.05 VAT 8%.

TEST METERS

U4315 Budget Meter 20KΩV DC 2KΩV AC 1000V AC/DC 2.5A AC/DC 500K res. in robust steel case and leads £15.85.

PLUG IN SAVE BATTERIES

3300 fits into 13A socket 6-7, 5-9V 300mA multipoint outlet £3.30
A122 3, 4-5, 6, 7-5, 9, 12V 500mA
VAT 12 1/2% P & P 55p £9.21

TRANSFORMERS SPECIAL OFFER (Limited Stocks)

B61 Prim 0-120-0-120V (120 or 240V) Sec 24V 10A £5.50 P & P £1.66

7559, 250-0-250V 6-3V, 12.9-0-12.9V. £6.50 P & P 90p

B63 100V line to 4D 7/10W £2.05 P & P 66p

B64 0-120V x 2 (120V or 240V) Screen sec 9-0-9V 1A £2.40 P & P 71p

SPECIAL OFFER AVO Meter (107)

Ranges DC volts 2.5, 10, 50, 100, 500, 1000V - current 1mA, 2.5, 10, 50, 100, 500, 1 amp, AC 10V, 100, 1000, 3 ohmic ranges to 10M ohms. 10,000V DC, 1000 AC Safety cut out £40.00. P & P £1.15 VAT 8%.

ISOLATOR 1KVA 240V to 240V enclosed style terminal connection Special Offer @ £18.70. Carriage £2.75.

DECS SOLDERLESS BREAD-BOARDING

S Dec 70 contacts £1.98
T Dec 208 contacts £3.63
U Dec 'A' for I.C.s etc £3.99
U Dec 'B' for I.C.s etc £6.99
VAT 8% P & P 40p

ANTEX SOLDERING IRONS

15W	£3.75
25W	£3.95

Stand £1.40
P & P 46p VAT 8%.

PANEL METERS

Ref	VA	£	P & P
2" 0-50µA	5.50	4" 0-50µA	6.70
0-500µA	5.50	0-500µA	6.70
0-1mA	5.50	0-1mA	8.40
0-50V	5.50	0-50V	8.40
0-100µA	5.50	0-100µA	6.70

VU Indicator Panel 48 x 45 250µA FSD £2.60
VU Indicator Edge 54 x 14 250µA FSD £2.60

BRIDGE RECTIFIERS


50V	50A	£2.00
200V	2A	£0.45
400V	4A	£0.85
500V	10A	£2.35

VAT 12 1/2% *VAT 8% 15p P & P

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

DORAM

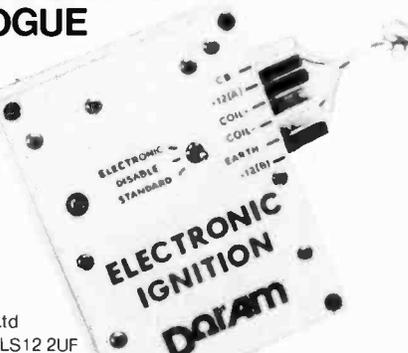SEE THE ELECTRONIC IGNITION MKII IN THE NEW HOBBIES CATALOGUE



Doram Electronics Ltd
PC Box TR8, Leeds LS12 2UF
REG. No. LONDON 1155856

Please send my FREE Hobbies Catalogue.
I enclose **25p** contribution to p. & p.
Name.....
Address.....

DORAM Doram Electronics Ltd
PO Box TR8, Leeds LS12 2UF
REG. No. LONDON 1155856

Overseas customers (except for N. Ireland) -60p including despatch by Air (or all-up post).

T.T.L. 74 I.C.'s By TEXAS, NATIONAL, I.T.T., FAIRCHILD etc

7400	14p	7426	25p	7473	30p	74121	30p	74151	65p	74179	140p
7401	14p	7427	25p	7474	30p	74122	40p	74152	55p	74180	100p
7402	14p	7428	40p	7475	30p	74123	60p	74153	120p	74181	200p
7403	14p	7430	15p	7476	30p	74125	50p	74155	70p	74182	75p
7404	14p	7432	25p	7483	85p	74126	50p	74156	70p	74184	150p
7405	14p	7437	25p	7485	100p	74130	130p	74157	70p	74185	150p
7406	40p	7438	25p	7486	30p	74131	100p	74160	90p	74188	350p
7407	60p	7440	15p	7489	25p	74132	65p	74161	90p	74189	350p
7408	20p	7441	65p	7490	35p	74135	100p	74162	90p	74190	140p
7409	20p	7442	65p	7491	75p	74136	80p	74163	90p	74191	140p
7410	15p	7445	80p	7492	45p	74137	100p	74164	125p	74192	120p
7411	20p	7446	85p	7493	40p	74138	125p	74165	125p	74193	120p
7412	20p	7447	75p	7495	60p	74139	100p	74166	125p	74194	100p
7413	30p	7448	70p	7498	70p	74141	60p	74167	325p	74195	100p
7414	60p	7450	15p	7499	95p	74142	270p	74170	200p	74196	100p
7416	30p	7451	15p	74104	40p	74143	270p	74173	150p	74197	100p
7417	30p	7453	15p	74105	40p	74144	270p	74174	100p	74198	185p
7420	15p	7454	15p	74107	30p	74145	75p	74175	75p	74199	185p
7422	20p	7460	15p	74109	50p	74147	230p	74176	100p		
7423	25p	7470	30p	74118	90p	74148	160p	74177	100p		
7425	25p	7472	25p	74120	90p	74150	120p	74178	140p		

C. MOS.

4000	14p	4030	55p
4001	14p	4032	95p
4002	14p	4033	120p
4006	90p	4047	100p
4007	16p	4049	40p
4009	55p	4050	40p
4011	14p	4050	40p
4012	14p	4054	120p
4013	50p	4055	140p
4015	90p	4056	135p
4016	40p	4060	120p
4017	90p	4066	55p
4018	90p	4069	20p
4020	100p	4071	16p
4022	90p	4072	16p
4023	16p	4081	16p
4024	65p	4082	16p
4025	16p	4510	120p
4026	160p	4511	150p
4027	50p	4516	110p
4028	90p	4518	130p
4029	110p	4528	100p

IN4148 BY ITT/TEXAS 100 for £1.50.

UNENCODED HEXADECIMAL 19 KEY-BOARD. 1-10 A.B.C.D.E.F. 2 OPTIONAL KEYS. SHIFT KEY £12.50.

555 Timer, 10 for £2.50.

741 Op. amp. 10 for £2.00.

RCA SCR TO3 case 100V 12.5A £2.50.

MURATA ULTRASONIC TRANSDUCERS MA40LR £2.50 each. £4.00 pair.

2102AN-2L 1024 x 1 BIT 250 NANO SEC. STATIC RAM. £2.20 each. 4/£8.40. 8/£16.00.

2102AN-4L 1024 x 1 BIT 450 NANO SEC. STATIC RAM. £1.60. 4/£6.00. 8/£11.60.

2112-4 256 x 4 BIT 450 NANO SEC. STATIC RAM. £2.95 each. 4/£11.60. 8/£22.80.

2 513 CHARACTER GENERATOR. UPPER CASE £7.00.

2 513 CHARACTER GENERATOR. LOWER CASE £7.00.

MM5204AQ PROM 4096 BIT READ ONLY MEMORY £8.00.

8212 8 BIT IN/OUT PORT £3.00.


8831 TRI-STATE QUAD LINE DRIVER £2.00.

8833 TRI-STATE TRANS-CEIVER (TRUE) £2.00.

8835 TRI-STATE TRANS-CEIVER (INVERTING) £2.00.

AY5-1013 UART/ £6.00. LM309K/LM340K VOLTAGE REGULATOR £1.00 each.

Gould Advance Instruments— Professional quality at a realistic price.

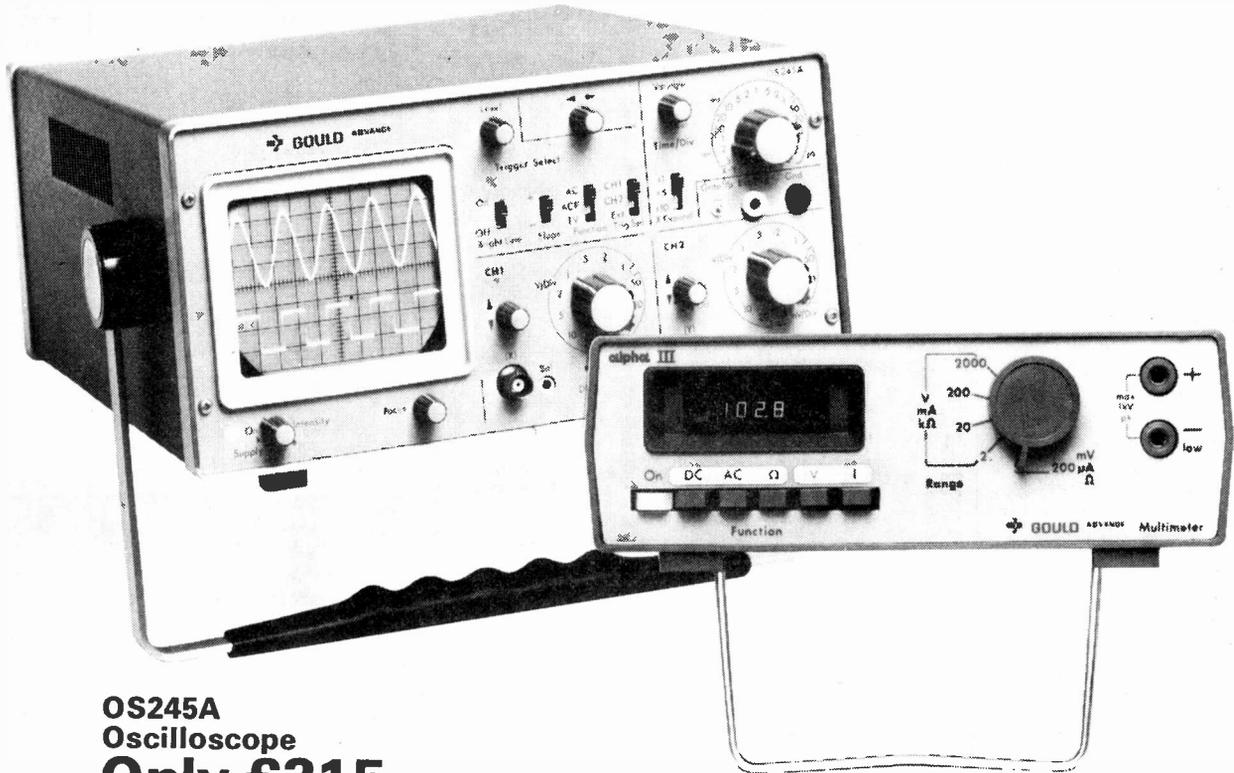

**OS245A
Oscilloscope
Only £215** (excluding VAT)

**Alpha III Digital
Multimeter Only £89** (excluding VAT)

OS245A Oscilloscope

Fault-finding, circuit testing or servicing – an oscilloscope is indispensable. It saves time, prevents costly mistakes, and enables you to tackle bigger, better projects.

Now, Gould Advance offer you this professional-quality, dual-trace instrument, at a price which brings it within reach of the amateur enthusiast.

Just look at these great Gould Advance features – then compare the OS245A for value!

- *DC-10MHz bandwidth
- *Dual trace
- *Clear controls, simple operation
- *Fully guaranteed for 2 years
- *5mV/div. sensitivity
- *Time-base speeds to 100 ns/div.
- *4" CRT with 8 × 10 div.

Gould Instruments Division,
Roebuck Road, Hainault, Essex IG6 3UE.
Telephone: 01-500 1000 Telex: 263785.
Registered Number 263834 England.

Alpha III Digital Multimeter

With a choice of 25 ranges and basic accuracy of $\pm 0.2\%$, the Alpha III is a professional's multimeter, yet it is versatile enough to cover every amateur application.

And although it is offered at such a modest price, it shares the advanced design features of the more expensive Gould Advance instruments – in particular, the purpose-built chip, incorporating all analogue and digital circuitry.

- *2,000 scale length (100mV resolution)
- *Tough, attractive moulded case
- *Bright red LED display
- *25 ranges
- *Fully guaranteed for 2 years

 **GOULD**

TO Bob Wheeler, Gould Instruments Division,
Roebuck Road, HAINAULT, Essex IG6 3UE.

PLEASE SEND ME:—

AN OS245A OSCILLOSCOPE at £234 (inc. p&p and VAT) *

AN Alpha III DIGITAL MULTIMETER at £99.00 (inc. p&p and VAT) *

I enclose
CHEQUE * POSTAL ORDER * CASH *

for the amount of £ _____

Or please charge my Access *

Barclaycard *

Account for the amount of £ _____

MY ACCOUNT NUMBER IS

Signature _____ (I am over 18)

Surname _____

Initials _____ (Mr/Mrs/Miss)


Address _____

Postal Code _____ (PE3)

*Tick which appropriate Block Capitals Please

Note: This offer applies to the U.K. and Ireland only.

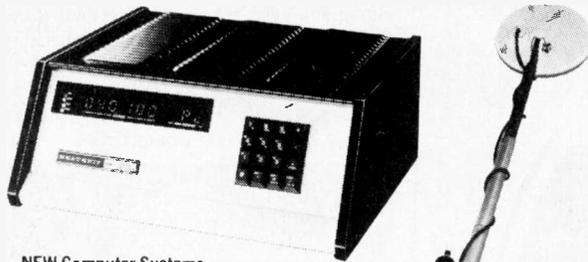
You'll learn a lot from the Heathkit catalogue.




NEW Computer Systems
Send for a special 16 page brochure.



NEW Bi-directional RF Wattmeter

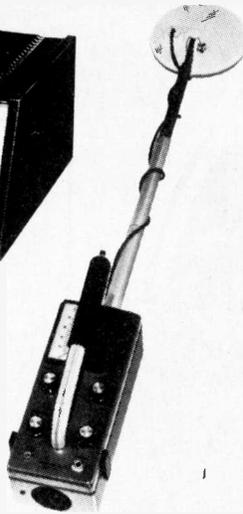

NEW De-luxe Coin-tracking Metal Locator

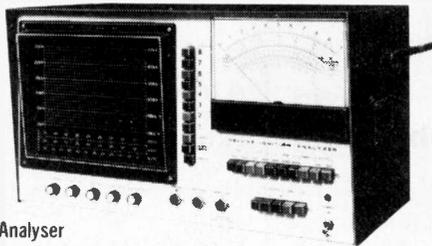

NEW De-luxe 12" CRT Ignition Analyser

The Heathkit catalogue is packed with scores of top quality electronic kits. Educational, practical and fascinating items which you can build yourself.



Send for the catalogue now.

To Heath (Gloucester) Limited,
Department PE9B Bristol Road,
Gloucester, GL2 6EE. (Registered number 606177)

Name

Address

Please tick the literature you want and enclose the appropriate amount in postage stamps.

Heathkit catalogue only (enclose 20p).

16 page computer brochure only (enclose 20p).

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest catalogue without having to use this coupon.

Soldering iron offer FREE

When you receive your catalogue you'll get details of this free offer worth approximately £4.75.

HEATH Schlumberger
The world's biggest producers of electronic kits.

ACCESS AND BAR/CARD WELCOMED

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (Gloucester 29451).

The better catalogue

IT CAN SAVE YOU POUNDS!

Stirling Sound

Modules - power amps 3 to 100 watts R.M.S., power supplies, control units, etc. - electronic ignition for your car - D.I.Y. disco/P.A. - bargain disco assemblies - plenty to choose from with technical gen, diagrams and good instructions. Send only 20p for postage and handling for your copy by return. You can't be without it!



Audio and Electronic Eq

SEND FOR YOURS NOW

Stirling Sound

Dept. PE 9, 37 VANGUARD WAY,
SHOEBURYNESS, ESSEX. Phone (03708) 5543
Shop & Showroom (personal callers only)
222-224 West Road, Westcliff-on-Sea.
Phone: Southend (0702) 35-1048.

ASTRA-PAK

92 GODSTONE ROAD
WHYTELEAF SURREY CR3 0EB

All prices include V.A.T. Add 25p for P&P (Extra for overseas). Discounts over £10 less 5%, over £20 less 10%, over £50 less 15%, over £100 less 20%. Send SAE for complete list of components.

7400	0.12	7482	0.44	74181	1.92	74LS75	0.45	74LS293	0.90	4052	0.84
7401	0.12	7483	0.40	74182	0.75	74LS76	0.32	74LS298	1.60	4053	0.84
7402	0.12	7484	0.80	74183	1.20	74LS78	0.32	74LS352	0.82	4054	1.10
7403	0.12	7485	0.54	74185A	1.20	74LS83	0.78	74LS353	1.05	4055	1.00
7404	0.13	7486	0.60	74186	7.20	74LS85	0.90	74LS365	0.50	4060	0.98
7405	0.13	7487	2.38	74188	2.70	74LS86	0.35	74LS366	0.50	4066	0.48
7406	0.28	74100	0.94	74190	1.05	74LS93	0.95	74LS367	0.50	4067	3.50
7407	0.28	74104	0.40	74191	0.95	74LS95	1.10	74LS368	0.50	4068	0.24
7408	0.14	74105	0.40	74192	0.95	74LS107	0.36	74LS368	0.37	4069	0.12
7409	0.14	74107	0.28	74193	1.05	74LS109	0.36	74LS368	0.37	4070	0.17
7410	0.13	74109	0.45	74194	0.90	74LS112	0.38	74LS670	2.00	4071	0.17
7411	0.18	74110	0.46	74195	0.84	74LS113	0.36			4072	0.17
7412	0.21	74111	0.70	74196	0.90	74LS114	0.36	4000	0.14	4073	0.17
7413	0.25	74116	1.60	74197	0.90	74LS123	0.82	4001	0.15	4075	0.17
7414	0.54	74118	0.82	74198	1.48	74LS124	2.45	4002	0.16	4076	1.05
7415	0.27	74119	1.30	74199	1.48	74LS125	0.44	4006	0.92	4077	0.48
7417	0.27	74120	0.82	74221	1.50	74LS126	0.44	4007	0.16	4078	0.22
7420	0.13	74121	0.25	74273	2.15	74LS132	0.69	4008	0.92	4081	0.17
7421	0.28	74122	0.40	74279	1.25	74LS136	0.40	4009	0.45	4082	0.20
7422	0.17	74123	0.53	74283	1.70	74LS138	0.53	4010	0.48	4085	0.72
7423	0.25	74125	0.44	74284	6.85	74LS139	0.53	4011	0.15	4086	0.76
7425	0.20	74126	0.45	74293	1.35	74LS125	1.05	4012	0.16	4089	1.55
7426	0.25	74128	0.62	74298	1.92	74LS153	0.50	4013	0.42	4093	0.65
7427	0.25	74132	0.68	74390	1.92	74LS154	1.20	4014	0.80	4094	1.80
7428	0.34	74135	0.68	74393	2.12	74LS155	0.86	4015	0.77	4095	1.10
7430	0.13	74136	0.75			74LS156	0.86	4016	0.42	4096	1.10
7432	0.24	74137	0.94			74LS157	0.47	4017	0.77	4097	3.50
7433	0.32	74141	0.58	74LS00	0.19	74LS158	0.53	4018	0.87	4098	1.12
7437	0.24	74142	2.00	74LS01	0.19	74LS160	1.22	4019	0.42	4099	1.90
7438	0.24	74143	2.00	74LS02	0.19	74LS161	0.69	4020	0.92	4404	1.00
7440	0.13	74144	2.00	74LS03	0.19	74LS162	1.22	4021	0.82	4412	0.30
7441	0.52	74145	0.64	74LS04	0.20	74LS163	0.69	4022	0.82	4428	0.80
7442	0.55	74147	1.30	74LS05	0.20	74LS164	1.20	4023	0.15	4445	1.50
7443	0.90	74148	1.18	74LS08	0.19	74LS168	2.00	4024	0.68	4449	0.30
7444	0.90	74150	0.99	74LS09	0.19	74LS169	2.00	4025	0.15	4501	0.17
7445	0.70	74151	0.60	74LS10	0.19	74LS170	1.76	4026	1.28	4502	0.88
7446	0.70	74153	0.60	74LS11	0.19	74LS173	1.05	4027	0.50	4507	0.50
7447A	0.64	74154	1.05	74LS12	0.19	74LS174	1.12	4028	0.67	4508	2.25
7448	0.60	74155	0.63	74LS13	0.48	74LS175	1.05	4029	0.88	4510	1.05
7450	0.13	74156	0.63	74LS14	1.10	74LS189	2.85	4030	0.15	4511	0.84
7451	0.13	74157	0.63	74LS15	0.19	74LS190	0.81	4031	2.34	4512	0.92
7453	0.13	74159	1.70	74LS20	0.19	74LS191	0.81	4033	1.26	4514	2.85
7454	0.13	74160	0.80	74LS21	0.19	74LS192	1.80	4034	2.00	4515	2.80
7460	0.13	74161	0.80	74LS22	0.19	74LS193	1.80	4035	1.00	4516	1.02
7470	0.28	74162	0.80	74LS26	0.24	74LS195	1.12	4036	2.40	4518	0.99
7472	0.22	74163	0.80	74LS27	0.40	74LS196	1.20	4037	0.59	4519	0.50
7473	0.20	74164	0.89	74LS30	0.19	74LS197	1.26	4038	1.00	4520	1.05
7474	0.26	74165	0.89	74LS32	0.25	74LS221	1.12	4039	2.80	4521	2.00
7475	0.30	74166	0.99	74LS37	0.27	74LS247	0.97	4040	0.88	4522	1.35
7476	0.26	74167	2.70	74LS38	0.27	74LS248	0.97	4041	0.77	4527	1.60
7480	0.45	74170	1.68	74LS40	0.19	74LS249	0.97	4042	0.72	4528	0.92
7481	0.90	74172	4.00	74LS42	0.53	74LS251	1.00	4043	0.82	4529	1.10
7482	0.80	74173	1.18	74LS47	0.97	74LS253	1.05	4044	0.52	4536	3.56
7483	0.72	74174	0.89	74LS48	0.97	74LS257	1.05	4045	1.40	4553	4.20
7484	0.90	74175	0.88	74LS49	0.97	74LS258	1.05	4046	1.32	4555	0.85
7485	0.88	74176	0.88	74LS51	0.19	74LS266	0.39	4047	0.96	4556	0.85
7486	0.26	74177	0.88	74LS54	0.19	74LS273	2.50	4048	0.80	4558	1.25
7489	2.00	74178	1.20	74LS55	0.20	74LS279	0.50	4049	0.42	4566	1.40
7490	0.35	74179	1.10	74LS73	0.10	74LS283	1.00	4050	0.42	4569	0.75
7491	0.65	74180	0.90	74LS74	0.34	74LS289	2.85	4051	0.84	4585	1.03

Market Place

Items mentioned are usually available from electronic equipment and component retailers. However, where a full address is given, general enquiries may be made direct to the firm concerned.

All quoted prices are correct at time of going to press.

by
**Alan
Turpin**

and
**David
Shortland**


VERO ELECTRONICS AND VEROSPEED

Vero Electronics make a range of housings and passive components for the construction of electronic equipment, much of it allied to computer assembly. The range includes: circuit and breadboards, microprocessor boards, card frames, module racks and cases, wirewrapping tools and wire, connectors—direct/indirect/coaxial, Scotchflex cable/connector system, busbars, pin bars, backplane boards, fan units.


Verospeed is a service which specialises in the rapid supply of regularly required components: boxes, cases, Veroboard (up to 454mm x 179mm), 2mm plugs and sockets, terminal pins, d.i.l. sockets, standoffs, switches, precision resistors/trimmer pots, miniature capacitors, p.c.b. etching packs, standard and sub. min. toggle switches. Orders received up to 3pm are despatched the same day.

Catalogues are available from both divisions.

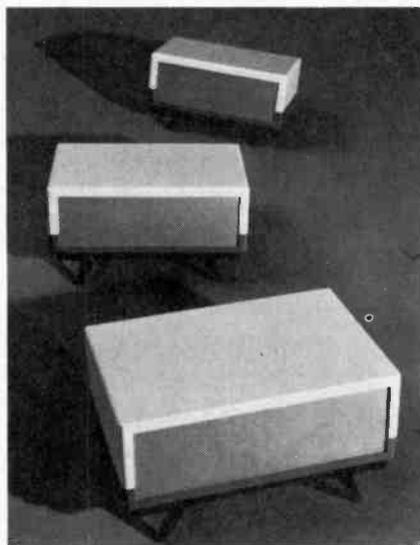Vero Electronics Ltd., Industrial Estate, Chandlers Ford, Hants SO5 3ZR. (042 15) 69911.
Verospeed, Barton Park Industrial Estate, Eastleigh, Hants. (0703) 618525.



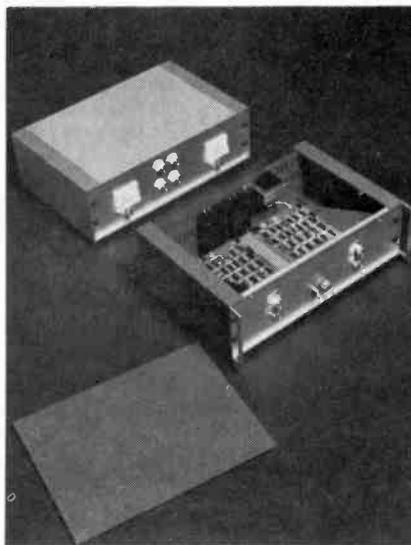Tilt leg assembly enabling type A and type C Veroboxes to be canted at a comfortable viewing angle for displays, at 62p and 82p per kit. From Verospeed.




Top access version of Vero D series instrument case; two screws gain access; multiple front panel fixing and four optional colour finishes. By Vero Electronics.

DIAL A BOX

If you want to house a project in an aluminium case but are not too neat with the Gilbows (tin shears) then this service may appeal to you.

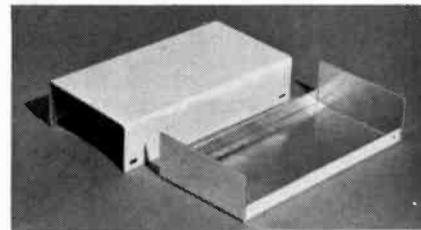Custom made, pin seal vinyl coated project boxes are available with next to immediate delivery from Cannon Components.



Starting at the minimum size of a one inch cube, any size of box can be made up to a maxima of 13 x 8 x 3 inches. Price guide from small boxes to large is 65p to £3.50, including postage.

The boxes may be painted with vinyl or cellulose paints which bond well to the vinyl pin seal coating.

Cannon Components, 322 Whitehorse Rd, Croydon, Surrey CR0 2LF (01-684 9872).

A NEW PROM

What is believed to be the world's first 16K PROM to go into production was recently announced by Signetics. This new addition to their range of industry standard PROMs is available only in sample quantities at present, to allow designers to evaluate the new PROM and demonstrate its cost effectiveness. Production, capable of meeting full-scale demand, is planned for 1979.

Designated the 82S190/191 the chip itself measures only 4.7 x 5.8mm, which is only 40 per cent larger than the 8K PROM! Manufacturing process is the standard diffused isolation, nichrome fuse system utilising dual-layer aluminium interconnect. Its access time is guaranteed at 80ns (60ns being typical), which is almost as fast as its 8K counterpart.

Using a bit of ingenious technology, Mullard have kept the power dissipation the same as the 4K and 8K PROMs, which is 925mW maximum (650mW being typical). The major problem overcome here was that array power would increase proportionately to the total number of rows and columns in the array. To allow size to be kept down without temperature going up, due to current consumption in the internal decoder circuitry, a technique called "power predecoding" has been used. The 128 rows of the array are predecoded into 16 blocks of 8 rows each, and only one block is powered up at any given time. A similar approach is used in the 128 columns, where a 1:16 decode is required for each of the eight outputs. The circuit is split into two 1:4 predecoding sections resulting in a further substantial reduction in power consumption.

With the addition of one TTL inverter, four 82S191s can be wired together to make up an 8K x 8 PROM, or provide two additional bits of addressing capability. Since the device outputs are tri-state, giving high Z when not selected, all four PROMs can be simply wire ORed together.

Details from Mullard Ltd., Mullard House, Torrington Place, London WC1E 7HD.

BYTE FROM THE APPLE

There is no longer doubt that minicomputers will eventually become an accepted part of everyday life at work *and at home*.

For teaching, such subjects as mathematics, physics, and even history (why not?), perhaps these machines will become the *interactive* text book of the future.

For entertainment, games are unlimited and can be as much fun to invent as to play.

However, not every potential user likes to dab around with a soldering iron; hence the trend towards the complete package personal computer. Another one of these has marched onto the scene: Apple II. The size of a portable typewriter, this personal computer built around the 6502 micro has a machine monitor with dis-assembler and mini-assembler, with optional 6K Basic available from plug-in PROMs.

The full ASC11 typewriter style keyboard is "beefy" enough for *real* fingers, and direct colour TV interface means you can plug it into yours, or anyone else's television set, via the aerial socket. It also interfaces to your cassette recorder for dumping programs into permanent storage.

Video games are no fun unless you get plenty of noise (engines roaring and bombs going off etc), and for this purpose a built-in loudspeaker is provided. You can also use Apple II as a music synthesiser. There are eight connectors for most peripherals such as a hard copy printer, or jacking into the Post Office Viewdata service (one computer talking to another!!!).

Where there are input and output ports, and *some imagination*, there is always need of a soldering iron. So, if you are an amateur of practical leaning, there is still plenty of scope for experiment.

The computer is powered by a switching type power supply (screened they hasten to add) for less weight to hump around—*after*



all it is supposed to be portable.

Incidentally, to aid ball type video games, paddles are included. With four analogue inputs, and a memory that can be displayed as either text, colour graphics (15 colours), or high resolution graphics, all modes being software selectable, the machine lends itself to interesting video game possibilities.


The high level language is a fast translated BASIC allowing multiple statements on one line, syntax and range errors being indicated immediately when entered. Integers from -32767 to +32767. String arrays up to 255 characters. Memory boundary adjust (does not destroy current program). Break and continue program execution. Debug commands are line number trace and variable trace.

DMA facilities are PEEK, POKE and CALL commands.

The technical details go on too long for Market Place, but for a case measuring 387 × 457 × 113mm, the contents are pretty powerful with BASIC plugged in (and a TV of course!). The display format gives 24 lines of 40 characters.

Some prices. Apple II with 4K bytes of RAM will set you back £995, and is available with memory increments up to 48K bytes of RAM at £1,900. The printer costs £100, and the Applesoft BASIC cassette tape will cost you £20.

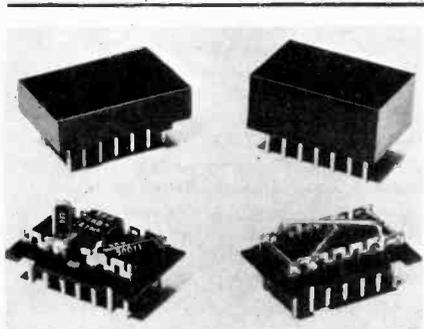Further details from **Topmark Computers, 77 Wilkinson Close, Eaton Socon, Huntingdon, Cambs PE19 3HJ.**



D.I.Y. D.I.L.

Make up your own dedicated devices on these skeletal d.i.l. packages. Ideal for plugging in a series of timing constants; personal code keys; program addressing.

The low profile snap-on covers are a tight fit enabling the pack to be encapsulated. Two covers are available at 5.7mm or 8.9mm height.

On each row, all seven terminals are manufactured linked and individual disconnections are made using only wire cutters.



The Dipack 14 is available in quantities of ten for £3.50 from **Erg Industrial Corp. Ltd., Luton Road, Dunstable, Beds LU5 4LJ.**

BREADBLOC

A compact breadboard system ideal for design and testing is now available from Lascar Electronics.

The unit has both a +5V 1,000mA power supply and dual tracking outputs adjustable between ±5V and ±15V at 100mA per rail. Both supplies are isolated from earth and each other.

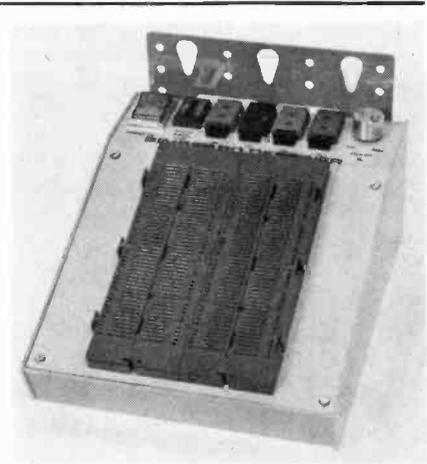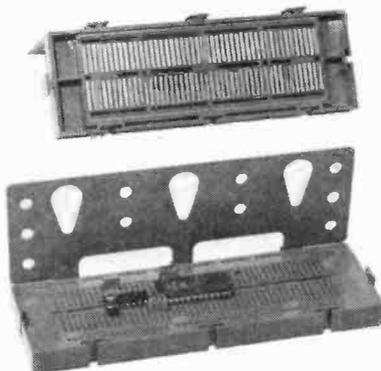The system enables most digital, linear, bipolar and CMOS circuitry to be accommodated on its 0.1in matrix board which contains 47 rows of 5 interconnected



contacts and two continuous contact rows for the power supply rails.

The system is available with one or two boards at £39.96 and £47.95 respectively or one breadboard alone can be obtained for £7.99. To enable designers to construct a unit to suit their own power supply requirements the case itself can also be purchased for £4.48.

For further information contact **Lascar Electronics, P.O. Box 12, Second Avenue, Billericay, Essex.**



DIGITALS

Details of the watches above are, from left to right, as follows:


1) LLED/45, ladies l.e.d., date, stainless steel case and strap, £9.50. 2) LLCD/3S, ladies l.c.d., cocktail bracelet, stainless steel, fully adjustable, date, £26.50. 3) LCCRO1, l.c.d., chronograph, American electronics, six digit, net/lap/place times, back light, stainless steel, water resistant, £20.56. 4) and 6) GLCDB4, l.c.d. quartz, date, back light, American electronics, stainless steel, water resistant, £11.88. 5) Solar 1, operates without batteries even in subdued or artificial light, batteries fitted provide power at night for watch and back light, batteries charged by solar panel during the day; am/pm., date, polished stainless steel, £28.98. 7) LLCD8, ladies l.c.d., date, back light, stainless steel, water resistant, approx. size 18mm face x 8mm thick, £15.99. 8) LLED/43, as 1) but in gold or silver cocktail bracelet, £13.99.

All watches are available by post (add 50p for p&p) from Readers P.C.B. Services Ltd., P.O. Box 11, Worksop, Notts.

SINCLAIR MULTIMETER

The latest digital multimeter available from Sinclair Radionics is the DM 235. The design is a direct development of their DM 2 and is a five function 21 range $3\frac{1}{2}$ digit unit which has an additional five test ranges for diodes.

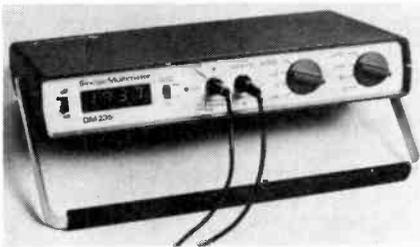The DM 235 is designed for both bench and field work and has a basic accuracy of 0.5 per cent on its d.c. voltage range of 1mV to 1,000V, 1.5 per cent on its a.c. voltage range of 1mV to 750V, 1.0 per cent on its d.c. current and 1.5 per cent on its a.c. current ranges of 1µA to 1A and a basic accuracy of 1.0 per cent on its resistance range of 1Ω to 20MΩ.




The unit is very light—less than 1½lbs—and measures 255 x 148 x 40mm. It is powered by four dry cell batteries and optional extras include a rechargeable battery pack, carrying case and a 30kV probe.

The price of the DM 235 is £49.80 plus VAT. For further details contact Instrument Division, Sinclair Radionics Ltd., London Road, St. Ives, Huntingdon.

SOMBRE SCOPE

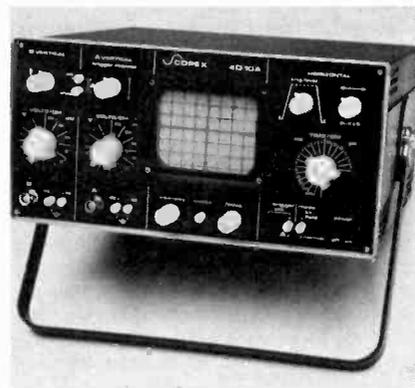Black will be the season's fashion colour for oscilloscopes. This is the pronouncement of Scopex who carried out a European marketing survey earlier this year. They were surprised to find that, while turquoise casings with white front panels were the popular twin-set colours in 1976, continental engineers are all for black gear now.




The black 4D10A dual trace scope, at £180, still retains the characteristics of the 4D10; stabilised power supplies in both the low voltage areas and e.h.t. allowing mains variation of as much as ten per cent. Accuracy on both time and voltage measurements is three per cent.

Scopex Sales, Pixmore Avenue, Letchworth, Hertfordshire SG6 1JJ.

LIGHT TOUCH

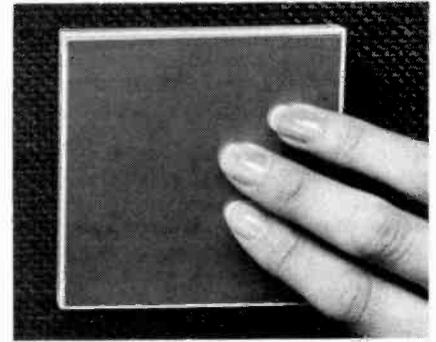The new touch dimmer control from Superswitch can be operated by a quick firm touch anywhere on its front panel whilst a long touch will vary the light output at a pre-set rate. To complete a full cycle from bright to dim and back to full brilliance again takes approximately six seconds.



A subsequent long touch will alter the light level in the reverse direction and removing the hand from the control during the cycle will establish the light level.

Further switching on and off will not alter the selected brilliance and thus the control acts as a pre-set dimmer.

A number of slave units can be used with a master to enable two way and multi switching to be obtained.

The price of a Master unit is £11.60 and a Slave unit is £4.50. For further details contact Superswitch, 7 Station Trading Estate, Blackwater, Camberley, Surrey.

FOURTH BATCH

Scruppy is a crude cider, but John Miller-Kirkpatrick's Scruppi seems to become more refined with each brew. Scruppi 4 offers the following features: 1K RAM + 7K expansion sockets (2114), 8K expansion PROM sockets (2708/16), an additional socket for 2K/4K ROM, a socket for 8K ROM, an 8-bit bidirectional I/O port, a cassette interface option, a 2708 programmer option, and on-board voltage regulators. But new is the 4K ROM containing BASIC!

Up to personal computer standard, this SC/MP-2 based MPU is supplied with the ROM ready to speak NIBL (National Industrial BASIC Language) which requires the 1K of RAM capacity to operate. The price of the Scruppi 4 basic system p.c.b. is £150.

As part of the deal you get the circuit for a PROM programmer, and components for this are available as an add-on pack. An interface is provided to any 20mA loop TTY device (which could be Scruppi 3!), whereby all main I/O commands are processed by the NIBL ROM.

A fully extended Scruppi 4 could have 16K RAM plus 16K ROM/PROM, or 8K RAM plus 24K ROM/PROM. Bywood Electronics can support their MPU kits with education facilities and a good range of i.c.s for interfacing with the outside world. A set of books for beginners, called Microsense (complete with cartoons), is available from Bywood, and are given away free with all Scruppi kits.

More from Bywood Electronics, 68 Ebbens Road, Hemel Hempstead, Herts HP3 9QR.

Strictly Instrumental

by K. Lenton-Smith

Organ "nuts" are often mentioned on *The Organist Entertains*, a good example being the case of Stephen Capaldi. According to a recent newspaper report, he said he had been let down by women so often that his third marriage would be to his £8,000 organ. The vicar of St. Paul's, Gloucester, had agreed to perform a service blessing this organ and, at the climax of the service, Mr Capaldi had planned to play his favourite piece "Don't Cry For Me Argentina". However, the vicar, cancelled the service when he heard that it was to be regarded as a wedding ceremony. So another sorry chapter was added to his love life!

At least he tried to be different—but a far better approach would be to consider the latest electronic music i.e. to be announced by Signetics. A frequent complaint in this column is that basic circuit principles have remained unchanged for several decades, counting aside miniaturisation. The TDA 1008 is no exception, but its design is such that it is destined to become an extremely popular device. This extended article will be devoted to looking at some of the many features it offers.

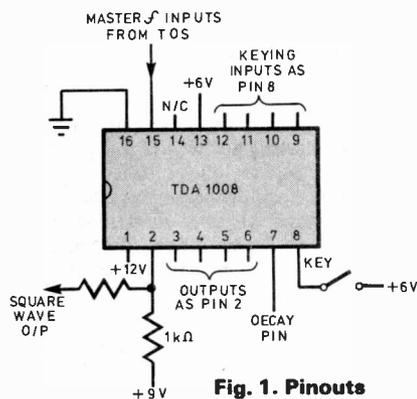


Fig. 1. Pinouts

OUTPUT PINS	8	9	10	11	12
2	f*	f/2	f/4	f/8	f/16
3	f/2	f/4	f/8	f/16	f/32
4	f/4	f/8	f/16	f/32	f/64
5	f/8	f/16	f/32	f/64	f/128
6	f/16	f/32	f/64	f/128	f/256

* f = master frequency from TOS

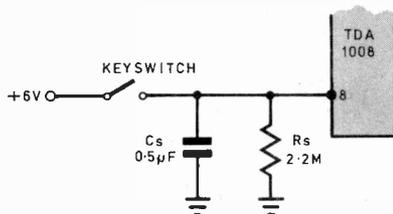



Fig. 2. Sustain mode

TDA 1008 Based on integrated injection logic, this monolithic bipolar device produces square wave output voltages that are symmetrical about a given d.c. voltage, thus overcoming key click problems. It can be driven directly by a Top Octave Synthesiser (TOS) and applies this signal to an internal chain of eight bistable dividers. The nine resulting frequencies are matrixed with nine gates so that each of five keying inputs can select a different combination of five successive octaves.

Bistable divider i.c.s have been in existence for a good many years, and gating i.c.s, but the TDA 1008 combines both functions in a 16 pin package, with the added advantages of TOS drive and ability to control the envelope widely. Assuming a single manual instrument was required, this could now consist of 13 i.c.s (TOS and 12 x TDA 1008), tone forming and amplification; a single keyswitch would control its five pitches.


Three positive supply voltages are required (6, 9 and 12V), the supply current being some 13mA with all keys activated. Keying input impedance is greater than 8MΩ and the input frequency can be up to 100kHz if required. Fig. 1 gives pin connections for the device, which will be seen to have five keying inputs (pins 8 to 12), five outputs (pins 2 to 6), and a Decay pin (pin 7). Fig. 1 shows the truth table.

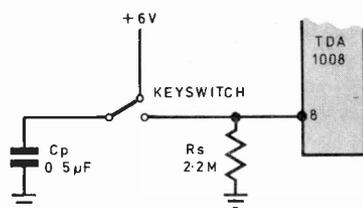Master frequencies from the TOS are applied to pin 15, the truth table indicating the effect of keying various inputs. Using a 5 octave keyboard, pin 8 of the twelve TDA 1008s would be used to key the top octave, pin 9 for the next, etc. In its simplest form,



keying is achieved by supplying +6V through a keyswitch. Signal output voltage is proportional to keyed input voltage, whilst multiple inputs produce sum signals. Unused outputs should be connected to +6V to avoid intermodulation, though all five will normally be in use.

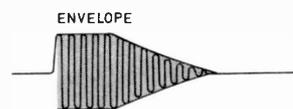SUSTAIN The simple keying of Fig. 1 is not pleasing musically, as attack is immediate and decay non-existent. Adding a Sustain capacitor Cs and Sustain resistor Rs will cause the output to die away gradually, as shown in Fig. 2.



Because Cs is charged when the playing key is depressed, a resistor could be inserted between the 6V supply and keyswitch if there is any tendency for the key contacts to spark. This situation would probably be abnormal, but such a resistor could be chosen to imitate the slower attack of a pipe organ. The desired time constant RC could be calculated (where C = Cs).

DECAY Overall control of Decay is by means of pin 7, where all twelve pins are commoned and provided with a small variable voltage. Fig. 3 suggests a method of obtaining the Decay voltage from the 6V line (variable between 0.7V and 2.5V) which will control Sustain period across the manual. See Fig. 3.

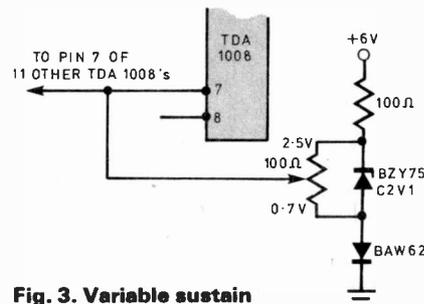


Fig. 3. Variable sustain

PERCUSSION If a changeover keyswitch is employed so that +6V keeps a Percussion capacitor Cp charged in "key up" mode, depressing the playing key will allow Cp to discharge through the input gate. Rs provides sustain as before, the principle being shown in Fig. 4.

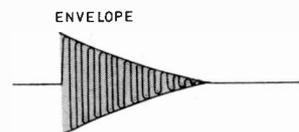


Fig. 4. Percussion

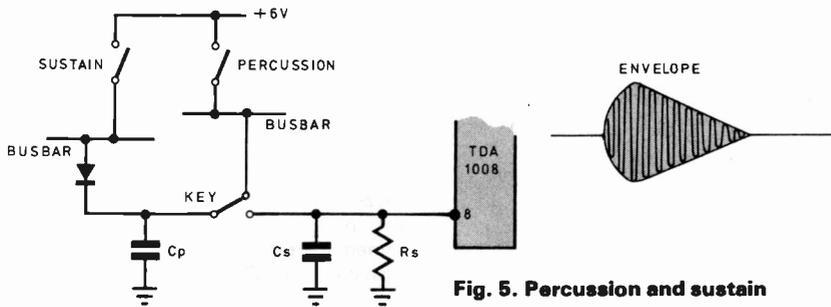


Fig. 5. Percussion and sustain

A combination of Percussion and Sustain is shown in Fig. 5. One capacitor now loads the other, so that staccato playing will produce a larger output than legato. Because the TDA 1008 gives an output voltage that is proportional to the input, we now have *touch-sensitivity*. The effect is similar to an acoustic piano with "loud" pedal in operation.

There are a number of possible variations on this theme. Joining the earthy ends of several Cs together, though not actually earthing them, will cause other gates to open momentarily. This effect may be switched out by earthing the common Cs point. If the seventeenth interval (or 29th note higher) is coupled in this fashion, *chiff* can be produced.

DAMPER ACTION Unless the "loud" pedal of an acoustic piano is pressed, the string is damped as the key is released. To imitate this effect, three more components may be added to the input circuitry, as shown in Fig. 6. Here we require percussion with decay that falls to zero. On releasing the key, the 6V supply is pulsed through Ck, making the transistor conduct briefly and so discharge Cs. The time constant RkCk is sufficient to prevent the transistor conducting if the playing key is struck repeatedly.

QUINT The gate of one TDA 1008 may be controlled by a different chromatic playing key if mutations are required. Fig. 7 shows the method for obtaining a Quint. If F is keyed, C will sound when 6V is supplied to the isolating transistor. The Quint, or other mutation, will still be subject to Sustain and Percussion as before.

Although the proportional nature of input to output voltages has been mentioned, 6V should be regarded as the maximum for the

Percussion busbar. Failing this precaution, gates other than those actually keyed could open. Aside from this warning, the possibilities for envelope control are legion. These brief circuit details may serve to give some idea of the flexibility of the TDA 1008.

OUTPUTS The square wave signals could be rounded off individually by low pass filters, and applied to drawbars for an *additive* harmonic synthesis system. With this in view, it is essential to filter individual frequencies rather than trying to filter the mixture from the drawbar busbars.

With *subtractive* tone forming, the best starting point is a sawtooth waveform, containing both even and odd harmonics. A staircase waveform is a close approximation to sawtooth and is obtained by mixing octave related square waves in given proportions. The resistive network of Fig. 8 shows how to apply this principle for feeding subtractive filters. Compared with Fig. 1, alteration has been made in the value of load resistors, and the output pins are now resistively coupled together.

Fig. 7. Mutations


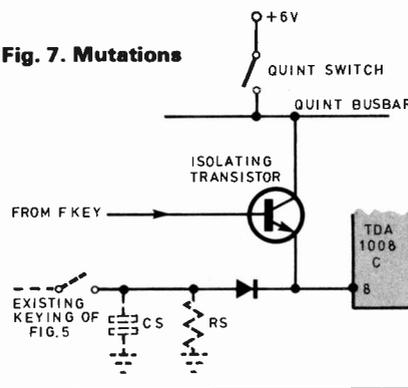


Fig. 6. Damper action

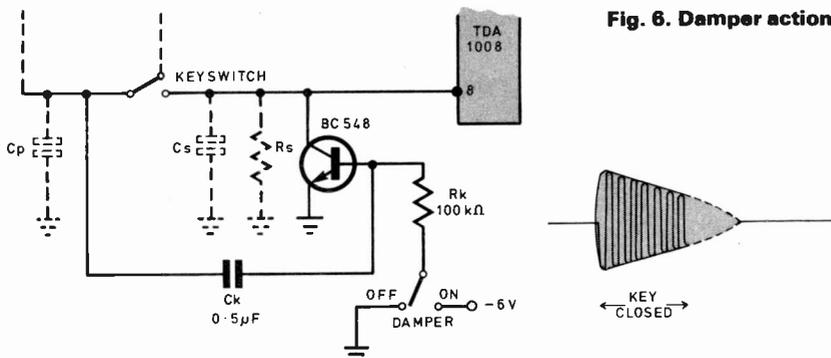

APPLICATIONS The many features of TDA 1008 would appear to make it ideal for the rhythmic player. Organ tones would be available on an electric piano and vice versa.

Before serious musicians dismiss this device as just another gadget for popular music, it should be noted that the only commercial organs made using the TDA 1008 to date are strictly *classical*. Details of this i.c. have been released to the press only within recent weeks but *Electroponic Organs* of 56 Bedford Place, Southampton, have been building instruments to customers' specification using this device for some time. First in this field, their price list quotes a typical three manual organ, classically voiced and with mutations, at £2,865; eight sets of twelve TDA 1008s are used. This firm will be pleased to quote for a given specification, their telephone number is 0703 21265.

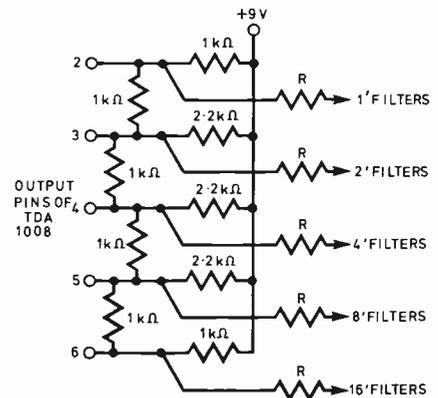


Fig. 8. A method for staircasing the output pitches as an alternative to square waves produced by the simple arrangement in Fig. 1

COST This article will have made it clear that a set of twelve TDA 1008s will have 60 gates in all, to cover one five octave manual (with top C breaking back). The second manual will require a further set and, for the small additional cost of another TOS for these, chorus effect is possible.

A single unit costs £2.90, whereas 25 off is at £2.32 per device. Although this may seem rather expensive compared with other i.c. systems, its versatility makes it an excellent proposition for anyone embarking on construction of a fully comprehensive instrument. Commercial firms will certainly opt for it increasingly because of the reduction in both interwiring and keyswitching it allows.

Ideally, the Pedal section requires a set of TDA 1008s to itself, though a monophonic system might be used here for the sake of economy. But if cost was not important, three sets per manual would allow a full range of pitches, including mutation stops, and form the basis of an excellent instrument. All in all, the TDA 1008 is bound to become an important part of the current generation of commercial and home-constructed electronic instruments.

ELECTRONIC COMBINATION LOCK


E.A. PARR B.Sc.

THIS article describes an electronic code lock suitable for door or cupboard. To gain entry a person has to dial up a four digit code on the key panel and press a push button. The four decade switches then have to be all returned to zero and the button pressed again. The lock will then open for a preset time.

This double entry on the switches ensures that the important first code *is not left set* on the switches after entry.

CIRCUIT DESCRIPTION

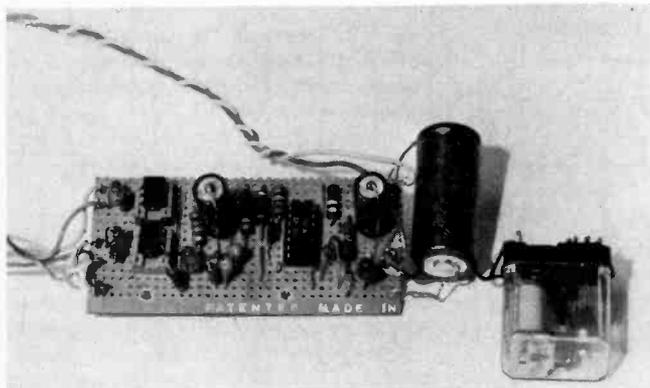The circuit is shown in Fig. 1 and the key panel is identified by the shaded area at the top of the diagram. The principle of the circuit is to detect current flowing from S4 to S1 on the first code, and from S1 to S4 on the second code. Diodes D1 to D6 on the coding board pass current when the correct code is set up.



As drawn, the first code is 4057, and D2, D4, D6 allow current to flow from the first code cable to S5. Similarly the second code is 0000; D1, D3, D5 allowing current to flow from S5 to the second code cable.

The code is set up on the red and black flying leads from the coding circuit board. Black leads set up the first code and red leads the second code. There are no restrictions on either code (except the least significant digits cannot be the same), and the codes can be easily changed.

The supply for the currents through the switches is derived from a $\pm 15V$ supply and S5 applies the centre common. The current flows through opto-isolators IC1 and IC2 which pass the signals to the remainder of the electronic circuit. Opto isolation was considered advisable in view of the likely distance between the key panel and the electronics box. Thus IC1 is energised for a successful first code and IC2


for a successful second code. D9 and D10 are in the current paths for each code, and are useful for checking the operation of the key panel. IC3 is a dual timer, with circuit (a) connected as a monostable with a period of 30 secs and circuit (b) as a monostable with a period 10 secs.

The correct first code fires IC3(a) via the filter R1, C2 and R4. The output of IC3(a) is connected to the reset of IC3(b) (pins 5 and 10 linked). IC3(b) is thus normally inhibited but can now be triggered. The correct second code now fires IC3(b), operating the lock solenoid via RLA contacts. Note D7 in series with RL1 coil as well as the usual diode (D8) across it. This is necessary with 555 timers, because the $-0.8V$ at the coil as D8 clips the back e.m.f. can cause re-triggering problems.

After 30 seconds IC3(a) times out and the reset signal is applied again to IC3(b). It is therefore necessary to reset the code and open the door within 30 seconds of setting up the first code *or you have to start again*.

The power supply is straightforward. The 12V supply for the 556 is obtained from an i.c. regulator (IC4), but note that for maximum noise immunity the $\pm 15V$ supply for the switches is floating, and is not connected electrically to the rest of the circuit. The two secondaries of 15V and 12-0-12V could, of course, be obtained from two independent transformers.

Any 10-way switches will suffice for setting up the unlock code. Although the author has used the type shown below, a cheaper alternative is to use wafer switches with the switch positions marked on the front panel. The push button switch S5 is shown adjacent to the code switches. S5 can be a miniature type

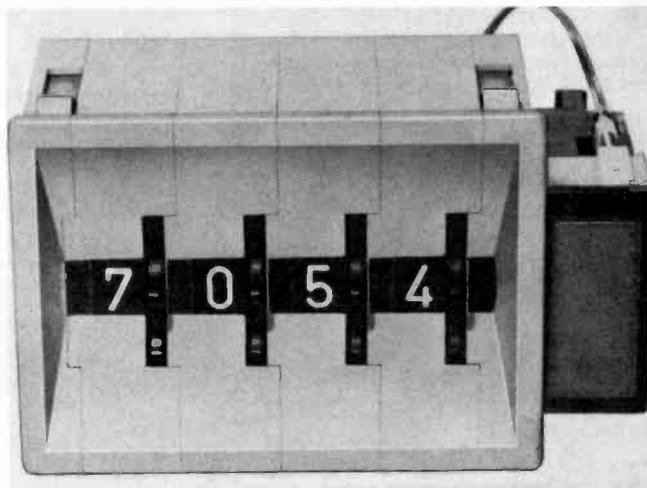

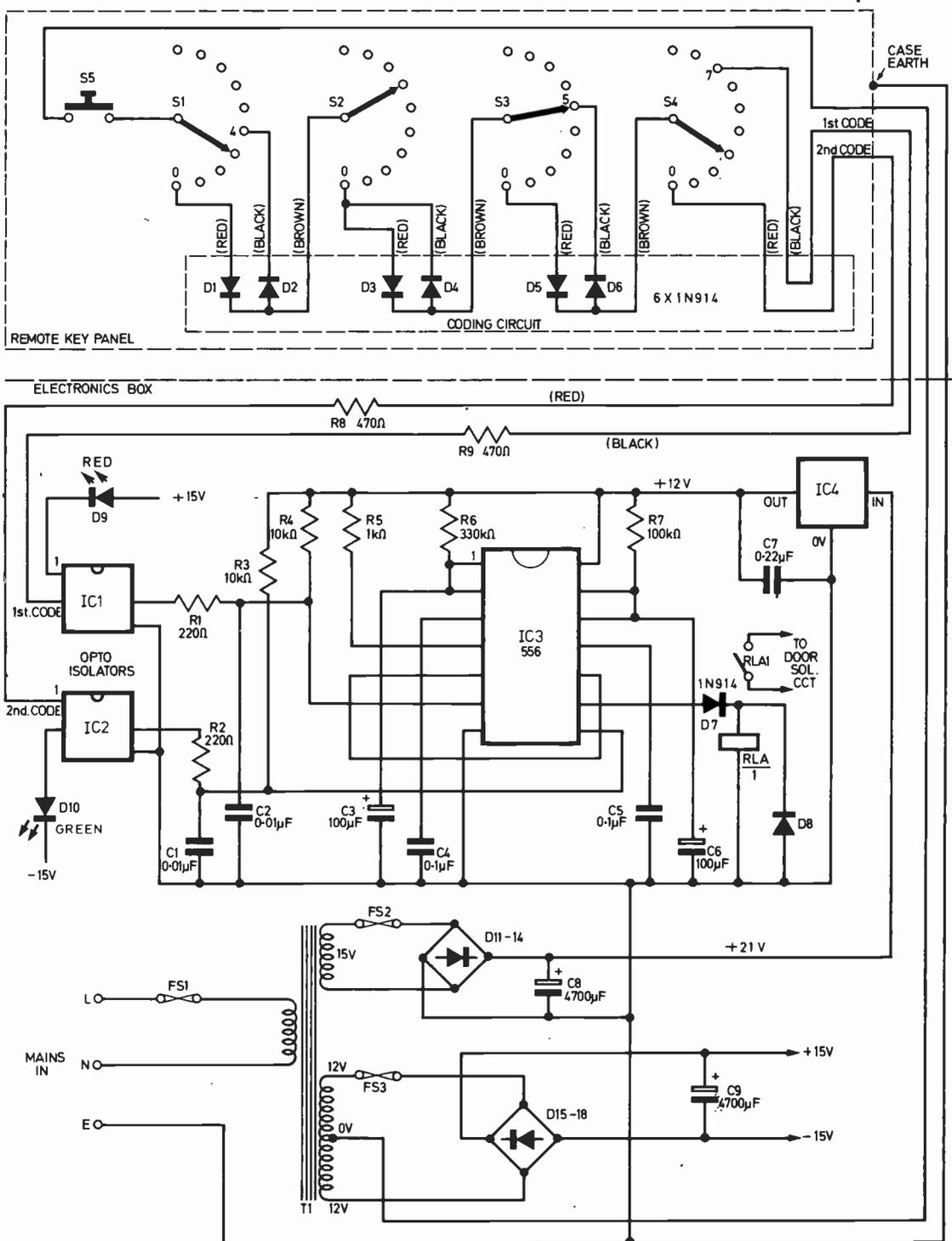


Fig. 1. Full circuit diagram including suggested power supply arrangement

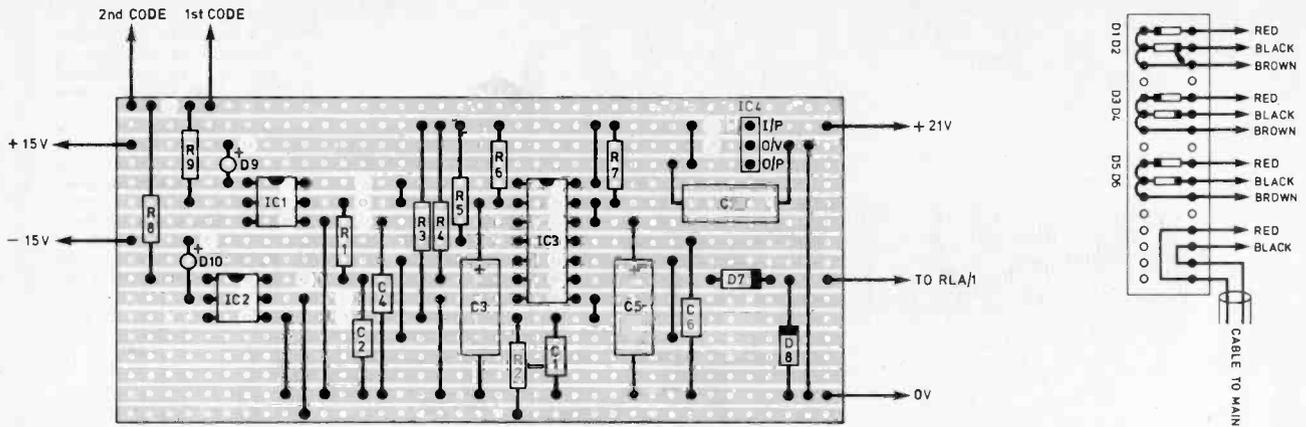


Fig. 2. Stripboard layout of the Combination Lock. The diodes D1 to D6 are mounted separately on a tag board which can be placed next to the code switches. The diode tag board is shown above right

COMPONENTS . . .

Resistors

R1, R2	220Ω (2 off)
R3, R4	10kΩ (2 off)
R5	1kΩ
R6	330kΩ
R7	100kΩ
R8, R9	470Ω ½W (2 off)
All resistors ¼W 5% except where stated.	

Capacitors

C1, C2	0.01μF (2 off)
C3, C6	100μF 25V elect (2 off)
C4, C5	0.1μF (2 off)
C7	0.22μF
C8, C9	4,700μF 40V (2 off)

Diodes

D1-D8	IN914 (8 off)
D9	0.1 in l.e.d. (red)
D10	0.1 in l.e.d. (green)
D11-14, D15-18	Rectifier stack 1A (2 off)

Integrated circuits

IC1, IC2	Opto-isolator (Maplin)
IC3	556 Dual timer
IC4	12V 1A Regulator. μA7812UC

Solenoid

240V operation (R.S: 349-478 is suitable)

Miscellaneous

S1-S4	Any type of numbered decade switch (4 off)
S5	Push button switch
RLA/1	12V relay with n.o. mains contacts.
T1	Mains transformer with 0-15V (1A) and 12-0-12V (100mA) outputs. (This can be two transformers)

CONSTRUCTION AND INSTALLATION

The circuit was constructed on Veroboard, the layouts being shown in Fig. 2. The code is set up using the red and black leads along the switch bank.

The unit consists of two boxes, the control box and the key panel. The control box can be any normal electronic case, but the key panel should be constructed with care if tampering is likely. For example, this box should be made so that its innards are accessible only from inside the building, or the lid fitted with Allen keys, then the Allen key holes drilled out to the lid can only be removed with a drill. If necessary the key panel box should be weatherproofed.

The door lock can be any 240V solenoid. Connection of the various units is shown in Fig. 3. Normal care should be taken with the solenoid connections to prevent danger of shock from the 240V mains.

Because of the simplicity of the circuit, testing is straightforward. The two l.e.d.s in series with the opto-isolators allow the correct operation of the key panel to be monitored. D9 should illuminate for a correct first code, and D10 for a correct second code.

One final word of warning: In case of component failure, always have a concealed standby means of opening the door. Even if this standby method is pretty inconvenient, you will have the peace of mind of knowing that should there be a power cut when you wish to gain access, you can get in one way or another. ★

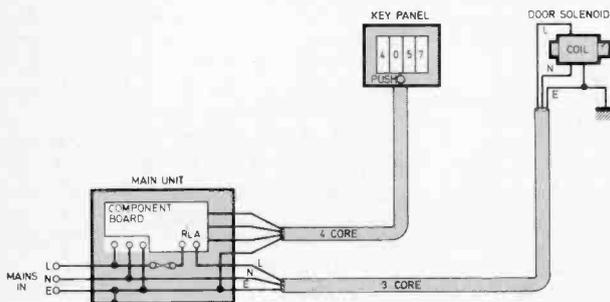


Fig. 3. Wiring diagram of solenoid circuit. Care should be taken when wiring up this mains portion of the system

ELECTRONIC COMBINATION LOCK

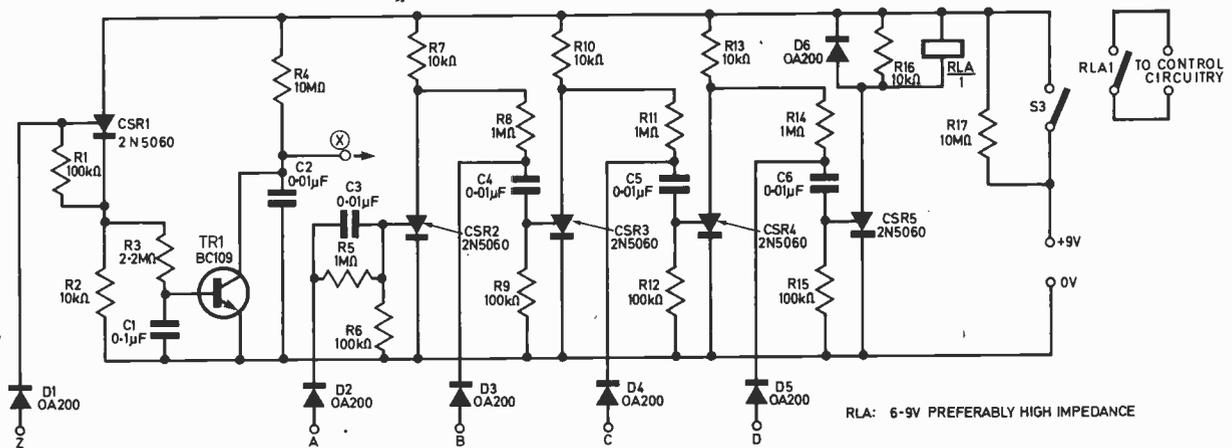


Fig. 1

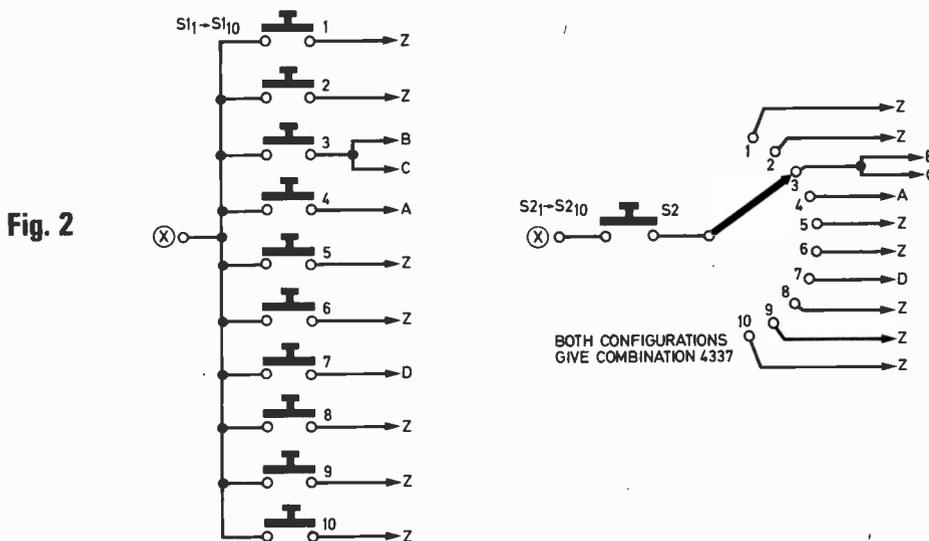


Fig. 2

THE circuit diagram of a 4 character electronic combination lock is shown in Fig. 1.

The character selector may take the form of a calculator type keyboard (Fig. 2), in which case the combination is entered simply by depressing the buttons in their correct order or, alternatively, the arrangement shown in Fig. 3 may be used, in which case the combination is entered by dialling and registering (by depressing S2) each character in its turn.

Basically the circuit operates by switching on a thyristor each time a character is registered. The triggering pulse is provided by C2 which is normally charged (via R4) to +9V. Initially the gate capacitors C4, C5, C6 are also charged to +9V, so any attempt to trigger CSR3,

CSR4, CSR5 (at points B, C, D) will be unsuccessful. By registering (at A) the first character of the combination, TR2 is switched on and its anode potential falls to about 0.7V. C4 rapidly discharges. A triggering pulse may now be applied to B, to turn on CSR3 which discharges C5 etc.

The circuitry to the left of C2, R4 hinders attempts to break the combination. If a wrong character is chosen, TR1 is turned on and this, after a short delay provided by R3, C1, to permit the thyristor to trigger properly, turns on TR1 which saturates; thus preventing further attempts to register characters until S3 is reset. D1 prevents a form of bistable action occurring between CSR1 and TR1.

The 2N5060 thyristor has a tabulated maximum holding current of 5mA. In

practice, a realistic typical figure is about 0.1mA; thus the 10kΩ anode resistors should be adequate.

These thyristors have particularly sensitive gates and gate-cathode resistors (100kΩ) are included to dampen the sensitivity. Diodes D2-D5 isolate the gates of those thyristors with a common character. All the diodes are included for convenience.

R17 is a trickle resistor to keep C4, C5, C6 topped up; thus preventing either CSR3, CSR4, CSR5 from being triggered when S3 is closed. R16 ensures that CSR5 switches on even if its load is highly inductive.

P. Hutchinson,
Brockenhurst,
Hants.

DISTORTION ASSESSMENT

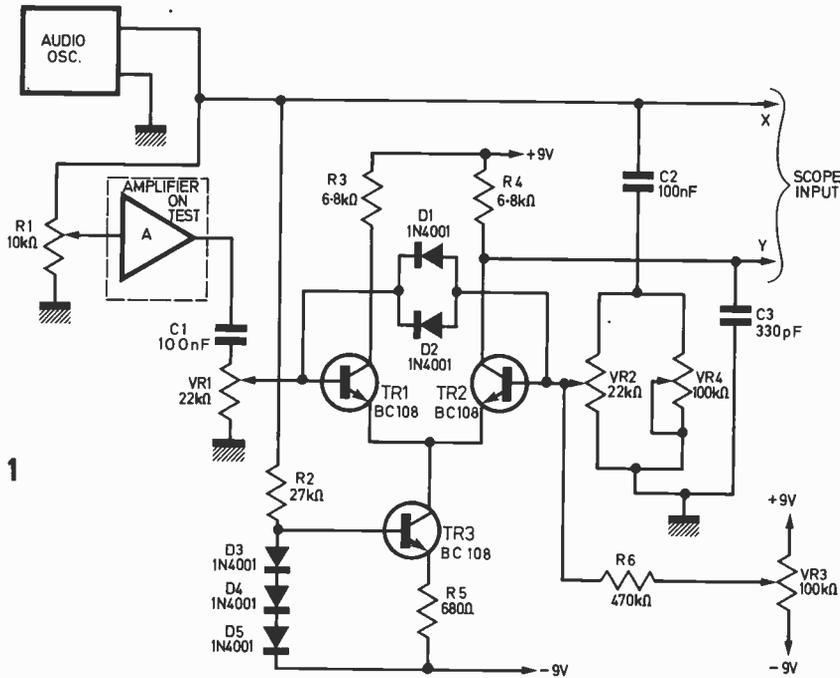


Fig. 1

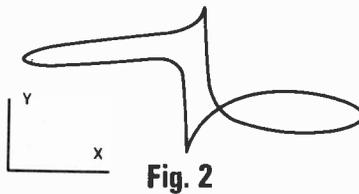


Fig. 2



Fig. 3



Fig. 4

THE circuit (Fig. 1) might be of interest to those readers who wish to test audio amplifiers for distortion without sophisticated test gear such as low distortion oscillators and tuned filters.

The principle is to match the amplitudes of signals derived from the input and output of the amplifier A under test and compare them in a long tailed pair. (An op amp is an obvious alternative.)

With about 1V r.m.s. fed to both inputs and VR1 and VR2 (Fig. 2) at near maximum settings, the residual output can be reduced below the noise level. VR3 is set to

balance the TR1 and TR2 collector currents approximately. D1 and D2 protect TR1 and TR2 against surges, reverse voltages, etc.

The circuit is easily set up. Limiting problems are hum in the amplifier under test and phase shift. Passive phase correction components (e.g. VR4) might be needed.


Unless the oscillator is fairly free from harmonics, differential phase shift versus frequency might give misleading results if attempts are made to assess harmonic distortion at high or very low frequencies.

Displaying the output in X-Y form has the advantage of expanding the crossover region in X. The traces show some results from an experimental amplifier, feeding 9V p-p into 3Ω. Scale in all traces is about 4mV/cm in Y.

Fig. 3 shows crossover distortion, only just detectable on a conventional scope display of the output. That in Fig. 3 could not be seen at all. Fig. 4 shows remaining second harmonic, after increasing the amplifier bias current in the output stage. Frequency in all cases was about 700Hz.

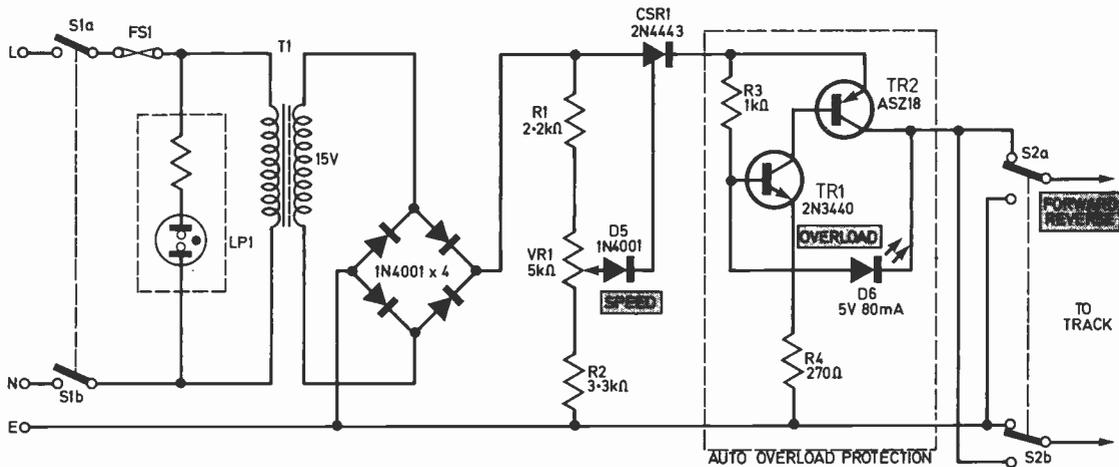C. J. Collins,
Letchworth,
Herts.

PROTECTION FOR A MODEL TRAIN SPEED CONTROLLER



THE circuit shown in the diagram is based on the "Model Train Speed Controller" that appeared in PE December, 1976. The additional circuitry is shown within the dotted lines. This addition, which is suitable for one engine only, can be included to perform three functions:

1. To protect the controller against temporary overload by automatically reducing the available output current when such a condition occurs. This could happen due to a train becoming derailed, or due to incorrect track wiring, etc. This is an important consideration when the system may be operated by young children.
2. To provide a visual indication that an overload has occurred.
3. To eliminate the necessity of providing extra hardware to cope with a manual reset of the controller once the appropriate corrective action has been taken.

Under normal conditions both TR1 and

TR2 are switched on, TR1 providing sufficient collector current to drive the base of TR2. The l.e.d. is reverse biased and therefore has no effect.

Should the impedance of the load reduce to a point whereby the potential at the collector of TR2 falls approximately 1.9V below that at the base of TR1, then the l.e.d. becomes forward biased and will illuminate indicating that an overload condition exists.

Once the l.e.d. attains this state it clamps the potential at the base of TR1 to that at the collector of TR2, thereby tending to switch off TR1. This situation results in a reduction in the base current available to TR2, which is reflected as a current limitation into the load. Once the load impedance is restored, the state of the l.e.d. and the two transistors reverts to normal.

In operation the limiter has been found to reduce the current through a short circuited load to approximately 20 per cent of that available to a normal condition with the engine running at full speed. This is

particularly useful in the situation whereby a heavy duty transformer can supply power to a number of controllers and trains, since the s.c.r. would burn out very quickly if the limiter were not present.


Should an electro-mechanical cut-out system be required, offering a complete shut-down on overload, then this circuit (with the illuminating l.e.d. positioned in close proximity to a photo-transistor or l.d.r., etc.) will interface directly with the *Multichannel Overload Protector* in PE October, 1977.

No component values are critical, the values of R1, R2 and VR1 being given for the 2N4443, as opposed to the CRS1/05 specified in the original article.

TR1 should be a silicon n-p-n transistor capable of maintaining approximately 40mA of base current into TR2, which itself is *pn*p output transistor supplying approximately 1A to the engine.

R. Chapman,
Walton-on-Thames,
Surrey.

SIMPLE ALARM

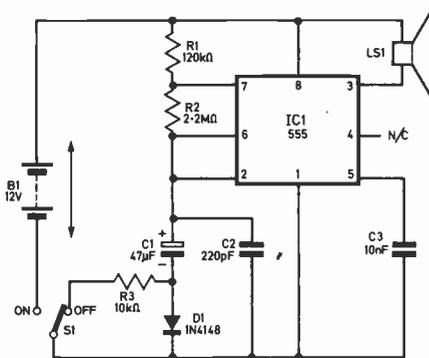

THE enclosed circuit utilises the timing capability of the 555, together with its capacity to directly drive a small audio transducer. It provides an economical arrangement to provide an audible alarm.

C1, charging via R1, R2 and D1, provides the initial timing delay. When the discharge is initiated, D1 virtually isolates C1 from the circuit and C2 effectively governs the charge/discharge cycle, resulting in audio frequency oscillation.

In practice, C1 isolation is not complete, resulting in a slightly rough tone initially, by no means a drawback as regards audibility. Resistive shunting of D1 increases the roughness, if required (it also alters the frequency).

With the values shown, the circuit gives a three minute delay and an audio frequency of about 1,500Hz, using a 12V supply. Performance as an oscillator can be affected by supply impedance; with some dry battery supplies a shunt capacitor might be desirable across the battery.

C1 is discharged at switch-off via R3, included as a (perhaps unnecessary) precaution to reduce reverse base-emitter potentials in the threshold comparator Darlington long tailed pair. It should certainly not be necessary with supply potentials below 7.5V.

C. J. Collins,
Letchworth,
Herts.

Semiconductor UPDATE...

FEATURING : PBL 3708 TS 04700/10000 SC 100

R.W. Coles

FIT TO BURST

As many readers will no doubt be aware, there are two quite different ways to drive a triac in a.c. power control circuits.

The most familiar of these is probably "phase control", where the triac, off at the start of a half cycle, is turned on part way through by a trigger pulse which can occur at any phase angle selected by external circuitry.

An example of this type of control is the well known lamp-dimmer circuit, quite common these days in the more "switched-on" households! The control for this application comes from a simple variable CR circuit and a diac trigger device, the diac generating a trigger pulse for the triac when the voltage across the CR circuit (which lags the mains input) reaches a sufficiently high value, usually about 40 volts. Adjusting the CR time controls the phase lag and hence the conduction angle of the triac.

Unfortunately, the fact that the triac can be switched on when a considerable voltage exists across it means that the voltage waveform delivered to the load will often contain square edges of large amplitude. Square edges contain harmonics of course, and here we have the makings of an excellent radio and TV jamming system! The only way out is to use an r.f. filter at the device inputs, and to

restrict this sort of system to low power applications, say, 200W. If greater power must be controlled, use "plan B," called "burst-firing."

Burst-firing eliminates the RFI (Radio Frequency Interference) problem by delivering only integral numbers of mains half cycles or cycles to the load. The trick here is to always trigger the triac as the mains voltage crosses zero at the start or end of a half cycle, and this does away with all those nasty square edges. Using this technique, loads of several kW can be controlled, at the expense of control circuit complexity, and it is ideal for the proportional control of heating in electric cookers and other domestic appliances.

Despite the availability of this burst-fire technique, and the cheapness of triacs, white-goods manufacturers have been slow to abandon their mechanical gadgets and ingenious bi-metal strips, which are in the stone age by comparison with the smooth, accurate, control now available from the triac.

The problem, as always, is price. The burst fire control circuitry can be expensive, but not for long if the Swedish firm of RIFA have their way. They have introduced a complete trigger control circuit for temperature control applications which fits into a single 8-pin mini-d.i.p. The device is coded **PBL 3708**, is available from Jermyrn,

and contains almost everything you need apart from a few discretes and a triac. The bits inside include a zero crossing detector, a ramp generator and a comparator, and the whole thing can be powered straight from the mains, thanks to an internal regulator.

KNEES-UP


Ordinary Zeners are a bit of a disaster at low currents. Drop much below 5mA operating current, and that breakdown "knee", which looked fine on the 50mA scale, begins to look more like a matronly "bosom"! If your applications are happy passing 5mA or more through the Zener, don't worry about it. But if, like me, you have ever needed a voltage reference in a micropower circuit, you will be interested in a new series of diodes from Teledyne. The **TS 04700 to TS 10000** range, covering 4.7 to 10V in 12 voltage increments, will operate at 1µA or less and yet have knees like set-squares!

To get the best from the range, choose a diode of 6V or greater because the performance here is at its zenith. As an example, a 10V diode (TS 10000) suffers a maximum voltage change of only 0.1V for a current range of 1 milliamp to 10 *nano-amps*! Team one of these up with an emitter follower using a high gain transistor such as the ZTX109 and you can drop your op-amp supply down to 5V for CMOS *without* the regulator taking more current than the logic!

HUNDRED AMP WHOPPER

A new candidate for the electronic "Guinness Book of Records" has just been introduced by the aptly names Germanium Power Devices Corporation. The new arrival is a power transistor with a 100A rating, coded **SC 100**, made with good old *p.n.p.* germanium technology. At 100A the SC 100 still has an h_{fe} of 15, so you only need to supply about 7A of base current.

The SC 100 has a TO 68 package, which looks a bit like two dustbin-lids clamped together, and is of course designed to be securely bolted to a heatsink. I should think that if you used output transistors like these in a domestic system, you could use the waste heat to drive your central heating boiler! Try as I might I cannot dream up much in the way of applications for this monster, "though you could probably make a nifty controller for your electric-car or fork-lift truck. I can't help thinking that the "SC" in SC 100 stands for short-circuit!

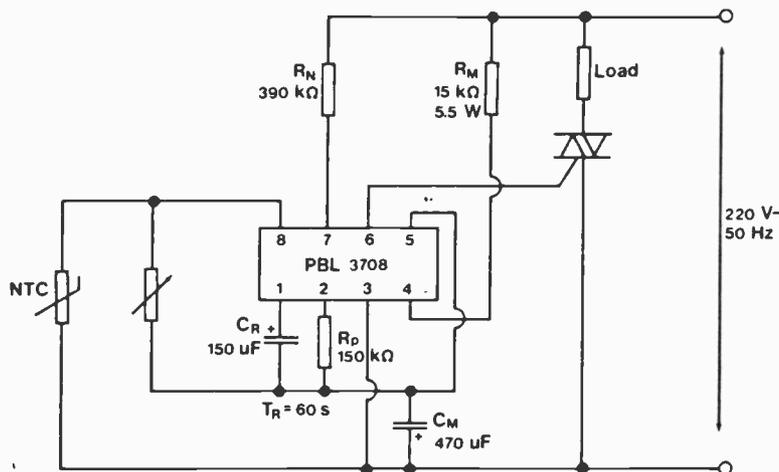

A typical design for control of room temperature with a heating element of 1,000W, 220V a.c. and a proportional band of 1°C.

QUALITY HI-FI AT BUDGET PRICES

Fight inflation with these super Hi-Fi offers. Compare these prices with the recommended retail prices and you will see that you can save £££££—and what is more, you will be purchasing quality equipment—that is why we are happy to give these amazing guarantees.

TREMENDOUS SAVINGS FOR THE HOME ENTHUSIAST

GOLDRING CK2 BELT-DRIVE TURNTABLE CONSTRUCTION KIT



Complete with arm, template and easy-to-follow instructions. Ready for operation in a short time. Wow/Flutter 0.15% peak. Rumble 60 dB weighted. Removable headshell. Viscous damped cueing device. Easily adjusted tracking force and bias setting.

Two-speed, 16-pole synchronous motor. Dimensions: 37.8 x 28.3 cms (Plinth, cover and cartridge available, prices on application.) R.R.P. £31.50
LION HOUSE PRICE £15.95
Postage and Packing £2.

MANY MORE EXCITING BARGAINS ARE AVAILABLE AT LION HOUSE—BRITAIN'S HI-FI SUPERSTORE WITH THE SUPERB DEMONSTRATION FACILITIES.

The MATSI TFS60 Tuner/Amplifier



AT LEAST THAN HALF THE RECOMMENDED RETAIL PRICE

Due to a successful bulk purchase, we are happy to offer this really top quality receiver from one of Japan's leading manufacturers at less than half price. 15 watts per channel FM/MW/LW. 12 MONTHS GUARANTEE. Recommended Retail Price £144. **OUR PRICE £65** (Securicor delivery £3.50)

GOLDRING TURNTABLE



Available to personal shoppers only, the Goldring belt-drive turntable comes complete with high quality active plinth and cover—12 MONTHS GUARANTEE.

TODAY'S VALUE £45
LION HOUSE PRICE £25


SANKYO STD-1610 STEREO CASSETTE DECK



Features include Dolby noise reduction system, Autochrome, Input/Output Level Control, Peak Indicator, Auto-stop, Ferro heads, Tape-run Indicator, Hinged Dust Cover—MORE FEATURES FOR LESS MONEY—12 MONTHS GUARANTEE—A beautifully compact machine of highest quality. Another successful bulk purchase from Lion House at **ONLY £69.95** (Recommended Retail Price £114.) (Securicor delivery £3.50)

RAMKO GULLIVER SPEAKERS

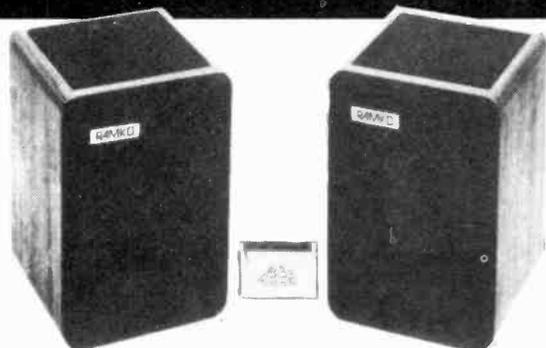GIANT PERFORMERS OF DWARF-LIKE DIMENSIONS



Two-way mini hi-fi studio quality loudspeakers. Despite their mini size, their clean, solid bass range is equal to that of much bigger systems, and the use of a high density, high temperature metal voice coil system greatly enhances durability. In a room filled with excitingly realistic sound, they seem almost undetectable. 4-inch woofers have high power handling capability and are as efficient as 6-inch woofers. Extra light 1-inch soft dome tweeters weigh only 0.2 grams. A powerful

10-ounce precision ceramic magnet, coupled to the dome, creates immense flux providing excellent transient responses. Acoustically suspended and impregnated with finest damping fluid, protecting dome against distortion break-up or coloration even after prolonged heavy loading. Dome shape and construction produces extra-wide dispersion, smooth frequency response and high resolution of musical detail.

Highly precise crossover network, matched to component speakers, gives accurate separation of audio spectrum and stable frequency response. Specially designed cabinets made of high density chipboard with wood welded joints and individually tested. Finished in the finest laminated rosewood veneer and crafted and oil finished by hand to a distinctive lustre. We are the sole agents and offer them direct to you at **only £79.95** per pair. (Securicor delivery £3.50)

SPECIFICATIONS

Nominal impedance	8 ohms
System components	4" woofer 1" dome tweeter
Frequency range	50-25,000 Hz
Sensitivity	1.5-3 watt
Nominal input	35 watt
Music power	50 watt
Dimensions	18 x 11.5 x 12.5 cm

WARRANTY

Every RAMKO loudspeaker model is guaranteed for a period of five years.

Televisions, Radios, Tape Recorders, Music Centres, Cassette Recorders, Earphones, Quality Audio and Video Equipment, Hi-Fi Accessories, Export Televisions, In-Car Equipment, Watches, Binoculars, Cameras, Calculators, etc and an entire floor devoted to Musical Instruments—all at keen prices!



Lion House

LONDON'S HI-FI SUPERSTORE
227 TOTTENHAM COURT ROAD LONDON W1
Tel: 01 580 7383 and 01 637 1601
Telex: 283394 LION G

Open 9 am to 6 pm Monday to Saturday
(Thursday until 7 pm)

SAME DAY CREDIT FACILITIES
TAX FREE EXPORT



Stockists for: A.D.C., Amstrad, Aiwa, B.S.R., Celestion, Empire, Fidelity, Goldring, Goodmans, Grundig, Harmon Kardon, Hitachi, J.B.L., Kef, K.L.H., Koss, Monitor Audio, Micro, Marantz, National Panasonic, National Technics, NAD, Nakamichi, JVC, Autofon, Philips, Quad, Revox, Sansui, Sennheiser, Shure, SME, Sony, Sharp, Superscope, Tannoy, Teac, Thorens, Transcriptor, Yamaha, etc

BEFORE YOU BUY AN AMPLIFIER MODULE—CHECK:

DOES IT HAVE

- ★ 30A power transistors
- ★ 2-year guarantee
- ★ 3A drivers (100W unit)
- ★ Integral output capacitor

Then compare with the Tamba range—excellent value—25, 50 and 100W R.M.S


TAM1000 100W 4 ohms 65V	£9.80
TAM500 50W 4 ohms 45V	£7.50
TAM250 25W 8 ohms 45V	£5.75

POWER SUPPLIES

For 1 or 2 TAM250/500	£7.50
For 1 or 2 TAM1000	£9.80
(Carriage 50p on supplies)	

- Suits loads 4–16 ohms
- 20–20,000 Hz \pm 1dB
- Silicon circuitry throughout
- Glass fibre P.C.B.
- High sensitivity (100mV 10k)

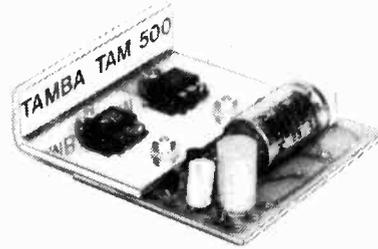High grade components used throughout: Texas, Mullard, R.C.A., Plessey, etc.



- Low distortion (0.1%)
- Low profile (1in high 3½in. x 3in)
- 75% efficient
- Accepts most mixer/pre-amplifiers
- Four simple connections

NEW

ALL PURPOSE MIXER/PRE-AMP.

(with 60mm slider volume)

- Suitable for multiple input systems
- High and low impedance inputs
- High sensitivity
- Built-in supply smoothing
- 20–20,000 Hz \pm 1dB
- –80dB noise level
- Accepts a wide variety of inputs
- Wide range bass and treble controls

Use up to 10 PRE-AMPS with 1 power supply

Printed circuit board assembly with treble and bass controls plus slider volume control **£6.50**

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s etc)—C.O.D. (60p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50 and 100W systems and at 12½% for 25W systems (including preamp if ordered at same time).

Hours, 9.30 a.m.–5 p.m.
Monday — Saturday.
Callers welcome. Tel. (01) 684 0098

TAMBA ELECTRONICS

Bensham Manor Road Passage, Bensham Manor Road, Thornton Heath, Surrey.

PROGRESSIVE RADIO

93 DALE STREET, LIVERPOOL L2 2JD. Tel: 051-236-0982

SEMICONDUCTORS ALL FULL SPEC. BC212, BC182, BC237, BF197, BC159 all 8p each. LM380 80p, LM381 95p, NE555 33p, 741 8 PIN 23p, 741S (wide bandwidth) 8 pin 35p, TL305 Alpha numerical display (with data) £2.50p. BX504 opto isolators infra red led to photo cell, 4 lead 25p. BFY50 plastic 14p, STC 3 volt 1 watt zener diodes 7p each, BD533 33p, MRD3051 photo transistors 35p, FETS similar to 2N3819 18p, MOSFET similar 40P73 35p, Intel C1103 1024 bit mos rams 95p, CD4051 45p, 723 14 pin I.C. s. 35p.

DIODES. BY127 9p, IN4002 4p, IN4005 7p, 600V 3 amp 17p, Lucas bridge recs, 400v 1.5 amp 30p. SPECIAL OFFER, TBA800 10 for £5.00

MAN3A 3mm led displays 50p. Min. Nixie 587 OST 75p.

Pot core unit, has six pot cores including one FX2243 (45mm) and two FX2242 (35mm) 3 TO3 sil. power transistors on heat sink, 3.20mm panel fuseholders and panel with various transistors, diodes and a 5 amp plastic SCR, £1.75p plus 75p postage.

MOTORS. Model type 1.5–6 volts 20p, 'BIG INCH' sub min motor 115 vac, 3 r.p.m. 25p, 24 OVAC SYNCH MOTORS WITH GEARBOX, 1/5 r.p.m. 75p, 1/24th r.p.m. 75p, 15 r.p.m. £1.20p, Crouzet 115 VAC 4 r.p.m. 95p, 12v dc 5 pole 35p.

HI-SPEED MORSE KEY, ALL METAL £2.25p.

PLESSEY WINKLER SWITCHES, 1 pole 30 way, 2 bank adj, stop 75p.

Crystal microphone inserts 37mm 45p. Grundig electret condenser inserts with built in FET preamp £1.50p, ELECTRET PENCIL HAND MICROPHONES 1K IMP WITH STANDARD JACK PLUG £2.85p, THE CLIP CONDENSER MIKES OMNI, 1K IMP, (uses dead air battery, supplied) £4.95p.

SOLDER SUCKER, high suction, eye protection shield £4.95p.

PROJECT BOXES, BLACK ABS PLASTIC WITH BRASS INSERTS AND LID, 75 x 56 x 35 44p, 95 x 71 x 35 52p, 115 x 95 x 36 60p.

BUZZERS. GPO open type 3–6V 30p. Large plastic domed type loud note 6 or 12 volts 35p, Solid State buzzers, miniature, 6–9–12–24 volt 15ma 75p each.

TAPE HEADS, Mono Cassette £1.30p. Stereo cassette £3.00, BSR MNI330 half track dual imp. heads £1.75p, TD10 Dual head assemblies 2 heads both ½ track R/P with built in erase, mounted on bracket, £1.20p.

Relays. Min. sealed 12v dc type 4 pole changeover 55p, Min. 24v dc 2 pole c/o 3 amp contacts 55p, Min sealed 220v ac 2 pole c/o 40p, Open type 12v dc 4 pole c/o 50p, 4 pole reed relays N/O 20p.

CRYSTALS, 300khz 40p, 4.43mhz CTV 45p. Aerosol 'Touch up' paint one colour yellow/grey, 6oz can 35p. 50v ac cam units, motor switching ten c/o micro switches, supplied with capacitor for 240v ac use £1.95p plus 35p postage.

Balling Lee L4305 masthead amplifiers and mains power unit, new but only for group A UHF £7.50p.

TRANSFORMERS, 6–0–6v 100ma, 9–0–9 75ma, 12–0–12 50ma 75p each, 12–0–12 100ma 95p, 12v 500ma 95p, 1:1 triac/kenon pulse transformers 30p, CHOKES 6MC 3 Amp 20p, U.H.F.V Tuners, push button (not varicap) new and boxed £2.50p. Miniature toggle switches, SPST 8 x 5 x 7.45p, DPDT 8 x 7 x 7.50p, DPDT c/o 12 x 11 x 9.75p, Min. push to make or push to break 16 x 16mm 15p each type. Slider switches, DPDT standard 15p, Min. 12p, Std. c/o 20p. Roller action micro switches 15p.

TOOLS Small side cutters 5" insulated handles £1.35p. Snub nosed pliers 5" insulated handles £1.35p. Watchmakers screwdriver sets, 5 drivers in wallet £1.00p. Large mains tester screwdrivers, fully insulated 8" 44p. Test lead jumper sets, 10 leads with insulated croc clips each end, different colours 80p. Telephone pick up coil, suction type with 3.5mm jack plug 50p, 9 volt battery eliminators, 240v ac input 9v dc out at 12 cma stabilised replaced PP3, PP6, PP7, PP9 £2.45p. Edge connectors, 0.1 64 way 65p, 34 way 4 op, 0.2 18 way 15p. Amplifier modules, OTL410 10 watt mono into 8 ohms 28v dc max £4.65p, 555S Stereo module, 3 watts output into 8 ohms, 12v dc £3.35p. Tape head demagnetisers, 240v ac with on/off switch, straight probe £2.00, curved probe (cassette) £2.35p.

TERMS: cash with order, (of official orders from colleges etc). Postage 30p unless otherwise shown, overseas post at cost. VAT inclusive prices S.A.E. for lists.

Progressive Radio, 31 Cheapside, Liverpool L2 2DY. Tel: 051-236-0982.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY
£16.95
+ VAT £1.36

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume. Conversation recording mode at £19.95 + VAT £1.60. P.&P. 89p. 10-day price refund guarantee on all items.

4-STATION INTERCOM



£22.95
+ VAT £1.84

Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. Adaptable for mains. P.&P. 99p.

WEST LONDON DIRECT SUPPLIES (PE9)

169 KENSINGTON HIGH STREET, LONDON W8 6SN
Tel: 01-937 5548


TRANSISTORS			DIODES			DIGITAL I.C.' TEXAS			W/W RESISTORS		
Device	10	100	Device	10	100	Device	10	100	Device	10	100
ACV 20	3.20	27.00	AA 119	60	4.00	7400	10	2.5W Axial	90	6.50	
ASY 65	80	65.00	BY 127	30	8.00	7401	2.40	5W Radial	80	6.00	
BC 107	80	7.00	IS 44	45	3.00	7404	2.40	10W Axial	80	6.00	
*BC 118	1.10	9.00	IS 940	40	2.50	7407	2.70	15W Radial	85	6.00	
*BC 132	95	8.00	IS 941	40	2.50	7413	4.80				
*BC 147	80	6.50				7414	4.30				
*BC 149	80	6.50				7417	4.30				
*BC 204B	80	6.00				7419	14.50				
BC 348	1.00	8.00	741 BP DIL	18	1.70						
BC 351	1.00	7.50	55 8P DIL	26	2.40						
BD 131	3.30	29.00									
BD 695A	5.50	42.00									
BD 696A	5.50	42.00									
BF 185	2.40	20.00									
BF 324	3.30	29.00									
BT 106	10.00	72.00									
*BU 205	14.00	115.00									
*BU 208	15.00	120.00									
*ZX 212B	1.10	9.00									
*ZX 302	1.00	8.00									
*ZX 502	1.10	9.00									
*ZN 930	1.60	12.00									
*ZN 2647	8.00	60.00									
*ZN 3703	80	6.50									
*ZN 3705	80	6.50									

Min. Order £2.00, P. & P. 30p. VAT please add 8% except those marked * which are 12.5%.

Export, Wholesale and Manufacturers Enquiries Welcome.


K & A DISTRIBUTORS

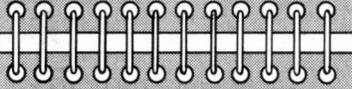52 Barkby Road, Syston, Leicester LE7 8AF. Tel: 0533 609391.



INDUSTRY NOTEBOOK

By Nexus

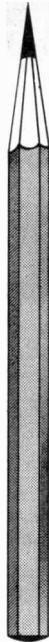

The Great Debate

It is all to the good that in the last few months both the promise and the threat of Very Large Scale Integration (VLSI) have received a great deal of public exposure through radio, TV and the printed word.

The promise is in electronic goodies which will make a lot of money for the electronics industry and save a lot of money and give greater convenience, sometimes both, for the VLSI user. The threat is that though the electronics industry may prosper and perhaps employ marginally more people, the end result will cause a great deal of unemployment elsewhere.

Even in the electronics industry itself the advent of comparatively simple (compared with what is yet to come) devices has had a dramatic effect on labour content in assembly of equipment. I recently saw one female assembler and two male technician testers handling the whole assembly and testing procedures of a product, the end value of which totalled some £3 million per year. These three people were not even working at full capacity. Nor were they highly skilled.

To produce an equivalent product with the discrete components and methods of, say, 20 years ago, would have demanded an assembly line of many more people, perhaps ten assemblers and five testers, all working flat out. And the product would have been larger, heavier, used more raw materials, consumed more power, been more expensive and less reliable.

The computing power of a £5 chip today is said to equal that of a first-class computer costing £250,000 in 1950. That's the way it's gone and very nice, too.

Now spare a thought for all those people, skilled mechanics, who have spent years patiently assembling the complicated mechanisms of the common cash register. The mechanical model, even the electro-mechanical, is on its way out. Market researchers Frost & Sullivan are predicting

a £2.5 billion market in the next ten years for the all-electronic model in 16 West European countries alone. There are many such examples where traditional skills will no longer be needed in the all-electronic age.

The media, ever-anxious to dramatise and popularise the issues of the day, and limited in time for any particular topic, naturally tend to over-simplify. It is a pity that historical perspective has been largely overlooked for if we face up to it the new "threat" is only another phase of a continuing process which has been with us since the beginning of the industrial revolution.

The old-time craftsmen and labourers were horrified by machines. Later, having become accustomed to machines they were horrified by automation which introduced a limited "intelligence" to machine operation. Today people are petrified at the prospect of microelectronics which promise a further level of "intelligence" to the machine and the transfer, if not the total abolition, of many formerly needed skills.

And yet all the evidence is that the natural inventive progression from manual labour and craftsmanship to automation and to microelectronics in all its aspects has enriched us all, at least in material goods.

The paradox remains that while, for example, a steel worker resists the introduction of a new and more efficient process in his mill, he would be the first to complain if his family car were to cost him £40,000 because it was made entirely by hand or his washing machine £1,000 or so, and the shirt on his back £50.

One sympathises naturally with legitimate fears but nobody can have it both ways. Self-interest is such that we all like to enjoy the fruits of modern invention as long as it is somewhere else, just as most people agree that more airports are needed provided they are located well away from their own area.

In Sweden, which has a small labour force, the trade unions discourage any worker to be employed on dirty or dangerous tasks which could more profitably and easily be undertaken by an industrial robot. Will the recently formed British Robot Association help to change attitudes and dispel fears in Britain?

It seems odd that while the world stock of nuclear weapons is sufficient to vaporise the whole of mankind we are all dead scared of a tiny chip of silicon.

The debate continues . . .

Getting Together

GEC looks like teaming up with the Japanese in colour TV manufacture. There are moves, too, on the computer front with ICL concluding a know-how exchange with Hitachi, and technical co-operation and cross-marketing in an agreement between Siemens in Germany and Fujitsu in Japan. The computer deals are said to be preparatory moves in the forthcoming sales battle expected to start in 1980 when IBM will introduce a new range.

European companies are anxious to get access to new technology being developed in Japan through huge government funding in VLSI, including exotic devices like a megabit memory. For their part, the Japanese are anxious to widen their market beyond Japan. ICL, for example, sells in 80 countries, Hitachi mainly in Japan.

The GEC attitude on colour TV appears to be that if you can't beat 'em then join 'em. Better to have half the cake than no cake at all.

Now it can be TOLD

The Post Office TOLD (Telecommunications On-Line Data) nationwide computer project is now in service. Costing £12 million, the Post Office expects to save £22 million through improved efficiency during the life of the equipment. Pilot trials started in 1975. Now the system is complete it uses 1,300 Cosor CD3005 VDU terminals all linked to ICL 4-72 computers with advantages in speed, control, accuracy and simplicity of use. Direct access to the computer now replaces form-filling and transferring the data from forms to punched cards or magnetic tape.

Qualifications

Starting reading now for an honours degree if you want to join the Institution of Electrical Engineers. As from 1982 second class honours will be the minimum qualification for membership plus relevant industrial experience plus a written professional test demonstrating competence and future potential.

IBC Sell-Out

The biennial International Broadcasting Convention is moving this year from the popular Park Lane venue of Grosvenor House to the new Wembley Conference Centre. Exhibitors are up to 85 as compared with 72 at IBC '76 and the exhibitors have 20 per cent more space. Some 180 technical papers have been submitted for the Conference, another record, but these will be trimmed down into 12 main topics for discussion. The dates this year are September 25-29.

The technical sessions will reflect all the latest techniques including MPU and minicomputers in broadcasting, teletext, quad sound, satellites, video processing, etc.

Car Radar

Anti-collision radar for motor cars was being considered by US General Motors 20 years ago. They will become a reality for the American motorist in the '80s. A simple system would have an audio warning for the driver. A more complex system has radar-activated braking. A combination of Gunn oscillators for the radar section and powerful MPUs for signal processing will help overcome the knotty problem of discriminating real targets (i.e. car "signatures") from roadside objects such as lamp posts, bollards or oil drums.

THERMOSTAT CONTROL

M. EDMUNDS

WHILE developing colour transparencies, particular attention must be paid to the control of the developing solution temperature. Most home developing kits require the temperature of the first and colour developers to be within ± 0.25 deg C of a stated temperature, usually in the range 20–40 deg C.

The device described in this article not only acts as a very accurate and stable thermostat, but also provides an analogue readout of the temperature in the bath.

To realise the full potential of the circuit it should be used in conjunction with a stirring device in the tank. This need only take the form of a small paddle driven fairly slowly by a geared down electric motor.

CIRCUIT DESIGN CONSIDERATIONS

The complete circuit is shown in Fig. 1. In order that the overall unit was simple and cheap, operational amplifiers were used throughout.

Although a thermistor has a non-linear resistance relationship with temperature (see Fig. 3a), by making it one of the elements in a potential divider network, the voltage output is almost linear against temperature in the range of 10–15 deg C (see Fig. 3b), assuming the potential divider is fed from a stable voltage.

Components R1, R2, D2, D3, form a sufficiently stable voltage source for this purpose and also serves to supply a switching reference voltage to comparator IC2.

Switch S1 selects either the thermistor TH1 or preset VR1 to be the lower element of the potential divider. VR1 is used to supply a calibration resistance so that the correct operation of the unit can be checked periodically.

The difference between the output voltage from the divider and reference chain R4, VR2 and R5 is amplified approximately 5 times by IC1, the output voltage being read on meter M1. Resistor R9 is a meter shunt and may be adjusted to suit a different meter movement.

As the temperature in the bath falls it is sensed by TH1 and causes an increase in its resistance, the voltage at the inverting input of IC1 increases and the output voltage decreases.

This voltage is fed via R10 to IC2 to be compared with the reference set by VR3 on the non-inverting input. As the temperature falls the output voltage of IC1 falls, and a point is reached when this crosses the reference voltage. The output of IC2 then rapidly swings high, to almost full supply volts. This action brings TR1 into conduction to energise RLA thus switching on a small immersion heater in the bath.


The components R12, R13, R14 form a positive feedback loop to put a hysteresis effect into the switching action.

Without this, at the switching temperature the output from IC2 would oscillate fairly rapidly due to the low level noise signals on the output of IC1. The operation of this network is as follows, as the output of IC2 goes high, the voltage at the junction of R13 and R14 increases slightly. This small voltage is effectively added to the reference voltage via R12, it is thus necessary for the voltage at the inverting input to rise slightly further before the output of IC2 drops to the low value, switching off TR1 and the relay.

When this occurs the feedback voltage becomes zero and the reference voltage returns to its pre-set value.

CONSTRUCTION

The prototype device was built on 0.1 in. matrix veroboard which after being checked for track shorts etc, was bolted directly onto the input terminals of the meter. Integrated circuit holders are used for the operational amplifiers to avoid soldering damage. Veroboard pins were used where connections were necessary to components not on the board.

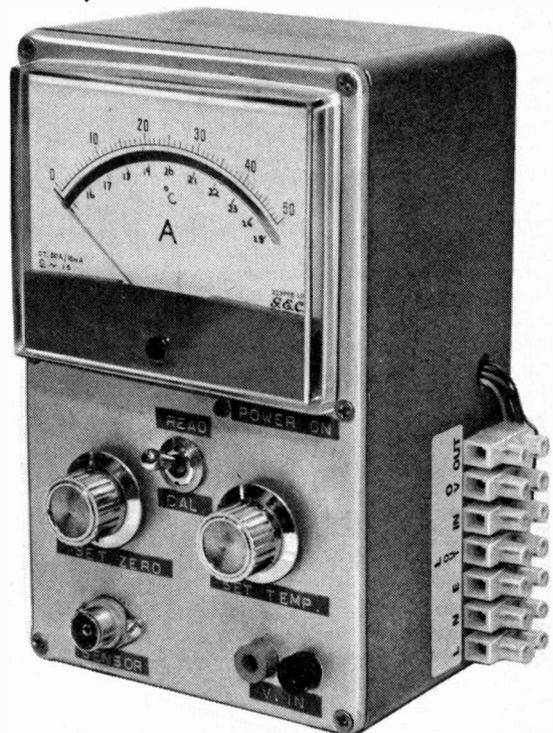

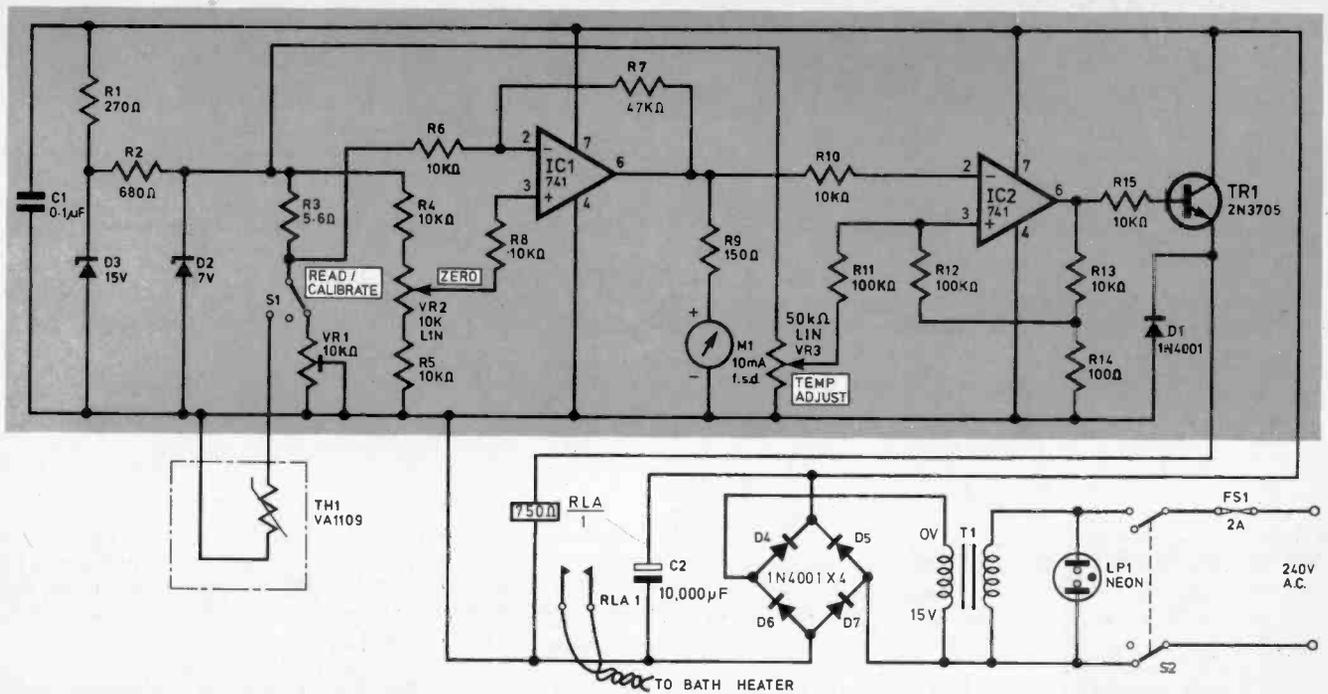


Fig. 1. Full circuit diagram, including suggested power supply circuit (shown outside shaded area)

COMPONENTS . . .

Resistors

R1	270Ω
R2	680Ω
R3	5.6Ω
R4-R6, R8, R10, R13, R15	10KΩ
R7	47KΩ
R9	150Ω
R11, R12	100KΩ
R14	100Ω
All ½W 5% unless otherwise stated	

Potentiometers

VR1	10KΩ multiturnd preset
VR2	10KΩ linear carbon
VR3	50KΩ linear carbon

Capacitors

C1	0.1µF/25V
C2	10,000µF/25V

Transistors and diodes


D1, D4-D7	1N4001
D2	6.8V 400mW Zener
D3	18V 400mW Zener
TR1	2N3705

Integrated circuits

IC1, IC2	741 op. amp.
----------	--------------

Miscellaneous

M1	10mA f.s.d. meter
RLA	15V operating relay with n.o. 240V 5A contacts
S1	S.p.d.t. toggle switch
S2	D.p.s.t. toggle switch (mains)
T1	Mains transformer. 15V/500mA secondary
FS1	2 amp fuse and holder
Diecast box	203 x 127 x 89mm (used for prototype)
Veroboard	0.1in
8 pin d.i.l. holders (2 off)	
Coaxial plug and socket for temperature probe	

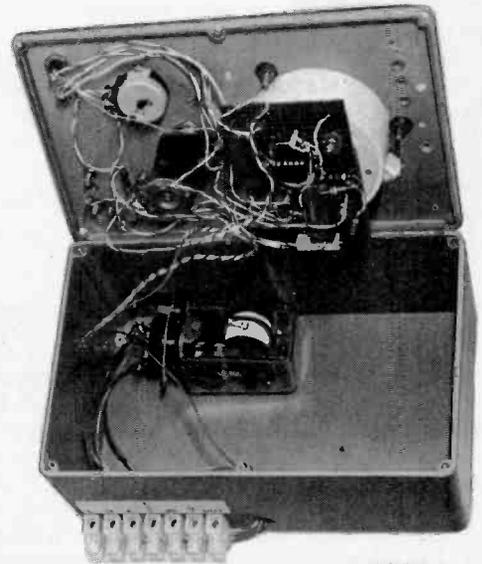


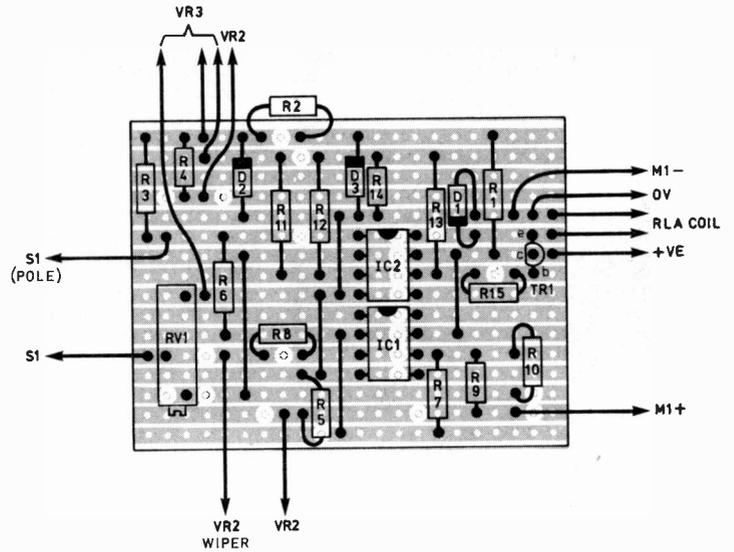
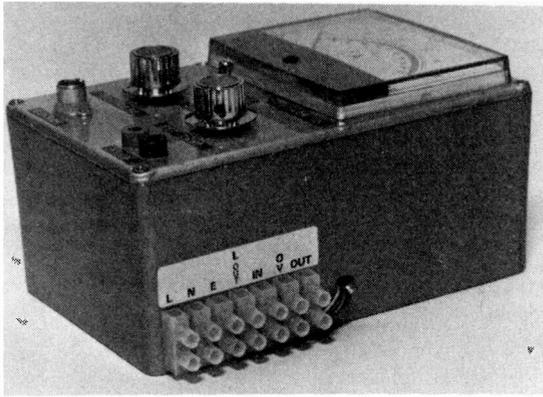


Fig. 2. Stripboard layout shown at full size. Note that C1 is not shown on this diagram

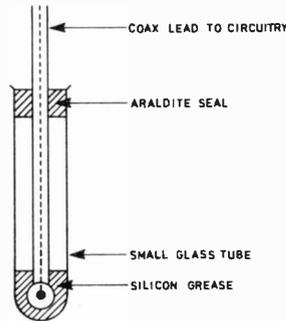

A temperature probe can be fabricated from a small test tube

The meter M1, switch S1 and controls VR2 and VR3 are panel mounted together with a coaxial socket for the connection of TH1. If the completed thermostat is to be run from a separate 20V supply then two extra sockets will be needed for this.

Sufficient room is available inside the specified diecast box to house a small mains transformer, rectifier and smoothing capacitor. Using the double Zener arrangement as shown in Fig. 1 the device is immune to $\pm 2V$ changes in supply voltage, and thus the stability of the supply is not too critical. The Veroboard layout is shown in Fig. 2, and the front panel layout can be seen above.

SETTING UP AND CALIBRATION

All that is needed for this procedure is an accurate thermometer and a vessel of water. After a 5 minute warm up period switch S1 to bring TH1 into circuit. Submerge the thermistor enclosure into water at exactly 20 deg C and adjust VR2 until the meter shows half-scale deflection. Now switch S1 to bring VR1 into circuit and adjust the potentiometer VR1 to return the deflection to half-scale.

Now return S1 to its original position bringing TH1 into circuit. Suspend the thermistor enclosure in water at several different temperatures marking the meter scale in each case with the temperature indicated by the glass thermometer. Using the value of R9 quoted with the specified thermistor, the device will have a full-scale range of 10 deg C (from 15 to 25 deg C).

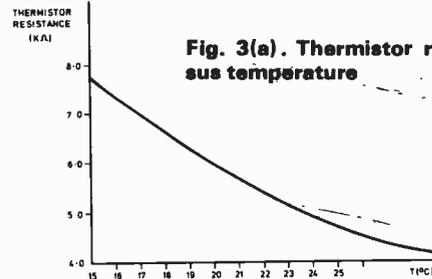


Fig. 3(a). Thermistor resistance versus temperature

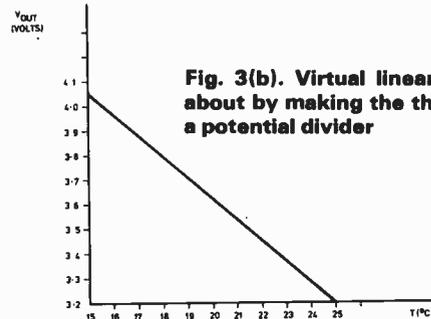



Fig. 3(b). Virtual linearisation brought about by making the thermistor part of a potential divider

To set the switching temperature, bring VR1 back into circuit by operating S1, the meter should read half-scale. Rotate VR2 to bring the meter to read the desired temperature. Now rotate VR3 slowly until the relay is heard to operate. This completes the setting up procedure. Slight adjustments may have to be made when the thermostat is in use, as changes in water-bath geometry may affect the required setting of VR3.

USE OF THE COMPLETED SYSTEM

Switch S1 to connect VR1 in circuit, check that the meter reads half-scale deflection. If not then adjust VR2 to obtain this condition. This checks (and compensates for) the input offset level of IC1, which may tend to drift with ambient temperature changes and age. Switch back to TH1 and the meter will then read the temperature of the water surrounding the thermistor enclosure.

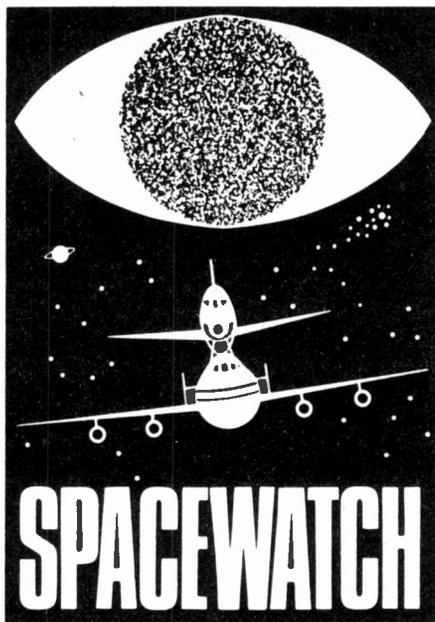Used in this way, the unit will prove reliable and the complete unit should give trouble free operation for a considerable number of operational hours. ★



FRANK W. HYDE

SOYUS-29 and SALYUT-6

On 17th June, 1978 the Soyus-29 space vehicle docked with Salyut-6 space station. The two cosmonauts, Vladimir Kovalynok and Alexander Ivanchenkov, will continue the programme of experiments on the same lines as those of the record breaking team, Yuri Romanenko and Georgi Grechko.

The programme consists of a wide range of experiments, among them studies of—The Earth's surface and atmosphere to obtain data of both scientific and commercial interest—Astrophysical experiments and investigations—Experiments directed toward new materials—Technical experiments and tests on structural parts of the space station itself and Medico-biological studies.

The biological experiments will be partly concerned with the problem of weightlessness. Both Romanenko and Grechko after their return to earth suffered some days of difficulty in returning to normal. The length of time they spent in the weightless condition was 96 days. During the time spent in this condition no deficiency showed up in their ability to carry out their tasks, indeed, there were signs that their efficiency did in fact improve.

After the flight the cosmonauts were very sensitive to the sensations of weight, not only of their bodies but also of other objects.

During the first few days back on Earth they had to make considerable effort to remain upright and their movements showed some indication of dis-orientation. For several days the cosmonauts wore specially designed suits to assist them to walk.

The studies of the adaptation of the biological machine to gravity was as interesting as that of adaptation to weightlessness, according to Academician Gazenko who controls the Medical and Biological Institute.

On the second day of the new mission of the space station and the supply vehicle, the

cosmonauts were engaged in re-activating the Salyut-6 and de-activating Soyus-29. The micro-climate in Salyut-6 is maintained at 20°C with a pressure of 750mm of mercury.

The space parameters of the combined unit Soyus/Salyut are at present apogee 368km, perigee 338km, orbital period 90.4 minutes, and the orbital inclination 51.6°.

The re-activating of the systems is done in stages. The water producing system had been dormant for three months. The system regenerates water from condensate. The cosmonauts enjoyed a cup of tea after the successful re-activation operation. The propulsion system has also been checked and found satisfactory.

Some details of the cosmonauts in the Soyus/Salyut latest mission may be of interest. Colonel Vladimir Kovalynok was the flight commander of Soyus-29, he made his first space flight in October 1977 as commander of Soyus-25 in the first unsuccessful attempt to dock with Salyut-6.

He was born in 1942 on March 3 in the village of Belye in the Krupsky district of the Minsk region. In 1963 he graduated from the Basahov Higher Military Flying School. He served in military transport aviation, training with several aircraft and clocking up 1,600 hours of flying time, then he became an air-force paratroop instructor.

In 1967 he joined the cosmonauts detachment and went through the complete course of space flight training. He took part in flight testing new spacecraft and in the flight control of piloted space vehicles and orbital stations. In 1976 he graduated from the Yuri Gagarin Military Air Force Academy.

His partner in the Soyus/Salyut mission is Alexander Ivanchenkov who is the flight engineer. Ivanchenkov was born on 29th September, 1940 in the town of Ivanteyevka in the Moscow region. He graduated in 1964 from the Moscow Aviation Institute, then worked in the design office, dealing with the design of new space vehicles in which he proved to be a gifted and ingenious engineer.

His space flight experience began with training for Soyus space ships and Salyut stations. On several missions he was standby flight engineer. He also trained as flight engineer for the joint Soyus/Apollo flight.

USSR LAUNCHINGS

A number of Soviet launchings took place in May and June this year. Cosmos 1011 was launched on 23rd May, with an orbital period of 104.9 minutes at an angle of 82.9°. Apogee is 1,026km and perigee 978km. Cosmos 1012 was launched on 26th May with orbital period 89.2 minutes and an orbital inclination of 62.8°. The apogee is 280km and the perigee 214km.

On 8th June a booster rocket put eight Cosmos satellites in orbit at one launch. The initial orbits ranged from 1,456km to 1,539km. The angle of inclination was 74° and the initial orbital period of revolution was 115.5 minutes.

Cosmos 1021 was launched on 10th June with an apogee of 336km and a perigee of 180km. The period of revolution was 89.4 minutes and the angle of inclination was 65°.

Cosmos 1022 was launched on 12th June with an apogee of 374km and a perigee of

182km. The period of revolution was 89.7 minutes and the inclination 72.9°.

A Molyniya satellite was launched on 2nd June. The parameters were apogee 40,837km, perigee 457km. Apogee is in the northern hemisphere and perigee is in the southern hemisphere. The orbital period is 12 hours 16 minutes and the angle of inclination is 62.5°.

The satellite carries apparatus for the transmission of television programmes and long distance multi-channel radio communication.

INDIA AND THE USSR

Preparations have been completed by the Soviet Union for the launching of India's second artificial satellite. The press were given the details by Nikolai Novikov who is Vice-Chairman of Interkosmos. The interview took place in Delhi.

Novikov heads the delegation of Soviet experts who have been testing a model of the new space laboratory at the Indian Space Centre. Discussions have been taking place between the Indian space experts and their Soviet counterparts.

It was remarked by Novikov that despite the short history of the joint activities, Soviet-Indian space research had brought practical results. The joint preparation of the first satellite, Aryabhata, helped to train India's experts who now handle a very wide range of complex scientific apparatus for space research.

Launching of the new satellite is expected to assist the development of India's economy and enable extensive study of her mineral, water and timber resources.

GOES-3

The geostationary Earth monitoring satellite has been launched. The launch was made from the Kennedy Space Centre in Florida. NASA were responsible for the launching on behalf of the National Oceanic Atmospheric Administration. GOES-3 is destined to play a key part in the Global Weather Experiment.


This is a worldwide project which will last a year. There will be an accumulation of data both oceanographic and meteorological in this period. GOES, or to give it its full title Geostationary Operational Environmental Satellite, will gather information from an area centred on the Indian Ocean.

PLACE IN SPACE

Dr. George Ellis of the University of Cape Town has resurrected an old theory of the pre-Copernican days. He is suggesting that the Earth is in fact the centre of the Universe.

He is able to put what will certainly be considered to be an outrageous suggestion, because the present day thinking and observation allows for curved space with a Universe with no edge but two centres in relation to each other. According to Dr. Ellis our galaxy is near to one of these centres. He does not accept an expanding universe but rather believes that the red shift is the result of gravity.

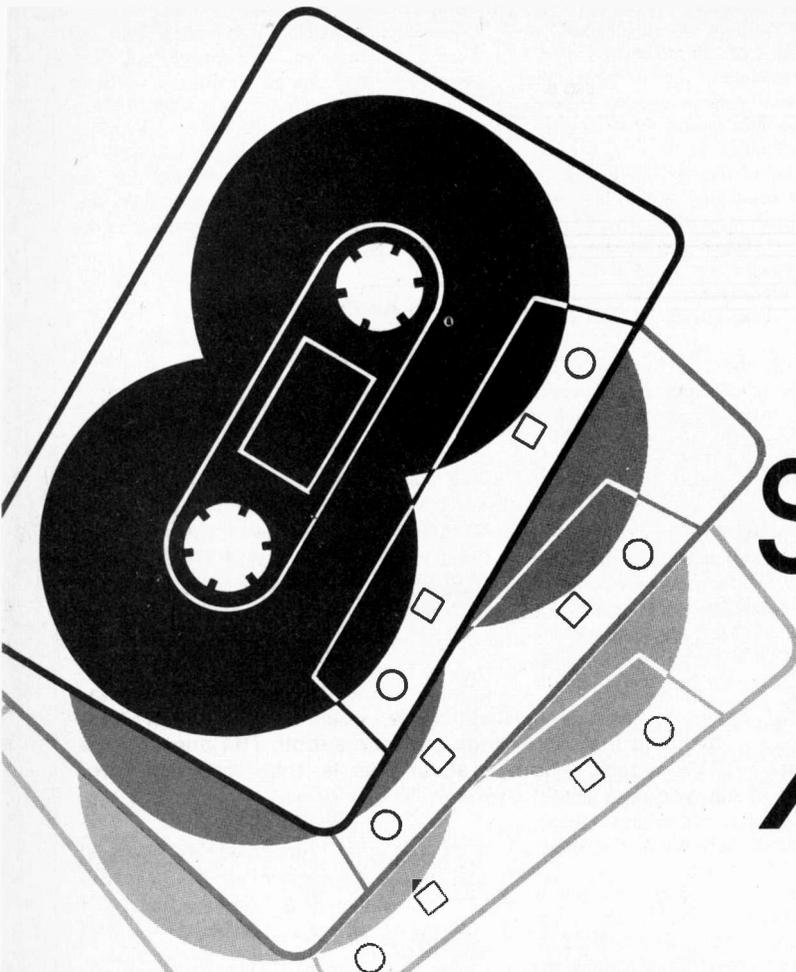Though there will be many opponents to this idea it must, in fairness to Dr. Ellis, be noted that he does not say that it is so, but that it could be.



SOUND TRACK MONITOR

J. SCHMID

WHEN two-track tapes carry a single recording extending to both tracks, the end-of-recording point on track 1 is usually some minutes away from the physical end of the tape, and for convenience both during recording and during playback the start-of-recording point on track 2 is at the same physical location. Thus, both during recording and during playback the tape has simply to be turned over to make it ready for the second track.

Now if copies of such tapes are to be made unattended, and the first side is allowed to run to the physical end of the tape, and since tape lengths are not normally exactly the same, it is not possible to simply turn over the tapes and start copying the second track. The second track of the copies would be out of synchronism with the first track by the difference in tape length. A rather tedious search for the physical location of the end-of-recording point would ensue, particularly if several copies are being made simultaneously.

The track monitor has been designed to avoid this by alerting the operator when the end of the recording (rather than the end of the reel) has been reached. It contains electronic circuitry which starts an oscillator 15 seconds after the last recorded sound has been received from the track. The 15-second delay ensures that the alarm is not raised because of intended pauses in the recording.

The oscillator is heard via a built-in loudspeaker when the selector switch is in the "Alarm" position. In the "Monitor" position the loudspeaker is connected across the programme line. There is one programme input and three programme outputs. This permits three simultaneous dubbings to be made. The instrument provides a constant 10-ohm load for the line, whether or not the speaker is used. The programme

circuit, though routed through the instrument, is not electronically processed in any way and the box can therefore serve as programme distributor, and the speaker as monitor, without being connected to mains power.

The circuit of course can be used in any situation where the cessation of speed or music on a line (whether radio, records, tape etc.) needs to be indicated by some kind of alarm signal.

CIRCUIT DESCRIPTION

The instrument is mains operated and contains a regulated +24V supply. The full-wave a.c. rectifier and filter is followed by a Zener referenced series regulator. Diode D9 temperature compensates D5. The values of C1 and C2 were chosen on grounds of adequacy and availability.

The rest of the circuit divides into sensing section and alarm section, with the relay linking the two. The programme signal is amplified by TR2, operating at 0V gate-to-source bias. Load resistor R4 is chosen to obtain a quiescent drain voltage of about 8V, so that a signal swing of up to 6V can be obtained without clipping the negative excursions. If the input of TR2 is overdriven, R2 will serve both to limit the f.e.t. gate current and to prevent any loading of the programme line. TR2 will in fact frequently be overdriven in normal operating practice.

The amplified signal is coupled through C3. R5 establishes a 0V quiescent level, from which excursions can go to +0.6 and -5.1V before being clipped by D6. The negative excursions are detected by D7 and serve to charge C4 to the negative peak level. This cuts off TR3, and the relay in its drain circuit opens.

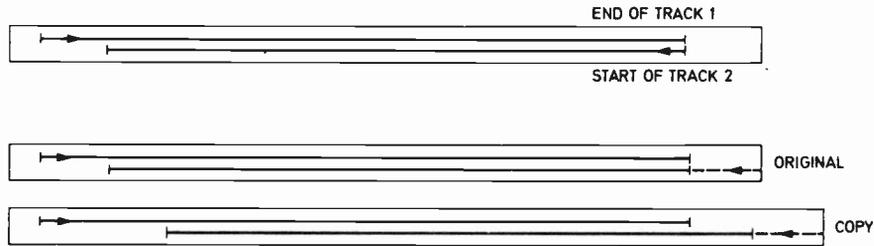


Fig. 1. Showing how copy tracks go out of sync

When no further programme signals arrive, the voltage on the gate of TR3 drifts back towards 0V as C4 discharged through R6. When the current through the f.e.t. reaches the relay switching point RLA1 pulls in and activates the alarm circuit.

The purpose of D6 is to standardise the negative excursions caused by signals of varying amplitudes, so that the return from cutoff to conduction of TR3 will take about 15 seconds regardless of whether the last recorded passage on the tape was loud or soft. TR2 must therefore provide at least a 5V signal swing to reach D6 limiting even on quiet passages, and will habitually be overdriven on loud passages. The minimum signal level on the programme line to reach limiting is 1V peak-to-peak.

The 15 second delay depends not only on the circuit time constant C4-R6, but also on the gate bias level at which TR3 provides enough drain current. When changing TR3, this level is almost bound to be different, and the easiest way to re-establish the 15-second delay is to change the circuit time constant.

ALARM SECTION

Turning now to the alarm section, this consists of

oscillator TR4 and speaker driver TR5. The unijunction transistor fires with about 6V at its emitter and then conducts heavily, pulling down the voltage on C5 rapidly to 1V, when the circuit relaxes and C5 charges up again through R7. The frequency of oscillation is about 700Hz.

The current produced when TR4 switches produces a 5V spike at R9, which is used to drive the speaker via TR5. The quiescent interbase current flow in TR4 is so small that the voltage across R9 is less than 0.6V, and TR5 is consequently non-conducting between spikes.

The advantage of using this spike (rather than the sawtooth at C5) can now be seen: because of its very short duration it requires exceptionally small dissipation in TR5, avoiding the use of large transistors (both TR1 and TR5 are 1W types). Another advantage is that this waveform provides a distinctive, harsh sound which should attract attention.

Because of the extremely short and heavy current demand by TR5, with which the regulated supply could not cope, decoupling has been introduced at TR5 collector, and D8 holds the decoupled voltage at 5V to protect both C6 and TR5.

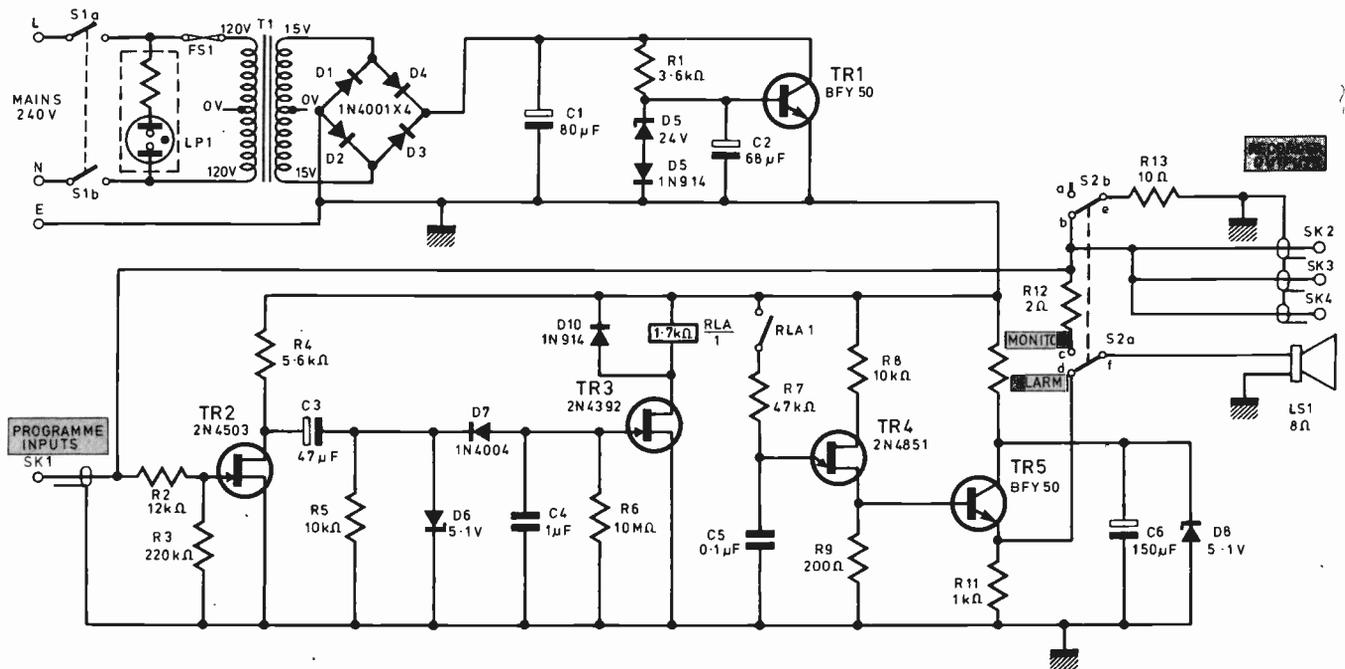


Fig. 2. Circuit of Sound Monitor

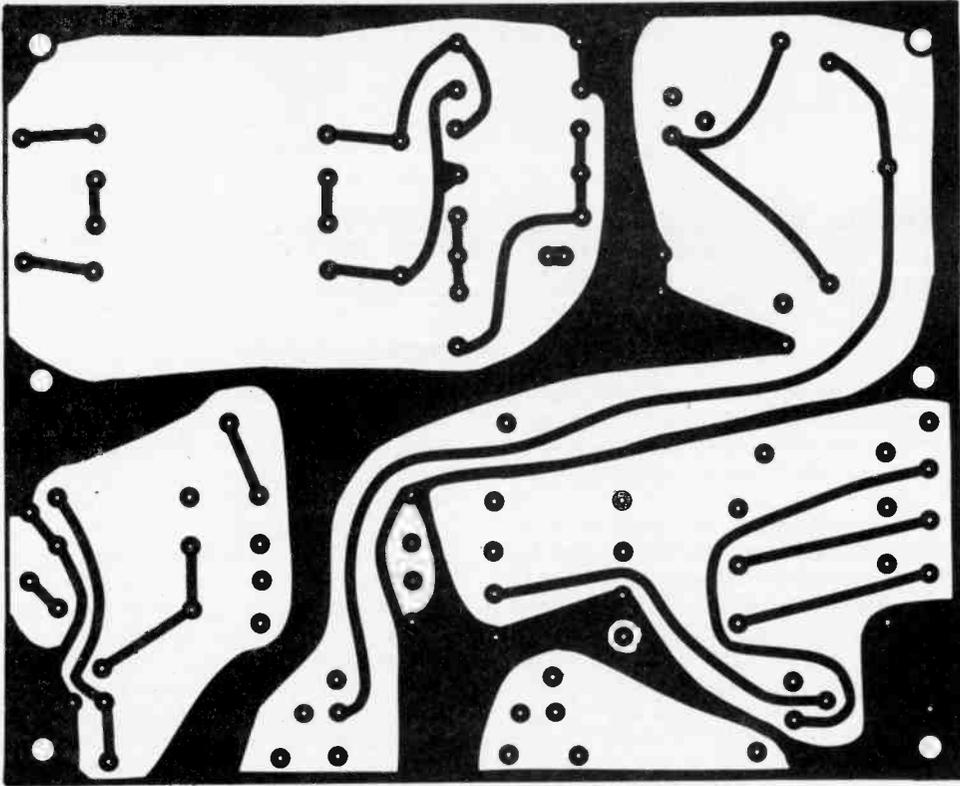


Fig. 3. P.c.b. layout for component side

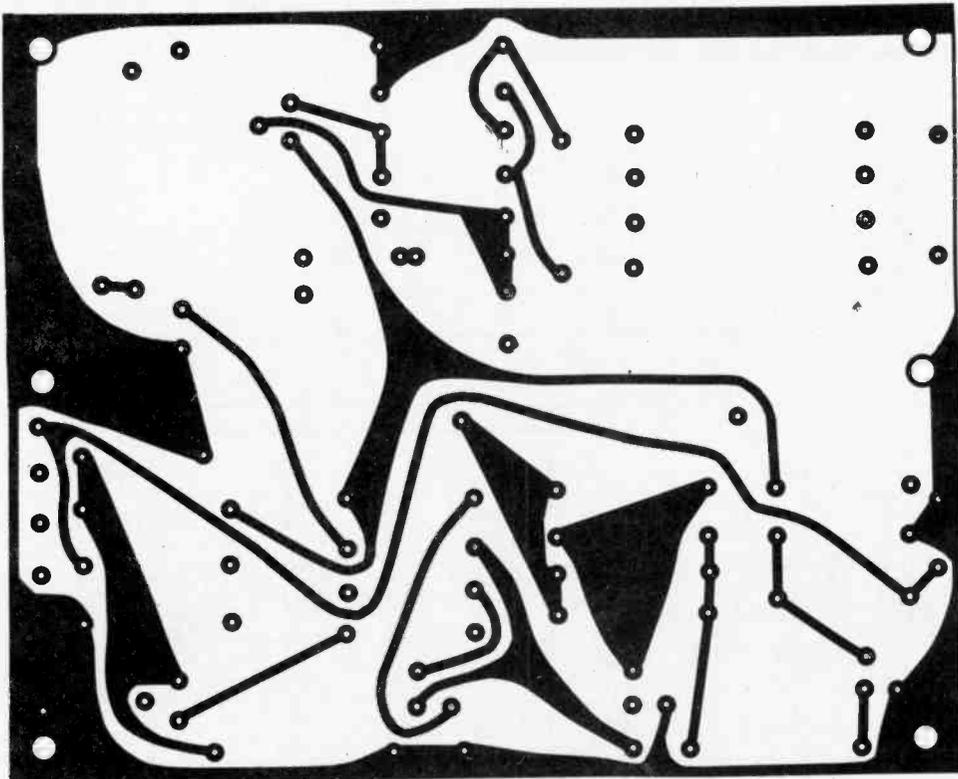


Fig. 4. Reverse of board showing p.c.b. layout

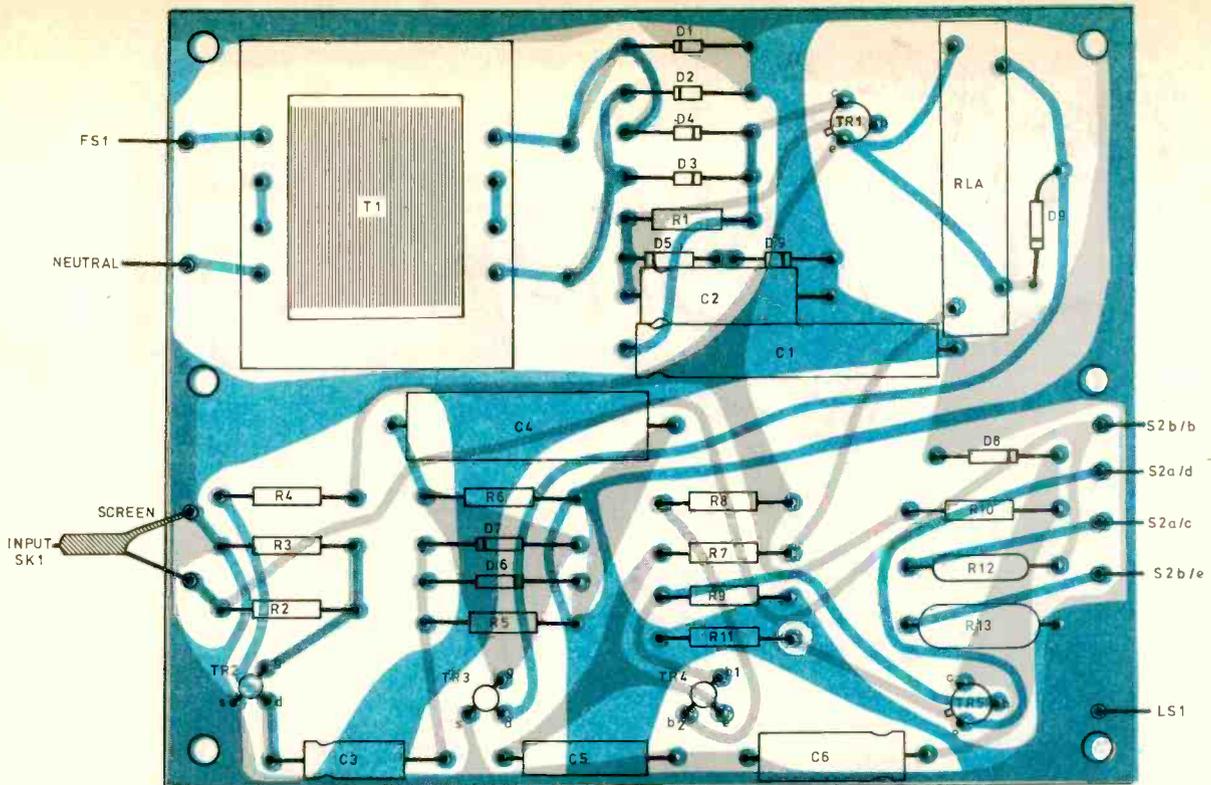


Fig. 5. Component assembly in double sided p.c.b.

At normal programme levels the speaker volume was thought to be adequate with a 2Ω series resistor R12.

No volume control is provided so that the user can gradually build up a mental picture of what constitutes the sound of correct playback volume. R13 provides an equivalent load to the line when the switch is in the "Alarm" position.

CONSTRUCTION

All components except those indicated on the front panel

are mounted on a double-sided printed circuit board. Connections to this board are made via square-pin push-on connectors. The board is held in place by six machine screws and can be withdrawn for servicing after removing these.

For the dubbing job the output was fed via a single cable looped to three DIN connectors. A similar cable with appropriate connectors was made for distributing the power from a single supply to the three recording machines, so that by turning on or off that power supply all three machines could be started or stopped simultaneously. ★

COMPONENTS . . .

Resistors

R1	3.6k Ω
R2	12k Ω
R3	220k Ω
R4	5.6k Ω
R5	10k Ω
R6	10M Ω
R7	47k Ω
R8	10k Ω
R9	200 Ω
R10	2.2k Ω $\frac{1}{2}$ W
R11	1k Ω
R12	2 Ω 3W
R13	10 Ω 2W
R14	390 Ω

All $\frac{1}{2}$ W carbon except where otherwise stated

Capacitors

C1	80 μ F elect. 50V
C2	68 μ F elect. 40V
C3	47 μ F elect. 30V
C4	1 μ F
C5	0.1 μ F
C6	150 μ F 50V

Diodes


D1-D4	1N4004 (4 off)
D5	BZY88-24 24V Zener
D6	BZY88-5.1 5.1V Zener
D7	1N4004
D8	BZY-5.1 5.1V Zener
D9	1N914

Transistors

TR1	BFY50
TR2	2N4303
TR3	2N4392
TR4	2N4851
TR5	BFY50

Miscellaneous

T1	240V pci-15V, 0.2A, 15V, 0.2A (Stock No. 207-598 R.S. Components)
LS1	1W 8 Ω loudspeaker
S1	Mains d.p.c.o
S2	S.p.c.o
RLA	Reed relay 18-30V 3k Ω (Stock No. 349-002 R.S. components)

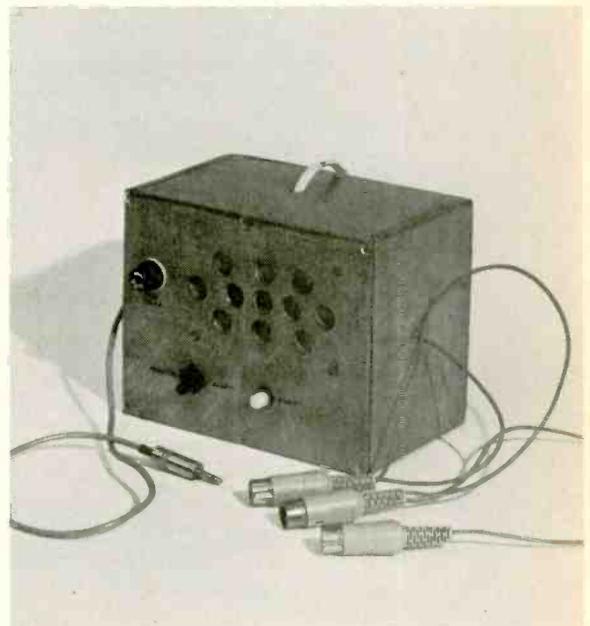



EMPHASISED BEAT

Metronome...

M. BUTT

THE electronic metronome described in this article, in addition to providing the normal variable tempo beat, can also give emphasised beat at the beginning of each bar for the common musical time signatures. The tempo of the metronome can be adjusted from approximately 33 to 220 beats per minute.

CIRCUIT DESCRIPTION

The circuit diagram of the metronome is shown in Fig. 1. The circuit uses CMOS logic i.c.s in order to minimise current consumption.

Referring to the circuit diagram, IC1a and b with the associated circuitry, form the master oscillator which runs at twice the beat frequency. The frequency of this oscillator is varied by potentiometer VR1.

IC2 is a resettable 7 stage binary divider. The master oscillator output is fed to the input of IC2 and the signal corresponding to the beat speed is taken from the divide by two output. This is inverted by IC3d and differentiated by R5 and C5, the short positive pulses so formed, enabling the

beat oscillator (comprising IC3a and b with C4 and R7). The negative pulses are clipped by the internal protection circuitry of IC3.

The output of this oscillator when enabled, is a short burst of pulses, the duration of this pulse train and its frequency being chosen to give a realistic sounding beat. This beat is fed via R4 to the output stage, which consists of a double emitter follower (TR1 and TR2), driving the loudspeaker.

When the beat oscillator is disabled, the output is high which biases TR1 and TR2 off, thus minimising current drain.

EMPHASISED BEAT

For the unemphasised beat the output from IC3c is high. D2 therefore conducts, and so VR2 with D2 forms a potential divider with R4 for the negative going portions of the beat waveforms fed to TR1. The strength of the unemphasised beat can thus be adjusted by VR2.

The divide by four, eight, sixteen and thirty-two outputs of IC2 are selected by switches S1a and b, and then fed to the two inputs of the NAND gate IC1c. The output of this is inverted by IC1d and fed to the reset input of the divider. This is reset when the number of beats selected by S1 have occurred. R2 and C2 delay the resetting long enough for C3 to be charged via D1, by the reset pulse. C3 and R3 form a hold circuit which keeps the input of IC3a high for a short time after the divider has been reset. IC3c output is inverted and so is low for this time, therefore D2 does not conduct.

The amplitude of the burst of oscillation fed to TR1 corresponding to the reset beat is greater than the other beats because VR2 has been switched out of circuit. This is the emphasised beat. The divider is reset on this beat, and begins to count again to the next emphasised beat where it is again reset.

The prototype Metronome was housed in a sloping metal case and powered by a 9 volt battery. The Time Signature control ranges from one to twelve beats to the bar.



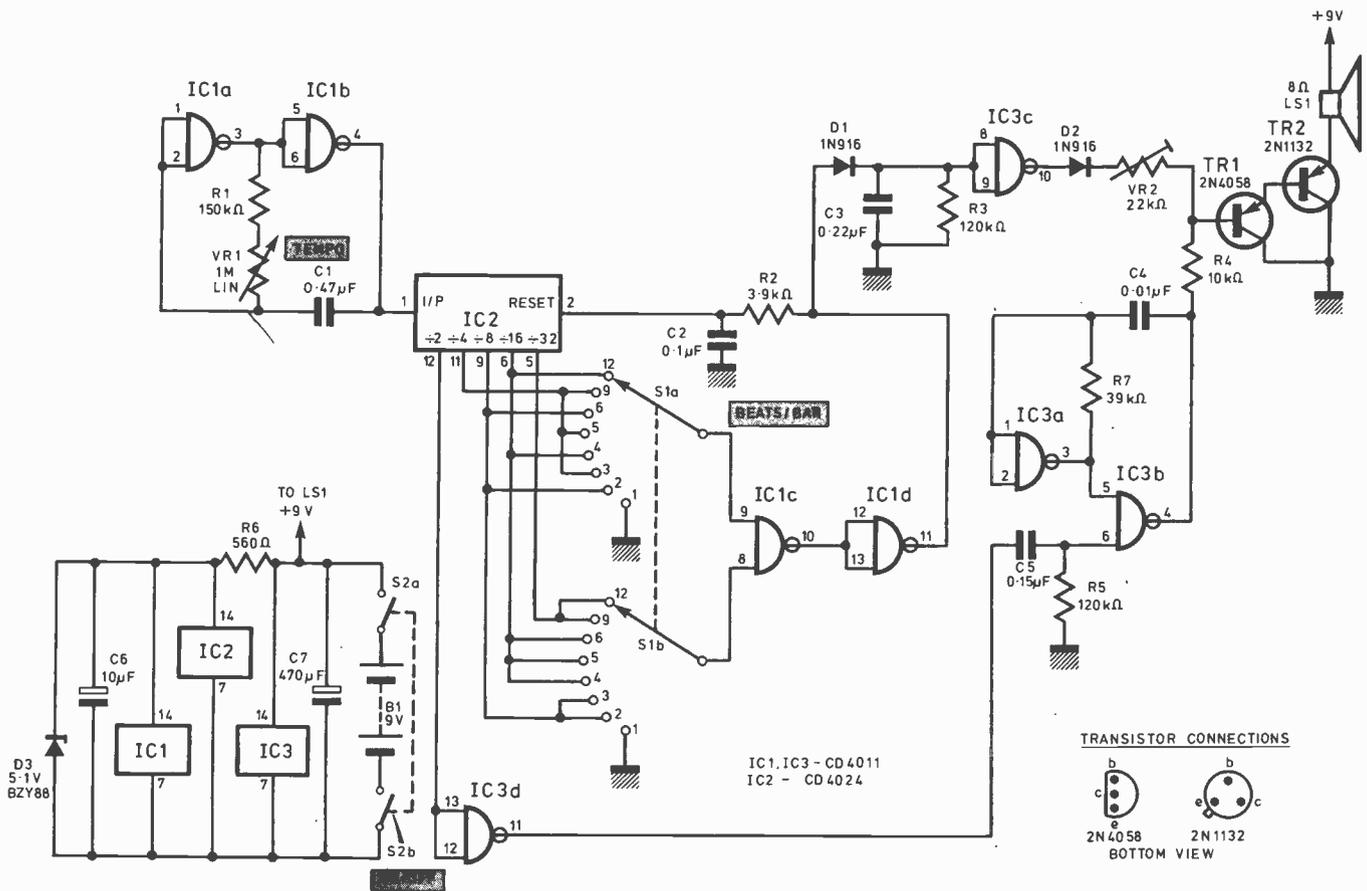


Fig. 1. Full circuit diagram of the Metronome

COMPONENTS . . .

Resistors

R1	150k Ω 2% m.o.
R2	3.9k Ω
R3	120k Ω
R4	10k Ω
R5	120k Ω
R6	560 Ω
R7	39k Ω

All resistors $\frac{1}{4}$ W 5% unless otherwise stated

Potentiometers

VR1	1M Ω lin carbon
VR2	22k Ω vert preset

Capacitors

C1	0.47 μ F 63V 2% polycarbonate
C2	0.1 μ F polyester
C3	0.22 μ F polyester
C4	0.01 μ F ceramic
C5	0.15 μ F polyester
C6	10 μ F 25V tant
C7	470 μ F 16V elect

Semiconductors

IC1, IC3	CD4011 (2 off)
IC2	CD4024
TR1	2N4058
TR2	2N1132
D1, D2	1N916 (2 off)
D3	5.1V Zener BZY88 400mW

Switches

S1	2-pole 8-way rotary wafer switch
S2	d.p.s.t. min toggle

Miscellaneous

LS1	8 Ω 57mm (2 $\frac{1}{4}$ in) dia loudspeaker, PP6 battery and clip, 0.1in matrix Veroboard (95 x 63.5mm), nuts, screws and wire. Case measuring 153 x 100 x 100mm.
-----	--

Constructor's Note

The 0.47 μ F 2% polycarbonate capacitor specified for C1 may be obtained from Minicost Trading Ltd. Tel Whixall (094 872) 464/465


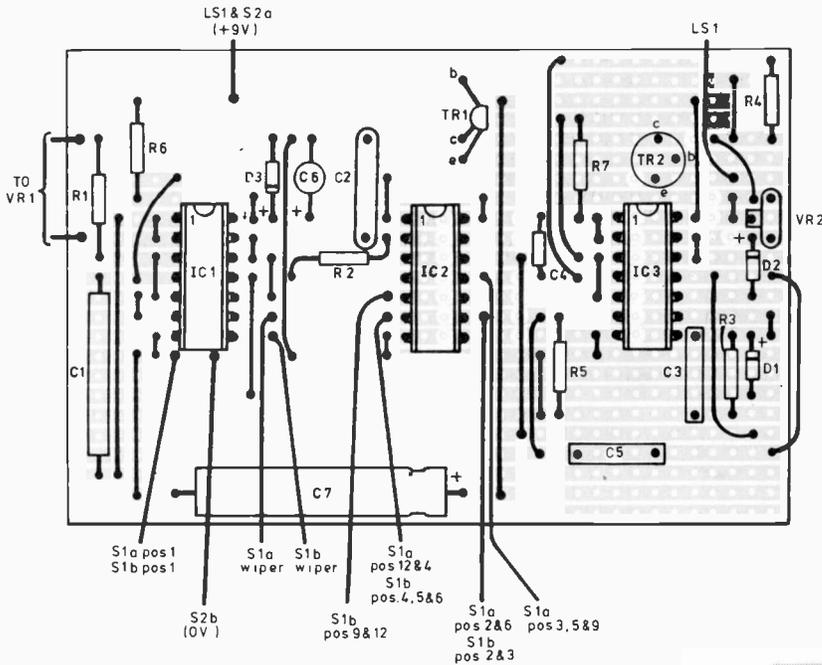


Fig. 2. Stripboard layout shown actual size



Fig. 3. Switch wiring diagram. The tag numbers refer to the beats per bar positions in order to relate to Figs. 1 and 2

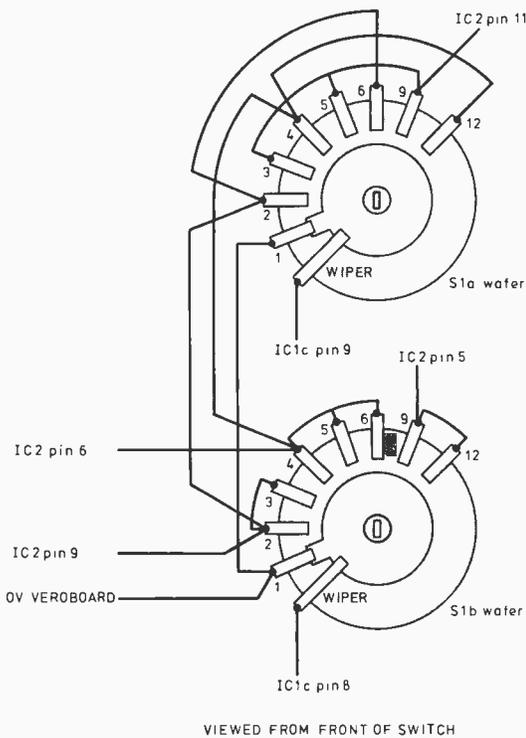


A method of mounting miniature loudspeakers which have no fastening lugs, is to fix four 6BA screw and nut assemblies around its perimeter so that they each clamp a 6BA solder tag. The soldering portion of these tags can then be pointed inwards and bent so as to captivate the loudspeaker

A simple battery clip can be made to hold the PP6, using a strip of aluminium about 25mm wide, drilled to give a 4BA fixing hole, and then formed around the battery by hand

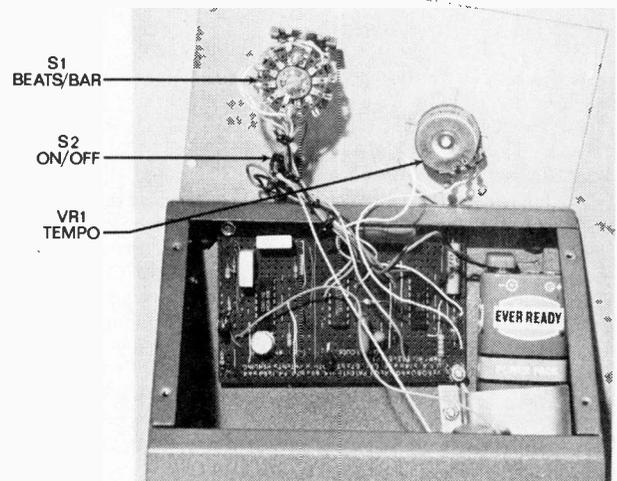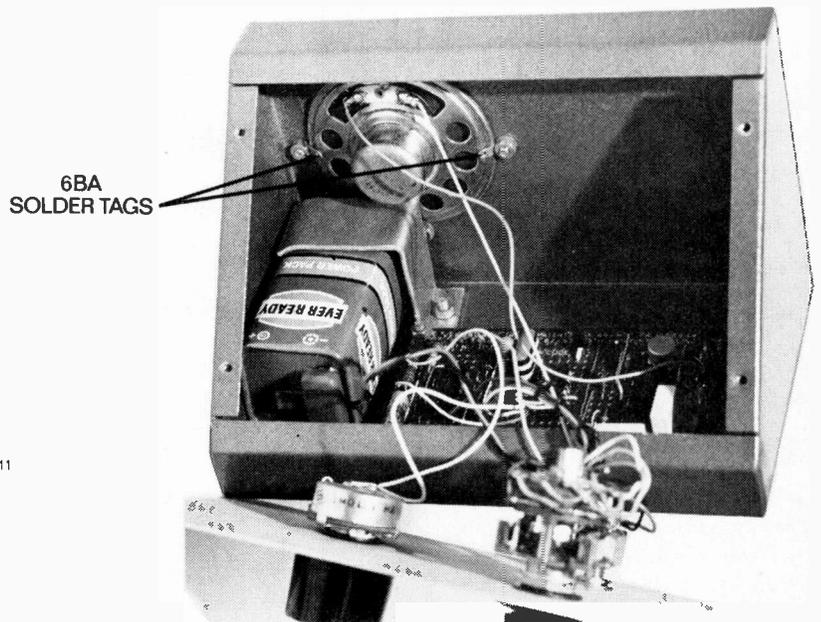Virtually any type of case will suffice to house the Metronome, but a sloping front panel will be found to have more appeal



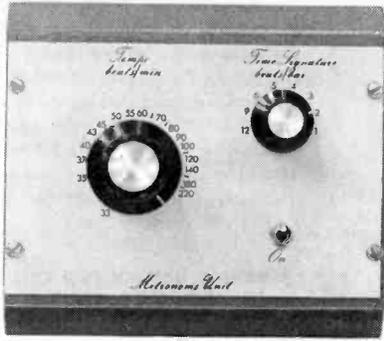

VR1 setting (beats per minute)		Name
50	—	Largo
70	—	Adagio
90	—	Andante
115	—	Moderato
144	—	Allegro
188	—	Presto

SUPPLY ARRANGEMENT

The supply to IC1 and IC2 are stabilised by D3 to keep the master oscillator stable. IC3 is supplied direct from the battery as its outputs have to swing over a larger range than the outputs of the other i.c.s. The circuit is powered from a 9V PP6 battery. The current drawn from it depends on the tempo at which the metronome is running, but is normally below 5mA.


Position 1 of the multiway switch gives a beat of one strength only, the inputs of IC1c being grounded to obtain this.

CONSTRUCTION

The circuit was assembled on 0.1 inch matrix stripboard and the layout is shown in Fig. 2. The inputs of the i.c.s used are protected by diodes, but the normal precautions taken with MOS devices should be observed to be on the safe side.

The metronome was housed in a small sloping fronted instrument case and the front panel labelled with dry transfer labels. A number of small holes were drilled in the case in front of the speaker.

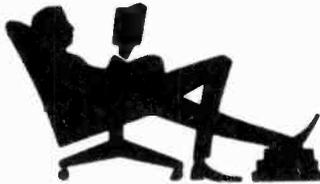The wiring of the multi way switch wafers is shown in Fig. 3, and if wired as shown, give minimum tempo in the fully anti-clockwise position. The metronome can be calibrated using a stopwatch or the second hand of a watch. ★



BOOK REVIEWS

MASTER IN-CAR ENTERTAINMENT

By Vivian Capel

Published by Newnes Technical Books.

122 pages, 135 x 215mm. Price £2.50.

SHOULD anyone consider installing an in-car music system, who is not a hi-fi or electronics "whizz-kid" as such, they would find this book most useful. The explanations throughout are very understandable to the non-technical mind. Coverage of the various options for entertainment source is comprehensive, and would assist a quick decision on which type of radio or tape machine to use if you were in doubt.

With hints and tips on both installation and fault finding, and methods of identifying and curing interference, the d.i.y. car improver could be saved considerable "aggro" by consulting this book. It is all easy to follow, and the use of spot-colour has enhanced the simplicity of electronic and mechanical diagrams.

Chapters are: The Car Equipment Scene, Mono Stereo Or Quad?, Mobile Tape Players, The Cartridge Player, The Cassette Player, Cassette Or Cartridge?, Car Radios, Car Antennas, Interference Suppression, Installing The System, and Trouble Shooting.

In Chapter 9 the author suggests that interference due to static in the bodywork can be identified by coasting down a hill with the engine switched off. I would imagine that this practice, along with the driver's concentration on interference coming from his new hi-fi installation, could well result in some sound effects far more realistic and convincing than any stereo or quad system might produce!

M.A.

PE

A Volume of Practical Know-how

... can be made using these new-look self binders for PRACTICAL ELECTRONICS to become your most valuable source of reference. With the Easi-Binder current copies can be inserted as they are received, without waiting for the completion of twelve issues.

They are attractively made with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers, please advise year and volume and a separate set of gold transfer figures will be supplied.

At **£2.85** inc. VAT and postage (£3.45 overseas) they are obtainable from:

Post Sales Department, IPC Magazines Ltd.
Lavington House, 25 Lavington Street
London SE1 0PF


I enclose P.O./cheque value for binders at **£2.85** each (£3.45 overseas) for **Practical Electronics** Vol. No's

Name

Address

Date

PE

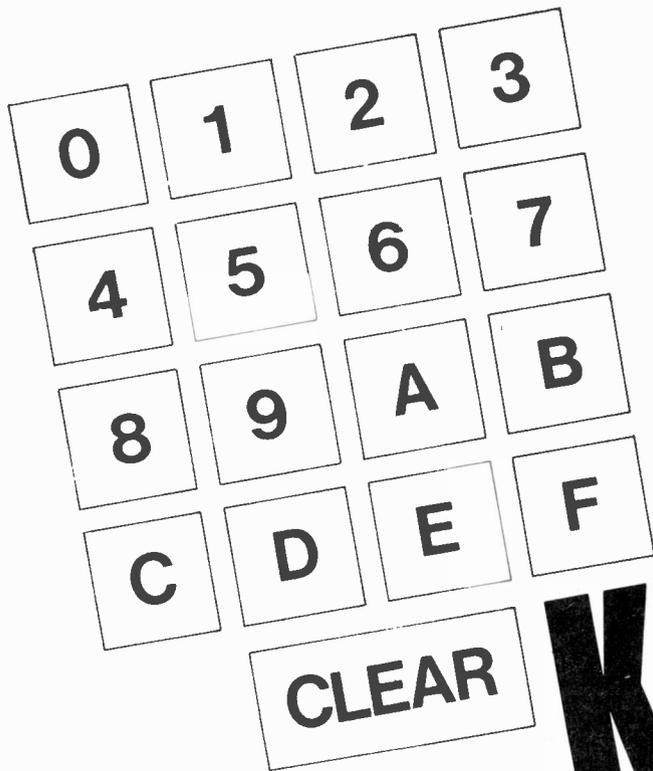

Easy to build keyboard that provides an eight bit binary word by pressing two keys with l.e.d. readout

By L.G. PARKIN B.A.

KEYBOARD

MOST microprocessors that are suitable for amateur use need data input in the form of an eight bit binary word and hexadecimal characters form a convenient way of handling such data.

The keyboard described here provides an eight bit binary word by pressing two keys in succession. Pressing the first key lights up one of the "byte" l.e.d.s (this is a reminder that another key has yet to be pressed for the full code). At the same time, the binary code corresponding to that character appears in the four left-hand l.e.d.s (H, G, F, E). Each lit l.e.d. represents a "1". Pressing another key puts the binary code for that character into the four right-hand l.e.d.s (D, C, B, A). The second byte l.e.d. now lights, indicating that the full eight bit word is assembled, and a signal is sent to the microprocessor that the data is ready. At any time, the data word can be set to all noughts by pressing the "Clear" key, or by a signal from the microprocessor itself.

This type of keyboard is much simpler to build than a full ASCII keyboard, and it is just as effective if programs are written in machine code.

There are i.c.s available specially developed to do this job, but they are expensive, and they certainly don't crop up in the amateur's stock of i.c.s, or in scrap computer boards.

This project was designed to use common i.c.s and the matrix diodes can be any silicon type. The ones used in the prototype came from an untested lot of 100 for 60p, advertised as "similar to 1N914". About 90 per cent of these were found to be good.

Power supply for the keyboard is standard TTL 5V at about 150mA (all l.e.d.s lit).

SETTING THE CODE

The full circuit is shown in Fig. 1. To help in identification, each pin of an i.c. is labelled with two numbers separated by a hyphen. Thus IC7-10 means pin 10 of IC7.

We can follow the operation of the keyboard by taking an example. Suppose we have a SC/MP microprocessor, and we wish to enter the code for "Load the accumulator". This is 1100 0100 in binary, or C4 in hexadecimal. Before any key is pressed, both data bistables (IC8) are in the reset state, so IC8-8 is at logic "1". This prepares the four gates of IC1 for a key being pressed. Suppose key "C" is now pressed. Lines c, d, and K go to logic "1", so NAND gate outputs IC1-3 and IC1-6 becomes logic "0".

The "0" on IC1-3 sets IC3-3 bistable output to logic "1", and the "0" on IC1-6 sets IC3-6 to logic "1". L.e.d.s G and H light, so setting up the left hand byte (1100).

Line K (now at logic "1" remember) charges C1 through R1, so the Schmitt trigger input IC7-5 arrives at logic "1" level, and IC7-6 goes to logic "0". This has no effect on the clock inputs of IC8 data bistables—they need a positive going edge.

However, when the key is released after setting up the first byte, there is a short delay while C1 discharges (about 10 milliseconds), then IC7-5 returns to logic "0". IC7-6 therefore goes to logic "1", and clocks IC8 bistables. IC8-9 changes to logic "1", but IC8-5 stays at "0" because its data input IC8-2 is at logic "0" when the clock pulse occurs. The "1" on IC8-9 prepares the gates of IC2 for the next key being pressed. The first "byte" l.e.d. is now lit.

Now, key "4" is pressed. This raises lines c and K to logic "1", IC2-3 becomes logic "0", so changing bistable output IC5-3 to logic "1", and l.e.d. C lights. The right hand byte is now set up (0100), and the full eight bit binary code is displayed in the l.e.d.s.

When the key is released, IC7-5 drops to logic "0" level, so IC7-6 rises to logic "1". This clocks the upper data bistable of IC8, so that IC8-5 now rises to logic "1" (its data input is at "1" level). The second "byte" l.e.d. now lights, and the output of IC8-5 also provides a signal to the microprocessor that the keyboard data is "ready".

The eight data bits, and their complements if required, are available to the microprocessor from the outputs of IC3, IC4, IC5, and IC6.

RESET


The "Reset" line shown in Fig. 1 is connected to the reset inputs of all bistables. If this line is pulled down to near 0V, all bistables will be reset. This must be done before another word is set up. There are three ways in which this can happen:

(1) **Keyboard reset.**—This is simple—the "Clear" key is pressed, which earths the reset line.

(2) **Microprocessor controlled.**—A logic "0" from the microprocessor to the "External reset" line does the same job as pressing "Clear". The diode D2 (a germanium diode for low volts drop) prevents the "External reset" line being pulled down when "Clear" is pressed. Note that the external reset line is resetting 10 i.c.s, so the reset signal from the microprocessor must come from a device capable of doing this. A normal TTL gate has a fan-out of 10, so this is no problem.

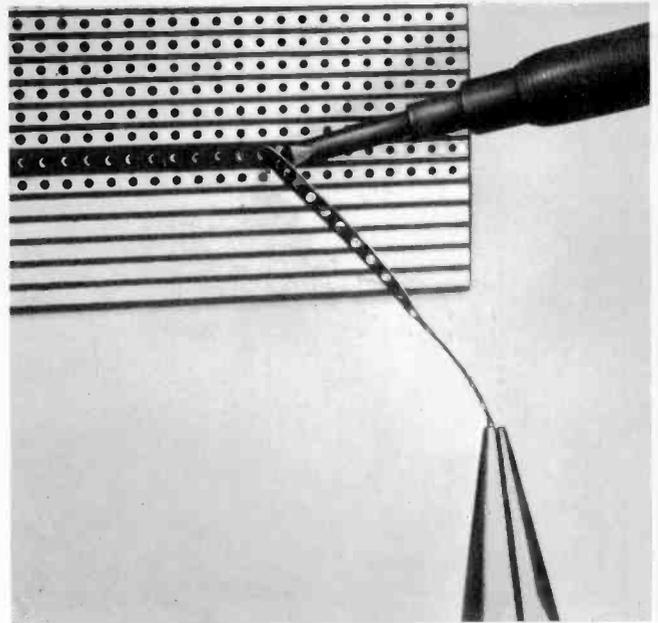(3) **Automatic reset.**—If nothing deliberate is done to clear the keyboard before another data word is entered, the previous data will be cleared automatically at the instant another key is pressed. Any key being pressed will raise line K to logic "1". IC7-8 falls to logic "0", and takes the reset line down to logic "0". All bistables reset, and IC8-5 goes to logic "0". IC7-9 also goes to logic "0", so closing that gate. Keeping the key down has no further effect on the reset circuit.

All this takes only a few milliseconds, so, while the key is still pressed, the left hand four bits of the new code are set into IC3 and IC4. Pressing another key sets up the remainder of the new data word. Using this facility, and some cunning program writing, data can be put into memory simply by pressing two consecutive keys.



Lifting a copper strip with iron and pliers

CONSTRUCTION

Veroboard is a convenient way of making the diode matrix, so the same board is used for the remainder of the circuit.

Cut a piece of 0.1 matrix Veroboard, 40 holes by 34, with the copper strips running across the long dimension. Remove four of the strips, as illustrated. This is done by heating the strip with a soldering iron, lifting the strip gently with pliers, and running the iron ahead of the point where the strip is lifting (see photo). Cut the copper tracks, as shown in the illustration, with a $\frac{1}{16}$ in drill.

COMPONENTS . . .

Resistors

R1	100 Ω
R2	470 Ω
R3	270 Ω
R4-R7	470 Ω (4 off)
R8-R9	1k Ω (2 off)
R10-R19	330 Ω (10 off)

Capacitors

C1-C2	10 μ F elect. 10V (2 off)
C3	0.1 μ F

Diodes


D1-D48	1N914 (any general purpose silicon) (48 off)
D49-D50	AA120 (2 off)

Integrated Circuits

IC1-IC6	7400 (6 off)
IC7	7413
IC8	7478

Keyboard

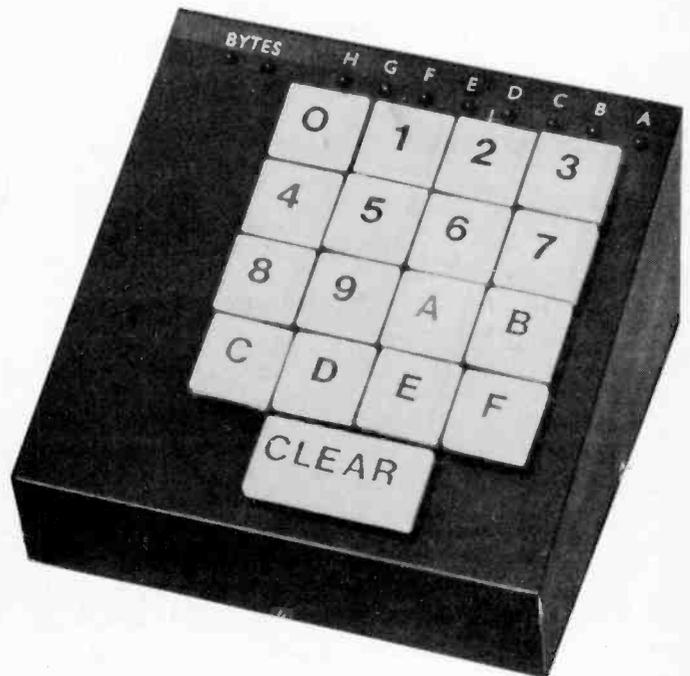S1-S17 S.p.s.t. push-to-make keyboard switches (17 off)
A double blank cap can be obtained for the "Clear" key (R.S. Components)



Wiring Schedule—Circuit Board

Component	From	To	Component	From	To
Wire	IC1-1	Row c	Wire	IC7-12	IC7-13
Wire	IC1-2	IC1-5	Wire	IC5-7	Earth
Wire	IC1-3	IC3-2	Wire	IC5-10	Reset row
Wire	IC1-4	Row d	Wire	IC5-13	IC5-10
Wire	IC1-5	IC8-8	Wire	IC5-14	5V row
Wire	IC1-6	IC3-5	Wire	IC6-1	IC6-11
Wire	IC1-7	Earth	Wire	IC6-4	IC6-8
Wire	IC1-8	IC4-2	Wire	IC6-7	Earth
Wire	IC1-9	Row a	Wire	IC6-10	Reset row
Wire	IC1-11	IC4-5	Wire	IC6-13	IC6-10
Wire	IC1-12	Row b	Wire	IC6-14	5V row
Wire	IC1-14	5V row	Wire	IC7-1	IC7-2
Wire	IC2-1	IC1-1	Wire	IC7-2	IC7-4
Wire	IC2-2	IC2-5	Wire	IC7-6	IC8-3
Wire	IC2-3	IC5-2	Wire	IC7-7	Earth
Wire	IC2-4	IC1-4	Wire	IC7-9	J row
Wire	IC2-5	IC8-9	Wire	IC7-14	5V row
Wire	IC2-6	IC5-5	Wire	IC8-1	IC8-13
Wire	IC2-7	Earth	Wire	IC8-2	IC8-9
Wire	IC2-8	IC6-2	Wire	IC8-3	IC8-11
Wire	IC2-9	IC1-9	Wire	IC8-7	Earth
Wire	IC2-11	IC6-5	Wire	IC8-13	Reset row
Wire	IC2-12	IC1-12	Wire	IC8-14	5V row
Wire	IC2-14	5V row	R1 (100Ω)	K row	IC7-5
Wire	IC3-1	IC3-11	R2 (470Ω)	IC7-5	Earth
Wire	IC3-4	IC3-8	R3 (270Ω)	IC8-5	J row
Wire	IC3-7	Earth	R4 (470Ω)	d row	Earth
Wire	IC3-10	IC3-13	R5 (470Ω)	c row	Earth
Wire	IC3-13	Reset row	R6 (470Ω)	b row	Earth
Wire	IC3-14	5V row	R7 (470Ω)	a row	Earth
Wire	IC4-1	IC4-11	R8 (1kΩ)	IC8-12	5V row
Wire	IC4-4	IC4-8	R9 (1kΩ)	IC7-1	5V row
Wire	IC4-7	Earth	C1 (10μF)	IC7-5 (pos)	Earth (neg)
Wire	IC4-10	IC4-13	C2 (10μF)	J rows (pos)	Earth (neg)
Wire	IC4-13	Reset row	C3 (0.1μF)	5V row	Earth
Wire	IC4-14	5V row	D1 (germanium)	IC7-8	Reset row
Wire	IC5-1	IC5-11	D2 (germanium)	Reset row	Ext. reset row
Wire	IC5-4	IC4-8	Wire	Earth (upper)	Earth (lower)
Wire	IC7-4	IC7-12	Wire	Reset (upper)	Reset (lower)

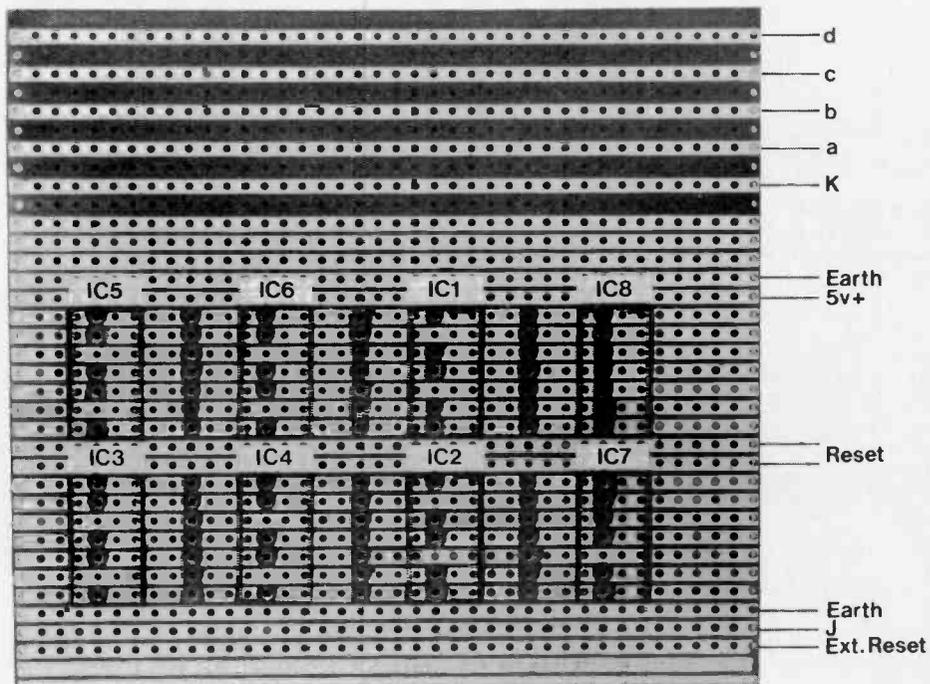


Fig. 2. Identification of rows on the circuit board for the wiring schedule. Copper cuts for the i.c.s are also shown


Wiring Schedule—Keys and I.e.d.s

Component	From	To	Component	From	To
Wire	Key 0	"0" column	R10 (330Ω)	Pad H	I.e.d. H (pos)
Wire	Key 1	"1" column	R11 (330Ω)	Pad G	I.e.d. G (pos)
Wire	Key 2	"2" column	R12 (330Ω)	Pad F	I.e.d. F (pos)
Wire	Key 3	"3" column	R13 (330Ω)	Pad E	I.e.d. E (pos)
Wire	Key 4	"4" column	R14 (330Ω)	Pad D	I.e.d. D (pos)
Wire	Key 5	"5" column	R15 (330Ω)	Pad C	I.e.d. C (pos)
Wire	Key 6	"6" column	R16 (330Ω)	Pad B	I.e.d. B (pos)
Wire	Key 7	"7" column	R17 (330Ω)	Pad A	I.e.d. A (pos)
Wire	Key 8	"8" column	R18 (330Ω)	Pad B1	I.e.d. B1 (pos)
Wire	Key 9	"9" column	R19 (330Ω)	Pad B2	I.e.d. B2 (pos)
Wire	Key A	"A" column	Wire	Case earth	Cct. board earth
Wire	Key B	"B" column			
Wire	Key C	"C" column			
Wire	Key D	"D" column			
Wire	Key E	"E" column			
Wire	Key F	"F" column			
Wire	Key "Clear"	Reset row			
Wire	5V row	Keys "0" to "F" (one side of each)			
Wire	Earth	"Clear" key (other side)			
Wire	Pad A	IC6-3			
Wire	Pad B	IC6-6			
Wire	Pad C	IC5-3			
Wire	Pad D	IC5-6			
Wire	Pad E	IC4-3			
Wire	Pad F	IC4-6			
Wire	Pad G	IC3-3			
Wire	Pad H	IC3-6			
Wire	Pad B1	IC2-13			
Wire	Pad B2	IC8-5			


Connections of a 16 pin plug (mating to microprocessor)

- pin 1—bit A (least significant)
- pin 2—bit B
- pin 3—bit C
- pin 4—bit D
- pin 5—bit E
- pin 6—bit F
- pin 7—bit G
- pin 8—bit H (most significant)
- pin 9—common earth
- pin 10—interrupt key
- pin 11—go key
- pin 12—reset key
- pin 13—run/program key
- pin 14—reset line from microprocessor
- pin 15—keyboard flag to microprocessor
- pin 16—5V supply

Fig. 3. Showing the connection of the matrix diodes and i.c.s

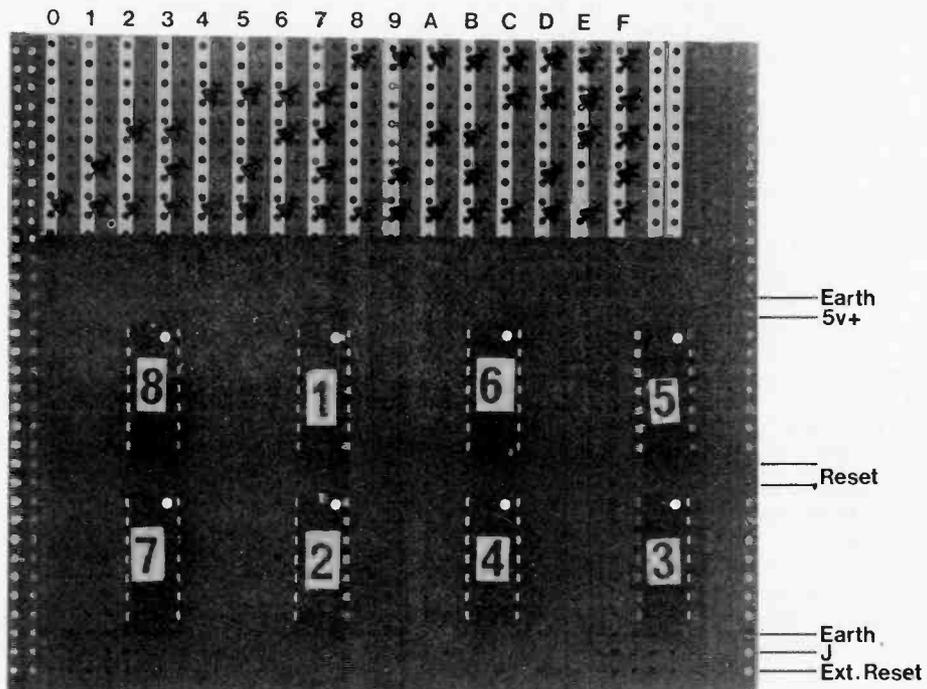

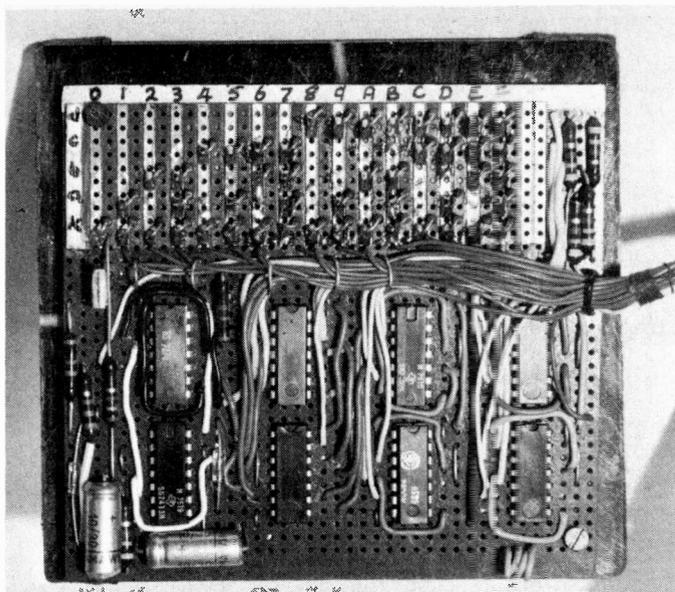Main board prototype showing component layout and surface wiring. Note that the copper tracks of the two boards for the diode matrix are at right angles and the diodes are mounted diagonally so that each diode wire passes through the copper strip of only one board



Mount the ten I.e.d.s by gluing them with Araldite into the holes in the top panel, so that they just project above the surface. When the glue has set, connect each I.e.d. negative wire to the earth strip on the inside of the back panel. Connect the positive wires to the appropriate pad on the same panel.

Now follow the wiring schedule again, connecting the ten I.e.d. resistors, and the keyswitches, to the circuit board. Connect power and output wires. Mount the circuit board to the base panel, using 8 BA screws and insulating spacers. Take the power and output wires, plus eight wires from the unallocated keys, through the hole in the back panel.

TESTING

When power is first applied to the keyboard, a random display will probably appear. Press "Clear", and then a single key. One "byte" lamp should light, and the I.e.d.s H to E should display the chosen code. Press a second key, and I.e.d.s D to A should respond to that code. Check that both "byte" I.e.d.s are now lit.

A quick check on all I.e.d.s can be made by keying in "FF", which lights them all. Now test each key methodically, including the "Clear" key, which should always extinguish all I.e.d.s. One can assume that if the correct code appears in the display, it will also be presented to the microprocessor.

The design has been checked for repeatability, by building a second unit, which worked first time power was applied. Compatibility with the requirements of a microprocessor was checked by using the keyboard to input data to a Motorola 6800 evaluation kit.

KEYSWITCHES

The keyswitches used came from a desk calculator keyboard, sold for 50p, but supplies of these in the surplus shops is very spasmodic, so it is a case of scanning current advertising. The front panel dimensions given suit a keyswitch no larger than $\frac{3}{4}$ in square. Radiospares list a keyboard switch which measures less than $\frac{5}{8}$ in square, and this would be suitable in this design, though more expensive.


A useful feature of the design of this project is that it needs only a simple "make" contact for each key. Sophisticated low contact bounce double throw switches are not needed, so there is scope for personal ingenuity, even if the resulting keyswitch is electrically rather crude.

Prepare another board, 34 holes by 10, with the copper strips running across the short dimension. Remove alternate

strips, giving the pattern shown. Glue this board face to face with the larger board, with the copper strips at right angles. Use pins passing through both boards in two places to keep the holes in alignment until the glue sets. The relative positions of the two boards can be seen in the photo.

Next, mount the matrix diodes on the copper side of the smaller board, in the pattern shown. Each diode has its anode connected to a hole in a copper strip of the smaller board, and its cathode is taken through holes in both boards, to row a, b, c, d, or K of the larger board. When wiring the diodes of row K, leave the anode wires projecting about $\frac{1}{4}$ in beyond the board. These will serve as pins to which the wires to the keyboard are attached.

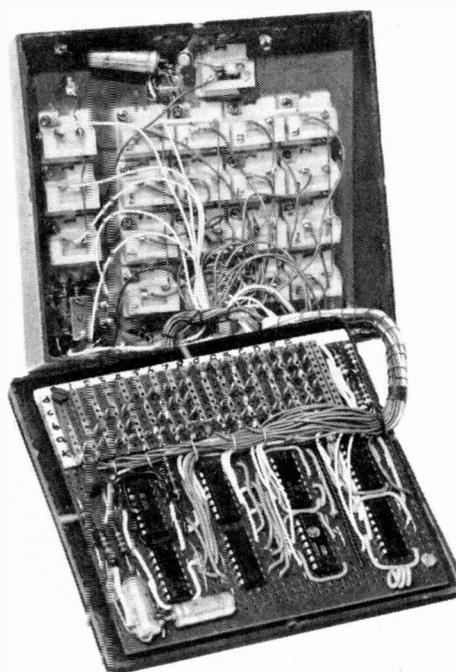Solder the i.c.s in position, with the locator of each towards the matrix. Now follow the Wiring Schedule to complete the assembly of the board. ★





PATENTS REVIEW...

BP 1509 212

The Federal Communications Commission in the USA is currently considering which of five rival systems should be adopted to provide the option for stereo transmissions on the AM (amplitude modulation) medium and long wave bands.

The five systems originate from Belar, Harris, Magnavox, Motorola and Leonard Kahn, a pioneering inventor in this field.

Kahn's system is favoured in some quarters because he claims that it enables anyone owning two existing AM mono sets to receive stereo without the need to purchase any additional equipment.

Doubtless with an eye to the likely adoption by the UK of whatever AM system is chosen by the FCC, Kahn has over recent years been busily patenting his ideas in the UK (BPs 970 051, 1 119 333 and most recently 1509 212).

Copies of Patents can be obtained from :
the Patent Office Sales, St. Mary Cray, Orpington, Kent Price 95p each


Optionally an infrasonic frequency (eg. 15Hz) is also impressed on the carrier to provide a switching signal for receivers equipped to decode stereo. Kahn suggests that for mono compatibility with existing radio receivers the transmitted signals should have the carrier wave envelope modulated by the stereo sum signal (L + R) and phase modulated by the difference signal (L - R). Existing sets receive only L + R and reproduce a mono sum signal; sets equipped with a stereo decoder matrix L + R and L - R to reproduce L and R as a stereo pair.

In Kahn's most recent patent he proposes a modified means of phase modulating the carrier with the difference signal. The claim is that, by phase modulating the carrier with a stereo difference signal formed from L-R fundamental, together with added second harmonic content varying in amplitude as a square law function of the fundamental,

stage. To develop the phase modulation components for the carrier the L and R signals are also fed to a difference circuit 28 and a +45° phase shift imparted to one fraction of the output. This signal now serves as the fundamental phase modulation component and is fed to sum circuit 36.

Further output fractions of the difference circuit 28 are fed to frequency doublers 46 and 48 and the harmonic outputs of these doublers routed to difference circuit 54. The frequency doubled difference output passes through a level squarer formed by a variable gain amplifier 58, controlled by a fraction of the fundamental component tapped off ahead of sum circuit 36.

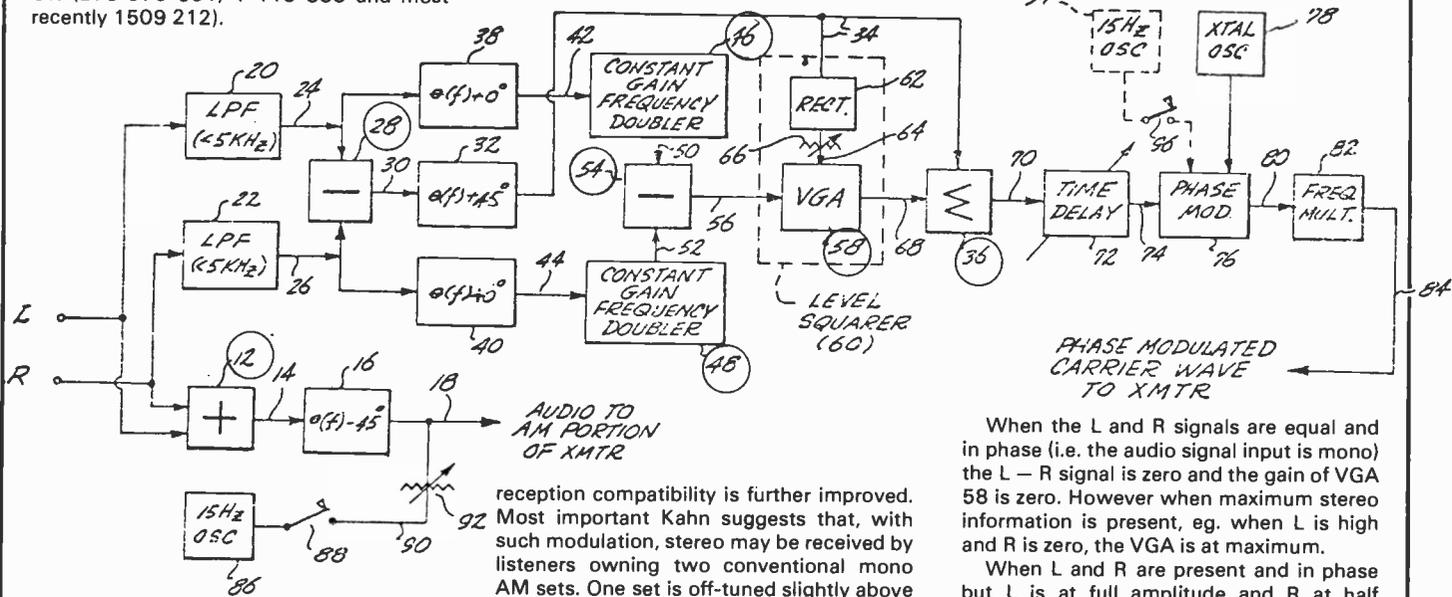The VGA feeds sum circuit 36 of which the output is supplied via a time delay to the transmitter for phase modulation of the carrier.



reception compatibility is further improved. Most important Kahn suggests that, with such modulation, stereo may be received by listeners owning two conventional mono AM sets. One set is off-tuned slightly above the carrier and the other slightly below the carrier to provide combined reception in the stereophonic mode.

The figure shows the transmitter encoder. Left and right signals (L and R) are summed at 12 and, with the addition of a -45° phase shift, the sum signal used without further treatment to amplitude modulate the transmitted carrier. The 15Hz stereo switching tone may also be added at this

When the L and R signals are equal and in phase (i.e. the audio signal input is mono) the L - R signal is zero and the gain of VGA 58 is zero. However when maximum stereo information is present, eg. when L is high and R is zero, the VGA is at maximum.

When L and R are present and in phase but L is at full amplitude and R at half amplitude the gain of VGA is reduced to limit the second harmonic component.

It follows that when stereo information is present the phase modulating component is composed not only of the fundamental of the stereo difference signal but also a controlled amount of frequency doubled difference signal, the level of the latter being a square law function of the fundamental.

If Kahn's system is chosen by the FCC, these and the American equivalent patents could quite conceivably make Kahn a millionaire.

The basic concept as protected by BP 970 051 is that of modulating the transmitted carrier wave so that the stereo related intelligence appears as respective upper and lower sidebands.

U.K. RETURN OF POST MAIL ORDER SERVICE also WORLDWIDE EXPORT SERVICE

R.C.S. 10 WATT AMPLIFIER KIT



This kit is suitable for record players, tape play backs, guitars, electronic instruments or small P.A. systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume, bass and treble controls. Spec. 10W output into 8 ohms, 1W into 15 ohms. Response 20c/s to 30kc/s. Input 100mV, high imp. Size 9 1/2 x 3 x 2in. A/C mains operated.

Mono kit **£12.50** Stereo kit **£20** post 45p
Easy to build Full instructions supplied



ELAC SPEAKER 10 inch £4.50

Twin cone. Large ceramic magnet 50-16,000 c/s. Bass resonance 55 c/s. 10W. 8 ohm impedance.

RCS STEREO PRE-AMP KIT. All parts to build this pre-amp. Inputs for high, medium or low imp. per channel, with volume control and P.C. Board. Can be ganged to make multi-way mixers.

£2.95 Post 35p

MAINS TRANSFORMERS

ALL POST 75p each

250-0-250V 70mA, 6.3 2A	£3.45
250-0-250 80mA, 6.3V 3 5A, 6.3V 1A or 5V 2A	£4.60
350-0-350 80mA, 6.3V 3 5A, 6.3V 1A or 5V 2A	£5.80
300-0-300 120mA 2 x 6.3V 2A C.T., 6.3V 2A	£8.50
220V 45mA, 6.3V 2A	£1.75
HEATER TRANS. 6.3V 3A, £1.45, 1/2 amp.	£1.00
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V	£5.30
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 80	£5.30
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£8.50
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£11.00
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£14.50
5, 8, 10, 16V 1/2A £2. 12V 100mA £1. 12V 300mA £1.	

12V 750mA **£1.30**. 40V 2A tapped 10V or 30V **£2.95**. 20V 2A **£2**. 40V 2A **£2.95**. 30V 5A 34V 2A ct. **£3.75**. 2 x 18V 6A **£9**. 12-0-12V 2 amp **£2.95**. 20-0-20V 1A **£2.95**. 30V 1A **£2.75**. 20V 1A **£2.20**. 9V 3 amp **£2.75**. 60V, 40V, 20V or 20-0-20V, 1A **£3.50**. 30-0-30 2A **£7**. 9V 250mA **£1.30**.

AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £5; 250W £8; 400W £7; 500W £8. CHARGER TRANSFORMERS Input 200/250V for 6 or 12V 1 1/2 £2.75; 4A £5.20. FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs 1 1/2A 40p; 2A 55p; 4A 95p. HALF WAVE 12V 1 1/2A 25p.

GOODMAN'S COMPACT 12in BASS WOOFER

Standard 12in diameter fixing with cut sides 10 1/2in square 14,000 gauss magnet. 3watt r.m.s. 4 ohm impedance. Bass resonance 30 c/s. Frequency response 30-8,000 c.p.s. £10.95 each. Post £1.00. 20 Watt model £9.95.



10 WATT PER CHANNEL STEREO AMPLIFIER In chassis form. A.C. mains operated. Volume, balance, treble and bass slider controls. Pick up and tape inputs. Recording output. Socket. Front panel size: 16 1/2 x 1 1/2in. Chassis size: 13 x 1 1/2in. Bargain **£18.50** Post 50p

HEATING ELEMENTS WAFER THIN

Size 10 1/2 x 8 1/2 in Operating voltage 200/250V a.c. 250W approx Suitable for Heating Pads, Food Warmers, Convector Heaters etc Must be clamped between two sheets of metal or asbestos **ONLY 40p EACH (FOUR FOR £1.50)** ALL POST PAID—Discounts for quantity

E.M.I. 13 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover.

10W Model	£7.95
State 4 or 8 ohm.	Post 45p
15W model	£10.50
8 ohms	Post 65p
20W model	£11.50
State 8 or 15 ohms.	Post 75p



TEAK VENEER HI-FI SPEAKER CABINETS MODEL "A" 20 x 13 x 12in. For 12in. dia. or 10in. speaker. Illustrated **£14.50** Post £1.60 MODEL "B" BOOKSHELF For 13 x 8in. EMI **£8.50** Post £1 Loudspeakers. R.C.S. BOOKSHELF complete with speakers. Size 14 x 9 x 6in. approx. Response 50 to 14,000 cps 12 watt rms 8 ohms **£19 pair** Post £1.50 ACOUSTIC WADDING 18in. wide, 20p ft.

MONO PRE-AMPLIFIER

A mains operated solid state pre-amplifier unit designed to complement amplifiers without low level phono and tape input stages. This free standing cabinet incorporates circuitry for automatic R.I.A.A. equalisation on magnetic phono input and N.A.B. equalisation for tape heads. Power ON/OFF, PHONO/TAPE switches and pilot lamp are on the front panel; phono socket input and output are rear located. AC mains 240V. Size 6 x 3 1/2 x 2in.



£4.50 ea. - 2 for £8. Post 50p.

BAKER MAJOR 12 INCH £16.88



30-14,500 c/s. 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W. NOTE: 4 or 8 or 16 ohms available.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle, 18 x 12 1/2in. instructions. As illustrated. **£20.52** Please state 4 or 8 or 16 ohms. Post £1 60

"BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos Useful response 30-13,000 c/s Bass Resonance 55 c/s

GROUP "25" 12in 30W 4, 8 or 16 ohms. **£12.96** Post £1

GROUP "35" 12in 40W 4, 8 or 16 ohms. **£15.12** Post £1

GROUP 50/12in 12in 60W 4 or 8 or 16 ohms with aluminium presence dome. **£22.68** Post £1 60

GROUP 50/15in 15in 75W 8 or 16 ohms. **£28.08** Post £1 60



Discs, Group - PA Cabinets in stock. Send for Leaflet. Cabinet Fittings, Handles, Corners, Feet, Covering Material all in stock.

BAKER 150 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

Ideal for Groups, Disco, P.A. and Musical Instruments 4 inputs speech and music 4 way mixing Output 4/8/16 ohm. a.c. Mains 240V. Separate treble and bass controls. **£85** Carr £1 50



NEW "DISCO 100 WATT" £59 ALL TRANSISTOR AMPLIFIER Carr £1 2 inputs. 4 outputs separate volume treble and bass controls. Ideal disco or slave amplifier chassis. Made by Jennings

R.C.S. SOUND TO LIGHT DISPLAY MK II Complete kit of parts with R.C.S. printed circuit. Three 1000W channels. Will operate from 20mV signal source. CABINET extra £4. **KIT = £17.00**

GOODMANS CONE TWEETER 18,000 c/s. 25W 8 ohm. Price **£3.25** 3 WAY CROSSOVER WITH TREBLE & MID RANGE CONTROLS. 50 WATT. £5 POST £1.

R.C.S. 100 WATT VALVE AMPLIFIER CHASSIS



Professional model Four inputs Treble, Bass, Master Volume Controls. Ideal disco, P.A. or groups. S.A.E. for **£94** details. 5 speaker outputs 3 or 8 or 15 ohm 100V line to order. Suitable carrying case **£16.50**. plus £2 50 carr

LOW VOLTAGE ELECTROLYTICS 1 2 4 5 8 16 25 30 50 100, 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p. 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p; 2000mF 6V 25p; 25V 42p. 2500mF 50V 62p; 3000mF 25V 47p; 50V 65p. 3900mF 100V £1.60. 4700mF 63V £1.20. 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 5600mF 76V £1.80; 1200/76V 80p.

HIGH VOLTAGE ELECTROLYTICS 8/350V 22p 8+8/450V 50p 50+50/300V 50p 16/350V 30p 8+16/450V 50p 32+32/450V 75p 32/500V 75p 16+16/450V 50p 100+100/275V 65p 50/350V 50p 32+32/350V 50p 150+200/275V 70p

ROBUST BLACK PLASTIC BOX Size 6 1/2 x 3 1/2 x 2in with brushed aluminium facia. Ideal for constructional projects. **£1.50** Post 30p

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS All parts and instructions with Zener diode, printed circuit rectifiers and double wound mains transformer input 200/240V a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2in. Please state voltage required **£2.95** Post 45p

ELECTRO MAGNETIC PENDULUM MECHANISM 1.5V d.c. operation over 300 hours continuous on SP2 battery. fully adjustable swing and speed ideal displays, teaching electro magnetism or for metronome, strobe, etc. **95p** Post 30p

BSR AUTOCHANGER


Plays 12in, 10in or 7in records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. a.c. 200/250V. Size 13 1/2 x 11 1/2in. Above motor board 3 1/2in. Below motor board 2 1/2in. With STEREO/MONO CARTRIDGE **£12.95** All Post 75p Single Player version **£15.50** BSR P128 with Magnetic Cartridge **£24.50** GARRARD AUTOCHANGER plays all records **£14.95** BSR P163 BELT DRIVE DECK, less cartridge **£27.50** GARRARD AP76 Single Player less cartridge **£27.50**



BSR DE LUXE AUTOCHANGER Features balanced arm, Cueing device, stylus pressure gauge, 3 speed - plays all size records. Fitted with stereo ceramic cartridge. Size: 13 x 12in. Post £1. **£17.50** Or with Sonotone V100 magnetic cartridge **£21.50**




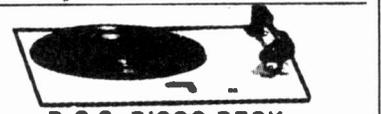R.C.S. DISCO DECK SINGLE RECORD PLAYER Fitted with auto stop, stereo compatible cartridge, Baseplate. Size 11 x 8 1/2in. Turntable Size 7in diameter a.c. mains. 220/250V, 3 speeds plays all size records **£7.95** Post 45p Two for £15. Post 75p.



HEAVY METAL PLINTHS

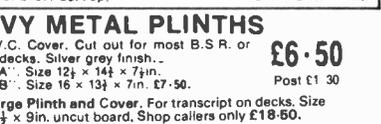With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Model "A": Size 12 1/2 x 14 1/2 in. £7.50. Model "B": Size 16 x 13 1/2 x 7in. £7.50. **£6.50** Post £1 30



Extra Large Plinth and Cover. For transcript on decks. Size 20 x 17 1/2 x 9in. uncut board. Shop callery only **£18.80**.

BAKER HI-FI SPEAKERS

HIGH QUALITY—BRITISH MADE SUPERB **£24.75** 12in 25 watt Post £1 80

Quality loudspeaker low cone resonance ensures clear reproduction of the deepest bass. Special copper drive and concentric tweeter cone. Full range reproduction with remarkable efficiency in the upper register. Bass Resonance 25 c/s Flux Density 16,500 gauss Useful response 20-17,000 c/s 8 or 16 ohms models

AUDITORIUM £22.68 12in 35 watt Post £1 60

A full range reproducer for high power Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques. Bass Resonance 35 c/s Flux Density 15,000 gauss Useful response 25-16,000 c/s 8 or 16 ohms models

AUDITORIUM £28.08 15in 45 watt Post £1 60

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in. sides, 6 x 4in. 95p; 8 x 6in. £1.40; 10 x 7in. £1.55; 14 x 9in. £1.90; 16 x 6in. £1.85; 12 x 3in. £1.20; 16 x 10in. £2.20; 12 x 8in. £1.70. ALUMINIUM PANELS: 18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p; 10 x 7in. 54p; 12 x 5in. 50p; 12 x 8in. 70p; 16 x 6in. 70p; 14 x 9in. 94p; 12 x 12in. £1; 16 x 10in. £1.16. ALUMINIUM ANGLE BRACKET, 6 x 1 1/2 x 1in. 15p. ALUMINIUM BOXES, MANY SIZES IN STOCK 4 x 2 x 2in. 85p; 3 x 2 x 1in. 65p; 6 x 4 x 2in. 95p; 8 x 6 x 3in. £1.50; 9 x 4 x 4in. £1.70; 12 x 4 x 4in. £1.95.



THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. a.c. mains 200/240V Leaflet S.A.E. **£4.95** Post 50p



RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K. Tel. 01-684 1665

Minimum post 30p. Access/Eurocard and Barclaycard/Visa. Same day despatch. Radio Books and Components Lists 20p. Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)



WIRE WRAPPING CENTRE



HOBBOY WRAP Model BW 630



Battery Wire-Wrapping Tool Complete with Bit and S1 Line

A£24.77 B£29.58 C£26.61 D£6.89

WIRE-WRAPPING TOOL

For .025" (0.63mm) sq. post "MODIFIED" wrap, positive indexing, anti-overwrapping device.


A	For AWG 30	BW-630
B	For AWG 26-28	BW-2628
C	Bit for AWG 30	BT-30
D	Bit for AWG 26-28	BT-2628



3 IN 1 WIRE DISPENSER

New wire dispenser cuts and strips three different colours of wire. Quick and easy to use pocket size.

£3.77

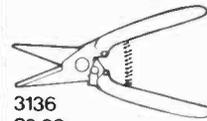

OK PLIERS AND CUTTERS

UNIVERSAL CUTTER Cuts everything. Leather, wire, plastic, tin-plate, cardboard. Stainless steel blades. Just one of the range of high quality pliers, cutters, tweezers and screwdrivers.

3136 £3.20

DIP/IC EXTRACTOR TOOL £1.18


The EX-1 Extractor is ideally suited for hobby enthusiast or lab engineer. Featuring one piece spring steel construction, it will extract all LSI, MSI and SSI devices of from 8 to 24 pins. Extractor Tool EX-1.



DIP/IC INSERTION TOOL WITH PIN STRAIGHTENER

£2.58


INS-1416

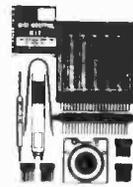

WIRE-WRAPPING KIT

Contains: Hobby Wrap Tool WSU-30 M, Wire Dispenser WD-30-B, (2) 14 DIP's, (2) 16 DIP's, Hobby Board H-PCB-1, DIP/IC Insertion Tool INS-1416 and DIP/IC Extractor Tool EX-1.


Wire-Wrapping Kit WK-4B (Blue) £17.82

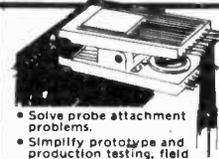

IC TEST CLIPS £2.77

FOR DUAL-IN-LINE PACKAGES

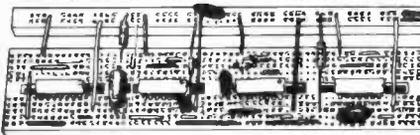- Provide full access to integrated circuit DIP leads.
- Remove DIP's damage free.
- Available in sizes to accommodate all DIP's; TC-14 fits 14-pin DIP's etc.



FROM 75p TERMINAL AND DISTRIBUTION STRIPS

Bread boarding building blocks with universal matrices of solderless plug-in tiepoints. Facilitate quick, solderless circuit build-up and check-out on universal .1" x .1" matrix.

- Are offered in ten configurations.
- Accept all components with leads up to .032" diameter.
- Require no special patch cords.
- Includes integral non-shorting instant mounting backing.



HOBBOY WRAP TOOL

Wire-wrapping, stripping, unwrapping tool for AWG 30 on .025 (0.63mm) Square Post.

A£4.39 B£4.69

Regular Wrap	A	WSU-30
Modified Wrap	B	WSU-30M



DIP SOCKET

Dual-in-line package, 3 level wire-wrapping, phosphor bronze contact, gold plated pins, .025 (0.63mm) sq., .100 (2.54mm) centre spacing.

14 Pin Dip Socket	14 Dip
16 Pin Dip Socket	16 Dip



RIBBON CABLE ASSEMBLY £2.40

With 14 Pin Dip Plug - 2" Long	DE 14.2
With 14 Pin Dip Plug - 4" Long	DE 14.4
With 14 Pin Dip Plug - 6" Long	DE 14.6
With 16 Pin Dip Plug - 2" Long	DE 16.2
With 16 Pin Dip Plug - 4" Long	DE 16.4
With 16 Pin Dip Plug - 6" Long	DE 16.6

DISTRIBUTORS WANTED***

OK Machine & Tool U.K. Limited

48a The Avenue, Southampton SO12SY

Telephone Southampton (0703) 38966 7 Telex 477222 Cablegram OKMAC

DISTRIBUTORS WANTED***

DIGITAL VOLTMETER/THERMOMETER KIT



Based on the 7106 single IC 3 1/2 digit D.V.M. the Kit contains a PCB, resistors, capacitors, presets, I.C. and 0.5" liquid crystal display. Components are also included to enable the basic D.V.M. kit to be modified to a Digital Thermometer using a single transistor as the sensor.

ONLY £23.75

TRICAC BARGAINS

400V Plastic Case	
3A	68p
6.5A with trigger	86p
8A	85p
12A	90p
16A	113p
20A	178p
25A	205p
SCR (C106D) 5A/400V	54p
Diac	23p

* SPECIALS *

4 x 555	£1.08
4 x 2N3055	£1.19
5 x 741	£1.08
LM3911	97p

OPTO ELECTRONICS

0.2" L.E.D.s	555	31p
Red 11p (86p/10)	ZN1034E	£1.94
Green 23p	AY-5-1230	£5.24
Yellow 27p	AY-5-1224	£3.51

DL727 0.5" display £1.62

TIMER I.C.s

MINI MAINS TRANSFORMERS

Standard 240V mains primary 100mA secondary	
6-0-6V	92p
9-0-9V	97p
12-0-12V	102p

24HR CLOCK/APPLIANCE TIMER KIT



Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, complete with PCBs and full instructions. £14.85 White box (56 x 131 x 71mm) - drilled £2.70 - undrilled £2.38

TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains rewiring. Insulated Touch Plates. Easy to follow instructions.

TSD300K - TOUCHSWITCH & DIMMER combined. One touch plate for on/off. Small knob controls brightness.	£5.62
TS300K - TOUCHSWITCH, TWO touch plates. ON and OFF.	£4.32
TSA300K - AUTOMATIC. ONE touch plate. Preset time delay OFF.	£4.32
LD300K - 300W LIGHT DIMMER KIT.	£3.02

ABOVE PRICES INCLUDE V.A.T.
Quantity discounts on request. Add 25p postage and packing. Mail order only to:
T.K. ELECTRONICS (PE) 106 Studley Grange Road, London, W7 2LX.

TRAMPUS

TRAMPUS ELECTRONICS LTD. 58-60 GROVE ROAD, WINDSOR, BERKS. SL4 1HS. TELEPHONE WINDSOR (07535) 54525.

Cash & cheque orders over £5 post free. Credit cards by post or phone £5 min. Post & packing 20p. CWO add VAT to prices marked * 8%, others 12 1/2%. Free price list of our full range send addressed envelope. Quote this ad as prices may change. All devices to makers specifications. Normally 24 hour turn around on orders. For ex-stock product.

LEDS 1/4" or D-2"	FULL SPEC PAKS	DEVELOPMENT PARCELS	REDUCED LINES
Red no clip 9p	PAK A: 12 red LEDs £1*	SET 1: 250 x 50V ceramics 5% 10 each £1*	A small selection from our lists
PAK of 100 LEDs £8*	B: 5 x 741 8 pin £1*	22of to 0-1uf £5	7815 1A15V 60p*
Til 209 & clip 11p	C: 4 x 2N3055 T03 £1*	SET 2: TANTULUMS £1*	7805/AL309K £1*
0-2" LED Red & clip 12p	PAK D: 12 x BC109 £1*	SET 3: 4 Watt 5% CF £1*	BC107 or BC108 8p*
Color LEDs All 16p*	PAK E: 7 x BY51 £1*	SET 4: 3 Watt 5% CF £1*	BC109-10p* BC109C 15p*
	H: 7 x 2N3819E FET £1*	1uf to 200uf 20V £5	AC178 only 10p
	K: 40 x 1N4148 £1*	35V 50 ohm £1*	BC182, 3, 4 A or L 10p
	M: 4 x pair 2A NPN/PNP £1*	Resistors 10 each 10% £1*	BC122, 3, 4 A or L 11p
	PAK N: 50 x 0A81/91 £1*	to 1 MEG total 500 £5	2N3055 90W 29p*
	PAK O: 20 x P/BC109 £1*	SET 5: Zeners 400mW £1*	2N3055 115W T03 45p*
	PAK R: 14 x BC 107 £1*	5 each 20 volts 3V to 33 volts (100 ohm) £5	2N3819E FET 16p
	PAK S: 14 x BC 108 £1*	SET 6: Presets PR £1*	DRP12 60p*
	T: 10 x BC131 type £1*	VERT 100 mixed £5	741 8 pin 21p*
	V: 50 x 5 mfd 10V £1*	SET 7: Heatsinks £1*	555 timer 29p*
	X: 4 x 555 timer £1*	10 off each. T018, T05, TV4, small T03 £5	2N414 RX 75p
	Z: 20 x PNP 2702 type £1*		LM380 amp 75p
	Y: 4 x LM301/14P £1*		LM3900 69p
	U: 4 x 1A 50V SCR £1*		CMOS 4011 15p
	NEW PAK D: 50 x 220 mfd 6-3V electrolytes £1		4013, 4049 39p
VERB STOCKED less 10%			TTL 7400 8p
DIP SOCKETS			74121 25p etc etc
8 pin 12p 14 or 16 15p			
PP3 battery clips 10p			

EVERYBODY'S DOING IT!

Doing what? Sending for the latest Home Radio Catalogue. It's the most comprehensive components catalogue you can get. 128 pages, about 2,500 items listed, and profusely illustrated. Now only £1.00, with a free bargain list. Send your cheque or postal order now.

Home Radio Components Ltd.
Dept. PE, 234 London Road, Mitcham, Surrey CR4 3HD



15-240 WATTS!

HY5 Pre-amplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: complete pre-amplifier in single pack; multi-function equalisation, low noise, low distortion; high overload, two simply combined for stereo.

APPLICATIONS: hi-fi, mixers, disco; guitar and organ, public address.

SPECIFICATION: Inputs—magnetic pick-up 3mV, ceramic pick-up 30mV; tuner 100mV, microphone 10mV, auxiliary 3-100mV, input impedance 47k Ω at 1kHz. Outputs—tape 100mV, main output 500mV R.M.S. Active Tone Controls—treble \pm 12dB at 10kHz, bass \pm 12dB at 100Hz. Distortion—0.1% at 1kHz, signal/noise ratio 68dB. Overload—38dB on magnetic pick-up. Supply Voltage— \pm 16-50V

Price £6.27 + 78p VAT. P. & P. free

HY5 mounting board B.1. 48p + 6p VAT. P. & P. free



HY30 15W into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

FEATURES: complete kit, low distortion, short, open and thermal protection, easy to build

APPLICATIONS: updating audio equipment, guitar practice amplifier, test amplifier; audio oscillator

SPECIFICATION: Output Power—15W R.M.S. into 8 Ω . Distortion—0.1% at 15W. Input Sensitivity—500mV. Frequency Response—10Hz-16kHz - 3dB.

Price £6.27 + 78p VAT. P. & P. free

HY50 25W into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: low distortion, integral heatsink, only five connections, 7 amp output transistors, no external components.

APPLICATIONS: medium power hi-fi systems, low power disco, guitar amplifier

SPECIFICATION: Input Sensitivity—500mV. Output Power—25W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 25W at 1kHz. Signal/Noise Ratio—75dB. Frequency Response—10Hz-45kHz - 3dB. Supply Voltage— \pm 25V. Size—105 x 50 x 25mm

Price £8.18 + £1.02 VAT. P. & P. free



HY120 60W into 8 Ω


The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: very low distortion, integral heatsink, load line protection, thermal protection, five connections, no external components

APPLICATIONS: hi-fi, high quality disco, public address, monitor amplifier, guitar and organ

SPECIFICATION: Input Sensitivity—500mV. Output Power—60W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 60W at 1kHz. Signal/Noise Ratio—90dB. Frequency Response—10Hz-45kHz - 3dB. Supply Voltage— \pm 35V. Size—114 x 50 x 85mm

Price £19.01 + £1.52 VAT. P. & P. free

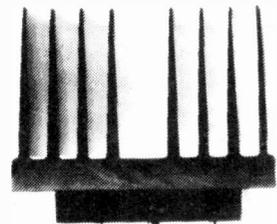

HY200 120W into 8 Ω

The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

FEATURES: thermal shutdown, very low distortion, load line protection, integral heatsink, no external components

APPLICATIONS: hi-fi, disco, monitor, power slave, industrial, public address.

SPECIFICATION: Input Sensitivity—500mV. Output Power—120W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.05% at 100W at 1kHz. Signal/Noise Ratio—96dB. Frequency Response—10Hz-45kHz - 3dB. Supply Voltage— \pm 45V. Size—114 x 50 x 85mm.

Price £27.99 + £2.24 VAT. P. & P. free

HY400 240W into 4 Ω


The HY400 is I.L.P.'s Big Daddy of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: thermal shutdown, very low distortion, load line protection, no external components

APPLICATIONS: public address, disco, power slave, industrial

SPECIFICATION: Output Power—240W R.M.S. into 4 Ω . Load Impedance—4-16 Ω . Distortion—0.1% at 240W at 1kHz. Signal/Noise Ratio—94dB. Frequency Response—10Hz-45kHz - 3dB. Supply Voltage— \pm 45V. Input Sensitivity—500mV. Size—114 x 100 x 85mm

Price £38.61 + £3.09 VAT. P. & P. free

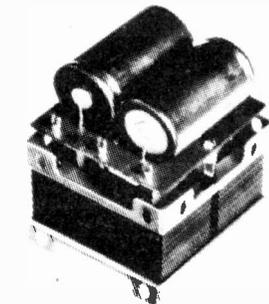

POWER SUPPLIES: PSU36—suitable for two HY30s £6.44 + 81p VAT. P. & P. free. PSU50—suitable for two HY50s £8.18 + £1.02 VAT. P. & P. free. PSU70—suitable for two HY120s £14.58 + £1.17 VAT. P. & P. free. PSU90—suitable for one HY200 £15.19 + £1.21 VAT. P. & P. free. PSU180—suitable for two HY200s or one HY400 £25.42 + £2.03. VAT. P. & P. free.

Free post + packing applicable to U.K. only.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please supply

Total Purchase price

I Enclose: Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

Signature

Registered office No. 1032630

GODDARD'S COMPONENTS

110 LONDON ROAD, ST. ALBANS, HERTS. AL1 1NX

MAIL ORDER DEPT.


Callers Welcome MON-SAT: 9.30-5.30

THURS: Closed all day

Lunch: MON-FRI: 1.30-2.30, SAT: 1.00-2.00

STEREO

CASSETTE RECORDER DECK

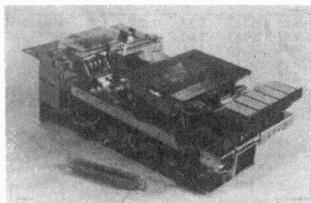


- with + solenoid auto-stop
- + CrO2 switch
- + piano key operation
- + twin level meters
- + mic. sockets

Tech. Spec.:
Bias and erase freq. 88 kHz
4 ICs 8 Transistors
1 SCR 10 Diodes

Diagrams and top panel template supplied

£25.75 + £1.25 p&p

HIT-BOX

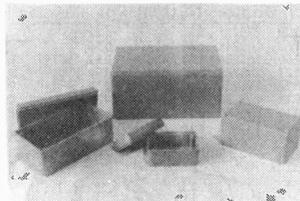

SHOCK-PROOF POLYSTYROL IN GREY
4mm thick walls
Larger sizes are pillar fixing
Smaller sizes are slotted

Inside Measurements:

Box No.	Breadth mm	Length mm	Height mm	Weight gm
1001	60	90	50	100
1002	75	130	61	175
1003	90	160	71	285
1004	93	193	95	340
1005	125	220	110	575


1001 - 90p 1004 - £2.00
1002 - £1.60 1005 - £3.00
1003 - £1.80 50p each p&p. £1.00 for 3 p&p

TRADE ENQUIRIES WELCOME!

DIGITAL CLOCK

BATTERY DROP LEAF CLOCK MOVEMENT

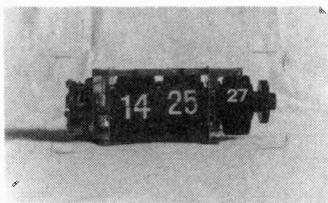Hrs. Mins. Date
Easy-to-set regulator screw
Size: 140mm x 85mm x 60mm
Window size: 63mm x 28mm
No. height: 19mm
Date height: 10mm
Weight: 270gm



£4.95 + 50p p&p

LCD WATCHES

TOUCH GENTS CTG

£14.95

UNISEX C551

6 Colours

£11.95

LADIES S/S C652

£16.95

LARGE GENTS C165

£9.95

ALL WATCHES 5 FUNCTION ... 1 YEAR GUARANTEE
P&P 50p per watch, Inc. Insurance

We can also supply components for 'ELECTRONIC SOUND MONITOR' P.E. Sept. 1978 • ALL PRICES INCLUDE VAT

SINCLAIR PRODUCTS*

Microvision TV now in stock £200. PDM35 digital multimeter £25-95. mains adaptor £3-24. deluxe padded case £3-25. new DM235 digital multimeter P.O.A. cambridge programmable calculator £13-15. prog. library £2-95. mains adaptor £3-20.

S-DECS AND T-DECS*

S-Dec £3-39. T-Dec £4-44. u-DeCA £4-52. u-DeCB £6-73. 16dil or 10T05 adaptors with sockets £2-14.

CONTINENTAL SPECIALITIES

EXP300 £6-21. EXP350 £3-40. EXP600 £6-80. EXP650 £3-89. EXP48 £2-48. P86 £9-94. P8100 £12-74. LM1 £30-99. LP1 £33-48. LP2 £19-44.

TV GAMES

Send sae for free data. new racing car tv games chip AY-3-8603 plus economy kit £20-60. tank battle chip AY-3-8710 plus economy kit £13-95. stunt motor cycle chip AY-3-8760-1 plus economy kit £12-50. 10 game paddle 2 chip AY-3-8600 plus economy kit £14-70. AY-3-8500 chip plus economy kit £8-95. modified shoot kit £4-95. rifle kit £4-95. colour generator kit £7-50. attractively cased assembled tv games:- 4 game models (Tennis, football, squash and pelotal):- black and white £11-95. colour £14-50. deluxe 6 game black and white model with pistol attachment £17-95. tv games mains adaptors £3-10.

MAINS TRANSFORMERS

6-0-6V 100ma 79p. 1 1/2 £2-35. 6.3V 1 1/2 £1-89. 9-0-9V 75ma 79p. 1a £1-99. 2a £2-80. 12-0-12V 50ma 79p. 100ma 90p. 1a £2-49. 13V 1a 95p. 15-0-15V 1a £2-79. 30-0-30V 1a £3-59.

JC12, JC20 AND JC40 AMPLIFIERS

A range of integrated circuit audio amplifiers supplied with free data and printed circuits. JC12 6 watts £1-60. JC20 10 watts £2-95. JC40 20 watts £4-20. Send sae for free data on our range of matching power and preamp kits.

FERRANTI ZN414

IC radio chip £1-05. extra parts and pcb for radio £3-85. case £1. Send sae for free data.

PRINTED CIRCUIT MATERIALS

PC etching kits:- economy £1-70. standard £3-82. 50 sq ins pcb 40p. 1 lb FeCl £1-05. etch resist pens:- economy 45p. dalo 73p. small drill bits 1/32 ins or 1mm 20p each. etching dish 68p. laminate cutter 75p.

SWANLEY ELECTRONICS

DEPT. PE. 32 Goldsel Rd., Swanley, Kent BR8 8TO.

Mail order only. Please add 30p to the total cost of order for postage. Prices include VAT. Overseas customers deduct 7% on items marked * and 11% on others. Official credit orders welcome.

BATTERY ELIMINATOR BARGAINS

tv games power unit stabilized 7.7V 100ma £3-10. 3-way models with switched output and 4-way multi-jack:- 3/4/6V 100ma £2-92. 6/7 1/2/9V 300ma £3-30. 100ma radio models same size as a PP9 battery. with press stud connectors. 9V £2-85. 6V £2-85. 4 1/2V £2-85. 9V+9V £4-50. 6V+6V £4-50. 4 1/2V+4 1/2V £4-50. cassette recorder mains unit 7 1/2V 100ma with 5 pin din plug £2-85. car converters 12V dc input. output 9V 300ma £1-50. output 7 1/2V 300ma £1-50.

BATTERY ELIMINATOR KITS

Send sae for free leaflet on range. 100ma radio types with press stud connectors. 4 1/2V £1-80. 6V £1-80. 9V £1-80. 4+4 1/2V £2-50. 6+6V £2-50. 9+9V £2-50. cassette type 7 1/2V 100ma with din plug £1-80. heavy-duty 13 way types 4 1/2/6/7/8 1/1/13/14/17/21/25/28/34/42V. 1 Amp £4-65. 2 Amp £7-25. transistor stabilized 8-way types for low hum 3/4 1/2/6/7 1/2/9/12/15/18V 100ma £3-20. 1 Amp £6-40. variable voltage stabilized models. 2-18V 100ma £3-60. 2-30V 1A £6-95. 2-30V 2A £10-95. car converters 12V dc input. output 9V 300ma £1-50. output 7 1/2V 300ma £1-50.

BI-PAK AUDIO MODULES

Send sae for data. S450 tuner £23-51. AL60 £4-86. PA100 £16-71. SPM80 £4-47. 8MT80 £5-95. MK60 £38-74. stereo 30 £20-12.

BULK BUY OFFERS

Minimum purchase £3 any mix from this section. IN4148 1.3p. IN4002 3.6p. BC212 8p. 741 8 dil 15p. NE555 8 dil 29p. 723 14 dil 43p. dalo pens 59p. AC76023N exact equiv of SN76023N with improved heat sink 79p. plastic equivs of popular transistors:- BC108 3.8p. BC109 4.4p. 8CY71 4.7p. 8CY72 4.4p. fuses 20mm x 5mm cartridge .25. .5, 1.2, 3.5 Amp. quickblow type 0.7p. ant surger type 3.4p. resistors 5% E12 10 ohm to 10M. 1/2W 0.8p. 1W 1.9p. polyester capacitors 250V .01. .022. .033. .047mf 2.7p. .015mf 1.1p. .068mf 1.4p. .031mf 1.5p. .022mf 3p. .033mf 2.5p. .047mf 4.8p. polystyrene capacitors E12 63V 15 to 6800 pf 2 1/2p. ceramic capacitors 50V E12 22pf to 1000pf 1.7p. E6 1500 to 33000pf 1.7p. 47000 pf 2p. electrolytics 60V .47. 1.2mf 5p. 25V 5mf 5p. 10mf 4p. 16V 22mf 5p. 33.47. 100mf 6p. 220. 330mf 9p. 470mf 11p. 1000mf 8 1/2p. zeners 400mW E24 2V7 to 33V 5.5p. preset pots sub miniature 0.1W horiz or vert 100 to 4M7 6.8p. potentiometers 1W 4K7 to 2M2 log or lin. single 26p. dual 78p.

HAVE YOU DONE IT LATELY!

Fit a new tape head and transform the performance of your tape recorder

MONOLITH THE MONOLITH ELECTRONICS CO. LTD.

QUALITY REEL TO REEL AND CASSETTE TAPE HEADS



Please enclose 20p P&P with order

Full Catalogue 25p

B24-RP stereo cassette glass/ferrite record/playback £9.84
B12-01 mono cass. playbk. £1.60 B24-01 stereo cass. playbk. £2.80
A28-05 stereo 8tk cartridge £1.80 E12-09 stereo/mono cass. erase £1.80

5/7 Church St, Crewkerne, Som. Tel. (0460) 74321



Clef Products

P. E. JOANNA & 'STRING ENSEMBLE'

Send S.A.E. for details of Kits & P.C.B.s

Please indicate which instrument required.

16 Mayfield Road, Bramhall, Cheshire SK7 1JU

Marshall's

Come and get a great deal

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat
Express Mail Order Tel. orders on credit cards £10 min.
Trade and export enquiries welcome

A. Marshall (London) Ltd, Dept. PE. Head Office mail order: Kingsgate House, Kingsgate Place, NW6 4TA. Tel: 01-624 0805. Retail Sales London: 40-42 Cricklewood Bdvwy, NW2 3ET. Tel: 01-452 016/12. Telex: 21492. London: 325 Edgware Rd, W2. Tel: 01-723 4242. Glasgow: 85 West Regent St, G2 2QD. Tel: 041-332 4133. Bristol: 1 Straits Pde, Fishponds Rd, BS16 2LX. Tel: 0272 654201.

2M696	0.39	2N2219	0.38	2N3397	0.19	2N4062	0.20	2N5247	0.44	40410	0.82	BC2148	0.17	BC5498	0.14	BD244A	0.70	BF182	0.37	BFX89	1.37	MJE520	0.50						
2M697	0.31	2N219A	0.39	2N3438	0.85	2N4064	1.35	2N5248	0.44	40411	3.10	BC214C	0.17	BC549C	0.15	BD244C	0.87	BF183	0.44	BFY50	0.27	MJE521	0.70						
2M698	0.49	2N2220	0.39	2N3440	0.75	2N4074	2.65	2N5254	0.44	40594	0.87	BC147	0.13	BC182B	0.13	BC214E	0.18	BC557	0.14	BD245A	0.89	BF184	0.41	BFY51	0.27	MJE2955	1.85		
2M699	0.58	2N2221	0.25	2N3441	0.92	2N4101	0.27	2N5259	0.44	40595	0.88	BC147B	0.13	BC182L	0.15	BC214B	0.18	BC558	0.13	BD245B	0.89	BF185	0.37	BFY52	0.27	MFP3055	1.05		
2M706	0.30	2N2221A	0.25	2N3442	1.45	2N4122	0.27	2N5266	0.44	40597	0.80	BC148	0.13	BC182LA	0.15	BC214C	0.18	BC559	0.15	BD246A	0.72	BF194	0.16	BFY50	0.16	BPY90	1.35	MPF102	0.44
2M705A	0.30	2N2222	0.25	2N3638	0.17	2N4123	0.19	2N5298	0.44	40688	1.30	BC148B	0.13	BC182L	0.15	BC214E	0.18	BC570	0.21	BD246C	0.93	BF195	0.16	BFY51	0.16	BR101	0.55	MPF103	0.44
2M708	0.30	2N2222A	0.25	2N3638A	0.17	2N4124	0.19	2N5447	0.16	40126	0.48	BC148C	0.13	BC183	0.12	BC238A	0.13	BCY71	0.26	BD433	0.44	BF196	0.16	BRY39	0.55	MPF104	0.44		
2M718	0.30	2N2369	0.27	2N3702	0.14	2N4125	0.19	2N5448	0.16	40127	0.48	BC149	0.15	BC183A	0.12	BC238B	0.13	BCY72	0.18	BD434	0.46	BF197	0.18	BSX19	0.35	MP5105	0.44		
2M718A	0.54	2N2369A	0.27	2N3703	0.14	2N4126	0.19	2N5449	0.20	40128	0.48	BC149C	0.15	BC183B	0.13	BC238C	0.13	BD115	0.88	BD435	0.46	BF198	0.19	BSX20	0.35	MP5A05	0.27		
2M720A	0.85	2N2646	0.80	2N3704	0.14	2N4284	0.38	2N5457	0.38	40151	0.43	BC157A	0.15	BC183C	0.13	BC239B	0.16	BD131	0.55	BD436	0.46	BF199	0.19	BSX21	0.35	MP5A06	0.27		
2M722	0.45	2N2647	1.55	2N3705	0.14	2N4288	0.22	2N5458	0.35	40152	0.54	BC158A	0.15	BC183L	0.15	BC239C	0.17	BD132	0.75	BD437	0.55	BF224J	0.22	BU104	1.80	MP5A12	0.44		
2M727	0.50	2N2903	0.60	2N3706	0.14	2N4287	0.22	2N5459	0.32	40153	0.63	BC158B	0.15	BC183LA	0.15	BC239A	0.16	BD133	0.40	BD438	0.55	BF251	0.27	BU105	1.65	MP5A14	0.33		
2N914	0.38	2N3204	0.31	2N3707	0.14	2N4288	0.22	2N5460	0.65	40153K	0.59	BC159A	0.17	BC183LA	0.15	BC258B	0.19	BD136	0.40	BD529	0.49	BF244	0.38	BU126	1.08	MP5A55	0.27		
2N916	0.33	2N2904A	0.31	2N3708	0.12	2N4289	0.22	2N5484	0.37	40176K	0.70	BC159B	0.17	BC183LC	0.15	BC259B	0.19	BD137	0.41	BD530	0.55	BF246	0.33	BU204	2.20	MP5A56	0.27		
2N917	0.38	2N2905	0.31	2N3709	0.12	2N4347	2.20	2N5485	0.40	40176	0.54	BC160	0.38	BC184	0.12	BC300	0.43	BD138	0.41	BD535	0.70	BF245A	0.44	BU205	2.40	R2008	2.45		
2N918	0.45	2N2905A	0.31	2N3717	2.16	2N4348	2.65	2N5486	0.40	40176	0.59	BC161	0.38	BC184B	0.12	BC301	0.43	BD139	0.43	BD536	0.70	BF245B	0.44	BU206	2.70	R2009	2.15		
2N929	0.37	2N2906	0.25	2N3712	2.20	2N4918	0.65	2N5490	0.64	40187K	0.65	BC167	0.13	BC184C	0.13	BC302	0.37	BD140	0.40	BD537	0.74	BF257	0.35	BU208	2.70	TIP32A	0.49		
2N929A	0.37	2N2906A	0.25	2N3713	3.15	2N4919	0.70	2N5492	0.64	40188	0.54	BC167B	0.13	BC184L	0.15	BC303	0.54	BD181	1.90	BD538	0.77	BF258	0.35	ME0401	0.22	TIP39C	0.65		
2N930	0.37	2N2907	0.25	2N3901	0.19	2N4920	0.83	2N5494	0.65	40188K	0.65	BC168A	0.13	BC184B	0.15	BC307	0.16	BD182	2.20	BD539	0.60	BF259	0.35	ME0402	0.22	TIP30A	0.54		
2N930A	0.95	2N2907A	0.25	2N3920	0.39	2N4921	0.54	2N5496	0.67	40161	1.00	BC168B	0.13	BC184C	0.15	BC307A	0.16	BD183	2.35	BD540	0.60	BF236	0.42	ME0404	0.17	TIP39C	0.65		
2N1171	0.30	2N2923	0.17	2N3921	0.96	2N4922	0.60	2N6027	0.64	40162	1.00	BC168C	0.13	BC212	0.15	BC307B	0.16	BD187	0.95	BDX14	1.32	BF337	0.49	ME0412	0.22	TIP31A	0.54		
2N1189	0.30	2N2924	0.17	2N3900	0.28	2N4923	0.75	2N6107	0.45	40160	0.60	BC169B	0.13	BC212A	0.15	BC308	0.16	BD235	0.46	BDX18	1.00	BF338	0.52	ME0414	0.22	TIP31C	0.27		
2N1890	0.30	2N2925	0.19	2N3901	0.30	2N4924	1.15	2N6108	0.55	40169	0.52	BC169C	0.13	BC212B	0.15	BC308B	0.16	BD235	0.44	BDY20	1.10	BF339	0.30	ME0416	0.16	TIP32A	0.59		
2N1921	0.27	2N3023	0.17	2N3903	0.20	2N5092	0.36	2N6109	0.55	40167	0.18	BC177	0.22	BC212L	0.18	BC309A	0.16	BD237	0.44	BDY56	2.10	BF41	0.30	ME0403	0.16	TIP41A	0.76		
2N2192	0.58	2N3054	0.72	2N3904	0.18	2N5087	0.30	2N6111	0.49	40107A	0.16	BC177A	0.22	BC212LA	0.18	BC309B	0.16	BD238	0.44	BFY56	2.10	BF41	0.30	ME0403	0.16	TIP41A	0.76		
2N2197	0.58	2N3054	0.72	2N3905	0.18	2N5088	0.30	2N6121	0.41	40107B	0.16	BC177B	0.25	BC212LB	0.18	BC309C	0.16	BD239A	0.44	BF115	0.39	BF79	0.30	ME4101	0.11	TIP41C	0.76		
2N2193	0.50	2N3055	0.75	2N3906	0.18	2N5089	0.30	2N6122	0.44	40108	0.16	BC178	0.22	BC213	0.15	BC327	0.22	BD239C	0.59	BF160	0.33	BF80	0.30	ME4102	0.11	TIP42A	0.86		
2N2193A	0.52	2N3055	0.75	2N3901	0.30	2N5130	0.65	2N6123	0.48	40108A	0.16	BC178A	0.25	BC213A	0.15	BC328	0.20	BD240A	0.59	BF161	0.65	BF81	0.30	ME4103	0.11	TIP42C	1.08		
2N2194	0.42	2N3391	0.40	2N4032	0.65	2N5191	0.75	2N6124	0.45	40108B	0.16	BC178B	0.35	BC213B	0.15	BC337	0.20	BD240C	0.59	BF172	0.37	BF29	0.34	ME4104	0.11	TIP2955	0.70		
2N2194A	0.45	2N3391A	0.45	2N4036	0.72	2N5192	0.80	2N6125	0.47	40108C	0.17	BC179	0.25	BC213C	0.15	BC338	0.20	BD241A	0.59	BF173	0.37	BF30	0.34	ME6101	0.22	TIP305	0.59		
2N2195	0.40	2N3392	0.17	2N4037	0.60	2N5193	0.75	40361	0.55	40109	0.16	BC179A	0.25	BC213L	0.17	BC347	0.13	BD241C	0.65	BF174	0.37	BF31	0.34	ME8102	0.22	TIS3A	1.05		
2N2195A	0.40	2N3393	0.17	2N4058	0.22	2N5194	0.80	40362	0.55	40109B	0.17	BC179B	0.25	BC213LA	0.17	BC347A	0.13	BD242A	0.55	BF178	0.27	BF32	0.38	MJE2955	1.35	TIS42	5.00		
2N2217	0.55	2N3394	0.17	2N4059	0.22	2N5195	0.97	40363	1.45	40109C	0.18	BC179C	0.26	BC213LB	0.17	BC347B	0.13	BD242C	0.62	BF179	0.33	BF36	0.30	MJE340	0.62	TIS43	4.07		
2N2218	0.38	2N3395	0.19	2N4060	0.22	2N5245	0.37	40408	0.82	40140	0.30	BC182	0.12	BC213LC	0.17	BC348	0.13	BD243A	0.65	BF180	0.37	BF37	0.35	MJE370	0.62	TIS50	0.22		
2N2218A	0.35	2N3396	0.19	2N4061	0.19	2N5246	0.38	40409	0.82	40141	0.32	BC182A	0.12	BC214	0.17	BC349	0.14	BD243C	0.67	BF181	0.37	BF38	0.30	MJE371	0.62	TIS51	0.22		

LINEAR CIRCUITS

CA301B	1.10	LM3080N	0.96	LM7815L	1.75	TA0100	2.00
CA3020	2.20	LM3801A	1.15	LM7824K	1.75	TA0120	0.80
CA3020A	2.50	1.08	LM78L05CZ	TA6500	2.24		
CA3028A	0.90	LM3818A	2.70	0.30	TA65000	2.34	
CA3028B	1.25	LM3818	1.69	LM78L12CZ	TA6510	2.35	
CA3030	1.50	LM3821	1.32	0.30	TA65100	2.48	
CA3030A	2.20	LM3848A	1.55	LM78L15CZ	TA6520	2.60	
CA3038	2.90	LM3868	0.88	0.30	TA65200	2.70	
CA3038A	4.10	LM3871N	1.10	MM5531A	4.60	TA6530	2.35
CA3045	1.55	LM3888	1.00	MM5531B	4.60	TA65300	2.45
CA3046	0.77	LM3889	1.00	NE555	0.33	TA6540	2.60
CA3046A	2.45	LM702C	0.61	NE555	0.85	TA65400	2.70
CA3052	1.78	LM702B	0.97	NE555B	0.90	TA6550	2.80
CA3080	0.85	LM7098	0.50	NE560	4.50	TA65500	3.80
CA3080A	2.10	LM7091A	0.49	NE561	4.50	TA65600	3.00
CA3086	0.50	LM710	0.67	NE562	4.50	TA6570	2.10
CA3088B	1.87	LM7101A	0.64	NE565	1.39	TA65700	2.20
CA3089B	2.90	LM711C	0.72	NE566	1.75	TA67000	2.20
CA3090Q	4.40	LM723	0.75	NE561	1.90	TA67200	2.08
CA3130	1.06	LM723C1A	0.45	NE571N	4.95	TA6750	2.36
CA3140	1.04	LM726	5.80	SAS560	4.70	TA67500	2.45
LM301	0.30	LM741C	0.70	SAS570	2.70	TA6800	1.30
LM307N	0.50	LM741C8	0.30	SAU110	2.10	TA68105	1.30
LM308N	0.95	LM741C10	0.30	S041P	1.35	TA6820	0.80
LM309NC	1.95	LM741C10	0.59	TA623	1.35	TA6820	2.89
LM317K	3.35	LM7488	0.58	SN76001N	TC1A160C	2.36	
LM318A	2.						

NEW FROM CASIO

NEW

THE INCREDIBLE FX 8000



43 Scientific funct.
100 sec. Stopwatch.
Five Alarm-Timers,
sequential (self-clearing) or repeat.
2 level parenthesis.
Memory, Deg, Rad, Gra.
Standard Deviations.
Fractions. Sexagesimal.
Rect/Polar convert.
LCD. 1300 hr batteries.
1/4 x 2 1/2 x 5 1/2 in. 2.7 oz.
RRP £35.95
£29.95

NEW

CQ-81 CALCULATING ALARM

CLOCK PLUS 2 ALARM/TIMERS

Two AA batteries last for 10,000 hrs (1 year).
LCD 6 digit clock, large angled display.
24 hr Alarm, also two 24 hr Alarm/timers with countdown (one self-clearing, one repeats).
Full Memory, Constants, %, $\sqrt{\quad}$, $1 \frac{1}{2} \times 2 \frac{1}{2} \times 5$ in.



RRP £22.95 **£17.95**

NEW

FX-48 SCIENTIFIC MINI CARD

Full scientific with 2 level parenthesis.
Full Memory, Deg, Rad, Grad, Sexagesimal, Standard Deviations.
600 hrs battery life.



RRP £24.95
£19.95

NEW

CALCULATING ALARM CLOCK MINI CARD

Available Aug./Sept. Similar size to FX-48. Similar specification to CQ-81.

RRP £24.95. Our Price **£19.95**

CASIO QUALITY AND VALUE

31QR-17B

Left. 8.4mm
£29.95



31QS-12B

Right. 7.7mm
£39.95

Stopwatch,
Dual Time,
Water Resistant,
All S/S.

31QR-16B (Round face - not illustrated). Luxury version of 31QR-17B. Only 7.45mm thick. **£34.95**

SPORTS WATCHES

F-100 (left)

9.45mm thick
RRP £29.95
£24.95



52QS-14B

8.0mm
£34.95
Net, Lap and
1st & 2nd Place
times to 1/100.
Water Res. 66ft.



38CS14B Chronograph £49.95

ALARM WATCHES. 25CR-16B (round) £49.95

25CS-14B (square) £59.95

WORLD TIME WATCH. 29CS-11B £59.95

SEIKO Calculator/Watch (£165) £135

CITIZEN Multi-Alarm (£135) £108

MAINS DIGITAL ALARM CLOCKS

Fairchild Timeband C500, Black or white £9.95

CASIO CALCULATORS

ST-1 Stopwatch (four way) £24.95

LCD LC822 £10.95. LC78 £16.95

AQ-1000 Clock, alarm, stopwatch £21.95

CASIO SCIENTIFICS

DIGITRON: FX-31 £11.95. FX-39 £15.95.

FX-140 £17.95. FX-120 £19.95. FX-360 £49.95.

Send 25p for our illustrated catalogue.

Prices include VAT and P & P.

Send cheque, P.O. or phone your credit card no. to:-

TEMPUS
Dept. P.E.
19-21 Fitzroy Street
Cambridge CB1 1EH
Telephone (0223) 312866

CANON COMPONENTS

**OFFER A FANTASTIC RANGE AT VERY
COMPETITIVE PRICES including...**

- R.F.
- DIGITAL
- TRANSISTORS
- LINEAR I.C.'s
- DISPLAYS
- LED's
- RESISTORS
- CAPACITORS
- HARDWARE
- CHASSIS
- BOXES
- S-DEC
- T-DEC
- TRANSFORMERS
- SPEAKERS
- CABINETS
- AMPLIFIERS
- MICROPHONES
- MIXERS
- HEADPHONES
- TURNTABLES
- LIGHT MODULATORS
- LIGHT BOXES
- SPOTS
- BULBS
- JINGLE MACHINES
- PACKS
- TWEETERS
- LEADS
- PLUGS
- JACKS
- POWER SUPPLIES
- METERS
- SURPLUS ITEMS
- TAPES
- RADIO's
- CALCULATORS
- TEST EQUIPMENT
- KITS
- VERO BOARD
- SOLDERING IRONS
- SOLDER

PHONE OR SEND S.A.E. FOR LISTS ACCESS OR BARCLAYCARD
ACCEPTED

**322-324 WHITEHORSE ROAD CROYDON
SURREY CRO 2LF**

OPEN DAILY 9.30 A.M. - 6 P.M.

TEL. 01-684 9872

FREE CATALOGUE/ORDER FORM

SEND S.A.E.

Send stamped
addressed envelope for catalogue/
order form and up to four price lists of com-
ponents for PE projects from November 1977.
Examples from the Ace range of 700+ components.

741 ONLY 30p	555 ONLY 50p	TIL209 ONLY 15p	IN4001 ONLY 5p
----------------------------------	----------------------------------	-------------------------------------	------------------------------------

All prices include VAT. P&P FREE over £2.

Name _____

Address _____

ACE


Get an ACE up your sleeve!

ACE MAILTRONIX LTD
Dept. PE Tootal Street
Wakefield, W. Yorkshire WF1 5JR

FOR YOUR GUIDANCE VALUE ADDED TAX

Unless otherwise shown, all prices in advertisements are inclusive of VAT. Where prices are exclusive, readers should ensure that they have added the correct amount of VAT before ordering.

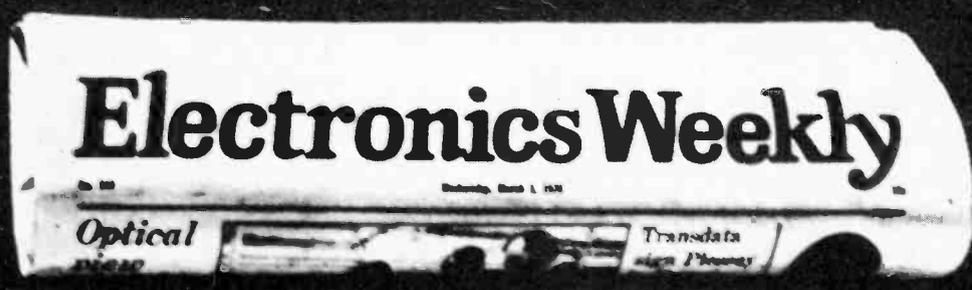Export orders are not subject to the addition of Value Added Tax.



Electronics Weekly

Communications of the first kind.

Every copy of Electronics Weekly is a close encounter with two worlds – the telecommunications and the electronics industry.

A quality subscription newspaper, Electronics Weekly is specifically designed to provide you with a full briefing on every factor important to senior management decisions.

Competitor activities . . . prices . . . new products . . . takeovers . . . government plans, legal and financial . . . export

opportunities . . . stock exchange developments . . . future trends . . .

Electronics Weekly reports in depth on all these areas, giving you a regular insight into where both industries are heading – and what your competitors are doing.

52% of its readers are in financial or general management – which makes Electronics Weekly not only essential reading for you, but the natural medium for launching new products and selling overseas through our European edition.

For a specimen copy, and advertisement rates contact: Brian Moloney on 01-261 8000 or write to him at the address below.

Electronics Weekly
communicates the facts

Published by IPC Electrical/Electronic Press Ltd.
Dorset House, Stamford Street, London SE1 9LU
A member of IPC Business Press Ltd.



NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

RECEIVERS AND COMPONENTS



SPECIAL OFFERS.

Buy NOW while stocks last. PRICES INCLUDE V.A.T.

2N3055	33p each
TIP31 or TIP32	39p each
TIP41 or TIP42	39p each
0.022uF Polyester	3p each
0.033uF Polyester	6p each
22uF 450V Electrolytic	19p each
47uF 25V Electrolytic	5p each
150uF 16V Electrolytic	5p each
680uF 16V Electrolytic	12p each
Red LED's (5mm)	10 for £1.00

ALL COMPONENTS ARE BRAND NEW AND GUARANTEED ONLY AVAILABLE AT THESE PRICES WHILE STOCKS LAST. Please add 15p for Postage. Send 2 stamps for Catalogue. BARCLAYCARD phone service available. Tel. 0473 50975.

FRASER-MANNING LTD.,
26 HERVEY STREET, IPSWICH, IP4 2ES.

ASSORTED SMALL JAPANESE IF. Transformers 20 for £1.25, Assorted Nuts, Bolts, Washers, Eyelets Self Tapping, Self cutting screws a real bargain 1 lb weight £1.75. Assorted Ceramic Capacitors 100 for £1.00, Assorted Polystyrene Capacitors 100 for £1.50, Assorted Polyester Capacitors 100 for £2.00, Assorted Carbon and Carbon Film Resistors 100 for £1.00, Assorted Wire-Wound Resistors 100 for £2.00, Assorted Transistors/Zeners Diodes all marked 100 for £2.00. Mullard Modules LP 1152 £1.00; LP 1153 £4.00; LP 1165 £4.00; LP 1166 £4.00; LP 1169 £4.00; LP1173 £4.00; LP 1181 £4.00. All above prices include VAT & Postage. T. Powell, 306 St. Paul's Road, London N.1. Telephone 01-226 1489.

PCBs Paxolin 10½" x 4½" 4 - £1.25. 12" x 9" 70p. 17½" x 9½" £1.15. Fibre Glass Double Sided 13" x 6" £1.30. 12" x 10½" £2.10. Unit with 8 Silicon Diodes 600V 20 amp. 8 SCRs 400V 16 amp. 6 Vinkors w.w. resistors etc. £8.75. 300 Small Components Trans. Diodes £1.30. 7lbs. Assorted Components £2.95. List 15p Refundable. Post 20p under £1. Insurance add 15p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL

VALVES. Radio - T.V. - Industrial - Transmitting and Projector Lamps. We dispatch Valves to all parts of the world by return of post, Air or Sea mail, 4000 Types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors. COX RADIO (SUSSEX) LTD., Dept. P.W. The Parade, East Wittering, Sussex, PO20 8BN, West Wittering 2023 (STD Code) 024366.

SMALL ADS

The prepaid rate for classified advertisements is 18 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337; IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

- Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
- The publishers reserve the right to refuse or withdraw any advertisement.
- Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

RECEIVERS AND COMPONENTS

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., 103 South Brink, Wisbech, Cambs, 0945-4188. Immediate settlement.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V. 0-47, 1-0, 2-2, 4-7 & 10 mfd. — 5p. 22, 47 — 5½p. 150V — 8p. 100 — 7p. 150V — 8p. 220 — 8p. 150V — 10p. 470 — 11p. (50V — 10p. 1000/15V — 15p. 1000/25V — 18p. 1000/50V — 22p. Subminiature bead tantalum electrolytics. 0-1, 0-22, 0-47, 1-0 @ 35V, 4-7 @ 6.3V — 8p. 2-2/35V & 4-7/25V — 9p. 10/25V, 15/16V — 12p. 22/16V, 33/10V, 47/6V, 68 & 100 @ 3V — 14p. Mullard Miniature Ceramic E12 Series 63V 2%. 10 pf. to 47 pf. — 3p. 56 pf. to 330 pf. — 4p. Vertical Mounting Ceramic Plate Caps. 50V. E12 22 pf. — 1000 pf. E6 1500 pf. — 47000 pf. — 2p. Polystyrene E12 Series 63V. Hor. Mounting. 10 pf. to 1000 pf. — 3p. 1200 pf. to 10000 pf. — 4p. Mullard Polyester 250V Vert. Mtg. E6 Series. .01 to 1 — 4p. .15, .22 — 5p. .33, .47 — 8p. .68 — 11p. 1-0 — 14p. 1.5 — 20p. 2-2 — 24p. Mylar (Polyester) Film 100V. Vertical Mtg. .001, .002, .005 — 3p. .01, .02 — 4p. .04, .05 — 5p. Miniature Film Resistors Highstab. E12 5%. 0.125 watt 100 to 2M20 1p. 0.250 watt 10 to 10M10 (10% over 1M) 1p. 0.500 watt 100 to 2M70 1p. 1.000 watt 100 to 10M0 1p. 1N4148 — 3p. 1N4002 — 5p. 1N4006 — 7p. 1N4007 — 8p. BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7 — 9p. 20mm. fuses .15, .25, .5, 1-0, 2-0, 3-0 & 5A — 3p. Printed Circuit Holders for 20mm. fuses — 8p. Post 10p (Free over £4). Prices VAT inclusive.

THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN

LED'S. Mixed bags of 4 different sizes and 4 different colours. 50 @ £5.25, 100 @ £9.25 including VAT and post and packing. CWO. Michael Williams Electronics, 47 Vicarage Avenue, Cheadle Hulme, Cheshire. SK8 7JP.

LADDERS

LADDERS. Varnished 25ft. Extd. £34.56. Carr. £2.70. Leaflet. Callers welcome. Open Sat. Ladder Centre, (PEE4) Halesfield (1) Telford, Salop. Tel: 586644.

SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc. 75p plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc. With free Fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

FOR SALE

NATIONAL SEMICONDUCTOR SC/MP development kit plus 4K RAM and 4K PROM. J. Harbour, Holdway House, Child Okeford, Blandford, Dorset. Tel: 0258 86701.

FOR SALE - Back issues of Practical Wireless, Television, Electronics, and Radio Constructor. Some complete years copies, 1959-1969. SAE with offers and enquiries to: T.F. Engineering, 261 Crofton Road, Orpington BR6 8JF.

CHIPS 555 Timers 25p, 741 8 pin 18p, P&P 20p. Web Optics Ltd., 3 Albany Street, Edinburgh.

SEEN MY CAT? 5000 Odds and ends. Mechanical Electrical. Cat free. Whiston, Dept. PRE, New Mills, Stockport.

200 ELECTRONIC Magazines P.E. P.W. W.W. E.T.I. Back to 1964. Old advance signal generator. Video Game. R/C Car. Total £70. Telephone: 0909-78-3918.

PROJECT SUPERSAVE WITH CODESPEED

Full Spec. Devices

PACK M1 2 Calculator Keyboards £1.00
PACK M2 1 x 2102, a 1024 bit static RAM. The most popular of all random access memories in professional and amateur electronics. With full data. £1.25
PACK M3 1 x MM5725 4 function Calculator Chip (not designed for use with Pack M1). With data book. £1.00
PACK E2 1 x 8 digit 0.33" high 7 segment Liquid Crystal calculator style display. With data. £2.95
PACK E3 1 x 8 digit 0.5" high 7 segment Liquid Crystal calculator style display. With data. £4.25
PACK T2 Back by popular demand. A 0.2" 3½ digit Liquid Crystal wristwatch display with data. £1.00
PACK T3 1 x MM5316 Digital Alarm Clock I.C. 12 or 24 hour. Will drive LED, LCD or fluorescent displays. With full instructions. £2.75
PACK T4 1 x 0.8" giant red LED Clock Display. 3½ digit with amp/pm indicator. An excellent display for your digital clock project at only £4.95
PACK DM1 5 x 14 pin dual in line chips each containing 23 matrix signal diodes. With data. 50p.

Untested Packs

PACK D1 180% Guaranteed Good! 15 x DTL logic I.C.'s. Mainly dual J-K flip flops. Replaces those costly TTL flip flops in most projects. Saves £££'s. £1.00
PACK D2 25 x SN7400 type I.C.'s. 100 two 1/2 NAND gates. We guarantee at least 50 good. A giveaway at only £1.00
PACK E1 180% Guaranteed Good! 5 x MM5316 7 segment 0.127" LED displays. Excellent value. £1.00
PACK MU1 (Untested - so no guarantees). Another bargain. 2 x Upper half of a calculator case with built-in keyboard. A snip at only 80p the pair

Satisfaction guaranteed or return complete pack for replacement or refund
MAIL ORDER ONLY - NO CALLERS PLEASE
Postage and Packing please add 25p

CODESPEED

P.O. Box 23, 34 Seafield Road
Copnor, Portsmouth, Hants., PO3 5BJ

BOOKS AND PUBLICATIONS

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £4.50, request free circuit diagram. Stamp brings details unique. TV Publications, (AUSEPE) 76 Church Street, Larkhall, Lanarkshire.

THE END OF COMPUTER CONFUSION: what point have we reached - where are we going? Read Computer Lib/Dream Machine by Ted Nelson. £5.95 from your Local Computer Store, or send £6.45 to Computer Bookshop, Temple House (1), 43-48 New Street, Birmingham.

"RUN YOUR OWN BUSINESS AS AN EXTRA HOME ACTIVITY. LARGE PROFITS. A GENUINE OPPORTUNITY TO SUCCESS." Full details on receipt of s.a.e. Industrial Supplies, 102 Parrswood Road, Withington, Manchester 20.

NEW BACK ISSUES of "PRACTICAL ELECTRONICS" available 65p each Post Free. Open P.O./Cheque returned if not in stock - Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

ELECTRICAL

STYL1 - illustrated equivalents (List 28) also cartridges, leads, etc. Superb quality and service at lowest prices. Fully guaranteed. Free for S.A.E. from FELSTEAD ELECTRONICS (PE), Longley Lane, Gatley, Cheadle, Cheshire SK8 4EE.

EDUCATIONAL

TELEVISION TRAINING

15 MONTHS full-time course for beginners to include all the undermentioned subjects. Short courses, combining one or more subjects, for applicants with previous electronics knowledge.

- 13 WEEKS** ELECTRONICS AND RADIO
- 13 WEEKS** MONOCHROME TELEVISION
- 13 WEEKS** COLOUR TELEVISION
- 13 WEEKS** CLOSED CIRCUIT TV AND VCR

The training incorporates a high percentage of practical work.

NEXT SESSION starts on September 11th

Prospectus from:
LONDON ELECTRONICS COLLEGE,
 DEPT A9 20 Penywern Road,
 London SW5 9SU.
 Tel: 01-373 8721.

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
 Dept. 272Y Intertext House, London SW8 4UJ
 Tel. 01-622 9911 (all hours)
 State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
 Dept. 272Y Intertext House, London SW8 4UJ
 Tel. 01-622 9911 (all hours)
 State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
 Dept. 272Y Intertext House, London SW8 4UJ
 Tel. 01-622 9911 (all hours)
 State if under 18

MISCELLANEOUS

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £9.75 plus 25p P. & P.

'Brain-Freeze' 'em with a MINI-STROBE Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4.30 plus 20p P. & P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5 each plus 20p P. & P.

LOTS MORE! Send 20p for lists. Prices include VAT. (Mail order U.K. only).

BOFFIN PROJECTS

Cunliffe Road, Stoneleigh
 Ewell, Surrey (P.E.)

NEED THE TIME?

MSF 60 KHZ RECEIVER, internal ferrite rod, 1000 Km range, £13.70, or with parts (no case, pcb) for sequential YEAR, MONTH, DATE, DAY, HOURS, MINUTES, SECONDS display only £24.40.

PROGRAM YOUR OWN tunes with this MUSICAL DOORBELL, new jingle every day, just needs bell transformer and speaker, £19.50.

NO LONG WAVE? 100-600 KHz Converter, feeds your 4.1-4.6 MHz receiver, only £9.90.

Each easy-assembly kit includes all parts, printed circuit, case, postage etc, instructions, money back assurance, so **SEND off NOW**. Giro 21-923-4000, foreign prices IRC.

CAMBRIDGE KITS

45 (FJ) Old School Lane, Milton, Cambridge.

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware. Printed circuit boards, top quality for individual designs. Prompt service. Send 25p for catalogue. From:

RAMAR CONSTRUCTOR SERVICES,
 Masons Road, Stratford upon Avon, Warwicks.
 Tel. 4879.

LED DISPLAYS:

0.3" Canode	80p each.
0.5" C.an/cath (specify)	110p pair.
0.8" C.an/cath (specify)	120p each.

CLOCK MODULE: 24hr. Alarm LT801H £5.50 requires T1mr, switches, buzzer, sim MA1002.

FCM7001 Time/Cal/Alm chip	£8.00
MK50397 MM.SS.99 up/down counter	£10.00
SCRUMPI 2 SC/MP MPU kit	£80.00
SCRUMPI 3 SC/MP MPU kit	£107.30

MICROSENSE MPUs for beginners books, two books for beginners £2.00 pair.

CATALOGUE: send SAE.

Prices include VAT, add 30p P&P.

BYWOOD ELECTRONICS, 66 Ebbwens Road,
 Hemel Hempstead HP3 9QR. Tel: 0442-62757.

ARMATURE AND COIL WINDING

ENAMELLED COPPER WIRE

Only top quality materials supplied.
 All orders despatched within 24 hours.

S.W.G.	1 lb reel	1/2 lb reel
10 to 19	£2.95	£1.60
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All prices inclusive of P. & P. in U.K.

COPPER SUPPLIES
 102 Parrswood Road, Withington,
 Manchester 20 Telephone 061-445 8753

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p, chassis punching facilities at very competitive prices, 400 models to choose from, free literature (stamp would be appreciated). BAZELLI, Dept: No. 23, St. Wilfred's, Foundry Lane, Halton, Lancaster. LA2 6LT.

100 Resistors 75p

±W 5% c/FILM 2-20-2-2MΩ (E12)
 10 each of any value. Send S.A.E. for free sample

C60 CASSETTES 30p
C90 CASSETTES 45p

All prices include VAT.
 Quantity Discounts
 10 Units 5%
 50 Units 7%
 100 Units 10%

All Cassettes in Plastic Case with Index and Screwed Assembly

Add Postage 10p in £1
SALOP ELECTRONICS
 23 WYLE COP
 SHREWSBURY
 Tel. 53206



RADIO CONTROL SPECIALISTS

Kits for multi channel systems. Special parts and accessories.

S.A.E. FOR LEAFLETS
 Tel: 0602 395418

MICRON R/C, Hayworth Road,
 Sandiacre, Nottingham.

SITUATIONS VACANT

Radio Technicians

Government Communications Headquarters has vacancies for Radio Technicians. Applicants should be 19 or over

STANDARDS required call for a sound knowledge of the principles of electricity and radio, together with appropriate experience of using and maintaining radio and electronic test gear.

DUTIES cover highly skilled telecommunications/electronic work, including the construction, installation, maintenance and testing of radio and radar telecommunications equipment and advanced computer and analytic machinery.

QUALIFICATIONS: Candidates must hold either the City and Guilds Telecommunications Part 1 (Intermediate) Certificate or equivalent HM Forces qualification.

SALARY (inc. supps.) from £2,673 at 19 to £3,379 at 25 (highest pay on entry) rising to £3,883 with opportunity for advancement to higher grades up to £4,297 with a few posts carrying still higher salaries.

Opportunities for service overseas.

Further particulars and application forms available from:

GCHQ

Recruitment Officer, (Ref PE/9)
 GCHQ, Oakley,
 Priors Road, Cheltenham, GL52 5AJ.
 Cheltenham (0242) 21491 Ext 2270



WANTED

TRAINEE

COMPUTER ENGINEERS

O/A Levels ONC or City and Guilds or TV Engineering?

The UK Training Division of Control Data who manufacture the world's most powerful computer wishes to meet suitable young people between the ages of 21-35 to train as computer engineers with a view to subsequent employment at various locations. This is an opportunity to be trained in computer skills by a leading computer manufacturer for an occupation and industry which offers progressive salaries, really interesting work and excellent career prospects.

Spend an evening with us and investigate our training entry scheme in detail. Find out whether you would qualify for support under TOPS*

FOR LONDON INTERVIEWS CALL 01-637 2171 AND ASK OUR RECEPTIONIST TO CONNECT YOU TO PROGRAM 2E.

For outer London interviews please call either:
BIRMINGHAM OFFICE 021 622 7383
MANCHESTER OFFICE 061 832 3114
LEEDS OFFICE 0532 450145
SOUTHAMPTON OFFICE 0703 38644

*TOPS - The NATIONAL TRAINING OPPORTUNITIES SCHEME under which training costs and personal subsistence are paid to suitable candidates whilst undergoing training which is designed to lead to employment.

PLEASE
MENTION
'PRACTICAL
ELECTRONICS'
WHEN
REPLYING
TO
ADVERTISEMENTS

SINTEL FOR BOOKS, CMOS AND COMPONENTS

6800 Booklet 1.80, MOT CMOS Databk 3.50, 6800 Appl Mon 12.95, 6800 Prog Mon 5.35, SC/MP Introkit Mon 0.75 NS TTL Databk 2.10, RCA CMOS Databk 5.45, 8085 User's Mon 5.15, Z80 Ass Long Prog Mon 7.50, Z80 CPU Mon 5.60, Z80 CTC Spec 0.80, Z80 PIO Mon 3.30. Also a full range of CMOS - send for free catalogue MPUs: MEK6800D2 205.20, MC6820 7.50, Z80 18.14, Z80A 24.19, Z80CTC 10.96, Z80PIO 10.96, Memories: 2102-A 2.00, 2112A-4 3.13, Displays: Type FND500 C.C. 1.40, Type TL321 C.A. 1.40, SLOI 5.29, Crystals: 32.768KHz 3.19, Clock ICs: AY51202 3.35, AY51224 3.73, MK50253 5.83, Soldercon Pins: 100 0.54, 1000 4.32, 3000 11.34. Free catalogue by return. All items C.W.O. Prices inclusive of VAT. Add 35p p&p. SINTEL, P.O. Box 758, 209 Cowley Road, Oxford. Tel. (0865) 49791.

THE FABULOUS D2 MICROPROCESSOR EVALUATION KIT FROM MOTOROLA.

Featuring *24 key keyboard *Seven segment display *Cassette interface *Erom & Ram Expandable *Interface Capability *Full Documentation *5 Volt power supply Required *One years FREE membership of The Amateur Computer Club with every purchase*. £176 + £1.50 P & P + 8% VAT.

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10-19	2.60	1.40	.66	.55
20-29	2.80	1.60	.85	.65
30-34	3.00	1.70	.95	.70
35-40	3.35	1.90	1.10	.79
40-43	4.50	2.50	1.90	1.25
44-46	5.00	3.00	2.10	1.65
47	8.00	5.00	3.00	1.76
48	15.00	9.00	6.00	3.30

Tinned Copper, Even Gauges 14-30 £3 per lb. Multicore 60/40 Solder 18SWG £3.24 per lb. Prices include P & P and VAT.

SAE brings list of copper and resistance Wires.


THE SCIENTIFIC WIRE COMPANY

PO Box 30 London E.4.
Reg. Office, 22 Coningsby Gdns.

MISCELLANEOUS - Continued

BEST OFFER EVER £99.99 Total £110.64 inc p p & VAT TV CAMERA

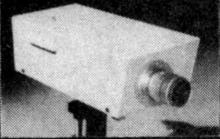Complete TV Camera Kit for under £100.00 (excluding P/P and VAT). Offer includes Lens, Tube and FREE Modulator. Plugs directly into AE socket of TV or VCR. Reliable high performance design. Suitable for Security, Education, Industry, etc. Fully compatible with other CCTV Equipment. Fully Guaranteed Parts. Buy it with your Credit Card.



CROFTON ELECTRONICS LIMITED

35 Grosvenor Road, Twickenham, Middlesex TW1 4AD. Tel. 01-891 1923

CABINET FITTINGS

FOR

Stage Loudspeakers and Amplifier Cabs
Fretcloths, Coverings, Sirap & Recess Handles, Feet, Castors, Jacks & Sockets, Cannons, Bulgin 8 ways, Reverb Trays, Locks & Hinges, Corners, Trim, Speaker Bolts etc.
Send 2 x 9p Stamps for samples and illustrated catalogue.

ADAM HALL (P.E. SUPPLIES)

Unit 3, Carlton Court, Grainger Road
Southend-on-Sea, Essex.

CLEARING LABORATORY. Scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

BELLS AND SIRENS

Carters Siren £5-53
Industrial Six Inch Bell £8-27
Prices inclusive


Send Cheque, P.O. to

CWAS ALARM

11, Denbrook Walk

Bradford B D4 0QS

S.A.E. for full Price List

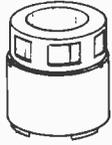

6 to 12V D.C.

12V D.C.

MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination.
Cassette B: 12-24 w.p.m. for professional examination preparation.
Morse by light system available. Morse Key and Buzzer unit for sending practice.
Prices each cassette (including booklets) £4.50. Morse Key and Buzzer £4.50.
Prices include postage etc., Overseas Airmail £1.50 extra.

MHEL ELECTRONICS (Dept. PE)

12 Longshore Way, Milton,
Portsmouth PO4 8LS.

PRACTICAL ELECTRONICS P.C.B.'s

in glass fibre tinned and drilled

Dec. 77 Car Burglar Alarm 1412-1 88p.

May 78 Moving Light Display £2.96.

May 78 Workshop Power Supply £1.97.

May 78 Chorus Generator £2.56.

July 78 Dimwit £1.48. C.W.O. Please.

For full list and current boards please send S.A.E.

P.C.B.'s also produced from customer's own master - please send for quote.

PROTO DESIGN

14 Downham Road, Ramsden Heath, Billericay, Essex

PRINTED CIRCUIT BOARDS made to your requirements. Write for details and price list. Western Circuit Designs, 31 Great Hinton, Trowbridge, Wilts. BA14 6BY.

BUILD THE TREASURE TRACER

MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- 4,000 already sold
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screw-driver, pliers and snips
- As seen on BBC-1 and BBC-2 TV

Send stamped addressed envelope for leaflet

Complete Kit

£15.95

Built and tested

£20.95

Post £1.20 - £1.37 VAT

Post £1.20 - £1.77 VAT

MINIKITS ELECTRONICS

6g CLEVELAND ROAD

LONDON E18 2AN (Mail Order Only)

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

BARGAIN PARCELS SAVE POUNDS

Huge quantities of electronic components must be cleared as space required. 1000's of capacitors, resistors, transistors, Ex equipment panels etc. covered in valuable components. No time to sort. Must sell by weight 7 lbs - £4.95; 14 lbs - £7.95; 28 lbs - £12.00; 56 lbs - £20.00, 112 lbs - £30.00.

BARGAIN PACKS

Don't let your environment dehydrate you. Buy a Honeywell Humidity Controller membrane operated with 1" shaft, ideal for greenhouses, centrally heated homes, etc. Build your own humidity alarm, 3.75A. Contacts at 250V £1.50 each 3 for £4.00

4 aluminium boxes 128 x 44 x 38 mm ideal for signal injectors, etc. £1.00.

100 miniature reed switches ideal for burglar alarms, model railways, etc. £3.30.

6 x 6-pole 12 volt reed relays on board £2.45.

High quality computer panels smothered in top grade components: 5 lbs £4.75; 10 lbs £8.95.

Miniature edge-wise panel mounting level meters 200 ua.fsd 90p.

Miniature transistorised f.m. front end with integral tuning gang 88-108MHz £2.50.

New U.H.F. transistor TV tuners 4 pushbutton type £3.50.

Rotary type with slow drive and AE. socket £2.50.

Aluminium TV coax plugs. 10 for £1.00.

Hardware Packs each containing 100's of items including: BA nuts and bolts, Nylon, Self-lapping, Posidrive, "P" clips, Cable clamps, Fuse holders, Spare nuts etc., etc. £1.00 per pound. Heavily insulated E.H.T. Discharging Probe with lead and earth connector 60p each.

Ultrasonic transducers, transmitter and receiver 14mm diam. 40kcs £4.25 per pair.

Magnetic earpieces with plug and lead 25p each, 5 for £1.00.

Crystal earpieces with lead 40p each, 3 for £1.00.

10 assorted convergence pots £1

12 quill, low profile I.C. sockets, 14 pin £1

DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS

Includes 150 sq. ins. copper clad f/g board, 1 lb ferric chloride, 1 dolo etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions - only £5.30.

150 sq. in. fibre glass board.....£2.00

Dolo pen.....90p

1 lb ferric chloride to mil spec.....£1.25

5 lbs ferric chloride to mil spec.....£5.00

Instruction sheet.....20p

40p P & P ON ALL ABOVE ITEMS. SEND CHEQUE OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY, DEPT PE, 149A BROOKMILL RD., DEPTFORD SE8

VERNITRON FM4 10.7mHz miniature ceramic filters 50p each, 3 for £1.00.

Miniature mains transformers, fully shrouded. 240V in 6-0-6V at 100MA. out. Ex. New equipment, complete with mains lead and plug on input and short leads on output. 95p.

Semiconductor Bargains TH3 Thermistors 10 for £1.00.

100 new and marked transistors. Lots of types including BC148, BC154, BF274, BC212L, BF200 etc. £4.95.

200 new and marked transistors, including all above plus 2N3055, AC128, BFY50, BD131 etc. £9.95.

100 mixed diodes including zener, power and bridge types £3.30.

Bridge rectifier 100V 2.5 amp. 4 for £1.00.

Brand new ITT 25kV T.V. triplers for Decca Bradford chassis £2.50, 5 for £10.00.

50 Germanium diodes ideal for crystal sets etc. £1.00.

Motorola, 1 watt audio amplifier I.C. 9-16V 8-14Ω, 10-400MV sensitivity, S.C. proof, no heat sink required. Supplied with data and circuits. 90p.

Data and circuits alone, 20p + SAE.

Full spec. I.R. diodes, 200V 1A. 20 for £1.00.

100 for £4.50. SN76115N £1.00.

BF200, 6 for £1. BC212L, 10 for £1.

BC154, 12 for £1. BF274, 12 for £1.

BC148, 12 for £1.


Voricap diodes, 10 for £1.

Component Bargains

300 mixed resistors 1/2 & 1/4 watt £1.50. 300 modern mixed caps, most types, £3.30. 200 mixed resistors, mostly 1 & 2 watt, £1.50. 100 mixed polyester caps £2.20. 100 mixed modern miniature and ceramic plate caps £1.20. 100 mixed electrolytics £2.20. 300 printed circuit resistors £1.00. 25 mixed pots and presets £1.50. 100 mixed carbon film and metal film resistors mostly miniature lots of values, £1.20.

500 for £4.90. 100 mixed high wattage resistors, wirewound, etc. £2.20. 20 assorted VDRs and Thermistors £1.20. 25 assorted preset pots, skeleton, etc. £1.20.

STORAGE CABINETS

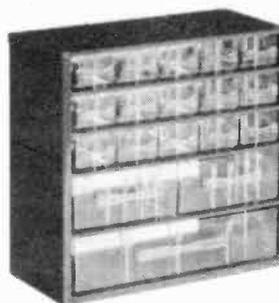

Type 1118

Metal cabinets with transparent plastic drawers. Ideal for components, small parts, nuts, bolts etc. Many other uses in the home, workshop, laboratory etc.

Choose from the following range to suit your own needs:

Type	Height (ins.)	No. of Drawers			Price
		Total	Small	Medium Large	
1118	11	18	15	2 1	£8.65
1130	11	30	30	-	£8.95
1633	16	33	30	2 1	£10.95
1150	18	50	50	-	£12.95
1860	22	60	60	-	£14.95

All cabinets are finished Blue, 12" wide x 5 3/4" deep. Prices include VAT and Post. Satisfaction or money refunded. Cheque/P.O. to:

MILLHILL SUPPLIES (TOOLS)

35 PRESTON CROWMARSH, BENSON, OXON. OX9 6SL

New from Mantec

A comprehensive Home Study Course in Electronics

Suitable for Beginners and Students

The Course which gives you "Right from the Start" the practical experience as well as the all important back-up theory.

Suitable preparation for C and G examinations

Ensure your future in tomorrow's technology

The home study course that tells not only how but why

The Course includes:- 1 The Manual. Easy to read and understand, set out in a clear and concise way, includes numerous experiments and diagrams.

2 The Kit. All components necessary for the experiments and projects covered. Mantec also provides

a tutorial support service for students requiring further advice.

Send today for your "Right from the start" Home Study Course. Price £35.00 including VAT.

Fill in the coupon Now!

Mantec the leaders in Manufacturing Technology

Mantec, 7 Dellsome Lane, Welham Green, Hatfield, Herts.

To: Mantec, 7 Dellsome Lane, Welham Green, Hatfield, Herts.

Please send me..... "Right from the Start" home study course(s).

I enclose Cheque/Postal Order for £.....

Name: _____

Address: _____



Wilmslow Audio

THE firm for speakers!

SEND 15p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND DISCOUNT PRICE LIST

ACT ● AUDAX ● BAKER
BOWERS & WILKINS ● CASTLE ● CELESTION
CHARTWELL ● COLES ● DALESFORD
DECCA ● EMI ● EAGLE ● ELAC ● FANE
GAUSS ● GOODMAN ● HELME ● I.M.F.
ISOPHON ● JR ● JORDON WATTS
KEF ● LEAK ● LOWTHER ● MCKENZIE
MONITOR AUDIO ● PEERLESS ● RADFORD
RAM ● RICHARD ALLAN ● SEAS
TANNOY ● VIDEOTONE ● WHARFEDALE

WILMSLOW AUDIO (Dept. P.E. 8)
SWAN WORKS, BANK SQUARE, WILMSLOW,
CHESHIRE SK9 1HF

Discount Hi-Fi, etc. at 5 Swan Street and 10 Swan Street
Tel.: Wilmslow 29599 for Speakers Tel.: Wilmslow 26213 for Hi-Fi

TTLs BY TEXAS			74LS SERIES			LINEAR ICs			TRANSISTORS			BFY5/2			TIP41C			0100ES			BRIDGE RECTIFIERS		
7400	13p	74116	200p	74388	150p	8302	175p	4015	84p	MC1495	400p	AC127/8	20p	BFY56	33p	TIP42A	78p	2N3823	70p	*BY127	12p	RECTIFIERS	
7401	14p	74118	130p	74390	200p	8308	316p	4018	45p	*AY1-0212	800p	AD143	70p	BFY90	50p	TIP42B	70p	2N3886	90p	*BY127	12p	RECTIFIERS	
7402	14p	74119	110p	74392	200p	8310	276p	4017	45p	*AY1-5050	212p	AD181/2	45p	BLV57	700p	TIP295	78p	*2N3856/6	18p	*OAR1	15p	RECTIFIERS	
7403	14p	74121	28p	74394	225p	8312	160p	4019	45p	*AY1-3115	63p	BC107/8	11p	BRV39	40p	TIP305	70p	*2N4036	65p	*OAR5	15p	RECTIFIERS	
7404	17p	74122	28p	74LS SERIES		8316	160p	4020	100p	*AY5-1317	63p	BC109	11p	BSX19/20	20p	*TIS43	34p	*2N4058/9	12p	*OAR9	9p	RECTIFIERS	
7405	18p	74122	48p	74LS00	22p	8318	225p	4021	100p	*AY5-1320	320p	BC147/8	9p	*BU105	190p	*TIS93	30p	*2N4081/2	18p	*OAR9	9p	RECTIFIERS	
7406	32p	74123	55p	74LS00	22p	8320	225p	4022	100p	*AY5-1320	320p	*BC157/8	12p	*BU205	220p	*TIZ108	12p	*2N4123/4	22p	*OAR9	9p	RECTIFIERS	
7407	32p	74125	55p	74LS00	22p	8322	225p	4023	22p	*AY5-1320	320p	*BC157/8	12p	*BU208	200p	*TIZ300	13p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7408	19p	74126	60p	74LS00	22p	8324	225p	4024	20p	*AY5-1320	320p	*BC157/8	12p	*BU208	200p	*TIZ300	13p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7409	19p	74128	75p	74LS00	22p	8326	225p	4025	20p	*AY5-1320	320p	*BC189C	12p	*BU406	145p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7410	15p	74132	75p	74LS10	24p	8328	225p	4026	20p	*AY5-1320	320p	*BF181	11p	*MJ3001	225p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7411	24p	74136	50p	74LS10	24p	8330	225p	4027	50p	*AY5-1320	320p	*BC173/7	12p	*MJ491	200p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7412	20p	74141	70p	74LS14	100p	8332	225p	4028	100p	*AY5-1320	320p	*BC173/7	12p	*MJ491	200p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7413	30p	74142	200p	74LS14	100p	8334	225p	4029	100p	*AY5-1320	320p	*BC173/7	12p	*MJ491	200p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7414	60p	74145	90p	74LS22	28p	8336	225p	4030	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7415	27p	74148	150p	74LS22	28p	8338	225p	4031	200p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7416	17p	74150	100p	74LS22	28p	8340	225p	4032	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7417	40p	74151A	70p	74LS22	28p	8342	225p	4033	180p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7418	22p	74153	100p	74LS22	28p	8344	225p	4034	200p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7419	36p	74154	100p	74LS22	28p	8346	225p	4035	110p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7420	17p	74150	100p	74LS22	28p	8348	225p	4036	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7421	40p	74151A	70p	74LS22	28p	8350	225p	4037	80p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7422	22p	74153	100p	74LS22	28p	8352	225p	4038	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7423	36p	74154	100p	74LS22	28p	8354	225p	4039	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7424	30p	74155	90p	74LS22	28p	8356	225p	4040	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7425	40p	74156	90p	74LS22	28p	8358	225p	4041	80p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7426	40p	74156	90p	74LS22	28p	8360	225p	4042	80p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7427	36p	74157	70p	74LS22	28p	8362	225p	4043	80p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7428	36p	74157	70p	74LS22	28p	8364	225p	4044	80p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7429	36p	74157	70p	74LS22	28p	8366	225p	4045	80p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7430	17p	74160	100p	74LS22	28p	8368	225p	4046	130p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7431	36p	74161	100p	74LS22	28p	8370	225p	4047	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7432	30p	74161	100p	74LS22	28p	8372	225p	4048	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7433	40p	74162	100p	74LS22	28p	8374	225p	4049	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7434	36p	74162	100p	74LS22	28p	8376	225p	4050	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7435	36p	74162	100p	74LS22	28p	8378	225p	4051	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7436	36p	74162	100p	74LS22	28p	8380	225p	4052	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7437	36p	74162	100p	74LS22	28p	8382	225p	4053	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7438	36p	74162	100p	74LS22	28p	8384	225p	4054	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7439	36p	74162	100p	74LS22	28p	8386	225p	4055	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7440	36p	74162	100p	74LS22	28p	8388	225p	4056	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7441	70p	74166	140p	74LS22	28p	8390	225p	4057	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7442	60p	74168	140p	74LS22	28p	8392	225p	4058	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7443	112p	74170	240p	74LS22	28p	8394	225p	4059	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7444	112p	74172	240p	74LS22	28p	8396	225p	4060	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7445	100p	74173	120p	74LS22	28p	8398	225p	4061	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7446	80p	74174	90p	74LS22	28p	8400	225p	4062	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7447	80p	74175	85p	74LS22	28p	8402	225p	4063	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7448	80p	74176	90p	74LS22	28p	8404	225p	4064	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7449	100p	74177	90p	74LS22	28p	8406	225p	4065	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7450	100p	74178	90p	74LS22	28p	8408	225p	4066	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7451	17p	74181	150p	74LS22	28p	8410	225p	4067	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7452	17p	74180	90p	74LS22	28p	8412	225p	4068	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7453	17p	74180	90p	74LS22	28p	8414	225p	4069	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7454	17p	74181	90p	74LS22	28p	8416	225p	4070	100p	*AY5-1320	320p	*BC182/3	10p	*MJ2955	100p	*TIZ502	18p	*2N4125/6	22p	*OAR9	9p	RECTIFIERS	
7455	17p	74181	90p	74LS22	28p	8418	225p	407															



Nights of Delight.....

(sent in a plain
brown envelope)

DORAM

EDITION 5 CATALOGUE

Name

Address

.....

.....

I enclose cheque/P.O. **75p** inc. p.p.

Signed

Date

Doram Electronics Ltd
P.O. Box TR8
Wellington Road Estate,
Wellington Bridge,
Leeds LS12 2UF

PE 4

The new '78-'79 edition 5
catalogue is packed full of
new merchandise including

**MICRO PROCESSOR
BASED KITS.**

There are over 2,000 items
in the 120 pages for your

Night of Delight and
**50p WORTH OF FREE
GOODS**

Send for your copy now.


Overseas orders,
except for N. Ireland,

Please add **35p**
to cover despatch by Air.

Doram Electronics Ltd
P.O. Box TR8
Wellington Road Estate,
Wellington Bridge,
Leeds LS12 2UF


MAPLIN

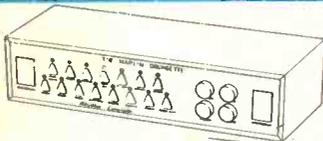everything for the modern D.I.Y. electronics enthusiast and more.




THE 'DRUMSETTE' RHYTHM GENERATOR

Organists, pianists, guitarists... an automatic drum set to accompany you! Nine highly realistic instruments play fifteen different rhythms. Fifteen rhythm-select touch switches and a touch plate for stop/start without rhythm change gives absolute ease of operation. Build it yourself for under £65 including smart teak-effect cabinet. See it and hear it in our shop! Send for full construction details now: MES49 price 25p. (All prices include V.A.T. and postage & packing).

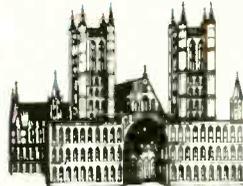

REVERBERATION SYSTEMS

High quality spring line driver module uses 4 integrated circuits and two transistors. Built and tested circuit board with wiring instructions for spring line. XBB5G, price £6.00. Power supply to suit driver module costs around £2.50 and construction details are in catalogue, or ask for leaflet MES24. Mechanical spring lines: Short line (XL08J): £4.49; Long line (XBB4F) £10.39. (All prices include V.A.T. and p & p.)

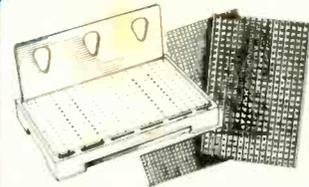

BOARDS AND PCB'S

Pages 59 to 61 of our catalogue show you our range of Veroboards and S-Decs or if you prefer to make your own pcb's a range of etching systems including the novel etch-in-a-bag system, plus printed circuit transfers for the professional finish to your boards.




9-CHANNEL RADIO CONTROL SYSTEM

A comprehensive model control system, featuring nine independent fully proportional channels achieved by a design using very few components thus keeping the cost to a minimum. Full construction details in our booklet (XF03D)


price £1.20.

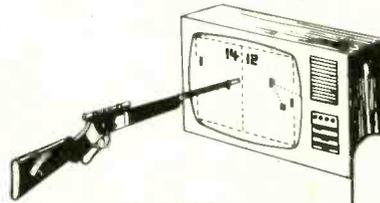All prices include V.A.T. and postage & packing.



T.V. GAME

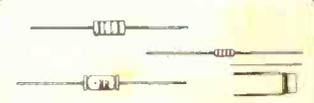A fascinating TV game kit that plays football, tennis, squash and practice for only £21.59. Reprint of construction details 25p. Add on rifle kit only £10.60. (All prices include V.A.T. and p&p).




MASSIVE RANGE OF COMPONENTS

For instance the capacitor section in our catalogue includes non-polarised electrolytics and our resistor section includes even 1% tolerance types. Get our fascinating catalogue now—you won't regret it.




AUDIO MIXER

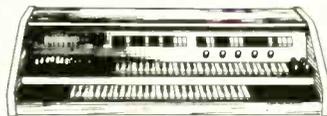A superb stereo audio mixer. It can be equipped with up to 16 input modules of your choice and its performance matches that of the very best tape-recorders and hi-fi equipment. It meets the requirements of professional recording studios, FM radio stations, concert halls and theatres. Full construction details in our catalogue. A component schedule is available on request.



ELECTRONIC ORGAN

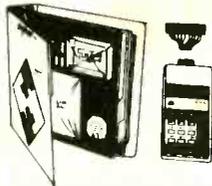The only organ you can build in stages and tailor to your requirements as you go along—and at each stage you'll have a fully working instrument. We haven't got the gimmicks yet—(they're coming soon) but we have got the most beautiful sounds—you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.



MICROPROCESSOR

Build a mini-computer with our microprocessor kit. Features: 46 different instruction types; 256 bytes of read/write memory (more are easily added) microprocessor can address up to 65,536 8-bit-bytes. Complete kit for use with teletype etc (XB91Y) £74.10. 20-key keyboard for use with above (in place of teletype) (XB92A) £71.11. Both kits with detailed instruction books. See our newsletters for details of additional RAM's, tri-state interfacing chips, number-cruncher and standard cassette tape-recorder interface to store your programmes. (All prices include V.A.T. and p&p.)



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices - our latest special offers - details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).



POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

NAME _____

ADDRESS _____

IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations! Over 30 pages of complete projects to build! Thousands and thousands of useful components described and illustrated!

No wonder it's a bestseller!

DON'T MISS OUT! SEND 60p NOW!

MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155

Shop: 284, London Road, Westcliff-on-Sea, Essex

(Closed on Monday) Telephone: Southend (0702) 715157