

12 SEP
PRACTICAL

ELECTRONICS

AUGUST 1980

55p



PE
TELETEXT
 with
INFRA-RED
REMOTE CONTROL

Also inside...


PE MAGNUM... METAL LOCATOR

NEW GIANT SUPERPRINTS PLUS FREE FILM

for every one you send for processing
by the Practical Electronics
Colour Print Service

**GIANT
SUPERPRINTS**

30% more print area
for only 1p extra

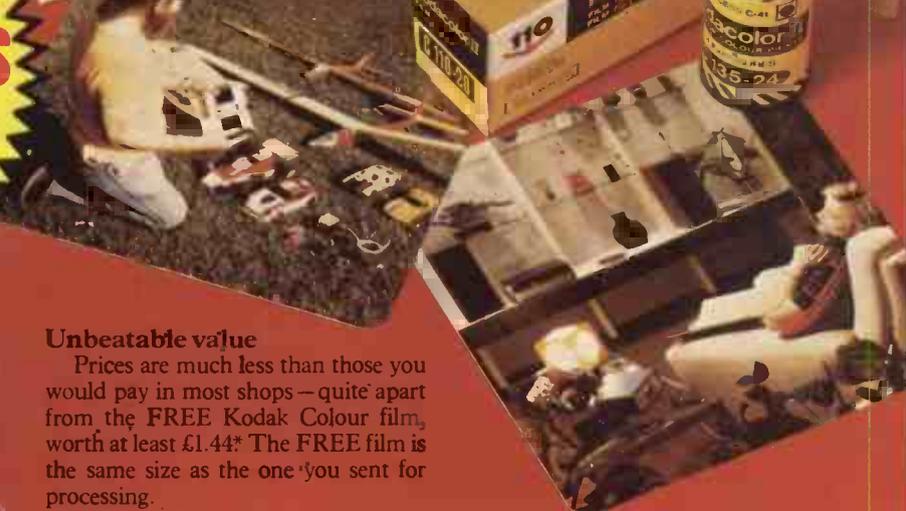

Photography can cost you a lot less these days if you know how to go about it. Hundreds of thousands of magazine readers are delighted with this reliable Colour Print Service — and the replacement films that come FREE every time they use it! So why don't you give it a try? Here's what you do. Send any make of colour print film inside the envelope enclosed in this issue. Or fill in the coupon below and send it with your film in a strong envelope to: Practical Electronics Colour Print Service, Freepost, Teddington, Middlesex, TW11 8BR. No stamp is required.

Send no money

We are so confident in the reliability of the service and the quality of our prints, every one of which is checked by professionals at our laboratories, that you don't pay until you have received them!

Luxury colour prints

You will be amazed at the crisp, sharp, hi-definition sheen finish of the prints we supply... with elegant rounded corners and borderless to give you maximum picture area. And now with the new Giant Superprints you get 30% more picture area for just 1p extra per print.

Unbeatable value

Prices are much less than those you would pay in most shops — quite apart from the FREE Kodak Colour film, worth at least £1.44*. The FREE film is the same size as the one you sent for processing.

The new Giant Superprints cost you only 17p each, compared with 16p for the standard enprints available with this service. A further charge of £1 is made towards development, postage and packing. The offer is limited to the UK. For Eire, CI and BFPO a handling surcharge will be made.

Free Album Sheets

One album voucher is sent with each film we process. Collect 3 vouchers and we send you a set of FREE album sheets.

More benefits to you

You benefit in two additional ways. Firstly, you enjoy a personal service with every care taken over each individual order. And secondly, you pay only for what you get — with no credit vouchers as with many other companies. An invoice comes with your prints, so it is a straight business transaction.

*Kodak Recommended Retail Prices: 110/20 — £1.44; 126/20 — £1.51; 135/24 — £1.67; 135/36 — £2.12.

Offer exc. Minolta & Sub-miniature. Roll film 20p surcharge. 400 ASA 20p surcharge. Superprints can only be produced from Kodacolor II, C41 and Agfa CNS cassette and cartridge film. Prices correct at time of going to press.

**USE THIS LABEL
IF YOU HAVE NO
ENVELOPE,
OR PASS IT TO A
FRIEND. IT IS
USED TO SEND
YOUR PRINTS
& FREE FILM**

From: Practical Electronics Colour Print Service, Freepost, Teddington, Middlesex, TW11 8BR. Please print my film Superprint/Standard Enprint size (delete size which is not required).

Mr/Ms _____

Address _____

Postcode _____

Prints are normally despatched within four working days of receipt of film.

PRACTICAL ELECTRONICS

VOLUME 16 No. 8 AUGUST 1980

CONSTRUCTIONAL PROJECTS

DOORBELL MONITOR by <i>J. A. Barrow</i>	30
Logs calls and lights up for callers	
PE TELETEXT Part 1 by <i>David Shortland</i>	38
Introduction, transmitter and receiver circuits	
PE MAGNUM METAL LOCATOR Part 1 by <i>Andy Flind</i>	51
Supersensitive detector that puts practicality into divination	
CONSTANT CURRENT SOURCES by <i>I. Millar</i>	60
Equipment for Electrochemistry	

GENERAL FEATURES

ACORN REVIEW by <i>Dr A. A. Berk</i>	22
System 3	
STRICTLY INSTRUMENTAL by <i>K. Lenton-Smith</i>	26
Matching the speaker signal from your organ to an external amplifier	
SEMICONDUCTOR UPDATE by <i>R. W. Coles</i>	33
7910 UAA1003 MN9106	
ELECTROCHEMISTRY by <i>A. T. Kuhn MA DPhil</i>	35
A molecular marvel	
MICROBUS by <i>D.J.D.</i>	46
Morse-code Generator—Bulls and Cows for ZX80—Inverted Characters on VDU— Digital Alarm Clock	
INGENUITY UNLIMITED	66
Hex Keypad—Multiplexer—Keyboard Scanner—Inexpensive A-to-D Converter— Portable Tennis	

NEWS & COMMENT

EDITORIAL	17
MARKET PLACE	18
New products	
INDUSTRY NOTEBOOK by <i>Nexus</i>	21
What's happening inside industry	
CAPACITOR OFFER	45
A bargain not to be missed	
SPACEWATCH by <i>Frank W. Hyde</i>	49
Solar Energy and the Satellite Power System	
PATENTS REVIEW	59
READOUT	70

OUR SEPTEMBER ISSUE WILL BE ON SALE SATURDAY, 16 AUGUST 1980
(for details of contents see page 29)

© IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

WATFORD ELECTRONICS

Continued from opposite side)

DIODES	BRIDGE RECTIFIERS	SPEAKERS	ALUM. BOXES	VEROBOARD	NOISE DIODE	TRIACS	VERO WIRING PEN	FERRIC CHLORIDE	EURO BREADBOARD	DALO ETCH RESIST	BIMBOARDS	COPPER CLAD BOARDS	DIAC	SOLDERCON PINS
AA129 25	1A/50V 20	80.0-3W 2" x 2" 75	3x2x1" 55	0-1 0-15 0-1 0-15	25J 180	3A/100V 48	Pkt of 36 pins 20p	1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	100 pins 60p
AA129 15	1A/200V 22	400 2.5" 80	2 1/2 x 5 1/2 75	(copper clad) (plain)		3A/400V 50	Spot face cutter 107p	1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	500 pins 250p
BA102 15	1A/50V 20	800 2.5" 80	4 1/2 x 1 1/2 75			3A/400V 50	Pin insertion tool 147p	1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
BY100 24	1A/200V 22	800 2.5" 80	4 1/2 x 1 1/2 75			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
BY127 12	1A/400V 29	800 2.5" 80	4 1/2 x 1 1/2 75			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CRO33 158	1A/600V 34	80 5W 80	4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CA9 45	2A/50V 35	7" x 4" 250	4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CA47 18	2A/100V 44	80 3W 160	4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CA70 12	2A/200V 46	6" x 4" 250	4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CA79 12	2A/800V 65		4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CA81 15	4A/100V 72		4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CA85 15	6A/100V 73		4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CA90 8	6A/200V 78		4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CA91 8	6A/400V 85		4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CA95 8	8Y184 56		4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CA95 8	VM18 DIL 50		4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CA200 9			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
CA202 9			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
IN914 4			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
IN916 6			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
IN4002 5			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
IN4003 6			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
IN4004/5 6			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
IN4006/7 7			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
IN4148 4			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
IS44 20			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
0-BA30V 28			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
0-BA100V 30			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
0-BA200V 35			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
1A/50V 37			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
1A/100V 42			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
1A/200V 47			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
1A800V 70			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
5A300V 43			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
5A600V 43			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
8A300V 48			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
8A600V 55			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
12A300V 59			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
12A500V 62			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
12A800V 65			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
15A700V 195			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
BT106 150			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
BT116 150			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
C106D 38			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
MCR101 32			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
TC14 22			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
TC145 28			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	
2N444 140			4 1/2 x 2 1/2 100			3A/400V 50		1 lb bag Anhydrous 175p	4x17" 387p	20p VQ board 144p	25p DIP board 326p	20p VQ board 144p	25p DIP board 326p	

REPT ELECTRONICS	VOLTAGE REGULATORS	WATFORD'S BOOKSHOP CORNER. (No VAT on Books)
LEDS Plus, Clip	1A T03 +ve -ve	Silicon Chip & You 250p
TIL209 Red 125" 13	5V 7805 145p 7905 220p	Running Wild: Next Industrial Revolution 250p
TIL211 Grn 125" 18	12V 7812 145p 7912 220p	The Mighty Micro 550p
TIL212 Yellow 22	15V 7815 145p	Future with Micro-Electronics 430p
TIL220 2" Red 15	18V 7818 145p	Introduction to Microcomputer Beginners Book Vol. 0 500p
0-2" Yellow, green and Amber 18	1A T0220 Plastic Casing 5V 7805 60p 7905 65p	Beginners Book Vol. 1 590p
Rectangular LEADS, Red, Green and Yellow 30	45V 7812 60p 7912 65p	C201 Microprocessors: From Chlps to Systems 690p
2N5777 45	15V 7815 60p 7915 65p	Illustrating BASIC 280p
OC71 120	18V 7818 60p 7918 65p	Little Book of BASIC 540p
ORP12 63	24V 7824 60p	Programming in BASIC for Business 690p
0-2" Infra Red (emit) 40	100mA T092 Plastic Casing 5V 7805 30p 7905 35p	Computer Programs that work Basic Computer Games 550p
TIL32 Infra Red (emit) 58	6V 7812 30p 7912 35p	CRYSTALS
SFH205 (detector) 70	8V 7812 30p 7912 35p	100kHz 323p
TIL78 (detector) 70	12V 7812 30p 7912 35p	455kHz 385p
OPTO isolators	15V 7815 30p 7915 35p	1MHz 323p
TIL 111/2 or 117 100	18V 7818 30p 7918 35p	1.6MHz 395p
7 Segment Displays	CA3085 95 LM323K 625p	1.008MHz 383p
TIL312 & 313 3" 105	LM3000 170 LM325N 240	1.80MHz 389p
TIL321 5" C.An 115	LM305H 140 LM326N 240	1.8432MHz 362p
TIL322 5" C.Th 115	LM309K 135 LM327N 270	2.4576MHz 362p
TIL704 3" C.Ch 99	LM317K 350 LM327Z 39	3.2768MHz 323p
DL1747 6" C.An 180	7805 5V/5A 595p	4MHz 290p
8" Orange C.A. 250	UA78HG +5 to +24V 5A 650	4.032MHz 323p
FND357 C.A. 120		4.433619M 135p
3" Green C.A. 150		5.0MHz 355p
±1.3" Red or Green 150		5.4288 425p
10x4x3" 198		6.5536MHz 200p
12x8x3" 215		
12x8x3" 265		
Liquid Crystal Display		
3 digit 875p; 4 digit 975p		
SWITCHES		
SLIDE 250V 1A DPDT C/OFF 15		
1A DPDT 14		
1A DPDT C/OFF 15		
4 pole on off 54		
1A DPDT 13		
pole 2-way 24		
PUSH BUTTON		
Spring loaded red button, Latching		
SPST on off 65		
SPDT C/over 75		
DPDT 6 tag 95		
MINIATURE		
Non Locking		
Push to make 15p		
Push to change cover momentary 85p		
ROCKER: 5A, 250V, SPST		
ROCKER: (white) 5A 250V SP change-over centre off 52p		
ROCKER: Lights red when on, Chrome Bezel, 3A 250V, DPST		
ROCKER: (white) 10A/250V DPST 85p		
ROTARY: "Make-A-Switch" Make your own multiway Switch as required. Shafting assembly has adjustable stop. Accommodates up to 6 Wafers		
Break before make Wafers, Silver contacts		

Enter the 80's with SAXON

£30 FREE!

Vouchers with our new catalogue over 200 items of disco systems, lighting and accessories. Send £1.00 now.

- EXAMPLES:**
- Fuzz lights **£26.75**
 - Projectors from **£55.50**
 - Strobes **£35-£220**
 - Rope lights 8 mtr **£59**
 - Disco stands **£29.75**
 - Echo chambers **£77.50**
 - 100W speaker **£29.50**
 - 10 way chaser **£399**
 - 100W twin horn bin **£125**
 - 800W spot bank **£55**

Mixers, mics, amplifiers, goose-necks, light units, bubble machines, mirror balls, helicopters, bins, consoles, and much more.

AND IF WE HAVEN'T GOT IT - WE'LL GET IT!

Full range of Pluto, D.J. Lightomat products in stock
Send £1 now for your catalogue - worth £30!!!

STEREO DISCO SYSTEMS WITH LIGHT SHOW & DISPLAY

STANDARD CENTAUR 100W

£299 inc. VAT + £19 carr. Deposit £84
12 mth + £25.50 or 24 mth + £14.93

SUPER CENTAUR 200W

£399 inc. VAT + £19 carr. Deposit £84.00
12 mth + £33.54 or 24 mth + £19.63

GXL 200W with PDF BINS (illus)

£489 inc. VAT + £19 carr. Deposit £102
12 mth + £40.77 or 24 mth + £29.73

CUSTOM CENTAUR

400/600W

with four PDF 100A Bins

£899 inc. VAT + £19 carr. Deposit £154
12 mth + £73.70 or 24 mth + £43.13

MINI DISCO 100W

MONO

£249 inc. VAT + £19 carr. Deposit £54
12 mth + £21.49 or 24 mth + £12.55

JUST PLUG IN AND GO!!

AP100 100W
4CH AMP £67.50
AP200 200W 6CH £119



- * Headphone monitor/cue light
- * Full mixing/crosstape
- * Tape & mic inputs
- * Top Quality
- * 4 channel soundlight

200 Watt £370 inc. carr. & VAT
* Twin 200W cabinets
* Six inputs—three channels

All systems complete with loudspeakers, leads, & 2 years warranty

20% DEPOSIT CREDIT TERMS

6 MONTHS INTEREST FREE CREDIT
PHONE FOR DETAILS

P.A. SYSTEMS
C/W LOUDSPEAKERS

100 WATT
£248 inc. carr. & VAT
Dep. £50
or 12 mth + £19.88
or 24 mth + £11.64

- * Four mixing inputs & master
- * Bass & treble controls
- * Sturdy construction
- * Twin Piezo cabinets

Dep. £74
12 mth + £29.72
12 mth + £17.39



SAXON ENTERTAINMENTS
333 WHITEHORSE ROAD
CROYDON
SURREY CR0 2HS
Tues-Sat 9am-5pm

ALL MAIL & CREDIT ENQUIRIES TO CROYDON TO ORDER
Send cheque/crossed POS or Telephone (01) 684 6385
Access/Barclaycard. Telephone orders accepted
For Credit Sales & Enquiries Ring
SUE ABEGG ON (01) 684 8007/0098

TRANSFORMERS + VAT 15%

30 VOLT RANGE
Pri 220/240 Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V.

Ref	Amps	Price	P & P
112	0.5	2.90	0.90
79	1.0	3.93	1.10
3	2.0	6.35	1.10
20	3.0	8.82	1.31
21	4.0	9.79	1.31
51	5.0	10.86	1.52
117	6.0	12.29	1.67
88	8.0	16.45	1.89
89	10.0	18.89	1.89
90	12.0	21.09	2.24
91	15.0	24.18	2.39
92	20.0	32.40	O.A.

50 VOLT RANGE
Pri 220/240V Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V or 25V-0-25V.

Ref	Amps	Price	P & P
102	0.5	3.75	0.90
103	1.0	4.87	1.10
104	2.0	7.88	1.31
105	3.0	9.42	1.52
106	4.0	12.82	1.73
107	6.0	16.37	1.89
118	8.0	22.29	2.39
119	10.0	27.48	O.A.
109	12.0	32.88	O.A.

MAINS ISOLATORS (SCREENED)
PM 120/240 Sec 120/240V CT

Ref	VA	Price	P & P
107	20	6.34	0.91
149	60	7.37	1.10
150	100	8.38	1.31
151	200	12.28	1.31
152	250	14.61	1.73
153	350	18.07	2.12
154	500	22.52	2.47
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	56.52	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

*Pri 0-220-240V Sec 115 or 240V. State sec. volts required.

CASED AUTO TRANSFORMERS

240V cable in 115V USA flat pin outlet.

VA	Price	P & P	Ref
20	6.85	1.03	56W
75	8.50	1.31	64W
150	11.00	1.31	4W
250	12.55	1.67	69W
500	20.13	1.89	67W
1000	30.67	2.65	84W
2000	44.97	O.A.	95W

CONTINUOUS RATINGS

All voltages given are at full load

60 VOLT RANGE

Pri 220/240V Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24-0-24V or 30-0-30V.

Ref	Amps	Price	P & P
124	0.5	4.27	1.10
126	1.0	6.50	1.10
127	2.0	8.36	1.31
125	3.0	12.10	1.31
123	4.0	13.77	2.12
40	5.0	17.42	1.89
120	6.0	19.87	2.12
121	8.0	27.92	O.A.
122	10.0	32.51	O.A.
189	12.0	37.47	O.A.

TRANSFORMERS

END OF LINE OFFERS

30-Isolator 240V:240V 200VA **£4.54** £1.04

M816 - 240V: Screen 1) 13-0-13 1A. 2) 12V 150ma **£1.50** 60p

M489 - 240V: 1400V • 150ma 6,3V • 4A. **£5.50** £1.04

M708 - 6K to 3KΩ matching transformer 5W **90p** 40p

M679 - 120V x 2: 36V 1.6A **£3.00** 78p

M865 - 100V Line to 4Q 10 watts **£1.90** 60p

M1020 - 0-240V 12-0-12V • 50ma **75p** 41p

M1126 - 120/240V: 9-0-9V • 1A **£1.75** 11p

M1165 - 0-115-240V: 14V 50ma **75p** 30p

NEW-ADCOLA professional soldering irons to BS3456

K1000 - 12 watt long life bit **£6.47** + p&p 60p + VAT

K2000 - 14 watt stainless steel shim **£5.72** + p&p 60p + VAT

Antex Soldering Irons 15W, 25W **£4.58**

Safety Stand **£1.75** P & P 52p each

Metal Oxide Resistors 1/2W 5% TR4 (Electrosil)

390Ω/470Ω/510Ω/560Ω/820Ω/1K/1K1/1K2

1K6/1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/

100K/110K/120K/130K/180K/200K/220K/270K/300K

£1.50/100 30p P.&P. +VAT in 100s only.

12 OR 24V OR 12-0-12V

Pri 220-240 volts

Ref	12V	24V	Price	P & P
111	0.5	0.25	2.42	0.52
213	1.0	0.5	2.90	0.90
71	2	1	3.86	0.90
18	4	2	4.46	1.10
85	5	2.5	6.16	1.10
70	6	3	6.99	1.10
108	8	4	8.16	1.31
72	10	5	8.93	1.31
116	12	6	9.85	1.52
17	16	8	11.79	1.52
115	20	10	15.38	2.39
187	30	15	19.72	2.39
226	60	30	40.41	O.A.

Bridge Rectifier

100V 2.5A **£2.40**

200V 4A **46**

200V 4M **66**

400V 4A **1.85**

500V PM7A6 12A **£1.25**

P & P 17p VAT 15%

20,000 ohm V Multimeter

mirror. Scale ranges AC/DC to 1000V DC current to 250ma.

Resistance to 3 M Ohms

5"x3 1/2"x1 1/2" **£14.36** P.&P.

£1.00, VAT 15%.

AUTO TRANSFORMERS

Voltage for step up or step down

Ref	VA	(Watts)	£	P&P
113	15	0-115-210-240	2.73	0.81
34	75	0-115-210-240	4.41	1.10
4	150	0-115-200-220-240	5.70	1.10
67	500	0-115-200-220-240	12.09	1.91
84	1000	0-115-200-220-240	20.64	2.39
93	1500	0-115-200-220-240	25.41	O.A.
95	2000	0-115-200-220-240	30.31	O.A.
73	3000	0-115-200-220-240	65.13	O.A.
80S	4000	0-10-115-200-220-240	84.55	O.A.
57S	5000	0-10-115-200-220-240	98.46	O.A.

AVO TEST METERS

AVO 8 MK5 **£100.50**

AVO 71 **£40.80**

AVO 73 **£55.40**

AVO MM5 minor **£35.95**

AVO Wee Megger **£82.20**

AVO TT169 in circuit transistor tester **£42.60**

AVO EM272 316K - Volts **£63.40**

AVO DA116 digital **£110.90**

AVO Bliv7 Megger **£55.10**

AVO clamp meter to 300A **£59.40**

All Avos Meggers and accessories available

P & P £1 32 15% VAT

U4315 Budget Meter

20Kv/Ω Ranges to 1000V, 2.5A AC/DC

500K Res. In steel case **£15.85** P & P £1.32

SPECIAL OFFER Multimeter (20KΩ/Ω/V with

combined audio/L.F. test oscillator at 1KHz,

and 465 KHz. AC/DC to 1000 volts DC

current to 500 MA resistance to 1Ω size

160x97x40mm **£8.50**, P & P £1.00, VAT 15%

Split Bobbin Type - 0-12-15-20-24-30V.

Ref 009 - 1 Amp **£2.98**, P. & P. £1.10.

Ref 010 - 2 Amp **£4.65**, P. & P. £1.10 open

frame fixing. Other types available.

£4.50 P & P 66p + VAT

"Educational" Meters (Moving coil)

0-10A, 0-1A, 0-2A, 0-15V, 0-30V.

Free standing large scale easily read meters

with top screw terminals for quick connections.

£4.50 P & P 66p + VAT

PANEL METERS

43mm x 43mm 82mm x 78mm

0-50mA 6.20 0-50µA 6.70

0-500µA 5.95 0-500V/A 6.70

0-1mA 5.95 0-1mA 6.70

0-30V 5.95 0-30V 6.70

VU ind. Panel 48mm x 45mm or

40mm x 40mm 250µA f.s.d.

SV041 Edge VU centre

zero f.s.d. **£2.80**

Carriage 76p. VAT 15%

1 Send 20p stamp for catalogue

Prices correct 31/1/80

CONNECTORS

Thorn, Cannon, Plessey, Bendix,

Greepar, available on request.

W/V Resistors 2.5W, 6W,

10W, 12W, available on

request.

P.W., Purbeck oscilloscope

transformer 250-0-250V

6.9V:12.9V **£8.42**, P.&P. £1.04..

NEW RANGE TRANSFORMERS

2 windings - 0-36V-48V/36V-0-36V

0-48V 72V or 96V.

Amps

PLUME COMPONENTS LOW PRICES

Also our micro chips are at micro prices. Don't be fooled by low prices. We do not offer for sale, surplus, sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of p&p and VAT - please refer to "Ordering Information" before ordering. Official orders from Schools, Colleges, Universities and Gov. Authorities annotated.

DTL		MEMORIES		SHIFT REGISTERS	
930	65p	4041	89p	3341 PCIF0 700KHZ	495p
937	65p	4042	75p	3341 PC FIF0 1MHz	550p
944	65p	4043	85p	3342 PC 64 bit shift reg	495p
947	65p	4044	88p	3347 PC 80 bit shift reg	495p
956	65p	4045	100p		
967	65p	4047	89p		
967	65p	4048	59p		
967	65p	4049	38p		
9099	90p	4050	40p		
		4051	89p		
		4052	75p		
		4053	111p		
		4055	121p		
		4056	121p		
		4059	560p		
		4060	112p		
		4063	112p		
		4066	56p		
		4067	422p		
		4068	118p		
		4069	18p		
		4070	28p		
		4071	25p		
		4072	15p		
		4073	25p		
		4075	20p		
		4076	88p		
		4077	23p		
		4078	32p		
		4081	25p		
		4082	25p		
		4085	88p		
		4086	130p		
		4093	15p		
		4094	225p		
		4095	99p		
		4096	65p		
		4098	110p		
		4099	180p		
		4501	25p		
		4502	112p		
		4503	180p		
		4507	52p		
		4508	285p		
		4510	78p		
		4511	125p		
		4512	75p		
		4514	250p		
		4515	200p		
		4516	109p		
		4518	99p		
		4520	32p		
		4521	230p		
		4526	105p		
		4527	130p		
		4528	89p		
		4529	140p		
		4531	160p		
		4532	125p		
		4538	150p		
		4539	180p		
		4556	70p		
		4559	240p		
		4572	46p		
		4584	79p		
		4585	125p		
		4586	30p		
		4590	40p		
		4592	40p		
		74C20	30p		
		74C85	145p		
		74C97	125p		
		74C98	125p		
		74C107	100p		
		74C160	110p		
		74C162	145p		
		74C163	145p		
		74C192	175p		
		74C194	175p		
		74C195	175p		
		74C903	45p		

7400		EPROMS		DIP SWITCHES	
7400	11p	1702A	450p	4 pole	89p
7401	12p	2708 450 NS	425p	6 pole	115p
7402	13p	2716 5V 450 NS	1095p	8 pole	140p
7404	13p	2532 32K 450 NS	£39.95	10 pole	175p
7405	17p				
7409	18p				
7410	18p				
7412	18p				
7513	28p				
7420	18p				
7430	18p				
7432	25p				
7440	18p				
7442	68p				
7448	75p				
7473	32p				
7475	40p				
7476	40p				
7490	35p				
7492	50p				
7493	50p				
7496	45p				
74121	35p				
74123	45p				
74124	45p				
74127	58p				
74122	45p				
74125	50p				
74195	100p				
74196	100p				
74283	140p				
74290	120p				
74365	90p				
74366	90p				

74LS		CPU'S		KEYBOARD ENCODER	
74LS00	18p	6502	795p	AY-5-2376	795p
74LS01	12p	6504	795p		
74LS04	15p	6505	795p		
74LS08	20p	6800	695p		
74LS10	18p	8802	895p		
74LS11	30p	8080A	525p		
74LS12	30p	8085A	1095p		
74LS14	80p	280	785p		
74LS15	38p	280A	785p		
74LS20	18p	2801	12500p		
74LS30	18p	2802	9000p		
74LS32	25p	WD3000B	18900p		
74LS40	25p	28000DA	£10.99		
74LS42	58p				
74LS47	78p				
74LS48	85p				
74LS49	85p				
74LS73	30p				
74LS74	30p				
74LS75	38p				
74LS86	30p				
74LS90	40p				
74LS107	40p				
74LS123	80p				
74LS125	50p				
74LS132	78p				
74LS138	68p				
74LS151	75p				
74LS155	75p				
74LS161	78p				
74LS163	90p				
74LS164	90p				
74LS168	100p				
74LS174	80p				
74LS175	80p				
74LS195	87p				
74LS221	110p				
74LS244	275p				
74LS245	295p				
74LS251	120p				
74LS252	110p				
74LS290	80p				
74LS293	120p				
74LS366	75p				
74LS373	170p				
74LS374	170p				
74LS375	140p				
74LS377	180p				
74LS393	135p				
74LS490	140p				
74LS670	280p				

74LS		INTERFACE LINEAR		LED BAR GRAPH AND ANALOG METER DRIVER	
74LS107	40p	DM8123	125p		
74LS123	80p	75150	125p		
74LS125	50p	75154	125p		
74LS132	78p	75182	180p		
74LS138	68p	75322	250p		
74LS151	75p	75334	328p		
74LS155	75p	75325	328p		
74LS161	78p	75361	350p		
74LS163	90p	75365	285p		
74LS164	90p	75461	50p		
74LS168	100p	75481/2	75p		
74LS174	80p	8728	175p		
74LS175	80p	8795	175p		
74LS195	87p	8797	175p		
74LS221	110p	LEDS	45p		
74LS244	275p	TIL209	9p		
74LS245	295p	TIL211	13p		
74LS251	120p	TIL212	15p		
74LS252	110p	TIL220	12p		
74LS290	80p	TIL222	15p		
74LS293	120p	TIL224	18p		
74LS366	75p	DISPLAYS			
74LS373	170p	FND510	80p		
74LS374	170p	FND527	125p		
74LS375	140p	DL704	85p		
74LS377	180p	DL707	85p		
74LS393	135p	MV5164	225p		
74LS490	140p				
74LS670	280p				

CMOS		LED BAR GRAPH AND ANALOG METER DRIVER	
4001	18p		
4002	18p		
4006	75p		
4007	18p		
4009	35p		
4010	35p		
4011	24p		
4012	24p		
4013	38p		
4014	70p		
4015	75p		
4016	35p		
4017	75p		
4018	78p		
4019	42p		
4020	88p		
4021	100p		
4022	88p		
4023	22p		
4024	50p		
4025	20p		
4026	130p		
4027	45p		
4028	75p		
4029	80p		
4030	50p		
4031	185p		
4033	145p		
4035	105p		
4036	205p		
4038	110p		
4039	280p		

INTERLS CHIPS ARE DOWN		LIQUID CRYSTAL DISPLAY	
4030	50p		
4031	185p		
4033	145p		
4035	105p		
4036	205p		
4038	110p		
4039	280p		

INTERLS CHIPS ARE DOWN		LIQUID CRYSTAL DISPLAY	
4030	50p		
4031	185p		
4033	145p		
4035	105p		
4036	205p		
4038	110p		
4039	280p		

D.I.Y. KITS FOR SYNTHESISERS, SOUND EFFECTS



BASIC COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits PCBs and parts are shown in our lists.

LAYOUT DIAGRAMS are supplied free with all PCBs unless "as published".

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

P.E. MINISONIC MK2 SYNTHESISER

A portable mains operated miniature sound synthesiser with keyboard circuits. Although having slightly fewer facilities than the large Formant and P.E. synthesisers the functions offered by this design give it great scope and versatility.

Set of basic component kits (excl. KBD R's & tuning pots - see list for options available) and PCBs (incl. layout charts)
KIT 38-25 **£80.12**
"Sound Design" booklet **£1.00**

P.E. 128-NOTE SEQUENCER

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable.

Set of basic comps, PCBs and charts
KIT 76-7 **£35.56**
Set of text photocopies **£1.36**

P.E. 16-NOTE SEQUENCER

Sequences of up to 16 notes may be programmed by the use of external panel controls and fed into most voltage controlled synthesisers.

Set of basic comps, PCBs and charts
KIT 86-5 **£33.60**
Set text photocopies **£1.84**

P.E. STRING ENSEMBLE

A multivoiced polyphonic string instrument synthesiser. Set of basic comps, PCBs & charts

KIT 77-8 **£107.66**

ELEKTOR ELECTRONIC PIANO

A touch-sensitive multiple-voicing piano using the latest integrated circuit techniques for the keying and envelope shaping, and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos.

5-octave set of basic comps and PCBs (as publ.)
KIT 80-9 **£146.66**
Additional 3-octave extension and basic parts and PCBs (as published)
KIT 80-10 **£56.36**
Set of text photocopies **£1.81**

ELEKTOR FORMANT SYNTHESISER

A very sophisticated synthesiser for the advanced constructor who puts performance before price.

Set of basic comps, PCBs (as publ.)
KIT 66-14 **£252.45**
Set of text photocopies **£7.83**

ELEKTOR DIGITAL REVERB UNIT

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring lines. The basic delay range of 24 to 90ms can be extended up to 450ms using the extension unit. Further delays can be obtained using more extensions.

Main unit basic comps and PCB (as publ.)
KIT 78-3 **£55.40**
Extension unit basic comps and PCB (as publ.)
KIT 78-4 **£58.77**
Text photocopy **86p**

ELEKTOR ANALOGUE REVERB

Using i.c.s instead of spring-lines the main unit has a maximum delay of up to 100ms, and the additional set extends this up to 200ms. May be used in either mono or stereo mode.

Main unit basic component set
KIT 83-1 **£29.49**
Additional delay basic components
KIT 83-2 **£20.07**
PCB (as publ.) to hold both kits
PCB9973 **£4.52**
Text photocopy **67p**

ELEKTOR RING MODULATOR

Compatible with the Formant & most other synthesisers. Set of basic comps & PCB (as publ.)

KIT 87-2 **£6.84**
Text photocopy **38p**

NEW KITS

ELEKTOR CHOROSYNTH

A 2½-octave Chorus synthesiser with an amazing variety of sounds ranging from violin to cello and flute to clarinet amongst many others. Experienced constructors can readily extend the octave coverage.

Basic comps, PCBs and charts but excl. sw's
KIT 100B **£44.39**
Text photocopy **70p**

ELEKTOR SEWAR

For use with Elektor Analogue Reverb to give greater flexibility to the reverb effects.

Basic comps, PCB (as publ.)
KIT 101-1 **£22.53**
Text photocopy **60p**

ELEKTOR FUNNY TALKER

Incorporates a ring modulator, chopper & frequency modulator to produce fascinating sounds when used with speech & music signals.

Basic comps, PCB (as publ.)
KIT 99-1 **£9.60**
Text photocopy **40p**

ELEKTOR FREQUENCY DOUBLER

For use with guitars & other electronic instruments to produce an output one octave higher than the input. Inputs and outputs may be mixed to give greater depth.

Basic comps, PCB (as publ.)
KIT 98-1 **£5.48**
Text photocopy **20p**

P.E. SPLIT-PHASE TREMOLO

A simple but effective substitute for a rotary cabinet. The output of an internal generator is phase-split and modulated by an input signal from an electronic guitar or other instrument. Output amplitudes, depth & rate are variable. May be fed to one or two amplifiers.

Basic comps, PCB & chart
KIT 102-3 **£17.58**
Text photocopy **65p**

P.E. MINISONIC WAVEFORM CONVERTER

A simple converter that modifies the Minisonic sawtooth waveform to produce triangle and sine outputs. Ideally one should be used with each Minisonic VCO.

Basic comps, PCB & chart
KIT 96-1 **£3.98**

DISCO-CROSS FADER

The cross-fade between 2 decks is switch-initiated and can be preset on the panel for a cross fade rate of between about ½ sec & 24 secs. Basically a stereo unit but may be used in mono.

Basic comps, PCB & chart
KIT 94-1 **£11.83**

P.E. GUITAR MULTIPROCESSOR

An extremely versatile sound processing unit capable of producing, for example, flanging, vibrato, reverb, fuzz and tremolo as well as other fascinating sounds. May be used with most electronic instruments.

Set of basic comps, PCBs & charts
KIT 85-5 **£54.66**
Set of text photocopies **£2.52**

P.E. PHASER

An automatically controlled 6-stage phasing unit with integral oscillator.

Basic components, PCB & chart
KIT 88-1 **£10.69**
2-Notch extension, PCB & chart
KIT 88-2 **£6.36**
Text photocopy **68p**

ELEKTOR PHASING & VIBRATO

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 2-input mixer stage.

Set of basic comps, PCB & chart
KIT 70-2 **£21.67**
Text photocopy **67p**

ELEKTOR RESONANCE FILTER

Allows a synthesiser to produce a more realistic simulation of natural musical instruments.

Set of basic comps, & PCB (as publ.)
KIT 82-2 **£22.45**
Text photocopy **57p**

P.E. GUITAR EFFECTS UNIT

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls.

Basic comps, PCB & chart
KIT 42-3 **£10.37**
Text photocopy **28p**

P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit incl. variable controls affecting the fuzz quality whilst retaining attack and decay, and also providing filtering. Usable with most electronic instruments.

Basic components, PCB & chart
KIT 56-3 **£11.82**
Text photocopy **68p**

P.E. SMOOTH FUZZ

Basic components, PCB & chart
KIT 91-1 **£6.40**
Text photocopy **55p**

TREMOLO UNIT

A slightly modified version of the simple P.E. unit.
Basic components, PCB & chart
KIT 54-1 **£3.74**

GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit.
Basic components, PCB & chart
KIT 74-1 **£5.19**
Text photocopy **39p**

P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration.
Basic components, PCB & chart
KIT 75-1 **£6.73**
Text photocopy **38p**

P.E. WAH-WAH UNIT

Can be controlled manually or by integral automatic control.
Basic components, PCB & chart
KIT 51-1 **£4.93**

P.E. AUTO-WAH UNIT

Automatically gives Wah or Swell sounds with each note played.
Basic components, PCB & chart
KIT 58-1 **£9.68**
Text photocopy **58p**

ELEKTOR WAVEFORM CONVERTER

Converts a saw-tooth waveform into sinewave, mark-space sawtooth, regular triangle, or square-wave with variable mark-space.
Basic comps, PCB & chart, but excl. sw's
KIT 67-1 **£9.24**

P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses.
Basic components, PCB & chart
KIT 89-1 **£4.34**
Text photocopy **78p**

P.E. TREBLE BOOST UNIT

A simple treble boost unit with manual control depth.
Basic components, PCB & chart
KIT 53-1 **£2.92**

P.E. SYNTHESISER

The well acclaimed and highly versatile large scale mains operated synthesiser. Other circuits in our lists may be used with it to good advantage.

Basic comps, PCBs & charts
KIT 23-33 **£167.67**
Set of text photocopies **£8.21**

10% DISCOUNT VOUCHER (PE 83)

TERMS: Goods in current adverts & lists over £50 goods value (excl P&P & VAT). Correctly coded, C.V.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of P.E. Does not apply to credit card orders.

ADD: POST & HANDLING

U.K. orders: Keyboards add £2.70 each. Other goods: Under £1 add 35p, under £20 add 75p, over £20 add £1. Recommended insurance against postal mishaps: add 50p for cover up to £50, £1 for £100 cover, etc., pro-rata. Insurance must be added for credit card orders. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

ADD 15% VAT

(or current rate if changed). Must be added to full total of kits, discount post & handling on all U.K. orders. Does not apply to Exports, or photocopies.

EXPORT ORDERS ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list - Europe send 35p, other countries send 75p. Note that we do not offer a C.O.D. service and that our terms are payment in advance.

PHONOSONICS · DEPT PE83 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL 01-302 6184)

AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list Europe—send 35p; other countries—send 75p.



KIMBER-ALLEN KEYBOARDS AND CONTACTS

KIMBER-ALLEN KEYBOARDS as required for many published projects. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

3 Octave (37 notes) £25.50 4 Octave (49 notes) £32.25 5 Octave (61 notes) £39.75

CONTACT ASSEMBLIES (gold-clad wire) — 1 required for each KBD note:

Type GJ — SPCO 33p ea. Type GA — 1 pr of contacts, normally open 33p ea. Type GB — 2 pr N/O 37 1/2p ea. Type 4PS — 3 pr N/O plus SPCO 78p ea.

P.E. V.C.F.

A voltage controlled filter extracted from P.E. Minisonic project.

Basic comps, PCB & chart KIT 65-1 £8.45

P.E. RING MODULATOR

Extracted from P.E. Minisonic project.

Basic comps, PCB & chart KIT 69-1 £6.35

WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit.

Basic comps, PCB & chart KIT 28-1 £4.84

Text photocopy 28p

P.E. ENVELOPE SHAPER WITHOUT VCA

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing VCA.

Basic comps, PCB & chart KIT 44-1 £5.73

Text photocopy 49p

P.E. ENVELOPE SHAPER WITH VCA

Has an integral Voltage Controlled Amplifier, and has full manual control over the A.D.S.R. functions.

Basic comps, PCB & chart KIT 50-1 £8.03

Text photocopy 58p

P.E. TRANSIENT GENERATOR

An ADSR envelope shaper without VCA, and additionally providing Repeat-triggering enabling a synthesiser to be programmed for mandolin or banjo effects.

Basic comps, PCB & chart KIT 63-2 £7.62

Text photocopy 58p

P.E. EXTERNAL-INPUT SYNTHESISER-INTERFACE

Allows external inputs such as guitars, microphone etc., to be processed by synthesiser circuits.

Basic comps, PCB & chart KIT 81-1 £3.90

P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments.

Set of basic components, incl. power supply, PCBs & charts KIT 46-3 £23.32

Text photocopy 97p

P.E. TUNING INDICATOR

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of KIT 46 is not required.

Basic components, PCB & chart, but excl. sw. KIT 69-1 £8.19

Text photocopy 58p

P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels.

Basic comps, PCB & chart KIT 62-1 £5.31

P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 4-digit counter for 1Hz to 99kHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking.

Basic components, PCB & chart KIT 79-4 £31.35

Text photocopy 78p

P.E. 6-CHANNEL MIXER

A high specification stereo mixer with variable input impedances.

Basic components, (excl. sw's.) and set of PCBs and charts. KIT 90-8 £61.25

Extra 2-channel set with PCB KIT 90-9 £11.62

Set of Text photocopies £1.50

STEREO HEADPHONE AMPLIFIER

Extracted from P.E. 6-channel mixer.

Basic components, PCB & chart KIT 92-1 £5.68

DIGITAL EXPOSURE UNIT

Controls up to 750 watts in 1/2 second steps up to 10 minutes, with built-in audio alarm.

Basic components, PCBs & charts KIT 93-3 £23.27

Text photocopy £1.20

P.E. DISCOSTROBE

A 4-channel light show controller giving a choice of sequential, random, or full strobe mode of operation, and with extra audio input.

Basic components, PCB & chart KIT 57-2 £25.12

Text photocopy 78p

RHYTHM GENERATORS

Several available, including programmable 16 beat 64000 pattern, 128 beat almost infinite pattern, and pre-programmed 15 pattern using either M252 or M253 rhythm chips. A selection of effects instrument circuits is also available.

P.E. VOICE OPERATED FADER

For automatically reducing music volume during talkover — particularly useful for discos.

Basic components, PCB & chart KIT 30-1 £4.37

Text photocopy 28p

P.E. DYNAMIC NOISE LIMITER

Very effective stereo circuit for reducing the hiss found in most tape recordings.

Basic components, PCB & chart KIT 97-1 £8.07

Text photocopy 75p



PRICES ARE CORRECT AT TIME OF PRESS.
E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

PHONOSONICS

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics — now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, T.V. Electronics Technicians
Radio Amateurs
Electrical Installation Work

Diploma Courses

Colour T.V. Servicing
CCTV Engineering
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE
BOOK

Post this coupon or 'phone today for free Electronics careers guide.

Name _____

Address _____

Age _____

ICS

To ICS, Dept. X273, Intertext House,
London SW8 4UJ
or telephone 01-622 9911 (all hours)

DorAm

a de boer company

Buying one of our PROJECT PACKS will save you the frustration of tracking down those evasive components that hold up the completion of your project. Our packs include Printed Circuit Board, all the components listed in the article together with sockets and solder. Cases, knobs etc can be supplied as extra items if required. Ask for more information . . .



- **Battery protection (80109).** Forgetting to turn off the headlights need no longer be a motorist's nightmare. This project is designed to monitor the battery voltage and switch off the lights automatically in all kinds of motor vehicles. **£5.15**
- **Transistor ignition (80084).** A system which combines the most significant advantages of other systems including the conventional system! **£20.45**
- **A dip-stick probe (80102).** There are all kinds of indicators and warning lights in modern cars, but an oil temperature indicator is rarely included. The easiest way to add this type of indicator to an existing car is to mount a temperature sensor in the dip-stick. **£3.65**
Project without dip-stick **£11.00**
Dip-stick with indicator (short) **£11.45**
Dip-stick with indicator (long)
- **Intelligent wiper delay (80086).** This wiper delay only needs to be told once what is required of it. It will then carry out your orders until you change them, which you can at any time, instantly. **£15.85**
- **Active car aerial (80018-1+2).** If there is one place to use a good aerial it is in a car. **£13.85**
- **Stop thief! (80097).** There are all sorts of systems for protecting cars, but this one is unusual: it is deception, rather than protection . . . **£4.20**
- **Battery voltage indicator (80101).** Only a few components are needed to obtain an optional indication of the battery condition: a single lamp that changes colour as the battery goes into the danger area. **£6.85**
- **Fuel consumption meter (80096).** This unit gives instant indication of your present fuel consumption in miles per gallon. Project without transducers! Ask for information and price of transducers. **£45.10**



HOW TO ORDER

Send a cheque or postal order to Doram Electronics Ltd, Fitzroy House, Market Place, Swaffham, Norfolk PE37 7QH. All prices INCLUDE VAT, please add 40p for postage and packing. 24 Hour Answering Service available for ACCESS orders.

Telephone: Swaffham (0760) 21627. Telex 817912 Doram G.

a de boer
company

J. BIRKETT

(Partners: J. H. Birkett, J. L. Birkett)
Radio Component Suppliers
25 The Strait, Lincoln. LN2 1JF

- 10 WATT STUD MOUNTING ZENERS** 4.7, 6.8, 7.5, 8.2, 12, 15, 18, 20, 24, 27, 30, 33, 36, 39, 43, 47, 51, 62, 68, 75, 82, 91, 100, 120, 130, 150, 180, 200 Volt All at 50p each.
- 5 WATT PLASTIC ZENER DIODES** Wire Ended 3.6, 4.3, 5.6, 6, 6.2, 7.5, 8.2, 9, 10, 11, 13, 14, 15, 16, 17, 18, 19, 20, 22, 27, 36, 39, 40, 47, 51, 56, 60, 62, 68, 87 Volt All at 30p each.
- 1 WATT ZENERS** 3.6, 5.6, 6.8, 8.2, 9.1, 11, 12, 13, 15, 16, 20, 22, 27, 30, 36, 56, 62, 91, 110, 120, 130, 150, 160, 180, 200 Volt. All at 15p each.
- LM 7542 DUAL CORE MEMORY SENSE AMPLIFIER** at 50p.
P4001 @ 50p, N82238 @ 50p, AM931159C @ £1.50, C1702A @ £3.50, MC 846 @ 30p, IM5600CP @ £1, MC 2007F @ 50p, 2516N @ £1.15, SN15836 @ 30p, SN15846 @ 30p, 4102 @ £1.50, N8875A @ 50p, SN74154 @ 60p, AM250559C @ £2, 6300DJ @ 50p, 5603C @ £1.15, MC1414 @ 60p.
- MIDGET 6 To 12 VOLT SINGLE POLE CHANGE OVER RELAY** 5 amp Contacts @ 60p.
- SUB-MINIATURE SPCO TOGGLE SWITCHES** @ 50p each.
- BECKMAN 3 DIGIT 7 SEGMENT GAS DISCHARGE ORANGE DISPLAYS** Type SP 353 @ £1.95.
- 9 VOLT ITRON 9 DIGIT SEVEN SEGMENT DISPLAY** Type FG 95A @ £1.80.
- SPECIAL 5 NPN DARLINGTON PAIRS** in 14 PIN DIL Package HFE 5000 10 volt 500mA with connections @ 50p.
- PAPER CAPACITORS** 10uf 370 Volt A.C.W. $5\frac{1}{2} \times 2\frac{1}{2} \times 1\frac{1}{2}$ @ £1.50.
- STUDMOUNTING DIODES** 100 PIV 10 amp @ 15p, 100 PIV 30 amp @ 25p.
- 50. BC 107-8-9 TRANSISTORS** Assorted untested @ 60p.
- 50. MULLARD C280 CAPACITORS** assorted for 60p.
- 10 ASSORTED PUSH BUTTON ASSEMBLIES** less knobs @ £1.30.
- THYRISTORS (S.C.R.'s)** 10 amp Type 100 PIV @ 28p, 400 PIV @ 55p, 800 PIV @ 65p.
- MINIATURE TRANSISTOR TRANSFORMERS** Input Types Impedance Ratio. 100K To 1K @ 35p, Ratio 150K To 1K @ 35p, Ratio 20K To 1K @ 35p, Driver Type 10K To 2K @ 35p, Output types 250mW 1.2K To 8 ohm @ 35p, 250mW 500 ohm To 8 ohm @ 35p, 500mW 400 ohm To 8 ohm @ 35p.
- WIRE ENDED RF CHOKES** 30 uH at 25 for 50p.
- OP-TO ISOLATORS** IL-74 with data at 50p.
- CLOSE TOLERANCE CAPACITORS** 1288pf, 1670pf, 5979pf, 19689pf All 1% 125v.w., at 5p each, .01uf 2%, .11uf 2% @ 8p, .1uf 1% at 12p.
- VALVE HOLDERS** b7G, b9A Both 10p, Ceramic B9D @ 15p.
- QUAD COMPARATOR LM 339** with data @ 50p, OP-AMPS MC 1439G @ 3 for £1.
- 50. OC 71 TRANSISTORS** untested for 75p.
- 20 PHOTO TRANSISTORS AND DARLINGTONS** assorted Untested @ £1.
- NKT 274 or NKT 214 TRANSISTORS** PNP @ 10p, 6 for 50p.
- TTL I.C.'s** 7400, 7410, 74L00, 7453, 7430 All @ 6 for 50p.
- MINIATURE MULTI-TURN 5K LIN POTENTIOMETER** at 30p.
- MINIATURE SINGLE TURN POTENTIOMETERS** Short Spindle 250K Lin 1 Meg Lin Both 4 for 50p.
- MAINS TRANSFORMERS** 240 Volt Input, 24 Volt Tapped at 14 volt 1 amp @ £1.30 (P&P 25p), Type 2, 30-0-30 Volt 500mA @ £1.30 (P&P 25p).
- WIRE POTENTIOMETERS** 2 watts 2K, 5K, 10K, 4 watt 100k All 30p each.

Please add 20p for post and packing on U.K. orders under £2.
Overseas postage orders at cost.

ELECTROVALUE

FOR COMPONENTS THAT COUNT



SIEMENS
SEMI-CONDUCTOR
CAPACITORS
FERRITES

NASCOM
MICRO COMPUTERS
AND
ANCILLARIES

VERO
BOARDS
CASES &
KITS

ISKRA
RESISTORS

RADIOHM
POTENTIOMETERS

BREADBOARDS
SOLDER TOOLS

OPTO-ELECTRONICS

SWITCHES CATALOGUE 10

GOOD DISCOUNTS AND FREE POSTAGE ON SUBSTANTIAL C.W.O. U.K. ORDERS
COMPUTER-CONTROLLED SERVICE AIDS PROMPT DELIVERY
128-PAGE CATALOGUE FREE FOR THE ASKING

ELECTROVALUE LTD., (PEB), 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB. (Phone: 33603 (London 87) STD 0784. Telex 264475.

NORTHERN BRANCH (Personal Shoppers Only): 680 Burnage Lane, Burnage, Manchester M19 1NA. (Phone (061) 432 4945.


The Acorn modular system

A range and price unmatched by any other manufacturer in the world.
Designed and produced in Britain.

For the absolute beginner...

System One

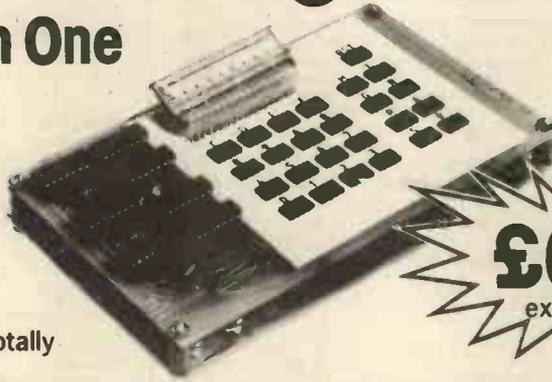A compact stand-alone microcomputer based on standard Eurocard modules, and employing the highly popular 6502 MPU (as used in APPLE, PET, KIM, etc). Throughout, the design philosophy has been to provide full expandability, versatility and economy. Many thousands have already been sold throughout the world.



£65 in kit form
excluding VAT

System One is complemented by a range of totally compatible eurocards including:

● 8K+8K Static RAM and EPROM	£95	● Laboratory Interface (isolated inputs, high current outputs)	£122
● Colour Prestel Compatible VDU Interface	£88	● 6809 CPU Card	£98
● Versatile (serial, parallel, RS232 etc) Interface	£69	● Professional Keyboard (parallel ASCII encoded)	£96
● Dual Mini-floppy Controller	£45	● AIM 65 Bus Interface adaptor	£33
● PROM/EPROM Programmer (Bipolar and UV erasable)	£55	● PAL Encoder	£22.50
● A to D, and D to A Interface (12 bit, high speed)	£132		
● Printer Interface (for 12 data 3 strobe)	£60		

All prices exclude VAT

Available soon:


- 80 x 24 character VDU Interface
- 32K Dynamic RAM Card
- 5V/12V Switched mode power supply (1" deep)
- In circuit emulator (block relocating)

- IEEE Bus Interface (Full implementation)
- Real time clock with CMOS RAM

All these cards utilise 'state of the art' devices and represent an elegant and long lasting solution to today's requirements.

...and the absolute professional

System Three

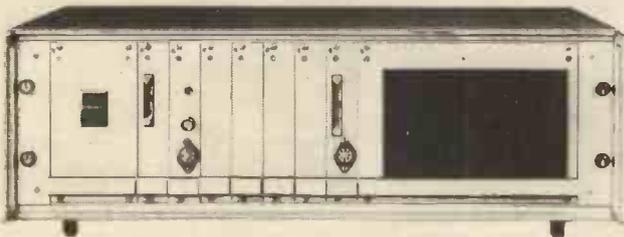

System 3, contains the 6502 CPU, 16K RAM with DOS and BASIC, VDU Interface, Disc controller and 5" drive, Printer Interface, backplane and power supplies. The entire unit costs about £1,000 and can be added to or reformatted as required.

If you need the facilities of the 6809 processor this can be substituted for the 6502 CPU (all other hardware remains unchanged.)

Acorn's fast BASIC combined with what is probably the most efficient disc operating system available may be linked with a control oriented ONLI BASIC addition for laboratory control, or an accounts/stock control package for small businesses.

A twin disc System Four is available if two drives and several peripheral interfaces are required in one case. Full service and software facilities available.

For more information and order form ring or write to



Acorn Computer Limited,
4a Market Hill,
Cambridge, CB2 3NJ
Cambridge (0223) 312772

Please send me further information of Acorn products.

My application concerns

Name

Address

Telephone

Acorn Computer Limited, 4a Market Hill, Cambridge, Cambs. Cambridge (0233) 312772

PE/8/80

Marshall's

A. Marshall (London) Ltd., Kingsgate House,
Kingsgate Place, London NW6 4TA
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582
Also retail shops: 325 Edgware Road, London W2.
40 Cricklewood Broadway, London NW2. 85 West Regent St., Glasgow.
108A Stokes Croft, Bristol.

Build the P.E./Marshall's Teletext Project and convert your standard colour television receiver to receive Teletext and Oracle. We can supply either a complete kit of parts at £200 inclusive of VAT/postage & packing, alternatively kits of parts for the various sub assembly as follows:

- | | | |
|--|--------|------------------------------|
| 1. Transmitter | £19.00 | |
| 2. Receiver | £13.00 | |
| 3. Decoder (supplied as a complete unit) | £87.00 | All prices inclusive of VAT, |
| 4. Summer Board | £27.00 | postage & packing. |
| 5. Tuner | £60.00 | |
| 6. Power Supply | £16.00 | |
| 7. Hardware and other parts | £ 9.00 | |

We accept American Express: Access: Barclay Card: Diners Card: also our own Marshall's Credit Charge.
Phone your order now to Margaret O'Donnell on 01-624 0805

Get a great deal from
Marshall's

CT4000 CLOCK/APPLIANCE TIMER KIT

The CT4000 has been designed to preset the state (on or off) of four outputs at four times per day for up to 7 days in advance, enabling the unit to control tape recorders, appliances, central heating, lights, etc. The times are set on a 0.1" high red LED display by means of a keyboard and the output states are displayed on four LEDs. Each output can switch up to 20mA at 9V. For mains loads use our Solid State Relay Kit (MK2). The kit includes a PCB, keyswitches, I.C., 4 digit LED display, transformer, plus all other components and a screen printed and drilled box which can also accommodate up to 4 Solid State Relay Kits.



Size: 10x12x4.5 cms
Colour: Black

£25.25

NEW

D.V.M. THERMOMETER KIT

Based on the ICL7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery).

£20.75

TOUCH CONTROL LIGHTING KITS

These KITS replace light switches and control up to 300 Watts of lighting. No rewiring, fit plaster depth boxes, insulated touchplates. Easy to follow instructions.

TD300K TOUCHDIMMER. Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamps. Neon lamp helps find the switch in the dark. £8.50
TDE/K Extension kit for TD300K for 2-way switching, etc. £1.50

TS300K TOUCHSWITCH & DIMMER. Single touchplate, small knob controls brightness. £5.50

TS4300K TIME DELAY TOUCHSWITCH. Turns off after preset delay (2 secs. to 3 1/2 mins.) £4.30

LD300K. Conventional light dimmer £2.90

INTEGRATED CIRCUITS

- | | |
|--|-------|
| 555 Timer | 21p |
| 741 Op. Amp. | 19p |
| AY-5-1224 Clock | £2.60 |
| AY-5-1230/2 Clock/Timer | £4.50 |
| AY-3-1270 Thermometer | £8.20 |
| ICL7106 DVM (LCD drive) | £7.00 |
| LM377 Dual 2W Amp. | £1.45 |
| LM379S Dual 6W Amp. | £3.50 |
| LM380 2W Audio Amp. | 80p |
| LM382 Dual low noise Preamp. | £1.00 |
| LM386 250mW low voltage Amp. | 75p |
| MM74C911 4 digit display controller | £6.50 |
| MM74C915 7 segment BCD converter | 96p |
| MM74C926 4 digit counter with 7 seg. o/p | £4.50 |
| S568B Touchdimmer | £2.50 |
| S9263 Touchswitch 16-way | £4.85 |
| SN76477 Complex Sound Generator | £2.52 |
| TB800 5W Audio Amp. | 58p |
| TB810AS 7W Audio Amp. | 85p |
| TDA1024 Zero Voltage Switch | £1.20 |
| TDA2020 20W Audio Amp. | £2.85 |
| ZN1034E Timer | £1.80 |
- All ICs supplied with data sheets.
Data Sheets only, 5p each device.

DO MAGAZINE REMOTE CONTROL PROJECTS MAKE YOU SEE INFRA RED?



How many times have you considered building a remote control project but were put off by the dozens of ICs, special coils, lenses and other hard to get components, not to mention the need for a well equipped lab. to set the unit up. T. K. ELECTRONICS have changed all that. Three ICs can build a sophisticated system that requires only a capacitor and resistor to set the clock frequency (which can drift by up to 20% without affecting performance). Control radios, hi-fi (including bass, treble and volume), lighting, toys, garage doors, etc. Still not convinced? then look at the prices!

- | | |
|--|-------|
| LD271 IR Emitting Diode | 36p |
| SFH205 Photodiode Detector | 95p |
| SL480 IC Pulse Amplifier | £1.40 |
| SL490 Keyboard Controlled Encoder/Transmitter | £2.40 |
| ML922 10-channel Receiver & 3 Analogue Outputs | £4.20 |
| ML926 16-channel Receiver (4 Momentary binary outputs) | £1.40 |
| ML928 16-channel Receiver (4 latched binary outputs) | £1.40 |
| Data sheets (per device) | 5p |

These ICs can also be used with ultrasonic and radio links, depending on range, cost and speed of operation. For more details, why not give us a ring - we will be pleased to advise you.

NEW KIT

If you do not require a sophisticated multi-channel remote control, we have developed a simple single-channel ON/OFF infra red transmitter and receiver. The transmitter unit comes complete with a hand held box and requires a PP3 (9V) battery. The receiver includes a triac capable of switching up to 500W at 240V a.c. and comprises a preamplifier, bistable latch and a mains power supply, making the unit completely self-contained. The small size of the receiver enables the unit to be "built into" all kinds of equipment from lamps to tape recorders. The minimum range is 20 feet. A suitable box for the receiver is available if required.


ONLY £12.00

TRIACS



- | | |
|---------------------------|------|
| 400V Plastic Case (Texas) | |
| 3A | 49p |
| 16A | 90p |
| BA | 58p |
| 20A | 185p |
| 12A | 85p |
| 25A | 190p |
| 6A with trigger | 80p |
| 8A isolated tab | 85p |
| Disc | 18p |

MINI TRANSFORMERS

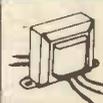

- | | |
|------------------------------------|-----|
| Standard mains primaries 240V a.c. | |
| 100mA secondaries | |
| 6-0-6V | 80p |
| 9-0-9V | 85p |
| 12-0-12V | 90p |

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION ADD VAT AT CURRENT RATE TO ABOVE PRICES PLUS 40p P&P

TRADE ENQUIRIES WELCOME

MAIL ORDER - CALLERS WELCOME BY APPOINTMENT.

TK Electronics
(P.E.), 106 STUDLEY GRANGE ROAD,
LONDON W7 2LX. TEL. 01-579 9794



Conquer the chip.

Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

ELECTRONICS



Build your own oscilloscope.

Learn to draw and understand circuits.

Carry out over 40 experiments.


DIGITAL TECHNIQUES

From watches to sophisticated instrumentation, Digital Electronics adds scope to hobby or career.



COMPUTER TECHNOLOGY

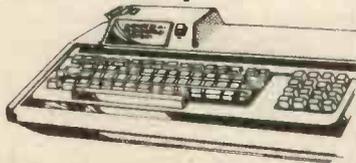
Learn to operate and programme your own home computer.



FREE BROCHURES



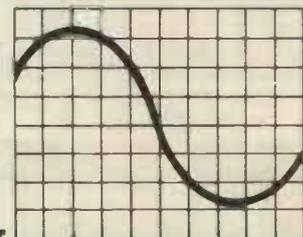No previous knowledge is necessary.
— Just clip the coupon for a brochure



TUTORCOURSE ELECTRONICS

Please rush me details of your ELECTRONICS COURSE

Name _____

Address _____

Block Caps. Please Post now, without obligation to:

British National Radio & Electronics School.

P.O.Box 156, Jersey, Channel Isles

Marshall's

A. Marshall (London) Ltd., Kingsgate House,
Kingsgate Place, London NW6 4TA
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582
Also retail shops: 325 Edgware Road, London W2.
40 Cricklewood Broadway, London NW2. 85 West Regent St., Glasgow.
108A Stokes Croft Bristol.

CAPACITORS:

Mullard Ceramic 63v range
1pF to 10,000pF E 24 range
all at £0.06 each
Siemens Ceramic 63v B37448/9
.01: .022: .033: .047mF @ £0.06
.068: .1mF @ £0.08: .22mF @
£0.11
CSF High Voltage Ceramic Discs
Prices £0.07 to £0.18 Range
100pF to 10,000pF
Voltage range up to 6Kv.
See catalogue for details.
Comprehensive range Siemens
Layer Polyester Caps: .001 to
3.3mF
Prices £0.07 to £0.63.
See catalogue for details.
Large range of Mullard/Siemens
Electrolytic Axial/Radial
Capacitance values 1.0mF to
10,000mF
Voltage ranges 25v: 40v: 63v:
100v:
Prices and types as catalogue
Also Mullard C280; Siemens
B32231/4 and B32110. All prices
net + VAT and postage/packaging.

TOOLS BAHCO

Side Cutter with Bezel.
Side Cutter without Bezel.
End Cutter without Bezel.
Vero Metal Shears.
Other items as catalogue.



BOXES & CASES

See catalogue for full range.
Aluminium boxes 13 sizes.
Rexine Covered boxes 7 sizes.
NEW RANGE TMEC CASES
Send S.A.E. for details & types
Price range. £14.04 to £17.00
ABS PLASTIC BOXES
3" x 2 1/4" x 1 3/8"
3 1/4" x 2 1/4" x 1 3/8" Prices as
4 1/2" x 3 1/4" x 1 1/2" catalogue
8" x 4 1/2" x 3"
BAZELLI INSTRUMENT CASES
5 sizes.

Miscellaneous hardware
including
Vero Board: Superstrips:
Vero Breadboard.
Vero boxes (see catalogue for
full range).



Card Frames: Fliptop boxes:
etc etc.

1980 CATALOGUE

U.K.: 65p post paid
Europe 85p post paid
Rest of World £1.25
post paid

Mail order: 01-624 8582



TTL see catalogue for full range

SN7400N	£0.14	SN7491AN	£0.54
SN7401N	£0.14	SN7492N	£0.31
SN7402N	£0.14	SN7493N	£0.32
SN7403N	£0.14	SN7494N	£0.80
SN7404N	£0.14	SN7495N	£0.55
SN7405N	£0.15	SN7496N	£0.34
SN7406N	£0.34	SN7497N	£1.80
SN7407N	£0.26	SN74100N	£1.10
SN7408N	£0.15	SN74107N	£0.21
SN7409N	£0.16	SN74118N	£0.76
SN7410	£0.15	SN74119N	£1.20
SN7411N	£0.15	SN74121N	£0.25
SN7412N	£0.22	SN74122N	£0.48
SN7413N	£0.28	SN74123N	£0.42
SN7414N	£0.47	SN74124N	£0.53
SN7416N	£0.22	SN74125N	£0.40
SN7417N	£0.22	SN74161N	£0.50
SN7420N	£0.15	SN74145N	£0.64
SN7423N	£0.18	SN74148N	£1.05
SN7425N	£0.19	SN74150N	£0.79
SN7426N	£0.19	SN74151N	£0.55
SN7427N	£0.19	SN74153N	£0.55
SN7430N	£0.15	SN74154N	£0.90
SN7432N	£0.17	SN74155N	£0.50
SN7437N	£0.21	SN74157N	£0.59
SN7438N	£0.21	SN74160AN	£0.70
SN7440N	£0.15	SN74161AN	£0.70
SN7441AN	£0.52	SN74162AN	£0.70
SN7442N	£0.40	SN74163AN	£0.80
SN7445N	£0.66	SN74164AN	£0.80
SN7446AN	£0.48	SN74165N	£0.80
SN7447AN	£0.45	SN74167N	£1.20
SN7448N	£0.45	SN74174AN	£0.80
SN7450N	£0.15	SN74175N	£0.63
SN7451N	£0.15	SN74176N	£0.74
SN7453N	£0.15	SN74177N	£0.73
SN7454N	£0.15	SN74180N	£0.70
SN7460N	£0.15	SN74181N	£1.65
SN7470N	£0.26	SN74182N	£0.83
SN7472N	£0.24	SN74184N	£1.29
SN7473N	£0.25	SN74185AN	£1.10
SN7474N	£0.28	SN74186N	£1.35
SN7475N	£0.31	SN74188AN	£1.84
SN7476N	£0.26	SN74189N	£2.26
SN7480N	£0.39	SN74190N	£0.74
SN7481N	£0.71	SN74191N	£0.79
SN7482N	£0.65	SN74192N	£0.79
SN7483N	£0.60	SN74193N	£0.79
SN7484N	£0.55	SN74196N	£0.74
SN7485N	£0.70	SN74197N	£0.74
SN7486N	£0.25	SN74198N	£1.09
SN7489N	£1.66	SN74199N	£1.09
SN7490AN	£0.33		

KNOBS & SWITCHES

Big selection as catalogue
Also Resistors; Presets; Pots;
Opto; Semiconductors etc.


SOLDERING EQUIPMENT IRONS-ANTEX

15 watt C15 £3.95
15 watt CCN £4.20
17 watt CX17 £4.20
25 watt X25 £4.20
Stand £1.50



DESOLDERING TOOL

Solder £6.50

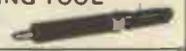

SINCLAIR INSTRUMENTS

Digital Multimeter
" " PDM35 £ 34.50
" " DM235 £ 52.50
" " DM350 £ 72.50
" " DM450 £ 99.00
Digital Frequency Meter
PFM200 £ 49.80
Low Power Oscilloscope
SC110 £139.00

CRIMSON ELEKTRIK HI FI MODULES

CE608 Power Amp £18.26
CE1004 " " £21.30
CE1008 " " £23.91
CE1704 " " £30.43
CE1708 " " £30.43
CPS1 Power Unit £16.96
CPS3 " " £20.43
CPS6 " " £26.09
CPR1 Pre Amp £29.57
CPR1S Pre Amp £38.70
All prices + VAT + postage/
packaging

3 1/2 DIGIT LCD MULTI-METER KIT

NEW

Build the Practical Electronics handheld DMM. This superb product offers professional precision with extended battery life. Five function operation (AC and DC VOLTS, AC and DC CURRENT, RESISTANCE) with ability to check diodes. 0.5" LCD display with 'Battery Low' warning. Auto-polarity, Auto-zero. Full protection against transients and overloads with ability to withstand mains on any range. 0.5% basic DC accuracy and 15 different ranges. It measures AC/DC voltages from 0.1mV to 500V. AC/DC current from 0.1µA to 2A. Resistance from 0.1Ω to 2MΩ. 200 hour battery life.

The Kit contains all parts needed to construct the multimeter plus assembly instructions, battery and test leads.

We also offer a calibration service (£5.00 + VAT) and a trouble-shooting and calibration service (£7.50 + VAT). Various other component parts are also available as listed.

The multimeter is also available fully assembled and calibrated at a cost of £39.70 + P&P + VAT.

Lascar Electronics Ltd., Unit 1, Thomasin Road, Basildon, Essex. Telephone No: Basildon (0268) 727383.



FEATURED ASA PROJECT IN PRACTICAL ELECTRONICS

	£	P & P	VAT	TOTAL
PE-DMM KIT	32.95	1.00	5.09	39.04
ICL 7106	8.95	0.50	1.42	10.87
LCD DISPLAY	7.95	0.50	1.27	9.72
PCB	4.95	0.50	0.82	6.27
FULLY ASSEMBLED DMM (INC. LEADS)	39.70	1.25	6.14	47.09

To: Lascar Electronics, Unit 1, Thomasin Road, Basildon, Essex.

Please send me Data FULLY ASSEMBLED DMM (INC. LEADS) £47.09

PE-DMM KIT £39.04 ICL 7106 £10.87 LCD DISPLAY £9.72 PCB £6.27

Name _____

Address _____

Tel. No. _____

I enclose cheque/P.O. value

1
GENTS QUARTZ LCD, 5-function. Hours, minutes, secs, month, date, backlight.
ONLY £4.95

2
GENTS QUARTZ LCD. SAME AS 1 - Alternative style.
ONLY £4.95

3
QUARTZ LCD Slim Chronograph. 11-function. Hours, mins, secs, 6 digit-month, date, day of week, 1/100 sec stopwatch, split and lap modes, backlight.
ONLY £7.95

4
QUARTZ LCD ALARM. 6 digit, hours, mins, secs, day, date. 24-hour alarm with on/off indicator.
ONLY £8.95


5
QUARTZ LCD Alarm/Chronograph. 22 functions. Hours, mins, secs, day, date, month, 1/10 sec stopwatch, split and lap modes, 12 and 24 hour modes, 24 hour alarm.
ONLY £12.95

We don't believe you can find better value combined with quality, than these - our special introductory prices. Compare the savings we offer and order now.





6
QUARTZ LCD Musical Multi-Alarm/Chronograph. 6-digit. Hours, mins, secs, day, date, 1/100 second stopwatch, split and lap modes, 24 hour alarm, dual time zone.
ONLY £13.45

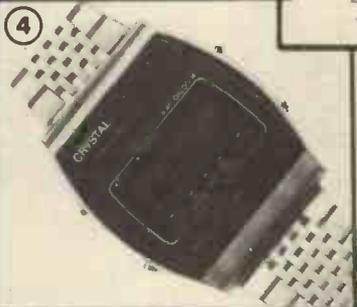14
CREDIT CARD CALCULATOR. Very slim with standard 4 functions plus memory, percentage and square root. Complete with a mock leather wallet with credit card pocket.
ONLY £6.95




7
SINCLAIR PROGRAMMABLE SCIENTIFIC CALCULATOR
Genuine programmable model using micro processor technology, this amazing device is more like a computer than a calculator. Complete with programme library book containing approx. 370 programmes for ELECTRONICS, MATHS, PHYSICS, ENGINEERING ETC. Limited quantity available.
ONLY £7.95
+ 75p carriage.

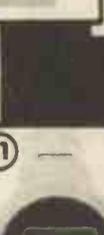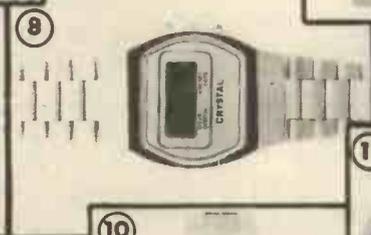13
BELTIME 29F. Alarm/Chrono. Advanced and accurate, this watch has 8 time functions, 4 alarm functions and 17 chronograph functions. Complete with backlight and stainless steel bracelet.
ONLY £19.95



8
LADIES QUARTZ LCD. 5-function as Gents No. 1. Available with black or white face.
ONLY £5.95

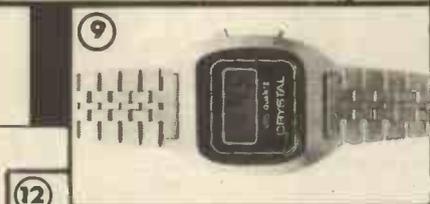12
GENTS ANALOGUE QUARTZ. Conventional display, accuracy normally associated with digital watches. Automatic calendar, elegant and robust.
ONLY £19.95



9
LADIES QUARTZ LCD. SAME FUNCTIONS AS 8. - Alternative style. Available with black or white face.
ONLY £5.95

11
LADIES QUARTZ LCD SAME AS 10. Alternative "Round" shape. Available in gold or silver colour.
ONLY £8.95



All watches have fully adjustable, matching stainless steel straps, and demonstration battery fitted (this battery is not guaranteed). Please add 60p for each spare battery required.

10
LADIES QUARTZ LCD. 5 functions. Dress Style. Functions same as 1. Available in gold or silver colour.
ONLY £8.95



All products carry a Full 7-Day Money-Back Reassurance, plus 12-Month Guarantee. Prices include VAT.

Send stamped addressed envelope for Colour Brochure of 120 other bargains.

PEELMOOR LTD

78 CASTLE STREET,
MELBOURNE, DERBY,
DE7 1DY

Please send me items..... (list numbers)

I enclose cheques/P.O.s for £.....

NAME.....

ADDRESS.....

Please add 35p P/P per item

PE3

Britain's first com computer kit.

The Sinclair ZX80.

£79.95 Price breakdown
ZX80 and manual: £69.52
VAT: £10.43
Post and packing FREE

Please note: many kit makers quote VAT-exclusive prices.

You've seen the reviews... you've heard the excitement... now make the kit!

This is the ZX80. 'Personal Computer World' gave it 5 stars for 'excellent value.' Benchmark tests say it's faster than all previous personal computers. And the response from kit enthusiasts has been tremendous.

To help you appreciate its value, the price is shown above with and without VAT. This is so you can compare the ZX80 with competitive kits that don't appear with inclusive prices.

'Excellent value' indeed!

For just £79.95 (including VAT and p&p) you get everything you need to build a personal computer at home... PCB, with IC sockets for all ICs; case; leads for direct connection to a cassette recorder and television (black and white or colour); everything!

Yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers at several times the price.

The ZX80 is programmed in BASIC, and you can use it to do quite literally anything from playing chess to managing a business.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. It immediately proves what a good job you've done: connect it to your TV... link it to an appropriate power source*... and you're ready to go.

Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs - all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be SAVED and LOADED on to a portable cassette recorder.)
- FREE course in BASIC programming and user manual.

Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately - see coupon).
- Additional memory expansion boards allowing up to 16K bytes RAM. (Extra RAM chips also available - see coupon).

*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).

The unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.

The unique Sinclair BASIC interpreter offers remarkable programming advantages:

- Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability - takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input to request a line of text when necessary. Strings do not need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions, USR causes jump to a user's machine language sub-routine.
- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.


Fewer chips, compact design, volume production - more power per pound!

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer - typically storing 100 lines of BASIC. (Key words occupy only a single byte.)




The display shows 32 characters by 24 lines.

And Benchmark tests show that the ZX80 is faster than all other personal computers.

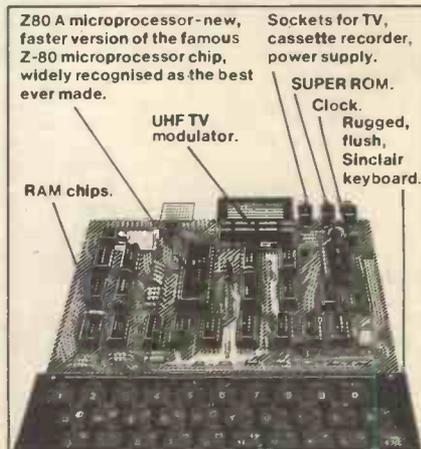No other personal computer offers this unique combination of high capability and low price.



plete

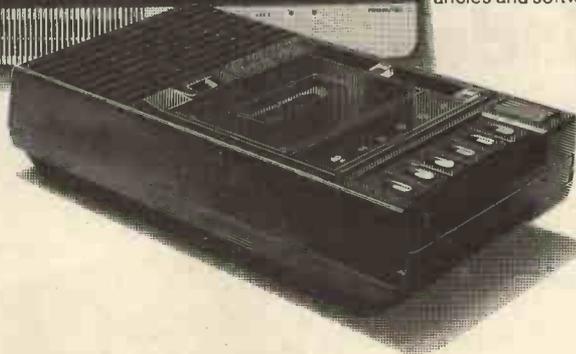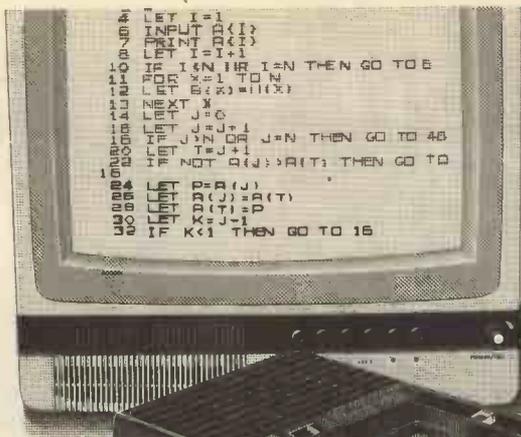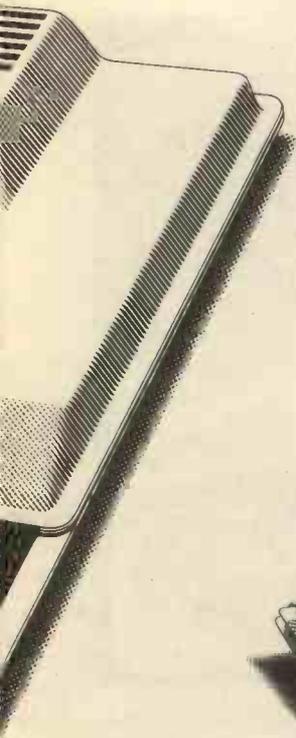

ZX80 software – now available!

See the advertisements in Personal Computer World (June) and Electronics Today International (July).

New dedicated software – developed independently of Science of Cambridge – reflects the enormous interest in the ZX80. More software available soon – from leading consultancies and software houses.

The Sinclair teach-yourself BASIC manual.

If the specifications of the Sinclair ZX80 mean little to you – don't worry. They're all explained in the specially-written 128-page book *free* with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming – from first principles to complex programs. (Available separately – purchase price refunded if you buy a ZX80 later.) A hardware manual is also included with every kit.

The Sinclair ZX80. Kit: £79.95. Assembled: £99.95. Complete!

The ZX80 kit costs a mere £79.95. Can't wait to have a ZX80 up and running? No problem! It's also available, ready assembled, for only £99.95.

Demand for the ZX80 is very high: use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. We'll acknowledge each order by return, and tell you exactly when your ZX80 will be delivered. If you choose not to wait, you can cancel your order immediately, and your money will be refunded at once. Again, of course, you may return your ZX80 as received within 14 days for a full refund. We want you to be satisfied beyond all doubt – and we have no doubt that you will be.

sinclair
ZX80
Science of Cambridge Ltd

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488.

ORDER FORM

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Remember: all prices shown include VAT, postage and packing. No hidden extras.
Please send me:

Quantity	Item	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	£79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	£99.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	8.95	
	Memory Expansion Board(s) (each one takes up to 3K bytes).	12.00	
	RAM Memory chips – standard 1K bytes capacity.	16.00	
	Sinclair ZX80 Manual(s) (manual free with every ZX80 kit or ready-made computer).	5.00	
		TOTAL	£

NB. Your Sinclair ZX80 may qualify as a business expense.

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £ _____
Please print
Name: Mr/Mrs/Miss _____
Address _____

PE

CONSTRUCTORS PACK 7

ALL THE PARTS TO BUILD THE PRACTICAL ELECTRONICS TRAVELLER CAR RADIO

*** EASY TO BUILD * 5 PUSH BUTTON TUNING * MODERN STYLING DESIGN * ALL NEW UNUSED COMPONENTS * 6 WATT OUTPUT * READY ETCHED & PUNCHED P.C.B. * INCORPORATES SUPPRESSION CIRCUITS**



£10.50 p&p £1.75

The pack contains all the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March Issue. The P.E. Traveller features pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, negative ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The P.E. Traveller fits easily in or under dashboards. Complete with instructions.

CONSTRUCTORS PACK 7A
Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete.

£1.95 Per Pack, p & p £1.00.
Pack 7A may only be purchased at the same time as Pack 7.
NOTE: Constructor's pack 7A sold complete with radio kit **£15.20** including p&p.

A FEATURED PROJECT IN PRACTICAL ELECTRONICS



323 EDGWARE ROAD, LONDON W2. For Personal Shoppers Only.
21C HIGH STREET, ACTON W3 6NG. Mail Order Only. No Callers.

Mon-Sat 9.30am-5.30pm
Closed Thursday

NEW 12+12

AMPLIFIER KIT

An opportunity to build your own 12 watts per channel stereo amplifier with up-to-the-minute features. To complete you just supply screws connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disc amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits. Also featured 4 slider-level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free Size 9 1/4" x 8 1/4" x 4" approx with kit **£13.95**

TWO WAY SPEAKER KIT To suit above amp. Comprising 2, 8" approx Philips base unit, and 2, 3 1/2" approx tweeters with 2 crossover capacitors **£4.95** p&p £1.65.
Available only to first time purchasers of the 12 + 12 kit.

50 WATT MONO DISCO AMP

£30.60
p&p £3.20

Size approx 13 1/2" x 5 1/2" x 6 1/2"
50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

NOW AVAILABLE

30 + 30 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and push buttons with matching fascia. red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/2" x 3" x 10" approx. **£32.90**
p&p £3.30

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE PRICE AT OVER

£25 PER PACK SEE OUR PRICES

1 PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE £5.00**
p&p £1.10

2 PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **illus. OUR PRICE £7.65** p&p £1.15

ACCESSORIES Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£3.00** plus p&p £1.60

Two Way Speaker Kit Comprising of two 8" x 5" approx 4 ohm bass and two 3 1/2" 15 ohm mid range tweeter with two cross-over capacitors. **Per stereo pair plus p&p £4.05**

ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS

£76.00 p&p £4.00

100 WATT MONO DISCO AMP

Brushed aluminium fascia and rotary controls. Size approx. 14" x 4" x 10 1/4"
Five vertical slide controls, master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak

EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx woofer with rolled surround. 3 1/2" Goodman tweeter crossover components and circuit diagram. Frequency response 20 Hz to 20 kHz. Power handling 15 watts RMS. 20 watts max 8 ohm impedance

£18.25

Per stereo pair p&p £4.20

BSR P200

£25.50

Belt drive chassis turntable unit semi-automatic, cueing device. p&p £3.00
Shure M75 6 Magnetic Cartridge to suit.

£7.95



BSR Manual single play record deck with auto return and cueing lever, fitted with stereo ceramic cartridge 2 speeds with 45 r p m spindle adaptor ideally suited for home or disco use. **p&p OUR PRICE £12.25** £2.75



323 EDGWARE ROAD, LONDON W2
21C HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 15%
All items subject to availability. Price correct at and subject to change without notice.
All enquiries Stamped Addressed Envelope.

NOTE: Persons under 16 years not served without parent's authorisation.

PHILLIPS RECORD PLAYER DECK GC037

Hi-Fi record player deck, belt drive complete with GP401 magnetic cartridge—LIMITED STOCK. **£27.50** complete.
UNBEATABLE OFFER AT BUYER COLLECT ONLY.

BARGAIN OFFER

Ariston pick-up arm manufactured in Japan. Complete with headshell. **OUR £11.95**
Listed price over £30.00. **PRICE p&p £2.50**

PE TELETEXT

BACK in June '79 an announcement was made that we would be publishing a Teletext system in the near future. A lecture on Teletext was presented by PE at the Great British Electronics Bazaar and development was under way. Since that time our Projects Editor David Shortland has been developing a system. Why has it taken so long? A brief look at the problems we have had to overcome will answer this question and we are sure will be interesting to all readers.

The *PE Teletext* was first discussed at a meeting in London involving two representatives of Mullard (who had developed the chips and system we were to use), a director and technical representative of Marshall's (who were, as a Mullard distributor, to provide parts and technical expertise) and the Editor.

After that meeting things started to move quite fast, a range of components and boards were supplied by Marshall's and David set to work building a system that would interface directly to the set. It was felt that this was the most satisfactory way to obtain the quality of picture we required, and Mullard claimed to have a number of interface circuits for various sets that they would make available to us.

Work proceeded at a reasonable pace until David came to build the interface

board to match the system to his own Philips set. Mullard provided a "circuit idea" which did not give enough information, so David approached Philips who were using the chips in their set. Philips of course own Mullard so we expected some "company" line and agreement.

Philips informed us that what we were trying to do would not work. A visit to Philips followed. More investigation and more questions to Mullard indicated that the interface circuits they had supplied were theoretical. What was more worrying was that we were discovering a very high proportion of existing sets were not suitable for a direct interface, mainly due to the i.f. not being good enough.

Having wasted a few months because of misleading information we decided that we had two options: 1) Drop the whole thing, 2) Redesign to incorporate a u.h.f. modulator so that the system could plug in the aerial socket of any set.

We chose the latter option, Marshall's supplied more parts and David started work again. The system looked good, we planned publication for the April issue and were only waiting for a colour modulator board to set the whole thing up for cover shots. Then more problems, the quality of the final picture was not up to the standard we required and relied too heavily on a high signal strength. A criticism we had of other

systems and a problem we were determined to avoid.

It looked for the second time as if the whole project would come to grief. This time we were saved by some developments at Mullard. A new PAL encoder chip had been developed and Mullard kindly supplied us with pre-production units to try in our system. The new chips worked well and at last we had the quality we were after.

But wait! Mullard had yet to decide to produce the chip so again we were in danger of losing the project. Luckily they have gone ahead and we are finally able to publish the long awaited system.

The change to an external plug-in unit and the use of the new developments from Mullard have pushed up the anticipated price. But we believe the quality now available is better than any other plug-in system and we are proud to bring you *PE Teletext*.

The story has been shortened—for instance, our main contact at Mullard left and Marshall's technical man left before we had got very far. Some of the chips originally used are now in short supply, so alternatives have had to be found. David's wife gave birth to twins, severely testing his development time and concentration! Looking back it's a wonder anything came forth. Part one starts on page 38.

Mike Kenward.

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

David Shortland PROJECTS EDITOR

Jasper Scott PRODUCTION EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Colette McKenzie SECRETARY

Editorial Offices:

Practical Electronics,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: *Editorial* Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone (see below).

Advertising Offices:

Practical Electronics Advertisements,
King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Telex: 915748 MAGDIV-G

Make Up/Copy Dept.: 01-261 6601

ADVERTISEMENT MANAGER

D. W. B. Tilleard

SECRETARY **Christine Pocknell**

} 01-261 6676

AD. SALES EXEC. **Alfred Tonge** 01-261 6819

CLASSIFIED MANAGER **Colin Brown** 01-261 5762

Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in *Practical Electronics*.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to **one published project only**.

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

Back Numbers

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 75p each including Inland/Overseas p&p.

Binders

Binders for PE are available from the same address as back numbers at £4.30 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

Market Place

Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

by
David Shortland

and
Jasper Scott

GUNNED DOWN

Anyone who is rewiring their house, or installing microbore central heating pipes would find their job made easier by the use of one of the Arrow range of tacking guns, now available from Telequip of Bristol.

Four different sizes of gun and twelve different sizes of staple are available, and cable sizes from 5 to 15mm diameter can be fastened with a considerable saving in time and money over conventional cable clips.



All guns retail at £20.90 plus VAT, and further details of the range can be obtained from: **Telequip, 2 Oakfields Road, Clifton, Bristol BS8 2AL. (0272 312271)**

ERASE YOUR EPROMS


A range of ultraviolet EPROM erasers, manufactured by the U.S. Spectronics Corporation, is now available in this country from Chiptech Ltd.

Claimed to be the fastest and most efficient erasers of their size on the market, they have been designed primarily for the small systems and computer hobbyist at a cost which is well

within their reach.

The cheapest of the range, the PE-14, has the capacity to erase up to 6 EPROM chips in as little as 19 minutes. A similarly rated unit, the PE-14T, is fitted with a 60-minute timer to automatically shut off the unit.

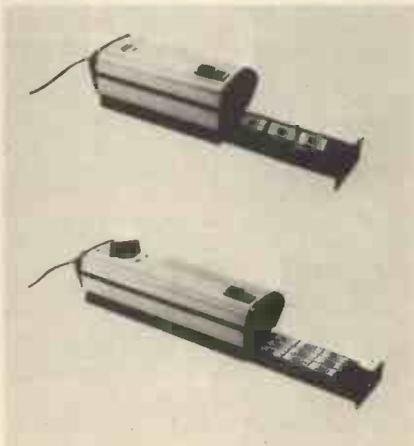The PE-24T, which is a faster and more powerful version of the PE-14 series, will erase up to 9 EPROMS at once, in as little as 15 minutes.




All erasers are fitted with safety interlocks and housed in gold anodised aluminium casings, which combine to make them extremely safe.

Prices for the range are as follows: PE-14—£56; PE-14T—£76.58; PE-24T—£111.22. Further information is available from: **Chiptech Ltd., Unit 1, Tewin Court, Welwyn Garden City, Hertfordshire AL7 1AU. (07073 33260)**

WORK CENTRE

One of the best multi-position work holders to come on the market so far is the new 324 work-centre, made by Panavise and distributed by Toolrange, which provides a versatile and compact unit for constructors working on p.c.b.s.

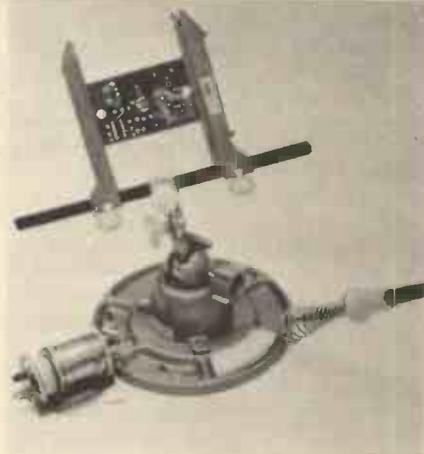The 324 consists of the 312 Tray Base mount with six useful component compartments, the standard 300 vice base, permitting positioning through a 360 degrees hemisphere, the 315 p.c.b. Holder and the 371 Solder Sta-



tion. The 315 p.c.b. Holder handles circuit boards up to 200mm wide and 4mm thick and extra pairs of arms and an extension bar are available to enable several p.c.b.'s to be worked on at once. The 371 Solder Station consists of a wire spring soldering iron holder, capable of holding most popular irons, a shaped sponge which fits the tray base and a combined wire and solder reel holder. (Soldering iron, reel of solder and wire not supplied).

The price of the complete station is £35.00 + VAT and delivery is ex-stock from: **Toolrange Ltd., Upton Road, Reading, Berks. RG3 2JA (0734 29446)**

SAXON CATALOGUE

Saxon Entertainments are well known among the disco fraternity, and their 1980 catalogue is now available, and packed with everything from jack plugs to complete disco consoles.

Saxon's comprehensive range includes some exciting lighting effects units, and as well as the "pay and play" complete systems, there are chassis speakers, turntables, cabinet fittings—in fact everything you need to build your own disco system.

The catalogue also contains ten vouchers worth a total of £30. One voucher may be used towards each £30 worth of equipment purchased.

To obtain your copy of the catalogue, send £1 to: **Saxon Entertainments 327/333 Whitehorse Road, West Croydon, CR0 2HS (01-684 0098)**

PET PROGRAMMER

A hardware/software package which turns the Commodore Pet into a powerful and flexible programmer for 4K type 2532/2732 EPROMs is now available from GR Electronics Ltd. of Newport, Gwent. It complements the company's existing programmer for

2516/2716 devices, both allowing Pet users to produce firmware to run on their own, or other microcomputer systems.

Owners of the 3016, large keyboard Pet can use the package to give themselves up to 12K of custom-written firmware housed in the machine's three spare EPROM sockets. Older type 2001 Pets can also benefit, but using an adaptor for the memory expansion connector.

The new programmer is for 5V rail type 2532/2732 EPROMs, and comprises a plug-in circuit board which uses the IEEE port for data, the user port for control lines and takes 5V power from the Pet's external cassette drive. Full EPROM programming software is supplied on cassette, with functions including READ/WRITE to and from RAM and EPROM, sequencing, verification and READ/WRITE/MODIFY with addresses and data in hex.

And extension socket is also available for the convenience of users programming EPROMs in batches. It incorporates a header, extension cable and plinth-mounted zero insertion force socket which allows all device handling to be carried out adjacent to the Pet's keyboard.

Although both 2532 and 2732 (Intel) EPROMs can be programmed with the GR Electronics device, only the 2532 is directly compatible with the new Pet's internal ROM sockets.

The price of the programmer board and software is £80 plus VAT, and the extension is £35 plus VAT. Both may be obtained direct from: GR Electronics Ltd., Fair Oak House, Church Road, Newport, Gwent NPT 7EJ. (0633 214147)

SIMWOOD

The latest DMM from Simwood is the MC545. This $4\frac{1}{2}$ digit meter has a measurement capability of 19999 and a basic d.c. accuracy of 0.05 per cent. The 545 will operate from either a.c. mains or batteries with rechargeable cells available as an option.

Press-button selection is available for all functions and ranges (five functions and 26 ranges). Typical measurement accuracies are:



between 0.15 and 0.8 per cent on the resistance range; 0.05 per cent on the d.c. voltage range and 0.5 per cent on the a.c. voltage range.

The 545 which has overload protection on every function and range measure 180x64x200mm and weighs approximately 1.42 kg. Each instrument is supplied complete with an operator's manual, test leads, spare fuses and batteries. The 545 is priced at £139.00.

Simwood Limited, Garretta Hall, Shalford Green, Essex.

GOT A LIGHT, MIC?

A new, small, lightweight microphone, with appearance, handling and performance features ideally suited to highly professional on-cameras or on-stage use, has been announced by Shure Electronics Limited.

Designated the SM63-CN, the new unit is less than six inches long and weighs only 2.8 oz., making it significantly more comfortable to handle and considerably less obtrusive in performing situations than any other comparable microphone.



The SM63-CN is a dynamic, omnidirectional type with an output that is about 6dB higher than larger, comparable units. Other performance advantages include a controlled low-frequency rolloff to ensure natural sounding voice and music pickup, as well as smooth high frequency response for an overall clear, crisp clean sound similar to some condenser microphones.

Additionally, the SM63-CN features a hum-bucking coil that makes it insensitive to strong hum fields, such as those produced by studio lighting; a mechanical-elastomer isolation system that makes it resistant to handling noise; built-in breath and pop filter; and a robust polyester grille that is impervious to dents, rust and moisture.

Normal list price of the SM63-CN is £57.00 plus VAT, which includes a swivel adapter, windscreen and three-pin audio connectors on both ends of the cable. For further information contact: Shure Electronics Ltd, Eccleston Road, Maidstone, ME15 6AU (0622 59881)

HI-FI ON THE MOVE

If high fidelity is important to you wherever you are, you will no doubt drool over the three new portable radio/cassette recorders recently introduced by JVC. All three models have the facility of metal tape compatibility which will certainly help to give you the sound quality you're after.

The RC M80L (FM/ MW/ LW/ SW) uses a portable version of the JVC synthesiser tuning system with 32 l.e.d. indicators, and has a 12 station random preset capability, with automatic station scanning.

A twin motor, full logic, solenoid operated tape transport, and optional remote control are particularly noteworthy features of the RC M60L, while the 15 watts per channel RC M70L has a 16 programme multi music scanner.



Once you have decided which model best suits your needs, all you then need to do is find between two and three hundred pounds. Recommended prices for the three models are as follows: RC M60L—£220; RC M70L—£240; RC M80L—£290, though if you shop around, you should be able to get about ten per cent off. Pictured above is by far the best looking of the three, the RC M70L.

SOUND BOX

A simple tone generator sound box which is suitable for use with both the UK101 and the Ohio Superboard II is now available from John Mortimer Electronics.

The unit is *not* based on the GIM AY-3-8910, sound chip, but employs a VCO which can be activated direct from the keyboard. It is available either ready assembled and tested or in kit form. All that is required to construct the kit, comprising a couple of CMOS chips, transistors, and about ten potentiometers, is a soldering iron, solder and wire cutters. When assembled the unit is easily connected to either computer and will run off the on-board power supply unit. Unlike more sophisticated sound generators, this unit is easy to control, with hardware volume control and tuning, and can produce music from a simple program of keyboard row address POKEing.

Each box comes complete with full instructions and a cassette of interesting effects. The kit is priced at £14.95 or assembled for £19.95 (including VAT and p&p).

John Mortimer Electronics, PO Box 71, Norwich NR6 7JE.

MK14

The long awaited full-length programming guide for the Science of Cambridge MK14 will be available in September. The book which is called *Understanding Microprocessors with the MK14* contains just about every aspect of MK14 Assembly language/machine code programming, from number systems and addressing modes to number crunching, interrupts, DMA, multiprocessing and real-time applications. The appendices include a useful instruction set summary, a full listing for the "Hi-lo Game" (used in the text as an example of designing a complex program), and circuits for a $1\frac{1}{2}$ K memory expansion.

Priced at £5.95 plus 35p p&p the book will be available direct from Tony Watson, Globe Book Services, Little Essex Street, London WC2.



by **AURA SOUNDS**

SEE US AT RECRO '80, LEAMINGTON SPA. 1-8th AUGUST.
A great day out for all. Continuous Wersi Demonstrations.

The winning combination offering you the world of do-it-yourself organ making – at a price you can afford.

AURA SOUNDS are the first company to successfully market WERSI Kits in the UK.



Franz Lambert is seen playing the latest addition to WERSI's range – "The Entertainer". It has a split keyboard, with Horn 16', Tibia 16', Tibia 8' and clarinet 8', vibrato, percussion and 19 note accompaniment section with Bass Guitar and Piano effects coupled to a rhythm unit offering March, Beat, Slow Rock, Waltz, Samba and Swing, with autochords. *The complete kit is just*
£220!

Send now for full details.

WHY WERSI?

A fresh approach and top quality are the secret behind WERSI's worldwide success. The advanced technology used in WERSI organs should dismiss any apprehension against the do-it-yourself construction of an organ. It also offers unlimited possibilities for exploring new areas of musical experience. New aids for the organist help even the beginner to enjoy the instrument from the start and the advanced musician will reach new heights of satisfaction. The novel approach to organ building is highly acclaimed by professional musicians like Klaus Wunderlich as well as by the demanding home organist.

Today WERSI is one of the leading organ manufacturers in the world and exports to over 25 countries.

D-I-Y organ building is no longer the exclusive pastime of a few technically versed buffs. The construction phases consist of assembling printed circuit boards, the installation of the sub units and hardware and the wiring. The organ console comes to you already assembled and complete. Prefabricated laced wiring harnesses contain almost all wiring, eliminating a major source of problems.

WERSI MAKES DO-IT-YOUSELF CONSTRUCTION EASIER THAN EVER BEFORE AT A FRACTION OF THE PRICE OF THE FULLY ASSEMBLED WERSI RANGE. GET THE FACTS NOW.

AURA SOUNDS 14-15 Royal Oak Centre, Brighton Rd., Purley, Surrey. Tel: 01-668-9733
and at 17 Upper Charter Arcade, Barnsley, W. Yorks. Tel: Barnsley (0226) 5248.

AURA is WERSI is AURA is WERSI is AURA



Send now for the 104 page full-colour catalogue.

Please send me the full colour WERSI catalogue, price lists and supporting literature (weighing 1 lb!) I enclose a cheque/p.o. for £1.00.

Name.....

Address.....

Send to Aura Sounds (PE8) 14/15 Royal Oak Centre, Brighton Rd., Purley, Surrey.



INDUSTRY NOTEBOOK

By Nexus



Irish Expansion

Ireland's Industrial Development Authority (IDA) is reported as having forecast that the Republic will be Europe's 'Silicon Valley' by the early 1980s. A touch of euphoria is perhaps forgivable since Mostek decided to set up a plant on the outskirts of Dublin as the best backdoor through which to enter the European Common Market.

The immediate work flow is wafer fabrication in Dallas, dicing and assembly in Malaysia and final test in Dublin. Future development is expected to result in wafer fabrication in Ireland by 1983 and some 1,200 people employed by 1984.

There are now some 70 electronics manufacturing plants in the Republic, over 60 percent being American with the balance almost entirely from Europe. This is a remarkable performance by the IDA in selling Ireland as an electronics base. Particularly so as the country has no history or reputation in engineering industry of any sort compared, for example, with Scotland which has also been dubbed a 'Silicon Valley' with its first semiconductor plants set up some 20 years ago and since mightily expanded.

Ireland is a fine country for both visiting executives and local workforce. A good vacation area with marvellous fishing, riding and other outdoor amenities: But the real attraction appears to be the low cost of entry. The IDA smooths the path with incentives such as low-cost factories and tax-free arrangements for profits on exports amounting to indirect subsidy. The IDA has spent £75 million on factories for the immigrant companies.

On the debit side there is no great pool of cheap labour as in offshore operations in the Far East, inflation is high, the cost of living is higher and industrial unrest greater than in the UK. There is also a chronic shortage of engineers and technicians, so much

so that the Irish Government pays £2,000 towards the cost of a house to attract key people, mainly from the UK.

Ireland has an export growth rate in electronics of 50 percent per annum. It sounds fantastic until you remember the base line of absolute zero only ten years ago. In fact by world standards the true figures of size are not outstanding. One of the oldest-established American companies in Ireland is Digital Equipment Corporation who set up an operation in Galway in 1971 but still employs only just over 1,000 workers.

Present projections are that total electronic exports of all types will reach a level of £400 million this year, roughly equivalent to the turnover of a company the size of Racal in the UK.

Ireland has done remarkably well as an off-shore assembly area but has as yet little indigenous innovative capability. There is therefore no real threat to high technology countries. Nonetheless Ireland has a foot on the ladder and deserves watching.

UK Employment

With so much talk of recession and redundancy a heartening note appeared in the annual report of the Electronic Engineering Association which covers the activities of companies solely engaged in the electronic capital goods sector of the market. The employment trend remains upwards with almost 100,000 people employed (a two percent increase) and this despite the fact that widespread use of ICs and now LSI is continually reducing the labour content of assembly and wiring.

Output of the capital goods sector rose by 20 percent in 1979 to over £1.4 billion which allowing for inflation is an underlying growth rate of five percent. Direct exports are running at the rate of 42 percent to which should be added the equipment sold to others in the UK for export in their own products such as aircraft and ships.

Forward order books are at their highest ever level and still lengthening. The only serious difficulty is, 'Too many employers competing for too small a pool of high skilled people', a situation in which the EEA's outgoing President, J. W. Sutherland, comments that 'the scope for immediate remedy is sorely limited'.

This year's EEA President is Dr. P. E. Trier who graduated as a Mathematical Wrangler from Cambridge. After war-time and post-war employment with the Royal Naval Scientific Service he joined the Philips Group and was director of the Mullard (now re-named Philips) Research Laboratories at Redhill from 1953-69. He is now a director of Philips Industries, the parent organisation of all the Philips Companies in the UK.

As a mathematician, engineer and industrialist, Dr. Trier ought to be uniquely qualified to find out why there are always conflicts between industry and Customs and Excise exports statistics. Even if improved correlation of the figures won't tell us where we are going it would at least tell us with greater certainty where we have been.

Scanner Sold

The sale by Thorn-EMI of their X-ray scanner business to US General Electric for £17 million is a sad end to an enterprise once so full of promise. EMI's breakthrough in medical diagnostics was sensational. So, at first, were the profits. US GE came in as a me-too company and then still more companies elbowed into the business. In the end EMI couldn't stand the losses, some £26 million in the past two years, and the recently formed Thorn-EMI just had to give up.

It is a pity that a brilliant invention which has done so much for suffering humanity should have seen such vicious in-fighting for market shares. There were patent disputes all round and part of the deal with US GE is that Thorn-EMI will now receive royalties in return for a licence on the patents.


Thorn-EMI is not, however, entirely out of the business. They still have their latest model which, apparently, US GE didn't want, and they have an interest in a new body-scanning technique using the principle of nuclear magnetic resonance in place of traditional X-rays. An experimental machine is to be tried out at Hammersmith Hospital. But it is clear that Thorn-EMI will approach further entry into the scanner market with more than usual caution.

Good News

Britain's first System X telephone exchange is entering service this month (July) six months ahead of schedule. Other big BPO up-date programmes include extending the radio paging system to cover most of the UK through more than 250 VHF transmitters, and replacement of all the pay phones with a new type controlled by microprocessor. On the broad front there will be a 50 percent increase in telephone system capacity by 1990.

Among recent defence orders is one worth £50 million for Type 2016 sonar systems for the Royal Navy and a £75 million development contract for a Mk 2 version of the British Aerospace Sky Flash radar-guided air-to-air missile. The aerospace sector of industry which includes radar, radio and electronic navigation aids exported nearly £400 million of equipment in the first quarter, all set for yet another record year.

New Scotland Yard is to have a £40 million up-date of command and control systems for the Metropolitan Police. The BPO has ordered 215 noise measuring sets from Eddystone Radio to enhance detection and rectification of radio interference sources. Robot enthusiasts will be delighted to hear that 28 of them are being installed on the new Mini Metro production lines at BL cars. And Marconi Communications Systems has completed ahead of schedule a second earth satellite terminal worth £1.75 million in Bahrain, the 17th Marconi major earth terminal to enter service throughout the world.

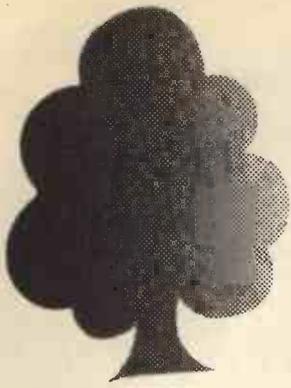

ACORN Review...

Dr. A.A. BERK

THIS REVIEW should start—"from little acorns, giant oak trees grow". The machine is Science of Cambridge's modular computer system, starting with *System One* and ending with *System Four*. The photographs show the System Three level lent by S. of C. for review. To a great extent it is the Software which distinguishes this machine; and, as the photograph shows, its compatibility as a Prestel terminal for the Post Office's new remote processing link. The video from the machine is in full colour, which unfortunately cannot be appreciated from accompanying photos.

HARDWARE AND PRICES

There are four system levels of the computer—the first, called System One, is more commonly known as the Acorn Computer (see PE review Sept. 79). This consists of two boards—a 6502-based processor and memory board, plus the display, keyboard and cassette interface p.c.b. The photograph here shows what happens to the basic Acorn when it is expanded. Facia panels are added along with sockets to fit a backplane. The keyboard and display sections are removed and the two p.c.b.s slotted into a backplane and rack of the 19in. Eurocard variety.

The System One costs £65, and the System Two with card frame, backplane (and four sockets), CPU board, cassette and VDU interface, 4K RAM, Software monitor and 4K BASIC will set you back £285 as a kit. A further £200 will buy a fully assembled and tested version, with the additions of case, 5V 3A PSU, buffered backplane and 8 sockets, 4K more of RAM, front panels, connectors and an 8K BASIC. At the time of writing, software was being supplied in EPROM (2732's) and an EPROM surcharge of £50 on the System Two was in force. Each additional component is available separately from S. of C., and this is one of the great advantages of the device, a small start does not imply that you'll need to buy a different computer to gain greater sophistication.

The System Three takes the user to mini-floppy disk storage, all neatly fitting into the rack, and the System Four adds another rack to give maximum expandability for the system up to full memory and two 5¼" drives. The System Three photographed here has three 8K RAM boards, CPU card, cassette interface card, VDU card, PSU, fully socketed card rack (with one blank panel here) and mini floppy. The total cost without TV monitor would be around £1,300 assembled and tested (including an ASCII keyboard, which comes cased). S. of C. will also sell you a Sony Trinitron colour monitor for £350. The total disk storage included is 80–90K.


Physically, the p.c.b.s are a high-quality plated-through product which seem easy enough to assemble and are, of course, fully solder-resist coated. The VDU Controller used is the 6845, which is fast becoming the industry standard, and the disk controller—the 8271 chip. S. of C. supply data sheets on all the devices used within their system at £1 each.

Expansions to the basic system include a Universal Interface board with parallel and serial ports, for hardware control, and a 6809 board to evaluate this processor via a software monitor (which is also included).

The photographs of the working system show a picture of the Post Office's "Busby" logo for a very good reason—S. of C. provide software and hardware to interface with the Prestel and Teletext System.

DISK OPERATING SYSTEM

The Disk Operating System (DOS) has some pleasant and sophisticated features which make its operation neat and less time-consuming than some others. Generous abbreviations are allowed, and qualifiers may be used to separate out a portion of the catalogue for special use. All the usual features are present—definition of drive number (0 and 1 only, as a maximum of 2 drives exist), protection for given files etc. Eight

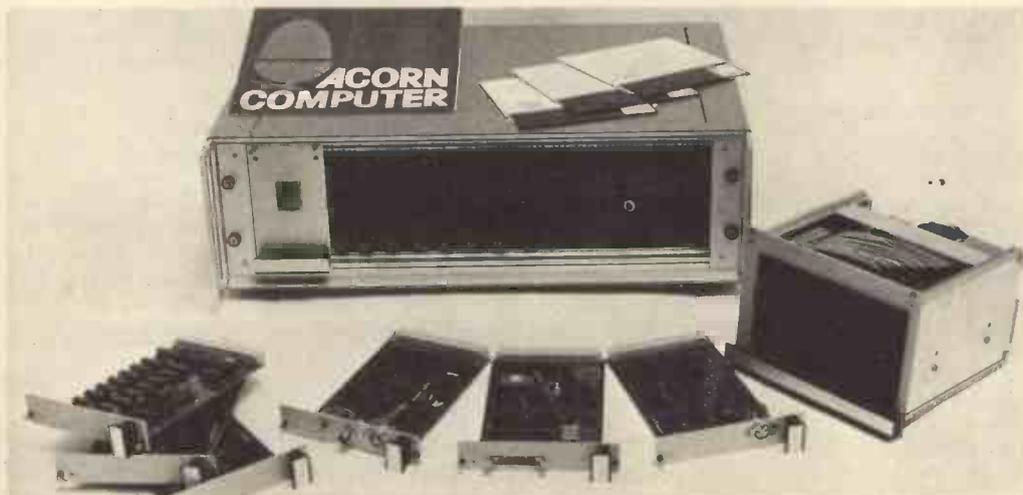

characters are allowed for a file name on disk, and these may be non alpha-numeric. Error messages are quite informative and not just numeric.

Automatic "booting" of a program stored on disk is possible on RESET, and the disk is given an "option" number by the OPTION command to allow the following modes:

- Option 0: do nothing upon RESET (i.e. stay in DOS)
- Option 1: load the file "BOOT"
- Option 2: run the file "BOOT"
- Option 3: execute the file "BOOT".

The last option allows the file called "BOOT" to contain Commands as if typed in from the keyboard. Thus, if BOOT contains the Bytes "BASIC" (a five-byte string: B,A,S,I,C.); then, assuming the BASIC interpreter is resident on the disk, BASIC will be booted in automatically on RESET.

Any other commands may be contained in "BOOT" for this option, and BOOT is called a "command" file—very useful for some clever software tricks.

Automatic messages may be produced upon accessing given files, and these give programs a more professional and "turnkey" air when used along with Option 3 above. Other DOS commands available are the usual LOAD, SAVE and DELETE for disk files; EXEC and GO for executing machine-code routines directly and INFO to find out about the files stored in a disk, usually after a CAT command, to display the catalogue of existing files. The information returned is: qualifier, whether or not protected, file name, LOAD and RUN addresses, length of file and start-sector on disk.

The DOS also produces a familiar set of disk error messages such as "clock error", "sector not found" etc., which can help to locate bugs in the hardware of the drive if necessary.

SOFTWARE AVAILABLE ON THE SYSTEM

The languages available for the system are BASIC, LISP and 6502 Assembler, while the potentially ubiquitous PASCAL is in preparation. In addition to these, many games are in existence, and a word-processing package (described below) is also in existence.

BASIC

The Basic on disk has some very interesting and uncommon features, as it was originally conceived to control psychology experiments. Multi-statement lines are allowed, separated by semicolons; and abbreviations (with a full stop) are allowed for all

the BASIC keywords, down to the minimum number of letters necessary to make the word unique (this is as for DOS). Additionally, spaces are more important than usual in BASIC. A useful feature is that the "@" sign stands for a variable which determines the fields within which numbers in a PRINT statement are printed. If @ equals 5, for instance, then 5 spaces (including sign if negative) are reserved for printing each number (right justified) when commas are used in the PRINT list.

The processor card contains 1K of RAM and 104 of these locations are reserved especially for the upper-case single-letter variable names (A,B,C, etc.). These are always tested first, and provide a set of fast-access variables. In addition, single lower-case letters are available for line labels. Thus:

```
10 a PRINT "hello"
```

```
20 Goto a
```

would put "hello" endlessly onto the screen.


A feature called "word indirection" is available whereby the result of a calculation can be stored directly into a given set of four contiguously addressed bytes. In such a process, direct access to the Addresses of data bytes is thus greatly simplified. In addition, hexadecimal numbers may be used directly within a calculation by using the £ sign as a prefix. Thus, PRINT £AF gives the result 175, on the screen. Thus Hex numbers may be added and printed using:

```
PRINT £AF + £13
```

this gives the result C2—*great for hex calculations!* The DO—UNTIL statement is provided in System Three BASIC, allowing loops to be processed until a given condition is satisfied. This can be useful in numerical methods for instance, or in control functions.

The statement "LINK" allows machine code statements to be run from BASIC, in a similar manner to the more familiar "USR" function. Bytes, complete frames of 4 bytes and strings, may be "got" from and "put" to sequential data files using the usual variety of statements which one would expect in a disk BASIC. All the familiar BASIC statements are available, with the usual optional use of LET and END statements. No ELSE is allowed in IF statements, and the basic BASIC supplied has no floating point package. This is available as an extension.

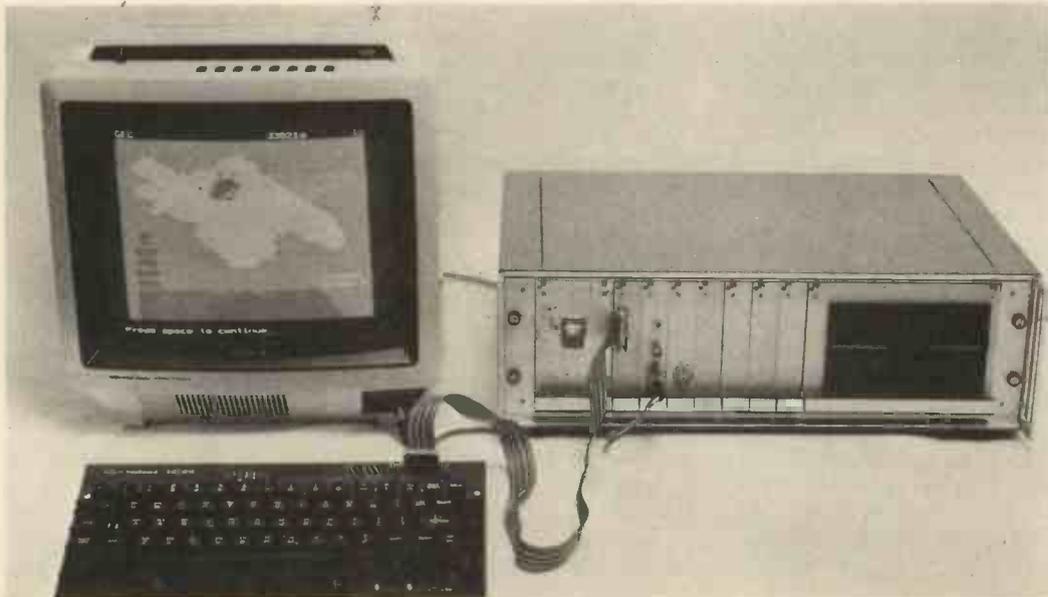Another extension is the graphic package which functions as follows: The screen is divided into 78 x 75 dots or Pixels (picture elements). The Busby picture shows the resolution of the system. Individual pixels are rather large, but adequate for Teletext and Prestel.



To set up a pattern on the screen, several commands are available. CLEAR clears the screen and places it in graphics mode, as well as setting the colour of the pixels to be plotted. PLOP, MOVE and DRAW then allow lines and points to be displayed on an X,Y Co-ordinate system based at the bottom left-hand corner of the screen.



LISP

Finally, the language LISP is supplied if required. This package, produced by OWL Computers, appears to be well thought out and reasonably documented, though perhaps a little difficult to follow for the beginner—the program is adapted from a version written for the Apple computer.

FLOATING POINT EXTENSION

The F.P.E. allows accuracy of $9\frac{1}{2}$ digits in a range from 10^{-38} to 10^{+38} , approximately. All the standard integer BASIC statements have F.P. equivalents—mostly using the prefix F. For instance, FINPUT is as for INPUT, but uses a floating point variable only. In this way, the F.P.E. is a true add-on and is not fully integrated into the BASIC on the machine.

SCREEN EDITOR

This program allows the computer to be used, effectively, as a word-processor. Files containing letters or documents may be input from the keyboard and printed out on a hard-copy printer. Normally, a word-processor would organise words on the screen to prevent their being split from one line to the next. This does not appear to be the case with the screen editor, though upon print-out the words are organised so that no splits occur, and the text can be justified. The absence of “arrow keys” to move the cursor around the screen is a drawback from the operator point of view. He has to memorise which of the keys perform which cursor movement commands—though the keys are arranged in a logical manner on the keyboard.

Special letters are left in the text to signal particular printing modes, such as justification, given line-widths and the centering of a heading on the page. Strings may be located, deleted, and changed as normal. Only one character may be inserted after the cursor for each use of the insert command, which is rather limiting as far as speed is concerned. Text is entered one page at a time, and the operator must not exceed this limit, or an overflow message occurs. A page is defined as a full screen.

The version of the editor supplied with the machine for review appeared rather combersome and slow to use compared with other packages, but this may well have been due to the rather scant and embryonic documentation accompanying the program.

Science of Cambridge can provide software and hardware which will interface the Acorn system with Prestel and Teletext

LISP is a language which is orientated towards the processing of strings and lists of characters as opposed to scientific and numerical calculations, though calculations are possible. Complex data structures are easy to construct, and the language can process and act upon complex “Boolean” or logical conditions. This type of programming is suitable for highly interactive routines using human language for communication. The computer can easily be made to act as if it understands syntax and grammar. As an example, as a demonstration of LISP’s capabilities, OWL computers have a program called DOCTOR which pretends to be your psychiatrist, and asks personal questions in an English conversation—could become addictive!

CONCLUSION

The system is modular, as mentioned before, and appears to be well conceived from a hardware point of view, if rather expensive. The software is still in development, but is quite wide. My version only ran a converted colour monitor, and it would be interesting to see the resolution through the encoder and UHF modulator on a domestic TV.

The exact market place of the machine is difficult to assess. Medium-sized business applications would be difficult with such small disk space, and the system would have to be cheaper for the hobbyist to buy it. That leaves Education and hardware control. Both of these would surely benefit from the modularity and Input/Output expansions available. ★

PE POPULAR PROJECTS... CONTENTS

MOTORING

SOLID STATE CAR INSTRUMENTS by Michael Tooley B.A. and David Whitfield B.A., M.Sc.	
1. BATTERY VOLTAGE INDICATOR	2
2. REV COUNTER	7
3. AMMETER	10
4. ENGINE TEMPERATURE	13
5. DWELL METER	16
HAZARD WARNING AND CASCADING	18
HEADLIGHT WARNING by P. G. Wagstaff	21
AUTOMATIC CAR AERIAL by S. M. Bennett	24

HOUSEHOLD

DIGITAL TEMPERATURE CONTROLLER by D. Coultts and P. McAllister	27
ULTRASONIC BURGLAR ALARM by G. Davies	32
HOME FREEZER ALARM by P. E. Chaplin	37

PHOTOGRAPHIC

PE DIAMATIC by J. R. Ames B.Sc., and W. L. Blyth B.Sc.	40
DIGITAL EXPOSURE TIMER by John Becker	55

MUSICAL EFFECTS

SMOOTH FUZZ by D. S. Gibbs and I. M. Shaw C. Eng. M.I.E.E.	62
PHASER by D. S. Gibbs and I. M. Shaw C. Eng. M.I.E.E.	65
GUITAR SOUND MULTIPROCESSOR by Dr. M. Sawicki and A. Kowalewski B.Sc.	69

RADIO CONTROL

R. C. FAILSAFE by Tony Jenkins	85
--------------------------------	----

TEST GEAR

WAVEFORM GENERATOR by Michael Tooley B.A. and David Whitfield B.A., M.Sc.	88
PULSE GENERATOR by Michael Tooley B.A. and David Whitfield B.A., M.Sc.	93

A PRACTICAL ELECTRONICS Publication...

With electronics playing such an important role in every aspect of modern living PE have pleasure in presenting the pick of some of its most popular projects in this 96-page book. Two of these projects are completely new, the remainder are as originally published in PE save for the incorporation of certain designer approved amendments or corrections.

Our new book *PE Popular Projects* is now on sale at newsagents and component stores; the contents of this book are shown above. The book costs £1.25 from retail outlets and is also available for £1.50, UK post paid or £1.80, overseas surface post paid, from Post Sales Department (PE Popular Projects), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

Strictly Instrumental

by K. Lenton-Smith

A problem that can confront the electronic musician is fitting a further amplifier and speaker system to an existing installation. Though apparently simply in theory, the task can be complicated if the instrument is not provided with a pre-amplified output and the end product is supplied only to the speaker terminals.

MATCHED PAIR

The practical difficulty is matching the main speaker signal to a further amplifier. It is possible, of course, to find a pre-amplified source somewhere in the instrument's circuitry but the main speaker signal can be useful in other respects: for the moment we will assume that the speaker signal has to be the starting point.

Another speaker in parallel would seem to be the simplest solution, but would not only result in a mismatch but probably endanger the output transistors. Placing a (say) 50k potentiometer across the main speaker and feeding the extension amplifier from its slider will give results of sorts but losses in tonal quality will perhaps be unacceptable.

Ruling that out, we try a step-up transformer: here the primary can act as a dummy load if the main speaker is to be switched out. Although this will give better results than using a simple pot., there will still be losses in tonal quality.

UNCOMMON

In the early days of the transistor, available types were of low gain, high leakage and very restricted in their cut-off frequency. It was not unusual to have to resort to *common base* configuration in order to handle even the i.f. of a suphet receiver—perhaps operating at 470kHz. Today's device is a totally different matter and alpha cut-off is no problem anyway where audio frequencies are concerned. Where common (or grounded) base is employed, the stage will handle low impedance inputs and provide a high impedance output with voltage gain—which is precisely what we are looking for in this instance. The input signal is fed to the emitter, the base ground to a.c. but biased as usual and the signal taken from the collector. A suggested circuit is shown in Fig. 1.

Power for this stage can be derived from the extension amplifier, using a suitable

series resistor to ensure that the Zener diode's dissipation is within bounds. If the constructor intends to use the extension system for a doppler-effect speaker, a dummy load must be presented to the main amplifier if switching is envisaged.

LIMITER

The main speaker signal is useful as the source for driving a spring unit, so both this drive and the signal for the common base

amplifier can come from the same point. Assuming that one side of the main speaker signal is earthed, Fig. 2 shows a suitable system that was used by Hammond in their M-100 series instruments. An appropriate lamp to use is 6V 0.36W, where the filament has a d.c. resistance of some 14Ω. It acts as the volume limiter and is only likely to glow on loud passages. The reverberation spring can be driven directly as indicated in Fig. 2 or this same signal can be reduced resistively and fed to the reverberation drive amplifier if it is already incorporated in the spring unit.

With a little care, the pre-amplified signal from the spring unit can be mixed with the output from the common base stage so that the extension amplifier handles both signals. It is a wise precaution to refer to the instrument's service manual to ensure that the main speaker is not provided with a push-pull, centre tapped to earth, signal. If this is the case, suitable resistors will have to be inserted after the limiter to avoid losing half of the signal because of the common earth between the main and extension amplifiers.

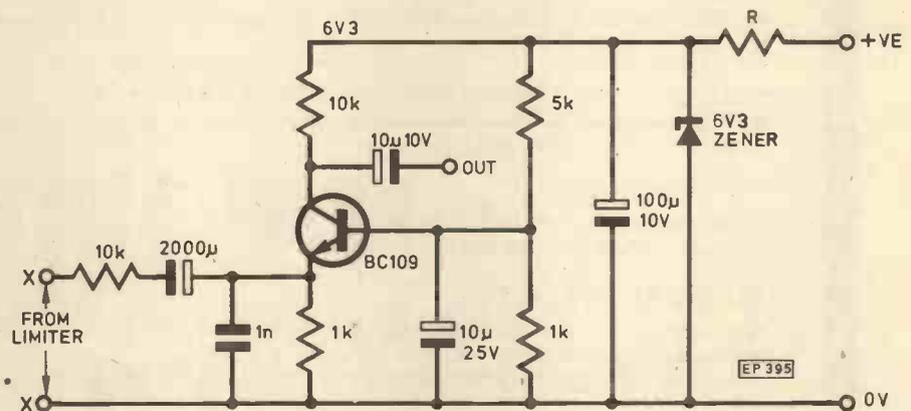


Fig. 1. Common Base Stage

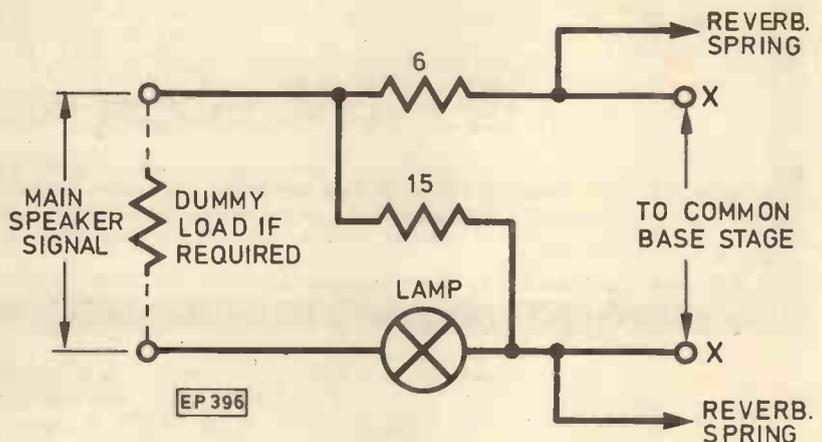


Fig. 2. Limiter

MONITOR

Whilst dealing with practical aspects, the musician reader will hardly need reminding that recording at the keyboard can be problematical at the best of times. However, nothing is more annoying than having to use a pre-amplified tape recorder that has to be carted to the hi-fi system (possibly in another room?) to check each result. Some organs can be used to play back tape—though this may have to be monophonic—but headphone facilities are ideal. In order to preserve the musical train

of thought, the simple circuitry of Fig. 3 may be found useful.

This can be built in mono or stereo form on the smallest stripboard available (both amplifiers being identical) and possibly mounted somewhere inside the recorder, borrowing power from that source. The nominal 10V is not critical but allows small electrolytics to be used: the series resistor must again be chosen to limit the zener diode's dissipation. Quiescent current is some 2mA and the quality of reproduction is excellent for this purpose. Two components call for comment: the 1M Ω feedback

resistor controls volume and can be varied to suit individual taste, whilst the 330K inverting input resistor may require amendment according to the tape recorder's output signal.

Headphones with mylar diaphragms can be extremely sensitive and, should there be any tendency to overload, a series resistor—say 100 Ω —in each output lead of this type of phone will overcome the problem. A simple but effective system of checking musical efforts quickly is a great help in getting the required result—eventually!


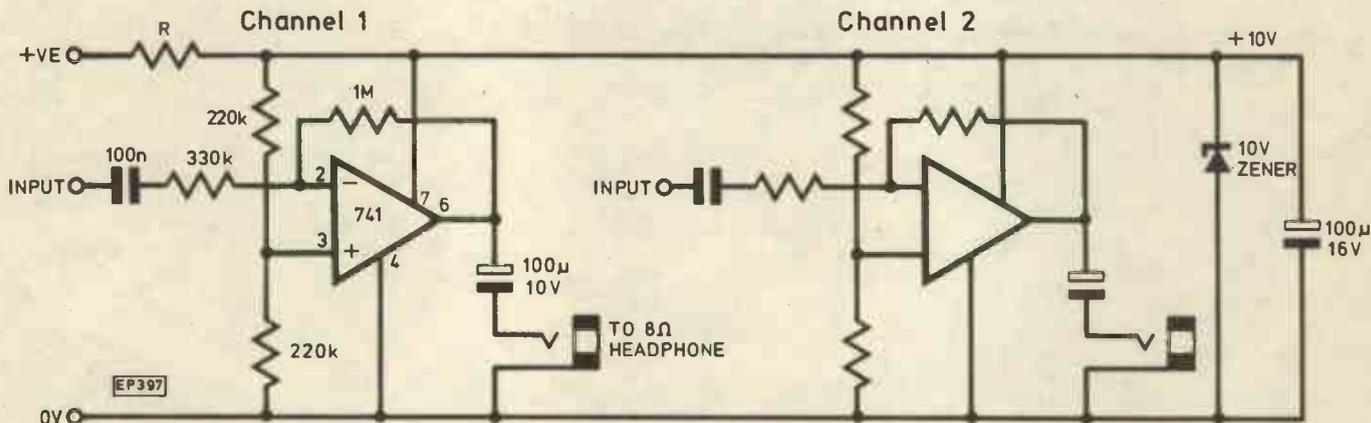


Fig. 3. Stereo Headphone Amplifier

**I.C.
REMOVAL
TOOLS**

**IT'S NOT
TOO
LATE!**

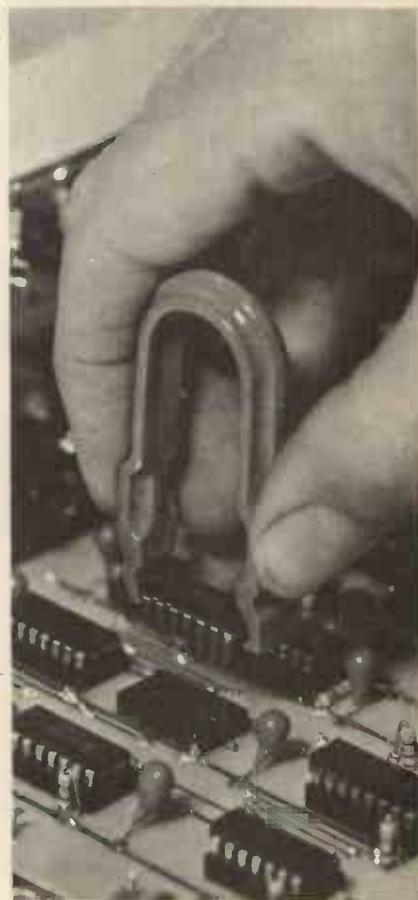

Last October we gave you a free I.C. removal tool, and we still have a limited number available for those of you who missed out last time.

All you need to do is send a postal order for thirty pence (made payable to IPC Magazines) and a stamped addressed envelope to:

Practical Electronics (I.C. Removal Tool), Westover House, West Quay Road, Poole, Dorset BH15 1JG.

(Please do not enclose any other correspondence.)

'TUSCAN' FROM TRANSAM



Take a step up to your next Computer!

THE CONCEPT

How many ways are there to build an S100 system? Not many, and all expensive. TUSCAN changes all that.

Five S100 boards on one single board — just for starters. Plus five extra slots for future expansion.

What a combination! Z80 and S100 with the TRANSAM total package of system and applications software.

How do we do it? Our prices start at £195 and you can build up in easy stages to a fully CP/M compatible disc based system. Something to think about!

THE HARDWARE

The first Z80 single board computer with integral S100 expansion. British designed to the new IEEE (8 BIT) S100 specification, the TUSCAN offers total system flexibility. A flexibility available now.

The board holds the equivalent of a Z80 cpu card, 8k ram, 8k rom video and I/O cards with 5 spare S100 expansion slots and offers a price/performance ratio which is hard to beat.

Just compare our price with a commercial S100 ten slot motherboard with this specification.

THE SOFTWARE

TUSCAN offers the user the choice of system monitor, editor, resident 8k basic, resident Pascal compiler or full CP/M disk operating system. All options are upwards

compatible and fully supported with applications software. Both 5¼" and 8" drives are supported in double density.

THE PACKAGE

TUSCAN is available in kit form or assembled. With several hardware and software options to suit your requirements and budget. Attractive desk top case also available holds 2 x 5¼" Drives.

TRANSAM

NOBODY DOES IT BETTER!

Send to Transam Components Ltd., 12 Chapel Street, London NW1

I am interested in the TUSCAN Z80 based single board computer with S100 expansion and enclose a S.A.E. for further details.

Name _____

Address _____

Telephone _____

NEXT MONTH...

DISCO DESK

A control desk for high power, high fidelity mobile sound systems that can equally be used for permanent installation. It can be readily modified for recording and broadcasting in a closed circuit such as hospital radio.



*Also in
this
issue...*

PROGRAMMABLE SOUND GENERATOR

An exciting computer sound unit based on the AY-3-8912 PSG. Full waveform, envelope and noise capability for your UK101.

Bombs, bells, creaking doors, banshees that wail like out of tune violins, the fierce organ playing of Count Dracula in the chapel at midnight, laser beams, hyperspace travel, tanks and field guns... You'll be interfacing your imagination to the real world!

Plus


PE TELETEXT Pt.2

PE MAGNUM Pt.2

PRACTICAL

ELECTRONICS

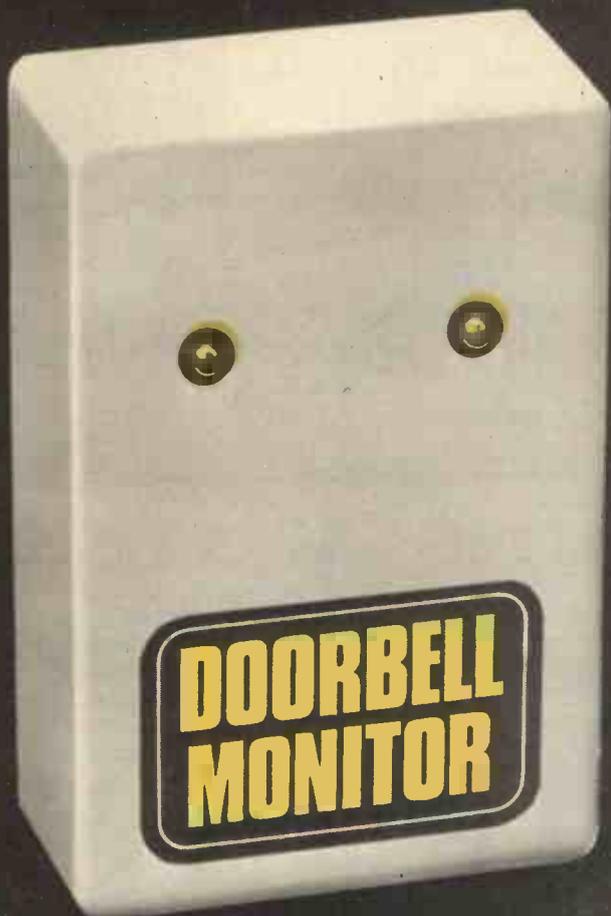OUR SEPTEMBER ISSUE WILL BE ON SALE SATURDAY 16 AUGUST 1980



J.A. Barrow describes— An indicator which gives a silent flashing display to the hard of hearing or in noisy environments and logs calls in your absence

HERE is a useful gadget for the deaf, the hard of hearing, or, the enthusiast who likes to play music very loudly! Primarily designed to overcome the problem of not hearing someone at the door by providing a visual indication, it has the additional feature of a memory, which indicates whether you missed a caller while you were out.

The complete unit can be made very compact as it can be simply connected to the existing bell-push wires.

CIRCUIT

IC1a and b, R3, R4 and C3 in Fig. 1 form a low frequency oscillator which is switched on when the threshold voltage at pin 2/IC1a is exceeded. The output is connected to TR1 via R5 which drives the l.e.d.s D3 and D4. The power for the circuit is from the bell battery.

Consider the circuit in the following state with C2 fully charged and pin 4/IC1d at logic '1'. A logic '0' at pin 2/IC1a ensures the oscillator is off. Pin 11/IC1b is at logic '0' so no l.e.d.s are lit. Shorting point 'A' to 'B' causes C2 to discharge rapidly through D2, so when the power returns to the circuit (i.e. when the bell push is released) C2 starts to charge via R2 causing a logic '1' to be present at pin 2/IC1a—the oscillator then functions and the l.e.d.s flash for a period determined by R2, C2 (about 30 seconds with values shown). During oscillations pin 3/IC1a goes to a logic '0' causing the latch (gates c and d) to change state. Pin 4/IC1d becomes logic '0'. This state remains until S1 is pressed when pin 11/IC1b then becomes a logic '1' and the l.e.d.s light, indicating that the oscillator has been activated. While the switch is held depressed, capacitor C4 will charge via R8 and the logic level at pin 6/IC1d will change to a '0' after about 2 seconds, resetting the latch and cancelling the lit l.e.d.s.

ALTERNATIVE SUPPLY

The circuit was designed for use with battery operated bells, but use with a.c. types up to a maximum of 10V r.m.s. is possible using additional circuitry shown in Fig. 1.

Diode D1 prevents circuit damage if input connections are reversed during installation, in which case the bell will ring continually.

CONSTRUCTION

The components are mounted on 0.1 in Veroboard as shown (in Fig. 2) which in turn is mounted onto the lid of a small plastic box. Two holes were drilled in the lid to form a

COMPONENTS

Resistors

R1	1k 0.5W
R2	3M6
R3	56k
R4	2M
R5	10k
R6	100k
R7*	180
R8	10M
R9*	

All resistors 0.25W carbon except where otherwise stated

*Selected for 6V operation

Capacitors

C1	100 μ 16V elect
C2	10 μ tantalum 16V
C3	100n polyester
C4	220n polyester

Semiconductors

TR1	BC 109
IC1	4093
D1	1N4006
D2	OA200
D3 } D4 }	Hi brightness l.e.d.s

Miscellaneous

S1 D.p.d.t. push switch (miniature) Veroboard (0.1in) 3in x 2.2in REC1 — 100 mA bridge rectifier, Plastic box.

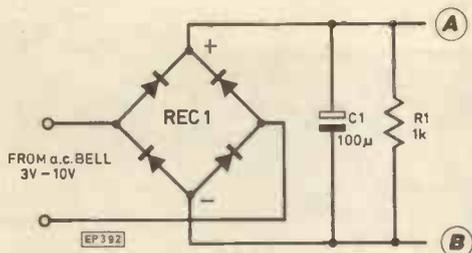


Fig. 1. If used with a battery operated bell connect A and B to the existing bell-push switch wires. For a.c. bells (3-10V) connect the rectifier circuit as shown.


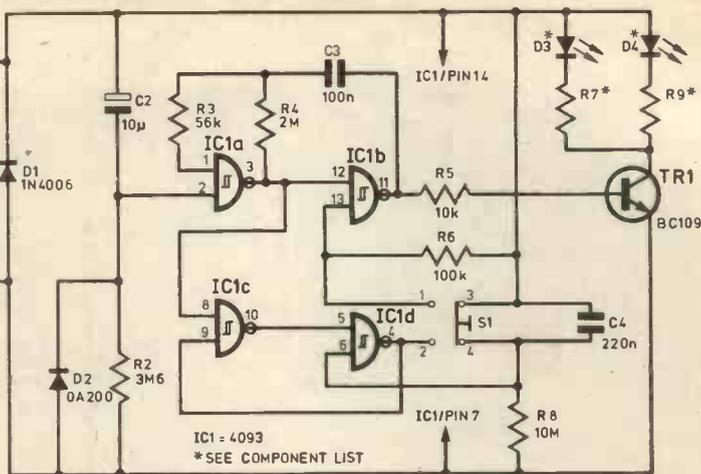


Fig. 2. (Below) Veroboard layout for monitor

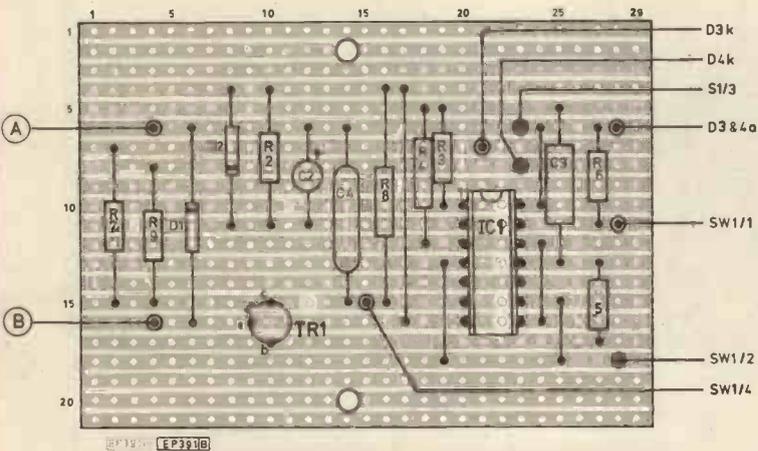

'key-hole', which enabled the unit to be fitted on a wall with one round-headed screw—the keyhole locating over the head of the screw.

CHECKING

After making connections to the bell-push wires, press the switch and release. L.e.d.s should flash for about 30 seconds then extinguish. Press S1 and hold, the l.e.d.s should light for about 2 seconds then extinguish. Press S1 again and the l.e.d.s should remain off.

The unit should be sited, of course, where it can be easily seen—perhaps close to the television or stereo.

In normal operation it looks after itself—switching itself off 30 seconds or so after the bell push was pressed. When, however, the memory facility is required, the push button on the unit should be depressed until the l.e.d.s extinguish before going out. Then, on your return, press the button again—if the l.e.d.s do not light, then visitors did not call in your absence. ★

POINTS ARISING


SPLIT-PHASE TREMOLO (May 1980)

- 1) The bottom end of VR1 should go to earth (as defined by the centre point between the power supply lines) and not to the -6V supply.
- 2) The 'In' and 'Out' positions on switch S1, as marked on the circuit diagram, should be interchanged.
- 3) The three jack sockets (JK1, 2 and 3) should all have their screens connected to earth, and not to the -6V supply.

Either R10 or R13 may be replaced by a preset variable resistor of value around 4k7. The setting of this variable resistor should be so as to cause the signal amplitude across it to be the same as the signal amplitude across the remaining fixed resistor. Omission of this adjustment may cause the extremely discerning listener to observe that the modulation depths on the two channels is not quite identical. The difference in modulation depths is, of course, caused by the emitter load having a signal generated across it by virtue of the base current which flows through it. Adjustment of the preset variable resistor as described above results in the cancellation of this effect.

STARLITE 4000

NEW!

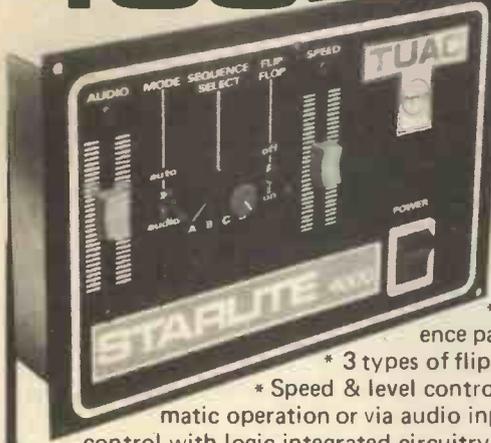

ONLY
£55.00

Size 9" x 6" x 3"
Weight 1.2 kg

- * 4 channel 1000W each
- * 4 basic sequence pattern selections
- * 3 types of flip-flop selections
- * Speed & level control sliders
- * Automatic operation or via audio input
- * Full wave-control with logic integrated circuitry
- * Fully suppressed and fused
- * Superb TUAC quality and reliability


VOYAGER STEREO MIXER



The **NEW**
Superior Stereo
Mixer at an incredibly low
price ONLY **£159.00.**

- * 2 Mag deck channels + tone controls
- * Aux channel complete with tone controls
- * Mic channel with tone controls
- * Full autofade
- * Full headphone/Q facility
- * Precision L.E.D. VU output/Q facility
- * Size 25" x 6" x 3"

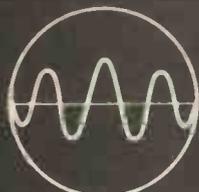Send for our **FREE 28 page catalogue.** Please enclose a stamp.




TUAC

TUAC Ltd., 119 Charlmont Road, SW17.
Tel: 01-672 3137/9080
PRICE INCLUDES VAT. P+P FREE

TO ORDER BY POST. Make cheques/P.O.s payable to TUAC LTD. or quote Access/Barclaycard No. and post to TUAC LTD. 119 Charlmont Road, London SW17 9AB. We accept telephone orders from Access/Barclaycard Holders. Phone 01-672 9080.

TUAC MAIN DISTRIBUTORS

- Birmingham, George Matthews, 85/87 Hurst Street, (Tel: 622 1941).
- Cheshire, Cookies Disco Centre, 126 West Street, Crewe, (Tel: 0270 214739).
- London, Garland Bros., Deptford Broadway, (Tel: 01-692 4412).
- London, Session Music, 163 Mitcham Road, Tooting, SW17, (Tel: 01-672 3413) Mon-Sat 10am to 5.30pm. Closed Wed.
- Kingston, ABC Music, 56 Surbiton Road, Kingston, Surrey, (Tel: 01-546 9877).
- Luton, Luton Disco Centre, 75 Wellington Street, (Tel: 411733).
- Manchester, A1 Music, 88 Oxford Street, (Tel: 236 0340).
- Middlesborough, Salcojen, 43 Bo.ugh Road, (Tel: 242851).
- Watford, Component Centre, 7 Langley Road, (Tel: 45335).

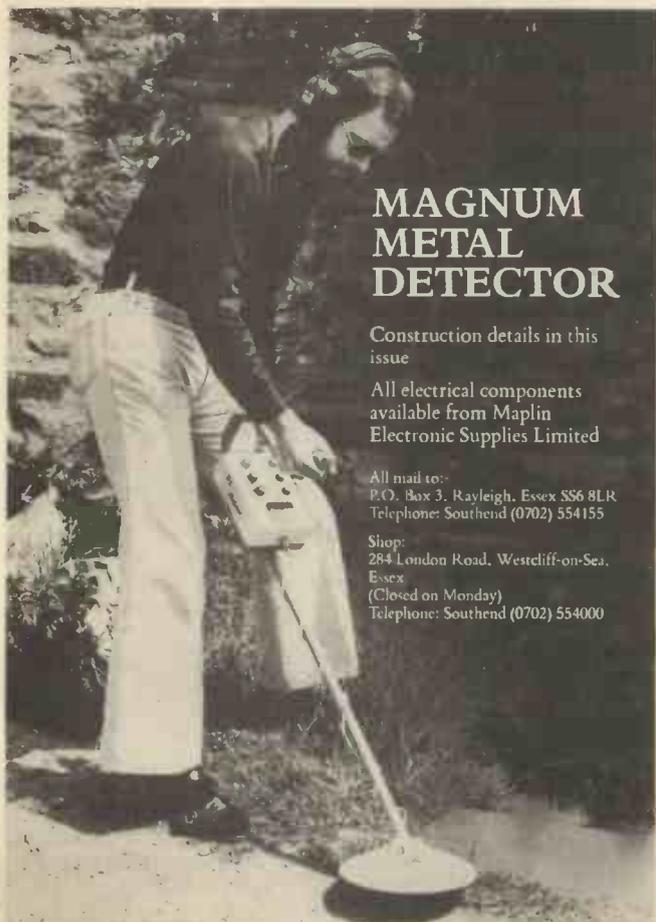

MAGNUM METAL DETECTOR

Construction details in this issue

All electrical components available from Maplin Electronic Supplies Limited

All mail to:
P.O. Box 3, Rayleigh, Essex SS6 8LR
Telephone: Southend (0702) 554155

Shop:
284 London Road, Westcliff-on-Sea, Essex
(Closed on Monday)
Telephone: Southend (0702) 554000

<p>MULLARD CAPACITORS Special purchase of factory clearance capacitors enables us to offer: C290 Polysters (Liquorice Allsorts) at £2.50 for 100 mixed. And Miniature Electrolytics at £1.50 for 100 mixed. Pack of each only £3. These consist of spillages floor sweepings cosmetic imperfects etc. As we have no time to sort them they are magnificent value for the constructor.</p>	<p>MINIATURE MAINS TRANSFORMERS Top quality. Split bobbin construction will give 4.5V-0-4.5V at 250 MA 1 1/2" x 1 1/2" x 1 1/2". all sorts of uses: ONLY 90p. 3 for £2.20. 2,200 µf 40V Radial 1 1/2" x 2" 60p. 3 for £1-50 1,000 µf 100V Radial 1 1/2" x 2" ONLY 70p. 3 for £1-50.</p>
<p>Don't Let Your Environment Dehydrate You! Buy our Honeywell Humidity Controller. Membrane actuated, very sensitive. 1/2" shaft, 250V, 3.75A Contacts. Ideal for greenhouses, centrally heated homes, offices etc. Build your own humidifiers or alarms. Fraction of original cost 90p ea. 3 for £2.</p>	<p>20mm ANTI SURGE FUSES 630mA, 800mA, 1A, 1-24A, 1-6A, 2A, 2-5A, 3-15A, 12 of one type £1.12 of each type £7.100 of one type £7.100 of each type £48.</p>
<p>20 ASSORTED ZENER DIODES 1 watt and 400MW. £1.50</p> <p>100 MIXED DIODES Includes: Zener, power, bridge, germanium, silicon etc. All full spec. £4.95 0-2" LEDs with 2 piece clips. Red 4 for 50p. Green and Yellow 4 for 60p.</p>	<p>TRANSISTOR PACKS 100. Full spec, new and marked. Includes BC148, BC184L, MED412, BF274, BC154 etc. etc. £4.95 200 as above and includes AC128, 2N3055, 8PY50, BC131, BF200 etc. £8.95 Buy bulk and save money, these packs are worth at least double.</p>
<p>ULTRASONIC TRANSDUCERS Transmitter and receiver 40 kHz 14 mm dia. £3-25 pair.</p>	<p>P/B SWITCH BANKS These cost a fortune! Were made for various music centres. Includes independent and interdependent latching types multi pole etc. Can be modified. Can't be repaired. 3 Banks for £1. Knobs for P/B Switches. Fit 3/8" mm sq. shaft. 10 for £1. Chrome or Spun Aluminium Finish.</p>
<p>MINIATURE REED SWITCHES We are the cheapest! 12 for £1.00 100 for £4.20</p>	<p>BULK BARGAINS, STOCK UP FOR SUMMER 300 mixed 1/2 & 1/2 watt resistors £1.50 150 mixed 1 & 2 watt resistors £1.50 300 mixed capacitors, modern, most types £3.75 100 mixed ceramic end plate caps £1.20 400 mixed film resistors £2.95 100 mixed polystyrene caps £2.20 25 pots and presets £1.50 25 presets, skaton etc. £1.20 20 VDRs and thermistors £1.20 100 Hi-wattage resistors wirewound etc. £2.20 100 electrolytics, nice values £2.20 300 printed circuit resistors £1 300 printed circuit components £1.50</p>
<p>G.E.C. UHF TRANSISTOR TV TUNERS Rotary type with slow motion drive. leads and aerial socket £1.50 3 for £3.50 "for G.E.C. "2010" series etc."</p>	<p>100K MINIATURE THUMBWHEEL SLIDER POTS Very neat. can be banked side by side. Ideal for v. cap tuning, graphic equalisers etc. 10 for £1</p>
<p>DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS Includes 150 sq. ins. copper clad F/G board. 1 lb ferric chloride 1 delo etch resist pen. Abrasive cleaner. Etch tray plus instructions. Special Price £4.95 1 lb FE. C1. To mil spec. £1.25 5 lb FE. C1. To mil spec. £5.00 150 sq. in. Single sided board £2.00 150 sq. in. Double sided board £3.00</p>	<p>MINIATURE LEVEL/BATT. METERS 200µA F.S.D. as fitted to many cassette recorders 80p</p>

50p P & P on all above items. Cheque or P.D. with order to:

SENTINEL SUPPLY, DEPT. P.E.
149A BROOKMILL RD., DEPTFORD, LONDON, SE8

Semiconductor UPDATE...

FEATURING 7910 UAA1003 MN9106

R. W. Coles

DESERT ISLAND CHIPS

If like me, you feel that some things are better left as they are, unimproved by generous helpings of electronic technology, then your interest in my first two devices this month may be tinged with something of a sense of foreboding.

The Stylophone was tolerable, no worse in fact than the kids tin drums and xylophones which preceded it, I even manage a wry smile when greeted by a perky rendition of "Colonel Bogey" from one of those dreadful musical door bells. I do get just a little peeved, though, when forced into a corner with one of those "Space Invaders" games which makes continuous rude noises while I'm trying to enjoy my pint, but at least I can leave them behind in the pub.

The thing that worries me about the new 7910 series of six integrated-circuit-music-makers is that they are so easy to use and so cheap that I have a vision of our homes being inundated with musical food mixers, vacuum cleaners, clocks, tooth brushes, and biscuit tins in the not too distant future.

The 7910 series can provide a tune for every occasion including "Home on the Range", "Mary had a little Lamb" and "Greensleeves", and four of the chips can also imitate door chimes and produce bleeping alarm noises. Two specials in the range are dedicated for clock applications, producing ersatz "Westminster Chimes" no less.

The thing which sets these chips apart from the microprocessor door bells of yesteryear is the fact that they (a) come in diddy 16 pin DIP packages (b) run from a single 1.5V battery, with a standby drain of typically 2 micro amps and (c) they are selling; even in small quantities, at less than £2 each.

The secret seems to be that the 7910 series is *not* based on a true microprocessor architecture but on a dedicated design with no "fat". The tunes are produced by an on chip combo which consists of an oscillator, two envelope generators, an output pre-amp and a collection of ROMs. The ROMs define the tunes, and custom programming is therefore possible at the mask level. The melody ROM, twelve bits wide and 128 words deep, can store 128 notes or rests, the tempo ROM provides cadences from prestissimo to largo, and the control ROM welds the whole thing together by keeping track of start addresses, tune selections, and sequence repetitions.

The pre-amp provides at least 150

microamps of base current for an external pair of transistors in a push-pull configuration, but apart from those devices, only a few cheap passives and a pen cell are all you need to drive you and your friends crazy.

The 7910 series are only available in the U.S.A. at the moment, from Epson America Inc., (who I've never heard of). If you can't wait, they live at 23844 Hawthorne Blvd., Torrance, CA 90505.

SPEAKING CLOCK

As if the threat of musical biscuit tins were not enough, it seems we are also faced with the prospect of alarm clocks which rouse us from our slumbers with a spoken announcement of the time, no doubt delivered in a supercilious tone of "voice". This terrifying prospect is brought to us courtesy of ITT Semiconductors, in the shape of a forty pin NMOS integrated circuit coded UAA1003.

All those pins are needed because the new device is designed to be connected to the seven-segment multiplexed display outputs of your favourite digital clock chip in parallel with the display LEDs. Yes, that's right, it not only speaks, it understands digital clock-ese too.

The UAA1003 can speak up to 25 separate words; and can be programmed to string these in any sequence to amaze and delight your friends. Each word consists of a number of staircase shaped pulses lasting 10 milliseconds and produced via an on-chip 7 bit digital-to-analogue converter to give 128 possible amplitude levels.

One problem though, they haven't taught the UAA1003 to speak English yet, only French and German, so unless you relish the thought of being awakened by "Bonjour. Il est sept heures et demi" (Followed no doubt by a quick burst of "Mary had a little Lamb" from the Teasmaid), you will have to wait a few weeks before "modding" your trusty alarm clock. Your alarm clock should have no trouble powering the UAA1003 when it arrives though, it only needs five millamps at 5 volts.

Personally I am working on suitable countermeasures. In my wardrobe there is a well used hob-nail boot which I occasionally fling with unerring accuracy at the frisky cats who sometimes frequent my garden at night. I wonder if the UAA1003 could stand a direct hit from *that!*

NOVOL CHIP

I have mentioned the ingenious NOVOL devices before in this column. They are

made by Plessey (yes they really are *British*) and their strength lies in the clever combination of high speed but volatile CMOS memory and slower but non-volatile MNOS latches. The mixture yields memory devices which can be written-to and read-from like any other memory part in normal operation, with the added advantage that the contents of the memory can be saved almost indefinitely, even without power, after the application of a short SAVE pulse to effect a transfer to the MNOS section. This technology is invaluable where the loss of data due to power loss must be avoided and the data must also be easily changed during normal operation with power applied.

When power is reapplied to a NOVOL device, the data stored in the long-term MNOS latches can be recalled by applying a five micro second pulse to a RECALL input.

The only reservations I have had about NOVOL in the past have concerned the limited number of "save" cycles possible (about a million), and the fact that only small arrays, such as four bit latches for example, were available.


Well, the first problem is a fact of life with MNOS, but I withdraw my second reservation now that I have seen data on the MN9106/7/8 series of NOVOL counter chips. The MN9106 is a six decade up-counter complete with a multiplexed seven segment display driver and overflow logic, capable of counting at up to 200KHz. The 25 bits of count data (6 x 4 bits and 1 bit for overflow status) can be stored in an MNOS array by application of a 10 millisecond SAVE pulse, and recalled rapidly when required so that the count can continue from where it had stopped, when the power failed for example.

The other devices in the series have certain decades changed into divide by six counters to provide a timer function. The MN9107 counts 99 hours, 59 minutes, 59 seconds and the MN9108 counts 9999 hours 59 minutes (or 9999 minutes 59 seconds).

The nonvolatility of these counters makes them suitable for applications where in the past only electro-mechanical gadgets could be used, things like car odometers, hours-run indicators and production line parts counting could all benefit from NOVOL technology.

The MN9106 series all operate from a 12 volt supply, can be interfaced to CMOS or TTL logic, and come in 24 pin packages.

Hands off.

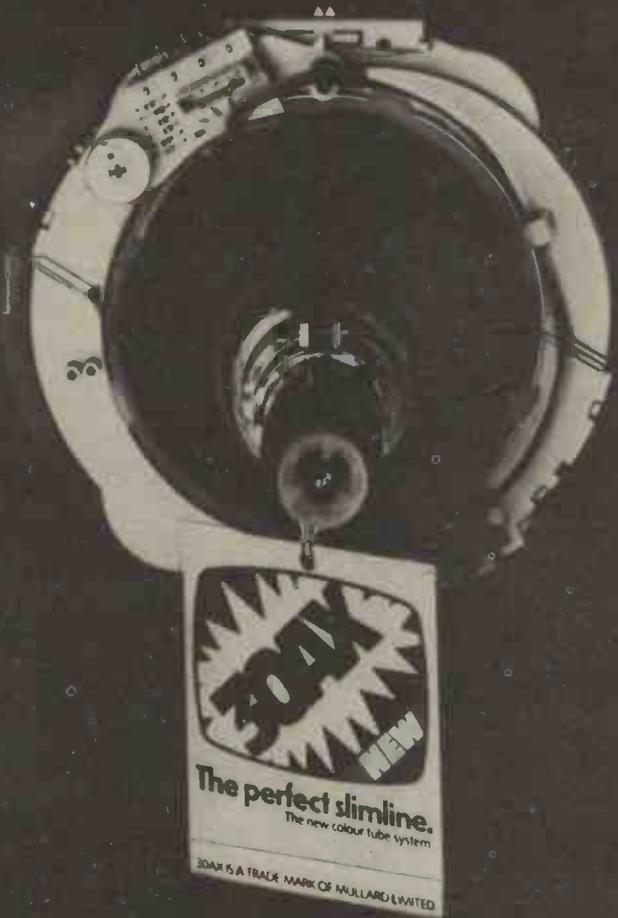

We mean it.

The new 30AX colour tube system from Mullard doesn't need innumerable twists and turns of a screw-driver to set it up.

It needs no adjustments at all. Because every one has been 'designed out'. Every tube that leaves our factory is completely pre-adjusted by us. Leaving only the turn of one screw to affix or remove the coil.

No dynamic convergence adjustments.

No colour purity adjustments.

And no raster orientation adjustment.

As for what it has to offer, the 30AX's focus is sharper and its definition greatly improved.

Its in-line guns and specially built coil provide the best picture shape yet.

And rest assured it'll stay that way. In a slim

110° package that trims about 3" off conventional 22" 90° TV cabinet depths.

Some features of the 30AX however, are a little more established.

Like its excellent colour registration.

High brightness. Soft flash protection. Fast warm-up. And of course, greater overall reliability. This is the new 30AX colour tube system.

If you'd like more information about it simply write to us here at Department MCG, Mullard Limited, Mullard House, Torrington Place, London, WC1E 7HD.

30AX is a trademark of Mullard Ltd.



Mullard
30AX. The perfect slimline.

Electrochemistry

and the instrumentation it needs

A.T. Kuhn M.A. DPhil.

WHAT IS electrochemistry? And whatever it is, why is chemistry rearing its ugly head in a magazine devoted to electronics? Taking the quick answers to these questions, we can say first that electrochemistry is that branch of science which deals with the frontiers between electricity and chemistry. Just how important this little branch of science is, one must judge for oneself. Suffice to say that it underlies the working of batteries, and accumulators; it provides the explanation of corrosion, and at the same time suggests how we might combat it. It is the means used for production of all the world's aluminium, much of its magnesium, all of its chlorine and many other vital chemicals besides. Electroplating and anodising, electrophoretic paint deposition on cars or refrigerators, the monitoring of medical parameters, prevention of damp in old buildings by electro-osmotic action—one could go on and on!

As for the second question, the Editor has decided to run a series of projects (*not* consecutively) which will encompass the complete range of the major instruments required to study or demonstrate this important discipline, either in research laboratories or in colleges or secondary schools. These instruments will be specified to the full professional level required for research at the highest level. In many cases, they will not be cheap to build—but then their commercial counterparts with comparable performance would cost many times the same amount. In many cases too, options will be shown by means of which the builder can construct a less expensive machine, to be upgraded at a later date when funds permit.

THE SCOPE OF ELECTROCHEMISTRY

One of the best-known electrochemists today, Professor J. O'M. Bockris, of Texas, has shown how the subject can be divided into "Ionics" and "Electrodics". The first term relates to events taking place in solutions of conducting media, for example salts or acids dissolved in water, while the second relates to the interface between a metal or other conductor, and the solution in which it is immersed.

IONICS

Far and away the most important measurement we make in relation to water and other species dissolved in it, is pH, or acidity. To a first approximation, we can define this as:

$$\text{pH} = -\log [\text{H}^+]$$

and in the laboratory, in the food, drug or chemical industry, we are constantly concerned with the acidity of whatever we are making, for not only must the value be *right* but also we can use it as a guide to all sorts of other things happening. But then the biologist, the gardener or soil scientist, the aquarist, the doctor and vet, are all concerned with the application of this same term to their own discipline. There are many ways in which we can measure this quantity. But the most commonly used one is to use a pH *electrode*, and, having first calibrated it against solutions whose pH is known, we can measure pH by measuring the potential difference generated between this electrode and another one, the response of which is not affected by the pH of a solution. This voltage must be measured with a circuit of moderately

high impedance, of the order of 10^8 Ohms or so, and this requires special design. Formerly this was done with electrometer valves, but now we have FET op. amps. The technique of pH measurement with an electrode is some 40 years old or so. But in the last decade a staggering advance has been made, in that we now have a series of *Ion-specific* Electrodes which can be used in very much the same way, to measure the concentrations of Cl^- , F^- or Na^+ in a solution.


Numerous ion-selective electrodes are now available. Their number increases every year. There cannot be an easier way of measuring the calcium levels in milk or the amount of nitrate in drinking water than by using one of these new electrodes. The principles on which they operate are very similar to the glass electrodes used to measure pH, and both devices follow more or less closely the relationship known as Nernst's Equation:

$$E = E_0 + \frac{2.3RT}{nF} \log [\text{Cl}^-] \quad (1)$$

where E_0 is a constant, and E is the measured voltage. The other terms relate to the concentrations of the ions we wish to measure. In practical terms, these electrodes are still a little more difficult to use than the pH electrodes which preceded them. The actual slope of the relationship between $\log (X)$, where X is a species and the measured voltage is not always that suggested by equation (1), where the factor


$$\frac{2.3RT}{nF} = 0.059\text{V at room temperature.}$$

but can deviate some way from it. Therefore these instruments must incorporate variable slope controls.

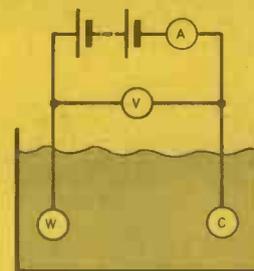

EQ374

Fig. 1. Two electrode system

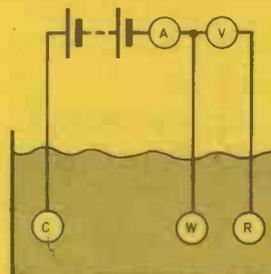

EQ375

Fig. 2. Three electrode system showing working counter, and reference electrodes

From the measurement of pH or pX, it is only a step to an instrument which uses this information to actuate some means for controlling the same parameter. This is sometimes known as a *pH stat* or auto-titrator and the commonest use is perhaps in the treatment of effluent discharges from factories, where a discharge must be held between pH 6 and 8 to be acceptable. The actual pH of the effluent is measured and if it is too acid, a valve is actuated, to effect addition of some alkali.

ELECTRODICS

The second major branch of electrochemistry, electrodics, deals with the passage of a current from a metal electrode and into solution. Though much research has been published in the past hundred years in this exciting field, a great deal remains to be done, not least in the field of electro-organic chemistry; that branch which deals with the reactions of organic molecules at electrodes, where they are reduced or oxidised (at the cathode or anode respectively) or can undergo a range of other fascinating reactions such as dimerisation (doubling up). Here is a vast territory for novel ideas and research, and what is more, as such things go, the tools for this research are far less costly than those required for almost any other branch of chemistry. Indeed, apart from certain items of glassware, the instruments required will be those it is planned to present in the coming series.

The first laws of electrolysis are those laid down by Sir Michael Faraday, over a hundred years ago, in which he stated that a given quantity of electrical charge (the Faraday 96,500 coulombs) will liberate one gramme-molecule of a given substance for every electron required in the reaction. This opens up a number of important experiments, for we now know that by passing a certain charge (a known current for a known time), we can release precisely determined amounts of material. Indeed, the ampere is defined as a standard in these terms, as the current, passed for one second, which will deposit the appropriate amount of silver from a solution of this metal. However in practical terms, we face a problem, since the effective resistance of an electrolyte solution with two electrodes immersed in it, is rarely constant, and varies not only with temperature but also with time, as substances deposit on the electrodes the latter change their behaviour thus simulating a change

in resistance. For this reason, and unlike the electronics scientist, the electrochemist frequently requires the constant current device in place of the constant voltage source more commonly found in physics. With a constant current device, we can set up a current of, say, 50mA and know that it will hold at this value even though the voltage required to drive that current changes from perhaps 10 volts initially to as much as 18 volts after 30 minutes. Designs for two such units are presented in this issue. One is a simple single transistor unit with an output from 0-20mA or so. The second is a more advanced unit with switchable ranged outputs up to 3A.

If we wish to learn more about what is taking place during an electrolysis with two electrodes dipping into an electrolyte, we soon recognise that, in such a simple system, we cannot distinguish between what is happening at one electrode from that happening at the other. The reason for this is the voltage required to drive a current from an electrode into solution or vice-versa is related to it by:

$$V = a + b \log i$$

where *a* and *b* are constants which depend on the metal used, its size, condition (roughness) and what electrolysis reaction is taking place. We can describe an electrode whose voltage is changed as current flows according to this equation, as being *polarised*. Note that it is a non-linear relationship between current and voltage; in other words, one of the few cases where Ohm's Law is not obeyed. So with two electrodes in a beaker, each obeying the above law, and the ohmic drop through the solution as well, we end up with:

$$\begin{aligned} \text{(anode or positive electrode) } V &= a + b \log i \\ \text{(cathode, negative electrode) } V' &= a' + b' \log i \end{aligned}$$

All the constants are different, but the same current, *i*, must flow into the solution at one electrode and out at the other.

Adding these two terms together, we get an equation that describes the voltage across a cell:

$$V_{\text{cell}} = a'' + b'' \log i + iR$$

where the last term expresses the ohmic resistance of the electrolyte in the cell and leads etc. V_{cell} is what we measure with a voltmeter across the two electrodes when current *i* flows, *E* is the voltage across the same two electrodes before we pass voltage and *V* and *V'* apply to each of the two electrodes. *R* is the resistance of the electrolyte. The "Working" electrode is the one we are interested in, the one whose current-voltage characteristics (measured against the reference electrode) are plotted in Figs. 3 and 4. The "Counter" electrode we must have to ensure continuity of current flow through the solution. The "reference" electrode, because it passes no current, other than the leakage through the high impedance voltmeter, is assumed to be constant. Because three things are changing all at the same time, it is not possible to isolate any one effect. The solution is simple. Instead of adopting the circuit as in Fig. 1, we go rather for the three-electrode system shown in Fig. 2. The third electrode is called a *reference electrode*. Because no current flows through it, other than the minute drain due to the voltage measurement circuit, it is not polarised and remains at the same voltage even though the voltage of the other two electrodes, through which we are forcing current, does change.

If we take two electrodes, and lead is the most easily obtainable metal, dip them into weak sulphuric acid and pass a gradually increasing current, we can get values of *V* and *i*, and plot them. The result should be like that shown in Fig. 3. If we can obtain some semi-logarithmic graph paper, the result will instead be a straight line the gradient of which gives us "b" from the equation above, while the intercept is "a". The better our electrode is, the greater the value of "a" and a great deal of industrial research is now concerned with looking for novel electrode materials having a better value of "a" for key reactions

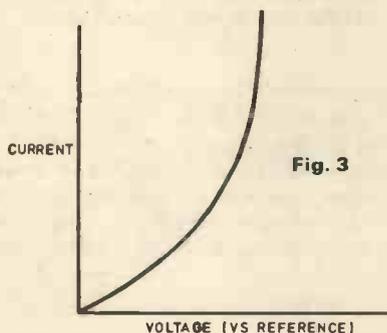


Fig. 3

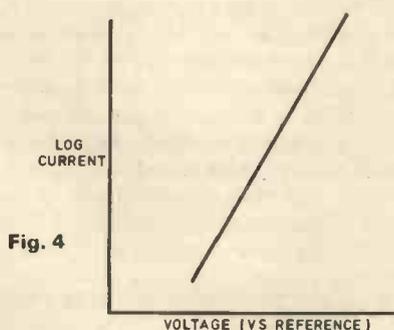


Fig. 4

such as hydrogen evolution or oxygen evolution (both involved in the "hydrogen economy") or for the chlorine evolution reaction. A more sophisticated instrument for following the relationship between current and voltage, is the potentiostat. This, unlike the constant current supply (or galvanostat) is a feedback device which measures the potential between the electrode whose behaviour we are anxious to study (working electrode) and the reference electrode, and compares this value with a pre-determined voltage which has been set up. By regulation of the current flowing in the circuit working electrode to counter electrode, that is to say variation not only of the magnitude but also the sense of this current, the desired potential is held constant. We may, in some cases, wish not so much as to hold this potential constant, but rather to vary it in a linear manner as a function of time. In such a case, we need a ramp generator, which is coupled to the sensing side of the potentiostat.

MAKING MEASUREMENTS

With these instruments we have the essentials for doing electrochemical experiments. However a certain number of other peripherals are also desirable. The measurement of current and voltage call for some thought. Current can be measured either using a d.c. ammeter in series with the instruments, or by measurement of voltage drop across a fixed-value precision resistor. Electrochemistry is unusual as a discipline, in that currents in a single experiment may vary from a few microamperes to an ampere or more. Thus, auto-ranging current measurement devices, though not widely used at present, would be useful. A further difficulty arises because, for reasons that will be explained, the resistor across which the p.d. is measured (sometimes known as the "counting resistor") may well stand 50V off earth potential, or even more. This calls for a voltage follower with rather special properties. The same wide span of currents (expressed as voltage drop across a resistor) could also suggest a log-response amplifier.

Application of a given current with measurement of the resulting voltage, or the converse process of maintaining a defined potential in order to observe the current, are the two most basic techniques we use in electrochemistry. By changing either the applied voltage or current and observing the value of the other parameter, we can obtain a graph of current vs. voltage, and from this graph a great deal can be learned about the nature of the reaction. Is the current responsive to stirring? What is the effect of change of temperature or pH or concentration of any other species? There is nothing like a little simple automation, and application of a simple voltage ramp either to the potentiostat or the galvanostat allows us to monitor one parameter while the other is continuously changing. We can feed the input and output to an X-Y chart recorder and go away for our tea until the scan is complete. For a faster scan, we shall use an oscilloscope to record the i - V trace, though more recently this has been challenged by the transient-recorder.

SOME EXPERIMENTS

In the project series, it is intended that all the instrumentation required for the study of electrochemistry will be described. That is to say a pH or pX meter, a constant current unit, a potentiostat, a function generator and a log amplifier. If space permits current followers and voltage followers as well as coulometers will also be described. Other equipment which is useful is an oscilloscope and, or, a V-t chart recorder. What sort of experiments can we do with this equipment? All sorts of ideas come to mind. The following simple experiments are suggested:

- i) Take 2 lead plates and place them in a beaker with dilute sulphuric acid. Apply a d.c. current (approximately 100mA


per cm^2 for a few hours) and we have now formed a simple lead acid battery. Measure the voltage at open circuit. It should be approximately 2.01 Volts. Now connect the constant current unit across the two plates and pass current in the reverse direction. The "battery" will be discharged. Measure the voltage while this is being done and it will slowly decrease for several minutes (or longer if you have a low current or a good battery) until suddenly the voltage will plunge downwards. This is called the *knee* of the discharge curve, and if we measure the charge passed (in ampere hours) from start of discharge till the knee, we obtain the capacity of the battery—it won't be as good as an Exide!

- ii) Take a clean metal electrode and plate onto it a thick layer of metallic copper from an acid copper sulphate bath. Using a constant current unit, measure the charge required. After the experiment, use a microscope to measure the thickness of the deposit. From Faraday's law and the Avogadro number, you can estimate the size of a copper atom.
- iii) Using a potentiostat and a dilute solution of sodium hydroxide (take care this does not splash!) follow the rate of hydrogen evolution at electrodes made of silver, gold, lead, iron or other metals. See how some are much better electrodes and evolve the same amount of gas at a lower voltage. Use a burette upturned to collect the hydrogen and verify Faraday's law (but do not forget to correct for water vapour pressure).
- iv) Using a potentiostat as a zero-resistance ammeter, connect a piece of steel and a piece of copper through the ammeter to one another. When both are immersed in water, you will observe a current flow and after a time, evidence of the corrosion of the steel will be seen. With this instrument, which measures current without imposing any "meter resistance" even at the micro-ampere level, we can follow the corrosion process. Similar experiments can be done using stainless steel, only here the currents will rapidly decrease as the metal *passivates* and forms its protective skin. Scratch that skin and the current will shoot up again.
- v) Make up a solution with small amounts of copper, iron and zinc salts in it, in dilute acid. Using a 25mV per sec. voltage ramp from the function generator connected to the potentiostat observe the current traced out. It should show three distinct plateaus corresponding to the three metals in solution and this principle forms the basis of polarographic analysis, each metal plating out as the potential becomes more negative.

The foregoing experiments are intended only as a guide to show some of the wide range that can be tackled with the equipment whose construction will be described in detail in later issues. These being scientific instruments, it follows that there is a wide range of textbooks in which electrochemistry is explained and discussed and ideas for experiments are suggested. A list of these books will be supplied by the author on request. It must be confessed that it is mainly with schools and colleges in mind that the present series has been launched, and the authors of the various articles will be happy to help interested readers in every possible way, whether in the construction of their instruments or in using them once they are built. Where possible, queries will be referred to the nearest known scientist working in the field to the address of the questioner. Happy experimenting! ★

PE TELETEXT

with **INFRA-RED**
REMOTE CONTROL

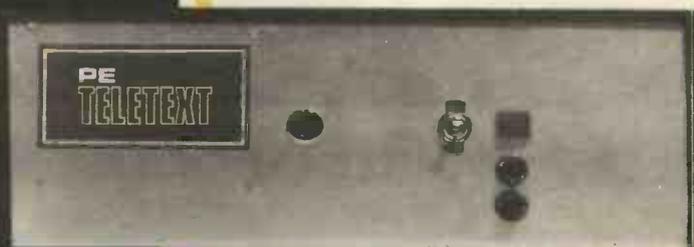

PART ONE...

David Shortland

THE PE Teletext system, which has been designed around the Mullard set of dedicated LSI chips, enables a TV set to decode and display the magazine information services transmitted by both the BBC and ITV networks (Ceefax, Orbit and Oracle).


The teletext information is transmitted in digital form along with the normal television signal using the spare lines in the field blanking interval which is usually of 25 lines duration. Some of these lines are used for test and signalling purposes and although any of them can be used for teletext transmissions, only lines 17(330) and 18(331) are used at present.

To reduce setting up and alignment problems the decoder board is available fully aligned and tested. The video summer board which has been designed by Mullards enables an excellent teletext display to be obtained via the aerial socket of a TV.

BLOCK DIAGRAM

A block diagram of the system is shown in Fig. 1.1. The aerial signal is fed to the tuner board where the video and audio information is extracted. The audio signal is then taken direct to the video summer board. The tuner board is also used for remote control channel changing. If a channel change key is pressed on the infra-red transmitter then a four-bit binary signal is sent to the tuner from the receiver to operate the changeover.

The video signal is fed to the decoder board where the teletext information is retrieved and then checked for errors. The decoder board also generates all the timing signals for the teletext display. After checking, the information is stored in two 1K x 4 static RAMs ready to be displayed. When enabled the RAM outputs are converted by a character generator into a dot matrix pattern. The matrix is in a 7 x 5 dot form for each character but as the character generator also has a character rounding facility to improve character definition, this effectively increases the matrix to 14 x 10 dots. The outputs from the decoder board are then taken via an interface daughter board to the video summer board where the colour burst and audio signals are added to the

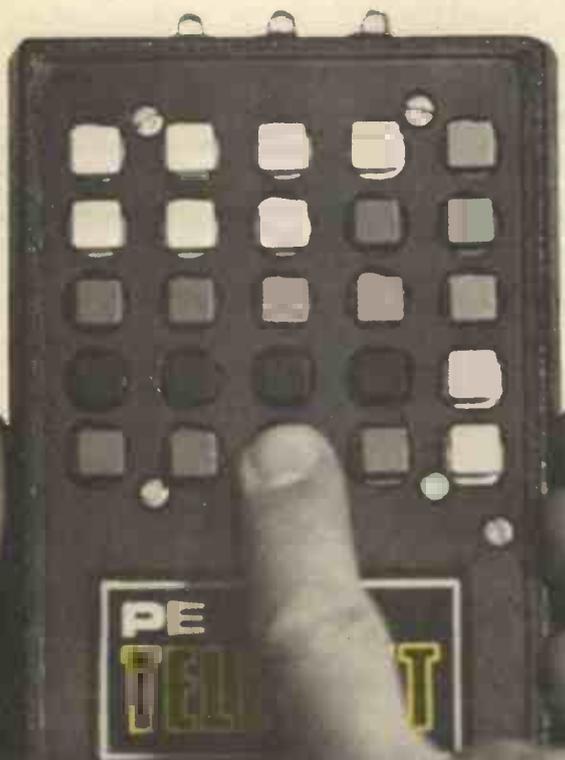

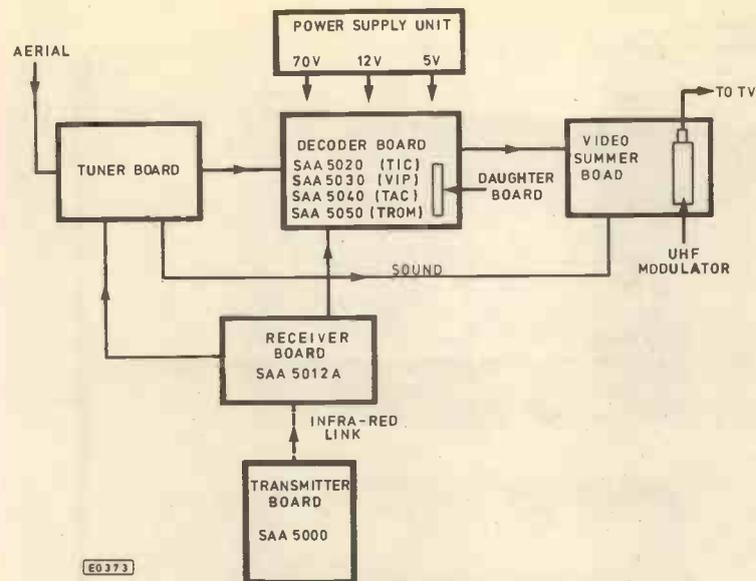


Fig. 1.1. Block diagram of the PE Teletext system

composite video signal which is then sent via a UHF modulator to the TV.

The system is connected to the TV via its aerial socket and in order to receive a good teletext display the aerial must be capable of delivering a strong signal to the set. If there are any problems with the reception then the teletext display information will be corrupted with random data and if the corruption is very bad then no text at all will be displayed.

When the system is first switched on or the reset button pressed BBC1 is automatically selected. Either of the other two channels can be chosen by pressing the appropriate button. The channel change buttons on the remote control are dual function: in the teletext mode they are the page selection numbers 1, 2, 3, etc.

REMOTE CONTROL FUNCTIONS

When the teletext mode is first selected after switch on, page 100 is automatically selected. Any other page in the magazine can be selected by pressing the appropriate page selection numbers (0 to 9) in turn. As each digit is entered the page number is built up in the left-hand corner of the screen. When the final digit, of the three digit number, has been entered the page header turns green (all except the left-hand page number) and the green page number in the header will "rotate" showing each page number as it is transmitted. When the selected page is transmitted the page number stops rotating and after the page has been captured the header reverts to white and the page is displayed.

HOLD


Some of the pages in the system contain more information than can be displayed on the screen at one time. To overcome this they are divided into a number of sub-pages and a different page is transmitted during each sweep of the system. As each sub-page is sent it is automatically displayed. The particular page in the series being shown is displayed in the right-hand corner of the screen, below the time (e.g. 1/4, 2/4, etc, etc). The hold key facility enables any rotating page to be held indefinitely. After pressing the hold key the word hold will appear in the top-right hand corner of the screen in place of the 24hr clock. The hold command can be cancelled by pressing the text button.

TIME


If the time button is pressed when the television picture is being viewed the 24hr clock will be inset in the video picture. The clock will disappear after 5 seconds.

TEXT

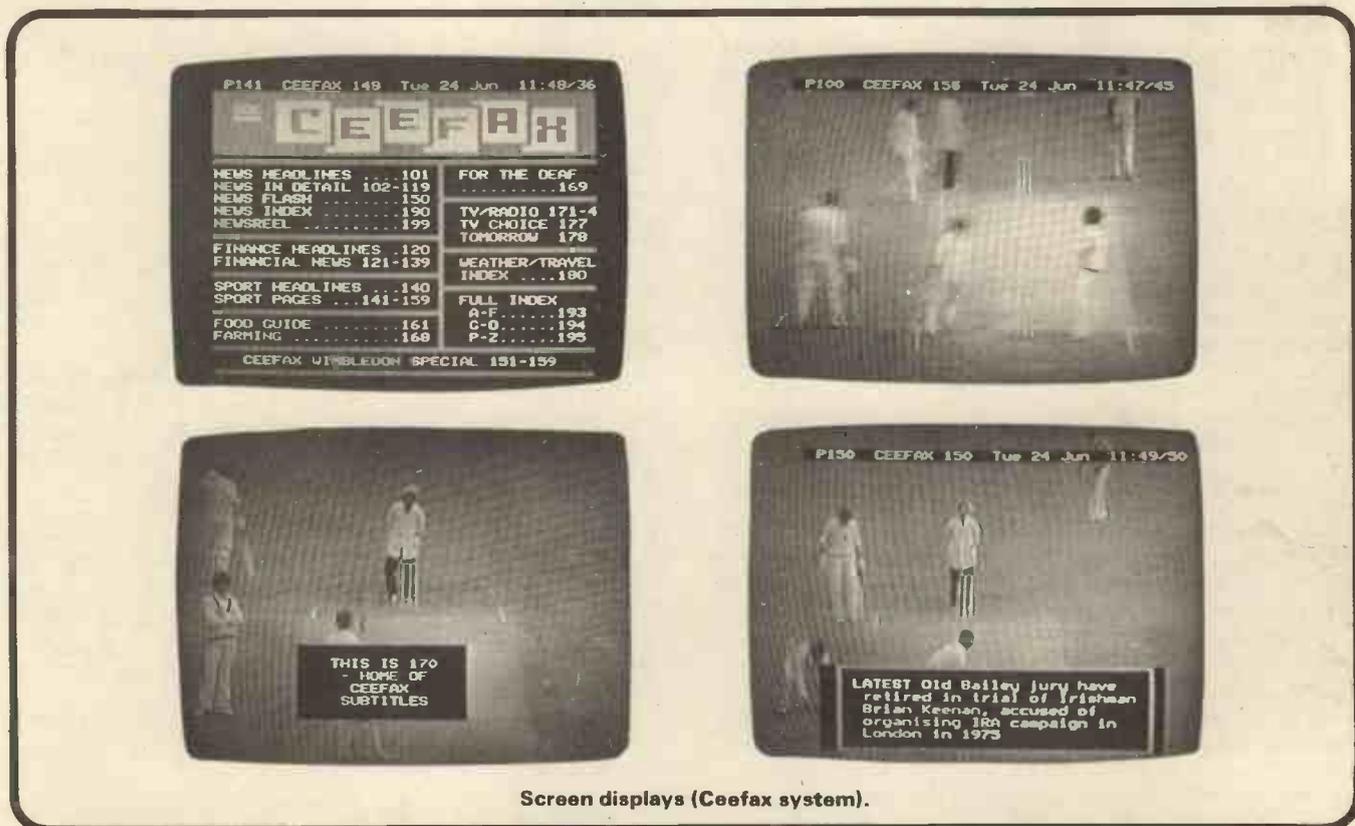The text command switches the system into the teletext mode and page 100 (the index) of either Ceefax or Oracle is



Screen displays (Ceefax system).

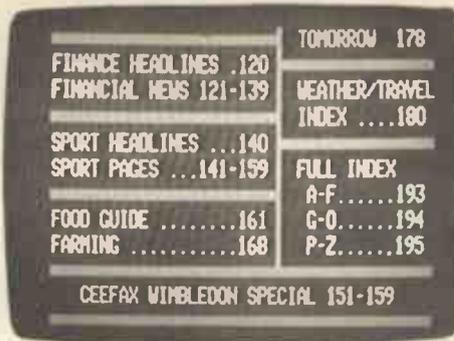

Screen displays (Ceefax system)

displayed depending on which channel was selected before the text button was pressed. This does not apply to BBC2 as the Orbit index is on page 200.

TOP, BOTTOM AND NORMAL

When in the teletext mode the top and bottom buttons select the double height characters and displays one half of the page for easier viewing at a distance. The normal button changes the display back to a full page. If a new page is selected whilst the double height characters are being used the top half of the new page will appear irrespective of which half page was previously selected.

REVEAL

Pages in the system which have parts of their display concealed (i.e. quiz pages) can have these parts displayed by pressing the reveal button.

PICTURE

To switch the system back to the television picture when it is in the teletext mode, press the picture mode.

TIMED TEXT

The timed text button enables any single page in the system to be stored for viewing at a pre-determined time. To use the timed text mode, switch the system into text and select the teletext page to be stored, then press timed text. This will replace the 24hr clock with the letter 'T' followed by a flashing 00:00 display. The page selection buttons can then be used to set the time the page is to be viewed (e.g. for 8-35 pm press 2035). When this has been completed press the cancel button to return the system to the picture. When the pre-determined time is reached the page number appears in the top left-hand corner of the screen. The page can be viewed by pressing the text button. The time code

can be cleared from the decoder by pressing the cancel time text key.

STATUS

The television channel being viewed can be identified at any time by pressing the status button. The channel is displayed in the left-hand corner of the screen for 5 seconds.

RESET

The reset button puts the system into the television mode and cancels all previous teletext commands.

MIX

The mix button will inset the page header into the television picture.

NEWSFLASH

If the new page is a newsflash or subtitle page then the system automatically switches back to the television video and the newsflash or subtitle information is inset into the picture. Switching back from a newsflash or subtitle page automatically turns the video off.

REMOTE CONTROL TRANSMITTER

The infra-red remote control unit which is used to control all the teletext functions is based on time-ratio discrimination and does not require any accurate timing components. The circuit diagram of the transmitter unit which is shown in Fig. 1.2 has been designed around the SAA5000 LSI chip and can transmit up to 32 commands.

To protect the system against interference of reflections the data is encoded as shown in Fig. 1.3. When a command is entered on the keypad a short pseudo-random sequence is transmitted followed by a 24-bit data stream which comprises a 7-bit start code and a 5-bit message. This 12-bit

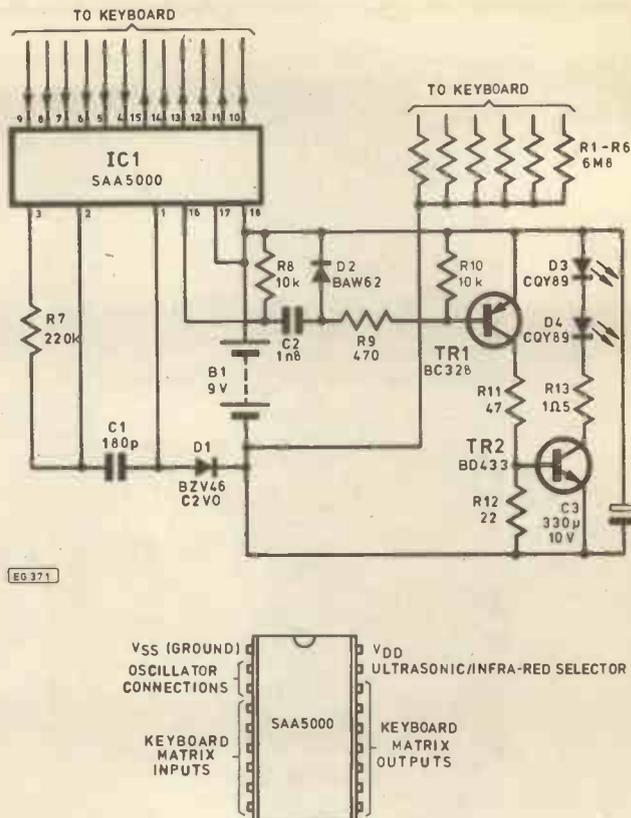
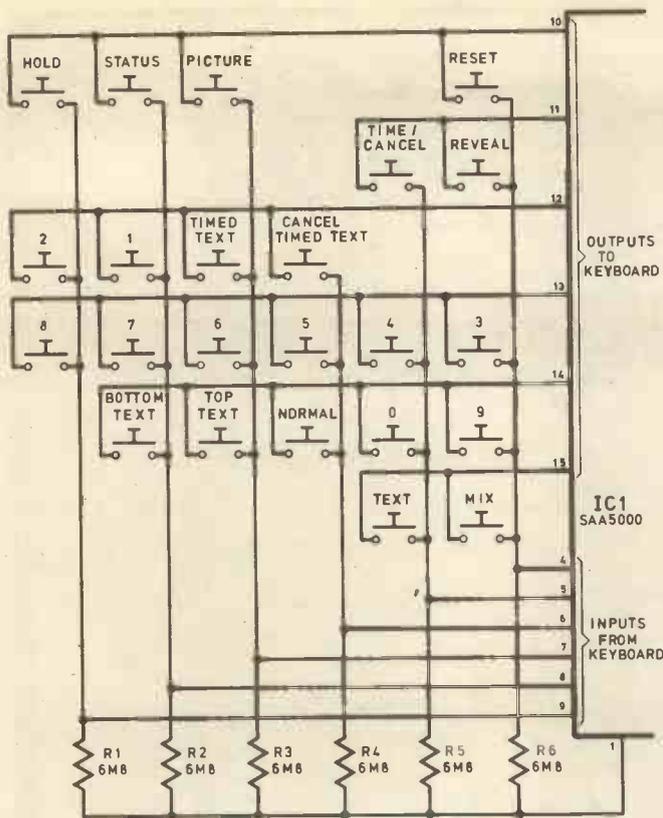


Fig. 1.2. Circuit diagram of the Transmitter unit

sequence is then inverted and transmitted again. When a key is pressed the whole data stream is automatically transmitted so the user does not have to keep the key depressed for any specific period of time. The receiver will not respond until the whole 24-bits have been received and checked.

The transmitter automatically 'powers up' when a key is pressed and will revert to standby when the transmission is completed. The push buttons are connected to 12 pins of IC1 with pins 10 to 15 being held high. When a button is pressed a high is connected to one of the input pins (4 to 9). These pins are connected to ground via resistors R1 to R6 which are pull-down resistors used to determine the input sensitivity of the chip. As the circuit 'powers up' an on chip oscillator produces a 24-bit data stream at pin 16. The oscillator is timed via resistor R7 and capacitor C1 with its frequency being used to determine the output data bit rate. The output signal is fed to TR1 which provides the base current to operate TR2. The resistor R13 defines the current for the epitaxial gallium arsenide i.e.d.s which when forward biased emit radiation in the near infra-red region. As high currents are used in the transmitter (approx 4 amps), which is supplied by C3, great care should be taken not to touch the pins of IC1 when the transmitter is being operated. This is because the time duration of the current pulses through the output diode can be greatly increased resulting in the diodes being permanently damaged.

	START	MESSAGE	START	MESSAGE
PSEUDO RANDOM SEQUENCE	1010011	11001	0101100	00110

Fig. 1.3. Encoding system for the transmitter data

CONSTRUCTION

The transmitter circuit is mounted on a double-sided p.c.b. which is shown in Fig. 1.4. Before any components are mounted on the board all the through board links, shown in Fig. 1.5, by the square pads, should be soldered using tinned copper wire. After soldering, check all the links for continuity with a multimeter. The components are mounted on one side of the board and the switches on the other. The push-button switches can be soldered next and as they can only be mounted one way round, carefully check the orientation before soldering. With the switches soldered, turn the board over and mount the components. Make sure the components are mounted as close as possible to the p.c.b. especially the transistor TR2. An i.c. socket should be used for IC1.

The two infra-red diodes are fitted into the end of the case using i.e.d. holders. The wiring for the diodes is shown in Fig. 1.6 along with the p.c.b. mounting details.

The p.c.b. should be mounted into the case before the i.c. is inserted. The case should be drilled to allow the 23 push-button switches to pass through. The p.c.b. should be mounted using 6BA counter sunk screws and the board spaced away from the case using either 6BA nuts or a spacer. When the board has been fitted into position check that each key operates correctly without fouling the case.

The keys can be annotated using rub-on transfers either on the key tops or on the case. If they are put on the keys then clear varnish should be used to protect them from wear. The battery can be held in place using double-sided tape.

RECEIVER CIRCUIT

The receiver circuit shown in Fig. 1.7 detects the infra-red signals from the transmitter via the photo-diode D5. A gyrator circuit designed around TR3 improves the rejection

COMPONENTS . . .

TRANSMITTER BOARD

Resistors

R1-R6	6M8 (6 off)
R7	220k
R8,R10	10k (2 off)
R9	470
R11	47
R12	22
R13	1Ω 5 2.5W

All resistors $\frac{1}{4}$ W 10% except where otherwise stated

Capacitors

C1	180p
C2	1n8
C3	330μ 10V elect.

Semiconductors

D1	BZV46 C2V0
D2	BAW62
D3,D4	CQY89 (2 off)
TR1	BC328
TR2	BD433
IC1	SAA5000

Miscellaneous

- PP3 battery
- Battery connector
- Holders for l.e.d.s (2 off)
- Case pac-tec type HP
- P.c.b.
- Switches (23 off)
- Holder for i.c.

RECEIVER BOARD

Resistors

R14,R15,R20	1M (3 off)
R16	330k
R17, R23	10k (2 off)
R18	47k
R19	8k2
R21	470k
R22	4k7
R24	27k

All resistors $\frac{1}{4}$ W 10% carbon

Capacitors

C4	1n
C5	470n
C6	2μ2 10V elect.
C7	22n
C8	68μ 10V elect.
C9	27p

Semiconductors

*D5	BPW34
D6,D7	BAW 62 (2 off)
TR3,TR4	BC159 (2 off)
TR5	BC148
TR6	BC149
IC2	SAA 5012A

Miscellaneous

- P.c.b.
- Holder for i.c.
- *See Fig. 1.7.

Constructor's Note

A complete kit of parts or individual boards for the PE Teletext system will be available from *A. Marshall's (London) Ltd.*, Kingsgate House, Kingsgate Place, London NW6 4TA. The main decoder board, which is mounted on a double-sided p.c.b. with plated-through holes, will be supplied ready built, tested and aligned. The board is not suitable for home construction and its design will not be published.

of low frequencies whilst allowing the maximum response to the narrow transmitted pulses. The output from the diode (D5) is a.c. coupled to the voltage amplifier of TR4 and TR5. The response of the amplifier which is controlled by C6 and the feedback capacitance of TR5's collector has been designed to cut off low and high frequency interference. The high frequency cut off also improves the stability of the amplifier. The output of the amplifier is a.c. coupled via D6 and D7 to the base of TR6. The diodes D6 and D7 eliminate any noise which is generated in D5.

The 24-bit message code is applied to pin 22 of IC2 where it is decoded and checked for errors. The DATA output (pin 5) pin of IC2 provides a 7-bit output, 5 bits of which are identical to the input message code and the other two bits control the mode of the system (i.e. TV or teletext). The DLIM output of the chip (pin 7) is clocking pulse which is used to clock the output data from IC2. The internal functions of the circuit are controlled by an oscillator which is timed by the resistor and capacitor connected to pins 18 and

19. The 4-bit outputs from the chip (pins 2, 3, 8 and 21) are used to select the TV channel to be viewed.


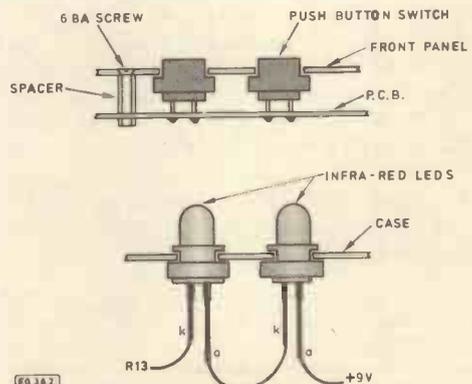


Fig. 1.6. Wiring diagram for the infra-red diodes (D3 and D4) and the mounting details for the p.c.b.

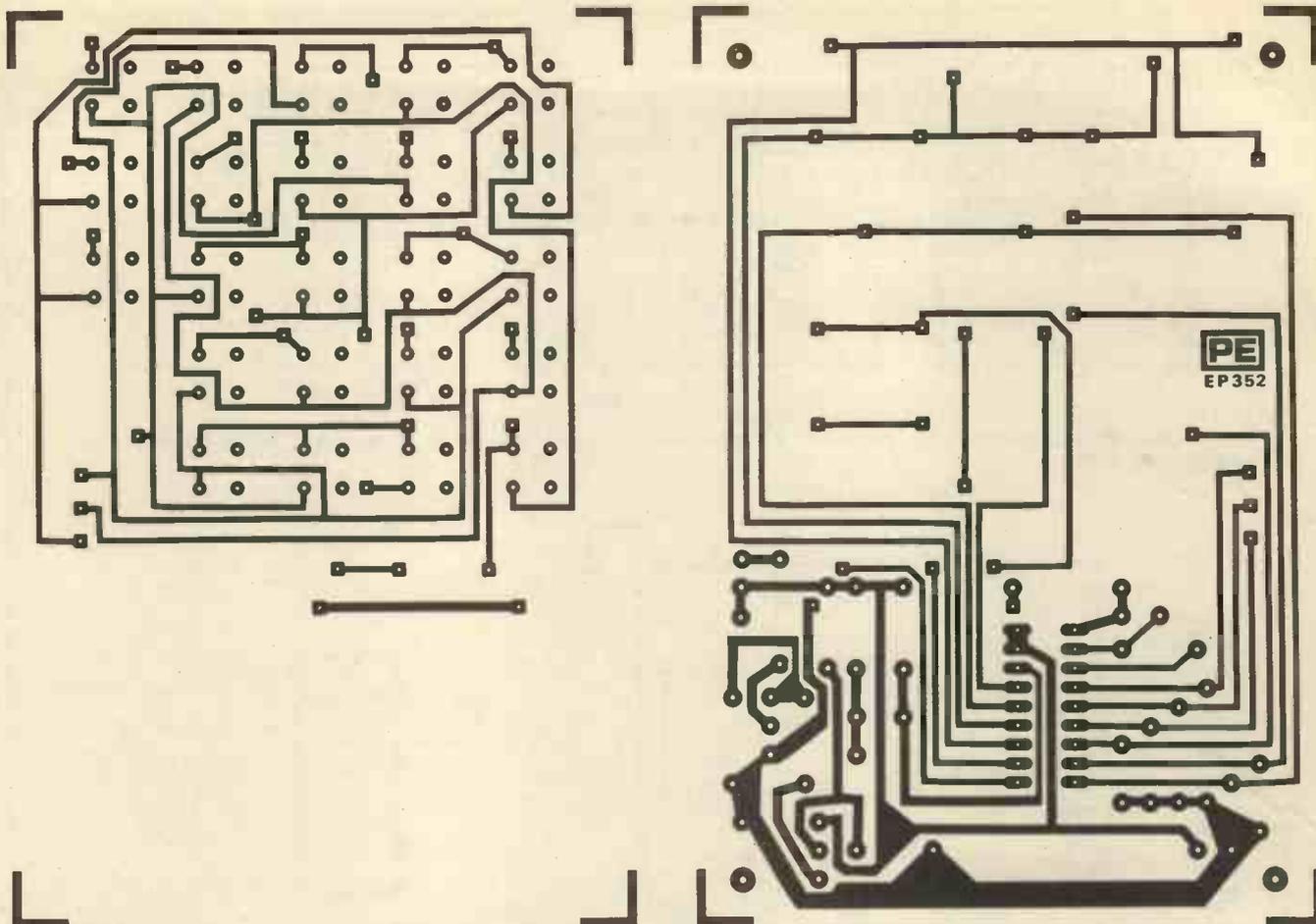

EP353

Fig. 1.4. Double-sided p.c.b. design for the Transmitter



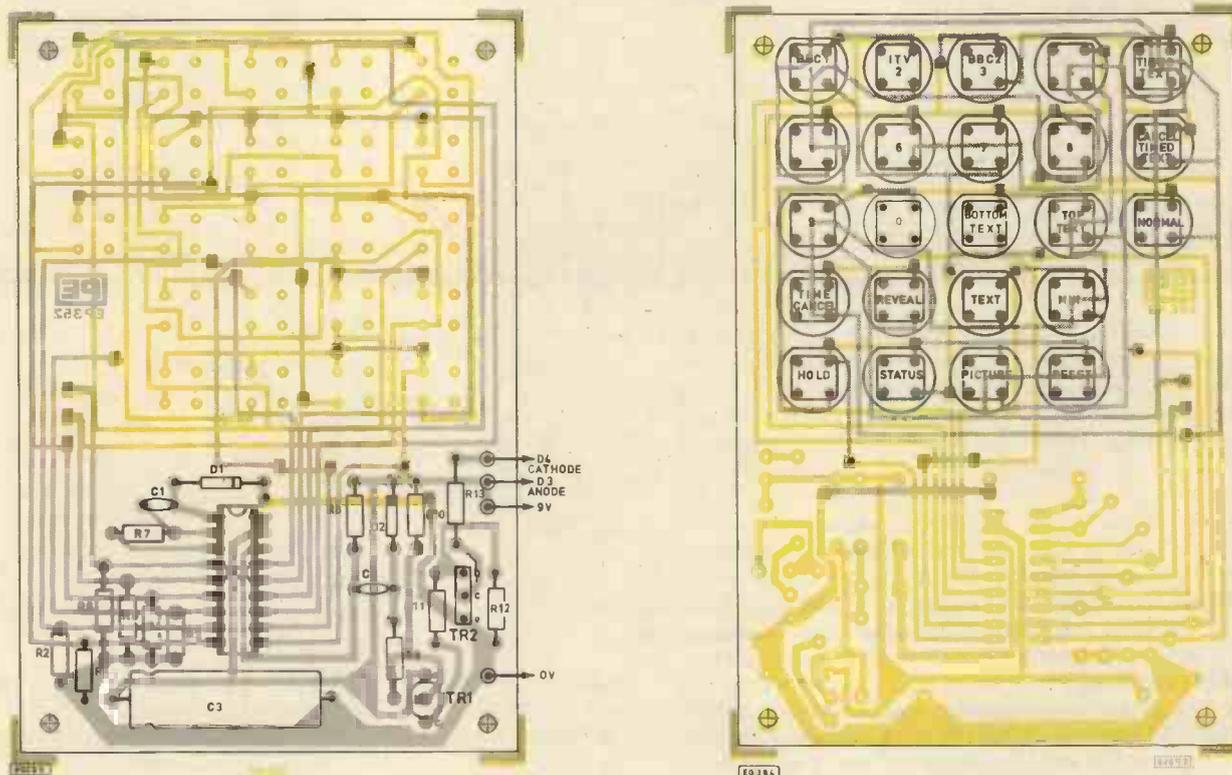


Fig. 1.5. Component layout for the transmitter board which also shows the through board links (square pads)

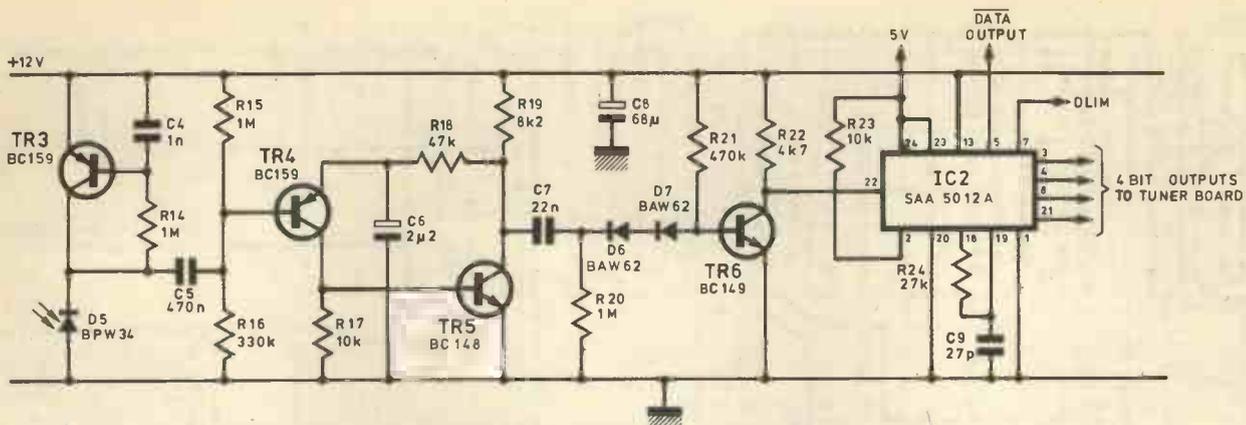



EG381

Fig. 1.7. Circuit diagram of the Receiver unit. The range of the transmitter can be increased by fitting a plastic lens in front of D5

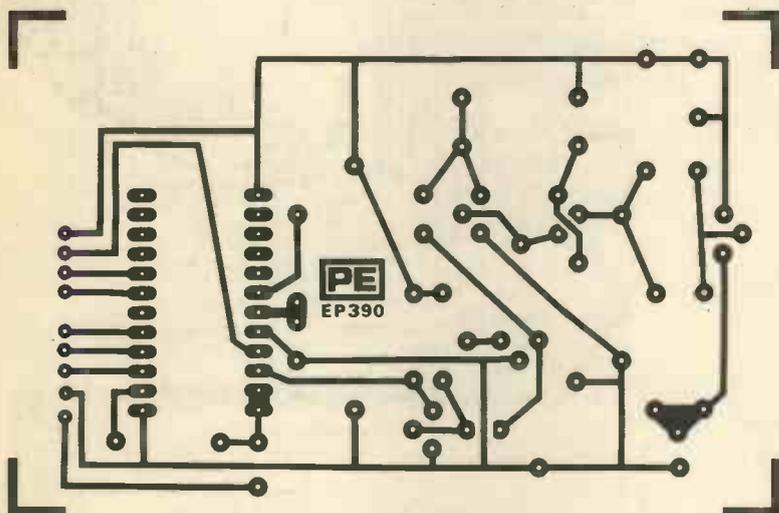

EG392

Fig. 1.8. Receiver p.c.b. design

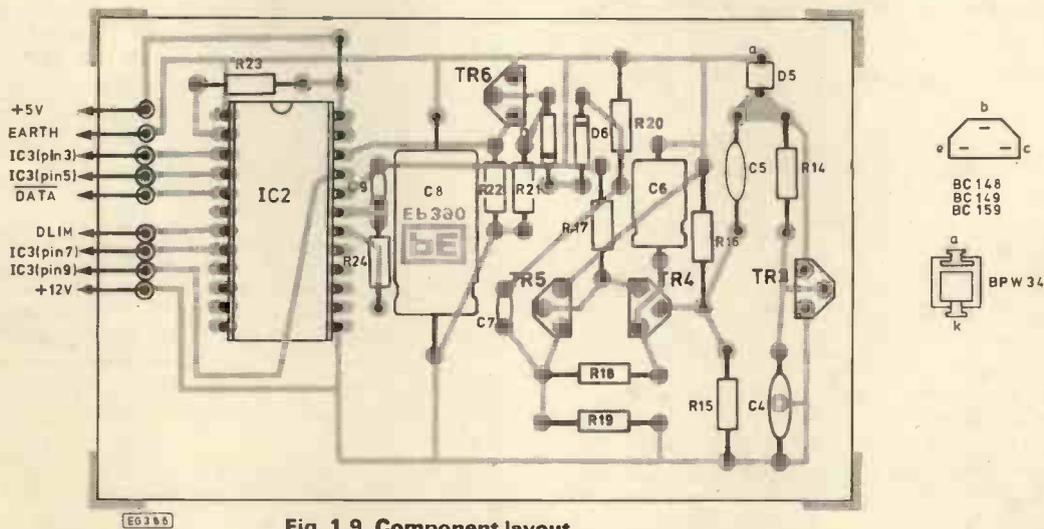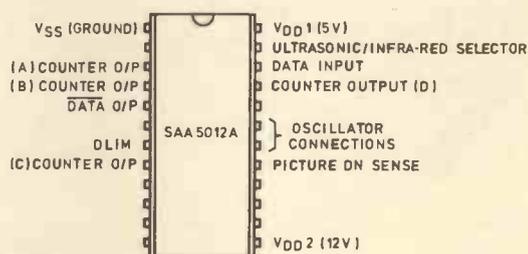

EG390

Fig. 1.9. Component layout

RECEIVER CIRCUIT

The receiver circuit is mounted on the p.c.b. shown in Fig. 1.8. All the components, except for the photo-diode D5, should be mounted on the board as shown in Fig. 1.9. A holder should be used for IC2 and after all the components have been soldered into position the p.c.b. can be turned


over and the diode D5 soldered onto the track side of the board taking care that it is correctly orientated.

The inter wiring for the receiver board and the complete system will be covered after the construction of the rest of the boards.

NEXT MONTH: CONSTRUCTION CONTINUED

SPECIAL OFFER!

CAPACITOR PACKS...

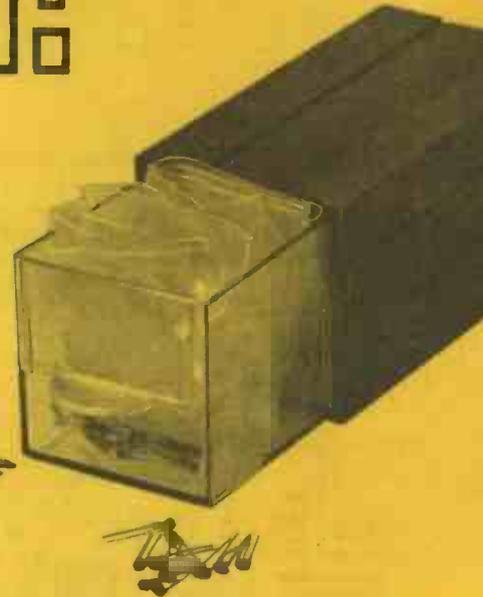

200 Mullard ceramic capacitors with drawer £6-50 including VAT p. & p.

130 Siemens layer capacitors with two drawers £13-50 including VAT p. & p.

We have arranged that these special offer packs are available to PE readers from Marshalls. The packs represent excellent value for money, the ceramics are normally sold by Marshalls at 6p each and the Siemens layer type at 7p to 36p each (depending on value).

PACK 1. 200 Mullard 63V d.c. working miniature ceramic plate capacitors, 0.1 inch lead spacing.

Tolerance—1-10pf ± 0.25 pF
 22-330pf $\pm 2\%$
 470p-1n $\pm 5\%$
 2n2-10n 10%

The pack contains 10 each of the following values: 1p, 2p2, 3p3, 4p7, 6p8, 10p, 22p, 33p, 47p, 68p, 100p, 220p, 330p, 470p, 680p, 1n, 2n2, 3n3, 4n7, 10n.

PACK 2. 130 Siemens self-healing layer capacitors with polyester dielectric, 7mm pin spacing except 1u which is 10mm.

Tolerance $\pm 10\%$
 250V or 400V up to 100n, 100V 220n to 1u.

The pack contains 10 of each of the following values: 1n, 2n2, 4n7, 6n8, 10n, 22n, 47n, 68n, 100n, 220n, 470n, 680n, 1u.

To: Marshall's (PE Capacitor Offer), Kingsgate House, Kingsgate Place, London NW6 4AT. Tel. 01-624 0805.

Mail order only

Please send me

<input type="checkbox"/>	Pack 1 Ceramic
<input type="checkbox"/>	Pack 2 Layer

Capacitor packs at £6-50 (Pack 1) or £13-50 (Pack 2) each

I enclose PO/Cheque No.Value

Name

Address

.....

.....

Please allow 28 days for delivery
OFFER CLOSES FRIDAY, 26 SEPT. 1980

Name

Address

.....

.....

To: Marshall's (PE Capacitor Offer), Kingsgate House, Kingsgate Place, London NW6 4AT. Tel. 01-624 0805

Please complete both parts of the coupon in BLOCK CAPITALS

MICRO-BUS

Compiled by DJD.

Appearing every two months, Micro-Bus presents ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data books. The most original ideas often come from readers working on their own systems, and payment will be made for any contribution featured.

THE five topics in this month's Micro-Bus are all totally unrelated, and include an automatic Morse-code generator, a game for the ZX80, and a program to multiply enormous numbers together.

MORSE-CODE GENERATOR

The following program was developed on an Mk14 microcomputer by *Andrew Chadwick of Hull* to produce Morse code as a teaching aid for a Scout troop. The program has other uses, such as the automatic generation of call signs and test sequences, and can easily be modified to generate Morse code from characters as they are typed in at a keyboard. The message to be transmitted is simply set up in memory and, using a look-up table, the program translates the message into Morse-code format and transmits it via the flag outputs of the microprocessor. The message is written using the simple code of 1 for A, 2 for B, etc., as shown in Fig. 1. A blank (39) must be inserted between each word, and the message must finish with the end-of-message character 37. A simple

CHARACTER	HEX CODE	MORSE CODE
0	27	-----
1	28	-----
2	29	-----
3	30	-----
4	31	-----
5	32	-----
6	33	-----
7	34	-----
8	35	-----
9	36	-----
End of message	37	-----
Erase/Error	38	-----
Blank	39	(dot)
Long space	40	(2 dash)

Fig. 1. List of characters with their Morse codes, and the hexadecimal codes used by the program in Fig. 4.

modification would enable the program to generate Morse code from a message written in ASCII.

The output can be fed directly to a high-impedance speaker by connecting the speaker between flag 0 or 1, and ground. Alternatively

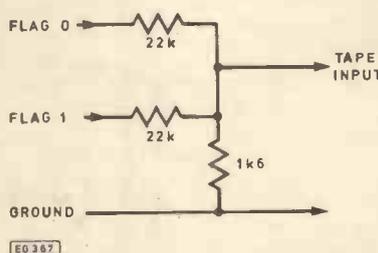


Fig. 2. Interface circuit to enable the Mk14 to drive the auxiliary input of a tape recorder.

the output can feed a tape recorder via the simple interface shown in Fig. 2, which reduces the output to about 400 mV peak to peak, suitable for an auxiliary input.

MORSE CODE

The Morse code for the letters and numbers consists of a series of up to five dots and/or dashes, and the program uses a look-up table to convert the character to be transmitted into a single byte which specifies the Morse code; see Fig. 3. The three low-order bits of this byte, D0 to D2, indicate how many dots or dashes there are in the Morse code for the character, and whether or not they will be sounded. Values of one to five imply one to five dots and dashes which will all be sounded, whereas six and seven imply one and two dots/dashes respectively which will not be sounded. This format enables spaces to be treated in a similar way to characters.

The upper five bits in the byte, D4 to D7, give the Morse code itself, a one representing a dash and a zero representing a dot. D4 corresponds to the first dot or dash.

MORSE PROGRAM

The program, shown in Fig. 4, takes up the whole of the Mk14's standard 256 bytes of RAM. It is divided into three sections: a look-up table from OF1B to OF43 containing the Morse-code bytes for the various characters, the main program from OF44 to OFC2, and a subroutine from OFC3 to OFF6. The subroutine generates either a tone or a space of length equivalent to either a dot or a dash. Which of these possible outputs is produced is determined by the two variables DDF (Dot/Dash Flag) and MSSF (Master Sound/Silence Flag) which are set up by the main program before the subroutine is called. Setting DDF to 0 gives an output of dot length whereas 1 gives an output of dash length.

CHARACTER	HEX CODE	MORSE CODE
A	1	--
B	2	----
C	3	----
D	4	----
E	5	----
F	6	----
G	7	----
H	8	----
I	9	----
J	10	----
K	11	----
L	12	----
M	13	----
N	14	----
O	15	----
P	16	----
Q	17	----
R	18	----
S	19	----
T	20	----
U	21	----
V	22	----
W	23	----
X	24	----
Y	25	----
Z	26	----

CHARACTER	MORSE CODE	FORMAT IN LOOK-UP TABLE	
		Binary	Hexadecimal
A	--	00010 010	12
1	----	11110 101	F5
Blank	(length = dot)	00000 110	06

Fig. 3. Examples showing how the Morse codes for the characters are stored within one byte.

Setting MSSF to 0 gives no output, whereas 1 indicates that a tone is to be produced.

PROGRAM OPERATION

Before execution of the program the speed of transmission, in words per minute, is set as

```

;
; MORSE-CODE GENERATOR
OE00 MESS = OE00 ;MESSAGE AREA
OF00 RAM = OF00 ;RAM
OFC2 SUBR = OFC2
OOLP MON = OOLP ;MONITOR
;
0000 ;.=OFLB ;CODE TABLES:
OFA8 .BYTE 012,00C,02C,00B,00L,024
OF21 .BYTE 01B,004,002,074,02B,014
OF27 .BYTE 01A,00A,03B,034,05C,013
OF2D .BYTE 003,009,023,044,033,04C
OF33 .BYTE 06C,01C,0FD,0F5,0E5,0C5
OF39 .BYTE 0B5,005,00D,01D,03D,07D
OF3F .BYTE 055,005,006,01F,000
;
OF44 C0AE ENTRY: LDI H(MESS) ;P1 = MESSAGE
OF46 35 XPAH 1
OF47 C400 LDI L(MESS)
OF49 31 XPAL 1
OF4A C40F LDI H(RAM) ;P2 = RAM
OF4C 36 XPAH 2
OF4D C400 LDI L(RAM)
OF4F 32 XPAL 2
OF50 C40F LDI H(SUBR) ;P3 = SUBROUTINE
OF52 37 XPAH 3
OF53 C4C2 LDI L(SUBR)
OF55 33 XPAL 3
OF56 C400 LDI X'00 ;INITIALIZE MLC
OF58 CA13 ST MLC(2) ; AND E TO
OF5A 01 XAE ; ZERO.
OF5B AA13 ADD: LLD MLC(2) ;ADD SPEED
OF5D C212 CLD WPM(2) ; SPECIFIED IN
OF5F 02 CCL ; WPM TO F
OF60 70 ADE ; UNTIL CARRY
OF61 01 XAE ; GENERATED.
OF62 06 CSA
OF63 94F6 JP ADD ;MLC=256/WPM
OF65 C501 LD @1(1) ;GET LETTER
OF67 D4F0 ANI X'FO ;CONVERT FROM
OF69 02 CCL ; BASE 10 TO
OF6A 1C SR ; BASE 16.
OF6B 01 XAE
OF6C 40 ADE
OF6D 1C SR
OF6E 1C SR
OF6F 70 ADE
OF70 01 XAE
OF71 C1FF LD -1(1)
OF73 D40F ANI X'0F
OF75 70 ADE
OF76 F41A ADI TDISP ;ADD LOOK-UP
OF78 01 XAE ; TABLE DISP.
OF79 C280 LD -128(2) ;GET CODE FROM
OF7B CA15 ST CODE(2) ; TABLE + SAVE.
OF7D D407 ANI X'07 ;REMOVE CODE
OF7F CA16 ST DDC(2) ;STORE NO. DOTS
OF81 03 SCL ; OR DASHES.
OF82 FC06 CAI X'06 ;SEE IF SOUND
OF84 9406 JP SDC ; OR SILENCE.
OF86 C401 LDI X'01 ;SET MSSF=1
OF88 CA14 ST MSSF(2) ; FOR SOUND.
OF8A 9009 JMP ROT
OF8C 02 SDDC CCL ;SILENCE:
OF8D F401 ADI X'01 ;SET DDC
OF8F CA16 ST DDC(2) ; CORRECTLY.
OF91 C400 LDI X'00 ;SET MSSF=0
OF93 CA14 ST MSSF(2) ; FOR SILENCE.
OF95 C215 LD CODE(2) ;GET CODE
OF97 1E RR ;GET FIRST DOT
OF98 1E RR ; OR DASH INTO
OF99 CA15 ST CODE(2) ; LOW BIT + 1
OF9B C215 SIG: LD CODE(2) ;GET DOT/DASH
OF9D 1E RR ; INTO LOW BIT
OF9E CA15 ST CODE(2)

```

Morse-code byte, and transmits it a dot or a dash at a time by giving the two variables DDF and MSSF the necessary values, and then calling the subroutine. A dash has three times the length of a dot, and the space between each dot and dash is the same length as

```

OFA0 D401 ANI X'01 ;TEST LOW BIT
OFA2 CA17 ST DDF(2) ;SET DDF
OFA4 C214 LD MSSF(2) ;SET MSSF FROM
OFA5 CA18 ST MSSF(2) ; MSSF
OFA8 3F XPPC 3 ;TEST FIRST ./-
OFA9 C400 LDI X'00 ;SEND ONE DOT
OFAB CA17 ST DDF(2) ; SPACE.
OFAC CA18 ST XPPC 3 ;SSSF(2)
OFAD 3F XPPC 3
OFB0 BA16 DDI DDC(2) ;TEST FOR ANY
OFB2 9C7 JNZ SIG ; MORE
OFB4 3F XPPC 3 ;SEND ONE DASH
OFB5 3F XPPC 3 ; SPACE.
OFB6 C215 LD CODE(2) ;TEST IF JUST
OFB8 4AA XRI X'AA ; SENT END.
OFBA 9A9 JNZ GETL ;NO-GET ANOTHER
OFBC C400 OFBC LDI H(MON) ;JUMP BACK TO
OFBE 37 XPAH 3 ; TO MONITOR.
OFBF CA1F LDI L(MON)
OFC1 33 XPAL 3
OFC2 3F XPPC 3 ;RETURN.
;
; SUBROUTINE TO SEND DOT/DASH
OFC3 C217 START: LD DDF(2) ;DOT OR DASH TO
OFC5 9804 JZ DOT ; BE SENT?
OFC7 C406 LDI DALE ;DASH: GET THE
OFC9 9002 JMP STLE ; LENGTH.
OFCB C412 LDI DOLE ;DOT: GET LENGTH
OFCD CA19 STLE: ST OLD(2) ;STORE LENGTH
OFCE C213 SILC: LD MLC(2) ;SET INNER COUNT
OFD1 CA13 ST LDI L(2) ; FROM MASTER
OFD3 C218 TSSF: LD SSSF(2) ;TEST FOR SOUND
OFD5 02 JZ SIL ; OR SILENCE
OFD7 C403 LDI X'03 ;SOUND: GENERATE
OFD9 07 CAS ; TONE ON FO,F1
OFDA C400 LDI X'00
OFDE 8F02 DLY X'02
OFDF C400 LDI X'04
OFE0 07 CAS ;SILENCE: WAIT
OFE1 8F02 DLY X'02
OFE3 9004 JMP DELC ;SILENCE: WAIT
OFE5 C400 SIL: LDI X'00 ;SILENCE: WAIT
OFE7 8F04 DLY X'04
OFE9 BA1A DILC: DDI L(2) ;TEST INNER
OFEB 9C86 JNZ TSSF ; COUNT.
OFED BA19 DDI OLC(2) ;TEST OUTER: IF
OFEF 9C0E JNZ SILC ; ZERO STOP.
OFF1 C401 LDI X'01 ;SO SET OUTPUT
OFF3 07 CAS ; TO MEAN
OFF4 3F XPPC 3 ;RETURN
OFF5 90CC JMP START ;FOR RE-CALL
;
; CONSTANTS AND RAM OFFSETS
0002 DOLE = 2 ;DOT LENGTH
0006 DALE = 2 ;DASH LENGTH
0012 WPM = 12 ;WORDS/MINUTE
0013 MLC = 013 ;INNER LOOP COUNT
0014 MSSF = 014 ;SOUND/SILENCE
0015 CODE = 015 ;MORSE CODE
0016 DDC = 016 ;DOT/DASH COUNT
0017 DDF = 017 ;DOT/DASH FLAG
0018 SSSF = 018 ;SLAVE S/S FLAG
0019 OLC = 019 ;OUTER LOOP COUNT
001A ILC = 01A ;INNER LOOP COUNT
001A TDISP = 01A ;LOOK-UP TABLE
0000 ;END

```

Fig. 4. Program for the Mk14 generates Morse code from a message stored in memory.

a hexadecimal number in the location WPM (OF12). On running the program, pointer 1 is set to point to the location of the first character in the message; in the listing of Fig. 4 this is at address OE00, but for the extra RAM on a standard Mk14 this would be OB00. Pointer 2 is set to the beginning of the standard RAM (OF00), and pointer 3 to the start of the subroutine.

The section of program between OF56 and OF64 divides 256 by the specified speed of transmission to give the appropriate value for the subroutine's inner-loop counter. At OF65 the character code is loaded from the message, converted from base 10 to base 16, and then used as a displacement to fetch the corresponding Morse-code byte from the look-up table. The instructions from OF70 to OF9A sort out the information stored in bits D0 to D2 of the Morse-code byte, and set the appropriate variables.

The main loop, beginning at OF9B, deals with the code stored in bits D3 to D7 of the

a dot. The space between each character is three dots long, and between each word is seven dots long. The required spaces between dots and dashes, and between letters, are inserted by the instructions between OFA9 and OFAF, and OFB4 to OFB5, respectively.

When the end-of-message character has been detected and transmitted the program returns to the monitor. The timing throughout the program is based on a system using a 4.43 MHz crystal, and will have to be altered for any other clock frequency. Note that, with the program as it stands, only the standard alphanumeric characters, whose Morse code runs to a maximum of five dots or dashes, can be produced; characters with six or more dots or dashes, such as punctuation marks, are not possible.

BULLS AND COWS FOR ZX80

The following program to play 'Bulls and Cows', which is probably better known in the form of the plastic peg game 'Mastermind', is

the first program feature in Micro-Bus to run on the Sinclair ZX80 BASIC-programmed microcomputer. It was devised by S. Murrell of Sunderland. The computer generates a random 4-digit 'code' which the player must try and deduce in eight or less attempts. Each digit in the code can be from 1 to 6, and each guess is entered as a string of four digits followed by a NEWLINE. The computer replies with a solid rectangle for each 'Bull', or correct digit in the correct position, and a shaded rectangle for each 'Cow', or correct digit in the wrong position. Each digit may only contribute towards one Bull or one Cow.

PROGRAM OPERATION

The program, shown in Fig. 5, works as follows. The computer first generates a code in the array Z(0) to Z(3). The guess string is then entered into G\$, and the program converts it into an array of four numbers in G(0) to G(3).

```

10 PRINT "MASTERMIND"
20 PRINT
30 PRINT
40 PRINT "NO.OF YOUR MY"
50 PRINT "TRIES GUESS REPLY"
60 PRINT
70 DIM Z(3)
80 DIM X(3)
90 DIM G(3)
100 FOR I=0 TO 3
110 LET Z(I)=RND(6)
120 NEXT I
130 LET A=1
140 INPUT G$
150 PRINT A
160 PRINT G$,
170 LET B=0
180 FOR I=0 TO 3
190 LET X(I)=Z(I)
200 LET G(I)=CODE(G$)-28
210 LET G5=TL(G$)
220 IF NOT X(I)=G(I) THEN GO TO 270
230 LET X(I)=10
240 LET G(I)=11
250 LET B=B+1
260 PRINT " "
270 NEXT I
280 FOR J=0 TO 3
290 FOR I=0 TO 3
300 IF NOT X(I)=G(I) THEN GO TO 340
310 LET X(I)=10
320 LET G(I)=11
330 PRINT " +";
340 NEXT I
350 NEXT J
360 PRINT
370 IF B=4 THEN GO TO 410
380 IF A=8 THEN GO TO 440
390 LET A=A+1
400 GO TO 140
410 PRINT
420 PRINT "YOU WIN... WELL DONE"
430 GO TO 460
440 PRINT
450 PRINT "I WIN..THE NUMBER WAS "Z(0);Z(1);Z(2);Z(3)
460 PRINT
470 PRINT
480 PRINT "HIT NEWLINE TO PLAY AGAIN"
490 CLEAR
500 INPUT K$
510 CLS
520 IF K$="" THEN GO TO 10

```

Fig. 5. Mastermind program for the ZX80; the task is to guess the computer's code.

The computer makes a copy of its code in X(0) to X(3), and compares this, element by element, with the guess array. If there is a match a Bull is scored, and a white block is printed. The matching numbers in X and G are converted to 10 and 11 respectively so that they will not be counted as Cows later on. Next, the number of Cows is obtained by comparing every element of the array X with every element of the array G; for every match a shaded rectangle is printed, and again the elements are set to 10 and 11 so that they will not be counted again. Finally, if the score is four Bulls the code has been correctly guessed, and the human has won; otherwise the computer will declare a victory after the eighth attempt.

In the program listing of Fig. 5 "*" is used to

represent a solid rectangle, which is obtained on the ZX80 by typing SHIFT-W, and "+" represents a shaded rectangle, which is obtained by typing SHIFT-T.

64-DIGIT MULTIPLY

The following short program for the humble Mk14 can multiply two numbers together to give a result of up to 64 digits, thus amply demonstrating the superiority of the microcomputer over the pocket calculator! The program, shown in Fig. 6, was written by Geoff Phillips who edits the Mk14 Users

```

;
; 64-DIGIT MULTIPLY
O800 OPA = O800 ;1ST OPERAND
O810 OPB = O810 ;2ND OPERAND
;
; OFFSETS FROM OPA
O020 ANS = O20 ;ANSWER
O040 DIGITB = O40 ;DIGIT COUNTER
O041 MULT = O41 ;MULTIPLY COUNT
O042 DIGITA = O42 ;DIGIT COUNTER
O043 TEMP = O43
O044 COUNT = O44 ;COUNTER
;
O000 ;
O012 C40B ENTRY: LDI H(OPA) ;P2=O800
O014 36 XPAH 2
O015 C400 LDI L(OPA)
O017 32 XPAL 2
O018 C40B LDI H(OPB) ;P1=O810
O01A 35 XPAH 1
O01B C410 LDI L(OPB)
O01D 31 XPAL 1
O01E C420 LDI 32 ;SET UP LOOP
O020 CA44 ST COUNT(2)
O022 C21F NEXT: LD OIF(2) ;NEXT DIGIT OF
O024 D40F ANI OF ; OPB.
O026 CA41 ST MULT(2) ;SET LOOP
O028 9815 JZ DONE ;IF 0, SKIP
O02A C410 ADD: LDI O10 ;ADD NUMBER
O02C CA42 ST DIGITA(2)
O02E O2 CCL
O02F C5FF MULTI: LD @-1(1) ;NEXT 2 DIGITS
O031 E920 DAD ANS(1) ;ADD TO TOTAL
O033 C920 ST ANS(1)
O035 BA42 DLD DIGITA(2)
O037 9CF6 JNZ MULTI
O039 C510 LD @O10(1) ;RESET P1=O810
O03B BA41 DLD MULT(2) ;ADD A AGAIN
O03D 9CEB JNZ ADD ;UNTIL DONE.
O03F C410 DONE: LDI O10
O041 CA40 ST DIGITB(2)
O043 C400 LDI O
O045 O1 XAE ;SHIFT OPB
O046 C501 MOVE: LD @1(1) ;GET NEXT BYTE
O048 1C SR
O049 1C SR
O04A 1C SR ;PUT HIGH DIGIT
O04B 1C SR ; LOW.
O04C CA43 ST TEMP(2) ;KEEP IT
O04E C1FF LD -1(1) ;PICK OUT LOW
O050 D40F ANI OF ; DIGIT.
O052 O1 XAE ;PUT IN E
O053 1E RR
O054 1E RR
O055 1E RR
O056 1E RR
O057 DA43 OR TEMP(2)
O059 C9FF ST -1(1)
O05B BA40 DLD DIGITB(2)
O05D 9CE7 JNZ MOVE
O05F C420 LDI 32 ;SHIFT RESULT
O061 CA40 ST DIGITB(2) ; RIGHT.
O063 C400 LDI 0
O065 O1 XAE
O066 C501 SHIFT: LD @1(1)
O068 1C SR
O069 1C SR
O06A 1C SR
O06B 1C SR
O06C CA43 ST TEMP(2)
O06E C1FF LD -1(1)
O070 D40F ANI OF
O072 O1 XAE
O073 1E RR
O074 1E RR
O075 1E RR
O076 1E RR
O077 DA43 OR TEMP(2)
O079 C9FF ST -1(1)
O07B BA40 DLD DIGITB(2) ;END OF SHIFT
O07D 9CE7 JNZ SHIFT
O07F C410 LDI O10
O081 11 XPAL 1
O082 BA44 DLD COUNT(2) ;END OF LOOP
O084 9C9C JNZ NEXT
O086 3F XPPC 3 ;RETURN
;
O000 .END

```

Fig. 6. Program for an Mk14 will multiply two numbers together to give an answer of up to 64 digits.

Group magazine 'Complement and Add' where the program first appeared.

The two numbers to be multiplied are stored in BCD format, two decimal digits per byte; the first number may be up to 30 decimal digits long, and the second up to 32 decimal digits long. The result is produced as a

BCD number of up to 64 digits. The program is surprisingly short, yet takes only two seconds, on average, to perform the calculation.

The numbers should be entered into memory as follows:


- OB00 Highest digits of first operand
- OB0F Lowest digits of first operand
- OB10 Highest digits of second operand
- OB1F Lowest digits of second operand

The program should then be executed from OF12, and the answer will be put into memory as follows:

- OB20 Highest digits of answer
- OB3F Lowest digits of answer.

INVERTED CHARACTERS ON VDU

The Mk14 VDU interface can be adapted to display reverse-video characters (black character on white background) mixed in with normal characters (white character on black background) with the addition of the simple circuit shown in Fig. 7. The circuit was sub-

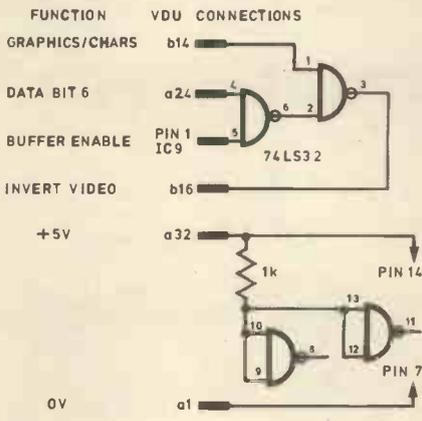

EG 368

Fig. 7. Circuit to enable an Mk14 VDU to display characters in inverse video.

mitted by Anthony D. Love of Swansea, and is designed so that the state of bit 6 of the character determines how the character is displayed. If the bit is zero, the character is displayed in reverse video; otherwise it is displayed normally. Thus, for example, X'41 will give an A displayed normally, and X'01 will give a reversed A.

CIRCUIT OPERATION

The circuit checks that the byte presented on the data bus is in fact for display by checking that the tri-state address-line buffers are enabled; i.e. that pin 1 of IC9 or IC10 is low. The graphics/characters input is also checked to ensure that the VDU is in character mode and, if not, sets the invert-video input high to prevent the circuit from interfering with the graphics.

The necessary logic is contained in a 74LS32 Quad 2-input OR gate package, which should be situated as close as possible to the VDU board. All the unused inputs are connected through a 1k resistor to the positive supply rail.

DIGITAL ALARM-CLOCK

The following program will make an Acorn (System One) function as an alarm clock. The time is displayed as 'hours-minutes-seconds' on the 7-segment displays, and at the set alarm time A's replace the dashes on the displays and the output line PBO oscillates at 0.5 Hz so that a buzzer or relay can be operated; the normal display is resumed after one minute. The program, shown as a hex dump in Fig. 8, was submitted by Peter Mayne, whose 'Data Find Routine' was featured in the last Micro-Bus.

```

DIGITAL ALARM CLOCK
0200 A9 01 8D 23 09 F8 A2 03
0208 20 0C FE 0A 0A 0A 0A 85
0210 60 20 0C FE 65 60 95 20
0218 CA 0D ED A9 77 85 10 A2
0220 24 20 88 FE A9 1F 85 0E
0228 A9 40 85 15 85 12 A0 06
0230 A2 01 B5 20 20 6F FE 88
0238 88 88 E8 E0 04 D0 F3 A2
0240 2C 20 0C FE CA D0 FA A2
0248 01 B5 20 18 69 01 95 20
0250 C9 60 D0 09 A9 00 95 20
0258 E8 E0 04 D0 EC A5 15 C9
0260 77 F0 12 A2 1C 20 A6 FE
0268 D0 C4 A9 77 85 15 85 12
0270 8D 18 09 D0 F3 A5 25 C5
0278 23 D0 ED 8D 08 09 4C 28
0280 02


```

Fig. 8. Hex dump of a digital alarm-clock program for the 6502-based Acorn microcomputer.

To set up the clock execute the program from 0200. You should then enter the correct time as a sequence of six digits; for example, at 7:30 and 20 seconds enter '073020'. Then enter the alarm time as a sequence of four digits; for example, if the required time is 7:31 enter '0731'. Finally type any control key to start the clock. The speed at which the clock runs is controlled by the value at 0240; since the Acorn runs from a 1 MHz crystal the clock can be extremely accurate.

ADDENDUM

The following modifications to the 'Low-Cost SC/MP System' which appeared in the April Micro-Bus are recommended by the author, Andrew Aitken.

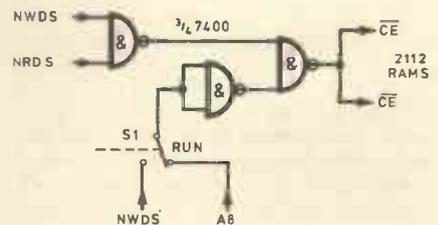

EG 369

Fig. 9. Modification to the 'Low Cost SC/MP System' in the April Micro-Bus.

In the main circuit of Fig. 3 the \overline{CE} signal to the RAMs should be gated with a signal which is high when NRDS or NWDS is active to prevent a conflict on the databus; see Fig. 9.

In the hex keyboard circuit of Fig. 4 the D input of the 7474 latch should be connected to the Q output, not to the \overline{Q} output as shown, so that the flip/flop will toggle correctly.



FRANK W. HYDE

FOR THE YEAR 2000

The year 2000 is the present target date for the Satellite Power System. Already some five years of intensive research has shown that there are many facets to the ultimate success, some with spin-off and some showing a whole new field of technology. In this issue of *Spacewatch* a general outline of what is to be the main approach to the utilisation of Solar Energy by the United States will be reviewed. This will show not only the magnitude of the concept but also the attention to the environment and the philosophy of living in the next century. It can be seen perhaps that the thinking is not only world wide in its operation but initiates the practical possibilities and benefits for mankind.

In this project is embodied the basic dreams for a future in which man turns technology toward the concept for "The resources of the Earth for the benefit of the people of the Earth" and leads that benefit toward every man, woman and child that lives and will continue to live on Planet Earth.

THE SYSTEM

The basic principle is the collection of the energy of the Sun and its conversion into electromagnetic waves transmitted to an aerial system on Earth where it is converted to a form suitable for the existing power lines. This, the Satellite Power System, is one of the possibilities of the tapping of the power of the Sun.

THE SATELLITE

This would take the form of a flat structure 10km long and 5km wide, and to this will be attached a high power beam antenna 1km in diameter. To it would be assembled the d.c.-r.f. power amplifiers and waveguides.

At the Earth end there will be the collecting antenna, which, because it rectifies the microwave beam from the satellite, is given the name of rectenna. This will be 13.2km by

10km at a location of 35° latitude. Other locations nearer the equator could be of different design.

The frequency of operation will be 2.45GHz. This frequency is chosen because it has been established that at a power of 23mW/cm² it will have negligible effect on the environment and human as well as animal life.

The satellite would be put first into a low earth orbit (LEO), then later raised to the geostationary orbit (GEO).

The first impact of the magnitude of the items in the satellite and the physical extent involved, leads to some queries. It is perhaps easier to accept the receiving antenna dimensions on the ground and be less concerned with any hazards that might be involved. Each situation needs some answers. In order to get the psychological aspect in perspective and relieve anxieties of misunderstanding, the fears will be answered in advance.

The question that first arises is the safety of such large units even at the distances from the Earth when geostationary orbits are considered. Questions like: will it be stable? Can it de-orbit like Skylab? Is it likely to be a danger to people on the ground? The answer is that the density of the atmosphere at the geostationary orbit level is very low and generally satellites are considered to have a very long lifetime; indeed theoretically an indefinite lifetime. The construction of the SPS satellite is however rather different from the usual type of satellite. It will have a much smaller mass to area ratio than previous satellites and would be more subject to atmospheric drag.

The SPS satellite has been designed for a 30 year life and the orbital decay would lie between 0.25 and 2,500 metres. That is less than one part in ten thousand in the worst condition. The other associated components such as the work platforms, the normal construction facilities, the personnel and their vehicles would be less influenced since these would have higher mass to area ratios. There will be perturbations from solar radiation and from lunar and solar gravity effects. Also there are the variations like the ellipticity of the Earth. These effects would be slightly larger than the atmospheric drag but it would be a normal part of station-keeping to correct such conditions.

NO HAZARD?

Perhaps the short answer is that there is no reason to suppose that there would be any increased hazard to these large assemblies and little likelihood of danger situations. The units can be large because gravity is small.

Another question that might be raised is: How vulnerable will the units be to random events like meteor showers? This is not very likely. The large scale is such that built-in redundancy would take care of this. It must however be said that overt action military or otherwise could do damage, but when examined this is unlikely except in case of deliberate hostilities. This aspect will be considered later.

Another question might be: What is the possible danger from terrorism or the activities of rivals. The answer here is that when the system is fully operational there would be 60 satellites and a similar number of ground units

(rectenna and associated facilities). Here the very nature of the organisation is such that normal security would be of such a nature as to take care of such possibilities. Therefore, short of war, the possibility is remote, since a pilot beam first is needed to enable the system and give the instruction to the satellite to focus the beam on the rectenna. If the transmitting antenna is pointed away from the rectenna the beam will at once de-focus. In this case there would only appear a level of background which would preclude any damage from the antenna pointed to the Earth.

One of the areas where doom thinking has taken root is the question of damage to the ozone layer and the creation of a "Greenhouse Effect".

The answer to this can be positive. Most of the ozone is between 10 and 40km in the Stratosphere. Intensive investigation of this area has continued over the past ten years. The effects from the effluents from SPS rocket launches is negligible. Above the 50km level the ozone is less than 1 per cent of the peak value in the Stratosphere. However there is the possibility that over the 70km level there may be an increase of ambient water concentrations. There are complex chemical mechanisms which control ozone at these levels, but is still not considered to be a hazard.


So far as the Greenhouse Effect is concerned, this is more difficult to deal with though there is no expectation that the situation would be aggravated by the advent of the satellites.

NEW NIGHT SKY

Some people are concerned about the aesthetic effects on the night sky. This has been considered carefully and the answer is that the satellites will be visible on clear nights. The actual brightness would be about 1/1000 of the light of the moon. In the night sky the satellites would be most noticeable at midnight and equivalent to the light of Venus. Binoculars with a magnification of seven would show them as rectangular objects and not as points of light. It could be said that they will enhance the aesthetics because of the general appearance. There would be a contrast between the random stars of the constellations and they would present an apparent straight line of objects of equal brightness. They would appear to be separated by a distance of slightly less than that of the stars in Orion's belt.

At intervals of six months, the satellites would be eclipsed and would pass through the Earth's shadow at about midnight for a number of days in succession. This would be an occurrence similar to a lunar eclipse. The satellites would first dim and then redden when reaching the edges of the shadow then darken and appear a few minutes later.

Consideration of these matters is continuing and being constantly updated. The next issue of *Spacewatch* will contain more technical details of the design and the conversion systems from the microwave transmissions to the feeding of the power lines for general distribution. After this aspect then, the possible effects on the future of meteorological conditions will be noted with the ecological and resource effects.

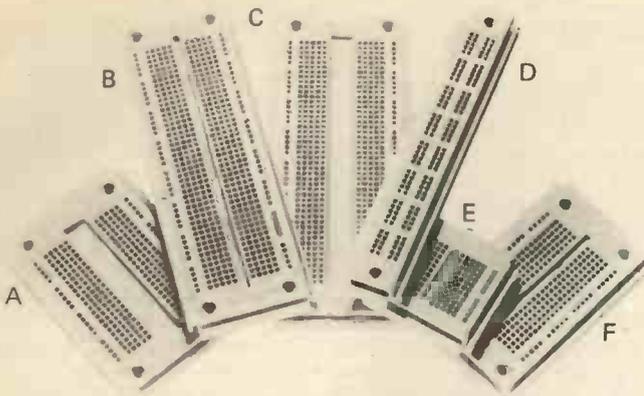

- A EXP 650 For microprocessor chips: £3.60
- B EXP 300 The most widely sold breadboard in the UK; for the serious hobbyist. £5.75
- C EXP 600 .6" centre channel makes this the Microprocessor Breadboard. £6.30
- D EXP 4B An extra 4 bus-bars in one unit. £2.30
- E EXP 325 Built in bus-bars accepts 8, 14, 16 and up to 22 pin ICS. £1.60
- F EXP 350 270 contact points, ideal for working with up to 3 x 14 pin DIPS. £3.15
- G PB6 Professional breadboard in easily assembled kit form. £9.20 (Not illustrated.)
- H PB 100 Kit form breadboard recommended for students and educational uses. £11.80 (Not illustrated.)

& IT'S AS EASY AS 1,2,3 with THE EXPERIMENTOR SYSTEM

- SCRATCHBOARD
- BREADBOARD
- MATCHBOARD

1. EXP 300PC which includes one item. A matchboard pre-drilled PCB - £1.32
2. EXP 302 which includes three items. Three 50-sheet scratchboard workpads - £1.68
3. EXP 303 which includes three items. Two matchboards and an EXP 300 solderless breadboard - £8.60.
4. EXP 304 which includes four items. Two matchboards and EXP 300 breadboard and a scratchboard workpad - £9.30

The above prices do not include P&P and 15% VAT

TOMORROW'S TOOLS TODAY

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited, Dept. 500
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682
Telex: 817477

NAME _____

ADDRESS _____

I enclose cheque/PO for £ _____
or debit my Barclaycard, Access, American Express card
No. _____ Exp. date _____
or Tel: (0799) 21682 with your card number and your order will be in the
post immediately.

A EXP 650 £5.00	Qty. Reqd.	B EXP 300 £7.76	Qty. Reqd.
C EXP 600 £8.39	Qty. Reqd.	D EXP 4B £3.50	Qty. Reqd.
E EXP 325 £2.70	Qty. Reqd.	F EXP 350 £4.48	Qty. Reqd.
G PB6 £11.73	Qty. Reqd.	H PB 100 £14.72	Qty. Reqd.

Experimenter System

1 EXP 300 PC £2.38	Qty. Reqd.	2 EXP 302 £2.79	Qty. Reqd.
3 EXP 303 £11.04	Qty. Reqd.	4 EXP 304 £11.85	Qty. Reqd.

Boxed prices include P & P and 15% VAT
If no dealer in your area contact CSC direct. FREE catalogue tick box

Continental Specialties Corporation, (U.K.) Limited, Dept. 500,
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex. Tel: (0799) 21682

AITKEN BROTHERS,

35 High Bridge, Newcastle Upon Tyne, NE1 1EW.
Tel: 0632 26729.

ARROW ELECTRONICS LTD.,

Leader House, Coptfold Road, Brentwood, Essex.
Tel: 0277 226470.

BASIC ELECTRONICS LTD.,

18 Epsom Road, Guildford, Surrey, GU1 3JN.
Tel: 0483 39984.

BI-PAK SEMICONDUCTORS,

P.O. Box 6, Ware, Herts.
Tel: 0920 3442.

F. BROWN & CO.,

45 George IV Bridge, Edinburgh, EH1 1EJ, Scotland.
Tel: 031 225 3461. Telex: 922131.

THE CHILDRENS SHOP & TACKLE BOX.,

73-75 High Street, Ryde, Isle of Wight.
Tel: 0983 63437.

CUBEGATE LTD.,

301 Edgware Road, London, W2 1BN.
Tel: 01 724 3565.

ETESON ELECTRONICS,

15b Lower Green, Poulton-Le-Fylde, Blackpool, FY6 7JL.
Tel: 0253 885107.

H. GEE ELECTRONIC SUPPLIES,

94a Mill Road, Cambridge, CB1 2BD.
Tel: 0223 358019.

LEEDS AMATEUR RADIO,

27 Cookridge Street, Leeds, LS2 3AG.
Tel: 0532 452657.

MARSHALLS,

108A Stokes Croft, Bristol.
Tel: 0272 426801.

85 West Regent Street, Glasgow, G2, Scotland.

Tel: 041 332 4133.

325 Edgware Road, London, W2.

Tel: 01 723 4242.

40 Cricklewood Broadway, London, NW2 3ET.

Tel: 01 452 0161.

RASTRA ELECTRONICS LTD.,

275-281 King Street, Hammersmith, London, W6.
Tel: 01 748 3143. Telex: 24443 RASTRA G.

SHUDEHILL SUPPLY COMPANY,

53 Shudehill, Manchester, M4 4AW.
Tel: 061 834 1449.

SPECTRON ELECTRONICS (M/C) LTD.,

7 Oldfield Road, Salford, M5 4NE.
Tel: 061 834 4583.

SWANLEY ELECTRONICS,

32 Goldsel Road, Swanley, Kent, BR8 8EZ.
Tel: 0322 64851.

TECHNOMATIC LTD.,

17 Burnley Road, London, NW10 1ED.
Tel: 01 452 1500. Telex: 922800.

TOMORROW'S TOOLS TODAY


Also ask your local stockist.

If no dealer in your area, contact CSC direct.

CONTINENTAL SPECIALTIES CORPORATION



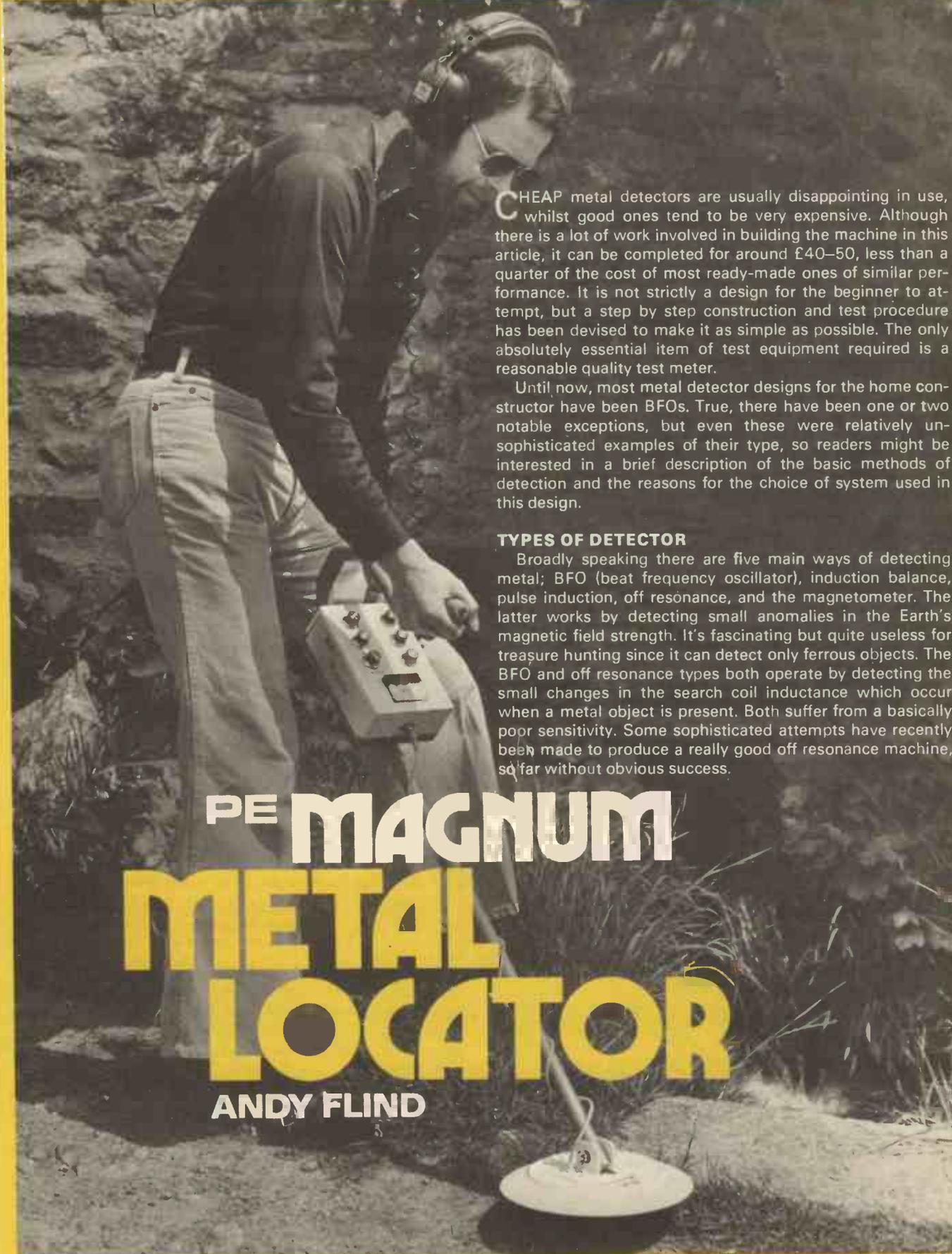C.S.C. (UK) Limited, Dept. 500
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682
Telex: 817477



CHEAP metal detectors are usually disappointing in use, whilst good ones tend to be very expensive. Although there is a lot of work involved in building the machine in this article, it can be completed for around £40-50, less than a quarter of the cost of most ready-made ones of similar performance. It is not strictly a design for the beginner to attempt, but a step by step construction and test procedure has been devised to make it as simple as possible. The only absolutely essential item of test equipment required is a reasonable quality test meter.

Until now, most metal detector designs for the home constructor have been BFOs. True, there have been one or two notable exceptions, but even these were relatively unsophisticated examples of their type, so readers might be interested in a brief description of the basic methods of detection and the reasons for the choice of system used in this design.

TYPES OF DETECTOR

Broadly speaking there are five main ways of detecting metal; BFO (beat frequency oscillator), induction balance, pulse induction, off resonance, and the magnetometer. The latter works by detecting small anomalies in the Earth's magnetic field strength. It's fascinating but quite useless for treasure hunting since it can detect only ferrous objects. The BFO and off resonance types both operate by detecting the small changes in the search coil inductance which occur when a metal object is present. Both suffer from a basically poor sensitivity. Some sophisticated attempts have recently been made to produce a really good off resonance machine, so far without obvious success.

PE MAGNUM METAL LOCATOR

ANDY FLIND

Pulse induction detectors are another matter however; good ones are very sensitive indeed and some of the most expensive detectors currently available are these. They operate by exposing the ground to powerful pulses of magnetism and listening between the pulses for signals due to eddy currents set up in any metal objects present in the field. Despite their sensitivity they have a couple of important drawbacks. Their battery consumption is heavy due to the power required by the pulsed transmitter, and they are extremely sensitive to even tiny ferrous objects. Their use is thus primarily restricted to beach searching, where objects are likely to be buried at considerable depths, and where large holes can be easily and rapidly dug. On inland sites, their users can become discouraged by the frequent digging of large holes in hard ground to recover rusty nails, etc.

This leaves the induction balance types which have become more or less the standard general purpose detector for both serious treasure hunters and detecting hobbyists alike. It has two coils in its search head, one of which is fed with a signal which sets up an alternating field around it. The other coil is placed so that normally the field around it balances and it has no electrical output. A metal object approaching the coils will distort the field, resulting in an imbalance so the the pickup coil will produce an output. This can be amplified and used to inform the operator of a "find" in a variety of ways. Frequently in simple detectors an audio modulated transmitted signal is used, the output from the pickup coil then being amplified and demodulated like an AM radio signal. There are many possible coil arrangements, but most detectors available today use one of the two shown in Fig. 1. Fig. 1(a) shows a "widescan" coil, so called because its most sensitive area (shaded) extends right across the coils. Fig. 1(b) shows a "pinpoint" type, also known as a "4B". In the author's experience the pinpoint is by far the better coil in use, as widescans have poor pinpointing ability and tend to give false signals for ferrous objects off centre, coins on edge and the like. It's noticeable that many of the best imported American machines use pinpoint coils.

DISCRIMINATION

All of this is fine, but there are a couple of extra refinements necessary in a really good metal detector. One of these is the ability to discriminate between unwanted junk such as silver paper, scraps of iron etc, and desired objects. The other is some means of eliminating false signals due to "ground effect". Ground capacitance effects can easily be prevented by Faraday shielding around the coils, but most inland soils contain a proportion of iron oxide which gives a signal similar to a piece of ferrite. Beaches wet with seawater on the other hand are slightly conductive, and this too causes false signals to be produced in the pickup coil. Obviously some means of "tuning out" these effects will improve the detector considerably.

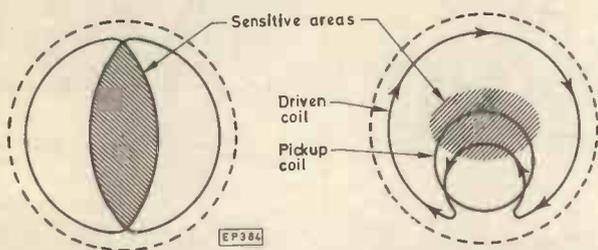


Fig. 1 (left). 'Widescan' coil layout; (right) 'Pinpoint' coil layout

Fortunately the signals from the search coil consist of more than just amplitude variations; they also contain information in the form of phase shifts which differ markedly according to the type of object causing the signal. With a relatively simple phase sensitive detector therefore, a machine can be designed which will totally reject ground effects and can also, with practice on the part of the user, eliminate the majority of the rubbish detected without the necessity of having to dig it up!

NOMENCLATURE




Some of the terms used by manufacturers to describe their machines in recent years have been somewhat confusing so, before we proceed, a note on these may not be amiss. 'VLF' stands for "very low frequency". The ability to discriminate from phase information against thin section objects like foil depends on frequency. At higher frequencies, 'Skin effect' eddy current conduction makes such discrimination ineffective. Therefore manufacturers began using lower and lower frequencies, at least one machine actually worked at less than 2kHz. This created problems of its own, as at such low frequencies sensitivity to cupro-nickel coins is not so good and "Q" problems arise in the coil design. Most detectors nowadays operate somewhere between 10 and 20kHz, where discrimination is still excellent but sensitivity and coil design problems do not arise.

"GEB" means "ground exclusion balance" and refers to the phase sensitive means of excluding ground effect. "TR" means "transmit-receive", and is often used to describe the discriminate mode, suggesting that the machines operate with different frequencies or coil configurations in the different modes—they don't; the only thing that is changed between modes is the phase reference point. It is not possible to avoid ground effect and discriminate at the same time, so one normally searches in GEB mode, and on finding an object, checks it with the discriminate mode before digging. Beer can pull rings can be rejected by the way, but machines capable of doing this will also reject any cupro-nickel coin smaller than a 10p when set to do so. It is probably better to tolerate the rings—many charities now collect these anyway.

BLOCK

Fig. 2 (dotted) shows a schematic of the Magnum detector. The drive oscillator sets up a field around the search coil, and the pickup coil is positioned so that it only gives an electrical output when a metal object distorts this field. The operating frequency of these stages is approximately 15kHz. Signals from the pickup coil are amplified, buffered and then inverted so that non-inverted and inverted versions of it are simultaneously available. These are fed to the two inputs of an electronic changeover switch, operated by a reference signal derived from the drive oscillator. This reference signal has first been passed through a phase shifting network which can be adjusted as required by the user. The output from the switch is passed through a 3rd order low-pass active filter with a cut-off point set at 40Hz, which removes practically all of the 15kHz signal, leaving only the average d.c. level.

Any given signal producing object causes changes in both magnitude and phase of the received signal, so by adjusting the phase shift network correctly a point can be found where these changes either cancel out or cause a net fall in the d.c. level, enabling unwanted signals from ground, foil, iron etc, to be eliminated. Incidentally, most similar designs to date have used either pulse sampling phase detectors, or have selected only half-cycles of the input signal. The use of the

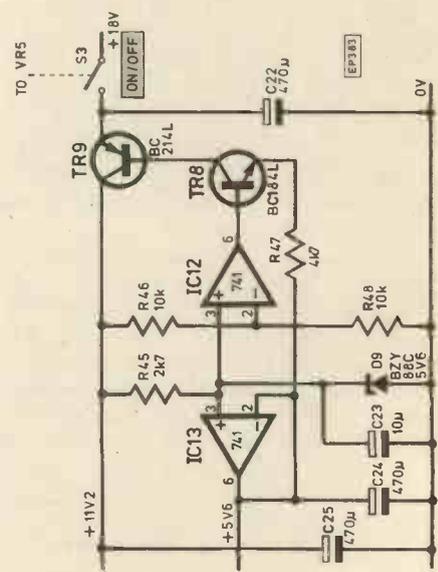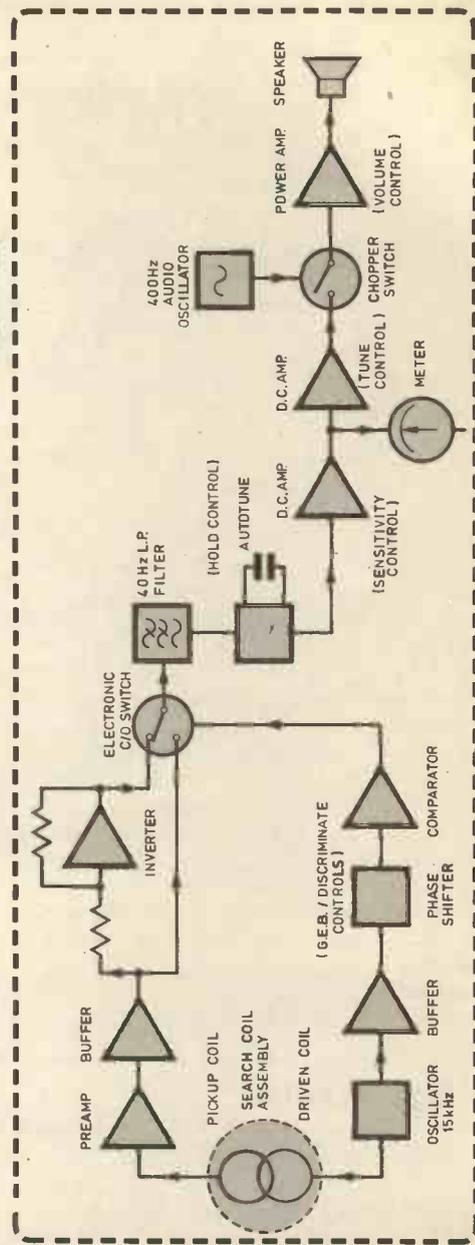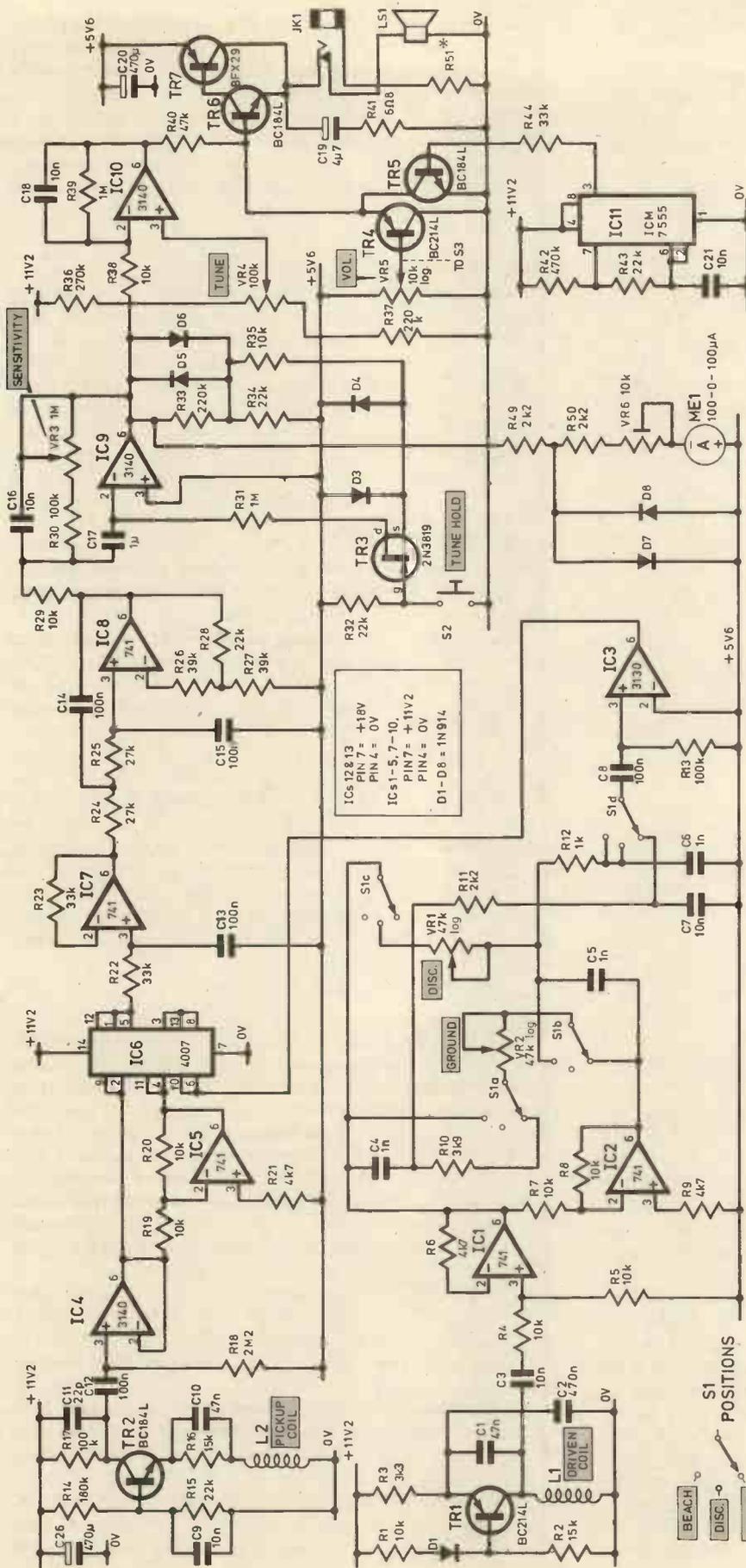

inverter and changeover switch requires very few extra components and greatly improves the signal-to-noise ratio, ultimately resulting in more sensitivity.

After the filter, the d.c. signal is amplified. It is only changes in the signal that are of interest, so a means of "tuning out" the initial standing d.c. level is required. In simple machines this is a manual control, but the need for readjustment after each operation of the phase controls—say switching from "ground" to "discriminate"—makes some form of automatic tuning desirable. On most commercial machines a "tune" button resets the output to zero every time it is pressed, but these are notoriously prone to drift. Attempts to use continuously resetting systems have been made, but this tends to lower the overall sensitivity as most manufacturers use rather crude filtering, resulting in considerable delay in the response to a detected object. In effect the autotune tries to reset the output to zero at the same time as the detected object is trying to cause it to rise! The highly efficient filtering used in this design ensures an instant response to a signal, so a continuously resetting tuning system can be used. This does away with all the drift problems, and allows the machine to be used continuously at maximum sensitivity if required. A "freeze" button is provided to stop the tuning action whilst pinpointing the exact position of finds or discriminating.

After the autotune and amplifier stage the signal is fed to a centre-zero meter; in "discriminate" this indicates positive for "good" finds and negative for "bad" ones. Then it goes to a further amplifier with a control which sets the point at which the audio output is to start. The output from this is of course still d.c., so it is chopped up by an audio oscillator, providing a signal which only needs a power output stage to drive the loudspeaker.

CIRCUIT

Fig. 2 shows the complete circuit of the machine. TR1 and associated components form the drive oscillator, which provides a very pure 15kHz sinewave output. IC1 buffers part of this signal and the circuitry around IC2 introduces the phase shift as required. In "ground" the available shift is about -10 to $+40$ degrees, whilst in "discriminate" and "beach" it is about 0 to -170 degrees. IC3 is a comparator; the 3130 was chosen for its high slew rate and good output drive signal for the CMOS switch IC6. TR2 is the received signal preamp and is connected as a common base amplifier. This and oscillator TR1 are both based on designs which have been used in several manufactured machines because they are simple and work well. The receive coil L2 is untuned; this, coupled with the low impedance input load of TR2 ensures the predictable phase response required for reliable discrimination. The output of TR2 is at high impedance so IC4 acts as a buffer, whilst IC5 is a unity gain inverter. IC6 is connected as a CMOS electronic changeover analogue signal switch. IC7 and IC8 together are the 3rd order low-phase active filter.

IC9 is a d.c. amplifier and also the auto-tune stage. The action of this is probably easier to understand if one first considers an ordinary op-amp inverting amplifier, as shown in Fig. 3. If the +input is at 0 volts, the -input must also be at 0 volts, so if a voltage is applied to the input resistor R_{in} the output will change until it restores the 0 volts at the -input via R_f . Now consider the effect of placing a capacitor at point "x". If the output is connected directly to the -input, it will go to 0 volts. If at the same time a voltage is applied to R_{in} , the capacitor will acquire a charge. If the output is now disconnected from the -input it will remain at 0 volts because the capacitor will retain the charge necessary to

COMPONENTS

Resistors

R1, 4, 5, 7, 8, 19, 20, 29, 35, 38, 46, 48,—10k.
R2, 16,—15k
R3,—3k3
R6, 9, 21, 47,—4k7
R10,—3k9
R11, 49, 50,—2k2
R12,—1k
R13, 17, 30,—100k
R14,—180k
R15, 28, 32, 34, 43,—22k
R18,—2M2.
R22, 23, 44.—33k
R24, 25,—27k
R26, 27,—39k
R31, 39,—1M.
R33, 37,—220k
R36,—270k
R40,—47k
R41,—6R8
R42,—470k
R45,—2k7.

Potentiometers

VR1, 2,—47k log carbon.
VR3—1M lin. carbon.
VR4,—100k lin. carbon.
VR5,—10k log. with switch.
VR6,—10k preset, sub min horizontal.

Capacitors

C1, 10,—47n polyester
C2,—470n polyester
C3, 7, 9, 16, 18, 21,—10n polyester
C4, 5, 6,—1n polystyrene
C8, 12, 13, 14, 15,—100n polyester
C11,—22p polystyrene
C17,—1 μ polycarbonate
C19,—4.7 μ 63V electrolytic
C20, 24, 25, 26—470 μ 16V electrolytic
C22,—470 μ 25V electrolytic
C23,—10 μ 25V electrolytic

Diodes

D1 to 8,—1N914.
D9—BZY88C 5V6, 5.6 volt Zener.

Transistors

TR1, 4, 9,—BC214L
TR2, 5, 6, 8,—BC184L.
TR3—2N3819.
TR7—BFX29.

Integrated Circuits

IC1, 2, 5, 7, 8, 12, 13,—741 8-pin d.i.l.
IC3,—CA3130 8-pin d.i.l. or T079.
IC4, 9, 10,—CA3140 8-pin d.i.l. or T079.
IC6,—4007UBE (CMOS).
IC11,—ICM7555—low power 555 timer 8-pin d.i.l.

Miscellaneous

S1, 4-pole 3-way rotary switch, S2, pushbutton, miniature, press to make, Meter, 100-0-100 microamp centre zero, LS1—2 $\frac{1}{2}$ in. 8ohm Loudspeaker, 12 off 8-pin d.i.l. i.c. holders, 1 off 14-pin d.i.l. i.c. holder, 5-pin DIN plug and socket, Headphone socket, 3 PP3 battery clips, 32 and 36 SWG enamelled copper wire, 5A bare tinned copper fuse wire, 2 metres of 4-core individually screened cable, Case, Vero type 75-1411-D, 6 control knobs, approx 25mm skirt, Plus plastic plumbing components, "Melaware" plate, glassfibre repair kit etc. to make coil, stem and handle—see text.

Kits available from **Maplin Electronic Supplies Ltd.**

offset the input voltage. A change in the input voltage will now be reflected in a change in the output voltage, the gain being given by R_f/R_{in} . In this way an amplifier can be constructed using only one op-amp which will offset large d.c. input voltages and yet provide high d.c. amplification of very small input voltage changes.

In the main circuit TR3 provides a means of connecting the output to the -input. The output is divided by R33 and R34 and fed through R31, so that the reset rate is relatively slow but continuous, as TR3 is normally conducting. If the tuning error is very large however, as it would be after switching on or operating the discriminating controls, D5 or D6 will conduct and greatly accelerate the tuning rate. D3 and D4 prevent the gate junction of TR3 from becoming forward biased at any time.

VR4 sets the threshold of IC10 and is normally adjusted so that its output is at negative rail voltage. On receipt of a signal it rises towards positive. IC11 is a low-power 555 timer connected as an astable oscillator, giving very short (about 100 microsecond) negative pulses at about 400Hz. Thus TR5 is normally on and turns off only during these pulses so after R40 any output from IC10 is chopped into short positive going pulses. This is the ideal waveform to create lots of noise with an economic power consumption. The volume control in a design such as this is normally only required to limit the maximum noise level, so in this design VR5 and TR4 act as an adjustable clamp. In this way the sensitivity is not reduced if the volume has to be kept turned down. TR6 and TR7 are a complementary Darlington pair, their current gain enabling the signal to drive the loudspeaker or headphones.

SUPPLIES

Two separate power supplies are used in this machine. The bulk of the circuitry is supplied with 18 volts from two PP3 batteries in series, regulated by the circuit around IC12 and IC13. With so many op-amps it's easier to arrange the design around a centre-tapped supply, so the reference generated by the Zener is buffered by IC13. It is then doubled by IC12, TR8 and TR9, to give a regulated positive rail of twice the Zener voltage, nominally +11.2 volts. This arrangement has been used in preference to an integrated regulator since it will operate until the battery voltage has fallen to only 0.1 volt above the regulator output. Most integrated regulators require a differential of at least 2 volts, which in practice means that the batteries have to be replaced rather more frequently. The total power consumption of all this circuitry is about 20mA, less than many radios at normal volume.

Power for the loudspeaker output stage comes from a separate 9 volt battery, as this is the simplest way of avoiding decoupling difficulties in this very sensitive circuit. An extra PP3 is far smaller than the decoupling capacitors which would otherwise be required! Only the one power supply switch is required as the output draws no current unless an input signal is present.

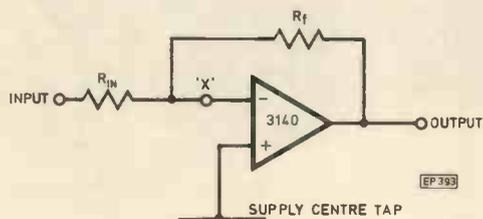


Fig. 3. Op-amp inverter

CONSTRUCTION

Construction is on two printed circuit boards and should be adhered to as this is a very sensitive circuit indeed; the result of any changes may well prove to be severe instability!

The two boards are stacked vertically in the final assembly resulting in a control box which is smaller and neater than many very expensive manufactured products.

The board containing the power supply, autotune and output should be built first as the power supply will be required for testing the "front end" board (Fig. 5).

ASSEMBLY DETAILS


Start construction by fitting the six links. The fit R45 to R48, C22 to C25, ZD1, TR8, TR9, IC12 and IC13. Apply the 18 volt battery via a 100mA meter and a 220 ohm series resistor, which will limit the current if any faults are present. It's as well to use this resistor throughout the testing of both boards. After a brief surge as the electrolytics charge the current should settle to about 5mA. Check that about 11 volts appears across C25, and about 5.5 volts across C24. This completes the power supply section.

Continue by fitting R40 and R41, C19 and C20, TR6 and TR7. Hook up the speaker, apply the 9 volt power supply via the 100mA meter and a 100 ohm resistor, again in case a fault is present. After a brief surge the current drawn should drop to zero. A finger on R40 and the battery positive at the same time should cause a crackle and an indicated current flow. Fit R42 to R44, C21, TR5 and IC11. IC11 is the low-power 555 timer; despite the manufacturers' notes to the contrary these are a little sensitive to handling so treat it with care and use a holder. I.c. holders are advisable throughout in fact; there is ample room for them. Apply both power supplies. A finger on 9 volts positive and on R40 should now produce the 400Hz output tone, albeit possibly at rather low volume. After this the 100R resistor can be left out of the 9 volt supply during testing, although the 220R in the 18 volt supply should be retained. Fit TR4 and hook up VR5. Apply power supplies, place fingers on R40 and 9 volts positive, and check that the volume can be controlled with VR5. This is one of those many jobs in electronics for which one requires three hands!


Fit R33, R34, R36 to R39, C18, and IC10. IC10 may be in



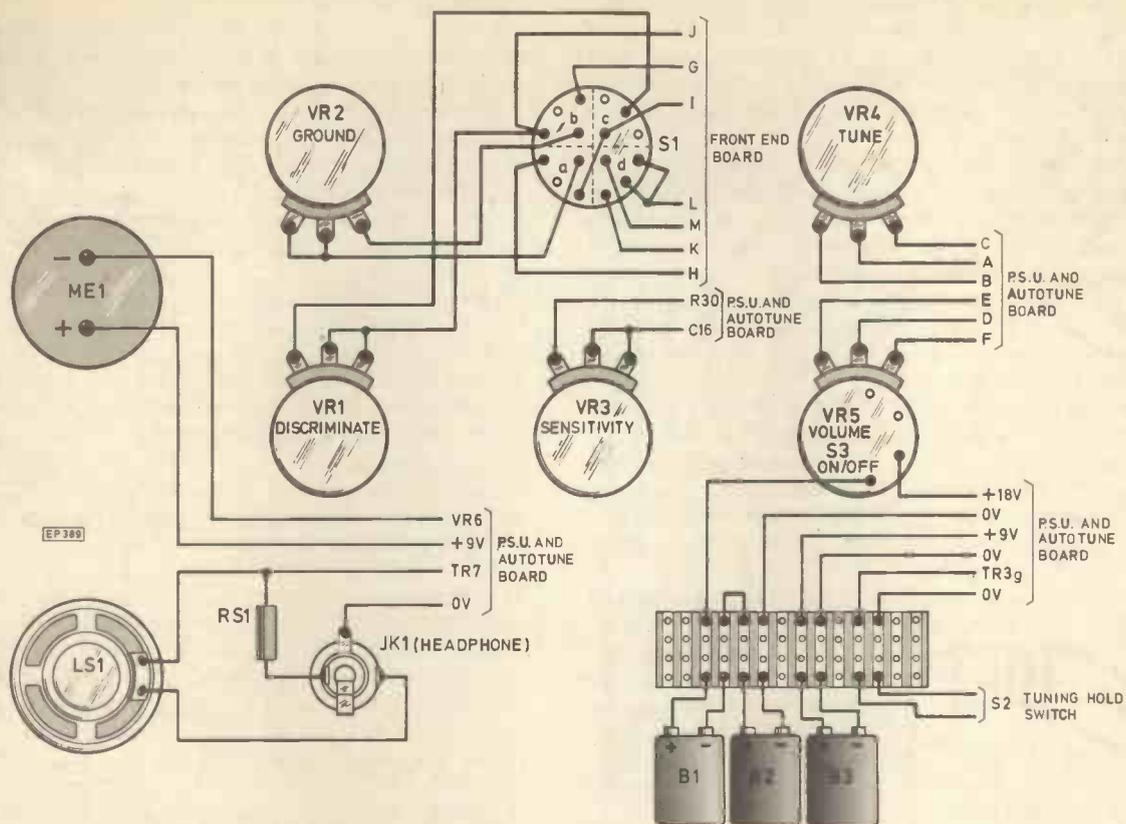
Control fascia of P.E. Magnum detector. Note 'Tune Hold' switch on handle.



BOARD ASSEMBLIES

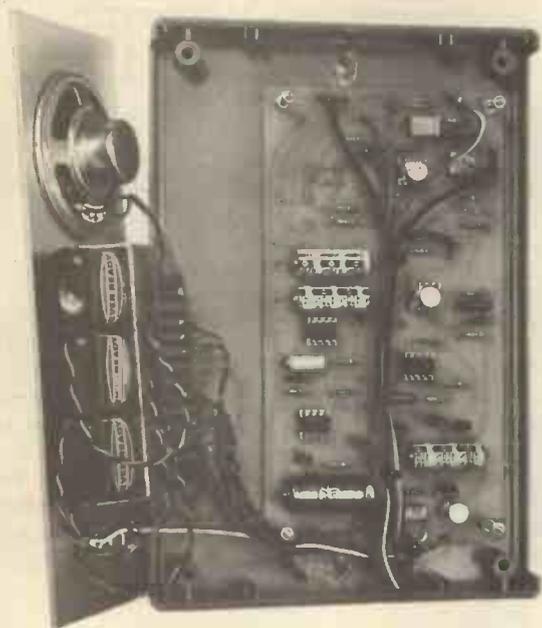

Power supply, autotune and output board

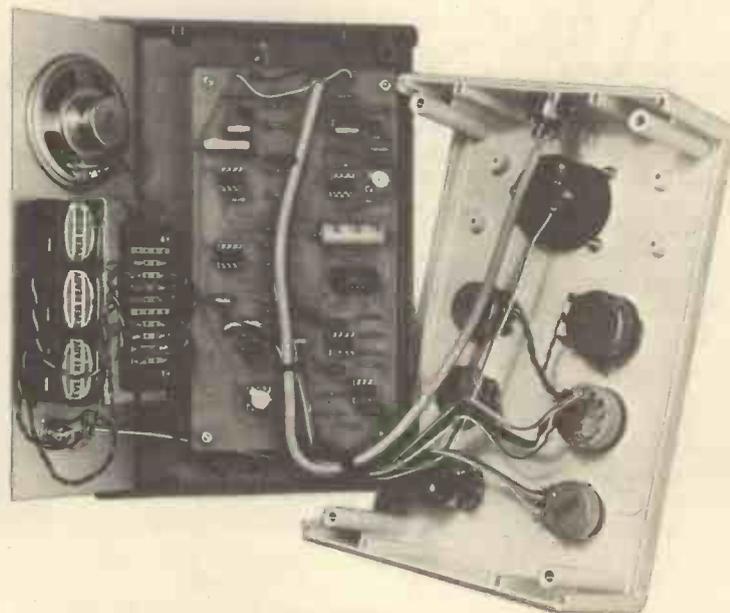

Front-end board in position


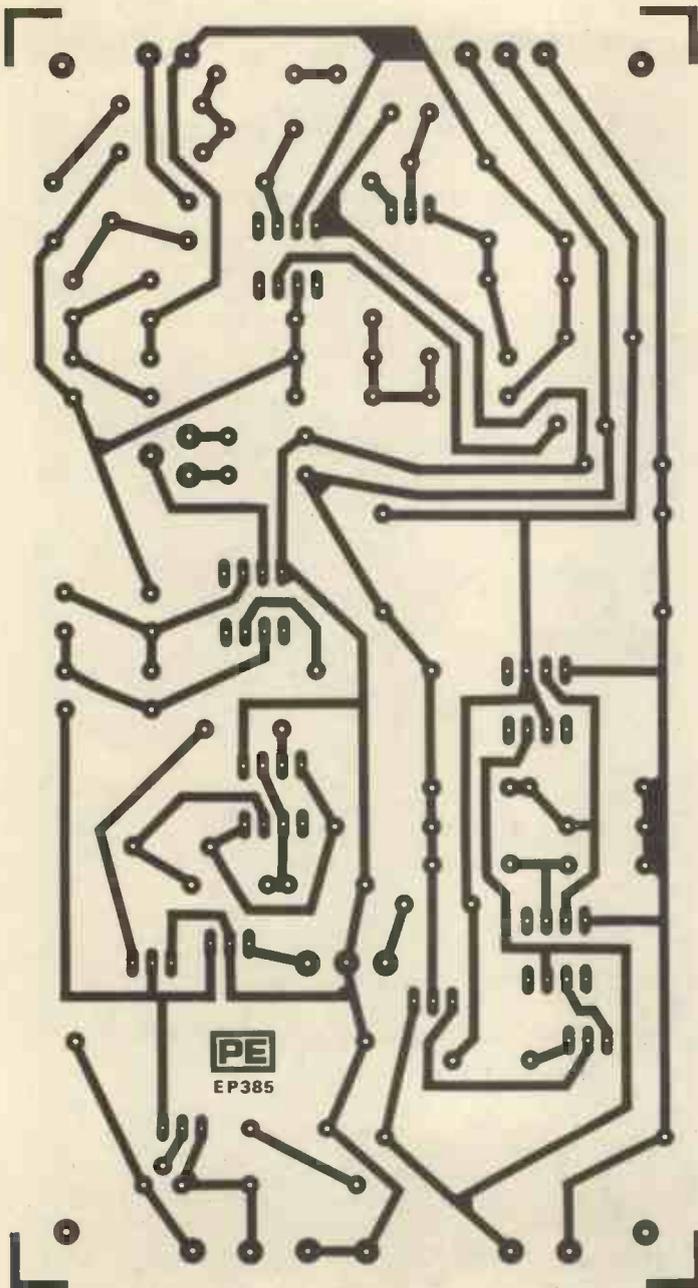


Fig. 5. Etching detail and board layout for power supply, autotune and output

either an 8-pin d.i.l. package, or the round metal T079 version. You can now hook up VR4 and apply power. It should be possible to turn the output tone on and off with VR4—gradually, since the input of IC10 at this stage is effectively taken to the supply centre-tap via R33 and R34 which reduces its gain somewhat. If there is no output tone check that the volume isn't turned right down.

FINAL TEST

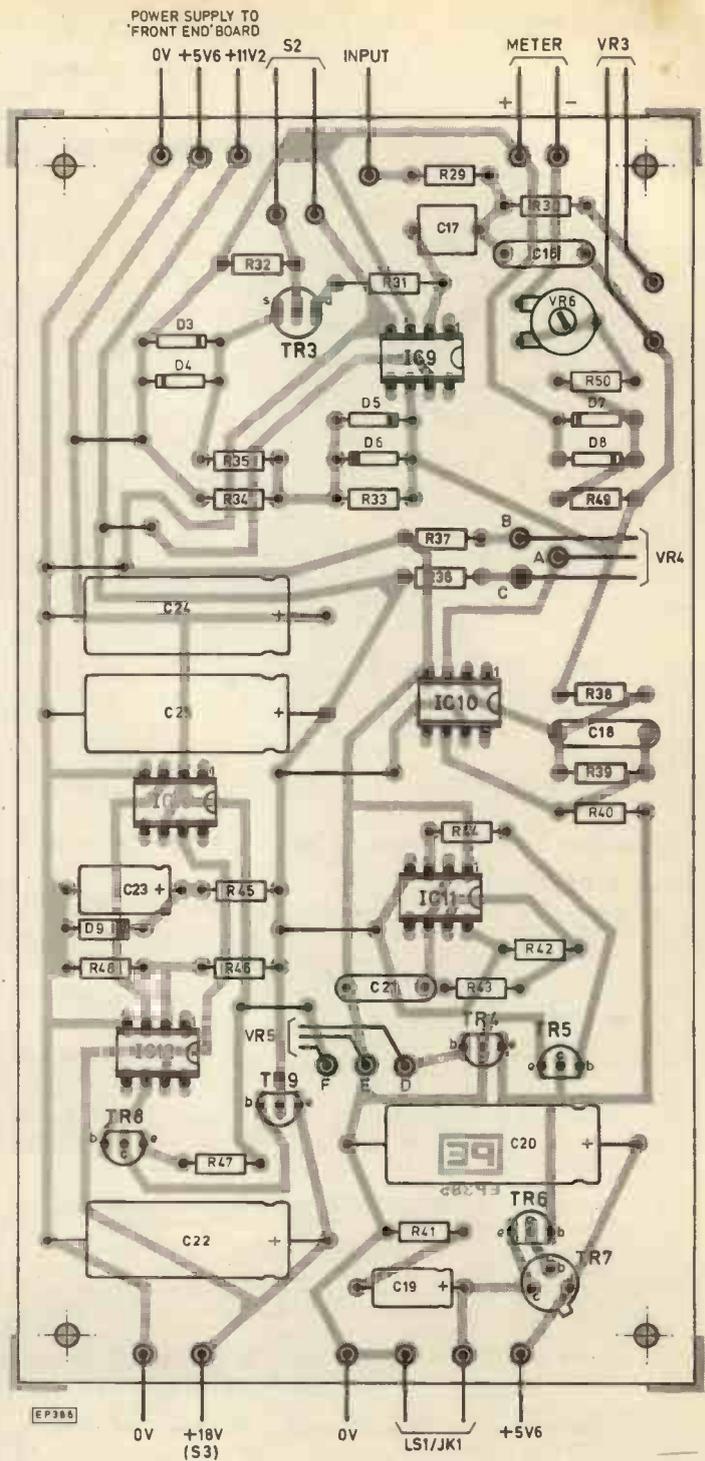
Fit all the remaining components to this board. Hook up S2, VR3 and the meter. Short the input point to the battery centre-tap. Apply power; the meter should return to zero within a couple of seconds due to the autotune action. Adjust VR4 to just below the tone threshold point. Touch the



18 volt battery positive with one hand, and, taking a 10M resistor in the other, touch the top end of R29 via the resistor. This should produce a brief burst of tone and a positive jump on the meter, which will then return to zero. Repeat this procedure whilst pressing S2—the sound and meter deflection produced should then be continuous. Press the button, and touch either of the 18 volt battery leads and the bottom of C17. This should cause the meter to drive fully up or down, and its full scale deflection can then be adjusted with VR6.

Next month: details will be given of the remainder of the construction and using the detector.

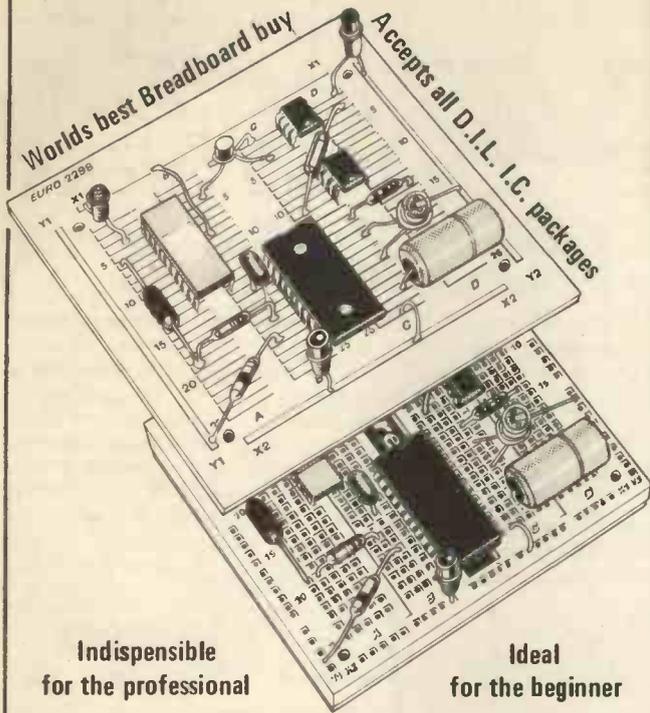**First the EuroBreadBoard
Now the EuroSolderBoard**



Design on a EuroBreadBoard — Instal on a EuroSolderBoard

First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths. All rows and columns numbered or lettered for exact location indexing (ideal for educational projects) Long life, low resistance (<10m ohms) nickel silver contacts £6.20 each or £11.70 for 2 including 1 or 2 EuroSolderBoards FREE

Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-tinned tracks identically laid out, numbered and lettered to EuroBreadBoard pattern. Four 2.5mm dia fixing holes. £2.00 for set of three ESB's or FREE with every EuroBreadBoard)

And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales, Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

David George Sales,
Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.
Please send me:-


- | | | | |
|-----------------------|----------|-----------------------|--------|
| 1 EuroBreadBoard | @ £6.20 | <input type="radio"/> | |
| or 2 EuroBreadBoards | @ £11.70 | <input type="radio"/> | Please |
| or 3 EuroSolderBoards | @ £2.00 | <input type="radio"/> | Tick |
| or 1 EuroSolderSucker | @ £7.25 | <input type="radio"/> | |

All prices are applicable from Jan. 1st 1980 and include VAT and PP but add 15% for overseas orders.

Name
Company
Address

Tel. No
Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing PE.8.

All these advantages...

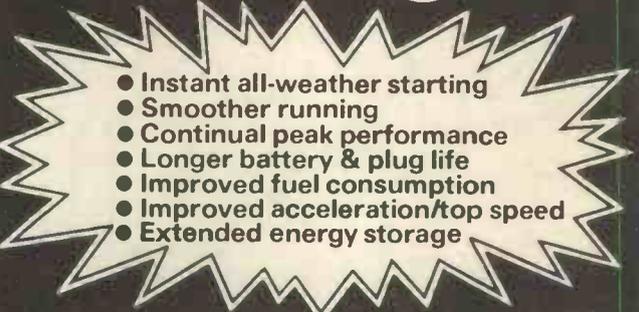

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light, systems function light and security changeover switch. Will work all rev counters.



Fits all 12 v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed case. Ready drilled aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite

HIGH PERFORMANCE
ELECTRONIC IGNITION

Electronics Design Associates, Dept. PE1179, 82 Bath St., Walsall, WS1 3DE

Electronics Design Associates, Dept. PE 8/80
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____
Address _____

Phone your order with Access or Barclaycard
Inc. V.A.T. and P.P. QUANTITY REQD. I enclose cheque PO's for
X5KIT £16.95 £
ACCESS OR BARCLAY CARD No. _____ Cheque No. _____
Send SAE if brochure only required

PATENTS REVIEW...

Copies of Patents can be obtained from :
the Patent Office Sales, St. Mary Cray, Orpington, Kent Price 95p each

LOW-LIGHT VIEWFINDER

English Electric Valve Company Ltd. patents (BP 1 559 586, filed in 1976 under the old laws) a greatly simplified low-light tv system. Such a system can, for example, be used as the viewfinder for a camera operating in the invisible infra red (or ultra-violet) regions. Normally an infra-red camera, with a vidicon tube of the thermal-imaging or pyro-electric type, requires a separate monitor as a viewfinder which in turn requires external synchronization. This is expensive and the aim is to provide an inexpensive viewfinder built into the camera.

In many respects the new invention borrows from ideas as old as television—i.e. mechanical scanning by synchronously locked discs in the Baird system. A pyro-electric tube produces an output signal only when its target area is either heating up or cooling down under the influence of infra-red. No output is produced in a steady state condition so the tube must be associated with a shutter which regularly interrupts the infra-red image. Normally, the tube target gives a positive signal from areas that are warming up and a negative signal from areas that are cooling down. The negative signals are then all inverted electronically

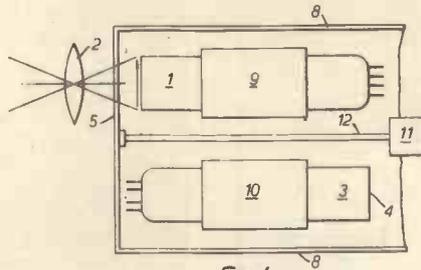


FIG. 1.

Figure 1 shows a camera with a pyro-electric pick-up tube 1 and an imaging lens 2. Monitor display tube 3 provides the reconstituted image on phosphor screen 4. The image from lens 2 is chopped by cylindrical shutter 5 which rotates with a cylinder 8 on axis 12 around both the pick-up and display tubes. The shutter can provide one cut-off per revolution (Figure 2) or two cut-offs per revolution (Figure 3). The crux

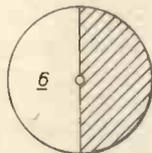


FIG. 2.

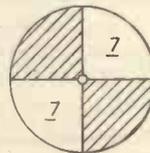


FIG. 3.

of the invention is the provision of deflection coils on the body of the cylinder 8. These thus rotate in mechanically locked synchronism with the shutter; so both the tv tubes display a deflection pattern which is synchronously locked irrespective of the speed at which the cylinder rotates.

An AC scanning field is fed to the deflector coils and the reproduced picture is superimposed on a tv raster pattern. Although, as shown in Figure 5, this may

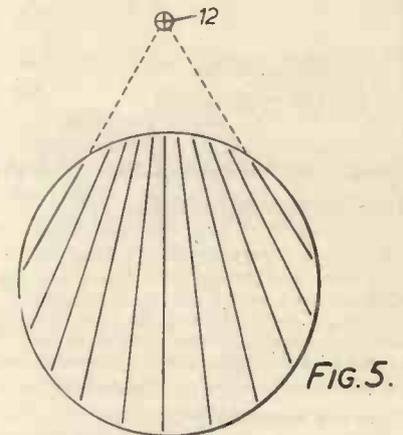


FIG. 5.

well be non linear, i.e. the raster lines may be non parallel, this is of no consequence. Both the camera tube and the display tube are mechanically locked to exactly the same scan pattern, so the displayed picture shows no distortion of shape.

News Briefs

THIRD MADLEY AERIAL

WORK HAS started on a new space communications aerial for the PO at Madley in Herts. This erection is necessary to keep pace with the enormous volume of overseas telephone calls from the UK, currently ten million a month, and doubling every four years. With telex and computer data increasing as fast, the £7.5m project will add to the satellite earth station's £17m worth of existing hardware. The PO is spending an overall £1000m annually on new plant to constantly update Britain's communications with the rest of the world.

A £3m contract goes to Marconi Communications Systems, who will supply everything except the dish itself, and its control electronics and receivers. The remainder of the aerial and its electronics will be supplied by the Mitsubishi Electric Corporation. To be completed in

1981, the aerial will work with a satellite in a geostationary orbit 23,000 miles above the Indian Ocean, one of the eight satellites now operating the Intelsat (International Telecomms Satellite Organisation) global system. "Madley Three" will be a 32m diameter dish capable of transmitting 2000 telephone calls and two TV programmes simultaneously. Its satellite is capable of handling up to 12,000 calls at once.

TI 58/59 CLUB

A NATIONAL TI 58/59 calculator club has been started by Mr. R. M. Murphy of the Dept. Electronics Engineering, University College Swansea, Singleton Park, Swansea.

The basis of the club will be direct exchanging of programs, or purchase of programs at 50 pence each. There will be a newsletter every two months, and since a PDP 11/32 computer is to be used for administration, the club should be very efficient. Guide books on conversion, upgrading and such things as a cheap cassette interface, will be available.

Work is taking place to interface a SC/MP micro to the calculator to drive a 10-digit, 16-segment alphanumeric display.

Membership will cost £5, or £3 to those who include a program plus flow diagram and instructions.

Constant Current Sources

I. MILLAR

WHEN dealing with purely electronic circuits, whose resistance changes little with time, it matters little whether one uses a constant current or constant voltage source, and indeed most electronic engineers are quite content to use the latter. However as soon as we move either to heavier current loads—where resistive heating becomes significant—or to more complex systems such as electrolyses, where total cell impedance depends on the sum of resistance through the electrolyte and *reaction impedance*, a constant current source becomes mandatory for any quantitative measurements. Briefly to elaborate on the foregoing terms, it will be obvious that passage of any significant current through the electrolyte will cause resistive heating and thus lower the solution resistance. In this, its behaviour differs from the resistance coefficient of a metal, which is of opposite sign. It will be noted that the sign of the solution temperature coefficient, like that of an electric arc or a fluorescent tube, could induce a runaway condition. The second component is the so-called reaction impedance, that is to say, the resistance to passage of current at the electrodes themselves. This is a function of electrode materials, their size and not least, the type of electrolysis taking place. In short, the simplest electrolysis can in practice require a voltage increase of 50% or more in order to maintain a given current. Nothing could better demonstrate the need for the type of equipment to be described here. Knowing that current remains invariant with time, enables us to perform experiments such as the experimental verification of Faraday's Laws, where total charge passed is current \times time. Then too, using the same principle, we can pass a known charge and thereby generate a given quantity of a chemical or a metal ion. Such techniques are widely used in analysis where they correspond to an electrochemical means of "weighing out" from a bottle, but are far more accurate in most cases. Used with an oscilloscope the constant current source can tell us about species adsorbed on an electrode surface, for as long as many species exist, the potential will change only slowly, if at all. Once they are all gone, it will rise sharply. Last but not least, by passing a constant current, and measuring the rate of potential change of an electrode, we can determine the effective capacitance, from the simple equation:

$$i = C \cdot dV/dt$$

That capacitance is directly related to surface roughness, or the presence of foreign species adsorbed on its surface. In short, this is a most useful tool.

Early constant current sources consisted simply of a high voltage—up to 100V DC connected across the electrolysis cell through a substantial resistance (which of course was required to dissipate a substantial wattage without too much temperature rise). But some years ago, solid state power sources began to find favour.

DESIGN AND SPECIFICATION

Our specification will depend on the purposes for which we use the constant current source, or galvanostat, as it is often known. The prime question relates to the current output. For such work, an output of 20mA will suffice, especially when electro-analysis is the major interest. But for much other work, such as studies in electrolysis of brine, or battery research, a higher output, such as 1–2A is more useful, in that it enables us to do what we wish on electrodes of reasonable size, say 1–5cm² in area. The second feature must of course be current stability, and this is defined both with respect to time, into a constant load, and also with respect to load variation, over a short space of time. A one per cent constancy would be the lowest acceptable value, while a figure such as 0.3 per cent would be better. Again, the effect of ambient temperature on output current should not be neglected here, and can be lumped into the above figures.

Finally we have two further specifications to meet. Ripple content should be less than 0.1 per cent and then there is the question of rise-time which depends very much on the proposed duty. But in some applications the device is switched onto load extremely fast, using a mercury-wetted reed relay or a CMOS and VMOS switch. Into a purely resistive load, the rise time should be fast—of the order of 1 microsecond.

Various circuits have been published, from time to time, which fulfil these specifications.

We shall show here the construction of two units. The simpler one, based on a design of Dr. Colin Vincent, of the University of St. Andrews, is a single transistor galvanostat.

It will deliver up to 22mA. The more sophisticated instrument is based on a design that was evolved at Salford University. It will deliver from 5 microamperes to 3 Amperes in 6 switched ranges. To extend the utility of the latter instrument, we have included a switch to convert it from constant current to constant voltage mode. The range switch and ten-turn potentiometer then provide a voltage range from 0V to 30V.

A further feature incorporated in this instrument is an input socket which allows an applied voltage function to control the current output as a function of time. Thus by application of a square wave voltage function, the corresponding current output will be produced. Suitable function generators are readily available commercially, though their construction will form the basis of a future article in this series.

20mA GALVANOSTAT

a) Circuit

The circuit consists of a full wave rectified power supply comprising:—T1, D1, D2, C1, C2 and R1 which delivers approximately 30V D.C. Transistor TR1 operates in the common base mode giving a very high impedance collector circuit. The current flowing in the load R_L (collector current) is determined by the voltage applied to the transistor base V_p and the value of R_3 , and is approximately equal to:

$$\frac{V_p - V_{BE}}{R_3}$$

where V_{BE} is the potential drop across the base emitter junction; this being about 0.6V for a silicon transistor.

Therefore the maximum load current for the circuit is

$$\frac{6.2 - 0.6}{270} = \text{approx. } 20\text{mA}$$

By varying the base voltage using VR1 the output current can be varied between 1 and 20mA. The circuit will keep the current constant to 0.1 per cent for 1 hour after reaching working temperature. In order to keep the circuit under load and at working temperature when not in use, a standby clearing load has been incorporated consisting of S2 and R4. The ability to supply maximum output current into high resistance loads is restricted by the available output voltage of 30V.

CONSTRUCTION

The circuit is constructed on a small printed circuit board no particular problems being envisaged.

The original circuit was constructed in a small metal box measuring 135 x 80 x 55mm.

CALIBRATION

The circuit was loaded with a 100 ohm 0.5 watt resistor and allowed to warm up for one hour.

The scale was then marked by adjusting VR1 and measuring the output current with a meter.

Fig. 1. Circuit diagram of 20mA Galvanostat

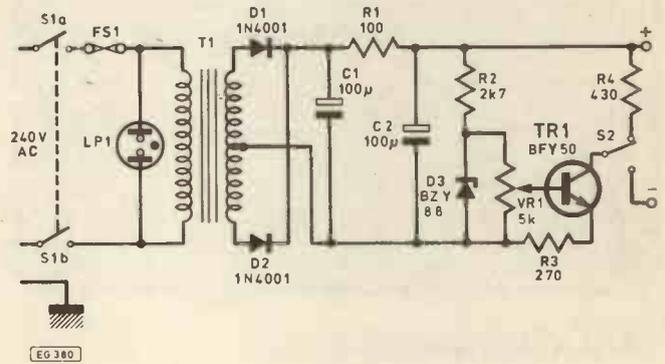


Fig. 2. Printed circuit (actual size)


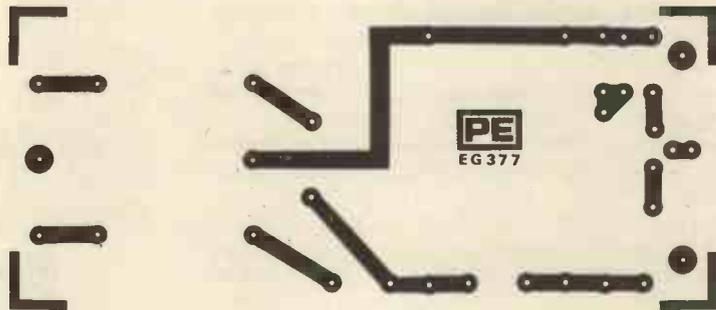


Fig. 3. Component overlay

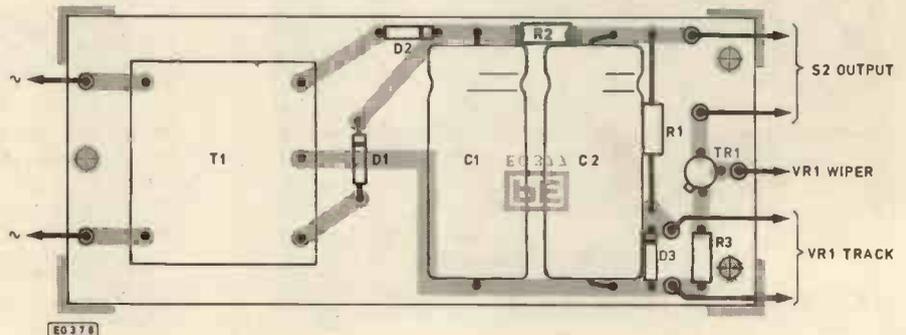

COMPONENTS . . .

Resistors

R1	100
R2	2k7
R3	270
R4	430

All 0.5W 2% Thick Film

Potentiometers

VR1	5k lin	1 watt wirewound
-----	--------	------------------

Capacitors

C1, C2	100 μ	63V Electrolytic (2 off)
--------	-----------	--------------------------

Semiconductors


D1, D2	1N4001 (2 off)
D3	BZY88 6.2V 400mW
TR1	BFY50 (2N3053)

Transformer

T1	240V primary 20-0-20 V r.m.s. Secondary 1.2VA printed circuit mounting R.S. Components 207-908
----	---

Miscellaneous

S1	DPDT Min. toggle
S2	SPDT Min. toggle
Fuseholder + 1A Fuse	
240V Neon	
P.c.b.	
Output socket	

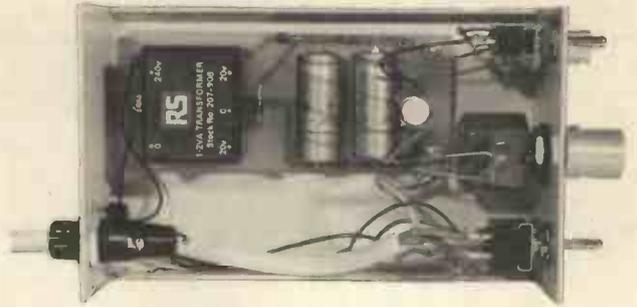

3A GALVANOSTAT

CIRCUIT

The circuit provides an output voltage of up to 30V d.c. at currents up to 3A.

The circuit functions as either a constant voltage or constant current power supply, depending on the position of function switch S3.


The output voltage or current is dependent on how much output transistors TR2 and TR3 are turned on by operational amplifier IC1, and TR1.

Initial setting of voltage or current is achieved by adjusting the voltage at the non-inverting input of IC1 using VR1 to vary the reference voltage derived from the Zener diode

stabilising network R1, D9, R2, D10 and C2. Resistors R3 and R4 determine the limits within which VR1 operates.

The circuit can be controlled externally, e.g. from a sweep generator via the external input socket SK1. For full output a control voltage of one volt d.c. is then required.

In the constant current mode, one of the resistors R8-R13, selected by range switch S4, is connected in series with the load. Voltage developed across this resistor is fed back to the inverting input of IC1 so that if the output current increases the voltage across R8-R13 will increase thus causing the output voltage of the circuit to decrease holding the output current constant. The reverse occurs should the output current drop.

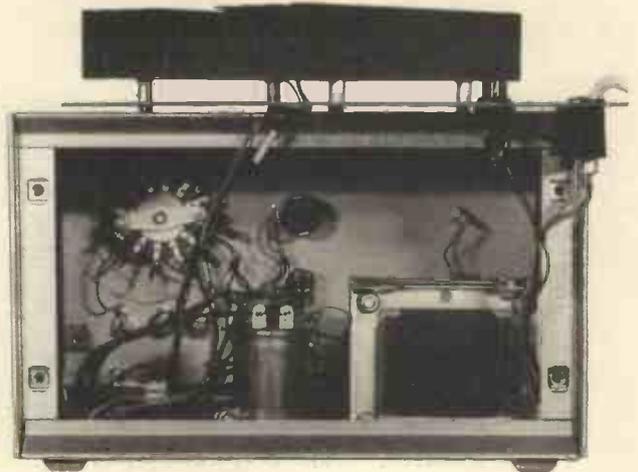

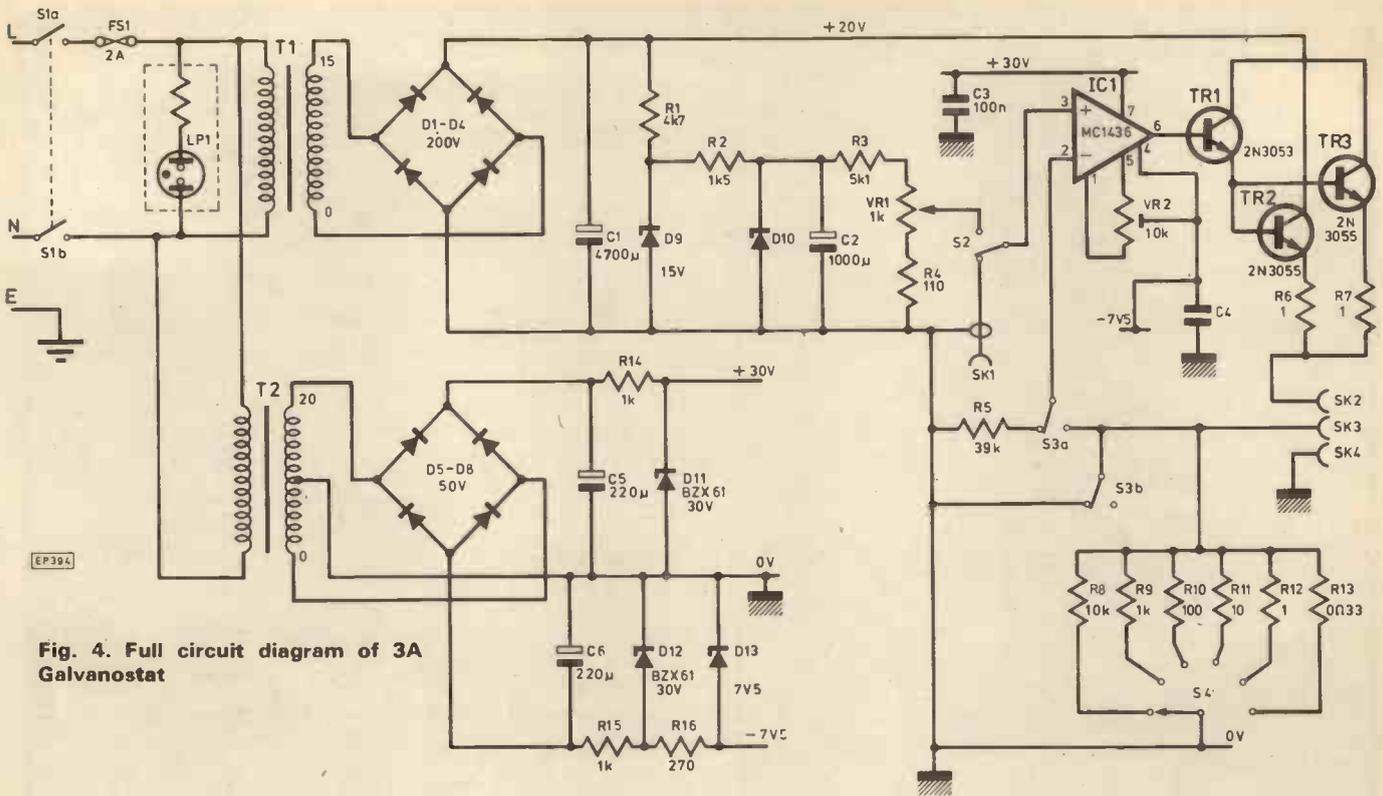


Fig. 4. Full circuit diagram of 3A Galvanostat

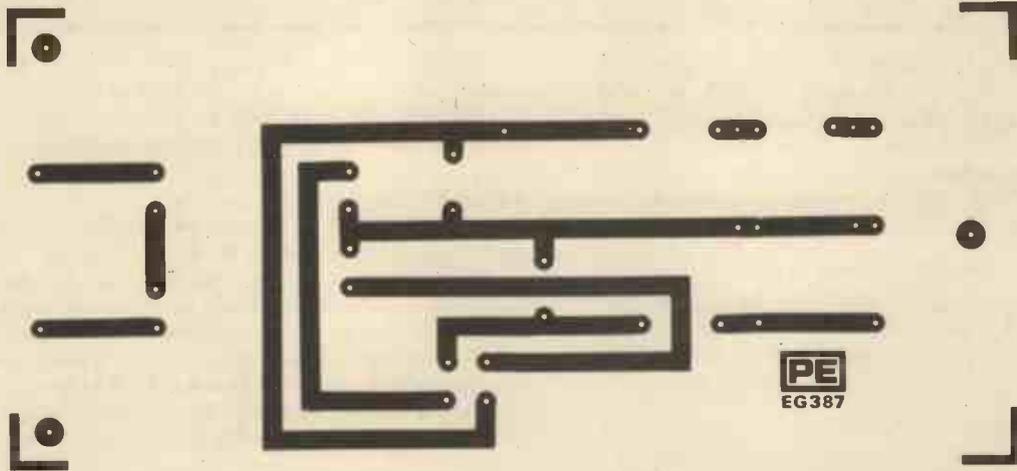


Fig. 5. Printed circuit for op. amp. power supply board (actual size)

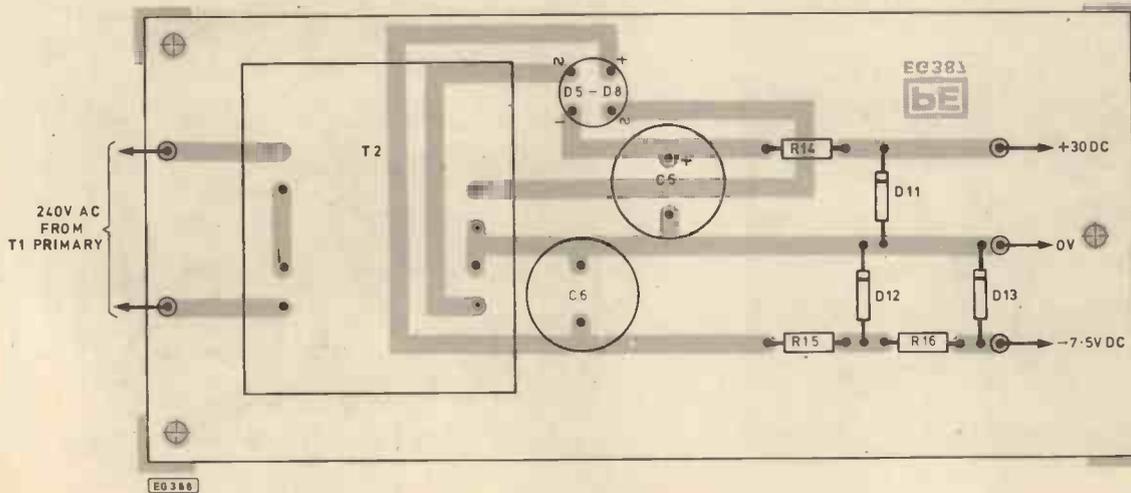


Fig. 6. Component overlay for above

COMPONENTS ...

Resistors

R1	4k7	Thick Film
R2	1k5	Thick Film
R3	5k1	Metal Oxide
R4	110	Metal Oxide
R5	39k	Thick Film
R6, R7, R12	1R	2.5W Wirewound (3 off)
R8	10k	Thick Film
R9	1k	Thick Film
R10	100R	Thick Film
R11	10R	Thick Film
R13	0.33	2.5W Wirewound
R14, R15	1k	Thick Film (2 off)
R16	270	Thick Film

All resistors $\frac{1}{2}$ W 2% unless otherwise stated.

Potentiometers

VR1	1k	3W 10 turn linear
VR2	10k	Enclosed cermet preset linear

Capacitors

C1	4700 μ	63V	Can electrolytic
C2	1000 μ	25V	Wire ended electrolytic
C3, C4	100n	Disc	Ceramic (2 off)
C5, C6	220 μ	63V	Wire ended electrolytic

Semiconductors

D1-D4	4A	200V	Bridge rectifier
D5-D8	1A	50V	Bridge rectifier
D9	BZY88	15V	400mW Zener diode
D10	BZY88	5.1V	400mW Zener diode
D11, D12	BZX61	30V	1.3W Zener diode (2 off)
D13	BZY88	7.5V	400mW Zener diode
TR1	2N3053		
TR2	2N3055		
TR3	2N3055		
IC1	MC1436 CG.		(Motorola)

Transformers

T1	240V Primary 0-15V, 0-15V 100VA Secondary
T2	240V Primary 0-20, 0-20 6VA Secondary (R.S. Components) printed circuit mounting

Switches

S1, S2	DPDT Miniature toggle. 250V AC 1A (2 off)
S3	DPDT Miniature toggle
S4	1P 6W Rotary 6A 30V DC

Miscellaneous

Fuseholder and fuse
Neon
Sockets
Printed circuit board
Heatsinks
Case

In the constant voltage mode R8-R13 are shorted by S3B and IC1 inverting input is grounded via R5 by S3A. Capacitors C3 and C4 provide supply decoupling for IC1.

The output voltage is provided by T1, D1-D4 and C1, and IC1 has a separate power supply providing +30V and -7.5V. Switch S5 was also incorporated to reverse the polarity of the output.

CONSTRUCTION

The prototype circuit was constructed on two printed circuit boards, one for the main circuit and one for the operational amplifier power supply. C1 was mounted separately and resistors R8-R13 were mounted directly on S4.



TR2 and TR3 were mounted on a heatsink with a thermal capacity of 1.1°C per watt, which was mounted away from the case on 10mm spacers to give improved ventilation. A small clip-on heatsink was also fitted to TR1.

SETTING UP AND USE

Firstly the offset null is adjusted. With both inputs of IC1 grounded, adjust VR2 to give 0V at IC1 output.

The circuit will supply between 10 μ A and 3A in six overlapping ranges, although when using the 1A and 3A ranges, the output transistors will become quite hot (up to 65°C), and load resistances of not less than 1 Ω should be used on the 1A range and 8 Ω on the 3A range.

When used as a constant voltage power supply the output current should be restricted to 1A. ★

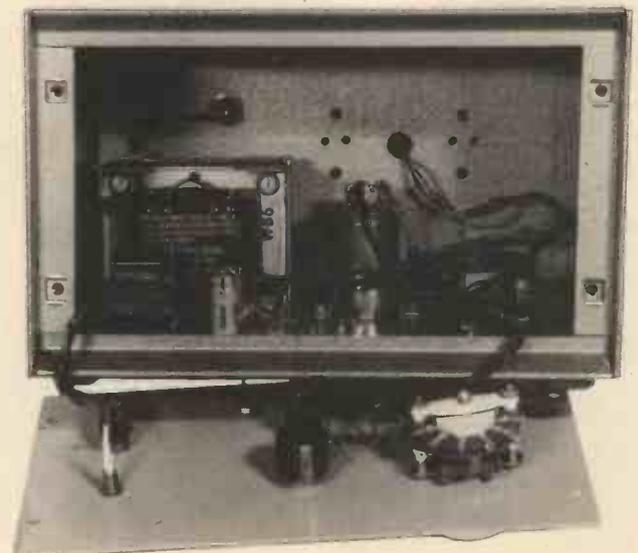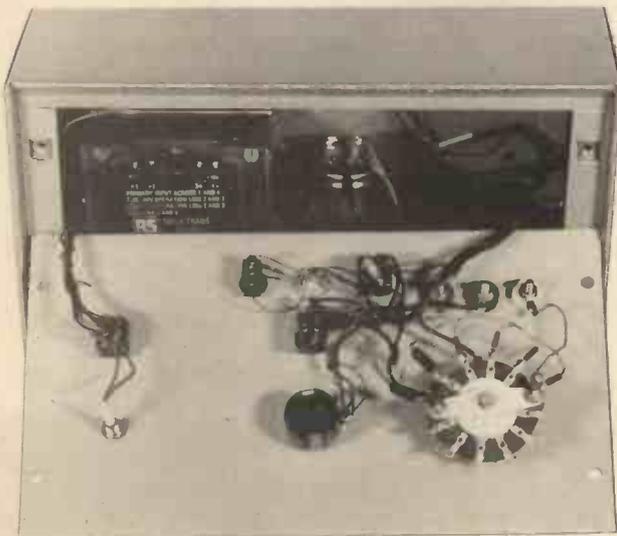

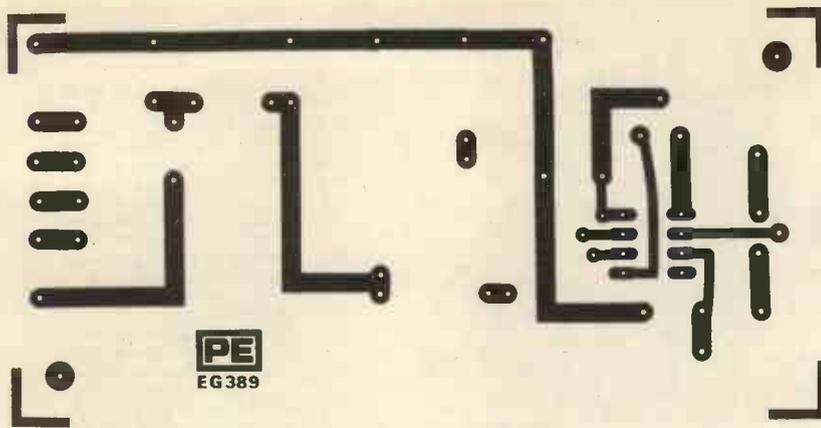


Fig. 7. Main board p.c.b. (actual size)

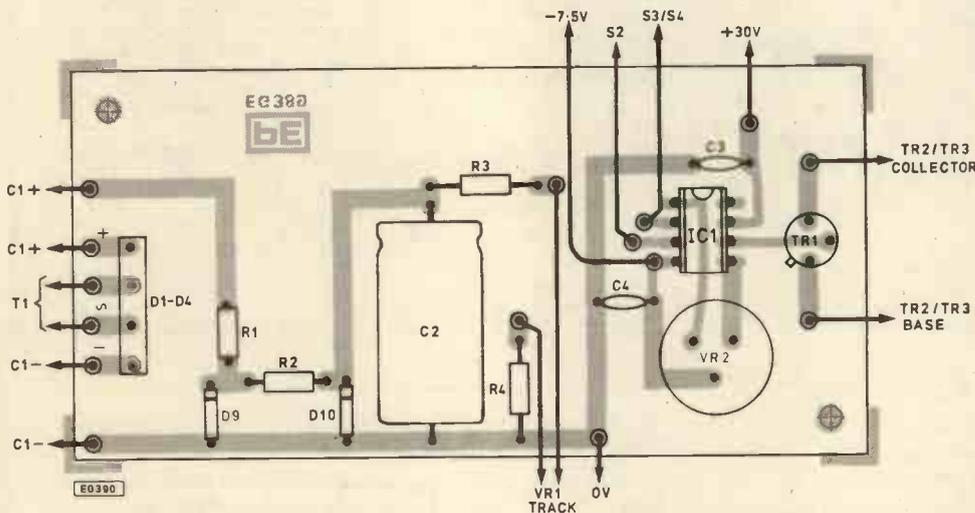



Fig. 8. Component overlay for above

Countdown

Computer Graphics (exhibition & conference) Aug. 12-14. Metropole, Birmingham. **O**
Harrogate International Festival of Sound Aug. 16-19 (18 & 19 trade). The Exhibition Centre + hotels. **X**
Edtech Aug. 19-21. Holland Park School, London. **C1**
Personal Computer World Show Sept. 4-6. Cunard Hotel, Hammersmith, London. **M**
Laboratory Sept. 9-11. Grosvenor Ho., Park Lane, London. **E**
Intron 80 Sept. 9-11. RDS, Simonscourt Pavilion, Dublin. **V**
West of England Electronics Exhibition Sept. 9-11. Bristol Exhibition Centre. **Q**
Electrathon (Lucas battery vehicle race) Sept. 13, 1980. Fashioned on last year's event, this "whispering Grand Prix" is a contest for home made electric vehicles. It will again be held at Donington Park Race Circuit, nr. Derby. Details: ☎ 021-554 5252.
Avionics (symposium) Sept. University of Surrey. **S1**
Emix (Electronic Measuring Instruments Exhibition) Sept. 30, Oct. 1-2. Post House Hotel, Southampton. **I**
BEX (Business Equipment Exhibition) Oct. 1-2. The Guildhall, Plymouth. **K**
Emix Oct. 7-8. Centre hotel, Newcastle. **I**
Emix Oct. 14-15. Guildhall, Cambridge. **I**
Drive Electric October 14-17. Wembley Conf. Centre, London. Organiser: ☎ 01-834 2333.
BEX Oct. 15-16. Assembly Rooms, Edinburgh. **K**
Engineering Ireland Oct. 15-18. Leopardstown Exhibition Centre. **V**

Testmex (exhibition and conference) Oct. 28-30. Wembley Conference Centre. **T**
Viewdata Exhibition for Professional & Business People Oct. 29-31. West Centre Hotel, London. **Z1**
Compec Nov. 4-6. Olympia. **Z1**
BEX Nov. 5-6. Sophia Gardens, Cardiff. **K**
Semiconductor International 80 Nov. 25-27. Metropole Convention Centre. **T1**
Breadboard Nov. 26-30. Royal Horticultural Halls, Westminster. **T**
Solar Energy Exhibition Aug. 23-28, 1981. Brighton. **M**

E Evan Steadman. ☎ 0799 22612
I ITF. ☎ 021-705 6707
K Douglas Temple Studios, 1046 Old Christchurch Rd., Bournemouth.
M Montbuild. ☎ 01-486 1951
O Online Conferences. ☎ 0895 39262
Q Exhibitions For Industry Ltd. ☎ 08833-4371
T Trident International Exhibitions. ☎ 0822 4671
V SDL Exhibitions, 68 Fitzwilliam Square, Dublin, Ireland.
X Exhibition & Conference Services, Claremont Ho., Victoria Ave., Harrogate, Yorks. ☎ 0423 62677
C1 Stereoscopic Television Ltd., 41/43 Charlbert St., St. John's Wood, London NW8 6JN. ☎ 01-722 4139
S1 Society of Electronics & Radio Technicians, 57-61 Newington Causeway, London SE1 6BL. ☎ 01-403 2351
T1 Kiver Communications U.K., Millbank House, 171/185 Ewell Road, Surbiton, Surrey KT6 6AX
Z1 IPC Exhibitions Ltd., 40 Bowling Green Lane, London EC1R 0NE. ☎ 01-837 3636

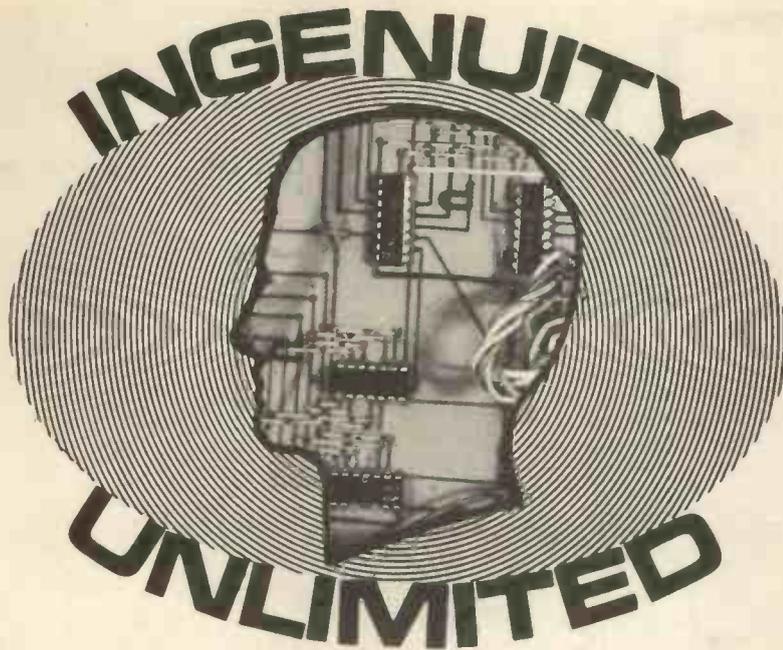

A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit *your* idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

A HEX KEYPAD


THE accompanying circuit shows a hexadecimal keyboard interface which can be used as both a peripheral to a microprocessor or for inserting data under DMA. It gives visual indication of the output on a bank of eight leds.


Each key is strobed low in turn by the configuration of IC1 and IC2. When a closed key is found, C1 is discharged and the clock IC6b stopped. IC2 clocks on the up-stroke, so IC6a is included to stop extra pulses reaching the counter. As the voltage on C1 falls, it produces a clock pulse for IC5, which is wired as a divide by two counter. Falling edges on IC5's output, latch the four bit number on IC2 (representing the button pressed) alternately into IC3 and IC4. C1 debounces the keys.

If the circuit is used for DMA, the output can be connected to the data bus. The two hex digit byte is entered and the Chip Enable pin of the memory strobed low to insert the byte. If a wrong number is entered, it can be re-entered before the CE line is strobed.

If the circuit is used as a peripheral, then it must be interfaced through a tri-state buffer like the 74125, in which case it would have to be polled. A cheaper method of interface is via a 7401 NAND gate with open collector outputs. Because this performs an inversion, the data should be taken from the Q outputs of the 7475.

D. Greaves,
Romsey,
Hants.

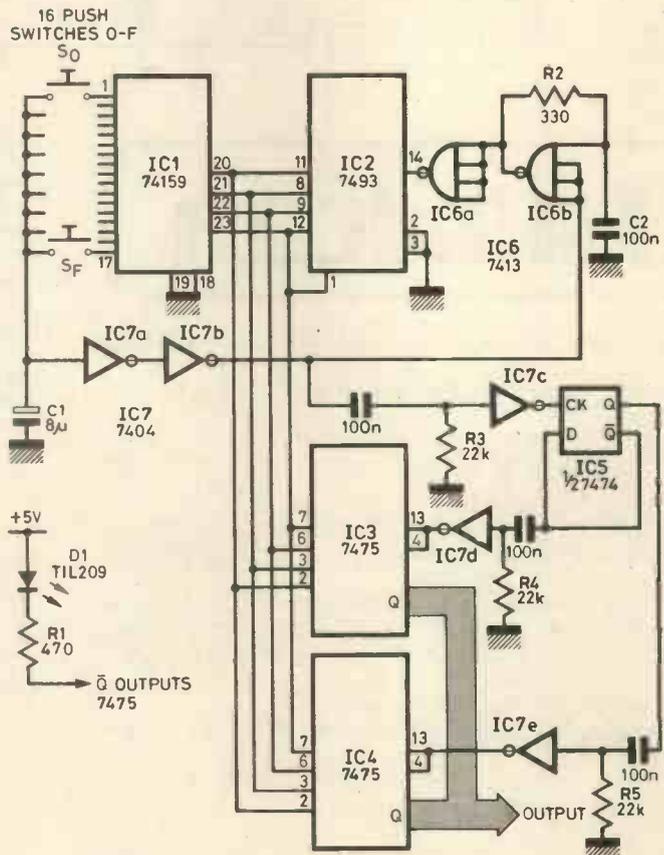

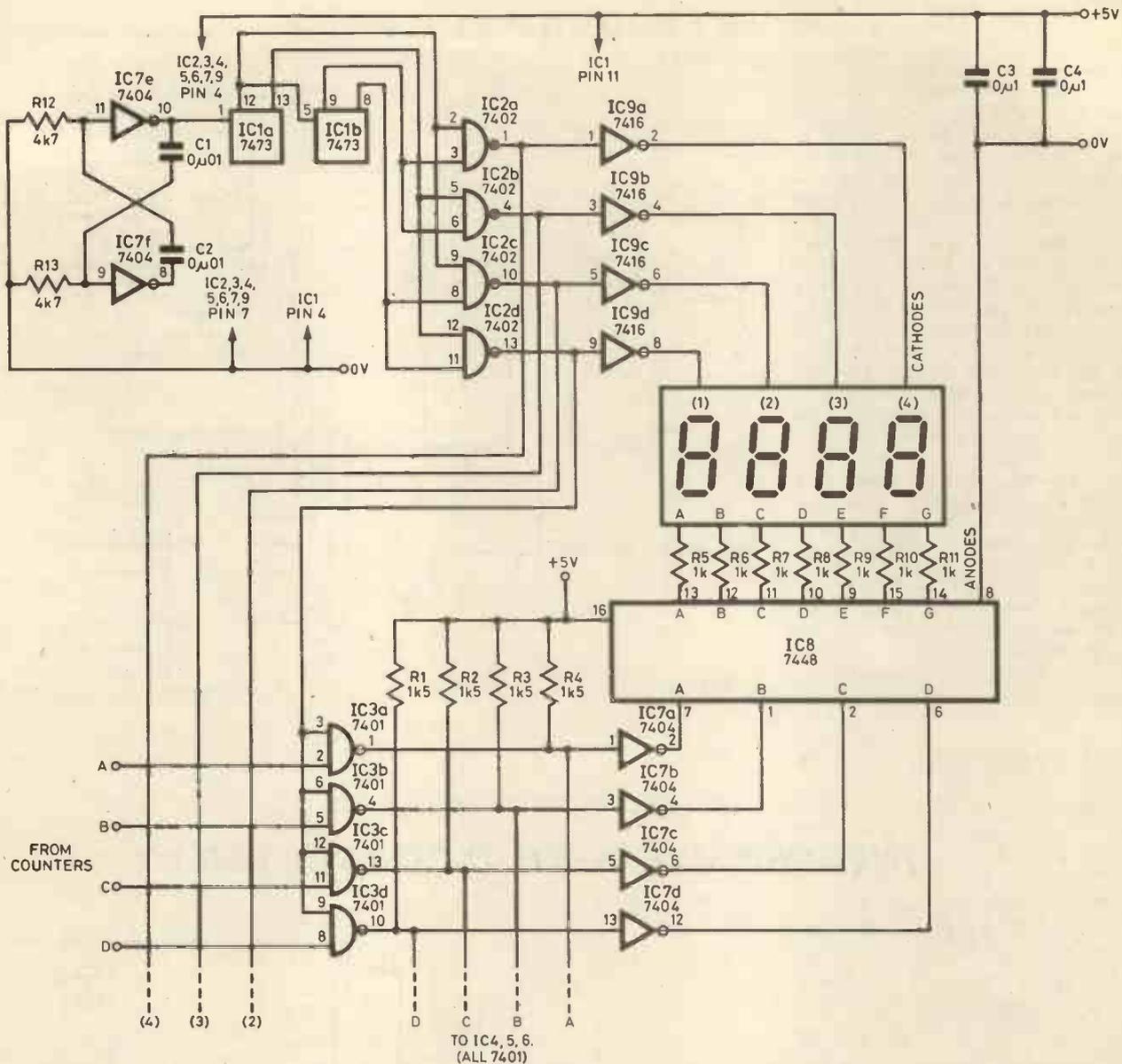

MULTIPLEXER

THE circuit is of a four digit multiplexer, which was designed to facilitate the use of a multiplex connected type of l.e.d. display. The circuit can also be used to advantage with unmultiplexed l.e.d. displays, but the total current which may be drawn from each digit driver is limited to 40 mA. Alternatively discrete transistor drivers could be used. The type of display for which this circuit was intended is the miniature calculator displays now available at low cost. With the values of R5-R11 the current per segment is just over 3 mA, which will give adequate brightness in most applications. The circuit is for common cathode l.e.d. displays.

The circuit functions as follows: IC1 and IC2 form a divide by four counter with decimal outputs, which is used to

scan the digits and multiplexer gates, simultaneously.

IC9 is an inverting buffer with 40 mA open collector outputs. These are wire-O Red together to enable the BCD outputs of the counters to be connected to the inverters of IC7 and so to the decoder driver i.e., one after the other in sequence. With their respective digits, IC7 reinverts the BCD information because it becomes inverted by the NAND gates. R1-R4 pull up the open collector outputs of the NAND gates.

IC8 is the BCD to decimal decoder driver IC and is for common cathode type displays. R5-R11 are the current limiting resistors for the digits. The remaining two inverters of IC7 are used to form a multivibrator which is used to clock the divide

by four decimal counter. C3 and C4 are supply decoupling capacitors and should be spaced approximately 4 IC's apart. Common anode type displays could be used with a 7447 for IC8. Discrete digit drivers must be used. More than four digits could be displayed by the use of more 7401s and a suitable decimal decoded counter.

C. F. Shorto,
Weymouth,
Dorset.

THIS circuit produces a 4 bit binary word for a key pressed on a keyboard.


IC1 is wired in its astable mode. Pulses produced at pin 3 are taken to IC2, a 4 bit binary counter. The three most significant digits are taken to IC5, a BCD to decimal decoder. The outputs of this are low on select. As IC2 counts, one row of the keyboard matrix is low, followed by the next in sequence, thus the scanning action is produced. If a key is pressed then that row becomes low when IC5's "scan" reaches it. One of IC3b's inputs also becomes low at this moment, the output going high. ICs 3a and 4a detect when the clock is high and the output "A" of IC2 is low. IC4b detects when IC3b and IC4a are high and enables the latch, IC6. The "D" input to IC6 is derived from a column which contains the lower eight keys of the keyboard. A correct four bit binary code will then be obtained

If a new key is pressed, its binary code will be accepted regardless of the code already present. Both true and complementary outputs are obtainable.

The whole circuit was constructed on stripboard, with ribbon wire interfacing the keyboard. Outputs were accessible via solder con pins for easy connection to a breadboard. Two 100n ceramic capacitors are also necessary for decoupling especially near IC1.

A. Piper
Newport Pagnell,
Bucks

KEYBOARD SCANNER

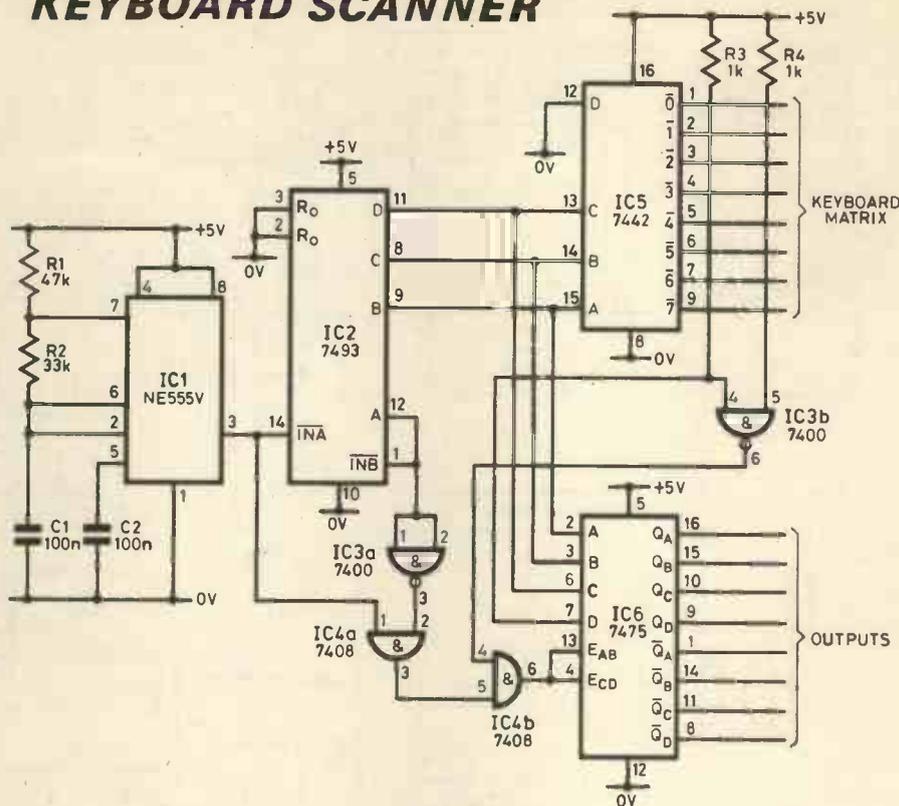


INEXPENSIVE A-TO-D CONVERTER

THE circuit shown converts the input voltage from VR2 into a four bit binary number suitable for many computer games (e.g. lunar landing). More bits can easily be added, however this method of conversion will not be sufficiently accurate for more than eight bits. Four i.c. packages are used.

Initially counter IC1 is set at zero; however it is quickly clocked by the astable configuration IC4c and IC4d. As it counts, the four resistors R1 to R4 produce an increasing voltage proportional to the count. When this voltage is higher than the voltage at the wiper of VR2, IC3's output swings to +5V which saturates transistor TR1 and stops the clock. Now the count on IC1 points to the input voltage and it can be read via the buffer IC2. IC4a and IC4b detect the end of the reading and reset the counter so the cycle re-starts.


Although during the counting period the reading on IC1 is incorrect, this will never be noticed because it is pointless reading the converter more than twice a second, as the user will not have appreciably moved VR2. VR1 is set to give a full scale setting of VR2 of all ones (1111).

D. Greaves,
Romsey,
Hants.

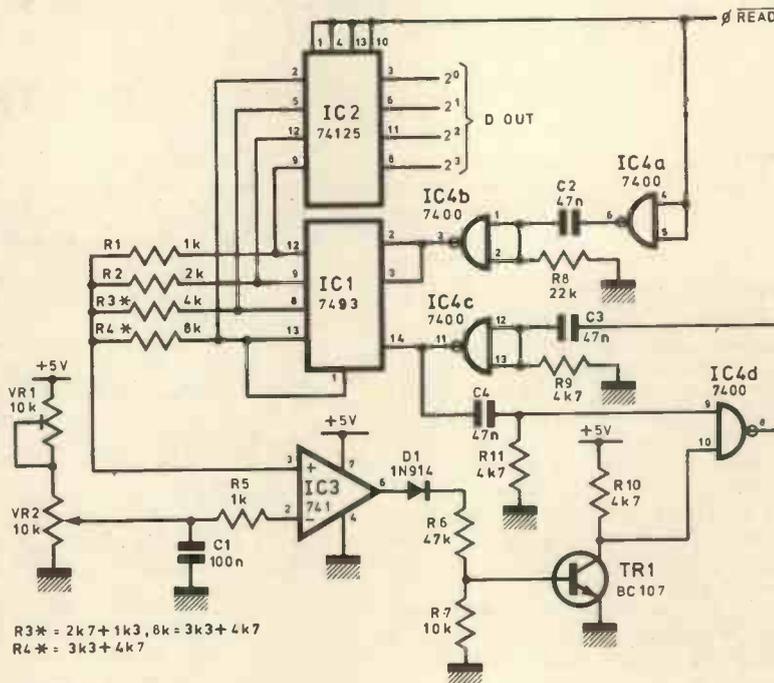

$R3^* = 2k7 + 1k3, 8k = 3k3 + 4k7$
 $R4^* = 3k3 + 4k7$

EG 343

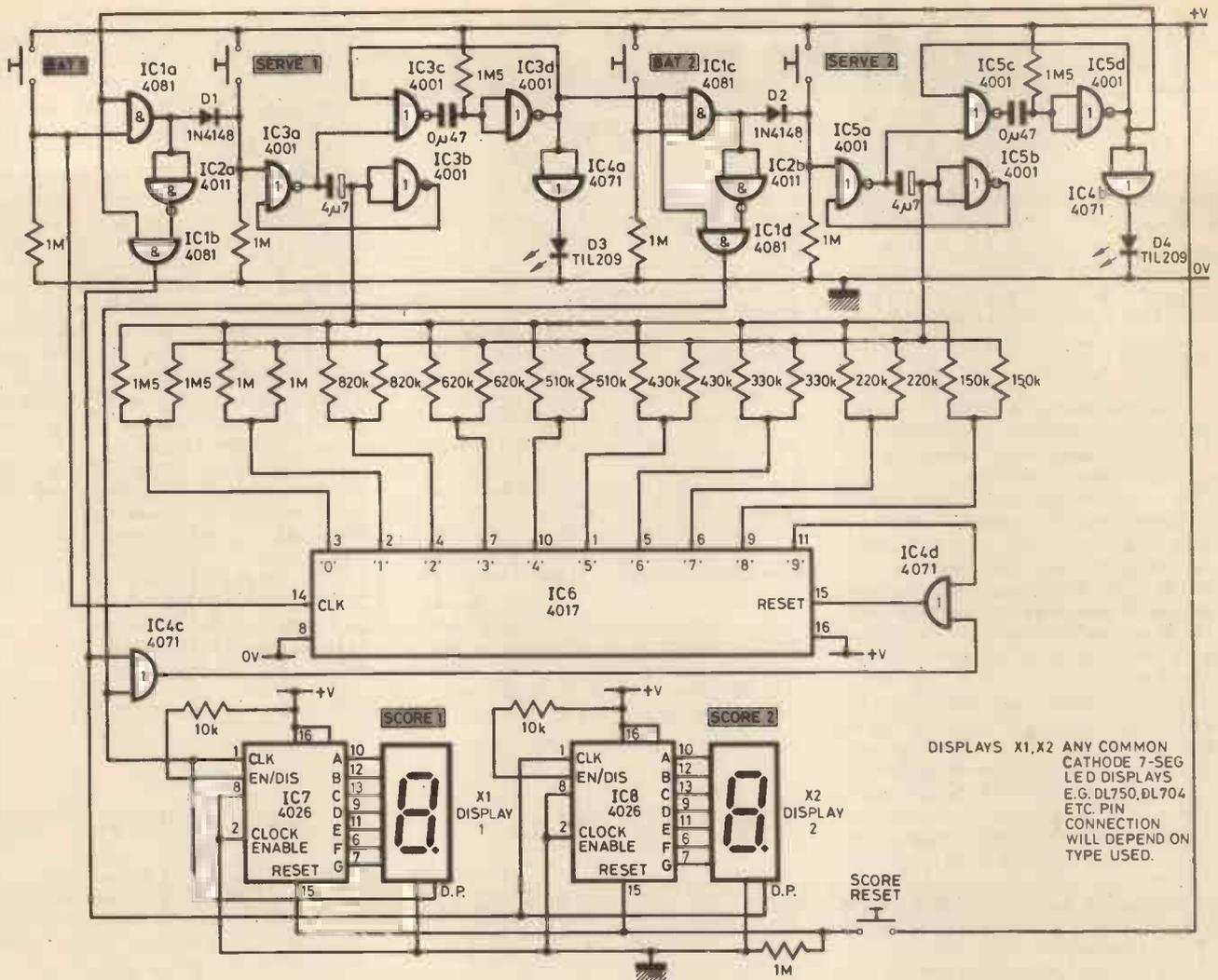

PORTABLE TENNIS

THE circuit diagram is shown up above and if the logic is followed through, the circuit operation should be fairly self explanatory.

To start a game the "Reset" button is pressed to clear any scores on the counters. A player then serves by pressing his "Serve" button. After a period of time the 'ball' reaches the other player. This is signified by his l.e.d. lighting up. While this is, lit he must press his "Bat" button to return the ball. If he fails to press the button at the right time, this is a miss and registers a point on his opponent's score counter. If he hits it then, after a period of time, it reaches the first player lighting up his l.e.d., he tries to hit it and so on. Each miss is counted as a point on the other player's counter.

Some skill is required in playing this game since the time taken for the "ball" to cross the "court" does not remain constant. Rather the time decreases during play until either a player misses a


ball or the counter has gone through the eight speeds. At this time it reverts to the slowest speed and gets faster again.

Serving triggers the monostable IC3a and b or IC5a and b. At the completion of its cycle it sends a pulse, which is generated by IC3c and d or IC5c and d, to the other player's circuitry. The period of monostables IC3a and b and IC5a and b is determined by the resistor selected by the counter IC6. Each second hit advances the counter until it is reset.

A suggested top-panel layout is shown right.

Incidentally, a sort of doubles game can be produced by inserting another push switch across each of the "Bat" switches. Thus if one player missed the "ball", the other would have a good chance of hitting it.

P. Bailey,
Rutherglen,
Glasgow.

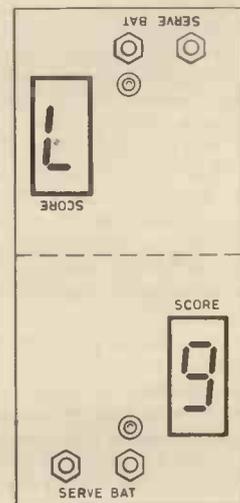

Readout...

A selection from our Postbag

Readers requiring a reply to any letter must include a stamped addressed envelope.
Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

Velikovsky: Pure Myths

Sir—While leafing through my father's copy of *PE* (June 1980) I was rather surprised to find a serious letter supporting the ridiculous theories of Immanuel Velikovsky. In the letter, Mr. Austin "looks forward to reasoned argument" on the subject. For those readers interested in such, I should like to recommend the book *The Stars in Their Courses* by Dr. Isaac Asimov which contains, among other fascinating essays, a chapter entitled 'Worlds in confusion', from which I shall draw a few comments to the attention of your readers.

Velikovsky's book was claimed to be the work of a scientist (which Velikovsky is not) who had proved the Bible to be true. The basis of his theory is that Jupiter spewed out a huge comet, leaving behind the Red Spot, which careered about the solar system causing no end of interesting effects, before settling down to become Venus. The book is full of nonsense physics and ludicrous assumptions. For example, Velikovsky states that the laws of astronomy predict that a satellite will rotate slower than its planet and then points out that this is not so for the inner planet of Mars, thus demonstrating that all astronomic laws are wrong. It looks very nice but is nothing but transparent twaddle. There is nothing any astronomic law predicts about the speeds of rotation, which depend only on the primary and satellite distance and mass. In fact, the inner satellite of Mars has a rotational period of exactly that predicted by physics.

Velikovsky also makes heavy use of medieval Jewish legends and the writings of the ancients, taking metaphor and legend as fact, and constructs his own chronology to fit his "facts". His theory contains glaring errors of chemistry and physics that could be spotted by an A-level student (in one part he transforms hydrocarbons into carbohydrates in the space of a paragraph although the two classes of compound are completely different), and mis-interpretation of scientific observation. He uses scientific results when they agree with his theory and throws them away when they do not. He draws heavily on the spectroscopic analysis of comets tails without explaining why scientists who cannot handle the simple calculations of celestial mechanics should be trusted with such complex analysis!

When he needs a rain of fire to explain certain biblical tales he hits on the theory that the hydrocarbons in comets' tails will burst into flame when passing through the Earth's atmosphere. Is this plausible? No sir, not a

chance. Gas does not come much thinner than that in comets' tails and it certainly would not burn in the atmosphere. You may say how do we know? Well, in 1910 we passed through the tail of Halley's comet and absolutely nothing happened! (as predicted by the scientists and completely opposite to the prophets of doom).

I could go on, but do not think it necessary. In short, Velikovsky's work is nonsense and demonstrates nothing except the gullibility of the non-scientific public. It has more in common with crank mail (Dear Sir, I have recently disproved the theory of relativity, etc., etc.) than a serious work. Copernicus developed his Sun-centred theory only because he was a thorough student of the Earth centred theories; Einstein developed relativity while a thorough student of Newtonian mechanics. Point taken?

David G. W. Birch, B.Sc.,
Swindon.

The AY-3 Saga

Sir—Last year I wanted a GIM integrated TOG, the AY-3-0214, to make a copy of the Wersi master oscillator for my Maplin organ. Recent comment in your magazine reminds me of this.

GIM very promptly sent me their product guide, and the data sheet on their music i.c.s. In the back of the product guide are listed their distributors so I set out to contact them. (I had already tried about 10 of the retailers who advertise the AY-1-0212 and other GIM

ICs in the various hobby magazines and they were all useless, so I suggest that Mr. Partridge's solution does not work!) (*Readout May 1980*). Of the distributors, one was down-right rude, two just did not want to know. Crellon Electronics were helpful but said that they had to order a minimum of 25, and did not wish to be left with 24. They could only supply if I would have 25, at £13.50 each!—fair enough.

I then wrote to GIM again and thanked them for the information but suggested that it was a pity that their excellent i.c.s were not available, and told them why. Within a week or so I received a letter from them, stating that if I wrote to Semiconductor Specialists at West Drayton, they would now be able to supply me, which indeed they did for the sum of £13.80. Previously they had "not got it in stock." and "had never had it" and "didn't want to know about getting it".

So if your readers are trying without success to obtain GIM i.c.s then I suggest they write to: General Instruments MicroElectronics Ltd., Regency House, 1/4 Warwick Street, London W1R 5WB. They won't supply directly, but they do seem to be quite good at waking their distributors up!


Lastly, since buying that i.c. I have seen that it is on the "Doram" list at £10.10. Oh well, you can't win them all.

A. Jaques,
Urmston, Manchester.

CPUs: The Last Word

Sir—Re the letter by C. R. Harris in your June issue, I would like to point out that the article was originally credited to Roy Featherstone, now at Edinburgh researching into artificial intelligence, and secondly, that the ultimate CPU described has the advantage over its silicon rivals of being mass produced by unskilled labour!

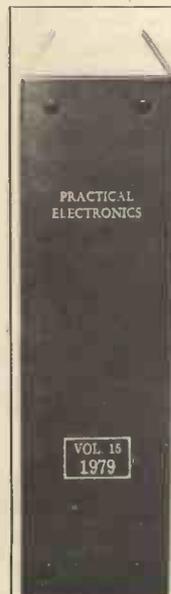Tim Sutherns,
President, S.U. Computer Club,
Southampton.



Create your own LIBRARY

A real bind

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately 12 issues and is attractively bound and blocked with the PRACTICAL ELECTRONICS logo. Gold lettraset supplied for self blocking of volume numbers and years.

Price £4.30 including postage, packing and VAT. Why not place your order now and send the completed coupon below with remittance to:— IPC Magazines Ltd, Post Sales Dept, Lavington House, 26 Lavington St, London, SE1 0PF.

it's easy with **EASIBIND**

Order Form

PRACTICAL ELECTRONICS
I enclose P.O./cheque value for binders
Years required
(BLOCK LETTERS PLEASE)
Name
Address
.....
Date



GERM. DIODES
 200 Mixed Diodes - mainly Germ OA81-91-1N34/60 GC61/62 etc. Case DO-7, Coded and uncoded - You to test - Value all the way!
 O/No. SJ127. £1.00 per Pak.

BC108 FALLOUTS
 Manufacturers out of spec on volts or gain or neither - Metal TO18 case - You test.
 O/No. SJ124. 50 for £1.00

NPN
 BD131 TO-126-NPN untested.
 O/No. SJ84. 25 for £1.00
 SCR's
 TO66 SCR's 5 Amp - ALL good - untested for volt - good yield 400+.
 O/No. SJ130. 10 for £1.00

IC SOCKET PACKS

SJ36	14	8 pin	SJ41	6	22 pin
SJ37	12	14 pin	SJ42	5	24 pin
SJ38	11	16 pin	SJ43	4	28 pin
SJ39	8	18 pin	SJ44	3	40 pin
SJ40	7	20 pin			

ALL AT ONLY £1.00 each

SILICONS
 200 Mixed Diodes - mainly SILICON case DO-7 OA200/202 General purpose 200mA marked and uncoded - you to sort & test - Outstanding Value!
 O/No. SJ128. £1.00 per Pak.

DIODES
 300 IN4148 Type - uncoded Silicon Diodes Case DO-35 - you to test.
 O/No. SJ129. £1.00 per Pak
 Silicon Fast Switch
 NPN - like 2N706/2N2369
 You select by test!
 O/No. SJ125. 50 for £1.00

AERIALS
 FM Indoor Tape/Ribbon Aerial
 O/No. 107. 40p each
 HI-FI CAR AERIAL
 4-section fully retractable & locking SPECIAL PRICE.
 O/No. 109. £1.40 each

VOLTAGE REGULATORS
 Cast TO220

	Positive	Negative
uA7805	£0.65	uA7905 £0.70
uA7812	£0.65	uA7912 £0.70
uA7815	£0.65	uA7915 £0.70
uA7818	£0.65	uA7918 £0.70
uA7824	£0.65	uA7924 £0.70

AUDIO AMPLIFIER
 5 watt Audio Amplifier Module.
 Special Clearance Offer
 O/No. AL20. £2.50

GERM. TRANSISTORS
 The last of the Germanium PNP - OC71-71-75 etc. Mullard Black/Glass Type - You test (5 could cost you that!)
 O/No. SJ126. 50 pcs £1.00
 GERM. POWER TRANS.
 AD149-OC26-AD140 £0.50 each
 AD142-OC28-2N3614 £0.65 each

STEREO 30
 Complete 7 watt per channel Stereo Amplifier Board - includes amps, pre-amp, power supply, front panel, knobs etc. PLUS transformer and real Teak Cabinet for that professional finish!

TEXAS NPN
 Texas NPN silicon transistors metal can - perfect and coded. 2503-8C108 TO-18.
 O/No. SJ29. 50 off £2.50, 100 off £4.00, 1,000 off £35.00.

HEADPHONES
 NEW Improved Lightweight Stereo Headphones including double headband and padded earcups - Impedance 8 ohms - Frequency 30-18000Hz ALL Black.
 O/No. 885. £4.00
 As above but with coiled lead and rotary volume controls.
 O/No. 884. £7.00

VERO PLASTIC CASE
 Complete with lid and fixing screws. Finished white.
 Size: 72mm x 50mm x 25mm.
 O/No. 173. £0.35 each

SPECIAL SALE PRICE
SAVING £5!
OUR PRICE £25.00

AUDIO ACCESSORIES
 SJ75 FM coax cable - plain copper conduction cellular polythene insulated & plain copper braided PVC sheath - impedance 75 ohms £0.10 per metre
 SJ76 1 Board containing 2x5 pin DIN sockets 180° 02-2 pin DIN loudspeaker sockets £0.30
 SJ77 A 5-pin DIN 180° chassis/normal socket incl. DPDT switch £0.20

HEADPHONE ACCESSORIES
 7 metre Headphone Extension Lead
 O/No. 136 £1.50
 HEADPHONE JUNCTION BOX
 Gives facility of using Stereo Headphones with amplifiers and radiogramms which do not have a headphone outlet. TO CLEAR
 O/No. 881 £1.20 each

BI-PAK'S OPTO BARGAIN OF THE YEAR!

Valued at over £10 - Normal Retail - we offer you a pack of 25 Opto devices to include LED's Large and Small in Red, Green, Yellow & Clear. 7 segment Displays both Common Cathode and Common Anode PLUS bubble type displays - like DL-33. Photo Transistors - similar to OCP71 and Photo Detectors - like MEL11-12. This whole pack of 25 devices will cost you just...

£4.00!

AND we guarantee your money back if you are not completely satisfied.
 FULL data etc included.
 O/No. SJ120

DISC CERAMIC CAP
 100 Disc Ceramic Cap. Mixed values covering complete range 3PF-4,700PF.
 SUPER VALUE
 O/No. SJ121. £1.00

ANTEX
 Antex X25 Iron - 25 watt soldering iron. OUR SUPER SALE PRICE. Great reduction.
 O/No. 1931. £4.00
 ST3 Iron Stand - Suitable for above - OUR Sale Price
 O/No. 1939. £1.25 each

SILICON TRANS.
 SJ25 100 Silicon NPN transistors all perfect & coded - mixed types with data - equivalent sheet - no rejects £2.50
 SJ26 100 Silicon PNP transistors all perfect & coded - mixed types and cases data & equivalent sheet £2.50
 SJ27 50 Assorted pieces of SCR's, diodes & rectifiers incl. stud types, all perfect - no rejects, fully coded - data incl. £2.50

PRECISION VOM MULTIMETER
 20,000 ohms/ volts DC. Complete with test leads & instructions.
 OUR SPECIAL OFFER
 PRICE £11.00 each.
 O/No. 1323
 Use your Barclay or Access Card

SWITCHES
 Push-to-make. 6mm panel mounting.
 O/No. SJ131. 5 for £0.50
 Push-to-break as above.
 O/No. SJ132. 4 for £0.50

METERS
 23mm Level Meter
 Special Sale Price.
 O/No. 1320. £1.00
 40mm V.U. Meter
 OUR SPECIAL PRICE
 O/No. 1321. £1.50

TTL's
 SJ28 20 TTL74 series gates - assorted 7401-7460 £1.00
 SJ53 Mammoth IC Pak. Approx 200 pcs assorted fall-out integrated circuits including logic 74 series - Linear audio and DTL. Many coded devices but some unmarked - you to identify £1.00

NPN TRANSISTORS
 SJ68 30 ZTX300 type transistors NPN pre-formed for P/C Board colour coded Blue - all perfect. £1.00
 SJ70 25 BC107 NPN TO106 case perfect transistors code Green Spot. £1.00
 SJ71 25 BC177 PNP TO106 case perfect transistors code C1395. £1.00
 SJ72 4 2N3055 silicon power NPN transistors TO3 £1.00

LED.
 2nd Quality Paks
 1507 10 Assorted colours & sizes £0.65
 S122 10 125 RED £0.50
 S123 10 2 RED £0.50
 LED CLIPS
 1508/125 125 5 for £0.10
 1508/2 2 5 for £0.12

PLUGS & SOCKETS
 Set of 4 1-metre Colour coiled leads with phono plug ends - ideal for audio and test use. Outstanding Value.
 O/No. SJ122. £1.00 per Pak
 1mm Plugs & Sockets in Red & Black.
 O/No. SJ123. 5 pks £1.00

RESISTORS
 SJ1 200 Resistors mixed values. £0.50
 SJ2 200 Carbon resistors 1/2 watt preformed. £0.50
 SJ3 100 1/4 watt miniature resistors mixed values. £0.50
 SJ4 60 1/4 watt resistors mixed values. £0.50
 SJ5 50 1/2 watt resistors mixed pot values. £0.50
 SJ7 30 2-10 watt wirewound resistors mixed. £0.50

POTENTIOMETERS
 16173 15 Assorted Pots £0.50
 SJ54 20 Assorted Slider Pots £1.00
 SJ56 10 100 K Lin Slider Pots 40mm £0.50
 16186 25 Pre-sets Assorted £0.50
 SJ49 8 Dual gang carbon pots log and lin mixed values. £1.00
 SJ50 20 Assorted slider knobs - chrome/black £1.00

MISCELLANEOUS
 SJ20 2 Large croc clips 25A rated - ideal for battery chargers etc. £0.30
 SJ21 Large 7 1/2 Mains Neon Tester - screwdriver chrome finish. £0.85
 SJ22 Small pocket size Mains Neon Tester screwdriver. £0.55
 SJ23 Siemens 220v AC relay DPDT contacts 10 amp rating - housed in plastic case. £1.00

CAPACITORS
 SJ11 150 Caps. mixed types & values. £0.50
 SJ12 60 Electrolytics all sorts mixed. £0.50
 SJ13 40 Polyester/polystyrene capacitors mixed. £0.50
 SJ14 50 C280 type capacitors mixed. £1.00
 SJ15 40 High quality electrolytics 100-470mfd. £1.00
 SJ16 40 Low volts electrolytics mixed values up to 10v. £0.50

TRANSFORMERS
 MINIATURE MAINS Primary 240v
 No. Secondary
 2021 6v-0-6v 100mA £0.75
 2022 9v-0-9v 100mA £0.75
 2023 12v-0-12v 100mA £0.95
 2035 240v Primary 0-55v 2A Secondary £5.50

METAL SLIDERS
 Metal Case Dual Slider Pots: 45mm travel
 SJ65 10K log £0.25 each
 SJ66 100K lin £0.25 each
 SJ67 Chrome slider knobs to fit £0.10 each

ODDMENTS
 16170 50 metres asst. colours single strand wire. £0.50
 16187 30 metres stranded wire mixed colours. £0.50
 16178 5 Main slider switches assorted. £0.50
 SJ76 1 Board containing 2x5-pin DIN sockets 180° & 2x2-pin DIN loudspeaker sockets. £0.30

TRANSFORMERS
 MINIATURE MAINS Primary 240v
 No. Secondary
 2021 6v-0-6v 100mA £0.75
 2022 9v-0-9v 100mA £0.75
 2023 12v-0-12v 100mA £0.95
 2035 240v Primary 0-55v 2A Secondary £5.50

CASSETTES
 SUPER VALUE & A GREAT SAVING!!!
 C120 Dinky Cassettes - Low noise - astounding value and sound.
 O/No. SJ32. 10 for £3.50

METAL SLIDERS
 Metal Case Dual Slider Pots: 45mm travel
 SJ65 10K log £0.25 each
 SJ66 100K lin £0.25 each
 SJ67 Chrome slider knobs to fit £0.10 each

KNOBBS
 SJ62 5 15mm chrome knobs standard push fit. £0.50
 SJ63 Instrument knob - black winged (29x20mm) with pointer. 1/4" standard screw fit. £0.18
 SJ64 Instrument knob - black/silver aluminium top (17x15mm). 1/4" standard screw fit. £0.12

BI-PAK

Send your orders to: Dept PE8, BI-PAK, PO BOX 6, WARE HERTS.
 SHOP AT: 3 BALDOCK ST, WARE, HERTS.
 TERMS: CASH WITH ORDER, SAME DAY DESPATCH, ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL: (0920) 3182. GIRO 388 7006
 ADD 15% VAT AND 50p PER ORDER POSTAGE AND PACKING.

TUNE IN!

Build the World Famous CHROMA~CHIME



Give your friends a warm welcome

This kit has been carefully prepared so that practically anyone capable of neat soldering will have complete success in building it. The kit manual contains step by step constructional details together with a fault finding guide, circuit description, installation details and operational instructions all well illustrated with numerous figures and diagrams.

- Handsome purpose built cabinet
- Easy to build and install
- Uses Texas Instruments TMS1000 microcomputer
- Absolutely all parts supplied including I.C. socket
- Ready drilled and legended PCB included
- Comprehensive kit manual with full circuit details
- No previous microcomputer experience necessary
- All programming permanently retained is on chip ROM
- Can be built in about 3 hours!
- Runs off 2 PP3 type batteries.
- Fully Guaranteed

* Save pounds on normal retail price by building yourself.

ONLY
£11.95
+ 75p p&p
UK ONLY

TMS 1000N



—MP0027A Micro-computer chip available separately if required. Full 24 tune spec device fully guaranteed.

This unique chip can be used not only for electronic door chimes but for other projects requiring musical output: New low price only

- Car Horns
- Musical Boxes
- Amusement Machines
- Alarms
- Public Address etc

£4.95 inc. p & p.

Free applications manual and data supplied with device! (Or 30p separately.)

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE
PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me: PE.8.80.
TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

NAME _____
ADDRESS _____

I enclose cheque/PO value £ _____
or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____

CHROMATRONICS

CONGRESS AMPLIFIER

We supply all the designer approved parts for this exceptional kit, including high quality printed circuit boards and transformer.

Complete kit, excluding metalwork with 20% discount on parts. **£73.74**

All parts to assemble pre-amp i.e. R's, C's, PCB's, semicons, controls etc, but excluding transformer with 10% discount on parts. **£41.79**

All parts to build main amp board **£20.48**

Mains transformer **£12.82**

Smoothing caps & clips **£8.86**

Front Panel **£3.20**

Chassis (unpainted, pre-punched) **£13.40**

Front panel and chassis not subject to reduction but if ordered together with complete kit available at special price of **£11.50**

This offer also applies to previous purchasers of complete kits.

MAIL ORDER ONLY.

Prices include VAT and p&p

Please send A5 S.A.E. for full price details.

Terms: Cash with order. Cheques etc. should be made payable to:

CONGRESS ELECTRONICS PROJECT

Allow 14-21 days after sending order for delivery. Send order to:

Photostat of article available at £1.20.

WICCA SYSTEMS LTD,

24 HILLCREST PARADE, COULSDON, SURREY.

Tel. 01-668 5256

DISCO LIGHTING KITS!!!

First class constructional projects, c/w glass fibre P.C.B.'s & full instructions. No extra components needed to make a top rate working unit.

LK1 3 channel sound-to-light.
£9.90 300 w/channel 1v - 100w input

LK3 2kW slider dimmer
£5.50 suitable for clubs/pubs.
A professional unit c/w face plate.

LK2 3 channel 3kW
£17.90 zero voltage firing
200mV - 100 watts input.

LK4 4 channel 4kW
£16.50 audio - forward/reverse
auto - two speed ranges.

ALL KITS C/W
Facia panel,
circuit, comprehensive
instructions & full
parts guarantee



Suitable case for
LK 1/2/4 **£3.50**
100w spots ES or BC
£1.50.
Coloured pigmy lamps
65p.


Carriage on above 70p

UNREPEATABLE HI-FI BARGAIN

3 WAY LOUDSPEAKER KIT C/W BAFFLE (pre-cut)

- Comprises:
- ★ 6 1/2" linen surround bass unit
 - ★ 5" mid-range unit
 - ★ 3" tweeter
 - ★ 3 way crossover, fixing screws & baffle
 - ★ 20 watts handling capability.
- Full instructions provided
Must be heard to be believed!!

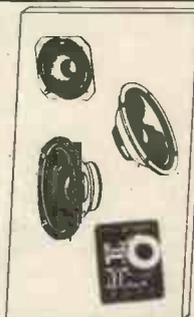£9.95 + £1 carr. or two kits for £20 carr. free.



SAXON ENTERTAINMENTS

327-333 Whitehorse Rd., Croydon, Surrey CR0 2HS.

(01) 684 0098.

Order by phone - Access/Barclaycard/C.O.D.
Open Mon. - Sat. 9am - 5pm.

Watch NEWS

JULY 1980

60p

SPECIAL REPORT


Just £1
to all readers

Don't buy a digital watch until you read this report

There are so many digital watches on the market, with varying functions, that the average person is bound to feel somewhat confused.

A new survey of the electronic watch industry has been produced to clarify this confusion and to give an unbiased and objective answer to the many questions that are constantly being raised.

by Trevor Raven.
C.Eng. AMBIM. MIERE

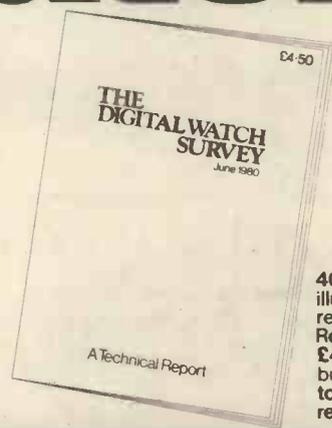

40 page illustrated report. Retail price £4.50 but just £1 to our readers.

- * How accurate are electronic watches?
- * Who makes Seiko's?
- * What is the importance between brand names?
- * Is solar power worth the extra money?
- * What are the most important features in a watch?
- * When will prices stop falling?

The survey answers all of these questions and tells you what to look for in a quartz watch; how they work; why the prices vary so much; what the future holds.

SPECIAL OFFER

Send today for this technical report, plus news of a unique Metac offer to beat all special offers.

Complete the coupon below and send it FREEPOST (no stamp required) and we will post, Same Day Despatch, the technical report giving you all you need to know about electronic watches and details of our special offer.

Which is the best watch?



These four watches are very different in price, durability and functions. How would you choose between them?

This unbiased and objective report helps you to make this decision and gives you a deeper insight into the rapidly changing and exciting world of the micro-chip.

For your copy of the report complete and return the coupon to: Metac Electronic & Time Centres, 24-hour Despatch Centre, FREE-POST, 47A High St., Daventry, Northants.

Name _____


Address _____

PE8

Simply ahead...

POWER AMPLIFIERS

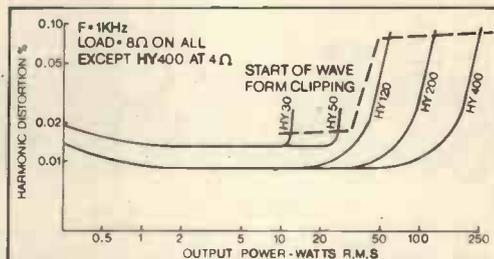ILP Power Amplifiers are encapsulated within heatsinks designed to meet total heat dissipation needs. They are rugged and made to last a lifetime. Advanced circuitry ensures their suitability for use with the finest loudspeakers, pick-ups, tuners, etc. using digital or analogue sound sources.



Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	100 dB	-20 -0- +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	100 dB	-25 -0- +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100 dB	-35 -0- +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100 dB	-45 -0- +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100 dB	-45 -0- +45	114x100x85	1.15Kg	£27.68 + £4.15

Load Impedance - all models 4 Ω - ∞
 Input sensitivity - all models 500 mV
 Input impedance - all models 100K Ω
 Frequency response - all models 10Hz - 45 KHz - 3dB



ILP PRE-AMPS ARE COMPATIBLE WITH ALL ILP POWER AMPS AND PSUs

POWER SUPPLY UNITS



ILP Power Supply Units with transformers made in our own factory are designed specifically for use with ILP power amplifiers and are in two basic forms - one with circuit panel mounted on conventionally styled laminated transformer, for smaller PSU's - in the other, for larger PSU's, ILP toroidal transformers are used which are half the size and weight of laminated equivalents, are more efficient and have greatly reduced radiation.

PSU 30 $\pm 15V$ at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + £0.68 VAT

THE FOLLOWING WILL ALSO DRIVE ILP PRE-AMPS

PSU 36 for 1 or 2 HY30's £8.10 + £1.22 VAT

PSU 50 for 1 or 2 HY50's £8.10 + £1.22 VAT

PSU 60 with toroidal transformer for 1 HY 120 £9.75 + £1.46 VAT

PSU 70 with toroidal transformer for 1 or 2 HY120's £13.61 + £2.04 VAT


PSU 90 with toroidal transformer for 1 HY200 £13.61 + £2.04 VAT

PSU 180 with toroidal transformer for 1 HY400 or 2 x HY200 £23.02 + £3.45 VAT



AVAILABLE ALSO FROM WATFORD ELECTRONICS, MARSHALLS AND CERTAIN OTHER SELECTED STOCKISTS.

this time with two new pre - amps

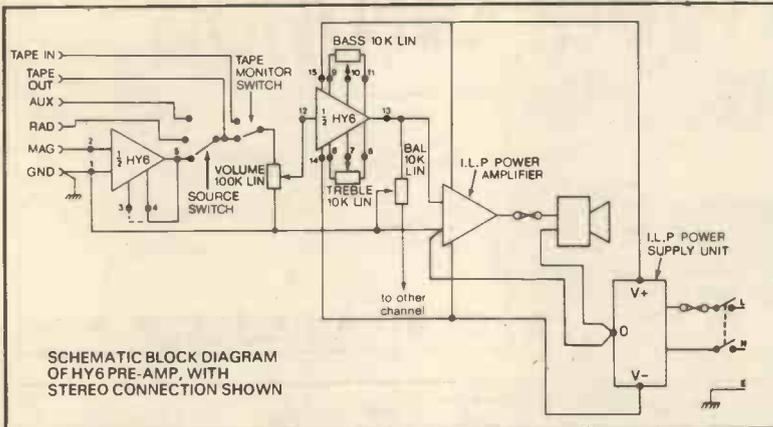

HY6 mono HY66 stereo

When ILP add a new design to their audio-module range, there have to be very special reasons for doing so. You expect even better results. We have achieved this with two new pre-amplifiers – HY6 for mono operation, HY66 for stereo. We have simplified connections, and improved performance figures all round. Our new pre-amps are short-circuit and polarity protected; mounting boards are available to simplify construction.

Sizes – HY6 – 45 x 20 x 40 mm. HY66 90 x 20 x 40 mm. Active Tone Control circuits provide ± 12 dB cut and boost. Inputs Sensitivity – Mag. PU. – 3mV; Mic – selectable 1-12mV; All others 100mV; Tape O/P – 100mV; Main O/P – 500mV; Frequency response – D.C. to 100kHz – 3dB.

HY6 mono

£5.60
+ VAT 84p

HY66 stereo

£10.60
+ VAT £1 59

Connectors included

B6 Mounting Board
78p + 12p VAT

B66 Mounting Board
99p + 15p VAT

- LOW DISTORTION - Typically 0.005%
- S/N RATIO - Typically 90 dB (Mag. P.U. - 68 dB).
- HIGH OVERLOAD FACTOR - 38 dB on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS.
- REQUIRE ONLY POTS, SWITCHES, PLUGS AND SOCKETS.
- COMPATIBLE WITH ALL ILP POWER AMPS AND PSUs.
- NEEDS ONLY UNREGULATED POWER SUPPLY ± 15 V to ± 50 V.

NO QUIBBLE
5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE
- see below

★ ALL U.K. ORDERS DESPATCHED POST PAID

HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope – we pay postage on all letters sent to us by readers of this journal.

ILP ELECTRONICS LTD.

FREEPOST 5 Graham Bell House, Roper Close,
Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 Telex 965780

Please supply PE.8.

..... Total purchase price £.....


Enclose Cheque Postal Orders International Money Order

Please debit my Access/Barclaycard Account No.

NAME

ADDRESS

Signature

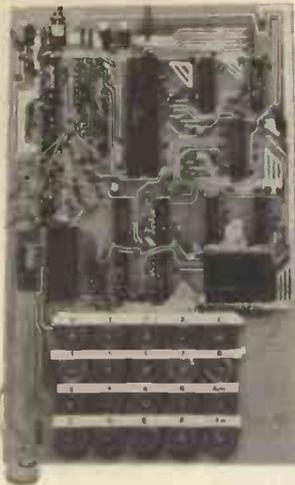

SPECIAL OFFER

of £34.10 (inc. P&P & VAT)
extended due to demand.

Designed by
Dr. A. A. BERK
— see PE review (April edition) and PE special offer in
May and June.

THE EDUKIT

The EDUKIT has proven a great success providing an excellent introduction to silicon chip technology from the bottom upwards. Many schools and colleges are using the kit, and sales now extend world-wide. The machine is not meant to form the basis of a large and expandable personal computer system. The EDUKIT teaches all those things which a purely BASIC-running machine cannot. I.e., the basis of hardware electronic control, down-to-earth Bits and Bytes, Machine Code etc. — and all this at a really throw-away price. The manual is written by Dr. A. A. Berk to impart educational understanding from the beginning.

The success of the EDUKIT allows us to extend the PE special offer £34.10 (fully inclusive of P&P and VAT).

**GET TO GRIPS WITH THE MICROPROCESSOR ITSELF
WITH THE EDUKIT.**

MODUS SYSTEMS LTD

Phone Letchworth (04626) 74468

29A EAST CHEAP, LETCHWORTH, HERTS SG6 3DA.

TECHNICAL SPEC.

- CMOS 1802 Processor (RCA) — excellent MPU for control.
- 256 bytes of RAM — plenty for learning machine code.
- Hexadecimal display — large and readable.
- Full hex keyboard — positive "click" type switches.
- Full manual — starts at soldering, ends with control circuits.
- Loudspeaker output — simple audio experiments.
- Excellent for all ages from secondary school level upwards.

EPROM PROGRAMMER

For 2708's & (multi-supply) 2716's

£37.30

inc. P&P, VAT and PCB (available separately).

Designed by **Dr. A. A. BERK**
As featured in PE project: **DEC '79, JAN '80.**

Ever wanted to save your programs in solid-state to prevent their having to be recalled each time? — 2708's are now cheap enough to allow those simple applications to be stored "forever". The Eprom programmer is memory mapped to allow its addition to any bug-oriented machine. See PE articles for easy

ADDITION TO COMPUKIT.

TECH. SPEC:

- 1k of use — RAM included — just write program into this RAM, press the button and the programmer "burns" it in automatically.
- Easy verification — Eprom can even be used in-situ on the board.
- 3-level power supply included — just needs 9-0-9V transformer and +5V supply.
- Many reliably in use in domestic and industrial applications.

COMPUTER SUNDRIES

1802 USER'S MANUAL (essential for full understanding of 1802. MPU used in EDUKIT) £3.99 + 50p P&P.

Full socket set for EDUKIT — £2.60 + VAT + 30p P&P.

EPROM PROGRAMMER PCB — £8.45 inc. VAT & P&P.

SPECIAL OFFER (1 OFF) — ITT 2020 (Apple) Computer System 48K RAM, 2 disk drives, electronics printer card, all in good condition — £1,249 + VAT.

FLOPPY DISCS — 5½" hard or soft sectored £3.30 + VAT.

PRINTER PAPER — 80 column sprocket-fed — for Anadex, CITO, Dolphin, Paper Tiger, etc. £21.25 for 2,000 sheets.

PROGRAMMABLE INTELLIGENT VDUs — (6800 based) green phosphor, full professional standards. RS232, any band up to 9600, solid, robust keyboard — £745 + VAT + £10 carriage.

MAIL ORDER PROTECTION SCHEME

INTRODUCTION

The Office of Fair Trading have agreed that the notice of the Mail Order Protection Scheme to appear in periodicals carrying mail order advertising should appear as follows:—

"MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfill orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Practical Electronics will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Practical Electronics summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded."

SOUTH EAST ENGLAND'S ELECTRONICS CENTRE

Interested in Electronics? Then why not pay us a visit and see our vast range of Test Equipment, Oscilloscopes, PSUs, Computer Equipment, Government Surplus, VDUs, ICs, Transistors, Relays, Motors, Bulbs, Cable Transformers, PCBs, Resistors, Amplifiers, etc., etc.

★ ★ ★ THIS MONTHS SPECIALS ★ ★ ★



SUPER 77 KEY KEYBOARD KIT

We've done it again! We've purchased a large quantity of CP CLARE top quality keyboard reed switches plus full QWERTY keytop sets and thrown in a PCB to enable you to customise the keys just as YOU want them, just add and wire an encoder chip and you can arrange ASCII, BAUDOT, anything! Adding up to a quality keyboard which would normally cost around £100.00. Supplied with layout and assembly info at only £26.99 + £1.50pp.

Miniature 5V 3 amp PSU, compact fully regulated, + crowbar protection. £8.50 + P&P 70p Super value PCB pack. Contents include 1 C's res. caps etc., etc. Guaranteed to include TTL and CMOS I/O Boards, Our choice. £2.50 + P&P 60p

Wire wrap patch panels inc. 10 16 pin and 54 14 pin gold plated DIL WW sockets + 64 TTL and DTL IC's dim. 6" x 7". £8.95 + P&P 85p

49 key coded QWERTY keyboard, 8 bit output, delayed strobe, 5V rail, TTL output. Ex-equip. un-tested. Supplied with edge conn. & connection diagram. £20.00 + P&P £1.50

NE555 10 for £2.40. 741 10 for £1.80. 1N4004 18 for £1.00. 0.125" RED LEDS 12 for £1.00. 2N3055H (RCA) 4 for £2.25. 1S44/1N4148 50 for £1.00. Stock list 50p. Where P&P not shown please add 40p per order.

Prices include VAT.

- ★ ELECTRONIC EQUIPMENT AND COMPONENTS PURCHASED FOR CASH
- ★ OPEN 9.30 TO 5.30 MONDAY TO SATURDAY
- ★ RETAIL AND TRADE
- ★ NO PARKING RESTRICTIONS
- ★ ACCESS & BARCLAYCARD

DISPLAY
ELECTRONICS

64-66 MELFORD ROAD
THORNTON HEATH
SURREY. 01-689 7702

SERVICE TRADING CO

FT3 NEON FLASH TUBE

High intensity multi turn high voltage, neon glow discharge flash tube. Design for ignition timing etc. £1.50, P. & P. 25p (£2.01 incl. VAT) 3 for £3. P. & P. 50p (£4.03 incl. VAT & P.)



WHY PAY MORE?

MULTI RANGE METER TYPE MF15A a.c. d.c. volts 10 - 50 250, 500, 1000 Ma 0-5, 0-10, 0-100. Sensitivity 2000V 24 range. diameter 133 by 93 by 46mm including test leads. Price £7.00 plus 50p P. & P. (£8.53 incl. VAT & P.)



METERS (New) - 90 mm DIAMETER

A.C. Amp., Type 62T2, 0-1A, 0-5A, 10A, 0-20A, 50A A.C. Volt, 0-150V, 0-200V.
D.C. Amp., Type 65C5, 0-2A, 5A, 0-10A, 0-20A, 0-50A, 0-100A.
D.C. Volt, 15V, 30V.



All types £3.50 ea. + P. & P. 50p (£4.00 incl. VAT), except 0-50A, 0-100A, D.C. price £5.00 + 50p P. & P. (£5.53 incl. VAT).

HEAVY DUTY SOLENOID

mf. by Magnetic Devices. 240V, A.C. intermittent operation. Approx. 20 lb. pull at 1.25 in. Ex-equip. Tested. Price: £4.75 + 75p. P. & P. (£5.53 incl. VAT & P.)



12V D.C. SOLENOID

12V, D.C. heavy duty Solenoid 4 Kp. pull. Easily removable from plate. All chassis containing 4x24V, D.C. Push Solenoids (1 1/2 lb. approx.). 5-gig. Counter, 6 min. photo cells. Sub-min. Micro-switches etc. etc. Ex-equip. London Transport Printer. Price: £9.00 + £1.00 p. & p. (total incl. VAT £11.50).

12V, D.C. Solenoid approx. 1lb. pull. Price: £1.40 + p. & p. 30p (total incl. VAT £1.96).

SOLENOIDS

WESTOOL SERIES 06 Model A3 24V, D.C. Price £1.50 + 50p p. & p. (Total incl. VAT £2.30)

WESTOOL SERIES D4 Model A, 24V, D.C. Price £1.00 + 30p p. & p. (Total incl. VAT £1.50)

AG/GT 24V, D.C. 70 ohm Coil Solenoid. Push or Pull. Adjustable travel to 3/16 in. Fitted with mounting brackets and spark suppressor. Size: 100 x 65 x 25 mm. Price: 3 for £2.40 + 30p. P. & P. (min 3 off.) (£3.11 incl. VAT & P.)

800 WATT DIMMER SWITCH

Easily fitted. Will control up to 800 W. of all lights except fluorescent at mains voltage. Price: £3.90 + 50p p. & p. (£5.08 incl. VAT).



REED SWITCHES

Size 28mm x 4mm dia. Price: 10 for £1.00 + p. & p. 20p. (total incl. VAT £1.38). 100 for £8.00 + p. & p. 30p. (total incl. VAT £9.55).

MICRO SWITCHES

Sub. Min. Honeywell Lever m/s type 3115m 906ft. 10 for £3.50 post paid (£4.03 incl. VAT)

These V3 types.

Button type (Pye) 10 for £3.00 (£3.45 incl. VAT)

Short Lever type 16amp. rating (Grouzet) £4.00 (£4.60 incl. VAT)

Roller Type (Bonnelia) 10 for £3.50. (£4.03 incl. VAT). N.M.S.

D.P. C/O lever m/switch mfg. by Cherry Co. USA. Precious metal low resistance contacts. 10 for £2.25 P. & P. 30p. Total incl. VAT £2.93 (min. 10).

MERCURY SWITCH

Size 27mm x 5mm, 10 for £5.00 + 30p P. & P. (incl. VAT £6.12) min quantity 10.

Heavy duty type, size 38 x 16 x 10mm, minimum quantity 10. £7.50 post paid (£8.53 incl. VAT & P.).

A.E.G. CONTACTOR

Type L56/L11. Coil 240V 50 Rs. Contacts - 3 make: 600V/20amp, 1 break: 600V/20 amp. Price: £8.50 + 50p P. & P. (£9.00 incl. VAT & P.).

ARROW-HART MAINS CONTRACTOR, Cat. No. 130A30. Coil 250V, or 500V, A.C. Contacts, 3 make 50 amp up to 600V, A.C. 20 hp. at 440V, 3 phase 50 Hz. Price: £7.75 + p. & p. £1.00 (incl. VAT, total: £10.06). N.M.S.

SMITH BLOWER

Type FF8. 1706. Small, quiet, smooth running, 240V, A.C. operation. Output aperture 45x40cm. Overall size 135x165 cm. Flange mounting. Price: £4.25, P. & P. 75p. (Total: £5.75 incl. P. & V.A.T. N.M.S.)

Other types available. S.A.E. for details

24 volt, D.C. BLOWER UNIT

Precision 24 volt, D.C. 0.8 amp Blower that works well on 12V 0.4 amp D.C. Producing 30 cu.ft. min at normal air pressure. £4.50 P. & P. 75p (incl. VAT £6.04). N.M.S.

INSULATION TESTERS NEW!

Test to I E E Spec. Rugged metal construction suitable for bench or field work constant speed clutch Size L 8in W 4in H 6in weight 6lb, 500V, 500 megohms. £49. Post 80p (£57.27 incl. VAT & P.). 1,000V, 1,000MΩ, £55. Post 80p (£64.17 incl. VAT & P. SAE for leaflet).

Yet another outstanding offer.

IMFD 600V Dubilier wire ended capacitors. N.M.S. 10 for £1.50 p&p 50p. (£2.30 incl. VAT + p&p) (min 10)

230V a.c. FAN ASSEMBLY.

Powerful continuously rated a.c. motor complete with 5 blade 6in. or 4 blade 3in. aluminium fan. Price £3.00. P. & P. 65p. (£3.20 incl. VAT & P.)



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT 0-260V

200 watt (1 amp inc. a.c. voltmeter) £14.50
0.5 KVA (2 amp MAX) £17.00
1 KVA (5 amp MAX) £22.50
2 KVA (10 amp MAX) £37.00
3 KVA (15 amp MAX) £45.50
5 KVA (25 amp MAX) £74.00
10 KVA (50 amp MAX) £168.00
15 KVA (75 amp MAX) £280.00



3-PHASE VARIABLE VOLTAGE TRANSFORMERS

3KVA (max. 15 amp.) £106-43 All plus Carriage
6KVA (max. 30 amp.) £159-37 & V.A.T.
10KVA (max. 50 amp.) £327-43

LT TRANSFORMERS

13-0-13V at 1 amp £2.50 P. & P. 50p (£3.45 incl. VAT)
0.4-4V/8V/24V/32V at 12 amp £18.50 P. & P. £1.90 (£23.46 incl. VAT & P.)

0-6V/12V at 20 amp £14.70 P. & P. £1.50 (£18.63 incl. VAT)

0-12V at 20 amp or 0-24V at 10 amp £12.00 P. & P. £1.50 (£15.53 incl. VAT & P.)

0-6V/12V at 10 amp £8.25 P. & P. £1.25 (£10.93 incl. VAT)

0-6V/12V/17V/18V/20V at 20 amp £19.00 P. & P. £1.50 (£23.58 incl. VAT & P.)

0-10V/17V/18V at 10 amp £10.50 P. & P. £1.50 (£13.80 incl. VAT)

Other types in stock; phone for enquiries or send sale for leaflet.

HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 t.p.s. Light output greater than many so called 4 Joule strobes. Hy-Light Strobe Kit Mk IV. £22.00 incl. £1.50 P. & P. (incl. VAT total £27.00). Specially designed case and reflector for Hy-Light £9.00. Post £1.50 (£12.08 incl. VAT & P.). Super Hy-Light Strobe (approx. 16 joules) Price £33. P. & P. £1.50 (incl. VAT total £39.68). Suitable case £11.00 + £1.50 P. & P. (£14.30 incl. VAT & P.).

XENON FLASHGUN TUBES

Range available from stock
S A E for details



ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft. 40 watt £8.70 incl. VAT £10.00 (callers only).

2ft. 20 watt £6.20. Post 75p. (£7.99 incl. VAT & P.)

(For use in stan bi-pin fittings).

12in. 8 watt £2.80. Post 35p. (£3.62 incl. VAT & P.)

9in. 6 watt £2.25. Post 35p. (£2.95 incl. VAT & P.)

8in. 4 watt £2.25. Post 35p. (£2.99 incl. VAT & P.)

Complete ballast unit, for either 6", 9" or 12" tube 230V AC op. £4.50. Post 45p. (£5.69 incl. VAT & P.). Also available for 12V DC op. £4.50. Post 45p. (£5.69 incl. VAT & P.).

400 watt UV lamp and ballast complete £38.00. Post £3.50 (£47.73 incl. VAT & P.). 400 watt UV lamp only £14.00. Post £1.50. (£17.83 incl. VAT & P.).

WIDE RANGE OF DISCO LIGHTING EQUIPMENT S.A.E. (foolscap) for details.

PROGRAMME TIMERS

240V A.C. operation. 12 individually adjustable cams. £7.50 + 75p P. & P. (£8.49 incl. VAT). R. T.

6 adjustable 6 fixed cams. Price £6.00 + 75p p. & p. (£7.78 incl. VAT). R. & T.

Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, embedded winding heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/250/500/1kΩ/1.5kΩ. £2.40. Post 20p (£2.99 incl. VAT & P.)

50 WATT 2500 £2.90. Post 25p (£3.62 incl. VAT & P.)

100 WATT 1/5/10/25/50/100/250/500/1kΩ/1.5kΩ/2.5kΩ/3.5kΩ £6.90 p. & p. 35p (£8.34 incl. VAT).

Black, Silver, Skinned knob calibrated in Nos. 1-9 1/2 in. dia. brass bush. Ideal for above Rheostats 24p each.

Wide range of AC and DC relays available from stock. Phone or write in your enquiries.

Other types available - phone for details. N.M.S.

230/240V A.C. Relays: Arrow 2 c/o. 15 amp £1.50 (£1.98 incl. VAT & P.)

T.E.C. open type 3 c/o. 10 amp £1.10 (£1.50 incl. VAT & P.)

KMKI Relay, 230V, A.C. 1 c/o. open type 10 amp contact, mf. by "Keyswitch" 80p. + 20p. p. & p. (£1.15 incl. VAT). 5 for £3.75 postpaid (£4.32 incl. VAT).

D.C. Relays: Open type 9/12V 3 c/o 7 amp £1.00 (£1.38 incl. VAT & P.) Sealed 12V 1 c/o 7 amp octal base. £1.00 (£1.38 incl. VAT & P.) Sealed 12V 2 c/o 7 amp octal base. £1.25 (£1.67 incl. VAT & P.) Sealed 12V 3 c/o 7 amp 11-pin. £1.35 (£1.78 incl. VAT & P.) 24V. Sealed 3 c/o 7 amp 11-pin £1.38 (£1.78 incl. VAT & P.) (lamps = contact rating). P & P on any Relay 20p.

Hallermann Deutsch. Hermetically sealed sub-min. Relay. 12-24V, D.C. 2 c/o. 850 ohm coil, 0.2 pitch. P.C. mounting. L 20 mm. W. 10mm. H. 12mm. Fraction of maker's price: £2.50 postpaid (£2.88 incl. VAT). N.M.S.

Diamond H heavy duty A.C. relay 230/240V a.c. two C/O contacts 25 amps res at 250 a.c. £2.50 p&p 50p. (£3.45 incl. VAT + p&p). Special base 60p. (incl. VAT 58p) N.M.S.

GEARED MOTORS

4.5rpm SIGMA motors approx. 35lbs inch

7 1/2rpm KLAXON motors approx. 25lb inch

28rpm WYNSCALE motors approx. 20lb inch

71rpm WYNSCALE motor approx. 10lb inch

Above four motors are designed for 110V. A.C. supplied with auto transformer 240V. A.C. operation. £7.75 p. & p. 75p. Total incl. VAT £9.78. N.M.S.

19 rpm FHP 220/240V. a.c. reversible, torque 14.5kg. Gear ratio 144-1. Brand new including capacitors mf. CITENCO. Price: £14.25 + £1.25 P. & P. (£17.83 incl. VAT). N.M.S.

30rpm. 230/240V. a.c. 50lb. in. mf. PARVALUX. Price: £15.00 + £1.50 P. & P. (£18.98 incl. VAT). N.M.S.

56 rpm. 240V. a.c. 50lb. in. 50Hz 0.7 amp. Shaft length 35mm. Dia. 15mm. Wt. 6kg. 600p. mf. FRACMO. Price: £15.00 + £1.50 P. & P. (£18.98 incl. VAT). N.M.S.

100 rpm. 110V. a.c. 115lb. in. 50Hz 2.8 amp. single phase split capacitor. (Immersed power).

Totally enclosed. In-line gearbox. Length 250mm. Dia. 135mm. Spindle dia. 15.5mm. length 145mm. Tested. Price: £12.00 + £1.50 P. & P. (£15.53 incl. VAT). R. & T. Suitable Transformer for 230/240V operation. Price £8.00 + 75p. P. & P. (£10.08 incl. VAT).

500rpm. 35 lbs. in. 115V. 50Hz. Price: £16.00 + £1.50 P. & P. (£20.13 incl. VAT). N.M.S.

Suitable Transformer for 230/240V. a.c. Price: £8.00 + £1.00 P. & P. (£10.35 incl. VAT). N.M.S.

12V, D.C. type SD2. Shunt w/p continuously rated 4000 rpm. mf. PARVALUX. Price: £10.00 + 75p. P. & P. (£12.38 incl. VAT). N.M.S.

1rpm 230/240V a.c. Synchronous geared Motor, mf. HAYDON. 21mm. 230/240V. a.c. Synchronous geared Motor, mf. CROUZET. Either type £2.90 + 30p. P. & P. (£3.68 incl. VAT). N.M.S.

1.400 rpm 115V. a.c. Motor, HP & continuously rated. Fitted with anti-vibration cradle mounting. Mf. FRACMO. Supplied complete with Transformer for 230/240V. a.c. operation. Price: £10.00 + £1.00 P. & P. (£12.65 incl. VAT). N.M.S.

24V, D.C. GEARED MOTOR

24V, D.C. 200 rpm 10lbs/in. continuously rated geared Motor mfg. by either Parvalux or Carter. Easily removable from heavy all. chassis containing 9x24V, D.C. Solenoids, microswitches, friction clutch, precision gearing etc. Ex-equipment London Transport Ticket Printer. Price: £11.00 + £2.00 p. & p. (total incl. VAT £14.95).

24V, D.C. REVERSIBLE MOTOR

Parvalux type SD12L 24 D.C. shunt wound Motor, either 133 rpm 65lbs in Gearbox ratio 30:1. Current 6.8 amp. Rating continuous. Will operate on reduced power and speed at 9V D.C. or less. Size Dia. 16mm, Width 150mm, Shaft dia. 16mm. Price £18.00 + £2.00 p. & p. (£20.70 incl. VAT). N.M.S. or 60 rpm 100lb in rating. Price as above. N.M.S.

100W Rheostat 1 ohm speed control available £6.90 (£7.94 incl. VAT).

ROTARY CARBON VANE VACUUM & COMPRESSOR.

Direct coupled to 1/3 hp. 110/115V. A.C. Motor 4.2 amp. 1380 rpm. Motor manu. by A.E.I. or G.E.C. Pump by Williams. Max. Vac. 25" H.G. Max. pressure cont. 10 p.s.i. int. 15 p.s.i. Max. air-flow 3 c.f.m. at "0" H.G. Price: £30.00 + £30.00 P. & P. (£37.95 incl. VAT). N.M.S.

Suitable transformer for 240V. op. £10.00 P. & P. £2.00 (£13.80 incl. VAT). N.M.S.

COMPRESSOR

Precision built USA. Horizontally opposed twin head diaphragm type producing 20lbs. approx. P.S.I. per head. 3.5 plus C.F.M. Output virtually pulse free. Powered by 110V A.C. motor size 30x23x15cm. Weight 7 kilos. Price £25.00 + £2.00 P. & P. (Total incl. VAT £31.05). N.M.S.

Suitable transformer for 240V op. £8.00 P. & P. £1.50 (£10.93 incl. VAT).

VERY EXCEPTIONAL OFFER

REDUCTION DRIVE GEAR BOX.

Ratio 72:1. Input spindle 1/2 x 1/2 in. Output spindle 3/4 x 3 in. long. Overall size approx: 120 x 98 x 88 mm. All metal construction. Ex-equip. tested. Price: £2.00 + 50p. (incl. VAT £2.88).

A.C. Wkg. TUBULAR CAPACITORS.

Fraction of makers price. Motor start etc.

1.5 mfd. 440V. A.C. 60p 7.5 mfd. 200V. A.C. £1.00

2 mfd. 250V. A.C. 60p 10 mfd. 250V. A.C. £1.00

2 mfd. 450V. A.C. 75p 10 mfd. 400V. A.C. £1.75

2.2 mfd. 440V. A.C. 75p 14 mfd. 400V. A.C. £3.00

3 mfd. 440V. A.C. £1.00 15 mfd. 250V. A.C. £1.50

4.1 mfd. 440V. A.C. £1.00 (Block) 15 mfd. 280V. A.C. £2.00

5.9 mfd. 180V. A.C. 80p 20 mfd. 250V. A.C. £2.25

5.4 mfd. 280V. A.C. 75p 50 mfd. 370V. £5.00

6.5 mfd. 280V. A.C. £1.00 (Block)









P. & P. up to 2.5 mfd. 25p. 3 mfd to 20 mfd. 50p. 50 mfd. £1.50. All plus V.A.T. N.M.S.

Time Switch

Venner Type ERD Time switch 200/250V a.c. 30 amp contact 2 on/2 off every 24 hrs. at any manually pre-set time. 36 hour Spring Reserve and day omitting device. Built to highest Electricity Board specification. Price £9.00. P. & P. 75p (£11.22). R. & T.

SANGAMO WESTON TIME SWITCH

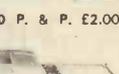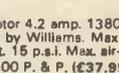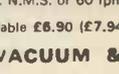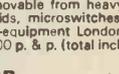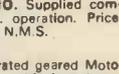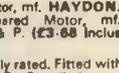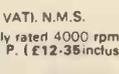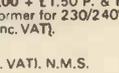Type S251 200/250V. a.c. 2 on/2 off every 24 hours. 20 amps contacts with override switch dia. 4 x 3 price £8.00 P. & P. 50p incl. VAT £9.78. Also available with Solar dial. R. & T.



CAMBRIDGE LEARNING ENTERPRISES

Self Instruction Courses

Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency, with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, and clear documentation

BOOK 1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs. BOOK 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition. BOOK 3 Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB BOOK 4 Advanced BASIC; subroutines; strings; files; complex programming; examples; glossary.

Also THE BASIC HANDBOOK (BHB) £11.50 An encyclopaedic guide to the major BASIC dialects. A must if you use other peoples' programs

and: **ALGORITHM WRITER'S GUIDE (AWG) £4.00** Communicate by flow chart! Learn to use Yes/No questions for: procedures, system design, safety, legislation etc.

Understand Digital Electronics

Written for the student or enthusiast, this course is packed with information, diagrams, and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters, and simple arithmetic circuits; and finally to an understanding of the design and operation of calculators and computers

BOOK 1 *Decimal, Octal, hexadecimal, and binary number systems and conversion between number systems; negative numbers; complementary systems.* BOOK 2 *OR and AND functions; multiple-input gates; truth tables; De Morgan's Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.* BOOK 3 *Half, full, serial, and parallel adders; subtraction; processors and ALU's; multiplication and division.* BOOK 4 *flip flops; shift registers; asynchronous, synchronous, ring, Johnson, and exclusive-OR feedback counters; ROMS and RAMS.* BOOK 5 *Structure of calculators; keyboard encoding; decoding display-data; register systems; control unit; PROM; address de-coding.* BOOK 6 *CPU; memory organisation character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming, assemblers; computers; executive programs; operating systems.*

DIGITAL COMPUTER LOGIC & ELECTRONICS (DCL) £7.00 A course covering the material in italics above, but at a slower pace. (4 vols)

GUARANTEE - No risk to you. If you are not completely satisfied your money will be refunded without question, on return of the books in good condition.

CAMBRIDGE LEARNING ENTERPRISES, RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON.

PLEASE SEND ME:-

CPB (£9.00)	Quantity □ □ □ □
BHB (£11.50)	
AWG (£4.00)	
DDS (£12.50)	
DCL (£7.00)	


FOUR WAYS TO PAY:

- 1) A U.K. cheque or a U.K. postal order (Not Eire or overseas)
- 2) A bank draft, in sterling on a London bank (available at any major bank)
- 3) Please charge my Access/M.Ch Barclay/TrustC/Visa Am. Exp. Diners
- 4) Or phone us with these credit card details - 0480 67446 (ansaphone) 24 hour service.

Card No. Signed
THESE PRICES COVER THE COST OF SURFACE MAIL WORLDWIDE. AIRMAIL:
 Eur, N.Af, Mid.E. add 1/2 to price of books; Jpn, Aus, N.Z, Pcfc add 1/2; elsewhere add 1/2

Name
 Address

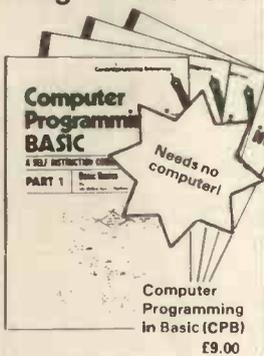Cambridge Learning Enterprises, Unit 23, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR England. U.K. Delivery: up to 21 days
 Proprietors: Drayridge Ltd., address as above, Reg. in Eng. No. 1328762



AT BLINKIN' LAST COLOURBOARD II

THE NEW 50HZ COLOUR VERSION OF OHIO SCIENTIFIC'S SUPERBOARD II IS HERE AND LIKE A TON OF BRICKS DOWN CRASHES THE PRICE OF STANDARD SUPERBOARD II

50HZ UK BLACK AND WHITE SUPERBOARD II £159.95+15% VAT POST FREE.
 COLOURBOARD II £205 + 15% VAT.



THE UNIQUE SPECIAL OFFER YOU CAN'T RESIST

- * * * * *
- * If bought with superboard or colour board these items are at the reduced prices shown first. Also sold separately at the bracketed prices. Add 15% VAT. Modulator and power supply kit £7.95 (£11), 4K extra ram £20 (£24), Case £23 (£26), Cassette recorder £13 (£15).
- * * * * *

BATTERY ELIMINATOR KIT

100ma radio types with press-stud connectors 4 1/2v £1.49, 6v £1.49, 9v £1.49, 4 1/2+4 1/2v £1.92, 6+6v £1.92, 9+9v £1.92. Stabilized TTL computer supply 5v 2A £7.44, 5v 4A £12.60. Stabilized 8-way types 3/4/8/7 1/2/15/18v 100ma £2.60, 1A £6.50, 2A £9.84. Stabilized variable voltage models 2-18v 100ma £2.60, 1-30v 1A £6.75, 1-30v 2A £12.10. 12v car converter 6/7 1/2/9v 1A £1.35.

SINCLAIR (THANDAR) PRODUCTS



SC110 10MHz oscilloscope (illustrated) £144.95. PFM200 £51.95, case £2.07, adaptor £4.20, connector kit £13.95. Microvision TV £89, mains adaptor £6.88. PDM35 £34.23, mains adaptor £4.20, case £2.07, DM350 £76.70, DM450 £102.17, DM235 £55.55. Accessories for all 3 models:- rechargeable batteries £7.99, mains adaptor/charger £4.20, case £8.90. Enterprise prog calculator £19.95.

BATTERY ELIMINATORS

3-way switched type with 4-way multijack 6/7 1/2/9v 300ma £3.14. 100ma radio models with press-stud connectors 9v £3.77, 9+9v £4.99. Fully stabilized model 3/6/7 1/2/9v 400ma £6.50. Car converter 12v dc input, output 3/4 1/2/9v/12v 800ma £2.76.

SWANLEY ELECTRONICS

Dept. PE, 32 Goldsai Rd., Swanley, Kent BR8 8EZ.

Mail order only. Please add 35p postage. Prices include VAT unless stated. Lists 27p post free. Overseas customers deduct 13%. Official credit orders welcome.



Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

- AUDAX ● AUDIOMASTER ● BAKER ● BOWER & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN'S ● HARBETH ● JISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO (Dept. P.E.)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Tel: 0625 529599

FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS ETC.

Tel: 0625 526213

(SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKERS

AITKEN BROS

35, High Bridge, Newcastle upon Tyne

Tel: 0632 26729



EXP300



PB6 Kit

EXP300

550 contacts with two 50-point BUS bars. Size 152x53mm. £6-95.

PROTO-BOARD 6 KIT

630 contacts, four 5 way binding posts, accepts up to 6 14 pin DIPs. £10-98.

CSC LOGIC PROBES

LP-2 ECONOMY PROBE

Min. pulse width 300 nanoseconds, 300 KΩ input impedance, tests circuits up to 1.5MHz. Detecting pulse trains or single-shot event in TTL, DTL, HTL, and CMOS circuits. £20-95.

LP-1 Memory Probe £35-65

LP-3 High Speed Memory Probe £58-75

CSC catalogue available. Please send S.A.E.

CALSCOPE SUPER 6 £186-30

A portable single beam 8MHz bandwidth oscilloscope with easy to use controls. High gain to 10 mV/cm and wide time base range from 1μs to 100 m/cm. Full specification on request. Please send S.A.E. Professional scopes you can afford.

CALSCOPE SUPER 10 £251-85

A dual trace 10MHz instrument of the very highest performance and quality. It has an accuracy of 3% which is achieved by the use of built-in stabilised power supplies which keep the trace rock steady over a wide range of mains fluctuations. Full specification on request. Please send S.A.E.

SINCLAIR LOW POWER PORTABLE

OSCILLOSCOPE SC110 £159-85

The SC110 has a 10MHz bandwidth and sensitivity down to 10mV per division. Full trigger facilities are provided, including bright line, auto with TV line and frame positions. Please send for full spec. and illustrated brochure.

TMK 500 MULTIMETER 30,000 o.p.v. AC

volts 2.5, 10, 25, 100, 250, 500, 1000, DC volts. 0.25, 1, 2.5, 10, 25, 100, 250, 1000, DC current 50μa, 5mA, 50mA, 12 amp. Resistance 0-6K, 60K, 6MEG, 60MEG, Decibels, -20 to +56 db. Buzzer continuity test size, 160 x 110 x 55MM. Batteries & leads included.

PRICE £25-95.

CSC EXPERIMENTOR BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter/number identified nickel-silver contact holes. Start small and simply snap lock boards together to build breadboards of any size.

SINCLAIR DM350

£83-95

SINCLAIR DM450

£114-95

Size 255x148x40mm. DM350 3½ digit display DM450 4½ digit display. Both provide six functions in 34 ranges. D.C. voltage 10μV to 1200V (100μV on DM350) A.C. voltage 100μV to 750V. D.C. current 1nA to 10A. A.C. current 1nA to 10A resistance 10mΩ to 20MΩ (100mΩ on DM350). Accessories for DM350 & 450 as for DM235 below. Full spec. on request. Please send S.A.E.

Sinclair PFM200 frequency meter

Size 157x76x32mm. Range 20Hz to 200MHz. Accessories and illustration as for PDM35 below. £57-95.

SINCLAIR PDM35

DIGITAL POCKET MULTIMETER

DC volts (4 ranges) 1mV to 1000V AC volts 1V to 500V DC current (6 ranges) 1nA to 200mA. Resistance (5 ranges) 1Ω to 20 MEGΩ. PRICE £39.95 AC Adaptor £4-25 de luxe padded carrying case £1-95 MN 1604 Battery £1-28. Size 157x76x32mm.

SINCLAIR DM235

BENCH-PORTABLE DIGITAL

MULTIMETER.

DC volts (4 ranges) 1mV to 1000V AC volts (4 ranges) 1mV to 750V AC & DC current 1μA to 1000mA Resistance (5 ranges) 1Ω to 20 MEGΩ. PRICE £60-98. Carrying case £8-95. AC adaptor/charger. £4-25. Rechargeable Battery Pack. £8-95. Size 255x148x40mm.

PANEL METERS

DIMS 60MM x 45MM. 50μ amp, 100μ amp 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50v AC, 300V ac, "S", "VU" 50-0-50μa, 100-0-100μa, 500-0-500μa. PRICE £5-95.

DESOLDERING TOOL

£6-45


SUCTION PUMP.

Education Establishment Orders Accepted.

PHONE OR SEND YOUR ACCESS OR

BARCLAYCARD NUMBER

ALL PRICES INCLUDE POSTAGE AND VAT.

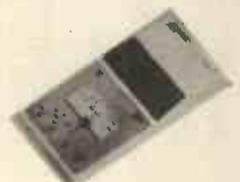

MONITORS MONITORS MONITORS



Uncased from 3" to 12"
Cased from 5" to 20"

Semi professional or professional available from stock.

Monitor PCB's including Transformers and Tubes also in stock.

Phone or write for details.

CROFTON ELECTRONICS

Crofton Electronics Limited
35 Grosvenor Road, Twickenham, Midx.
Tel: 01 891 1513

PROGRESSIVE RADIO

31, CHEAPSIDE, LIVERPOOL L2 2DY
SEMICONDUCTORS. Texas R1038 TO3 power trans 50p. TBAR00 50p. 741 8 pin 22p. NE555 24p. TAG4443 SCR 45p. 723 14 PIN REGS. 35p. AD 161/2 MATCHED PAIRS 70p. 2N5062 SCR 18p. TIL209 RED LEDS 10 for 75p. BD238 28p. BD438 28p. MPU131 P.U.T. 40V, 200mA. 375MMW 15p each 2N3773 £1.75. Infra Red 0.2 LEDs 30p.
MINIATURE MAINS TRANSFORMERS. ALL 240VAC PRIMARY. 6-0-6 100mA. 9-0-9 75mA. 12-0-12 50mA all 75p each. 12V 200mA 75p. 6V 500mA £1.10p 0-6V-0-6V 280mA £1.30.
PULSE TRANSFORMERS. 1:1 (GPO type) 30p. 1:1 plus 1 min. P.C. mounting 60p.
MINIATURE SOLID STATE BUZZER. 33x17x15mm. output at 3 feet 70db, only 15mA drain, operating range 4-15VDC 75p each.
LOUD BUZZER. 6-12 volts 63p. Rotary Alarm siren, 12VDC. Red plastic body and mounting bracket 68x75mm £4.50p.
POCKET MULTIMETER. MODEL NH55 2,000 ohms per volt. 1,000 volts AC/DC. 100mA DC current, 2 resistance ranges to 1 meg £5.50p.
SOLDER SUCKER. High suction/teflon nozzle. £4.85p.
MURATA TRANSDUCERS. 40KHz., REC/SENDER £3.50 pair.
MOTORS. 3V model type 22p. 6V cassette motor £1.20p. Replacement 12VDC 8 track motors 55p. Ex. equip 5-7 volt cassette motors 70p. Low rev. mains motor 240VAC motor with gearbox 21 RPM 75p.
AMPHENOL COAX CONNECTORS. Plugs 47p. Sockets 42p. Elbows 90p. Reducers 13p. BNC plugs. crimp 38p.
HIGH IMPEDANCE HEADPHONES, mono 2,000 ohms imp. transducer type, adjustable band and padded ear-piece £2.75.
SPECIAL OFFER STEREO HEADPHONES. 8 ohms, adjustable, standard stereo plug only £2.95p
INTERCOM UNITS (can be used as baby alarm) supplied with approx. 60' cable, call button. 2 was £8.25 pair, 3 way £7.25p. WIRELESS INTERCOM. 2 units both operate on 240VAC and mains connected. AM frequency 180KHz. £29.95p.
MINIATURE TIE PIN MICROPHONE. Omni, 1K imp., uses dead aid battery (supplied) £4.95p. LOW COST CONDENSER MIKE. Stick type Omni, 600 ohms on/off switch, standard jack plug only £2.95p. EM807 CONDENSER MICROPHONE. Highly polished metal stick mike, uni directional, 600 ohms. 30-18KHz., on/off switch only £7.95p. DYNAMIC STICK MIKE. CARDIOD, dual imp., 600 ohms or 20K. 70-15KHz., attractive black metal case only £7.75p.
PUBLIC ADDRESS HORN SPEAKERS. Suitable for outdoor use. 5" round 8 watts. 8 ohms, adjustable bracket £4.95p. 6" 15 watts 8 ohms adjustable bracket £8.25p.
CRIMPING TOOL, for standard terminals also 6 gauge stripper and wire cutter, insulated handles only £2.30. Cash with order please, official orders welcome from schools etc. please add 30p post and packing. VAT inclusive. SAE for latest illustrated stock list. ALL ORDERS DESPATCHED BY RETURN POST

LB ELECTRONICS


PROCESSOR ICS (ALL FULL SPEC.)

1702A £2.50, 2708 £6.25, 2716 single rail £28.50, LM323K 5 volts 3 amps £4.50, 7805 £1, 7812 £1, 214 £4.50.
DIL SKTS LOW PROFILE: 8 way 12p, 14 way, 15p, 18 way 20p, 16 way 17p, 20 way 23p, 22 way 28p, 28 way 45p, 24 way 35p, DIL 16 WAY HEADER SPECIAL OFFER ONLY 45p.
74116 SPECIAL OFFER 75p, 74125 4 for £1, 74198 75p, 74194 50p, 74181 80p, TIL 209 RED 10p, 2" RED 12p.
MM5240 character generator + data £3.50.
4 digit EX calculator display 4 for £1 + data.
P.E.T. edge connector (memory expansion) £1.40.
74LS, C.MOSS, sub miniature toggles, 74TTL, and computer equipment is stocked, i.e. V.D.U. printers etc. vast range of power supplies for callers.
ALL ITEMS P/P 30p.
L.B. ELECTRONICS, 11, HERCIES ROAD, HILLINGDON, MIDDLESEX.
UXBRIDGE 55 399
(Just off A 40)



OPEN: Monday, Thursday, Friday and Saturday 9.30-6.00.

Toroidal Transformers

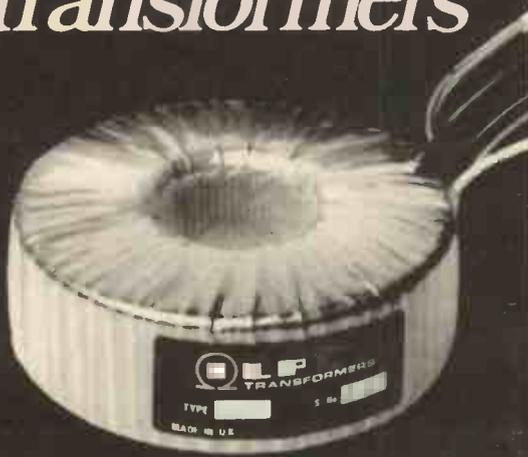

Yet another new development from I.L.P

(covered by 5 year guarantee)



A division of
I.L.P. ELECTRONICS LTD.
Graham Bell House, Roper Close,
Canterbury CT2 7EP
(0227) 54778 Telex 965780

We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents within the range and are appreciably more efficient. Our toroidals cost virtually the same as their now outdated laminated equivalents and hum is down to a negligible tenth of what it used to be. Each I.L.P. toroidal transformer is supplied with rigid mounting kit comprising centre bolt, two neoprene and one steel washer.

TYPE	VA	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT	DIMENSIONS OIA-HT	WEIGHT KG	PRICE
2X010 2X011 2X012 2X013 2X014 2X015 2X016	50	6+6 9+9 12+12 15+15 18+18 22+22 25+25	4.16 2.77 2.08 1.66 1.38 1.13 1.00	70x40mm	0.9	TRANSFORMERS IN THIS RANGE £5.40 + £1.10 P/P + £0.80 VAT
3X010 3X011 3X012 3X013 3X014 3X015 3X016	80	6+6 9+9 12+12 15+15 18+18 22+22 25+25	6.64 4.44 3.33 2.66 2.22 1.81 1.60	90x30mm	1.0	TRANSFORMERS IN THIS RANGE £5.70 + £1.20 P/P + £1.04 VAT
4X010 4X011 4X012 4X013 4X014 4X015 4X016	120	6+6 9+9 12+12 15+15 18+18 22+22 25+25	10.00 6.66 5.00 4.00 3.33 2.72 2.40	90x40mm	1.2	TRANSFORMERS IN THIS RANGE £6.72 + £1.30 P/P + £1.20 VAT
5X016 5X017	160	25+25 30+30	3.20 2.66	110x40mm	1.8	£8.88 + £1.40 P/P + £1.54 VAT
6X016 6X017	300	25+25 30+30	6.00 5.00	110x50mm	2.8	£12.27 + £2.50 P/P + £2.22 VAT

NOTE: For 220V Primary please insert 1 in place of X in type number. Example: 120VA 240V 15+15V, 4A=42013.
For 240V Primary please insert 2 in place of X in type number. Custom design and O.E.M. enquiries welcomed.

FREEPOST

We pay postage on your enquiries and orders. Simply address your envelope: FREEPOST T2, I.L.P. ELECTRONICS, Graham Bell House, Roper Close, Canterbury CT2 7EP. (No stamp required).

I.L.P. ELECTRONICS, ROPER CLOSE, CANTERBURY CT2 7EP

Please supply.....

I enclose Cheque Postal Orders International Money Order Access

Barclaycard Account No.

Name.....

Address.....

High performance, low cost AUDIO SIGNAL GENERATOR

Battery model
AO113.
£29.50
(UK tax extra £4.40)
Mains version
£36.00
(+ UK tax £5.40)



Available also as
kit of parts at
£23.00
(+vat £3.45 UK only)
p. & p. £1.50

Spec. 10hz-100KHz. Output 1v rms, attenuated. Distortion better than .02% (1KHz).

TELERADIO ELECTRONICS

325 Fore Street, Edmonton N90 OPE. Tel. 807 3719.

Also RF signal generators. SWR meters. MVMt. Function (sweep Generators) etc.

Details sent on request.




Top Priority for every constructor- HOME RADIO CATALOGUE

- Over 2,000 items clearly listed.
- Profusely illustrated throughout.
- Over 100 A-4 size pages.
- Bargain list included free.

Send cheque or P.O. for £1.30

HOME RADIO Components LTD
Dept. PE, P.O. Box 92, 215 London Road,
Mitcham, Surrey. 01-648 8422

— CLEF KITS —

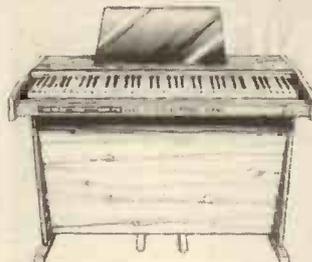

ELECTRONIC ROTOR

Two speed organ rotor simulation plus a three phase chorus generator on a single p.c.b. (8"x5"). Kit includes all components/IC sockets throughout/mains operation and stereo headphone. Driver p.c.b. Easily integrates with existing organ.

COMPONENT KIT - £89

KEYBOARDS

We believe that we have located the best manufacturer of square front Keyboards, as used in our Kits, and can also supply Keyswitch hardware including the industry standard soft plated contact springs.

49 NOTE C-C £23.80
73 NOTE F-F £37.00
88 NOTE A-C £45.00

All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

BUILDING SERVICE

We are specialists in Electronic Piano Manufacture and can build your Piano for you - see lists.

INFORMATION

Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted, all prices include V.A.T., carriage & Insurance.

VISITS

Are welcome by appointment, otherwise Mail Order Only.

EXPORT

Enquiries welcome - In Australia please contact JAYCAR (Sydney).

Back up TELEPHONE advice is available from the Designer to supplement the clear instructions included with the above Kits.

High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.

JOANNA 72 & 88 PIANOS

Six and 7 1/2 Octave Electronic Pianos with unique Touch Sensitive Action as used in the P.E. JOANNA, which electronically simulates piano key inertia - a feature not available in any other design. Build this widely acclaimed professional instrument, for either domestic or Stage use, from our top quality Component Kits.

SIX OCTAVES - £207
7 1/2 OCTAVES - £232

P.E. STRING ENSEMBLE

The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.

COMPONENT KIT - £169

P.A.'s - SPEAKERS - CABINETS

Units can be supplied to add to the Piano Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. PE) 16, Mayfield Road, Bramhall, Cheshire SK7 1JU.
061-439 3297



RECEIVERS AND COMPONENTS

TUNBRIDGE WELLS COMPONENTS. Ballards, 108 Camden Road, Tunbridge Wells. Phone 31803. No Lists. Enquiries S.A.E.

TURN YOUR SURPLUS Capacitors, transistors, etc., into cash. Contact **COLES-HARDING CO.**, 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 15V, 25V, 50V.
 0.47 1.0 2.2 4.7 10 Mfds. — 5p.
 22 & 47 51p. (50V-6p). 100—7p. (50V—8p).
 220—8p. (50V—10p). 470—11p. (40V—16p).
 1000/15V—15p. 1000/25V—18p. 1000/40V—35p.
Subminiature bead Tantalum electrolytics.
 0.1—0.22 0.47 1.0 \pm 35V 4.7 \pm 6.3V — 14p.
 2.2/35V. 4.7/25V—15p. 10/25V. 15/16V—20p.
 22/16V. 33/10V. 47/6V. 68/3V & 100/3V—30p.
 15/25V. 22/25V. 47/10V—35p. 47/16V—80p.
Subminiature Ceramic Caps. E12 Series 100V.
 2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.
 10% 390 pf. to 4700 pf.—4p.
Vertical Mounting Ceramic Plate Caps. 50V.
 E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf.—2p.
Polystyrene E12 Series 63V. Horizontal Mtng.
 10 pf. to 820 pf.—3p. 1000 pf. to 10,000 pf.—4p.
Miniature Polyester 250V Vert. Mtg. E6 Series.
 .01 to .068—4p. .1—5p. 15. 22—8p. .33. 47—10p.
 .68—12p. 1.0—15p. 1.5—22p. 2.2—24p.
Mylar (Polyester) Film 100V. Vertical Mounting.
 .001. .0022. .0047—3p. .01. .022—4p. .04. .05. 0.1—5p.
Miniature Film Resistors Highstab. E12 Ser. 5%.
 0.125W mixed carbon/metal 100 to 1M Ω —1p.
 0.25W Carbon 1 Ω to 10M Ω (10% over 1M Ω)—1p.
 (E24 Series av. In 1W C. Film 1 Ω to 5M Ω).
 0.25W. 0.5W & 1.0W Metal Film 100 to 2M Ω —2p.
 1N4148—2p. 1N4002—4p. 1N4006—8p. 1N4007—7p.
 BC107/8/9. BC147/8/9. BC157/8/9. BF194 & 7—10p.
 8 Pin Ic's. 741 Op. amp.—18p. 555 Timer—24p.
 Di! Holders 8 pin—9p. 14 pin—12p. 16 pin—14p.
 LED's. 3 & 5mm. Red—10p. Green & Yellow—14p.
 Grommets for 3mm.—14p. 2 pce. holders 5mm.—24p.
 20mm. O.B. Fuses .15. .25. .5. 1. 2. 3 & 5A—3p.
 20mm. Antil Surge 100mA. to 50A—5p.
 20mm. Fuseholders P.C. or Chassis Mtg.—5p.
 Solid A1. knobs 15mm.—25p. 25mm.—35p. 30mm.—50p.
 400mW Zener diodes E24 series 2V7 to 33V—8p.
 Prices VAT inclusive Post 15p. (Free over £5.00).

THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

BURNEMOUTH/POOLE. Electronic Components for the Hobbyist, and FRIENDLY Service. Why not pay us a visit. H & H Electric Ltd., 353 Ashley Rd., Parkstone. 742643.

T & J ELECTRONICS COMPONENTS — Quality Components — Sensible Prices. Same day Service. Send 30p in stamps for our full lists. 98 Burrow Road, Chigwell, Essex IG7 4HB.

SLOAN ELECTRONIC EQUIPMENT

117 Orby Drive, Belfast BT5 6AG

NE555 8 pin DIL 18p	10-way rotary switch. Make before break 22p	741 8-pin DIL 18p
PP3 Battery Clip 12p	2-pole changeover. 8A/250v a.c. rocker. 22p	100 Resistors 85p
	BC337 9p. BFY52 20p	
	35p Post and Pack	

PHOTOTRANSISTORS — TIL 78. Brand New devices 0.40p each Inc P&P. Quantity price on application. Trilec Instruments Ltd., 17 Church Street, Mkt. Lavington, Deves, Wilts. Tel: Lavington 2361.

RESISTORS 1W and 1/2W surplus to requirements 50p per hundred. Send S.A.E. for Lists. PHONOSONICS, 22 High Street, Sidcup, Kent. 01-3026184.

2000 BRAND NEW Capacitors Silver-Micro Pulse Bead Electrolytics etc., Fantastic value £32, Post Paid. Zero VAT. 200 Mixed sub-min skeleton presets £5. (Free with Capacitors) Calder Components, 19 Sandbeds Road, Pellon, Halifax.

SMALL ADS

The prepaid rate for classified advertisements is 24 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £8.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

100. ASSORTED COMPONENTS 115p. 100. assorted resistors 60p. 100. assorted capacitors 150p. 50. reed switches 20p. 10. mains neons 50p. 10. Micro Switches 150p. Add 25p P&P. DURRANTS, 9 St. Mary's Street, Shrewsbury, Salop.

CLEARANCE PARCELS: Transistors, Resistors, Boards, Hardware, 10lbs only £5.80! 1,000 Resistors £4.25, 500 Capacitors £3.75. BC108, BC171, BC204, BC230, 2N5061, CV7497 Transistors 10 70p, 100 £5.80. 2N 3055, 10 for £3.50. S.A.E. Lists: W.V.E. (2), 15 High Street, Lydney, Gloucestershire.

EX EQUIPMENT Radiospares 30 O-HM microphone transformers £1.75. Components + Designs for Digital Music Synthesizers, Mixers, Amplifiers. SAE list. M. Bryant, 49 Mowbray Grove, South Queensferry, West Lothian.

POTENTIOMETERS. Resistors, D.I.L. Sockets-Quality Components at keen prices. Send large S.A.E. for lists. T. Milner, 203 Goodman Park, Slough, Berkshire SL2 5NP.

100 DIODES 85p. 50 Transistors 95p. 10 I.C.s 75p. All mixed. Post Paid. Lists 15p. Sole Electronics, (P.E.) 37 Stanley Street, Ormskirk, Lancs. L39 2DH.

SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets on Radio, Tv, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

EDUCATIONAL

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
 Dept. X272 Intertex House, London SW8 4UJ
 Tel. 01-622 9911 (all hours)
 State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
 Dept. X272 Intertex House, London SW8 4UJ
 Tel. 01-622 9911 (all hours)
 State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
 Dept. X272 Intertex House, London SW8 4UJ
 Tel. 01-622 9911 (all hours)
 State if under 18

BOOKS AND PUBLICATIONS

INTRODUCTION TO MICROPROCESSORS And Computing (Starter book) £2.30. Send SAE for descriptive list of micro, electronic IC project books and solderless breadboard. **EDUCATIONAL DATA AND TECHNICAL SERVICES**, 59 Station Road, Cogenhoe, Northampton NN7 1LU.

ANY REQUESTED SERVICE SHEET £1 + Large S.A.E. Full repair data any named TV £5.50 (with circuits, layouts etc. £7). SAE brings newsletter, bargain offers, etc. AUSPEL, 76 Church St, Larkhall, Lanarks ML9 1HE.

BOOKS, BOOKS, BOOKS. — Large range of Electronics Books in stock. Send S.A.E. for list. Servio Radio, (Dept PE8), 156/8 Merton Road, Wimbledon, SW19 1EG.

FOR SALE

37 NOTE KEYBOARDS with 3 Pole Contacts £15 each. Brand New Top quality I.C.'s ICL8038 £2. CA723 25p, 741 15p, 748 25p. Pots 10K LIN 10p. 250K LIN Tandem 20p. Also have brand new synthesizers complete with Audio Lead and instruction book. Guaranteed for 1 year and after sales service. All at manufacturers clearance prices. Ring Banbury 58792 before 2 p.m. or after 5.30.

FOR SALE "P.E.JOANNA" Electronic Piano £55. Double Beam Oscilloscope £12. Phone Derby 73408.

"SOLARTRON" modern double-beam oscilloscope Type 'CD1400', plug in modules. Exceptional condition, £180 or V.N.O. 051-355 2833 (evenings). Also 'Heathkit' transistor-tester, NOT HOME BUILT. Type IM-36. Reasonable offer?

NEW BACK ISSUES of "Practical Electronics" available 80p each Post Free. Open P.O./Cheque returned if not in stock — **BELL'S TELEVISION SERVICES**, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

SITUATIONS VACANT

INDUSTRIAL ELECTRONICS: Are you an Electronic Test Technician or Service Mechanic? Have you had an apprenticeship followed by at least 5 years recent practical experience with a manufacturing or servicing organisation? If so we can offer you employment as an **INSTRUCTOR**, with good promotion opportunities and pensionable security, at Gloucester, Bristol and Swindon skillcentres. Starting salary £6,000 p.a. rising by two increments to £7,110 p.a. For more information contact Miss A. Curran, M.S.C., T.S.D., 11 Park Place, Clifton, Bristol. Telephone Bristol 20661.

WHETHER sea-going or shore-based, an exciting life awaits you as a Marine Radio Officer. Full details from The Principal, Barking College of Technology, Dagenham Road, Romford, RM7 0XU. (Telephone Romford 66841).

INDUSTRIAL ELECTRONICS. Are you an Electronic Wireman/Tester or Prototype Wireman? Have you had an apprenticeship followed by at least 5 years recent practical experience? If so we can offer you employment as an **INSTRUCTOR**, with good promotion opportunities and pensionable security at Bristol and Swindon skillcentres. Starting salary £6,000 p.a. rising by two increments to £7,110 p.a. For more information contact Miss A. Curran, M.S.C., T.S.D., 11 Park Place, Clifton, Bristol. Telephone Bristol 20661.

MISCELLANEOUS

COMPUKIT SOFTWARE & INFORMATION. Basic Line Renumber, only uses 1/2 K. 4K or 8K version cassette £2.95 inc. Also Full Screen Editor, Calendar & Diary, Alphabetical Directory etc. S.A.E. for details & Free Information Sheet. N. V. Davies, 11 Holloway, Haverfordwest, Dyfed.


RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.45 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call: Sandwell Plant Ltd, 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS, 021-354 9764. or see them at T.L.C. 32 Craven Street, Charing Cross, London WC2.

NEAT! TIDY! HANDY!

INTERLOCKING PLASTIC STORAGE DRAWERS

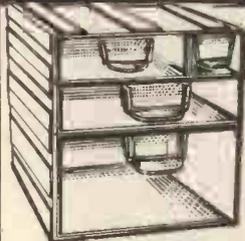

AS SUPPLIED: TO POST OFFICE & GOVT DEPTS

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units

interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

SINGLE UNITS (1D) (5in+2½in+2½in) £3.90 DOZEN

DOUBLE UNITS (2D) (5in+4½in+2½in) £6.50 DOZEN

TREBLE (3D) £5.90 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £8.90 for 8.

Extra large size (6D1) £7.90 for 8.

PLUS QUALITY DISCOUNTS

Orders over £60, less 5%. Packing/Postage/Carriage: Add £1.30 to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES

Please add 15% V.A.T. to total remittance.

All prices correct at time of going to press.

FLAIRLINE SUPPLIES

(PE8) 124 Cricklewood Broadway, London N.W.2. Tel: 01-450 4844.

UK 101 SOFTWARE. Try our original programmes (on cassette) GRAPHIC PAINT BRUSH-GRAPHIC PLOTTER etc. Working programmes that will give you ideas of your own. S.A.E. M & B SERVICES, 182a, High Street, Margate, Kent.

MAKE YOUR OWN PRINTED CIRCUITS
Etch Resist Transfers - Starter pack (5 sheets, lines, pads, I.C. pads) £1.60. Large range of single sheets in stock at 34p per sheet.

Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. Full instructions supplied, 2 sheets (20 x 25cm) negative paper and 2 sheets (18 x 24cm) positive film £1.80. Drafting film (30 x 21cm) 22p per sheet.

17p stamp for lists and information. P&P 30p/order
P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac Light Sensitive Lacquer - now greatly improved and very much faster. Aerosol cans with full instructions. £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1.70 sq. ft. Post/Packing 60p. **WHITE HOUSE ELECTRONICS, P.O. Box 19, Castle Drive, Penzance, Cornwall.**

BURGLARS

Safeguard your home, shop etc. from burglars and vandals with the best D.I.Y. equipment available. Send S.A.E. for comprehensive price list, or £6, for one of our fully weather-proofed steel Bell/Boxes the professionals use.

Lawrence, 81a New Road, Chippenham, Wiltshire.

"Don't buy in Kits, buy in bits".

SEEN MY CAT? 5000 Odds and ends. Mechanical, Electrical. Cat free. Whiston Dept. PRE, New Mills, Stockport.

PRACTICAL ELECTRONICS P.C.B.'s

Professional quality glassfibre, Fry's roller tinned and drilled.

For full list and current pcb's please send SAE. Pcb's also produced to customers own masters. Trade enquiries welcome. Please write for quote.

PROTO DESIGN

14 Downham Road, Ramsden Heath Billericay, Essex CM11 1PU
Telephone 0268-710722

RYDER ORGAN SYSTEM

The W.W. classical design for full-size keyboards, including couplers. Expanded range of units now includes chorus, vibrato, combination stop-control and a new reverb.

Data, p.c. boards, from:

HIYKON LTD. (P),

Woodside Croft, Ladybridge Lane, Bolton BL1 5ED.

UK 101 GAMES TAPE, 6 Different; Breakout, Pontoon, Torpedo, Air-Attack, Invader, Space-Station. All for £6 inclusive. G. C. Church (Software), 40 Begonia Close, Chelmsford, Essex.

P.C. BOARDS FOR INDUSTRY 'and' THE AMATEUR

- One off or production runs
- Assembly of P.C.B.s or kits
- Expert hand soldering
- Design service if required
- Artwork & Photography

SEAHORSE ELECTRONICS LTD.

Unit 2 Picow Farm Road
Service Industry Estate,
Runcorn, Cheshire.
(09285) 75950

SUPERB INSTRUMENT CASES BY BAZELLI. manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a Low £1.05. Chassis punching facilities at very competitive prices. 400 models to choose from. Suppliers only to Industry & The Trade. **BAZELLI (Dept. No. 23), St. Wilfrids, Foundry Lane, Halton, Lancaster, LA1 6LT.**

SOUNDEFFECTS & MUSIC

FOR UK101, PET, SUPERBOARD, NASCOM

Add phasers, explosions, music and other effects just like the professional arcade machines, to your own programs. Controlled by simple poke statements or if desired in machine code, this 3 channel synthesizer can produce almost any sound. Using stereo output and carefully designed hardware truly dynamic effects can be created using a minimum of processor time. The unit also includes 2 8-bit parallel I/O ports for control/monitoring applications.

Complete built and tested with demonstration program and instructions.

EX STOCK **£45** ALL INC.
Easicomp 0508 - 46484 Ltd.

57 Parana Court, Sprowston, Norwich.

ENTHUSIASTS!

We need you to ● ASSEMBLE P.C.B.'s
VERIFY PERFORMANCE

Materials supplied. Why not make your hobby pay?

BURGESS LANE & CO. LTD,
Thornton Works, Thornton Avenue,
London W4 1QE. 01-994 5752

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4

ENAMELLED COPPER WIRE

SWG	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
35 to 40	3.40	2.00	1.10	0.80
41 to 43	4.75	2.60	2.00	1.42
47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 30 6.50 3.75 2.20 1.40

TINNED COPPER WIRE

14 to 30 3.85 2.36 1.34 0.90

Prices include P&P, VAT and wire Data.
SAE for list. Dealer enquiries welcome.
Reg office 22 Coningsby Gardens.

Cabinet and Flightcase Fittings

Fretcloths, Coverings, Handles, Castors etc. Jacks and Sockets, Cannons, Bulgins, Reverb Trays, Emilia Compression Drivers, AKG Mics, Celestion Speakers, ASS, Glassfibre Horns.

Send 30p in stamps for illustrated catalogues to:-

ADAM HALL (P. E. SUPPLIES)

Unit G, Carlton Court, Grainger Road,
Southend-on-Sea, Essex SS2 5BZ.

MK14 CORNER. Interface Board, includes flag driven mains relays, LED Indicators for all Serial I/O, D/A and single step chips, and prototype area; also suitable for other Microcomputers; PCB and circuit £3.95. Replace calculator display with ½" FND 500's; PCB, filter, instructions £1.95. Ready Built replacement Keyboard £11. Useful notes on MK14 75p. Rayner, 'Kismet' High Street, Colnbrook, Bucks.

DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener, also one doz. assort. push pieces, full instructions and battery identification chart. We then supply replacement batteries—you fit them. Begin now. Send £9.00 for complete kit and get into a fast growing business. Prompt despatch.

BOLSTER INSTRUMENT CO. (PE15)

11 Percy Avenue, Ashford, Middx. TW15 2PB.

CLEARING LABORATORY: scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders, etc. 0403-76236.

Readily available Hardware and Accessories for Home Constructors, Dev. Engineers, Modelmakers. Selected range of quality components, Drawing materials for p.c. boards, Reliable resist coated epoxy glass laminate, no unusual chemicals. Printed circuit boards, top quality to personal designs, prompt service. Photography for p.c.b. Solid tungsten carbide drills

All immediately available.
Catalogue 15p stamps please to:

RAMAR CONSTRUCTOR SERVICES,

Masons Rd. Stratford on Avon
Warwks. CV37 9NF 0789-4879

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

GUITAR/PA/ MUSIC AMPLIFIERS

100 watt superb treble bass, overdrive, 12 months guarantee. Unbeatable at £48, 60 watt £39; 200 watt £65; 100 watt twin channel sep. treble/bass per channel £58; 60 watt £80; 200 watt £72; 100 watt four channel sep. treble/bass per channel £78; 200 watt £98; slaves 100 watt £34; 200 watt £50; fuzz boxes, great sound £10.00; bass fuzz £10.90; overdriver fuzz with treble and bass boosters £20.00; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable £98; twin channel £108; bass combo £105; speakers 15in. 100 watt £38; 12in. 100 watt £23; 60 watt £16; microphone Shure Unidyne B £26.

Send cheque or P.O. to:

WILLIAMSON AMPLIFICATION
62 Thorncliffe Avenue, Dukinfield, Cheshire.
Tel: 061-308 2064

DIGITAL WATCH BATTERIES, any sort 75p each. Send SAE or 15p with number old battery to Disclec, 511 Fulbridge Road, Werrington, Peterborough PE4 6SB.

UK 101 BASIC RENUMBERING PROGRAMME tape, listing and data for £4. Send cheque to: P. J. Barden, 517 Becontree Ave., Dagenham, Essex.

BURGLAR ALARM EQUIPMENT. Latest Discount Catalogue out now! Phone C.W.A.S. Alarm 0274 682674.

PRINTED CIRCUIT BOARDS. Glass Fibre tinned & Drilled, Proto types to batch runs. Quick turn-round, competitive prices. Send S.A.E. for quotations. R. D. Electronics, 12 Whiteoaks Road, Oadby, Leicester. 0533-716273.

SINCLAIR ZX80 (Unexpanded) Programs. Five for £2, on Cassette, or S.A.E. for details. Milner, 251 Henley Road, Coventry.

ULTRASONIC TRANSDUCERS. £2.85 per pair + 25p P&P. Datapuls Developments, 81 Cholmeley Road, Reading, Berks.

PRINTERS' 80-Columns Plain Paper. RS232 Centronics IEEE 20mA Interfaces £375 + VAT. Eproms 2708 £5.40p (+VAT) 2716 £21.60 (+VAT). Postage 35p. Software for most micros. Zero-One Electronics, 36 Oaklands Avenue, Thornton Heath, Surrey CR4 7PH.

CENTURION ALARMS

BURGLAR ALARM EQUIPMENT AT UNBEATABLE VALUE JUST LOOK!

Order No
100 ALARM TRIGGER MODULE, 100% Solid State. Battery operation, Pos & Neg Rings, N/C for 4-wire contacts, N/O for Mats etc. One Amp switching capacity. Only£9.95p
210 Quality White Flush fitting 4-wire MAGNETIC REED CONTACT + matching magnet£1.10p
220 Surface 4-wire MAGNETIC REED CONTACT£1.50p
240 PRESSURE MAT, Standard Size 4-wire 30" x 15"£2.20p
250 PRESSURE MAT, Stair Size 4-wire 23" x 6"£1.73p
280 VIBRATION DETECTOR, Pendulum Type in Ivory Case with contacted Lid + self-adhesive backing, Adjustable Sensitivity£3.50p
360 SIX INCH UNDER DOME BELL£9.95p
390 BEST QUALITY BELL HOUSING, P.V.C. coated Metal, not to be confused with cheaper decoy covers. Fully Sign Written with our Centurion In-signia£9.50p
400 DECOY P.V.C. BELL COVER£6.60p

Note: All Equipment Operates on 12 Volts DC

710 SCOOP Offer SMOKE ALARMS, Self-Contained Ionisation Type (15% obscuration) With Low Battery Warning at the UNREPEATABLE PRICE OF ONLY £8.75p White Stocks Last!!

Terms: Add 15% VAT to Prices + 40p Postage & Packing



No Minimum Order. Access telephone



Orders welcome on:
0484-35527 or Send
S.A.E. for Full List to

CENTURION ALARMS & ELECTRONIC SALES,
Dept. PE, 265 Wakefield Rd., Huddersfield,
W. Yorks, HD5 9BE.

TIME?

MSF CLOCK is ALWAYS CORRECT - never gains or loses, self setting at switch-on, 8 digits show Date, Hours, Minutes and Seconds, larger digit Hours and Minutes for easy QUICK GLANCE time, also second-in-a-month STOP CLOCK and parallel BCD output - for your computer, alarm etc. receives Rugby time signals, 1000Km range, now get ABSOLUTE TIME - always, £54.80.
60KHZ RUGBY RECEIVER, as in MSF Clock, serial data output, built-in antenna, £15.70.

Each fun-to-build kit includes all parts, printed circuit, case, postage etc, money back assurance so SEND off NOW.

CAMBRIDGE KITS

45 (FH) Old School Lane, Milton, Cambridge.

PLEASE
MENTION
PRACTICAL
ELECTRONICS

When
replying
to
Advertisements



£137.00*
**SAFGAN
ST-45**

SINGLE TRACE OSCILLOSCOPE
● 10mv/div ● 5MHz ● BRITISH
● ONE YEAR GUARANTEE ●
TRIGGER

Internal 0.5div (20Hz-2MHz), 1 div (2MHz-5MHz)
External 100mv (20Hz-2MHz), 200mv (2MHz-5MHz)
Bright Line Auto

Trace free runs in absence of signal
Trigger Level selects triggering point
Trigger (+)ive and (-)ive slope selection

FRONT PANEL
Black-Silver-White-ST-45-S The Silver Scope
or
Black-Gold-White-ST-45-G The Gold Scope

GENERAL
Blue display graticule ruled 8 x 10 div (6.4cm x 8cm)

Power consumption 10VA approx.
Mains selection 200V-220V-240V rms (40Hz-60Hz)

Size: H 215mm; W 165mm; D 280mm
Weight 10lbs 4.5kg approx.
Case aluminium with black pvc finish and black handle, scratch-resist front panel, black control knobs, black feet and tilt bar.

Safgan Electronics Ltd.,
56 Bishops Wood, St. Johns,
Woking, Surrey GU1 3QB

ST-45 SPECIFICATION VERTICAL SYSTEM

Sensitivity 10mv/div 5v/div in 9 cal. steps
Bandwidth (3uB)
DC Coupled DC 5MHz
AC Coupled 5Hz-5MHz
Risetime 70µsec
Input Impedance 1MΩ +22 PF approx. (for all ranges) 50Ω for 10mv/div 50mv/div
Input coupling AC/DC
Input volts: 400V max.
Accuracy ±5%

HORIZONTAL SYSTEM

Time base speeds
50ms/div 1µsec/div in 15 cal. steps with X5
Multiplier to 250msec/div and X5 Expansion to 200nsec/div
External - X sensitivity 1v/div
External - X Bandwidth 500KHz
Accuracy ±5%

ACCESSORIES

Passive Probe switched (X1, REF, x10)
100MHz bandwidth £11.50 + VAT
BNC to 4mm Socket Adaptor £2.95 + VAT

ORDERS TO: SAFGAN ELECTRONICS LTD.

56 Bishops Wood, St. Johns, Woking
Surrey GU21 3QB or Tel: Woking 66836.

Please send me.....ST-45-£.....ST-45-G.....Probe.....Adaptor

I enclose PO/Cheque.....(Goods + £3.00 p&p + 15% VAT)

Name.....

Address.....

*Ex VAT UK

PE

OFFER TO READERS OF THIS MAGAZINE


SYLVANIA PRODUCTS

From the world's most advanced electronics factory and due to "shipment error" this is your chance to purchase **NEW** the highly sophisticated "PRESIDENT MOONRAKER" at only £11.95 including VAT (suggested retail price £29.95) or five units at £10.95 each including VAT.

Electronic specialists are invited to examine this specification:

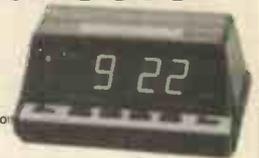- (1) Large bright 24mm digits.
- (2) Auto brightness control.
- (3) Displays month and date in addition to hours, minutes plus P.M. and Alarm "on" dots.
- (4) Total setting control, both forward and reverse on rocking switches - This is unique to our range.
- (5) Two separate alarm call positions.
- (6) Volume control loud/soft option.
- (7) Two sensor touch plates activating both the nine minute snooze and twentyfour hour off switch, plus a manual alarm off switch.
- (8) Exquisitely finished in very superior woodgrain and gilt trim - beautiful coloured unit box. Quantity discounts available in the United Kingdom only. Also many other offers available to the amateur and hobbyist.

PRESCOTT CLOCK & WATCH COMPANY LTD
Prescott House, Mumber Road, London NW2 6ER.
01-452 9871.



BUILD A SYNTHESISER! SPECIAL SKILLS SPECIAL EQUIPMENT REQUIRED



Using **Dewtron** (Reg'd)

PROFESSIONAL MODULES

Over 20 different electronic modules to select what YOU want to build a synthesiser, simple or complex. Start simple and add to it as you can afford. New attractive prices for the long-popular, well-tried range of Dewtron synthesiser and other effects modules. Also "Mister Bassman" Bass Pedal Units. Send 35p for Musical Miracles Catalogue NOW!

D.E.W. LTD.

254 RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AR.

CHROMASONIC electronics

56 FORTIS GREEN ROAD MUSWELL HILL LONDON N10 3HN
TELEPHONE 01-883 3705 01-883 2289

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS

PETS

2001-8N (8K RAM)
£449

2001-16N (16K RAM) **£549**
2001-32N (32K RAM) **£649**

ALL WITH NEW KEYBOARD AND GREEN SCREEN.

PERIPHERALS

Service & Assistance available.

Interfaces available are:

X-Y plotters, analogue to digital converter, 16 channel interfaces, bi-directional interfaces, etc.

EXTERNAL CASSETTE DECK SUITABLE FOR ALL PETS **£55**



UK101

£199 in kit form
£249 ready built & tested
£275 complete in case

ASSEMBLER
EDITOR
TAPE
£14.95

NO EXTRAS REQUIRED

- * FREE SAMPLER TAPE
- * FULL QWERTY KEYBOARD
- * 8K BASIC
- * RAM EXPANDABLE TO 8K ON BOARD (4K INC)
- * KANSAS CITY TAPE INTERFACE

* New monitor allows full editing & cursor control.

£22



LATEST STOP PRESS AND PRICE LIST

SEND SAE OR PHONE FOR UP TO DATE **PRICES** OF ALL OUR RANGE OF ITEMS STOCKED

CASES

Available for UK101, Superboard, NASCOM. Approx. dlm. 17" x 15" 435mm x 384mm

Price £24.50
Post and packing £1.50

TAPES

Unique stackable tape storage unit. Interlocking drawers. 5 drawers each containing 2 C12 tapes.

10 drawers **£9.50**
5 drawers **£5.25**
Single drawer **£1.10**

MEMORY EXPANSION KIT

Suitable for UK101, Superboard expansion using 2 114's. Each board has 16K RAM capacity.

Kit contains:

- * On board power supply
- * 4K EPROM expansion
- * Fully buffered for easy expansion via 40 pin socket

* **8K KIT £99.95**

* **16K KIT £139.90**



PRINTERS

TX-80 £395

EPSON TX-80 £395
Dot-matrix printer with Pet graphics Interface: Centronics parallel, options: PET, Apple and serial.

MEMORY

D. RAMS	£ p.
4027	2.75
4050 (350NS)	2.35
4060 (300NS)	2.39
4116	4.35

S. RAMS	
2102A	1.09
2102A-2	1.09
2112A	2.25
21L02	98
2114-4045	2.95
4035	1.07
4044-5257	6.93

BULK PURCHASE	
8. 2114	22.50
8. 4116	29.95
8. 21L02	7.00
BULK PURCHASE	
16 2114	39.95
16 21L02	13.00
32 21L02	25.00
64 21L02	45.00

EPROM'S

2708	4.95
2716 (5v)	13.95
2532	39.95

ROM'S

2513(UC)	5.95
2513(LC)	5.95

CPU'S

6502	9.50
8080	4.75
9900	25.95
6800	5.90
Z80	8.95

BUFFERS

81LS95	1.25
81LS96	1.25
81LS97	1.25
81LS98	1.25
SN74365	52
SN74366	52
SN74367	52
SN74368	52
8T26	1.75
8T28	1.75
8T95	1.57
8T96	1.57
8T97	1.50
8T98	1.57

BAUD RATE GENS

MC14411	8.75
MM5307	8.75

UARTS

AY-5-1013	3.45
AY-5-1015	3.98
MM5503	4.75
6011	3.55



PLEASE ADD VAT 15% TO ALL PRICES. POSTAGE ON COMPUTERS, PRINTERS & CASSETTE DECKS CHARGED AT COST. ALL OTHER ITEMS P&P 30p. PLACE YOUR ORDER USING YOUR ACCESS OR BARCLAYCARD (Min. Tel. order £5.00). TRADE & EXPORT ENQUIRIES WELCOME, CREDIT FACILITIES ARRANGED.



BAKER 50 WATT AMPLIFIER £69 Post £2



Superior quality ideal for Halls/PA systems, Discos and Groups. Two inputs with Mixer Volume Controls, Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available). Blue wording on black cabinet.

BAKER 150 Watt AMPLIFIER 4 Inputs £89

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains.

Printed circuit and components Post 50p £3.25

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £2.95

R.C.S. SOUND TO LIGHT DISPLAY MK 2

Complete kit of parts with R.C.S. printed circuit. Three channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi £18

250-0-250V 80mA. 6-3V 3A. 6-3V 1A £4.60
330-0-330V 200mA. 6-3V 3A+6-3V 2A+6-3V 2A £10.00
300-0-300V 120mA. 2x6-3V 2A C.T. 5V 2A £10.00
220V 45mA. 6-3V 2A £2.50

GENERAL PURPOSE LOW VOLTAGE.

Tapped outputs available
2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V £6.00
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £6.00
2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £9.50
3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £12.50
5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £16.00

6V, 500mA £2.00 6-0-6V, 100mA £1.50
12V, 100mA £2.50 20V, 40V, 60V, 1 amp £4.00
12V, 750mA £1.75 12V, 3 amp £3.50
10-0-10V 2 amp £3.00 10V, 30V, 40V, 2 amp £3.50
30V, 5 amp and 17V-0-17V 12V, 2 amp £3.25
2 amp £4.00 20V, 1 amp £3.00
0-5, 8, 10, 16V, 1 amp £2.50 20-0-20V, 1 amp £3.50
9V, 3 amp £3.50 10V, 0-10V, 2 amp £3.50
15-0-15V 2 amp £3.75 2 of 18V, 6 amp, each £11.00
30V, 2 amp £3.50 12-0-12V, 2 amp £3.50
30V, 1 amp £3.30 9V, 1 amp £1.50

AUTO TRANSFORMERS

115V to 230V to 115V 500MW £10.00

CHARGER TRANSFORMERS

6 and 12V 3 amp £6.50 4 amp £7.50

FULL WAVE BRIDGE CHARGERS RECTIFIERS.

6 or 12V outputs, 2 amp, 75p, 4 amp, £1.75

R.C.S. LOUDSPEAKER BARGAINS

3 ohm, 6x4in, £1.50, 7x4in, £1.50, 8x5in, £2.50, 6.4in, £2-20, 8in, £2.60, 10in, £3.50, 12in, £4.50, 14x9in, £1.90, 16x6in, £1.85, 12x3in, £1.20, 16x10in, £2.20, 12x8in, £1.70, 8x6in, £2.60, 10in, £3.50, 12in, £4.50, 16 ohm 6 x 4in, £1.50, 7 x 4in, £1.50, 8 x 5in, £1.50, 8in, £3.10in, £3.50, 12in, £4.50, 10 x 6in, £3.50.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS Post 50p £2-95

All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200-240 ac. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 24 x 1 1/2in. Please state voltage required.


THE "INSTANT" BULK TAPE ERASER

Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/249V. Leaflet S.A.E. £7.50 Post 50p



HEAD DEMAGNETISER PROBE £5-00

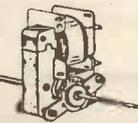A.C. ELECTRIC MOTORS POST 50p.
2 Pole, 240V, .2 Amp. Spindle - 1.43 x 0.212in. £1.75, 2 pole, 240V, .15 Amp. Double spindle - 1.75 x 0.16in. Each £1.50, 2 Pole, 120V, .5 Amp. Spindle - 0.75 x 0.2in. Two in series 240V, .75p each. Brush Motor. From a Food Mixer 240V, .3 Amp. High speed and Powerful. Spindle - 0.5 x 0.25in. £2.95



BLANK ALUMINIUM CHASSIS.

18 s.w.g. 2 1/2in. sides, 6 x 4in. 95p; 8 x 6in. £1.40; 10 x 7in. £1.45; 14 x 9in. £1.90; 16 x 6in. £1.85; 12 x 3in. £1.20; 16 x 10in. £2.20; 12 x 8in. £1.70.

ALUMINIUM PANELS.

18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p; 10 x 7in. 54p; 12 x 5in. 44p; 12 x 8in. 70p; 16 x 6in. 70p; 14 x 9in. 94p; 12 x 7in. £1; 16 x 10in. £1.16.

ALUMINIUM ANGLE BRACKETS

6 x 4 x 1/2 in. 25p.

ALUMINIUM BOXES, MANY SIZES IN STOCK

4 x 2 x 2in. 86p; 3 x 2 x 1in. 60p; 6 x 4 x 2in. £1; 8 x 6 x 3in. £1.90; 12 x 5 x 3in. £2.6 x 4 x 4in. £1.30; 10 x 7 x 3in. £2.20.

HIGH VOLTAGE ELECTROLYTICS

8/800V £1.20 50/500V £1.20 50+50/500V £1.80
16/500V £0.75 220/450V £0.95 40+80/500V £2.20
32/500V £0.75 16+32+32/500V £2.20

DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in., 10in., or 7in records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 1/2 x 11 1/2in. Above motor board 3 1/2in. Below motor board 2 1/2in. With CERAMIC STEREO CARTRIDGE £20 Post on All Decks £2.



BSR Single Player P207 cueing device, ceramic cartridge.

£15 Garrard Single Player 6-200 metal turntable, cueing device, aluminium arm. Stereo cartridge. £22

BSR, P182, Snake arm, flared Aluminium Turntable

ADC QLM30 Magnetic Cartridge. £30

B.S.R. Auto Changer. 11in. Turntable. Budget price.

£17-50

RSC Disco Deck 3 speed Stereo

£9.95 or £18 pair

Rapid Mail Order Service. Callers Welcome. Access - Visa. Lists 20p. Closed Wed.

Radio Components Specialists

337 WHITEHORSE ROAD

CROYDON, SURREY, U.K. TEL 01-684 1665

SCS Components

Halifax Road, Keighley, West Yorkshire BD21 5HR

All our products are guaranteed high quality components from leading Semiconductor Manufacturers.

CMOS	4055	1.23	LINEAR	CA555CG	.20	SWITCHES	
4000	.19	4056	1.23	CA741CG	.38	Toggle	
4001	.26	4059	4.45			8295K7 - 3 amp SPST	.98
4002	.22	4060	1.10			7321K3 - 6 amp SPST	.85
4006	.86	4063	1.05			8810K6 - 10 amp SPDT	1.14
4007	.26	4066	.48			8327K8 - 3 amp DPST	.82
4008	.78	4067	3.60	DIDDIES		7320K3 - 6 amp DPST	.82
4009	.40	4068	.22	IN4001	.05	8824K5 - 10 amp DPST	1.66
4010	.40	4069	.26	IN4002	.05		
4011	.26	4070	.33	IN4003	.06	Miniature Toggle	
4012	.22	4071	.24	IN4005	.06	E2012 - 3 amp SPDT	.59
4013	.40	4072	.24	IN4008	.07	E2022 - 3 amp DPDT	.74
4014	.78	4073	.24	IN4007	.07	Slide Switches	
4015	.78	4075	.21			SM1-1 - 1 amp SP on/off	.23
4016	.40	4076	.93	ZENERS		SM2-2 - 1 amp DPST	.31
4017	.74	4077	.30	BZY88 3.3V to 30V		SM2-3 - 1 amp DPDT	.61
4018	.78	4078	.22	400mW	.07 each		
4019	.40	4081	.22			LED's	
4020	.92	4082	.22			MAN3640 - 7.6mm Orange	1.70
4021	.98	4085	.75	RESISTORS		MAN6660 - 14.2mm Orange	2.00
4022	.87	4086	.75	5% carbon film resistors. High stability, low noise 1/4W E24 range of values 1R-1M. .07 for 5 pieces 1 value only.		MV52 - 2.3mm Green	1.00
4023	.22	4089	1.40			MV53 - 2.3mm Yellow	.21
4024	.66	4093	.68	TRANSISTORS		MV5021 - 4.7mm Red	.20
4025	.20	4094	1.70	ZTX107	.09	MV5054/1 - 5mm Red	.15
4026	1.56	4095	.95	ZTX108	.09	MV5054/2 - 5mm Red	.17
4027	.40	4096	.95	ZTX109	.09	MV5054/3 - 5mm Red	.10
4028	.72	4097	3.18	ZTX300	.10	MV50748 - 3mm Red	.43
4029	1.04	4098	1.05	ZTX310	.10	MV52124 - Rectangular Green	.44
4030	.45	4099	1.25	ZTX300	.10	MV52124 - Rectangular Yellow	.44
4031	2.08	4502	.97	ZTX310	.10	MV5124A - Rectangular Red	.44
4032	1.10	4508	2.35	ZTX320	.11		
4033	1.37	4510	.87	ZTX330	.11		
4034	1.99	4511	.87	ZTX330	.11		
4035	.92	4512	.85	ZTX330	.11		
4037	.96	4514	2.21	ZTX450	.12		
4038	1.03	4515	2.21	ZTX500	.12		
4040	.98	4516	.97	ZTX502	.12		
4041	.77	4517	3.55	ZTX502	.12		
4042	.69	4518	.97	ZTX504	.12		
4043	.84	4520	.97	ZTX504	.12		
4044	.84	4527	1.37	ZTX750	.12		
4045	1.27	4532	1.07				
4046	1.09	4556	.59	DIL SOCKETS			
4047	.82	4585	1.02	8P	.09		
4048	.50	40106	.65	14P	.11		
4049	.40	40180	.74	16P	.13		
4050	.45	40161	.74	18P	.15		
4051	.70	40162	.74	20P	.17		
4052	.70	40163	.74	22P	.18		
4053	.70	40174	.74	24P	.20		
4054	1.05	40194	.93	28P	.25		
				40P	.35		

Cash/Cheques/P.O.'s with order. P & P add 30p to all orders. Add 15% VAT to total order. All items ex. stock - orders by return post.

Codespeed Electronics

P.O. BOX 23, 34 SEAFIELD ROAD, COPNOR, PORTSMOUTH, HANTS., PO3 5BJ

GIANT 0.8" LED clock display, common cathode, non-multiplexed. With data £3.95 each. **ALARM** clock module with 0.7" LED display. With data £5.99 each. **LIQUID** crystal clock display, 0.5" digits. With data and FREE socket, £5.25 each. **FLOURESCENT** reject calculators. Modern, 10 function with full memory. Most repairable but no g 'teers. £2.99 each. **TEN**, transistors I.F. transformers. All brand new. May include several types, 55p for 10. **CLOCK CHIP** MM5316 I.C. (has alarm output). Brand new, with data £2.35 each. **POLARIZING** filter, plastic, 0.006" thick. Any size cut from 1 sq. in. to max. size 19" x 250 feet. 3p per sq. inch. **MOMENTARY** (push to 'make') switch. Red cap. 15p each. **SLIDE** switch, 2 pole c.o. 16p each. **TWO** calculator keyboards (not compatible with 4204 calc. chip). 99p the pair. **MULTIMETER CHIP**, MM5330 I.C. to build 4 1/2 digit d.m.m. (needs additional circuitry). With data £3.55 each. **KNOBS** Slider control knobs, fits 5 or 8mm shafts. State colour 14p each. Rotary control knobs, black (18mm diam) with coloured cap, state colour required. 20p each. Skirted rotary knob, same as rotary control knob above but has 'flared' skirt around base. State cap colour required. 27p each. Colours available, black, red, green, blue, yellow, grey, white. 8 DIGIT common cathode calculator display, 0.1", multiplexed, with data, 99p each. **LED WRISTWATCH CHIP** with data, 95p each. **LED WRISTWATCH DISPLAY** matches above watch chip. With data, 95p each. **NOTE** the wristwatch chip and display are housed in 'legless flatpack' style and require some fairly fine soldering. **QUALITY** jack sockets, mono 25p each, stereo 30p each. **LM555** timer i.c. with applications booklet. 25p each. **MEMORIES** 2102 static RAM, with data, 99p each. **NORTEC** 4204, 4 function calc. chip. With data, 80p each. **UNTESTED** 0.1" LED displays. 10 single digit displays for 92p. 'U' to test.

POST AND PACKING PLEASE ADD 40p (Overseas Orders Add £1)
For your FREE copy of our latest catalogue please send MEDIUM size SAE
V.A.T. ADD 15% TO TOTAL COST (Including Post and Packing).
CASH BACK! Satisfaction Guarantee on all items.

MICROPROCESSORS FOR HOBBYISTS

by R. Coles Price: £3.30

DISCOVER DATA COMMUNICATIONS

by B. Warrington Price: £5.00

110 IC TIMER PROJECTS FOR THE HOME CONSTRUCTOR

by J. H. Gilder Price: £4.50

THE OSCILLOSCOPE IN USE

by I. R. Sinclair Price: £3.00

COLOUR T.V. WITH PARTICULAR REF. TO THE PAL SYSTEM

by G. N. Patchett Price: £6.00

TELETEXT & VIEWDATA

by S. A. Money Price: £6.00

PROGRAMMING THE Z80

by R. Zaks Price: £9.70

WORLD RADIO TV HANDBOOK

Price: £9.50

CB BIBLE THE COMPLETE GUIDE TO CITIZENS BAND 2-WAY RADIO

Price: £4.25

1980 THE RADIO AMATEUR'S H/B

by A.R.R.L. Price: £8.00

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-402 9176

Closed Saturday 1 p.m.

INDEX TO ADVERTISERS

Acorn Computers	9
Adam Hall (P.E. Supplies)	83
Aitken Bros	80
Aura	20
Barrie Electronics	4
B. Bamber	3
Bi-Pak	71
Blrktett J.	8
Bolster Instruments Co.	83
British National Radio & Electronics School	11
Burgess Lane & Co. Ltd.	83
Cambridge Kits	84
Cambridge Learning	78
Centurion Alarms & Electronics	84
Chromasonic Electronics	85
Chromatronics	72
Clef Products	81
Codespeed	86
Colour Print Express	
Computer Components (Teleplay)	Cover II
Continental Spec.	Cover III
Crofton Electronics	80
C.R. Supply Co.	82
David George Sales	58
Dewtron	84
Display Electronics	76
Doram	8
Easicomp Ltd.	83
E.D.A.	58
Electrovalue	8
Fladar	79
Fairline Supplies	83
Hiykon Ltd.	83
Home Radio	81
I.C.S. Intertext	7, 82
I.L.P. Electronics	74, 75, 81
Jayan Developments	79
Keelmoor	13
Lascar	12
Lawrence	83
L.B. Electronics	80
Maplin Electronics	Cover IV, 32
Marshall, A.	10, 12
Metac	73
Micro Circuits	5
Modern Book Co.	86
Modus Systems	76
Mullard	34
Phonosonics	6, 7
PKG Electronics	83
Prescott Clocks	84
Progressive Radio	80
Proto Design	83
Radio Component Specialists	86
Radio & T.V. Components	16
Ramar Constructor Services	83
Safgan	84
Sandwell Plant Ltd.	83
Saxon Entertainments	4, 72
Science of Cambridge	14, 15
Scientific Wire Co.	83
Seahorse Electronics	83
Service Trading	77
Semi-Comp Northern	86
Sentinel Supply	32
Sloan Electronic Equipment	82
Swanley Electronics	78
Telgrado	81
Tempus	87
T.K. Electronics	10
Technomatic	88
Toolrange	79
Transam Components	28
T.U.A.C.	32
Watford Electronics	2, 3
Wicca Electronics	72
Williamson Amplification	84
Wilmslow Audio	78

THIS MONTH'S STAR BUYS

F-300
SPORTS WATCH



ONLY £12.95

110QS-37B
CHRONOGRAPH



ONLY £17.95

C-801
CALCULATOR WATCH



ONLY £29.95

Hours, minutes, seconds, am/pm, day and date. Automatic calendar. 1/100 second chronograph to 12 hours; net lap and 1st and 2nd place times. Backlight. 2 year lithium battery. Water resistant case. Mineral glass face. F-300. Resin case, s/s trim. (RRP £14.95). 110QS-37B. Chromed case, s/s bracelet. (£19.95).

WATCHES

F-8C (Resin) now only **£8.95**
111QS-35B Comprehensive display **£14.95**

Chronographs

95QS-36B 1/100 second, 12 or 24 hour. Dual time. Solid s/s case **£19.95**

Alarm chronographs with hourly chimes

83QS-41B 1/10 second. Comprehensive display. S/s jacket **£24.95**

83QGS-41B Gold plated **£29.95**

81QS-40B 1/100 second. 12 or 24 hour. Chrome plated case **£24.95**

81QS-35B Solid s/s **£29.95**

81QGS-35B Gold plated **£34.95**

79QS-39B 8 digits. Universal calendar. Chrome plated **£29.95**

Many other CASIO watches available from stock. Ladies models from **£12.95**.

Calculators

FX-7100 **£24.95**. FX-8100 **£24.95**.

MC-34 **£11.95**. HR-10 **£29.95**.

MELODY 90 (ML-90)

Clock, hourly chimes, calendar to 1999. Alarm 1:- 7 different melodies changing daily, a fixed melody or buzzer. Alarm 2:- a fixed melody or buzzer. Date memory 1:- "Happy Birthday". Date memory 2:- "Wedding March" or "Drinking Song". On December 24/25 plays "Jingle Bells". Calculator with 11-note keyboard, full access memory, square roots, $\%$, $7/32 \times 24 \times 44$ inches. Wallet. 1 year batteries.

ONLY £19.95

SUMMERTIME SPECIAL OFFERS

FREE on request

With any purchase made from this section before September 30th 1980 **GENTLEMAN'S DIGITAL WATCH** with comprehensive display and long life battery from world famous manufacturer. Value around **£12**. An ideal working watch for you or a present for someone else.

Offers subject to availability.

Chronograph watches

95QS-42B. 1/100 second. 12 or 24 hour. Dual time. **£17.95**

S/s encased **£24.95**

56QS-38B. Analogue/digital **£24.95**

C-80. Calculator, dual time **£24.95**

Clock calculators

PW-81 **£14.95**. AQ-1500 **£14.95**. AQ-2200 **£19.95**.

ML-71 **£22.95**. ML-81 **£22.95**. ML-82 **£19.95**.

Scientific calculators

FX-510 **£19.95**. FX-3200 **£21.95**.

FREE on request

With any purchase made from this section before September 30th 1980. **GENTS DIGITAL WATCH**, around **£17**, or **LADIES DIGITAL WATCH**, around **£15**, or **CALCULATOR/CLOCK**, around **£17**.

Offers subject to availability.

Watches

56QS-50B. Analogue/digital **£34.95**

79CS-51B. Alarm chrono with universal calendar, chimes, s/s case **£39.95**

59CS-33B. Alarm, slim dress **£44.95**

Calculator

FX-8000. Stopwatch, 2 countdown alarms. Full scientific **£31.95**

SEIKO. Latest water resistant alarm chronographs from **£49.95**. Other models from **£39.95**. New analogue/alarm **£69.95**.

RETURN OF POST SERVICE (subject to availability).

Send 25p for our illustrated catalogue of Casio and Seiko products.

Price includes VAT, P&P. Send cheques, PO or phone your Access or Barclaycard number to:

TEMPUS

Tempus (Dept. PE)
FREEPOST, 164-167 East Road
Cambridge CB1 1BR. Tel. 0223 312866

COMPUKIT UK101 EUROPE'S FASTEST SELLING ONE BOARD COMPUTER

SPACE INVADERS PROG. £5 + VAT



★ 6502 based system — best value for money on the market.
 ★ Powerful 8K Basic — Fastest around ★ Full Qwerty Keyboard ★ 4K RAM Expandable to 8K on board. ★ Power supply and RF Modulator on board. ★ No Extras needed — Plug-in and go. ★ Kansas City Tape Interface on board. ★ Free Sampler Tape including powerful Dissassembler and Monitor with each Kit. ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

Build, Understand and Program your own Computer for only a small outlay.

KIT ONLY £199 + VAT NO EXTRAS NEEDED

AVAILABLE READY ASSEMBLED & TESTED READY TO GO FOR £249 + VAT

Specialy designed case for CompuKit in orange/black. With room for accessories. **£29.50 + VAT**

6502 Assembler/Editor for CompuKit £14.90 + VAT

The **CompuKit UK101** comes in kit form with all the parts necessary to be up and working, supplied. No extras are needed. After plugging in just press the reset keys and the whole world of computing is at your fingertips. Should you wish to work in the machine code of the 6502 then just press the M key and the machine will be ready to execute your commands and programs. By pressing the C key the world of Basic is open to you.

This machine is ideal to the computing student or Maths student, ideal to teach your children arithmetic, and is also great fun to use.

Because of the enormous volume of users of this kit we are able to offer a **new reduced price of £199 + VAT**

NEW MONITOR FOR COMPUKIT UK101 • In 2K Eprom 2716
 • Allows screen editing • Saves data on tape
 • Flashing cursor • Text scrolls down **£22.00 + VAT**

- 8MHz Super Quality Modulators **£4.90**
- 6MHz Standard Modulators **£2.90**
- C12 Computer Grade Cassettes 10 for **£4.00**
- Super Multi-rail P.S.U. +5 -5 +12v **£29.50**
- Anadex Printer Paper - 2000 sheets **£25.00**

NASCOM-2 MICRO-COMPUTER

only **£305 + VAT**

With **FREE 16K RAM Board Type B**

Your choice of freebies with every Nascom 2 purchased from us
 either **FREE POWER SUPPLY**
 OR **FREE GRAPHICS ROM**
 OR **FREE VERO CASE TO TAKE NASCOM 2**

Microprocessors Z80A 8 bit CPU. This will run at 4MHz but is selectable between 1/2/4 MHz. This CPU has now been generally accepted as the most powerful, 8-bit processor on the market.

INTERFACE
Keyboard New expanded 57 key Licon solid state keyboard especially built for Nascom. Uses standard Nascom, monitor controlled, decoding.

T.V. The tv peak to peak video signal can drive a monitor directly and is also fed to the on-board modulator to drive the domestic T.V.

I.O. On-board UART (Int.6402) which provides serial handling for the on-board cassette interface or the RS232/20mA teletype Interface.

The cassette interface is Kansas City standard at either 300 or 1200 baud. This is a link option on the NASCOM-2. The RS232 and 20mA loop connector will interface directly into any standard teletype.

The input and output sides of the UART are independently switchable between any of the options — i.e. it is possible to house input on the cassette and output on the printer.

PIO There is also a totally uncommitted Parallel I/O (MK3881) giving 16, programmable, I/O lines. These are addressable as 2 x 8 bit ports with complete handshake controls.

Documentation Full construction article is provided for those who buy a kit and an extensive software manual is provided for the monitor and Basic.

Basic The Nascom 2 contains a full 8K Microsoft Basic in one ROM chip with additional features like DEEK, DOKE, SET, RESET for simple programming.

only **£356 + VAT**

TRS80/LEVEL 2 16K

Fully converted to UK T.V. Standard. Comes complete with easy to follow manuals. UK Power Supply — Cassette Leads — Sample tapes. Special box to enable you to plug into your own TV. Recommended for first time-buyers. Just plug in and go. Full Range of Software Available

NEW REDUCED PRICES

8K **£449**
 16K **£549**
 32K **£649**

RRP £795 for 32K

The PEDIGREE PETS

Very popular for home & business use. 8K Microsoft Basic in ROM. 8K Pet 32K & 16K with new improved keyboard. All with green screen. Extra cassette deck **£55** Full range of software available.

THE ATARI VIDEO COMPUTER SYSTEM

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty great Game Program™ cartridge!

Have fun while you sharpen your mental and physical coordination. You can play rousing, challenging, sophisticated video games, the games that made Atari famous. You'll have thrill after thrill, whether you're in the thick of a dogfight, screeching around a racetrack, or dodging asteroids in an alien galaxy. With crisp bright colour (on colour TV) and incredible, true-to-life sound effects. With special circuits to protect your TV.

Cartridges now available All at **£13.90** each + VAT

Basic maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score*, Space War, Sky Diver, Air Sea Battle Codebreaker*, Miniature Golf.

SPACE INVADERS CARTRIDGE £27.00 + VAT Ex-Stock

Extra Paddle Controllers — **£14.90 + VAT** *Keyboard Controllers — **£16.90 + VAT**

NEW TV GAME BREAK OUT

Has got to be one of the world's greatest TV games. You really get hooked. As featured in ETI. Has also 4 other pinball games and lots of options. Good kit for up-grading old amusement games.

MINI KIT — PCB, sound & vision modulator, memory chip and de-code chip. Very simple to construct. **£14.90 + VAT**
OR PCB £2.90 MAIN LSI £8.50 Both plus VAT

video 100

12" BLACK & WHITE LOW COST VIDEO MONITOR

RRP £79

only **£69 + VAT**

- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Composite video input
- Compatible with many computer systems
- Solid-state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz + 3dB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum In Central 80% of CRT; 550 Lines Minimum beyond central 80%.

"Europe's Largest Discount Personal Computer Store"

Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to **COMP SHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS** number. **CREDIT FACILITIES ARRANGED** — send S.A.E. for application form.

14 Station Road, New Barnet, Hertfordshire, EN5 1QW Telex: 298755 TELCOM G
 Telephone: 01-441 2922 (Sales) 01-449 6596
OPEN - 10 am - 7 pm — Monday to Saturday
 Close to New Barnet BR Station — Moorgate Line.
 ★ **NOW in IRELAND** at: 80 Marlborough St., Dublin 1. Tel: Dublin 749933

COMP COMPUTER COMPONENTS
 (Part of the Compshop Ltd. Group)

STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

Send the coupon for your copy
and **STEP UP TO
MAPLIN SERVICE
NOW**



Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME _____

ADDRESS _____



PE880

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-

P.O. Box 3, Rayleigh, Essex SS6 8LR.

Telephone: Southend (0702) 554155.

Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).

Telephone: Southend (0702) 554000.

Catalogue now available in all branches of WHSMITH  Price £1.00