


PRACTICAL

ELECTRONICS

JUNE 1984


90p

HYPERCHASER

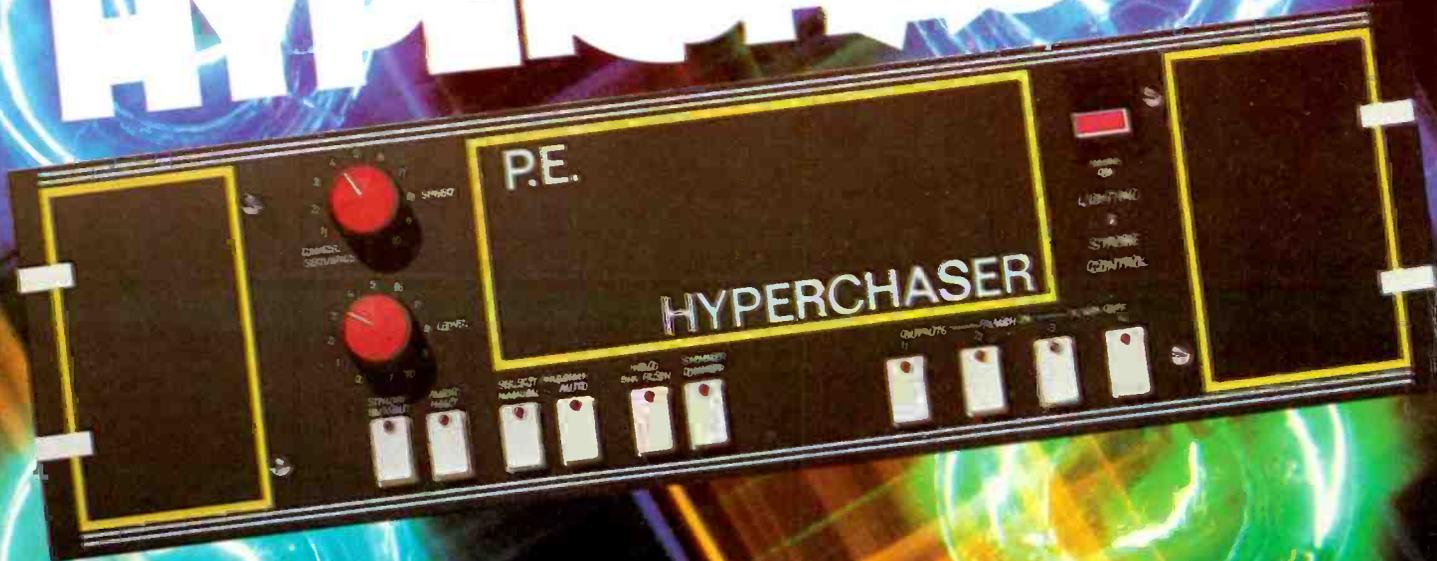

**TEST GEAR
BUYERS GUIDE**
OSCILLOSCOPES · PSU's
FUNCTION GENERATORS

FREE! LOGIC DESIGN CARD N°4

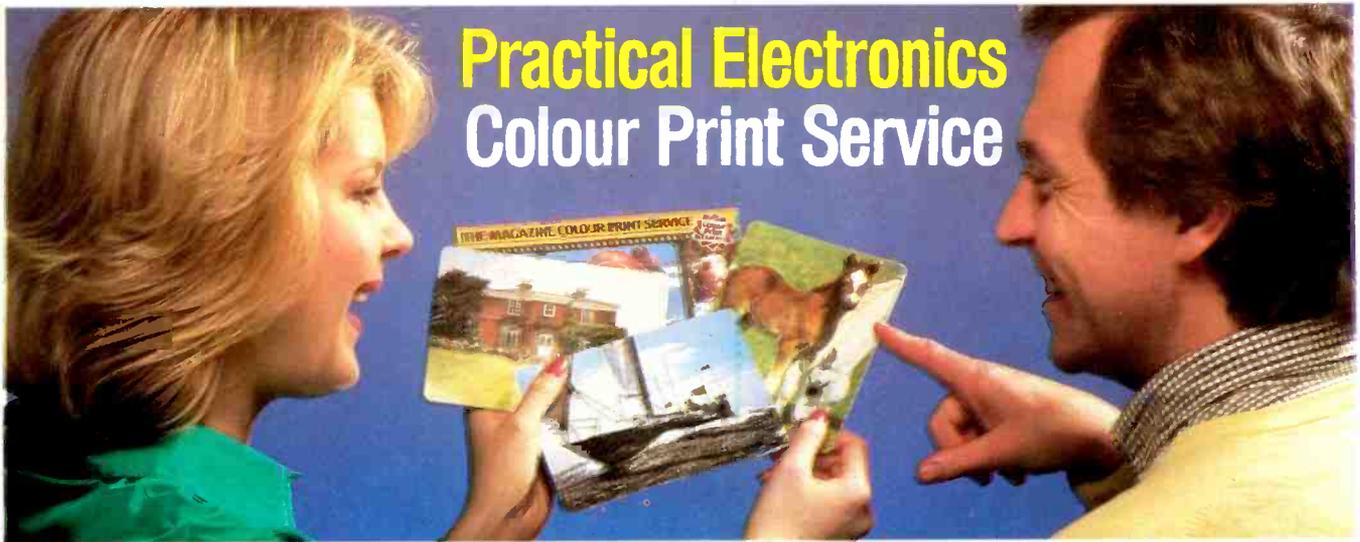

Practical Electronics Colour Print Service

What better way of ensuring your pleasure than to actually see your prints before you pay—and then to be charged only for the successful pictures within the price ranges quoted. That is the deal you get from our colour print service providing the best all-round value for money available.

Over the past ten years, hundreds of thousands of magazine readers have been delighted with our postal service. They have sent their films in to us again and again. So why not give it a whirl yourself?

QUALITY

Every print is checked at every stage of processing to ensure accurate colour reproduction.

RELIABILITY

Processing and printing take up to 48 hours. Allowing for postal or peak-period delays, you should normally expect your prints after seven to ten days.

LARGER PRINTS

Our Superprints give you 30 per cent more picture area at *no extra charge*.

EASY CREDIT

You pay only for your successful shots within the price ranges quoted—and then only *after* you have seen the prints.

FREE FILM

When you order a replacement film, we send you a second film free.

COMPARE PRICES

If you are invoiced for £2.70, plus 30p postage and packing per film, that could be for as many as 24 successful prints.

See your prints before you pay

See our price range:

No. of Superprints or standard prints	Price (inc. 15% VAT)
0-6	£1.20
7-12	£1.70
13-18	£2.20
19-24	£2.70
25-30	£3.20
31-36	£3.70

LUXURY COLOUR PRINTS

You will be amazed at the beautiful colours and sheen finish of your prints. They have elegant rounded corners and are borderless to give you maximum picture area. Choose either standard prints or the larger Superprints by ticking the appropriate box on the enclosed envelope or on the coupon below.

Superprints Print size (approx.)

35mm	110	126	Disc
4" x 5 3/4"	4" x 5 1/8"	4" x 4"	4" x 5 1/8"

Standard prints Print size (approx.)

3 1/2" x 5"	3 1/2" x 4 1/2"	3 1/2" x 3 1/2"	N/A
-------------	-----------------	-----------------	-----

NO MONEY—NO STAMP

Just send any good make of colour print film, including disc film, inside the Freepost envelope enclosed with this

issue. Or fill in the coupon below and send with your colour print film in a strong envelope to: Practical Electronics Colour Print Service, FREEPOST, Reading, RG1 1BR.

PERSONALISED SERVICE

Our valued readers know we care for their prints. If you have any queries about this highly-personalised service, contact Customer Service, Kenavon Drive, Reading, RG1 3HT, or ring Reading (0734) 597332.

YOU BENEFIT IN FOUR WAYS

1. Processing is free—you pay only for successful prints (plus p & p).
2. You enjoy a highly personalised service with every care taken over each individual print.
3. You are not hampered with credit vouchers.
4. You get more prints for your money, so it is worth your while always having your camera action-ready. Compare the shop prices.

FREE COLOURPRINT FILM OFFER

For every 110, 126, 135 (all 24 exp, ASA100) film you order from this Colour Print Service at our specially reduced price of £1.20, you receive *in addition* a FREE high-quality Colourprint film specially packed by one of the world's leading manufacturers. Offer excludes Black & White, transparency, sub-miniature, C22 & Agfa CNS film. Superprints can be produced only from Kodacolor II, C41 cassette, cartridge and disc film, not half frame. Prices are correct at the time of going to press and are for UK readers only. Standard terms of business are available on request.



USE THIS LABEL IF YOU HAVE NO ENVELOPE, OR PASS IT TO A FRIEND. IT IS USED TO SEND YOUR PRINTS.

To: Practical Electronics Colour Print Service, FREEPOST, Reading, RG1 1BR.

● Print my enclosed film (Please tick box)

Superprint size
Standard size

● Rush me _____ of 35/24 _____ of 110/24 _____ of 126/24 at £1.20 each together with one FREE film for each film ordered.

From: Practical Electronics Colour Print Service, FREEPOST, Reading, RG1 1BR.

Name _____

Address _____

Postcode _____

PRACTICAL ELECTRONICS

VOLUME 20

No. 6

JUNE 1984

CONSTRUCTIONAL PROJECTS

HYPERCHASER <i>By P. Newbury</i>	24
Disco lights sequencer	
CROSS HATCH GENERATOR <i>by R. A. Penfold</i>	48
Aid to TV servicing	
CONTINUITY CHECKER <i>by Chris Lare</i>	52
Test unit for low values of resistance	
SPOT FREQUENCY OSCILLATOR <i>by Tom Gaskell BA(Hons) AMIEE</i>	60
'Quick check' instrument for simple audio systems	

GENERAL FEATURES

TEST INSTRUMENTS—BUYER'S GUIDE	14
Our guide to test instruments	
INGENUITY UNLIMITED	34
Audible reversing alarm—Scalectrix motor control	
SPOT-PRICING <i>by T. W. Berrie</i>	35
Interactive consumer/supplier energy tariff system	
INTRODUCTION TO DIGITAL ELECTRONICS <i>by M. Tooley BA and D. Whitfield MA MSc CEng MIEE</i>	38
A look at CMOS technology	
VERNON TRENT AT LARGE	47
MICRO-BUS	56
Our monthly focus on micro's for the home constructor	
SEMICONDUCTOR CIRCUITS <i>by Tom Gaskell BA(Hons) AMIEE</i>	58
Touch Tuners (SAS580 and SAS590)	

NEWS AND COMMENT

EDITORIAL	11
NEWS AND MARKET PLACE	12
Including Countdown and Points Arising	
INDUSTRY NOTEBOOK <i>by Nexus</i>	23
News and views on the electronics industry	
SPACEWATCH <i>by Frank W. Hyde</i>	33
An Obituary	
BAZAAR	44, 51
Free readers' advertisements	

SPECIAL SUPPLEMENT

MICRO-FILE <i>by R. W. Coles</i>	between pages 34 and 35
Filesheet 16 NS 16032	


OUR JULY ISSUE WILL BE ON SALE FRIDAY, JUNE 1st, 1984
(for details of contents see page 16/6 of Micro-file)

© IPC Magazines Limited 1984. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Heathkit - IT'S A PLEASURE TO BUILD

Bring the enjoyment back into your hobby with a kit from Heathkit. The beautifully illustrated documentation and step-by-step instructions make building a Heathkit a relaxing, absorbing pleasure! Choose from their huge range of fascinating kits and self-instruction electronics and computing courses.

The Heathkit range includes the ultimate in amateur radio kits, computerised weather stations, a highly sophisticated robot, a 16-bit computer kit and a range of home (or classroom) learning courses. These state-of-the-art courses have easy-to-understand texts and illustrations, divided into sections so that you can progress at your own pace, whilst the hands-on experiments ensure long-term retention of the material covered.

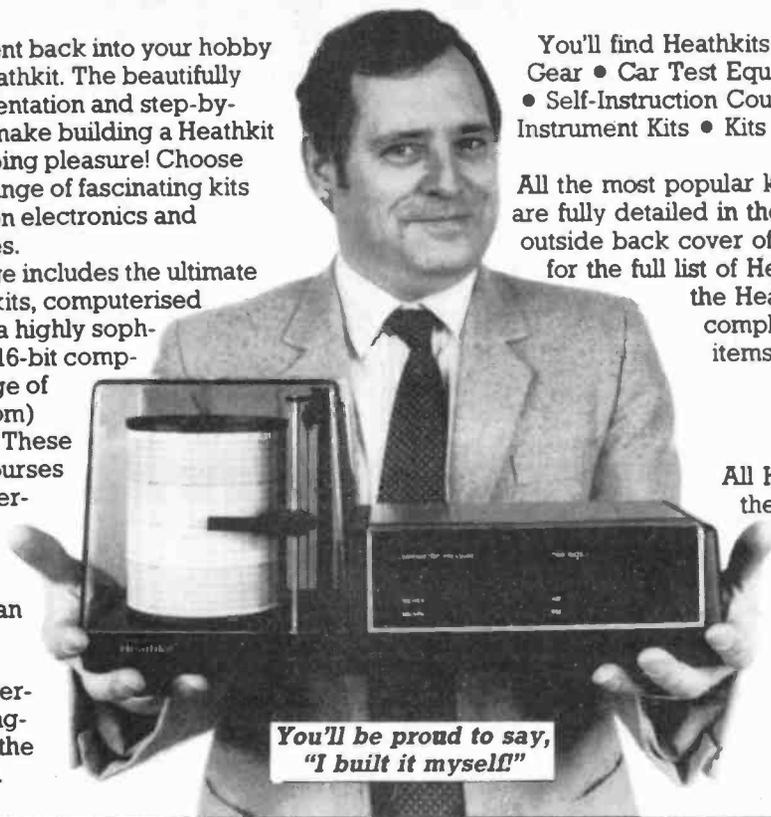

*You'll be proud to say,
"I built it myself!"*

You'll find Heathkits available for Amateur Radio Gear • Car Test Equipment • Kits For The Home • Self-Instruction Courses • Computer Kits • Test Instrument Kits • Kits For Weather Measurements.

All the most popular kits and educational products are fully detailed in the 1984 Maplin catalogue (see outside back cover of this magazine for details) or for the full list of Heathkit products send 50p for the Heathkit International Catalogue complete with a UK price list of all items.

All Heathkit products available in the UK from:

Maplin Electronic Supplies Ltd.
P.O. Box 3, Rayleigh,
Essex, SS6 8LR.
Tel: (0702) 552911.

(For shop addresses see back cover.)

MASTER ELECTRONICS NOW! The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY
THIS IS THE AGE OF ELECTRONICS!
the world's fastest growth industry...

Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer. All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.



British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE!
COLOUR
BROCHURE

Please send your brochure without any obligation to

I am Interested In:

NAME _____

ADDRESS _____

PE/6/842

BLOCK CAPS PLEASE

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS
please state below

Post now to:

British National Radio & Electronics School Reading, Berks. RG1 1BR



OR TELEPHONE US
0734 51516 OR
TELEX 22758
(24 HR SERVICE)

HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w of lighting

- TDR300K Remote Control Dimmer £14.95
- MK6 Transmitter for above £4.50
- TD300K Touchdimmer £7.75
- TS300K Touchswitch £7.75
- TD6K Extension kit for 2-way switching for TD300K £2.50
- LD300K Rotary Controlled Dimmer £3.95



MINI KITS


- MK1 ELECTRONIC THERMOSTAT Uses LM3911 IC to sense temperature (80°C max) and track to switch heater (1KW). Mains powered. £4.89
- MK2 SOLID STATE RELAY Switches 240V ac motors, lights, heaters from logic/computer circuits. Zero voltage switching, opto-isolated. Supplied without track. £2.60
- MK3 PROPORTIONAL TEMPERATURE CONTROLLER Uses "burst fire" technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wire making, etc. Max. load 3KW (240V ac). Temp. range up to 90°C. £6.30
- MKS MAINS TIMER Mains powered timer enabling a load up to 1KW at 240V ac to be switched on (or off) for a variable time from 20 mins to 35 hrs. Longer or shorter periods possible with minor component changes. £6.50
- MK15 DUAL LATCHED SOLID STATE RELAY Comprises two MK2's with latch circuit enabling the MK12 kit to control two mains loads independently. Two output tracks not supplied. (See remote control kits.) £4.50

NEW! MK15 DC CONTROLLED AUDIO AMPLIFIER

May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK13 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) £10.70

MICROPROCESSOR CONTROLLED MULTI-PURPOSE TIMER

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a 7 day cycle, e.g. to control your central heating including different switching times for weekends, just connect it to your system programme and set it and forget it — the clock will do the rest.

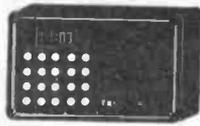

NOW ONLY £39.00

- 7mm LED 12 hour display
- Day of week, am/pm and output status indicators
- 4 open collector outputs for driving relays, tracks, etc.
- 50/60Hz mains operation
- Battery backup saves store-programmes and continues time-keeping during power failures. (Battery not supplied).
- Display blanking during power failure to conserve battery power.
- 18 programme time sets
- Powerful "Evervital" function enabling output to switch every day but use only one time set
- Useful "sleep" function turns on output for one hour
- Direct switch control enabling output to be turned on immediately or after a specified time interval
- 20 function keypad for programme entry

- Programme verification at the touch of 5 buttons
 - Plastic box with attractive screen printed front panel 15 x 10 x 8.5cm
- Kit includes all components PCB, box, assembly and programming instructions. Order as CT16000
- XR114 OPTIONAL RELAY KIT**
Kit includes one relay PCB to accommodate up to 4 relays, terminal blocks, etc. to fit inside CT16000 box. Provides up to 4 3amp 240V AC changeover contacts. £3.90
- Additional Relays £1.65 each

DISCO LIGHTING KITS

- DL 1000K This value for money kit features a bidirectional sequenced speed of rotation, adjustable frequency of direction change being variable by means of potentiometers and incorporating a master dimming control. £15.95
- DLZ 1000K A lower cost version of the above featuring unidirectional channel sequenced speed of rotation, adjustable frequency of direction change being variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to avoid radio interference to a minimum. £8.95



Optional opto input DLA1 Allowing audio ("beat") light response. 60p

DL3000K This 3 channel sound to light kit features zero voltage switching, automatic level control and built-in amp. No connections to speaker or amp required. No knobs to adjust — simply connect to mains supply and lamps (18w channel). Only £12.95

24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at preset times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.

- CT1000K Basic Kit £14.90
- CT1000K with white box 156.131 x 71mm. £17.40
- (Ready Built) £22.50



DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL 7126 (a lower power version of the ICL 7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required — details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week. Price £15.50



3-NOTE DOOR CHIME

Based on the SAB8060 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS. Order as XK 102. £5.50

COMPONENT PACKS

- PACK 1 650 Resistors 47 ohm to 10 Mohm — 10 per value £4.00
- PACK 2 40 — 16V Electrolytic Capacitors 10µF to 1000µF — 5 per value £3.25
- PACK 3 60 Polyester Capacitors 0.01 to 1µF 250V — 5 per value £5.55
- PACK 4 45 Sub-miniature Presets 100ohm to 1 Mohm — 5 per value £2.90
- PACK 5 30 Low Profile IC Sockets 8, 14 and 16 pin — 10 of each £2.40
- PACK 6 25 Red LEDs (5mm dia) £1.50


XK113 MW RADIO KIT

Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires PP3 9V battery. IDEAL FOR BEGINNERS. £5.50

ELECTRONIC LOCK KIT

With hundreds of uses in doors, garages, car anti-theft devices, electronic equipment etc. Only the correct easily changed four digit code will open it! Requires a 5 to 15V dc supply. Output 750mA. Fits into standard electrical wall box. Complete kit (excl. front panel) XK101 £11.50

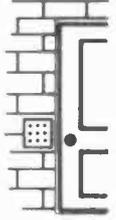Electronic lock mechanism for use with the above kit, 70 150 £14.95



INFRA RED GARAGE DOOR CONTROLLER KIT

For opening and closing motorised garage doors plus switching garage and drive lights on and off up to a range of 40ft and numerous other applications like controlling lights and TV's etc. in the home. Ideal for aged or disabled persons, this coded kit comprises of a mains powered infra red remote control receiver with a normally open relay output plus two latched transistor outputs; battery-powered four button transmitter and an opto isolated solid state mains switch. As with all our kits, full instructions are supplied.



- XK103 £25
- Extra transmitters
- XK105 £10.00

HOME CONTROL CENTRE

This kit enables you to control up to 16 different appliances by means of coded pulses in the mains wiring which may be decoded by special receivers anywhere in the house. The transmitter may be controlled manually or by the computer interface enabling your favourite micro to make your coffee in the morning, switch lights anywhere in the house, or your electric blanket in your bedroom. Just think of the possibilities and no wiring!



The Kit comprises a transmitter with pre-drilled box and two receivers.

- XK112 £42.00
- ADDITIONAL RECEIVERS
- XK111 £10.00

REMOTE CONTROL KITS

- These kits have been designed to enable infra red remote control to be incorporated into virtually any application from switching car locks or alarms to controlling hi-fi or TV. The exact application will determine the interface circuitry not supplied between the receiver and the device to be controlled. In many cases this could be a relay or triac. General instructions and applications are supplied with the kits. The kits are coded and provide a high degree of noise immunity and security.
- MK18 Transmitter KH For use with MK11-MK12 Receivers and MK3 10 13 keyboards. Requires PP3 battery. Size 8.2 x 13 cms. Range approximately 60ft. £8.80
 - MK11 Receiver KH Mains powered. Provides 10 latched plus 3 analogue outputs. Ideal for controlling audio amplifiers, TV or lighting circuits where control of lamp brightness is required. £13.50
 - MK13 Transmitter Keyboard £4.35
 - MK15 DC Controlled Stereo Amplifier KH If control of stereo amplifier required the MK15 may be used providing for remote control of tone, treble and volume (or balance). This kit also includes a one of 10 decoder with LEDs for remote selection of programme or channel. The momentary version provides an output only during transmission. Lines may be latched separately if required (circuit supplied). This may be used in conjunction with the MK13 Dual Latched Solid State Relay to switch mains leads to radio lights. TV £10.70
 - MK12 Receiver KH Mains powered. Provides up to 16 latched or momentary on/off outputs. The latched version is suitable for applications where only one of the 16 outputs is to be on at any one time, e.g. TV channel selection. The momentary version provides an output only during transmission. Lines may be latched separately if required (circuit supplied). This may be used in conjunction with the MK13 Dual Latched Solid State Relay to switch mains leads to radio lights. TV £13.50
 - MK9 4 way Transmitter Keyboard £1.90
 - MK10 16 way Transmitter Keyboard £4.50
 - MK15 Dual Latched Solid State Relay £4.50
 - SINGLE CHANNEL UNCODED INFRA RED KITS
 - MK6 CHANNEL — supplied with hand held transmitter. Requires a 9V PP3 battery. Range approximately 20ft. £4.50
 - MK7 Receiver Mains powered with track output to switch up to 500W at 240V a.c. On/off momentary output available. £10.50
 - MK15 Mains Powered Transmitter For continuous operation such as burglar alarm, automatic door operators, etc. Range approximately 6ft. May also be powered from 3v dc. £3.50
 - MK17 12v d.c. Receiver For use with MK6 or MK15. Relay output with DP 3A change over contacts. May be used as latched momentary or break beam receiver. Operates from 6.12V d.c. £10.50

WE ALSO STOCK A WIDE RANGE OF ELECTRONIC COMPONENTS

SEE CATALOGUE FOR DETAILS

Send SAE 9" x 6" for our FREE YELLOW CATALOGUE. It's packed with a full list of our stock range all at very competitive prices.

Add 65p postage & packing + 15% VAT to total Overseas Customers; Add £2.50 (Europe), £6.00 (elsewhere) for p&p. Send S.A.E. for further STOCK DETAILS. Goods by return subject to availability.

OPEN 9am to 5pm (Mon to Fri)
10am to 4pm (Sat)

COMPUTER SHOWROOM TOP HARDWARE, LATEST SOFTWARE PERIPHERALS, ACCESSORIES AND MUCH, MUCH MORE!

FAST SERVICE · TOP QUALITY · LOW LOW PRICES

No circuit is complete without a call to —


TELETRONICS

11-13 Boston Road
London W7 3SJ

01-567 8910 ORDERS
01-579 9794 ENQUIRIES
01-579 2842 TECHNICAL AFTER 3PM



ALL PRICES EXCLUDE VAT

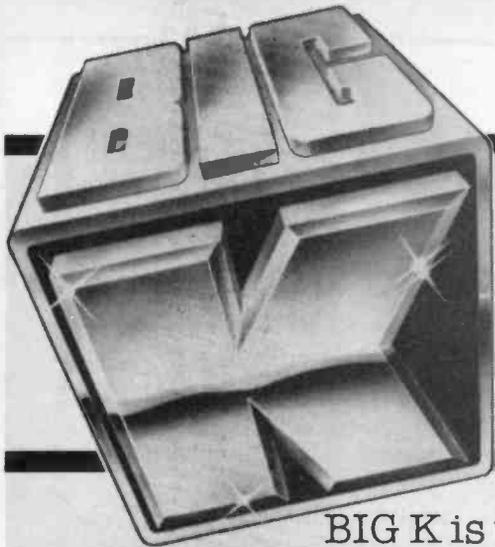

THE ONLY COMPUTER MAGAZINE YOU'LL EVER NEED

BIG K is the magazine with the most for maestros of the micro. No-holds-barred reviews – of hardware, software and other wares too numerous to mention. Flash techniques to help you clean up your programming. Type-in games listings to stimulate your imagination. And much, much more. **If you haven't got a micro you'll want one after reading BIG K.**

THIS ISSUE: Modem Living – access the world through your micro and telephone – Big K makes the right connections.

Win a full-sized BATTLEZONE arcade game in Big K's extravagant competition.

What's all the fuss about? Big K examines the 68000 wonderchip.

Atari 800XL review.

7 games programs for Commodore, Vic 20, BBC, Spectrum, ZX 81, Oric, Atari.

Atari graphics – read Big K's special feature.

Plus – Arcade Alley, dozens of games reviews, expert technical features, lots of fun and lashings of colour.



**Third amazing issue
on sale 17th May**

**Ask your newsagent
for a copy – 85p**

MIDWICH

COMPUTER COMPANY LIMITED

RICKINGHALL HOUSE, HINDERCLAY ROAD, RICKINGHALL, SUFFOLK IP22 1HH. TEL: DISS (0379) 898751.

BBC Microcomputers

Model B 348 26
Model B + Disc Int. 433 21
NB Credit cards are not accepted in payment for BBC Microcomputers

BBC Micro Econet

Full range of products available. Installation service available

BBC Compatible Disc Drives

Cased drives, finished to match the BBC Micro are supplied complete with connecting cables, manual and utilities disc

All single cased drives may be expanded to dual configuration by the addition of the appropriate uncased mechanism

Disc capacity	Single	Dual	Uncased
100K 407	180 35	291 35	130 00
400K 40/80T D S'	264 35	479 15	215 00

Trade/quantity discounts are available.

BBC 3 Disc Interface 84 95

Please send for our BBC Micro price list. Full range of accessories available

Memories

2114L-20	D1	0.92
4116-15	D2	1.05
4116-20	D2	0.88
4116-15	D1	3.75
4184-15	D2	4.33
4184-20	D2	3.35
4416-20	D2	6.60
4564-15		5.25
5516-25		7.73
6116-3	D1	3.72
6116-LP3	D2	4.67
2532-45	D2	3.50
Z708-45	D2	3.25
Z716-35	D1	5.50
Z716-45	D1	3.50
Z716-3	D1	4.50
Z732-35	D1	4.58
Z732-45	D1	3.75
Z764-30	D1	3.92
Z764-250NS TI		3.92
Z764-250NS BBC		5.95
2564-30	D2	6.00
Z7128-30	D2	24.50

Buffers

81LS95	0.95
81LS96	0.95
81LS97	0.95
81LS98	0.95
8T26A (6880AP)	0.78
8T28A (6885)	0.78
8T35 (6885)	0.78
8T37A (6887)	0.78
8T38 (6888)	0.78

Data Converters

ZN435	D1	3.70
UPD7002	D1	4.65
ZN425E-8	D1	3.13
ZN425E-8	D1	1.67
ZN427E-8	D1	5.75
ZN428E-8	D1	4.38
ZN429E-8	D1	1.33
ZN432C1-10	D1	25.98
ZN432E-10	D1	10.88
ZN433C1-10	D1	20.98
ZN440	D1	1.67
ZN447	D1	6.70
ZN448	D1	5.75
ZN449	D1	2.35
ZN441	D1	40.32

Crystals

A111B 1MHz	4.22
A112A 1.008MHz	3.42
A113A 1.0432MHz	2.88
A116A 2.4576MHz	1.00
A169A 3.6864MHz	1.55
A120B 4MHz	0.85
A132A 6MHz	0.72
A140A 8MHz	1.00
A173A 9.8304MHz	1.40
A182A 19.6608MHz	2.07

UHF Modulators

UM1111 6MHz	2.17
UM1233 8MHz	3.25

Floppy Disc Controllers

8271P	53.33
FD1771P	D5 21.25
FD1791	D6 17.00
FD1793	D6 17.00
FD1795	D6 24.35
FD1797	D6 24.35
WD1691	D2 12.00
WD2143.01	D2 7.90

6500 Family

6502A	D3	4.40
6502	D3	4.67
6520	D1	2.67
6520A	D1	2.80
6522	D5	3.47
6522A	D5	4.40
6532	D2	5.33
6532A	D2	5.87

Linear & Interface Devices

6402		6.00
AY3-1015	D2	2.92
AY3-1270		6.50
AY3-8910	D6	4.48
AY5-3600	D2	7.37
DF8304	D1	1.92
1283		0.80
LF398		3.17
LM301AN		0.24
LM308AN		0.73
LM308N		0.47
LM311N		0.84
LM319		2.23
LM324N		0.32
LM339N		0.37
LM348N		0.53
LM358N		0.28
LM393N		0.34
LM725CN		1.33
LM741CP		0.18
LM747CP		0.48
LM748CP		0.22
MC1413P	D1	0.66
MC1416	D1	0.66
MC1458CPL		0.26
MC1495L		7.13
MC1496P		0.65
MC1723P		0.32
MC3242A		5.25
MC3302P		0.40
MC3340P		1.97
MC3357P		1.56
MC3423PL		0.67
MC3441AP		2.40
MC3446AP	D1	2.40
MC3477P		3.58
MC348AP	D1	3.32
MC3470P		5.23
MC3480P	D5	6.47
MC3487P	D1	1.50
MC14411	D1	8.52
MC14412		11.87
NE555P		0.19
NE556CP		0.45
RO3-2513L	D1	7.82
RO3-2513U	D1	7.82
SN75107BP		0.58
SN75110AP		0.68
SN75150P		0.72
SN75154N		0.87
SN75158N		1.19
SN75160AN		2.15
SN75161AN		2.35
SN75162AN		3.31
SN75172NG		1.64
SN75173N		1.21
SN75174		1.64
SN75175		1.21
SN75182		0.62
SN75183		0.62
SN75188		0.44
SN75189		0.44
SN75451BP		0.24
SN75452BP		0.24
SN75453BP		0.24

SN75454BP

SN75468N	1.08
SN75481AN	0.46
SN75492AN	0.61
TL010CP	0.98
TL061CLP	0.28
TL062CP	0.47
TL064CN	0.89
TL066CP	0.28
TL071CP	0.28
TL072CP	0.47
TL074CN	0.91
TL081CP	0.24
TL082CP	0.41
TL084CN	0.85
TL091CP	0.41
TL092CP	0.60
TL094CN	1.37
TL487CP	0.55
TL489CP	0.55
TL494CN	1.66
TL496CP	0.30
TL507CP	1.02
ZN450E	5.25
ZN451E	6.38
ZN451KIT	25.65

DIL Sockets

Pin	Tin	Gold	W/W
8	0.10	0.24	0.58
14	0.12	0.28	0.77
16	0.13	0.32	0.86
18	0.16	0.32	1.08
20	0.17	0.41	1.23
22	0.17	0.48	1.31
24	0.20	0.63	1.44
28	0.23	0.57	1.59
40	0.33	0.99	1.96

ZIF Sockets

24 Pin	5.80
28 Pin	6.35
40 Pin	8.45

Data sheets are available on items marked D.

D1	0.75	D5	2.50
D2	1.00	D6	3.00
D3	1.25	D7	4.00
D4	2.00		

A full range of the following products is carried in stock and is listed in our FREE catalogue.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

ELECTRONICS ENGINEERING

A Diploma Course, recognised by the Institute of Engineers & Technicians as meeting all academic standards for application as an Associate.

T.V. & AUDIO SERVICING

A Diploma Course, training you in all aspects of installing, maintaining and repairing T.V. and Audio equipment, domestic and industrial.

ELECTRICAL ENGINEERING

A further Diploma Course recognised by the Institute of Engineers & Technicians, also covering business aspects of electrical contracting.

RUNNING YOUR OWN BUSINESS

If running your own electronics, T.V. servicing or electrical business appeals, then this Diploma Course trains you in the vital business knowledge and techniques you'll need.

Name

Address

ICS ICS
Dept V273
160 Stewarts Road,
London SW8 4UJ.

01-622 9911
(all hours)

Prices: all prices exclude V.A.T. and carriage. Please add these to your order. All prices correct at time of going to press.

For FREE CATALOGUE post to Midwich Computer Company Limited, Rickingham House, Hinderclay Road, Rickingham, Suffolk IP22 1HH

Name

Address

Telephone

SPECIAL TELEPHONE NUMBER FOR FAST, IMMEDIATE SERVICE, TELEPHONE YOUR ORDER TO: DISS (0379) 898751

SPECIAL OFFER SPECTRUM 32K UPGRADE KIT £24.95

Carriage Orders up to £199 are sent by 1st class post and £200+ by Securion.

0-£100 0.50 £100-£199 1.25 £200+ 5.00 by Securion

Prices quoted (+ carriage charges) are exclusive of VAT and are subject to change without notice.

Quantity Discounts are available on many products, please ring for details.

Official Orders are welcome from Education Establishments, Government Bodies and Public Companies

Credit Accounts are available to others subject to status. Payment is due strictly net by the 15th of the month

Credit Cards are accepted (Access and Visa) for telephone and postal orders and NO SURCHARGE is made.

Out of stock items will follow automatically, at our discretion, or a refund will be given if requested.

T.V. SOUND TUNER

SERIES II BUILT AND TESTED Complete with case. £26.50 + £2.00 p&p.

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains-operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 10 1/2" x 7 1/2" x 2 1/2". E.T.I. kit version of above without chassis, case and hardware. £16.20 plus £1.50 p&p.




Also available with built-in headphone amp. ONLY £32.50 + £2.00 p&p.

PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT

COMPLETE WITH CASE ONLY £34.50 plus £2.75 p&p.

- NOISE REDUCTION SYSTEM. • AUTO STOP. • TAPE COUNTER. • SWITCHABLE E.Q. • INDEPENDENT LEVEL CONTROLS. • TWIN V.U. METER. • WOW & FLUTTER 0.1%. • RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING. • FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF AEL TYPES.

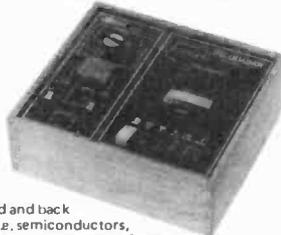
Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts, i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook-up wire. Featured in April P.E. reprint 50p. Free with kit.



BSR RECORD DECKS

Auto-Changer model - takes up to 6 records with manual override. Supplied with stereo ceramic cartridge.

£12.95 plus £1.75 p&p.

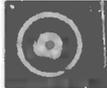

3 speed, auto, set-down; with auto return. Fitted with viscous damped cue, tubular aluminium counter-weighted arm, fitted with ADC magnetic head. Ideally suited for home or disco use. £25.95 plus £1.75 p&p.

Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco. 13" x 11" approx. £14.95 plus £1.75 p&p.



125W HIGH POWER AMP MODULES

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

Accessories: Stereo mains power supply kit with trans. £10.50 + £2 p&p. Mono: £7.50 + £2 p&p.



SPECIFICATIONS:
Max. output power (RMS): 125 W. Operating voltage (DC): 50 - 80 max. Loads: 4 - 16 ohm. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100w: 400mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205x90 and 190x36mm.

KIT £12.00 + £1.15 p&p. BUILT £17.50 + £1.15 p&p.

HI-FI SPEAKER BARGAINS

AUDAX 8" SPEAKER £5.95 + £2.20 p&p.

High quality 40 watts RMS bass/mid. Ideal for either HiFi or Disco use this speaker features an aluminium voice coil and a heavy 70mm dia. magnet. Freq. Res.: 20Hz to 7kHz. Imp.: 8 ohms.

AUDAX 40W FERRO-FLUID HI-FI TWEETER Freq. res.: 5KHz - 22KHz. Imp.: 8 ohms. 60mm sq. £5.50 + 60p p&p.

GOODMANS TWEETERS 8 ohm soft dome radiator tweeter (3 1/2" sq) for use in systems up to 40W. £3.95 ea + £1 p&p. £6.95 pr + £1.50.

MONO MIXER AMP

Ideal for halls and clubs. £45.00 + £2 p&p.

50 Watt, six individually mixed inputs for 2 pickups (Cer. or mag), 2 moving coil microphones and 2 auxiliary for tape tuner, organs etc. Eight slider controls - 6 for level and 2 for master bass and treble, 4 extra treble controls for mic. and aux. inputs. Size: 13 1/2" x 6 1/2" x 3 1/2" app. Power output 50 W RMS (cont.) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.



All mail to: 21B HIGH ST, ACTON W3 6NG. Callers: Mon - Sat 9.30 - 5.30. Half day Wed. Access phone orders on 01-992 8430.

Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 30/1/83 and subject to change without notice. Please allow 14 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. All enquiries send S.A.E. Telephone or mail orders by ACCESS welcome.

CALLERS TO: 323 EDGWARE ROAD, LONDON W2. Telephone: 01-723 8432. (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 5.30. Prices include VAT.



ORIC AND SINCLAIR COMPUTERS



Oric 1 computer 48K £143 (£141) £151. Oric Colour Printer £134 (£123) £140. New Sinclair QL Computer £495 (£455) £475. Sinclair Spectrum 48K £131 (£131) £143. Spectrum 16K £101 (£105) £117. Microdrive £70 (£65) £75. RS232 Interface £70 (£65) £75. Blank micro-drive cartridges £8 (£8) £9. 32K memory upgrade kit for 16K Spectrum (Issue 2 and 3 only) £31 (£28) £30. Fuller Master Unit for the spectrum including speech unit, sound synthesizer, amplifier and joystick port £56 (£56) £62. Fuller full sized FDS keyboard for the spectrum with proper space bar £52 (£52) £62. Spectrum printer interfaces with cables: Centronics £57 (£53) £58, RS232 £35 (£33) £38. ZX printer £41 (£40) £50. 5 printer rolls £13 (£16) £21. ZX81 computer £45 (£44) £54. ZX81 16K ram packs £28 (£25) £30.

COMMODORE COMPUTERS

Commodore 64 £204 (£184) £204. Vic 20 £104 (£97) £117. Converter to allow most ordinary mono cassette recorders to be used with the Vic 20 and Commodore 64: £10.95 (£11) £13. Bargain package: cassette convertor + compatible cassette recorder £37 (£38) £44. Commodore cassette recorder £43 (£44) £50. Centronics printer interfaces: for Vic 20 and Commodore 64 £45 (£44) £50. RS232 printer interface £45 (£44) £50. 1541 Disc drive £233 (£209) £234. 1525 Printer £235 (£220) £245. 1526 Printer £350 (£330) £360.

SWANLEY ELECTRONICS


The Computer Export Specialists
Dept PE, 32 Golds Rd., Swanley, Kent BR8 8EZ, England.
Please allow 7 days for delivery.

Tel: Swanley (0322) 64851. Nothing extra to pay. All prices are inclusive. UK prices are shown first and include post and VAT. The second price in brackets is for export customers in Europe and includes insured air mail postage. The third price is for export customers outside Europe (including Australia etc) and includes insured airmail postage. Official orders welcome.

ACORN COMPUTERS

Electron £203 (£209) £229. BBC Model B £404 (£357) £487. 14" Colour monitor £228 (£299) £319. Kenda double density disk interface system for beeb £139 (£125) £135. 3" Floppy disc drive £175 (£160) £190. 80 track double sided 5.25" drives: Single 400/800K £245 (£230) £250, Dual 800/1600K £455 (£420) £450.

PRINTERS

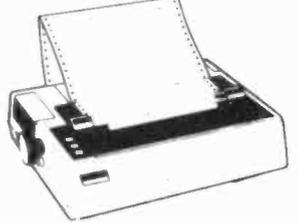

Brother HR5 £185 (£171) £190. Epson RX80 £306 (£271) £302. Epson RX80F/T £346 (£316) £346. Shinwa CTI CP90 £225 (£218) £248. Epson FX80 £440 (£408) £438. Epson MX100/3 £494 (£465) £495. Oki Microline 80 £213 (£197) £238. Oki Microline 84 £831. Combined matrix printers and electric typewriters: Brother EP22 £173 (£166) £186. Brother EP44 £258 (£235) £260. Smith Corona TP1 Daisy wheel printer £252 (£225) £255. Oric colour printer £134 (£123) £140. Interfaces to run the above printers from Vic and the Commodore 64 £45 (£44) £50. We can supply interfaces to run the above printers from Sharp computers £58 (£52) £55.

ELECTROVALUE

Your SPECIALIST SUPPLIERS for CONNECTORS



Not only will you find a wide selection of all the usual types you may require in our A-Z products list; there are also many others made necessary by today's ever-advancing electronics - just one more example of how much better Electrovalue serves you.

Please mention this journal when getting in touch with Electrovalue

D SERIES CONNECTORS

9, 15, 25, 37 or 50 way connectors with corresponding covers and retainers. Gold-plated contacts. Max current per contact - 5A.

For connecting ribbon cable to PCBs. Insulation Displacement Type: 16, 20, 26, 34 or 40 way. 1A per contact. Straight or right angle plug fitting; cable socket has strain relief.

RPC CONNECTORS

5 way and 7 way chassis plus and sockets. DIN style layout. Gold-plated pins 250V/5A rating per socket.

OTHER TYPES

Edge connectors, DIN, jack plugs and sockets, phono, XLR, BNC, UHF and power.

BRITAIN'S LEADING QUALITY COMPONENT SUPPLIERS - SEND FOR FREE 36 PAGE A-Z LIST
ATTRACTIVE DISCOUNTS - FREE POSTAGE - GOOD SERVICE & DELIVERY

ELECTROVALUE LTD

20 St Jude's St, Egham
Englefield Grn, Egham
Surrey TW20 0HB

Phone (0784) 33603. Telex 264475

North: 680 Burnage Lane, Manchester (061) 432 4945

EV Computing Shop: 700 Burnage Lane, Manchester (061) 431 4866

ACCESS AND
BARCLAYCARD
Phoned Orders
Welcome

Low-price robots from POWERTRAN

— hydraulically powered
— microprocessor controlled

The UK-designed and manufactured range of Genesis general purpose robots provides a first-rate introduction to robotics for both education and industry.

Each robot in the Genesis range has a self-contained hydraulic power source operated from single phase 240 or 120v AC or from a 12v DC supply. Up to six independent axes are capable of simultaneous operation and all except the grip axis have sensing devices fitted to provide positional control by a closed loop system based on a dedicated microprocessor. Movement sequences can be programmed by means of a hand-held controller or the systems can be interfaced with an external computer via a standard RS232C link.



GENESIS P101

The top-of-the-range P102 has dual speed control, enhanced memory and double acting cylinders for increased torque on the wrist and arm joints. There is position interrogation via the RS232C interface, increasing the versatility of computer control and inputs are provided for machine tool interfacing.

All Genesis robots are available either ready-built or in kit form. The latter provides not only extra economy but also valuable additional training as an assembly project.



GENESIS P102



HEBOT II Turtle-type robot

For a little over £100, Hebot II takes programming off the VDU and into the real world. Each wheel is independently controlled by a computer, enabling the robot to perform an almost infinite number of moves. It has blinking eyes, a two-tone bleep and a solenoid-operated pen to chart its moves. Touch sensors, coupled to its shell return data about its environment to the computer enabling evasive or exploratory action to be calculated.

The robot connects directly to an I/O port or, via the Interface board, to the expansion bus of a ZX81 or other microcomputer.

HEBOT II

Weight 1.8kg
complete kit with assembly instructions **£95**
Interface board kit **£11**

MICROGRASP



A real programmable robot for under £300! Micrograsp has an articulated arm jointed at shoulder, elbow and wrist positions. The entire arm rotates about its base and there is a motor driven gripper. All five axes are motor driven and four of these are servo controlled giving positive positioning. The robot can be controlled by any microcomputer with an expansion bus - the Sinclair ZX81 being particularly suitable.

MICROGRASP

Weight 8.7kg, max. lifting capacity 100g
Robot kit with power supply **£215.00**

Universal computer interface board kit **£57.00**
23 way edge connector **£3.00**
ZX81 peripheral/RAM pack splitter board **£3.50**

GENESIS P101

Weight 34kg, max lifting capacity 1.8kg
6-axis model (kit form) **£750**
6-axis complete system (kit form) **£1050**

GENESIS P102

Weight 36kg, max lifting capacity 2kg
6-axis system (kit form) **£1476**
Powertran Cortex microcomputer self-assembly kit **£295.00**

Cortex 16 bit microcomputer

Goods subject to availability. All prices exclusive of V.A.T. and correct at time of going to press.



POWERTRAN cybernetics Ltd.

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3PE. TEL (0264) 64455

ALL PRICES ARE EXCLUSIVE OF VAT AND APPLY TO THE U.K. ONLY - ALLOW 21 DAYS FOR DELIVERY. OVERSEAS CUSTOMERS - PLEASE CONTACT OUR EXPORT DEPARTMENT FOR THE NAME AND ADDRESS OF YOUR LOCAL DEALER.



TECHNOLOGY AND UNEMPLOYMENT

THIS issue carries a feature which describes a development of significance to all householders; a development which would not be possible without modern technology; a development which will probably mean a reduction in jobs; a development which could save us all money. The feature to which we are referring is *Spot-Pricing Needs Electronics*. No mention is made in the article of job losses, but we believe total introduction of such a system could result in the need for fewer employees in the electricity supply industry. This leads to the question of job losses caused by the introduction of new technology and automation in general.

Of course the question has been posed over many years and some commentators have suggested that increased sales, resulting from automation reducing product prices, will mean similar or even greater staffing levels. It is now becoming clear that, so far, this has not proved to be the case. A few years ago most companies were optimistic about the effects of new technology on employment but a re-

cent survey by the Policy Studies Institute suggests that about 30,000 jobs will be lost in the next two years because of the use of microelectronics. Perhaps this is one reason why unemployment figures continue to rise in the face of a gradual economic recovery.

Spot-pricing could save us all money but this could well be partially achieved as a result of job losses. Does this mean that we should not introduce new technology? If we don't our industry will soon become out of step with the rest of the world and not only will we need import restrictions to compete in the UK but we will lose our export market on which we depend for much of our prosperity. Surely it means that we must find ways of spreading employment to keep everyone in a worthwhile, paying job.

RESPONSIBILITY

Since electronics must carry the responsibility for many of the lost jobs should the electronics industry start to put things right by introducing a lower retirement age and a shorter working week? While this sounds wonderful on paper, in practice it leads to a number of problems, not the least being the

lack of qualified, experienced electronic engineers. This lack of skilled personnel will only be solved gradually with the aid of our educational system. It must gear itself to produce workers to fill the demands of industry not simply to educate for the sake of education.

However, there are areas where something could be done now to make room for qualified unemployed personnel, for instance we find it unbelievable that doctors are able to work into their seventies and eighties when young qualified doctors cannot get jobs. A compulsory retirement age for all would start to sort out the problem and a gradual reduction of that age would possibly help in the future.

The lead to a better future for all must be set by government, not by the industry that spawns the developments from which the problems start. Surely it is better to pay a pension than unemployment benefit?



Editor Mike Kenward

Assistant Editors

Dave Barrington (Production)
David Shortland (Technical)

Technical Editor

Mike Abbott

Projects Editor

David Brunskill

Technical Sub-Editors

Richard Barron
Brian Butler

Art Editor

Jack Pountney

Assistant Art Editor

Keith Woodruff

Senior Tech. Illustrator

John Pickering

Tech. Illustrator

Isabelle Greenaway

Technical and editorial queries and letters (see note below) to:

Practical Electronics Editorial,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG

Phone: Editorial Poole 671191

We regret that lengthy technical enquiries cannot be answered over the telephone

Queries and letters concerning advertisements to:

Practical Electronics Advertisements,
King's Reach Tower,
Stamford Street, London SE1 9LS
Telex: 915748 MAGDIV-G

Advertisement Manager David Tilleard 01-261 6676

Secretary Christine Pocknell 01-261 6676

Advertisement Sales Executives

Alfred Tonge 01-261 6819

Richard Willett 01-261 6865

Classified Supervisor Barbara Blake 01-261 5897

Ad. Make-up/Copy Brian Lamb 01-261 6601

Letters and Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in PE. All letters requiring a reply should be accompanied by a stamped, self addressed envelope, or addressed envelope and international reply coupons, and each letter should relate to one published project only.

Components and p.c.b.s are usually available from advertisers; where we anticipate difficulties a source will be suggested.

Back Numbers and Binders

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at £1 each including Inland/Overseas p&p. Please state month and year of issue required.

Binders for PE are available from the same address as back numbers at £5.50 each to UK or overseas addresses, including postage, packing and VAT where appropriate. State year and volume required.

Subscriptions

Copies of Practical Electronics are available by post, inland for £13, overseas for £14 per 12 issues, from: Practical Electronics, Subscription Department, IPC Magazines Ltd., Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. Cheques, postal orders and international money orders should be made payable to IPC Magazines Limited. Payment for subscriptions can also be made using any credit card and orders placed via Teledata. Tel. 01-200 0200.

Items mentioned are available through normal retail outlets, unless otherwise specified. Prices correct at time of going to press.

NEWS &

TOP OF THE FORM

Most of us at one time or another would like to see our projects housed in a more professional manner. Now we can do just that with a one-off vacuum forming service from Origin Products. A heated thermoplastic sheet is sucked over a wooden pattern forming a 'shell' facsimile of the original.

All the items shown here were vacuum formed using the Formech range of machines. Two machines are available from the company—the 300 and the 450. The 300 has a maximum material handling size of 300mm square and 10mm deep, and is a bench-top model. The 450 is somewhat larger and is freestanding, its maximum capabilities are 450mm square and 250mm deep. Both these machines can be used directly from a standard 13A supply. The maximum size of mouldings available

from the one-off service are the same as those stated for the Formech 450 machine.


The materials used include high-impact Polystyrene, ABS, PVC, Polycarbonate and perspex. Many different colours and textures are available, 'clear' being a further option. Origin will produce a mould from a customer's own pattern, which must fulfil a few basic requirements such as allowances for release angles, etc. A detailed advice sheet giving simple tips will be supplied by the company on receipt of a s.a.e.



Typical prices for one-off mouldings in 1mm thick styrene are 150mm x 150mm—£3.00, 300mm x 300mm—£4.50, and 450mm x 450mm—£6.00. The machines, however, cost £950 for the 300 and £1450 for the 450. Details from Origin Products Ltd, 10 Lambton Place, Westbourne Grove, London W11 2SH (01-221 4121).

PANTOGRAPHIC PLOTTER

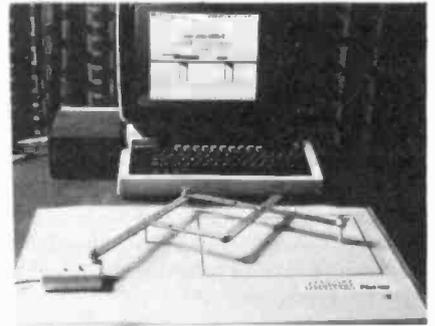The Reekie Technology Co is launching a versatile drawing aid for BBC model B micro's. Software is available on disc




or cassette. Software is presently being written for the Commodore 64, Spectrum and the IBM/PC.

The Image Plotter allows the reproduction of diagrams, maps and charts etc with great precision. Even the most irregular and complex shapes can be enlarged or reduced in vivid colour. Using a printer, disc or cassette these diagrams can then be saved for future use.

The plotter costs £49.45 inc VAT and p&p. It comes complete with calibration sheet, detailed handbook and software (state disc or cassette). It is only available through mail-order at the moment, from Reekie Technology Company, Beaufort Road, Off Richmond Road, East Twickenham, Middx. TW1 2PH. (01-892 2877).

TRACK REPORT

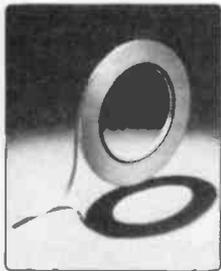

A range of self-adhesive copper foil strips has been launched by Copperfoil Enterprises. As well as for p.c.b. track repairs and modifications the foil will be of great value in prototype applications.

The soldering-proof adhesive bonds the strip monolithically to all insulating surfaces including paper. The strip conforms to BS safety regulations and has an a.c./d.c. voltage rating of 24V, current 5A. Being almost pure copper (99.999%) excellent heat dissipation can be expected. Present uses include alarm systems, proximity switches, moisture detection, level detection and capacitive applications etc, etc.

Copperfoil is available in four widths: 4mm, 4.75mm, 6mm, and 8mm; prices per 33 metre roll are £2.95, £3.35, £3.95 and £4.25 respectively, includes VAT and p&p. Copperfoil Enterprises, 141 Lyndhurst Drv, Hornchurch, Essex. (04020 56697).


KEYBOARDS

Membrane QWERTY keyboards 350mm x 100mm x 2mm and 16-way 0-9 plus A-F keyboards 100mm x 100mm x 2mm are available from Semiconductor Supplies.

These very thin keyboards consist of glass fibre PCB's faced with a tough, attractively colour-printed polycarbonate film. A light touch on the film makes a silver-plated contact.

The full-size 55 key non-encoded QWERTY keyboard has a matrix output via a 16-pin DIL socket. On the 16-way board connections are via 17 pins (one common).

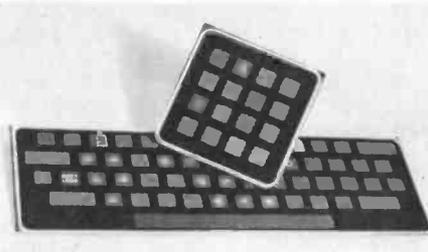Prices: £17.75 and £7.90 inc VAT and p&p. For further details contact Mr. Dennis Cresswell, Semiconductor Supplies, Sutton. (01-643 1126).



FORTH FIRST

In our February edition we reported on a multitasking FORTH ROM for the ZX81, by David Husband (now Skywave Software). Not surprisingly, this product has been a success and has allowed a move to larger premises. Work in progress now includes a multitasking FORTH I/O cartridge for the Spectrum.

Prompted by the release of the new FORTH-83 standard by the FORTH Standards team, David Husband has brought forward the release of his Multi-FORTH 83 for the BBC Micro, which, naturally, includes multitasking. The product is purposely priced only a few pounds above the old 8K version associated with the early BBC Micros, whilst featuring a performance far exceeding those old versions. Skywave Software, 73 Curzon Road, Boscombe, Bournemouth BH1 4PW. (0202 302385).

MARKEE PLACE

POINTS ARISING...

STARDESK January/February '84

TR27-34 are shown correctly for the devices used in the original unit. However, most other manufacturers have the pinouts in the reverse fashion. Constructors should check the pinout for the manufacturer they use.

Diodes D62-69 are shown the wrong way round on the component layout.

Through board link not shown (above R121).

R169 not marked on overlay and is between S7 and S8.

The pin layout for the small signal transistors given at the top right of the layout diagram should read "all transistors except TR27-34".

To get the correct relationship between slider and switches heights, the sliders are mounted on top of the board and soldered to short lengths of 1.2mm/18s.w.g. tinned copper wire which itself occupies the p.c. holes.

C34 is incorrectly shown in the parts list as 2 μ 2. It is shown correctly on the circuit as 22 μ .

The tinned copper wire reinforcement mentioned in the text should bridge the *live* bus which is on the back of the board, not the neutral as stated. The reinforcement is best applied at the junctions of the triac terminal pins and C13/16, C35/42 with sleeving between. This avoids the need to remove the solder resist, and prevents fouling of the GRP backing strip by the wire.

Note: The 1N4148 diodes supplied with the kit have a yellow band as polarity marker (+ve or cathode). The grey band should be ignored.

COMPUTER TERMINAL Feb/March '84

Some readers may wish to know that the AY-5-2376 keyboard encoder referred to in the article is now obsolete. The article assumes the use of a keyboard incorporating its own encoder, in conjunction with the Computer Terminal p.c.b. However, a constructor wishing to either build his own keyboard encoder section, or replace an AY-5-2376 already found on an old keyboard assembly, can use the pin-compatible SNC KR2376, supplied by Campbell Collins of Stevenage. £0438 69466. The i.c. costs around £10.

Briefly...

The British Amateur Electronics Club (BAEC) is an amateur electronics club based in the UK, helping all who are in-

terested in electronics. The key to the club's success lies in their quarterly Newsletter which contains many pages of circuits, advice, letters, news and exchanges etc. The club was formed in 1966 and now has many members from beginners to experts in all parts of the UK.

Membership for UK and Eire members is £5.50, overseas £7.00 (£8.50 air-mail). For details contact: The BAEC Hon. Sec. Mr Margetts, 113 South Rd, Horndean, Hants PO8 0ER.



The long-awaited breakthrough has finally been made. Using the latest silicon technology, over one million transistors can be crammed into one chip.

At the International Solid-State Circuits Conference in San Francisco 1-Mbit dynamic RAMs were on display. Made by Hitachi Ltd, these chips are organised as 1M by 1 bit and can be squeezed into an 18-pin package.

Silicon News Corner

Motorola ♦ Fast new HMOS 16K-bit static RAM (16K x 1) is the MCM2167H.

♦ Fast new 16K-bit static RAM (2048 x 8) is the MCM2016H.

♦ Extensive new line of RF power MOSFETs (5W-125W @ 150MHz) using TMOS. Designated MRF134, MRF136, MRF171, MRF172 and MRF174.

♦ MC3412/3512 is a high speed 12-bit DAC which minimises external adjustments.

♦ New series plastic Schottky rectifiers to 240A. These are: MBR2003SCT and MBR2004SCT.

♦ New 8-bit HCMOS μ P incorporating EEPROM and ADC. Type MC68HC11.

♦ New 8-bit μ P has 96 bytes RAM. 2K ROM plus EEPROM, called MC6805K2.

♦ New CMOS 8-bit ADC is the MC14442, μ P compatible.

♦ 400V transistor opto-couplers MOC8204, MOC8205 and MOC8206.

♦ Three-volume data book set, covers all CMOS devices.

Motorola Ltd., European Literature Centre, 88 Tanners Drive, Blakelands, Milton Keynes MK14 5BP.

Countdown ...

Please check dates before setting out, as we cannot guarantee the accuracy of the information presented below. Note: some exhibitions may be trade only. If you are organising any electrical/electronics, radio or scientific event, big or small, we shall be glad to include it here. Address details to Mike Abbott.

Biotech Europe May 15-17. Wembley Conf. Cntr., London. O
DEC User May 15-17. Cunard Int. Hotel, Hammersmith, London. Q1
Micro City May 15-17. Exhibition Complex, Bristol. F3
EXPO 84 (West Midlands) May 26-June 3. N.E.C. J4
Energy Management & Control May 29-31. W3
Scotex June 5-7. Royal Highland Exhibition Halls, Ingleston, Edinburgh. O5
IBM System User Show June 12-14. Wembley Conf. Cntr., London. O
Computer Fair June 14-17. Earls Court. K2
Qualex June 19-21. Corn Exchange, Brighton. D4
Compec North June 19-21. Belle Vue, Manchester. K2
Surface Treatment & Finishing Show June 25-29. Birmingham. M
Office Automation Show June. Barbican, London. T1

Leeds Electronics July 3-5. University. E
Networks July 3-5. Wembley Conf. Cntr., London. O
Cable July 10-12. Wembley Conf. Cntr., London. O
Laboratory Sept. 4-6. Barbican, London. E
Testmex Sept. 11-13. Grosvenor Ho. Pk. Lane, London. E
Personal Computer World Show Sept. 19-23. Olympia 2, London. M
Building & Home Improvement Sept. 25-30. Earls Court, London. M
Computer Graphics Oct. 9-11. Wembley Conf. Cntr., London. O
Software Expo Oct. 16-18. Wembley Conf. Cntr., London. O
Drives, Motors & Controls Oct. 24-26. Harrogate Exhibition Cntr. E
Computers In The City Nov. 20-22. Barbican, London. O
Data Security Nov. 20-22. Barbican, London. O

D4 Network £ 0280 815226
E Evan Steadman £ 0799 26699
F3 Tomorrow's World £ 0272 292156
J4 N.E.C. Birmingham £ 021-780 4141
K2 Reed Exhibitions, Sutton, Surrey
M Montbuild £ 01-486 1951
O Online £ 01-868 4466
O5 Institute of Electronics £ 0706 43661
Q1 W.P. Association £ 01-242 8697
T1 Cahners £ 0483 38085
W3 MCM Publishing £ 01-231 1481



The GSC range of logic probes have been designed to simplify the troubleshooting of digital circuits. All four probes shown here are powered from the circuit under test. The **LP1** probe combines the functions of a level detector, pulse detector, pulse stretcher and pulse memory. The unit responds to 50nsec pulses at up to 10MHz. The **LP2** is a basic probe for applications where high speed and memory are not required. The **LP3** is for high speed troubleshooting and is capable of capturing pulses as narrow as 10nsec or pulse trains over 50MHz. The **LPK1** is a kit probe which is suitable for lower speed logic systems. The **4001** pulse generator can drive up to 40 TTL loads and has four modes: run, triggered, gated and one shot. Prices: LP1 £39.67, LP2 £24.15, LP3 £61.52, LPK1 £16.67, 4001 £184. **GSC (UK) Ltd**, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex. (0799 21682).

TEST INSTRUMENTS buyer's guide

At some time during the building or testing of an electronic circuit there will always be a need for test equipment. Whether it is just a simple logic probe or an oscilloscope, test equipment can make the troubleshooting of circuits both easier and more interesting.


In this buyer's guide we have chosen an interesting cross section of instruments to cover most applications.


Further information and complete specifications on all models mentioned can be obtained from the addresses shown. Please note that all the prices shown include VAT but not p&p or carriage.



The **TG 105** from Thandar is a 5Hz to 5MHz pulse generator. The unit operates over 6 overlapping decade ranges with a separate vernier providing continuously variable control within each range. Run, gated, triggered, squarewave, complement or one shot modes are available and the output amplitude is switch selected over two variable ranges (0.1V to 1V and 1V to 10V). The TG 105 is priced at £120.75. **Audio Electronics**, 301 Edgware Road, London. (01-724 3564).

The **Hameg 605** is a dual trace 60MHz oscilloscope with a built-in component tester for checking either single components or for in-circuit testing. Triggering is possible up to 80MHz and it is possible to display two unrelated time signals at one time. Small sections of signals can be analysed using a sweep delay feature which allows 'X' expansion of 1000 or more. A built in delay line permits viewing of the trigger leading edge. The HM 605 is priced at £560.00 and is available from **Hameg Ltd.**, 74-78 Collington Street, Luton, Beds. (0582 413174).

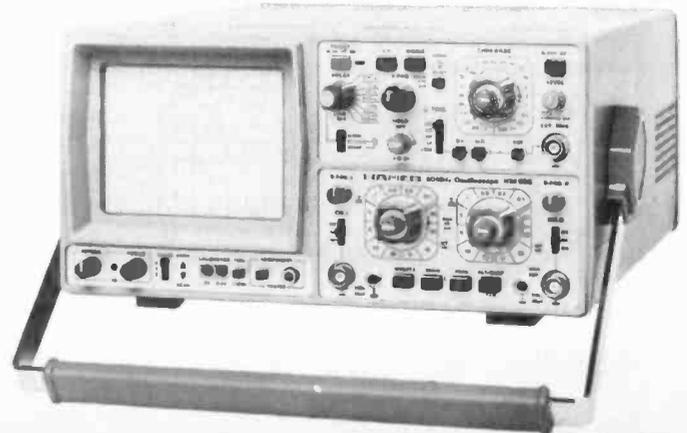

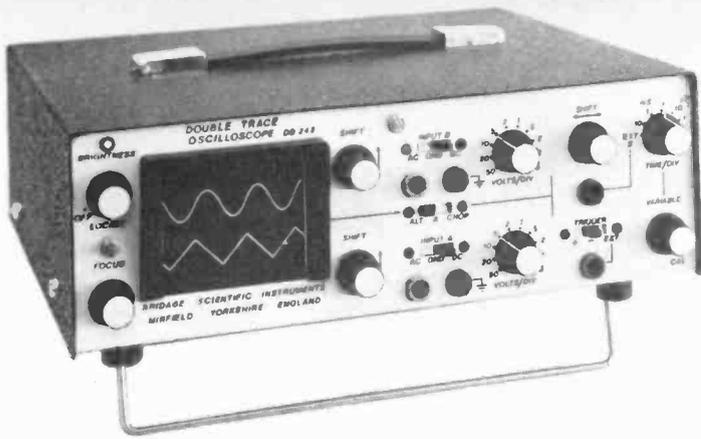

The **DB242** general purpose oscilloscope is a portable unit which has been designed for educational, service and hobby use. Sensitivity can be varied from 50mV/cm and sweep speeds varied between 1 μ s/cm and 0.2s/cm using calibrated switch positions. A cheaper single trace version, the Bridge **SB121** is also available and its general specification is similar to the DB242 but without the twin channel facility. The DB242 is priced at £258.75 and the SB121 at £224.25. **Bridge Scientific Instruments Ltd.**, 63/65 High Street, Skipton, North Yorkshire. (0756 69511).





The **PFM 200A** is a pocket sized counter with an 8-digit l.e.d. display covering a frequency range from 20Hz to 200MHz using two ranges. Resolution for the unit is down to 0.1Hz and the sensitivity is typically 10mV r.m.s. Battery life, depending upon range and display, is around 10 hours. Two prescalers (up to 600MHz and 1GHz) are available as optional accessories. The PFM 200A is priced at £79.93 and is available from **Audio Electronics**, 301 Edgware Road, London. (01-724 3564).

The **TG303** function generator produces sine, square, triangle, pulse, sawtooth ramp and asymmetrical sine waveforms over the frequency range of 0.02Hz to 2MHz. A d.c. offset can be superimposed on the output signal. The TTL output is a fixed amplitude square or pulse waveform with a fast rise time able to drive up to 20 TTL loads. The unit has a 6-digit frequency counter that can be switched to measure the frequency of the generator or an external source up to 10MHz. A CMOS output variable from 5 to 15V is also available. The TG303 is priced at £224.00 and is available from **Levell Electronics Ltd.**, Moxon Street, Barnet, Herts. (01-440 8686).



The **TG101** function generator covers the frequency range 0.02Hz to 200kHz in five overlapping decade ranges with a vernier fine adjustment. The input impedance is 10k Ω . The output level of the three operating modes: sine, square and triangular, is adjustable from 0 to 5 volts pk-pk into 600 ohms. There is also a TTL output which is capable of driving up to 20 standard TTL loads. Priced at £120.75 the TG101 is available from **Audio Electronics**, 301 Edgware Road, London. (01-724 3564).

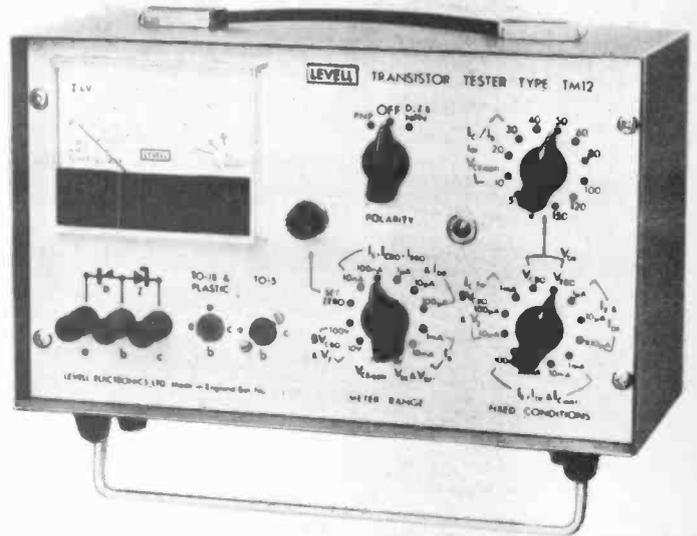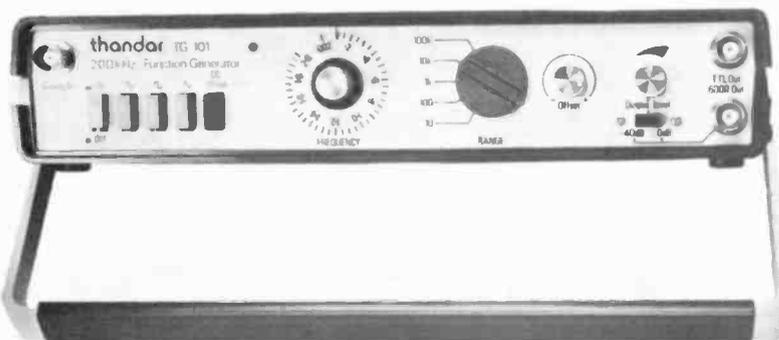


The **TM12** measures the characteristics of bipolar transistors, diodes and Zeners. Current gains are checked at collector currents from 1 μ A to 100mA. Breakdown voltages up to 100V are measured at currents of 10 μ A, 100mA and 1mA. Leakage currents down to 0.5nA are measured from 2V to 150V. The collector to emitter saturation voltage of the transistor is measured at collector currents of 1mA, 10mA, 30mA and 100mA for Ic/Ib ratios of 10, 20 and 30. The instrument is powered by a 9V battery. The TM12 is priced at £207.00 and is available from **Levell Electronics Ltd.**, Moxon Street, Barnet, Herts. (01-440 8686).

TEST INSTRUMENTS


buyer's guide



The Soar FC-841 Frequency Counter is capable of measuring frequencies from 10Hz to 50 MHz. The instrument has a 4 digit 10mm l.e.d. display and is battery powered. A feature of this unit is the range switch, which allows up to a 7 digit accuracy. Input impedance is 1Mohm plus stray capacity, input sensitivity being 60mV. Oscillator stability is 1.5p.p.m. (0.0015%). Supplied with batteries this counter is priced at £49.90 and is available from **Maplin Electronic Supplies Ltd**, 159-161 Kings Street, Hammersmith, London W6 (01-748 0926).

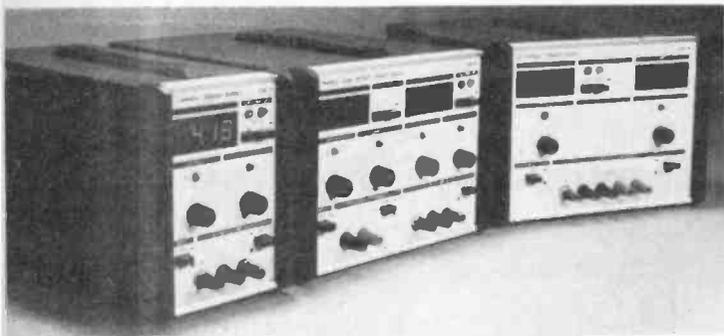

The **D Range** of power supplies from Farnell includes: the **D30-2** a 30V(2A) single output unit, the **D30-2T** a 30V(2A) dual output unit, the **D30-4** a 30V(4A) single output unit, and the **D100-1** 100V(1A) single output unit. Output voltages on all the models are variable from zero. Current control is continuously variable from 1% to 100% of maximum rated output. These models will measure external voltages (39-99V) max on 30V units and 399.9V max on 100V units). Prices, respectively are: £159.85, £313.95, £289.80 and £284.05. From **Farnell Instruments Ltd**, Sandbeck Way, Wetherby, West Yorkshire LS22 4DH (0937 61961).

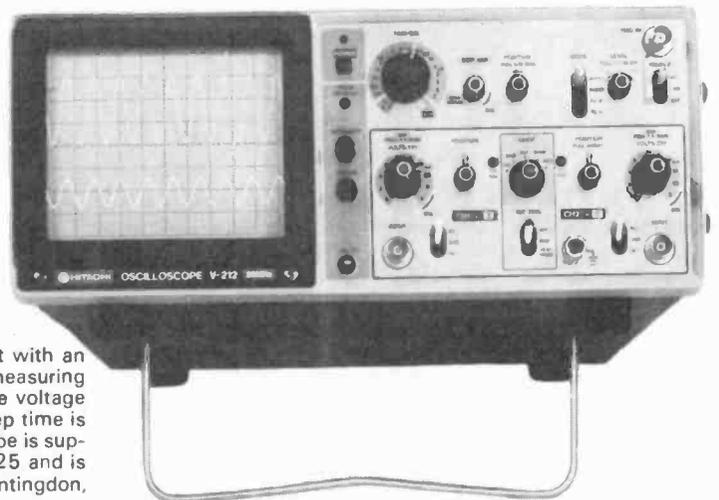

The **Hitachi V-212** 20MHz oscilloscope is a dual trace unit with an internal graticule to eliminate parallax errors when measuring waveforms. The output of channel one is provided to enable voltage measurement using an external frequency counter. The sweep time is from 0.2µs/div to 0.2s/div in 19 calibrated steps and the scope is supplied with two probes (x10). The V-212 is priced at £339.25 and is available from **Thurlby-Reltech**, New Road, St. Ives, Huntingdon, Cambs. PE17 48G (0480 63570).

FREQUENCY COUNTERS

HIGH PERFORMANCE
HIGH RELIABILITY
LOW COST

Ex-Stock Delivery


The brand new Meteor series of 8-digit Frequency Counters offer the lowest cost professional performance available anywhere.

- ★ Measuring typically 2Hz - 1.2GHz
- ★ Sensitivity < 50mV at 1GHz
- ★ Setability 0.5ppm
- ★ High Accuracy
- ★ 3 Gate Times
- ★ Low Pass Filter
- ★ Battery or Mains
- ★ Factory Calibrated
- ★ 1-Year Guarantee
- ★ 0.5" easy to read L.E.D. Display

PRICES (Inc. adaptor/charger, P & P and VAT)

METEOR 100	(100MHz)	£104.36
METEOR 600	(600MHz)	£134.26
METEOR 1000	(1GHz)	£184.86

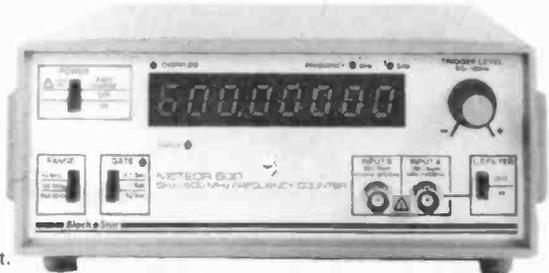Illustrated colour brochure with technical specification and prices available on request.



Designed and manufactured in Britain.

Black Star

BLACK STAR LTD (Dept. P.E.), 9A Crown Street, St. Ives, Huntingdon, Cambs, PE17 4EB, England.
Tel: (0480) 62440 Telex: 32339

HAMEG

*the source of performance
...the ultimate choice*



HM 103
Single Trace
2mV – 20V/cm
10MHz Bandwidth
Component Tester

£158

HM 204
Dual Trace
2mV – 20V/cm
20MHz Bandwidth
Algebraic Add, Invert
Variable Sweep Delay
Variable Hold Off
Peak Auto Trigger to 50MHz
X – Y
Single Shot
Z Mod
Component Tester

£365

HM 203.4
Dual Trace
2mV – 20V/cm
20 MHz Bandwidth
Algebraic Add, Invert
X – Y
Component Tester

£264

HM 605
60MHz Bandwidth
5mV – 20V Sensitivity at 60MHz
1mV Sensitivity at 30MHz
Timebase Range 5ns – 2.5s/cm
Reliable Triggering to 80MHz
Normal and Peak Value Triggering
Alternate Triggering
Variable Sweep Delay
14kV Rectangular CRT
Y – Output
1kHz/1MHz Calibrator
Component Tester

2 YEAR WARRANTY


£487

Prices U.K. list ex. VAT

For free data sheets of the full range contact:

HAMEG LTD. 74–78 Collingdon Street, Luton, LU1 1RX. Tel: (0582) 413174 Telex: 825484

The 2001 sweeps the board at only £140*

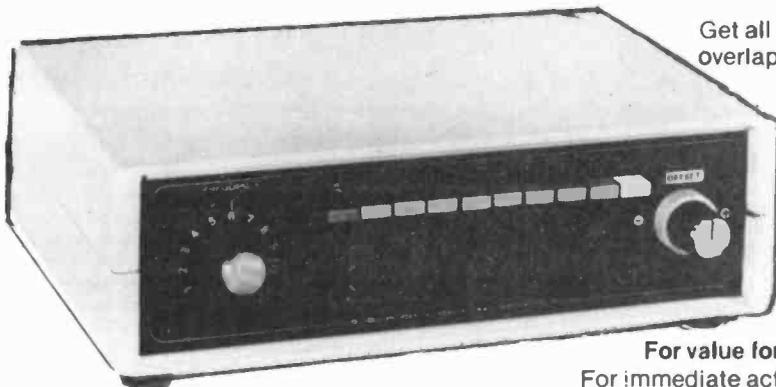

Get all the waveforms you need – 1 Hz to 0.1 MHz in five overlapping ranges: stable, low-distortion sine waves, fast rise/fall-time square waves, high linearity triangle waves — even a separate TTL square wave output. Plus high- and low-level main outputs.

An applied DC Voltage at the Sweep input can shift the 2001's frequency; or sweep up to 100: 1 with an AC signal.

A pushbutton activates the DC Offset control, which shifts the output waveform up or down on command.

For value for money the 2001 sweeps the rest off the board.

For immediate action — The G.S.C. 24 hour, 5 day a week service Tel: (0799) 21682 and give us your Access, American Express, Barclaycard number and your order will be in the post immediately or just clip out the coupon.

GOODS DESPATCHED WITHIN 48 HRS

*price excluding P&P and 15% VAT

GLOBAL SPECIALTIES CORPORATION



G.S.C. (U.K.) Limited, Dept. 5HH,
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ
Tel: Saffron Walden (0799) 21682 Telex: 81477

Global Specialties Corporation (UK) Limited Dept. 5HH,
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

Model 2001 Sweepable Function Generator	£164.45 (Inc. P&P and 15% VAT)	Qty Reqd.	For FREE catalogue tick box <input type="checkbox"/>
Name		Address	
I enclose PO/Cheque for £.....		or debit my Barclaycard/Access/American Express No	
		exp date	




The **ALT-A1 PP241** is a regulated variable power supply unit with overload protection. Simple switching enables the meter to read either voltage or current. There are two voltage ranges 0V – 12V and 12V – 24V, stability is within 0.75%. Two versions of this unit are available with different output ratings: the PP241 (1A) and the **PP243** (3A), they cost £32.20 and £48.30 respectively. Available from **Semiconductor Supplies International Ltd.**, Dawson House, 128/130 Carshalton Road, Sutton, Surrey (01-643 1126).

Global's 3002 Auto-ranging Capacitance Meter provides direct readings from 1pF to 19,999µF. A dual threshold measurement technique eliminates reading errors due to dielectric absorption. Capacitance in cables, switches and other electric components can be measured by using d.c. charging characteristics to determine true capacitance. Priced at £165.60. From **Global Specialties Corporation (UK) Ltd.**, Shire Hill Ind Est, Unit 1 & 2, Saffron Walden, Essex CB11 3AQ (0799 21682).




The **Global 1301** is a fully regulated triple-output power supply. Features include a fixed 5V (1A) output and two independently variable 5V–18V (0.5A) outputs. It is possible to link the outputs to increase the output range. Built-in current limiting circuitry protects against short circuits. The front panel meters allow current monitoring up to 1A and voltage up to 20V. Price £182.85, from **Global Specialties Corporation (UK) Ltd.**, Shire Hill Ind Est, Saffron Walden, Essex CB11 3AQ. (0799 21682).

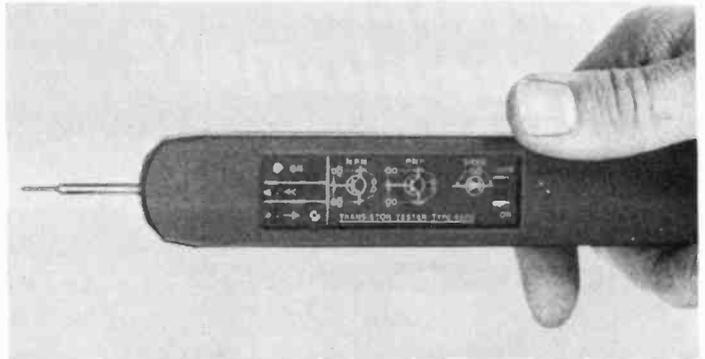

The **4500** transistor tester simplifies and speeds up the task of checking the p.n. junctions of discrete semiconductors, in or out of circuit. This lightweight hand held device features a series of l.e.d.s, which indicate the junction status. PNP or NPN transistors, diodes and open or short circuit junctions can be identified with parallel circuit values as high as 270 ohms or 33 microfarads. Price £18.40 from **Osborne Electronics**, Binstead Road, Ryde, Isle of Wight (0983 63622).



The **PR 651** is a regulated power supply, 0V to 18V at 1.5A. Both voltage and current can be read at the same time. The unit features circuit protection to minimise constant current/voltage output drift. Also available is the **PR 653**, this is a 0 to 35V at 1.5A supply with the same characteristics and features. Prices respectively are £212.75 and £228.85. From **House of Instruments**, Clifton Chambers, 62 High Street, Saffron Walden, Essex CB10 1EE (0799 24922).

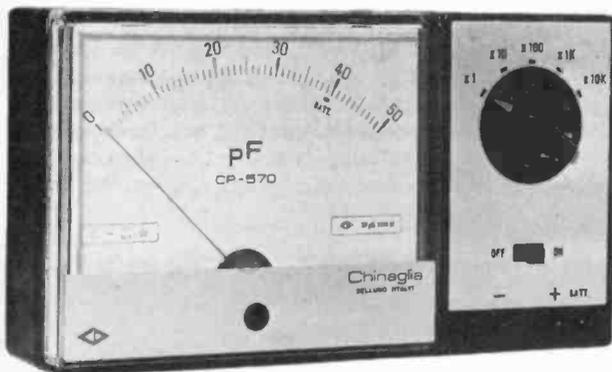

The **Chinaglia CP570** capacitance meter can accurately identify any capacitor within its range. An up to date meter suspension system is incorporated along with a shockproof ABS case. Both the test probes and the sockets in which they engage are designed to reduce contact resistance and wear. Five ranges can be set from 0 to 0.5µF, accuracy is within 3% of reading. The CP570 is priced at £51 and is available from **Alcon Instruments Ltd.**, 19 Mulberry Walk, London SW3 6DZ (01-352 1897).

A BRITISH MADE OSCILLOSCOPE AT AN AFFORDABLE PRICE


The new Bridge single and dual trace oscilloscopes.

Single beam £195 Dual trace £225

★ Send for details today ★

Agents and distributors required worldwide.

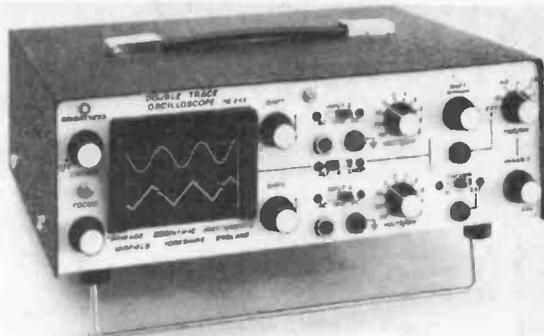Bridge Scientific Instruments
63-65 High Street, North Yorkshire BD23 1EF.
Tel: (0756) 69511 (10 lines)




Manufactured in association with Scopex Electronics Limited

Add 8 channels to your 'scope New Thurlby OM358 multiplexer £169.00 vat


The Thurlby OM358 gives any oscilloscope an 8 channel display. Observing many waveforms simultaneously can be essential when analysing sophisticated equipment. Application areas include microprocessor based products, data transmission systems, A to D converters, frequency synthesizers etc. The OM358 is ideal for digital equipment (it can often solve problems that would otherwise need a fast logic analyser) but, unlike dedicated logic test instruments, it is equally suited to analogue waveforms.

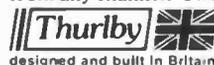The OM358 has a bandwidth of 35MHz and 3% calibration accuracy. Each input has an impedance of $1M\Omega - 20pF$ and accepts signals up to $\pm 6V$. An 8 channel, 4 channel, or single channel display can be selected with triggering from any channel. *Colour data sheet with full specifications available.*



Thurlby Electronics Ltd
New Road, St. Ives, Cambs.
PE17 4BG Tel: (0480) 63570

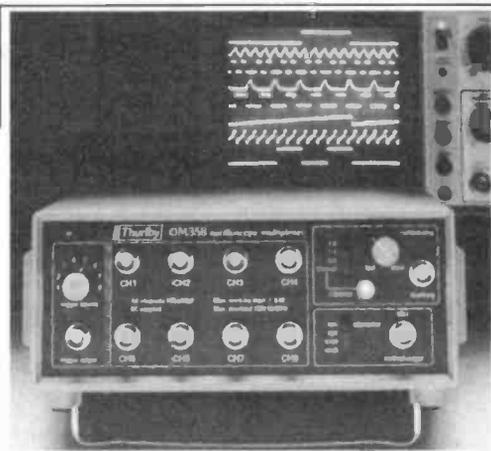OM358 with two BNC
cables £197.80
(inc P & P and VAT)



A Healthy Pulse Rate

*£160 for 0.5Hz to 5MHz



Here's a precision digital pulse generator with fast rise and fall times covering 0.5Hz to 5MHz in five overlapping ranges.

With pulse width and pulse spacing each independently variable from 100 nsec to 1 sec for an amazing $10^7:1$ duty cycle range.

You'll find the 4001 delivers the pulse modes you need: Continuous, One-Shot, Triggered, Gated, Square Wave, even a Complement mode. The Trigger/Gate input, 50 ohm variable output, TTL-level output and Sync output connectors are BNCs.

The 4001. A specification to get your pulse racing.

For immediate action — The G.S.C. 24 hour, 5 day a week service
Tel: (0799) 21682 and give us your Access, American Express, Barclaycard
number and your order will be in the post immediately or just clip out the coupon.

GOODS DESPATCHED WITHIN 48 HRS.

GLOBAL SPECIALTIES CORPORATION



G.S.C. (U.K.) Limited, Dept. 5GG,
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ
Tel: Saffron Walden (0799) 21682 Telex: 81477

Global Specialties Corporation (UK) Limited Dept. 5GG,
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

Model 4001 Ultra Variable Pulse Generator	£168.60 (inc. P&P and 15% VAT)	Qty Reqd.	For FREE catalogue tick box <input type="checkbox"/>
--	-----------------------------------	--------------	--

Name Address

I enclose PO/Cheque for £..... or debit my
Barclaycard/Access/American Express No exp date

TWO FABULOUS OFFERS FROM

ALCON

The incredible 'MINI 20'

28 ranges
20kΩ/V d.c. & 4kΩ/V a.c.
(With protective fuse)


Accuracy: 2% d.c. and resistance,
3% a.c.

28 ranges: d.c. V 100mV, 3V, 10V,
30V, 100V, 300V, 600V. d.c. 150μA,
600μA, 6mA, 600mA. a.c. V 15V,
50V, 150V, 500V, 1500V. a.c.
130mA, 300mA, 3.0A. Ohms 0-
2kΩ, 0-2MΩ. dB from -10 to +62 in
6 ranges.

Dimensions: 105 x 130 x 40mm.

The 28 ranges cover all likely re-
quirements. Operation is straight-
forward, just turn the selection
switch to the required range.

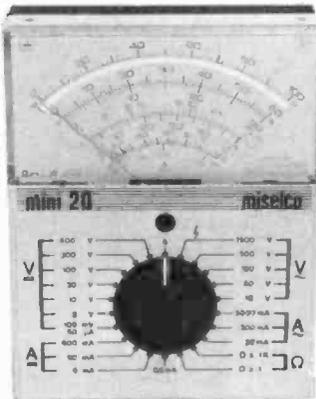This special offer is a wonderful
opportunity to acquire an essen-
tial piece of test gear with a sav-
ing of nearly £10.00.




THE IDEAL INSTRUMENT
FOR THE CONSTRUCTOR

ONLY £21.60

(complete with carrying case, leads and instructions)

'SUPER TESTER 50'

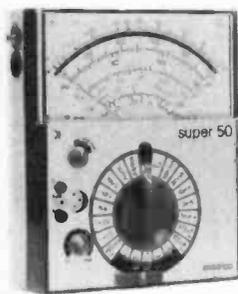THE PROFESSIONAL SOLUTION
TO GENERAL MEASUREMENT PROBLEMS



★ 50KΩ/V
AC AND DC

★ 39 RANGES

★ FOOL-PROOF
FITTED WITH PROTECTIVE DI-
ODES QUICK ACTING 1.25A
FUSE & RESETTABLE CUT-OUT

Accuracy: d.c. ranges and Ω 2% a.c. 3% (off.s.d.)
39 ranges: d.c. 150mV, 1V, 3V, 10V, 30V, 100V, 300V, 1000V;
d.c. 1 20μA, 100μA, 300μA, 1.0mA, 3mA, 10mA,
30mA, 100mA, 1A, 3A.
a.c. V 10, 30V, 100V, 300V, 1000V;
a.c. 1 3mA, 10mA, 30mA, 100mA, 1A, 3A.
Ohms 5kΩ, 50kΩ, 500kΩ, 5MΩ, 50MΩ.
dB from -10 to +61 in 5 ranges.

Dimensions: 105 x 130 x 40mm.

The best instrument for the workshop, school, toolbox, TV
shop and anywhere accurate measurement is needed quickly
and simply.

(complete with carrying case,
leads and instructions)

ONLY £36.30

PRICES Our prices include VAT and postage and goods are normally
despatched by return.

For details of these and the many other instruments in the Alcon range,
including multimeters, components measuring, automotive and elec-
tronic instruments, please write or telephone:

ALCON Instruments Ltd.

19 MULBERRY WALK · LONDON SW3 6DZ · TEL: 01-352 1897 · TELEX: 918867

HENRY'S

AUDIO ELECTRONICS

COMPUTERS • COMMUNICATIONS • TEST EQUIPMENT • COMPONENTS

VISIT OR PHONE • OPEN 6 DAYS A WEEK • ALL PRICES INC VAT

STEREO TUNER/AMPLIFIER

4 wave-band stereo tuner amplifier
by GEC. MW/LW/
SW/stereo FM radio.
10 + 10 watt stereo
amplifier. Inputs for PU
tape in/out. Supplied as two
assembled units
as illustrated **£21.95**
- easy to connect (UK C/P £1.50)

CASSETTE MECHANISMS

Filtered counter, motor, record
and erase heads, solenoid,
etc. Brand new available 6V
DC or 12V DC (state which) **£5.95** (UK
C/P £5p)

TOROIDAL TRANSFORMER

100 watts Isolation 230/240 V AC
plus 8-0-8V 4A 15-0-15V 0.645A 30V
0.16A Size approx 4 1/2" dia. x 1 1/2" **£7.95** (UK C/P 75p)

ASTEC UHF MODULATORS

UK UM1 233 cased for computers, etc. **£3.50** C/P 40p

MULLARD MODULES

UK C/P 65p per 1-3)
LP1171 IF and LP1179 AM/FM Tuner **pr £5.75**
LP1186 Varicap Tuner **£5.00**
LP1157 AM Tuner **£2.50**

PRESTEL ADAPTOR

3 card set
with data etc (P/S +/-12V
and +5V) **£69.95** inc. VAT

MODEM CARD

BT approved ready assembled
unit with data and
accessories. **£29.95** inc. VAT

QWERTY KEYBOARDS

+5V and -12V suitable
P/S **£8.95**
c/p 60p
69SD5
Exclusive Special
Purchase compact half effect: 64 keys plus 5 function
keys -ve/+ve strobe ASCII but all definable, steel
frame all facilities UK c/p £1.00 **£35.00**

69 key ASCII. General purpose, steel plate
Redefinable output, +5 and -12V supply, neg. strobe
pulse, 4 user definable keys,
shift & control key, etc. **£42.95**
(UK C/P 85p)

I.T.T. 2020 CABINET

Professional
Computer Case
18" x 15 1/2" x 4 1/2"
(front sloped). As previously advertised.
£27.50 inc. VAT (UK C/P £2.50)

THERMAL MATRIX & LINE PRINTER

**NEW LOW
PRICE**

COMPLETE WITH FULL HANDBOOK, 3 ROLLS PAPER
(UK post etc £1.05)
(List approx £187)
£49.95 inc. VAT
SUITABLE FOR TANDY • BBC • ORIC • NASCOM • GEMINI •
ACORN • NEW BRAIN • DRAGON • etc. etc. (interface unit
with leads £13 - state model). (Your enquiries invited)

STOCKISTS FOR Frequency counters - Signal generators
Power supplies - Plus huge range of components, tools,
accessories and parts for callers -
Send large SAE for leaflets (state items)

ORDER
BY
POST
OR
PHONE.



HENRY'S Shop at
404-406 Edgware Road, London, W2
Computers 01-402 6822 Equipment 01-724 0323
Components 01-723 1008

AUDIO ELECTRONICS Shop at
301 Edgware Road, London, W2
Test Equipment, Audio Communications 01-724 3564

Details
any model
send S.A.E.

All mail to
Cubegate Ltd
1st floor,
406 Edgware Road,
London, W2 1ED

DIGITAL MULTIMETERS

Hand Held Models
All feature AC/DC volts,
DC Amps (Many with
AC Amps) Ohms etc.
(UK C/P 65p)

Controls S = Slide
R = Rotary PB = Push Button

K025C ■ 12 range 0.2A DC 2 Meg ohm (S) **£26.95**
K030S ■ 14 range 10A DC 2 Meg ohm (S) **£27.95**
K030C ■ 26 range 1A AC/DC 20 Meg ohm (R) **£33.50**
METEX 3000 ■ 30 range 10A AC/DC
20 Meg ohm (R) **£37.95**
6010 ■ 28 range 10A AC/DC 20 Meg ohm (PB) **£37.95**
K055C ■ 28 range 10A AC/DC 20 Meg ohm (R) **£39.95**
K0615 ■ 18 range 10A DC 2 Meg ohm
plus HFE tester (R) **£39.95**
7030 ■ As 6010 but 0.1% basic (PB) **£47.50**
OM3350 ■ Autorange plus Cont. Tester
18 ranges 10A AC/DC 2 Meg ohm (R) **£49.95**
Bench Models (UK C/P £1.00)
TM355 3 1/2; Digit 29 range LEO 10A AC/DC
20 Meg ohm **£97.75**
TM356 3 1/2; Digit 27 range LEO 10A AC/DC
20 Meg ohm **£109.25**

GENERATORS

(UK C/P £1.00)
LS617 RF 100KHz to 150MHz
(Up to 450MHz Harmonic) **£109.25**
SG402 RF 100KHz to 30MHz **£82.80**
A6202A Audio Sine/Square 20Hz to 200KHz **£102.35**
LAG27 Audio sine/Square 10Hz to 1MHz **£106.95**

MULTIMETERS

(UK C/P 65p)
MC6015 15 range pocket 10k/Volt **£8.50**
M200 30 range 20k/Volt. Many features
20KHz (list £21.85) **£9.95**
HM102BZ 22 range 20k/Volt 10A
DC Plus cont Buzzer 10 Meg ohm **£13.50**
TMM500 23 range bench 30k/Volt De Luxe,
12A DC, plus cont. Buzzer, 20 Meg ohm
MM56R 22 range 10k/Volt 6 Meg ohm
B30A 25 range 30k/Volt 10 AC/DC
10 Meg ohm **£23.95**
VM360TR 19 range 20k/Volt plus HFE tester
1 Meg ohm **£13.95**
ST303TR 22 range 20k/Volt plus HFE tester
12A DC 1 Meg ohm **£17.95**
KRT5001 Range doubler 35 ranges
50k/Volt 10A DC 20 Meg ohm **£19.95**

HIGH VOLTAGE METER

Direct reading 0/40 kV.
20k/Volt. **£25.30** (UK C/P 65p)

DIGITAL CAPACITANCE METER

(UK C/P 65p)
0.1 pF to 2000 mfd LCO 8 ranges
DM6013 **£59.95**

TRANSISTOR TESTER

Meter reading NPN/PNP Hfe and leakage
also diode test **£26.95** (UK C/P 65p)


OSCILLOSCOPES

Specifications any model.
send SAE.
Single Trace (UK C/P £3.50)

3030 15MHz 5mV plus components
tester (Crotech) **£177.10**
HM103 10MHz 2mV plus components
tester (Hameg) **£181.70**
SC110A • 10MHz battery portable
(Thandar) **£189.75**
• Carry case £6.84 AC Adaptor £7.99.
Dual Trace (UK C/P £4.50)
CS1562A 10MHz with 2 probes (Triol)
HM203 20MHz plus components tester
(Hameg) **£303.60**
3132 20MHz plus component comparator
(Crotech) **£325.45**
CS1566A
20MHz with 2 probes (Triol) **£374.90**
HM204 20MHz sweep delay plus component
tester (Hameg) **£419.75**
V212 20MHz with 2 probes (Hiachi) **£385.25**
V203F 20MHz sweep delay with 2 probes
(Hiachi) **£431.25**

OPTIONAL PROBE KITS
X1 - £7.95, X10 - £9.45, X1/X10 - £11.50.


TEST INSTRUMENTS buyer's guide

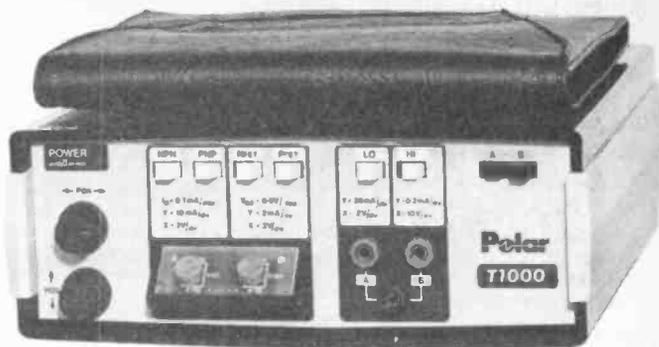

Polar T1000 converts a standard oscilloscope into an in-circuit component tester/curve tracer. It features automatic plotting and comparison of semiconductor characteristics. Produces a Lissajous signature for any combination of component elements, be they capacitive, inductive, and/or resistive. Allows swift comparisons and trouble shooting of unpowered boards, possibly without knowledge of the circuit. Usage is as much an art as a science, with applications yet to be discovered. Oscilloscope must have timebase switch-off with X input. Price £373.75. Available from **Antron**. (0428 54541). Note: Antron is offering a £50 discount on submission of a "Bazaar" coupon as proof of PE readership.



Hy-Trak 100D high resolution digital meter for p.c.b. short circuit location and measurement of resistances below the range of standard multimeters ($20\text{m}\Omega$ f.s.d.). Audio tone or meter reading indicates the position of the short. Has d.c. injection facility to prevent decoupling capacitors from introducing a "false short," and the Hy-Trak range ensures that shorts between voltage planes are detected. Price £249.17 (£224.25 c.w.o.). Available from **Omnitest Ltd.**, Highcliffe House, 411-413 Lymington Rd., Highcliffe, Christchurch, Dorset BH23 5EN. (04252 77731)

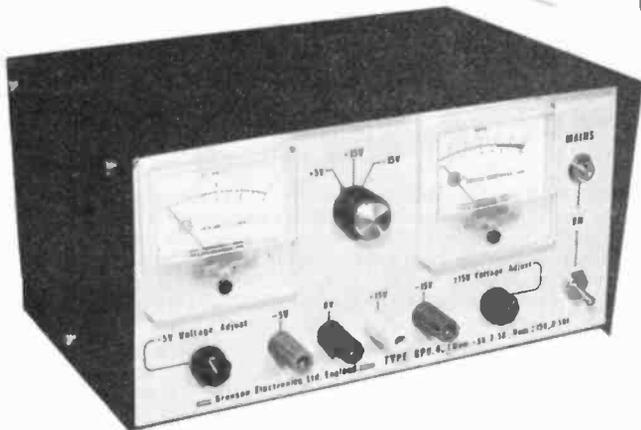


Grenson BPU-4 bench power supply has three variable outputs: +3 to +8V @ 2.5A +8 to +16V @ 500mA and -8 to -16V @ 500mA. Outputs are highly stabilised and fully protected against long term overload, short circuits and the injection of an external voltage. Voltage and current are independently monitored. Price £59 kit (£98 assembled). Available from **Grenson Electronics Ltd.**, High March, Daventry, Northants N11 4HQ. (0327 705521)




Digimax 500 series frequency counters offer an accuracy of 1 p.p.m. Measuring only $135 \times 128 \times 40\text{mm}$ separate models cover ranges of 10Hz to 512MHz and 50Hz to 1GHz with resolutions of 1Hz and 10Hz respectively. Powered by rechargeable battery pack or mains adaptor. Input sensitivities of 15 to 50mV at input impedance of 50 Ω . Price £217.35 (model D-510 shown). Available from **Aspen Electronics Ltd.**, 2-3 Kildare Close, Eastcote, Ruislip, Middlesex HA4 9UR. (01-868 1188)

Polar Toneohm 580 is a sensitivity adjustable current tracer which can "sniff" out short circuits and partial shorts (up to 200 Ω) with a non-contact probe. Source and sink clips introduce a safe current path through the populated, but unpowered board under test. A pitch variable whistle gives audible indication of the short's proximity. The 580 can also isolate faulty i.c.s. Price £193.20. Available from **Antron Electronics**, Hamilton House, 39 Kings Rd., Haslemere, Surrey GU27 2QA. (0428 54541). Note: Antron is offering a £25 discount on submission of a "Bazaar" coupon as proof of PE readership.



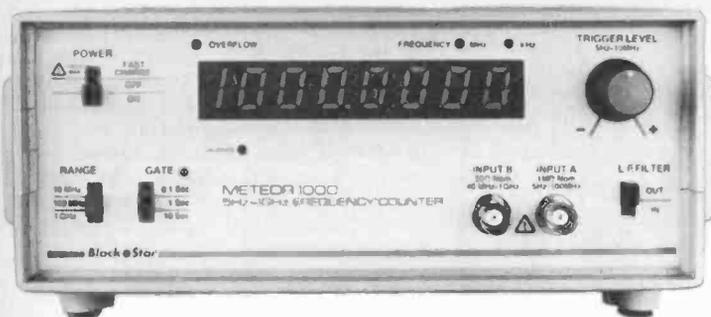

Meteor 1000X 5Hz to 1GHz precision frequency counter has temperature compensated crystal. Sensitivity is $<50\text{mV}$ at 1GHz. Stability is ± 0.5 p.p.m. at -10°C to 40°C with aging at ± 1 p.p.m. per year, and stability of ± 0.2 p.p.m. Battery or mains powered. Trigger level control. Three gate times: 0.1 sec, 1 sec and 10 sec. Price £258.75. Available from **Black Star Ltd.**, 9A Crown St., St. Ives, Huntingdon, Cambs PE17 4EB. (0480 62440)

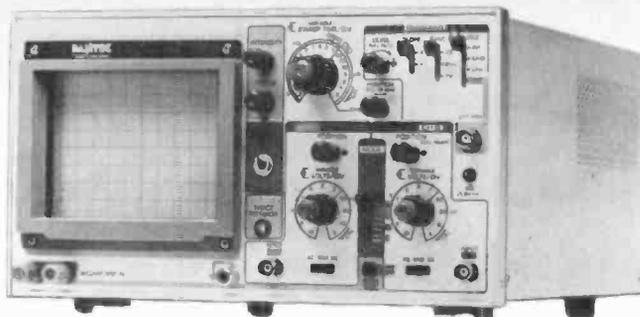

Pantec PAN8022 is a 20MHz dual trace oscilloscope with built-in component tester. Incorporates add and invert, alternate or chop (@ 200kHz). There are 12 ranges in 1-2-5 steps with fine control. Maximum input voltage of 300V. Timebase linearity better than 3%, with X5 magnifier. Ranges from 0.2 $\mu\text{s}/\text{div}$ to 0.5s/div on 20 ranges. Includes intensity modulation. Component tester generates 9V a.c. at 2mA max. (source resistance 4k Ω). Price £447.35. Available from **Pantec Divn., Carlo Gavazzi (UK) Ltd.**, 162-164 Upper Richmond Rd., Putney, London SW15 2SL. (01-785 9022)




Linstead S3 HT/LT bench PSU has 0-300V (@ 60mA) and 0-30V d.c. (ripple = 100mA). Also incorporates two isolated 6.3V @ 2A heater supplies. The PSU is fully protected against overload and short circuit by a variable trip. Voltage outputs monitored by switched meter. Price £140.30. Available from **Supercat Electronics Ltd.**, PO Box 201, St. Albans, Herts AL1 4EN. (0727 62171)




Levell TG302 function generator can generate triangle, square, sine, pulse and ramp waveforms from 0.02Hz to 2MHz in 7 ranges. It provides 20V p.p. from a 50 Ω source with variable offset. TTL output. External sweep over three decades. Built-in frequency counter to 10MHz. Price £155.25. Available from **Levell Electronics Ltd.**, Moxon St., Barnet, Herts EN5 5SD. (01-440 8686)



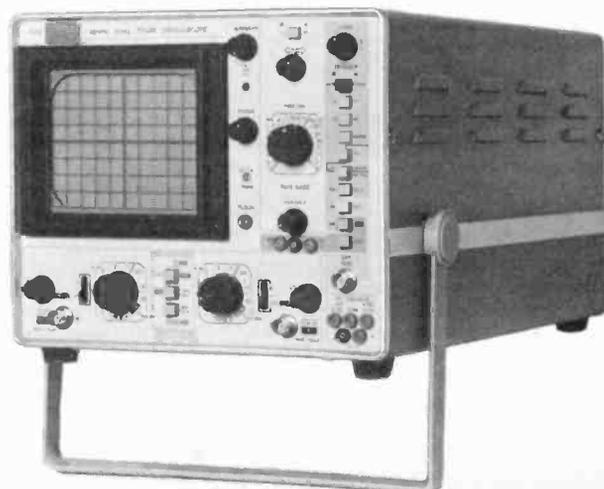Altai PP154 variable stabilised PSU with overload protection, ranges from 5-15V d.c. output at 4A. Stability is 0.1% with ripple confined to 5mV. Meter reads voltage or current (switched). Price £46. Available from **Semiconductor Supplies International Ltd.**, Dawson House, 128/130 Carshalton Rd., Sutton, Surrey SM1 4RS. (01-643 1126)



Crotech 3132 oscilloscope incorporates a semiconductor and passive component tester and component comparator for checking against known standards. This dual trace (Alt or Chop) oscilloscope can also check complete circuits using signature techniques. It includes a mini PSU: +12V, -12V @ 200mA and 5V @ 1A. Basic scope bandwidth is d.c. to 20MHz with a maximum speed of 40ns/div. Price £325.45. Available from **Crotech Instruments**, 5 Nimrod Way, Elgar Rd., Reading, Berks RG2 0EB. (0734 866945)

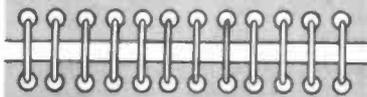

INDUSTRY NOTEBOOK

By Nexus



Productivity

I remember some years back, when hand-held digital multimeters were just becoming popular, being amazed to find on a factory visit that the production line was just two girls and three youths. The two girls 'stuffed' the p.c.b.s with components. The assembled p.c.b.s then went off to a flow-soldering machine and returned to the three youths who tested, calibrated and cased the instruments. Throughput was 100 instruments per 8-hour shift with a then retail value of about £100; so we might estimate an ex-factory unit value of £50, or £5,000 per shift, giving £25,000 per 5-day single shift week, say £1.2 million per working year.

The 'secret' of the low labour-cost was in clever design by production engineers. As well as being simple to make, the work was also de-skilled. The girls were guided by light beam where to mount each component, the technicians testers aided by automatic test equipment. Since those early days a number of look-alikes have appeared forcing the price down to less than half. As they became more popular so volume would have increased, making automatic component insertion economically viable.

I was reminded of this experience by what I confess is only a third-hand (via a friend of a friend) report of a visit to Japan where the itinerary included a visit to a large factory devoted to the manufacture of video recorders. The figures are hard to believe and may have been distorted in the telling. Throughput of this factory was 500,000 units a month. There were 250 production engineers beavering away in offices on the periphery of the production area, where only 17 operators handled the whole production which, one must assume, was as fully automated as modern technology would allow.

This, however, is not the end of the story. Production engineers, ever in search of lower assembly costs, are pushing hard for

an emerging technique called surface mounting. This calls for component with lead forms which contact solder pads on the track side of a p.c.b., making through-holes unnecessary. Similarly, the multi-way connectors may be surface-mounted and designed to be clamped or soldered to the p.c.b. tracks, the clamp design permitting separable connection without de-soldering. The hold-up at the moment is that the whole range of components is not yet available for surface mounting, but few doubt that it must come. *This technique was featured in the article SO/SMD's, by M. Abbott, in the May '84 issue of PE.*

Another promising new production technique is to switch from conventional laminated p.c.b.s to injection-moulded substrates using polymides as a material which has the necessary mechanical, chemical and electrical characteristics. Among its advantages are that all holes can be moulded in, thus eliminating all drilling, the ability to mould-in three-dimensional features such as structural ribs or stand-off pillars, and no scrap material because scrap can be melted and re-processed. Because of the high tooling costs, production runs should ideally be at least 100,000 units, but cost savings could amount to 30 per cent.

Robots

Britain's robot population increased by over 50 per cent in 1983, according to statistics from the British Robot Association. At the year end the number was 1,753, but the predicted growth in use of robots is for at least 3,000 by May next year. Even so, Britain still lags behind the USA, Japan, West Germany, Sweden, France and Italy.

The most popular applications are in injection-moulding, spot-welding and arc-welding, but with increasing sophistication the number employed on assembly work is increasing. Biggest impact of the robot revolution is in the automotive industry, where robots have had a significant effect on the number of people employed on production lines.

Experience in the electronics industry in the USA is that few people, if any, have been displaced by robots, although those at work have been re-allocated to new tasks in the factories. This is most probably because the electronics market is still growing, whereas the automotive market is near saturation. Applications in electronics have been mainly in highly repetitive jobs which are boring to human operators, particularly in some stages of p.c.b. manufacture. Robots for electronics assembly are still in the research stage, but we may expect them soon to be on production lines loading components, handling loaded boards, soldering, and final testing.

Reports from leading electronics companies in the USA are that robots are providing productivity gains of up to 300 per cent with improved quality of product. And, whereas to remain competitive some companies had to farm out some operations to cheap labour areas in the Far East, such work can now return to in-house in the home country.

Tartan Spring

Hard on the heels of Scotland winning the Triple Crown (for overseas readers it is a Rugby Football honour last won by Scotland 46 years ago) came news that National Semiconductors were to back Scotland with a further £100 million of investment which, with existing investment by other electronics companies, makes Scotland one of the fastest growing sunrise industry areas in Europe. What is especially welcome is that National's plan is not for just another off-shore assembly plant but a pioneer in use of the 6-inch wafer and all that goes with it. The only pity is that of the 1,000 new jobs to be created, very few are suitable for the horny-handed workers being laid-off in nearby shipyards.

In the Edinburgh area, Hewlett-Packard are expanding with a new microwave facility on top of the big expansion at South Queensferry last year. H-P has doubled turnover since 1980 in UK-based operations, and productivity measured in sales per employee is running at over £83,000. Present plans forecast an increase in the labour force of 700 in the foreseeable future.

Sweethearts

Since I last mentioned the role of trade unions we have had the GCHQ rumpus which quickly faded from the scene as the miners sprang into militant action.

What has passed almost unnoticed during the torrents of press and TV coverage is the continuing emergence of what have been dubbed sweetheart deals, an agreement for no strikes freely entered into between management and unions.

For this new development we have to thank the Japanese, who as part of the bargain for setting up plants in the UK, notably in South Wales, insisted on a single union rather than a multiplicity to represent the workers. With declining membership and influence the unions are all too anxious to move into new enterprises, and union rivalry provides an element of competition which results in union concessions with winner takes all.


Experience so far indicates that a single-union workforce makes for a happier environment. If nothing else, it cuts out inter-union squabbles over who does what and for how much. The first purely British company in the electronics industry to adopt a single-union policy is probably Inmos. I have heard of no other so far. At the old Philips factory at Lowestoft, now taken over by Sanyo, the former seven unions have been replaced by one, and it seems to work. There is much greater flexibility in work practices, greater co-operation between management and labour, greater harmony and more understanding.

Spearheading the new movement is the electricians' union, a progressive body interested more in members' welfare than in grabbing headlines and TV coverage. Togetherness, in their view, is preferable to futile confrontation which helps nobody.

HYPERCHASER

Lighting Effects Unit

PETER NEWBURY

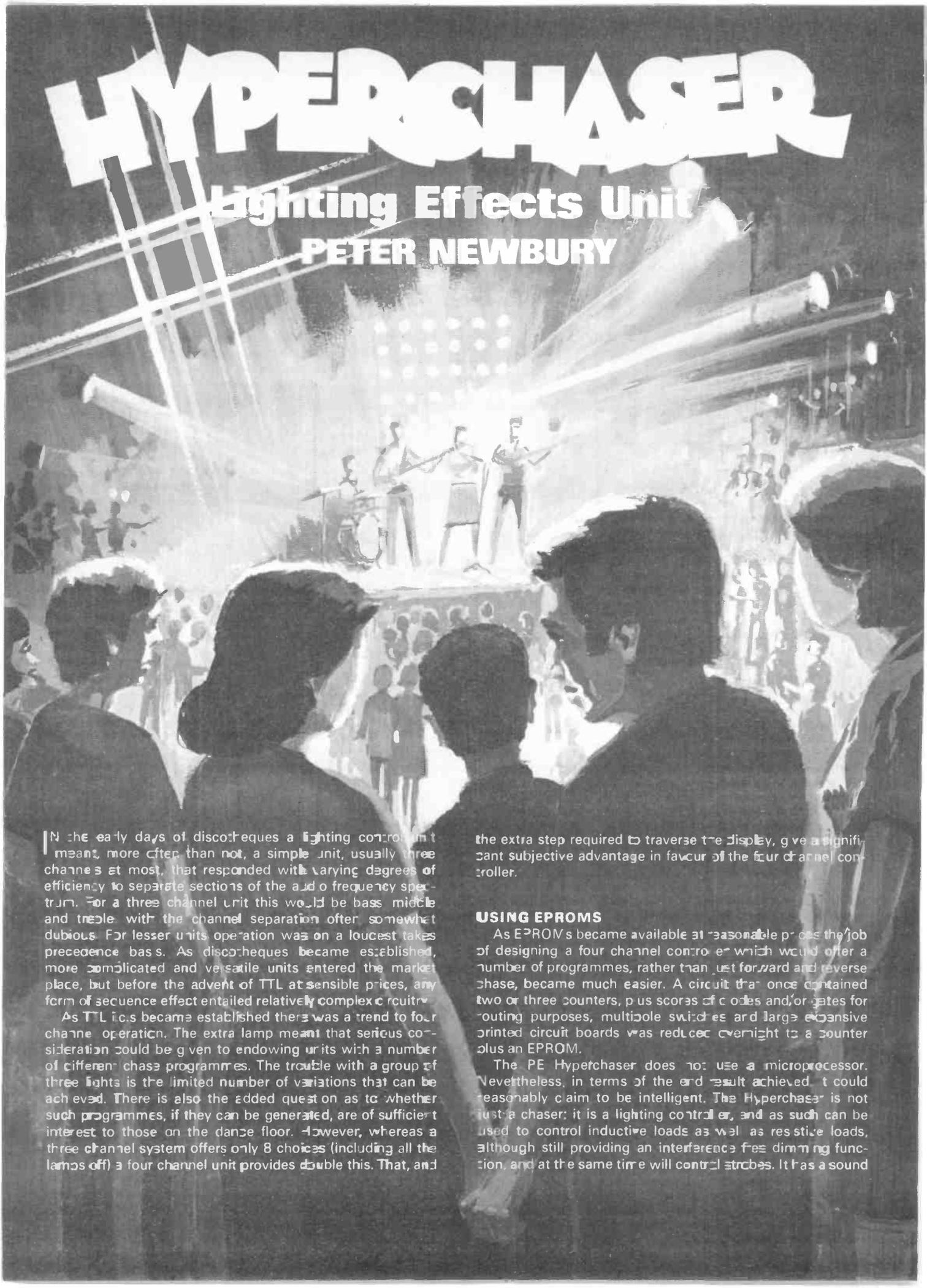

In the early days of discotheques a lighting control unit meant, more often than not, a simple unit, usually three channels at most, that responded with varying degrees of efficiency to separate sections of the audio frequency spectrum. For a three channel unit this would be bass middle and treble with the channel separation often somewhat dubious. For lesser units operation was on a loudest takes precedence basis. As discotheques became established, more complicated and versatile units entered the market place, but before the advent of TTL at sensible prices, any form of sequence effect entailed relatively complex circuitry.

As TTL i.c.s became established there was a trend to four channel operation. The extra lamp meant that serious consideration could be given to endowing units with a number of different chase programmes. The trouble with a group of three lights is the limited number of variations that can be achieved. There is also the added question as to whether such programmes, if they can be generated, are of sufficient interest to those on the dance floor. However, whereas a three channel system offers only 8 choices (including all the lamps off) a four channel unit provides double this. That, and

the extra step required to traverse the display, give a significant subjective advantage in favour of the four channel controller.

USING EPROMS

As EPROMs became available at reasonable prices the job of designing a four channel controller which would offer a number of programmes, rather than just forward and reverse chase, became much easier. A circuit that once contained two or three counters, plus scores of codes and/or gates for routing purposes, multicoile switches and large expensive printed circuit boards was reduced overnight to a counter plus an EPROM.

The PE Hyperchaser does not use a microprocessor. Nevertheless, in terms of the end result achieved, it could reasonably claim to be intelligent. The Hyperchaser is not just a chaser; it is a lighting controller, and as such can be used to control inductive loads as well as resistive loads, although still providing an interference free dimming function, and at the same time will control strobes. It has a sound

operated facility, and is capable of sequence operation on four, three, two or even one channels.

The controller is of compact size, being $5\frac{1}{4}$ " high, in keeping with standard rack practice. It is less than the standard 19" wide for those who are not rack mounting equipment but can obviously still be rack mounted if the occasion demands. It is particularly slim, only $2\frac{1}{4}$ " behind the front panel, and the front panel layout is simple, with a single row of keyboard switches, two rotary controls, and a mains on/off switch. Power handling on normal resistive loads, including tungsten lamps, which are the most common, is 750W/channel, limited by the mains capability for a 13A plug. This should be derated to 500W/channel for tungsten halogen lamps, which have much lower cold resistances and similarly for inductive loads where dV/dT considerations exist.

There are ten keyboard switches in all, some having double functions. Starting with the righthand four switches, these provide, in the absence of the operation of other switches, a manual flash function. The operator can depress any or all of these switches to provide a momentary or sustained flash on the channels in question. Incorporated at the top of each switch is a l.e.d. channel output indicator. The flash switches override the sequence. The sequence itself is controlled by the top of the two rotary controls. At the lowest setting the sequence is disabled. Rotating the control clockwise brings the sequence effect into being with increasing speed as the control is rotated. This "Sequence Disabled" setting allows the unit to be used purely for ambient lighting control, if so desired.

HOLD AND DIM

To the left of the manual flash switches are the hold and dim switches. If the hold switch is depressed at the same time as a channel switch or switches, the channel/s in question are switched on permanently, or at least until the process is repeated. If the manual flash button is depressed on its own whilst that channel is in the hold mode, the channel will flash off, rather than on as before—a useful effect. When any channel is placed on hold, the memory is informed accordingly and selects a suitable group of programmes from its repertoire for the remaining channels. Thus, no matter whether one, two, or for that matter, three channels are on hold, the remaining channels present programme information that makes visual sense. The memory holds sixteen 4 channel programmes, 8 three channel programmes, four two channel programmes and two rates of flash for single channel operation. Used thus, the controller can provide ambient lighting, can work into other than four channel display configurations and is generally pretty flexible. The dimming function has been nicknamed "Shimmer Dimmer". With today's discos using a variety of light sources such as pinspots which, using a low voltage lamp, incorporate a transformer, any truly versatile controller must be able to work into inductive loads. Since a transformer is decidedly unhappy when presented with d.c., it is important to ensure that a proper a.c. waveform leaves the controller. This affects output stage design as will be discussed later in the article, and also means that a popular method of dimming, that of blocking alternate half-cycles, is definitely not on. The Hyperchaser dimmer works by allowing every other complete cycle of power to leave the unit, presenting any transformers that comprise the load, or part of the load, with a.c., albeit interrupted a.c. As with the half-wave method, a degree of flicker is introduced. This is actually quite pleasant when used as part of a kinetic effect, and is useful to balance

lamps of unequal brilliance, or simply to *tone-down* the overall brightness of a display.

Anyway, the Shimmer Dimmer function works as for the hold function. Holding down the dimmer switch and simultaneously depressing any of the channel switches will dim that channel. Repeating the process will restore the channel to full output.

To the left of the Hold and Dimmer switches are the Manual and Auto Programme selection switches. These are self explanatory, the Manual switch advancing to the next programme when depressed, and the Auto switch when operated, making the change at the end of each programme run.

Carrying on to the left is the audio switch. The audio input is very sensitive, less than 100mV, and can thus be run direct from a mixer. It will however handle the output voltage of amplifiers up to 200 watts quite happily. Rather than the normal audio chase effect where the pulses derived from the beat of the music are used to trigger the sequence along, necessitating that the initial sequence speed be set fairly low, the audio effect on the Hyperchaser is called audio halt. As the name implies, the beat derived pulses are used to *stop* the sequence clock in its tracks. This has two advantages over the conventional method. Firstly, there is no need to adjust the sequence speed every time the audio effect is selected, or, for that matter, to incorporate circuitry to remove control of speed from the operator whenever the audio switch is depressed, reverting to a preselected speed. Secondly, the sudden arresting of the sequence in time with the beat of the music is very effective, if the pun may be pardoned, and certainly subjectively better than the other option.

CIRCUIT DESCRIPTION

The unit was designed around the 2716 single rail 16K memory. At the time of writing the article I was warned that this device was being phased out in favour of the 2732, which has twice the capacity. There is no problem using the 2732 instead, and, at present, the 2716 is still cheaper than the 2732.

PSU, CLOCK AND CIRCUITRY

This includes the 25Hz signal which is derived for the dimming function and the zero-voltage pulse circuitry (see Fig. 1). The power supply is a simple bi-phase arrangement, using D1 and D2. However, instead of feeding the output of these two diodes directly to the 5 volt regulator, IC1 (7805), the 100Hz waveform is fed to the smoothing capacitors, C1 and C2, through D3 and fed to TR2. This results in a positive pulse at the collector of TR1 every time the input to D1 or D2 drops below about 1 volt. When the collector of TR2 goes negative again, TR3 is biased hard off for a very short period decided by the combination of R31 and C9, again producing a positive pulse but this time much narrower and better defined. This pulse is used to clock IC17a, half of a 4027 dual JK flipflop, producing a 50Hz output from the 100Hz input. That output is again divided by the second half of IC17, resulting in a 25Hz waveform. The output of TR3 also switches TR4, when on for that brief period, pulls a 47k resistor connected to pin 5 of the 555 timer, IC19, to ground potential. This has the effect of reducing the threshold voltage of the timer for that instant. Figs. 2a, b, and c show the waveforms at the rectifiers, TR2 and TR3 respectively, whilst Fig. 2d shows the threshold voltage of IC19 superimposed on the timer capacitor waveform. The waveform shown corresponds to the highest sequence speed attainable on the unit, with the speed control at maximum and

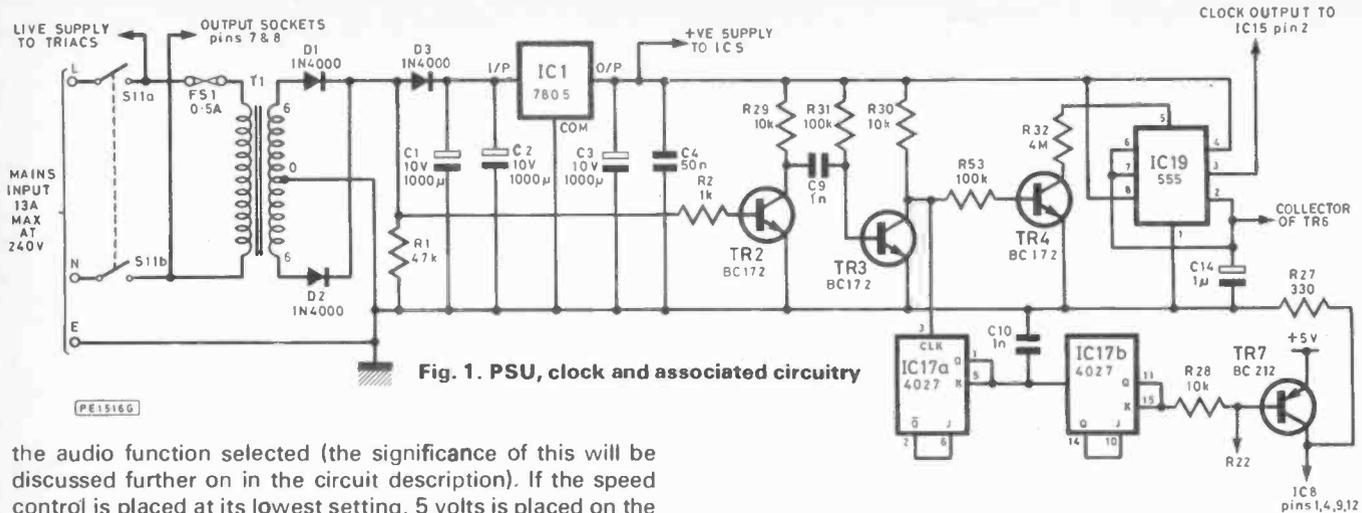


Fig. 1. PSU, clock and associated circuitry

the audio function selected (the significance of this will be discussed further on in the circuit description). If the speed control is placed at its lowest setting, 5 volts is placed on the \overline{OE} input of the 2716 and this disables the sequence, leaving the flash, hold and dim functions unaffected. Because the internal potential divider deciding the 555's threshold voltage consists of three 5k resistors in series, with the junction of the top and middle resistors defining the threshold voltage; e.g. normally $2/3$ the supply voltage, the effect of the 47k resistor R32 being grounded is to lower the threshold voltage by about 7%, ignoring the saturation voltage of TR4. If the voltage on the timing capacitor C14 is sufficiently high that within the next half cycle of the mains input it would reach the threshold voltage and trigger pulse at the output, thus changing the state of the counter and, further along the line, the memory, then it is also high enough to exceed the short term reduced threshold voltage that corresponds with the pulse from TR3. Thus, the timer will only produce an output pulse and the output stage will only change state at the nominal zero crossing point. I say nominal, because this point is in truth after the zero crossing point, but in practice not so far that it causes even the least hint of interference problems. If the purist wished, he could include a capacitor on the base of TR2, to ground, add a preset potentiometer (say 10k) in series with R2, reduce R1 to 1k and then set the unit up with an oscilloscope to give truly accurate zero-crossing switching, at the end of the half cycle, but whether this is worthwhile is highly debatable.


The output of the second JK flipflop is fed to TR7 which acts as a buffer, supplying the 25Hz square wave to IC8. An override signal from the strobe selection switch circuitry also connects to TR7's base. Again, more in a moment, but suffice it to say that the dimming function must be cancelled when the strobe function is selected in order to preclude a series of pulses, rather than one pulse, being fed to the strobe outputs with each change of state of the output.

FLASH, HOLD AND DIM FUNCTIONS

We will deal with channel one as an example, since all four channels are identical (see Fig. 3). All i.c. sections are numbered and reference to the component layout, Fig. 5, will simplify identification of the physical route through the unit of a particular channel.

Taking the output stage first, this consists of a buffered NAND gate, IC18a (7437). This sinks enough current for the MOC3020 opto triac that isolates the low voltage circuitry from the output stage and also for the indicator i.e.d. D4. A further feed from the output of IC18a goes to the strobe output NOR gate IC16c, but since this is a 74C02 and therefore a CMOS device its input requirements may be ignored. The anode of the opto triac IC23 (MOC3020) is returned to sup-

Fig. 2. Graphs of zero voltage circuitry etc.

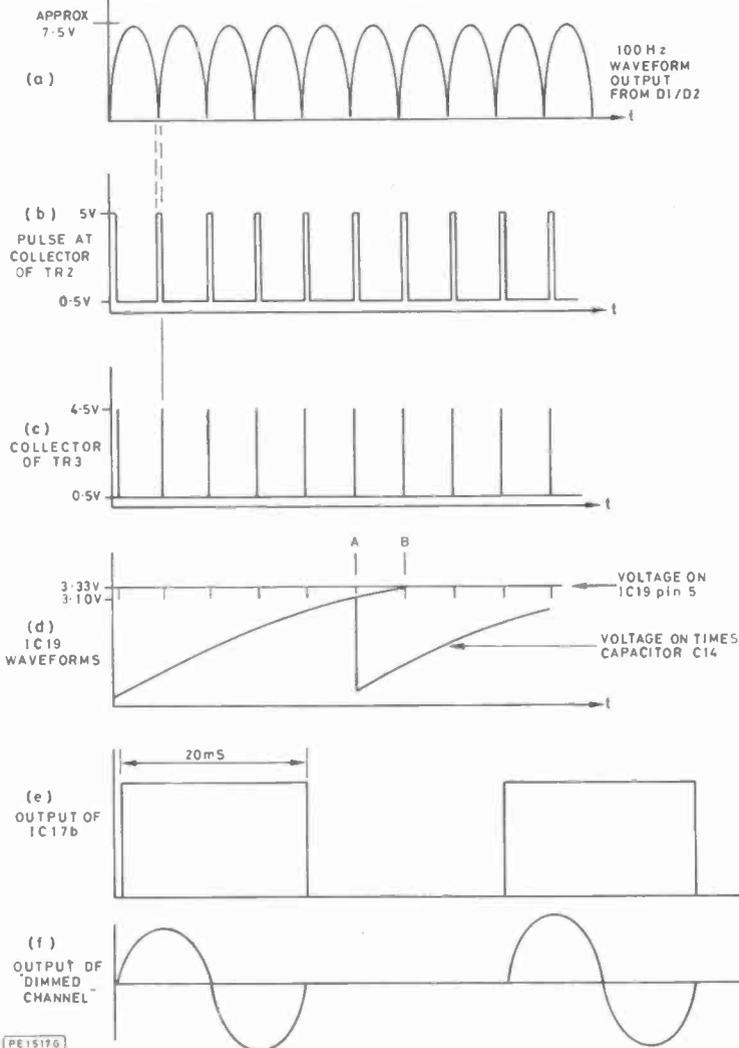

ply, in common with its three counterparts IC20-22, via TR1. TR1 is switched off by operation of the Strobe switch, thus disabling the output stage, and extinguishing all lights except the strobes. For an output from channel 1, both inputs of the NAND gate must be high. One input derives from the dimming circuitry and the other from the signal path.

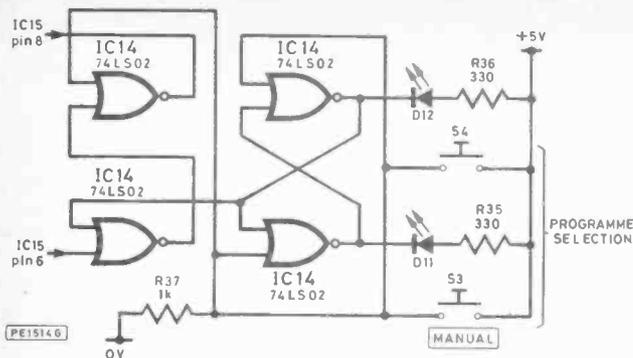


Fig. 3(b). Programme selection

With the channel not on hold, the EXOR gate will have a '0' on both inputs and operation of the channel button on its own will result in a high output from the EXOR gate and corresponding switching of the NAND buffer. When the Hold function is selected, there is already a '1' on one input of the gate; operating the channel button will result in a '1' on both inputs of the EXOR and thus a '0' on the output. In this manner the channel can be made to flash off when on Hold, providing the Invert Flash function.

If the Dim button and the channel button are depressed, the output of IC3c, the second AND gate, goes high and clocks IC7a, the second half of the 4027. The \bar{Q} output of IC7a had been high and was therefore keeping the output of

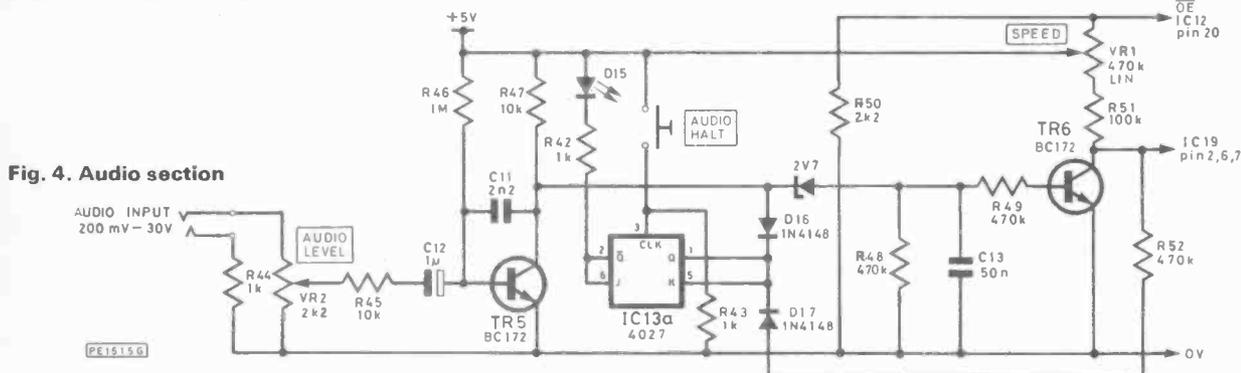


Fig. 4. Audio section

Proceeding to the beginning of the circuitry for channel 1, the Flash/Hold/Dim switch, S7 connects to one gate each of the two input AND gates IC3b and IC3c, and also to the input of an EXOR gate IC10d (74LS86). The remaining inputs of the AND gate are commoned to their neighbours on the other three channels and taken to the Hold and Dim switches respectively. If the Hold switch is depressed at the same time as the channel 1 button, then the output of the AND gate IC3b goes high, and IC7b, half of a 4027 JK flip-flop, changes state. The '1' output is fed to the other input of the EXOR gate. With the switches released, the output of the EXOR gate is high and this is fed via the 2 input OR gate IC11c (74LS32) to the NAND buffer mentioned above. At the same time, the \bar{Q} output of IC7b is taken to one input of the four input NAND gate IC9b (74LS20) whose output promptly goes high and is used to provide an indication that the Hold function has been selected. The \bar{Q} output also goes to an input on the 2716 memory to instruct it that channel 1 is on hold and to produce, forthwith, a selection of three channel programmes based on channels 2, 3 and 4. There is no particular reason that the \bar{Q} , rather than the Q, output is used to perform this task, simply that the NAND gate driving the Hold indicator is located close by and circuit layout is thus simplified by the omission of four extra pieces of track. A word on the indicator drivers. The published spec of an LS gate will show its sourcing capability, i.e. its High output current only guaranteed to be 400 μ A. This is however the current for correct logic high level output; the output capability is much greater when the output voltage is not critical, such as when used to drive an l.e.d.

As for channel 1, the \bar{Q} outputs of the Hold flip-flops are taken to the memory, occupying in all the A7-A10 inputs. These four inputs are used to select programs for the channels remaining, whatever the number of channels. Although there are 16 four channel programs the choices for 3, 2 and 1 channel operation are limited and thus 8, 4 and 2 programs respectively are incorporated.

the OR gate IC8d, high, allowing IC18a, the NAND buffer, to be wholly dependent on what appeared at its other input. When the \bar{Q} output of IC7a goes low, the output of IC8d will now follow the 25Hz waveform from the collector of TR7 and in turn, IC18a will only be able to operate the indicator and opto-triac every other complete cycle, thus accomplishing the effect described earlier in the article. The same \bar{Q} output drives the Dim indicator via IC9b (74LS20).

STROBE FUNCTION

As previously mentioned, this facility disables the main outputs, and puts a positive signal for each stage of the sequence on the appropriate output jack. When the strobe mode is selected, the dim function must be overridden to prevent a series of pulses appearing at these outputs when the dim function is selected. The strobe mode is selected by S1 and IC13b, the final 4027 in the unit, the other half of which is used for the audio selection. When the strobe mode is invoked, the Q output goes high, placing logic '1' on the A6 input of the 2716 memory, via D13. This address input is one of four used to give a total choice of 16 programmes. The arrangement of the programmes is such that every other programme is suitable for strobe work, i.e. it does not consist of fill and empty type routines that would be ineffective when used with a strobe. Overriding the A6 input thus restricts the programme range to 8 rather than 16 programmes (in the 4 channel mode) and ensures that all of these 8 programmes are the correct type for strobe use. The same applies for three and two channel operation.

A further noteworthy point is that the maximum speed of pulses to the strobe outputs is limited by the clock and audio circuitry design to well below the critical speed that has caused so much controversy with local authorities in the past. It is more or less agreed that under the correct circumstances, epileptic fits can be induced, viz in an epileptic sufferer by the operation of strobes at frequencies in the order of just over 16Hz. The risk of such a happenstance is not

so clearly defined, but in any case, the effect of direct strobe light at this rate of flash on a non-epileptic is to cause breaking up of the vision and is not to be recommended.

AUDIO SECTION

Audio inputs from below 100mV to 40V r.m.s. are fed into J5 (see Fig. 4). If the sound system is stereo, it is only necessary to use one channel as the audio halt circuitry is basically bass orientated and such signals should be present on both channels of a stereo system. TR5 is biased directly from the supply via R46, rather than feedback being taken from its collector. Thus the collector voltage is low and is, provided the transistor is up to spec., below 1 volt. Negative going half cycles of the audio input will produce positive pulses on the collector of TR5, with a bass emphasis provided by the capacitor C11, which causes the stage to roll off above 100Hz. If the audio effect is not selected, the Q output of IC13a is low and the signal at the collector of TR5 cannot rise above about 1 volt, due to the clamping effect of D16. When the audio effect is selected, D16 becomes reverse biased and whenever the collector voltage of TR5 rises above the rated voltage of ZD1, C13 starts charging. When sufficient energy is available, such as with the bass notes, as the input level is set high enough, C13 will charge sufficiently high enough and for long enough to keep TR6 held on, thus stopping the clock (IC19). R49 allows the discharge through the base emitter junction of TR6 to be gradual, rather than immediate, when there would be less or

no effect on the clock. R48 limits the time constant without which the time constant would vary, as the reducing voltage approached the knee voltage of that junction, according to the gain of TR6.

With the effect selected, if the speed control were to be reduced, the effect would be more and more reduced as the speed was lowered. To avoid this, regardless of the speed setting prior to selecting the audio halt effect, the Q output of IC13a also places R52, via D17, in parallel with the speed control. This has the result of narrowing the range of the speed control and restricting that range to the higher speeds so that, whatever the speed setting before the audio effect is switched in, the effect will not be lost.

CONSTRUCTION

As mentioned earlier, the whole unit is slimline in appearance. All components are mounted on a single rectangular double sided p.c.b. which fits inside a purpose designed case. The output sockets, which are the standard 8 pin Bulgin P552 type, used on many commercial units, are mounted on the rear panel and hard wired to the p.c.b. Approximately 2/3 of the back of the case is removable, and the front panel need only be screwed in place after the unit is finished and tested, thus accessibility to all components is good. Fig. 5 shows the component layout looking at the front of the unit, with rear mounted components such as triacs shown in dotted lines. The printed circuit board is

COMPONENTS . . .

Resistors

R1, 32	47k (2 off)
R2-6, 37, 38, 40-44	1k (12 off)
R7, 8, 17-21, 27, 33-36	330 (12 off)
R9-12, 50	2k2 (5 off)
R13-16	100 (4 off)
R22, 28-30, 39, 45-47	10k (8 off)
R23-26	150 (4 off)
R31, 51, 53	100k (3 off)
R46	1M
R48, 49, 52	470k (3 off)
All resistors 1/4W 5%	

Potentiometers

VR1	470k lin. through-board mounting (Radiohm)
VR2	2k2 log. through-board mounting (Radiohm)

Capacitors

C1-3	1000µ 10V axial elect. (3 off)
C4, 13	50n ceramic or mylar type (2 off)
C5-8, 11	2n2 " " " (5 off)
C9, 10	1n " " " (2 off)
C12, 14	1µ radial elect. or tant. bead (2 off)

Transistors & Diodes

TR1	2N5551 (or BFX 84 etc)
TR2-6	BC172 (5 off)
TR7	BC212
D1-3	1N4000 (3 off)
D4-7, 9-12, 14, 15	3mm red l.e.d.—must be splayed leg type 0.1" spacing (10 off)
D8, 13, 16, 17	1N4148 (4 off)
D18	2V7 400 mW Zener

Integrated Circuits

IC1	7805
IC2,3	74LS08 (2 off)
IC4-7, 13, 17	4027 (6 off)
IC8, 11	74LS32 (2 off)
IC9	74LS20
IC10	74LS86
IC12	2716(5V)*
IC14	74LS02
IC16	74C02
IC18	7437
IC19	555
IC20-23	MOC3020 (4 off)
CSR1-4	TXAL228B isolated tab triac (4 off)
J1-5	Mono p.c. jack
F1	20 x 5mm 0.5A
F2-5	20 x 5mm 3A HRC
S1-10	TRS keyboard switch set comprising switch, fingerpad and l.e.d. holder
T1	Transformer 7-0-7 volts 6VA
DPDT rocker switch; 2 knobs to suit pots; 2 Bulgin P552 sockets; double sided p.c.b.; case, front panel, back panel, and heatsink spreader	

Constructors' Note

A full set of parts, including printed facia, case, p.c.b., and transformer may be obtained from:

Bensham Recording Ltd., 327 Whitehorse Road, Croydon, Surrey CR0 2HS. (01) 684 8007. Price £78.50 inc VAT & P.P.

The kit may be purchased whole or in sets of resistors etc. Board, case etc available separately.

*EPROM listing available from PE (Poole Office). Send 10 x 7in. S.A.E.

solder resisted both sides for ease of assembly, the case is plated and the front panel painted and printed.


When assembling, leave the switches and larger components until last, fitting resistors, etc. first. There are half a dozen through board links that should be inserted at the beginning, lest they be forgotten later, especially since two of them are located between C1 and C2 and could easily be missed later on during assembly. There are a good few top-side connections on both i.c.s and resistors. Neglect these at your peril. These are necessary in such a compact unit and preclude the need for wire links and consequently even more cramping in the layout. The disadvantage of such connections only becomes apparent when an i.c. is inserted wrongly and has to be removed. So, unless you are an expert with a solder-sucker, take care! Some components, particularly the capacitors, may need to be bent over to clear the front panel. Alternatively, such items, C4 as an instance, could be rear mounted if the constructor so desired. The switch assemblies should ideally be made up all at once and inserted in one fell swoop to avoid slip-ups. For convenience, the board was laid out with the positive lead of the l.e.d.s to the right of the unit. Take care when deciding the positive lead; most are indicated by the longest lead, but this is not always the case, as the author has found to his chagrin in the past. Fit the transformer last, and before the Bulgin sockets are fitted, slide the board into the case from the back, inserting it at the left hand end, gently bending it slightly to clear the transfor-

mer past the flange on the part of the back of the case that is permanent. Screw the board into place, and also the triacs. These mount against the top of the case via an aluminium thermal "spreader". Use thermal compound liberally here. It is probably wise to delay soldering the triacs until they are screwed down, in order to avoid stressing the leads.

Before fitting the Bulgin sockets, of which more later, fit the mains input lead, securing well and leaving about 3 inches stripped and tinned for connection to the switch. Also solder two flying wires into the board as shown in Fig. 9 for connection also to the switch. Both the mains input and the flying leads should be of sufficient current rating to cope with the full output of the unit, viz 13A. For the time being link the two pairs of wires in a piece of terminal block so that the unit can be tested without the front panel being in the way.

The easiest way to fit the Bulgin sockets is as follows: cut, for each socket, seven pieces of 16g tinned copper wire, varying in length from 5cm to 10cm. Solder these, in ascending order of size around the tags on the socket, leaving out tag number 6. Starting with the socket nearest the mains input, and with the flat on the centre section towards the top of the unit, locate the wires, one by one, starting with the longest. When all the wires on the first socket are in place, push the socket all the way home and screw or pop-riquet in place. Solder the wires to the pcb, feeding the iron through the nearest appropriate hole. Note that some wires

Fig. 5. Component layout

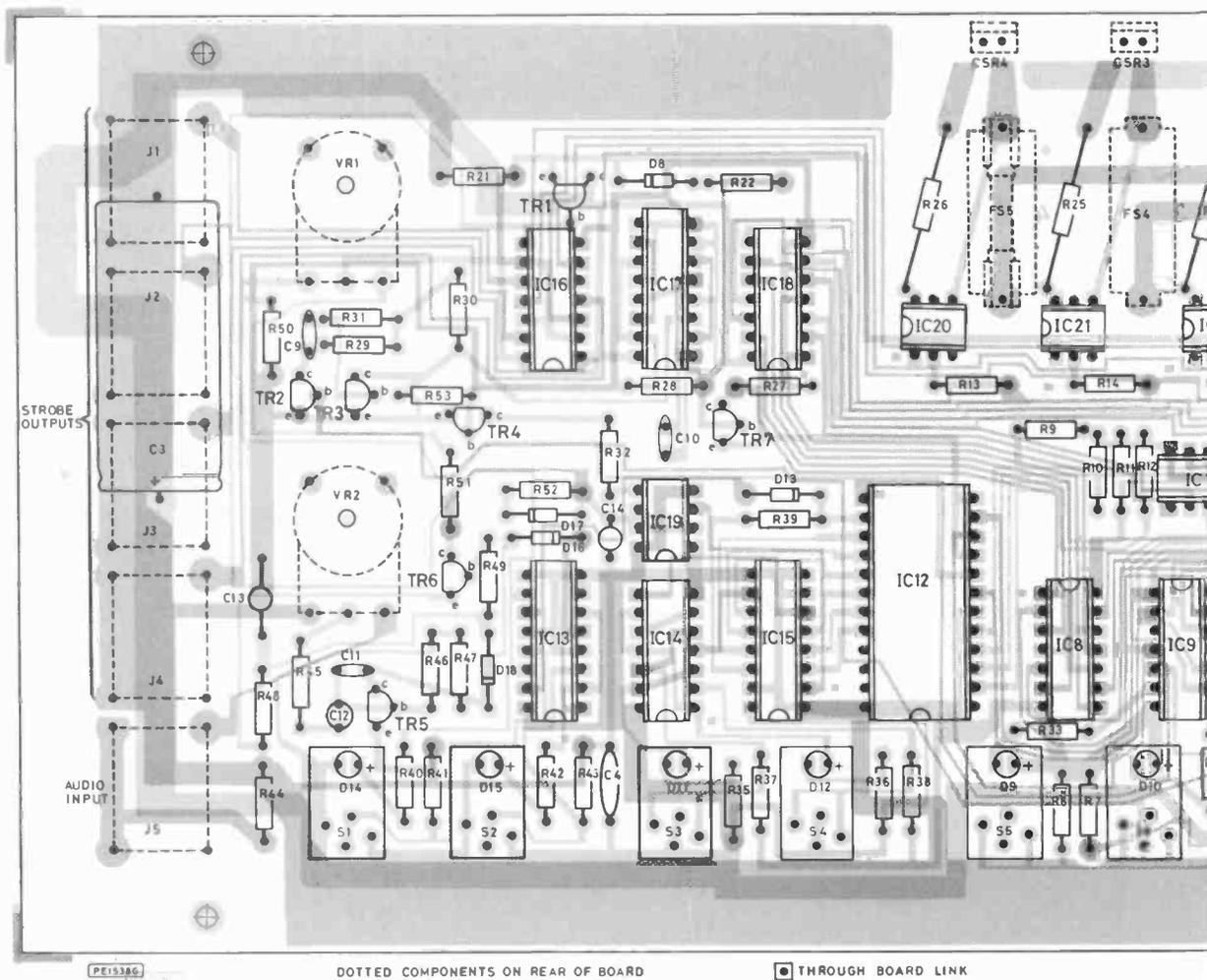

are also soldered above the board. Repeat the process for the second sockets. The Hyperchaser should now be ready for testing.


TESTING

Connect the output to a set of lamps, preferably all the same colour (for the test only) and preferably fairly low power, unless they are mounted behind a diffuser. The output connections for the Bulgin socket are: Channel 1—pin 2, Channel 2—pin 3, Channel 3—pin 4, Channel 4—pin 5, Common neutral return from lamps—pins 7/8, Earth—pin 1 (centre). This follows the accepted standard for these connectors. Before connecting the mains supply (and remember when testing that there is live mains on parts of the unit) check the supply lines for shorts and also for continuity around the board. Connect the supply, and switch on, immediately checking for 5 volts output on IC1. The manual switch should be illuminated, but no others. If the strobe or audio functions switches are illuminated, switch them off by simply depressing the fingerpads. A 4027 will normally come on with the Q output low, but no fail safe circuitry is incorporated to ensure this. Thus occasionally one may encounter a recalcitrant i.c. that will need to be manually set after switch-on. Turn the speed control to minimum, thus disabling the memory, and then check the flash buttons in turn. Next try the hold function and then the dim effect. With

the dim function invoked, operate the strobe button, which should illuminate. The output i.e.d. indicators which should have been operated at a reduced brilliance showing a degree of flicker should be restored to full brilliance until the strobe button is pressed again. There will also be an amount of flicker on the load lamps, but not so significant as the i.e.d.s due to the thermal inertia of the lamps. Take all of the channels off Dim and Hold (in that order, since monitoring correct switch operation is easier in this fashion) and advance the sequence speed control and observe the display.

The unit should now perform a sequence. Advance the programme by pressing the Manual button and check that each of the 16 programmes are being selected correctly, i.e. that all outputs of the 4520 are getting to the 2716. Place each channel in turn on Hold and check the three channel programmes that result. This is a long winded process if you do the whole bit, going through every permutation of channels, and checking every programme, and is really only to ascertain that the memory is in fact correctly programmed. Since all the programming devices I have encountered throw up a clear warning if the programming sequence has gone awry, it is perhaps enough to confine this stage of the testing to checking that the operation of each hold button is having the desired effect and that it is therefore connected properly.

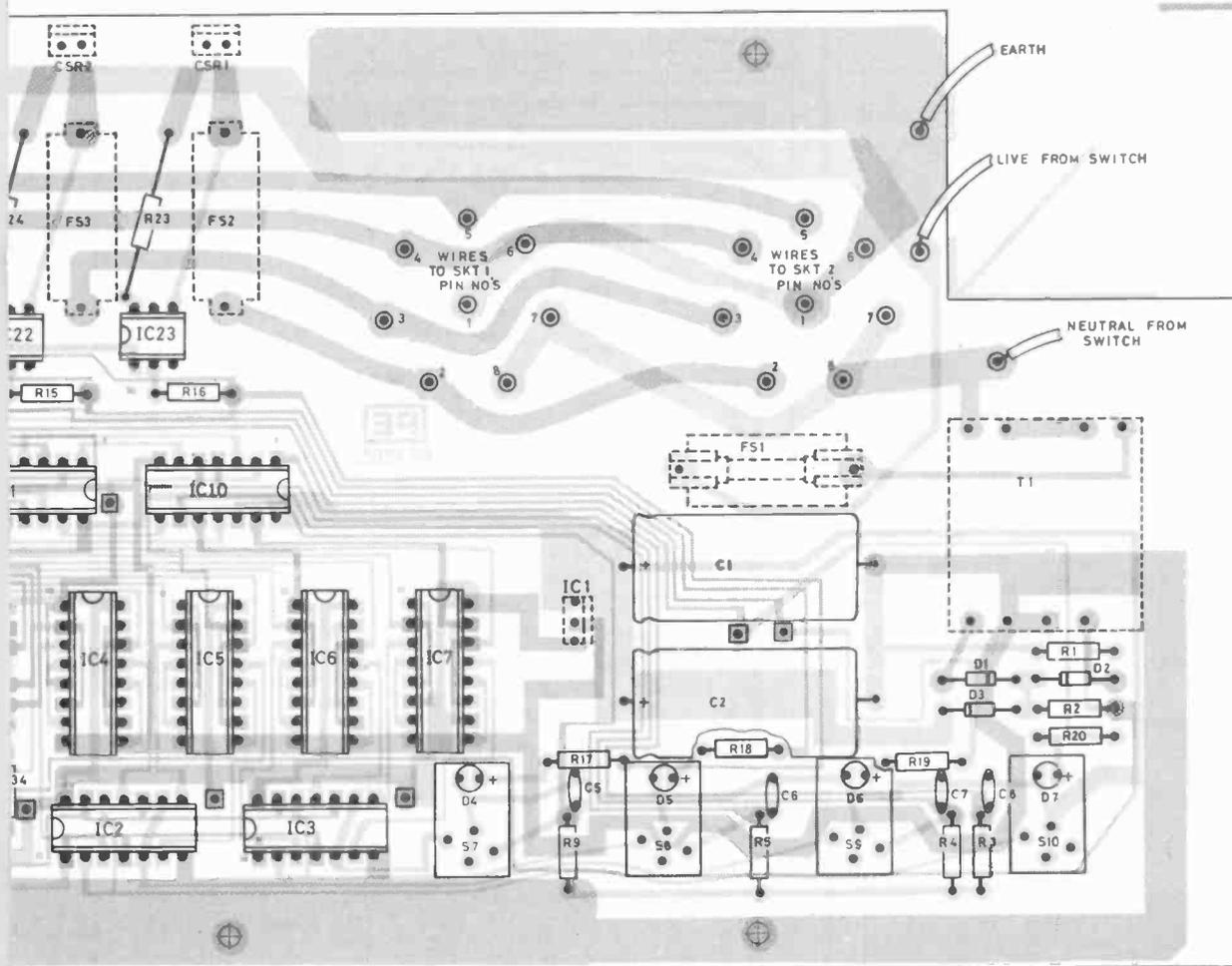To check the strobe function, a simple indicator may be made from four i.e.d.s each in series with a 1k resistor and the positive of each i.e.d. connected to a strobe output. ★



SECURITY

Install your own system and save using built and tested modules

A COMPLETE INTRUDER ALARM

EASILY ASSEMBLED ULTRASONIC UNIT CK 5063

Requires no installation. Easily assembled using our professionally built and tested modules.

- Adjustable range up to 25ft.
- Built-in entrance & exit delay
- Built-in timed alarm
- Key operated switch - On, Test and Operate
- Provision for an extension speaker
- Fully self-contained
- Uses US 5063, PSL 1865, Key Switch 3901.
- 3" Speaker 3515

only
£37.00
+ V.A.T.

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built-in LED indicator and test position the unit is easily set-up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 90dbs of sound, or even 110dbs with an additional speaker. All parts included and supplied with full instructions for ease of assembly. Size 200 x 180 x 70mm. Order as CK 5063

DIGITAL ULTRASONIC DETECTOR

US 5063



only **£13.95** + V.A.T.
NEW

- 3 levels of discrimination against false alarms
- Crystal control for greater stability
- Adjustable range up to 25ft.
- Built-in delays
- 12V operation

This advanced new module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions. The module has a built-in exit delay and timed alarm period, together with a selectable entrance delay, plus many more outstanding features.

ULTRASONIC MODULE

US 4012




£10.95 + V.A.T.

- Adjustable range from 5-25ft.
- This popular low cost ultrasonic detector is already used in a wider range of applications from intruder detectors to automatic light switches and door opening equipment, featuring 2 LED indicators for ease of setting up.

INFRA-RED SYSTEM

IR 1470 only **£25.61** + V.A.T.

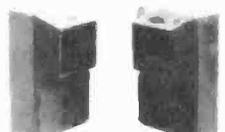

Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft, operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications. Size 80 by 50 by 35mm.

POWER SUPPLY & RELAY UNIT

PS 4012

Provides stabilised 12V output at 85mA and contains a relay with 3 amp contacts. The unit is designed to operate with up to 2 ultrasonic units or 1 infra-red unit IR 1470. Price **£4.75** + V.A.T.

SIREN MODULE SL 157

Produces a loud penetrating sliding tone which, when coupled to a suitable horn speaker, produces S.P.L.'s of 110dbs at 2 metres. Operating from 9-15V. Price **£2.95** + V.A.T.

5 1/2" HORN SPEAKER HS 588

This weather-proof horn speaker provides extremely high sound pressure levels (110dbs at 2 metres) when used with the CA 1250, PS 1865 or SL 157. Price **£4.95** + V.A.T.

3-POS. KEY SWITCH 3901

Single pole, 3-pos. key switch intended for use with the CA 1250. Price **£3.43** + V.A.T. Please allow 7 days for delivery

Add 15% VAT to all prices
Add 50p post & packing to all orders
Units on demonstration
Shop hours 9.00 to 5.30 p.m.
Closed Wednesday
Saturday 9.00 to 1.00 p.m.
SAE with all enquiries
Order by telephone or post
using your credit card

ALARM CONTROL UNIT

CA 1250



Price **£19.95** + V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system whether a highly sophisticated installation or simply controlling a single magnetic switch on the front door.

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charging facility
- Operates with magnetic switches, pressure pads, ultrasonic or IR units
- Anti-tamper and panic facility
- Stabilised output voltage
- 2 operating modes - full alarm/anti-tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for external loads
- Test loop facility

SIREN & POWER SUPPLY MODULE

PSL 1865

only
£9.95
+ V.A.T.



A complete siren and power supply module which is capable of providing sound levels of 110dbs at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 to form a complete alarm.

HARDWARE KIT

HW 1250

only
£9.50
+ V.A.T.



This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label. Size 200 by 180 by 70mm

ULTRASONIC MODULE ENCLOSURE

only
£2.95
+ V.A.T.



Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063; for US 4012 order SC 4012.

RISCOMP LIMITED

Dept PE12
21 Duke Street,
Princes Risborough,
Bucks. HP17 0AT
Princes Risborough (084 44) 6326

P.E. HYPERCHASER 4 CHANNEL CONTROLLER



A full kit of parts for this pseudo intelligent light unit.


A TRULY SOPHISTICATED 4 CHANNEL LIGHTING & STROBE CONTROLLER **£78.50**
Inc. carr/VAT

SAE FOR LIST OF INDIVIDUAL PARTS

IT INCLUDES CASE, P.C.B. PRINTED FASCIA ETC.

P.E. STAR DESK

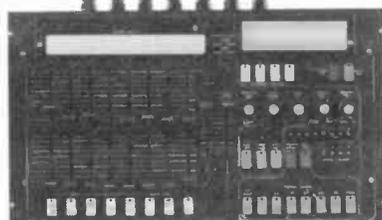8+4 CHANNEL COMPREHENSIVE EFFECTS LIGHTING DESK



- ☆ 1KW/Channel
- ☆ 8 Twin Presets
- ☆ 4 Independent Channels
- ☆ 8 Chase Routines
- ☆ Sound to Light and Manual Flash Functions

A full kit of parts for this exciting project including case, panel, P.C.B. etc. is available from us for **£195***

*Includes VAT & Carr.

Telephone your order on 01-684 8007 or send Cash/Cheque/Credit Card No. to:



BENSHAM RECORDING LTD.,
327-333 Whitehorse Road, Croydon, Surrey CR0 2HS.
Shop open 9am-5pm Mon.-Sat.



Please allow 14 days for delivery.

KITS FROM £7 ...TO £60

Sparkrite

Buy Sparkrite Brand Leading Auto Electronics in self-assembly kit form - And save pounds!!

- Electronic Ignition systems - contact triggered and contactless
- Electronic Car Security Systems - including a new ultrasonic unit
- Car Drive Computer - with 12 functions

SEND FOR FREE LITERATURE PACK - TODAY!

8 SOPHISTICATED KITS TO CHOOSE FROM.

To:

SPARKRITE (A Division of Stadium Ltd.), Queensway, Enfield, EN3 4SD.
Telephone: 01-804 4343

NAME

ADDRESS

PE

Space Watch...

LA PALMA OBSERVATORY

It is not always appreciated that the level of precision engineering required for modern telescopes is exceptionally high. Over the last three decades almost every aspect of looking at and seeking to understand what exists outside the Earth on which we live, has undergone change. The telescopes at La Palma continue this trend.

Aids for use with optical telescopes have reached a high standard also. There will be the Image Photon Counting System. This consists of a special television camera with an image intensifier. This also has a computer device which helps to sharpen the image by 'freezing' the 'snow' on the picture. This is particularly useful for studying spectra.

For direct pictures of small areas of the sky a charge coupled device (CCD) will be used. This consists of a large silicon chip which is sensitive to light. The CCD is about thirty times more sensitive than the best photographic emulsion. It is therefore possible for the exposure time to be cut from hours to a few minutes, thus cutting the exposure time of each observation and also getting more reliable data at a greatly increased rate.

Other facilities available will be 'speckle interferometry' which will enable images to be reliably photographed. This method enabled astronomers to show that the planet Pluto consisted of two bodies separated by only a short distance. The density also was much lower than had been previously thought.

These new techniques are very useful especially when false colour is used to model very faint and distant objects like the recently discovered 'black hole'.

Although there will always be resident astronomers at the La Palma observatory British astronomers will be able to control the three main telescopes from the Royal Greenwich Observatory at Herstmonceux in Sussex. This is the remote operation which will be made by telephone; from the control room they will be able to look through to the telescopes via their television screens. This will save time and money and enable those in the observatory to watch the screens at Herstmonceux, even collectively, if anything specially interesting is found.

WHY LA PALMA?

With the emphasis moving from the bright stars to distant faint objects some of the original objectives have been revised and by the time that the Isaac Newton 100 inch mirror telescope had been fully available the emphasis in astronomy had moved to the investigation of faint objects. It was this new area of astronomical research that led to the choice of La Palma as the final site for this telescope.

In 1969 a committee was set up to decide upon the best site for a telescope and

to be a very dark sky, far from man made sources of interference. In 1971 a team tested places in Italy, the South mainland of Spain, the Cape Verde Islands, Madeira, Hawaii, Tenerife and La Palma. The sites were narrowed down to a choice between Hawaii and La Palma. It was decided that there would be difficulties at Hawaii because of the altitude and so La Palma was chosen. Hawaii however is more suitable for infra-red and millimetre astronomy.

The peak of La Palma, which is on the edge of its volcanic caldera, is 2,400 metres high. It is elevated enough to be a suitable site but it is not inconveniently high. Its great advantage is that it is above the clouds for most of the time and above the inversion layer which keeps down the water vapour and the dust in the lower atmosphere. The air above comes in a steady stream from over the Atlantic. The sea temperature alters less between day and night than land temperatures. So this is favourable and light is less likely to blur the images of the stars and faint objects. It is likely that this will be a successful venture for the Northern Hemisphere and future source of research and new discovery.

VENUS

It is well established now that there are indications of volcanism on Venus though there may not be direct and short term eruptions. Better methods have been developed over the last few years of gathering details. A great deal of the credit for this must go to the Russian spacecraft and probes. Peter Cattermole of Sheffield University is very active in this field and Anglo - Australian research, particularly in the infra-red, has led to greater accuracy in mapping the dark side of this planet.

Be that as it may the news recently from America suggests that there are signs of eruptions every 5 to 10 years. The last one, it is suggested, was in 1976. This was thought to be as catastrophic as Krakatoa. There are two regions, thousands of kilometres apart, that are suggested as being the main places of activity. There seems to be great structural differences between Venus and the Earth, though they came into being at the same time some 4,000 million years ago.

In February this year three American astronomers released information about the results of their findings using data from NASA's Ames Research Centre. The three researchers were H. Masursky of the US Geological Survey, L. Esposito from the

Frank Wilsenham Hyde

FRANK Wilsenham Hyde, author of *Spacewatch*, died on March 22, aged 75. A respected and admired contributor well known to readers of *Practical Electronics* for his enlightening monthly commentary on extra terrestrial exploratory matters, Frank was also, to those who knew him personally, a kindly and unassuming individual though always capable of provoking deep thought and discussion in many subjects. Indeed his scientific and engineering knowledge and experience encompassed many disciplines. However it was to radio astronomy that Frank was especially devoted for most of his life. This interest commenced in his teens, for it was while an engineering apprentice with Crompton-Parkinson at Chelmsford he first began pioneer investigations in radio physics.

In 1950 he began serious work in radio astronomy and set up at Little Claston, in Essex, what was the largest privately owned radio observatory in the world. He worked with Cambridge and Jodrell Bank and had a special assignment when the first earth satellite was launched and made certain discoveries regarding the ionosphere. Also at this time he was engaged in the special electrical Meeting of Jupiter which was later funded by the National Aeronautics and Space Administration of America (NASA). Some of the experiments on Pioneer 10 and 11 were the direct sequel to this work. He continued to work in collaboration with Cambridge in the study of the Crab Nebula, Quasars and the Solar Wind.

The unique experience of working closely with leading academics in this young branch of science, and being associated with major discoveries in space, made Frank Hyde the ideal choice as commentator for *Practical Electronics* on this emergent field in which electronics

played a vital part. The first *Spacewatch* appeared in October 1967, and for two years was bi-monthly until March 1969 when increasing activity in the space sciences made a regular monthly article imperative.

Spacewatch soon became compulsive reading even for those who had no special interest in satellites or space exploration in general, for it frequently contained snippets of information of even wider interest and potential application—the so-called spin-offs from space technology. Frank was often the first into print with such technical tidbits.

Frank Hyde's story seems to confirm the view that there is intellectual or philosophical reward in the study of space; that it unshackles the mind from earthly prejudices and limited vision. Right up to his death Frank actively pursued a number of interests, with dedication. These included some less than conventional "fringe" topics such as parapsysics and he also became a keen advocate for the revival of the airship as a commercially viable form of transport, particularly for bulky loads to not easily accessible places.

Frank was the author of two books on radio astronomy and he contributed articles to various magazines. He was an accomplished lecturer, delivering lucid accounts of radio astronomy techniques to Societies, Schools and Universities. He appeared in a number of television programmes and had also been interviewed on radio in connection with space matters. He was a Fellow of the Society of Engineers, Fellow of the Society of Professional Engineers, and Past President of both. He was a founder member of the Airship Association and a Fellow of the Royal Astronomical Society. Awards were made by several learned societies to Frank Hyde for his contributions to radio astronomy.

Fred Bennett

observatory to be known as the Northern Hemisphere Observatory. It needed to be able to provide clear 'seeing' free from dust in the atmosphere. The images were not to be of such a nature that there was turbulence which would spread and distort the image. There had

PE micro~file

R.W.Coles

FILESHEET 16 16032

DURING the last two file articles we have focused the spotlight on National Semiconductor and two of its most popular processors, the 8073 and the NSC 800. We have found that National, while being indisputably the largest semiconductor manufacturer in Silicon Valley, and despite having been involved in the microprocessor scene from its early days, has nevertheless managed to come fourth in what is essentially a four horse race.

This rather mediocre performance has not been ignored in the National boardroom, and the obvious success of upstarts like Intel and Zilog was not to be left unchallenged for long. The National response has now arrived, in the form of the NS16000 microprocessor family, and for once the whole industry has had to stop and take stock in the face of what can only be described as a massive onslaught from a company that hitherto had been considered to be a rank outsider!

It is the sheer *scale* of the National response which takes one's breath away. Having seen Intel's 8086 architectural problems caused by 8080 compatibility, Zilog's Z8000 failure caused by a messy instruction set and lack of an 8 bit bus version, and Motorola's lateness in providing a proper family of peripheral devices for its 68000, National decided to take on the whole bunch with a processor family which would suffer from none of these drawbacks. Easy to say, of course, but actually pulling it off was a mammoth task. It involved introducing a complete new family of microprocessors and peripherals all within the space of about twelve months, which would be a remarkable achievement for anyone, if, indeed, it could be done at all.

The first family member, the NS16032 16 bit processor described here, arrived in late 1982, and, keyed to an unprecedented barrage of marketing ballyhoo which kept potential designers saturated with relevant facts and figures, the other family members arrived as if fired from a machine gun. Now, not much more than a year later, we find ourselves able to choose from a compatible family which includes the basic NS16032, the 8 bit bus NS16008 and the 32 bit NS32032, and able also to select the NS16081 floating point math unit and the NS16082 memory manager to complement them if needed. From being the last to introduce a modern 16 bit processor, National now find themselves the first into 32 bits, a quite extraordinary situation.

It is tempting to think that such a rapid evolution must have resulted in a lot of rough edges and shortcomings in the National designs, but this does not appear to be the case. The basic family architecture is at least as elegant as that of last year's "Miss-Microprocessor", the 68000, and yet it offers higher performance and better intra-family compatibility.

It is difficult to judge just how well any new device is actually supported, because what is promised in the ads is not always fulfilled in practice, but one thing National *have* managed to convince me of is their on-going *commitment* to the new family, a feature often sadly lacking or short-lived in their earlier efforts. Certainly, National have had to work twice as hard as their competition to convince doubting designers of their sincerity, thanks mainly to their rather unimpressive track record!

The basic 16032 processor is most easily compared with the 68000, because like that Motorola processor, it uses 32 bit internal data pathways and registers and has a simple, regular, instruction set which supports a wide range of addressing modes and data types. Unlike the basic 68000 though, the 16032 and all its cousins support virtual memory operations directly, making it com-

petitive not just with earlier mini-computers such as the PDP 11 but also with full blown 32 bit midi-computers such as the ubiquitous VAX.

A major aim of the National designers was to make their architecture as compatible as possible with the data structures and concepts used in modern high level languages such as Pascal so that compiled code would run as efficiently as assembled code without suffering the speed penalties usually encountered (particularly with 8 bit machines) in trying to force the high level language "square-peg" into the processor "round-hole". I think they have succeeded in this aim, and I doubt whether many users, even those designing fast real-time controllers, will ever have to bother with the tedium of assembly language when using a member of the 16000 family.

REGISTERS

The 16032 register set is similar in many respects to that available on the 68000. Most registers are 32 bits long to provide immediate compatibility with the 32032 processor and a potential address space of 4 Gigabytes, 16 Megabytes of which are directly implemented by the 16032.

The set is organised into two main groups consisting of eight general purpose data or address registers and eight special purpose registers. The general purpose registers are all 32 bits long and can be used for high speed access to data or address information. The registers in this group will store bytes, words, double words, or (in pairs) quad words, and can be used as accumulators, data registers, or as address pointers; any instruction can use them without restriction. Another eight general registers are made available externally when the 16081 Floating Point Unit (FPU) is added to a system.

The special purpose group contains six 32 bit registers which are reduced in the 16032 to 24 bits (the width of the address bus) by having the high order 8 bits set to zero. In addition there are two 16 bit special purpose registers, making eight in all. The individual members of this group are described below:

Interrupt Base Register; this register holds the base address of the interrupt vector table (called the dispatch table by National) which can be located anywhere in the 16 M byte address range. A single external 16202 Interrupt Control Unit (ICU) can provide up to 16 separate interrupt vectors, expandable to a maximum of 256 levels with additional ICUs. Each entry in the dispatch table is 32 bits long.

Static Base Register; this points to the base address for address calculations used to access the global variables of a particular software module. All procedures within a module access any common module variables relative to the base address stored in this register. The provision of this feature is particularly valuable in supporting the modular code produced as a natural consequence of using high level languages such as Pascal.

Frame Pointer; while the SBR is used as a base address for module-wide *global* variables, the Frame Pointer performs a similar function but provides a base pointer for a frame of *local* variables and parameters which are relevant only to the currently executing procedure. This register is therefore reloaded for each new procedure within a module, whereas the SBR is only reloaded on the commencement of a new module, which may itself contain many procedures.

GENERAL

With a poor record for being disloyal to users of its previous microprocessor designs, National has had to go all-out with its marketing effort for the 16032. Although this processor is probably the best 16 bit device available, and despite National's creditable efforts in providing a high level of hardware and software support, the late arrival of this chip has virtually precluded it from achieving a leading position. This situation may change with the early introduction of the compatible 32 bit 32032, since it will be the first mainline 32 bit device to become available and this will undoubtedly boost sales of the whole family.

REGISTERS THE 16032 HAS A USEFUL SET OF DEDICATED AND GENERAL PURPOSE REGISTERS, MOST OF WHICH ARE 32 BITS WIDE.

31	23	16	8	
'0'	INTERRUPT BASE REG			INTBASE
'0'	STATIC BASE REG			SB
'0'	FRAME POINTER			FP
'0'	USER STACK POINTER			SPL
'0'	INTERRUPT STACK POINTER			SPO
'0'	PROGRAM COUNTER			PC
PROGRAM STATUS				PSR
MODULE				MOD

EIGHT SPECIAL PURPOSE REGISTERS

31								0
								R0
								R1
								R2
								R3
								R4
								R5
								R6
								R7

EIGHT GENERAL REGISTERS

FLAGS

15 SUPERVISOR ONLY								8 USER & SUPERVISOR								4 BIT CONFIGURATION REGISTER				
																C	M	F	I	CFG

I P S U Z F L T C y

PERFORMANCE DATA

16032


MEMORY ADDRESS RANGE :- 16M byte
 I/O ADDRESS RANGE :- (MEMORY MAPPED)
 CLOCK FREQUENCY :- 6 MHz*
 POWER SUPPLIES :- 5V
 INTERRUPTS :- INT, NMI
 *10 MHz ALSO AVAILABLE

BENCHMARKS

	16032
ADD REG TO REG	0.67µs
O/P REG TO PORT	2.7µs
MOVE FROM MEMORY TO MEMORY (16 BIT DATA, ABSOLUTE ADDRESSING)	4.7µs

INSTRUCTION SET AND SOFTWARE

With a 16 M byte linear address space, virtual memory capability and a powerful two address instruction set optimised for high level language compilation, the 16032 will probably appeal to all data processing fans. National have put together a useful software development environment which includes UNIX and CP/M operating systems and most of the popular languages. Until someone introduces a popular 16032 based PC, however, application software will remain a problem.

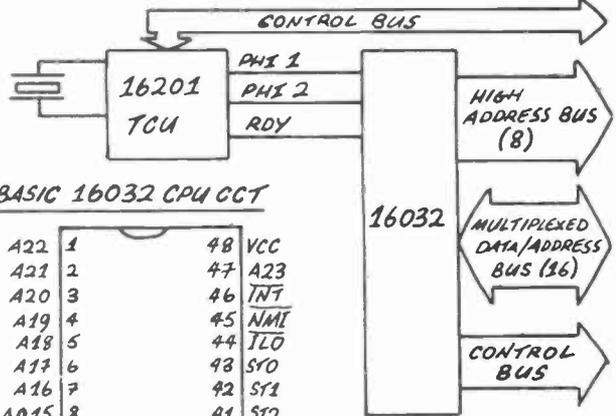

BASIC 16032 CPU CCT

A22	1	48	VCC
A21	2	47	A23
A20	3	46	INT
A19	4	45	NMI
A18	5	44	TLO
A17	6	43	SY0
A16	7	42	SY1
AD15	8	41	SY2
AD14	9	40	SY3
AD13	10	39	PFS
AD12	11	38	DDIN
AD11	12	37	ADS
AD10	13	36	U/S
AD9	14	35	AT/SPC
AD8	15	34	RST/ABT
AD7	16	33	DS/FLT
AD6	17	32	HBE
AD5	18	31	HLDA
AD4	19	30	HOLD
AD3	20	29	BBG
AD2	21	28	RDY
AD1	22	27	PHI2
AD0	23	26	PHI1
GNOL	24	25	GNDB

OTHER FAMILY MEMBERS

16008 16032 WITH 8 BIT EXTERNAL DATA BUS. 48 PIN PACKAGE.
 32032 16032 WITH FULL 32 BIT EXTERNAL DATA BUS. USES 68 PIN L.C.C. PACKAGE.

MANUFACTURERS

ORIGINATOR :- NATIONAL SEMICONDUCTOR
 2ND SOURCE :- FAIRCHILD

SUPPORT CHIPS

THE 16032 NEEDS AN EXTERNAL TIMING CONTROL UNIT (TCU) TO ACT AS CLOCK AND WAIT STATE GENERATOR AND HAS A USEFUL, GROWING, FAMILY OF POWERFUL PERIPHERAL CIRCUITS SUCH AS THE 16081 FLOATING POINT MATH UNIT, THE 16082 MEMORY MANAGEMENT UNIT AND THE 16202 INTERRUPT CONTROL UNIT.

Module Register; all NS16000 programs are organized as modules, and each module consists of three components, namely the program code, the static data, and a link table which contains entries describing any variables or procedures which may be needed but happen to be resident in other modules. Also provided is a Module Table which must be set up in low memory to contain a Module Descriptor for each module used by a program. There are three 32 bit entries in each Module Table comprising a Static Base address (to load into the SBR), a Link Base address, which points to the start of the module's Link Table, and a Program Base address which points to the start of the code. The 16 bit Module Register is used to hold the base address to the Module Descriptor for the current module. (Phew!)

PC, SPO, SP1 and PSR; the remaining four dedicated registers are fairly conventional, and consist of a 24 bit program counter (PC), two 24 bit stack pointers (SPO and SP1) and a 16 bit flag or status register (PSR).

Also worthy of note is the four bit Configuration Register (CFG) which lives within the control section of the CPU architecture. This register can only be modified via the special SET CFG instruction, and it is used by the programmer to declare the presence of various external peripheral devices. The I bit informs the processor that an external vectored interrupt controller (e.g. the NS 16202) is present, and that a vector will be provided. The F, M, and C bits perform a similar function for the floating point arithmetic unit (NS-16081), the memory management unit (NS16082), and any presently unspecified "Custom Slave Processors".

Before leaving the subject of the sophisticated register set of the NS16000 series, it is also interesting to note that the register addressing scheme used actually supports the use of additional registers *outside* the CPU chip itself. For example the NS16081 provides another eight general purpose registers and one special, all of which can be treated as though they are part of the basic CPU set. This is an extremely useful facility and provides a lot of "stretch" potential to the current architecture.

INSTRUCTION SET

The instruction set of the 16000 series of processors will bring tears of joy to the eyes of system software writers, because it is so symmetrical and efficient, and because it comes closer than any I have seen to the ideal for use with high level language compilers.

Instructions can be used with any of nine addressing modes, any of the byte, word, and double word data types, and can employ any of the general purpose registers. In addition, the instructions can all specify at least two operands, and in some cases up to five. Each basic instruction consists of between one and three bytes of code which may be optionally extended depending on the instruction type and addressing modes selected as follows:—

OPTIONAL			BASIC				OPCODE
IMPLIED IMMEDIATE OPERAND(S)	DISP. 2 IMM 2	DISP. 1 IMM 1	INDEX BYTE 2	INDEX BYTE 1	GEN. ADDR. MODE 1	GEN. ADDR. MODE 2	

There are over 100 basic instruction types as shown in the listing. Four standard addressing modes are provided as follows:—

REGISTER Used to specify an operand located in one of eight *internal* general purpose registers, or in the case of certain slave processor instructions, one of eight *external* general purpose registers.

IMMEDIATE Used to specify an operand encoded with the instruction (as usual).

ABSOLUTE Used to specify an absolute memory address, although in this case the "absolute" value is really a displacement from a base register.

REGISTER RELATIVE used to form a register-indirect address computed from the contents of a general purpose register and a displacement value issued with the instruction.

And in addition a group of five so-called high-level-language modes are provided to satisfy the needs of compiler writers:—

MEMORY MODE This mode is similar to Register Relative, but in this case a dedicated register is used.

MEMORY RELATIVE This mode allows the direct use of address pointers stored in main memory without the need to first load the pointer value into a CPU register. This is useful for rapid access to tables of data or records in RAM.

EXTERNAL This mode is unique to the NS16000 series and provides support for the "software-module" approach (mentioned in the register section) by providing a means to access operands that do not reside in the currently executing module.

TOP OF STACK Another NS16000 family special, this mode provides push and pop access to operands on the stack for *all* instructions, not just those provided specifically for the purpose as in most other processors. This is particularly useful for arithmetic procedures.

SCALED INDEX This mode provides "smart" indexed addressing to allow access to arrays of data organised on a byte, word, double word, or quad word, basis. A general purpose register value is used as the index, and this is automatically multiplied by one, two, four or eight to achieve the correct stepping increment for the particular array data type involved. Thus a single register increment operation can be used to step through arrays of data organised to contain 64 bit entries.

No doubt many readers (including, it must be admitted, the author!) will find the above addressing modes rather daunting and beyond past experience or recognised need. Fortunately, the only people who really need to come to grips with these fancy features are the system software and compiler writers. This is because, as mentioned earlier, ordinary mortals like us will only need to write code for the NS16000 in a high level language such as Pascal, where all these sophisticated capabilities only become obvious when we notice that our program runs very fast indeed and uses very little memory. What a relief!

Trying to summarise the instruction types available is also a daunting task. Suffice to say that everything you are likely to need is there in abundance including multiply and divide, BCD arithmetic, string handling and bit manipulation. If there is anything missing, however, it can always be provided via a "custom slave" processor since the instruction set provides direct access to this facility. In a similar vein, a complete set of floating point math and memory management instructions are included for use on systems containing the 16081 and 16082 devices. This is a great deal simpler than the load/unload operations often required by other micro-processors to gain access to their dedicated slaves.

VIRTUAL MEMORY

One of the most important features of the NS16032 and its cousins is that they support the concept of "Virtual Memory". Since this National family is the first we have covered in the Microfile series to feature this useful capability, it is necessary to have a look at the concept and the way that NS16032 handles it, in more detail.

With the size of software modules growing ever larger, and with the need for multiple programs to "time-share" the CPU resources, then even with the low cost of today's dynamic RAM chips, system designers find it difficult to provide a sufficiently large physical memory space to allow all programs and users sufficient space.

One way to overcome this problem which is supported by many disc BASICs, is to use an overlay mechanism by which the programmer, realising that his code is becoming too large to fit comfortably in memory, can divide his program into a number of overlay segments, only one of which is loaded from disc into RAM at any one time. The trouble with this technique is that the programmer must make the overlay decisions himself while writing the program and on multi-user systems it is virtually impossible to decide in advance just how much memory will be available at run time.

A much neater technique would be to let the programmer use as much memory space as he needs, without the need to worry about overlays, and then let the *system* decide at run time how much physical memory can be allocated. This is just what the Virtual Memory concept provides, but a processor using it has a problem on its hands which can only be solved by additional chip complexity. If the operating system allocates 4K bytes, for example, and the program happens to be 40K bytes long, then when the processor attempts to fetch the (4K + 1)th code byte, it must be able to recognise its "mistake", abort the current instruction, and ensure

that the operating system is informed so that another chunk of code can be loaded from disc into the allotted space, and execution resumed without the loss of a single instruction. This is obviously a neat trick if you can pull it off, and fortunately for us, the NS16000 family can!

When mated with an NS16082 MMU the NS16032's 16M byte *logical* address space is effectively divided into 32,768 pages, each of a fixed size of 512 bytes, which may (or may not) be represented in *physical* memory. Each program or task can make use of an apparent 16M bytes of memory, although in fact, the MMU relocates the addresses it receives by mapping them into the actual physical memory available. Programs and data are swapped in and out of memory in units of a page, in an operation transparent to the programmer (other than by its effect on execution time), stage managed by the MMU and processor working together under the control of an appropriate virtual memory operating system software package.

The MMU uses an address table stored in RAM to map from *logical* to *physical* space, and in addition to address information, table entries include five bits which provide the MMU with information about the status of the page concerned, as follows:—

V=Valid Bit, which indicates whether the page is actually present in memory. **R**=Referenced Bit, which indicates whether the page has been accessed. **M**=Modified Bit which indicates whether the page has been written into. **PL**=Protection Level field (2 bits) which indicates whether the page can be used for Read Only or Read/Write operations.

These status bits provide all the necessary information for the proper implementation of a Virtual Memory operating system and its page swapping algorithms.

When the MMU receives an address for translation, it checks the Valid Bit in the page entry to see whether the required page is actually resident in physical memory. If it is not, then the MMU detects a "page fault" and generates an ABORT signal which causes the processor to halt execution of the current instruction.

In effect the ABORT signal is like an interrupt, and causes the processor to restore register information to its status *before* the current instruction was attempted, and then to call the operating system to sort the whole mess out. Horrific and tangled though the job may seem to us, the NS16032 (with the aid of suitable system software) is able to find a suitable page space, store the code already resident there onto the disc, load the next page from disc into RAM, and get the whole thing up and running again in next to no time.

Needless to say, the availability of a Virtual Memory operating system on a desk top microprocessor will endow that humble system with capabilities which are currently far above its status. Such systems will no doubt become available quite soon, thanks not only to the NS16000 family, but also to the availability of capacious, cheap and fast access Winchester hard-disc drives.

SOFTWARE

The Achilles heel of all radically new microprocessors is to be found in the level of software support that they enjoy. With the NS16032 National have had to start from scratch, but despite this fundamental obstacle, they have managed to produce (with the help of third party software houses) a creditable array of software

tools which includes about five operating systems and thirteen languages!

Included among the operating systems are old favourites like UNIX (employing Virtual Memory), and CP/M in its Concurrent CP/M form from Digital Research.

All of this is very encouraging, but what counts in the end will be the availability of applications packages such as spread-sheets, word-processors, and payroll ledgers, and these are traditionally supplied by a lower echelon of third party software houses over which National can have no control.

What National have to do, and they know it, is to keep up such a barrage of ballyhoo that the World will finally succumb and generate a demand for such software. If they stop now, regardless of how wonderful their new processor family may be, the whole thing will fizzle out like a damp squid.

INTERFACING

There seems to be little point in delving too deeply into the hardware interfacing of such a mighty machine, because it will be some time before the average hobbyist will pluck up the courage to tackle a project based upon the NS16032! Not that there is anything especially *difficult* about designing and building such a system, the problem in this case lies in developing the software to do the system justice. With the availability of easy-to-interface memory and peripheral chips we enjoy today, the assembly of an NS16032 system would probably be a lot simpler than building one of those "8080A and 4K of dynamic RAM" systems of yesteryear.

Suffice to say that, as we have come to expect, the 16032 uses a form of NMOS technology, operates from a five volt supply, and provides all the necessary bus signals to make interfacing straightforward. About the only surprising thing concerning this device, in fact, is that it does require a separate clock generator and controller chip, the NS16201, which uses a 24 pin package.

APPLICATIONS

There can be little doubt that the NS16032 is the most powerful and capable 16 bit microprocessor yet developed, and if there is any justice in this world, it should go on to establish a star-studded career for itself in the data processing system market.

At present, however, it is difficult to imagine how such a device can be used to advantage in a small home computer application unless it is provided with at least one Winchester disc drive to act as a backing store. An NS16032 saddled with only a cassette port would be rather like a Porsche deprived of its wheels: lots of fun revving the engine but it won't actually be able to go anywhere!

Fortunately for us, Winchester disc drives are getting cheaper, and even Sir Clive will be offering one as an optional peripheral with his new QL machine so perhaps we won't have too long to wait before we can all tap the power of National's behemoth. One system which may be first in line for an NS16032 upgrade is the BBC micro, for which such a facility has been planned since before the original launch, while the NS16000 family was still just a twinkle in National's eye.

One thing is for sure though, this device is *not* the thing to use for your doorbell or central heating controller!

INSTRUCTION SET SUMMARY

MNEMONIC	DESCRIPTION	MNEMONIC	DESCRIPTION
MOVES		LOGICAL AND BOOLEAN	
MOV _i	Move a value.	AND _i	Logical AND.
MOVQ _i	Extend and move a 4-bit constant.	OR _i	Logical OR.
MOV _M	Move Multiple: disp bytes.	BIC _i	Clear selected bits.
MOVZ _{BW}	Move with zero extension.	XOR _i	Logical Exclusive OR.
MOVZ _{ID}	Move with zero extension.	COM _i	Complement all bits.
MOVX _{BW}	Move with sign extension.	NOT _i	Boolean complement: LSB only.
MOVX _{ID}	Move with sign extension.	Scond _i	Save condition code (cond) as a Boolean variable of size <i>i</i> .
ADDR	Move Effective Address.		

INTEGER ARITHMETIC

ADDi	Add.
ADDQi	Add 4-bit constant.
ADDci	Add with carry.
SUBi	Subtract.
SUBCi	Subtract with carry (borrow).
NEGi	Negate (2's complement).
ABSi	Take absolute value.
MULi	Multiply.
QUOi	Divide, rounding toward zero.
REMi	Remainder from QUO.
DIVi	Divide, rounding down.
MODi	Remainder from DIV (Modulus).
MEIi	Multiply to Extended Integer.
DEIi	Divide Extended Integer.

INTEGER COMPARISON

CMPi	Compare.
CMPQi	Compare to 4-bit constant.
CMPMi	Compare Multiple: disp bytes.

PACKED DECIMAL (BCD)

ADDPi	Add Packed.
SUBPi	Subtract Packed.

FLOATING POINT

MOVf	Move a Floating Point value.
MOVLF	Move and shorten a Long value to Standard.
MOVFL	Move and lengthen a Standard value to Long.
MOVif	Convert any integer to Standard or Long Floating.
ROUNDfi	Convert to integer by rounding.
TRUNCfi	Convert to integer by truncating, toward zero.
FLOORfi	Convert to largest integer less than or equal to value.
ADDf	Add.
SUBf	Subtract.
MULf	Multiply.
DIVf	Divide.
CMPf	Compare.
NEGf	Negate.
ABSf	Take absolute value.
LFSR	Load FSR.
SFSR	Store FSR.

SHIFTS

LSHi	Logical Shift, left or right.
ASHi	Arithmetic Shift, left or right.
ROTi	Rotate, left or right.

BITS

TBITi	Test bit.
SBITi	Test and set bit.
SBITli	Test and set bit, interlocked.
CBITi	Test and clear bit.
CBITli	Test and clear bit, interlocked.
IBITi	Test and invert bit.
FFSi	Find first set bit.

JUMPS AND LINKAGE

JUMP	Jump.
BR	Branch (PC Relative).
Bcond	Conditional branch.
CASEi	Multiway branch.
ACBi	Add 4-bit constant and branch if non-zero.
JSR	Jump to subroutine.
BSR	Branch to subroutine.
CXP	Call external procedure.
CXPD	Call external procedure using descriptor.
SVC	Supervisor Call.
FLAG	Flag Trap.
BPT	Breakpoint Trap.
ENTER	Save registers and allocate stack frame.
EXIT	Restore registers and reclaim stack frame.
RET	Return from subroutine.
RXP	Return from external procedure call.
RETT	Return from trap. (Privileged)
RETI	Return from interrupt. (Privileged)

CPU REGISTER MANIPULATION

SAVE	Save General Purpose Registers.
RESTORE	Restore General Purpose Registers.
LPRI	Load Dedicated Register.
SPRI	Store Dedicated Register.
ADJSPi	Adjust Stack Pointer.
BISPSRi	Set selected bits in PSR.
BICPSRi	Clear selected bits in PSR.
SETCFG	Set Configuration Register.

MEMORY MANAGEMENT

LMR	Load Memory Management Register. (Privileged)
SMR	Store Memory Management Register. (Privileged)
RDVAL	Validate address for reading. (Privileged)
WRVAL	Validate address for writing. (Privileged)
MOVSi	Move a value from Supervisor Space to User Space. (Privileged)
MOVUSi	Move a value from User Space to Supervisor Space. (Privileged)

ARRAYS

CHECKi	Index bounds check.
INDEXi	Recursive indexing step for multiple-dimensional arrays.

MISCELLANEOUS

NOP	No Operation.
WAIT	Wait for interrupt.
DIA	Diagnose. Single-byte.

CUSTOM SLAVE

CCAL0c	Custom Calculate.
CCAL1c	
CCAL2c	
CCAL3c	
CMOV0c	Custom Move.
CMOV1c	
CMOV2c	
CCMPc	Custom Compare.
CCV0ci	Custom Convert.
CCV1ci	
CCV2ci	
CCV3ci	
CCV4QD	
CCV5QD	
LCSR	Load Custom Status Register.
SCSR	Store Custom Status Register.
CATST0	Custom Address/Test. (Privileged)
CATST1	
LCR	Load Custom Register. (Privileged)
SCR	Store Custom Register. (Privileged)

STRINGS

MOVSi	Move String 1 to String 2.
MOVST	Move string, translating bytes.
CMPSi	Compare String 1 to String 2.
CMPST	Compare, translating String 1 bytes.
SKPSi	Skip over String 1 entries.
SKPST	Skip, translating bytes for Until/While.

BIT FIELDS

EXTi	Extract bit field (array oriented).
INSi	Insert bit field (array oriented).
EXTSi	Extract bit field (short form).
INSSi	Insert bit field (short form).
CVTP	Convert to Bit Field Pointer.

all in your **JULY** issue!

SIMPLE LOGIC ANALYSER

With four address, and two data displays this simple micro' debugging tool can reveal memory contents, look for preset data and generate an oscilloscope trigger pulse at the required time.



SLIDE DISSOLVE CONTROL

Ideal for the budding audio-visual enthusiast this dissolve unit allows two projectors to be coupled together to give a slide dissolve with automatic slide change on the dimmed projector.

Also...

ADD ON SUB-WOOFER

Fibre Optics

A FEATURE ARTICLE...

Fibre optics have generated a great deal of interest in recent years and we'll be looking at the way in which they are revolutionising both military and commercial systems as well as looking at the fibres themselves.

PRACTICAL

ELECTRONICS

THE JULY ISSUE IS ON SALE FRIDAY, JUNE 1ST

Spot Pricing

needs Electronics!

T.W. BERRIE Consultant

THE advent of cheap reliable small micro-computers, micro-processors and micro-controllers should usher in an era of spot-pricing for energy and public utility services which means cheaper energy and public utilities for all. To keep up the momentum, electronics experts must continue the good work by rising to the challenge, studying spot-pricing systems and putting the hardware and software elements of such systems together so that they work efficiently.

INTRODUCTION

The energy and public utilities sectors will have to depend a great deal for their future viability on electronic systems. Such sectors are desperate to get their prices down following the oil price rises of the 1970s, but to achieve this some drastic re-thinking and restructuring of their methods of planning and operation is needed. Fortunately today technology can cope with such re-thinking and restructuring by encouraging spot-pricing of these services, using the widest range of electronic systems now available. Massive savings could be achieved by using an interactive supply/demand spot-pricing system.

£200M per annum could be saved by remote meter reading

for instance. It is further estimated that £600-£700M might be saved from oil burning power stations if this type of control scheme were introduced.

The forecasting of demand is all important and an interactive control system could save another £500M here. Stand-by stations and peak-time power availability could be optimised. In all then savings in these sectors could reach £1400M+ per annum.

At present the planning of energy and public utilities' sectors is much complicated by the fact that it takes many years, possibly ten, to construct a project in them. The traditional planning process therefore tends to play safe by building up a margin of spare equipment in case, in the event, demand for energy or the services is greater than was forecast and/or more plant providing these services is out of commission than was forecast. Such margins of spare equipment can amount to 35% or more compared with planned requirements and they are very costly to provide. For operational planning, e.g. next week, month or year, smaller margins of spare equipment are planned for.

SPOT-PRICING

Spot-pricing eliminates this traditional "playing safe" in planning and operation because it ensures that the demand for the

Costs (at 1979/80 price levels)	Stage 1 1983	Stage 2 1984	Stage 3 1985	Stage 4 1986	Stage 5 1987	Stage 6 1988
1 Cumulative savings possible in England and Wales (see Part 1)	£100m	£350m	£650m	£900m	£1,100m	£1,400m
2 Savings per year equals capital charges per annum allowable in equipment for spot-pricing (per year)	£100m	£250m	£300m	£250m	£200m	£300m
3 Capital costs of equipment for spot-pricing (using 10% annuity factor) allowable (per year)	£1,000m	£2,500m	£3,000m	£2,500m	£2,000m	£3,000m
4 Number of consumers changed over to spot-pricing (per year)	50,000	150,000	500,000	5 million	10 million	5 million
5 Capital costs of equipment for spot-pricing allowable per consumer (3 + 4)	£20,000	£16,500	£6,000	£500	£200	£600
6 Allowable cost of microprocessors, activating devices and communications channel (per consumer)	£15,000	£12,500	£4,000	£300	£150	£350
7 Allowable cost of experimentation and consumer education (per consumer)	£5,000	£4,000	£2,000	£200	£50	£250
8 Main thrust of implementation	Large industrial and large commercial: initial stage	Large industrial & commercial: Follow-on stage	Medium industrial and medium commercial	Small commercial and residential: initial stage	Small commercial and residential: Follow-on stage	Residential: Final stage

Fig. 1. Implementation programme for interactive control with spot-pricing

energy or service in question in the event never exceeds the supply. It does this by:

- (i) charging short-run marginal cost prices.
- (ii) providing virtually instantaneous communication between supplier and consumer by electronic hardware and software systems which not only transmit information to ensure that supply and demand always balance but also control the joint producers/consumers systems to operate in an optimum manner, in real time if necessary.

ECONOMY

Economists are satisfied that spot-pricing jointly optimises the "welfare" (overall intrinsic benefits) of producers and consumers at any instant in time; this must be an improvement on the present pricing systems which are designed to optimise on a hypothetical situation expected to occur in the energy or public utility sectors at some point on the planning horizon. The spot-price for energy or a public utility service is the short-run variable costs, in the electricity case mainly fuel costs at any particular instant in time, except on those rare occasions when demand is trying to run ahead of supply, when a surcharge must be added to bring supply and demand back into line. There are no capital charges, fixed charges etc., because investment is part of a related but quite separate process to pricing. Investment will have a much more entrepreneurial nature. Spot-pricing enables all producers of energy or suppliers of the service, part-time or full-time, private or public, to fully play a part in supplying the total need, not as is the case today when part-time electricity generators, for example, do not get a fair price for their product.

IMPLEMENTATION OF SPOT-PRICING

Fig. 1 gives an illustration of the kind of stages of implementation of a spot-pricing scheme and of the costs and cost savings that might be involved. Such an implementation table must eventually be drawn up for all energy and public utilities sectors for every country in the world. Implementation may well be carried out first in the developing countries because these countries have most proportionally to gain from the savings made by spot-pricing, especially the oil-importing developing countries where both investment capital and fuels are in short supply.

The equipment needed for implementing spot-pricing is illustrated in Fig. 2 and Fig. 3. This equipment, especially when used in the industrial sectors, must allow data and information to pass accurately and instantaneously between producers and consumers and vice-versa. The equipment can be broken down into three broad categories:

- (i) Producer control and data/information, supplier/receiver apparatus.
- (ii) Consumer control and data/information, supplier/receiver apparatus.
- (iii) Transmission hardware and software systems between producers and consumers.

Fig. 4 (overleaf) shows this in greater detail.

Producers' and consumers' control apparatus has been under development for many years, e.g. to cater for the needs of load management control in the energy and electricity sectors, especially for industrial users. One such system has been devised by the South Eastern Electricity Board (Fig. 5). It incorporates microprocessor based Credit and Load Management Units (CALMU's). These units would replace present meters and their associated equipment. This system is in its infancy and at present is undergoing tests. What is needed after these tests is a hard look at how to make such apparatus as reliable and as cheap as possible, and to make any improvements in the other apparatus listed.

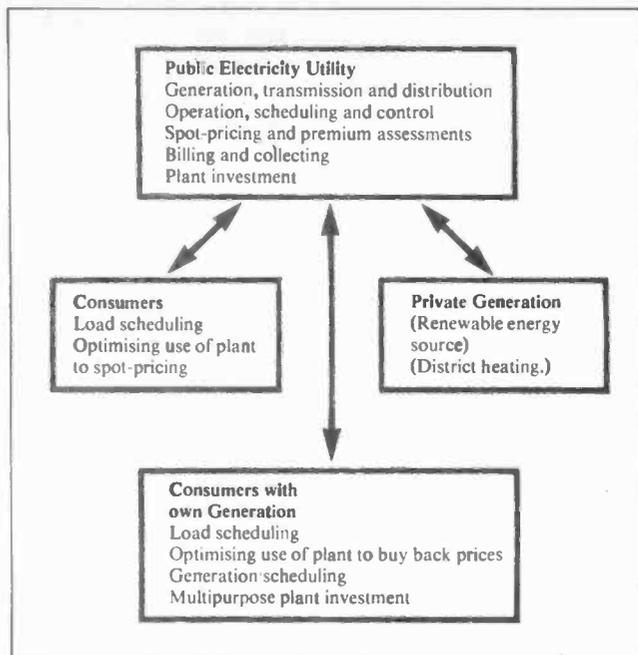


Fig. 2. The market place and institutional framework with full interactive control

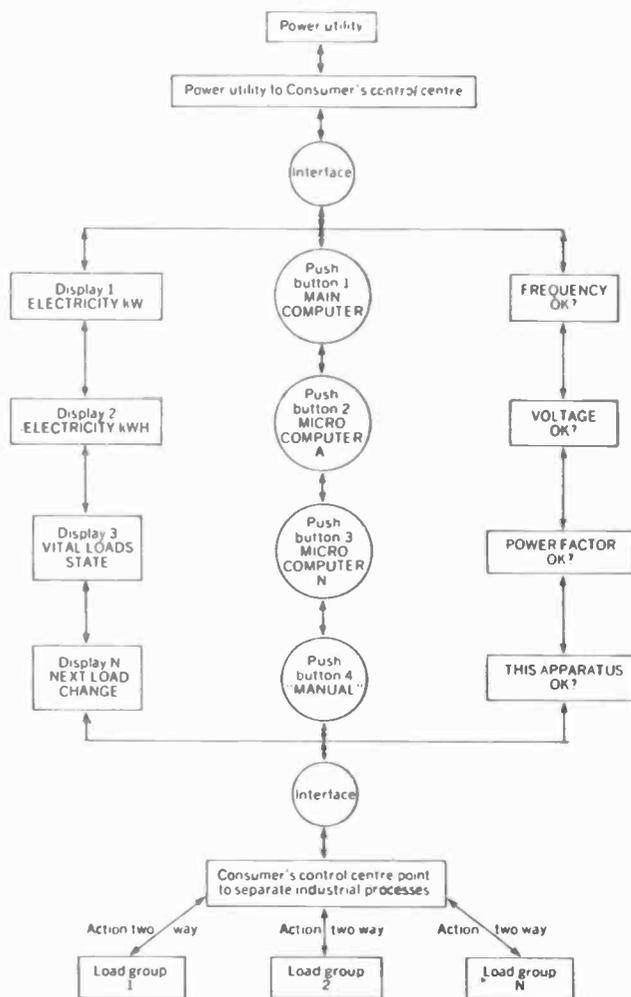


Fig. 3. Basic elements of an industrial consumer's interactive load control unit

Electricity Producers (full-time or part-time)

- Automatic generator control
- Automatic system control
- Automatic data collection, storage and processing
- Data and information systems
- Data transmission systems (internal)
- Management information systems
- Producers/consumers interfaces

Data Transmission

- Electricity, mains-borne
- Public radio, private radio, transmission and reception
- Public telecommunications network

Electricity Consumers (Industrial)


- Micro-computers and micro-processors
- Micro-controllers for industrial processes
- Data and information systems
- Data transmission systems (internal)
- Management information systems
- Consumers/producers interfaces

Electricity Consumers (Commercial and Domestic)

- Micro-computers
- Mini-controllers for energy and energy related systems
- Management information systems
- Consumers/producers interfaces

Other applications

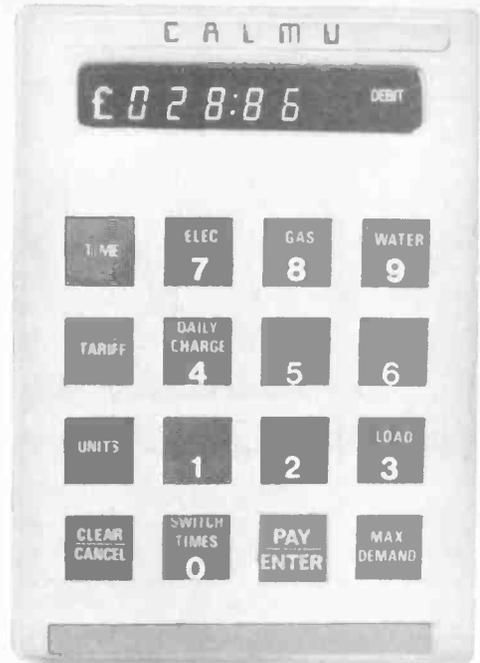- Remote reading of electricity, gas, water and telephone usage
- Payment of accounts for public utility and other services
- Consumer relations with producers
- Fault recording



Credit and Load Management Unit (CALMU). This microprocessor controlled consumer unit will interact with the electricity board, optimising tariff rates and replacing the old meter system

These three modes, and especially the first two, have undergone extensive testing over many years and must be counted as technologically proven. However, there is still room for improvement and reductions in cost.

Fig. 4. Opportunities for equipment manufacturers and contractors with energy spot-pricing

OPENING FOR ELECTRONICS

The author believes that spot-pricing of all energy and public utilities' services in every country in the world is inevitable and will be completed over the next 25 years. This includes a number of sectors: coal, oil, gas, electricity, water supply, telephones, roads, railways, shipping, airways, and probably banking and wholesale/retail marketing. The amount of cheap, reliable, small, efficient, plentiful electronic hardware and software equipment that will be required is truly immense, and it is up to the electronics industry as a whole to make it, sell it, supply it, test it, install it, and maintain it. ★

TRANSMISSION HARDWARE AND SOFTWARE SYSTEMS

Fig. 5 shows the three modes for data/information transmission:

- (i) Using the public utilities' own system of wires/pipes, etc.
- (ii) Using radio.
- (iii) Using the public telecommunications network (PTN).

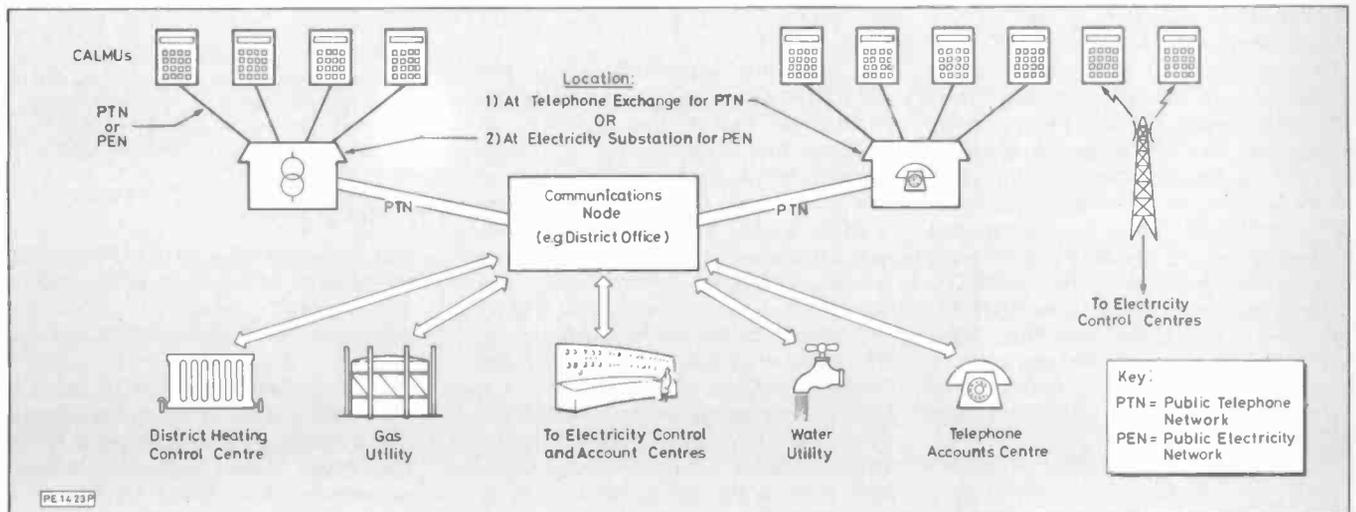


Fig. 5. SEEBoard CALMU interactive control communications network

INTRODUCTION TO DIGITAL ELECTRONICS

MICHAEL TOOLEY BA DAVID WHITFIELD MA MSc CEng MIEE

O & A Level CMOS

In this series so far we have used TTL gates to illustrate many of the basic principles of digital electronics. We also mentioned in Part One that these basic principles apply equally to logic families other than TTL, and in this last part of the series we will be looking to see how well the theory works in practice. As an alternative to the TTL family, we have chosen CMOS, a logic family which is fast emerging as a rival to TTL. We will start, therefore, by looking at some of the background to this emergence of CMOS as a popular general purpose logic family.

HISTORY OF CMOS

Until 1962 the only monolithic integrated circuits which were available used bipolar transistors as their basic active elements. In that year RCA developed the first i.c.s to use field effect transistors (FETs) as their basic elements. Since then, quite a number of ranges of digital i.c.s based on FET technology have been produced, and these have been given the general classification of MOS (metal-oxide-silicon) devices. Many of them actually now use a technology which has moved on beyond the basic FET, and usually now involves insulated gate FET types (IGFETs), but the general name remains. Some MOS digital logic uses only p-channel (PMOS) IGFETs, and some uses only n-channel (NMOS) IGFETs. The Complementary MOS (CMOS) logic family, however, uses a combination of both p-channel and n-channel IGFETs in its basic gate circuit.

Single-channel PMOS, developed from 1962 onwards, has been widely used in complex digital systems. Its use, however, has been largely con-

finied to custom-designed devices. PMOS is easily recognised because of its negative supply rail, and is commercially much easier to produce than NMOS. Even so, only a few off-the-shelf PMOS i.c. families have appeared from more than one manufacturer, and consequently there has been little support for PMOS as a general purpose logic family.

With CMOS, however, the story has been rather different. The first commercial CMOS logic circuits (the CD4000 series) were produced by RCA in 1968. Although successful in their own way, the real breakthrough came in 1971 with the introduction of the much improved CD4000A series. This was due in no small part to the simultaneous production of the first "COS/MOS Integrated Circuit Manual". This designer's handbook has since achieved the same sort of following as TI's legendary "TTL Data Book", and is required reading for any CMOS designer.

Since the introduction of the CD4000A series, the range and performance of CMOS has steadily improved, and CMOS i.c.s are now offered by a significant number of manufacturers. The current standard CMOS range, the CD4000B series, was introduced in 1976 and represents a very significant improvement over the earlier A-series. Meanwhile, CMOS technology continues to advance, and the latest high-speed CMOS has the speed and drive capability to match LSTTL. This brings the story of CMOS up to date and identifies the B-series as the designer's current standard. It is now time, therefore, for us to look at the technology behind the name: "What is CMOS?"

BASIC PRINCIPLES OF CMOS

We will begin our study of CMOS by looking at some of the basic characteristics of the most popular CMOS logic range. The essential features of the CMOS 4000B series are summarised in Table 1. We would point out

The circuits work over a very wide power supply voltage range, typically from +3 to +15 volts.

The output changes from 0 to 1 at exactly halfway between V_{DD} and V_{SS} , giving good noise immunity.

Operating current is extremely low, particularly at low switching frequencies. CMOS circuits consequently run very cool.

The inputs to gates behave almost as if they are open circuits, and are thus very easy to drive.

The unloaded output logic swing goes from V_{SS} to V_{DD} .


The output stages do not generate large current spikes on the power lines, and thus CMOS circuits generate little noise of their own.

The output transition times are usually longer than the gate delay times. This means that gates tend to swallow glitches and system noise.

Table 1. Essential features of CMOS logic

that the supply connections in CMOS are referred to as V_{DD} and V_{SS} , where the 'D' and 'S' refer to the drain and source of an n-channel FET, respectively.

The simplest of all CMOS gates is the inverter, and the internal circuit of a typical CMOS inverter is shown in Fig. 1. The circuit shows how an n-channel pull-down driver device (TR2), and a p-channel load device (TR1) are used in a complementary configuration. When

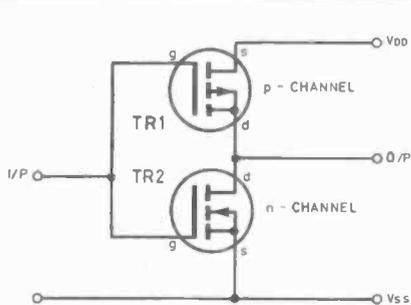


PE15226

Fig. 1. Internal circuit of a CMOS inverter

the output is at either logic 0 or logic 1, the gate draws only an extremely low (leakage) current from the supply. The only significant power dissipation therefore occurs during transitions of the input signal. This causes power dissipation in a CMOS circuit to depend primarily on the frequency of signal changes. The quiescent consumption is simply the product of supply voltage and the (very low) leakage current. This is in significant contrast to, say, TTL where the power dissipation is essentially constant.

The internal circuits for CMOS NAND and NOR gates are shown in Fig. 2 and Fig. 3, respectively. One of the things we notice when comparing these circuits with their TTL counterparts is the lack of an equivalent to the multi-emitter transistor which is characteristic of TTL gates. The FETs in the input circuit are distinct devices, rather than being part of any multi-gate FET arrangement. The end result, however, is little different since the advantages of FET technology remove the need for such a device; no overall advantage would be gained.

In practice, the complete circuits for these gates are rather more complex than those shown because, for clarity,

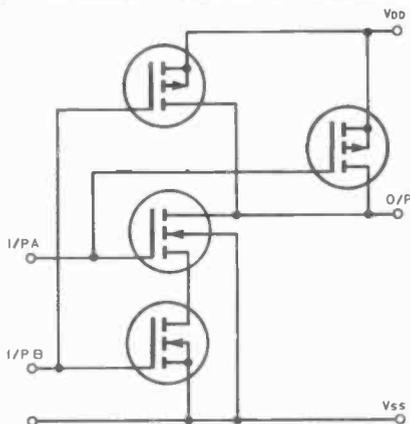


PE15236

Fig. 2. CMOS NAND gate circuit

we have omitted the diode clamp protection circuits which are usually found on the gate inputs. The breakdown voltage of the MOS gate oxide is about 100V, and although this may seem a lot, the very high resistance and low capacitance of the gate inputs mean that this voltage can easily be exceeded by static electricity. As may be imagined, this caused many problems with the handling of the early MOS circuits, and input clamp circuits are now usually to be found on each CMOS input. The input clamp circuits found in CMOS i.c.s are usually similar to the one shown in Fig. 4.

The internal circuits shown so far relate to the original A-series CMOS gates. The B-series was introduced in 1976 to overcome some of the shortcomings of the earlier CMOS devices. Internal buffers, usually consisting of a pair of inverters, were added to all outputs. The difference between the A- and B-series devices can be seen by looking at the internal circuit of a B-series NOR gate shown in Fig. 5. The equivalent logic arrangement for this circuit is shown in Fig. 6.

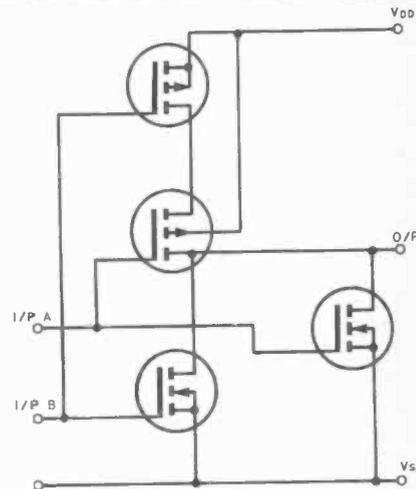

PE15246

Fig. 3. CMOS NOR gate circuit


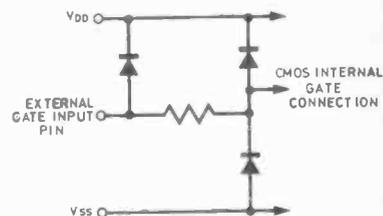


Fig. 4. Input clamp circuit

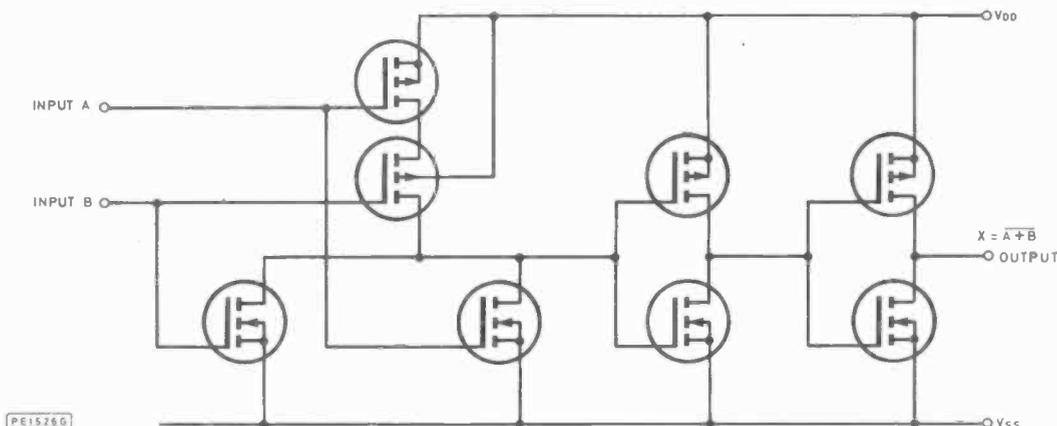

Fig. 6. Equivalent circuit for B-series NOR gate

These buffers equalise the output drive in both directions, equalise the signal rise and fall times, and improve the gate speed. In addition, the B-series generally puts right a number of 'undesirable' characteristics which found their way into some of the earlier A-series devices.



PE15260

Fig. 5. B-series CMOS NOR gate

A more recent development in CMOS is based on the B-series. The UB-series is similar to the B-series, but the gates have no output buffers, resulting in a reduced propagation delay, and hence increased speed. Generally speaking, the B-series devices have now completely replaced the A-series CMOS devices, and for the remainder of this article we will concern ourselves only with the B-series.

The transfer function for a CMOS inverter is shown in Fig. 7, and is significantly different from the com-

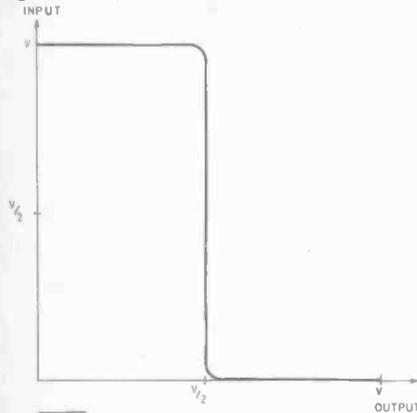


Fig. 7. Transfer function for a CMOS inverter

parable TTL characteristic. The output of a CMOS gate changes state exactly halfway between the two extremes of the power supply voltage limits V_{DD} and V_{SS} , usually the +ve and ground rails, respectively. This type of transfer function gives CMOS the best possible noise immunity. The actual logic thresholds for CMOS gates are given in Table 2, where we note that the thresholds are specified in terms of V_{DD} and V_{SS} , rather than absolute voltages. This is a reflection also of the wide range of supply voltages over which CMOS can operate.

Input Logic Thresholds	
Logic 0:	70% to 100% of V_{DD}
Logic 1:	V_{SS} to 30% of V_{DD}

Table 2. CMOS logic input thresholds

POWER SUPPLIES

CMOS is basically a low power logic family, and one which can operate from a wide range of supplies. The two supply rails for CMOS, V_{SS} and V_{DD} , are usually arranged so that V_{SS} is at 0 volts and V_{DD} is at +ve volts. This, however, is not always the case, and the supply rails could for example run at -5/+5 volts, respectively. For the remainder of this discussion, however,

we will assume the normal supply configuration.

CMOS will operate from any supply in the range +3 to +18 volts, and is reasonably tolerant of voltage ripple and line regulation. The optimum supply voltage, however, is in the range +9 to +12 volts, where fast operation, good noise immunity and high drive capability is available. At +5 volts, we find that these factors are degraded by a factor of about two. On the other hand, running CMOS at much above +12 volts does not provide any significant improvements in performance, and can lead to overheating problems.

Although CMOS is much more tolerant than TTL, it is still always good practice to pay due attention to proper supply decoupling and distribution. To this end, we can apply much the same rules to CMOS as we have been using for power supply distribution and decoupling in TTL circuits. If we follow the guidelines used for TTL, we will usually end up with a 'safe' design. In general, the current required from the power supply will be significantly less than a TTL circuit of comparable size. For example, a +12 volt, 200mA supply should be adequate for all but the largest CMOS circuits. We should always remember, however, that non-logic loads (such as l.e.d.s) require the same amount of power, irrespective of the logic family in use. This is an easy point to overlook. As always, it is better to play safe when designing the power supply and its distribution, rather than have to go back later and do it again properly.

Working out the expected power dissipation for a CMOS circuit is a little more involved than it was for TTL. This is due mainly to the fact that the supply current for a CMOS gate depends on switching frequency, in a manner

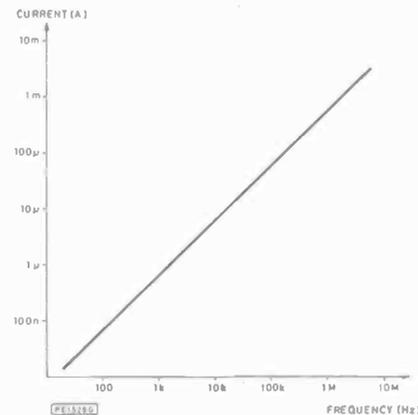


Fig. 8. Supply current variation with frequency

typically as shown in Fig. 8. In practice, i.e. supply current figures are usually quoted at one or more operating frequencies, and often for more than one supply voltage. Typically supply currents are quoted at 1MHz and at +5/+10/+15 volts. For intermediate conditions, we can calculate the corresponding figures from the fact that doubling/halving the frequency has the effect of exactly doubling/halving the supply current, respectively. Similarly, doubling/halving the supply voltage will double/halve the supply current.

As an example, a CD4000B NOR/inverter connected to a +10 volt supply will typically draw a quiescent current of around 10nA (0.00001mA). Operating at 1MHz, however, the supply current will typically rise to 0.6mA. Reducing the supply voltage to +5 volts, on the other hand, will cause the supply current to fall to 0.3mA. By reducing the frequency to 500kHz, the current will be further reduced to 0.15mA. For comparison, the supply current for a TTL 7400 gate is around 8 mA at a 50% duty cycle, and is substantially independent of frequency.

UNUSED INPUTS

CMOS logic gates are intended to be used in digital mode, with their inputs at either V_{SS} or V_{DD} , and under these circumstances we have seen that almost no supply current is drawn. If, however, an input is left to float, it can cause the gate to stray from its digital region into the linear (active) region. One effect of this change of operating mode will be to significantly increase the supply current being drawn. This rise in supply current will be in addition to the effect we encountered with TTL, and which applies equally to CMOS, whereby any floating input can cause the circuit to behave randomly.

Unlike TTL, a CMOS gate input cannot be assumed to take up any particular default state. Some positive action must therefore be taken to condition all unused gates/inputs in order to prevent unexpected circuit behaviour. In TTL, we are only normally concerned with unused inputs on gates actually being used in the circuit (e.g. the unused fourth input of a 4-input NAND gate). With CMOS, however, we must consider *all* of the gates in any i.c. which is connected to the power supply rails. If we forget about these otherwise unused gates, they may still consume considerable amounts of power. Since this rise in supply current

is often very difficult to track down, our basic rule should be to disable all unused gates when they are *first* put into the circuit. This will avoid many problems later.

We can disable CMOS inputs by connecting them directly to one of the supply rails, although which one is used will depend on the type of gate involved. One input of an AND/NAND gate connected to V_{SS} (logic 0) will disable the whole gate, whereas $+V_{DD}$ (logic 1) should be used for OR/NOR gates. Either of the supply rails may be used to disable buffers and inverters. As with TTL gates, unused inputs on multi-input gates may be tied to a used input in order to disable it and prevent unwanted circuit behaviour.

REAL CMOS GATES

Readers will by now probably have become familiar with the device numbers of at least a few of the more common TTL devices. As time passes, the pin numbers even start to spring readily (if not always correctly!) to mind—if in doubt always check with the PE Logic Design Cards. One of the problems often encountered when starting to use a new logic family is a feeling of being 'lost'. None of the familiar numbers apply any more, and the temptation is to return to TTL as 'the devil we know'. However, CMOS offers significant advantages over TTL in a number of areas, and even a limited study can pay substantial dividends. We will proceed, therefore, by trying to fill in some of the missing practical background by looking at some of the currently available CMOS devices.

Table 3 lists a selection of CMOS i.c.s from the 4000B series, together with typical figures for supply current when operating from a +5 volt supply at 1MHz. The gates are all available in standard 14-pin or 16-pin d.i.l. packages which are identical in outline to those we described for TTL devices.

Although CMOS devices are now much more robust than the early types, it is still advisable to observe some simple handling rules. The main problem, as we mentioned earlier, is that CMOS inputs represent a very high input resistance and a low capacitance. This means that a relatively small static charge can raise the voltage at the gate input to quite significant levels, and in extreme cases this can still damage the i.c.s, despite the input clamp circuits. The only safe way to store CMOS i.c.s, therefore, is

Device Number	Function	Package	No of Current Pins
NOR/NAND			
4002	Dual 4-input NOR		0.4mA 14
4012	Dual 4-input NAND		0.4mA 14
4025	Triple 3-input NOR		1.2mA 14
4023	Triple 3-input NAND		0.6mA 14
4001	Quad 2-input NOR		0.4mA 14
4011	Quad 2-input NAND		0.4mA 14
4078	8-input NOR		0.4mA 14
4068	8-input NAND		0.5mA 14
4000	Dual 3-input NOR plus inverter		0.3mA 14
4077	Quad Ex-NOR		0.2mA 14
4093	Quad 2-input NAND Schmitt		0.4mA 14
OR/AND			
4072	Dual 4-input OR		0.5mA 14
4082	Dual 4-input AND		0.5mA 14
4075	Triple 3-input OR		0.5mA 14
4073	Triple 3-input AND		0.5mA 14
4071	Quad 2-input OR		0.5mA 14
4081	Quad 2-input AND		0.5mA 14
4070	Quad Ex-OR		0.2mA 14
Buffers/Inverters			
4069	Hex inverter		0.5mA 14
4502	Hex inverter/driver 3-S		3.0mA 16
4049	Hex inverter/TTL translator		0.8mA 16*
4050	Hex buffer/TTL translator		0.8mA 16*
4041	Quad inverter/buffer		1.6mA 14
Flip-Flops			
4013	Dual D-type		0.8mA 14
4027	Dual J-K		0.4mA 16
4043	Quad R-S NOR		1.0mA 16
4044	Quad R-S NAND		1.0mA 16
Monostables			
4047	Single monostable		14
4098	Dual monostable		16

* V_{SS} = pin 8 and $+V_{CC}$ = pin 1
 All other devices have: V_{SS} = pin 7/8
 V_{DD} = pin 14/16

Table 3. A selection of CMOS devices

with all of the pins connected together in some way. This prevents any voltage difference between the gate input(s) and the rest of the i.c. The easiest methods of storing i.c.s in this way is to wrap them in aluminium foil, use black conducting foam (loaded with carbon particles), or keep them in anti-static i.c. carriers.

While in circuit, it is a wise precaution to ensure that any gate input which goes off the circuit board is never left completely unconnected and floating. A 1M Ω resistor between the gate input and ground will avoid this

problem, but without affecting normal circuit operation. The resistor provides a discharge path for the static, but without upsetting the logic levels.

PE LOGIC TUTOR WITH CMOS

Now that we are familiar with some of the basic principles, we can look at how the PE Logic Tutor can be used for developing CMOS circuits. In fact this turns out to be almost as easy as for TTL. No modifications, other than a few simple additions, are required in order to use the Logic Tutor with CMOS, so long as a +5 volt supply rail is adequate for the circuit in question. This will only actually be a limitation where high speed CMOS applications are involved.

This said, there are a number of factors which we *should* consider when using CMOS with the PE Logic Tutor, and which arise because it is basically a TTL unit. We hope to use the discussion of these points to demonstrate some of the techniques involved in interfacing CMOS to TTL. We begin by looking at the interface requirements and the buffer i.c.s which are available specifically for converting between CMOS and TTL.

INTERFACING CMOS AND TTL

The basic principle involved in interfacing between logic families is to make logic signals from one family appear as if they could have come from the other family, and vice versa. If we can do this for CMOS and TTL, we should then be able to connect CMOS and TTL circuits together and take advantage of the special features of both types of logic. As we might guess, the i.c. manufacturers have anticipated our needs in this area, and most of them provide a range of devices to simplify the interfacing task. Before looking at these i.c.s, however, we will first look at what is actually required to interface between TTL and CMOS. When discussing CMOS/TTL interfacing, we have limited the discussions which follow to the most common situation of CMOS operating from the same +5 volt supply as the TTL circuits.

TTL TO CMOS

At the input of a CMOS gate, the logic levels should ideally be kept as close as possible to 0V and +5V, for logic 0 and logic 1, respectively. In extreme cases these levels can be allowed to rise/fall to +1.5V and +3.5V, respectively. In practice, however, it is generally recommended

that the input signals should keep logic 0 below 1V and logic 1 above 4V. Looking back to TTL's output specifications, we recall that logic 0 is below 0.8V, and logic 1 is above 2.4V. A TTL logic 0, therefore, represents no problem at a CMOS input, but something must be done, however, to guarantee that the logic 1 level provided by a TTL gate (still marginal at typically +3.5V) is correctly recognised by a CMOS gate. What we need to do is to pull the logic 1 level closer to the positive supply rail, while leaving the logic 0 level unaffected.

The usual method of interfacing a TTL output to a CMOS input is shown in Fig. 9, and this arrangement works

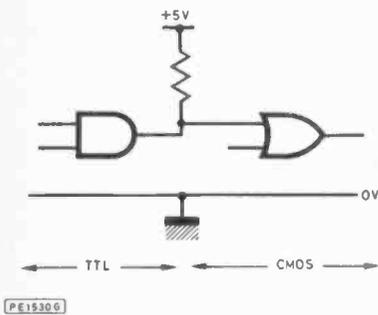


Fig. 9. Driving CMOS from TTL

equally well for any of the TTL sub-families. Because CMOS inputs behave almost like open circuits, and require only around 100nA each, there is no problem obtaining the necessary drive current from a TTL gate. A single TTL gate can then drive almost any number of CMOS gates, and the usual practical limit of around 50 is due more to the extra capacitance represented by each additional gate connected, than any inherent drive limitation.

CMOS TO TTL

At the output of a CMOS gate, we find that the voltages used for logic 0 and 1 present no problems for TTL gates. The problem, instead, is with the available drive current—just the opposite of the situation at a CMOS input! A B-series CMOS gate is able to sink approximately 0.44mA at logic 0, and source approximately 0.16mA at logic 1. This compares with the current requirement of 1.6mA per standard TTL load at logic 0. There is, however, sufficient drive available for a standard B-series CMOS output to drive *one* (and only one) LS TTL gate. This has the additional benefit of allowing us to use an LS TTL gate as a high drive CMOS buffer.

To allow CMOS circuits to drive more than one LS TTL load, or any standard TTL loads at all, we must provide additional current-driving capability. The simplest way of doing this is to use one of the CMOS-to-TTL converters, the most common of which are the 4049 and 4050 hex inverters and buffers, respectively. These are each able to drive up to two standard or four LS TTL loads, or any other equivalent load requiring up to 3.2mA of current sinking capability. These devices are extremely useful in all types of interfacing applications, and we will now look at how they can be used to help CMOS circuit development with the PE Logic Tutor.

THE 4050 AND 4049 TTL BUFFERS

The internal arrangement of the 4050 hex non-inverting buffer and TTL driver is shown in Fig. 10. We note in

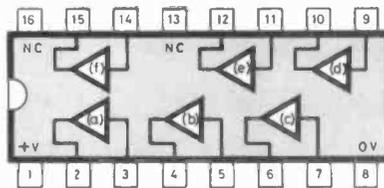


Fig. 10. The 4050 non-inverting CMOS/TTL buffer

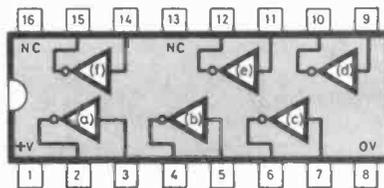


Fig. 11. The 4049 inverting CMOS/TTL buffer

passing that the CMOS/TTL buffers are among the few i.c.s in the B-series which do *not* follow the standard arrangement of power supply pin numbering. The six buffers in the package are all electrically identical, and each can drive up to two standard TTL loads, or their equivalent. The 4049 is the inverting version of the 4050, and is otherwise similar in all respects. The internal arrangement of the 4049 is shown in Fig. 11. Both the 4049 and the 4050 can operate from power supplies in the range 3V to 15V, but must be used from a +5V supply when used with TTL.

In order to use the PE Logic Tutor to

full effect with CMOS, we should ideally buffer some of its facilities. The logic state indicators in particular should be buffered for reliable operation, although in many cases they will not adversely affect the circuit if this is not done. We suggest that a 4050 non-inverting buffer is used between the CMOS circuit and the indicators D1 to D4. This may be wired up in a convenient socket, and then used for all future CMOS circuit development. The modified logic state indicator circuit then becomes as shown in Fig. 12. We

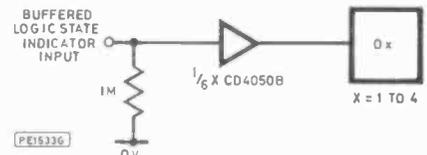


Fig. 12. Logic state indicators modified for CMOS

have included 1MΩ pull-down resistors in order to protect the floating logic state indicator inputs. The two unused buffers in the package must also be disabled to prevent excessive current drain.

The preferred method of wiring up the modified indicator circuits (or any other CMOS circuit) is to install the wiring first, and only *then* insert any i.c.s; this minimises the possibility of any static-induced damage. The links required for a 4050 in socket B are as follows:

- B3 to 0V (via 1MΩ) ... New D1 i/p
- B2 to D1
- B5 to 0V (via 1MΩ) ... New D2 i/p
- B4 to D2
- B12 to 0V (via 1MΩ) ... New D3 i/p
- B11 to D3
- B15 to 0V (via 1MΩ) ... New D4 i/p
- B14 to D4
- B7 to 0V (Unused gate i/p)
- B9 to 0V (Unused gate i/p)
- B1 to +5V(Supply)
- B8 to 0V (Supply)

With the circuit above completed, the logic state indicators D1/D2/D3/D4 now have their inputs at pins B3/B5/B12/B15, respectively.

In order to ensure that the logic level generators S1/S2/S3/S4 and the CLOCK all produce CMOS-compatible logic levels, we must add five 2.2kΩ pull-up resistors at the signal outputs. Each should be connected between one of the S1/S2/S3/S4/CLOCK connectors, and a convenient +5V point. The generators/clock sources may then be used as for TTL.

Now that we have optimised the Logic Tutor for CMOS, we can conclude this final part of the series by looking at a few examples of practical CMOS circuits. Rather than repeat any of the ideas used for TTL, which for the most part will work just as well in CMOS, we will concentrate on applications which are special to CMOS.

TOUCH SENSITIVE SWITCHES

Touch sensitive switches are an increasingly common part of everyday life. They have come into widespread use mainly as a result of the development of MOS technology, which allows them to be produced easily at low cost. We can actually make a touch sensitive switch from standard CMOS logic gates, although in many applications custom-designed multiple-switch i.c.s are used. Whichever implementation is chosen, the basic principles remain the same.

Touch sensitive switch circuits all have one feature in common; they have a very high input impedance. We have seen, however, that this is also true of a CMOS gate input, which typically has an input impedance in excess of 100M Ω . The problem facing us as designers is how to use this property to produce a touch sensitive switch? We know that the high impedance/low capacitance of a CMOS input means that only a very low charge is required to influence the voltage at the input. The human body acts as a quite reasonable aerial when it comes to picking up 50Hz hum from the electrical field produced by the mains distribution system. Thus contact with the hand can be used to trigger a suitable high impedance switch.

The circuit shown in Fig. 13 is based on the 'human aerial' effect. The figure shows the complete circuit, including

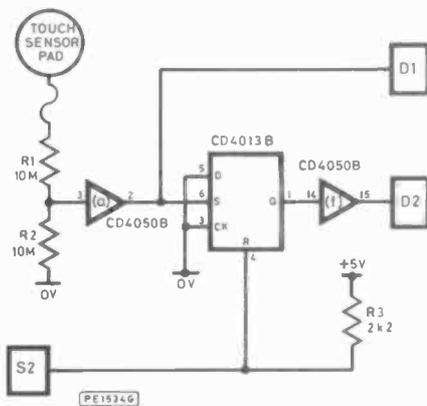


Fig. 13. Touch sensitive switch circuit

all of the necessary interfacing between CMOS and the Logic Tutor. The sensor pad is connected to R1, and can take any convenient form, e.g. a small circular piece of foil or copper laminate. For initial tests, the lead of R1 itself is quite adequate. Large sensors should, however, be avoided because they tend to act as aerials in their own right, and thus reduce the sensitivity of the switch. If we experiment with ever-larger pieces of foil, there eventually comes a point when the switch is always on. The switch circuit works most reliably if it has a good earth, but it will usually work quite adequately without any additional earthing.


The sensor pad is connected via R1 to the input of one of the CMOS/TTL translators in a 4050. R2 is included in the circuit to tie the input to ground when no signal is present; the switch behaviour is otherwise indeterminate. The combination of R1 and R2 sets the sensitivity of the switch, which should be kept as low as possible. Reducing R1 or increasing R2 increases the sensitivity, but be warned that a high sensitivity makes the circuit more liable to static damage and/or false switching caused by power transients, etc. The output of the gate is connected to the Set input of a 4013 D-type latch (similar to the TTL 7474, but with non-inverted Set/Reset inputs). This latch is set whenever the switch is activated, and remains in this state until reset by pressing S2 (whose output is pulled up by R3). The output state of the switching gate is shown by D1, while the output of the overall switch (i.e. the Q output of the latch) is shown by D2.

The circuit is built on the Logic Tutor by inserting a 4050 into socket B (pin 1 in B1), and a 4013 into socket F (pin 1 in F1), and adding the following links:

- B3 to 10M Ω (R1: to touch sensor)
- B3 to 10M Ω (R2: other end to 0V)
- B2 to D1 (Switch o/p display)
- B2 to F6 (Switch o/p to latch)
- F5 to 0V (Disable D i/p)
- F3 to 0V (Disable CK i/p)
- S2 to 2.2k Ω (R3: other end to +5V)
- S2 to F4 (Reset i/p)
- F1 to B14 (Latch o/p)
- B15 to D2 (Latch o/p display)
- B5 to 0V (Disable i/p)
- B7 to 0V (Disable i/p)
- B9 to 0V (Disable i/p)
- B11 to 0V (Disable i/p)
- F10 to 0V (Disable i/p)
- F11 to 0V (Disable i/p)
- F12 to 0V (Disable i/p)
- F13 to 0V (Disable i/p)

- B1 to +5V (Supply)
- B8 to 0V (Supply)
- F15 to +5V (Supply)
- F7 to 0V (Supply)

As a final thought on touch switches, we invite readers to extend our simple switch circuit for use as an intruder alarm. Adding a single 4000 i.c. should make it possible to cause the switch to trigger a pair of alternately flashing lights whenever the sensor is touched. As a suggestion, use the inverter in the 4000 to produce anti-phase CLOCK signals to apply to the two OR gates, use the \bar{Q} output from the latch to drive both OR gates, two 4050 buffers to interface the OR gate outputs to D3/D4, and don't forget the unused OR gate inputs! The whole circuit should still be reset by pressing S2. The internal circuit and pin configuration for the 4000 dual 3-input NOR gate plus inverter is shown in Fig. 14.

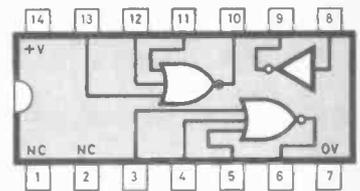

FE1535G

Fig. 14. The 4000 dual 3-input NOR plus inverter

LIQUID DETECTORS

Touch switches are not the only way we can take advantage of the high input impedance of CMOS gates. Liquid level detectors are another interesting application area, and here we use the conductivity of the liquid itself to activate a CMOS switch. Liquids are usually considered to be poor conductors, representing high impedances to the flow of electrical current. In CMOS terms, however, liquids must be viewed in a rather different light. The conductance of many liquids is actually enough to allow simple fluid detector circuits to be easily constructed.

The circuit of Fig. 15 shows a simple liquid level detector. The liquid sensors can be any convenient conductors, such as two lengths of bared wire, or a pair of Veroboard tracks. Using two tinned wires 10mm apart, D1 is illuminated when they just touch the surface of a glass of water. A damp sponge has a similar effect, and the sensitivity of the switch can be varied by changing the spacing of the sensors or the value of R1. These simple sensors are suitable for a wide range of applications, and due to their low cost, a

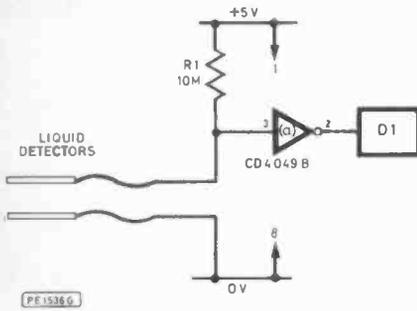


Fig. 15. Liquid level detector circuit

large number can easily be used to give accurate monitoring. It is an interesting experiment to try different sensors and adjust the switch sensitivity to allow

the ultimate in gardening luxury—automatic garden watering! The idea is to detect the falling conductivity of soil as the moisture content of the soil falls, and then turn on the sprinklers.

These few examples give an idea of the versatility of CMOS, and indicate that it is a logic family with which it is fun to experiment. It obeys all the laws of standard logic, but has a number of added advantages, not least of which is very low power consumption. When used in conjunction with TTL, the designer has perhaps the best of both worlds.

We hope this brief look at CMOS will give readers the confidence to experiment with this 'new-fangled' logic family. Good luck!

74C00 SERIES

As a final note, we feel it necessary to mention the existence of one other rather interesting CMOS family. The 74C00 series is a pin-for-pin, function-for-function equivalent to the various 7400 TTL sub-families. All of the 74C00 series devices are compatible with low power TTL, and their outputs are each capable of driving one LS TTL load. As such, the family can provide a very convenient way of converting an application from TTL to CMOS with the minimum of circuit modification. It is perhaps worth considering the 74C00 series as a possible alternative introduction to CMOS. ★

FREE! READERS' ADVERTISEMENT SERVICE

PE BAZAAR

RULES Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a cut-out valid "date corner". Ads. will not appear (or be returned) if these rules are broken.

WANTED manual to buy or loan for Teletype oscilloscope, type D43, time base type TD41. R. Lilley, 184 Mitchel Hey, College Bank Rd., Rochdale, Lancs. Tel: 0706 359389.

I.C.'s for sale TMS 4030 40 off @ 50p. 8279 3 off @ £2. 8755 8 off @ £2. 2516 @ £1. 08833 4503. Mr. G. Heath, 103 Pollards Oak Road, Ox-ted, Surrey RH8 0JE. Tel: Oxted 4503.

TANDY DMP100 Graphics printer par/serial interface. As new with lead, manual, paper. Cost £299. Now £185. Derek Kennedy, 12 Herries Road, Glasgow G41. Tel: 041 423 2115.

WANTED broken Spectrum for bits. Dave Stewart. Tel: 0772 634897 Mr. D.I. Stewart, 22 Blenheim Drive, Warton, Lancs. PR4 1DH.

ULTIMUM mother board (working) in case with all psu's. Also chips for 16K Ram board £50. Mr. J. Stevens, 18 The Harrage, Romsey, Hants. Tel: (0794) 515884.

DATA dynamics 390 teletype. Includes printer, keyboard, punch, reader, pedestal, and RS232 interface. £50. Tel: Horndean 592036 M. Droney.

WANTED UK 101 Memory expansion board, eg magnum electronics type. Have one already and need further 8-16K. C. F. Bashford, 12 Swansholme Gardens, Sandy, Beds. Tel. (0767) 80860.

BI Directional printer RS323/Centronics interfaces. Can be seen working or s.a.e. for print out. Phone Southampton (0703) 788278. £125. R.H. Pearce, 8 Holly Oak Road, Coxford, Southampton SO1 6GD.

ELECTRONIC ignition. Capacitive discharge for negative or positive earth (no data). £6.50. Write or phone. T.C. Sheridan, 46 Seymour Court, Whitehall Road, North Chingford, London E4 6DZ. Tel: 01-529 0612.

WANTED Add On RAM for 8K UK101, 32K if possible. T.E.D. White, The Gate, Llandinam, Powys. Tel: Caerswys 630.

TEKTRONIX 502A Scope. User Manual and or Circuit Schematic wanted. J. Bartle, 28 High Street, Bishopston, Stockton-on-Tees, Cleveland TS21 1HA. Tel: 0740 30512.

CLEARING out mixed bags transistors, capacitors, resistors. 100+ items £2.50. Pots 22K LIN 10 £1. (List s.a.e.). D. Martin, 29 St. Johns Close, Leatherhead, Surrey.

PC1500, Printer, 4K Rampack, power supply, manuals, case, all user-magazines and machine code details. £200. Dave Jackson, Liverpool. Tel: 051-489 9842.

WANTED Television magazine 1976-1981. Must be complete. Also 8 amp Variac. Must be v.g.c. Brian Ward, Burnley. Tel: (0282) 50574.

COLLINS mechanical filters 455kHz, 3.1kHz, 1.5kHz BW. Mullard crystal filter 455kHz, 600Hz BW. £6 ea. Chelmsford 59033. J. H. Gooday, 53 Lawn Lane, Chelmsford, Essex.

I need back numbers of Practical Electronics in 1982 and 1983 years. Ali Reza Mahabadi, 121 Emam Mousa Sadr Street, Rey Avenue, Tehran 11797, Iran.

TEST equipment HP5245L counter £75. HP606A H.F. generator £50. Advance HI audio generator £10. Chelmsford 59033. J. H. Gooday, 53 Lawn Lane, Chelmsford, Essex.

TWO Mullard fast valve testers with cards £35; Avo valve tester and analyser with manual £28. Mr. A. Mabrouk, 21 Redington House, Rodney Street, London N1 9QQ. Tel: 01-278 4806.

TRIO TR2300 £100. New 4CX250B plus base and chimney £60. Kenwood DM81 DIP-Meter £25. C. Leyson, 56 Park Road, Whitchurch, Cardiff. CF4 7BR. Tel: (0222) 626466.

WANTED: Ohio 610 Board and DOS 65D3.3 or Vortex + FDC. Ockier Jan, MGR Christiaensstraat 16, 8880 Tielt, Belgium.

8" disk drive, with interface for the UK101. Power supply, leads, manuals and operating software. £220. D. Fellows, 26 Westbourne Avenue, Emsworth, Hants. PO10 7QU. Tel: (02434) 5548.

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a cut-out valid date corner.

SignatureDate

Please read the RULES then write your advertisement here— one word to each box. Add your name, address and/or phone no.

COUPON VALID FOR POSTING BEFORE 1 JUNE 1984

(One month later for overseas readers.)

SEND TO: PE BAZAAR, PRACTICAL ELECTRONICS, WESTOVER HOUSE, WEST QUAY ROAD, POOLE, DORSET BH15 1JG.


BLOCK CAPITALS PLEASE

Name & Address:			

For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a cut-out valid "date corner"

BI-PAK BARGAINS


PRECISION MORSE KEYS

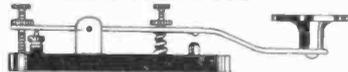

Well designed beginners key. Fully adjustable. Dims: Base 82mm x 45mm. O/No. VP 122. **£1.85**



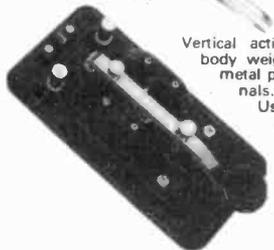Double-paddle, squeeze action. Body dims: 83 x 65 x 35mm. Weight 150g. O/No. VP 123. **£20.00**



Vertical action. Robust ABS body weighted with heavy metal plate. Screw terminals. Silver contacts. Usual adjustments. Body dims: 150 x 75 x 50mm. Weight 0.5kg. O/No. VP 124. **£21.00**

ANTENNA SWITCH 2 and 3 WAY

Co-axial switch for one transceiver to two antennae or one antenna to two transceivers. Dims: 86 x 55 x 32mm (Body). O/No. VP 113. **£4.50**

As above but 3-way. O/No. VP 114. **£4.75**

HIGH PASS FILTER/SUPPRESSOR

CB/TV. High pass filter. Reduces unwanted signals picked up by antenna. Dims: 45 x 25 x 17mm. O/No. VP 115. **45p**

LOW PASS FILTER

Designed to reduce harmonics on the VHS and TV band. Cut-off frequency: 30MHz V.S.W.R.: Less than 1.2 to 1. Insertion loss: -0.2dB @ 27MHz Impedance: 50ohms. Dims: 80 x 55 x 40mm. O/No. VP 116. **£2.75**

ANTENNA COUPLER

Transceiver/car radio antenna coupler. With co-axial cables. One co-axial terminates in antenna plug and the other in PL259 plug. Dims: 67 x 46 x 30mm. O/No. VP 117. **£2.00**

TAPE RECORDER SWITCH

Unit to control motor of tape recorder. 1.8m cord and 2.5mm plug attached. On/Off switch. Dims: 55 x 20 x 20mm. O/No. VP 127. **£1.00**

DC-DC POWER SUPPLY

DC to DC adaptor. Plugs into car lighter aperture. Output 3, 4.5, 6, 7.5, 9, 12V @ 800mA. Has universal output spidger plug, also 9V battery snap and polarity reversing facility. O/No. VP 119. **£2.45**

SPEAKER PROTECTOR

Limits voltage to speaker or to the permissible max. by automatically introducing a resistor in series with speakers. When excessive voltage is reduced the unit resets itself. Electronic voltage-sensing relay circuit. Spring terminals. Cut-off level adjustable from 10W-120W. Full instructions included. Dims: 85 x 74 x 25mm. O/No. VP 118. **£9.95**

ELECT & PIEZO BUZZERS



PIEZO
Miniature round piezo-electronic buzzer. White plastic. Low consumption. Frequency: 4Hz approx. Output: 100dB (A) @ 1.1y. Power: 127mW @ 4mA. Dims: 22 (dia) x 11.5mm. Fixing Centres: 26.5mm. O/No. VP 107. **95p**



PIEZO
Piezo buzzer. White plastic. 90mm leads for use on a.c. mains. Frequency: 3.5kHz approx. Output: 85dB (A) @ 1m ty. Power: 24W @ 5mA. Dims: 32 (dia) x 14mm. Fixing centres: 38mm. O/No. VP 108. **£1.15**



ELECTRONIC
Miniature electronic buzzers. Solid state. Ivory plastic. 150 leads. Frequency: 500 Hz approx. Dims: 22 x 16 x 15mm. Output: 82dB (A) @ 1m ty. Fixing centres: 26mm. 5V 25mA. VP 83. 3V 25mA. O/No. VP 82. 9V 25mA. O/No. VP 84. **80p each**

SUB-BOX

A neat swivelling disc provides close tolerance substitution resistors of 35 preferred values from 50ohms to 1Kohm. Simply fix clips into circuit and swivel until optimum result is achieved. O/No. VP 112. **£4.75**

MINIATURE VICE

Miniature plastic and metal vice with strong suction base for portability. Single action to secure or release suction. Plastic jaws with rubber pads 20mm wide, open out to 40mm. Dims: 85 x 65 x 60mm approx. **FANTASTIC VALUE** O/No. VP 95 ONLY **£1.60**

LEARN A LINGO!

PILLOW SPEAKER
Slim under pillow unit. 8ohms 2" speaker. 1.5m lead with 3.5mm mono jack plug. Black. Dims: 65 (dia) x 17mm. O/No. VP 88. **£1.25**

METRIC & BRITISH MEASURES

Steel tapes in sturdy ABS plastic case. Silk wrist strap. These yellow coated convex tapes have inch and metric graduations. Automatic push-button return. 2m long x 13mm wide. O/No. VP 89. **£1.00**
3m long x 13mm wide. O/No. VP 90. **£1.50**
5m long x 16mm wide. O/No. VP 91. **£2.00**

BATTERY TESTER

Tests all types of battery including standard, NICAAD, Alkaline etc. Takes all standard sizes including 6V lantern batteries and watch/hearing aid cells. Also tests fuses and lamps by means of internal 9V (PP3) battery. Can also be used to recharge NICAAD batteries by means of external 3.12V d.c. power supply (not included). Full instructions provided. Dims: 185 x 103 x 30mm (approx). O/No. VP 101. **£7.00**

FM MONITOR

FM monitor for 2 metre band. All metal. Attached earphone PL259/SO239 connectors. 144MHz 10W maximum. Dims: (body) 55 x 30 x 23mm. O/No. VP 120. **£4.20**

DUMMY LOAD

50 ohms 30W. UHF co-axial plug fitting (PL259). O/No. VP 121. **£5.20**

PICK-UP COIL

Large telephone pick-up coil for high sensitivity. Section paid to stick to telephone 30cm lead to 35 jack plug. Connects direct to cassette recorder. Dims: 32 (dia) x 17mm (body) 36mm (dia) x sucker. **£1.00**

VALUE PACKS

Pak No.	Qty	Description	Mixed Types	Price
VP1	300	Assorted Resistors		£1.00
VP2	300	Carbon Resistors	Watt Pre-Formed	£1.00
VP3	200			£1.00
VP4	150	Watt Resistors	100 ohm 1/4W Mixed	£1.00
VP5	200	Assorted Capacitors	All Types	£1.00
VP6	200	Ceramic Caps	Miniature - Mixed	£1.00
VP7	100	Mixed Ceramic Disc	1pf - 50pf	£1.00
VP8	100	Mixed Ceramic Disc	50pf - 100pf	£1.00
VP9	100	Assorted Polyester/Polystyrene Caps		£1.00
VP10	80	C280 Type Caps	Metal Foil Mixed	£1.00
VP11	100	Electrolytics	All Sorts	£1.00
VP12	60	Bread Type Polystyrene Mini Caps		£1.00
VP13	50	Silver Mica Caps	Ass 1.5pf - 150pf	£1.00
VP14	50	Silver Mica Caps	Ass 180pf - 4700pf	£1.00
VP15	50	High Voltage Disc	Ceramic 700v - 8kv Mixed	£1.00
VP16	50	Wirewound Res	9W (avg) Ass 1 ohm - 17k	£1.00
VP17	50	Metres PVC Covered Single Strand	Wire Mixed Colours	£1.00
VP18	30	Metres PVC Covered Multi Strand	Wire Mixed Colours	£1.00
VP19	40	Metres PVC Single/Multi Strand	Hook-Up Wire Mixed	£1.00
VP20	6	Rectifier Switches	5 Amp 240v	£1.00
VP21	20	Pcs 1 - 2 & 4 mm Plugs & Sockets	Matching Sues	£1.00

VP22	20	Sq. Inches Total Copper Clad Board	Mixed Sizes	£1.00
VP23	20	Assorted Slider Pots	Mixed Values	£1.00
VP24	10	Slider Pots	40 mm 22K 5 x Log 5 x Lin	£1.00
VP25	10	Slider Pots	40 mm 47K 5 x Log 5 x Lin	£1.00
VP26	20	Small .125" Red LEDs		£1.00
VP27	20	Large 2" Red LEDs		£1.00
VP28	10	Rectangular 2" Green LEDs		£1.00
VP29	30	Ass. Zener Diodes	250mW - 7W Mixed Vts Coded	£1.00
VP30	10	Ass 10W Zener Diodes	Mixed Vts Coded	£1.00
VP31	10	5 Amp SCRs	TO-66 50-400v Coded	£1.00
VP32	20	3 Amp SCRs	TO-66 Up To 400v Uncoded	£1.00
VP33	200	SA Diodes	Switching Like IN4148 DO-35	£1.00
VP34	200	SA Diodes	Gen. Purpose Like DA200/BA113/16	£1.00
VP35	50	1 Amp IN4000 Series SA Diodes	Uncoded All Good	£1.00
VP36	8	Bridge Rects	4 x 1 Amp 4 x 2 Amp Mixed Vts Coded	£1.00
VP37	8	Black Instrument Type Knobs	With Pointer 1" Std	£1.00
VP42	10	Black Heatsinks	To Fit TO-3 TO-220 Ready Drilled	£1.00
VP43	4	Power-Fin Heatsinks	2 x TO-3 2 x TO-66 Size	£1.00

TRANSISTOR CLEARANCE

All Sorts Transistors. A mixed bag NPN-PNP Silicon & Germ. Mainly Uncoded You To Sort Pack includes Instructions For making Simple Transistor Tester. Super Value. Order No. VP60. **£1.00**

BI-PAK SOLDER — DESOLDER KIT

Kit comprises: O/No. VP 80
1 High Quality 25 Watt General Purpose Lightweight Soldering Iron 240v mains incl. 3/16" (4.7mm) bit.
1 Quality Desoldering Pump High Suction with automatic ejection Kuratied anti-corrosive casing and TeFlo nozzle 1.5 metres of De-Soldering braud on plastic dispenser.
2 yds (1.83m) Resin Cored Solder on Card
1 Heat Shunt too tweezer Type
Total Retail Value over £12.00
OUR SPECIAL KIT PRICE £9.95

BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
1 Expo Mini Drill 10000RPM 12Vd.c. incl. 3 collets & 3 x Twist Bits
1 Sheet PCB Transfers 210mm x 150mm
1 Etch Resist Pen
1 Jib pack FERRIC CHLORIDE crystals
3 sheets copper clad board
2 sheets Fibreglass copper clad board
Full instructions for making your own PCB boards
Retail value over £15.00
DUR BI-PAK SPECIAL KIT PRICE £9.95
ORDER NO. VP 81

TECASBOTY

THE ELECTRONIC COMPONENTS AND SEMICONDUCTOR BARGAIN OF THE YEAR!

This collection of Components and Semiconductors for the hobbyist is probably the most value-packed selection ever offered, it consists of Resistors, carbon and wirewound of various values. Capacitors: All types, sorts and sizes including electrolytics. Potentiometers - single, dual, slider and preset. Switches, Fuses, Heatsinks, Wire, P.C.B. Board, Plugs, Sockets etc.. PLUS a selection of Semiconductors for everyday use in popular Hobby Projects. These include: SCR's, Diodes, Rectifiers, Triacs & Bridges as well as a first class mix of Transistors and I.C.'s. In all, we estimate the value of this in current retail catalogues to be over £25! So, help yourself to a great surprise and order a Box TODAY for ONLY at BI-PAK. Remember, stocks are limited so - hurry! You can call us on 0920 3182/3442 and order just **£6.50** with your Barclaycard or Access Card - 24hr Answerphone Service NOW. Order No. VP 85.

OUR GREAT NEW 1984 CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components. Semiconductors and other Accessories ALL at realistic prices. There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what he have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO. We hold vast stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock. The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

To receive your NEW 1984 BI-PAK Catalogue, send 75p PLUS 25p p&P to:-

BI-PAK

Send your orders to Dept PEG BI-PAK PO BOX 6 WARE, HERTS SHOP AT 3 BALDOCK ST. WARE, HERTS TERMS CASH WITH ORDER, SAME DAY DESPATCH, ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL. (0920) 3182, GIRD 388 7006 ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING

Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total Postage add 75p per Total order.

There's an extra bonus for householders in May...

home plus

FOR HOME, CAR AND GARDEN

SPECIAL FEATURES

- * Laying paths and drives
- * Choosing a Lawn Mower
- * Garages, Greenhouses and Gazebos



Home Plus, the colour magazine for Home, Car and Garden will be carried in...

Britain's No 1
Practical Motoring
Magazine

MOTORIST

JUNE ISSUE

For DIY Home
Improvement

Practical
Householder JUNE ISSUE

The leading
weekly gardening
magazine

amateur
gardening MAY 12th ISSUE

Don't miss out - ORDER YOUR COPY TODAY

VERNON at TRENT Large!

V.T.'s views and opinions are entirely his own and not necessarily those of PE

YOU can safely bet your last copper coin that whenever some new kind of human activity crops up—for business or pleasure—its emergence will be followed in a trice by a flurry of publications devoted to its interests.

So, if you should be so clever one of these days as to launch, say, some new sport on the world—like indoor marathon running or bingo on ice—you can be as sure as tomorrow's sunrise that some smart publisher will rapidly be in there doing his stuff. Doing it, by the way, not only for the running and bingo buffs, but also for the suppliers of the appropriate goods and services. Fair enough, perhaps, for it's the gold they spend on advertising space that makes the whole project possible.

The electronics industry has never been short of its attendant publications. Some of them have been first-class and have gone from strength to strength. Others have not been so good, but have nevertheless managed to scratch a living. A few, because they ought never to have been born in the first place, have inevitably gone the way of all flesh.

The marked element of chance in this sort of venture, however, has never been a deterrent. New organs pop up like mushrooms in the dawn. The pace has quickened in recent times with the phenomenal growth of computers and microprocessors. Enough papers are published in a month in this field to stuff a cushion. And it's a sign of the times that one of the latest magazines in the technological field is called 'Satellite & Cable TV News'. This is one, I think, that cannot fail. It is likely to have enough material at its disposal to last a lifetime. Unless, that is, SCTV itself goes down the drain. And, in spite of the sorting out that still has to be done, I don't reckon that's on the cards.

There is one outstanding pioneer in the electronics publishing business which, without fundamentally changing its approach or its basic policy and format, has not only withstood the ravages of environmental change and increasing competition, but steadfastly holds a leading position. I am not referring to *PE* (though I might well have been doing so) but to 'Electronics Weekly'.

I was talking recently to 36-year-old Mick Elliott, its engaging Cockney editor. We were seated in his office at the HQ of Business Press International, the publishers, at Quadrant House, Sutton, in suburban Surrey. One wry wit who used to work for *EW* described the place as 'a plastic Lubianka'. I don't know about that, but there's nothing wrong with its central heating.

As the editor of what was Britain's first weekly newspaper for a technical readership, Mick is, quite properly, well-versed in its

origins. He reminded me that *EW* was sired by a monthly called 'British Communications & Electronics', and was launched in 1960 by Heywood & Co. Its ownership underwent several convulsions over the years, involving Odhams, Newnes, the Daily Mirror Group and IPC. Geographically, it moved around a bit as well. From Russell Street off Drury Lane to Fleet Street. From Bowling Green Lane in historic Clerkenwell to Dorset House, that imposing memorial to grandiose architecture within puffing distance of Waterloo Station. And thence a few years ago to Sutton. "But," said Mick, "in other directions there has been a good deal of consistency. In 24 years the paper has known only three Editors: Cyril Gee (who never held the title of Editor, but that of Managing Editor), John Wilson (arguably one of the best writers in the electronics business who did an eminently sensible thing and semi-retired to the Cardigan coast—an area said to be highly-conducive to literary creation), Roger Woolnough (now successfully freelancing) and myself.

"Only three editors in twenty-four years"

"From the start, *EW* adopted the unique policy of staff specialisation. Few, if any, journals have it. Mike Payne, for example, has been dealing for years with avionics and defence. David Manners is exclusively concerned with the wide-ranging field of components. And there are other specialist correspondents handling computers and communications. These are all key areas. And we have other staff covering finance, non-specific technology and sundry news items. *EW*'s policy has always been to cater—in the news, features and comment senses—for people professionally concerned with electronics who need information about current developments in an easily assimilated form—and fast. This can only be achieved by weekly newspaper techniques. In this respect, if none other, *EW* has proved a trail-blazer."

A major change in the paper's philosophy was when it went over to controlled circulation. This, for the uninitiated, means that it is mailed automatically to a selected readership, free of charge, instead of being sold on the news-stands. Finance comes entirely from advertising.

"Requested readership alone," said Mick, "already stands at 35,000 and the call is

growing fast. I wouldn't say we're all the way we want to go yet, but we're certainly moving in the right direction. We think we've got our editorial just right and, more importantly, we're bringing into the readership field many more of the younger engineers and designers upon whose flair, talent and innovative ability the future of the industry depends."

Mick himself is no stranger to or enemy of change. He studied journalism at the City Literary Institute. He could have gone on from there to a local newspaper. But, as he says: "It would have to have been in a sports capacity (he's a mad-keen footballer), and you can't be a player and a reporter at the same time." So instead he worked on journals as diverse as 'Point of Sale News' and 'Electronics Manufacturer' before joining 'Electronics Weekly' as a sub-editor. He reckons that the latter four-year stint was invaluable in giving him an insight into the complexities of the products and policies of the electronics industry.

How does he see *EW* in 20 years from now? "I can't really see any drastic changes in the newspaper itself. Its appearance isn't likely to change much. I'm sure it will never become a magazine. Or what's worse, a hybrid. And if management and financial support continues at its present level, we shall go on leading the field in weekly electronics industry journalism.


"One thing I would like to see over the next couple of decades is a greater use by us, as a newspaper, of electronics techniques. So far as production is concerned, this is at present restricted to the telephone and facsimile machine. In the current state of the art this seems to be the optimum. After all, when your printer is 54 miles away there isn't much opportunity to make use of such techniques as direct input of copy. Maybe this will come. I don't know. In an industry that moves as swiftly as ours anything can happen and there is no such thing as surprise."

★ ★ ★

The electronics industry, especially where components are concerned, is ill-placed when it comes to displaying its wares to the general public. Consumer items, like TV receivers, music centres, VCRs and the like, tend to lend themselves to attractive display in shop windows. They're tangible things that John Citizen can easily be attracted to and appraise. But how do you whip up visual enthusiasm about resistors, capacitors and all the rest of the vital guts which hobbyists in their thousands use?

Most, of course, base their purchases on the non-pictorial advertisements and on manufacturer-reputations and past experience. But isn't there a case for component manufacturers putting a bit of zip into their sales promotions?

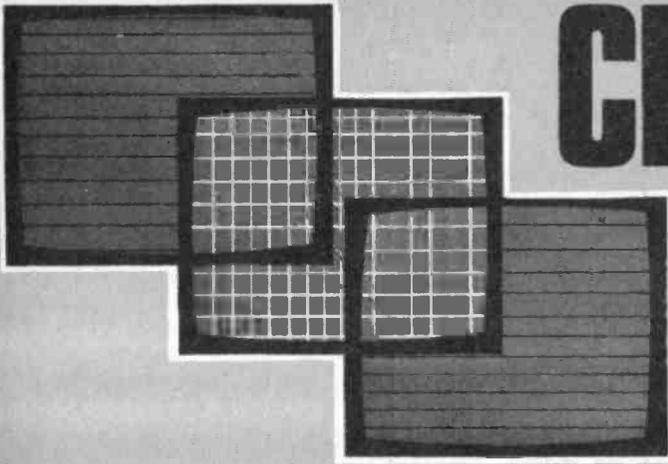How about transistors, tastefully laid on a bed of ice and marked: 'Were diffusing yesterday'? Or picture tubes bearing the popular label: 'As seen on TV'? Or, taking a leaf out of the wonderful world of Woolies, offering baskets of passives on the pick 'n' mix principle of selection? And what about tuners in family packs of half-a-dozen? Or is this just plain heresy?



CROSSHATCH GENERATOR

R. A. PENFOLD

AS its name implies, a cross-hatch generator merely produces a pattern of horizontal and vertical lines on a t.v. screen. The principal use of a cross-hatch generator is as an aid to making colour television dynamic convergence adjustments, but a device of this type can also be used when adjusting horizontal and vertical picture linearity, and it can be useful as a video signal generator for general test purposes.

The cross-hatch generator has been made as simple as possible without resorting to the use of expensive or difficult to obtain components. It simply feeds into the aerial socket of the television set and the use of a ready-made u.h.f. modulator makes the unit very easy to set up ready for use. Power is obtained from an internal 9 volt battery so that the unit is self-contained and fully portable. The display produced has 12 vertical lines by 8 horizontal lines.

THE SYSTEM

The circuit has to provide four basic signals which are mixed and then applied to the u.h.f. modulator, and the block diagram of Fig. 1 helps to explain how this is achieved. A clock oscillator and divider chain are used to provide outputs at the four frequencies required, and in this design a single integrated circuit is used as the basis of the clock and divider circuit. This will be discussed in more detail shortly. The two important frequencies are the 50Hz frame synchronisation signal and the 15.625kHz line synchronisation signal. A t.v. picture is made up from 625 lines, but these are transmitted as two frames of 312.5 lines each, with the two frames interlacing to produce a complete picture. Twenty five pictures per second are transmitted so that the 50Hz frame frequency and the 15.625kHz ($50\text{Hz} \times 312.5$) line frequency mentioned above are obtained. The line synchronisation pulse is only about $4\mu\text{s}$ in duration but the field synchronisation pulse is much longer at about $300\mu\text{s}$. Two monostable multivibrators are used to give pulses of appropriate durations.

The vertical lines are produced by a number of pulses during each line scan which generate a series of evenly spaced dots on every line of the picture. These dots must occur at the same points on each line scan so that they are vertically aligned and produce neat, properly vertical lines. The pulses must be very brief in order to give reasonably narrow lines, and they must be at a much higher frequency than the line frequency in order to give a reasonable number of vertical lines. The number of lines generated is simply equal to the pulse frequency divided by the 15.625kHz line frequency, but some of the lines will effectively be off the edges of the screen and the number actually displayed is somewhat less

than the calculated figure. In this design a simple pulse shaper is used to process the squarewave output signal from the divider chain to give the required brief pulses.


In order to produce the horizontal lines it is necessary to provide a modulation signal which is equal in length to one or more line scans, and timed to coincide with line scans. Gaps of suitable length between these pulses space the lines down the screen as required. The number of lines produced is equal to the pulse frequency divided by the 50Hz frame frequency, but like the vertical lines, some of those that are generated are not displayed on the screen. Two monostable circuits are used to ensure that the pulses appear at the appropriate times and are of the correct length. Without the delay provided by the first monostable the lines would commence in the middle of scans and not at the beginning.

A mixer stage is used to combine the four signals before they are applied to the modulator, and this circuit must be arranged so that the synchronisation signals blank the modulation signals. Note that the synchronisation pulses are negative whereas the modulation pulses must be positive in order to generate a conventional display having white lines on a dark background.

DIVIDER CHAIN

The clock oscillator and divider chain are based on a CMOS 4060BE device which is a 14 stage binary divider and oscillator. This is used in the manner shown in Fig. 2.

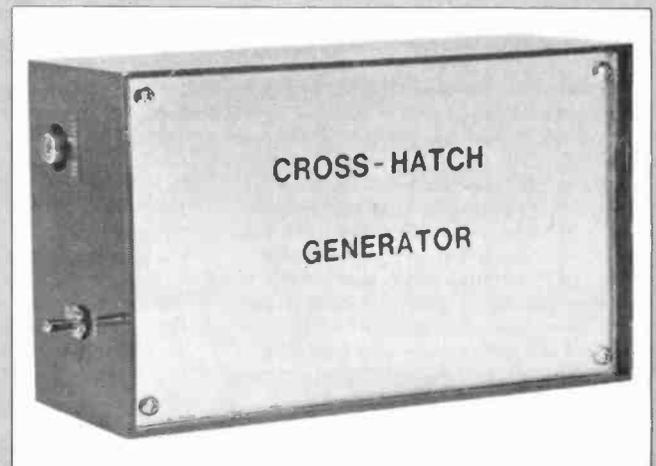A clock frequency of 250kHz is used, and this undivided signal is used to provide the vertical lines. The first four stages of the divider chain give a divide-by-sixteen action




and give the 15.625kHz line synchronisation frequency. The output from stage nine of the divider gives a further reduction in frequency by a factor of 32 and produces an output frequency of about 488Hz which is used to give the horizontal lines.

A five input AND gate is used to reset the counter when the Q4, Q7, Q8, Q9 and Q13 outputs of the divider are at logic 1, and this effectively gives a divide-by-625 action to the 31.25kHz output from the third stage of the divider. This gives the 50Hz field synchronisation signal.

Using a single divider chain in this way is obviously rather limiting in that it is not possible to obtain any desired number of horizontal or vertical lines. However, in practice a 12 by 8 display is perfectly satisfactory. An advantage of this system is that it enables a very simple and inexpensive circuit to be used, and it also ensures that the signals are all properly synchronised so that a "rolling" picture is avoided.

Fig. 1. Block diagram

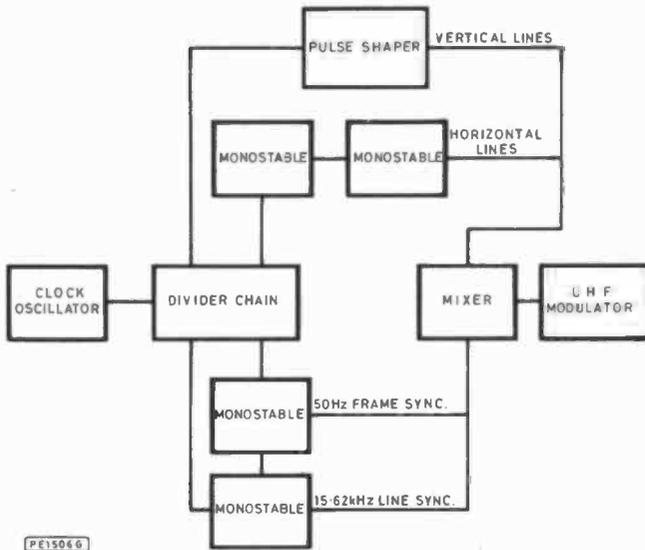

PE1506G

THE CIRCUIT

Fig. 3 shows the full circuit diagram of the cross-hatch generator.


It is possible to use the oscillator of the 4060 (IC1) as either a crystal or a C-R type. In this circuit the C-R option is used as it is cheaper and provides adequate performances. Also, a 250kHz crystal could be difficult to obtain. C1 enables the frequency of operation to be trimmed to the correct figure.

Resistor R5 plus D1 to D5 form a simple AND gate which provides the reset signal to inverter TR1 via C3. The 50Hz frame synchronisation signal is obtained from this gate and is used to trigger a simple CMOS monostable circuit formed from two gates of IC2. The other two gates of IC2 are used to form the line synchronisation monostable, and this is triggered by the 15.625kHz output of IC1. These two monostables produce positive output pulses, but these are mixed by R8-R9 and then inverted by TR2 before being applied to the input of the modulator.

TR3 is used to buffer the output of the clock oscillator before it is fed to the simple pulse shaper which comprises C6, R15 and D6. The latter ensures that only positive pulses are applied to the modulator by the pulse shaper, and that no blanking of the horizontal lines is produced by this signal.


C9 couples the 488Hz output of IC1 to the series of two monostables. These use the two sections of 556 device IC3 (this is a dual 555 timer). IC3b provides a delay and IC3a gives a pulse which is equal to one line scan in duration. Due

Fig. 2. Simple divider arrangement

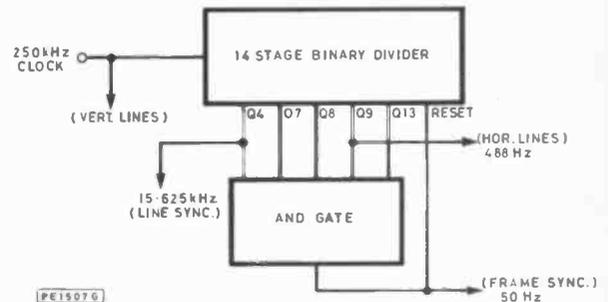

PE1507G

Fig. 3. Circuit diagram

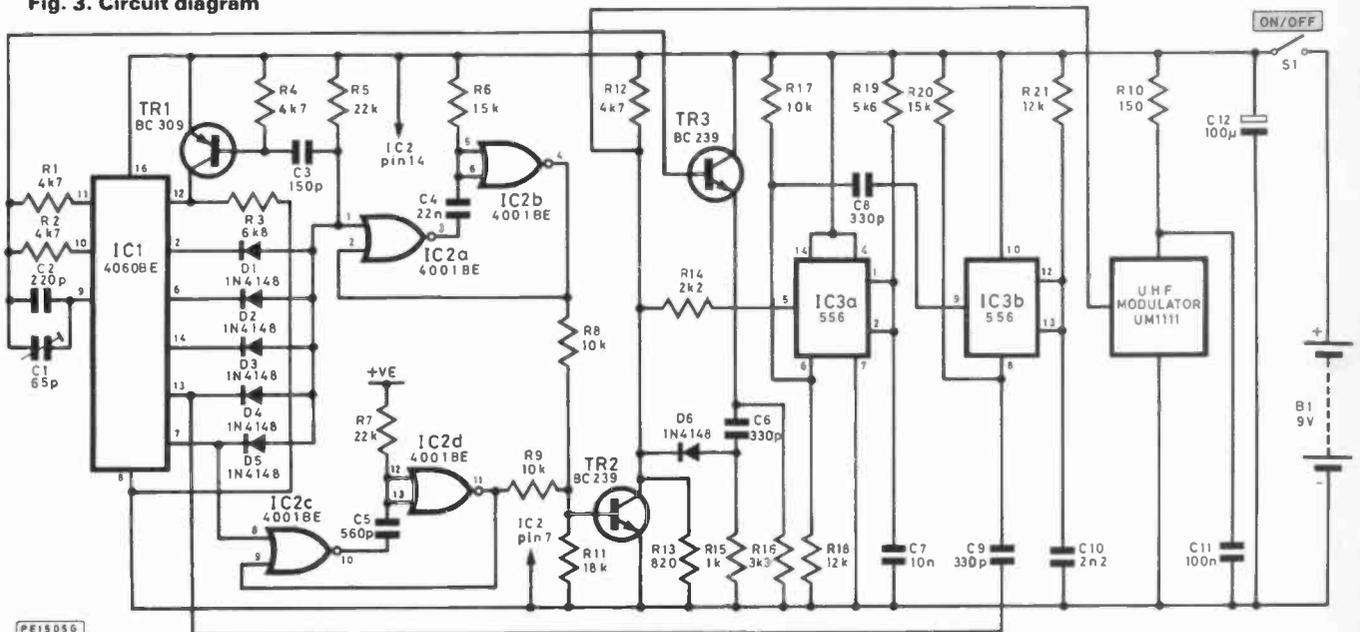

PE1505G

COMPONENTS . . .

Resistors

R1,2,4,12	4k7 (4 off)
R3	6k8
R5,7	22k (2 off)
R6,20	15k (2 off)
R8,9,17	10k (3 off)
R10	150
R11	18k
R13	820
R14	2k2
R15	1k
R16	3k3
R18,21	12k (2 off)
R19	5k6

All resistors 5% 0.25W carbon

Capacitors

C1	65p miniature film dielectric trimmer
C2	220p ceramic plate 2%
C3	150p ceramic plate
C4	22n carbonate 5%

C5	560p ceramic plate 2%
C6,8,9	330p ceramic plate (3 off)
C7	10n carbonate 5%
C10	2n2 carbonate 5%
C11	100n polyester
C12	100µ 10V radial elect

Semiconductors

IC1	4060BE
IC2	4001BE or 4001UBE
IC3	NE556
TR1	BC309
TR2,3	BC239 (2 off)
D1 to D6	1N4148 (6 off)

Miscellaneous

S1	SPST miniature toggle type
B1	9 volt battery (e.g. 6 x HP7s in plastic holder)
Modulator	Astek type UM111E36 (6MHz)
	16 pin DIL socket
	14 pin DIL socket (2 off)
	Printed circuit board (155 x 60mm)
	Metal/plastic case about 156.5 x 91.5 x 50mm
	PP3 type battery connector
	6BA fixings, wire, etc.

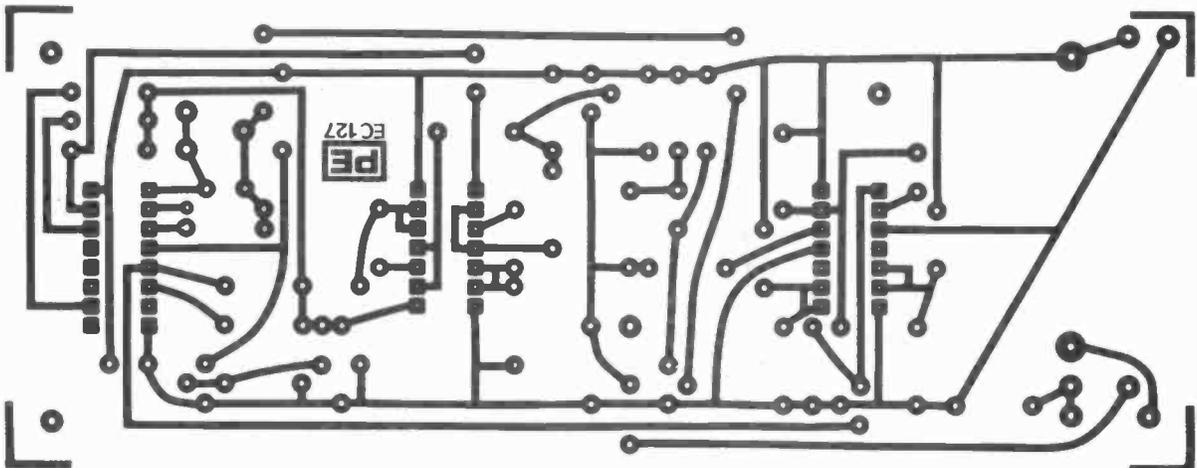


Fig. 4. P.c.b. layout (actual size)


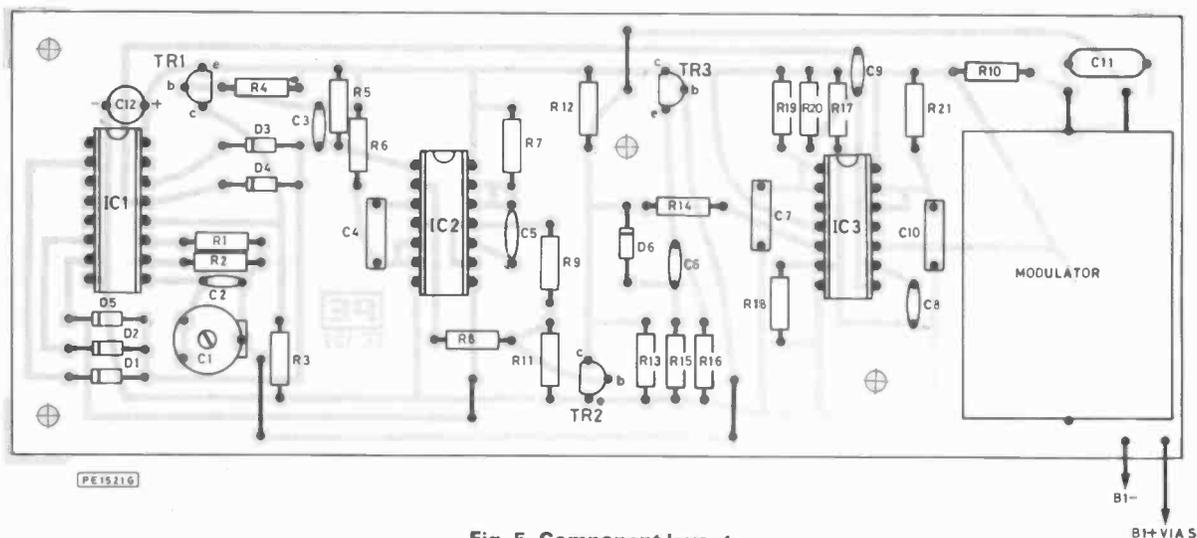
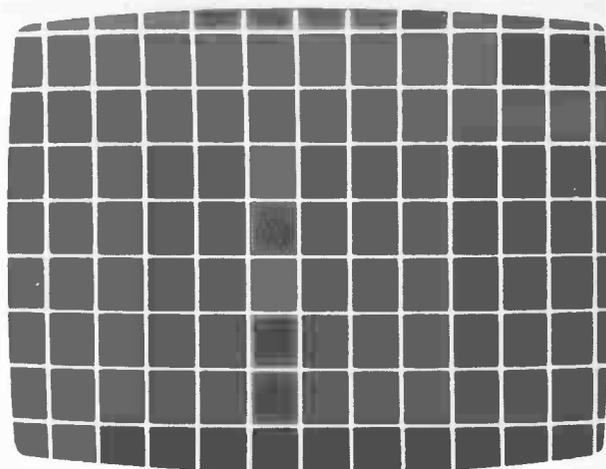


Fig. 5. Component layout

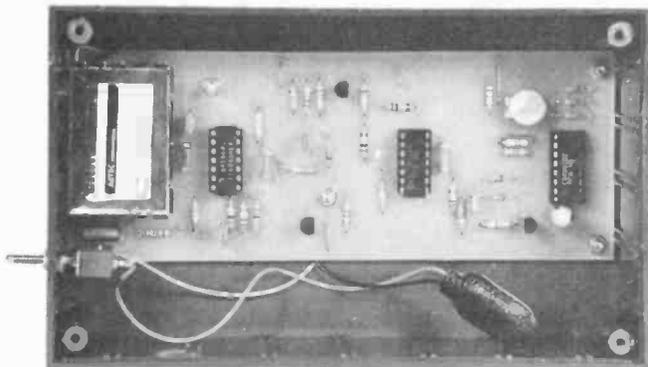

to the interlacing this gives two scans per horizontal line. The values in the pulse shaper have been chosen to give vertical lines of approximately the same width. If desired broader lines can be obtained by raising the values of R15 and R19.

When TR1 is switched on by a frame or line synchronisation pulse it has such a low collector to emitter impedance that the required blanking of the modulation signals is obtained.

CONSTRUCTION

With the only exceptions of the on/off switch and battery the components all fit onto the printed circuit board. Details of this board are shown in Figs. 4 and 5.

IC1 and IC2 should be fitted in i.c. sockets as these are both CMOS devices, and the other normal CMOS handling precautions should be taken. C1 must be the specified miniature foil trimmer if it is to fit onto the printed circuit board without the need for any modifications to the design. Any type having a maximum value of about 65p is electrically suitable. Similarly, it is advisable to use the specified Astek modulator as this will fit onto the printed circuit without difficulty, and this particular type is also quite inexpensive and easy to obtain.

A plastic box having a metal lid and approximate outside

dimensions of 156.5 by 91.5 by 50mm will accommodate all the components, but this is about the smallest type that is suitable. The printed circuit board is mounted on the base panel of the case using 6BA fixings, and a hole about 12.5mm in diameter is made in the case at the appropriate point so that access to the phono output socket of the modulator is possible. The on/off switch can conveniently be mounted at this end of the case.

As the current consumption of the circuit is about 24 milliamps it is advisable to power the unit from a fairly large 9 volt battery such as a PP7 size, or six HP7 cells mounted in a plastic battery holder. If this second method is used connection to the battery holder is by way of an ordinary PP3 style battery connector.

The completed unit is connected to the t.v. set using a standard phono to coaxial cable of the type used with video games machines and home computers. The only adjustment which the finished unit requires is to set C1 to give an output frequency of 50Hz from pin 4 of IC2. Most t.v. sets will synchronise properly over a fairly wide frequency range, but if possible the unit should be accurately set up so that the possibility of picture distortion due to poor frame frequency accuracy is avoided. The output of the modulator is preset at around channel 36 by the manufacturer, and this component should not need any adjustment. ★

BAZAAR

ZX-81 16K with assembler, MCTT monitor, forth, toolkit, flight simulator, £55. Tel: 051-608 8617. D. Stephens, 411 Woodchurch Road, Birkenhead, Merseyside L42 8PF.

WANTED 88C 8271 Disc Controller and/or Watford D.F.S. Rom. Vincent. Tel: 0524 411780 Morecambe after 6 p.m. V. Haworth, Rosebank, 377 Marine Rd., Morecambe. Lancs. LA4 5AM.

LARGE quantity electronic items for sale. Multicores, connectors, chokes, motors, meters, s.a.e. for complete list. Kerry Williams, 10 Wilmot Street, Melyn Neath, West Glamorgan. SA11 1AH (0639) 51948.

EVERYDAY Electronics for sale. Aug. 80 to Dec. 82. 29 issues. Offers. R. Yates, Heathcote, Eastbourne Road, Blindley Heath, Nr. Lingfield, Surrey. RH7 6PY. Tel: (0342) 832078.

SOLARTRON CD 1400 scope, double beam, OC-15MHz, in working condition, with manual. £60 plus postage. Mr. M. V. Call, 16 Mill Lane, Broomfield, Chelmsford, Essex. CM1 5BQ. Tel: 0245 441965.

HALL effect K/Board 83 keys parallel ASCII output metal framed p.c.b. New, unused. £35 inc. (0782) 550684. N. L. Smith, 31 Meadow Avenue, Wetley Rocks, Stoke-on-Trent ST9 0BD.

WANTED manual to buy or loan for Telegroup oscilloscope, type D43, time base type TD41. R. Lilley, 184 Mitchel Hey, College Bank Rd., Rochdale, Lancs. Tel: 0706 359389.

20 used 50V coil relays 11 pin round base, 3 sets of contacts rated at approx. 5 amps. Ian Wright, 86 Planks Lane, Wombourne, West Midlands. Tel: (0902) 892864.

PRACTICAL Electronics 1969-1983 less 2. Offers. Buyer collects. E. L. Yates, 5 Whinney Moor Lane, Retford, Notts. Tel: Retford 704995.

SINCLAIR Project 60 stereo equipment. Stereo tuner, pre-amp, power amplifiers, power unit, no cabinet. Serviceable, offers please. N. Besant, 3 Brimley Drive, Downend, Bristol BS16 6JQ.

32K UK101 2 x 70K disks, full manuals. 9 inch B + W TV. Needs good clean. 20 + discs. £250 o.n.o. J. Young, The Glen, Salisbury Road, Shrewton, Wilts. Tel: Shrewton 620561.

WANTED 1960's Midland transceiver (Model 13-115) in any condition for cash. A. K. Porwel, 9 Argyle Place, Cliftonwood, Bristol BS8 4RH. Tel: (after 6p.m.) 0272 298946.

WANTED Sinclair Spectrum 48K (may be interested in 16K) preferably in working order, also w.h.y. A. Slater, 172 St. Lucia Park, Bordon, Hants. GU35 0LF.

MAGAZINES from 1956 to 1983. Full and part years. Practical Television/Wireless/Electronics. Offers or inquiries. Mr Halsall, 47 Smalley Street, Castleton, Rochdale, Lancs OL11 3EB. Tel: (0706) 33511.

TANGERINE Microtan 65 in case with psu includes Tanex Xbug basic keypad. £150. Tel: Aldershot 310661. C. W. Murray, 21 Canterbury Road, Ash, Aldershot, Hants 9U12 6SP.

UK101 fully expanded, £45. 8" disc drive with interface for above, £220. Both together for £245. D. J. Fellows, 26 Westbourne Avenue, Emsworth, Hants PO10 7QU. Tel: (024 34) 554B.

QUASAR Practical Electronics tape deck for sale. built from kit. Working but needs new heads. £20. Michael Bond, 2 The Grange, Eastbourne Road, South Godstone, Surrey RH9 8JQ. Tel: (0342) 893168.

TETRONICS 543 Oscilloscope v.g.c., broadcast video, J.V.C.7115 rec/mon (mint, guaranteed). For details contact: Mr A. Gould, 31 Lugard Road, London SE15 2SZ. Tel: 01-639 3855 (Answerphone) or (0303) 24141.

Continuity Checker

CHRIS LARE

THE normal method of measuring resistance is to use a multimeter. With cheaper meters the lowest resistance measurable can be in the order of several ohms which is not always useful, particularly when the item to be measured has a natural resistance of that order. Furthermore, even cheap multimeters are far too expensive to leave lying around in a garage or the home. More expensive meters will resolve the lower resistance ranges but the cost of accidental damage results in a much greater reluctance to allow them to leave the work bench. In view of this there is a requirement for a cheap and robust resistance measuring unit for low values of resistance typically found around the car and home. In most cases in this application the exact value of the resistance is not important and it is sufficient to know that a resistance is, or is not, present.

The unit works by comparing the resistance between the probes with a preset value. If the probe resistance is lower than the preset value an i.e.d. lights and a tone sounds allowing the checker to be used in awkward and dark corners. The prototype unit was built with five preset values, 1 ohm, 10 ohms, 50 ohms, 100 ohms and 1 kilohm and although these may be altered it has been found that this set offers the most flexibility. The unit is battery powered and quite compact.

BALANCING OP-AMP AND COMPARATOR INPUTS

There are some applications of op-amps and comparators where high accuracy and matching between the two inputs is required. Typically this will be most critical where low levels of signals are envisaged of which the circuit described here is an application. It is not really possible to make op-amps and comparators with very accurate input stages at a reasonable cost due to production tolerances during the actual manufacture of the silicon chip and so many parts allow the end user some means of nulling-out any errors. Obviously accurate parts are made but these will be specially selected and trimmed during the final chip assembly stages and are thus very expensive.

Theoretically any device should give a balanced output (half supply rail) when the inputs are joined together and grounded through a resistor. If this is done it will be noticed that the output of the device is usually hard over in one direction and a small voltage appears on the inputs even though they are supposedly grounded. The device output sitting at one of the rails is caused by a small voltage mismatch in the actual comparator circuit, whereas the small voltage seen is a result of the inputs themselves sourcing a small current. This voltage is called the 'offset' voltage. As the source impedance becomes larger the effect of this offset becomes worse because the current flow from the input is essentially constant. Fig. 1 shows a typical device with source impedances. Even if both resistors are the same, differences in the two currents will result in error. The method adopted by the device designer is to allow the user to slightly vary the input stage currents by providing two extra pins on the device which give access to the input stage balancing network. The user may allow current to flow into

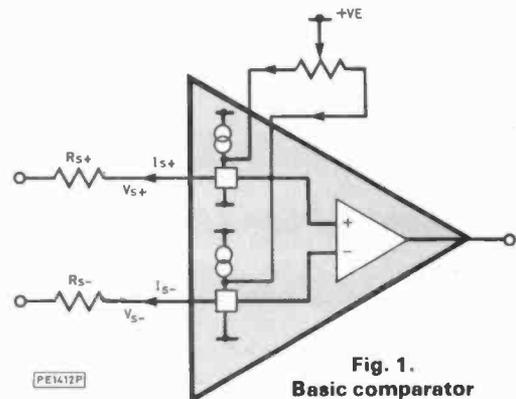



Fig. 1.
Basic comparator

these pins to cancel out the actual device error.

The most simple way of doing this is illustrated where a potentiometer has been connected between the two correction pins. When the wiper is in mid position the current injected into both input stages will be equal and thus the adjustment has no overall effect. As soon as the wiper is moved different amounts of current are injected which can be used to cancel out any imbalances in the input stages. It is worth noting that this technique will also cancel out effects through the source resistors not being properly matched, although severe mismatch will be outside the adjustment range.

In actual practice a resistor is connected in series with the potentiometer wiper to limit the current if it is set fully over to one end which would allow large, and potentially damaging, currents to flow into the device. A capacitor can be connected between the ends of the potentiometer to help prevent oscillation when a comparator is used but this is not too common for op-amps. It is also possible to use one of the adjustment pins to add hysteresis to the comparator by making use of offset errors.

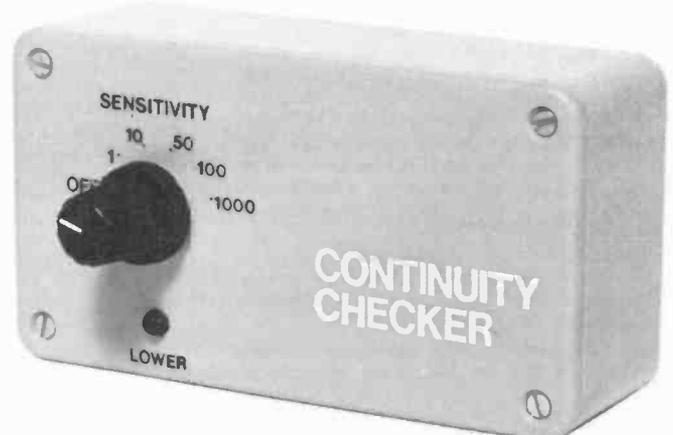Although Fig. 1 shows the offset adjustment connected to the positive supply care should always be taken to ascertain which supply should be used since many devices use the negative rail for this form of correction. The device pins will be labelled 'balance' or 'offset null'.



CIRCUIT

The resistance sensing part of the circuit is built around a traditional balanced resistor bridge. Consider the effect of switch S1 being set to the '1' position. This will give rise to a voltage at point A. If the probes are connected across a one ohm resistor as well, the voltage at point B will be equal to that at point A and the bridge will be balanced. If the resistance across the probes is slightly less than one ohm the voltage at point B will increase very slightly, a condition which is fairly easy to detect with a voltage comparator. The voltages are fed to the comparator, an LM311, through two equal resistors R10 and R11. These are included for two reasons: firstly they provide a defined input impedance for the comparator allowing offsets to be nulled-out and secondly, together with D3-D6, they limit the comparator input differential voltage if the probes are accidentally connected to something unpleasant. The diodes play no normal part in the operation of the circuit. Now, in the case above where point B is higher than point A the inverting input of the comparator will be higher than the non-inverting and so the comparator output will go low which will light the l.e.d., D7.

Possibly the most important trimming fitted is the supply voltage derivation for the bridge circuit. Normally the bridge is connected directly across the supply but this would imply that the comparator was required to operate within millivolts of its supply which it will not do effectively. To avoid this the bridge is fed with 3.7 volts which sets the comparator inputs at almost half supply rail which is the best point. This scheme also gives the advantage that the bridge supply is very well decoupled from the main battery supply and is thus fairly immune to noise created by other parts of the circuit, in particular the tone generator. The actual value of the supply to the bridge is not important since it is fed to both sides of the balancing network and so it was derived from a 4.3 volt Zener. D2 drops this voltage a further 600mV but is mainly intended to prevent damage to the Zener should a high voltage be applied to the probes. The supply is well decoupled by C1.

The preset resistances are selected by a rotary switch, S1. The 50 ohm setting is obviously not absolutely accurate but it was felt that it was good enough for the intended application. Obviously more precise 1% resistors could be used in-

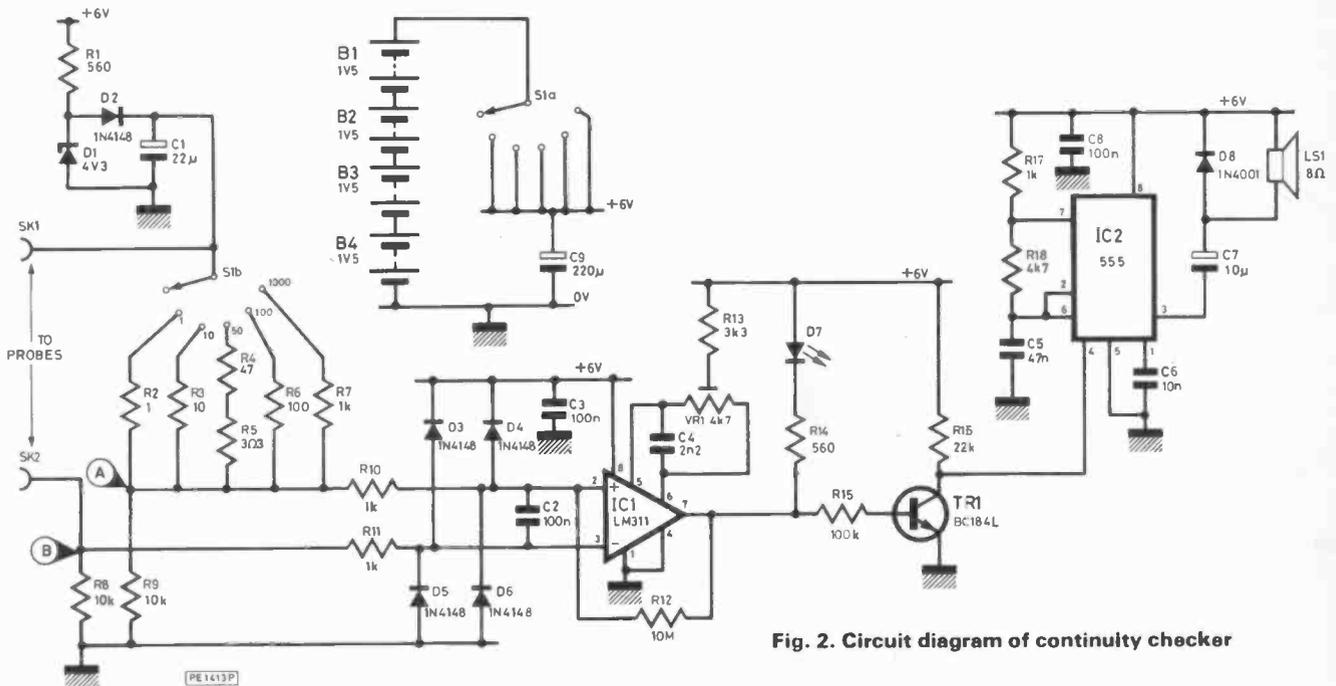


Fig. 2. Circuit diagram of continuity checker

Several circuit trimmings are required to make this work as intended. Firstly comparator circuits of this type tend to oscillate when the theoretical switching point is reached. This is caused by a variety of reasons, all due to the fact that the comparator is a very high gain device. The tendency to oscillate can be removed by small amounts of positive feedback which is supplied by R12. It is important that R12 is not made any smaller (which would be better for the circuit) because the hysteresis effect thus created would swamp any small input voltage changes. The reduction of oscillation is continued by the addition of C2 which effectively lowers the a.c. input differential and C3 which acts as a decoupling capacitor very close to the comparator.

The offset null adjustment circuit as previously mentioned consisting of VR1, R13 and C4 allows the circuit to be properly balanced.

stead of the 5% ones specified but the value of this is again open to debate.

The tone generator consists of a standard 555 timer astable circuit running at 400Hz. When the comparator output goes low TR1 turns off which allows the reset pin (4) of the 555 to be pulled high by R16 thus enabling the tone. An 8 ohm speaker was used in the prototype which gave sufficient volume. C7 blocks any d.c. current flow when the tone is not sounding (the 555 output will be low) and also acts as a series impedance when the tone is sounding to limit the current flow through the speaker. The 555 is decoupled with a 100nF C8 close to it and the usual control voltage input decoupling capacitor C6.

The entire circuit is decoupled by a 220µF electrolytic which although larger than usual is probably a good idea for a circuit as sensitive as this. The checker is switched by the

other pole of S1 which simply connects the battery to the rest of the circuit when any of the resistance values are set. The current consumption is about 14mA standing, which rises to some 36mA when the l.e.d. and tone are operational.

CONSTRUCTION

The complete unit was designed to fit into a small plastic box and only requires 5 holes to be drilled for the switch, l.e.d., speaker and terminals.

The holes for the l.e.d. and S1 should be marked as follows: S1 and the l.e.d. are on a centre line 33mm from the left hand side of the lid, switch S1 being centred 32mm from the top of the lid and the l.e.d. 54mm from the top of the lid. The hole for the l.e.d. is 5mm diameter and the switch 9.5mm diameter. Since these components are p.c.b. mounted it is very important to make accurate measurements. The p.c.b. is held in place solely by the switch retaining nut.

The two holes for the 4mm terminals should be drilled so that they fit above the speaker but do not interfere with the p.c.b. A 10mm hole should be drilled for the speaker in the bottom of the box and covered with a small piece of cloth. After glueing down the speaker, the terminals should be fitted and the flying leads attached to both the speaker and the terminals.

Assemble the circuit board which should be used in preference to Veroboard. Fit all the components in any order although the l.e.d. is probably best left until last. The rotary switch specified is supplied with tag (ends) which should be cut off. Insert the switch with care and solder only two pins in before checking it is flush with the board and soldering the other pins in. The l.e.d. should be fitted so that its rim is level with the top of the switch so that it will appear through the lid of the box in final assembly.

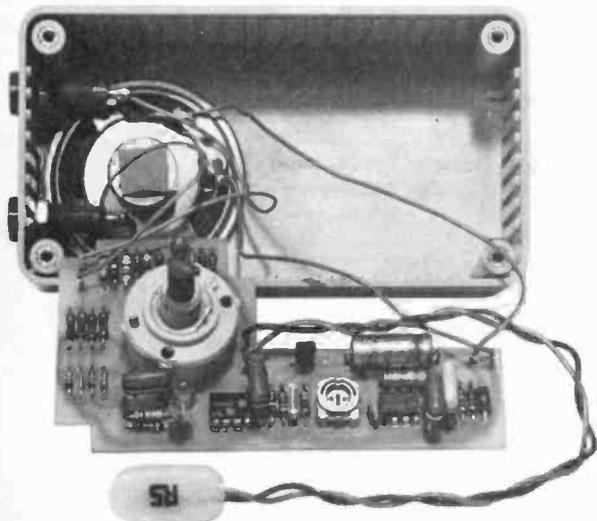


Fig. 3. Complete assembly of continuity checker

Testing the board should be very simple, although it should be mentioned that the loading of an average multi-meter will upset the bridge operation. Check firstly the operation of the on/off switch wafer and check that the battery voltage appears on the circuit and that the current consumption does not exceed 17mA. Set the resistance switch to 1 and join the probe sockets together whereupon the l.e.d. should light and the tone sound. Check that all the other settings work as well and then set up the offset adjust-

ment. This is most easily done by firmly joining points A and B (not the terminals) and adjusting the preset until the l.e.d. just comes on and then turning it back very very slightly to counteract the hysteresis effect. It may happen that the circuit will just oscillate but this is not of any consequence. The l.e.d. should not go out at this stage. Finally test the unit by connecting known resistances between the probes, remembering that the contact resistance can be in the order of a few ohms and so soldered connections are recommended for testing.

Complete the final assembly by fixing the circuit board into the box lid (using a washer to space it if necessary) and then connecting the flying leads and the battery clip to the relevant terminals. Give the unit a final check and fit the lid onto the box. ★

COMPONENTS . . .

Resistors

R1, R14	560 (2 off)
R2*	1
R3*	10
R4*	47
R5*	303
R6*	100
R7*, R10, R11, R17	1k (4 off)
R8, R9	10k
R12	10M
R13	3k3
R15	100k
R16	22k
R18	4k7

All 5% 1/4W unless greater accuracy is required when *items should be replaced by 1% types

Potentiometer

VR1	4k7 miniature horizontal preset
-----	---------------------------------

Capacitors

C1	22μ 10V tantalum
C2, C3, C8	100n C280 type polyester (3 off)
C4	2n2 polyester block 0.3in pitch
C5	47n C280 type
C6	10n disc ceramic
C7	10μ 10V elect.
C9	220μ 10V elect.

Semiconductors

D1	4V3 400mW Zener
D2, D3, D4, D5, D6	1N4148 (5 off)
D7	Green l.e.d.
D8	1N4001
TR1	BC184L
IC1	LM311
IC2	NE555

Miscellaneous

Plastic box 120 x 45 x 60mm
 Printed circuit board
 Suitable knob and pointer
 Terminal pins
 S1 — 2 pole 6-way switch (Lorlin 'Wavechange' type)
 Battery clip, holder for four HP7 in square format
 B1-4 — HP7 batteries (4 off)
 2 of 4mm terminal sockets, test probes
 LS1 — Miniature 8 ohm 2 inch speaker
 Speaker cloth, connecting wire, small piece of paxolin, washer for switch
 Letraset to suit

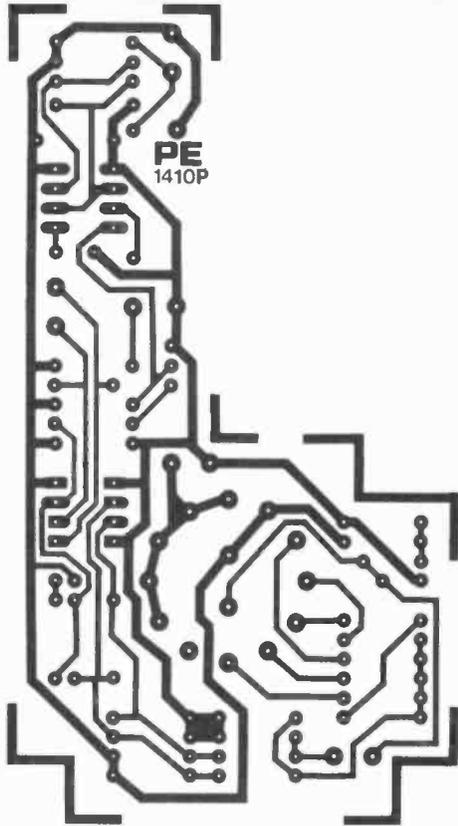


Fig. 4. Printed circuit board layout (actual size)

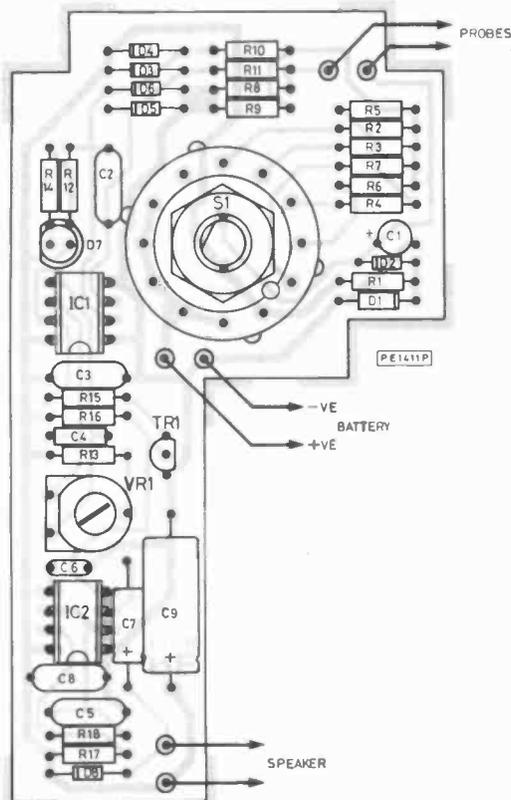


Fig. 5. Component layout

JUNE ISSUE...

ELECTRONIC SURVEILLANCE SYSTEMS

How can electronics effectively guard property? What are the various surveillance options? This series explains the advantages and disadvantages of relative systems and presents the following three alarm projects:


Passive Infrared, Ultrasonic, and Microwave.

All these provide a secure area in which any movement is detected, and alarm sounded.

SPECTRUM PSU

This digitally controlled bench PSU has been designed for use with the ZX Spectrum. It has a maximum output voltage of 24 volts which can be incremented in 0.1 volt steps and is current limited over four switched levels; 50mA, 100mA, 500mA and 1A.

TRAIN WAIT

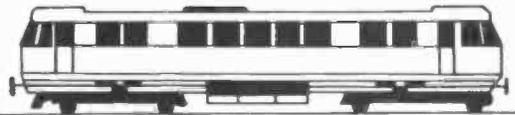

This is a must for model train enthusiasts, wanting more realism and automation. This circuit provides automatic wait facility for selected trains at stations and crossings.

EVERYDAY ELECTRONICS and computer PROJECTS

JUNE 1984 ISSUE ON SALE FRIDAY, MAY 18

MICRO-BUS

and MICROPROMPT

Appearing every month, Micro-Bus now presents ideas, applications and programs for the most popular micro-computers and all micro-related projects so far published in PE. Ideas must be original, and payment will be made for any contribution featured.

UK101 M/C TRACE

The Trace facility of PE April 1983 was most interesting but unfortunately it does not give a complete trace, in fact only interrupting instructions of two clock cycles in length. 6502 microprocessor instructions vary from two to six cycles of the 1MHz clock and therefore some additional refinements would have to be incorporated to display the addresses of all instructions.

The 6502 microprocessor has certain conditions to be fulfilled before initiating an interrupt sequence. Essentially the IRQ or NMI lines must go low and remain low for at least two clock cycles to be recognised. In addition the IRQ line must remain low until the end of the current instruction sequence to be recognised. If an IRQ interrupt is to be used to drive a Trace facility and be driven from the sync pin of the 6502 then a method must be found to "stretch" the sync pulse until the interrupt is recognised. This stretched pulse must then be terminated on completion of the IRQ routine or the microprocessor will, on returning to the main program, immediately repeat the interrupt. One way of doing this is to provide a latch which will be set by the sync pulse and be reset on completion of the interrupt loop by a pulse derived from "ANDing" the sync pulse with a decoded RTI instruction from the data bus. Fig. 1

shows a simple circuit to implement this which can be built on a piece of stripboard.

IC1 partially decodes the data bus and the decoding is completed by IC2a. In order to ensure that the data on the bus is stable the $\overline{\text{O2}}$ clock pulse used to trigger the latch IC3 is delayed some 100ns by IC2b. To allow for stray capacitances some adjustment may be required to the value of the capacitor. IC3 is set by a sync pulse but reset when a sync pulse occurs in conjunction with the RTI instruction.

D0 to D7 can be connected to the spare connecting pads to the left of IC14. (On the UK101 D0 is nearest the keyboard.) $\overline{\text{O2}}$ can be connected to W6. Ground and Vcc can be connected to pins 1 and 12 respectively of IC14. IRQ and SYNC are connected to the 6502 pins 4 and 7. There is no need to disconnect R11 as the circuit will operate in the wired-OR configuration. Mr Beckett's software will now print out at the top of the screen the current address of the operation code being performed.

For those who have fitted the WEMON monitor the Trace machine code shown here will provide much more information. This program will print out on the top, normally non-printing line, of the screen the contents of all the registers namely program counter, flags, stack pointer, accumulator, X and Y registers. It should be

noted that the data shown in the registers is that existing before the instruction to be found in the program counter is executed. Wemon uses locations 0241 to 0247 to store this information and this program uses the sub-routine at F98F to print it out. An additional facility provided by the program is that the Trace will wait in the interrupt loop until the left-hand shift key is pressed. This allows the user to "single step" through a program, viewing the contents of all the registers at each step, a most useful feature in de-bugging.

If Trace is being used to step through a BASIC program then "MEMORY SIZE?" should be answered by 8115. The WEMON IRQ vector is set to point to the correct location by POKE561,76: POKE562,184: POKE563,31 and this should be placed at the start of the program. The Trace speed is set by a poke to 8191, 1 for fast, 0 for slow and 127 for medium. The IRQ mask is cleared by POKE11,182: POKE12,31: X=USR(X). The switch is used to turn Trace on and off.

J. H. Howarth,
W. Lothian.

Trace program for use with WEMON monitor

1FB6 58	CLI	Clear interrupt mask	1FDB D0F4	BNE \$1FD1	Shift not pressed go back & try again
1FB7 60	RTS	and return to program	1FDD AEF1F	LDX \$1FFF	Shift pressed. Continue via
1FB8 8E4602	STX \$0246	Store X register in Wemon store	1FE0 ACFF1F	LDY \$1FFF	the delay stored in address 1FFF
1FBB 8C4702	STY \$0247	Store Y register in Wemon store	1FE3 88	DEY	
1FBE 68	PLA	Pull status off stack and	1FE4 D0FD	BNE \$1FE3	
1FBF 8D4302	STA \$0243	store	1FE6 CA	DEX	
1FC2 68	PLA	Pull program counter hi- byte	1FE7 D0FA	BNE \$1FE3	Delay incomplete. Return again
1FC3 8D4202	STA \$0242	off stack and store	1FE9 AD4102	LDA \$0241	Fetch program counter lo- byte
1FC6 68	PLA	Pull program counter lo- byte off	1FEC 48	PHA	and push on the stack
1FC7 8D4102	STA \$0241	stack and store	1FED AD4202	LDA \$0242	Fetch program counter hi- byte
1FCA BA	TSX	Transfer stack pointer to X register	1FF0 48	PHA	and push on the stack
1FCB 8E4402	STX \$0244	and store	1FF1 AD4302	LDA \$0243	Fetch status and
1FCE 208FF9	JSR \$F98F	Print contents of Wemon stored	1FF4 48	PHA	push on the stack
		registers	1FF5 AD4502	LDA \$0245	Reload original value of
1FD1 A9FE	LDA \$5FE	Address row which contains the l.h.	1FF8 AE4602	LDX \$0246	accumulator
1FD3 8D00DF	STA \$DF00	shift key in the keyboard latch	1FFB AC4702	LDY \$0247	Reload original value of X register
1FD6 A905	LDA \$05	Address column in keyboard to see	1FFE 40	RTI	Reload original value of Y register
1FD8 2C00DF	BIT \$DF00	if l.h. shift has been pressed	1FFF 00	BRK	Return from interrupt routine
					Space reserved for delay counter

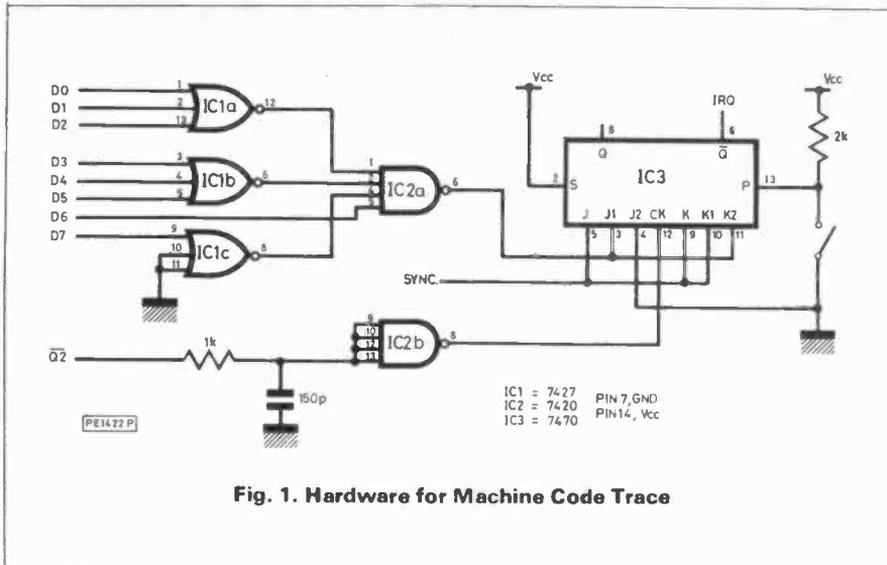


Fig. 1. Hardware for Machine Code Trace

It is emphasised that material presented in Micro-Bus has not necessarily been proved by us. Neither can compatibility with all generations of the computer equipment to which it relates be guaranteed.

Software and hardware designs submitted should be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

RESONANCE

Sir—I have been reading your magazine for the past eighteen years and think it's about time I made a contribution. The adjacent program was written for the Dragon 32 computer and should run on any machine, without too much alteration, as only text is used. The program will calculate values of capacitance, inductance and frequency at the resonant frequency of a parallel or series connected coil and capacitor combination.

The computer will first ask which of the three variables needs to be calculated and will then request the other two. All the usual denominations are taken care of, i.e. Hz, kHz, pF, mH, etc., and all the answers are presented in the same form.

I hope that this program will interest some of your readers and perhaps inspire someone to tackle the problem of coil construction. Who knows? I might come up with something within the next eighteen years!

Mr. A. D. Flower,
Staffordshire.

```

10 PI=3.1415926
20 CLS:PRINT @107,"RESONANCE (23
spaces) *****"
30 PRINT @233,"BY A.D.FLOWER."
40 PRINT @362,"MARCH 1983"
50 FOR T=1 TO 4000:NEXT T:CLS
60 PRINT @132,"DO YOU WISH
CAPACITANCE,(8 spaces)INDUC-
TANCE OR FREQUENCY (11
spaces)TO BE CALCULATED?"
70 PRINT @357,"PRESS KEY
'C','I'OR'F'"
80 A$=INKEY$
90 IF A$="C" THEN 130
100 IF A$="I" THEN 260
110 IF A$="F" THEN 410
120 GOTO 80
130 CLS:PRINT @42,"CAPACITANCE
(21 spaces)-----"

```

```

140 PRINT @97,"PLEASE ENTER IN-
DUCTANCE VALUE (3 spaces)AND
(WHEN REQUESTED) ITS (8 spaces)
DENOMINATION. (19 spaces) DO
LIKEWISE FOR THE FRE-
QUENCY."
150 GOSUB 560:GOSUB 590:GOSUB 650
160 IF F=0 OR L=0 THEN 140
170 C=((1/(2*PI*F)) ^2)/L
180 C=C*1E06:REM C=MICROFARADS
190 IF C>999.99 THEN GOSUB 750
200 IF C<0.0005 THEN 220
210 PRINT:PRINT" CAPACITANCE =
";:PRINT
USING"# # #.# # #";C::PRINT
"UF":GOTO 50
220 C=C*1E06:REM C=PICOFARADS
230 IF C<0.5 THEN GOSUB 740
240 PRINT:PRINT" CAPACITANCE =
";:PRINT
USING"# # #.# # #";C::PRINT"PF"
250 GOTO 50
260 CLS:PRINT @43,"INDUCTANCE (22
spaces)-----"
270 PRINT @97,"PLEASE ENTER
CAPACITANCE VALUE (2 spaces)
AND (WHEN REQUESTED) ITS (8
spaces) DENOMINATION.(19 spaces)
DO LIKEWISE FOR THE FRE-
QUENCY."
280 GOSUB 620:GOSUB 590:GOSUB 650
290 IF F=0 OR C=0 THEN 270
300 L=((1/(2*PI*F)) ^2)/C
310 L=L*1E06:REM L=MICROHENRYS
320 IF L>999.99 THEN 350
330 IF L<0.05 THEN GOSUB 740
340 PRINT:PRINT" INDUCTANCE =
";:PRINT
USING"# # #.# # #";L::PRINT
"UH":GOTO 50
350 L=L*1E-03:REM
L=MILLIHENRYS
360 IF L>999.99 THEN 380
370 PRINT:PRINT" INDUCTANCE
=";:PRINT
USING"# # #.# # #";L::PRINT
"MH":GOTO 50
380 L=L*1E-03:REM L=HENRYS
390 IF L>999.99 THEN GOSUB 750
400 PRINT:PRINT" INDUCTANCE =

```

```

";:PRINT
USING"# # #.# # #";L::PRINT
"H":GOTO 50
410 CLS:PRINT @43,"FREQUENCY (23
spaces)-----"
420 PRINT @96,"PLEASE ENTER IN-
DUCTANCE VALUE (3 spaces) AND
(WHEN REQUESTED) ITS (8 spaces)
DENOMINATION. (19 spaces) DO
LIKEWISE FOR THE
CAPACITANCE."
430 GOSUB 560:GOSUB 620:GOSUB 650
440 IF L=0 OR C=0 THEN 420
450 F=1/((2*PI)*SQR(L*C))
460 REM F=HERTZ
470 IF F>999.99 THEN 500
480 IF F<1 THEN GOSUB 770
490 PRINT:PRINT" FREQUENCY =
";:PRINT
USING"# # #.# # #";F::PRINT
"HZ":GOTO 50
500 F=F*1E-03:REM F=KILOHERTZ
510 IF F>999.99 THEN 530
520 PRINT:PRINT" FREQUENCY =
";:PRINT
USING"# # #.# # #";F::PRINT
"KHZ":GOTO 50
530 F=F*1E-03:REM F=MEGAHERTZ
540 IF F>999.99 THEN GOSUB 760
550 PRINT:PRINT" FREQUENCY =
";:PRINT
USING"# # #.# # #";F::PRINT
"MHZ":GOTO 50
560 PRINT:INPUT" INDUCTANCE";L
570 INPUT"(4 spaces) H:MH:UH";DI$
580 RETURN
590 PRINT:INPUT"(2 spaces) FRE-
QUENCY";F
600 INPUT" HZ:KHZ:MHZ";DF$
610 RETURN
620 PRINT:INPUT" CAPACITANCE";C
630 INPUT"(6 spaces) UF:PF";DC$
640 RETURN
650 IF DI$="H" THEN L=L
660 IF DI$="MH" THEN L=L*1E-03
670 IF DI$="UH" THEN L=L*1E-06
680 IF DF$="HZ" THEN F=F
690 IF DF$="KHZ" THEN F=F*1E03
700 IF DF$="MHZ" THEN F=F*1E06
710 IF DC$="UF" THEN C=C*1E-06
720 IF DC$="PF" THEN C=C*1E-12
730 RETURN
740 PRINT @449,"VALUE TOO
SMALL":RETURN
750 PRINT @449,"VALUE TOO
LARGE":RETURN
760 PRINT @449,"FREQUENCY TOO
HIGH":RETURN
770 PRINT @449,"FREQUENCY TOO
LOW":RETURN

```

SEMICONDUCTOR CIRCUITS

TOM GASKELL BA (Hons) AMIEE

TOUCH TUNERS (SAS 580 and SAS 590)

MANY integrated circuits are specifically designed to fulfil well defined roles. Indeed, most of the i.c.s featured in Semiconductor Circuits to date fall into this category, being specifically intended for use as door chimes, combination locks, audio preamplifiers, i.e.d. bargraphs, etc. It is often interesting to apply some lateral thinking to the way in which these i.c.s are used; this can often result in unusual designs of considerable effectiveness and simplicity which are very different to the original intentions of the i.c. manufacturers. The Siemens SAS 580 and SAS 590 are perfect examples of this. They were designed as touch tuning amplifiers for television and radio tuners, but in practice they offer marvellous facilities for use in a whole host of switching and controlling applications.

The basic intention of the i.c.s is to provide a tuning voltage for varicap diodes. This tuning voltage alters the capacitance of the diode, which in turn causes the radio or television receiver to tune in to the appropriate station. Four different analogue voltages can be fed into the i.c., and four switches are provided to allow the relevant voltage to be switched through to the diode. If each analogue voltage represents the tuning voltage for a different station, the switches enable instantaneous selection of any of these four different stations. Furthermore, four load driving outputs are provided, suitable for driving lamps, i.e.d.s, relays, or waveband selection circuitry as required.

INGENIOUS FACILITIES

Although the basic description of i.c. operation seems simple enough, numerous more


complex extra facilities are provided. Full interlocking is arranged such that only one input is switched to the output at any one time, except when two control inputs are deliberately turned on together as a momentary action. The control inputs themselves (switch 1, switch 2, switch 3, and switch 4) have been made touch sensitive, so that either non-moving touch plates or conventional switches may be used as the switch input device.

A clock input is provided so that the stations can be switched in sequence to 'scan' through the available stations automatically, and the system can be expanded in blocks of four channels at a time, almost without limit. Even more subtle features will become evident

as the detailed operation of the i.c.s is considered!

BLOCK OPERATION

The SAS 580 and SAS 590 are both 18 pin bipolar i.c.s with pinout and specifications shown in Fig. 1 and a block diagram shown in Fig. 2. Four RS type flip-flops control the switching in such a way that the 'setting' of any flip-flop causes the resetting of all others in the circuit. This is the means by which interlocking of the switches is provided. The flip-flops can be set either by a clock input (pin 18) or by individual switch inputs (pins 2, 4, 6 and 8). Whenever the clock input is pulsed to logic 1 (a high level) the next flip-flop along the

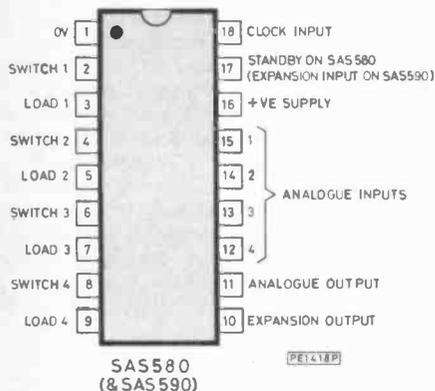

Characteristic	Notes	Min	Typically	Max	Units
Supply voltage	All specs measured at +30V supply	10		36	V
Quiescent current		2.9	7	9.5	mA
Temperature range		0		+70	°C
Analogue input voltage	Pins 15, 14, 13, 12	0.3		(+ve supply -2)	V
Analogue offset voltage	Between pins 15, 14, 13, or 12, and pin 11			±100	mV
Temperature drift	20°C to 50°C, at pin 11			5	mV
Analogue input current	Pins 15, 14, 13, 12		150	300	nA
Analogue output impedance	Pin 11		3		k
Switch input threshold	Pins 2, 4, 6, 8		5.5		V
Switch input current	Pins 2, 4, 6, 8	20	80	200	nA
Clock frequency				10	kHz
Driver load current	Pins 3, 5, 7, 9			55	mA
Saturation voltage	Pins 3, 5, 7, 9 { 1k load		0.8	1.5	V
Reverse voltage	Pins 3, 5, 7, 9 { 30k load	50	30	60	mV
	5µA to 100µA current				V
Reset to channel 1	(Pin 18) { Pulse duration	70			µs
	{ Pulse rise time			1	µs
Clock to next channel	(Pin 18) { Pulse duration		2.5		µs
	{ Pulse rise time			1	µs
Zener voltage	Pin 16 (at typically 10mA)	34		39	V
Supply current	Via resistor, when using Zener			15	mA

Fig. 1. Pinout and specifications for the SAS 580 and SAS 590

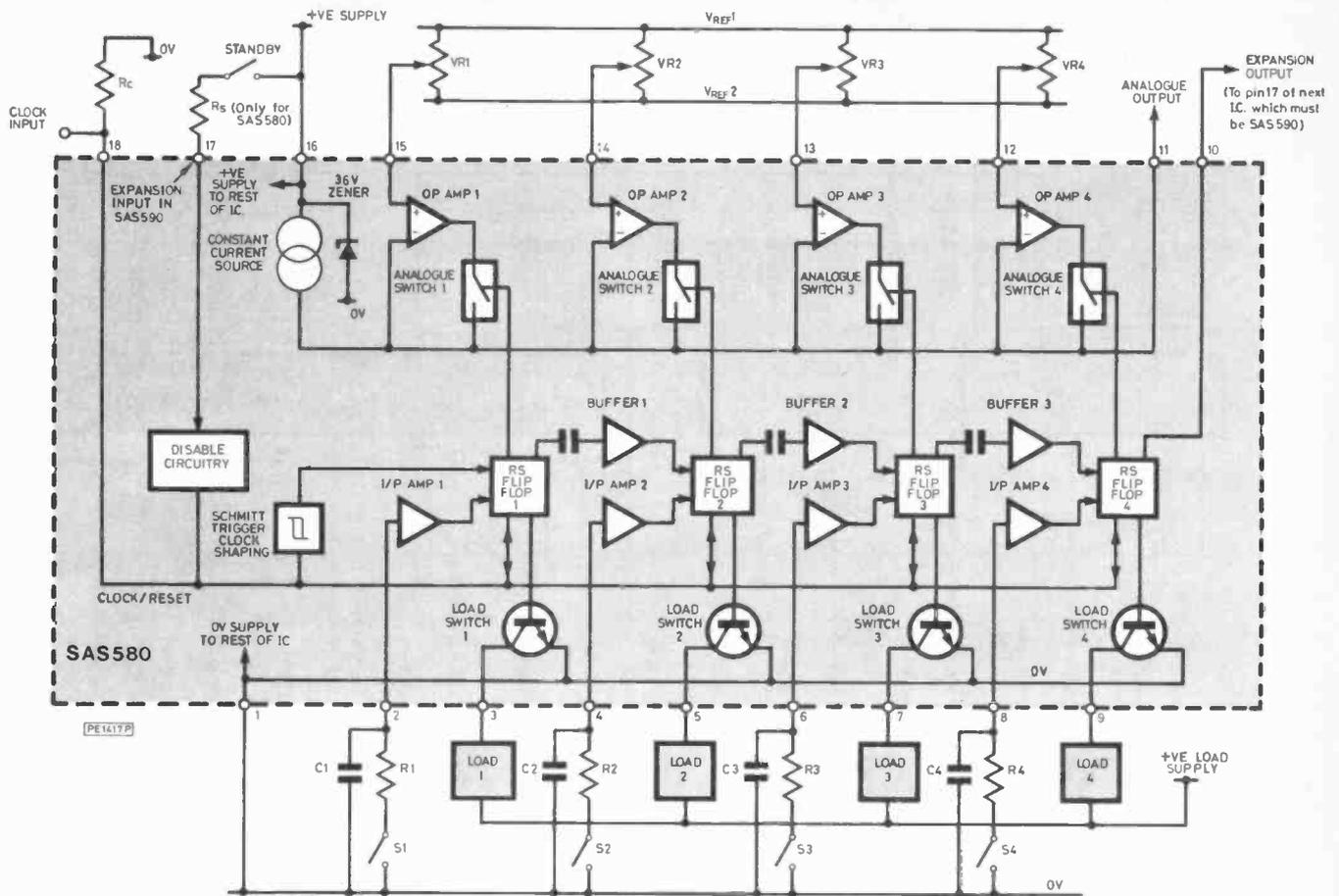


Fig. 2. Block diagram of the SAS 580 and 590

chain turns on, i.e. is set with all others turning off, i.e. reset. Hence, if flip-flop 1 is turned on, then the clock pulsed, 1 turns off as 2 turns on. On the next pulse, 2 turns off as 3 turns on, etc. At any time the individual switch inputs can override the clocking, turning on only the flip-flop required, and the clocking will start from any given flip-flop being on; 1, 2, 3 or 4.

Each flip-flop controls a load switch, which is basically an open collector *npn* transistor which can sink up to 55mA of current to 0 volts when turned on. This can be used to light an indicator, for example, to show the channel selected. The flip-flop also turns on an analogue switch around the feedback loop of a voltage following op-amp. When turned on, this switch completes the feedback loop of that op-amp, allowing the relevant analogue input voltage to be accurately reproduced, with unity gain, at pin 11 of the i.c. This can be any voltage within the limits of the specification, of course, which frees the i.c.s for use in many different applications other than varicap diode control. A constant current source provides suitable loading and biasing of the op-amp outputs.

The 'standby' facility is only provided on the SAS 580, not on the SAS 590. When R_s , normally 100k, is taken to the positive supply rail, the action is normal, but when disconnected from the positive supply the voltage at pin 17 drops to less than 0.5 volts, causing the currently selected channel to remain selected

irrespective of any switch or clock action. The i.c. is nominally rated at up to +36V supply. If higher supply voltages are to be used then adding a suitable resistor in series with the positive supply allows the internal Zener diode to regulate the voltage to between 34 and 39 volts. (This is quite safe for the i.c., even though potentially higher than the specified +36V.) Typically 13mA, and certainly no more than 15mA, should be arranged to flow into pin 16 when using this Zener facility.

INPUTS AND OUTPUTS

The switch inputs to the i.c.s, pins 2, 4, 6 and 8, are very high impedance inputs suitable for use both in touch sensitive and mechanically switched applications. The inputs are activated by momentarily connecting them to 0 volts via a large value resistor; typically 1M for mechanical switches, and 10M for touch switches. In the latter case, the switches should consist of two metal pads spaced apart by a small gap. The finger should bridge this gap to turn the input on. As with all touch controlled circuitry, great care must be taken if the equipment has a mains derived power supply, with the 0 volts supply line, and all metalwork, connected to mains earth. To provide a measure of interference rejection, capacitors should normally be connected between pins 2, 4, 6 and 8, and 0 volts. These should all be typically around 10nF, with the exception of C1 on the SAS 580 only, which should be a little larger; typically 22nF. Note

that more than one channel can be selected at once if several inputs are connected to 0 volts simultaneously. This condition only lasts until the inputs are disconnected from 0 volts, but if it causes problems then mechanical switches with electrical interlocking should be used to prevent more than one input being active at any time.

The analogue inputs and output are fairly self-explanatory. The minimum voltage that can accurately be switched is 0.3V, and the maximum is 2 volts less than the supply voltage at pin 16. Inputs as low as 0 volts or as high as the pin 16 voltage will not cause damage, but cannot be reproduced at pin 11. The output impedance at pin 11 is typically 3k, so a buffer amplifier should be provided if driving into anything other than a high impedance. The clock input, pin 18, provides both clocking and reset functions. If a positive going (high level) pulse of typically 2.5µs is fed to pin 18 it will 'clock the channels along' by one position, e.g. if channel 2 is turned on before the pulse, channel 3 will be turned on after it. If the pulse is longer than 70µs, however, the i.c. will be reset, causing channel 1 to be selected automatically irrespective of the number of i.c.s in the system. Resetting to channel 1 will also occur when power is first applied.

EXPANSION

The first i.c. in any 'chain' of devices must be an SAS 580. After that, SAS 590s must

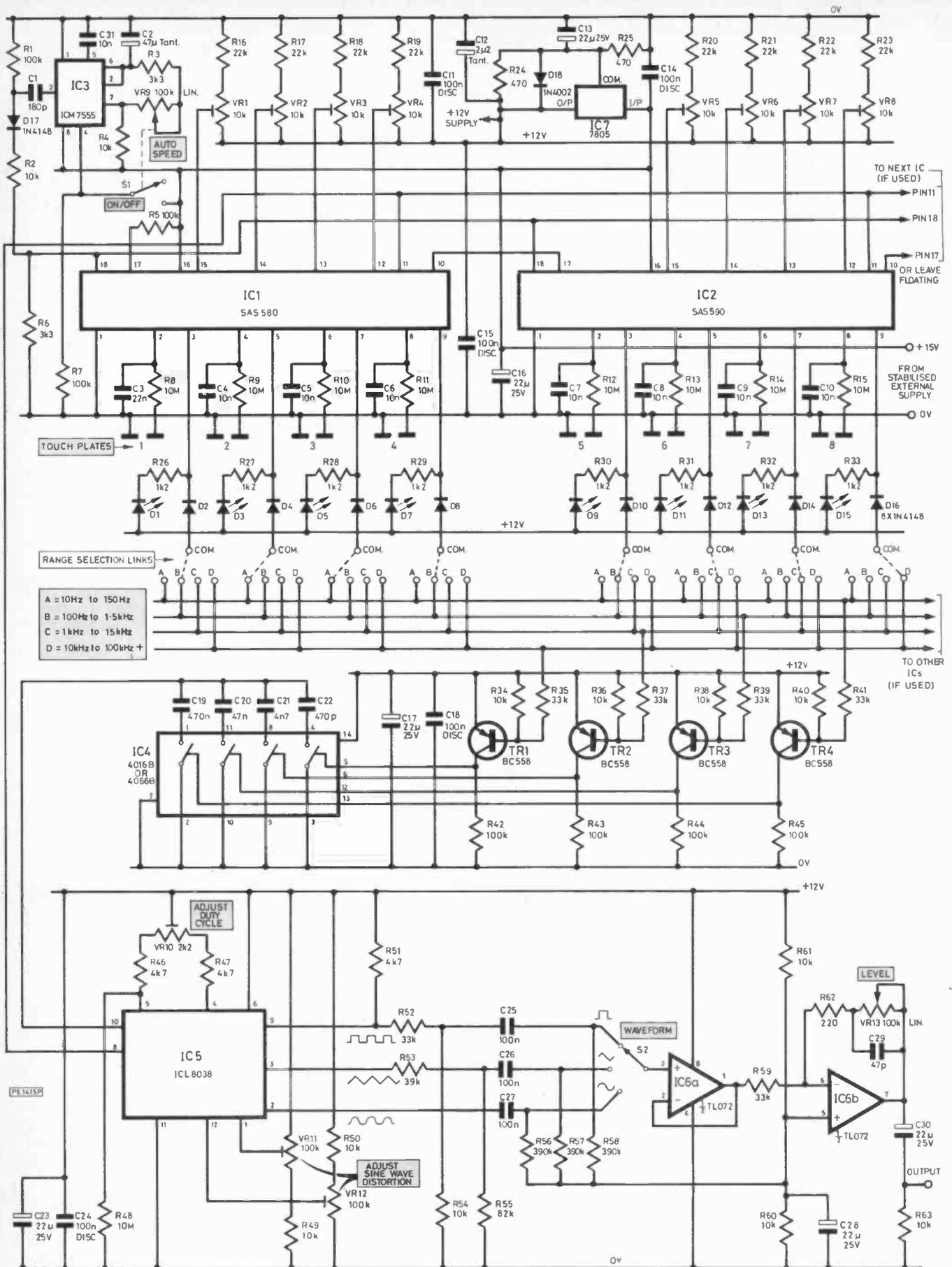


Fig. 3. Circuit diagram of the Spot Frequency Oscillator

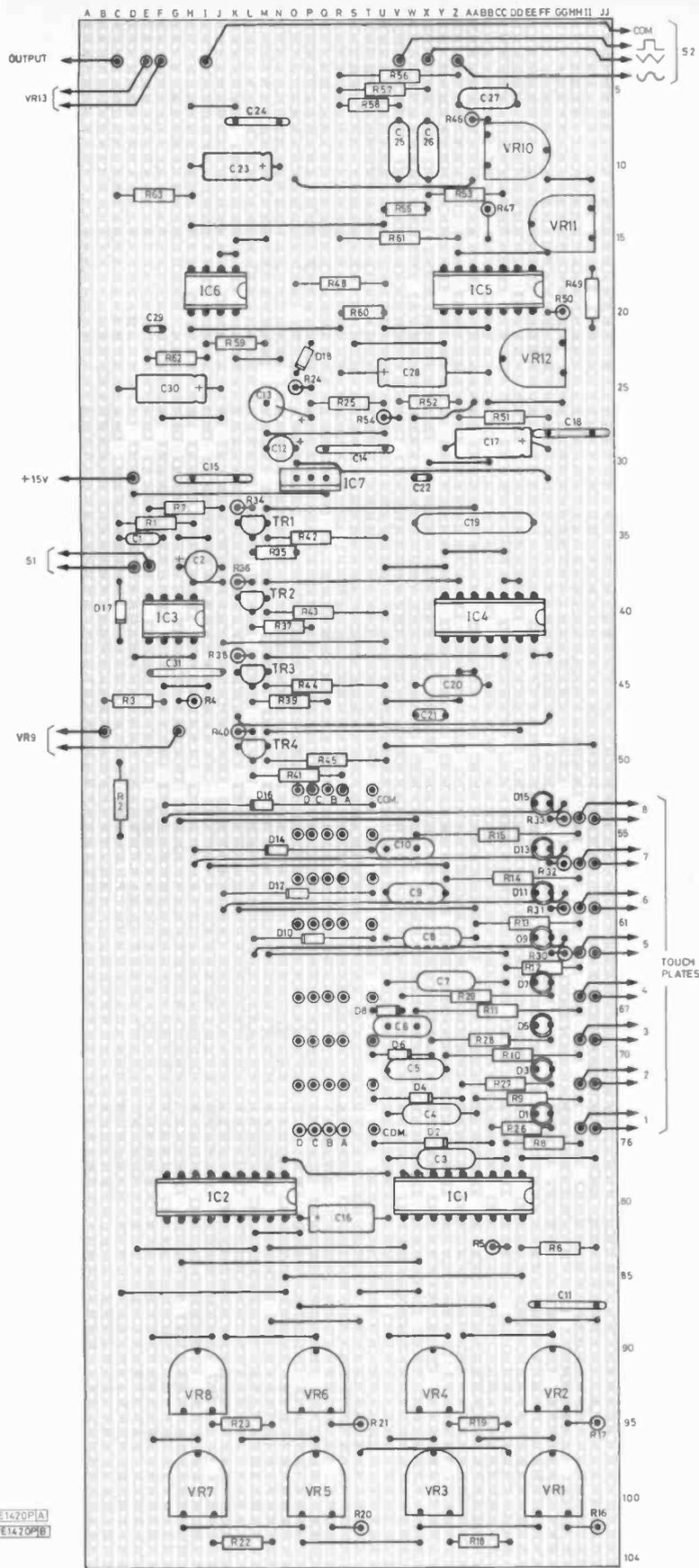


Fig. 4. Veroboard design

be used to add four channels at a time to the system. There is no limit to the number of SAS 590s which can be cascaded in this way. For all i.c.s, both 580 and 590, pins 18 should be commoned, as should all pins 11. Pin 10 of the first i.c. should connect to pin 17 of the second, then pin 10 of the second should be connected to pin 17 of the third, etc, etc, all down the line. See Fig. 3 for a simple example of this. (The 'standby' facility, and R_s , are only used on the SAS 580.) A really clever touch is that the i.c.s can detect how many devices have been connected in the chain! If only one i.c. is provided, then when clocked the sequence is 1-2-3-4-1-2-3-4-1-2 etc. If two are connected the system counts 1-2-3-4-5-6-7-8-1-2-3-4-5-6 etc. Hence, the circuit will always count round the maximum number of channels provided, without requiring special links or circuitry.

APPLICATIONS CIRCUIT

Fig. 3 shows the circuit diagram of a spot frequency oscillator, used as a 'quick check' instrument for simple audio systems. Eight different frequencies can be generated, each one variable from 10Hz to 100kHz in four bands. The switching can be manual, via touch plates, or automatic with a variable change rate.

The circuit is based around one SAS 580, one SAS 590, and a voltage controlled oscillator, the popular ICL 8038. Square, triangular, and sine waves of different amplitudes are produced by the 8038, and these are adjusted to be approximately equal in amplitude by R_{52} , R_{53} , R_{54} , and R_{55} . S_2 selects the output waveform required, and IC6 with associated components provides a variable level a.c. coupled output from the circuit. The maximum output voltage is approximately 9V pk/pk, and the minimum is around 20mV, although different output amplifier configurations could extend this range further. Four frequency bands have been provided: 10Hz to 150Hz, 100Hz to 1.5kHz, 1kHz to 15kHz, and 10kHz to 100kHz or more. The range selection is implemented by a CMOS analogue switch i.c., IC4, which connects timing capacitors C19, C20, C21, or C22 from pin 10 of IC5 to 0 volts. Wire links on the Veroboard layout shown in Fig. 4 are used to select the range chosen for each channel of the system, with TR1, TR2, TR3, and TR4 inverting and buffering the control signals from the links to IC4.

Clocking is provided by IC3, a 7555 CMOS timer connected as a low frequency oscillator. C1, R1, D17, R2, and R6 ensure that pin 18 of IC1 and IC2 receives a pulse of approximately 2.5µs duration, to clock it without danger of resetting it to channel 1. VR9 is a switched potentiometer, switch S1 ensuring that the oscillator is turned off when the potentiometer is in the extreme anti-clockwise position. IC5 requires a wide range of voltages to allow the maximum possible sweep of output frequencies. Ideally, the voltage at pin 8 of IC5 should be allowed to reach right up to the positive supply voltage. Unfortunately, the maximum output from IC1 or IC2 is 2 volts less than their positive supply. To avoid this problem, IC1, IC2, and IC3 are run from a higher supply than the rest of the circuitry; this should be a +15V regulated supply. IC7 is a +5V regulator with R24 and R25 connected in such a way that it actually provides a +12V supply to the rest of the circuitry.

In use, the range selection link for each channel should be soldered to the appropriate p.c.b. tags, and the relevant preset should be tuned to give the required output frequency. VR10 should be adjusted to give an output waveform duty cycle of exactly 50% (equivalent to a 1:1 square wave mark/space ratio). VR11 and VR12 should be adjusted for minimum distortion on the sine wave output, either visually or using a distortion analyser.

Both the SAS 580 and the SAS 590 can be obtained from Cricklewood Electronics Ltd., 40 Cricklewood Broadway, London NW2 3ET. (01-452 0161).

PE1420PIA
PE1420PIB

IT PAYS TO HAVE THE BEST CONNECTIONS

especially to PRACTICAL ELECTRONICS—the magazine for connecting hobbyists. The latest technology in a monthly selection of useful constructional projects for your home...for your car—in fact, there are hundreds of ways PRACTICAL ELECTRONICS can help you.

The biggest problem is avoiding breakdowns, like missing important issues—but now it's made easy with the PRACTICAL ELECTRONICS subscription service.

Just fill in the coupon below and have PRACTICAL ELECTRONICS delivered direct to your door every month. Avoid disconnection send off the coupon today.

Alternatively ring our special Teledata Hotline. And why not order a subscription for a friend too!

PRACTICAL ELECTRONICS SUBSCRIPTION ORDER FORM

Complete this form and post it, with payment or Credit Card authorisation to: IPC Magazines Ltd., Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. You can use this form to order a gift subscription too. Hotline. Phone TELEDATA 01-200 0200 with your Credit Card No. Allow 4 weeks for order processing.



HOTLINE
PHONE
TELEDATA

01 200 0 200

Post copies to:

NAME: _____

ADDRESS: _____

Post Code: _____

If a Gift Subscription enter your own name and address here.

NAME: _____

ADDRESS: _____

Post Code: _____


I enclose my cheque/P.O. payable to IPC Magazines Ltd. for £.

Charge my Credit Card A/C at quoted rate.

Card Valid from: _____ to _____

Signature _____

Annual Subscription Rates	
U.K.	£13.00
U.S.A. CANADA	\$28.60
Other Overseas Surface Mail	£14.00
(Students: Deduct £1.00 (\$2.20) and quote Student number.)	

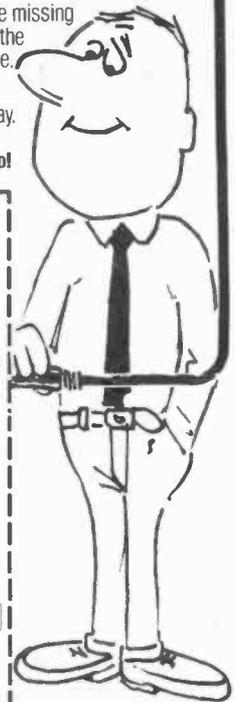

SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical uses, etc.

Approx. 16 joules. Adjustable speed. Price £45 + £2 p&p (Total inc. VAT £54.05). Case and reflector price £15 + £2 p&p (total inc. VAT £19.55). Footscap SAE for further details including Hy-Light and Industrial Strobe Kits.

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 20 watt £8.70 + VAT (Callers only)
2ft 20 watt £6.20 + £1.25 p&p (£9.57 inc. VAT)
18in 15 watt £3.50 + 75p p&p (£4.88 inc. VAT)
13in 10 watt £3.25 + 75p p&p (£4.60 inc. VAT)
12in 8 watt £3.00 + 45p p&p (£3.97 inc. VAT)
9in 6 watt £2.50 + 45p p&p (£3.39 inc. VAT)
6in 4 watt £2.50 + 45p p&p (£3.39 inc. VAT)



230V AC Ballast Kit for either 6in, 9in, or 12in tubes £5.50 p&p 55p (£6.96 inc. VAT)

For 13in, & 18in. Tubes £6 p&p 75p (£7.76 inc. VAT)

For 12V DC op. 12in, & 13in. tubes only £5.50 p&p 75p (£7.18 inc. VAT)

175 WATT SELF-BALLASTED MERCURY BULBS Available for either B.C. or E.S. fitting, price £11.79 inc. p&p and VAT

400W UV LAMP AND BALLAST complete £38 post £3.50 (£47.73 inc. VAT & p&p) 400W UV LAMP only £14 post £2 (£18.40 inc. VAT & p&p)

L.T. TRANSFORMERS

*Special Offer 0-6.3V-0-6.3V at 10 Amp (12V 0.10 Amp or 6V at 20 Amp) Price £9.00, p&p £2.00—inclusive of VAT £11.50 N.M.S.

12/24V.D.C. Reversible Precision built motor manufactured by Escap—will operate from 24-V down to 2-V DC—Current consumption negligible.

A range of speeds between 2 to 36 RPM obtainable:

6 Volt DC—9 r.p.m. N/L 6 MA, 12 Volt DC—18 r.p.m. N/L 10 MA, 24 Volt DC—36 r.p.m. N/L 18 MA. Total length of motor and gear box 90 M/M. Max. Dia 42 M/M. Shaft Length 15 M/M. Shaft Dia 6 M/M.

Approx. Half manufacturer's price: £15.00, p&p £2.00—total inclusive of VAT £19.55.

HEAVY DUTY SOLENOID, mf by Magnetic Devices, 240V A.C. intermittent operation. Approx. 20lb pull at 1.25 in. Fe. equip. Tested Price: £7.50 p&p £1.50 (£10.35 inc. VAT), R & T



VORTEX BLOWER & SUCTION UNIT

Powerful multi stage dynamically balanced, totally enclosed 9 dia Rotators, 3.500 rpm, 1 1/2" ID inlet and outlet, 110V A.C. Price £20. Suitable transformer for 240V A.C. £5 + £3 p&p (total inc. VAT £32.20) N.M.S.

COOLING or EXTRACTOR FAN Quiet smooth running. Size 4 3/4 x 4 3/4 x 1 1/2. Supplied for 240V A.C. operation Price £4.75 + £1 p&p (total inc. VAT £6.62) N.M.S.



240V A.C. SOLENOID VALVE

Designed for Air/Gas at 0.7, Water 5 psi. Inlet/outlet 3/8. Forged brass body Manuf Dewar switch Asco Price £5.50 + £1 p&p (£7.48 inc. VAT) N.M.S.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230, 240V a.e. 50/60 OUTPUT 0-260V.

200V, 1A Max.	£15.00
0.5KVA 2JA Max.	£19.00
1KVA 5A Max.	£27.00
2KVA 10A Max.	£41.00
3KVA 15A Max.	£54.00
5KVA 25A Max.	£95.00
10KVA 50A Max.	£181.00
15KVA 75A Max.	£275.00



3-PHASE VARIABLE VOLTAGE TRANSFORMERS

Dual input 200-240V or 380-415V, Star connected

3KVA 5amp per phase max	£113.40
6KVA 10amp per phase max	£170.10
10KVA 16amp per phase max	£345.45

All V V Ts plus carriage and VAT

Comprehensive range of TRANSFORMERS L.T ISOLATION & AUTO (110-240V) Either cased with American socket and mains lead or open frame type available for immediate delivery. Leaflet on request

12V D.C. BILGE PUMPS

700 G.P.H. 10ft. head, 3.5amp. £11.50 + £1.50 p&p (£14.95 inc. VAT)

1750 G.P.H. 15ft. head, 9amp. £15.00 + £1.75 p&p (£19.26 inc. VAT)



SINGLE DIAPHRAGM COMPRESSOR

Max 20 PSI. One CFM approx. 240 volts A.C.

£18 + £2 p&p (£23 inc. VAT)

EPROM ERASURE KIT

Why waste money? Build your own EPROM ERASURE for a fraction of the price of a made-up unit. Complete kit of parts less case to include 12, 8 watt 2537 Angst Tube, Ballast unit, pair of bi-pin leads, Neon indicator, safety microswitch, on/off switch and circuit.

LESS CASE Price £13.60 + 75p p&p (Total inc. VAT £16.50)

Warning: Tube used in this circuit is highly dangerous to the eyes. Unit must be fitted in suitable case.

FROM STOCK AT PRICES THAT DEFY COMPETITION!

- AC GEARED MOTORS
- DC MOTORS
- MICROSWITCHES
- RELAYS
- REED SWITCHES
- SOLENOIDS A.C. or D.C.
- PROGRAMME TIMERS
- C.F. BLOWERS
- AC CAPACITORS
- STROBE KITS
- FLASH TUBES
- CONTACTORS
- SYNCHRONOUS MOTORS

Phone in your enquiries

Superior Quality Precision Made NEW POWER RHEOSTATS



New ceramic construction, heavy duty brush assembly, continuously rated.

25 WATT 5/10/25/50/100/150/250/300/500/1K Ω

1.5k Ω £2.80 + 30p p&p (£4.71 inc. VAT).

50 WATT 250 Ω £5.50 + 50p p&p (£6.90 inc. VAT).

100 WATT 1/5/10/25/50/100/250/500/1K Ω/1.5k Ω/2.5k Ω/3.5k Ω

£7.75 + 75p p&p (£9.77 inc. VAT).

Black Silver Skirted Knob calibrated in Nos 1-9, 1 1/2 in. dia. brass bush. Ideal for above Rheostats 30p ea. + VAT.

WHY PAY MORE?

MULTI RANGE METER, Type MF15A, a.c. d.c. volts 10, 50, 250, 500, 1000, Ma 0-5, 0-10

0-100. Sensitivity 2000V, 24 range diameter 133 by 93 by 46mm including test leads.

Price £10.35 inc. VAT & p&p



INSULATED TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction suitable for bench or field work. Constant speed clutch. Size L 8in, W 4in, H 6in, weight 6lb. 500V, 300 megohms, £49, p&p £2 (£58.65 inc. VAT) 1000V 1000MΩ £55 + p&p £2 (£65.55 inc. VAT) SAE for leaflet.



GEARED MOTORS

5 rpm 240V A.C. Mf by Carter, £6.05 £1 p&p (£8.11 inc. VAT) N.M.S.

38.3 rpm GEARED MOTOR, Torque 35lb in reversible 115V AC inc. start capacity Price £11.55 + p&p (total inc. VAT £15.58) N.M.S.

Suitable TRANSFORMER 230V A.C. operation Price £4.50 + 50p p&p (total inc. VAT £5.75)

CROWN 37 rpm 200lb.in. approx. 110V AC, reversible geared motor. Price £35 p&p £4.50 (£45.42 inc. VAT) N.M.S.

Suitable transformer for above (£10 p&p £1.50 (£13.22 inc. VAT))

CROWN 42 rpm 110/230V A.C. 50 Hz, 100 lb.in. approx. Reversible geared Motor. Price £18.15 + £2.50 p&p (total inc. VAT £23.75)

120 RPM 1/10 HP APPROX. 15 lb in. 230V A.C. Cont Rating Non-reversible. Size 150mm x 90mm x 85mm spindle 8mm dia. x 30mm long. Complete with capacitor and relay for max load starting. Offered at mere fraction of mfrs price—£11.50 inc. p&p & VAT. N.M.S.

CHECK METER

200-240V A.C. 50amp. fully reconditioned, £7.50 + £1.75 p&p (total inc. VAT £10.64)

SANGAMO WESTON TIME SWITCH

Type S251 200/250 A.C. 2 on/2 off every 24 hours, 20 amps contacts with override switch Diameter 4 x 3 price £9.50 + £1.50 p&p (£12.65 inc. VAT & p&p) Also available with solar dia R&T

Other types available from stock

N.M.S. New Manufacturers' Surplus

R&T Reconditioned and tested

Good normally despatched within 7 days.



Ample parking space
Showroom open
Monday-Friday



SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB. 01-995 1560
ACCOUNT CUSTOMERS MIN. ORDER £10

Personal callers only. Open Saturdays

9 Little Newport Street
London WC2H 7JJ
Tel: 01-437 0576

Affordable Accuracy - Low Cost Multimeters from Armon

SPECIFICATION MODELS

HC-6010 & HC-7030 DIGITAL

- ★ 10 amp AC/DC
- ★ Battery: Single 9V drycell. Life 200 hrs.
- ★ Dimensions: 170 x 89 x 38mm
- ★ Weight: 400g inc. battery
- ★ Mode Select: Push Button
- ★ AC DC Current: 200µA to 10A
- ★ AC Voltage: 200mV to 750V
- ★ DC Voltage: 200mV to 1000V
- ★ Resistance: 200Ω to 20MΩ
- ★ Input Impedance: 10MΩ
- ★ Display: 3 1/2 Digit 13mm LCD
- ★ O/Load Protection: All ranges

28 RANGES, EACH WITH FULL OVERLOAD PROTECTION



SPECIFICATION

HM 102R ANALOGUE

- ★ DC Voltage: 0.25, 2.5, 10, 50, 250, 500, 1000 volts
- 20,000 ohms/volt.
- ★ AC Voltage: 2.5, 10, 50, 250, 500, 1000 volts
- 8,000 ohms/volt.
- ★ Decibels: -20 to +62dB.
- ★ DC Current: 0-50, 500µA, 0-5, 50, 500mA.
- ★ Ohmmeter: 0-10 Megohms in 4 ranges. 50 ohms Centre Scale.
- ★ Power Supply: One 1.5 V Size 'AA' battery (incl).
- ★ Size & Weight: 135 x 91 x 39mm, 280gr.

HC 102BZ WITH BUZZER, BATTERY SCALE & 10A DC RANGE



ARMON ELECTRONICS LTD.

Dept L, Cottrell House, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH,
Telephone 01-902 4321 (3 lines). Telex 923985

Please add 15% to your order for VAT. P&P free of charge. Payment by cheque with order.
Offer applicable to mainland UK only. Please allow 15 days for delivery.



CLEF ELECTRONIC MUSIC



(As Published in P.E.)

2 1/2 Octave Music Synthesizer with 2 Oscillators, 2 Sub-Octs. Switched Routing and Thumbwheel. A comprehensive instrument offering the full range of Synth. Music & effects. FULL KIT £137 Also available in 3 parts

PERCUSSION MICROSYNTH

As Published in P.E.

Two Channel touch Sensitive unit plus variable angle L.F.O., phaser, internal and external triggering. ELECTRONIC COMPONENT KIT £89

MASTER RHYTHM PROGRAMMABLE DRUMS



As Published in P.E.

Twenty-Four Rhythm programmable Drum Machine with twelve instruments. Eight sections are extended to 24/32 measures for two bar programming. Sequence operation and instrument tone adjust. COMPLETE KIT £79

STRING ENSEMBLE ROTOR-CHORUS £198.50

SQUARE FRONT KEYBOARDS 88 NOTE £60 49 NOTE £29

73 NOTE £50 30 NOTE £19

KEYSWITCH ITEMS ALSO AVAILABLE

88/72 NOTE PIANOS SPECIALISTS SINCE 1972

Using Patented electronic technique to give advanced simulation of Piano Key Inertia.

COMPONENT KITS

including Keyboard
88 NOTE £266
72 NOTE £234

The above may also be purchased in four parts.

DOMESTIC KITS

inc. Cabinet, P.A. & Spkr
88 NOTE £442
72 NOTE £398

STAGE MODEL

inc. Cabinet & Stand
72 NOTE £383

ALL PRICES INC. VAT. CARR & TELEPHONE ADVICE. S.A.E. for full Specs & MANF. PRICES. VISA-ACCESS-AMERICAN EXPRESS. Competitive quotes can be given for export. Allow 3-14 days for normal despatch.

CLEF PRODUCTS (ELECTRONICS) LIMITED
(Dept P.E.) 44A BRAMHALL LANE SOUTH BRAMHALL
STOCKPORT CHESHIRE SK7 1AH TEL 061-439 3297

BAND-BOX PROGRAMMABLE BACKING TRIO



As Published in P.E.

THREE PIECE BACKING BAND
Generates the sounds of three instrumentalists to back Soloists
DRUMS + BASS + KEYBOARDS
Over 3,000 chord changes (60 scores) on 132 different chords - extendable to 200 scores. Master RHYTHM also required.

FULL KIT EXTENSION £235 £82

ADVANCED TELECOMMUNICATIONS

Careers with extensive scope at Cheltenham

Join the Government Communications Headquarters, one of the world's foremost centres for R & D and production in voice/data communications ranging from HF to satellite - and their security. Some of GCHQ's facilities are unique and there is substantial emphasis on creative solutions for solving complex communications problems using state-of-the-art techniques including computer/microprocessor applications. Current opportunities are for:

Telecommunication Technical Officers

Two levels of entry providing two salary scales: £6262 - £8580 & £8420 - £9522

Minimum qualifications are TEC/SCOTEC in Electronics/Telecommunications or a similar discipline or C & G Part II Telecommunications Technicians Certificate or Part I plus Maths B, Telecommunication Principles B and either Radio Line Transmission B or Computers B or equivalent: ONC in Electrical, Electronics or Telecommunications Engineering or a CIE Part I Pass, or formal approved Service technical training. Additionally, at least 4 years' (lower level) or seven years' (higher level) appropriate experience is essential in either radio communications or radar, data, computer or similar electronic systems.

At the lower entry level first line technical/supervisory control of technicians involves "hands-on" participation and may involve individual work of a highly technical nature. The higher level involves application of technical knowledge and experience to work planning including implementation of medium to large scale projects.

Radio Technicians - £5485 - £7818

To provide all aspects of technical support. Promotion prospects are good and linked with active encouragement to acquire further skills and experience. Minimum qualifications are a TEC Certificate in Telecommunications or equivalent plus 2 or more years' practical experience.

Cheltenham, a handsome Regency town, is finely-endowed with cultural, sports and other facilities which are equally available in nearby Gloucester. Close to some of Britain's most magnificent countryside, the area also offers reasonably-priced housing. Relocation assistance may be available.

For further information and your application form, please telephone:

Cheltenham (0242) 32912/3 or write to:



Recruitment Office, Government Communications Headquarters,
Oakley, Priors Road, Cheltenham,
Gloucestershire, GL52 5AJ.

BAKER LOUSPEAKERS

Model	Inches	Ohms	Watts	Type	Price	Post
Mid 100/10	10	8	100	Mid Range	£25	£2
DG 50	10	8-16	50	PA	£18	£2
Major	12	4-8-16	30	Hi-Fi	£16	£2
Superb	12	8-16	30	Hi-Fi	£26	£2
Wooler	12	8	30	Hi-Fi/Woof	£25	£2
Auditorium	15	8-16	60	Hi-Fi/Woof	£37	£2
DG 45	12	4-8-16	45	PA Disco	£16	£2
DG 75	12	4-8-16	75	PA Disco	£20	£2
DG 100	12	8-16	100	PA Disco	£26	£2
DG 100	15	8-16	100	PA Disco	£36	£2
Goodmans 15	8	250	PA Disco	£72	£4	
Goodmans 18	8	230	PA Disco	£84	£4	
P.A. CABINETS (Imped. Single 12 Ω): Double 12 Ω, carr £10.						
WITH SPEAKERS 60W £26, 75W £50, 90W £68, 150W £80.						
HORNBOXES 200 Watt £30, 300 Watt £35 post £4.						
BAKER AMPLIFIERS All Transistor post £2.00						
60w, 4 inputs, 240v AC and 12v DC, 8 ohm + 100v line £88.00						
150w, 4 inputs, mains, all purpose mixer amplifier £99.00						
150w, 8 inputs, mains PA mixer amplifier £129.00						
150+150w stereo slave amplifier 300W mono £125.00						
DISCO CONSOLE Twin Decks, mixer pre amp £106, Carr £12.						
COMPLETE DISCO 150 watt £330, 300 watt £399, Carr £70.						
GENERAL PURPOSE LOW VOLTAGE MAINS TRANSFORMERS						
Tapped outputs available						
2 amp	3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V	£6.00	£2			
1 amp	6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6.00	£2			
2 amp	6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£10.50	£2			
3 amp	6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£12.50	£2			
5 amp	6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£16.00	£2			
5-8-10-16V, 1 amp	£2.50	£1	15-0-15V, 1 amp	£4.00	£1	
6V, 1 amp	£2.00	£1	15-0-15V, 2 amps	£5.00	£1	
6-0-6V, 1 amp	£3.50	£1	16V 2 amps	£4.00	£1	
9V, 250ma	£1.50	£0	20V 1 amp	£4.00	£1	
9V, 3 amps	£4.00	£1	0-12-27V 2 amps	£5.00	£1	
9-0-9V, 50 ma.	£1.50	£0	20-0-20V, 1 amp	£3.50	£1	
9-0-9V, 1 amp	£3.50	£1	20-40-60V, 1 amp	£3.50	£2	
10-0-10V, 2 amps	£4.00	£1	25-0-25V, 2 amps	£5.50	£2	
10-30-40V, 2 amps	£5.50	£1	28V, 1 amp Twice	£7.00	£2	
12V, 300 ma.	£2.00	£0	30V, 1 amp	£5.00	£1	
12V, 750 ma.	£2.50	£0	30V 5 amp and	£4.50	£2	
12V, 3 amps	£4.50	£1	17-0-17 2a	£4.50	£2	
12-0-12V, 2 amps	£4.50	£1	35V, 2 amps	£4.90	£2	
ALUMINIUM CHASSIS: 6x4-£1.75, 8x6-£2.20, 10x7-£2.75;						
12x8-£3.20; 14x9-£3.60; 16x16-£2.50; 16x10-£3.90;						
12x3-£2.20; 14x3-£2.50, 2 1/2in sides 18 swg.						
ALUMINIUM PANELS: 6x4-55p; 8x6-90p; 14x3-90p;						
10x7-£1.15; 12x8-£1.30; 12x5-90p; 16x6-£1.30; 14x9-£1.75;						
12x12-£1.80; 16x10-£2.10. ANGLE ALL 6x4-£1.30p.						
ALUMINIUM BOXES: 4x4x1 £1.20; 4x2x2 £1.20;						
3x2x1 £1.20; 6x4x2 £1.90; 7x5x3 £2.90; 8x6x3 £3;						
10x7x3 £3.60; 12x5x3 £3.60; 12x8x3 £4.30.						
BLACK PLASTIC BOX with All Fascia 6 1/2x3 1/2x2 1/2 £1.50						
HIGH VOLTAGE ELECTROLYTICS: 125/500V £2.00						
2/350V 35p 8+ 8/500V £1.00 16+ 16+16/275V 50p						
4/350V 35p 8+ 16/450V 75p 100+100/275V 50p						
20/500V 75p 16+16/350V 75p 150+200/275V 50p						
32/350V 50p 32+32/350V 75p 32+32+16/350V 75p						
32/500V 95p 20+20/350V 75p 32+32+32/325V 50p						
16/450V 45p 50+50/300V 50p 32+32+32/450V 95p						
9 volt 400ma. Mains/Battery Eliminator: PP9 £5 post £1						

RADIO COMPONENT SPECIALISTS

Dept 3, 337, WHITEHORSE ROAD, CROYDON
SURREY, U.K. Tel: 01-684 1665
ACCESS Post 65p Minimum. Callers Welcome. VISA
Lists 32p. Same day despatch. Closed Wed.

SERVICE SHEETS

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

COURSES

CONQUER THE CHIP... Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to British National Radio & Electronics School, Dept. C2, Reading, Berks. RG1 1BR.

SECURITY

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
- HIGHEST QUALITY EQUIPMENT
- FREE DIY DESIGN GUIDE
- FULLY ILLUSTRATED
- MICROCHIP CIRCUITRY
- QUICK DESPATCH SERVICE
- FULL INSTRUCTIONS

SEND SAE OR PHONE

C-TEC SECURITY, Dept PW
60 Market St, Wigan WN1 1HX.
Telephone (0942) 42444



HOME SECURITY

WHO CAN PUT A PRICE ON PEACE OF MIND
PROFESSIONAL EQUIPMENT AT LOW LOW PRICES.
HOME SECURITY IS NOW AVAILABLE AT TRADE PRICES
ADVANCED SECURITY PRODUCTS LTD
2 Ealing Road, Aintree,
Liverpool L9 0HU, Merseyside.
Tel: 051-525 3440
FREE CATALOGUE
PHONE OR S.A.E.

SERVICES

INVENTORS

Think of something new?
Write it down!—

American industry offers potential royalties for your innovations and new products. We offer free confidential disclosure registration and initial consultation in London regarding your idea's potential value. Write without delay for your free information package.

American Inventors Corporation
82, Broad Street, Dept PT
Westfield, Massachusetts 01086
United States of America.

A fee based marketing company.

FOR SALE

DEWTRON 4 OCTAVE KEYBOARD synthesiser/8 channel sequence. Offers. 08833 3706.

COMPONENTS & EQUIPMENT - 1984 Catalogue 70p + 20p P&P. Callers: 18 Victoria Road, Tamworth, 369 Alumrock Road, Birmingham. 103 Coventry Street, Kidderminster. Express Mail Order Service. LIGHTNING ELECTRONICS, P.O. Box 8, Tamworth, Staffs.

SHEET METAL FOLDERS 18" x 18G, bench or vice held £38. Leaflet, 01-890 7838. 90 Granville Avenue, Feltham, Middx. TW13 4JN.

LOGIC BOARDS Astro Wars ex-arcade games containing processor. P.I.A. 10x2708 Eproms, sixty integrated circuits. Ideal for parts or experimentation. £25.00 each includes post & packing. A.L.S. LTD., The Maltings, Westmore Road, Burton upon Trent, Staffs. Telephone Staffs 0283 67421.

MISCELLANEOUS

CLEARING LABORATORY: scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders, etc. 0403-76236.

OPTICAL AIDS, MAGNIFIERS. Free Catalogue. MASON & GANTLETT, 29 Surrey Street, Norwich.

INCREASE YOUR MEMORY HM6116LP-3 for sale. Fully guaranteed. £2 each 25pp per order. RONALD POTTS, 37 Heathcote Street, Chesterton, Newcastle, Staffs. 564037.

BURGLAR ALARM EQUIPMENT. Ring Bradford (0274) 308920 for our Catalogue or call at our large showrooms opposite Odsal Stadium.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from PVC faced steel. Vast range. Competitive prices start at a low £1.50. Punching facilities at very competitive prices. - Bazelli (Dept 23), St Wilfreds, Foundry Lane, Halton, Lancaster LA2 6LT.

PCB DESIGN manually taped artwork at competitive prices. JAMES GLEDHILL, Telephone 01-674 8511

MAKE YOUR OWN PRINTED CIRCUITS

Alfac Etch Resist Transfers - Starter pack (5 sheets), lines, pads, I.C. pads) £2.80. Large range of single sheets in stock at 56p per sheet.
Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. 2 sheets document paper, 2 sheets MSM film (A4) £2.50.
Photo-resist spray (200 ml) £3.90 (p+p 65p).
Drafting Film (A4) 30p. Precision Grids (A4) 65p.
20p stamp for lists and information. P&P 50p per order plus extra where indicated. No VAT payable.

P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE.

SCOPES

REPAIRED AND RECALIBRATED
ALL MAKES, ALL MODELS
SCOPEX, SAFGAN, OLDER TEK & TO

Mendascope Ltd.

OTTER HOUSE,
WESTON UNDERWOOD
OLNEY, BUCKS, MK46 5JS
BEDFORD (0234) 712445

THE SCIENTIFIC WIRE COMPANY

811 Forest Road, London E17. Telephone 01-531 1568

SWG	ENAMELLED COPPER WIRE			
	1 lb	8 oz	4 oz	2 oz
8 to 34	3.63	2.09	1.10	0.88
35 to 39	3.82	2.31	1.27	0.93
40 to 43	6.00	3.20	2.25	1.61
44 to 47	8.67	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69

14 to 30	SILVER PLATED COPPER WIRE	
	9.09	5.20
14 to 30	3.97	2.41

14 to 30	TINNED COPPER WIRE	
	3.97	2.41
Fluxcore Solder	5.90	3.25

Prices include P&P VAT. Orders under £2 add 20p. SAE for list of copper and resistance wire. Dealer enquiries welcome.

the Leader of the Packs

BIG VALUE RESISTOR PACKS

1/2 WATT CARBON FILM
1Ω-10MΩ ten values.
Total 720 resistors. **£5**

1/2 WATT METAL FILM
1% 50ppm 10Ω-1MΩ E24 range.
Total 960 resistors. **£25**

FREE CATALOGUE

Sent to every new customer

AC/DC COMPONENT PACKS

Pack No.	Qty	Description	Price
TF11	12	RED 5mm LED	£1.00
TF12	30	500mz ZENERS 5%	£1.00
TF13	100	IN4148 Diode	£1.00
TF14	100	IN4151 Diode	£1.00
TF15	50	1 amp Rect. Diodes in 4000 series	£1.00
TF16	6	1 amp Bridge Rect.	£1.00
TF17	100	Transistor pads	£1.00
TF18	20	A/S Fuses 20mm	£1.00
TF19	10	3A Rect. Diodes	£1.00
TF110	2	ORP 12	£1.00
TF111	5	BR 100 DIAC	£1.00
TF112	10	BC109B	£1.00
TF113	10	IC's all different	£1.00
TF114	50	BFR86	£1.00
TF115	12	8 pin DIL sockets	£1.00
TF116	20	10mm Horiz. Pre set (10 values)	£1.00
TF21	200	47pf 160v Polystone cap	£2.00
TF22	10	LM 3900 N	£2.00
TF23	10	Mixed DTL	£2.00
TF24	5	4700 mf 25v Tag Elect 2" x 1"	£2.00
TF25	10	1000 mf 63v Ax Elect.	£2.00
TF26	50	.022 mf 400v RAD POLY	£2.00
TF27	10	100mf 250v Ax	£2.00
TF28	10	2.2mf 160v Polyester RAD	£2.00
TF51	100	white/red 5mm LED	£5.00
TF52	50	BC 108C	£5.00
TF53	2	10,000mf 63v comp. grade elect.	£5.00
TF54		1/2 kg reel 22g ersin multicore solder	£5.00
TF55	10	2N3055 H(RCA)	£5.00
TF56	5	0CP71	£5.00

ALL PRICES INCLUDE VAT - ALL GOODS BRAND NEW & NORMALLY DESPATCHED BY RETURN POST.

TERMS: Cash with order. POST & PACKING: Please add 75p to total order.

AC/DC ELECTRONICS COMPONENTS

DEPT P.E., 45 CHURCH STREET,
ENFIELD, MIDDLESEX.

WORLD RADIO T.V. HANDBOOK

1984 ed. Price: £12.00

1984 THE RADIO AMATEUR'S H/B
by A.R.R.L. Price: £12.50

BEGINNER'S GUIDE TO INTEGRATED CIRCUITS
by I. R. Sinclair Price: £4.50

ELECTRONIC PROTOTYPE CONSTRUCTION
by S. D. Kasten Price: £15.95

UNDERSTANDING ELECTRONIC SECURITY
SYSTEMS
by M. D. LaMont Price: £2.30

UNDERSTANDING DIGITAL ELECTRONICS
by G. McWhorter Price: £4.30

INTRODUCTION TO ELECTRONIC SPEECH
SYNTHESIS
by N. Sclater Price: £8.00

ELECTRONICS FOR HIGHER TEC
by S. A. Knight Price: £10.00

DOMESTIC VIDEOCASSETTE RECORDERS
A SERVICING GUIDE
by S. Beeching Price: £15.50

SEMICONDUCTOR DATA BOOK
by A. M. Ball Price: £7.50

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-402 9176

Closed Saturday 1 p.m.

Please allow 14 days for reply or delivery.

INDEX TO ADVERTISERS

A.C. Electronics	64
AC/DC Electronics	65
A.D.E.	65
Alcon Instruments	20
Armon Products	63
Audio Electronics	20
Barrie Electronics	9
Bensham Recordings	32
Blackstar	16
Bi-Pak	45
Bridage	19
British National Radio & Electronics School	4
Clef Products	63
Colour Print Express	Cover 2
Computonics	65
Cricklewood	Cover 3
C.R. Supply Co. The	64
Electrovalve	8
Hameg	17
G.C.H.Q.	63
Gemini	65
G.S.C.	17 & 19
ICS Intertext	7
ILP Electronics	9
Mapln Supplies	4 & Cover 4
M.D. Marketing	9
Mendascopes	65
Midwich	7
Millhill	66
Modern Book Co.	66
Phonosonics	66
P.K.G. Electronics	65
Powertran	10
Radio Component Specialists	63
Radio & T.V. Components	8
Riscomp	32
Scientific Wire Co. The	65
Service Trading	62
Sparkrite	32
Swanley Electronics	8
Thurby Electronics	19
T.K. Electronics	5
Wattford Electronics	2 & 3

SUPERKITS! FOR BETTER MUSIC & EFFECTS

Sets include PCBs, Electronic Parts, Instructions, Boxes, Wire, Solder, Batteries not included, but most will run from 9V to 15V DC supplies. Fuller details in list.

CHORUS UNIT: A solo voice or instrument sounds like more! ...KIT162	£31.40
COMPRESSOR: Limits & levels maximum signal strength ...KIT133	£10.86
COMPUTER RHYTHM GEN: 9 drums for digital control ...KIT185	£30.64
COMPUTER-SYNTH INTERFACE: Sequencing & composing aid ...KIT184	£17.44
DRUM SIRENS: Triggered variable siren effects ...KIT199	£19.93
ECHO UNIT: With double tracking ...KIT168	£44.30
FREQUENCY DOUBLER: Raises guitar frequency by 1 octave ...KIT98	£9.80
FREQUENCY CHANGER & WAVEFORM MODIFIER - Tunable ...KIT172	£34.46
FLANGER: Fascinating effects plus phasing ...KIT153	£22.74
FUZZ: Smooth distortion whilst keeping natural attack & decay ...KIT91	£10.57
GUITAR EFFECTS: Multiple variation of level & filter modulation ...KIT42	£15.40
GUITAR OVERDRIVE: Fuzz plus variable filter quality ...KIT56	£19.73
GUITAR SUSTAIN: Extends effective note duration ...KIT75	£10.04
GUITAR TO SYNTH INTERFACE: With voltage & trig outputs ...KIT173	£32.87
HAND CLAPPER: Triggered & auto claps, variable tone ...KIT197	£22.69
METRONOME: With audio & visual beat & down beat ...KIT143	£13.81
MULTIPROCESSOR: Flng, Rvb, Faze, Fuz, Wah, Trem, Vib ...KIT189	£57.14
MICROPHONE PRE-AMP: with base & treble switching ...KIT144	£9.21
NOISE LIMITER: reduces tape & system hiss ...KIT145	£9.97
PHASER: with automatic & manual depth & rate controls ...KIT164	£18.40
REVERB: Mono/stereo, variable depth & delays ...KIT203	£25.54
RHYTHM GENERATOR: 15 switchable rhythms ...KIT170	£35.64
RING MODULATOR: with integral oscillator control ...KIT179	£15.76
ROBOVOX: versatile robot type voice modifier ...KIT165	£21.03
ROGER 2-GONG: 2 gongs sounded at end of transmission ...KIT126	£11.38
SPEECH PROCESSOR: for clearer transmission ...KIT110	£9.68
STORM EFFECTS: Automatic & manual, wind, rain, surf ...KIT154	£15.86
TOM-TOM SYNTH: Triggered variable tone drum effects ...KIT190	£15.05
TREMLO: deep tremolo with depth & rate control ...KIT136	£9.71
VOCODAVOX: modular vocoder ...KIT152	£64.31
VOICE-OP-SWITCH: with variable sensitivity & delay ...KIT123	£13.41
WAH-WAH: with auto-trigger, manual & oscillator control ...KIT140	£17.26

MANY OTHER GREAT KITS IN CATALOGUE such as Autowah, bass boost, call sign, comparator, frequency generator, Funky-wobulol, hamonola, hum-cut, mixers, sequencers, synthesiser interface, treble boost, tone control, vibrato, voice filter, voice operated fader, Wheeby-jeebyl, wobble-wah. Plus digital synthesiser, junior synthesiser, envelope shapers, D-A converter, multiwaveform VCO, Keyboards, contacts, etc. - Send S.A.E. for comprehensive catalogue (overseas send £1).

YES - WE ALSO HAVE A KIT MAINTENANCE & REPAIR SERVICE!

Add £1 P&P & 15% VAT to all orders. (Overseas post details stated in cat). Payment CWO, Chq, PO, Access, Barclay, or pre-arranged collection. Despatch usually 10-14 days. Details correct at press, E&OE.

PHONOSONICS, DEPT PE46, 8 Finucan Drive, Orpington, Kent, BR5 4ED.
Tel: Orpington (STD 0689) 37821. Mon-Fri 10-7. Callers by appointment.

OVERSEAS ORDERS

Overseas readers are reminded that unless otherwise stated, postage and packing charges published in advertisements apply to the United Kingdom only.

Readers wishing to import goods from the United Kingdom are advised to first obtain from the advertiser(s) concerned an exact quotation of the cost of supplying their requirements carriage paid home.

STORAGE CABINETS

Steel cabinets, 12" wide x 5 1/2" deep x 22" high finished blue with clear plastic drawers.


Available units:-

Type	Drawers
2260	60 x A
2248	48 x B
2224	24 x C

Type	Drawers
2216	16 x D
2208	8 x E

30 x A, 4 x D, 2 x E

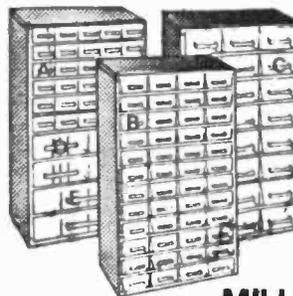Price each £22.75
Price per 3 ONLY £60.00
(inc. p&p and VAT)



Access/Barclaycard welcome or cheque/PO to:-

MILLHILL SUPPLIES
66 THE STREET, CROWMARSH, WALLINGFORD
OXON. OX10 8ES. Tel. 0491 38653
Delivery within 14 days.



**THE TELEPHONE
& MAIL ORDER
SPECIALISTS**
PRICES SUBJECT TO
ALTERATION, PHONE
FOR LATEST PRICES
AND DELIVERY

**CRICKLEWOOD
ELECTRONICS LTD**
40 CRICKLEWOOD BROADWAY
LONDON NW2 3ET
01-452 0161/01-450 0995 Tlx: 914977

This list contains only a fraction of
CRICKLEWOOD'S stock. Please add
60p p&p & 15 VAT to all orders.
Official orders from schools, colleges,
Govt. Depts. etc. welcome.

All in stock items despatched same day unless notified

RESISTORS	Siemens	7491	74LS161	4072	19p	1 Amp TO220	40412	90p	BC338	15p	BFY50	36p	ZTX500	14p	3amp type	SL490	3.47	100 x 160 2.10
CARBON FILM	AXIALS Wires	7492	74LS162	4073	19p	79p	40623	70p	BC440	32p	BFY51	36p	ZTX501	14p	Square with hole	SL490	3.47	100 x 220 5.20
5% HI-BL	each and 10	7493	74LS163	4074	19p	79p	40627	180p	BC441	32p	BFY52	36p	ZTX502	14p	PW02 (100) 99p	SN78003	2.95	203 x 114 2.30
LOW NOISE	100 to 10M	7494	74LS164	4075	19p	79p	40671	100p	BC460	32p	BFY53	31p	ZTX503	17p	PW02 (100) 99p	SN78013	2.95	203 x 220 5.20
100 to 10M	100 to 10M	7495	74LS165	4076	19p	79p	40672	100p	BC461	32p	BSX19	24p	ZTX504	24p	PW06 (16001) 39p	SN78033	2.95	Double Sided
1/4W E24 2p	1/4W E24 2p	7496	74LS166	4077	19p	79p	40673	100p	BC462	32p	BSX21	24p	ZTX505	24p	PW06 (16001) 39p	TA7204	1.99	100 x 160 2.20
1/4W E24 2p	1/4W E24 2p	7497	74LS167	4078	19p	79p	40674	100p	BC463	32p	BSX22	24p	ZTX506	24p	PW06 (16001) 39p	TA7205	1.99	100 x 200 2.80
1/4W E24 2p	1/4W E24 2p	7498	74LS168	4079	19p	79p	40675	100p	BC464	32p	BSX23	24p	ZTX507	24p	PW06 (16001) 39p	TA7206	1.99	203 x 114 2.30
1/4W E24 2p	1/4W E24 2p	7499	74LS169	4080	19p	79p	40676	100p	BC465	32p	BSX24	24p	ZTX508	24p	PW06 (16001) 39p	TA7207	1.99	233 x 220 5.90
1/4W E24 2p	1/4W E24 2p	7500	74LS170	4081	19p	79p	40677	100p	BC466	32p	BSX25	24p	ZTX509	24p	PW06 (16001) 39p	TA7208	1.99	Developer for above info use Sodium Hydroxide
1/4W E24 2p	1/4W E24 2p	7501	74LS171	4082	19p	79p	40678	100p	BC467	32p	BSX26	24p	ZTX510	24p	PW06 (16001) 39p	TA7209	1.99	500ml 2.95
1/4W E24 2p	1/4W E24 2p	7502	74LS172	4083	19p	79p	40679	100p	BC468	32p	BSX27	24p	ZTX511	24p	PW06 (16001) 39p	TA7210	1.99	
1/4W E24 2p	1/4W E24 2p	7503	74LS173	4084	19p	79p	40680	100p	BC469	32p	BSX28	24p	ZTX512	24p	PW06 (16001) 39p	TA7211	1.99	
1/4W E24 2p	1/4W E24 2p	7504	74LS174	4085	19p	79p	40681	100p	BC470	32p	BSX29	24p	ZTX513	24p	PW06 (16001) 39p	TA7212	1.99	
1/4W E24 2p	1/4W E24 2p	7505	74LS175	4086	19p	79p	40682	100p	BC471	32p	BSX30	24p	ZTX514	24p	PW06 (16001) 39p	TA7213	1.99	
1/4W E24 2p	1/4W E24 2p	7506	74LS176	4087	19p	79p	40683	100p	BC472	32p	BSX31	24p	ZTX515	24p	PW06 (16001) 39p	TA7214	1.99	
1/4W E24 2p	1/4W E24 2p	7507	74LS177	4088	19p	79p	40684	100p	BC473	32p	BSX32	24p	ZTX516	24p	PW06 (16001) 39p	TA7215	1.99	
1/4W E24 2p	1/4W E24 2p	7508	74LS178	4089	19p	79p	40685	100p	BC474	32p	BSX33	24p	ZTX517	24p	PW06 (16001) 39p	TA7216	1.99	
1/4W E24 2p	1/4W E24 2p	7509	74LS179	4090	19p	79p	40686	100p	BC475	32p	BSX34	24p	ZTX518	24p	PW06 (16001) 39p	TA7217	1.99	
1/4W E24 2p	1/4W E24 2p	7510	74LS180	4091	19p	79p	40687	100p	BC476	32p	BSX35	24p	ZTX519	24p	PW06 (16001) 39p	TA7218	1.99	
1/4W E24 2p	1/4W E24 2p	7511	74LS181	4092	19p	79p	40688	100p	BC477	32p	BSX36	24p	ZTX520	24p	PW06 (16001) 39p	TA7219	1.99	
1/4W E24 2p	1/4W E24 2p	7512	74LS182	4093	19p	79p	40689	100p	BC478	32p	BSX37	24p	ZTX521	24p	PW06 (16001) 39p	TA7220	1.99	
1/4W E24 2p	1/4W E24 2p	7513	74LS183	4094	19p	79p	40690	100p	BC479	32p	BSX38	24p	ZTX522	24p	PW06 (16001) 39p	TA7221	1.99	
1/4W E24 2p	1/4W E24 2p	7514	74LS184	4095	19p	79p	40691	100p	BC480	32p	BSX39	24p	ZTX523	24p	PW06 (16001) 39p	TA7222	1.99	
1/4W E24 2p	1/4W E24 2p	7515	74LS185	4096	19p	79p	40692	100p	BC481	32p	BSX40	24p	ZTX524	24p	PW06 (16001) 39p	TA7223	1.99	
1/4W E24 2p	1/4W E24 2p	7516	74LS186	4097	19p	79p	40693	100p	BC482	32p	BSX41	24p	ZTX525	24p	PW06 (16001) 39p	TA7224	1.99	
1/4W E24 2p	1/4W E24 2p	7517	74LS187	4098	19p	79p	40694	100p	BC483	32p	BSX42	24p	ZTX526	24p	PW06 (16001) 39p	TA7225	1.99	
1/4W E24 2p	1/4W E24 2p	7518	74LS188	4099	19p	79p	40695	100p	BC484	32p	BSX43	24p	ZTX527	24p	PW06 (16001) 39p	TA7226	1.99	
1/4W E24 2p	1/4W E24 2p	7519	74LS189	4100	19p	79p	40696	100p	BC485	32p	BSX44	24p	ZTX528	24p	PW06 (16001) 39p	TA7227	1.99	
1/4W E24 2p	1/4W E24 2p	7520	74LS190	4101	19p	79p	40697	100p	BC486	32p	BSX45	24p	ZTX529	24p	PW06 (16001) 39p	TA7228	1.99	
1/4W E24 2p	1/4W E24 2p	7521	74LS191	4102	19p	79p	40698	100p	BC487	32p	BSX46	24p	ZTX530	24p	PW06 (16001) 39p	TA7229	1.99	
1/4W E24 2p	1/4W E24 2p	7522	74LS192	4103	19p	79p	40699	100p	BC488	32p	BSX47	24p	ZTX531	24p	PW06 (16001) 39p	TA7230	1.99	
1/4W E24 2p	1/4W E24 2p	7523	74LS193	4104	19p	79p	40700	100p	BC489	32p	BSX48	24p	ZTX532	24p	PW06 (16001) 39p	TA7231	1.99	
1/4W E24 2p	1/4W E24 2p	7524	74LS194	4105	19p	79p	40701	100p	BC490	32p	BSX49	24p	ZTX533	24p	PW06 (16001) 39p	TA7232	1.99	
1/4W E24 2p	1/4W E24 2p	7525	74LS195	4106	19p	79p	40702	100p	BC491	32p	BSX50	24p	ZTX534	24p	PW06 (16001) 39p	TA7233	1.99	
1/4W E24 2p	1/4W E24 2p	7526	74LS196	4107	19p	79p	40703	100p	BC492	32p	BSX51	24p	ZTX535	24p	PW06 (16001) 39p	TA7234	1.99	
1/4W E24 2p	1/4W E24 2p	7527	74LS197	4108	19p	79p	40704	100p	BC493	32p	BSX52	24p	ZTX536	24p	PW06 (16001) 39p	TA7235	1.99	
1/4W E24 2p	1/4W E24 2p	7528	74LS198	4109	19p	79p	40705	100p	BC494	32p	BSX53	24p	ZTX537	24p	PW06 (16001) 39p	TA7236	1.99	
1/4W E24 2p	1/4W E24 2p	7529	74LS199	4110	19p	79p	40706	100p	BC495	32p	BSX54	24p	ZTX538	24p	PW06 (16001) 39p	TA7237	1.99	
1/4W E24 2p	1/4W E24 2p	7530	74LS200	4111	19p	79p	40707	100p	BC496	32p	BSX55	24p	ZTX539	24p	PW06 (16001) 39p	TA7238	1.99	
1/4W E24 2p	1/4W E24 2p	7531	74LS201	4112	19p	79p	40708	100p	BC497	32p	BSX56	24p	ZTX540	24p	PW06 (16001) 39p	TA7239	1.99	
1/4W E24 2p	1/4W E24 2p	7532	74LS202	4113	19p	79p	40709	100p	BC498	32p	BSX57	24p	ZTX541	24p	PW06 (16001) 39p	TA7240	1.99	
1/4W E24 2p	1/4W E24 2p	7533	74LS203	4114	19p	79p	40710	100p	BC499	32p	BSX58	24p	ZTX542	24p	PW06 (16001) 39p	TA7241	1.99	
1/4W E24 2p	1/4W E24 2p	7534	74LS204	4115	19p	79p	40711	100p	BC500	32p	BSX59	24p	ZTX543	24p	PW06 (16001) 39p	TA7242	1.99	
1/4W E24 2p	1/4W E24 2p	7535	74LS205	4116	19p	79p	40712	100p	BC501	32p	BSX60	24p	ZTX544	24p	PW06 (16001) 39p	TA7243	1.99	
1/4W E24 2p	1/4W E24 2p	7536	74LS206	4117	19p	79p	40713	100p	BC502	32p	BSX61	24p	ZTX545	24p	PW06 (16001) 39p	TA7244	1.99	
1/4W E24 2p	1/4W E24 2p	7537	74LS207	4118	19p	79p	40714	100p	BC503	32p	BSX62	24p	ZTX546	24p	PW06 (16001) 39p	TA7245	1.99	
1/4W E24 2p	1/4W E24 2p	7538	74LS208	4119	19p	79p	40715	100p	BC504	32p	BSX63	24p	ZTX547	24p	PW06 (16001) 39p	TA7246	1.99	
1/4W E24 2p	1/4W E24 2p	7539	74LS209	4120	19p	79p	40716	100p	BC505	32p	BSX64	24p	ZTX548	24p	PW06 (16001) 39p	TA7247	1.99	
1/4W E24 2p	1/4W E24 2p	7540	74LS210	4121	19p	79p	40717	100p	BC506	32p	BSX65	24p	ZTX549	24p	PW06 (16001) 39p	TA7248	1.99	
1/4W E24 2p	1/4W E24 2p	7541	74LS211	4122	19p	79p	40718	100p	BC507	32p	BSX66	24p	ZTX550	24p	PW06 (16001) 39p	TA7249	1.99	
1/4W E24 2p	1/4W E24 2p	7542	74LS212	4123	19p	79p	40719	100p	BC508	32p	BSX67	24p	ZTX551	24p	PW06 (16001) 39p	TA7250	1.99	
1/4W E24 2p	1/4W E24 2p	7543	74LS213	4124	19p	79p	40720	100p	BC509	32p	BSX68	24p	ZTX552	24p	PW06 (16001) 39p	TA7251	1.99	
1/4W E24 2p	1/4W E24 2p	7544	74LS214	4125	19p	79p	40721	100p	BC510	32p	BSX69	24p	ZTX553	24p	PW06 (16001) 39p	TA7252	1	

MAPLIN Massive range of components for your hobby....insist on Maplin quality!

MAPLIN'S TOP TWENTY KITS

THIS LAST MONTH	DESCRIPTION OF KIT	ORDER CODE	KIT PRICE	DETAILS IN PROJECT BOOK
1. (1)	75W Mosfet Amp Module	LW51F	£12.95	Best of E&MM
2. (2)	Modem	LW99H	£44.95	5 XA05F
<i>Case also available: YK62S Price £9.95.</i>				
3. (4)	Car Burglar Alarm	LW78K	£6.95	4 XA04E
4. (5)	Partylite	LW93B	£9.45	Best of E&MM
5. (3)	ZX81 I/O Port	LW76H	£9.25	4 XA04E
6. (19)	Spectrum Keyboard	LK29G	£28.50	9 XA09K
<i>Also required: LK30H £6.50; Case: XG35Q £4.95 — Total £39.95.</i>				
<i>Also available complete ready-built: XG36P £44.95.</i>				
7. (9)	Syntom Drum Synthesiser	LW86T	£11.95	Best of E&MM
8. (8)	VIC20/64 RS232 Interface	LK11M	£9.45	7 XA07H
9. (7)	8W Amp Module	LW36P	£4.45	Catalogue
10. (10)	Harmony Generator	LW91Y	£17.95	Best of E&MM
11. (15)	Logic Probe	LK13P	£9.95	8 XA08J
12. (6)	Keyboard for ZX81	LW72P	£23.95	3 XA03D
<i>Case also available: XG17T £4.95. Complete ready-built: XG22Y £32.50.</i>				
13. (14)	Ultrasonic Intruder Detector	LW83E	£10.95	4 XA04E
14. (11)	Spectrum RS232 Interface	LK21X	£17.95	8 XA08J
15. (17)	Hexadrum	LW85G	£19.95	Best of E&MM
16. (-)	Noise Gate	LK43W	£9.95	Best of E&MM
17. (-)	Guitar Tuner	LW90X	£10.75	Best of E&MM
18. (-)	Freq. Meter Adaptor	LK20W	£8.99	9 XA09K
19. (16)	Car Battery Monitor	LK42V	£6.25	Best of E&MM
20. (20)	ZX81 Speech Synthesiser	LK01B	£16.95	6 XA06G

Over 80 other kits also available. All kits supplied with instructions. The descriptions above are necessarily short. Please ensure you know exactly what the kit is and what it comprises before ordering, by checking the appropriate Project Book mentioned in the list above.



MAPLIN'S FASCINATING PROJECTS BOOKS

Full details in our Project Books
Price 70p each.

In Book 1 (XA01B) 120W rms Mosfet Combo-Amplifier • Universal Timer with 18 program times and 4 outputs • Temperature Gauge • 6 Vero Projects.

In Book 2 (XA02C) Home Security System • Train Controller for 14 trains on one circuit • Stopwatch with multiple modes • Miles-per-Gallon Meter.

In Book 3 (XA03D) ZX81 Keyboard with electronics • Stereo 25W Mosfet Amplifier • Doppler Radar Intruder Detector • Remote Control for Train Controller.

In Book 4 (XA04E) Telephone Exchange for 16 extensions • Frequency Counter 10Hz to 600MHz • Ultrasonic Intruder Detector • I/O Port for ZX81 • Car Burglar Alarm • Remote Control for 25W Stereo Amp.



In Book 5 (XA05F) 300 Baud Duplex Modem to European Standard • 100W 240VAC Inverter • Sounds Generator for ZX81 • Central Heating Controller • Panic Button for Home Security System • Model Train Projects • Timer for External Alarm.

In Book 6 (XA06G) Speech Synthesiser for ZX81 & VIC20 • Module to Bridge two of our Mosfet Amps to make a 350W Amp • ZX81 Sound on your TV • Scratch Filter • Damp Meter • Four Simple Projects.

In Book 7 (XA07H) Modem (RS232) Interface for ZX81/VIC20/Commodore 64 • Digital Enlarger Timer/Controller • DXers Audio Processor • Sweep Oscillator • CMOS Crystal Calibrator.

In Book 8 (XA08J) Modem (RS232) Interface for Dragon 32 & Spectrum • Synchime • I/O Ports for Dragon 32 • Electronic Lock • Minilab Power Supply • Logic Probe • Doorbell for the Deaf.

In Book 9 (XA09K) Keyboard with Electronics for ZX Spectrum • Infra-

Red Intruder Detector • Multimeter to Frequency Meter Converter • FM Radio needs no alignment • Hi-Res Graphics for ZX81 • Speech Synthesiser for Oric 1 • VIC20 Extendiboard • ZX81 ExtendiRAM • Dynamic Noise Limiter for Personal Cassette Players • TTL Levels to RS232 Converter • Logic Pulser • Pseudo-Stereo AM Radio • Ni-Cad Charger Timer •

Adder-Subtractor • Syndrum's Interface • Microphone Pre-Amp Limiter. **In Book 10 (XA10L)** Cassette Easyload for ZX Spectrum • 80m Amateur Receiver • Auto Waa-Waa Effects Unit • Oric 1 Modem Interface • 2.8kW Mains Power Controller • Extendiport for Dragon 32 • 12V Fluorescent Tube Driver • 32-Line Extension for Digi-Tel.

1984 CATALOGUE

A massive 480 big pages of description, pictures and data and now with prices on the page. The new Maplin catalogue is the one book no constructor should be without. Now includes new Heathkit section. On sale in all branches of W.H. Smith. Price £1.35 — It's incredible value for money. Or send £1.65 (including p & p) to our mail-order address.

GREAT PROJECTS FROM E&MM

Our book "Best of E&MM Projects Vol. 1" brings together 21 fascinating and novel projects from E&MM's first Year.

Projects include Harmony Generator, Guitar Tuner, Hexadrum, Syntom, Auto Swell, Partylite, Car Aerial Booster, MOS-FET Amp and other musical, hi-fi and car projects. Order As XH61R. Price £1.

Post this coupon now for your copy of the 1984 catalogue. Price £1.35 + 30p post and packaging. If you live outside the U.K. send £2.20 or 11 International Reply Coupons. I enclose £1.65

Name

Address



PE684

MAPLIN ELECTRONIC SUPPLIES LTD

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 • Shops at: 159-161 King Street, Hammersmith, London W6. Tel: 01-748-0926. • 8 Oxford Road, Manchester. Tel: 061-236-0281. • Lynton Square, Perry Barr, Birmingham. Tel: 021-356-7292. • 282-284 London Road, Westcliff-on-Sea, Essex. Tel: 0702 554000. • 46-48 Bevois Valley Road, Southampton. Tel: 0703 25831. All shops closed all day Monday. All prices include VAT and carriage. Please add 50p handling charge to orders under £5 total value (except catalogue).

Despatch by return of post where goods available

809

PE LOGIC DESIGN CARD

No.4

PRESENTED FREE WITH PRACTICAL ELECTRONICS JUNE '84

No.4


OSCILLATOR CIRCUITS

(a) Simple Oscillator using a Schmitt Inverter

This circuit uses a single inverting gate and requires only one capacitor and one resistor. The output duty cycle is approximately 1:3. It is good practice to follow the stage with an additional inverting gate to act as a buffer. Where a square wave output is required the duty cycle can be improved by placing a 1kΩ resistor in parallel with the capacitor. A precise 1:1 duty cycle can be obtained by applying the oscillator output to the clock input of a J-K bistable. This technique can also be used to provide complementary outputs where necessary. Note that the bistable output frequency will be half that of the oscillator. The table gives capacitor values for a range of approximate output frequencies:-

frequency, as shown in the circuit below. Note that this stage should normally be followed by a buffer which may be either inverting or non-inverting, as required.

Crystal Frequency Range	C1(F)
1-3 MHz	150p
3-6 MHz	68p
6-12MHz	47p

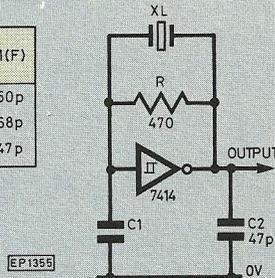


EP1355

SWITCH DE-BOUNCING

De-bouncing switch inputs is usually essential with all types of switch. In general, immunity to transient spikes is enhanced by the use of active-low inputs. The following circuit can be used to remove switch bounce. Note that the value chosen for R2 must take into account the low-state sink current required by IC1. This will normally be 1.6mA and 0.4mA maximum for standard and LS TTL gates, respectively. R2 should not normally exceed approximately 470 ohms. Note also that, on power-up, this circuit generates a logic 1 level for approximately 1ms before the output reverts to a logic 0 in the inactive state.


f (Hz)	C (F)
350k	4n7
40k	47n
4k	470n
400	4μ7
40	47μ
4	470μ

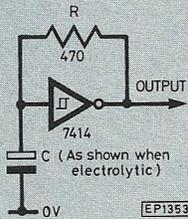

EP1353

(b) Oscillator using an I.C. Timer

A 555 timer connected in astable mode can be used to provide a clock, as shown in the circuit below. For a near unity duty cycle, R2 should be very much larger than R1. To vary the frequency, R2 may be replaced by a variable resistor.

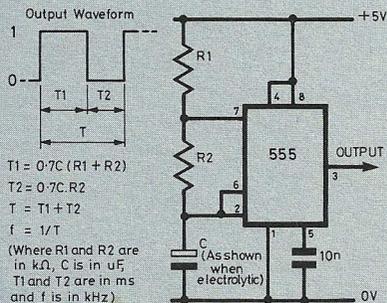


EP1354

(c) Crystal Oscillator

A quartz crystal should be used as the frequency determining element in an oscillator which is to have a precise output

DISCRETE BISTABLES

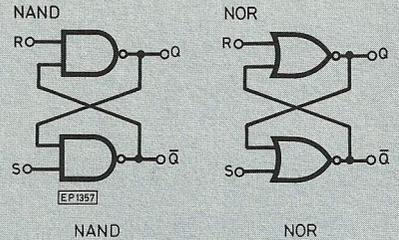
Occasionally it is expedient to construct simple R-S bistable elements using spare logic gates. This can be done using either NAND or NOR, as shown below. Note, however, that care should



be taken to avoid the input condition when both S and R are taken to logic 1 at the same time since, in this condition, the output state is indeterminate. Either of these arrangements can be used to form the R-S bistable used in the switch de-bounce arrangement described previously.


DECOUPLING CAPACITORS

When the output of a TTL gate changes from 0 to 1, or vice-versa, a surge of current is drawn from the supply. This 'spike' must be prevented from spreading to other parts of the circuit via the supply rails. If not, it can affect the operation of other i.c.s in the circuit. The solution is to add small-value (decoupling) capacitors along the supply rails near to the i.c. supply pins. These supply the energy for the spikes, thus preventing them from spreading. Decoupling capacitors should be high frequency types (e.g. 10V disc ceramic), connected according to the rules below.

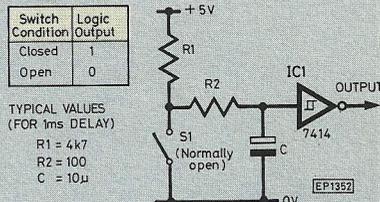


EP1352

An alternative de-bouncing technique uses a bistable element as shown below.

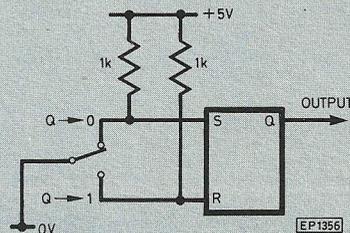


EP1355

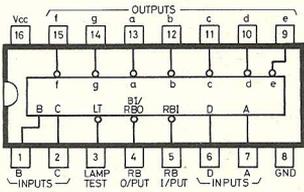
1. Use h.f. capacitors of 4.7 to 100n, typically 10n.
2. Connect close to the i.c. supply pins, using short leads.
3. Use one capacitor for every 4-5 i.c.s.
4. Add a capacitor at any i.c. more than 10cms from decoupling.
5. Distribute the decoupling around the circuit board.
6. Add a 10μ 10V tantalum capacitor for every 10-20 i.c.s.
7. If in doubt, add more decoupling capacitors.




74247 BCD
7-segment decoder

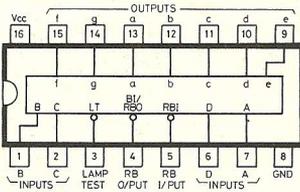


74248 BCD
7-segment decoder

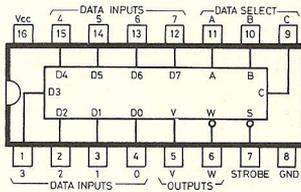


74251 8-input
selector 3-state

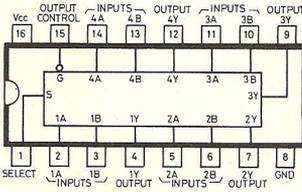


74257A Quad
2-input multiplexer 3-state

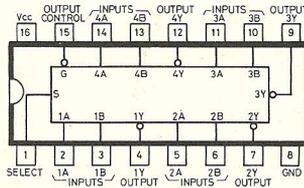


74258A Quad
2-input multiplexer 3-state

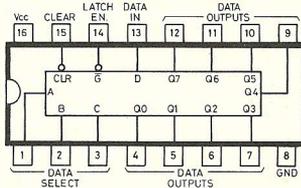


74259
8-bit addressable latch

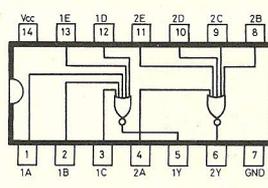


74260 Dual
5-input NOR gate

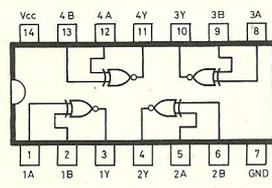


74266 Quad
2-input Ex-OR oc

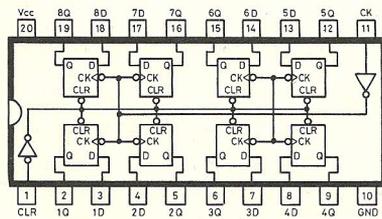


74273 Octal
D-type

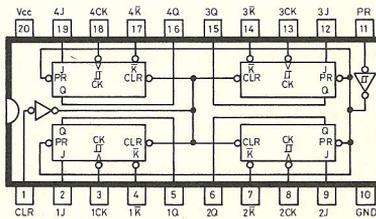


74276 Quad
J-K

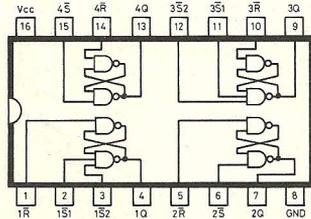


74279 Quad
S-R latch

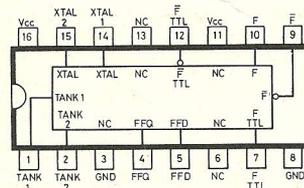


74320
Crystal-controlled osc LS

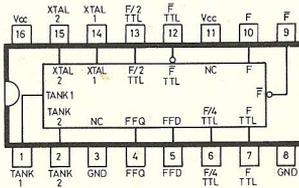


74321
Crystal-controlled osc LS

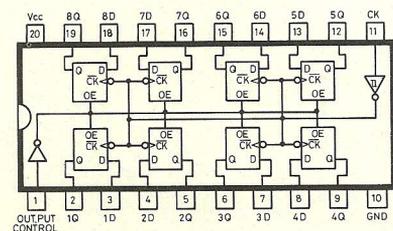


74374 Octal D-type LS

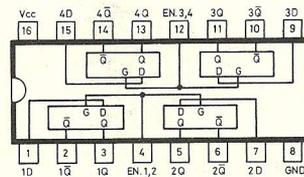


74375 Dual
2-bit bistable with enable LS

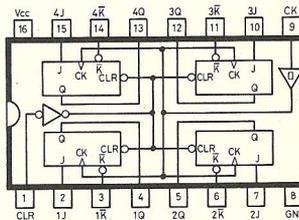


74376 Quad
J-K

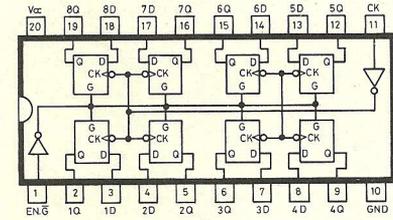


74377 Octal
D-type with enable LS

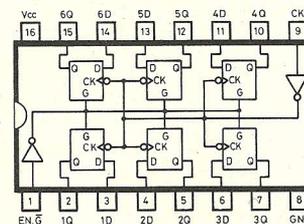


74378 Hex D-type LS

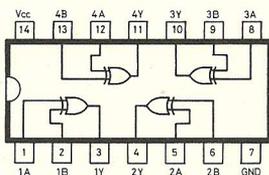

74386 Quad
2-input Ex-OR

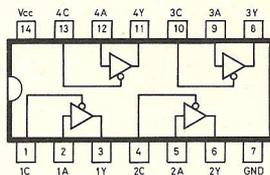

74425 Quad 3-state
outputs active low

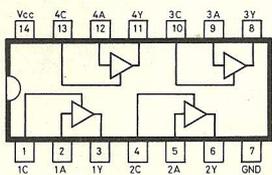

74426 Quad 3-state
outputs active high