

SHARED AERIALS

# PRACTICAL TELEVISION

AND TELEVISION TIMES

A NEWNES PUBLICATION

Vol. 6 No. 61

JUNE, 1955

1/4

EDITOR  
F. J. CAMM




## A TELEVISION SIGNAL GENERATOR

FEATURED IN THIS ISSUE


Experimental Video  
and Sync Amplifier  
T.R.F. Receivers  
Making a Test Meter

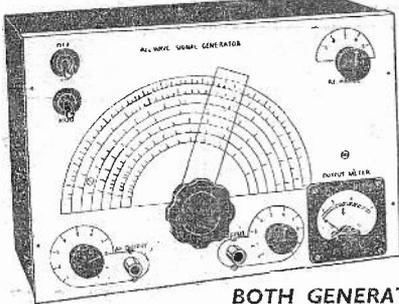Frame Flyback Suppression  
Servicing The G.E.C.  
BT 7092 and 7094  
The Miller Timebase



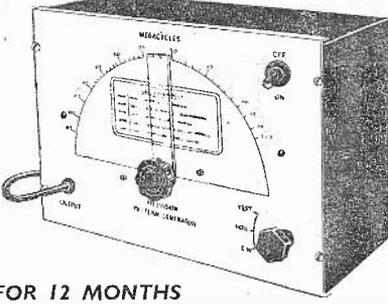**USED MULLARD TUBES GUARANTEED 3 MONTHS**

with heater cathode short. M.W. 31/74 12in. bent gun, £3.17.6. P. & P. 7/6 extra. M.W. 31/16 12in. bent gun, £3.17.6. P. & P. 7/6 extra. M.W. 22/16 9in. bent gun, £1.17.6. P. & P. 7/6 extra. Any of the above complete with Line E.H.T. trans. 9 KV. Ferrocort core. Line and width control scan coils and frame O/P trans. 35/- extra.



**BOTH GENERATORS GUARANTEED FOR 12 MONTHS**


**COMPLETELY BUILT SIGNAL GENERATOR**

Coverage 120 Kc/s-320 Kc/s, 300 Kc/s-900 Kc/s, 900 Kc/s-2.75 Mc/s, 2.75 Mc/s-9.5 Mc/s, 8.5 Mc/s-25 Mc/s, 17 Mc/s-50 Mc/s, 25.5 Mc/s-75 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated, R.F. output continuously variable 100 milli volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle finished case and white panel. Accuracy plus or minus 2%. £4/19/6, or 34/- deposit and 3 monthly payments 25/- P. & P. 4/- extra.

**PATTERN GENERATOR**

40-70 Mc/s direct calibration, checks frame and line time base, frequency and linearity, vision channel alignment, sound channel and sound rejection circuits and vision channel band width. Silver plated coils, black crackle finished case 10 x 6 1/2 x 4 1/2 in. and white front panel. A.C. mains 200/250 volts. This instrument will align any T.V. receiver, accuracy plus or minus 1%. Cash price £3.19.6 or 29/- deposit and 3 monthly payments of £1. P. & P. 4/- extra.

**PERMEABILITY TUNED T.V. UNIT**

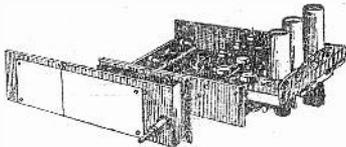

Input 300 ohm balanced line, coverage 54 Mc/s-39 Mc/s and 174 Mc/s-217 Mc/s. Vision I.F. -45 Mc/s, sound 40.5 Mc/s. Uses 6AK5 RF valve, 6AK5 as mixer, and 6C4 oscillator. Provision for auto-gain control. Dimensions 9in. wide, 6 1/2 in. deep, 4 1/2 in. high, 5in. blank-scale. Width including scale covers 14 1/2 in. Four stages permeability tuned. Complete with 3 valves. P. & P. 3/- £2.19.6.

Used Mazda C.R.M. 123 Cathode heater short aluminised. Complete with rubber mask. Elac P.M. focus unit, scan coils, low line, low frame and frame O/P trans. £5.10.0. P. & P. 7/6.

USED 9in. TUBE 22/14C with ion burn, 17/3. Post paid.

USED Mullard 12in. with ion burn, 50/-. P. & P. 7/6.

T.V. Converter for the new commercial stations complete with 2 valves. Frequency: can be set to any channel within the 189-196 Mc/s band. I.F.: will work into any existing T.V. receiver designed to work between 42-63 Mc/s. Sensitivity 10 mV with any normal T.V. set. Input: arranged for 300 ohm feeder, 80 ohm feeder can be used with slight reduction in R.F. gain. Circuit EF80 as local oscillator. ECC31 as R.F. amplifier and mixer. The gain of the first stage, grounded grid R.F. amplifier 10 db. Required power supply of 200 v. D.C. at 25 mA., 6.3 v. A.C. at 0.6 amp. Input filter ensuring complete freedom from unwanted signals. 2 simple adjustments only. £2.10.0 P. & P. 2/6.

Line and E.H.T. Transformer. 9KV. Ferrocort core. EY51 heater winding. Complete with scan coils and frame output transformer and line and width control. £2.5.0. P. & P. 3/-.

As above but complete with line and frame blocking transformers, 5 henry 250 mA. choke, 100 mfd. and 150 mfd. 350 wkg. 380 mA. A.C. ripple. £3.19.6. P. & P. 3/-.

Standard wave-change switches, 7-pole 3-way, 1/9; 5-pole 3-way, 1/9; 3-pole 3-way, 1/9; 4-pole 3-way, 3/6; Miniature type, long spindle 3-pole 4-way, 4-pole 3-way and 4-pole 2-way, 2/6 each. 2-pole 11-way twin wafer, 5/-; 1-pole 12-way single wafer, 5/-. P. & P. 3d.

T.V. Filter in lightly tinted perspex, size 1 1/2 x 1 1/2 x 3/16 in., 4/6.

USED metal rectifier, 250 v. 150 mA., 6/6.

R. and A.T.V. energised 6in. Speaker with O/P Trans., field coil 175 ohms. Requires minimum 150 mA. to energise maximum current 250 mA. 9/6. P. & P. 2/6.

R. and A.M.E. 6in. with O/P Trans., 440 ohms field, 10/6 plus 2/6 P. & P.

Combined 12in. Mask and Escutcheon in lightly tinted perspex. New aspect, edged in brown. Fits on front of cabinet. 12/6. As above for 15in. tube, 17/6.

Frame Oscillator Blocking Trans., 4/6 each.

Smoothing Choke, 250 mA., 5 henry, 9/6; 250 mA., 10 henry, 10/6;

Wide Angle P.M. Focus Unit, Vernier adj., state tube, 25/-.

Ion Traps for Mullard or English Electric tubes, 5/-. Post paid. T.V. Coils: moulded former, iron cored, wound for rewinding purposes only. All-can 1 1/2 in. x 1 in., 1/- each; 2 iron-cores All-can, 2 1/2 in. x 1 in., 1/6 each.

Dubitier .001 10KV. working, 3/6.

**MAINS TRANSFORMERS**

Primary, 200-250 v. P. & P. 2/-.

300-0-300, 100 mA., 6 v. 3 amp., 5 v. 2 amp., 22/6.

Drop thro' 350-0-350 v. 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., 14/6.

Drop thro' 250-0-250 v. 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6.

280-0-280, drop through, 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6.

250-0-250 80 mA., 6 v. 4 amp., 14/-.

Drop thro' 270-0-270 60 mA., 6 v. 3 amp., 4 v. 1.5 amp., 13/6.

Drop thro' 270-0-270 60 mA., 6 v. 3 amp., 11/6.

250 v. 350 mA., 6.3 v. 4 a., twice 2 v. 2 a., 16/8.

Shunt-shrouded drop-through 380-0-380 120 mA., 6.3 v. 3 amp., 5 v. 2 amp., 25/-.

Auto-trans. Input 200/250, H.T. 500 v. 250 mA., 6 v. 4 a., twice 2 v. 2 a., 19/6.

250-0-250, 60 mA., 6.3 v. 1.5 a., 0.5-6.3 v. 1.5 a., 10/6.

Auto Trans. Input 200-250. H.T. 350 v. 350 mA. Separate L.T. 6.3 v. 7 a., 6.3 v. 1 1/2 amp., 5 v. 3 amp., 25/- P. & P. 3/-.

Heater Transformer, Pri 230/250v. 6v-11 amp., 6/-; 2v. 21amp, 5/-.

Pri. 200/250. Secondary 9 v. 3.5 amp., 6.3 v. 3 amp., 12/6.

Pri. 230 v. Sec. 500-0-500 and 500-0-500 250 mA., both windings. 4 v. 3 amp., 4 v. 3 amp., 39/3. P. & P. 5/-.

Full-shrouded screened primary 13 v. 1 amp., 7/6.

Input 210, 220, 230 and 240. Sec. 000-0-500, 275 mA., and 200 v. at 20 amp. complete with separate heater transformer. Input 210, 220, 230, 240. Sec. 6.3 v. 2 amp. three times, 0, 4, 6.3 v. at 3 amp. and 5 v. 3 amp., 45/- P. & P. 5/-.

Input 210, 220, 230, 240. Sec. 350-0-350 100 mA., with separate heater transformer. Pri. 210, 220, 230, 240. Sec. 6.3 v. 2 amp., 6.3 v. 3 amp., 4 v. 6 amp., and 5 v. 2 amp., 30/- P. & P. 5/-.

Mains Transformers, chassis, mounting, feet and voltage panel. Primaries 200/250.

350-0-350 75 mA., 6.3 v. 3 a. tap, 4 v. 6.3 v. 1 a., 13/6.

500-0-500 125 mA., 4 v. C.T. 4 a., 4 v. C.T. 4 a., 4 v. C.T. 2.5 a., 27/6.

500-0-500 250 mA., 4 v. C.T. 5 a., 4 v. C.T. 5 a., 4 v. C.T. 4 a., 39/6.

Valve Holders, moulded octal Mazda and loctal, 7d. each	8 mfd., 500v. wkg., wire ends 2/6
Paxolin, octal Mazda and loctal, 4d. each. Moulded BTG, B8A and B9A, 7d. each	8 mfd., 350 v. wkg., tag ends 1/6
BTG moulded with screening can, 1/6 each.	50 mfd., 25 v. wkg., wire ends 1/9
32 mfd., 350 wkg. .... 2/-	100 mfd., 350 wkg. .... 4/-
18 x 24, 350 wkg. .... 4/3	100 mfd., 350 wkg. .... 4/-
4 mfd., 200 wkg. .... 1/3	100 mfd., 450 v. wkg., 260 mA., A.C. ripple ... 3/11
40 mfd., 400 wkg. .... 3/6	150 mfd., 350 v. wkg., 260 mA., A.C. ripple ... 4/6
16 x 8 mfd., 500 wkg. .... 4/6	100 + 200 mfd., 350 wkg. .... 9/6
16 x 16 mfd., 500 wkg. .... 5/9	16 + 16 mfd., 350 wkg. .... 8/3
16 x 16 mfd., 450 wkg. .... 5/9	50 mfd., 180 wkg. .... 1/9
32 x 32 mfd., 350 wkg. .... 6/6	65 mfd., 220 wkg. .... 1/6
32 x 32 mfd., 350 wkg., and 25 mfd., 25 wkg. .... 6/6	8 mfd., 150 wkg. .... 1/6
250 mfd., 25 wkg. .... 11d.	60 + 100 mfd., 280 wkg. .... 7/6
16 mfd., 500 wkg., wire ends 3/3	50 mfd., 12 wkg. .... 1/4
	32 + 32 mfd. min. 275 wkg. .... 4/9
	50 mfd., 50 wkg. .... 1/9
	Miniature wire ends moulded, 100 pf., 500 pf., and .001, ea. .... 7d.

Where cost and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries S.A.E. Lists 5d. each.

**R. AND T.V. COMPONENTS (ACTON) LTD. 23 HIGH STREET, ACTON, W.3 Telephone: ACOrn 5901 (Opposite Granada Cinema)**

# Bigger and Better Pictures

# WITH BRIMAR

Shortly available—The BRIMAR  
21-in TELETUBE C21HM

This Rectangular Wide Deflection Teletube with Aluminized Screen and external Conductive Coating, operates at 16 kV. It is fitted with an improved tetrode gun assembly giving excellent overall focus and minimum astigmatism.

**Brimar** have developed powerful valves suitable for use with existing or future types with larger screen areas

**6CD6G/50CD6G (AC/DC)**—Line Output Valves with a peak current of  $\frac{1}{2}$  amp. and plenty of power in hand for wide angle scanning.

**6U4GT**—Efficiency Diode—The high working peak heater to cathode potential renders a separate highly insulated heater supply unnecessary.

**R19**—E.H.T. Rectifier—A replacement for the American IX2A but with higher Ratings.

**RM5**—H.T. Rectifier—A worthy successor to the RM4, with a rating of 300 mA. This rectifier has a reserve of power and should be used initially in equipment so that additional valves may be added if required without redesigning the power supply stages.

**Valves for the BAND III CONVERTOR**  
(for 6 volt operation)

\***ECC84**—Consists of two separate high slope triode units designed for use as a V.H.F. cascode amplifier.

\***ECF82**—is a triode pentode frequency changer featuring a high slope triode and a high slope pentode with a high input impedance.

**6BW7**—The 6BW7 is recommended in areas where extra sensitivity is required. It has a slope of 9.3 mA/V with anode and screen voltages of 180v.

\* The PCC84 and PCF82 are 3 amp equivalents of these types and are suitable for equipments where series connected valves are used.

Standard Telephones and Cables Limited **FOOTSCRAY, SIDCUP, KENT.** Footscray 3333

**LASKY'S RADIO**

**SPECIAL OFFER!**  
**MULTI-TEST METERS**

1,000 ohms per volt. Basic movement 3in. 400 micro-amp. AC/DC 0-5,000v. 0-1 amp. 11 switched ranges: 100,000 ohms and 1 meg. also decible range. In polished wood carrying case (6 x 6 1/2 x 4in. closed), with leather handle and space for test leads. Made in U.S.A. New and unused but cases slightly soiled.

**LASKY'S PRICE 95/-**  
Post & Insur., 3/6.  
**TEST LEADS, 3/6 extra.**


**CRYSTAL DIODES**  
Glass type, wire ends. 1/6 each. Higher Grades. 12 Assorted for 30/-. Post free.

**THE HANDSOME "ROTHESAY" CABINET**

Absolutely rigid construction with 1in. finest laminated woods, veneered in walnut, polished light, medium or dark shade. Fitted gold anodised speaker grille. The C.R.T. aperture frame is detachable, supplied to order to suit any size tube.

Outside dim. 34in. high, 21in. wide, 21in. deep. Inside 18in. wide, 19in. deep. Size of top 22in. x 21in.

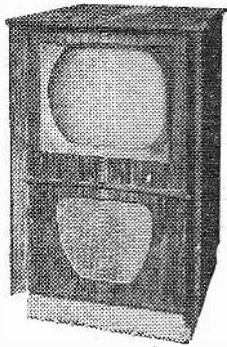**Lasky's Price £9.19.6**  
Carriage 15/- extra. With full length doors. £14.9.6.



Available on H.P. terms.

**CONVERT YOUR "VIEW MASTER" TO 14, 16 or 18in. SCREEN**

Wide Angle Conversion Kit using only W/B components as specified, viz., line trans., filament trans., frame trans., scanning coils, width and linearity controls, focus magnet, ion trap, 1-K3/100, 1-K3/40 metal rectifiers, 1-6CD6, 1-6U4GT valves, 3 resistors, 9 condensers. Complete parcel including valves and data book.

**£7.19.6** Post & Pkg. 2/6 extra.

"View Master" Conversion Booklet, 3/6 post free.

**SPECIAL PURCHASE OF 16in. C.T. TUBES.** Famous make offered at nearly Half-Price. Metal cone, 3 amp. heater, e.h.t. required 10-14 Kv. Limited quantity only.  
**LASKY'S PRICE £12.19.6**  
Carr. & Ins. 22/6 ex.

**ALL MAIL ORDERS TO HARROW ROAD**

Open all day SAT. Half day Thurs.

**MAKERS' SURPLUS COMPONENT BARGAINS**

**WIDE ANGLE 38 mm.**

Line E.H.T. trans., ferro-cube core, 9-16 kV ...	25/-
Scanning Coils, low imp. line and frame ...	25/-
Frame Output Transformer	10/6
Scanning Coils low imp. line and frame ...	17/6
Frame or line blocking osc. transformer ...	4/6
Focus Magnets Ferro-dure ...	25/-
P.M. Focus Magnets, Iron Cored ...	19/6
Duomag Focallisers ...	29/6
300 m/a. Smoothing chokes ...	15/-
Electromagnetic focus coil, with combined scan coils ...	25/-


**STANDARD 35 mm.**

Line Output Transformers. No E.H.T. ...	12/6
Line Output Transformers 6-9 kV. E.H.T. and 6.3v. winding. Ferro-cube ...	19/6
Scanning coils. Low imp. line and frame ...	12/6
Ditto by Igranic ...	14/6
Frame or line blocking oscillator transformer ...	4/6
Frame output transformer ...	7/6
Focus Magnets: Without Vernier ...	12/6
With Vernier ...	17/6
Focus Coils. Electro-magnetic ...	12/6
200 m/a. Smoothing chokes ...	10/6

**SALE OF REMAINDER OF OUR 12in. "VIEW MASTER" STOCK. MOSTLY HALF PRICE OR LESS. Write for list**

**LASKY'S (HARROW ROAD) LTD.,**  
370, HARROW ROAD, PADDINGTON, W.9.  
Telephone: CUNningham 1978-7214.  
42, TOTENHAM COURT ROAD, W.1.  
Telephone: MUSsum 2895.

# THE NEW **Osram** KT55 output valve

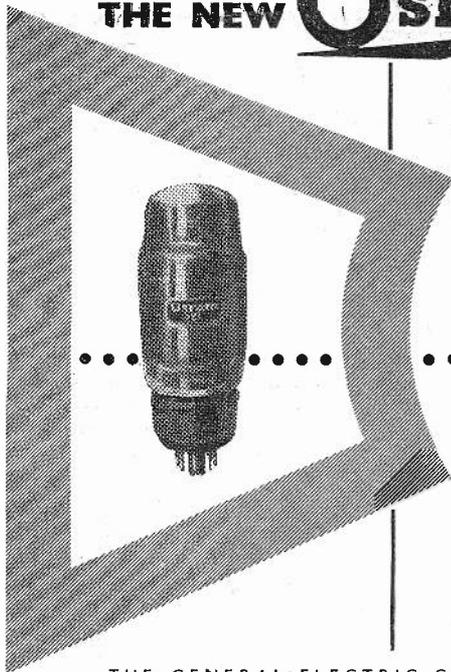

The new Osram KT55 beam tetrode has a heater rating of 0.3A, 52V. It is intended for use in a series heater chain for either DC or AC/DC mains amplifiers.

Outstanding characteristic is its high power output (25 watts per pair) with minimum distortion at comparatively low H.T. voltage (200V).

The Osram KT55 will form a popular companion-type to the well-known KT66. Two valves, type KT55, will supersede the need for four valves, type KT33C, in AC/DC amplifiers required to deliver up to 25 watts at 200 volts.

**KT55. List price: 25/- plus P. Tax 8/2**


### HEATER

I <sub>h</sub> .....	0.3	A
V <sub>h</sub> .....	52	V

### TYPICAL OPERATION

Tetrode connection. Push-pull.  
Data per pair unless otherwise stated.

	Quiescent	Max signal	
V <sub>a</sub> (b).....	225	215	V
V <sub>a</sub> .....	200	190	V
V <sub>g2</sub> .....	200	190	V
V <sub>in</sub> (g <sub>1</sub> -g <sub>1</sub> ) (pk).....		28.8	V
V <sub>g1</sub> (approx.).....	-20.5	-23.5	V
I <sub>a</sub> .....	220	225	mA

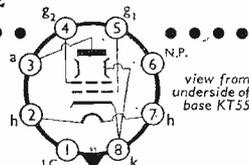

	Quiescent	Max signal	
I <sub>g2</sub> .....	15	45	mA
R <sub>k</sub> (per valve).....	175	175	Ω
RL (a-a).....	2	2	kΩ
P <sub>out</sub> .....		25	W
D.....		2	%
Z <sub>out</sub> .....		9	kΩ

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, W.C.2

## PREMIER RADIO COMPANY


OPEN TILL  
6 P.M. SATURDAYS

(Regd.) B. H. MORRIS & CO. (RADIO) LTD.

(Dept. P.T.) 207, EDGWARE ROAD, LONDON, W.2

Telephone:  
AMBASSADOR 4033  
PADDINGTON 3271

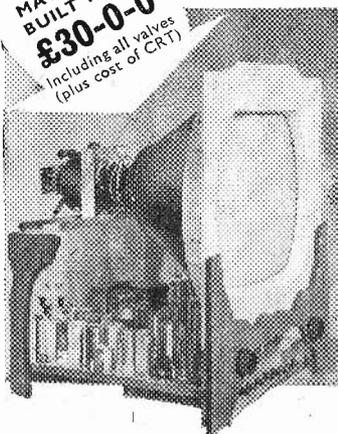MAY BE  
BUILT FOR  
**£30-0-0**  
Including all valves  
(plus cost of CRT)



**MULTI-CHANNEL TUNER  
AVAILABLE SHORTLY**  
WATCH FOR ANNOUNCEMENT

## The NEW PREMIER TELEVISOR

SUITABLE FOR USE WITH THE ENGLISH ELECTRIC CATHODE RAY TUBE T901 OR ANY POPULAR WIDE ANGLE TUBE

20 valves (plus tube) Superhet Receiver, tunable from 40-68 Mc/s without coil or core changing. Wide angle scanning Flyback EHT giving 14 kV. Duomag Focalsiser, permanent, magnet focussing with simple picture centring adjustments, suitable for any wide angle Tube, may also be used with a 12 in. Tube with very minor modifications.

**VISION CIRCUIT.** Common RF Amplifier, single valve frequency changer, two IF stages, Video Detector and Noise Limiter followed by special type of Video Output Valve. ALL COILS PRE-TUNED ASSURING ACCURATE ALIGNMENT AND EXCELLENT BANDWIDTH.

**SOUND CIRCUIT.** Coupling from anode of frequency changer, two IF stages Double Diode Triode detector and first LF Amplifier, Diode Noise Limiter and Beam type Output Valve, feeding a 10in. Speaker. ALL COILS PRE-TUNED.

**TIME BASES.** 2 valve sync. Separator, giving very firm lock and excellent interlace. **LINE TIME BASE.** Blocking Oscillator using a pentode driving a high efficiency output stage comprising Ferroxcube Cored Output Transformer with Booster Diode.

**FRAME TIME BASE.** Blocking Oscillator driving a Beam Output Valve coupled through a Transformer to the high efficiency FERROXCUBE Cored Scanning Coils.


**POWER PACK.** Double wound Mains Transformer supplying all L.T. and H.T. using two full-wave Rectifiers.

The Television may be constructed in 5 easy stages: (1) Vision, (2) Time Base, (3) Sound, (4) Power Pack, (5) Final Assembly. Each stage is fully covered in the Instruction Book, which includes layout, circuit diagrams and point-to-point wiring instructions. The Instruction Book also includes full details for converting existing Premier Magnetic Televisors for use with modern wide angle tubes. All components are individually priced. All preset controls can be adjusted from the front, making setting up very simple.


Instruction book 3/6, Post Free.

Send Stamp For Latest Catalogue

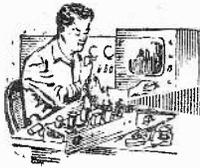Console Cabinets in figured walnut can be supplied for the above receiver at a cost of £13/10/-, plus 21/- pkg. & carr. H.P. Terms for cabinet on request.



# Practical Television

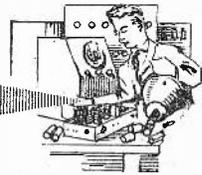

## & TELEVISION TIMES

Editor : F. J. CAMM

Editorial and Advertisement Offices : " Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. 'Phone : Temple Bar 4363. Telegrams : Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

Vol. 6 No. 61

EVERY MONTH

JUNE, 1955

## Televiews

**M**ANUFACTURERS of TV receivers and equipment are now well advanced in their plans to enable the viewing public to receive the I.T.A. programmes, which are due to commence in September. The receivers not already designed for these programmes will need an adaptor or to be adapted, and it is clear that a special aerial will also be required. We shall, therefore, review in a later issue the arrangements made by the various manufacturers for the adaptation of their receivers. We shall also describe how to make an I.T.A. adaptor, the design for which is now complete and awaits test.

At this stage it is impossible to say whether the I.T.A. programmes will appeal to the public to the extent anticipated. It is obvious that the price of programme time—nearly a thousand pounds a minute—will place the new service in the hands of large advertisers only. Such advertisers are unlikely to continue to spend such large sums of money merely to provide an alternative service at no cost to the State or to the viewer. A manufacturer must recover his costs, and it is problematical whether results in the form of sales will be sufficient to warrant such a large outlay. It is possible that advertisers will find that older forms of advertising are still the best means of bringing home the bacon.

The amount of "plugging" to be permitted in these programmes is to be severely limited and such as will be permitted must be on a dignified scale. No doubt the whole of the I.T.A. programme arrangements and regulations will be reviewed after the first year. It seems a pity, however, that cost will preclude many small firms from taking advantage of this new method of expanding their businesses. It might to some indeed seem unfair that large concerns should be virtually granted a monopoly merely because their purses are larger.

### TELEVISION TRADE TEST TRANSMISSIONS

**W**E are glad that the BBC has decided that the existing schedule of Trade Test transmissions are to continue until August 31, 1955. It

will be recalled that it was announced at the end of 1954 that the additional hour introduced on September 1st, 1954, into the morning transmissions on week days would be continued until April 30th. But in order to assist the radio industry and trade to test and adjust television receivers the date has been extended as stated above, subject of course to any interruption that might be necessary for technical reasons.

### "TELEVISION PRINCIPLES AND PRACTICE"—NEW EDITION

**T**HE second edition of *Television Principles and Practice* is now available at 25s. from booksellers (or 25s. 6d. from the offices of this journal). It has been fully revised and includes a dictionary of television terms. The contents are : The Television System ; The Television Camera ; From Transmitter to Receiver ; Projection Receivers ; Stereoscopic and Colour Television ; Time Bases ; D.C. Receivers ; Aerials ; A London-Birmingham Converter ; Servicing ; Interference ; A Pattern Generator ; Choosing a Receiver ; The Beveridge Report.

We also publish *Practical Television Circuits* at 15s. or 15s. 6d. by post. It contains instructions for building a number of cheap receivers and a spot wobbler, a black spotter, E.H.T. generators, a pattern generator and pre-amplifiers.

### INDEX FOR VOLUME 5

**T**HIS issue commences Volume 6. Indexes for Volume 5 will be available shortly at 1s. 1d. by post from the offices of this journal. Readers who wish to have their copies bound will be glad to know that we have made arrangements with Hazell, Watson and Viney, Ltd., 52, Long Acre, W.C.2, to undertake the binding of your issues in complete volumes with the appropriate index. If you are desirous of having your parts bound, Messrs. Hazell, Watson and Viney will be pleased to let you have a quotation for the work on receipt of an inquiry. Those readers who prefer to have their copies bound by a local bookbinder can obtain not only the above-mentioned index but also an index for any previous volume from us direct for 1s. 1d. each. — F. J. C.

# Experimental Video and Sync Amplifier

CIRCUITS FOR PROVIDING IMPROVED PICTURE QUALITY IN POOR RECEPTION AREAS

**A**MATEUR television constructors share in common with fishermen a distressing tendency towards exaggeration and tall stories.

The tale of "the picture we had last week" is getting as common as "the one that got away." These candid comments apply only to the "fringe area" man.

Seriously though, it is surprising how few home constructors care to view Test Card "C"—assuming, of course, the meagre showings by the BBC of this almost indispensable card are convenient for them to do so.

The most common picture defects met with in fringe areas, apart from fading signals, are "snow," line tearing and poor resolution—the latter usually being excused (or considered necessary) to minimise the former.

Line tearing is a fault which should only be met with in weak signal areas, as its primary cause is random "noise" pulses which erratically trigger the line timebase.

With a low signal this triggering can be caused by valve "noise" alone—as distinct from outside electrical disturbances—and in a poorly designed receiver can make an otherwise usable signal unwatchable.

Sheer gain—as the user of converted "surplus" equipment will be well aware—is not the answer to this problem. The remedy—assuming an efficient aerial array and low-noise preamplifier stages are already in use—lies in the careful design of the synchronising circuits themselves.

If one is just starting to build completely new equipment, some form of "fly-wheel" synchronisation would be the obvious choice, but there are many improvements which can be made to the ordinary triggered timebase—the more advanced circuits to be described—comparing very favourably with the best "fly-wheel" type.

Many keen amateur enthusiasts receiving pictures well outside the accepted range of the TV transmitter will protest that they do very well without the need for fancy circuits, but—in many cases—it is merely the distance that seems impressive; the measured signal strength may be well in excess of that met with in the poorer reception areas within 30 or so miles of the transmitter.

In undulating country—south-west England for

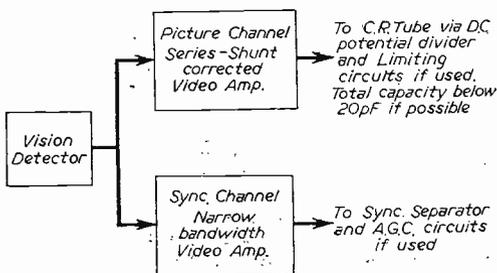


Fig. 1(a).—Block diagram of picture and sync channels.

example—as distinct from predominately flat areas, distance bears little relationship to the prevailing signal strength, and the terms "fringe area" and "long-distance reception" can be very misleading.

The increasing popularity of "fly-wheel" sync in commercial "fringe area" receivers and their inherent immunity from line tearing has "laid by the heels" the generally accepted belief that a

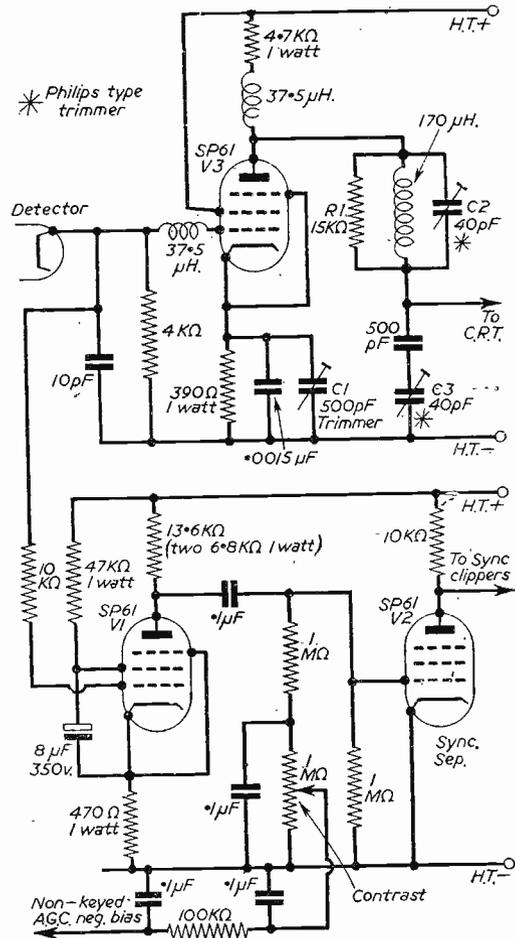


Fig. 1(b).—Theoretical circuits of the Fig. 1(a) scheme.

C1.—Adjust to reduce smearing with minimum overshoot.  
C2.—Turn C3 to minimum capacity then adjust for maximum response on highest frequency grating visible, i.e., 3 or 2.5 megacycles.

R1.—Reduce value to 6.8 KΩ if excessive "ringing" experienced.

C3.—Increase to maximum value possible without visible response cutting—this trimmer is useful to eliminate any 3.5 megacycle patterning which may be present.

restricted band-width in the vision channel was beneficial in reducing picture "noise" or "snow." Anyone who has seen the very much finer textures of the picture "snow" prevalent with a normal band-width, and how much less noticeable it is at the correct viewing distance, will be very dissatisfied with the "smeary" picture inevitable with a reduced response.

Of course, the reduced band-width fan (who may sometimes regard sound rejectors as an unnecessary encumbrance) will insist that response cutting is still essential to minimise line tearing; but the band-width can be narrowed in or to—the sync circuits themselves, where it is unquestionably beneficial with the triggered type timebase.

For the effective sync separation—and to avoid that annoying fault "pulling on whites"—a response of  $1\frac{1}{2}$  megacycles is required, so a separate narrow band-width channel to the sync circuits is quite practicable.

**A Simple Scheme**

One of the easiest methods of adapting an existing

receiver chassis is simply to add an extra narrow response amplifier stage for the sync pulses, and utilise the existing video amplifier for picture signals only.

In this way both functions can be carried out separately and; consequently, with greater efficiency, with the additional advantage that there is now unlimited scope for experiment with the video amplifier (a much neglected field among amateurs) there being no longer the danger of interfering with picture synchronisation.


A practical circuit for experimental video and sync amplifiers is shown in Fig. 1, with several variable components which can be adjusted for optimum performance under the varying conditions that are met with in fringe areas.

The line sync pulse can also be much improved after the sync separator by adopting the technique shown in Fig. 2 (A) and (B). Basically both these circuits work on the principle that better results should be obtained by removing from the sync pulse all that is not wanted, and improving what is left.

With this in mind the first step is to clip the negative going line sync pulse as it appears at the anode of the sync separator. Then it is differentiated, and the positive-going half so produced, removed; finally the negative-going pulse remaining is again clipped and fed to the line timebase.

In the second circuit, Fig. 3, using triode valves, it is, of course, the negative-going trailing edge which is removed, the output pulse, being positive-going, should be fed to the anode if a blocking oscillator is used, the necessary negative pulse on the grid being obtained by reversal action in the transformer.

Having (we hope) reduced line tearing and made an improved video response possible, it may be necessary to widen the vision channel bandwidth to obtain full advantage of the modification. If no signal generator is available this is best accomplished by using Test Card "C," and, as the most favoured I.F. strips among amateurs seem to be "stagger tuned anode or grid circuits" broadening the response curve by "trial and error" requires only a little patience. Contrary to what many articles published on converting surplus I.F. strips would lead one to think, it is virtually impossible for the amateur to use a receiver with a three megacycle bandwidth without the aid of sound rejectors. This statement must, of course, be qualified by ex-

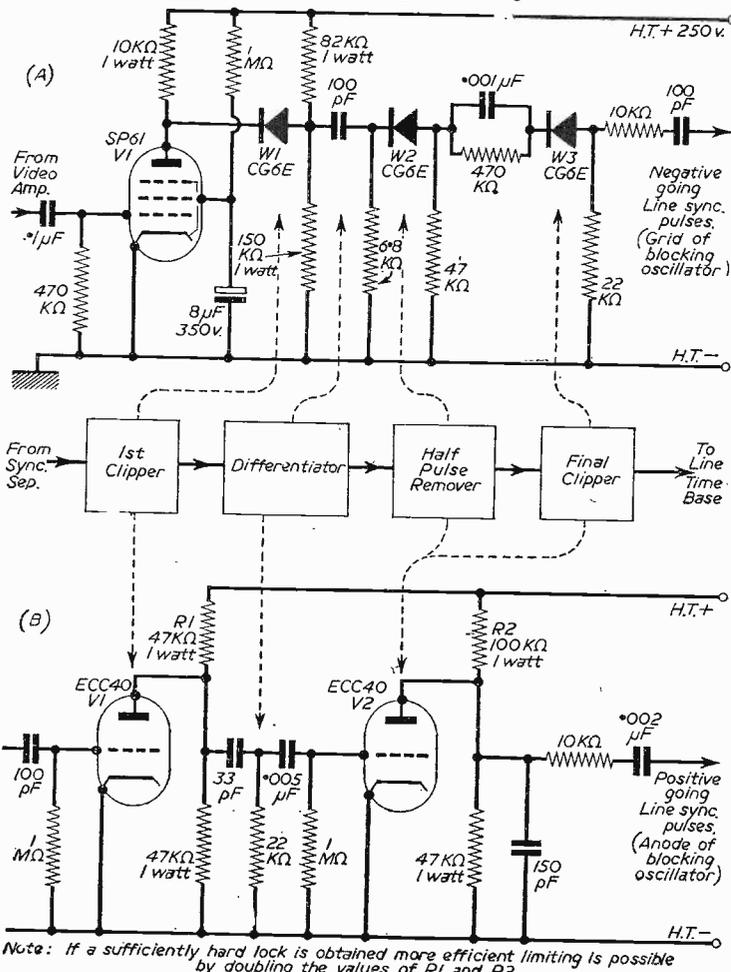

Note: If a sufficiently hard lock is obtained more efficient limiting is possible by doubling the values of R1 and R2

Fig. 2.—Two methods of line-pulse shaping.

cluding Channel 1, where the use of the alternative side-band makes this practicable.

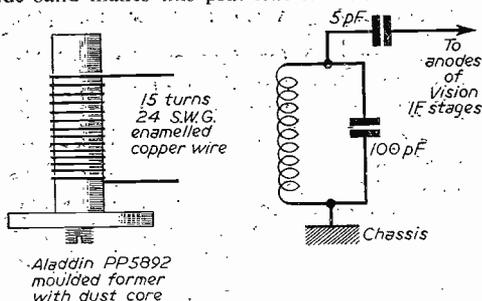


Fig. 3.—Suitable retractor for use with ex-Government I.F. strips.

## New BBC Stations

### Channel Islands

THE BBC announces that it has placed a contract for building work at the Television Station at Les Platons, Jersey, with Messrs. J. A. Parr, 62, Rouge Bouillon, Jersey.

The contract covers the construction of the transmitting station building, installation of water supply and drainage, and the provision of the access and service roads.

Work is starting almost at once and it is hoped that the installation of plant will be completed, and the station brought into service, before the end of this year.

### Crystal Palace

The latest of a series of contracts signed between the BBC and Marconi's Wireless Telegraph Co., Ltd., for equipment for the Crystal Palace television station provides for the construction and erection of the transmitting aerial array.

This follows upon orders for the two vision transmitters, the two sound transmitters, Control and Monitoring equipment, two Vestigial Sideband Filters, two Combining Units and the main Transmission Lines, work upon all of which has been in progress for some time at Marconi's.

The Crystal Palace installation, which is to replace Alexandra Palace, will be the BBC's largest television station, and will incorporate the most modern transmission techniques. It is scheduled to go on the air early next year.

In the system planned for this station, the two 15 kW. vision transmitters and the two  $4\frac{1}{2}$  kW. sound transmitters will be fed into one aerial. This will be accomplished by feeding the respective outputs from one vision and one sound transmitter into a Combining Unit, whence it is conducted by a common main transmission line to half the aerial system. The remaining pair of transmitters will be connected in a similar manner to the other half of the aerial.

The two vision transmitters will thus be effectively working in parallel, as also will their sound counterparts. One big advantage of this procedure is that, in the event of one transmitter developing a fault, the station does not cease transmission, but merely operates at reduced power until the fault is rectified.

### Sound Rejectors

For the other channels—even by using band-pass coupling transformers throughout—it is exceedingly doubtful whether a response up to three megacycles could be obtained with the necessary drop of 35 decibels at three-and-a-half megacycles.

Sound rejectors should present no problem, however, and three—including a sound take-off point—are usually sufficient. Constructional details of a type suitable for use with most "surplus" I.F. strips (13 Mc/s) is given in Fig. 3.

The final results of all or some of these modifications should be some improvement in overall picture quality, but at least one has a very adaptable circuit which will give a range of control over video response which is impossible in the average receiver without affecting picture synchronisation.

## TV Advertising

TV ADVERTISING LTD. announces that Terry Bishop, well-known film director and writer, has been placed under exclusive contract to the company.

Terry Bishop is best known for his documentary film "Daybreak in Udi," a film which received worldwide theatrical and TV release and won both American and British TV awards.

He spent a number of years writing, producing and directing subjects covering the entire shorts, documentary, advertising and instructional range. He was for two years senior director with the Crown Film Unit and for three years under contract to Ealing Studios.

He joins a lively, creative group in TV Advertising, Ltd., which already includes Stanley Black as musical director and composer and script writers including Peter Myers, Alec Graham and David Climie, among whose theatrical and film successes is the current West End review "Intimacy at 8.30."

Terry Bishop will work mostly with Robert King, TV Advertising producer, and M. Danischewsky, who is in charge of the company's planning and production and whose colleague he was at Ealing Studios.

### Production Manager

Another new appointment in the production department of TV Advertising Ltd., is that of Clive Freedman, who has joined the company as a production manager.

Clive Freedman has been production manager and writer for the Crown Film Unit, studio manager for the Film Producers' Guild, and his last feature film was "The End of the Affair," in which he acted as location manager.

**A NEW HANDBOOK**

**"PRACTICAL TELEVISION CIRCUITS"**

288 pages, 156 illustrations

15/- net or 15/6 by post from :


**GEO. NEWNES LTD.**

Tower House, Southampton Street, Strand, W.C.2

# A TELEVISION SIGNAL GENERATOR

A USEFUL SERVICE INSTRUMENT FOR  
USE ON BAND I

By Denis C. Jefferies

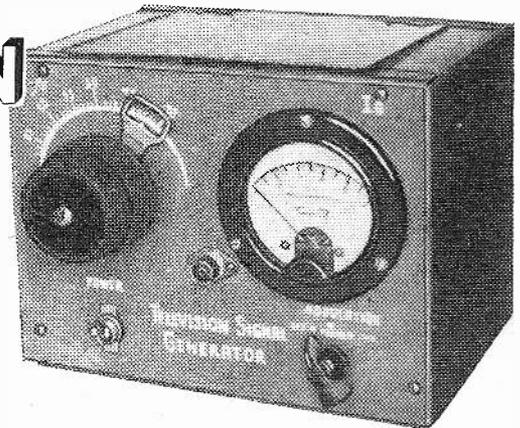

**W**HETHER servicing or constructing television receivers, some form of signal generator will be found invaluable to the television engineer. The minimum requirements are that it should provide an unmodulated, and line or frame modulated, carrier for any channel in Band I. It should also be accurate and reliable and should, in the interest of safety, be isolated from the mains.

Such an instrument has recently been constructed by the author and the complete circuit diagram is shown in Fig. 1. It uses only one valve plus a voltage regulator and provides, in addition to the above-mentioned features, grid-dip tuning facilities. The grid-dip tuning feature enables the engineer to ascertain the resonant frequency of a particular L/C combination, providing it occurs within the frequency range of the generator. The signal generator output loop is simply placed over the inductor and the frequency of resonance is indicated by a dip in the meter.

In order to ensure good frequency stability of the carrier oscillator it is essential that wide variations of temperature and voltage do not occur in the unit. The total power consumption of the generator is less than 10 watts and the components are therefore subjected to very little temperature change after switching on. Slight changes in the H.T. voltage bus-bar are taken care of by the voltage regulator. In

practice the oscillator frequency reaches a steady value within one minute of switching on and the long-term frequency stability has been found to be very good.


The valve used is a 12AT7 high-slope double triode. This was designed primarily for use as a frequency changer operating at frequencies up to 300 Mc/s and no trouble will be experienced in getting it working at Band I frequencies.

The first half of the valve is used for the carrier oscillator. This uses a Colpitts circuit with an inductance of about  $.5 \mu\text{H}$  tuned by a  $5-35 \text{ pF}$  split-stator variable capacitor. The tuning capacitor used by the author was a surplus twin-gang short-wave tuning condenser with a capacity of about  $100 \text{ pF}$  per section. However, this gave a wider frequency range than was really required and a  $35 \text{ pF}$  maximum capacity would be more suitable. With the modulation switch in the "off" position the cathode is earthed and the grid current varies between  $400 \mu\text{A}$  and  $800 \mu\text{A}$  depending on the L/C ratio of the tuned circuit. This corresponds to an oscillator voltage of 4 to 8 volts across the  $10 \text{ k}\Omega$  grid resistor.

The output from the oscillator coil L1 is inductively coupled to a single turn on the former and wired to the co-axial output socket. From the socket it feeds into about a yard of flexible co-axial cable terminated with a single  $\frac{1}{2}$  in. dia. loop of 16 s.w.g. copper wire. This probe coil holder was made from a polystyrene coil former the base being drilled to make the co-axial cable a tight fit into it. As no buffer stage is provided in the unit the carrier frequency will be found to vary slightly if the co-axial output lead and probe are disconnected. It should not be normally necessary to do this, however, as the radiation from the probe coil is ample for normal work and it is usually quite sufficient to lay the probe coil near to the aerial input connection of the receiver to be lined up.

The calibration of the unit can be checked from time to time by beating the output from it against a known television sound channel frequency. Trimmer C2 is included in order that the unit may be very simply re-calibrated if the 12AT7 is changed at any time.

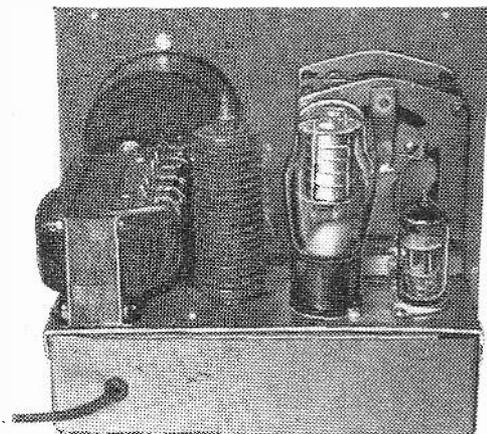If frame and line linearity checks are to be made on receivers, two modulating frequencies are required in the signal generator. These frequencies must be multiples of the frame and line timebases if the cathode ray tube is to display a fixed pattern. The British television system uses 50 c/s frame and 10,125 c/s line repetition frequencies and therefore 300 c/s



A rear view of the completed signal generator.

and 81 kc/s were chosen as the two respective modulating frequencies in the generator. These produce six white bars in the frame and eight white bars in the line position of the modulation switch. These give a bar

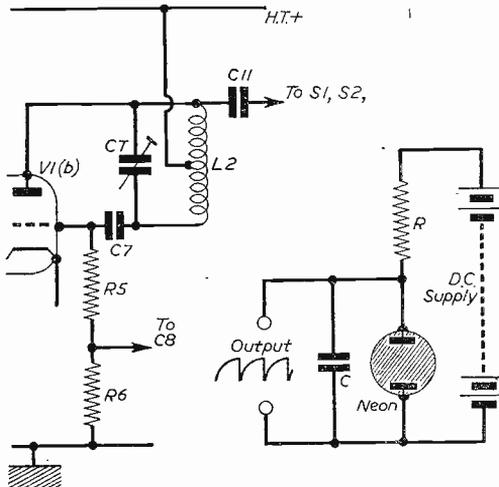


Fig. 2 (left).—Alternative 81 kc/s oscillator circuit if centre-tapped coil is available. C1=250 pF trimmer. R4, C5 and C6 are not required. Fig. 3 (right).—Basic circuit of a neon relaxation oscillator. The D.C. supply charges C through R until the potential of C is sufficient to cause the neon to strike. On striking, the neon discharges C and the cycle is repeated.

ratio of 3 : 4 which is the same as the picture aspect ratio and the bar widths, therefore, should be exactly the same on frame or line if the timebase amplitude controls of the receiver are correctly set. Lack of

linearity in the receiver timebases shows up as differing bar widths down or across the screen.

The 81 kc/s oscillator producing the line modulation is another Colpitts circuit using the other half of the 12AT7. The coil used by the author was a 100 kc/s oscillator coil obtained from Government surplus radar gear. However, a bias oscillator coil as supplied for use in tape recorders would do very well. These are usually centre-tapped and a slightly modified oscillator circuit can be used as shown in Fig. 2.

Modulation of the television carrier is effected by means of the cathode resistor R2 which is common to both VI(a) and VI(b). This is short-circuited when C.W. is required as a greater amount of grid current is then obtained for accurate grid-dip tuning.


The frame modulation frequency generator is a simple neon relaxation oscillator working at 300 c/s. This feeds into the grid of VI(b) which acts as a cathode follower buffer stage modulating VI(a). A neon relaxation oscillator circuit is shown in Fig. 3. With a particular neon lamp and supply voltage the frequency of oscillation is determined by the product of the components R and C. In the prototype these worked out to 150 kΩ and .01 μF, but constructors will have to experiment with the values in order to get the frequency exactly right. R7 could conveniently be made up from a 50 kΩ fixed and a 200 kΩ variable resistor in series in order to save time in the initial setting up.

The 300 c/s frame modulation also provides a tone source for the alignment of the sound section of television receivers.

The striking voltage of neon lamps is affected by the amount of light falling on them. Any variations caused by this phenomena will not be enough normally to matter, however. The meticulous constructor will of course paint the neon bulb black!

The power supply is quite conventional and consists of a small instrument-type mains transformer supply-

Fig. 1.—Theoretical circuit diagram.

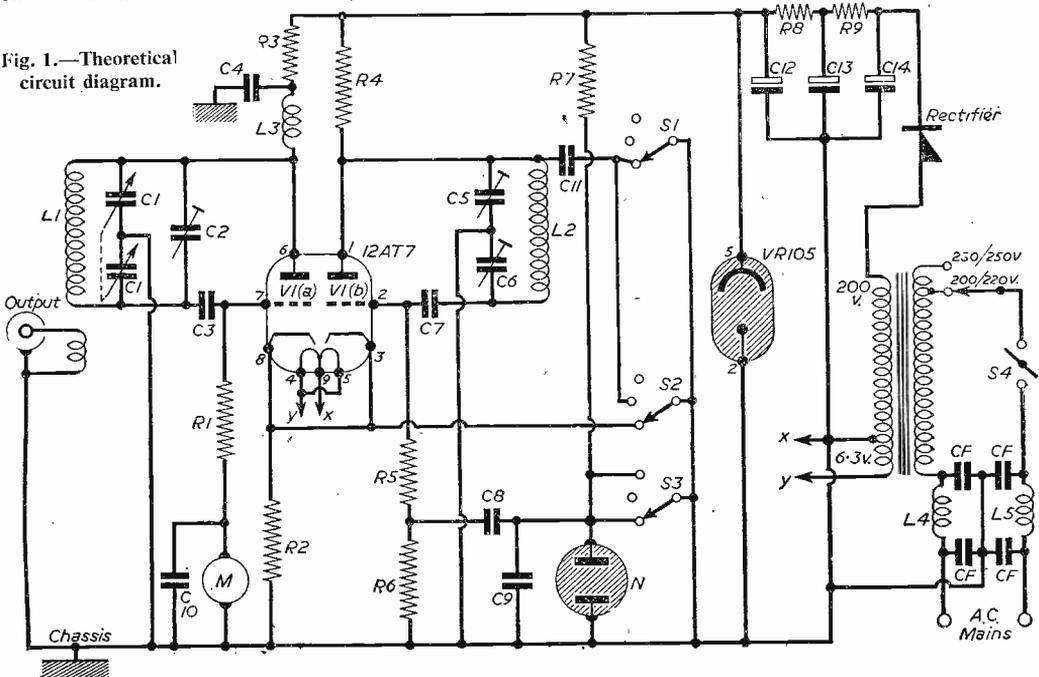

ing 200 volts at 30 mA and 6.3 volts at 1.5 amps., followed by a metal rectifier feeding a resistance capacity smoothing network. Where test gear is concerned it is well worth paying a few shillings extra for a completely isolated mains transformer as there is a very real danger when using unisolated test equipment with A.C./D.C. television receivers. To reduce radiation from the unit via the mains lead an R.F. filter is fitted in the lead where it enters the generator. Putting the filter on the other side of the power switch would have meant that quite long lengths of mains lead in the generator would be unfiltered. The only disadvantage with the system used is that there is mains leakage through the four C.F. filter condensers. Their combined capacity is .001  $\mu$ F and at 50 c/s they have a reactance of about 4 m $\Omega$  giving less than 100  $\mu$ A drain across the mains supply. Good quality new capacitors are essential here if they are not to break down after a short period of use.

The half-wave metal rectifier feeds into an 8+16  $\mu$ F electrolytic smoothing condenser followed by a 2  $\mu$ F paper block condenser. A 2  $\mu$ F electrolytic could, however, be used. Resistance capacity smoothing is quite sufficient and it avoids the expense of smoothing chokes as well as saving space. The H.T. supply to the 12AT7 and neon oscillator is regulated by means of the VR105 voltage regulator. This maintains the H.T. voltage to within a few per cent. of 105 volts, despite mains voltage fluctuations and changes in the current drain of the 12AT7 occurring in different positions of the modulation switch.

**Construction**

The unit was built in a ready-made steel instrument case size 8in.  $\times$  6in.  $\times$  5 $\frac{1}{2}$ in. This was supplied

complete with an aluminium chassis, and the only metal work involved was the drilling of valve meter and component mounting holes. A 0.1 mA meter is used to indicate the grid current of VI(a). Its resistance is not important providing it is less than about 2 k $\Omega$ . The main variable capacitor C1 is controlled by a 100 : 1. Utility slow-motion drive and the calibration frequencies are painted directly

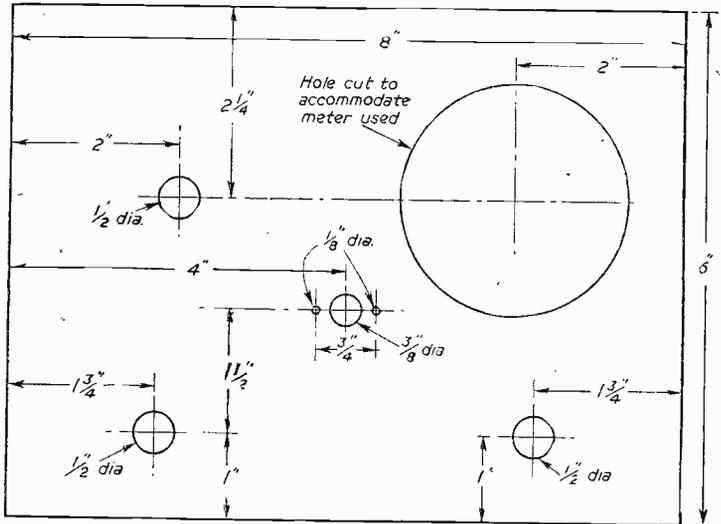


Fig. 4.—Front panel drilling.

on to the faceplate of the case. Figs. 4 and 5 show the layout of the front panel and chassis respectively.

Wiring the generator should present no difficulty providing the components are set out approximately as shown. The generous use of tag strips greatly simplifies the wiring and enables all small components to be rigidly mounted. The carrier-frequency oscillator wiring, carried out with bare 16 s.w.g. tinned copper wire, is prevented from shorting to the chassis by the use of rubber grommets placed in the feed-through holes. Heavy gauge wire is used for wiring this section to ensure rigidity and to reduce the losses in the resonant circuit. It is essential to use a trimmer capacitor with an insulated mounting for C2, as both plates are at H.T. potential.

When the wiring has been completed it is advisable to check it over thoroughly to ensure that no mistakes have been made. This is especially important in the meter circuit, as the meter can be permanently damaged if the wiring is in contact with the L.T. or H.T. supplies. If the polarity of the meter is known, the negative side should be connected to the grid resistor.

**Calibration**

Calibration of the unit should be carried out when it is in its metal case. Another television

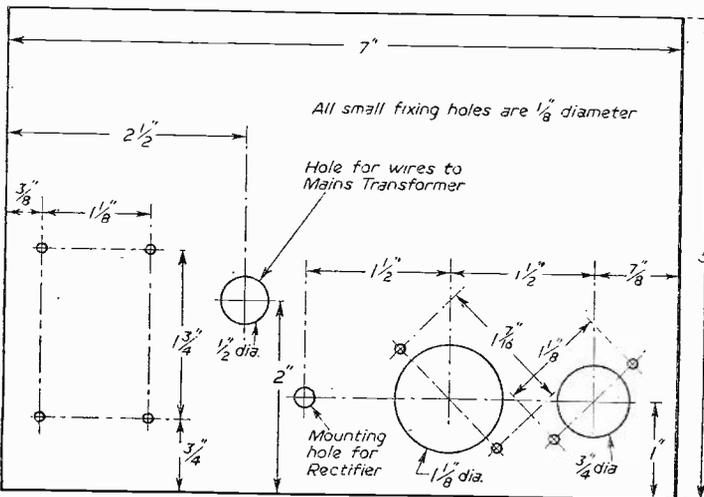


Fig. 5.—Plan of chassis.

signal generator covering Band I is not required for the calibration. The author, in fact, used a radio type signal generator over the range of 13 to 23 Mc/s. These generators usually have quite a usable third harmonic output and therefore the above frequencies will give check points in the range of 39 to 69 Mc/s.

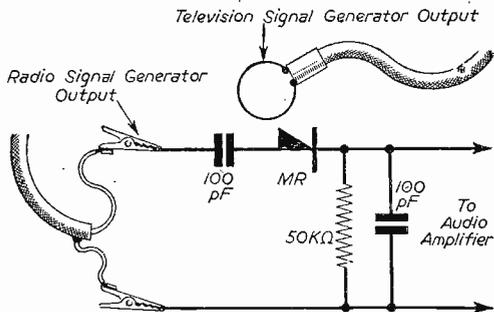


Fig. 6.—Circuit used for beating the outputs of two generators together.

The output from the radio signal generator is connected directly to the probe of a signal tracer and the output loop of the television signal generator is placed near to this connection. When the third harmonic is near the carrier of the TV signal generator a "squeal" will be heard in the signal tracer speaker. The two frequencies can then be adjusted until the beat note is zero. If a signal tracer is not available, an audio-amplifier can be made to work as such with the hook-up shown in Fig. 6. MR is a germanium diode. The "pick-up" facilities provided on a broadcast receiver can be used for audio amplification.

A correctly adjusted television receiver is required to set up the 300 c/s and 81 kc/s oscillators in the generator. The aerial of the television receiver is disconnected and the output loop from the generator is placed near to its aerial socket. With the modulation switch in the "frame" position the generator output should be adjusted to the sound frequency appropriate to the receiver. A tone will be heard in

the receiver if the neon oscillator is working correctly. If the generator output is then shifted to the vision frequency of the receiver a horizontal bar pattern will be seen on the screen. Resistor R7 should then be adjusted as previously mentioned until six steady white bars are obtained. The modulation switch should then be turned to the "line" position and the 81 kc/s oscillator capacitors adjusted until eight vertical white bars are seen. The trimmers can then be set with quick-drying cement if it is thought necessary.

#### Receiver Alignment

It is essential that the television engineer be familiar with the nature of a vestigial sideband transmission if he is to obtain the best possible performance from the receiver he is working on. The transmitted waveform is shown in Fig. 7(a). V is the vision carrier frequency and S its associated sound carrier. It will be seen that the transmitted sidebands extend

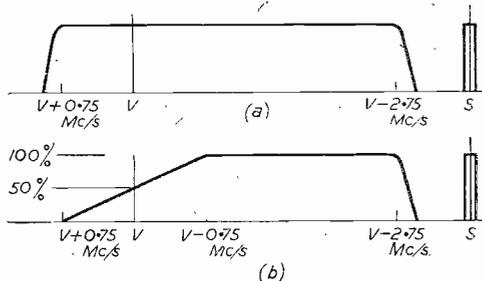



Fig. 7.—Showing (a) a vestigial-sideband transmission; and (b) the correct receiver alignment curve.

to  $V-2.75$  Mc/s and  $V+0.75$  Mc/s. After demodulation the outputs of the sideband frequencies each side of V are added, and it is necessary to make the receiver response curve the same as shown in Fig. 7(b) if the receiver is to perform correctly. It will be seen that the receiver response should drop steadily from maximum at  $V-0.75$  Mc/s to zero output at  $V+0.75$  Mc/s and will therefore be 50 per cent. down at V.
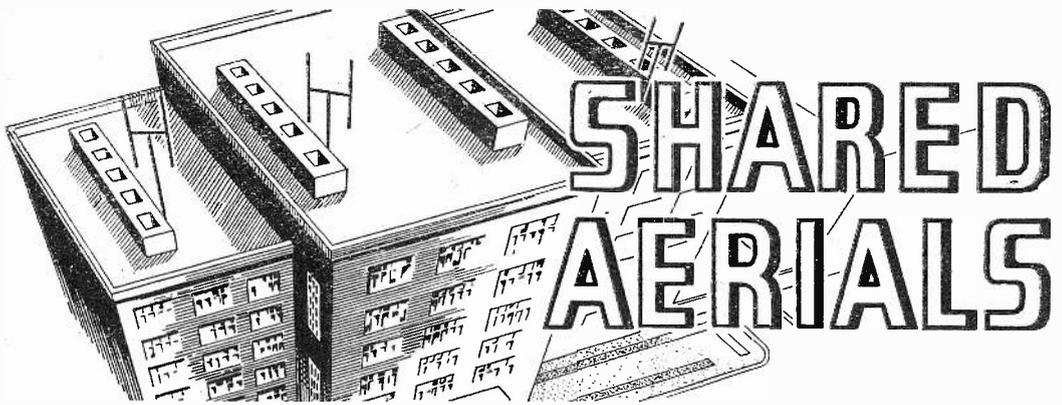
#### LIST OF COMPONENTS

- C1—0.35 pF split-stator variable condenser.
  - C2—0.10 pF airspaced pre-set trimmer.
  - C3—20 pF (250 v.).
  - C4, C10 and CF condensers—0.01  $\mu$ F (500 v.).
  - C5, C6—100 pF trimmers.
  - C7—500 pF (250 v.).
  - C8, C11—1  $\mu$ F (250 v.).
  - C9—0.1  $\mu$ F (250 v.) (see text).
  - C12—2  $\mu$ F paper or electrolytic (300 v.).
  - C13—16  $\mu$ F electrolytic (300 v.).
  - C14—8  $\mu$ F electrolytic (300 v.).
  - R1—10 K  $\frac{1}{2}$  watt.
  - R2—1.2 K  $\frac{1}{2}$  watt.
  - R3—5.6 K  $\frac{1}{2}$  watt.
  - R4—12 K  $\frac{1}{2}$  watt.
  - R5—50 K  $\frac{1}{2}$  watt.
  - R6—470 K  $\frac{1}{2}$  watt.
  - R7—150 K  $\frac{1}{2}$  watt (see text).
  - R8—3.9 K 2 watt.
  - R9—2.2 K 2 watt.
- All resistors are carbon.  
N—Small neon bulb striking at about 70 v. (with-out internal resistor).

- Metal instrument case 8in. x 6in. x 5 $\frac{1}{2}$ in. with aluminium chassis.
- 0.1 mA meter.
- 100-1 "Utility" slow-motion drive.
- Co-axial plug and socket.
- Four 5-way tag strips.
- S1-S2-S3—3 p., 3 w. switch
- S4—On/off toggle switch.
- Miniature mains transformer: Pri. 200/250 v. sec., 200 v. at 30 mA, 6.3 v. at 1.5 amp.
- Metal rectifier: 250 v. 40 mA (2 type RM1's suitable).
- L1—Main coil approx. 3 turns on  $\frac{3}{4}$ in. diameter ceramic former.
- L2—81 kc/s oscillator coil (Osmor) (Type QT8 suitable).
- L3, L4, L5—40 turns 30 s.w.g. D.C.C. spaced in four sections on  $\frac{1}{4}$ in. diameter former.
- One B9A valve base and one International Octal valve base.
- One valve type 12AT7 and one valve type VR105.
- One yard of  $\frac{1}{4}$ in. diameter co-axial cable and three yards of mains lead.
- 4BA and 6BA nuts, bolts, washers, etc.



HOW TO FEED TWO OR MORE RECEIVERS FROM A SINGLE AERIAL ARRAY

By "Serviceman"

**T**HE rapid advance of television has resulted in an alteration of the skyline of Great Britain; wherever one goes, chimney stacks are adorned with TV aerials of all sorts of shapes and sizes.

A few years ago there was very little difficulty with the erection of an aerial on the chimney. So much of the country consisted of fringe area that only the foolhardy or the brave attempted reception. One or two neighbours who shared a chimney stack decided to "have a go" and an aerial was duly erected.

Nowadays, things are different and it is very common to see two aerials perched on the same chimney stack, neither being of the slightest assistance to the other nor to the stack. When Band III gets really going, and both neighbours have dual aerial systems, we shall have the sight of four aerials on the one chimney stack.

erection of high-gain aerials in many places within the service area.

Let us make no mistake about it; in a poor service area a good aerial system is a *must*, but in many cases within the service area a good dipole erected in the loft will provide all the picture signal which is necessary.

As an example of the unnecessary use of outside aerials I would like to quote the position in my own immediate locality. We are situated less than 30 miles from Wenvoe, yet from the window of the room where I am writing I can see 14 "X" aerials on chimneys, five "H" aerials on chimneys, two "H" aerials fitted on the fascia board, three "X" aerials fitted on the fascia board, two dipoles, one on the chimney and one on the fascia board. In addition, I know that three of my immediate neighbours have dipoles in the lofts as I have myself, and reception with these is adequate.

The first thing to do then is to verify that an aerial on the chimney is really necessary. The home-Constructor can quite easily make up a dipole and try it in the loft, and if he then finds the signal pick-up is inadequate, elaborations can be made.

If there is room in the loft, an "X" or an "H" aerial can be tried, but if reception or conditions do not allow this, then the possibility of two neighbours sharing one aerial should be considered.

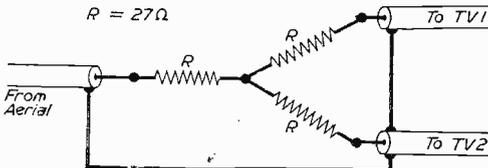


Fig. 1.—A simple method of providing two channels from one aerial.

Not only is the multiplicity of aerial systems unsightly, but when aerials are erected in such close proximity to each other, then they are not working really efficiently. Permanent and fleeting ghosts often result and the automatic gain controls are worked hard to retain a steady picture during high winds when the two arrays sway to and fro.

Fitting an Outside Aerial

The first thing to consider when confronted with the problem of an additional aerial on a dual chimney stack is whether the outside aerial is really necessary.

*There are very many elaborate aerials erected on chimney stacks which are totally unnecessary.*

If one were to remark that the system is good for business it would, perhaps, be considered unfair, but the writer can conceive no other notion for the

Sharing an Aerial

The simplest arrangement possible is where the circuit from the aerial is divided into two channels. Fig. 1 shows the arrangement. The coaxial lead from the aerial is terminated in a small junction box (one of the round plastic type available from multiple stores can be used), and two feeds are taken out. All

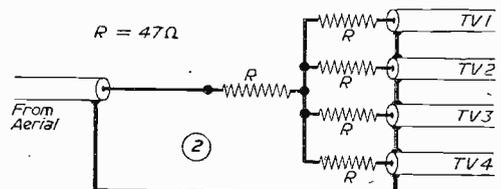


Fig. 2.—In this scheme four receivers may be fed from a single aerial.

outers of the coaxial cables are connected in parallel and the centres are connected via resistances of 27 ohms. Half-watt resistances can be used.

Although simple, the arrangement is perfectly workable, though some losses must be expected. If the area is one in which the signal strength is on the

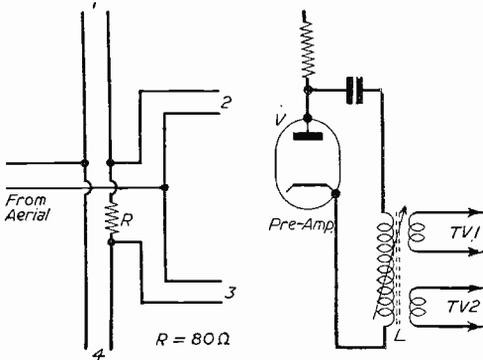


Fig. 3 (left).—Using a balanced twin feeder. Fig. 4 (right).—Splitting the output of a pre-amplifier.

low side, it would be beneficial to erect an aerial of a more elaborate type so as to counter losses. It is better for there to be a single high-gain aerial than for two aerials to be erected on the same chimney, both from the point of view of possible strain on the chimney stack, and from the electrical angle.

It is possible to operate more than two televisions from one aerial, and a scheme catering for a total of four receivers is given in Fig. 2. The system is very similar to the first case, but the total losses will, of course, be greater.

Another circuit which uses a balanced twin feeder is shown in Fig. 3. Four outputs are available, and for its successful working each branch should be terminated. Any branch which does not have a receiver at the end should have an 80-ohm non-inductive resistance fitted across the termination.

**Pre-amp Output**

In each case so far quoted the fitting of the extra circuit(s) involves a certain loss in the overall signal available. In the fringe areas this loss cannot be tolerated so an alternative must be found.

The simple answer is to use a pre-amplifier with a divided output.

In Fig. 4 will be found the simple case. V is the output valve of the pre-amplifier and L is the output coil. Normally, this coil has one secondary winding which feeds the television receiver. It is a very simple matter to add a further output coil on top of the existing primary.

The idea can be further extended and split feeds fed from the two separate outputs. By this method it is practicable to feed eight television receivers from a single aerial system.

When a single pre-amp feeds two houses, there may be difficulty in arranging its switching; it is wasteful to have the amplifier switched on permanently. A solution to the problem is shown in Fig. 5.

With this arrangement a relay is employed to switch on the mains supply to the pre-amp. The relay is shown as "A" in the diagram.

The scheme is for the relay to operate when either television receiver is switched on; for this reason it is operated from the H.T. supply of each receiver, a relay with dual coils being employed. There are a large number of relays of this description on the market from ex-Government apparatus. All that is necessary is for the relay to operate from either H.T. supply, the resistance "R" being used to limit the current.

When one of the television receivers is switched on the relay "A" operates, and the contacts A1 and A2 switch on the mains supply for the pre-amp. When both television receivers are switched off the pre-amp automatically switches off.

The location of the pre-amp will depend upon local arrangements, but it could quite conveniently be mounted in the loft of one of the houses and leads fed to each house.

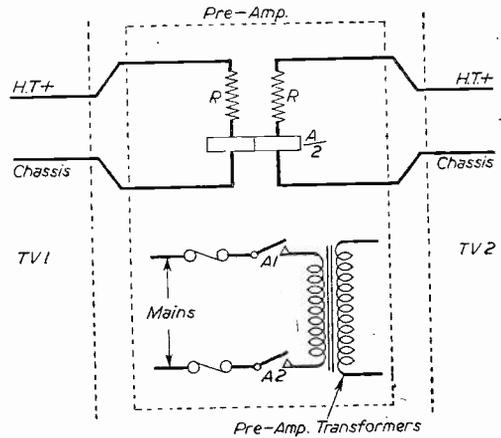


Fig. 5.—Using a mains-operated relay for switching on and off.

**Conveyor Speeds Production**

AT the Romford factory of Regentone Radio & Television, Ltd., a new "soak test" conveyor has been installed to speed up the testing of television chassis before final assembly and despatch.

For the satisfactory testing of newly assembled television chassis, several hours of continuous operation are necessary, since it is during this period that any faults in new sets are normally discovered by the purchaser. The ever-increasing rate of manufacture at the Regentone factory made the stationary testing of assembled chassis for this period a drag upon the production line and the "soak test" conveyor has been introduced to speed up this part of the process.

Supplying electricity to the individual chassis whilst in motion presented a problem which has been successfully overcome by the use of miniature current collection arms running along hard-drawn copper bars. Each bank of three television chassis is supplied via two of these miniature arms, which are completely swivelling and are particularly suitable for installations of this kind, having been specially developed by British Insulated Callender's Cables, Ltd., who co-operated with Regentone in the design and installation of the current collection equipment.





thus, as well as the later BT7092 table models. The H.T. supply to both frame and line timebase is decoupled by an 8  $\mu$ F 500-volt electrolytic condenser marked C33 in the top chassis diagram. If this condenser dries up erratic operation of timebases coupled with poor focus will result. The focus coil is in series with the H.T. supply to the timebases and is shunted by the focus control and its series resistors and is bypassed by a 50  $\mu$ F 50-volt electrolytic. Note that the MU14 rectifier marked V9 is solely concerned with supplying the line and frame timebase. The H.T. voltage at the smoothed point of supply to the timebases, i.e., at C33, should be approximately 340 volts.

**The Line Timebase**

This consists of a two-valve unit preceded by a triode pulse inverter. The line output, KT45, marked as V22, acts as part oscillator as does the frame output. In this case, however, the coupling to the control grid of V21, L63, is from the secondary of the line output transformer via a 47 pF condenser. The anode of V21 is condenser coupled to the control grid of V22 (.005  $\mu$ F).

The cathode of the KT45 is joined to chassis via a 68 ohm and a 1 K variable resistor, this latter functioning as the width control. Neither of these has a bypass condenser, and the control grid leak,

220 K, is taken to the junction, that is, the bottom of the 68 ohm and the top of the 1 K variable. Horizontal form is a 1 K variable which, in series with a resistor condenser network, comprises the linearity arrangement across the scan coils.

I have found that if the raster tends to compress at the left-hand side the linearity network is not generally at fault. The cause is more often to be found at the screen grid of the KT45. This is supplied from the H.T. supply by a 10 K resistor and is decoupled to chassis by a 1  $\mu$ F paper condenser. This condenser appears to dry up or otherwise go open circuit and causes a decreased line scan with the left-hand side compressed as stated. The testing of this component is extremely simple, as it is mounted just behind the previously mentioned frame cathode condenser, and as it is much taller it is more obvious, and its "hot" end is at the top. Therefore, all that is required is for the lead to be removed and the condenser tested in the normal way with the reactive clip of the meter to chassis and the positive probe just touched on the tag at the top of the condenser. The swing of the meter will, of course, be very small compared with that of a higher capacity electrolytic, but assuming a meter of reasonable sensitivity is used sufficient indication will be given to prove the component up to capacity. If there is any doubt a suitable condenser of 1  $\mu$ F or more may be shunted across to check any change in the raster. An electro-

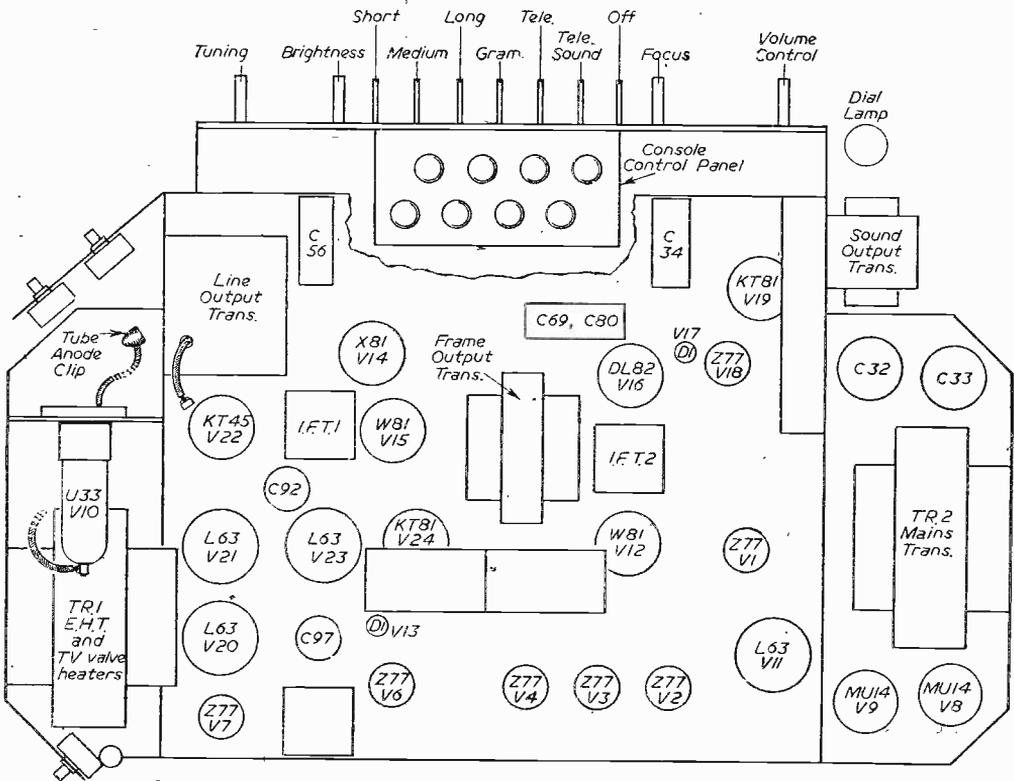


Fig. 4.—Top chassis view of table model. The side transformer "wings" are combined to form a power pack on the console version. The panel marked "Console control panel" is only mounted on the Console and is actually located under the P.B. selector unit. The positions of C92, C97 and C33 should be noted.

lytic may be used if a paper type is not available, attention being paid to polarity and working voltage, not less than 450 volt being used for this test. If no line scan is obtainable, a white line extending vertically down the screen centre, attention should be directed first to the valves V21 and V22.

If these prove good the voltage at the top of the previously mentioned condenser should be checked; 175 volts is approximately correct. If this voltage is absent remove the lead from the tag and check the voltage on the lead. If voltage is now present it will normally indicate a shorted condenser, and a meter check should reveal a short circuit from the tag to chassis. If, however, there is no voltage when the lead is free it will indicate one of two things—either the 10 K 2-watt dropping resistor is open circuit; quite possible if the condenser has shorted, or the KT45 has an internal short. This, of course, presupposes that the KT45 (V22) was not checked for emission or shorts previously. However, if a higher voltage than 175 is found at the condenser tag it could well indicate that the width control (1 K series cathode of KT45) is open circuit. It is as well to point out here that it is essential to check the cathode bias resistors of any valve if an internal short has occurred which could result in a heavy flow of current passing through these components.

**Tube Defects**

The effects of a heater-to-cathode leak or short are well known and should not need reiterating. However, a short in the tube of this receiver will not cause uncontrollable brilliance as the heater has an isolated winding on the mains transformer. The vision interference limiter V13, Mazda DI, also has its heater fed from a tapping on this winding, and this point should be borne in mind as one side of this diode's heater is decoupled by a .01  $\mu$ F condenser. If there is any doubt as to the cause of a particular defect the diode should be removed altogether. Excessive brilliance will most often be caused by a defective condenser in the video amplifier anode circuit; a study of the diagram will show that there are several of these components which may cause a drop in cathode tube voltage should a defect occur. The voltage at the anode of the video amplifier should read approximately 240 volts.

If this voltage is at or near this figure the tube grid potential should be checked and a high reading here will indicate that the voltage divider network comprising three resistors is at fault. This network is made up of a 56 K  $\frac{1}{2}$  watt from H.T. to the top of the brilliance control, which is a 250 K variable,

(Concluded on page 36)


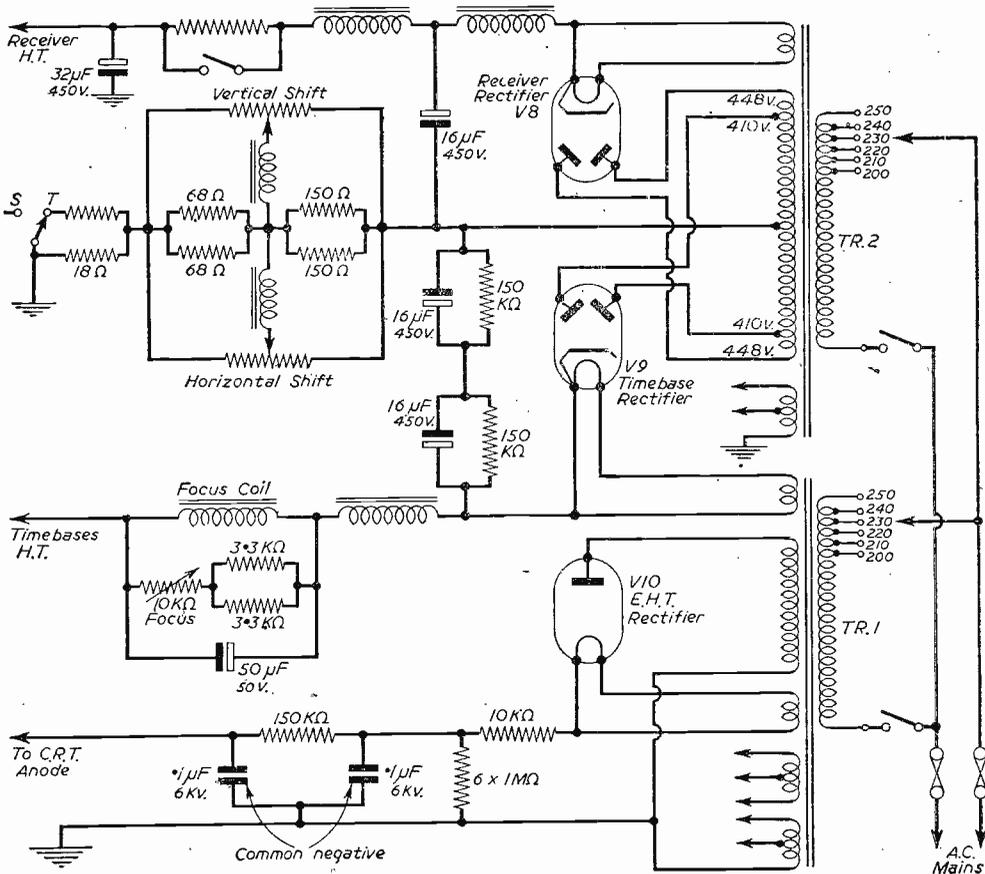


Fig. 5.—H.T. and heater supply. TR1 is disconnected on radio.
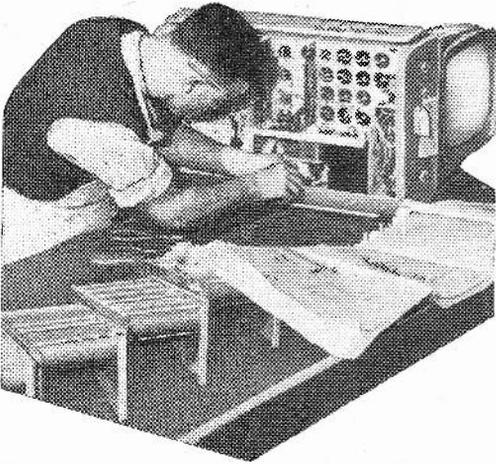
# PAGES FROM A TELEVISION ENGINEER'S NOTEBOOK



## A VALVE SELECTION CHART

(where C is this total valve capacity) is called the bandwidth of the system, then

$$\text{Gain} \times \text{Bandwidth} = \frac{gm}{2\pi C}$$

which depends solely upon C and gm. For the maximum bandwidth, therefore, a large gm and a small capacity C is necessary. In valve design, of course, these two requirements conflict with one another, and a high gm leads to an increase in input capacity.

Complicated networks will increase the bandwidth of a particular amplifier, but the criterion is always dependent upon the ratio of gm to C.

**T**HERE are many types of valves now available to the television constructor and experimenter, and no doubt the supply of ex-Government types is still far from exhaustion. The valves in mind are those suitable for R.F. and video voltage amplification, and so cover those characterised by high mutual conductance and low inter-electrode capacity.

These types are almost invariably pentodes or tetrodes, and it is often difficult to select a suitable valve for a particular purpose without wading through manufacturers' catalogues and characteristic data. For this reason the valve selection chart to be described has been drawn up; with this it is possible to get the main points of suitability of a particular valve almost immediately, and it can be built up by the user as newer types are released so that its information is always up to date.

The important features of a pentode for television and other wide-band work are its mutual conductance gm and its input and output capacities, Cgc and Cac respectively. The anode impedance Ra is usually very large compared with the anode loading R, and so may be ignored.

As we have seen in previous articles in this series the gain of a pentode amplifier is given to a close approximation by the equation

$$\text{Gain} = gm.R$$

If the stage is uncompensated, this gain falls at the high frequency end of the range, and is actually 0.707 of the above amount when the reactance of the shunting capacity across R is equal to R. As the bulk of such capacity comes from the sum of the input and output capacities of the valves used, it is seen that these reactances are very important in consideration of wide-band design.

$$\text{If the frequency } f = \frac{1}{2\pi CR}$$

### The Selection Chart

Fig. 1 shows the basic idea of the chart under discussion, though this is by no means complete.

To draw the chart, gm is taken as the horizontal axis, with C, the sum of the valve input and output capacities, as the vertical axis. Logarithmic scales are used in both directions because this permits lines representing a constant gain-bandwidth product to be drawn in as 45 deg. diagonals, shown in the figure as broken lines. As the chart is built up, the best valves for the purpose of wideband requirements are those positioned towards the bottom right-hand corner.

For the constructor who wishes to make up his own chart for ready reference, get a large sheet of double log. graph paper and mark out the co-ordinate axes as shown in the figure. It is of little purpose taking gm beyond 20 mA per volt or the sum of the capacities beyond 30 pF. The positions of the various valves are then marked in by taking the figures of gm and the capacities from the manufacturer's list and plotting these in the usual way, the

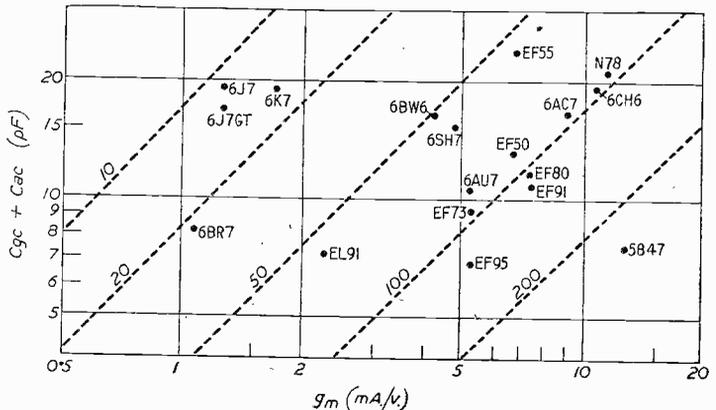


Fig. 1.—A basic idea of the valve selection chart discussed in this article.

name of the valve type being marked beside its own locating point. Equivalent types, such as the EF91, 6AM6, Z77, etc., are, of course, all represented by one point.

The diagonals are marked in to give the appropriate gain-bandwidth products; they run parallel to each other as shown.

In addition to showing the best valves for wide-band working as mentioned above, the chart shows valves which are electrically similar, such as the

EF91 and EF80. It also shows how a valve is improved by a higher mutual conductance (6AU7 compared with the EF91), or by a reduced capacity (6AU6 compared with the EF95).

Valves on the same diagonal line are revealed as having the same gain-bandwidth product, but different values of gm and C, such as the 6AC7 and the 6CH6.

With a large sheet of paper it is not difficult to list over a hundred valve types for easy reference without confusion.

## "TeleVet" Tester

EVERY service engineer who is called upon to retrim a television receiver needs other apparatus besides a signal generator. Usually, for some particular types of receiver a wobulator is essential for accurately lining up the I.F. circuits, and in addition to these an audio output for the sound section, plus a pattern generator, might also be needed at certain times of the day when there is no actual signal on the air. This means that usually a receiver cannot be serviced in the customer's home, but must be taken away where the full facilities of a service workshop may be obtained. The Airmec people have tackled this problem, and as a result have produced the neat instrument shown below, and known as the "TeleVet." Consisting basically of a signal generator, it incorporates a C.R. tube for indications, and by means of the various test leads and controls it is possible to obtain a video output at any frequency on Band I or Band III, with a wobulated signal controlled at 5 Mc/s intervals by means of a self-contained crystal; a pattern consisting of a horizontal bar and two vertical bars; an audio oscillator; an A.C. and a D.C. voltmeter measuring up to 20 kV, and an output meter.

### Fixed Leads


Unlike many multi-instruments, this instrument has all the various test leads permanently attached, and stowed, when not needed, in pockets on each side of the cabinet. Screened leads are used for the various

R.F. outputs, and each lead or termination is identified by means of a letter. The very exhaustive manual supplied with the instrument makes it a simple matter to select the required lead when first using the instrument, and after a short period of use it becomes a simple matter automatically to choose the required lead. The unused leads may be left lying on the bench or stowed inside the pockets and do not affect the results on the used leads. A standard signal generator round which the instrument is assembled covers the ranges from 8 to 70 Mc/s and from 168 to 230 Mc/s, and a 5 Mc/s crystal incorporated with a special circuit enables the instrument to be set to any multiple of 5 Mc/s—an accuracy better than .02 per cent. A mechanical wobulator varies the setting over a 12 Mc/s sweep, and an initial setting of the controls enables the waveform on the tube to be centred with three pips at 5 Mc/s spacing so that bandwidth may easily be read off or identified. The wobulator can, of course, be switched off, and an unmodulated R.F. output obtained, or alternatively, the signal generator may be switched off and the tube used at a straightforward oscilloscope with built-in D.C. "Y" amplifier.
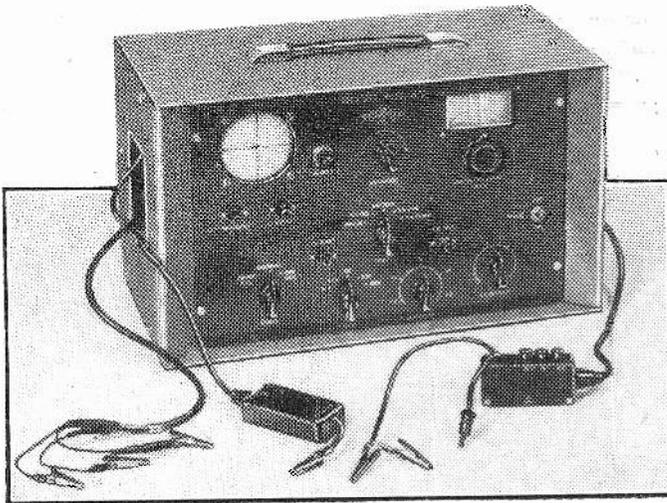
### Dial Readings


The scale provided has a deep-set cursor with a vernier, and the built-in oscillator produces beats which may be ignored for rough tuning, but where a high degree of accuracy is required, a little skill and some calculation are called for in finding, by means of the audio output, two dial settings on the vernier and then calculating an intermediate setting, but although a little complicated when first using the instrument one soon gets accustomed to the procedure; and one or two short cuts become evident—dependent upon the type of receiver being serviced and the accuracy which is required. The chassis and earth line are isolated, and the tester may thus be employed in servicing A.C./D.C. apparatus, and all the facilities mentioned have been incorporated in a case measuring overall 15½ in. long, 8½ in. high and 9½ in. deep, and weighing only 25lb. The case size is actually larger than the instrument itself, as this includes the two pockets on each side of the case. We have had one of these testers in use in our lab. for some time now and have found it to be one of the most useful pieces of equipment which we have come across.

The price of the instrument is 57 guineas, and the makers are Airmec, Ltd., High Wycombe, Bucks.



The Airmec "TeleVet" Tester.

# Amateur Television Equipment

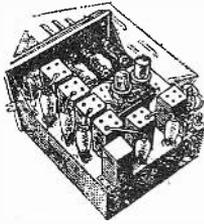

**RESPONDER UNIT**

Ideal for Commercial TV. These contain 6 valves type SP61, and one each RL7, RL16 and EA50. Six IF transformers 12 Mc/s. band, and hundreds of other useful components. Price 39/6, plus carriage and packing 7/6. These receivers are unused.

## SPECIAL SNIP R.F. UNITS

TYPES 24 & 25

Complete and in good order. Price 7/6 each, plus 1/6 postage.




## CONNECTING WIRE SNIP

P.V.C. insulated 23 s.w.g. copper wire in 100ft. coils, 2/9 each. Colours available: Black, Brown, Red, Orange, Pink, Yellow, White, Transparent. 4 coils for 10/-.

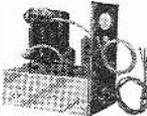
## THE ELPREQ E.H.T. GENERATOR

This is a made up unit working on the blocking oscillator / over-wound amplifying stages principle. It is of moderate power consumption (6.3 volt, 8 amp. filament and approx. 59 mA. H.T.) and contains three BVA valves. Output obtainable ranges from 6kV to 9kV with normal H.T. rail input but somewhat higher outputs can be obtained with higher H.T. supply. Valve rectification is employed in the output stage. The dimensions are 6 1/2 x 4 1/2 x 7 1/2 in. Price 69/6, post, packing, etc., 5/-.


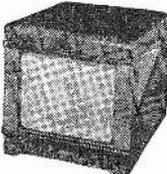
## CABINETS 19/6

You can make an excellent bass reflex cabinet with this well-made veneered and polished walnut cabinet. Limited quantity offered at 19/6. Carriage, etc., 3/6.



## A SIGNAL GENERATOR FOR BAND III

A Signal and Bar Pattern Generator complete with calibration equipment, 25/-, post free.

With the inception of Band III the home constructor is working on new ground and accurate checking instruments are a MUST!

The "ELPREQ" Band III SIGNAL GENERATOR is the very efficient and inexpensive answer. It:

1. Will provide the signal for tuning to any Band III station.
2. Can be used as a grid-dip meter for checking the frequency of Band III TV aerials, coils, etc.
3. Can be made to give a pattern on TV Receiver screen.
4. Can be accurately calibrated with included equipment.

All the parts including valves, tuning condenser and metal chassis are available as a Kit at 25/-, post free. Constructional data free with Kit or available separately price 2/6.




## BETTER VIEWING with NOVASPEX

It is a scientific fact that aperture size controls glare and increases depth of focus and our newly patented NovaspeX adapts this principle to TV. They definitely:

- Improve contrast and definition.
  - Sharpen focus, increasing picture depth.
  - Banish eye-strain and headaches.
  - Suppress incident light.
  - Permit comfortable viewing in total darkness.
- NovaspeX are as comfortable as sun-glasses. Send your order today and enjoy better TV tomorrow. Price only 6/6 post free. Full money back guarantee.
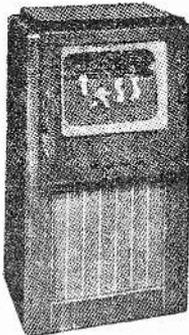
## A FEW REMAIN

This cabinet is offered below cost. It is suitable for a television using tube sizes varying from 12in. to 17in. Its overall dimensions being 31.5in. high, 1ft. 4in. deep, 1ft. 10in. wide. It is complete with plywood back and "Bowler Hat." Originally made for a very expensive television and really good quality. Unrepeatable. Offered at £6.19.6 carriage, packing, etc., 12/6. Note: These are cut for 12in. tubes, but the holes for the controls are not drilled.



## TUBES ALL SIZES

All makes repaired at a little over half price—SIX MONTHS' GUAR.

## STOP PRESS BAND III CONVERTER KIT


suitable for any type of TV. £3.10.0 complete. Instructional data available separately for 2/6 p. free

## THIS MONTH'S SNIP

Mains Transformer and choke by Haines Radio, Ltd. Standard 50 cycle input with 10 volts tappings. Secondaries 500-0-500 volt at 500 milliamperes and 6.3 volt at 6 amps., also choke to match 10 Henry's at 500 milliamperes. Limited quantity only at 45/- the pair. Carriage and packing 5/- extra.
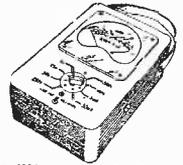
## NOW AVAILABLE A.C./D.C. MULTIMETER KITS


We can now offer a kit of parts suitable for making a multimeter to measure A.C. volts as well as



D.C. volts, milliamms and ohms. Price for kit containing all the essential items including moving-coil meter, metal rectifier, resistors, range selector, calibrated scale, etc., etc., is 19/6, plus 1/- post and packing. The D.C. only version is 15/-, plus 9d. post and packing.
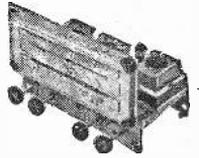
## THE CLEVELAND ORGANTONE

5 valve 3 waveband superhet covering Long, Medium, and Short waves. Osram miniature valves—low loss



iron coils—permeability—tuned I.F.S.—full A.V.C.—variable negative feedback—gram. position—4 watts output—particularly fine tone. Chassis size 7 x 7 x 7 approx. Tested in difficult areas where exceptional results have been obtained. Price £11.10.0 or £3.16.0 deposit. Carriage, etc. 7/6.

## GREATLY REDUCED CATHODE RAY TUBES

VCR97. Brand new and unused, "cut off type," ideal for 'scope, etc. Price 12/6. Carriage and insurance 5/- extra. Ditto but full picture type for TV 39/6, plus carriage 5/-.

VCR517. 6 1/2 in. guaranteed full picture, 39/6, plus 5/- carriage and insurance.

VCR139A. 2 1/2 in., 32/6, plus 2/6 carriage, etc..

VCR138. 3 1/2 in. electrostatic short persistence, suitable for TV and ideal for 'scope work, 37/6, plus 3/6, carriage etc.

VCR112. 5in. electrostatic, persistence not known, 15/- each, plus 5/- carriage, etc.

CV996. 6in. electrostatic, persistence not known, 15/- each, plus 5/- carriage, etc.

CV1140, CV1590, CV1546. All 12in. magnetic long persistence, £4.10.0, plus 10/- carriage.

## ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to Dept. 5, RUISLIP.

Personal shoppers, however, can call at:

- |   |   |  |  |
|---|---|--|--|
| 42-46 Windmill Hill, Ruislip, Middx. Phone: RUISLIP 5780 Half day, Wednesday. | 152-3, Fleet Street, E.C.4. Phone: CENTRAL 2833 Half day, Saturday. | 29, Stroud Green Road, Finsbury Park, N.A. Phone: ARCHWAY 1049 Half day, Thursday. | 249, High Road, Kilburn. Phone: MAIDA VALE 4921. Half day Thurs. |
|---|---|--|--|

# BUILDING THE "SIMPLEX"?

Thousands of enthusiasts are building the "Simplex" Television, now being featured in "Practical Television." WHY NOT YOU? **CONSTRUCTOR'S ENVELOPE** containing full constructional details and Blue Print, additional notes and suggestions, and Query Service form, sent for **ONLY 5/-**. All components available ex stock as follows:

**ALUMINIUM CHASSIS.** — 18 s.w.g. DRILLED, for VCR97 version with screens and tube holder bracket, 22/6.

**TRANSFORMER.**—350-0-350 v. 150 ma. 6.3 v. 5 a., 5 v. 3 a. tapped at 4 v., **ONLY 37/6.** (Postage 2/-.)

**CLOKE.**—10 h. 120 ma., 10/6. (Post 1/-)

**RECTIFIERS.**—RM3 5/- ea., K3/40 6/- ea. VALVES.—EF50 6/6. SP61 4/-, 6SN7 9/-, 6J5 5/6, 6BM 8/6, EA50 3/6.

**VALVEHOLDERS.**—B9G/EF50 10d., I.O. and M.O. 6d., Diode (EA50) 6d., VCR97 2/6.

**VCR97 TUBE.**—Tested full screen, 42/6.

**CONDENSERS.**—Electrolytics 25 mfd. 25 v. 1/10, 16 x 8 mfd. 450 v. 5/6, 32 x 32 mfd. 450 v. 6/-. Mica, silver mica, and tubulars, 350 v. 6d. each.

**POTENTIOMETERS.**—All values, pre-set 1/9 each, long spindle 3/-. with switch, 4/6.

**RESISTORS.**— $\frac{1}{2}$  watt 4d.,  $\frac{1}{4}$  watt 5d., 1 watt 6d., 1.5 k. 5 watt, 1/6.

**COIL FORMERS.**— $\frac{1}{2}$  in. 8d.,  $\frac{1}{4}$  in. 10d.

**SPEAKER.**—5 in. P.M. less trans. 16/6 (postage 2/-).

**O.P. TRANSFORMER, 5/-.**

All Components, Brand New and Unused. Full Price List available on request.

## VALVES

1G6	6/6	7A7	8/6	5Z4	10/-
1E7	6/6	7C5	8/6	5U4	10/-
1LH4	8/-	7F7	8/6	6AC7	6/6
1LN5	8/-	7W7	8/6	6K7GT	5/6
1L4	7/6	12H3	8/6	807	7/6
2B7	8/6	12J5	6/-	ECH35	12/6
3A4	9/-	12A7	12/6	EA50	3/6
3B7	8/6	12S7	7/6	EBC33	8/6
6AG5	7/6	12SK7	8/6	EB34	3/6
6AK7	9/6	12SR7	7/6	EF33	6/6
6B4	7/6	8-25D7	7/6	EF39	6/6
6B8	7/6	8-32	7/6	EF50	6/6
6C8	8/-	9-35	7/6	.. Red	
6G6	6/6	9-50Y6	8/6	Sylvania	8/6
6H6	5/-	58	8/6	EF91	12/6
6K6	9/-	1622	11/-	EF51	15/-
6L7	7/6	1626	4/-	EK32	6/6
6N7	7/6	1299A	7/6	EL32	7/6
6R6	8/6	VR150/30	8/6	SP61	4/-
6U5	8/6	VR137	5/9	MU14	10/6
6V6	8/6	KT44	8/6	RL37	6/6
6V6GT	8/6	KT2	5/-	VS70	7/6
6SA7	8/6	VP23	6/6	855	6/-
6SA7	8/6	HL33DD	6/6	853	6/-
6SH7	7/6	TP25	8/-	903	6/-
6SJ7	8/6	1S5	8/-	904	6/-
6SK7	7/6	1T4	8/-	901	6/-
6SL7	9/-	1R5	8/-	931A	50/-
6SS7	7/6				

**R.F. UNIT'S TYPE 26 and 27.** For use with the R.1355 or any receiver with a 6.3 v. supply. These are the variable tuning units which use 2 valves EF54 and 1 of EC52. Type 26 covers 65-50 Mc/s (5-5 metres), and Type 27 covers 85-65 Mc/s (3.5-3.0 metres). Complete with valves, and BRAND NEW IN MAKER'S CARTONS. **ONLY 29/6 each.**

**CHASSIS OF INDICATOR 233.**—Contains VCR97 C.R.T. holder, 11 valveholders, resistors, condensers, etc. etc.. **BRAND NEW. ONLY 10/-** (carr., etc., 5/-).

**E.H.T. TRANSFORMER.**—Normal 230 v. Primary, with Secondary of 2,000 v. r.m.s. (approx. 2,800 v. D.C.). A special offer of interest to all using the VCR97 or similar tube. Size 2 1/2 in. W. x 2 1/2 in. D. x 3 in. H. + 1 in. for tag panel. **AN UNREPEATABLE SNIP,** and well worth buying as an insurance against failure of existing E.H.T. supplies. **ONLY 15/-** (postage, etc., 2/-).


**TRANSFORMERS.**—Manufactured to our specifications and fully guaranteed. Normal Primaries, 425-0-425 v. 230 ma. 6.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a., **ONLY 65/-**; 350 v. 0-350 v. 160 ma., 6.3 v. 5 a., 6.3 v. 3 a., 5 v. 3 a., **ONLY 47/6**; 250 v. 0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., **ONLY 37/6**; 350 v. 0-350 v., 150 ma., 6.3 v. 5 a., 5 v. 3 a., **ONLY 37/6**; 250 v. 0-250 v. 80 ma., 6.3 v. 3 a., 5 v. 2 a., **ONLY 21/-**. The above are fully shrouded, upright mounting, 5.5 kV. E.H.T. with 2 windings of 2 v. 1 a., **ONLY 79/6**; 7 kV. E.H.T. with 4 v. 1 a., **ONLY 89/6**. PLEASE ADD 2/- POSTAGE FOR EACH TRANSFORMER.

**PYE 45 mc/s I.F. STRIPS.**—The strip that is ready made for the London Vision Channel. Complete with 6 valves EF50 and 1 of EA50. **BRAND NEW. ONLY 59/6.**

Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn (Chancery Lane Station); 5 mins. by bus from King's Cross. Cash with order, please, and print name and address clearly. Include postage as specified and on Component Orders under £2.

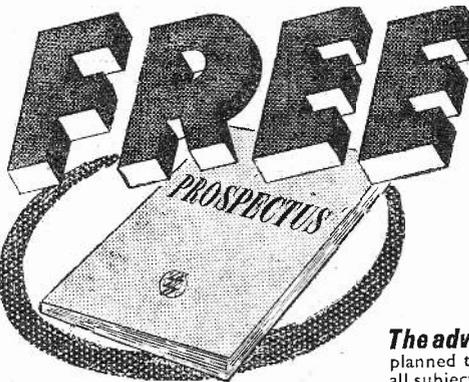**U.E.I. CORPN.**

THE RADIO CORNER, 138, GRAY'S INN ROAD, LONDON, W.C.1 (Phone TERMINUS 7937.)



**POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES**

**PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME**

City and Guilds Grouped Certificates in Telecommunications: A.M.Brit.I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

**The advantages of E.M.I. training.** ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

Equipment supplied upon enrolment and remains your property.

Courses from 15/- per month

**POST THIS COUPON TODAY**


Send without obligation your FREE book. E.M.I. INSTITUTES, Dept. 138K, 43 Grove Park Road, London, W.4.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

6/55 SUBJECT(S) OF INTEREST \_\_\_\_\_

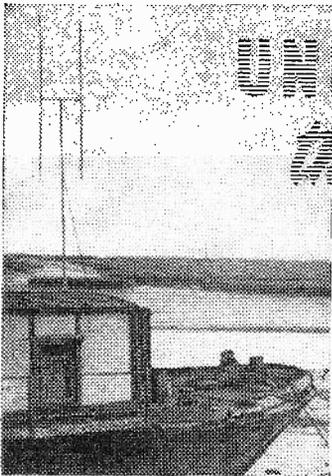**EMI INSTITUTES**  
The only Postal College which is part of a world-wide Industrial Organisation.



# UNDERNEATH *the* DIPOLE

TELEVISION PICK-UPS AND  
REFLECTIONS

By *Iconos*

of steady consolidation in other branches of show business. No wonder the national advertisers are getting all steamed up about sponsored TV in Britain.

## LAUGHTER THE ATTRACTION

**I**F it's laughter you're after . . . " was Tommy Trinder's publicity catch-phrase a few years ago. To-day, it seems to be an appropriate slogan for almost any kind of entertainment—theatre, radio, films or TV—which is destined to click with the audiences. The general public seems to laugh easily and eagerly at the moment and responds to any feature-title which shows promise of laughter, particularly when it is coupled with the name of a star comedian.

## "ASKEY-ITIS"

**B**EFORE *Your Very Eyes*, with Arthur Askey, has now finished its run but has established the Big-Hearted Arthur as the finest TV comedian in England; his timing of gags, impromptu chit-chat to viewers, easy, relaxed style and excellent diction all add up to his complete mastery of the extremely difficult technique of being funny in front of the television camera. Sabrina, the dumb blonde of the show, was put into the series as a "gimmick" by Bill Ward, the producer, with the astonishing result that she is now in demand for personal appearances at sporting events, for films and for stage work. She will continue to puzzle us with her extraordinary Robey-ish eyebrows which, I am told, are the new fashionable style. This comedy series will have broken new ground by creating a new starlet, starting a new fashion and consolidating the reputation of Arthur Askey. We've all got Askey-itis now and his name soars to the top. Such is the impact of TV; it achieves in two or three shows the same progress as years

## MRS. SHUFFLEWICK

**A**NOTHER name which has shot to the top of the music hall bills as a result of a TV series is Mrs. Shufflewick, the "gimmick" of the Ralph Reader show, *It's a Great Life*. Mrs. Shufflewick is the name which has been adopted by Rex Jameson, a first-class comic dame in pantomime style. The Shufflewick interruptions of the Reader Show were amusing and I thought that Rex Jameson made the most of rather poor dialogue material. Comedy scripts are not easy to write but usually take the form of presenting old, well-tried chestnuts in a new shape. The introduction of catch-phrases, character stooges and gimmicks, if successful in the first episode of a comedy series, definitely builds up goodwill for subsequent instalments. Even the introductory music to a feature can create anticipatory laughter—for instance, the title music of early Laurel and Hardy films, seen occasionally (not often enough!) on television.

## SUNDAY NIGHT GLOOM

**S**UNDAY night is a peak viewing time. The BBC's ace TV drama producers are given their heads, and the result seems to be either horrific or merely boring. Rudolph Cartier, whose skilled direction has been devoted to quite a few of the full-length Grand Guignol-type plays, changed his style to some extent in "Midsummer Fire," a play by Hermann Suderman, translated by Ashley Dukes. The TV version sets the piece in modern Mexico instead of in East Germany eighty years ago, as originally written. The modernising pep-up (which seems

to be applied to most plays written more than twenty years ago) fails to sustain the piece, in spite of good performances by such experienced TV players as George Coulouris, Laurence Payne and Jeannette Sterke. It seems to me that when adapting old three- or four-act plays for television, the transposition should concentrate upon shortening the playing time from ninety minutes to sixty or less. The speeding-up process should be achieved by deletions rather than by speeding up the dialogue delivery. An American TV producer visiting England said of British actors: "They talk too fast and move too slowly." There is a great deal of truth in this criticism, though the effect of too-speedy a delivery is often achieved by poor diction, heavy dialect, or the ultra-natural throwing away of lines. In due course, recorded versions of our television plays will be exported to the U.S.A., Canada and elsewhere. It will then be necessary for the dialogue to be easily understood internationally. These remarks do not particularly apply to "Midsummer Fire," which played its full hour-and-a-half for those who stayed to its end, but to dramatic plays in general.

## "FABIAN OF SCOTLAND YARD"

**T**HE half-hour episodes of Fabian's adventures, made in England primarily for American Television, are models of the type of presentation suitable for the international market. Bruce Seton is a most convincing detective and each story is well-worked out and played, partly with commentary and also with directly-recorded scenes. "The Executioner" was a very good example of a taut half-hour's "who-done-it" entertainment. I understand that the producers turn out two "Fabian" films a week at the Twickenham Studios. This is fast going for this type of feature, which required specially built settings as well as exterior scenes. Compare any "Fabian" episode with some of the BBC 90-minute dramas which play in one or two sets. Each Fabian episode must have at least eight sets, though some of them are quite small and others, such as the Scotland Yard Offices, are used again and again. The ingenuity of the Art Director in arranging for "revamps" of sets in a few hours, changing drawing-rooms into kitchens and such-like,

is a most important factor in this type of production, and can save hundreds of pounds in costs.

### TELEVISION LIGHTING

**T**HE Video-Film camera is likely to be taken up by several of the American TV organisations. Nevertheless, it will be appreciated that a higher level of lighting is usually necessary for filming as compared with live television; and when a combination of both methods is used, sufficient light is required for film photography. This level is particularly high for colour photography, sometimes requiring intensities of up to 1,000ft. candles as compared with less than 100ft. candles for electronic cameras. In practice, rather more light than 100ft. candles is used in TV studios, and the difference is not so great with black-and-white film photography. There would, therefore, seem to be a definite place in this complicated business for the Video-Film type of camera, of which a great deal will be heard in the next few months.

### THE VIDEO-FILM CAMERA


**A**MERICAN technical magazines carry advertising for dozens of equipment companies offering all kinds of gadgets as aids to television production, either live or on film. Camera dollies of all varieties, magnetic recorders, special types of lights, microphone booms and other impedimenta crowd the pages. One of the latest innovations is the Video-Film Camera, which is capable of transmitting a live image via TV and at the same time photographing on 35 mm. film the same picture. The scene is picked up by the normal camera lens, one of three of different focal lengths mounted in a turret, which transmits it to a normal film gate. Between the lens and the film, however, a beam-splitter is interposed which diverts a proportion of the rays to a vidicon tube contained in the camera. There is an electronic viewfinder inset in the back of the camera, enabling the operator to see the actual scene transmitted and filmed, and duplicate outlets feed monitor tubes for the producer or others. The camera is, therefore, two cameras in one—a film camera and a television camera. It is being used at present for filming the Burns and Allen weekly show and the popular *I Love Lucy* feature, the electronic

side being used, for the time being, mainly to assist the producer in cutting-in and out the appropriate cameras when required. The image seen by the camera operator is exactly the same as that filmed, since it is picked up through the same lens, and is not subject to the parallax troubles experienced with the normal separate viewfinder attached to the side of the camera. Producers also appreciate that they can spot any errors immediately, without having to wait for the film rushes to be processed and printed. They are able to instruct the operators and grips, via an intercommunication system, as to camera movements with the same accuracy as with live TV camera set-ups. Naturally, the camera is somewhat larger than either a TV or a film camera, and has to be fitted with a sound-proof blimp.
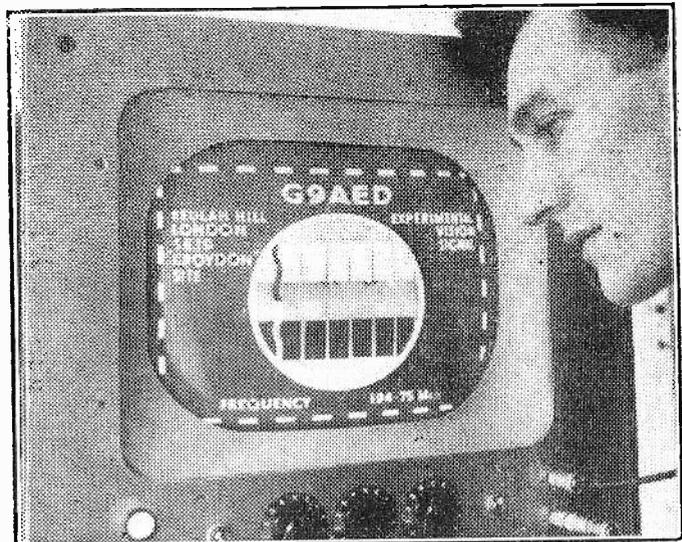
### 16 mm. OR 35 mm. ?

**E**VER since the commencement of BBC television the film side has been standardised on 35 mm. film for picture and variable area photographic recording for sound. In the course of time magnetic recording has been introduced in 35 mm. perforated form and also on magnetic tape which is used on exteriors when extreme mobility is required. Synchronisation of tape with picture has been maintained by recording a time-

base signal from the picture camera motor on the tape at the side of the sound recording. This is used as a speed reference when the tape recording is re-recorded on to photographic film. Such use of twin-track tape recording is now in general use by film studios as well as the BBC on the Leavers Rich Synchronpulse recorder. On the picture side the 35 mm. standard has been maintained because of the greater ease in scanning and telerecording. But now the problems of 16 mm. film scanning have been tackled and the considerable economies to be obtained are likely to bring about changes of technique both here and in the U.S.A. Colour television is now in commercial use in America and it has been found that the cost of film stock and processing of Kodachrome 16 mm. film is precisely one tenth that of 35 mm. Eastman Colour. Consequently, there has been a very rapid development in 16 mm. work. Some of the most popular weekly commercial features, such as the Hank McCune Show, are now filmed in 16 mm. colour, using a new combined sound-and-picture camera, the Auricon. Kodachrome is a reversal film stock, however, and if more than one copy is required, duplicate 16 mm. negatives have to be printed, during which process the sound track is likely to suffer degradation unless it is re-recorded electrically.




Engineer Mr. C. F. Whitbread, of Edmonton, London, examines the monitor screen in the experimental test station on the I.T.A. site at Croydon, during a broadcast of test signals.

# MAKING A TEST METER

BUILDING A UNIVERSAL INSTRUMENT ROUND AN EX-GOVERNMENT VISUAL INDICATOR UNIT


By P. Green

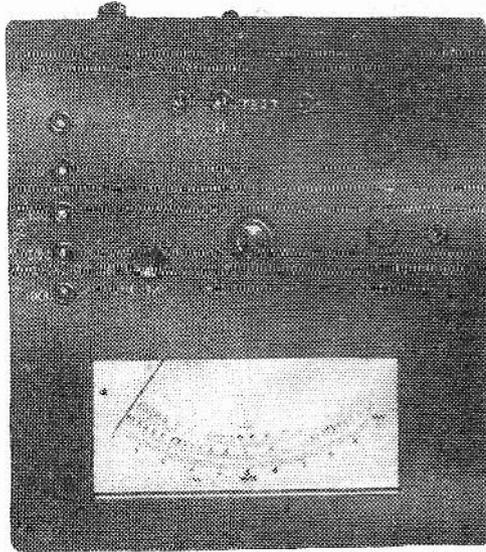

Front view of the finished meter.

A RELIABLE test meter is an essential piece of equipment to any amateur who intends to build his own radio or television receiver. From surplus supply stores instruments containing good moving-coil movements may be obtained, and these may be modified and used to make a good test meter. Visual indicator type 3 (10Q4) is one, and may be obtained for a few shillings. The writer recently bought six of these for a shilling each, and all have

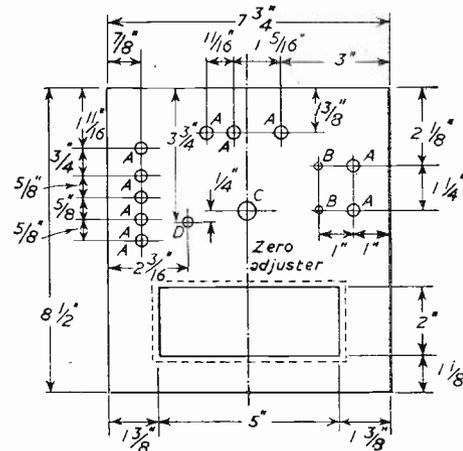been used to construct the meter described. There seems to be a good supply of them, and a practical description of how to adapt this fine movement of approximately 500 microamps F.S.D. to make a test meter may be of interest to others. The movement



- Holes A Drill for sockets
- B " " Terminals
- C " " Tooth past tube top
- D " " Switch

Fig. 1.—Details of the plywood top of instrument.

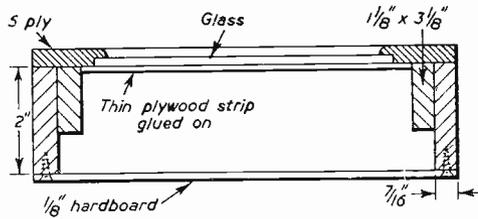


Fig. 2.—Section through case.


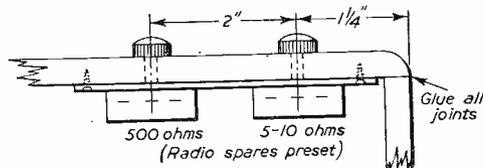


Fig. 4.—Corner of case showing potentiometers.

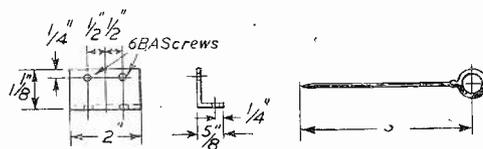

1/16 Thk. ALUMINIUM

No 24 (.022") S.W.G. STEELWIRE


Fig. 5.—Movement support.

Fig. 6.—Tool for pointer.

used is the vertical one. The other, a centre zero movement, is not suitable, although this may be used to make a light or exposure meter.
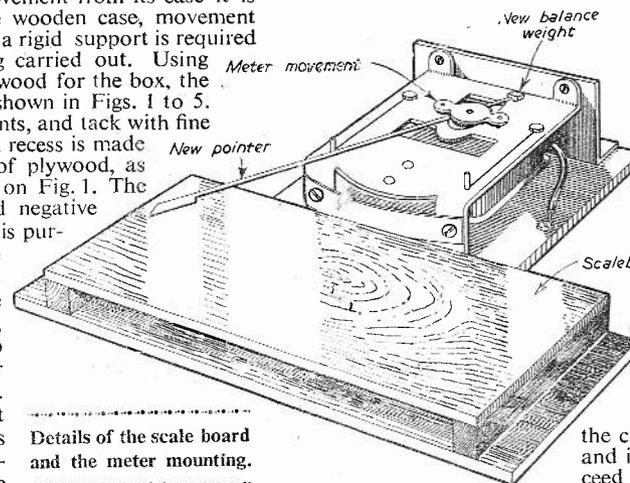
### Construction

Before removing the movement from its case it is advisable to construct the wooden case, movement support and scaleboard, as a rigid support is required while other work is being carried out. Using clean 5-ply wood and baywood for the box, the constructional details are shown in Figs. 1 to 5. Use "cold" glue on all joints, and tack with fine sprigs. For the window, a recess is made by removing two layers of plywood, as shown by the dotted line on Fig. 1. The glass is cut from an old negative plate, which is ideal for this purpose as it is thin and free from flaws. To fix the glass peel off from a spare piece of plywood the top layer, sufficient to make a strip 1/2 in. wide. Glue down over the glass as shown in Fig. 2. A little Bostik cement round the edges of the glass will make a seal. It is important to keep the case



Details of the scale board and the meter mounting.

dustproof, and to keep metallic particles away from the movement.

### Dismantling

When all the parts are ready, remove the movement from its case, handle carefully, and mount on the angle bracket on the scale board with 6 B.A. screws. Now snip off the end of the pointer with a razor blade, using a piece of wood under the pointer as an anvil. This leaves the pointer 1 1/4 in. long from the centre of the movement. Now to start experimenting in making an extension pointer. First, make a wire tool (Fig. 6)


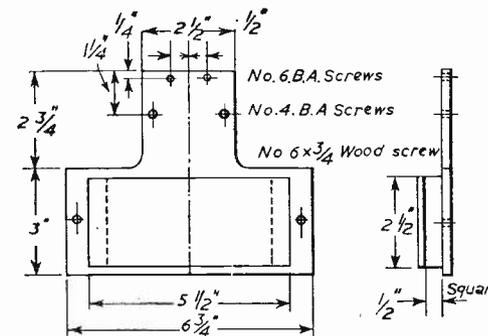


Fig. 3.—Details of the 5-ply support and scale board.

from a piece of steel wire 0.022, 24 s.w.g. The new pointer is made from thin aluminium foil removed from an old electrolytic condenser; the thickness of which will be anything from .0018 in. to .0025 in. thick. Cut strips 5/64 in. wide (.002 in. thick approximately). These strips are now bent round the wire to make a tube, and after a little practice you will be able to make quite good pointers. When you have been successful, draw 3/4 in. of the tube off the wire; flatten out this end by scraping with a penknife; trim with scissors and cut down to a length of 2 7/16 in. Now carefully push this extension piece on to the movement pointer for approximately 1/4 in. The total length from centre of the movement to be 3 7/16 in. Fix with a little Durofix.
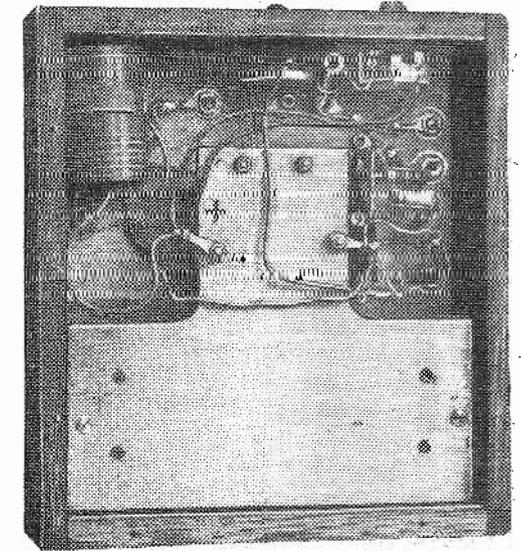
### Balancing the Movement

The meter will now have to be re-balanced. The pointer of a perfectly balanced instrument will return to zero when the case is placed on any of its sides, and it is by this method you can proceed to balance your instrument. First



Inside details of the meter.

wind on the wire tool about six turns of 36 s.w.g. copper wire. Place this on the stub end of the pointer. You will note there is already one on but do not attempt to remove this, as you may damage the movement. Having placed the additional weight, which will fit, loosely proceed to place the instrument on all its sides and note how the pointer behaves. You will be able to judge if the weight is too light or too heavy, and will have to make your adjustments to suit. When sure your instrument is well balanced fix the weight with a little Durofix.

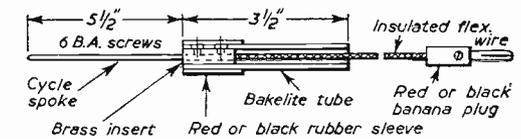


Fig. 7.—Details of the prods.


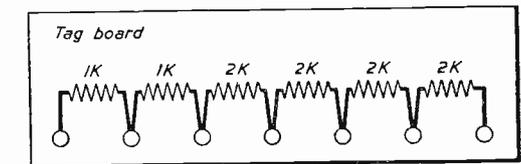


Fig. 8.—Check panel for high range.

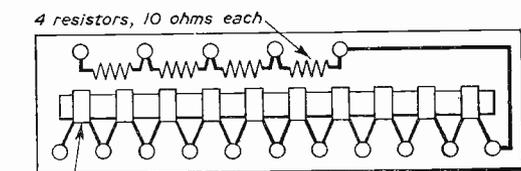

10 coils, 1 ohm each (27" of 40 s.w.g. copper wire wound on bakelite tube)

Fig. 9.—Check panel for low range.

### The Scale

The scale can now be attached to the scale board, but do not stick down with glue or paste as this will warp the scale. Fix round edges with cellulose tape. Solder the instrument leads now to the heads of the 4 B.A. brass screws, and this part of the meter is now finished.

Proceed to fit the sockets and terminals in the meter case, using a solder tag at each one. Fix also the 500 ohm and 5 to 10 ohm potentiometers (Fig. 4) and the switch for changing over the resistance ranges.

### Calibration

The voltage ranges can now be calibrated, and new batteries may be used to carry out the tests. As the movement gives a linear scale adjust the resistances to

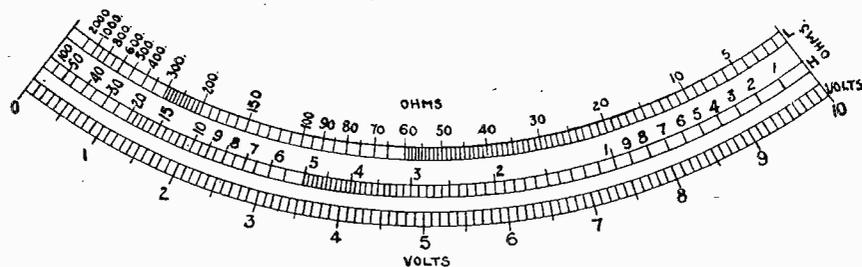


Fig. 11.—Circuit of the meter.

error" method must be used for the meter to read correctly on the low-resistance scale.

External shunts are used for current readings and connections are brought out from the meter move-

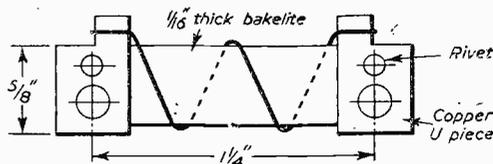


Fig. 10.—Details of the shunts.

ment to two large terminals, which are then connected to the sockets. The method of making the shunts

This scale may be cut out and stuck to the scale board. It is accurately drawn for this instrument.

suit one voltage reading, say 6 volts on the 10 volts range. Similarly choose a suitable voltage for the other ranges. Sometimes a resistance is found that will give a correct reading, but a combination of two chosen resistors in series or parallel will give the reading required. For each range an approximate value is given in the diagram. All resistors are 10 per cent. tolerance. When calibrating it is an advantage to have a number of the same kind of resistors, and also a few very high ones, viz.  $\frac{1}{2}$ ,  $\frac{2}{3}$  and 1 M  $\Omega$ . Figs. 8 and 9 show two panels which may be used to check the resistance ranges. The 2,200 ohm resistor and the 500 ohm potentiometer for the high resistance scale are not critical, but the low resistance range is rather critical of adjustment, and a total resistance of approximately 50 ohms is required. The potentiometer Y in the diagram should be 5 to 10 ohms; the resistor X must be self-wound, and "trial and

error" method must be used for the meter to read correctly on the low-resistance scale. Testing prods may be made as shown in Fig. 7.

Socket and plug connections have been used which give "at a glance" safety positions, but if the constructor desires he may incorporate switches. No attempt has been made to provide a laboratory meter, but a useful and practical instrument which will meet any amateur constructor's requirements.

## Viewer Research

LATEST Viewer Research figures issued by the BBC reveal the following interesting details:

Average level of evening viewing among the whole adult population of the United Kingdom (approx. 37,600,000 persons):

	% of the adult population
January-March, 1955 ... ..	14.9
January-March, 1954 ... ..	11.5

Average level of evening viewing among the "television public":

	% of the "television public"
January-March, 1955 ... ..	43.8
January-March, 1954 ... ..	45.0

The increase in the size of the audience for the average broadcast on television in the evening from 11.5% to 14.9% of the adult population closely parallels the increase in the number of TV sets in use.

In January-March, 1955, the average audience of evening television broadcasts included 43.8% of the (enlarged) TV public; the corresponding figure for January-March, 1954 (when the TV public was appreciably smaller) was 45.0%.

# T.R.F. RECEIVERS

THERE IS NO NEED TO SCRAP OLD-PATTERN SETS AS EXPLAINED HERE

By W. J. Delaney

A QUERY which we are often receiving to-day is whether or not a T.R.F. receiver should be scrapped, or whether it is possible to modify it for the reception of the I.T.A. programmes. Most television receivers of this type were designed in the very first days of television, when the only station on the air was the London transmitter, and this, unlike the remainder of the BBC transmitters, uses double-sideband transmission. Further, at that time, the 9in. tube was in general use, and thus these receivers will not be very useful to-day unless they have been modified to take a larger tube. However, many viewers are quite content with this size of picture and it is quite conceivable that the majority of users of this type of receiver would prefer to retain it. The problem is, however, what can be done about the I.T.A. programmes when they commence. It will be appreciated that in a superhet the majority of the tuned circuits are pre-set to one frequency and, so long as the frequency changer is tuned to the required station and the oscillator coil is suitable, the set can be tuned to any station quite easily. In the T.R.F., however, it becomes necessary, if another station is required, to retune all the coils, and this is impracticable. Does this mean, then, that receivers of the T.R.F. pattern must be scrapped, or the user restricted to only one station? Fortunately, there are solutions to this problem, although they are not simple.

### Conversion

First, of course, the entire circuit may be redesigned to use a superhet arrangement. This would, of course, be a major reconstruction, and in receivers of the type of the P.W. Receiver might also call for a modification in the layout, as the coils are all unscreened and instability might arise with the higher efficiency and gain of the superhet. One could, however, replace the coils in the final stages by screened components of modern design and rearrange the first two stages. The first stage would be left in its original form to act as an R.F. stage, with the second converted into a frequency changer. As the custom was sometimes to take the aerial to both sound and vision (no common stages), this would mean that there would be a need to change the input circuit to the sound section and feed this from the frequency changer in the usual way. The result of this might be to provide too much sound, and the possibility would then have to be explored of using the first sound stage as a separate oscillator to work in the frequency changer circuit. This might avoid the necessity of purchasing new valves, but much will depend upon those which are in use in the existing circuit. Alternatively, it might be found that the circuit which is now being used would, on conversion on the lines above mentioned, provide insufficient amplification at the I.F. for the vision, and perhaps, therefore, one of the sound stages could be rearranged to add to the vision I.F.

### Sound Rejection

The T.R.F. circuit would, undoubtedly, have sound rejector circuits in it, and these, too, would have to be replaced by suitable rejectors at the sound I.F.

It will be seen, therefore, that there would be a fair amount of work involved in modifying a T.R.F. set for modern two-station reception, but such a rearrangement of parts would be advisable in many cases. Of course, there is also the question of redesigning the timebases at the same time, to take advantage of the larger tubes which are now available, and if this is considered worth while, the entire receiver would practically have to be rebuilt, and in such a case it would no doubt be thought desirable to start by building a completely new design. A market for the old receiver would no doubt be difficult to find, but as a second transmitter becomes available the market will undoubtedly grow smaller, and therefore the user of this type of receiver has to consider seriously now, what may be done.

### An Alternative

In addition to the modifications which have been outlined above, there is one very useful alternative which might eventually prove the most satisfactory way out. Converters for the new commercial stations will shortly be available and will be described in these pages, but in most cases they will consist of frequency changers designed to cover one Band I and one or two Band III stations, and the output from such converters will be at the now more or less standardised I.F., round about 34 Mc/s. This output if normally intended for connection to the I.F. stages of existing television receivers, and most commercial models which have been produced during the recent period have been provided with input arrangements to enable this to be done. The home-constructed models will, however, have no such provision, and therefore any such converter which is used will have to be designed for the I.F. which is employed in the receiver, and then the latter will have to be modified so that the input may be applied at a suitable point. The T.R.F. receiver which we have been discussing, however, will offer a more useful application in this connection, as it will only be necessary to retune the existing coils to the I.F. output of the added converter. If the coils permit, it might be possible to do this merely by changing the cores or, alternatively, the converter may be designed to provide an output at the same frequency as is used in the existing receiver and merely to use the latter as an I.F. amplifier. The big problem which will arise in many cases, however, will be the production of patterns on the screen due to the existing receiver picking up one of the transmissions on its wiring. The older type of receiver was not so comprehensively screened as modern models, and in areas which are close to one of the stations not only the coils but also the actual wiring may function as miniature aerials and pick up the unwanted signal, resulting in either a background pattern on the screen or cross-talk on the sound side. This trouble may, indeed, arise even in some modern commercial receivers, but this will depend upon the proximity of the transmitter, the reception conditions, and whether or not the aerial(s) and leading-in cable are suitably disposed.

# Frame Flyback Suppression—3

SOME CIRCUITS FOR THE EXPERIMENTER

By "Erg"

(Continued from page 567, May issue)

ASSUME that the circuit is once again stabilised so that anode and cathode potentials are equal. Now if a negative pulse is applied to the cathode current will flow in the circuit for the duration of the pulse. The current will cause a voltage drop across the anode load R, and the

Fig. 12 shows one method as applied to the Simplex electrostatic model. If this is compared with Fig. 9 it will be seen that the same basic principles are retained, but a diode is inserted between the frame oscillator and the cathode of the tube. VRa is adjusted so that the diode passes no current.

Now during the forward stroke, when the scan is negative going, the diode will not conduct due to the fact that the anode is driven in the negative direction. However, when the flyback pulse occurs the diode is driven positive at the anode, it conducts, and the positive pulse appears at the cathode of the tube.

One defect of the arrangement is that the potential applied to the cathode of the diode is dependent upon the setting of the brilliance control. A rather more elegant way of doing the job would be to feed the cathode from a separate potential divider. This need not be variable, but can be fixed, VRa being retained for adjusting the point at which the gate operates.

The refinement is shown in Fig. 13.

It is possible to apply the method to a cathode-modulated C.R.T. by reversing the diode action so that a negative pulse only is passed.

A typical example is given in Fig. 14, which shows the system applied to the Lynx television.

In this case the frame scan is positive, the flyback being negative. The flyback is connected to the diode via C, which is the same as C in Fig. 7. VRa is adjusted in the first instance so that no current flows through the valve. During the forward stroke the cathode is made positive and the diode does not conduct. During the next part of the cycle the fly-back which is nega-

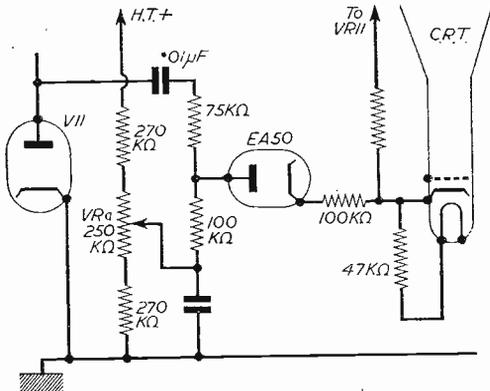


Fig. 12.—Details of the "Simplex" with diode gate.

voltage at the anode of the valve will be less than it was previously. In other words, the anode moves in a negative direction. The negative pulse at the cathode has produced a negative pulse at the anode and this can be passed on to a circuit via the outlet B.

Should a positive pulse be applied to the cathode, then no current will flow through the valve, and therefore no positive pulse will be felt at the anode and no pulse appears at outlet B.

The diode gate can be reversed quite easily so that it will pass a positive pulse and not a negative one.

In this case let us assume that the circuit is balanced and no current flows. Now apply a positive pulse to the anode; this will cause the valve to pass current which will be drawn from the cathode. The current will be drawn from the circuit attached to the point A and there will therefore be a positive pulse at point A.

Summarising, a diode gate used for negative pulses has the cathode as input and anode as output; a diode gate used for positive pulses has the anode as input and the cathode as output.

### Practical Application

Now let us see how this useful feature can be applied to our suppression circuit.

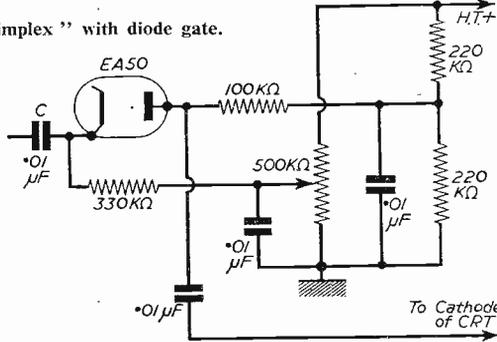


Fig. 15.—Diode with separate potential divider.

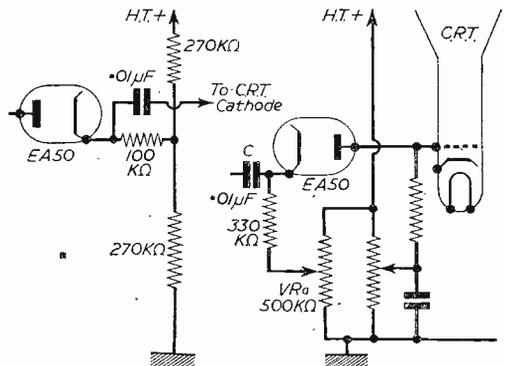


Fig. 13 (left).—Modification of Fig. 12. Fig. 14 (right).—Diode gate fitted to the Lynx.

tive is applied to the cathode of the diode; the anode therefore becomes more positive than the cathode, current will flow, and in the manner explained previously the pulse will appear on the grid of the C.R.T.

As in the previous case, the operation of the diode will depend upon the setting of the brilliance control and to make the circuit independent of the brilliance the diode anode can be fed from a separate potentiometer network.

A suitable circuit is shown in Fig. 15.

It is not always necessary to provide blocking condensers on both sides of the diode. In some cases the diode can be directly coupled to the frame circuit, and a single potentiometer used for balancing the valve.

This method is shown clearly in the circuit given in Fig. 16.

### Conclusion

It will be appreciated that it has not been possible to test out the circuits given on every type of home-constructed television now on the market. The method

has been tried out in a mixed sample of models and has proved very satisfactory.

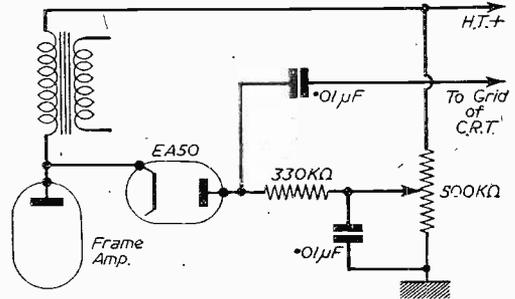


Fig. 16.—Directly-coupled gate.

It is hoped that the basic information given, coupled with the practical circuits and examples, will enable the constructor to adapt the principles to his own particular needs.

## TV in the Isle of Man

THE following statement was agreed by His Excellency the Lieutenant-Governor of the Isle of Man, the Lt.-Governor's Advisory Committee on Broadcasting, and the BBC, as the result of a meeting held on Thursday, April 14.

After consultation with His Excellency the Lieutenant-Governor of the Broadcasting Committee of the Isle of Man, and with their full agreement, the BBC has now decided its plans for the future development of television and sound broadcasting for the island.

### Divis Transmitter

The immediate situation is as follows: The temporary TV transmitter at Carnane, near Douglas, is giving a satisfactory service to about 60 per cent. of the island's population. In addition to this, a new permanent TV station has been erected at Divis, near Belfast. This station is expected to begin operating in July of this year, and it is hoped that it will give a satisfactory service to viewers living in the north of the Isle of Man, provided they are favourably situated and use good aerials. This transmission from Divis, together with the transmission from Carnane and also with the transmission already received in reasonable quality by viewers of Holme Moss direct, will mean that from summer this year the majority of the population of the island should receive satisfactory service.

Meanwhile the BBC has been searching for a suitable site on which to erect a permanent TV transmitter for coverage of the whole island.

### New Station on Snaefell

After considering and testing a number of alterna-

tive proposals, it became obvious that the summit of Snaefell would give an entirely satisfactory service to the island as a whole. Approval, therefore, was sought to build the new station there. The Ministry of Transport and Civil Aviation, for reasons of safety of life, was not prepared to grant permission for such a station to be erected unless the BBC could demonstrate by tests that no interference would be caused to the Ministry's transmitting and receiving station which is already operating on Snaefell. Two difficulties arose. For reasons of geography and other commitments, these tests cannot take place until early summer, 1956. Secondly, the Ministry reserves the right to close down the transmitters temporarily should the safety of aircraft be in danger. In spite of this, and having regard to the long-term welfare of broadcasting in the island, the Broadcasting Committee and the BBC are convinced that the advantages of the Snaefell site are over-riding and that the proposal to use this site should be pursued. This means that the necessary tests will be carried out early in 1956. Thus, dependent upon their success, the BBC confidently hopes to begin the erection of the permanent television transmitter on the Snaefell site immediately after. At the same time, in order to improve the island's sound broadcasting reception, the BBC proposes, subject to Post Office approval, to incorporate in the Snaefell site, three VHF-FM transmitters, designed to carry respectively the Home, Light and Third Programmes, as this site is also the only one which will provide an entirely satisfactory service for sound broadcasting in the island.

The whole project at Snaefell will be completed as quickly as transport and weather conditions permit.

The Entirely New 12th Edition of The Famous Standard Work

## THE PRACTICAL WIRELESS ENCYCLOPÆDIA

By F. J. GAMM

Considerably enlarged, amplified and entirely re-written and re-illustrated. Complete Television Section, with theoretical and constructional data.

All the facts, figures, and constructional data of Radio and Television—Definition, Terms—Units—Principles, Circuits, etc.

Over 300,000 copies sold Price 21/- or 22/- by post from:

GEORGE NEWNES, LTD., Tower House, Southampton Street, Strand, W.C.2.

# ARTHURS HAVE IT!

LARGE STOCKS OF VALVES AND C.R.T.s.

AVO METERS IN STOCK

Avo Model 7	—	—	—	£19	10	0
Avo Model 8	—	—	—	23	10	0
Electronic Test Unit	—	—	—	27	10	0
Electronic Test Meter	—	—	—	40	0	0
AC/DC Minor	—	—	—	10	10	0
★ Cossor Oscilloscopes Model 1052	—	—	—	104	0	0
				1049	—	—
				132	0	0

Full range Taylors Meters. List on request.

Leak—TL/IO Amplifier and "Point One"	—	—	—	—	—	—
Pre-Amplifier	—	—	—	Complete	28	7
F.M. Kit of parts £5 less valves. Ref. Radio Constructor July, 1954.	—	—	—	—	—	—
Jayson F.M. Tuner Unit	—	—	—	15	17	0
Chapman Tuning Units	—	—	—	from	16	0

LATEST VALVE MANUALS

MULLARD, OSRAM, & BRIMAR No. 5, 5/- each,  
 MAZDA 2/- each. Postage 6d. each extra.  
 SCOPE SOLDERING IRON A.C./D.C. HEATING  
 TIME : 4 v. 6 sec. 6 v. 4 sec. 39/6.  
 TRANSFORMER for 200/230 v. 37/6.

Terms C.O.D. OR CASH with order and subject to price alterations and being unsold.

*Arthur's* Est. 1919

PROPS: ARTHUR GRAY, LTD.


OUR ONLY ADDRESS: Gray House,

150-152 Charing Cross Road, London, W.C.2

TEmpLe Bar 5833/4 and 4765.

TELEGRAMS—"TELEGRAy, WESTCENT, LONDON."

CABLES—"TELEGRAy, LONDON."

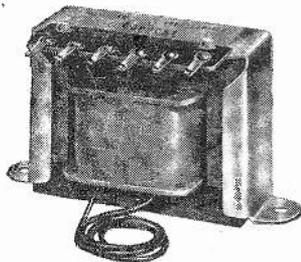

## Forrest COMBINED BOOSTER AND ISOLATING TRANSFORMERS

Cheap and easy to fit to any Receiver, they enable Tubes with low emission or with Cathode-Heater short to be used again. Supplied in any voltage from 2v.—13.3v.

OPTIONAL BOOST (12½% and 25%).


Price 21/- (Retail)

**H. W. FORREST**

349 HASLUCKS GREEN ROAD  
 SHIRLEY, BIRMINGHAM. SHI. 2483

## NEWNES
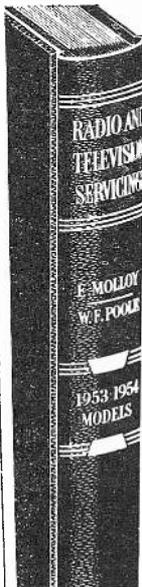
# Radio & Television SERVICING 1953-1954 Models



This single volume gives you in compact form all the essential data you need for dealing with faults and for tuning—circuit diagrams, valve voltages, alignment procedures, component lay-outs, etc.

The book constitutes a special limited edition and there is a copy for you for FREE Examination if you hurry. You need data for the popular 1953/1954 models, so CLAIM A COPY NOW on coupon below.

### Free for 7 days' EXAMINATION

TELEVISION MODELS by . . .

Ace, Alba, Ambassador, Argosy, Baird, Beethoven, Bush, Champion, Cossor, Decca, Ekcovision, English Electric, Ferguson, Ferranti, G.E.C., Invicta, K-B, McMichael, Marconiphone, Masteradio, Murphy, Pam, Peto Scott, Philco, Philips, Pilot, Pye, Raymond, Regentone, R.G.D., Sobell, Stella, Ultra, Vidor.

**385 Pages**

of Television Servicing Data.

RADIO MODELS by . . .

Ace, Ambassador, Beethoven, Bush, Champion, Cossor, Decca, Ekco, Ever Ready, Ferguson, Ferranti, G.E.C., Invicta, McCarthy, McMichael, Marconiphone, Masteradio, Murphy, Peto Scott, Philco, Philips, Pilot, Pye, Raymond, Regentone, R.G.D., Sobell, Ultra, Vidor.

**215 Pages**

of Radio Servicing Data.

"A great help and worth a fortune!" says owner of Newnes previous Servicing books.

POST THIS COUPON TO-DAY!

**GEORGE NEWNES, LTD.,**

66-69, Great Queen Street, London, W.C.2.

Please send me the special VOLUME of Newnes RADIO AND TELEVISION SERVICING. It is understood that I may return the work within eight days. If I keep it I will send a first payment of 10s. eight days after delivery, and 10s. 0d. monthly thereafter, until the sum of 50s. has been paid. Cash price within eight days is 45s.

Name.....

Address.....


Place X where it applies

Occupation.....  HouseOWNER  Householder

Signature.....  Living with Parents


(Or your Parent's Signature if under 21)  Lodging Address

R.9

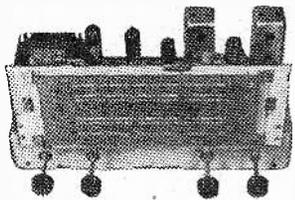

ALL WAVE RADIOGRAM CHASSIS

**THREE WAVEBANDS FIVE VALVES**  
 S.W. 16 m.—50 m. LATEST MULLARD  
 M.W. 200 m.—350 m. ECH42, EF41, EBC41  
 L.W. 800 m.—2,000 m. ELA1, EF240.  
 12 month Guarantee, with 10in. P.M. Speaker,  
 A.C. 200/250 v. Switch. Short-Medium-Long-  
 Grain. A.V.C. and Negative feedback. 4.2 watts.  
 Chassis 1 1/2 x 5 1/2 x 2 1/2 in.; Class Dial—10in. x 4 1/2 in.  
 Horizontal or vertical available. 2 Pilot Lamps.  
 Four Knobs. Walnut or Ivory, aligned and cali-  
 brated. Chassis isolated from mains. PRICE £10/15/0.  
 Without 10in. Speaker, £9/15/0. Carr. & Ins., 4/6.  
**CONDENSERS**—New stock. 001 mfd. 5 pfs to 500 pf.  
 T.C.C. 5/6. Ditto, 12.5 kv. 9/6; 2 pf. to 500 pf.  
 Mica. 61. .001, .01, .02, 500 v.—1 mfd. 350 v. 9d. r  
 Hunts Moldable 300 v. .005, .01, .04, .1, .05 mfd. and  
 1 mfd., 1/8; 25 mfd., 1/8; 5 mfd., 500 v., 1/9.  
**SILVER MICA CONDENSERS**—10mfd., 500 v., 1/3.  
 1/2; 500 pf. to 3,000 pf., 1/3. DITTO 1/3  
 1.5 pf. to 500 pf., 1/3; 515 pf. to 1,000 pf., 2/-.  
 Tubular Electrolytics (Can Type, Clips, 3d. ea.  
 4/500 v. B.E.C. 2/- 16/450 v. T.C.C. 3/6  
 8/450 v. Hunts 2/3 60/350 v. T.C.C. 3/6  
 16/500 v. Dubilier 4/- 8+16/450 v. B.E.C. 5/6  
 8+8/500 v. Dubilier 4/6 16+16/450 v. B.E.C. 5/6  
 18+18/500 v. Dub. 6/- 18+18/500 v. T.C.C. 6/-  
 32/500 v. Dubilier 6/- 32/350 v. Dubilier 4/6  
 25/25 v. Hunts. 1/9 60+100/350 v. 1/6  
 50/50 v. Plessey 2/- 100+200/275 v. 12/6  
**SPECIALS**—500 mfd. 12 v., 3/-; 1500 mfd. 6 v., 4/6  
 1000+1000 mfd. 6 v., 8/6; 1 mfd. 1.5 kv., 3/6.  
**T.C.C. SCREW BASE TYPE 512**—8 mfd. 500 v., 3/-;  
 15 mfd. 500 v., 4/-  
**C.R.T. LOW LEAKAGE ISOLATION TRANS.** Ratio  
 1:1.25, 25% boost, 2 v., 10/6; 4 v., 10/8; 6.3 v.,  
 10/6; 10 v., 10/6; 13.3 v., 10/6.  
**MAINS TYPE Multi Output**—2, 2A, 2I, 2J, 2K, 3 v.  
 2 amp., 17/6.  
**MAINS TYPE Multi Output**, 2, 4, 6.3 v., 7.3 v.,  
 10 v., 13 v., two taps boost output 25%, or 50%, 21/-

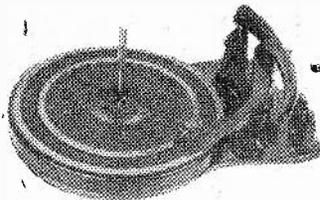

Brand new Plessey 3-speed Autochanger Mixer Unit  
 for 7, 10 and 12in. Records. Twin Hi-Fi Xtal Head  
 with Duopoint sapphire stylus. Plays 4,000 records.  
 Spring mounting. Baseboard required, 15in. x  
 12 1/2 in. Height 5 1/2 in. Depth 2 1/2 in. Superb Quality.  
 Bargain Price, 91 sns. post free.  
**SIMILAR MODEL**—3 speed Single Record unit  
 with Acos 37 Turnover Head, each Sapphire Stylus  
 plays 2,000 records. Starting Switch Automatically  
 places Pick-up on records 7in., 10in. or 12in. Auto  
 Stop. Baseplate 12in. x 8in. Height 2 1/2 in. Depth  
 1 1/2 in. Price £7/15/6, post free.

**TV. PRE-AMP.**—Channel 1, easily modified to  
 other channels or converter use. Midget chassis  
 6in. x 3in. x 1 1/2 in. Complete with coax. lead,  
 plug and EF42 valve. Brand new (boxed).  
 Listed £3/15/-. Special clearance, 21/-.

**WIRE-WOUND POTS. 3 WATT FANOUS MAXIES**  
 Pre-Set Min. TV. Type. Standard Size Pots, 2 1/2 in.  
 All values 25 ohms to 30 Spindle. 100 ohms to  
 K. 3/- ea. 50 K., 4/- 50 K., 5/6; 100 K., 6/8.  
 Ditto Carbon Track 50K. W/W EXT. SPEAKER  
 to 2 Meg., 3/-.  
**CONTROL** 10/2, 3/-.  
**L.F. CHOKES**—15 H 60 ma, 5/-; 20H 120 ma, 11/6;  
 15 H 150 ma, 12/6. H.F. Choke, 14 m.H., 2/6.  
**HEATER TRANS.**—Tapped prim., 200/250 v. 6.3 v.  
 1A amp., 7/6, tapped sec. 2, 4, 6.3 v., 1 1/2 amp., 3/6.  
**MAINS TRANS.** 350-0-350, 80 ma., 6.3 v. 4 a., 5 v.  
 2 a., ditto 250-0-250, 21/-, 3-way mounting.

No connection with any other firm. Please address  
 all correspondence correctly as below.

**Radio Component Specialists**  
 307, Whitehorse Road, West Croydon.  
 THO 1665  
 Post 6d. £1 orders post free. C.O.D. 1/6. Lists s.a.e.

**7/6 VALVE SALE 7/6**  
 New boxed. All guaranteed

1R5, 1B5, 1T4, 1S4, 384, 3V4, 6AM6, 6P12,  
 6BE6, 6BW6, 6KT4, 6K8, 6SA7, 6SL7, 6V6,  
 6X4, 6X5, 7S7, 8D9, 12AX7, 607, 6C91,  
 6E89, 6F91, 6H7, 6H9, 6H12, 6H13, 6H15,  
 6U2, 12U1. AT 8/6; 5U4, 5Z4, 6AK5, 6AT6,  
 6C9, 6L6, 6Q7, 6S7, 80, ECH42, Sylvania  
 EF50, MU14. AT 10/6; ECL80, EF80, EL41.

**Volume Controls**  
 Long spindles. Guaranteed 1 year. All values  
 10,000 ohms to 2 Meg-ohms.  
 No Sw. S.P.S.W. D.P.S.W.  
 3/- 4/- 4/8

**80 ohm COAX**  
 Semi-insulated spaced poly-  
 thetiene insulated, 1in. diam.  
 Stranded core. 9d., yd.  
 Losses cut 50%.  
**STANDARD**  
 1in. Coax. 8d., yd.

**COAX PLUGS** ... 1/2 **DOUBLE SOCKET** ... 1/2  
**SOCKETS** ... 1/- **OUTLET BOXES** ... 4/6

**BALANCED TWIN FEEDER** per yd. 6d. } 80  
**TWIN SCREENED FEEDER** per yd. 1/- } 100  
**50 OHM COAX CABLE**, 8d. per yd. 100 yds.  
**TRIMMERS**, Ceramic, 30, 70 pf., 9d.; 10m pf.  
 150 pf., 1/3; 250 pf., 1/6; 600 pf., 2/9.

**TYANA**—Midget Soldering Iron, 200/220 v. or  
 230/250 v., 14/11. Triple Three mod. with detach-  
 able bench stand. 19/8. Solon Midget Iron, 13/6.  
**XTAL DIODE**—Sensitive G.E.C. type, 3/6. H.R.  
 Phones (S. G. Brown) or Hi-grade Amer., 15/6 pair.

**STOP PRESS.—B.S.R. MONARCH 3-SPEED**  
**MIXER CHANGER, ACOS XTAL HEADS**—  
 Baseboard, 14in. x 12in. Height 5 1/2 in. Brand  
 New in Maker's Boxes. £10/19/6, post free.

**ALADDIN FORMERS** and core, 1in., 8d.; 1 1/2 in., 10d.  
**KNOBBS, GOLD ENGRAVED**—Walnut or Ivory,  
 1 1/2 in. diam., 1/6 each. Not engraved, 1/- each.  
**SENTERCEL RECTIFIERS**—EHT Type. Ply-  
 back Voltage.—K3/25 k.V., 4/3; K3/40, 3.2 kv., 6/-;  
 K3/45, 3.5 kv., 6/6; K3/50 4 kv., 7/3; K3/100 8 kv.,  
 12/6; K3/160 14 kv., 18/- **MAINS TYPE**—RML,  
 125 v., 60 ma 4/-; RML, 100 ma., 4/9; RML,  
 122 ma., 5/9; RML, 250 v., 7/5 ma., 16/-.

**LOUDSPEAKERS P.M., 3 OHM**—5in., 16/6; 6in.,  
 17/8; 8in., 19/6; 10in., 25/-; 6in. with transf., 19/6.  
**T.V. AERIALS**—All channels, indoor Inv. T., 13/6.  
**CHARGER TRANS.** for 2, 6 or 12 v., 1 1/2 amp., 13/6;  
 4 amp., 21/-; Bridge rectifiers, 1 1/2 amp., 3/8; 4  
 amp., 17/6.  
**RECORDING TAPE**, Exclusive Bargain, 1,200 ft.  
 reels High Coercitivity. Brand new, 17/6.

**HANNEY of BATH offers:—**

**VIEWMASTER**—Constructor's Envelope, 7/6. Stage 1, 62/3;  
 two, 43/3; three, 25/1/3; four, 9/10; five, £10/4; six, £27/7/3;  
 seven, 64/-; Control Panel Kit, (less 6/6), £29/2/6.  
**WB100** (sound and vision chassis), 18/6; **WB101**, 6/-; **WB102**, 13/6;  
**WB103**, 42/-; **WB103A**, 52/6; **WB104**, 15/6; **WB105**, 47/2; **WB106**,  
 25/6; **WB107**, 32/6; **WB108**, 33/3; **WB109**, 1.2 or 3 (state tube type),  
 22/6; **WB110**, 7/6; **WB112**, 21/6; **WB Console conversion kit**, 35/-;  
**WB300** pre-amp chassis, 17/6; Westinghouse Rectifiers, 14/9c,  
 20/4; 14D36, 11/7; WX3 and WX3, 2/9 each; 36EHT100, 29/5;  
 36EHT50, 26/1; 36EHT45, 23/8; K3100, 14/8; K3150, 8/9; E3/45,  
 8/2. T.C.C. Condensers, £7/10/- (any condenser supplied separately).  
 Morganite pots, 5/- each; Morganite resistors, 35/3. Colvern  
 pots, 22/6; or CLR4901, 3/3 each and CLR4909, 22, 6/4. Belling-Lee  
 1707, 8/9; Fuses 6d. each. Wearite Coils/sets (with L9), L'don and  
 Belfast, 22/-; Wenvoe and Pontop Pike, 28/-; H. Moss, K.O.S.  
 B'ham and Brighton, 30/-. Pre-amp coils, 4/- per (any channel).

**TELEKING**—Constructor's Envelope, 6/-; Coils/sets, 44/6; Chassis  
 kit, 50/-; T.C.C. kit, £7/4/6; RMA rectifier, 21/-; Allen Compen-  
 ts, L0308, 40/-; FO305, 21/-; DC300C, 39/6; FC302, 31/-; GL16  
 and GL18, 7/6 each; BT314, 15/-; SC312, 21/-; AT310, 30/-; OP117,  
 9/-; Dubilier Resistor/pot, kit, 81/6.

**P.T. SUPERVISOR**—T.C.C. Condenser kit, £8/6/4; Erie resistor  
 kit, 54/4; 4 w/w pots, 26/-; 7 Erie carbon pots, 35/-; Allen coils-  
 sets, 44/6; Allen DC300C, 39/6; GL16 and GL18, 7/6 each;  
 SC312, 21/-; FC302, 31/-; OP117 output trans., 9/-; Denco  
 WA/FM21, 21/-; WA/LOT, 42/-; Denco chassis kit, 51/6; West-  
 ington house WX3, 31/0; WGA4, 7/6; LW7, 28/8; English Electric  
 polystyrene mask, 45/8; perspex filter, 32/8; anti-corona ring,  
 6/8; Tube sheath, 6/2; T.901 tube, inc. carriage and insurance,  
 £22/14/10; Elac IT8 ion trap, 5/-.

**OSRAM 912** Erie resistor-pot kit with ceramic tube resistors,  
 very highly recommended, 29/6; Lab. resistor kit, 32/4; T.C.C.  
 condensers, 55/-; PARTRIDGE Components, with loose lead  
 terminations, Mains trans., 44/-; Smoothing Choke, 29/6; Output  
 trans., 76/9. Price includes Partridge carriage/charge. Printed  
 panel, 14/6. W.B. chassis, 28/6. Send for complete list.


**MULLARD 5 VALVE 10 WATT AMPLIFIER**, T.C.C. Con-  
 densers, 45/-; Erie resistor-pot kit, 37/6; Elstone Mains trans.,  
 39/-; Elstone Output trans., 45/- (both types); Denco chassis,  
 14/6. Small parts as per our list. Matched pairs of valves are  
 available for both the above designs.

Send 6d. in stamps for our complete list

**L. F. HANNEY, 77 Lower Bristol Road, West.**

Tel: 3811


**LAFCO "E. PAYMENT" CORNER**

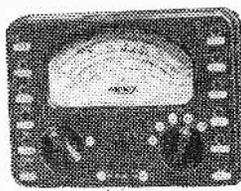

**THE "METRIX" MULTIMETER 460**  
 with 28 ranges. Internal  
 resistance 10,000 ohms per  
 volt A.C. and D.C. Volts:  
 3-7.5-30-75-150-300-750 v. A.C.  
 and D.C. Resistance from  
 0 to 2 megohms in two  
 ranges. Dimensions: 5 1/2 in.  
 x 4 in. x 1 1/2 in. Weight 1  
 lb. 5 ozs. Cash Price £14.6.4  
 or 35/- deposit and 8 monthly  
 payments of 35/-.

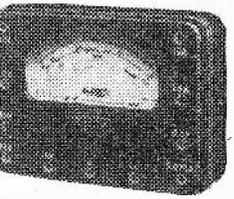**THE "METRIX" MODEL 410**

—10 ranges with a sensitivity  
 of 100 ohms per volt from  
 75-750 volts. A.C. and D.C.  
 Volts 15-75-150-300-750. Re-  
 sistance 100-ohms. Weight:  
 1 lb. 2 ozs. Cash Price £9.2.11  
 or 22/5 deposit and 8 monthly  
 payments of 22/5.



**There is a "Metrix" Meter for YOUR needs**

**MODEL 400 TRANSLIP**—Currents can be measured  
 without any volts drop. All voltages (A.C.) up to 600 v. may  
 be measured. A.C. currents 0.10, 30, 100, 300 A. Accuracy ± 5%  
 F.S.D. £17.8.0 cash or 42/7 deposit and 8 by 42/7.

**MODEL 422E**—Sensitivity 5,000 ohms per volt. A.C. and D.C.  
 volts 1.5-5-15-50-150-500-1,500. A.C. and D.C. currents 1.5-5-15-  
 50-150-500 mA., 1.5-5 amps. resistance, 0-2 meg. in 2 ranges.  
 Accuracy 1.5% on D.C., 2.5% on A.C. Weighs 21 lbs. £22.14.10  
 cash or 55/7 deposit and 8 by 55/7.

Send stamp for leaflets of the Metrix range, all of which are available  
 on easy terms.

**"LAFCO" (Desk 17)**

3, Corbetts Passage, Rotherhithe New Road, London,  
 S.E.16. Telephone: BRMonday 4341. Ext. 1



and the circuit is nicely balanced, trapezium distortion being avoided by suitable choice of components.

A basic working circuit is given in Fig. 12. A portion of the output of the oscillator valve V1 is fed to the grid of V2 via the coupling condenser C1. Note that the component values of C1 and R2 must be carefully chosen having regard to the time constants of the circuit as given in previous chapters.

V2 is a conventional R.C. amplifier, the same class of valve being used as for V1. A certain pro-

portion of the output of V2 is fed back by means of C2 and this tends to cancel the input signal. Actually, a state of equilibrium is reached by suitable choice of components so that there is just sufficient input to V2 for the production of an equal and opposite voltage at the second deflector plate.

Typical values for the frame circuit are 0.001  $\mu$ F for C1 and C2 and 5 M $\Omega$  for R2. R3 should be of the same magnitude as R1, and R4 should be chosen according to the characteristics of the valve. For an H.F. pentode about 220 K $\Omega$  with 0.1  $\mu$ F for C5 should be found sufficient. C4 should be of the same value as C3.

**Dual Amplifiers**

In Fig. 14 is shown the circuit of a dual amplifier. In this amplifier the output from the oscillator is fed directly to the amplifier which comprises two valves, one being used to feed one deflector plate, and the other valve feeding the second deflector plate.

The output from the oscillator is taken from the anode load resistor which, in this case, is made variable. Its value should be the same as that of R1 in Fig. 11. The input to the amplifier is thereby made variable, and control over the total amplification is obtained. This particular circuit is to be used for a frame circuit and VR1 could therefore be labelled "Height Control."

The first triode acts as a normal R.C.-coupled amplifier, but its anode load is split, part of it being in the form of a potentiometer VR2, which controls the amount of input to V2. V1 feeds the first deflector plate, the second deflector being fed from V2; thus we have a balanced push-pull amplifier.

The second portion of the amplifier V2 has its input tapped down the grid resistor R5, R6. This is in order to reduce the possibilities of hum from V1 being amplified by V2.

It is quite practicable to make V1, V2 a single valve, such as the 6SN7, though single triodes, such as the 6J5, can be employed.

Typical values for the frame circuit are: C1 0.1  $\mu$ F, C2 0.1  $\mu$ F, C3 0.05  $\mu$ F; R1 5 M $\Omega$ , R2 22K., R3 100 K., R4 100 K., R5 2 M $\Omega$ , R6 8M $\Omega$ .

In Fig. 15 we have an amplifier for the line circuit. In the case of the line frequency we not only have to consider the different time constants of the circuit, but also the question of hum which can be quite a thorny problem. Any hum reaching the deflector plates will show as a wavy edge to the raster.

(Continued on page 35)

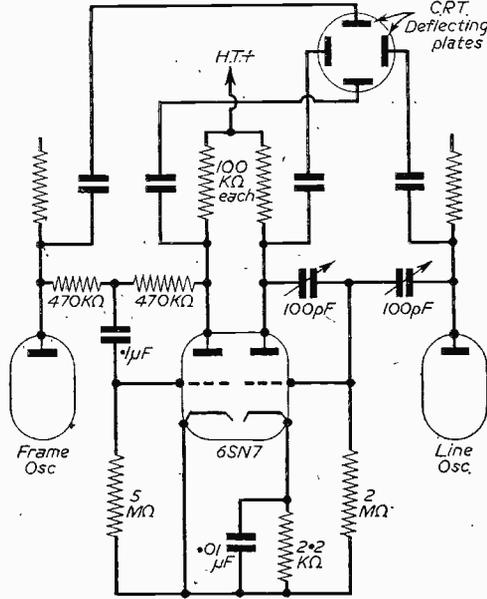


Fig. 13.—An economy circuit.

portion of the output of V2 is fed back by means of C2 and this tends to cancel the input signal. Actually, a state of equilibrium is reached by suitable choice of components so that there is just sufficient input to V2 for the production of an equal and opposite voltage at the second deflector plate.

Typical values for the frame circuit are 0.001  $\mu$ F for C1 and C2 and 5 M $\Omega$  for R2. R3 should be of the same magnitude as R1, and R4 should be chosen according to the characteristics of the valve. For an H.F. pentode about 220 K $\Omega$  with 0.1  $\mu$ F for C5 should be found sufficient. C4 should be of the same value as C3.

For the line circuit typical values are 100 pF for C1 and C2 and 2 M $\Omega$  for R2. Other values can be as for the frame circuit.

Note that an increase in C1 will increase the scan but care must be taken to avoid distortion of the trace. Similarly, a reduction of C2 will also increase the scan.

In the line circuit optimum working can be obtained by making C1 and C2 variable, say about 200 pF for C1 and 100 pF for C2. By this method it should be possible to obtain maximum amplitude with minimum distortion.

**Economy Circuit**

Fig. 13 shows a circuit which uses a single valve for provision of amplification for line and frame circuits. It will be seen that conventional practice is

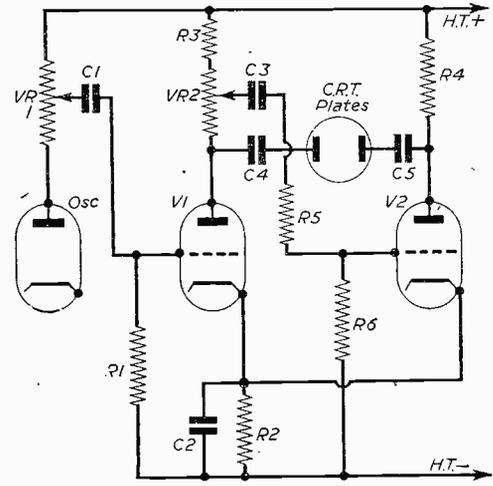


Fig. 14.—A dual amplifier (frame)

# RADIO SUPPLY CO. (LEEDS) LTD.

Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/- extra under 10/-; 1/6 extra under £1; 2/- under £3. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 5d.; Trade List 6d.

## R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s Screened.

### TOP SHROUDED, DROP THROUGH

- 280-0-260 v 70 ma. 6.3 v 2 a, 5 v 2 a ... 16/9
- 280-0-350 v 80 ma. 6.3 v 2 a, 5 v 2 a ... 18/9
- 250-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 26/9
- 350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 23/9
- 350-0-350 v 150 ma. 6.3 v 4 a, 5 v 3 a ... 29/9

### FULLY SHROUDED UPRIGHT

- 250-0-250 v 60 ma. 6.3 v 2 a, 5 v 2 a ... 17/6
- 250-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 26/9
- 250-0-250 v 100 ma. 6.3 v 6 a, 5 v 3 a, for R335 Conversion ... 31/-
- 300-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 27/9
- 350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 27/9
- 350-0-350 v 150 ma. 6.3 v 4 a, 0-4.5 v 3 a ... 31/6
- 425-0-425 v 200 ma. 6.3 v 4 a, C.T. 6.3 v 4 a, C.T. 5 v 3 a ... 49/9

### FILAMENT TRANSFORMERS

- All with 200-250 v 50 c/s Primaries; 6.3 v 1.5 a, 5/9; 6.3 v 2 a, 7/6; 0-4.6-3 v 2 a, 7/9; 12 v 1 a, 7/11; 6.3 v 3 a, 9/11; 6.3 v 6 a, 17/9.

### CHARGER TRANSFORMERS

- 200-250 v 0-9-15 v 1 a, 11/9; 0-9-15 v 3 a, 16/9; 0-9-15 v 4 a, 19/9; 0-9-15 v 6 a, 22/9.

### OUTPUT TRANSFORMERS

- Standard Pentode 5,000 to 30hms ... 4/9
- Standard Pentode 7,000 to 30hms ... 4/9
- Small Pentode 5,000 to 30hms ... 3/9

### E.H.T. TRANSFORMERS 200-230-250 v

- 2,500 v 5 ma, 2-0-2 v 11 a, 2-0-2 v 11 a for VCR37, VCR317 ... 37/6

### SMOOTHING CHOKES

- 250 ma 3 h 100 ohms ... 11/9
- 100 ma 10 h 200 ohms Potted ... 8/9
- 80 ma 10 h 350 ohms ... 5/6
- 60 ma 10 h 400 ohms ... 4/11

### BATTERY CONVERTER KIT

All parts for converting any type of Battery Receiver to A.C. mains 200-250 v 50 c/s. Supplied 120 v 90 v or 60 v at 40 ma. Fully smoothed and fully smoothed L.T. of 2 v at 0.4 a, 0.1 a. Price including circuit 48/9. Or ready for use 8/9 extra.

### TV. PREAMPLIFIER.—For Fringe Areas.

Brand New. Complete with 6F13 valve. Only 22/6.

### SELENIUM METAL RECTIFIERS

- RM4 250 v 250 ma, 11/9; G.E.C. 300 v 250 ma, 12/9; 120 v 40 ma, 3/9; 612 v 1 a F.W., 5/9; 240 v 50 ma, 5/9; 612 v 2 a F.W., 9/9; 250 v 50 ma, 7/9;

### ALL DRY RECEIVER BATTERY SUPERSEDER KIT

All parts for the construction of a unit (metal case 5-4-4in.) to supply 4-valve Battery receivers requiring 90 v 10 ma, and 1.5 v 250 ma. Fully smoothed. From 200-250 v 50 c/s mains. Price, inc. point-to-point wiring diagrams, 35/9. Or assembled and tested at 42/6.

### R.S.C. 25 WATT AMPLIFIER

Push Pull Output. Quality comparable with the best in amplifiers. Includes 7 valves. Preamplifier and Tone Control Unit is incorporated. Separate Bass and Treble controls. Two separately controlled inputs for Mike and Gram, or Tape and Radio. Sensitivity is very high, making the unit suitable for use with any type of pick-up and microphones. IDEAL FOR PLANK HALLS, CLUBS, SCHOOLS, HOMES, OR LARGE AUDITORIUMS, FOR ELECTRONIC ORGAN OR GUITAR. For operation on normal Mains 200/250 v 50 c/s. Outputs for 3 and 15 ohm speakers. Available in kit form with point to point wiring diagrams and instructions at the amazingly low price of ..... Carr. 10/- Or supplied ready for use for 50/- extra. 12 months guarantee (Valves 3 months). Suitable speakers, mikes, etc. available. H.P. TERMS on assembled units: Deposit 25/- and 12 mthly. p'ments, 20/-

## Dept. N., 32, THE CALLS, LEEDS, 2.

### CO-AXIAL CABLE 1in.

- 75 ohms 14/38 ... 7d yd
- Twin-Screened Feeder ... 10d yd

### EX-GOVT. SMOOTHING CHOKES.

- 50 ma 5-10 h ... 2/9
- 100 ma 10 h 500 ohms Tropicalised ... 1/9
- 150 ma 10 h 150 ohms ... 11/9
- 250 ma 10 h 150 ohms ... 14/9
- 250 ma 10 h 50 ohms ... 14/9

### EX-GOVT. MAINS TRANSFORMERS

- Primaries 230/250 v 50 c/s, 48 v 1 a, 9/9; 400 v C.T. 150 ma 4 v 6 a, 6.3 v 6 a, 6.3 v 0.6 a, 4 v 6 a, 4 v 3 a, 5 v 3 a, 4 v 3 a, 5 v 2 a, 22/9; 300-0-300 v 120 ma 4 v 1 a, 17/6. Add 5/0 carr. to types at 29/6.

### EX-GOVT. E.H.T. SMOOTHERS


- 02 mid 8,000 v, 11/1; 25 mid 4,000 v (Block), 4/9; 5 mid 3,500 v, 3/6.

### BATTERY CHARGER KITS.—Consisting of attractive Green Crackle Case, Transformer, F.W. Rectifier, Fuse, Fuseholder, Tag strip, Grommets, and Circuit.

For mains input 200-230-250 v 50 c/s 6 v 2 a, 22/9; 6 v or 12 v, 2 a, 31/6; 6 v or 12 v, 4 a, 48/9; Any type assembled and tested for 6/9 extra.
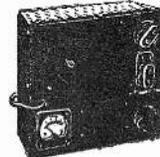
### R.S.C. 6v or 12v BATTERY CHARGER

For normal A.C. mains input 200-230-250 v 50 c/s. Selector panel for 6 v or 12 v charging. Variable charge rate of up to 4 AMPS. Fused, and with 5 amp meter. Well ventilated metal case with attractive crackle finish. Guaranteed for 12 months, 69/6. Carr. 2/6.



### BATTERY CHARGERS.—For mains 200-250 v 50 c/s. Output for charging 6 v or 12 v at 1 amp. In strong metal case. Only 19/9. Above can also be used for electric train power supply.

R.F. UNIT TYPE 26.—Brand new. Cartoned, 39/6, plus carr. 2/6.

# HENRY'S (RADIO LTD.)

## SPECIAL OFFER '38' WALKIE TALKIE SETS

We have purchased large quantity of the above '38' Sets, and can now offer same complete with 5 valves: 4—VP23 and ATP4. Throat microphone, headphones, junction box and collapsible aerial. Freq. range 7.4 to 9 mc/s. Range approx. 5 miles. In absolutely new condition and Guaranteed Air Tested at 59/6, carriage 5/-.

We have over 20,000 American and B.V.A. valves in stock. ALL VALVES NEW AND GUARANTEED.

1D8GT	10/-	6N7GT	7/8	12SA7GT	8/6	EF36	6/8	SP41	4/-
1A7GT	12/6	6L7	7/6	12SQ7GT	8/6	EF39	6/6	D41	5/-
1H5GT	10/-	6AM6	9/-	12SJ7GT	8/6	EK32	6/6	VP23	6/6
1N5GT	10/-	6243	8/6	12SK7GT	8/6	EL32	7/6	HL23DD	
1L4	7/6	75R0	8/6	12SR7	7/6	EF50 (Red)		TP25	6/6
1Q5GT	10/-	6L63	10/-	6D5	6/6	SP1	10/-	PEN25	8/6
1A5GT	10/-	807GT	8/6	6C8	6/6	HL2	3/6	PEN25	8/6
1S5	7/6	6SQ7GT	8/6	8A7G	8/6	LP2	4/-	QP25	6/6
1S4	7/6	6S7GT	6/6	6A8G	8/6	KT2	5/-	QP21	8/6
1R4	7/6	6SJ7GT	8/6	TZ40	35/-	VP2	8/6	TP22	2/6
1T5	7/6	6S7GT	8/6	OZ4	7/-	SP2	8/6	ATP4	4/6
3A4	7/6	6SN7GT	9/-	25Z5G	8/6	PTD2A	8/6	MS/PENB	8/6
3Q5GT	10/-	6SL7GT	9/-	25Z6G	8/6	VP2B	8/6		
3S4	7/6	6S7GT	10/-	35Z4GT	8/6	215SG	4/-	MS/PEN	7/6
3V4	7/6	6V6G	7/6	35Z5GT	8/6	866A	15/-	PX25	12/6
1L1N5	8/-	6V6GT	7/6	35L6GT	8/6	354V	5/-	6A6	10/-
1LD5	8/-	6F6G	7/6	50L8GT	8/6	4D1	4/-	46	10/-
6Y4C	8/6	6AC7	6/6	25A8T	8/6	BD2	4/-	AC/PEN 104	10/-
5Z4G	8/6	6A6GT	12/6	KT33C	10/-	8D2	4/-	FC13C	10/-
5Z3G	8/6	6CS7GT	5/-	KT66	12/6	PEN46	7/6	FC13s/c	10/-
MU14	8/6	6J5GT	5/-	EBC33	8/6	AC6PEN	6/6	42SP1	6/6
6B8	7/6	12A6	7/6	EF54	6/-	VP41	7/6	PENTD4020	
6K8G	9/-	12K7GT	8/6	EB34	3/6	TH233	10/-		
6Y7C	6/6	12A7GT	6/6	25A50	2/6	6M4	7/6	VT501	12/6
6J7G	6/6	12Q7GT	8/6	D1	2/-	SP61	4/-	U19	10/-

EY51	12/-	UL41	11/-	EF80	10/6	PL81	12/6	12A7E	8/-
EF41	11/-	UY41	11/-	EAB80	10/-	PL82	10/-	12A7T	9/-
EL41	11/-	UF40	11/-	ECC85	10/-	PY81	10/-	12BA6	9/-
EZ40	10/-	DK40	10/-	ECC80	9/-	PY82	10/-	12BA6	9/-
EM34	10/-	50B5	10/-	EM80	10/-	FCC84	12/6	12EB6	10/-
39W4	9/-	50C5	10/-	ECL80	12/6	PCF82	12/6	6X4	8/6

28-page Catalogue, 3d. Open Mon.-Sat. 9-6. Thurs. 1 p.m.

## CRYSTAL MICROPHONE INSERTS



8/6 POST FREE

## SPECIAL REDUCTION

- 1A7GT, 1N5GT, 1H5GT, 1A5GT (1CSGT or 1Q5GT) 40/- Set
- 10 EF50 (Ex-Brand New Units) only ... 45/-
- 6K8G, 6K7G, 6Q7G, 37/6
- 1R5, 1S5, 1T4, 1S4 (or 3S4 or 3V4) ... 27/6
- TP25, HL23/DD
- VP23, PEN25 (or 6Q25) ... 25/-
- 6K8G, 6K7G, 6Q7G, 25A6G, 25Z5 (or 25Z6G) ... 37/6
- 12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT (or 50L6GT) ... 37/6
- 12SA7GT, 12SK7GT, 12SQ7GT, 35Z4GT (or 35L6GT) ... 37/6

## PACKARD BELL AMPLIFIER

Brand new complete with 2817 and 6SL7GT and instruction book 12/6. P. & P. 2/-.

## "R.F. 26" F.M. CONVERTER UNIT

85/100 Mc/s. We can now offer this self-contained Unit comprising 6 valves: 2—6BA6, EB91, VR137, EF54, EF54. Two I.F. stages and separate local oscillator, also a Mutual Graded Vernier Drive ensuring easy tuning. Special offer of above item and RF26, including circuit, postage 3/- ... £6-5-0


## RECEIVER 25/73

Part of the TR196, this 6-valve unit makes an ideal basis for a mains operated All-wave Superhet, full modification can be supplied. Complete with valves, 2 each EF36 and EF39, and 1 each EK32 and EBC33. AS NEW. ONLY 27/6. (Postage, etc., 2/6.) Mod. data FREE.

## INDICATOR UNIT TYPE


Unit contains VCR517 Cathode Ray 6in. tube, complete with Mu-metal screen, 3 EF50, 4 SP61, and 1 5U4G valves, 9 wire-wound volume controls and quantity of resistors and condensers. Suitable either for basis of television (full picture guaranteed) or Oscilloscope. Offered BRAND NEW (less relay), 67/6. Plus 7/6 for "Radio Constructor" scope circuit included.

All Items sold separately.

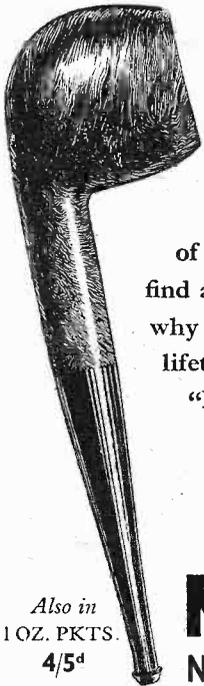
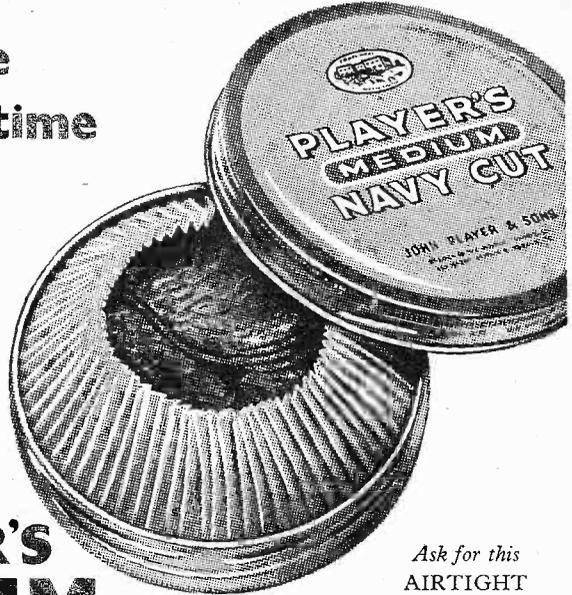
# The choice for a lifetime

In the natural process  
of trial and error you'll  
find all the good reasons  
why so many men get a  
lifetime of pleasure from  
"Player's Medium".



Also in  
1 OZ. PKTS.  
4/5<sup>d</sup>

## PLAYER'S MEDIUM NAVY CUT TOBACCO

Ask for this  
AIRTIGHT  
2 oz. pocket tin  
8/10<sup>d</sup>

John Player & Sons, Branch of The Imperial Tobacco Co. (of Great Britain & Ireland) Ltd.

[NCT 82T]

# NEW!

## EXPERIMENTAL KITS in Radio, T.V. etc.

### LEARN THE PRACTICAL WAY

Specially prepared sets of television parts (which you receive upon enrolment) with which we teach you, in your own home, the working of circuits and bring you easily to the point when you can construct and service a television set. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — this Practical Course is intended for YOU — and may be yours at very moderate cost.

#### EASY TERMS FROM 15/- A MONTH

A tutor is available to give individual help and guidance throughout the Course.



#### POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses:  
To: E.M.I. INSTITUTES, Dept. 138X, Grove Park  
Road, London, W.4.

NAME.....

ADDRESS .....

SUBJECT(S) ..... JUNE

#### EXPERIMENTAL OUTFITS:

**TELEVISION** — Instruction and equipment for building a Television Receiver.

**BEGINNER'S RADIO OUTFITS** — A course in basic principles.

**ADVANCED RADIO OUTFITS** — Instruction and equipment from which you build a Radio Receiver.

Also for Mechanics, Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S. W. Radio, Languages.

## E.M.I. INSTITUTES

The only Postal College which is part  
of a world-wide Industrial Organisation.

V1 circuit follows the conventional pattern, but the coupling circuit is made via a small variable condenser C4. At the line frequency the input capacitance of V2 has an appreciable effect, and this, together with C4, forms a capacitance bridge across the anode load resistor R7.

However, at the lower frequencies, such as 50 or 100 cycle hum conditions, the coupling becomes essentially that of C4 and R5, which thereby offers a high impedance path to the hum.

Typical circuit values are C1 0.005  $\mu$ F, C2 0.1  $\mu$ F, C3 0.1  $\mu$ F, C4 0-10 pF, R1 470 $\Omega$ , R2 1M $\Omega$ , R3

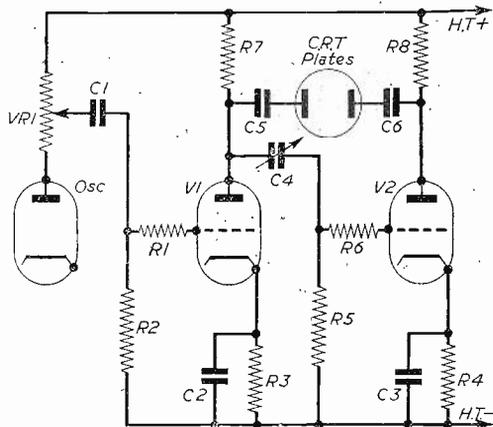


Fig. 15.—A dual amplifier (line).

4.7 K., R4 4.7 K., R5 1 M $\Omega$ , R6 470 $\Omega$ , R7 100 K., R8 100 K.

V1 and V2 can be 6J5 valves, or for the sake of economy a single 6SN7 can be used.

**Hum**

Hum is usually more distressing on the line circuit rather than the frame. In the frame the usual result is a false-looking condition, and the cure is fairly obvious but in the line circuit the symptoms are not so obvious. There will be a wavy edge to the raster, but this can be caused by direct pick-up on the deflector plates themselves, by poor smoothing, by interaction from the frame circuit, or by over-amplification of residual hum due to faulty coupling components or incorrect choice of component values.

Direct pick-up can usually be avoided by careful positioning of mains equipment and the use of a mu-metal screen; poor smoothing can be corrected by simply increasing the smoothing arrangements; interaction from the frame circuit can best be avoided by adequate decoupling and careful layout of components and wiring; residual hum troubles have been dealt with in the previous paragraphs.

In the frame circuit, very severe hum will cause the frame to lock solidly at a position removed from that of the signal giving a picture which is often split into two halves. Moderate hum will cause the scan to be non-linear, generally by cramping at top and bottom or simply cramped in the middle. This must not be confused with normal non-linearity, which does not have this particular characteristic of dual appearance.

Hum which causes light and dark bars across the screen is not due to leakage in the timebase but more usually to leakage to the grid or cathode of the C.R.T.

**Synchronising**

It is not intended to deal extensively with synchronisation as this is a different subject, but a few pointers will be made which assumes that the sync pulses for both frame and line are being correctly produced.

One defect of the Miller circuit is that only a small sync pulse is required for its operation. This often makes synchronisation of the frame circuit a little tricky as spurious pulses from the line circuit can cause triggering. For this reason really accurate interlace is difficult to obtain.

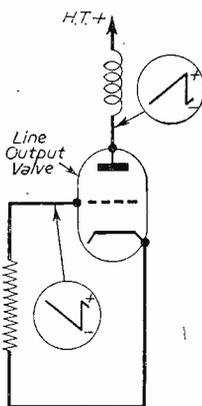


Fig. 16.—Waveform at grid and anode.

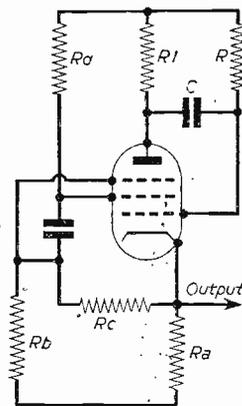


Fig. 17.—Producing a positive scan.

To achieve good interlace it is advisable to ensure adequate filtering of the sync, and a two-valve separator is often desirable. Frame and line circuits should be kept well clear of each other and adequately screened. Decoupling of both circuits should be very efficient.

When using the smaller screen the problem of interlace is not so acute but the larger screen may show defective interlace. Even so, a well-designed Miller circuit gives as good an interlace as many commercial receivers.

In the line circuit the amplitude of the sync pulse is of great importance. In some circuit layouts it is almost unnecessary to couple the sync directly to the oscillator, there being sufficient pick-up in the wiring.

The ideal arrangement is a firm lock without line

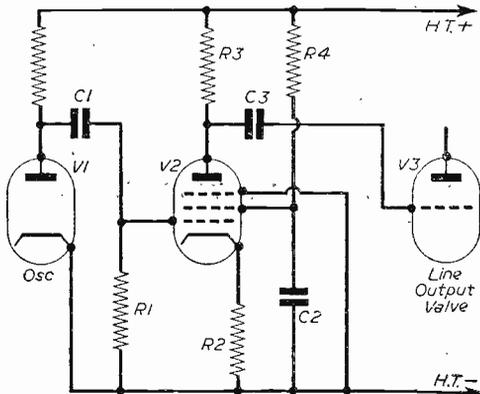


Fig. 18.—A reversal stage.

tearing, and the minimum value of sync pulse which will bring this about is a desirable feature. For this reason, the coupling condenser is often made variable, a small component of about 50 pF usually being quite sufficient.

Too heavy a sync pulse results in the picture appearing watery or produces a tearing of the lines, all sharp edges appearing jagged.

The simplest form of integrator will be found adequate for the line circuit. Frame pulses do not disturb it.

Where the top few lines of the picture are inclined to wander, then the fault generally lies in the sync circuit itself rather than the timebase proper.

### Reversing the Output

The output from the Miller oscillator is the reverse of the general rule, the trace being negative-going on scan. This is because the forward stroke is brought about by the discharge of a condenser rather than the more usual charge method.

Where the output is to be fed to an electrostatic C.R.T. the polarity of the output is of no importance, but where it is desired to drive an electromagnetic tube, then the polarity of the line circuit must be in the positive direction. The main reason for this lies in the high voltages produced by the line flyback due to the inductances of the scanning coils and output circuits.

A negative-going scan produces a positive flyback. If this type of waveform is applied to the output valve then at the anode we shall have a positive-going waveform which is negative on the flyback. As the flyback voltage at the anode rises to over 2,000 volts a sudden transition on the anode from the positive position to a highly negative one may result in severe damage to the valve itself, which is not designed to withstand such conditions.

A further important point is that modern practice inclines to the use of the flyback pulse for the production of E.H.T., which obviously precludes the use of a negative pulse.

Yet another reason is the safe and efficient running

of the output valve. If a negative-going scan is applied to the grid, the valve must be very lightly biased or it would be quickly driven to the cut-off point. A very light bias means that under static conditions the valve would draw a very heavy current. It is preferable to bias the valve back as far as is practical so as to reduce the standard running anode current and to use a positive-going waveform.

A simple circuit for producing a positive-going waveform directly from the oscillator is given in Fig. 17. The waveform is taken from the cathode by means of the voltage produced across the cathode resistor  $R_a$ , which should be of the same order as  $R_1$ .  $R_b$  should be 1 M $\Omega$  and  $R_c$  and  $R_d$  are of standard values.

One disadvantage of the circuit is that the amplitude of the waveform produced is about half of that available from the anode.

Where maximum amplitude is required the best method is to use a phase reversal stage. This is simply another valve inserted between the oscillator and the output valve in order to reverse the phase.

Fig. 18 shows a basic reversal circuit. The output from the oscillator is fed to the reversing valve V2, via C. C and  $R_1$  should have a time constant which is adequate to cope with the frequencies involved.

V2 is a standard power output valve (a triode could be used or a pentode of the 6V6 class). The cathode resistor is un-bypassed, but if extra gain is required a condenser up to 25 $\mu$ F can be used for decoupling providing the linearity is not affected.

The anode load resistor  $R_3$  is comparatively low in value (around 5 K) and should be rated at about 10 watts.

Some typical values for the line circuit are C1 0.005 $\mu$ F, C2 0.1 $\mu$ F, C3 0.005 $\mu$ F,  $R_1$  2 M $\Omega$ ,  $R_2$  235  $\Omega$ ,  $R_3$  5 K,  $R_4$  2.2 K used with a 6V6 valve.

The frame circuit needs no reversal stage as the flyback does not produce such high voltages. The use of such a stage does, however, allow the output valve to work at a much easier rating and this may possibly be sufficient justification for its use.

## SERVICING TELEVISION RECEIVERS

(Concluded from page 16)

the bottom end of which is taken to chassis by a 100 K  $\frac{1}{2}$  watt. Should this 100 K go high or open circuit the grid voltage would rise and cause a high brightness level. A grid-to-cathode leak in the tube itself will also give similar symptoms.

It is pointed out that the cathode bias resistor of the video amplifier is shunted by a 25  $\mu$ F electrolytic condenser. If this component dries up, a large amount of negative feedback will be generated, resulting in a marked loss of video signal or contrast as it may be termed. This will also cause a loss of sync, especially the frame pulses, which, being of low frequency, will be most affected. This condenser is located under the chassis near video detector V5. The video amplifier is a Z77 and is marked V6 in the diagram. V5 is another D1, and is used as the video detector. These valves cannot be replaced by the Mullard EA50 as they have a 4-volt heater.

Vertical and horizontal shift controls are provided and they control the amount of D.C. passing through the respective shift coils. This circuit is in the negative return from chassis to the H.T. negative centre tap on

the right-hand transformer, as viewed from the rear.

The left-hand transformer is concerned with supplying the E.H.T. (approx. 4 kV) and the heaters of the valves which are used on TV only.

The radio receiver is quite straightforward, V17 (Mazda D1) being rendered inoperative whilst the broadcast section is in use. The valve is the sound noise limiter, and is required on TV or TV sound only.

V14 is the X81M frequency changer, V15 the I.F. amplifier for both TV and broadcast sound (W81).

V16 is the DL82 double diode triode, V18 the Z77 A.F. amplifier, and V19 the KT81 sound output. The volume control is in the grid circuit of this last valve.

When replacing the tube on this receiver it is advisable to check that the value of  $R_{124}$  in Fig. 4 is the value marked on the tube. This has a marked effect upon the efficiency of the interference limiter.

### Correction

In the April issue the receivers dealt with were the Philips 1101U and 1200U. In the May issue the reference EK10 should be deleted from the heading of the article, and from the cover.

Volume Controls

Midget Ediswan type. Long spindles Guaranteed 1 year. All values 10,000 ohms to 2 Meg-ohms. No Sw. S.P.Sw. D.P.Sw. 3/- 4/9 COAX PLUGS ... 1/2 SOCKETS ... 1/- LINE CONNECTOR 1/2 OUTLET BOXES ... 4/6

80 ohm CABLE COAX

STANDARD 1/4 in. diam. Polythene insulated. GRADE "A" ONLY 8d. yd. SPECIAL - Semi-air spaced polythene, 80 ohm coax 1/4 in. diam. Stranded core. Losses cut 50%. 12 yds. 8/9. 9d. yd.

BALANCED TWIN FEEDER per yd. 6d. } 80 TWIN SCREENED FEEDER per yd. 1/- } ohms

TRIMMERS, Ceramic, 4pf.-70pf., 8d., 100 pf., 150 pf., 1/3, 250 pf., 1/6; 600 pf., 1/3. PHILIPS Beehive Type-2 to 8 pf. or 3 to 30 pf. 1/3 each. RESISTORS.-All values: 10 ohms to 10 meg., 1/4 w. 3d.; 1 w., 6d.; 1 w., 6d.; 2 w., 9d.; High Stability, 1 w. 1/6, 2/-, 100 ohms to 10 Meg.

WIRE-WOUND RESISTORS.-Silicone coated. 5 watt } 25 ohms-10,000 ohms ... 1/3 10 watt } 15 watt

WIRE-WOUND POTS. 3W-LAB. COLVERN, Etc. Pre-Set Min. T.V. Type. 1/4 Standard Size Pots, 24in Knurled Slotted Knob. Spindle. High Grade. All values 25 ohms to 30 K., 50 K., 4/-

O/P TRANSFORMERS.-Standard Pentode, 4/6; ditto tapped min. 4/9; small pentode, 3/9; Midget battery pentode (3V4, etc.), 4/6.

L.F. CHOKES 10 h. 63 ma., 5/-, 20/25 h. 100/150 ma., 12/6, 10 h. 120 ma., 10/6, 15 h. 100 ma., 10/6. I.V.M.C. Sh. 250 ma., 13/6, 50/60, 10 h. 150 ma., 10/6. MAINS TRANS.-Made in our own workshops to high grade specification. Fully interleaved and impregnated. Tapped prim. 200 v./230 v., Heater Trans., 6.3 v., 11 amp., 7/8; ditto 6.3 v., 3 amp., 10/8; ditto, 12 v., 75 amp., 7/8; 350-0-350, 50 ma., 6.3 v., 4/-, 5 v., 2/-, ditto 300-0-300, ditto 250-0-250, 250 v. Viewmaster Auto Type, 35/-

Specials to requirements. SOUNDMASTER SPECIALS.-Mains Trans., 35/-; L.F. Choke, 10/8, O/P Trans., 6/8, Envelope, 6/8. Specified Water Switches, 2/6 per set of 3.

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-


CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-

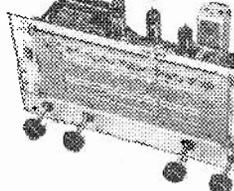CRYSTAL DIODE.-Very sensitive. G.E.C., 2/-; WOULDERS.-Fax: Int. Oct., 4d.; EF50, EA30, 6d.; B12A CRT, 1/3. Moulded: Int. Oct. 7d.; B7G, 9d.; with screening can, 1/8; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, BTG, 1/-; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-



ALL WAVE RADIOGRAM CHASSIS THREE WAVEBANDS FIVE VALVES

M.W. 16 m.-50 m. LATEST MIDGET L.W. 200 m.-350 m. B.V.A. SERIES. Brand New and Guaranteed. A.C. 200/250 v. Four position Wavechange Switch. Short-Medium-Long-Gram. Slow Motion Tuning. Speaker and Pick-up connections. High Q Iron-dust core coils, 465 Kc/s. L.F. Latest circuit technique, delayed A.V.C. and Negative feedback. Output approx. 4 watts. 3 ohm output transformer on chassis. Chassis size 13 x 5 1/2 x 2 1/2 in. Glass Dial-10in. x 4 1/2 in. horizontal or vertical type available. Hit by 2 Pilot Lamps. Colour Black Station names, L.W. Green. M.W. Red. S.W. White. Four Knobs supplied. Walnut or Ivory to choice, aligned and calibrated. Chassis isolated from mains. PRICE £9.15.0 Carriage and Insurance, 4/6. 8in. or 10in. speakers to match available.

RADIO CHASSIS KIT

All components available for building up chassis as per illustrated photo above. Printed and punched chassis 13 1/2 in. x 5 1/2 in. complete with fixing brackets, backplate and dial 10in. x 4 1/2 in. Tuning Drum, Pulleys, Pointer Spring, Drive Cord, etc., 22/6. P. & p. 2/6. Mains Trans., 2/6; L.F. Trans., 10/6 pr.; Twin Gang, 8/6; Coils, 2/6 ea., etc., etc.

BARGAIN VALUE IN RECORD CHANGERS

Recommended for above chassis B.S.R. MONARCH. 3 sp. Auto Changer. Plays Mixed 7in., 10in. and 12in. records. Twin Sapphire Stylus. As used by leading Radio Gram Manufacturers. Brand new, boxed and guaranteed. Listed, £10/10/0. Our Bargain Price 10 gu., carriage 4/6. Plessey 6-speed Autochanger Mixer Unit for 7. 16 and 15in. Records. Twin Hi-Fi Head with Dupoint sapphire stylus. Plays 4,000 records. Sprung mounting. Superb Quality. Bargain Price 9 1/2 gu.

NEW BOXED VALVES GUARANTEED ALL

Table listing various vacuum tube models and their prices, such as 1R5, 1R57, 1T4, 184, 354, 3V4, 3D5, 5Z4, 6AM0, 6AT6, 6CH6, 6HY, 6K8, 6X4, 6X5, 6X6, 6X99, 6X100.

SPECIAL PRICE PER SET 1R5, 1T4, 1R5 and 354 or 3V4 ... 27/6 6K8, 6K7, 6K7, 6V6, 6V6, 6V6 or 6X3 ... 35/-

3 VALVE AMPLIFIER

With variable Tone and Volume controls. 3 Midget B.V.A. valves. 4 watts output. Neg. feedback. Chassis isolated from mains. A.C. 200/250 v. A quality amplifier at an economical price. Price £3.19.8. Carr. 2/6. Wired and tested, 7/6 extra. Circuit and instr. free.

WAVECHANGE SWITCHES.-Midget type, single-wafer. 2 pole, 2-way, 3 pole 2-way, 2/6 ea.; 1 pole 12-way, 2 pole 6-way, 3 pole 4-way, 3/6 ea.; 4 pole 2-way, 4 pole 3-way, 2/6 ea. 2 WAFER TYPE.-3 pole 4-way, 6/9.

CONDENSERS.-Mica, S. Mica, Ceramics. All pref. values. 3 pf. to 680 pf., 6d. ea., 5/- doz. Tubulars, 450 v., Hunts and T.C.C. .0005, .001, .005, .01, .02 and 1.350 v., .01, .05, 1.500 v. Hunts Moldcase, U.-.25 Hunts, 1/6, .5 Hunts, 1/9, 1.1, 900 v. T.C.C. (Simplex), 3/6, .001, 6kV, T.C.C., 5/6, .001 12.5 kV. T.C.C., 8/6.

SILVER MICA CONDENSERS.-10%. 5 pf. to 500 pf., 1/- 600 pf. to 5,000 pf., 1/3. DITTO 10% (ex stock). 1.5 pf. to 500 pf., 1/8. 515 pf. to 5,000 pf., 2/-.

ELECTROLYTICS ALL TYPES NEW STOCK

Table listing electrolytic capacitor values and prices, such as Tubular Wire ends, 8 + 16450 v. Hufs 5/-, 25/25 v., 30/12 v., 1/9, 8 + 16500 v. Dub. 5/6, 50/50 v., 4500 v., 2/-, 16 + 16450 v. B.E.C. 5/6, S/500 v., Dub., 2/6, 16 + 16500 v. Dub. 6/6, 8 + 8500 v. Dub., 4/6, 32 + 350 v. B.E.C. 4/-, 8 + 16 450 v. Hunts 5/-, 82 + 32450 v. B.E.C. 6/6, 16 + 16 450 v. B.E.C. 3/6, 60 + 100 250 v. 11/6, 60 + 200 275 v., 12/6, 32 + 350 v. Dub., 5/6, 100 + 200 275 v. B.E.C. 4/6, 32 + 32350 v. B.E.C. 5/6, 1500 6 v. B.E.C. 2/6, 32 + 32 300 v. Dub. 7/6, 1000 + 1000 6 v. B.E.C. 6/6, Can Types, Clips, 3d. ea., 8 + 8450 v. T.C.C. 4/6, 500 mfd. 12 v., 3/-

SENTECEAL RECTIFIERS. E.H.T. TYPE 12V4-3.2 kV. BACK VOLTAGES.-K3/25 2 kV., 4/3; K2/40 3.2 kV., 6/-; K3/45 3.6 kV., 6/6; K3/50 4 kV., 7/3; K3/100 8 kV., 12/6; K3/160 14 kV., 18/-. MAINS TYPE.-RM1, 125 v., 60 ma., 4/-; RM2, 100 ma., 4/9; RM3, 120 ma., 5/8; RM4, 250 v. 275 ma., 18/-. ENGRAVED CONTROL KNOBS for 4in. Spindle, 1 1/2 in. diam. Walnut or Ivory. Gold Filled. "Focus", "Contrast", "Brightness", "Brilliance", "On-Off", "Brilliance-On-Off", "Record-Play", "Vol.-On-Off", "Volume", "Tuning", "Tone", "Wavechange", "Trebble", "Bass", "S.M.L. Gram", "Radio-Gram", 1/6 ea. Plain knobs to match above, 1/10, ea., 4in. dia., 8d. ea. Superior Unmarked Knobs with Gold Ring, Walnut or Ivory, 1 1/2 in., 1 in., 8d. ea. Pointer Knobs, Black with White Line, 8d.

WEARITE "P" TYPE COILS. All ranges. 1 to 7. 2/6 ea. Osmor Q series Coils. Stung tuned. All ranges from 3/6. Allen Coils L. M., S. Aerial and Osc. Just core tuned. 2/6 ea.

REACTION COND.-0001, 0003, 0005 mfd., 3/6 ea.

I.F. TRANSFORMERS. 465 K/c.s.

Plessey Semi Midget, 6/9 pr. Allen Standard Size, 10/6 pr. Wearite Standard Size 50L, 12/6 pr. Wearite Midget M800, 15/6 pr.

ALUMINIUM CHASSIS.-18 s.w.g. Plain, un drilled, folded 4 sides and riveted corners

lattice fixing holes. Strong and soundly constructed with 2 1/2 in. sides. 7in. x 4in., 4/6; 8in. x 6in., 5/9; 11in. x 7in., 6/9; 13in. x 8in., 8/6; 14in. x 11in., 10/6; and 18in. x 16in. x 3in., 16/6.

CHARGER TRANS.-Prim. 500-250v., Sec. 0-9 v.-15 v. (for charging 6 v. and 12 v.) 1.5 a., 13/6, 2a., 16/-; 3 a., 18/6; 4 a., 21/-; 6 a., 26/-.

FULL WAVE BRIDGE SELENIUM RECTIFIERS. 6 or 12 v. 1 1/2 amp., 8/9; 2 1/2 amp., 11/3; 2 1/2 a., 12/-; 4 a., 15/6; 5 a., 20/6. 13 v. 4 a. P.V. only, 4/6. CARBON MIKE INSERT.-Superior quality type. 2 1/2 in. x 1 in. Brand new and boxed only 3/6 each. BRIMISTONS.-CZL for CZa heater chains, 3/6. CZ2 for 1.5 a., or 2 a., 2/6. CZ3 (Pilot Lamp), 1/6.

COPPER ENAMEL WIRE.-1 lb. 15 to 50 s.w.g., 2/-; 22 to 28 s.w.g., 2/6; 30 to 40 s.w.g., 3/6. SWITCH CLEANER Fluid, squirt sprig, 3/9 tin.

TWIN GANG TUNING CONDENSERS.-375 pf. Midget, 6/6; ditto, with dust cover and trimmers, 8/8; .0005 mfd. Standard size with feet, 8/6; ditto, with trimmers, 9/6.

RECORDING TAPE.-Scotch Boy 1,200 ft. reels, 30/- each. Spare spool, 5in., 3/8; 7in., 4/3. LOUDSPEAKERS P.M., 3 OHM. Richard Allen, 5in., 10/6; 6in. Goodmans, with trimp., 21/6; 8in. Goodmans, 17/6; 7in. Elliptical, 18/6; 8in. Goodmans, 15/6; 8in. Eloc., 20/-; 10in. Plessey, 25/-; 12in. Plessey, 37/6.

T.R.S. RADIO COMPONENT SPECIALISTS (THO. 2188) Now at 70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY

PLEASE NOTE OUR NEW AND ONLY ADDRESS

BIGGER PREMISES BETTER BARGAINS

Buses 130A, 133, 159, 166 Send 3d. stamp for Bargain Lists Hours: 9 a.m.-6 p.m. | p.m.-Wednesday. OPEN ALL DAY SATURDAY.

N.B.-Terms C.W.O. or C.O.D. Post/Packing up to 1 lb. 6d., 1 lb. 1/-, 3 lb. 1/3, 5 lb. 2/-, 10 lb. 2/6.

# VIEWMASTER AND SIMPLEX KITS

ON EXTENDED PAYMENTS

**Only 3/- in the £ Deposit**

## ★ SIMPLEX ★

Six-inch kit, less tube. Deposit **£2.11.0** and 12 monthly payments of **£1.5.9**.

Conversion to Twelve-inch kit, less tube. Deposit **£2.6.0** and 12 monthly payments of **£1.4.1**.

Twelve-inch kit, less tube. Deposit **£4.10.0** and 12 monthly payments of **£2.5.10**.

## ★ VIEWMASTER ★

Nine- or Twelve-inch kit, less tube. Deposit **£5.8.6** and 12 monthly payments of **£2.15.10**.

Wide Angle Model, less tube. Deposit **£6.6.0** and 12 monthly payments of **£3.5.6**.

Full details of these Kits are given in our lists which will be sent free upon request.

## WATTS RADIO

8, Apple Market, Kingston-on-Thames, Surrey.

Telephone : KINGston 4099.



## QUALITY TELEVISION COMPONENTS

SCANNING COILS

6/10 kv. R.F., E.H.T. UNITS

E.H.T. and OUTPUT TRANSFORMERS  
LINE FLY-BACK E.H.T. UNITS

Write for illustrated list (Publication 75)

**HAYNES RADIO Ltd.,** Queensway, Enfield, Middlesex.

**IT'S 60% CHEAPER!!**

to construct your own aerial, whether  
**TELEVISION or YAGI**

Write for our catalogue, illustrating all fittings, prices, etc. Included in the range we offer Alloy Masts, Insulators, Reflector and Director rod holders, Mast head fittings, together with formulae, useful construction hints for designing your own aerial, etc.

Send 9d. in stamps to cover the cost of postage and catalogue to :—

*Fringlevision Ltd.*

MARLBOROUGH, WILTS.

Phone 605.

MONEY BACK  
GUARANTEE

**DUKE** *E.CO*

Tele: GRA 6677

CWO  
OR  
COD

621 ROMFORD RD. LONDON. E.12.

### RADIO-GRAM CHASSIS

29/9. Including Speaker.

5 valve s/het., 3 w/band. A.C. mains, complete, but less valves and dial. All used, tested guaranteed. P. & P. 4/6. Drawings 2/6 or free with order. Knobs, 1/6 set extra. Complete with valves. 97/6.

**RADIO CHASSIS, 7/9.** A.C. or universal, s/het. receivers. Less valves, dial and electrolytics. Otherwise believed to be in working order. Note—our 8in. M.E. speaker fits some of these sets. We match on request with order. P. & P. 3/6.

**RADIO CHASSIS, 14/9.** As above, with 3-band coil packs. 465 I.F.s. All used bargains. P. & P. 3/6.

**SPEAKERS, 12/9.** 8in., 6in., 5in. or 3in. std. P.M. 3-5 ohms, or with O.P. trans. 14/9. Used, tested guaranteed. Post 1/9.

**SPEAKERS, 2/9.** 8in. M.E. field 1k, 2k, 5k ohms. With O.P. trans. 4/9. Post 1/9. Used, tested guaranteed.

**V.H.F. RECEIVER, 1124.** 17/6, with 6 valves. X.W.D. New condition. 6 channel switching. Receives T.V. sound, police, fire and amateurs. 30.5 to 40 mc/s. I.F. 7 mc/s. Post 2/6. Drawings and conversion data free with each set.

**V.H.F. 1125 SET, 7/9.** New and boxed. This little set is a V.H.F. receiver. Requires modification to put it into service. Complete with valves. Post 2/-.

**R.F. UNIT 24.** 12/6. New and packed, tuning 20-30 mc/s. Including 3 valves. Post 2/-.

**12" T.V. TUBES** £5, 14" £8.10., 17" £12.10, guaranteed 6 mths. Ins. carr; 15/6. C.W.O. 12" Mullard, 6 mths. guar. Other makes 3 mths. guar.

**(O.P.) TRANSFORMERS, 1/9.** Used, tested, guaranteed. Std. size. Post 9d.

**2 GANG CONDENSERS, 2/9.** Std. size .0005, used, tested guaranteed. Also 3 gang, 2/9; post 9d.

**T.V. CONDENSERS, 12/6.** Electrolytic, 120 mfd.+64 mfd. 350 volt. Post 1/-.

**MAINS TRANSFORMERS, 5/9.** 350-0-350 v., 12 v.+4 v. Primary, 100, 120, 200, 250. Make ideal auto trans. Post 2/-.

**AMPLIFIERS, 57/6.** 3 valve, 4 watt output, A.C. or universal. Post 2/6.

**AMPLIFIERS, 77/6.** 4 valve, 7 watt output, A.C. or universal. Post 3/6.

**AMPLIFIERS, 97/6.** 5 valve, 10 watt output, A.C. only, with extra pre-amp. stage, 3 controls. Post 3/6.

2d. stamp only for complete catalogue.

## HOME RADIO OF MITCHAM

offer

BIB wire cutters and strippers ... ..	3/6
MULTICORE solder, 14 or 18 s.w.g. ... ..	per box 5/-
PAN crackle paint, brown, green, black ... ..	per tin 3/-
SWITCH cleaner with sputum ... ..	per tin 3/9
SOLON 825 instrument soldering iron ... ..	19/8
CO-AXIAL CABLE, new, semi-airspaced ... ..	per yd. 9d.
GRAM SPEED INDICATOR, 33, 45 and 78 r.p.m., A.C. mains ... ..	1/6

### VALVES

VR91 (EF50), ex equipment, all tested ... ..	6/6
EF50, New and Sealed ... ..	11/6
EB34 (ARDD5), Guaranteed ... ..	2/6
EF39 (ARP34) ... ..	5/-
PEN25 (CV65) ... ..	3/6
HL23DD (AR8) ... ..	3/6
VP23 (ARF12) ... ..	3/6

All components stocked for Viewmaster and Teleking. etc.

### HOME RADIO

187, London Road, Mitcham, Surrey. MIT 3282

## NEW-MAX ELECTRONICS LTD.

307, EDGWARE ROAD (JUST PAST THE MET.)

Tel. : PAD 5607

London's Best T.V. and Radio Bargain Store

We have just completed a large purchase of used and H.P. repossessed T.V. sets—all types and all sizes—to be sold at knock-out prices. Special item : 1807 H.M.V. 10in. chassis adapted to be used with Mazda 12in. tube, £19/10/-, including tube. Also large selection of used radios, gram chassis, instruments, amplifiers.

## TAPE RECORDERS, ETC.

STOP PRESS!—Special Offer : T.V. Tubes—All Sizes : 9in., £4; 12in., from £4/10/-; 14in., £6; 15in., £7. Every tube guaranteed.

Callers can see picture before purchase.

# TELENEWS

**Television Liaison Officer**

**MR. JOHN ELLIOT**, producer of the series of BBC television films, "War in the Air" has been appointed Television Liaison Officer to the film division of United Nations in New York and took up his appointment for a term of one year on March 14th.

Mr. Elliot hopes to return to BBC television in April, 1956.

**May Lose Licence.**

**MR. GAMMANS**, Assistant Postmaster-General, said in the House of Commons recently that the owner of a television receiver that caused interference to sound radio reception is liable to have his licence withdrawn if the trouble is not rectified.

**Television Licences**

**THE** following statement shows the approximate number of television licences issued during the year ended March, 1955. The grand total of sound and television licences was 13,980,496.

Region	Number
London Postal ... ..	1,124,779
Home Counties ... ..	488,030
Midland ... ..	824,752
North Eastern ... ..	653,220
North Western ... ..	653,644
South Western ... ..	246,697
Wales and Border Counties ... ..	244,816
<b>Total England and Wales ... ..</b>	<b>4,235,938</b>
Scotland ... ..	244,020
Northern Ireland ... ..	23,808
<b>Grand Total ... ..</b>	<b>4,503,766</b>

**School Extension**

**A** NEW dormitory block is being added to the BBC's Engineering Training School at Wood Norton Hall, near Evesham.

This will mean accommodation for another 90 to 100 members of the BBC staff attending the residential engineering courses, bringing the total capacity of the school to about 200.

**"Live" Sport Better**

**TELEFILMS** of soccer matches show that in addition to the slightly hazy picture effect, the ball appears to move in rather jerky movements as compared with "live" transmissions of matches.

Thus, telefilming major sporting events is only second best to an actual broadcast.

**Channel Islands Station**

**WORK** is progressing on the BBC television station at Les Platons, Jersey, which is to serve the Channel Islands. It will probably be ready for service by September, although at first the transmissions may not be up to the final standard because the link from the mainland may not be reliable until the permanent station at North Hessary Tor in Devon is completed at the end of the year.

**Agreement for Artists**

**THE** Variety Artists' Federation have agreed with the BBC that V.A.F. members may be engaged for broadcasts to be given simultaneously in sound and television, subject to the assurance which has been given by the BBC that the fee shall take into full consideration the demands likely to be made on the artiste by way of rehearsal, material, etc., by the TV medium.

**Bob Hope for Commercial TV.**

**THE** Associated Broadcasting Company announce that they will be presenting two big Sunday

night shows when commercial television begins in September.

One will be a 60-minute variety programme, "Sunday Night at the Palladium," for which Bob Hope, Norman Wisdom and Gracie Fields have been contracted; the other a series of 30-minute filmed playlets entitled "Theatre Royal." The artistes signed for these short plays include Sir Ralph Richardson, Eric Portman and Wendy Hiller.


**Charge for Aerial**

**TELEVISION** viewers wishing to erect aerials on Bootle Corporation property are to be charged a premium of 1s. 6d. per annum.

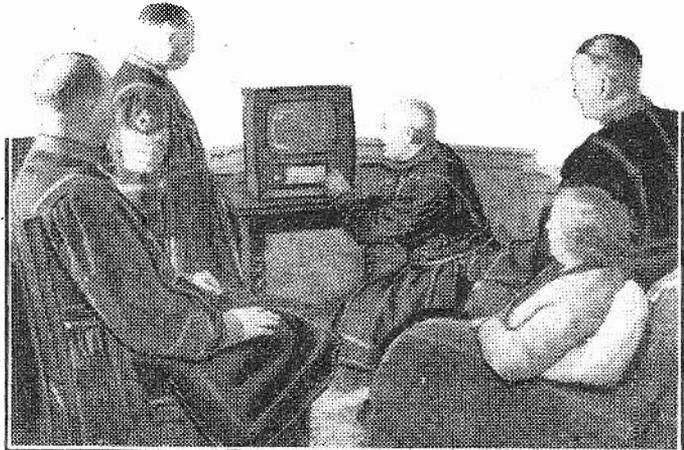**BBC Buy Film Cameras**

**BRITISH ACOUSTIC FILMS LTD.**, have received an order from the BBC for the manufacture of 12 combined sound and picture film cameras.

The new cameras, for which the BBC is preparing its own specification, will produce either a 35 mm. picture film with a separate 35 mm. magnetic sound track or a 16 mm. picture film with a separate 16 mm. sound track. The picture section of each instrument will consist of a Cameflex 35/16 mm. camera.



Yeomen Warders off duty at the Tower of London spend some of their spare time "looking in." All H aerials have disappeared from the Tower and a new E.M.I. central aerial system has been installed.

### New Aerialite Factory

WE learn from Aerialite, Limited, that they have bought a new factory specially for the manufacture of television aerial equipment, converters and electronic components.

The factory is sited at West End, Congleton, Cheshire.

### German Exhibition

THE German Radio, Television and Gramophone Industry Exhibition this year will be held for 10 days from August 26th to September 4th.

The show will be sited in the big Düsseldorf exhibition park on the bank of the Rhine.

### Microwave Link

THE G.E.C., Ltd., has supplied the equipment for another microwave radio-television link in Switzerland. It connects Uetliberg (Zurich) with La Dole (Geneva) and on the way ties in with the trans-Alpine Chasseral-Monte Generoso link, which was supplied by the G.E.C. one year ago for

the Eurovision exchange of programmes.

The new link forms part of a TV network to cover most of Switzerland.

### Ship Communications

CLOSED circuit television is being installed in a ship of the Canadian Royal Navy by Pye (Canada), Ltd. The intention is to communicate visually to various key points in the ship tactical information that has hitherto been transmitted by telephone.

A camera in the Operations Room will be focused on the plotting chart upon which the movements of enemy aircraft, surface or undersea craft as well as those of friendly ships may be recorded.

### Tests at Sea

TELEVISION reception tests at sea have been made recently by the *Loch Carron*, a Clyde cargo boat which carried an experimental receiver on its journey among the coastal islands on the west coast of Scotland.

### New BBC Mast

A 240ft. erecting crane was placed in position at the Crystal Palace in south-east London recently in readiness for the construction of a new BBC television mast.

The mast, the largest of its kind in this country, will be 640ft. high, 700ft. with the aerial extension, and will be situated over 1,000ft. above sea level.

### Sales Drive in Europe

PYE, LIMITED, held a series of demonstrations of industrial and underwater tele-



Grand old character actor Bransby Williams, who returned to television during May under producer Kenneth Milne-Buckley.

vision at the Kongresshaus in Zurich early in May. Prominent businessmen from all over Europe were invited to the demonstrations, which were designed to show how the technique of television can be applied to assist production in modern industry.

### North Scotland Transmitter

THE BBC has acquired a site for the proposed north of Scotland television station, to be known as Rosemarkie. It is about 11½ miles from Inverness and covers an area of six acres.

The new station is expected to be ready for service by the end of 1956.

### Master Aerials

COMMUNAL television aerials may be erected by the Brighton Corporation on corporation flats.

### Engineering Division Appointment

THE BBC has appointed Mr. T. P. Douglas, M.B.E., as Engineer in Charge, Sutton Coldfield television transmitting station.

Mr. Douglas joined the BBC in 1938 as a junior maintenance engineer at the Daventry transmitting station.



Workmen operating a winch by one of the giant base plates, which goes 40ft. under the ground and will take one of the four legs of the aerial. (See a New BBC Mast.)

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

## COVENTRY RADIO

189, DUNSTABLE ROAD,  
LUTON, BEDS.

Phone : Luton 2677

The Quality Component Specialists offer you Kits of Parts for the following :—

- |                              |        |       |
|------------------------------|--------|-------|
|                              | Manual |       |
| Osram "912" Amplifier        | ...    | 3/6   |
| Mullard 10-watt Amplifier    | ...    | 3/6   |
| The Coventry                 |        |       |
| 2-watt Amplifier             | ...    | } 1/- |
| 4-watt Amplifier             | ...    |       |
| 6-watt Quality Amplifier     | ...    |       |
| The Coventry A.M. Tuner Unit | 1/-    |       |
| Denco F.M. Tuner Unit        | ...    | 1/6   |

Complete Component Price Lists will be supplied with each Manual.

Have you had a copy of our 1954/5 60-page illustrated Component Catalogue, price 1/- plus 3d. postage ?

## RADIO & TELEVISION COMPONENTS

Brand new and guaranteed by the leading makers. Orders dealt with by return.

**VIEWMASTER. TELE-KING, ETC.**  
Constructional manuals : Viewmaster, 7/6. Viewmaster Wide Angle Conversion, 3/6. Tele-King, 6/-. Mullard 5 valve 10 watt amplifier, 2/6. Osram 912 12 watt amplifier, 3/6.

FREE CATALOGUE.

56 page illustrated on fine art paper.

**SOUTHERN RADIO & ELECTRICAL SUPPLIES**  
SORAD WORKS, REDLYNCH,  
SALISBURY

Telephone : Downton 207.

## Television, Radio, Record CABINETS MADE TO ORDER

ANY SIZE OR FINISH  
CALL OR SEND DRAWINGS FOR QUOTATION

**B. KOSKIE**

(DEPT. B)

72-76 Leather Lane,  
Holborn, E.C.1

Phone : CHAncery 6791/2

## OUTSTANDING SCIENTIFIC BOOKS AT ONLY A FRACTION OF THE NORMAL PUBLISHED PRICES !

# Save Money ! Join The Scientific Book Club

You Buy Books published at  
**10/6, 12/6, 15/- for ONLY 3/6**

Each month the Scientific Book Club brings to its members the fascinating story of the march of modern science, told in thoroughly dependable books by the front-rank scientific writers of our time—vivid, vital, constructive contributions to Man's unceasing struggle to solve the problems of the Universe. And, although the ordinary editions of these books are sold to the general public for 10s. 6d., 12s. 6d. and 15s., THE PRICE TO MEMBERS OF THE SCIENTIFIC BOOK CLUB IS ONLY 3s. 6d. Remember, too, that Scientific Book Club selections are full-length, unabridged. These are, we say with certainty, books that you will be glad to read, proud to own. The Scientific Book Club brings these great books to you each month; helping you to build up, at a *sensational bargain price*, a first-class collection of scientific books. *Now is the time to join !*



## YOU SAVE £3 12s. ON THESE BOOKS ALONE !

Recent and forthcoming selections—at only 3s. 6d. to members—include INTO SPACE by P. E. Cleator (Published at 15s.); THE ART OF SCIENTIFIC INVESTIGATION by W. I. B. Beveridge (10s. 6d.); THE SCIENCES OF ENERGY by J. G. Crowther (12s. 6d.); DON QUIXOTE OF THE MICROSCOPE by Harley Williams (15s.); LADY WITH A SPEAR by Eugenie Clark (12s. 6d.); V2 by Major-Gen. Walter Domberger (16s.); WAYS OF THE ANT by John Crompton (15s.); *All wonderful value !*

### FILL IN THIS ENROLMENT FORM TODAY

To the Scientific Book Club, 121 Charing Cross Rd., London, W.C.2

I wish to become a member of the Scientific Book Club and agree to purchase the special edition of the selected book issued each month to members at a cost of 3s. 6d. (postage 6d.). I agree to continue my membership for a minimum of six books and thereafter until countermanded.

Practical Television/June 55

\*I will pay for selections on receipt.


Or if you wish to save time, postage and postal-order costs, you may send an advance subscription. Six months 24s. 0d.; twelve books, 48s. 0d.

\*I enclose 24s./48s. (strike out amount not applicable).

\* Place ✓ in the space above, as required.

NAME .....  
(BLOCK LETTERS PLEASE)

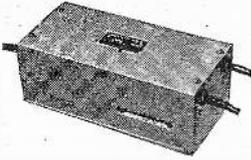ADDRESS .....  
Overseas enrolments must be accompanied by an advance subscription.



**CONVERTOR TYPE 26.**  
For conversion from channel 3 to channel 1, complete with self contained power supply unit and totally enclosed in a handsome, well finished steel case. Price complete .....£11-17-0

\*Also available in chassis form less H.T. supply but including mains operated heater supply for inclusion in receivers. Price complete .....£8-0-0

**CONVERTOR TYPE AC/4**  
For weak signal areas. Price complete .....£15-15-0

(Leaflets on request)

**SPENCER-WEST**  
**QUAY WORKS,**  
**Gt. YARMOUTH.**

Tel. : 3009. \*Grams : Spencer-West, Gt. Yarmouth.

**TELEVISION COMPONENTS**

always in stock for the  
**P.T. LYNX, TELE-KING**  
**P.T. SUPER-VISOR**  
**THE E.E. TELEVISOR**  
**VIEWMASTER**  
**AND WIDE ANGLE**  
**MODIFICATIONS**

Separate price lists available free on request to

**J. T. FILMER,**  
Maypole Estate, Bexley, Kent  
Tel. : Bexleyheath 7267

**ALUMINIUM, LIGHT ALLOYS,**  
**BRASS, COPPER, BRONZE,**

IN ROD, BAR, SHEET, TUBE, STRIP, WIRE, ANGLE, CHANNEL, TEE

3000 STANDARD STOCK SIZES

**H. ROLLET & CO., LTD.**  
6, CHESHAM PLACE, LONDON, S.W.1.  
SLOane 3463

Works :  
33, ROSEBERY AVE., LONDON, E.C.1.  
Branches at Liverpool, Manchester, Birmingham, Leeds.

"No Quantity too Small"

**VALVES**


**SAME DAY SERVICE**

**All Guaranteed New and Boxed**

1.4v. miniatures, 1R5, 1S5, 1T4, 3S4, DAF91, DF91, DK91, DL92, 7/3 : any 4 for 27/6.					
1A7GT	6K25 11/9	35Z5GT8/6	EZ41	9/-	
1C5GT	11/6 6L6G 10/6	50L6GT8/6	FC2	9/6	
	6LD20 9/6	80	8/6	GZ32	15/-
1D5	11/6 6P23 14/8	AZ31	10/6	KT63	7/6
1H5GT	11/6 6P28 18/6	B36	18/6	KT68	11/6
	6Q7GT 9/-	CL33	12/6	MU14	9/-
1NSGT	11/6 6SN7GT 8/6	D1	3/6	N78	14/6
		D77	6/9	P61	3/6
		DAC32	Pen45	15/-	
1R5	7/3			PCC84	10/-
1S5	7/3 6V6G 7/6	DF33	11/6	PCF80	
1T4	7/3 6V8GT 7/8	DH77	8/6		
3Q5GT	11/6 6X4 7/8	DK32	11/6	PL33	11/6
3S4	7/3 6X5GT 6/9	DK92	7/6	PL81	11/6
3V4	8/6 7B7 8/3	DL33	11/6	PL32	9/6
5U4G	8/6 7C3 8/6	DL33	11/6	PL33	12/6
5Y3GT	7/9 7C3 8/6	EB91	6/9	PY80	9/6
5Z4G	9/- 7H/ 7/6	EBC33 7/5	PY81	10/-	
6AL5	6/9 7S7 7/8	EBC41 10/-	PY82	7/9	
6AM5	6/8 7Y4 8/3	EBF80	PY30	17/-	
6AM6	6/8 10C1 12/6		TS1	13/-	
6AT8	8/6 10F1 13/-	ECC81 9/-	U22	7/6	
6BA8	8/6 10P13 10/-	ECC83 9/-	U24	17/6	
6BE6	6/6 10P14 12/6		U25	12/-	
6BH6	6/6 12AT7 9/-	ECC31 7/-	U50	7/9	
6BJ6	6/6 12AU6 7/8	ECH35	U78	8/3	
6BW6	7/6 12AU7 10/6		U81	10/-	
6BW7	9/6 12J7GT 10/6	ECH42 10/-	U404	9/-	
6C4	7/8	ECL80 9/6	UBC41 9/-		
6C9	8/3 12K7GT9/6	EF37A	UBF80		
6E1	19/3 12Q7GT			14/6	10/3
6F6G	7/8	EF37	6/6	UCH42 9/9	
6E12	6/3 12SK7 6/6	EF41	8/6	UF41 8/6	
6E13	19/6 20F2 11/6	EF55	7/8	UF42 13/6	
6E14	12/- 20P1 17/-	EF80	10/-	UL41 9/9	
6J6	7/6 25L6GT	EF91	6/3	U66 10/6	
6J7GT	7/8	EF92	5/-	U68 17/-	
6K7G	6/- 25Z4G 9/-	EL41	11/6	UY41 9/-	
6K7GT	6/- 25Z5 8/6	EL81	6/6	W71 5/-	
6K8G	8/6 35L6GT8/6	EY51	12/-	Y63 7/6	
6K8GT	9/- 35Z4GT8/6	EZ40	8/6	Z77 6/3	

**READERS RADIO**  
24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA. 4587

**SUPERB CABINETS**

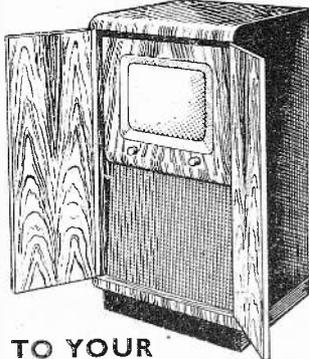

**TO YOUR OWN SPECIFICATION**

Supplied in Wainut, Oak, Mahogany or to order. Expertly hand-made and beautifully polished. Cabinet as illustrated with full length doors £17.10.0, or with half length doors £15.10.0. Other models without doors £12.7.6 and £16.10.0.

Send 1/- for complete catalogue of cabinets, etc. (Refunded on receipt of order.)

**LEWIS RADIO COMPANY**

(Dept. S.1.) 120, GREEN LANES, PALMERS GREEN, LONDON, N.13.  
Phone : BOWes Park 6064.

**FIRST-CLASS TELEVISION and RADIO COURSES . . .**

**GET A CERTIFICATE!**

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

**FREE GUIDE**

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., etc., together with particulars of our remarkable Guarantee of

**SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER

150,000 SUCCESSSES.

**NATIONAL INSTITUTE OF ENGINEERING**

(Dept. 462), 143, HOLBORN, LONDON, E.C.1.

**HIGH GRADE TRANSFORMERS**

FOR ALL PURPOSES  
SINGLY OR IN QUANTITIES  
TO YOUR SPECIFICATION  
VARNISH IMPREGNATED  
BAKED WINDINGS  
WITH OR WITHOUT TAG PANELS  
GOOD DELIVERIES

Our rewind dept. will handle your repairs promptly and efficiently.


S.A.E. with enquiries please.

**P. HOWORTH**

(Dept. P.T.)

51 POLLARD LANE • BRADFORD

Tel. : 37030

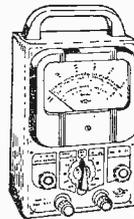

**PULLIN**  
SERIES 100  
**TEST METER**  
AC/DC 10,000 Ω/V  
21 RANGES  
100ΩA to 1000 V

COMPLETE IN DIE-CAST CASE WITH TEST LEADS  
CLIPS AND PRODS  
FULLY GUARANTEED

SENT POST FREE FOR £2.10s.

DEPOSIT AND TEN FURTHER MONTHLY PAYMENTS OF £1. CASH PRICE 11gns

**Frith**  
**RADIOCRAFT Ltd**  
PHONE 58927  
69-71 CHURCH GATE LEICESTER

# CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

## STEREOPHONIC-STEREOSCOPIC TV

**SIR**,—I should like to inform other readers, through the medium of your correspondence columns, of a most startling effect that can be derived from television viewing and which is almost akin to a visit to the best West End cinemas so far as technical "gimmicks" are concerned.

A friend of mine told me that by looking at his TV set through the narrowed slits between his fingers, he had been amazed to find that it produced a three-dimensional effect and that sometimes he obtained the same results by merely screwing up his eyes and squinting at the picture. I told him I had heard vaguely of that "stunt" before but did not believe him. On arriving home, however, I was just in time for the Cambridge-Oxford Boat Race and decided to try out the theory. At first the picture seemed the same, but after a little while I found that the 3-D effect was there and bridges and trees along the course stood out clearly.

That same evening I had an inspiration. I switched on "In Town Tonight" on my TV receiver and also on my sound radio set. I sat midway between the television and the radio and was thus able to enjoy the wonder of stereophonic-stereoscopic viewing. Too much at a time of course tires the eyes, but the sensation is really remarkable.—A. REES (Cardiff).

## VIEWING TIP

**SIR**,—If any other reader is plagued with neighbours and relations practically every evening as I am, just to see television, he might be interested in a little hint on the accommodation of the "invaders" so that all are in a comfortable viewing position. Silence will then prevail and enable the owner of the set to look in himself without disturbance.

I have fixed a large sloping mirror to the wall opposite the TV screen so that those people who normally have to stand to see over the heads of the other "invaders" can sit on the floor with their backs to the set itself and view the programmes via the mirror. This system actually works very well and viewing conditions have been much quieter since I first introduced it. Now that commercial TV is in the offing I suppose my potential audience is likely to increase, in which case I may have to buy a larger mirror. Or, of course, I can always sell the set.—"CRUSHED VIEWER" (Birmingham).

## BAND III RESULTS

**SIR**,—It may be of interest to your readers who have built their own T.R.F. Television Receivers that I have been able to pick up quite a strong signal from the new Beulah Hill I.T.A. Station, using a Band III TV Converter Type C1, manufactured by Channel Electronic Industries of Burnham-on-Sea, Somerset. The set I am using is an "Electronic Engineering."

I was rather surprised at receiving it without any adaptor on my Dublex aerial, and at the same time without any modification to the coils in the set. I am working on top contrast for Band I, and when switching over to Band III I received a steady picture showing clear outlines. I realise I am within 4.5

miles of the transmitter, but as you know this is on very low power.

The converter uses its own power pack and is easily fitted with coaxial plugs, and retails at 9 gns.—K. FIGG (Croydon).

## CONTINUOUS SPORT

**SIR**,—For the first time this year I have been looking at an afternoon's tennis on television. Although I quite enjoyed it, I have great misgivings when I think that this is only the beginning of what we were given last year and the year before—that is, so much sport that not only are we tired of looking at two hours of the same game continuously but other programmes will probably be affected as well.

I remember last year when after two and a half hours of tennis Children's Hour was due to begin. Instead of giving the children the scheduled programme, the announcer said with a smile: "I am sure the children will all want to know how the tennis match finishes, so we will stay at Wimbledon for another fifteen minutes or so."

Let us have sporting programmes by all means, but let them be in digestible doses.—A. REES (Croydon).

## AN UNUSUAL FAULT

**SIR**,—Recently, when watching my television set, I was struck by a fault which consisted of intermittent flashing across the screen. As it persisted I realised that the flashing occurred at regular intervals and, having no time-piece handy with a seconds hand, I counted my heart beats and found that the interference occurred at the end of a period of 35-36 heart beats (with a subsequent speed-up to 37-38, as the effect of having discovered something caused a slight increase in the heart rate).

Having established that the 30 second interval remained constant, I looked for the source of the trouble and found that a large public electric clock situated 120 yards away was the offender.

The dial of this clock is illuminated by a lamp having a screw base, the holder of which is fitted inside the hollow spindle carrying the hands. Owing to the lamp being loose in the holder the dial was not illuminated, but the lamp flashed each time the minute hand vibrated the holder as it jumped a half-minute space on the pulse from the master clock, thus causing interference over a very large area.—F. J. H. WOOD (Maidstone).

## AMPLIFIER TYPE 178

**SIR**,—I should like to express my thanks for the aid which your paper has given me, and also in the pleasure which has resulted therefrom. I have had several pieces of ex-Government equipment hanging about for years now, and often wondered what to do with them. Amongst these was the amplifier type 178, and in your January issue you gave some very explicit details for the conversion of this. Although by no means a radio "expert," I found the details easy to follow and, barring one or two snags, did not find it over-difficult to carry out the modification. I fitted the vision section to a home-made set which I have had in use for a long time (I did not make it) and get a very much better picture

than I have had before, and apart from the enjoyment of the programmes I found the work of conversion most interesting. Unlike the construction of a complete set, I think the converting of ex-Government apparatus has an interest far and away above anything else, as you start off with a piece of equipment designed for one purpose (and very well made at that) and proceed to turn it into something else. The final success of the effort I find most satisfying.—G. WATTS (N.W.9).

### THE SUPERVISOR

SIR,—I have had one of these receivers in use now for a long time, with not a very satisfactory frame hold. It would appear to jump at the least provocation, and I have tried various suggestions to improve this. In your recent issue you gave some details concerning this fault, if I may call it so, and although I carried out these ideas it did not really effect an improvement. I then suddenly thought of changing over V15 and V20—I don't know why I had not thought of this before. The frame then locked perfectly, but the line was slightly erratic. I took the valve now in V20 to the shop for test, and it was below standard—not actually faulty, the dealer told me, but in such a condition that it was less use in the frame circuit than the line. It is still working in V20 socket and gives less trouble there. This only goes to show that one cannot be too careful in having parts tested—when a circuit fails to function as described—before blaming the design.—B. E. BETTERTON (Kingsbury).

### BAND III SNAGS

SIR,—I have recently had the opportunity of picking up the experimental trade Band III transmissions, and have been most unlucky—or viewers are in for a bad time. First, I used a commercially made unit, and easily picked up the transmission. But it was in a terrible state, and with the converter connected, and the set switched to Band I, this also was in a sorry state. I had made a Band III aerial, but decided to buy a ready-made item. This I fitted to the chimney stack, in place of my home-made one, with no improvement. After a lot of experimental work I found the following troubles: reflections from one aerial on the other; interaction between down leads; direct pick-up on the wiring in the receiver from London when on Band III, and any amount of background noises on each of the signals. After much trouble, I lined the bottom of my cabinet with a sheet of very thin aluminium, and then on placing the set back (one which was home-made) the aluminium effectively closed in the bottom of the chassis and all the troubles ceased. I can now get a clean picture on either Band I or Band III, and although the latter is only a test card and on weak power it promises very well for the future. But in my case the closing in of the bottom of the chassis was a "must."—G. FRANCIES (N.W.5).

### THE BRITISH SERVICEMAN

SIR,—Whilst reading an old copy of a journal (not PRACTICAL WIRELESS) I came upon an article written by an American radio engineer. I wonder how many of our British radiomen have read it? To quote the writer, "The British Service engineer is a dignified individual who wears a white coat." As a

lone wolf enthusiast for twenty years, I think I would have said something stronger.

I have always been of the opinion that our service radio men and dealers are stuffed up, snooty individuals who have no time for a genuine enthusiast, nor can they tell the difference between a would-be "tuppenny-ha'penny" radio repairer and a genuine man.

Also, I find that dealers especially are determined year after year to keep prices (even of junk) sky high. They place a false value on everything connected with radio. They bought up all the ex-W.D. gear at ridiculous prices, but are charging fantastic prices from the public. The R1155's are a good example.

We all know that it cost a lot to build them, but that is no excuse for the dealer to charge high.

Lastly, I have had contacts with radio clubs, but as soon as I wanted help with some theoretical problems the clubmen were anything but helpful. I am still a keen enthusiast and I have not become a "tuppenny ha'penny" jobber, although I could be quite easily. Hoping to see a lot more American radio men come over here.—S. MALLOY (Dundee).

### BRITISH STANDARDS

SIR,—We are shortly to have a new set-up in this country under the I.T.A., and I should like to make a plea for the Authority to make, at the same time, a change of standards more in agreement with Continental or American systems. We are restricted to low-definition here, compared with the 625 lines or other systems, and service engineers who I know have seen the American pictures claim that they are better—although the studio technique etc., is not so good and, therefore, the final result does not come up to ours. Furthermore, why do we adhere to the vertically polarised transmission, which gives greater troubles from car interference than the radiation difficulties of a horizontal system. Could not the new transmitter make a change—I know many receivers would apparently be rendered obsolete, but again, our technical experts could no doubt introduce some form of timebase adapter to be connected in circuit with the tuning converter, and I am sure the result when switching over to an alternative programme with better definition would "sell" the new arrangement.—H. J. KELVIN (Brighton).

### BAD NEWS SERVICE

SIR,—The recent newspaper strike should have been the BBC's big chance to show the viewing public the true value and efficiency of "News and Newsreel." But they failed miserably.

Television means sound with pictures; we can get all the sound we want from radio but we look to TV to give us a pictorial record of topical events, instead of which most of the time in "News and Newsreel" is allotted to close-ups and stills of correspondents and scenes. The remainder of the time is filled in with very poor quality pictures and sound which have all the earmarks of having been hurriedly processed and scrambled together. Practically all the papers and magazines which I read have had letters from viewers complaining of the poor quality, and I would have thought, with the imminent competition of the commercial rivals, the BBC would have taken heed of the all-round dissatisfaction and reverted to the original type of "Newsreel."—J. BAKER (Beckenham).

**BRAND NEW R.F. Units, 26 or 27, 27/6, 24 12/-, 25 (used) 10/-; TUNER 161, 160/220 mcs. Valves: 1/CV66, 1/VR137, 2/VR136, 17/6; (postage 2/4 above), Transformers, input 230/250v, outputs 6v, 3a (twice) tapped at 4 and 5v, 9/6; 2,000v, 5ma and 2v, 2a, 17/6; 350-0-350v, 150ma and 5v, 3a, 25/-; 6.3v, 10a and 5a, 17/6; 250-0-250v, 6.3v, 3a and 5v, 2a, 16/6 (350v same price); (postage each 2/-).**

**STC Mc Recs.,** 600v, 300ma, 6/-; 450v, 80ma, 6/-; 300v, 300ma, 15/-; W/whose, 250v, 200ma, 10/-; all H.W. Bells, A.C., underdone, 5/-; hand generators for these, 5/-; Condensers, bakelite tub, 0.25 mfd, 1.5kVw, 1/6; 500pf or 001 4kVw, 1/3; .001, .01 and 1 mfd, 350/500v, rubber sleeved, 5/- doz; metal cased, .1 mfd, 500v or .01, 1kVw, 9d.; 4 met. recs., 15v, 8ma, with 2/500 ohm min. pots, w.w., 3/6; wire-wound pots, from 500 ohms to 100k, each 2/6. Lists and enquiries, 1 1/2; s.a.e.; cash with order; postage extra. **W. A. BENSON, 308, Rathbone Rd., Liverpool, 13.**

**JIM'S RADIO COMPONENTS, 23, Alexandra Rd., Sleaford, Lincs.** Send s.a.e. for free price lists and order forms.

**CONDENSERS, .1mf, 2,500v., d.c., wkg., 5/6; .1mf, 1,500v. d.c., wkg., 2/6; tubulars, 500v. d.c., wkg., .001, .002, .005, .01, .02, .05, .1mf, 5/- doz., can be mixed; .0005, .002, .003, .005, .01, .03mf, 4,000v. d.c., wkg., moulded tubulars, 1/6 each; .003mf, 5,000v. d.c., w., 2/-. Alum. alloy "H" Aerials, complete with chimney lashings and 5ft. pole, 45/-; money back guarantee. **GLADSTONE RADIO, Gladstone Place, Newton Abbot, Devon.****

**SERVICE SHEETS, T.V. and Radio,** over 2,000 models, sale or hire, Valves and Components, S.A.E. with enquiries. **W. J. GILBERT, 24, Frithville Gardens, London, W.12.**

**TV WITHOUT MAINS.**—Absolutely first-class picture, plus DC circuit for lighting, as supplied to the B.B.C. Special AC/DC "Chorehorse" Generators, self-starting, compact, and complete, AC 220/250 volts, 50/60 cycles, 250/350 watts AVC. Will run radios, vacuum cleaners, small tools, etc., £47/10/- plus 10/- delivery. Below:—

**STORAGE BATTERIES, 12v, 75AH** heavy duty, 19 plates, separate cells in hardwood cases; finest possible specification, £5/17/6, 9/6 delivery; 12v, 22AH almost similar specification, surprisingly powerful, £2/14/-, delivery 5/6. **TEDDINGTON ENGINEERING CO., LTD., Dept. "C," High St., Teddington, Middx. (Kingston 1193-4.)**

**BUILD YOUR OWN TV.** All Viewmaster specified components in stock. Stamp details. **FRANKLIN & HALL, 371, Havant Rd., Farington, Portsmouth.**

**R.F. UNITS, Types 26 at 27/6, 25 at 12/6, 24 at 11/-;** and brand new with valves; post 2/6. **E.W.S. CO., 69, Church Road, Moseley, Birmingham.**

**LOUDSPEAKERS** repaired promptly. **MODEL LOUDSPEAKER SERVICE, Bullington Rd., Oxford.**

**SERVICE SHEETS, T.V. and Radio,** S.A.E. with enquiries. **F.I.E.L.D., 30, Oldfield Road, London, N.16.**

**"VIEWMASTER" valves,** exact to specification, guaranteed new and boxed, set of 12 £5/15/-; "Tele-King," complete set of 17, £8/19/6; 14v miniatures: 1S5, DAF91, 1R5, DK91, 1T4, DF91, 3S4, DL92, DK92, any 4 for 27/6, post 1/-; all new and boxed. For individual prices and other types see displayed advertisement page 570. **READERS RADIO, 24, Colberg Place, Stamford Hill, London, N.16. (STA 4587.)**

**RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines, Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.**

**RADIO UNLIMITED** offer guaranteed new Valves: 1L4, 3A4, DF92, EB91, CV785, CV286, EF36, 6K7G, 1T4, 1S5, 6J5M, 6K7M, all at 5/- each, post free; U329, 6V6M, 6SL7, 6SN7, EB33, 5U4G, 6BE6, 7/- each; 1A7 and 807, 8/- each; 9D2, 8D2, 3/6 each; 17,000 Valves in stock. Lists free. Iso/trans., 1-to-1, 25% boost, 2v, 4v or 6v types, 6/3 each; door-rud Aerial, with co-ax lead, 17/6; Co-ax Cable, 70/80 ohms, 8/6 doz, yds.; 3-wave Coilpacks, 1 m. and s. 21/-; **RADIO UNLIMITED, Elm Road, London, E.17. (KEY 4813.)**

**SITUATIONS VACANT**

The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-64, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempt from the provisions of the Notification of Vacancies Order, 1952.

**TELEVISION TECHNICIANS**—all districts. Big money for you in your spare time. Opportunity to establish your own business. Write, giving fullest particulars of training, experience, whether owner of test equipment, age. All replies treated in strictest confidence. Apply to **TELE-PATROL LTD.,** Federation House, Epsom.

**PYE TELECOMMUNICATIONS LTD.,** Ditton Works, Cambridge, offer excellent opportunities for Junior and Senior Development Engineers in the electronics and communications field. Duties include development work on H.P., V.H.F., microwave and recording equipments. Applications from persons possessing B.Sc., Higher National or Ordinary National Certificates are especially welcomed. Good facilities are available, however, to keen young men wishing to train and study in these fields. Pleasant working conditions in modern factory. Single accommodation available. Write, giving fullest details, to Personnel Manager.

**TELEKIT SUPPLY**

Chantry Lane, Bromley, Kent.

Please mention P.T.V. and enclose 6d. postage

**VALVES GUARANTEED**

0Z4	4/-	6B8	6/-	9D2	5/-
1B24	35/-	6BA6	6/-	11D3	6/-
1L4	5/6	6BE6	6/-	12A5 12B9	6/-
1LN5 (soiled)		6BH7	8/6	(soiled) 5-	
		6BS7	7/-	12A16	7/6
1S5	6/-	6BW6	6/6	12BE6	6/6
1T4	6/6	6CH6	6/6	12BH7	7-8
1U5	6/-	6C5	5/-	13D1	7/-
3V4	6/6	6C5	6/6	15D2	4-
6A8	8/-	6V6	7/-	15D2	4-
6AK6	6/6	6X4	6/6	50C5	8-
6AL5	6/-	6X5	7/-	5763	8-
6AM6	6/-	7D5	6/-	EF50	5/-
6AQ5	8/-	7D8	6/-	TT11	6/-
6AT8	7/6	7HT	6/-	W77	5/-

**BECKENHAM, KENT**

**THE SHOP FOR THE CONSTRUCTOR NOW OPEN AT 104, HIGH STREET BECKENHAM 3720**

**R.F. OSC. E.H.T. COILS**

Type "D" 2-9 kV 25/-  
Type "F" 9-14 kV 30/-.

For use with valve or metal rectifier. Current available 1-2 mA. Ideal for oscilloscopes and television. Dimensions 3 1/2in. x 1 1/2in. dia. Wave wound winding. Complete with circuit. Terms: C.W.O. Post orders only.

**THE WATSON WATCH CO., 29, LEIGH ROAD, LONDON, N.5.**

**MAKING YOUR OWN? Telescopes, Enlargers, Binoculars, Microscopes, Projectors, or in fact anything that needs lenses.** Then get our booklets "How to Use Ex-Gov. Lenses & Prisms." Nos. 1 & 2, price 2/6 ea. Also our stereo book, "3-D Without Viewers," price 7/6. Comprehensive lists of lenses, optical, radio and scientific gear free for s.a.e. **H. W. ENGLISH, Rayleigh Road, Hutton, Brentwood, Essex.**

**TV SIMPLEX COILS, 21/-;** TV 3in. Canned Formers, 2/3 ea. **BEL, Marlborough Yard, Archway, N.19. (ARC 5078.)**

**FOR SALE, 10 Cossor Double Beam Oscilloscopes, Model 3339;** all in working order; £275, or £30 each, plus carriage and insurance. **COX RADIO, 39, West Street, Bognor Regis.**

**DIRECT T.V. REPLACEMENTS** offer the most complete Handbook of T/V Components and Rewinds, price 1/-; T/V Components for all kit sets in stock. "Nuray" heater booster isolator for 2-wolt C.R.T.s, just plugs in, 27/6, plus 2/- packing and postage. 134-136, Lewisham Way, S.E.14. (TIIDWAY 3696-2330.)

**T.V. (perfect working order.** All makes. Pye, 9in., £17; H.M.V., 10in., £15; Murphy, 9in., £15; Ultra, 12in., £25; Ekco, 12in., £27/10/-; many others. Lists sent on request. Service Manuals loaned against sets supplied. T/Vs needing attention from £7. S.A.E., please. **HIGH STREET RADIO, 284-6, High St., Croydon, Surrey. (CRO 8030.)**

**RATEL, 171, Norris St., Preston.** Radio and Television Service Sheets. Enquiries s.a.e. above address only.

**WINWOOD** for Value. New Valves: 6V6, 6K7, 6K8, 6Q7, 5Z4, 31/- set; 1T4, 1S5, 1R5, 3S4, 29/- set; ECL80, 8/6; EF39, EB33, 6SL7, 6SN7, 6V6M, 5U4, 1A7, 7/6 each. W.W. Cntrls., 5K, 3-watt, 3/9; Fresh stock 16 x 16mf-500v, 3/9; 32 x 32-450v, 4/6; 1-0-500v, 7/6 doz.; 0.05-500, 7/6 doz. Lists. **WINWOOD, 12, Carnarvon Road, Leyton, E.10. (Mail only.)**

**VALVES**

**WANTED, large or small quantities** of new Valves, Loudspeakers, Components, Receivers, etc.; prompt cash paid. **R.H.S. LTD., 155, Swan Arcade, Bradford, 1.**

**WANTED VALVES, 5Z4, ECL80, EY51, EP30, KT66, 6U4GT, KT61,** and all T.V. types, also P.M. Speaker Units, 3in., 5in., 6in., 8in., 10in., prompt cash. **WM. CARVIS LTD., 103, North Street, Leeds, 7.**

**ALL TYPES OF VALVES REQUIRED** for cash. State quantity and condition. **RADIO FACILITIES LTD., 38, Chalcot Road, N.W.1. (PRImrose 9090.)**

**EDUCATIONAL**

**FREE!** Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the college operated by Britain's largest electronic organization; moderate fees. Write to Dept. PT28, E.M.I. INSTITUTES, London, W.4.

**I.P.R.E.** Data for constructing TV Aerial-strength Meter, 7/6; 5,500 Alignment Peaks for superhets, 5/9; sample copy "Practical Radio Engineer," 2/-; Membership-examination particulars, 1/-; Syllabus of seven postal courses free and post free. **SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.**

**THE MODERN BOOK CO.**

BRITAIN'S LARGEST STOCKIST OF BRITISH & AMERICAN TECHNICAL BOOKS

- Television Principles & Practice, by F. J. Camm. 25s. 0d., postage 9d.
- Electronic Musical Instruments, by R. H. Dorf. 55s. 0d., postage 1s. 0d.
- Fundamentals of Transistors, by L. M. Krugman. 21s. 0d., postage 9d.
- Radio & TV Test Instruments. Gernsback Library. 12s. 0d., postage 6d.
- The Oscilloscope, by G. Zwick. 18s. 0d., postage 6d.
- TV Repair Techniques. Gernsback Library. 12s. 0d., postage 6d.
- Television for Radiomen, by E. M. Noll. 52s. 6d., postage 1s. 0d.
- The Oscilloscope at Work, by A. Haas and R. W. Hallows. 15s. 0d., postage 9d.
- Radio & Television Engineers' Reference Book, edited by E. Molloy. 70s. 0d., postage free.
- TV Fault Finding: Data Book No. 5. 5s. 0d., postage 3d.
- The (Radio Amateur's) Handbook, 1956, by "A.R.R.L.". 30s. 0d., postage 1s. 0d.
- Tape & Wire Recording: Data Book No. 8. 2s. 6d., postage 2d.

Please write or call for our catalogue.  
**19-23, PRÆD STREET (Dept. T.6) LONDON, W.2.**

Phone: PAddington 4185  
Open 6 days 9-6 p.m.

**THE VALVE SPECIALISTS**  
**Bentley Acoustic Corp. Ltd.**  
38, CHALCOT ROAD, N.W.1.  
PRImrose 9090

074	6/-	6S7J	8/-	956	3/6	KT44	7/-
1A5	6/-	6SK7	8/-	1203	7/6	KT74	12/-
1D6	8/6	6BL7	8/-	2051	10/6	KTW61	7/-
1E7	6/6	6BSN7	8/6	2524	8/6	KTW62	5/-
1G6	6/6	6BSR7	7/6	4032X	7/6	KTZ41	6/6
1LA	6/6	6U5(UX)	7/-	3783	9/-	LP2	4/6
1LA1	9/6	6U5(10)	7/8	1183	2/6	ML4	5/6
1LD5	7/6	6V6GG	7/-	9001	5/6	ML4	6/6
1LN5	6/-	6V6GGT	7/6	9002	5/6	ML6	6/6
1R5	7/-	6X4	7/6	9008	5/6	N77	7/6
1S3	7/-	6X5	6/6	9006	5/6	N142	10/6
1T4	7/-	6Y6	8/-	AC/HL	6/6	PO	20/6
2C26	4/-	6Y7	15/-	AC/P	6/6	OM5	7/6
2D13C	4/-	6Z484	8/6	ACP4	8/-	OM5A	10/8
2D21	8/6	7A7	8/6	AP4	7/6	OM5B	10/8
2X2	4/6	7AN7	11/-	ARP3(A)	5/-	OC3	9/-
3A4	7/6	7B7	7/6	ATP4	3/-	OD3	8/6
3C6	2/6	7C5	8/-	AC/P	6/6	PO	20/6
3C6	9/6	7C6	8/-	R309	9/-	PC84	11/-
384	7/-	7D5	8/-	B319	11/-	PCF80	11/-
3V4	7/-	7H7	7/6	BL63	7/6	PL83	12/8
4D1	3/-	7Q7	8/-	CK505	6/6	Pen 25	6/6
5U4	8/-	7R7	8/6	CK523	8/6	Pen 46	7/6
5V4	10/-	7Y7	8/6	CK525	6/6	Pen 34	6/6
6X3	8/6	8A8	11/-	D77	8/-	PL81	10/6
5Y3	7/6	8D2	2/6	DA90	8/6	PL82	9/6
5Z3	8/6	10D1	4/6	DAF91	7/-	PL83	11/8
5Z4	8/6	10LD11	10/-	DF91	7/-	PM12	4/-
6A3	10/6	12A6	6/6	DF92	6/-	PM13M	6/6
GA7	8/6	12AH7	12/6	DH30	15/6	PC86	9/6
GA7	8/-	12AW	10/6	DH77	8/-	PY80	9/6
6AB3	10/-	12A7	8/-	DH142	10/-	PY81	10/-
6AC7	6/6	12A7	9/-	DH150	10/-	PY82	7/6
6AG5	6/6	12BA6	9/6	DK92	7/-	QP21	7/6
GAG7	12/6	12BB6	8/6	DK96	8/6	Q905/10	10/6
6AK5	7/6	12BH7	12/6	DL72	7/-		
6AL2	8/-	12L2	30/6	DL98	8/-	Q575/20	10/8
6AM5	6/6	12H3	3/-	DL94	7/-	QS150/15	10/8
6AM6	6/6	12J5	6/-	DL810	10/6		
6AQ5	8/6	12K3	8/6	DL143	2/-	QV047	9/6
6AT6	8/-	12SC7	7/6	EA50	2/-	RK34	2/-
6B4	8/-	12SG7	5/6	EA76	9/6	RL37	2/-
6B7	7/6	12S7	8/-	EAC91	9/-	R37	12/-
6BA6	7/6	12SK7	6/-	EB24	2/-	S130	8/-
6BR6	4/-	12S97	8/6	EB41	11/-	SP4(7)	8/6
6BSM	4/6	12SR7	7/6	EB91	6/-	SP61	2/6
6BE6	6/6	12U5G	7/-	EB333	7/6	TP22	3/6
6BJ6	6/6	14H7	10/6	EBCA41	10/-	TP220	10/6
6D5	10/6	14R7	10/6	EB91	7/-	U16	12/-
6BR7	9/-	14A3	9/6	EC82	5/6	U25	12/-
6BW6	7/6	17Z3	10/-	EC32	10/6	U31	8/6
6BX6	10/6	19H1	10/-	EC35	9/-	U50	7/6
6C4	7/6	19Y7	8/6	EC81	9/-	U92	9/6
6C6	6/6	25A6	8/6	EC82	10/6	U142	9/6
6C8	8/-	25A6	8/6	EC83	10/6	U150	9/-
6C10	10/-	30	7/6	EC91	7/6	U153	10/-
6CH6	6/6	35L6	8/-	ECH42	10/-	U154	8/6
6D5	6/6	35W4	10/-	EC810	10/-	U319	8/6
6R6G	7/6	35Z4	8/6	EP22	9/-	U329	10/6
6R6M	8/-	35Z5	8/6	EP26	4/6	U404	9/-
6R8	7/-	42	8/-	EF37	10/6	UREC41	9/-
6P12	6/6	50C5	10/-	EF37A	10/6	UCH2	9/6
6P17	6/6	50L6	8/-	EF39	6/6	UCH81	12/8
6P32	6/-	50Y6	8/6	EP41	9/-	UP41	8/6
6P33	9/6	57	8/6	EP50(A)	8/-	UP85	12/6
6G6	6/6	59	8/6	EP50(B)	5/-	UL41	6/6
6H6G	2/6	62DDT	15/-	EP54	5/-	UL44	20/-
6J5G	5/-	62TH	10/-	EP55	12/-	UL46	10/-
6J5M	6/-	62VP	9/-	EP59	10/6	UY41	9/-
6J6	7/6	63ME	10/6	EP91	6/6	VLS42A	2/6
6G7E	5/6	63E2	9/-	EP92	7/6	VP47	8/6
6J7M	7/6	72	4/6	EL11	10/6	VP13K	7/6
6K6	7/-	75	8/6	EL84	11/-	VP23	6/6
6K7G	5/-	76	7/-	EL91	6/6	VR63	5/-
6K7M	6/-	78	8/6	EM34	10/-	VT601	6/6
6K9G	8/-	83	8/6	EY51	11/-	VU111	3/-
6K9GT	8/6	85A2	10/6	EY91	7/6	VU133	4/-
6K8M	9/-	121VP	9/-	EZ40	9/-	W150	9/6
6L6G	9/-	141TH	10/-	EZ41	9/-	X66	7/6
6L7	7/6	210LF	3/-	H30	5/-	X142	9/6
6LD3	10/6	2158G	4/-	H32	3/-	X150	10/-
6N7G	7/6	301	10/-	HL33	7/6	XPV10	6/6
6N7M	8/-	3118U	9/-	HL33D	6/6	XFY10	6/6
6Q7	8/6	451PT	10/-	HL41	7/6	XFY12	8/6
6R7	8/-	507	7/6	HL320	6/-	XH(1.5)	4/6
6R47	8/-	813	7/6	HVR2A	7/6	XSG15	6/6
6R67	10/-	832	25/-	KB32	8/6	Y63	7/6
6R67	6/6	866A	15/-	KL53	9/-	Z77	6/6
6R77	6/-	1385	7/6	KT2	5/-	Z719	10/6

All boxed and guaranteed. Post 6d. each. Same day service. Shop hours 8.30 to 5.30, Sats. 1 p.m. Why not phone or wire that urgent order for immediate despatch C.O.D.?

**OPPORTUNITIES IN TELEVISION**



144 pages

**Free!**

Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M.Brit.I.R.E., R.T.E.B. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 144-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointments Dept.

**We Guarantee "NO PASS—NO FEE"**

If you are earning less than £15 a week you must read this enlightening book.

Send for your copy NOW—FREE and without obligation.

**WRITE TODAY!**

British Institute of Engineering Technology  
237, College House,  
29-31, White's Lane, **BIET**  
Kensington, W.8.

**DISTRESS BAND RECEIVERS TRF.** 4 of Battery Valves Type APR12 (VP23). Coils could be added for Medium and Short Wave Bands. 27/6. Post 2/6.

**INDICATOR UNIT TYPE 233**, with VCR97 and 3 valves. Ideal for Simplex, etc. only 42/6.

**MICROAMPMETERS**—100 uA. 2 1/2 in. Proj. Min.-Max. scale but a standard 100 uA. movement. 27/6. 500 uA. 1 1/2 in. Rd. Fl. 0-10 scale, 8/6; 50 mA., Mc/s., 2in. sq. 6/-.

**MAINS TRANSFORMERS**—350-0-350 v. 80 mA., 6.3 v. 3.5 a. 5 v. 2 a. new, D.T. covered, 17/6. P.P. 1/-.

**NEONS**—Strike on 80 v. Supplied with series res. for mains, 1in. x 1in. dia. 2/-; Metal Recs. 300 v. 80 mA., 5/6. Pots. 100 K. 3 K. Sp. 1/- ea. 1 meg. 1/6. H/R Headsets, 3,000 ohm. 7/6. 100 pF. Mica, 500 pF. Mica, 2,600 pF. and 5,600 pF. Silver Mica, 3 for 1/-.

**PILOTS HELMET MIKES**, 2/- each. Post extra. Ex. Equip. only if stated. S.A.E. for Lists.

**Bates Surplus Store**

49, IVY ST., BIRKENHEAD, CHESHIRE

**RADIO AND TELEVISION COMPONENTS**

All parts in stock for: VIEWMASTER, SOUNDMASTER, TELEKING, ETC. Easy Terms Available. Stamp for list, NOT S.A.E. **JAMES H. MARTIN & CO.** Finsthwaite, Newby Bridge, Ulverston, Lancs.

**LYONS RADIO Ltd.**

3, GOLDHAWK ROAD, Dept. M.T., SHEPHERDS BUSH, LONDON, W.12.  
Telephone: SHEpherds Bush 1729

**AMPLIFIER UNITS TYPE 178**.—These units for TV conversion as described in the January issue of Practical Television. PRICE with valves as specified, i.e., 2-6ACT's, 2-BA50's, 5-VR65's, 35/-, or less valves, 15/- Postage 2/-.

**VALVE BARGAINS**.—VR65A (SP41), 2/6 each, post 6d.; 3 for 6/-; 6 for 10/-; VR91 (EP50), 5/6 each, post 6d.; 3 for 14/6; 6 for 25/6; VR136 (EP54), 5/- each, post 6d.; 3 for 12/9; 6 for 22/6. All tested and guaranteed.

**CATHODE-RAY TUBES**  
**VCR97**.—Brand new and unused in maker's special transit cases. Unvision picture tested to ensure freedom from cut-off. PRICE 39/6, carriage 3/6.

**VCR517**.—Ex. new equipment and TV picture tested to ensure freedom from cut-off. PRICE 35/-, carriage 3/6.

**SPEAKER GRILLE**.—Woven metal, 3 sizes available. "A"—14 1/2 x 13 1/2 ins.; "B"—13 x 12 ins.; "C"—16 1/2 x 11 1/2 ins. With smart gold-sprayed finish. Please state clearly size required. PRICE all sizes, 3/6 each, post paid.

**5-WAY CABLE**.—Outside dia. 5/16in., each conductor 9/012 tinned copper, rubber insulated and colour coded. PRICE 1/- per yard, post any qty., 1/6. Substantial reduction for 100 yd. coils. Trade enquiries invited.

**BARGAINS FOR CALLERS**.—Resulting on tidying up one of our Warehouses we are finding many useful chassis, meters, transmitter and radio units, etc. Quantities are too small to advertise, but callers can inspect these items which will all be available at CLEARANCE PRICES.

# Your problems solved



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** The coupon from p. 43 must be attached to all queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

## K.B. EV305

When the picture started to fade I sent it for repair. An RM4 rectifier was fitted. The picture is quite good, but after operating the set for about an hour I get what you describe recently as corona discharge, and quite a pronounced sparking on the neck of the tube. I returned the set for repair, and since having it back the trouble persisted until the sound and picture failed, and the 15-ohm 5-watt resistor and a .1  $\mu$ F condenser were found to be burnt out. These have been replaced, but the noise, such as one gets from a sparking plug, persists together with the spark of light. I have inspected the base of the receiver after an hour or so of operating, and I find that the resistor mentioned runs very hot indeed, almost hot enough to melt the solder. There is much evidence of melting wax on surrounding condensers. Can you kindly advise which may be the offending component? The set is about three years old and has given good service so far; the tube is quite clean.—H. Moore (Bristol).

It is quite normal for the resistor mentioned to work very hot, and it is also quite normal for soft wax to be in evidence on various components, particularly small capacitors, after the receiver has been operational for three years.

We are not clear as to the actual point where the flashover is occurring; if it is taking place inside the tube, we fear that the tube itself may be responsible. If, however, it is occurring in the vicinity of the scanning coils or focus unit, it may mean that the insulation of one or other of the windings is defective.

## CATHOVISOR 9MW2 TUBE

I would be grateful if you could supply me with the following information on the above tube:

- Base connections.
- Anode voltage.
- Filament voltage and current.

—G. Smith (Thornton Heath, Surrey).

As the Cinema-Television C.R.T. type 9MW2 has been obsolete for quite a long period, we are having difficulty in tracing its details as requested; the tube is not listed in the current issue of the tube Encyclopaedia, and, furthermore, Cinema Television, Ltd., themselves are unable to assist. We would mention, however, that we have noted your name and address, and if any details come to light in the future we will advise you accordingly.

## EKCO TU142B

I cannot receive sufficient volume. I tune the volume in from under the chassis to the maximum, which is then just audible, then when I turn the volume-control it has no effect. I would be obliged for your advice.—H. Owen.

No one could possibly tell the cause of the trouble with your receiver from such limited detail. Is the vision affected? How did the symptom occur? Does the volume alter when the volume-control is adjusted? We shall need to know much more than just "insufficient volume" before we can possibly assist you.

## EKCO T.161

The picture has the appearance of being out of focus. After the set has been on for a time bands of the picture from  $\frac{1}{4}$  in. to 1 in. or more wide move a fraction of an inch to the right and are then in perfect focus, but only remaining there for less than a second. The picture is very light, but when these bands appear there is an excellent contrast.

I have tested all resistances and condensers, coils, etc., but can find nothing amiss.—R. B. Wadman (Wokingham).

This is one of the symptoms of an intermittent heater to cathode short in the picture-tube. A separate heater winding is used for the tube in your particular model, and a heater to cathode short causes excessive attenuation of the higher modulation frequencies as the result of losses in the transformer. You may be able to continue employing the tube by making use of a separate low-loss transformer for energising its heater.

## ULTRA VA722

It has been necessary to change a valve, and from a service chart which I was able to borrow, the valve is a UL46, but on examination of this new valve and the existing valve there seems to be some difference in its internal make-up. As this service chart is one taken from a trade journal, I feel that perhaps a mistake has been made in the identification of the valves.

I am sending you the old valve for your identification. Since replacing this valve with a UL46 the set has not worked as well as previously. It is very slow opening out to the full picture height, and the picture quality is not as good as before.

I hope you will be able to give me the necessary assistance, and should be glad if you could give me the full valve line-up for my set, with alternatives.—E. Walker (Walkden).

Two UL46 valves are used in your type receiver; one functions as the frame amplifier and the other

as sound output. We would point out that there is a slight physical difference between the old style UL46 and the current issue.

Your model uses four 6F1's, a 6L1, a 6LD20, a D1, a 6F14, a 6F15, a 6D2, a 6P28, a 6K25, two UL46's, two PZ30's, and a U25.

It is recommended that only the above valve types be used as replacements.

#### "SIMPLEX"—FRAME FAULTS

When I advance the brilliance control the picture blurs and flies off at the bottom of the tube, leaving it blank. The next fault a folded raster. The top is rolled back and the bottom is rolled up until they meet.

Now I can get a picture on the centre part of the tube, showing head and shoulders of a person, but if I release the mains plug I get waist downward.

If I operate the height control the picture opens up but breaks up into five or six bands with widely spaced lines between each band.—C. Lethbridge (Bamber Bridge).

A leaky C29, 30 or 31 would cause raster to fly off tube with operation of brilliance.

The double appearance of the raster is due to too fast a frame speed. Double the value of C24.

Check the whole of the frame circuit if the above modification does not clear the trouble.

#### PYE B.18.T

I notice this set has a tube type Mullard MW22/14. I would like to know if I could use any other tube in place of this one. Also could I put a 12in. tube on this set?

As I have no circuit for this set I wondered if you could tell me if this is fitted with a pre-amplifier; if not, would my reception be improved with one fitted?—R. P. Byhan (Sudbury).

The current substitute for your tube is the Mullard MW22/18, but this necessitates a base change. From the electrical aspect, you should be able to use the 12in. type MW31/18 with slightly less brightness, but we have no data concerning any possible mechanical alterations.

A separate pre-amplifier is not incorporated in your set, though it should be sensitive enough to operate successfully in your district without one. If it does not, then we would advise you to ensure that your aerial is up to standard.

#### "SIMPLEX"—NO SOUND

I have recently built the "Simplex," complete with sound output stage, and have had considerable difficulty with it. At the present moment I have a picture (of sorts) but no sound is available.

The picture fault is a non-linear frame timebase, the lines on the top half of the picture being too well defined, then there appears to be a bend and on the lower part of the picture the frame timebase is cramped. This results in the artistes having large heads, very short bodies and no legs. As a matter of interest, when the timebase valves are taken out of their sockets there is no spot on the screen, but a long trace. This, I presume should not have any effect on the frame timebase.

The contrast control appears to make the line timebase to come off lock when retarded from the maximum gain position.—A. E. Harrison (Liverpool, 20).

It would appear that the frame is not operating at the correct speed. This is possibly due to tolerance values in the scan circuit and we suggest you try doubling the value of C24.

#### MURPHY V200A

I shall be glad if you can help me with my Murphy V200A.

The fault is cramping on the bottom half of the picture—I can't "pull it down."

I have the service sheet. V15 has been replaced with a big improvement, but the cramp is still there. I have thought of removing R37 but don't know whether this would be detrimental. Height control is all out and the linearity control nearly so. The latter only affects the top half of the picture.

Further, the left-hand bands on Test Card C are longer than those on the right hand and they get progressively wider as they go up from black, i.e., the white is the widest.

Both frame and line seem, therefore, to be at fault and I shall be glad of your suggestions.—E. W. Warren (Bristol, 6).

Since both scans are affected, we feel that the trouble may be caused, or at least aggravated, by low H.T. voltage. This often happens if the RM4 metal H.T. rectifier reduces in efficiency. You should suspect this trouble, and replace the rectifier, if the H.T. voltage, relative to chassis, is less than 205—that is measured from the output of the smoothing choke, i.e., measured across C65.

#### ULTRA V470

On switching on a good picture is obtained. After a quarter of an hour a continuous hum on sound commences which drowns speech and music. This hum on sound varies in pitch as cameras switch from one scene to another. Then thin black and white curved vertical lines appear on the screen, generally moving downwards, but occasionally upwards. Also, the brilliance fluctuates and for a time one has to keep getting up to adjust the brilliance control. After a time the hum on sound ceases and speech and music come back. Also the curved lines disappear. The set will then be O.K. for some time. Suddenly a loud ripping sound is heard on sound with dark and light bars moving up and down on the screen. The noise is so bad that sound has to be turned right off. After a time this rights itself and sound can then be turned up again.—Reginald W. Plimsaul (Welling).

Your remarks indicate that the frequency of the local oscillator drifts as the inside of the receiver increases in temperature. Sometimes this trouble is caused by a defective oscillator valve, but if you are sure that the valves are up to standard, an alteration in the value of a capacitor associated with the oscillator circuit should be suspected.

#### QUERIES COUPON

This coupon is available until JUNE, 21st, 1955, and must accompany all Queries.

PRACTICAL TELEVISION, JUNE, 1955.

# Finest Soldering? Always specify ERSIN MULTICORE to be precise

Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

**SIZE 1 CARTON**  
4 specifications for radio enthusiasts.

5/-



**HANDYMAN'S CARTON**  
Sufficient for 200 average joints. **6d.**

**TAPE SOLDER**  
MELTS WITH A MATCH!  
Real thin/lead solder containing cores of Ersin Flux. Needs no soldering iron or extra flux.

1/-

PER CARD



**BIB WIRE STRIPPER AND CUTTER**

The 3 in 1 tool. For stripping insulation without nicking wire, cutting without leaving rough edges and splitting extruded flex. **3/6 EACH**




MANUFACTURERS ARE INVITED TO WRITE FOR DETAILS OF BULK PACKS AT BULK PRICES

## MULTICORE SOLDERS LTD.

MULTICORE WORKS, REMEL HEMPSTEAD, HERTS. (BOXMOOR 3636)

# BUILD THIS RADIO FOR 49/6

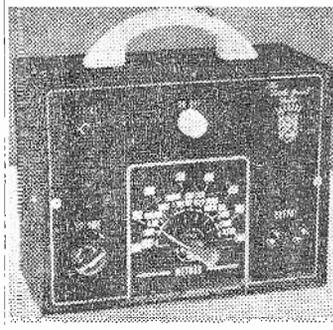

Build this exceptionally sensitive twin-triode radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6in. x 5in. x 3in. Covers all Medium and Long Waves—uses one only all-dry battery which lasts many months, as H.T. consumption is only 1 to 1 1/2 mA. Ideal for Bedroom, Garden, Holidays, etc. Read a few of our many unsolicited testimonials: Mr. Robinson of Harrogate, writes: "The set is working very well. It gets all the stations I need. It is also very loud. I am greatly pleased with it. Will you please send me details of anything else you have?" Mr. Norton of Oxford, writes: "Yesterday evening on the medium waveband, I counted 32 separate stations—I am very pleased with the set, which is well worth the money." Mr. Beckwith, of London, W.3, writes: "I must say that I was rather surprised and very pleased indeed with the performance for such a small set. I do not think there is anything on the market to beat it! The tone is perfect, reception very clear, and the stations just roll in. Up to now I have received about 20 stations and all very clear. I may add I am more than satisfied."

Build this powerful, long-range set. Total cost of parts, 49/6 post free (for headphone reception). Parts for adding further valve and speaker—which fits inside case, 34/6. All parts sold separately. (Parts lists, and full set of easy-to-follow, crystal-clear plans, 2/-). Note—We stock full range of components and valves. **ORDERS DESPATCHED BY RETURN.** Overseas orders welcomed—but regret no C.O.D. abroad. **SEND TO-DAY!**

**BRIGHTON RADIO & TELEVISION CO.**  
(DEPT. E.) 69, PRESTON ST., BRIGHTON, 1.

**WE SPECIALISE ONLY IN RADIO COMPONENTS—**

LET US QUOTE YOU BY RETURN FOR ANY RADIO VALVES OR PARTS YOU REQUIRE

HIRE PURCHASE TERMS ON KITS, INSTRUMENTS, ETC.

Osram "912" and Mullard "510" Amplifier Parts in Stock.

NEW CATALOGUE WITH H.P. TERMS 6d. QUOTES S.A.E.

**RADIO SERVICING COMPANY**  
82 SOUTH EALING ROAD  
LONDON W.5 EAL. 5737  
NEXT DOOR SOUTH EALING TUBE STATION (TURN LEFT)

**SIMPLEX**

**MAGNETIC 12" MODEL**

STAGE I, £3 STAGE II, £3 STAGE III, £4/18/-  
STAGE IV, £2/7/- STAGE V, £6/19/- STAGE VI, £3/10/-

**6" MODEL**

COMPLETE **£16** WITH TUBE (LESS SPEAKER)

**VALVES**

EF50	4/-	VU508	10/-	FW4/500	9/-	EA50	2/-
EF59 (Syl.)	6/3	SP61	2/6	SP41	2/6	6V6	8/6
6J5	5/-	D1	2/-	EB34	2/-	6SN7	9/-
BF34	5/-	6K7	6/-	6K7(m)	7/6	ECC81	7/-
1T4	7/-	1S5	7/6	EC54	4/6	3S4	8/6
EF39	7/6	3A4	6/-	1R5	7/6	VT501	6/-
HL2	4/-	EBC33	7/6	EL32	7/-	BF37A	11/-
VU111	3/6	VU133	3/6	EP36	4/6	VU194	8/-
VU123	3/6	2X2	3/-	955	5/-	5U4G	8/6
6X5	7/6	6K8	11/-	5Z4	8/6	Pen36	4/6
6SK7	4/6	6SH7	4/6	6SL7	7/6	9BW7	9/-
6SA7	7/6	6SJ7	4/6	EL50	9/-	RK34	2/6
R19	13/-	Pen220	3/-	KT66	11/-	35T	17/6
ARP12	5/9	AR8	6/6	V570	5/-	12SJ7	4/6

**CONDENSERS.**—Elect. 450 volt wkg., 8 mfd., 2/-; 8+8 mfd., 3/9; 8+16 mfd., 4/-; 16+16 mfd., 4/6; 32+32 mfd., 6/-; Dabliiter 500 volt wkg., 20 mfd., 3/-; 32 mfd., 5/-; Bias. 25/25 or 50/50, 2/-.

**RESISTORS.**—Our Selection, all different values, 1, 1, 1, 2 watt, 12/6 per 100.

**CONDENSERS.**—5 pF to 1 mfd., £1 per 100.

**METERS.**—M.C. T.C., etc., £1. Sample 6 Meters, £2 per dozen, all different.

**CONDENSERS.**—E.H.T. 1 mfd. 2.5 kv. 5/6 each (limited). 45 M/C STRIPS.—Less valves, post paid, 17/6.

**VINER'S (Middlesbrough)**  
Radio Government Surplus Electrical  
26, EAST STREET, MIDDLESBROUGH  
Telephone: MID 3418.

