

# Practical Television '61

MAY  
1961

AND TELEVISION TIMES

*How to use  
oscilloscopes*



**HARVERSON SURPLUS CO. LTD.**  
83 HIGH ST., MERTON, S.W.19. Cherrywood 3985/6/7

Introducing . . . **39'6**  
**HARVERSON'S**

**Monaural Amplifier Kit**

In response to numerous requests from delighted purchasers of our "SUPER STEREO KIT", we have produced a "MONAURAL AMPLIFIER" on similar lines.

★ A UCL 82 valve provides a triode amplifying stage, and a pentode output stage (3 watts), enabling good amplification and sparkling reproduction to be combined with physical compactness (amplifier size, 7 x 3 1/2 x 6 1/2 in. high).

★ Modern circuitry design and good quality O.P. transformer (to match 3Ω) keep hum and distortion to a low level.

★ The controls, volume on/off, and tone, are complete with attractive cream and gold knobs.

★ The amplifier has a built-in fully smoothed power supply, using a good quality mains transformer (A.C. mains only) and metal rectifier.

★ All you need is supplied including easy to follow instructions which guarantee good results for the beginner and expert. All components, leads, chassis, valve, knobs, etc., are first grade items by prominent manufacturers.

**OUR PRICE**, Plus 4/6 Post **39/6** and Packing.

**5" LOUDSPEAKER 14/6 EXTRA.**



**COSSOR C.R.T. SNIP**

108K 10-in. New and boxed, 15/-, plus 6 - P. & P.

75K 10-in. New and boxed, 15/-, plus 6 - P. & P.

**Ion trap magnets** to suit the above, 2/9, 3d. P. & P.

17 in. **MAZDA CRM 172**—

Not a Regun. Picture tested—12 months Guarantee.

**£3.17.6.** 12/6 P. & P.

**C.R.T. TESTER/REACTIVATOR**



- ★ **TESTS** any tube without removal from set or carton.
- ★ **REPAIRS** tubes discarded for low emission.
- ★ **MEASURES** A.C. Volts. ★D.C. Volts, E.H.T.

The Radar Model 202 Tester-Reactivator is the most comprehensive instrument of its type on the British Market.

(Complete with E.H.T. probe)

- Measures TRUE Beam Current ● Visual Indication when reactivating is complete (a Radar exclusive)
- Tests and Measures ALL tube Voltages including E.H.T. (another exclusive)
- Measures Resistance up to 100 Megohms ● Clears leaks by pressing a button ● Heater Current measurement 0-0.5A and 0-2.5A Linear Scale ● Adjusts heater current to ensure accurate Emission Test ● Portable for field or bench service.

**BRIEF SPECIFICATION**

Tests: Filament Continuity, Heater Current, Inter-Electrode Insulation, Final Anode Beam Current, Heater-Cathode Leakage, 4-stage Reactivation by New Pulsing Method. Universal socket fits all tubes. E.H.T. Probe. Measures: 0-25k Volts A.C., 0-500 Volts D.C., 0-25 kV., 0-100 MegΩ. 0-250 μA. 200-250 Volts A.C. Mains. Size 13in. by 10in. by 6in. Weight 14lb

List Price **£39** OUR PRICE **17 GNS.**  
Plus 9/- P. & P.

**AERIALS**

BAND I BAND II BAND III

**Combined Arrays I and II**

- 1-3 Element Loft Mounting . . . 38/3
- 1-5 Element Loft Mounting . . . 48/9
- 1-3 Element Wall Mounting . . . 45/3
- 1-5 Element Wall Mounting . . . 61/-
- 1-3 Element Chimney M'ting. . . 57/10
- 1-5 Element Chimney M'ting. . . 66/9

**Band I**

- Single Dipole Wall Mounting . . . 24/7
- Single Dipole Chimney M'ting. . . 40/2
- X Aerial Chimney Mounting . . . 62/3
- H Aerial Chimney Mounting . . . 67/7

**Band III**

- 3 Element Yagi Wall Mounting . . . 33/-
- 6 Element Yagi Wall Mounting . . . 43/-
- 9 Element Yagi Wall Mounting . . . 56/-
- Chimney Lashing Mounting add 10/-
- Double 6 Array only with clamp 83/-

**Band II**

- Single Dipole Wall Mounting . . . 20/5
- Single Dipole Chimney M'ting. . . 28/9
- H Array Chimney Mounting . . . 52/4



**REPAIR KITS**

- Band III Folded Dipole With Insulator. Complete . . . 9/3
- Band I Insulator With Two 1 inch Dipoles For 1 or 1 inch Booms. Complete . . . 19/5
- 6 inch Lashing Kit. 12/11. 7 inch Lashing Kit . . . 14/8
- 6 inch Wall Bracket With U Bolts . . . 7/10
- 1-1: 1-1 inch Clamps. 3/10. 1-2 inch Clamps Universal . . . 5/4
- Bracket Repair Kit. J Bolts: U Bolts: 20ft. Lashing Wire, Thimbles, Corner Plates . . . 6/-
- Insulators, All Types . . . (Enquire)
- Co-Ax. Semi Air Spaced. 7d. vd. . . . . Plugs. 1/2
- Send 6d. for Lists. Please state Channel when ordering. Cash with Order. Post and Packing 3/- extra.

**SATISFACTION OR MONEY BACK GUARANTEE**  
**WALKER & SQUIRES**

PINNOX STREET, TUNSTALL, STOKE-ON-TRENT

Phone: Stoke-on-Trent 88767

**1000's & 1000's**

OF SATISFIED PEOPLE

VIEW ON

**E.M.S.**

**REBUILT TELEVISION TUBES**

- ★ A NEW GUN IN EVERY TUBE
- ★ BUY DIRECT FROM THE FACTORY
- ★ 18 MONTHS' GUARANTEE

12 inch **£5.00** 14 inch **£5.10.0**  
17 inch **£6.10.0**

Immediate dispatch on receipt of Remittance

Carriage and insurance 12/6 extra

**£1 Refunded on receipt of your old Tube**


**SPECIAL TERMS TO THE TRADE**

**MARSHALL'S for TELEVISION LTD.**

131 St. Ann's Road, Tottenham, London, N.15

STAMFORD HILL 3267 & 5555

# DOUBLE BEAM "SCOPE"

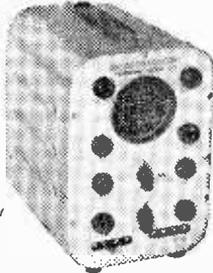

for D.C. & A.C. APPLICATIONS

Engineered to precision standards, this high-grade instrument is made available at the lowest possible price, incorporating the essential features usually associated with luxury instruments.

This "SCOPE" will appeal particularly to Service engineers and Amateurs. A high gain, extremely stable differential provides ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurements of transistor operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking TV Line O/P Transformers, etc.; Provision for external -1/P and CRT Brightness Modulation. A.C. mains 200/250 v. £19.19.0, plus P. & P. 7/6, or 50/- deposit, plus P. & P. 7/6 and 12 monthly payments of 33/4.

**Y-amplifier (30 mV/C.M.).** Provides ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurements of transistor operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking TV Line O/P Transformers, etc.; Provision for external -1/P and CRT Brightness Modulation. A.C. mains 200/250 v. £19.19.0, plus P. & P. 7/6, or 50/- deposit, plus P. & P. 7/6 and 12 monthly payments of 33/4.

**FULL 12 MONTHS' GUARANTEE INCLUDING VALVES AND TUBE**

## ALIGNMENT ANALYSER TYPE MCT2

A.C. mains 200/250 v. Provides: "Wobblinator" (Sweep Frequency) operation, for FM/TV alignment linear frequency sweep up to 12 Mc/s. From 400 kc/s-80 Mc/s. Capacitance Measurement. Two ranges provided 0-80pF and 0-120pF. Special Facility enables true resonant frequency of any tuned cct. I.F. transformer, etc., to be rapidly determined. Cash price £8.19.6, plus 5/- P. & P. H.P. terms 25/- deposit plus 5/- P. & P. and six monthly payments of 21/6.




## LINE E.H.T. TRANSFORMER

With built-in line and width control, 14 KV. Scan coil, 90in. deflection, on ferrite yokes. Frame O.P. transformer pf. 18 KV. smoothing condenser. Can be used for 14in., 17in. or 21in. tubes. Complete with circuit diagram.

29/6 Plus 4/- P. & P.

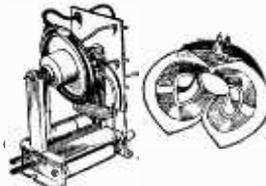As above, but for 625 lines, £2.10.0, plus 4/- P. & P.



Focus Magnet suitable for the above (state tube). 10/-, plus 2/6 P. & P.

## CYLDON TURRET TELETUNER

I.F. 24/38Mc/s. Brand new, complete with biscuits for channels 2, 4, 8, and 13, less valves. Valves required P.C.C. 84, P.C.F. 80. 10/- plus 2/6 P. & P.

## MAINS TRANSFORMERS

All with tapped primaries, 200-250 volts. 0-160, 180, 200 v., 60 mA. 6.3 v. 2 amp., 10/6. 280-0-280 80 mA. 6.3 v. 2 amp., 6.3 v. 1 amp., 10/6. 350-0-350 v., 70 mA. 6.3 v. 1 amp., 10/6. 250-250 v., 70 mA. 6.3 v. 2 amp., 10/6. Postage and packing on the above. 3/- each.

## SURFACE BARRIER TRANSISTORS

Type SB305, 15 Mc/s, 7/6 each. 100% AUDIO TRANSISTORS, 5/- each.


## TRANSISTOR TESTER

For both P.N.P. and N.P.N. transistors incorporating moving coil meter. In metal case, size 4 1/2 x 3 1/2 in. Scale marked in gain and leakage. Complete and ready for use. 19/6 Plus 2/6 P. & P.

## A.C./D.C. POCKET MULTIMETER KIT

2in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamps. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500, Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wired-out pot (for ohms zero setting), toggle switch, resistor and rectifier, 19/6, P. & P. 1/6. Wiring diagram 1/- free with kit.


## SIGNAL GENERATOR

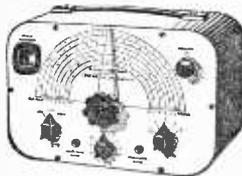


£8.19.6 or 25/- deposit and 6 monthly payments of 21/6. P. & P. 5/- extra. Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10in. x 6in. x 5in., grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250. Internal modulation of 400 c.p.s. to a depth of 30%, modulated or unmodulated R.F. output continuously variable, 100 milli-volts. A.F. output, incorporating magi-eye as output indicator. Accuracy plus or minus 2%.

C.W. and mod. switch, variable A.F. output, incorporating magi-eye as output indicator. Accuracy plus or minus 2%.

Cash £4.19.6 or 25/- deposit and 4 monthly payments of 21/6. Plus Postage and Packing 5/-. Coverage 120 Kc/s-84 Mc/s. Metal case 10in. x 6in. x 4in. Size of scale 9in. x 3in. 2 valves and rectifier. A.C. mains 200-250 v. Internal modulation of 400 c.p.s. to a depth of 30% modulated or unmodulated R.F. output continuously variable, 100 milli-volts. C.W. and mod. switch variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%

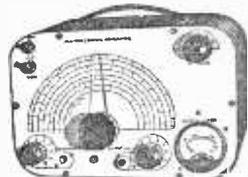

## SIGNAL & PATTERN GENERATOR

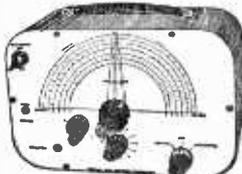


£6.19.6 P. & P. 5/-  
Or 25/- deposit, P. & P. 5/- and 6 monthly payments of 21/6. Coverage 7.6 Mc/s-210 Mc/s. In five bands, all on fundamental, slow motion tuning and audio output, 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy ± 1% A.C. mains 200/250 v.

## CHANNEL TUNER

Will tune to all Band I and Band III stations. BRAND NEW by famous manufacturer. Complete with P.C.C. 84 and P.C.F. 80 valves (in series), I.F. 16-19 or 33-38. Also can be modified as an aerial converter (instructions supplied). Complete with knobs.

32/6 Plus 3/6 P. & P.

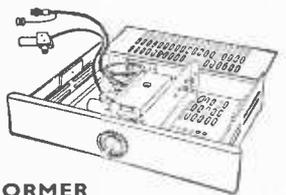

## HEATER TRANSFORMER

To suit the above, 200-250 v., 6/-, Plus 1/6 P. & P.



## 8-WATT PUSH-PULL AMPLIFIER

COMPLETE WITH CRYSTAL M.I.E. AND 8in. LOUDSPEAKER  
A.C. mains 200-250 v. Size 10 1/2 in. x 6 in. x 2 in. Incorporating 6 valves, H.F. pen., 2 triodes, 2 output pens and rectifier. For use with all makes and type of pick-up and mike. Negative feedback. Two inputs, mike and gram., and controls for same. Separate controls for Bass and Treble lift. Response at from 40 cycles to 15 Kc/s., ± 2 db; 4 db down to 20 Kc/s. Output 8 watts at 5% total distortion. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohm speech coils. For use with Std. or L.P. records, musical instruments such as Guitars, etc. £4.19.6 Plus P. & P. 7/6.

## RADIO & T.V. COMPONENTS (Acton) LTD.

23c HIGH STREET, ACTON, LONDON, W.3

All enquiries S.A.E. GOODS NOT DESPATCHED OUTSIDE U.K.

# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1.

Telephone: PRIMROSE 9090

**EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. TELEPHONE AND TELEGRAM ORDERS FOR CASH ON DELIVERY SERVICE ACCEPTED UP TO 3.30 P.M.**

OA2 17/6 6F11 17/3	10F1 26/6 35Z3 10/6	DK91 6/6 EF54 5/-	KLL32 24/7	PM24M 21/3	U4020 16/7	XYF12 9/6
OB2 17/6 6F12 4/6	10F9 11/6 35Z4GT 6/-	DK92 9/6 EF73 10/6	KT2 5/-	PM84 17/3	U4ABC80 9/-	XYF3 17/6
OZ4 5/- 6F13 11/6	10LD3 8/6 35Z5GT 6/-	DK96 8/6 EF80 6/-	KT33C 10/-	PK4 10/6	U4AF42 9/6	XY(1.5) 6/6
IA5 6/- 6F15 15/6	10LD11 4/3	DL33 9/6 EF85 6/-	KT36 29/10	PK31 16/7	UB41 12/-	XSG(1.5) 6/6
IA7GT 12/- 6F23 10/3	15/11 50C5 10/-	DL66 17/6 EF86 10/6	KT41 23/3	PK32 17/11	UBC41 8/6	Y63 7/6
IC5 12/6 6F32 10/6	10P13 15/- 50C6DG 6/-	DL68 15/- EF89 9/-	KT44 12/6	PK80 7/6	UBC81 11/4	Z63 7/6
ID6 10/6 6F33 7/6	10P14 19/3 36/6	DL72 15/- EF91 4/6	KT61 12/6	PK81 8/6	UBF80 9/-	Z66 17/6
IG6 17/6 6G6 6/6	12A6 5/- 50L6KT 9/6	DL92 7/- EF92 4/6	KT63 7/1	PK82 7/1	UBF89 9/6	Z77 6/6
IH5GT 10/6 6H6 3/6	12AC6 15/3 53KU 19/11	DL94 7/6 EF97 13/3	KT66 15/-	PK83 8/6	UBL21 23/3	Z719 6/1
IL4 3/6 6I5 5/6	12AD6 17/3 77	DL96 8/6 EF98 13/3	KT88 24/-	PK88 13/3	UCC84 14/7	Transistors and diodes
ILD5 5/- 6I6 5/6	12AE6 13/11 78	DM70 7/6 EF183 18/7	KTW61 6/6	PY20 19/11	UCC85 9/-	
ILN5 5/- 6I7G 6/-	12AH7 8/- 80	EA50 20/- EF184 18/7	KTW62 7/6	QP21 7/-	UCF80 16/7	
IN5GT 10/6 6I7GT 10/6	12AH8 12/6 83	EA52 2/- EK32 8/6	KTW63 6/6	QP25 14/6	UCH21 23/3	
IS4 6/6 6K7G 5/-	12AT6 7/6 85A2 25/-	EA76 9/6 EL32 5/-	KTZ41 8/-	QS150/15	UCH42 9/6	
IR5 9/- 6K7GT 6/-	12AT7 6/- 150B2 15/-	EABC80 9/6 EL33 12/6	KTZ63 7/6	RL2 10/6	UCH81 9/6	
IS5 6/- 6K8GT 10/6	12AU6 23/3 161	EAC91 4/6 EL34 15/-	L63 6/-	R12 9/-	UCL82 11/6	
IT4 3/6 6K8G 6/6	12AU7 6/6 185BT 33/2	EAF42 9/6 EL38 26/6	LN152 9/6	R18 14/-	UCL83 19/3	
IU5 6/- 6K25 19/11	12AV6 12/8 304	EB34 2/6 EL41 9/-	MHL4 7/6	R19 19/11	UF41 9/-	
2P 26/6 6L1 23/3	12AX7 7/6 305	EB41 8/6 EL42 10/6	MHLD6 12/6	RG1/240A	UF42 12/6	
2X2 4/6 6L6G 8/6	12BA6 8/- 807	EB91 4/- EL81 16/7	ML4 8/6	45/-	UF80 10/6	6, 8 4/-
3A4 6/- 6L6M 9/6	12BE6 9/- 956	EC3 23/3 EB33 5/-	MF48 23/3	RK34 7/6	UF85 9/-	OA70 4/-
3A5 10/6 6L7GT 13/1	12BH7 21/3 1821	EC33 5/- EL84 7/6	MU12/14 8/-	S130 22/6	UF86 17/11	OA73 4/-
3B7 12/6 6L18 13/1	12E1 30/4 4033L 12/6	EC41 8/6 EL85 13/11	N37 23/3	SP47 14/6	UF89 9/-	OA79 4/-
3D6 5/- 6L19 23/3	12J5GT 4/6 5763	EC81 8/6 EL86 17/3	N78 19/11	SP41 3/6	UL41 9/-	OA81 4/-
3Q4 7/6 6LD3 8/6	12J7GT 6/6 7193	EF80 9/- EL91 5/-	N108 23/3	SP42 12/6	UL44 26/6	OA86 6/-
3Q5GT 9/6 6L02 15/11	12K5 17/11 7475	EF83 13/11 EL95 10/6	N308 20/7	SP61 3/6	UL46 14/6	OA91 5/-
3S4 7/1 6N7 8/-	12K7GT 5/6 9002	EF89 9/6 EL820 18/7	N339 15/-	SU25 26/6	UL84 8/6	OA95 5/-
3V4 7/6 6P25 12/6	12KBGT 14/- AC/PEN	EBL21 23/3 EL822 25/-	P61 3/6	SU61 9/6	UM4 17/3	OA210 25/-
5R4GY 17/6 6P26 19/11	12Q7GT 5/- 5-pin 23/3	EBL31 23/3 EM34 23/3	PAB80 9/6	T41 9/6	UM34 17/3	OA211 40/-
5U4G 6/6 6P28 26/6	12SA7 8/- 5-pin 15/-	EC52 5/6 EM71 9/6	23/3	TD4 12/6	UM80 15/3	OC16 54/-
5V4G 10/- 6Q7G 6/6	12SC7 8/- AC2/PEN	EC54 6/- EM80 9/-	PCC84 8/-	TH41 26/6	UR1C 18/7	OC19 54/-
5Y3 6/6 6Q7GT 11/6	12SG7 7/1 DD 12/6	EC70 12/6 EC81 8/6	PCC85 9/6	TH233 33/2	U06 19/11	OC23 87/-
5Z3 12/6 6R7G 10/6	12SH7 8/6 AC6/PEN 7/6	EC92 13/3 EM84 10/6	PCC88 18/-	TH2321 20/-	U07 16/7	OC26 44/-
5Z4G 9/- 6SA7GT 8/6	12SJT 8/6 AC/TP 33/2	EC32 5/6 EM85 17/3	PCC89 11/6	TP22 15/-	U08 26/6	OC28 25/-
6A7 10/6 6SCT 7/6	12SK7 8/- ATP4 5/-	EC33 8/6 EN1 37/-	PCF80 8/-	TP25 15/-	U09 7/6	OC35 48/-
6A8 9/- 6S7GT 8/6	12SQ7 11/6 AZ1 18/7	EC34 24/7 EY31 9/6	PCF82 10/6	TP2620 33/2	UY1N 18/7	OC44 26/-
6AC7 4/- 6SHT 8/6	12SR7 8/6 AZ31 10/6	EC35 8/6 EY83 16/7	PCF84 16/7	TY86F 13/3	UY21 13/11	OC45 23/-
6AG5 5/6 6SJTGT 8/6	12TY4 8/6 AZ41 13/11	ECC40 23/3 EY84 14/-	PCF86 15/-	UI2/14 8/6	UY41 7/6	OC65 22/6
6AK5 8/- 6SK7GT 6/-	14S7 27/10 B36 15/-	ECC81 6/- EY86 9/-	PCL82 10/-	U16 10/6	UY45 7/6	OC66 25/-
6AL5 4/- 6SL7GT 6/6	19AQ5 10/6 BL63 7/6	EC82 6/6 EZ35 6/-	PCL83 10/6	18/20 8/6	VMP48 15/-	OC70 14/-
6AM6 4/6 6SN7GT 5/6	19H1 10/- C1 12/6	EC83 7/6 EZ40 7/-	PCL84 12/6	U19 36/-	VMS4B 15/-	OC71 14/-
6AQ5 7/6 6S7GT 9/6	20D1 15/- C1C 12/6	EC84 9/- EZ41 7/-	PCL85 16/7	U22 8/-	VP2 12/6	OC72 17/-
6AT6 7/1 6S7GT 8/6	20F2 26/6 CBL1 26/6	EC88 8/6 EZ80 7/-	PCN4 23/3	U24 29/10	VP4 15/-	OC73 20/-
6AU6 10/- 6UAGT 12/6	20L1 26/6 CBL31 23/3	EC88 18/- EZ81 7/-	PEN84 26/6	U25 17/11	VP2B 14/6	OC75 15/-
6AV6 12/8 6USG 7/6	20P1 26/6 CCH35 23/3	EC99 19/11 FC4 15/-	PEN4DD	U26 10/6	VP4B 23/3	OC77 21/-
6B8 5/- 6U7G 8/6	20P3 23/3 CK506 6/6	EC99 5/6 FW4/500 8/6	26/6	U31 9/6	VP13C 7/1	OC78 17/-
6BA6 7/6 6V6G 7/6	20P4 26/6 CL33 19/3	ECF80 10/6 FW4/800 8/6	26/6	PEN25 4/6	VP23 6/6	OC81 18/-
6BE6 6/- 6V6GTG 8/-	20P5 23/3 CV63 10/6	ECF82 10/6 GU50 27/6	PEN40DD	U35 26/6	VP41 6/-	OC170 35/-
6BG6G 23/3 6X4 5/-	25A6G 10/6 CY1 18/7	ECF86 19/11 GZ30 9/6	25/-	U37 26/6	VR105 8/-	OC200 54/-
6BH6 8/- 6X5GT 6/-	25L6GT 10/- CY31 16/7	ECH3 26/6 GZ32 10/-	PEN44 26/6	U43 9/-	VR150 7/6	OC203 58/-
6B16 6/- 6/30L2 10/-	25Y5G 10/- D1 3/-	ECH21 23/3 GZ33 19/11	PEN45 19/6	U45 9/-	VT61A 5/-	T11 40/-
6BQ7A 15/- 7A7 12/6	25Z4G 9/6 D15 10/6	ECH35 6/6 GZ34 14/-	PEN45DD	U50 6/6	VT501 5/-	T12 45/-
6BR7 23/3 7B6 21/3	25Z5 9/6 D63 5/6	ECH42 9/6 GZ37 19/11	4/6	U52 6/6	W76 5/6	T13 50/-
6BS7 25/- 7B7 8/6	25Z6U 10/- D77 4/-	ECH81 9/- H63 12/6	PEN46 7/6	U54 19/11	W81M 6/-	TP1 40/-
6BW6 8/6 7C5 8/6	27S5 19/11 DAC32 10/6	ECH83 13/11 HABC80	PEN383 23/3	U76 6/-	W107 18/7	TP2 40/-
6BW7 6/- 7C6 8/-	28D7 7/- DAF91 6/-	ECL80 9/6	13/6	U078 5/-	W279 19/11	TS1 10/-
6BX6 6/- 7H7 8/-	30C1 8/- DAP96 8/6	ECL82 10/6	HL2 7/6	U167 16/7	X24M 24/7	TS2 12/6
6C4 5/- 7R7 12/6	30F5 6/- DD41 13/11	ECL83 19/3	HL23 15/3	PEN/DO	U191 16/7	X41 15/-
6C5 6/6 757 9/6	30FL1 10/- DET25 7/6	EP9 23/3	HL23DD 7/6	40/20 33/2	U201 16/7	X61(C) 12/6
6C6 6/6 77 8/6	30L1 8/- DF33 10/6	EP22 14/-	HL41DD	PL33 19/3	U251 14/-	X63 9/-
6C9 13/6 774 7/6	30L15 11/6 DF66 15/6	EP36 4/-	HL42DD 19/3	PL36 12/6	U281 19/11	X65 12/6
6C10 9/- 8D2 3/6	30P4 12/6 D591 3/6	EP37A 8/-	HL42DD 19/3	PL38 26/6	U282 22/7	X66 12/6
6CDH6 36/6 8D3 4/6	30P12 7/6 DF96 8/6	EP39 5/6	HN309 24/7	PL81 10/6	U301 23/3	X76M 14/-
6C6G 9/- 9BW6 15/3	30P11 10/6 DF97 9/6	EP40 15/-	HV2R 20/-	PL82 9/6	U329 14/7	X78 23/3
6D6 6/6 9D2 4/6	30PL13 12/6 DH63 6/6	EP41 9/-	HV2R2 6/-	PL84 12/8	U403 16/7	X79 23/3
6E5 12/6 10C1 13/-	35A5 21/3 DH76 5/6	EP42 10/6	KF35 8/6	PL820 18/7	U404 8/6	X810 10/6
6F1 26/6 10C2 26/6	35VL6T 9/6 DH77 7/-	EP50(A) 5/-	KL35 8/6	PM2B 12/6	U801 29/10	XDF(1.5) 6/6
6F6G 7/- 10D2 12/-	35W4 7/6 DH32 12/-	EP50(E) 5/-				XG1 18/-

**RADIO BOOKS. MULLARD AMPLIFIER MANUAL 9/6d. MULLARD TRANSISTOR MANUAL 13/6d. BRIMAR VALVE MANUAL 7/- ALL POST FREE.**

**VOLUME CONTROLS**

All with Long Spindle and Double-pole Switch, 4/6 each.	DRM1B 13/-	RM-1 5/3
10K 25K 50K 100K	DRM2B 15/6	RM-2 7/6
1/2 mg. 1/2 mg. 1 meg. 2 meg.	DRM3B 15/6	RM-3 7/9
	LW7 21/-	RM-4 14/-
	RM-0 7/11	RM-5 19/6

**METAL RECTIFIERS**

4A86 17/6	4A97 25/-	4A100 27/-	4A124 28/-	4A163 38/-
4A97 25/-	4A100 27/-	4A124 28/-	4A163 38/-	

Full List with ratings free for S.A.E.

4A130 35/-	4A142 11/6	4A142 11/6	4A142 11/6	4A142 11/6
4A142 11/6				

**JUST OUT. MIDGET SILICON RECTIFIERS. OUTPUT 120 VOLTS AT 1/2 AMP. TWO IN SERIES GIVE 240 VOLTS AT 1/4 AMP. NO LARGER THAN A RESISTOR. 10/6 EACH.**

**ELECTROLYTIC CONDENSERS**

Standard Can	60 x 250 mfd., 275 v. 9/6	200 mfd., 275 v. 4/-	Wire-ended tubular	8 x 8 mfd., 450 v. 3/-
16 x 8 x 8 mfd., 500 v. 4/-	100 x 400 mfd., 275 v. 12/6	100 x 200 mfd., 275 v. 9/6	8 mfd., 450 v. 1/9	16 x 16 mfd., 450 v. 4/-
32 x 32 mfd., 450 v. 5/9	100 mfd., 275 v. 3/-		16 mfd., 450 v. 2/9	32 x 32 mfd., 350 v. 4/-
64 x 120 mfd., 350 v. 8/3			32 mfd., 450 v. 3/9	8 x 16 mfd., 450 v. 3/9

Post/Packing Charge 6d. per item. Orders over £3 post free. C.O.D. 2/6 extra. Full List, with Terms of Business, 6d. Any parcel insured against damage in transit for only 6d. extra. Shop Hours 8.30-5.30. Early Closing Saturday.

# The A.T.R. Group

## Rebuilt and Rescreened

### Cathode Ray Tubes

**SUFFOLK TUBES LIMITED**  
1/3 UPPER RICHMOND ROAD  
PUTNEY, LONDON, S.W.15.  
Tel: Vandyke 4304/5267

**MIDLAND TUBES LIMITED**  
37 GEORGE STREET  
MANCHESTER, 1.  
Tel: Central 4568/4569

**VIDIÓ REPLACEMENTS LIMITED**  
HALES STREET  
DEPTFORD HIGH STREET  
DEPTFORD, S.E.8.  
Tel: 2177/4506

**Scotts Radio Ltd.**  
4 Church Street  
Brighton  
Tel: Brighton 26891

**Weston Hart Ltd.**  
236/8 Fratton Road  
Portsmouth  
Tel: Portsmouth 24125

**Lawsons Ltd.**  
36 Cornhill  
Bury St. Edmunds, Suffolk  
Tel: Bury St. Edmunds 3304

**Millward Ltd.**  
3 Dudley Road  
Wolverhampton  
Tel: Wolverhampton 21162

**Wizard Productions**  
16 Withy Grove  
Manchester  
Tel: Dea 2772

**J. Charlesworth & Son**  
14 Hightown  
Crewe, Cheshire  
Tel: Crewe 2535

**Taylor's**  
162 Eastney Road  
Milton, Portsmouth  
Tel: Portsmouth 35000

**Wanda Electrics**  
9 Manor Road  
Gravesend  
Tel: Gravesend 3766

**Stowmarket Co-operative**  
Bury Street  
Stowmarket, Suffolk  
Tel: Stowmarket 51/52

**Frank H. Hunt & Co.**  
Stepcote Hill  
Exeter, Devon  
Tel: Exeter 56687

**H. Knowles**  
54/56 Chester Road  
Manchester  
Tel: BLA 9031

**Radio Services Ltd.**  
30 Mona Street  
Amlwch, Anglesey  
Tel: Amlwch 594

**Hi-Lite Ltd.**  
89 Southbourne Grove  
Southbourne, Bournemouth  
Tel: Bournemouth 44344

**R. Watson**  
Leathern Bottel  
Wavenden, Woburn Sands, Bucks  
Tel: Woburn Sands 2027

**R.E.S. Ltd.**  
17/19 Paynes Lane  
Coventry  
Tel: Coventry 28781

**Gwalia Radio & T.V.**  
Llanstephan  
Carmarthen  
Tel: Llanstephan 284


**J. Wildbore Ltd.**  
6-12 Peter Street  
Oldham  
Tel: Mai 4475

**Tele-Care Ltd.**  
66 Osborne Street  
Glasgow, C.1  
Tel: Bell 1912/3

BEST VALUE

FINEST QUALITY

12 MONTHS' GUARANTEE

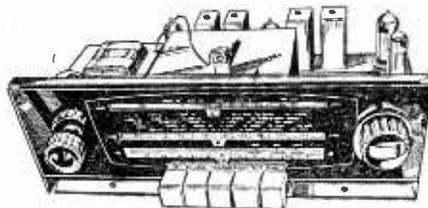


## BRAND NEW AM/FM (V.H.F.) CHASSIS AT £14 (carr. pd.)

Tapped input 200-225 v. and 228-250 v. A.C. ONLY. Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dial 1 1/4 x 4 in. In gold and black. Pick-up. Extension Speaker, A.E., E., and Dipole sockets. Five "piano" push buttons—O.F. L.W., M.W., F.M. and Gram. Aligned and tested. With all valves & O.P. Transformer. Tone-control fitted. Covers 1,000-1,900 M.; 200-500 M.: 88-98 Mc/s. Valves E730 rect. ECH81, EF89, EABC80, EL84, ECC85. Speaker & Cabinet to fit chassis. 47/6 (post 3/6), 10 x 6 in. ELLIPT. SPEAKER, 20/-.

TERMS:—(Chassis) £5.10.0 down—and 8 monthly pymts. of 30/-, or with Cabinet and Speaker £5.17.0 down and 7 monthly pymts. of 32/-.



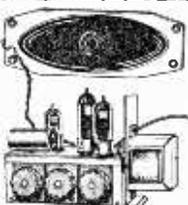**OFFER OF 12-CHANNEL 716** (2/6 P. & P.)  
**INCREMENTAL TUNER**  
LF 34-38 Mc/s without valves. Removed from chassis but in working order PCF80 and PCC84 required. Knobs 2/6 extra



**3-VALVE AMPLIFIER (INC. RECT.)**. Capable of giving 4 watts. Mains and output transformers. Valves ECC83, EL84, and EZZ0. 3 Controls, volume, bass and treble. On/Off switch. Fully guaranteed. Chassis size 6 1/2 x 3 x 2 1/2 in. 6 in. round or 7 x 4 elliptical speaker, state which. Not suitable for microphone input.

**75/- (3/- p. & p.)**


**NEW WAXED TUBULARS**, 350 v. or above, 0.001, 0.002, 0.005, 0.01, 0.02, 0.05, 0.1, 0.25, 0.5 mF. Total 2/ for 4/6, post 6d.

Delivery by return. C.O.D. 2/- extra. All new goods unless stated Send 6d. for NEW 20-page catalogue.



**GRAMOPHONE AMPLIFIER** with 5in. SPEAKER. On Fabric-covered Baffle 12 x 6 in. Mains and Output Transformers. Valves EZZ40 and EL41. Tone and Volume controls. On/Off switch. Plenty of Volume. Fully Guaranteed. Two Knobs supplied. Ready to play. Useful for Stereo.

**ONLY 63/-, post 3/-**

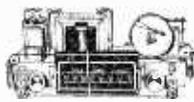

**SELF-POWERED VHF TUNER CHASSIS**

Covering 88-95 Mc/s Mullard permeability Tuner. Dims. 10 1/2 x 4 1/2 x 5 1/2 in. High. ECC85, EF89, EF91 and 2 diodes. Metal Rectifier. Mains Transformer. Fully wired and tested. Only £7.10.0 (4/- carr.). Room dipole 10/-, 300 ohm twin feeder 6d. vd. Tuner without power pack £8.10.0 (3/- carr.).

**£7.10.0 (4/- carr.)**

**PLESSEY FRAME OUTPUT TRANS (18 Mc) 5/- (2/- P. & P.)**,  
**PHILCO SCANNING COIL 90 DEG. 12/6 (P. & P. 2/6)**,  
**REGENTONE SCANNING COILS 70 DEG., 12/6 (P. & P. 2/6)**,  
**REGENTONE LINE OUTPUT TRANS, 20/- (P. & P. 2/6)**.

## GLADSTONE RADIO

(Camberley closed Sats., Bristol & Portsmouth closed Weds.)

## POSTED ORDERS TO CAMBERLEY PLEASE

58A HIGH STREET, CAMBERLEY, SURREY. Tel. 22791  
56 Stokes Croft, Bristol, and 247 NEW RD., PORTSMOUTH

**For Safety's Sake**  
use  
**AVO Prodclips**

Pat. No. 748811

..with Trigger-Action Spring-Loaded Clips

**PRESS TRIGGER TO OPEN**  
**RELEASE TO GRIP**

Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads. Post Free 15/- per pair.

**AVO LTD** • AVOCET HOUSE,  
92-94 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.  
VICTORIA 3404 (12 lines)  
A Member of the Metal Industries Group of Companies

# KENDAL TUBES

100% REPROCESSED AND ABSOLUTELY AS NEW

Crisp, high definition pictures with brand new Mullard, Mazda, Emiscope, etc., gun units

Latest type rescreening and aluminising, giving 60% more brilliance.

All types 50°, 70°, 90°, 110° Direct plug-in replacements

Fully guaranteed 12 months

**REAL SERVICE**  
Ordered today  
Travelling tonight  
Delivered tomorrow

TRADE AND EXPORT INVITED  
SPECIAL DIRECT SERVICES TO IRELAND & SCOTLAND  
Tel.: MILNTHORPE 2368

12" . . . . .£4.15.0  
14" . . . . .£5. 9.0  
15"-17" . . .£5.15.0 C.W.O.-C.O.D. Post & Ins. 7/6 (pass.)

**KENDAL TUBES**  
LEAGILL  
MILNTHORPE  
WESTMORLAND

# Practical Television

AND TELEVISION TIMES

VOL. 11, No. 128, MAY, 1961

Editorial and Advertisement  
Offices:

**PRACTICAL TELEVISION**

George Newnes, Ltd., Tower House  
Southampton Street, W.C.2.

© George Newnes Ltd., 1961

Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for trans-  
mission by Canadian Magazine Post.

## SUBSCRIPTION RATES

including postage for one year

Inland - - - £12.0 per annum  
Abroad - - - £19.0 per annum  
Canada - - - 19s. per annum

## Contents

	Page
Editorial ... ..	401
Telenews ... ..	402
The "Olympic" Cabinet ...	404
Servicing TV Receivers ...	406
Choosing a Valve Voltmeter	409
Television Sound Faults ...	412
Flywheel Synchronisation ...	417
How to Use Oscilloscopes ...	420
Special TV Tools ... ..	423
Underneath the Dipole ...	425
Letters to the Editor ...	427
Trade News ... ..	431
Your Problems Solved ...	435

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television". Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for the manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

## Television Aerials

WHEN television first began, one of the common criticisms levelled against it was the unattractive appearance of the aerials which were soon installed on many rooftops. However, it is only within recent years that this problem has been capable of solution—modern receivers are much more sensitive than early models and therefore require a less strong input signal. Modern transmitters are more powerful than their predecessors and their service areas extend for much greater distances. The result of these improvements in transmitter and receiver technique has been an increase in the use of indoor aerials which are not only more attractive but are also less expensive than outdoor types. However, it is not generally realised, especially by the layman, that the use of such aerials must be accompanied by a certain amount of care if picture quality is not to be marred. The main problem is to minimise the effect of reflections within the room; as the viewers move about, it may be found that the contrast of the received picture varies in sympathy. The solution is to position the aerial so that any disturbance is slight.

In certain circumstances, in flats for example, it may be obligatory to use an indoor aerial and the use of loft space will be precluded. Here, such aerials may give very poor results owing to the large amounts of screening metalwork which are likely to surround them. In flats, in particular, multiple reflections are liable to impair the definition of the picture—reflections from objects, and those caused by mismatches along the aerial cable, are both contributing factors. The effect is to cause a series of images on the screen of the receiver rather than a single, clearly defined picture. A very similar effect occurs when the bandwidth of the receiver is reduced from 3Mc/s to, say, 2Mc/s.

There is no easy solution to this problem and we think that in instances where the use of indoor aerials is enforced, then the provision of a multiple outlet amplified distribution system should also be compulsory.

### The "best" Aerials

Our experts are often asked which is the "best" television aerial. This, and other correspondence, shows that it is not generally realised that the aerial to be employed depends on the conditions at the particular location. In general, the stronger the signal, the simpler the aerial. However, it may be found that while in one house an indoor aerial suffices, across the road a five-element array is required to secure an acceptable picture. The strength and direction of interfering signals must also be taken into account: it may be possible to use the directive properties of a complicated aerial array to minimise the effects of both man-made interference and reflections of the television signals.

Thus, selection of an aerial for a particular site is only possible by a combination of experience, and trial and error. However, we are always pleased to help readers in this and other television problems provided that their queries are accompanied by the Query Coupon from the current issue, and by a stamped, addressed, envelope for our reply.

Our next issue, dated June, 1961, will be published on May 21st.

# Telenews

## Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of February, 1961, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal .. .. .	897,246
Home Counties .. .. .	657,662
Midland .. .. .	477,279
North Eastern .. .. .	524,914
North Western .. .. .	450,971
South Western .. .. .	383,652
Wales and Border Counties .. .. .	233,133
<b>Total England and Wales .. .. .</b>	<b>3,435,157</b>
Scotland .. .. .	387,517
Northern Ireland .. .. .	118,193
<b>Grand Total .. .. .</b>	<b>3,940,859</b>

## Printed Circuit Equipment

MAINLY as a result of the installation of the automatic, electronically controlled, equipment now installed in a new factory at Boreham Wood, Herts., Printed Circuits Limited are obtaining more and more export orders for all types of printed circuits.

During the month of January, orders were received from Western Germany, Hong Kong, New Zealand, Austria, Australia, Southern Rhodesia and Ireland.

The new equipment enables the firm to produce circuits of all types, rapidly, quality controlled at all stages of processing at a price which is now more than competitive with local production.

## Packaged Television Station

AN acute shortage of trained teachers and lack of suitable educational equipment in many areas of the world can be overcome by a new "packaged" television station now being marketed by EMI Electronics Ltd.

Costing less than £10,000, including the studio building and a number of receivers, the EMI packaged TV Station provides a low-cost, uncomplicated television

transmitter system which has been specially designed to meet the problems of education in television. The system has vast potentialities, not only in schools, but also in the field of adult instruction in such subjects as child welfare, public health and agriculture. In a region with flat terrain, good reception in schools should be obtained within 15 miles radius of the transmitter.

## Plastics for TV Set Design

MATERIALS such as plaster and papier mâché have been used for many years in the construction of television and theatrical sets. Bakelite Limited have now announced the introduction of an important addition to the range of materials available to the set designer—phenolic foam—a cellular plastics material which is fire resistant and easy to prepare.

The foam making process is basically simple and comprises the mixing together in a container of carefully calculated amounts of


phenolic resin and an accelerator. This results in a foaming action followed by rapid setting of the material.

In practical terms, a landscape set can be built to rough shape by constructing a light timber framework covered with hessian. The foam is mixed and then poured on to the supporting structure where it will harden within the half hour.

Usually the natural flow of the foam is sufficient for the effect required without any further forming or modelling. Where the sets to be constructed serve to add character to the production, however, the hardened foam can be shaped or finished with the greatest of ease without requiring special tools.
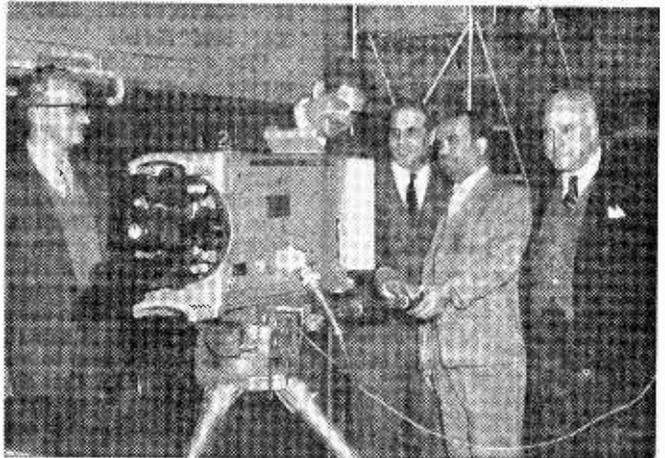
## 15 Colour TV Cameras for U.S.A.

EMI ELECTRONICS LTD. has been given orders totalling over a quarter of a million pounds for 15 colour television cameras, 250 monochrome cameras and other electronic equipment by its



Mr. Salah Amer and other members of his party inspect a Marconi Mark IV television camera at the company's TV Development laboratories.

American distributors, Fairbanks, Morse and Co., West Hartford, Connecticut.

EMI's colour TV camera utilises a novel optical system, several times more efficient than relay lens systems. It is compact and simple to operate, so is ideal for industrial use.

First colour and monochrome cameras under these contracts have already been dispatched to the United States and deliveries are continuing during the next six months.

### The BBC Sphere at Olympia

THIS year the BBC celebrates the 25th anniversary of its Television Broadcasting, and, at the Daily Mail Ideal Home Exhibition, the story of its birth and development to the present day was historically traced and visually described.


In a sphere which might be described as "an Aladdin's cave of electronic delights", 36ft in diameter and 12ft in height, a cascade of light and sound told the story.

Visitors passed through a dimly lit passageway into an even darker centre, and there saw light spots picking out a model of the Television Centre at White City—the largest television headquarters in Europe—and, appearing suddenly all round, were the flags of all the countries in the Eurovision link-up.

On the stand most of the activities of the BBC were illustrated, ranging from programmes in this country to those which from London now go out to Europe through the Eurovision network, originally sponsored and developed by the BBC, together with the French Television Service, and to North America through the BBC invention of Cablefilm.
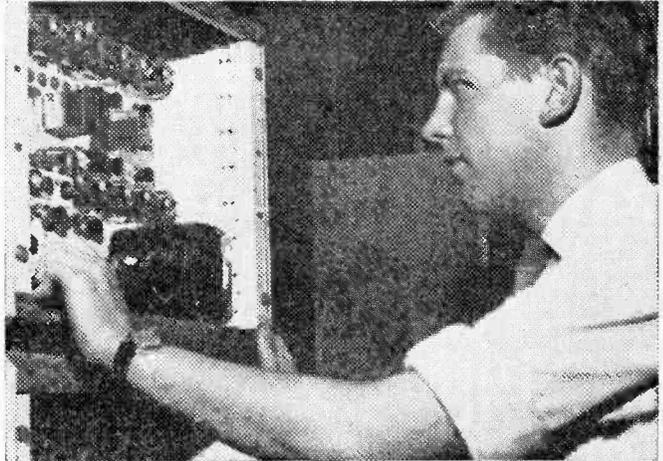
### Research Rockets

A SMALL exhibition of research rockets was held in the Science Museum recently. It was lent by the United States Navy Headquarters in London. Such rockets are fired to a height of nearly fifty miles and can be used to take samples of the atmosphere as they travel, and to transmit back to earth measurements of the temperature, pressure and radiation. When clear of the earth's atmosphere they can take photographs of the sun or of cloud formations over the earth.



The Pye special Effects equipment in Studio 2 Vision Control at Tyne Tees Television Centre.

The exhibition included five actual rockets of various sizes up to 14ft in length, and a nose-cone which has been recovered by parachute after firing to more than 100,000ft. The methods of firing and the results obtained from photographs were explained on screens.

### Russian TV Exchange

NEGOTIATIONS between ATV and the Soviet TV authorities have recently been concluded for a series of "live" programmes from Moscow during the British Trade Fair (19th May to 4th June). Programmes from Britain will cover the Soviet State Fair in London in July.

The opening of the British Trade Fair will be covered by a Russian OB unit under the direction of an ATV producer. Other programmes include ballet from the Bolshoi Theatre and a documentary on life in Moscow. In July, a Russian producer will direct an ATV OB unit covering the Soviet State Fair in London.

### New TV Tuner

THE American TV company, Zenith, has produced a new TV tuner which, they claim, can operate in the VHF or UHF bands without the need for conventional fine tuning controls to overcome frequency drift. It is built round a neutralised frame grid triode. A special gold-platinum-silver alloy is used on switching contacts with the object of eliminating corrosion and wear. Frequency stability is enhanced

by the use of a glass-filled alkyl material for the channel strips. This is not only stronger than materials normally used, but resists moisture, a major cause of frequency drift. The tuner uses no printed circuitry and is individually wired and soldered by hand.

### Egyptian Visitors

RECENTLY Mr. Salah Amer, deputy director of the United Arab Republic Broadcasting Corporation visited the Chelmsford works of Marconi's Wireless Telegraph Company Ltd. With other members of his party and Mr. D. Law, assistant chief of sales (studios), Broadcasting Division, he toured the company's TV Development laboratories.

### North East Electronic Engineering Exhibition

AMONG the exhibits of the Tyne Tees Television display-stand, at the first North East Electronic Engineering Exhibition, which was held in the City Baths Hall, Newcastle upon Tyne, from Tuesday, 28th February to Thursday, 2nd March, were two Marconi Mark IV 4½in. Image Orthicon Camera Channels, complete with all control equipment. These Cameras are normally used on Outside Broadcasts. Also shown was some of the Pye special effects equipment, as used in the Television Centre, Newcastle upon Tyne. An EMI TR90 sound tape recorder was demonstrated, and the public was able to record and listen to their own voices, with various special effects.

BUILDING A  
CABINET  
FOR THE

# OLYMPIC

(Continued from page 380 of the April issue.)

By R. Edwards


**F**INALLY the front and side edges of the stool base (Fig. 9 last month) may be covered. The top and bottom panels may be beaded in, and the speaker slats positioned and fastened by pinning from the back. A piece of gold finished aluminium grille is fixed immediately behind the opening.

**Back and Inspection Cover in the Base**


Cut out the back to size from  $\frac{1}{4}$  in. peg-board with a hole as shown (Fig. 8, last month). Drill and countersink around the edges for  $\frac{3}{8}$  in. No. 6 screws for fastening to the fillets. Make the cover to the dimensions shown in Fig. 10 and glue and pin to the back over the aperture. The purpose of this projecting cover is to allow a greater air space around the dropper resistance on the chassis.

The holes in the back for aerial, mains lead, control knobs, etc., are best marked out and cut after the chassis has been positioned.

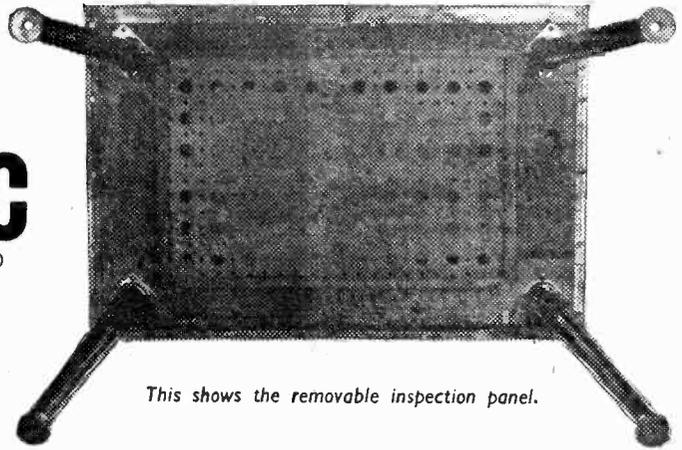Fit the bottom inspection cover to slide into rebates (see Fig. 9). To give good ventilation it is advisable to enlarge every other hole in the peg-board to  $\frac{1}{2}$  in. diameter.



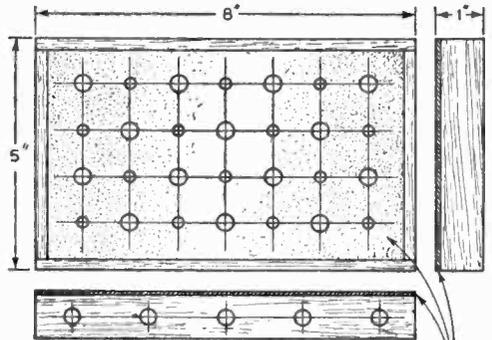This shows the removable inspection panel.



Recessed cover  $\frac{1}{8}$  thick Hardboard  
Fig. 10.—The dimensions of the ventilation panel on the back—see Fig. 8, last month.

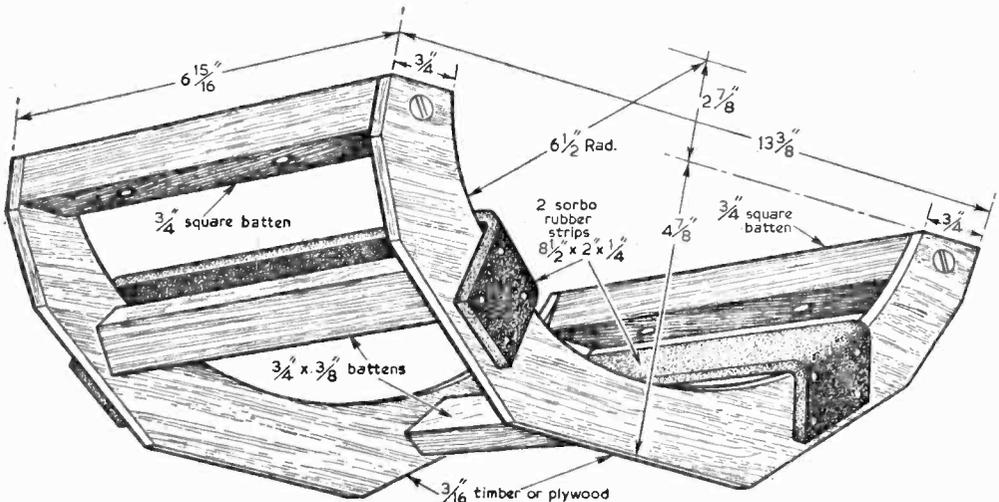


Fig. 11.—Constructional details of the tube cradle.

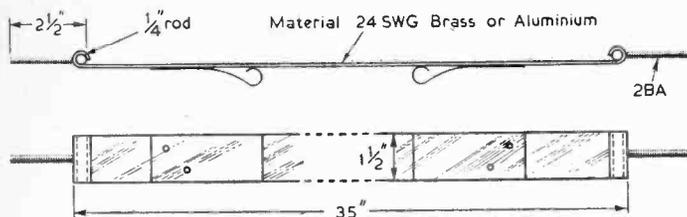


Fig. 12 (left).—Details of the metal tube clamp.


#### Mounting the Tube

Cut out a 2in. x  $\frac{1}{4}$ in. wide sponge rubber strip sufficient to encompass the periphery of the tube face, and sew the ends together to form a band. This should be a fairly tight fit around the tube. Place the aluminium strip in position.

Left:—The tube clamp.

When inserted into the frame, the tube face should project beyond the panel, leaving about  $\frac{1}{4}$ in. clearance from the "Perspex" front. Tighten the nuts on stems to clamp the tube and check that it is in centre of mask. Place the cradle in position and screw to edges of frame.

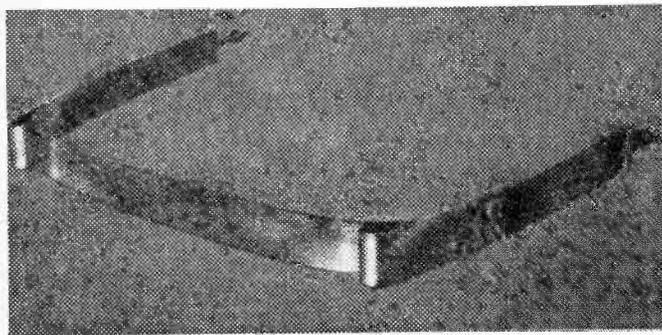The inside of the cabinet should have two coats of French polish brushed in to seal the woodwork, and finally be painted a flat black.




#### Tube Supports and Clamp

A section of wood, as shown, is cut out and fastened to the bottom of the frame (see Figs. 6 and 7, last month) and this is scribed and cut out to the shape of tube. Holes to take 2B.A. screws are drilled through the ends. The metal strip (Fig. 12) with additional curved pieces riveted on is cut from 24s.w.g. aluminium. The ends are bent round  $\frac{1}{4}$ in. brass rods, which in turn are drilled to receive 2B.A. x 2 $\frac{1}{2}$ in. stems. These form, with a nut, the tensioning devices required to clamp the tube.

Blocks 2in. x 2in. x  $\frac{1}{2}$ in. are glued to the top corners of the frame (Fig. 6, last month) and are for the strap projections to rest against.

The cradle, which is mounted behind the tube, is made up from  $\frac{3}{8}$ in. plywood sides with solid wood connecting pieces—Fig. 11. Two pieces of rubber strip are tacked across the top and bottom to bear against the tube as shown.

Fig. 13 (right).—The positions of the cradle and loud speaker baffle.

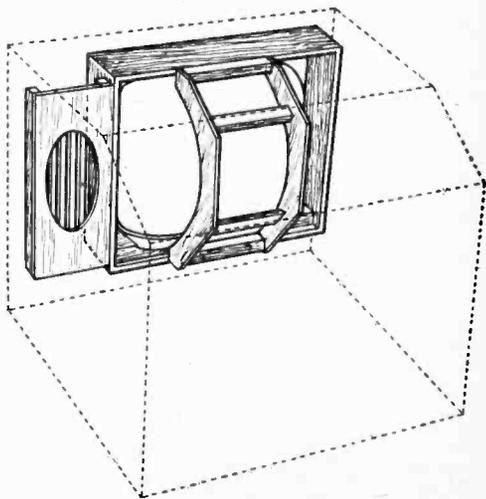

## THE OTHER MAN'S FARM


Electronic equipment which will control mechanism to open and close gates automatically, was one of the items shown in the popular ABC Television programme "The Other Man's Farm," televised from the farm of Mr. N. D. O. Capper, Ullingswick, near Hereford, on Sunday, 26th March, 1961, at 2 p.m. It was seen in the Midlands, North, TWW, Tyne Tees, Scotland and Ulster, where a similar type of programme has already been featured.

Discussing this electronic device with Franklin Engelmann and Ernest Milner was Mr. J. T. Taylor, Agricultural Development Engineer, and Mr. J. A.

Stokes, Manager, Industrial Electronics Engineering Department, both of Associated Electrical Industries Ltd. They also described other equipment which, although well known to many industries, may well be unfamiliar to farmers as aids to their everyday tasks.

Viewers saw electronic equipment which permits fluorescent lighting to be operated from normal tractor batteries, a vehicle which can be remotely controlled, and an automatic control for artificial lighting which can be used in poultry houses to simulate daylight in an endeavour to increase egg production.

# Servicing Television Receivers

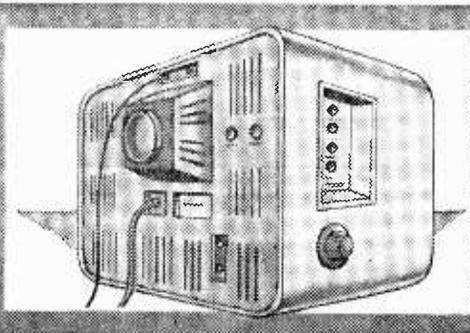

No. 67—THE DECCA DM45

(Continued from page 357 of the April issue.)

By L. Lawry-Johns

### Line Hold Troubles (see Fig. 1, last month)

VALVE V9 (ECC82) is used as the line oscillator in a multivibrator circuit and in the event of loss of line hold this valve should be the first suspect. As a general rule, the circuit components do not give much trouble and if a replacement ECC82 does not give the desired result, attention should be turned to the flywheel phase discriminator valve V8 (ECL80) and its associated components, although the only items likely to give trouble apart from the valve are the  $2\mu\text{F}$  capacitors C58 and C56.

### The Frame Timebase (see Fig. 2, last month)

This consists of a multivibrator formed by the triodes of V6 (PCL84), the pentode of which is the video amplifier, and V7 (ECL80), the pentode of which is the sync separator, feeding an output pentode V16 (PL84). The first fault condition which is likely to occur is frame cramping whereby the bottom of the picture is cramped and the top elongated, probably leaving a gap at the bottom.

This is normally due to a low emission PL84 and replacement of this valve will probably put this right—if it does not, check the cathode components R78 and C76.

The second most common fault is lack of height, leaving an equal gap at the top and bottom. This should direct attention to R70 (4-7M, yellow-mauve-green), which is connected to pin 1 of V7B. Replacement will usually clear the condition and restore normal height. Fluctuating height may be due to a faulty height control or a defective thermistor, TH2 (Varite Va 1008).

When V16 is replaced it is usually necessary to reset VR8 and VR9 to provide optimum linearity (equal spacing of the scanning lines).

### No Frame Scan

When the raster fails to form beyond a thin white line across the centre of the screen check V16, V6 and V7 and check the anode voltage of V16 at pin 7. If there is no H.T. present the output transformer (T2) almost certainly has an OC winding and this normally means replacement.

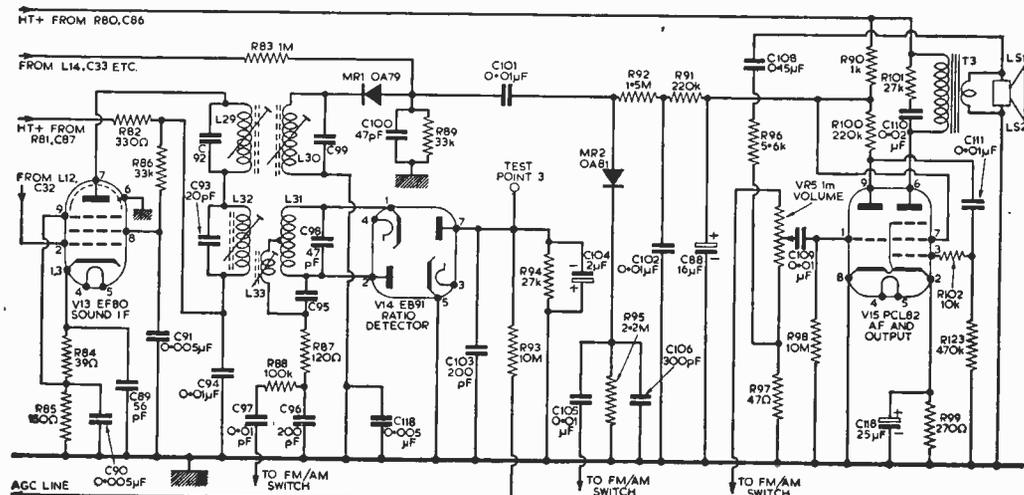


Fig. 5.—Circuits of the sound I.F., detector and output stages.

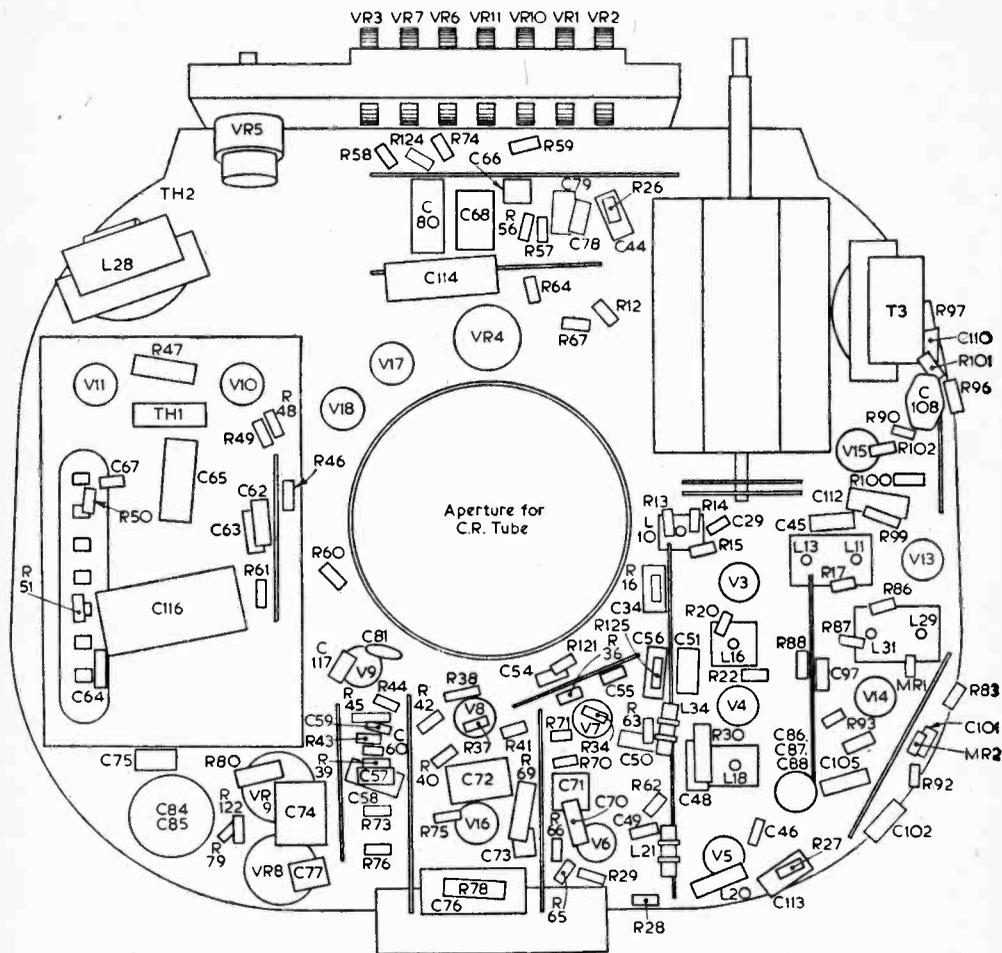


Fig. 6.—A simplified front view of the chassis.

If the H.T. is present and the valves are in order check VR7, TH2, C72 and R70.

**Loss of Frame Hold**

If the control VR6 is at one end of its travel and the picture is still revolving, check R64, although adjustment to VR4 may well stop the effect for a time. The purpose of VR4 is to enable optimum interlace to be obtained in conjunction with the hold control VR6. Interlace means the correct structure of the frame scan whereby all 405 lines are visible. If the picture is coarse and the line structure is made obvious by thick lines, the frame oscillator is not "firing" correctly and the interlace control should be adjusted until the lines appear finer and the picture detail at once improves. (See "use of controls"). If R64 is not at fault, and the picture continues to revolve, check V6 and V7, R71, R65 and R66 (R67 if necessary). C70, C71 and C73 are not often at fault.

**Poor Sync**

If the picture is a scramble in both directions, i.e., rolling freely and also pulling sideways, check V7 and V8. Although V8 is concerned with the line timebase the screen of V7 is strapped to its cathode and thus if V8 is faulty the frame sync will be impaired. In this connection C56 should not be overlooked and it is only the work of a moment to shunt a similar value capacitor across it for a quick test.

**No Picture—Raster Normal—Sound Normal**

If advancing the brilliance displays the line structure (raster) with no vision signal, the sound being normally received, check V4, V5 and V6. Check H.T. to pin 7 and pin 8 of V4. If absent, check the 330Ω feed resistors and the 0.005μF decoupling capacitors, C42 and C43. If these points are in order, check the video choke L20 which connects from pin 1 of V5 to pin 8 of V6. This coil may be o.c. at one end.

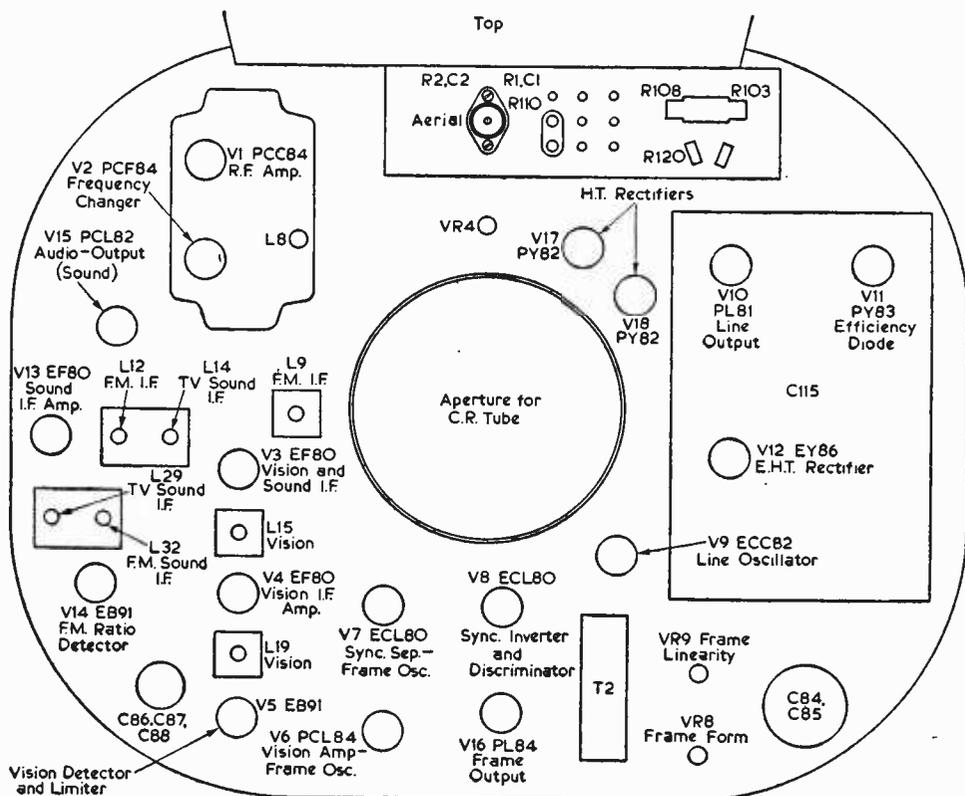


Fig. 7.—Rear view of the chassis.

**Vision Normal—No Sound**

Check V13, V14 (VHF—MR1 OA79—TV Sound) and V15, having ensured that the loudspeakers are connected.

**Distortion of Sound**

If on VHF only, check aerial, V14 and F.M. coil alignment, C104, etc.

If on TV sound only, check R92 (1.5M), MR1 and MR2 (OA81).

VHF and TV sound affected, check V15 (PCL82), which often develops grid-cathode leakage, R100 (220k) which sometimes "goes high", and if the distortion is accompanied by loud rustling-crackling, etc., check the switch wafer and disconnect H.T. leads for test. "Tracking" across the paxolin sometimes occurs, resulting in varying H.T. being applied to the volume control.

**Sound on Vision. R.F. Gain Set Correctly**

This refers to ripples or bars across the screen which vary with the sound modulation. Normally it is due to mistuning, but if the fine tuner is at one end of its travel it should be set mid-way and the oscillator core coil adjusted.

There is a hole in the front of the tuner next to the fine tuner spindle which allows a suitable trimming tool to be inserted for this purpose. If the effect cannot be cleared by this means without loss of sound or picture definition, set the core for maximum sound (which should correspond to optimum resolution) and adjust the core of L15. This is between V3 and V4.

(To be continued)

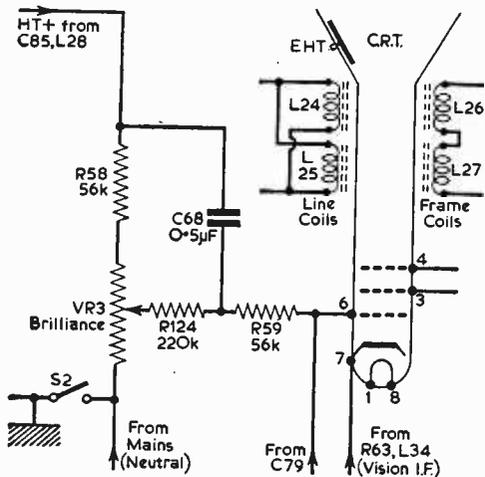


Fig. 8.—Scanning coils, brilliance control and tube connection details.

*There are many valve voltmeter circuits from which the amateur may select his design; this article will help you in*

# Choosing a Valve Voltmeter

*to suit your requirements*

By R. Brown

**T**HE universal multirange meter is a very useful instrument, and few of us would like to find ourselves without one. Its frequency range is, however, very limited, usually to the low audio frequencies, and it is impossible to measure frequencies above this limit. To measure such voltages, and to make measurements in high impedance circuits, the valve voltmeter has to be used.

This is an instrument, using valves, which measures voltage over the same range as the multimeter; but which presents a very high input impedance to the circuit being tested, and covers a very wide frequency range. A great many of these instruments are commercially available, either in kit form or made-up, and articles describing their construction regularly appear.

The type of circuitry used in any particular instrument will depend largely upon the job it is intended to do.

## Rectifier Plus Amplifier Instruments

The most common type of valve voltmeter is the one shown in Fig. 1. The audio or radio frequency voltage to be measured is fed into a diode detector. The output from this detector will be a direct voltage which will be proportional to the peak value of the signal being measured.

This is shown in Fig. 2. On the positive half-cycles of the signal the diode conducts and charges the capacitor. On the negative half-cycles the capacitor discharges slowly through the load resistor. As a result of this alternative charge and discharge the voltage across the resistor will be slightly less than the peak value of the signal; but R is usually very large so that the discharge is very slow, and the voltage across R can be assumed to be equal to the peak value of the signal for practical purposes.

A D.C. meter cannot be connected directly across the anode load to read this voltage, since its low resistance would cause the capacitor to discharge rapidly during the negative half-cycles of the signal; ruining the accuracy of the instrument, and making its input impedance very low. So some form of electronic circuit must be included between the diode load and the meter. This circuit should provide a very high input

impedance, since it is connected across the load resistance.

A high impedance input can be easily arranged using a triode valve, but since the voltage is direct the valve, or valves, must be directly coupled, and the meter readings tend to drift with changes in the mains voltage, valve ageing, etc. Some means of counteracting this must be found, and one such arrangement is shown in Fig. 3.


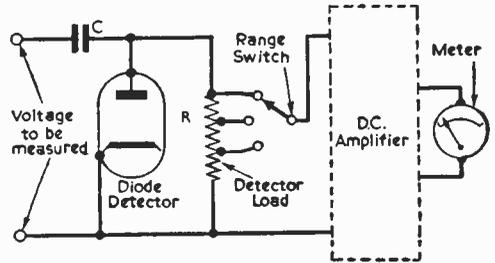


Fig. 1 (above).—The circuit of a rectifier-amplifier valve voltmeter.

Fig. 2 (below).—The voltages and currents in the detector circuit.

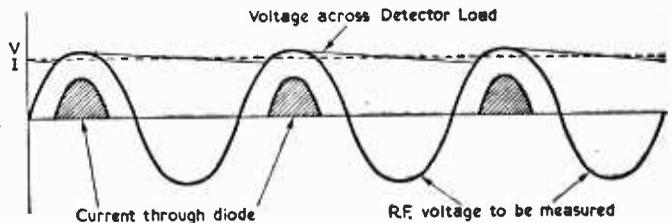

Two triode valves are used, of the same type, and connected in the same way. The meter is connected from the cathode of one valve to the cathode of the other valve, and the circuit values are chosen so that when there is zero input voltage the cathodes of the two valves are at the same potential; there is, therefore, no current through the meter, which indicates zero.

Any change in the mains voltage should now affect both valves equally, and, it is hoped, the valves will age at the same rate. This is probably

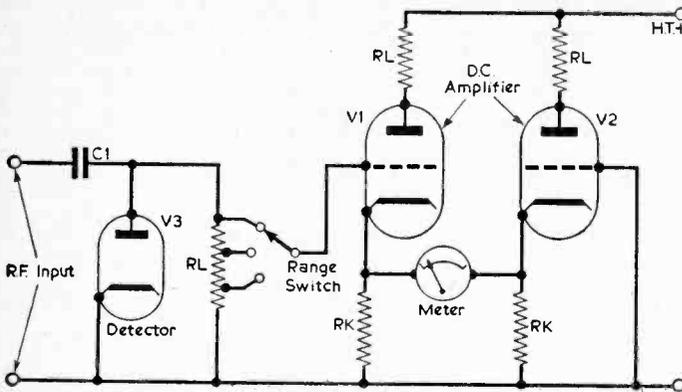


Fig. 3.—Another form of valve voltmeter.

the simplest form this type of voltmeter can take. It reduces drift by quite a lot; but other more complicated circuits are used, and these circuits reduce the drift to a correspondingly greater extent.

The drift is most noticeable on the most sensitive range of the instrument, and generally speaking the more complicated the circuit, and the more valves it uses, the less the drift, and the greater the sensitivity. With the circuit shown in Fig. 3, for example, the most sensitive range would probably have a full scale deflection of about two volts. With more complicated circuits, however, the full scale deflection could be as low as 300mV.

With most diodes the highest voltage that can be measured is 100V, although there are several diodes suitable for voltmeter use which can be used up to 300V.

The frequency range of the instrument depends largely upon the diode. Up to about 100Mc/s the frequency response is flat for almost all small receiving diodes. Above this frequency the inductance of the leads to the diode, and the transit time of the electrons from cathode to anode of the diode become important. The equivalent circuit of a diode at VHF is shown in Fig. 4 to be a series resonant circuit. The resonant frequency of the circuit, may be anywhere between 600 and 3,000Mc/s; but long before the resonant frequency itself is reached the inductance and the capacitance of the diode will have caused the voltmeter to give readings much higher than they should be. This is shown in Fig. 5.

The relatively long transit time of the electrons at VHF will have opposite effect to this. The positive half-cycles of the signal will be over before all the electrons have reached the anode. The charge on the capacitor will thus be less than it should, and the voltmeter will read low. This is also shown in Fig. 5, and the combined effect of transit time error and resonance are also given.

A full scale deflection of 300mV on the most sensitive range is the best one can hope for with this type of voltmeter, and this sensitivity can only be achieved using the more complicated and expensive instruments. It is, however, possible to improve on this sensitivity, and with a reasonably cheap instrument. Instead of a diode detector, a

leaky grid triode detector is used, the triode valve being in the probe.

With such an instrument the full scale deflection on the most sensitive range can be as low as 150mV. The maximum voltage that can be applied between grid and cathode of a triode valve suitable for this job is, however, limited to about two volts. This rather limits the applications of this type of instrument, and it is essentially a cheap method of measuring low radio frequency voltages, and is not a universal valve-voltmeter.

#### Amplifier-Rectifier Instruments

This is the second most used type of valve voltmeter. The voltage to be measured is first amplified in a wide band amplifier, and then rectified and fed to a moving-coil voltmeter.

The circuit of a simple instrument of this type is shown in Fig. 6. A cathode follower input is used, followed by a two-stage R.C. coupled amplifier. The output from the amplifier is fed

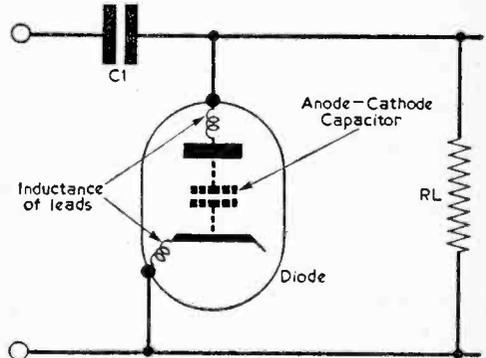


Fig. 4.—The effective circuit of a diode at VHF.

to a full wave rectifier which feeds the moving coil voltmeter.

Heavy negative feedback is applied over individual stages of the amplifier, and the output current from the amplifier flows through resistance R1, providing overall negative feedback. The effect of this feedback is to stabilise the gain of the amplifier so that it is largely independent of variations in mains voltage, component changes, and valve changes. It also helps to make the voltmeter scale more linear. This scale would otherwise be very crowded at low voltages because of the curvature of the rectifier characteristic.

The amplifier is usually fitted with high-frequency compensation circuits which, with the heavy negative feedback, ensures that its response is flat over a wide frequency range.

With a circuit similar to the one in Fig. 6, an instrument with a full scale deflection of between

10mV and 50mV on the most sensitive range can be produced. By including one or more further stages of amplification this sensitivity can be greatly increased, and instruments with a full scale deflection of as low as 1mV can be produced. The frequency coverage is very much less than with rectifier-amplifier instruments, typical figures

this voltage is fed to the amplifier. The range covered by the instrument is further increased by including an attenuator between the input of the instrument, and the cathode follower. This attenuator can then be used to attenuate voltages which are too large to be applied directly to the input of the cathode follower. In this way complete coverage from say 1mV full scale deflection to as much as 300V full scale deflection can be achieved.

The amplifier-rectifier valve voltmeter has much more sensitivity than the rectifier-amplifier valve voltmeter, although it covers a much more restricted frequency range. The rectifier-amplifier valve-voltmeter is also of more general use since it is possible to measure direct voltage and ohms with it, while the amplifier-detector instrument is A.C. only.

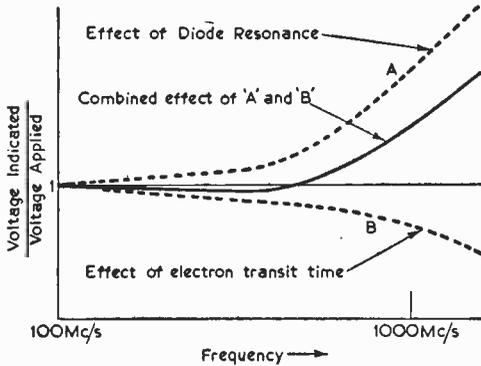


Fig. 5.—Before the resonant frequency is reached, the inductance and capacitance of the diode will have caused the voltmeter to give readings higher than normal.

**Interpreting Specifications**

It is not always quite clear what an instrument manufacturer or instrument kit manufacturer means by the details set out in the published specification. Not that this is an attempt, as is sometimes rather ruefully said by people who have bought an instrument only to find that it doesn't do quite what they expected, to pull the wool over the customer's eyes. It is just that it is difficult to state the range and accuracy of a valve-voltmeter in a simple manner. The voltage range, for example, is usually quoted in two ways, the specification states that the instrument will measure voltage over the range of, say, 25mV to 300V with an accuracy of 3per cent of full scale deflection,  $\pm 10mV$ . The ranges of full scale deflection being 300mV, 1V, 3V, 10V, 30V, 100V and 300V.


for the upper frequency limit being 1Mc/s to 5Mc/s, although instruments with upper frequency limits of as high as 10Mc/s or even 30Mc/s have been produced.

Now just what sort of results is this instrument going to give? Well, the first point to note is that, in common with almost all valve-voltmeters, the accuracy is greatest at full scale deflection; it falls off fairly rapidly as the voltage being measured

Switching of voltage ranges is normally carried out in two ways. The load resistor, R2, of the cathode follower usually has a number of tapping points on it. The voltage developed across the whole of R2 is fed to the amplifier on the most sensitive range, on other ranges only a portion of

(Continued on page 428)

Fig. 6.—The circuit of the amplifier-rectifier instrument.

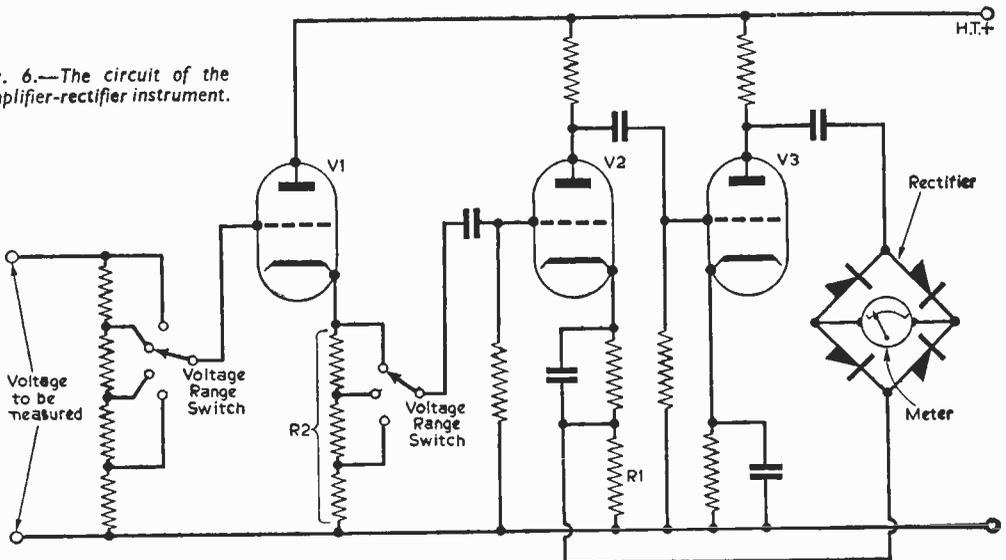

# Television Sound Faults

## TRACING INSTABILITY AND DISTORTION

By L. E. Higgs

**T**HE sound circuit of television receivers is often considered an "also ran" by some TV enthusiasts—and certain manufacturers—but a detailed examination of this necessary part of the set reveals it comprises at least one-fifth of the total circuitry and can produce some interesting fault symptoms peculiar to TV only.

### Response

The good frequency response of TV sound, noticed since early days of TV, is due to the virtually unrestricted bandwidth of sound transmission compared with the restricted range of AM radio sound. The TV sound tuned circuits are adjusted to give a wider pass-band than strictly needed to reproduce the highest audible sound in order to accommodate local oscillator drift without sound loss and, strangely enough, to allow ignition pulses to reach the detector undistorted where they can operate a limiter more effectively. This does not mean that sound circuit trimmers cannot be

peaked, because the coil coupling within the sound I.F. coils is often pre-set to give the required pass-band width.

The circuit of a typical TV sound section from the detector onwards is shown in Fig. 1, and most circuits will be found to correspond generally in most respects with this model.

### Frame Tick

This trouble is recognised by a regular fast ticking or high pitched buzz in the background of the sound which does not change with the picture content, and is present when not tuned to a station and which varies when the vertical hold control is

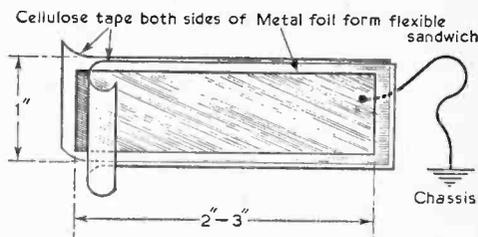


Fig. 2.—An insulated screen for reducing hum.

turned. Check the main H.T. smoothing capacitors for reduced capacity by bridging across with a spare 60 $\mu$ F, making sure the polarity is correct (Fig. 3). Hum and horizontal whistle from the speaker may also be present with this fault, and if the bridging clears it then the smoothing capacitor bank is deteriorating and should be replaced. Poor volume control input wiring screening can cause "frame tick" also, but, in this case, turning the volume control down either increases or decreases the sound. The best remedy is to probe gently and pull the wiring in the region of the volume control and high gain points of the circuit and try screening those most susceptible to hum. Use a

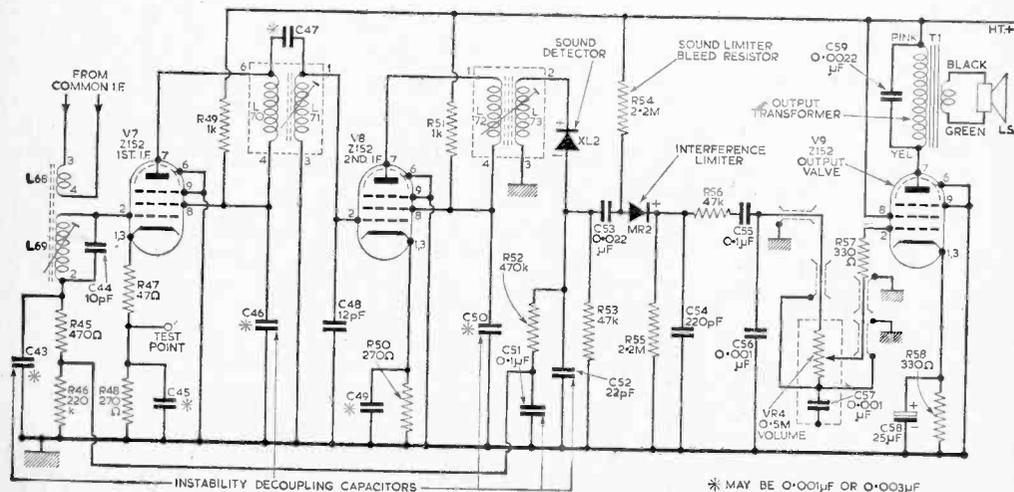


Fig. 1.—A typical sound section circuit.

strip of metal foil, well earthed, sandwiched between two layers of adhesive transparent tape (Fig. 2). If screening a component or wire silences the "tick", then the screen might be left in the chassis permanently or the offending wire replaced with a screened type. Poor bonding of screened wires also gives rise to this effect. Finally, this fault can also be caused by inter-electrode leaks in multiple valves where vertical oscillator and sound share the same vacuum space or cathode. Valve substitution is the quickest check here.

**Horizontal Whistle**

Like the vertical "tick", this trouble is due to part of the horizontal timebase voltage leaking back into the sound circuits, and the remedies to try are the same as above. Test for this by listening closely to the speaker while adjusting the line hold with the aerial disconnected, and the note should change and be heard through the speaker.

**Hum**

If present without the aerial plugged in, hum can be due to H.T. decoupling—test by bridging as explained under "frame tick".

Heater to cathode leaks can cause a larger proportion of hum faults in TV than in radio because there are so many more valves that can be involved. As many receivers put A.F. stages in multiple valves (double triodes, triode pentodes and double diode pentodes) with other sections performing "noisy" functions unconnected with sound, the results of leakage between sections (Fig. 4) can cause strong hum, possibly aggravated when the valve is tapped—again substitution is the quickest test as valve testers do not always show up intermittent defects. Do not confuse the prominent frame buzz that is emitted from the scan coils direct, and not from the speaker, with hum, and take care to differentiate between the sound of 25c/s of coils mains hum from the rattling buzz of vision-on-sound.

**Vision-on-Sound**

This is a harsh buzz that breaks through the sound only when a channel is being received—it cannot occur with the aerial disconnected. On a normally operating TV, tuning the fine tuner on the channel selector until the sound fades out, without losing or wobbling the picture, gives a buzz that rises over the sound; this is the video signal and will vary with the picture content—quiet with a grey or blank background and loud with large black and white areas. This is a good exercise to enable one to recognise this fault—on a normal set off-tune. Obviously if this trouble crops up, retuning the local oscillator is the first check. Remember, that if the fine tuner on one channel does not quite reduce this buzz—but the other channel is normal, there is a good chance that the coarse tuning slug in the turret is off-set and requires a slight adjustment on that channel only.

Another cause of vision-on-sound is overloading of the R.F. stage by too much sensitivity or too strong a signal from the aerial. Fitting attenuators in the aerial lead will cut out this type of sound buzz.

Leakage across common sound and vision valve sections—such as vision limiters in the same envelope as A.F. amplifiers—can cause vision-on-sound, and valve substitution is required for a quick test. Tuning misadjustment of the I.F. and R.F.

tuned circuits as a result of tampering with the slugs or trimmers is difficult to clear without a complete re-alignment exactly following the maker's procedure.

**Intermittency**

Crackles and fading in the sound, if accompanied by disturbances on the screen, are caused in the common sound and vision stages of the receiver—including the aerial and feeder. However, noise, with no picture disturbance, generally arises

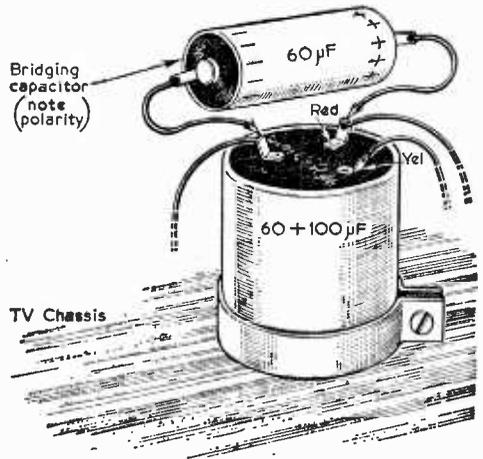


Fig. 3 (above).—The method of bridging a main smoothing capacitor.

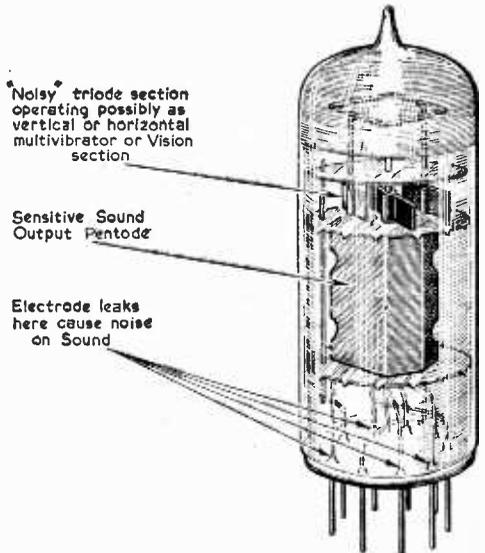


Fig. 4 (above).—The cause of inter-electrode noise.

subsequent to the sound take-off point in the common circuitry. Valve pin contacts, defective components, faulty valves and the volume control constitute the main sources of crackles. Gentle probing and tapping of suspect parts is the best

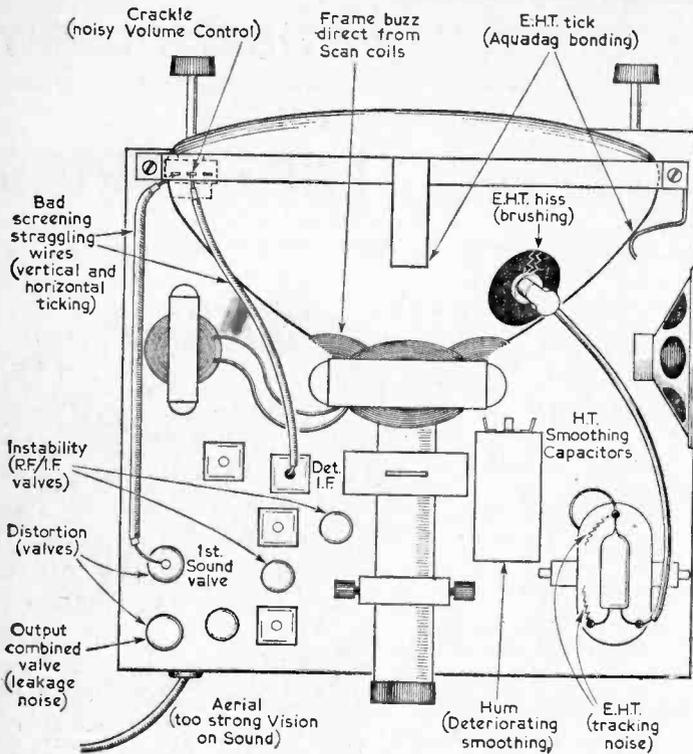


Fig. 5.—Possible points on the chassis where noises may originate.

approach to locate intermittent noise. It is advisable with intermittents to notice whether they are affected by a warming up delay and not to try looking for the trouble until the conditions exist.

#### Interference Limiter

This part of the circuit is peculiar to TV circuits and generally takes the form of a diode in series with the audio output from the detector (Fig. 1). With audible frequencies, the diode acts as a low resistance and passes the speech or music on to the amplifier stages. But, by a long time constant coupling arrangement, steep fronted high frequencies, e.g. motor vehicle interference pulses, bias off the diode momentarily switching off the sound circuit for the fraction of time that the impulse exists.

The efficiency of these arrangements varies considerably. The transient-triggered circuit is pre-set by the maker's choice of circuit components to "switch off" when a frequency just above audio range is received. Now, as these parts deteriorate, the upper trigger limit is reduced to *within* the audio range with an initial effect of exaggerated sibilant sounds—hisses and ssh's following "ess" sounds. This is nearly always due to a high value H.T. bleed resistor (Fig. 1) of around 2-3M going high in value (possibly 5-20M). The rise in value lowers the circuit time constant, causing audio clipping. When the resistor goes really high the sound output is weakened and distorted.

The diode in these circuits can be of the metal

(germanium) or thermionic valve types.

#### Distortion

Generally, distortion only takes place after the sound detector, as overloading in tuned circuits is unaccompanied by wave distortion due to the integrating effect of the resonant anode circuit. But, after the detector, everything can be suspect. The detector itself, the interference limiter (above), the usual two valve stages and their feeds, or even the loud-speaker itself. The best test for distortion is to "listen in" at the output valve grid, the live upper volume control tag and the detector in turn to isolate where the distortion stops—with phones (isolating capacitors in each lead: 350V A.C.), and trace forward from there.

#### EHT Tick

Spasmodic ticking that is sometimes missing, seldom rhythmic that occurs with the aerial disconnected and varies with picture brilliance, usually comes from the EHT D.C. circuit. Switch off all the room lights for this trouble and often, around poor bonding on the tube coating, a spark may be seen to flash with each tick. The EHT rectifier, too, may be defective and twinkle within when ticking takes place (Fig. 5).

#### EHT Hiss

A rushing noise in the sound, accompanied by random spots all over the screen or vertical ragged bars down the raster, is sometimes encountered on damp days for a little while after switching on. This is the effect of EHT tracking or brushing, over damp or dirty insulation in the line EHT high voltage points.

Cleaning insulating surfaces and adding a smear of silicone grease clears up this trouble if the materials are not pitted and carbonised (Fig. 5).

#### Instability

This effect is a roaring sound, distortion or a faint plop with permanent or occasional loss of sound. The alteration of the sensitivity, contrast, and fine tuning control may affect the condition, and there will be patterning on the screen to accompany it. If the internal trimmers have not been tampered with at any time, then this most difficult fault can be cleared by eventually tracing back to a faulty sound or vision valve which is oscillating—often owing to a screen, cathode, or H.T. decoupling capacitor deteriorating to a low value. Bridging all suspect capacitors with a 1000pF capacitor with short leads is the quickest check (Fig. 1).

# VITAL TO ALL IN THE INDUSTRY



## NEWNES PRACTICAL ELECTRICAL ENGINEERING

Written by 87 Recognised Authorities assisted by 170 World-famous Companies

Advisory Editor: G. F. Tagg, B.Sc., Ph.D., M.I.E.E., F.Inst.P.

Produced with the full technical resources of NEWNES, this new edition covers every important activity in the industry—it enables you, the forward-looking engineer, to acquire and retain knowledge so essential to your career. Every facet of the vast field of modern electrical engineering is dealt with—by qualified electrical engineers, who draw upon their knowledge and long experience to guide you to advancement. Prove its value by Free Examination for 7 days—post coupon to-day!


### Everything you want to know about—

- Installation Work of All Kinds—Commercial buildings, small houses and flats, hospitals, schools, theatres, cinemas, electric appliances, alarm systems.
- Instruments, Machines, Equipment—Electric motors, control gear, transformers, rectifiers, electronic control in industry, measuring and recording instruments and electricity supply meters.
- Operation, Maintenance, Repair—Welding plant, electric traction, cranes, lifts, X-ray equipment, testing domestic equipment, batteries.
- Generation, Transmission, Distribution—Power stations, power cables, public supply, underground distribution systems, town and rural supplies, cable-laying and faults.

### This is what you receive without obligation—

4 Volumes strongly bound in Grey Moroquette. 2,352 pages of instructive information on latest practice. 2,100 Photographs. Diagrams, Perspective and Working Drawings, Electrical Circuits, and Data on test procedure, etc. 24 Data Sheets in colour and 12 Quick-reference Blueprint Charts complete in Strong Chart Case. Nuclear Power Stations Booklet. Fascinating cut-away sections in full colour enabling you to see how they operate. With full explanatory text. NEWNES ELECTRICAL POCKET BOOK. The Electrical Engineer's "bible". Nearly 400 pages with 258 illustrations, diagrams, tables.

PLUS 2 YEARS' TECHNICAL ADVISORY SERVICE

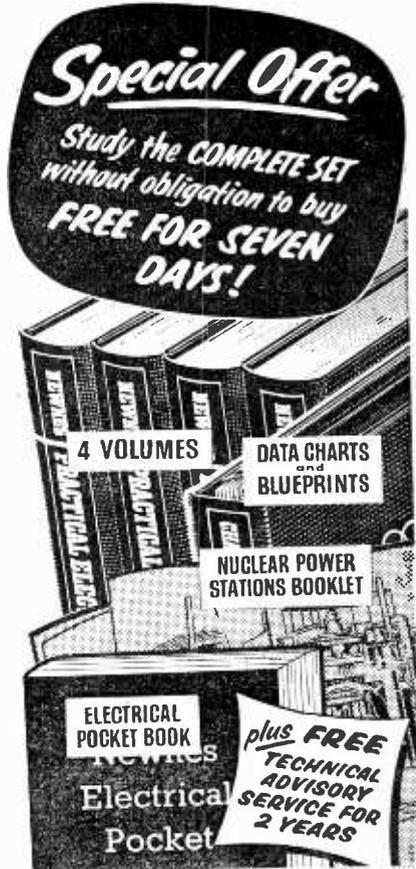

Act now for this thoroughly practical work—the complete set is yours for 7 days without cost or obligation to purchase.

Post Coupon To-day

To: George Newnes Ltd., 15-17 Long Acre, London, W.C.2

Name \_\_\_\_\_

Address \_\_\_\_\_

Occupation \_\_\_\_\_

Your Signature \_\_\_\_\_

(Or Parent's signature if you are under 21)

Tick (✓) where applicable

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

Please send me Newnes PRACTICAL ELECTRICAL ENGINEERING without obligation to purchase. I will return it in 8 days or send the first payment of 15/- eight days after delivery, and 15 monthly subscriptions of 20/- until the sum of £15 15s. has been paid. Cash price within eight days is £15.



# Flywheel Synchronisation

## Part 2

### COMMERCIAL CIRCUIT I

By R. Talks

In this circuit g1 and g2 of the pentode section of V2 are the oscillator electrodes. The coils S1 and S2 consists of 675 and 2265 turns of 42s.w.g. S.S.C. wire wave-wound on a 6mm diameter former. A long ferroxcube core of 3mm diameter is a coarse frequency control. The line hold control consists of a fine control in the form of a hinged metal flap. This acts as a shorted turn with variable coupling to the coil, the long core passing through it. The oscillator, of course, works in Class C, and its anode current pulses provide the drive waveform for the line output valve V3. The rising edge is shaped by R12 and C11 to bring the pentode back

sipation exceeding the valve limit; it has to be bypassed at oscillator frequency by C13.

The triode of V2 is the reactance valve. The anode resistance (ra) would normally give heavy damping of the oscillator tuned circuit. This is prevented by feeding the grid with a signal in antiphase to that at the anode and  $1/\mu$  of its amplitude. In addition, of course, we need a quadrature component at the grid to produce the variable reactance. In this circuit we require an increasingly positive discriminator output to increase the oscillator frequency. This is economically arranged by feeding the reactance valve grid via C9 from the opposite end of the tuned circuit from the anode. The grid circuit is effectively a capacity shunted by a resistance. This provides both the antiphase (to the anode) component and the correct quadrature component.

In the discriminator, T1, is the phase splitting transformer fed with sync pulses via V1, the function of which will be discussed later. The

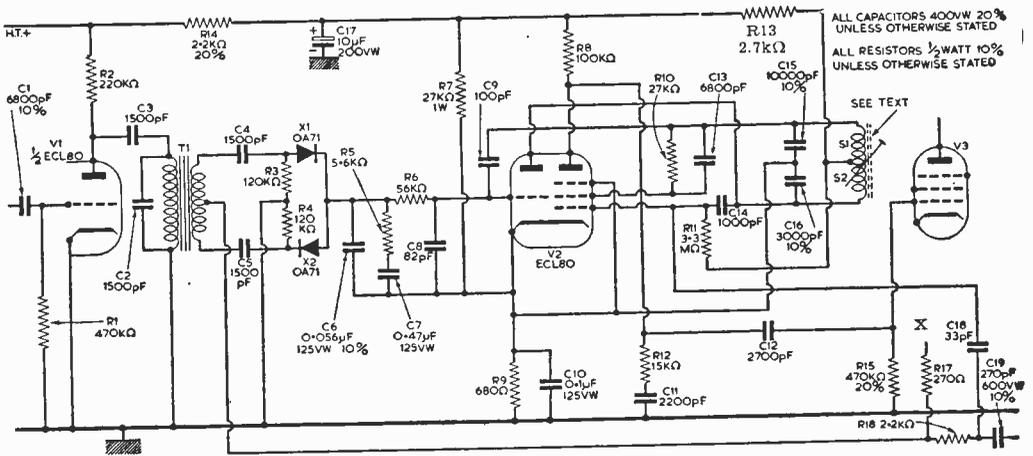


Fig. 8.—A commercial flywheel sync circuit. (Point 'X' is connected to the cathode of V3, from which point R16—10Ω—is wired to earth).

into conduction gradually. It is necessary to keep V3 cut off for a sufficiently long period; the flyback must not be damped, and, in any case, we do not require V3 to conduct in the early part of the scan. The grid leak, R11, is therefore returned to a positive point to give appreciable discharge of C14 during the non-grid conduction period. This ensures a long grid conduction period and so produces a long negative pulse at the grid of V3. The leading edge of this pulse must be steep. Its rate of fall is increased by adding C18. A positive pulse, derived from the line output transformer, is fed via C18 to the oscillator grid. As soon as this grid passes cut-off, causing flyback to start, the fed-back positive pulse rapidly drives the grid into grid current, so steepening the rate of rise of anode current. Resistor R10 merely prevents the g2 dis-

timebase waveform is obtained from the line transformer, where the flyback pulse is a half cycle of a sine wave. This is differentiated via C19 and produces at the secondary tap of T1 a waveform vaguely reminiscent of the ideal previously discussed (see Fig. 9). The diode circuit is "telescoped" somewhat compared with Fig. 5 last month, which served mainly to indicate the principle. The diode outputs are added directly in C6. This is the filter and its size largely determines the pull-in range.

#### Damping Circuit

We now come to R5 and C7—the damping circuit. Here it must be confessed that the earlier description of the mechanism of pull-in, whilst being correct in essence, was oversimplified. With-

out the damping circuit, the oscillator frequency "hunts" about the sync pulse frequency. After any disturbance, this leads to "wavy" verticals in the picture. The mechanism is as follows.

Firstly, we recall the three points enumerated at the start of the "pull-in behaviour" section and return to Fig. 7 (last month). When the sync-pulse phase reaches P, where, in steady conditions, the discriminator output would just lock the oscillator, the control voltage is lagging behind the discriminator output owing to the action of the filter. Consequently, the oscillator frequency has not been lowered to that of the sync pulses which pass, therefore, beyond P. Eventually the control voltage rises enough to bring the oscillator down to sync frequency, but now the discriminator output is higher than it was at P—the sync pulses are somewhere between P and N. This higher output raises

pulses, then we have achieved the ideal case and there is no overshooting of P, and therefore no hunting. That there is a suitable compromise in practice can be seen by looking at the two extremes of the damping circuit time constant. Assume C7 is very large and can be taken as a battery over the period considered. Now if R5 is very large, it is effectively an open circuit, and we have no damping circuit at all! If R5 is very small, then C6 is restored to equilibrium voltage almost instantaneously. In this case it takes a very long time for the phase to become correct again. Somewhere in between is a compromise. Playing about with the components in the damping circuit is a very easy way of achieving another half-hour of tax-free entertainment.

**Frame Sync Effects**

We come next to VI. All flywheel circuits find the frame sync period a rather indigestible morsel. Generally speaking, it alters the discriminator output and so changes the oscillator frequency. This

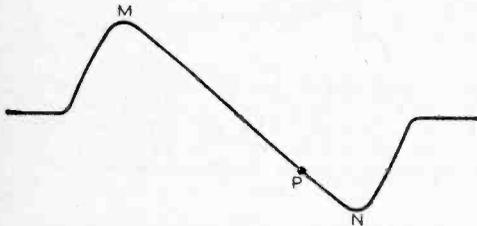


Fig. 9.—Waveform at the secondary tap of T1.

the control voltage still further, the oscillator frequency falls still further and the pulses start to move back towards P. At some point, the discriminator output falls below the control voltage and the above process repeats with the directions of change reversed. In theory, this hunting could carry on indefinitely, but in practice various things would damp it out. However, without R5 and C7, the damping is not sufficiently heavy and there is a train of "wiggles" after any sync disturbance.

It is easier to explain the action of the damping circuit in Fig. 8 by considering what happens after a sync disturbance. This, in any case, is the important problem in practice. Suppose the timebase to be running synchronised at some point, such as P of Fig. 9. Then C6 and C7 are both charged to the same voltage—the equilibrium voltage. Now suppose the sync pulses disappear for a time. Capacitor C6 starts to discharge via the diodes as soon as C4 and C5 have discharged enough to allow this. C7 falls in voltage much more slowly than C6 because the current flowing from it equals the difference of voltage on it and C6 divided by R5. That is to say, its rate of discharge is only small until C6 has discharged appreciably. Furthermore, the time constant of C7 and R5 is relatively long, giving a slow rate of fall of voltage on C7. So when sync pulses reappear, C7 is still pretty much at equilibrium voltage, but C6 has discharged and so the oscillator frequency has risen. The sync pulses are now somewhere between P and N, say. Now, we are back to the situation described in the preceding paragraph, but with this difference: C6 is recharged via the diodes and also from C7. Therefore, its voltage rises more rapidly than it would by charging via the diodes alone. If we can make C6 rise in voltage exactly in step with the phase of the sync

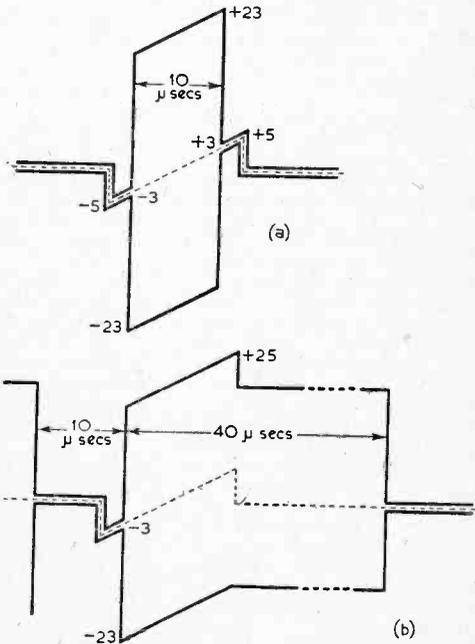


Fig. 10.—Waveforms with sync pulses of 20V amplitude—(a) with symmetrically situated line sync pulses; (b) during a frame sync pulse.

recovers once the frame sync period is over, but normally a residual effect is left which gives curved verticals at the top of the raster. The discriminator output is usually sensitive to pulse length, but the effect would happen even with our ideal rectifiers. Fig. 10 shows the waveforms with sync pulses of 20V amplitude, a timebase waveform running from (-5)V to (+5)V, and the relative durations more correctly shown than previously—10μsec sync pulse and 15μsec flyback time.

Suppose the line sync pulses to be symmetrically situated as in Fig. 10(a). The peak voltages are equal, and so the resultant output from the discriminator is zero. Fig. 10(b) shows the state of affairs during a frame sync pulse. The negative peak is not altered, but the positive peak has risen by 2V. It is the function of V1 to prevent this from happening. The grid of V1 is fed from the usual sync separator but, at its anode, the frame sync pulses are missing. The sync separator output has the form shown in Fig. 11. When the separator is brought into conduction, the valve current rapidly discharges the stray capacities, and there is a sharp fall of voltage at its anode. When the valve again cuts off, however, the capacities have to recharge via the anode load, which is a high resistance. So, the rising edges at the anode are a normal capacitor charging waveform with a time constant somewhat longer than 10μsec. A is a normal line pulse, B and C are twice line pulses. Their tips only rise to the level shown dotted. If this level is below the cut-off of V1, then they produce no output at the anode. Thus, in the frame sync period, the discriminator receives a long pulse (4 lines duration) which gives equal positive and negative peak voltages, and tends to produce zero discriminator output. This is no change if the original setting was as in Fig. 10(a). This "central" adjustment is important for several reasons. Firstly, it is the centre of the pull-in range and so allows most oscillator frequency drift (owing to mains variations, etc.) before readjustment is necessary. Secondly, loss of sync pulses will produce no change of output, and therefore no change of oscillator frequency. Thus, the picture will not have moved sideways in the raster when sync pulses reappear and there is least disturbance of the picture. Thirdly, spurious sync pulses outside the MN region give zero output because they are applied equally to both discriminator outputs. Thus, they give no change of frequency. Some flywheel receivers have made special provision for achieving this best adjustment.

Commonly, the line hold control knob has to be pushed in before it engages its electrical control. The pushing in also operates a switch which removes sync from the discriminator, thus ensuring zero output. The control is adjusted until the oscillator is as near sync frequency as possible, which is easily seen from the picture. Releasing the control reapplies the sync pulses. Despite these precautions, there is almost invariably a small residual curvature remaining at the top of the picture. The effect of the frame sync period is easily observed by turning the frame hold control until sync just breaks above 50c/s. As the picture drifts down, the frame blanking period can be studied (it can often be held steady near the middle of the tube face). The end of each line has a falling edge from black to sync level whether it be a line or a twice line pulse. If the brightness is turned up this edge can be seen, and its deviations from the straight (and narrow path of propriety) observed.

**Function of C2**

Picture centering with a flywheel always presents a practical problem. As shown in all previous



Fig. 11.—Sync separator output waveform.

diagrams, the flyback starts before the sync pulse at all settings within the pull-in range (in fact, within the hold range). This means that the right-hand side of the picture is folded over, except perhaps at one extreme of pull-in, where conceivably only the front porch is folded over. Capacitor C2 Fig. 8 corrects this. It delays the rise of the sync

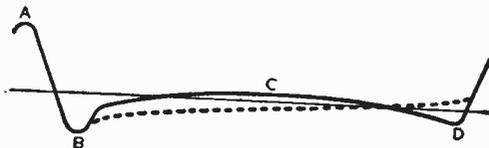


Fig. 12.—The addition of R17 prevents a spurious lock position—initially, CD has the same direction of slope as AB and lock is possible; adding R17 alters the slope of the curve as shown and this curve has the wrong slope for locking everywhere except between A and B.


pulse at the discriminator. In fact, the pulses shown in the diagrams should be "sloped off" appreciably, and their peaks occur later than the leading edge of the transmitted pulse.

One final component calls for some comment—R17. This is added simply to prevent a spurious lock position. The actual timebase waveform at the discriminator does not have zero slope during the forward stroke (see Fig. 12). In fact, the portion CD has the same direction of slope as AB. Consequently, locking with the sync pulses or CD, though weak, is possible. The waveform across R16 (which is wired from V3 cathode to earth) has no falling portion during scan, so it is added via R17, and so produces the dotted waveform of Fig. 12. This has the wrong slope for locking everywhere except between A and B.

Precautions must always be taken to prevent hum voltages, etc., reaching the reactance valve. Naturally, it cannot distinguish between "proper" control voltages and any hum picked up incidentally. Leads and components should not be placed near high voltage mains leads. An extra stage of smoothing is provided for the H.T. supply to the flywheel: R14 and C17.

Finally, it is of interest to see how far this timebase meets our requirements set out at the end of the section on Interference. Noise cancels out, largely because the sync pulse affects both discriminator outputs equally. Any slight lack of balance is not serious, though, because the flywheel filter reduces the effect of random variations. Provided that we are set to the zero output position, then change of shape of the sync pulses should have little effect, again owing to the balanced nature of the discriminator. Loss of sync pulses also has minimum effect since this condition too gives zero output. Interference and spurious pulses can have little effect as long as they fall outside the region AB of Fig. 12.

(To be continued)

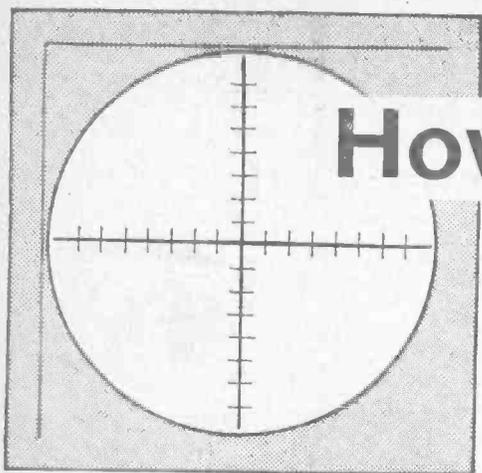

# How to use Os

By D. R. Bowman

**A**NYONE who takes up the study of electronics, whether for pleasure or to earn a living, sooner or later says to himself, "I wish I could see what is going on". This article is written to cater for those who have arrived at that point; they will be those who have perhaps built up a few circuits and have a working knowledge of practical circuitry.

In a very wide variety of circumstances, it is possible to "see what is going on"—providing one knows what to look for. The idea is not to persuade the constructor to buy an oscilloscope, but if it happens that any reader who possesses no such instrument decides afterwards that it is a "must", so much the better. For the real beginner—the man who "hardly knows a red volt from a black one"—the best advice is perhaps to keep copies of *Practical Television* carefully—the time will come!

## Use with D.C. and A.C. Circuits

Where direct current is concerned the oscilloscope is not unrivalled for making measurements, since other more portable and less expensive instruments do the job well. However, A.C. is the heart and soul of electronics, and as soon as voltages and currents begin to vary regularly with time it may at any moment become important to know just how, how much and how fast they are varying, and where they start from. The 'scope now comes into its own.

The astute reader will have spotted in the last paragraph the statement, in paraphrase, that alternating voltages and currents possess the properties of wave-form, amplitude, frequency and phase. This is perhaps a debatable statement, but it is near enough for practical purposes in most cases. All these quantities can be presented in visual form, and at least rough measurements made. It is fair to say that for precision work, measurements nearly always have to be made by means other than the oscilloscope. However, this is normally a requirement of the research or development engineer. The man servicing his own television receiver, setting up an F.M. receiver or

checking the fidelity of an audio amplifier rarely needs to undertake precise measurements; 5per cent is usually near enough, and often a "general idea" is quite useful.

## The Display as a Graph

The most instructive summary of a physical process in which cause and effect are related is the graph. The oscilloscope exists to draw graphs, rapidly and consecutively, which show the behaviour of currents and voltages. It is possible for the oscilloscope to show also the behaviour of fields—a good example is the television receiver where a linear scan indicates immediately that the magnetic field causing the scan is varying linearly with time.

Fig. 1(a) shows a typical graph. It represents the behaviour of the current in the circuit in Fig. 1(b). The reader will be familiar with the experiment, which consists essentially of putting the switch over to the right at a given moment and measuring the current flowing into the capacitor C at various later intervals of time. It is a simple enough matter to arrange circuit values so that the current can be measured with a milliammeter or microammeter at intervals of, say, 5secs, and to plot the results: 100 $\mu$ F with R1, 100k and a microammeter with a 9V battery. If R2 is 1k a slow drop in current over a minute or more is obtained with a much more rapid effect when the switch is reversed to discharge the capacitor.

The point about this armchair experiment is that time is related to current, and a recognisable wave-form of definite shape, amplitude and phase is produced. This gives a suitable introduction to the importance of time in electrical measurements. Not only time as the horizontal axis of the graph—the intended part of the experiment—but also the time taken to plot just one change at all accurately. To obtain a plot of the quantities just described takes at least three minutes. The oscilloscope can do no better in this particular case, but when circuit parameters include pF rather than hundreds of microfarads, and resistances of a few hundred ohms only it is vastly superior to the meter and the seconds-hand of a watch. In the experiment just outlined,  $t_1-t_0$  is at least 3 minutes; when it is 3 $\mu$ sec, the watch is not much use, and neither is the meter.

The oscilloscope is, therefore, predominantly a means of representing time—and very small intervals of time perhaps—along a horizontal axis, and the instantaneous value of a current or voltage along the vertical axis. The fact that it shows the result in a visual form is a handy by-product, but intrinsically the visual presentation is only a bonus—nevertheless a most useful one.

## The Importance of the Massless Electron Beam

It was remarked a moment ago that where time intervals are small, watch and meter are not very

# oscilloscopes

useful. It may be instructive to enquire why. Suppose the pointer of the meter and its attached moving coil were completely massless and offered no area to the surrounding air to cause damping of its movement, it might be supposed that the pointer would follow the voltage or current exactly. Then by repeating the experiment at regular intervals, hundreds of times a second, nothing could be seen but a blur where the meter pointer oscillated. However, by arranging a stroboscope to flash a little faster than the experiment was repeated, and illuminating the pointer with this device, a slow-motion picture of the experiment would be obtained. Note here, please, that the speed of movement is no real difficulty; what is the difficulty is in approximating to a massless meter movement.

In the original oscilloscopes, the mass of the movement was reduced by making it very small and light and using a beam of light as a weightless pointer. Extraordinarily good results have been achieved with these instruments, which still find a limited application. However, the mass still existed, and consequently speed of movement and ability to "follow" the waveform were such that the device could only cope with waves of low frequency. In the cathode ray tube there can be formed a pointer and "movement" of ridiculously small mass in the shape of a narrow beam of electrons. If the relatively high mass of the meter movement is "sluggish", the electron beam can be said to have a high "agility". One is tempted to write an equation at this point, but the temptation will be resisted. There will be plenty of equations for the experimenter later on when he starts to work with his instrument.

## The Electrostatic Tube

The cathode ray tube has been often enough described, in these pages and elsewhere, and it is not proposed to detail the construction and mode of operation here. Our discussion will deal, however, with the oscilloscope tube only, and except for specialised apparatus the only type used is the electrostatically focused and deflected tube.

This type of tube contains the usual electron gun, modulating tube or "grid", and anode together with an electron lens system. All these electrodes, provided with the correct potentials, contribute to the formation on the fluorescent screen of the tube of a small bright spot—the visible end of the massless pointer. In addition, means are provided for deflecting the pointer and so moving the spot. A further consideration of Fig. 1 will show that the horizontal deflection of the spot in that case would be proportional to time. This is very general in oscilloscopes. The horizontal axis of a graph is generically termed the "x-axis"; consequently there is required a means of X-deflection of the spot regularly with time. The axis of the graph at right

angles to this is known in general terms as the "y-axis"; consequently the waveform to be investigated will require Y-deflection of the spot, proportional to the instantaneous measure of the quantity concerned—usually voltage or current.

## Non-Temporal Quantities

So far it has been assumed that the x-axis will always be a measure of time, and it is true that very many of the measurements made with an oscilloscope do actually require a horizontal time scale. However, quite a number of useful comparisons can be made in which the horizontal axis of the graph is not temporal but concerned with some other quantity. An example is the use of the instrument to plot valve characteristic curves, either Ia-Vg or Ia-Va. Nevertheless, it is usually conventional to express any such x-quantity as if it were proportional to time, and to use the oscilloscope accordingly, for reasons of practical convenience.

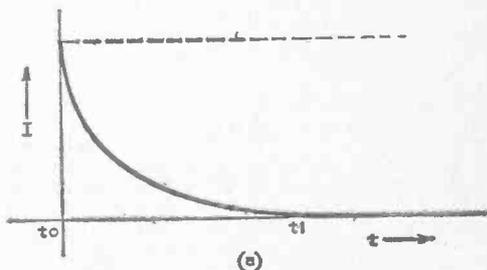


Fig. 1a.—A graph which represents the behaviour of the current in the circuit of Fig. 1b.

## Deflecting Plates X and Y

To accomplish the deflection of the electron beam, small metal plates are inserted into the envelope of the cathode ray tube—in the neck as a rule. They must not be placed too near the electron lens assembly, or the electric fields which focus the spot will be distorted. Nor must they be placed too near the tube face—or the electron beam's deflection will be too small to be useful. The plates are arranged in pairs as shown (Fig. 2). The Y-plates are usually


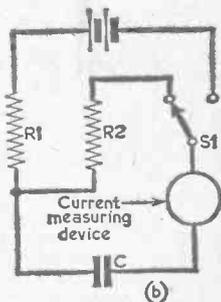


Fig. 1b (right).—An experimental circuit for obtaining the curve of Fig. 1a; the experiment consists essentially of putting the switch over to the right at a given moment and measuring the current at various later intervals of time.

placed nearer the electron gun so that improved deflection sensitivity can be obtained. The X-plates need not as a rule have such good sensitivity, and are put nearer the tube face. Sometimes, however, this arrangement is reversed, for special purposes.

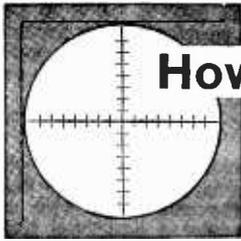The operation is simple to visualise. The



# How to use Oscilloscopes

beam of electrons, passing between a pair of plates, is affected—either attracted or repelled—by the field instantaneously existing between the plates. The beam is deflected, and continues in its new direction until affected by some other electric or magnetic field or until it strikes the fluorescent screen. If the plates are connected to sources of steady potential, a constant deflection will be obtained.

If the potential is doubled, twice the deflection should be obtained, and so on proportionately. This proportionality can be secured, by the correct shaping and spacing of the plates, to a high degree of accuracy. The angle of deflection is then a linear function of the potential difference between opposite deflecting plates.

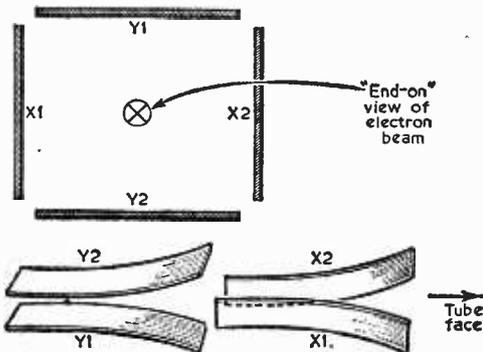


Fig. 2.—Arrangement of the deflecting plates.

## Sensitivity of the Tube

These considerations apply to both pairs of deflecting plates, and it will thus be seen that both X- and Y-deflections can be obtained, simultaneously, of the electron beam. The deflection of the beam, owing to a pair of plates, is given by the equation

$$\text{Deflection} = \frac{Vd}{Va} \times \frac{a}{b} \times l$$

where  $Vd$  = potential between deflecting plates  
 $Va$  = anode voltage  
 $a$  = length of deflecting plate in the direction of the beam  
 $b$  = distance between deflecting plates  
 $l$  = distance from centre of deflecting plates to fluorescent screen.

This formula applies only to electrostatically deflected electron beams. Where magnetic deflection is used, a different formula applies.

The equation may be obtained simply on theoretical grounds and can be shown to apply closely to practical cases. Two important

inferences can be made from this equation. First, that the lower the anode voltage, the greater the deflection sensitivity; and, second, that the deflection is proportional to the deflecting voltage.

## Linearity Requirements

It is worthwhile to consider again, at this point, the simple experiment discussed previously.

In order to show the graph of the experiment on the oscilloscope tube face, a number of requirements exist, as follows:—

- the movement of the spot along the horizontal (x) axis must be a linear function of time.
- the movement of the spot in the Y-direction must be a linear function of the current flowing.
- the experiment—the charging of the capacitor and noting current at equal intervals of time—has to be conducted as frequently as may be necessary so that by “persistence of vision”, the moving spot on the tube face may appear to trace out the appropriate curves.

The last consideration involves the discharge of the capacitor, the return of the spot to the beginning of the graph, and the reconnection of the capacitor to the charging circuit. The mechanical and electrical arrangements would be simple enough to devise in practice. If, as in the particular example quoted, the trace is too slow to appear as a line on the tube face, a photographic exposure—or the use of a tube with long-afterglow or “long persistence” qualities—could be arranged.

The requirement that spot movement in the X-direction must be linear with time necessitates the design of circuits which will set up a potential difference between the X-deflecting plates which increases linearly with time. Such circuits are known generally as linear timebase generators. Since the potential can hardly go on increasing indefinitely with time, a halt is called at some convenient point. At this point the spot is returned, as rapidly as practicable, to the beginning of the trace ready for the “sweep” to start again. This is known as the “flyback”.

The requirement that deflection in the Y-direction must be a linear function of the quantity being measured, means that unless the latter is a sufficiently high voltage to be applied direct to the Y-plates, a Y-amplifier of linear characteristics is needed, together perhaps with other linear circuit elements such as resistors. “Linearity” is another name for absence of distortion, and it might be thought that normal good amplifier design would be sufficient to ensure good results. This is actually a mistake; very great care indeed has to be taken in designing suitable circuits, as will be seen later.

(To be continued)

## NEXT MONTH

Building a simple check 'scope  
for TV

# SPECIAL TV TOOLS

## HINTS AND AIDS FOR SERVICING

By H. Bedford

**O**VER the years, a special collection of tools that have proved their worth by easing difficulties and speeding the job has appeared in the boxes and bags of TV enthusiasts and full-time engineers.

Most of these aids are simple and inexpensive, such as the insulated dental mirror used to detect concealed burn spots on the inaccessible side of wirewound resistors, read labels on valves too hot to withdraw, and turned away from the user, and to check for dry joints under tags. Mirrors can be obtained for a couple of shillings or so from tool shops, but you will have to insulate the metal stem and backing before using them on a live chassis.

Mirrors are usually accompanied by the light from a torch, but so often it is not practical to shine a light from behind or under the subject to be illuminated. An idea that overcomes this problem is to connect the base of a broken flashlight bulb to an MES bulb holder via a length of coaxial cable, the inner core connecting the centre contacts and the outer braid the threaded body. The connections are soldered and bound with tape (Fig. 1). This accessory takes up no room in the tool box and can be screwed into a flashlamp when an awkward job is encountered.

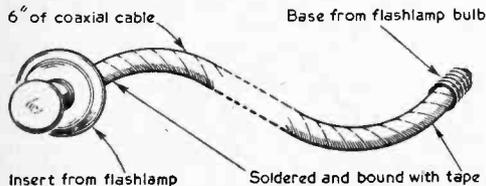


Fig. 1.—Flexible inspection lamps made from odd lengths of coaxial cable.

Trimming tools are fast becoming specialised items with the many types of adjustment encountered on various receivers issued over the years. Many of these tools can be most easily made up from a collection of knitting needles filed to shape. Certain types of earthed studding adjusters are not affected by metallic contact and flattened brass tube can be used. The hexagonal hole found in later slug cores is ingenious because it permits the lower core in a tuned inductance to be adjusted *through* the upper core by a special plastic tool with a turned-down shank section (Fig. 2). This circular section does not disturb the upper core while the lower is adjusted, and when lifted out of engagement with the lower core, the upper core can be manipulated.

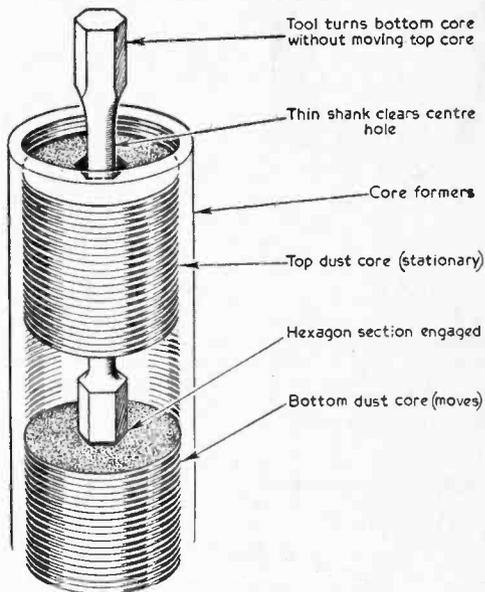


Fig. 2.—This tool enables the bottom core of an I.F. transformer to be turned, without moving the top core.

Soldering methods have changed greatly during recent years, and the 65W irons common years ago are almost displaced by miniature types of less than 25W consumption and the quick-heat type powered by a transformer. Printed circuits have accelerated this change, and the transformer type of iron enables the tedious job of melting six connections at once to be carried out easily (Fig. 3) when replacing I.F. transformers on printed circuits.

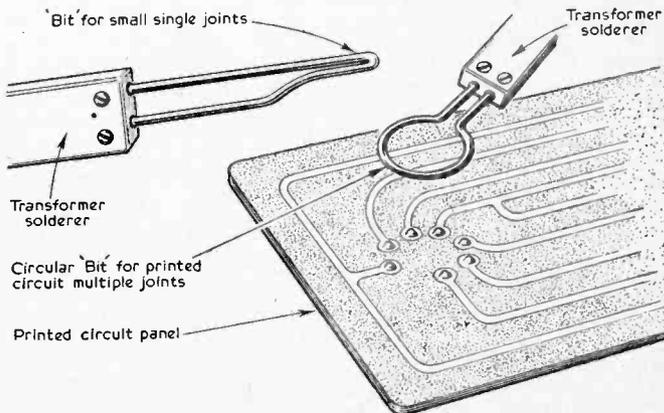


Fig. 3.—Transformer soldering irons with special "bits".

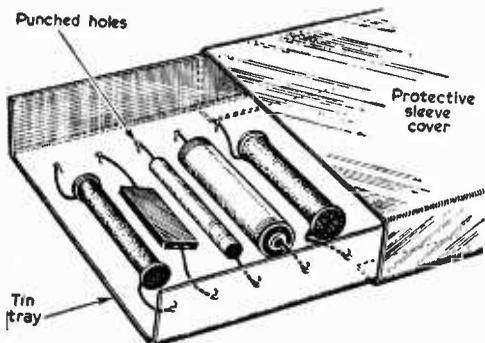


Fig. 4.—A convenient method of storing wire-ended components.

Printed circuits also demand a needle-sharp probe on the multimeter for contacting through the layer of varnish with which many circuits are coated.

A watchmaker's lens for checking suspect joints on printed circuitry and inspecting the small components found in modern TV sets is becoming virtually a necessity.

The high magnetic fields surrounding loudspeaker speech coils and focus assemblies make work with ordinary steel tools difficult, if not impossible. A pair of slender, plated, non-magnetic tweezers simplify the work considerably when removing particles from the speaker gap or soldering moving coil connections. Some of the older focus and picture centring assemblies were sensitive to steel tools used when adjusting the raster position. The picture shifts over to one side when the screwdriver is brought near the adjustment, and after

adjustments are made removal of the tool again displaces the raster. All that is required to overcome this disadvantage is a piece of brass rod fixed to a screwdriver blade and set in a wooden handle. This tool has no shifting effect on the magnetic field at all as it is non-magnetic.

Generally magnetic effects cause difficulties, yet it is often an advantage to carry a small magnet in the tool kit; for example, when a screw has to be fitted in a narrow aperture that only the screwdriver can reach. By holding the magnet in contact with the screwdriver shank the tip of the tool becomes magnetised and the screw will remain on the blade while it is gently carried to its inaccessible spot. If the screw is dropped at all then fishing with a magnet or magnetised tool quickly finds it. Small powerful magnets can be obtained from scrap focus assemblies.

Volume and brightness controls are nearly all fixed with a standard locking nut,  $\frac{1}{16}$  in. Whitworth. By keeping a box spanner with a thin wall in the kit it is sometimes possible to remove and refit these controls through the bottom of the cabinet after slackening the control nut first through the front panel hole.

Certain of the more usual tools can be conveniently kept in wallets, saving room and weight in the tool-kit. These tools need not be particularly expensive. However, items such as long-nosed pliers and side cutters should be the best quality obtainable.

The loose jumble of resistors and capacitors that accumulate in the bottom of a tool-kit is bad for the parts themselves, and time is wasted in looking for the value that has been half erased. A tidy way of stocking these parts is to mount them in a thin "match box" type of container that can be bent up from thin sheet metal with small pierced holes to hold the wire ends as shown in Fig. 4.

#### International Award for "Outstanding Contributions to the Advancement of Television"

The Committee of Honour of the world's first International Festival of Television Arts and Sciences announces that 71-year-old Sir Noel Ashbridge will be one of six internationally famous scientists to receive a Citation "for outstanding contributions to the advancement of television and broadcasting".

Others to be honoured are: General David Sarnoff (U.S.A.), Professor J. Boutry (France), Professor P. V. Shmakov (U.S.S.R.), Doctor Kenjiro Takayanagi (Japan), and Mr. Eric Esping (Sweden).

It was stated from Montreux, where the Festival will be held from 15th to 27th May, that a Presentation Ceremony will take place at Montreux Palace Hotel on the afternoon of Saturday, 20th May.

A welcome will be given to those receiving Citations by a member of the Festival Committee of Honour, after which there will be a keynote address.

Actual presentation will then be made by the Festival Committee of Honour to which recipients, or their representatives, will no doubt wish to reply.


The Citation will take the form of a Scroll, which will mention the outstanding contributions made by the recipient in the advancement of television and broadcasting.

## PRACTICAL WIRELESS

Chief Contents of the  
May issue

Now on Sale, 1/6

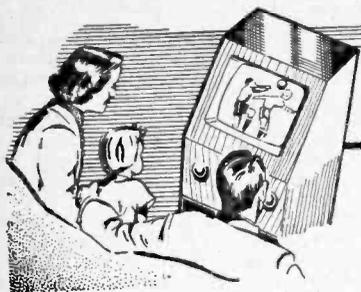A VHF TUNER  
AN AUDIO BOOSTER STAGE  
AN INTRODUCTION TO STEREO  
A COMPACT ADD-IN B.F.O. UNIT  
TRANSISTOR CHARACTERISTICS  
TRANSMITTING TOPICS  
SHORT WAVE SECTION  
CLUB NEWS  
ETC., ETC., ETC.



## UNDERNEATH THE DIPOLE

TELEVISION PICK-UPS AND REFLECTIONS

By Iconos

**T**HE closing of the Walton-on-Thames studios is a blow to British television as well as to British films. It was here that the phenomenally successful Robin Hood series was made, still being shown and reshowed at television stations all over the world. Advertising filmlets, "The Buccaneers", "Sir Lancelot", TV serials, and, of course, a large number of important British feature films were made here.

### The Walton Stages

Walton studios had five stages, three of them very large and capable of coping with the largest type of film production in Cinemascope and colour. There has been a film studio on its site since 1898, when Cecil M. Hepworth started making films in the back garden of a villa in Hurst Grove, Walton, including the historic four-minute drama, "Rescued by Rover", which has been seen on television many times. Hepworth was a fine photographer and technician besides a practical film producer (as film directors were called at that time). He was the inventor of the original machine for automatically developing and printing cinematograph films, which replaced the clumsy method of winding the films on frames and dipping them in deep developing and fixing tanks. Hepworth's machine was the forerunner of the modern Lawley automatic film processor, used in all the BBC and most of the ITA television centres for developing 35mm and 16mm news and documentary film. Hepworth built two of the first all-glass "daylight" film studios at Walton, which operated continuously making silent film features for many years until talking films arrived, when the plant was expanded with an addi-

tional soundproofed stage and a large exterior "lot". Television requirements plus its normal cinema film output strained its capacity, and more stages, workshops and an elaborate sound dubbing theatre were added.

This theatre was acoustically treated to make it suitable for recording large symphony orchestras; it also included a closed-circuit system for telecine and television. Now, it seems, the whole historic site is likely to fall into the hands of a land development company who will erect flats, offices and, I suppose, the inevitable supermarkets. This seems to be the fate of many theatres, film studios and music halls in these days of increasing site values and diminishing box office takings. Henry Irving, Dan Leno and Cecil Hepworth wouldn't have liked it at all.


On the other hand, I feel pretty certain that all of them would have studied and embraced the

newer medium of television with enthusiasm as another field of show-business.
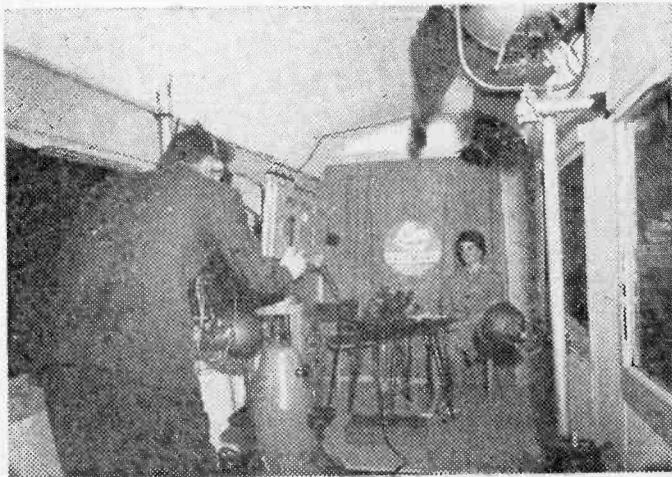
### Early days at Ealing and Lime Grove

Hepworth's rival in the film pioneering days was Will Barker, who built a three-stage film studio at Ealing Green in about 1906, where dozens of short melodramas and comedy films were turned out at the rate of one every two days! I am told that chases by comic looking policemen in the Keystone tradition were a familiar sight to the residents of Ealing in those days. Later, rebuilt and modernised, it turned out many world-famous films under the direction of Sir Michael Balcon until it was taken over by the BBC for its very comprehensive documentary film services on 35 and 16mm film.

Gaumont's original British film studio was at Lime Grove,



The exhibition train which toured the West Country to publicise Westward Television's new commercial service, which begins transmission on April 29th, contained this fully operational TV studio equipped by Marconi's.

Shepherd's Bush, and was copied from Hepworth's all-glass "daylight" studio at Walton, which was on the first floor with workshops underneath. This studio also expanded to four sound-proofed stages when talkies arrived, but one of them retained the shape, size and exact location of the pioneer Gaumont studio stage. When taken over by the BBC, this original stage was one of the first to be brought into use for television and continues to give excellent service.

At any rate, it seems that Ealing and Lime Grove will carry on in the true tradition of show business. The show must go on!

In case any reader wonders what an all-glass daylight studio is, I must explain that in the early days of silent films, most cinema studios relied upon daylight as an illuminant, sometimes adding a few supplementary arc lights or low-pressure mercury vapour lamps for effects. Other lighting control was with blinds or scrim diffusers supported on wires beneath the glass roof. The results were then much better photographically when compared with films shot entirely with artificial light.

But there were difficulties on days when the light varied with the sunshine and clouds. The advent of talking films and the need for soundproofing spelt the end of these elaborate greenhouses. Some of the original studios were bricked-up, roofed and soundproofed and are in use to this day. Apart from the original Lime Grove stage already mentioned, one of the smaller stages at the National Studios, Elstree (now modernised by ATV) was a pioneer silent film studio that is still "in business". This stage had its height raised by seven feet by digging down that amount and fitting a new floor.

### History of Television

THERE are several different ways of presenting history on television, varying from the elaborately edited film of the actual events to the simple straight-forward lecture, in which the speaker uses few notes and fewer diagrams. With a really competent and sincere speaker who is completely at home with both his subject and with the television camera, the informal off-the-cuff "fireside" chat is probably just as effective as the

edited film. But there are not many television lecturers of the standard of General Sir Brian Horrocks and Alan Taylor, who are able to retain the interest of viewers by sheer personality apart from their thorough grasp of every historic subject they discuss.

Documentary television films of actual events in the last war are the product of much patient research and the collection of film excerpts from many sources, followed by skilled editing and the addition of commentaries and background music. Good though these are, one is acutely conscious of the professional polish applied in the editing process and the opportunity it might give for manipulation or falsification. On television, the war film montages with rapidly succeeding shots of shell bursts, guns firing and bombs dropping, etc., all accompanied by heavy dramatic music, all tend to lose their impact upon the viewer when seen, in the same form but in different context, for the umpteenth time. This type of television history presentation is naturally confined to the last sixty-three years, for it was not until 1898 that an important historic event was recorded on motion picture film—Persimmon winning the Derby. Before this time, history was visually recorded by the artist-reporter or, from about 1850, by the earliest of still photographers.

### "Meet Mr. Lincoln"

A fine example of the use of visual stills was seen in "Meet Mr. Lincoln" an American TV documentary by the N.B.C., presented on BBC television. Very early photographs taken during the American civil war together with reproductions of artists drawings and contemporary Press cuttings were brilliantly edited to form a coherent visual story, with long shots, close-ups, panning and tracking shots. Intelligent use of camera movement on the title bench when photographing these drawings seemed almost to give the illusion of moving pictures. The narration and background music told the story and set the mood with great effect—leading

up to the assassination of President Lincoln at a theatrical performance, a sequence which came over with an impact which conveyed the full tragedy of the event. I thought that "Meet Mr. Lincoln" was one of the best television documentaries we have had from the U.S.A.

### Regional Competition

THE BBC's television studios and facilities in the various provincial areas cannot be said to be on a grand scale, when compared with their ITA rivals—excepting in the London area, where the BBC's studios at Wood Lane, Lime Grove, Shepherd's Bush TV Theatre, Riverside Studios, Ealing Studios and the Alexandra Palace must amount to a staggering figure in capital investment, not to mention the huge running cost and hundreds of staff required. In the provinces, BBC facilities are good, but on the whole, comparatively modest.

In Scotland, the expanding studio stage space and facilities of Scottish Television may indirectly have had something to do with the BBC's recent decision to double the capacity of their television building in St. Margaret's Drive, Glasgow, at a cost of about £800,000. The same trend is reflected in other places where competition is expected. Even in Plymouth, the BBC TV facilities have been greatly expanded to compete with Westward's opening at the end of April. The competition in this area intensifies in those parts of Somerset and North Devon where there is an overlap between TWW and Westward—where viewers will have a choice of three programmes. The new ITA transmitter at Stockland Hill has received excellent reception report from Weston-super-Mare and from parts of Bristol. A three-way choice of TV programmes is quite a possibility these days, with more than one line connection between various parts of the country. As far as I can make out, there is nothing to prevent Westward taking items from ATV and ABC—TV at the same time as TWW is taking, say, Granada and A.R.—all on the same evening.

**Practical Wireless May issue . . .**

**NOW ON SALE! Don't forget to get your copy**

# Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents.

**SPECIAL NOTE:** Will readers please note that we are unable to supply Service Sheets or Circuits of ex-Government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

## CORONA DISCHARGE

**SIR,**—For some time I have experienced intermittent corona discharge in my home-made receiver, and this appeared to vary in such a way that I could not put it down to any one factor. Recently I decided to try and find a solution and noted that this discharge, which was accompanied not only by sound in the speaker, but also by spots on the screen, seemed to vary with the picture content. It finally transpired that a dark picture, which obviously did not fully load the EHT circuit, caused corona, and this disappeared when a very bright screen was displayed. I thought, therefore, that a load across the EHT might work, but such a load would have to be removed on bright images or larger current drain. I thought of a thermistor in the EHT lead, or one across the EHT supply, but could not find a valve which would work, and finally I made a considerable improvement in a very simple manner. I was utilising the screening of the tube as the EHT condenser, via a spring contact, and in the course of testing the efficiency of this I used a separate condenser I had available. It was marked  $0.001\mu\text{F}$  and it appeared to give better results than the tube coating. This I found on looking at a circuit was rated at  $0.0005\mu\text{F}$  so I concluded, rightly as it turned out, that a much larger condenser was required. Finally I used two  $0.001\mu\text{F}$  condensers in parallel and the corona does not now occur. Perhaps one of your experts will say whether or not this large capacity will do any harm to the rectifier.—G. BENSON (Watford).

## STELLA ST6417

**SIR,**—Mr. Sirl (Salisbury) complains that the line hold needs to be continually readjusted (Your Problems Solved, February 1961). Changing the 220k to 100k sometimes helps with stronger lock. The most effective cure is to replace the line blocking oscillator transformer, as a slight leak between windings or short-circuited turns will make the line hold very critical indeed. This was the fault on one particular set I had to repair. The changing of the 220k to 100k gave a much better lock, but when switching on from cold, the line hold needed to be adjusted and it slipped out

of lock again after about  $\frac{1}{2}$  to 1 hour.—S. WHITTEN (Buckingham).

## VALVE FAULTS

**SIR,**—Some time ago I saw in your pages a criticism from a reader who had experienced difficulties caused by valves not being standard. I recently had a strange experience which might be of interest to others who come across an apparently incurable fault. I have a set in which there are no less than three ECC82's, and one of these is used in the frame timebase. Recently the hold was getting very weak and eventually I had to do something about it. I realised that substitution of the valve would be the first thing to do, so I removed one of the other valves and changed it over with the frame valve. The trouble was not removed, but hold was a little firmer, and the original valve did not seem to affect the other part of the circuit to which it was transferred. I did the same thing with the other ECC82, and again there was not a complete cure. I thought it very unlikely that three valves would all be faulty, but thought it worth while having them tested. When put on a tester at the local shop all three showed the need for replacement. I did purchase a new one, which when inserted in the frame section returned the set to its original condition, but the other parts of the circuit work perfectly with any of the three valves. It would appear that after just over four years' working all three have fallen to the same level, but the frame timebase is the only part of the complete circuit where the characteristics of the valve are critical.—F. H. ROBERTSON (York).

## ADVERTISING AWARDS

**SIR,**—The ITA have recently announced that they will no longer televise any advertisements which compare one product with another. This would appear to be a result of the severe criticism that all television advertising has received during the last few months. There is, therefore, a need for something that would encourage advertisers to produce advertisements that are in every way enjoyable for the viewing public. Why not, then, have a "Television Advertisers Awards" scheme, where, each year, Oscars are given to the companies whose advertisements are, in the opinion of either, a committee or the public, most appealing (not, of course, meaning free gift offers and the like). Awards could be given for such qualities as, the most interesting, the most amusing, or the advertisement with the most pleasant musical arrangement. If enough publicity were given to such a scheme, advertisers would surely make an effort to raise the standards of their advertisements.—R. BROOKS (Staines).

**DECCA DM45**

**SIR**,—R. Houston, Your Problems Solved (January issue), complains of lack of height at bottom of the picture on his Decca DM45. If after replacing V16, —PL84 vertical output, V7—ECL80 sync separator and half-frame multivibrator, V6—PCL84 vision amplifier and half-frame multivibrator, a cure is not effected, I would suggest a check is made on the following two capacitors, C76 (500 $\mu$ F cathode capacitor of V16) and C77 (0.03 $\mu$ F) feedback capacitor in linearity circuit, from anode of V16—PL84). If C77 develops a leak or short circuit it causes cramp at the bottom, or even complete foldover at the bottom. C77 has been faulty in two of these sets I have serviced; C76 was faulty in another set.—S. WHITTON (Buckingham).

**LINE CONTROVERSY**

**SIR**,—I feel that any suggestions that, in this country we should change our television system to one using 625 lines, are quite useless. My reasons

for this are, firstly that on any size screen, smaller than a 21in. model, the difference would not be easily noticeable by the average viewer; and secondly that, if two receivers each having a different number of lines, were viewed side-by-side the superior quality of the 625 line set would be obvious, but viewed apart, I am sure that the improved picture would not be appreciated.—G. REENSLEVE (Walthamstow).

**TV MASTS**

**SIR**,—I have only recently become interested in television construction and servicing, and must confess that, as yet, I know very little about this subject. There is one thing that worries me in particular, and that is how to tell the difference between a television transmitting aerial and the many other masts that litter our countryside. I do not even know if there is any structural difference that may be easily recognised and is common to TV masts, but if any reader knows one, I would be obliged if he would write in.—M. A. STUART (Coulsdon).

## CHOOSING A VALVE VOLTMETER

(Continued from page 411)

decreases, and generally speaking the lower part of the scale is very inaccurate. Taking the three-volt range as an example, the accuracy with which 3V can be measured is 3per cent of 3V,  $\pm 10$ mV, which is  $\pm 100$ mV, about 3 $\frac{1}{2}$ per cent. When measuring 2V on this range the accuracy is again  $\pm 100$ mV but this now corresponds to 5per cent, and at 1V the accuracy has deteriorated to 10per cent. The voltmeter ranges are, however, usually chosen so that the lower part of any range is covered by the next lowest range. To measure 1V or lower in the example given, one would switch over to the 1V range.

This cannot be done, however, on the lowest range, 300mV in this example, and one can only make rough measurements on the lower part of the range. At 100mV, for example, the accuracy is  $\pm 3$ per cent of 300mV  $\pm 10$ mV, which is  $\pm 19$ mV or 19per cent, and this error increases rapidly at lower voltages on this range.

Details of the frequency response are also included in the specification, and must be taken into consideration when estimating the accuracy of the instrument. The frequency response curve is usually flat over a wide portion of the frequency coverage, and the figures for measurement accuracy already discussed apply here.

At the low frequency end, however, the response of both types of valve-voltmeter start to fall off, while at the high-frequency end the response of rectifier-amplifier instruments becomes high (Fig. 5) and the response of amplifier-rectifier instruments falls off. Over these upper and lower portions of the frequency coverage the error due to the change in frequency response, which is usually quoted in decibels relative to the response at mid-frequency, must be added to the other

errors quoted to obtain the total possible error in the voltmeter reading.

## BRITAIN'S FIRST SCHOOL-TO-SCHOOL TELEVISION LESSONS

An unusual experiment in the use of closed-circuit television as an aid to teaching is being tested by High Definition Television Ltd., a company of the Pye Group, in co-operation with the Middlesex Education Committee, the Hayes and Harlington Divisional Executive and the School Governors.

Two schools two miles apart—Hayes Grammar School and Barnhill Secondary Modern School—have been linked by microwave equipment so that science lessons from the Grammar School can be televised direct to the Secondary Modern School. This is the first time that such an experiment has been made part of the regular curriculum in a British school, and it will be seen that this is a *school-to-school* television operation as distinct from the national schools television service offered by both BBC and ITV. This experiment will last for a complete term and is registered with the National Foundation for Educational Research.

In Hayes Grammar School a Science Master teaches his own class, using various apparatus to illustrate the lesson. He faces not only his pupils but two small Pye industrial television cameras. One of these is situated directly opposite the teacher and covers his desk and the blackboard. The second camera, on the teacher's extreme right, is used for enlarging small objects and to give close-up views during scientific experiments.

The teacher wears a microphone hung around his neck and is able to select cameras and sound circuits by means of a specially designed switcher unit placed on his desk. A monitor screen shows him the picture being transmitted to the other school.

At Barnhill Secondary Modern School a large High Definition Television schools receiver with a 27in. screen faces the class.

FURTHER HUGE PURCHASES DIRECT FROM SOURCE

# 13 CHANNEL TVs

TABLE MODELS, FAMOUS MAKERS. Complete with all valves and tubes. Unequaled in value. They are untested and not guaranteed to be in working order.

AMAZINGLY POPULAR-IDEAL SECOND SETS

12" - £3.19. (p. & p.) 12/6

14" - £5.19. (p. & p.) 15/-

12" 5 CHANNEL TV's 45/- (p. & p.) 12/6  
14" 5 CHANNEL TV's 85/- (p. & p.) 12/6

## UA8 Stereo Changers

B.S.R. famous Monarch autochangers, fitted with quality stereo cartridge. Truly amazing value. P. & P. 3/- £6.19.0

100 RESISTORS 6/6

100 CONDENSERS 10/-

Miniature Ceramic and Silver Mica Condensers, 3 pF to 5,000 pF. LIST VALUE OVER 85.

CO-AX standard and low loss, 25 yds., 12/6, 50 yds., 22/6, 100 yds., 42/6. Co-ax. Plugs 1/8. Wall outlet boxes 3/6.

External ITV Converters with power pack. Hammered finish. Very compact. Gain and Trimming controls. Listed at £7.7. Carriage 2/6. OUR PRICE 39/-

MIRROR GALVANOMETERS. Everashed and Vignoles, 45 second swing, high sensitivity, heavy metal cases with spares in transit case. Unused. £3.10.0. A "MUST" for School Laboratories.

# TUBES DIRECT FROM OUR FACTORY

Due to the increasing demand for our wide range of CRT's and our efficient handling methods we offer unbeatable values.

TOP QUALITY GUARANTEED	6 MONTHS	12 MONTHS	12 MONTHS
Carriage and Insurance 12/6	SECONDS	REGUNNED	BRAND NEW TYPES
CRM92, MW22-7, MW22-14, MW22-14C, MW22-17, MW22-18	£1-10	£3	MW31/74 £4
12KPA, 12K, C12B, CRM121, CRM121A, CRM121B, CRM122, CRM123, MW31-14C, MW31/16, MW31/18, MW31/74	£1-15	£3-10	MW38/44 £4 MW38/24 £5
141K, 7201A, C14FM, CRM141, CRM142, CRM143, MW36-24, MW36-44, 17ASP4, 171K, C17FM, CRM171, CRM172, MW43-64, MW43-88	£2	£4	CRM172 MW43/64 £5
7401A, AW43-80, C14BM, C17BM, CRM151, CRM152A, CRM152B, CRM153, CRM173, MW43-80, MW41-1	£2-15	£4-15	CRM172 MW43/64 £6
AW53-80, CRM212, MW53-80, MW53-80	£3-15	£5-15	

PLEASE NOTE: Many other types not listed available. S.A.E. enquiries.

## SPECIAL OFFERS

4-SPD. RECORD PLAYERS. Latest B.S.R. PU9 Turntable, together with lightweight Star Gaxay dual sapphire crystal turnover pick-up head. Truly amazing value. £3.10.0. Carr. 3/-.

GALAXY PICK-UPS, as above, only 2/6.

TRANSISTORS. Yellow Spot, 2/6, Green spot, 2/6, Red Spot, 3/6, White Spot, 4/6, Ediswan XB104, 8/6, XA103 (4 Mc/s), 10/-, XA104 (6.8 Mc/s), 12/-, O.C. 44 15/6, O.C. 45 15/-, O.C. 70, 14/-, O.C. 71, 8/-, O.C. 72, 12/-, (Matched Pairs 22/-), V15/10P (10 watt power), 14/-, Yellow/Green, 5/-.

SILICON DIODES. 125 V. 500 M.A., 2 in series make superior replacement for R.M.4 and R.M.5, etc. 8/- each.

TV PROJECTION UNITS. Complete Standard Philips optical units with Mullard MW-2 projection tube. £3.10.0 (untested) at a fraction of cost.

12in. TV's 5 channel table models in cabinet. Top making speaker, line trans. and tube to complete your choice if available. (Carr. 4/-). (Or 28 per dozen, carr. free.) 15/-

14in. TV's 5 channel as above 35/-

Chassis Bargains ALUMINIUM BOX FORM. Heavy gauge steel ends, un drilled. 6in. x 4in. x 2in. 4/-; 8in. x 6in. x 2in. 5/2; 10in. x 7in. x 2in. 5/9; 16in. x 8in. x 2in. 10/-; 12in. x 8in. x 2in. 8/9; 14in. x 10in. x 2in. 9/9.

4 Transistor Amplifiers. ONE WAIT - From single 6V all-dry battery. Latest GEF15 Power Transistors. In PUSH-PULL Two-Transistor High Gain pre-amplifier stages. Output 3 ohms. £3.19.0

Test Sets Type 74A. A service scope easily convertible for standard use, 200/250 v.a.c., all valves, E.C.R.30 tube. £4.10.0. Excellent case worth £10. Our price.

# ★ VALVES BY RETURN OF POST ★

10% DISCOUNT SPECIAL OFFER TO PURCHASERS of any SIX VALVES marked in black type (15% in dozens). Post: 1 valve, 6d., 2-11/-.

NEW LOW PRICES GUARANTEED 3 MONTHS

FREE TRANSIT INSURANCE. All valves are new or fully guaranteed ex-Government or ex-equipment origin. Satisfaction or Money back Guarantee on goods if returned unused within 14 days.

0Z1	8/-	8AQ5	8/-	8K6GT	8/6	8X6GT	5/8	12K7GT	5/-	43	7/6	DA90	2/6	ECC40	19/-	EL50	9/-	N47	11/-	SU2150A	UCL83	12/6	
1A3GT	5/-	8AT6	6/6	8K7	5/8	7A7	7/6	12K8	12/-	30C5	7/6	DA32	9/6	ECC81	5/6	EL84	7/6	N78	11/-	4U6	UP41	8/6	
1A7GT	11/6	8A6U6	7/6	8K7G	2/8	7B5	12/6	12K8GT11	50C6D	832/6	DA91	9/6	ECC82	6/6	EL80	6/6	N108	16/-	T41	7/6	UP42	5/6	
1C6GT	8/6	8B7	8/6	8K7GT	4/8	7B6	9/6	12Q7GT	3/-	5016GT	3/6	DA96	7/3	ECC83	6/6	EL91	4/6	N152	8/6	TD44	7/6	UP80	7/6
1D5	8/6	8B8G	3/6	8K8	11/-	7B7	7/6	12R67	8/6	52KU	10/6	DF33	6/6	ECC84	8/6	EM34	8/6	P41	8/6	P41	8/6	UP85	8/6
1L6	9/6	8B14	6/6	8K8G	5/6	7C5	7/3	12S17	8/6	53KU	10/6	DF31	3/6	ECC85	7/6	EM80	8/6	P61	2/3	U18	8/6	UP86	14/6
115GT	9/6	8B26	5/6	8K8GT	9/6	7C6	7/3	12S17	4/8	54KU	8/6	DF56	7/3	ECC86	8/6	EM81	8/6	PAB	PC8011/-	U22	6/6	UP89	7/6
1L4	8/6	8B26G	12/6	8K25	7/6	7D10	8/3	12SK7GT4/9	61B7	16/-	DH63	6/3	ECC82	8/6	EM84	9/6	PCCR4	7/-	U34	15/-	UL41	7/-	
1LD5	3/6	8B16	6/6	8L1	12/6	7H7	9/6	12S17GT	61B7P	11/-	DH76	5/-	ECH21	12/6	EM85	10/6	PCCR5	10/-	U26	9/6	UL46	9/6	
1LN5	4/6	8B16	6/6	8L9	9/6	7K7	9/6	12Y4G	8/6	75	8/-	DK32	11/3	ECH35	8/6	EN31	15/-	PCCR8	10/-	U26	9/6	UL46	9/6
1N5GT	9/6	8B16	7/6	8L9G	7/6	7Q2	7/6	12Y4G	3/-	77	8/6	DK91	5/6	ECH43	8/6	EY51	1/-	PCCR9	13/6	U31	7/6	UL54	7/6
1R5	5/6	8B17	5/6	8L7	6/6	7B7	10/6	19A6G	7/6	78	8/6	DK92	7/6	ECH81	8/6	Small	8/6	PCFR0	7/-	U35	11/-	UL10	9/6
1R4	6/-	8B26	4/6	8L8	8/6	7B7	9/6	19B6G	15/-	80	5/6	DK96	7/6	ECH80	7/-	EY88	8/6	PCFR2	7/3	U37	28/-	UL10	9/6
1R5	4/6	8C4	3/6	8L9	12/6	7V7	7/6	20D1	8/6	83	8/6	DL3	8/6	ECL82	9/6	EZ35	5/6	PCFR4	15/-	U43	8/6	UL16	12/6
1T4	3/6	8C3	5/6	8LD3	8/6	7Y4	7/-	20F2	5/6	80AV	9/-	DL35	9/6	ECL83	12/-	EZ40	6/6	PCLR2	7/3	U50	6/6	UL17	9/6
2D1	4/6	8C4	4/6	8LD12	7/6	7Z4	7/6	20L1	16/-	117Z6GT	DLR2	9/-	EFP2	7/-	EY41	7/-	PCLR3	10/6	U52	4/6	UL18	17/-	
2A4	4/6	8C9	8/6	8LD20	8/6	8D3	3/-	30P1	9/6	10/6	DL91	8/6	EFP3	3/6	EZ60	6/6	PCLR4	7/6	U76	5/6	UL19	11/-	
2A5	0/-	8C16G	21/-	8N7	16/6	10C1	11/-	20P3	12/6	183BT	18/-	DL92	6/6	EFP3	4/6	EZ81	6/6	PEN25	4/6	U78	5/-	UL21	11/-
3D4	4/6	8C16	8/6	8N7	12/6	16C2	13/6	30P4	3/6	187(A)	5/6	DL94	6/6	EFP4	13/6	EY40	13/6	PEN45	7/3	U81	11/-	UL24	11/-
3Q1	7/-	8D1	9/6	8P15	7/-	10C14	8/6	30P2	15/-	807(L)	3/6	EL96	2/6	EY41	12/6	EY42	8/6	PEN46	8/6	U81	11/-	UL24	11/-
3Q2	8/6	8D2	3/6	8P25	2/6	10C14	5/6	25AG	6/6	908	15/-	EABCR0	7/6	EY42	7/6	EL96	2/6	PEN46	8/6	U82	15/-	VR10/30	3/6
3R4	6/6	8D3	12/6	8P28	12/6	10L14	7/6	25L6G	9/6	913	5/6	EAC91	4/6	EY43	8/6	EL96	2/6	PCLR0	16/6	U38	7/6	UL30/50	8/6
3V4	9/6	8D6	4/6	8Q7G	6/3	10LD3	7/6	25L6GT	9/-	954	2/-	EAF42	8/6	HVR2	7/6	PL38	16/6	U39	7/6	U39	7/6	UL30/50	8/6
5R4G	9/6	8E1	4/6	8Q7GT	8/6	10LD11	14/6	33Y9G	9/6	955	3/6	EAF44	1/6	EY50-USA	KL55	7/6	PL81	8/6	U42	11/-	UL42	8/6	
5F4G	4/6	8F8G	6/3	8K7	9/6	10LD12	8/6	327AG	7/6	956	2/6	EBC11	7/-	EY50	8/6	PL82	8/6	U43	9/6	U43	9/6	UL44	11/-
5R5GT	5/6	8F10	7/-	8E7G	7/6	10P13	5/6	25Z2	8/-	5763	10/6	EBC1	3/6	EY54	3/6	KT3C	6/6	PL83	6/6	U44	6/6	UL46	11/-
5Y3G	5/6	8F12	3/6	8S7A	5/6	10P14	9/6	25Z6G	9/-	9001	4/-	EBC3	9/6	EY50	4/6	KT38	9/6	PL44	9/6	U40	17/-	UL47	5/6
5Y3GT	6/-	8F13	6/6	8S7G	4/6	10P18	7/6	25Z6GT	12/-	9002	4/6	EBC3	4/6	EY54	6/6	KT44	7/6	PM54	11/-	U45	11/-	UL48	11/-
5Y4G	11/-	8F14	9/6	8H7	4/6	12A6	5/6	27U	11/6	9003	4/6	EBC4	8/6	EY56	8/6	KT45	8/6	PX25	11/6	U46	11/-	UL49	11/-
5Z1	11/-	8F16	8/6	8I7	4/6	12A7	6/6	30C1	7/-	ATP4	2/6	EBC5	9/6	EY59	8/6	KT52	8/6	PY31	7/6	U47	11/-	UL50	11/-
5Z2	11/-	8F18	8/6	8K7	5/6	12A8H	8/6	30P5	6/6	AZ31	9/6	EBC6	7/6	EY91	3/6	KT63	6/3	PY32	10/-	U48	11/-	UL51	11/-
5Z4G	5/6	8F18	8/6	8K7GT	6/6	12A7S	7/6	30FL	9/6	836	8/6	EBC9	8/6	EY92	4/6	KT66	12/6	PY40	7/6	U49	11/-	UL52	11/-
5Z4GT	11/-	8F33	6/6	8A17GT	6/6	12A7S	7/6	30L1	5/6	1011	7/-	EBC8	4/6	EY95	6/6	KT76	8/6	PY81	8/6	U50	11/-	UL53	11/-
6A7	10/-	8H8	2/-	8N7GT	4/6	12A7	7/6	30P4	12/6	CBL1	26/6	EBC11	21/-	EY92	3/6	KT79	14/-	PY82	7/6	U51	11/-	UL54	11/-
6A8G	9/6	8J3	4/3	8Q7	6/6	12A7	6/6	30P12	8/6	CBL21	21/-	EBC2	3/6	EL22	12/6	KT81	14/-	PY83	7/6	U52	11/-	UL55	11/-
6A8GT	12/6	8J5G	9/6	8S7	4/6	12A7	6/6	30P16	6/6	CCH35	4/6	EBC9	3/6	EL32	4/6	KT82	5/6	PY90	8/6	U53	11/-	UL56	11/-
6A8G	7/-	8J5GT	3/6	8I4GT	10/6	12BA6	8/6	30P11	10/6	CL33	11/6	EBC9	3/6	EL33	8/-	KT83	5/6	PY90	8/6	U54	11/-	UL57	11/-
6A9G	2/6	8J7	7/6	8V6G	5/6	12B17	10/6	35L6GT	9/-	CY31	9/6	ECC1	9/6	EL35	7/-	KT263	5/6	R19	11/-	U55	11/-	UL58	11/-
6A9GT	7/6	8J7G	5/6	8V6GT	8/6	12C8	8/6	35W4	8/6	D63	13/6	ECC2	4/6	EL37	11/6	KT264	5/6	R19	11/-	U56	11/-	UL59	11/-
6A15	3/6	8J8	7/6	8X2	8/6	12E1	16/6	35ZAGT	5/6	D77	3/6	ECC3	4/6	EL38	12/6	LN152	7/-	SP8	3/6	U57	11/-	UL60	11/-
6A15G	6/6	8J8GT	9/6	8X4	8/6	12E1GT	3/6	35Z5GT	7/6	D192	5/6	ECC4	9/6	EL41	8/-	LZ19	7/-	SP41	2/6	U58	11/-	UL61	11/-
6A16	3/6	8K6G	5/6	8X5G	5/6	12A7GT	9/3	42	7/6	DA30	18/6	ECC35	6/-	EL42	9/-	M214	8/-	SP61	2/6	U59	11/-	UL62	11/-

Post: 2 lbs. 1/6, 4 lbs. 2/-, 7 lbs. 2/9, 15 lbs. 3/6, etc. No O.C.D. ALL ITEMS 5% & POST FREE IN DOZENS.

# TECHNICAL TRADING CO.

(Callers always welcome). LIST OF 1000 SNIPS 6d. P.O. BOX 21 (W) 350-352 FRATTON ROAD, PORTSMOUTH.

## "BRILLION" TV TUBES

12/14in. Tube ... ..	£4. 5.0
17in. Tube ... ..	£5. 0.0
21in. Tube ... ..	£6. 0.0
Shell allowance on 17 and 21in.	10.0

**C.W.O. OR C.O.D.  
CARR. & INS. 10/-.**

### GUARANTEE

Except for the glass shell all materials used in the manufacture of "BRILLION" Tubes are new and we confidently give 12 Months guarantee with every Tube.

## ASHLEY T.V.

**39 LOWER ASHLEY ROAD  
BRISTOL, 2.**

Tel: 56383


### TAPE RECORDER AMPLIFIER £7.19.6



Compact, well designed 5 valve amplifier. Output 3.5 watts. Input for Microphone, Radio and Gram. Rise, 8 1/2 x 3 x 4 1/2 in. Ins., carr. 4/6. 12 months' guarantee. Terms available. Extras: Dial plate including sockets and superimpose switch, 2/6. Knobs, 2/6.
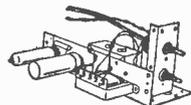
### RECORD PLAYER AMPLIFIERS

12 months' guarantee  
MK. D.2. 79/6. Latest design incorporating negative feedback, giving 4 watts undistorted output. Valves: ECL82 and metal rectifier. Tone and volume control panel on flying leads. P. & P. 3/6.



MK. D3. 89/6. As above de luxe model, with separate tone controls for treble and base boost. P. & P. 3/6.  
MK. D5. 89/6. New circuit employing ECL80 triode pentode output valve giving 3 watts output. A.C. only. Mains isolated. Single control for volume and on/off switch with knob. P. & P. 3/6.

### 14in. TUBES 35/-

(36/24)  
SALVAGE PURCHASE OF GUARANTEED REPLACEMENT TUBES. Carr. 3/-.

### TV VALVES

SALVAGE GUARANTEED

2/9 each 30/- dos.  
6P1, 6P13, 6K25, 6SN7, 10F1, 10P14, 6F80, 6Y61, PL18, U801, U8.

### I.T.A. AERIALS

For all I.T.A. channels. For outdoor or loft. 3 elements. Famous manufacturer. Sold at half the normal price. P. & P. 2/6.



CO-AX CABLE. Only 6d. per yd. Cut to any length. Good quality at a very low price. Allow 1/6 post on 20 yds. 45/- per 100 yds. P. & P. 3/6.

5/9 each 60/- dos.  
6V8, 12AU7, 20P2, 20L1, 20P1, 6BF80, ECC81, ECC82, 6CF80, ECL80, EL38, PCF80, PC884, PL38, PL81, PL82, PL88, PY81, PZ80.

250 other types on list.

Post on 1 valve—7d. Post on 6—1/6. Post on 12—2/6.

### DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12  
Phone: ILFord 6001/3

LATEST FREE LIST

**FREE** THIS BOOK WILL INTEREST YOU!  
LEARNING the PRACTICAL WAY  
**Radiostructor** EQUIPMENT COURSES

FOR .. Your Career  
.. Your Own Business  
.. An Absorbing Hobby

## A NEW-PRACTICAL WAY of UNDERSTANDING Radio · Television Electronics

Including: Transistors; VHF/FM; Hi-Fi equipment; Computers; Servo-mechs; Test instruments; Photo-electrics; Nuclonics, etc.

Radiostructor—an organisation specialising in electronic training systems—offers a new self-instructional method using specially designed equipment on a "do-it-yourself" basis. You learn by building actual equipment with the big kits of components which we send you.

You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact, you really have fun whilst learning! Fill in the coupon below, for full particulars.

### POST NOW

TO RADIOSTRUCTOR (DEPT. G.40)  
READING, BERKS.

Please send brochure, without obligation to:

★Name ..... }  
Address ..... } **BLOCK CAPS PLEASE**  
(We do not employ representatives) 5/61

# RADIOSTRUCTOR


LEADS THE WORLD IN ELECTRONICS TRAINING

# Trade News

## NEW PROSPECTS AND DEVELOPMENTS
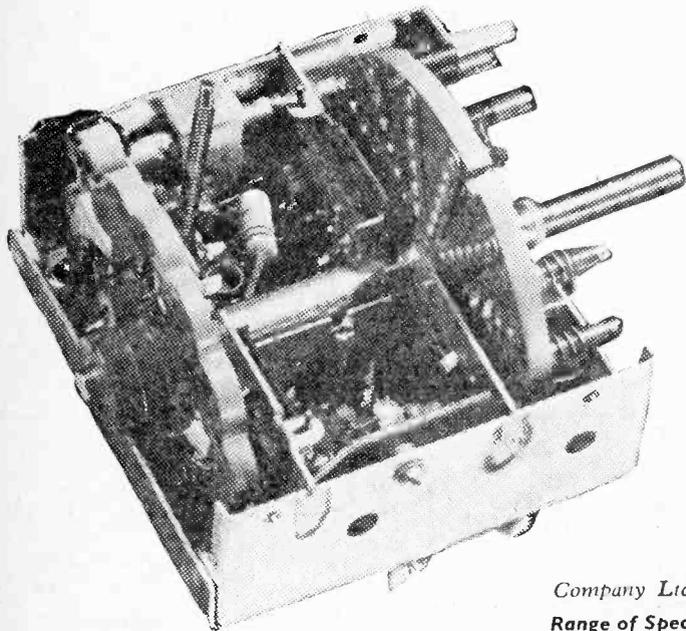
### Silicone Compound

A SILICONE compound named MS4 is manufactured by Midland Silicones Ltd., and is non-melting and retains a grease-like consistency from  $(-50)^{\circ}\text{C}$  to  $200^{\circ}\text{C}$ , and has excellent dielectric



MS4 is widely used for lubricating switch contacts and moving parts such as are employed in this multi-channel tuner. It is also used to prevent arcing and corrosion around the anode terminals of cathode ray tube EHT connections.

characteristics, is highly water-repellent and resists oxidation. Some of its uses are, a dielectrical potting material for transistors and other electronic equipment; a lubricant on electrical contacts, meter bearings and other mechanisms; a seal for electric heating elements, aerial connectors, plugs and sockets against the ingress of moisture; and to prevent corrosion on battery terminals, leads, spark plugs and almost any equipment liable to rust or corrode.

MS4 is in common use today by the world's major airlines, by Post Office authorities in Britain and abroad, and the fighting services, by leading motor companies in several countries, by all the principal electrical and electronic manufacturers and by many other companies in every industry.

MS4 is produced by Midland Silicones Ltd., 68 Knightsbridge, London, S.W.1.

### Closed-circuit Television Camera

THE "NEVEYE" closed-circuit television camera has been designed and developed by the Nottingham Electronic Valve Company Ltd.

This camera uses modern circuit design, transistors and semi-conductors. It has been designed to work into any standard domestic television receiver from ordinary mains supply and is so simple that it can be operated by the least technically minded.

The output from the camera is a composite modulated radio frequency signal, and is tunable to any channel in Band I. Synchronising impulses and blanketing impulses are derived within the camera and are mixed with the vision signal to form a composite waveform which will lock any standard receiver working on the British 405 line system, or alternatively on the Continental 625 line system. The radio frequency output is approximately  $10,000\text{V}$  into  $75\Omega$  for peak white modulation.


The camera tube is of the photo-conductive type and can be supplied with infra red or ultra violet sensitive targets at extra cost.

The camera is made by the Nottingham Electronic Valve Company Ltd., East Bridgford, Nottingham.
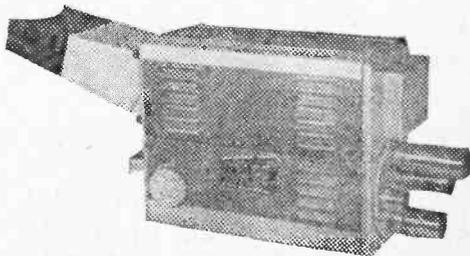
### Range of Specialised Television Equipment

A WIDE range of closed-circuit television equipment is now being marketed by Rank Precision Industries Ltd., whose TV consultancy service has been expanded to meet the growing demand of industry, education and medicine.

Flexibility and simplicity in their design of individual installations are now increased by the




A high resolution studio broadcast TV camera, manufactured by Dage of America and distributed by Rank Precision Industries Limited. This camera has an electronic viewfinder.

availability of ten different types of television cameras ranging from a miniature nuclear camera to a high resolution industrial image-orthicon model.

From January 1961, the company has had exclusive selling rights in the United Kingdom and many overseas territories for the Dage range manufactured by Thompson Ramo Wooldridge.

The model 320B/V, for example, is a studio broadcast Vidicon camera with 700 line horizontal resolution. The 4-lens turret or zoom lens are rear controlled. The 5in. electronic viewfinder is removable, enabling it to be used as a film camera, when fitted with dust cover-blower assembly. It has built-in indicator lights and intercom facilities and is fitted with an overscan protection switch. The 320B/V is manufactured by Thompson Ramo Wooldridge, Michigan City, Indiana, U.S.A.

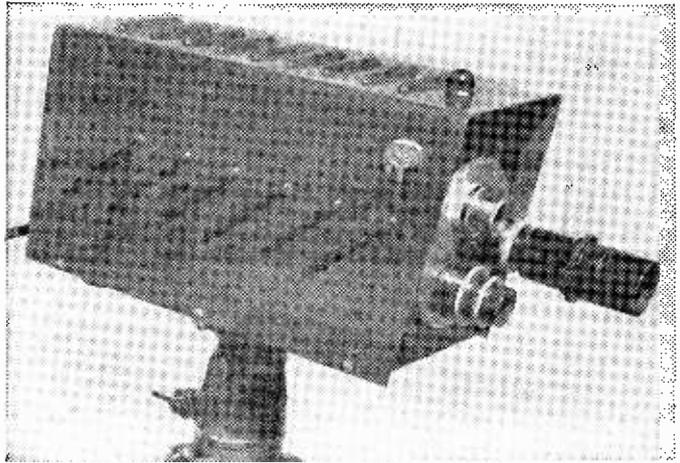


A view of the "Neveye" closed-circuit TV camera fitted with a lens turret for wide angle and telephoto shots.

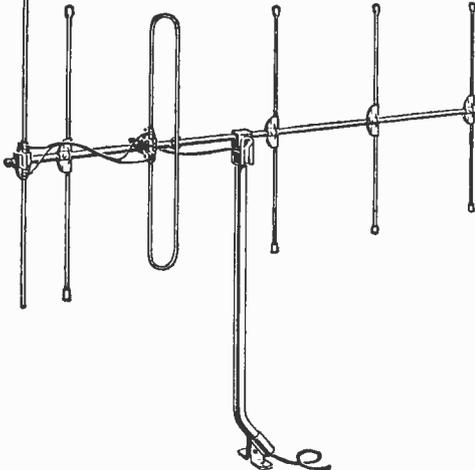**New Aerial and Attenuators**

THE following new products are now available from all Antiference Distributors.

The HL514 loft aerial is available in all vertical Band I/III channel combinations, has a double-driven array incorporating a telescopic single dipole for Band I and five Band III elements. The aerial is complete with angled arm and bracket and is supplied fully assembled with automatic "click-mec" elements in individual envelopes. The price (from 1st April) is 42s. 0d.



The new Antiference TV aerial—type HL514

The Balancer, BA/1 is a "frequency conscious attenuator" and is designed for easy insertion into TV aerial downleads to provide variable attenuation

of Band I signals without affecting Band III, or of Band III signals without affecting Band I; so enabling a balanced signal to be easily obtained in areas where non-cositing of transmitters, different power or reception conditions result in an unequal signal being received. The unit is housed in a streamlined cream plastic cover. The price of the BA/1 is 16s. 0d., complete with lead and plug. Both the BA/1 and the HL514 are made by Antiference Ltd., Bicester Road, Aylesbury, Bucks.

**Colour Television at "Daily Mirror" Opening**


When, on Tuesday, 7th March, Mr. Cecil Harmsworth King, chairman of the "Daily Mirror" Group, carried out the official opening of the impressive new headquarters of the "Daily Mirror" and "Sunday Pictorial" in Holborn, the proceedings were televised in full colour to overflow audiences in the building.

The operation was carried out by the Marconi Company using two colour cameras and 35mm colour telecine equipment. An 8ft x 6ft screen was installed in the staff canteen, and a further twenty 21in. monitors in various parts of the building.

The opening ceremony, which took place in the foyer, was followed by a colour telecine programme which included a film showing the building itself under construction. The programme was recorded on Videotape for subsequent performances in black-and-white.

<b>JOIN THE PRACTICAL GROUP</b>	
<b>PRACTICAL WIRELESS</b> ... .. 1/6	
Every Month.	
<b>PRACTICAL MECHANICS</b> ... .. 1/3	
Every Month.	
<b>PRACTICAL MOTORIST</b> ... .. 1/6	
Every Month.	
<b>PRACTICAL HOUSEHOLDER</b> ... .. 1/3	
Every Month.	

**Now** for less...

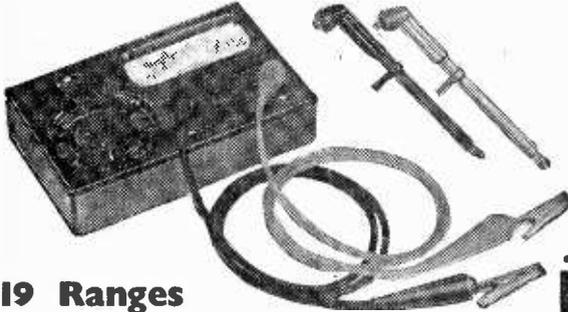

**19 Ranges**

- |                     |                     |
|---------------------|---------------------|
| <b>D.C. Voltage</b> | <b>A.C. Voltage</b> |
| 0—100 mV.           | 0—10 V.             |
| 0—2.5 V.            | 0—25 V.             |
| 0—10 V.             | 0—100 V.            |
| 0—25 V.             | 0—250 V.            |
| 0—100 V.            | 0—1000 V.           |
| 0—250 V.            |                     |
| 0—1000 V.           |                     |
| <b>D.C. Current</b> |                     |
| 0—100µA             |                     |
| 0—1mA               |                     |
| 0—10mA              |                     |
| 0—100mA             |                     |
| 0—1A                |                     |
| <b>Resistance</b>   |                     |
| 0—20,000Ω           |                     |
| 0—2MΩ               |                     |

List Price: **£9:10s.**  
complete with Test Leads and Crocodile Clips.  
Leather case if required 39/-

Size: 5½ x 3½ x 1½ in.  
Weight: 1 lb. approx.

MM12

Designed to offer the widest possible range of accurate and reliable measurements at the lowest possible price, the versatility and usefulness of the Multiminor is now further extended by specially designed leads. These new leads, available at no extra cost, will accept crocodile clips or PRODCLIPS. The Multiminor takes full advantage of the possibilities of printed circuit techniques to achieve outstanding compactness and economy of weight. The scale is clear and open. The fine red coloured pointer and effectively damped movement facilitate easy and rapid reading.

For use in Radio, TV, Electronics, Motor Vehicles, domestic appliances, workshop equipment, you'll find the Multiminor a great little meter.

**Use PRODCLIPS with the MULTIMINOR (Pat. No. 748811)**

These cleverly designed spring-loaded insulated prods are the complete answer to a long-standing problem. Press the trigger to open, release to grip. Keep your hands free no matter how difficult of access your test points may be. 15/- per pair.

...with the

**MULTIMINOR**

**R.E.C.M.F. EXHIBITION**

May 30 - June 2 Stand No. 225

Write now for illustrated literature to:—

**AVO LTD**  
AVOCET HOUSE - 92-96 Vauxhall Bridge Road  
LONDON - S.W.1 VICTORIA 3404 (12 lines)  
A Member of the Metal Industries Group of Companies

VACUUM ELECTRONIC LIMITED

**KEEPS YOU IN THE PICTURE**

WITH THE FINEST REBUILT CATHODE RAY TUBES

12 MONTHS GUARANTEE

12" - 14" £4-15-0

15" - 17" £5-5-0

21" £7-15-0

CASH WITH ORDER OR PRD FORM A, ADD 12/6 FOR CARRIAGE AND INSURANCE.

DELIVERY FREE IN LONDON AREA

**15/-**

ALLOWED ON RECEIPT OF OLD TUBE

VACUUM ELECTRONIC LTD.

WRITE PHONE OR CALL  
35, SACKVILLE STREET  
LONDON, W.1  
REGENT 6404

**New and Rebuilt**



18 Months' Guarantee on all Tubes

**Television Tubes**

10/- gladly refunded on old 17 and 21in. tubes.

NEW		REBUILT	
17in. _____	£7 9 6	12in. _____	£5 7 6
21in. _____	£9 9 6	14/16in. _____	£5 10 0
		17in. _____	£6 19 6
		21in. _____	£8 19 6

C.W.O. or C.O.D. carr. and Ins. 10/-.

**TELEVIEWER SUPPLIES**

95 Coldmore Road, Walsall, Staffs.

# VALVES SAME DAY SERVICE

**NEW! TESTED! GUARANTEED!**

SETS	IR5, IS5, IT4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 ..	any 4 for 19/6
	DAF96, DF96, DK96, DL96	4 for 27/6
	6K7G, 6K8G, 6Q7G, 6V6G, 6X5G, or 5Y3G .. .. .	5 for 24/6

1A7GT 11/6	6LD20 8/-	25Z6GT 9/6	EC92 11/-	EZ40 6/9	PY83 7/9
1D5 8/-	6PF 13/6	30L15 11/-	ECC40 17/6	EZ41 7/-	PZ90 17/-
1HG7 10/6	6E25 8/-	35A5 9/6	ECC31 5/-	EZ80 6/3	EZ80 8/6
1NSGT 10/-	6Q7G 8/-	35L6GT 9/-	ECC32 9/3	EZ81 7/-	U22 7/3
1R5 5/6	6Q7GT 9/6	35Z4GT 6/9	ECC83 7/-	FW4/500 8/-	U25 13/-
1S4 8/-	6SL7GT 6/3	35Z5GT 8/6	ECC84 8/9	GZ30 8/6	U26 10/-
1S5 5/3	6SN7GT 4/9	50L6GT 8/9	ECC85 8/3	GZ32 9/6	U50 6/6
1T4 3/6	6U4GT 11/-	AC/TH1 16/9	ECC80 8/6	HBC90 7/-	U52 4/6
1U5 5/9	6V6G 7/6	AZ91 3/6	ECC82 8/8	KT33C 7/-	U73 4/9
3A5 9/-	6V6GT 6/6	B36 8/9	ECH21 13/6	KT41 11/6	UABC80 2/9
3Q4 7/-	6X4 4/9	CL33 12/3	ECH35 6/3	KT44 6/6	UAF42 9/9
3S4 6/-	6X5GT 5/-	DAC32 10/-	ECH42 8/9	KT61 10/-	UBC41 7/9
3V4 7/-	7B6 5/9	DAF91 5/3	ECH81 9/-	KT63 6/6	UBF80 8/9
5U4G 4/6	7B7 7/6	DAF93 7/6	ECL80 7/6	MU14 7/6	UBF89 8/-
5V4G 8/-	7C5 7/6	DDC90 9/-	ECL82 9/6	MX40 9/6	UC82 12/6
5Y3GT 6/-	7C6 7/6	DF33 10/-	EF39 4/6	N18 7/-	UCC84 12/9
5Z4G 7/9	7H7 7/6	DF91 3/6	EF40 12/6	N37 10/6	UCC85 7/6
6AL5 3/9	7S7 7/-	DF96 7/6	EF41 8/3	PC35 10/-	UCF80 14/-
6AM5 6/6	7Y4 7/6	DH76 4/9	EF42 9/3	PC38 7/6	UCH21 15/6
6AQ5 6/-	10C1 11/6	DH77 6/9	EF80 5/6	PCC89 11/-	UCH42 8/-
6AT6 6/9	10C2 17/6	DK32 11/6	EF85 5/6	PCF80 7/9	UCH81 8/-
6BA6 6/-	10P13 14/6	DK91 5/6	EF86 9/9	PCF82 8/-	UCL32 10/9
6B26 5/9	12AT6 5/3	DK92 7/6	EF89 7/-	PCF88 14/-	UCL83 13/3
6BH6 5/9	12AT7 5/-	DK96 7/6	EF91 3/6	PCL22 7/6	UF41 8/9
6BU6 5/9	12AU6 8/6	DL33 9/-	EF92 4/3	PCL83 11/6	UF85 8/6
6BW6 8/-	12AU7 6/3	DL35 9/6	EF183 14/-	PCL84 7/6	UF89 7/6
6C9 9/-	12AX7 7/-	DL92 8/-	EL33 10/-	PEN4 11/-	UL41 8/-
6OD6G 2/9	12K7GT 5/3	DL94 7/-	EL41 8/6	PEN36C 8/-	UL84 7/6
6P1 12/6	12K8GT 11/6	DL96 7/6	EL42 9/-	UR16 9/-	UY16 8/6
6PF6 6/6	13Q7GT 4/9	EAB80 7/-	EL94 7/-	PL81 8/6	UY21 11/3
6F13 11/-	12Z3 7/6	EAF42 8/6	EM34 6/9	PL82 7/-	UY41 6/6
6F14 16/6	14S7 18/6	EB91 3/9	EM80 8/6	PL83 7/6	UY85 9/6
6K3G 2/6	20P2 17/6	EB33 5/6	EM91 8/6	PT84 10/-	VP43 9/6
6K7GT 5/-	20L1 17/6	EC41 8/6	EM84 10/-	PY32 11/-	VP41 8/-
6K8G 6/3	25A6G 8/-	EBP80 8/-	EY51 7/6	PY80 7/6	W76 5/3
6K8GT 9/3	25L6GT 7/9	EBP89 8/9	EY84 10/-	PY81 6/9	W77 4/6
6L18 10/3	25Z4G 7/6	EBL21 13/6	EY86 7/9	PY82 6/6	Z77 3/6

# "TELFAC" Regunned TV Tubes

Supplied from stock and despatched per British Railways SAME DAY. COMPLETE NEW GUNS fitted in every tube and fully guaranteed for TWELVE MONTHS.

	Mullard	Mazda
12 in. ...	£4. 0. 0	£4.10. 0
14 in. MW ...	£4.10. 0	£5. 0. 0
14 in. AV ...	£5. 0. 0	£5. 0. 0
15 in. 2 Volt ...	£5.10. 0	£5.10. 0
15 in. 12 Volt ...	£5. 0. 0	£5. 0. 0
16 in. ...	£5.10. 0	£5.10. 0
17 in. MW ...	£5. 0. 0	£5. 0. 0
17 in. AV ...	£5.10. 0	£5.10. 0
21 in. MW ...	£6.10. 0	£6.10. 0
21 in. AV ...	£7. 0. 0	£7. 0. 0

MW=Magnetic Focus  
 AW=Electrostatic Focus  
 Plus 10/- for Carr. & Ins.

Other types not listed available. Please contact:—

**J. P. WRIGHT**  
 Television Factors  
 103 Carr House Road, Doncaster  
 Sole Distribution Agency  
 'Phone: DON 2636

## READERS RADIO

24 COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA. 4587

# FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

**Have you sent for your copy?**  
 ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

**We definitely Guarantee "NO PASS — NO FEE"**  
 Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Incorporating E.M.I. Institutes)  
 (Dept. SE/20), 29 Wright's Lane, London, W.8

**THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD**

### WHICH IS YOUR PET SUBJECT ?

- Mechanical Eng..
- Electrical Eng..
- Civil Engineering,
- Radio Engineering,
- Automobile Eng..
- Aeronautical Eng..
- Production Eng..
- Building, Plastics,
- Draughtsmanship,
- Television, etc.

### GET SOME LETTERS AFTER YOUR NAME!

- A. M. I. Mech. E.
- A. M. I. C. E.
- A. M. I. Prod. E.
- A. M. I. M. I.
- A. I. O. B.
- A. F. R. A. S.
- B. Sc.
- A. M. Brit. I. R. E.
- City & Guilds
- Gen. Cert. of Education
- Etc., etc.

### PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

### INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

### B.I.E.T. SCHOOL OF ELECTRONICS

### POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

NAME .....

ADDRESS .....

SUBJECT OR EXAM THAT INTERESTS ME .....





Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDER-TAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 439 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

#### FERGUSON 306T

I would like to install a new tube but I am not sure of how to remove the old one. Also, I think the tuner is faulty for when it is operated thin black lines run across the screen accompanied by crackling noises. This stops a few seconds after tuning.—J. Harkness (Greenock).

The tube is removed as follows: remove the focus dome, the tube base connector and ion trap magnet. Slacken off the deflector coil adjusting screws and after discharging the final anode of the tube to chassis, remove the EHT connector. Unhook the tube earthing spring and withdraw the tensioning screws on the retaining strap. The strap may then be removed and the tube carefully drawn away from the deflector coil assembly.

When replacing the tube, ensure that the deflector coils are as far as possible forward and that the screen end of the tube is correctly positioned in its cradle. The tension spring which contacts the external conductive coating on the tube must be stretched between the hook on the top support and the tag.

Dust or grease on the contact pips of the turret coils may be responsible for the tuner fault. These contacts should be very carefully cleaned and polished with a soft cloth.

#### VIDOR CN 4221

Having replaced the line output transformer, on switching on, the sound comes up, as does the line timebase whistle. They then immediately cut out and at the same time the two H.T. rectifiers (PY82) glow very bright and the two fuses blow. No other components have been touched other than the PL81, PY81, ECL80 and EY51 which I have replaced with no avail.—R. Robinson (Maidstone).

Although we cannot say that this is the cause in your case, we have often found that a lead passing through the chassis near the PL81-PY81 valve bases breaks down and shorts to the chassis. You should check this point.

#### McMICHAEL CR52

The trouble is seemingly situated between the 32 $\mu$ F electrolytic condenser and the 120 $\mu$ F electrolytic. Connecting the positive sides of these condensers is a 1,000 $\Omega$ ,  $\pm$  20per cent tolerance resistor which becomes red hot when the receiver is in use. The picture disappears but the tube functions correctly. Also the sound has vanished. I tested both condensers and found a short in the 120 $\mu$ F, but the 32 $\mu$ F was in order. I also tested valves GZ32 and PL38 and these proved to be in working order. When I disconnect the 1,000 $\Omega$  resistor there is a raster which can be reduced with the brilliance control. Upon connecting a new 120 $\mu$ F condenser the same symptoms occurred. I really think the fault lies somewhere on the EHT side as this 1,000 $\Omega$  resistor only gets hot when the picture is coming on, or as the EY51 lights up along with the EHT whistle associated with the picture.—J. Greenshields (Glasgow E.3).

There are two 1k 6W resistors from the 120 $\mu$ F capacitor. One feeds H.T. to the vision strip, the other to the sound. We are inclined to suspect the latter. If no other components are damaged check the 0.003 $\mu$ F capacitor which decouples the H.T. line at the sound I.F. stage. This is a small capacitor and you will have to trace the H.T. line along from the resistor to locate and disconnect it.

#### PETO SCOTT 1712T

This set has recently been converted to receive ITA using a Brayhead tuner as prescribed. The BBC programmes are good but the ITA at times is covered with a herring-bone pattern (horizontal). I have tried to adjust the oscillator coil but this fails to cure it. Would wiring directly into the chassis and cutting out the adaptor coil be a better solution?—M. Williams (Retford).

Since the pattern interference is not present all the time it may well be a form of external interference picked up by the aerials. If this is the case, it may be alleviated by carefully orientating the Band III aerial for maximum signal pick-up consistent with minimum patterning.

#### PAM 754

I replaced the H.T. rectifier on the above set and the set worked fine for some time, but now on switching on, the top of the picture is cramped about a quarter of the way down. On warming up this gradually recedes to about 1in. down each side. Also on increasing the brilliance with the fine tuner on the right-hand side I lose volume, is this in order?—W. Couper (Port Glasgow).

Your symptoms are still those of low H.T. and you may easily have another faulty rectifier. Other items to check are the PL81 line output valve, and the CRT which may have a first anode leak reducing the boosted H.T. line.

#### PYE VT7

The CRT on my set has lost a great deal of emission. The set is being run on a 250V D.C. supply. Is there any way the tube can be boosted? As I live in a fringe area, will a preamplifier fitted to a standard set make it equivalent to a fringe model? Is there available commercially some form

of booster to fit at the aerial end when the aerial is fitted 100 to 150yd away from the house?—J. Jones (Llandyssul).

You may boost your tube a little by connecting a 5,000 $\Omega$  10W resistor between the voltage selector terminal 5 and the "hot" side of the CRT heater—usually pin 1. We cannot advise you about a head amplifier.

You may like to try fitting a 30L15 frame grid valve in place of your PCC84 R.F. amplifier, and retuning the tuner; or alternatively writing to the manufacturers who have designed a higher gain replacement tuner for this model.

#### EKCO T141B

I would like advice on the following faults of this receiver. The picture is displaced to the left, leaving  $\frac{1}{2}$ in. space on the right, which cannot be filled by the line hold or width control. The picture is also smudgy to the right of the outlines; is this called "flaring"? Also when contrast or brilliance is advanced the raster becomes defocused and even if carefully set to prevent defocusing a few lines on top of the picture begin to tear to the left. If, as I suspect, the tube is failing, is it possible to boost it with any success? If so I would appreciate advice on how to go about it. The tube is a Mazda CRM 121B, which I think is the original.—J. Gibson (Wirral).

Gaps on the right normally denote a low emission 6P28 line output valve. Your other symptoms all point to a faulty tube which may be low emission and heater-cathode. Try fitting a low capacity 2V CRT transformer. Connect the secondary to pins 1 and 8, having removed and isolated each previous connection and connect the mains side of the transformer between the chassis and the copper strip behind the voltage selector.

#### SOBELL T224

When the set is switched on for about an hour both the picture and sound fluctuate. After that it seems to settle down to an almost normal picture.—W. Eaton (Shipbourne).

It would appear that there is a poor contact at one of the V1, 2 or 3 valvebases. If the receiver has not been converted, check the seating of the rear left side ECL80 and centre EF80 and the base connections. If the receiver has a turret tuner check the seating and base contacts of the tuner valve and clean the turret studs etc.

#### BUSH TV24

I have replaced an isolation and booster transformer to feed the CRT owing to the deterioration of the picture. On a 25per cent boost the picture is better but still not really good. On placing it on a 50per cent boost it gives a good quality picture but after a few minutes the picture darkens and is hardly visible. When the set is switched off and on again after a few seconds, it does the same thing again. I would like to point out that on the 25per cent boost the picture remains the same all the time, but as already stated, it is not of really good quality.—A. Glover (Leicester).

Excessive application of boost (50per cent) will result in a complete loss of emission. If you wish to retain the tube (which should really be replaced

since it has given good service) you will have to run it on the original 6.3V or on low boost (25per cent).

#### K.B. LVT30

The set gives constant trouble after an hour of running on both BBC and ITA. The set develops heavy horizontal lines varying in number from four or five and sometimes they cover the whole screen. I have replaced the 6AL5, 12AX7, 12AU7, 6BW6, 6DC6G valves, the common I.F. 8D3, and also 2 and 3 vision 8D3's. The tube is only six months old and has been tested for leakages. All the voltages given on the service sheet have been tested and found to correspond with those of my set.—J. Kenny (Chester-le-Street).

Whilst the lines may denote a poor contact in the frame timebase control (check effect of operating height etc), a faulty H.T. feed resistor could cause a similar effect in the vision I.F. strip.

Remove the 6AM6 valves in turn, V3, V4, V6, to try to locate the defective stage. Probing the valve-base components could well show up the faulty one immediately.

#### ENGLISH ELECTRIC 1550

The picture only fills about three-quarters of the screen, but when I move the focus control the picture fills the screen, but it loses its brightness and goes out of focus. What components should I check or change. When I touch the TV and F.M. switch on the front of the set I lose the picture but the screen remains illuminated.—T. Morgan (Weybridge).

You should replace the large metal rectifier situated on the lower power pack. The type number of this is H45-21-1BFL. You should clean and if necessary adjust the TV/F.M. switch contacts.

#### FERRANTI 24K6

The picture collapsed to a vertical band about one-third of the width and then broke up and finally disappeared. The sound is still present.—H. Wroe (Oldham).

The symptoms denote a collapse of the line timebase operation. Check the line oscillator output PL81 valve, which is the most likely cause of failure and then check the PY81, R105 (1.8k) R106 (500 $\Omega$ ) and R107 (300 $\Omega$ ).

#### G.E.C. B.T. 1252



Can I replace the G.E.C. 7203A CRT with the Mullard MW 36-24, and what circuit modifications and ion trap magnet will be required? Can the same modification be carried out on model B.T. 5643? If so which Mullard tube can be used, this being a G.E.C. 6901A 16in. CRT?—B. Thomas (Chorley).

When using the MW36-24, a new CRT base is required and provision made for the anode volts. This can be obtained from one side of the height control. The ion trap magnet is an 1T9.

With reference to the B.T. 5643, it would be possible to use a Mullard MW41-1. This tube has metal cone envelope and again provision must be made for the first anode volts. The previous answer applies here.

# LAWSON

## DIRECT REPLACEMENT Reprocessed TUBES

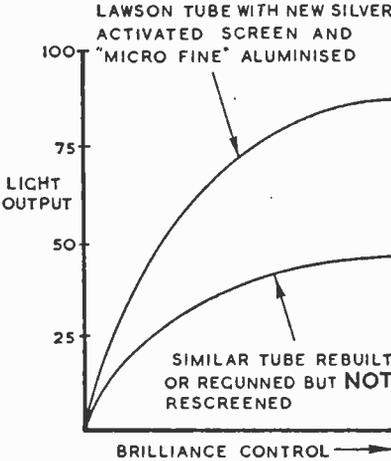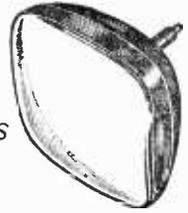

FULLY GUARANTEED 12 MONTHS

IF YOU WANT  
REAL 1961 PERFORMANCE

Then INSIST that your new tube is not just regunned or rebuilt, but is completely REPROCESSED. This means, a tube brand new in every respect (except the glass) and incorporating the very latest screening and aluminising techniques, together, with new direct replacement electron guns by Mullard, Emicope, Mazda etc.

ALL TYPES FROM STOCK

12" - £4.15.0

C.O.D. or C.W.O.

14" - £5.9.0

10'

15-17" - £5.15.0

Gladly refunded if you wish to return your old tube.

CARR. and INS. 7/6

## LAWSON TUBES

156. PICKERSLEIGH RD. MALVERN. Worcs.  
TEL. 3798

### RECORDING TAPE— SPECIAL OFFER

Famous American COLUMBIA (C.R.S.) Premier Quality Tape. Leader and stop coils. Brand New and boxed. Double Play and other sizes in stock.

Standard		Long/Play	
5in. 600ft. . . . .	15/-	900ft. . . . .	19/6
5 1/2in. 900ft. . . . .	16/6	1200ft. . . . .	22/6
7in. 1200ft. . . . .	21/-	1800ft. . . . .	32/6

Plastic Tape Spools  
3in., 2/9; 5in., 3/-; 5 1/2in., 3/3; 7in., 3/6

Reduced Prices	VALVES	All Guaranteed
1T4 0/-	6X4 10/6	6X4 9/6
1R3, 1R5 7/6	6F50 9/-	6X5 12/6
384, 3V4 7/6	6F80 12/6	6L81 12/6
DAF90 9/-	6L84 8/6	6L82 9/6
DF90 C/-	6Y51 9/6	6L83 10/6
DK90 9/-	6Y90 10/-	6Y81 9/6
DL90 9/-	6Z90 7/6	6Y82 7/6
6CL50 10/6	6CC84 9/6	6U2 12/6

### "6 plus 1" TRANSISTOR RADIO KIT — UNBEATABLE VALUE —

Mrs. Current Production Offer—A fortunate bulk purchase enables us to offer one of the season's most outstanding bargains in Portable Transistor Radio Kits. This kit is a modern, sensitive quality circuit Receiver Unit with all the latest features. Six latest Transistors and 1 Diode, Printed Circuit, Med. and Long Waves, Ferrite Aerial, Car Radio In, ut, & Push-Pull output into 3 ohm Speaker, Calibrated Dial and slow Motion Tuning, etc. size: approx. 7 x 2 1/2in.



- Kit, including printed circuit and components **£5. 5.0** p. & p. 2/6
- Set of 6 Transistors and 1 Diode..... **£2. 5.0** p. & p. 6d.
- Complete Kit—Bargain offer—only..... **£6.19.6** p. & p. 2/6

3 ohm Speaker only required—from 17/6.  
Send for leaflet (3d, stamp) and judge for yourself

### RE-GUNNED TV TUBES

PRICES REDUCED AGAIN—12 MONTHS' GUARANTEE!  
New Heater, Cathode and Gun Assembly fitted to all tubes, and now re-screened and aluminised at no extra cost!  
12in., 25; 14in., 25.5.0; 17in., 25.10.0  
EXCHANGE ALLOWANCE on old tube—12in., 5/-; 14-17in., 7/6.  
Carr. and Ins. 10/-  
Comprehensive stocks—Quick Delivery

LIMITED BARGAIN OFFER!



## PORTABLE TRANSISTOR RECORD PLAYER



1 Watt  
4-Transistor Amplifier

High quality unit with negative feedback giving 1 watt Audio output into 3 ohm speaker.

AMP KIT only **£3.19.6** Carr. 2/6.  
Wired and tested, 17/6 extra.

SEND FOR DETAILS NOW

ONLY A FEW ITEMS ARE LISTED FROM OUR COMPREHENSIVE STOCK.  
WRITE NOW FOR FULL BARGAIN LISTS. 3d.

### BARGAIN OFFER

- 6 v. operation (2 E/R Type 800 bats.)
- 1 watt Push-Pull output
- 4 latest G.E.C. Transistors
- 3 ohm 7 x 4in. Quality Speaker
- GARRARD Fidelity Gram. Unit

### COMPLETE RECORD PLAYER KIT

(3 Units) only **£7.19.6** Carr. 3/6.  
Circuit diagram, full technical spec. and constructional details (free with kit), 2/6, post free.  
Size: 11 x 9 x 3in.  
Colour: Two-tone Red/White with Polka Dot relief. Alternative Blue/Fawn with Polka Dot relief.

- \* CABINET incl. Motor Board and 7 x 4 in. Speaker, 39/6. Carr. 2/6.
- \* GARRARD BA 1 Gram. unit, 59/6. Carr. 2/6.



## RADIO COMPONENT SPECIALISTS

70 Brigstock Road, Thornton Heath, Surrey

Phone: THO 2188. Hours 9 a.m.—6 p.m. 1 p.m. Wed.  
Open all day Saturday. By Thornton Heath Station.

Terms. C.W.O. or C.O.D. post and packing up to 1/2lb. 7d. 1/6.  
1 1/2lb. 3/6. 1 1/6.  
5lb. 2/-; 10lb. 2/9; 15lb. 3/6.

# BRAND NEW TUBES

12 months' guarantee

TOP CLASS MAKE

GARR. & INSURANCE PAID

- 12" MW 31-74 etc. £5.50
- 14" MW 36-24 etc. £6.60 (in short supply)
- 17" CRM 171, 172 £7.00

Completely REPROCESSED

to makers' specifications!

Rebuilt, Rescreened, Realuminised

- 14" ... .. £5.50
- 15"-17" ... .. £5.10.0
- 21" ... .. £8.0.0

Carriage FREE

These are tubes of the HIGHEST QUALITY

That "difficult" tube? Let us quote.

TRADE ENQUIRIES INVITED

# LINE OUTPUT TRANSFORMERS

Direct Replacements for 500 sets.

- Haird, T29, T183 .. .. 53/-
- T164, T167, T172, 2014, 1712 .. .. 60/-
- Bush, TV 11A, B; 12A, B; TVF 12A, TUG12A, B; TRG 12A, B .. .. 45/-
- TV12AM; TV22, 24; TRG24, TUG 24 .. .. 60/-
- Cossor: 330, 331, 333, 934, 948, etc. .. .. 58/-
- Ekeco: TS148; TS113-114; T161, 164; T221, 231; TSC311, etc. .. .. 47/6
- Ferguson: 841, 2, 3; 941 to 945 .. .. 55/-
- 9907-9987; 103-1437; 203-2467 .. .. 66/6
- Ferranti: 1473, 1474, 17K3, 17T3 .. .. 45/-
- 1472, T1205, T1215, T1225, T1325, T1405, T1415, T1425, T1505, T1825 .. .. 65/-
- G.E.C. and H.M.V. mostly 55/- to .. .. 60/-
- Invidia: T101-104; T108-110 .. .. 52/-
- T114-126; T133-142 .. .. 60/-
- Murphy: V114C, V116C, V118C .. .. 45/-
- V120C, V180, V178, V200, V202C .. .. 57/6
- Philips: 114 UF/UM, 1115 U, 1437 U, 1446 U, 1726 U, 1746 U, 1747 U .. .. 65/-
- 383A, 463A, 563, 683 .. .. 60/-
- Pvc: LV30, 16T, CS17, VT17 .. .. 52/8
- CTM4, V4, VT4; V7, VT7; .. .. 85/-
- Ultra: 815,917 (with rect. etc.) .. .. 85/-

Add Post 2/6.

**SPECIAL! NEW L.O.T. COMPLETE**  
with: — Linearity and width controls. — EY86 base and top cap. — Valve connectors. — F.H.T. leads. — Circuit diagram. Beautifully made. **ONLY £1** Post 2/6.

### IS IT THE L.O.T.?

Be SURE with the SKANTEST. The most complete, low priced line output and time base component shorting turn tester. Will indicate even one shorting turn. £7.10.0. Carriage 5/-.

# VALVES! UNUSED. GUARANTEED.

ECC81	5/-	6CH6	8/-
ECC82	6/-	6F1	12/6
ECC83	6/-	6F14	15/-
EB91	3/6	6C7GT	8/6
EF91	3/-	7C6	7/-
OZ4	5/-	7H7	8/6
85A2	12/6	12E1	12/6

Post 6d. per valve. Insur. 6d. extra.

**MAINS TRANSFORMERS—SPECIAL!**  
Semi-shrouded, drop-through. Ex new equipment. By well-known manufacturer. 350-0-350 v. at 80 mA, 6.3 v. at 8 amp, 5 v. at 2 amp. ONLY 13/6 ea., plus 2/6 P. & P.

**POCKET VOLT TEST METER.** Two D.C. ranges, 0-25 v. 0-250 v. with test prods and leather case. 12/6 ea., P. & P. 1/6.

**LIGHTWEIGHT MINIATURE CRYSTAL EARPIECE** for transistor sets. Complete with transparent ear insert, 3 feet very fine cord, sub-miniature plug and socket. 12/6 ea., Post 1/-.

**RECORD PLAYERS**  
Famous B.S.R. UA8 Autochanger, 4 speeds, plus manual play; intermixes 7, 10 and 12in. discs. With Full-Fi crystal turnover head. £6.15.0. Carriage 5/-.

**TAPE RECORDER DECK**  
The Collaro "Studio" Transcriptor. Latest 1960 model. 3 speeds—3 separate motors, digital counter, press button switching, provision for extra stereo head. Brand new—guaranteed. With spare 7in. spool. £12.10.0. Carr. 5/- (Dist. price £16.16.0).

S.A.E. with enquiries please.

**5 Westward Way**  
Preston Road, Harrow, Middx.  
Tel: WOR 2663

# WESTWAY RADIO

## 1961 EDITION RADIO AMATEUR'S HANDBOOK

32/6 by The A.R.R.L. Post 2/-

**TELEVISION SERVING HANDBOOK** by G. J. King. 30/- Postage 1/-.

**TELEVISION EXPLAINED** by W. E. Miller, Revsd. by E. A. W. Spreading, 12/6. Postage 1/-.

**INTRODUCTION TO HI-FI**, by C. Brown, 21/-, Postage 1/-.

**HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER**, by P. J. Guy, 8/6, Postage 6d.

**TELEVISION ENGINEERS' POCKET BOOK**, by J. P. Hawker, 12/6. Postage 6d.

**PIN POINT TV TROUBLES IN 10 MINUTES**, Coyne Pub: 31/6. Postage 1/-.

**TELEVISION SERVICING**, Vol. 4, by G. N. Patchett, 7/6. Postage 6d.

**COMPLETE CATALOGUE**, 1/-.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-21 PRAED STREET  
LONDON, W.2

Phone: PADdington 4185

Open 6 days 9-6 p.m.

## NEW VALVES!

Guaranteed Set Tested  
24 HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET of 4, 18/6.

DAF96, DF96, DK96, DL96, SET of 4, 26/-.

1D5	7/-	DL92	5/11	PCF80	7/8
1R5	5/-	DL94	6/9	PCF82	7/8
1S5	4/6	DL96	6/9	PCL82	7/8
1T4	3/3	EB91	3/-	PCL83	11/-
3S4	5/11	EBC41	7/6	PCL84	7/6
3V4	4/9	EBF80	7/9	PL36	10/9
5Z94G	6/8	EBL21	12/6	PL81	9/-
5Y3GT	5/6	ECC40	17/-	PL82	7/-
5Z4G	7/3	ECC81	4/9	PL83	7/-
6AM6	2/9	ECC82	5/9	PL84	9/6
6K7G	1/9	ECC83	6/3	PY32	10/3
6K8G	4/9	ECC84	8/-	PY80	7/-
6A7C	5/6	ECC85	7/9	PY81	6/6
6V6G	4/9	ECP80	8/3	PY82	6/3
6V6GT	6/6	ECP82	8/3	PY83	7/3
6X5GT	4/9	ECH21	12/6	U25	12/-
12K7GT	4/9	ECH42	7/9	UAB80	7/6
12K8GT	11/-	ECL80	7/3	UAF42	8/6
12Q7GT	4/6	EF40	12/3	UBC83	6/6
35L8GT	8/6	EF41	7/6	UBF80	8/6
35Z4GT	5/9	EF80	4/9	UCC35	7/-
AZ31	8/9	EF85	5/-	UCH21	12/6
CI32	1/8	EF86	9/6	UCH42	7/6
DAC32	1/8	EF89	6/6	UCH81	9/-
DAF91	4/6	EF91	2/9	UCL82	10/-
DAF96	6/9	EL41	7/-	UCL83	13/-
DF33	9/8	EL84	6/3	UF41	7/9
DH31	3/3	EY51	7/3	UF83	8/-
DF96	6/9	EY86	7/9	UF89	6/6
DH77	6/-	EZ40	6/-	UL41	6/6
DK32	11/-	EZ41	6/9	UL84	7/-
DK91	5/-	EZ80	5/9	UY21	11/-
DK96	7/3	EZ81	6/6	UY81	5/9
DLK36	6/9	MU14	7/-	UX85	6/3
DL91	8/6	PCC84	7/3	VP4B	8/6
DL35	9/6	PCC89	10/-	Z77	2/9

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra

Office address, no callers.

**GERALD BERNARD**  
(Note new address—formerly of Leeds)  
25 NEWBURY ROAD,  
HIGHAMS PARK, LONDON, E.4.

## FIRST-CLASS TELEVISION and RADIO COURSES GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how.

### FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as **A.M. Brit. I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ. London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches)** etc., together with particulars of our remarkable Guarantee of

### SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career

FOUNDED 1885—OVER  
150,000 SUCCESSES

**NATIONAL INSTITUTE OF  
ENGINEERING**  
(Dept. 62), 148 HOLBORN  
LONDON, E.C.1

S. Africa: P.O. Box 8417, Jo'burg.  
Australia: P.O. Box 4570, Melbourne.

**K.B. MV60**

The picture suddenly collapsed and left a thin horizontal line. The picture seems to be there and the sound is working correctly. I also have a Bush TV32, which gives a good picture, but the bottom is compressed and leaves a gap at the bottom of the screen.—C. Simpson (Hounslow).

Check the frame timebase valves on the MV60 model, 12AU7 and 6BW6. If these are in order (under tube) check continuity of frame oscillator and output transformers, height control etc. On the TV32, check the right side ECL80 valve and  $8\mu\text{F}$  electrolytic which decouples pin 8.

**DECCA DMC17**

When the above set was switched on, the picture was normal for a few minutes then broke down into wide zig-zag lines, then disappeared altogether. I discovered that the video amplifying valve (EF80) was glowing bright blue, so I substituted a spare valve, but still without results. The sound is still there.—A. Ward (London, S.E.19).

First ensure that the line timebase whistle is normal and that EHT is present at the CRT anode, EY51 etc. Then check the video amplifier circuit; anode load  $68\text{k}\Omega$  pin 7, grid  $3.9\text{k}\Omega$ - $2.2\text{k}\Omega$  pin 2 and cathode  $15\Omega$ - $200\Omega$ , pins 1 and 3.

**PHILCO TI412**

There are three dark lines on the left of the picture and it is slightly darker on the right side, also it is critical on the vertical hold.—F. Hood (Seaham).

There are two  $0.001\mu\text{F}$  capacitors associated with the scanning coils and one associated with pin 2 of the tube base to chassis. Replace the latter  $0.001\mu\text{F}$  first, and if the symptoms persist, check the other two. Regarding the poor frame hold, check the ECL80 immediately to the front of the PY82 valve on the left of the tube and the resistors associated with pin 8 of this valve base.

**SOBELL TS14**

The picture on this set has been fading over the past few weeks and now with the brilliance control fully advanced and no signal the raster is not visible. The tube appears to be in order as interference spots show up quite white. The EHT also appears to be correct as the picture has not altered in size.—D. Pettitt (Cumberland).

The ion trap magnet on the rear of the tube neck must be aligned for maximum brilliance. Also check the tube base contacts, the resistors associated with the brilliance network to pin 2 and the video amplifier resistors. These are  $47\text{k}\Omega$  to pins 1, 3 and 9 (from H.T. pin 8) and  $470\Omega$  from pins 1, 3 and 9 to chassis.

**GEC BT6542**

This is a 16in. model with I.F.'s of 38M to which I have added a tuner unit, type BT204. I have secured a good picture from Holme Moss—Band I and from Winter Hill—Band III, but the sound output is low. Unconverted, the set gives excellent sound and picture. There are no

obvious valve faults. The set also has a loud line whistle. Is it possible to reduce the noise without interfering with the line output transformer?—N. Logan (Royton).

Adjust the Band III oscillator tuner for loudest sound with the fine tuner midway. Readjust the aerial and R.R. slugs for optimum picture and then readjust the oscillator for minimum sound-on-vision. Curing the noise is difficult on this model. Try packing round the line output transformer with sorbo rubber.

**DEFIANT**

This set has developed a peculiar fault. On BBC there is a bright picture with plenty of contrast, but it is very prone to any kind of interference, which seems to be present all the time, and the sound level is well down. On ITV, however, the sound is fine but the picture is weak owing to a poor aerial. After a while the line timebase begins to slip and continues to do so every few minutes. This does not happen on BBC. I have changed over two ECL80 valves on the chassis and replaced both valves in the tuner with working valves. This restored the ITV picture but the other faults remain.—S. Dinnair (Crawley).

As you omitted to mention the model number of the set we are somewhat handicapped in our reply. However, it would appear that the alignment of the BBC coils is inaccurate. This may have been done deliberately in order to reduce the BBC signal which may have been excessive. If the model is one of the 1456 series you should release the rear right side thumb-screw and rotate the BBC tuning cam for maximum sound. If the input is excessive, use an aerial attenuator to the BBC socket. We will advise you further if necessary, but if, as you say, the ITV signal is weak, an effort should be made to improve the aerial.

**VIDOR C.N. 4218**

There is no EHT on this set. I have changed all valves in the circuit and checked windings. The recovery diode valve has a cathode voltage of only 175.—J. Hackworth (Oxon).

We presume the valve check included the frame output-part line oscillator, ECL80, the PL81 and PY81. You should now check the  $1.5\text{k}\Omega$   $5\text{W}$  resistor to pin 8 of the PY81, also the  $1.2\text{M}\Omega$  to pin 1 of the ECL80. Then check in turn the  $0.25\mu\text{F}$  boost capacitor (shorted), the  $100\text{pF}$  across the line output transformer windings, before suspecting the line output transformer. Make a check on the hold control etc. If the PL81 overheats check the  $0.01\mu\text{F}$  capacitor from pin 1 of the ECF80.

**QUERIES COUPON**

This coupon is available until MAY 19th, 1961, and must accompany all Queries sent in accordance with the notice on page 435.

PRACTICAL TELEVISION, MAY, 1961.

**SETS & COMPONENTS**

**RECLAIMED VALVES.** All tested and perfect, modern and obsolete; huge stocks; all one price, 5/-, plus 6d. postage each, delivered by return. LEWIS, 46 Woodford Avenue, Ilford, Essex.

**REBUILT TELEVISION TUBES—12in.** £5; 14in. £5/10/-; 17in. £8/10/-  
Twelve months' guarantee. 10/- car. TRANSISTORS, WHITE SPOT 5/-; RED SPOT 5/-; YELLOW/GREEN 5/6; RED/YELLOW 7/6; CRYSTAL DIODES 1/-, 2/-, 4/6. ELECTROLYTICS, all values; CONDENSERS, silver and paper. RESISTORS, all types; RECLAIMED VALVES, most types, 5/- each. AIRSPACED CO-AXIAL CABLE from 6d. per yard. BRAYHEAD TURRET TUNERS £6/19/6; REPLACEMENT VOLUME CONTROLS. TRANSFORMERS, TELEVISION and MAINS; SMALL PARTS REPLACEMENTS and numerous SECOND HAND COMPONENTS. S. & M. P. addressed envelope please with all enquiries.

**DEVIZES TELEVISION SERVICE**  
29-30 The Nursery, Bath Road, Devizes, Wilts. Tel.: Devizes 1100.

**TELEVISION TUBES!** 1st quality, new guns. Year's guarantee, most 75/- exchange. Rescreened from 85/- 3 Park Ave., New Barnet. BAR 1934.

**APPROX 150 Faulty TV tubes.** offers for whole or part. Buyer collects. 9 Blenheim Road, Redlands, Weymouth, Dorset.

**In Scotland . . . . .**  
**RENVUE**  
**for Better Value**

**COMPLETELY REPROCESSED TUBE (NEW GUN, RESCREENED, ALUMINISED)**

- 12.6v and 6.5v, 0.3 amp., ... .. £6.10.0
  - 17 and 15in. Types ... ..
  - 12.6v and 6.5v., 0.3 amp., ... ..
  - 14in. Types ... .. £6. 0.0
  - 12v., 15in. Types ... .. £7. 0.0
  - 2v, 12 and 15in. Types ... .. £6. 0.0
- Electrostatic 90 degree and 110 degree tubes 10/- extra. Carr. paid.

**10/- ALLOWED ON OLD TUBE**  
Terms arranged.

**FERGUSON**

- 14in. BBC and STV Consoles ... £12.10.0
  - 14in. BBC and STV Receivers ... £10.10.0
  - 17in. BBC and STV Receivers ... £19. 0.0
- COMPLETELY OVERHAULED AND FITTED WITH COMPLETELY REBUILT TUBE**

with One Year's Guarantee

£5 Deposit. Terms on Balance

**Renfrew Electronics Ltd.**  
**Anderson Drive**  
**Renfrew : Scotland**

Tel.: Renfrew 2642

**RATES:** 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television" Tower House, Southampton St., London, W.C.2.

**SETS & COMPONENTS**  
*(continued)*

**TV SPARES**

**London's Largest Range—New or Used**  
**LINE OUTPUT TRANSFORMERS and SCAN COILS**  
for nearly every make and model.  
New from 45/-. Used from 20/-.  
Just a few examples from our extensive range **IN STOCK.** Add 2/6 for P. & P. TELEPHONE ORDERS SENT SAME DAY C.O.D.

**NEW LINE O.P. TRANSFORMERS**

- Pye V4/7, VT4/7, 52/6; LV30, FV1, 52/6
  - Ferranti 14T2/3/4/5, 45/-; T1225, 62/6
  - Ferguson 992/6/7/8, 66/9, 941-55, 57/6
  - Ekco T221/231, 50/-; T161 etc., 45/-
  - H.M.V. 1824-9, 58/6; 1840-8, 59/6
  - Cossor 930-9, 58/6; 916-25, 75/-
  - Alba T301/504, 45/-, 362/441, 47/6
  - Murphy V240/250, 62/6; V200, 49/6
  - Ultra VT9-17 etc., 108/6, with U25,
  - Bush TV24, 66/6; TV53, 65/-; TUG34, 5 gns.
  - Philips 1114U, 91/8; 1768U, 102/6
  - Peto-Scott TV1411-15, TV1711-15, 49/6
  - Pilot TV/CV-76, 77, 84, DDC87, 75/-
  - New Scan Coils for Pye, V4/7, VT4/7, 62/6
- We also stock a complete range of spares for nearly all makes and models, e.g. LOT's, Line and Frame Blocking Trans., Frame Output Trans., valves, resistors capacitors, ion traps, etc., etc.

PLEASE SEND S.A.E. FOR IMMEDIATE QUOTE

Transtronic Transistor Kit, £5.4.8.  
Silicon Power Diodes, 250v, 300mA, 25/-  
Latest V Aerials, 15/-, plus P. & P.  
Guaranteed Valves, EF80, 10F1, 6F1, EF91, EB91, U Series, all 4/6, P. & P. 6d.  
Cabinets, all types from only 5/-.

**TELEVISION CONSUMER SERVICES LTD.**

**28 BROCKLEY CROSS, S.E.4.**  
TIDewey 5394

**112 CAMBERWELL RD., S.E.5.**  
RODney 7917

**ST. HELENS 4246** for Television tubes.  
S.A.E. list. DARWINS, 45 Shaw St., St. Helens Station, Lances.

**SALVAGED VALVES**  
**Now from 1/3 each**  
**New and Boxed Valves**  
**all at 10/- each**

Send 9d. for full list of valves and components.

**ARION TELEVISION, 4 Maxted Road S.E.15**  
**NEWX 7152**

**SETS & COMPONENTS**  
*(continued)*

**LIVER TUBES**

Fully Guaranteed 12 months

All makes—12" to 21"

**Blane & Martin**

**Electronics**

**70 HIGH STREET**

**WAVERTREE**

**LIVERPOOL**

Details on request

Tel. SEF. 3428

**TUBES — AERIALS — VALVES**  
Regunned tubes, guaranteed one year, prices from £4.12/6. Revacuumed tubes, all sizes, 50/- guaranteed 4 months. Full range of aerials at trade prices, double five costs only 50/-. Full range of valves, example FCC84 cost 8/-, ITV pre-amplifiers, £3.15.0. Self-contained in case, ITV converters, £5. Brayhead tuners, £4.12.6. New TV sets and transistor radios supplied, ask for quotation. Low loss co-axial, 1/1 yd.: Standard 8d. yd.  
Diplexers, 9/8 each. Chromed car aerials, 19/- each completed with head and plug, all types quoted for. All items carriage, extra. S.A.E. for lists.

G. A. STRANGE  
**BROADFIELD, NORTH WRAXHALL,**  
Nr. Chippenham, Wilts. Tel. Marshfield 236

**ELECTRICAL . . . . .**  
**FACTORS**

**OFFER THE FOLLOWING UNREPEATABLE BARGAINS**

**Brand New Television 12in. Tubes.**  
Type M.W. 31-74. £2.19.6 (Carr. & ins. 12/6)

**8-watt Push-pull Amplifiers, EL84 x EL84, ECC83, EZ80.** Complete production line purchased, enables us to sell at £2.15.0 (carriage 2/6).

**Beautifully made American Telescopic Car Aerials, heavily plated.** Were £2.10.0, OUR PRICE 24/- (carriage free).

**Fantastic clearance of Stereo Amplifiers, including two Mullard ECL82 and EZ80, pilot lights, knobs, one speaker circuit diagram, etc.** £2.19.6 (carriage 3/6).

**Rigidly tested Television Valves, individually boxed, 3/- to 7/6 each.**  
**Television Chassis, complete less valves, 30/- (carriage 5/-).**

**TELEVISION COMPONENTS AT BARGAIN PRICES**

Please write for your individual requirements. S.A.E. for Free Lists.

**4 HENDERSON ROAD EASTNEY : PORTSMOUTH**

**SETS & COMPONENTS**  
(continued)

**C. EDWARDS**

1070 HARROW ROAD  
LONDON, N.W.10  
LADBROOKE 1734

Offers  
5/8 TV in  
First-class  
Condition



12in. £5.00  
14in. £7.10.0  
(all 5 channel)  
+ 15/- carriage.  
Guaranteed

**VALVES**

10F1, 67-, 10C2.  
10/6; 20D1, 67-  
6F1, 57-, 5P61, 77-, 6K25, 87-, 20P1, 107-,  
PZ30, 87-, PL33, 77-, ECL80, 67-, EB91,  
67- Plus 6d. post.  
5/8 12in. Tubes, 30/- plus 7/6 post.  
Modern 13 Channel, 17in. Flye, £16.10.0  
plus 15/- carriage.

**H.P. on Regunned  
C.R.Ts.**

At No Extra Charge

12 Months' guarantee  
12" & 14" .. £3.10.0  
17" .. £4.10.0  
21" .. £5.10.0

Phone or Call only:  
Rod 7778

**P. J. F. Andrews**  
61-63 ROSEMARY RD.  
LONDON, S.E.15

**Television Tube Shop**

now stock

Tubes for every make of set

NEW REDUCED PRICES

12 inch, Mullard type ... £4.5.0  
12 inch, Mazda type ... £4.15.0  
14 inch, Mullard type ... £5. 5.0  
14 and 15 inch, Mazda type ... £5.15.0  
17 inch, All types ... £6.10.0  
17 inch, Slim line 110° ... £6.17.6  
21 inch, All types ... £8.10.0

Also G.S.C., BRIMAR, E.M.I. types,  
Add 10/- for delivery to your door within  
48 hours or 5/- B.R.S. Terms £2 down.

All Tubes Carry 12 months' guarantee.

A few shop-soiled tubes available. Good  
picture. Fully guaranteed, from 50/-.  
Spare-time Service Engineers—send for  
details of our rebate scheme,  
500 Tubes always in stock.

**VALVES**

A very wide range at 50% off list price. Send  
for complete price list of these and other  
Bargains.

**TELEVISION TUBE SHOP**

48 Battersea Bridge Road, LONDON  
S.W.11 BA7 6B59. Open Saturdays.

**SETS & COMPONENTS**  
(continued)

**REBUILT TV TUBES**

FULLY GUARANTEED 12 MONTHS  
New Gun fitted in every tube.  
12, 14in. ... £4.10.0  
15, 17in. ... £5.10.0  
21in. ... £7.10.0

TERMS C.W.O.

Carriage and Insurance 10/- extra.  
Allowance made on old tubes.

**DAVIS (CR TUBES) LTD.**  
34a CHURCH STREET  
EASTBOURNE  
Phone: 3279.

"HEATHKITS" can now be seen in  
London and purchased on easy terms.  
Free brochure DIRECT TV REPLACEMENTS  
LTD., Dept. PT/22/4, 138  
Lewisham Way, S.E.14. Tideway 6666.

**RADIO & TV SPARES**  
LINE OUTPUT TRANSFORMERS

All types of spares for all makes and  
models, List 3d.

**GUARANTEED VALVES**

EF91 3/-, EF90 5/-, 6F1, 10P1, PC84 6/6,  
20F2, UF41 7/6. Postage 6d. List 3d.

**SERVICE SHEETS**

List 6000 Models, 1/-, S.A.E. Enquiries  
Hamilton Radio (7), 18 Western Rd.,  
St. Leonards, Sx.

14in. TELEVISIONS, BBC/ITA, newly  
fitted rebuilt tubes. To clear £8.  
Tube guaranteed 12 months. Callers  
only. NU-GUN TELETUBES LTD., 3  
The Mews, Duckett Road, N.4. MOU  
2903.

**FINEST REPLACEMENT  
TV TUBES**

High Quality, True Fidelity  
Pictures, Exact Replacements.

12 inch ... £5.5.0  
14 inch ... £5.17.6  
15, 16, 17 inch ... £6.0.0  
21 inch ... £7.10.0

12 months' Guarantee.

Price includes Carr. and Insurance.  
Dispatched same day. Cash with  
order.

Free advisory service on tube  
changing etc., S.A.E., please, Callers  
welcome.

**STAN CHESHAM**  
HIGH STREET, MISTERTON,  
Nr. DONCASTER.  
Tel.: 368

**MISCELLANEOUS**

ASTRO MIRRORS, Flats, Eyepeices,  
Object Lenses, Prisms, Geared Heads,  
Drivers, Motors etc. Ex-Gov. Tele-  
scopes, Microscopes etc. Gunsights,  
Reflector Sights, Binoculars etc. List  
of over 1,000 items for S.A.E. How to  
use Ex-Gov. Lenses and Prisms. Nos.  
1 and 2 2/6 ea. H. W. ENGLISH, 469  
Rayleigh Road, Hutton, Brentwood,  
Essex.

**TV PHONE  
TRANSFORMERS** BY 3 p.m.  
SENT SAME DAY C.O.D. ON  
ALL ITEMS BELOW in STOCK

LINE OUTPUT TRANSFORMERS

Makes	Models	Prices
ARGOBY:	T9, CTV517 .. ..	58/8
DECCA:	D17 & C .. ..	58/8
DEFIANT:	TK1753 .. ..	58/8
R.G.D.:	6017T, 7017C, C54 .. ..	58/8
REGENTONE:	17C, 17T, 17, 21A, 2117 .. ..	58/8
BAIRD:	2014, 2017, 2114, 2117 .. ..	49/8
COSSOR:	926 & T, 931, 933-4-5, 937, 938 & A & F, 939 & A & F, 943 T, 946 .. ..	58/8
H.M.V.:	1428 & A, 1825 & A, 1826 & A, 1827 & A, 1829 & A .. ..	65/-
MARCONI:	VT99DA, VT89DA .. ..	68/-
ROSELL:	TS17, T346 .. ..	58/8
FERGUSON:	3057, 408T .. ..	63/-
H.M.V.:	1855, 1869 .. ..	68/-
FERGUSON:	992T-997T, 998T .. ..	69/8
PYE:	V4, VT4, V7, VT7, CTM4 .. ..	58/-

All other makes available (8-9 4899)

LINE BLOCKING OSC. TRANSFORMERS

ARGOBY:	T2-3, CTV517 .. ..	8/8
DECCA:	D14, D17, D17C .. ..	8/8
DEFIANT:	TK1454-6-8, 1552, 1764-5-6 .. ..	8/8
R.G.D.:	VT99DA, VT89DA .. ..	8/8
REGENTONE:	14.5-7T, 143T, 173T .. ..	8/8
R.G.D.:	6012-4-5-7T series .. ..	8/8
H.M.V.:	1824 & A, 1825 & A, 1826 & A, 1827 & A, 1829 & A, 1840-1-2- 3, 6-7-8 .. ..	14/8
MARCONI:	VT88DA, VT89DA, VT160, VC & VT161, VC162-3 .. ..	14/8
FERGUSON:	992T-997T, 998T .. ..	18/8
PYE:	V4, VT4, V7, VT7, CTM4 .. ..	16/8

FRAME BLOCKING OSC. TRANSFORMERS

ALBA:	T801, 904, 912, 972 & B, 394, 438 & B series .. ..	12/8
ARGOBY:	T8-3, CTV517 .. ..	12/8
DECCA:	D14, D17, D17C .. ..	12/8
DEFIANT:	TK1454-6, 1552, 1764-5-6 .. ..	12/8
MARCONI:	VT43DA .. ..	12/8
R.G.D.:	6012-4-5-7T series .. ..	12/8
REGENTONE:	14.5-7T, 143T, 173T .. ..	12/8
VIDOR:	CN4216, CN4925 series .. ..	12/8
PHILIPS:	335U, 485U, 492U, 683U, 704A, 1609U .. ..	15/-
STELLA:	1522U .. ..	15/-
PHILIPS:	1400A, 1700A, 1800A, 2947A .. ..	15/-
PHILIPS:	E.H.T., Omc.Tx.1400A, 1700A, 1800A, 2947A .. ..	15/-
PHILIPS:	1101U, 1300U & VF, 1400A, 2387A, 2847A .. ..	16/-
PHILIPS:	1114UM, 116U, T01497U, 1440U & 45, 1726U, 1740U & 45, 1747U .. ..	16/-
STELLA:	8314U, 8317U .. ..	16/-
PYE:	FV1&C, FV2C, V2, FV4C&CDL 904, 906, 962-3-4, 958 .. ..	11/8
PAM:	T105, 107-8, 110-1-2-4-5-7-8-9, 2224, 2274 .. ..	11/8
FERRANTI:	1473-4-5-6, 1773-4-5-6, 2074- 5-6, 21K5-6, 24K4, T1325, 1696, 1825 .. ..	14/8

SOBELL:	TS17, T174, T175 & C, T174&C, TRG174, T176 & LO, TR60 175, T274, T277, T346 .. ..	15/-
BANNER:	BT114, BT117 & C .. ..	15/-
COLUMBIA:	503, 605-6 .. ..	15/-
H.M.V.:	1814, 1816, 1821, 1824 & A, 1825 & A, 1826 & A, 1827 & A, 1829 & A, 1840, 1841, 1842, 1843, 1844, 1845-6-7-8 .. ..	14/8
MARCONI:	VC89DA, VT99DA, VC80DA, VT89DA, VT88DA, VT88DA, VT160, VC & VT161, VC82-3 .. ..	14/8
PYE:	V4, VT4, V7, VT7, CTM4 .. ..	13/8

FRAME OUTPUT TRANSFORMERS

BANNER:	BT114, BT117 & C .. ..	25/-
COLUMBIA:	C503, C505, C506 .. ..	25/-
SOBELL:	TS17, T191, T199, T143, T144, T145 & C, T171C, TRG174, T175 & LO, TRG176, T176, T224, T274, T277, T346 .. ..	25/-
PYE:	V4, VT4, V7, VT7, CTM4 .. ..	28/8
FERGUSON:	992-998T .. ..	21/-

SOAN COILS

PYE:	V4, VT4, V7, VT7, CTM4 .. ..	59/8
FERGUSON:	992T-998T series .. ..	58/8
EKCO:	T217, TC178, TC196, T905, T206, VC207 .. ..	90/8

All Makes Available for ALL Models.  
S.A.E. All ENQUIRIES

Post and Packing all Items. 1/6. C.O.D. 1/6 extra.

**Wyndor Television Service**  
ST. ALBANS ROAD  
BARNET, HERTS.  
BAR 1769 Closed Thursday 1 o'clock

**FOR SALE**

**100 BAYS** Brand New Adjustable Steel Shelving, 72in. high x 34in. wide x 12in. deep; stove enamelled dark green, sent unassembled. Six shelf bay **£3/15/0**. Sample delivered free. Quantity discounts. **N. C. BROWN LTD.**, Eagle Steelworks, Heywood, Lancs. Tel.: 69018.

**TELEVISIONS**

All sizes including Projections. Require attention from **£3**. In working order—  
12in. BBC from **£5**,  
12in. and 14in. BBC/ITA from **£10**.  
Regunned CRT **£6** extra 17in. from **£25**.  
Send for Lists **Carriage Paid**.

**CADMAN'S**

SERVICE DEPARTMENT  
BRYAN STREET, HANLEY  
STOKE-ON-TRENT

**VALVE CARTONS** at keen prices. Send 1/- for sample and list. **J. & A. BOXMAKERS**, 75a Godwin Street, Bradford 1.

**1,000 TELEVISIONS**, all makes, from **£3** working, 10/- not. Callers only. 9 till 6 including Sats. 39 Whitehorse Lane, Stepney, London.

## Star TV Tubes

### 70/-

all sizes up to and including 17in. includes old glass or plus 7/6 without  
C.W.O. Carriage 7/6.

**WHY PAY MORE ?**

new guns, 12 months' guarantee.

also 20/- each

12in., 14in., Part Exchange Televisions

**ARTHUR SLARK**

43-45 Thicketford Road, Tonge Moor, Bolton.  
Phone: 6684.

**SERVICE SHEETS**: also Current and Obsolete Valves for sale. **JOHN GILBERT RADIO**, 20 Extension, Shepherd's Bush Market, London W.12 (Phone: SHE 3052).

## TELEVISION ENGINEERS

### and Dealers

to act as Agents for our rebuilt TV Tubes, guaranteed for 18 months. Write in first instance.—

**E. M. SERVICES**

131 St. Anns Road, London, N.15.

**SIX VOLS.** Radio and TV servicing (Molloy and Poole). Vols. 1-5 and 1955-56 models, as new, lot **£5**. **ROSS**, 11 Campbell Dr., Barrhead, Glasgow.

**FOR SALE (continued)****TURRET TUNERS**

**BRAYHEAD £3.19.6.**

Brand New, any area, complete with fitting instructions. State set and 2 channels. 10 M/e only. **EXTRA COILS 10/6**, per channel. **RECTIFIERS — CONTACT COOLED.**  
14RA1282 (FC101) type, 250 v., 250 mA, 13/8;  
14RA1283 (PC31) type, 250 v., 300 mA, 17/8;  
350 mA 19/8.

**RECTIFIERS — FIN TYPES.**

Equivs. for RM4 250 v., 250 mA, 14/-; RM5 250 v., 300 mA, 17/8; 14A989 400 mA, 18/6; 14A86 16/6; 14A97 20/-; 14A100 22/6; 14A124 22/6.

**CABYMETERS.** A10, £4.17.6; B20, £6.10.0, with either meter 36 mixed resistors, 6d. only. **ARMCHAIR EXTENSION VOLUME CONTROL** unit for TV, Radio Amplifiers, etc. Easily fitted perfectly safe. 22/6. **TRANSISTOR OC1627/-**.

Cash with order. Post Free. C.O.D. 2/6.

**DURHAM SUPPLIES**

175 Durham Road, Bradford 8, Yorkshire.

**WANTED**

**WANTED** Service Sheets. No quantity too large, highest prices paid. **SULTAN RADIO**, 29 Church Road, Tunbridge Wells, Kent.

**A PROMPT CASH OFFER** for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. **R.H.S.**, 155 Swan Arcade, Bradford 1.

**BEST PRICE** paid by return for new Valves and equipment. **STAN WILLETS**, 43 Spon Lane, West Bromwich, Staffs. Tel: WES 2392.

**NEW TV VALVES WANTED.** Send valves, cash by return, to **P. J. P. ANDREWS**, 61-63 Rosemary Road, London S.E.15

**NEW VALVES WANTED.** — EY51, ECL80, PCC84, PCF80, PCL83, PL81, PCL82, PY81, R19, U801, 30P4, etc. Best cash prices by return. **DURHAM SUPPLIES**, 175 Durham Road, Bradford 8, Yorkshire.

**WANTED** 1957/58 edition of Newnes Radio and TV Servicing, Box 24.

**NEW 12A7 valve** or secondhand in good condition. **REGENT 2283** between 9 and 12.

**BOOKS**

**FIND TV SET TROUBLES IN MINUTES** from that great book "The Principles of TV Receiver Servicing," 10/6 all book houses and radio wholesalers. If not in stock from: **Secretary, I.P.R.E.**, 20 Fairfield Road, London N.8.

**SERVICE SHEETS**

**SERVICE SHEETS** Radio, TV, 5,000 models. Lists 1/-. S.A.E. enquiries: **TELRAY**, 11 Maudland Bk., Preston.

**FAULTFINDER FILES (TV)** showing common faults that each receiver is prone to and other useful servicing information, 2/- each. List **9d.**, plus postage. **S.P. DISTRIBUTORS**, 44 Old Bond Street, London W.1.

**SERVICE SHEETS.** TV 4/- ea. Radio 3/- ea. List 1/-. All orders dispatched on day received. Also Manuals for sale and hire. **SULTAN RADIO**, 29 Church Road, Tunbridge Wells, Kent.

**SERVICE SHEETS** from 3/-. Some for hire. **S.A.E. DARWINS**, 45 Shaw Street, St. Helens, Lancashire.

**SERVICE SHEETS**

(continued)

**SERVICE SHEETS (1930-1961)** from 1/- with Free Fault-Finding Guide. Catalogue 6,000 models 1/-, 125 Radio/TV Sheets covering 370 popular models 20/- S.A.E. enquiries. **HAMILTON RADIO**, Western Road, St. Leonards, Sussex.

**SERVICE SHEETS.** — We have the largest stock of Radio and TV Service Sheets in the country for sale at 4/- each. Why tolerate delay in obtaining your supplies when we will dispatch by return? Service Sheet List 1/-. Also Manufacturers' Manuals for sale and hire 1961. Lists now available 1/- S.A.E. please. Mail orders only to: **S.P. DISTRIBUTORS**, 44 Old Bond Street, London W.1.

**EDUCATIONAL**

**"HOW AND WHY"** of Radio and Electronics made easy by a new, non-maths practical way. Postal instructions based on hosts of experiments and equipment building carried out at home. New courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from Dept. 12. **P.T. RADIOSTRUCTOR**, 40 Russell Street, Reading.

## Radio Television & Electronics

Learn at home with the world's largest home study organisation. **Brit. I.R.E.**; City & Guilds; **R.T.E.B.**, etc. Also Practical Courses with equipment. No books to buy.

Write for **FREE prospectus** stating subject to

**I.C.S.**

Dept. 516  
Intertext House, Parkgate Road,  
London, S.W.11.

**FREE FROM THE I.P.R.E.** Syllabus of famous radio and TV courses. Membership Condition booklets. 1/-. Sample copy the Practical Radio Engineer 2/- post free. Secretary, 22 Fairfield Road, London N.8.

## ★ LEARN ★

### RADIO & TV SERVICING

#### for your OWN BUSINESS/HOBBY

by a new exciting no-maths system, using practical equipment recently introduced to this country

**FREE Brochure from:—**  
**RADIOSTRUCTOR**  
DEPT. G78


READING, BERKS.

5/61

**EDDY'S (Nottm.) LTD.**  
172 ALFRETON ROAD, NOTTINGHAM

**Build your own  
CAR RADIO!**

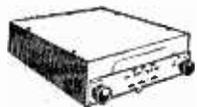★ 7 Transistors ● Long and Medium Waves ● Two Watts Output ● R.F. Stage and Automatic Gain Control



**10½**

**Gns.**

**P & P**

**5/- extra**

6 or 12 volts (state which)  
Supplied with full instructions  
Size 7½ x 7½ x 2½ in.  
**SPEAKER, extra 1/11**

**POCKET RADIO** 2 Transistor with miniature speaker. Complete with all parts wiring diagram and full instructions, 27/6. Batteries 1/-, P. & P. 1/6.

**P.W. 6 TRANSISTOR** Medium and Long wave pocket superhet. 6 matched transistors and diode. 150M.V.V. push-pull output. Easy to follow, printed circuit with all parts. Components marked. High "Q" internal ferrite aerial. Quality 2½ in. speaker size 5½ x 3 x 1½ in. No technical knowledge required. No extras to buy. Total cost of all items £9/5/0. P. & P. 2/6.

**VIBRATORS** 12v4 pin 4/11. Post 1/-.

All above are **NEW and Guaranteed** New or Surplus Valves, Guaranteed and Tested by Return Post.

IA7GT 1/16	IA2A 5/3	EF37A 7/6
IC5GT 9/9	IA2AT6 7/6	EF41 7/9
ID5 7/6	IA2K7 5/3	EF42 7/6
IH5GT 9/9	IA2Q7 5/3	EF80 5/-
IN5GT 9/6	25L6GT 7/6	EF85 5/11
IR5 5/6	25Z4G 7/6	EF86 9/6
IS5 4/9	30F5 8/6	EF89 7/-
IT4 3/11	35W4 6/9	EF91 3/6
3Q4 7/-	35L6GT 8/11	EL41 7/3
3Q5GT 8/6	35Z4 5/3	EL84 6/6
3S4 5/11	80 7/-	EL91 4/6
3Y4 6/9	954 1/6	EL95 7/11
5U4G 4/9	955 2/6	EY86 7/9
5Y3GT 5/9	956 3/6	EZ40 6/3
5Z4G 7/6	CC 7/6	EZ41 7/-
6AG5 4/-	DAF91 4/9	EZ80 6/-
6AQ5 6/-	DAF96 6/11	EZ81 6/9
6AT6 7/-	DF91 3/11	KT33C 6/6
6BA6 5/11	DF96 6/11	MU14 7/-
6BE6 5/11	DK91 5/6	PC884 7/3
6BBG 2/11	DK96 6/11	PCF80 7/3
6C4 3/-	DL96 6/11	PLC83 12/6
6C6 4/9	DM70 7/6	PEN46 7/-
6F33 6/9	EAF42 8/6	PL81 9/-
6J5G 2/9	EB41 6/11	PL82 7/-
6J5GT 3/9	EB91 3/6	PL83 7/-
6K7G 1/11	EB41 7/6	PL84 10/11
6K7GT 6/-	EBF80 8/-	PY80 7/-
6K8G 5/3	ECC81 5/3	PY81 6/6
6SN7GT 4/3	ECC82 5/11	PY82 6/9
6Q7G 5/9	ECC83 4/6	U25 12/6
6SG7M 4/9	ECC84 8/3	UAF42 8/9
6S17M 5/9	ECC85 7/11	UBC41 7/3
6U4GT 10/6	ECF80 9/6	UJ42 7/6
6V6G 4/9	ECF82 9/-	UL41 7/6
6V6GT 4/9	ECH42 8/3	UL84 7/6
6X4 5/9	ECL80 7/-	UY41 6/3
6X5G 4/11	ECL82 10/-	UY85 6/3
10F1 6/11	EF36 3/-	VP23 6/6

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers' risk. Post and Packing 6d. per valve extra. C.W.O. or C.O.D. only. C.O.D. charge 3/- extra. S.A.E. with enquiries.

**REBUILT TV TUBES**

**FULLY GUARANTEED  
12 MONTHS**

Complete New Gun fitted in every Tube

12in. ...	... £4.00
14-15in. ...	... £4.10.0
17in. ...	... £5.00
21in. ...	... £7.00

**Immediate Delivery**  
Carriage and Insurance 10/- extra  
Allowance on old tube

**NU-GUN TELETUBES LTD.**

3 The Mews, Duckett Rd.  
Harringay, London, N.4  
Telephone: MOUntview 2903

**B.B.C. - I.T.V. - F.M. AERIALS**



**B.B.C. (BAND 1).** Telescopic loft, 19/6. External, S/D, 20/3.  
**I.T.V. (BAND 3).** 3 Element loft array. 14/-, 5 Element. 32/6. Wall mounting, 3 Element, 33/9, 5 Element, 41/3.

**COMBINED B.B.C. + I.T.V.** Loft 1+3 Element, 41/3. 1+5 Element, 48/3. Wall mounting, 1+3 Element, 56/3. 1+5 Element, 63/9. Chimney and mast mounting units also available.

**F.M. (BAND 2).** Loft "H" 28/-, 3 Element loft, 52/6. S/D loft, 12/6. External S/D, 20/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3. Send 6d. stamp for illustrated lists.

**K.V.A. ELECTRONICS (Dept. T.P.)**  
38 Godstone Road, Kenley, Surrey

**TRANSISTORS**

OC44, OC45, OC71, OC72  
all 10/- each  
Red Spot 3/- White Spot 4/6  
Crystal Diodes 1/-  
OA70, OA81, GD4, GEX34,  
GEX35, all 4/- each

**TRANSISTOR HOLDERS 1/3** each  
Connecting Wire, six assorted colours  
1 yd. each colour, 1/9, 2 yds. each, 2/9,  
10 yds. each 10/6. Valveholder, can  
and spring complete 1/6, size B7G or  
B9A. Resistors, all values 10% 1V, 6d., 1V, 9d. Condensers .01 mfd  
1000V, T.C.C. 10d. All prices post paid.  
Send S.A.E. for our Bargain list.

**OAKFIELD RADIO**

121 MACCLESFIELD ROAD, HAZEL GROVE,  
STOCKPORT, CHESHIRE

**MAIL ORDER ONLY**

**RES/CAP. BRIDGE 38/-**  
p. & p. 2/-

Checks all types of resistors, condensers  
& RANGES  
Built in 1 hour Direct reading  
**READY CALIBRATED**  
Stamp for details of this and other kits  
**RADIO MAIL (Dept. LV)**  
Raleigh Mews, Raleigh Street, Nottingham

**OUR COMPREHENSIVE SERVICE INCLUDES:**

12 CHANNEL TURRET TUNERS, 10, 18, 38 Mc/s. 40/-; VALVES, PCF80 and PC84, 7/3 each. Cabinets, Glasses, Masks, Condensers, Resistors, Ion Traps, Speakers.

**RECLAIMED C.R. TUBES**  
(Not boosted or reactivated)  
9in. and 12in. 35/-; 14in. 50/-; 17in. 60/-  
All picture tested, taken from stripped TV's.

**REGUNNED C.R. TUBES**  
(12 month guarantee)  
12in. 80/-; 14in. 90/-; 17in. 100/-  
**EXAMPLE OF TRANSFORMER LIST**  
L.O.P.T. SCAN COILS

**FERGUSON:** (New) (Used) (New) (Used)  
103T 105T 89/9 35/- 80/- 35/-  
9524/6/8 .. 88/9 35/- 60/- 35/-  
P.Y.E.

V4, V5, V6, V7 35/- 55/- 35/-  
VT7, CTM4 52/6 35/- 55/- 35/-

These are only examples of stocks, we have many thousands more, and would be pleased to quote for any component you may require.

We pride ourselves that we can obtain and supply any TV spare.

**OUR GIGANTIC STOCKS INCLUDE:**

LINE OUTPUT, FRAME OUTPUT, SOUND OUTPUT, LINE AND FRAME BLOCKING OSC. TRANS. AND SCAN COILS. FOR ANY MAKE OR MODEL TELEVISION.

AZ31 8/6	PCL82 10/9	SP41 2/3
B36 5/6	PCL83 11/3	SP61 2/3
D77 3/-	PL84 9/6	W77 5/-
DH77 4/6	PL83 8/6	Z77 9/-
DK91 5/9	PL36 10/9	5V4 5/-
DK92 8/-	PL36 14/6	5V4 9/-
DK96 7/6	PL81 8/6	5Y3 10/6
DL82 5/9	PL83 8/9	5Z4 10/-
DL84 3/6	PL83 6/9	6AL5 3/6
DL86 7/6	PY31 7/-	6AM6 3/-
EB91 3/-	PY32 10/-	6CD6 27/6
EB33 5/-	PY80 6/6	6D2 3/-
EBF80 9/6	PY81 6/6	6F1 5/-
ECC83 6/3	PY82 6/6	6F12 3/-
ECC82 5/9	PZ20 10/-	6F13 7/-
ECC84 8/-	U22 9/6	6F14 9/6
ECC80 8/-	U24 10/-	6F15 9/6
ECC85 9/-	U25 12/-	6L1 12/6
ECH81 6/-	U26 12/-	6V8 5/6
ECL80 6/9	U31 9/6	10F1 4/6
EF39 5/-	U50 8/6	10C1 10/-
EF50 3/9	U52 7/-	10C2 13/-
EF80 4/6	U191 9/6	10P13 9/-
EF91 3/-	U281 8/6	12A17 5/6
EF92 5/-	U282 20/-	12A17 5/6
EL33 8/6	U301 20/-	12AU7 5/9
EL38 14/6	U301 22/6	20D1 8/6
EL84 7/-	UAF42 8/6	20F2 9/-
EY51SE 6/9	UBC41 7/9	20F2 9/-
EY51 7/9	UCH42 7/-	20L1 12/6
EY86 7/6	UF41 8/6	20F1 12/6
EZ40 6/6	UJ42 3/9	20P3 12/6
KT33C 8/6	UL 7/3	20P4 16/6
KT86 8/6	UL46 7/3	27B5 14/-
KT86 15/-	UL44 11/6	30C1 7/-
PC884 7/-	UY41 8/6	30L1 7/-
PC889 8/6	U08 14/6	30P4 10/9
PCF80 8/6	U09 8/6	185BT 14/-

These are only examples of our valves: if you do not see what you require send stamped addressed envelope for special quotation.

For the Finest, Fastest Service in the country, contact—

**D. & B. TELEVISION**  
131a KINGSTON ROAD  
SOUTH WIMBLEDON  
LONDON S.W.19

Phone: Cherrywood 3865

And that's not all—  
WE ARE OPEN FROM 10 a.m. UNTIL MIDNIGHT

For any information or problems you have call on us or Phone, we are always pleased to help.

TERMS: S.A.E. all enquiries. C.W.O. or C.O.D. 3/- extra.

Postage on Valve 6d. each, C.R.T.'s 12/6 inc. insurance.  
SATISFACTION ASSURED  
RETURN POST SERVICE

**T.V. SPARES!**



★ **SPEAKERS** 8/8 to Clear. Mid salvage. 5, 6 and 8in., 7 x 4in. Other sizes available. "Money back Guaranteed." P. & P. 2/6.  
 ★ **CABINETS** 2/9 In Lizard leatherette. Size 14 1/2 x 6 x 10in. With s/d doors. For portable radios. P. & P. 3/6.

★ **R.F. E.H.T. COILS** 7/9 10kV. R.F. Uses 6V6 osc. P. & P. 2/6.

★ **SALVAGE STRIP, 1/-.** Contains 30 varied resistors including slider resistors, 25 varied condensers, including Beehive trimmer, 5-BSA valve holders, 1-B91 and 1-B7G valve holders, H.P. choke and 8 x 4in. aluminium chassis. **BARGAIN AT THIS PRICE.** P. & P. 1/9.

★ **VOLUME/TONE CONTROLS.** 2/8 per doz. Assorted volume and tone controls, stripped from working chassis. P. & P. 2/-.

★ **RECTIFIERS.** 2/9. 250V, 100mA, 1-wave. Salvage. P. & P. 1/3.

A host of Valves, Condensers, Droppers, Chokes, Speakers, Coils, Magnets, Changers, Amplifiers, Cabinets, etc. Stamp for latest **FREE LIST.**

**P.P. COMPONENTS LTD.**  
 219, Ilford Lane, Ilford, Essex

**CLARKSON'S TUBE CHANGE**

6A DENISON ROAD, LEEDS 2 Tel. Leeds 24576

We are now able to offer **SUPER SCREEN TV TUBES** with 12 months' guarantee at the keenest exchange price ever.

Example:

Tubes all Types	Cash allowance on return of old tube	Actual Cost of Tube
12"—14": £5	15/-	£4. 5. 0
15"—17": £6	25/-	£4. 15. 0
21": £8	30/-	£6. 10. 0

Carriage and Insurance 10/- extra

These tubes are **COMPLETELY REBUILT** by experts, with the most up-to-date electronic equipment, and are fitted with the famous American Superior Electron Gun. Many thousands of these tubes are in service today. Our factory is open to inspection to readers of "Practical TV". Technical advice and queries are answered free of obligation. All tubes are dispatched with adhesive paper and return labels. Cash allowance is sent on receipt of old tube.

**COYNE'S NEW JOB TRAINING BOOKS**

Free Trial Offer

Put Money-Making Time Saving Know-how At Your Fingertips!



Shows you the way to easier TV—Radio repair—time saving, practical working knowledge that helps you to repair sets faster! How to install, service and align ALL radio and TV sets, even colour-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick." No complicated maths or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home.

No. 8

*Pin-Point*

**TV troubles in 10 minutes**



Find the exact sound or picture trouble in ANY TV set from 700 possibilities! Latest edition now has 332 pages of solid TV servicing information; 300 diagrams, check charts. 31/6, postage 1/-.

**SPECIAL OFFER**

Circle Book No. 8 on coupon, send only 16/3 after 7 days, and 16/3 in 30 days, making a total of 32/6 including postage.

No. 9

*Pin-Point*  
**Transistor troubles in 12 minutes**



Trouble-shoot every type of circuit in ALL transistorized equipment! 525 pages; hundreds of illustrations; 120 check charts. 47/6, postage 1/6. Circle Book No. 9 on coupon.

**TRY ANY THREE BOOKS NO RISK FREE TRIAL**

- No. 1—**EVERYTHING ON TV-RADIO PRINCIPLES!** 300 pages of practical explanations; hundreds of illustrations. 29/-. (An ideal book for the beginner).
  - No. 2—**EVERYTHING ON TV-RADIO-FM RECEIVERS!** 403 pages; fully illustrated. 26/-.
  - No. 3—**EVERYTHING ON TV-RADIO CIRCUITS!** 336 pages; hundreds of illustrations, circuit diagrams. 26/-.
  - No. 4—**EVERYTHING ON SERVICING INSTRUMENTS!** How they work, how to use them. 298 pages; illustrated. 26/-.
  - No. 5—**EVERYTHING ON TV-TROUBLE-SHOOTING!** Covers all types of sets. 437 pages; illustrations, diagrams. 34/-.
  - No. 6—**TV CYCLOPEDIA!** Quick and concise answers to TV problems in alphabetical order, including UHF, Colour TV and Transistors; 868 pages. 47/6.
  - No. 7—**TRANSISTOR CIRCUIT HANDBOOK!** Practical Reference covering Transistor Applications; over 200 Circuit Diagrams; 410 pages. 39/6.
  - In addition to the above you may also choose from the following:
  - No. 10—**REFERENCE MANUAL OF TRANSISTOR CIRCUITS** (Mullard). Features 60 circuits you can build, 241 diagrams, 308 pages. Price 12/6.
  - No. 11—**FM SERVICING HANDBOOK.** Gordon J. King (Odhams). A practical book on design, construction, alignment and repair of FM/VHF radios. Price 25/-.
  - No. 12—**TELEVISION SERVICING HANDBOOK.** Gordon J. King (Odhams). An excellent book on fault tracing, alignment and repairs. (This book AND Pin-Point TV Troubles combined will provide most of the information you will ever need on TV.) 276 pages. Price 30/-.
  - No. 13—**THE PRACTICAL HI-FI HANDBOOK.** Gordon J. King (Odhams). About the best book on HI-FI we have ever seen. 219 pages. Price 25/-.
- Just mail coupon for free trial. After 7 days send only low price or return books and pay nothing. If you keep more than one book, send £1 after 7 days and £1 each month until completed (maximum three books). To buy one book send one half in 7 days, one half in 30 days.

**SEND NO MONEY—POST COUPON NOW FOR SPECIAL OFFER**

**To SIM-TECH BOOK COMPANY**

Mail Order Division, DEPT. PT99, Gaters Mill, West-End, Southampton, Hants.

Rush the books circled below for 7-day FREE TRIAL as per offer.

1 2 3 4 5 6 7 8 9 10 11 12 13

Name .....

Address .....

City ..... County .....

Tick here if enclosed full price, we pay postage. Same 7 day money back guarantee. Postage £2 or less 1/3. £3 or more 2/-.

# SENSATIONAL NEW 1961 DESIGNS— LOW PRICES★ PICTORIAL STEP-BY-STEP PLANS

## THE NEW "LISBON" TRANSISTOR SET

Build the miniature highly sensitive "LISBON" design. This is a pocket 2-stage transistor set not much larger than a matchbox. Excellent clear reception covering all medium waves and working for months and months off a tiny 11 or 3 volt battery costing only 3/6d. A very simple set to build and an excellent introduction to transistor circuitry. Everything can be supplied down to the last nut and bolt including SIMPLE AS A.B.C. PICTORIAL STEP-BY-STEP PLANS FOR ONLY 19/6, plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.

**19/6**



## THE NEW 4 STAGE "MINUETTE"

Build this newly-designed "MINUETTE" 4 STAGE transistor set in very strong ready drilled ULTRA-MODERN CASE, size only 6 x 3 1/2 x 1/2 in. Uses three transistors and diode and SELF CONTAINED LOUD-SPEAKER. Very sensitive, ideal for office, bedroom, holidays, etc. Months and months of listening off an 8d. battery. Can be built FOR ONLY 39/6, including PROPER CASE, miniature speaker etc. SIMPLE AS A.B.C. PICTORIAL STEP-BY-STEP PLANS, etc. plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.

**39/6**



## OUR NOVEL WRIST RADIO

Our engineers have designed this novel Wrist Radio using latest transistor techniques. Size only 1 1/2 x 1 x 1/2 in. "Featherweight" yet gives clear, crisp reception over all medium waves. Tiny battery lasts months and months costing only 4d. No snags—anyone can build it in an hour or two using our SIMPLE AS A.B.C. PICTORIAL STEP-BY-STEP PLANS. All parts can be supplied including case and strap FOR ONLY 22/6, plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.

**22/6**



## THE NEW 3-STAGE "RIO"


Our fabulous new 3-STAGE MINIATURE LOUDSPEAKER DESIGN THE "RIO" covers all medium waves including Home, Light, etc. Very reliable and lightweight. Works for months and months off an 8d. battery. Can be assembled in an hour or two. All parts can be supplied including miniature speaker and everything down to the last nut and bolt with SIMPLE AS A.B.C. PICTORIAL STEP-BY-STEP PLANS FOR ONLY 29/6, plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.

**29/6**



CONCORD ELECTRONICS Dept, P.T.3, 210 CHURCH RD., HOVE, Sussex

# Build your own Aerials...

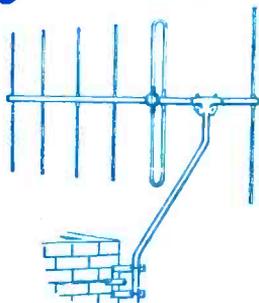

## AT HOME

AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M. Useful formulæ and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above, to:—

# Fringelevision Ltd.

MARLBOROUGH, WILTS. Phone: 657/8

**C.R.T. BOOSTER TRANSFORMERS**  
 TYPE A, OPTIMUM 25% and 50% BOOST.  
 2 V. OR 4 V. OR 6.3 V. OR 10.8 V. OR  
 13.8 V. MAINS INPUT. 12/6  
 TYPE A2. HIGH QUALITY. LOW CAPACIT-  
 ITY. 10/15 pF. OPTIONAL BOOST 25%, 50%,  
 75%. MAINS INPUT. 16/8  
 TYPE B. MAINS INPUT. MULTI OUTPUT 2,  
 4, 6.3, 7.3, 10 and 13 VOLTS. BOOST 25%  
 AND 50%. LOW CAPACITY. 21/-  
 Full instructions supplied

TRIMMERS. Ceramic. 30, 50, 70 pF. 9d., 100 pF.  
 150 pF. 1/3; 250 pF. 1/6; 500 pF. 750 pF. 1/8.  
 RESISTORS. Preferred values. 10 ohms to 10 meg.;  
 1 w., 4d.; 1 w., 4d.; 1 w., 6d.; 1 1/2 w., 8d.; 2 w., 1/-;  
 HIGH STABILITY. 1 w., 1/-; 2/-; Preferred values  
 10 to 10 meg. Ditto, 5Ω, 100Ω to 5 meg. 2d., 9d.

5 watt } WIRE-WOUND RESISTORS } 1/3  
 10 watt } 25 ohms-10,000 ohms } 2/6  
 15 watt } } 2/-  
 12.5K to 50K 10 } 3/-

**AMERICAN "BRAND FIVE" PLASTIC RECORDING TAPE**  
 Double Play 7in. reel, 2,400ft 60/- Spare  
 5in. reel, 1,200ft 37/6 Plastic  
 Long Play 7in. reel, 1,800ft 35/- Reels  
 5 1/2in. reel, 1,200ft 23/6 3 in. 1/-  
 5in. reel, 900ft 18/6 5 in. 2/-  
 Standard 7in. reel, 1,200ft 25/- 5 1/2 in. 2/-  
 5in. reel, 600ft 18/- 7 in. 2/6  
 "Instant" Bulk Tape Eraser and Head De-  
 fluxer. 200/250 v. A.C. 27/6. Leadlet. S.A.E.

**O.P. TRANSFORMERS.** Heavy Duty 50 mA. 4/6.  
 Multiple, push button 7/8. Miniature 384, etc., 4/6.  
 Push-pull 15 to 15/8. L.F. CHOKES 15/10 H. 60/65  
 mA. 5/-; 10 H. 85 mA. 10/8; 10 H. 150 mA. 14/-

**MAINS TRANSFORMERS 200/250 v. A.C.**  
 STANDARD, 250-0-250, 80 mA, 6.3 v. 3.5 a.  
 tapped 4 v. 4 a. ditto, 6.3 v. 1 a. 5 v. 2 a.  
 2 a. or 4 v. 2 ditto, 350-0-350 22/6  
 MINIATURE 200 v. 20 mA, 6.3 v. 1 a. 10/6  
 MIDGET, 220 v. 45 mA, 6.3 v. 2 a. 15/6  
 SMALL, 220-0-220, 50 mA, 6.3 v. 2 a. 17/6  
 STD., 250-0-250, 65 mA, 6.3 v. 3.5 a. 17/8  
 HEATER TRANS. 6.3 v. 13 amp. 7/6  
 Ditto, tapped sec. 2, 4, 6.3 v., 11 amp. 8/6  
 Ditto, sec. 6.3 v. 3 amp. 10/6  
**GENERAL PURPOSE LOW VOLTAGE.** 2a.  
 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30. 22/6  
**AUTO TRANSFORMERS.** 150 w. 22/6  
 0, 10, 120, 200, 220, 250 v. 22/6

**ALADDIN FORMERS** and core. 1in., 8d.; 1in., 10d.  
 0.3in. FORMERS 5987/8 and Cans TV1/2. 1in. sq. x  
 2 1/2in. and 1in. sq. x 1 1/2in. 2/- ea., with cores.  
**SOLO SOLDIER IRON.** 220/40 v. 25 w. 2/6  
**MAIS DROPPERS.** 3in. x 1 1/2in. Adj. Sliders.  
 0.3 amp., 1,000 ohms, 4/3. 0.2 amp., 1,000 ohms, 4/3.  
**LINE CORD.** 0.3 amp., 60 ohms per ft., 0.2 amp., 100  
 ohms per ft., 2-way, 8d. per ft., 3-way, 7d. per ft.  
**LOUDSPEAKER P.M.** 3 OHM. 5in. Rola, 17/6.  
 8in. Plessey, 12/6. 6in. x 3in. Rola, 18/6. 6in.  
 Rola, 18/6. 10 x 6in., 27/6. 10in. Rola, 30/-  
 4in. Hi-Fi Tweeter, 25/-, 12 in. R.A., 30/-  
**STENTORIAN HF1012.** 10in. 3 to 15 ohms, 10w., 95/-  
 12in. Baker 15 watt 3 ohms, or 15 ohms, 105/-  
**CRYSTAL DIODE G.E.C.** 2/-; GEX34, 4/-  
**HIGH RESISTANCE PHONES.** 4,000 ohms, 15/-  
**MIKE TRAFFIC.** 50. 1, 3/8 ea.; 100. 1/6; Potted, 10/8.  
**SWITCH CLEANER.** Fluid squirt spout, 4/3 tin.  
**TWIN GANG TUNING CONDENSERS.** 365 pF  
 miniature 1in. x 1 1/4in. x 1 1/2in. 10/-; 0.0005 standard  
 with trimmers, 9/-; 10 trimmers, 8/-; midget, 7/6.  
**SINGLE.** 50 pF, 2/6; 75 pF, 100 pF, 160 pF, 7/-  
 Solid dielectric 100, 300, 500 pF, 3/6.  
**SPEAKER FRET. GOLD CLOTH.** 17in., 25in., 5/-  
 25in. x 35in., 10/-; Tylan 4ft. 6in. wide, 10/-; 2ft.  
 3in. wide, 5/-; Brown, green or red. Samples S.A.E.

New and boxed VALVES 90-day Guarantee.

1R5	7/6	6X80	7/6	EABC30	8/6	HABC90	
185	7/6	6L6G	10/6	E191	6/-		12/6
174	6/-	6N7M	6/6	EBC33	8/6	HVR2A	6/6
2X2	3/6	6Q7G	8/6	EBC41	8/6	MU14	9/-
384	7/6	6AS7	8/6	EBF80	10/-	PA1	3/6
3V4	7/6	6BR7M	8/6	ECC84	9/6	PC84	8/6
514	7/6	6BS7	6/6	ECF80	9/6	CF80	9/6
5Y3	7/6	6X6G	6/6	ECH49	10/6	PL82	11/8
5Z4	9/6	6X4	7/6	ECH29	10/6	PEN25	6/6
6AM6	5/-	6X5	6/6	EPF39	5/6	PL82	10/6
6BR	5/-	12AT7	8/6	EPF41	9/6	PY80	7/6
6BE6	7/6	12AU7	8/6	EPF50	5/6	PY82	7/6
6BD6	9/6	12AX7	8/6	EPF81	8/-	RP61	3/6
6BW6	9/6	12RE6	8/6	EPF91	5/-	RP41	9/6
6D6	6/-	12K7	6/6	EPF92	5/6	ECH42	9/6
6F6G	7/6	12Q7	6/6	EPF92	5/6	UF41	9/6
6H6	3/6	35L6	9/6	EPF92	5/6	UL1	9/6
6J5	5/6	35Z4	7/6	EPM81	9/6	UY41	8/6
6K6	5/6	60	8/6	EZ40	7/6	UZ22	8/6
6G7G	6/6	807	8/6	EZ40	7/6	VR105	9/6
6K6GT	6/6	954	1/8	EZ40	7/6	VR105	9/6
6K7G	5/6	EA50	1/8	E1148	1/8	VR150	9/6

**THE "PW" ROADFARER AM/FM RADIO**

Transistorised throughout.

Advanced design, operated from internal batteries or direct from mains.

Four sections on printed circuits: A.M. tuner; F.M. tuner; audio amplifier; mains supply unit.

Attractive plastic cabinet. Ferrite rod aerial for A.M., telescopic aerial for F.M.

Order now, lowest prices.

**TELEVISION REPLACEMENT LINE OUTPUT TRANSFORMERS**  
 from 45/- ea.

Most makes available S.A.E. with all enquiries.

- LINE BLOCKING TRANSFORMERS, from 10/-.
- FRAME BLOCKING TRANSFORMERS, from 13/6.
- FRAME OUTPUT TRANSFORMERS, from 27/8.

**NEW MULLARD TRANSISTORS**  
 Audio OC71 10/- RF OC44 15/6  
 OC72 12/6 OC45 12/6  
 Sub Miniature Electrolytics, 15 volt.  
 1, 2, 4, 5, 8, 25, 50, 100 mfd. 3/- each.  
 Weyrad Printed Circuit Components in Stock.

**HIGH GANG TV PRE-AMP KITS**  
**BAND I BBC**  
 Tunable channels 1 to 5. Gain 18dB. ECC84 valve. Kit price 29/8 or 49/8 with power pack. Details 6d. (PCC84 valves if preferred).  
**BAND III ITA**—Same prices.  
 Tunable channels 8 to 13. Gain 17dB. ECC84 valve. (PCC84 valves if preferred).

**CRYSTAL MIKE INSERT** by Acos precision engineered. Size only 1in. x 3/16in., 6/6.  
**ALUMINIUM CHASSIS.** 18 s.w.g. undrilled. With 4 sides, riveted corners and lattice fixing holes. 2 1/2in. sides, 7 x 4in., 4/6; 9 x 7in., 5/6; 11 x 7in., 6/8; 13 x 9in., 8/8; 14 x 11in., 10/8; 15 x 14in., 12/8; 18 x 16 x 3in., 18/6.

**ALUMINIUM PANELS.** 18 s.w.g. 12in. x 12in., 4/8; 14 x 9in., 4/-; 12 x 8in., 3/6; 10 x 7in., 2/3.

**JASON F.M. TUNER COIL SET.** 29/-, H.F. coil, aerial coil, Oscillator coil, Two I.F. transformers, 10 Me/s Ratio Detector and heater choke. Circuit book using four 6AM6, 2/6.  
**COMPLETE JASON F.M. KIT.** FMTL, with set of 4 valves, etc., £8.50.

**BBC TRANSISTOR RADIO.** Med. and Long Wave. Two transistors and diode. Complete kit, 32/8, plus 7/6 extra. Deaf Aid Earpiece with Special Lead, 12/8. Details 10d.

**CYLDON TURRET TELEVISION**  
 I.F. 333Mc, complete with frame-grim valves, 30C1, 30L15. With coils for TV and FM Channels 1 to 13. Brand new, price 45/-, operating data and circuit supplied. IDEAL for P.T. "OLYMPIC".

**RECORD PLAYER BARGAINS**



- 4 Speed Autochangers, B.S.R., U.A.8 26.15.0
- 4 Speed Autochangers, B.S.R., U.A.14 27.10.0
- Collaro Autochanger 27.19.6
- Garrard Model 210, GC8 Head 21.0.10.0
- 4 speed Single Players, EMI 26.19.0
- Garrard T.A. Mk.II, GC8 Head 28.0.0
- Garrard 4 H.F. transcription, GC8 217.19.6
- Garrard Stereo Head, 22 extra 49/6
- Suitable player cabinets (except 4 H.F.) 49/6
- Amplifier player cabinets (except 4 H.F.) 63/-
- 2-valve amplifier and 6 1/2in. speaker 79/6
- 3-valve amplifier and 6 1/2in. speaker 95/-

Wired and tested ready for use with above.

**Volume Controls 80 ohm COAX CABLE**

Long spindles. Guaranteed 1 year. Midget 5K ohms to 2 Meg. No Sw. D.P. 5W. 3/- Linear or Log Tracks. Semi-air, spaced, in. dia. Losses cut 50%. Fringe Quality 1/- yd. Air Spaced. 6d. yd.

**COAX PLUGS 1/- LEAD SOCKET 2/-**  
**PANEL SOCKETS 1/- OUTLET BOXES 4/6**  
**BALANCED TWIN FEEDER** yd. 6d. 80 or 300 ohms. DITTO SCREENED per yd. 1/8. 80 ohms only.  
**WIRE-WOUND POTS.** 3 WATT. Pre-set. Min. TV Type. All valve 25 ohms to 25 K., 3/- ea.; 30 K., 50 K., 4/-; (Carbon 30 K., to 2 meg., 2/-)  
**WIRE-WOUND 4 WATT.** Pots Long Spindle Value. 30 ohms to 50 K., 8/6; 100 K., 7/6.  
**CONDENSERS.** New Stock. 0.001 mfd., 7 kV. T.C.C. 5/8; Ditto, 30 kV., 9/8; 0.1 mfd., 7 kV., 9/8; Tubular 500 v. 0.001 to 0.05 mfd., 9d.; 0.1, 1/6; 0.25, 1/8; 0.5/500 v., 1/8; 0.1/350 v., 9d.; 0.01/2,000 v. 0.1/1,000 v., 1/8; 0.1 mfd., 2,000 volts 3/8.  
**CERAMIC CONDS.** 500 v., 0.3 pF to 6.01 mfd., 9d.  
**WIRE MICA CONDENSERS.** 10% 5 pF to 500 pF. 1/-; 600 pF to 3,600 pF, 1/3. Close tolerance (±1 pF) 1.5 pF to 47 pF, 1/8. Ditto 1%, 50 pF to 815 pF, 1/8; 1,000 pF to 5,000 pF, 2/-.

**L.F. TRANSFORMERS 7/6 pair**

465 Kcs Slug Tuning Miniature Can. 1 1/2 x 1 x 1 in. High Q and good bandwidth. By Eye Read. Data sheet supplied.

WEYMOUTH. Standard size, 465 Kcs/10/8 pair.

**NEW ELECTROLYTICS. FAMOUS MAKES**  
**TUBULAR TUBULAR CAN TYPES**  
 1/350v. 2/- 50/350v. 5/8 16/450v. 5/-  
 2/450v. 2/3 100/25v. 2/- 32/350v. 4/-  
 4/450v. 2/3 250/25v. 2/6 100/270v. 5/8  
 8/450v. 2/3 500/12v. 3/- 2,500/3v. 4/6  
 8/500v. 2/8 8+8/450v. 3/6 5,000/6v. 6/-  
 16/450v. 3/- 8+16/450v. 3/8 32+34/450v. 6/-  
 16/500v. 4/- 8+16/500v. 5/8 32+32+32/350v. 7/-  
 32/450v. 3/8 16+16/450v. 4/3 50+50/350v. 7/-  
 25/25v. 1/8 16+16/100v. 6/6 64+120/350v. 11/8  
 50/50v. 2/- 32+32/350v. 4/6 100+200/275v. 12/8

**RECTIFIERS SELENIUM** 300 v. 85 mA. 7/8.  
**CONTACT COOLED** 250 v. 50 mA. 7/-; 60 mA. 8/8; 85 mA. 9/8; 200 mA. 21/-; 300 mA. 27/8.  
**COILS** Wearite "P" type, 3/- each. Osmor Midget "Q" type, 4/-; dist. extra from 4/-. All ranges.  
**TELETRON** L. Med. T.R.F. with reaction, 3/6.  
**FERRITE ROD AERIALS.** M.W. 8/9, M. & L. 12/6.  
**T.R.F. COILS** 4/H.F. 7/- pair. H.P. CHOKES 2/8.  
**FERRITE ROD**, 8in. x 3in., dia., 2/6.  
**FULL WAVE BRIDGE SELENIUM RECTIFIER:** 2, 5 or 12 v. 1 1/2 amp., 8/8; 2 v. 1 1/2; 4 v. 17/8.  
**CHARGER TRANSFORMERS.** Tapped input 200/250 v. for charging at 2, 6 or 12 v., 11 amp., 15/6. 2 amps., 17/8; 4 amps., 22/8. Circuit included.  
**VALVE and TV TUBE equivalent books.** 5/-  
**TOGGLE SWITCHES.** 3/2. D.P. 3/8. D.P.D. 4/-  
**WAVELENGTH SWITCHES.** 4/6  
 5 p. 4-way 2 water finger spindle 6/8  
 2 p. 2-way, 4 p. 2-way short spindle 2/8  
 2 p. 6-way, 4 p. 3-way, 4 p. 3-way long spindle 3/8  
 3 p. 4-way, or 1 p. 12-way long spindle 5/6  
**VALVE HOLDERS.** Pac. Int. Oct. 4d. EP50, EA50, 6d. B12A, CRT. 1/3. Eng. and Amer. 4, 5, 6 and 7 pin. 1/-. MOULDED MAZDA and Int. Oct., 6d. B7G, B8A, B8C, B9A, 8d. B7G with can., 1/8. B9A with can., 1/8. CERAMIC EP50, B7G, B9A. Int. Oct., 1/-; S/CANS B7G, B9A, 1/- ea.

**RADIO COMPONENT SPECIALISTS**

Post and Packing 1/-, over £2 free. (Export post Extra). C.O.D. 1/6. (Wed. 1 p.m.) THO 1665 Buses 133 or 68